

March 1995

# Electronics

## NOW

Combined with  
**Radio Electronics**

## A brief history of the **MICROPROCESSOR**

and how it has changed our lives

Build and install a  
**Car Security System**

that even thwarts  
carjackers

How to use  
**Active Op-Amp Filters**


for audio signal  
processing

Build a  
**WWV Receiver**

for atomic-clock timekeeping

Easy-to-build  
**Solid State Thermometer**

lets you monitor temperatures accurately

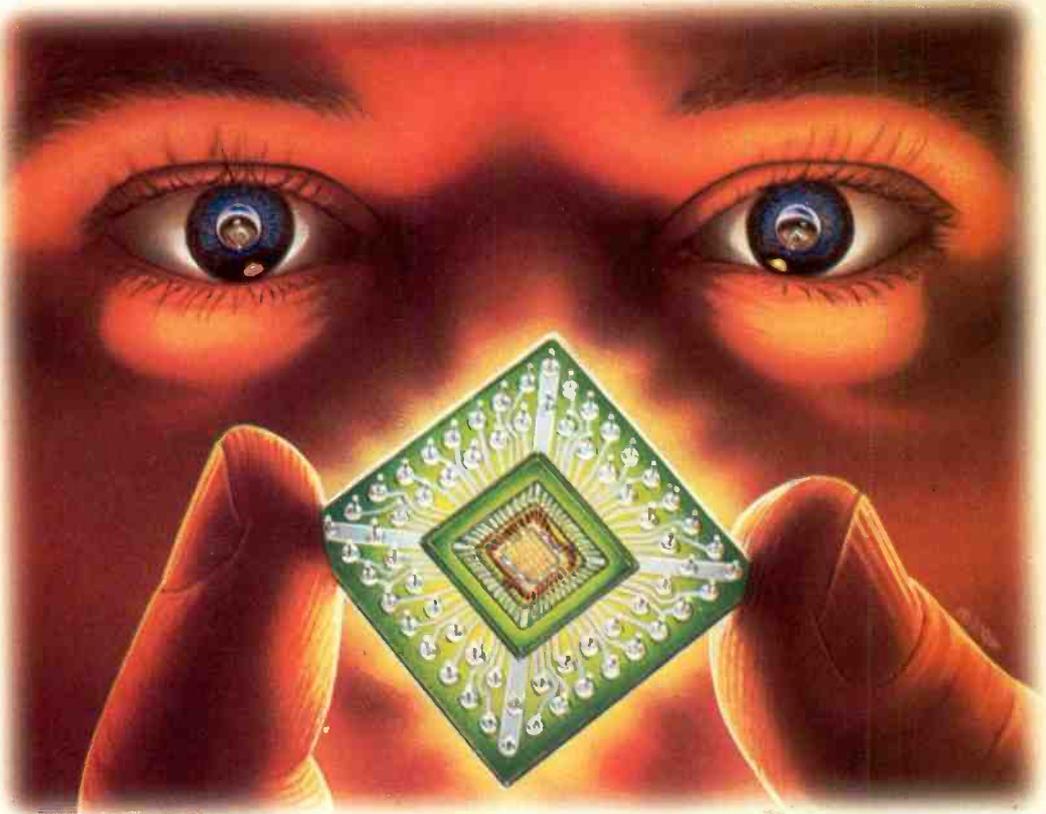


\$3.50 U.S.  
\$3.95 CAN.

A GERNSBACK  
PUBLICATION


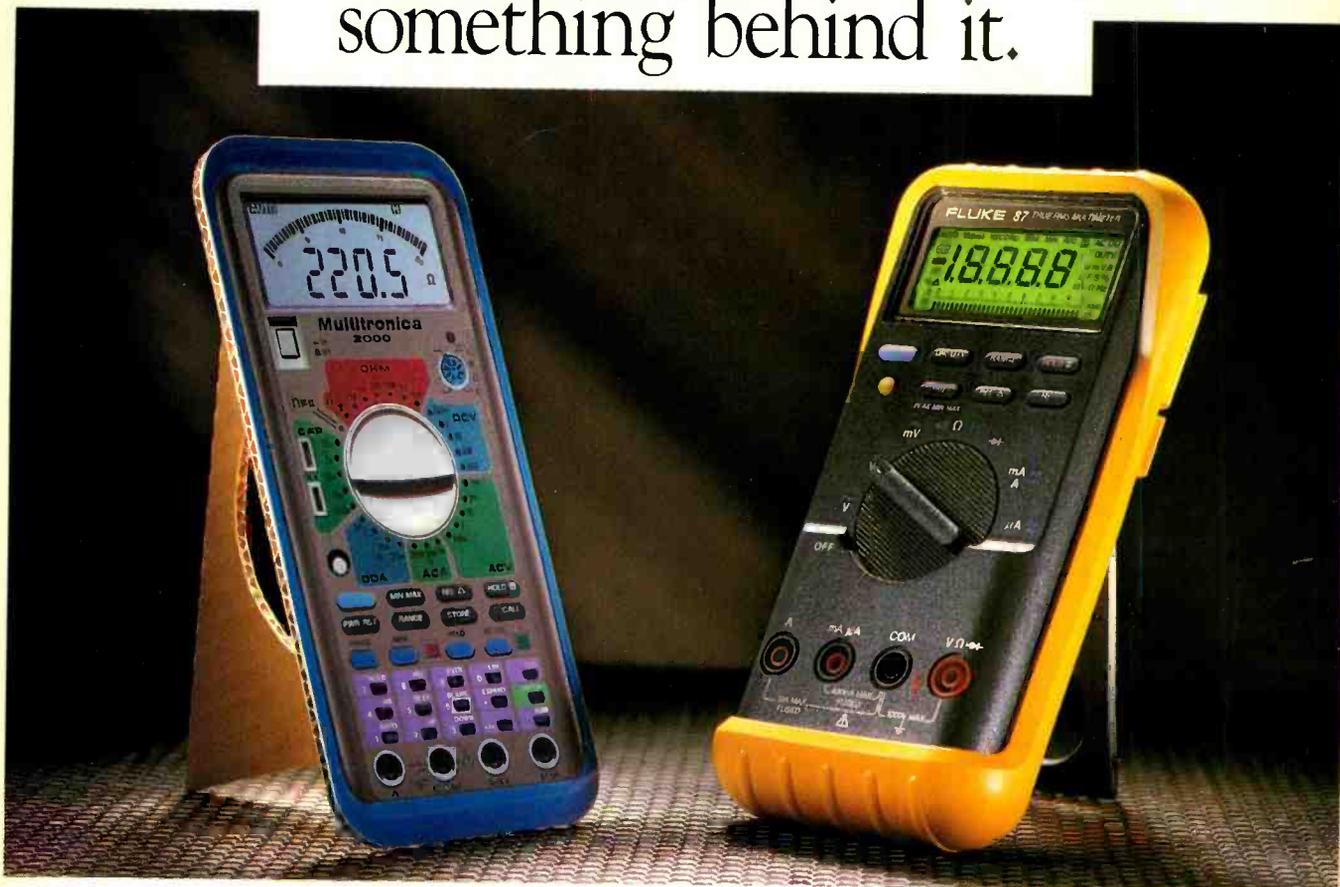
#BXNBQMF\*\*\*\*\*MIXED CITY 95060  
#BRKPOB67397 5#303178 0A  
CHRIS BARKER  
DITS VALLEY  
APR 95  
UCMS  
7 30 02

Before you get turned on  
by the front of a meter, make sure there's  
something behind it.



**Fluke meters are designed for professionals who value function over frills.**

There's nothing superficial about the Fluke family of versatile digital multimeters. Pick one up and you feel that it's a substantial tool. Designed to fit the application and the way you work. With features like our patented Touch Hold® function that freezes a reading on the display, and intelligently updates with each new reading. Automatically. Without requiring a third hand to push a button. Fluke meters attain stable, accurate readings in half the time of most imitations, making you more productive on the job.



Other meters are merely "designed to meet" certain guidelines; Fluke designs and builds a full line of meters that actually achieve UL, VDE and TÜV safety certification. Fluke's guarantee goes beyond manufacturing defects to include meter specifications for an entire year, so you can trust the readings. And Fluke backs you with toll-free customer assistance numbers, and a world-wide service organization. Discover why more professionals around the world say, "Hand me the Fluke." See your local distributor, or call **1-800-87-FLUKE** for a catalog and the name of the distributor nearest you.

Serious Tools for Serious Work

**FLUKE**®

© 1994 Fluke Corporation. P.O. Box 9090, M/S 250E, Everett, WA,  
USA 98206-9090. U.S. (206) 356-5400. Canada (905) 890-7600.  
Europe (31 40) 644200. Other Countries (206) 356-5500.  
All rights reserved. Ad No. 00567


CIRCLE 121 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

“Design work is faster and cheaper with Electronics Workbench.”

Mark Weaver  
Production Engineer Technician  
Colorado Memory Systems/HP


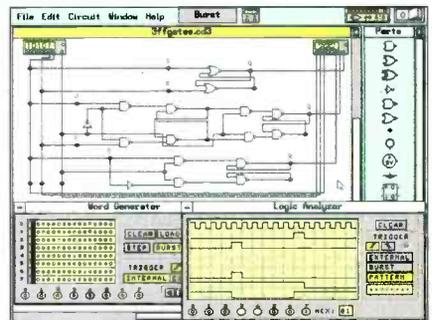
Electronics Workbench is a highly productive bench where you design and verify circuits in a fraction of the time. Connections are always perfect. Wires route themselves. And the simulated components and test instruments work just like the real thing.




Digital Module: Analyzing a logic circuit.

It's faster than building with actual components because you change connections and component values instantly. And since the simulated components are free, you don't need to replace burnt-out parts or keep an extensive inventory. The result: You save precious time and money. Guaranteed!\*

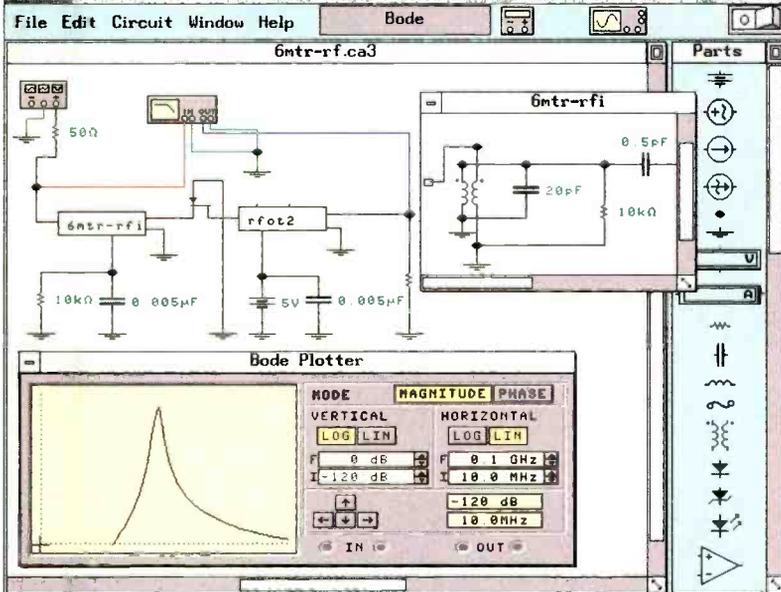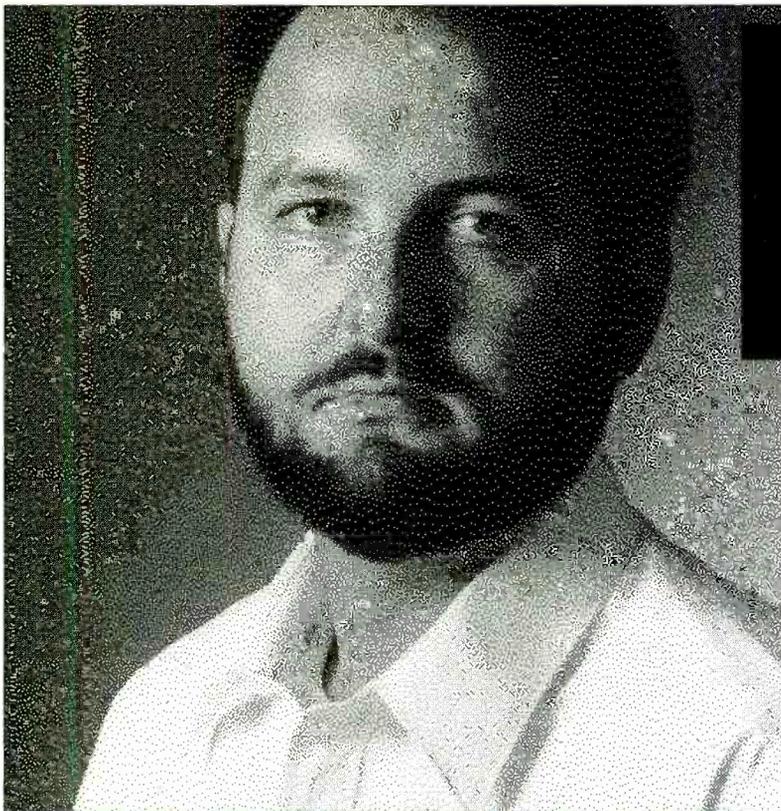The standard for simplicity and power for over six years, Electronics Workbench is the most popular tool of its kind. It has gained worldwide acclaim as the ideal complement to any test bench. **Fact: Over 90% of our customers recommend it to their friends and colleagues.**



Analog Module: Tuning an RF front end.

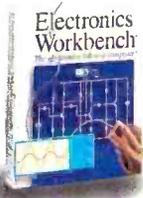

**Just \$299\***  
For DOS, Windows or Mac Version.



# Electronics Workbench<sup>®</sup>

The electronics lab in a computer™

## Call: 800 263-5552

INTERACTIVE IMAGE TECHNOLOGIES LTD.  
908 Niagara Falls Blvd. #068, North Tonawanda, NY 14120-2060  
Telephone: (416) 361-0333 FAX: (416) 368-5799

\*30-day money-back guarantee.

Prices in U.S. dollars, shipping \$15. Offer valid in U.S. and Canada only.  
All trademarks are the property of their respective owners.




CIRCLE 126 ON FREE INFORMATION CARD

# CONTENTS

MARCH 1995

**ON THE COVER****35 MICROPROCESSORS**

Serving as the heart of today's computers, the microprocessor is a vital part of our lives on and off the job. The development of better microprocessors leads directly to the advancement of other products and technologies. This month, we take an in-depth look at the evolution of microprocessors, examining two decades of microprocessor history. Required reading for computer users, hobbyists, technicians, and designers, this article will help you understand what microprocessors are, how they work, and how they developed. It also includes a capsule history of the early days of computers, as well as a glossary of microprocessor-related terms.

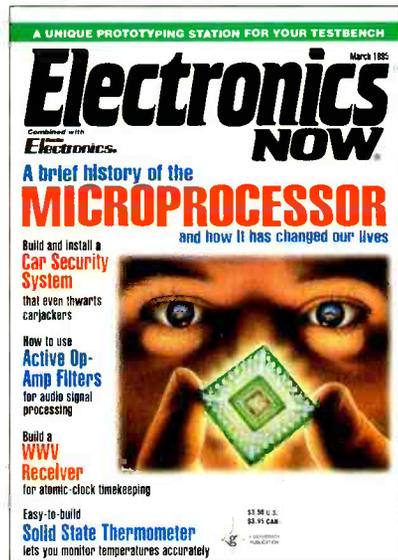— *Stephen J. Bigelow***BUILD THIS****45 SOLID-STATE THERMOMETER**

You can build this accurate handheld thermometer from scratch or from a kit.

— *Marc Spiwak***49 WWV RECEIVER**

Pick up the time signals broadcast by the National Institute of Standards and Technology using

this simple heterodyne receiver.

— *Neil Heckt***54 PROTOTYPING STATION**

How to build a custom workbench for testing your next project.

— *Carl Bergquist***65 THE PROCAR SECURITY SYSTEM**

This automobile alarm, anti-theft, and anti-carjacking system sounds an alarm and then disables the car.

— *David T. Miga*

As a service to readers, ELECTRONICS NOW publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, ELECTRONICS NOW disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry in ELECTRONICS NOW may relate to or be covered by U.S. patents, ELECTRONICS NOW disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

ELECTRONICS NOW, (ISSN 1067-9294) March 1995. Published monthly by Gernsback Publications, Inc., 500-B Bi-County Boulevard, Farmingdale, NY 11735. Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Canada Post IPM Agreement No. 334103, authorized at Mississauga, Canada. One-year subscription rate U.S.A. and possessions \$19.97, Canada \$27.79 (includes G.S.T. Canadian Goods and Services Tax, Registration No. R125166280), all other countries \$28.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$3.50. © 1995 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to ELECTRONICS NOW, Subscription Dept., Box 55115, Boulder, CO 80321-5115.


A stamped self-address envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

**TECHNOLOGY**

**87 ACTIVE AUDIO FILTERS FOR SIGNAL PROCESSING AND CONTROL**

Learn how active filters are used in audio signal processing and control, and how you can use them in your own circuit designs.

— *Ray Marston*

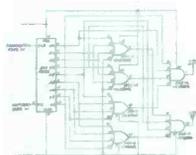

**DEPARTMENTS**

**6 VIDEO NEWS**

What's new in this fast-changing field. — *David Lachenbruch*

**16 EQUIPMENT REPORT**

Sencore Computer-Monitor Tester.



**79 HARDWARE HACKER**

Low-cost TV data displays, thoughts on brain implants, and more.

— *Don Lancaster*

**86 DRAWING BOARD**

Descrambler notes, and more.

— *Robert Grossblatt*



**92 COMPUTER CONNECTIONS**

UberSoft uber alles.

— *Jeff Holtzman*

— **AND MORE** —

**4 WHAT'S NEWS**

**8 Q&A**

**14 LETTERS**

**18 NEW PRODUCTS**

**28 NEW LITERATURE**

**97 BUYER'S MART**

**100 ADVERTISING SALES OFFICES**

**100 ADVERTISING INDEX**

**Electronics NOW®**

Hugo Gernsback (1884-1967) founder

**LARRY STECKLER, EHF, CET,**  
Editor-in-chief and publisher

**EDITORIAL DEPARTMENT**

- BRIAN C. FENTON**, editor
- MARC SPIWAK**, associate editor
- NEIL SCLATER**, associate editor
- TERI SCADUTO**, assistant editor
- JEFFREY K. HOLTZMAN**  
computer editor
- ROBERT GROSSBLATT**, circuits editor
- LARRY KLEIN**, audio editor
- DAVID LACHENBRUCH**  
contributing editor
- DON LANCASTER**  
contributing editor
- EVELYN ROSE**, editorial assistant

**ART DEPARTMENT**

- ANDRE DUZANT**, art director
- RUSSELL C. TRUELSON**, illustrator

**PRODUCTION DEPARTMENT**

- RUBY M. YEE**, production director
- KAREN S. BROWN**  
advertising production
- KATHRYN R. CAMPBELL**  
production assistant

**CIRCULATION DEPARTMENT**

- JACQUELINE P. CHEESEBORO**  
circulation director
- WENDY ALANKO**  
circulation analyst
- THERESA LOMBARDO**  
circulation assistant
- MICHELE TORRILLO**  
reprint bookstore

Typography by Mates Graphics  
Cover design by David Loewy

**Electronics Now** is indexed in *Applied Science & Technology Index*, and *Readers Guide to Periodical Literature*, *Academic Abstracts*, and *Magazine Article Summaries*.

Microfilm & Microfiche editions are available. Contact circulation department for details.

**Advertising Sales Offices listed on page 94.**

Electronics Now Executive and Administrative Offices  
**1-516-293-3000.**

Subscriber Customer Service:  
**1-800-288-0652.**

Order Entry for New Subscribers:  
**1-800-999-7139.**



Audit Bureau  
of Circulations  
Member



# WHAT'S NEWS

*A review of the latest happenings in electronics.*

## **Legal cable equipment sales**

The Nebraska Supreme Court has upheld the right of independent vendors to sell cable converters and descramblers legally in Nebraska, and the National Consumer Cable Association (NCCA) has hailed the decision as "a major victory for the cable equipment manufacturing and distributing industry."

The Nebraska Supreme Court decision followed an appeal on a lower court decision in the case of illegal seizure of cable receiving equipment by the Omaha police. In November of 1988, the Omaha police confiscated and later destroyed 200 converters and descramblers owned by Imperial Trading Company. The District Court determined that the Omaha Police had wrongfully destroyed Imperial's property, but it only awarded the company a token \$1 in damages.

After reviewing the lower court decision, the Nebraska Supreme Court ruled that Imperial must be properly compensated for its property losses for an amount equal to the market value of the equipment when it was seized. The Supreme Court also decided that the District Court made a mistake in finding that no lawful market for the equipment existed outside of the cable industry.

The NCCA sees the decision as an important step toward preserving the freedom of independent companies to manufacture and sell cable equipment. Moreover, it says the decision gives consumers the right to purchase and own their own cable receiving equipment rather than requiring them to rent it from cable companies.

## **Battery-powered cars tested**

Twenty battery-powered "station cars," are being tested in a year-long Massachusetts Electric Vehicle Demonstration Project that was launched in April of 1994. The commuters selected to test drive the



**ONE OF THE 20 ELECTRIC CARS** being tested in Massachusetts over short commuting distances..

*Force* vehicles, Geo Metros modified by Solectria Corporation, Wilmington, Mass., offer high praise for their performance.

The commuters have been driving the electric cars, owned by the state-sponsored program, between their homes and nearby rapid transit stations. The drivers plug the batteries into electric outlets at the stations during the day and into household outlets when they arrive home. The chargers are built into the vehicles.

Karl Thidemann, Solectria's marketing director, reports that all of the participating drivers have expressed satisfaction with the vehicles. "No drivers have called to say they were stranded because of battery problems," he declared. Fifteen of the cars are powered by lead-acid batteries and five are powered by nickel-cadmium batteries.

The *Force* cars have direct-drive, brushless AC induction motors and an electronic motor controller with power-assisted regenerative brakes. The onboard chargers for the vehicles powered by lead-acid batteries are rated 1 kilowatt/120 volts AC, and those for the nickel-cadmium batteries are rated 2 kilowatts/208-240 volts AC. System

power is 42 kilowatts. The test cars are equipped with many of the same standard safety and convenience features found in gasoline-powered cars.

The nickel-cadmium batteries in the five cars were produced by Saft America, Valdosta, GA. Jim Miller, Saft's project manager, said that these batteries function more efficiently in the bitter New England winter weather than lead-acid batteries. "At freezing temperatures, nickel-cadmium batteries lose only 5% of their capacity," he explained. "By contrast, lead-acid batteries can fall to 25 to 50% of their capacity."

Miller said the nickel-cadmium batteries give the test cars a range of 100 miles at 45 mph, while the lead-acid battery-powered have a range of only 60 miles at 45 mph.

## **Test Equipment sales to rebound**

The communication test-equipment market will grow from \$776 million in 1993 to \$1.3 billion by the year 2000 according to a report entitled "U.S. Communications Test Equipment Market Sales," published by Frost & Sullivan.

The report says that the market will expand at an 8% compound annual rate, and this expansion will be driven by growth in both the computer and telecommunications markets, as well as generally recovering capital goods sales following the economic recovery.


The report predicts that by the year 2000, dedicated communication and telecommunication test equipment will account for 53% of all communications test equipment sales. General purpose signal sources will account for 15%, spectrum analyzers 11%, power meters 8%, and optical time-domain reflectometers 7%.

The largest growth will be in the  
*Continued on page 96*


# Why Design Circuits The Hard Way?
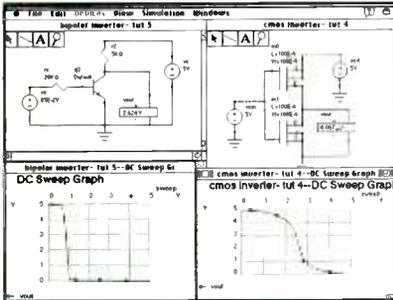
## B<sup>2</sup> SPICE and B<sup>2</sup> LOGIC Make It Easy!

Introducing B<sup>2</sup> SPICE and B<sup>2</sup> LOGIC for Windows™  
Macintosh™, and NEW for Power Macintosh™



**B<sup>2</sup> SPICE**

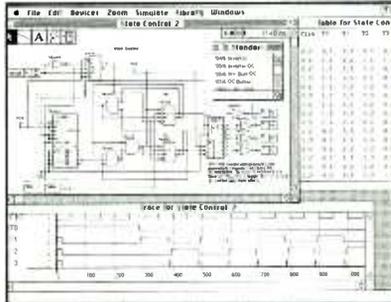

**B<sup>2</sup> LOGIC**

**B<sup>2</sup> SPICE v.1.1** and **B<sup>2</sup> LOGIC v.3.0** are the most powerful and affordable integrated analog and digital circuit design, simulation, and analysis packages available. B<sup>2</sup> SPICE and B<sup>2</sup> LOGIC neatly integrate the schematic editor, simulator, and graphics post processor. Each is fully integrated and interactive and are extremely easy to use for **Windows™, Macintosh™, and Power Mac™**. Both B<sup>2</sup> SPICE and B<sup>2</sup> LOGIC are currently in use at over 100 major universities and many leading Fortune 500 companies such as The University of Michigan, Stanford, AT&T, General Electric, and Hewlett Packard, to mention a few!

### **B<sup>2</sup> SPICE v 1.1 \$149**

- Simulation: Transient, DC Operating Point, DC sweep, and AC sweep
- Library: MOSFETs, BJTs, JFETs, op amps, & many more
- Circuit analysis based on Berkeley SPICE
- Device & Model Property Editing
- Flexible Visualization of Results: Customized Graphs and Tables

### **B<sup>2</sup> LOGIC v 3.0 \$199**

- State-of-the-art Circuit Editor Includes support for Buses, Virtual Net Connectors, and Subcircuits.
- Simulator provides realistic timing to 0.1 nanoseconds
- Define your own components using Subcircuits and PLD's
- Subcircuit Probing
- Multiple Libraries
- Customize Device Properties
- EDIF File Format Output

### **ELECTRONIC DESIGN PACKAGE \$270**

- Includes B<sup>2</sup> SPICE and B<sup>2</sup> LOGIC
- Demo Disks Available
- University & Student Prices Available
- Site Licenses Available
- Dealer Inquiries Welcome
- Visa/Master Card Accepted



**Beige Bag Software**  
2000 Hogback Rd, Ste. 2  
Ann Arbor, Michigan 48105

**Phone** 313. 971. 4227  
**Fax** 313. 971. 3632  
**E-Mail** info@beigebag.com or  
71620.3474@compuserve.com

CIRCLE 198 ON FREE INFORMATION CARD



*What's new in the fast-changing video industry.*

**DAVID LACHENBRUCH**

● **Digital Video Disc Clash.**

Smoldering dispute over standards for the next-generation video-disc system has broken into the open, threatening exactly the standards battle the movie industry had hoped to avoid. As reported here (*Electronics Now*, January 1995), the major movie companies established a *de facto* group to select a digital video disc (DVD) standard offering 135 minutes of playing time on a five-inch disc with higher quality than current laser discs. The stated aim was to avoid a repetition of the Beta-VHS wars.

Now, Sony and Philips have gone public with their system, forcing the competitive Toshiba-Time Warner system into the spotlight as well. The Sony-Philips system, as announced, uses a single-sided, five-inch, high-density CD (HDCD) that is capable of storing 135 minutes of MPEG-2-quality video "together with multitracks of compressed digital audio and subtitling." The use of "variable transfer rate" for video of up to 10 megabytes per second (mbps) "means that the picture quality will be superior to that of current consumer video," the announcement said. The companies indicated that the system could be modified in order to achieve a "uniform standard." They said that their HDCD platform will be capable of storing 3.2 gigabytes (GB) of data—more than five times the data capacity of existing music CDs. They emphasized that the discs could be produced at "conventional manufacturing facilities with only minor modifications. That means, they said, that "production costs of the proposed new discs will be similar to that of conventional CDs, a major advantage for consumers and media manufacturers as well for the hardware and software industries."

Philips and Sony said that they are also discussing CD-ROM applications of their HDCD with Apple, Compaq, IBM, and Microsoft,



**PHILIPS' LATEST GENERATION CD-i PLAYER is capable of playing full-motion-video movies and music videos recorded on five-inch digital video discs.**

and are planning other multimedia uses, including interactive entertainment, video games, or "ultra-high sound quality audio." They also revealed specifications for a dual-layer version, developed in collaboration with 3M, which doubles disc capacity to about 7.4 GB. It uses two reflective layers within the disc, making possible double playing time without turning the disc over. Both the single- and dual-layer versions will be 1.2mm thick. The two companies said that standards will be finalized by mid-1995.

● **The other system.** The Philips-Sony announcement smoked out some details of the Toshiba-Time Warner proposal, which had been kept secret. A statement from Toshiba said that a prototype had already been developed and "mass production technology" was being completed for double-sided discs. The system has storage capacity of 4.8 GB per side, Toshiba said, adding that "we believe the number of sub-channels for dubbing soundtracks in different languages and the long recording time offered by our system ... satisfy the needs and expectations" of the movie industry. Toshiba said that "a storage capacity of 4.5 gigabytes is the minimum required to realize quality pictures and sound."

Toshiba's partner, Warner Home

Video, said that the system should produce "radically improved pictures and audio quality at affordable prices on equipment that can sustain software upgrades," and added that, "We believe our manufacturing costs of discs should be comparable to those claimed by Sony and we have proven its manufacturability using existing CD equipment."

Warner Home Video's president, Warren Lieberfarb, was quoted in *Television Digest* as saying that manufacturability of discs was proven at Warner's CD plant, which he called the world's largest. "We do not believe Sony has proven the manufacturability or costing of its discs," he added. "We believe that both the yield and cycle time of the double-sided disc for these high-density formats is vastly superior to the 1.2mm proposal of Sony. We also do not think there is a material cost factor associated with our player achieving backward compatibility with CD."

Toshiba sources have suggested that the two-sided discs might accommodate two complete movies—one on each side, or possibly a movie on one side and a derivative video game or CD-ROM on the other. The larger data capacity presumably could accommodate five audio tracks and as many as 30 subtitle tracks.

● **Video CD, too.** The fanfare over DVD has left Video CD in a sort of limbo. That format, widely used in Japan for karaoke, stores 74 minutes of VHS-quality, full-motion video on a single five-inch disc. In the U.S., Philips is emphasizing Video CD as a significant add-on to its CD-i interactive system, although Video CD is the least interactive of its features, being designed to show linear movies. CD-i's main competitor, 3DO, is also featuring Video CD as an add-on, although currently only about 30

*Continued on page 96*


# Look beyond our scope.

## Tektronix gives you an entire bench of affordable test instruments.

You know us for our oscilloscopes. (Considering we are the widely accepted market leader, it's not surprising.) ■ Now we've expanded our vision. And it's grown to include function generators, counters, timers, multimeters, power supplies, and accessories. All built with the same devotion to accuracy and reliability that you've experienced in our scopes. It's all compatible, fully integrated and best of all, simple to use. ■ And all made available to you in a comprehensive, affordable portfolio we call TekBench™.

■ Come, try one out when you next need something for your bench. We believe we'll be well within your scope. For more information or the name of the Authorized TekBench™ Distributor nearest you, call 1-800-426-2200. (When prompted, press 3 and request ext. 335.)

**TEKBENCH™**  
from Tektronix

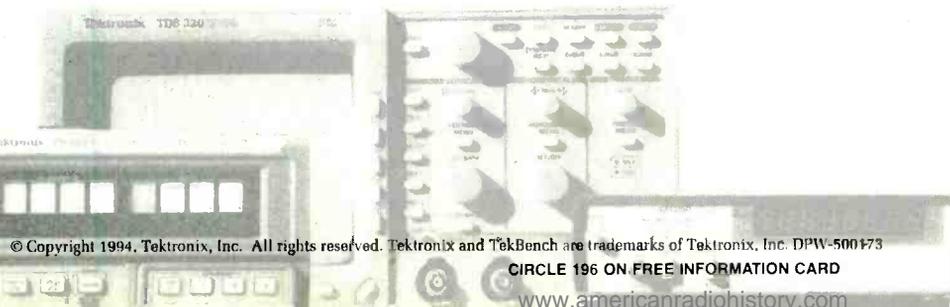

Write to Q & A, Electronics Now, 500-B Bi-County Blvd., Farmingdale, NY 11735

## LOW-POWER CLOCK

I'm building a circuit that needs a relatively slow clock to control it. The frequency of the clock has to have a range from about 0.1 to 2 Hz. I'm not looking for crystal accuracy. However, because the circuit must be battery powered and mounted in a remote location where it will be difficult to service, I do want a circuit that uses very little power. Do you have a simple off-the-shelf circuit I can use?—D. Katz, Great Neck, NY

The development of low-power components over the last several years has made the working life of batteries approach their shelf life in some circuits. This made the whole digital wristwatch industry possible. While it's not easy to steal clock pulses from a digital watch, there are some alternatives you can use for your application. You should find the circuits shown in Fig. 1 to be what you need.

The LM3909 is an LED flasher IC that is designed to oscillate at about the frequencies you're looking for. It can be set to one frequency or its frequency can be trimmer-adjustable. The 3909 will work reliably with a wide supply voltage range, and if you power it with a single alkaline D cell, the cell should last more than two years. Even though you need only clock pulses, remember that the 3909 can supply current pulses of up to 45 milliamperes at greater than 2 volts.

The clock output of the first circuit can be changed by changing the value of the capacitor, as indicated in the drawing. If you want to be able to adjust the clock frequency on the fly, use the second circuit and adjust the frequency with the trimmer shown in the schematic.

## DECELERATION DETECTOR

I'm looking for a way to detect deceleration in an automobile. Do you have any ideas about how this could be done? I'd like

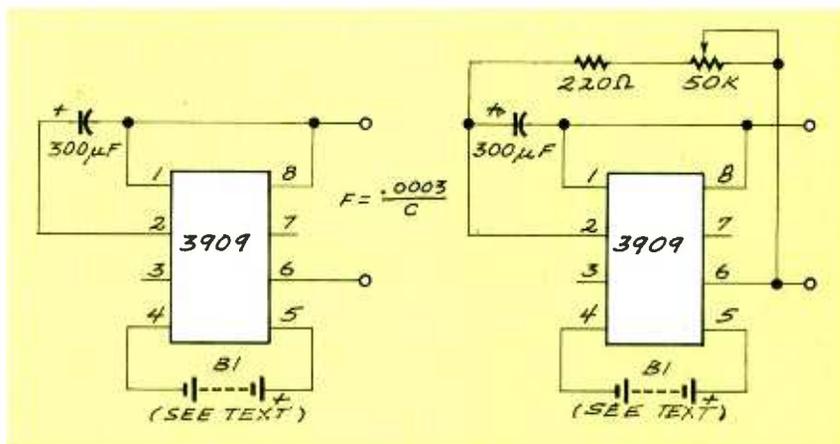


FIG. 1—THE LM3909 is an LED flasher IC that is designed to oscillate at low frequencies. The clock output of the first circuit can be changed by changing the value of the capacitor, and the second circuit lets you adjust the frequency with the trimmer.

the device to be completely electronic because I think that would make it more reliable.—P. Pezzino, Cedar Grove, NJ

Detecting acceleration or deceleration always requires some kind of mechanical sensor. Even the accelerometers used in the most modern missiles and airplanes contain mechanical components.

This type of circuit can be broken into two basic parts. The first part detects changes in movement and converts those changes into an electronic signal. The second part measures the signal and displays it.

One technique is to measure the rotational speed of either the wheels or the drive shaft. How you do this depends on the particular car; front wheel drive cars don't have drive shafts in the traditional sense. In that case, you'd have to measure the speed of the wheels.

The basic procedure is to attach something to the moving part that can sense the rotational speed. This can be done optically or magnetically, but considering the harsh environment under a car, a magnetic pickup is the better choice. Magnetically coupled switches—such as the kind used in alarms to detect when a door or window opens—are readily available.

Another possibility is to use a de-

vice made specifically for the job, such as Analog Devices' ADXL50 solid-state accelerometer. The ADXL50 is essentially a capacitor with one stationary plate and one flexible plate. Acceleration can be determined by measuring the change in capacitance that occurs when the device is accelerated.

You could also try experimenting with your own accelerometer design. The resistance of conductive foam (the kind that protects static-sensitive CMOS ICs) changes as the foam is compressed. If you suspend a relatively heavy object between two pieces of this foam, changes in speed will cause the object to compress the foam in front when you decelerate, and compress the foam in back when you accelerate. By constantly measuring the minute changes in the resistance of the two pieces of foam, you'll have a signal that can tell you how much your car is accelerating or decelerating.

The circuit you need to convert the signal to a number on a dial depends on which approach you take to produce the signal in the first place. For example, the magnetic-pickup approach would require a counter circuit to count the change in rate of the number of switch closures per second.

# Be a high-paid computer service technician

Train With NRI — America's #1 Choice in Computer Training

Only NRI gets you inside a powerful 486DX2/66 MHz Intel-based computer system you keep—giving you the hands-on experience you need to work with, troubleshoot, and repair today's most widely used computer systems. There's no more affordable way to start a money-making career, even a business of your own, as a computer service technician.

## Rely on the original -- NRI

Over a decade ago, NRI pioneered at-home training in computer servicing. Today, NRI offers the *only* computer servicing course with real-world experiments using state-of-the-art computer equipment and professional diagnostic tools.

There's no doubt about it: Working "hands-on" with all the most sought-after technology gives you practical skills and lasting confidence. Performing key tests and demonstrations, you're able to see for yourself how things work, what can go wrong, and how you can fix it.

## Train with and keep the most advanced computer in home study today

NRI's unique training has you explore a top-notch computer system and its peripherals, beginning with the 486DX2 Intel CPU and Pentium Overdrive-ready motherboard.


Your computer features 8 meg RAM, 420 meg hard drive, and fax/modem to store, receive, and send huge amounts of data.

You'll also appreciate the brilliant display of your Super VGA color monitor, the drama of your CD-ROM drive and 16-bit sound card, as well as the cutting-edge technology of Windows 95.

Plus learn to use Ultra-X professional diagnostic hardware and software to pinpoint problems on any IBM-compatible machine.
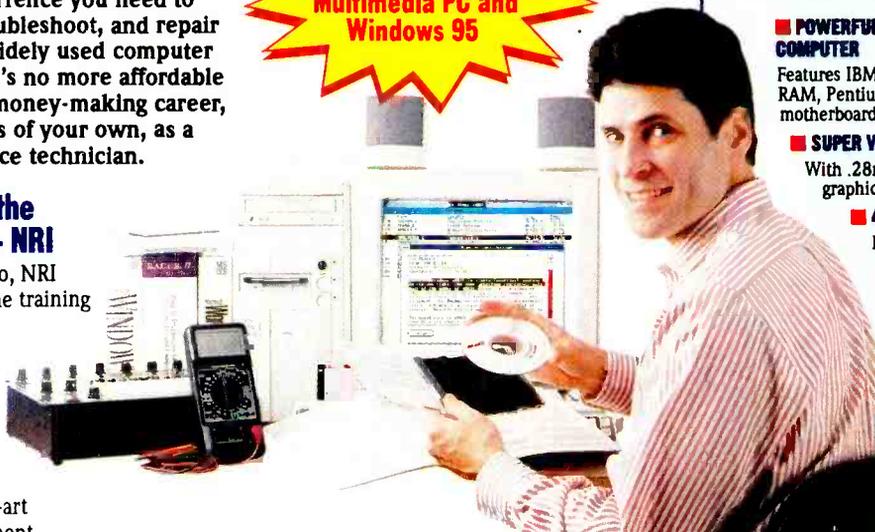
## No experience needed, NRI builds it in

Studies show that jobs for computer service technicians will be up by 38% in the next 10 years. Even if you've never worked with



## YOU GET EVERYTHING YOU NEED FOR SUCCESS

### ■ POWERFUL 486DX2/66 MHz INTEL-BASED COMPUTER

Features IBM compatibility, 8 meg RAM, Pentium Overdrive-ready motherboard, and math coprocessor

### ■ SUPER VGA COLOR MONITOR

With .28mm dot pitch for high-resolution graphics and tilt-swivel base

### ■ 420 MEG HARD DRIVE

For greater data storage capacity and data access speed

### ■ EXCITING MULTIMEDIA PERIPHERALS

Double-speed CD-ROM drive, 16-bit sound card with speakers, and reference CD

### ■ FAX/MODEM

Gives you access to a world of on-line information

### ■ ULTRA-X DIAGNOSTIC PACKAGE

R.A.C.E.R. plug-in card and

QuickTech-PRO software help you detect problems on virtually all IBM-compatible machines, even if computer is 5% operational.

### ■ NRI DISCOVERY LAB

Complete breadboarding system lets you design and modify circuits, diagnose and repair faults

### ■ DIGITAL MULTIMETER

Professional, hand-held test instrument for quick and easy measurements

### ■ WINDOWS 95

The time-saving operating system that everyone will be using tomorrow

computers before, NRI's interactive training builds such a solid foundation of know-how and practical experience that tomorrow's jobs can be yours.

Right from the start, hands-on experiments reinforce concepts presented in NRI's bite-sized lessons. And because your work is reviewed by your personal instructor, you know for certain that you can apply theory to real-world demands.

## FREE NRI catalog tells more

Send today for your free, full-color catalog describing every aspect of NRI's innovative computer training in the up-and-coming field of your choice.

If the coupon is missing, write to: NRI Schools, McGraw-Hill Continuing Education Center, 4401 Connecticut Avenue, NW, Washington, DC 20008.

IBM is a registered trademark of the IBM Corporation. R.A.C.E.R. and QuickTech-PRO are registered trademarks of Ultra-X, Inc.

## SEND TODAY FOR FREE NRI CATALOG!



McGraw-Hill Continuing Education Center  
4401 Connecticut Avenue, NW, Washington, DC 20008



### Check one FREE catalog only

#### MICROCOMPUTER SERVICING

- Computer Programming
- TV/Video/Audio Servicing
- Desktop Publishing & Design

- LAN Specialist
- Bookkeeping and Accounting
- Programming in C++ with Windows

Check for details on career courses approved under GI Bill

Name (please print)		Age	
Address			
City		State	Zip

Accredited Member, National Home Study Council

3-0395



# Measure It All!

## The DMM/LCR Meter/ Frequency Counter. All in One.

**T**roubleshoot down to the component level — any component! Verify poorly marked parts, test for tolerances and damage. Wavetek's new DM27XT is not only a full-function DMM, but also includes complete inductance, capacitance, and frequency measurement capabilities.

- **Wide LCR range:**  
10  $\Omega$  to 2000 M $\Omega$   
10 pF to 2000  $\mu$ F  
100  $\mu$ H to 20 H
- **Autoranging frequency meter** 10 Hz to 20 MHz
- **Ac and dc current to 20 A**
- **Logic test, diode test, max reading hold, continuity beeper, input warning beeper, fused input protection, battery saver**

Consolidate your test bench with one meter that does it all — Wavetek's high-performing, full-function XT Series DMM. It's all in one compact, rugged, field-ready package with a big 0.7-inch, 3 1/2-digit display. Insulated probes and alligator clip leads are included, and there is a huge selection of accessories, including current, rf and HV probes, temperature converters, holsters, and cases. Ask for Wavetek DMMs. They're the meters to pick when you have things to fix.

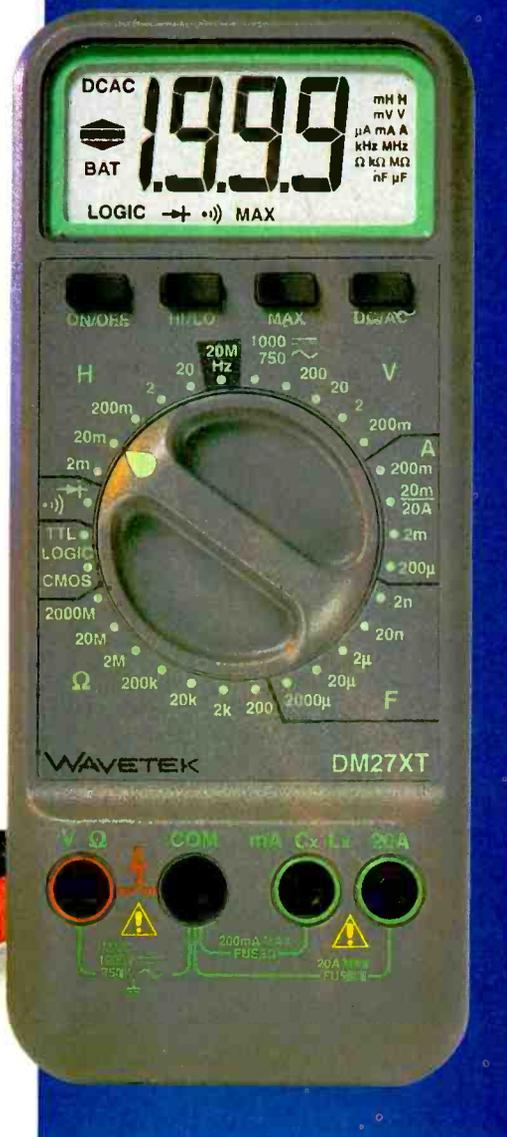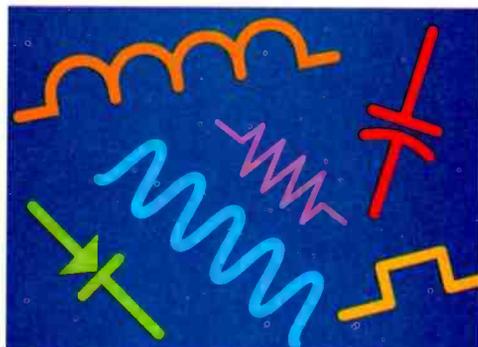

### MOTHERBOARD MISERY

I recently upgraded my computer by replacing its 8088-based motherboard with one based on an 80386. I reinstalled all my original expansion cards and peripherals, and while the computer turns on without any apparent problem, it won't recognize my hard drive. If I boot the computer from a floppy and try to access the hard drive, I get an "invalid drive" error message. I've checked all my cable connections and everything seems correct. Do you know what I'm doing wrong?—G. Fischer, New York, NY

The cause of the problem is the difference in the way the two microprocessors are designed to address the hard drives. To control the hard drive, the computer needs a collection of primitive routines that can control the cylinder and head selection, sector read and write, and so on.

In the design of an 8088-based computer, these routines were in the firmware on the hard drive controller card. In machines based on 80286 and later microprocessors, these routines were incorporated in the BIOS (basic input output system), usually contained in one or more EPROMs on the motherboard, and the computer's setup program stored the hard-drive specifications in permanent (battery-backed) CMOS memory.

If you use the hard drive and controller from an 8088 in a later computer, the hard drive must be accessed with the controlling firmware on the controller card. This means you have to tell the CMOS setup program that there are no hard drives installed in the computer. If you set the drive types in the computer's CMOS setup memory, all software, including DOS, will try to access the hard drive using the primitive routines in the computer's BIOS. This will result in a failure, and an "invalid drive" message.

The way to correct this problem is to run the setup program again and tell the computer that there are no hard drives installed. This will allow the controller card's firmware to address the drives and everything will work correctly.

**\$119<sup>95</sup>**

Other XT Series DMMs from \$89.95

U.S.A.: (619)279-2200  
Europe: (44)243) 531323  
Asia Pacific: (852)865-1903

©1993 Wavetek Corporation

CIRCLE 98 ON FREE INFORMATION CARD

**WAVETEK**

# Take this GIANT CIRCUIT LIBRARY for only \$9.95

when you join the *Electronics Engineers' Book Club*®


## THE ENCYCLOPEDIA OF ELECTRONIC CIRCUITS —Vols. 1, 2 & 3 by Rudolf F. Graf

*Hundreds of circuit ideas alphabetically arranged — from Alarm circuits to Zero crossing detector circuits!*

*"... includes schematics for the latest electronics circuits from industry leaders..."*

*—Popular Electronics*

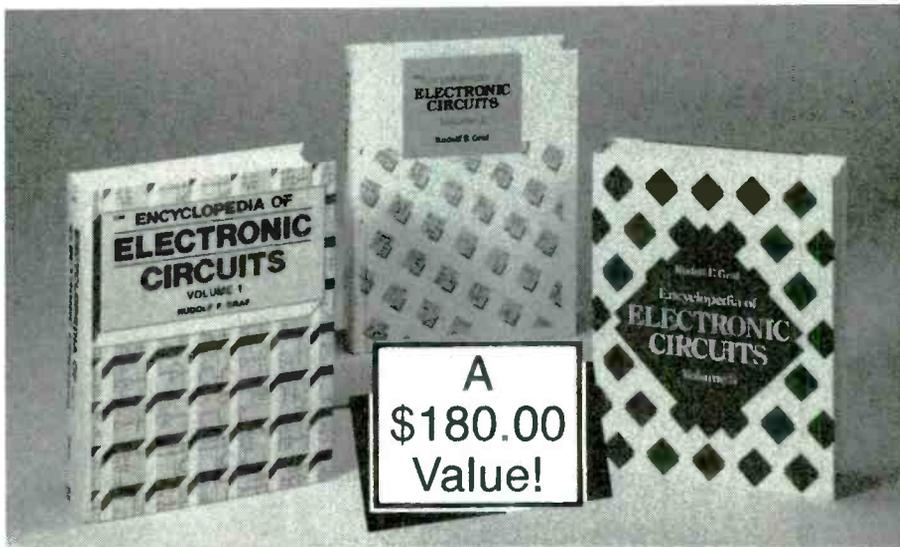Turn to this comprehensive circuit library for hundreds of project ideas . . . valuable troubleshooting and repair tips . . . and concise pinout diagrams and schematics. In each volume you'll find more than 700 electronic and integrated circuits and 100+ circuit categories right at your fingertips to give you ideas you can use on the job or at your workbench.



2,344 total pages 3,490 total illustrations

**Book No. 5489C Hardcover**

If coupon is missing, write to: *Electronic Engineers' Book Club*, P.O. Box 549, Blacklick, OH 43004-9918

### As a member of the *Electronics Engineers' Book Club* . . .

. . . you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off of regular publishers' prices. If you want the Main Selection do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. And you'll be eligible for *FREE BOOKS* through the Bonus Book Plan. Your only obligation is to purchase 3 more books during the next 2 years, after which you may cancel your membership at any time.

Publisher's price shown. © 1995 EEBC

### **ELECTRONICS ENGINEERS'** BOOK CLUB

A Division of McGraw-Hill, Inc., P.O. Box 549, Blacklick, OH 43004-9918

**YES!** Please send me *The Encyclopedia of Electronic Circuits—Vols. 1, 2 & 3 (5489C)*, billing me \$9.95 plus shipping/handling & tax. Enroll me as a member of the *Electronics Engineers' Book Club* according to the terms outlined in this ad. If not satisfied, I may return the books within 10 days and have my membership cancelled.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_ Phone \_\_\_\_\_

Valid for new members only, subject to acceptance by EEBC. Canada must remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions. A shipping/handling charge & sales tax will be added to all orders.

RPIF395

March 1995, Electronics Now

13

# LETTERS

Write to Letters, Electronics Now, 500-B Bi-County Blvd., Farmingdale, NY 11735

## REPRINTED PROGRAM

In the article, "Programmable Sinewave Generator" (Electronics Now, January 1995), program Listing 1 (pages 46 and 47) was printed on a background that was too dark and so the listing was hard to read. A clearer version is reprinted here.—Editor

## WRONG ADDRESS

In the article, "Power Controller" (Electronics Now, January 1995), on page 60 the address of Richard L. Roan is incorrect. It is P.O. Box 752, Saluda, VA, 23149.—Editor

## SWEEP/FUNCTION CORRECTIONS

The following corrections should be made to the article "Sweep/Function Generator," Electronics Now, December 1994, page 53:

Fig. 1—(1) Ground the negative side of capacitor C1 and the positive sides of capacitors C2 and C3. (2) Connect the collector of Q1 to the junction of R13, D4, and C9. (3) Connect the wiper lead of trimmer R22 to the "+" side of C10. (4) Ground the junction of resistors R37 and R40 and the collector of Q4. (5) Indicate that the -15-volt supply for IC1 is obtained from the anode of D8.

Fig. 4—(1) Diameters of three pilot holes (lowest row) should be 0.062, not 0.62 inch. (2) Diameter of first 0.375-inch hole (lower left) should be 0.234, not 0.375 inch. Diameters of two holes, right end of row, should be 0.375, not 0.234 inch.

Fig. 5—(1) Switch S2 pinout: connect pin 6 to the R27 wiper. (2) Switch S5 pinout: jumper pin 2 to pin 5 (R31) and jumper pin 1 to pin 3 (1, 3).

Page 56 "Circuit description:" In column 3, lines 17 and 18, change R11 to R12 and R15 to R16; line 24, change R11 to R30. Refer to the corrected schematic, Fig. 1.

Page 56 "Power supply:" The AC input is supplied by a 120-volt AC to 15- to 18-volt AC wall-outlet trans-

former, not a DC wall-outlet adapter. (Make this change in the parts list, page 60.)

Page 59 "Test and checkout:" In column 3, line 3, change R6 to R7; line 7, change R5 to R6.—Editor

## RETHINKING THE RESISTOR CUBE

As a retired electrical engineer, I enjoy the diversity of topics covered in Electronics Now. The article "Solving the Resistor Cube" (December 1994) triggered my memories of the early 1930s when I first

encountered the problem.

I agree that it's a good teaching aid, but please let's not give the upcoming generation of young engineers and technicians the impression that the solution is complex and difficult—four pages of diagrams and calculations—shame!

The author says that this is a beautiful example of "electronic symmetry" but he fails to take full advantage of that fact.

I didn't have a pencil and paper handy at the time, but by just look-

### LISTING 1

```
.....
*                               PSG CONTROL PROGRAM                               *
*                               COPYRIGHT 5/94 by R.J. PORTUGAL, NORTH HAVEN, CT. 06473, U.S.A. *
.....
DECLARE SUB FREQUENCY (L1, L2, FLAG)      '**** Frequency input routine
DECLARE SUB FREQCLR (L1, L2)              '**** Clear frequency entries
DECLARE SUB LOAD ()                       '**** Parallel-serial data convert
DECLARE SUB ERMSG (L1, L2)                '**** Error messages
DECLARE SUB DSPLY ()                       '**** Display screen

COMMON SHARED FMT$, N1%, N2%, K, DP, PORT$, MSG$( ), L1, L2
DIM Z AS STRING * 1: DIM MSG$(20)
FMT$ = "###,###,###,###.####": CLK = 32000283: K = (2 ^ 32 / CLK)

'-----
' To select NCO parallel printer remove the (') "comment symbol"
' in front of the appropriate program line.
' PRINTER PORT "LPT2" will be selected by the following:

'port$ = "LPT1": dp = &H3BC      '**** LPT1 DATA PORT ADDRESS
PORT$ = "LPT2": DP = &H378      '**** LPT2 DATA PORT ADDRESS
'port$ = "LPT3": dp = &H278      '**** LPT3 DATA PORT ADDRESS
'-----
***** (Message list) *****
MSG$(1) = "      Input range is from 0.00Hz to 10,000,000.00Hz      "
MSG$(2) = "      Program accepts numerals and a single decimal point  "
MSG$(3) = STRING$(64, " "): MSG$(4) = STRING$(21, " ")
MSG$(5) = "Last input not transferred to NCO": MSG$(6) = STRING$(50, " ")
MSG$(7) = "PSG output signal OFF"
MSG$(8) = "PROGRAMMABLE SINEWAVE GENERATOR CONTROL SCREEN"
MSG$(9) = "PSG printer port is " + PORT$ + ". "
MSG$(10) = PORT$ + " uses I/O port " + HEX$(DP) + " + HEX"
MSG$(11) = "COPYRIGHT 5/94 by R.J. PORTUGAL, NORTH HAVEN, CT. 06473, U.S.A."

COLOR 15, 1: CLS : CALL DSPLY: N1% = 0: N2% = 0: CALL LOAD
-----
DO: K$ = INKEY$                                '**** Main Program
IF LEN(K$) = 2 THEN                            'check keyboard entry for 2 character scan code
  IF ASC(RIGHT$(K$, 1)) = 59 THEN CALL FREQUENCY(5, 6, 1)      '**** [F1]
  IF ASC(RIGHT$(K$, 1)) = 60 THEN CALL FREQUENCY(8, 9, 2)      '**** [F2]
  IF ASC(RIGHT$(K$, 1)) = 61 THEN                                '**** [F3]
    N1% = 0: N2% = 0: CALL LOAD
    CALL FREQCLR(5, 6): CALL FREQCLR(8, 9)
  END IF
  IF ASC(RIGHT$(K$, 1)) = 62 THEN CALL LOAD      '*** [F4]
  IF ASC(RIGHT$(K$, 1)) = 63 THEN                '*** [F5]
    COLOR 6 + 16, 7: OUT DP, 1 + 8
    LOCATE 15, 40 - LEN(MSG$(7)) / 2: PRINT MSG$(7)          '*** Prints message
  DO: K$ = INKEY$: LOOP UNTIL K$ = CHR$(0) + CHR$(63)        '*** Wait for "F5" key
  COLOR 15, 1: LOCATE 15, 40 - LEN(MSG$(4)) / 2: PRINT MSG$(4) '*** Turns NCO clock ON
  OUT DP, 1
  END IF
  IF ASC(RIGHT$(K$, 1)) = 68 THEN GOTO endp      '*** [F6]
END IF
LOOP
endp: COLOR 7, 0: CLS
END                                             'xxxxx END PROGRAM xxxxx END PROGRAM xxxxx END PROGRAM
'-----
```

ing at the cube it was apparent to me that the battery current (I) entering one corner, the "in" junction will divide equally three ways—the three resistors at that junction will carry (I/3) current each. The three resistors on the "out" junction also will carry (I/3) each, and all other resistors will carry half that amount because the (I/3) current divides equally between them (as a result of symmetry).

The total voltage drop across the cube will equal the sum of voltage drop across the three resistors comprising a pathway—any pathway—from the "in" junction to the "out" junction. Thus, the voltage drops of the first "in" resistor as well as the last "out" resistor are  $R(I/3)$  each, and the resistor between

is  $R(I/6)$ .

Then I called on my grandson (who is in the fifth-grade and is a whiz at adding fractions in his head) to do the calculations. He said that  $\frac{1}{3} + \frac{1}{3} + \frac{1}{6} = \frac{5}{6}$ , so the cube voltage (E) is  $R(\frac{5}{6}I)$ . The net cube "in" to "out" resistance is  $E/R = (\frac{5}{6}R)$ .

Thus, I really didn't need my pencil and paper after all. A bit of advice here: Be sure to use a negative sign in summing if any pathway in a similar kind of problem includes a resistor in which current flows in the opposite direction.

I appreciated the opportunity to dig this little gem out from my dusty old memory files.

E.D. SISSON  
Columbus, OH

Ω

```

SUB DSDPLY
COLOR 15, 10: LOCATE 2, 40 - LEN(MSG$(8)) / 2: PRINT MSG$(8)
COLOR 15, 1: LOCATE 5, 1
PRINT "      [F1]      Enter Frequency 1          Hz"
PRINT "              (0.00 to 10,000,000.00Hz)    usec"
PRINT "
PRINT "      [F2]      Enter Frequency 2          Hz"
PRINT "              (0.00 to 10,000,000.00Hz)    usec"
PRINT "
PRINT "      [F3]      Clear Frequency 1 and 2 to zero": LOCATE 19, 1
PRINT "      [F4] Load NCO          [F5] Start/Stop PSG output"
PRINT "
PRINT "              [F10] End program-return to DOS"
COLOR 15, 10
LOCATE 23, 40 - (LEN(MSG$(9)) + LEN(MSG$(10))) / 2: PRINT MSG$(9) + MSG$(10)
COLOR 7, 9: LOCATE 25, 40 - LEN(MSG$(11)) / 2: PRINT MSG$(11); : COLOR 15, 1
END SUB

SUB ERMSG (L1, L2)          *** Displays 2 line error message
CALL FREQLR(L1, L2)
COLOR 14, 4: FOR i = 14 TO 15: LOCATE i, 9: PRINT MSG$(i - 13); : NEXT i
SLEEP 4: COLOR 15, 1: FOR i = 14 TO 16: LOCATE i, 9: PRINT MSG$(3): NEXT i
END SUB


SUB FREQLR (L1, L2)        *** Clears control panel F1 & F2 display areas
COLOR 14, 4: LOCATE L1, 45: PRINT MSG$(4): LOCATE L2, 45: PRINT MSG$(4)
END SUB

SUB FREQUENCY (L1, L2, flg)      *** F1 & F2 input routine
COLOR 14, 4: CALL FREQLR(L1, L2): LOCATE L1, 45: LINE INPUT f$
IF VAL(f$) > 10000000 OR VAL(f$) < 0 THEN CALL ERMSG(L1, L2): GOTO esub
dpf = 0
FOR i = 1 TO LEN(f$)          *** F1/2 numeral & multiple decimal point
  x$ = MID$(f$, i, 1)          *** check
  IF x$ = "." AND dpf = 0 THEN : dpf = 1: GOTO x
  IF x$ = "-" AND dpf = 1 THEN CALL ERMSG(L1, L2): GOTO esub
  IF ASC(x$) < 48 OR ASC(x$) > 57 THEN CALL ERMSG(L1, L2): GOTO esub
x: NEXT i
f = VAL(f$): LOCATE L1, 45: PRINT USING FMT$; f; '*** prints freq
LOCATE L2, 45
IF f <> 0 THEN PRINT USING FMT$; 1000000 / f;          *** period of F1 or F2
IF flg = 1 THEN N1$ = K * f          *** Converts F1 or F2 to a 32bit word
IF flg = 2 THEN N2$ = K * f          *** compatible with NCO input specs
COLOR 22, 7: LOCATE 16, 40 - LEN(MSG$(5)) / 2: PRINT MSG$(5): COLOR 15, 1
esub:
END SUB

SUB LOAD          *** Converts F1&2 into serial format & shifts them into NCO
FOR j = 3 TO 0 STEP -1: FOR x = 7 TO 0 STEP -1          ***** Xfer first 32 bits
  IF (PEEK(VARPTR(N2$) + j) AND 2 ^ x) > 0 THEN dt = 2 ELSE dt = 0
OUT DP, dt + 4: OUT DP, 1 + dt + 4          *** Serial data and shift
NEXT x: NEXT j          *** pulse generator
FOR j = 3 TO 0 STEP -1: FOR x = 7 TO 0 STEP -1          ***** Xfer second 32 bits
  IF (PEEK(VARPTR(N1$) + j) AND 2 ^ x) > 0 THEN dt = 2 ELSE dt = 0
OUT DP, dt + 4 + 16: OUT DP, 1 + dt + 4 + 16          *** Serial data and shift
NEXT x: NEXT j          *** pulse generator
OUT DP, 1 + 16          *** Xfers new F1&2 to NCO
COLOR 15, 1
LOCATE 16, 10: PRINT MSG$(6)
END SUB

```
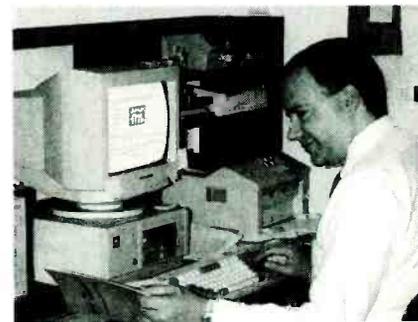
# EARN YOUR B.S. DEGREE IN COMPUTERS OR ELECTRONICS



## By Studying at Home

Grantham College of Engineering, now in our 45th year, is highly experienced in "distance education"—teaching by correspondence—through printed materials, computer materials, fax, modem, and phone.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand but complete and thorough lesson materials, with additional help from our instructors.

Our Engineering Technology B.S. Degree Program is available in either of two options:

- (1) The B.S.E.T. with Major Emphasis in Electronics, OR
- (2) The B.S.E.T. with Major Emphasis in Computers.

Our Computer Science B.S. Degree Program leads to the B.S.C.S.—the Bachelor of Science in Computer Science.

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Write or phone for our free catalog. Toll free, 1-800-955-2527, or see mailing address below.

Accredited by  
the Accrediting Commission of the  
Distance Education and  
Training Council


**GRANTHAM**  
College of Engineering  
Grantham College Road  
Slidell, LA 70460

# EQUIPMENT REPORTS

## Sencore CM125 Computer Monitor Signal Generator

*If you regularly test computer monitors, the Sencore CM125 computer monitor signal generator will make your work easier and you'll do it faster.*

CIRCLE 15 ON FREE INFORMATION CARD

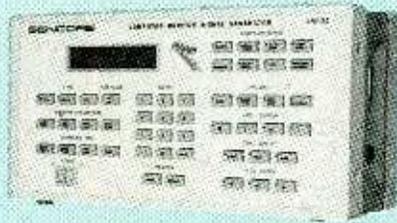

**T**he need for specialized computer monitor test equipment has increased dramatically in the last decade, not only in repair shops but at the factories where they are made. Monitor video bandwidth has expanded as a result of the increases in horizontal scan frequency and the display resolution.

Computer monitors with cathode ray tubes are among the most expensive personal computer peripherals, and they are those most likely to fail because of their high-voltage power requirements and the complexity of their scanning circuitry. With the price and performance of monitors increasing, they are no longer disposable components.

The CM125 "Pix Pak" computer monitor signal generator from Sencore is intended for testing, troubleshooting, evaluating, and comparing all brands of computer monitors and projectors on the shop test bench, at the burn-in rack, or in the field.

The CM125 offers a 125-MHz video bandwidth and pixel resolution of 2048 × 2048. The portable instrument is output protected to prevent it from being damaged by defective computer monitors under test. It weighs less than five pounds and has a price tag of \$2,995. (Sencore, 3200 Sencore Drive, Sioux Falls, SD 57107, 605-339-0100, 1-800-SENCORE.)

### How is it organized?

The CM125 is packaged in a book-sized rectangular case with an

array of resilient pushbutton controls and a liquid-crystal digital display on its front panel. Some of the pushbuttons contain LED function indicators. The pushbuttons on the left side are organized as TYPE, INTERLACE, MONITOR PARAMETERS, BLANKING TIME and POWER.

The middle pushbuttons are ENTRY AND MEMORY and those on the right side are VIDEO PATTERNS, POLARITY, VIDEO OUTPUT, SYNC OUTPUT, and SYNC ADDER. The two-line LCD readout shows the scan frequency, pixel resolution, and blanking timing of signals generated by the CM125.

The output terminal for phase-locking accessories, a 15-pin D-type connector, and sync and video outputs for driving the monitor under test are on the right side. An RS-232 connector for connecting a personal computer to automate test functions and an AC power jack are on the left side. A fold-down handle on top makes the instrument easy to carry, and fold-out bails on the back permit it to be positioned at different angles.

The first step in setting signal parameters is to select one of the three pushbuttons designated for the three different kinds of monitors—digital, analog, or ECL (emitter-coupled logic). A digital monitor receives TTL logic signals and can display a limited number of colors while an analog monitor receives a 0.714-volt signal and can display an infinite number of colors.

An ECL monitor, a form of digital monitor that receives a signal be-

tween -1.6 and -0.9 volts, can display a limited number of shades of gray. A fourth pushbutton turns the interlace scan on and off. Most computer monitors in service today are noninterlaced analog units.

The next step is to select the monitor parameters including horizontal sync frequency, horizontal pixel resolution, vertical sync frequency, and vertical pixel resolution. After a function is selected, numerical values are entered from a keypad. Horizontal frequency can be in the range of 10 to 250 kHz, vertical frequency can be from 10 to 250 Hz, and both horizontal and vertical pixels can range from 80 to 2048. The LCD normally displays the numerical value of those four settings.

Next, four blanking parameters must be set: front porch time, sync time, back porch time, and active video time. The combination of front porch, back porch, and sync times makes up the blanking time. That value added to the active video time equals the total scan time.


Four pushbuttons set the polarity of the video, horizontal sync, vertical sync, and blanking signals. Other pushbuttons activate red, green, blue (R, G, B), and (intensity (I) lines). Only digital monitors have an I output. Other controls turn the horizontal, vertical, and composite sync signals on and off, and add composite sync to the video.

The process of entering all parameters for certain monitors can be time-consuming, but the CM125 can test most popular monitors conveniently with the 43 factory setups stored permanently in memory. Moreover, the other 57 custom settings can also be stored.

### Available test patterns

After the CM125 is set for a specific monitor, a video pattern must be selected from the seven available patterns: raster, circle/cross, color bars, staircase, windows, multi-

*Continued on page 33*

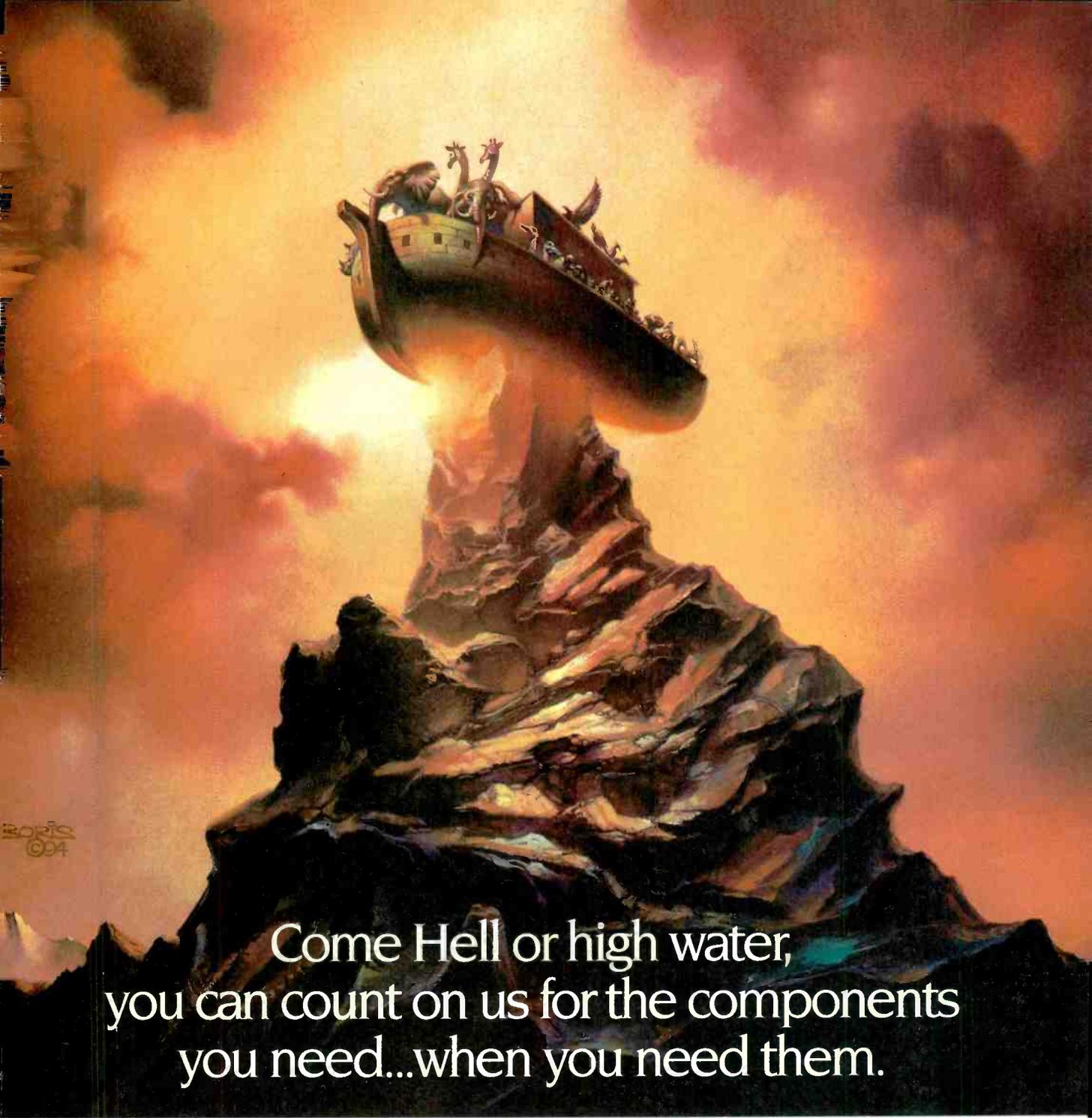

Come Hell or high water,  
you can count on us for the components  
you need...when you need them.

NTE distributors will move heaven and earth to make sure you get the critical part you need. And if for some reason they don't have




the exact resistor, capacitor, semiconductor, relay, or flyback transformer you're looking for, you won't have to wait 40 days and 40 nights. We'll drop ship it to your door the next day!

Best of all, NTE parts are easily cross-referenced to match over 250,000 U.S., Japanese and European components.

For information, the name of your local NTE distributor,

and a copy of our FREE Short Form Catalog, call us at 1-800-683-6837.

NTE. Action...not empty promises.

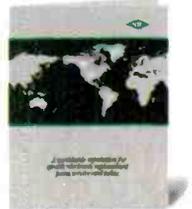

**NTE ELECTRONICS, INC.**

A WORLDWIDE REPUTATION FOR QUALITY, SERVICE AND VALUE

CIRCLE 71 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# NEW PRODUCTS

Use the Free Information Card for more details on these products.

**PC TRAINING KITS.** The Tech-Knowledge system is intended for teaching personal computer servicing, troubleshooting, and networking. Offered by Heathkit Educational Systems, it is now available in a single, comprehensive package, the EZS-400 for PC servicing, troubleshooting, and networking, or as three separate complementary units. They are the EZS-401 for PC Servicing, the EZS-402 for PC Troubleshooting, and the EZS-403 for PC local area networking.

Each training unit is complete with hardware, software, and course materials. The system is based on an IBM-compatible personal computer with an Intel 486 microprocessor. The PC can be upgraded by replacing the 486 processor with an Intel P24T Pentium processor.

The personal computer servicing course covers substantially all a student needs to know about servicing, maintaining, upgrading, and optimizing a personal computer. Hands-on exercises reinforce each topic covered in the textbook.

Students will be able to study the operation of various computer circuits with the guidance offered by



CIRCLE 20 ON FREE INFORMATION CARD

manufacturer's technical manuals and schematics. That knowledge can be applied to troubleshooting personal computers with the aid of diagnostic software and standard test equipment.

Instruction is also given in specifying, installing, and troubleshooting local area networks. The course also explains how to install and configure modems and communications software. It includes Microsoft Windows for Workgroups Software and Novell Personal NetWare.

The courses include seven of Heathkit's fault insertion and removal modules (FIRMs), circuit boards with DIP switches that permit the simulation of circuit faults without altering the training computer or its peripherals. Each course includes a student

text book, student work book, instructor's guide and course experiment parts packages.

The complete EZS-400 package includes two Zenith Data Systems computer trainers with multi-frequency color monitors, 210 Mbyte hard-disk drives and PS/2 compatible keyboard and mice. If purchased as separate units, the EZS-401 and EZS-402 packages each contain one computer and monitor. The EZS-403 package includes two computers and two monitors.

The pricing of the instruction packages is as follows: EZS-400—\$7495, EZS-401 and EZS-402—\$2495, and EZS-403 —\$5995.

### Heathkit Educational Systems

455 Riverview Drive  
Benton Harbor, MI 49022

**DSP DEVELOPMENT SYSTEM.** The digital signal processing development system from Domain Technologies is an integrated software development platform for the Texas Instrument TMS230C31 float-


ing-point, digital-signal processor (DSP). The system is intended for developing, testing, debugging, and running DSP software. It includes an assembler, a symbolic debugger, and a target card.

Applications for the system include algorithm development, data acquisition, instrumentation, telecommunications, and signal processing. The PC plug-in card contains a TMS320C31 IC, static

memory, an analog input/output port, and two independent personal computer interfaces.

The analog I/O unit includes an analog interface IC with 14-bit resolution and two RCA jacks. The interface IC can sample up to 19,200 samples per second, and it contains filters for anti-aliasing and smoothing.

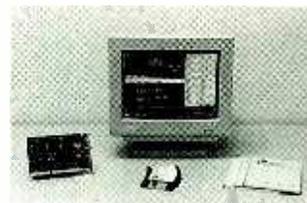The debugger screen interface is symbolic and visual. Each of the DSP's resources is displayed in its own window. A built-in assembler/disassembler can monitor and edit the application routine. Data can be displayed in one of seven modes, and up to 128 breakpoints can be set simultaneously. Programs written in C can be debugged at the source level.



CIRCLE 21 ON FREE INFORMATION CARD

The floating-point macro assembler is fully compatible with the TMS320C3x instruction set. It supports macro capabilities, conditional assembly, symbol table generation, source-level information, and full error diagnostics.

The DSP Development System is priced at \$600. **Domain Technologies, Inc.** 1700 Alma Drive #245 Plano, TX 75075 Phone: 214-895-7593 Fax: 214-985-8579 E-mail: domain@metro-net.com

# The Four-Year Electronics Degree Program That Really Hits Home!

## Bring The Technology Home With A Bachelor Of Electronics Engineering Degree. No Hassles. No High Cost!



Now's the time to prepare for a profitable career.

### We've lowered the cost of higher education.

It's true! You can earn a four-year Bachelor of Electronics Engineering Technology degree today ... and prepare yourself for a high-paying electronics career ... without quitting your job or ever leaving your home. Because World College, an affiliate of the Cleveland Institute of Electronics, offers you the total flexibility of independent study programs proven effective for people like you who truly want to succeed! World College independent study lessons help you build valuable skills

**Mail/Fax Today  
or Call  
1-800-696-7532**

step-by-step, and expert instructors are personally available to you with a toll-free call. What a way to earn an education!

### A world of opportunity.

Where is your career headed? With a four-year bachelor's degree from World College, you call the shots, choosing from incredible, high-paying opportunities in electronics, telecommunications, computer, electrical power, and many other growing fields.

World College gives you the skills, the knowledge, the power to take advantage of your best opportunity in electronics. And you can do it all at your own pace!

### Without leaving home.


World College continually works to provide its students with the most advanced education tools. From the latest equipment and reference books to breakthrough computer-simulated experiments, students are exposed to the latest technological advancements.

All the equipment, parts, and software you need are included in your affordable tuition, including more than 300 hands-on lab experiments you can complete in your home.
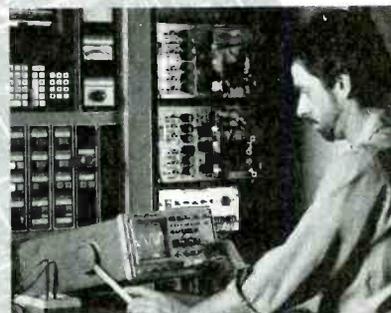
### Choose your own pace.

Earn your bachelor's degree on your time — and at your pace — because you pay tuition to World College only as you complete the upper-level semesters close to graduation. The faster you make it through, the less you pay. So you have an incentive to make your future happen quickly — yet the freedom to choose your own pace!

Send today for your FREE course catalog — and give yourself that future you've always wanted — with an electronics degree education from World College.




Take charge of your future in electronics.

### Four Powerful Reasons To Connect With World College Today:

1. Earn your four-year degree!
2. Self-paced training!
3. Independent study in your home!
4. Expert instruction!
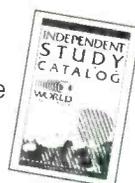
### Give Me The Power!

Send me a FREE World College course catalog today!



(Please Print Neatly)

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State, Zip \_\_\_\_\_

Phone ( ) \_\_\_\_\_

Age \_\_\_\_\_

**For faster service, call  
1-800-696-7532,  
or call  
1-804-464-4600.**

**Or fax this coupon to  
1-804-464-3687.**

  
**WORLD  
COLLEGE**

Lake Shores Plaza  
5193 Drive, Suite 113  
Virginia Beach, VA 23455-2500



Affiliated with  
Cleveland Institute of Electronics

WAE19

**CONSTANT-CURRENT POWER SUPPLY.** The Model 930 constant-current power supply from Calex has a temperature coefficient of 0.001%/°C and an output impedance of 10 megohms. Its power requirements are +12 to +32 volts. It is sold with a mounting kit that includes a potentiometer for setting constant current from 0 to +50 milliamperes.



**CIRCLE 22 ON FREE INFORMATION CARD**

The Model 930 can function as a bridge excitation supply. By adding a 10,000-ohm resistor, the supply becomes a stable 100-microampere current source for resistance-temperature sensors (RTD).

The Model 930 is priced at \$115.


**Calex Manufacturing Company, Inc.**

2401 Stanwell Drive  
Concord, CA 94520  
Phone: 800-542-3355  
Fax: 510-687-3333

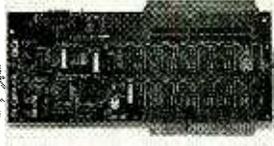**SMART EISA EXTENDER CARD.**

The EISA-EXT EISA extender card from ICS Electronics allows EISA and ISA bus add-on cards for IBM or compatible personal computers to be tested and debugged in the PC card cage without powering the computer up and down to change cards.

The EISA-EXT card protects the computer against power-supply overloads caused by the card under test. Solid-state switches on all signal lines permit the card under test to be



**CIRCLE 23 ON FREE INFORMATION CARD**

changed while the computer is running. The card can be operated either by a switch on the card or by I/O commands from the test program.

The turn-on sequence applies power and signals to the card under test in a sequence that avoids any conflict with the computer bus signals. The card continuously monitors the power lines to the card under test and shuts down all power and signals if an overcurrent condition is detected. Light-emitting diodes on the card indicate power, signal connection, and overcurrent.

The EISA-EXT card, including a disk with sample control programs and integrating software for Windows, is priced at \$595.


**ICS Electronics Corporation**

473 Los Coches Street  
Milpitas, CA 95035  
Phone: 408-263-5896

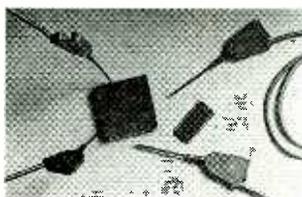**ULTRA-THIN TEST CLIPS.**

The Ultra-Thin Micrograbber series test clips from ITT Pomona are intended for microcircuit packages with finely spaced pins with up to 0.050 inch pitch. Narrow bodies that measure 0.12 inches permit close stacking of the clips.

The clip wiring is flexible to permit easy access from



**CIRCLE 24 ON FREE INFORMATION CARD**

different angles. Serrated surfaces on the plunger and finger tabs improve the holding ability of the test clips. The contact pincers open to 0.024 inch to grip the leads.

Two styles of test clips are available: single-ended and double ended. Single-ended clips with 40-inch lead wires are available in 10 colors. Double-ended clips (contacts on both ends) are available with black or red lead wires in 10-, 20-, or 30-inch lengths.


Ultra-Thin Micrograbber test clips are priced from \$4.50 each.

**ITT Pomona Electronics**

1500 East Ninth Street  
Pomona, CA 91766  
Phone: 909-469-2928  
Fax: 909-629-3317

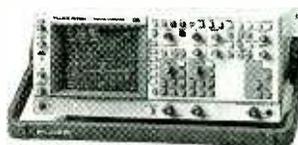**TWO-CHANNEL DIGITAL STORAGE OSCILLOSCOPE.**

The new PM 3380A from Fluke is a two-channel digital storage oscilloscope (DSO) with autoranging. The PM 3380 can automatically scale to signals. Autoranging continuously adjusts the timebase, and attenuators keep the signal on-screen during signal changes or while a circuit is being probed.



**CIRCLE 25 ON FREE INFORMATION CARD**

Special probes included with the PM 3380A have a user-programmable command switch near the tip. The switch, in conjunction with autoranging, allows the user to probe a circuit without having to make frequent changes on the control panel.

The probe-tip switch speeds up measurement

by allowing the user to switch between DSO and analog modes, recall stored setups, perform voltage and time measurements, and initiate an auto-set routine.

The PM 3380A can display the waveform on the external trigger input. It also has an over-sampling peak-detector, which reveals spikes and high-frequency noise at all time-base speeds. Other features include closed-case calibration with built-in voltage and time standards, TV line and field triggering, a built-in video line counter and standard computer. An RS-232-C interface permits printing out results.

The PM 3380A two-channel, autoranging digital oscilloscope is priced at \$3495.

**Fluke Corporation**

P. O. Box 9090  
Everett, WA 98206  
Phone: 800-44-FLUKE  
Fax: 206-356-5116

**DEOXIDIZER/CLEANER/PRESERVATIVE TREATMENT.**

DeoxIT from Caig Laboratories is a fast-acting, one-step deoxidizing solution for cleaning, preserving, lubricating, and enhancing conductivity of metal connectors and contacts on products such as switches, potentiometers, and relays.

The solution contains deoxidizers, preservatives, conductivity enhancers, anti-tarnishing compounds, and arcing and RFI



**CIRCLE 26 ON FREE INFORMATION CARD**



# TekMeter™ can show you the answer before you even know the question.

TekMeter™ is the new handheld instrument from Tektronix that combines the functions of a DMM and an oscilloscope. It's practically "auto everything" which in the service business means you'll get the answers you need faster than ever before.

It's easy. Just connect the probes. TekMeter finds the signal then makes the correct scope or DMM settings to display voltage, current or waveforms in the most meaningful way. What's more, your hands



CHECK OUT THE ENTIRE TEKTOOLS™ LINE FOR ALL YOUR MEASUREMENT NEEDS.

remain free to probe more accurately and safely. Especially in small places.

Weighing barely 2 pounds, TekMeter includes a host of features like cursors and spike detect that improve your ability to maintain and troubleshoot a wide range of equipment. TekMeter can even capture incoming line voltage spikes and sags, measure voltage and current simultaneously, compute true power, and more. All automatically. For as little as \$875\*



TekMeter is the answer you've been looking for. Contact your local authorized Tektronix distributor today, or call 800-426-2200, ext 299.

\*Suggested retail price, model TMS 550 © Copyright 1994, Tektronix, Inc. All rights reserved. TekMeter, TekTools, and Tektronix are trademarks of Tektronix, Inc. DPW-284597

# World's first wireless home theater system makes professional-quality surround sound affordable...

Now you can add surround sound to your home entertainment lineup with the amazing new Chase Technologies decoder that works with your existing stereo and an assortment of wired and wireless speakers.

by John Lindner

Let's face it. As much fun as renting a video can be, it's just not the same as seeing a movie in a theater. I remember the first time I saw *Jurassic Park*—I nearly jumped out of my seat when the dinosaurs roared. One of the reasons movies seem so real is because surround sound makes it seem

## The secret of surround sound

Surround sound has become the rage of the '90s because it adds depth and realism to stereo sound, giving you the home theater experience. In short, it makes you feel like you are actually at a concert a theater.

To get surround sound, some people have tried simply adding additional speakers to their home entertainment lineup. But it takes more than additional speakers to get surround sound; there needs to be a way of separating the original signal into distinct channels so that you're not just duplicating the same sounds and broadcasting them from different areas of the room.

The new Chase Technologies HTS-1 surround sound decoder does just that, and in a revolutionary way that rivals the best Dolby Pro-Logic and THX systems available. The HTS-1 provides five channels of sound from any two-channel stereo source.

The HTS-1 works with a variety of speakers. In the front, you can use your existing stereo speakers. For the rear, choose from inexpensive wired speakers, high-quality wireless speakers, or even an audiophile-quality wireless satellite subwoofer system. The HTS-1 also gives you the ability to add a powered center channel speaker (instead of using your TV's built-in speaker).



like you're actually there when events are happening. Now there's an incredible new device that lets you use your stereo receiver to get that same surround sound in your home.


**The secret's in the signal.** To get surround sound, you need to do more than simply add extra speakers. There needs to be a way of separating the signal from the musical score or movie soundtrack into distinct channel for each speaker. The new Chase Technologies HTS-1 surround sound decoder does just that, and in a revolutionary way that rivals the best Dolby Pro-Logic and THX systems available today.

**Wins over critics.** In the September 1994 issue of "High Performance Review," noted audio critic Daniel Kumin said "the HTS-1 can do quite a job of recreating a 3D theatrical experience...surround effects emanated with satisfying fullness...sound was clean at any level...with quite involving and natural sound ambience."



The new HTS-1 decoder won the **Design and Engineering Award at the Consumer Electronics Show** for being one of the best and most innovative new products.

**Surround™** signals in every stereo, videotape or laserdisc. This passive method is superior to active decoders such as Dolby and THX because it requires no AC current to decode. As a result, you experience more clarity, more detail, and a greater sense of space. Plus, you won't experience the noise or distortion which can occur with active decoding methods. You don't need any extra amps! Just connect the HTS-1 to your stereo, add your speakers, and you'll experience the magic of home theater at a fraction of the cost of other systems.

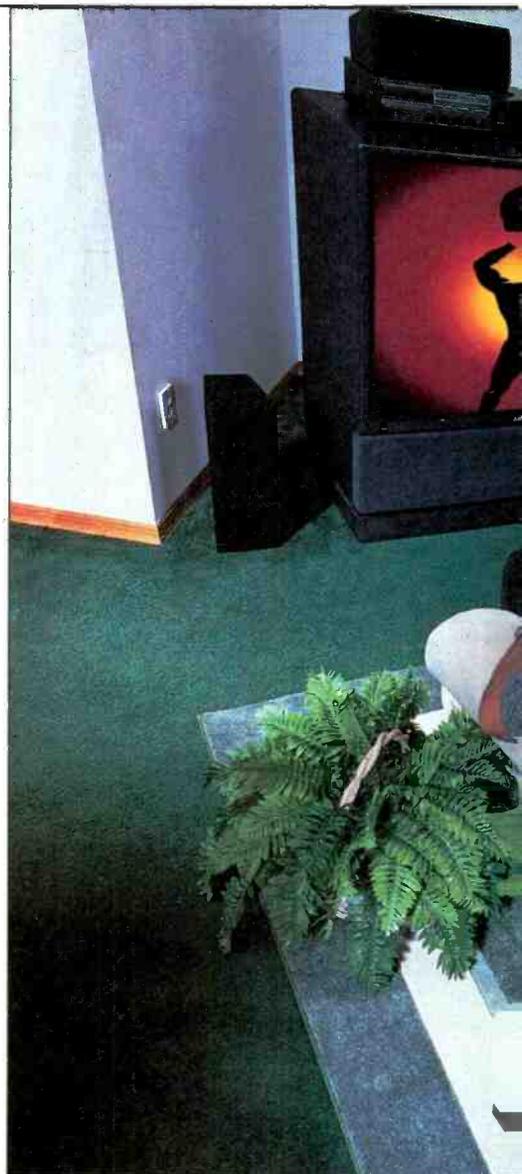

**Five channel options.** The HTS-1 decoder can be used with two, three, four or five channels of amplification, making it the most cost effective method for upgrading your stereo system to full home theater performance on the market. Best of all, the HTS-1 works with a variety of hard wired and wireless speakers.

In the front, most people use wired stereo speakers. Use your existing stereo's speakers or use one of a variety of wired speakers. Comtrad also offers the Chase Dialog center channel speaker. If your front speakers are more than eight feet apart, adding a center channel speaker will help keep voices and sound effects centered on the screen for stunning localization and clarity. The Dialog is self powered and video shielded to prevent interference with your television set.

The Chase HTS-1 decoder is the most cost-effective method for upgrading an existing stereo system to full home theater performance on the market.





The new Chase Technologies HTS-1 surround sound decoder gives you the option of using either traditional wired speakers like the Chase ELF-1s, or using wireless speakers or a wireless satellite subwoofer system for additional convenience and enhanced sound quality.

**Wireless freedom.** When it comes to rear speakers, you can again choose standard wired speakers like the Chase ELF-1s. But if you want to avoid the hassle of running speaker wire up and down walls, behind furniture, and under carpet, you can add the freedom and convenience of wireless speakers.

Recoton wireless speakers utilize a transmitter which broadcasts sound signals up to 150 feet through walls, floors and ceilings. The speakers can be placed anywhere; they plug into a standard electric outlet. This eliminates the need to have wires running from the stereo to the speakers, which can be a nuisance with surround sound since the rear speakers are often elevated or wall mounted.

**Affordable option.** Recoton's W440 speakers allow you to add wireless rear channel speakers without compromising the sound quality that wired speakers deliver. Each self-amplified speaker contains a two-inch tweeter and four-inch woofer. They deliver 10 watts per channel for strong, clear fill sound. Their compact design (9" high x 6" wide x 5.5" long), make them the perfect bookshelf-sized companion to your home entertainment set up.

**Audiophile quality.** For the true stereo enthusiast, we offer the Recoton self-amplified wireless satellite subwoofer system. The satellite speakers in the system each bolster 25 watts of clean, distortion-free sound. The subwoofer adds a whole new dimension to your home theater with its 50-watt amplifier that's capable of creating enough rumble to make you feel like you're in the middle of an earthquake.

The Recoton wireless subwoofer's 50-watt 10-inch speaker delivers thunderous bass that adds depth and realism to the surround sound experience.



Even the most discriminating surround sound enthusiast will be engulfed by the abundant power and delighted with the full-range, first-rate sound from these black oak vinyl veneer speakers.

**Easy to install.** Every speaker option offered by Comtrad can be easily installed with the HTS-1 in a matter of minutes. Just connect the speaker outputs of your receiver or amp to the HTS-1, then

## Speaker Options

### Wired Speaker Options

**Front Speakers:** The Chase HTS-1 surround sound decoder can utilize your existing stereo speakers, or any of a variety of wired speakers available through Comtrad or your local electronics dealer.



**Center channel speaker.** If the front speakers are more than eight feet apart, adding a center channel speaker will keep voice cues centered on the screen. We offer the Dialog. It is self-powered and video shielded to prevent interference with TVs. Dialog \$75 \$8 S&H



**Rear channel speakers.** We recommend the quality Chase ELF-1 in either white or black for inexpensive rear channel speakers. Mount them with the enclosed color-matched mounting brackets or flush mount them on the wall. ELF-1 . . . . . \$99/pair \$10 S&H

### Wireless Speaker Options



**Rear channel speakers.** Recoton W440 wireless speakers are the perfect option for people who want quality stereo rear channel speakers without having to run speaker wire. Their two-inch tweeters and four-inch woofers deliver 10 watts per channel—clear, strong stereo fill sound. The speakers work up to 150 feet from the transmitter without loss of sound quality. TX1000 transmitter (works unlimited speakers) . . . . \$69 \$7 S&H W440 wireless speaker (each) . . . \$89 \$9 S&H

Get the Chase HTS-1 half off (\$49) when you buy the W440 speaker system!



**Rear channel speakers.** For true audiophile-quality rear channel speakers, we offer the Recoton wireless satellite subwoofer system. This first-of-its-kind system combines a 10-inch rear-firing subwoofer with a pair of 25-watt satellite speakers. The subwoofer provides that distinctive "low-end punch" that you feel in movie theaters, while the satellites are designed to coincide



with surround sound processor specifications balance perfectly with the front speakers. WHT470 transmitter . . . \$69 \$7 S&H WHT421 wireless 50-watt subwoofer . . . . . \$299 \$24 S&H WHT462 pair of wireless 25-watt satellite speakers \$329 \$24 S&H

Get the Chase HTS-1 FREE when you buy the satellite subwoofer system!

connect speaker wire to the front and rear speakers. When using wireless speakers, connect the transmitter to the output. One transmitter will broadcast to each wireless speaker.

**Risk-free home trial.** The best way to evaluate surround sound is in your home—not a showroom. That's why we're offering the 30-day risk-free home trial. Try these products in your home and if you're not delighted with the the surround sound experience, return them for a full "No Questions Asked" refund.

HTS-1 surround sound decoder . . . . . \$99 \$10 S&H

Please mention promotional code 711-ET-1107.

For fastest service call toll-free 24 hours a day

**800-704-1211**



To order by mail, send check or money order for the total amount including S&H (VA residents add 4.5% sales tax.) Or charge it to your credit card, enclosing your account number and expiration date.

**COMTRAD INDUSTRIES**

2820 Waterford Lake Drive, Suite 106  
Midlothian, Virginia 23113

inhibitors. It is effective in the temperature range of  $-34^{\circ}\text{C}$  to  $200^{\circ}\text{C}$ .

DeoxIT is sold in spray and liquid containers and in wipes and pen applicators. Prices start at \$3.95 for a 2.3-milliliter vial.

**Caig Laboratories, Inc.**

16744 West Bernardo Drive, San Diego, CA 92127-1904  
Phone: 619-451-179  
Fax: 619-451-2799

**“GREEN” MICROCONTROLLER.** The MTE1122 energy management controller from Microchip Technology reduces total energy consumption up to 30% in products powered by AC motors. It is suitable for installation in residential, commercial, and industrial equipment and appliances such as refrigerators, washing machines, dryers, and heating, ventilation, and air-conditioning (HVAC) equipment.



CIRCLE 27 ON FREE INFORMATION CARD

The MTE1122 controller includes Microchip's eight-bit, RISC-based PIC16/17 microcontroller with proprietary power-management firmware. The controller monitors the motor load and then digitally controls power consumption by sampling at high rates.

When an AC motor is operating under light or no-load conditions, the controller monitors the AC signal and senses when the motor is consuming more power than is required. It then modifies the AC signal to allow the motor to

rotate at the same speed and maintain that speed while consuming less power.


MTE1122 energy management controllers are packaged in 18-pin plastic DIP and SOIC packages and work from 5-volt sources. The list price for the plastic DIP version is \$7.49 each in thousand-piece quantities.

**Microchip Technology Inc.**

2355 West Chandler Blvd. Chandler, AZ 85224-6199  
Phone: 602-786-7200  
Fax: 602-899-9210

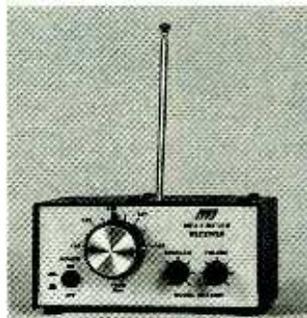**TWO-METER REPEATER MONITOR/RECEIVER KIT.**

The MFJ-8400K repeater monitor receiver kit from MFJ Associates is intended for the circuit builder who wants to build a two-meter receiver that will rival factory-made units costing hundreds of dollars more.



CIRCLE 28 ON FREE INFORMATION CARD

The completed monitor receiver offers a low-noise, high-gain, radio-frequency preamplifier for hearing weak signals. An air-variable tuning capacitor with a smooth 6:1 reduction drive simplifies receiver tuning. A dual-conversion superheterodyne receiver with ceramic filters and a crystal-controlled second oscillator is said to provide excellent selectivity and stability.

A 19-inch,  $\frac{1}{4}$ -wave whip antenna is included in the kit. A 50-ohm antenna in-

put accepts an external groundplane or Yagi antenna array.

The MFJ-8400K kit with a circuit board, metal cabinet, and an instruction manual is priced at \$69.95. A wired and tested receiver (MFJ-8400W) is priced at \$89.95.

**MFJ Enterprises, Inc.**


P. O. Box 494  
Mississippi State, MS 39762  
Phone: 601-323-5869  
Fax: 601-323-6551

**PHOTODIODE/AMPLIFIER IC.**

The OPT202 photodiode/amplifier from Burr-Brown is packaged in a five-pin, single-in-line package. It includes a 0.09-inch square photodiode, a precision FET-input transimpedance amplifier, and a 1-megohm feedback resistor on a single substrate. Its package allows light to enter the side of the package rather than from perpendicular sources.

The OPT202 is intended for industrial, medical, and laboratory instrumentation, position and proximity

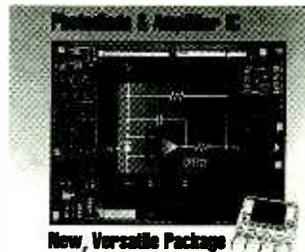sensors, photographic analyzers, machine tool controllers, and smoke detectors. The integrated device offers advantages over hybrid or discrete equivalent circuits by reducing or eliminating leakage-current errors, noise pick-up, and gain peaking from stray capacitance. The photodiode responsivity is 0.45 amperes per



New, Versatile Package

CIRCLE 29 ON FREE INFORMATION CARD

watt at 650 nanometers. OPT202 photodiode/amplifier ICs are priced at \$4.95 each in quantities of thousands.

**Burr-Brown Corporation**

Mary Douglas, Inquiry Handling Manager  
P. O. Box 11400  
Tucson, AZ 85734  
Tel: 602-746-1111  
Fax: 602-889-1510

**BE LESS PRODUCTIVE AT THE OFFICE.**

The office has always been a place to get ahead. Unfortunately, it's also a place where natural resources can fall behind. So here are some easy ways to reduce waste at the office. Turn off your lights when you leave. Help set up a recycling program. Try drinking out of a mug instead of throwaway cups. And always use both sides of a memo. It'll cut down on trash. Doing these things today will help save resources for tomorrow. Which is truly a job well done. 1-800-MY-SHARE.


IT'S A CONNECTED WORLD. DO YOUR SHARE.



A Public Service of This Publication



Earth Share

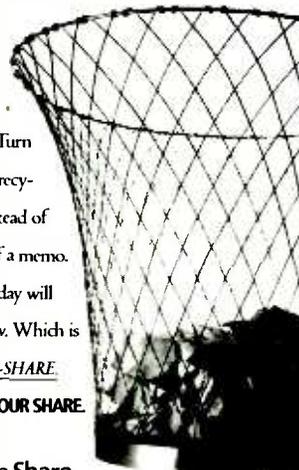

# Countersurveillance

**Never before has so much professional information on the art of detecting and eliminating electronic snooping devices—and how to defend against experienced information thieves—been placed in one VHS video. If you are a Fortune 500 CEO, an executive in any hi-tech industry, or a novice seeking entry into an honorable, rewarding field of work in countersurveillance, you must view this video presentation again and again.**

*Wake up!* You may be the victim of stolen words—precious ideas that would have made you very wealthy! Yes, professionals, even rank amateurs, may be listening to your most private conversations.

*Wake up!* If you are not the victim, then you are surrounded by countless victims who need your help if you know how to discover telephone taps, locate bugs, or “sweep” a room clean.

There is a thriving professional service steeped in high-tech techniques that you can become a part of! But first, you must know and understand Countersurveillance Technology. Your very first insight into this highly rewarding field is made possible by a video VHS presentation that you cannot view on broadcast television, satellite, or cable. It presents an informative program prepared by professionals in the field who know their industry, its techniques, kinks and loopholes. Men who can tell you more in 45 minutes in a straightforward, exclusive talk than was ever attempted before.

## Foiling Information Thieves

Discover the targets professional snoopers seek out! The prey are stock brokers, arbitrage firms, manufacturers, high-tech companies, any competitive industry, or even small businesses in the same community. The valuable information they filch may be marketing strategies, customer lists, product formulas, manufacturing techniques, even advertising plans. Information thieves eavesdrop on court decisions, bidding information, financial data. The list is unlimited in the mind of man—especially if he is a thief!

You know that the Russians secretly installed countless microphones in the concrete work of the American Embassy building in Moscow. They converted



**CALL NOW!**

**1-516-293-3751**

**HAVE YOUR  
VISA or MC CARD  
AVAILABLE**

what was to be an embassy and private residence into the most sophisticated recording studio the world had ever known. The building had to be torn down in order to remove all the bugs.

## Stolen Information

The open taps from where the information pours out may be from FAX's, computer communications, telephone calls, and everyday business meetings and lunchtime encounters. Businessmen need counselling on how to eliminate this information drain. Basic telephone use coupled with the user's understanding that someone may be listening or recording vital data and information greatly reduces the opportunity for others to purloin meaningful information.

**CLAGGK INC. EN**  
**P.O. Box 4099 • Farmingdale, NY 11735**

Please rush my copy of the Countersurveillance Techniques Video VHS Cassette for a total cost of \$53.95 each (which includes \$4.00 postage and handling).

No. of Cassettes ordered \_\_\_\_\_  
Amount of payment \$ \_\_\_\_\_  
Sales tax (N.Y.S. only) \_\_\_\_\_  
Total enclosed \_\_\_\_\_  
Bill my  VISA  MasterCard  
Card No. \_\_\_\_\_  
Expire Date \_\_\_\_\_ / \_\_\_\_\_  
Signature \_\_\_\_\_  
Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

All payments in U.S.A. funds. Canadians add \$4.00 per VHS cassette. No foreign orders.

The professional discussions seen on the TV screen in your home reveals how to detect and disable wiretaps, midget radio-frequency transmitters, and other bugs, plus when to use disinformation to confuse the unwanted listener, and the technique of voice scrambling telephone communications. In fact, do you know how to look for a bug, where to look for a bug, and what to do when you find it?

Bugs of a very small size are easy to build and they can be placed quickly in a matter of seconds, in any object or room. Today you may have used a telephone handset that was bugged. It probably contained three bugs. One was a phony bug to fool you into believing you found a bug and secured the telephone. The second bug placates the investigator when he finds the real thing! And the third bug is found only by the professional, who continued to search just in case there were more bugs.

The professional is not without his tools. Special equipment has been designed so that the professional can sweep a room so that he can detect voice-activated (VOX) and remote-activated bugs. Some of this equipment can be operated by novices, others require a trained countersurveillance professional.

The professionals viewed on your television screen reveal information on the latest technological advances like laser-beam snoopers that are installed hundreds of feet away from the room they snoop on. The professionals disclose that computers yield information too easily.

This advertisement was not written by a countersurveillance professional, but by a beginner whose only experience came from viewing the video tape in the privacy of his home. After you review the video carefully and understand its contents, you have taken the first important step in either acquiring professional help with your surveillance problems, or you may very well consider a career as a countersurveillance professional.

## The Dollars You Save

To obtain the information contained in the video VHS cassette, you would attend a professional seminar costing \$350-750 and possibly pay hundreds of dollars more if you had to travel to a distant city to attend. Now, for only \$49.95 (plus \$4.00 P&H) you can view *Countersurveillance Techniques* at home and take refresher views often. To obtain your copy, complete the coupon or call .

# NEW LITERATURE

Use The Free Information Card for fast response.

**Create Your Own Multimedia System; by John McCormick.** Windcrest/McGraw-Hill, Blue Ridge Summit, PA 17294-0850; Phone: 1-800-233-1128; Fax: 717-794-2103; \$32.95, including disk.


This book explains how to assemble a complete multimedia production system including monitors, input devices, CD-ROM drives, MIDI sound controllers and software. It explains multimedia issues, including computer system requirements, performance specifications, hardware and software sources, installation procedures, and operation tips. The diskette included with McCormick's book contains sample commercial multimedia demonstration and shareware programs.



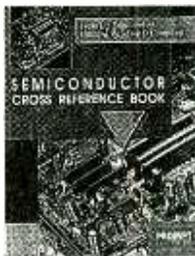**CIRCLE 337 ON FREE INFORMATION CARD**

The topics covered in this book include Macintosh and IBM PC and compatible operating environments; graphics, sound, and animation hardware and software; JPEG, MPEG, QuickTime and other compression standards; and storage devices and CD-ROM drives.

**Semiconductor Cross Reference Book; from the Engineers of Howard W. Sams & Company.** Prompt Publica-



**CIRCLE 338 ON FREE INFORMATION CARD**

**tions, 2647 Waterfront Parkway, East Drive, Indianapolis, IN 46214-2012; Phone: 800-428-7267 or 317-298-5710; Fax: 317-298-5604; \$24.95.**

This book from the publishers of "Photofact" documentation is a cross-reference guide for semiconductor device replacements and substitutions. It includes more than 490,000 part numbers, type numbers, and other identification for devices made in the United States, Europe, and the Far East.

By including replacements for NTE, ECG, Radio Shack, and TCE devices, the book functions as a four-way cross reference. All major classes of semiconductors are included: bipolar transistors, MOSFETs, diodes, rectifiers, ICs, and SCRs. Light-emitting diodes and thermal sensors are also included. An appendix has an updated listing of device original equipment manufacturers.

**1995 Full-Line Catalog. Hub Material Company (HMC), 33 Springdale Avenue, Canton, MA 02021; Phone: 617-821-1870; Fax: 821-4133; free.**

This pictorial 1995 catalog from Hub Material Co.

includes descriptions of tools, test equipment, and technical materials for the assembly, testing, and repair of electronic products offered by Hub.

Among the items listed and pictured in this catalog are precision hand tools including screwdrivers, pliers, wire strippers, and tweezers. Soldering supplies include solder, fluxes,



**CIRCLE 339 ON FREE INFORMATION CARD**

soldering irons, tips, sponges and wicks. ESD prevention products include wrist straps, protective bags, conductive mats, and special tools. Test equipment includes power supplies and oscilloscopes. Also offered are tool kits and cases. The catalog contains tables for comparing the product features.

**Pager Power; by Ted Strauss.** Ten Speed Press, P. O. Box 7123, Berkeley, CA 94707; Phone: 800-841-2665 or 510-559-1600; Fax: 510-524-4588; \$4.95.

This pocket-sized book explains how to turn your inexpensive numeric pager into a powerful communications device and save the expense of a cellular phone. The techniques described also save money



**CIRCLE 340 ON FREE INFORMATION CARD**

over the use of alphanumeric pagers.

A handy code dictionary in the book provides more than 11,000 easy-to-use codes for frequently used words and phrases. It also gives users an easy way to add many personally selected words and phrases. A form at the back of the book, when filled in, becomes a directory for active names and phone numbers. You look up the words and phrases to be sent, key in the recipient's pager number, and press the code numbers. The recipient looks up the code or codes in his copy of your code book to interpret the message.

Entries include single words that are listed alphabetically and phrases that are listed both by situation (e.g., change in plans, emergency, reminders) and alphabetic order. The book provides XPress codes (those most often used) and shortcuts (100 of the most frequently used words, prefixes, and suffixes).

**Data Acquisition Catalog & Reference Guide. Keithley MetraByte, 440 Myles Standish Blvd., Taunton, MA 02780; Phone:**

## Just like these Fully Trained Electronics Professionals



"Thanks to CIE I have tripled my previous salary, and I am now in a challenging and rewarding new field where only the sky is the limit."  
**Daniel Wade Reynolds**  
**Industrial Electrician**  
 Ore-Ida Foods



"CIE was recommended to me by my boss. It was appealing since I could study at my own pace at home and during business travel."  
**Dan Parks**  
**Marketing Manager/Consumer Products**  
 Analog Devices, Inc.



"I loved the flexibility CIE offered. It was the only way I could continue both school and my demanding job."  
**Britt A. Hanks**  
**Director of Engineering**  
 Petroleum Helicopters, Inc.




"I liked the way the school was set up with laboratory assignments to enforce conceptual learning. The thing which impressed me the most about CIE's curriculum is the way they show application for all the theory that is presented."  
**Daniel N. Parkman**  
**Missile Electro-Mechanical Technician**  
 U.S. Air Force



"Completing the course gave me the ability to efficiently troubleshoot modern microprocessor based audio and video systems and enjoy a sense of job security."  
**Tony Reynolds**  
**Service Manager/Technician**  
 Threshold Audio & Video
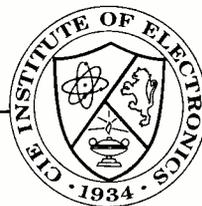
# Graduate with an Associate Degree from CIE!



CIE is the best educational value you can receive if you want to learn about electronics, and earn a good income with that knowledge. CIE's reputation as the world leader in home study electronics is based solely on the success of our graduates. And we've earned our reputation with an unconditional commitment to provide our students with the very best electronics training.

Just ask any of the 150,000-plus graduates of the Cleveland Institute of Electronics who are working in high-paying positions with aerospace, computer, medical, automotive and communications firms throughout the world. They'll tell you success didn't come easy...but it did come...thanks to their CIE training. And today, a career in electronics offers more rewards than ever before.

### CIE'S COMMITTED TO BEING THE BEST...IN ONE AREA...ELECTRONICS.

CIE isn't another be-everything-to-everyone school. CIE teaches only one subject and we believe we're the best at what we do. Also, CIE is accredited by the National Home Study Council. And with more than 1,000 graduates each year, we're the largest home study school specializing exclusively in electronics. CIE has been training career-minded students for nearly sixty years and we're the best at our subject...  
**ELECTRONICS... IT'S THE ONLY SUBJECT WE TEACH!**

### CIE PROVIDES A LEARNING METHOD SO GOOD IT'S PATENTED.

CIE's AUTO-PRO-GRAMMED® lessons are a proven learning method for building valuable electronics

career skills. Each lesson is designed to take you step-by-step and principle-by-principle. And while all of CIE's lessons are designed for independent study, CIE's instructors are personally available to assist you with just a toll free call. The result is practical training... the kind of experience you can put to work in today's marketplace.

### LEARN BY DOING...WITH STATE-OF-THE-ART EQUIPMENT AND TRAINING.

CIE pioneered the first Electronics Laboratory



Course and the first Microprocessor Course. Today, no other home study school can match CIE's state-of-the-art equipment and training. And all your laboratory equipment, books and lessons are included in your tuition. It's all yours to use while you study and for on-the-job after you graduate.

### PERSONALIZED TRAINING...TO MATCH YOUR BACKGROUND.

While some of our students have a working knowledge of electronics others are just starting out. That's why CIE has developed twelve career courses and an A.A.S. Degree program to choose from. So, even if you're not sure which electronics career is best for you, CIE can get you started with core lessons applicable to all areas in

electronics. And every CIE Course earns credit towards the completion of your Associate in Applied Science Degree. So you can work toward your degree in stages or as fast as you wish. In fact, CIE is the only school that actually rewards you for fast study, which can save you money.



## YES!

I want to get started. Send me my CIE course catalog including details about the Associate Degree Program. (For your convenience, CIE will have a representative contact you - there is no obligation.)

Please Print Clearly

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_ Age \_\_\_\_\_

Phone No. \_\_\_\_\_

Check box for G.I. Bill Benefits.  
 Veteran  
 Active Duty **AE72**

Cleveland Institute of Electronics, Inc.  
 1776 East 17th Street  
 Cleveland, OH 44114

A School of Thousands.  
 A Class of One. Since 1934.

Send for CIE's FREE Course Catalog and See How We Can Help Your Career Too!

**1-800-348-0033; Fax: 508-880-0179; free.**

This 288-page catalog from Keithley MetraByte describes more than 40 hardware, software, and accessory products that it is offering. Many have been optimized for Windows-based data-acquisition applications. The products pictured and described include the DAS-1800 and DAS-800 families of plug-in data-acquisition boards, the DAS-TC thermocouple input board, the VisualDAS custom control software package, and the TestPoint multitasking, object-oriented software package.

The full color catalog also describes the company's plug-in boards and software packages, signal-conditioning products and accessories, IEEE-488.2 personal computer interfaces, serial interfaces, Personal Computer Instrument Product (PCIP) boards, Series 500 data acquisition instruments, and industrial data acquisition systems.




**CIRCLE 341 ON FREE INFORMATION CARD**

Expanded technical reference sections include product-selection indexes, application notes, technical tips, and a glossary. An enclosed project block-diagram worksheet is intended to help readers document their application requirements. Worksheets can be faxed to Keithley MetraByte for free advice on the most cost-effective way to implement those requirements.

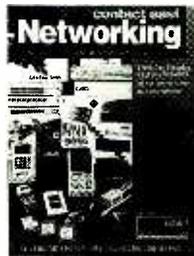**Networking: Products for Installing, Maintaining & Repairing Networks. Contact East, 335 Willow Street, North Andover, MA 01845; Phone: 508-688-2000; Fax: 508-688-7829; free.**

This 48-page catalog from Contact East contains information on its products for installing, maintaining, and repairing networks. The products highlighted in this catalog include new insulated hand tools, digital multimeters and accessories, cordless power tools, clamp meters, infrared temperature probes, and handheld and remote digital storage oscilloscopes.



**CIRCLE 342 ON FREE INFORMATION CARD**

The catalog also describes Contact East's lines of tools for wire crimping, stripping, and cutting as well as its soldering supplies, wire sorters, circuit testers, network testers, communication test equipment, and measuring tools.

**Mosaic Quick Tour for Windows: Accessing & Navigating the Internet's World Wide Web; by Gareth Branwyn. Ventana Press, P. O. Box 2468, Chapel Hill, NC 27515; Phone: 919-942-0220; Fax: 919-942-1140; \$12.**

This book describes the World Wide Web, a system for interlinking information on the Internet. Mosaic, with its graphically rich interface and point-and-click access, is said to be ideal for navigating the Web. Branwyn's book will help



**CIRCLE 343 ON FREE INFORMATION CARD**

the reader to obtain maximum benefit from Mosaic.

The book defines hyperlinked World Wide Web, Mosaic, hypertext, and HTML, and it discusses its underlying language. Also covered are system requirements and software downloading and configuration. You will learn how to use Mosaic for FTP, telnet, and newsgroup reading. The book also contains a listing of art galleries, magazines, music archives, software libraries, and other resources. It also describes special ways to explore the World Wide Web.

**1994/1995 Embedded Control Handbook. Microchip Technology Inc., 2355 West Chandler Blvd., Chandler, AZ 85224-6199; Phone: 602-786-7200; Fax: 602-899-9210; free**

This 1376-page technical reference book from Microchip Technology on embedded control is available through any authorized Microchip distributor or sales representative. It discusses Microchip's PIC16/17 field-programmable eight-bit microcontrollers and nonvolatile memory products. In-




**CIRCLE 344 ON FREE INFORMATION CARD**

cluded are more than 78 application notes as well as software code written for specific embedded-control applications.

Sections include those on multiplexing LED drives and a 4 x 4 keypad for sampling; implementation of an asynchronous serial I/O; serial port utilities; implementing ohmmeter/temperature sensors and serial port utilities. The book includes schematic and timing diagrams, math routines, and illustrations to explain applications.

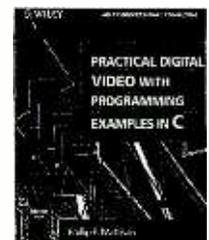**Practical Digital Video with Programming Examples in C; by Phillip Mattison. John Wiley & Sons, Inc. 605 Third Avenue, New York, NY 10158-0012; Phone: 1-800-CALL-WILEY; \$39.95 including disk.**

Mattison's book will help software developers gain a comprehensive working knowledge of digital video and multimedia programming in C language. This practical guide explains the vital elements of personal computer motion video in a comprehensible, non-mathematical style. The companion diskette includes 20 sample programs with source code, plus clips of sample motion videos.



**CIRCLE 345 ON FREE INFORMATION CARD**

The book points out the differences between graphical and natural images, and the reasons for compressing image data. It describes and compares

various computer displays and comments on their suitability for natural video. Different methods of color representation are explained, and their applications to multimedia are described. Also covered are available video-storage techniques and major data-compression techniques. It presents several PC video hardware systems, and discusses two popular PC video environments—Microsoft Video for Windows and Apple Quicktime.

**Mega-Brite Lites Selection Guide No. 84-3. Lumex Opto/Components Inc., 292 East Hellen Road, Palatine, IL 60067; Phone: 708-359-2790; Fax: 1-800-944-2790; free.**

This product selection guide describes a family of 35 high-intensity red,


green, and yellow light-emitting diodes sold under the Mega-brite Lites label. Available in six sizes of radial-lead plastic packages, the LEDs can serve as illumination sources, indicators that can be seen as far away as 100 feet, and indoor signs. They can also serve as outdoor lights automobiles. The guide includes full specifications, including detailed outline drawings and emission patterns for each of the six package sizes.  $\Omega$



**CIRCLE 346 ON FREE INFORMATION CARD**

**Coil Design and Construction Manual**

• • •

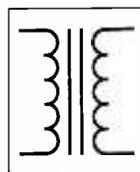

# YOU CAN WIND YOUR OWN COILS?

There's no trick to it except knowing what you are doing. In a unique, 106-page book you can become expert in winding RF, IF, audio and power coils, chokes and transformers. Practically every type of coil is discussed and necessary calculations are given

with the mathematical data simplified for use by anyone. Get your copy today!

Mail coupon to:

**Electronics Technology Today, Inc.  
P.O. Box 240 • Massapequa Park, NY 11762-0240**

Please send me my copy of *Coil Design and Construction Manual* (BP160). I enclose a check or money order for \$8.45 to cover the book's cost and shipping-and-handling expenses. NY state residents must add local sales tax.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

All orders must be paid in U.S. funds only. Sorry, no orders accepted outside of USA and Canada. Please allow 6-8 weeks for delivery.

## EQUIPMENT REPORTS

*continued from page 16*

burst, and text. The patterns can be cycled automatically to prevent the electron beam from damaging the CRT screen of the monitor under test.

The *raster* pattern produces a solid box on the monitor's screen surrounded by a one-pixel wide border. This border indicates color purity and high-voltage power supply regulation. The box should be pure white when all video outputs are on, and it should switch to solid black when the video polarity is reversed. The edges of the box must be straight and ripple-free.

The *circle/cross* pattern of light colored circles and grid on a black background provides a test of the monitor's linearity and convergence. Each line should be straight and each box should be square. The circles must be round and without distortion. The dots permit checking static convergence and the dots and lines permit check-

ing dynamic convergence.

The *color bar* pattern tests a monitor's ability to produce proper color. All color bars should be present and the colors should be uniform in intensity from top to bottom and left to right to detect possible video amplifier defects.

The *staircase* pattern tests brightness and contrast linearity of analog and monochrome digital monitors. If those monitors are working correctly, they will display of 16 evenly spaced bars ranging from black to 100 % white.

The *windows* pattern tests the monitor's power supply regulation. It shows up as a checkerboard pattern of four black and five white squares on a field of nine squares. Transitions between the black and white squares should be clear and distinct. All the white boxes should have the same brightness level and the entire screen should be ripple free.

The *window* pattern, a white box on a black field, is widely used by monitor manufacturers for making internal contrast and brightness adjustments.

The *multiburst* pattern, similar in appearance to the *windows* pattern except that the vertical and horizontal resolution lines replace the white boxes, test monitor resolution and bandwidth. The vertical lines test the horizontal pixel resolution and the horizontal lines test the vertical resolution. The one-pixel wide lines should be discernible on a properly operating monitor.

The *text* pattern fills the screen with upper- and lower-case text characters that duplicate user conditions. All characters on the screen should be focused and easy to read. This pattern is used to make the final performance test on the monitor.

The CM125 computer monitor signal generator is an expensive instrument, but its performance is not easily matched by features in other computer monitor testers at any price, especially portable instruments suitable for field use. It can make short work of high-volume symptom, field, burn-in testing, and quality assurance testing. It is also suitable for giving monitor demonstrations.  $\Omega$

# GET THE LATEST ADVANCES IN ELECTRONICS

SUBSCRIBE TO—

# Electronics NOW<sup>®</sup>



## ENJOY THE WORLD OF ELECTRONICS EACH MONTH!

Subscribe to the best informed electronics magazine—the one that brings you the latest high-tech construction projects, feature articles on new technology, practical troubleshooting techniques, circuit design fundamentals, and much more.

**Electronics Now** looks to the future and shows you what new video, audio and computer products are on the horizon. You'll find helpful, monthly departments such as Video News, Equipment Reports, Hardware Hacker, Audio Update, Drawing Board, Computer Connections, New Products, and more. All designed to give you instruction, tips, and fun.

### Electronics Now gives you exciting articles like:

- Buyer's Guide to Digital Oscilloscopes
- Build A Scanner Converter
- Single-Chip Voice Recorder
- Build A MIDI Interface for your PC
- Troubleshoot Microprocessor Circuits
- Build A High-Power Amplifier for your Car
- Add Music On Hold to your Phone
- All About Binaural Recording
- VGA-to-NTSC Converter



FOR FAST SERVICE CALL OUR TOLL-FREE NUMBER!

# 1-800-999-7139

## DON'T DELAY — SUBSCRIBE TODAY!

If you prefer, just fill out the order card in this magazine and mail it in today.

JTAG / COP

PLL

# MICROPROCESSORS

## Two decades of microprocessor history

STEPHEN J. BIGELOW

SINCE THE DAYS OF THE FIRST vacuum-tube computer, designers have sought better, faster, and cheaper computer performance. Improvements in these areas directly mirror the evolution of device technology from vacuum tubes to transistors, integrated circuits, Large Scale Integration (LSI), and Very Large Scale Integration (VLSI). Important milestones along the way include the introduction of integrated circuits in 1964, and the introduction of the microprocessor—often called the MPU (microprocessing unit) or, more commonly, CPU (central processing unit)—in 1971.

This article provides an overview of how both microprocessors and the computer industry have evolved. Whether you are a computer user, hobbyist, technician, or designer, this article will help you understand what microprocessors are, how they work, and how they developed. The article also includes a capsule history of microprocessor development (see "Early Times in the PC Biz"), and a glossary of microprocessor-related terms (see "Microprocessor Glossary and Nomenclature").

### What is a microprocessor?

The internal workings of today's microprocessors are certainly more sophisticated than those of such pioneers as the 6502 (MOS Technology), the MC6800 (Motorola) or the 8080 (Intel). Even so, today's complexity only builds on underlying architectures that have remained almost unchanged for 20 years.

At heart, the microprocessor is an "engine" that performs arithmetic and logic functions in a generalized way. Ordinary logic ICs are designed to pro-

duce specific outputs based on specific inputs and internal logic. By contrast, the microprocessor's outputs are determined by stored logic—software—that can vary.

For example, Fig. 1 shows a block diagram of the 8-bit 8080A CPU. Although it might appear imposing at first glance, each block falls into one of three categories: registers, instruction/control elements, and the arithmetic logic unit or ALU.

**Registers** are individual RAM locations that are contained within the microprocessor itself. Nearly every microprocessor has a register called the *accumulator*, which stores values and the results of arithmetic and logical operations.

Another important register shared by nearly all microprocessors is called the *program counter*, which tracks the address in the computer's main RAM memory where the next program instruction will come from. While the microprocessor is executing a current instruction, it also updates the program counter to point to the address of the next instruction. The actual program instruction that is to be executed is passed to the *instruction decoder* via the *instruction register*.

The CPU can also jump to another location in RAM to execute an instruction, in several ways. One is to Jump or Branch directly to that location and continue program execution there. Another is to execute a *subroutine*, usually via a Call, Jump to Subroutine, or Branch to Subroutine instruction. After the subroutine completes its duties, the CPU resumes pro-

gram execution at the instruction that immediately follows subroutine-Call, -Jump, or -Branch instruction.

When the CPU performs a Call, it *pushes* the contents of the program counter onto a special section of main computer memory called the *stack*. Conversely, when returning from a subroutine, the address is then *popped* off the stack and loaded back into the program counter. Another CPU register called the *stack pointer* keeps track of the next free location on the stack. As the CPU calls subroutines (pushes) and returns from them (pops), the stack pointer slides up and down the stack. The stack can also store the contents of various CPU registers.

Other registers are used for temporary data storage and to index memory. For example, in the 8080, the H, L, D, E, B, C, W, Z, as well as the Accumulator, are all 8-bit registers that serve as general-purpose (or *scratchpad*) registers. Newer microprocessors contain more and larger registers, but the concept is the same.

**Instruction/Control** To execute a program instruction, the CPU must usually perform a series of steps such as reading data from a memory or input/output (I/O) location, writing data to a memory or I/O location, manipulating the contents of one or more CPU registers, and handling the results of ALU operations. The actual series of steps depends on the particular instruction. Thus, each instruction must be translated by an *instruction decoder* from the single machine-language instruction into a series of simple functions that the CPU can execute.

Keeping all of the components of a CPU running smoothly re-



MOTOROLA's 68030 second-generation 32-bit microprocessor.

quires precise timing and synchronization, which is usually managed by a crystal-based clock/oscillator. Early CPUs such as the 8080A required an external oscillator. Today's CPUs contain internal oscillators that require only an external crystal and perhaps a small capacitor or two.

Each clock pulse allows the CPU to perform one operation. However, one instruction can require several operations. As a result, it may take 20 to 30 clock pulses for a CPU to perform a complete instruction, such as adding two numbers.

There are two basic ways to enhance CPU speed: 1) increase clock speed, and 2) decrease the number of operations that are required to execute each instruction. For example, suppose that 25 clock pulses are needed to perform a simple addition. If the CPU clock ran at 10 MHz, each clock pulse would take 0.1 microsecond ( $\mu\text{s}$ ), so the addition would be completed in  $(25 \times 0.1 \mu\text{s}) = 2.5 \mu\text{s}$ . If the CPU ran at 60 MHz, each clock pulse would be only 16.7 nanoseconds ( $0.0167 \mu\text{s}$ ), so the same addition would be complete in  $(25 \times 0.0167 \mu\text{s}) = 0.4175 \mu\text{s}$ . That value represents a six times improvement in raw speed. The other way to improve performance is to re-

duce the number of operations required per instruction. Today's microprocessors use both techniques.

Several control signals influence a microprocessor's operation. One important function, for example, is reading and writing memory and I/O ports. How does the system distinguish between reads and writes? Some microprocessor families have a single read/write line; the Intel family has separate read and write lines. Whenever the CPU wants to write some data to memory or to an input/output (I/O) port, it asserts (brings low) its WRITE line. Likewise, when it wants to read data, it asserts its READ line.

Another important function involves *interrupts*. Whenever a situation requiring the CPU's attention occurs, the CPU's current task can be interrupted, and its focus shifted to the interrupting task. Devices such as keyboards, disk drives, and memory-refresh circuits demand the CPU's attention with *interrupt requests* (IRQs). Early CPUs such as the 6800, the 6502, and the 8080 had a single interrupt input. Many current devices offer as many as 16.

Another potential problem that a microprocessor must contend with is the varying speeds of devices in a computer

system. The CPU is usually the fastest device in a system; memory and I/O ports are typically slower, and mechanical devices such as disk drives are slower yet. Because of these speed differences, an external device may not be ready when the CPU tries to read it. To ensure coordination, microprocessors have WAIT and READY signal lines, which allow the CPU to idle for a clock pulse. That idle period is called a *wait state*. Although wait states are still common in computer systems today, good system design minimizes their use.

The last control function to be discussed here is microprocessor reset. When asserted, the RESET line of a microprocessor sets all the registers to known states and begins program execution at a specific location in memory.

**ALU** The real power in a CPU is not in its registers or control section, but in its *Arithmetic/Logic Unit* (ALU). The ALU is the "brain" within the CPU; it is what carries out most logical operations, comparisons, and arithmetic functions. Some CPUs delegate high-order math functions to a separate math coprocessor, but most ALUs add, subtract, increment, decrement, compare, and perform logical operations (AND, OR, NOT, XOR). After each ALU operation, a set of *result flags* indicates the status of the result (carry, borrow, or zero).

### The Intel family

Intel CPUs have been at the forefront of desktop personal computing since IBM selected the 8088 for use in its first IBM PC. Since it was introduced, the so-called x86 architecture has undergone five major evolutionary stages. The first generation includes the 8088, the 8086, and the 80186. The next three generations include the 80286, the 80386, and the 80486. The fifth and most recent includes the Pentium. Intel is already working on both the sixth and seventh generations, as yet unnamed. Table 1 summarizes differences between the various CPU family members, ranging

from the early 8088 (as used in the original IBM PC) to what many consider today's performance leader, the Pentium.

The head of the family is the 8086. In the era ruled by 8-bit microprocessors, the 8086 quickly became the first widely-used 16-bit microprocessor. (When speaking of the number of bits a microprocessor has, data-bus width is usually the value referred to.) In addition to doubling the data bus width from 8 to 16, the 8086 also increased the number of address lines from 16 to 20, thereby providing what seemed at the time an abundant one megabyte of addressable memory.

The 8088 is essentially the same chip as the 8086, except that its 16-bit data bus is multiplexed down to 8 bits. That trades off system costs at the expense of performance. Note in Table 1 how data-bus band-

width decreases by more than a factor of two from the 8086 to the 8088. Multiplexing the data bus down to half its internal width is a "trick" Intel played over and over in the evolution of the 8086 line.

The 80186 is an 8086 with several common support functions built right in: clock generator, system controller, interrupt controller, DMA (Direct Memory Access) controller, and timer/counter. No Intel CPU before or since has offered as much integration in a single package. The 80186 was also the first to abandon 5-MHz clock speeds in favor of 8-, 10-, and 12.5-MHz rates. The 186 was not used as a mainstream CPU for desktop computers; rather, it was limited to "embedded" applications.

The 80286 offered the first real architectural advance over the 8086. The 286 pushed

memory to 24 address lines, resulting in a 16-megabyte address space. In order to access all that memory, the 286 also introduced a new mode of operation, called *protected mode*.

The 80286 booted in an 8088/86-compatible mode called *real mode*, but through a special instruction, it could switch into the more advanced protected mode to gain access to the additional memory, as well as to advanced programming features. However the only way to get back into real mode from protected mode is to force a complete reset of the microprocessor—a time-consuming process that eliminated the 80286 as a viable engine for running multitasking operating systems such as Windows and OS/2.

The next major advance came in 1985: the 80386. It was Intel's first 32-bit microprocessor, and

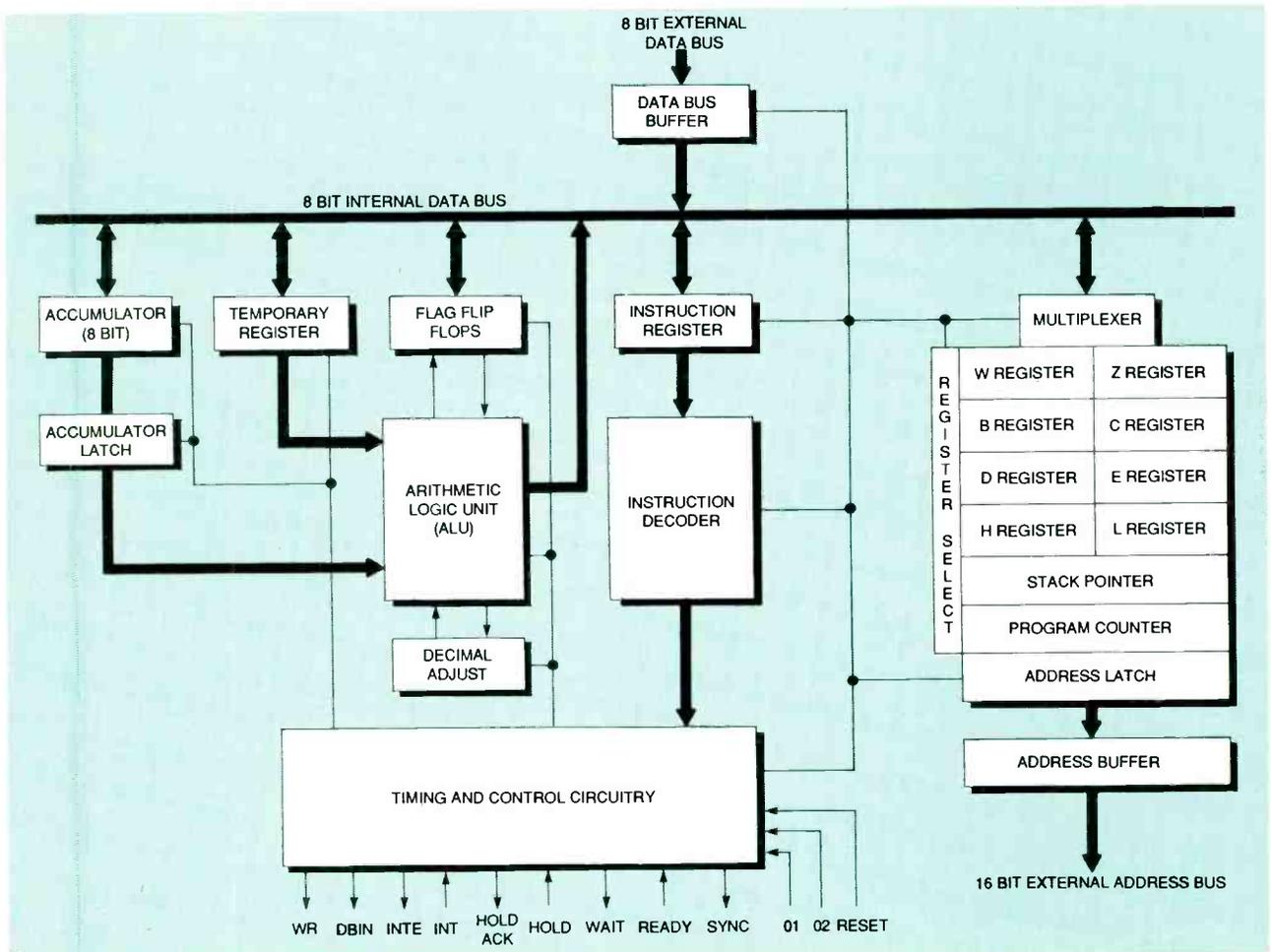


FIG. 1—ARCHITECTURE FOR A GENERATION: Intel's 8088 microprocessor, as used in the original IBM PC.

TABLE 1—INTEL CPU FAMILY CHARACTERISTICS

CPU	Date Introduced	Number of Transistors	Data Bits	Address Bits	Physical Address Space (Virtual)	Clock Speeds (MHz)	Data Bus Bandwidth (MB/sec)	MIPS (at Max Clock Speed)	Math Coprocessor
8086	1978	29,000	16	20	1 MB	5, 8, 10	5	0.75	8087
8088	1978		16 (8 external)	20	1 MB	5, 8	2	0.75	8087
80186	1980		16	20	1 MB	8, 10, 12.5			
80286	1982	134,000		24	16 MB (1 GB)	8, 10, 12.5	12.5	2.66	80287
80386	1985	275,000	32	32	4 GB (64 TB)	16, 20, 25, 33	50	11.4	80387
80386SX	1988		32 (16 external)	24	16 MB	16, 20, 33		3.6	80387SX
80386SL	1990	855,000 (external)	32 (16 external)	24	16 MB	16, 20, 33			80387SL
80486	1989	1,200,000	32	32	4 GB (64 TB)	25, 33		26.9	Internal
80486SX	1991		32	32	4 GB (64 TB)	16, 20, 25, 33		20.2	80487
80486 DX/50	1991		32	32	4 GB (64 TB)	50		41.1	Internal
80486DX2/50	1992		32	32	4 GB (64 TB)	25 (50 internal)		40.5	Internal
80486DX2/66	1992				4 GB (64 TB)	33 (66 internal)		54.4	Internal
80486SL	1992	1,400,000	32	32	4 GB (64 TB)	25, 33		26.9	Internal
80486dx2/40	1993				4 GB (64 TB)	20 (40 Internal)		21.1	Internal
80486SX/SL	1993				4 GB (64 TB)	33		26.9	Internal
80486DX/SL	1993				4 GB (64 TB)	33		26.9	Internal
80486DX4	1994				4 GB (64 TB)	33 (100 internal)			Internal
Pentium	1993	3,210,000	64 (32 internal)	32	16 MB (64 TB)	60, 66, 90, 100		111.6 (at 66 MHz)	Internal

provided 32 bits on both the data and address buses. Like the 286, the 386 boots in real mode. It also offers a protected mode, multiple simultaneous "virtual" real-mode sessions, and efficient mode switching. The 386 was the first Intel CPU to enhance processing speed through the use of *instruction pipelining* (also known as *scalar architecture*), which allows the CPU to start working on a new instruction before completing the current one.

In 1988, Intel took a step "backward" with the 80386SX. It was built around the core 32-bit CPU of the 386, but provided only a 16-bit external data bus, and a 24-bit address bus. Although the performance of the 386SX was significantly lower than the 386, so was its price, so system costs could be reduced. Another version of the 386 came in 1990: the 80386SL. With its 24 address lines and 16-bit external data bus, the 386SL closely resembled the 386SX. But it also incorporated system functions for running a standard PC, and power-management circuitry that optimized the device for

use in portable computers.

All members of the 386 family can operate with stand-alone math coprocessors (80387DX, 80387SX, and 80387SL).

### The 486 family

Like the 80386, the 80486 incorporates pipelining to improve instruction execution performance. The 486 also adds a new wrinkle: on-chip cache memory. Cache reduces memory-access time by storing copies of recently used instructions and data in fast static RAM, rather than relatively slow DRAM. Another improvement was the inclusion of a floating-point unit in the CPU itself.

Of course, Intel found ways to "SX" the 486 line to provide a less expensive option for system designers. Unlike previous SXs, the data-bus width was not halved on the 486SX. However, the 486SX does not include the on-chip floating-point unit or math coprocessor. One important innovation in the 486 line was the introduction of 3-volt devices for laptop computers and other low-power applications.

Another interesting feature of

the 486 is its upgradeability. Computer systems based on prior generations were pretty much locked in to the performance level attainable by whatever the built-in CPU offered. But the 486 was designed from the beginning for upgradeability via what Intel calls "OverDrive" technology. OverDrive technology generally replaces your current CPU with one that runs twice as fast—internally. But you don't get twice the overall performance. Nonetheless, an OverDrive CPU is cheaper than buying a whole new PC. It is vital to note that not all 486 systems are upgradeable via OverDrive technology; check with your computer's manufacturer to be sure.

The 486 has spawned numerous variations, including a full 50-MHz model (the 80486DX/50), and the aforementioned 486SX, which is upgradeable if the computer's motherboard was designed to accept an OverDrive CPU.

The first wave of OverDrive CPUs arrived in 1992 with the introduction of the 80486DX2/50 and the 80486DX2/66. The DX2/50

# Earn Top Dollar as a Multimedia Programmer!

**America's #1 choice for at-home training. Only NRI gives you hands-on experience with a fast, powerful 486DX2/66 MHz multimedia computer system you train with and keep!**

Today, computer programming is not only the fastest-growing computer career field, it's also one of the most respected, highest-paid professions in America. And no wonder: Recent advances in multimedia applications have put programmers at the forefront of yet another new revolution — one that's changing forever the way the world lives, learns, and works with computers.



Opportunities to create interactive multimedia programs are everywhere: in retail, to increase sales with immediate, point-of-purchase kiosks; in education,


to increase students' level of understanding and retention in all subject areas; and in business and industry, for more persuasive sales presentations and for cost-efficient and effective skills training.

Now, with NRI's one-of-a-kind training in Multimedia Programming, you can take advantage of this growing specialty field and chart your future in an exciting, money-making career.

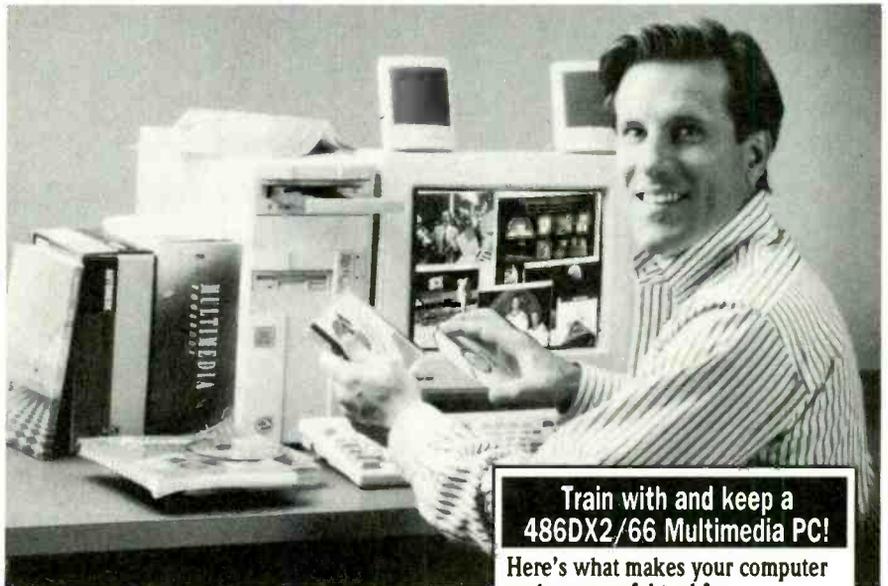**NRI's Multimedia Programming course includes everything you need for a fast start in a new career**

NRI's unique modular training gets you started fast with step-by-step lessons and hands-on projects that bring theory to life and reinforce every important concept. Your training is *complete* computer programming training, starting with the basics and moving on to the more advanced languages used in today's multimedia authoring programs.

Best of all, you train with and keep a powerful, state-of-the-art 486DX2/66 MHz computer, Windows 95 — the newest version of this popular graphical user interface — and Multimedia Toolkit authoring software. What's



**Train with and keep a 486DX2/66 Multimedia PC!**

**Here's what makes your computer such a powerful tool for multimedia programming:**

- High speed Intel 80486DX2 CPU with 66 MHz clock
- 420 megabyte hard disk drive
- Built-in math coprocessor
- ZIF socket
- Pentium Overdrive-ready motherboard
- 8 meg RAM installed
- High density 3.5" floppy disk drive
- Fax/modem
- Double-speed CD-ROM drive, sound card, and speakers
- 14" Super VGA color monitor with .28mm pitch and tilt-swivel base

more, you turn this powerful computer into an MPC-2 system when you add the CD-ROM drive, sound card, and stereo speakers included in your course!

## You're backed by a team of pros

NRI's team of professional instructors is behind you all the way — on hand and ready to assist if you need help at any point in your training. And now, you can complete your training even faster with NRI's new TeleGrading system that lets you take your tests and get your grades 24 hours a day by phone!



Send for your free full-color catalog that describes every aspect of NRI's breakthrough training in multimedia programming as well as at-home training in other high-tech career fields.

If the coupon is missing, write to NRI Schools, McGraw-Hill Continuing Education Center, 4401 Connecticut Ave., NW, Washington, DC 20008.

**Send Today For Your Free Catalog  
Or call 1-800-321-4634 extension 1068**

**SEND THIS COUPON TODAY!**

**NRI Schools** McGraw-Hill Continuing Education Center  
4401 Connecticut Ave., NW, Washington, DC 20008

**YES! I'm interested in learning more about this exciting new course! Please rush my FREE catalog today!**



- Check one only:
- |  |   |   |
|--|---|---|
| <input type="checkbox"/> Multimedia Programming  | <input type="checkbox"/> Programming in C++         | <input type="checkbox"/> Bookkeeping                |
| <input type="checkbox"/> Computer Programming    | <input type="checkbox"/> With Windows               | <input type="checkbox"/> Fiction/Nonfiction Writing |
| <input type="checkbox"/> Microcomputer Servicing | <input type="checkbox"/> PC Applications Specialist | <input type="checkbox"/> Desktop Publishing         |


Name \_\_\_\_\_ (Please Print) Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

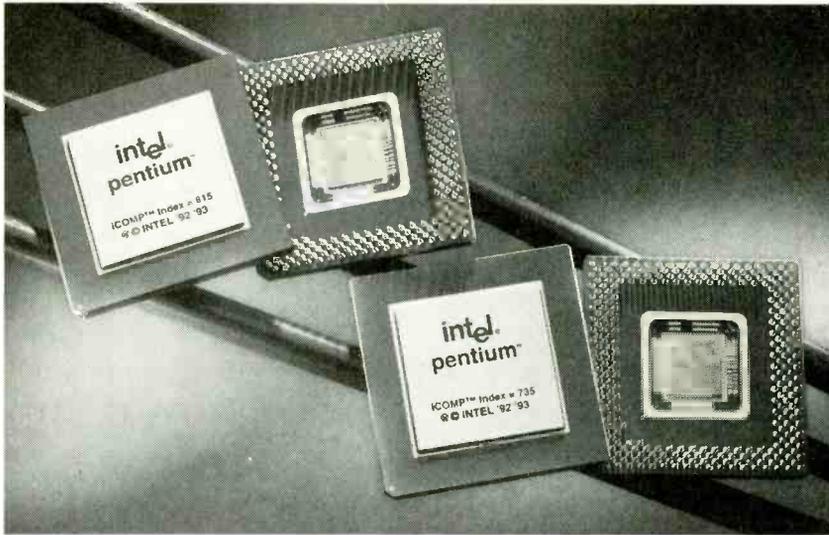Accredited Member, National Home Study Council 1900-0395



INTEL'S Pentium.

runs on a 25-MHz bus, but at 50-MHz internally; the DX2/66 runs at 66 MHz on a 33-MHz bus. The slower bus speeds allowed the OverDrive CPUs to work directly with existing PC motherboard designs. Both OverDrive CPUs offer internal math coprocessors, and are themselves upgradeable to even faster OverDrive versions. The DX2/50 is available in 3- and 5-volt versions, while the DX2/66 is available only in the 5-volt version.

In 1992, Intel produced a highly-integrated, low-power version of the 80486 called the 80486SL. Its 32-bit data bus, 32-bit address bus, 8 kilobytes of on-board cache, and integrated math coprocessor make it similar to other 486 CPUs. However, the SL includes power-management circuitry that optimizes the device for use in mobile computers. The 486SL is available in 25- and 33-MHz versions, and in both 3- and 5-volt designs.

In 1993 Intel rounded out the 486 family by introducing the 486DX2/40, the 80486SX/SL, and the 80486DX/SL. The DX2/40 is another OverDrive CPU, this one intended to run in 20-MHz PCs. The SX/SL and DX/SL devices are similar to the original versions, but with SL-type power-management capabilities. These devices in essence made the special 486SL mentioned previously obsolete, angering several manufac-

turers in the process.

The latest addition to the 486 line is the DX4 series, which are clock-tripled devices that run on 25- and 33-MHz buses. With the X4 nomenclature Intel appears to imply that the DX4's larger cache (16 kilobytes vs. 8 kilobytes in prior models) achieves greater than a three

times performance improvement. All versions of the 486 run the same software, and are backward compatible with all x86 CPUs going all the way back to the 8086/8088.

## The Pentium

By 1992, the 486 had become well-entrenched in everyday desktop computing, but Intel was already laying the groundwork for the next generation. Nearly everyone expected Intel to continue its traditional numbering scheme and dub the next CPU the 80586. However, Intel wanted more control over who used similar names for competing processors, so it changed to a name that is more easily trademarked: Pentium. It was introduced in 1993.

The Pentium retains the 32-bit address bus of the 486, but doubles the data bus to 64 bits. All versions of the Pentium include an on-board math coprocessor, and are intended

## Early Times in the PC Biz

The CPU powering the PC on your desk probably contains more than a million transistors. However, its lineage traces all the back to Intel's 4004, which was developed in 1971. The 4004 was a four-bit processor. It contained 2,300 transistors, and ran at 108 kHz. The 4004 sold well and found service in early desktop calculators.

Following the 4004, Intel developed the 8008 (in 1972) and the 8080 (in 1974). It was the 8080 that really helped launch the personal-computer revolution. The 8080 could address only 64 kilobytes of memory, but it was the first well-accepted 8-bit microprocessor. Later (in 1976) Intel introduced the 8085, which was basically an 8080 with some built-in system logic. Then a company called Zilog produced what was probably the first clone microprocessor, the Z80. The Z80 was 8080 compatible, but included enhancements such as faster clock rates and a richer instruction set. Motorola entered the CPU market in 1975 with its 8-bit 6800, and the 6502 was developed around the same time by MOS Technology.

By the late 1970's, the first wave of personal computers had hit the market. Tandy introduced the 8080-based TRS-80 Model I in 1977. The 6502-based Apple II also appeared in 1977. In 1979 came the 6502-based Commodore PET. Dozens of companies produced 8080- and Z80-based machines that ran the first "business" operating system, CP/M. CP/M originally stood for

Control Program/Monitor, but eventually took on the meaning Control Program for Microcomputers.

But even as the 8-bit market was developing, the era of the 16-bit computing loomed ahead. By 1978, Intel developed its first 16-bit CPU: the 8086. Then, in 1979, Intel found a way to multiplex the 16-bit data bus down to 8 bits, thereby allowing systems to be built less expensively. The 8088 contained 29,000 transistors, and was available in 5- and 8-MHz versions. Both the 8088 and the 8086 offered 20 address lines, which gave them a memory capacity of 1 megabyte—16 times more than the 64 kilobytes offered by the 8080, 6800, and 6502.

Motorola parried Intel by introducing the 68000, a true 16-bit CPU. Apple shortly abandoned the aging 6502 and used the 68000 in the Macintosh. Zilog attempted to stay in the 16-bit competition with the Z8000, but was unable to attract interest from major computer manufacturers.

What helped Intel gain the prominence that it has today was IBM's selection of the 8088 for the original IBM PC, introduced in 1981. The PC made many compromises in the name of cost-effectiveness. Major functions including video and disk storage were stripped out and incorporated on separate plug-in boards. That in turn helped to create a huge market for peripherals. No one, including IBM, accurately forecast the impact the PC would have.


to be compatible with future OverDrive designs.

The Pentium has two 8-kilo-byte caches—one for instructions and another for data. A dual-pipeline technique (known as *superscalar* architecture) allows the Pentium to process more than one instruction per clock cycle. Other substantial improvements include on-board power management (similar to the 486SL line). Currently the fastest released model runs at 100 MHz, and Intel has publicly demonstrated 150-MHz versions.
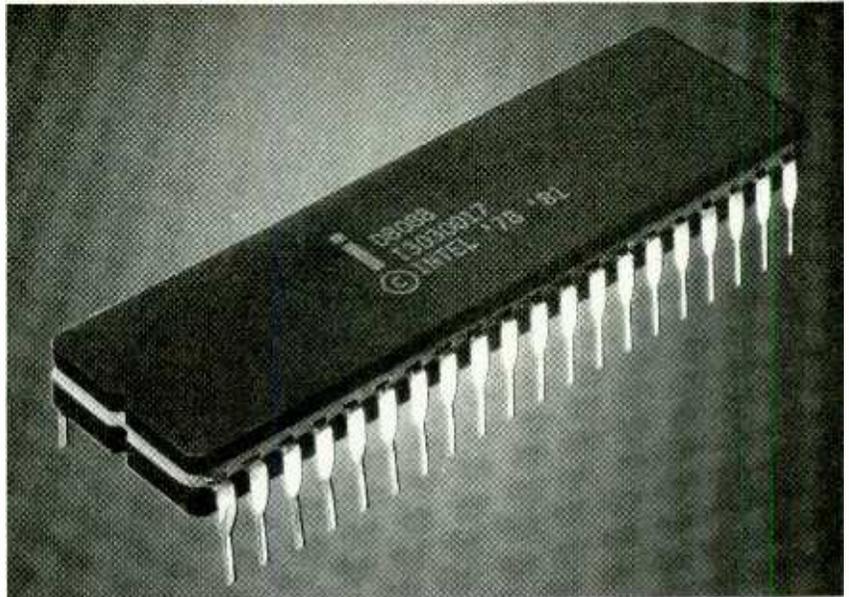
### The Motorola family

Intel CPUs (and the computers built on them) capture the majority of customers and market share in the PC industry. Nonetheless, Motorola has also enjoyed an excellent reputation in the microprocessor arena. Motorola CPUs have long been—and continue to be—the microprocessor of choice for Apple's line of personal computers. Many embedded and high-performance computer designs have also carried Motorola CPUs. Table 2 summarizes features of the Motorola line of CPUs.

Motorola's initial microprocessor introduction was the 6800 in 1975. It was strictly an 8-bit processor capable of addressing 64 kilobytes of memory. Probably the most striking difference between the Motorola and Intel architectures is that early members of the 6800 family tended to minimize register



INTEL's 8088.

usage in favor of general-purpose RAM.

Motorola introduced numerous variations of the 6800. The 6802 incorporated 128 bytes of RAM on the CPU itself. The 6803/6808 ran faster (3.58 MHz), incorporated 128 bytes of RAM, and included both a UART (universal asynchronous receiver/transmitter) for serial communications, and a counter/timer. The last variation of the 8-bit Motorola family was the 6809. It was similar to the 6802, but offered an enhanced instruction set, including what was probably the first multiply instruction on an 8-bit CPU.

Some of the earliest personal-computer kits were based on the 6800 family, and Tandy built a version of the Color Computer

that was rather advanced (for its day) around a 6809. However, by 1978, the age of the 16-bit CPU had begun, and the second generation of personal computers that included the Apple Macintosh and the IBM PC would be 16-bit machines.

### The 68000 family

In 1978 Motorola introduced its first 16-bit CPU: the 68000. Unlike Intel's 8086/8088, which could address only one megabyte of physical RAM, the 68000 had 24 address lines that could access 16 megabytes of RAM directly—it was an almost inconceivable amount of memory at the time. In addition, the 68000 ran faster than mainstream Intel processors of the day: 16 MHz. Also, Motorola abandoned

TABLE 2—MOTOROLA CPU FAMILY CHARACTERISTICS

CPU	Data Bits	Address Bits	Physical Address Space (Virtual)	Clock Speeds (MHz)	Notes	MIPS	Math Coprocessor
6800	8	16	64 K	2			
6802	8	16	64 K	3.58	128 bytes RAM		
6803/6808	8	16	64 K		128 bytes RAM + UART		
6809		16	64 K				
68000	16	24	16 MB	16		1.6 MIPS	6881
68020	32	32	4 GB	16, 33		5.5 MIPS	68882
68030	32	32	4 GB	16+–50	256 byte cache	12 MIPS	6882
68040	32	32	4 GB	25, 40	8 K cache	35 MIPS	Internal
68060	32	32	4 GB	50, 66	16 K cache	100 MIPS	Internal

the idea of RAM-based registers and incorporated 16 general-purpose registers in the 68000. It would be four years until Intel could approach the technology of the 68000.

Motorola entered the 32-bit CPU arena with the 68020. Like the 68000, the 68020 has 16 general-purpose registers, and can address four gigabytes of RAM directly. A first for the 68020 was the inclusion of an internal 256-byte instruction cache—negligible by today's standards, but a true architectural advance at the time.

The 68030 is Motorola's second-generation 32-bit CPU. It is very similar to the '020, but is available in faster speeds, and with one 256-byte cache each for data and instructions.

The 68040 is the third generation. It increases the data and instruction caches to 4 kilobytes each, and, for the first time, includes an on-board math coprocessor and memory-management unit.

One of the latest members of the 680x0 family is the 68060. The 68060 is a *superscalar* design that has multiple instruction pipelines, and on-board memory and power management.

### PowerPC

After more than a decade of development, the 680x0 architecture simply ran out of steam, so Motorola teamed up with IBM and Apple to produce a new microprocessor with improved performance. The MPC601, or PowerPC, is a 64-bit superscalar CPU that can effectively execute up to three instructions per clock cycle. The PowerPC is the first implementation of reduced instruction set computing (RISC) for personal computers. (The 680x0 and 80x86 families use complex instruction set computing (CISC) technology.) With RISC, most instructions execute in only one clock cycle. Instructions can even be completed out of order, but the CPU will make them appear sequential. The MPC601 has a 32-bit address bus, 32 kilobytes of cache memory, and an internal math coprocessor.

## MICROPROCESSOR GLOSSARY AND NOMENCLATURE

**Cache**—A small amount of high-speed memory that stores information for immediate use by the CPU. Primary cache may be built into the CPU itself, and additional (secondary) cache may be available as fast static RAM.

**CISC**—Complex instruction set computing: Typified by complex instruction sets and address modes, and relatively expensive silicon. Compare RISC.

**DLC**—Suffix used by Cyrix for its 486SX-compatible CPUs. Cyrix's 486DLC is pin-compatible with the Intel 386DX and has only 1 kilobyte of on-chip cache, versus 8 kilobytes on an Intel 486.

**DX**—Intel suffix indicating several different features. The 80386DX supports a full 32-bit data bus, and the 80486DX contains an 8-kilobyte cache and a math coprocessor. Advanced Micro Devices also uses the DX suffix. Compare SX, DX2.

**DX2**—Intel suffix indicating that the CPU runs internally at twice the bus speed. For example, a DX2/50 runs at 50 MHz internally, but the memory interface runs at 25 MHz. Compare SX, DX.

**DXLV**—Advanced Micro Devices suffix for a low-voltage 386DX.

**FPU**—Floating point unit, also called a math coprocessor. A specialized IC designed to perform floating-point math more efficiently than an ordinary CPU.

**MIPS**—Millions of instructions per sec-

ond, a relative measure of CPU performance. A higher value indicates a faster CPU.

**OverDrive**—Intel's trade name for its line of DX2 microprocessors.

**Pentium**—Intel's trade name for its fifth-generation microprocessor.

**Pipelining**—Design technique used to improve performance by allowing the processor to begin work on a subsequent instruction before completing the current instruction.

**Power management**—Circuitry that regulates the power consumption of a computer by effectively "turning off" power-hungry devices that are not being used.

**RISC**—Reduced instruction set computing: Typified by simple instruction sets and address modes, and relatively inexpensive silicon. Compare CISC.

**SL**—Intel suffix representing a low-power CPU (usually for mobile computers). The SL line has been canceled, and its features folded into more recent 486 and Pentium CPUs.

**SX**—Intel suffix with various meanings. Internally, the 80386SX supports a full 32-bit data bus, but externally, only 16 bits. The 80486DX allows the full bus width, but disables the internal math coprocessor. Compare DX, DX2.

**SXL**—Advanced Micro Devices suffix for a low-power SX CPU.

Apple appears to have bet its future hardware designs on the PowerPC architecture.

### MICROPROCESSOR VENDORS

**Cyrix**  
P.O. Box 853018  
Richardson, TX 75085  
(214) 994-8388

**IBM Microelectronics**  
Route 100  
Somerset, NY 10589

**Intel Corporation**  
2200 Mission College Blvd.  
P.O. Box 58119  
Santa Clara, CA 95052-8119  
(408) 987-8080

**Advanced Micro Devices**  
P.O. Box 3453  
Sunnyvale, CA 94088-3453  
(408) 732-2400

**NEC Electronics, Inc.**  
475 Ellis Street  
Mountain View, CA 94039  
(415) 960-6000

**Motorola**  
3102 No. 56th Street  
Phoenix, AZ 85018  
(602) 244-6900

### The clones

The huge microprocessor market has attracted other manufacturers who want to cash in. In the mid-1980's, NEC "cloned" the 8088 and 8086. More recently, American Micro Devices cloned Intel's 386 and 486 CPUs. AMD strategy was not to cut prices, but to improve performance. For example, when 33-MHz 386's dominated the market, AMD introduced its model running at 40 MHz. The company has continued that strategy.

More recently, several manufacturers, including AMD, Cyrix, and NexGen have jumped in to the fray, attempting to produce Pentium-class CPUs. None of these has been released yet, but several introductions are planned for this year. IBM has signed deals to manufacture CPUs for both Cyrix and NexGen, so it looks like choices are going to multiply rapidly. Ω

# SOLID STATE THERMOMETER


THE LIQUID-CRYSTAL display (LCD) and the single-chip analog-to-digital converter (ADC) have made possible an almost endless list of battery-powered, handheld test instruments. The most prominent of these are the digital multimeter (DMM) and the digital panel meter (DPM), but others include digital capacitance meters, thermometers, timers, sound-level meters, and light meters.

The single chip ADC eliminated a slew of discrete components and increased circuit reliability, while the LCD presents large characters that are easily seen in daylight. But of more importance in battery-powered instruments, both of these components are miserly in power consumption. This is especially important for battery conservation.

Within recent years the prices of single-chip ADC ICs and large-character LCDs have fallen, and they are now readily available as low-cost, off-the-shelf items from electronics stores and distributors.

The digital thermometer described here can be made from an available kit or the parts can be obtained from most electronics distributors. By building the thermometer, the builder will gain experience in working with advanced ICs and display modules, and at the same time gain insight into circuitry common to many different instruments.

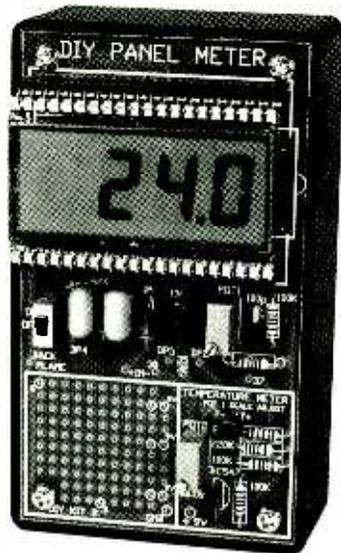The digital thermometer can make accurate, reliable, and repeatable temperature measurements in the laboratory or in the field over a wide range of temperatures. It will save money over the price of a factory-built instrument and, as a bonus, it provides circuit board space for



**Build an accurate, 3½-digit, handheld thermometer from a kit or from scratch.**

MARC SPIWAK

adding extra components for experiments.

The basic digital thermometer circuit displays temperature in degrees Celsius to an accuracy of a tenth of a degree on its 3½-digit LCD in half-inch high characters. The PC board can be purchased as part of the kit or made with the foil pattern included here. The electronic components are visible on the top surface of the instrument case, as shown in the illustration of the meter.

### How does it work?

Figure 1 is a schematic for the digital thermometer. The key semiconductor device in the circuit is IC1, an ICL7106CPL single-chip analog-to-digital converter from Harris Semiconductor. It is a 3½-digit ADC with a built-in LCD display driver, BCD to seven-segment de-

coders, clock and voltage reference. The ADC is packaged in a 40-pin plastic DIP. In the digital thermometer described in this article, IC1 will be set to display 200 millivolts full scale (199.9), plus or minus.

The temperature sensor for this digital thermometer is an NPN transistor modified to act like a silicon diode. The base of transistor Q1 is short-circuited to the collector, so it functions as a diode. However, it has a response curve that is more linear over a wider temperature range than a diode.

Transistor Q1 provides a variable input voltage to IC1. The voltage drop across the effective diode, typically about 0.7 volt, depends on the temperature of the diode's junction and the current flowing through it. The voltage drop is nearly linear, and will typically vary by 2.2 millivolts per degree Celsius.

A silicon diode has a negative temperature coefficient. Thus, in this application, as the temperature rises, voltage falls, and as the temperature falls the voltage rises. For example, if the ambient temperature rises by 2° Celsius, the voltage drop across the diode will decrease by about 4.4 millivolts. This linear voltage drop is measured to determine temperature.

The kit for the digital thermometer includes two transistors (Q1 and Q2) identified as BC-547s (but marked C547B). Pin identification is shown in Fig. 1. However, more readily available, industry-standard 2N2222 transistors can be substituted, although they have different pinout arrangements. Refer to the instructions given later if you want to make this substitution.

Trimmer potentiometers R9

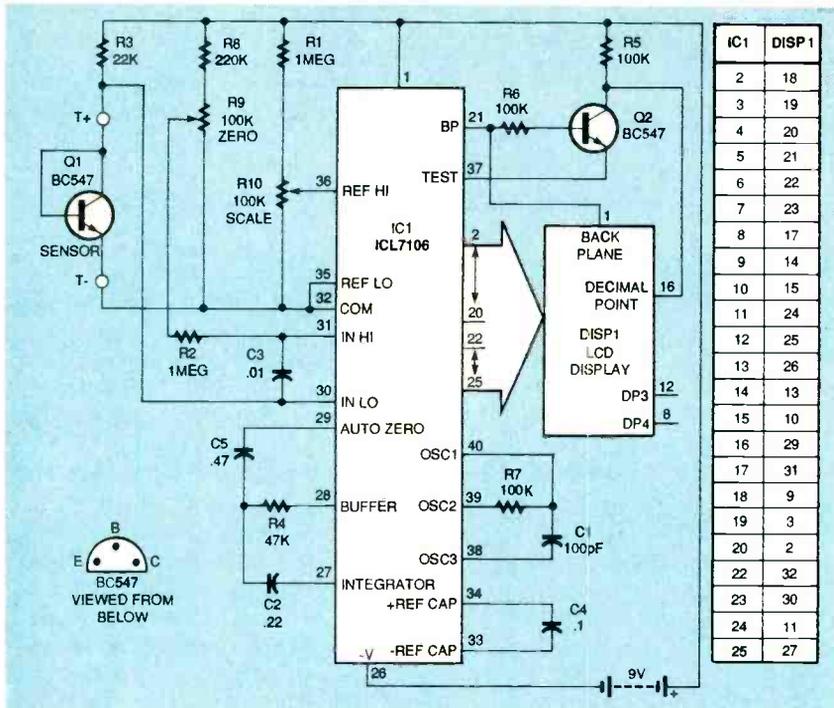


FIG. 1—SOLID-STATE THERMOMETER SCHEMATIC. The ICL7106 contains an analog-to-digital converter, BCD to 7-segment decoders, display drivers, a clock, and a reference voltage source.

and the display temperature must increment in degrees Celsius. The multiturn potentiometers permit precise settings.

Because IC1 can also indicate the polarity of the input voltage, the digital thermometer is theoretically capable of displaying temperature measurements from -200 to +200 degrees Celsius. However, the transistor used as a temperature sensor and its leads could be damaged by those temperature extremes.

The digital thermometer is effectively a solid-state voltmeter that could be adapted for making other measurements such as voltage, current, power, light level, and sound intensity, and more. If the output of the sensor for the variable you want to measure can be scaled between 0 and 200 millivolts, the circuit presented here can display that variable in appropriate standard units with little or no circuit modification.


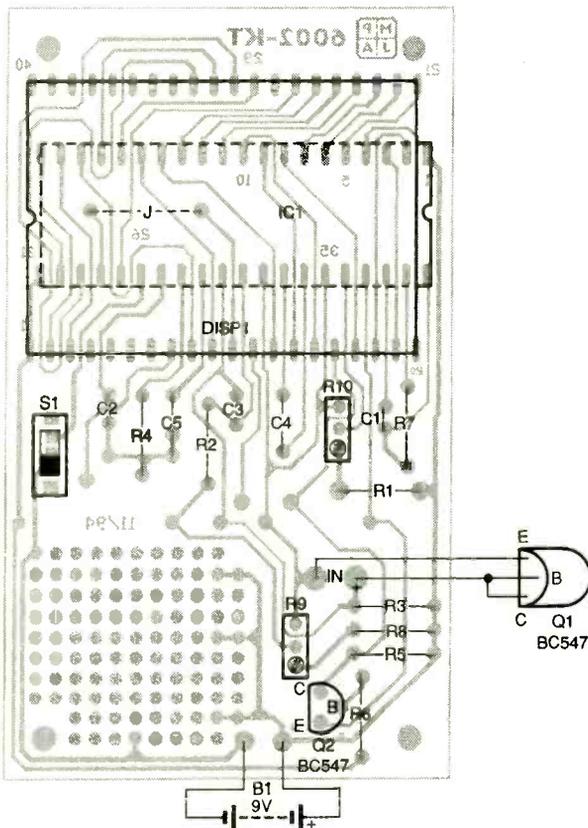


FIG. 2—PARTS-PLACEMENT DIAGRAM. IC1 is located beneath the liquid-crystal display module.

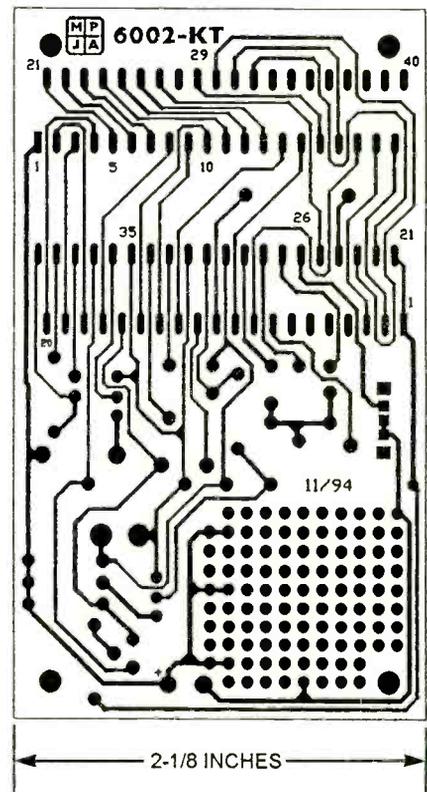

THERMOMETER FOIL PATTERN.

(ZERO control) and R10 (SCALE control) can be set to zero the meter and make scale adjust-

ments in the input voltage to IC1. A display of 00.0 must correspond to zero degrees Celsius

The PC board for this project contains a small space where additional components can be

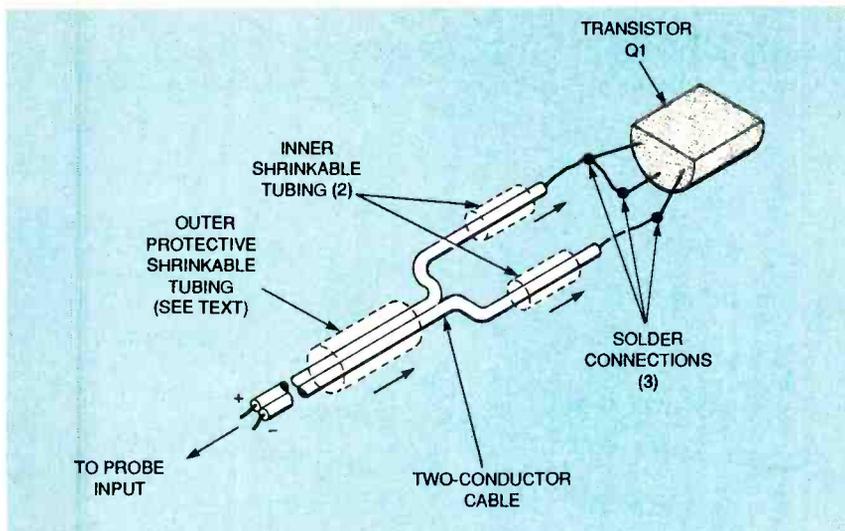


FIG. 3—THERMAL PROBE. The base and collector leads of transistor Q1 are bent together and soldered near the transistor's base and a two-conductor cable is attached.

### PARTS LIST

All resistors are 1/4-watt, 1%, unless otherwise noted.

- R1, R2—1 megohm
- R3—22,000 ohms
- R4—47,000 ohms
- R5—R7—100,000 ohms
- R8—220,000 ohms
- R9, R10—100,000 ohms, potentiometer 10-turn PCB

#### Capacitors

- C1—100 pF, polyester
- C2—0.22  $\mu$ F, polyester
- C3—0.01  $\mu$ F, polyester
- C4—0.1  $\mu$ F, polyester
- C5—0.47  $\mu$ F, polyester

#### Semiconductors

IC1—ICL7106CPL ADC, Harris or equiv.

Q1, Q2—BC547 NPN transistor (or 2N2222, see text and Fig. 5)

#### Other components

S1—slide switch, SPST, PCB-mount  
DISP1—VI-302-DP-RC LCD module, 3 1/2-digit, 40-pin package, Varitronix or equivalent)

**Miscellaneous:** PC board: three 40-pin IC sockets (see text); five machined pin sockets (optional); insulated hookup wire, 9-volt battery, battery clip with wires, project case with cover; miscellaneous hardware; solder.

**Note:** A kit for the digital thermometer (No. 6002-KT) can be purchased for \$29.95 plus \$4.00 for shipping and handling from Marlin P. Jones & Associates, Inc., P.O. Box 12685, Lake Park, FL 33403-0685, Phone: 407-848-8236, Fax: 407-844-8764. Florida residents please add local sales tax.

Figure 2 is the parts placement diagram for this meter. The circuit could be wired point-to-point, but that would call for a lot of wiring, especially in the display section. Consequently, the use of a PC board is recommended.

Insert all leaded components and sockets, and solder them in place on the solder side of the board. Insert resistor R1 and trimmer potentiometer R10 in individual machined pin sockets (two for R1 and three for R10) if you might want to replace those components with others having different values for different applications.

However, if you have no intention of experimenting with the finished meter, solder all resistors directly to the board. If you intend to substitute 2N2222 transistors, insert Q2 with its flat side opposite that shown in Fig. 2. More instructions on the substitution of 2N2222s will be given later.

Notice that analog-to-digital converter, IC1, is located under the LCD display, DISP1. When IC1 is installed, mount the LCD directly above it while orienting it to the opposite polarity (the notches are on opposite sides of the board). First install a socket for IC1. Then cut two 40-pin sockets apart along their long axes to provide four single in-line (SIP) sockets. Insert one SIP socket within another to form two double-height SIP sockets.

These will leave enough "headroom" for positioning IC1.

Solder the two double-deck SIP sockets to the board for DISP1, as shown in Fig. 2, and then install IC1. Then insert DISP1 in the double-height SIP sockets. This arrangement makes it easy to remove DISP1 by leaving the upper socket strips attached to the LCD and prying them away from the two lower socket strips that are soldered to the board. CAUTION: Do not attempt to remove the LCD from the upper sockets because the display pins can bend, and the glass body can break.

Cut a scrap of tinned lead wire to form jumper "J," insert and solder it. If you buy the digital thermometer kit, a case is included. The PC board fits securely in the top of the case to form a cover. Therefore, the inside the case provides enough space for the 9-volt battery. Solder the battery clip leads to the solder side of the board at the points shown in Fig. 2.

Refer to Fig. 3 and short-circuit Q1's base lead to its collector lead near the body of the transistor by bending them together and soldering them. Slip short lengths of heat shrinkable tubing over each input end of a two-conductor cable. Solder the two shorted transistor leads to the positive sensor input wire and

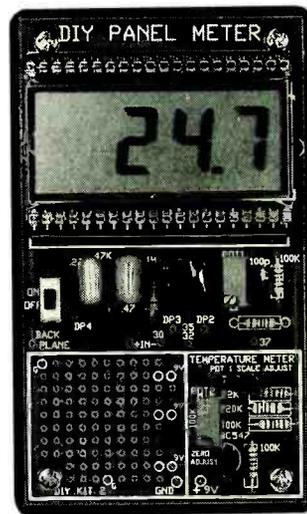


FIG. 4—THE TEMPERATURE-SENSING transistor can be located on the PC board, but leads must be attached for calibration.

located and powered to perform experiments and make other kinds of measurements.

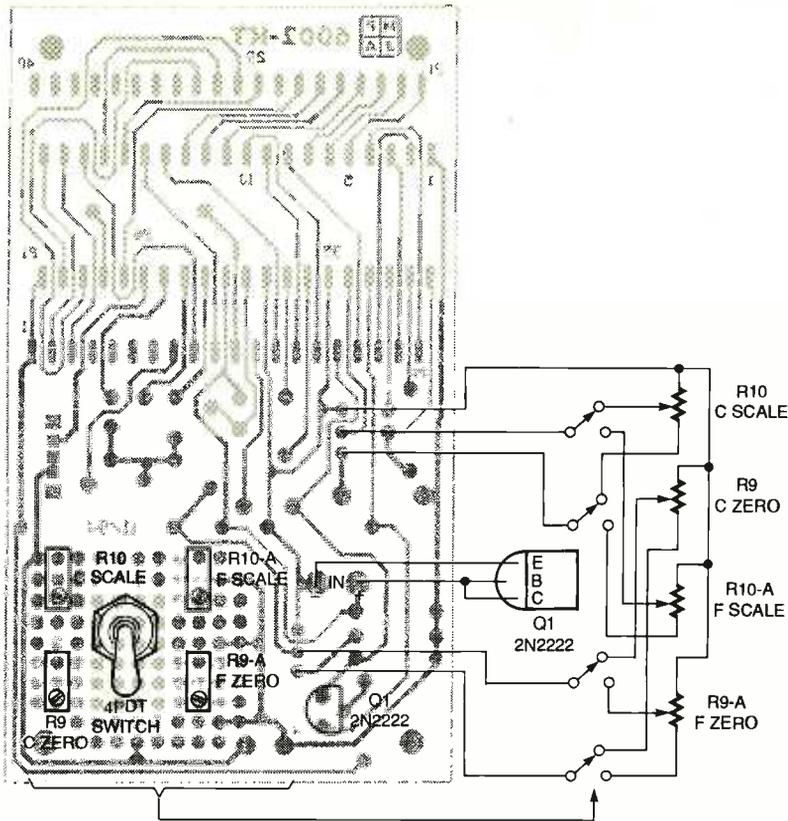


FIG. 5—THE CIRCUIT CAN BE MODIFIED as shown here to display part of the Fahrenheit scale in addition to the Celsius scale. Alternative 2N2222 transistors are installed as shown.

the emitter lead to the negative input wire.

Slip a short length of heat-shrinkable tubing on both leads and pull it over the end of the transistor to form an outer protective jacket, as shown in Fig. 3. Heat the tubing so that it forms a tight shrink fit around both the end of the transistor and the cable.

Standard insulated hookup wire leads are suitable for the temperature probe up to about 6 inches long. However, if the probe is to be mounted on leads longer than 6 inches, use thin shielded cable.

The temperature probe can also be mounted on the PC board directly with leads soldered to the "+" and "-" probe inputs. This arrangement will, however, make thermometer calibration more difficult. If you elect this option, temporarily attach the probe to the board with leads for calibration and mount it permanently to the board afterward. Figure 4 shows the completed digital thermometer.

well as Celsius degrees. Those modifications are shown in Fig. 5. The same figure also gives details for installing the alternative 2N2222 transistors, should you decide to substitute them.

Our tests showed that the meter's response is not perfectly linear for the Fahrenheit scale, and it is impossible to calibrate it at the boiling point of water because 212° cannot be displayed on the 3½-digit display. However, the response was linear enough for the display to give an accurate Fahrenheit reading from about 60 to 80°, the range in which most temperature readings are likely to be taken.

### Calibrating the meter

Carefully inspect the circuit board for soldering errors and correct them before proceeding. If the board passes visual inspection, connect a 9-volt battery to it and switch on power. The display will either indicate a "1" or some other reading. If the display shows a "1," adjust potentiometers R9 and R10 to obtain a reading other than a "1."

Fill a container with ice cubes and add a small amount of water. Turn on the digital thermometer and submerge its temperature probe in the ice water, holding it in close contact with an ice cube. Wait until the display stabilizes and then adjust ZERO control potentiometer R9 until the display reads 00.0.

Boil water in a kettle and carefully hold the probe over the kettle spout in the steam with tongs to prevent accidentally scalding yourself. When the display reading stabilizes, adjust SCALE control potentiometer R10 until the display reads 100. If you have access to a digital multimeter with a temperature probe that is known to be calibrated, compare readings and adjust trimmers R9 and R10 more precisely.

If you added the Fahrenheit potentiometers, as shown in Fig. 5, calibrate the Fahrenheit scale next, bearing in mind the limitations discussed earlier. It is recommended that the tem-

*Continued on page 53*

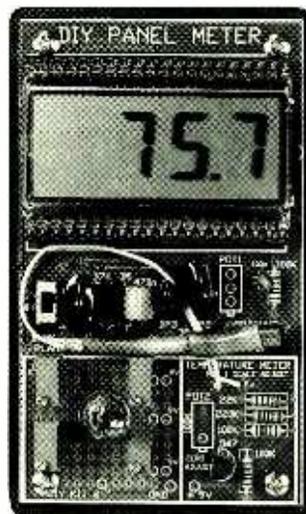


FIG. 6—MODIFIED THERMOMETER can display the full Celsius range and Fahrenheit from about 60° to about 80°.

### Modifying the meter

As mentioned earlier, a small area on the PC board is set aside to accommodate components for experiments. We added two more potentiometers and a 4PDT switch to the circuit so the digital thermometer could be calibrated in Fahrenheit as

BROADCASTING THE EXACT TIME OF day is just one of the many services provided by radio stations WWV and WWVH operated by the National Institute of Standards and Technology (NIST). Their ultra-accurate 10-megahertz carrier frequencies can be used to calibrate signal generators in a process called "zero beating" against the carrier frequency. The stations also transmit many other accurate frequencies, storm warnings for mariners at sea, and GPS (Global Positioning Satellite) position data.

This article explains how to build a simple, inexpensive superheterodyne radio receiver for WWV and WWVH signals. The objective in the design of this receiver was to obtain reliable reception with an antenna only 3- to 6-feet long. The sensitivity obtained with this receiver equals that obtainable from a \$1000 communications receiver operating from a 60-foot antenna.

Can the performance of a receiver made from \$30 worth of parts equal the performance of a \$1000 factory-built receiver? The answer is no because sensitivity is only one measure of receiver performance. The most significant difference between receivers is in their overall signal-to-noise ratios. However, the WWV/WWVH receiver described here has sufficient sensitivity to achieve its dedicated function.

This receiver economizes in the quality of its filters. Most factory-made communications receivers contain expensive precision crystal intermediate frequency (IF) filters which greatly improve the signal-to-noise ratio by screening out most of the noise in the radio-frequency spectrum. Moreover, those communications receivers also have superior intermodulation distortion (IMD) and dynamic range not required for WWV/WWVH reception.

#### WWV/WWVH transmissions

The WWV transmitter is located in Fort Collins, Colorado, and its signal can be identified by male voice announcements.

**Build this simple  
superheterodyne receiver  
to receive time and other  
useful signals from NIST's  
WWV and  
WWVH.**

# WWV RECEIVER

NEIL HECKT



TABLE 1—UTC TIME ZONE CONVERSION

UTC	Eastern	Central	Mountain	Pacific Alaska	Alaska Hawaii
0000	7:00PM	6:00PM	5:00PM	4:00PM	2:00PM
0100	8:00PM	7:00PM	6:00PM	5:00PM	3:00PM
0200	9:00PM	8:00PM	7:00PM	6:00PM	4:00PM
0300	10:00PM	9:00PM	8:00PM	7:00PM	5:00PM
0400	11:00PM	10:00PM	9:00PM	8:00PM	6:00PM
0500	Midnight	11:00PM	10:00PM	9:00PM	7:00PM
0600	1:00AM	Midnight	11:00PM	10:00PM	8:00PM
0700	2:00AM	1:00AM	Midnight	11:00PM	9:00PM
0800	3:00AM	2:00AM	1:00AM	Midnight	10:00PM
0900	4:00AM	3:00AM	2:00AM	1:00AM	11:00PM
1000	5:00AM	4:00AM	3:00AM	2:00AM	Midnight
1100	6:00AM	5:00AM	4:00AM	3:00AM	1:00AM
1200	7:00AM	6:00AM	5:00AM	4:00AM	2:00AM
1300	8:00AM	7:00AM	6:00AM	5:00AM	3:00AM
1400	9:00AM	8:00AM	7:00AM	6:00AM	4:00AM
1500	10:00AM	9:00AM	8:00AM	7:00AM	5:00AM
1600	11:00AM	10:00AM	9:00AM	8:00AM	6:00AM
1700	Noon	11:00AM	10:00AM	9:00AM	7:00AM
1800	1:00PM	Noon	11:00AM	10:00AM	8:00AM
1900	2:00PM	1:00PM	Noon	11:00AM	9:00AM
2000	3:00PM	2:00PM	1:00PM	Noon	10:00AM
2100	4:00PM	3:00PM	2:00PM	1:00PM	11:00AM
2200	5:00PM	4:00PM	3:00PM	2:00PM	Noon
2300	6:00PM	5:00PM	4:00PM	3:00PM	1:00PM

(add one hour during daylight savings time)

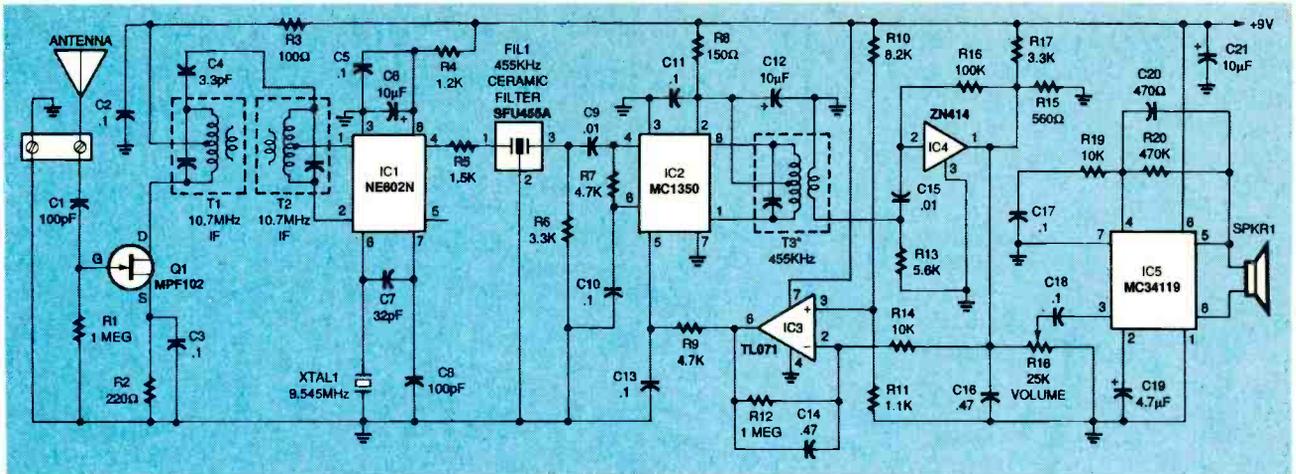


FIG. 1—SCHEMATIC OF THE WWV RECEIVER. A short antenna from three to six feet long is sufficient.

WWVH's transmitter is located in Kauai, Hawaii, and its signal can be identified by female voice announcements. Both stations broadcast on exactly the same frequencies, but they do not interfere with each other because their bands are so narrow they sound like a single station when both are received with equal signal strength.

Stations WWV and WWVH operate on a carrier frequency of 2.5 MHz. Station WWV broadcasts with 2.5 kilowatts (kW) of power, while WWVH broadcasts with 5 kW of power. Other frequency-power relationships are 5, 10, and 15 MHz at 10 kW and 20 and 25 MHz at 2.5 kW. The receiver described in this article was designed to receive 10-MHz signals because the author has found that they provide the most reliable reception.

Carrier frequency and all other time-related data is derived from cesium-controlled oscillators that are accurate to within  $\pm 1$  part in  $10^{11}$ . Daily deviations are less than one part in  $10^{12}$  from day-to-day. Phenomena such as Doppler and diurnal shifts can degrade the accuracy at the receiver, but long-term accuracy of one part in  $10^9$  can easily be obtained.

There are many different time zones around the world, so it would be impractical to broadcast time for each time zone. To simplify matters, WWV/WWVH transmit time data in *Coordinated Universal Time (UTC)*, also known as Greenwich Mean

Time (GMT), World Time and Zulu Time.

What is UTC? It is the time in England, uncorrected for daylight savings time, and it is always stated in a 24-hour format. It is called GMT because the zero or Greenwich meridian passes through England, west of London. Table 1 provides information that will permit you to determine the local time-of-day from the UTC announced by WWV and WWVH.


Refer to the sidebar for more

technical details on the WWV and WWVH transmission formats. More information on the services of WWV and WWVH can be obtained by writing Frequency-Time Broadcast Services Section, Time and Frequency Division, National Institute of Standards and Technology, Boulder, CO 80302.

### Circuit description

A schematic of the WWV receiver is shown in Fig. 5. A short antenna (three to six feet) represents a high-impedance source. Transistor Q1, a Motorola

### WWV and WWVH minute signals

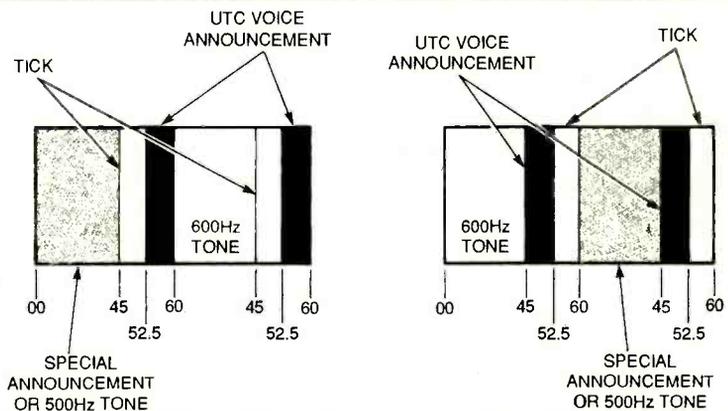

WWV and WWVH each have different one minute increments of time, as shown. Minute zero, and all even numbered minutes of WWV begin with a 45-second interval containing either a special announcement or a 500-Hz tone. This is followed by 7.5 seconds of silence except for the one-second tick.

The last 7.5 seconds contains the voice UTC time announcement. Minute 1, and all odd numbered minutes, have 45 seconds of a 600-Hz tone followed by

the 7.5 seconds of silence except for tick and the 7.5-second UTC time announcement.

WWVH broadcasts with a similar format except even and odd minutes are reversed, and the silent and UTC time announcement intervals are reversed. This prevents interference if both stations are received simultaneously (this occurs on the West Coast of the U.S.). The 45-second interval of each minute might contain variations.

MPF102 JFET, provides input impedance matching and some gain. A double-tuned input filter, consisting of T1, T2, and C4, provides adequate selectivity to attenuate the image frequency of 9.09 MHz.

A Philips NE602N mixer (IC1) contains a double-balanced mixer and oscillator which supplies approximately 14 dB of conversion gain. The oscillator section is crystal controlled to provide stability and eliminate the need for tuning. The output of the NE602N is coupled to a 455-kHz ceramic IF filter (FIL1) with about a 6-kHz bandwidth. The filter's 3000-ohm input and output impedance is matched by resistors R5 and R7. The output impedance of IC1 is 1500 ohms which, with R5, equals about 3000 ohms.

A Motorola MC1350P IF amplifier (IC2) provides about 60 dB of gain with about 80 dB of

automatic gain control (AGC) control range. The output is coupled through 455-kHz IF transformer T3. The output impedance of IC2 at 455 kHz is about 200 kilohms. Transformer T3 has a turns ratio of 6:1, and it provides an impedance transformation of 36:1.

Resistor R13 terminates the secondary of T3 with 5600 ohms, to provide the proper primary matching impedance. Other turns ratios can be used for T3 provided that R13 is also changed to maintain the proper impedance match. The input impedance of IC4 is high and it does not significantly affect the impedance match.

The GEC Plessey ZN414Z, an amplifier detector, is packaged in a typical plastic transistor case, but it is actually a ten-transistor IC which provides about 70 dB of gain, detection and some AGC response. It is

## PARTS LIST

All resistors are 1/2-watt, 5%, unless otherwise noted.

R1, R12—1 megohm  
R2—220 ohms  
R3—100 ohms  
R4—1200 ohms  
R5—1500 ohms  
R6, R17—3300 ohms  
R7, R9—4700 ohms  
R8—150 ohms  
R10—8200 ohms  
R11—1100 ohms  
R13—5600 ohms  
R14, R19—10,000 ohms  
R15—560 ohms  
R16—100,000 ohms  
R18—25,000 ohms, potentiometer  
PCB-mount  
R20—470,000 ohms

### Capacitors

C1, C8—100 pF, ceramic  
C2, C3, C5, C10, C11, C13, C17, C18—0.1 μF, ceramic  
C4—3.3 pF, ceramic  
C6, C12, C21—10 μF, 10 volts, aluminum electrolytic  
C7—33 pF, ceramic  
C9, C15—0.01 μF, ceramic  
C14, C16—0.47 μF, ceramic  
C19—4.7 μF, 10 volts, aluminum electrolytic  
C20—470 pF, ceramic

### Semiconductors

IC1—NE602AN mixer, Philips or equiv.  
IC2—MC1350P IF amplifier, Motorola or equiv.  
IC3—TL071 operational amplifier, Texas Instruments or equiv.  
IC4—ZN414Z amplifier/detector (GEC Plessey)

IC5—MC34119P power amplifier, Motorola or equiv.

Q1—MPF102 JFET, Motorola or equiv.

### Other components

FIL1—455-kHz ceramic filter, SFU455A or equiv.

T1, T2—10.7-MHz IF transformer (Toko or equivalent)

T3—455-kHz IF transformer, 6:1 ratio (Toko or equivalent)

XTAL1—9.545-MHz crystal

SPKR1—speaker, square, 2.5-inch, 8-ohms

S1—SPDT switch, PCB mount

Miscellaneous: 5.3 × 4 × 2-inch plastic project case, PC board, 9-volt battery, battery clip, hookup wire, solder.

**Note:** The following items are available from Almost All Digital Electronics, 1412 Elm Street S.E., Auburn, WA 98092:

● Complete kit—\$36.95 + \$4.00 S&H

● Partial kit (includes all electronic components, PC board, and crystal—does not include project case, speaker, or antenna)—\$24.95 + \$4.00 S&H

● PC board and crystal, only—\$10.00 + \$2.90 S&H


● Case and speaker, only—\$10.00 + \$2.90 S&H

● Antenna—\$3.00 + \$2.90 S&H

● Fully assembled unit—\$45.95 + \$4.00 S&H


Send check or money order. Washington State residents add local sales tax.

## WWV hour signals

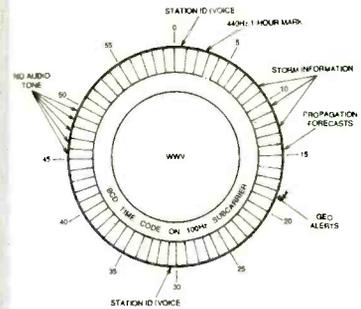

The figure shows how the WWV hour is divided. The beginning of each hour is identified by a 0.8-second, 1500-Hz tone. The beginning of each minute is identified by a 0.8 second, 1200-Hz tone. The 29th and 59th second pulse of each minute is omitted.

## WWVH hour signals

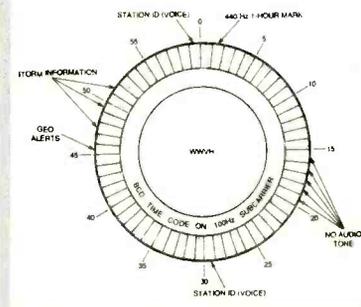


The figure illustrates how the WWVH hour is divided. The beginning of each hour is identified by a 0.8-second, 1500-Hz tone. The beginning of each minute is identified by a 0.8-second, 1200-Hz tone. The 29th and 59th second pulse of each minute is omitted.

WWV and WWVH broadcasts are approximate mirror images of each other. This prevents the two stations from creating interference mutual interference during voice announcements.

designed to be powered from a 1.5-volt DC power supply with a 500-ohm load. This is emulated by resistors R15 and R17 whose equivalent circuit is 1.5-volts DC flowing through 500 ohms. The DC level at the output of IC4 is about 1.1-volts DC with no signal, and 0.9-volt DC with a strong signal.

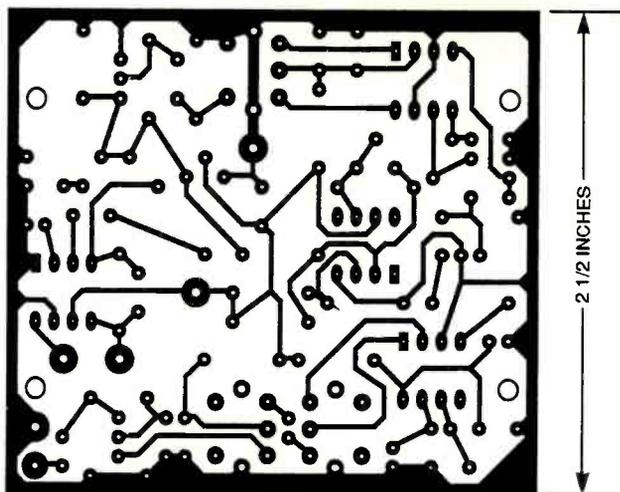The output signal is amplified, inverted, and filtered by IC3. Capacitor C14 removes any audio from the signal before it is applied to the gain control input



WWV RECEIVER FOIL PATTERN.

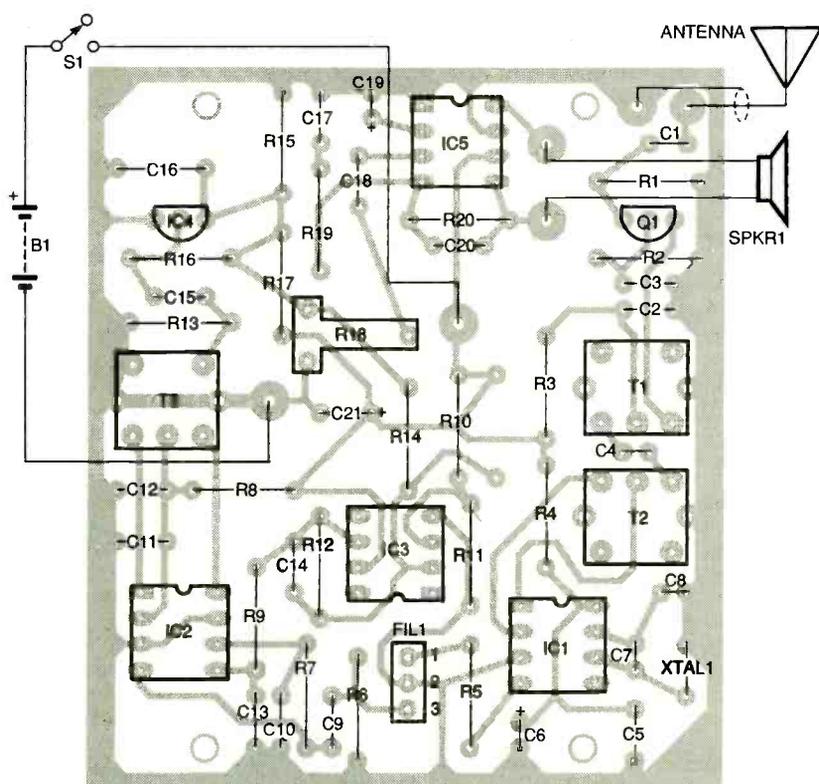


FIG. 2—PARTS-PLACEMENT DIAGRAM. The volume control is mounted on the PC board and adjusted before closing up the case.

pin 5 of the Motorola MC1350P IF amplifier (IC2). When the voltage at the output of IC4 exceeds the 1-volt DC reference level set by R10 and R11, the gain of IC2 starts to roll off. As a result, the AGC response of IC2 and IC3 tries to maintain the signal level so that the DC level at the output of IC4 is 1-volt DC.

The gain of the Motorola MC34119P audio amplifier (IC5) is set by the ratio of R20 to R19, which equals 47 (about 16 dB).

This audio amplifier was selected because it is a bridge amplifier and does not require a large coupling capacitor to drive the speaker.

The overall maximum gain of the receiver is about 144 dB. This is the sum of a -10 dB in the input filter, +14 dB from IC1, -6 dB in FIL1, +60 dB from IC2, +70 dB from IC3, and +16 dB from IC4. Ordinarily a gain of 144 dB is too much. Normal operation can be expected

to be with about a 120 dB maximum gain, which is typical of a high-quality communications receiver. However, the gain is usually less than that, as set by the volume-control potentiometer R18 and AGC loop.

### Building the receiver

You can build the receiver on a single-sided PC board that you make yourself from the foil pattern provided here. Alternatively, partial and complete kits containing a finished PC board, as well as complete receivers, are available from the source given in the Parts List.

Figure 6 is a parts-placement diagram. The order of assembling the components to the circuit board and soldering them is not critical. Pay particular attention to the orientation of the semiconductors, that is the location of pin 1. Mount the volume control on the PC board. Keep in mind that it cannot be adjusted after it is installed in the case.


The author designed the circuit assuming that the receiver would be turned on only for brief periods to obtain the correct time, and that convenient access to the volume control would not be necessary. However, if you want an external volume control, one can be mounted on the case and wired directly to the pads intended for the PCB-mounted control.

After all the electronic components are inserted and soldered to the circuit board, wire the speaker, battery clip, power switch, and antenna. Install the completed circuit board in the case as shown in Fig. 7. Install a 9-volt battery.

### Circuit alignment

To align the circuit, adjust transformers T1, T2, and T3 for peak AGC voltage at pin 6 of IC3. The desired tuning is broad for receiving a strong signal. Attach an antenna that is as short as practical to pick up an extremely weak signal for the alignment procedure. Even with those precautions, the tuning range of the IF transformers will appear to be quite broad.

## Dividing Up Time For Broadcast

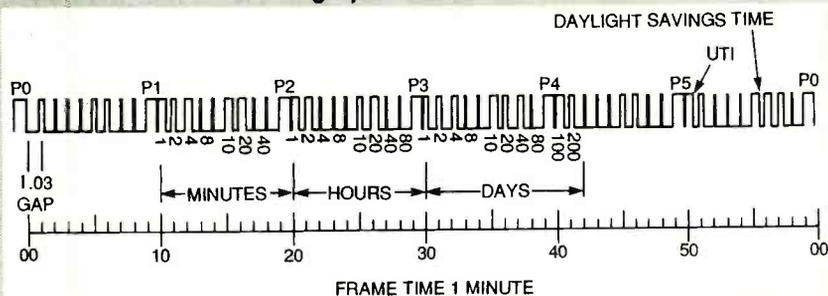

The figure illustrates the pulse format for the BCD time code (100-Hz subcarrier). During the passage of a minute, both stations broadcast the time of year on a pulse-width modulated 100-Hz subcarrier. Three different pulse widths are used:

1. P0-P5—position identifiers—0.8 seconds (80 cycles)
2. Logic 1—data bit—0.5 seconds (50 cycles)
3. Logic 0—data bit—0.2 seconds (20 cycles)

In addition there is a 1.03 second (103 cycles) "hole" in the code for synchronization at the beginning of each minute signal. The minute is divided into six parts of 10 seconds duration. Each part consists of nine data bits and a position identifier pulse. The following listing is the contents of the various sections.

- 1.—Synchronization "hole" and eight

logic zeros.

- 2.—Four data bits encoding the unit minutes in binary-coded decimal (BCD), a logic 0, three data bits encoding the tens of minutes in BCD and another logic 0.
- 3.—Four data bits encoding the unit hours in BCD, a logic 0, and two data bits encoding the tens of hours in BCD and two logic 0's.
- 4.—Four data bits encoding the unit days in BCD, a logic 0, and four data bits encoding the tens of days in BCD.
- 5.—Two data bits encoding the hundreds of days in BCD and seven logic 0's.
- 6.—One data bit if UT1 correction should be applied, four logic 0's, a data bit which is logic 1 if daylight saving time and three data bits with the UT1 correction in tenths of a second. The UT1 correction accounts for the Earth's rotation which varies slightly over time.

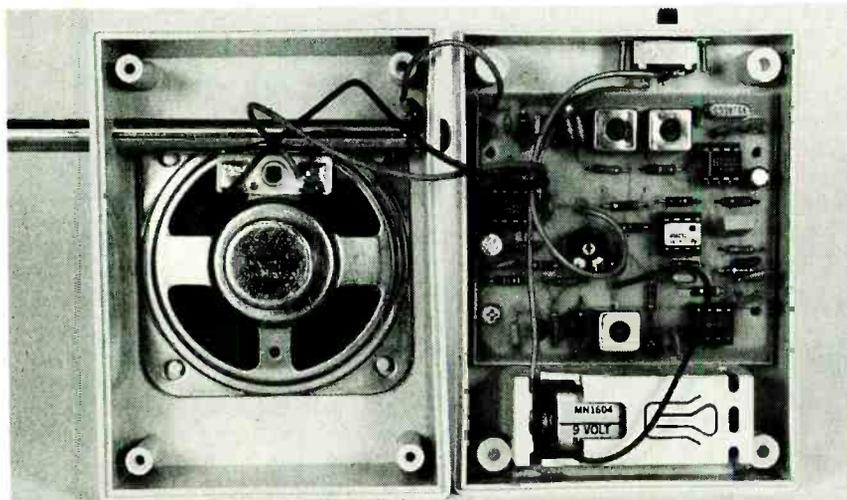


FIG. 3—THE FINAL ASSEMBLY consists of wiring the speaker, battery clip, power switch, and antenna. The author's prototype is shown here.

As an alternative to "on-air tuning," set up a 10-megahertz signal source. It will make the task of circuit alignment easier by providing a constant, local, easy to control signal. The author set a frequency counter at 10-megahertz and its internal oscillator provided sufficient ambient signal leakage to act as an excellent signal source for

alignment.

The most difficult step is the alignment of the double-tuned input filter, T1/T2. To overcome that obstacle, all of the transformers that are supplied with the kit from the source listed in the Parts List are pre-aligned. Only slight adjustments are then necessary for the transformers after assembly.

## Antenna considerations

The author lives near Seattle, Washington—about 1000 miles from Fort Collins, Colorado. Moreover, there are several mountain ranges between Seattle and Fort Collins. The quality of reception is usually excellent during the day with an antenna consisting of a 3- to 6-foot length of wire. When the signal is particularly strong, no antenna is needed.

The prototype receiver shown in the photographs has a 30-inch telescopic rod antenna that works quite well, but this a convenience feature rather than a requirement. There are two pads on the board for the connecting the antenna: one is connected to the antenna and the other is the ground connection. While a single wire on the antenna terminal usually works well, reception can generally be improved with a simple dipole antenna formed by a second wire connected to ground.  $\Omega$

## THERMOMETER

*continued from page 48*

perature of ice water (32°F) and 80°F water be the test points.

The temperature of the hot water can be determined accurately with a standard laboratory mercury thermometer, but a high-quality, liquid-filled confectioner's thermometer will also give satisfactory results.

## Measuring temperature

Observe common sense precautions when measuring temperature with your digital thermometer. If the transistor/sensor is held near an open flame or heating coil it will be damaged or destroyed.

If you put the digital thermometer in a protective case to protect it from dust, rain, and salt spray, it will work reliably out of doors, in boats, or even on camping trips.

Keep the digital thermometer's temperature measurement limits in mind. The Harris ICL7106CPL has a rated temperature range of 0 and 70° Celsius.  $\Omega$

ONE OF THE MOST GRATIFYING BENEFITS of being an electronics hobbyist is the opportunity to design and build custom projects for a particular need or purpose. The incredible number of new integrated circuits that are

# PROTOTYPING STATION

**Build this full-featured breadboard laboratory, and add custom features to suit your own needs.**

introduced each year provides building blocks for circuits and fertile ground for experimentation in electronics.

One requirement for successful prototyping and experimentation is a quick, convenient way to connect and disconnect components. Solderless breadboards are a good start, but all too often one is likely to end up with the board in the center surrounded by a maze of wires that connect switches, potentiometers, meters, power supplies, and any number of other components that dangle in all directions. The arrangement of components can be both frustrating and irritating. The solution is to combine the breadboard, power supply, and other commonly used parts into a self-contained unit.

Factory-made laboratories like that are available, but they

can be quite expensive. The lab described in this article, however, combines economy, expansion, and easy customization—you can use many of the parts you might already have on hand in your junkbox.

## Design

The prototyping station base consists of a 20-inch length of 1-by 12-inch pine board that is sanded, stained and finished. The various power supplies are located to the right; the center section is reserved for three breadboards and the main equipment backboard. The left side is left open to accommodate additional modular backboards, or any other peripherals such as keypads or data-entry terminals. The base can be raised to make room for plastic drawers, power transformers, or other equipment. Rubber feet can be used to ensure

that the lab is stable on the bench. That basic layout is shown in Fig. 1.

## Power supplies

Since the availability of power is always a requirement for successful prototyping, a variety of different power sources is incorporated on the right-hand section of the station (Fig. 2 shows a close-up view of the power section). The first power supply on the upper left is a surplus Texas Instruments computer board, bought at a clearance sale for \$5. With the addition of an LED indicator, it provides a good clean source of  $\pm 5$  volts and +12 volts. Being a computer-grade supply, the outputs are well-regulated, well-filtered, and can output about 1 ampere each. Power for this supply comes from an off-board wall-outlet transformer, and it is input to the supply via a two-position pushbutton terminal (the kind you might see on the back of a speaker).

Since a standard dry cell is appropriate to power many circuits, the second supply shown on the upper right of Fig. 2 consists of four AA cells and one 9-volt battery. The case from an old nickel-cadmium battery charger holds the AA cells, and a rotary switch and power indicator were added. The battery holder is tapped at each of the four positive battery pads, and each pad is wired to one pole of the rotary switch. The 9-volt battery is wired to a fifth pole on the rotary switch. This allows the selection of 1.5, 3, 4.5, or 6 volts DC from the AA pack, and 9 volts from the 9-volt battery. The LED indicator is a 0.3-inch


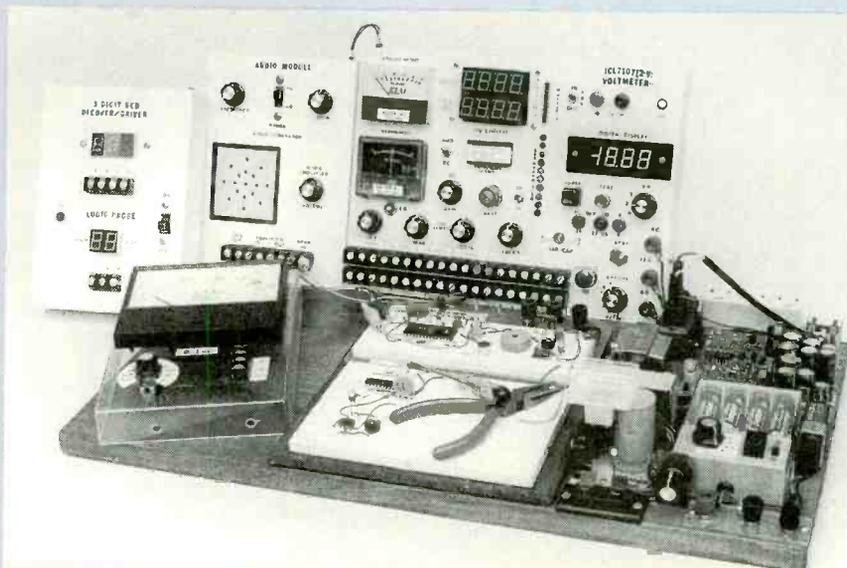


FIG. 1—BASIC PROTOTYPING LAYOUT. The base can be raised to make room for plastic drawers, power transformers, or other equipment.

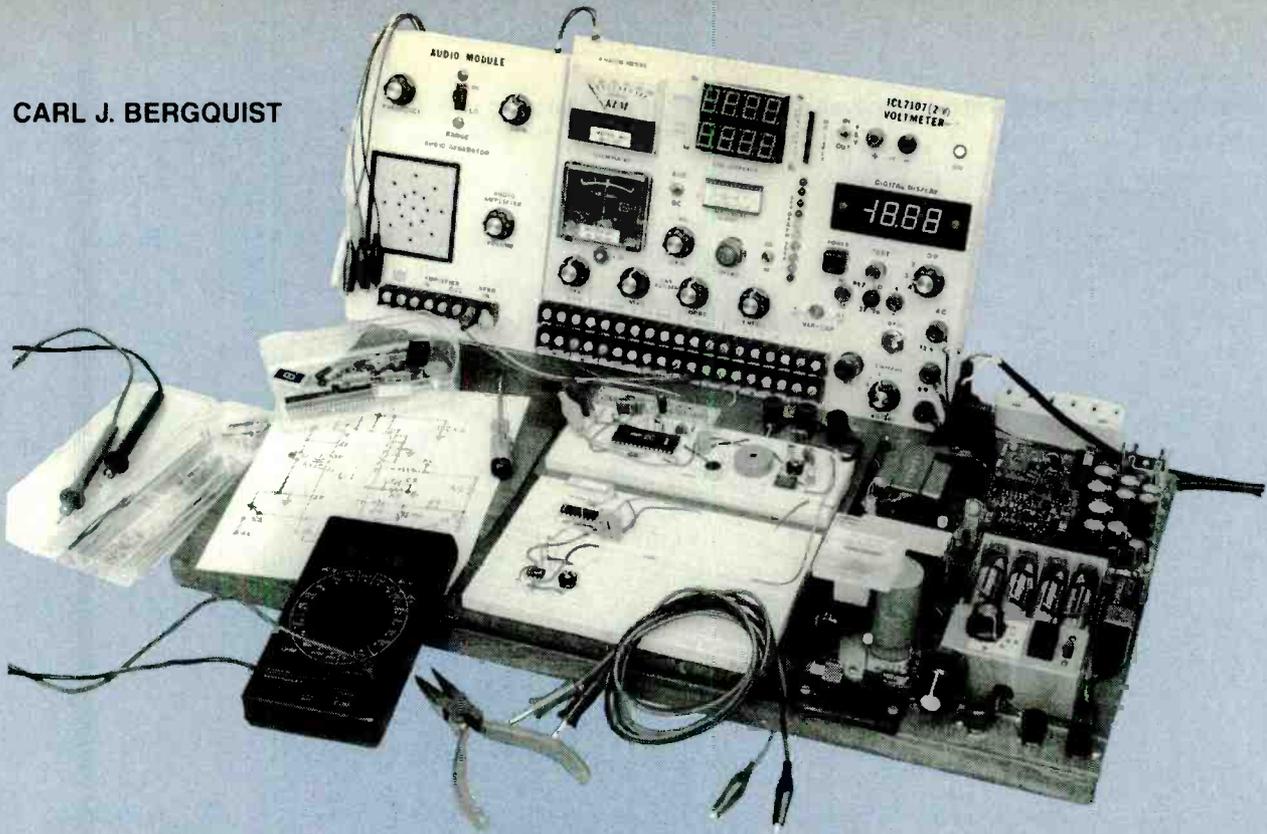

high, seven-segment display, with all segments turned on to form an "8," which is a more noticeable reminder of the "on" status of the battery pack than a single LED. The output from this supply is connected to two of three binding posts for easy access. The third binding post is the negative 5-volt supply from the TI computer supply.

Another voltage source is provided by a +1.2- to 20-volt DC variable power supply that was built from a kit some years ago.

The potentiometer next to the battery pack allows for adjustment of the output voltage, which is available at another two-position pushbutton terminal. An analog meter indicates the voltage at the pushbutton terminals.

Next to the variable supply is a 12.6-volt, center-tapped transformer, complete with a switch and indicator LED, that provides 6- and 12-volts AC. An

SPST slide switch is connected to one side of the 120-volt AC input to the transformer primary. The outputs are wired to multipurpose posts on the main backboard.

AC power is made available at a triple-outlet AC strip, which gets its power via a heavy-duty line cord. The power inputs for the AC and variable supplies are also connected to this line cord.

The five separate power supplies can be customized to suit your needs. If you decide to enclose the power supplies, be sure to provide for adequate ventilation to allow heat to escape. The main 120-volt AC input should be protected against surges and spikes if you anticipate prototyping computer circuits.

### Breadboards

In the center of the base board are three 640-point solderless breadboards, laid out side-by-side (see Fig. 3). The top breadboard is a Radio Shack unit on a metal base with three multipurpose posts. The other two breadboards are plug-in panels mounted on a plywood base. All three breadboards have dual two-connection bus lines at their tops and bottoms, and will accommodate SIPs, DIPs, dis-



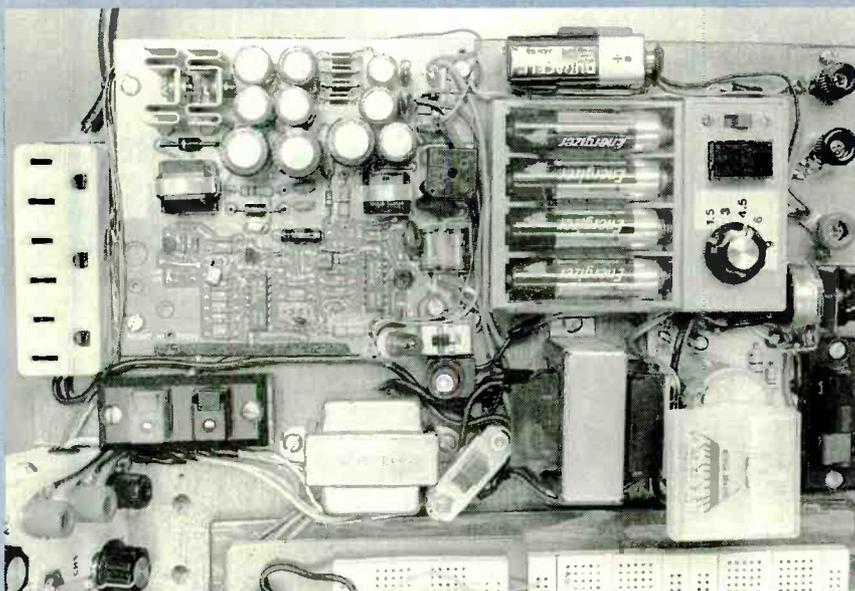



FIG. 2—A VARIETY OF POWER SOURCES is incorporated into the lab.

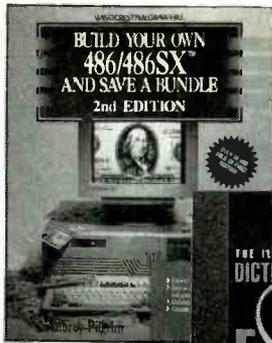


4270H \$29.95  
Hardcover

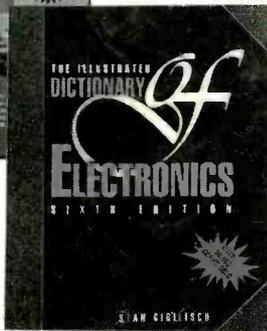

3621H-XX \$39.95  
Hardcover/Counts as 2

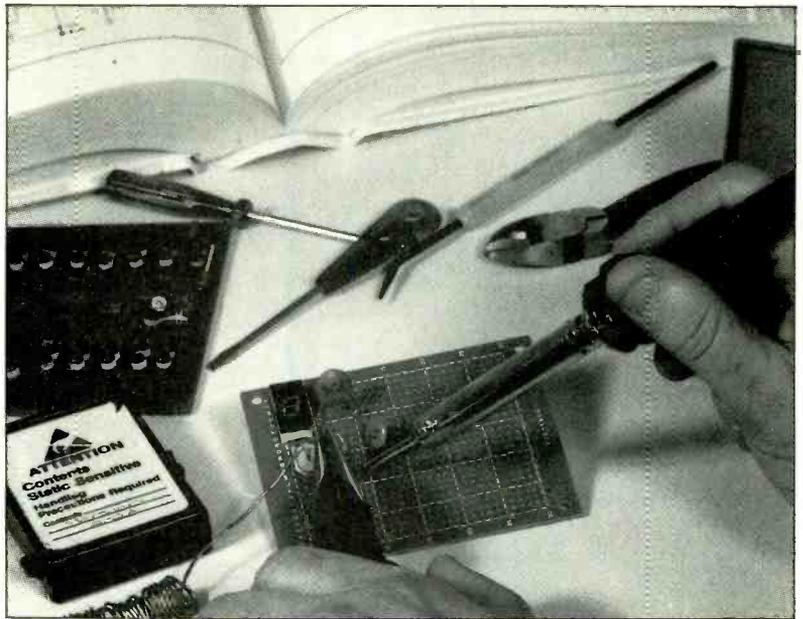


3671P \$18.95

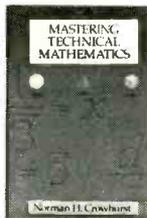


3438P \$24.95




0156778 \$44.95  
Hardcover

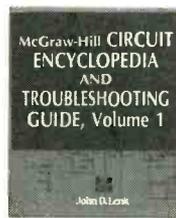

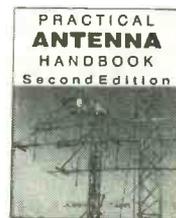
037603-XX \$59.50  
Counts as 2/Hardcover



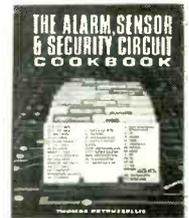
0111049-XX \$49.95  
Counts as 2/Hardcover



4334H \$29.95  
Hardcover

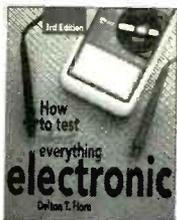


4227P \$15.95

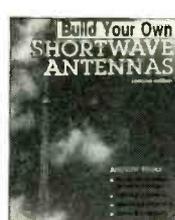


0765340 \$16.95



3279P \$26.95

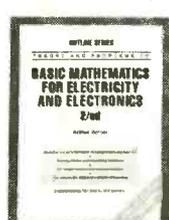

0044392 \$12.95

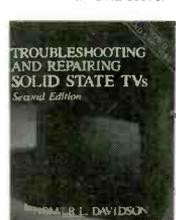

3700H-XX \$36.95  
Hardcover/Counts as 2



3258P \$19.95




4394H \$35.00  
Hardcover



3765P \$19.95




0039615 \$40.00  
Hardcover

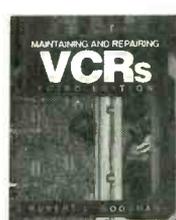


4204H-XX \$39.95  
Hardcover/Counts as 2




3887H \$26.95  
Hardcover

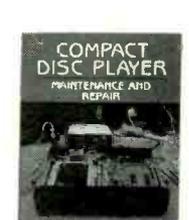


2790P \$17.95

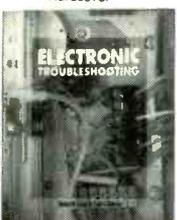

4360H-XX \$34.95  
Hardcover/Counts as 2

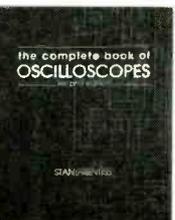


3825P \$17.95

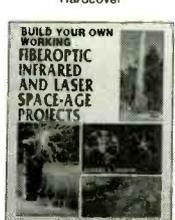


2724P \$17.95



4362P \$16.95

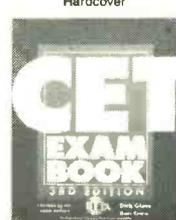


4199H \$29.95  
Hardcover

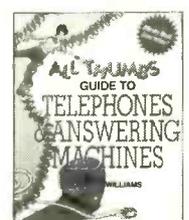


4416P \$9.95
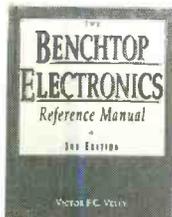
# Select any 5 books for only \$4<sup>95</sup>


when you join the **ELECTRONICS BOOK CLUB**® (values up to \$194.85)



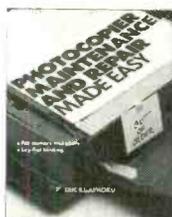0673764-XX \$54.95  
Hardcover/Counts as 2



4326P \$14.95

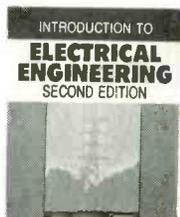


011322X-XX \$49.16  
Counts as 2




2613P \$19.95



3711P \$19.95

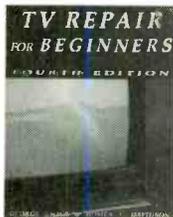


3627P \$19.95

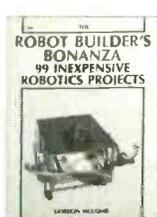


2800P \$17.95




0156697 \$44.95  
Hardcover

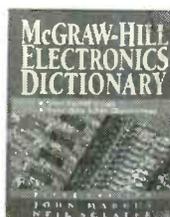

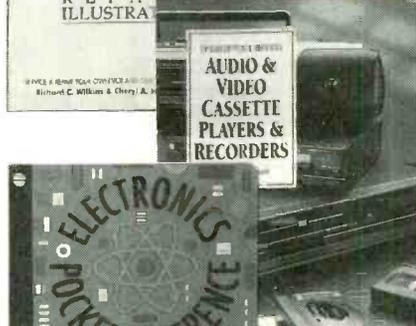
0404348-XX \$49.50  
Hardcover/Counts as 2




3795P \$19.95

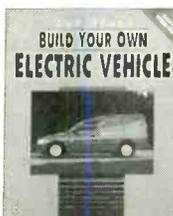


4283H \$26.95  
Hardcover

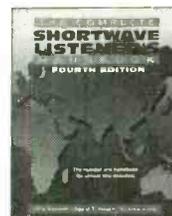


4354P \$19.95

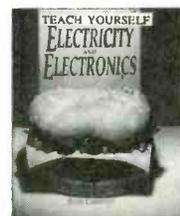

4230H-XX \$39.95  
Counts as 2/Hardcover

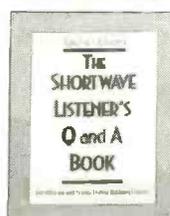

0447748 \$12.95

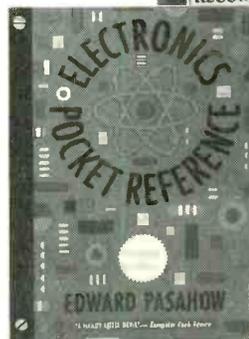

0487375 \$24.95

If coupon is missing, write to: Electronics Book Club, A Division of McGraw-Hill, Inc., Blue Ridge Summit, PA 17214-9975

## As a member of the Electronics Book Club...

... you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off of regular publishers' prices. If you want the Main Selection do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. And you'll be eligible for **FREE BOOKS** through our Bonus Book Program. If you ever receive a book you don't want due to late delivery of the News, you can return it at our expense. Ironclad guarantee: if you are not completely satisfied, return it for a refund. Your only obligation is to purchase 3 more books during the next 12 months, after which you may cancel your membership at any time.

A shipping/handling charge and sales tax will be added to all orders. All books are softcover unless otherwise noted.

If you select a book that counts as 2 choices, write the book number in one box and XX in the next. (Publishers' Prices Shown) ©1995 EBC

**Your most complete and comprehensive source for the finest electronics books**

## ELECTRONICS BOOK CLUB®

A Division of McGraw-Hill, Inc., Blue Ridge Summit, PA 17214-9975

**YES!** Send the 5 books listed below, billing me just \$4.95 plus shipping/handling & tax. Enroll me as a member of the **Electronics Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books within ten days and have my membership cancelled. A shipping/handling charge and sales tax will be added to all orders.

--	--	--	--

If you select a book that counts as 2 choices, write the book number in one box and XX in the next.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_ Phone \_\_\_\_\_

Valid for new members only, subject to acceptance by EBC. Canada *must* remit in U.S. funds drawn on U.S. banks. Applicants outside the U.S. and Canada will receive special ordering instructions.

RE395

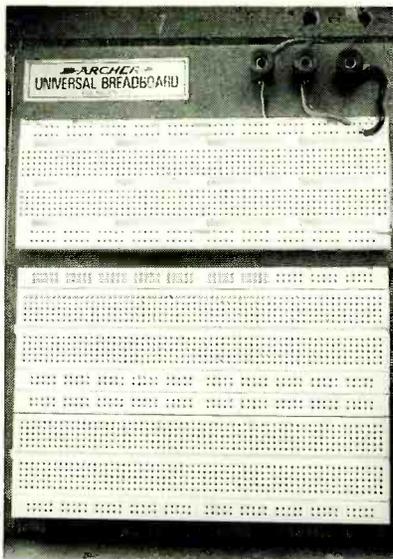


FIG. 3—THREE 640-POINT breadboards are laid out side-by-side. The top breadboard is on a metal base with three multipurpose posts, and the other two are plug-in panels mounted on a plywood base.

crete components, and jumper wires. While this breadboard arrangement has provided the author with enough space and has been versatile enough for all of his projects to date, it is certainly not the only arrangement possible. The breadboards are available in a variety of shapes and sizes, with from 250 contact points to 2500 or more. Some thought about the types of circuits you'll be working on will help you make a final decision on this part of the lab.

### Backboards and modules

The main function of the backboard is to support more cumbersome components, modules, and any other circuits that the builder wants to add—items such as switches, potentiometers, meters, displays. The main backboard occupies

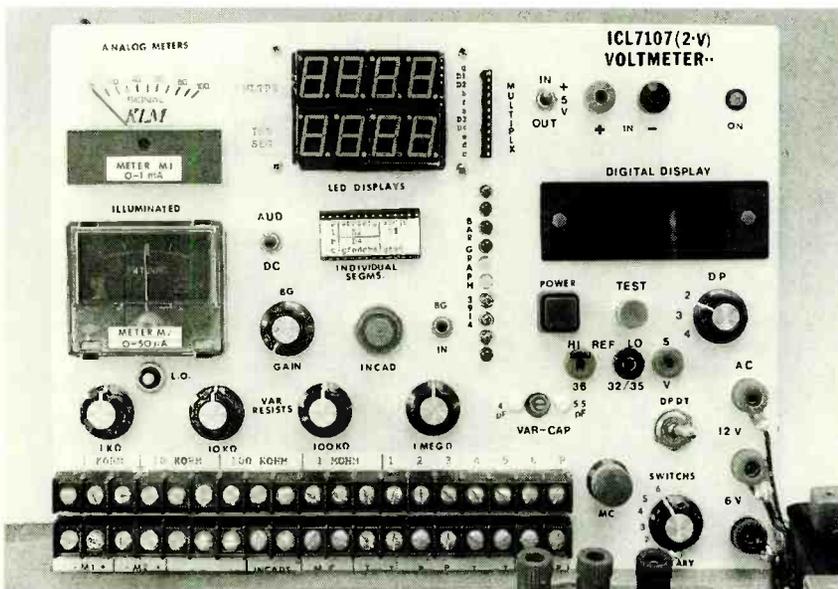


FIG. 4—THE MAIN BACKBOARD occupies about 10 inches across the back edge of the base. The backboard holds many of the accessories.

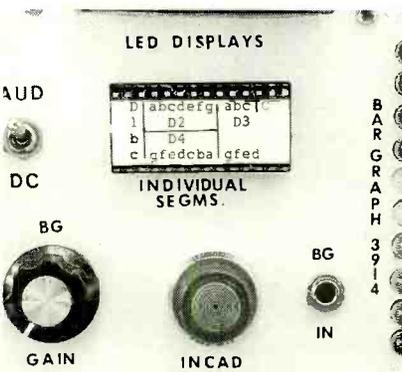


FIG. 5—A BARGRAPH is mounted in the center of the backboard.

about 10 inches across the back edge of the base (see Fig. 4).

Two 19-position terminal strips provide access to the parts mounted on the backboard. The strips on the prototype were removed from a surplus alarm board. The screw terminals allow connections to be made with alligator clips, bare wire, and spade lugs. However, spring-loaded terminals, SIP sockets, or any other connector you might have on hand can be used here. Each point on the terminal strips is wired to a

### PARTS LIST—MAIN UNIT

#### Resistors

- 1K panel-mount potentiometer
- 10K panel-mount potentiometer
- 100K panel-mount potentiometer
- 1 megohm panel-mount potentiometer

#### Capacitors

- 4 to 55 pF variable capacitor

#### Semiconductors

- One 0.3-inch 7-segment display, common anode
- Four 0.56-inch 7-segment displays, common anode
- Four 0.56-inch 7-segment displays, common cathode

#### Power supplies

- Texas Instrument surplus computer power supply, or equivalent
- 12.6-volt AC transformer
- 4-AA battery holder
- 9-volt battery connector
- 1.2 to 20 volt variable DC supply
- 120 VAC power strip

#### Other components

- Two spring-loaded speaker-type terminals, six binding posts, 6-foot AC line-cord, plastic project cases, three 640-point breadboards, two 19-point terminal strips, heavy-duty DPDT toggle switch, momentary pushbutton switch, 6-position rotary switch, 0 to 1 mA analog meter movement, small push-on push-off switch, 11-pin SIP socket, 28-pin DIP socket, bayonet lamp socket with lens and bulb assortment, hookup wire and zip cord, hardware, seven panel knobs, TO-220 10-watt heatsink, 4-contact tie point.

### PARTS LIST—BARGRAPH

- IC1—LM3914 bargraph driver and 18-pin DIP socket, National Semiconductor
- R1—1000 ohms, ¼-watt resistor
- R2—5000 ohms, panel-mount potentiometer with switch
- T1—audio transformer, 1K primary, 8-ohm secondary (Radio Shack 273-1380)
- J1—½-inch phono jack and plug
- D1—1N4001 diode
- LED1-LED10—light-emitting diode, any color
- S1—DPDT switch

connection on the component, and labeled for identification.

The row of components above the terminal strips consists of four potentiometers (1-, 10-, and 100-kilohms and 1 megohm) and a 4- to 55-pF variable capacitor. To the right of that row is a DPDT toggle switch and six-position rotary switch. The binding posts on the extreme right output the 6- and 12-volts AC, previously mentioned.

On the left side are two analog meters (M1 and M2). Meter M1 is

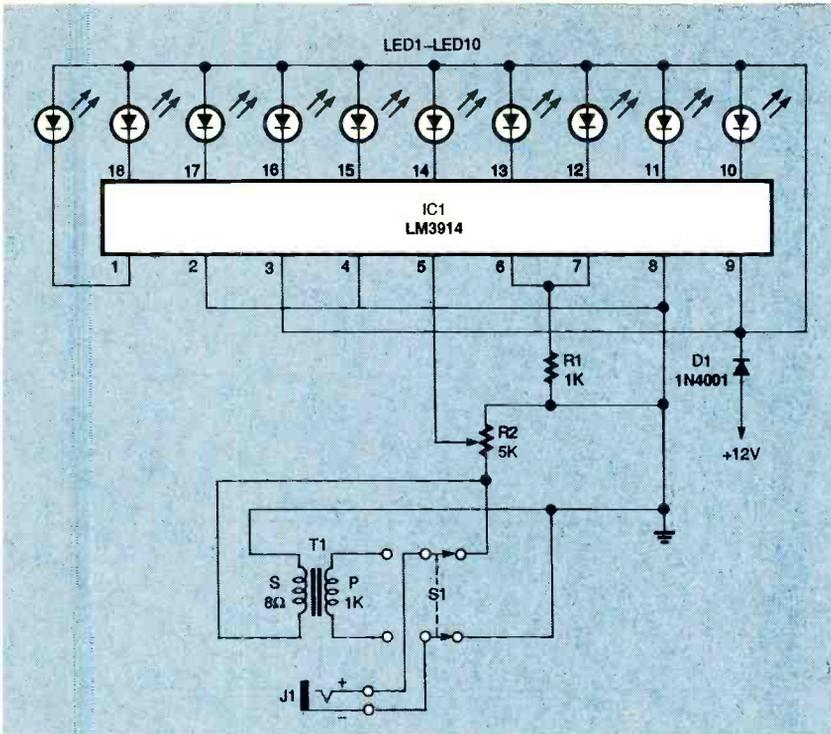


FIG. 6—LED BARGRAPH SCHEMATIC. The circuit consists mainly of an LM3914 bargraph display driver IC.

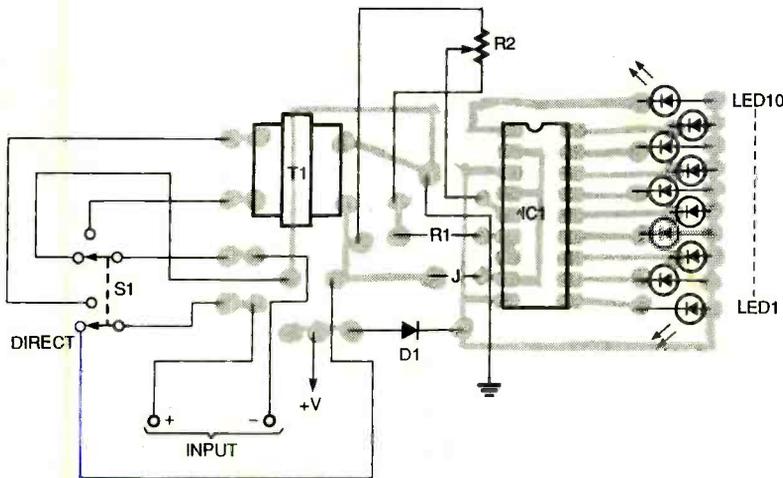


FIG. 7—PARTS-PLACEMENT DIAGRAM for the bargraph circuit.

rated for 0 to 1 milliamper, which is a useful value for many circuit designs, and M2 is 500 microampere.  $\pm$  center scale unit. This is essential when designing a circuit where the output can swing either positive or negative. Meter M2 is illuminated, and the small push-button switch labeled L.O. activates the 6-volt lamp.

A bank of seven-segment LED displays is mounted in the top center of the backboard. The first row of four is in a multi-

plexed arrangement, with all like segments tied together. Connection to the multiplexed displays is accomplished via the SIP socket to the right, which is labeled accordingly. The second row of seven-segment displays is wired as a 3½-digit display that allows individual access to each of the 24 segments and the common anode. Connections to this display row are made via the DIP socket below it, which is marked appropriately for use with digital circuits having that

type of output.

Below the DIP socket is an incandescent lamp indicator with a bayonet-type socket. Bulbs are easily changed, and they are available in 6-, 12-, 14-, and 28-volt versions.

The author installed a ten-step LED bargraph and a 3½-digit voltmeter on the backboard, both as a matter of personal preference. The bargraph is mounted in the center of the backboard as shown in Fig. 5. A schematic of the LED bargraph circuit is shown in Fig. 6. The circuit consists mainly of an LM3914 bargraph display driver IC. Switch S1 allows signals to be input to the driver chip

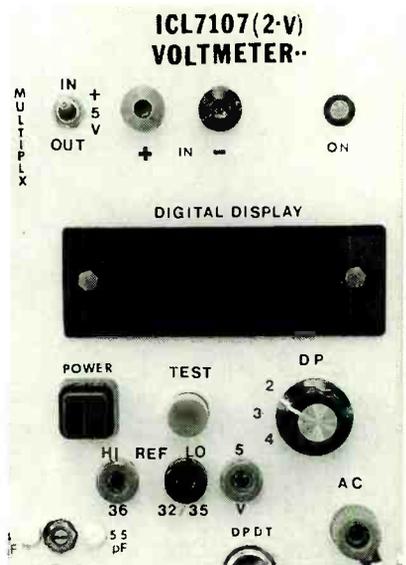


FIG. 8—A 3½-DIGIT VOLTMETER occupies the upper right hand corner of the backboard.

#### PARTS LIST—VOLTMETER

- IC1—ICL7107CPL A/D converter/LED display driver, Harris
- DISP1—two 2-digit common-anode 7-segment displays source
- C1—0.22  $\mu$ F, mica capacitor
- C2—0.047  $\mu$ F, mica capacitor
- C3—0.01  $\mu$ F, mica capacitor
- C4—0.1  $\mu$ F, mica capacitor
- C1—100 pF, ceramic disc capacitor
- R1—470,000 ohms, ¼-watt, 5% resistor
- R2—1 megohm, ¼-watt, 5% resistor
- R3—25,000 ohms, PC-mount potentiometer
- R4—22,000 ohms, ¼-watt, 5% resistor
- R5—100,000 ohms, ¼-watt, 5% resistor
- S1—SPDT toggle switch
- Miscellaneous: pushbutton switch, 3-position rotary switch, five banana jacks, green LED

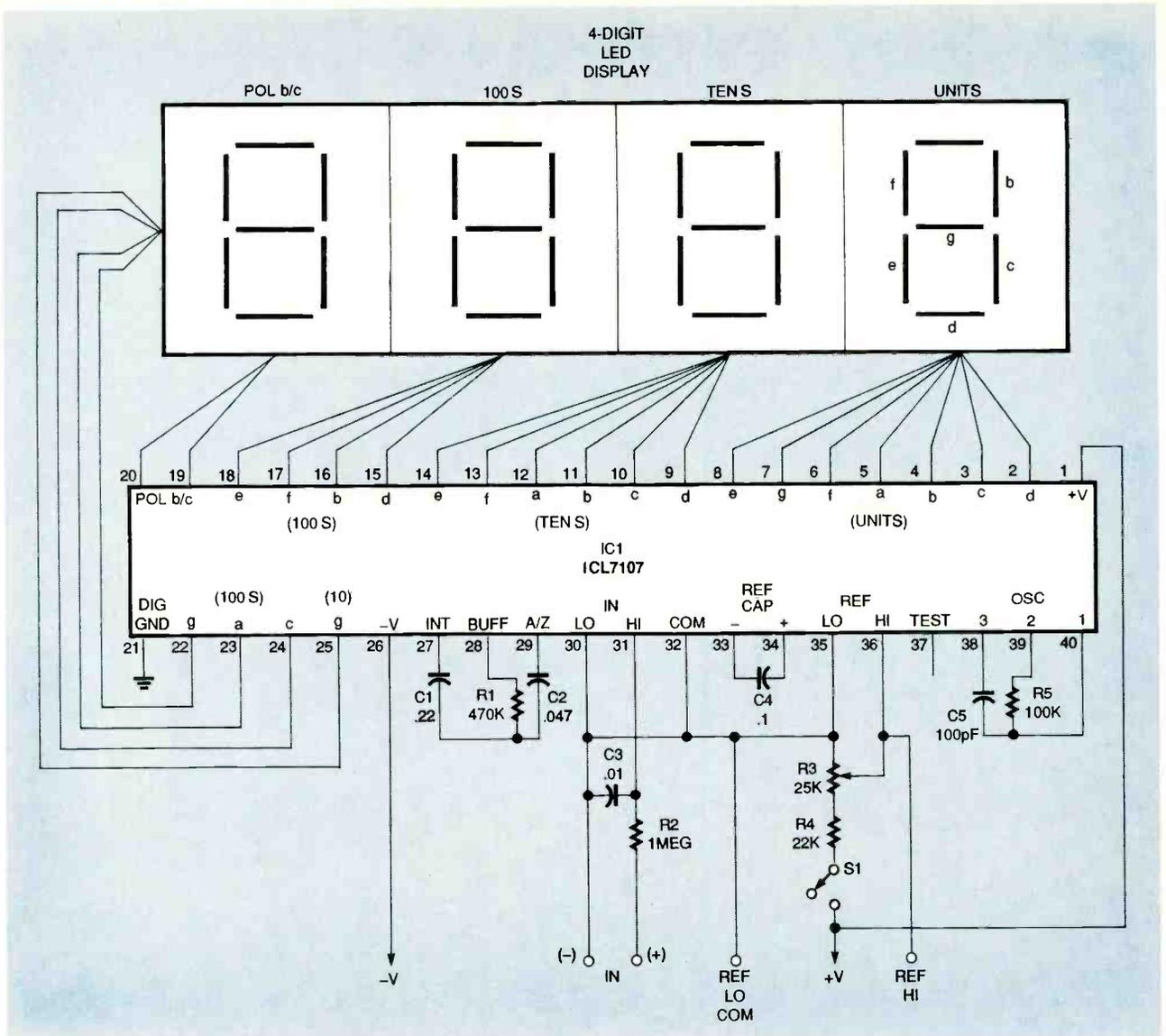



FIG. 9—THE SCHEMATIC DIAGRAM of the voltmeter circuit.

**PARTS LIST—BCD DECODER**

- IC1—74LS48 BCD to 7-segment decoder
- IC2—CD4553 3-digit BCD counter, Harris
- Q1—Q3—2N3906 PNP transistors
- R1—R7—220 ohms, ¼-watt, 5% resistor
- R8—R10—1000 ohms, ¼-watt, 5% resistor
- C1—0.001 µF, ceramic disc capacitor
- DISP1—three common-cathode 7-segment displays

directly, or through a matching transformer T1 for audio.

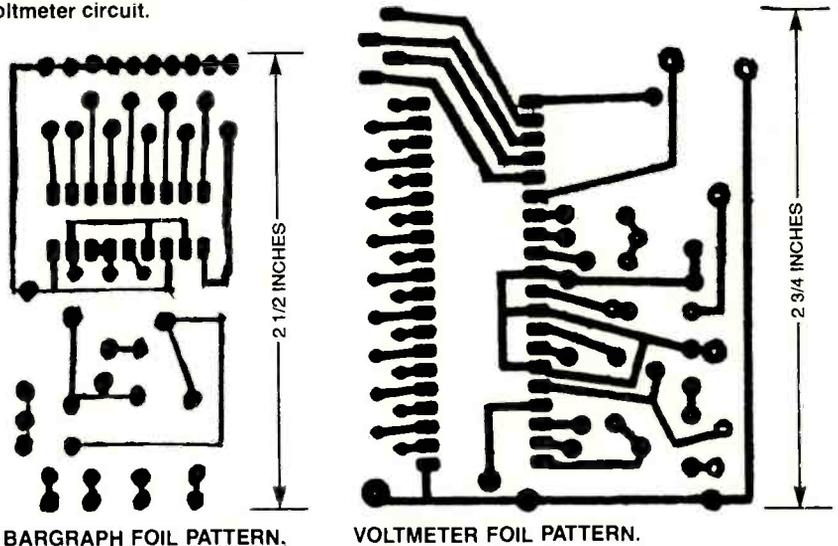Signals are input to the bargraph circuit at J1, a ¼-inch mini phono jack. The 5-kilohm potentiometer (R2) controls gain. The author used a potentiometer with a built-in on/off switch so that power to the bargraph display could be turned



on and off independently. You can either do the same, or use a separate switch for power.

Power for the bargraph circuit is provided by the TI computer supply.

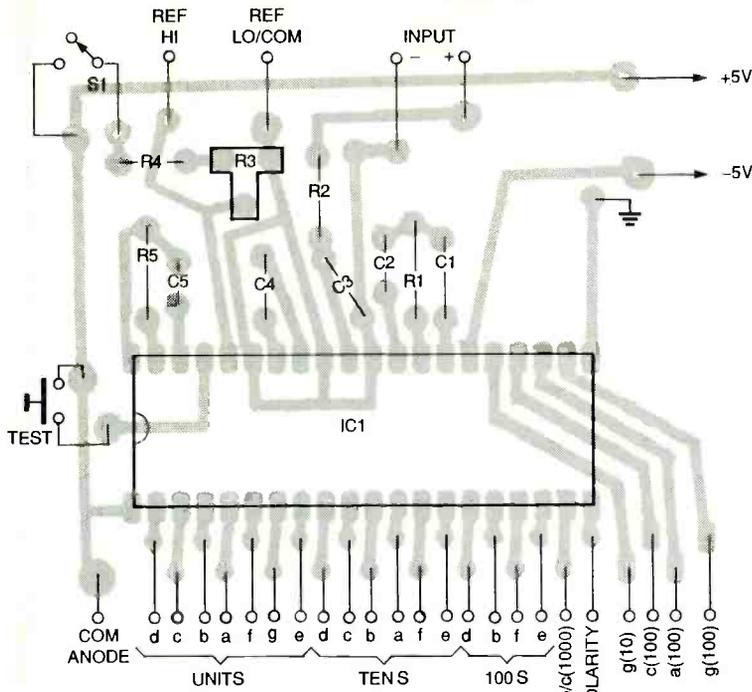


FIG. 10—PARTS-PLACEMENT DIAGRAM for the voltmeter circuit.

### PARTS LIST AUDIO AMPLIFIER

- IC1—LM386 audio amplifier, National Semiconductor
- R1—10,000 ohms, panel-mount potentiometer with switch (or use separate potentiometer and switch)
- C1—20  $\mu$ F, 25 volts, electrolytic
- 8-position terminal strip
- 1½-inch, 8-ohm speaker

### PARTS LIST—METER

- M1—4- to 6-inch, 0 to 1 mA analog-meter movement
- S1—8-position rotary switch
- D1—1N4002 diode
- R1—10 ohms, ¼-watt, 5% resistor
- R2—100 ohms, ¼-watt, 5% resistor
- R3—1000 ohms, ¼-watt, 5% resistor
- R4—10,000 ohms, ¼-watt, 5% resistor
- R5—100,000 ohms, ¼-watt, 5% resistor
- R6—1 megohm, ¼-watt, 5% resistor
- R6—10 megohms, ¼-watt, 5% resistor
- Two banana jacks

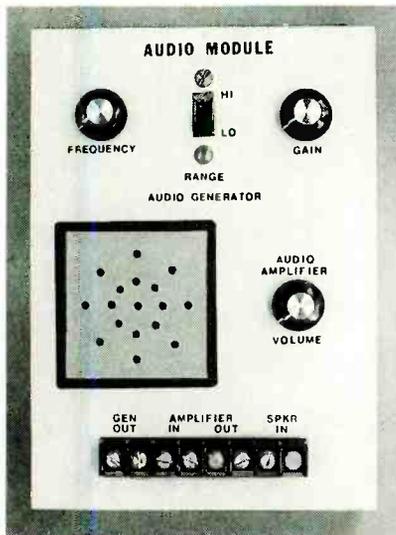


FIG. 11—THE AUDIO MODULE consists of an audio generator, an amplifier, a speaker, and a terminal strip.

A foil pattern is provided for the bargraph circuit, and the parts-placement diagram for it is shown in Fig. 7.

The 3½-digit voltmeter occupies the upper right hand corner of the backboard, as shown in Fig. 8. Figure 9 is the schematic diagram of the voltmeter circuit. A foil pattern is provided for this circuit, and Fig. 10 is its parts-placement diagram. This circuit can also be point-to-point wired. The circuit contains a Harris ICL 7107

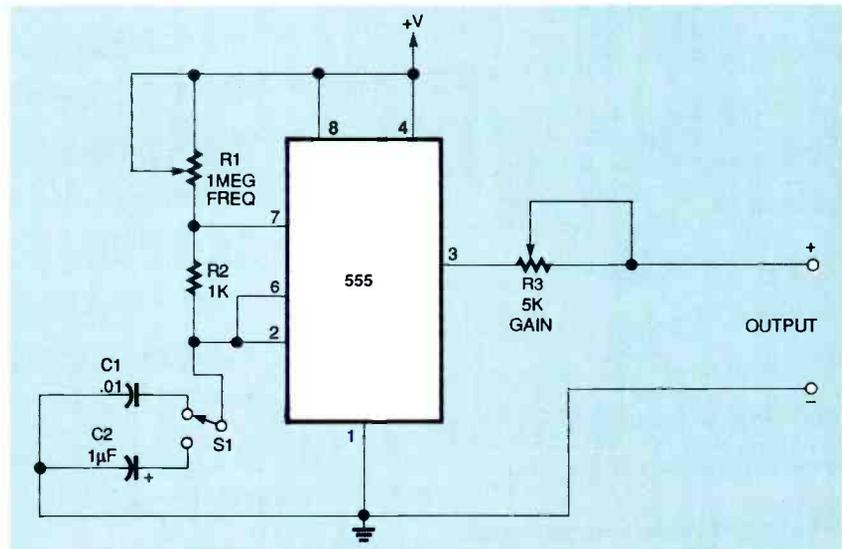


FIG. 12—SIGNAL GENERATOR. Potentiometer R1 sets the output frequency.

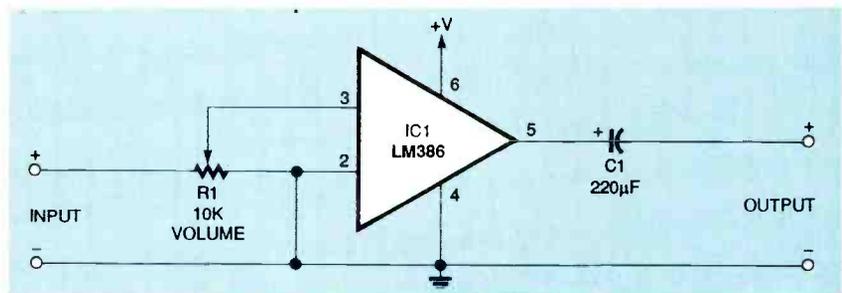


FIG. 13—AUDIO AMPLIFIER. This circuit has a gain of about 20.

analog-to-digital converter/ display driver. A standard 2-volt configuration was chosen for

this circuit. Switch S1 allows the +5-volt source to be routed either to the on-board 25-kilo-

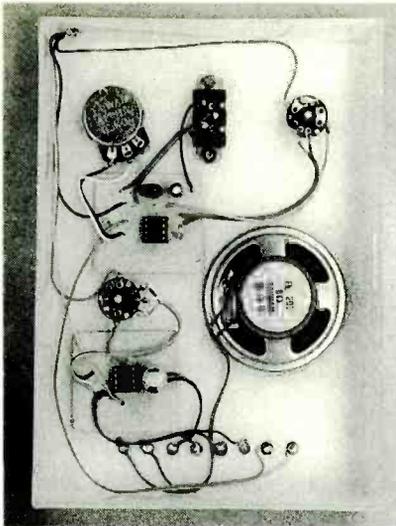


FIG. 14—THE AUDIO MODULE is too simple to call for a PC board, so point-to-point wiring was used.

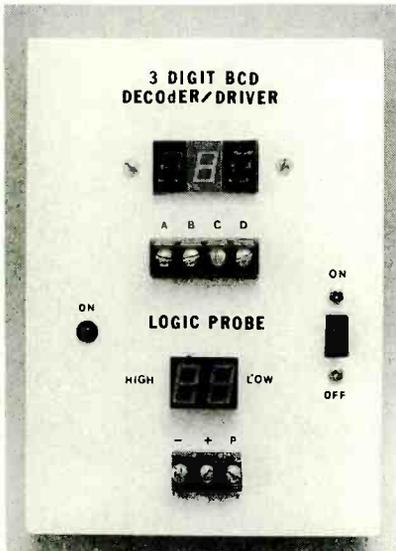


FIG. 15—3-DIGIT BCD DECODER-driver is another practical function block.

**PARTS LIST—AUDIO MODULE**

- IC1—L555 timer
- R1—1 megohm, panel-mount potentiometer with switch
- R2—1000 ohms, 1/4-watt, 5% resistor
- R3—5000 ohms, panel-mount potentiometer
- C1—0.01  $\mu$ F, Tantalum
- C2—1  $\mu$ F, Tantalum
- S1—SPDT switch

hm potentiometer, or to an external jack, depending on the need. To calibrate the meter, apply 1.2 volts from the variable power supply to the input, and adjust R3 until the display reads 1.200. Then, switch the input leads, and the display should read -1.200.

**PARTS LIST—LOGIC PROBE**

- IC1—7404 hex inverter
- R1—220 ohms, 1/4-watt, 5% resistor
- LED1—green light-emitting diode
- LED2—red light-emitting diode
- Two common-anode 7-segment displays (optional, see text) source

The left side of the base is reserved for add-on modules, which can have a number of different functions depending on what is needed. The audio module shown in Fig. 11 consists of an audio signal generator, an

*Continued on page 78*

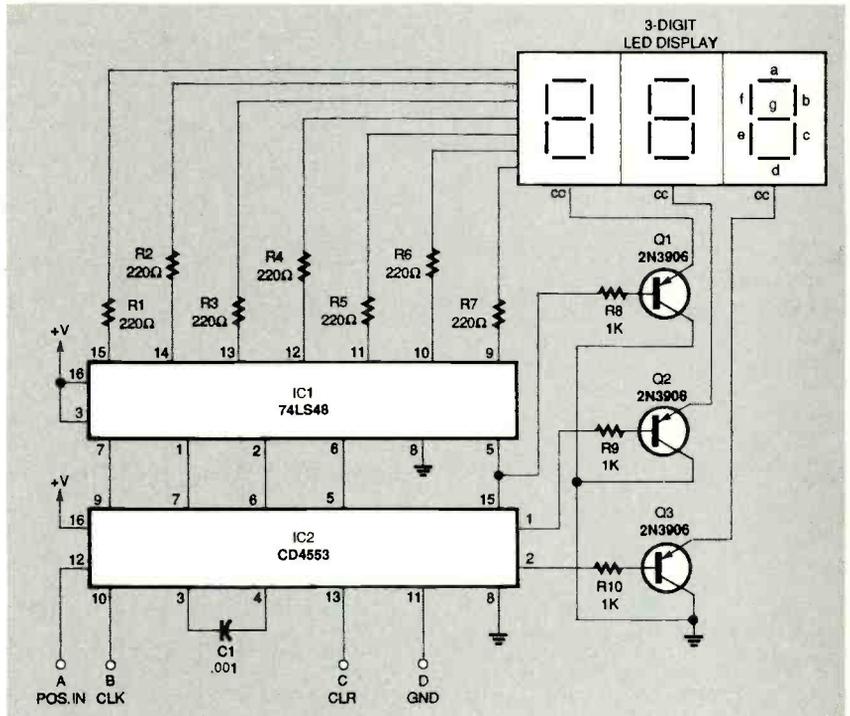


FIG. 16—THE BCD DECODER-DRIVER circuit will interface with any standard BCD output to produce a digital display.

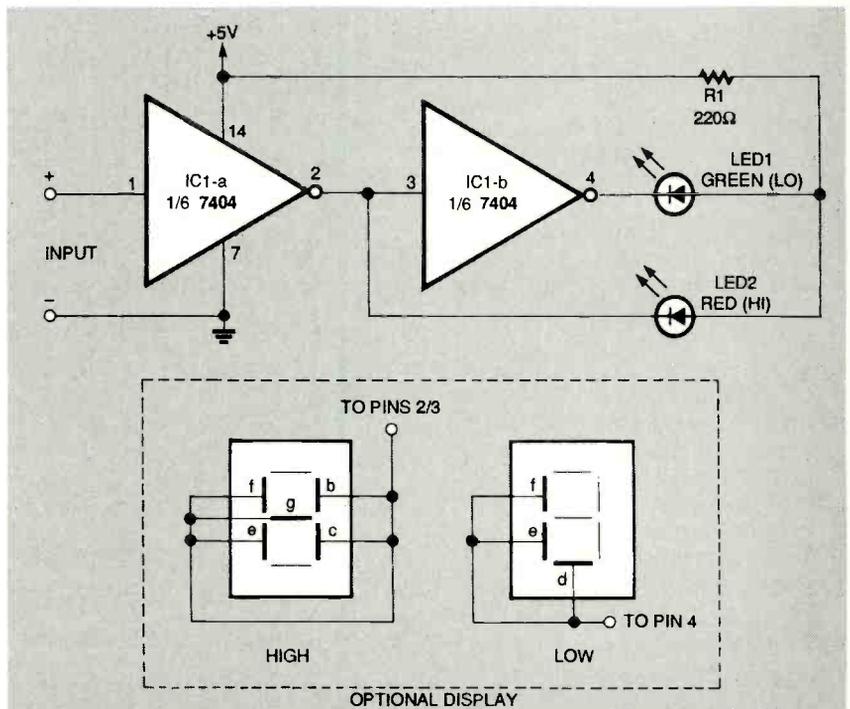


FIG. 17—A LOGIC PROBE is also included in BCD decoder module. The red LED lights to indicate a logic high, and the green LED lights to indicate a logic low.

# The PROCAR SECURITY SYSTEM

***This is the second part of a series of articles about building an automobile alarm, anti-theft, and anti-carjacking system that sounds off before it disables the car.***

DAVID T. MIGA

IN THE FIRST PART OF THIS ARTICLE (*Electronics Now*, March, 1995, page 35) the ProCar system was explained and its functions were described. This part picks up with a discussion of the Power Module and goes on to describe the assembly of components to the Main Alarm, Voice/Options, and Power Module circuit boards.

Procedures discussed in this part include wiring the Power Module board, the assembly of the board to the aluminum case and interboard wiring. Other subjects covered include the formation of the wiring harnesses and the packaging of the Logic Module.



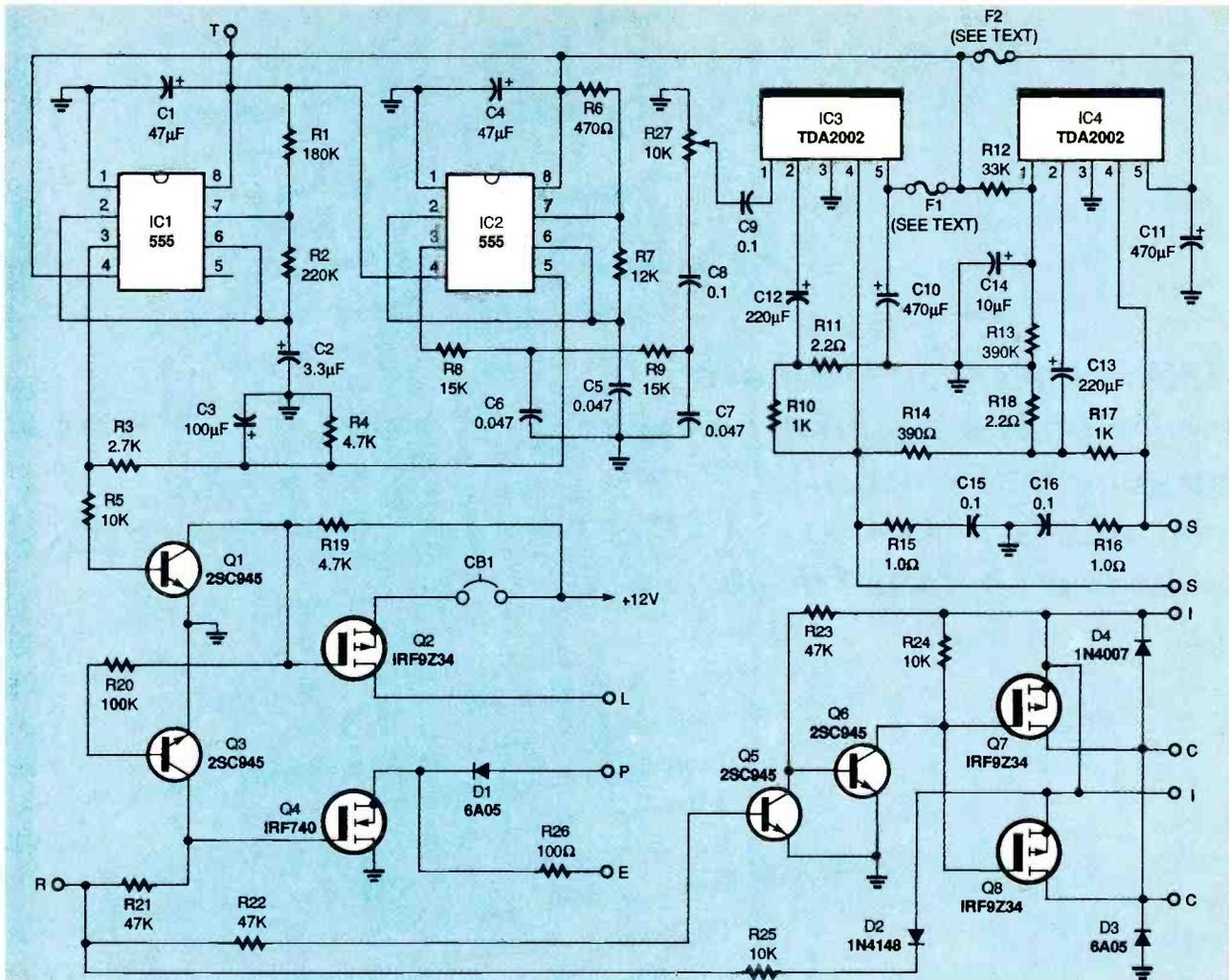


FIG. 4—SCHEMATIC FOR THE POWER MODULE. Off-board power ICs and MOSFETs power the alarm siren and other functions.

**Power module**

The Power Module is a small, aluminum, two-part case containing the single-sided Power Module circuit board. Figure 4 is the schematic for the Power Module circuit board, which includes the siren/amplifier circuit, the engine-stop circuits, and the light-flashing circuit.

**Siren circuit**

IC1 and IC2 are 555 timers configured as astable oscillators whose output can closely simulate a police siren. (If that kind of warning signal is illegal where you live, the omission of capacitor C3 will alter the output to the European police car and fire truck "he-haw" sound.

A filter consisting of 15-kilohm resistor R8 and 0.047µF capacitor C7 corrects the squarewave output, and TDA2002 power amplifiers IC3

and IC4, configured in a bridge, supply up to 16 watts of output.

**Light-flashing circuit**

Oscillator IC1, which oscillates at about 1 hertz, is part of the siren circuit. It also activates NPN transistor Q1 and P-channel depletion-mode MOSFET Q2 to provide up to 18 amperes of 12-volt power to flash the parking lights while the siren sounds. Transistor Q1 also triggers transistor Q3, which is part of the engine-cut-off circuitry.

When the lights flash and the siren sounds, the engine will temporarily stall and then restart. The driver will soon realize that there is engine trouble and stop the vehicle. This response occurs only when the *Armed line* is at logic high, as would occur in an attempted carjacking.

**Engine disable**

ProCar contains two completely unrelated engine disable circuits. The choice will depend on the builder's selection of interrupt. The simplest is the starter interrupt (the engine pulse circuit described in the previous paragraph), or a complete engine disable circuit that cuts off both fuel and ignition.

The complete engine disable circuit is recommended for automobiles with standard stick-shift transmissions because the engine will still be turning as long as the car is coasting, thus retaining both steering and braking power.

However, the engine pulse and starter interrupt circuit should be selected for automobiles with automatic transmissions. Completely disabling the engine of an automobile with an automatic transmis-

sion and power brakes and steering will make steering and braking difficult. That part of the circuit including N-channel MOSFET Q4 will apply ground to lines "P" or "E" that are synchronized to the siren and light flasher.

If the car has a carburetor and a single ignition coil, the "P" line is connected to the ignition points or negative coil, causing the engine to alternately stall and restart in short cycles when the siren and lights are activated. The coil will not be damaged because MOSFET Q4 has a high output impedance which is enhanced by diode D1 so that the voltage drop across the coil is only 7 volts, rather than 12 volts.

The "E" output, called the Engine Sensor Defeat (ESD) line, should be selected for newer automobiles with engine microcontrollers, fuel injection, or multiple-coil systems. The ESD (E) line is grounded through 100-ohm protective resistor R26.

The E wire can be connected to the throttle position sensor or mass air sensor output to upset the microcontroller, which will not be damaged because of the presence of resistor R26. The engine will not stall, but because of the incorrect signals, the engine controller will make the engine perform erratically. (Some fault codes are stored in the computer's memory.) This will cause the CHECK ENGINE indicator to turn on.

The alternative engine circuit performs in a way that is the exact opposite the "P-E" output from Q4. Where that circuit grounds the "P" and "E" lines, the interrupt circuitry that includes P-channel depletion mode MOSFETs Q7 and Q8 interrupts power between the "I" and "C" lines. This circuit can power the fuel injectors or be wired as a simple starter-interrupt function.

When ProCar is activated, the Armed line is high, saturating NPN transistor Q5 connected to NPN transistor Q6. As a result, the pair will not conduct. The pair of P-channel depletion-mode MOSFETs, Q7 and Q8,


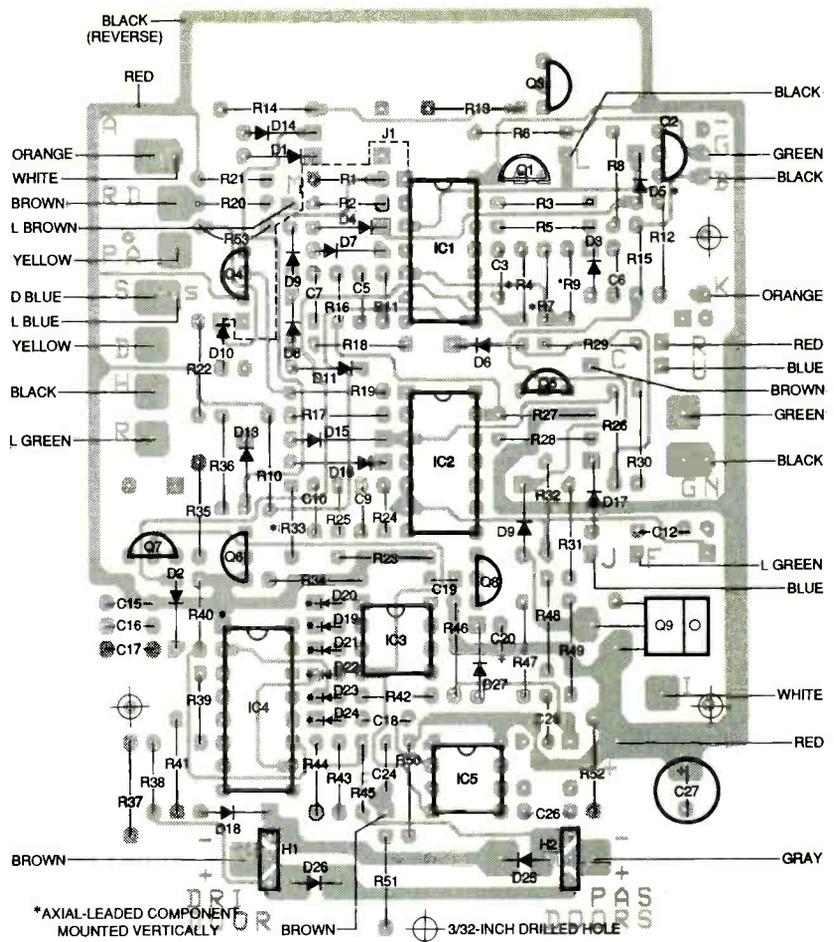


FIG. 5—MAIN ALARM BOARD PARTS PLACEMENT DIAGRAM. All components but 10 capacitors are on this side of the board. All inter-board wiring starts here.

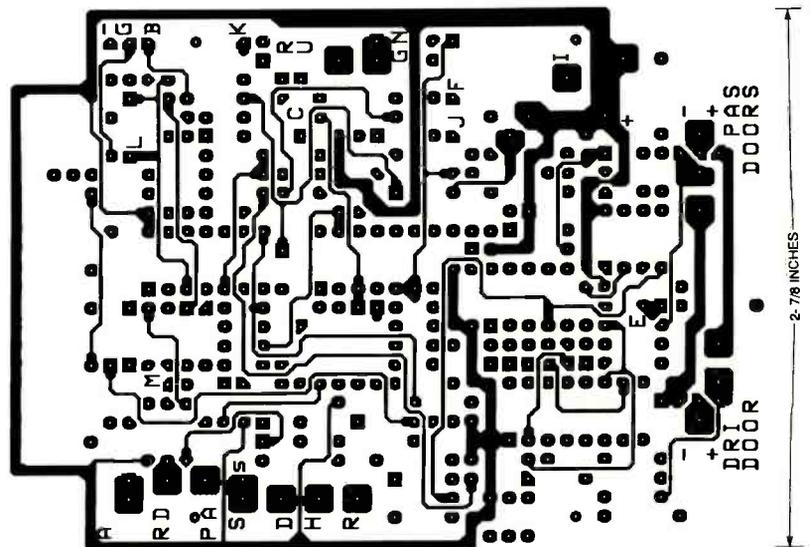


MAIN ALARM BOARD FOIL PATTERN (principal component side)

provide backup or failsafe so that the owner/authorized driver will never be stranded.

Moreover, each MOSFET is rated for 18 amperes so there will be adequate built-in capaci-

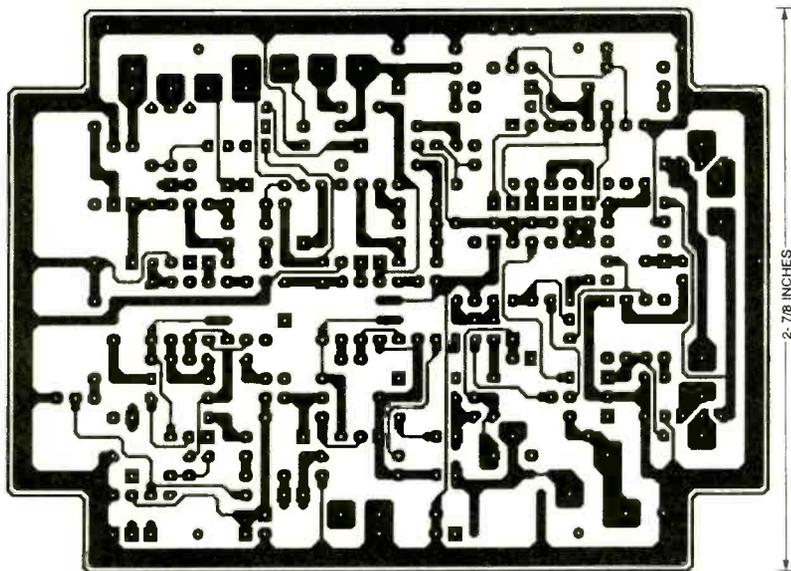ty for powering high-current circuits such as fuel injectors or fuel pumps. Diode D3 protects MOSFETs Q7 and Q8 from inductive spikes originating at the starter relay, and diode D4



MAIN ALARM BOARD FOIL PATTERN (10 capacitor side)

### PARTS LIST

#### Power module

All fixed resistors are 1/4-watt, 10%.

R1—180,000 ohms  
 R2—220,000 ohms  
 R3—2,700 ohms  
 R4, R19—4,700 ohms  
 R5, R24, R25—10,000 ohms  
 R6—470 ohms R7—12,000 ohms  
 R8, R9—15,000 ohms  
 R10, R17—1,000 ohms  
 R11, R18—2.2 ohms  
 R12—33,000 ohms  
 R13—390,000ohms  
 R14—390 ohms  
 R15, R16—1 ohm  
 R20—100,000  
 R21, R22, R23—47,000 ohms  
 R26—100 ohms  
 R27—10,000 ohms, trimmer potentiometer, PCB mount

#### Capacitors

C1, C4—47 $\mu$ F, 16 C2—3.3 $\mu$ F, 50 volts, aluminum electrolytic  
 C3—100 $\mu$ F, 16 volts, aluminum electrolytic  
 C5, C6, C7—0.047 $\mu$ F, 50 volts, polyester  
 C8, C9, C15, C16—0.1 $\mu$ F, 50 volts, polyester  
 C10, C11—470 $\mu$ F, 16 volts, aluminum electrolytic  
 C12, C13—220 $\mu$ F 16 volts, aluminum electrolytic  
 C14—10 $\mu$ F 25 volts, aluminum electrolytic

#### Semiconductors

D1, D3—6A05 silicon diode, 6 ampere, 50 volts, Diodes Inc. or equiv.  
 D2—1N4148 silicon diode

D4—1N4007 silicon diode  
 IC1, IC2—555 timer  
 IC3, IC34—TDA2002 power amplifier, 10 watt, National Semiconductor or equiv.  
 Q1, Q3, Q5, Q6—2SC945 NP transistor, NEC or equiv.  
 Q2, Q7, Q8—IRF9Z34 PN-channel, depletion mode MOSFET International Rectifier or equiv.  
 Q4—IRF740—PN-channel, depletion mode MOSFET International Rectifier or equiv.

#### Other components

LED1—light-emitting diode, dual color, green/blinking red T1 $\frac{3}{4}$  Toshiba No. 111DC or equiv. PL1—15-pin plug, nylon shell, AMP A1462 with A1440 male contacts or equiv.  
 SO1—15-pin jack, nylon shell AMP A1463 with A1441 female contacts or equiv.

**Miscellaneous:** main alarm circuit board; voice/options circuit board; power module circuit board; two-part logic module case (LMB Heeger No. 402, 4.0 L x 3.0 W x 1.25 H inches, inside), plastic; two-part power module case (LMB Heeger No. J875 4.0 L x 2.25 W x 2.25 H inches, aluminum; three-wire cable (red, black, and green), type CM, Carol or equiv., five feet; lengths of stranded insulated hookup wire in a range of colors suitable for the automotive environment; rectangular T)-220 mica insulators (2); miscellaneous nuts and bolts; rubber grommet, 0.5-inch ID; solder.

protects the MOSFETs if the system installer should accidentally interchange the input and output wires.

The possibility that the car thief might know enough about the protective system to cut the three wires between the Logic module and the power module was considered in the design. The *Armed line* must be at logic high to stop the engine, and sufficient voltage through diode D2 will keep the engine cut off. During normal operation, the *Armed line* is grounded by the NPN transistor Q7 in the Main Alarm board (shown in Fig. 1 last month).

### ProCar circuit boards


If you prefer to make your own circuit boards, the foil patterns of all three boards are included here. The two double-sided boards with plated-through holes (Main Alarm and Voice/Options) have clear-drilled mounting holes, and the single-sided Power Module board has clear-drilled mounting holes. However, completed boards can be purchased from the source given in the Parts List.

Follow standard leaded-component insertion and soldering practice in constructing the electronic circuits. Before inserting components with polarities (diode cathodes and positive terminals of electrolytic capacitors), verify that they are correctly oriented as shown in the five parts placement diagrams. Position all integrated circuits in DIP cases so that the notches or dots indicating the position of pin 1 are as shown on the three parts placement diagrams where they are shown.
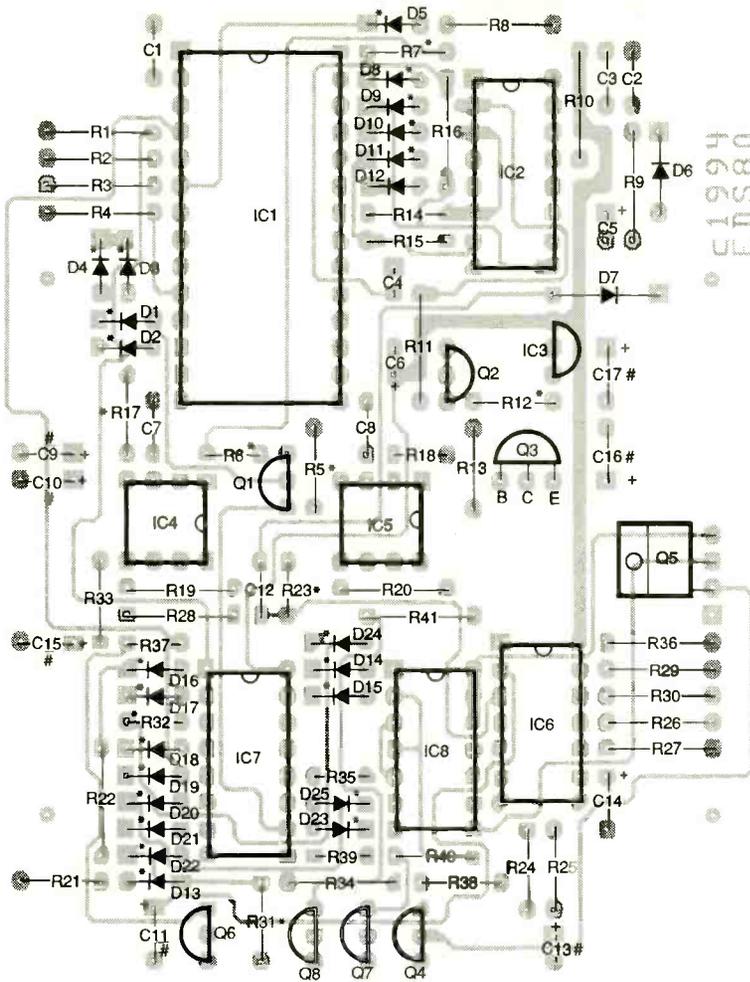
### Logic module



The Main Alarm and Voice/Options boards will both be mounted in a two-part "clamshell" plastic case made as two matching covers. The Main Alarm board will be mounted sandwich-like in one cover and the Voice/Options board will be mounted in the opposing cover in later steps. The inter-board connections and external harness wiring will also be performed in later steps.





CLEAR DRILLED HOLE: 3/32 INCH  
 \* AXIAL-LEADED PART MOUNTED VERTICALLY  
 # RADIAL-LEADED PART, LEADS BENT 90° TO LIE FLAT AGAINST BOARD

FIG. 7—VOICE/OPTIONS PARTS PLACEMENT DIAGRAM. The voice record/playback IC1 provides 16 seconds of voice messages.

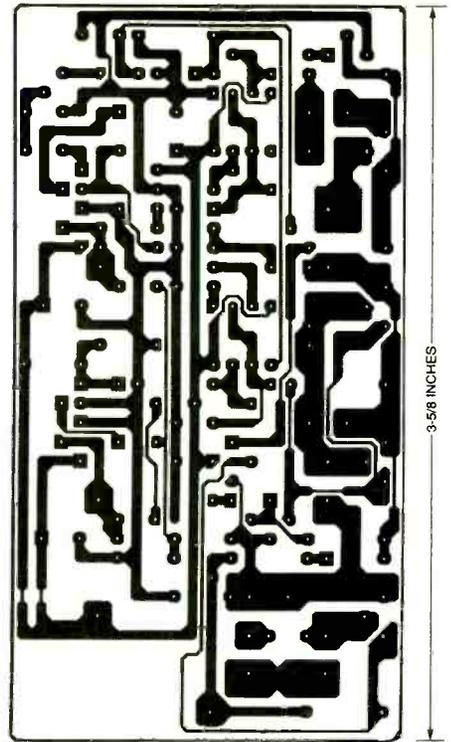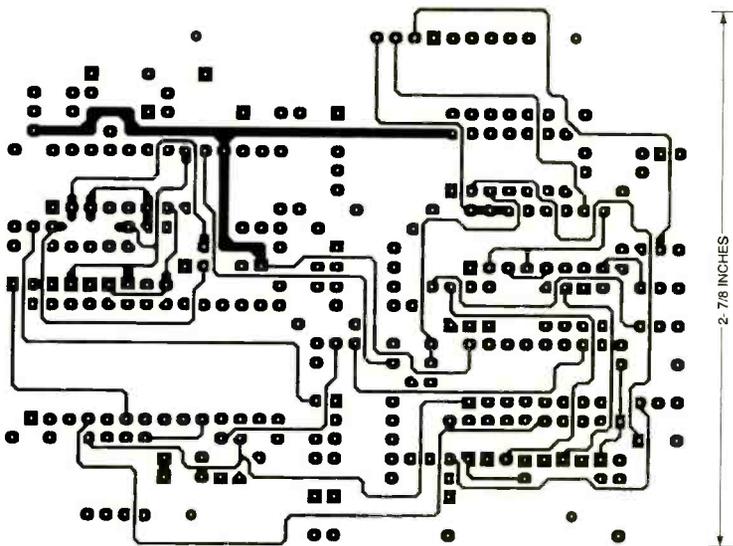

FOIL PATTERN FOR THE POWER MODULE.

NOTE: Omit all external and inter-board wiring at this time. This wiring will be done after completing the component insertion and soldering on all three boards.

Refer to the parts placement diagram Fig. 6. Mount the eight capacitors on the reverse side: C1, C2, C4, C8, C11, C13, C14, C20, C22 and C25. Capacitors C2 and C11 are 0.1µF monolithic ceramic capacitors that are soldered between IC1 and IC2 in the pads under those ICs. Form right-angle bends in the leads of all capacitors (indicated by the pound sign in Fig. 6) so that they can be positioned flat against the board and take up less space.

After soldering all leads, verify that all solder joints are clean and shiny. Resolder any cold solder joints, indicated by their gray, irregular surfaces. Verify that there are no inadvertent solder bridges. Recheck the orientation of all diode and capacitor polarities.

**Voice/options board**

Insert all components of the Voice/Options board on the component side of the board, as shown in Fig. 7, as close as pos-

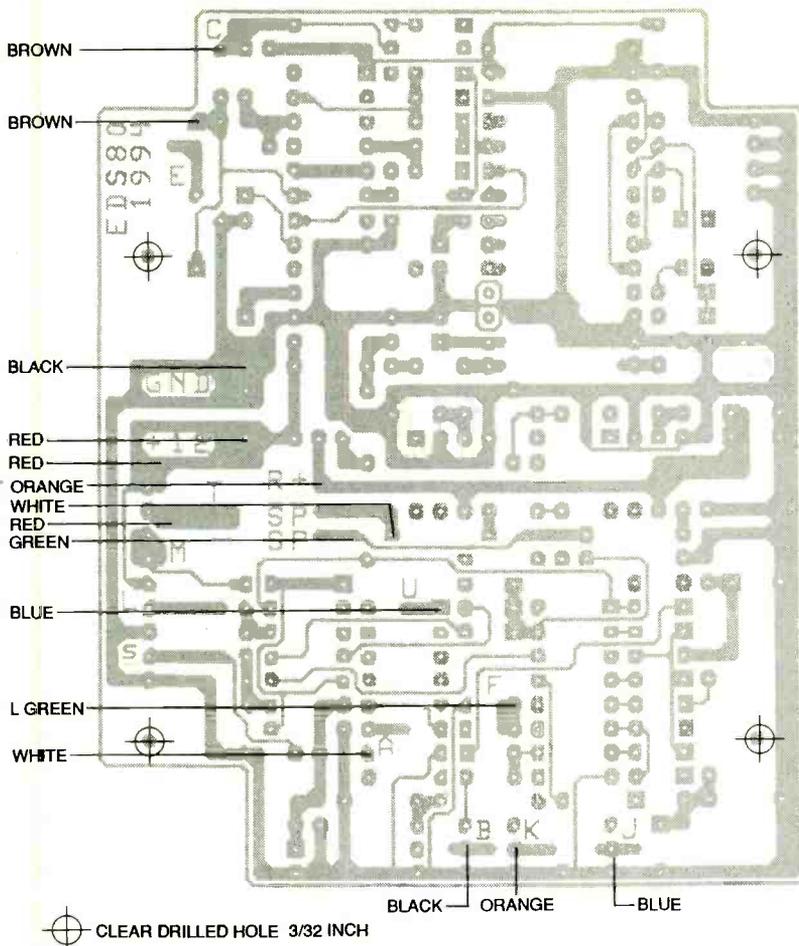


FIG. 8—VOICE/OPTIONS PARTS PLACEMENT DIAGRAM reverse side. Wiring for the main alarm board is located here.

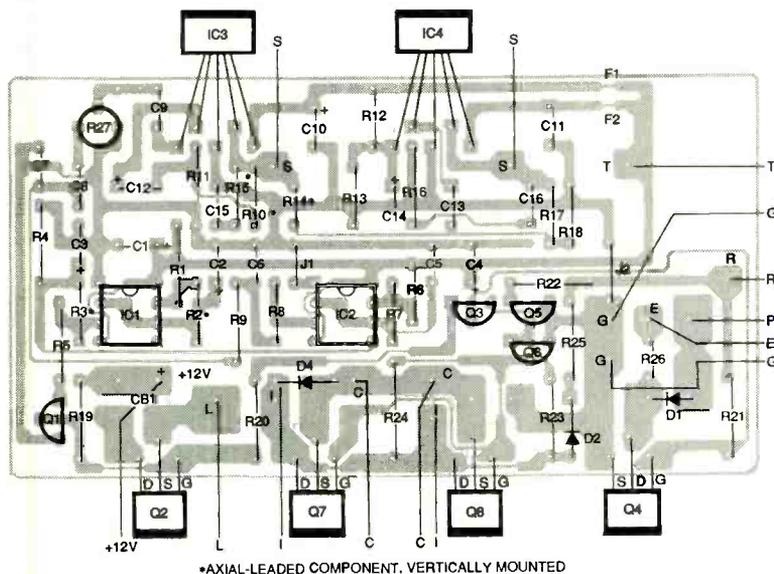


FIG. 9—POWER MODULE PARTS PLACEMENT DIAGRAM. Power transistors and ICs are mounted on sidewalls of aluminum case for heat sinking.

sible to the board. (The space available inside the covers of the case is limited.) Solder all components, but do not trim excess lead lengths.

Figure 8 shows the locations of the connecting wires on the reverse side of the Voice/Options board to be inserted and soldered later.

### Power Module board

Refer to the Power Module parts placement diagram Fig. 9. NOTE: The schematic for the power module board shows two fuses, F1 between terminal "T" and C10 and F2 between terminal "T" and C11. The effective resistance of the narrow copper traces on the board will function as fuses so that no discrete fuses are required.

Start assembly by bending and inserting the two jumper wires, J1 and J2. Then insert all of the small resistors and capacitors (including those whose leads are to be bent for vertical mounting, as indicated by the asterisks on Fig. 9). Position these components close to the board, and solder them in position. Do not trim excess component lead lengths at this time. Insert and solder the small-signal transistors paying attention to polarity.

Insert the DIP-packaged integrated circuits IC1 and IC2, observing the correct orientation of pins. Then insert the radial-leaded capacitors observing their polarities. Solder all the leads of these components.

Bend the leads of integrated circuits IC3 and IC4, and four power transistors, Q2, Q4, Q7 and Q8, so that they stand vertically at the edges of the circuit board with the heatsink tabs facing outward. Solder them in position, and trim all excess lead lengths at this time. Verify that there are no inadvertent solder bridges and cold solder joints. Correct all soldering errors found before proceeding any further.

The Power Module circuit board is to be mounted in an aluminum channel, one of two-parts of an aluminum case, in later steps. It will be necessary to insert the circuit board in the aluminum channel and mark the locations of holes in the power semiconductor heatsink tabs on the sidewalls of the case for drilling and fastening with nuts, and bolts. This procedure as well as all wiring between circuit boards and the formation of external wire harnesses will be described in the next few paragraphs.

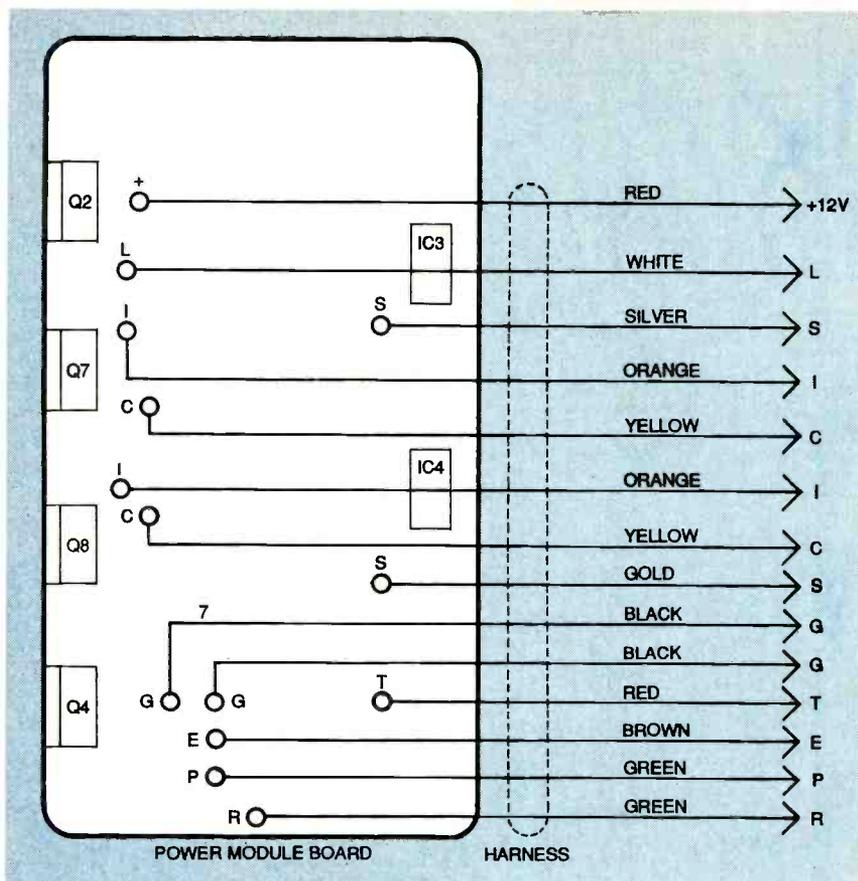


FIG. 10—POWER-MODULE WIRING HARNESS. Color-coded hookup wires are soldered to the circuit board, as shown.

### Power Module wiring

Refer to Fig. 10 for the wiring of the Power Module board to form the external wiring harness. Cut lengths of No. 18 AWG insulated, stranded, tinned hookup wire in the colors shown to 8-inch lengths. Follow the color coding shown in Fig. 10 and strip both ends of the wire. Solder one end of each wire to the pad locations on the board designated by letters. Verify that all wiring is correct, and make any corrections necessary. Then trim all excess component lead and wire lengths.

NOTE: In a later step, the wires will be bundled to form a harness that will be passed through a grommet in the sidewall of the aluminum case opposite the location of Q4.

### Power Module packaging

Refer to the exploded view of the Power Module in Fig. 11. Position the circuit board in the channel half of the aluminum case so that there is a clearance distance of about  $\frac{1}{16}$ -inch be-

tween the solder side of the board and the bottom of the channel. Verify that the centers of the holes in the TO-220 packaged power semiconductors are about  $\frac{7}{8}$ -inch above the bottom of the channel.

Mark and centerpunch the locations of the six  $\frac{1}{8}$ -inch holes to match those in the heatsink tabs of power transistors Q2, Q7, Q8 and Q4 on one sidewall and IC3 and IC4 on the opposite sidewall. Mark and centerpunch the location of the  $\frac{1}{16}$ -inch grommet hole as shown in Fig. 11. Drill or form all holes and insert the  $\frac{5}{8}$ -inch rubber grommet in the large hole.

Position the circuit board in the case channel, as shown in Fig. 11. Align the drilled holes in the case with the punched holes in the heatsink tabs. Slight misalignment of the holes in the case and power MOSFET heat-sink tabs can be corrected by carefully bending the leads of the power semiconductors.

Place rectangular mica transistors under the heatsink tabs

of power MOSFET transistors Q2, Q7, Q8, and Q4 and fasten them to the case sidewalls with  $\frac{1}{4}$ -inch long screws and nuts, as shown in Fig. 11. Then fasten power amplifiers IC3 and IC4 to the case sidewalls with  $\frac{1}{4}$ -inch long screws and nuts, as shown in Fig. 11. NOTE: the power amplifiers, IC3 and IC4, are grounded, so they need not be insulated.

Carefully gather the 14 soldered wires together and form them into a bundle and pass it through the grommet in the sidewall. The bundle can be cabled with wire ties or a length of heat-shrinkable tubing to form a jacket. Terminate the bundle with the 15-position connector socket SO1.

### Module Interconnection

Refer to Fig. 12, the inter-board wiring diagram. Place the two circuit boards together in the orientation shown in Fig. 12 with a separation of about 1 inch. The color-coded interconnecting wires connect (reading from left to right and down) points A, L, B, M, S, K, C, U, GND, J, F, +12V, and E.

Cut color-coded No. 28 AWG stranded, tinned, hookup wire to lengths so that, when soldered in position, they will connect the labeled circuit board pads. The 1-inch separation distance provides enough slack to permit the boards to be opened out for testing and maintenance. NOTE: Excessive wire lengths or heavier wire will make it difficult close the case halves when the interconnected boards are fastened into the plastic case. Strip both ends of the wires and solder one end of each in position.

### External module wiring

Refer to Fig. 13, the external wiring diagram. The wires that form the external harness are terminated in the Main Alarm board pads designated (reading counterclockwise) A, RD, PA, S, D, H, R, +DRI DOOR, +PAS DOOR, I, R G, and "-". On the Voice/Options board, these wires are designated (reading left to right) GND, T, +12V, SP, SP, and R+.

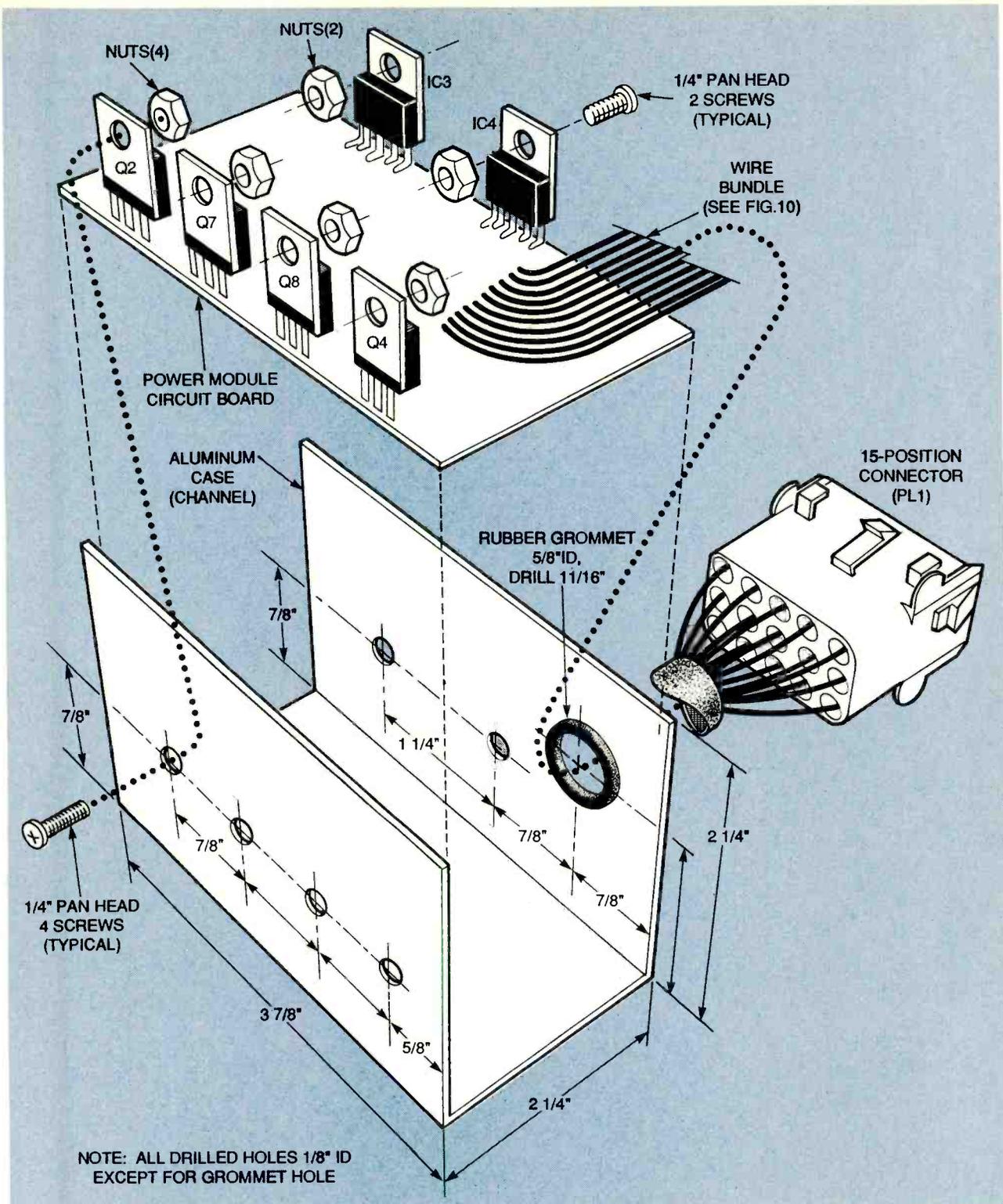


FIG. 11—POWER MODULE/CASE ASSEMBLY. Drilled holes permit mounting the power semiconductor heatsink tabs to the case sidewalls. The grommet protects the bundled wires.

The black, green, and red wires that connect to pads "—," G, and R, respectively, on the Main Alarm board are part of a three-wire cable to LED1. Cut this cable to a length of at least 3 feet. Cut another 10-inch length

of the same type of three-wire cable for the connection to the Power Module. The black and green wires terminate of the Main Alarm board, and the red wire on the T pad of the Voice/Options board.

The black, brown, yellow, and red wires (upper left side of the Main Alarm board) will connect it to the Remote RF Receiver. If you intend to include this unit, cut 12-inch lengths in those colors from No. 28 AWG, stranded, tinned hookup wire. Strip both ends of the wires.


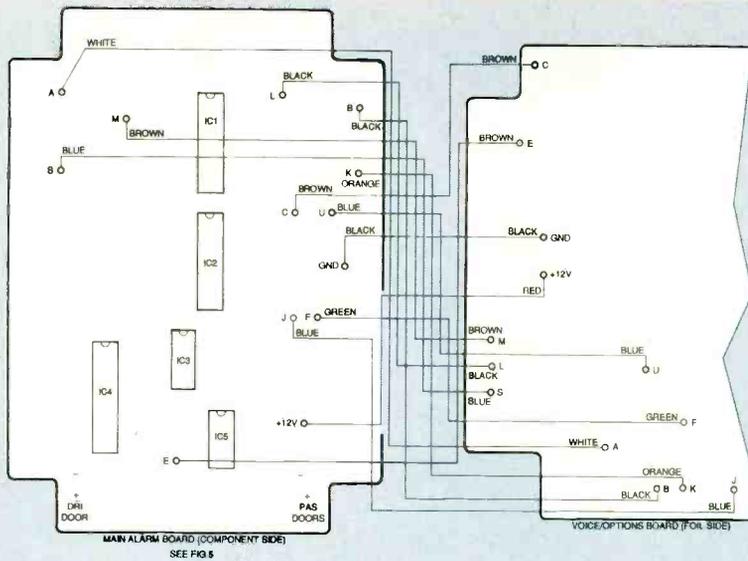


FIG. 12—INTERBOARD WIRING BETWEEN THE MAIN ALARM AND VOICE/OPTIONS boards. Slack in the wires permit the boards to be separated for service.

FIG. 13—LOGIC MODULE WIRING HARNESS. Color-coded wires from the Main Alarm and Voice/Options boards form the harness that terminates in connector socket S01.

PIN NUMBER	3	6	5	15	14	11	12	10	2	13	1	8	9	7
FUNCTION	A	S	D	H	R	DRI	PAS	I	GND	T	+12V	SP	CP	R+

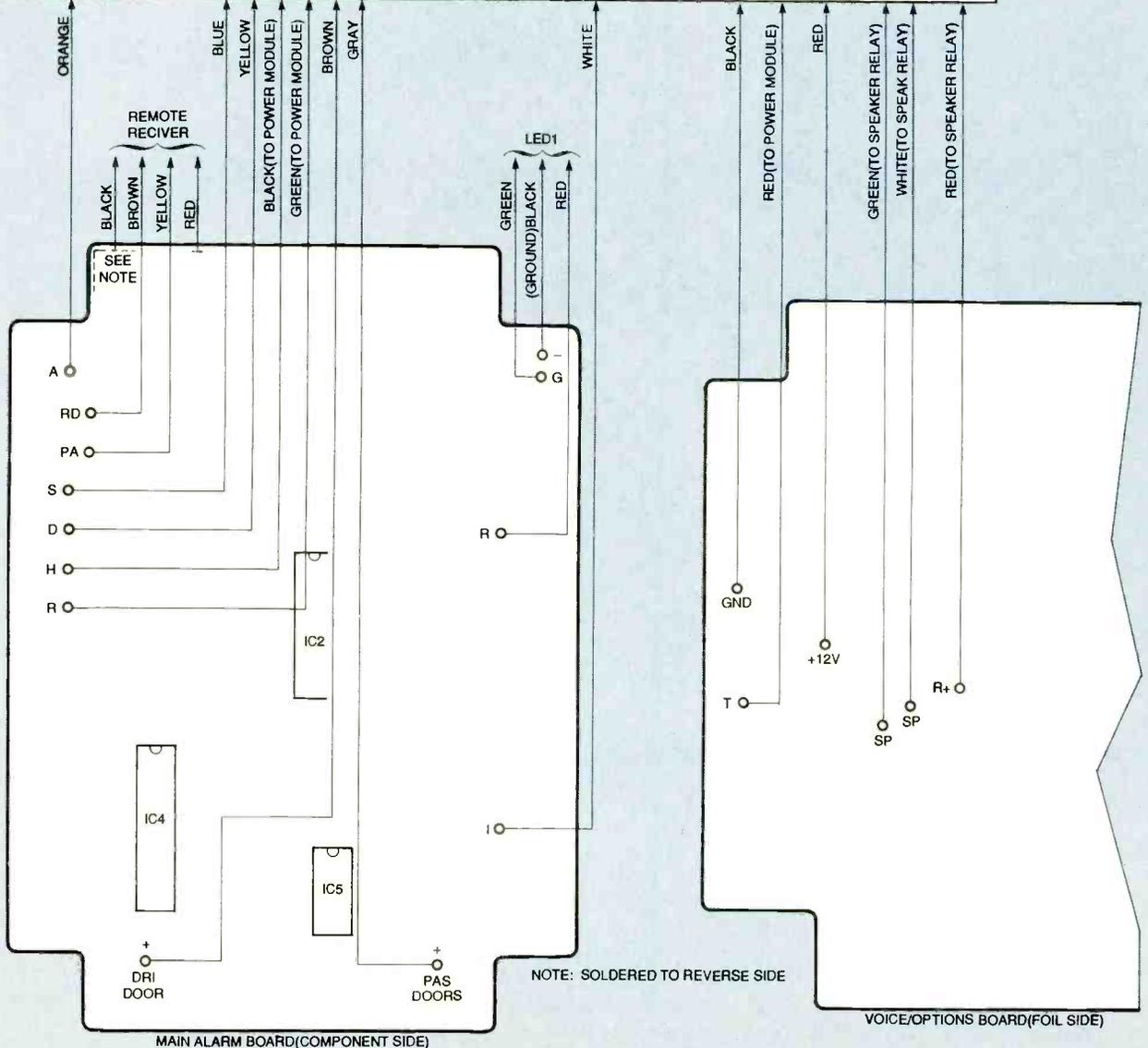

# HARDWARE HACKER

Low-cost TV data displays, thoughts on brain implants, digital sinewave generators, a stunning new radio receiver, and distortion reduction schemes.

DON LANCASTER

I am going to start off by recalling my articles on the subject of television data display. Articles on Hacker TV data displays first appeared in the September 1973 issue *Radio-Electronics* with my *TV Typewriter*. This was followed by *Put the Time on Your TV Screen* in the September 1974 issue starting on page 33. These soon led to the *TV Typewriter Cookbook*, that *Cheap Video Cookbook*, and *Son of Cheap Video*. Sadly, these are long out of print, but I hope to reissue them on CD-ROM someday.

The the fastest, cheapest, and simplest way to put data on a TV screen is with a Commodore C-64 that you should be able to get for about \$30 from a yard or flea market sale. If you want to superimpose data over existing video, the obvious choice is with a *Video Toaster* from *NewTek*, a company that, incidentally, offers some dandy free demo videos.

But *Philips* (formerly *Signetics*) makes the SAA5252 line 21 acquisition and display IC that sells for about \$8. It can superimpose a full screen of first quality data over existing video program material. The circuit shown in Fig. 1 is simple and can be built easily. Unfortunately, advanced hardware, interface and programming skills are required to perform the initial design and debug steps.

For display of custom messages or data, an additional computer source or a companion microcontroller is needed. A PIC microcontroller is ideal for this.

The SAA5252 has several modes: It intercepts existing red, green, and blue video input lines. Then, at your bidding it can do nothing, overlay data, superimpose standard line 21 information, or enhance the line 21 information. Examples include shadowed or rounded characters and several unique dis-

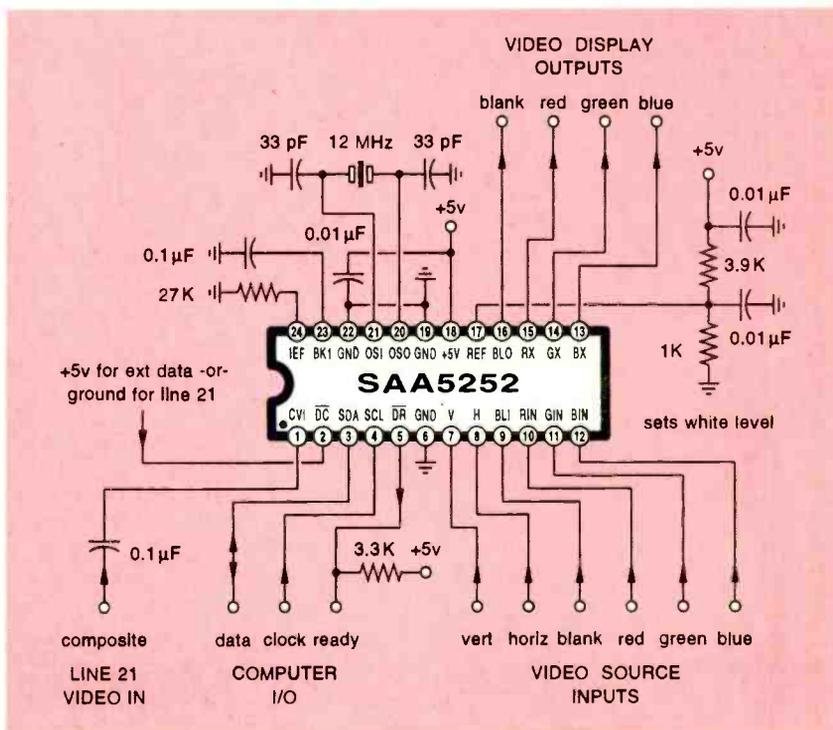


FIG. 1—THIS \$8 TV DATA DISPLAY doubles as a line 21 decoder. The final circuit is simple, but interface and programming skills are required to build and run it.

play modes.

Line 21 services often include hearing impaired or foreign language subtitles. Both fields are selectable when offered. The line 21 information need *not* come from the same source as your final display.

Full genlocking is included. This is done by pre-storing the data. There are 80 characters in its set. Note that "zero" and "oh" share the same \$4F character code. Separate control commands give you seven colors, optional flashing, italics, or an underline. A host computer or local microcontroller inputs data with a pair of *clock* and *data* buses in the usual manner.

Internal control registers set the position, colors, signal polarity, custom data versus line 21, channel selection, and row address. See the Philips data book for the exact command codes to be used.

If any of the horizontal, vertical, or blanking inputs are absent from your video source, add a National Semiconductor LM1881 video sync separator or one of the CD1881s made by Harris Semiconductor. There is a separate or "stand-alone" mode that does not need a computer, but this mode is limited to the stock display of line 21 captions only. Be sure you have the data book on hand before you start using this device. Give me a call if you need any more technical applications help.

## Thoughts on brain implants

My tech helpline receives calls on a wide variety of topics. A surprisingly large number of my callers genuinely believe they have been the unwilling recipients of brain implants. It seems there are even implant support groups and networks. There has been a multi-billion dollar

lawsuit aimed at a big transportation company and a foreign government. The "men in black" and extraterrestrials are sometimes blamed—as are disgruntled divorcees.

The obvious step these folks should take if they believe they have this problem is to see if extended time in a cave can make any difference. Or they can take long-term herbal remedies such as *Ginkgo Biloba* or *CoEnzyme Q10*.

Now, it's easy to dismiss such claims out of hand. But I don't like to discourage people calling me about most off-the-wall topics, regardless of how bizarre they seem—at least not until I find out what "real" science and "real" engineering have to say about the subject. If, after my careful research, the topic obviously becomes a "useful adjunct to porcine cleanliness," then so be it.

Well, the amazing answer is that implants are routinely available as off-the-shelf operations at modest cost. But the most popular models only hold your net worth and Social Security Number. They only measure how hot you are under the col-

### NEED HELP?

Phone or write your Hardware Hacker questions to:

Don Lancaster  
Synergetics  
Box 809-EN  
Thatcher, AZ, 85552  
(602) 428-4073

For fast PSRT access, modem (800) 638-8369. On prompt, enter JOINGENIE. When asked for the keyword, enter DMD524.

Internet email access link:  
SYNERGETICS@GENIE.GEIS.COM.

lar. And they only have a useful range of several inches. Most applications are totally unlicensed and unregulated.

I strongly believe that one of the next major hardware hacking arenas will involve the direct computer-to-brain interface. First and foremost, because direct access offers the prospect of immortality—at least as far as your thoughts and feelings go. Typical used car dealers would gladly pay \$44.95 for a box with three buttons on it that is marked ENTER LOT, BUY, and LEAVE.

Politicians would spring an extra \$10 if the same box had a 100-mile range. Historians would appreciate its "instant replay" features, as would crime investigators. Most medical professionals would definitely welcome new routes towards effective cures.

Especially for addictions.

The more conservative elements of society are bound to be horrified at the prospect of direct personal access to brain pleasure centers. "Press one for psychedelics; two for sex; three for rapture; or four for a coconut-anchovy pizza." This appliance would instantly obsolete most of the more popular forms of entertainment.

Obviously the present problems with direct access include the input/output scheme and understanding the brain's operating system and its instruction set. But there's bound to be a system monitor in there somewhere. It can't be any worse than the Unix operating system. But the solutions to these problems are a lot closer to realization than you think—and clearly solvable.

The leading manufacturer of new

implants is Bio Medic Data Systems. Its DAS series is intended primarily for laboratory animals. The implants are normally located in the animal's back or shoulder, rather than its brain. These have a read, record, and write capability. Stock models can log body temperature. The usual range is normally only a few inches. One major supplier of implantable integrated circuits is Dallas Semiconductor.

Professional and trade journals that report on this subject include *Identification Journal*, *Automatic ID News*, *Access Control*, and *I.D. Systems*. Clearly, the human brain is sure to become the ultimate hack.

### Another contest

For this month's contest, just tell me in 175,000 words or less all the possibilities and consequences of the "real soon now" direct brain access that is almost certainly to occur sooner or later.

There are about a dozen of my *Incredible Secret Money Machine II* books set aside for the better entries, with an all expense paid (FOB, Thatcher, AZ), *tinaja quest* going to the very best of all. Entries must be written and sent to me here at *Synergetics*.

### Sinewaves—old and new

A new algorithm for generating digital sinewaves showed up in the December 1994 *Byte* on pages 217 to 218. This is one of the finest examples of elegant simplicity I have ever seen. Amazingly, it takes only two registers and six bytes of working eight-bit code to set up the PIC micros!

I have repeated *Byte's* algorithm in Fig. 2, and included some simple PostScript code which will let you interactively explore, model, analyze, or plot this new sinewave scheme. This method is extremely attractive for use in one of many small microcontrollers.

Before I explain the details, I think it would be a good idea to review some of the standard methods for generating sinewaves. I've long been both a student of and developer of sinewave sources.

In the *bandpass filter* method, you wrap an amplifier with unity loop gain around a resonant coil and ca-

## NEW FROM DON LANCASTER

### HARDWARE HACKING

Incredible Secret Money Machine II	18.50
The Case Against Patents	28.50
Hardware Hacker Reprints II, III, or IV	24.50
Blatant Opportunist Reprints	24.50
Resource Bin Reprints	24.50
Ask The Guru Reprints I, II or III	24.50
CMOS Cookbook	24.50
TTL Cookbook	24.50
Active Filter Cookbook	24.50
Micro Cookbook I	19.50
Lancaster Classics Library	119.50

### POSTSCRIPT STUFF

PostScript Secrets (Ile/Mac/PC)	29.50
Book-on-demand resource kit	39.50
Intro to PostScript VHS Video	29.50
PostScript Beginner Stuff	29.50
PostScript Show & Tell	29.50
PostScript Cookbook (Adobe)	19.50
PostScript Ref. Manual II (Adobe)	32.50
PostScript Program Design (Adobe)	24.50
Type I Font Format (Adobe)	15.50
Acrobat Reference (Adobe)	24.50
LaserWriter Reference (Apple)	19.50
PostScript by Example (McGilton)	29.50
Pgm Display PostScript with X	29.50
PostScript Visual Approach (Smith)	22.50
Thinking in PostScript (Reid)	22.50
Undst PS Pgrmmg (Holtzgang)	29.50
The Whole Works (all PostScript)	379.50

FREE VOICE HELPLINE

VISA/MC

## SYNERGETICS

Box 809-RE  
Thatcher, AZ 85552  
(602) 428-4073

CIRCLE 205 ON FREE INFORMATION CARD

pacitor. If you tap the coil for feedback, you have a *Hartley* (or "hardly") circuit for your oscillator. Tap the capacitor instead, and you'll end up with a *Colpitts* (or "pole-cats") circuit.

A *Wein Bridge* includes an RC network that can be considered as overlapping highpass and lowpass filters. Put just enough gain around this one, and you get a sine wave out. For "just enough" gain, you will need some kind of amplitude stabilization scheme. This could be the nonlinear resistance of a pilot incandescent lamp.


Almost any repetitive waveform consists of a fundamental sine wave and several harmonics. With the *filter* method, you generate a waveform and then pass the output through a lowpass or bandpass filter to extract the fundamental wave. Starting with symmetric waveforms gets rid of all the even harmonics—particularly that troublesome second harmonic.

While square waves are an obvious starting waveform, the third harmonic is a horrific 0.33 of the fundamental. It is only 10 decibels down. A triangle wave's third harmonic is only 0.11 of the fundamental, and it can be a lot easier to process. Filtering can become tricky very rapidly if the frequency shifts significantly.

Those *triangle game* methods all start with a triangular wave that you play around with. If you softly clip the "points", you'll get a sine wave out. Or, you can add a new triangle wave that has three times the frequency and 1/9th the amplitude to cancel out the original third harmonic. It will leave that easily processed fifth harmonic at 1/25th down.

The horribly obsolete *breakpoints* method is related to triangle games. It constructs an analog sine wave with straight-line approximations.

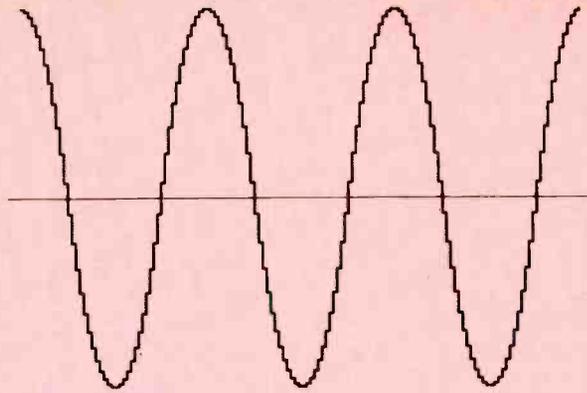The *double integrator* seems the purest form of sine wave generator. Start with any waveform "S," add up, or continuously integrate the area under "S" to produce a new waveform "C". Then integrate "C" and invert it. Make this inverted and integrated "C" output your "S" input, and you've got yourself a pure sine wave.



#### THE ALGORITHM:

1. Initialize a SIZE stash to a magic value.
2. Initialize a SPEED stash to zero.
3. If SIZE is positive, decrement SPEED. If SIZE is negative, increment SPEED.
4. Add SIZE to SPEED to get the new SIZE.
5. Use your digitally generated sine wave.
6. Repeat steps 3-5 as required.

#### POSTSCRIPT DEMO:

```
% Draw a 48 step digital sine wave...
200 300 translate           % set position on page
/steps 48 def              % set steps per cycle
/size 72 def               % set zero to peak size
/speed 0 def              % initialize speed
0 size moveto             % move to starting point
1 1 size {                % start a for loop
  /val exch store         % save position
  /speed speed size 0 gt {-1}{+1} % do the algorithm
  /size size speed add store
  1 0 rlineto            % draw horizontal step
  val size lineto       % draw vertical step
} for                    % complete loop
stroke showpage          % draw it and print it
```

**FIG. 2—AN AMAZINGLY COMPACT AND EFFICIENT digital sine wave generator. Only six machine language bytes are needed. When magnified, the fattened waveshape reveals a 4% distortion.**

Guaranteed results.

Why does this happen? Because you just set up a big, old, *differential equation* whose solution is always a pure sine wave. And "S," stands for the *sine*. And "C" for the quadrature (90° phase-shifted) *cosine*. This method is often called the *analog computer* method.

There is more on the double integrator in my *Active Filter Cookbook*. One of the variations on this is

known as a *state variable filter*.

All of these sine waves can be generated by analog or digital methods. The advantage of digital methods is that they offer frequencies that are both stable and easily changed. They can be instantly swept with ease, usually without any nasty transients.

Moreover, no large, costly, and field-sensitive coils are needed. Amplitude is easily controlled and

inherently stable. In addition, distortion products and phase are precisely known. Today, digital methods are accomplished by smaller, cheaper, better, and lower powered circuits.

The *walking ring* is an example of an older but still rather elegant hybrid sinewave generator. Connect a walking-ring counter and some carefully selected summing resistors to *all but one* of those output phases. Introduce a digital clock signal and the output is an analog sine-wave with surprisingly low distortion. The full details of this are in my *CMOS Cookbook*.

*Table lookup* is the most popular "pure" digital methods in use today. Start with a direct input signal or an up-down counter and route the signal to an EPROM or other read-only memory that looks up the sine of

the counter state representing the present angle. This method is very fast, but it requires a lot of memory for reasonable accuracy. Certain symmetry and interpolation tricks can be used to ease the memory requirement.

A frequency synthesizer can use a *phase accumulator*, which is just a phase adder in front of one or more lookup tables.

Almost any waveform can be represented by a *power series*. For instance, the cosine of  $x$  can be calculated by:

$$1 - x^2/2! + x^4/4! + \dots$$

For angles up to about 60°, you need only the square term. But more terms will be needed for higher angles. The power series calculations take time and have precision limits. Variations on these power series methods are applied in most

#### THE ALGORITHM:

1. Initialize a SIZE stash to magic value #1.
2. Initialize a SPEED stash to zero.
3. Select a magic value #2 for CLIP.
4. If SIZE is positive, decrement SPEED.  
If SIZE is negative, increment SPEED.
5. Set FIX to SPEED.  
If FIX > +CLIP, then FIX = +CLIP  
If FIX < -CLIP, then FIX = -CLIP
6. Add SIZE to FIX to get the new SIZE.
7. Use your digitally generated sinewave.
8. Repeat steps 4-7 as required.

#### A POSTSCRIPT UTILITY:

```
% Calculate a 48 step low distortion digital sinewave...
/steps 48 def % set steps per cycle
/size 64 def % set zero to peak size
/speed 0 def % initialize speed
/clip 8 def % initialize clip
1 1 size { % start a for loop
  /val exch store % save position
  /speed speed size 0 gt {-1}{+1} % start the algorithm
  ifelse add store
  speed dup clip gt % clip a copy of speed
  {pop clip} ifelse
  speed dup clip neg lt
  {pop clip neg} ifelse
  /size exch size add store % finish the algorithm
  % use your sinewave here
} for % complete loop
```

## NAMES AND NUMBERS

### Access Control

6151 Powers Ferry Rd NW  
Atlanta GA 30339  
(404) 955-2500

### Amateur Seismologist

2155 Verdugo Blvd #528  
Montrose CA 91020  
(818) 249-1759

### American Laboratory

30 Controls Drive  
Shelton CT 06484  
(203) 926-9300

### Antique Automobile Radio

700 Tampa Road  
Palm Harbor FL 34683  
(800) 933-4926

### Antique Radio Classified

PO Box 802  
Carlisle MA 01741  
(508) 371-0512

### Automatic ID News

7500 Old Oak Blvd  
Cleveland OH 44130  
(216) 243-8100

### Bio Medic Data Systems

255 W Spring Valley Avenue  
Maywood NJ 07607  
(800) 526-2637

### Jim DuBois

330 State Road 101  
Amherst NH 03031  
(603) 673-3645

### GENie

401 N Washington St  
Rockville MD 20850  
(800) 638-9636

### GeoSpace

7334 N Gessner  
Houston TX 77040  
(713) 939-7093

math coprocessor circuits. Sinewaves can be related to exponentials and similar functions. The details can become complex rapidly. There is also the obscure and slow *rate multiplier* scheme for generating digital sinewaves, but it is no longer widely applied.

### The new method

My reaction when I first saw the code was "That can't work!" There simply can *not* be any overlooked fundamentally new sinewave method today. That would be about the same as discovering a new trigonometric identity.

However, it turned out that what I

FIG. 3—A LOW DISTORTION VARIATION that requires a few more bytes. The third harmonic might be eliminated completely.

#### Handmade Electronics

1825 Roth Ave  
Allentown PA 18104  
(610) 432-5732

#### Horn Speaker

PO Box 1193  
Mabank TX 75147  
(903) 848-0304

#### ID Systems

174 Concord St  
Peterborough NH 03458  
(603) 924-9631

#### Identification Journal

2640 N Halsted St  
Chicago IL 60614  
(312) 528-6600

#### National Semiconductor Corp.

2900 Semiconductor Rd  
Santa Clara CA 95052  
(800) 272-9959

#### NewTek

1200 SW Executive Dr  
Topeka KS 66615  
(800) 847-6111

#### Microchip Technology

2355 W Chandler Blvd  
Chandler AZ 85224  
(602) 963-7373

#### RF Design

6300 S Syracuse Wy #650  
Englewood CO 80111  
(303) 220-0600

#### Philips

PO Box 3409  
Sunnyvale CA 94088  
(408) 991-2000

#### AG Tannenbaum

PO Box 110  
E Rockaway NY 11518  
(516) 887-0057

really have here is an extremely fast and compact (but slightly flawed) variation on the double integrator method. You can view it as a *numeric sequence generator* that happens to trace out a waveform that's roughly similar to a real sine-wave.

Take an eight-bit stash and call it *size*. Take a second eight-bit stash and call it *speed*. Select a magic initial value for *size*: 0.72 will do. Set *speed* to zero. Now apply the following rules:

- If *size* is positive, *decrement* the *speed* value.
- If it is not, *increment* the *speed* stash.

- Finally, add *speed* to *size* to find the new *size* value.

This method does *not* generate a true sine-wave. Rather, it creates a "partially hydrogenated" cosine wave with a little extra fat on its leading edges.


Out of the box, your third harmonic distortion is typically in the 4%. This might or might not be acceptable. Four percent just barely shows up on a graphic plot, but its harshness is easily spotted when you listen to it as audio. Many applications cannot tolerate this level.

Thankfully, there are zero even harmonics. Often, there will be zero DC offset. This distortion is caused by the fact that *speed* is supposed to be a cosine wave, and the algorithm.

#### Improving it

I could not leave well enough alone. This beast is highly obsessive, like the old shop joke of one machinist drawing out the world's thinnest wire. Well, the second machinist then drilled the world's smallest hole down through

# WAVE GOODBYE TO PRICEY TEST EQUIPMENT

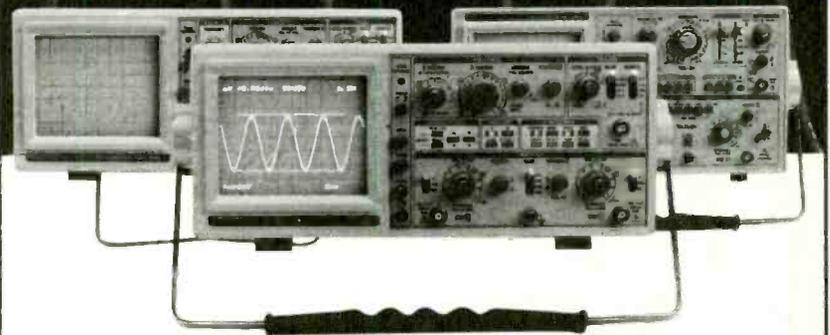

GoldStar offers a comprehensive line of affordable Analog and Digital Storage Oscilloscopes for your diagnostic needs.

- Signal Delay Lines
- Variable Holdoff
- TV Sync
- Max. Sweep Time of 2ns/div.

Digital Storage with CRT Readout and Cursor Control	Analog CRT Readout and Cursor Control	Analog
OS-3020: 20 MHz, 20 MS/s OS-3040: 40 MHz, 20 MS/s OS-3060: 60 MHz, 20 MS/s	OS-902RB: 20 MHz, Delayed Sweep OS-904RD: 40 MHz, Delayed Sweep	OS-9020A: 20MHz, Basic OS-9040D: 40MHz, Delayed Sweep OS-9060D: 60MHz, Delayed Sweep OS-8100A: 100MHz, Delayed Sweep OS-9020G: 20MHz with 1MHz Function Generator

Don't forget the other sensibly priced instruments available from GoldStar (Sweep Function Generators, Frequency and Universal-Counters, Bench Power Supplies, and Bench and Handheld-Digital Multimeters).



## GoldStar Precision

The Sensible Source

13013 East 166th St., Cerritos, CA 90701 310-404-0101 fax: 310-921-6227

CIRCLE 199 ON FREE INFORMATION CARD

it. Finally, of course, the third machinist tapped that hole.

It turns out there is a simple way to dramatically reduce the distortion. You might completely eliminate the third while significantly reducing the rest of them. All those higher odd harmonics are usually easy to filter out. Of course, this might be at the cost of speed and code length. Exact details will vary with the implementation selected.

Once again, the cause of all the original distortion is the generation of a triangle wave, which is called a cosine wave. Admittedly, real cosines become difficult to deal with when you are only allowed to use six bytes worth of small integers. But if you chop the top and bottom off the triangle, you can get a lot closer to perfection. This is shown in Fig. 3.

Any repetitive waveform can be

analyzed by *Fourier Series* techniques. The general purpose PostScript language is ideal for this analysis. I'll discuss the details in another column. However, Fig. 4 reveals several magic amplitude and distortion values for both algorithm versions.

If a DC offset is present in the listed values, it's half a step one way or the other. Capacitor coupling can eliminate this, when permitted.

Note that *none* of the 128 or higher amplitude sequences can be realized as single eight-bit words. Because of state zero and negative values, 257 or more states are involved. PostScript, of course, handles those higher values with ease and aplomb. There are several other possible amplitudes. These either have extra DC in their outputs or worse distortion is present.

I am fairly certain I've shown all possible eight-bit steps-per-cycle values. These are just four times the maximum unclipped *speed* values. An ultralow distortion variant is shown in Fig. 5. It offers a low 0.24% distortion, and most of that is easily filtered seventh harmonic.

But this takes a few extra bytes of code and has limited sets of useful values. Moreover, There is an aesthetically unsatisfactory wrinkle in the sine plot as well. In one variation, the fifth is 62 dB down—before any filtering!

A much more detailed analysis, full sequences, and ready-to-run code appears in my files `FOURIER.PS` and `NEWSINE.PS` on *GENie PSRT*. The *Golly Gee Mister Science* tinaja questing society has just announced its award for the best data book rear cover. The award goes to Philips for the latest update of its *Desktop Video Data Handbook*.

Philips also has the best front cover, by far. Moreover, the inside of the book ain't half bad either. This gem is crammed full of neat products on digital TV, teletext for video capture, sync generators, and color coders.

### New tech Literature

Also from Philips are new editions of its *Audio/Radio*, and *Wireless* data handbooks. From *Analog Devices*, there is the incredibly fat new *Design-In Reference Manual*.

There is a fascinating article on *molecular* computers based on DNA strands in the November 11, 1994 issue of *Science*, pages 993 and 1021 to 1023. One of the problems solved by this DNA computer was the determination of an optimum route for a traveling salesman between a number of cities.

The problem was solved a thousand times faster than it could be solved on the the best existing supercomputer. The biological computer needs only a fraction of the space and energy of a supercomputer. The secret lies in using *billions* of parallel molecular coprocessors.

A mind-boggling breakthrough in micropower receivers is described in the December, 1994 *R. F. Design*. Look for it on pages 32 to 44. These receivers easily extend the max-

steps per cycle	peak amplitude	clipping level	dc offset present?	3rd harm. distortion	total harm. distortion
8	2	none	no	5.74%	9.76%
12	4	2	no	0%	2.72%
12	5	none	yes	4.92%	5.32%
16	8	3	yes	1.79%	2.18%
16	8	none	no	4.33%	4.65%
20	10	3	yes	1.56%	2.11%
20	12	none	yes	4.09%	4.29%
24	16	4	no	0%	1.08%
24	20	none	no	3.96%	4.12%
28	22	5	yes	0.96%	1.25%
28	24	none	yes	3.89%	4.03%
32	28	5	yes	0.90%	1.42%
32	32	none	no	3.84%	3.98%
36	36	6	no	0%	0.94%
36	40	none	yes	3.8%	3.94%
40	46	7	yes	0.67%	1.03%
40	50	none	no	3.79%	3.81%
44	52	7	yes	0.63%	1.19%
44	60	none	yes	3.81%	3.89%
48	64	8	no	0%	0.90%
48	72	none	no	3.77%	3.88%
56	76	9	yes	0.51%	0.94%
56	84	none	yes	3.76%	3.87%
56	86	9	yes	0.49%	1.08%
56	98	none	no	3.75%	3.86%
60	100	10	no	0%	0.88%
60	110	none	yes	3.74%	3.85%
64	116	11	yes	0.41%	0.91%
64	128	none	no	3.74%	3.84%
68	126	11	yes	0.41%	1.02%
68	138	none	yes	3.76%	3.84%

FIG. 4—DATA VALUES for the more interesting and useful digital sinewave generators. Both "regular" and "low-distortion" schemes are shown.

% Copyright c 1995 by Don Lancaster and Synergetics, Box 809, Thatcher, AZ,  
 % 85552. (602) 428-4073. All commercial and all media rights fully reserved.  
 % Personal use permitted so long as this header remains present and intact.

% Variation #1 has 60 steps per cycle and a 96 peak amplitude.  
 % The DC term and harmonics 2,3,4,6,8,9,10, and 12 are ZERO!  
 % The fifth harmonic distortion is 0.061%. Total distortion is 0.342%.

```
/size 96 def
/speed 0 def
0 1 60 {
    /val exch def
    /speed speed size 0 gt {-1}{+1} ifelse add store
    /size size speed dup 10 eq {pop 6} if dup -10 eq {pop -6} if
    dup 10 gt {pop 10} if dup -10 lt {pop -10} if add store
    % use your sinewave here
} for
```

% Variation #2 has 60 steps per cycle and a 97 peak amplitude.  
 % The DC term and harmonics 2,3,4,6,8,9,10, and 12 are ZERO!  
 % The fifth harmonic distortion is 0.162%. Total distortion is 0.247%.

```
/size 97 def
/speed 0 def
0 1 60 {
    /val exch def
    /speed speed size 0 gt {-1}{+1} ifelse add store
    /size size speed dup 10 eq {pop 7} if dup -10 eq {pop -7} if
    dup 10 gt {pop 10} if dup -10 lt {pop -10} if add store
    % use your sinewave here
} for
```

% Variation #3 gives you 48 steps per cycle and a 62 peak amplitude.  
 % The DC term and harmonics 2,3,4,6,8,9,10, and 12 are ZERO!  
 % The fifth harmonic distortion is 0.149%. Total distortion is 0.241%.

```
/size 62 def
/speed 0 def
0 1 48 {
    /val exch def
    /speed speed size 0 gt {-1}{+1} ifelse add store
    /size size speed dup 8 eq {pop 6} if dup -8 eq {pop -6} if
    dup 8 gt {pop 8} if dup -8 lt {pop -8} if add store
    % use sinewave here
} for
```

FIG. 5—ULTRALOW DISTORTION digital sinewaves depend on black magic.

imum range for legal and unlicensed transmitters to 1000 feet and beyond.

The secret to this tuned radio frequency (TRF) variant is two cascaded, high-gain, radio-frequency amplifiers; *only one of them is switched on at any time!* Its performance greatly exceeds the best of the superregenerative receivers or single conversion superhetrodyne receivers. Moreover, there are zero radiation and image problems.

The *Amateur Seismologist* offers low-cost earthquake detectors and personal computer support software. Professional geophones are available from *GeoSpace*.

Outstanding buys for precision CAD/CAM steppers, X-Y tables,

and similar bits and pieces are offered by *Jim DuBois*. His stock is mostly one-of-a-kind used and surplus products.

Here are some more antique radio resources: The *Horn Speaker* is a new labor-of-love tabloid alternative to *Antique Radio Classified*. Hard-to-find classic repair manuals and *Photofacts* are offered by *A. G. Tannenbaum*. He also stocks, wonder of wonders, 1945 edition *Radiotron Designer's Handbooks* at \$15.

Replacement automobile radio vibrators are offered by *Antique Automobile Radio*, while audio vacuum-tube components are sold by *Handmade Electronics*.

The secrets to starting your own



**CRYSTAL-CONTROLLED! 5 MINUTE ASSEMBLY! MONEYBACK GUARANTEE!** Attach 3 wires and hear every whisper up to 2 miles away on any programmable scanner or VHF surveillance receiver. Pre-tested surface mount module uses standard 9V battery for 100mW output! Includes battery box and crystal for 140MHZ. Custom frequencies available for Law Enforcement. Model VX-100 only **\$79.95 + 2.00 S&H. VISA, MC, MO. COD add \$5.00. DECO INDUSTRIES, BOX 607, BEDFORD HILLS, NY 10507. 914-232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD

## CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$1,000.00 each insertion.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call **516-293-3000** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, ELECTRONICS NOW, 500-B Bi-County Blvd., Farmingdale, NY 11735.

**FAX: 516-293-3115**

technical venture appear in my *Incredible Secret Money Machine II*. See my nearby *Synergetics* ad. I've also accumulated a large stock of classic Apples computers and replacement parts. They are cheap enough for use as dedicated controllers. Write, E-mail, or call me for a complete listing.

Here is a reminder that unique downloads, freebie insider secrets, catalogs, and technical help are available on *GENie* PSRT. A ten-hour free trial offer is available if you sign up with a credit account; see my *Need Help?* box.

As usual, most of the resources I've mentioned appear in the *Names & Numbers* sidebar. Be sure to check this sidebar first before calling our no-charge tech helpline.

Let's hear from you.

# DRAWING BOARD

A couple of "old" circuits, and a brand new topic.

ROBERT GROSSBLATT

I've been getting a lot of mail about a series of columns I did on video and video descrambling. When the series was reprinted, a gates-only way of decoding the magic line numbers (24 and 257) was omitted. When I was doing the series, I showed how to decode those lines with an EPROM and, several months later, published two schematics sent in by readers who had done the same thing using gates.

In the spirit of completeness, I'm going to reprint these here and, once again, give credit where credit is due.

The first circuit, from David Siegel of Livonia, Michigan, is shown in Fig. 1. It's a pretty slick design. The second decoder is from Chris Carson of Ottawa, Ontario. His design is a bit more complicated, as you can see in Fig. 2. One nice feature is that only one pin is used for the line indicator. This is handy if you want the rest of your descrambler to have the start and end of the vertical interval to be indicated on a single line.

The descrambling series was never intended as a construction article for a working SSAVI descrambler. Instead, it was meant to be a starting point for experimentation and for those who want to understand video scrambling techniques. Different cable companies use different variations on the basic scheme. In New York City, for example, there are two cable companies, both owned by the same parent company Time-Warner. While the scrambling method for each is similar, they differ in how they invert the video. The video scrambling you encounter will undoubtedly be different.

## Audio

Regular readers might remember that I've mentioned several times

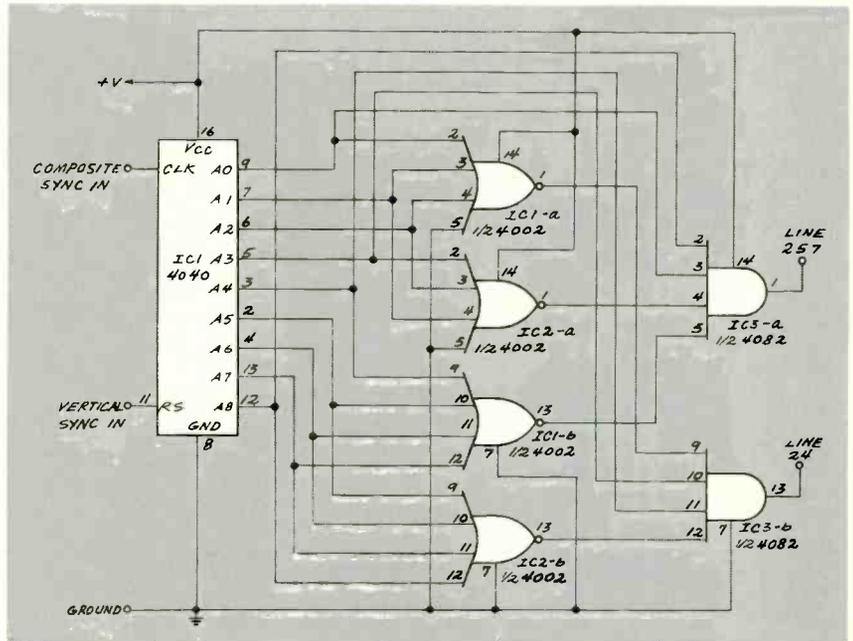


FIG. 1—THIS CIRCUIT WILL DECODE line numbers 24 and 257.

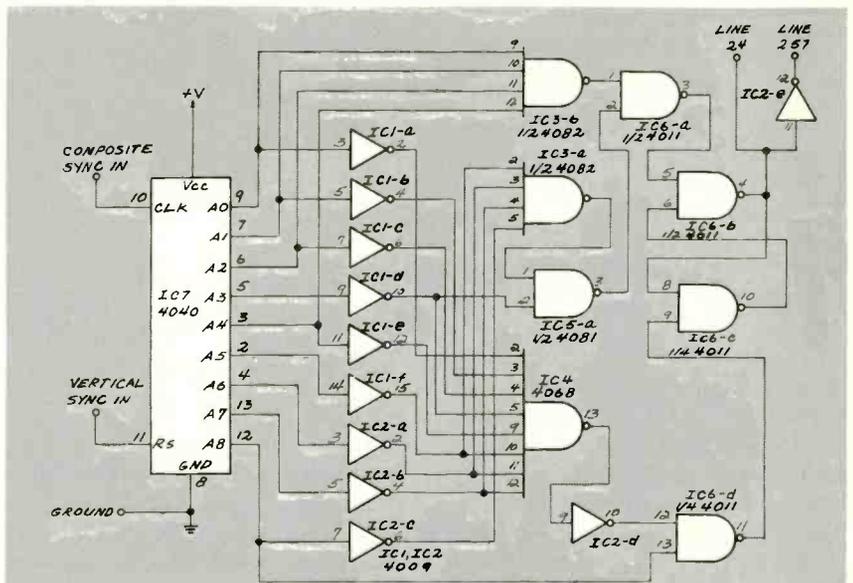


FIG. 2—ANOTHER LINE DECODER. This one uses only one pin for the line indicator.

that I have a house in the country. Now, I'm not going to say where it is, but I will tell you that the winters up there are really cold and, since we go up nearly every weekend, winter weekends are usually indoor week-

ends. I like to have some project to work on, and my latest one is to wire the house for sound. I thought this would be simple to do, but I should have known better.

Continued on page 91

THIS THIRD ARTICLE IN A SERIES ON active filters focuses on audio signal processing and amplitude control circuits. The last article, in the February 1995 issue of *Electronics Now*, page 65, discussed popular passive control networks including high- and low-pass filtering circuits. This article picks up where that article left off with a discussion of active tone-control circuits, and it goes on to explain amplitude-regulating circuits.

**Active tone controls**

An active tone-control circuit can be made by connecting a passive tone-control network to the negative feedback loop of a linear amplifier, typically an operational amplifier. This circuit provides signal gain rather than attenuation.

Tone-control networks can be simplified versions of Fig. 15 in the February 1995 article. However, they are more likely to be based on the alternative passive tone-control circuit shown here as Fig. 1. This circuit's performance is comparable, but requires fewer components, and it includes two linear control potentiometers.

If the input signals to the circuit in Fig. 1 are low enough so that capacitors C1 and C2 act like open circuits, the output signal amplitudes are controlled entirely by resistor R5. This occurs because resistor R6


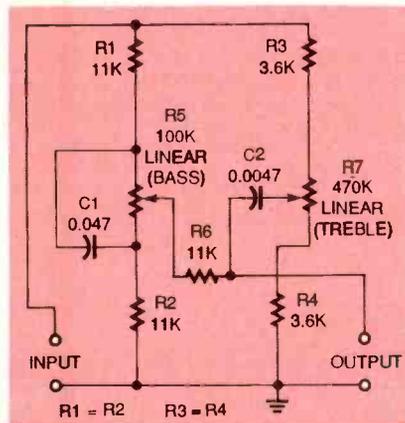


FIG. 1—ALTERNATIVE TONE-CONTROL circuit that includes two potentiometers.
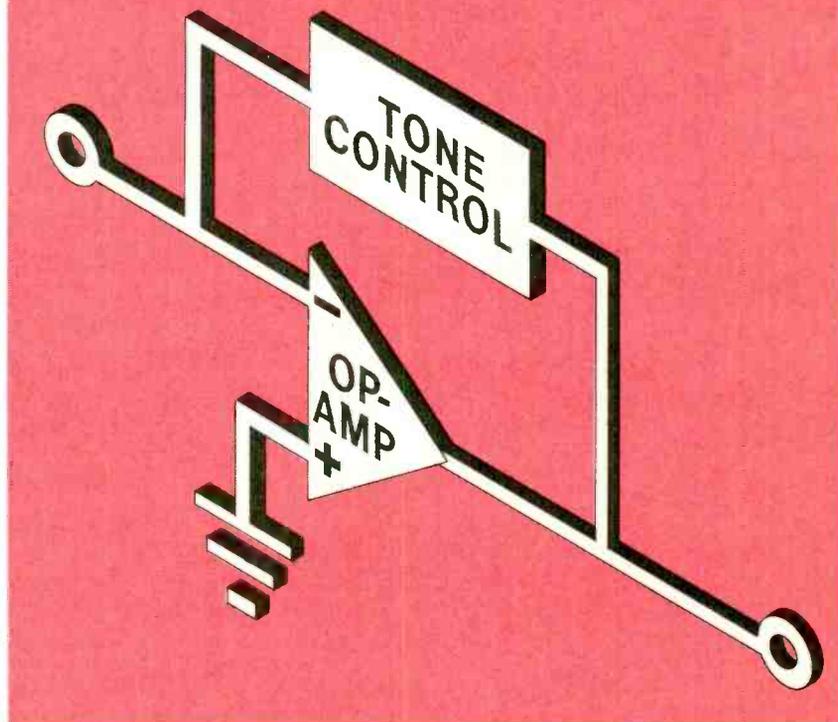
# ACTIVE AUDIO FILTERS for Signal Processing and Control



**Learn about active filters in audio signal processing and control, and apply that knowledge to your circuit designs**

is isolated from the output by capacitor C2.

However, at input frequencies that are high enough so that the two capacitors act like short circuits, the output signal amplitudes are controlled entirely by resistor R6. In this situation, resistor R5 is short circuited by C1.

The low-frequency (*bass*) circuit cutoff is determined by the values of R1 and C1, and the high-frequency (*treble*) cutoff is determined by C2 and the values of R1 to R3.

Figure 2 illustrates how the network in Fig. 1 network is integrated into an active tone control circuit that can provide up

to 20 decibels (dB) of boost or cut to bass or treble signals.

The circuit shown in Fig. 3, although similar to that of Fig. 2, is more versatile. It has an additional filter control network that is centered on the 1-kHz *midband* of the audio spectrum. This network permits the midband to be boosted or cut by as much as 20 dB.

**Graphic equalizers**

The more sophisticated graphic equalizer tone-control system consists of a many parallel-connected, variable-response filters that overlap and have narrow-passbands to cover the entire audio spectrum. This cir-

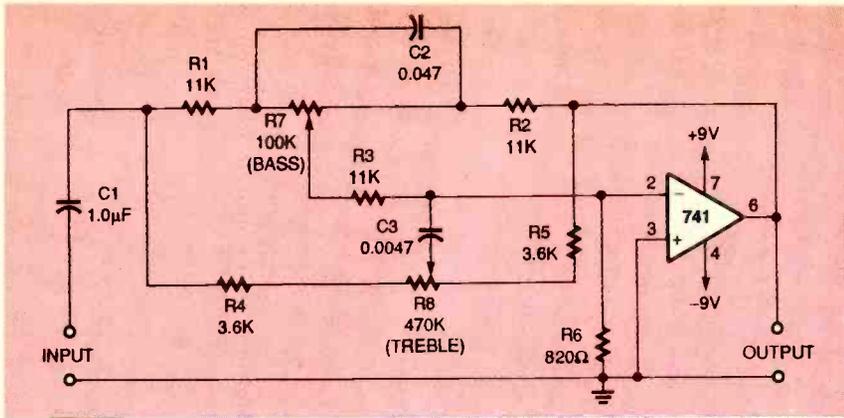


FIG. 2—ACTIVE TONE-CONTROL CIRCUIT that includes the Fig. 1 circuit.

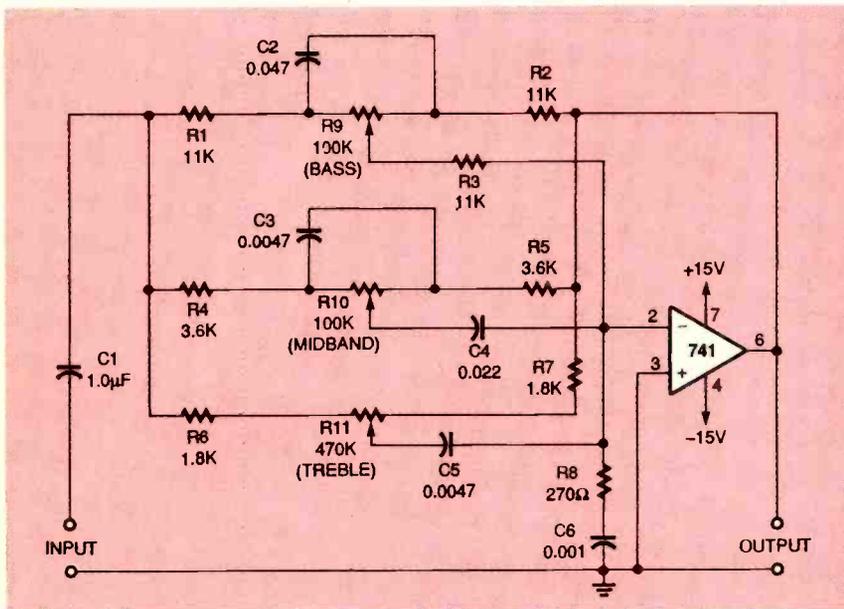


FIG. 3—THREE-BAND ACTIVE TONE-CONTROL control (bass, midband, treble).

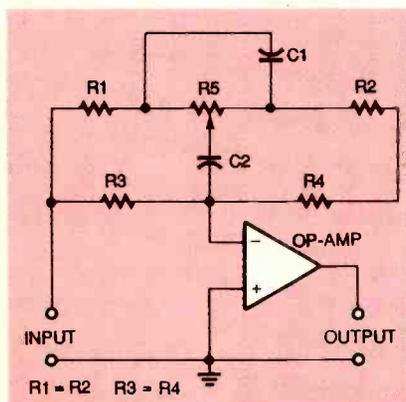


FIG. 4—TYPICAL OCTAVE (GRAPHIC) equalizer section.

cuitry permits tailoring an amplifier circuit's spectral response to suit individual needs. The filter center frequencies are typically spaced at one octave intervals. As a result, those systems are also called *octave*

*equalizers*.

Figure 4 is the schematic for a typical octave (graphic) equalizer section. It is similar to the active tone-control circuit shown in Fig. 2, except that *treble control* network consisting of C2, R3, and R4 is fixed rather than variable, and the bass and treble cutoff frequencies are spaced closely. As a result, the two response curves overlap.

Consequently, the circuit in Fig. 4 circuit acts as a narrow-band filter with a center frequency response that is fully variable between +12 dB (full boost) and -12 dB (full cut) by adjusting potentiometer R5.

Figure 5 shows how the circuits of Figs. 3 and 4 are interconnected to form a high quality, ten-band graphic equalizer. The ten equalizer sections

are in parallel, and their outputs are summed in the output stage that includes the IC11 operational amplifier.

The operational amplifiers in this circuit can be the industry-standard LM741 or comparable dual versions such as the LM747. Stereo amplifier systems visually contain two complete circuits of the kind shown in Fig. 5.

### RIAA equalization

Phonograph records are no longer the preferred media for storing and reproducing music, having been replaced years ago by tape cassettes and compact discs (CDs). Nevertheless, many people still own turntables for playing 33 RPM long-playing record (LPs) or 45 RPM records. The pickup arms of those record players include either ceramic, crystal, or magnetic cartridges and needles that are in direct contact with the grooves in the records.

The ceramic and crystal cartridges were inexpensive, but they produced large-amplitude and fairly linear outputs suitable for low-priced record players. However, magnetic cartridges were preferred for high-performance, high-fidelity stereo systems. Although their output is low, and they have nonlinear frequency response characteristics, their corrected output provides more faithful music reproduction.

The characteristics of any record playback system can be determined with a test record containing a three-decade span of sinewave tone signals with constant amplitude from 20 Hz to 20 kHz. A quality magnetic cartridge should generate a nonlinear frequency response that rises at a rate of 6 dB per octave (equal to 20 dB per decade). Thus the output signals would be weak at 20 Hz, but would be one thousand times greater (equal to +60 dB) at 20 kHz.

This nonlinear frequency response is an inherent characteristic of all magnetic pickups because their output voltage is directly proportional to the pickup needle movement rate

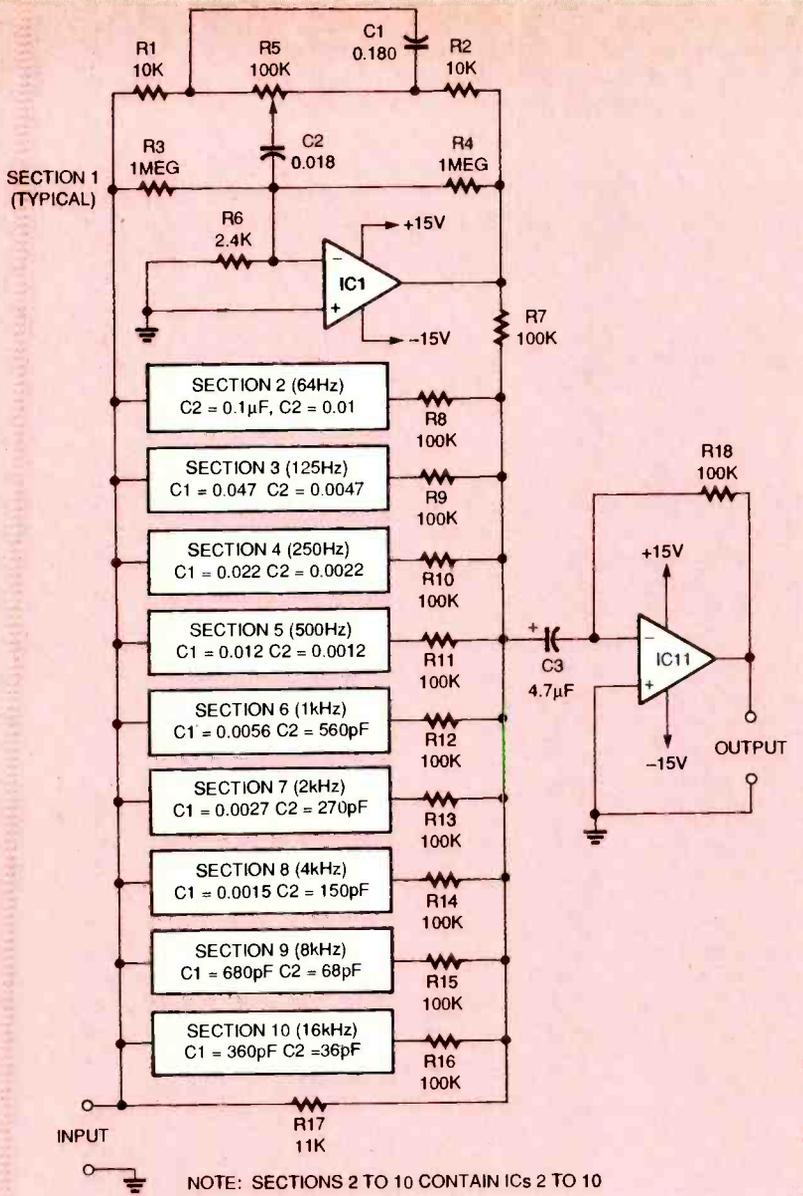


FIG. 5—TEN-OCTAVE (GRAPHIC) equalizer circuit.

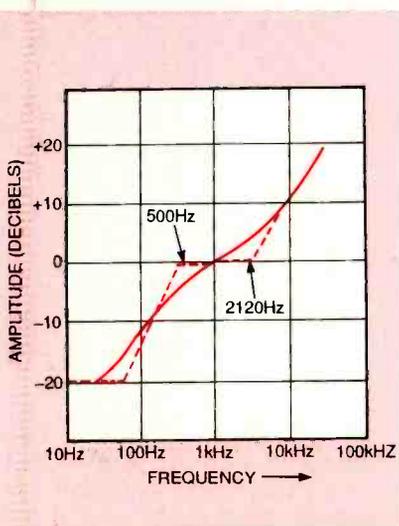


FIG. 6—TYPICAL PHONOGRAPH record playback frequency response curve.

which, in turn, is proportional to recording frequency.

Phono disk recording equipment usually did not provide truly linear frequency response. To enhance the effective dynamic range and signal-to-noise ratio of records, frequencies below 50 Hz and those in the 500-Hz to 2.12-kHz midband range were recorded nonlinearly in accordance with a standard curve defined by the Recording Industry Association of America (RIAA).

This nonlinearity causes a midband drop of 12 dB when the record is played through linear-response ceramic or crystal pickups, but this decrease was too small to be objectionable in

most low-end record players.

Figure 6 shows a plot of a typical phonograph record playback frequency response curve as a solid line and dotted line superimposed on the solid line that represents the ideal response curve. The ideal (dotted-line) curve is flat to 50 Hz where it rises at a 6 dB/octave rate to 500 Hz. It remains flat from 500 Hz to 2120 Hz, then rises again at a 6 dB/octave rate to about 20 kHz.

When a record is played through a magnetic pickup in a high quality hi-fi system, the output of the pickup is pre-amplified before going to the power amplifier. The pre-amplifier must have a frequency equalization curve that is the exact inverse of that shown in Fig. 6, so that an overall linear response is obtained. Figure 7 shows the RIAA equalization

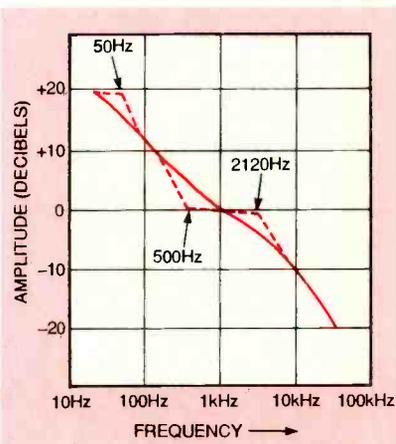


FIG. 7—RIAA PLAYBACK equalization curve.

curve. It is the inverse of recording curve shown in Fig. 6.

### RIAA preamplifier

Magnetic pickup cartridges are low-sensitivity devices that give typical midband outputs of only a few millivolts. Consequently, their output signals must be preamplified by a dedicated, low-noise preamplifier integrated circuits rather than general-purpose operational amplifiers. A schematic for a preamplifier with integral RIAA magnetic-pickup equalization is shown in Fig. 8. The circuit includes an LM381 low-noise, dual preamplifier IC.

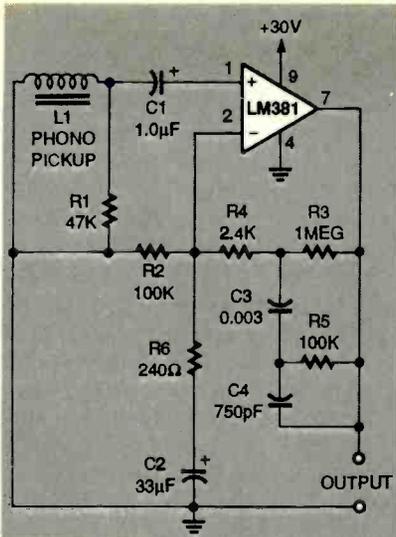


FIG. 8—LOW-NOISE MAGNETIC phono cartridge preamplifier that includes RIAA equalization.

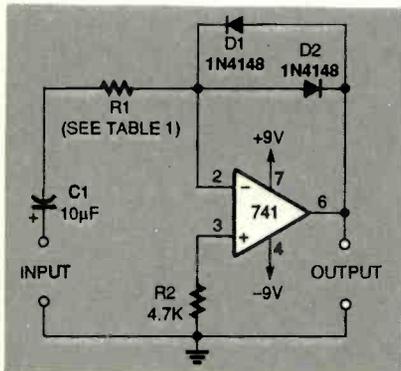


FIG. 9—NONLINEAR (SEMILOG) amplifier based on the 741 operational amplifier.

aged in an 8-pin DIP.) Because two of these preamplifier circuits are needed in a stereo audio system, both sections of the dual preamplifier ICs are used.

The LM381 has a high, open-loop gain of 112 dB, and a total input noise rating of 0.5 microvolts. Its output voltage swing equals the supply voltage minus 2 volts and it has a wide power bandwidth of 75 kHz, 20 volts peak-to-peak. The LM387 is similar to the LM381 except that it has an open-loop gain of 104 dB and a total input noise rating of 1.0 microvolt. The amplifiers in both ICs are electrically independent of each other.

The LM381 in Fig. 8 is configured as a noninverting amplifier. Negative feedback is applied from the output to the inverting input terminal. The voltage divider consisting of resistors R3 and R4, and the network formed by resistor R6 and capacitor C2 determines AC signal gain.

At the audio frequency mid-band (centered on 1 kHz) capacitors C2 and C3 have low impedances and C4 has a high impedance. As a result, AC gain is determined principally by the value of resistor R5 divided by R6, and it equals about 400. At lower frequencies, the impedance of C3 becomes significant

nals form the magnetic pickup cartridge are AC coupled to the LM381 by C1.

### Nonlinear amplifiers

An operational amplifier will act as a nonlinear amplifier if a nonlinear component is included in its negative feedback network. Figure 9 shows two square-law response (nonlinear) feedback elements, a pair of diodes connected back-to-back in the feedback loop.

When small signals are applied to this circuit, the diodes act as infinite resistance (open circuits), so circuit gain is high. However, when large signals are applied, the diodes act a low resistances, so circuit gain is low.

The gain follows a semi-logarithmic function, and circuit sensitivity can be varied by altering the value of resistor R1. Table 1 summarizes the circuit performance with two different values of R1—1 and 10 kilohms. For example, it can be seen that a 1000:1 change in input signal amplitude causes a change as small as 2:1 in output level. This characteristic can be put to practical use in single-range bridge-balance detectors and signal-strength indicators. Voltage measurements can be made with an AC millivoltmeter.

When a sinewave input is ap-

TABLE 1  
NONLINEAR AMPLIFIER PERFORMANCE

Millivolts (input, RMS)	R1 = 1K		R1 = 10K	
	V <sub>OUT</sub> mV RMS	V <sub>GAIN</sub>	V <sub>OUT</sub> mV RMS	V <sub>GAIN</sub>
1.0	110	×110	21	×21
10.0	330	×33	170	×17
100.0	450	×4.5	360	×3.6
1000.0	560	×0.56	470	×0.47
10,000.0	600	×0.07	560	×0.56

TABLE 2  
CONSTANT - VOLUME  
AMPLIFIER PERFORMANCE

R1 = 100K		
Millivolts (input)	V <sub>OUT</sub> (volts)	V <sub>GAIN</sub>
500	2.85	×5
200	2.81	×14
100	2.79	×28
50	2.60	×52
20	2.03	×101
10	1.48	×148
5	0.89	×180
2	0.4	×200
1	0.2	×200
0.5	0.1	×200

As an alternative, a National Semiconductor LM387, another low-noise, dual preamplifier will work in the circuit. Both the National LM381 and LM387 are suitable as amplifiers in audio-tape playback preamplifiers.

The pin numbers shown in Fig. 8 are those of the first half of the LM381, packaged in a 14-pin DIP. (The LM387 is pack-

and it causes AC gain to increase until, at very low frequencies, it is limited to 4000 by the ratio of the value of resistor R3 with respect to R6.

By contrast, at high frequencies, the impedance of C4 falls significantly, shunting R5. This causes the AC gain to decrease until, at very high frequencies, it is limited to 10 by the ration of the values of R4 to R6. The sig-

plied to the circuit, the two diodes limit the output voltage swing to about 1.4 volts peak-to-peak by clipping the waveform. The output approximates a

*Continued on page 93*

## DRAWING BOARD

continued from page 86

Running speaker cable throughout the house from a central location where I have all the audio equipment is certainly not a big deal from an electronic point of view, although keeping it hidden in the walls can be difficult. The complexity of the project was increased by a factor of ten when I was informed that everybody wanted a system that would allow different sources to be routed to different speakers at the same time—the cassette player to the kitchen, CDs to the bedroom, the TV to the den, and so on.

The easiest way to do this would be with a patch panel, but the thought of endless patch cable repairs wasn't too appealing. Besides, an all electronic router is a lot more elegant. My winter project now is now to build an easy-to-use audio router. Easy-to-use means it should have a minimum of controls and a display panel that shows exactly what audio is going where.

Here's my list of design criteria:

1. The circuit shall accept eight stereo audio inputs (each input shall consist of a left and right channel).
2. The circuit shall have four stereo audio outputs (each output shall consist of a left and right channel).
3. The device shall display routing on LEDs.
4. There shall be a simple way to clear the inputs and outputs.

While there's no reason why I couldn't incorporate a power amplifier on each output channel, but for the moment I want to keep everything as simple as possible by dealing only with line-level signals. As we get into the design of the circuit, you'll see how easy it is to make changes.

Every circuit design starts with a block diagram, and that's what you'll find in Fig. 3. The keyboard selects the input and output channels. That information is sent to the display which I've specified in the design criteria. From that point on, the control signals are sent to the I/O sections where the actual audio routing will take place.

Before I get into the nitty gritty of the design, I want to explain how the device will be organized. The simplest way to set things up is on a grid system like that shown in Fig. 4. The inputs and outputs are arranged as intersecting lines, and the circuit I'm going to build makes the connections I want at the corresponding intersection of the desired column and row. Once the connection is made, the chosen input is routed to the chosen output. The display will indicate the status of the output channel.

Both the block diagram and the grid drawing show that there is one control line per channel. I'm mentioning this now because it reflects a

decision I made about the parts I'll be using. All the audio switching will be done in the I/O section with analog switches—I'll be using CD4066B-CMOS ICs, ganging them together as DPST switches.

My decision about the design of the output stage affects the design of the whole circuit. The keyboard, for example, has to generate only a single-line address as opposed to an address with three or more lines if I were using binary addressing. This makes the design of the keyboard much simpler. Next month I'll explain the keyboard design.  $\Omega$

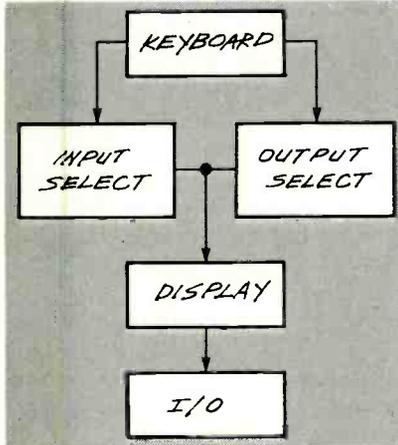
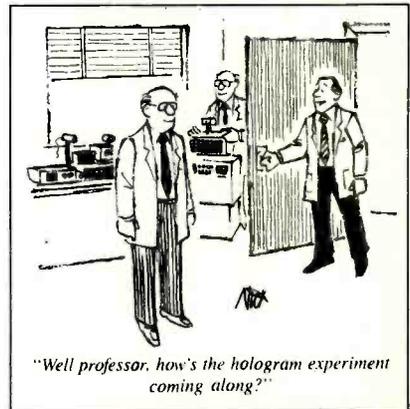


FIG. 3—AUDIO ROUTER BLOCK DIAGRAM. The keyboard is used to select the input and output channels.

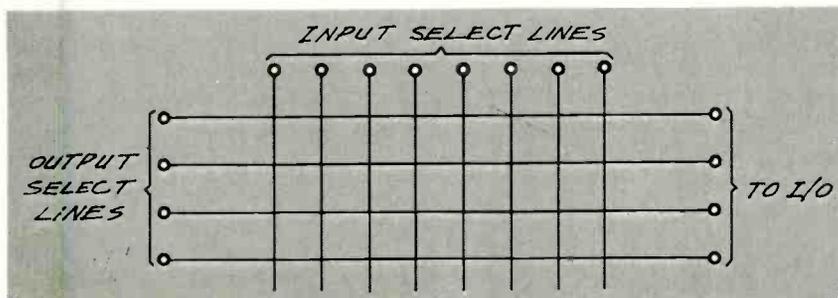


FIG. 4—THE DEVICE WILL BE ORGANIZED as a grid system. The inputs and outputs are arranged as intersecting lines.

# Be an FCC LICENSED ELECTRONIC TECHNICIAN!

**Earn up to \$60 an hour and more!**

Learn at home in spare time. No previous experience needed!

No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more... even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

**No Need to Quit Your Job or Go To School** This proven course is easy, fast and low cost! **GUARANTEED PASS**—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

**COMMAND PRODUCTIONS**  
 FCC LICENSE TRAINING, Dept. 90  
 P.O. Box 2824, San Francisco, CA 94126  
 Please rush FREE details immediately!

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

# COMPUTER CONNECTIONS

UberSoft uber alles.

JEFF HOLTZMAN


**D**eep underground lies the Command and Information Center, the hub of the most extensive computer network on Earth. This CIC differs from many corporate and military computing centers because it has direct, on-demand connectivity to many tens of millions of computers worldwide. The majority of these connections link private individuals to the CIC. A significant fraction of the remaining connections link corporate accounts located throughout the developed nations of the Earth.

The CIC is owned and operated by the richest, most powerful corporation on Earth: UberSoft. UberSoft is, in turn, owned and operated by one man: Charlie Haines. Haines started UberSoft on a shoestring; over a period of more than twenty years, a series of brilliant, opportunistic moves by Haines propelled UberSoft to its current position.

Today, total employment of the company exceeds that of any government on Earth save that of China. Haines pays his employees well, and rewards performance with shares in the company. Everyone works toward a common, well-articulated goal: UberSoft Uber Alles. The closer the company gets to that goal, the better the reward. Haines, nonetheless, always maintains a 51% share in the company.

UberSoft's early growth was achieved mostly by hard work and a healthy measure of intuition. Haines's intuition about directions in technology and fickle consumer tastes was legendary. By itself, that intuition was enough to build UberSoft into the mightiest corporation on Earth.

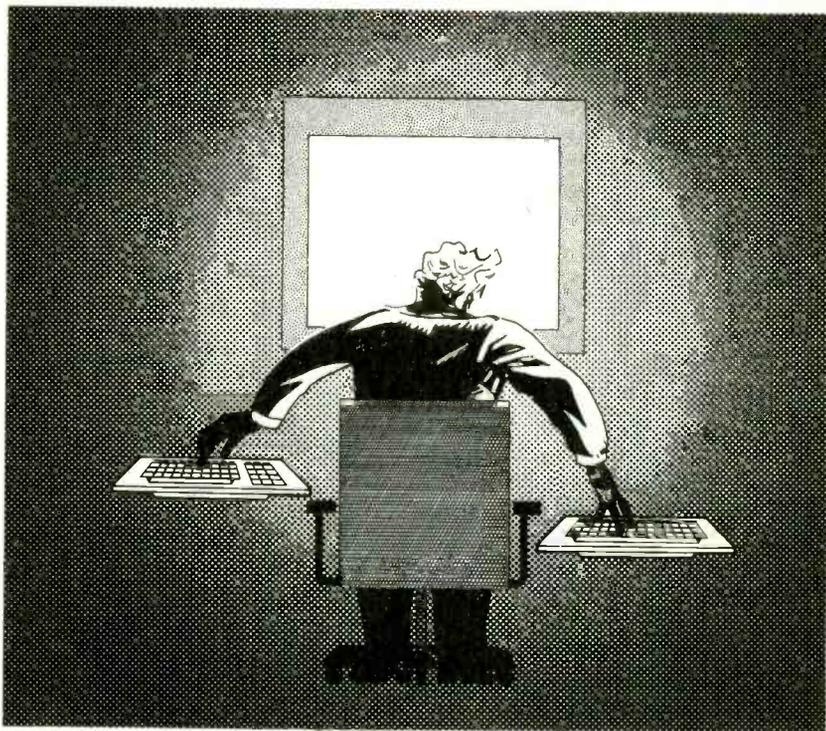But Haines was not satisfied. He knew that his intuition could go only so far. He knew that at some point he would need a more direct means of measuring consumer tastes, something that could provide feed-



**THIS GUY PLAYED HIS CARDS RIGHT** from the very beginning. He knows everything about everything.

back in real time. Haines also knew that achieving such instantaneous feedback could be accomplished only by means of instantaneous real-time hookups to UberSoft's tens of millions of customers. That would entail a tremendous network infrastructure, on the order of that provided by the telephone companies. It would require tremendous advances in computer architecture, database design, transaction processing, and analysis software. It would also require extremely subtle software that would run on millions of UberSoft customer machines so as to provide UberSoft with the information it needed, but not alarm the owners of those machines that anything out of the ordinary was happening.

Haines knew that the scheme would be highly controversial. He knew that if even a single word ever

leaked out about his plan, legal and ethical questions would be raised by the press, questions that could easily derail the plan, and possibly even UberSoft itself, questions that politicians and competitors would seize on to dismantle UberSoft and destroy Haines' empire.

Thus no one knew of the plan. That is, no one knew how all the pieces fit together. Haines instructed various marketing and technical groups throughout the company to work on various facets of the problem. Most people were content merely to be working for Haines and for UberSoft—content to be making good money; content to be working on interesting, challenging problems; and content to be astride a winner so far ahead of the competition that, in essence, there was no competition.

In his mind, Haines assembled a

## AUDIO FILTERS

continued from page 64

square waveform, and it is rich in odd harmonics. If this waveform is amplified, it sounds like a clarinet.

### Constant-volume amplifier

The nonlinear amplifier shown in Fig. 9 gives a near constant-amplitude output signal over a wide range of input signal levels, but it does this at the cost of introducing large signal distortion. Figure 10 is a schematic for a constant-volume or constant-amplitude amplifier that amplifies without distorting the signal. A self-adjusting, voltage-controlled linear network replaces the nonlinear element in the feedback loop of Fig. 9.

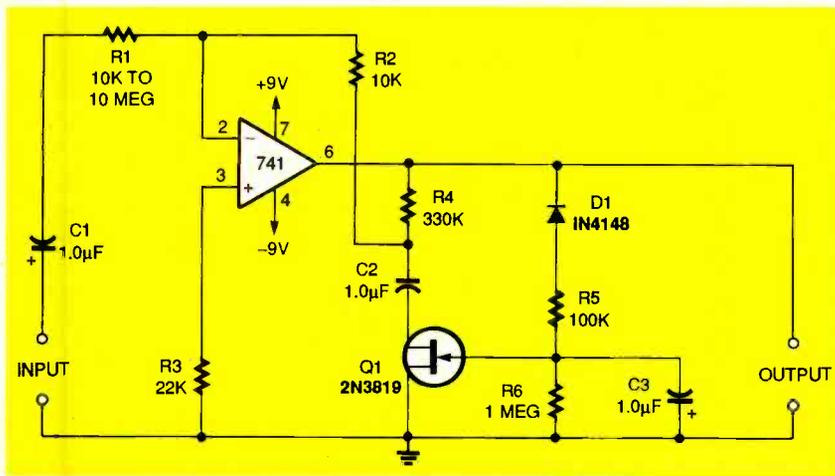


FIG. 10—CONSTANT-VOLUME amplifier that includes a JFET.

The operational amplifier is configured as an AC amplifier with its gain controlled by the ratio of the values of resistor R1 with respect to R2 and by the AC voltage divider formed by R4 in series with the internal impedance of Q1.

This FET functions as a voltage-controlled resistor. Its control voltage is obtained from the output of the operational amplifier with a network formed by diode D1 in series with resistor R5 and resistor R6 in parallel with capacitor C3.

When a small signal is applied to the 741, its output is small. Consequently, very little negative bias is developed on the

FET gate from the network consisting of D1, R5, R6 and C3. The FET functions as a resistance with a value of several hundred ohms. The voltage divider formed from R4 and Q1 causes slight negative feedback that is applied to the 741, so it provides high voltage gain.

By contrast, if a large signal is applied to the 741, its output is large, so a large negative bias is developed on the gate of FET Q1 from the D1, R5, C3 network. As a result, Q1 acts like a very high resistance. In this condition, the R4/Q1 divider applies large negative feedback to the 741, and it provides low voltage gain.

The overall effect of this response characteristic is that the mean level of the output signal is self-regulated at 1.5 to 2.85 volts over a 50:1 range of input


signal level. (This is equal to 500 to 10 millivolts.) It does this without generating audible signal distortion. The circuit's performance is summarized in Table 2.

The value of resistor R1 determines the sensitivity of the circuit. It is selected to accommodate the maximum input signal amplitude that the circuit is expected to handle. This is determined on a basis of 200 kilohms per RMS volt of input signal.

For example, to accommodate a maximum input of 50 volts, R1 should have a value of 10 megohms. Capacitor C3 determines the automatic gain control time constant of the circuit. Ω

### •MICRO MICON BOARD AKI-80

The AKI-80 is a Z80015BF 12 applied (CPU, PIO, CTC, SIO, DDC, etc.) Z80 software-compatible, high-quality 8-bit micon that can be installed in one tic. The flat IC is not easily soldered, and has been already installed.  
AKI-80 <26K SRAM Ver.> \$40.00  
AKI-80 <256 SRAM Ver.> \$43.00

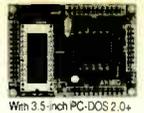


With 3.5-inch PC-DOS 2.0+
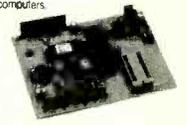
### •AKI-80 ROM WRITER KIT 1K: \$90.00

• Available for use with IBM PC-DOS/V personal computers.  
• Corresponds to ROM2764, 27128, 27256  
• Internal Z80 developing function

Contents:  
Dedicated board <AKI-80 with gold>  
Pin-Assigner Z80 (28 Pin)  
D-sub 28  
Assembly technology data collection  
form WRITER Hexachary software  
for IBM PC-DOS/V with 3.5-inch FDD



### Parallax Development Tools (PIC 16Cxx Microcontrollers)

•BASIC Stamp Programming Package \$99.00



Package includes everything necessary to program Stamps.

•PIC 16Cxx Programmer \$188

Programs, reads, and verifies PIC16Cxx devices.

•Supports PIC16C5x, PIC16C71 and PIC16C84

•PIC 16C71-84 TrueFlight \$299

Programmer/downloader for PIC16C71/84

•PIC 16C5x Downloader \$299

Acts as ROM emulator for PIC16C5x devices.



To use the Programming Package, you'll need an IBM PC or compatible with a parallel port, 3.5-inch disk drive, and DOS 2.0+

### Data Acquisition for your PC

•ADC-10 \$98.00


(1 channel, 8-bit)

•ADC-12 \$158.00

(1 channel, 12-bit)

0-5V analog input

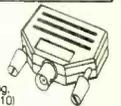(with picoscope and picolog, oscilloscope probes (X1, X10))



Akizuki Denshi Co., Ltd. was established in 1944, and is currently engaged in the selling of electronic components and electronic measuring instruments in Akihabara, Tokyo. If you are interested in our products, please enclose payment (in \$US) in the amount of the price indicated for and handling costs. We will fill your order and send the product to you as soon as payment is received.

### Akizuki Denshi Co., Ltd.

1st Floor, Nomizu Bldg., 1-8-3 Sotokanda, Chiyoda-ku, Tokyo, Japan 101  
CALL: 81-3-3431-6279 FAX: 81-3-3251-3357  
Supervisor: Aiko Tsujimoto

## Choose from 46 Career Opportunities!

Get Your Specialized Associate Degree or Career Diploma at Home in Spare Time

Now without attending college classes and with no previous experience, you can train for a money-making career...even get a Degree. Send for free facts and color brochure on employment opportunities in the field that interests you most. See how easy it is to train at home for a great career or advancement in your present job.



CALL TOLL FREE 1-800-595-5505 Ext. 5742  
CALL ANYTIME—24 hours a day, 7 days a week.  
OR MAIL COUPON TODAY!

### ICS International Correspondence Schools

Dept. ADES255, 925 Oak Street, Scranton, PA 18515

Please send me free facts, color brochure and full information on how I can study at home for the career I have chosen.

No obligation. No salesman will visit. CHECK ONE BOX ONLY!

ASSOCIATE IN SPECIALIZED BUSINESS DEGREE PROGRAMS

- Accounting
- Bus. Mgmt.—Finance Option
- Bus. Mgmt.—Marketing Option
- Applied Computer Science

ASSOCIATE IN SPECIALIZED TECHNOLOGY DEGREE PROGRAMS

- Civil Engineering Technology
- Mechanical Engineering Tech.
- Electrical Engineering Technology
- Electronics Technology
- Industrial Engineering Technology

CAREER DIPLOMA COURSES

- High School
- Auto Mechanics
- Surveying and Mapping
- Drafting
- Air Conditioning & Refrigeration
- Wildlife/Forestry Conservation
- Fashion Merchandising
- Diesel Mechanics
- Electrician
- Small Business Management
- Gun Repair
- Electronics
- Hotel/Restaurant Management
- Child Day Care
- Legal Assistant
- Interior Decorating
- Medical Office Assistant
- Bookkeeping
- Motorcycle Repair
- Catering/Gourmet Cooking
- Computer Programming
- Personal Computer Specialist
- Computer-Assisted Bookkeeping
- PC Repair
- Desktop Publishing & Design
- Secretary with Computer
- Fitness & Nutrition
- TV/VCR Repair
- Animal Care Specialist
- Photography
- Journalism/Short Story Writing
- Florist
- Teacher Aide
- Medical Transcriptionist
- Professional Locksmithing
- Appliance Repair

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ Apt. # \_\_\_\_\_

City/State \_\_\_\_\_ Zip \_\_\_\_\_

Phone ( ) \_\_\_\_\_

March 1995, Electronics Now

master plan that took more than a decade to put into practice. It involved insinuating UberSoft products at the every level of the computing hierarchy. It involved applications programs, operating systems, and network operating systems. It involved alliances with telecommunications providers (telephone and cable TV companies, and on-line service providers). It involved strategic influence over hardware designs ranging from CPUs to memory architectures to mass-storage devices to sound and video services.

Early efforts involved alliances. Subsequent efforts involved takeovers. Over time, UberSoft absorbed or destroyed every company with which it ever formed an alliance. Gradually, UberSoft grew from a supplier of programming languages and a few applications to a supplier of every element of hardware and software across all levels of the computing food chain, ranging from personal computers and software, to networking equipment and software, to wide-area communications systems, to content providers including a television network, a publishing conglomerate, and a Hollywood studio. UberSoft owned newspapers, television stations, production studios, rock bands, libraries, movie stars, directors, and entire multimedia production companies.

During the decade when all that was being built, Haines innocuously began building his personal mansion, home to his collection of expensive sports cars. To the public, the mansion was ostensibly a rich man's plaything, a technophile's dream home, replete with multimedia computers and communications systems in every room of the house. Unbeknownst to even Haines's closest associates, however, was a simultaneous subterranean construction effort, what we know now as the CIC, brilliantly hidden under the guise of being part of the mansion.

Several key pieces of Haines's plan kicked into place in late 1994, when UberSoft executed three strategic moves: 1) Launched its own on-line telecommunications service, 2) Made freely available

software for accessing it, and 3) Swallowed up yet another competitor, a billion-dollar firm that wrote software for personal and small-business software: OutOfIt. OutOfIt had grown steadily from humble beginnings in a very Hainesian, yet more focused manner. The company held an unassailable position in its market segment. Hitherto, that segment had been one of Haines' few disappointments, but with the acquisition of OutOfIt, all the pieces were in place for UberSoft and Haines' next move.

In addition to being a brilliant business tactician and strategist, Haines was also brilliant technically. He did not know the detailed workings of every product sold by UberSoft, but it wasn't because he was incapable. In fact, as time passed, Haines knew progressively less and less about the internal workings of UberSoft products. Some thought he was losing interest. The truth was that his interests had evolved to a higher-level focus on systems, system architectures, and interoperability of systems. Again, that was all part of his master plan.

### The war room

Deep underground lies the Command and Information Center, the hub of Haines' wide-area computer network. The CIC is laid out like a war room, with huge displays covering every square inch of wall space in a circular room with a diameter of 60 feet. Throughout the room are clusters of computers. One group serves as the hub of the on-line service network. Another functions as the primary repository for UberSoft's corporate data, including all technical, financial, and market information. Yet another serves clients of the former financial software company OutOfIt. Others link the CIC to UberSoft's telephone network, communications satellites, and production companies.

In the center of the CIC, raised above the myriad blinking lights and computer screens, rests a huge dais, on which sits a chair, something like a convoluted, high-tech dentist's chair. This chair is the center of Haines' universe. Its electronic tentacles spread out to cover vast portions of civilization. These

tentacles pulse with information, the lifeblood of civilization today, information detailing every activity performed by every one of the tens of millions of computers connected to UberSoft's network.

Unbeknownst to his customers, indeed, to all but a select few of his employees, the software that connects individual customers to the network also serves as an on-demand two-way information pipe. Special hidden features of the software can be awakened remotely by the UberSoft network, automatically or on demand by whoever sits in the hot seat at the basin of the CIC.

Those hidden software features allow Haines to interrogate and view information on his customers' computers. He can, at any time, switch among any of millions of nodes in his network. He can view the contents of his customers' hard disks. He can read their E-mail. He can read their personal files. He can also read files of interest to UberSoft, files that can increase the company's already formidable business advantage.

Actually, Haines found that after the initial thrill, those millions of hard drives were pretty boring. Most of the data-collection effort was thenceforth carried out automatically, in the background, without anyone's noticing. Gradually, the data allowed Haines to develop market profiles of unprecedented scope and accuracy. Everything in his database could be sorted by age, race, income, location, education, and myriad other characteristics.

### Questions

Is that scenario far-fetched, unrealistic? Not really. Much of what is described could be accomplished today—without a big, expensive "war room." Any computer user with an Internet connection and a little knowledge of network protocols could easily gain similar access to all sorts of corporate and private data.

Any telecommunications software—for example, the software you use to access CompuServe, America On-line, or Prodigy, or a generic program like Crosstalk or

Procomm, or a built-in program like the one that will appear in Windows 95 for the purpose of connecting to Microsoft's new on-line service with a single click—any such program could easily be adapted to transparently upload to the host all sorts of information about your system. And you.

That could include technical information, such as your CPU, hard disk size, or amount of memory, that would enable the provider to better tune its software to your needs. But it could also include any other data stored on your computer, or on any other computer to which your computer has access. In other words, not only is your personal and technical data at risk, but so is your company's.

Many people and corporations fear the possible effects of computer viruses. But who considers the possibility of a "Trojan Horse," a seemingly benign piece of software that could easily reveal your innermost secrets?

**CD redux**

My E-mail drew lots of interesting comments to my December column, in which I advocated a new kind of software documentation called Conceptual Documentation. Conceptual Documentation is the antithesis of the trivia promulgated by the "Dummies" books. It teach-


es you about the skeleton and the muscles so you can figure out how to walk, and maybe even run, all by yourself.

S. Fingerman, a software instructor, points out that "Unfortunately, a lot more people buy TV Guide than Electronics Now, and they still can't figure out how to use their VCRs." That's right. As I said, it's a social problem. As a society, we want easy answers. We don't want to think.

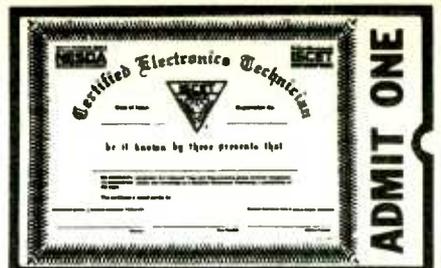D. Wigginton, an IBM survivor, has a good analogy for the typical process of learning a new piece of software: "How obvious it is that having an overall floor plan of the house would make it so much easier to use effectively. Instead, we wander throughout our software as if we were playing some permutation of Myst, looking for clues and repeatedly drawing revised visual sketches in our minds of what the thing we're working with really is."

Last, T. Nichols, a self-described RF/microwave engineer with a PhD in electromagnetics, states that "What people tend to miss, in my experience, is that those 'high-falutin' concepts' may slow down the solution to their problem the first time around. But it will greatly speed up the solution to their problem the second and third and fourth. . . ."

Please feel free to send any comments to [jkh@acm.org](mailto:jkh@acm.org). Ω



**Your Ticket To SUCCESS**

Over 28,000 technicians have gained admittance worldwide as certified professionals. Let your ticket start opening doors for you.

IS CET offers Journeyman certification in Consumer Electronics, Industrial, Medical, Communications, Radar, Computer and Video. For more information, contact the International Society of Certified Electronics Technicians, 2708 West Berry Street, Fort Worth, TX 76109; (817) 921-9101.


Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_  
 State \_\_\_\_\_ Zip \_\_\_\_\_  
 Send material about IS CET and becoming certified.  
 Send one "Study Guide for the Associate Level CET Test." Enclosed is \$10 (inc. postage).

**BECOME AN ELECTRICIAN!**

PROFESSIONAL-LEVEL HOME STUDY

Train now to make good money working on electrical systems in homes and businesses.

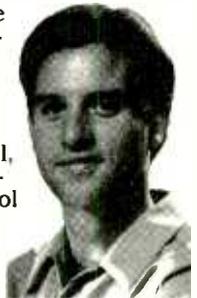Learn all about how to wire, install, and maintain lighting, circuits, control panels, cables, appliances, phone systems, utilities, and much more.



Fascinating, fun, and easy-to-follow. Learn at your own pace, in the comfort of your home. For free literature, send or call 24 hours a day.

**CALL 800-223-4542**

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_  
 State \_\_\_\_\_ Zip \_\_\_\_\_  
 Age \_\_\_\_\_ Phone ( ) \_\_\_\_\_

**THE ELECTRICIAN SCHOOL**  
 Dept. TEC342, 6065 Roswell Road  
 PCDI, Atlanta, Georgia 30328

March 1995, Electronics Now

**CABLE CONVERTER DIAGNOSTIC MODULES**

PIONEER BOARD 3-WIRE	1 PC - 10 PC	
BA-51XX - BA-61XX	34.95 - 29.95	
BA-63XX - BA-67XX	44.95 - 39.95	
STARCOM 6-DPV-5XXX	19.95 - 16.95	
STARCOM VII-DPV-7 QUICK BOARD	44.95 - 39.95	
STARCOM VII-DPBB QUICK BOARD	44.95 - 39.95	
NEW JERROLD DIAGNOSTIC. . . .		
CUBE MULTI-FREQUENCY 108.5 106.5 97.5	154.95 - 144.95	

NOTE: ALL QUICK BOARDS ARE WIRELESS

S/A 8536 AUTO BOARD (NO SWITCH)	34.95 - 29.95
S/A 8535 AUTO BOARD (NO SWITCH)	34.95 - 29.95
S/A 8570,8550 QUICK BOARD. . . .	39.95 - 34.95
S/A 8600,8590,8580 QUICK BOARD	39.95 - 34.95
S/A 8580 40 PIN PLUS + MICRO	39.95 - 34.95
S/A 8570 /90 /8600 40 PIN MICRO	39.95 - 34.95

**NEW NEVER RESET E-4 PIONEER BOARD**

**VISUAL COMMUNICATIONS INC.**  
 800-GO-CABLE TECH.SUPP 718-229-2358

ANYONE IMPLYING THEFT OF SERVICE IN ANY WAY SHAPE OR FORM. DO US AND YOURSELF A FAVOR DON'T BOTHER CALLING US.  
 "AND YES WE DO MEAN YOU"  
 THESE PRODUCTS ARE FOR DIAGNOSTIC PURPOSES ONLY PERIOD !!! NO N.Y. SALES

CIRCLE 183 ON FREE INFORMATION CARD

CIRCLE 100 ON FREE INFORMATION CARD

## WHAT'S NEWS

*continued from page 4*

data-communication and telecommunication segments that serve the computer and telecommunication industries. Protocol analyzers, Equipment that finds transmission problem, BERTs (bit error rate testers), and BLERTs (block error rate testers) will show rapid sales increases.

Hewlett-Packard continues to be the leading share holder in most product categories. Other major players include Anritsu, Tektronix, John Fluke, Marconi Instruments, Rhode & Schwarz, Network General, and Telecommunication Techniques.

### **Collision warning for cars**

Three different kinds of automotive anti-collision systems have been announced so far—those based on sensors which respond to reflected radio frequency, microwaves and infrared energy. Their purpose is to warn drivers about the presence of vehicles in their "blind zones" when they are about to change lanes. The manufacturers of these systems are competing to develop systems that will be accepted as standards by auto manufacturers for installation on automobiles.

So far no automoto manufacturer has announced a date when any anti-collision system will be installed, either as standard or optional equipment on automobiles. This leaves an opportunity for a lucrative automotive aftermarket for independent manufacturers of the systems. Car owners would be able to buy one of the systems available that they could install or let the seller install, as is now done with add-on accessories.

Statistics from the U.S. Department of Transportation reveal that 13% to 15% of all vehicle collisions occur as a result of the drivers' inability to see other vehicles in blind spots as they change lanes. However, some automotive experts believe that number is inflated and the true figure is nearer to 7%.

The latest introduction in the anti-collision sweepstakes is the SideMinder system, based on infrared

and LED technology. Developed by Autosense, Denver, Co., the system includes infrared sensors and detectors and an LED display developed by Siemens Optoelectronics Div., Cupertino, Calif.

Autosense expects to make SideMinder systems available in production quantities to auto manufacturers for less than \$50 each. This figure compares with the \$100 to \$500 estimates of systems costs for systems based on other technologies.

SideMinder is activated when the vehicle's turn signal is activated. Infrared sensor modules, located behind the host vehicle's tail-light lens assemblies, monitor "blind" spots on both sides of the car for a distance of up to 15 feet.

When the driver wants to change lanes, he activates the turn signal which, in turn, activates the system. Infrared energy from the module that is reflected from nearby vehicles activates a circuit in the host vehicle to lights LED lamps located in either the passenger- or driver-side rear-view mirrors if a vehicle is one of the blind spots. Detection occurs in a fraction of a second.

Cars equipped with prototype SideMinders are now being tested in the United States and Europe. Autosense reports that the systems could be offered as optional equipment on passenger cars and vans within the next five year.

Recently the Delco Electronics Corporation announced the development of a car radar system that would accomplish the same objective. Delco, a division of General Motors, said it is unlikely that the system will be offered as an option on cars until about 1998 or 1999. However, it is expected to have a version for trucks available this year.

Delco has had its collision avoidance systems on school buses for a year to warn bus drivers of nearby objects. Nissan Motor Company developed a laser-based warning systems for trucks three years ago, but has no plans to put them in automobiles.

Delco's radar system for trucks has four-inch square transceivers mounted on the sides of the truck's cargo box. When the driver signals a lane change, the system is acti-

ated. Microwaves emitted by the transceivers reflect from any cars that are in the driver's blind spots, and returned signals are detected. An audible signal sounds and lights mounted on the sideview mirrors flash. This system also has a range of 12 to 15 feet.

TRW Inc. has also developed a microwave radar system collision avoidance system but Amerigon Inc., Monrovia Calif., has developed a pulsed radio-frequency system. Both Chrysler Corporation and Ford Motor Company are reported to be developing their own collision avoidance systems.  $\Omega$

## VIDEO NEWS

*continued from page 6*

movies are available in the Video CD format.

• **Balance of power.** At least two hardware manufacturers and one movie studio are believed to wield the greatest influence over the final selection—if, indeed, a single system is chosen. Matsushita Electronic (Panasonic), the world's largest consumer-electronics manufacturer, originally was believed to be in the Sony-Philips camp, but released a brief statement saying that it "considers it desirable that a uniform standard eventually be selected ... [to] meet the needs of the software industry, avoid confusion among consumers, and increase the availability of software." Matsushita said that it was "conducting its own study of the matter."

The other major hardware power holding the balance is Thomson Consumer Electronics, maker of RCA and GE TV sets, which holds the biggest share of the U.S. market and is also a power in Europe. Among the Hollywood movie companies, Disney could be the biggest influence, since it is unaffiliated with a hardware manufacturer. Matsushita owns MCA, parent of Universal Pictures, while Sony owns the former Columbia Pictures, and, of course, Toshiba is allied with Time Warner, parent of Warner Brothers.  $\Omega$

# BUYER'S MART

## FOR SALE

**TUBES:** "oldest", "latest". Parts and schematics. SASE for lists. **STEINMETZ**, 7519 Maplewood Ave. R.E., Hammond, IN 46324.

**CB Radio Modifications!** Frequencies, 10M, sliders, FM, amplifiers, books, kits, repairs, high-performance accessories. The best since 1976! Catalog \$3.00. **CBCI**, Box 31500EN, Phoenix, AZ 85046.

**THE Case Against the Patents.** Thoroughly tested and proven alternatives that work in the real world. \$28.50. **SYNERGETICS PRESS**, Box 809-C, Thatcher, AZ 85552. (602) 428-4073. Visa/MC.

**CABLE descrambling.** New secret manual. Build your own descramblers for cable and subscription TV. Instructions, schematics for SSAVI, gated sync, sinewave, (HBO, Cinemax, Showtime, UHF, Adult) \$12.95, \$2.00 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

## CLASSIFIED AD ORDER FORM

To run your own classified ad, put one word on each of the lines below and send this form along with your check to:

**Electronics Now Classified Ads**, 500-B Bi-County Boulevard, Farmingdale, NY 11735

**PLEASE INDICATE** in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of **\$25.00**.

( ) Plans/Kits ( ) Business Opportunities ( ) For Sale  
( ) Education/Instruction ( ) Wanted ( ) Satellite Television

Special Category: \$25.00

### PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

(No refunds or credits for typesetting errors can be made unless you clearly print or type your copy.) Rates indicated are for standard style classified ads only. See below for additional charges for special ads. **Minimum: 15 words.**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (\$46.50)
16 (\$49.60)	17 (\$52.70)	18 (\$55.80)	19 (\$58.90)	20 (\$62.00)
21 (\$65.10)	22 (\$68.20)	23 (\$71.30)	24 (\$74.40)	25 (\$77.50)
26 (\$80.60)	27 (\$83.70)	28 (\$86.80)	29 (\$89.90)	30 (\$93.00)
31 (\$96.10)	32 (\$99.20)	33 (\$102.30)	34 (\$105.40)	35 (\$108.50)

We accept MasterCard and Visa for payment of orders. If you wish to use your credit card to pay for your ad fill in the following additional information (Sorry, no telephone orders can be accepted):

Card Number \_\_\_\_\_ Expiration Date \_\_\_\_\_

Please Print Name \_\_\_\_\_ Signature \_\_\_\_\_

**IF YOU USE A BOX NUMBER YOU MUST INCLUDE YOUR PERMANENT ADDRESS AND PHONE NUMBER FOR OUR FILES. ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.**  
**CLASSIFIED COMMERCIAL RATE:** (for firms or individuals offering commercial products or services) \$3.10 per word prepaid (no charge for zip code)...**MINIMUM 15 WORDS**, 5% discount for same ad in 6 issues; 10% discount for same ad in 12 issues within one year; if prepaid (not applicable on credit card orders). **NON-COMMERCIAL RATE:** (for individuals who want to buy or sell a personal item) \$2.50 per word, prepaid....no minimum. **ONLY FIRST WORD AND NAME** set in bold caps at no extra charge. Additional bold face (not available as all caps) **55¢ per word additional**. Entire ad in boldface, \$3.70 per word. **TINT SCREEN BEHIND ENTIRE AD: \$3.85 per word**. **TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD: \$4.50 per word**. **EXPANDED TYPE AD: \$4.70 per word prepaid**. Entire ad in boldface, \$5.60 per word. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD: \$5.90 per word**. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD: \$6.80 per word**. **DISPLAY ADS:** 1" x 2 1/2"—\$410.00; 2" x 2 1/2"—\$820.00; 3" x 2 1/2"—\$1230.00. **General Information:** Frequency rates and prepayment discounts are available. **ALL COPY SUBJECT TO PUBLISHERS APPROVAL. ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 1st of the third month preceding the date of the issue. (i.e., March issue copy must be received by December 1st). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding working day. Send for the classified brochure. Circle Number 49 on the Free Information Card.

**CABLE TV CHANNELS**

**EQUIPMENT** **GUARANTEED**

*Direct!* **The nationwide source for cable TV equipment.**

**"BUY WHERE THE DEALERS BUY."**

**FREE** **TV Cable Descramblers and Converters Catalog. Open Every Day!**

**YOUR VCR TAPES** Why put up with inconsistent Color, Flashes and Streaking and Interference!  
**CAN PLAY AS CLEAR AS DAY!**

**UNJAM NOW WITH Video Decoder**

- Easy Connections
- Eliminates "jamming"
- Copy any tape
- RC Plugs included
- 2 Year Warranty
- 30 Day Money Back Guarantee

**MEGA ELECTRONICS**  
VISA • MC C.O.D. **1-800-676-6342** SAVE 1000¢

**21 S. Main St., Winter Garden, FL 34787**

**DESCRAMBLE** cable with simple circuit added to Radio Shack RF modulator and using VCR as tuner. Instructions \$10.00. **TELCOM**, Box 832-E2, Brusly, LA 70719.

**PRINTED** circuit boards — etched, drilled, tin plated. Single sided \$1.25/sq. inch. **CHELCO ELECTRONICS**, 61 Water Street, Mayville, NY 14757. 1 (800) 388-8521. Fax (716) 753-3220.

**PRINTED circuit boards.** Design and make PC boards to your requirements. Small runs OK. Fast turnaround. 28 years experience. Call, write or fax for information. **SHORE PRINTED CIRCUITS**, 1658 Route 9, Toms River, NJ 08753. 1 (800) 752-1574, NJ (908) 505-6363, fax 505-6266.

**CABLE TV why rent? When you can own. Low prices, quality products.** Call tonite 6pm - 11pm EST. 1 (800) 865-7493. Free catalog. **TRUE VALUE ELECTRONICS**, PO Box 591, Lincoln, NH 03251.

**REAL STUFF!** Surveillance, people tracking, entry, night vision — lowest prices. Catalog \$15.00 1(800) 805-5544. **INTELLIGENCE INCORPORATED**, Dept. CQ, 2228 El Camino Real, San Mateo, CA 94403.

FREE

★ 1995 CATALOG ★

OF THE WORLD'S MOST FAMOUS  
CB ANTENNAS & ACCESSORIES

— FIRESTIK : FREE CATALOG OFFER —

2614 E. Adams · Phoenix, AZ 85034

Write or Call, 602-273-7151

FREE

# CABLE BOX WHOLESALE, INC.

**BEST BOXES—BEST PRICES**

**Immediate Shipping—COD's  
Satisfaction Guaranteed**

**FREE Catalog—Call Now**

## 800-841-7835

TUBES, new, up to 90% off, SASE, KIRBY, 298 West Carmel Drive, Carmel, IN 46032.

**CABLE test chips.** Jerrold, Tocom, S.A., Zenith. Puts cable boxes into full service model \$29.95 to \$59.95. 1 (800) 452-7090. (310) 902-0841.

**SECRET cable descramblers!** Build your own descrambler for less than \$12.00 in seven easy steps! Radio Shack parts list and free descrambling methods that cost nothing to try, included. Send \$10.00 to: **INFORMATION FACTORY**, Dept. 4, PO Box 669, Seabrook, TX 77586. For COD's (713) 922-3512 any time.

**300 Experimenters Circuits** — Complete in 6 practical books using diodes, relays, FET's, LED's, IC 555's, and IC CA3130's for building blocks. Only \$33.00 plus \$5.50 for shipping. USA and Canada only. US funds. **ETT, INC.**, PO Box 240, Massapequa Park, NY 11762-0240.

**RESTRICTED** information: surveillance, schematics, locksmithing, cable, hacking, etc. Send stamp: **MENTOR**, Box 1549-Z, Asbury, NJ 07712.

**CABLE TV converters.** Jerrold, Zenith, Pioneer, Oak, Scientific Atlanta, and many more. 12 years experience gives us the advantage. Visa/MC Amex COD **ADVANTAGE ELECTRONICS, INC.**, 1 (800) 952-3916 1125 Riverwood Dr., Burnsville, MN 55337.

**CABLE TV converters & accessories.** Wholesalers welcome! 30 day moneyback guarantee! Free catalog! **PERFORMANCE ELECTRONICS, INC.**, 1 (800) 815-1512.

**CABLE TV converters.** Jerrold, Zenith, Oak, Scientific Atlanta, all brands available. Link yourself to the future. Visa Mastercard, COD accepted. **CABLE LINX INC.**, 1 (800) 501-0095.

**TV Notch filters.** free brochure, **MICRO THINC.**, Box 63/6025, Margate, FL 33063. (305) 752-9202.

**TEST Chips.** Put your cable box in full test mode. Call (303) 731-9400.

# CABLE - TV NOTCH FILTERS

- FOR ELIMINATING RF INTERFERENCE
- FOR BLOCKING UNWANTED CHANNELS



□ AVAILABLE FOR VHF CHANNELS  
Ø THRU 36 AND 95 THRU 99

□ PRICING AS LOW AS \$12 EACH

Call or write for a  
**FREE brochure today!**

## STAR CIRCUITS

PO. BOX 94917  
LAS VEGAS, NV 89193

**1-800-535-STAR**

**CABLE test-chips** as low as \$9.95, for testing cable boxes in full service mode. Jerrold: Starcom VI, VII & R2 V5, Jerrold cubes, Pioneer, clears E2 thru E5; Pioneer cubes: BA-5000 thru BA-6700; Tocom: 5503/5507; Scientific Atlanta: 8500 thru 8600; Zenith: all but PZ1; N.E. ENGINEERING, 1 (800) 926-4030 sales (617) 770-3830 tech, (617) 770-2305 fax

**DEALERS Only:** Test chips at below wholesale prices. Scientific Atlanta quick boards and 40-pin micros. Jerrold compatible for all models starting with DP, DPV, DPBB & CFT, including R2 & V5. Pioneer 3-wire and custom 6300's. Zenith & Tocom. Direct from manufacturer, we guarantee the lowest prices. Software and master files available. We also have converters & descramblers priced to move. Visa, Mastercard, C.O.D. 1 (800) 618-7480 ext. 111.

**TEST equipment** pre-owned now at affordable prices. Signal generators from \$50.00, oscilloscopes from \$50.00. Other equipment including manuals available. Send \$2.00 U.S. for catalog refunded on first order. **J.B. ELECTRONICS**, 3446 Dempster, Skokie, IL 60076. (708) 982-1973.

### PAY TV AND SATELLITE DESCRAMBLING all new info VOLUME 6 all new info

- \* Volume 6—our best yet—details all known fixes for all cable, wireless and satellite systems. Many do-it-yourself. Schematics included. Only \$15.95
- \* Pay TV Volumes 1-5 (all different)
- \* Hacker Video (VHS)
- \* Wireless Cable Hacking Build Satellite Systems (includes DBS)
- \* Complete Wizard (VC2+) all these titles \$15.95 each 3/34.95 5/52.95
- \* Monthly Newsletter \$29.95/yr. \* new catalog \$1 \* All our info \$129.95

Scrambling News, 1552 Hertel Ave., #123  
Buffalo, NY, 14216. Voice/Fax/BBS (716) 874-2088  
COD'S ARE OK. ADD \$6

## ANTIQUE RADIO CLASSIFIED Free Sample!

Antique Radio's  
Largest Circulation Monthly.  
Articles, Ads & Classifieds.  
6-Month Trial: \$17.95. 1-Yr: \$34.95 (\$51.95-1st Class).  
A.R.C., P.O. Box 802-L15, Carlisle, MA 01741  
Phone: (508) 371-0512 VISA/MC Fax: (508) 371-7129



## Be a TV/VCR Repair Specialist

Now you can train for a money-making career as a TV/VCR Repair Specialist. No previous experience necessary. No need to quit your job or school. Everything is explained in easy-to-understand language with plenty of drawings, diagrams and photos. We show you how to troubleshoot and repair video cassette recorders and TV sets. Send for free facts about the exciting opportunities in TV/VCR Repair and find out how you can start making money in this great career.

**MAIL COUPON TODAY OR CALL TOLL FREE:**

**1-800-595-5505 Ext. 7248**  
CALL ANYTIME—24 hours a day, 7 days a week.

**ICS SCHOOL OF TV/VCR REPAIR, Dept. ADE0255**  
925 Oak Street, Scranton, PA 18515

Please send me full information and color brochure on how I can learn TV/VCR Repair at home in my spare time. I understand there is no obligation and no salesman will visit me.

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_ Apt. # \_\_\_\_\_  
City/State \_\_\_\_\_ Zip \_\_\_\_\_  
Phone ( ) \_\_\_\_\_

Electronics Now, March 1995

## SATELLITE TV

**FREE** catalog — Lowest prices worldwide. **SKYVISION**, 1012 Frontier, Fergus Falls, MN 56537. 1 (800) 334-6455 See full page at the Shopper section.

**VIDEOCYPHER II** descrambling manual. Schematics, video and audio. Explains DES, Eprom, CloneMaster, Pay-per-view (HBO, Cinemax, Showtime, Adult, etc.) \$16.95, \$2.00 postage. Schematics for Videocypher II Plus, \$20.00. Schematics for Videocypher II 032, \$15.00. Software to copy and alter Eprom codes, \$25.00. VCII Plus Eprom, binary and source code, \$30.00. **CABLETRONICS**, Box 30502R, Bethesda, MD 20824.

**REPAIR your own C/KU satellite TV.** SatPen simulates satellite signal in each stage — view trouble on TV. Radiates into dish to spot misalignment. Injects into any stage to detect outage. Cigar sized, rechargeable battery, charger, pocket clip/cord. Instructions. Simple to use by homeowner and professional. \$99.00. (MC-Visa) **NOVA LAB**, (803) 539-9200.

## SECURITY PRODUCTS

**ALARM** industry equipment, huge discounts. Cameras, control panels, motion detectors, sirens, batteries, switches, more. 1 (800) 335-2296, fax (519) 541-1277.

## INVENTIONS

**FREE invention package: DAVISON AND ASSOCIATES** offers customized development, patenting, and licensing for new products and ideas. Proven results: 1 (800) 677-6382.

## BUSINESS OPPORTUNITIES

**EASY work!** Excellent pay! Assemble products at home. Call toll free 1 (800) 467-5566 Ext. 5192.

**START your own technical venture!** Don Lancaster's newly updated **Incredible Secret Money Machine II** tells how. We now have autographed copies of the Guru's underground classic for \$18.50. **SYNERGETICS PRESS**, Box 809-C, Thatcher, AZ 85552. (602) 428-4073. Visa/MC.

## WANTED

**TEST equipment wanted;** top prices paid! Please send or fax your offer to: **HTB ELEKTRONIK**, Alter Apeler Weg 5, 27619 Schiffdorf, West Germany. Fax: 01149-4706-7049.

**WANTED:** Sony "superwalkman" WM-F10. Mid 1980's, cassette box sized. (216) 543-4372.

## CABLE TV TURN-ON CHIPS

**SUPER Cable TV "Test Chips"**. Provides full service activation. Excellent; instructions & illustrations. **Jerrold Starcom:** DP(V)5, DP(V)7, DPBB7, CFT-2000 series. **Pioneer:** BA-5000 thru BA-6700. **Scientific Atlanta:** 8500 thru 8600. **Tocom:** 5503-VIP.5507. **Zenith:** ST-1000 thru ST-5000. **Call now!! MASTER COMPONENTS.** 1 (800) 233-0570.

**MASTERCARD AND VISA** are now accepted for payment of your advertising. Simply complete the form on the first page of the Market Center and we will bill. \$15.00 minimum.

# BUY BONDS

## Be a PC repair expert!

Home study. Learn PC repairs, troubleshooting, installation, upgrading, servicing. For free career literature, call now: 800-223-4542.

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
**The School of PC Repair, Dept. JJC342, PCOI**  
6065 Roswell Road, Atlanta, Georgia 30328



**Learn VCR repair!**  
 Home study. Learn high-profit repairs without investing in high tech instruments. **Free career literature: 800-223-4542.**

Name \_\_\_\_\_ Age \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
**The School of VCR Repair, Dept. VRC342**  
 PCDI, 6065 Roswell Rd., Atlanta, GA 30328

# It started in America!

## The creators are the masters in manufacturing the finest video products...

You probably don't associate VCR's with American technology. Fact is, video recording has its origins in America and it was 3M that brought video recording out of the lab and into your living room. Today, 3M video tape is the choice of all the major networks. No other tape company has ever won an Oscar or an Emmy. 3M Black Watch tape follows in this tradition—service and quality go hand in hand. Here are three Black Watch products you should be using at home!



**For the clearest pictures you ever record!**

**Clean up!** With constant playing and using of degrading dry or wet cleaners, the output of your video tapes has slowly diminished to an unacceptable level and the VCR plays as if it has a head cold! The culprit is most likely clogged and dirty video and/or audio heads. The 3M Black Watch™ Head Cleaner Videocassette uses a patented magnetic tape-based cleaning formation to remove head clogging debris. No foreign substances such as cloth, plastics or messy liquids and no harsh abrasive materials are present. The cleaner's usable life is 400 cleanings or more!

production. This means your Hi 8 format camcorder will produce the best video and audio definition possible. With the 3M Black Watch™ 8mm cassette, the recording capability and performance of your camcorder will be significantly enhanced. Priced at \$14.95.

It's easy to use. Place the 3M Black Watch™ Head Cleaner Videocassette in the VCR and press the Play button. A pre-recorded message will appear clearly on your screen and an audible tone is heard, telling you that the cleaning process is now completed. No guess work; you never over clean! Priced at \$19.95.

**For the VCR!** Once your VCR's record and playback heads are cured, and the unit plays like new, consider using the finest videocassette you can buy—the 3M Black Watch™ T120 Hi Pro VHS 4410 Videocassette. The 4410 is the highest performing videocassette available today for use with all standard format VHS recording hardware!

Here's what you hear and see... A sharp, clear picture—brightest ever colors—freedom from streaks, flashes and snow—outstanding high-fidelity audio reproduction—optimum camcorder performance—maintains recording integrity. 3M Black Watch™ video tape is 100% laser inspected to guarantee surface smoothness and drop-out free performance. Priced at \$8.00

**You saw it here first!** 3M Black Watch™ 0900 8mm video tape cassette loaded into your Hi Band camcorder delivers the finest picture and sound possible in the 8mm format. Extremely fine particles of pure iron alloyed with nickel and cobalt deliver a video performance exceeding 400 lines of horizontal resolution. You get the advantage of an exceptional video image with superior audio re-

### EDUCATION & INSTRUCTION

**F.C.C. Commercial General Radiotelephone license.** Electronics home study. Fast, inexpensive! "Free" details. **COMMAND, D-176, Box 2824, San Francisco, CA 94126.**

**ELECTRONIC engineering.** 8 volumes complete. \$109.95. No prior knowledge required. Free brochure. **BANNER TECHNICAL BOOKS, 1203 Grant Avenue, Rockford, IL 61103.**

### PLANS AND KITS

**60 SOLDERLESS Breadboard Projects** in two easy-to-read pocket books. Complete with circuit descriptions, schematics, parts layouts, component listings, etc. Both books (BP107 & BP113) only \$11.90 plus \$3.50 for shipping. USA and Canada only. US funds. **ETT, INC., PO Box 240, Masapequa Park, NY 11762-0240.**

**SURVEILLANCE Transmitter kits, 65 to 305 MHz. Quick & Easy** Partially assembled units. Five minutes completion. 110-volt duplex receptacle, room battery types, and telephone. Counter-surveillance. Catalog: \$2.00. **SHEFFIELD ELECTRONICS, PO Box 377940-C, Chicago, IL 60637-7940.**

**CRYSTAL set Handbook** — Visit antiquity by building the radios your grandfather built. Assemble a "Quaker Oats" rig, wind coils that work and make it look like the 1920's! Only \$10.95 plus \$3.50 for shipping and handling. **CLAGG INC., PO Box 4099, Farmingdale, NY 11735.** US funds only! USA and Canada — no foreign orders.

**SURVEILLANCE/Countersurveillance, bugging/phone tapping detector, telephone/fax encryption, vehicle tracking, covert video, transmitters kit, and more... A.B. ELECTRONICS, 1(800)U-ANTI-BUG.**

**COUNTER-Surveillance technicians earn \$250.00 hr!** Free catalog and complete dealer information shows you how! 1 (800) 732-5000.

**FIBER Optics experimenters parts, supplies and tools:** Fiber, cable, connectors, splices, detectors, lasers, kits, plans, newsletter. Send \$2.00 for catalog. **LIGHTLINE ENGINEERING, PO Box 24, Mullica Hill, NJ 08062.**

**TOP quality imported, domestic kits; computers, components; surplus, discount electronics, parts; auto, home electronics; lasers. Catalog \$2.00. TEKTRASONIX, 740 E. Bay Avenue, Manahawkin, NJ 08050.**

**EASY to install, low cost, home/auto alarm system schematic diagrams/tips. \$14.95 QCDOBH, 270 North Canon #1632H, Beverly Hills, CA 90212-5323.**

**Clagg Inc. — 3M VHS Special Offer**  
 P.O. Box 4099,  
 Farmingdale,  
 New York 11735

Yes, I like your offer and here is my order for 3M Black Watch™ products!

- \_\_\_ 3M Black Watch™ 0900 Hi Band-120 8mm Cassette (\$14.95 each) \$ \_\_\_\_\_
- \_\_\_ 3M Black Watch™ T120 Hi Pro VHS 4410 Videocassette (\$8.00 each) \$ \_\_\_\_\_
- \_\_\_ 3M Black Watch™ Head Cleaner Videocassette (\$19.95 each) \$ \_\_\_\_\_

Shipping and handling per order \$4.00  
 Total Amount in U.S. Funds only \$ \_\_\_\_\_

New York residents add local sales tax. Canadians add \$6.00 per order. No foreign orders. Do not send cash.

Bill my  VISA  MasterCard  
 Card No. \_\_\_\_\_  
 Expire Date \_\_\_/\_\_\_/\_\_\_  
 Signature \_\_\_\_\_  
 Name (Please print) \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

**SUPPORT RESEARCH.**

It Works Wonders.

American Heart Association

March 1995, Electronics Now

# ALL ELECTRONICS

FAST SERVICE • DISCOUNT PRICES

## 7 Vdc MOTOR

Matsushita  
# MMX-7AC O 8A  
1.25" diameter x 1.25" high  
motor. Prepped with 1.61"  
diameter flywheel, pulley  
and fiberglass mounting  
board.



CAT# DCM-54

100 for \$80.00

**\$1.00**

## "HI-8" VIDEO CASSETTE (USED)

SONY HI-8 T-120  
Top quality, metal  
particle 120 minute  
video cassettes.  
Used for a short  
time, then bulk-  
erased, each  
cassette has its own plastic storage box.  
New, these high quality cassettes sell for  
considerably more.  
Satisfaction Guaranteed.



**\$3.00**  
each

CAT# VCU-8

10 for \$28.00 • 100 for \$250.00

## MINIATURE TOGGLE

### D.P.D.T. (ON-ON)

ALCOSWITCH # MTM206NPC  
Short bat handle, 0.25" long.  
PC terminals.



**\$1.25**  
each

CAT# MTS-82PC

25 for \$25.00 • 100 for \$90.00

## 9 VOLT 60 MA SOLAR PANEL



These 6" X 6" glass enclosed  
photovoltaic panels produce  
9 Vdc at 60 ma. Ideal for charging  
batteries and powering small devices.

Put two or more together for more current  
and voltage. Includes  
hook-up instructions.

**\$5.25**  
each

CAT # SPL-960

ORDER TOLL FREE

**1-800-826-5432**

CHARGE ORDERS to Visa, Mastercard or Discover

TERMS: Minimum order \$10.00. Shipping and handling for the  
48 continental U.S.A. \$4.00 per order. All others including AK,  
HI, PR or Canada must pay full shipping. All orders delivered  
in CALIFORNIA must include local state sales tax. Quantities  
limited. NO COD. Prices subject to change without notice.

CALL, WRITE or  
FAX for a FREE

64 Page  
CATALOG

Outside the U.S.A.  
send \$2.00 postage.

MAIL ORDERS TO:  
**ALL ELECTRONICS  
CORPORATION**  
P.O. Box 567  
Van Nuys, CA 91408  
FAX (818)781-2653

CIRCLE 107 ON FREE INFORMATION CARD

## ADVERTISING INDEX

Electronics Now does not assume any  
responsibility for errors that may appear  
in the index below.

Free Information Number	Page
212	Ace Communications . . . . . 117
—	Akizuki Denshi Tsusho Ltd. . . . . 93
213	Alfa Electronics . . . . . 110
107	All Electronics . . . . . 100
—	Allen Engineering . . . . . 106
325	Allison Technology . . . . . 128
—	AlphaLab . . . . . 114
217	B&S Sales . . . . . 121
284	Basic Electrical Supply . . . . . 112
198	Beige Bag . . . . . 5
291	Bel-Merit . . . . . 115
220	Blue Earth Research . . . . . 107
317	Cellsoft . . . . . 118
—	CLAGGK Inc. . . . . 99
—	CLAGGK Video . . . . . 27
—	Cleveland Inst. of Electronics . . . . . 31
—	Command Productions . . . . . 91
175	Computer Monitor Maint. . . . . 130
—	Comtrad Industries . . . . . 24
226	Consumertronics . . . . . 108
228	Cool Amp Conducto Lube . . . . . 102
230	Debco Electronics . . . . . 108
127	Deco Industries . . . . . 85
241	Electronic Goldmine . . . . . 109
—	Electronics Technology Today . . . . . 101
—	Fluke Corporation . . . . . CV2
130	Fotronic . . . . . 106
—	Geo-Ban Engineering . . . . . 127
199	Goldstar . . . . . 83
—	Grantham College of Eng. . . . . 15
—	Halcyon Group . . . . . 120
319	Highlander (Gault) . . . . . 104
—	ICS Computer Training . . . . . 93
—	Information Unlimited . . . . . 129
126	Interactive Image Technologies . . . . . 1
320	Island LogiX Inc. . . . . 127
—	ISCET . . . . . 95
132	ITC Instruments . . . . . 113
249	Kelvin Electronics . . . . . 125
—	M&G Electronics . . . . . 120
252	Meredith Instruments . . . . . 112
321	Micro 2000 . . . . . 103
197	Mini-Circuits . . . . . CV4
—	Mondo-tronics . . . . . 128
—	MWK Industries . . . . . 106
257	Needham Electronics . . . . . 116
—	NRI Schools . . . . . 11
71	NTE Electronics, Inc. . . . . 17
—	Oatley Electronics . . . . . 119
260	Ocean State Electronics . . . . . 123
195	Parallax . . . . . CV3
100	The School of VCR Repair . . . . . 95
—	Tab Books . . . . . 13, 56
92	Tektronix, Inc. . . . . 7
196	Tektronix, Inc. . . . . 23
275	Timeline . . . . . 132
323	Trisys . . . . . 116
183	Visual Communications . . . . . 95
98	Wavetek Corp. . . . . 12
324	Weka Publishing . . . . . 131
—	World College (Div. of C.I.E.) . . . . . 21
—	WPT Publications . . . . . 127
281	Xandi Electronics . . . . . 118

**Gernsback Publications, Inc.**  
500-B Bi-County Blvd.  
Farmingdale, NY 11735  
1-(516) 293-3000  
**Larry Steckler, EHF/CET**  
President

**Christina Estrada**  
assistant to the President

**For Advertising ONLY**  
516-293-3000  
Fax 1-516-293-3115

**Larry Steckler**  
publisher

**Arline Fishman**  
advertising director

**Denise Mullen**  
advertising assistant

**Kelly Twist**  
credit manager

**Subscriber Customer Service**  
1-800-288-0652

**Order Entry for New Subscribers**  
1-800-999-7139  
7:00 AM - 6:00 PM M-F MST

## ADVERTISING SALES OFFICES

### EAST/SOUTHEAST

**Stanley Levitan**  
Eastern Advertising  
1 Overlook Ave.  
Great Neck, NY 11021  
1-516-487-9357  
Fax 1-516-487-8402

### MIDWEST/Texas/Arkansas/Okla.

**Ralph Bergen**  
Midwest Advertising  
One Northfield Plaza, Suite 300  
Northfield, IL 60093-1214  
1-708-446-1444  
Fax 1-708-559-0562

### PACIFIC COAST

**Blake Murphy**  
Pacific Advertising  
Hutch Looney & Associates, Inc.  
6310 San Vicente Blvd.  
Suite 360  
Los Angeles, CA 90048  
1-213-931-3444  
Fax 1-213-931-7309

**Electronic Shopper**  
**Joe Shere**  
National Representative  
P.O. Box 169  
Idyllwild, CA 92549  
1-909-659-9743  
Fax 1-909-659-2469


# Electronic SHOPPER<sup>®</sup>

## Paperback Books

GREAT PAPERBACKS AT SPECIAL PRICES

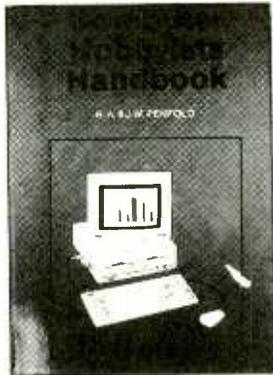**COMPUTER HOBBYISTS HANDBOOK—BP251—\$8.95**


Subjects covered include microprocessors and their register sets; interfacing serial, parallel, monitor, games and MIDI ports; numbering systems, operating systems and computer graphics. While the book is aimed at the computer hobbyist, it should also prove useful to anyone who intends to use a computer to follow their interests.



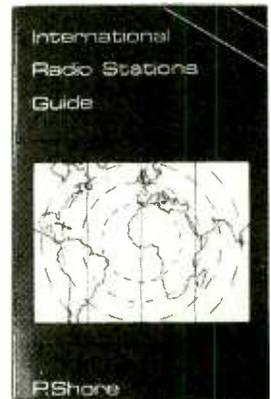**INTERNATIONAL RADIO STATIONS GUIDE—BP255—\$9.95**


Provides the casual listener, amateur radio DXer and the professional radio monitor with an essential reference work designed as a guide for the complex radio bands.

Includes coverage on Listening to Short Wave Radio, ITU Country Codes, Worldwide Radio Stations, European Long Wave and Medium Wave Stations, Broadcasts in English and more.




**Further Practical Electronics Calculations and Formulae**

I. A. WILSON

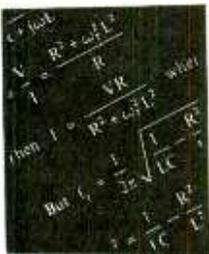

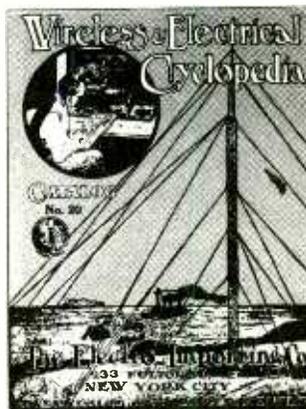**FURTHER PRACTICAL ELECTRONICS CALCULATIONS—BP144—\$9.00**

450 pages crammed full of all the formulae you are likely to need. Covers Electricity, Electrostatics, Electromagnetism, Complex Numbers, Amplifiers, Signal Generation and Processing, Communications, Statistics, Reliability, Audio, Radio Systems, Transmission Lines, Digital Logic, Power Supplies. Then there's an appendix of Conversion Factors, Mathematical Formulae and more.



**WIRELESS & ELECTRICAL CYCLOPEDIA—ETT1—\$5.75**

A slice of history. This early electronics catalog was issued in 1918. It consists of 176 pages that document the early history of electricity, radio and electronics. It was the "bible" of the electrical experimenter of the period. Take a look at history and see how far we have come. And by the way, don't try to order any of the merchandise shown, it's unlikely that it will be available. And if it is, the prices will be many times higher.

**ELECTRONIC TECHNOLOGY TODAY INC.**  
P.O. Box 240, Massapequa Park, NY 11762-0240

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

EN395

**SHIPPING CHARGES IN USA AND CANADA**

\$0.01 to \$5.00 . . . . .	\$1.50
\$5.01 to \$10.00 . . . . .	\$2.50
\$10.01 to 20.00 . . . . .	\$3.50
\$20.01 to 30.00 . . . . .	\$4.50
\$30.01 to 40.00 . . . . .	\$5.50
\$40.01 to 50.00 . . . . .	\$6.50
\$50.01 and above . . . . .	\$8.00

**SORRY No orders accepted outside of USA & Canada**

Total price of merchandise . . . . .	\$ _____
Shipping (see chart) . . . . .	\$ _____
<b>Subtotal</b> . . . . .	\$ _____
Sales Tax (NYS only) . . . . .	\$ _____
<b>Total Enclosed</b> . . . . .	\$ _____

All payments must be in U.S. funds


Number of books ordered

March 1995, Electronics Now


# In recent independent tests Cool-Amp is proven better than electroplating.

(For 50 years we've said Cool-Amp is "equal to" electroplating in performance. It is better.)

## Cool-Amp

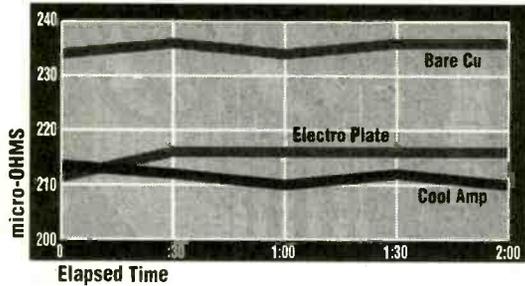

## Conducto-Lube

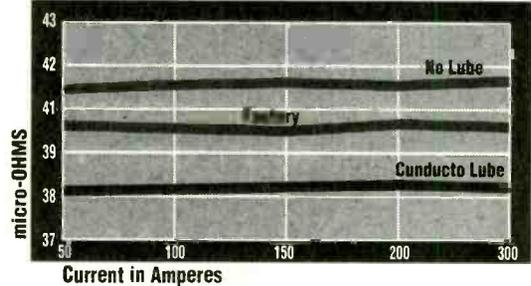

### From the report:

"...compare the conducting properties of Cool-Amp silver plating compound with factory silver electro-plated bus and bare copper bus.

"The test results indicated that the contact resistance of the Cool-Amp plated bus connection was slightly lower than that of the electro-plated bus connection and much lower than that of the bare copper bus connection. The final temperature at temperature equilibrium of the bus connection employing Cool-Amp was slightly lower than that of the electro-plated bus connection and the bare copper bus connection..."


### From the report:

"...compare the conducting properties of Conducto-Lube lubricant with factory lubrication and non-lubricated connections on an air switch. Identical test setups and procedures were used for each test so that comparative data could be collected and the relative performance of each type of connection could be quantified.

"The test results indicated that the contact resistance of the switch employing Conducto-Lube was generally lower than that of the factory lubricated switch and the switch that used no lubricant."
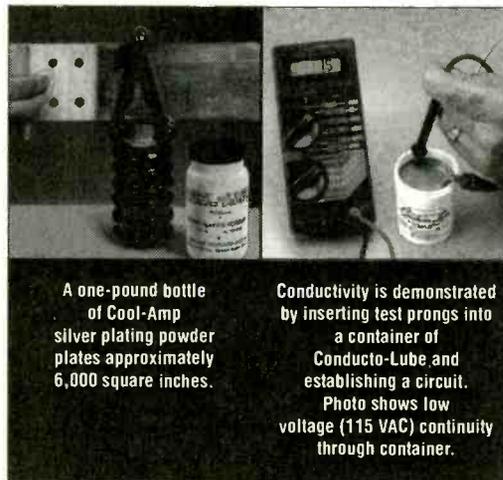
### Cool-Amp How it works:

- Applies *on the job*. Application is simple. Yet Cool-Amp adheres permanently. As tests show, it is better than electroplating.
- Minimizes overheating and power loss by silver plating high amperage connections.
- Saves time, reduces maintenance. Cool-Amp is so simple to apply on the job. It assures maximum conductivity for copper, brass, or bronze contacts and prevents losses due to oxidation.



A one-pound bottle of Cool-Amp silver plating powder plates approximately 6,000 square inches.

Conductivity is demonstrated by inserting test prongs into a container of Conducto-Lube and establishing a circuit. Photo shows low voltage (115 VAC) continuity through container.

### Conducto-Lube How it works:

- This is *the* conductive lubricant; highly conductive because it contains pure silver.
- Originally developed to lubricate switches, to the point tension can be adjusted to factory specs allowing full rated capacity of the switch to be maintained at all times.
- Uses have continued to expand—from switches and breakers—to any application where a conductive lubricant is needed.

\*Various tests were performed on both products in the Electro-Test, Inc. facilities in Portland, Oregon during January-March, 1994. Evaluation of plating thickness of Cool-Amp was performed by Surface Science Laboratories of Mountain View, California.

**COOL-AMP**

*Conducto-Lube*


### Cool-Amp Conducto-Lube Company

15834 Upper Boones Ferry Road  
Lake Oswego, Oregon 97035  
Order factory direct:  
503/624-6426, Fax 503/624-6436
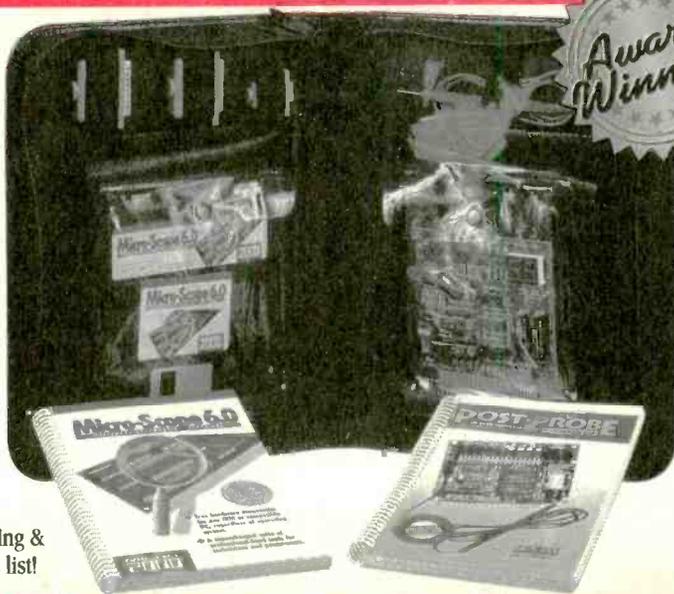
# Get the Best Universal Diagnostics Toolkit on the market!

Works on any PC!

Featuring these  
two top-rated,  
award-winning  
diagnostic  
tools from  
**MICRO 2000, Inc.:**



Award  
Winning

Winners of these awards:



"You name it,  
this tests it. If you  
maintain PC's,  
you'll love it."  
—Jerry Pournelle,  
BYTE Magazine, May 94



Govt. Serv. #: GS-00K-94AGS-5396

New  
Version  
Release

Call for upgrade pricing &  
complete new features list!

## Micro-Scope 6.0

UNIVERSAL DIAGNOSTIC SOFTWARE

Fully O/S independent  
diagnostic software...

**MICRO-SCOPE** Universal Computer Diagnostics was developed to satisfy the expanding need for accurate system diagnosis in the rapidly growing desktop computer market. Patterned after super-mini and mainframe diagnostic routines, **MICRO-SCOPE** runs independently of any standard operating system, and is therefore at home on any machine in the Intel world. Speed, ease-of-use, and razor sharp accuracy are a few of the advantages that arise from this system independence, together with an impressive list of functions including the ability to perform low level formatting on every drive currently manufactured, including all IDE drives.

- ◆ **LOW-LEVEL FORMAT**—Performs Low-level format on all drive types including IDE drives. This function cannot hurt IDE drives.
- ◆ **USE CONTROLLER BIOS**—Program will access BIOS format built into any hard disk controller—even Controllers yet to be invented.
- ◆ **O/S INDEPENDENT**—Does not rely on O/S for diagnostics. Talks to PC on hardware level. All tests are full function regardless of O/S (i.e. Novell, UNIX, OS/2).
- ◆ **TRUE HARDWARE DIAGNOSTICS**—Accurate testing of CPL, IRQ's, DMA's, memory, hard drives, floppy drives, video cards, etc.
- ◆ **BATCH CONTROL**—All tests, even destructive, may

be selected for testing. ◆ **ERROR LOGGING**—Automatically inputs errors during testing to an error log.

- ◆ **AUTOMAPPING**—Automatically bad sector maps errors found on hard disks.
- ◆ **IRQ DISPLAY**—Show bits enabled in IRQ chip for finding cards that are software driven. (Network, Tape Backup, etc.)
- ◆ **IRQ CHECK**—Talks directly to hardware and shows I/O address and IRQ of devices that respond.
- ◆ **MEMORY EXAMINE**—Displays any physical bit of memory under 1 Meg. Very useful for determining memory conflicts. Very useful for determining available memory space.
- ◆ **SECTOR EDITOR**—Allows the editing of any sector of floppy or hard disk media (even track 0).
- ◆ **AND MUCH MORE**—We don't have enough space here for everything this software can do!

## POST-PROBE

1ST EVER UNIVERSAL POST CARD FOR ALL PCs!

The only Power-On Self-Test  
card you need to debug any  
"dead" PC...

"This is the only card that will function in every system on the market. The documentation is extensive, and not only covers the expected POST Codes for different BIOS versions, but also includes a detailed reference to the bus signals monitored by the card."  
—Scott Mueller from his globally recognized book, 'Upgrading & Repairing PCs, Second Edition'

- ◆ Includes pads for voltmeter to attach for actual voltage testing under load.
- ◆ 4 LEDs monitor +5vdc -5vdc +12vdc -12vdc.
- ◆ Monitors Hi & Lo clock and OSC cycles to distinguish between clock chip or crystal failure.
- ◆ Monitors I/O Write and I/O Read to distinguish between write and read errors.
- ◆ Monitors memory write/ read to distinguish between address line failures and memory chip failures.
- ◆ Monitors M/F for proper CPU/DMA operation.
- ◆ Monitors Reset to determine if reset is occurring during POST, indicating short.
- ◆ Monitors progress of POST *without* POST codes.
- ◆ Reads POST codes from any IBM or compatible that emits POST codes. ISA/EISA/VMECA.
- ◆ Compatible with Micro Channel computers.
- ◆ Dip switch allows easy selection of I/O ports to read.
- ◆ Includes tri-state **LOGIC PROBE** to determine actual chip failures.
- ◆ Manual includes chip layouts and detailed POST procedures for all major BIOS's.
- ◆ **AND MUCH MORE...**

Also Ask About our Other Universally  
Compatible Products—

**MICRO-SCOPE CLIENT:** The practical answer to remote diagnosis (no modem required).

**THE COMPUTER CONSULTANT:** 100% accurate real-time benchmarking tool.

**MICRO-SCOPE CENSUS:** Inventory software to see and record what's inside all of your PCs.

**911-RECOVER:** Proof/proof data recovery for everyone.

**MICRO  
2000**

Call Now for Special Pricing: **1-800-864-8008** or Fax (818) 547-0397

1100 East Broadway, Suite 301, Glendale, California • Phone 818/547-0125 • Fax 818/547-0397

International Orders please call: MICRO 2000 Australia: 61-42-574144 • MICRO 2000 Europe (UK): 44-462-483-483

CIRCLE 321 ON FREE INFORMATION CARD

www.americanradiohistory.com

# WE HAVE WHAT YOU

**\$59**

Converter only

**\$125**

With built-in  
Stealth descramblers  
for all Jerrold Systems  
except Baseband



**BRAND  
★ NEW ★**

- ★ 550 MHZ Converter
- ★ Wireless Remote
- ★ STD/HRC Switchable
- ★ Last Channel Recall

**Introducing the MERLIN!  
Available from Highlander Now!!!**

- I. *Merlin I* replaces all **Pioneer** and **Scientific Atlanta**, including Baseband
- II. *Merlin II* replaces all **Tocom** models
- III. *Merlin III* replaces all **Zenith PZ** and **PM** models.

- ★ 550 MHZ
- ★ Volume Control
- ★ Parental Lock-out
- ★ Wireless Remote
- ★ Last Channel Recall

**Call for pricing**



# HIGHLANDER

**6325-9 Falls of the Neuse Road, Raleigh, NC 27615**

CIRCLE 319 ON FREE INFORMATION CARD

www.americanradiohistory.com

# WANT AND MORE !!!



TVT-GOLD	\$42	PIO+	\$65
TVT-MINI	\$42	GREEN	\$65
FTB	\$39	SA-3	\$43
SIP/PURPLE	\$49	M-80	\$65
STEALTH	\$50	TNT	\$65

## FACTORY EQUIPMENT

ST 1600	\$239	DRZ-DIC	\$ 79
6300	\$319	SB-3	\$ 19
6150	\$299	DPV-7	\$249

All makes and models available!!!



## NOVAVISION

The Novavision offers video pass-through technology and a host of advanced features including parental control, favorite channel memory, last channel recall, volume control, sleep timer, and channel ID, all controlled by a simple, user-friendly, menu-driven on-screen display system. While others talk about the future, we deliver it...now! Only with Novavision!

All prices are for 10 pieces, subject to change without notice. Some quantities may be limited. 30-Day Money Back Guarantee. One year parts and labor warranty.

### \$199

#### NV 56 COMBO

Pioneer compatible. Replaces all models 5000-6310.

#### NV 57 COMBO

Jerrold/GI compatible. Replaces all models except baseband.

#### NV 58 COMBO

Scientific Atlanta compatible. Replaces all models except baseband.

## TEST KITS

#### For JERROLD

Star 7 BB	\$13
Star 6 BB	\$13
DP-5	\$10
R2/V5/CFT Kit	\$29 <sup>99</sup>

#### For PIONEER

51XX-61XX	\$25
<b>NEW!!!</b> Pio Kit	
Never Goes E-4	\$29 <sup>99</sup>

#### For TOCOM

5503	\$14
5507	\$14

#### For ZENITH

ST-1000-ST 16XX	\$11
-----------------	------

#### For SCIENTIFIC ATLANTA

Motorola Micros	\$19 <sup>99</sup>
Quick Boards	CALL
8 Wire Spider Board	\$17 <sup>50</sup>

# 1-800-854-7119

Mon-Fri 10-7 EST; Sat 10-3 EST-FAX 1-800-854-7118

CIRCLE 319 ON FREE INFORMATION CARD

www.americanradiohistory.com

# New and Pre-Owned Test Equipment

SALES • RENTALS • SERVICE

Substantial Savings on new & pre-owned Fluke, Hewlett Packard, Leader, Tektronix and more ...

**LEADER**  
FOR PROFESSIONALS WHO KNOW THE DIFFERENCE



Sale  
Call for latest sale price!

We buy surplus Electronic Equipment. Fax us your list!

\* Pre-Owned Oscilloscope Specials \*

- Tektronix 465 100 MHz.....\$499.00
- Tektronix 465B 100 MHz.....\$599.00
- Tektronix 475 200 MHz.....\$679.00

Fully refurbished and calibrated to original specifications

OSCILLOSCOPES		Reg. \$
8020	20 MHz 2-Ch. High Sens., TV Sync.....	\$525.00
8060	60 MHz 3-Ch. Dlyd. Swp., TV Sync.....	\$1,345.00
8100	100 MHz 2-Ch. Dlyd. Swp., TV Sync.....	\$1,595.00
FREQUENCY COUNTERS		
LDC-822	80 MHz, 7 digit, 5 ppm.....	\$395.00
LDC-823S	250 MHz, 8 digit, 1 ppm.....	\$595.00
FUNCTION & RF SIGNAL GENERATORS		
LFG-1300S	2 MHz Sweep/Function Generator.....	\$575.00
LFG-1310	10 MHz Sweep/Function Generator.....	\$1,095.00
POWER SUPPLIES		
LPS-151	Triple Output, +6V/3A, +/- 25V/0.5A.....	\$555.00
LPS-152	Triple Output, +6A/5A, +/- 25V/1.0A.....	\$645.00

Full line of Oscilloscopes, Video & Audio Test Equipment, Power Supplies, Probes and Accessories. Call for a FREE Line Catalog!



TOLL FREE 1-800-99-METER




For more GREAT VALUES Call, Write or FAX • P.O. Box 708, Medford, MA 02155 • FAX (617) 665-0780

CIRCLE 130 ON FREE INFORMATION CARD
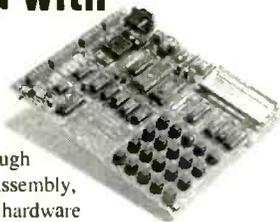
## Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING with the AES-10

The AES-10... a complete learning system, a complete embedded control system. Extensive manuals guide you through your 8051 development project. Assembly, BASIC, and C programming. All hardware details, complete schematics. Learn to program the LCD, keypad, digital and analog I/Os for your applications.



80C32 Computer/Microcontroller board with:

- 32K ROM • 32K RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Digital, A/D, D/A, and PWM, I/O • Built in Logic Probe • Power supply (can also be battery operated) • Extended AES BASIC and AES Monitor in ROM • RS-232 cable to connect to PC for programming • 8051/52 DOS Cross Assembler • Program disks with well documented examples • User's Manual, Language Manual, and Textbook • AES-20 (a smaller board without Keypad and LCD)


AES-10 \$365  
Money Back Guarantee

AES-20 \$245  
Free Brochure, M/C Visa  
714 - 744-0981  
Fax 714 - 744-2693

800 - 730-3232



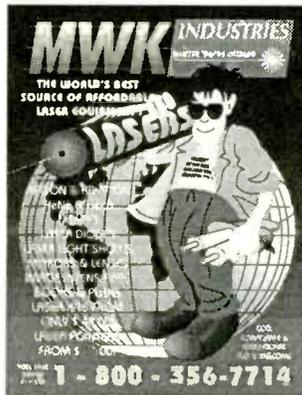1407 North Batavia Street, Orange, California 92667, USA



IT'S  
HERE!  
YOUR  
NEW  
MWK

## L A S E R C A T A L O G IS NOW AVAILABLE!

Hundreds of LASERS, LASER experiments, plans, LASER light-shows, books, hard-to-find items, all at surprisingly affordable prices.

Call for your free copy today!

(909) 278-0563

ALSO USE OUR FAX-ON-DEMAND CATALOG

(909) 278-1225

24hr catalog, call from your FAX machine.

# eXplore the Opportunities

## Create Your Own Automated Systems Using Xplor PDCs and Simple BASIC Programs

Xplor Personal Digital Controllers can propel you into the wide open frontier of computerized control and monitoring with minimal effort and cost. No mere novelty, these "mini-sports" pack surprising power and are loaded with extras that make the journey from idea to working reality fun and rewarding.

Professionals will find Xplor PDCs an efficient, economical way to add simple, yet reliable control capabilities to prototypes or full-scale production runs. Beginners and hobbyists can use PDCs to sharpen their programming skills while developing original concepts. Just identify a need and hit the accelerator - Embedded Control, Simple Robotics, PC Peripherals, Monitoring Systems, Data Logging - Xplor PDCs will take you to the far reaches of your imagination.




**XPLOR™ 32c \$89.95**

- 80C32 CPU with 12 digital I/O lines
- 64K bit EEPROM for program/data storage
- I/O socket block for transistors, resistors, etc.
- Screw terminal block and project case.

Also available with 11 channel 10-bit A/D converter - Xplor-32ca
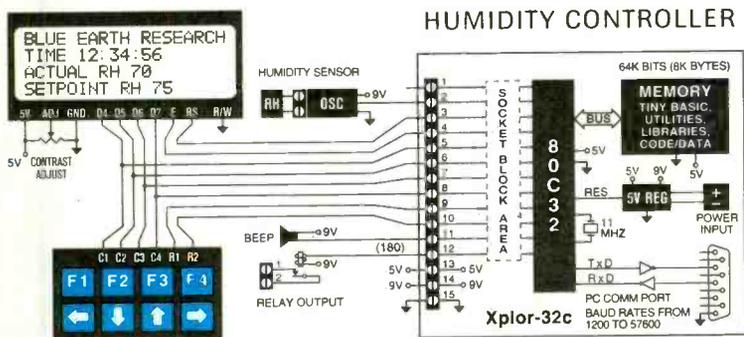
## Built-in BASIC Language, Powerful Utilities, and Library Functions Make Programming Easy

The example below shows how easy it is to wire-up and program the Xplor-32c for a simple on/off controller application. The built-in software gives you the power to write programs like this in just minutes. Your program is stored in nonvolatile memory and will automatically execute when power is applied.



**ALL YOU NEED IS A PC and a Terminal Program**  
(Or Xplor Starter Package)


**No Other Programming Equipment Required!**

```

10 CALL 8132 (LIBRARY FUNC: Initialize LCD)
20 ONTIME 200 (Initialize 1 second interrupt)
30 PRINT "BLUE EARTH RESEARCH"; (Display sign-on message)
40 PRINT "\\ ACTUAL RH "; FREQ 0; (Display actual sensor frequency)
50 PRINT "\\ SETPOINT RH "; S; (Display desired setpoint value)
60 CALL 8140 (LIBRARY FUNC: Get keypad input)
70 IF DBY 27=6 THEN S=S-1 (Decrement setpoint if down arrow)
80 IF DBY 27=7 THEN S=S+1 (Increment setpoint if up arrow)
100 IF FREQ 0<S THEN BIT 180=1 (If actual < setpoint then relay on)
110 IF FREQ 0>S THEN BIT 180=0 (If actual > setpoint then relay off)
120 GOTO 40 (Loop back to repeat program)
200 PRINT "\TIME "; DBY 51; ": "; (This 1 second interrupt routine)
210 PRINT DBY 50; ": "; DBY 49; ": IRET (refreshes LCD with current time.)
    
```

CIRCLE 220 ON FREE INFORMATION CARD
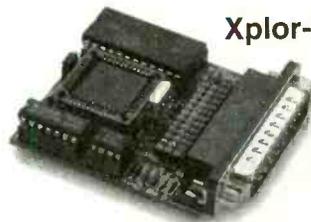
## Xplor PDCs - MORE CHOICES FOR GREATER FLEXIBILITY



**Xplor-32 \$59.95**

Same features as the 32c less case and terminal block. Board is only 2.15" x 2.2".

**Xplor-32a \$79.95**

with 11 channel 10-bit A/D converter.

**Xplor-32d \$79.95**

with 24 extra digital I/O lines.

## Complete Packages from \$99.95

All Xplor PDCs are available in starter packages that include the Xplor board, screw terminal blocks, RS-232 cable, 9V power supply, users manual, application notes, and MSDOS format disk. The disk includes sample BASIC programs, library source code, BXA-51 and TB-QComm. The BXA-51 assembler can be used for making library changes or other assembly language programming. TB-QComm is a communications utility that allows you to load HEX files and load, edit, or save BASIC programs.



## SUPPORT PERIPHERALS

To complete your projects, we offer various peripherals including a customizable 4x4 keypad, dot matrix LCD modules, X-10 power line modules, pressure, temperature, and humidity sensors, screw terminal interface boards, etc.

For more information on Xplor PDCs, or our many other Creative Microcontroller Solutions, call today for our free 28 page catalog.



**BLUE EARTH™ RESEARCH**

165 West Lind Ct., Mankato, MN 56001  
Voice: 507-387-4001 FAX: 507-387-4008  
BBS: 507-387-4007



March 1995, Electronics Now

# Decco Electronics

4025 Edwards Road, Cincinnati, OH 45209

Toll Free Order Hot Line 1 (800) 423-4499  
Information - (513) 531-4499

## Millions of Chips, Transistors and Components in Stock!

74LS00	74LS192	74HC75	LM318	MC1404	ICM7556
74LS01	74LS193	74HC76	LM319	MC1406	ICM7660
74LS02	74LS194	74HC79	LM322	MC1408	ICM7663
74LS03	74LS195	74HC109	LM323	MC1411	ICM7665
74LS04	74LS196	74HC123	LM324	MC1414	ICM7668
74LS05	74LS197	74HC125	LM325	MC1456	ICM7671
74LS06	74LS221	74HC132	LM329	MC1458	LF13741
74LS07	74LS224	74HC138	LM331	LM1488	5017000
74LS08	74LS240	74HC139	AM333	DS14C08	5017007
74LS09	74LS241	74HC151	LM334	LM1489	5017126
74LS10	74LS242	74HC152	LM335	DS14C09	5017129
74LS11	74LS243	74HC157	LM336	LM1490	5017130
74LS12	74LS244	74HC158	LM337	TCM1520	5017150
74LS13	74LS245	74HC161	LM338	MC1558	5017154
74LS14	74LS246	74HC163	LM339	MC1566	5017159
74LS15	74LS247	74HC164	LM339	MC1733CL	129 75174
74LS16	74LS248	74HC165	LM339	LM1830	459 75176
74LS17	74LS249	74HC166	LM339	LM1831	459 75183
74LS18	74LS251	74HC167	LM339	LM1881	495 75189
74LS19	74LS252	74HC168	LM339	LM1889	395 75202
74LS20	74LS253	74HC169	LM339	LM1929	75365
74LS21	74LS254	74HC170	LM339	LM2003	75481
74LS22	74LS255	74HC171	LM339	LM2004	75452
74LS23	74LS256	74HC172	LM339	LM2007	75453
74LS24	74LS257	74HC173	LM339	LM2008	75454
74LS25	74LS258	74HC174	LM339	LM2009	75477
74LS26	74LS259	74HC175	LM339	LM2010	75491
74LS27	74LS260	74HC176	LM339	LM2011	75492
74LS28	74LS261	74HC177	LM339	LM2012	75493
74LS178	74LS411	74HC327	LM339	LM2162	75643
74LS17					

### HIGH QUALITY SOLAR PANEL



**FRONT** **BACK**  
Brand new solar panels made to provide the power for call boxes on the California freeway system! These are glass type panels with a nice frame and a snap in heavy duty power connector. Use it to trickle charge your car battery or electric boat battery. Power radios, power transmitters, small fans, etc. Size about 12" x 6 1/8". Peak output power: 2.25 watt, VDC: 22.5V, ISC: 170 mA. Normal operating voltage 14.5V at 150mA. With 2 ft. long connection cable with connector.

**G6415**  
was \$29.95 **SALE! ONLY \$19.95!**

**Optional:**  
Car adaptor plug and diode to prevent discharge at night. **G6431 \$1.25**

### SPORTSCAR PHONE

Sporty phone for the car enthusiast in your family. These are bright red and black sports car shape. They are sleek with a contemporary design. Features: redial, mute buttons, ringer on/off, tone/pulse switchable. Complete and ready to go with instructions and cable. In sealed blister packs. Model F40.

**G6138**  
was \$16.95 **SALE! ONLY \$12.00!**

### 2 IN 1 PERSONAL & DOMESTIC ALARM

This is actually 2 alarms in one. Hang it on any metal door knob and the instant that an intruder touches the outside knob it sounds off. It also is designed to be a great personal emergency alarm. Simply pull out the metal chain and the alarm sounds continuously to call for help. No installation or wiring needed. Operates on one 9V battery (not included). In retail box. Size: 2 3/16" x 4 1/4" x 1"

**G6151**  
was \$14.95 **SALE! ONLY \$7.95!**

**ULTRABRIGHT SMD RED LED**  
Very intense clear lens tiny SMD ultrabright red LED made by Panasonic Type LN1261CAL Prime-on-tape and reel. **G6447 \$4/\$1.00**


### ELECTRONIC SURPRISE BOX



We have a tremendous quantity of various items which we have too few to advertise. We have packaged a good assortment containing various semiconductors, resistors, capacitors, hardware, coils, etc. None of these items are seconds or rejects - all are factory prime and the package is really worth the price!

**\$2200 \$3.00**

### HEAVY DUTY 12VDC MOTOR

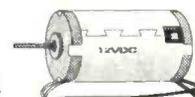

Made by Barber Coleman, these high quality 12VDC motors have a separate set of leads that put out an AC voltage in proportion to the shaft speed which can be measured on a meter. The part # is FYQM-33560-4. New, high quality with great torque. Use in robots or hundreds of other applications. Size: 1 7/8" L x 1 1/4" Dia. with 5/8" long shaft. **G6539 \$2.95**

### DC TO DC CONVERTER

Super efficient tiny DC to DC converter converts lower voltage DC to a higher voltage DC (see table below). These are brand new made by TDK and are only 1 3/8" L x 7/8" W x 3/8" T. Very efficient and latest technology using SMD and standard technology. Power a 9V transistor radio from 1 AA battery, charge several AA batteries from one solar cell, power a 9V project using 1 or 2 AA cells, etc. Has only 4 leads (+ in and + out). With hookup diagram.

Power Table		
Voltage Input DC	Voltage Output DC	Current Output
0.5VDC (solar)	3V	1mA
1.5VDC	9V	15mA
3VDC	9V	40mA

**G6344 \$3.98**

### CONTROL PANEL KEYBOARD

Keyboard with 6 LEDs and ribbon cable. Make fake alarms as this is the same unit found on the front door control panels for many professional home alarms. Size: 4 9/16" sq. **G2904**

was \$3.00 **SALE! ONLY \$2.75!** 10/\$23.00

**IF YOU CAN'T FIND WHAT YOU ARE LOOKING FOR, CALL FOR A FREE COPY OF OUR LATEST CATALOG. THIS CATALOG CONTAINS OUR ENTIRE PRODUCT LINE OF OVER 3,000 ITEMS AND IT IS STILL GROWING!**

### UNIVERSAL BREAD-BOARD

Giant project board is very handy for making all types of prototype circuits. Has 126 groups of 5 connected terminal points. The grid is alphanumeric labeled for ease of use. In addition to the main group of terminals, it also has 8 bus lines of 25 connected terminals. Simply insert your components and jumper wires to make electronic prototypes without PC boards. Overall size: 6 1/2" x 2 1/8". **G6042 \$5.00**

**INSULATED JUMPER WIRES** (for the above)  
3 inch long orange .4 inch long yellow  
**G6043 G6044**  
YOUR CHOICE **25/\$1.00**

### TDK VOLTAGE CONVERTER

Brand new voltage converter converts 3VDC to 9VDC. Size only 1 7/8" x 1 3/16" x 1/4". Made by TDK for a major manufacturer. Output current is 60 ma at 9VDC. Use 2 pentight batteries to operate transistor radios, calculators, etc. or any electronic device that can operate on 9VDC at up to 60ma. With hookup diagram (only 3 leads are used). **G6546 \$2.00**

### HEAVY DUTY 12VDC MOTOR WITH REGULATOR

Precision 1 7/16" Dia motor has a 3 transistor regulator board attached. We don't have the hookup diagram on these, but they look like sophisticated electronic regulator boards. Size of board: 1 1/2" x 2 1/8". Size of motor: 1 7/16" Dia x 1 7/8" L. The shaft is a "D" type and 1/2" long. Brand new - no other info available except that these were made by Sonar Radio Corp., part# 27-030-008. **G6540 \$1.50**

### TINY TRACKBALL

Made for a tiny laptop!  
This is probably the tiniest trackball ever made! It measures only 1 1/16" L x 13/16" W x 3/8" H. Made by Alps for a major laptop computer maker that went out of business. They are very precision made and highest quality. The components are all SMD with an IC marked 3JA1D7002/T86012CF and a tiny 8 position connector. They appear to be complete, new and very recent in manufacture. We have no hookup info or schematic, but at this price we know that you'll be impressed and want to experiment with them. Use them for replacement or figure out the hookup! Hurry, these may not last long! **G5514 \$1.95 10/\$15.00**

### MAGIC SOUND SWITCH

Small circuit board triggers a scr from a built in microphone circuit. Turn on low voltage lamps, motors, relays etc. Operates from 3VDC. Comes with schematic. Size only about 2" square. **G5554 \$1.00**

### SUPER SENSITIVE SOUND ACTIVATED 2 CHANNEL COLOR ORGAN

This ultra sensitive 2 Channel Color Organ produces brilliant flashes of light (from any incandescent lamps of your choice - up to 200W) in response to music or other sounds. This is probably the best and brightest color organ we have ever seen. It is fully assembled (except for line cord and outlets) and features 2 response controls, on/off switch, sensitive FET microphone (no hookup to stereo needed) and 3 transistor, 2 SCR circuitry. Operates from standard 120VAC and requires only that you solder your line cord and 2 outlets (for your lamps) to the board. We strongly recommend that you install the color organ in an insulated case for safety reasons as it operates from the AC line. Connect up a couple of your brightest, colorful lamps and watch the fireworks with each beat of the music! Great for DJ's as there is no connection to the sound source. Size of board 3 3/4" x 4 1/4". Color organ board only - you supply lamps, line cord, knobs, case and outlets. Hurry, these will sell very fast! **G3319 was \$5.95 SALE! ONLY \$4.95!**

### COLLAPSIBLE ANTENNAS

Chrome plated collapsible antennas for replacement or new construction. Most have 8 sections. We have 5 different types. NOTE: These are new but they may have slight marks or scratches because they were packaged in bulk. Antennas only - no mounting hardware.

Stock#	Collapsed	Extended	Price
G6541	3 7/8"	18"	\$1.00
G6542	4 7/8"	26"	\$1.25
G6543	5 3/4"	38"	\$2.00
G6544	6 1/2"	26"	\$1.25
G6545	7"	28"	\$1.75

### HI-FI AM RADIO CHASSIS

Make a great sounding AM radio using this chassis. You'll be impressed by how good it sounds! Complete chassis features sensitive 7 transistor circuit with volume, tone and tuning controls on a fully assembled chassis - you only need to provide a speaker and 12VAC or DC to power it. You may want to build a creative antique or an ultra-modern style cabinet. Output is 2 watts. Size: 2 1/2" x 5" With wire hookup information. Radio Chassis only - adaptor and speaker sold separately. **S2022**

was \$3.00 **SALE! ONLY \$2.49!**

### TRI COLOR RECTANGULAR LED

White diffused case LED can light up red, green or yellow (when both red and green are lit at the same time). Prime-made by Sharp. **G6434 \$4/\$1.00**

NOTE: All sale prices advertised are valid only through the month of the cover date.

**For Phone Orders Call (602) 451-7454**  
**Or Fax Your Orders To (602) 451-9495**



Minimum Order: \$10.00 plus \$4.00 Shipping and Handling. We accept MasterCard, Visa and Money orders. Canadians and others that need US MAIL send minimum \$5.00 S&H.

**ELECTRONIC GOLDMINE**  
P.O. Box 5408  
Scottsdale, AZ 85261

CIRCLE 241 ON FREE INFORMATION CARD

# ALFA ELECTRONICS

HIGH QUALITY TEST EQUIPMENT  
BEST PRICE



**DMM 89 \$199.95**  
**Most Advanced DMM**  
*All Purpose & Communication*  
-80.7 to 81.4 dBm with 4Ω -1200Ω  
20 reference impedances  
True RMS  
Frequency counter: 0.01Hz-10MHz  
Capacitance: 1pF-50,000μF  
Measure AC volt to 20kHz  
5000 counts, 0.1% accuracy  
Auto/manual range, fast bar graph  
Min/Max/Ave/DH/R/Relative/Zoom  
Auto power off  
Input warning  
Splash proof  
Volt, amp, ohm, logic, diode, continuity  
Ruggedized case  
Rubber holster included



**DMM 2360 \$119.95**  
**DMM+LCR Meter**  
*Very Versatile DMM*  
Inductance: 1μH-40H  
Capacitance: 1pF-40μF  
Frequency: 1Hz - 4MHz  
Temperature: -40-302 °F  
TTL Logic Test: 20MHz  
Diode, Continuity  
Volt, Amp, Ohm  
3999 count display  
Peak Hold  
Auto power off  
Ruggedized case.  
Temperature probe included  
Rubber Holster \$8.00



**DMM 20 \$74.95**  
Inductance: 1μH-40H  
Capacitance: 1pF-200μF  
Frequency: 1Hz-20MHz  
Volt, amp, ohm, diode,  
20 Amp AC/DC current  
Transistor hFE  
Continuity, duty %  
Peak hold/Max  
Ruggedized case  
Rubber holster \$8.00

Full line of DMMs,  
economy, compact,  
ruggedized, solar cell,  
automotive, heavy  
duty, industrial,  
starts from \$15.95


Fluke Multimeter  
Fluke 12 \$84.95  
Holster C-10 \$10  
Fluke 70 II \$67.5  
Fluke 73 II \$94  
Fluke 75 II \$129  
Holster C-70 \$169  
Fluke 77 II \$149  
Fluke 79 II \$169  
Fluke 29 II \$169  
Fluke 83 \$225  
Fluke 85 \$259  
Fluke 87 \$287  
Fluke 97  
Scope Meter \$1785



**LCR Meter 131D \$229.95**  
**Most Advanced LCR**  
Dual display: L/Q or C/D  
Inductance: 0.1μH-1000H  
Capacitance: 0.1pF-10,000μF  
Impedance: 1mΩ-10MΩ  
0.7% basic accuracy  
Auto/manual range  
Dissipation factor & Q factor  
Serial & parallel mode  
Relative mode for comparison  
and to remove parasitics  
Statistics, tolerance,  
Best for design, incoming  
testing & production  
SMD and chip component  
test probe \$25.00





**LCR Meter 814 \$189.95**  
**Best Resolution LCR**  
Inductance: 0.1μH-200H  
Capacitance: 0.1pF-20,000μF  
Resistance: 1mΩ-20MΩ  
1% basic accuracy  
Dissipation factor indicates leakage  
in capacitor and Q factor in inductor  
Zero adjustment to reduce parasitics  
Best for high frequency RF  
SMD and chip component test probe  
\$25.00  
**LIMITED QUANTITY SPECIAL**  
**DIGITAL LCR METER \$74.95**  
0.1pF, 1μH, 10mΩ resolution

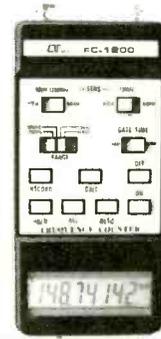


**Frequency Counter FC-1200 \$129.95**  
Frequency: 0.1Hz-1.25GHz  
Display: 8 digit LCD  
Period: 0.1μs-0.1s  
Records Max/Min/Average  
Data hold, relative mode  
Telescoping antenna \$8.00  
Deluxe case \$5.00

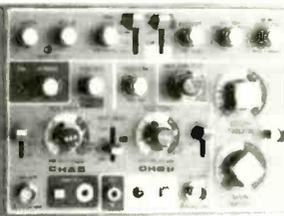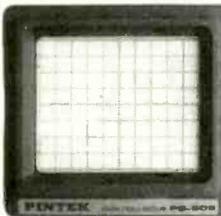Also Available:  
AC/DC clamp meter, Light meter,  
Thermometer, pH meter, High  
voltage probe, Digital caliper,  
Anemometer, Electronic scale,  
Force gauge, Tachometer,  
Stroboscope, Humidity & EMF  
adapter, Sound level meter,  
Frequency counter, SWR/field  
strength/power meter, Dip meter



**20 MHz Oscilloscope with Delay Sweep PS-205 \$429.95**  
Dual Trace, Component test, 6" CRT, X-Y Operation, TV Sync, Z-Modulation, CH2 Output, Graticule Illum, 2 probes each has x1, x10 switch. Best price with delay sweep.  
PS-200 20 MHz DUAL TRACE \$339.95  
PS-400 40 MHz DUAL TRACE \$494.95  
PS-405 40 MHz DELAY SWEEP \$569.95  
PS-605 60 MHz DELAY SWEEP \$769.95  
Scope Probe: 60MHz x1, x10 \$15, 100MHz x1, x10 \$22  
250MHz x1, x10 \$29, 250MHz x100 \$39

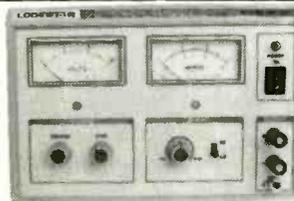**Digital Storage Scope**  
DS-203 20MHz, 10M Sample/sec \$729.95  
DS-303 30MHz, 20M Sample/sec \$849.95  
DS-303P with RS-232 Interface \$1,049.95  
Switchable between digital and analog modes  
2 K word per channel storage  
8 bit vertical resolution (25 Lere/div)  
Expanded Timebase 10ms/div - 0.5 s/div  
Refresh, Roll, Save all, Save CH2, Pre-Trig  
Plotter control



**DC Power Supply PS-303 \$159.00**  
0-30 VDC, 0-3A output  
Constant voltage & constant current mode  
0.02% + 2mV line regulation  
0.02% + 3mV load regulation  
1 mVrms noise and ripple  
Short circuit and overload protected  
PS-8200 with digital voltmeter \$179.00  
Also available: 30V/5A, 60V/3A, 60V/5A  
16V/10A, 30V/10A



**DC Power Supply Triple Output PS-8202 \$499.95**  
Two 0-30 VDC, 0-3A outputs  
One fixed 5VDC, 3A output  
Capable of independent or tracking operation  
Constant voltage and constant current mode  
Four digital meters for volt and current display  
Excellent regulation and low ripple  
Short circuit and overload protected  
Also available: 30V/5A, triple output \$549.95  
Dual tracking 30V/3A, 30V/5A, 60V/3A, 60V/5A



**RF SIGNAL GENERATOR SG-4160B \$119.00**  
100 kHz-150MHz sinewave in 8 ranges  
RF Output 100mVrms to 35 MHz  
Internal 1kHz, External 50Hz-20kHz  
AM modulation  
Audio output 1 kHz, 1 Vrms

**AUDIO GENERATOR AG-2601A \$119.00**  
10Hz - 1MHz in 5 ranges  
Output: 0-8Vrms sinewave  
0-10Vp-p squarewave  
Synchronization: ±3% of oscillation  
frequency per Vrms  
Output distortion:  
0.05% 500Hz - 50kHz  
0.5 % 50Hz - 500kHz  
Output impedance: 600 ohm

**FUNCTION GENERATOR FG-2100A \$169.95**  
0.2 Hz - 2 MHz in 7 ranges  
Sine, square, triangle, pulse and ramp  
Output: 5mV-20Vp-p  
1% distortion, DC offset ± 10V  
VCF: 0-10V control frequency to 1000.1



**RF SIGNAL GEN./COUNTER SG-4162 AD \$229.95**  
Generates RF signal same as SG-4160B  
6 digit frequency counter 1Hz - 150 MHz for internal and external source Sensitivity <50mV

**AUDIO GEN./COUNTER AG-2603AD \$229.95**  
Generates audio signal same as AG-2601A  
6 digit frequency counter 1Hz-150MHz for internal and external sources Sensitivity <50mV

**FUNCTION GEN./COUNTER FG-2102AD \$229.95**  
Generates signal same as FG-2100A  
Frequency counter 4 digits  
Feature TTL and CMOS output

**SWEEP FUNCTION GEN./COUNTER \$329.95**  
0.5Hz to 5 MHz in 7 ranges  
Sweep: Linear 10:1/Log 10:1 20ms to 2s  
AM Modulation  
Gated Burst, Voltage Control Generator  
Generator Control Voltage & 6 digit counter  
1Hz-10MHz for internal & external sources

**ALFA ELECTRONICS**  
741 Alexander Rd., Princeton, NJ 08540

(800) 526-2532/(609) 520-2002 15 DAY MONEY BACK GUARANTEE. 1 YEAR WARRANTY  
FAX:(609) 520-2007 CALL OR WRITE FOR FREE CATALOG AND BEST OFFER.  
Visa, Master Card, American Express, COD, Purchase Order Welcome

CIRCLE 213 ON FREE INFORMATION CARD

### 100 MHz Cursor Readout Scope 4 ch, 8 traces OS-6101 \$1,499.95




- \* 4 independent channels, 8 traces
- \* Time /Voltage cursor measurement
- \* ALT triggering function for 4 ch
- \* Sweeps to 2ns/div, Delayed Sweep
- \* TV Sync, Ch. 1 output, Z-axis input
- \* 2 probes(x1, x10)

### 100 MHz Scope, 4ch. 8 traces Best value all purpose scope OS-6100B \$1,329.95



- \* 4 channels, 8 traces
- \* High sensitivity 500uV/div
- \* Sweeps to 2ns/div, Delayed sweep
- \* 20 kV accelerating voltage
- \* TV sync., Z-axis input
- \* A and B gate output
- \* Best price 100 MHz scope
- \* 2 probes(x1, x10)
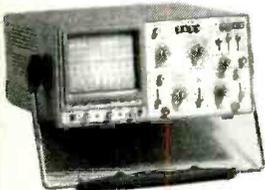
### 50 MHz Triggering Oscilloscope OS-653 \$699.95



- \* Dual Channel
- \* Hold Off Function
- \* Delayed Sweep
- \* Built-in Delay Line
- \* TV Sync
- \* ALT Triggering
- \* High sensitivity 1 mV/div
- \* Trigger level lock function
- \* Z-axis input, CH1 output
- \* 2 probes(x1, x10)

### 20 MHz Oscilloscope OS-622B \$344.95



- \* Dual trace, X-Y operation
  - \* TV Sync, Z-axis input, CH 1 output
  - \* High sensitivity 1 mV/div
  - \* Trigger level lock
  - \* 2 probes (x1, x10)
- |                                       |           |
|---------------------------------------|-----------|
| OS-645B - 40 MHz Cursor readout.....  | \$ 734.95 |
| OS-625B - 20 MHz Cursor readout.....  | \$ 549.95 |
| OS-623B - 20 MHz w/Delayed Sweep..... | \$ 449.95 |
| OS-935 - 5 MHz One channel.....       | \$ 209.95 |

### DC Linear Power Supplies Single Output



- \* Constant voltage and constant current mode
- \* Voltage regulation  $\leq 0.01\%$
- \* Current regulation  $\leq 0.2\%$
- \* Low ripple and noise
- \* Overload and reverse polarity protection
- \* Features 2 analog or 1 digital meter(PS series)  
2 analog or 2 digital meters(PR series)

PS-1830 : (0-18V, 0-3A).....	\$209.95
PS-1830D : Digital Display.....	\$219.95
PS-1850 : (0-18V, 0-5A).....	\$219.95
PS-1850D : Digital Display.....	\$244.95
PS-3030 : (0-30V, 0-3A).....	\$224.95
PS-3030D : Digital display.....	\$254.95
PS-6010 : (0-60V, 0-1A).....	\$209.95
PR-1810H : (0-18V, 0-10A).....	\$349.95
PR-3060 : (0-30V, 0-6A).....	\$314.95
PR-6030 : (0-60V, 0-3A).....	\$299.95
PR-6030D : Digital Display.....	\$399.95

### Triple Output DC Power Supplies



- \* Two variable 0-30VDC, 0-3A outputs
- \* One fixed 5VDC, 3A output
- \* Auto tracking
- \* Auto serial and parallel operation
- \* Constant voltage and constant current mode
- \* Continuous/dynamic load can be selected
- \* Features 4 analog or 2 digital displays

PC-3030 : (0-30V, 0-3Ax2).....	\$499.95
PC-3030D : Digital display.....	\$549.95

### Programmable DC Power Supplies



- \* High stability, low drift, 4 digit display
  - \* Front/rear output-sense switch selectable
  - \* Auto step running w/timer settings
  - \* 100 point programmability (PPS series)
  - \* 50 point programmability (PPT series)
  - \* Auto serial and parallel operation (PPT series)
  - \* Auto tracking (PPT series), IEEE-488.2 and SCPI compatible command set (optional)
- |  |           |
|--|-----------|
| PPS-1860G : (0-18V, 0-6A).....                 | \$1099.95 |
| PPS-3635G : (0-36V, 0-3.5A).....               | \$1099.95 |
| PPS-6020G : (0-60V, 0-2A).....                 | \$1099.95 |
| PPT-1830G : (0-18V, 0-3Ax2, 0-6V, 0-5A).....   | \$1399.95 |
| PPT-3615G : (0-36V, 0-1.5Ax2, 0-6V, 0-3A)..... | \$1399.95 |

### Digital Display Function Generator FG-8016G \$239.95



- \* Frequency Range: 0.02Hz to 2MHz
  - \* Three Instruments in one: Function generator, Pulse generator & Frequency counter.
  - \* Sine, Triangle, Square, TTL Pulse and CMOS output
  - \* Built-in 6 digit counter with INT/EXT function
  - \* 1000:1 tuning range
  - \* Variable DC offset control
- FG-8015 Function Generator
- \* 0.02Hz-2MHz (No Counter).....
  - FC-8131 Intelligent Counter 1.3GHz.....
  - FC-8270 Intelligent Counter 2.7GHz.....
  - UC-2010G Universal Counter.....

### Digital Multimeter & C Meter DM-8034(3½ digits) \$179.95



- \* 8 Function, AC/DC voltage, AC/DC current, resistance
- \* Built-in C meter, diode test and audible continuity check
- \* High voltage 1000V and 20A range
- \* 0.5% basic accuracy
- DM-8040 (3½ Digits, True RMS).....
- \* Measures ACV to 50 kHz.....
- DM-8055 (5½ Digits).....
- \* 0.006% basic accuracy
- \* 1uV, 1m $\Omega$ , 1nA resolution
- \* dBm measurement
- \* Auto range, relative mode, Max/Min
- DM-8055G(5½ Digits, GPIB).....

### Model DM-392 (3½ digits) \$109.95



- \* Auto/Manual ranging (38 ranges)
- \* 42 Segment analog bar graph
- \* Data Hold/Min-Max memory
- \* Relative mode
- \* Auto power off
- \* Overload protection
- \* Audible continuity check /diode test
- \* Capacitance: 1pF-40uF
- \* Frequency: 0.1Hz-1MHz
- \* 20 Amp range
- \* Double high energy fused (1A, 20A)
- \* 0.3% DCV accuracy
- \* AC True RMS (DM-394 only)


DM-351 : 3½ Digits w/Continuity, Auto Off.....	\$54.95
DM-352 : 3½ Digits, Cap. Freq. hFE, 20 Amp.....	\$79.95
DM-353 : 3½ Digits, Cap. Freq. Temp. hFE.....	\$84.95
DM-391 : 3½ Digits, Auto. Cap. Freq. Min/Max.....	\$99.95
DM-392 : 3½ Digits, Hold, Min/Max 20Amp.....	\$109.95
DM-393 : 3½ Digits, Peak, Logic, hFE, Freq.....	\$119.95
DM-394 : 3½ Digits, TRMS, Same as DM 392.....	\$129.95

# Laser Pointer Kit


## \$39<sup>00</sup>
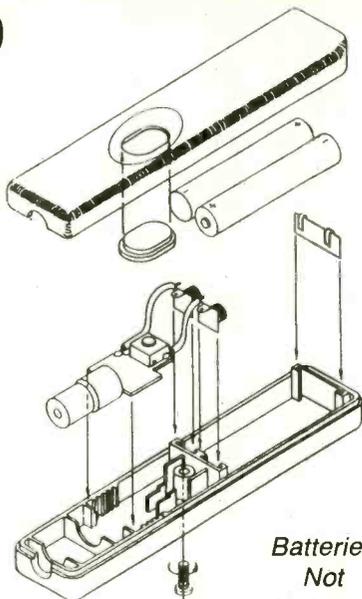
### Features:

- 4 mW, 670 nm Red Output.
- Adjustable Focus Lens.
- Operates for Hours on 2 AAA Batteries.
- Compact Size: 4.5" x .95" x .60"
- Easy to Assemble.



Batteries  
Not  
Included

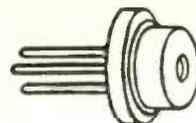

## Laser Diodes


Factory **NEW** Units with  
Specification Sheets.

Toshiba #TOLD-9200  
3 mW, 670 nm **\$20<sup>00</sup>**

Hitachi #HL-6411G  
3 mW, 635 nm **\$99<sup>00</sup>**

Sharp #LTO-15MD  
40 mW, 830 nm **\$75<sup>00</sup>**

## Collimating Lens

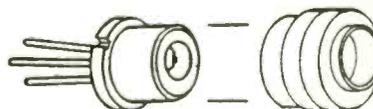

Press Fit  
Over Diode  
**\$15<sup>00</sup>**

**MEREDITH**   
**INSTRUMENTS**

**FREE SHIPPING** on orders over \$100.

Call or write for a **FREE CATALOG** on Lasers & Optics.  
5035 N. 55th AVE., #5 / P.O. BOX 1724 / GLENDALE, AZ 85301  
Phone: **602-934-9387** Fax: **602-934-9482**



CIRCLE 252 ON FREE INFORMATION CARD

# ❖ ATTENTION CABLE VIEWERS ❖

**CABLE VIEWERS. . .get back to your BASIC Cable Needs**

**Call 800-577-8775**

For information regarding all of your **BASIC** cable needs.

**5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT**

- ❖ **PRICE**
- ❖ **EFFICIENT SALES AND SERVICE**
- ❖ **WE SPECIALIZE IN 5, 10 LOT PRICING**
- ❖ **ALL FUNCTIONS (COMPATIBLE WITH ALL MAJOR BRANDS)**
- ❖ **ANY SIZE ORDER FILLED WITH SAME DAY SHIPPING**

We handle **NEW** equipment **ONLY** - Don't trust last year's **OBSOLETE** and **UNSOLD** stock!  
**COMPETITIVE PRICING—DEALERS WELCOME**

**HOURS: Monday-Saturday 9-5 C.S.T.**


It is not the intent of B.E.S.W. to defraud any pay television operator and we will not assist any company or individual in doing the same.  
\*Refer to sales personnel for specifications.

**BASIC**  
**ELECTRICAL**  
**SUPPLY &**  
**WAREHOUSING**  
**CORPORATION**

**P.O. Box 8180 ■ Bartlett, IL 60103 ■ 800-577-8775**

CIRCLE 284 ON FREE INFORMATION CARD

# 500 MHz SPECTRUM ANALYZER \$895

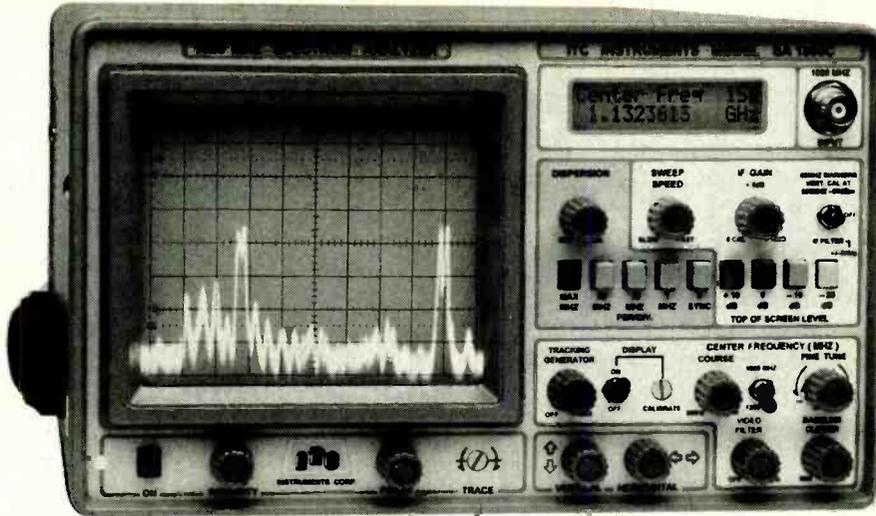

6" x 12" x 16" (H x W x D)  
(only 16 LB)

SA1800C SHOWN  
\$2295.00

## 1-1300 MHz *In One Sweep* \$1895 MADE IN THE USA


**ALL NEW SPECTRUM DISPLAY MONITOR PLUS FULL FUNCTION SPECTRUM ANALYZER**

**LET THE SA500A SPOT THOSE HIDDEN SIGNALS**  
The SA500A easily attaches to any receiver IF output jack. Providing a panoramic signal display of your 1-30 MHz and 30 to 2000 MHz scanner or communication receiver. The SA500A is a Professional Spectrum Surveillance Technology Monitor. A Full Function Spectrum Analyzer with +/- 5KHz Narrow Band Filter, Center Freq. Display, 50 MHz Marker Generator. Capable of Tuning Duplexers, Amps, Filters Receivers, Transmitters & Perform EMI, RFI, FCC, Testing. SA500A First affordable Professional Spectrum Monitor/Analyzer for all serious Ham Radio and Radio Monitoring Operators. just **\$895.00**

**.2-1.3GHz SA1300B THE ULTIMATE LOW COST ANALYZER**  
Quality & Performance that's what ITC Spectrum Analyzers are known for. 80 dB on Screen, -110 dBm Sensitivity, Center Frequency Display, +/- 5KHz Narrow Band Filter (for 5KHz resolution band width) 50 MHz Marker. DISPERSION ZOOM, Baseline Clipper, Sweep Speed, Adjustable Video Filter, 40dB of Input Attenuation. Standard on all **ADVANTAGE** Spectrum Analyzer specials. The SA1300B and SA1800C provide Laboratory Performance at a fraction of the normal cost. The SA1300B **\$1895.00** -SA1800C .2-1.3GHz & .8-1.8GHz **\$2295.00**. Add a 1.3GHz Tracking Generator to any unit

## 1.3GHz FREQUENCY COUNTER .001 ppm

**\$479.00**

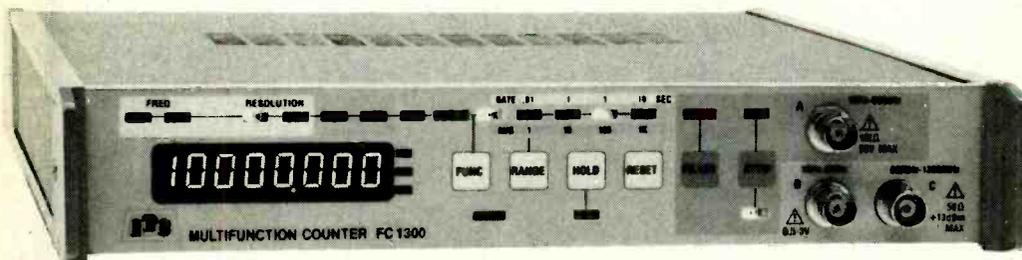

ISO9002 CERTIFIED  
**FIVE YEAR  
WARRANTEE**  
REG. PRICE \$599.00  
SAVE \$120.00

## Laboratory Performance PROCESSOR STABILIZED OVEN OSCILLATOR .001 ppm

**ITC FC1300: the first truly Accurate low cost** Frequency Counter. Accuracy is the #1 Frequency Counter Requirement. The \$200 - \$800 counters being advertised the past few years are but toys when it comes to accuracy. These **guess-so-matic** units are off 5 to 10 PPM over temperature & time (That's +/- 6,000 -13,000 Hz at 1.3 GHz) The **FC1300** is accurate to within **+/-13 Hz at 1.3 GHz 0-40 degrees C**. Sensitivity is < 5mV 1Hz to 13 GHz, 50 Ohm & 1 Meg Ohm inputs, LP filter, 1x -10x input Att. Frequency Measurement, Period Averaging, Time Interval, External Counter, Freq. Ratio, Hold & Reset Functions, 4 Gate times .01 to 10 Sec. Tired of **guess-so-matic** Counters: **Serious About Accuracy**: Ready to step up to **Laboratory Performance Accuracy**: Call Today & **Order**

**ADVANTAGE INSTRUMENTS CORP. MASTER CARD -VISA - DISCOVER - AMX**

3579 Highway 50, East-#301, Carson City, NV 89701

Terms: **COD - Check - Money Order**

702-885-0234 FAX 702-885-7600 Call Toll Free 800-566-1818 - BBS 310-549-0321

PRICES & SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE OR OBLIGATION. F.O.B. CARSON CITY NV. NV. RESIDENTS ADD SALES TAX.


CIRCLE 132 ON FREE INFORMATION CARD

Call 800-566-1818  
To Order or Info.  
Free 1995 Catalog  
**ADVANTAGE**  
Carries a full line of  
Scopes - Analyzers  
Frequency Counters  
Generators  
LCR Bridges & DMM'S

March 1995, Electronics Now

**NOW  
YOU CAN "SEE"  
INVISIBLE FIELDS  
AND AVOID THEM**

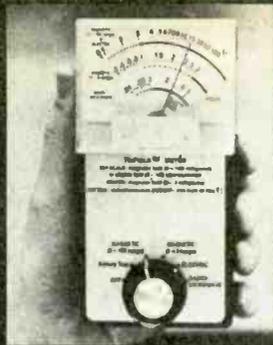Most homes and offices have hot spots with strong artificial electro-magnetic fields, where chronic exposure may cause mental or physical problems. Even the EPA names these fields as suspected carcinogens. You can reduce your risk by avoiding these high-field areas.



The **TriField™** meter detects *far more* of these fields than any other electromagnetic pollution meter. It's the only one that independently reads AC electric fields, AC magnetic fields, and radio/microwaves. It also reads field strengths in *all directions simultaneously*. Every other meter that sells for under \$500 reads only magnetic and only in one direction — they can entirely miss a magnetic field unless pointed correctly and are blind to radio/microwaves and electric fields, both of which cause biological effects.

The **TriField™** meter reads all three types of fields numerically and with a SAFE/BORDERLINE/HIGH SCALE, weighted proportional to effect on the body. Thresholds are based on epidemiological and laboratory studies. (While no *absolute* hazard thresholds have been established, reduction of *relative* exposure is prudent.)

The **TriField™** meter comes ready-to-use with battery, instructions, and one-year limited warranty. The cost is \$144.50 postpaid.

AlphaLab, Inc. / 1280 South Third West / Salt Lake City, UT 84101-3049  
For literature and information, call (503) 543-6545

**NOT WEARING A  
SAFETY BELT CAN COST  
YOU AN ARM & A LEG.**



It's against the law. So if you don't want a ticket, buckle up. Or, you could become broke in more ways than one.

**YOU COULD LEARN A LOT FROM A DUMMY.®  
BUCKLE YOUR SAFETY BELT.**



**Plant Trees for America™**

**T**rees provide food, shelter, and nesting sites for songbirds.

Trees increase property values, and make our homes and neighborhoods more livable.

Trees help conserve energy. They cool our homes and entire cities in the summer, and slow cold winter winds. Shade trees and windbreaks can cut home utility bills 15-35%.

Trees clear the air we breathe. They provide life-giving oxygen while they remove particulates from the air and reduce atmospheric carbon dioxide.

**America needs more trees**

The United States has lost a third of its forest cover in the last 200 years.

Our towns should have twice as many street trees as they have today.

We need more trees around our homes and throughout our communities. We



need more trees to protect our farm fields and our rivers and streams. To provide wood for our homes and a thousand products we use every day.

**10 Free Trees**

Ten Colorado blue spruces, or other conifers selected to grow in your area, will be given to each person who joins the Arbor Day Foundation.

Your trees will be shipped postpaid at the right time for planting in your area, February through May in the spring or October through mid December in the fall. The six to twelve inch trees are guaranteed to grow, or they will be replaced free.


To become a member and to receive your free trees, send a \$10 membership contribution to Ter Blue Spruces, National Arbor Day Foundation, 100 Arbor Avenue, Nebraska City, NE 68410.

Join today, and plant your Trees for America!


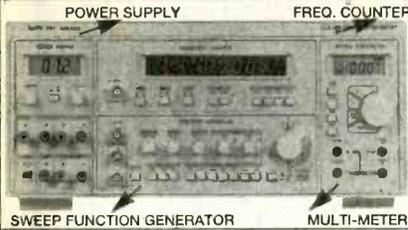
# Solutions for the Test Instrument

1 YEAR WARRANTY  
15 DAY MONEY BACK GUARANTEE



## MT-100

Reg. \$599.

**\$399.00**

### Four Instruments in One Instrument

#### 1 Function Generator

- Sine, Square, Triangle, Pulse, Skewed Sine, Ramp, TTL
- 0.2 Hz ~ 2MHz

#### 2 Frequency Counter

- 8 Digit LED
- 1 Hz ~ 100MHz
- $\pm (1 \text{ Hz} + 1 \text{ dgt.} + \text{Time Base Error})$

#### 3 Power Supply

- 3-1/2 Digit LCD
- Triple output: #1 0-50V, 0.5A MAX #2, 15V, 1A #3, 5V, 2A

#### 4 Digital Multimeter

- 3-1/2 Digit LCD
- DCV, ACV,  $\Omega$ , DCA, ACA
- $\pm (0.5\% + 2 \text{ dgt})$

### FG-140 2MHz Function Generator

Reg. \$249. **\$149.00**



- 0.2 Hz ~ 2.0 MHz, 7 Decades
- Sine, Square, Triangle, Pulse, Ramp, Skewed Sine
- VCF, Symmetry
- Variable DC Offset Control

### 2MHz Sweep Function Gen. w/Freq. Counter

Reg. \$399. **\$229.00**



- 4 Digit LED Display
- Sine, Square, Triangle, TTL, Pulse, Ramp, Skewed Sine
- Linear/Logarithmic Sweep
- 10 MHz Freq. Counter

### 1.0GHz Frequency Counter, High Resolution

Reg. \$399. **\$209.00**



- 1.0 Hz ~ 1.0 GHz
- 8 Digit LED Display
- Auto & Manual Range
- 4 Selectable Gate Times
- 1M $\Omega$  & 50 $\Omega$  Input Impedance

### AG-350 Audio Generator

Reg. \$199. **\$119.00**



- 10 Hz ~ 1 MHz, 5 Ranges
- Sine Output: 10Hz - 1MHz
- Square Output: 10Hz - 100KHz

### PS-500 DC Power Supply

Reg. \$249. **\$159.00**



- 0-30 VDC
- 0.1 - 3A
- Short & Overload Protection

### PS-540 DC Power Supply

Reg. \$399. **\$289.00**



- 0-16 VDC
- 0.1 - 10A
- Short & Overload Protection

## Deluxe Oscilloscopes w/Phillips CRT. 2 yr. Parts/Labor Warranty

OS-3304 Reg. \$499. **\$339.00**



### OS-3304 25MHz, Dual Trace

- DC to 25 MHz. Dual Channel
- 6" Rectangular CRT with Internal Graticule 10x8cm (Phillips P31)
- Uncalibration LED.
- High Sensitivity 1 mV/div to 20V/div X-Y modes, Z Axis (intensity modulation)
- Rise time 14n Sec. or less.
- Full TV Trigger for TV-V & TV-H
- Acceleration Potential 2kV
- 60MHz (X1.X10) Probe Kit: 2 sets
- Power: 115/230V AC

OS-3324 Reg. \$599. **\$399.00**



### OS-3324, 3 Function

- OS-3304
- Dual Component Tester/Comparator

OS-3344 Reg. \$899. **\$649.00**



### OS-3344, 5 Function

- + 2 + 3 • OS-3324
- Frequency Counter 100MHz, 7 Digit LED Display
- Function Generator 0.02 Hz to 2.0 MHz

OS-3315 40MHz, Dual Trace Sweep Delayed Reg. \$799. **\$549.00**



- DC to 40 MHz. Dual Channel
- Delayed Sweep 100nS to I.O.S. 7 decade
- 6" Rectangular CRT with Internal Graticule 10x8cm (Phillips P31)
- Uncalibration LED.
- High Sensitivity 1 mV/div to 20V/div X-Y modes, Z Axis (intensity modulation)
- Rise time 8.5nS or less.
- Full TV Trigger for TV-V & TV-H
- Acceleration Potential 12kV
- Variable Hold Off
- 16ns ~ 1.0s Time Base
- 60MHz (X1.X10) Probe Kit: 2 sets
- Power: 115/230V AC

### Capacitance Meter

Reg. \$79. **\$49.00**



### Digital Clamp-On

Reg. \$89. **\$54.00**



### Multimeter+ Extended Range Capacitance

Reg. \$149. **\$89.00**



- 9 Function / 42 Range
- Basic DCV Accu.:  $\pm 0.25\%$
- Multimeter
- Volt: AC/DC
- Amp: AC/DC 2A
- Ohm: Up to 2000M $\Omega$  Diode, Continuity Beeper
- Capacitance (9 Range) 0.1pF - 20,000 pF Zero Adj. Knob
- Trig Lamp
- Double Insulated Jack
- Alligator Clip Test Leads
- Deluxe Holster w/Strap

### Wide Range Multimeter w/Logic

Reg. \$149. **\$89.00**



- 11 Function / 45 Range
- Basic DCV Accu.:  $\pm 0.25\%$
- 3 1/2 Digit Manual
- Auto Power Off
- Data Hold & Peak Hold
- Amp: Up to 20A AC/DC
- Ohm: Up to 200 M $\Omega$
- Freq: Up to 20MHz
- Capacitance: 1p - 200 $\mu$ F
- Logic: TTL
- TR hFE, Diode
- Continuity Beeper
- Double Insulated Jack
- Alligator Clip Test Leads
- Deluxe Holster w/Strap

### Oscilloscope Probe Kit

Switch Selectable X1/X10



- HP-9060, 60MHz Reg. \$29. **\$17.00**
- HP-9150, 150MHz Reg. \$49. **\$24.00**
- HP-9250, 250MHz Reg. \$59. **\$32.00**

### Pen-Type DMM w/Logic

Reg. \$79. **\$59.00**



- 3 1/2 Digit
- Dual Display
- Auto & Manual
- DCV, ACV, ACA, DCA,  $\Omega$
- Logic CMOS/TTL
- Data Hold
- Diode
- Continuity

### DMM w/Holster

Reg. \$59. **\$39.00**



- 3 1/2 Digit
- 1.5" Big LCD
- 10A AC/DC AC/DC V,  $\Omega$
- Signal Injector
- Diode
- Continuity
- Holster

### Multifunction DMM

Reg. \$89. **\$59.00**



- 3 1/2 Digit
- 1.5" Big LCD
- Heavy Duty, 20A AC/DC
- Capacitance
- Frequency
- TR hFE
- Diode
- Continuity
- Holster

**BMC** Your Best Source for High Standard Electronics

20 Highpoint, Dove Canyon, CA 92679

Order & Free Catalog

**800-532-3221**

(714) 586-2310 Fax (714) 586-3399



March 1995, Electronics Now


\$449<sup>95</sup>

# Device Programmers

\$139<sup>95</sup>

48 PIN ZIF

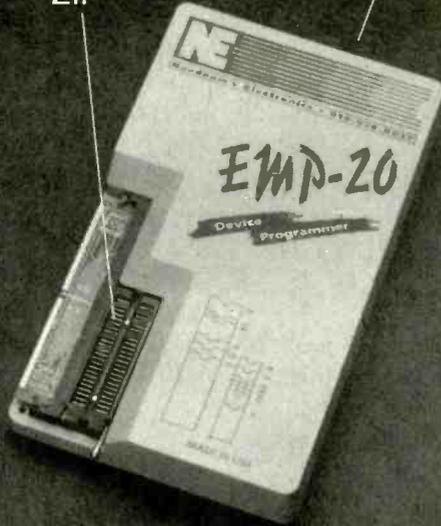Connects to standard PC parallel printer port




9 1/2 x 5 3/4 x 1 1/4

EMP-20

- Easy to use software, on-line help, full screen editor
- **Fast Programming (EMP-20)**  
27C010A, 23 seconds  
28C020, 34 seconds  
27C040, 95 seconds
- **Made in USA**
- 1 Year Warranty
- Technical Support by phone
- 30 day Money Back Guarantee
- FREE software upgrades available via BBS
- Demo SW via BBS (EM20DEMO.EXE) (PB10DEMO.EXE)
- E(e)proms 2716 - 8 megabit, 16 bit 27210-27240, 27C400 & 27C800,
- Flash 28F256-28F020, (29C256-29C010 (EMP-20 only))
- Micros 8741A, 42A, 42AH, 48, 49, 48H, 49H, 55, 87C51, 87C51FX, 87C751,752
- GAL, PLD from NS, Lattice, AMD-16V8, 20V8, 22V10 (EMP-20 only)

## PB-10 Internal Card for PC

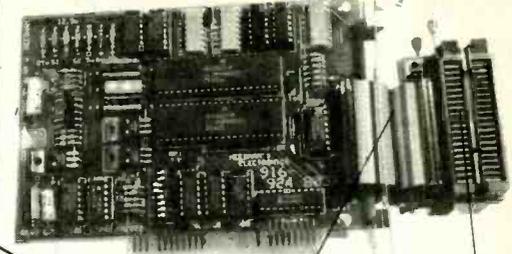

2 ft. Cable

40 PIN ZIF

### FOR MORE INFORMATION CALL

4630 Beloit Drive, Suite 20  
Sacramento, CA 95838  
(Monday-Friday, 8 am-5 pm PST)

**NEEDHAM'S ELECTRONICS, INC.**



C.O.D.



**(916) 924-8037**

**BBS (916) 972-8042**

**FAX (916) 972-9960**


CIRCLE 257 ON FREE INFORMATION CARD

# PIC

Interactive Development Environments for the Microchip Technology, Inc. PIC family of microcontrollers. Microsoft Windows 3.1 MDI Applications

## MicroView™ Simulation Environment

## Assemble!™ Universal PIC Assembler

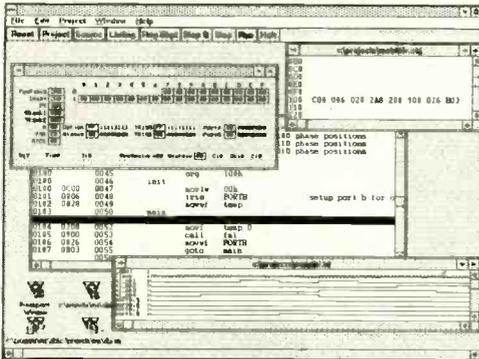

MICROVIEW™ is a full-featured simulation environment for the Microchip Technology, Inc. PIC 16C5X microcontrollers. Other simulation engines available.

### Features:

- Integrated Programming Editor, Macro-Assembler
- Simultaneous Multiple Device Simulations
- Graphical Timing Diagrams, Input Stimulus Generation
- Step. Register, Full Break Point Capability
- Direct Download to PICSTART. Compatible with PICMASTER. and the Parallax Downloader

ASSEMBLE! is a universal macro assembler for the Microchip Technology, Inc. microcontrollers. Assemble! supports all of the Microchip device families.

### Features:

- Integrated Programming Editor, Macro-Assembler
- Bookmarks, Macro Key Recording, Search and Replace
- Error Report. Listings, Context Sensitive On-Line Help
- COD File Format. INHX8S, INHX8M, INHX16
- Direct Download to PICSTART. Compatible with PICMASTER. and the Parallax Downloader

MicroView™ \$149.95USD

VISA/MC

Assemble!™ \$99.95USD

VISA/MC

TRISYS

Send check or Money Order. VISA/MC Accepted, Company Purchased Orders Accepted, Shipping and Handling Included.

TRISYS, Inc. P.O. Box 11087 • Glendale, AZ 85318-1087 • USA • PH: (602) 581-1760 • FAX: (602) 516-0582

[PIC, PICMASTER, and PICSTART are trademarks and tradenames of Microchip Technology, Inc., Parallax is the tradename of Parallax, Inc.]

CIRCLE 322 ON FREE INFORMATION CARD

www.americanradiohistory.com



# TRIDENT

# Beacont

# GRUNDIG

TR2400 \$449  
100KHz to 2.06 GHz



TR980 \$259  
5000KHz to 1 GHz



BC220 \$219  
Turbo Scan  
with 800MHz



BC2500 \$319  
25MHz to 1.36 GHz



YB400 \$179  
Top Rated Compact  
Shortwave Receiver

# SANGEAN



ATS818 \$145  
Best Buy Portable  
Shortwave Receiver

MVT7100 \$529  
530KHz to 1.6GHz  
Not for sale in USA




TR1200 \$349  
500KHz to 1.3GHz



BC120 \$149  
LoHi/UHF Turbo



SC150 \$179  
Turbo Scan w/800

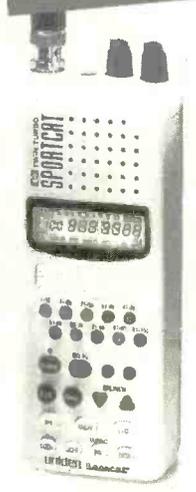

ATS808 \$99.95  
Digital Tuning  
Shortwave Receiver



TR4500 \$469  
1MHz to 1.3GHz  
Computer Control



BC890 \$249  
29MHz to 956MHz  
Continuous w/ turbo



GW2 Signal  
Amplifier,  
100KHz to  
2.GHz  
\$79.00  
Call for other  
accessory  
products

**What's the easiest way to get Radio Active?  
Dial 1 800 445 7717**

Toll Free, 24 Hours! For orders, tech support, Inbound fax and Fax Facts Instant catalog sheet service. Computer BBS Modem & Fax/Modem, 317-579-2045. International Fax: en Espanol, en Francals, und auf Deutsch, or just fax in plain English to:317-849-8794



**AMERICAN RADIO HISTORY COMMUNICATIONS**  
10707 East 106th St. Fishers, IN 46038  
CIRCLE 212 ON FREE INFORMATION CARD

Service & Support hours: Mon.-Fri. 9AM to 6PM, Sat. 10-4 EST. Mastercard, Visa, Checks, Approved P.O.'s & COD (add \$5.50) & AMEX, Discover. Prices, specifications and availability subject to change. Flat rate ground shipping and handling charge only \$6.95 per unit. Express Air only \$9.95, for most units, to most locations.



# CELLULAR PROGRAMMING SOFTWARE



**PROGRAM EXTENSION PHONES, ESN'S & NAMS !**  
**ENJOY THE SAME ADVANTAGES AS SOME CUSTOMERS THAT SUBSCRIBE TO GTE MOBILNET OR BELL SOUTH MOBILTY FOR CELLULAR SERVICE !**  
**CELLULAR PROGRAMMING SERVICE IS ALSO AVAILABLE !**



**FOR FREE INFO CALL !!**  
**MOTOROLA ABOVE 9122**

**OUR SOFTWARE PROGRAMS MANY NEW CELLULAR PHONES DIRECTLY FROM THE DATA PORT WITHOUT OPENING THE PHONE , NO SOLDERING !**

**DON'T BE FOOLED BY CHEAP IMITATIONS. GUARANTEED & TESTED.**  
**SOFTWARE AVAILABLE FOR MOTOROLA, GE, ERICSSON, SONY, MITSUBISHI, NOKIA, PANASONIC, DIAMONDTTEL, TECHNPHONE, OTHER PRODUCTS COMING SOON.**  
**SOLD FOR EDUCATIONAL PURPOSES ONLY**

**CELLSOFT**

**609-751-2242 EXT # 2 FAX 609-751-5549**

**JEM MARKETING, LLC 100 SPRINGDALE ROAD A3 SUITE 113 CHERRY HILL NJ 08003**

CIRCLE 317 ON FREE INFORMATION CARD

*Serving the public since 1981*

## **XANDI ELECTRONICS**

1270 E Broadway Rd. # 113, Tempe AZ 85282

**SATISFACTION GUARANTEED!**

**BUY WITH CONFIDENCE FROM XANDI**

- 30-DAY REFUND POLICY
- TECH SUPPORT NUMBER (602-894-0992)


<ul style="list-style-type: none"> <li>• Tunes 88-108 MHz.</li> <li>• Powerful 2 stage audio amplifier.</li> <li>• Sensitive, picks up sounds at the level of a whisper.</li> <li>• Up to 1 mile range.</li> <li>• Requires 9V battery. (Not incl.)</li> </ul> <p><b>SUPER-MINIATURE FM TRANSMITTER</b>                  Super small FM transmitter. Use with any FM broadcast receiver. Easy to assemble, all chip (SMT) parts are pre-assembled to the circuit board.</p> <p><b>XST500 (E-Z) Kit ..... \$44.95</b></p>	<ul style="list-style-type: none"> <li>• Miniature photo battery mounts right on circuit board. (Included)</li> <li>• Tunes 88-108 MHz.</li> <li>• Up to 1/2 mile range.</li> <li>• Sensitive 2 stage audio amplifier, picks up sounds at the level of a whisper.</li> </ul> <p><b>MICRO-MINIATURE FM TRANSMITTER</b>                  Including the battery, this is the Worlds smallest FM transmitter. Use with any FM broadcast receiver. Easy to assemble, uses pre-assembled circuit board.</p> <p><b>XWB1000 E-Z KIT ..... \$49.95</b></p>	<ul style="list-style-type: none"> <li>• Transmits at 143 MHz.</li> <li>• Up to 1 mile range.</li> <li>• Miniature photo battery mounts right on circuit board. (Included)</li> <li>• Amazing audio sensitivity, picks up sounds at the level of a whisper.</li> </ul> <p><b>CRYSTAL CONTROLLED FM TRANSMITTER</b>                  Including the battery, this is the Worlds smallest crystal controlled FM transmitter. Transmits to any scanner type receiver. Easy to assemble, uses pre-assembled circuit board.</p> <p><b>XTL1000 E-Z KIT ..... \$69.95</b></p>	<ul style="list-style-type: none"> <li>• Smallest Phone transmitter anywhere!</li> <li>• Tunes 88-108 MHz.</li> <li>• No batteries required, powered by phone line.</li> <li>• Up to 1/4 mile range.</li> <li>• Attach to phone line anywhere in house, even inside phone.</li> </ul> <p><b>SUPER-MINIATURE PHONE TRANSMITTER</b>                  Worlds smallest FM phone transmitter. Use with any FM broadcast receiver. Easy to assemble, all chip components are pre-assembled to the circuit board.</p> <p><b>XSP250 (E-Z) Kit ..... \$34.95</b></p>
<ul style="list-style-type: none"> <li>• Dial your phone from anywhere and listen to the sounds inside your home.</li> <li>• Two digit Touch Tone code for secure operation.</li> </ul> <p><b>TELEPHONE SNOOP</b>                  The latest in home or office security. Call home from anywhere, enter a two digit security code, and hear the sounds in your home. Automatically turns on without ringing the phone, verifies code, then activates for one and a half minutes.</p> <p><b>XPS-CASEKIT ..... \$13.95</b>  <b>XPS1000 (C) KIT ..... \$49.95</b></p>	<ul style="list-style-type: none"> <li>• Transmits a continuous beeping tone.</li> <li>• Adjustable from 88 to 108 MHz.</li> <li>• Up to 1 mile range.</li> <li>• Works with any FM broadcast receiver.</li> </ul> <p><b>TRACKING TRANSMITTER</b>                  Only 0.7 by 2.4 inches, the XTR100 operates at voltages of 3 to 18 Volts and is ideal for use in locating lost model rockets, bicycles, automobiles, games of hide and seek, and contests.</p> <p><b>XTR100 (C) Kit ..... \$33.95</b></p>	<ul style="list-style-type: none"> <li>• Uses sensitive microwave transistor amplifier.</li> <li>• Covers 1 to 2,000 MHz.</li> <li>• Compact hand held unit.</li> <li>• Includes miniature loud speaker for audio indication of detected signals.</li> </ul> <p><b>SUPER SENSITIVE BUG DETECTOR</b>                  When the XBD200 intercepts a signal in the 1 to 2,000 MHz range, it emits a growl that increases to a high pitched squeal as the signal strength increases.</p> <p><b>XBD200 (C) Kit ..... \$49.95</b></p>	<ul style="list-style-type: none"> <li>• Use with any FM broadcast receiver.</li> <li>• Hear every sound in an entire house!</li> <li>• Up to 1 mile range</li> <li>• Powerful 2 stage audio amplifier.</li> </ul> <p><b>MINIATURE FM TRANSMITTER</b>                  The XFM100 has a super sensitive microphone and is capable of picking up sounds at the level of a whisper and transmitting them to any FM broadcast receiver.</p> <p><b>XFM100 (C) Kit ..... \$32.95</b></p>
<ul style="list-style-type: none"> <li>• Digital voice changing: male to female, female to male, adult to child, child to adult.</li> <li>• Anonymity on any call.</li> <li>• Button for normal operation.</li> <li>• 16 levels of voice masking.</li> </ul> <p><b>VOICE CHANGING TELEPHONE</b>                  STOP THOSE ANNOYING TELEPHONE CALLS! Sound older and tougher when you want to. Not a kit. Fully assembled. Single phone operation only.</p> <p><b>TRANSITION 2000 ..... \$89.95</b></p>	<ul style="list-style-type: none"> <li>• Digital voice changing: male to female, female to male, adult to child, child to adult.</li> <li>• Use with any modulator phone.</li> <li>• 16 levels of voice masking.</li> <li>• Connects between handset and phone.</li> </ul> <p><b>VOICE CHANGING ACCESSORY</b>                  STOP THOSE ANNOYING TELEPHONE CALLS! Sound older and tougher when you want to. Not a kit. Fully assembled. Use with single or multi-line phones.</p> <p><b>TRANSITION 2001 ..... \$59.95</b></p>	<ul style="list-style-type: none"> <li>• Uninterrupted coverage of 800 to 950 MHz.</li> <li>• Works with any scanner that can receive 400 to 550 MHz.</li> </ul> <p><b>800-950 MHz SCANNER CONVERTER KIT</b>                  If your scanner can receive 400-550 MHz, just add the XLC900 for uninterrupted 800-950 MHz coverage. It converts all 800-950 MHz signals down to 400-550 MHz so your scanner can receive them! Add our custom case kit for that "Professional" look.</p> <p><b>XLC-CASE KIT ..... \$13.95</b>  <b>XLC900 (C) KIT ..... \$49.95</b></p>	<ul style="list-style-type: none"> <li>• Transmit high quality stereo to any FM stereo receiver.</li> <li>• Built-in output level monitor for quick and easy tuning.</li> <li>• Ideal for use with personal CD player.</li> </ul> <p><b>FM STEREO TRANSMITTER</b>                  Transmit full-bodied Hi Fi stereo to any FM stereo receiver. Separate left and right inputs and gain controls. Includes an output booster stage for greater range.</p> <p><b>XFS-CASE KIT ..... \$13.95</b>  <b>XFS108 (C) KIT ..... \$41.95</b></p>

**WE ACCEPT VISA, MC, MO, COD**  
**SHIPPING & HANDLING EXTRA**

**TOLL FREE ORDER LINE**  
**1-800-336-7389**  
**ASK FOR FREE CATALOG OF OUR PRODUCTS**

**SEND MAIL XANDI ELECTRONICS**  
**ORDERS TO: BOX 25647**  
**TEMPE, AZ 85285-5647**

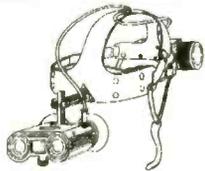**THE TOTAL COST FOR SHIPPING MOST MIXED ORDERS FROM THIS ADVERTISEMENT BY FEDERAL EXPRESS IS \$15 - \$25 ALL PRICES ARE IN US DOLLARS.**



**HEAD MOUNTED IR BINOCULARS**


These lightweight USSR made binoculars will produce good vision with 1/4 moonlight illumination, but can also be IR assisted at lower light levels: Work well with our \$11 IR filter. Powered by 4 AAA batteries (6V), 1 X magnification, angle of vision 28 deg., focuses from 2' to infinity.

**\$380**

**VISIBLE LASER DIODE KIT**

Just the basics: A 5mW / 670nm visible laser diode plus a collimating lens, plus an APC driver kit UNBELIEVABLE PRICE:

**\$26**

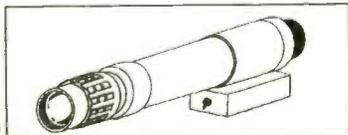


**INTENSIFIED NIGHT VIEWER KIT**

See in the dark! Make your own night scope that will produce good vision in sub-starlight illumination! We supply a three stage fibre optically coupled Image Intensifier tube, EHT power supply kit, and sufficient plastics to make a monocular scope. The three tubes are supplied already wired and bonded together.

**\$200 for the 25mm version  
\$280 for the 40mm version**

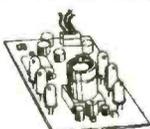
We can also supply the lens (100mm f2: \$50) and the eyepiece (\$12) which would be everything that is necessary to make an incredible viewer!



**CCD CAMERA**

Monochrome CCD Camera which is totally assembled on a small PCB and includes an Auto Iris lens. 9-12V DC operation. It can work with illumination of as little as 0.1Lux, and is IR responsive: Can be used in total darkness with Infra Red illumination. A suitable illuminator is our HIGH POWER LED IR ILLUMINATOR kit. Overall dimensions of camera are 24 X 46 X 70mm and it weighs less than 40 grams! Can be connected to any standard monitor or the video input on a Video cassette recorder: EIA ( US - NTSC) compatible.

**\$145**

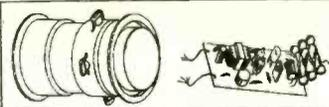


**FIBRE OPTIC TUBES**

These US made tubes are "pulls" from equipment, in excellent condition. Have 25 / 40 mm diameter, fibre - optically coupled input and output windows. The 25mm tube has an overall diameter of 57mm and is 60 mm long, the 40mm tube has an overall diameter of 80mm and is 92mm long. The gain of these is such that they would produce a good image in approximately 1/2 moon illumination, when used with suitable "fast" lens, but they can also be IR assisted to see in total darkness. Our \$11 IR filter is suitable for use with these tubes. Suitable for low light video preamplifiers, wild life observation, etc. Each of the tubes is supplied with an 9V - EHT power supply kit. REDUCED PRICES:

**\$75** .....For the 25mm intensifier tube and supply kit.

**\$110** .....For the 40mm intensifier tube and supply kit.

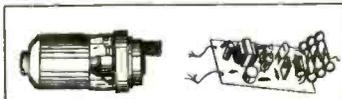
*We also have a good supply of the same tubes that may have a blemish which is not in the central viewing area! Satisfaction guaranteed! IION SPECIALII \$40* .....For a blemished 25 or 40mm (Specify preference) image intensifier tube and supply kit. Matching good quality eyepiece lens only, \$6 *Extra! That's almost a complete night viewer kit for \$46.*



**IR TUBE AND SUPPLY**

A tube and supply combination that can be used as the basis of making a very sensitive IR responsive viewer. The tube employed is probably the most sensitive IR responsive tube we ever supplied, and the EHT supply kit enables the tube to be operated from a small 9V battery. Basic Instructions provided.

**\$80**

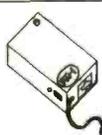

**MINIATURE FM TRANSMITTER**

Not a kit, but a very small ready made self contained FM transmitter enclosed in a small black metal case. It is powered by a single small 1.5V silver oxide battery, and has an inbuilt electret microphone. SPECIFICATIONS: Tuning range: 88 - 108MHz, Antenna: Wire antenna - attached, Microphone: Electret condenser, Battery: One 1.5V silver oxide LR44 / G13, Battery life: 60 hours, Weight: 15g, Dimensions: 1.3" X 0.9" X 0.4".

**\$25**

**SECOND GENERATION TUBES**

WE SHOULD HAVE A REGULAR SUPPLY OF SOME NEW USSR MADE 18mm 2"ND. GEN. FIBRE OPTICALLY COUPLED IMAGE INTENSIFIER TUBES @ APPROX. \$500.



**INFRA RED FILTER**

Very high quality IR filter and a RUBBER lens cover that would fit over most torches including MAGLITE's, and convert them to a good source of IR. Suitable for use with passive and active viewers.

**\$11**

For the filter and the rubber lens cover.

**GLASS PRISMS**

Precision 90 deg. glass prisms with a mirrored backing. We have a limited quantity of these prisms

**\$10**

For the smaller prism: Approximately 18 X 18 X 24 X 64mm.

**\$20**

For the larger prism: Approximately 18 X 18 X 24 X 127mm.



**PASSIVE NIGHT VIEWER KIT**

See Electronics Now Oct. 94. This kit is based on a BRAND NEW passive night vision scope, which is completely assembled and has an EHT coaxial cable connected. This assembly employs a high gain passive tube which is made in Russia. It has a very high luminous gain, and the resultant viewer will produce useful pictures with starlight illumination. It needs an EHT power supply to make it functional, and we supply a suitable supply and it's casing in kit form.

**\$220**

**MISCELLANEOUS ITEMS COMPONENTS AND KITS**

- FM TRANSMITTER KIT - MKII: .....\$8
- SINGLE CHANNEL UHF REMOTE CONTROL KIT: One transmitter and one receiver: \$32 additional transmitter \$11
- 4 CHANNEL UHF REMOTE CONTROL KIT: Two transmitters and one receiver: \$68
- ELECTRIC FENCE KIT: PCB and components .....\$28
- GARAGE - DOOR - GATE REMOTE CONTROL KIT: ..Tx \$13 ..Rx \$56
- LASER BEAM COMMUNICATOR KIT: Tx, Rx, plus IR Laser .....\$39
- PLASMA BALL KIT: PCB and components kit, needs any bulb .....\$18
- HIGH POWER IR LED's - 880nm / 30mW / 12deg. @ 100mA .10 for \$6

**OATLEY ELECTRONICS  
5 LANSDOWNE PDE. OATLEY,  
SYDNEY. NSW. AUSTRALIA 2223**

**PHONE ORDERS**

East Coast between 7pm and 2am  
West Coast between 4pm and 11pm  
**011 61 2 579 4985**

**FAX ORDERS**

**011 61 2 570 7910**

**MASTERCARD - VISACARD -  
AMERICAN EXPRESS CARD WITH  
TELEPHONE OR FAX ORDERS,  
INTERNATIONAL BANK DRAFTS WITH  
MAIL ORDERS**



# CABLE TV Universal Product-New Technology



Lower Your Monthly Fees

## MODEL 5000 Fully Assembled \$199.95

Our fully assembled product is tested and *Guaranteed* to work on your system. We will also include an AC adaptor and complete hookup instructions. This unique product will be available for a limited time only!

### 4000 And 5000 Features

- The latest in Video Amplification Technology.
- New clocking circuits to stabilize color and picture performance.
- The most advanced picture locking circuitry.
- Inverted Video Option is available.
- Connects easily to your VCR.
- NO converter box is necessary.

*The Halcyon Group*  
**1-800-664-6999**

Anyone implying theft of cable service will be denied assistance.

## MODEL 4000 KIT \$79.95

The 4000 KIT comes with electronic components and Cad designed PC board. We provide schematic, parts list, wiring diagram, tutorial guide, and FREE in-house support.

## Model 4000A Enc Pak \$44.95

The 4000A Enclosure Pak provides the hobbyist, a custom enclosure, AC adaptor and finish accessories to give your kit the professional look.

*From Canada Call*  
**1-813-751-3262**

# CABLE TV DESCRAMBLER KITS

## "New & Improved Version"

### **Universal Descrambler**

*Includes all the parts and an etched & Drilled PC Board. Not included is AC adaptor or enclosure.....***\$69.00**

### **Tri-Mode Descrambler**

*Includes all the parts and an etched & drilled PC board & AC adaptor. Not included is the enclosure.....***\$49.00**

### **SB-3 Descrambler**

*Includes all the parts & an etched & drilled PC board & AC adaptor. Not included is the enclosure.....***\$39.00**

# Call Toll Free 1-800-886-8699

## Visa, MasterCard & COD.

**M & G Electronics, Inc. 2 Aborn Street, Providence, RI. 02903**

*It is not the intent of M & G Electronics, Inc. to assist any individual to defraud any pay TV operator or to violate any state or federal laws regarding the use of the descrambler kits. You must understand the kits being purchased for educational and or experimental use only.*

American Heart Association 

TRAVEL LIGHT.



EXERCISE.

# B&S SALES

**CALL (810) 566-7248 • FAX (810) 566-7258 24 hrs.**

**Hours: Monday through Friday 8am to 7:30pm EST - Saturday 10am to 3pm.**

**51756 Van Dyke St. #330, Shelby Township, MI 48316**

*Free Calculator with order!*

## CONVERTER

	5	10		5	10
PANASONIC TZ-PC 145362 ..	\$68	\$64	DRX-3 PJ.....	\$37	\$33
WAVEMASTER .....	\$65	\$60	DRZ-3 PJ.....	\$38	\$34
DRZ-3 A & B DUAL INPUT.....	\$39	\$35	8528 PJ .....	\$45	\$42

## CONVERTER/DESCRAMBLERS

	5	10		5	10
8600 .....	\$275	\$265	DPV-5 .....	\$145	\$130
8590 .....	\$260	\$250	DP-5 .....	\$125	\$110
8580 .....	\$195	\$185	DRZ-3-DIC .....	\$95	\$85
DPV-7 .....	\$225	\$215	DRX-3-DIC .....	\$89	\$79

## ADD-ON DESCRAMBLERS

### 10 LOT SPECIAL

PIONEER GREEN .....	\$65	J-TVT-GOLD.....	\$42
SA-M80 .....	\$65	J-MINI TVT.....	\$42
J-TNT .....	\$65	H-MLD 1200-3 .....	\$35
J-PURPLE .....	\$49		

**NOTE: MENTION AD FOR THESE PRICES!**

**NO MICHIGAN SALES**

We are now offering a 6 month warranty. In order for warranty to be in effect, this form must be signed and returned. FOR VCR, SECOND, THIRD, ETC. HOOK-UPS.

**YES**, I agree all units are to be used or resold in compliance with Federal and State laws.

Signature \_\_\_\_\_ Date \_\_\_\_\_

NAME \_\_\_\_\_ ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_ PHONE \_\_\_\_\_

*It is not the intent of B&S Sales to defraud any pay television operator and we will not assist any company or individual in doing the same.*

CIRCLE 217 ON FREE INFORMATION CARD

# What Do These Prestigious Companies Have In Common?

**Aerovox®**

DC Film and RFI Suppression Capacitors, Aluminum Electrolytic and AC Oil Capacitors, EMI Filters

**AMP**

Electrical/Electronic Connectors, IC Sockets, PCB Switches

**AMRAD Engineering, Inc.**

Motor Run Capacitors, HID Lighting Capacitors, Power Factor Correction Capacitors

**AEP**

Miniature and Subminiature Coaxial Connectors and Cable Assemblies.

**AVX CORPORATION**  
A VICTOR GROUP COMPANY

MLC, Tantalum and Thin Film Capacitors, Resistors, Networks, Integrated Passive Components, Trimmers, Oscillators, Resonators, Filters, Piezo Devices, and Connectors

**BERG ELECTRONICS**

High Density and Industry Standard Connectors/Subsystems

**CAROL**  
CAROL CABLE COMPANY INC.

Electronic and Electrical Wire and Cable and Power Supply Cords

**COLE FLEX**

Tubing, Conduits, Hose, Sleeveings, Splices, Insulation and Cable Harness Products, Power Cords and Cordsets

**Communications Instruments, Inc.**

CI Midtex  
Relays and Solenoids

**COOPER**

**Bussmann**  
Fuses, Fuseholders, Fuse Blocks, and Fuse Accessories

**CORNELL DUBILIER**

Capacitors-Aluminum Electrolytics, Mica, AC Oil, Film, MICA Paper and Relays

A COMPANY OF  
**DALE**

**Dale Electronics, Inc.**

Resistors, Networks, Oscillators, Displays, Inductors, Thermistors, Connectors, & Transformers

**DI DANTONA INDUSTRIES, INC.**

Batteries: Computer, Cordless Phone, Laptop, Scanner, Alarm and Medical  
Antennas: Cordless Phone and Scanner

**DEARBORN WIRE AND CABLE L.P.**



**EATON**

**Eaton Corporation, Commercial & Military Controls Operation**

Switches, Relays, Displays and Keyboards

**FOX ELECTRONICS**

Quartz Crystals, Clock Oscillators, Surface Mount Products, Programmable Devices

A  
**GERNSBACK PUBLICATION**  
Applied Electronics  
Electronics Now Magazine

**GUARDIAN**

Relays and Solenoids

**KEMET**

Electronics Corporation

Multilayer Ceramic and Solid Tantalum Capacitors

**KOA SPEER**

Resistors, SMT Tantalum Capacitors Inductors, Resistor Networks, SMT Thermistors

**MALLORY**

North American Capacitor Company

Tantalums, Aluminums, Sonalerts® Ceramics, Films and AC's

**M-tron**

Quartz Crystal  
Hybrid Oscillators

**muRata®**

Fixed Ceramic Capacitors, Variable Capacitors and Resistors, Crystal Oscillators, Ceramic Filters, Resonators, EMI Filters, Hybrid Circuits and more.

**Panasonic Industrial Company**

Resistors, Resistor Networks, Ceramic, Film, Electrolytic, Double Layer Capacitors, Potentiometers, Switches, Inductors, Filters, Resonators, Varistors, Thermistors

**Philips Components**

Philips Electronics North America Corporation  
Resistors, Ferrite Components  
Aluminum Electrolytic, Film & Ceramic Capacitors

They sell through distributors.

They belong to the E.I.A.

They belong on your vendor list.

**Quam**

Loudspeakers and Commercial Sound Products

**ROHM**

Rohm Electronics Division  
Resistors, Ceramic Capacitors, Transistors/Diodes, Opto Components and IC's

**SELECTA**  
Electronic Electronic Products

Switches, Relays, Terminals, Indicator/Pilot Lights, LED Indicators, Test Clips, Test Leads, Cable Ties and Heat Shrinkable Tubing

A COMPANY OF  
**SPRAGUE**

Tantalum Capacitors, Wet & Foil Capacitors, Resistor Networks, Resistor Capacitor Networks, Filters

**Switchcraft**  
A Raytheon Company

Switches, Connectors, Jacks, Plugs, Jackfields & Audio Accessories, Cable Assemblies

Leadership in electronics is not just a matter of designing products better and manufacturing them better, but also of marketing them better. And the sponsors of this message understand that better service to customers requires effectively involving distributors as part of their marketing teams.

Distributor involvement means lower prices, quicker deliveries, better service over-all. The Buyer wins...the Seller wins.

Distributors help achieve marketing leadership. So does the manufacturer's involvement in the Components Group of the Electronic Industries Association. EIA fosters better industry relations, coherent industry standards, and the sharing of ideas, which helps one another and serves customers better.

In choosing your component supplier, look for the marks of leadership--

availability through distribution membership in E.I.A.



Our 70th Anniversary Year

Electronic Industries Association/Components Group  
2001 Pennsylvania Avenue, N.W., 11th Floor  
Washington, D.C. 20006  
Phone: (202) 457-4930  
Fax: (202) 457-4985

Committed to the competitiveness of the American electronics producer.

# OCEAN STATE ELECTRONICS

HOBBYIST, AMATEUR, OR COMMERCIAL — WE'RE YOUR ONE STOP ELECTRONIC SOURCE  
CALL OR WRITE FOR OUR FREE 120 PAGE CATALOG 1-401-596-3080

## DELUX CODE KEY



Adjustable, heavy duty brass base with ball bearing pivots. Designed for hard usage. 3/16" plated contacts.

\$12.75

## CODE PRACTICE OSCILLATOR & MONITOR IN KIT FORM OR WIRED

A solid-state code practice oscillator and monitor that uses the latest IC circuitry. It contains a 3" built-in speaker, headphone terminals, a volume control and a tone control. It is a attractively packaged with a two color panel. With the addition of a few parts, the unit can easily be converted into CW monitor. It can therefore be used as an operating aid after the code has been learned.



Kit .....\$19.95  
Wired .....\$24.95

## TOROIDS

IRON	FERRITE
T-25-2 .....35	FT37-43 .....60
T-25-6 .....35	FT37-61 .....60
T-37-6 .....45	FT37-77 .....60
T-37-12 .....45	FT50-43 .....75
T-50-2 .....55	FT50-61 .....75
T-50-3 .....55	FT50-77 .....75
T50-6 .....55	FT82-43 .....1.00
T68-0 .....75	FT82-67 .....1.00
T68-2 .....75	FT82-68 .....1.00
T68-6 .....75	FT114-61 .....1.90
T80-2 .....90	FT140-43 .....3.15
T200-2 .....5.00	FT240-61 .....8.00

WE STOCK A COMPLETE LINE OF TOROIDS AND BEADS.

## Q-DOPE

Solution of pure polystyrene in solvents. Dries fast and leaves a clear, protective coating on toroids, coils and transformers, with no or minimal effect on inductive values. May also be used as a cement for molded or fabricated items made of polystyrene.  
(Bottle with Brush 2 fl. oz. 59 ml) .....\$3.75



## VERNIER DIALS

1-1/2" Diameter 0-10 Marking .....\$8.25  
1-1/2" Diameter 0-100 Marking .....\$9.25  
2" Diameter 0-100 Marking .....\$10.25

## SIGNETICS NE602AN

Balanced Mixer/OSC. Popular IC among experimenters for building DC and super-het receivers.  .....\$2.49

## MINI-CIRCUITS SBL-1 DIODE RING MIXER



Double balance Mixer  
LO/RF - 1.500MHz  
RF DC - 500 MHz  
\$7.75

## LINEAR IC'S

NE555	.45
NE564	1.75
LM733N	.65
LM741	.40
UA7805	.49
UA7812	.49
UA7912	.75
LM317T	.79
CA3126E	1.60
CD22402E	9.95

## TRANSISTORS

PN2222A	.10
2N2222A	.32
2N3055	.69
2N3553	2.75
2N3563	.40
2N3866	1.05
2N3904	.10
2N3906	.10
2N4401	.15
MPF102	.49

## MAKE CIRCUIT BOARDS THE NEW, EASY WAY WITH TEC-200 FILM



### JUST 3 EASY STEPS:

- Copy circuit pattern on TEC-200 film using any plain paper copier
  - Iron film on to copper clad board
  - Peel off film and etch
- Convenient 8 1/2 x 11 size  
With Complete Instructions

5 SHEETS .....\$6.25  
10 SHEETS .....\$10.75  
20 SHEETS .....\$16.25  
50 SHEETS .....\$33.50

## NEW! SOFTWARE FOR MAKING PRINTED CIRCUIT BOARDS ON ANY MS-DOS IBM COMPATIBLE PC

- Make single or double sided PC Board artwork, up to 30" x 30".
- Print your artwork on any PostScript™ Laser Printer.
- Produces a 1X positive, ready to use with precoated board. No other artwork required.
- Produce industry standard solder mask and component layout for silkscreen art.


The NEW PCDATAK™ software lets you create PC boards ranging from prototypes to hobby projects, and on a par with the Pro's. You may do the complete printed circuit board layout artwork on your own PC, at a fraction of the cost of other programs. Print the layout on any PostScript™ compatible printer, either on regular paper to be photographed for a positive or negative, or on clear film to be used directly as a positive with other Datak products.

PCDATAK™ will produce soldering pads for all standard components, including the latest in surface mount products. Custom "features" (components) may be designed easily, when needed. User selectable pads and connecting trace widths lets you do any circuit that you can imagine.

The NEW PCDATAK™ software from DATAK may be used on any MS-DOS, IBM compatible personal computer with a system minimum of: a hard drive, 2 megabyte free drive space, 640K RAM, a high density 3.5" diskette drive and a mouse is recommended. Printing does require a PostScript™ printer which can often be found at a local copy center if you do not have your own.

PCDATAK™ is supplied on one 3.5" diskette with a quick start manual. The full user's manual is larger and must be printed by the user (dot matrix printer ok); approximately 75 pages in length

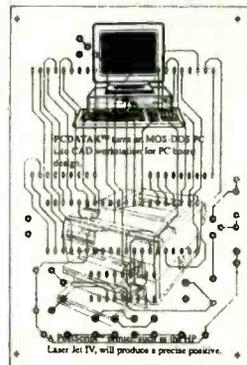12-077 ....PCDATAK™ software with quickstart manual .....\$59.95



## AIRCRAFT RECEIVER KIT

...puts you in the pilots seat!!



Tune into the exciting world of aviation. Listen to airlines, big business corporate jets, hot-shot military pilots, local private pilots, controllers, approach and departure radar control and other interesting and fascinating air-band communications. You'll hear planes up to a hundred miles away as well as all local traffic.

The AR-1 features smooth varactor tuning of the entire air band from 118 to 136 MHz, effective AGC, superheterodyne circuitry, squelch, convenient 9 volt operation and plenty of speaker volume. Don't forget to add our matching case and knob set for a fine looking project you'll love to show. Our detailed instruction manual makes the AR-1 an ideal introduction to two life-long fascinating hobbies at once — electronics and aviation!

AR-1 .... AIRCRAFT RADIO KIT .....\$29.95  
C-AR .... CASE SET FOR AR-1 .....\$14.95

## LEARN COMPUTER THEORY BY BUILDING THIS KIT DIGITAL TRAINER MODEL MM-8000

Starting from scratch you build a complete computer system. Our Micro-Master trainer teaches you to write into RAMs, ROMs and run a 8085 microprocessor. You will write the initial instructions to tell the 8085 processor to get started and store these instructions in permanent memory in a 2816 EPROM. Teaches you all about input and output ports, computer timers. Build your own keyboard and learn how to scan keyboard and display. No previous computer knowledge required. Simple easy to understand instruction teaches you to write in machine language. Upon completion of this course you will be proficient in computer technology.

- Uses the 8085 Microprocessor
- Uses the 2816 EPROM, electrically erasable programmable ROM
- Uses the 8156C, 2048 Bit static MOS RAM with I/O ports and timer
- Memory expandable option
- Built in 5V power supply
- 28 key keyboard
- Complete with lesson manual, instructions and experiments



\$119.95

## TO ORDER

Call 1-800-866-6626 ORDERS ONLY  
(Catalog requests can not be taken on toll free number.)

8:30 a.m. - 5 p.m. EST  
Monday through Friday



OR WRITE TO:  
Ocean State Electronics,  
P.O. Box 1458, Westerly, R.I. 02891

OR FAX TO: CATALOG/ORDERS  
(401) 596-3590 (401) 596-3080

If paying by CREDIT CARD include Card No. and Expiration Date

Mail in orders include \$4.50 shipping/handling  
ALASKA & HAWAII \$11.00  
CANADA \$8.50 - OVERSEAS \$14.00  
Minimum order \$10.00 (before shipping)  
R. I. Residents add 7% Sales Tax

ORDERS RECEIVED BY 1:00 PM EST— SHIP SAME DAY!

Catalog FREE to US Customers.  
Canada, Please send \$2.00 (American funds or US stamps).  
Overseas, Please send \$3.00 (American funds or US stamps).



## COPPER CLAD PC BOARDS

One oz. copper, phenolic base.  
7" x 5" SINGLE SIDED .....\$1.50  
3 1/4" x 6 1/2" DOUBLE SIDED .....\$1.25



## DIGITAL CAPACITANCE/ INDUCTANCE METER

DIGITAL LCR METER measures inductance, capacitance and resistance. At Last! An LCR meter that everyone can afford. Now you can measure coils, transformers, chokes from 1µH to 200H. Capacitors from 1 pfd to 200 mfd and resistors from 1 ohms to 20 meg ohms. All in one handheld instrument.

MODEL LCR-1801 .....\$119.95

## SIGNAL INJECTOR/TRACER KIT

This handy tester is both a signal generator and receiver. As a generator use it to check out an amplifier, stage by stage. Also tests AM radio IF and RF stages. As a receiver you can pin point where a defective part exists. Will transmit and receive simultaneously.

\$18.95



## MAGNET WIRE

Enamel coated solid copper. For winding coils, transformers and toroids. Prices for 1/4 lb. spools

#14	4.00	#20	4.00	#28	4.85	#36	6.85
#16	4.00	#22	4.25	#30	4.85	#38	6.95
#18	4.00	#24	4.25	#32	4.85	#40	7.85
		#26	4.85	#34	6.25		

CIRCLE 260 ON FREE INFORMATION CARD

Enter A World Of Excitement with a Subscription to

# Popular Electronics®

Get the latest electronic technology and information monthly!

Now you can subscribe to the magazine that plugs you into the exciting world of electronics. With every issue of **Popular Electronics** you'll find a wide variety of electronics projects you can build and enjoy.

**Popular Electronics** brings you informative new product and literature listings, feature articles on test equipment and tools—all designed to keep you tuned in to the latest developments in electronics. So if you love to build fascinating electronics, just fill out the subscription form below to subscribe to **Popular Electronics**... It's a power-house of fun for the electronics enthusiast.

## EXCITING MONTHLY FEATURES LIKE:

- CONSTRUCTION**—Building projects from crystal sets to electronic roulette
- FEATURES**—Educational training on digital electronics, Ohm's Law, Antennas, Communications, Antique Radio, Simplified Theory
- HANDS-ON-REPORTS**—User test comments on new and unusual consumer products
- SPECIAL COLUMNS**—Think Tank, Circuit Circus, Computer Bits, DX Listening, Antique Radio, Scanner Scene, Amateur Radio

## PLUS: ALL OUR GREAT DEPARTMENTS!

You'll get 12 exciting and informative issues of **Popular Electronics** for only \$18.95. That's a savings of \$23.05 off the regular single copy price. Subscribe to **Popular Electronics** today! Just fill out the subscription order form below.



FOR FASTER SERVICE CALL TODAY

**1-800-827-0383**

(7:30AM-8:30PM) EASTERN STANDARD TIME

## Popular Electronics® SUBSCRIPTION ORDER FORM

APEC5

P.O. Box 338, Mt. Morris IL. 61054

**YES!** I want to subscribe to **Popular Electronics** for 1 Full year (12 Issues) for only \$18.95. That's a savings of \$23.05 off the newstand price.

(Basic Subscription Rate—1 yr/\$21.95)

Payment Enclosed  Bill me later

Please charge my:  Visa  Mastercard

Acct. #

Signature \_\_\_\_\_

Exp. Date \_\_\_\_\_

PLEASE PRINT BELOW:

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_

ZIP \_\_\_\_\_

Allow 6 to 8 weeks for delivery of first issue. U.S. Funds only.

In Canada add \$6.68 Postage (Includes C.S.T.). All Other Foreign add \$7.50 Postage.



150 LE - Student 200 LE - Technician 300 LE - Auto-Range 400 LE - Engineer

**KELVIN 100 Basic**  
 # 990087 **\$19.95**

- AC & DC VOLTAGES
- DC CURRENT
- RESISTANCE
- 3 1/2 Digit LCD
- CONTINUITY TEST
- -Buzzer
- LOW BATTERY INDICATOR
- DIODE TEST ● BATTERY TEST



**CAPACITANCE KELVIN METER 250 LE \$59.95**  
 # 990126

- 0.5% ACCURACY
- RANGES: 20mF, 2000uF, 200uF, 20uF, 2uF, 200nF, 20nF, 2000pF, 200pF
- Zero Adjust
- Safety Test Leads
- Test Socket for Plug-in Components



**Standard Features** ● AC & DC VOLTAGES ● DC CURRENT ● RESISTANCE ● CONTINUITY TESTER - Buzzer ● DIODE TEST ● 10M ohm INPUT IMPEDANCE ● ACCURACY +/- 0.5% RDG

TRANSISTOR BATTERY TEST  
 DC CURRENT  
 10 Amp

FREQ COUNTER up to 20MHz  
 CAPACITANCE from 1pF to 20uF  
 TRANSISTOR  
 AC/DC CURRENT  
 10 Amp

AUTO RANGE with 3200 counts  
 AC CURRENT  
 DC CURRENT  
 ANALOG BAR  
 10 Amp

INDUCTANCE Resolution 1uH  
 FREQ COUNTER up to 20MHz  
 CAPACITANCE from 1pF to 200uF  
 AC/DC CURRENT  
 TRANSISTOR DUTY %  
 20 Amp

**150 LE**  
 Stock # 990122  
**\$29.95**

**200 LE**  
 Stock # 990123  
**\$49.95**

**300 LE**  
 Stock # 990125  
**\$49.95**

**400 LE**  
 Stock # 990124  
**\$79.95**

Designed to meet IEC-348 & UL-1244 safety specifications.

### Protective Cases

For Models 100 Basic, 150LE, 200LE, 300LE

..... \$4.95 (#990088)  
 Case For Model 400LE ..... \$9.95 (#990116)

**2 Year Warranty (Parts & Labor)**

## The Ultimate Meter

### TRUE RMS - LCR - Hz - dBm

Popular Electronics (Reviewed - May 1993)

"Not only does the Kelvin 94 boast alot of features ... the features go the extra distance."

"If we had to run into a burning building to do some emergency trouble-shooting and could carry in only one piece of equipment, the Kelvin 94 would be it!"

### 12 INSTRUMENTS IN ONE -

DC VOLTMETER, AC VOLTMETER, OHMMETER, AC CURRENT, DC CURRENT, DIODE TESTER, AUDIBLE CONTINUITY TESTER, dBm, FREQ COUNTER, CAPACITANCE METER, INDUCTANCE METER, LOGIC PROBE

- 0.1% ACCURACY ON DC VOLTAGES
- TRUE RMS ON AC VOLTAGES & CURRENT
- FREQUENCY COUNTER TO 20 MHz
- LARGE EASY-TO-READ 3 3/4 DIGIT LCD DISPLAY
- AUTO SLEEP & AUTO POWER OFF BUILT-IN TO SAVE BATTERY LIFE with Bypass
- SHOCK RESISTANT HEAVY DUTY CASE WITH YELLOW RUBBER HOLSTER & TILT STAND
- WATER RESISTANT SEALED CASE
- 30 DAY MONEY BACK SATISFACTION GUARANTEE

**\$199.95** MODEL 94 #990111

COMES COMPLETE WITH YELLOW HOLSTER, PROBES, BATTERY, FUSE, STAND


0.1% ACCURACY on DC Voltages Water Resistant

Freq Counter to 20 MHz
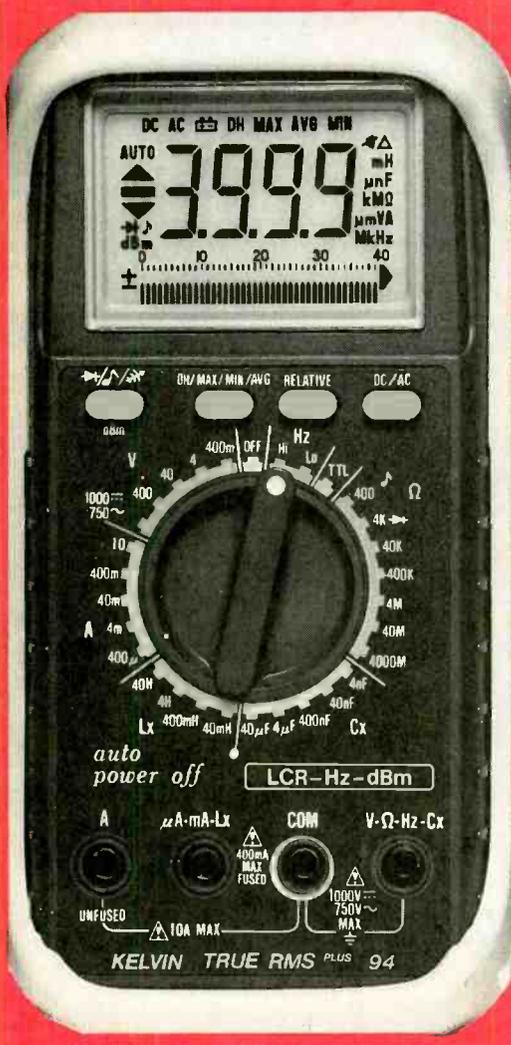
### Protective Cases for Model 94

Regular Padded Zippered ..... \$9.95 (#990116)  
 Deluxe Padded Zippered ..... \$14.95 (#990115)

Meter is designed in accordance with safety requirements specified in IEC-348, UL-1244 VDE-0411.



# USE ELECTRONIC SHOPPER CLASSIFIEDS READ BY MORE THAN 100,000 ELECTRONICS BUYERS AND SELLERS AND TRADERS

## INSTRUCTION FOR PLACING YOUR AD!

### HOW TO WRITE YOUR AD

**TYPE or PRINT** your classified ad copy **CLEARLY** (not in all capitals) using the form below. If you wish to place more than one ad, use a separate sheet for the additional ads (a photocopy of this form works well). Choose a category from the list below and write that category number into the space at the top of the order form. If you do not specify a category, we will place your ad under Miscellaneous or whatever section we deem most appropriate.

We cannot bill for classified ads. Payment in full must accompany your order. We do permit repeat ad or multiple ads in the same issue, but in all cases, full payment must accompany your order.

### WHAT WE DO

The first two words of each ad are set in bold caps at no extra charge. No special positioning, centering, dots, extra space, etc. can be accommodated.

### RATES

Our classified ad rate is \$1.25 per word. Minimum charge is

\$18.75 per ad per insertion (15 words). Any words that you want set in bold or caps are 20¢ each extra. Bold caps are 40¢ each extra. Indicate bold words by underlining. Words normally written in all caps and accepted abbreviations are not charged as all-caps words. State abbreviations must be Post Office 2-letter abbreviations. A phone number is one word.

### CONTENT

All classified advertising in the **Electronic Shopper** is limited to electronics items only. All ads are subject to the publisher's approval. We reserve the right to reject or edit all ads.

### DEADLINES

Ads received by our closing date will run in the next issue. For example, ads received by April 1 will appear in the July, 1995 issue that is on sale in June 1. Shopper ads will appear Jan., Mar., May etc. No cancellations permitted after the closing date. No copy changes can be made after we have typeset your ad. **NO REFUNDS**, advertising credit only. No phone orders.

**AD RATES: \$1.25 per word, Minimum \$18.75**

Send your ads with payment to:

**Electronic SHOPPER, 500-B Bi-County Blvd. Farmingdale, NY 11735**

## CATEGORIES

100 — Antique Electronics	270 — Computer Equipment Wanted	450 — Ham Gear Wanted	630 — Repairs-Services
130 — Audio-Video-Lasers	300 — Computer Hardware	480 — Miscellaneous Electronics For Sale	660 — Satellite Equipment
160 — Business Opportunities	330 — Computer Software	510 — Miscellaneous Electronics Wanted	690 — Security
190 — Cable TV	360 — Education	540 — Music & Accessories	710 — Telephone
210 — CB-Scanners	390 — FAX	570 — Plans-Kits-Schematics	720 — Test Equipment
240 — Components	420 — Ham Gear For Sale	600 — Publications	

## CLASSIFIED AD COPY ORDER FORM

Ad No. 1—Place this ad in Category # \_\_\_\_\_

1 - \$18.75	2 - \$18.75	3 - \$18.75	4 - \$18.75
5 - \$18.75	6 - \$18.75	7 - \$18.75	8 - \$18.75
9 - \$18.75	10 - \$18.75	11 - \$18.75	12 - \$18.75
13 - \$18.75	14 - \$18.75	15 - \$18.75	16 - \$20.00
17 - \$21.25	18 - \$22.50	19 - \$23.75	20 - \$25.00
21 - \$26.25	22 - \$27.50	23 - \$28.75	24 - \$30.00
25 - \$31.25	26 - \$32.50	27 - \$33.75	28 - \$35.00

29 - \$36.25	30 - \$37.50	31 - \$38.75	32 - \$40.00
33 - \$41.25	34 - \$42.50	35 - \$43.75	36 - \$45.00
37 - \$46.25	38 - \$47.50	39 - \$48.75	40 - \$50.00

Ad No 1—Total words \_\_\_\_\_ × \$1.25 per word = \$ \_\_\_\_\_  
 All Caps words \_\_\_\_\_ × .20 per word = \$ \_\_\_\_\_  
 Bold words \_\_\_\_\_ × .20 per word = \$ \_\_\_\_\_  
 Bold Cap words \_\_\_\_\_ × .40 per word = \$ \_\_\_\_\_

**TOTAL COST OF AD No. 1 \$ \_\_\_\_\_**

Card # \_\_\_\_\_

Expiration Date \_\_\_\_ / \_\_\_\_ / \_\_\_\_

Signature \_\_\_\_\_

Total classified ad Payment \$ \_\_\_\_\_ enclosed.

Check  Mastercard  Visa (\$18.75 minimum credit card order)

Name \_\_\_\_\_ Phone \_\_\_\_\_

Address \_\_\_\_\_ City State Zip \_\_\_\_\_

Powerful Integrated Digital and Analog (Berkeley Compatible Spice)  
Circuit Design and Simulation Software for Microsoft Windows (network compatible)



Great Features For Less!! Includes 4 Integrated Modules: LogicDesigner + WinSpice + WinScope + Symbol Editor

Perfect For Students, Technicians and Engineers!!!

Simply connect your circuit on the screen, enter simulation options, then kick back and watch it work!! Comes with two Spice libraries plus 5 more libraries of Active Digital Devices CMOS, 74xx, 74xxx, ALUs, counters, MUX, FFs etc. Plus a Passive symbol library of Microprocessors and more. Use the Symbol Library Editor to Design your own symbols and symbols to represent Sub-circuits, True Bussing, Buss pins can be assigned Unique Names, Parts Billing List, Legends, Nested Subcircuits for Hierarchical Top Down or Bottom Up Design, Checks Fan Out Violation and Electronic Rules, Device Unit Numbers/Chip Pinouts Automatically added as per Data Books, Connectors, Spice Netlist Generation, Continuous ZOOM In/Out, Cut/Copy/Paste, Multiple Rotatable Fonts, Rotatable Symbols, Multiple Zoomed In/Out Printouts to Windows Compatible Printers. ON LINE HELP.

LogicDesigner Digital Simulation/Schematic Capture Module

Interactive Digital Simulation and Schematic Capture, Single Step Mode, Variable Speed Simulation, Programmable Digital Delays, Multi Waveform Scrolling Timing Diagram Memorizes up to 30000 Ticks Worth Of Timing Data, Truth Table Generation, Binary to 7 Segment Displays, Hex Keypads, Programmable Clock Sources, Logic Probes. Built in Logic Analyzer can be set up to generate Edge or Level Sensitive Breakpoints, or when Signals are Equal To, Greater Than, or Less Than a Certain Value or any AND/OR Combination. Sequential Breakpoints help Track Down and Debug Circuit Race Conditions Glitches, Setup and Hold Violation and other Circuit Design Errors. Simulates Tri State, Open Collector & Don't Care Logic, RAM/ROM, One Shot, Carry Look Ahead, Shift reg, Pull Up/Down Resistors, Test Vectors.

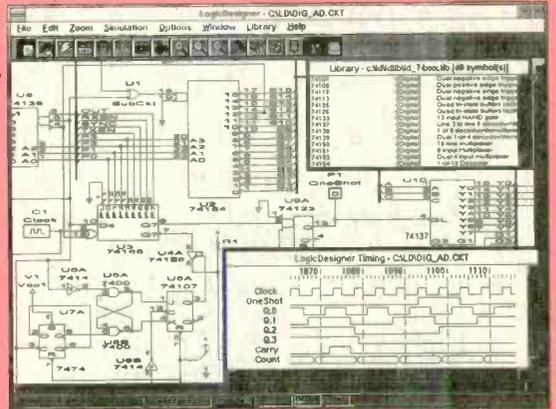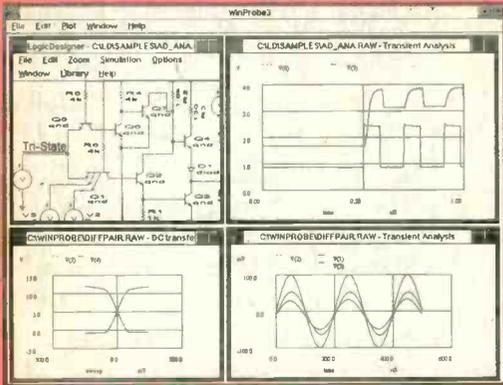

WinSpice Simulator & WinScope Data Analyzer Modules

SPICE LIBRARY: MOSFET, GaSfET, BJT, FET, Diode, OpAmps, Comparators, 555 Timer, Resistor, Cap, Inductor, Transmission Line, Controlled, Independent, Dependent, Arbitrary Source, Pulse, Sin, Piece Wise Linear, and FM Sources, Current and Voltage Controlled Switches. All models Expandable And User Modifiable. Imports MACRO MODELS of Your Favorite Manufacturer Supplied Parts.

ANALYSIS TYPES: AC, DC, TRANSIENT, POLE-ZERO, NOISE, SENSITIVITY, FOURIER, TRANSFER FUNCTION, AND OPERATING POINT ANALYSIS.

DATA ANALYZER: Graphs Simulation Results using Multiple Plot Windows and Waveforms. Plots Linear, Logarithmic, Polar, Smith Chart, BODE Type Plots + More. ZOOM In and out of Plot Waveforms. Plots Complex Math Expressions Using Plot Variables As Arguments, Calculates Derivatives, Log, Trig functions, Define Macros of Complex Math Formulas.

\$69.99 (limited time offer) Regular Price \$179.99 S&H \$3.00 VISA/MC

ISLAND LOGIX INC.

920 South West 95 Terrace  
Pembroke Pines, Florida 33025 U.S.A.  
PH (305) 435-7665 FAX (305) 435-7891



New Version!!!



CIRCLE 320 ON FREE INFORMATION CARD

Professional Electronic Engineering Software

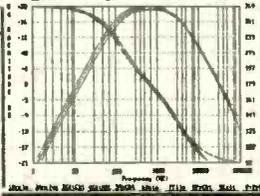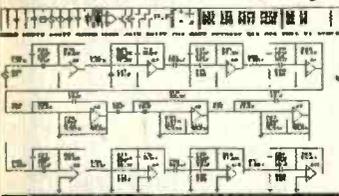Unbeatable Prices. Any Program just \$19.99



LINEAR AC/DC CKT ANALYSIS

Active & Passive circuits. Up to 70 nodes, 225 elements. Models for active devices. Calc, Plot & Print AC voltages & currents. Calc DC current, voltage & power. Plots: Lin, Log, Semi, Polar, etc.

LINEAR TRANSIENT CKT ANALYSIS

10 Programmable Input Transients. Active, passive ckt. Up to 70 nodes, 225 elements. Models for active devices. Calc, plot & print output Transient voltages. Calc dc current, voltage & power. More.

ACTIVE FILTERS DESIGN ANALYSIS

Design/Analyze active LPF, BPF, HPF, Butterworth, Chebyshev, Bessel & All pass filters. Plot response.

TRANSIENT SYSTEM ANALYSIS

Calc, plot transient response of system H(s). 14 Input Transients. Inverse Laplace. Edit H(s). More.

POLYNOMIAL OPERATIONS

Calc polynomials Roots, Product & Coefficients.

- ★ Flexible, Powerful & Easy to use
- ★ Essential Tool Set for Engineers
- ★ Dot Matrix/Laser/Mouse Support
- ★ User's Manual Included on Disk

SPECIAL 9-PROGRAM INTEGRATED PACKAGE  
V3.1 WITHOUT SCHEMATIC DRAW \$249.99 \$79.99

COMPLETE 12-PROGRAM INTEGRATED PACKAGE  
V3.2 WITH SCHEMATIC DRAW \$329.99 \$129.99

VISA/MC ACCEPTED, \$5.95 SHIPPING, CA ADD 7.25% TAX

Performance Guaranteed

REQ: PC AT, 640K BASE MEM, EGA/VGA COLOR DISPLAY WITH 256K RAM, DOS 3.2 OR HIGHER, MS MOUSE, 3MB SPACE ON HARD DRIVE

To order or info call/fax 1(619)384-3042 or

send check or money order to

GEOMB ENGINEERING, PO BOX 658, RIDGECREST CA 93556

Radiotelephone - Radiotelegraph

FCC Commercial License

Why Take Chances?

Discover how easy it is to pass the exams. Study with the most current materials available. Our Homestudy Guides, Audio, Video or PC "Q&A" disks make it so fast, easy and inexpensive. No college or experience needed. The new commercial FCC exams have been revised, covering updated Aviation, Marine, Radar, Microwave, New Rules & Regs, Digital Circuitry & more. We feature the Popular "Complete Electronic Career Guide". 1000's of satisfied customers Guarantee to pass or money back. Newest Q&A pools.

Send for FREE DETAILS or call 1-800-800-7588

WPT Publications  
4701 N.E. 47th St.  
Vancouver, WA 98661

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ St. \_\_\_\_\_ Zip \_\_\_\_\_

1-800-800-7588

March 1995, Electronics Now

# Digital Storage Oscilloscope

Digital Volt Meter




Data Logger


Frequency Counter

Spectrum Analyzer

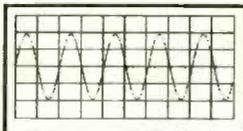Allison O-Scope Modules convert PC-ATs into multipurpose test and measuring instruments



Low Distortion Sine Wave and Spectrum

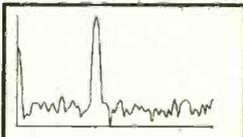

## Features:

- Small & Portable
- Easy to Use
- Software Included
- Uses Printer Port
- AC or DC Input
- 10v/div. to 50 mv/div.
- Sample Rate to 100KHz
- Optional Dual Trace
- Logging to Disk
- Print Screens
- Optional Probe Sets
- Optional Ext. Trigger
- Power 12VDC, 40 ma.
- Made in U.S.A.

## Screen Captures of Actual Signals

## Uses:

- Audio/Stereo Equip.
- Automotive Diagnostics
- Analytical Instruments
- Education & Training
- Field Service
- Industrial Controls
- Laser Repair
- Medical Electronics
- Power Supplies
- Sound Systems
- Vibration Analysis

Orders & Inquiries: 1-800-980-9806  
 Technical Assistance: 1-713-777-0401  
 Fax & BBS: 1-713-777-4746

Allison Technology Corporation  
 8343 Carvel, Houston, TX 77036

CIRCLE 325 ON FREE INFORMATION CARD

# Miniature Robots!



Build a real walking robot just 14 cm long!

## Muscle Wires Project Book & Deluxe Kit

Create direct linear action with *Muscle Wires*. They actually contract up to 5% when powered! For robots, planes, railroads - anything needing small, strong all-electric motion. Our new info packed 128 page *Project Book* has full plans for *Boris* the motorless robot and 14 other projects. Deluxe Kit includes one meter each 50, 100 and 150  $\mu$ m diameter Muscle Wires. *Get moving today!*

#3-168 \$59.95

New!

## Electric Piston Deluxe 5-Pack

Incredible miniature cylinders lift 1 pound each! Just 10 cm long, they shorten by 23 mm with just 1 volt, 5 amps. Cycles up to 6 times per minute. Pack has 5 Electric Pistons, one high current battery and complete plans for four unique projects.


#3-137 \$39.95



## Robot Builder's Bonanza, 99 Inexpensive Robotics Projects

A huge collection of practical, ready-to-use circuits & devices. Sections on parts, tools, methods, remote control, vision, grippers, navigation & more! 336 pages, 280 illus. A great value for robot builders of all experience levels.

#3-114 \$17.95

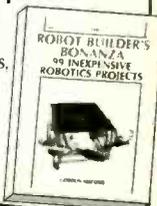

## Space Wings II - now variable speed

Sleek silver wings flap silently using only 5 cm of Muscle Wire. Perches on your PC, annoys cats! Flaps up to 36 times per minute. With circuit board, parts, detailed instructions. Requires soldering and 2 AA batteries. Makes an ideal introduction to electronics and Muscle Wires.

#3-001 \$19.95



Order Toll Free!

24-hour Voice Order Line - VISA MasterCard

800-374-5764

Request our FREE Muscle Wires Technical Brochure

Mondo-tronics

524 San Anselmo Ave. #107-74  
 San Anselmo, CA 94960


Questions: 415-455-9330  
 Fax: 415-455-9333  
 Internet: info@mondo.com

To Order: Send check, MO or credit card info. All orders add \$5.00 P & H. Calif. orders also add sales tax.

International Orders Welcome! First Class P&H: \$11.00

# AMAZING Electronic and Scientific Products

## Mystery Levitating Device!

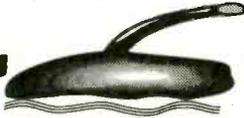

Remember War of the World? Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or great science project.

ANT1K Easy to Assemble Kit / Plans ..... \$19.50

## Laser Ray Gun



**DANGER**  
 INVISIBLE LASER RADIATION  
 AVOID EYE OR SKIN EXPOSURE  
 TO DIRECT OR SCATTER RADIATION  
 CLASS IV LASER PRODUCT

Advanced project produces a burst of light energy capable of burning holes in most materials. Hand-held device uses rechargeable batteries. 500 joules of flash energy excite either a neodymium glass, yag or other suitable 3" laser rod. This is a dangerous CLASS IV project (individual parts/assemblies available). LAGUN1 Plans ..... \$20.00  
 LAGUN1K Kit / Plans ..... Price on Request

## Extended Play Telephone



## Recording System

READY TO USE! Automatically controls and records on our X-4 extended play recorder, taping both sides of a telephone conversation. Intended for order entry verification. Check your local laws as some states may require an alerting beeper.

TAP20X Ready to Use System ..... \$129.50



## Shocker Force Field / Vehicle Electrifier

Neat little device allows you to make hand and shock balls, shock wands and electrify objects, charge capacitors. Great payback for those wise guys who have wronged you!

SHK1K1M Easy to Assemble Electronic Kit ..... \$24.50



**BANG!**

## Blaster Pulsar


Pocket-sized wand produces 100,000 watts of power for personal defense, field and lab use, etc. BLS3 Plans ..... \$10.00  
 BLS3K Kit / Plans ..... \$69.50

## Homing / Tracking Transmitter

Beeper device, 3 mile range.  
 HOD1 Plans ..... \$10.00 HOD1K Kit / Plans ..... \$49.50
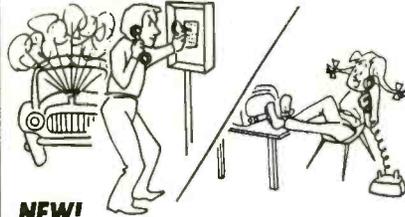
## Listen Through Walls, Floors

Highly sensitive stethoscope mike.  
 STETH1 Plans ..... \$8.00 STETH1K Kit/Plans ..... \$44.50



**NEW!**

## INFINITY TRANSMITTER++

### Room Monitor / Phone Line Grabber

**ALL NEW!** The Ultimate in Home or Office Security & Safety! Simple to Use! Call your home or office phone, push a secret tone on your telephone keypad to access either: A. On premises sounds and voices; or B. Existing telephone conversation with break in capability for emergency messages. CAUTION: Before assembly or use, check legalities with your state Attorney General's office as you may require "beepers" or other 3rd party alerts. TELEGRAB1 Plans Only ..... \$10.00  
 TELEGRAB1K Kit / Plans ..... \$99.50

## Visible Beam Laser

Easy to build, RED Beam, visible for miles. Use for light shows, window bounce holography, cloud illumination and much more! LAS1KM Kit w/1mw Laser Tube, Class II ..... \$69.50  
 LAS3KM Kit w/2.5mw Laser Tube, Class IIIA ..... \$99.50

## 100,000V Intimidator / Shock Wand Module

Build an electrical device that is effective up to 20 feet. May be enclosed for handheld, portable field or laboratory applications.  
 ITM2KM Easy-to-Assemble Electronics Kit ..... \$49.50  
 ITM2 Plans only, credit-able to kit ..... \$10.00



## Ion Ray Gun

Projects charged ions that induce shocks in people and objects without any connection! Great science project as well as a high tech party prank. IOG3 Plans ..... \$8.00  
 IOG3K Kit/Plans ..... \$69.50

## Invisible Pain Field Generator

Shirt pocket size electronic device produces time variant complex shock waves of intense directional acoustic energy, capable of warding off aggressive animals, etc.  
 IPG7 Plans ..... \$8.00 IPG7K Kit/Plans ..... \$49.50  
 IPG70 Assembled ..... \$74.50

## 1000 Ft++ Potato Cannon

**NOT A TOY.** Uses electronic or piezo ignition. CAUTION REQUIRED!  
 POT1 Plans ..... \$10.00  
 (Dangerous Product).....\$10.00

## FireBall Gun

Shoots flaming ball - two shot capacity  
 Great for special effects and remote fire starting. CAUTION REQUIRED!  
 FIREBALL Plans (Dangerous Product).....\$10.00



## TV & FM Joker / Jammer

Shirt pocket device allows you to totally control and remotely disrupt TV or radio reception. Great gag to play on family or friends. Discretion required.  
 EJK1KM Easy to Assemble Electronic Kit ..... \$24.50

## ATTENTION: High Voltage Fans!

4,000 volts in the palm of your hand! Experiment with anti-gravity, hovercraft, ion guns, force fields, plasma guns, shock devices, wireless energy and electrical pyrotechnics. Input: 9-14VDC.  
 MINIMAX4 Ready to Use ..... \$19.50



## "Laser Bounce" Listener System

Allows you to hear sounds from an area via a lite beam reflected from a window or other similar objects. System uses our ready-to-use LATR1 Laser Terminator gun site as the transmitter. The receiver section is supplied as an easy-to-build kit, including our cushioned HS10 headsets. LLIST2 Plans ..... \$20.00  
 LLIST1K Kit of Both Transmitter and Receiver .... \$199.50  
 LLIST20 Assemble with Laser Gun Site ..... \$299.50

## 3mw Visible Red Pocket Laser

Utilizes our touch power control!  
 VRL3KM Kit / Plans ..... \$74.50



## Electronic Hypnotism

Puts subjects under control using highly effective electronic stimuli. Intended for parties and entertainment but must be used with caution. Includes valuable text book reference and plans.  
 EH2 Plans and Text Book ..... \$19.50

## Automotive NEON!



Easy-to-Install 4-Tube Kit for Cars, Trucks, Vans! Available in Pink, Purple, Blue or Green - please specify color when ordering.  
 RG4K (Specify Color) ..... \$129.50  
 License Frame Kit (Specify Color) LIC1K ..... \$29.50  
 Flash-To-Music Option for above kit FMU1 ..... \$29.50

## 3 Mi FM Wireless Microphone



Subminiature! Crystal clear, ultra sensitive pickup transmits voices and sounds to FM radio. Excellent for security, monitoring of children or invalids. Become the neighborhood disk jockey!  
 FMV1 Plans ..... \$7.00 FMV1K Kit and Plans ..... \$39.50

## Telephone Transmitter - 3 Mi

Automatically transmits both sides of a telephone conversation to an FM radio. • Tunable Frequency • Undetectable on Phone • Easy to Build and Use • Up to 3 Mile Range • Only transmits during phone use. VWPM7 Plans ..... \$7.00  
 VWPM7K Kit/Plans ..... \$39.50

**INFORMATION UNLIMITED**

Dept ENS17, Box 716, Amherst, NH 03031  
 Phone: 603-673-4730 FAX 603-672-5406  
 MC, VISA, COD, Checks accepted Please add \$5.00 Shipping & Handling

**CATALOG**  
 With many more items!  
 Free with Order or send \$1 P&H

Order by Mail or by 24 Hour Orders-Only Phone  
**800-221-1705**



# Invest a stamp Save a bundle

For the price of a stamp, you can get the latest edition of the federal government's free **Consumer Information Catalog**. It lists more than 200 free or low-cost publications on federal benefits, jobs, health, housing, education, cars, and more, to help you save money, make money, and spend it a little more wisely.

So stamp out ignorance with our free **Catalog**. Send your name and address to:

**Consumer Information Center, Department SB, Pueblo, Colorado 81009**



The "Checker 12" is a hand held, battery/AC operated computer color monitor pattern generator.

The "Checker 12" fills a need in both the field service and shop maintenance areas. With the "Checker 12", a field service technician can quickly isolate display problems without having to open the computer. By simply connecting the monitor to the "Checker 12", most problems can be quickly isolated. No more swapping video cards or monitors. In the shop, no longer will you need to search for the correct video card, or tie up a computer system to test or burn in a monitor. With its support of CGA, EGA, MACII, and VGA modes 1,2,3, 300x600, 1024x768NI, 1024x768NI with sync on Green, you can easily checkout a monitor in all of its modes.

With the "Checker 12", it is easy to test those monitors in the warehouse or on a storage shelf. You can quickly tell if the monitor is a VGA, SVGA, or a SVGA/NI. No more guessing. With its ease of operation, anyone can checkout a monitor. Even a non technical person can demonstrate proper monitor operation for the customer.

The "Checker 12" provides various test patterns for VGA monitors. With cross hatch, White screen, and Color bars with GRAY SCALE, monitor testing is easier than ever. The pattern and mode are selected with the single mode switch. Both size and position can be set with the "CHECKER 12". Its' colorbar/8 step gray scale pattern allows quick evaluation and/or setting of color balance and tracking.

The "Checker 12" is one piece of equipment that any organization that supports monitor must have.

**Price: \$295.00 includes battery, AC adapter, MAC adapter, and 120 day warranty.**

We also have the "Checker VI", a 6 port, stand-alone VGA (640x480) test pattern generator. NO computer required. only \$249.95



**Computer & Monitor Maintenance**

6649 Peachtree Ind., Blvd., Suite N-1 • Norcross GA 30092  
1-800-466-4411, 404-662-5633 (Voice), 404-840-8814 (Fax)

Whaddya Say To  
A Guy Who's Had  
The Same Job  
For 50 Years,  
Has Never Called  
In Sick Or  
Showed Up Late,  
Never Taken A  
Vacation Or A  
Holiday, Never  
Asked For A  
Raise Or Griped  
About His Bonus  
And, Believe It Or  
Not, Has No  
Plans For  
Retirement?



Thanks.

Remember - only you can prevent forest fires.

# Don't Despair...REPAIR!

Here's how to troubleshoot and repair your electronics successfully!

## You Can Be Your Own Repair Expert!

For VCRs, camcorders, audio equipment, TV equipment, computer hardware, office equipment, home appliances, automobile electronics, and outdoor equipment.

- Pinpoint and analyze problems quickly.
- Successfully complete repairs with hands-on troubleshooting instructions.
- Become skilled understanding flowcharts and schematic diagrams.
- Confidently use test equipment such as oscilloscopes, frequency counters, and video analyzers.
- Keep your equipment in top condition with effective preventive maintenance techniques.

## Continue to Broaden Your Repair Expertise!

You'll receive quarterly supplements, up to 160 pages, with new step-by-step repair and maintenance instructions, valuable schematics and new repair techniques. Learn how to repair a growing variety of appliances with hands-on repair projects that will keep you up-to-date with later models and technology. You'll be thrilled with your ability to repair a growing list of electronic equipment! Supplements may be returned or cancelled at any time.

### SAVE \$10

Call our toll-free number, pay by credit card, and mention this ad. We'll deduct \$10!

We'll also waive shipping and handling.

Order today for your 30-day, no-risk review of *The Electronics Repair Manual*.

For Faster Service Call TOLL-FREE  
**1-800-222-WEKA**  
 Or Fax To: 1-800-256-5915

CIRCLE 324 ON FREE INFORMATION CARD



## One Source For All Your Repair Needs!

Better organized than a magazine, more current than a book.

- 900-page manual
- easy-to-follow, detailed instructions
- trouble analysis flowcharts
- safety precaution checklists
- comprehensive replacement parts list
- directory of manufacturers



Order your copy today!

### MONEYBACK GUARANTEE

There's no risk in trying the **ELECTRONICS REPAIR MANUAL** to see if it's right for you. If you are not delighted, simply return the manual after the 30-day trial period and receive a prompt refund.



1077 Bridgeport Ave.  
 Shelton, CT 06484

**YES!** Please rush me a copy of the new *Electronics Repair Manual* for only \$59.95 + \$5.50 shipping and handling. I understand that if I am not satisfied I may return the manual within 30 days for a complete refund. Supplements are sent quarterly for 25¢ per page (never more than \$30) and may be returned or cancelled at any time.

My payment is enclosed  Bill me later  
 Charge my  Visa  MasterCard

Acct. No. \_\_\_\_\_ Exp. Date \_\_\_\_\_

Signature \_\_\_\_\_

Phone ( ) \_\_\_\_\_ Signature and phone number are required for all orders.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

All payments must be in U.S. funds. Canada add \$10. All other countries add \$15. CT residents add 6% sales tax.

Mail to: WEKA Publishing, 1077 Bridgeport Ave.  
 Shelton, CT 06484

30380

**BLOWOUT!**

# TIMELINE INC.

Over 8 years and 23,000 customers and still growing.

**BLOWOUT!**

## LIQUID CRYSTAL DISPLAYS

**160 x 128 dot LCD**  
with Built-in controller. (T6963C)

20 character x 16 line capability.

**\$79.00** 2 for **\$149.00**

Mfr: Toshiba TLX-1013-EO.

Unit is EL back-lit. Dim: 5" 1/16 L x 4" 1/16 H.

The built-in controller allows you to do text and graphics without adding an additional controller card.

### Alphanumeric—parallel interface

16 x 1	3 for \$25.00	16 x 2	\$8.00
20 x 2	\$12.00	16 x 4	\$25.00
20 x 4	\$25.00	24 x 2	\$12.00
32 x 4	\$20.00	40 x 2	2 for \$25.00
40 x 4	\$25.00	4 x 2	\$5.00

5V power required • Built in C-MOS LCD driver & controller • Easy "Microprocessor" interface • 98 ASCII character generator • Certain models are backlit, call for more info.

### Graphic and alphanumeric—serial interface

Size	Mfr.	Price
640 x 480	Epson	\$50.00
640 x 400 (backlit)	Panasonic	\$35.00
640 x 200	Toshiba	\$19.00
480 x 128	Hitachi	\$15.00
256 x 128	Epson	\$25.00
240 x 128 (backlit)	Optrex	\$20.00
160 x 128	Optrex	\$15.00

## LASER PRODUCTS

**HeNe Laser Head** (10mw max. output) TEM00, 15.5" long MFG:NEC **\$99.00**  
**Laser Power Supply** (for HeNe tube) **\$100.00**

**LASER SCANNER ASSEMBLY \$29.00**

Assembly intended for a laser printer. Includes laser diode, polygon motor (6 sided) and misc. optics and lenses.

**LASER DIODE (5mW) with collimator \$20.00**

**LASER DIODE: Sharp part#: LT022MC**  
5mw at 780 nm, single transverse mode **\$10.00**

## NETWORK

**IRMA BOARD 8 bit \$99.00**

Links 3270 mainframe systems to IBM PC

**Proton ProNet-4 Model p1347 Token Ring Board \$79.00**

16 bit • 4 Mbps • IEEE 802.2 and 802.5 compatible • twisted pair • interoperable with IBM Token Ring network

## POS & BAR CODE

**MAGNETIC CARD READER \$25.00**

Includes: • 20 character dot matrix display with full alpha-numeric capability • keypanel with full alpha-numeric entry • separate 7.5 VDC/0.5 Amp power supply • standard telephone interface extension cord • lithium battery and flat-cone speaker.

**HP bar code wand (HBCS 2300).....\$35.00**

## POWER SUPPLIES

**73 WATT SWITCHING \$15.00 or 2 @ \$25.00**, (2) 4 pin power connectors attached • 115/230 Volt, Dim: 8.5" L x 4.5" W x 2" H • Output: +5V @ 2-9.75 A, +12V @ 0-1.5 A, -5V @ 0-0.4 A, -12V @ 0-0.5 A

**68 WATT SWITCHING \$12.00 or 2 for \$20.00**, 115/230 Volt, Dim: 5.5" L x 3.2" W x 1.7" H • Output: 5V @ 4 A, 12V @ 4 A

## MISCELLANEOUS

**ADAPTEC 4070A (RL) OR 4000A (MFM) SCSI Controller, your choice \$40.00**

**IBM 370 option XT and AT emulation boards \$50.00**

23605 TELO Ave, Torrance, CA 90505

Order desk only: USA: (800) 872-8878 CA: (800) 223-9977 L.A. & Technical Info: (310) 784-5488 Fax: (310) 784-7590

**OEM INQUIRIES WELCOME**

Minimum Order: \$20.00. Minimum shipping and handling charge \$5.00. We accept cashiers checks, MC or VISA. No personal checks or COD's. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders..

## MONITORS

**Non-Enclosed TTL**      **Enclosed**

Comes with pinout. 12V at 1.4 Amp input.      9" Green BNC composite 115V/230V      \$69.00  
Horizontal frequency 15Khz.      12" White BNC composite 24V      \$79.00  
Ability to do 40 and 80 column.

5 inch Black & White      \$35.00  
7 inch Amber      \$39.00  
9 inch Amber      \$29.95  
12" Green or B/W      \$19.95

Mfr.: Electrhome • For Very High Quality Medical & Industrial Applications

**5" COLOR MONITOR \$69.00**



• Flat Faceplate • 320 x 200 Dot Resolution • CGA & Hercules Compatible  
• 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq.  
• Open Frame Construction • Standard Interface Connector  
• Degaussing Coil Included • Mfg.: Samtran

## CHARGE COUPLED DEVICES

**MATRIX TYPE**



**"The Spy In The Sky" \$49.00**

Sony CCD Imager - designed for black and white composite video cameras. Picture elements: 384 (H) x 491 (V)

Chip size 10.7 (H) x 9.3 (V) mm<sup>2</sup> • Unit cell size 23.0 (H) x 13.4 (V) um<sup>2</sup> • Ceramic 24 pin DIP package. • Mfr: Sony, Part# 016AL

**4096 element CCD \$29.00**

**LINEAR TYPE**

**2048 element CCD \$15.00 • 1728 element CCD \$15.00**

## HACKER CORNER

**CELL SITE TRANSCEIVER \$99.00**

These transceivers were designed for operation in an AMPS (Advanced Mobile Phone Service) cell site. The 20 MHz bandwidth of the transceiver allows it to operate on all 666 channels allocated. The transmit channels are 870.030-889.980 MHz with the receive channels 45 MHz below those frequencies. A digital synthesizer is utilized to generate the selected frequency. Each unit contains two independent receivers to demodulate voice and data with a Receive Signal Strength Indicator (RSSI) circuit to select the one with the best signal strength. The transmitter provides a 1.5 watt modulated signal to drive an external power amplifier. Channel selection is accomplished with a 10 bit binary input via a connector on the back panel. Other interface requirements for operation are 26 VDC (unregulated) and an 18.990 MHz reference frequency for the digital synthesizer. The units contain independent boards for receivers, exciter, synthesizer, tunable front end, and interface assembly (which includes power supplies and voltage-controlled oscillator). Service manual, schematics and circuit descriptions are available.

**Proxim — Spread Spectrum RF Modem \$99.00**

The Proxlink is a small communication device that replaces the use of an RS-232 cable hook-up with wireless (Radio Frequency) technology. Each module combines the functions of an RS-232 compatible modem (or any other RS-232 device) and a transmitter/receiver operating in the 902-928 MHz band. Indoor range of up to 500 feet possible using standard 1/4 wave antenna. Units support data rates up to 19.2 KBaud (full duplex) and use multiple channels to allow for non-interfering overlapping systems. Message format is 8 data bits, no parity, and 1 stop bit. Each unit requires 5 VDC supply at a maximum of 230 mA. A wide variety of configurations can be accommodated with parameters stored in non-volatile memory (EEPROM). Configuration changes are supported by menu driven, on-board software. Installation schematics and application details are available. Original cost on these units is around \$600.

## Portable Micro Terminal

Flip up LCD display (9-16 VDC) • Can communicate with any computer having RS 232 port • Can communicate with another Microterminal • Use by itself as electronic notebook • Onboard microprocessor, data RAM (32K) and Video RAM (64K) • Complex built in diagnostics and set up capabilities. • Original intention for POS applications. • display size 40x16 (256 x 128 pixels.) Dimensions: 6.3" W, 11"L, 2"H. (With LCD up height is 7.1") **\$99.00**  
or 2 for **\$149.00**




**All in one 286 board \$29.00**

Includes: • 286-12Mhz CPU (1 wait state) • Built in IDE & floppy controller • 80287 math coprocessor socket • FAST! on board SVGA with 256K RAM • 2 serial ports, 1 printer port, mouse port • EMS-LIM ver 4.0 memory & shadow RAM support • Up to 8 mb memory (256K or 1 Mb SIMMS) • Comes with OK on board • On board speaker • REAL TIME CLOCK • Phoenix BIOS • Note: There is one long non standard bus connector on board


Electronics Now, March 1995

# NEW BASIC STAMPS!®


## Stamp-Sized Modules Run BASIC

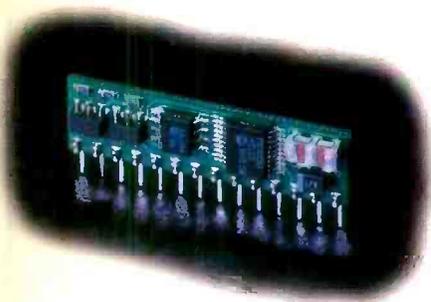

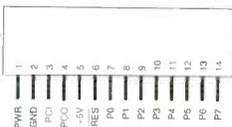**BASIC Stamp I Module (BS1-IC)**  
 8 general-purpose I/O lines  
 256-byte program space (100 instructions)  
 4-MHz clock (2400 baud serial, etc.)  
**\$29, \$39 with carrier board\***



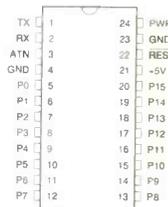**BASIC Stamp II Module (BS2-IC)**  
 16 general-purpose I/O lines  
 2048-byte program space (600 instructions)  
 20-MHz clock (9600 baud serial, etc.)  
**\$49, \$59 with carrier board\***



They're here! These new BASIC Stamp modules are the latest computers. These modules are perfect for numerous applications, from controlling model trains to monitoring factory sensors. They have 8 or 16 I/O lines, which can be used for a variety of digital and analog purposes. And like the original BASIC Stamp, these modules are programmed in BASIC. Our special "PBASIC" language includes familiar instructions, such as GOTO, FOR...NEXT, and IF...THEN, as well as SBC instructions for serial I/O, pulse measurement, and button debounce. In the new BS2-IC, there are even instructions for interfacing to popular devices from other companies, such as the Dallas Semiconductor "Time-In-a-Can" real-time clock.

\*Carrier board provides battery clips, prototype area, and PC connector.

The BASIC Stamp Programming Package contains everything you need to program Stamps using your PC. The package includes our editor software, programming cables, manuals, application notes, and free technical support. The package is available for \$99. Stamps must be purchased separately.

# PIC<sup>®</sup>16/17Cxx DEVELOPMENT TOOLS

## New prices make PIC development more affordable



### ClearView<sup>™</sup> In-Circuit Emulators

20-MHz in-circuit debugging for PIC16C5x/64/71/84/...  
 Set breakpoints, step through code, and modify registers.  
 Friendly DOS and Windows software.  
**\$499 each!** (separate units for "5x" and "xx" PICs)



3805 Atherton Road, #102 • Rocklin, CA 95765 • USA  
 (916) 624-8333 • Fax: 624-8003 • BBS: 624-7101

**PIC Programmer Hobbist Pack**  
 Programmer for PIC16C5x/64/71/74/84/...  
 Documentation on disk.  
 User-supplied cables and power supply.  
**Just \$99!**



Clearview is a trademark and BASIC Stamp & the Parallax logo are registered trademarks of Parallax, Inc. • PIC is a registered trademark of Microchip Technology, Inc. Features and prices subject to change without notice. • Prices are U.S. prices only; prices in other countries may vary.

CIRCLE 195 ON FREE INFORMATION CARD  
[www.americanradiohistory.com](http://www.americanradiohistory.com)


# WNA!



Actual Size
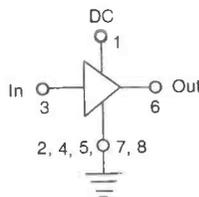
## VNA Amplifiers +17.5dBm, 0.5 to 2.5GHz **\$295** only (1000 qty.)

*Very New Amplifiers...* at a very affordable price, from Mini-Circuits! Yes, VNA-25 RF amplifiers are very small, yet incredibly powerful (+17.5dBm typ. output at 1dB compression). The SOIC-8 pin surface mount units operate directly from a +3V to +5V single DC supply with 18dB typ. gain and cover the popular 0.50-2.50GHz wireless band. These units are very easy to use because all capacitors are internal and RF/DC connections are separate, eliminating the need for both external coupling capacitors and an RF choke. You can buy these very new amplifiers for the low price of just \$2.95 ea., qty.1000. Development qty.10, only \$4.95ea.! So, call Mini-Circuits today for immediate off-the-shelf availability and guaranteed 1 week shipment.



Freq.(GHz)	.5-.8	.8-1.0	1.0-2.0	2.0-2.5
Gain (dB) typ.	14.0	17.0	18.0	16.0
Max. Output (dBm)				
@1dB Comp. typ.	+18.0	+18.5	+17.5	+17.0
I/P 3rd Order (dBm) typ.	+27	+27	+27	+27
VSWR Output typ.	1.5:1	1.7:1	1.7:1	1.5:1
VSWR Input typ.	6.4:1	2.8:1	2.0:1	1.4:1

DC Power: +5.0V for specified performance.  
 Current (mA): 85 typ., 105 max.  
 Thermal Resistance, Junction-to-case: 125°C/W  
 Price (\$ ea. : 2.95 (qty. 1000), 4.95 (qty. 10).

- All specs at 25°C (case temp. 35°).
- Available in Tape and Reel.
- MTTF at 150°C max. junction temp.:  $3 \times 10^7$  hrs. typ.
- "Case" is defined as mounting surface of leads.

**Mini-Circuits...we're redefining what VALUE is all about!**

# Mini-Circuits®

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500 Fax (718) 332-4661

For detailed specs on all Mini-Circuits products refer to • THOMAS REGISTER Vol. 23 • MICROWAVES PRODUCTS DIRECTORY • EEM • MINI-CIRCUITS' 740- pg. HANDBOOK.

**CUSTOM PRODUCT NEEDS...Let Our Experience Work For You.**

F 180 Rev Orig