

RADIO NEWS.

MAY
1947
35c

*2 tubes
1 ham radio
having 2 6J6's*



LAURENCE THORSON
RN-57-J60789-48
DALLAS WIS

ARTS SHOW
MAY 13-16



The Collins 310B Exciter puts Versatility and Precision into your rig

The 310B is the answer to many requests for a multi-band exciter utilizing the Collins 70E-8 P.T.O. (Permeability Tuned Oscillator). Conservatively rated at 15 watts output on all amateur bands up to 30 mc, it will drive a kilowatt pentode final on phone or cw. It provides accuracy and stability of $\frac{1}{2}$ kc on 80 meters, and precision control on all bands.

The bandswitching buffer stages are ganged, condenser tuned, and permeability trimmed. All trimmers are adjusted from the top of the chassis. In the M. O. Test position the plate voltage is removed from the output tube; thus the exciter can be tuned while you listen to a

received signal. The power switch can be interconnected with other equipment so that one switch controls the entire transmitter.


The 2E26 output tube has protective bias for keying purposes. Clean keying is accomplished in the cathode of the first 6AG7. Metering is provided for the 2E26 grid and plate currents. Output coupling is by means of a link on the plate tank coil.

Enjoy the many advantages of this new exciter. Use it also in your 6 meter and 2 meter rigs. The 310B makes multi-band operation a pleasure. Write now for full details and the name of your nearest dealer.

FOR RESULTS IN AMATEUR RADIO, IT'S . . .

COLLINS RADIO COMPANY, Cedar Rapids, Iowa

11 West 42nd Street, New York 18, N. Y.

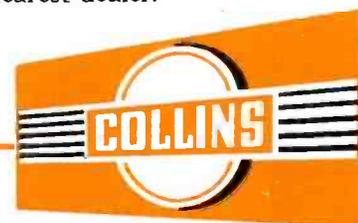

458 South Spring Street, Los Angeles 13, California

A FREE LESSON SHOWED BILL HOW HE COULD MAKE GOOD PAY IN RADIO!

BILL, YOU'RE ALWAYS FOOLING WITH RADIO -- OUR SET WON'T WORK -- WILL YOU FIX IT?

I'LL TRY, MARY. I'LL SEE WHAT I CAN DO WITH IT TONIGHT




I CAN'T FIND OUT WHAT'S WRONG -- GUESS I'LL MAKE A FOOL OF MYSELF WITH MARY



HELLO, BILL -- GOT A TOUGH ONE TO FIX? LET ME HELP YOU



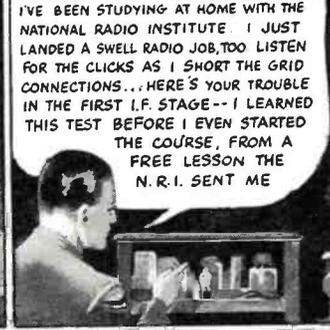YES, JOE -- I'M STUMPED -- BUT SINCE WHEN ARE YOU A RADIO EXPERT?



I'VE BEEN STUDYING AT HOME WITH THE NATIONAL RADIO INSTITUTE. I JUST LANDED A SWELL RADIO JOB, TOO. LISTEN FOR THE CLICKS AS I SHORT THE GRID CONNECTIONS... HERE'S YOUR TROUBLE IN THE FIRST I.F. STAGE -- I LEARNED THIS TEST BEFORE I EVEN STARTED THE COURSE, FROM A FREE LESSON THE N.R.I. SENT ME



SAY, I'VE SEEN THEIR ADS BUT I NEVER THOUGHT I COULD LEARN RADIO AT HOME. I'LL MAIL A COUPON FOR A FREE LESSON RIGHT AWAY



I'M CONVINCED NOW THAT THE N.R.I. COURSE IS PRACTICAL AND THOROUGH. I'LL ENROLL NOW. THEN I CAN MAKE EXTRA MONEY FIXING RADIOS IN SPARE TIME WHILE LEARNING

SOON I CAN HAVE MY OWN FULL-TIME RADIO REPAIR BUSINESS, OR BE READY FOR A GOOD JOB IN A BROADCASTING STATION, AVIATION RADIO, POLICE RADIO OR SOME OTHER BUSY RADIO FIELD



YOU CERTAINLY KNOW RADIO. SOUNDS AS GOOD AS THE DAY I BOUGHT IT!

THANKS! I WAS JUST A TINKERER A FEW MONTHS AGO, BEFORE I STARTED THE N.R.I. COURSE -- BUT N.R.I.'S '50-50 METHOD' GIVES A FELLOW THE PRACTICAL KNOWLEDGE AND EXPERIENCE TO BE A SUCCESSFUL RADIO TECHNICIAN



OH, BILL -- I'M SO GLAD I ASKED YOU TO FIX OUR RADIO! IT GOT YOU STARTED THINKING ABOUT RADIO AS A CAREER, AND NOW YOU'RE GOING AHEAD SO FAST!



YES, OUR WORRIES ARE OVER. I HAVE A GOOD JOB AND THERE'S A BRIGHT FUTURE FOR US IN RADIO

I will send you a Lesson on Radio Servicing Tips **FREE**

TO SHOW HOW PRACTICAL IT IS TO TRAIN AT HOME FOR

GOOD JOBS IN RADIO

I want to give you a copy of my Lesson, "Getting Acquainted With Receiver Servicing"—absolutely FREE! And with it, I'll send my 64-page illustrated book, "How to Be a Success in Radio," also FREE. It describes many fascinating Radio jobs, tells how N.R.I. trains you at home in spare time, how you get practical experience with **BIG KITS OF RADIO PARTS** I send. **MAIL THE COUPON!**

VETERANS

You can get this training in your own home under G. I. Bill. Mail coupon for full details.



parts I send—USE your knowledge to make EXTRA money fixing neighbors' Radios in spare time while still learning! From here it's a short step to your own full-time Radio Shop or a good Radio job!

Find Out What NRI Can Do for You Mail Coupon for Sample Lesson and my FREE 64-page book. It's packed with facts about Radio's opportunities for you. Read the details about my Course. Read letters from men I trained, telling what they are doing, earning. See how quickly, easily you can get started. No obligation! Just MAIL COUPON NOW in an envelope or paste it on a penny postal. **J. E. SMITH, President, Dept. 7ER, National Radio Institute, Pioneer Home Study Radio School, Washington 9, D. C.**

Our 33rd Year of Training Men for Success in Radio

Future for Trained Men is Bright in Radio, Television, Electronics

It's probably easier to get started in Radio now than ever before, because the Radio Repair Business is booming. Trained Radio Technicians also find profitable opportunities in Broadcasting, Radio Manufacturing, Public Address work. Think of even greater opportunities as Television, FM, and many new, war-developed Electronic devices become available. Get the facts on all these opportunities. Send for FREE books now!

Many Beginners Soon Make Extra Money in Spare Time While Learning

The day you enroll I start sending EXTRA MONEY JOB SHEETS. You LEARN Radio Principles from my easy-to-understand, illustrated lessons—PRACTICE what you learn by building, testing and experimenting with

You Build These and Other Radio Circuits with **BIG KITS OF PARTS** I SEND YOU!

By the time you've conducted 60 sets of Experiments with Radio Parts I supply, made hundreds of measurements and adjustments, you'll have valuable PRACTICAL Radio experience for a good full or part-time Radio job!



MEASURING INSTRUMENT (above) you build early in Course. Use it in practical Radio work to make EXTRA money. Vacuum tube multimeter, measures A.C., D.C., and R.F. volts, D.C. currents, resistance, receiver output.



A. M. SIGNAL-GENERATOR (left) build it yourself! Provides amplitude-modulated signals for test and experimental purposes. Gives valuable practice!

SUPERHETERODYNE CIRCUIT (right) Preselector, oscillator-mixer-first detector, i.f. stage, diode detector—a.v.c. stage, audio stage. Bring in local and distant stations on this circuit you build yourself!



GET BOTH 64 PAGE BOOK **FREE**

Mr. J. E. Smith, President, Dept. 7ER NATIONAL RADIO INSTITUTE, Washington 9, D. C.

Mail me FREE, without obligation, sample Lesson and 64-page book about how to win success in Radio and Television—Electronics. (No salesman will call. Please write plainly.)

Age.....

Name.....

Address.....

City..... Zone..... State.....

APPROVED FOR TRAINING UNDER G.I. BILL

My Radio Course Includes Training in TELEVISION • ELECTRONICS • FREQUENCY MODULATION

Chairman of the Board and Publisher
WILLIAM B. ZIFF

President
B. G. DAVIS

Secretary-Treasurer
ARTHUR T. PULLEN

Vice-Presidents

GEORGE BERNER
Advertising and Sales Director

MICHAEL H. FROELICH
Editorial Director

H. J. MORGANROTH
Production Director

H. G. STRONG
Circulation Director

Art Director
HERMAN R. BOLLIN



THE COVER by Arthur E. Haug, Staff Photographer—Complementing the handsome new Meissner '18th Century' AM-FM radio-phonograph is Carmen Garcia, 'Miss Radio News' of the 1947 Radio Parts Conference & Show.

EDITORIAL

OLIVER READ, W9ETI
Editor

WM. A. STOCKLIN
Asst. to the Editor

H. S. RENNE, Ex. WBPIS
Technical Editor

RAY FRANK, W9JU
Amateur Radio Editor

PAUL H. WENDEL
East Coast Editor

GAITHER LITRELL
West Coast Editor

FRED HAMLIN
Washington Editor

P. B. HOEFER
Assistant Editor

ARTHUR E. HAUG
WALTER STEINHARD
Staff Photographers

R. S. KUPJACK
Staff Artist

ADVERTISING

Advertising Manager
L. L. OSTEN

Midwestern Advertising Manager
JOHN A. RONAN, JR.

BRANCH OFFICES

NEW YORK (1)
Empire State Bldg., W17-0400

Manager, Eastern Division
CHARLES R. TIGHE

LOS ANGELES (14)
815 S. Hill St., T Ucker 9213

Manager, Western Division
WILLIAM L. PINNEY

WASHINGTON (4)
International Bldg., EXecutive 2502

TORONTO
21 King Street, East

ASSOCIATED COMPANIES
Ziff-Davis, Ltd., Gramplan Bldg.
Western Gate, London W. 6, England
Ziff-Davis-Patel, Ltd.
190 Hornby Road, Bombay, India



First in radio-electronics

Average Paid Circulation over 135,000

Reg. U. S. Pat. Off.

MAY, 1947

FOR THE SERVICEMAN-DEALER

A Simple FM Converter.....	Stanley N. Finley	50
FM Tuner Conversion with LC Circuits.....	Norman L. Chalfin	51
Micrometer Tuning Signal Generator.....	Samuel Miller	57
Where Will You Find Them?.....		60
A Sales Control System.....	Fred Merish	64
Practical Radio Course.....	Alfred A. Ghirardi	66
Sensitive Probe Uses Crystal Diode.....	Rufus P. Turner, W1AY	68
RN Circuit Page.....		82
New Receivers for Summer Market.....		146

FOR THE AMATEUR

Simple Two-Tube Ham Super.....	Ray Frank, W9JU	48
Ham Ticket in 30 Days.....	John T. Frye, W9EGV	56
Narrow Band Phase Modulation Exciter.....	Sol Sterman, W2JWX	69
Deluxe Amateur Transmitter.....	James N. Whitaker, W2BFB	71

OF GENERAL INTEREST

Mobile Radio-Telephone Service Links Nation.....	Frank E. Butler	45
1947 Radio Parts and Electronic Equipment Conference and Show.....		54
The Recording and Reproduction of Sound (Part 3).....	Oliver Read	61
A Novel Input Circuit.....	Zygmunt Hof	90

DEPARTMENTS

For the Record.....	The Editor	8	What's New in Radio.....	86
Spot Radio News.....	Fred Hamlin	18	Letters from Our Readers.....	138
Within the Industry.....		32	Biz Quiz.....	152
Short-Wave.....	K. R. Boord	70	Manufacturer's Literature.....	166
For the Experimenter.....		172		



COPYRIGHT 1947
ZIFF-DAVIS PUBLISHING COMPANY
185 North Wabash Ave., Chicago 1, Ill.
VOLUME 37 • NUMBER 5



Member
Audit Bureau of
Circulations

RADIO NEWS is published monthly by the Ziff-Davis Publishing Company, 185 N. Wabash Ave., Chicago 1, Ill. Subscription Rates: in U.S. and Canada \$4.00 (12 issues), single copies 35 cents; in Mexico, South and Central America, and U.S. Possessions, \$4.00 (12 issues); in British Empire, \$5.00 (12 issues)—all other foreign countries \$5.00 (12 issues). Subscribers should allow at least 2 weeks for change of address. All communications about subscriptions should be addressed to: Director of Circulation, 185 N. Wabash Ave., Chicago 1, Ill. Entered as second class matter March 9, 1938, at the Post Office, Chicago, Illinois, under the Act of March 3, 1879. Entered as second class matter at the Post Office Dept., Ottawa, Canada. Contributors should retain a copy of contributions and include return postage. Contributions will be handled with reasonable care but this magazine assumes no responsibility for their safety. Accepted material is subject to whatever revisions and by-line changes that are necessary. Payment made at our current rates, covers all authors', contributors', or contestants' rights, title, and interest in and to accepted material, including photos and drawings.

RADIO NEWS

Going places
(AGAIN)


hallicrafters



Hallicrafters famous radio equipment, sold and distributed around the world before the war and used with superb effectiveness in every theater during the war is once again on the move. Watch the latest details of the Gatti Hallicrafters mobile radio equipped expedition to the Mountains of the Moon in deepest Africa—a new and exciting test for the ingenuity of hams and the performance of Hallicrafters equipment.

3

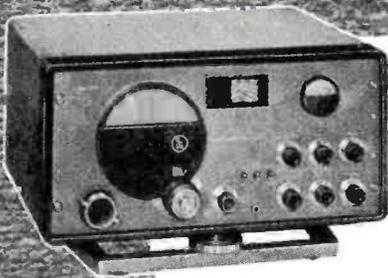
GREAT RECEIVERS designed and priced for hams who are going places, too



Model SX-42 Described by hams who have operated it as "the first real postwar receiver." One of the finest CW receivers yet developed. Greatest continuous frequency coverage of any communications receiver—from 540 kc to 110 Mc, in six bands. FM-AM-CW. 15 tubes. Matching speakers available. **\$275⁰⁰**




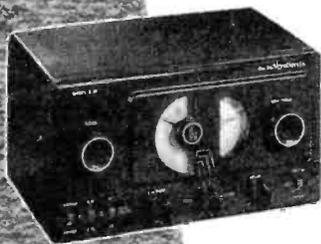Model S-40A Function, beauty, unusual radio performance and reasonable price are all combined in this fine receiver. Overall frequency range from 540 kc to 43 Mc, in four bands. Nine tubes. Built-in dynamic speaker. Many circuit refinements never before available in medium price class. **\$89⁵⁰**



Model S-38 Overall frequency range from 540 kc to 32 Mc, in four bands. Self contained speaker. Compact and rugged, high performance at a low price. Makes an ideal standby receiver for hams. CW pitch control is adjustable from front panel. Automatic noise limiter. **\$47⁵⁰**

Prices slightly higher in zone 2

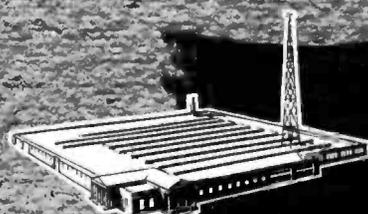

BURGERS OF *Skayfone* AVIATION RADIO TELEPHONE

hallicrafters RADIO

THE HALLICTRAFTERS CO., MANUFACTURERS OF RADIO AND ELECTRONIC EQUIPMENT, CHICAGO 16, U. S. A.

Sole Hallicrafters Representatives in Canada: Rogers Majestic Limited, Toronto-Montreal

FADA



The Radio of **TOMORROW...TODAY!**

**THE LAST WORD
IN
3-WAY PORTABLES**



MODEL P82

Tri-power portable Superheterodyne with Hi-Gain tuned RF stage in rich two-tone simulated leather covered wood cabinet. 5 tubes plus rectifier tube.

TOPS IN TABLE MODELS...

YOU CAN ALWAYS DEPEND ON

FADA Radio

Famous Since Broadcasting Began!



MODEL 1000 — 6 TUBES

AC-DC Superheterodyne in beautiful gem-like "Fada-lucent" cabinets. Five Tubes plus Rectifier Tube.



FADA 5-tubes—plus-rectifier-tube models are equipped with the new FADA "Sensitive-Tone" ...assuring greater sensitivity and clearer reception.



MODEL 605 — 5 TUBES

AC-DC Superheterodyne in modern walnut plastic cabinet. Four tubes plus rectifier tube.

FADA RADIO AND ELECTRIC COMPANY, INC., LONG ISLAND CITY, N. Y.




NOW! An Amazing Opportunity to LEARN RADIO AT HOME

I SEND YOU 8 BIG KITS OF RADIO PARTS

Including a COMPLETE 6 TUBE SUPER-HETERODYNE RECEIVER

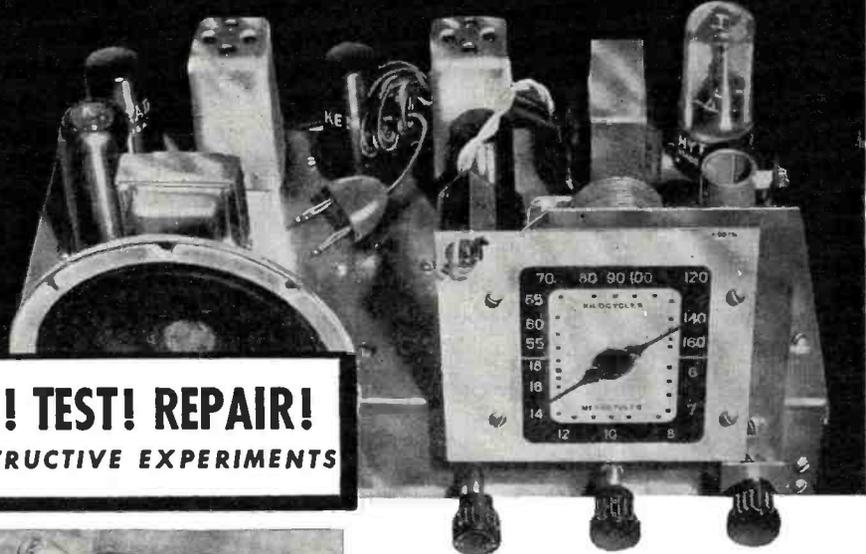I TRAIN YOU RIGHT by PUTTING YOU TO WORK with REAL PROFESSIONAL EQUIPMENT!



LEARN HOW TO BUILD CIRCUITS! TEST! REPAIR!
YOU DO OVER 175 INSTRUCTIVE EXPERIMENTS




HERE'S THE EASIEST, MOST PRACTICAL WAY OF ALL TO PREPARE FOR GOOD PAY in RADIO ELECTRONICS and TELEVISION!


I train your mind by putting you to work with your hands on a big 6-Tube Superheterodyne Receiver. And, believe me, when you get busy with real Radio Parts — 8 big Kits of them — you really LEARN Radio and learn it RIGHT! You get the practical stuff you need to be useful in Radio, and that's what it takes to make money. You don't have to worry about what to do with these 8 Kits of Parts. Step by step, I show you how to build circuits, test, experiment, trouble-shoot. And you don't need any previous experience. The Sprayberry Course starts right at the beginning of Radio! You can't get lost! Simplified lessons, coupled with real "Shop" practice, makes every subject plain and easy to understand and remember. Soon after you begin Sprayberry Training, I'll send you my sensational BUSINESS BUILDERS.

A BUSINESS OF YOUR OWN . . . OR A GOOD RADIO JOB
You'll find out how to get and do neighborhood Radio repair jobs for nice profits and rich experience while learning. This sort of work can easily pave the way for a Radio Service business of your own. But with Sprayberry Training, you're not limited. You can swing into any one of the swiftly expanding branches of Radio-Electronics INCLUDING Radio, Television, FM, Radar, Industrial Electronics. Be wise! Decide now to become a fully qualified RADIO - ELECTRONICIAN. Get full details about my Training at once! Mail coupon below for my 2 big FREE Books.

YOU BUILD THIS USEFUL TEST EQUIPMENT!

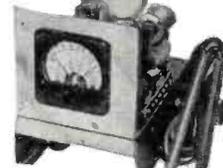

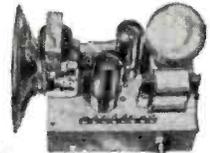I give you a fine, moving-coil type Meter Instrument on Jewel Bearings — with parts for a complete Analyzer Circuit Continuity Tester. You learn how to check and correct Receiver defects with professional accuracy and speed.



Soldering, wiring, connecting Radio parts . . . building circuits — you can't beat this method of learning. When you construct this Rectifier and Filter, Resistor and Condenser Tester, etc., you get a really practical slant on Radio.

You'll get valuable experience and practice building this Signal Generator and multi-purpose Tester. Makes a breeze out of fixing Radios and you don't have to spend money on outside, ready-made equipment.



GET THESE VALUABLE FREE BOOKS

"How to Read Radio Diagrams and Symbols"

Here's a valuable and wonderfully complete new book which explains in simple English how to read and understand any Radio Set Diagram. Includes translation of all Radio symbols. Send for this volume at once. It's free! Along with it, I will send you another Big Free book describing in detail my Radio-Electronic Training.

RUSH COUPON!

SPRAYBERRY ACADEMY OF RADIO

F. L. Sprayberry, President, Room 2557, Pueblo, Colorado

Please rush my FREE copies of "How to MAKE MONEY in RADIO, ELECTRONICS and TELEVISION," and "HOW to READ RADIO DIAGRAMS and SYMBOLS."

Name Age

Address

City State


(Mail in envelope or paste on penny postcard)



**ASK THE MAN
WHO KNOWS THEM!**

Spintite wrench sets are the next best thing to an extra pair of hands. When you are turning out radios on the assembly line as I am, you sure appreciate tools that help speed production.

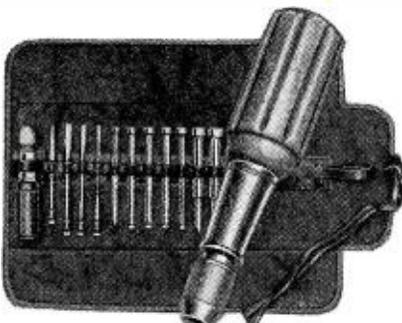Spintite is the wrench that's built and works like a screwdriver. Available to fit square, hex or knurled nuts, it can be had with either fixed or chuck-type handle. Ranging in size from 3/16" to 5/8", there are Spintites to meet every requirement of radio assembly and repair. If you ask me, Spintites are the answer.



No. T-51 chuck-type Spintite with seven Spintites, three Screw-drivers and Reamawl, in leatherette roll.



STEVENS • WALDEN
INCORPORATED
Worcester • Massachusetts

For the **RECORD.**

BY THE EDITOR

IT HAS been a long time since we have discussed the matter of conduct of amateur radio operators. We feel that we are not amiss in sounding off a bit on this subject especially since FCC Chairman, Charles R. Denny, Jr. struck an ominous note during his address at the IRE banquet recently in New York.

Denny said that the FCC has been undertaking widespread revisions in the Commission's standards and rules for all radio services throughout the United States. Mr. Denny further emphasized that, "It is our objective that one by one the technical requirements and operating requirements for each of the different individual radio services shall be completely overhauled and brought up to date. In making these revisions we are seeking to do a great deal more than simply codify the existing rules."

Mr. Denny then went on with what might well be a somber warning to the amateur by pointing out that the frequency spectrum between 4 and 25 megacycles is very much in the revision spotlight. These frequencies, said Mr. Denny, are those including the international channels and best suited for world-wide communications. "We are carefully reviewing each rule and each standard for the purpose of insuring that we retain only such requirements as are really essential for the proper functioning of the service in question."

That brings us to the topic at hand; the "conduct" of many amateurs who are, in many cases, abusing their privileges to operate. Interference is at an all time high and the QRM situation becomes worse with each passing day. Many 500 watt transmitters can be heard on the air emitting strong DX signals when many of them are merely talking "cross town." Such operators are doing little, if anything, to enhance the art of amateur radio and when the chips are down they will only have themselves to blame if they come out on the short end of the deal.

So important is the matter of frequency allocations to international communications that a special World Telecommunications Conference is to be held at Atlantic City beginning this month. Among the many subjects likely to come up for review and evaluation are the present amateur allocations. We know, for example, that there will be much pressure from some of the foreign representatives to have

certain amateur frequencies re-assigned to other services. In most cases the countries that will favor further restriction of amateur frequencies are those that allow little or no personal freedom. Many of them do not believe in freedom of the press and it is the wish of certain governments that no information be printed or transmitted outside of their own borders for the world to see or hear.

In view of the pressure that will be brought to bear, it becomes vitally essential that every amateur take careful stock of his own operating practices and to make certain that he is not open to criticism. One of the worst and most common of all violations of good operating ethics is the interference presently affecting established traffic nets. At times the interference is of such proportions that the nets are forced to cease operations and close down.

There has been a lot of general griping about this and that on the air by amateurs. In many cases these gripes have been justified but in others they have not. But regardless of whether these complaints have been in or out of order, the fact remains that those responsible for the conduct on the ether are not just sitting by and not taking notice. No organization is perfect in itself but the principles it represents, if sound, must be maintained by those whose very existence on the air depends upon loyalty and support of its tenets.

It is the personal responsibility of each amateur to look jealously upon the safety of his hobby. If amateurs are to preserve their rights it becomes their responsibility to avoid needless interference and to be a bit "prestige conscious." It takes but little time to listen in on the operating frequency before transmissions and to size up the general situation before proceeding. This will avoid much unnecessary QRM.


While we don't feel that the future of amateur radio is in present danger, we do take cognizance of the fact that there are many interests seeking any type of ammunition which would help destroy our hobby. We feel that the matter of *conduct* may have much to do in furthering our position as a necessary and vital part of communications particularly when disaster strikes or when, if ever, we again need a large backlog of skilled operators.

.....O. R.

Order Your
Communications Receiver
 from **ALLIED!**
IMMEDIATE DELIVERY
 on most models



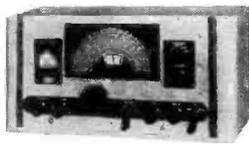NATIONAL HRO
 NET, less speaker, \$274.35



RME-45
 NET, with speaker, \$198.70

IMMEDIATE DELIVERY



RME-84
 NET, with speaker, \$98.70



NATIONAL NC-46
 NET, with speaker, \$107.40

Other Communications Equipment

Hallicrafters SX-42.....	\$275.00
Hallicrafters S-38.....	47.50
Hallicrafters S-40A.....	89.50
National NC-173.....	189.50
National NC-2-40D.....	225.00
Hammerlund SPC-400X.....	342.00
Hammerlund HQ-129X.....	173.25
RME VHF-152 Converter.....	86.60
RME DB-20 Preselector.....	68.20
Collins 75A-1 Receiver.....	375.00
Collins 32V-1 Transmitter.....	475.00
Collins 30K Transmitter.....	1250.00

Net F. O. B. Chicago. Prices subject to possible change.

Time Payments

Trade-Ins Accepted

ALLIED RADIO
Everything in Radio and Electronics

for Everything in Radio

Get **ALLIED'S NEW**
RADIO CATALOG

FREE
 Send for it Now!



VALUE-PACKED
BUYING GUIDE for Servicemen, Amateurs,
 Sound Men, Builders, Experimenters

Send today for this newest value-packed ALLIED Catalog—Radio's most complete Buying Guide from Radio's leading, dependable, supply house! It's crammed with thousands of radio and electronic supplies of nationally-known preferred brands—all at real money-saving prices. You'll find everything you need in every field of radio—replacement parts, tubes, test equipment, tools, home radios, Amateur receivers and gear, radio builders' and experimenters' kits, Public Address and sound equipment.

HUGE STOCKS—MORE THAN 10,000 ITEMS

Thousands of seasoned radio men depend upon ALLIED. Our tremendous stocks include over 10,000 individual items covering everything in Radio and Electronics—concentrated to serve you best from a single centralized source. We give your orders, large or small, our expert attention and speedy shipment to assure complete satisfaction. Whatever your needs, you'll get them satisfied better, faster, more economically at ALLIED—The World's Largest Radio Supply House.

FREE! Radio's Leading Buying Guide . . .

ALLIED RADIO CORP.
 833 W. Jackson Blvd., Dept. 1-EE-7
 Chicago 7, Illinois

- Send FREE 1947 ALLIED CATALOG
- Enter order for.....
- Enclosed \$..... Full Payment
 Part Payment (Balance C.O.D.)
- Send full information on Communications Receivers and Time Payment Plan, without obligation.

Name.....
 Address.....
 City.....Zone.....State.....





**WINNING
PERFORMANCE
NATURALLY
with
National
Equipment**

High scorer for his section in the recent sweepstakes of the American Radio Relay League was Frank Glenon of Canton, Mass., W1KQN, with an unofficial 26,624 score.

Basic units in W1KQN's enviable layout are the National NC-2-40D receiver and the National NTX-30 Exciter. In addition, many National components were used in his transmitter. Around them has been built the station with which W1KQN rang up his record.

Working DX that wasn't hearing enough W stations to know there was a sweepstakes contest, W1KQN operated for only 32 of the possible 40 hours and still racked up the top score.

Year after year, in thousands of ham shacks around the world, National equipment keeps delivering the kind of performance that wins.

National
EST. 1914
MALDEN, MASS.


NATIONAL
COMPANY, INCORPORATED

MAKERS OF LIFETIME RADIO PRODUCTS

\$400,000 WORTH OF RADIO SERVICE DATA

A Continuous Service for less than 9¢ a day in

PHOTOFACT* FOLDERS

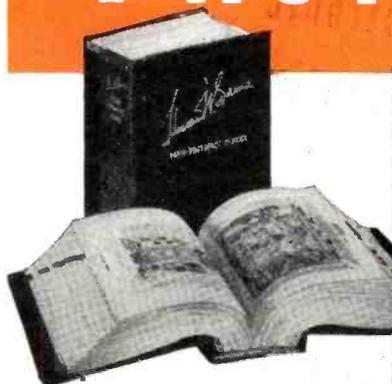

VOLUME 1, containing first ten sets of PHOTOFACT FOLDERS in deluxe binder, \$18.39. Individual sets Nos. 1 to 10, \$1.50 each. De Luxe Binder alone, \$3.39.

COMPLETE

Everything you need in one handy, unified form—large schematics, pictorials keyed to parts lists and alignment data, complete listings of parts values and replacements, alignment, stage gain, circuit voltage and resistance analysis, *coil resistances*, dial cord stringing, disassembly instructions, record changer analysis and repair.

ACCURATE



All sets are taken apart and analyzed by experts in the Sams laboratories. Every part is measured, tested and triple-checked for accuracy. All data is original. This means the data you get is *right*.

CORRECT

PHOTOFACT FOLDERS are issued twice monthly as the new receivers come off production lines. You don't have to wait for information. As receiver changes are made, you get correction and addition sheets for your files. Your data is always up to the minute.

EASY TO USE

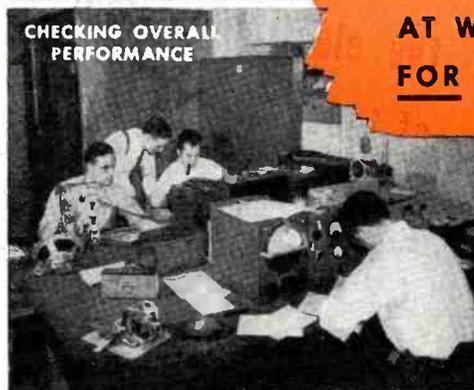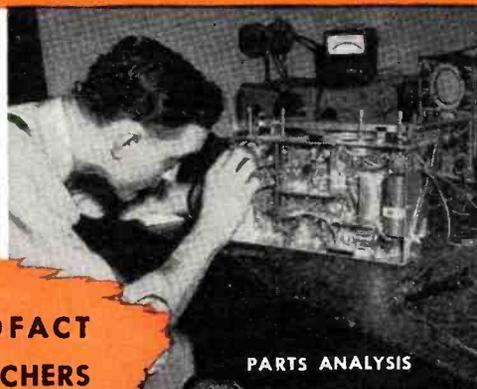All diagrams and pictures are coded to numbered parts lists. Everything is positively identified for fast work. All folders are set up in uniform, easy-to-follow style: big type, big illustrations—no hunting, guessing or eye strain—no more loss of time and temper.



**PHOTOFACT
RESEARCHERS
AT WORK
FOR YOU**

\$403,531.05†—that's what it actually cost us to create, print and distribute Volume 1 of Sams PHOTOFACT FOLDERS. Every penny of that money has been spent to bring the industry the most accurate, complete, up-to-the-minute data ever produced for radio servicemen. And this continuing service, designed to help you make up to *twice as many repairs daily*, actually costs you less than 9 cents a day.

PHOTOFACT FOLDERS could not be produced without the support of America's leading replacement parts manufacturers—without the support, too, of thousands of enthusiastic PHOTOFACT subscribers. With their cooperation, we will continue to place in your hands ALL the information you need to do a better job—facts, figures, photographs, full-page schematics—*information compiled from actual first-hand analysis of all*

* Trade Mark Reg.

new instruments. PHOTOFACT FOLDERS cover *all* radios, phonographs, record changers, recorders, communications systems and power amplifiers—and are *timed to reach you as these instruments are released*. The cost is only \$1.50 per set of 30 to 50 folders and includes membership in the Howard W. Sams Institute.

Set No. 17 will be ready for mailing April 10th. Set No. 18 on April 25th. Sets Nos. 11 to 16 inclusive, also priced at \$1.50 each, are available for immediate order.

Start using PHOTOFACTS to make more profits. Remember, PHOTOFACT FOLDERS actually cost you nothing: *they pay for themselves over and over!* See your replacement parts distributor—or write us direct. In Canada, address A. C. Simmonds & Sons, 301 King Street East, Toronto, Ontario. Canadian price, \$1.75.


†C.P.A. Statement Available

HOWARD W. **SAMS** & CO., INC.

2924 EAST WASHINGTON STREET, INDIANAPOLIS 6, INDIANA

PHOTOFACT SERVICE

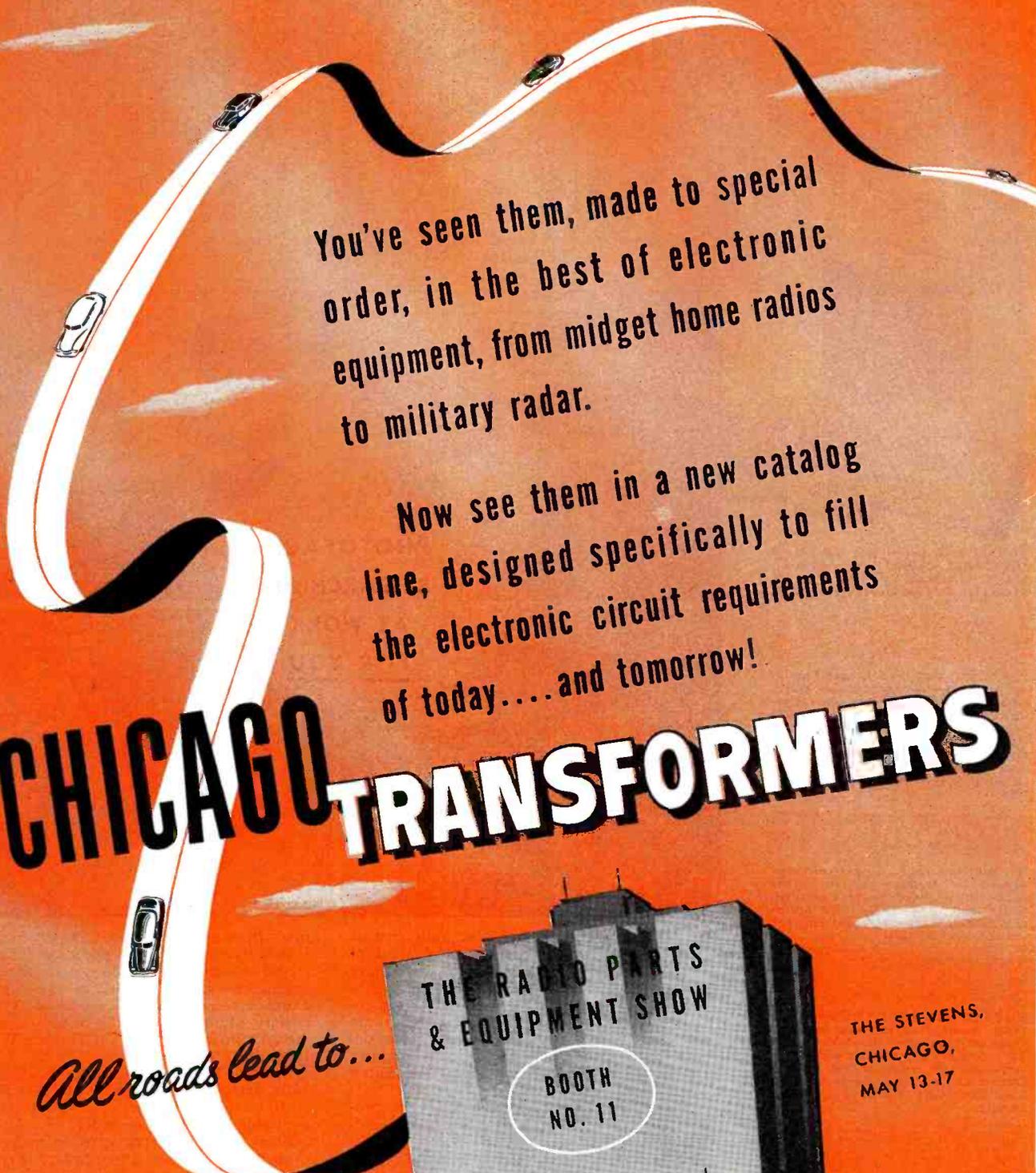"The service that pays for itself over and over again"



You've seen them, made to special order, in the best of electronic equipment, from midget home radios to military radar.

Now see them in a new catalog line, designed specifically to fill the electronic circuit requirements of today....and tomorrow!

CHICAGO TRANSFORMERS

All roads lead to...

THE RADIO PARTS
& EQUIPMENT SHOW

BOOTH
NO. 11

You are cordially invited
to visit us there

THE STEVENS,
CHICAGO,
MAY 13-17



CHICAGO TRANSFORMER

DIVISION OF ESSEX WIRE CORPORATION

3501 WEST ADDISON STREET • CHICAGO 18, ILLINOIS

Centralab announces
a NEW line of
ceramic by-pass and coupling
capacitors for distributors

*(BC "Hi-Kaps" made with
Centralab's original Ceramic-X)*


Centralab now offers its distributors a completely new sales program for ceramic capacitors, involving new packaging and new pricing. That means new sales opportunities . . . an entirely new market picture for

Centralab's established quality line of ceramic capacitors. For complete information, visit Centralab's exhibit, Booth 68, Stevens Hotel, Chicago, Illinois, May 13 to 16.

LOOK TO CENTRALAB IN 1947!
First in component research that means lower costs for the electronic industry. Before you place your order, get in touch with Centralab!



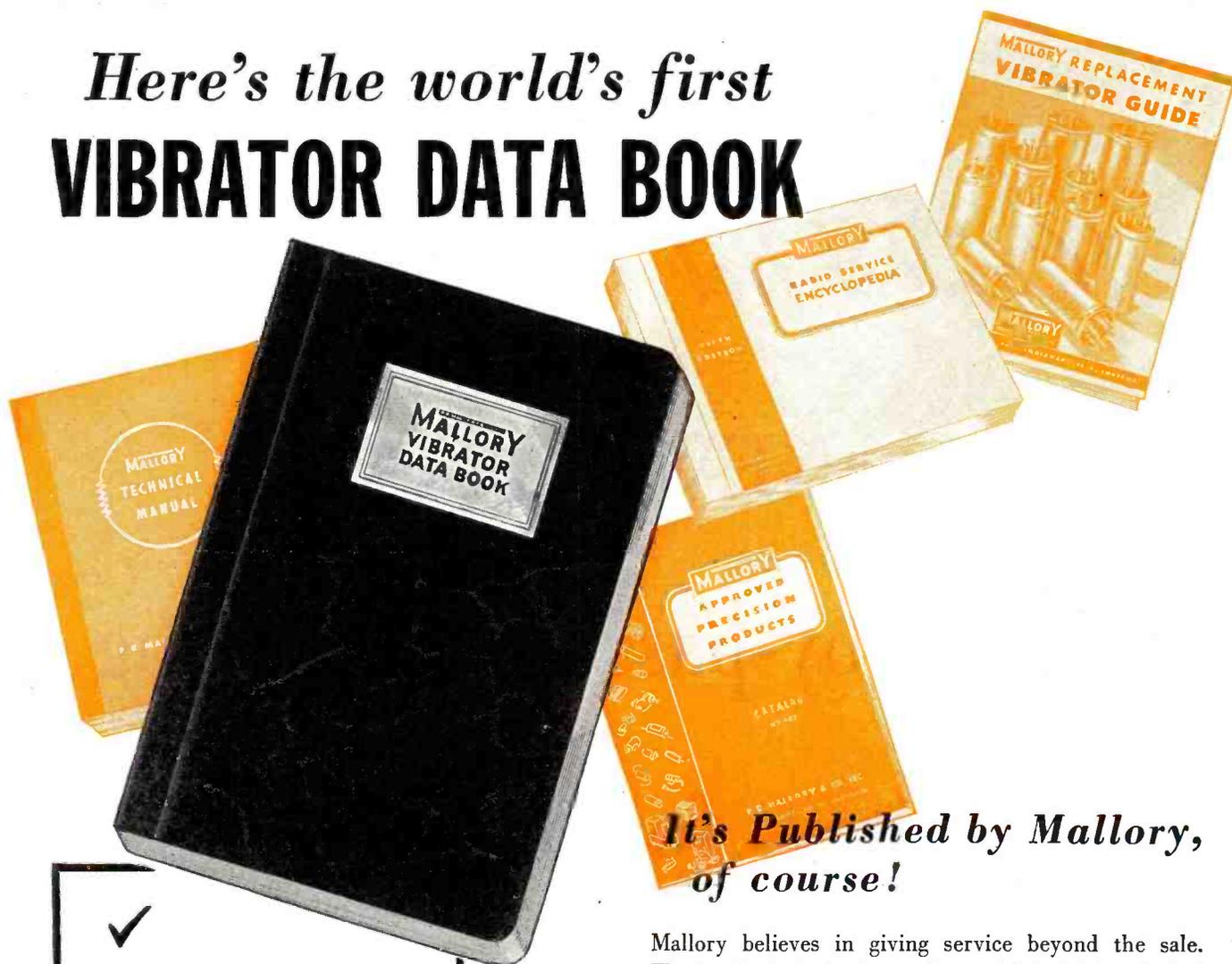Here's the world's first VIBRATOR DATA BOOK



*It's Published by Mallory,
of course!*



CHECK THIS LIST OF CONTENTS

Basic Vibrator Structures
Mallory Standard Vibrator Types
Selection of Correct Vibrator Power Transformer Characteristics
Typical Vibrator Characteristic Data Sheets
Power Transformer Design
General Procedure in Designing Transformers
Examples of Transformer Design
Design Considerations for Other Applications
High Frequency Vibrator Power Supply
Timing Capacitor Considerations
Design Practices and Methods of Interference Elimination
Vibrator Power Supply Circuits
Vibrator Inspection Procedures

Mallory believes in giving service beyond the sale. That's why it backs its products with helpful technical literature—outstanding books like the Mallory Technical Manual, the Radio Service Encyclopedia and others.

Now comes another important Mallory publication: the first of its kind in the world. It's the Vibrator Data Book, a comprehensive manual that tells you everything about vibrator power supply systems that Mallory has learned in sixteen years of building better vibrators and vibrator power supplies. Does your shop service auto radios? The Vibrator Data Book is an absolute *must* for you. Do you handle other types of equipment powered from a DC source? This volume very definitely belongs on your work bench.

The price? Only \$1.00. The supply? Limited at present. Better order *now* from your Mallory Distributor before the first edition runs out.

*See Your Mallory Distributor for a free copy of the
1947 Replacement Vibrator Guide*

P. R. MALLORY & CO. Inc.
MALLORY

VIBRATORS . . . VIBRAPACKS* . . . CAPACITORS . . .
VOLUME CONTROLS . . . SWITCHES . . . RESISTORS
. . . FILTERS . . . RECTIFIERS . . . POWER SUPPLIES.

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

YOUR CABINETS and CASES.... LOOK AT THEM AGAIN, PLEASE

Are you satisfied with the external appearance of your equipment? Perhaps you're handicapped by stock cabinets that look like those used twenty years ago.

Utilizing our long experience in manufacturing cabinets for mass-production users, we are now making a completely new line for smaller consumers. Some types are already in stock for prompt shipment; others will be ready soon.

Because all the dies are brand new our stock cabinets have up-to-the-minute appearance. They are Clean-Cut, Tasteful and Modern. They are well-made and sturdy. The color schemes are new and attractive. All are made of aluminum, the modern metal. They have many mechanical features that will interest you. May we send our descriptive literature?

CRONAME
INCORPORATED

Formerly Crowe Name Plate & Mfg. Co.

3701 RAVENSWOOD AVE.
CHICAGO 13, ILLINOIS

First Public Showing
Stevens Hotel, Chicago
Radio Parts Show, Booth 84
May 13, 14, 15, 16, 1947

CRONAME, Inc.

3701 Ravenswood Ave., Chicago 13, Ill.

You may send me literature on your stock cabinets.

Name _____
Firm _____
Position _____
Address _____
City _____ Zone _____ State _____

V Please Check V

- | | |
|---|--|
| <input type="checkbox"/> Amateur | <input type="checkbox"/> Experimenter |
| <input type="checkbox"/> Custom Builder | <input type="checkbox"/> Manufacturer |
| <input type="checkbox"/> Designer | <input type="checkbox"/> Serviceman |
| <input type="checkbox"/> Engineer | <input type="checkbox"/> Wholesale Distributor |

WEBSTER ELECTRIC meet demands for an All-around Good Cartridge

Check Your Requirements

- ✓ Weight
- ✓ Response characteristics
- ✓ Voltage output
- ✓ Dimensions and mountings
- ✓ Type of terminals
- ✓ Type of ground
- ✓ Tracking pressures




Designed to Meet Varied Requirements Depending Upon Tone Arm and Equipment

● The wide selection of Webster Electric cartridges offers a cartridge with correct characteristics for replacement use. Correct weight, response, voltage output and other requirements so necessary for top performance.

Webster Electric cartridges are GOOD cartridges of balanced construction that produce maximum output at designated tracking pressures with minimum distortion and minimum mechanical reproduction. All models offer exceptionally uniform response over the desired range of frequencies, with low distortion and minimum needle noise.

Complete tone arm assemblies of improved design, in a wide selection of models are also available for the replacement market.

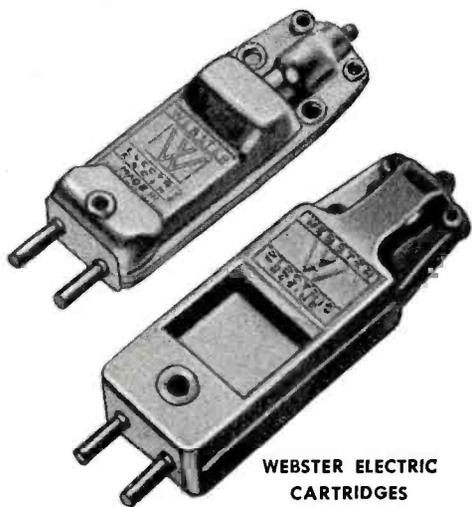All Webster Electric products are carefully designed and manufactured under highest quality standards. They have been on the market for years, and during this time have proved their value for long life and top performance.



WEBSTER ELECTRIC
CARTRIDGES

(Licensed under patents of the Brush Development Company)

WEBSTER  **ELECTRIC**
RACINE WISCONSIN

Established 1909

Export Dept. 13 E. 40th Street, New York (16), N. Y. Cable Address "ARLAB" New York City

"Where Quality is a Responsibility and Fair Dealing an Obligation"

The Smart
NEW
3-way Portable



MODEL A-510

AIR KING *Royal Troubador*

THE 3-WAY PORTABLE WITH TRIPLE SALES APPEAL

You can wrap the whole sales story of the Air King "Royal Troubador" in three words — Price, Performance and Eye-Appeal. It is a 3-way portable designed for beauty and tone with sales potential to match.

Your customers will be proud to own the new Air King "Royal Troubador"—proud as you will be to show it. Highly sensitive . . . critically selective . . . playable anywhere. The "Royal Troubador" can easily be the fastest moving portable you've so far seen.

The Royalty of Radio Since 1920

AIR KING
RADIO

Division of HYTRON RADIO & ELECTRONICS CORPORATION

SELLING FEATURES

- Latest design, high-performance miniature tubes (4) plus metallic selenium rectifier
- Superheterodyne with automatic volume control
- Special Alnico V PM Speaker
- Precision die-cut antenna for maximum signal
- 3-way power; AC-DC or battery
- Provision for external aerial
- All wood case bound in striking simulated leather

\$37⁹⁵

Retail Price (Tax Incl.) Less Batteries

★ WE HAVE A LIMITED NUMBER OF DISTRIBUTOR AND DEALER TERRITORIES OPEN ★

Write or wire: Air King Products Co., 1523-29 63rd St., Brooklyn, N. Y. Export Address: Air King International, 75 West Street, New York 6, N.Y.

The Royal Family of Radio



"Twenty-Six Years of Specialized Electronic Skill Behind Every Air King Radio"

performance
long life
economy

AMPEREX Tubes

TYPE HF 300: Introduced by Amperex and widely adopted for broadcasting equipment as well as the generation of industrial power. It will give more than 500 watts at frequencies up to 30 megacycles. Very versatile.



TYPE HF 201: Very useful for general purposes when a plate power output in the neighborhood of 350 watts per tube is needed. Originally developed by Amperex and now widely accepted. Standard in diathermy equipment.

TYPE HF 150: A smaller edition of the HF 201 above with the truly sturdy construction and exclusive design features. It will give as high as 200 watts in Class C service. A very popular member of the Amperex family.



TYPE 833 A: An exceedingly compact glass triode widely adopted for many functions in both the communications and industrial services. As a generator of frequencies up to 30 mc it will give 1000 watts output without forced air cooling and as much as 1600 watts with a small blower.

And all other types you need. Write for technical rating and data sheets.



AMPEREX

ELECTRONIC CORPORATION
25 Washington St., Bklyn 1, N. Y.
Cables "ARLAB" • in Canada and
Newfoundland: Rogers Majestic Ltd.,
622 Fleet St. West, Toronto 28, Can.

Spot Radio News

★ Presenting latest information on the Radio Industry.

By FRED HAMLIN

Washington Editor, RADIO NEWS

OUR EARS were slightly red on hearing that the Federal Communications Commission denied Columbia Broadcasting System its color television application—and for just the reasons which, last month, we predicted would make the decision exactly the opposite. We said that FCC would favor CBS because FCC policy favors competition and new developments. FCC denied CBS on almost identically those grounds. CBS wanted to colorcast in the 480 to 920 megacycle band. FCC denied this request on the grounds that if CBS broadcast in that band, there would not be much room for competition. As for new developments, the Commission said that "there may be other systems of transmitting color which offer the possibility of cheaper receivers and narrower bandwidths that have not been fully explored." In other words, they are open-minded toward further developments, even from CBS, which, the Commission rules, hadn't made enough field tests "for the Commission to be able to proceed with confidence that the system will work adequately in practice."

ONE FCC OBJECTION was that to achieve brightness and absence of flicker, CBS needed channels so wide that only 27 could be accommodated on the present band. FCC emphasized that this would cut competition down to a point that might become monopolistic, while "it was the Commission's hope . . . that in this band it would be possible to provide for a truly nationwide competitive television system." This led the Commission to re-emphasize the need for further development: "Every effort," it ruled, "must be made to narrow the bandwidth required for color television. It is quite possible as a result of wartime discoveries," the Commission added, "improvements can be made" all along the color television line. "Furthermore, wartime developments may show that there is an entirely different method from either the sequential or simultaneous system which is superior to both. Before standardizing television in the upper band, we should be sure that all of the wartime electronic developments have been explored to determine whether they can be applied to the advantage of television." In sum, FCC favors

more and more development—more and more competition. But the CBS proposal doesn't seem to offer enough of either. . . . We like to think that in predicting a CBS victory, we were betting on the right jockey, but picked the wrong horse.

GOOD RADIO JOBS are still available for qualified candidates. Latest indication is more than sixty civilian openings recently listed by the U. S. Navy, many of which featured radio experience. Typical are two, one for an electronics engineer, the second for a graduate radio engineer. To quote the Navy on qualifications for the electronics job, the candidate must be a "project engineer for programs such as radiological instruments and detection devices for harbor defenses, industrial electronic systems, radio control devices, and similar control applications." The radio engineer must, "under general supervision, serve as project engineer on specialized radar equipment." If you are interested in either of these, or other Navy openings, the trick is to go to the nearest post office, get a Civil Service Form 57, fill it out, and mail it to the U. S. Navy, Department Civilian Personnel Branch, Code 612, Main Navy Building, Washington, D. C. You will be notified if the Navy is interested enough to interview you and chances are—assuming you're qualified—that they will be. They report difficulty in filling the radio jobs, of which there are more than a dozen open as this goes to press. . . . And *puhleeze* don't write us—we haven't the vaguest idea of competing with the U. S. N. in the project business.

WE'VE JUST CHECKED around the circuit on the FM stations and how they're doing. The answer is—okay. Biggest question mark of the spring concerned advertising, with two problems at the top of the list. There was the problem of getting advertisers; beyond that, there was the problem of getting the advertisers to live up to FM's promise of high-level advertising copy. . . . If spot checks with FM stations already active are any indication, both problems are being worked out successfully. FM time is selling nicely, although at rates roughly one-third lower than comparable AM stations. They are bargain rates—one

RADIO ELECTRONICS

DeFOREST'S TRAINING, INC. CHICAGO, ILLINOIS

IT IS THE **WELL TRAINED** MAN WHO **WINS**

In the prize ring, as in the bigger contest of making a livelihood for ourselves and families, *training* makes the champion... brings the real **PAY OFF!**

You can prepare for bigger winnings, too, by training for one of America's great championship fields—**RADIO and ELECTRONICS**—the billion dollar opportunity-packed industry that is *in the match*.

Mail coupon below right now, for late facts about the exciting events in F.M. Radio, Broadcast Radio, Motion Picture Sound, Electronics, Sound Recording, the future developments in Television, Radar and other branches. See, too, how you may score a *knockout* against low pay, uninteresting work, an uneventful future.

You don't have to know a thing about Radio and Electronics at present. Over a period of 15 years, DeFOREST'S TRAINING, INC. has perfected a championship method of home training that **GETS RESULTS QUICKLY!**

We provide you, for use in your own home, with a **BIG FOUR** training method that includes:

(1) commercial type Radio-Electronic parts and assemblies for valuable **"LEARN-BY-DOING"** experience, (2) a 16 mm Motion Picture Projector and 12 reels of action-packed **"LEARN-BY-SEEING"** instructive movies to speed your understanding of important principles, (3) many easy-to-read loose-leaf lessons illustrated with handy fold-out diagrams, and (4) an effective **EMPLOYMENT SERVICE** to help you get started toward a good Radio Job when trained—or to assist you in starting your own Radio Business where you can be your own boss.


This championship method has started many men toward Real Pay, Fascinating Work, and a Grand Future—see **HOW** it may do the same for you. Mail coupon today for big free book that shows you the way.

**DeForest's Training, Inc. Wins
Coveted "Certificate of Merit".**

DeForest's Training, Inc. is the first school of its kind in the country to win the "Certificate of Merit" of the New York Museum of Science and Industry. This award is granted "in recognition of outstanding achievements in the pioneering, development and use of home study and laboratory courses to train men for the fields of Radio and Electronics."

YOU CAN BUILD 133 FASCINATING EXPERIMENTS

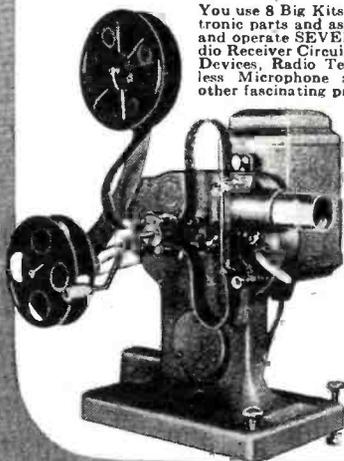You use 8 Big Kits of Radio-Electronic parts and assemblies. Build and operate **SEVEN** different Radio Receiver Circuits, Electric Eye Devices, Radio Telephone, Wireless Microphone and dozens of other fascinating projects.



YOU USE A 16 MM. MOTION PICTURE PROJECTOR with 12 reels of instructive movies to help you grasp important fundamentals faster, easier. You enjoy one of today's most modern, effective training aids, right in your own home.

VETERANS!!!

Both the Home Study and Chicago Laboratory courses of DeForest's Training, Inc. are approved for your training. If you qualify under the "G. I. Law", you can obtain this training without cost.

USE THIS *SHORT CUT* TO EARN REAL MONEY A BETTER JOB FUTURE SECURITY

FREE EMPLOYMENT SERVICE—When you complete your course, our free employment service goes to work to help you get started.



LEARN FASTER AT HOME WITH MOVIES

Without obligation, send for our valuable, information-packed book, **"VICTORY FOR YOU"**.

MAIL COUPON TODAY!

DeFOREST'S TRAINING, INC.
2533-41 N. Ashland Ave., Dept. R.N.-D5
Chicago 14, Illinois, U. S. A.

Send me both your big book "VICTORY FOR YOU" and Kit Supplement, showing how I may make my start in Radio-Electronics with your modern home training plan. No obligation.

Name..... Age.....

Address..... Apt.....

City..... Zone..... State.....

If under 16, check here for special information.

If a discharged veteran of World War II, check here.





Routine production and inspection to specifications do not end Merit's responsibility. Every transformer that leaves the factory must individually assure efficiency for severest and longest service. That's Merit Quality.

EXPORT DEPARTMENT:

1607 Howard Street, CHICAGO 26, U. S. A.
Cable Address: MERIT



MERIT COIL & TRANSFORMER CORP.

TELEPHONE
4427 North Clark St. Long Beach 6311 CHICAGO 40, ILL.

S P O T R A D I O N E W S

metropolitan station in the East, for example, is quoting Class A time at as low as \$15 an hour. But if the rates are bargain, the customers are definitely not bargain-counter. FM salesmen are emphasizing that their listeners are quality buyers. They want quality programs—including the commercials. To give them mine-run instead of institutional commercials is to lose their interest. Advertisers are heeding this advice with the result that FM plugs continue at a comparatively high level. So does the audience. In the words of Martin Schadi, sales manager of WASH, Washington, D. C., "Owners of the 5000 to 8000 FM-AM consoles sold in the Washington area to date are in the high income bracket and constitute a class audience."

LOOKING AHEAD, FMers anticipate that sales of sets will make possible increased rates, in many cases by mid-1947. Interest by advertisers and advertising agencies brightens this hope. That advertisers are aware of FM potentialities was illustrated recently in Washington when, for the first time in history, an advertising agency bought time for a program for themselves on an FM station. Said R. Willoughby Williams, head of the Williams, Stark and Hinkle advertising agency, in announcing purchase of half an hour of time once a week: "The future of FM is limitless, as the world is beginning to realize. We plan to make full use of it both for our clients and ourselves." . . . While we're on the subject, another thing to watch as a rapid and significant development in the FM field during the next few months is the growth of networks. First big hook-ups will probably be mostly in the East, but others will blossom across the country as more and more stations go into operation. It's more than passing significant that, while not mentioned on the program, one of the chief problems facing delegates at the first FM Association regional meeting in April was networks. . . . Chief goal: to keep network programs and plugs on the same high level now being achieved by the station broadcasts.

INVITE AN ADMIRAL TO SPEAK before the Institute of Radio Engineers and the odds should be heavy that you'll get yourself bored stiff, but such was not the case when Vice Admiral Charles A. Lockwood recently spoke to the Institute. His audience had all the elements of six movie thrillers wrapped into a super-production, yet not once did he get off his basic topic—electronics. Without dramatics—he didn't need them—he told of radar's role in submarine warfare. Three factors which made the submarine the deadly weapon it was, he said, were the personnel, improved underwater equipment, and electronics. . . . Especially in submarine-vs.-submarine

Look to WARD

for Greater FM Values!

Ward, world's largest producer of aerials, now offers you leading values in FM with antennas completely adaptable to the varying requirements of each installation. They provide maximum electrical efficiency needed for finest FM reception. The ease with which they may be securely installed, plus strong weather-proof construction assures trouble-free operation—and extra profits for YOU!

The Straight and Folded Di-Poles shown at the right operate in a range of 88 to 106 mc. The Folded Di-Pole model provides broader antenna tuning and matched impedance to the 300 ohm transmission line for maximum response and energy transfer.

The Ward Reflector Kit can be combined with either of the two Di-Poles as illustrated above.

NOTE ALL THESE OUTSTANDING FEATURES:

- Universal base mounts on any roof or wall angle.
- Sturdy vertical element revolves or tilts in base allowing complete flexibility in orienting Di-Pole for maximum gain.
- Di-Pole element constructed of corrosion-preventive aluminum. All other parts completely weather-proofed inside and out.
- Ring provided for attachment of guy wires assuring secure installation.
- Sixty feet of dielectric 300 ohm colinear transmission line is insulated with polyethylene.
- Stand-off insulators guiding transmission line to receiver are of exclusive design minimizing capacity to ground and eliminating reflections on the line.

WRITE FOR FREE CATALOG

THE WARD PRODUCTS CORPORATION
1525 EAST 45th STREET • CLEVELAND 3, OHIO

IN CANADA: Atlas Radio Corp., 560 King St., W., Toronto, Ontario, Canada
EXPORT DEPT.: C. O. Brondes, Mgr., 4900 Euclid Ave., Cleveland 3, Ohio

WARD

Aerials

REFLECTOR KIT MODEL FMR-63 LIST \$5.25



Ward's Reflector Kit combined with either the Straight or Folded Di-Poles as shown at left, provides maximum directional gain of the desired signal and eliminates undesirable and interfering reflections. Di-Pole elements can be rotated to any direction and tilted for any angle to facilitate orienting.

Folded Di-Pole with Reflector Kit

Straight Di-Pole with Reflector Kit

Folded Di-Pole Model FM-55 List \$10.25

Straight Di-Pole Model FM-60 List \$9.00



Get your hat . . . follow the crowds to Hallicrafters booth at the parts show. Get the details on Hallicrafters advanced developments in high frequency, short wave communications equipment. Hear all about the Gatti-Hallicrafters spectacular radio-equipped expedition to the Mountains of the Moon. This scientific safari, based on Hallicrafters-built mobile radio equipment, will spread the name and fame of "the radio man's radio" around the world. All the dope on this exciting adventure at Hallicrafters show headquarters.

hit the trail!



hallicrafters
EXHIBIT
BOOTH 86

hallicrafters

THE HALLICRAFTERS CO., MANUFACTURERS OF RADIO AND ELECTRONIC EQUIPMENT, CHICAGO 16, U. S. A.

warfare, the Admiral pointed out, electronics "demonstrated the tremendous advantage our fighting men were afforded." Perhaps most dramatic underwater battle was staged by the "Batfish," under Commander J. K. Fyfe of Seneca Falls, N. Y. Fyfe was assigned to keep Jap subs from taking emergency supplies to land troops under attack by General MacArthur. Working by night, within a period of 76 hours, and using radar, the "Batfish" nailed three enemy subs going to the rescue of Japs in Luzon. Not once was the U. S. submarine threatened with attack — apparently the Japs weren't even aware of its presence until it was too late. . . .

ANOTHER HIGH SPOT in the Pacific submarine campaign was when the "Sealion", under Commander Eli Reich, used radar to sneak up unobserved on a Japanese flotilla and tagged a battleship, the "Kongo." Commanders discovered early in the game that they — and radar — could work in all kinds of weather. Even when the waves were mountain-high, they stalked the enemy with radar antennas just out of the water, firing entirely on radar range and direction. At other times, with the enemy blinded by poor visibility, they made surface approaches. One bold commander approached a Jap convoy without submerging and at one point was so close that he was almost run down, accidentally, by an enemy ship. He got away untouched. Another, Commander Dick O'Kane of the "Tang", broke all records for a single patrol in October, 1944, by sinking 110,000 tons of enemy shipping, abandoning the attack only when one of the "Tang's" own torpedoes went bad and circled to sink the sub which had fired it. A third, the "Sailfish", under Commander Bob Ward, went after a Jap convoy in a typhoon—40-50 knots of wind with mountainous seas. The wind and waves were so strong that Ward even had difficulty making headway against them, but when he sighted his prize—an aircraft carrier—he fought through and sank it. Even the Japs used to cite this one as an example of daring and determination when they were lecturing new sub recruits. . . .

GETTING BACK TO EARTH, it's not too late to mention a heroic ham hook-up in the East Coast area during the last big snow of the winter in early March. One of the hardest hit towns was Cobleskill, N. Y., some forty miles west of Albany, with a population of 2300. Telephone and power lines went down under a twenty-six inch snowfall and the town was completely cut off from the outside world by 2 a.m. one bitter cold morning, save for a 100-watt ham station, W2DBX, operated by Stanley D. Conklin. He stuck to his set till 6 a.m. before establishing contact with the

outside world in the person of Corporal Albert Martin at Ft. Monmouth's 900-watt station, W2OEC, who picked up Conklin's weak signals asking that the Signal Corps relay messages to the New York Telephone Company and the New York Power and Light Company to get rescue crews on the job. Repairmen fought their way through drifts from Oneonta, N. Y., thirty miles away, finally restoring normal communications and power lines at 6 p.m. Conklin stayed on the job to that point—more than 24 hours without sleep and with a record of sixteen hours without rest at his radio. . . . Other ham stations throughout New England and the Middlewest did emergency work during the storm, with the result that no community hit by the snowfall was long out of touch with the outside world.

ON THE PRODUCTION FRONT, the promises of spring seem to be rocketing toward record fulfillment. Both industry and government sources are agreed that 1947 is going to be a banner year in all departments. "Radio manufacturers," reports the Civilian Production Administration, "are expected to gear their production to increased output of combination or radio-record player models and television sets. Production of table sets has already reached a record monthly rate almost twice the average of 1940-41, and current demand is now being met. Increases in car radio production will be possible as fast as steel is made available for cases, mountings, and parts." These will undoubtedly figure in the fall market, as will FM-AM receivers, already showing good production totals by late spring. FM sets have the backing of the industry, which declared early in the spring through the Board of Directors of the Radio Manufacturers Association that it was "doing everything in its power to expedite the production of FM-AM receivers." Results had already begun to show as early as January, when FM-AM set production totals jumped to 51,318 from the December score of 40,903. Television sets were also up almost two thousand units from December's 3561, reaching a January high of 5437. Table models featured in the television output but the FM-AM sets showed a heavy trend toward consoles. RMA member survey showed a total set output of 1,564,171.

FOREIGN PRODUCTION continues to be miniscule when contrasted with that in the United States. Reports from abroad, some delayed, most sketchy, would seem to indicate that U. S. manufacturers interested in export should find little competition so far as production is concerned for some time to come. Reports indicated that full-scale production might be expected by only two foreign manu-
(Continued on page 168)

Grasp the **NEW OPPORTUNITIES** in

RADIO ELECTRONICS AND TELEVISION NOW!



Modern Radio — FM Broadcast and Reception — Television — Industrial Electronics; Power, Control, Communications—new equipment and methods demand new technical ability and experience. Keep up to date with the latest.

MODERN RADIO EQUIPMENT FOR YOU TO USE AND KEEP



The very essence of National Shop Method Home Training is **EXPERIENCE**. You get actual experience by working with modern Radio and Electronic equipment—building many types of circuits. You may build a fine, long distance **MODERN SUPER-HETERODYNE** signal generator, miniature radio transmitter, audio oscillator, etc.—many other standard actual operating pieces of equipment—conduct cathode ray and other experiments. This practical work advances with your training—**YOU LEARN BY DOING!**

Shop Method Home Training

By a Real Established Resident School with its own FM Studios, Shops and Laboratories.

TRAIN WITH ADVANCED TECHNIQUE

The good jobs in Radio Electronics now go to the men who are equipped to handle them. It takes training and experience. National Schools, one of the oldest and largest trade schools in the country, makes it possible for you to get this training right in your own home **IN YOUR SPARE TIME**.

National maintains modern resident training Studios, Shops and Laboratories where instructors and engineers are working constantly to improve training methods. **SHOP METHOD HOME TRAINING** is a logical extension of this practical system.

A **FREE** lesson that shows you how practical and systematic this new training method is will be sent you without obligation. You may keep and use this lesson to prove to yourself just how practical National Training really is.

Get one of the many **NEW JOBS** that demand new techniques and methods in Modern Radio. Get your share of the **NEW BUSINESS** that servicing the new sets and equipment demands. Experts agree that Radio, Television and Electronics present opportunities

much greater than ever before! Radio is expanding with far-reaching improvements in reception. No one knows yet how great the Television market will be. Electronics will touch almost every walk of life—in industry and in the home.

TURN YOUR INTEREST IN RADIO INTO A CAREER THAT WILL ASSURE YOU SUCCESS AND SECURITY.

FIND OUT WHAT NATIONAL TRAINING CAN DO FOR YOU

Where do you stand today in modern industrial progress? What does the future hold for you? You owe it to yourself to investigate this opportunity. With National Training **YOU GET AHEAD FAST**—you may step into a good position or start a business of your own, with little capital, even before you complete your National Course.

Fit yourself for a career of independence, good earnings, success and security in one of the fastest growing fields in industry. For full information, just send your name and address on the coupon and mail it **TODAY**.

Get This Book FREE

This big book presents the facts about the field of Electronics and your opportunities in it together with full information about the advanced National Training. Read it and make up your own mind that National Training will equip you for a great future. No salesman will call on you from National. The book is **FREE** with your sample lesson. Clip and mail the coupon **TODAY!**



APPROVED FOR TRAINING UNDER GI BILL

See What National Training Has Done For These Men

National Shop Method Home Training wins good jobs, independence and security. Take the word of National men who have established records in their favorite Radio, Television, or other branches of Electronics.

From O. K. Ivey, Washington, D. C., comes this endorsement: "I believe National offers the best course to be had . . . Keep up the good work."

Here's a statement from R. R. Wright, Blackfoot, Idaho: "Due to my training at National I was selected to instruct in the laboratory work of Navy and Marines."



Clifford Hannah, l'ortage La Prairie, Manitoba, Canada, writes: "My training has brought results as I'm in line for another raise thanks to National's encouragement and thorough training."



Joseph Michel, Jr., Granite City, Illinois, writes: "I am enthused with National training. I am now earning \$225 a month as a radio operator and technician and \$20 a week more in my shop at home."

Read what other enthusiastic students have written about National Training in the big 40 page book we will send you.

NATIONAL SCHOOLS

LOS ANGELES 37, CALIFORNIA EST. 1905

MAIL OPPORTUNITY COUPON FOR QUICK ACTION

National Schools, Dept. 2-RN

4000 South Figueroa Street, Los Angeles 37, California

(Mail in envelope or paste on penny post card)

Mail me **FREE** the two books mentioned in your ad including a sample lesson of your course. I understand no salesman will call on me.

NAME AGE

ADDRESS

CITY STATE

Include your zone number

Check here if veteran of World War II

Start Your Own RADIO SERVICE SHOP

Choose one of these
3 GREAT NEW DEALS

Includes TEST EQUIPMENT, TUBES, PARTS, TOOLS

3 complete going-in-business packages. (If necessary they can be changed to suit your needs.)

There never was a better opportunity than now to start a profitable business of your own. No fuss, no worry. Here's everything you need. Details upon request. Write, wire or phone!

\$99⁵⁰

\$179⁵⁰

\$350⁰⁰



**Featherweight
Miniature**

TEST INSTRUMENTS

Compact — Accurate — Priced Right!

- Jeweled Meter • Range Selector Switch
- All multipliers bridge tested for 1% accuracy
- Zero adjustment—built in batteries
- Molded bakelite case only 3-15/16" x 2-7/8" x 2"



MODEL 450A Volt—Ohm— Milliammeter

A fine instrument having a sensitivity of 1000 ohms per volt.
Ranges: Volts DC, 0-5/10/50/500/1000;
Mills DC, 0-1;
Ohms full scale, 0-5000/50,000/500,000;
Ohms center scale, 30/300/3000.

NET complete with batteries **10.90**

MODEL 451A AC-DC Volt—Ohm— Milliammeter

A dependable instrument of wide utility—sensitivity 1000 ohms per volt.
Ranges: Volts AC, DC, and Output Ranges, 0-10/50/100/500/1000;
Ohms full scale, 500,000.
Ohms center scale, 7200.



NET complete with batteries..... **14.90**

MODEL 451B

Same instrument as above but has 2500 ohms per volt sensitivity.

NET complete with batteries..... **16.60**



MODEL 452A Volt—Ohmmeter

A superb instrument—100 microampere meter gives 10000 ohms per volt sensitivity.
Ranges: Volts DC, 0-10/50/100/500/1000;
Ohms full scale, 0-2000/20,000/200,000/2 Megs;
Ohms center scale, 30/300/3000/30,000.

NET complete with batteries..... **14.90**



MODEL 312 Volt—Ohm— Milliammeter

An economy pocket meter featuring a 2" moving vane meter.
Reads: AC-DC volts, 0-25/50/125/250;
Mills AC-DC, 0-50;
Ohms, 100,000;
mfd. .05-15.
Jacks provide range selection.

NET Complete with cord and plug..... **6.75**

TEST LEADS (Removable Needle Points).....**.59**
Excellent for above instruments.

TURNTABLE STAND



\$3.91

FREE

With each stand we send a stroboscope free.

All steel—adjustable—holds turntable 15" above bench—tilts to any position—speeds work—saves time—prevents damage to parts—pays for itself on first job—you need several at this low price.

PHILCO BEAM OF LIGHT

Selenium cell only, no holder, postpaid... **\$1.80**
(Puts new life into Philco Changers)
Sapphire needle only, no-mirror, postpaid **\$1.20**

SHORT WAVE RECEIVERS



Hallierafters S-38..... **\$47.50**
S-40 (Replaces S-20R)..... **89.50**
SX-42 (Replaces SX-28A)..... **275.00**



SELENIUM RECTIFIERS

Direct permanent replacement for 117Z6—117Z3, etc. No filament—no socket—no trouble.

1 to 5 **1.08** net 6 to 49 **98c** net 50 or more **90c** net

SLIDE RULE DIALS



Crowe No. 534—direct ratio drive—antique bronze escutcheon 2 3/8" x 4"—pointer travel 3 3/4".
NET with pilot lamp bracket... **\$1.74**

V. M. AUTOMATIC CHANGER




A Two Post Changer with well-made mechanism—plays 10" or 12" records intermixed. Low pressure crystal pickup. Size 14" x 14". Packed two to a factory-sealed carton, factory guaranteed.

SPECIAL EACH **15.95** CARTON OF TWO **29.95**

TRANSVISION

Television Kit

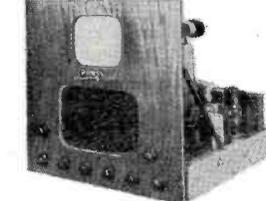

- Proven Circuit
- 7" Picture Tube
- Pre-tuned RF
- Special Antenna
- 100% Complete

Famous Television Kit as advertised by Transvision, Inc. complete with all tubes, panel, everything—now available from our stock. Another Radio Supply "First"..... **\$159.50**

When ordering, specify station channels needed.



JEWELLED PILOT LIGHT ASSEMBLIES

- Candelabra screw base for 110 volt lamp.
- Mount in 1" hole.
- Lamps removable from front of panel.
- Available marked 1-2-3 or 4 on back of lens.

YOUR CHOICE net **19c**

Include full remittance with orders of \$3.00 or less. Include 25% deposit with all C.O.D. orders of \$3.00 or more. Prices subject to change without notice.

SEND FOR FREE CATALOG

RADIO SUPPLY & ENGINEERING CO., Inc.

129 SELDEN AVE.

DETROIT 1, MICH.

For finer tone

GENERAL ELECTRIC
Electronic
RADIO TUBES



RADIO TUBES

◆ Monica Lewis, popular singing star, in this 21" by 26" window card, draws attention to the fact that YOU install and sell G-E radio tubes. Handsomely lithographed in four colors, varnished, backed and easled, the display is a "traffic-stopper". Like the many other G-E sales helps for 1947, it will make your cash-register ring to the tune of G-E product-popularity.



▲ Write for your free copy of the General Electric sales-helps Booklet ETR-51, illustrating and describing the big, elaborate array of G-E 1947 display, advertising, and promotion material available to radio servicemen and tube dealers. Also tells how to use each item best and most profitably. Filled with marketing hints! Send for Booklet ETR-51 TODAY!

In dealer displays and sales helps— as in quality— G-E TUBES LEAD!

EVEN THOUGH you're handling a product known to be the finest of its type, *it pays to advertise!* That way lies the path to profits! So when you install and sell General Electric radio tubes, the public still should be told and re-told that your shop is local sales headquarters.

Stunning displays like the one shown here, spark an aggressive campaign of G-E tube advertising and sales helps created for one purpose only: to acquaint radio owners in *your* area with *your* facilities to serve them. Thus your circle of customers widens; your income grows.

Many of the G-E pieces subordinate any tube message to the theme of your quality radio service. This service theme is carried through on counter displays, blotters, direct-mail cards, newspaper mats—many other items which actively *sell* for you day-in and day-out.

Make 1947 your biggest year by taking full advantage of G-E technical leadership—universal owner acceptance—brilliant new advertising material that's ready to help *you* secure the volume tube business waiting for you! *Electronics Department, General Electric Company, Schenectady 5, N. Y.*

GENERAL  **ELECTRIC**

176-F5-8850

FIRST AND GREATEST NAME IN ELECTRONICS

The Complete **E-V** Line Assures the Right Microphone for Every Need


● Only ELECTRO-VOICE provides such a complete line of microphones. With outstanding developments in Unidirectional, Differential†, Bi-directional, and Non-directional types . . . in Dynamic, Crystal, Carbon and Velocity models . . . you can more easily obtain the microphones best suited to your needs.

● Proved in critical service, E-V Microphones are widely used today by leading manufacturers and sound engineers in all kinds of applications. They are produced from finest materials under E-V quality control. Consult our engineers.

THE CARDYNE—True cardioid unidirectional dynamic microphone, with exclusive E-V *Mechanophase** principle, *Acoustalloy* diaphragm, smooth, wide range response, and high output.

THE CARDAX—The only high level cardioid crystal microphone with Dual Frequency response for high fidelity voice and music, or rising characteristic for extra crispness of speech.

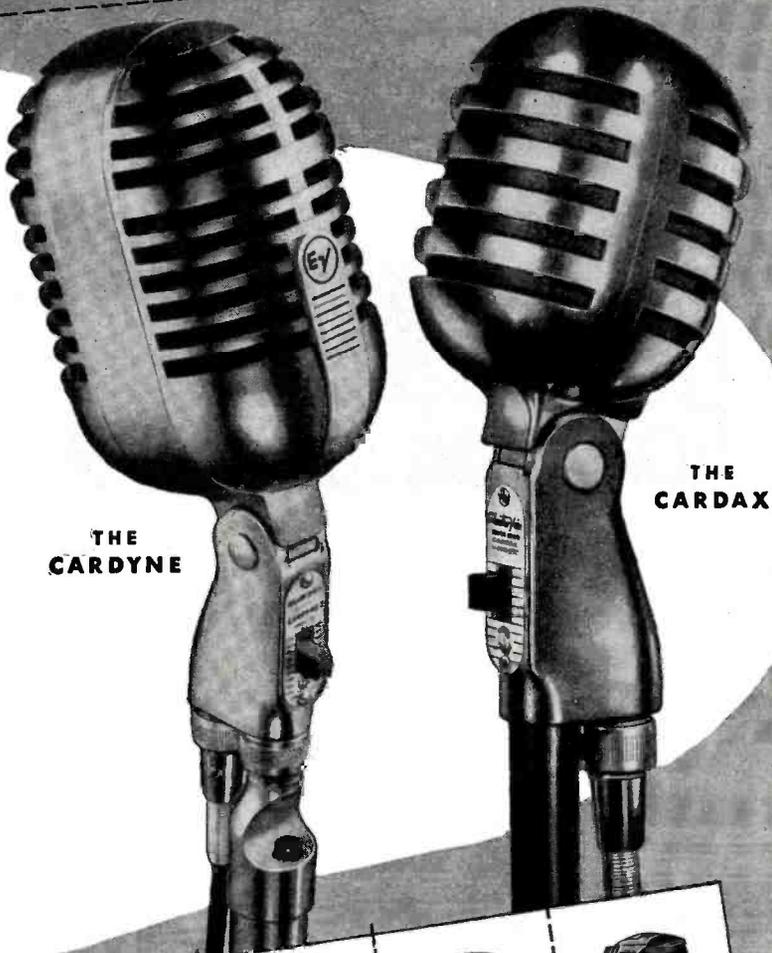†Patent No. 2,350,010 *Electro-Voice Patents Pending



THE CARDYNE

THE CARDAX



Send for Catalog No. 101
This illustrated catalog gives complete data and information on E-V Microphones. Includes helpful selection guide. Write for it today.

 V-3, V-2, V-1 Velocity	 640 Dynamic	 630 Dynamic	 605 Dynamic 905 Crystal	 610 Dynamic 910 Crystal	 600-D Dynamic 210-S Carbon 602 Differential	 205-S Differential
 606 Differential						 Comet Crystal Comet-D Dynamic

A portion of the Complete E-V Line is shown here

NO FINER
CHOICE THAN

Electro-Voice

ELECTRO-VOICE, INC., BUCHANAN, MICHIGAN

Export Division: 13 East 40th Street, New York 16, N. Y., U. S. A. Cables: Arlab

Crystal Microphones licensed under Brush patents

GET YOUR PROFIT-MAKING FEDERAL SELENIUM RECTIFIERS FROM THESE JOBBERS!

There's an authorized jobber near you who can supply your Federal Miniature Rectifiers — and give you free selling-aids that will help you cash in on the big market for this new component that replaces the rectifier tube

in AC-DC, Portable, Table, and Console radio receivers.

It's the modern way to give better service, improve set performance, get instant starting and longer life. . . Get in touch with your nearest jobber today.



- ALABAMA**
Mobile—Radio Labs
- ARIZONA**
Phoenix—Southwest Wholesale Radio & Appliance Co.
- ARKANSAS**
Ft. Smith—Wise Radio Supply
- CALIFORNIA**
Long Beach—Fred S. Dean Co.
Los Angeles—U. S. Grant Supply Co.
Radio Equipment Distributors
Radio Products Sales Co.
Radio Specialties Company
United Radio Supply Co.
Sacramento—Sacramento Electric Supply
San Diego—Electronic Distributors Radio Parts Co.
San Francisco—Leo J. Meyberg Co., Inc.
Schuyler-Wilson Co.
Zack-Radio Supply Co.
Santa Ana—Radio & Television Equipment Co.
- COLORADO**
Denver—Inter-State Radio & Supply Co.
Radio Products Sales Co.
- CONNECTICUT**
Bridgeport—R. G. Scell & Co.
Hartford—R. G. Scell & Co.
New Britain—United Radio Supply
- DELAWARE**
Wilmington—Radio Electric Service Co. of Pennsylvania
- DISTRICT OF COLUMBIA**
Washington—Capitol Radio Wholesalers
Emerson Radio of Washington
- FLORIDA**
Miami—Herman Radio Supply Co.
Thurow Distributors, Inc.
Jacksonville—Thurow Distributors, Inc.
Orlando—Thurow Distributors, Inc.
St. Petersburg—Welch Radio Supply
Tallahassee—Thurow Distributors, Inc.
Tampa—Thurow Distributors, Inc.
W. Palm Beach—Goddard Distributors
Thurow Distributors, Inc.
- GEORGIA**
Atlanta—Concord Radio Corp.
Augusta—Prestwood Electronics Co.
- IDAHO**
Boise—Craddock's Radio Supply
- ILLINOIS**
Chicago—Allied Radio Corporation
The Lukko Sales Corp.
Walker-Jimieson, Inc.
- INDIANA**
Anderson—Seybert's Radio Supply Co.
Evansville—Wesco Radio Parts
Indianapolis—Kiefer-Stewart Co.
Radio Distributing Company
Rodefied Co.
Van Sickle Radio Supply Co.
Muncie—Standard Radio Parts
South Bend—Colfax Co., Inc.
Terre Haute—Terre Haute Radio
- KANSAS**
Wichita—Radio Supply Company

- KENTUCKY**
Louisville—P. I. Burks & Co.
Universal Radio Supply Co.
Owensboro—General Electronic Supply
- LOUISIANA**
New Orleans—Radio Parts, Inc.
Shuler Supply Co.
Southern Radio Supply Co.
Walther Bros. Company
- MAINE**
Auburn—Radio Supply Co., Inc.
Bangor—Radio Service Laboratory of New Hampshire & Maine
Portland—Radio Service Laboratory of New Hampshire & Maine
- MARYLAND**
Baltimore—Kann-Ellert Electronics, Inc.
Wholesale Radio Parts Co., Inc.
Cumberland—Radio Wholesaler
- MASSACHUSETTS**
Boston—De Mambro Radio Supply Co.
Louis M. Herman Company
Hub Cycle and Radio Co., Inc.
Radio Shack Corporation
Cambridge—Electrical Supply Corp.
The Eastern Company
Fall River—Flint Radio Co.
Roxbury—Gerber Radio Supply Co.
Worcester—De Mambro Radio Supply Co.
- MICHIGAN**
Detroit—Ingram Distributing Co.
Grand Rapids—Milton Bursma
- MINNESOTA**
Minneapolis—Lew Bonn Co.
- MISSOURI**
Kansas City—Potter Radio Company
St. Louis—Radonics
- NEBRASKA**
Omaha—General Appliance Co.
- NEW HAMPSHIRE**
Manchester—De Mambro Radio Supply Co.
Radio Service Laboratory
- NEW JERSEY**
Camden—General Radio Supply Co.
Radio Electric Service Co. of Pennsylvania
Newark—T. A. O'Loughlin & Co.
Variety Electric Company
Perth Amboy—Bennett's Radio Supplies
Phillipsburg—Carl B. Williams
- NEW MEXICO**
Albuquerque—Radio Equipment Co.
- NEW YORK**
Albany—Hudson Valley Asbestos Corp.
E. E. Taylor Co.
Binghamton—Broome Distributing Co.
Federal Radio Supply
Morris Distributing Co., Inc.
Buffalo—Genesee Radio & Parts Co.
Radio Equipment Corp.
Standard Electronics Co.
Elmira—Fred C. Harrison Co.
Le Valley-McLeod-Kincaid Co.
Hempstead—Standard Parts Corp.
New York—Bronx—Slate and Company
Brooklyn—Benray Distributing Co.
Electronic Equipment Company, Inc.
Green Radio Distributors
Hornbeam Distributing Co.

- MANHATTAN**—H. L. Dalls, Inc.
Federated Purchaser Inc.
Harvey Radio Company, Inc.
Milo Radio & Electronics Corp.
Newark Electric Co., Inc.
Radio Wire Television Inc.
Radiomic Equipment Co.
Stan-Burn Radio & Electronics Co.
Terminal Radio Corporation
- QUEENS**—Peerless Radio Distributors
- ROCHESTER**—Hunter Electronics
Masline Radio & Electronic Equipment Co.
Rochester Radio Supply Co.
- SCHENECTADY**—M. Schwartz & Son
Syracuse—Broome Distributing Co.
W. E. Ferndt
Morris Distributing Co.
Syracuse Radio Supply Co.
- TROY**—Trojan Radio Co., Inc.
- UTICA**—Beacon Electronics, Inc.
Electronic Lab's & Supply Co.
Vaeth Electric Co.
- WHITE PLAINS**—Sound Products Co.
Westchester Electronics Supply Co.
- NORTH CAROLINA**
Charlotte—Radiotronic Distributors, Inc.
Raleigh—Supreme Radio Suppliers
- OHIO**
Akron—Brighton Sporting Goods Corp.
Cincinnati—Herrlinger Distributing Co.
Holub & Hogg
Cleveland—Goldhammer, Inc.
Columbus—Hughes-Peters, Inc.
Thompson Radio Supplies
Dayton—Hughes-Peters, Inc.
Standard Radio & Electronics Products Co.
Toledo—Lifetime Sound Equipment Co.
Warren Radio Company
- OKLAHOMA**
Lawton—Reynolds Radio Supply
- OREGON**
Portland—Lou Johnson Company
Tracy & Company, Inc.
- PENNSYLVANIA**
Allentown—Radio Electric Service Co. of Pennsylvania
Ardmore—O. K. Griffith Radio
Erie—Warren Radio Company
Harrisburg—Radio Distributing Co.
Lancaster—Geo. D. Barbey Co.
Mt. Carmel—Big Boys Auto Parts Co.

- PHILADELPHIA**—Almo Radio Co.
Emerson Radio of Pennsylvania
Electronic Research Laboratories
Radio Electric Service Co. of Pennsylvania
- PITTSBURGH**—Cameradio Co.
Tydings Company
- READING**—Geo. D. Barbey Co.
- SCRANTON**—Fred P. Pursell
- SUNBURY**—Big Boys Auto Parts Co.
- WILKES-BARRE**—General Radio & Electronic Co.
- YORK**—J. R. S. Distributors
- RHODE ISLAND**
Providence—Wm. Dandreta & Co.
De Mambro Radio Supply Co. (Branch)
W. H. Edwards Co.
- SOUTH DAKOTA**
Rapid City—Giraud Supply Co., Inc.
- TENNESSEE**
Memphis—Bluff City Distributor Co.
Nashville—Currey's, 109 16th Ave.
- TEXAS**
Dallas—Crabtree's Wholesale Radio Huey & Phillip Hardware Co.
Wilkinson Brothers
Ft. Worth—Fort Worth Radio Supply Co.
Houston—Sterling Radio Products Co.
San Antonio—Mission Radio, Inc.
- UTAH**
Salt Lake City—S. R. Ross
- VERMONT**
Burlington—Vermont Hardware Co.
Rutland—Rutland Center
- VIRGINIA**
Norfolk—Radio Parts Distributing Co.
Radio Supply Company
Roanoke—Leonard Electronic Supply
Staunton—Southern Electric Co.
- WASHINGTON**
Seattle—Seattle Radio Supply, Inc.
Herb E. Zobrist Co.
Yakima—Lay & Nord
- WISCONSIN**
Milwaukee—Radio Parts Co., Inc.
- OUTSIDE THE UNITED STATES**
HAWAII
Hilo—Photo Radio Products, Ltd.
Honolulu—Radio Wholesale & Supply Co.

GET THESE FREE SALES HELPS



SELF-SERVICE COUNTER DISPLAY
Holds 12 individually boxed units.



SERVICE MANUALS
Show how to apply and install Federal's Miniature Rectifiers.


ALSO — a 17-by-22 inch 3-color window poster, that gives all sales points at a glance. Available from your nearest jobber!

Federal Telephone and Radio Corporation

In Canada: — Federal Electric Manufacturing Company, Ltd., Montreal.
Export Distributors: — International Standard Electric Corp. 67 Broad St., N. Y.



100 Kingsland Road,
Clifton, New Jersey

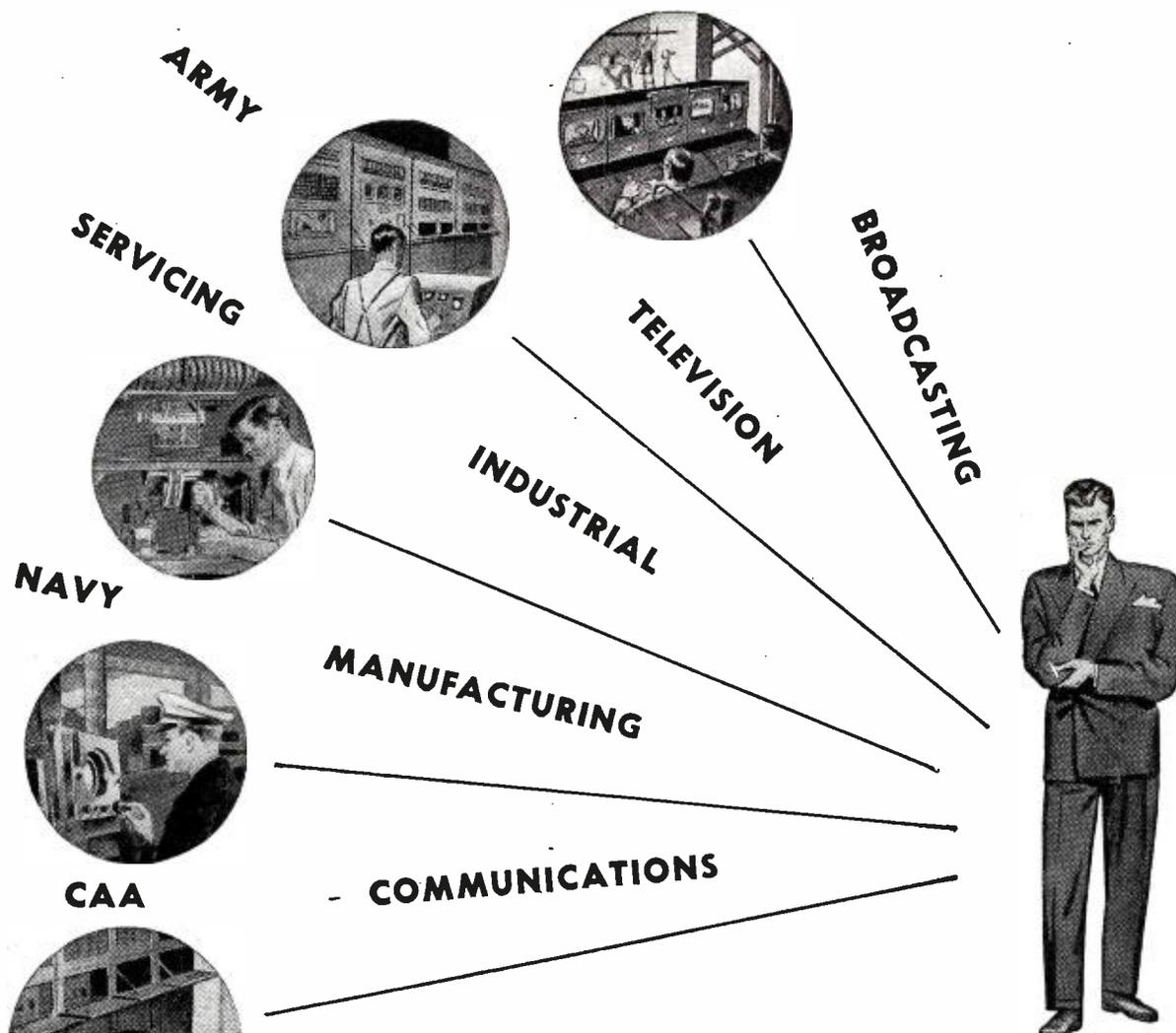

Where Do YOU Go From Here?

CREI Streamlined, spare time training is the DIRECT COURSE to that Secure, GOOD-PAYING JOB You Want

NEVER was there such widespread opportunity as exists today in every field of radio-electronics. Not only are there countless new jobs . . . but *more* jobs with good salaries. The demand, however, is far beyond the number of radiomen *qualified* to fill these positions.

You may have "gotten by" up to this point. But if you want to progress with the industry . . . if you want an important, good-paying position and the security that goes with it—you must acquire up-to-date technical training.

No matter if your interest lies in broadcasting, aviation, manufacturing, television or radio service, or in any of the many other radio-electronics applications that are

open today . . . you can enroll with CREI confident that this high-calibre, professional, practical radio-electronics engineering training will give you proper and sound qualifications for the field of your choice.

Decide today "where YOU will go from here". You can assure your future security . . . end the threat of competition challenging you for your job. CREI is prepared to train you for a better place in this new world of electronics. Mail the coupon today for details of the CREI self-improvement program. Yes, a 3c stamp can result in more security . . . a better job . . . happiness. Write *now*.

If you have had professional or amateur radio experience and want to make more money, let us prove to you we have the training you need to qualify for a radio job. To help us intelligently answer your inquiry—PLEASE STATE BRIEFLY YOUR BACKGROUND OF EXPERIENCE, EDUCATION AND PRESENT POSITION.



VETERANS! CREI TRAINING AVAILABLE UNDER THE "G. I." BILL!

Capitol Radio Engineering Institute

An Accredited Technical Institute

DEPT RN-5; 16TH AND PARK ROAD, N. W., WASHINGTON 10, D. C.

Branch Offices: New York (7): 170 Broadway • San Francisco (2): 760 Market St.

Mail Coupon for FREE BOOKLET

CAPITOL RADIO ENGINEERING INSTITUTE

16th & Park Rd., N. W., Dept. RN-5, Washington 10, D.C.

Gentlemen: Please send me your free booklet, "CREI Training for Your Better Job in RADIO-ELECTRONICS", together with full details of your home study training. I am attaching a brief resume of my experience, education and present position.

CHECK PRACTICAL RADIO ENGINEERING COURSE PRACTICAL TELEVISION ENGINEERING

NAME.....

STREET.....

CITY.....ZONE.....STATE.....

I am entitled to training under the G.I. Bill.

RADIO NEWS

Metropolitan Introduces for the first time
The NEW PREMIER Model 570
SIGNAL GENERATOR

With the NEW EXCLUSIVE

MICROMASTER BAND SPREAD DIAL

an important feature for testing and aligning
BROADCAST — SHORT WAVE
FM and TELEVISION RECEIVERS

Range: 75 Kc to 150 Mc

The PREMIER MODEL 570 is the **only** low priced Signal Generator incorporating a MICROMASTER BAND SPREAD DIAL . . . This Dial is geared to the tuning condenser and main dial, giving a total scale length of approximately 60 inches. It is a very important and major feature for tuning and aligning FM and Television receivers where tuning is very sharp and critical. Any frequency setting can be tuned and repeated very accurately.


The main nine-inch **THREE COLOR DIAL** is directly calibrated in Kilocycles and Megacycles, and the BAND SPREAD DIAL can be used for your own accurate calibrating purposes . . . it reads 0 to 100.

VERNIER and BAND SPREAD DIAL are housed in a casting which contains spring-loaded split-gears to eliminate backlash and provide smooth split-cycle tuning.

Complete dial and fine pointer are enclosed in a dust-proof casting with a glass window, which prevents the pointer from accidentally being bent or otherwise disturbed and thus putting the instrument out of calibration.

Dial is indirectly illuminated by two hooded pilot lights.

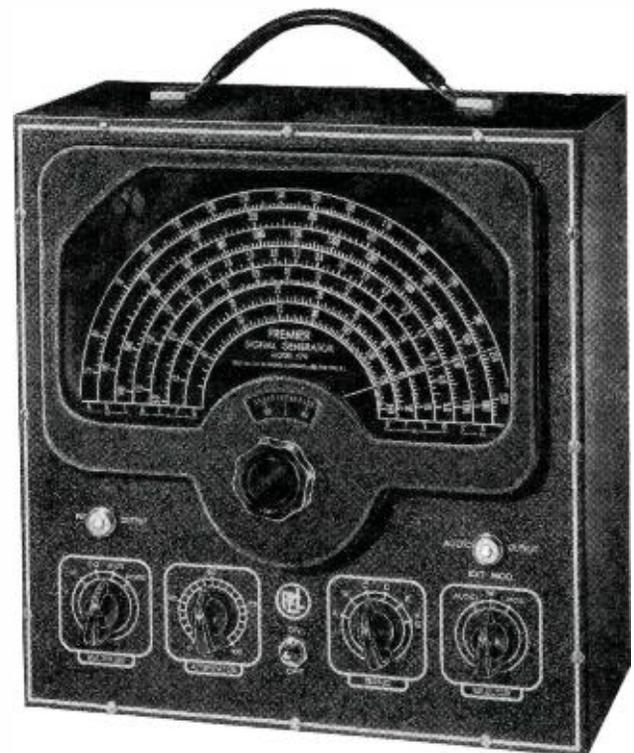Manufactured by PREMIER ELECTRONIC LABS., N. Y.



Specifications

- AIR TRIMMERS:** The use of Air Trimmers on all bands retains original calibration regardless of temperature or humidity changes.
- BUFFER STAGE:** The oscillator is electron coupled to a Buffer Stage, which is in turn modulated, resulting in frequency stability.
- ACCURACY:** Calibrations are stable and accurate better than 1%.
- TRIPLE SHIELDING:** Coils, Attenuator and Line Filter are individually shielded, then in addition the entire chassis is completely shielded. The metal cabinet offers final shielding. Chassis and shields are copper plated. This series of shielding reduces leakage and radiation to an absolute minimum.
- BANDS:** 75—220; 200—600; 550—1700 KC and 1.6—5.0; 5.0—16; 14—50 MC on fundamentals and 45—150 MC on third harmonic.
- COILS:** All coils are pretested and individually calibrated before they are installed, resulting in greatest possible accuracy in calibration. Unused coils are automatically shorted out, eliminating dead spots and absorption.
- CONDENSER:** A special geared wide spaced straight line frequency condenser provides linear calibrations over the entire dial range. (Does not crowd up towards the high frequency end of the dial as found in other signal generators.)
- SINE WAVE:** Internal 400 cycles Audio Generator provides a pure sine wave for modulation (Less than 5% distortion) as well as an audio signal for external testing purposes.
- EXTERNAL MODULATION:** High Fidelity modulation from 0 to 100% from below 50 cycles per second to over 15,000 cycles per second.
- ATTENUATOR:** Four step ladder type completely shielded attenuator provides a smooth control from zero to full output.
- LINE FILTER:** A very effective shielded Line Filter is incorporated consisting of two inductances and condensers (not merely bypassing the line) reduces line leakage to a negligible point.

IMMEDIATE DELIVERY FROM STOCK — GUARANTEED!

SIZE: 12" x 12½" x 5½".
WEIGHT: 16 lbs. net.

Spring action, snap-type leather carrying handle.

\$54⁷⁵
NET

Complete with coaxial cable.

TERMS: 25% DEPOSIT, BALANCE C.O.D.
 OR FULL PAYMENT WITH ORDER.

WRITE FOR FREE CATALOG


May, 1947

Metropolitan ELECTRONIC & INSTRUMENT CO.
 Dept. R, 6 MURRAY STREET Cable Address: METRONICS
 NEW YORK 7, N. Y., U. S. A. Phone: BARclay 7-5556

PHILCO

Aerial Merchandising

means Bigger Profits for YOU

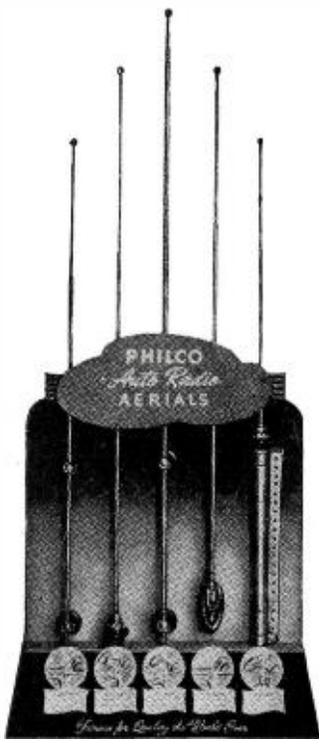


PHILCO 5-UNIT AUTO AERIAL DISPLAY

Shows a selection of 5 popular models. Smartly styled. Occupies minimum space. Permits customer to see them *all* and make his choice. Helps you sell-up. Get it **FREE** from your Philco Distributor.

PHILCO 2-UNIT AUTO AERIAL DISPLAY

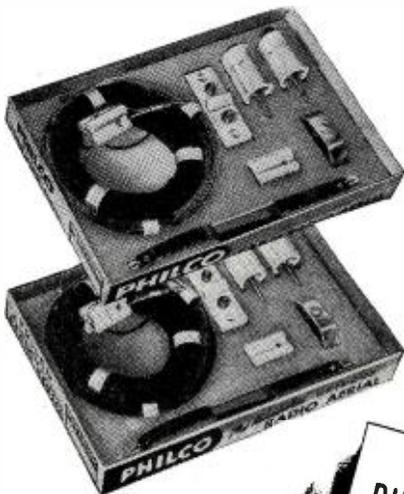Shows 2 models—the famous Philco Duo-flex and the sensational "Special," greatest auto aerial value of all time. The perfect sell-up display! Fits anywhere. Get it **FREE** from your Philco Distributor.



PHILCO OUTDOOR AERIAL

Everything in one package at a sure-fire low price. For months it's been selling like hot cakes. Profitable!

PHILCO FARM AERIAL

Another big selling package deal. A "must" for dealers selling in the farm areas.

PHILCO FM DIPOLE AERIAL

Makes any FM radio perform better. Get set for the swing to FM by featuring your installation service with this new Philco product.



Here it is from Philco—the aerial line that gives you everything to get a bigger share of this profitable business this year. *All* the best-selling types of aerials—*plus* sensational new models with quality and price appeal. Auto Aerials—Home and Farm Aerials—FM Aerials. Values that stand out above competition! Features that sell on sight! Displays that catch customer's eyes—lead to many extra sales!

PHILCO COOPERATIVE ADVERTISING Greatest in the Aerial Business


Yes, cooperative local advertising over *your* name—newspaper advertising, radio advertising, direct mail pieces, handbills—Philco goes *all out* to make *your* store the aerial headquarters of your community.

Every month, the year 'round, new PHILCO SALES-BUILDING PROMOTIONS help you get this profitable business

With Philco Aerials and other Accessory Products, you can take the seasonal dips out of your sales. Fresh new Philco promotions help you keep sales going up month after month—keep stocks moving. There's nothing like the Philco plan for profits! Get the facts at once from your Philco Distributor.


PHILCO ACCESSORY PRODUCTS ARE BIG BUSINESS!

Accent on

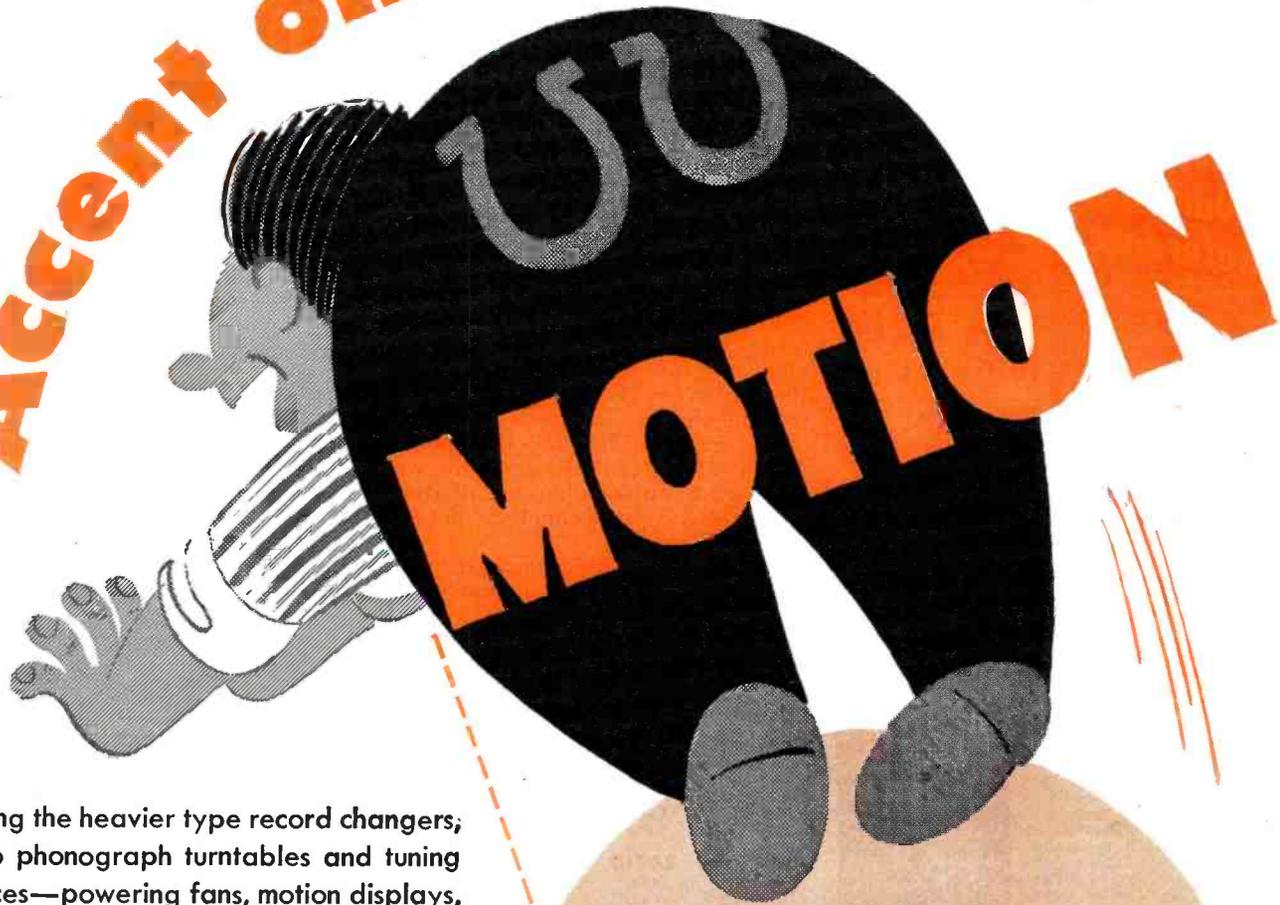

Driving the heavier type record changers, radio phonograph turntables and tuning devices—powering fans, motion displays, actuating switches, levers and timing devices—operating business and vending machines, toys—these are just a few of the tasks performed by Alliance's Model K Powr-Pakt motor.

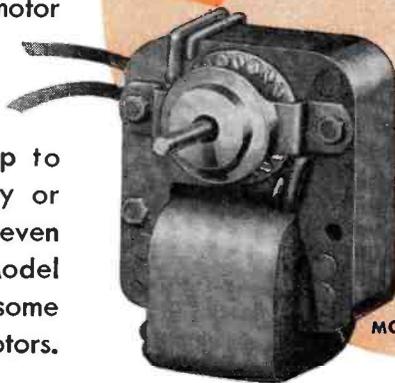This basic 2-pole induction type motor can be mass produced to meet variations in design. It will adapt to any standard AC voltage and frequency, and will develop up to 1/100th h. p. For intermittent duty or where forced ventilation is provided even greater output can be obtained. Model K is used in all 25-cycle and in some 50 and 60-cycle Alliance phonomotors.



MODEL K

The trend is to make things move!

Designs will call for more action—movement! Flexible product performance needs power sources which are compact, light weight! Alliance Powr-Pakt Motors rated from less than 1-400th on up to 1-20th h.p. will fit those "point-of-action" places! Alliance Motors are mass produced at low cost—engineered for small load jobs!

For vital component power links to actuate controls... to make things move... plan to use them!



WHEN YOU DESIGN—KEEP


alliance

MOTORS IN MIND

ALLIANCE MANUFACTURING COMPANY • ALLIANCE, OHIO

RADIOMEN! Here's the Way to Bigger Pay

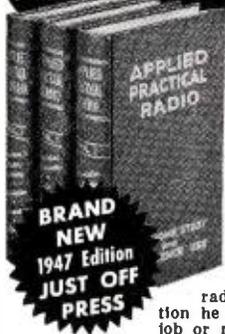A Complete Practical Set of **RADIO** Home Study and Reference Books for Only **\$9.75** CASH PRICE



BRAND NEW 1947 Edition JUST OFF PRESS

Yours FREE To Try 7 Days

NOW — a new 1947 set of practical, "down to earth" books for the man who wants to get ahead in RADIO and realizes he must know modern radio and television to handle a bigger job. "Applied Practical Radio" gives the radio worker the information he needs to advance in his job or radio business. Yet, this great set is written simple enough for the beginner. This is the only set of its kind in America today.

APPLIED PRACTICAL RADIO Tells All in 3 Handy Volumes

Here is practical, working knowledge of RADIO as it is used TODAY—from basic principles to latest advances in Television. The facts are boiled down, including the "know how" to construct, install and service all types of Radio and Television apparatus. Unique picture instruction method takes equipment apart to show what makes it work and how to keep it going.

FREE!

1 year of Consultation Service & Tech Bulletins included

Everything New in Radio Made Easy

The hundreds of interesting up-to-the-minute subjects covered include Frequency Modulation, Television, Auto Radio, Public Address Systems, Multi-Band Receivers, High Frequency and Short Wave—everything in radio today from A to Z. Almost 1000 pages with 600 illustrations and new diagrams.

10 to 1 GUARANTEE
Set must earn 10 times its cost or Coyne sends money back on its return at end of 1 year.

Send No Money — See Books Free

But don't take our word for what these great books can do for you—see them yourself. Just fill in coupon below and mail it today. Coyne sends you "APPLIED PRACTICAL RADIO" to look over 7 days FREE. If you feel set isn't everything we say AND MORE. Just return it at our expense and you owe nothing. If you keep the set you need pay only \$3 after 7 days and \$3 per month (see coupon). You can't lose on this offer, so don't delay—send that coupon NOW.

COYNE ELECTRICAL SCHOOL
Radio Division, Dept. 57-74,
CHICAGO 12, ILL.

Backed by Coyne School's 20 years of Radio shop experience



FREE TRIAL COUPON

EDUCATIONAL BOOK PUBLISHING DIVISION,
COYNE ELECTRICAL & RADIO SCHOOL, Dept. 57-74
800 S. Paulina St., Chicago 12, Ill.

Send me Coyne's new 3-Volume Set, "APPLIED PRACTICAL RADIO" for FREE examination. After 7 days I'll either return it and owe nothing, or pay \$3 and \$3 a month to total \$10.75. Or I'll pay \$9.75 cash price in 7 days. Include 1 yr. FREE Consultation Service, Technical Bulletins and 10 to 1 Guarantee.

NAME..... AGE.....

ADDRESS.....

TOWN..... ZONE..... STATE.....

Send C.O.D. I'll pay postman \$9.75 plus C.O.D. fee. Same money back guarantee after 7-day trial.

Within the INDUSTRY

D. E. NOBLE, vice-president in charge of the Communications and Electronics Division of *Motorola*, was awarded the grade of Fellow by the Institute of Radio Engineers at their banquet held in conjunction with the IRE New York meeting.



The grade of Fellow is honorary and awarded to IRE members who have made outstanding contributions to the science or technology of radio and allied fields.

Mr. Noble has been engaged in the development of FM equipment for mobile service and military applications since joining *Motorola* in 1940. He is chairman of Panel 13 of the Radio Technical Planning Board, chairman of the IRE technical committee on Railroad and Vehicular Communications and chairman of the RMA committee on Vehicular Radio Communications Equipment.

CONCORD RADIO CORPORATION recently opened the new *Concord Buying Center* at 229 West Madison Street, Chicago, to an enthusiastic preview audience.

The new store has been especially designed to feature several revolutionary merchandising ideas, including sound-proof demonstration salons to enable customers to sound test and inspect radios, radio-phonographs, amplifiers, microphones, sound equipment and movie equipment.

Special facilities have been provided for the comfort and convenience of servicemen, dealers, hams, and other buyers.

ALBERT C. GABLE has been named assistant engineer of the Tube Division of *General Electric Company's* Electronics Department.



Mr. Gable, who was formerly administrative assistant of the division's engineers, will continue to maintain his headquarters at Schenectady where he has worked on various engineering assignments since 1929.

A native of Macon, Ga., Mr. Gable holds a B. S. degree in electrical engineering from Georgia Tech. He joined *General Electric* in 1929, working in the Test Department and Vacuum Tube Engineering Department. In 1931 he became section leader on the

development of rectifier tubes. Responsibility for ignitron and thyatron tube engineering was added to his duties shortly thereafter.

NATIONAL ASSOCIATION OF BROADCASTERS announced the appointment of three new members to their Sales Managers Television Subcommittee.

Newly appointed members are Samuel H. Cuff, *Allen B. DuMont Laboratories, Inc.*, New York; G. Emerson Markham, WRGB, Schenectady, New York; and George Moskovics, commercial manager, WCBS-TV, New York.

EDWARD E. WINEBLATT was recently named as the first direct factory representative to handle the *JFD Manufacturing Co.'s* line of radio parts.



After an extensive training in the various company plants, Mr. Wineblatt is now prepared to serve the company's customers for dial belts, cables, battery plugs, ballast tubes, step-down ballasts and line cords.

Mr. Wineblatt will maintain headquarters at the Hotel Monterey, 808 Junior Terrace, Chicago 13, Illinois. He will cover the state of Illinois.

DONALD MacGREGOR, formerly executive vice-president of *Webster-Chicago Corporation*, has been elected vice-president in charge of production for the *Zenith Radio Corporation* of Chicago.

He began his business career with the *Belden Manufacturing Company* in 1920. Since that time, he has held positions with *All-American Mohawk Corporation*, *Rauland Corporation*, *Thordarson Electrical Manufacturing Company*, and *Watson town Cabinet Company*.

Mr. MacGregor is one of the founders of RMA and for several years held the post of director for the association.

JOHN C. WEBB, former sales manager for *Micro-Ferrocart Products Division*, of *Maguire Industries*, Stamford, Conn. and former vice-president of the *Ferrocart Corporation of America*, announces the organization of a new company to be known as the *Stanwyck-Webb Magnetic Core Corporation*, with both plant and laboratories to be located in Ossining, New York.

Large scale production is now underway with several recently completed new developments for low frequency application.


Mr. Webb is well known in the radio

RADIO NEWS

DESIGNED FOR THE BETTER SERVICE SHOP . . .



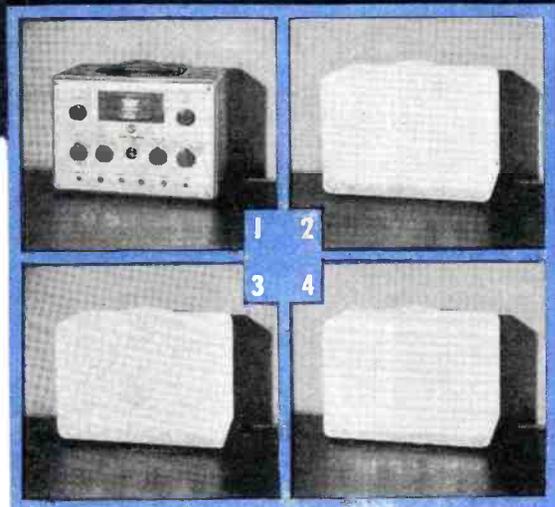RCA'S NEW AUDIO OSCILLATOR
. . . first unit of a
revolutionary new line



ON THE WAY—a superior line of test equipment that puts time-consuming service jobs on a profitable, production-line basis . . . that anticipates all FM and television needs. Matched styling of all instruments permits attractive, convenient grouping. Watch for announcements of the other units in this new line. *Keep in touch with your RCA Test Equipment Distributor.*

A real time-saver for loudspeaker testing and radio servicing

Profitable applications include such diverse jobs as finding the cause of loudspeaker rattle, measuring receiver fidelity and audio amplifier response.

The WA-54A is a temperature-compensated, beat-frequency oscillator with an electronic output-level indicator. The electronic eye serves as a reference to provide an even signal level at all frequencies, and also acts as a zero-beat calibration indicator.

Other outstanding features of this audio-frequency signal source include: wide range . . . continuous tuning . . . low distortion . . . low hum level . . . balanced line outputs . . . application as an a-f amplifier . . . all explained in the WA-54A bulletin, which is yours for the asking.



TEST AND MEASURING EQUIPMENT
RADIO CORPORATION of AMERICA
ENGINEERING PRODUCTS DEPARTMENT, CAMDEN, N.J.

In Canada: RCA VICTOR Company Limited, Montreal

Have you these 5 sales advantages?


Every Stromberg-Carlson sound equipment distributor now has available these 5 sales advantages for you—5 profitable products with all the latest scientific features that sound equipment customers are looking for ... designed and manufactured with the same skills and experience that make the famous Stromberg-Carlson

radios, telephones and telephone switchboards.

What's more, Stromberg-Carlson dealers have had this profitable line for over a year!

Look these quality products over—then you will decide to carry the profit line ... Stromberg-Carlson natural-voice Sound Equipment.

1. AMPLIFIER, MODEL AR-37

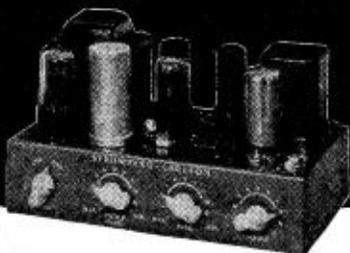

Two input jacks, one provides equalization network for crystal pick up, the other may be bridged across 500-600 ohm circuits without change in level. Treble attenuation and boost, base boost, base compensated volume control, separate gain control and fidelity control give the finest in record and wired music reproduction.

2. EXECUTIVE TELEPHONE, INTER-COM, MODEL 6240




Serving up to twenty-five private master stations, this telephone inter-com gives instant, reliable and private communication as well as providing for telephone conferences. Other systems available to fit your specific requirements.

3. AMPLIFIED INTER-COM, MODEL IM-514




In a cabinet of English Brown Mahogany with coffee brown trim, this unit is supplied with either seven or fourteen station push-buttons. Operating on AC or DC current, it has separate controls for incoming and outgoing volume and a telephone-type press-to-talk key. Remote stations are available in the same cabinet finish and with the same high quality Alnico V reproducer as the master station.

4. PORTABLE SOUND SYSTEM, MODEL PS-32

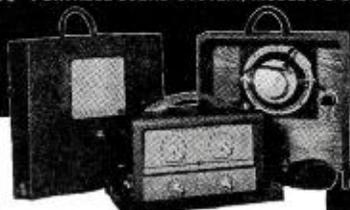

Portable system in a three-section, compact case. 15 watt amplifier with one phonograph and two microphone inputs, two heavy duty Alnico V reproducers, and 25 feet of durable cord with connectors attached. One case has the reproducer receptacle for connecting in cascade. Underwriters approved.

5. SOUND SYSTEM, MODEL SS-750

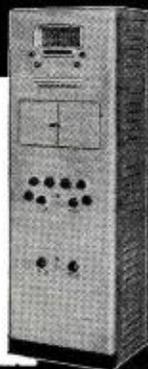

A completely pre-engineered system. Incorporates AM-FM radio tuner, record changer, controls, provision for wired music, and 90 watts of audio-power divided into four output circuits. Wired for optional remote control turret. Rugged all-metal cabinet with glacier-grey finish. Underwriters approved.

industry, having covered the entire United States and Canada as Field Sales Manager for the *Ferrocort Corporation*.

* * *

L. C. MCCARTHY of Chicago, well known radio sales representative, was recently elected to the board of directors of *Electronic Laboratories, Inc.*, of Indianapolis.



Mr. McCarthy's sales experience covers over 20 years in the radio business with the last fourteen years spent in Chicago representing *Electronic Laboratories, Inc.*

During the war he was general manager of the Canadian subsidiary of *Electronic Laboratories of Canada, Limited*, which was engaged in the production of specialized communications equipment.

* * *

RADIO MANUFACTURERS ASSOCIATION has recently initiated a new service for its member companies. Weekly reports are now issued from RMA headquarters for the benefit of set manufacturers and covering available surplus radio materials.

These new RMA surplus inventory reports were recommended by the Set Division, under Chairman Paul V. Galvin of Chicago, and authorized by the RMA Board of Directors.

To assist in inventory and production matters, RMA set manufacturers may report available surplus of parts, tubes, accessories, and other radio materials. These reports from the set manufacturers are then compiled and distributed weekly for the exchange or sale of surplus inventory between the RMA set companies.

* * *

LEO L. HELTERLINE, JR., was recently appointed Chief Engineer for *Sorensen & Company, Inc.*

Mr. Helterline has been with *Sorensen* since January, 1946 as senior project engineer. In his new capacity he will be responsible for the design and development of all company products which include voltage regulators, transformers, Nobatrons, and special electronic equipment.




Mr. Helterline is a graduate of Rensselaer Polytechnic Institute and prior to joining the *Sorensen* organization he was affiliated with *Sylvania Electric Products Inc.* as a quality control engineer doing test and liaison work on radar vacuum tube components.

* * *

RAYTHEON MANUFACTURING COMPANY'S new permanent sales headquarters for the Radio Receiving Tube Division are now located at 445 Lake Shore Drive, Chicago. All activities in connection with sales engineering, ad-

(Continued on page 176)

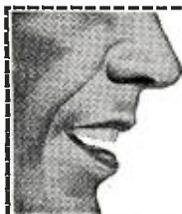

STROMBERG-CARLSON


NATURAL-VOICE



SOUND SYSTEMS



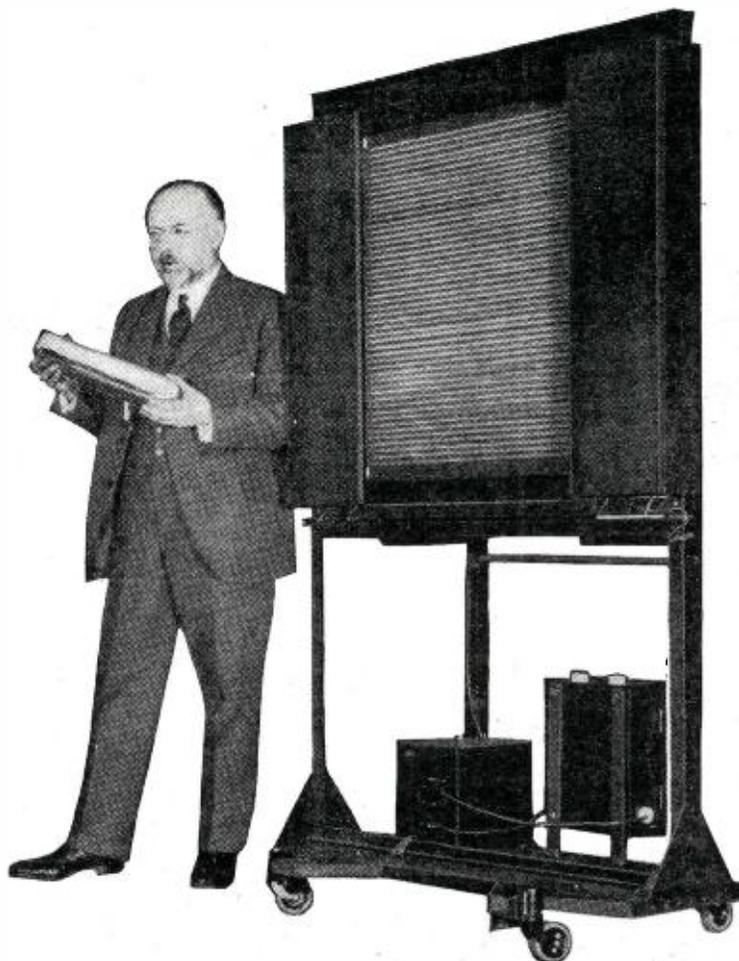Long-distance Television is twenty years old



At the 1927 demonstration, Dr. Herbert E. Ives explained the television system developed in Bell Telephone Laboratories.

APRIL 7 is a notable day in communication history, for on that day in 1927 was the first demonstration of television over long distances. Large-scale images were flashed from Washington, D.C., by wire and from Whippany, N.J., by radio to a public demonstration in New York City. "It was," said a newspaper, "as if a photograph had suddenly come to life and begun to smile, talk, nod its head and look this way and that."

That was the first of many public demonstrations, each to mark an advance in the television art. In 1929 came color television, and in 1930 a two-way system between the headquarters buildings of A. T. & T. and Bell Laboratories. When the first coaxial cable was installed

in 1937, television signals for 240-line pictures were transmitted between Philadelphia and New York and three years later 441-line signals were transmitted. By May, 1941, successful experiments had been made on an 800-mile circuit.

End of the war brought a heightened tempo of development. Early in 1946 began the regular experimental use of coaxial cable for television between New York and Washington, and a few months later a microwave system for television transmission was demonstrated in California.

Transmission facilities will keep pace as a great art advances to wide public usefulness.

BELL TELEPHONE LABORATORIES



SANGAMO METAL-CASED MINERAL-OIL PAPER CAPACITORS

TYPE 20
(Grounded)



TYPE 21
(Insulated)

STABLE
CAPACITY
FROM -55°C
TO $+85^{\circ}\text{C}$



MINERAL OIL
FILLED TO
ASSURE
LONGER LIFE



CREDENTIALS *that* **QUALIFY!**

EXCELLENT
BY-PASS AND
COUPLING
QUALITIES



AVAILABLE
WITHIN A
RANGE OF
200 to 2000 VOLTS
WORKING



TYPES 20 AND 21 AVAILABLE NOW FOR *IMMEDIATE DELIVERY*



CAPACITORS

SANGAMO CAPACITORS ARE NOW MANUFACTURED IN CANADA BY SANGAMO COMPANY LIMITED, LEASIDE, ONTARIO

SANGAMO ELECTRIC COMPANY • SPRINGFIELD, ILLINOIS

RADIO NEWS


Listen...IT'S A Jensen SPEAKER!




Model HNP-51
(15-inch)



Model JAP-60
(15-inch)

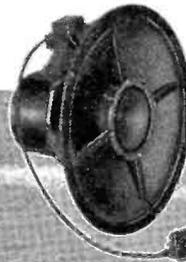

Model JHP-52
(15-inch)

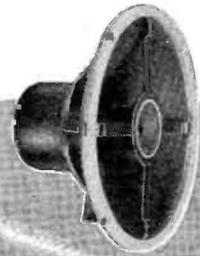

Model JCP-40
(12-inch)

JENSEN BASS REFLEX* REPRODUCERS with COAXIAL SPEAKERS

TYPE "RD"

REPRODUCER NO.	STOCK NO.	CABINET NO.	SPEAKER NO.	IMPEDANCE, OHMS	LIST PRICE
RD-122	ST-159	D-121	JCP-40	6-8	\$120.00
RD-151	ST-160	D-151	HNP-51	500-600	212.00
RD-152	ST-161	D-151	JAP-60	500-600	164.00
RD-153	ST-162	D-151	JHP-52	500-600	151.00

TYPE "RA"

RA-124	ST-134	A-121	JCP-40	6-8	\$ 76.45
RA-151	ST-136	A-151	HNP-51	500-600	177.40
RA-153	ST-138	A-151	JAP-60	500-600	128.90
RA-154	ST-139	A-151	JHP-52	500-600	115.90

JENSEN BASS REFLEX* CABINETS

TYPE "D"

MODEL NO.	STOCK NO.	SPEAKER SIZE	DIMENSIONS			LIST PRICE
			HEIGHT	WIDTH	DEPTH	
D-121	ST-156	12"	27 $\frac{7}{8}$ "	31 $\frac{3}{8}$ "	13 $\frac{3}{8}$ "	\$75.00
D-151	ST-157	15"	27 $\frac{7}{8}$ "	31 $\frac{3}{8}$ "	13 $\frac{3}{8}$ "	75.00

TYPE "A" (Finished)

A- 81	ST-123	8"	24"	18"	9 $\frac{1}{4}$ "	\$24.55
A-121	ST-124	12"	27"	24 $\frac{3}{4}$ "	13 $\frac{1}{2}$ "	34.05
A-151	ST-125	15"	32 $\frac{3}{8}$ "	27 $\frac{3}{8}$ "	13 $\frac{1}{2}$ "	42.15

TYPE "A" (Unfinished)

A- 82	ST-145	8"	24"	18"	9 $\frac{1}{4}$ "	\$24.55
A-122	ST-146	12"	27"	24 $\frac{3}{4}$ "	13 $\frac{1}{2}$ "	34.05
A-152	ST-147	15"	32 $\frac{3}{8}$ "	27 $\frac{3}{8}$ "	13 $\frac{1}{2}$ "	42.15

*Designers and Manufacturers
of Fine Acoustic Equipment*

JENSEN MANUFACTURING COMPANY
6617 SOUTH LARAMIE AVE., CHICAGO 38, U. S. A.
IN CANADA: Copper Wire Products Ltd., 11 King St. W., Toronto, Ont.
*Trade Mark Registered




Jensen
SPEAKERS
WITH **ALNICO 5**

SUN'S GREATEST OFFER!

WHILE THEY LAST!

CHECK THESE VALUES

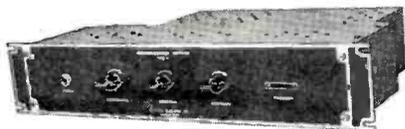

SUPERHETERODYNE RECEIVER

This crystal fixed frequency receiver comes with full conversion instructions for variable tuning of all ham bands and broadcast. A highly selective superheterodyne receiver, 110 V. A.C. power supply built in. Using the following tubes: 6K7-RF Amplifier; 6K8-Mixer and Oscillator; 6K7-L.F. Amplifier; 6F7-Detector and A.V.C.; 6CB-Output and Noise Suppressor; 80-Rectifier. Dimensions 3 1/2 x 19 x 11 1/2 inches. Comes complete, Brand New, with one set of coils and two sets of

tubes..... **\$16.95**
Extra set of coils..... **\$2.95**

BENDIX TRANSMITTER

\$49.95



Three 807 tubes; Four 12SK7; One 2-inch 5 amp. RF meter; Four Separate Master oscillators. (These can be easily changed to cover 20-40-80 meters and by using crystal for the 10 meter band you will have a complete coverage transmitter.) Four Separate output tanks; One 4 Position selector channel switch having seven sections which changes the ECO, IPA and output tanks simultaneously. All the controls are mounted on the front panel. The housing is cast aluminum; shields and case are sheet aluminum. Dimensions 11x12x15 inches, weighing 35 1/4 lbs. Complete, simple instructions for conversion furnished.

BRAND-NEW—Complete with tubes..... **\$49.95**



BC-684 F.M. 35 WATT TRANSMITTER

Brand new, complete with eight tubes, crystal control, 10 channel pushbutton, non-lentier modulation coil... less coverplate, crystal and power supply.... **\$17.95**



NAVY V.H.F. RADIO TRANSMITTER

Brand New
Battery operated (67 1/2 V.B. and 1 1/2 V.A.). Frequency 80 to 105 M.C. Complete with 2-1G4 tubes and full instruction manual..... **\$6.95**



NAVY SPEAKER

Stromberg Carlson and RCA waterproof speakers. Brand New in original cartons. 25 Watt PM driver unit with line matching transformer and projector mounted in heavy duty round metal baffle. Ideal for communication receivers and sound systems at lowest price ever offered.

\$14.95

• All items F.O.B. Washington, D. C. Orders \$30.00 or less, cash with order. Above \$30.00, 25 percent with order, balance C.O.D.

SUN RADIO

OF WASHINGTON, D. C.

938 F STREET, N. W. WASH. 4, D. C.

War Surplus Equipment!..

AT A FRACTION OF THEIR ORIGINAL GOVERNMENT COST



R.F. TUNING UNITS

Beautiful black crackled aluminum cabinet with two variable transmitting condensers and two vernier dials, one heavy duty ceramic four position wafer switch, mica condensers, 2,500 working volts and coils wound on porcelain ribbed forms. Available TU5B (1500-3000kc), TU75 (4500-6200), TU8B (6200-7700kc), TU9B (7700-10,000kc) and TU10B (10,000-12,500kc). Please specify model..... **\$3.89**



AUTOMATIC RECORD PLAYER

Including Webster No. 50 changer, three tube amplifier, 5" Alnico V speaker in a deluxe leatherette case. List..... **\$57.50**
YOUR cost..... **\$36.75**
Lots of six..... **\$34.50**



INTER-COM AMPLIFIER

Comes completely wired in aluminum cabinet with following: 2—12A6, 2—12J5 tubes, 1 bathtub condenser, 3 can filters, 12 precision resistors, 4 low loss octal sockets, shielded input and output transformers, 2 shielded R.F. chokes, 1 S.P.S.T. toggle, 28v D.C. dynamotor. Sun Radio furnishes the instructions for easy conversion to Hi-Fidelity phono or speech amplifier..... **\$8.95**

BRAND NEW RADIO TUBES SAVE UP TO 80% AT SUN RADIO ON

ALL STANDARD BRAND TUBES

No.	Price	No.	Price	No.	Price
0Z4	\$.132	6B7	\$1.00	12CB	\$1.59
1A5GT	.90	6B8	1.50	12F5GT	.81
1A7GT	1.08	6BA6	1.08	12G6GT	.90
1B5/255	1.08	6BE6	1.08	12J5GT	.81
1C5GT	1.08	6BF6	.90	12J7GT	.90
1C6	1.08	6C5	.80	12K7GT	.81
1E5GP	1.32	6C7	.57	12K8	1.32
1E7G	1.92	6D6	.80	12SA7GT	1.00
1F5G	1.08	6D7	1.08	12SC7	1.00
1F6	1.32	6D8G	1.32	12SF7	1.08
1G4GT	1.08	6E5	.90	12SG7	1.08
1G5G	1.08	6E6	.90	12SH7	1.08
1G6GT	1.32	6F6	.90	12SJ7GT	.90
1H4G	1.08	6F7	1.32	12SKGT	1.30
1H5GT	1.08	6F8G	1.00	12SL7GT	1.32
1M6G	1.08	6G6G	1.00	12SN7GT	1.08
1J5G	1.59	6H6	.75	12SQGT	.90
1J6G	1.08	6I5	.75	12SR7	.90
1LA4	1.92	6J6	1.59	12T3	.81
1LC6	1.92	6J7	1.08	14A7/12B7	1.30
1LB4	1.92	6K6	.80	14G6	1.32
1LH4	1.92	6K7	.90	14H7	1.32
1LL5	1.92	6L5G	.90	14I7	1.08
1M5GT	1.08	6L6	1.50	25L6GT	.90
1Q5GT	1.32	6L7	1.32	25P6GT	.81
1R5	1.25	6N7	1.32	26	.63
1S4	1.25	6P7	1.08	30	.57
1S5	1.25	6R7	1.32	30	.81
1T4	1.25	6SA7	.80	31	.81
1T5GT	1.32	6SA7GT	.90	12L7GT	1.59
1V	.81	6SB7-Y	1.59	35	.81
2A6	.81	6SC7	1.00	35L6GT	.81
2B7	.75	6SF5	1.70	38W4	.69
2E5	1.08	6SF7	1.08	35Z3	1.08
3A8CT	1.59	6SG7	1.08	35Z4GT	.69
3Q5GT	1.32	6SH7	1.90	35Z5GT	.69
3S4	1.25	6SJ7GT	.75	36	.81
5T4	1.50	6SK7	.80	37	.69
5U4G	.81	6SL7GT	1.10	38	.90
5V4G	1.32	6SN7GT	.90	39/44	.75
5W4	.90	6SQ7	.80	41	.69
5X4G	.90	6SR7	1.80	45	.66
6Y3GT	.57	6SS7	.80	45Z3	.90
5Y4G	.63	6US/6G5	1.08	46	.90
SZ3	.90	6U7G	.81	50A5	1.50
6Z4	1.20	6V6	1.35	50B5	1.08
6A4	1.32	6W7G	1.10	50L6GT	.90
6A6	1.25	6X5GT	1.10	55	.50
6A8	1.08	6Y6G	1.10	56	.66
6A8S/6N51	1.32	6Y7	1.08	59	1.32
6AB7/1853	1.50	6Y7G	1.08	75	.69
6AC5GT	.90	6Z5G	.90	75	.75
6AC7/1852	1.50	7A4	1.00	77	.75
6AD6	1.08	7A5	1.00	78	.44
6AD7	1.32	7A7	1.00	79	.75
6AD7G	1.32	7C7	1.08	80	.57
6A8GT	1.08	7E6	1.08	85	.75
6A8GT	1.08	7E7	1.08	85	.50
6A6G	1.08	7F7	1.32	117L7GT	1.32
6AF6G	1.32	7H7	1.30	117M7GT	1.32
6AG5	1.92	7J7	1.50	127	1.08
6AG7	1.92	7J7	1.32	117Z6GT	1.32
6AK6	1.32	7Q7	1.08	XXB	1.32
6AL5	1.08	7R7	1.08	XXFM	1.32
6AQ5	1.08	12A5	.90	VR-90/30	1.92
6AQ5	1.08	12A6	1.32	VR-105/30	1.92
6AT6	.90	12BGT	1.32	VR-150/30	1.92
6AU6	1.08	12AH7GT	1.32	182B	1.92
6B4G	1.30	12AT6	.90	485	1.92
6B4G	1.30	12BA6	1.08	151	.50
6B6G	.90	12BE6	1.08	2051	1.00

**Prepare
NOW**

for a Better Job in RADIO ENGINEERING



**Don't Delay—
Write Today!**

In This New World of Electronics Better Training Means Better Opportunities!

TODAY, the new war-developed techniques offer greater opportunities than ever existed in the early days of broadcasting! Micro-Wave Relay Systems, Television, FM Broadcasting, Mobile Communication Systems for Trains, Automobiles, Busses, Trucks, many Industrial Applications—these are just a few of the new techniques which offer marvelous, exciting opportunities to you who are alert—and are qualified!

Let Cleveland Institute Take Over Your Personal Up-Grading Problem! Qualified, competent instructors, ample, personalized instructional aids, orderly, progressively arranged study assignments in recognized, approved technical texts—these are only a few of the many superior advantages of CIRE's plan of personalized spare-time home study training for professional self-improvement.

CLEVELAND INSTITUTE COURSES OFFER COMPLETE TECHNICAL TRAINING RANGING FROM LOW-LEVEL TO COLLEGE-LEVEL.

- A. Master Course in Radio Communication.** Covers complete preparation for broadcast station employment including preparation for FCC License Examinations.
- B. Advanced Course in Radio Communication Engineering.** A college-level Radio Engineering Course.
- C. Specialized Television Engineering.** Including post-war Television Techniques.

All Courses Include

The Remarkable Workbooks of Instructional Aids, prepared by the instructing staff of Cleveland Institute. Choose the course best suited to your needs—Start with the section you are qualified to enter—Use the economical CIRE "Pay-As-You-Go-Plan."

ENROLL FOR INDIVIDUAL SECTIONS OF COURSES, IF YOU PREFER.

If you need only highly specialized training, you can study one or more of the following sections instead of a complete course.

1. Mathematics of Radio.
2. Fundamentals of DC and AC Theory.
3. Essentials of Radio Communication.
4. Communication Networks.
5. Advanced Radio Telephony for the Broadcast Operator.
6. Audio and Radio Components and Systems (Design of Receiver and Transmitter Equipment)

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

Contractors to the Canadian Broadcasting Corporation

RN-5 Terminal Tower
CLEVELAND 13, OHIO

Approved for Training under "G-I Bill of Rights"

(MAIL THIS COUPON)

Cleveland Institute of Radio Electronics, RN-5, Terminal Tower, Cleveland 13, Ohio.
Gentlemen: Please send information about your home courses in Radio Electronics.

I desire training in A B C

I have had experience in broadcasting servicing
operating mfg. CAA Army-Navy
amateur other I am a
High School Grad. College Degree ...
 Check here for Veteran Enrollment Information.

NAME
ADDRESS
CITY
ZONE STATE



Get your

FCC Commercial Radio Operators' LICENSE NOW!

IT'S EASY IF YOU FOLLOW OUR PLAN!

Thousands of new jobs are opening up—FM, TELEVISION, MOBILE COMMUNICATIONS SYSTEMS, are only a few of the radio fields which require licensed operators.

TIME IS IMPORTANT TO YOU!

You can get your License quickly with NILSON'S MASTER COURSE in RADIO COMMUNICATION and exclusive CIRE Workbooks of Instructional Aids. Saves you many hours or random, undirected study.

Assures a MINIMUM of time in getting your ticket.

FREE BOOKLET tells you the Government Requirements for all classes of commercial licenses—Sent immediately upon receipt of coupon.

**Don't Delay—
Write Today!**

Approved for Veteran Training under "G-I Bill of Rights"

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

Contractors to the Canadian Broadcasting Corporation

RN-5 Terminal Tower
CLEVELAND 13, OHIO


MAIL THIS COUPON

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
RN-5 Terminal Tower, Cleveland 13, Ohio

Gentlemen: Please send information about your Home Study Course for preparation for FCC Commercial License Examinations (this course does not cover amateur license examinations).


Name.....
Address.....
City..... Zone..... State.....
 If a Veteran check here

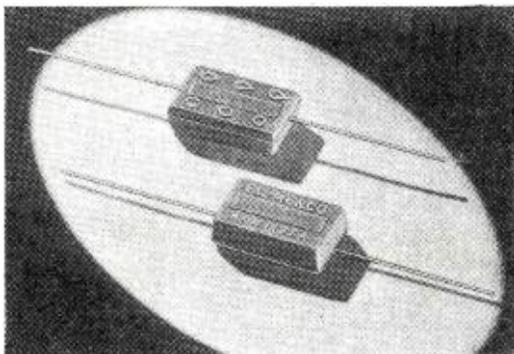For Dependable Performance . . .
 Choose Time-Tested
El-Menco CAPACITORS AND FUSED PLUGS




MOLDED MICA CAPACITORS

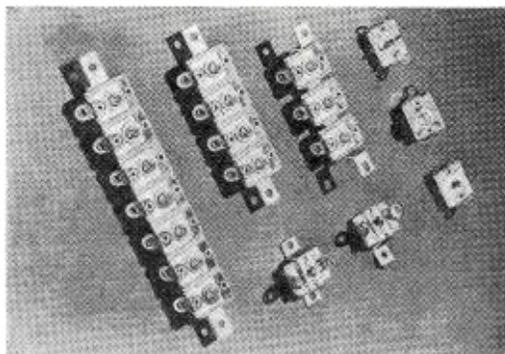Compact, precision made, fixed mica dielectric capacitors. Made in accordance with American military standards to meet Army and Navy JAN-C-5 specifications. All impregnated and JAN-C-5 color coded.




MICA TRIMMER CAPACITORS

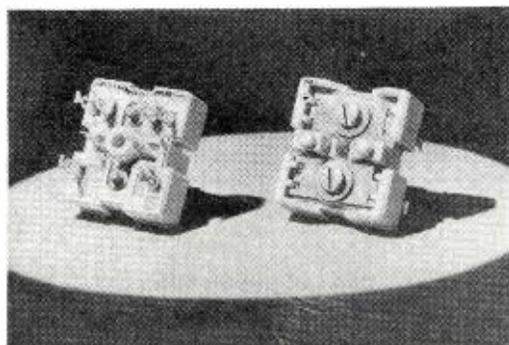Clear India ruby mica. Base made of low-loss ceramic materials. Treated for humidity resistance and permanence of capacity setting. Adjusting screw advances 1/64" for one complete rotation, thus insuring accurate adjustment of capacity setting.



PADDERS

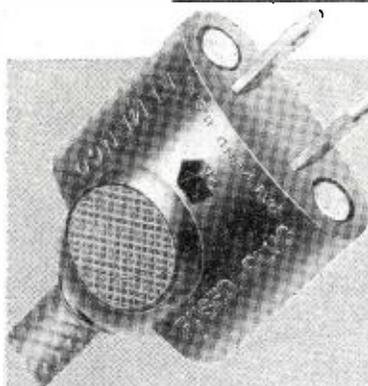Completely enclosed construction protects delicate edges of the clear India ruby mica films. Phosphor bronze adjusting plates assure permanent resilience and freedom from mechanical fatigue. All parts heavily plated to resist corrosion.



THE REVOLUTIONARY El-Menco Fused Plug
THE ONLY PLUG
THAT CARRIES ITS OWN FUSES

Provides complete protection against damage to product and main line. Contains two small fuses that are easily removed and replaced. Molded finger grips. Attaches to cord like any standard plug. Replacement fuses available in all amperages. Specify on equipment of all voltages up to 250 and currents up to 8 amperes. Approved by Underwriters Laboratories.

**ALL EL-MENCO PRODUCTS AVAILABLE
 FOR IMMEDIATE DELIVERY FROM STOCK**

ATTENTION JOBBERS!

A few valuable territories are still open. Contact Arco Electronics for information.

ARCO
ELECTRONICS Inc.

135 LIBERTY STREET

NEW YORK, N. Y.

SOLE DISTRIBUTOR FOR U.S. AND CANADA


Littlefuses for Immediate Delivery

3 AG up to 8 amps.

3 AB up to 15 amps.

YOU BUY PERFORMANCE IN THE HQ-129-X

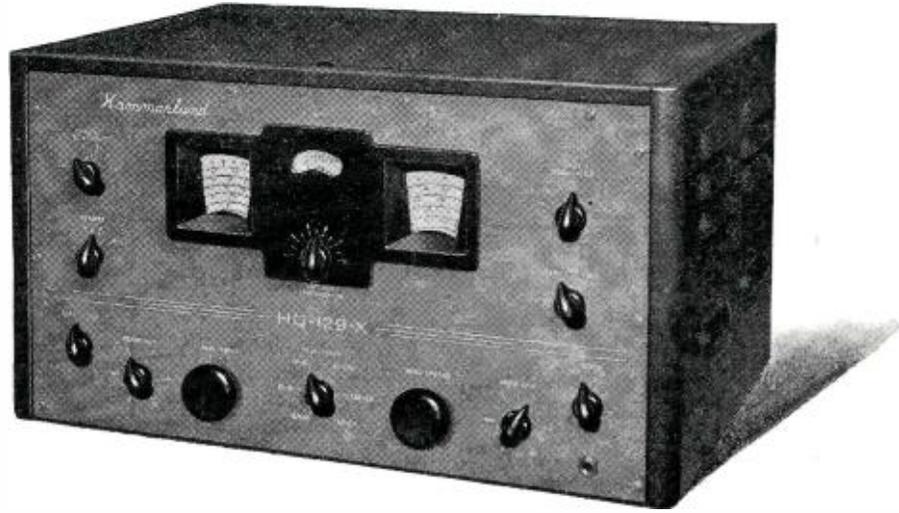Pull the weak ones out of the QRM—Tune in a "ZL" and hold on to him—Turn on the noise limiter and really kill ignition noise—That is what thousands of hams are doing every day with the HQ-129-X



36
BACKED BY

YEARS OF KNOW HOW


see
the HQ-129-X
at your dealer's



HAMMARLUND
THE HAMMARLUND MFG. CO., INC., 460 W. 34TH ST., NEW YORK 1, N.Y.
MANUFACTURERS OF PRECISION COMMUNICATIONS EQUIPMENT

*Come and See One of the
World's Largest Displays of
Radio-Electric Components*

**PARTS SHOW
VISITORS
WELCOME!**

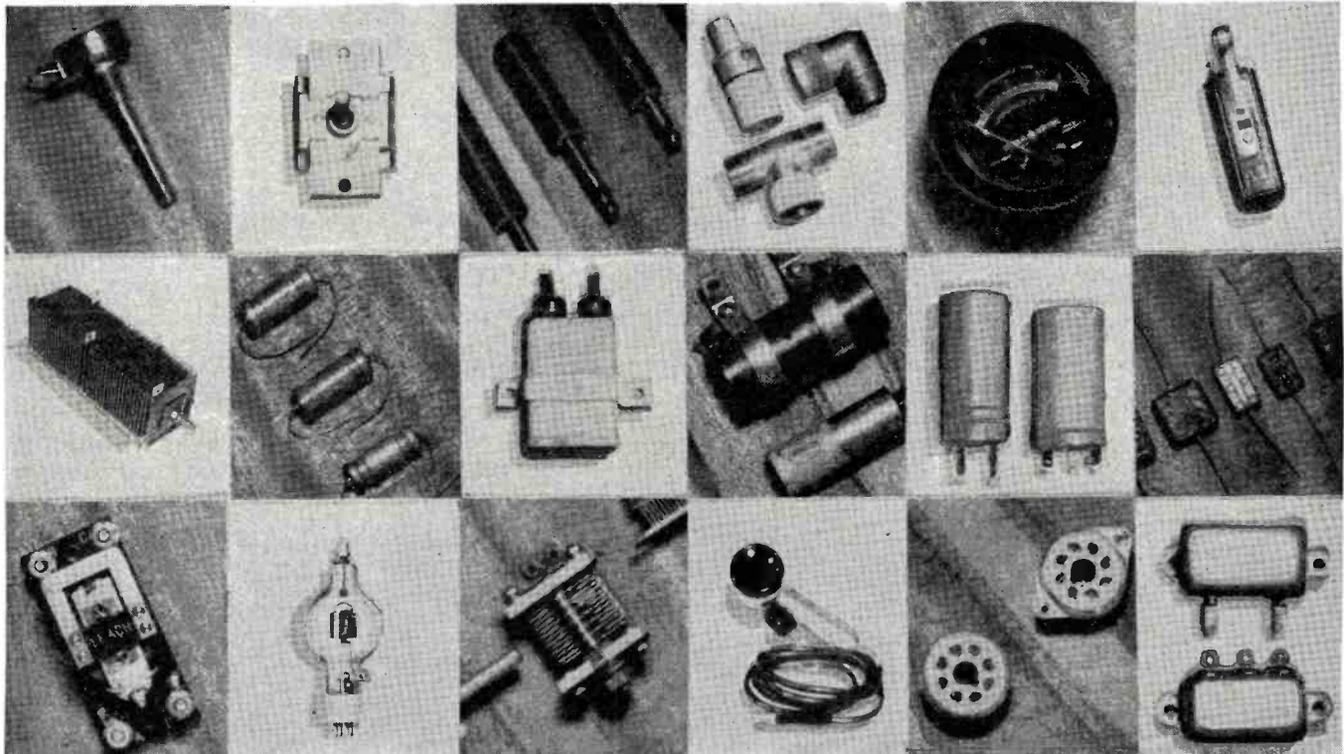

A National Service

For those who are unable to visit Chicago, Wells maintains a complete catalog service covering every item in our huge inventory. Catalogs or descriptive lists are now available in the following categories: Relays, Volume Controls, Micro Switches, Phone Jacks and Plugs, Transmitting Tubes, Condensers, Transformers, Resistors, Jones Strips, Wafer Switches, Radio Amateur Equipment, Dry Disc Rectifiers, Wire, and Coax Connectors. Send for your copies today.

Wells Moves to Convenient New Location


Thousands of types of radio-electric parts and equipment have been assembled in one tremendous display area located within easy walking distance of Chicago's Loop. Manufacturers, distributors and radio amateurs are cordially invited to see this extraordinary selection of the best of Government contract termination components. Everything is priced at a fraction of the original cost and is backed by the substantial Wells guarantee.



Distributors: Write for the Wells Jobber Manual

320 N. LA SALLE ST. DEPT. R-5, CHICAGO 10, ILL.

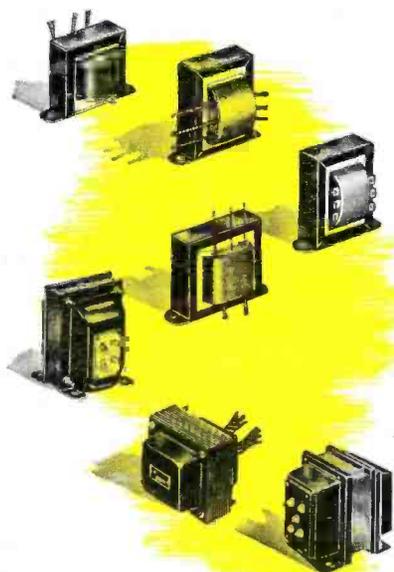when you order a
STANCOR product
 you order the
FINEST



The big black-and-yellow STANCOR catalog is the logical place for the radio serviceman to turn for a transformer to meet any standard need. . . . For there you will find the most complete selection of Replacement and General Purpose Transformers. . . . And there you'll find the FINEST. . . . For the most exacting quality is built into every STANCOR product. . . . Quality plus advanced design and universal application. . . . Yes, reach for the well-thumbed STANCOR catalog . . . for behind it are STANCOR's new streamlined plant facilities to give you better products and better service . . . to help you give your customers complete and lasting satisfaction.

standardize on

STANCOR



TRANSFORMERS

new

 **PYRAMID**
"twist-mount"
ELECTROLYTIC
CAPACITORS



Here's the latest addition to
the Pyramid family—an
ultra-compact, high quality,
metal-sealed, easy-to-mount capacitor!


Pyramid Type TM units are
available in a wide range
of capacity and voltage ratings,
for every application.

And, like all other Pyramid
capacitors, they're modestly priced!

W R I T E F O R L I T E R A T U R E

PYRAMID
ELECTRIC COMPANY

JERSEY CITY 6, N. J.

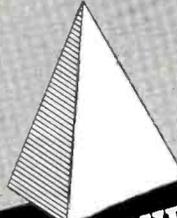
PYRAMID
"LONG-LIFE"
Dry Electrolytic
Capacitors



This truck driver is receiving instructions for his next assignment. Thus the new mobile telephone service will enable commercial vehicles to operate with increased efficiency and economy. The control unit mounted conveniently under the dashboard holds the telephone handset and contains the bell and signaling light. This service makes possible calls between any regular telephone and the telephone in the vehicle.

Mobile Radio-Telephone Service Links Nation

By FRANK E. BUTLER

Mobile radiotelephone service is now being provided to subscribers. This relatively new "Bell" system provides 2030 selective signaling combinations.

THE act of "calling" or "receiving" a mobile radiotelephone call is no more complex or difficult than performing the same operation with a regular wire line telephone. Transmission standards are equal to wire line service and no tricky operating procedure or "tuning" is necessary.

This new service, which combines regular wire telephone operation with shortwave radio is remarkably clear and free from "dead spots," fading or static. This perfection is obtained by using frequency modulation to bridge the gap between the regular wire telephone channels and the specially equipped vehicles. Two bands are allocated for this service. One operates in the 152-162 megacycle band and its counterpart operates in the 30-44 megacycle band.

Complete equipment on the vehicle consists of a radio receiver and transmitter, an 18 inch stand antenna, a selective signaling device and a telephone instrument. All controls and the cradle telephone are conveniently mounted under the instrument board of the car in a single unobstructive unit. On the left of the control panel is a small lamp which lights to in-

dicating an incoming call. A regulation bell signal is also used.

However, the bell stops ringing after a short interval but the lamp remains lighted until the driver acknowledges the call. Thus by having the lamp signal "lock in" the driver is notified that he had been called during his absence from the car.

Centered on the front panel is the main "On-Off" switch. With the switch in the "On" position, the receiver is in operating condition, ready to receive a call while the transmitter is in a standby condition. The transmitter is ready to operate when the handset is removed from the cradle, and operates when the "push-to-talk" button in the center of the handset is depressed. To the right of the switch is a lamp which indicates the power is on. The control weighs less than 8 pounds, including the handset. A retractile cord is used to prevent any fouling or tangling that might occur with a regular handset cord. The ringing bell is mounted inside the control unit.

Unique with the *Western Electric* equipment is a selective signaling device, incorporated as an integral part of the receiver. It is the "heart" of the mobile radiotelephone unit. This

selector and its associated filters and relays provide full selective signaling with 2030 combinations available. Each radio channel will serve a number of mobile stations. Each mobile installation is assigned a five digit number prefixed by a channel designation of two letters. Because the number "1" is used as a selector "return to normal" pulse, the station number never includes the digit "one." The selector is designed so that the total of the five digits add up to "23." As an example: "WJ6-2834" . . . WJ, is the channel designation and 62834 the mobile radiotelephone station number.

When a call comes in to the mobile telephone traffic operator she dials the digits for this particular station. In so doing, she causes the control terminal equipment to modulate the land transmitter with a series of pulses of 600 and 1500 cycles. These pulses, received and amplified at the mobile stations, cause all selector sets assigned to the same channel to be actuated. Stop pins in the cog wheel of the selector in the receiver called will cause only that selector to be positioned to ring a bell and light a call lamp in the vehicle. All other selectors will fail to reach the final or signaling operation.

Operation of mobile telephone service is very simple. All calls are handled by special mobile service operators at a central office. It is only necessary to give central the telephone number wanted, such as . . . "WJ6-2834." This numbering, by the way,

	HIGHWAY	URBAN
1. Frequency range (Transmitting) (Receiving)	42-44 mc. 30-40 mc.	152-162 mc. 152-162 mc.
2. Max. frequency tolerance (-20 to + 55 deg. C.)	.01%	.005%
3. Type of modulation	Phase	Phase
4. Predistortion (FM characteristic)	6 db./octave	6 db./octave
5. 100% modulation swing	±12kc., (±7.4 radians)	±15kc., (±10 radians)
6. Audio band transmitted	300-3000 c.p.s.	300-3000 c.p.s.
7. Max. radio bandwidth	40 kc.	60 kc.
8. Output power	20-40 watts	15-35 watts
9. Max. transmitter spurious radiation	70 db. below carrier	70 db. below carrier
10. Max. residual transmitter noise modulation	The measured residual transmitter noise should be 47 db. below the level of a 1000 c.p.s. sine wave tone which modulates the transmitter the full radian swing. The noise should be measured in a manner which takes into account its interfering effect on a telephone circuit.	
11. Receiver sensitivity limiter effectiveness Signal input for complete limiting	30 db. 5 μv.	30 db. 5 μv.
12. Receiver acceptance band	± 10 to ± 15 kc.	± 20 to ± 25 kc.
13. Receiver suppression	85 db. adjacent to midchannel -70 db.	85 db. adjacent to midchannel -70 db.
14. Receiver spurious response		
15. Max. squelch sensitivity (adj. inside equipment over 25 db. range)	1 μv.	1 μv.
16. Receiver noise figure	12 db.	8 db.
17. Max. residual receiver noise	The measured residual receiver noise (car engine operating) should be at least 50 db. below the level of a 1000 c.p.s. sine wave tone which modulates the test radio frequency signal the full radian swing.	
18. Radio receiver de-emphasis (FM characteristic)	6 db./octave	6 db./octave
19. Receiver output power (250 mw. required for operation of selector set—10 mw. for handset)	250 mw.	250 mw.
20. Audio characteristics with 100% modulation of transmitters or receivers	1000 c.p.s. reference; 250 c.p.s. 0 to -4 db.; 500 to 2000 c.p.s. 0 to -3 db.; 2000 to 3200 c.p.s. 0 to -4 db. Characteristics specified in terms of departure from the ideal 6 db./octave transmitter pre-emphasis or receiver de-emphasis.	
21. Selective signaling	The selector set must respond to the two-tone audio frequency signaling code transmitted by the land station. The transmitted code consists of a series of pulses of two tones, 600 and 1500 c.p.s. which are transmitted alternately at a uniform rate of 8 to 11 per second. The tones are transmitted successively without interruption, and all pulses are of equal length (.09 to .125 sec.). The local signal circuits associated with the selector set should provide a bell of suitable audibility and a lock-in lamp signal. The bell circuit should be arranged to remain operated (bell ringing) as long as the selector contact is closed. The lamp circuit should operate when the selector contact closes and remain operated (lamp lighted) until the local circuit is restored by the operation of a release button or contact. Full operation within 300 milliseconds after push-to-talk button is depressed.	
22. Transmitter warmup	6-12 volts	6-12 volts
23. Nominal battery voltages		
24. Ambient temperature	Satisfactory operation with ambient temperatures ranging between -40 and +65 degrees C.	
25. Voice frequency control unit	Bell System installations should include push-to-talk handset, equipped with a carbon-button type transmitter unit and a telephone type receiver unit having a 5 foot conductor cord. The frequency characteristics of the handset should be such as to utilize efficiently the voice frequency band specified above.	

does not conflict with any existing central code of the entire wire telephone system.

The mobile operator then checks channel "WJ" to determine whether it is in use. If the channel is idle the mobile service operator inserts a dial cord and dials "62834." The mobile station bell rings and the driver answers and talks. The mobile service cord circuit supervisory lamp is extinguished. The operator starts timing the ticket covering that particular call.

At the termination of the call, the supervisory lamp at the switchboard lights. The mobile service operator releases the channel and enters the time of the call on the ticket. The channel is now ready for the next call.

A call from the automobile to a wire-line subscriber is just as easily completed. The driver removes the handset from the control unit and "monitors," i.e., listens to check that the channel is not in use. This consumes about three seconds of time. If the channel is idle, the driver presses the "push-to-talk" button on the handset. The line lamp at the mobile service switchboard position lights. The mobile service operator answers, and asks for called number. The mobile service operator completes the call in the same manner as for wire line subscribers. As before, the cord supervisory lamp gives a continuous indication of the progress of the call.


The receiver and transmitter are housed in separate cases which can be easily carried in the luggage compartment of a passenger automobile. The transmitter with its 20 watt output is capable of providing reliable service in the area served, which is approximately 25 to 30 miles. A special dynamotor powered by 6 or 12 volts, depending on the vehicle in which the radiotelephone is installed, is used to operate the equipment.

Quartz plate crystal control of the transmitter frequency is provided, with a thermostatically controlled, constant temperature oven enclosing the quartz plate. Temperature control insures operation of the transmitter on its proper frequency.

The radio frequency carrier is modulated by a phase modulation circuit, resulting in excellent voice quality transmission with an extremely low noise level. Maximum deviation plus frequency tolerance of the carrier under speech modulation is normally a swing of plus or minus 15 kilocycles. The modulation circuit requires no adjustment, and only one vacuum tube is used.

Spurious radiation, that is, radiation of signals on other than the assigned frequency, is well below what is normally expected with mobile transmitters. An unusual double tuned circuit in the first doubler stage accounts for the absence of undesirable radiation.

Table 1. Technical characteristics of mobile equipment recommended for Bell System general mobile radiotelephone service.

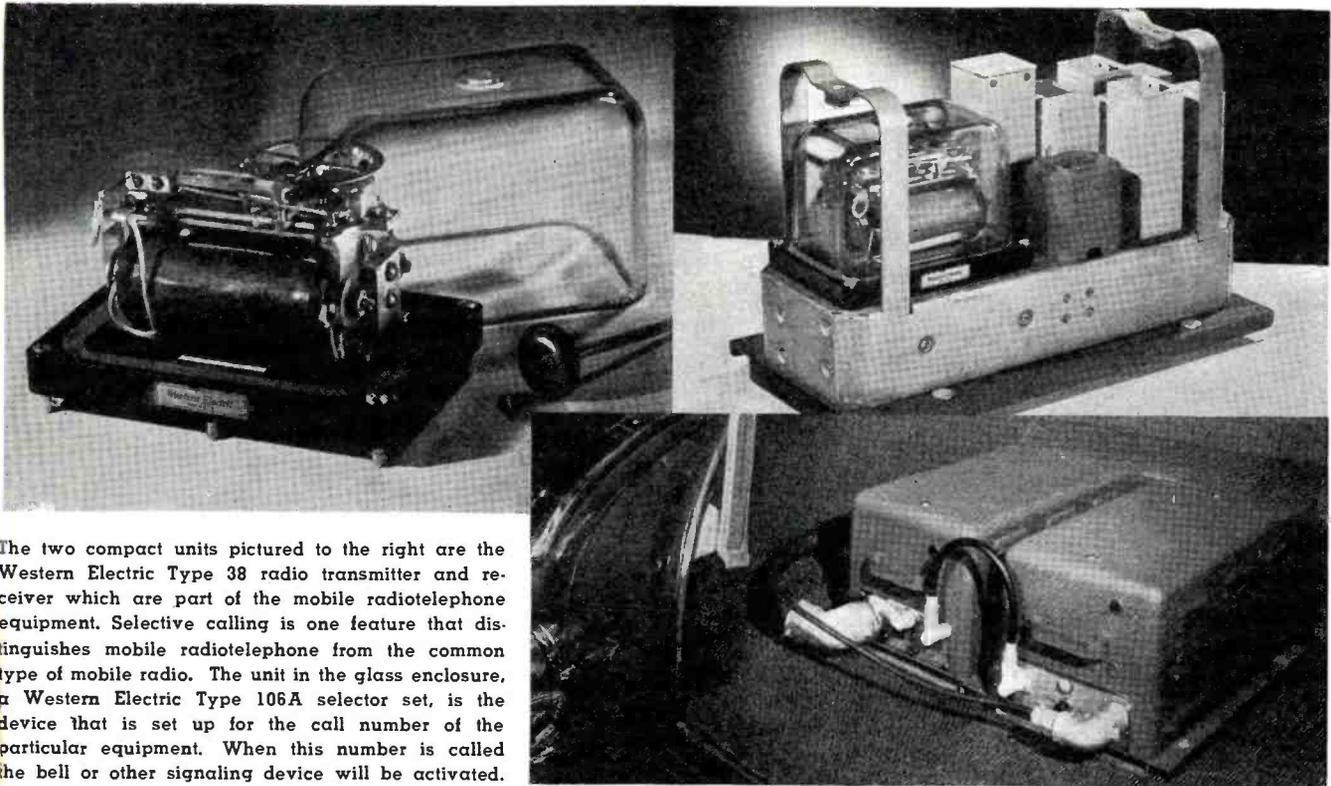

The two compact units pictured to the right are the Western Electric Type 38 radio transmitter and receiver which are part of the mobile radiotelephone equipment. Selective calling is one feature that distinguishes mobile radiotelephone from the common type of mobile radio. The unit in the glass enclosure, a Western Electric Type 106A selector set, is the device that is set up for the call number of the particular equipment. When this number is called the bell or other signaling device will be activated.

The receiver is a sensitive, triple detection superheterodyne type. It is fixed tuned, with quartz plate control or both conversion oscillators. Triple detection is a modification of the usual superheterodyne, and incorporates two converters and two intermediate frequencies. The great advantage of triple detection lies in its effective image suppression with no loss in selectivity. Images in superheterodyne receivers are spurious responses to signals separated from the frequency to which the receiver is tuned by twice the intermediate frequency. Further image rejection, along with added sensitivity, is gained by having a tuned radio frequency amplifier ahead of the first converter stage.

A non-synchronous vibrator is used in the power supply circuit. The advantage gained by using this type of vibrator is that no concern need be given as to whether the positive or negative side of the vehicle battery is grounded.

The intermediate frequency stages are designed to have bandpass characteristics that provide an unusual degree of selectivity. The audio frequency response of the receiver is flat in the voice frequency range with the resultant faithful reproduction of the speaker's voice. With less than a microvolt input to the receiver the signal-to-noise ratio is about plus 25 db. During the period when the voice circuit is in use, negative feedback is introduced, further providing for a high degree of distortionless reception. The selective signaling device incorporated in the receiver requires slightly more output power than is available when the feedback circuit is operative. Consequently when the

handset is not in use, i.e., when it is in the cradle, the feedback circuit is disconnected, thus providing additional power to operate the selector.

A frequency modulation type of squelch is used to make the audio circuit operative whenever a usable signal is received. An outstanding feature of the squelch circuit is that selected noise is amplified to bias the audio circuit to cut-off, reducing the possibility of anything but the desired radio frequency carrier opening the squelch and making the audio circuit operative. Such an arrangement greatly reduces the possibility of false operation of the selective signaling equipment by noise.

Two types of radiotelephone service are currently in service and supply both urban and highway service. Urban mobile radiotelephone service extends telephone service, not only to motor vehicles but to other mobile units, such as harbor craft, operating in a city or metropolitan area, the extent of coverage being determined by the needs of the subscribers.

A system of this kind requires a fixed plant comprising one or more land radio transmitters at locations which are favorable from the standpoint of radio transmission coverage, and a number of strategically located land radio receivers, all connected by wire lines to a centrally located control terminal and the telephone switchboard. Completing the system are the mobile radio transmitters, receivers, and signaling units of the motor vehicles and water craft equipped for radiotelephone communication with the land equipment.

In most cities, a single land radio transmitter for each frequency chan-

nel will suffice. Some of the larger cities may require two. Experience has indicated that little if any trouble will be experienced as a result of interference where more than one land transmitter is operated on the same frequency.

Radio frequencies allocated to urban radiotelephone service by the Federal Communications Commission are in the 152 to 162 megacycle band (See Table 1). At these frequencies radio waves are propagated over substantially line-of-sight paths between the transmitter and receiver. Therefore, the location of the land transmitter and receiver antennas greatly affects the coverage obtained. The antennas ordinarily will be the simple vertical half-wave coaxial type, the supporting structure being determined in each case by the height required and local mounting conditions. The vehicle or water craft antenna will be a simple quarter-wave vertical whip in most cases.

Vehicle transmitters are limited to relatively low power because of space and primary power available. Antenna heights are also restricted, so the range of transmission from the vehicle transmitter may be considerably less than that from the land transmitter. This makes it necessary to provide additional land station receivers at strategic locations.

High power is required in the land transmitter because of the antenna and power supply restrictions of the vehicle receiver and because of the presence of local radio-frequency noise. More than one land transmitter per channel may be necessary for a large area or for an area in which

(Continued on page 108)

Simple Two-Tube HAM SUPER

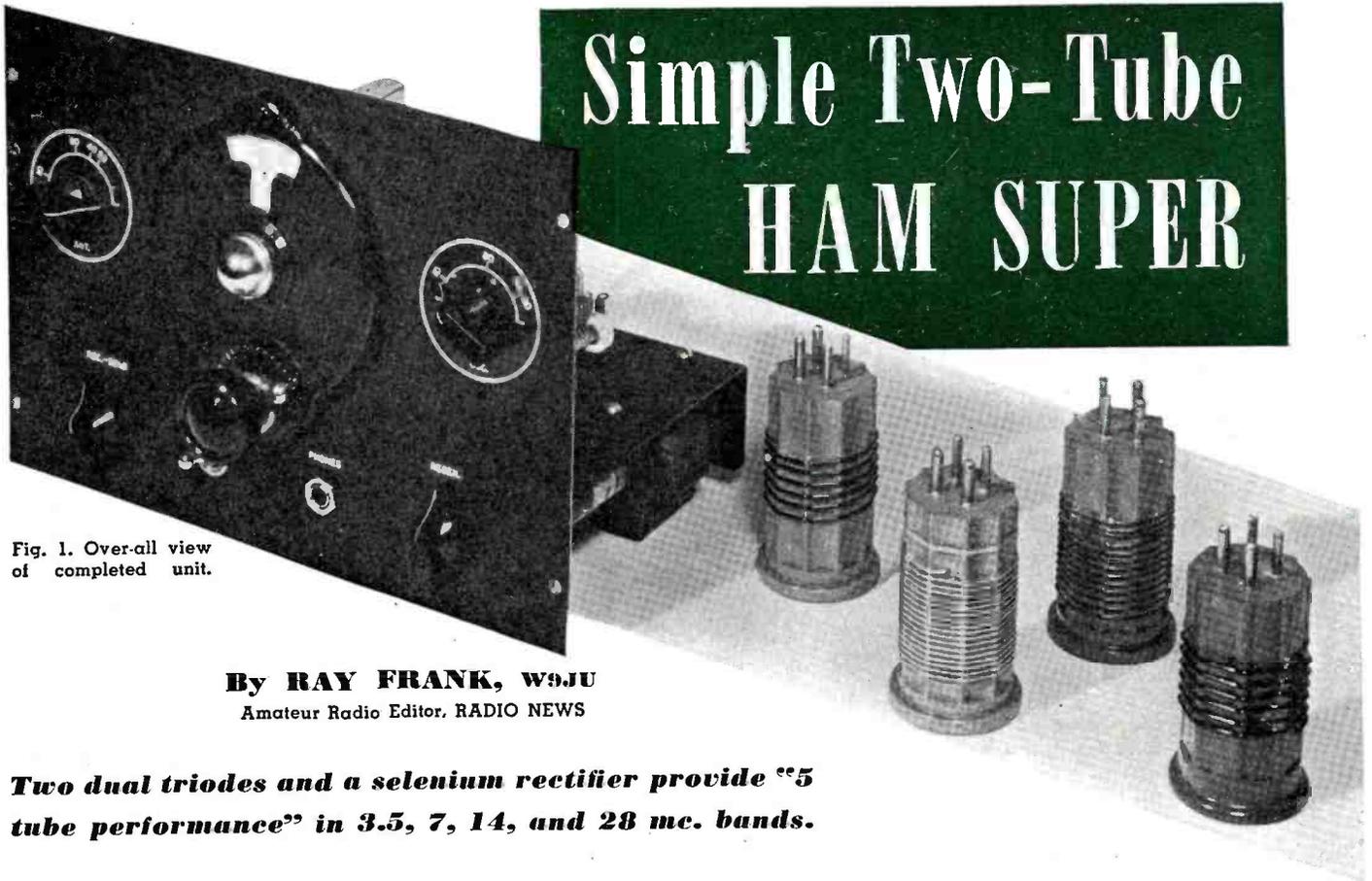


Fig. 1. Over-all view of completed unit.

By **RAY FRANK, W9JU**
Amateur Radio Editor, RADIO NEWS

Two dual triodes and a selenium rectifier provide "5 tube performance" in 3.5, 7, 14, and 28 mc. bands.

FREQUENTLY the embryo ham is confronted by the high cost of a complete station with all its accessories. Too often, when the transmitter has been built or purchased, the funds then available for a satisfactory receiver are found to be insufficient. The usual result is that the remaining funds are invested in a receiver that will not meet future requirements.

It was with this thought in mind that the receiver described in this article was designed. The complete cost is low, and when more funds are available, it may be discarded or kept as a

standby unit. In addition, its compact size lends itself well to portable work.

While the performance of this receiver cannot equal that of the regular communications jobs, ease in handling, plus sufficient selectivity to work under difficult conditions is attained. To keep the parts to a minimum, it was decided to dispense with the usual output stage, and confine the output to a level adequate for headphone use.

In order to have usable selectivity, it is almost essential that any ham receiver be of the superheterodyne


type. In these days of parts shortages this often entails considerable searching to locate the desired components. By the use of a regenerative second detector, however, it is possible to realize considerable gain. The use of a high frequency i.f. system insures adequate freedom from images.

As finally adopted, the lineup is as follows: 6J6 oscillator and first detector, with another 6J6 serving the dual purpose of a regenerative detector and audio amplifier. These tubes were chosen because of their small size, excellent performance, and availability on the surplus market. Pulling between the oscillator and first detector, so common in a receiver of this type, is practically absent, due to the low interelectrode capacities of the tube, and the low amount of oscillator injection needed to give satisfactory conversion.

The i.f. circuit consists of L_4 and a feedback winding L_5 . One section of the second 6J6 is used as a regenerative detector. The resistor, R_6 , controls the amount of feedback by adjusting the plate voltage on the detector section of this 6J6.

For maximum convenience a built-in power supply was included. This power supply consists of a selenium rectifier and a simple RC filter. Heater power for the tubes is supplied by a 1 ampere, 6.3 volt filament transformer rather than a dropping resistor. The heater current of 6J6's is .45 amperes each and the heat dissipated in a dropping resistor to carry this current would be considerable.

Fig. 2. Top view of receiver. Rectifier is shown mounted to rear of L_1 , L_2 .

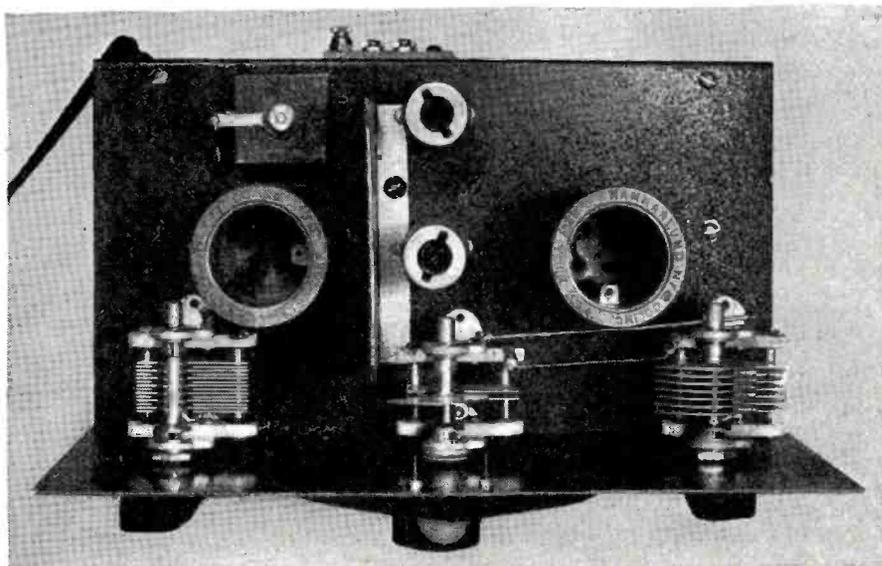

One of the bugaboos of transformerless power supplies is the danger to the operator when a metal chassis is used. To eliminate the possibility of shock, the variable condensers and the phone jack are insulated from the panel by means of fiber washers. All ground returns are made to a piece of tinned copper bus, insulated from the chassis. This bus is bypassed to the chassis by means of an .05 μ fd. condenser. This permits connection of the chassis to a direct ground with no danger to the user.

The entire receiver is built on a 5"x9 1/2"x1 1/2" black crackle finished chassis. A 7"x10" front panel is used. The lower edge of the chassis is mounted 1/2" above the lower edge of the panel to give greater clearance for the various knobs.

Coils L_4 and L_5 are wound on a 3/4" diameter bakelite form. L_4 consists of 55 turns of No. 30 enameled wire closewound, while L_5 is 10 turns of No. 36 single-silk covered, wound at the "cold" end of L_5 . It is essential that proper polarity of L_5 be observed or the i.f. will not oscillate. If this winding is reversed, it will be necessary to reverse the leads.

Tube shields should be used on both tubes, mainly to eliminate microphonics. A small shield formed of scrap aluminum measuring 3 1/2" wide x 3 1/2" high is used to separate the oscillator and mixer portions of the receiver.

The controls as seen from the front are, upper left hand knob C_2 , center dial, bandspread tuning C_4 , upper right hand knob, band set condenser C_3 . Along the lower edge are mounted the send-receive switch S_2 , the on-off switch S_1 , the phone jack, and the regeneration control R_6 .

The selenium rectifier is mounted on the antenna section of the chassis just to the rear of the antenna coil. This insures adequate ventilation for the rectifier. Parts below the chassis are mounted wherever convenient.

When construction has been completed, the receiver should be turned on and allowed to thoroughly warm up. The antenna coil should be removed and a 1 megohm resistor connected across the terminals of C_2 . A signal generator or other source of modulated signal should be applied across this resistor and the frequency of the signal source varied until the signal is heard in the headphones. This frequency should lie somewhere in the range of 1500 to 1700 kc. The exact frequency is not important as long as it is in an interference free spot. It is easy to change the frequency by changing the value of C_6 . In the particular unit constructed here, C_6 consisted of a 200 μ fd., 5 per-cent mica condenser shunted by a 25 μ fd. mica. This gave an i.f. frequency of 1630 kc.

With the regeneration control R_6 full on, the trimmer condenser C_{11} should be adjusted so that the i.f. just goes into oscillation at the maximum

(Continued on page 98)

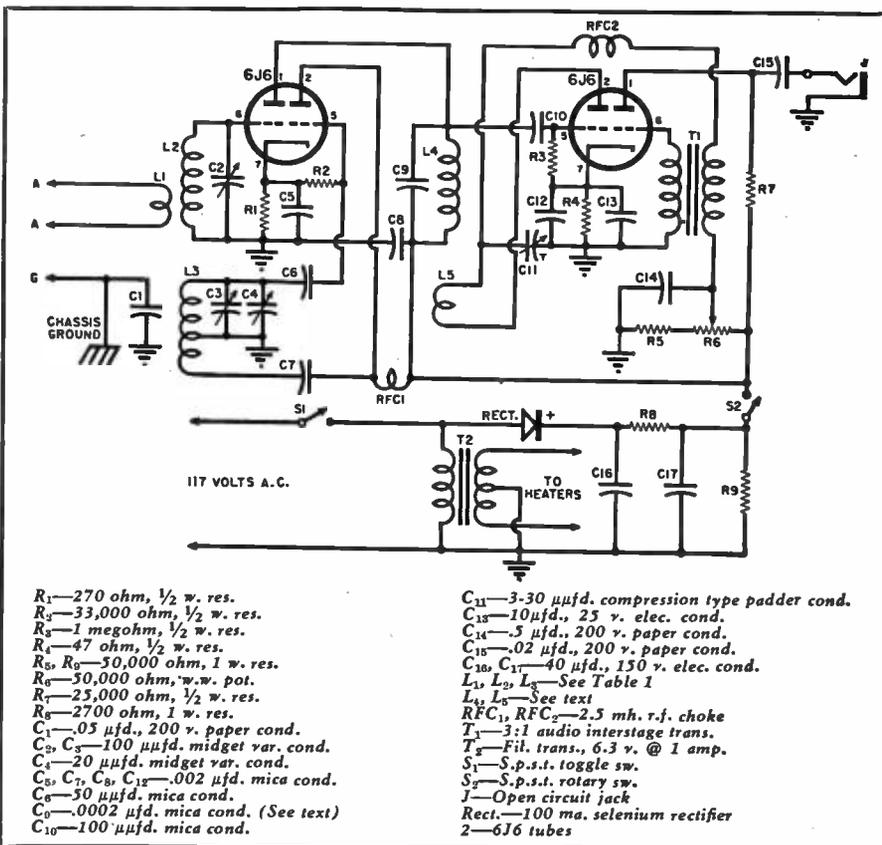



Fig. 3. Complete circuit diagram and parts list for simple two tube "ham-super."


Antenna Coil		Oscillator Coil
L_2 —37 t., #22 e., 1 1/2" long.	3.5 mc.	L_2 —26 t., #20 e., 1 3/8" long. Tap at 6th turn from bottom.
L_1 —11 t., #30 s.c., 1/4" from cold end.		
L_2 —17 t., #20 e., 1 1/2" long.	7 mc.	L_3 —13 t., #20 e., 1 1/2" long. Tap at 3 1/2 turns from bottom.
L_1 —6 t., #30 s.c., 1/4" from cold end.		
L_2 —6 t., #16 e., 1" long.	14 & 28 mc.	L_3 —6 t., #16 e., 1" long. Tap at 2 turns from bottom.
L_1 —2 t., #30 s.c., 1/8" from cold end.		

All coils wound on 1 1/2" diameter forms.

Table 1. Detailed specifications for constructing antenna and oscillator coils.

Fig. 4. Bottom view showing location of component parts. The i.f. coil, L_1, L_3 , may be seen in center of the chassis. C_{11} is mounted directly above i.f. coil.

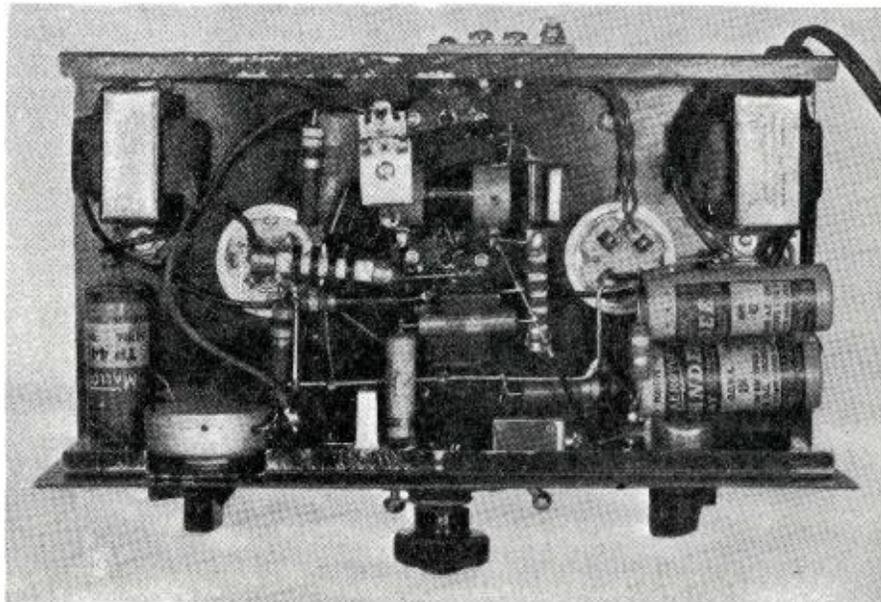

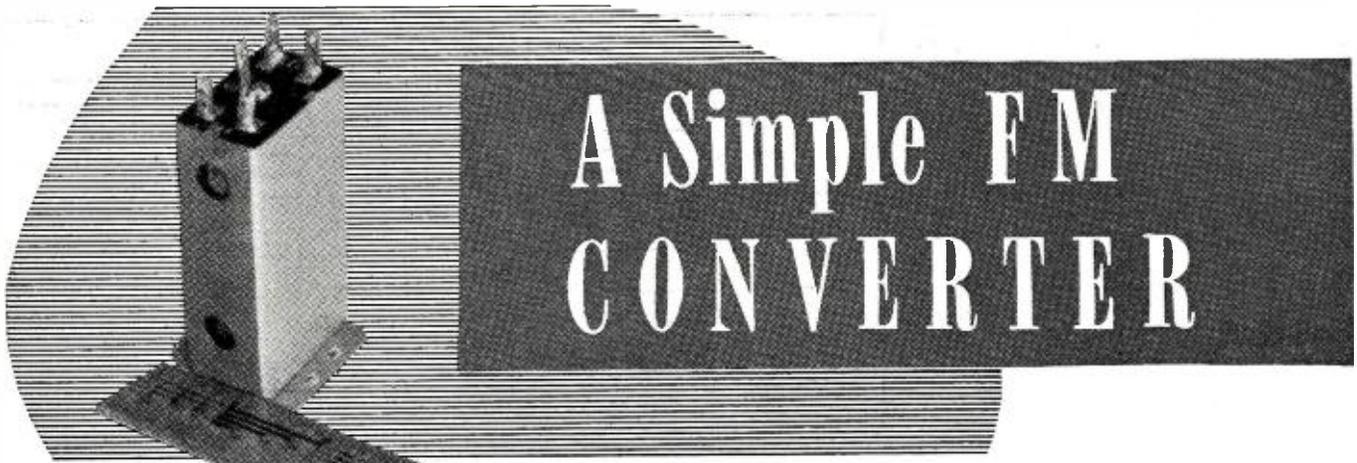

Although trimmers are pre-set, holes are provided in the case for later adjustments if found necessary.

By
STANLEY N. FINLEY

There are many FM stations now operating on the new 88-108 mc. band. This unit permits old band 40-50 mc. receivers to tune in the new FM band.

be tuned with the converter pictured in the photographs. Table 1 shows the range in which the new band falls on typical old band receivers, when using the crystal diode FM converter. For any other i.f. in an FM receiver the range can be determined from the formula:

$$88 - \frac{(88-i.f.)}{2} = \text{low end}$$

$$108 - \frac{(108-i.f.)}{2} = \text{high end}$$

The stations in the old band will be received through the converter as usual.

To make the present tuner operate over the *entire* new band is a very simple operation. Merely shift the tuning range upward by adjusting all capacitors used as trimmers on the tuning condensers in the direction of less capacity. This raises the minimum frequency and maximum frequency to which the dial will tune. The ranges listed in the table will cover all or nearly all the receiver types that were sold for the 40-50 mc. band. For the intermediate frequencies not listed the formula may be used to determine the range to which the set should tune to cover the entire new band.

In making the shift to a higher range the oscillator trimmer is first set to minimum capacity. Then with the signal generator set to some frequency in the middle of the former range tune in the generator signal. In the absence of a generator a mid-band (old band) station may be used. This mid-band signal should now fall near the low frequency end of the dial. Final adjustment is made with the other trimmers. These are tuned for maximum output.

Recalibration of the set is simply a matter of receiving known stations and marking their frequencies on the dial or a new dial plate. A typical scale change on one of the receivers (Meissner Tuner 9-1047) is shown in Fig. 1C.

There are two trimmers on the FM converter which can be preset for best
(Continued on page 181)

Receiver I.F.	Old band Tuning Range In which New Band Falls
5.0 mc.	46.5 mc. to 56.5 mc.
4.3 mc.	46.15 mc. to 56.15 mc.
3.0 mc.	45.5 mc. to 55.5 mc.

Table 1

THERE are many ways of converting FM receivers for operation in the new 88-108 mc. band. The simplest method yet devised is the conversion of the set into a double superheterodyne by the addition of a unit which requires only the connection of a suitable antenna to its input connections and then it is connected to your present old-band (40-50 mc.) FM receiver. It is then effectively in series with the doublet antenna lead-in.

The unit may be used without making any changes or adjustments in the present receiver but this limits the range to just the first half of the new band for some receivers. The intermediate frequency of the present set and its present range are factors in determining how much of the band can


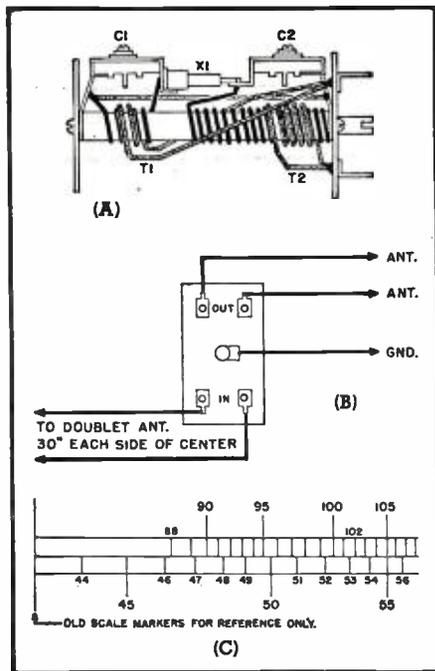


Fig. 1.

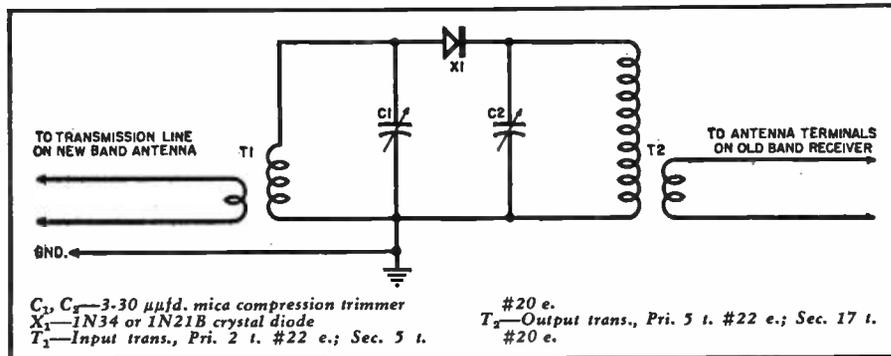Wiring diagram of FM converter. In using this unit with old band receivers simply connect it between the antenna and the antenna terminal posts on the receiver.



FM TUNER CONVERSION with LC Circuits

By **NORMAN L. CHALFIN**

Don't discard those Meissner and GE FM tuners. It is a simple process to convert them for operation in the new band.

IT SEEMS a shame that there are so many FM tuners lying idle or are now tuning only the one or two stations still available in the 40-50 mc. band for any area. Since new converters are unavailable and new sets are slow to appear on the market in any quantity these tuners can be made serviceable by coil and other

changes that will convert them for operation in the 88-108 mc. FM band. The *Meissner* 9-1047 and the *GE* JFM 90 were probably the most popular units and there are many of them around. These have been converted by the author with the changes described herein and are giving excellent service where they had previously been

unused. The cost of the conversion is entirely negligible in terms of the original cost of the set.

Since the conversion of the *Meissner* unit was accomplished most easily we will describe this first:

The first operation is to strip the unit of the three coil assemblies for the r.f., oscillator, and antenna tuning.

Fig. 1. Meissner FM tuner that has been converted for the new FM band. The 12SA7 mixer and 12SK7 r.f. tubes have been replaced by the 12BE6 and 12BA6 tubes respectively


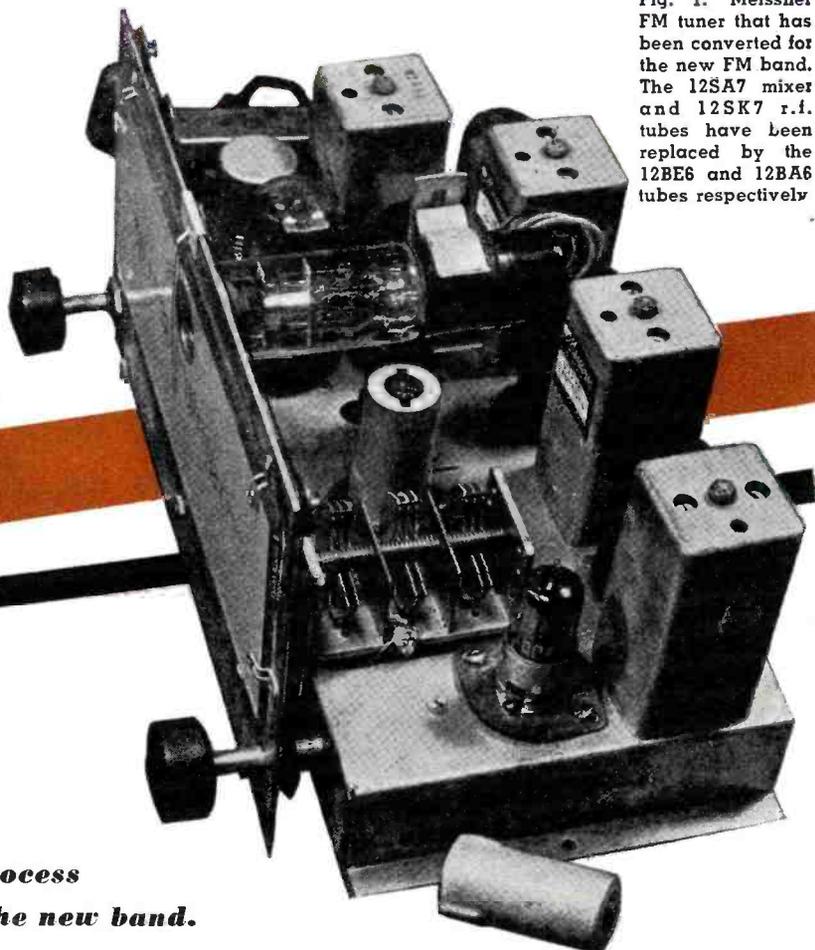


Fig. 2. Schematic diagram of the Meissner FM tuner before it was converted for operation in the new FM band.

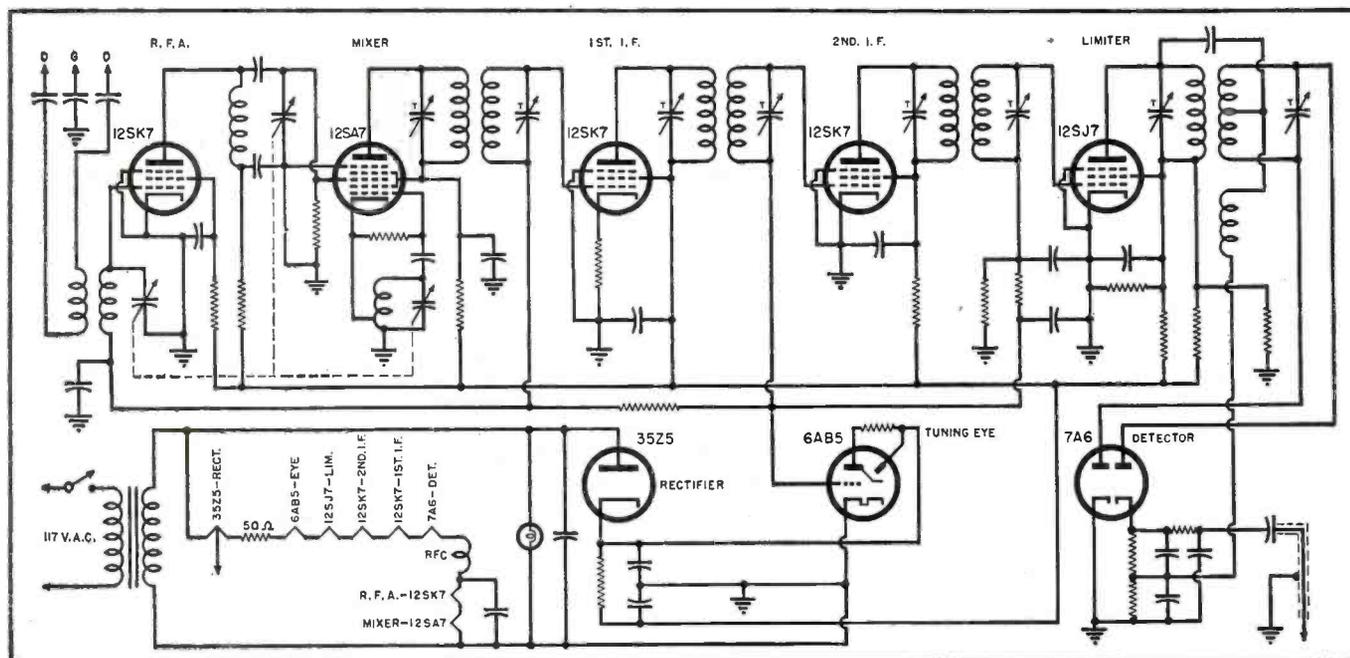

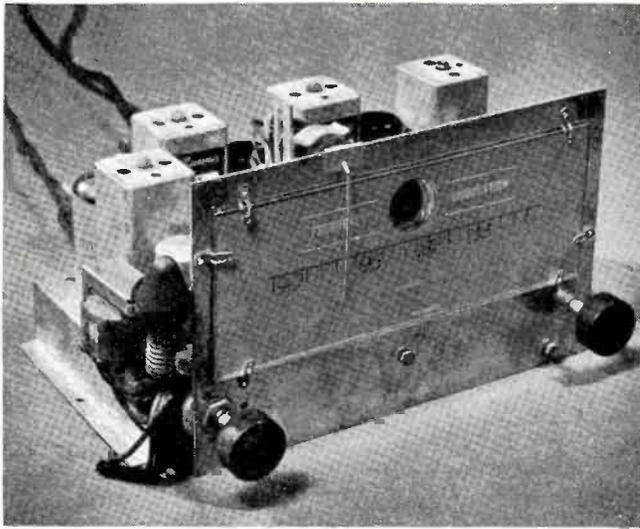


Fig. 3. Meissner tuner with the newly calibrated dial scale.

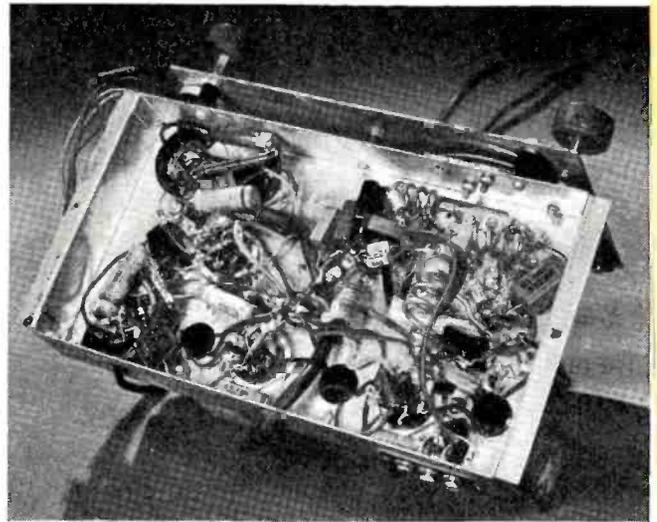


Fig. 4. Converted Meissner tuner showing coil placement.

If it is desired to retain the original tubes as in choice 1, below, make certain in this operation that all parts are left connected to their original points on the chassis and the tube sockets, removing only the coil assembly wires. Next remove the a.v.c. dropping resistance and its assembly tie points from the front wall of the chassis near the r.f. stage (12SK7). Connect the grid return end of the first i.f. transformer to ground (black wire). Remove the connections to the a.v.c. source resistances. (There is really no need for a.v.c. in this type of FM receiver since the limiter serves this function to a large extent). From this point on there are three choices from which to select a method of conversion. These are:

1. Use the existing tubes; 12SA7 mixer, 12SK7 r.f. or 6SK7, and 6SA7.
2. Change to the newer types with more transconductance (12SG7 r.f. and 12SA7 mixer) or the types for the 6 volt equivalent set: 6SG7 r.f. and 6SB7Y mixer.
3. Change the r.f. section over for miniature tube types: 6BA7 r.f. and 6BE6 mixer or, as was the case in the

unit pictured in the illustrations (Fig. 1), 12BA6 and 12BE6.

Our experience with the first was that the operation was satisfactory for the area within the immediate vicinity of the transmitters. When tried in suburban areas more gain was desirable. The second choice helped considerably for the twelve volt series. Use of the 6SB7Y and 6SG7 for a 6 volt filament unit left nothing to be desired. In order to equal the performance of the 6 volt unit it was necessary to use the miniature tubes.

The miniature tube sockets are mounted on deck switch separator shield plates drilled for the purpose. The r.f. tube socket (12BA6) was assembled and mounted so that pin 1 (grid) faces the front of the chassis. This makes pin 5 (plate) face the rear of the chassis, thus, short leads to the tuning capacitor and coils are assured. The 12BE6 socket is mounted so that pin 1 (oscillator grid) is directly facing the tuning capacitor. This places the signal grid connection (7) in line for close connection to the mixer grid tuning tank.


An r.f. choke (*Ohmite Z-1* or equiv-

alent) is now connected in the series filament connection between the 12BA6 and 12BE6: This is bypassed to ground with .01 μ f. at the 12BE6 socket. The filament series connections are completed as in the diagram Fig. 5.

The tuning coils are each four turns of #10 tinned copper wire wound on a $\frac{1}{4}$ inch form spaced approximately $\frac{3}{16}$ " per turn. The final spacings will vary for each coil when the set is aligned for tuning capacitor tracking as described later. The coils are assembled in the set as shown in the picture, Fig. 4.

The grid ends of the coils are mounted directly on the tuning capacitors; the antenna-r.f. stage is at right angles to the direction of the tuning capacitor mounting on the condenser nearest the front; the oscillator tank in the same direction on the middle tuning capacitor with the ground end of the coil away from the antenna tank; the mixer grid tuning coil is mounted at right angles to the other two with the ground end towards the rear of the chassis. Thus, the fields of the three coils are made to oppose one another—the antenna and oscillator

Fig. 5. Schematic diagram of the converted r.f. end of the Meissner tuner. The r.f. and mixer stages have been changed.

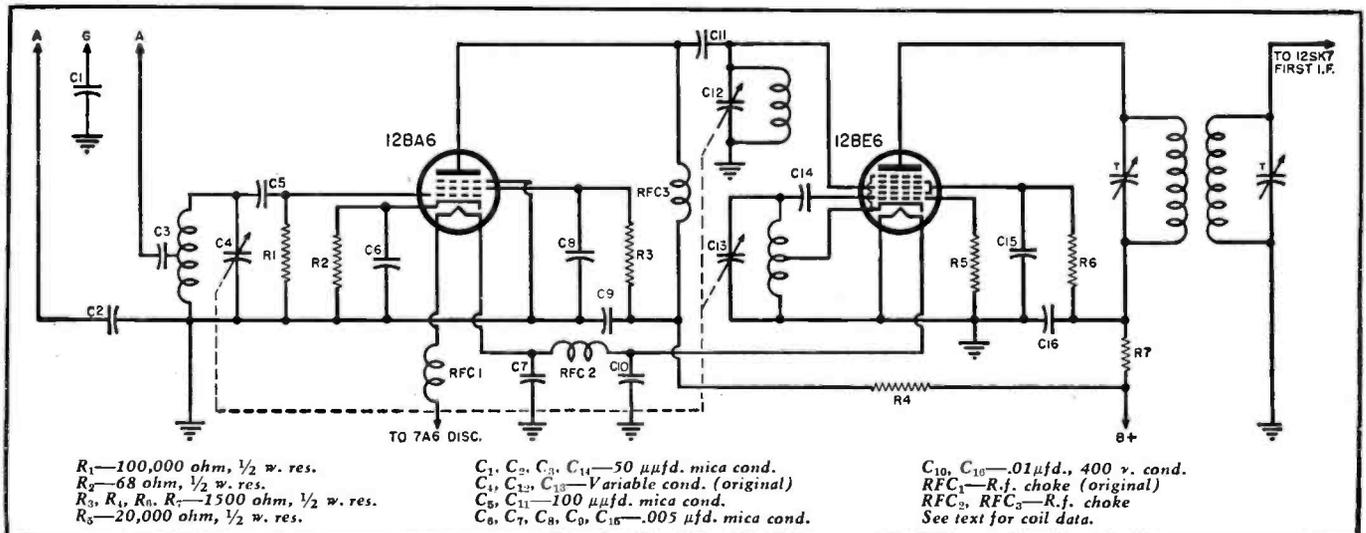

by virtue of winding direction and the mixer with respect to the other two by virtue of positioning at right angles to them.

Reference to the diagram and bottom view photograph (Figs. 4 and 5) will show that r.f. stage is capacitively coupled to the tuning coil $\frac{1}{2}$ turn down from the grid end. The grid is returned to ground through a 100,000 ohm grid leak.

The oscillator tank is arranged for Hartley operation and the tap is one and a half turns from the ground end.

The balance of the wiring can be done with only one major precaution in mind. The bypass capacitors should be connected with as short a lead connection as is possible and the ground ends should come to a common point for any one tube. For the r.f. stage all bypass capacitors are connected to the point where the ground end of the tank coil is connected. This is a little more difficult to do at the mixer stage but, if the screen and plate decoupling bypass capacitors are brought to the ground end of the signal tank and the filament bypass to the ground end of the oscillator tank, this will do the trick.

When the wiring is completed the condenser is made to track in tuning by squeezing together and separating the turns of the coils as required. The oscillator tuning range should be 83.7 mc. to 103.7 mc. If an absorption type wavemeter is handy this can be readily checked by observing the grid current dip on an 0-1 ma. meter inserted in the ground end of the local oscillator grid leak resistance. When doing this, bypass the meter to sustain oscillation.

In the absence of a signal generator the tracking can be checked with known stations.

The tracking that has been attained by the author is indicated in the photograph of Fig. 1.*

It has been assumed that the alignment of the i.f. has not been touched throughout this conversion. Some readjustment of the first and second i.f. transformers can be anticipated. A further improvement in limiter action can be had by making the limiter tube a 12SH7 replacing the 12SJ7. The i.f. transformers will require slight re-tuning if this is done. For the 6 volt counterparts the tube type for this change is the 6SH7.

The use of negative temperature coefficient capacitors (Erie Ceramics) would undoubtedly reduce any frequency drift of the oscillator due to heat generated within the tuner.

The JFM 90 Tuner

The conversion of the JFM 90 GE FM translator can be made readily. It is important first to understand its

* In the picture Fig. 1 there can be seen at the left of the chassis a small a.c.-d.c. filter choke that was added in place of the resistive power supply filter in the original set. This removed a tunable hum which appeared in the set both before and after the conversion. This choke is soldered to the chassis and made a considerable difference in the over-all performance.

May, 1947

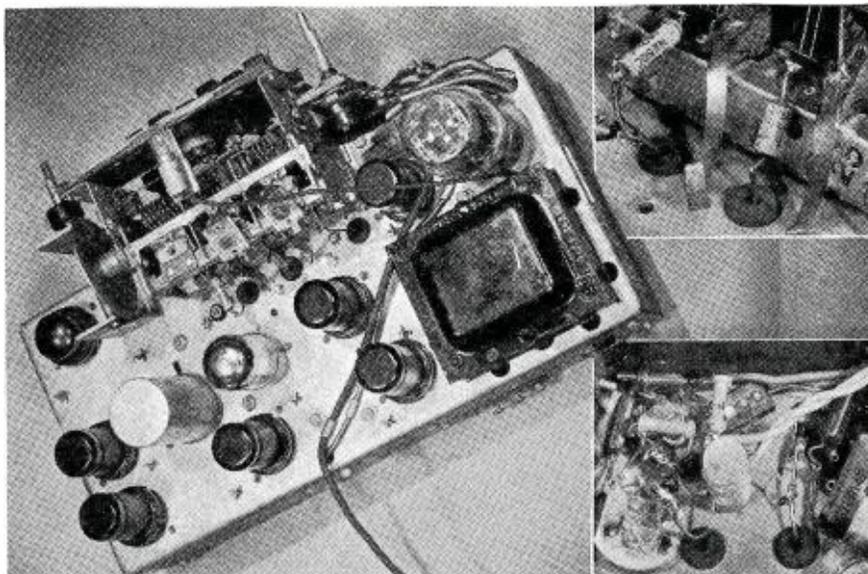


Fig. 6. Top view of the converted General Electric JFM-90 FM tuner. Insets show position of series condensers that are placed in the variable condenser leads and the under chassis position of the new oscillator coil.

operation. The tuner is a double superheterodyne of very unusual type. The first i.f. is tuned along with the oscillator and r.f. (1st mixer) stage. The operation is as follows:

The local oscillator beats with the carrier in the first mixer to produce the first i.f. This first i.f. is tunable with the oscillator and antenna stage. This difference frequency in turn beats with the same local oscillator frequency which passes through the first mixer and the resultant is the final i.f. If the final (second) i.f. is known the first i.f. range and the oscillator range can be determined from the formulas: $(F_c - F_2)/2 = F_1$ and $F_c - F_1 = F_2$, where: F_c = carrier frequency; F_1 = oscillator frequency; F_2 = first i.f. (variable); F_3 = second i.f. (fixed).

Thus for the 4.3 mc. i.f. of the set (F_2) the local oscillator (F_1) range for the FM band is 41.85 mc. to 51.85 mc. and the first i.f. (F_3) range is 46.15 mc. to 56.15 mc. The carrier (F_c) range, of course, is 88-108 mc.


It is quite apparent that this represents a nice tracking problem. In the original set the tracking was taken care of in a tuning capacitor with three (3) special units ganged together.

The antenna primary, the r.f. grid and the local oscillator coils are wound on a single form. The original coil assembly was removed and a new coil form of a one-half inch polystyrene rod was made. Nearest the bottom end of the form is wound seven (7) turns, center tapped, of #18 solid copper tinned wire. The turns are spaced 12 turns to the inch.

On the same form $3/16''$ above the oscillator coil wind one and three-quarter turns of #18 tinned copper wire spread $3/16''$ apart. Then $3/16''$ above this wind $1\frac{1}{4}$ turns (12 turns per inch) #18 tinned copper wire leaving very long ends, about 8 inches, covering these ends with spaghetti, then twist together. A sketch of this coil is shown in Fig. 9.

(Continued on page 120)

Fig. 7. Schematic diagram of the front end of the JFM-90 tuner after conversion. The oscillator tube is a 7A4. See Fig. 9 for complete coil specifications.

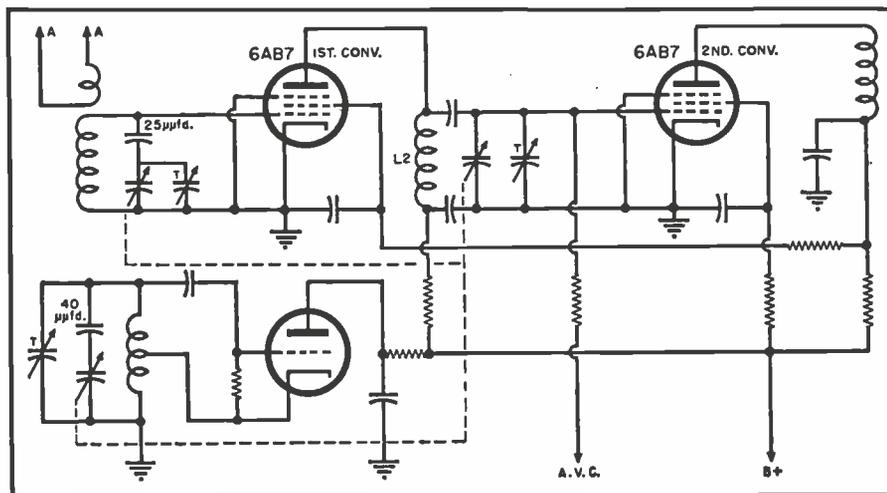



1947 RADIO PARTS and Electronic Equipment CONFERENCE and SHOW

The Trade Show will feature "Open House Day" this year on May 16th.

THE 1947 Radio Parts and Electronic Equipment Conference and Show, to be held at the Stevens Hotel, Chicago, is destined to break every record for attendance when it opens its doors on May 13th. From nearly every corner of the globe representatives will gather with their exhibits of brand new products, most of which will be shown for the first time.

The Show is sponsored by the Association of Electronic Parts and Equipment Manufacturers, The Radio Manufacturers Association (RMA), The Sales Managers Club, and the Na-

tional Electronic Distributors Associations (NEDA).

The editorial staff of RADIO NEWS will again publish the RADIO NEWS DAILY which was introduced at the 1946 Show. Widely heralded for its on-the-spot coverage of the conference, the paper will again be distributed early each morning from Monday to Friday, inclusive. Familiar faces in our industry will appear in the DAILY in the form of photos and specially drawn caricatures by a leading artist. Other features too will appear for the first time in a show daily.

As a further service to the industry, RADIO NEWS will conduct a Registration and Directory Service Booth. This innovation will make it possible to locate any registrant by simply inquiring at the Booth near the entrance to the Exhibition Hall where a complete up-to-the-minute card file system will be maintained. Manned by, or should we say womaned by, our RADIO NEWS cover girl, Carmen Garcia (see front cover) and other Chicago lovelies, this "Who's Who and Where" service will eliminate previous delays encountered in the typing and printing of registration lists in the DAILY. This becomes the Show's Official Registration and Directory Service. The cards, illustrated, will be distributed at every meeting during the convention and will be available at other strategic locations. Inasmuch as changes of room assignments sometimes occur, registration cards will be corrected upon notification.

RADIO NEWS will also have its Display Booth, No. 44½, in the Exhibition Hall.

"Radio's Old Timers," suspended back in 1941 on account of Hitler and Tojo, will again meet at a cocktail party at the Stevens, May 11. As qualifications for membership require members to have been connected commercially with the radio or electronic industry for twenty years or more, nearly all of the "Old Timers" have attended all the Trade Shows and have seen the Shows grow from a me-

(Continued on page 118)

Facsimile of Registration Card to be introduced as a new RADIONEWS service to Show.

WHO'S WHO AND WHERE

This is your Official Registration and Directory Service Card. It is designed to eliminate delay in locating exhibitors when attending the convention.

NAME		
(Please print)	(Last)	(Initial)
COMPANY		
TITLE		
ADDRESS		
HOTEL	ROOM NO.	DEPARTURE DATE
EXHIBITING IN—	BOOTH NO.	ROOM NO.
RADIO PARTS and ELECTRONIC CONFERENCE and SHOW		
STEVENS HOTEL — CHICAGO, ILL.		
REGISTRATION AND DIRECTORY SERVICE		
COURTESY RADIO NEWS, 185 N. WABASH AVE., CHICAGO 1, ILL.		
(Over)		

attendant at the
nce to the Exhibi-

will be available
and displaying".
that your card



Charles Golenpaul
Aerovox Corp.
Vice-pres., RPEE
Show



Bill Cunningham
Keynote Dinner
Speaker



J. A. Berman
Shure Brothers
President, RPEE Show



Kenneth C. Prince
General Mgr., RPEE
Show



J. J. Kahn
Standard Trans.
Secretary, RPEE
Show



R. J. Sherwood
The Hallcrafters Co.
Director, RPEE Show



R. C. Sprague
Sprague Electric Co.
Director, RPEE Show



Sam Poncher
Newark Electric Co.
Treasurer, RPEE Show



W. O. Schoning
Lukko Sales Co.
Director, RPEE Show



W. W. Jablon
Hammarlund Mfg.
Director, RPEE Show

**MEMBER-EXHIBITORS IN THE 1947 RADIO PARTS & ELECTRONIC EQUIPMENT
CONFERENCE & SHOW**

COMPANY NAME	BOOTH NUMBER
Advance Electric and Relay Co.	47
Aerovox Corporation	85
Alliance Manufacturing Co.	123
Alpha Metals, Inc.	144
Alpha Wire Corp.	125
American Coil & Eng. Co.	116
American Condenser Co.	129
American Microphone Co.	4
American Phenolic Corp.	65
American Radio Hardware Co., Inc.	75
Amperex Electronic Corp.	67
Amperite Co.	60
The Astatic Corp.	95
Atlas Sound Corp.	134
Audio Devices, Inc.	148
Barker & Williamson	77
Belden Manufacturing Co.	128
Bell Sound Systems, Inc.	43
Bibley Electric Co.	78
David Bogen Co.	40
William Brand & Co.	13
British Industries Sales Corp.	112
Bruno Tools	76
Brush Development Co.	118
*Bryant-Davis Pub. Co.	27 1/2
Bud Radio, Inc.	39
Burgess Battery Co.	147
Burlington Instrument Co.	22
*Boland & Boyce, Inc.	154 1/2
*Caldwell-Clements, Inc.	20 1/2
Camburn, Inc.	143
Carroll Mfg. Co.	57
Centralab	68
Chicago Transformer Div.	11
Cinacograph Speakers, Inc.	3
Clarostat Mfg. Co., Inc.	124
Condenser Products Co.	153
Continental Carbon, Inc.	150
Cornish Wire Co.	48
*Cowan Publishing Corp.	130 1/2
Croname, Inc.	84
Dial Light Co. of America, Inc.	109
Drake Electric Works, Inc.	61
Dumont Electric Corp.	12
Duotone Co., Inc.	20
Eastern Amplifier Corp.	34
Eastern Electronics Corp.	111
Eckstein Radio and Television Co.	29
Eitel-McCullough, Inc.	14
Electric Soldering Iron Co.	58
Electronic Engineering Co.	62
Electronic Laboratories, Inc.	56
Electro Products Laboratories	81
Electro-Voice, Inc.	15
Electrovox, Inc.	122
The Erwood Co.	105
Federal Telephone & Radio Corp.	135
Freed Transformer Corp.	113

COMPANY NAME	BOOTH NUMBER
General Cement Mfg. Co.	96
General Electric Co.	8
General Industries Co.	110
General Transformer Corp.	63
Guardian Electric Mfg. Co.	51
The Halldorson Co.	37
The Hallcrafters Co.	86
Hammarlund Mfg. Co.	90
Hardwick, Hindle, Inc.	36
Hickok Electrical Instrument Co.	142
Hytron Radio & Electronics	91
Indiana Steel Products Co.	38
Industrial Condenser Corp.	141
Insuline Corp. of America	114
International Resistance Co.	88A
International Resistance Co.	98
Jackson Electrical Instrument Co.	98
Jackson Industries Inc.	156
J-B-T Instruments, Inc.	5
Jensen Manufacturing Co.	4
J. F. D. Manufacturing Co.	117
E. F. Johnson	73
Kenyon Transformer Corp., Inc.	6
Kings Electronics Co.	94
Lectrohm, Inc.	132
Lenz Electric Mfg. Co.	104
P. R. Mallory & Co.	106
Marion Electrical Instrument	32
John Meck Industries, Inc.	133
Meissner Manufacturing Co.	93
Merit Coil and Transformer Corp.	52
James Millen Mfg. Co., Inc.	33
Milwaukee Stamping Co.	136A
National Co., Inc.	70
National Union Radio Corp.	10
Newcomb Audio Products Co.	7
Ohmite Manufacturing Co.	74
Operadio Manufacturing Co.	139
Oxford Radio Corp.	59
Panoramic Radio Corp.	115
Park Metalware Co., Inc.	136
Par-Metal Products Corp.	24
*The Parts Jobber, Inc.	28 1/2
Permo, Inc.	41
Philmore Manufacturing Co.	119
Pioneer Electric & Res.	9
Potter & Brumfield Mfg. Co.	53
Precision Apparatus Co., Inc.	152
Premax Products Division	18
Presto Recording Corp.	23
Price Recording Corp.	145
Pyramid Electric Co.	157
Quam-Nichols Co.	140
Racoon Electric Co., Inc.	158
*Radercraft Publications, Inc.	21 1/2
Rad-El-Co Manufacturing Co.	87A
Radiart Corp.	79
Radio City Products Co., Inc.	35
Radio Corporation of America	135A

COMPANY NAME	BOOTH NUMBER
The Radio Craftsmen, Inc.	25
*Radio & Electronic Jobber News	45 1/2
*Radio News	44 1/2
*Radio News Directory Service	Stair Lobby
*Radio & Television Weekly	129 1/2
The Rauland Corp.	83
Raytheon Manufacturing Co.	99
The Recordisc Corp.	27
Recaton Corp.	26
Reiner Electronics Co., Inc.	35
Rek-O-Kut Company	55
John F. Rider, Publisher, Inc.	120
Howard W. Sams & Co., Inc.	31
Sangamo Electric Co.	2
Walter L. Schott Co.	71
Shur-Antenna-Mount, Inc.	42
Shure Brothers	87
McMurdo Silver Co.	138
Simpson Electric Co.	149
Mark Simpson Mfg. Co., Inc.	46
SNC Manufacturing Co., Inc.	72
Snyder Manufacturing Co.	66
Sola Electric Co.	30
Solar Manufacturing Corp.	92
Special Products Co.	103
Speed X Manufacturing Co.	64
Spiraling Products Co.	159
Sprague Products Co.	89
Standard Transformer Corp.	88
Stromberg-Carlson Co.	108
Supreme Instruments Corp.	102
Sylvania Electric Products	50
Talk-A-Phone Co.	151
Technical Appliance Corp.	19
Telex, Inc.	131
Thordarson Electric Co.	126
Trimm, Inc.	100
Triplet Electrical Instrument	121
Tung-Sol Lamp Works, Inc.	107
The Turner Co.	49
*United Catalog Publishers	153 1/2
United Transformer Corp.	1
University Loudspeakers	16
Utah Radio Products Div.	97
Vaco Products Co.	82
Vertrod Corp.	69
Ward Leonard Electric Co.	127
Ward Products Corp.	80
Waterman Products Co.	101
Webster-Chicago Corp.	155
Webster Electric Co.	137
Weller Manufacturing Co.	43
Westinghouse Electric Corp.	17
Weston Electrical Instrument	54
Wirt Co.	146
Workshop Associates, Inc.	41A
*Ziff Davis Publishing Co.	44 1/2

* Guest-Exhibitor.



By JOHN T. FRYE, W9EGV

If you have postponed getting your ham ticket try this tested method of preparing for exams.

ARE you a SWL? In your case, do these letters stand for "Sure Would Like" a ham ticket? Do you hang around ham shacks, read all the short-wave magazines, build receivers and even dummy-loading transmitters, but still cannot go on the air because you do not have an amateur license? If so, this is your article.

If you will do what I tell you, whole-heartedly and with enthusiasm, you can earn a ham ticket in thirty days, devoting only an hour and a half each day to the project.

Learning the code is the highest barrier between the would-be ham and a license, but did you ever stop to think what a simple matter learning the code really is? There are twenty-six letters, ten numerals, and four marks of punctuation that you should learn to identify instantly when you hear them. That makes a total of forty. But the multiplication table, which you know frontwards and backwards, has a hundred and forty-four combinations!

Again, suppose I spell "c-a-t" out loud. Instantly you think of the word "cat." Consider the thousands of letter combinations that you can recognize in a split second when you hear or see the words spelled. Beside these two feats of learning *that you have*

already accomplished, learning the code dwindles to the small matter that it really is.

No, *learning the code is not hard*. It only seems so because you have fallen into the rut of thinking that it is. Make your mind up right now to quit stalling around and to get yourself a ham ticket. For once, just for the heck of it, show that naturally lazy mind of yours who is really the boss. Are you ready? Let's go!

Secure some 3" x 5" file cards. With a small paint brush and some India ink, paint on the blank face of each card a single different letter of the alphabet, numeral from 1 through 0, or a question mark, error sign, period, or comma. Make the letters as large and as bold as the space permits. Then, on the back of each card, write the code combination for the character appearing on the opposite side, using the word "dit" for each dot and "dah" for each dash.

Shuffle the cards and place them in front of you with the "dit-dah" sides up. Say the combination of the top card aloud, as rapidly as you can do so distinctly, while you turn the card over and stare fixedly at the big letter painted on the opposite face. "Dit" is pronounced as shortly and as sharply as you can make it. "Dah," by its very nature, is dragged out a

trifle longer. No appreciable space is left between the elements of a "dit-dah" combination in pronouncing it. For example, the combination for K, "dah-dit-dah," is pronounced with exactly the same rhythm as "shoot the chutes."

Speak the combination five times; then go on to the next card and do the same thing. Make no attempt to memorize the combination of letter and "dit-dahs." Simply keep the eyes glued to the letter while you repeat the correct "dit-dah" combination. Learning to read code is not a matter of memory. It is one of association.

Did you ever catch a whiff of perfume that instantly threw the face of a blonde you used to know on the screen of your mind, and then you searched around in your memory until you came up with her name? The first part of this process was instantaneous and purely automatic, like a reflex; the second part took time and effort. "Association" was working for you when the perfume recalled the blonde, and association is what we want to work for you in learning the code. If the ear is forced to listen to "dit-dah, dit-dah, dit-dah, dit-dah, dit-dah," an association is formed in the subconscious between the sound and the letter so that the instant the one is seen or heard the other is instantly called to mind.

As soon as you have gone through the pack, shuffle the cards and start right back through. Be sure and shuffle the cards. The mind must not be allowed to form any misleading sequence-patterns. Keep going through the cards again and again, saying each "dit-dah" combination aloud while you keep your attention—not just your eyes—sternly fixed on the big letter in front of you.

I suggest that you do this in private for two reasons: first, you need complete privacy and insulation from all distraction to get the full benefit from this method; secondly, the family will probably think that you are ready for one of those jackets with the wrap-around sleeves if they hear you muttering this baby-talk to yourself.

Keep at the practice for a solid hour and a quarter, not trying to hurry, but never stopping to get a drink of water, light a cigarette, or to do any of the hundred and one things that your squirring mind will suggest in an effort to escape from the unaccustomed work you are forcing it to perform. Stick right at it, and do not be surprised if, toward the end of the period, you catch yourself "seeing" the letter that is written on the opposite side just as soon as you say the "dit-dah" combination written on the ruled face of the card, even before you turn it over. When you do, this is a good sign that you are making progress, but do not try to force it. Always go on and turn the card over for a check and continue to repeat each combination of the regular five

(Continued on page 178)

By
SAMUEL MILLER

Premier Electronic Labs., N.Y.C.

PROGRESSIVE radio repairmen are coming more and more to the realization that there is no substitute for proper test equipment in servicing modern receivers, and that accurate and reliable test instruments are an absolute necessity for intelligent troubleshooting and repair. The time when it was possible for the serviceman to get by with a minimum number of test instruments (and sometimes with almost as little understanding or knowledge of the basic principles and operation of the receivers on which he was working) is rapidly disappearing.

It is true that in the past many types of receivers could be put back into some sort of operating condition without the use of any test equipment, especially under emergency conditions, but with the increasing complexity of modern receivers, such methods are now completely inadequate. Furthermore, as the newer AM, FM and television receivers appear in greater quantity, much of the equipment which is at the present time being used by servicemen in their work will be found to be inadequate and obsolete. If the radio serviceman expects to be a major factor in the postwar receiver servicing field in the face of increased competition from large service organizations and the manufacturers themselves, he will have to keep his equipment, as well as his knowledge of fundamentals and basic principles, abreast of the latest developments in his field.

One of the most important requirements in servicing any type of communications equipment is to have available a signal generator supplying an accurate and readily controllable signal which is similar to the actual signal present in the circuit under operating conditions. This signal can then be traced, analyzed and measured through every stage of the equipment until the source of any trouble is located. The signal generator is also used for final alignment of the r.f. and i.f. stages of the receiver, and the accuracy with which this can be done depends directly upon the accuracy of the signal generator. The requirements of modern radio servicing make a good signal generator one of the most important and crucial instruments the serviceman can have.

Commercial receivers are designed to track well and follow accurately the dial calibration for only one particular intermediate frequency, and therefore the i.f. amplifier must be aligned to this exact frequency for good tracking. If the i.f. is aligned to a different frequency, the dial calibration will be off over most of the range (even though the 600 kc. and 1400 kc. check points may have been set correctly by means of their respective

Fig. 1. One of the commercially built generators which may be used for servicing all types of home radio receivers.



With the increased acceptance of FM and television service a signal generator assumes an ever greater role in the servicing of these high frequency units.

trimmers), tracking will be poor and receiver sensitivity will vary over different portions of the dial. This is an important point in favor of using the most accurate signal generator in aligning i.f. channels, even though a rough and approximate alignment can be performed by ear. The accuracy of the signal generator is of considerable importance not only in guaranteeing the accuracy of the frequency to which the i.f. channel is aligned, but also in assuring the accuracy of the 600 and 1400 kc. points at which the dial calibration is checked, and of any additional radio frequency points at which the tracking may be spot checked.

The need for an accurate, stable and reliable signal generator assumes even more importance in the servicing and aligning of FM and television receivers than in the case of standard broadcast receivers. While broadcast receivers can sometimes be roughly

aligned without the use of good equipment, so that they will be acceptable to the uncritical customer, such a procedure becomes completely inadequate and unsuccessful for FM and television receivers. For example, a video amplifier certainly can not be aligned without a signal generator supplying a variable frequency signal up to about 10 mc.

A signal generator for universal use in all types of receivers, including FM and television as well as standard broadcast, has to possess many precision features. It must be capable of supplying a continuously variable tone-modulated signal whose frequency range extends to at least above 108 mc., in order to permit testing the performance of the r.f. sections of FM and television receivers under the new frequency allocations. The dial calibration must be accurate and have an easily read scale at even the highest frequencies, in order to permit accu-

rate testing of receiver bandwidth and dial calibration. External radiation from the circuit should be kept to a minimum, especially at the high frequencies. In testing FM receivers and high-fidelity phonographs, where audio fidelity is a much more important consideration than in broadcast receivers, a good source of pure sine wave audio frequency signal is required in order to test for fidelity and distortion characteristics. The r.f. carrier must also be capable of being externally modulated in order to be able to check video amplifiers in television receivers. At the same time, the signal generator possessing these features should be compact and portable for possible use in field servicing and for occasions when emergency repairs must be performed outside the repair shop.

The purpose of this article is to describe the design and constructional details of a new signal generator which provides the various features required in a modern servicing instrument. This signal generator is being made commercially available by the Premier Electronic Laboratories of New York City. A photograph of the instrument and the schematic circuit diagram are given in Figs. 1 and 2. The frequency range which is covered is from 75 kc. to 50 mc. on fundamental frequency of the r.f. oscillator, and to 150 mc. on third harmonic. This equipment possesses the following essential features:

A. It is extremely accurate and stable throughout its entire range. Accuracy is better than .5% throughout the broadcast band and 1% on higher frequencies.

B. The micrometer tuning mechanism provides that any frequency to which the generator has once been set can be repeated at any time to an accuracy of .02% of the frequency on the main dial.

C. The frequency scale is almost linear on all bands.

D. The 400-cycle audio modulation is essentially pure sine wave with well under 5% distortion.


Details of the circuit can be seen in the schematic diagram in Fig. 2. The radio-frequency signal is generated in a Hartley oscillator circuit using a 6J5 triode. Six coils are used to cover the entire band. The indicated values of the inductance of the oscillator coils were chosen so that, for convenience in operation, the entire broadcast band is covered in one range from 550 to 1700 kc. and no switching is necessary. On most of the frequency bands there is some overlap from one dial scale to the next. For best stability with variations in temperature and humidity, and under mechanical vibration, all the oscillator coils for the different bands are precision wound on bakelite forms and coated with Q-Max. The coils are tapped as indicated in the parts list at the point which gives best frequency stability. By means of a shorting type

coil selector switch, all oscillator tuning coils except the one in use are shorted out, to eliminate any absorption effects which might otherwise be present due to self-resonance of the coils.

Each coil has across it an air trimmer with a minimum capacity of 30 μfd . Air trimmers are used because they are less affected by changes in temperature and humidity than mica trimmers. The use of a relatively high minimum fixed capacity in the oscillator tuned circuit results in greater frequency stability and less effect upon the tuned circuit from heating of tube and circuit elements, and serves the additional function of spreading the tuning at minimum frequency setting of the main tuning condenser.

The 440 μfd . variable tuning condenser is of special straight-line-frequency design with specially shaped plates to give almost linear frequency variation as the condenser is rotated through its 180° range. A major feature of the construction of this equipment is the "Micromaster" Precision Tuning Dial. Spring-loaded split gears are used to completely eliminate play and backlash, and provide extremely smooth and accurate settings. The tuning condenser is driven by the tuning knob through a special vernier geared to the main drive. The vernier dial has calibrated reference points from 0 to 100 to provide a micrometer tuning accuracy, and thus makes the

Fig. 2. Wiring diagram of "Micrometer" tuning signal generator covering the range from 75 kc. to 50 mc. in six bands.

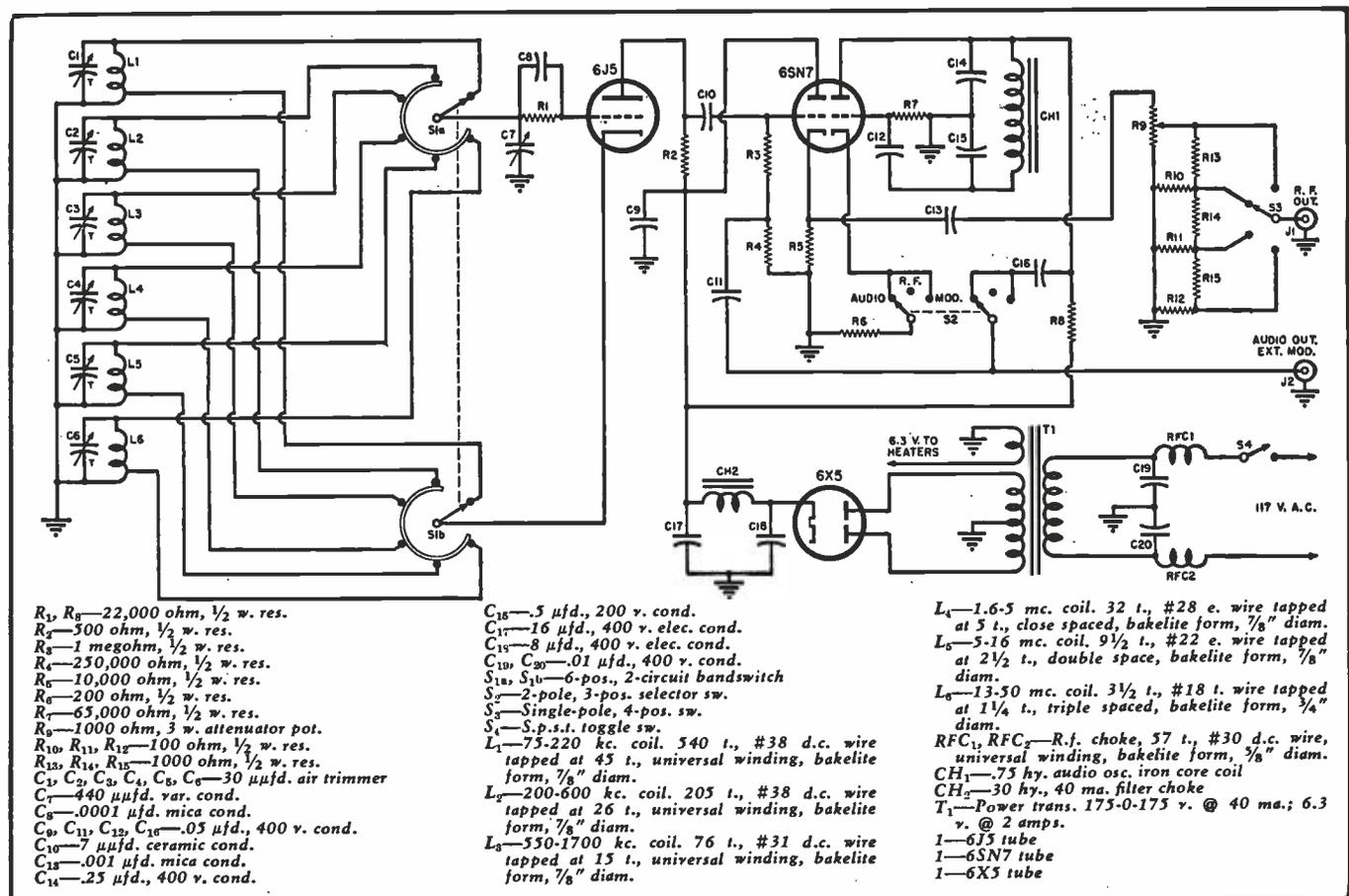

instrument suitable for fine tuning adjustments even at the highest frequencies. This vernier dial lends itself to *delta* tuning and calibrating purposes, and makes possible delta tuning adjustments to an accuracy of better than 1/5000 (i.e., .02%) of the frequency to which the main dial has been set.

The r.f. signal is amplified by a triode buffer amplifier consisting of one section of a 6SN7 dual triode tube, and modulation of the carrier is performed in the grid circuit of this stage by applying the audio modulating voltage to a tap in the grid resistor. The r.f. oscillator is not modulated directly, in order to obtain better stability and prevent the modulation from causing any carrier shift or frequency modulation. The buffer stage is modulated approximately 45% by the internal modulation.

The r.f. output is taken from the cathode of the buffer amplifier operating as a cathode-follower. This provides a low-impedance output to the attenuator. The output voltage from the unit may be varied from zero to maximum by means of the potentiometer gain control, and the maximum output may be varied in four decade steps by means of the multiplier. The output attenuator is completely shielded to reduce leakage to a minimum.

The internal 400-cycle audio modulating signal is generated in the second half of the 6SN7 serving as a triode audio oscillator. A tuned-circuit type of oscillator, with an iron-cored inductance of approximately .75 henry, is used in order to obtain good wave shape in the audio-frequency signal. The oscillogram in Fig. 5 shows the actual 400-cycle modulated waveform of this signal generator. It was taken after the signal passed through the r.f. and audio sections of a commercial receiver. The presence of a pure sine wave audio signal, available for external audio testing purposes as well as for modulation of the r.f. carrier, is an important factor in making it possible to check both the quality of the audio circuit and the overall distortion of any receiver. Without pure sine wave modulation such checks cannot be made.

The audio signal is applied to the grid circuit of the buffer amplifier-modulator stage as shown, and is also available as an audio signal at the "Audio-Out" plug when the "A.F.-R.F.-Mod." switch is in the "Audio-Modulate" position. The carrier is unmodulated when this switch is in the "R.F." position, and may be modulated by any signal fed into the "Audio-Out" plug, which also serves as the "External Modulation" input. In order to eliminate the possibility of any audio leakage into the carrier when it is desired unmodulated, an additional gang is used on the "A.F.-R.F.-Mod." switch to open the audio oscillator cathode circuit so that the audio oscillation stops at the same time the modulator output is disconnected from

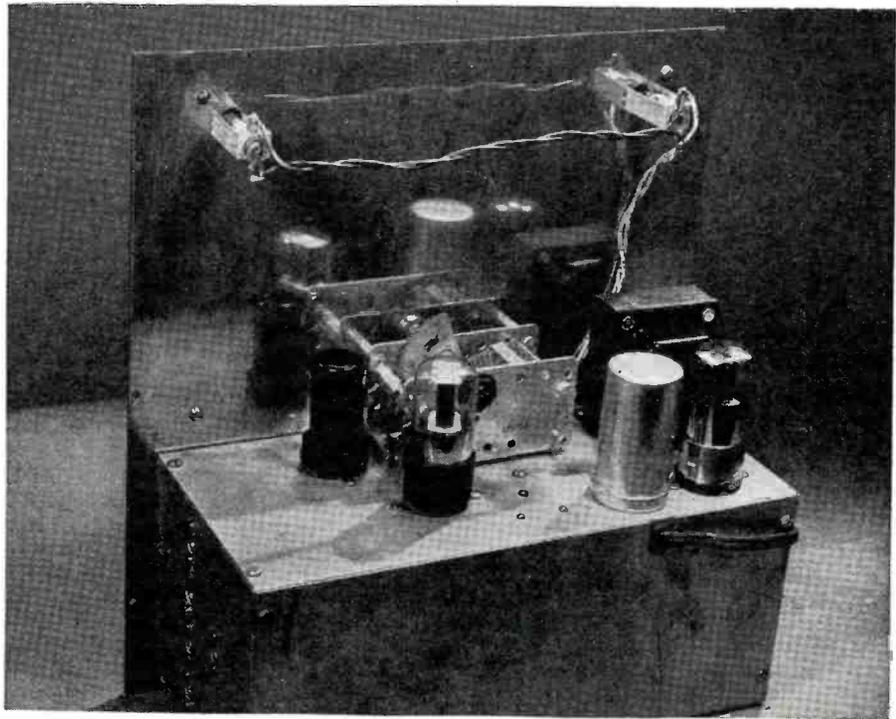


Fig. 3. Rear view of signal generator. Under chassis components of this r.f. section are completely shielded to prevent radiation to external circuits.

the grid of the r.f. buffer amplifier.

Physical details of the unit and its construction may be seen in the photographs in Figs. 1, 3, and 4. Fig. 1 shows the external details and all operating controls and input and output plugs, which are all located on the front panel. The entire unit is contained in a black crackle-finished metal case 12" wide, 12½" high and 5¼" deep.


The internal construction can be seen from Figs. 3 and 4. External radiation from the r.f. oscillator is kept to a minimum by placing an additional internal shield around the r.f. section inside the cabinet. This shielding may be seen in Fig. 4, which shows the inside of the unit with the cover removed, and with the internal shield

in place. Any r.f. leakage into the a.c. line is minimized by the low-pass line filter shown in the schematic. The wiring details of the completed unit may be seen in illustration Fig. 4, which shows the internal view. It may be noted that frequency stability of the r.f. oscillator is affected by the wiring between the bandswitch and the various coils, therefore stiff solid wire is used for these connections to provide maximum frequency stability over long periods of time.

The precision tuning dial is seen in the center of the front panel in Fig. 1. The entire "Micromaster" tuning dial and vernier drive mechanism is located in a dustproof, glass-front casing. Settings are easily read by means

(Continued on page 183)

Fig. 4. Under chassis view of r.f. section shows relative placement of components.

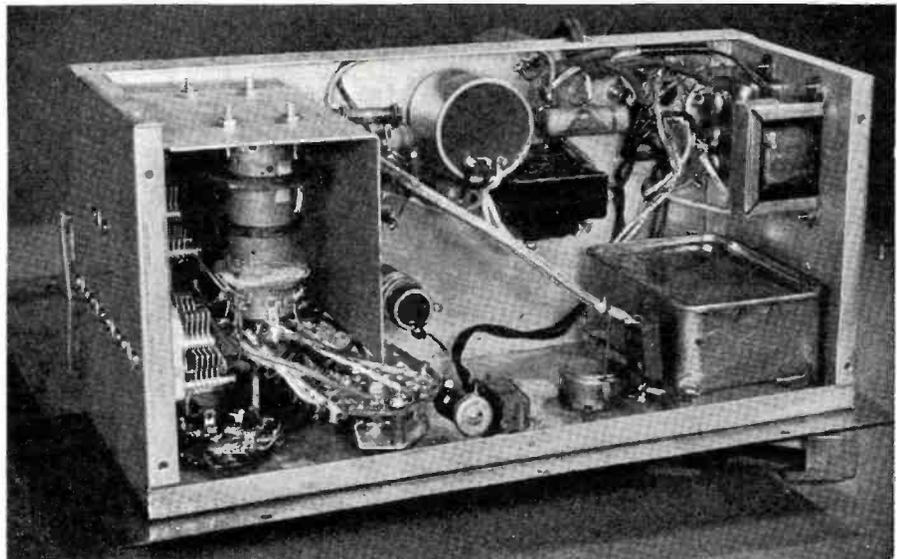

Where Will You Find Them?



← A good source of sales prospects is your prewar listing of customers. If you have lost touch with these people—bring your list up-to-date right now.

→ Your distributor or jobber is a good man to tie onto. He will give you names of prospects he has received for your territory. When your distributor gives you a name—make the call at once while the sale is active.



→ The mailman can give you much information on the whereabouts of your former customers and names of newcomers in your neighborhood. Keep him in mind.



← Meter readers get around. They know when new people move into your neighborhood. Good relations with them will pay off in increased business.

← Marriage license listing tell more than that another couple has said "I do." They are prospects par excellence for all types of appliances and radios.

NOW that the sellers' market has done a rapid about face and become a buyers' market, the radio and appliance dealer is again faced with the problem of finding good prospects.

Before the great rush of competition begins, it would be well for each and every dealer to start compiling a list of persons to whom he wishes to sell his line. This compilation cannot and should not be a hit or miss affair. Since your list will be the one from which your salesmen will work, your mailings will be made, and to whom your advertising messages will be addressed, it must be as complete and accurate as possible. Your file will be of little use to you if it contains the names of persons who have moved from your primary service area, people who are no longer financially able to purchase your products, or persons whose status as householders has undergone a drastic revision.

Shown on this page are eight tested methods of getting sales prospects. Perhaps all of these methods are not applicable to your particular community, but some of them are worth your consideration.


After compiling your prospect list, keep it up-to-date by constant revisions, additions and deletions. One excellent way to test your sales list is to make a mailing to all persons whose names appear on your records. If these letters or circulars are sent first class mail and in return address envelopes you can revise your list in the light of the mail which is returned to your office. This system is of no use unless all returns are carefully checked against your master copy—so don't adopt this plan unless you are willing to carry through with the scheme.

Business may be a bit slow now while your customers are shopping around or waiting to buy—so now is a good time to get your lists made out and the clerical work in connection with such a listing completed. It is not too early to get a head start on your competitor—in a few months you will be glad you had the jump on him!

—30—



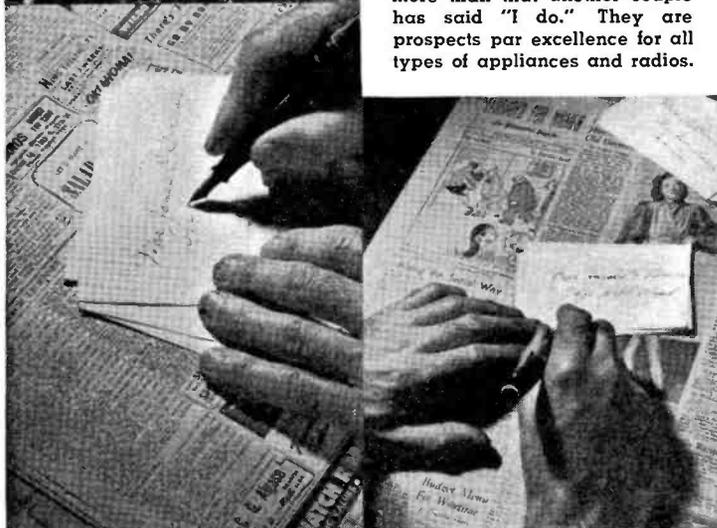← You can't go wrong in maintaining friendly relations with the milkman. He knows a lot about newcomers in your particular sales territory.



← A society page will provide a lot more information of importance to you than you might think possible. Try reading it carefully for the names of new and usually excellent prospects.



↑ The telephone book can help you bring your mailing list up-to-date in addition to furnishing you with names of newcomers.

The RECORDING and REPRODUCTION of SOUND

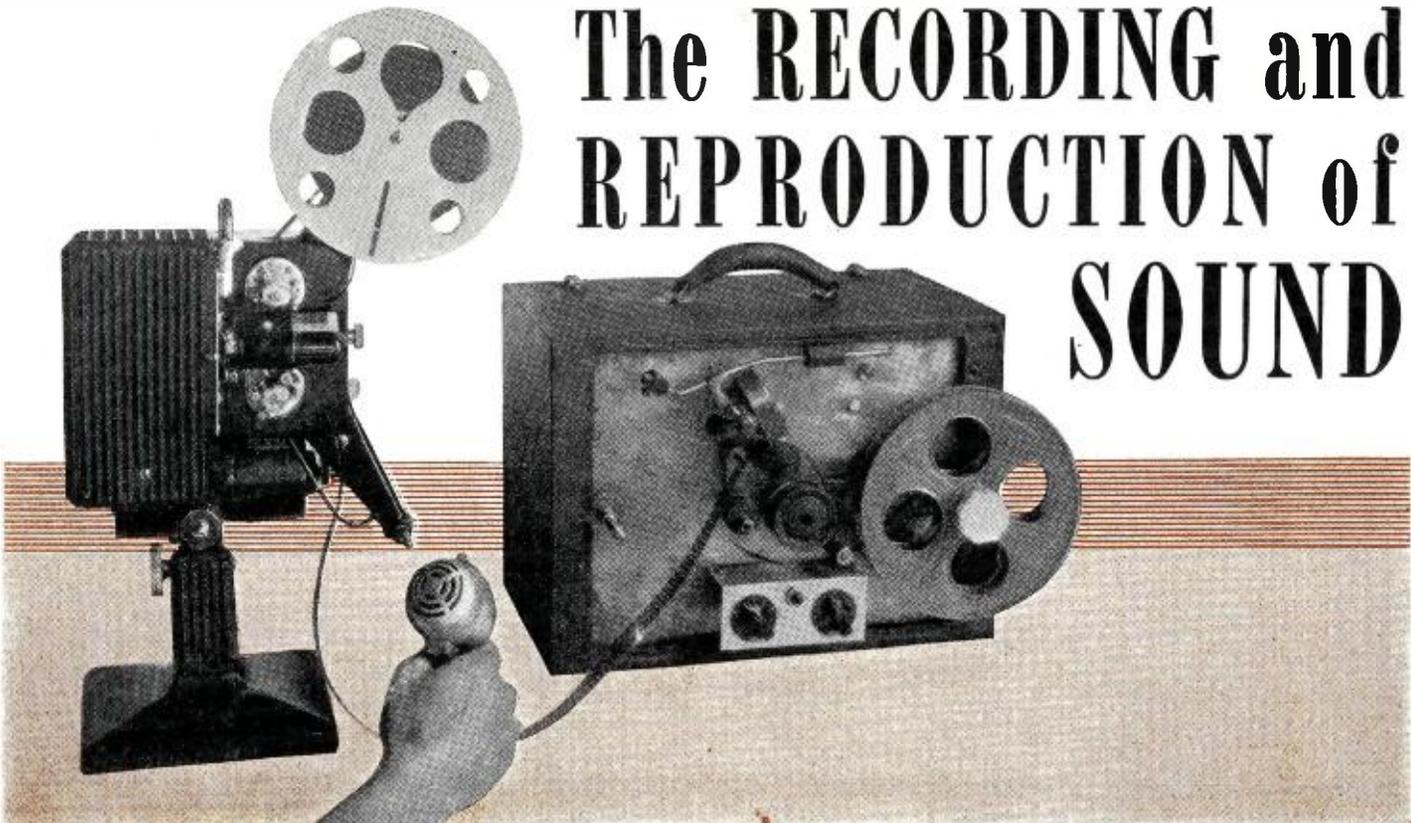


Fig. 1. A 16 mm. Filmgraph recorder in operation with home movie projector.

By **OLIVER READ**

Editor, RADIO NEWS

Part 3. Introduction to basic methods for embossing sound on film and disc, magnetic recording on tape, disc, and wire, and optical film recording systems.

SO FAR we have dealt briefly with the lateral type of disc recording whereby a moving stylus actually cuts from and modulates a groove in a plastic or lacquer coated disc. Several improvements have been made in order to gain more time on a record of given size. Among these are the methods for embossing sound on disc at constant groove speed.

Constant groove speed, as the words imply, means that the linear speed of the recording track or groove, in inches per second, is fixed (see Fig. 2A). This remains constant regardless of record diameter. In the conventional phonograph, a fixed turntable speed is employed resulting in a very high speed in the outer circumference. Linear speed becomes progressively slower as the smaller inner circumferences are approached (Fig. 2B). The result is that varying amounts of distortion of the original sound are present. This is especially true at 33½ r.p.m. In order to compensate for the variable speed, several forms of equalization are required in order to boost the high notes as the speed becomes slower at the smaller diameters.

Constant groove speed techniques have been employed successfully in

the design of highly efficient dictating machines such as the *Gray Audograph*. Vinylite records 10/1000 in. thick in sizes from 5½ to 8½ in. in diameter provide up to 31 minutes of dictation.


A roller drive at the stylus head provides constant recording speed. This speed is selected so that the maximum amount of dictation consistent with high intelligibility in sound reproduction can be embossed on the record (260 lines to the inch). This driving method does not require an extra mechanism to change rotational speed as the record center moves away from the stylus. The combination recording and reproducing head is illustrated in Fig. 3.

Three problems are encountered in playback stylus design; adjustment to vertical irregularities, adjustment to minute deviations from the Archimedes spiral that is theoretically traced during recording, and sensitive reproduction of the modulation pattern. The *Audograph* playback system comprises a stylus fixed on a flexible arm that is mounted on a heavy bar, a magnetic sleeve vertically set on the arm, a pivot shaft rubber-mounted in the sleeve, and a stationary coil surrounding the sleeve. Permanent magnets in the stylus head form a field about the

coil. Lateral compliance is furnished by the heavy bar turning on the pivot; vertical compliance by the spring-loaded flexible arm.

Modulation reproduction can be followed from the schematic sketch. The groove force acts on the flexible arm through the stylus and weak torsion resistance, caused by the notches in the rear of the flexible arm, will permit the arm to tilt. This action tilts the sleeve mounted on the arm. As the ends of the sleeve rock forward, (one pole, then the other) lines of flux

Fig. 2. (A) Modulation by constant groove speed. (B) Constant hub speed produces variable groove speeds.

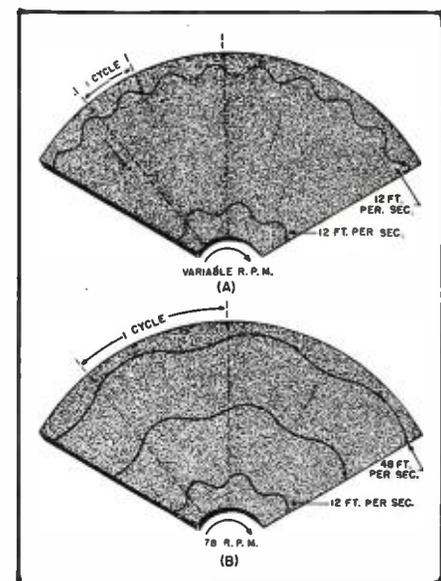

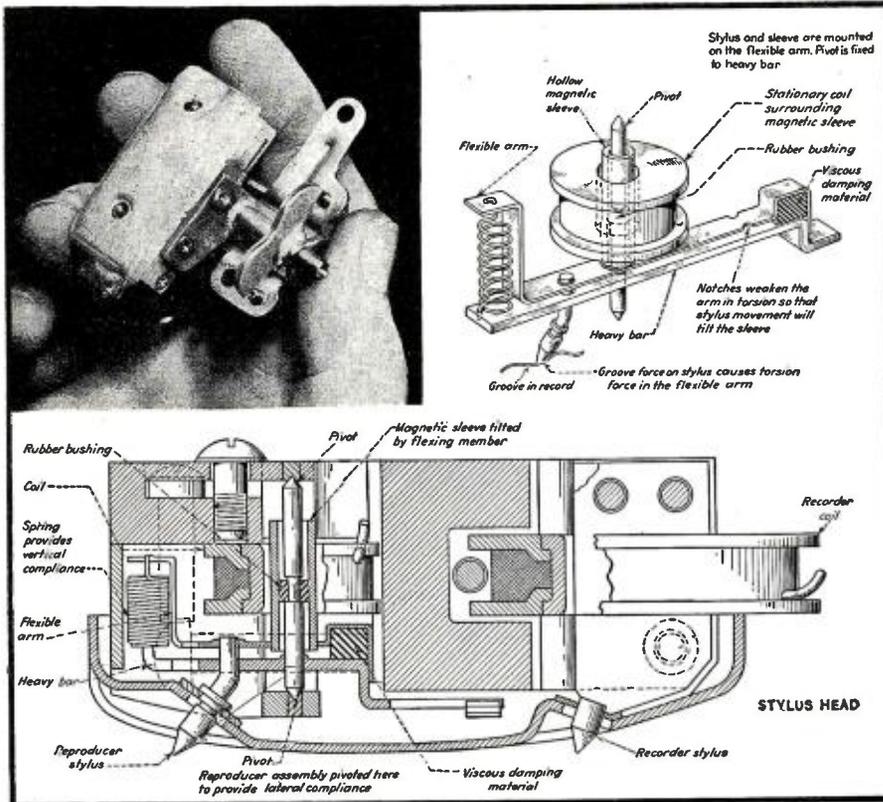



Fig. 3. Audograph record-playback head for embossing sound on Vinylite records.

flow through the magnetic sleeve, first in one direction and then in the other. This induces a voltage in the coil that electrically repeats the modulation pattern.

A belt reduction drive from the motor turns the driving roller. The idler

roller, pressing the record against the driving roller, turns the record at a constant groove speed which is maintained throughout the recording. The angular velocity varies with the linear distance of the driving roller from the record axis. As the record turns the

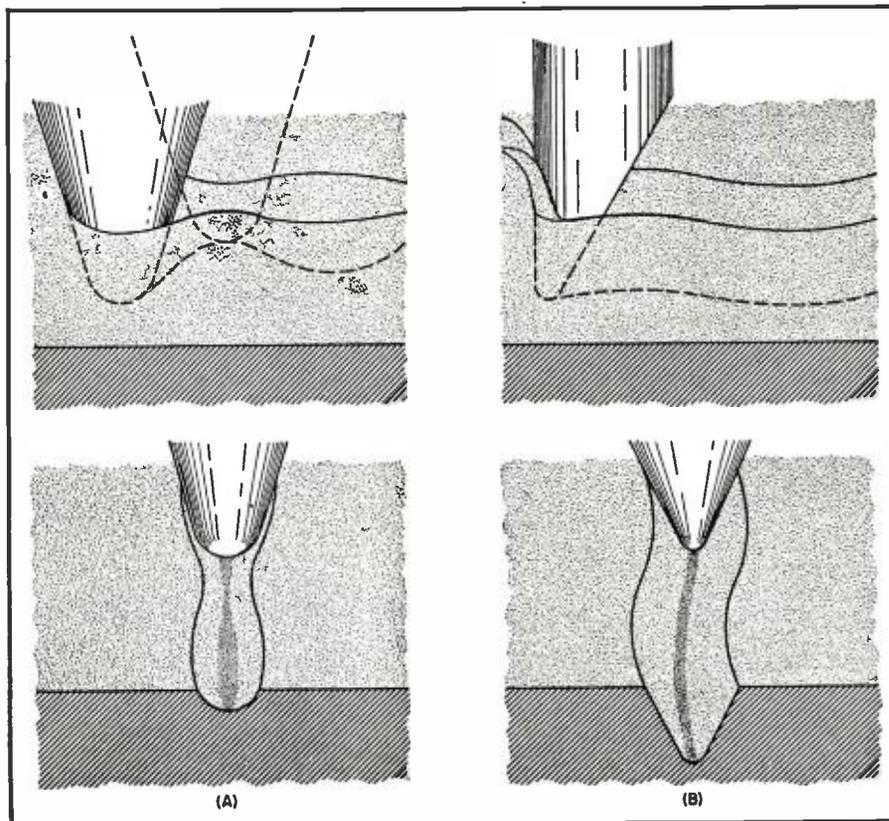(A) Embossing action of a dull stylus moving vertically. (B) Engraving action of a cutting stylus that is moving laterally.



spindle, the carriage mechanism inside the case moves the record to the left.

A worm gear on the end of the spindle shaft engages a pinion on the end of the feed screw. Thus when the record turns, the feed screw is rotated. The feed screw, turning in engagement with the fixed worm pinion, is moved to the left, taking with it the carriage assembly that holds the spindle and record. In this manner, the record is slowly moved to the left while the driving roller rotates it beneath the recording stylus.¹

Sound on Film

Original talking motion pictures were made possible by means of sound recorded on regular transcription discs and synchronized with the action as it appeared on the screen. This method became obsolete and was supplanted by the improved optical sound-on-film systems.

There are two general methods for recording sound on film. One is the *Movietone* method wherein the variations in sound are produced by *variable density* (variations in light through a sound track). This sound track has constant width along one edge of the film. See Fig. 4A. The other most commonly used method is the so-called *variable area* type. (*R.C.A. Photophone*.) Here the density remains fixed while the width of the sound track varies in accordance with the sound, as illustrated in Fig. 4B.

Variable density recording depends primarily upon the action of a "light valve." Basically, this valve consists of a loop of duraluminum ribbon, .003 in. thick and .006 in. wide, which is suspended in a very narrow slit between the two pole pieces of an electromagnet. Light from the exciter lamp is condensed and focused by means of a condenser lens system into a tiny path which shines through the slit in the light valve formed by the position of the duraluminum ribbons (Fig. 5). An objective lens system focuses and concentrates the tiny light beam onto the sensitized negative film which is traveling at a speed which is synchronized with the picture camera. The audio currents produce varying magnetic fields through the duraluminum ribbon loop. The varying magnetic fields cause the sides of the ribbon to repel each other. The amount of audio current flowing through the coils on the magnet governs the width of the slit, which in turn limits the amount of light that can pass through.

Reproduction from sound on film, employing the *variable density* technique, is shown in Fig. 6. The light from the exciter lamp, being focused into a very narrow beam, actually shines through the film to the photoelectric cell. The photocell, which is sensitive to variations of light, will pass minute variable electrical currents. These are then amplified by the audio system and fed through the

¹ Product Engineering, November 1946.

loudspeakers. The changes in the frequency of the sound are determined by the number of changes in film density per-inch-length of the sound track. The changes in the intensity of the sound are determined by the changes in the density or darkness of the lines on the sound track as the film passes the narrow beam of light. The light and dark lines on the sound track are continually interrupting the light going through the film. These interruptions vary the output currents of the photo-electric cell. Upon amplification, these variations or interruptions appear as sound waves and are heard through the speaker.

The fundamental setup for recording sound on film by means of the *variable area* method is shown in Fig. 7. Recording is accomplished by means of an oscillograph whose mirror is actuated by the variations in the intensity and frequency of the output voltage of the photocell. This, accordingly, throws a strong beam of variable light onto a moving film. These variations of light correspond to sound variations. They are recorded as a single heavy jagged line that looks very much like a series of high mountain peaks, as might be observed from a distance. Reproduction is similar to that of Fig. 6. Complete sound-on-film systems will be thoroughly discussed in later articles.

Embossing Sound on Film

One of the newer developments in sound-on-film is the technique employed to *emboss* sounds by means of a vertically driven stylus directly onto specially prepared film. See Fig. 8. One such machine, the *Filmgraph*, employs an endless loop of film which is placed in a magazine. The recording time depends upon the length of the loop used. Loops can be used for fifteen minutes', one hour's, two hours', five hours', and even up to eleven hours' recording. The loop moves forward continuously through the machine and no rewinding of the film is necessary. For example, if the recording is started on track No. 1, it automatically moves over to track No. 2 at the end of recording on track No. 1. This automatic movement continues until all tracks across the width of the film are indented or embossed. The track on which material is being recorded is indicated on a dial and this number changes as the stylus moves from one track to the other. Any track may be played back at any time by moving the stylus manually, by means of a control knob, to the desired number. Means are provided to start and stop the recording or playback instantly on a single word or syllable. A speed control is used on this type of machine for recording or playback.

The sound track is formed by indenting a groove into the film. The 16 mm. film is five-eighths of an inch wide and five-thousandths of an inch thick. A permanent type sapphire stylus of special design is used in the

dual-purpose head for recording and playback.

The number of sound tracks that can be recorded on film depends on the physical width of the film. Sixteen or thirty-five millimeter film provides between forty and one hundred sound tracks. Sound may also be recorded on home movie film as shown in Fig. 1.

On the *Recordgraph* machine, sound is permanently embossed on thirty-five millimeter cellulose acetate film having a base material which is fire resistant and free of abrasives. No processing of the film is required before reproduction. Continuous recording with automatic trackover from groove to groove in the film is available. One hundred and fifteen tracks can be accommodated on one side of thirty-five millimeter film. Means are provided for the recording and also the locating of a particular track for playback as desired.

One of the earlier known methods of embossing is known as the *Western Electric* hill-and-dale recording technique. This is still used for many electrical transcriptions. Instead of a stylus moving laterally within a groove of a record, the stylus moves in a vertical plane and sound is actually cut and embossed by this motion.

Magnetic Recording on Film

The first talkies used the phonograph disc synchronized with the picture as mentioned previously. An optical sound track, however, proved itself better for most sound-on-film work. It is now used almost exclusively. *Magnetic* recording on film apparently has been neglected although it has some worthwhile advantages over the conventional optical systems.

Any system, no matter how successful in its application, has certain advantages and disadvantages compared to other methods. In optical recording systems we find that there is better resolution and better high frequency response at a given speed. There is no direct contact of the recording head with the film and neither is there any wear or clogging problem. The duplication of films recorded by the optical system may be accomplished



(A)



(B)

Fig. 4. (A) Variable density sound track on 35 mm. movie film. (B) Variable area sound track as it appears on a single frame.

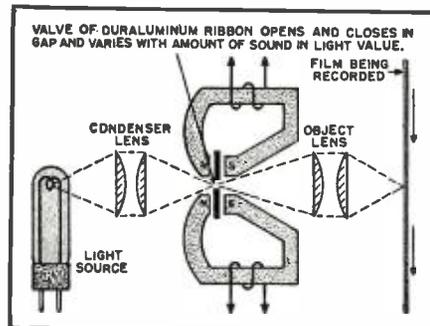



Fig. 5. The essential elements employed in variable density recording.

easily by direct contact printing.


The disadvantages of the optical recording systems are briefly as follows: The films must be developed before the sound can be played back. They are relatively expensive and cannot be monitored immediately and as far as film technique is concerned, film must be handled in the dark and the processing requires highly skilled labor.

In the case of magnetic recording
(Continued on page 102)

Fig. 6. Basic system for reproducing sound on film by optical methods.

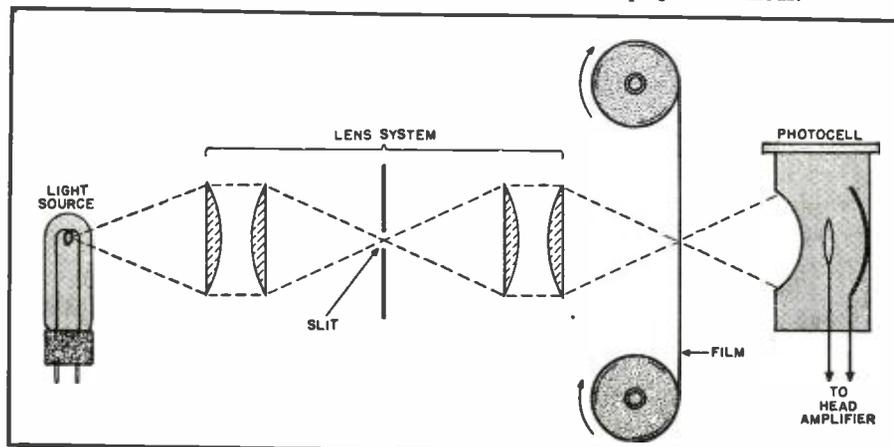

Practical RADIO COURSE

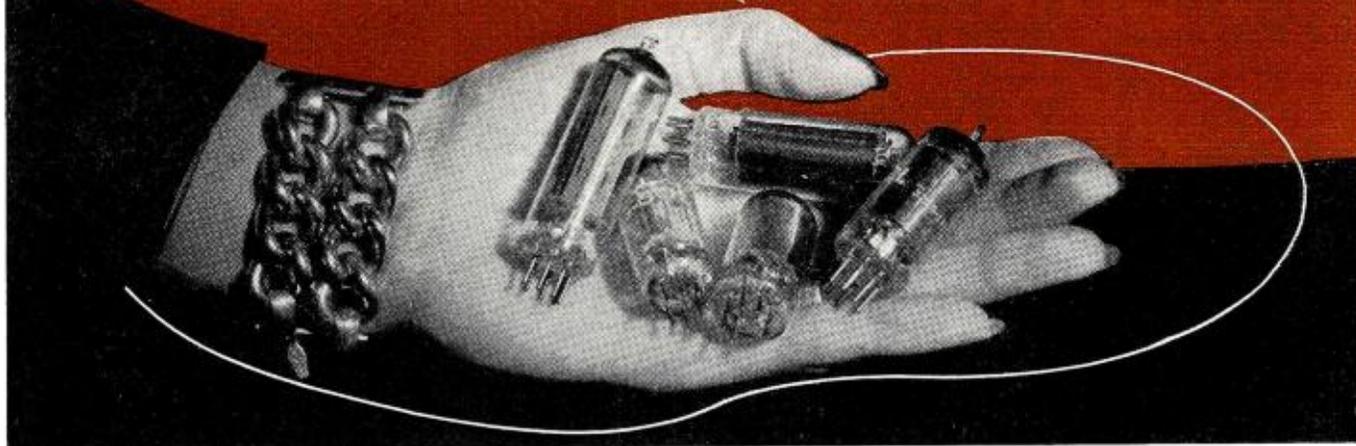

As soon as production permits, these new miniature tubes will be used in 5-tube, table model, a.c.-d.c. receivers. This new tube kit will consist of 35W4, 50B5, 12BA6, 12BE6 and 12AT6. They will replace the 35Z5, 50L6, 12SK7, 12SA7 and 12SQ7 respectively.

By **ALFRED A. GHIRARDI**

Part 53. Important factors which must be considered when choosing i.f. frequency of a superheterodyne.

If superheterodyne receivers are to provide satisfactory reception, very careful design of the i.f. amplifier (see Fig. 1) is necessary because they are subject to certain serious interference effects (spurious responses) that are largely controllable by the design of this amplifier. Probably the most important single factor in the design of a successful superheterodyne that will be free from such spurious responses is the choice of the intermediate frequency to be employed.

Unfortunately there is no simple, clear-cut choice of the best i.f. to employ for any particular class of receiver service, for this choice is intimately tied up with a number of conflicting requirements that make it

necessary for receiver designers to choose for this frequency value one that enables them to provide the best possible compromise as regards receiver cost and physical dimensions, adequate high amplification, and freedom from objectionable spurious responses due to various causes. Consequently, it is important to understand these controlling factors and the effect of the i.f. value upon each of them.

How I.F. Employed Affects Adjacent Channel Selectivity

In an AM receiver, adjacent-channel selectivity is the ability to discriminate against interfering signals on an adjacent broadcasting channel 10 or 15 kc. removed from the desired sig-

nal frequency. Detailed discussions of adjacent-channel (arithmetical) selectivity that were presented in two earlier articles¹ of this series clearly explained the reasons for the following very important inherent characteristics possessed by i.f. amplifiers:

1. *The major portion of the adjacent-channel selectivity of practical superheterodynes resides in the i.f. amplifier and results from the frequency conversion action in the superheterodyne.*


2. *The lower the i.f. employed, the greater will be the percentage frequency separation between the wanted signal and any unwanted adjacent-channel signal after frequency conversion has taken place; consequently the greater will be the adjacent-channel selectivity and rejection of the unwanted adjacent-channel signals.*

It is apparent that if the desirability of making the adjacent-channel selectivity as great as possible were the only factor involved, it would be advantageous to employ as low a value of i.f. as possible. Use of a low i.f. would have the further advantage that it would permit high gain per stage to be easily and cheaply obtained. However, several important conflicting considerations enter into the picture and, for a receiver designed to operate over a particular signal-tuning range, they place a definite practical limit on how low the i.f. may be made. The most important of these is the probability that image-frequency interference will occur.

Image-Frequency Interference

It will be recalled from an earlier article of this series² that image inter-

Fig. 1. Elements of a typical single stage i.f. amplifier between the frequency converter and the diode detector of an AM receiver. It employs two double-tuned coupling transformers and a single pentode i.f. amplifier tube.

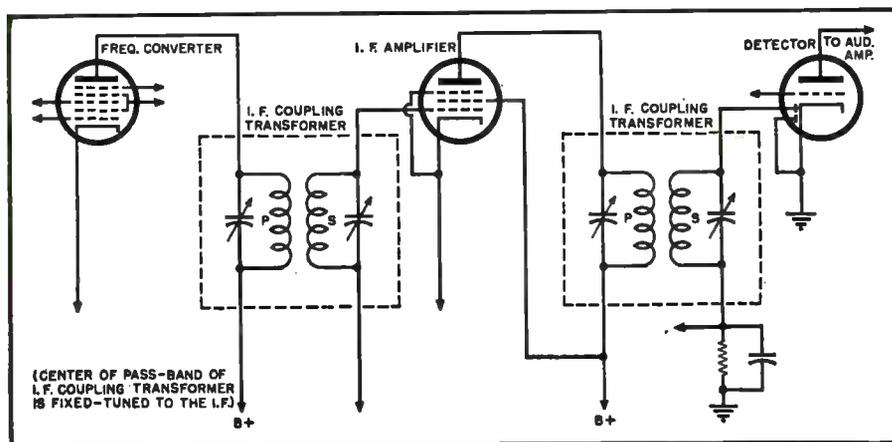

¹ For detailed explanations of adjacent-channel interference and selectivity see Alfred A. Ghirardi, Practical Radio Course, Part 26 (RADIO NEWS, Sept., 1944) and Part 52 (RADIO NEWS, March 1947).

² For a detailed explanation of image-frequency interference see Alfred A. Ghirardi, Practical Radio Course, Part 27 (RADIO NEWS, Oct. 1944).

ference, the interference caused by any sufficiently strong received signals having a carrier frequency *higher*³ (see Fig. 2A) than that of the desired signal by an amount numerically equal to *twice* the i.f. employed in the receiver ($f_{image} = f_{sig.} + 2f_{int.}$), is one of the outstanding undesired responses in superheterodynes. Figs. 2A and 2B show why a signal of this frequency will interfere with the desired signal. It is important that this type of interference be effectively reduced to a minimum in order to obtain satisfactory reception of desired signals.

It is evident that the i.f. value employed in the receiver has an important bearing upon whether or not image interference will be experienced during reception of any desired signal. The tabulation presented in Table 1 is interesting in this connection because it shows the AM broadcast signals that can be expected to be involved in image-frequency interference with one another when receivers employing the i.f. values indicated at the top of each column are used in the various localities specified in the left-hand column. For example, in New York City if a superhet receiver employing a 450 kc. i.f. amplifier is tuned to receive the 660 kc. signal from station WNBC, the 1560 kc. signal from station WQXR will tend to cause image-frequency interference with it. This is so because 1560 kc. is the *image frequency* for a superheterodyne receiver tuned to 660 kc. and employing a 450 kc. i.f. that is, $(660 + (2 \times 450) = 1560$ kc. Therefore, an incoming signal of this image frequency will be converted to a 450 kc. signal by the frequency converter in the receiver and be passed and amplified (along with the desired signal) by the i.f. amplifier. Whether or not annoying interference will actually occur in this case depends upon the relative strength of the two signals received at the locality of the receiver's antenna, the image-rejection ratio provided by the r.f. preselector tuning circuits employed in the receiver, etc.

The tabulation of Table 1 also shows that in this same locality if the receiver employs an i.f. of 455 kc., image interference cannot occur between the signals of the aforementioned stations but it is apt to occur between the signals of stations WMCA (570 kc.) and WHOM (1480 kc.). On the other hand, if the receiver employs an i.f. of 460 kc., no image interference is apt to occur between any of these signals if the receiver is operated in New York City. However, when this i.f. is employed, image interference might occur between the signals of stations WEEL (590 kc.) and WMEX (1510 kc.) if the receiver were located in Boston and did not employ a sufficient degree of r.f. preselection.

This illustrates how important becomes the matter of what i.f. is employed in a receiver under actual present-day receiving conditions in various localities.

It is important to remember that once the "conversion" of the wanted

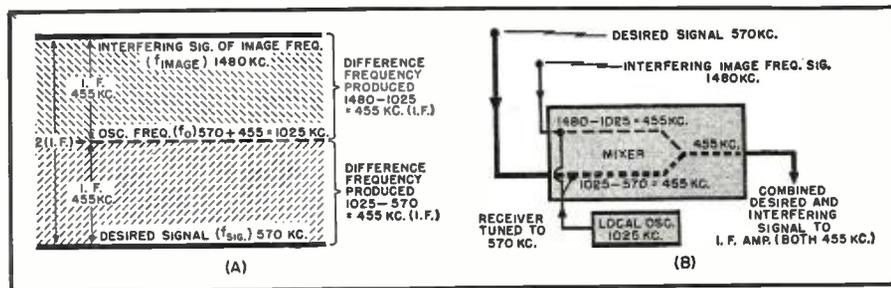


Fig. 2. (A) Should a superheterodyne receiver with an i.f. frequency of 455 kc. be tuned to 570 kc., a 1480 kc. image frequency interference will result. (B) How a desired and an image response signal can combine with the local oscillator output to produce two signals, both having a frequency equal to the i.f.

signal and an unwanted interfering signal of image frequency to a "common" intermediate frequency has been effected in the frequency converter (see Fig. 2B), they are inseparable, and no subsequent degree of selectivity in the i.f. amplifier will attenuate one of the signals more than the other. The interfering signal of *image frequency*, after its conversion to the intermediate frequency, is just as acceptable to i.f. amplifiers as is the *desired* signal after its conversion to the same i.f. The i.f. amplifier does not discriminate between them in any way.

It is quite obvious then that either, or both, of two courses are open to the receiver designer:

1. The undesired interfering image-frequency signal must be eliminated *prior* to its reaching the frequency-converter stage, or,
2. An i.f. value must be such that no possible signal that could be received (at the locality) with sufficient strength to cause annoying interference will be of the correct frequency to qualify as an *image-frequency* signal.


Use of Preselector for Suppressing Image Signal

In the first method, sufficient r.f. preselection⁴ (pretuning) is employed by providing specially designed variable-tuned r.f. preselector circuits ahead of the frequency converter. This provides sufficient r.f. selectivity ahead of the frequency converter so that the

³ In superhets whose oscillator frequency is normally maintained higher than that of the incoming signal by an amount exactly equal to the i.f. for which the receiver is designed.

⁴ For a detailed explanation of preselector circuits see Alfred A. Ghirardi, *Practical Radio Course*, Part 28 (RADIO NEWS, Nov. 1944).

Fig. 4. (A) How proper selection of i.f. value employed in a receiver can prevent a particular incoming signal from qualifying as an image frequency interfering signal. (B) Diagram illustrates how the 1480 kc. incoming signal of (A) is attenuated and eliminated by the tuning circuits of the i.f. amplifier.

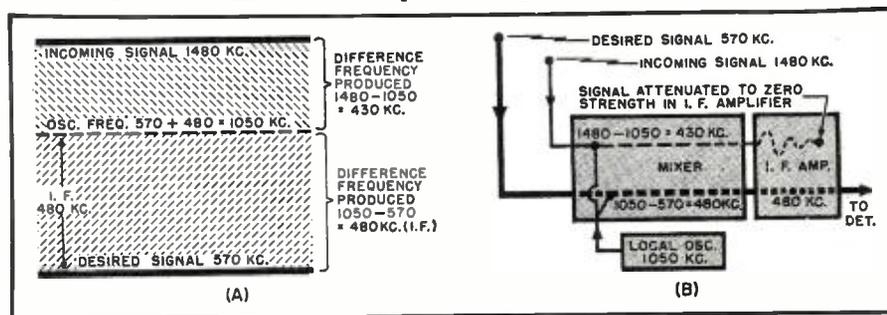

Locality	450 kc. I.F.	455 kc. I.F.	460 kc. I.F.	465 kc. I.F.
Boston, Mass.			WEEL-590 WMFX-1510	
Charleston, W. Va.		WCHS-580 WGKV-1490		
New York City	WNBC-660 WQXR-1560	WMCA-570 WHOM-1480		WMCA-570 WRWL-1600
Omaha, Neb.	WOW-590 KBON-1490			
Syracuse, N. Y.			WSYR-570 WOLF-1490	
Spokane, Wash.			KHQ-590 KGA-1510	
San Antonio, Tex.	KTSA-550 KABC-1450			

Courtesy of RCA Service News

Table 1. Broadcasting station signals and their carrier frequencies that become involved in image frequency interference in certain cities when the various i.f. values indicated are employed in the receivers.

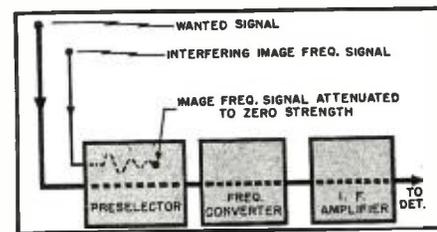


Fig. 3. Illustrating how an image frequency signal may be sufficiently attenuated by a preselector so that it does not reach the frequency converter.

image-frequency rejection ratio will be high and all signals of image frequencies will be sufficiently attenuated so they do not cause interference. The action is illustrated in Fig. 3.

At AM broadcast-band frequencies (535 to 1605 kc.) it is usually sufficient to include a well-designed tuned r.f. preselector ahead of the frequency converter to completely eliminate all

(Continued on page 124)

SENSITIVE PROBE uses Crystal Diode

Complete details for constructing
a multi-purpose a.f.-r.f. probe.

By RUFUS P. TURNER, W1AY

Consulting Eng., RADIO NEWS

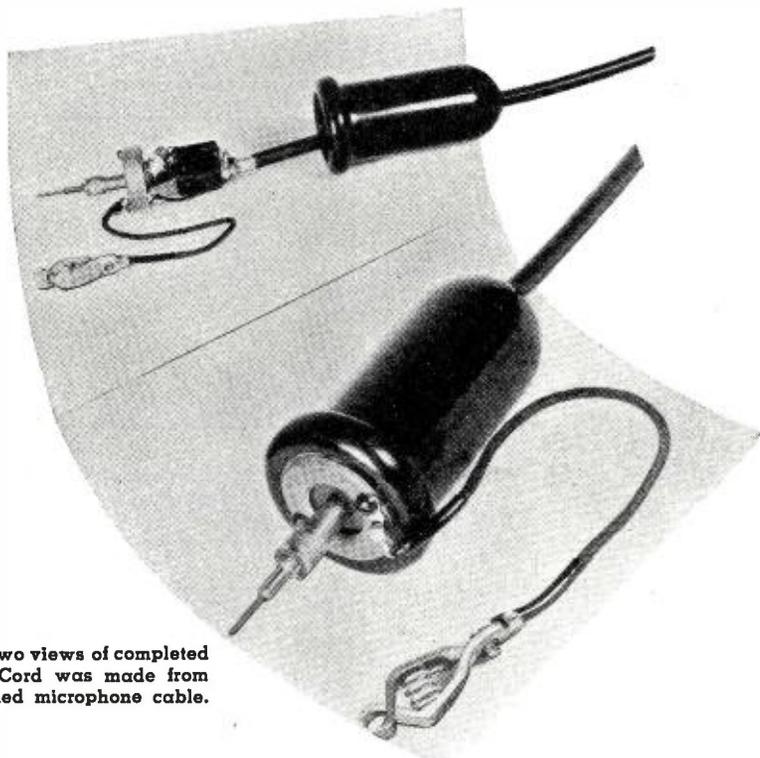



Fig. 1. Two views of completed probe. Cord was made from a shielded microphone cable.

Or it may be connected directly to a pair of headphones or to a magic-eye indicator tube. The probe may be used in measuring up to 100 megacycles, and it is provided with an .02 μ fd. input capacitor which isolates the crystal from direct current components. The circuit schematic appears in Fig. 2B.

The probe shown in the photograph, is built into the plastic case of a hospital pushbutton. This housing was used because it is unusually rugged, being thick molded, and fits the hand comfortably, having originally been intended to be grasped by a bedridden patient for ringing the nurse call bell. The threaded metal disc through which the pushbutton originally extended was unscrewed from the plastic housing and the switch mechanism removed. A thin bakelite disc (to cover the pushbutton hole) was attached to the inside of the metal disc by means of two 5-40 screws easily seen in Fig. 1. A 6-32 screw passes through a hole drilled in the center of the bakelite disc and holds the prod tip. The cord is a length of shielded microphone cable. Other builders may prefer other types of housings. Much latitude is permissible in this direction. Indeed, the small sizes of the crystal diode and of present-day capacitors and resistors make it possible to reduce the probe size to the dimensions of a jumbo multimeter test prod.

The crystal probe presents a high value of input impedance to the circuit under test. A low capacitance likewise is presented. These desirable characteristics reduce loading and detuning effects. Connected to high-resistance headphones, the probe is invaluable for tracing a signal through a radio circuit or audio amplifier; locating hum, oscillation, or noise; or localizing distortion. Connected to a d.c. vacuum-tube voltmeter or magic eye indicator, the probe makes possible the measurement of r.f. and a.f. voltages with negligible frequency error. It can serve also as a tuning indicator.

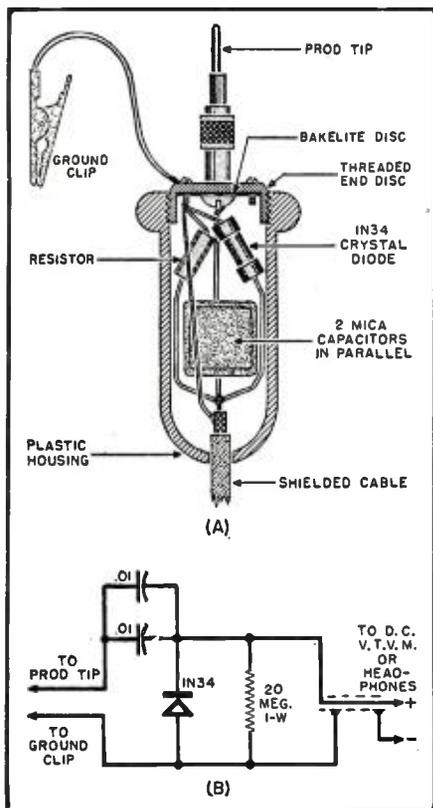Here is a useful accessory which is inexpensive, easy to build, and simple to operate.



A SYLVANIA 1N34 germanium crystal diode is the heart of the multi-purpose a.f.-r.f. probe shown in Fig. 1. This device will be useful to experimenters, amateurs, and servicemen. A crystal probe has the advantages that it can be made much more compact than the tube type probe, it requires no power supply of any kind, and it is free from the contact potential effects common to diode tubes. The 1N34 crystal diode may be used entirely safely whenever the inverse peak voltage does not exceed 50 volts.

The shunt capacitance of the 1N34 crystal diode is only 3 μ fd. in contrast to the 15 μ fd. (approximately) of the 6H6 tube ordinarily employed in home-made probes.

The probe illustrated here may be used in radio-frequency and audio-frequency voltage measurements or in a.f. and r.f. signal tracing by connecting its two output leads directly (or through a 1 megohm, 1 watt series resistor) to a d.c. vacuum-tube voltmeter such as the *VoltOhmyst*.

Fig. 2. (A) Structural details of probe. (B) Circuit diagram of probe. In using the 1N34 crystal diode, all contact potential effects, common to conventional diode tubes, are eliminated.

Narrow Band Phase MODULATION EXCITER

An inexpensive exciter unit that can be used to frequency modulate your present rig.



By
SOL STERMAN, W2JWX*
Newark Electric Company, Inc.

Front view of crystal controlled exciter unit shows parts placement. Jacks J₁ and J₂ are mounted on rear flange of chassis.

the 6SL7, r.f. is fed from the grid to the plate in two ways. One is by direct grid-to-plate capacity and the other by the electronic amplification of the triode. Degeneration due to the high unbypassed resistor in the cathode circuit keeps these two voltages nearly equal and slightly less than 180 degrees out-of-phase. The magnitude of the electronically amplified voltage will vary as the bias is varied by the audio input through C₄. This action changes the phase relationship between these two voltages and causes a current which is varying in phase to flow in the tank circuit.

The deviation produced by phase
(Continued on page 118)

BELIEVING that many hams will want to incorporate a narrow band phase modulation exciter into their present rigs we are describing this unit which produces the effect of equivalent frequency modulation.

The unit, as shown, is intended to replace a 40 meter crystal or v.f.o. for exciting a transmitter operating in the 26, 11, or 10 meter bands. The crystal oscillator is on 80 meters and the output of the doubler stage is on 40 meters.


This exciter presents several advantages to the amateur. It practically eliminates most cases of broadcast interference; it eliminates the necessity for class B modulators and drivers with their associated power supplies, thus permitting any c.w. transmitter, up to 1 kw. input, to be used for phone transmission in the 10 and 11 meter bands; and input to the final amplifier may be the same as in the case of c.w. ratings.

Theory

One half of the 6SL7 operates as a conventional Pierce oscillator while the second half is the phase modulator. This dual purpose tube is followed by a straightforward doubler. The two high gain audio stages are also conventional.

The output of the crystal oscillator is coupled by means of C₂ to the grid of the phase modulator section of the 6SL7 whose tank circuit is tuned to the crystal frequency. In this half of

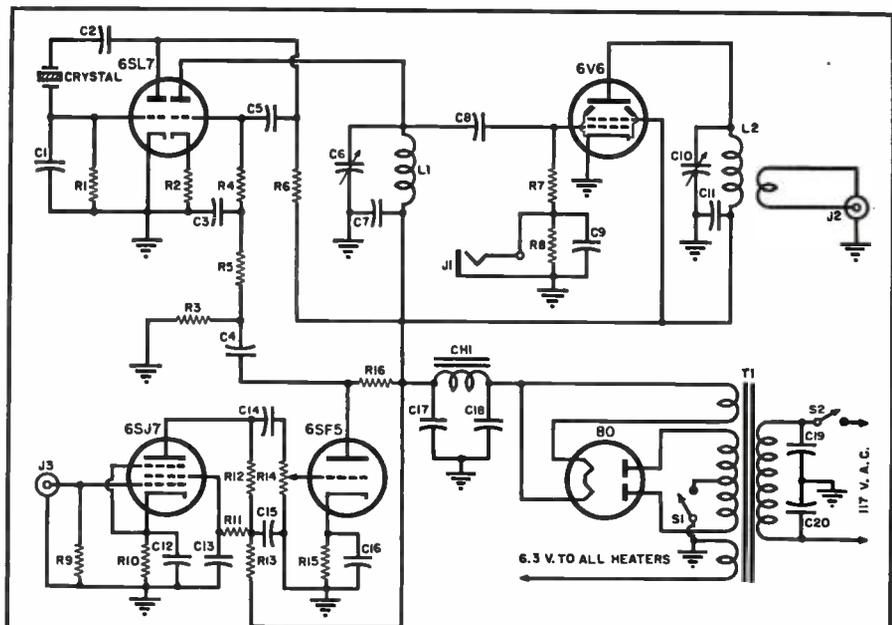Schematic diagram of exciter unit. Either a crystal or dynamic mike can be used.




R₁—20,000 ohm, 1/2 w. res.
R₂—30,000 ohm, 1/2 w. res.
R₃, R₇, R₁₃—100,000 ohm, 1/2 w. res.
R₄—30,000 ohm, 1/2 w. res.
R₅, R₁₂—250,000 ohm, 1/2 w. res.
R₆—50,000 ohm, 1 w. res.
R₈—1000 ohm, 1/2 w. res.
R₉—5 megohm, 1/2 w. res.
R₁₀—1500 ohm, 1/2 w. res.
R₁₁—1.5 megohm, 1/2 w. res.
R₁₄—10,000 ohm, 1/2 w. res.
R₁₅—2500 ohm, 1/2 w. res.
C₁—50 μfd. mica cond.
C₂, C₃, C₇, C₉, C₁₁—.002 μfd. mica cond.
C₄, C₁₄—.01 μfd., 400 v. cond.
C₅, C₆—100 μfd. mica cond.
C₈, C₁₀—50 μfd. midget var. cond.
C₁₂, C₁₈—10 μfd., 25 v. elec. cond.
C₁₅—.1 μfd., 400 v. cond.

C₁₆—4 μfd., 450 v. elec. cond.
C₁₇, C₁₉—Dual 8/8 μfd., 450 v. elec. cond.
C₂₀, C₂₁—.05 μfd., 400 v. cond.
J₁—Open circuit jack
J₂, J₃—Female connectors
S₁—S.p.s.t. toggle sw.
S₂—S.p.s.t. sw. on R₁₄
CH₁—8 hy., 60 ma. filter choke
T₁—Power trans. 300-0-300 v. @ 60 ma.; 5 v. @ 2 amp.; 6.3 v. @ 2 amp.
L₁—46 t., #28 e., winding length 1" wound on 1" coil form (National XR-1)
L₂—40 meter end linked output coil (B & W type 40 JEL)
Crystal—See text
1—6SL7 tube
1—6SJ7 tube
1—6SF5 tube
1—6V6GT tube
1—80 tube

* The design of this exciter unit is based upon original circuits developed by the Fred M. Link Company of New York.



International SHORT-WAVE

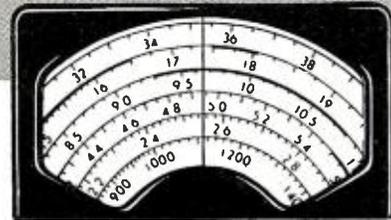

Compiled by **KENNETH R. BOORD**

THIS month's ISW Department is dedicated to The Czech Radio. Direct from M. Gregorova, Foreign Relations Department, The Czechoslovak Broadcasting Corporation, Praha XII, Stalinova 12, Prague (Praha), Czechoslovakia, we have just received a most interesting booklet (in English) dedicated to "listeners abroad," and bearing the title: "The Czechoslovak Radio in War and Revolution."

Here are some highlights from the booklet:

"The Broadcasting Company played a leading and often decisive part in the Prague Rising in May 1945. The call of the revolutionary announcers was one of the first and most authoritative calls to arms to the Czech nation in Prague and in the country. Broadcasting House in Stalinova trida, Prague, was heavily damaged inside and the inevitable repairs will take several months. In spite of this, there was feverish activity as the task of free broadcasting was expanding. Broadcasting House was sanctified by the blood of those who had come to the aid of the Broadcasting Company on May 5th, who had fought bravely inside the building and in the surrounding streets, and of whom more than one hundred had fallen in the struggle, and many had been wounded and some have been in hospitals for many months.

"The Prague Broadcasting Company has today employees who had

been suffering for years under the Nazi boot—but they had been working in illegal movements, had fought and remained at their technical stations, in the studios and everywhere where they had been needed in the center of Broadcasting House and other stations, they had remained in close touch with faithful companions from the trunk exchange and broadcasting stations, that is with the postal employees. They carried on everywhere, regardless of bombing and shooting. They now work again together with their new colleagues of the Czechoslovak Broadcasting Company, who had fought and worked abroad, separated from their families for the last few years, who had been broadcasting or taking part in other related branches of the resistance movement abroad, for the liberation of the Czechoslovak people and the Republic. Many of those who have come back have not found their dear ones, for they had had to sacrifice their lives and starve in concentration camps for the courage of their relations. The Czechoslovak Broadcasting Company today also incorporates the great organization of 'Soldiers of the Czechoslovak Broadcasting Company' and protects the flag of the 'Broadcasting Battalion' of the Tyrs and Fugner Infantry Regiment 28, forever called after the heroes who defended Broadcasting House. When the building has been repaired, a marble disk commemorating all those employees

who were executed or martyred and who fell during the May Revolution in the Battle for Broadcasting House, will be affixed over the entrance.


"The last German announcement to be broadcast on May 5 was the 'Unterhaltungsmusik' which the Czech announcers allowed the German announcer to make just before noon, after long discussions and constant threats by the German chiefs. After that, announcing was completely taken over by Czech announcers, even though the German intendant threatened them with immediate shooting. One of the greatest provocations, which strengthened the tension, was the very quick reading of the last news bulletin, when a unit of the Czech police entered the building. Outside Czechoslovak flags were beginning to come out.

At about 12:15 the Czechoslovak and American flags were flown on the mast of Broadcasting House; at the attempt to fly the British and Soviet flags, the Germans opened fire. The first revolutionary announcement was a call to the Czech police, the Czech gendarmes, and the Government Militia to come to the aid of the Broadcasting Company, as the Germans were murdering Czech people there. This was at about 12:33, and was one of the most powerful and most decisive signals of the national revolution. From the whole of Prague and the nearby countryside individuals and groups of determined Czechs started off to help their comrades in Broadcasting House. Many unarmed and inexperienced patriots were wounded by German assassins on the way. The battle in the wider circle round the building continued throughout the whole revolution until the coming of the Red Army, the battle in the building itself ended with the defeat of the Germans on the evening of the first day, after a battle of several hours during which Czech patriots fought from floor to floor, entering the building by the only free side entrance and over the roofs of the neighbouring houses.

"Of the later coordination of the revolutionary military forces and of the determination of the people of Prague, bears witness by the fact that, in the most difficult moments on Sunday, the tankists from industrial

(Continued on page 141)

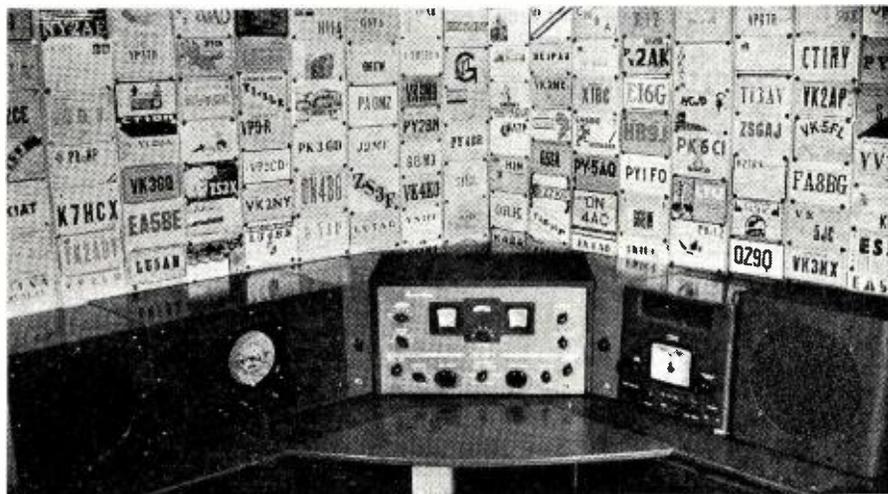This attractive corner is the SW Listening Post of Harry Kentzel, Sand Lake, New York. Receiver (center) is a new Hammarlund HQ129X.



Deluxe Amateur TRANSMITTER

By JAMES N. WHITAKER, W2BFB
Eng. Dept., Hammarlund Mfg. Co.

Part 2. Concluding article covering the design principles for a 1-kw. amateur type transmitter.



Fig. 1. Rear view of transmitter. Front view of this unit was shown last month.

IN CONTINUING the discussion of deluxe amateur transmitter design begun last month, we would like to point out to our readers that the circuit diagram for the complete transmitter was given in the April installment, along with a discussion of the oscillator and frequency multiplier stage. Reference should be made to this discussion before proceeding to a consideration of the driver stage.

Driver Stage

The driver stage uses a 4E27 beam tetrode in a more or less conventional amplifier circuit. When using a tube of this type it is well to observe the manufacturer's recommendations for maximum grid drive. This value should never be exceeded, and satisfactory operation will generally be obtained with driving power considerably below the maximum permitted. In the present instance it was found that the grid current should not exceed 0.3 ma. for optimum operation. With this value of grid drive the 4E27 tube is capable of delivering approximately 225 watts of r.f. power to the final amplifier. The plate and screen

grid power for the driver stage is obtained from the high voltage power supply which supplies plate power to the final amplifier. The full potential is applied directly to the anode of the tube while the screen grid potential is applied to the tube through a 100,000 ohm resistor. A 1200 ohm cathode biasing resistor is connected between the filament center tap and ground to provide normal operating bias for the tube. A 250,000 ohm grid resistor is also used to prevent excessive grid current when the plate potential is reduced and the drop across the cathode biasing resistor decreases correspondingly.

There has been much controversy regarding the use of the new beam type of tubes versus a neutralized triode. Unquestionably much of the reluctance to incorporate these new and wonderful tubes in equipment is due largely to a lack of understanding as to just how they may be satisfactorily incorporated in the equipment. The general complaint seems to be the difficulty in eliminating the tendency toward self-oscillation.

In designing any equipment using a beam tube, always bear in mind the fact that the power sensitivity of this new type of tube exceeds by far the power sensitivity of any tube heretofore known. It is this extremely high power sensitivity that makes this tube so highly desirable, and at the same time so apparently difficult to operate satisfactorily.

In order to successfully design an amplifier using a high-powered beam tube, it is extremely important to bear in mind that a very small amount of feedback, which in a triode amplifier would be practically undetectable will be a very serious amount indeed for a high gain beam tube.

The isolation of the input and output circuits must be as nearly perfect as possible. The r.f. bypassing must be complete with all leads as short as possible. Each filament ter-

minal must be bypassed directly to the chassis as close to the socket terminal as possible. The screen grid must be bypassed to the filament terminals as well as to the chassis, and if the suppressor grid is not directly connected to the filament, it must also be bypassed directly to the filament as well as to the chassis.

If the isolation between input and output circuits is complete, the amplifier will operate as smoothly as a conventional neutralized triode amplifier and the driving power required will be almost unbelievably small compared to the power required to drive any other type of amplifier having an equivalent power output.

If the designer is unable to eliminate feedback entirely, there are several ways to suppress spurious oscillations. One way is to insert a 50 ohm, non-inductive resistor in the screen grid circuit, between the screen grid terminal and the bypass condenser. Another method is to insert a 50 ohm resistor (around which has been wound eight or ten turns of wire forming a small inductance shunted by a 50 ohm resistor) in the grid or plate circuit.

Any of these suppression methods are subterfuges, serving to remove the symptoms rather than the ailment, and are, in reality, an admission that the equipment has not been properly designed.

It is possible to obtain satisfactory operation from a triode amplifier when departing widely from the manufacturer's recommended ratings regarding driving power, grid bias, and plate voltage.

In a beam power amplifier, such departures are a direct invitation to trouble, and should be attempted only by those completely familiar with every detail of the operational theory of a beam tube. Perhaps one of the most difficult things for the amateur to grasp is that the grid drive must be kept well within the maximum limits specified by the manufacturer

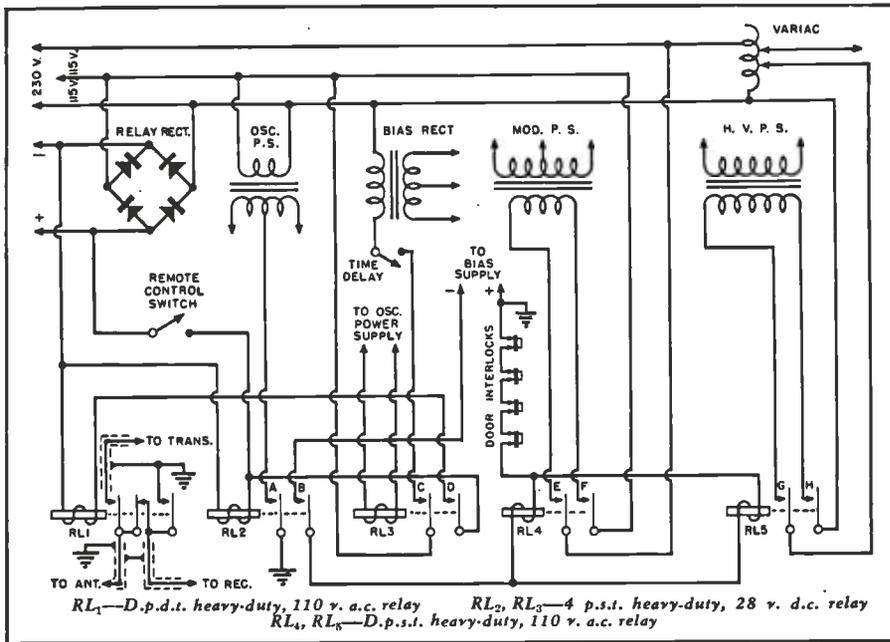


Fig. 2. Complete schematic diagram of remote control system. A copper oxide rectifier supplies power for the remote control relay and the antenna changeover relay.


of the tube. Excessive grid drive can not be tolerated by a beam tube regardless of other operating conditions, and the most satisfactory operation is generally obtained with a grid current of less than one milliamper. The manufacturer's maximum grid current rating is generally the maximum permissible current which will not damage the grid structure or cause sufficient heating of the grid leads to crack the glass seal.

Power Amplifier Stage

A rather wide selection of tubes is

available for use in the power amplifier stage. The choice of tubes depends largely upon the efficiency desired and the power output needed. Since the 4E27 driver stage is capable of supplying sufficient power to drive almost any 1 kw. amplifier stage, any tube or tubes of sufficient power capabilities may be used. One point to bear in mind is that amateur transmitters are limited to a maximum plate input of 1000 watts. For this reason one must consider the efficiency of the final amplifier rather than economy of tubes in order to obtain the greatest possible power output with

Fig. 3. Schematic diagram of the negative peak over-modulation indicator. The neon bulb flashes, indicating when a predetermined modulation percentage is reached.

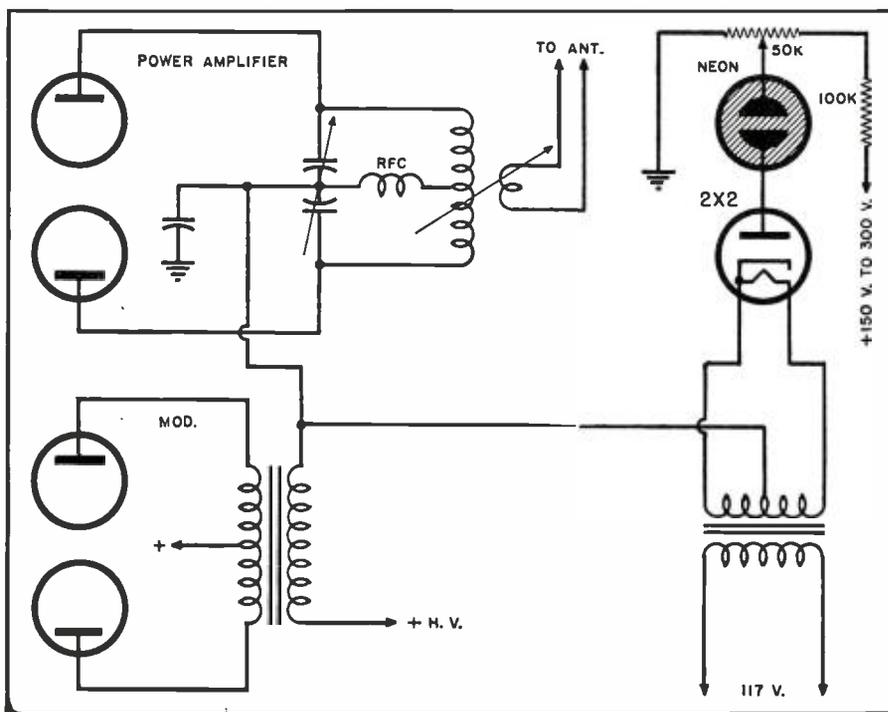

the permissible input. In order to obtain the best possible efficiency it is necessary to use tubes capable of considerably more power than is required. Another very good reason for using relatively high powered tubes is that the output need not be decreased in order to obtain satisfactory high-level modulation. This is not necessarily the most economical way to design a transmitter but it is the most satisfactory way of obtaining a maximum power output from a given input.

The power amplifier stage in a telephone transmitter should be a push-pull stage in order to discriminate against second harmonic radiations. Some objection may be raised because of the possibility of a third harmonic radiation from a push-pull amplifier but these radiations are never as serious as the second harmonic radiations because of discrimination against the higher frequencies in both the plate tank and antenna circuits.


In designing the power amplifier it is important to consider very carefully some arrangement for completely shielding the input and output circuits from each other and from the rest of the transmitter. The most satisfactory method of shielding is to arrange the power amplifier so that the input circuit, the tubes, and the output circuit are effectively in separate compartments with the neutralizing system in the compartment with the tubes. It will be found that with this arrangement the nearest approach to true neutralization is obtainable. If the shielding is not complete, the apparent neutralization will not be true neutralization since a certain amount of input-output coupling will be compensated for in the neutralizing. When this occurs there is danger of feedback, parasitic oscillations, and various other difficulties when the plate power, grid drive, or output coupling is changed. This is a condition which most commonly produces parasitic oscillations during modulation peaks which is easily understood when one remembers that high-level modulation actually varies the input power to the amplifier in accordance with the applied modulating power.

In a push-pull amplifier it is necessary to very carefully design the circuits to provide equal grid driving power to both tubes. The plate loading must also be equal. In practice it is very difficult to design a center tapped coil in such a way as to obtain a perfect electrical balance in each half of the coil. This may not be too serious at frequencies below 14 mc. but at higher frequencies irregularities which are almost unnoticeable may produce a serious unbalance. For this reason it is well to depend on a split stator tuning capacitor to provide electrical center tap rather than to bypass the center tap of the coil to ground. Tuning capacitors are manufactured to very close tolerances and are generally assembled with the aid of very accurate jigs and therefore, for all practical purposes, may be

considered as being perfectly balanced electrically as well as mechanically insofar as capacity is concerned.

Any tuned r.f. circuit is more efficient when the tuning capacitor is connected directly across the inductance. In order to do this it is usually necessary to insulate the rotor of the variable capacitor from ground instead of grounding the rotor section and connecting one side of the inductance to the rotor through a fixed capacitor. This is more important in the higher power stages because of the higher circulating currents but it is important in any stage since there

Fig. 4. Left side view of transmitter.

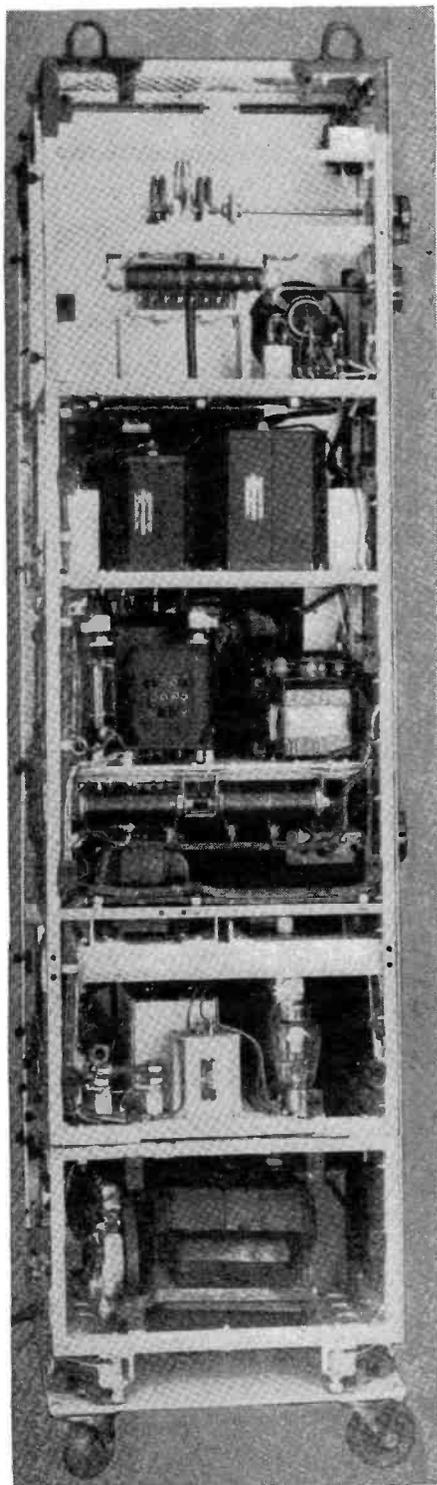

May, 1947

is always a certain amount of loss in even the highest grade of mica capacitors. This is also important in high power stages as it prevents grounding the high voltage power supply in the event that a flash-over of the capacitor occurs.

The antenna coupling circuit should be variable by means of a dial or knob accessible from the front panel. The number of turns and diameter of the coupling coil will depend upon the method of feeding the antenna and if the connection to the transmitter is by means of a coaxial transmission line, the coupling coil will be smaller or will contain fewer turns than if a higher impedance line is used. Where the same antenna is to be used for the receiver and the transmitter, the antenna changeover relay should be mounted inside the transmitter and as close as possible to the coupling coil. The relay and the connection should be adequately shielded from the power amplifier plate tank circuit. The location of the antenna changeover relay adjacent to the output coupling coil is very important where coaxial transmission line is used. If the relay is located outside the transmitter, it will cause a discontinuity of impedance which may result in serious standing waves along the transmission line.

Power Supply System

The power supply systems for a high-powered transmitter do not necessarily have to be complicated. Primary consideration should be given to designing the power supplies so that there will be a minimum of reaction between stages. This is particularly true of the reaction between the oscillator and the amplifier stages. It is always well to provide a separate power supply for the oscillator and multiplier stages rather than to attempt to use a common power supply for the entire transmitter. It is also well to use some sort of voltage regulation in the oscillator power supply although this is not absolutely necessary when using the oscillator circuit previously described. It should not be necessary in any case to use an elaborate vacuum tube voltage regulator. A regulator tube such as the OD3/VR150 or two such tubes connected in series should be ample. The intermediate or driver amplifier and the final amplifier may be operated successfully from a common power supply. It is very desirable to do this where a variac or some other means of primary power control is used.

The class "B" modulator tubes should be operated from a separate power supply unless the main power supply has unusually good regulation and the class "B" modulator tubes are operated with zero bias. Where grid bias is required for the modulator tubes a power supply should be provided to supply this bias and this power supply should be very heavily loaded to prevent a change in bias due to varying grid current.

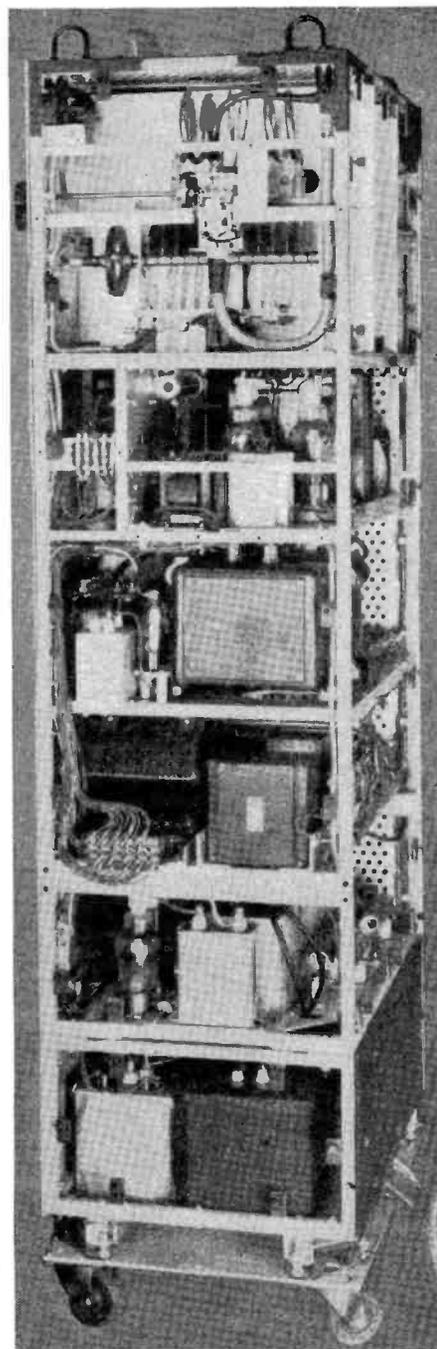


Fig. 5. Right side view of transmitter.

In the transmitter being described a small power supply provides the power for both the oscillator and multiplier stages. The main high voltage power supply provides power for the driver and final amplifier stages. The main power supply is equipped with a variac in the primary circuit to permit easy adjustment of the input power. The class "B" modulator stage has its own power supply and a bias rectifier system provides 60 volts of negative bias for the modulators. The bias supply is loaded with a 250 ohm resistance causing a normal drain of approximately 0.24 amperes. This high bleeder current assures a minimum of fluctuation in the bias supply due to the varying grid current of the modulator tubes. The bias supply also provides power for some of the relays.

73

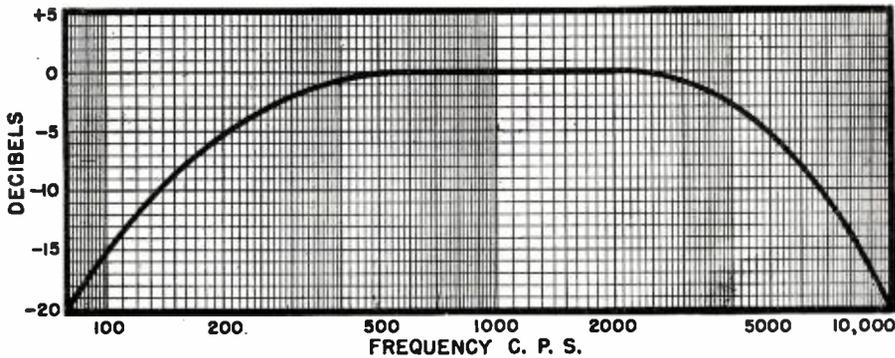


Fig. 6. Audio response curve of speech amplifier. Note that the output falls off rapidly below 300 cycles and over 3000 cycles. This is ideal for voice transmission.

Remote Control System

A positive acting remote control system should be provided in any transmitter in order that the transmitter may be started and stopped from the operating position by means of a toggle switch or other simple device.

A number of relay combinations may be worked out to suit the particular installation once the proper sequence of operations has been determined. The system should provide a means for applying power to the various parts of the transmitter in such a sequence as to prevent the application of power to the power stages in the transmitter before power has been applied to the oscillator and multiplier

stages. It must also provide means of transferring the antenna from the receiver to the transmitter before power is applied to the final stages. The system must also provide a means for removing the power from the final stages before the power is removed from the oscillator and multiplier stages and sufficient time must elapse between the removal of the power from the final stages and the operation of the antenna changeover relay to assure that there will be no power in the antenna circuit when the antenna changeover relay is operated.


The control system in the transmitter being described uses a total of five relays for performing all operations. A copper oxide rectifier supplies power

for the remote control relay and the antenna changeover relay. The circuit is shown in Fig. 2.

Relay RL_2 is the remote control relay, receiving its power from the copper oxide rectifier, through the remote control switch. The operating coil of relay RL_2 is connected in the oscillator power supply circuit as a filter section, and receives power when the oscillator power supply is energized. Power for relays RL_4 and RL_5 is obtained from the bias supply, through contacts B of relay RL_2 .

The operation of the system is as follows: When the remote control switch is closed, relay RL_2 operates, closing contacts A and B . Contacts A are in the center tap of the oscillator power supply transformer. When these contacts close, the power builds up in the oscillator power supply, energizing the operating coil of relay RL_4 . Relay RL_4 operates closing contacts C and D . Contacts C close the primary power circuit of the bias supply, through the time delay switch, and contacts D operate the antenna changeover relay. When the power builds up in the bias supply, relays RL_4 and RL_5 operate, since contacts B of relay RL_2 are closed. When contacts $E, F,$ and G, H of relays RL_4 and RL_5 close, power is applied to the modulator and the main high voltage supplies, and the transmitter is in operation.

Fig. 7. Schematic diagram of speech amplifier. The unit has an over-all gain of 100 db. and an undistorted output of 31 watts.

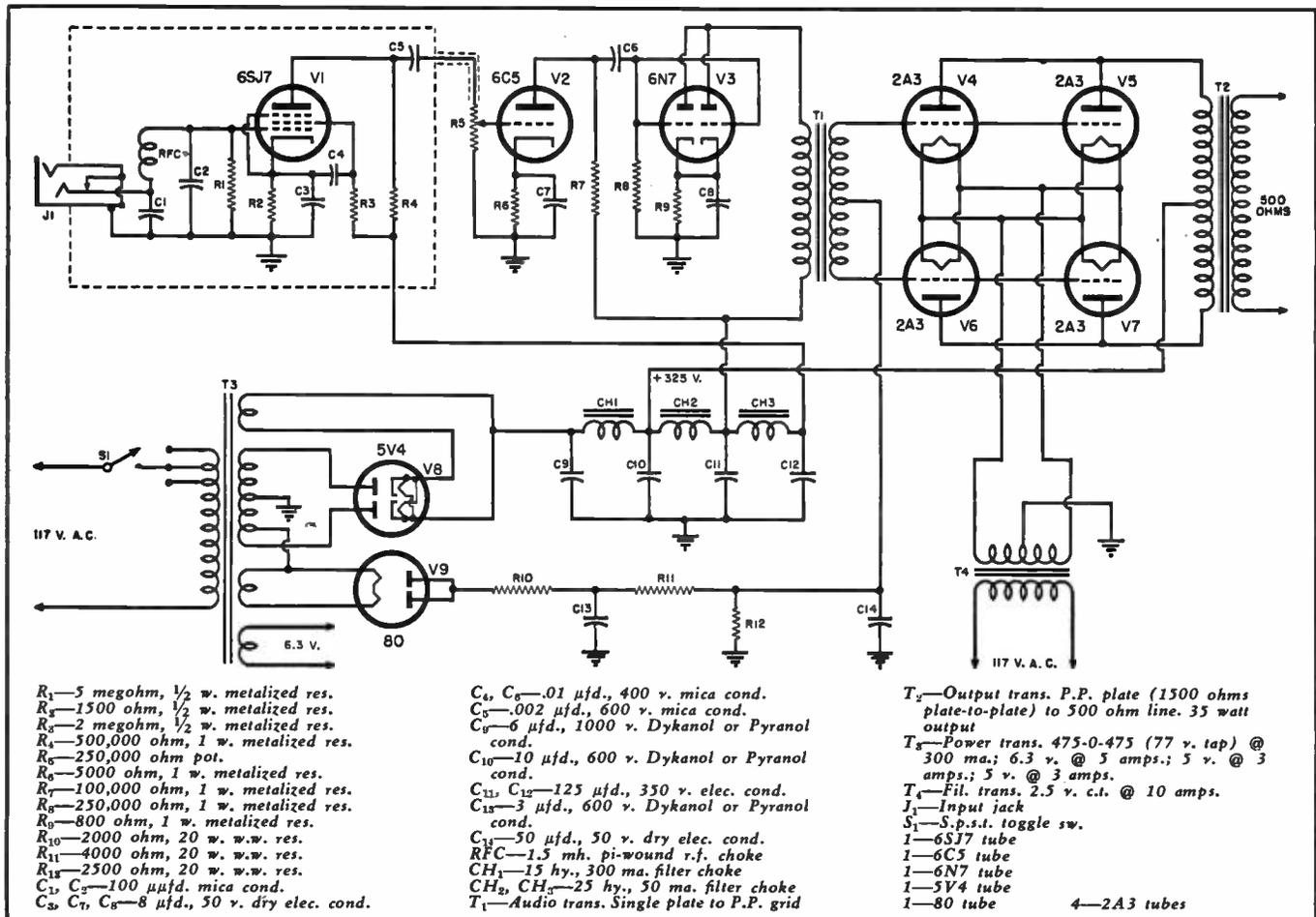

NEXT MONTH IN RADIO MAINTENANCE

June Issue



Test Equipment Maintenance

The first of a series of three big articles on maintaining your own test equipment. Every Serviceman knows the importance of keeping his test instruments properly calibrated and in good condition—and this series of articles will help you do just that. Read about preventive maintenance on Tube Testers, VTVM, Oscillographs, Multimeters, Signal Generators, etc. . . . How often they should be calibrated . . . How to service them and the laboratory techniques for fine adjustments . . . Hints and kinks . . . meter peculiarities . . . Replacement parts, etc. Your test instruments can mean the difference between success and failure of your business . . . This series of articles will be a valuable reference for your service library!

Television Receivers

Part of a series by Marton Scheraga, Television Editor for RADIO MAINTENANCE. Mr. Scheraga describes completely each of the sections in a television receiver and its component parts . . . Alignment, Maintenance and Repair are thoroughly covered . . . In Metropolitan areas, television receivers are already in wide use and smaller communities will soon have them. The public will demand competent repair and maintenance of these new sets, and the Serviceman who knows his television is assured a successful career. Follow television in RADIO MAINTENANCE and be prepared!

When the customer isn't right!

What to do to keep good customer relations. Have you ever had a customer say that your price is too high compared to others? Or that this repair job should be free because you fixed the same radio only a month previously? Find out how some of the leading servicemen in the country handle these difficult situations brought on by some customers. The most frequently encountered problems of customer relations were boiled down into ten questions and each is answered by a different service organization. Read these answers in the June issue, and they will help you meet awkward problems with tact and assurance, and keep all of your customers happy!

And in addition you'll find

- THE RADIO SERVICE BENCH
- SERVICE MEN'S ACTIVITIES
- ELECTRONICALLY SPEAKING
- REVIEW OF TRADE LITERATURE
- THE LATEST THING IN RADIO

**THE MAGAZINE
WITH EVERYTHING YOU NEED**

Start your Subscription with the

June Issue

SUBSCRIBE TODAY

RADIO MAINTENANCE is not sold on the newsstands

You'll feel this way too!

Although I am a comparative newcomer to the radio servicing field, I felt, as many other servicemen must have, that what our trade needed was a publisher who would devote a magazine entirely to the radio serviceman. After receiving only one copy, I am more than pleased with RADIO MAINTENANCE and wish to thank your organization in all sincerity for doing a great job.

J. M.
Chicago, Ill.

This is my first subscription to your magazine and as long as it continues to have such fine articles, you can count on me as a subscriber. It is the answer to a technician's prayer, and any one who misses your magazine is missing valuable material.

W. L. B.
Berkeley, Calif.

RADIO MAINTENANCE MAGAZINE

460 Bloomfield Avenue, Montclair, N. J.

Please send me RADIO MAINTENANCE magazine every month for

1 year at \$2.50 2 years at \$4.00

Name

Address

City-State

*Occupation

Title (Service Mgr., etc.)

Employed by

*Business or professional classifications are required to serve you better. Each subscriber will profit by writing one of the following classifications in space indicated.

**INDEPENDENT SERVICEMAN—DEALER SERVICEMAN—SERVICE
MANAGER—DEALER—DISTRIBUTOR—JOBBER**

State your trade or occupation if not listed

NEWARK HAS MORE RADIO BARGAINS THAN EVER BEFORE


OAK RECORD CHANGER



2-Post Model — Plays 10" and 12" records. A sturdy, dependable record changer at a remarkably low price that means bigger profits for servicemen. 110 volts AC. Limited Quantity. A wonderful buy **\$17.95** at ONLY.....

DUAL CONTROL BOXES

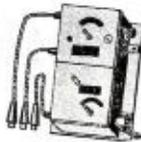2-Channel box for intercom, PA, Ham work. Parts alone worth many times the price! 3-12 pt. rotary switches, 1-double deck, 2-triple light, socket and bulb with translucent red cover, 1/4 watt resistor, 3 pointer knobs, 3-3 metal box 10 x 4 x 2". A hot buy for only **49¢**



SINGLE CONTROL BOXES

5 x 4 x 2". Two 3-deck, 12 pt. rotary switches, pilot light, 2-12 pt. recessed male connectors, 3 ft. 5-wire cable. With 2 bakelite knobs. Great Value! Only **39¢**



SINGLE BOX, as above, but with one rotary switch, 2-3 ft. 5-wire cables. Only **39¢**

SINGLE BOX — Push Button, high frequency buzzer, 2-3 ft. 5-wire connectors and several terminal strips. Parts alone worth twice as much. Only **39¢**



WAR SURPLUS TRANSMITTING and SPECIAL PURPOSE TUBES

1C21 \$.75	6J4 \$1.50	250TH \$9.00	808 \$3.00	830B \$5.25	872A/872 2.25	958A \$.75
1N21A .20	10Y 1.50	304TH 12.00	809 1.50	832A 4.05	884 .75	959 .75
1N23 .20	35TG 1.95	304TL 3.75	810 2.63	836 1.50	921 .75	1616 3.00
2AP1 2.25	75TL 2.25	715C 33.00	811 1.95	837 3.38	922 .73	1619 .75
2C40 2.63	VR90 .75	800 2.25	813 6.75	838 3.75	923 .45	1624 .90
2C44 1.50	100TH 4.13	801A 1.73	814 4.50	843 .75	927 1.05	1625 .75
2D21 .60	VR105 .75	802 1.58	815 2.25	845W 3.75	931A 1.88	1626 .60
2X2/879 .90	VR150 .75	803 9.00	816 .60	860 3.00	954 .75	1629 .27
3AP1 3.00	204A 60.00	804 6.75	826 2.25	861 90.00	955 .75	2051 .90
5AP1 9.00	211 1.13	805 3.75	828 9.00	864 .60	956 .75	8005 3.15
6AK5 .90	217C 7.50	807 1.05	829B 3.00	865 1.50	957 .75	8016 .53

PHONE and MICROPHONE ASSEMBLY

Dynamic type, adaptable for code practice sets, mobile equipment, PA systems, home recording, etc. Mike handset with 50-ohm impedance. Mike and Phones terminate in 5-wire male plug, 3 ft. cord with female receptacle facilitates disconnection. Special Value **\$1.95** at Only.....



CRYSTAL PICK-UP

A rare bargain! Brand New, High Fidelity, Famous Make crystal pickup. Featherweight, Tangent Head, 7" mounting center. While they last, only **\$1.99**



Receivers Now Available!

- HALLICRAFTERS**
- S-38 complete... \$47.50
- S-40 complete... 89.50
- SX-42 275.00
- NATIONAL**
- HRO-5Tal complete 306.71
- NC-240D with speaker 241.44
- NC-46 with speaker 107.40
- 1-10A with tubes, less speaker and power supply .. 67.50
- HAMMARLUND**
- HQ-129X complete. 173.25
- SP-400X complete. 342.00
- RME-45 complete.. 198.70
- RME-84 complete.. 98.70
- Panadaptor 99.50
- Supreme Transmitter 450.00

MAIL ORDERS FILLED FROM EITHER NEW YORK CITY OR CHICAGO
Write: 242-G W. 55th St., N.Y.C. OR 323-G W. Madison St., Chicago

50% Deposit Required with C.O.D. Orders
Send Full Amount of Order—Save C.O.D. Chgs.
Prices Subj. to Change

NEW YORK
Offices & Warehouse
242 W. 55th St., N.Y. 19

NEWARK CHICAGO
323 W. Madison St.
Chicago 6, Ill.
ELECTRIC COMPANY, INC.

New York City Stores: 115-17 W. 45th St. & 212 Fulton St.

HERE IT IS . . .

Narrow Band Phase Modulation

EXCITER

(As Described in This Issue)

➔ BASIC KIT OF PARTS (Including Chassis) ➔

➔ As listed in the Exciter article in this issue. **\$23.58** ➔

➔ All for only..... ➔

Order from Either New York or Chicago

NEWARK ELECTRIC
Company, Inc.

242-250 West 55th St., New York 19, N. Y.
323 W. Madison Street, Chicago 6, Illinois

As we have shown, the sequence of operation is as follows: The oscillator power supply comes up first, then the antenna changeover relay operates, then the bias supply comes up, and finally the power comes up in the modulator and p.a. power supplies.

When the transmitter is shut down, the remote control switch removes the operating power from relay RL_1 , which immediately opens contacts A and B of relay RL_2 . Contacts B of relay RL_2 open, removing operating power from relays RL_1 and RL_3 , causing contacts E, F, G, H to open, removing the primary power from the modulator and main power supply.

As the power in the oscillator power supply dies down, the operating coil of relay RL_3 is de-energized, permitting contacts C and D to open. The opening of contacts C removes the power from the bias supply, and the opening of contacts D operates the antenna changeover relay RL_1 .

From the above, we find that the sequence of operation for shutting down the transmitter is not exactly in the reverse of the starting sequence, but is as follows: The oscillator and all high voltage power supplies are shut off simultaneously; then the antenna relay operates and the bias supply is shut off after the oscillator power supply dies down, whereas in starting up, the oscillator power comes on, then the bias comes on and the antenna changeover relay operates, and lastly the high voltage power supplies come on.

With this arrangement, failure of the bias supply will remove the high voltages, and failure of the oscillator supply will shut down the entire transmitter. In this manner, the tubes are all protected from loss of bias, and from loss of excitation due to oscillator power supply failures.

Over-Modulation Indicator

Any transmitter used for telephony should be equipped with a very positive means for indicating over-modulation. An indicator which shows average modulation is not satisfactory for voice operation because of peaks which occur in normal voice frequencies. In order to be certain that serious over-modulation does not occur during the peaks of the voice frequencies, the over-modulation indicator must indicate over-modulation peaks. When an r.f. amplifier is fully modulated, the plate voltage swings from zero to twice the normal value. When over-modulation occurs the plate voltage will actually swing from a negative value to more than twice the normal positive value. Because of this action a negative peak over-modulation indicator may consist of simply a high voltage rectifier and a neon glow lamp as shown in Fig. 3 with a bias voltage applied between the neon lamp and ground. The rectifier filament supply transformer should be insulated for approximately three times the normal plate supply voltage of the transmitter. The filament of the rectifier is connected to the side of the

LOWEST LOSS *from Microphone to Chassis with Amphenol Connectors and Cables*

Rated high in dielectric value, and with an improved power factor, Amphenol low-loss Microphone Connectors and Cables insure maximum efficiency in sound equipment. Dependable and easy to install, they are widely used by leading manufacturers of sound equipment apparatus, photo electric devices, home recorders and a complete range of similar items.

The Amphenol line is precision-built, compact, lightweight and complete. Microphone plugs, mating connectors and receptacles have unbreakable, chromium-plated brass shells and low-loss bakelite inserts. Cord protectors or cable clamps relieve strain on contacts. Threaded coupling rings screw onto mating coupling threads to provide "yank-proof" connections that are free from noise, leaks or shorts. Accidental disconnects are impossible. Multi-contact connectors are polarized.


AMPHENOL MICROPHONE CABLES are unusually low in capacitance for their small diameters.* Light in weight, their durable plastic jackets remain flexible down to -40° F. May be used with standard connectors and cord protectors.

Cables are available in either of two plastic jackets: Vinyl, for heavy auditorium and outdoor use where cables are long and the trampling of crowds is a factor; polyethylene for home and cocktail lounge applications.

Write today for new booklet describing Amphenol Microphone Connectors and Cables.

*Capacitance per foot ranges from 20 mmi. for Amphenol No. 21-120 (.242" diam.) to 35 mmi. for 21-156 (.155" diam.).

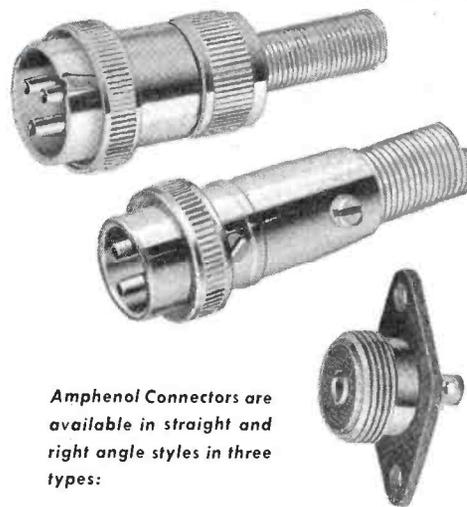AMERICAN PHENOLIC CORPORATION
1830 South 54th Avenue • Chicago 50, Illinois



Amphenol Connectors are available in straight and right angle styles in three types:

SERIES 91: Three and four contact microphone style, used on all types of portable apparatus. Since 1934, the standard of the sound industry.


SERIES 80: For standard single and two wire shielded cables such as: coaxial and microphone cables, twisted pairs, concentric lines, photo cell leads, etc.

SERIES 75: For standard single conductor shielded cable. Widely used in amplifiers, transmitters, photo electric devices, home recorders and similar equipment.

NOW AVAILABLE FOR IMMEDIATE SHIPMENT!

SCR-274-N COMMAND SET

This unit consists of 3 receivers, 2 transmitters, 4 dynamotors, 1 modulator, 2 tuning control boxes, 1 antenna coupling box with RF ammeter, antenna relay and 5000 v., 50 mmfd. W.E. vacuum condenser. Also complete set of 29 tubes with each unit. The receivers cover frequencies of 190-550 kc; 3-6 mc; 6-9.1 mc; Tubes included are: 12SK7—RF amp.; 12K8—mixer; 12SK7—1st IF; 12SK7—2nd IF; 12SR7—diode det. and CW osc.; 12A6 output or AF; Xmtrs cover freq. of 3-4 mc. and 4-5.3 mc.; tubes included are 1626 master oscillator driving 2 parallel 1625's; a 1629 and a calibrating crystal also included. Each receiver has its own dynamotor and another dynamotor powers the transmitter and modulator. Terrific Value. Complete, ready to operate.....\$39.00

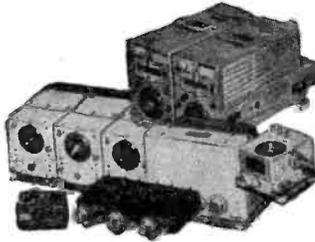


SCR 522 100-156 MC RECEIVER AND TRANSMITTER



Transmitter output 8-9 watts, voice amplitude modulated on any one of four xtal controlled frequencies. Receiver is readily switched to either one of the 4 present xtal controlled channels. Tubes used: 2—832's; 3—12A6's; 1—6G6; 2—6SS7's; 1—12J5GT; 1—12C8; 1—9002; 3—9003's; 1—12AH7G; 3—12SG7's. Super Special. Complete with tubes.....\$39.95

BC 375-E TRANSMITTER

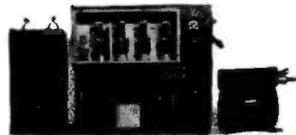


A complete transmitter giving 75 Watts output to the antenna, with a freq. coverage of 200 to 12,000 KC (except for Broadcast Band) in seven tuning units. Also included is the BC 306A antenna tuning unit with variometer and switch, plus PE 73-C dynamotor including relay switches and fuses, etc. Unit comes complete with 5 tubes, 211 oscillator, 211 RF amplifier, 10 speech amplifiers, and 2 211 push-pull modulators. A Bargain at. . \$45.00

BC-221 FREQUENCY METER

A superb frequency standard, this stable, heterodyne freq. meter checks up to the 125th harmonic. Fundamental ranges 125-250 and 2000 to 4000 KC. Makes a wonderful VFO accuracy that cannot be beat. . . Stability better than .005%. Comes complete with tubes, crystal and calibration chart from 125 kc. to 20,000 kc. A simple matter to meet FCC regulations on freq. measurements with this unit. \$39.50



BC 348 RECEIVER

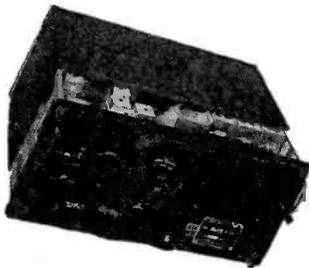

Built for continuous duty, this band switching, six band receiver with a freq. range of 200 to 500 kc. and complete 1,500 kc. to 18,000 kc. Has automatic noise compensator—constant sensitivity on all bands—output at 300 or 4000 ohms—xtal filter AVC-MVC-BFO; Smooth vernier tuning; 90 turns of tuning for ea. band. Tubes include 1st RF—6K7; 2nd RF—6K7; RF Osc.—6C5; 1st Det.—6J7; 1st IF—6K7; 2nd IF and CW Osc.—6F7; 3rd IF and 2nd Det.—

6B8; Aud. Out.—41. Complete with built-in dynamotor for 28 v. DC. (Conversion kit available for 110 v. operation 60 cy.—price on request.) Conversion instructions and schematics furnished with each unit.....\$49.50

20% deposit or full amount required with all orders.

Mail Your Order Today!

Write for Our Latest Bulletin

RADIO HAM SHACK Inc.

63 DEY ST., NEW YORK 7, N. Y.

modulation transformer secondary which feeds power to the modulated amplifier. The plate of the rectifier tube connects to one side of an ordinary neon glow lamp. The other connection to the neon glow lamp is to a positive bias. Since the starting voltage of the standard neon glow lamp which is on the order of 30 to 50 volts has been overcome by a biasing voltage, the glow lamp will flash on over-modulation peaks which are hardly detectable by any other means.

The current drawn by a standard neon lamp is very small, and therefore a bias adjusting potentiometer of 50,000 ohms is satisfactory. The bias potential may be taken from any convenient low voltage source such as the oscillator power supply.

With the main high voltage power supply off, adjust the neon bias to a value where the lamp just starts to glow.

With this adjustment, the lamp will flash whenever a modulation peak reaches exactly 100%, regardless of the plate voltage applied to the r.f. amplifier.

If the bias is not used, the over-modulation indicator will be less accurate, but will still be quite satisfactory for use where the d.c. plate potential applied to the r.f. amplifier is 1000 volts or more. If the starting voltage of the neon lamp is 50 volts, and the d.c. plate potential applied to the r.f. amplifier is 1000 volts, the lamp will flash when the peak modulating voltage becomes negative by a value of 50 volts, representing 5% over-modulation on a peak, which can be tolerated. The percentage of over-modulation detectable with an unbiased neon lamp system becomes increasingly less as the d.c. plate potential applied to the r.f. amplifier is increased, and will be 2.5% for a d.c. plate potential of 2000 volts, 1.6% for 3000 volts, etc.

Speech Amplifier


The speech amplifier in a large transmitter should be a separate unit and should be connected to the transmitter proper by means of a standard 500 ohm line. The amplifier should have sufficient gain to permit the use of any of the commercially available crystal microphones. The noise output from the amplifier should be at least minus 60 db. The audio frequency response of the amplifier should not be flat. Since we are interested only in voice frequencies, those frequencies below 200 cycles and above 3000 cycles should be appreciably attenuated. This may be conveniently accomplished by the proper selection of coupling capacitors and resistors in the amplifier without the use of special filter circuits. The amplifier designed for use with the transmitter described has a gain of 100 db. and has an undistorted output of 31 watts. The noise level with the gain control full on and the microphone disconnected is approximately minus 70 db. The audio response as is indicated (Continued on page 165)

RADIO NEWS

RHS TELEVISION—SCOPE—POWER EQUIP'T

NAVY MODEL Q SYNCHRO-OSCILLOSCOPE

105 - 120v. - 60
cyc. operation
Sweeps: 4, 15,
250, 1000 micro-
second triggered
sweeps, 25 to 3000
cps, saw-tooth
sweeps.
Trigger output:
+150 or -75
volts, 100 to 3200
cps.
Trigger input:
+10 to 150 volts.
Sawtooth-output: 250v. at 25
to 3000 cps. Amplifier response: 30 cps. to 2.5
megacycles. Grey wrinkle enamel cabinet, 9 tubes in-
cluding 2A1 scope tube.
Used as a regular scope plus the advantage of observing
high speed wave shapes as in pulse and television work.
COMPLETE with tubes, cables and carry-
ing case.....**\$89.50**

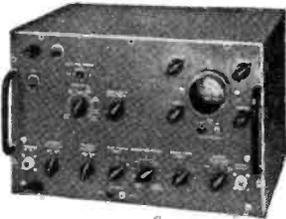

TUBES (Brand New) ARMY-NAVY INSPECTED

1E7G	\$1.25	836	\$2.95
2A1	4.95	837	3.75
2D21	1.50	838	5.95
2V3G	1.75	829A	3.99
211	6.95	841	1.75
3AP1	5.95	861	89.95
3BP1	6.95	866	.99
311	6.95	872A	2.75
5BP1	6.95	884	1.50
5BP4	6.95	885	1.50
6AB7	1.25	8001	8.95
6AC7	.95	8003	9.95
6AG5	1.10	8005	4.95
6AC7	1.25	8016	1.95
6AJ5	1.98	8025A	4.95
6AK5	1.60	9JP1	14.95
6AL5	.99	954	.99
6AR6	1.29	955	.99
6C4	.90	956	.99
6C5	.99	957	.99
6F6	.99	958	1.19
6J4	2.25	959	1.19
6J5	.99	9001	1.19
6J6	.99	9002	.99
6L6	1.59	9003	.99
6Q4	1.25	9004	.99
6SL7	.99	9005	1.10
6SN7	.99	9006	1.15
6V6	1.19	15E	4.95
6SH7	.89	1619	.99
7A4	1.45	1625	.89
801	2.30	1626	.89
806	15.95	250TH	14.95
803	9.95	2050	1.50
804	8.95	2051	1.50
805	5.50	257B	14.95
807	1.05	30	.89
808	6.95	35T	3.50
809	2.25	304TH	16.95
810	3.55	726A/C	7.50
811	2.95	100TH	7.95
813	7.95	1N21	.35
814	6.95	1N23	.35
815	3.95	2C26A	.99
VR90/30	.99	3E29	3.75
VR105/30	.99	CK1005	1.98
VR150/30	.99	HF200	14.95
VT127A	3.00	HK24G	1.49

PHOTOFLASH KIT

Build your own—Save \$100.00 to \$200.00!

Improved version of unit described in December, 1946
Radio News can be synchronized to camera. Contains
complete diagram, all parts, Xformers, tubes, capaci-
tors, resistors, etc., including the amglo 51Q4X repeat-
ing flash tube.

(Complete Parts Kit).....**\$49.95**

SELENIUM RECTIFIERS

Full Wave Bridge Types

INPUT	OUTPUT	
up to 18v A.C.	up to 12v D.C.	1 amp. \$ 2.49
up to 18v A.C.	up to 12v D.C.	5 amp. . 4.95
up to 18v A.C.	up to 12v D.C.	10 amp. . 7.95
up to 18v A.C.	up to 12v D.C.	15 amp. . 10.95
up to 18v A.C.	up to 12v D.C.	30 amp. . 16.95
up to 36v A.C.	up to 28v D.C.	1 amp. . 3.95
up to 36v A.C.	up to 28v D.C.	5 amp. . 7.95
up to 36v A.C.	up to 28v D.C.	10 amp. . 13.95
up to 36v A.C.	up to 28v D.C.	15 amp. . 19.95
up to 115v A.C.	up to 100v D.C.	.25 amp. . 2.95
up to 115v A.C.	up to 100v D.C.	.6 amp. . 6.95
up to 115v A.C.	up to 100v D.C.	5 amp. . 19.95

HIGH CAPACITY CONDENSERS

4000 mfd.—18WVDC	\$1.95
4000 mfd.—30WVDC	2.95
1000 mfd.—15WVDC	.99

MCW—CF1—OSCILLATOR UNIT

Utilizes one 12SL7 gt twin triode as a com-
bination 200KC calibration oscillator and
frequency tripler, one 12-SA7 tube as a
converter and one 12 SL7 gt tube as a signal
detector and MCW audio oscillator supply-
ing a 1000 cycle audio note. The CFI unit
employs a multivibrator circuit to obtain a
50 KC fundamental and harmonic, incor-
porating a 200 KC crystal as the controlling
standard and will yield from 50 KC to 18
megacycles. This unit can be adapted into
an excellent frequency meter, range 50 KC
to 18 megacycles by adding an externa
power supply Shipped with tubes, schematic
and crystal.

SPECIAL PRICE.....\$14.95

OIL CONDENSERS: G.E., AEROVOX, CD., etc.

1 mfd. 600v.....\$0.35	5 mfd. 2000v.....\$2.10
2 mfd. 600v......60	1 mfd. 2000v......95
4 mfd. 600v......75	2 mfd. 2000v..... 2.10
8 mfd. 600v..... 1.10	3 mfd. 2000v..... 2.95
10 mfd. 600v..... 1.40	4 mfd. 2000v..... 3.95
1 mfd. 1000v......90	15 mfd. 2000v..... 4.95
2 mfd. 1000v..... 1.05	12 mfd. 3000v..... 6.95
4 mfd. 1000v..... 1.10	05 mfd. 3000v..... 1.95
8 mfd. 1000v..... 2.00	25 mfd. 3000v..... 2.95
10 mfd. 1000v..... 2.40	1 mfd. 3000v..... 3.50
15 mfd. 1000v..... 2.60	1 mfd. 5000v..... 6.85
20 mfd. 1000v..... 5.95	2 mfd. 4000v..... 7.60
24 mfd. 1500v..... 8.95	1 mfd. 7000v..... 3.95

TRANSFORMERS—115v ac 60 cyc Hi-Voltage Insulation

6500v at 4 ma.....	\$ 9.95
6000v at 2 ma.....	7.95
3950v at 4 ma. tap at 1250v-1 ma.....	7.50
3710v at 10 ma.; 2.5v at 3A; 2.5v at 3A.....	9.95
2500v at 10 ma.....	6.50
Xformer, 1600v at 4ma., 700v ct at 150ma., 6.3v at 8A, 115 v 60 cyc.....ea.	8.50
442-0-442v at 1000 ma.....	9.95
2.5v. at 10 amps. 10 KV test.....	3.25
6.3v at 6.6. amps.....	3.25
6.3v at 21.5 amp.; 2.5 at 2 amp.; 6.3 at 2 amp.....	6.95
2.5v at 3 amp. 15 KV test.....	3.95
5v at 115 amp.....	14.95
5v at 190 amp. 35 KV test.....	17.50

FILTER CHOKES— HI-VOLTAGE INSULATION

12 Hy.—100 ma.....\$2.35	12 Hy.—300 ma.....\$3.95
4 Hy.—250 ma..... 3.95	15 Hy.— 30 ma..... 1.95
10 Hy.—150 ma..... 3.95	20 Hy.— 90 ma..... 2.25
4 Hy.—600 ma..... 5.95	.006 Hy.—5 amps..... 6.95
15 Hy.—100 ma..... 2.95	10 Hy.—250 ma..... 2.49

NATIONAL DRIVE UNIT ONLY

PW-O or
NPW-O.....**\$2.95**

RELAY

Sigma No. 4RJ 2000 ohms SPDT. Can adjust to
to less than
1 ma.....**\$1.98**

POWER SUPPLY FOR MARK 1-11-111 BC-19 OR OTHER EQUIPMENT

Use as plating unit, battery
charger, etc. 12 Amp-12v D.C.
from 110v A.C. Unnecessary to tear
set apart. Leave set portable.

**COMPLETE READY \$32.50
TO PLUG IN.....**

METERS—G.E., WESTON, etc. 3 1/2

0-5 Ma. D.C.	0-8 Amps. R.F.
0-50 Ma. D.C.	0-15 Amps. R.F.
0-100 Ma. D.C.	0-1.5 K.V. w/shunt
0-300 Ma. D.C.	0-3.5 K.V. w/shunt
0-500 Ma. D.C.	0-350 V. D.C.
0-8 V. A.C.	0-15 V. A.C.

Your choice any 3 1/2" METER...\$3.95

2 1/2" METERS

0-130 V. A.C.	0-1 Ma. D.C.
0-20 V. D.C.	0-8 Amp. D.C.


Your choice any 2 1/2" METER...\$2.95

BLOWER

Hi-air blast, designed for
transmitting tube service. Motor
operates on 100-125v 60 cycle at
7000 RPM. Noise free with self con-
tained chokes and filters. Enclosed
in satin finish, aluminum cabinet.
Measures 4" high x 2 3/4" x 3 3/4". Many
uses.

Super buy at.....\$5.95

CARBON PILE REGULATOR

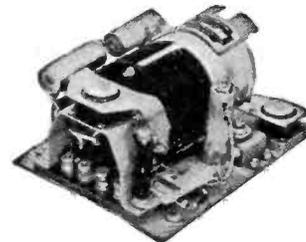

115V. 60 Cycles, 500 Watt LOAD, 750 W. AIR BLAST
Uniform voltage to all equipment at any load to 500
watts. Regulates voltages to test bench and sets under
test. Line voltage regulator for output of gas driven
generators. Regulates line voltage from outlets in the
average home. Used in rural areas where line voltage
surges.

Excellent Buy at.....\$14.95

All material is new and guaranteed, unless otherwise specified.

No orders for less than \$2.50—20% deposit required with all orders.


RADIO HAM SHACK Inc.
63 DEY STREET • NEW YORK 7, N. Y.

**Big
News!**

America's Famous 150 Openings for

Many Thousands of Dollars Worth of New Equipment Enables Us to Increase Our Enrollment Quota—Personal Instruction by Expert Teachers on Big, Modern Television Equipment—Students May Keep the Television Receivers They Build.

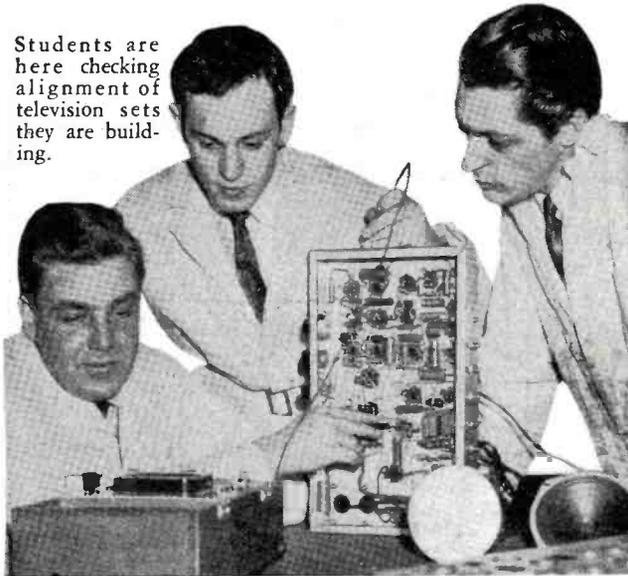Students are here checking alignment of television sets they are building.



The latest test equipment is available in volume to all students at N.Y.T.I. of N.J. Just learning how to use the latest types of television test equipment is an important part of your training.

IF YOU are interested in a big-money career in TELEVISION—here is good news! We have just purchased more thousands of dollars of up-to-the-minute television equipment. This enables us to accept 150 *additional* students in May, June and July. *New classes begin every 2 weeks.*

Television is a highly technical subject. You can't expect to make the best progress unless you get expert, PERSONAL instruction and study with the *right apparatus*. You've actually got to *handle* the big, technical equipment YOURSELF. You've got to be in daily PERSONAL contact with your teachers. You've actually got to BUILD television receivers to understand them—and don't let anybody tell you differently!

Here's the Best Way to Learn Television

At the New York Technical Institute of New Jersey—one of America's great technical schools—you can do all that. The school is located right in



Here you see one of the television laboratories in full swing. The class is building television receivers, using many advanced types of test devices.

Television School Will Have May, June & July

Newark, N. J.—smack in the heart of the television industry. It is lavishly equipped with the very latest television test equipment. It maintains a large staff of expert instructors—many of whom are also actively associated with the television industry.


Here you "live" right WITH these experts. They are all regular fellows who have come up "through the mill." They know your problems and they also *know* television. Working with these men makes it easier to understand even the most technical side of television. They help you with the 77 different electronic experiments which each student must complete before he starts to build his very own television receiver—and which he may *keep* as his own property, if he chooses.

School Approved for G.I. Training

N.Y.T.I. of N.J. is approved for training under the G.I. Bill of Rights. The government pays up to \$500 a year for a veteran's educational expenses and pays \$90 a month to veterans with dependents and \$65 a month to those without dependents for their living expenses. (Of course, you *don't* have to be a veteran to attend the school.)

We Will Teach You the Mathematics You Need

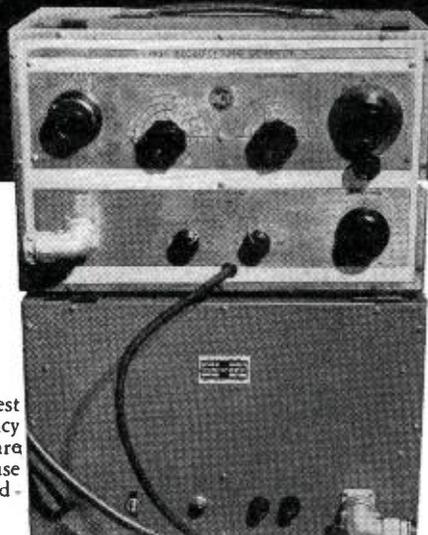N.Y.T.I. of N.J. is ideally located for Television Training—right in Newark, in the heart of the country's great radio and electronics industry, just 20 minutes from N. Y. City. The school is near such leading television, radio and electronics man-




Eight of these latest RCA High-Frequency Sweep Generators are in almost constant use by students in Advanced Television.

ufacturers as R.C.A., Western Electric, General Electric, DuMont, Federal, Westinghouse and Edison. It is also near some of the biggest television transmitting stations.

Here at the N.Y.T.I. of N.J.—you can really start from scratch and become a television expert. No high school diploma is required. All you need is a grammar school education and a sincere desire to learn, plus a willingness to make an all-out effort. If you are rusty in mathematics, we can teach you the radio and television math you will need.

Send for Our Special FREE Bulletin

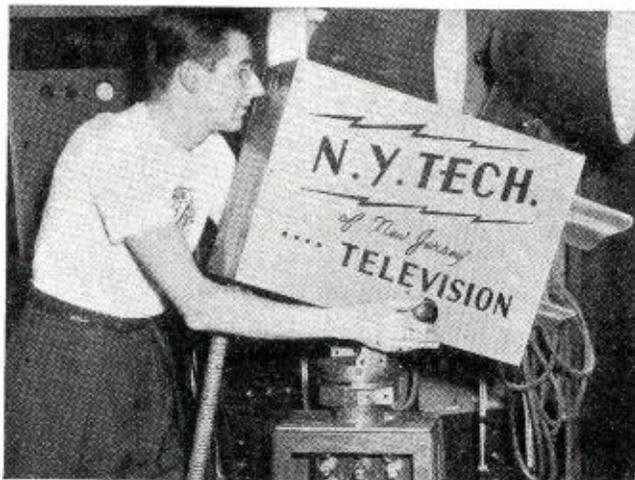The school issues a Special Bulletin, which describes and illustrates its facilities and equipment. The FREE Bulletin also describes classes which may be attended, housing conditions, costs, hours, etc. You can have it by mailing the coupon below to—*New York Technical Institute of New Jersey (Dept. 15), 158 Market Street, Newark, N. J.*



Here an ex-G.I. is shown taking pictures with N.Y. Tech's Iconoscope Television Camera. When it comes to television—you can't beat N.Y.T.I. of N.J.

**New York Technical Institute of New Jersey,
Dept. 15, 158 Market Street, Newark, New Jersey**

Please send me your FREE Bulletin describing the famous Resident School of the New York Technical Institute of New Jersey located in Newark, N.J.—including its facilities, equipment, courses offered, costs, hours, etc.

Check here if you are a Veteran of World War II.

Name..... Age.....

Address

City..... Zone
(if any)..... State.....

(N.Y.T.I. of N. J. employs no salesmen to call.)

LEONARD VALUES

ELECTRONIC MEASUREMENTS



VOLOMETERS

101A **\$17.50** NET
 3" METER Model 101B
 OPEN FACE 4" METER **\$20.95** NET
 OPEN FACE PORTABLE
 101AP 3" Meter.... \$21.50 net
 101BP 4" Meter.... \$24.95 net

PRECISION APPARATUS #920

Combination Mutual Conductance Tube Checker and Multi-Tester

\$84.22 NET

#832 S \$23.87 net
 #844 P Volt-Ohm Meter \$36.87 net



#954 P \$99.20 net

SPEAKER SALE

- 5" PM ALNICO #5.....\$1.89
- 6" PM ALNICO #5.....\$2.45
- 8" PM ALNICO #5.....\$3.95
- 12" PM ALNICO #5.....\$6.95

PERMEABILITY TUNING UNIT

Replaces Gang Cond. F-57 **\$268** NET
 Osc. Coil & Ant. Coil.....
 Loop to Match.....\$1.05 NET

PLUG-IN ELECTROLYTIC CONDENSER

60-30-30 mfd 450 V.D.C.W.

G-57 SPECIAL LIMITED QUANTITY **83c**

6L6 PUSH PULL OUTPUT 35 WATT

Completely shielded. Class AB1. Primary 6600 Ohms-Sec. 2-4-8-15-500 Ohms.


H-57 SPECIAL LIMITED QUANTITY **\$3.89**

PHONO MOTOR and PICK UP KIT

SPECIAL

\$5.45

Complete

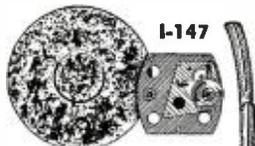

Crystal pick-up—Top quality constant speed motor. Motor Assembly only \$3.95

ELECTROLYTIC CONDENSERS

EXCEPTIONAL BUY!!
 50-50 mfd. C.D. 150 v. fresh stock—5 for **\$2.75**

- 8-450 38c 8-8-450 65c
- 16-450 56c 20-20-150 65c
- 30-150 40c 40-40-150 73c
- 40-150 42c 50-30-150 75c

Have a complete stock on hand of Sprague, Amperite, Aerovox, B & W, Turner, I.R.C., Shure, and other nationally known parts and equipment. Dealers and Servicemen supplied.

Send 25% deposit with order—balance Express Collect. Orders under \$5.00 send check or money order plus postage.

LEONARD RADIO INC.
 69 CORTLANDT ST.
 NEW YORK 7, N.Y.




CIRCUIT PAGE

(FOR PARTS LISTS SEE PAGE 94)


RADIO NEWS, MAY, 1947

BELMONT MODEL 5D110

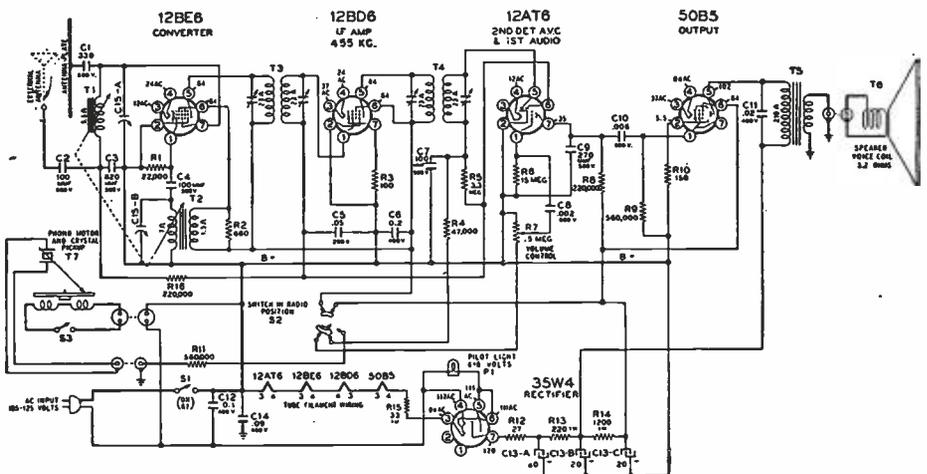


RADIO NEWS, MAY, 1947

CROSLLEY MODELS 56TZ, 57TQ

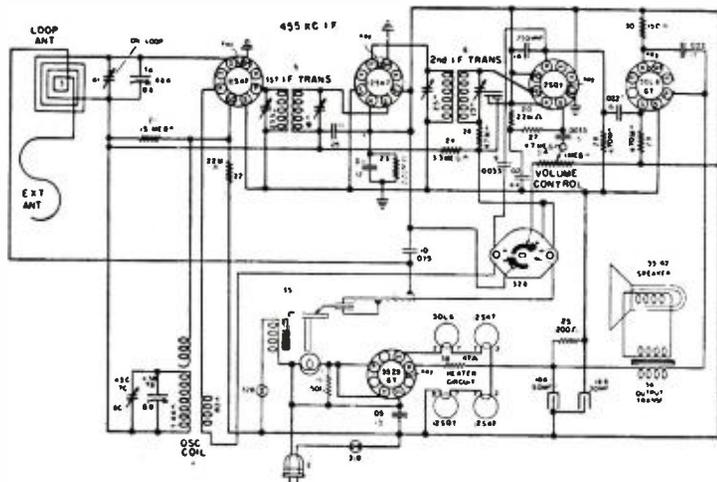

RADIO NEWS, MAY, 1947


BENDIX MODELS 636A, 636C, 636D

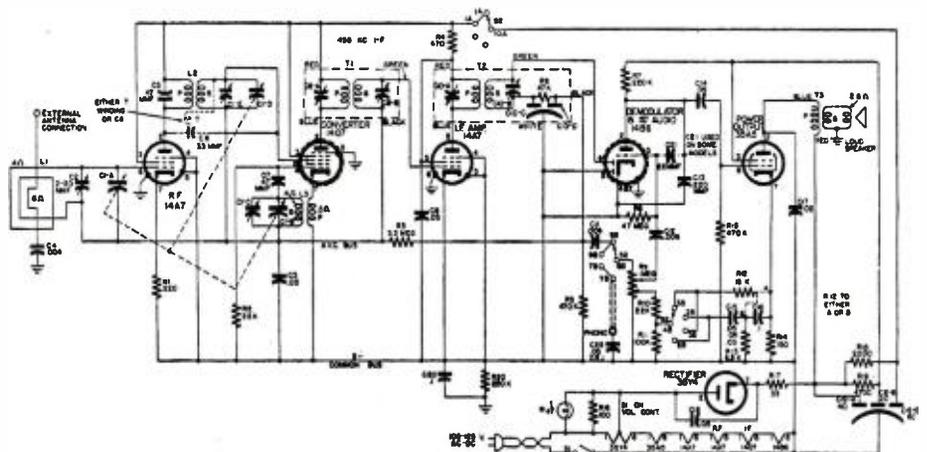


Here, and on following pages, are circuit diagrams and parts lists of many new postwar radio receivers. Radio News will bring to you other circuits as quickly as possible after we receive them from manufacturers.

RADIO NEWS, MAY, 1947

WARD MODELS 64BR-1808A

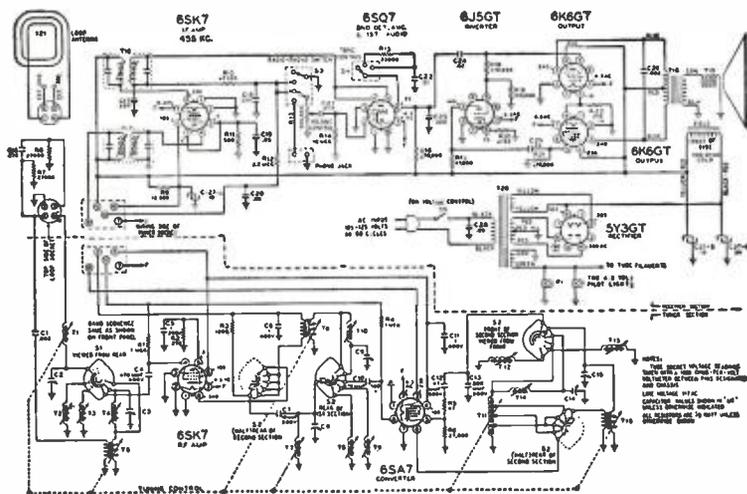


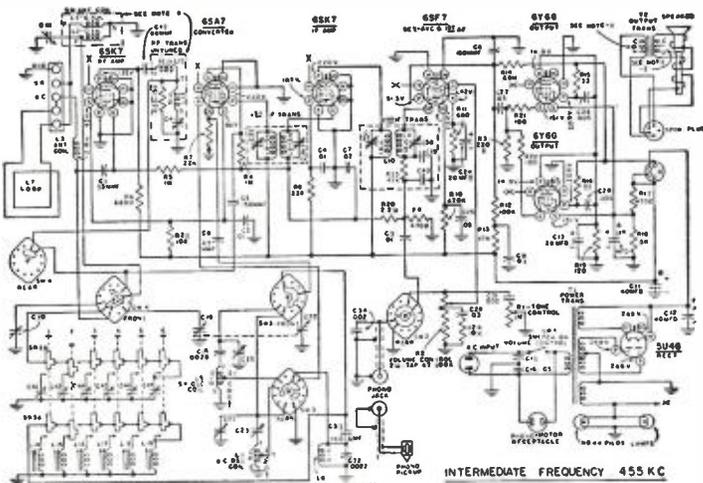RADIO NEWS, MAY, 1947 WESTINGHOUSE MODELS H-110, H-111, H-137, H-138



RADIO NEWS, MAY, 1947

ZENITH MODELS 5R080, 5R086

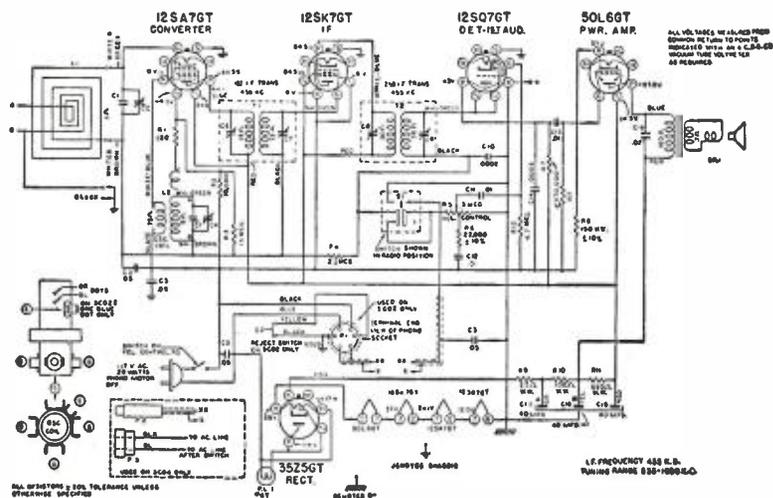

LEARN ELECTRIC MOTOR REPAIR!



A PROFITABLE ADDITION TO ANY RADIO SERVICE BUSINESS

This big book shows you how—every step of the way—
only \$5

IT PAYS TO SPECIALIZE IN SOMETHING DIFFERENT


There's good money in electric motor repair! The field is not crowded—and what could be a finer, more profitable addition to your already established radio service business? Every home you visit on radio work has many motor-driven appliances. Be the man who can repair them!

ELECTRIC MOTOR REPAIR, the unique new book by the publishers of the famous Ghirardi Radio-Electronic books, teaches you the work from the very beginning. Explains every detail of motor trouble diagnosing, repair and rewinding. Covers a-c and d-c motors, synchronous motors and generators and BOTH mechanical and electrical control systems.

A "BENCH" BOOK

Based on what you can learn from this big book alone, you can train for prompt, profitable motor service. Quick reference guides for use right at the bench show exactly how to handle specific jobs. Invaluable for beginners or for daily reference in busy shops. Unique Duo-Spiral Binding divides book into 2 sections permitting text and related illustrations to be seen AT THE SAME TIME. Book contains more than 900 diagrams and illustrations.

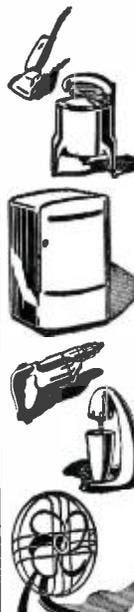Send coupon now! Practice from ELECTRIC MOTOR REPAIR for 5 days. If not more than satisfied, return book and every cent will be cheerfully refunded.



LEARN FAST!
LEARN RIGHT!

NO RISK COUPON mail today

Dept. RN-57, Murray Hill Books, Inc.
232 Madison Ave., New York 16, N. Y.

Enclosed is \$5 (\$5.50 foreign) for a copy of ELECTRIC MOTOR REPAIR Book; or send C.O.D. for \$5 plus postage (no foreign C.O.D.'s). In either event, if not satisfied, it is understood I may return book in 5 days for complete refund of my money.

Name
Address
City & Dist. No. State

McGEE OFFERS YOU COMPLETE RADIO-AMPLIFIER and PHONO-KITS


RADIO SERVICE MEN: EXPERIMENTERS, STUDENTS, ETC.—McGee offers you complete radio and amplifier kits. Every kit is carefully designed to our rigid electronic specifications. All chassis are punched and designed

to fit their respective cabinets. Matched kits of tubes are furnished, nothing else to buy. Schematic diagrams and photos of the completed chassis are furnished for rapid, easy assembly.

NEW SUPER MIDGET KIT 550 to 1650 K.C.

OUR SUPER VALUE

Build this new super Midget Radio. Has beautifully made, highly polished walnut cabinet. Size 7 1/2 x 4 1/2 x 5 1/2. Attractive slide rule dial. Incorporates a standard superhet circuit with 456 KC IFS & AVC. Has 2 gang condenser and loop ant. Every part including Alnico V.P.M. speaker and tubes. 12BE6, 12BA6, 12AT6, 50B5 & 35W4 furnished as well as photo and easy to follow diagram. Weight 5 lbs. Kit Model K-PT. Net Each \$12.95

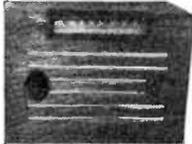


RADIO-PHONO COMB. KIT

Build this beautiful portable combination radio phonograph. We furnish everything. Beautiful two tone portable case, latest rim drive phono motor, Astatic crystal pick-up. All parts to build high quality 5 tube AC-DC radio. Tuning broadcast 550 to 1650 KC. Has tone control, loop antenna, 6" Alnico 5 PM speaker. Tubes 12SA7, 12SK7, 12SQ7, 50L6 and 35Z5. Simple diagram furnished. Kit Model RP-12. Wt. 20 lbs. Your Cost \$29.95



3-WAY PORTABLE RADIO KIT

Build this powerful, 5 tube, 3-way portable kit. Operates on 110 volts AC or DC or self contained batteries. Receives broadcast 550 to 1650 K.C. Incorporates a standard superhet circuit with AVC and loop Ant. Has Alnico 5 PM Speaker, 2 gang condenser. All parts and batteries are furnished including tubes 117Z6, 1R5, 1T4, 1S5 and 3S4. Has attractive leatherette portable cabinet size 7x9x3. Weight 14 lbs. Kit model 3-ZA. Net \$17.95

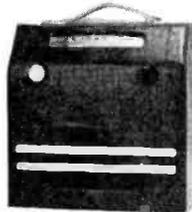

BATTERY RECORD PLAYER KIT

Something new in portable record players. Has spring wound phono motor. Latest type light weight crystal pick-up, and ready wired and tested push-pull 3S4 amplifier. Furnished with a heavy duty Alnico V PM speaker. This kit can be put together in a few minutes and will make a superb record player with superb tone and volume. Requires no AC power. Operates on self contained batteries. Priced complete with batteries and tubes ready to assemble. Dealers' Net Model AK 10. \$19.95



KIT J-17 PORTABLE SINGLE RECORD PLAYER NET \$17.95

OFFERED IN THE SAME CASE AS THE MODEL AK-10 shown above, except it is designed for 110 volt AC operation. Has standard 3-tube AC DC wired and tested amplifier (with tubes). 5 in. Alnico 5 PM speaker and 78 RPM AC rim drive phono motor and light weight crystal pick up. You can assemble this in a few minutes' time into a ready, salable item. Weight 18 lbs.

KIT J-18 Portable Automatic record player.

Beautiful portable leatherette case and latest single post automatic record changer and a powerful 3-tube AC (Trans Type) Wired and Tested amplifier with tone and volume control. Everything inc.; tubes furnished. Has heavy duty 6" Alnico V.P.M. speaker. We have sold hundreds of these to our dealers and they keep coming back for more; a real value. Weight 28 lbs. Kit J-18. Net complete EACH \$33.95



KIT J-15X SINGLE RECORD PLAYER

Attractive ready cut walnut cabinet, with latest 78 RPM phono motor and light weight crystal pick-up. Complete with a ready to play (wired and tested) 3 tube AC-DC amplifier; with tubes and 4" Alnico 5 PM speaker. You can assemble this kit in a few minutes. Wt. 10 lbs. Dealers Net. \$13.95



G.I. RECORDER MECHANISMS


Latest 1947 General Industries recording assemblies with 4 ohm magnetic cutters and crystal play back arms.
Model 12445—78 RPM. Net. \$24.50
Model 13700—33 and 78 RPM. Net. \$28.95
Model 13810—Automatic changer with cutter, 78 RPM. Net. 40.10

COMPLETE RADIO KITS FACTORY ENGINEERED


NEW PLASTIC CABINET AC-DC SUPERHET KIT. Cabinet size 7x9x10 1/2. Attractive slide rule dial. 2-gang tuning condenser. Receives broadcast 550 to 1650 KC. Has latest Alnico 5 PM speaker Loop antenna; all parts simplified diagram and tubes 12SA7, 12SK7, 12SQ7, 50L6 and 35Z5 furnished. Kit P-48. Wt. 9 lbs. Net \$12.95
4 TUBE 1 1/2-90 VOLT FARM RADIO KIT. Offered in same cabinet as the above Kit Model P-48. The same high gain broadcast superhet circuit. Complete with 4 tubes; 1R5, 1T4, 1S5, 3S4 and diagram. Less battery pack. Kit model PB-48. Your Cost \$10.95



DELUXE AC-DC KIT J-D5 Beautiful walnut cabinet and all the parts to build a broadcast 5 tube AC-DC radio. Superhet with slide rule dial, 2 gang tuning condenser and loop aerial. Everything furnished; includes speaker and tubes 12SA7, 12SK7, 12SQ7, 50L6 and 35Z5 and diagram. Kit J-D5. Wt. 10 lbs. Net \$14.95
KIT K-5D. Similar cabinet to above J-D5 except it is AC Trans. type and has 6 volt tubes. Net \$16.95

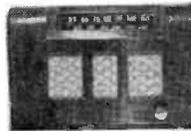

KIT K-7A. Easily assembled into a fine working, attractive, transformer type AC, broadcast receiver; 550 to 1700 KC. Has push-pull audio, tone control and 6 1/2" Alnico 5 PM speaker. Beautifully made 14" walnut cabinet. Incorporates a standard superhet circuit, with AVC and loop antenna. All parts, schematic and tubes 6SA7, 6SK7, 6H6, 6SN7, 2-6G0's and 5Y3 furnished. Nothing else to buy. Wt. 17 lbs. Dealers Net \$19.95

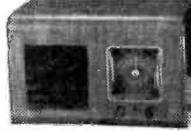


OUR LEADER KIT \$9.95. 2 gang cond. AC-DC. 4 tube TRF kit 550 to 1600 KC. Kit K-AR. A TRF job with a walnut cabinet and 5" alnico 5 PM speaker. All parts furnished; including tubes and diagram. Has direct drive dial and a very simple standard circuit. An ideal kit for the student or experimenter. Just a few hundred to sell. Wt. 8 lbs. Very Special at only \$9.95




WALNUT CABINET RECORD PLAYER

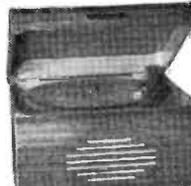Beautifully made, highly polished walnut cabinet with hinged lid. Plays 10" records with lid closed. Latest rim drive phono motor and a high output. Astatic crystal pick-up. 11 1/2" power 3 tube AC-DC phono amplifier (wired and tested). Heavy duty 4" Alnico 5 PM Speaker. Single record player kit. Model WL-3. Wt. 15 lbs. Your Cost \$19.95



SMALL RADIO-PHONO KIT

After carefully designing the record player and cabinet shown above (Model WL-3), we decided that it should also be offered as a radio-phonograph combination. The cabinet is both attractive and small (12x12x8). The radio kit part of this unit is similar, except for the dial, to our Kit Model K-PT shown in column 1 of this page. We furnish all parts, tubes, phono motor, pick-up, etc. Easy to follow diagram. Kit Model WL-3R. Wt. 16 lbs. Net. \$29.95

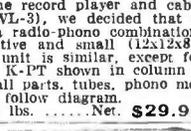

HOME RECORDER KIT J-K6.

Dealers. Net \$59.95 Consists of latest General Industries dual speed 33 or 78 RPM record-play-back mechanism. Beautifully made to fit walnut cabinet and a complete kit of parts to build a high quality recording amplifier with push-pull 6V6 outputs. All parts, tubes, 5" PM speaker, Astatic crystal mike and diagram furnished. This amplifier can also be used as a 15 watt PA system. Provisions made to connect 12" PM Speaker. (12" G. E. PM Speaker and wall baffle \$16.95 extra). Net Kit J-K6 \$59.95. JK-6 in Portable Leatherette Case and 6" PM Speaker \$5.00 extra. Wt. 33 lbs.



KIT J-19 SINGLE RECORD ATTACHMENT.

Attractive walnut finished base with motor cut out. latest 78 RPM rim drive phono motor and light weight, high output crystal pick-up. Easily attached to any radio or amplifier. Kit J-19 Dealers. Net \$9.95 complete Model B-4 phono oscillator (fits under base). Dealers Net \$3.69



8-TUBE RADIO-AMP. KIT

Build this High-Fi Radio Amplifier

● Standard Superhet Circuit covering Broadcast 550 to 1700 K.C.
● New Positive Drive Permeability Tuning.
● Offered with 12 or 15 in. PM Speakers. Push-pull 6V6 Output stage giving 15 watts of full range audio.
● Dual Tone Controls (Bass and Treble).
● Inputs for both Mike and Phono pick-up.
Here is something new in radio. A real 15 watt power amplifier with bass and treble controls. Has extra gain stage for crystal or dynamic mikes. And on the same chassis, a standard superhet radio receiver. We furnish all parts, knobs, escutcheon plate and tubes: 6SA7, 6SK7, 6SR7, 6SN7, 6SJ7, two 6V6 and 5Y3. No cabinet. Extra care in designing the power supply section assures low hum level, making this unit ideal for recording as well as P.A. use. We furnish everything as well as schematic diagram and photos of the completed chassis. Weight 35 lbs. PRK-10 Radio Amp. Kit with 12 P.M. Speaker. Net \$29.95
PRK-10X Radio Amp. Kit with 15 in. \$30.00 value Cinnadagraph P.M. speaker. Net \$42.95
If you desire a more powerful Audio section in the above kit we offer either the PRK-10 or PRK-10X with a full 200 mill power transformer and push pull 6L6 tubes in the final giving 25 watts of full range audio for \$10.00 extra on either kit.




MUSICAL AMP-KIT

Build this 10 watt AC-DC musical amplifier. Designed with the new selenium rectifier in a unique voltage doubler circuit. Has gain stage for crystal or dynamic mike and inputs for instrument or phono pick-ups. Variable tone control. Priced complete with 12" speaker and case as shown and tubes 2-50L6, 12SL7, 12SJ7. All parts, rectifiers and punched chassis and wiring diagram furnished. Kit Model MM-10. Net \$22.95
Crystal Mike and desk stand. \$7.95 extra



20-WATT PORTABLE AMP KIT

Build this 20 watt portable public address system. We furnish all parts and an easy to follow diagram. Attractive leatherette 3 piece case (snaps together to form one package). Has 12 Alnico 5 PM speaker. Inputs for mike and phono pick-up. Tone control. Full 150 mill power transformer. All parts, resistors, controls and condensers and tubes furnished. 5U4, 2-6L6GA 6SC7, 6SN7. 25 ft. of speaker cable included. Amplifier Kit model XX-20 with one 12" PM speaker. Net. \$34.95
With two 12" PM speakers. Net. \$43.95
Crystal Mike and 20 ft. of cable. Extra. \$7.95

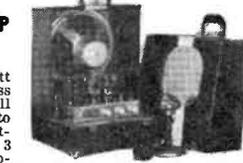

20-WATT UTILITY AMP. KIT

Build this 20 watt utility 110 volt AC. 20 Watt power amplifier. Ready punched aluminum chassis, size 12 x 6 x 2 1/2 inches. Has two input circuits, one mike and one phono. Mike stage has 135 DB gain, for crystal or dynamic mike. Has bass and treble controls. Designed for use with PM speakers; has 8-16 ohm output transformer. All parts, controls, transformers and easy-to-follow diagram furnished, including tubes: 2-6SN7, 6A5, 2-6L6GA, 5Z3. Kit Model 20-LX. Net. \$17.95
12" G. E. 12 watt Alnico 5 PM speaker. \$9.50 extra. Astatic crystal mike and desk stand. \$7.95 extra.



BUILD THIS AUTO-RADIO

550 to 1650 K.C. We furnish you a complete kit of parts to build a 4-tube superhet car radio. The UNDERDASH remote control case (Size 2 1/2 x 2 x 5) Houses the permeability tuning unit and converter tube. The output from this remote control (I.F. Freq.) is fed through 30' length of small coax to the radio proper. The metal case, size 6 x 9 x 5, Houses the I.F. Detector and Audio Stages; Vibrator supply and Alnico 5 P.M. speaker. All parts, metal case, vibrator, power supply and tubes 6BE6, 6SD7, 6SQ7, 6X6 & 6Y3. Vibrator furnished. Diagram and photo furnished for easy assembly. (Kit Model CR-4). Net \$19.95



McGEE RADIO COMPANY

Write for Catalog

Send 20% Deposit—Bal. Sent C.O.D.
1225 McGEE ST., KANSAS CITY, MISSOURI
ON PARCEL POST ORDERS INCLUDE AMPLE POSTAGE

AIRCRAFT RECEIVERS \$2.95

AIRCRAFT TRANSMITTERS \$9.95

WESTERN ELECTRIC AIRCRAFT SURPLUS

ALL OF THE RECEIVERS AND TRANSMITTERS LISTED BELOW ARE IN GOOD CONDITION. THE RECEIVERS ARE NEW, THE TRANSMITTERS ARE USED BUT GUARANTEED PERFECT. ORDER SURPLUS WITH CONFIDENCE FROM McGEE.

AIRCRAFT RECEIVERS


These Army surplus aircraft receivers may be operated from a 24 volt AC filament supply and any low power 250 volt B supply, or the tubes changed to the 6 volt type. There is plenty of room for a power transformer and rectifier tube; in place of the dynamotor. This receiver is very selective and sensitive; has RF stage and BFO. Made by Western Electric and you never saw finer wiring. Offered complete with tubes: 12B5, 3-12SR7, 12SH7 and 12A6, but less 28 volt dynamotor. Specify the frequency you desire. We have about 1500 available.



- BC-454-B-3 to 6 MC superhet receiver with all tubes. Net. **\$5.95**
- Less tubes. Net. **2.95**
- BC-453-B-200 to 500 KC superhet receiver with all tubes. Net. **5.95**
- Less tubes. Net. **2.95**
- BC-455-B-6 to 9 MC superhet receiver with all tubes. Net. **5.95**
- Less tubes. Net. **2.95**
- 28 volt dynamotor (snaps on receiver chassis) Net **\$1.95**. 3 for **5.50**

Aircraft Transmitters

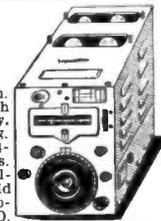- BC-457-A 4 to 5.5 MC
- BC-458-A 5.3 to 7 MC



This really fits the ham's dream. Ideal for a 55 watt transmitter with 575 volts at 250 MA plate supply, or VFO to drive a high power rig. It's a companion unit to the 454-455-453 series aircraft receivers. Made by Western Electric and really rugged. The oscillator will hold the frequency, even under rough operating conditions. Has 12J5 M. O. and 2-1625 (807) in parallel as final P. A.; or buffer to feed into a high power rig. Built in crystal dial calibration checker. Antenna loading inductance. Complete conversion data to VFO or FM oscillator is covered in CQ magazine; May '46 issue. Why not use this for your VPQ? It's a real buy. 1000 to sell; at the ridiculous price; with tubes.

- BC-457-A Transmitter 4 to 5.5 MC. Complete with 4600 KC crystal and tubes. Your Cost **\$9.95**
- BC-458-A Transmitter 5.3 to 7 MC. Complete with 6200 KC crystal and tubes. Your Cost **\$9.95**
- Special. Both of above on shock mounting rack **\$18.95**
- 2" 0 to 10 antenna current meter in case; ideal for loading above transmitter. Each **\$2.49**
- Transmitter; shipping weight, 12 lbs.

BC-456-E Western Electric Modulator Unit \$2.95

Companion unit of BC-457-A and BC-458-A. Complete with 12J5 and VR150 and 1625. Gives necessary output to modulate above transmitters. We have a few more modulators than transmitters and are offering them at a ridiculously low price. You can salvage many parts from this modulator unit. Offered complete with tubes. Very special **\$2.95**. 3 for **\$7.95**. Dynamotor 28 volts input; 250 volts 160 MA output continuous. Snaps on modulator **\$2.95** each; 3 for **\$7.95**.



JAN OR REGULAR BRAND TUBES CARTONED OR UNCARTONED

SPECIAL at .49			SPECIAL at .69		
30/44	27	1S5	1J6	6F6	1V
76	26	1T4	1D5	6Y6	75
37	6H6	384	1H4	12SF7	77
5Y4G	6AC7	1L4	30	12SQ7	24
5Y3GT	6SH7	3A4	5Z3	46	78
6C8G	56	1R5	6SA7GT	38	12SA7
6F8G	6B4G		6SK7GT	6SJ7	12SK7
1633	80		6SQ7GT	6G6	12SQ7
1634	6K7	50B5	5U4	6C5	12SR7
12SN7	12J5	12AT6	5T4	12Z3	12A6
6SN7		12BA6			
6SD7		13BE6			
42	6D6	35W4			
41	6C6				

VERY SPECIAL JAN 6L6M..... .99

NAVY RBZ RECEIVERS

RED HOT. We have about 200 of the navy miniature portable short wave receivers left, covering 2 to 5.5 M.C., offered complete with batteries and head phones and canvas carrying case. We will also include a 5 to 13 M.C. tuning unit which can be wired in. Very special all for only **\$14.88** Shipping weight 7 lbs.

BC-654 TRANSMITTER RECEIVER NET \$16.95



Portable voice and CW transmitter and receiver for portable, mobile, and fixed station operation. 7-tube super-heterodyne receiver with 3.5 microvolt sensitivity on voice and 0.5 micro-volt sensitivity on CW, and 100 milliwatts undistorted power output. 455 KC IF. Uses 3-1N5GT, 1-1A7GT, 2-3Q5GT, 1-1H5GT tubes. 6-tube transmitter with antenna tuning network, Colpitts thermal compensated oscillator, class C final with 2-307A tubes in parallel, and crystal oscillator for checking frequency every 200 KC. 25 watts output on CW and 11.2 watts output on voice. Frequency range, transmitter and receiver, 3800 to 5800 KC. Ideal for Hams! Comes complete with cover; set of tubes installed, 5 spare tubes and 3 spare pilot lights. Less power supplies. These units are used but in good condition. Shipping weight 50 lbs. Net price with all tubes and spares **\$16.95**

NET price, less the 1 1/2 volt receiver tubes but with trans. tubes. **\$12.95**

SCOOP IN RADIO TUBES

6 & 12 VOLT LOCAL TUBES 50A5 35A5					
7A4	7H7	7B5	7J7	7E6	7Y4
7A6	7C7	7B6	7R7	7E7	7Z1
7C5	7Q7	7C6	7V7	7A7	7H7
14Q7		14B6		35Y4	79c EACH
14A7		14H7		14R7	


1 1/2 VOLT LOCAL TUBES		
11D5	11B4	99c EACH
11H4	11N5	
11A4		

450 M. C. BC-645 15-TUBE I. F. F.

Easily Converted to a Voice—CW—Transmitter—Receiver

MADE BY GENERAL ELECTRIC

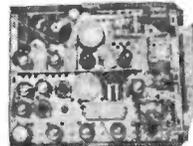- ★ Factory Printed—Conversion Diagram
 - ★ New ★ Pictured with Cover Removed
 - ★ With 15 Tubes. NET \$15.95. Two for \$31.00
- ANOTHER HOT WAR SURPLUS SCOOP



ARMY BC-645 I.F.F. UNIT. Early in the war, when radar picked up a plane, there was no way of knowing whether it was friendly or not. That was before BC-645 was invented. BC-645 sent out a signal that identified the plane as American. It probably saved more lives than any other piece of electronic equipment made. With some modifications the set can be used for 2-way communication, voice or code, on the following bands: ham hand 420-450 mc., citizens radio 460-470 mc., fixed and mobile 450-460 mc., television experimental 470-500 mc. Equipment capable of doing the jobs of the modified set sells for hundreds and hundreds of dollars. The 15 tubes alone are worth more than the sale price. 4-7F7, 4-7H7, 2-7E6, 2-6F6, 2-955 and 1-WE316A. It now covers 460 to 490 mc. Each BC-645 is shipped with a Belmont factory printed conversion diagram, showing how to make AC power supply modulator and how to make Transmitter and Receiver changes. Most Hams and experimenters already have the few parts necessary. New BC-645 with tubes less power supply. Shipping weight 25 lbs. Extra WE316A Tubes \$1.29 each. 12 Volt Dynamotor **\$4.95**

ARMY PARTS SALVAGE SCOOP NET \$2.95. TWO FOR \$5.00

Army PE-157 Vibrator type power supply, 2 volt-6 volt type. We have found no immediate use for this as a unit, but for salvage, it's a dream. Chuck full of transformers, resistors, condensers, relays, etc. One relay, which is a 10,000 plate type, is worth more than the sale price. Also there is a 4" heavy duty PM speaker with a dustproof waterproof cone and a handy dual section selenium rectifier rated at 1 1/2 amps. Has a handy, usable hinged lid metal case, size 6x6x12. A red hot value priced less vibrators. Shipping weight, 20 lbs. 2,500 to sell.



PHONO-OSCILLATOR 2-TUBES

NET \$3.69

Complete, wired and tested. 800 to 1500 KC. Model B-4. Has audio gain stage for proper power output. Complete with tubes ready to operate. **\$3.69**



MIKE-OSCILLATOR

800 to 1500 KC Mike Oscillator model C-4. Not only does the unit work as a phono-osc., but has added gain stage for a crystal mike. Priced complete, wired and tested with 3 tubes and fader control. Net **\$4.95**. Crystal Mike **\$4.90 extra**




DELUXE MIKE OSCILLATOR

800 to 1500 KC Phono-Mike Oscillator. Makes any receiver a P.A. system. Record player or Recording amplifier. 3 stage high output unit with power transformer for AC operation only. High gain input stage for crystal or dynamic mike. Control on panel for fading recording to voice, simulating an actual broadcast station. Used by dealers and servicemen for demonstrations, tests and for home entertainment. Model DL-5 Complete with 3 tubes, wired and tested. Net **\$7.95**. Crystal Mike **\$4.90 extra**

DETROLA CHANGER


\$14.95

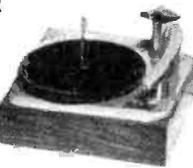Very Special. Detrola automatic changer (plays 12 10-in. or 10 12-in. records). New and factory cartoned. Dealers' net **\$14.95**. Attractive walnut made to fit base. Net **\$2.49**



AERO AUTOMATIC CHANGER SCOOP PRICE \$13.95

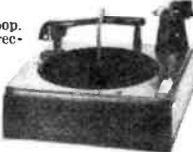This is a real changer scoop. Plays 12 10-in. or 10 12-in. records. Has all plastic arm with latest crystal cartridge. Brand new and factory cartoned. We have plenty at the scoop price of only **\$13.95**. Attractive walnut made to fit base **\$2.49 extra**.



PHONO-MOTOR. Latest rim drive 78 RPM 110 volt type with turntable scoop price 100 to sell. Net **\$3.19** G.I. Heavy Duty dual (adjustable) speed gear driven motor 110 volt AC governor type. Net **\$15.49** Astatic or shure light weight crystal pickups. Net **\$2.29** Each

Double 40 Watt Fluorescent Ballast made by General Transformer **\$3.98**

11A6 11C6 **\$1.49 EACH**
Regular net on these tubes is \$1.81. These tubes are all of leading make.

McGEE RADIO COMPANY

Write for Catalog

Send 20% Deposit—Bal. Sent C.O.D.
1225 McGEE ST., KANSAS CITY, MISSOURI
ON PARCEL POST ORDERS INCLUDE AMPLE POSTAGE

Radio & Electronic
Government Surplus

MINE DETECTORS



\$995

F.O.B. DETROIT

MODEL
AN-PRS-1

Brand new army mine detectors; portable, will detect metallic and non-metallic objects; very sensitive; using 955 tube in detecting head; two tube amplifier using two 1N5GT; headset, or microphone. Also 150 micrometer; power supply, 3-45V, one 6-V or two 3-V batteries. Complete with instrument less batteries. Packed in original cases. Shipping weight 108 lbs.

THIS MONTH'S RADIO BARGAINS

INTERPHONE AMPLIFIERS—complete with tubes and dynamotor.....	\$2.50
WIRE—14, 16, 18, 20, 22 gauge up to 50 ft. lengths.....per lb.	.20
AUTO ANTENNA—3 section 64" side cowl mount—2insulators	1.50
125 MFD. CONDENSERS at 350 Volts C.D.....	.25
500 MFD. CONDENSERS at 10 Volts.....	.25
.3 MFD. OIL FILLED CONDENSERS at 400 Volts.....	.05
BY-PASS CONDENSERS, ASSORTED SIZES—per hundred.	1.50
BUFFER CONDENSERS .01 1600 Volts per hundred C.D..	12.00

No order under \$5.00—please.
Send check or money order.

Orders shipped C.O.D. subject to 20% advance deposit.

Write us about your needs

RADIO CENTER


Radio & Electronic Surplus
2530 E. DAVISON AVE.
DETROIT 12, MICHIGAN

What's New in Radio

NEW V.O.M.

Star Measurements Company of New York has recently introduced its new low-priced volt-ohm-milliammeter to the service field.

The Model M 11 Star Tester covers

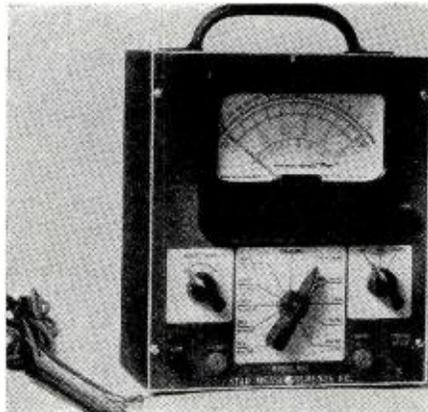

voltage ranges up to 1000 volts, both a.c. and d.c. Current ranges up to one ampere and resistance ranges up to five megohms are also included. Calibrated db. scales provide for measurements as high as 54 db.; the zero power level is based on a 6 mw. level in a 500 ohm line. In all, 27 separate ranges of measurement are provided.


The instrument features a large 4½", 400 microampere Marion meter, an etched aluminum panel, and a gray crackle finish metal cabinet for use under all operating conditions. The entire unit weighs four pounds and comes complete with test leads and batteries.

Prices and complete data will be furnished by Star Measurements Company, 442 East 166th Street, New York 56, New York.

PLASTIC PARTS

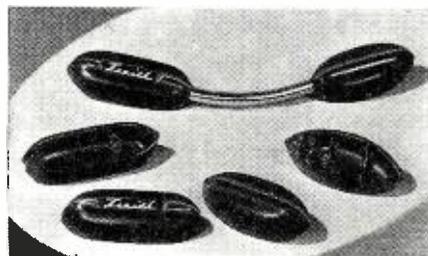G. Felsenthal & Sons of Chicago, molders and fabricators of plastics, are presently offering their services to radio manufacturers for the processing of plastic parts for the industry.

Lightweight, high impact polystyrene was used in the tone arm pickup assembly illustrated. Both heads are injection-molded and assembled to the



metal arm by means of cement. Trade-names and other identifying marks are etched in the mold and the recessed letters filled in with white paint in a separate operation after molding. The company invites inquiries by

manufacturers regarding their plastic problems. Complete specifications and information about the part to be molded should accompany requests for additional data. Address all requests to G. Felsenthal & Sons, 4100 W. Grand Avenue, Chicago 51, Illinois.

MODULATION METER

A new instrument, designed for use in the amateur phone bands falling between 3.5 and 54 mc., has been announced by Sylvania Electric Products Inc.

This modulation meter which operates without vacuum tubes and requires no batteries or a.c. line power can also be used by forestry, emergency, police, and marine services using AM transmitters.

This compact, lightweight instrument is used for monitoring signals with respect to modulation. Modulation percentage is indicated on a direct-reading, hermetically-sealed meter which is flush-mounted on a panel approximately 4" square. Elimination of vacuum tubes, batteries, and the need for a.c. line input is accomplished through the application of the Sylvania germanium crystal diode, Type 1N34.

The meter permits determination of the modulation percentage of either a sine-wave-modulated or a voice-mod-



ulated carrier, as well as giving an indication of carrier shift. It enables the user to avoid over-modulation.

The Model X-7018 modulation meter is supplied with a 75 ohm twin-lead transmission line for use with an external link circuit; handy toggle switches; trimmer condenser for convenient peaking of input circuit and a jack to disconnect meter and insert phones for audible signal check.

Sylvania Electric Products Inc. at 500 Fifth Avenue, New York 18, New York will furnish additional information upon request.

SIGNAL GENERATOR


Northeastern Engineering, Inc. of Manchester, New Hampshire has recently announced a new signal generator, Model 700A.

This generator covers the range from 160 kc. to 20 mc. on fundamental


GUARDIAN

presents...

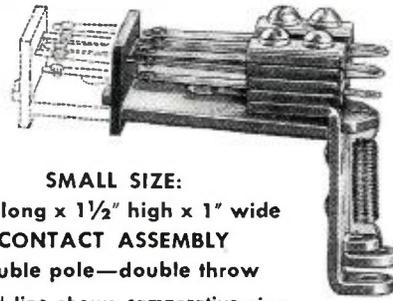a new **MIDGET**
CONTACT ASSEMBLY
Interchangeable
with the **GUARDIAN Series 200**
STANDARD CONTACT ASSEMBLY
AND COIL ASSEMBLY




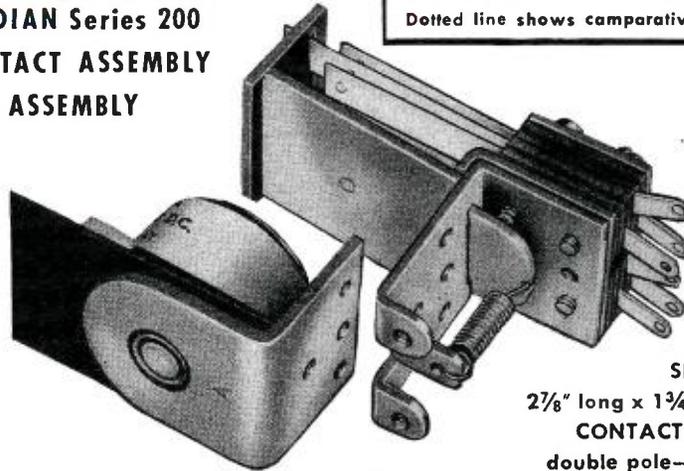SMALL SIZE:
1 5/8" long x 1 1/2" high x 1" wide
CONTACT ASSEMBLY
double pole—double throw
Dotted line shows comparative size




SIZE
2 7/8" long x 1 3/4" high x 1" wide
CONTACT ASSEMBLY
double pole—double throw

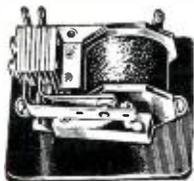Popular RADIO RELAYS in the GUARDIAN line:



K-100 Keying Relay For low voltage control of high voltage transmission. Guardian Series K-100 Relay will follow key or bug at highest WPM rate attainable. High speed response, strong magnet and return spring give clean make and break, produce best CW note. Coils: 5 to 16 v., A.C.; coils for other voltages on specifications.

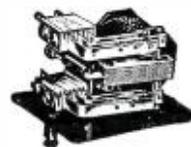B-100 Break-in Relay For break-in operation on amateur transmitters. The Guardian B-100 Relay has laminated field piece and armature. Fine 1/4" silver DPDT contacts, capacity to 1500 watts, 60 c., non-inductive A.C., and in A.C. primary circuit of any inductive power supply delivering up to 1 KW, inclusively.



T-100 Time Delay Relay. In radio transmitter circuits, Guardian's T-100 Time Delay Relay prevents damage of rectifiers and tube filaments by preventing plate current before filaments are sufficiently heated. Laminated field piece and armature. Mounted in dust-proof metal box.

L-250 Overload Relay Provides accurate, fixed overload protection against current surges and continuous overloads. Guardian's L-250 Relay replaces expensive, time-wasting fuses. Attracts armature on 250 mils. Max. drop across coil—10 v. Guardian's L-500 Relay attracts armature at 500 mils. Max. drop across coil—5 volts. Ideal for experimenters on new circuits.



A-100 Antenna Relay A low loss AISiMag insulated relay. For single wire fed installations specify the A-100-C, SPDT unit. Two A-100-C in place of one A-100 in open wire line systems will avoid possible impedance mismatch. A very popular relay with radio amateurs.

SEE THESE AND OTHER GUARDIAN RELAYS AT BOOTH 51, MAY 12-16, STEVENS HOTEL, CHICAGO, ILL.

Ask your jobber for the new midget contact switch assembly which is interchangeable with the Guardian's Series 200 coil assembly. Your jobber carries a complete line of Guardian radio relays. If unable to attend Radio Parts Show, write for Bulletin R-6.

GUARDIAN



ELECTRIC

1630F W. WALNUT STREET


CHICAGO 12, ILLINOIS

A COMPLETE LINE OF RELAYS SERVING AMERICAN INDUSTRY



HAS THE BARGAINS

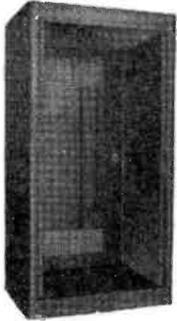SAVE \$10.00 ON THIS PROFESSIONAL RELAY RACK



Add Professional appearance to your transmitter, PA system or any Electronic equipment.

42" H x 22" W x 16 1/2" D — panel space 36 3/4" for standard notched panels. Made of 1-16" cold rolled steel, rounded front vertical corners, rear door with loose joint hinges and flush snap catch. Finished in Black Ripple Enamel.

Pat.-Metal ER 213, Brand New, shipped KD in original factory pkg. Cpte with all hdwe. Wt. 100 lbs. Regularly a Net \$28.50 Value.

Stk. No. 1A52
Special Each **\$18.50**



For 19 years, thousands upon thousands have found B-A as the place for honest, dependable and friendly service—a firm in which they have complete confidence.


You, too, can buy everything from B-A with the confidence—it will be right as described—or your money will be refunded.

ORDER NOW, from this ad while these Outstanding Values are still available—CHECK ALSO the big new B-A Catalog No. 471—84 pages of more Bargains and everything you need in Radio. WRITE US if you did not receive it.

Our terms: Cash with order or COD with 20% deposit please.

MEISSNER 6-TUBE

TWO BAND AC-DC SUPER HET KIT

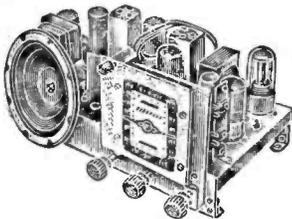

For those who like to "build their own," this kit is "tops." Kit includes all parts, tubes and speaker—everything except cabinet. Easy to build with the detailed step by step instructions included.

Covers broadcast band 550 to 1600 KC and short wave 6 to 18 MC. Tubes used: 12SK7 RF amp., 12SA7 osc. converter, 12SK7 1F amp., 12SQ7 det., AVC and 1st audio, 35L6-GT power output and 35Z5GT rectifier.

Chassis dimension overall when completed 12 1/4" L x 7" D x 5 3/4" H.

Stk. No. 31A60.
Net Per Kit **\$21.95**

JOHNSON VARIABLE



Dual section, 200 mmfd. per section, 2000 V. breakdown. Spacing .045". Type 200FD20.

List \$10.
No. 18A510 Special Ea. **\$2.95**

Johnson variable, dual section, 304 mmfd. per section. Spacing .045".

Type 30ED20. List \$9.95.
Stk. No. 18A509, Special Each. **\$3.45**

Johnson variable, dual section, 151 mmfd. per section. Spacing .175". Type 150DD70. List Value \$16.00.

Stk. No. 3A29, Special Each **\$5.95**

"RCA" Audio Oscillator

Range 30 to 15000 CPS Continuous



Provides audio signal for checking fidelity curves; testing speakers, PA systems, etc. Choice of 250, 500 or 5000 ohm output impedance. Output Voltages of 5.2 to 37.5 at no load. Distortion under 5%. 8 3/4" dial. Case size 9 1/2" x 13 1/4" x 6 1/2", wt. 19 lbs. Furnished Complete.

Comparable instruments at today's prices sell at over \$100.00. You get these Brand New in original factory packing.

Stk. No. 5A164. While They Last, Each **\$59.95**

BARGAINS in Aluminum Can Screw Neck Electrolytics


Direct Replacement for Upright Wet and Dry Electrolytics



Designed for heavy duty service—size 1 3/4" x 4" with 3/4" standard threaded neck—easy to mount in holes of old condenser to be replaced. Finest Quality, Fully Guaranteed.

8 Mfd.	No. 15A378	Ea.60
16 Mfd.	No. 15A379	Ea.82
20 Mfd.	No. 15A383	Ea.88
30 Mfd.	No. 15A380	Ea.	\$1.25
8-8 Mfd.	No. 15A381	Ea.97

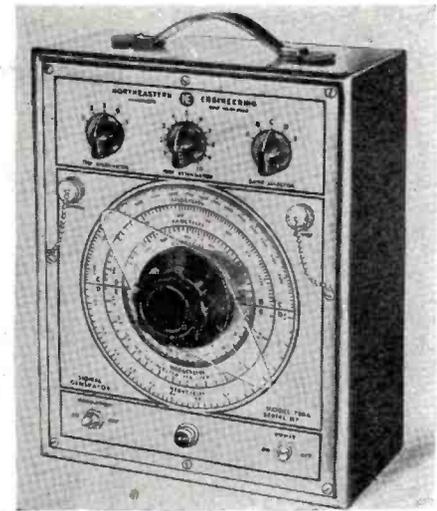frequencies in five bands; band A from 160 kc. to 370 kc.; band B from 370 to 1080 kc.; band C from 1080 kc. to 2500 kc.; band D from 2.5 mc. to 7.3 mc. and band E from 7.3 mc. to 20 mc. The dial of the unit is also equipped



to indicate a sixth band (band F) which has been calibrated in degrees for special calibrations.


Modulation of the unit is approximately 30 per-cent at 400 cycles with provision being made for external modulation. The signal generator uses two tubes and operates on 105-125 volt, 60 cycles.

Additional data on this unit will be supplied by *Northeastern Engineering, Inc.* of Manchester, New Hampshire upon request.

ANTENNA COUPLER

A universal type antenna insulator-connector for making a secure weather-proof junction between *Amphenol* "RG" type flexible coaxial line and any current fed antenna or array has been announced by *James Knights Company* of Sandwich, Illinois.

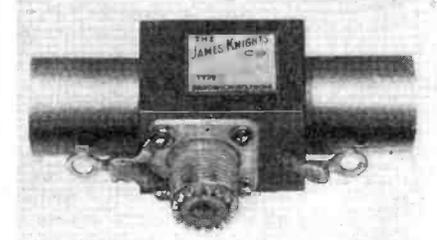Known as the J-K Impedacoupler, this unit may also be used with *Amphenol* "flat lines" or with the usual



type of open wire lines. Equipped with an *Amphenol* type 1R receptacle, the unit requires only the addition of an *Amphenol* type 1SP cable connector on the end of the coaxial line for quick, positive connection without fanning and without disrupting the terminal impedance of the line.

An insulator block provides optimum dielectric properties and ample strength to withstand the pull of the antenna and support the weight of the coaxial line.

The insulator is drilled at both ends for bolts or rivets for holding tubing

(Continued on page 136)

BURSTEIN-APPLEBEE Company
1012-14 MCGEE STREET,
KANSAS CITY 6, MISSOURI



Did You Get It?
The New B-A Catalog No. 471



TELEVISION-

Does it Hold

A Future

For You?

SPECIAL INVITATION TO WAR VETERANS

With extensive new training facilities under the personal supervision of the famed inventor of the radio vacuum tube, Dr. Lee de Forest, we are able to accept additional applications from Veterans for Television training under the G.I. Bill of Rights. For qualified men who are seriously considering entering a residence school, we have a limited number of Home Study Courses which are available free of charge. Your success with this course will not only help you to decide your own future in Television but will also aid us greatly in qualifying you for residence training.

Send your name and address for your Eligibility Questionnaire. If you qualify under the simple rules, you may start your Home Study Television Course at once and entirely without cost or obligation to you.

American Television Laboratories, Inc.

5050 BROADWAY • CHICAGO 40, ILLINOIS

A NOVEL INPUT CIRCUIT

By ZYGMUNT HOF

Transformerless matching from a low impedance microphone to the input tube of an amplifier is accomplished by a grounded grid circuit.

MANY servicemen are faced with the problem of matching p.a. amplifiers with dynamic microphones where the impedance of the mike proves to be 500 ohms while the amplifier has only a high impedance input—all this without an available matching transformer!

If such a problem is facing you, this special input circuit, which is a cousin to the cathode-follower, may be used. Known as the grounded grid amplifier, to use this circuit the input impedance must first be calculated.

Using a pentode, Fig. 1A shows the actual circuit and Fig. 1B the equivalent circuit. The mike may be seen connected between the cathode and grid, the latter being grounded. It is equivalent to a generator of a voltage E , with internal resistance, R_m , connected in series with the load resistance.

From Fig. 1B:

$$i_1 + i_2 = G_m e_g$$

$$R_a i_1 = E + i_2 (R_m + R_1)$$

$$e_g = E + R_m i_2$$

From these equations:

$$Z_{\text{Input}} = \frac{e_g}{i_2} = \frac{R_a + R_1}{\mu - 1} \text{ (approx.)}$$

where: μ = amplification factor
 R_a = plate resistance
 G_m = mutual conductance
 R_1 = load resistance


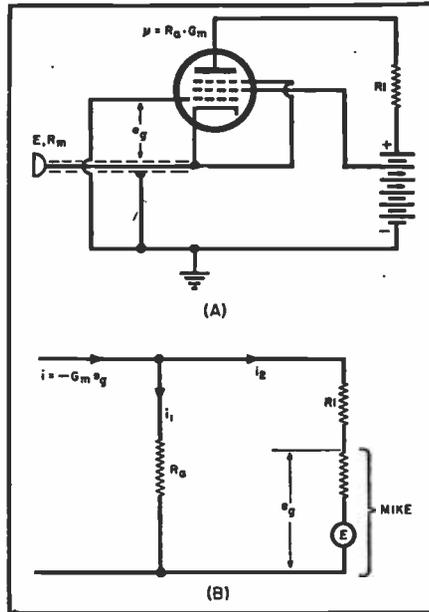


Fig. 1.

According to the formula, most pentodes, under recommended operating conditions, will be found to have an input impedance of around 1000 ohms in this circuit.

The particular p.a. amplifier used in this case had a 6SJ7 in the first stage.

Fig. 2.

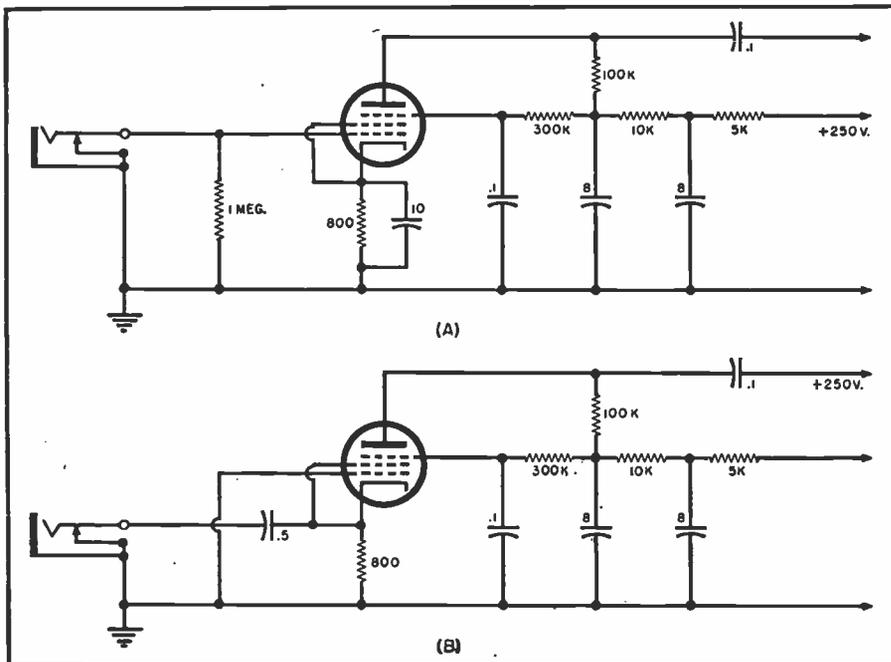

Buy books
 on radio
 from these leading
 radio parts dealers
 WHO REGULARLY STOCK MOST OF THESE
 BOOKS, AND CAN OBTAIN QUICKLY
 NEARLY ALL OTHERS CURRENTLY IN PRINT

- ALABAMA: Birmingham, Forbes Distributing, Reid Distributing.
- ALASKA: Anchorage, Robbie's Radio Supply, Fairbanks, Fairbanks Radio Supply, Juneau, Alaska Electronics.
- ARIZONA: Phoenix, Radio Parts, Radio Specialties.
- ARKANSAS: Little Rock, Tanner Radio & Electronics.
- CALIFORNIA: Fresno, Jack C. Arbuckle, Martin Distributing, Long Beach, Fred S. Dean Radio Electric Co., Scott Radio Supply, Los Angeles, Henry Radio Shop, Hollywood Radio Supply Co., Kierulff & Co., Pacific Radio Exchange, Inc., Radio Equipment Distributors, Radio Specialties, Oakland, Electric Supply, Pasadena, Dow Radio Supply Co., Sacramento, E. M. Kemp Co., San Diego, Western Radio & Television Supply Co., San Francisco, Offenbach-Reimus, Zack Radio, San Jose, Frank Quement, Santa Ana, Radio & Television Equipment, Santa Barbara, Channel Radio Supply.
- COLORADO: Colorado Springs, Murray Radio Co., Denver, Radio Products Sales, Western Electronic Lab. Co.
- CONNECTICUT: Hartford, Harty & Young, Inc., R. C. Scott & Co., New Haven, Congress Radio.
- D. C., Washington: Capital Radio Wholesaler, Kenyon Radio Supply, Sun Radio Service.
- FLORIDA: Miami, Electric Supply, Walder Radio, Pensacola, Grice Radio, Gulf Radio, Pensacola Appliance, St. Petersburg, Cooper Radio, Welch Radio Supply.
- GEORGIA: Atlanta, Concord Radio, Southeastern Radio Parts, Yancey Co., Inc., Columbus, Radio Sales & Service Co.
- IDaho: Boise, Craddock's Radio Supply.
- ILLINOIS: Chicago, Allied Radio, Concord Radio, Newark Electric, Peoria, Klusau Radio & Electric, Rock Island, Tri-City Radio Supply.
- INDIANA: Indianapolis, Radio Distributing Co., South Bend, Radio Distributing Co.
- IOWA: Des Moines, G. W. Omaha Co.
- KANSAS: Topeka, Overton Electric Co.
- KENTUCKY: Lexington, Radio Equipment, Owensboro, Central Electronic.
- MARYLAND: Baltimore, Kann-Eliert Electronics, Wholesale Radio Parts.
- MASSACHUSETTS: Boston, DeMambo Radio Supply, Radio Shack, Worcester, Radio Maintenance Supply Co.
- MICHIGAN: Detroit, M. N. Duffy & Co., Radio Electronic Supply, Radio Supply & Engineering Co., Inc., Grand Rapids, Wholesale Radio Co., Lansing, Budd's Music House, Muskegon, Industrial Electric Supply, Pontiac, Electronic Supply.
- MINNESOTA: Duluth, Lew Bonn Co., Minneapolis, Lew Bonn Co., Northwest Radio Electric Supply.
- MISSISSIPPI: Greenville, Goyer Supply Co., Jackson, Cabell Electric, Ellington Radio, Inc.
- MISSOURI: Joplin, 4-State Radio & Supply, Springfield, Harry Reid Radio Supply, St. Louis, Radonics.
- NEBRASKA: Omaha, Omaha Appliance, Radio Equipment Co.
- NEW JERSEY: Trenton, Allen & Hurley.
- NEW YORK: Albany, Port Orange Radio Distributing, E. E. Taylor Co., Buffalo, Bars Radio & Electronic Parts Co., Buffalo Radio Supply Co., Genesee Radio & Parts, Radio Equipment, Jamaica, Norman Radio Distributors, Middletown, L. & S. Radio Sales, New York City, Fordham Supply Co., Newark Electric Co., Terminal Radio Corp., Niagara Falls, Niagara Radio, Poughkeepsie, Chief Electronics, Rochester, Machine Radio & Electronic Equipment, Rochester Radio Supply, Syracuse, Broome Distributing, Stewart W. Smith, Troy, Trojan Radio, Utica, Yeath Electric Co., White Plains, Westchester Electronic Supply Co.
- NORTH CAROLINA: Fayetteville, Dugan's Radio Supply Co., Eastern Radio Supply, Winston-Salem, Lambeth Electric Supply.
- OHIO: Akron, Brighton Sporting Goods, Olson Radio Warehouse, Radio & Electronic Supply, Cincinnati, Holub & Hogg, Steinberg's, Cleveland, Pioneer Radio Supply, Progress Radio Supply, Radio & Electronic Parts, Columbus, Hughes-Peters, Inc., Thompson Radio Supplies, Dayton, Standard Radio & Electronic Products, Lima, Warren Radio, Toledo, Toledo Radio Specialties, Warren Radio, Warren, Radio Specialties.
- OKLAHOMA: Enid, Radio-Electronics, Oklahoma City, Radio Supply Co.
- OREGON: Portland, Bargett Supply, Harper-McGee, Lou Johnson Co., United Radio Supply.
- PENNSYLVANIA: Altoona, Kennedy's Radio Supply, Erie, Warren Radio, Philadelphia, Almo Radio, M. & H. Sporting Goods, Radio Electric Services, Sanders Electronics, Eugene G. Wile, Pittsburgh, Radio Parts Co., Tydings Co., Reading, George D. Barbey Co., Scranton, Scranton Radio and Television Supply, Wilkes-Barre, General Radio, York, C. R. Minnich.
- RHODE ISLAND: Providence, DeMambo Radio Supply.
- SOUTH CAROLINA: Anderson, Electronic Supply, Columbia, Dixie Radio Supply Co.
- TENNESSEE: Memphis, Bluff City Distributing.
- TEXAS: Beaumont, Montague Radio Dist. Co., Corpus Christi, Wicks-De Vilbiss, Dallas, Wilkinson Brothers, El Paso, Midland Specialty, Houston, R. C. Fall, Lubbock, R & R Parts & Supply Co., San Antonio, Modern Radio Supply, Odessa, Radio Supply.
- UTAH: Salt Lake City, Radio Supply Co., Standard Supply.
- VIRGINIA: Norfolk, Radio Parts Distributing, Radio Supply.
- WASHINGTON: Everett, Pringle Radio Wholesale Co., Seattle, Harper-McGee, Radio Products Sales, Seattle Radio, Spokane, Harper-McGee, Northwest Electronics.
- WEST VIRGINIA: Charleston, Hicks Radio Supply, Wheeling, General Distributors, Wheeling Radio Supply.
- WISCONSIN: Madison, Satterfield Radio Supply.

CANADA

BRITISH COLUMBIA: Vancouver, Rygrade Radio, Ltd., Western Agencies, Victoria, Ellison Quaise Radio Supply.

Our Dealers Also Regularly Stock Most of the Following Books and Can Obtain Rapidly Nearly Any Item Not in Stock

Send Stamp for Catalog

Elementary Theory	
"Fundamentals of Radio," Terman.....	\$4.00*
"Principles of Radio," Henney.....	3.75*
"Basic Elec. for Communications," Timbie.....	3.75*
"Electronics," Coyne.....	5.00*
"Radio Physics Course," Ghirardi.....	5.00*
"Elements of Radio," Marcus.....	4.00*
"Fundamentals of Radio," Avelut.....	4.00*
"New Radioman's Guide," Audel.....	4.00*
"Understanding Radio," Watson.....	2.80*
"Electrical Communication," Albert.....	5.50*
"Elec. Fund. of Communications," Albert.....	4.00*
"Basic Radio," Hoag.....	3.75*
"Short Wave Wireless Comm.," Ladner.....	6.50*
"Electrical Essentials of Radio," Sturberg.....	4.50*
"Foundations of Radio," Duncan.....	2.75*
"Radio: Fundamental Prin. & Prac.," Altmstead.....	1.80*
"Basic Radio Principles," Suffern.....	3.50*
"Radio Material Guide," Altmstead.....	3.50*
Intermed. & Advanced Theory & Engineering	
"Radio Engineering," Terman.....	\$6.00*
"Fund. of Engineering Electronics," Dow.....	5.50*
"Prin. of Radio Communication," Morecroft.....	5.50*
"Engineering Electronics," Fink.....	5.50*
"Applied Electronics," M. I. T.....	6.50*
"Communication Engineering," Everett.....	5.50*
"Electronics," Hines.....	5.50*
"Electronics for Engineers," Markus.....	6.00*
"Fund. of Electric Waves," Skilling.....	3.00*
"High-Freq. Alternating Current," Hillman.....	5.50*
"Radio Receiver Design," Sturley.....	5.00*
"The Technique of Radio Design," Zepler.....	4.00*
"Prin. of Radio Engineering," Glasow.....	4.50*
"Communication Networks Vol. 1.," Guillemin.....	5.50*
"Communication Networks Col. 2.," Guillemin.....	8.00*
Electron Tubes & Industrial Electronics	
"Electron Tubes in Industry," Henney.....	\$5.50*
"Industrial Electronic Control," Cockrell.....	5.50*
"Electronics in Industry," Chute.....	2.75*
"Theory & Appl. of Electron Tubes," Reich.....	4.00*
"Prin. of Electron Tubes," Reich.....	4.50*
"Inside the Vacuum Tube," Reich.....	4.50*
"Fund. of Vacuum Tubes," Eastman.....	4.00*
"Principles of Electronics," Kloeffer.....	2.75*
"The Physics of Electron Tubes," Koller.....	3.25*
"High-Freq. Thermionic Tubes," Harvey.....	6.50*
"Theory of Thermionic Vac. Tubes," Chaffee.....	2.00*
"Electronic Devices," Audel.....	5.00*
"Experimental Electronics," Muller.....	5.00*
"Electromagnetic Waves," Scott.....	7.50*
"Electromagnetic Theory," Stratton.....	6.50*
"Electric Circuits," M. I. T. Staff.....	7.50*
"Photocells & Their Applications," Zworykin.....	5.00*
"Graphical Const. for Vac. Tube Circuits," Eastman.....	3.00*
"Electron Optics & the Electron Microscope," Eastman.....	10.00*
"Theory of Gas-filled Tubes," Eastman.....	5.00*
"Electronic Control in Resistance Welding," Eastman.....	4.50*
Radio Mathematics	
"Math. for Electricians & Radiomen," Cooke.....	\$4.50*
"Applied Math. for Radio & Comm. Eng'rs," Smith.....	3.50*
"Math. of Radio Communication," Wang.....	2.00*
"Math. & Calculation for Mechanics," Audel.....	2.00*
"Math. for Radio and Comm. Book 1.," Maedel.....	3.75*
"Math. for Radio and Comm. Book 2.," Maedel.....	4.00*
"Mathematics for Electricians," Kuehn.....	1.80*
Ultra-High Frequencies	
"U.H.F. Radio Simplified," Kiver.....	\$3.25*
"Introduction to Microwaves," Ramo.....	2.00*
"Communication Circuits," Ward.....	7.50*
"U.H.F. Techniques," Brainerd & 4 authors.....	5.00*
"Hyper & U.H.F. Engineering," Sarbacher.....	6.00*
"Understanding Microwaves," Young.....	6.00*
"Ultra High Frequency Radio Engineering," Emery.....	3.80*
"Field & Waves in Modern Radio," Eastman.....	5.50*
"Trans. Lines, Antennas & Wave Guides," King.....	3.50*
"Microwave Transmission," Shier.....	3.00*
"Electromagnetic Engineering," King.....	6.00*
"Phenomena in High Freq. Systems," Hund.....	6.50*
Operating Practice—Commercial & Aero.	
"Practical Radio Communication," Nilson.....	\$5.50*
"The Radio Manual," Sterling.....	8.50*
"Radio Operating Ques. & Answers," Nilson.....	3.50*
"How to Pass Radio License Exams.," Drew.....	2.25*
"Radio Code Manual," Nilson.....	2.75*
"Radio Direction Finders," Bond.....	3.50*
"Prin. of Aeronautical Radio Eng'ing," Sandretto.....	4.00*
"Aircraft Radio & Elec. Equipment," Morgan.....	4.50*
"Aeronautic Radio," Edger.....	4.50*
"Radio Navigation for Pilots," McIntosh.....	2.75*
Radio Servicing	
"Modern Radio Servicing," Ghirardi.....	\$5.00*
"Prin. & Prac. of Radio Servicing," Hicks.....	4.00*
"Radio Service Trade Kinks," Simon.....	5.00*
"Radio Troubleshooter's Handbook," Ghirardi.....	5.00*
"Electrical and Radio Troubleshooting Manual," Coyne.....	8.00*
"Cathode Ray Patterns," Bly.....	1.75*
Books by John F. Rider:	
"Automatic Record Changers & Recorders,".....	\$9.00*
"Vacuum Tube Voltmeters,".....	2.50*
"Servicing by Signal Tracing,".....	2.50*
"Frequency Modulation,".....	2.00*
"The Meter at Work,".....	2.00*
"The Oscillator at Work,".....	2.00*
"The Cathode Ray Tube at Work,".....	4.00*
"Inside the Vacuum Tube,".....	4.50*
"Servicing Superheterodynes,".....	4.50*
"Automatic Frequency Control Systems,".....	1.75*
"Servicing Receivers by Resistance Measurement,".....	2.00*
"D.C. Voltage Distribution in Radio Receivers,".....	1.25*
"Alternating Current in Radio Receivers,".....	1.25*
"Resonance & Alignment,".....	1.25*
"Automatic Volume Control,".....	1.25*
F. M., Television and Radar	
"Principles of Radar," M. I. T.....	\$5.00*
"Prin. of Television Engineering," Fink.....	5.50*
"Television Standards and Practice," Fink.....	5.50*
"Television Simplified," Kiver.....	4.75*
"Television," Zworykin.....	7.00*
"Frequency Modulation," Hund.....	4.50*
"Radar—What it is," Rider.....	1.00*
"Electron Optics in Television," Maloff.....	4.00*
Handbooks and Reference Data	
"The Radio Handbook,".....	\$2.50*
"Radio Engineering Handbook," Henney.....	6.00*
"Radio Engineer's Handbook," Terman.....	7.00*
"The World's Radio Tubes," Brans.....	2.50*
"Standard Handbook for Elec. Engrs.," Knowlton.....	9.00*
"Electrical Engineers Handbook," Pender.....	6.00*
"Radioelectron Designer's Handbook,".....	1.25*
"Reference Data for Engrs.,".....	2.00*
"American Electrician's Handbook," Croft.....	5.00*
"Electricians Handbook," Coyne.....	2.75*
"The Inductance Authority," Shier.....	7.50*
"Electronics Dictionary," Cooke.....	5.00*
"Electrical Dictionary," Coyne.....	1.00*
Miscellaneous	
"Piezoelectricity," Cady.....	\$9.00*
"Measurements in Radio Eng'ing," Terman.....	4.50*
"High Frequency Measurements," Hund.....	5.50*
"Radio-Frequency Elec. Measurements," Ergun.....	4.50*
"Radio Frequency Measurements," Hartshorn.....	4.50*
"Drafting for Electronics," Carini.....	2.50*
"Radio-Freq. Meas. in Bridge & Res. Method,".....	4.75*
"Gaseous Conductors," Cobine.....	6.00*
"Electronics Laboratory Manual," Wright.....	1.00*
"Lab. Manual on Radio, Fund. Prin. & Prac.,".....	1.00*
"Fund. Radio Experiments," Higby.....	7.50*
"Pulsed Linear Networks," Frank.....	3.00*

Here they are

THE WORLD'S OUTSTANDING RADIO and ELECTRONIC BOOKS


PRAGMATIC RADIO COMMUNICATION
by A. R. Nilson and J. L. Hornung

A complete radio manual covering subjects of interest particularly to the commercial radio operator. Topics include basic electricity; transmitters, receivers, and associated apparatus; and operating instructions. FM and ultra-high frequencies are included in this new edition. May be mastered by the average high school or trade school student. Book No. NC10 927 pages, \$6.50*



HOW TO PASS RADIO LICENSE EXAMINATIONS
by C. E. Drew

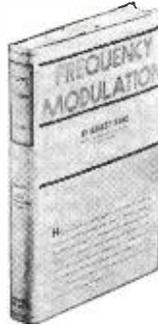A well illustrated and long-used question and answer manual for the coaching of candidates for the commercial radiotelegraph and radiotelephone operator license examinations. New post-war edition.



Book No. DH20
320 pages \$3.25*

FREQUENCY MODULATION
by August Hund

A comprehensive textbook of FM theory and engineering. Compares amplitude, phase, and frequency modulation and covers FM transmitters, receivers, and antennas. The leading basic text on this subject.

Book No. HM10
375 pages \$4.50*

PRINCIPLES AND PRACTICE OF RADIO SERVICING
by H. J. Hicks

Explains operating principles of radio circuits and service test equipment, and outlines methods of shooting trouble in radio receivers and making repairs. A good book for the radio man anticipating entry into his own repair business.



Book No. HS10
391 pages \$4.00*

Just out ELECTRONICS FOR INDUSTRY by Bendz

The principles and practical aspects of industrial, non-communications electronics. Numerous diagrams instead of mathematics clarify the discussions. Many control applications; 1- to 5-element control tubes; high-frequency induction heating; many others. The author is a leading engineer.

BOOK NO. BE20 501 PAGES \$5.00*

PRINCIPLES OF TELEVISION ENGINEERING
by D. G. Fink

A practical explanation of television receivers and transmitters. This book describes standard systems in simple language.

Book No. FT10
541 pages \$5.50*

UNDERSTANDING RADIO
by H. M. Watson, H. E. Welch, and G. S. Eby

A high-school type textbook and laboratory manual for either resident or home study. This book is distinguished by its picture layouts and step-by-step instructions.

Book No. WU10
601 pages \$2.80*

ELECTRONICS FOR ENGINEERS
by John Markus and Vincent Zeluff

This unique book condenses much invaluable electronic engineering data into graphs, charts, tables, and concise articles. In this way, it shortcuts the looking up of information. The tool value of this book is tremendous.

Book No. ME11
390 pages \$6.00*



THE OUTSTANDING PRACTICAL HANDBOOK



ENLARGED TENTH EDITION

Radio's outstanding practical text. How-to-build-it descriptions of dozens of tested-and-tried types of transmitting, receiving and test equipment. Supplemented by basic electrical and radio theory in the simplest possible language for those without mathematical or technical training. Illustrated with hundreds of diagrams and large photographs showing details of construction. Has the most complete tube tables to be found in any book.


New edition contains expanded U.H.F. sections, more test equipment which can be home-built, enlarged and modernized receiving and transmitting tubes tables, grounded-grid amplifier data, speech clipping, splatter suppressor, cathode follower data, pulse-time modulation, transformerless power supplies, wave guides, cavity resonators, butterfly circuit, klystron, U.H.F. crystal diode, radar and highly-efficient mobile antennas.

The **idea** text for the practical radioman. Over 700 pages, durably clothbound, gold-stamped. Book No. RH. \$2.50 at your dealers. Postpaid, \$2.75 in USA.; elsewhere, \$3.00.

RADIO SERVICE TRADE KINKS
by L. S. Simon

A practical trouble-shooter's manual dealing with household and car radios. Common receiver troubles are diagnosed and their remedies given. No lengthy technical discussions. A good "bench book" for the busy radio shop.

Book No. SK10 254 pages \$3.50*

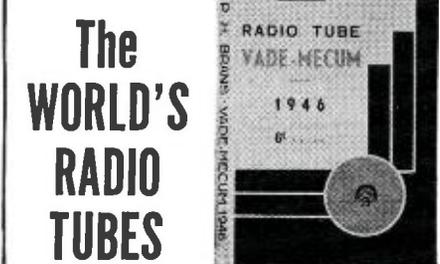

U. S., British, French, Czech, German, Italian, Russian, etc., etc.

240 pages of complete characteristics with explanations up to date—1946 edition just out

ELECTRONICS says, "Here at last is the radio tube handbook radio engineers have dreamed of... in seven carefully prepared tables and charts."

"Probably the most complete and authoritative set of tube-data in existence," says RADIO CRAFT.

BUY IT AT YOUR FAVORITE RADIO PARTS DEALER or direct by mail from us.

\$2.50 per copy; add 15¢ postage outside U.S.A.

* Add 3% (minimum, 10¢) for postage and packing; foreign, 10%. Prices are subject to change without notice.

If you don't live near or deal regularly with one of our dealers, you may order direct from

Editors and Engineers, 1302 KENWOOD ROAD, Santa Barbara, CALIFORNIA

RED HOT SPECIALS!

U. S. GOVERNMENT SURPLUS ELECTRON TUBES

Type	Your Cost	Type	Your Cost
3AP1.....	\$2.95	5Y3.....	43c
3BP1.....	2.95	50L6.....	69c
5BP1.....	3.95	6AG7.....	69c
5CP1.....	3.95	2X2.....	79c
5FP7.....	3.95	6SJ7.....	49c
7BP7.....	4.95	12SH7.....	49c
9LP7.....	5.95	6SS7.....	49c
12DP7.....	6.95	7S7.....	49c
300TH.....	7.95	6SF5.....	59c
829B.....	3.50	6V6GT.....	69c
837.....	1.85	12SQ7.....	59c
6AK5.....	.95	89.....	49c
5U4.....	.59	77.....	49c
78.....	.49	39-44.....	49c
12A6.....	.69	12SK7.....	49c
6K7.....	.49		

OIL-FILLED INPUT POWER TRANSFORMER

Mfd. by Western Electric. Navy inspected. H.V. Trans.: Pri. 115 V, 60 cycles, 7.4 amps.; sec. 2350 V @ .340 amps., metal case oil filled, four stand-off terminals; size overall 7"x7"x7 1/4", ea. \$3.95

FILTER CHOKES

All Fully Enclosed

- 15H. ±10% @ 165 MA. DC., .5 H., 60 cycles shielded, 2 stand-off terminals: size 4 1/4"x4"x3 3/4", each. 95¢
- Dual, 15H. @ 100 MA., 400 ohms DC. Each section, 500 VDC insulation test. 3 1/2"x3"x6" High; 4 MTG. Studs and 4 terminals, each. 79¢
- 59H. Min. @ 100 MA.; 10V RMS 60 cycles; 850 ohms DC. Res.; 4 MTG. Studs, size 4 1/4"x3 1/4"x3 3/4", each. 79¢
- 3.7 H. @ 145 MA. DC., 125 ohms DC. Res. 4 MTG. Studs, each. 95¢

OUTPUT TRANSFORMERS

- 50L6. 39¢
- IMPEDANCE 4000 ohms, SEC. 4000 ohms TAPPED AT 250 ohms, FREQ. RESPONSE 250 to 2500 CYCLES, HERMETICALLY SEALED METAL CASE 1 1/4"x1" O.D. 29¢
- IMPEDANCE 1184 ohms, SEC. 165 ohms, FREQ. RESPONSE 475 to 3000 CYCLES, ENCLOSED IN SHIELD 1.4" LG. 1" O.D. 29¢
- IMPEDANCE 25,000 ohms, SEC. 4000 ohms, FREQ. RESPONSE 2000 to 10,000 CYCLES, SHIELDED CASE 1 1/4" H. x 1" DIA. 29¢

Wholesalers, Dealers, Institutions and Other Quantity Purchasers ... Write, Wire, Phone for Quantity Prices, All Shipments F.O.B. Chicago—20% Deposit Required on All Orders.

DEPT. C

ARROW SALES, INC.
59 WEST HUBBARD STREET
CHICAGO 10, ILLINOIS
Telephone: SUPERIOR 5575

Study of the schematic diagram of the unit (Fig. 2A) shows an amplifier of conventional arrangement and values for a supply voltage of 250 volts.

If the 6SJ7 stage is converted to a grounded grid amplifier, as shown in Fig. 2B, the input impedance of the 6SJ7 is $(0.1 + 1.5) \times 10^6/2500$ or 640 ohms. Fig. 3 shows that the actual impedance, looking toward the mike, consists of the input impedance of the tube with open cathode circuit in shunt with the cathode bias resistor. The value of the combination is given by the following equation.

$$Z_i = \frac{Z \times R_k}{\sqrt{Z^2 + R_k^2}} = 500 \text{ ohms.}$$

When the results of this calculation indicated that the microphone and circuit input impedance were sufficiently matched, the necessary wiring changes were made. The only additional component required was a .5 µfd., 400 volt condenser in place of a cathode bypass condenser and the grid resistor in the amplifier.

Incidentally, since the first stage of the amplifier had a separate filament winding this was disconnected from ground and kept floating in order to keep a hum voltage from developing between cathode and ground. This was necessary inasmuch as this connection would have paralleled the input.

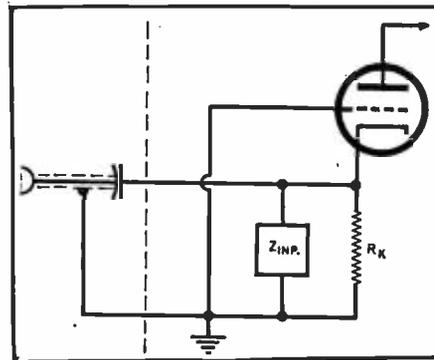


Fig. 3.

As a result of the perfect matching, the grounded grid circuit worked without noise, without any unwanted pick-up and with excellent frequency response and volume.

By choosing a suitable tube with a variable cathode resistor, a separate grounded grid input stage can be built (by using the equations and Fig. 2B) for microphones with an impedance of from 200 to 1000 ohms and added to existing amplifiers.

The simplicity and trouble-free operation of this circuit and the important saving in components should make this circuit popular with servicemen and experimenters.

—50—

DRESSING UP THE ANTENNA CONNECTION

ONE of the unsightly trappings of amateur radio is the usual antenna feeder line inside the house. Outdoors, the two-wire feeder may be as neat as a pin, but it takes a turn for the worse after it comes through the wall. Full of kinks, it either clutters up the floor or dangles from the ceiling. A lot of "72-ohm" lines are just as unlovely to behold as the open-line jobs. The women-folks object to this sort of thing, and rightly so.

The new coaxial cable and fittings which have become available to the public since the war ended offer a means of correcting this evil, and the accompanying photograph shows one way they can be used to do the job.

In this case, the antenna coupler is located down cellar just inside the sill through which the 2-wire feeder enters. The coupler is not re-tuned often, so can be remotely located in this manner. The coupler is link coupled to a section of Amphenol type "RC" concentric (coaxial) cable which, in turn, is run up through the wall and connected to a female coaxial connector (Amphenol 83-1R; Signal Corps No. SO-239) mounted in the center of a plain brass outlet plate on the baseboard as shown in the photograph. A 5/8-inch round hole in the brass plate will clear the rear protrusion of the coaxial connector, and a 1 1/4-inch round hole is all that is needed in the baseboard. The cable may be pushed up through the floor or fished through with a length of wire or string.

Another section of "RC" type cable, seen on the floor in the photograph, is used to connect the baseboard outlet to the transmitter. Each end of this second cable terminates in a male coaxial connector (Amphenol 83-1SP; Sig-


nal Corps No. PL-259), one of which may be seen on the end of the cable in the photograph.

The final amplifier plate tank also is link coupled to a female connector on its chassis. When the transmitter is to be put on the air, the cable plugs are inserted into floor and chassis connectors, the cable thus being run between the transmitter and "outlet." When transmissions are completed, the cable may be disconnected and stored out of sight. Even when this cable is connected between the transmitter and base plug and lies along the floor, its sleek, black coat makes a trim appearance. For this reason, some operators may prefer to leave it connected.

If a doublet antenna is used for transmitting, no antenna coupler is needed. The "cellar" length of coaxial cable then may be run through the wall of the house directly to the center of the antenna and the system is greatly simplified.

—50—

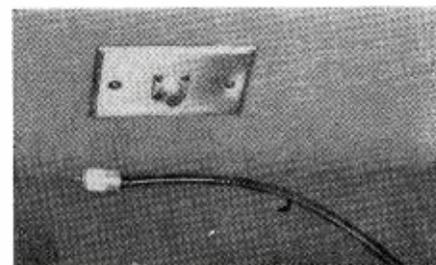The coaxial antenna outlet on the baseboard has the same neat appearance as the familiar power outlet. The coaxial cable for connecting to the transmitter is shown on the floor beneath the outlet.




RADIO NEWS

The BEST VALUES from ARROW!

ARMY AIRCRAFT RECEIVER

Model
BC-946-B

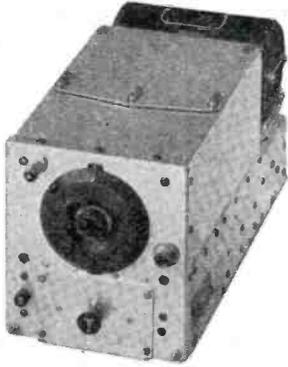Broadcast band from 520 to 1500 kc. Tube complement: 3-12SK7, 1-12SR7, 1-12A6, 1-12K8. Designed for dynamotor operation, but is easily converted to 110 or 32 volt operation. Has two I.F. stages and three gang condenser. Comes packed in sealed carton complete with tubes and instruction manual, but less dynamotor. **\$12.95**
DYNAMOTOR DM 32A. Each. **\$1.95**



RADIO RECEIVERS

BC-454-A; 3-6 mc. **\$6.95**
BC-453-A; 190-550 kc. **8.95**
BC-455-A; 6-9.1 mc. **6.95**

RADIO TRANSMITTERS

BC-457-A; 4-5.3 mc. **\$7.95**
BC-458-A; 5.3-7 mc. **7.95**

MODULATOR UNIT

BC-456-A **\$6.95**

REMOTE CONTROL BOX

BC-450-A **\$2.95**

ARMY SURPLUS, principal components of radio set SCR-274-N; includes 2 transmitters, 3 receivers, 1 modulator, 4 dynamotors, control box, etc.—original cost over \$600.00—NOW \$34.95 complete.



HICKOK 2 1/2" 0-150 Volt AC VOLTMETER
Each **\$2.49**

COAXIAL CABLE

26 ft. of Coaxial Cable RGU8. 52 ohm. with 2 amphenol plugs, one at each end. **89¢**

HEADPHONES

Signal Corps, 8000 ohms and 200 ohms, each. **\$2.49**
2000 ohms, Trimm, each. **1.79**
E ARPHONES, less headband, HS18 high impedance. **79¢**

POWER TRANSFORMER—NAVY TYPE

159 ma; 6.3 V at 6.5 amps; 5 V at 3 amps. 110 volt. each **\$3.29**

SURPRISE PACKAGE

For the experimenter, radio serviceman, handy man, repairman, "ham," hundreds of valuable miscellaneous parts, 10 pounds. **\$1.59**

SPEAKERS

5" PM speaker **\$1.19**
4x6 dynamic, 450 ohms. **1.65**
5x7 PM—hvy. slug. **2.15**
6" PM Alnico. **1.95**

RADIO TRANSMITTER and RECEIVER APS-13

Light weight air-borne radar system, radio transmitter and receiver APS-13; tube complement: 5-6J6; 9-6AG5; 1-VR105; 2-D21; unit is brand new, complete with tubes, the tubes alone are worth more than this LOW PRICE OF ONLY....

\$15⁰⁰

GLIDE PATH RECEIVER R-89/ARN-5

Glide Path Receiver used in the Instrument Landing System covering the frequency range 332 to 335 mc; complete with the following tubes: 7-6AJ5; 1-12SR7; 2-12SN7; 1-28D7; and including three crystals 6497KC; 6522KC; 6547KC... units are in A-1 condition for ONLY.....

\$6⁹⁵

SCR-522 TRANSMITTER and RECEIVER

The standard very-high frequency airborne receiver-transmitter. 100 to 156 megacycles. 4 crystal-controlled channels selected from remote control box. In excellent condition—ONLY.....

\$19⁹⁵

RADAR OSCILLOSCOPE

Complete with 27 tubes including 5" Cathode Ray tube—used. Each **\$24.95**

RADAR OSCILLOSCOPE

Complete with 29 tubes including 3" Cathode Ray tube—used. Each **\$24.95**

MARKER BEACON RECEIVER — AIRCRAFT



Complete with 2 tubes and sensitive relay to control external circuits from received signals. The receiver to control models, open doors from a distance, etc. **\$4.95**
Special.....

IFF RADIO RECEIVERS

Signal Corps, complete with 13 tubes. Model BC-966-A—only **\$9.99**

SETCHELL CARLSON RADIO RECEIVER BC-1206-C

Designed to receive A-N beam signals. 24-28 vdc 21.6 watts. Tube complement: 14H7 or 14A7, RF amplifier; 14H7 or 14J7, mixer; 14A7 or 14H7, IF amplifier; 14R7, detector and 1st audio amplifier; 28D7, output amplifier. 195 to 420 kc. 4" high x 4" wide x 6 3/4" long.—wt. 3 lbs., 14 oz. **\$4.95**
Used A-1 condition. **\$7.95**
BRAND NEW in original carton.....

Complete 4 tube INTERPHONE AMPLIFIER \$7.95

Yours for only.....
Comes in an aluminum cabinet 9 3/4 x 4 3/4 x 5 1/2 inches with two 12J5GT and two 12A6 tubes; also Electric Dynamotor 28DC Volt input and 250 V DC output at 60 MA.

HEAVY DUTY LINE FILTERS


Solar line filter—20 amps., 115 V. A.C., 600 V. D.C. Hermetically sealed, ideal for eliminating RF feedback in line or line noise pickup. **\$1.75**
Each.....

LS-3 SPEAKERS

Signal Corps, in steel case, weatherproof, self-contained, output transformer. **\$6.95**
VERY SPECIAL.....

Wholesalers, dealers, institutions and other quantity purchasers, write, wire, phone for quantity prices. All shipments F.O.B. Chicago. 20% deposit required on all orders.

DEPT. C

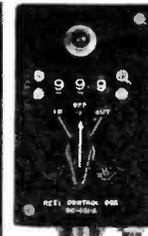

VEEDER-ROOT METER AND CASE

Counts number of feet of trailing wire antennae; number turns when winding on coil; applicable for many uses; beautiful bakelite case, jeweled dialite, pilot light enclosed, 3 position switch, counts up to 1000. **95¢**
Each.....

BATTERY FOR "GE" PORTABLES

2 volt Willard type 27/2 the exact replacement in Pre-War Model LB 530 "GE" Portable Radios. Plastic case, size 3 3/4 x 3 1/2 x 5 1/2" high. Shipped dry. Uses standard battery electrolyte. List value \$8.75. **\$2.89**
BRAND NEW! Your Cost.....

SWITCH

Multiple circuit telephone type key switch; available in momentary or locked position. Double pole, double throw. Each **89¢**

PLUGS

PL55 plugs.....each 20¢
PL68 plugs.....each 20¢

JACKS

JK 26.....each 20¢

CARBON MIKE

T-17-B Carbon Mike.....each \$1.49

EBY BINDING POST

No. 449.....100 for \$4.90

EXTENSION CORDS

Navy Type CW49561 Mike Extension Cords, complete with switch and PL68 Plug. Each **29¢**

CONDENSERS

50-30. 150 volt electrolytic tubular.....\$0.39
100 assorted, tubular, all 600 volt. .01, .02, .05, 1. 6.95
100 assorted mica.....1.95

RESISTORS

100 assorted 1/2 and 1 watt.....\$1.95
100 assorted 5 and 10 watt.....5.95

VOLUME CONTROLS

10 assorted volume controls, less switch.....\$1.75

IF TRANSFORMER

456 kc. matched sets.....79¢

SWITCH

SPST push-to-make switch.....\$0.19
10 for.....1.75
4-Prong Universal Vibrator.....\$1.49

ARROW SALES, INC.

59 WEST HUBBARD STREET • CHICAGO 10, ILLINOIS

Telephone: SUPERIOR 5575

GET THIS FREE CATALOG NOW



ALL THE BEST
BUYS IN RADIO,
HAM EQUIPMENT
AND P. A.
SYSTEMS.

SEND FOR YOUR COPY

of this new free book designed to save you money. Select the new Lafayette radio or famous-make ham equipment you want—at thrifty, low Lafayette prices. Do as thousands today are doing—make the big FREE Lafayette Catalog your buying guide. You save valuable time when you "shop" by mail. And you save real money on everything you buy. Every item in the great Lafayette Catalog is value-priced! Don't be without this book another day. It's FREE—just mail the coupon for your own copy. See what you get!

YEAR'S BEST P.A. BUY
Lafayette 8-watt Indoor System
Lafayette's value-leader in the Here's Lafayette's value-leader in the low-power field. If you sell P.A.—this system will go like hotcakes. If you use P.A.—it's your chance to save a lot of money.
MODEL 7015—Complete unit includes: Model 708 8-watt amplifier, complete with tubes. Amplifier has separate mikes and phono inputs, output impedances of 8, 15 and 500 ohms. Ten-inch PM speaker. Fabrikoid wall baffle. Crystal mike and constant with 7 1/2-foot cable with end connector. Twenty-five-foot speaker cable. Operates on 110-120 V.A.C., 60 cycles, 65 W.
COMPLETE READY TO OPERATE
—Your Cost Only \$44.60

LAFAYETTE Radio
RADIO WIRE TELEVISION INC.
100 SIXTH AVENUE, NEW YORK 13, N. Y.

110 Federal St., Boston 10 ☆ 24 Central Ave., Newark 2, N. J.

LAFAYETTE RADIO, Dept. RE7
100 Sixth Avenue, New York 13, N. Y.
Please RUSH big free radio catalog.
Enclosed is Check Money Order for PA System
Name.....
Address.....
City..... Zone..... State.....

Parts Lists

(FOR CIRCUIT DIAGRAMS APPEARING ON PAGES 82 AND 83)

WESTINGHOUSE MODELS H-110, H-111, H-137, H-138

Part No.	Code and Description
V-3222	R ₁ —2 megohm tone control
V-3221	R ₂ , SW ₁ —2 megohm vol. control & sw.
RC10AE224M	R ₁ —220,000 ohm, 1/4 w. res.
RC10AE105M	L ₄ , R ₅ —1 megohm, 1/4 w. res.
RC41AE682K	R ₆ —6800 ohm, 2 w. res.
RC10AE223M	R ₇ , R ₈ —22,000 ohm, 1/4 w. res.
RC10AE474M	R ₉ , R ₁₀ —470,000 ohm, 1/4 w. res.
RC10AE681M	R ₁₁ —680 ohm, 1/4 w. res.
RC10AE104M	R ₁₂ —100,000 ohm, 1/4 w. res.
RC10AE473	R ₁₃ —47,000 ohm, 1/4 w. res.
RC10AE684M	R ₁₄ —68 megohm, 1/4 w. res.
RC10AE330K	R ₁₅ , R ₁₆ —33 ohm, 1/4 w. res.
RC41AE472M	R ₁₇ —4700 ohm, 2 w. res.
RC41AE153M	R ₁₈ —15,000 ohm, 2 w. res.
V-3282	R ₁₉ —120 ohm, 2 w. res.
RC10AE225M	R ₂₀ —2.2 megohm, 1/4 w. res.
RC10AE101M	R ₂₁ , R ₂₂ —100 ohm, 1/4 w. res.
RC41AE103M	R ₂₃ —10,000 ohm, 2 w. res.
RC10AE103M	R ₂₄ —10,000 ohm, 1/4 w. res.
RCM20A330M	C ₁ —33 μfd. mica cond.
RCP10W4103A	C ₂ , C ₃ , C ₄ —.01 μfd., 400 v. cond.
RCM20A151M	C ₅ , C ₆ —150 μfd. mica cond.
RCP10W4203	C ₇ —.02 μfd., 400 v. cond.
RCM20B470M	C ₈ —47 μfd. mica cond.
RCP10W4104A	C ₉ —.1 μfd., 400 v. cond.
V-3170	C ₁₀ —S.w. ant. trimmer
V-3216	C ₁₁ , C ₁₂ , C ₁₃ , C ₁₄ —40/40/20/5 μfd., 350/350/25/250 v. elec. cond.
V-3241	C ₁₅ , C ₁₆ —Dual line filter cond.
RCM20A680M	C ₁₇ —68 μfd. mica cond.
RCM30C282H	C ₁₈ —.0028 μfd. s.w. padder
V-3233	C ₁₉ , C ₂₀ —2-gang var. cond.
V-3217	C ₂₁ , C ₂₂ , C ₂₃ —3-gang trimmer
V-3236	C ₂₄ —20 μfd., 25 v. elec. cond.
RCP10W4503A	C ₂₅ —.05 μfd., 400 v. cond.
RCP10W4303A	C ₂₆ —.03 μfd., 400 v. cond.
RCP10W4503A	C ₂₇ —.05 μfd., 400 v. cond.
RCP10M6502A	C ₂₈ , C ₂₉ —.005 μfd., 600 v. cond.
V-3191	C ₃₀ —Broadcast ant. trimmer
RCP10W6202A	C ₃₁ —.002 μfd., 600 v. cond.
RCM30B222M	C ₃₂ —.0022 μfd. mica cond.
RCM20C181J	C ₃₃ —180 μfd. mica cond.
RCP10W6202M	C ₃₄ —.002 μfd., 600 v. cond.
V-3224	L ₁ , L ₂ —S.w. ant. coil
V-3238	L ₃ —Ant. loading coil
V-3243	L ₄ , L ₅ —Broadcast and s.w. osc. coil
V-3313	L ₆ —Osc. coil

BENDIX MODELS 636A, 636C, 636D

Part No.	Code and Description
RC1H16	R ₁ —220 ohms, 1/2 w. res.
RC1H40	R ₂ , R ₁₀ —22,000 ohm, 1/4 w. res.
RC1H68	R ₃ —3.3 megohm, 1/4 w. res.
RC1H20	R ₄ —470 ohm, 1/4 w. res.
RC1H58	R ₅ , R ₁₅ —470,000 ohm, 1/4 w. res.
RC1H54	R ₆ —47,000 ohm, 1/4 w. res.
RC1H70	R ₇ , R ₂₀ —220,000 ohm, 1/4 w. res.
RV4500	R ₈ —4.7 megohm, 1/4 w. res.
RC1H51	R ₉ , S ₁ —1 megohm pot. & sw.
RC1H38	R ₁₁ —100,000 ohm, 1/4 w. res.
RC1H34	R ₁₂ —15,000 ohm, 1/4 w. res.
RC1H33	R ₁₃ —6800 ohm, 1/4 w. res.
RW1B14	R ₁₄ —150 ohm, 1 w. wirewound res.
RW1A06	R ₁₆ —100 ohm, 1 w. wirewound res.
RC4G28	R ₁₇ —33 ohm, 1/2 w. res.
RC1H32	R ₁₈ —2200 ohm, 2 w. res.
CVOC00	R ₁₉ —4700 ohm, 1/4 w. res.
CP4T40	C _{11A} , C _{11B} , C _{11C} , C _{11D} , C _{11E} —Var. cond.
CP6T16	C ₃ , C ₉ , C ₁₃ , C ₁₅ , C ₁₈ , C ₂₂ —.05 μfd., 400 v. cond.
CM5A14	C ₁ —.004 μfd., 600 v. cond.
CC9A16	C ₅ , C ₇ —47 μfd., mica cond.
CP4T20	C ₆ —3.3 μfd. ceramic cond.
CM5A05	C ₁₁ , C ₁₂ —.006 μfd., 400 v. cond.
CP2T51	C ₁₅ —220 μfd. mica cond.
CP4T34	C ₁₆ —.1 μfd., 200 v. cond.
CP4T51	C ₁₇ —.02 μfd., 400 v. cond.
CE3A00	C ₂₀ —.1 μfd., 440 v. cond.
T10C01	C ₂₁ —20/40/60 μfd., 150/150/150 v. elec. cond.
T10D01	T ₁ —First i.f. trans.
TA0001	T ₂ —Second i.f. trans. T ₃ —Audio output trans.

ZENITH MODELS SRO80, SRO86

Part No.	Code and Description
63-579	R ₁ —220 ohm, 1/4 w. res.
63-589	R ₂ —10,000 ohm, 1/4 w. res.
63-976	R ₃ —15 megohm, 1/4 w. res.
63-600	R ₄ —2.2 megohm, 1/4 w. res.
63-1348	R ₅ —5 megohm vol. control
63-644	R ₆ —22,000 ohm, 1/4 w. res.
63-597	R ₇ —470,000 ohm, 1/4 w. res.

63-686	R ₈ —150 ohm, 1/2 w. wirewound res.
63-1219	R ₉ —22 ohm, 1/2 w. wirewound res.
63-1220	R ₁₀ —100 ohm, 1 w. wirewound res.
63-1221	R ₁₁ —680 ohm, 1 w. wirewound res.
63-602	R ₁₂ —4.7 megohm, 1/4 w. res.
22-1419 or 22-1356	C ₁ —2-gang var. cond.
22-829	C ₂ —Broadcast ant. trimmer (on C ₁)
22-1017	C ₃ —.05 μfd., 200 v. cond.
22-953	C ₄ —Broadcast osc. trimmer (on C ₁)
22-669	C ₅ —.05 μfd., 200 v. cond.
22-826	C ₆ —First i.f. trans. pri. trimmer (on T ₁)
22-854	C ₇ —First i.f. trans. sec. trimmer (on T ₁)
22-196	C ₈ —Second i.f. trans. pri. trimmer (on T ₂)
22-1379	C ₉ —Second i.f. trans. sec. trimmer (on T ₂)
22-1381 or 22-1552	C ₁₀ —.0002 μfd., 600 v. cond.
95-919	C ₁₁ —.01 μfd., 600 v. cond.
95-906	C ₁₂ —.01 μfd., 200 v. cond.
	C ₁₃ —.01 μfd., 600 v. cond.
	C ₁₄ —.0005 μfd., 600 v. cond.
	C ₁₅ —.01 μfd., 600 v. cond.
	C ₁₆ —.02 μfd., 400 v. cond.
	C ₁₇ , C ₁₈ , C ₁₉ —40/40/40 μfd., 150/150/150 v. elec. cond.
	T ₁ —First i.f. trans.
	T ₂ —Second i.f. trans.

WARD MODELS 64BR-1808A

Part No.	Code and Description
BEC-9B1-31	R ₁ , R ₄ —1 megohm, 1/2 w. res.
BEC-9B1-35	R ₂ —270 ohm, 1/2 w. res.
BEC-9B1-64	R ₃ —1500 ohm, 1/2 w. res.
BEC-9B1-46	R ₅ —47 ohm, 1/2 w. res.
BEC-9B1-79	R ₆ —27,000 ohm, 1/2 w. res.
BEC-9B1-1987	R ₇ , R ₈ —27,000 ohm, 1/2 w. res.
BE10662	R ₉ —12,500 ohm, 3 w. res.
BEC-9B1-23	R ₁₀ —47,000 ohm, 1/2 w. res.
BEC-9B1-59	R ₁₁ —560 ohm, 1/2 w. res.
BEC-9B1-33	R ₁₂ —2.2 megohm, 1/2 w. res.
BEA-10A-10810	R ₁₃ , S ₅ —500,000 ohm vol. control & sw.
BEC-9B1-37	R ₁₄ —10 megohm, 1/2 w. res.
BEC-9B1-22	R ₁₅ —33,000 ohm, 1/2 w. res.
BEC-9B1-2091	R ₁₆ —270,000 ohm, 1/2 w. res.
BEC-9B1-82	R ₁₇ —47,000 ohm, 1/2 w. res.
BEC-9B1-94	R ₁₈ —470,000 ohm, 1/2 w. res.
BEC-9B1-86	R ₁₉ —100,000 ohm, 1/2 w. res.
BEC-9B1-70	R ₂₀ —4700 ohm, 1/2 w. res.
BEC-9B1-29	R ₂₁ —470,000 ohm, 1/2 w. res.
BEC-9B1-55	R ₂₂ —270 ohm, 1 w. res.
BEB-8F-10767	C ₁ —.002 μfd., 500 v. mica cond.
BE-124143	C ₂ , C ₃ —Dual 67-123 μfd./95-175 μfd. ant. trimmers
BEB-8F3-121	C ₄ , C ₁₀ —470 μfd., 500 v. cond.
BEC-8D-10771	C ₅ —.1 μfd., 200 v. cond.
BEC-8D-10760	C ₆ , C ₁₁ —.1 μfd., 400 v. cond.
BEB-8F5-101	C ₇ —10 μfd., 500 v. silver mica cond.
BEA-8G-7205	C ₈ —120-220 μfd. r.f. trimmer
BEA-8G-7206	C ₉ —60-110 μfd. r.f. trimmer
BEB-8F3-109	C ₁₂ —47 μfd., 500 v. mica cond.
BEB-8F-10763	C ₁₃ —200 μfd., 500 v. silver mica cond.
BE-124145	C ₁₄ —7-35 μfd. osc. trimmer
BE-124144	C ₁₅ —15-27 μfd. osc. trimmer
BEC-8F3-12	C ₁₆ —470 μfd. mica cond.
BEC-8F3-10	C ₁₇ , C ₁₈ , C ₂₂ —220 μfd. mica cond.
BEC-8D-10770	C ₁₉ , C ₂₀ —.05 μfd., 200 v. cond.
BEC-8D-10785	C ₂₁ —.006 μfd., 600 v. cond.
BEC-8D-10761	C ₂₃ —.01 μfd., 400 v. cond.
BEC-8D-10774	C ₂₄ , C ₂₅ —.02 μfd., 400 v. cond.
BEC-8D-10778	C ₂₆ —.002 μfd., 600 v. cond.
BEA-8C-10272	C _{27A} , C _{27B} , C _{27C} —10/10/20 μfd., 450/450/450 v. elec. cond.
BEC-8J-11388	C ₂₈ —.05 μfd., 600 v. cond.
BE-111195	T ₁ —Broadcast ant. coil
BE-111191	T ₂ —12 mc. ant. coil
BE-111192	T ₃ —15 mc. ant. coil
BE-111189	T ₄ —6 mc. ant. coil
BE-111190	T ₅ —9 mc. ant. coil
BE-10959	T ₆ —9 mc. r.f. coil
BE-10962	T ₇ —Broadcast r.f. coil
BE-10960	T ₈ —12 mc. r.f. coil
BE-10961	T ₉ —15 mc. r.f. coil
BE-10958	T ₁₀ —6 mc. r.f. coil
BE-110157	T ₁₁ —9 mc. osc. coil
BE-110159	T ₁₂ —15 mc. osc. coil
BE-110158	T ₁₃ —12 mc. osc. coil
BE-110156	T ₁₄ —6 mc. osc. coil
BE-110161	T ₁₅ —Broadcast osc. coil




Amazing Bargain Offer in Diagram Manuals

ALL NEW 1947 CIRCUITS—SERVICE DATA YOU NEED TO GET AHEAD

Be prepared to repair quickly all new 1947 sets. In this big single volume you have clearly-printed, large schematics, needed alignment data, replacement parts lists, voltage values, and information on stage gain, location of trimmers, and dial stringing, for almost all sets released between June 1, 1946, and March 1, 1947. A worthy companion to the six previous volumes used by over 100,000 shrewd radio servicemen. There is no

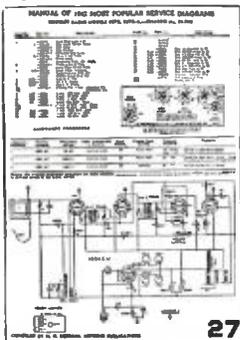need to spend large sums for bulky, space-wasting manuals or to buy additional drawings every few weeks—get this low-priced new SUPREME PUBLICATIONS manual and you have service information on all popular 1947 sets. Covers 327 models of 52 different manufacturers. Large size: 8½x11 in., 192 pages + index. Manual style binding. Price postpaid, **\$2.00** only



Actual page size is 8½x11 inches

Most Popular Models Made by:

R. C. A., Zenith, Philco, Sears, Fada, Emerson, Belmont, Detrola Radio, Majestic, United Motors, G.E., Westinghouse, Arvin, Stewart-Warner, Admiral, Delco, Stromberg - Carlson, Western Auto, Wards, Sperton, Motorola, Gamble, Crosley, and many others.

Guarantee

All manuals sold on 10-day trial basis. You must be entirely satisfied or your money will be refunded.

Supreme Publications
(In business 14 years)

Speed up and simplify all radio set repairs with SUPREME PUBLICATIONS Manuals. Service radios faster, better, easier, save money and time, use these most-often-needed diagram manuals to get ahead, earn more per hour. At unbelievable low cost (only \$2 for most volumes) you are assured of having in your shop and on the job, needed diagrams and other essential repair data on 4 out of 5 sets you will ever service. Every popular radio of every make from old-timers to new 1947 sets, is included. Clearly printed circuits, parts lists, alignment data, and helpful service hints are the facts you need to improve your servicing ability. Save hours each day, every day, let these seven volumes furnish diagrams for 80% of all sets. See pictures of these attractive manuals above. Each volume has between 192 and 240 pages, large size 8½ x 11 inches. Manual style binding. Send coupon today. Complete satisfaction guaranteed.



Compiled by M. N. Beitman, radio engineer, teacher, author, and serviceman.

Post-War Automatic Record Changers

Service expertly all new (1945-1947) record changers. Follow simplified factory instructions to make needed adjustments and repairs. Hundreds of photographs and exploded views; thousands of test hints; service instructions for all popular makes. Large size: 8½ x 11", 144 fact-filled pages. At your jobber or postpaid, only **\$1.50**

Pre-War Record Players, Changers, & Recorders.

Just what you need to repair quickly thousands of pre-War automatic record changers, manual units, pick-ups, wireless oscillators, recorders, and combinations. Hundreds of mechanical and electrical diagrams. Instructions for adjustments and repairs. Most popular units of all makes. 128 large pages. 8½ x 11 inches. Price, only **\$1.50**

Supreme Publications

PUBLISHERS OF RADIO BOOKS, MANUALS, AND DIAGRAMS

See Your Radio Jobber or Send Coupon →

May, 1947

NO RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 9 S. Kedzie Ave., Chicago 12, ILL.

Ship the following manuals: (Satisfaction guaranteed or money back)

- | | | |
|---|-------------------------------------|--|
| <input type="checkbox"/> 1947 | } PRICED AT ONLY \$2.00 EACH | <input type="checkbox"/> Post-War Record Changers... @ \$1.50 |
| <input type="checkbox"/> 1946 | | <input type="checkbox"/> Pre-War Record Players... @ 1.50 |
| <input type="checkbox"/> 1942 | | |
| <input type="checkbox"/> 1941 | | <input type="checkbox"/> I am enclosing \$..... send postpaid. |
| <input type="checkbox"/> 1940 | | <input type="checkbox"/> Send C.O.D. I am enclosing \$..... deposit. |
| <input type="checkbox"/> 1939 | | |
| <input type="checkbox"/> 1926-1938 @ \$2.50 | | |

Name:

Address:

3 WAYS TO BE AHEAD

in Buying Test Equipment



Model 599-A Tube and Set Tester

SPECIFICATIONS
 DC Volts — 5 ranges 0/6/15/150/600/1500 volts, 1000 ohms per volt.
 AC Volts — 3 ranges 0/15/150/600 volts.
 DC Current — 3 ranges 0/6/60/600 milliams.
 Output Volts — 0/15/150/600 volts.
 Ohmmeter — 4 ranges 0/200/20,000 ohms and 0/2/20 megohms.

Condenser Checker—Ohmmeter provides fast method of checking leakage of both paper and electrolytic condensers.

Battery Tester — Tests most commonly used dry portable batteries at 1.5/4.5/6.0/45/90 volts, English reading "Replace-Good" scale.



WRITE FOR NEW CATALOG

SUPREME INSTRUMENTS CORP., Greenwood, Miss., U.S.A.

Export Department: THE AMERICAN STEEL EXPORT CO. Inc., 1347 Madison Ave., New York 17, N. Y., U.S.A.

- 1 BUY ACCURACY
- 2 BUY DEPENDABILITY
- 3 BUY SUPREME-ACY

Ask your nearest SUPREME jobber for a demonstration of Model 599-A Tube and Set Tester (above), Model 561-AF & RF Oscillator, Model 546-A Oscilloscope, Model 592 Speed Tester. Ask to see the complete line of SUPREME equipment.

SUPREME

Tube Testing — Circuit incorporates proven and modernized emission circuit. Checks for short, leakage, and noise tests between elements.
 Power Supply — 100-133 volts—50/60 cycles. Special voltages and frequencies on request.

BEB-203-1813-3 T₁₀—Output i.f. trans.
 BEB-203-1813-2 T₁₇—Input i.f. trans.
 BEB-12C-10234-1 T₁₈—Output trans.
 BE104202-D T₂₀—Power trans.
 BED-212-11429 T₂₁—Loop ant. assembly

CROSLLEY MODELS 56TZ, 57TQ

Part No.	Code and Description
AC-138333	3—Antenna loop assembly
AW-135730	4—Osc. coil assembly
AW-135729	5—First i.f. trans.
AW-135731	6—Second i.f. trans.
B-135570	7A, 7B, 7C—Two section var. cond. & trimmer
39001-76	9, 15—0.03 μ fd., 600 v. cond.
39001-17	10, 11, 13—.05 μ fd., 600 v. cond.
39001-19	14—250 μ fd., 600 v. cond.
39001-80	16, 17, 44—.02 μ fd., 600 v. cond.
B-136770	18A, 18B—50/30 μ fd., 150/150 v. elec. cond.
39373-16	19, 30—150 ohm, 1/2 w. res.
39373-60	20, 22—22,000 ohm, 1/2 w. res.
39373-109	21—15 megohm, 1/2 w. res.
39373-80	23—220,000 ohm, 1/2 w. res.
39373-100	24—3.3 megohm, 1/2 w. res.
39373-144	25—1200 ohm, 1 w. res.
Part of #6	26—47,000 ohm, 1/2 w. res.
39373-35	27—4.7 megohm, 1/2 w. res.
39373-87	28, 29—470,000 ohm, 1/2 w. res.
B-135692	31A, 31B—1 megohm vol. control & sw.
W-137367	38—47 ohm, 1 w. res.

BELMONT MODEL 5D110

Part No.	Code and Description
C-9B1-78	R ₁ —22,000 ohm, 1/2 w. res.
C-9B1-60	R ₂ —680 ohm, 1/2 w. res.
C-9B1-50	R ₃ —100 ohm, 1/2 w. res.
C-9B1-82	R ₄ —47,000 ohm, 1/2 w. res.
C-9B1-34	R ₅ —3.3 megohm, 1/2 w. res.
C-9B1-302	R ₆ —15 megohm, 1/2 w. res.
A-10A-10720	R ₇ , S ₁ —500,000 ohm vol. control & sw.
C-9B1-90	R ₈ —220,000 ohm, 1/2 w. res.
C-9B1-95	R ₉ —560,000 ohm, 1/2 w. res.
C-9B1-52	R ₁₀ —150 ohm, 1/2 w. res.
C-9B1-43	R ₁₂ —27 ohm, 1/2 w. res.
C-9B2-54	R ₁₃ —220 ohm, 1 w. res.
C-9B2-63	R ₁₄ —1200 ohm, 1 w. res.
C-3B2-44	R ₁₅ —33 ohm, 1 w. res.
C-8F3-119	C ₁ —330 μ fd., 500 v. mica cond.
C-8F3-113	C ₂ , C ₃ —100 μ fd., 500 v. mica cond.
C-8F3-247	C ₄ —820 μ fd., 500 v. mica cond.
C-8D-10770	C ₅ —.05 μ fd., 200 v. cond.
C-8D-10942	C ₆ —.2 μ fd., 400 v. cond.
C-8D-10789	C ₈ —.002 μ fd., 600 v. cond.
C-8F3-118	C ₉ —270 μ fd., 500 v. mica cond.
C-8D-10785	C ₁₀ —.006 μ fd., 600 v. cond.
C-8D-10774	C ₁₁ —.02 μ fd., 400 v. cond.
C-8D-10760	C ₁₂ —.1 μ fd., 400 v. cond.
A-8C-10077	C _{13A} , C _{13B} , C _{13C} —40/20/20 μ fd., 150/150/150 v. elec. cond.
C-8D-11251	C ₁₄ —.09 μ fd., 400 v. cond.
A-8E-10723	C _{15A} , C _{15B} —Dual ant. and osc. trimmer cond.
C-211-10171	T ₁ , T ₂ —Tuner unit
B-13A10728	T ₃ —Input i.f. trans.
B-13B-10729	T ₄ —Output i.f. trans.
B-12C-10074-1	T ₅ —Output speaker trans.


-50-

WIDE BAND • HIGH GAIN SUPERRECEPTOR


(CODE: FMTV 44216)

INTERSTATE

ANTENNA for FM and Television

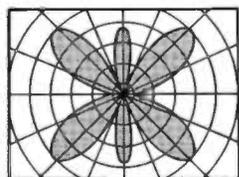

Theoretical field pattern at 180 mc

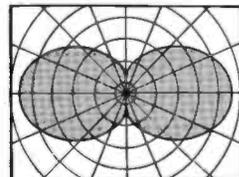

Theoretical field pattern at 80 mc

- ★ Blanket coverage 44 to 216 megacycles (13 television channels)
- ★ Complete with fittings and transmission line
- ★ Rugged, all-weather construction, easy to install
- ★ Feather weight, polished aluminum construction
- ★ Pretuned at factory for high gain at all frequencies
- ★ Relatively free from parasitic noise pick-up
- ★ Available with reflectors

Here's an FM and Television antenna designed from the installer's point of view. Easy to install, built for years of trouble-free service, it's factory pretuned for high gain at all frequencies from 44 to 216 Megacycles — requires no adjustment in the field. Improves the performance of any set. Reflectors available for elimination of "ghosts" and for special directional effects. The FMTV 44216 is available through jobber channels.




INTERSTATE MFG. COMPANY

GENERAL OFFICES: 138 SUSSEX AVE., NEWARK 4, N. J. • LABORATORIES: BOONTON, N. J.

DRESS DIAL LIGHT WIRES

DIAL light wires often contact rotating tuning mechanism and cause scratching noises as well as damage to the insulation on the wires.

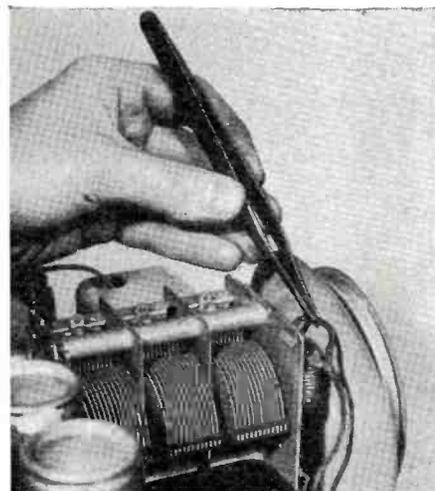Such wires should be dressed as shown to avoid rubbing contacts. H.L.



"Communications"

HOUSE OF
MICROWAVES



MAGNETRONS

Type 2132 (1AN) just released. The 2132 is designed for 10 cm. operation. Rated at 300 kw. peak pulse power. Complete information supplied. Brand new, packed in individual protective cartons. The 2132 is listed at \$200. (Our price \$250.00.)
3131's. One cm. magnetron listed at \$95.
OUR PRICE \$200.00.

- 720 magnetron value \$200. Special.....\$200.00
- 2138 (3245-3263 MCS) Complete with magnet 37.50
- 2142 (3 CM) complete with magnet..... 37.50
- 2126 (10 CM)..... 25.00
- Magnets for Magnetrons..... 12.00

KLYSTRONS!

- 21K25/723 AB (3CM) New; with data listed at \$38.00.....\$ 7.75
- 707 B. (Limited Quantity)..... 15.00
- External cavity for 707B..... 3.50
- 715 B Pulse power tube..... 9.50
- 30 mc oscillator-amplifier with 2 6AC7's. Uses 723ah. Waveguide input, xtal detector. With 6AC7's..... 10.00
- With 6AC7's and 723ah and INCI..... 16.50
- Thermistor Beads (D-176396), for use with UHF and Micro-Wave Equipment. (List \$3.00). In separate sealed containers..... .95

WAVE GUIDE PLUMBING 3 CENTIMETERS

- T Section with Choke Terminations.....\$5.00
- 2 1/2 foot silver plated with 180° bend (2" radius)..... 4.50
- 150° bend with 90° twist 3 1/2" radius with pressurizing nipple and coax coupler..... 3.95
- 2 1/2 foot 3 cm wave guides choke to cover fitting..... 4.50
- 5 foot 3 cm wave guide section per foot..... 1.95
- Slotted dipole antenna 3 cm..... 4.00
- 3 CM TR Box (Cavity) silvered for 712 ATR Tube..... 2.50
- Choke Flanges for 3 CM 1"x1/2" opening 2 for. 1.15
- Silver Plated Directional Couplers with a 20 DB drop with:.....
- A. 90° bend wave guide 15" long.....\$4.00
- B. 15° bend in wave guide 15"..... 4.40
- C. 30° bend in wave guide 10" long..... 3.95
- D. 90° bend in wave guide 15" long also 90° bend in coupler..... 5.00

1.25 CENTIMETERS

- Flexible Section 1" long Choke to Choke.....\$3.00
- Mitted elbow and "S" section cover to choke.. 3.50
- T-section choke to cover..... 4.50
- Section 1" long cover to cover..... 2.00

10 CENTIMETERS

- Wave Guide, per ft.....\$2.00
- 16 foot lengths
- Coax Coupler 9/16" to 3/4" coax..... 2.50
- Coax Rotary Joint with mounting plate..... 8.00
- Dummy Antenna Wave Guide Section. Sand Load with Cooling Fins..... 35.00

SO RADAR

- Transmitter unit (10 CM) includes 2126 magnetron, TR-ATR section, pulse transformer, McNally Klystron, 1P, strip, all tubes, blower motor. Used, but in good condition.....\$150.00
- SO Radar antenna assembly (10 CM) dipole, parabolic reflector, 24 in. diameter. Drive and selsyn motors, wave guide couplings, rotary joint. Masking dome 30x30x40". Used and in good condition.....\$ 45.00
- New..... 90.00
- SO Radar 10 cm echo boxes..... 15.00
- SO Radar indicator unit, with CR tube, focusing and deflection coils, azimuth scale, all controls, tubes and components used and good condition.....\$100.00
- SO Radar accessory range unit, with AC voltmeter on front of cabinet..... 35.00
- SO Motor-Generator..... 85.00
- In fact we have the complete SO Radar New and Used. Ask us for quotations.
- SO 13 Radar Complete, used, with new Ant.....\$500.00
- Signal Generator. 27000 to 3000 MC Regulated power supply. 115V/60 c. Contains output meter. Made by Western Electric. Value \$400. Our price.....\$ 75.00

ARC-5 SUPERHET RECEIVERS NEW—\$12.00

Tubes (included) 3-12SK7, 1-12K8; 1-12SH7; 1-12AG. Ranges (Specify freq. desired) 1500-3000 Kc; 3-6 Mc; 0-9.1 Mc. Power; 24-28 VDC. For only. new. \$12.00
Extra—To Go with ARC-5 Dynamotor.....\$2.25
Control Box..... 1.00
Drive Cable..... 2.50
Mounts..... 1.00
New ARC-5 Transmitters: 25 watts CW; 15 watts phone. Tubes (included): 2-1625; 1-1629; 1-1626; 1 crystal. Ranges (Specify frequency desired): 5-8 Mc; 8-1.3 Mc; 1.3-2.1 Mc; 4-5.3 Mc; 5.3-7 Mc. Power: 24-28 VDC.....\$12.00
Modulator unit: (with tubes) 1-1625: 1-vr150; 1-1215..... \$14.00
All These Units Are Brand New.



Sonar Sound Detection Unit!

Ideal for detecting underwater sounds, such as fish swimming in schools, within a 15 mile area. Using a Rochelle salt crystal which is about 1000 times more sensitive than quartz, as the active unit the sound is transmitted up a 60 ft. length of cable. It is completely enclosed in a solid rubber sheath whose physical size is: 1 1/2" L x 2 1/2" dia. This sound detector was originally used in harbor defense. Coupled to an audio amplifier, this can be found to have many valuable applications.
Ask for SD-1.....



\$6.95

DP U. S. NAVY DIRECTION FINDER




The DP-12 is a Navy direction finder, made by RCA with a frequency range of 100-1500 Kc. The input voltage is house current (115v/60c). The tube line up is 3-6V6; 1-6D6; 2-7G; 1-6AF6; 1-1523. This unit is equipped with loop output function box, flexible transmission line, input transformer, deck bearings, cable drums, operating pedestal, hand wheel, azimuth scale, loop antenna assembly, and loop pedestal. A Buy for Sea Going Vessels. Value \$2500.
New..... \$195

HI-VOLT TRANSFORMERS

2 KVA Transformer and choke—115v 50 to 70 Cycle input, single phase. Output 17,000 V. @ 144 Ma. choke 4,000 H @ 0 current, DCR 4,500 ohms. Dimensions 20"x29"W.x13"D. Amertran..... \$94.50
3200 volts, AC 150 M. A. 115 volt. primary, 60 cycles. Designed for half wave operation with 150 M.A. output each. Two transformers hooked up with secondaries in series and primaries in parallel will give 3,000 volts. output at 300 M.A. from a full wave rectifier. These are conservative, continuous commercial ratings.....\$7.25

RA-58-A HI-VOLTAGE POWER SUPPLY

Ideal for breakdown insulation testing, or as a source of power for a pulse transmitter. This unit supplies continuously variable voltages between 500 and 15,000 volts DC at 35 ma. A voltage Doubler circuit using two 705a rectifiers and two 1 mf condensers is employed. RMS ripple voltage at maximum power is 6%. THIS UNIT OPERATES FROM 115 v/60c. Variable voltage is obtained by means of a Variac in the primary circuit of the high voltage transformer. Size is 21"x17 1/2"x29" deep. Net weight 314 lbs. \$116.00

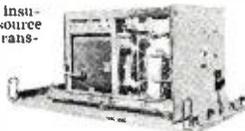

We have unbelievable bargains in 400 cycle transformers. Ideal for pulse work. At this price you can figure out your uses for them. Most sizes at 50 cents each. Send us your voltage requirements.

ALL MERCHANDISE GUARANTEED. MAIL ORDERS PROMPTLY FILLED. ALL PRICES F.O.B. NEW YORK CITY. SEND MONEY ORDER OR CHECK. SHIPPING CHARGES SENT C.O.D.

SEND FOR FLYER

COMMUNICATIONS EQUIPMENT CO.

131-A Liberty St., WH 4-7658, New York City 7, N. Y.

VALUES IN ALL FREQUENCIES

SPECIALS FOR THIS MONTH

- Visors for 5 inch scopes.....\$0.75
- Tube shields for 2A11..... .98
- Broadcast band push-button tuning units inductive types..... 1.49
- Mushroom rubber earphone cushions for light-weight set—pair for..... .89
- Oscilloscope chassis, completely punched for use with a 2 inch tube. Octal sockets included 15"x11"x3"..... 1.50
- Phones, leather covered head bands 8,000 ohm impedance, 6 ft. cord & plug, detachable cushions—new..... 1.95
- Used, in good condition..... 1.00
- 140 mmf split stator variable midge condenser. 1.49
- Silver button mica condensers. 175-135 mmf. ea. .05
- Lots of 100..... 4.50
- Silver button mica condensers: 500 mmf. ea..... .10
- Lots of 100..... 9.50
- Whip antenna—2 sections fasten together—Ideal for 10 meters..... 1.25
- B-29 computer amplifier contains 8-6SN7's 5 neons, 8 relays completely wired. New..... 9.95
- 115 volt 60 cycle transformers for plate and filament 570 V. CT. 60 MA-5 and 6.3 V..... 1.89
- 6 Hy (choke 60 MA. to match above..... .05
- I-F Crystal filter for BC-312. BC-342 Resonant at 470 kc. Crystal included..... 6.95

OIL FILLED CONDENSERS

- | | |
|--------------------------|---|
| 1 mf 300 vdc.....\$3.25 | 1 mf 1000 vdc.....\$0.85 |
| 2 mf 300 vdc..... .30 | 2 mf 1000 vdc..... .98 |
| 4 mf 300 vdc..... .35 | 1 mf 1500 vdc..... 1.05 |
| 4 mf 400 vdc..... .55 | 4 mf 1500 vdc..... .30 |
| 5-5 mf 400 vdc..... 1.15 | 2 mf 600 ac/1000..... .95 |
| 2 mf 550 vdc..... .30 | 4 mf 1500 vdc..... 1.39 |
| .25 mf 600 vdc..... .25 | 1 mf 2000 vdc..... 1.20 |
| .85 mf 600 vdc..... .30 | 1-1 Mf. 7000 vdc..... 2.00 |
| 1 mf 600 vdc..... .35 | 10-10-10 mfd synchro cap. 90v/60c..... 2.50 |
| 2 mf 600 vdc..... .40 | |

HI-VOLT MICA CONDENSERS

- F31, .0003 mfd 8000v list \$29.00.....\$3.75
- Solar type SX .0015 mf 3000v list \$9.95..... .75
- Sancamo G-3 .006 mf 10ky list \$87.50..... 17.50
- .0008 mf 5000vdc C-D 599-G11..... .80
- .0002 mf 5000vdc Aerovox..... .75
- .0004 mf 3000vdc Faradon..... .70

TUBE SPECIALS

- | Tube Type | Approx. Cost | Your Cost | Tube Type | Approx. Cost | Your Cost |
|-----------|--------------|-----------|-----------|--------------|-----------|
| 3BP1 | \$15.00 | \$3.95 | 8Y | \$2.80 | \$1.35 |
| 3BP7 | 27.00 | 3.50 | 872A | 7.50 | 2.45 |
| 5BP1 | 20.00 | 4.95 | 241B-WE | 85.00 | 40.00 |
| 5BP4 | 27.00 | 7.95 | 861 | 155.00 | 50.00 |
| 5CP1 | 45.00 | 4.95 | 3B2A | 12.00 | 3.95 |
| 705A | 92.50 | 6.75 | 3C45 | 36.00 | 5.95 |
- Sockets for 5CP1, 3BP1, & 3BP1 and similar types of tubes.....\$9.95

CHOKES

- 12 hy-12 hy @ 150 ma., 15 amp. rating. Price \$3.35
- 12 hy @ 165 ma 200 ohms DCR made by Thorndarson. Price..... 2.00
- 50 hy @ 100 ma 850 ohms DCR made by Jefferson. Price..... 2.00

AUDIO TRANSFORMERS, MODULATORS, ETC.

- Modulation xfmr: typical for 211's cl. A50W.....\$1.35
- Modulation xfmr: 807 to pr. 807's..... 1.00
- Modulation xfmr: pr. 811's to 814..... 5.00
- Audio output transformer Split pri. 1500 OHMS each side. Secondary impedance 85 ohms center-tapped—6:1 ratio. 100-watts output..... 5.50
- Line to Voice transformer Pri. 600 ohms. Sec. 6 ohms. 1200 Test volt..... 1.45
- Power supply transformer. Made by Subsig. Pri. 115/60 cps Sec. 1750vct. 113ma; Sec. 26vct-5a; Sec. 3.5v-3a. 2500TVA specially priced at..... 5.95
- Utah Pulse Transformer Blocking OSC. Type 9280 each..... .75

RELAYS

- SPST Latching relay made by Kurman. Make coil 115v/60 cps; DCR 1500 ohms. Break coil 115vdc. 10ma; DCR 5000vdc..... \$2.95
- DPST Telephone type; 2p. 1 cl; 1 open; cont. rating. 5a at 50v. coil rating 3.5 ma (at 12K ohms), 1000 vac..... 1.05

24-VOLT RELAY

Grab Bag Bargains

- LEACH, ALLED, ADVANCE, etc. Ea. \$0.50
- SUPT..... Ea. .63
- DPDT..... Ea. .70
- TPPT..... Ea. .70

EDISON GLASS SEALED

THERMAL RELAYS

- 45 to 60 Second Delay. Normally open. \$10 value. OUR PRICE. New.....\$3.45

We repeat— "PRICES DOWN!"

A. SCOPE PARTS

1. SCOPE TRANSFORMER



#77 NOT WAR SURPLUS

Brand new, made to our specs. High voltage plate and filament transformer. Fully enclosed job. Shell type with leads for television, scopes and photo flash units.

Pri. 110V. A.C. 60 cy. Sec. No. 1, 2500 V. at 2 Ma. Sec. No. 2, 6.3 V. at 6. amps. Sec. No. 3, 2.5 V. at 1.75 amps.

Popularly Priced to Accommodate All Our Customers—at Only \$5.55

2. SCOPE FILAMENT TRANSFORMER



110 V. AC. 60 cycle
6.3 V. @ .6 amp
Small and compact..... **95c**

3. SCOPE TUBE



3' 3BP1..... **\$2.95**
Socket for above **.35**

B. TRANSMITTING TUBES

1. 866	\$0.75
2. 807	.95
3. 809	1.50
4. 810	2.50
5. 811	1.95
6. 813	5.95
7. 250TH	7.95

C. TELEVISION PARTS

1. Book—"Television Simplified" \$4.75
2. 300 Ohm line..... .03 ft.
3. 300 Ohm line insulator..... .15 ea.
4. Write for RCA new list of Television Components

D. MODULATION TRANSFORMERS



U.T.C. TRANSFORMERS

No. VM3—125 Watt Mod. Transformer	\$18.00
No. VM4—300 Watt Mod. Transformer	30.00
No. VM5—600 Watt Mod. Transformer	69.00

E. TEST EQUIPMENT

RCA # 195A Volt Ohmyst	\$ 69.00
RCA # 162C Chanalyst	162.50
RCA # 167B Test Oscillator	63.75
WESTON # 697 V.O.M.	26.52
WESTON # 779 Analyzer	76.46
WESTON # 785 Circuit Tester	87.02
WESTON # 798 Mutual Conductance Tube Checker	187.09
HICKOK # 125 V.T.V.O.M.	94.95
HICKOK # 191X Microvolt Generator	145.92
HICKOK # 203 Electronic V.T.V.M.	79.80
HICKOK # 288X Signal Generator	144.60
HICKOK # 534 Tube & Set Tester	138.30

25% deposit, balance C.O.D.

Please include sufficient payment for transportation. Over payment will be refunded.

Write to Dept. R-5

Standard Parts Corp.
235 MAIN ST. HEMPSTEAD, N. Y.

Two-Tube Ham Super

(Continued from page 49)

setting of R_6 . This method of adjustment is considerably simpler than removing or adding turns from the tickler coil L_5 .

When adjustment of the i.f. has been completed, a set of coils for the desired bands should be plugged in and the signal generator set to some point within the range of these coils. As a representative figure for the 3.5 mc. band the antenna condenser is set at approximately half capacity while the oscillator bandset condenser C_3 is set to slightly greater than half capacity. With these settings, the 3.5 mc. band covers from 0 to 90 on the bandspread dial. For 7 mc. operation the antenna condenser C_2 should be set to slightly greater than half capacity and the oscillator bandset to about three-fourths capacity. The 7 mc. band will cover approximately 65 degrees in this case. For 14 mc. operation the antenna condenser C_2 is set to about two-thirds capacity and the oscillator to about approximately the same position as for the 7 mc. band. The 14 mc. band in this case covers 60 degrees on the bandspread.

The 28 mc. band uses the same set of coils as are used for 14 mc. making a total of only 6 coils necessary to cover the four popular bands. For this range the antenna condenser C_2 will be set near minimum capacity and the oscillator bandset about one-fourth meshed. The band covers approximately 62 degrees in this case.

After a signal has been tuned in, the regeneration control should be adjusted. If the station heard is a c.w. station, the proper adjustment for the regeneration control is with the second detector just weakly oscillating. This will give a marked "single signal" effect. If the received station is using phone, the regeneration control should be set just below the point of oscillation.

It will be found that the setting of the antenna condenser is rather broad and it is possible to tune across a considerable portion of any band without the necessity for readjustment. After the desired signal has been located, however, this condenser should be peaked for maximum response.

There will be a slight interaction between the regeneration control and the antenna condenser. For best results, both should be repeaked when necessary.

On the 3.5, 7 and 14 mc. bands the oscillator operates approximately 1600 kc. above the signal frequency. On the 28 mc. band the oscillator operates on the low frequency side of the signal. It will be found that in some cases the same signal may be heard at two settings of the oscillator bandset condenser C_3 . This will be useful occasionally if interference is encountered.

Performance of this receiver is quite satisfactory for most applications and although the audio output is low and insufficient to drive a speaker, worthwhile selectivity and sensitivity are attained. The total cost is approximately fifteen dollars.


—30—

LAYING OUT PANELS

LAYING out parts holes on the cracked surface of a standard 19-inch relay rack panel is a difficult and eye-straining job. It can be greatly simplified, and the surface of the panel saved from scratch marks, if a piece of brown wrapping paper is cemented on the panel by means of rubber cement. Don't use ordinary glue or paste; the paper


will shrivel up. The paper in which the panel itself is wrapped by the manufacturer is ideal for the purpose. Do all the marking in pencil, as shown; drill the holes and then simply pull off the paper.

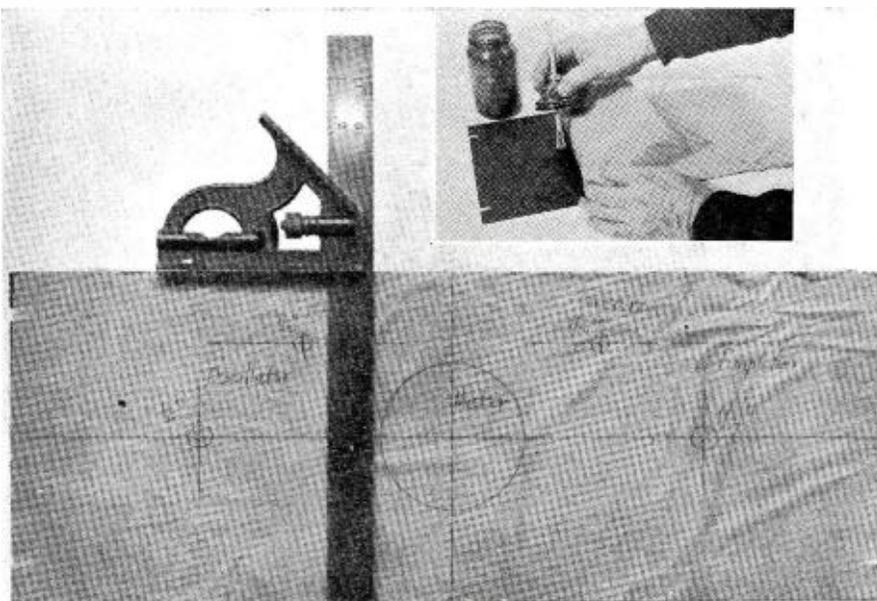If any rubber cement remains on the panel, roll it off with the ball of a finger. It will help to clean the surface. . D.J.B.



NOW AVAILABLE!

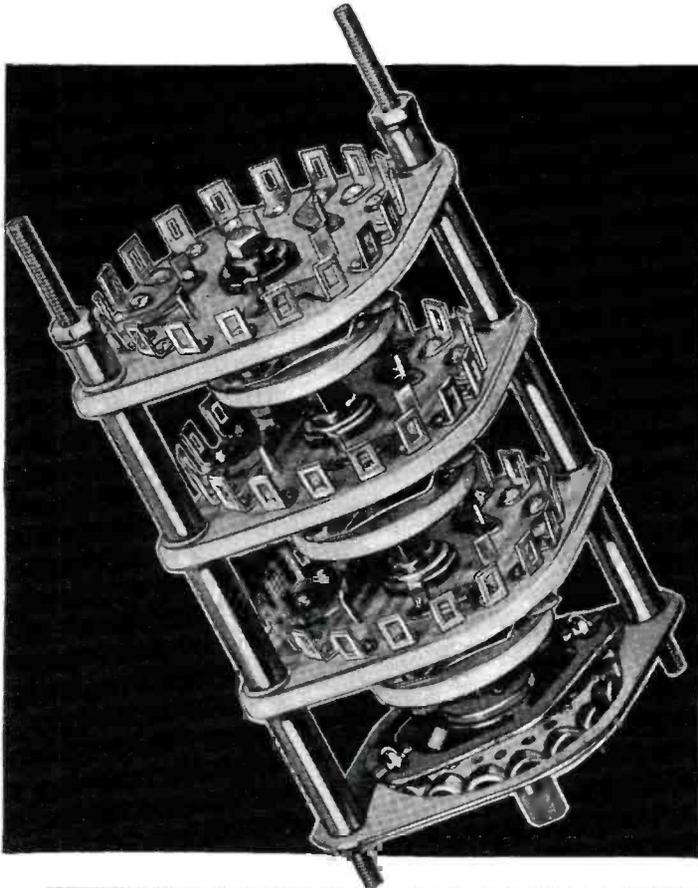**Centralab's medium-duty power switches
for special industrial and electronic uses!**



Efficient performance up to 20 megacycles — specially designed for transmitters, power supply converters, X-ray equipment etc.


HERE THEY ARE — Centralab's famous medium-duty power switches — now ready for a broad new range of industrial and electronic uses!

Look at some of the exclusive features which these sturdy switches offer you: 1) for accurate positioning, square operating shaft snugly fits staked sleeve in steatite rotors. 2) for peak performance, solid silver contacts are individually aligned and adjusted. 3) for flexibility, units can be assembled with shorting or non-shorting contacts. Switching combinations are 1 pole, 17 positions—and 3 poles, 5 positions per section. 20° double roller indexing.

Tests prove that these power switches have a minimum life operation of 25,000 cycles without failure. Switches have single hole bushing mounting, and tie rod extensions at front and rear serve as locating keys and added mounting support. Furnished with cadmium plated, steel and brass parts. Units in non-corrosive metals also available.

RATINGS: 7½ amperes at 60 cycles, 115 volts A. C. Minimum voltage breakdown between critical points is 3,000 volts RMS, 60 cycles. See how these fine Centralab switches can fit your industrial and electronic needs. Write today for Centralab's complete switch bulletin number 722!

Positive Action — Solid Silver Contacts

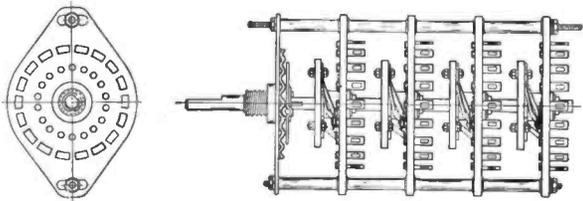


Ceramic Trimmers
Bulletin 630



Ceramics
Bulletin 720



Variable Resistors
Bulletin 697

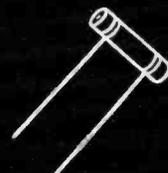


Ceramic Capacitors
Bulletin 630



Selector Switches
Bulletin 722

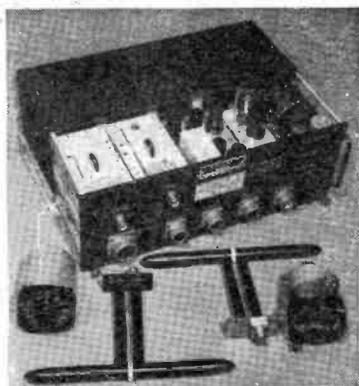Centralab
Division of GLOBE-UNION INC., Milwaukee



ELECTRONIC ALTIMETER ONLY \$75.00


BRAND NEW APN 1 14-tube electronic altimeter in original packing cases. This famous 18x9x7 unit, which weighs only 25 pounds, without plugs or cables, cost the government \$2000, and includes a transmitter, a receiver, all tubes, an altitude limit switch, and two easily installed 11" antennas. A 28 volt dynamotor is included which can be easily changed to other aircraft supply voltages. Working on the radar principle the receiver measures the absolute altitude from 3 to 4000 feet with precision enough for blind landings. In addition the altitude limit switch gives an alarm if the plane's height varies more than 10 feet from a preadjusted value. Another outstanding feature is that connections are provided to control an electronic automatic pilot. This unit might also be used to warn boats of any obstruction that is on their course.

BC-947A 3000 MC ULTRA HIGH FREQUENCY TRANSMITTER

This unit contains amplifier tubes and rectifier tubes, 115 V, 60 cycle power supply, 6 meters including 250 MA, 50 MA, 1 Amp thermo. for input modulating current, 150 V AC, and 1500 V for plate & screen at 1000 ohms per volt. Interior temperature controlled by heater resistances and blower. Plate supply automatically cut off if blower fails. Western Electric charged \$1500 for this unit. Your cost only \$69.95.


PE-109 32-VOLT DIRECT CURRENT POWER PLANT

This power plant consists of a gasoline engine that is direct coupled to a 2000 watt 32 volt DC generator. This unit is ideal for use in locations that are not serviced by commercial power or to run many of the surplus items that require 28-32v DC for operation. The price of this power plant is only \$100. We can also supply a converter that will supply 110v AC from the above unit or from any 28-32v DC source for \$29.95.

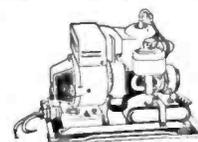

AT LAST YOU CAN AFFORD A LABORATORY STANDARD SIGNAL GENERATOR

The famous Measurements Corp. Model 78B, 5 Tube Laboratory Standard Signal Generator (currently selling new, FOB Boonton, N. J., for \$310.00 net), is available in perfect condition for 25 to 60 cycle, 115 V AC operation. Until now this is the sort of top-flight lab equipment that discriminating buyers have only vainly hoped would be released at a bargain price. Worth every cent the manufacturer asks, but available FOB Buffalo while our limited supply lasts, for only \$99.95. "REMEMBER THAT A STANDARD IS ONLY AS RELIABLE AS ITS MAKER."

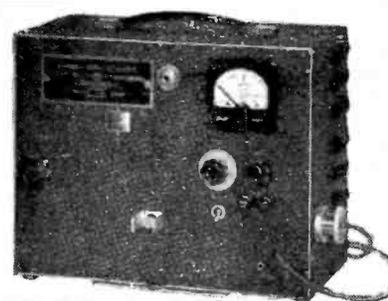

Model 78-B Standard Signal Generator. Two Frequency Bands between 15 and 250 megacycles.

5" RECEIVER INDICATOR OSCILLOSCOPE WITH 31 TUBES


This unit, sold by Western Electric for \$2500.00, includes a 13 tube receiver with 7 IF stages; 2 tube multivibrator sweep generator; 2 tube sweep amplifier; video amplifier; pedestal impulse and sweep generator; and 115 V, 60 cycle supply with 2X2 for high voltage. Makes a wonderful laboratory instrument, or can be more easily converted to a complete home television receiver than any other war surplus item. Only \$69.95.

RADAR OSCILLOSCOPES APN-4, complete with 27 tubes including 5-inch cathode ray tubes, 18"x9"x12". Shipping Weight 50 lb.—\$39.95.

5" RADAR OSCILLOSCOPE BC-412, these units are easily converted to first class laboratory instruments by a few hours work. 110v 60 cps.—\$59.95.

2" RADAR INDICATOR OSCILLOSCOPE complete with 10 tubes including a 2 inch cathode ray tube—\$49.95.


RADAR RANGE UNIT consists of a Helmholtz coil for manually introducing phase shift of 0° to 360°. This unit is ideal for use with oscilloscopes. Contains 3 tubes and a 110v 60 cps. supply.—\$14.95.

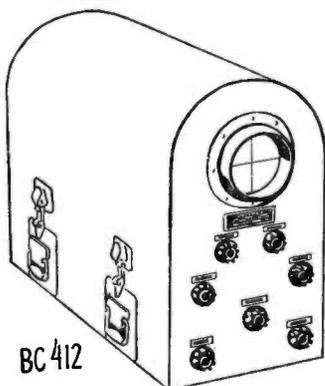

BC 412

MC 363A Range Converter containing 20 tubes, servo motor, oscillator, motor field amplifier, isolating amplifier with 3 stages, 3 stage summing amplifier, 2 stage preamplifier, control amplifier including band shaping motor supply networks to improve servo motor operation, and high current, regulated power supply, similar in construction to the well-known RA57A power unit. Govt. cost \$2000.00—only \$39.95.

BC 221 FREQUENCY METERS with calibrating Crystal and calibration charts. A precision frequency standard that is useful for innumerable applications for laboratory technician, service man, amateur, and experimenter, at the give away price of only \$39.95.

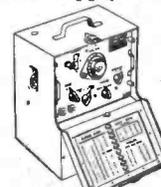

BC 221

BUFFALO RADIO SUPPLY, 219-221 Genesee St., Dept. 5N, BUFFALO 3, N. Y.
CABLE ADDRESS BUFRAD

RADIOMEN'S HEADQUARTERS WORLD WIDE MAIL ORDER SERVICE!!!

SERVICEMEN

Check This Column for Lowest Prices on Quality Parts

TUBES: A warehouse full, including the new miniatures. Order all types you need. We'll try to supply you completely. Special this month: Sylvania 6V6gt—3 for \$2.00; 6X4—75 or 307 transmitting tubes only \$2.50 each; 6L6G—90c; 6SD7 (replaces 6SK7)—50c.

POWER TRANSFORMERS— Half-shell type, 110V 60 cy. Centertapped HV winding. Specify either 2.5 or 6.3 filament when ordering.

For 4-5 tube sets—650V, 40MA, 5V & 2.5 or 6.3V.....\$1.49
 For 5-6 tube sets—650V, 45MA, 5V & 2.5 or 6.3V.....1.75
 For 6-7 tube sets—675V, 50MA, 5V & 2.5 or 6.3V.....1.90
 For 7-8 tube sets—700V, 70MA, 5V & 6.3 or two 2.5.....2.35
 For 9-11 tube sets—700V, 100MA, 5V & 6.3 or two 2.5V 2.85
 For 9-15 tube sets: 600V, 150MA; 5V & 6.3V.....2.95
TRANSFORMERS— All types in stock. **AUTO-TRANSFORMERS:** Steps up 110v to 220v, or steps down 220v to 110v—\$1.95. **FIL. TRANS.:** 6.3v, 8 Amps—\$1.98; 5v, 10 Amps—\$1.98; Universal Output Trans. 8 Watt—89c; 18 Watt—\$1.25; 30 Watt—\$1.59. **AUDIO TRANSFORMERS:** S. Plate to S. Grid 3:1—79c; S. Plate to P.P. Grids—79c; Heavy Duty Class AB or B, P.P. inputs—\$1.49; Midget Output for AC-DC sets—69c; **MIKE TRANSFORMER** for T-17 Shure microphone, similar to UTC ounce type—\$2.00.

CONDENSERS—PAPER TUBULAR 600 WV—.001; .002; .005—8c; .01—.05—9c; .1—10c; .25—23c; .5—36c; **ELECTROLYTICS:** 8mf 200v—20c; 10mf 35v—20c; 30mf 150v—23c; 20/20mf 150—35c; 30/20 150v—46c; 50mf 150v—43c; 8mf 475v—34c; 10mf 350v—65c; **OIL CONDENSERS:** 4mf 600v—49c; **BATH TUB TYPE CONDENSERS:** 3X.1mf—20c. **RESISTORS:** All types in stock at the lowest prices; Resistor Kits—100 2 watt resistors—\$1.95.

FILTER CHOKES: 200, 300, 400, 500 ohm light duty—59c; 200 or 300 ohm heavy duty—59c; 250 ma 35 ohm, made for U.S. Navy, fully shielded—\$1.95; 125 ma 25 ohm 25 or 25 for \$4.25; "Meissner type" tapped filter chokes—25c; 8 amp iron core A filter—25c; Choke-condenser combination, ideal to replace any size speaker field when installing PM speakers—79c.

110 V. CIRCUIT BREAKERS of Magnetic type: Following Current Ratings in Stock: 1, 2.5, 3, 4, 8 Amps. Please Specify, \$1.95 each. **SEVEN ASSORTED I.F. TRANSFORMERS—**\$1.98; Five Assd. Oscillator Coils—69c.

PERMEABILITY TUNERS— Attractive slide-rule dial, compactly replaces dial, tuning condensers, oscillator and antenna coils in broadcast band receivers. Special \$3.43.

WILLARD rechargeable 2 volt storage batteries for G.E. portable radios—\$2.95.

SPEAKERS—PM dynamic type—4"—\$1.55; 5"—\$1.55; 6"—\$1.95; 8"—\$3.95; 10"—\$5.95; 12"—\$7.50.

CRYSTAL PICK-UPS— Two nationally known makes, one \$1.90, the other at \$2.29.

PHONO-MOTORS—110V, 60 Cycle, with turntable—\$4.25.

HEADPHONES— Highest quality Signal Corps headsets with sponge rubber ear cushions. 12" cord and plug \$1.00, 5" rubber covered patchords with phone plug & socket—25c.

RELAYS—Guardian SPST 12-24v, has heavy duty 15 Amp. Contacts—\$1.25; Guardian 12 to 24v D.C. triple make, single break relay, 5 for \$3.75; Sigma super-sensitive 2000 ohm D.C. SPDT Relay. (May be adjusted to operate on less than 1 Milliamperes)—\$2.50; 6 Pole, Double Throw, Telephone Type 2000 ohm Relays, Super Sensitive, \$2.50 ea., or two for \$4.50.

SELENIUM RECTIFIERS— Dry disc type 1 1/2" by 1", 1.2 Amp. maximum, suitable for converting DC relays to AC, for supplying filament source in portable radios, converting DC meters to AC applications, and also may be used in low current chargers—90c.

METER RECTIFIERS— Full wave, may be used for replacement, or in construction of all types of test equipment—\$1.25. Half Wave—90c.

LINE FILTERS—110V— each unit contains two 2 mfd. oil filled condensers and a 15 amp. iron core choke. This filter has innumerable uses such as oil burner line filter, etc. A ten dollar value for 98c.

PHONO AMPLIFIERS— A real AC, 110V, 60 Cycle, 6 Watt Amplifier suitable for PA systems and phonographs; with a husky power transformer. Complete with tubes—\$12.95.

PUBLIC ADDRESS AMPLIFIERS— 25 Watts peak output, 5 tubes, separate controls for Microphone and Phono Inputs, \$65.00 value for only \$32.00.

WIRE—No. 18 POSJ 2 conductor parallel zipcord, brown, 250' spools—\$5.25, 500' spools—\$9.95, No. 18 PO brown rayon covered parallel lamcord, 500' spools—\$12.25. No. 18 SV round rubber covered double wire for wash machines, vacuum cleaners, etc. 250' spools—\$6.95. Rubber covered mike cable, 250' spools—\$15.00. All kinds hook-up wire 1c per ft., transmission line, 50 ohm impedance CMG81, cut to any length, 8c per ft. Single stranded conductor shielded lead with brown rubber over shield, super special, \$1.20 per 100 ft., \$10.00 per 1000 ft.



MICROPHONES— All nationally known brands. Bullet crystal—\$5.45; Bullet Dynamic—\$7.45; Mike Jr.—60c; Handy Mike—90c; Lapel Mike—95c; SHURE T-17 MIKES, with push to talk switch—99c.

20 ASSorted COIL FORMS, including 11 ceramic, 8 polystyrene, and 6 fiber, all useful sizes—50c.

VARIABLE CONDENSERS: 350 MMFD, 5 gang—\$1.95; 4 gang—\$1.49; 3 gang—\$1.32; 2 gang—79c; 7.5 to 25 MMFD, 1750v spacing, extra long shaft Hammarlund—69c; miniature variables—25 MMFD—39c; 50 MMFD—49c; 75 MMFD—59c; 100 MMFD—69c; 140 MMFD—79c.

TRANSMITTING RF CHOKES, 4 PIE, 350 Ma—25c or 4 for \$1.00.

INTERRUPTION FREQUENCY COILS for super-regenerative receivers or the tremendously popular FM adapters for standard broadcast sets. Iron core with a resonant frequency of 50 KC—39c; Air Core, 100 KC—29c.

VIDEO AMPLIFIER PLATE COILS— Slug Tuned—25c.


REMOTE CONTROL UNIT: Aluminum case 4x3x2" containing 2 potentiometers, triple pole switch, 4 knobs, gear mechanism, counter and phone jacks—59c.

MODULATION TRANSFORMERS: 10 watt, metal case—95c; 30 watt, open type—\$1.95; 40 watt, cast aluminum case—\$2.95.

6-BAND COMMUNICATIONS RECEIVER BC-348

Featuring coverage from 200 to 500 Kc. and 1500 to 18000 Kc. on a direct reading dial with the finest vernier drive to be found on any radio at any price—extreme sensitivity with a high degree of stability—crystal filter—BFO with pitch control—standard 6 volt tubes. Contains a plate supply dynamotor in compartment within the handsome black crackle finish cabinet, the removal of which leaves plenty of room for installation of a 110V, 25 or 60 cycle power supply. These receivers, which make any civilian communications receiver priced under \$200.00 look cheap and shabby by comparison, are only \$44.50. Power supply kit for conversion to 110V, 25 or 60 cycle, is only \$8.50 additional.

BENDIX SCR 522— Very High Frequency Voice Transmitter-Receiver—100 to 156 MC. This job was good enough for the Joint Command to make it standard equipment in everything that flew, even though each set cost the Gov't. \$2500.00. Crystal Controlled and Amplitude Modulated—HIGH TRANSMITTER OUTPUT and 3 Microvolt Receiver Sensitivity gave good communication up to 180 miles at high altitudes. Receiver has ten tubes and transmitter has seven tubes, including two 832's. Furnished complete with 17 tubes, remote control unit, dynamotor and Ant.—\$37.95. We include complete instructions for conversion to 110V AC.

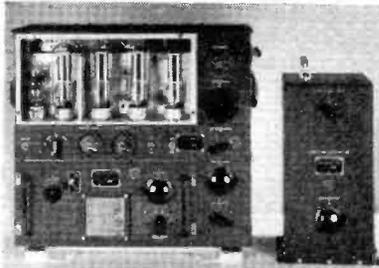

GENERAL ELECTRIC 150-WATT TRANSMITTER

Cost the Government \$1800.00
Now only \$44.50!!!

This is the famous transmitter used in U. S. Army bombers and ground stations, during the war. Its design and construction have been proved in service, under all kinds of conditions, all over the world. The entire frequency range is covered by means of plug-in tuning units which are included. Each tuning unit has its own oscillator and power amplifier coils and condensers, and antenna tuning circuits—all designed to operate at top efficiency within its particular frequency range. Transmitter and accessories are finished in black crackle, and the milliammeter, voltmeter, and RF ammeter are mounted on the front panel. Here are the specifications: **FREQUENCY RANGE:** 200 to 500 KC and 1500 to 12,500 KC. (Will operate on 10 and 20 meter band with slight modification.) **OSCILLATOR:** Self-excited, thermo compensated, and hand calibrated. **POWER AMPLIFIER:** Neutralized class "C" stage, using 211 tube, and equipped with antenna coupling circuit which matches practically any length antenna. **MODULATOR:** Class "B"—uses two 211 tubes. **POWER SUPPLY:** Supplied complete with dynamotor which furnishes 1000V at 350 MA. Complete instructions are furnished to operate set from 110V AC. **SIZE:** 21 1/2 x 23 x 9 1/4 inches. Total shipping weight 200 lbs., complete with all tubes, dynamotor power supply, five tuning units, antenna tuning unit and the essential plugs. These transmitters are priced to move fast: Order today and be the proud owner of one of the finest rigs obtainable.

GENERAL ELECTRIC RT-1248 15-TUBE TRANSMITTER-RECEIVER

TERRIFIC POWER—(20 watts) on any two instantly selected, easily pre-adjusted frequencies from 435 to 500 Mc. Transmitter uses 5 tubes including a Western Electric 316 A as final. Receiver uses 10 tubes including 955's, as first detector and oscillator, and 3 7H7's as IF's, with 4 slug-tuned 40 Mc. IF transformers, plus a 7H7, 7E6's and 7E7's. In addition unit contains 8 relays designed to operate any sort of external equipment when actuated by a received signal from a similar set elsewhere. Originally designed for 12 volt operation, power supply is not included, as it is a cinch for any amateur to connect this unit for 110V AC, using any supply capable of 400V DC at 135 MA. The ideal unit for use in mobile or stationary service in the Citizen's Radio Telephone Band where no license is necessary. Instructions and diagrams supplied for running the RT-1248 transmitter on either code or voice, in AM or FM transmission or reception, for use as a mobile public address system, as an 80 to 110 Mc. FM broadcast receiver, as a Facsimile transmitter or receiver, as an amateur television transmitter or receiver, for remote control relay hook-ups, for Geiger-Mueller counter applications, and it sells for only \$29.95 or two for \$53.90. If desired for marine or mobile use, the dynamotor which will work on either 12 or 24V DC and supply all power for the set, is only \$15.00 additional.

SCR-274 N COMMAND SETS, including 3 separate 6 tube superhet receivers, 2 separate transmitters, each with 40 watts output, modulator and DC power supply. Bargain price for all 6 pieces complete with tubes—\$39.95.

BC 659 TRANSMITTER-RECEIVER, FM voice only, frequency range 27 to 38.9 MC, crystal controlled, 2 watts output. This battery powered unit makes the ideal portable or mobile transmitter for the ten meter ham band. Get on ten meters for only \$49.95.

RADAR INTERCONNECTOR UNIT, contains 15 tubes—\$29.95. **C-144 TRANSMITTER,** 2 type 826 tubes as oscillator in lecher line tuning circuit that resonates between 150 and 200 Mc. Contains 3 DC power supplies that operate from 110v 60 cycles, 10 tubes, meter, circuit breaker, and carrying case—\$49.95.

AIR CRAFT MARKER BEACON RECEIVER— Complete with 3 tubes and sensitive relay to control external circuits from received signals. Just the receiver you have been waiting for to control models, open doors from a distance, etc. Priced at only \$4.95.

AIRPLANE INTERCOM AMPLIFIER— Complete with 4 tubes in aluminum case—\$4.95.

BC-654 TRANSMITTER-RECEIVER— Complete with 17 tubes and 200 Kc. calibrating crystal—\$29.95.

BUFFALO RADIO SUPPLY, 219-221 Genesee St., Dept. 5N, BUFFALO 3, N. Y.
CABLE ADDRESS BUFRAD

**SPECIAL! WRL MT-100
MULTITESTER
CAT. NO. 16-491**

Less leads

\$1945



Sturdy Steel Case—
30-60 Degree Angle—Stand it up or Lay it Down—
Ranges: DC Volts—0/50/250/500
V AC Volts—0/10/100/500/1000V
DC Mills—0/10/100 Mills. Ohm-meter—Low Range 0-500 Ohms. High Range—0-100,000—1 Meg. 3" Meter. Size 9 1/2x8x3 1/4. Here's a buy for every ham, experimenter, serviceman.



Our stocks of radio and electronic equipment are growing rapidly. We now have many items that have been scarce for years. Write for our latest Flyer or write us your needs. We are the only "personal service" radio parts mail order house in the country. For faster service order from WRL—Leo W0GFQ.

ORDER YOUR RECEIVER FROM LEO, TODAY!

We carry all types and models. S-40, SX42, RME45, HQ 129X, and all National models in stock for immediate delivery. Collins receivers available soon. Buy on our easy payment plan—lowest terms in the country. Liberal trade-in allowance.



READ WHAT ANOTHER AMATEUR SAYS

About the WRL Globe Trotter Kit from J. M. Reagan, Del Rio, Texas—
"... and am proud to say it's the best little transmitter I have ever had the pleasure to operate. It's amazing the way it bucks QRM. I wouldn't take double the price I paid for it."

Many other actual field reports of amateurs using the Globe Trotter testify to its excellent performance. It's the hottest ham equipment on the market today. The WRL Globe Trotter is capable of 40 watts input on C.W. and 25 watts input on phone on all bands from 1500 KC through 28 Megacycles. Incorporates the Tritet Oscillator using a 40 meter Xtal; Heising choke modulation; three bands, all pretuned; 10, 20, and 80 meters; two power supplies, one for 807 final and modulator tubes, one for speech amplifier and oscillator stage.

IMMEDIATE DELIVERY

*All prices quoted are domestic. Write for export prices.

40 WATT INPUT. Cat. No. 70-300... **\$69.95**

Complete including all parts, chassis panel, streamlined cabinets, less tubes, coils and meter.

No. 70-312 Same as above, wired by our engineers

1 Set Coils, Meter, Tubes\$79.50

1 Set Coils, Meter, Tubes\$15.15 Extra



Address Dept. RN-5, Council Bluffs, Iowa

Sound Recording

(Continued from page 63)

on film, we find the low cost of the magnetic system has much to offer in producing a picture more economically. The simplicity of handling this type of recording compares favorably with other forms of wire, tape and magnetic disc recording. Immediate monitoring is available with magnetic recording on film. No processing is necessary and the magnetic recording medium can be erased by demagnetizing. The sound strip may be used over and over until the quality and coordination of sound is perfect. No serious distortion with overmodulation is probable and any part of the sound track can be edited simply by erasing and dubbing in new sound.

There are two main disadvantages to magnetic recording on film: The recording head contacts the record surface which results in the possibility of wear, and the technical performance is not quite equal to the advanced optical methods now used by the large studios. However, it should be pointed out that the above facts are based on the present state of the art. As magnetic recording on film is perfected, it may even supplant the optical systems now commonly employed.

The method for recording and reproducing magnetic sound on film is illustrated in Fig. 9. A magnetic head assembly is employed and is mounted rigidly on an adjustable holder. In fact there are three heads each having an individual arm and a spring holding the head against the film while the latter rides against the brass drum. The upper head is used for erasing and removes sound from the magnetic track previous to the recording of new sound. The erase coil is fed with the conventional supersonic frequency of approximately 40 kc. Recording is accomplished at the center head. This contains a main audio winding plus an auxiliary high frequency coil. This

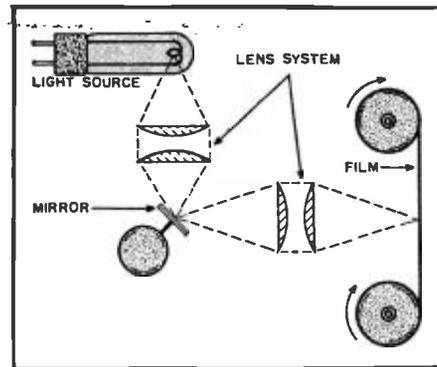


Fig. 7. The essential elements used for variable area optical recording.


coil is connected in series with the erase coil to secure proper high frequency excitation. The third head is the monitor or playback head. This feeds directly through the amplifier and follows the picture by approximately fifty milliseconds.

Sections of various films are illustrated in Fig. 10. A magnetic material of approximately one-half mil in thickness is added to the emulsion on the film. The relative positions for the magnetized sound track are illustrated for various types of film, mainly the 8, 16, and 35 millimeter.

Magnetic recording on film bids fair to become extremely popular with the amateur projectionist. Home talking movies have become an economical reality and it is expected that with further improvements inexpensive projecting systems will be developed and will gain much popularity even with the novice.

There are other methods now employed for magnetic recording and these include magnetic recording on separate film. This is particularly suited for nonsynchronized work; for example, an eight millimeter film could be used with a full width sound track. This would be played on a second machine and would be synchronized with the other machine carrying the picture. Editing is very

Fig. 8. Endless loop of 35 mm. film used in the Filmgraph recorder.

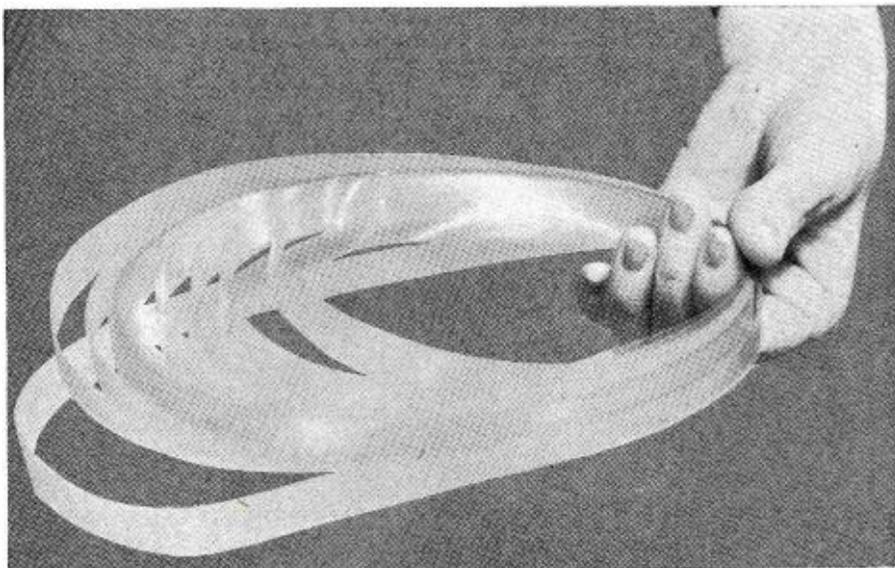

SPRAGUE TRADING POST

SWAP-BUY OR SELL!

SELL OR SWAP—35-watt Phone-CW transmitter, works three bands. Custom built. Complete 10-meter Xtal and coils, 80-meter Xtal and coils. With mike. Outfit in A-1 shape, now on air. Alden Sanford, W6KKU, 327 Cleburn Ave., Helena, Ark.

SELL OR SWAP—General Radio VTVM 722 with hi-frequency probe. RME-69 receiver with matching speaker. Both in excellent condition. Can use Sky Traveler or Sky Banger receiver. W9LNG, 6311 W. Grand Ave., Chicago, Ill.

SELL OR SWAP—National FB7XA with 7mc coils. Need TB-4, BC-211 or what have you? C. Borszewick, W2GWA, 1066 President St., Brooklyn, N. Y.

WILL SWAP—New G.E.-818, never used for new or slightly used RCA-8005. Mc-Morrow Wilkin, 182 Oakwood Ave., Troy, N. Y.

WANTED—Used mechanical code training set or Instructograph for learning code. Louis Borits, 172-14 82nd Ave., Jamaica, N. Y.

WANTED—Small 100-watt transmitter. Prefer Hallcraft HT-9. Describe fully. R. H. Wilson, 50 W. Dover St., Valley Stream, L. I., N. Y.

WANTED—Collins T47A/ABT-13 with dynamotor and cables. State price and condition. J. J. Lee, W1GEB/6, 441 Ellis, San Francisco 2, Calif.

WANTED—Will pay cash for all parts variable condenser, including dials, dial plate, pointer, etc., for Bosch model 510, serial #328804. Charles B. Twiss, 164 Meridian St., Groton, Mass.


WANTED—Thorndarson T-15D79 driver transformer, must be in new condition. Top price. Joseph Cairo, 6516 Cornelius St., Philadelphia 38, Penna.

WANTED—Rider's manual abridged 1 to 5. Also Rider's service books. Richard Clark, 157 Grand Ave., Grand Rapids, Mich.

WANTED—Following transformers: Thorndarson 15R05 UTC 1S-70 or Stancor P-3005. Will pay cash or trade for new Astatic B-10 pick-up. Harry Brodner, 1925 University Ave., New York 53, N. Y.

WANTED—Will pay cash for auto radio, 6-tube or more, controls to fit 1938 Dodge. Must be in good condition. Describe fully and state price. Wm. T. Seely, 709 Taraval St., San Francisco, Calif.

WHAT'S THIS ABOUT MIDGET TUBULARS?

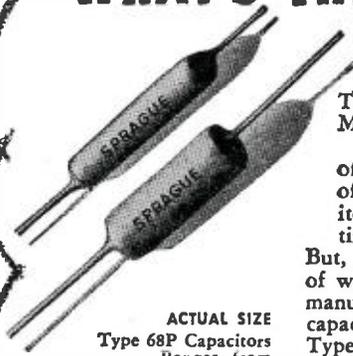

ACTUAL SIZE
Type 68P Capacitors
... Ranges from
.001 mfd. 400V to
0.5 mfd. 100V.

There's more about the new line of Sprague Type 68P Midget Tubular Capacitors than appears on the surface:

They're the smallest, most dependable midgets yet offered for normal applications. They're the direct result of Sprague engineering experience in developing capacitors for the famous VT fuse and other miniature wartime electronic assemblies...

But, even more important, they offer concrete evidence of what you can expect from Sprague in the future. No manufacturer was called upon to engineer as many unique capacitor types for war equipment as was Sprague. The Type 68P Midgets are the first of these to be converted for everyday service and amateur radio use. Many more are coming.

Look to Sprague for the newest—and the best!

See Us in BOOTH 89 at the Chicago Show!

WANTED—Hallcraft SX-28 or SX-28A. Must be in good condition, with or without matching speaker. Henry Musenden, 551 W. 178 St., New York 23, N. Y.

WANTED—BC-610-E Transmitter or similar commercially-built transmitter. Cash or trade. Also want mutual conductance tube tester, other good test equipment. K. H. Stello, 12026 Peoria St., Roscoe, Calif.

WANTED—Full set Rider's manuals and tube tester for cash. C. H. Miller, Highmore, S. D.

WANTED—Used Rider's manuals, reasonable. Quote price. Leo Senzio, 112 Harrison, Gloversville, N. Y.

WILL TRADE—Supreme 189 Multi-Wave sig. generator, hardly used, for a 500 or 750 watt 16mm movie projector, or what do you have? John Takish, 10307 Ave. F, Chicago 17, Ill.

WILL TRADE—Argus A2F like new. Need ham receiver. Harold Pyle, Conrad, Montana.

WILL TRADE—10" dynamic speakers; power transformer with four filament windings, 200 mls; other transformers; var. condensers. Need second-hand instruments: sig. generator; hi-range volt-ohm-ist; tube tester; short wave receiver, 3-band. S. Egelberg, 1485 Vyse Ave., Bronx 60, N. Y.

WANTED—Communications receiver SX-28 or similar. Swap three Lionel trains 027 gauge with accessories, \$315 value. Clarence Cook, 115 Chadwick St., Medina, N. Y.

WANTED—University RCP-12 chandelier-type speaker baffle. Ralph Senechal, 586 Hampton Rd., Hayward, Calif.

WANTED—2 Handle-talkies 144 mc-148 mc in working order; National receiver IC-40 good working order. Roger Mayrand, 1828 Valois St., Montreal 4, Canada.

WANTED—Radio control box BC-450A complete with instruction book. Will trade for SCR-274N also 6-12 V Sig. C. battery charger. Will pay reasonable price. John A. Seaman, Gentry, Ark.

WANTED—Meissner signal shifter with coils for all bands. Charles Costa (W2SIF), Box 97, Woodstock, N. Y.

WANTED—Class B transformers for 46's. Preferably from BC-223A; also SW-3. W6YKT, P. O. Box 769, Elnore, Calif.

WANTED—Used S-20-R or S-22-R receiver, any condition. Will swap Army field set valued at \$10 or cash. Carlton Cleveland, 1110 Fullerton St., Chicago 14, Ill.

WANTED—5" scope; schematic or service manuals, parts for CW-23012, CW-23098 Navy remote controls for Navy RU-16 rec. and GF-II transmitter. M. B. Hemby, 1240 Green St., San Francisco 9, Calif.

WANTED—Condenser tester; filament transformer, 5V-25 amps., 5000V, 110V a-c primary; power transformer 3000-0-3000, 350 MA, 110V a-c primary. Baney Radio Service, 115 Cleveland St., Butler, Pa.

WANTED—Used instruments: sig. generator; hi-range volt-ohm-ist; tube tester; or small s.w. receiver, three bands, plug in coils. Stanley Egelberg, 1485 Vyse Ave., Bronx 60, N. Y.

FOR SALE—SW-3-AC complete with power supply, 20, 40, 80-meter band spread coils, tubes \$25; FB rig. Xtal osc, 6L6's push-pull 40-watts, all coils, ready to go on air. \$35. Bou Radio Service (W9ESX), 3131 N. Percy St., Philadelphia 33, Pa.

FOR SALE—2-meter super-regen. receiver. Closed metal cabinet, 5" d.m. speaker in front panel, 955, 6C5, 6F6-self quenched detector. F. Craven, 2216 S. 7th St., Philadelphia 48, Penna.

FOR SALE—Six OC3-VR105 tubes, all new, \$1 each. John Tokalz, 30 Carver St., Fall River, Mass.

FOR SALE—Kato rotary converter 110V d-c to 110V, 60cy. a-c. 150 watts continuous. Never used. Perfect condition, \$37. Charles B. Wakeman, 495 Yale Station, New Haven, Conn.

FOR SALE—Weston Meters: 3" d-c 0-50-250, 1000 ohms per volt; 3" 301 metal 0-5V d-c; Thermo-Galy, 425 current squared 0-100V; Jewell 77 a-c 0-3-15-150; Tobe hi-voltage 4mfd 1000V d-c. F. H. Peran, 12 West Pultney Sq., Bath, N. Y.

FOR SALE—Two brand new General Radio 247 var. condensers, 250 mmfd. Both postpaid, \$3. J. Goldstein, 151-09 34th St., Flushing, L. I., N. Y.

FOR SALE—10-meter phone transmitter complete with all tubes, meter, mike, supply, 10' vertical antenna, 6L6 osc., 6L6 final, 6C5 speech, 6L6 mod. \$65. Stanley Zuchora, 2748 Meade St., Detroit 12, Mich.

FOR SALE—RCA phono osc. \$6; Bud code osc. with Instructograph and tapes 1-7 \$30; one-tube xtal osc. transmitter 0-5v, 5-watts with power supply. \$8. Send for details, all letters answered. Marvin Calvert, Lawrenceville, Ill.

FOR SALE—RCA phone motor 10" turntable, 50 cy. operation. Oil damped fiber gear, heavy duty, \$5. Harry Katz, 1647 Holbrook St. N.E., Washington, D.C.

WANTED—1-25B8 also 2-6B5. Must be new, preferably in carton. M. L. Grigsby, Granger, Iowa.

WANTED—Gud receiver covering 10-160 meters. National SW-3 or FB7X will do. Have Collins 32-RA 100-watt phone, 150-watt cw transmitter, 4-channels MOPA or Xtal; also BC-348, ES BC-221AC-W2SXV, 141 Sanford Ave., Lyndhurst, N. J.

YOUR OWN AD RUN HERE FREE

The Sprague Trading Post is a free advertising service for the benefit of our radio friends. Providing only that it fits in with the spirit of this service, we'll gladly run your own ad in the first available issue of one of the six radio magazines in which this feature appears. Write CAREFULLY or print. Hold it to 40 words or less. Confine it to

radio subjects. Make sure your meaning is clear. No commercial advertising or the offering of merchandise to the highest bidder is acceptable. Sprague, of course, assumes no responsibility in connection with merchandise bought or sold through these columns or for the resulting transactions.

Send your ad to Dept. RN-57

SPRAGUE PRODUCTS COMPANY
NORTH ADAMS, MASS.

(Jobbing distributing organization for products of the Sprague Electric Co.)

ASK FOR SPRAGUE CAPACITORS and *KOOLOHM RESISTORS by name!

May, 1947

* Trademark Reg. U.S. Pat. Off.

103

Light & Versatile

FOR BETTER SOLDERING

Patterned for durability and soldering ease, this nimble pencil iron is equally at home performing large heavy duty jobs or in the hard-to-reach spots requiring pin-point accuracy.

Check These Points!

- ★ QUICK HEATING . . . 90 SECONDS
- ★ LIGHTWEIGHT . . . 3.6 OUNCES
- ★ HANDY SIZE 7 INCHES
- ★ SAVES ELECTRICITY . . 20 WATTS

Perfect Balance!

These 4 INTERCHANGEABLE tips give you a point for each particular job.



No. 536 Pyramid Tip, made from Tellurium



No. 539 Chisel Tip, made from Tellurium



No. 538 Chisel Tip, made from Elkloy A, Tip 1/8" dia.



No. 537 Pencil Tip, made from Elkloy A, Tip 1/8" dia.

SEE YOUR NEAREST RADIO, HARDWARE OR HOBBY DEALER

UNGAR Electric Tools Co.
BOX 2255, TERMINAL ANNEX - LOS ANGELES 54, CALIF.

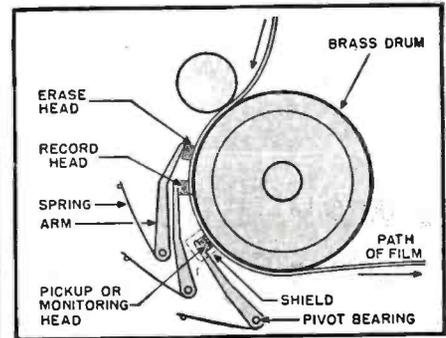


Fig. 9. Triple head assembly for recording and reproducing (magnetically) on film.

simple and the film may be cut and spliced in the usual way.

Magnetic Recording on Tape, Disc, and Wire


Fundamentally the recording on paper tape, paper disc, or wire is the same. The main difference lies in the mechanical means for driving the material to be magnetically recorded, in the means for playing back the sound, and in the employment of different techniques for recording the sound on the material.

Magnetic materials are drawn past a recording head. As the material passes the head, it becomes and remains magnetized. The amount of magnetism remaining in the material at each instant is governed by the signal impressed upon the recording head. In playing back, the magnetic material is drawn past a playback head. In many systems the recording and playback heads are the same, Fig. 11. The magnetization, which is variable, exists in the material and induces a corresponding voltage in the coil of the playback head. The functions of recording and playback are incorporated into a single record-playback head in most magnetic recorders.

It is a simple matter to erase any signal from any of the magnetic materials now employed. A strong field is set up within the erase head and this is impressed upon the material. This erases the old signal and makes the material ready to receive new signals. Basically, the tape, disc, and wire recorders consist of the magnetic material, the record-reproduce head and the erase head. In addition, of course, are the various types of driving systems used to draw the material through or over the head and the conventional amplifying and reproducing systems.

A supersonic oscillator, usually from approximately 30 to 40 kc., serves

Fig. 10. Sections of 35, 16 and 8 mm. film showing the actual position of the magnetic sound tracks.

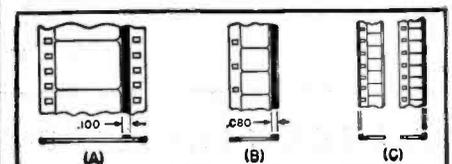

Presenting

The E.M.C. Volometer*

(trade name)

5 DC and 4 AC voltage ranges from 0 to 3000 V. Three current ranges. Four resistance ranges.

Resistances 1/20 ohm to 20 megohms. Low ohm scale is low drain back-up type. First ten divisions 1/20 ohm each.

AC volts 25 cycles to 1 megacycle. No external source of power required. Battery and rectifier replaceable without soldering iron. Matched-pair multiplier resistors accurate to 1%. 4 1/2" meter.

For further information about this and other models, write us direct. For a conclusive demonstration, see your regular jobber.



MODEL 101 B (above)
\$20.95

Portable	\$24.95
Model 101 A	\$17.50
Same as above with 3" meters.	
Portable	\$21.50

ELECTRONIC MEASUREMENTS CORP.

114 Liberty St. • New York 6, N. Y.

new

CONCORD

Radio

Catalog



**RADIO PARTS • RADIO SETS
 RECORD CHANGERS • PLAYERS
 HAM GEAR • AMPLIFIERS • TESTERS**

It's here—ready for you now—the new, comprehensive, 1947 Concord Catalog displaying a vast, complete selection of everything in Radio and Electronics. Send for your copy now. Select your needs from value-packed pages showing thousands of items available for IMMEDIATE SHIPMENT—hundreds of them now available for the first time—featuring new, latest 1947 prices. See the new LOWER prices on finest-quality RADIO SETS, PHONO-RADIOS, RECORD CHANGERS, RECORD PLAYERS, PORTABLES, AMPLIFIERS, COMPLETE SOUND SYSTEMS, TESTERS. See complete latest listings of all the well-known, standard, dependable lines of radio parts and equipment—tubes, condensers, transformers, relays, resistors, switches, speakers—all available for IMMEDIATE SHIPMENT from huge stocks in CHICAGO and ATLANTA. Whatever your needs in Radio and Electronic Parts, Supplies and Equipment—before you buy—SEE THIS GREAT NEW CONCORD CATALOG. Mail coupon for your FREE copy now.

free

**Radio Hams • Service Men • Engineers
 Sound Men • Maintenance Men
 Schools • Institutions • Manufacturers**

THIS CATALOG IS FOR YOU!

Mail **COUPON TODAY!**

Concord Radio Corporation, Dept. E-57
 901 W. Jackson Blvd., Chicago 7, Ill.

Yes, rush FREE COPY of the comprehensive new Concord Radio Catalog.


Name

Address

City State

CONCORD
 RADIO CORPORATION
 LAFAYETTE RADIO CORPORATION
 CHICAGO 7, ILL. ATLANTA 3, GA.
 901 W. Jackson Blvd. 265 Peachtree St.

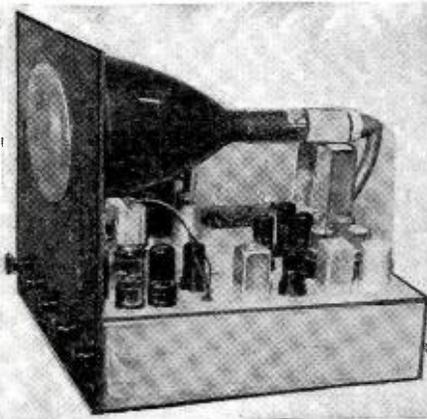HIGHBRIDGE'S BEST BUY NEW DYNAMIC TELEVISION KIT



COMPLETE With **\$159.50**
Tubes—Parts—Cabinet

Exclusive Mail Distributors

Check These Outstanding Features:

- Three stages of video I.F. amplification—3.5 MC bandwidth.
- Receiver may be aligned easily without use of signal generator.
- Complete resistance and voltage analysis chart for easy trouble shooting supplied with each kit.
- IF transformers are slug tuned for high gain and maximum efficiency.
- Safety interlock switch supplied with each unit.
- Simplicity of operation—only 5 controls on front panel.
- Schematic diagrams are broken down into simple circuits for ease in wiring.
- Picture is very stable—does not jump or tear out even under unusual receiving conditions.
- Seventeen tubes including large picture tube.
- Picture tube is seven inches in diameter and gives a picture 26 square inches in size.
- All parts are unconditionally guaranteed to be electrically and mechanically perfect.

Set comes complete with all necessary information sheets, parts, drilled and punched chassis, beautifully finished front panel and modernistic cabinet. Hardware and other necessary items are also included. NOTHING ELSE TO BUY.

SONAR SOUND DETECTION UNIT In Original Overseas Packing

Ideal for detecting underwater sounds within an area of 15 miles. Using a Rochelle salt crystal as the active unit the sound is transmitted up a 60 ft. cable. Completely enclosed in a solid rubber sheath. Originally used in harbor defense. Coupled with audio amplifier it has many valuable uses. **\$7.95**

ELECTRON SELENIUM RECTIFIERS
50 to 99.....85c
6 to 49.....90c
1 to 5.....99c



Quotations on larger quantities furnished upon request

USEFUL FOR: • AC-DC Portables
• Intercom Power Supplies
• Console Radios
• Replaces 29 Types of Rect. Tubes

Gives Instant Reception—Requires No "Warm Up"
Replaces Tube & Socket—Prolongs Life of Set
Requires Less Space—Increases Sensitivity
Made to Last the Life of the Set



NEW BATTERY BOOSTER Powerful—Efficient Economical

A compact, lightweight, automatic, constant voltage battery charger which is especially designed to help car, truck or tractor owners keep 6 volt storage batteries fully charged. 4"x4"x5". Weighs 4 lbs. packed. Operates on 105-120 v AC 60 Cy. DC 6 v 4-2 amp. Complete with 6 ft. AC cord with molded rubber plug and 6 ft. DC cord with alligator clips. **\$9.27**

Vision Research Laboratory design and construction of modern 5 or 7 inch television receiver. Instruction Book and complete set of coils. **\$6.95**

Special 100 By-pass Condensers, 10 varieties, complete assortment. Special. **\$4.95**
New #681P1/SNA—Glass Strobotron **\$3.25**

tubes. Each
All Prices FOB New York City, N. Y.
**Highbridge Radio—Television
and Appliance Co.**
343 Canal, CA 6-8661, New York 13

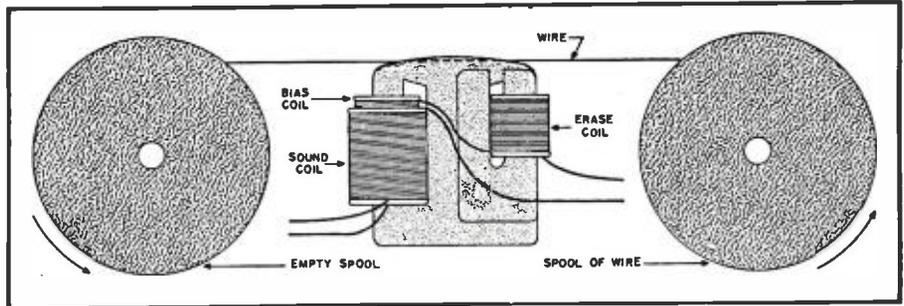


Fig. 11. Combined record-playback head assembly for wire.

the double purpose of providing high frequency for both the demagnetizing head and for the recording head. The material is first run through the erase head. Here it is demagnetized and made ready for the recording. The audio signal from the sound source appears at the recording head. The application of a supersonic signal to the recording head provides a bias. This is essential to overcome the non-linearity of the normal magnetization curve of the magnetic materials. Fundamentally these materials are the same. They differ only in their type of construction. These materials may be in the form of steel tape, wire, magnetized coating upon paper tape, or upon paper discs, or in fact the magnetized material may be coated or impregnated into various alloys.

Insofar as quality of recording-reproduction is concerned, we find that speed is an all-important factor. The higher the speed, generally, the greater will be the fidelity. This will be completely explained in following articles.


The development of record-erase heads has gone on at a rapid pace. Beginning from cumbersome units often measuring four inches square, new tiny heads have been developed which are no larger than a regular two cent postage stamp. The magnetic field in these new units has been concentrated and condensed to a very small area. The slot, for example, in the case of a wire recorder head, often

is not more than one-thousandth of an inch in width. The traveling wire passes through this slot and encounters the magnetic field set up by the head as in Fig. 11.

Three basic types of magnetic recording heads are illustrated in Fig. 12. In magnetic recording, frequency response, noise level, and signal amplitude are affected by the type of magnetic material used. At fixed speed and at lower frequencies, the retentivity, which is the measure of residual flux density, will determine the magnitude of the output voltage from the reproducing head. Generally speaking, the lower or bass notes must be suppressed when using magnetic recording. This too applies to the cutting of slow speed electrical transcriptions by means of lateral styli on discs.


Frequency response from the above systems, as mentioned, depends largely upon the speed of the magnetized material as it passes the head. A frequency response of between 60 and 8000 cycles per second can usually be obtained from most of the above machines. Recording time depends upon the material used and upon the physical size of the containers for the magnetized material. For example, the average wire recorder has enough stainless steel wire to operate for approximately 66 minutes at a speed of 2 feet per second. This type of recorder is being used to dictate this entire series of articles.

Fig. 12. Simplified diagrams of (A) record-reproduce head for transverse recording on tape, (B) offset, thick pole pieces which improve characteristics of head shown in (A), and (C) closed type wire record-reproduce head.

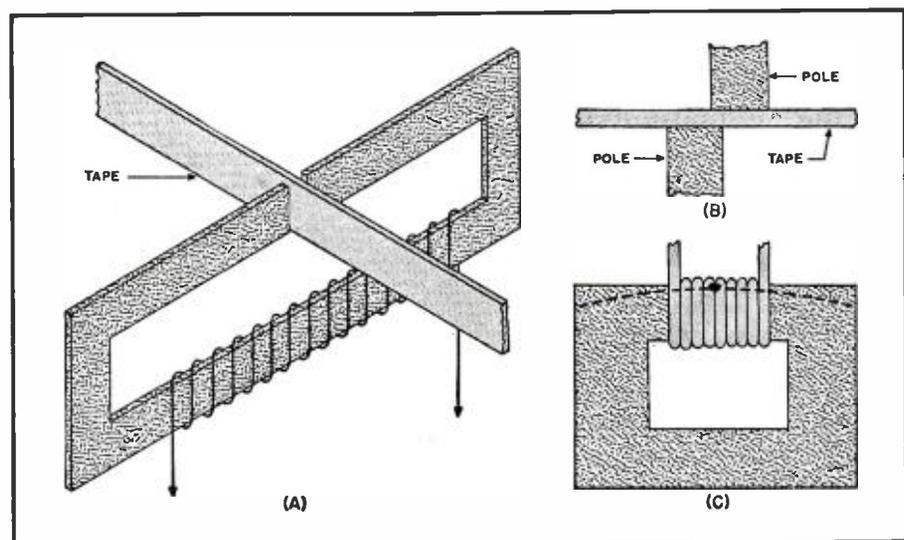

Announcing
**THE NEW ADDITION TO OUR
 RADIO SCHOOL**

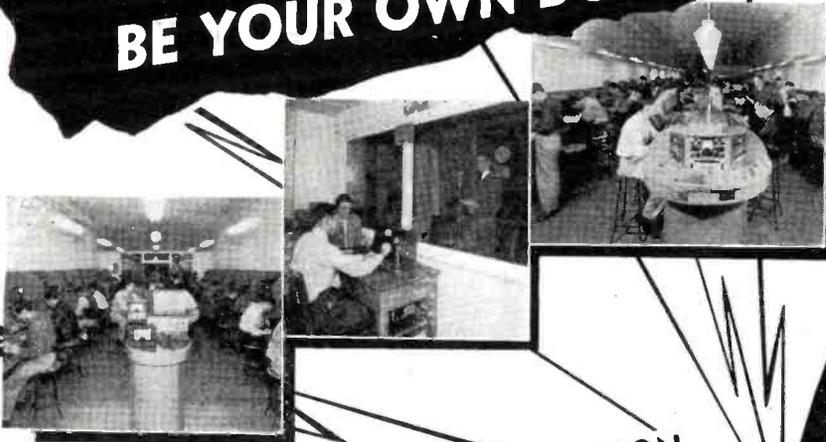**OWN YOUR OWN
 RADIO SHOP
 BE YOUR OWN BOSS**



**WITH A THOROUGH EDUCATION
 FROM OUR COMPLETE RADIO SCHOOL**


Radio (and its allied fields—electronics, television, radar) now looms as a major industry in the United States offering a constant and ever-expanding field of wealth and opportunities. Each new development points the way toward further improvements and an increasing demand for men and women, specialized in this field.

The Radio courses offered by the Tyler Commercial College are highly specialized to enable you to enter many branches of radio, both as your vocation or your profession. The present courses listed represent a partial list of the extensive and complete training offered by the Tyler Commercial College who have had over 30 years experience in the Radio Training Field.

They invite you to examine the content of their catalogue and determine for yourself how radio training at Tyler Commercial College will enable you to find your own place in one of the many interesting and profitable jobs in the vast radio industry.

TYLER COMMERCIAL COLLEGE
115 South College Tyler, Texas

APPROVED BY
 VETERANS ADMINISTRATION

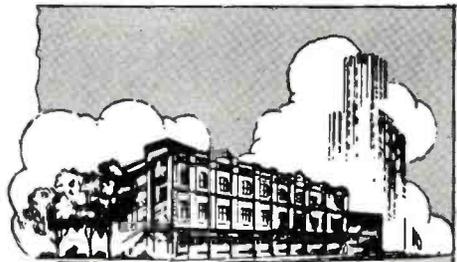

GENERAL RADIO COURSE

The course in General Radio is designed to provide a broad foundation for careers in the technical radio field. Among the various job objectives are Radiotelephone Operator (broadcast, police, or airline), Radiotelegraph Operator (marine, zone police, or airline), and Radio-Electronics Technician (industry). Success in qualifying for F.C.C. Radiotelephone or Radiotelegraph License is a requirement for graduation; therefore, an extensive study of radio theory, essential radio mathematics, and laws and regulations governing radio communications is included in preparation for operator license examinations.

Average Time to Complete Course . . .
12 Months

**RADIO MAINTENANCE
 AND REPAIR COURSE**

The Radio Maintenance and Repair Course offers preparation for a career as radio receiver repairman, sound-system technician, and radio service shop operator. Accurate, up-to-the-minute knowledge of radio principles and practice is essential for future success in this important field of radio. After a thorough introduction to radio and electrical principles, emphasis is directed to modern trouble-shooting methods, notable "signal-tracing." A section on facsimile receivers, frequency-modulation (FM) receivers and television sets is provided to bring the repairman up-to-date on recent developments. A wide range of topics is covered in this course, all of which are important to the modern repairman.

Average Time to Complete Course . . .
10 Months

Send for Free Catalogue

For full details and catalogue regarding this unique school, write to The Tyler Commercial College, Radio Department, RN, 115 South College, Tyler, Texas.

Attach this to your letter head or card.

MAIL TODAY

**A STATE APPROVED
 INSTITUTION**

GOVERNMENT SURPLUS

We have on hand a large selection of Radio and Electronic Equipment purchased from the United States Government, and solicit your inquiry on practically any equipment or component parts used by the Army or Navy. Listed below are only a few of the many items we now have in stock.

Milliammeter—0-150 MA DC, Weston Model 506 2"	\$2.95
Steatite Socket Amphenol RSS4, 4 prong.....	.12
Antenna Sections, 6 to unit, 18 ft. with insulated Mounting Bracket.....	6.50
without Mounting Bracket.....	3.00
Antenna Tuning Unit (used on Hallcrafters 400 Watt Army Transmitter). Has 15 amp RF meter Vacuum Cond., variable loading coils, etc.....	12.95
Condenser, MICA, .001 MFD—1000 V DC Aerovox type 1455—equipped with meter by-pass lugs.....	.08
Condenser, 8 MFD 2000 V. Solar oil filled 3DB8-92.....	2.50
Condenser, Electrolytic, 40 x 40 x 40 x 40 250VWVDC Mallory FP can.....	.75
Dynamotors, 12V DC, input to 1000 V DC output @ 350 MA. GE-BD-77 used with BC 191 transmitter.....	10.50
Fuse, FU-12A, ½ amp. 1000 V rating, ¾" ferrule, 3" long.....	.05
Headset, HB-33 NEW.....	2.25
Neon Bulbs, GE, ¼ W, 115 V, BAYONET base—base T 4 ¼ bulb, type NE.....	.15
Plastic transparent DISC, 6¼" dia x ¼" thick, useful as scope tube protector.....	.15
Plug, Jones (P-318AB) 18 contacts, male, chassis mount style.....	.20
Plug, PL-540.....	.15
Oil Capacitors, 1.0 MFD, 600 V Aerovox type 630.....	.30
Resistor, 12,500 ohms, 50 W, ¾" Ferrule type, Ward Leonard.....	.25
Resistor, 110 ohms, 50 W, ¾" Ferrule type, Ward Leonard.....	.20
Resistor, 1 ohm 1" Ferrule type, 200 W. Ward Leonard.....	.30
Selector Switches, Assortment of 10.....	2.00
Tuning Units for BC-375 and BC-191 contains Vernier tuning dials, variable condensers fixed cond., inductors, insulators, etc. \$50.00 worth of parts.....	3.75
Scope, 5" tube 5CP1, 115V 60 cycle Primary. Used with SCR-545 as control unit. Has 15 tubes. Power supply self contained. Easily converted for servicing, etc.....	40.00
Choke, 12H @ 150 MA, 3000 Volt Test cased and impregnated.....	1.50
Choke, 30H @ 25 MA, shielded for use with pre-amp 1500 VRMS test.....	.75
Choke, 9 H @ 300 MA, 1500 V DC cased and impregnated, 6¼ x 6¼ x 5¼.....	1.50
Cathode Ray tubes, 12DP7, NEW, electromagnetic deflection. Long persistence screen.....	12.00
Relay, overload 12 amps cont. Allen Bradley No. 810, adjustable from 6.3 to 18.1 amps complete w/dash pot oil.....	3.95
Spark plug suppressors—6 for.....	.35
Test Clip, Frankel w/point for making electrical connection, without removing insulation.....	.05
Message Holder, excellent for station logs, regular letter size 8½" x 11" with extra clip for holding spare sheets, also protective cover. Reg. Signal Corps Type.....	1.25
Jeweled lamp assembly, 1" diameter. Panel mount Candelabra screw base socket. Red Jewel.....	.35

SPECIAL \$25.00 OFFER

On a deposit of \$5.00 we will ship you C.O.D. Freight Collect a large quantity of Government Surplus Radio Items subject to your inspection and approval. If, after inspecting you are not more than satisfied, return to us Freight Collect and all it will have cost you will be freight charges one way. You should be able to dispose of a few of the items that you may not need for the entire cost. This is the cheapest way we can sell you War Surplus Radio Material. Our warehouses are filled with thousands of choice Government Surplus Radio Items. Lots of them we do not have in sufficient quantity to advertise nationally and the cost of inventorying, itemizing, corresponding, etc., would only increase their cost, therefore we make this offer. If you wish to mention a few items you desire we will endeavor to include them in this assortment.

Above Prices F.O.B. Baltimore

Minimum Order \$2.00

The ABELL DISTRIBUTING CO.
5 E. Biddle Street, Baltimore 2, Md.

Send for Our Flyer—
Name Items Interested In

Some of the paper tape machines run three or four hours. They employ regular 8 or 16 millimeter reels such as are used in movie projectors. They require more physical area for their mounting and are therefore a bit more cumbersome than the more compact disc or wire types.

We have touched but briefly on various methods for recording sound on disc, tape, wire, film, etc. Later articles will include the complete recording-playback systems for all of the above methods. Complete analysis will be given to each. There are so many means for recording and reproducing sound that we must first understand the functions of various component parts if we are to get maximum results from the systems.

Our next article will cover driving systems (cutters, embossers, etc.), their construction and characteristics.

(To be continued)

Mobile Radiotelephone

(Continued from page 47)

there is high local noise. Because of the large ratio of mobile units to fixed units, the over-all cost of service to the public is reduced by having the mobile units as small and simple as possible.

In determining the locations of the fixed land stations, field surveys are undertaken to determine propagation characteristics of the area. This is usually done by a combination of computation of field intensity over various paths and the making of actual field surveys.

Usually the land transmitter should be located at the highest available site in the vicinity of the area to be covered because of the line-of-sight propagation characteristics of very high frequencies. In general, the most suitable location for the land transmitting antenna will be on or above the roof of a centrally located building commanding a relatively unobstructed view in all directions of desired coverage. In some cities, hills may afford favorable sites; in others, a telephone central office or a midtown office building may be desirable to afford a high signal intensity where radio frequency noise is the highest. Here multiple-path transmission results from reflection and diffraction effects, causing signal field intensity to vary over a wide range within short distances. If the general level of signal intensity is relatively high, these variations are not very disturbing.

"Shadows," within which the signal intensity is considerably attenuated, may be cast by high buildings in the service area, and this effect is particularly marked on the far side of buildings near the transmitting antenna. In nearby "shadows," the high signal fields near the transmitter serve to offset the high attenuation enough to make the signal satisfactory, and the "shadow" area of high buildings a mile or more away from the transmitting antenna will be smaller and tend to

fill in as distance beyond the interfering building increases. Increasing the height of the transmitting antenna often reduces this "shadow" effect.

In the case of land station receiving sites, the foregoing also applies. Another important problem is local radio frequency noise. The principal sources of noise at frequencies used in this service are man-made, such as electrical machinery, diathermy apparatus, etc. Thus locations should be selected where such interference is at a minimum.

The control terminal is usually located in a telephone building where a toll switchboard and toll power supplies are available.

The coverage of an area in a given direction is considered sufficient if the average signal-to-noise ratio is approximately 17 db. This ratio is determined from two measurements. The measurement of the magnitude of the signal is made with the transmitter fully modulated with a 1000-c.p.s. tone; the noise measurement is made with the transmitter on, but not modulated. The difference in signal and noise measurements in db. is the signal-to-noise ratio. These measurements may be made with the *Western Electric 2B Noise Measuring Set*.

Coverage measurements must take into account radiated power, distance from transmitting antenna, effective height of both transmitting antenna and receiving antenna, local noise, type of intervening terrain, and objects in the optical line of sight between the transmitting antenna and receiving antenna. Profiles of the terrain, drawn to take into account the curvature of the earth, are used in computations of coverage.

In the selection of land receiver sites, all of the above mentioned problems apply. The receivers, and particularly their antennas, should be located well away from noise-generating devices. In some cases it may even be desirable to locate one of the land receivers at or near the land transmitter. In the absence of actual measurements, the noise conditions may be estimated by grouping into four classes:

A. *Very low noise*—outlying residential area, light traffic; B. *Moderate noise*—residential area, moderate traffic; C. *High noise*—residential area or business district, heavy traffic; and D. *Very high noise*—business or industrial area, heavy traffic.

Measurements have indicated the radiated power necessary for sufficient signal-to-noise ratio at various distances under varying noise conditions and with various effective antenna heights. For example; with an antenna height above the effective ground plane of approximately 200 feet, range to be expected with 100 watts of radiated power at a frequency of 160 mc. over smooth earth under varying noise conditions is: A. Very low noise, approximately 30 miles; B. Moderate noise, approximately 25 miles; C. High noise, approximately 17

(Continued on page 113)

**SINCE
1895**


THORDARSON

**THE OLDEST MANUFACTURER OF QUALITY
TRANSFORMER EQUIPMENT IN THE UNITED STATES**

For well over fifty years Thordarson has been turning out the finest in amateur and industrial transformer equipment. Founded in 1895 by Chester Thordarson, designer of the first amateur transmitting transformer, this company has pioneered many new developments, including the superior coil and core materials now used in its entire line. Describing quality transformers for every ham requirement, the Thordarson catalog is still regarded as the "bible" of the radio amateur.

In the industrial field, Thordarson was first to design and build transformers for specific applications. To this day, when there is a question of correct transformer design, Thordarson is usually consulted first. Thordarson Amplifiers, a logical outgrowth of this vast transformer manufacturing experience, are regarded by experts as the finest in present-day sound equipment.

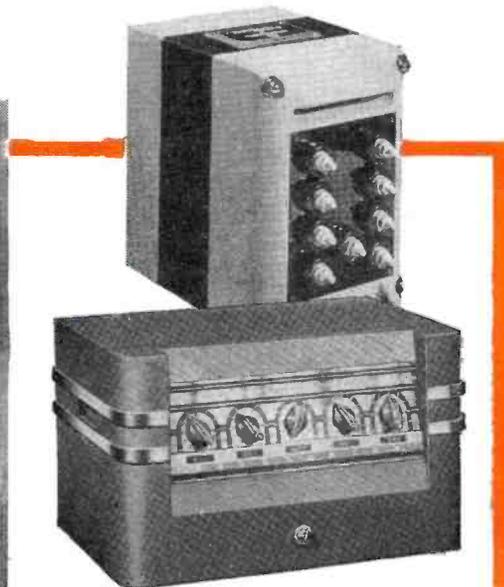In the future, as in the past, Thordarson Transformers and Amplifiers will continue to be manufactured to the same high standards, which have distinguished their production from the beginning. When you specify Thordarson you will always be sure of obtaining a product which is as perfect as a half century of electronic manufacturing experience can make it.



Thordarson Transformers and Amplifiers are designed for every electronic application

THORDARSON

**ELECTRONIC
DISTRIBUTOR AND INDUSTRIAL SALES DEPARTMENT
MAGUIRE INDUSTRIES, INC. 936 NORTH MICHIGAN AVENUE
CHICAGO 11, ILLINOIS**

**EXPORT SALES DIVISION • SCHEEL INTERNATIONAL INCORPORATED
4237-39 N. LINCOLN AVENUE, CHICAGO 18, ILL. CABLE ADDRESS HARSHEEL**




ESSE Specials!



C-1 AUTO PILOT AMPLIFIER

Used to control the operation of the Servo Units causing them to move the control surfaces of the airplane in one direction or the other in response to the signals received. The complete amp. includes one rect. 7Y4, three 7F7's for amplification and control, three 7N7's for signal discrimination, one power transformer, six relays, four control pots, chokes, condensers etc. Convert for use on radio controlled models, doors etc. Operates from 24 V. DC. Size 9 1/4" x 6 1/4" x 7 3/4". Complete with tubes as described.


Price.....\$9.95

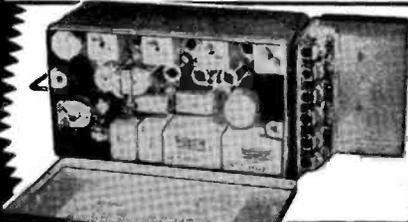

R-89/ARN 5A GLIDE PATH RECEIVER

Formerly used for blind landing but adaptable to many other uses such as receiver for new police or citizen's band. Band of operation 326-335 mc. on any of three pre-determined crystal controlled frequencies. Contains eleven tubes, 6 relays and other valuable parts. For 24 V. DC operation. Size 13 3/4" x 5 1/4" x 6 3/4"


Price, complete as shown.....\$12.45

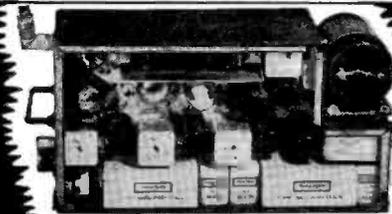

LOCALIZER RECEIVER BC-733-D

A part of aircraft blind landing equipment manufactured by WE. Operates on any six of its predetermined crystal controlled frequencies in the range of 108-120 mc. Contains 10 tubes, three of which are WE 717-A's — and crystals. Ideal receiver for conversion to 144 mc. ham band or mobile telephone bands. For 24 V. DC operation. Size 14 1/2" x 7" x 4 9/16". Complete with tubes.

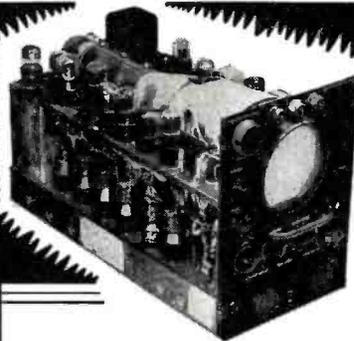Price, complete with dynamotor.....\$12.45



APN-4 RADAR SCOPE

Ideal for conversion to service scope or salvage for parts. Contains 27 tubes such as 6SN7GT, 6H6GT, 6SL7GT, 6SJ7GT and 5CP1 scope tube. 22 pots, switches, condensers, transformers etc. In aluminum case, approx. size 9" x 12" x 18".

Price.....\$17.95 ea.



AIRCRAFT RADIO RANGE FILTER FL-8-A

For helpful reduction of QRM on crowded CW bands. When attached to output of any communications receiver:

- 1 — Will pass signal of 1020 CPS, eliminating others.
- 2 — Will pass voice frequencies and eliminate 1020 CPS code signal.

Compact, light weight, with switch. Size 2 3/4" x 2 3/4" x 3 3/4".


Price.....\$2.25 ea.

Unless otherwise noted this merchandise was removed from surplus aircraft and is sold as used.

MARKER BEACON RECEIVER

Ideal for controlling remote circuits for model aircraft, boats, etc. Operates from 75 mc. Signal easily altered to 2 meter band. Tubes used and included: 1—6SH7, 1—6SL7GT, 1—12SN7GT. Also sensitive relay. Circuit diagram included inside case. Size 5 3/4" x 3 3/4" x 5 1/4". For 24 V. DC operation. Complete as shown.

Price.....\$3.95

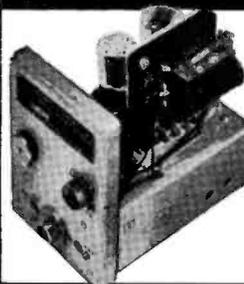

RECTIFIER UNIT RA-63-A


Charges 12V. batteries at 5 amp. rate hi charge or 2 amp. trickle. Easily converted to use as 6V. charger or battery eliminator for auto radio servicing in your shop. Sturdily built dry plate rectifier protected by overload circuit breaker. These units removed from famous SCR-299. Used but in good condition.

Price.....\$14.85 ea.

INTERVALOMETER

Electronic timing device for releasing bombs at preset intervals. Ideal for dark room timer, model train controller, etc. Contains relays, switches, pilot light, resistors, knobs, etc. Approximate weight, 7 lbs.


Price.....\$3.95 ea

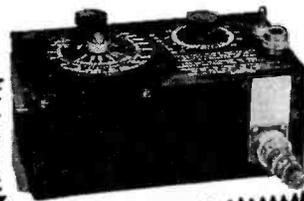

On orders less than \$10.00 allow additional charge of 25¢ to cover handling.




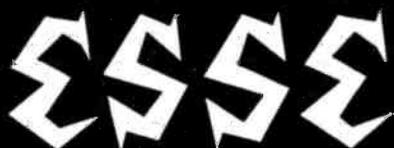TERMS:
CASH with ORDER
or 25%
BALANCE C.O.D.
All Items
Shipped Collect



Radio Company
130 W. New York St. - Indianapolis 4, Ind.



ESSE Specials!

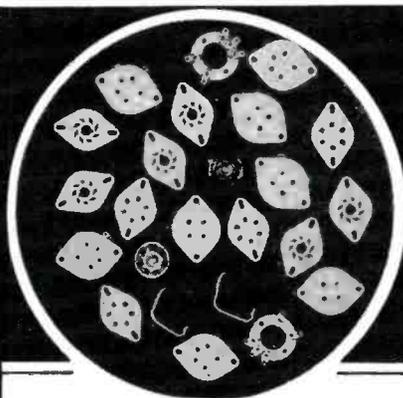

KIT — 24 TUBE SOCKETS

Containing the following new Ceramic 10-loss sockets: 2-Acorn, 6 octal Amphenol, 4-6 prong Millen, 4-5 prong wafer, 4-4 prong wafer, 2 molded bakelite, 2 octal female plugs and 2-7 prong tube tester sockets with center socket for checking pilot lamps.

Price, complete kit.....\$1.95

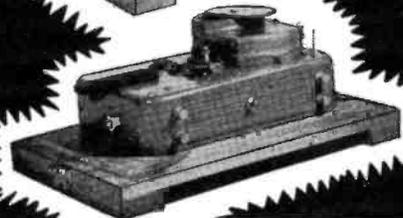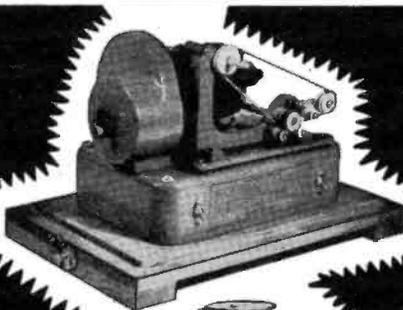

MC ELROY CODE EQUIPMENT BRAND NEW

A proud addition to any Ham Shack. Use it to ink paper tape for high speed sending or receiving, or convert to other uses. Original price several times this low price. Shipped as shown in individual wood carrying case. Tubes used: 1-1117Z6; 2-117P7—not included.


Price for both.....New.....\$50.00
Used.....\$35.00



SIGNAL CORPS TIME INTERVAL UNIT ML-138

This unit is housed in a sturdy metal case, 7½"x6"x5¼" with hinged top. Includes necessary adjustment tools. Powerful clock mechanism runs several days. Audio Tone, controlled by relay, is emitted for several seconds once every few minutes. Two flashlight cells needed. Has many possibilities for Radiomen or Model Makers. Parts alone are worth more than our price.


Price.....\$4.95 ea.

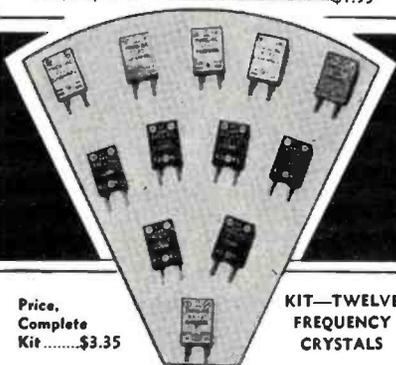

Price, Complete Kit.....\$3.35

KIT—TWELVE FREQUENCY CRYSTALS

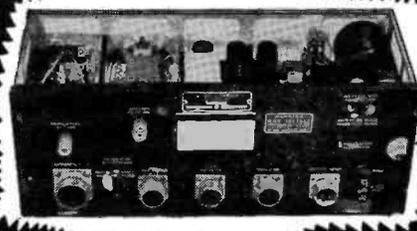
Contains assorted frequencies between 3,000 Kc. and 8,000 Kc. in FT 243 crystal holders. We pick at random from mixed supply and cannot select frequencies.



RADIO ALTIMETER APN/1

A complete 460 mc. radio receiver and transmitter which can be converted for ham or commercial use. Tubes used and included: 4-12SH7, 3-12SJ7, 2-6H6, 1-VR150, 2-955, 2-9004. Other components such as relays, 24V. dynamotor, transformers, pots, condensers, etc. make this a buy on which you can not go wrong. Complete as shown in aluminum case 18"x7"x7¼".

Price.....\$14.95

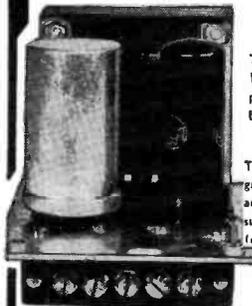


BC-348 POWER SUPPLY

To convert the BC-348 receiver for 110 V. AC operation. Constructed especially for the Esse Radio Company by a leading transformer company.

These power supplies have gained great popularity due to quality, price and simplicity in conversion. Filament supply 24V. Rectifier tube used: 6X5 (not included).

Price.....\$8.95 ea.

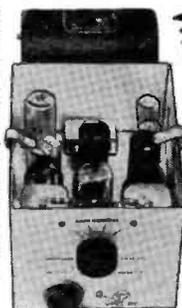

INTERPHONE AMPLIFIER AM-26/AIC

Convert to high fidelity phone amp. or speech amp. Case size 9¼"x4¼"x5½". Tubes used and included: 2—125J5GT, 2—12A6. Complete with dynamotor as shown, for 24 V. DC operation.

Price.....\$4.85 ea.

Unless otherwise noted this merchandise was removed from surplus aircraft and is sold as used.

On orders less than \$10.00 allow additional charge of 25¢ to cover handling.



Radio Company
130 W. New York St. - Indianapolis 4, Ind.



ESSE Specials!

ATTENTION PROSPECTORS, MINERS, OIL COMPANIES PLUMBERS ETC. BELOW IS THE FINEST METAL DETECTING MINE DETECTOR EVER BUILT
On orders less than \$10.00 allow additional charge of 25c to cover handling.

SCR-625 MINE DETECTOR - BRAND NEW Metallic Objects Only

Used by the Army to detect buried metallic mines. Its private use suggests the location of underground or underwater pipes, cables and ore bearing rock, the location of metallic fragments in scrap materials, logs, etc. and the screening of personnel in plants for carrying of metallic objects.

The unit consists of a balanced inductance bridge, a two-tube amp. and a 1,000 cycle oscillator. The presence of metal disturbs the bridge balance, resulting in a volume change of the 1,000 cycle tone. The tubes used are low battery drain types such as 1G6 and 1N5. The circuit may be modified for control of warning signals, stopping of machinery etc. when metal is detected. Operates from two flash light batteries and 103 V. "B". However, a power supply operating from 110 V. may be used. Comes complete with spare tubes, spare resonator and instruction manual — in wooden chest 8 1/4" x 28 1/4" x 16". Weight in operation is 15 lbs. New, complete in original overseas packing container. Originally sold by War Assets for \$166.00.

The U. S. Forestry Service has recommended procedure for using the SCR-625 Mine Detector to find concealed metal in tree logs and other timber products.


Price.....\$79.50 ea.



GASOLINE GENERATOR— 27.5 V. DC — 70 AMP.

Electrical starting when connected to 24 V. battery. Ideal for power for emergency, cabins, aircraft, welding etc. These units were used for auxiliary power on bombers.

Price, used.....\$72.50

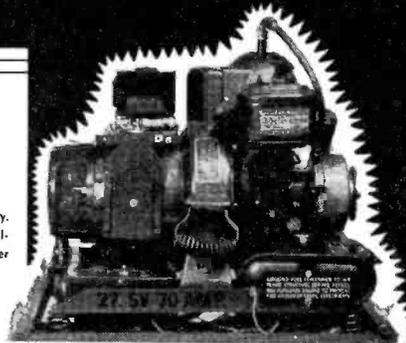

MOTOROLA POLICE TRANSMITTER AND RECEIVER—AM


An ideal unit to convert from its original 9 meter freq. to the 10 meter amateur band for mobile work. Complete with antenna relay, high voltage vibrator supply for both receiver and transmitter and most all tubes. These units were used by Army Military Police and are sold as received. Condition is good except for occasional missing tubes.

Price, Complete as shown, used.....\$65.00

LINK FM POLICE TRANSMITTER AND RECEIVER (Not Shown)

Received in same purchase as above equipment. For 27-38 mc. operation. Complete ready to operate.


Price per set, used.....\$65.00

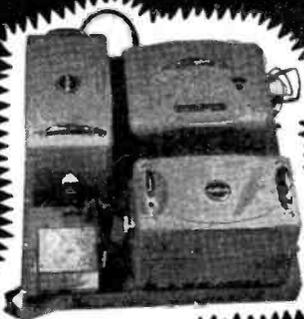

MINE DETECTOR AN/PRS-1 BRAND NEW

For detection of metallic and non-metallic objects. Used to locate buried pipe, cables, sewer tile etc. The unit is a UHF transmitter and indicates objects by deflection of the microammeter either to left or right depending upon whether metallic or non-metallic. Audio indication is also given by a change in volume of 1,000 cycle tone. Ready to operate with addition of 1-6 V. and 3-45 V. batteries. Comes complete with spare tubes, antennae, reflectors and instruction book — in wooden chest 9 1/2" x 28 1/4" x 15 1/2". Weight, in operation 22 lbs. Shipped new in original overseas moisture proof container.

Price.....\$14.95 ea.

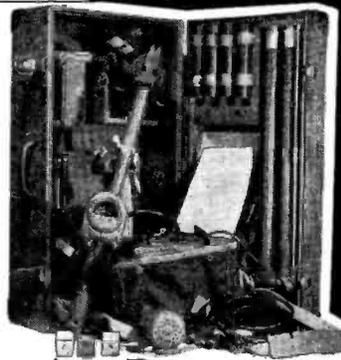

TERMS:
CASH with ORDER
or 25%
BALANCE C.O.D.
All Items
Shipped Collect

ESSE

Radio Company

130 W. New York St. Indianapolis 4, Ind.

miles; and *D.* Very high noise, approximately 10 miles.

The range increases, of course, with greater radiated power and with greater effective antenna height.

Highway service presents many similar problems. Since there is a marked difference in transmission at 40 mc. over good soil and poor soil, soil conditions must be carefully considered. Poor soil for radio transmission purposes is soil of relatively low conductivity and dielectric constant such as that consisting largely of rocks, gravel, or sand. Good soil from an engineering standpoint is soil of high conductivity and dielectric constant such as clay, loam, marsh or swamp land.

Heavy duty generating equipment is necessary for a vehicle equipped for highway mobile radiotelephone service. A storage battery of greater capacity will also be required. The choice of proper generating equipment depends upon the number of hours the vehicle is driven per day, the average speed at which it is driven, the number and duration of telephone calls per day.

There are also problems associated with the choice of closely coupled antennas or with use of a common antenna for transmission and reception.

In the case of closely coupled antennas involving a land transmitter and a land receiver, three primary conditions should be met:

1. The output of the transmitter

should not overload the r.f. stages of the receiver.


2. No spurious radiation from the transmitter should fall in the same channel as the fundamental response of the receiver.

3. The fundamental radiation from the transmitter should not occur at the same frequency as any spurious response of the receiver.

To meet condition 1, it must be remembered that the first r.f. stage is not very selective compared to the performance of the entire receiver. The tube may draw grid current when the input level is about 10 dbm., causing limiting in the stage with resulting noise and distortion. Since the output of a 250 watt transmitter is 54 dbm., a minimum loss of $54 - 10 = 44$ db. must be provided and to give considerable margin, this loss requirement is increased to 60 db. The loss may be provided by antenna separation, filters, or a combination of both.

If L is the transmission loss introduced, $L = L_1 - L_2$, where L_1 is loss introduced at the interfering frequency and L_2 is the accompanying loss at the operating frequency. Wave traps built of $\frac{1}{8}$ -inch coaxial transmission line and installed in the receiver lead would introduce approximate losses of $L_1 = 46$ db. and $L_2 = .04$ db. in the highway service, and $L_1 = 52$ db. $L_2 = .02$ db. in the urban service.

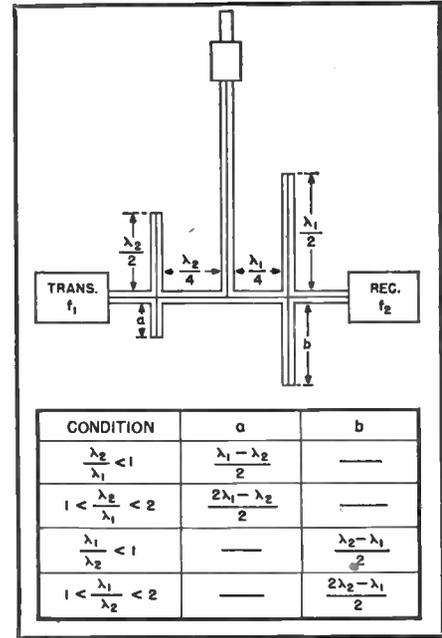The diagram, Fig. 1, shows a method of installing wave traps in the trans-



Courtesy of Bell Telephone Labs., Inc.

Fig. 1. Stub arrangement for reducing interference when one antenna is used for continuous operation of transmitter at frequency f_1 and receiver at frequency f_2 .

mission lines connecting a transmitter and a receiver to the same antenna. The wave trap in the transmitter lead is required only at very quiet locations. It prevents any portion of the incoming signal from being diverted from the receiver to the transmitter.

Fahnestock Clips

RADIO'S GREATEST CONVENIENCE

FAHNESTOCK SPRING BINDING POST GRIPS THE WIRE BY THE ACTION OF A SPRING

No tools required to make the connection. Grips the wire with just the right pressure for good electrical contact. Simply press down, insert the wire and let go. Does not injure wire, hence connection can be made or opened as often as desired. Available in large variety of types and sizes to fit any radio purpose and any requirement as to position, space or method of attachment. You will find them in the better sets.

Positive contact; cannot jar loose. Brass or bronze—nonrusting.

FAHNESTOCK ELECTRIC COMPANY, Inc.



46-44 ELEVENTH STREET
LONG ISLAND CITY 1, N. Y.

Dept. 12

Please send us at once, Descriptive Literature, Prices and Delivery Schedule on

FAHNESTOCK CLIPS

For
Name
Address
City State

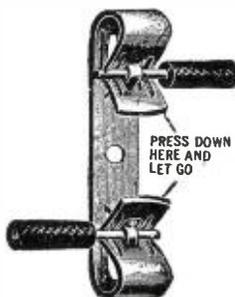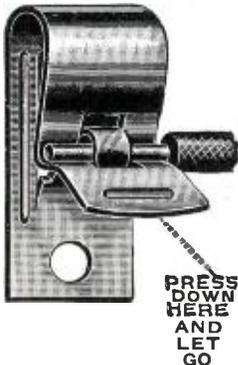



- ★ HS23U Telephone Handsets with Push-to-Talk Switch, \$3.95
- ★ Surplus Cornell-Dubilier Type TJ 1MFD 5000-volt Oil Cond., \$4.95
- ★ Surplus Cornell-Dubilier Type TLA 2MFD 1000-volt Oil Cond., \$1.29
- ★ Kit Kraft Crystal Set Kits, \$1.19
- ★ 9ft. AC Extension Cord with 2-way Table Tap, 42c
- ★ 1/2 Meg. Pot's 1 1/2" shaft with Switch 69c, 10 for \$5.90
- ★ SPST Toggle Switches, 24c
- ★ New JAN 807 Tubes, Boxed, Guaranteed, 2 for \$2.25
- ★ 25 MF 25-volt Tubular Electrolytics, 19c
- ★ 3.5 Watt AC-DC Amplifier Kit: Mic and Phono Input complete with tubes, \$10.95
- ★ Record Player Kit, complete with Alliance Motor, Cabinet, and Astatic Crystal Pickup, \$10.95
- ★ New Meissner Signal Shifter, \$120.00
- ★ Meissner 2-band 6-tube AC-DC Receiver Kit complete with Tubes, \$25.20
- ★ 4-Prong Universal Vibrators, \$1.69
- ★ New JAN 809 Tubes, Boxed, Guaranteed, \$1.79
- ★ New JAN 816 Tubes, Boxed, Guaranteed, 79c
- ★ .01 MFD 600-volt Oil Tubular Condensers, 15c
- ★ .5 MFD 100-volt Paper Tubular Condensers, 15c
- ★ .05 MFD 400-volt Paper Tubular Condensers, 12c
- ★ .02 MFD 400-volt Paper Tubular Condensers, 7c
- ★ .1 MFD 200-volt Paper Tubular Condensers, 9c
- ★ Heavy Duty Phono Motor, Famous Make, Rim Drive, with 10" Turntable, \$4.95

More than
150
LEADING LINES
in our complete
stocks. Latest
technical data
promptly supplied
on request.

UNIVERSAL
RADIO SUPPLY CO.

1404-06 VENICE BOULEVARD
LOS ANGELES 6, CALIF.

HIGHWAY SERVICE	
Land Station Transmitters	12 channels, .04 mc. apart and lying between 35.22 and 35.66 mc.
Mobile Transmitters	12 channels, .04 mc. apart and lying between 43.22 and 43.66 mc.
URBAN SERVICE	
Land Station Transmitters	12 channels, .06 mc. apart and lying between 152.03 and 152.69 mc.
Mobile Transmitters	12 channels, .06 mc. apart and lying between 157.29 and 157.95 mc.

Table 2. Frequency allocations for mobile radiotelephone service.

This is not a serious consideration at locations where set noise is not controlling. The wave trap in the receiver lead is always important, for it allows most of the transmitted signals to be radiated. Two or more wave traps may be installed in the receiver lead at half wavelength (at transmitter frequency) spacing, providing approximately the same suppression from each additional wave trap as obtained with the first. Sufficient loss may be provided with one filter and two should be more than sufficient.

If conditions 2 and 3 are met, the equipment design characteristics provide that an interfering transmitter signal will be at least 70 db. below the desired signal at the first limiter grid. Additional suppression of an interfering signal can be obtained by antenna decoupling or by the use of filters. For interference-free operation, the magnitude of the interfering signal should always be at least 70 db. + L below the desired signal at the first limiter grid of the receiver, and L should be approximately 100 db.

A subsidiary problem is to choose transmitter and receiver frequencies so that no spurious radiation from the transmitter occurs at the same frequency as any spurious radiation of the receiver or in the channels immediately adjacent to the fundamental response of the receiver.


For highway service, the receiving antenna will discriminate somewhat against the transmitter frequency since it will be adjusted in length to be more receptive at the receiver frequency. In the urban service, however, frequency separation relative to the operating frequency is so small for the two directions of transmission that the same antenna dimensions are used at the receiving site as at the transmitting site.

Another problem is to keep the radiation of spurious cross-modulation within tolerable limits during simultaneous operation of two transmitters operating into nearby antennas.

When appreciable r.f. voltages from one transmitter are impressed across the output tank circuit of another, spurious signals are generated because of the non-linear characteristics of the class "C" final amplifier circuits used in the transmitters. The problem of reducing materially the strength of the signal of one transmitter reach-

Sigmon's - WEST VIRGINIA'S
LARGEST RADIO SUPPLY HOUSE!

AMPLIFIER for GUITAR OR PHONO

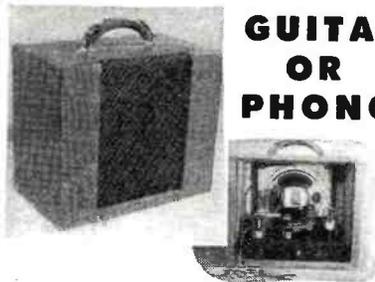

- ★ TUBES 6S5, 6J5 6L6, 5V4G
 - ★ 4 Tubes—Hi Gain
 - ★ Two Microphone or Instrument Inputs
 - ★ Phone Input
 - ★ 6 1/2 Watts—Beam Power
 - ★ Solid Wood Cabinet
 - ★ Aeroplane Cloth Covered
 - ★ Tone Control
 - ★ Heavy Duty 8" Speaker
 - ★ Complete with Tubes
- Complete with Tubes—List \$59.50 **Your Cost \$37.00**

VMI BRUSH CONTROL MIKE—Net \$10.40
MM TURNER CONTACT MIKE—Net \$ 9.45

PHONO AMPLIFIER

3 Tube AC-DC
Uses: 50L6, 35Z5, 12SR7,
and 450 ohm speaker
Net \$5.97



FOR LATEST CATALOG WRITE TO...

Sigmon's
RADIO SUPPLY

CHARLESTON, W. VA.

Carry 3000 RADIO FACTS IN YOUR POCKET!



RADIOMAN'S HANDBOOK

Helps You On the Job!

The handiest radio reference book on the market... a library of 3,000 facts, wiring diagrams, formulas, charts, tables, rules—condensed into one pocket-size 4 1/2" x 7" volume. Take it with you on the job—have the answers to daily problems always on hand. Saves time—helps you earn more. Flexible leatherette cover withstands hard usage. Get this book on free trial now!

350 PAGES
Circuits
Reactances and Energy Losses
Coils & Winding
Meters and Measurements
Resonance and Coupling
... and thousands of other facts!

SEE IT FREE

GET THIS BOOK FREE! FOR 7 DAYS FREE!

TRY IT ON THE JOB—see how often you refer to it—how much time it saves you. Then, if you are not satisfied, return it to us. If you keep the book, AFTER 7 days, you pay only \$2.75.

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
500 S. Paulina Street, Dept. 57-T3, Chicago 12, Ill.

FREE TRIAL COUPON

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. 57-T3
500 S. Paulina Street, Chicago 12, Ill.
Please send Radioman's Handbook on 7 days FREE TRIAL. If satisfied after 7 days, I will pay you \$2.75—if not, I will return book to you.

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

CHECK here if you want to pay postman \$2.75 on delivery. Same 7 days' trial arrangement and money-back guarantee.

Never so much radio for so little money —

\$10⁹⁵

Including Tubes
Postpaid in U. S. A.

**SUPER-HETERODYNE
FOUR TUBES and
SELENIUM RECTIFIER
110 Volt AC-DC KITS**

**direct from factory
to you —**

Never before has BELLTONE packed so much quality and value in a \$10.95 complete package. This four tube and selenium rectifier super-het kit of parts (chassis 10 1/2" x 5 1/2" x 7") has proven its selectivity, sensitivity and high quality radio reproduction in tens and tens of thousands of receivers sold during the past months. Today you can have this same chassis with all


post-war improvements at virtually cost of component parts, drawings, instructions, packing and mailing costs —complete except for cabinet, wire and solder.

**three big assembly and
hook-up prints and
ABC detailed instructions
supplied**

including schematic circuit, picture wiring diagram, top chassis layout, dial cord instructions and cabinet layout suggestion—makes assembly, wiring and final adjustments easy, instructive and foolproof.

**direct from factory to you
only — no sales to jobbers,
dealers or surplus outlets**

no cabinet, wire or solder supplied

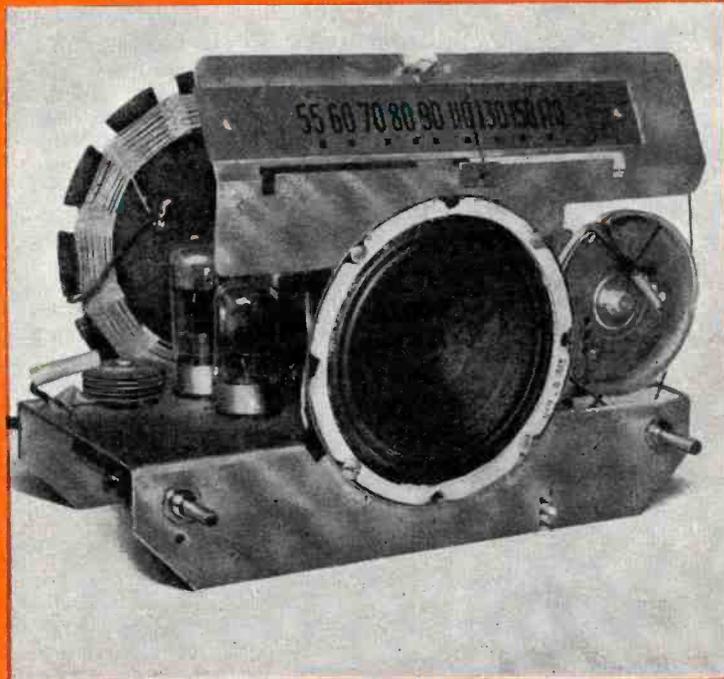

circuit improvements and parts include —

1. **SELENIUM RECTIFIER** — eliminates troublesome rectifier tube—it's unbreakable—lasts the lifetime of your set—starts instantly—increases sensitivity.
2. **PROTECTIVE FILAMENT RESISTOR**—prevents current surge through filaments—eliminates tube burn-outs and increases tube life.
3. **ALNICO PM SPEAKER**—1.47 ounce 5 inch speaker for high quality voice and music reception.
4. **GRIP-STRAIN RELIEF**—securely anchors power line cord to chassis—preventing short circuits.
5. **TUBES SUPPLIED**—one each 12SA7 - 12SK7 - 12SQ7 and 50L6.

**ORDER YOUR BELLTONE
SUPER-HET CHASSIS KIT--TODAY
SHIPPED BY RETURN MAIL**

BELLTONE RADIO and TELEVISION CORP.

583 Ave. of the Americas, New York 11, N. Y.

Yes, I want.....BELLTONE chassis kits. Enclosed find

money order check for \$.....

SHIP TO.....

STREET..... CITY..... STATE.....

GET YOUR HAT!



Get your hat . . . follow the crowds to Hallicrafters booth at the parts show. Get the details on Hallicrafters advanced developments in high frequency, short wave communications equipment. Hear all about the Gatti-Hallicrafters spectacular radio-equipped expedition to the Mountains of the Moon. This scientific safari, based on Hallicrafters-built mobile radio equipment, will spread the name and fame of "the radio man's radio" around the world. All the dope on this exciting adventure at Hallicrafters show headquarters.

hit the trail!



hallicrafters EXHIBIT BOOTH 86




hallicrafters

THE HALLICRAFTERS CO., MANUFACTURERS OF RADIO AND ELECTRONIC EQUIPMENT, CHICAGO 16, U. S. A.

ing the tank circuit of the other transmitter by way of the antenna coupling becomes of great importance. The use of a filter between each transmitter output and its associated antenna feed line with the series elements of each filter resonant at the operating frequency of the transmitter with which it is associated and the shunt elements of each filter resonant at the operating frequency of the interfering transmitter is the obvious solution. However, because of the small ratio of frequency separation over the operating frequency as it is possible to obtain in the urban band, it is extremely difficult to build a filter which will discriminate against the interfering frequency without prejudicing the operating frequency. In the highway band, physical size of these coaxial filters is somewhat unwieldy, a quarter wavelength section being about six feet. If it is necessary to locate two transmitters in close proximity, it may be desirable to place the transmitter frequencies either as close together as possible or as far apart as possible. If the two frequencies are close together, the difference frequency is small, and all cross-modulation products will be grouped closely around the assigned frequencies. If the frequency difference is large, it is unlikely that the antennas will radiate any of the spurious frequencies developed. Fig. 2 shows filters designed to reduce interference between nearby transmitting antennas.

With the superheterodyne type of receiver, the harmonics of the local oscillator in one receiver may reach a nearby receiver through the coupling of the antenna connected to the two receivers. Measurements on receivers to be used in the mobile service show that the order of magnitude of the spurious output is low enough so that it is not expected to cause interference

Fig. 2. Stub arrangement for reducing interference between transmitting antennas operating in nearby and adjacent areas. Courtesy of Bell Telephone Labs., Inc.

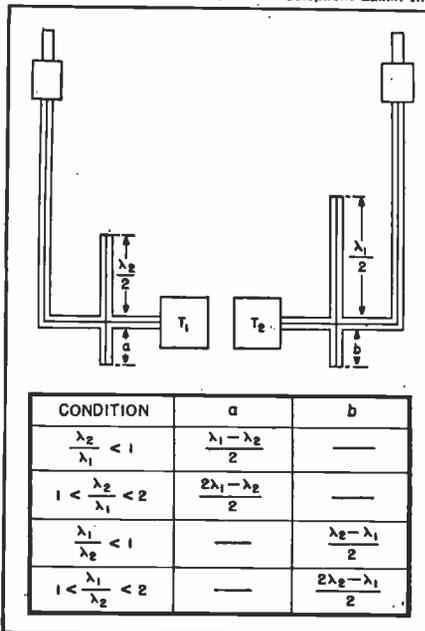

RAPIDDRIVER

The New Screwdriver That Is **FASTER — EASIER**



- EASY TO USE
Works with circular wrist motion
- NO MORE TWISTING — NO MORE PINCHING OF PALM
- INCREASED DRIVING POWER
- FASTER THAN ANY HAND SCREWDRIVER MADE
Cuts working time in half

SPECIFICATIONS
 1/4" Tool Steel Shank
 Lightweight Anodized Aluminum Handle
 Special Grease-Packed Bearing
 Overall Length—10 3/4"

Pat. Applied For
 RAPIDDRIVER also available for Phillip type head screws and for nut sockets — will clutch Phillip type head screws regardless of tolerance variation.

RAPIDDRIVER has been tested and is now extensively used in many large industrial and radio plants where efficiency and speed are vital factors of operation.

Individually Mounted on Display Card
 Retail Price **\$1.25**

Stop in and see us when in Chicago for the Show! National Radio Parts & Equipment Show, May 11 to May 16, Stevens Hotel, Chicago

DEALERS: Get special dealer prices direct from manufacturer.

SCHUH & HARPER

1251 Loyola Ave.

Chicago 26, Ill.



RADIO DEALERS • JOBBERS WHOLESALEERS • MANUFACTURERS PURCHASING AGENTS QUANTITY BUYERS

Don't miss the BIG show at Radio Bargain Headquarters—the MID-AMERICA COMPANY! See thousands upon thousands of square feet jammed to the ceiling with big buys in radio parts and electronic equipment . . . everything, including standard lines and nationally-known brands. Two convenient locations—both just a few minutes by auto, trolley or taxi from the Stevens Hotel. Open 8 AM to 5 PM daily. And if you can't attend the show, be sure to send your name and address for MID-AMERICA's big, FREE catalog that lists, describes and illustrates hundreds and hundreds of big buys! And get MID-AMERICA's timely, monthly bulletins that bring you the latest, greatest values in radio parts and electronic equipment. Address Desk E-57


MID-AMERICA CO. Inc.
 STORE 2412 S. MICHIGAN AVE. CHICAGO 16, ILL.
 WAREHOUSE 2307 S. ARCHER AVE. CHICAGO 16, ILL.

TEST EQUIPMENT for IMMEDIATE DELIVERY

TELEVISION—FM—RADIO KITS

TELEVISION KIT

BUILD YOUR OWN TELEVISION RECEIVER

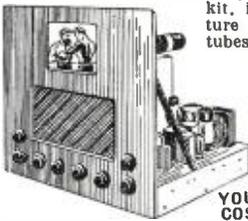

All parts included in the kit, including a 7" picture tube and 20 other tubes. Set pre-tuned for any of three Channels. Special antenna with 5 ft. upright aluminum mast and low loss lead in cable.

YOUR COST \$158⁵⁰


6 TUBE AC-DC SUPER HET



Complete including attractive Walnut cabinet with slide rule dial. Built in antenna. All major parts mounted. Uses 2—12SK7's, 1—12SQ7, 1—12SA7, 1—35Z5, 1—35L6. Schematic diagram furnished with each kit.

YOUR COST \$19⁹⁵ Including Tubes Less Wire and Solder

5 TUBE AC 2-BAND

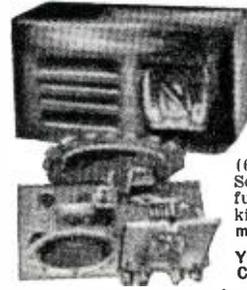

Complete with attractive Walnut cabinet and Air-plane dial. Uses 1—6SA7, 1—6SK7, 1—6SQ7, 1—5Y3. Covers standard Broadcast (540 K to 1700 KC and Short Wave band (6MC to 18 MC). Schematic diagram furnished with each kit. Major parts mounted.

YOUR COST \$25⁵⁰ Including Tubes Less Wire and Solder

9 TUBE FM KIT


Complete with 29" single dipole antenna, less transmission line. Covers New FM band. Includes amplifier and 9 tubes. Easy to build—all you need is soldering iron, wire and solder. Pictorial and Schematic diagram furnished with each kit. All standard parts.

YOUR COST \$48⁹⁵ Including Tubes Less Wire and Solder

5 TUBE Super Het RADIO KIT

Complete including attractive Bakelite cabinet. All major parts mounted. Uses 1—50L6, 1—35Z5, 1—12SA7, 1—12SK7. Pictorial diagram furnished with each kit.

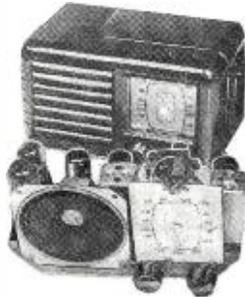YOUR COST \$15⁹⁵ Including Tubes Less Wire and Solder



The New Model 450 TUBE TESTER

Speedy operation—assured by newly designed rotary selector switch which replaces the usual snap, toggle, or lever action switches.

SPECIFICATIONS:

- Tests all tubes up to 117 volts.
 - Tests shorts and leakages up to 3 Megohms in all tubes.
 - Tests both plates in rectifiers.
 - New type line voltage adjuster.
 - Tests individual sections such as diodes, triodes, pentodes, etc., in multi-purpose tubes.
 - Noise-Test—detects microphonic tubes or noise due to faulty elements and loose internal connections.
 - Uses a 4 1/2" square rugged meter.
 - Works on 90 to 125 volts 60 cycles A.C.
- EXTRA SERVICE—May be used as an extremely sensitive condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute. **\$39⁵⁰**



The New Model 670 SUPER METER

A Combination VOLT-OHM MILLIAMMETER plus CAPACITY REACTANCE, INDUCTANCE and DECIBEL MEASUREMENTS

SPECIFICATIONS

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts
 A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
 OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
 D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5 Amperes
 RESISTANCE: 0 to 500/100,000 ohms 0 to 10 Megohms
 CAPACITY: .001 to .2 Mfd. .1 to 4 Mfd. (Quality test for electrolytics)
 REACTANCE: 700 to 27,000 ohms 13,000 Ohms to 3 Megohms
 INDUCTANCE: 1.75 to 70 Henries 35 to 8,000 Henries
 DECIBELS: -10 to +18, +10 to +38, +30 to +58
 The Model 670 comes housed in a rugged, crackle-finished steel cabinet complete with test leads and operating instructions. Size 5 1/2" x 7 1/2" x 3" **NET \$28⁴⁰**

The New Model 600 SET TESTER

A NEW COMBINATION TUBE TESTER AND MULTI-METER

A complete testing laboratory all in one unit. Test tubes. Reads A.C. Volts, D.C. Volts, D.C. Currents, Resistances and Decibels.

- TUBE TESTER SPECIFICATIONS:**
- Speedy operation—assured by newly designed rotary selector switch.
 - Tests all tubes up to 117 Volts.
 - Tests shorts and leakages up to 3 Megohms in all tubes.
 - Tests leakages and shorts of any one element against all elements in all tubes.
 - Tests both plates in rectifiers.
 - Tests individual sections such as diodes, triodes, pentodes, etc., in multi-purpose tubes.
 - New type line voltage adjuster.
- MULTI-METER SPECIFICATIONS:**
- D.C. VOLTS: (At 1,000 Ohms Per Volt) 0 to 7.5/15/75/150/750/1,500 Volts.
 - A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts.
 - D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5 Amperes.
 - RESISTANCE: 0 to 2,000/20,000/200,000 Ohms 0 to 20 Megohms.
 - DECIBELS: (Based on zero decibels equals .008 Watts into a 500-Ohm line.) -10 to +18 D.B., +10 to +38 D.B., +30 to +58 D.B. **\$62⁵⁰**



FIRST ON THE MARKET

New 1947 Model
PREMIER SIGNAL GENERATOR


Model 570 **\$54⁷⁵**
 YOUR COST

Micro-Master tuning dial. Eliminates back lash and provides smooth split-cycle tuning. Calibration accuracy better than 0.5% up to 1.6 MC, and 1% on higher frequencies. Air trimmers on all bands. Buffer stage modulated by 400 cycle generator. Pure sign wave—less than 5% distortion. 9" Three color dial face. Frequency range 75 KC to 50 MC on the fundamental frequency and up to 150 MC on the third harmonic.

The New Model 400 ELECTRONIC MULTI-METER

A COMBINATION VACUUM-TUBE VOLTMETER AND VOLT-OHM MILLIAMMETER PLUS CAPACITY, INDUCTANCE, REACTANCE AND DECIBEL MEASUREMENTS

- Specifications:**
- D.C. V.T.V.M. VOLTS: (At 11 Megohms Input Resistance) 0 to 3/15/30/75/150/300/750/1500/3000 Volts.
 - D.C. VOLTS: (At 1,000 Ohms Per Volt) 0 to 3/15/30/75/150/300/750/1500/3000 Volts.
 - A.C. VOLTS: (At 1,000 Ohms Per Volt) 0 to 3/15/30/75/150/300/750/1500/3000 Volts.
 - D.C. CURRENT: 0 to 3/15/30/75/150/300/750 Ma. 0 to 3/15 Amperes.
 - RESISTANCE: 0 to 1,000/10,000/100,000 Ohms; 0 to 1/10/1,000 Megohms.
 - CAPACITY: (in MFD) .0005—.2, .05—20. .5—200.
 - REACTANCE: 10 to 5M (Ohms, 100—50M (Ohms), .01—5 (Megohms).
 - INDUCTANCE: (in Henries) .035—14, .35—140, 35—14,000.
 - DECIBELS: -10 to +18, +10 to +38, +30 to +58.

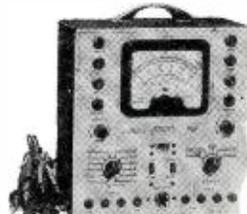

\$52⁵⁰
 NET

TERMS: 20% DEPOSIT WITH ORDER — BALANCE C. O. D. — SEND FOR OUR LATEST CATALOG AND CIRCULARS

LIBERTY SALES CO., INC.

115 WEST BROADWAY
 NEW YORK 13, N. Y.
 BRa clay 7-6063

HARVEY

for station equipment

Supreme Model AF-100 Transmitter. Commercial quality and stability in a ham transmitter at moderate cost. 100 watts output on CW, ICW, AM, and FM phone. VFO and xtal control. Designed for simplicity of operation, for the new ham or the old-timer. In stock for immediate delivery, complete.....\$450



Sonar VFX 680. For rack or table mounting ... a VFO, VFX and xtal unit in one. Narrow band FM exciter, plus monitor for earphone use. A versatile unit for the shack.....\$87.45

Also the **Sonar XE10**, narrow band FM exciter.....\$39.50



RECEIVERS

Most of these receivers in stock for immediate delivery. The rest as soon as released by the manufacturers.

Collins 75A	\$375
Hallicrafters S38 complete.....	\$47.50
Hallicrafters S40A	\$89.50
Hallicrafters SX 42.....	\$275
Hammarlund HQ129X and speaker....	\$173.25
Hammarlund SP-400-X and speaker....	\$347.25
National NC173, complete.....	\$189.50
National NC-2-40D (complete with speaker)	\$240
National HRO-5TA1 complete	\$306.71
National NC-46 less speaker.....	\$97.50
National 1-10A with tubes and coils..	\$67.50
RME-45 complete	\$198.70
Hallicrafter panadapter complete.....	\$99.50
Meck 60T transmitters.....	\$150
Millen 90700 ECO	\$42.50
Millen 90800 exciter	\$42.50
Millen 90281 power supply.....	\$84.50
Millen 90902 scope	\$42.50

Gordon, Abbott and other rotary beams and rotators

Note: All prices Net, F.O.B. New York City and subject to change without notice.

Telephone:  Longacre 3-1800

HARVEY
RADIO COMPANY INC.
103 West 43rd St., New York 18, N. Y.

unless it actually falls within the pass band of the disturbed receiver. Even in this case it will cause interference only when the antennas of the disturbing and the disturbed receiver are rather closely coupled.

-30-

RPEE Conference

(Continued from page 54)

diocre beginning to one of the largest of all annual conventions.

Whether you are an Old Timer or a newcomer in the radio industry, the Radio Parts and Electronic Equipment Conference and Show will give you a complete picture of the industry today, the progress made in past years and the bright promise of an even greater future in radio and electronics.

Friday, May 16th has been set aside as "Open House Day" in order to accommodate the thousands of visitors keenly interested in the radio industry and its displays. This is a golden opportunity for you servicemen and amateurs living within driving distance of Chicago to come in and meet your favorite manufacturers, publishers, service authorities and distributors and to talk to them personally.

There is little chance that you will be able to find sleeping quarters for an overnight stay so don't count on a bed unless you already have hotel accommodations or can stay with a friend.

Copies of the RADIO NEWS DAILY will be available to acquaint you with the happenings at the Show. We'll be looking for you.

-30-

Phase Modulation Exciter

(Continued from page 69)

modulation is relatively small so that it is necessary to multiply the fre-

quency in order to obtain sufficient deviation for satisfactory narrow band communication. By using an 80 meter crystal and multiplying the frequency eight times, a deviation of 2 to 3 kc. can be produced in the 10 meter band.

Construction

Most of the necessary construction details can be seen in the photographs.

The exciter unit is built on a standard 5½"x9"x3" chassis which can be obtained at any regular parts distributor.

The midget variable condensers are mounted directly to the chassis. There is no d.c. on the rotor which makes the mounting of these parts easy. In the r.f. section ceramic sockets and mica bypasses are employed.

In wiring, all grounds are made direct to the chassis and tie lugs are used freely for the mounting of resistors and condensers.

Operation

Tuning of the exciter is conventional and the procedure is as follows: With a 0-1 milliammeter plugged into jack, J₁, at the rear of the chassis, C₂ of the phase modulator tank circuit is tuned for maximum grid current reading. The meter should read from .1 ma. to .5 ma. depending on the activity of the crystal.


The tank circuit of the doubler stage is tuned to resonance with the help of a neon bulb. The output of the doubler stage is link-coupled through a microphone cable or twisted pair to a tuned circuit which plugs into the crystal stage of the transmitter that the exciter is feeding.

If the crystal stage is a tritet oscillator, the cathode coil should be shorted out. No attempt was made to feed the exciter into a Pierce oscillator.

The gain of the two speech stages is sufficient to accommodate a crystal or dynamic mike. The gain control is used in the conventional manner.

-30-

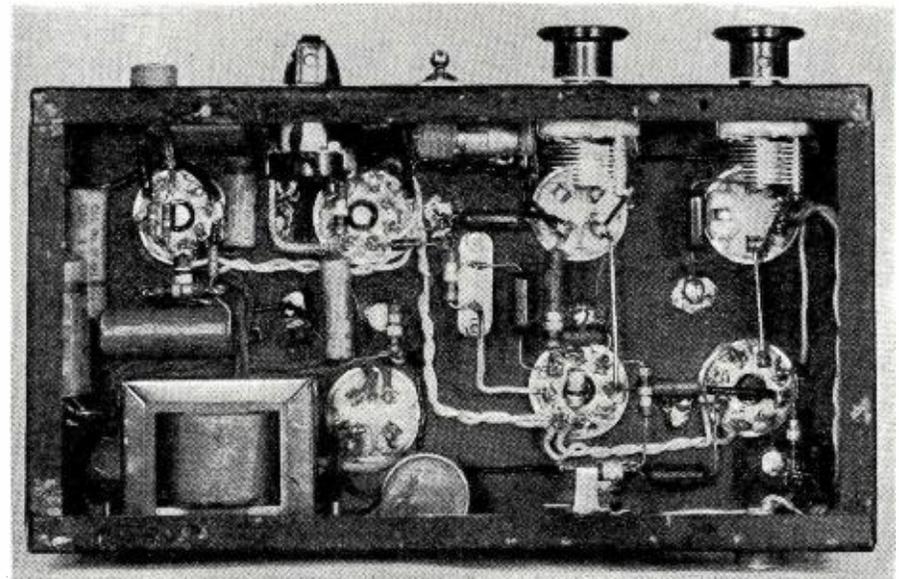Under chassis view of narrow-band phase modulation exciter unit.



11


SHORT CUTS TO SERVICING

"Quick, easy and efficient" . . . that's how servicemen describe IRC's 11 Tap-In Shafts. No fiddling or fussing with shaft inserts or "build-ups" . . . no money tied up in stocks of exact replacements. A smart tap of the hammer and the tapered surfaces of control and shaft lock together, forming a permanently tight attachment.

In combination with the IRC Century Line of Volume Controls, these 11 Tap-In Shafts are the logical answer for over 90% of your replacement problems. Save you time and money. Time saved means extra time for other money-making jobs . . . money saved means greater profits. The latest edition of the popular IRC Volume Control Replacement Manual is now available. Contains information on nearly all models up to 1946, complete listings for the 1941-42 sets coming in now for repair. 156 pages. 25c at your IRC Distributor. International Resistance Company, 401 N. Broad St., Philadelphia 8, Pa. *In Canada:* International Resistance Co., Ltd., Toronto, Licensee.



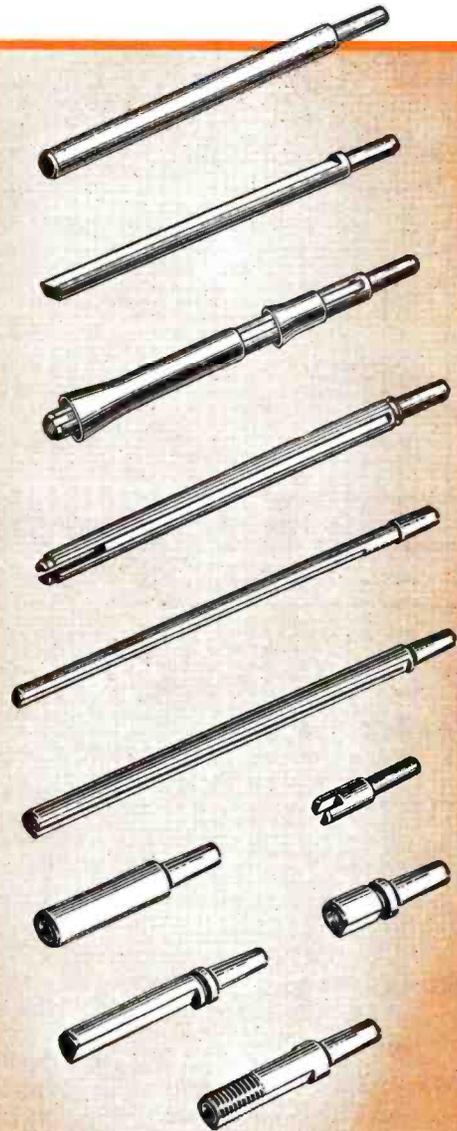YOU'RE ON THE AIR! A sensational new one minute spot announcement to boost service business has just been released by IRC through IRC Distributors. Listen in and cash in on this promotion!



INTERNATIONAL RESISTANCE COMPANY



Wherever the Circuit says Ω

NEW SOLDERING GUN

Heats in 5 Seconds



SPECIAL SOLDERING GUN ADVANTAGES

TIP STAYS TINNED
NO BURNING



SEE WHERE
YOU SOLDER



SOLDER AROUND
CORNERS

Service and maintenance men can save time by the fast heating of the Soldering Gun. By use of the new induction principle, 5 second soldering heat is supplied from a light weight built-in transformer.

The loop type tip gives you other advantages that are important in soldering. Good balance with weight close to your hand makes it easier to use. The narrow tip gets in between a lot of wiring with ease. Connections can be made without burning insulation. The tip can be formed readily to work in tight places.

See your radio parts distributor for a demonstration, or write direct for descriptive bulletin.

- ★ 100 Watts 115 Volts 60 Cycles
- ★ Intermittent Operation With Trigger Switch
- ★ Can't Overheat or Burn Out
- ★ Impact Resisting Case
- ★ Handle Stays Cool
- ★ Good Balance—Weight Close To Hand

810 PACKER ST.

WELLER MFG. CO. Easton, Pa.

Export Dept.—25 Warren Street, New York 7, N. Y.
In Canada—Atlas Radio Corp., Ltd., 560 King Street N. W., Toronto, Ont.

May Specials

PORTABLE PHONOGRAPHS
A.C.—D.C.—And battery portable phonographs. Complete with three tube amplifier and battery. Ready to play—Ideal for beach, picnics, etc. **Only \$21.99**



STANDARD BRAND TUBES

1LE3...\$.85 1LA4...\$1.10
12A6...\$1.10

CROWE AUTO ACCESSORIES

We can serve you with a complete line of Crowe Auto Radio Panel Kits and Accessories from 1940 to 1947. Underdash mounting for others.

ALNICO SPEAKERS

Square mounting Alnico 4" PM Speakers. **\$1.39**

EMMERSON SPEAR POINT NEEDLES

5 Needles per Package—10 packages 65 cents—100 packages \$5.

SPECIAL 6 VOLT VIBRATORS

Specially priced 4 prong 6 volt vibrators. **\$1.29 each**
10 for \$11.59

FLASHLIGHT BATTERIES

Specially priced Bright Star flashlight batteries. **10 for \$.50**
100 for \$3.99

A COMPLETE LINE OF TUBES ARE NOW AVAILABLE

Write for Our Latest Catalogue

RADIO PARTS COMPANY

612 W. Randolph Dept. "N" Chicago 6, Illinois

FM Tuner Conversion

(Continued from page 53)

Now, remove the wire connection from the oscillator tuning capacitor, (see photo Fig. 6 inset). A 40 μ fd. ceramicon is connected in series with this capacitor and the wire just removed.


Wire in the oscillator coil connections as in the original set. (See Fig. 7) The grid (1st converter) coil is connected to the 1st 6AB7 grid as was the original coil. The bottom end is grounded. The antenna primary is connected through the twisted insulated leads to the antenna posts. There is no center tap on the antenna primary. A 25 μ fd. capacitor is inserted in series with the first 6AB7 grid tuning capacitor (see photo Fig. 6 inset) as was done in the capacitor for the 7A4 oscillator tuning.

The next step is to remove turns from the existing second converter grid coil (L_2) until there are four turns left. With these turns spaced about 3/16" apart leave enough slack on the end of the coil to provide for some trimming as described later.

To align the set, another receiver which has previously been calibrated was used by the author. All the necessary adjustments were made on a cut and try basis until the individual variable sections of the tuning capacitor followed the tracking requirements mentioned earlier. If a wavemeter of the absorption type is available, the oscillator tracking can be checked as described previously for the Meissner unit. If a v.t.v.m. and signal generator are available, alignment can proceed by feeding signals for the i.f. frequency 46.15-56.15 mc. into the antenna with the oscillator inoperative (remove 7A4 tube).

With the v.t.v.m. measure the voltage appearing across the plate of the second mixer (6AB7) tube as the tuning capacitor tunes in the generator


Fig. 8. The ideal tracking conditions for the three tuned circuits for the JFM-90.

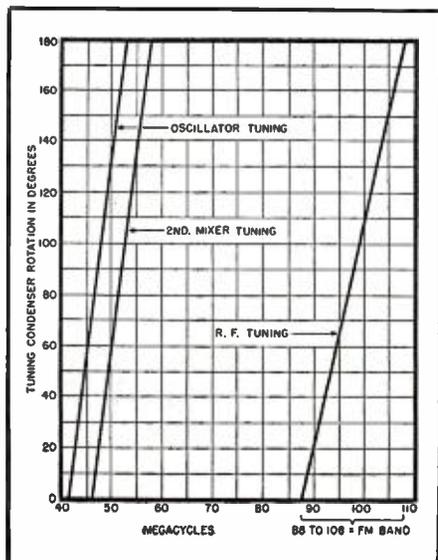

says **JOHN M. DERBY CO.** Chicago (AUTHORIZED HALLICRAFTERS SERVICE CENTER)

Your CCO is a Natural!

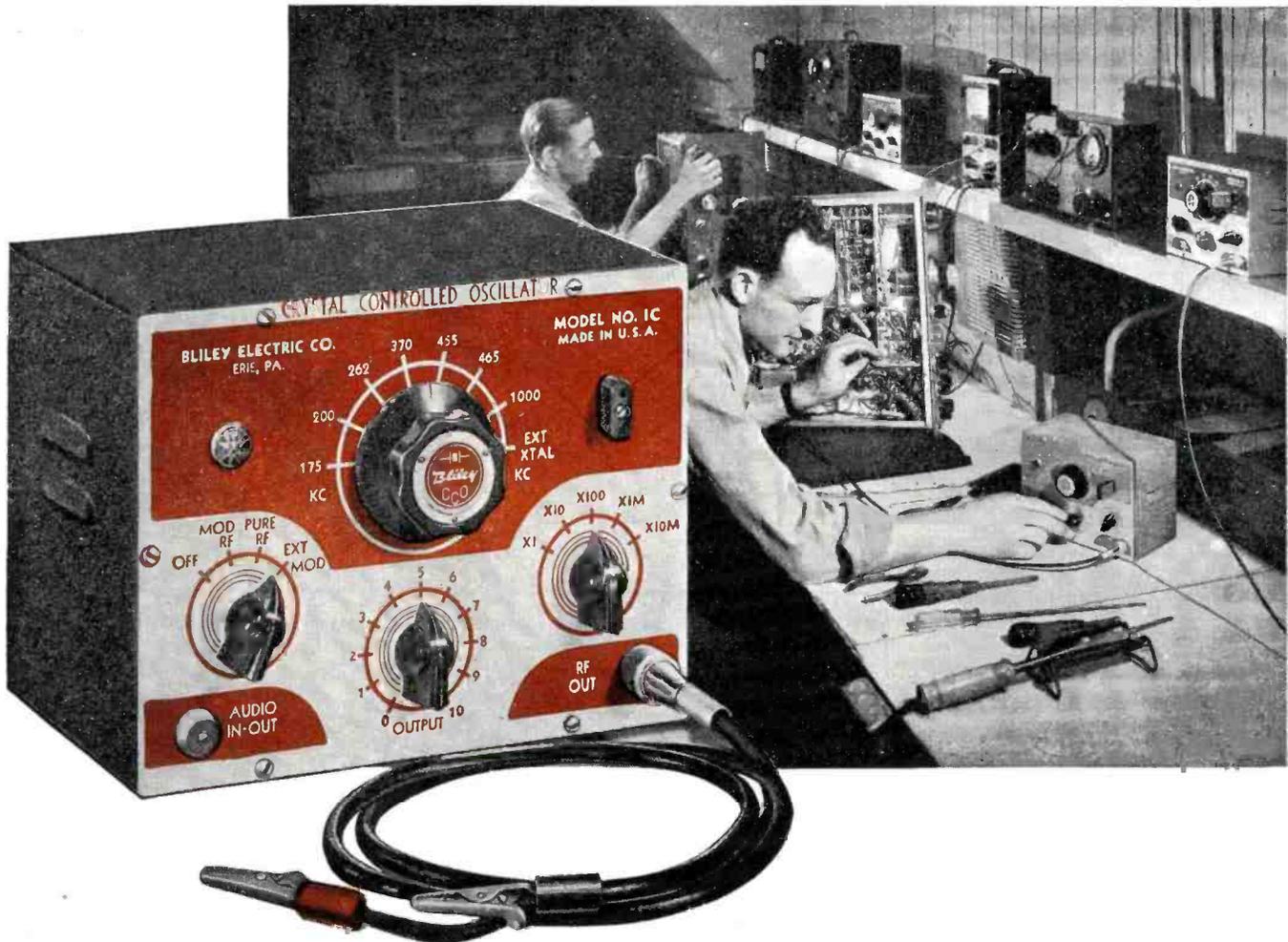NO GUESS WORK ABOUT IT... SIGNAL SELECTION IS POSITIVE AND PRECISE"



Yes, as John Derby says, the CCO eliminates any question or interpolation because each signal is directly controlled by an individual crystal oscillating at the required frequency. No need to identify confusing beat frequencies when you have *direct crystal control* in the CCO.

Precision is assured by seven Bliley crystals which are "on frequency" as soon as the oscillator is energized. No warm up time needed and no aging effects to compensate. All fre-

quencies are accurate, dependable and permanent with *direct crystal control* in the CCO.

This small compact instrument provides instant selection of crystals oscillating at 175 kc, 200 kc, 262 kc, 370 kc, 455 kc, 465 kc and 1000 kc. An external socket is provided to accommodate extra crystals that may be needed for special frequencies.

The CCO is a "techniquality" product of Bliley engineers and craftsmen who have pioneered in frequency control for over fifteen years. Ask your Bliley distributor, or write direct, for Bulletin 32 which gives complete details.


\$69.50

Complete with 7 Bliley crystals, tubes and concentric output cable.



BLILEY ELECTRIC COMPANY • UNION STATION BUILDING, ERIE, PENNSYLVANIA
May, 1947 121

7 Days Free Examination

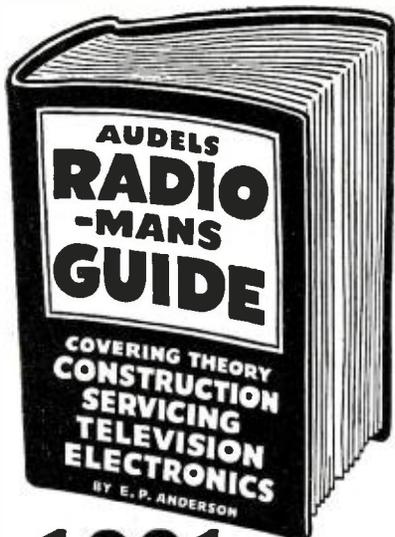

1001 RADIO FACTS AND FIGURES

AUDELS RADIOMANS GUIDE—914 Pages, 633 Illustrations, Photos, Wiring Diagrams, 38 Big Chapters, covering Radio Theory, Construction, Servicing, including Important Data on Developments in Television, Electronics and Frequency Modulation, Review, Questions and Answers, Calculations & Testing, Highly Endorsed—Indispensable for Ready Reference and Home Study.

\$4 COMPLETE • PAY ONLY \$1 A MONTH
Step up your own skill with the facts and figures of your trade. Audels Mechanics Guides contain Practical Inside Trade Information in a handy form. Fully illustrated and Easy to Understand. Highly Endorsed. Check the book you want for 7 days' Free Examination.

Send No Money. Nothing to pay postman.

CUT HERE MAIL ORDER

AUDELS, Publishers, 49 W. 23 St., NEW YORK 10, N. Y.

Please send me postpaid for FREE EXAMINATION books marked (x) below. If I decide to keep them I agree to mail \$1 in 7 Days on each book ordered and further mail \$1 monthly on each book until I have paid price. Otherwise, I will return them.

- RADIOMANS GUIDE, 914 Pages . . . \$4.
- ELECTRICIANS EXAMINATIONS, 250 Pages . . . 1.
- WIRING DIAGRAMS, 210 Pages . . . 1.
- ELECTRICAL DICTIONARY, 9000 Terms . . . 2.
- ELECTRICAL POWER CALCULATIONS, 425 Pgs. . . 2.
- HANDY BOOK OF ELECTRICITY, 1340 Pages . . . 4.
- ELECTRONIC DEVICES, 216 Pages . . . 2.
- ELECTRIC LIBRARY, 12 vol., 7000 Pgs., \$1.50 vol. . . 2.
- OIL BURNER GUIDE, 384 Pages . . . 1.
- REFRIGERATION & Air Conditioning, 1280 Pgs. . . 4.
- POWER PLANT ENGINEERS Guide, 1500 Pages. . . 4.
- PUMPS, Hydraulics & Air Compressors, 1658 Pgs. . . 4.
- WELDERS GUIDE, 400 Pages . . . 1.
- BLUE PRINT READING, 416 Pages . . . 2.
- SHEET METAL WORKERS Handy Book, 388 Pgs. . . 1.
- SHEET METAL PATTERN LAYOUTS, 1100 Pgs. . . 4.
- AIRCRAFT WORKER, 240 Pages . . . 1.
- MATHEMATICS & CALCULATIONS, 700 Pgs. . . 2.
- MACHINISTS Handy Book, 1600 Pages . . . 4.
- MECHANICAL Dictionary, 968 Pages . . . 4.
- AUTOMOBILE GUIDE, 1540 Pages . . . 4.
- DIESEL ENGINE MANUAL, 400 Pages . . . 2.
- MARINE ENGINEERS Handy Book, 1280 Pages . . . 4.
- SHIPFITTERS Handy Book, 272 Pages . . . 1.
- MECHANICAL DRAWING COURSE, 160 Pages . . . 1.
- MECHANICAL DRAWING & DESIGN, 480 Pgs. . . 2.
- MILLWRIGHTS & Mechanics Guide, 1200 Pgs. . . 4.
- CARPENTERS & Builders Guides (4 vols.) . . . 6.
- PLUMBERS & Steamfitters Guides (4 vols.) . . . 6.
- MASONS & Builders Guides (4 vols.) . . . 6.
- MASTER PAINTER & DECORATOR, 320 Pgs. . . 2.
- GARDENERS & GROWERS GUIDES (4 vols.) . . . 6.
- ENGINEERS and Mechanics Guides . . . 12.
- Nos. 1, 2, 3, 4, 5, 6, 7 and 8 complete . . . 12.
- Answers on Practical ENGINEERING . . . 1.
- ENGINEERS & FIREMANS EXAMINATIONS . . . 1.

Name _____
 Address _____
 Occupation _____
 Employed by _____ **RN**


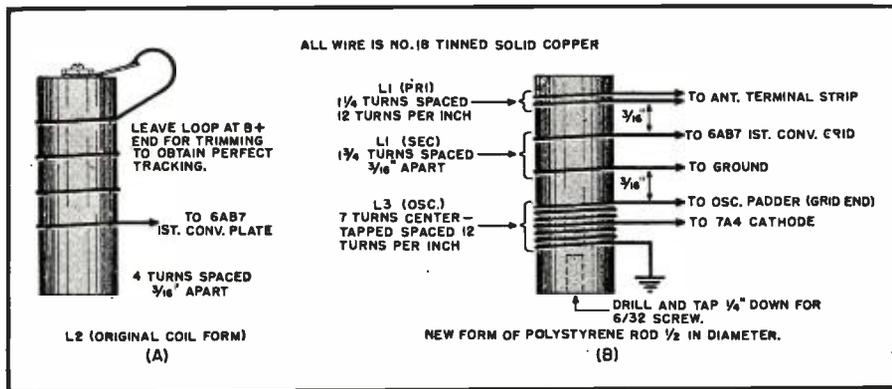


Fig. 9. Mechanical details of coil assembly for the General Electric JFM-90 tuner.

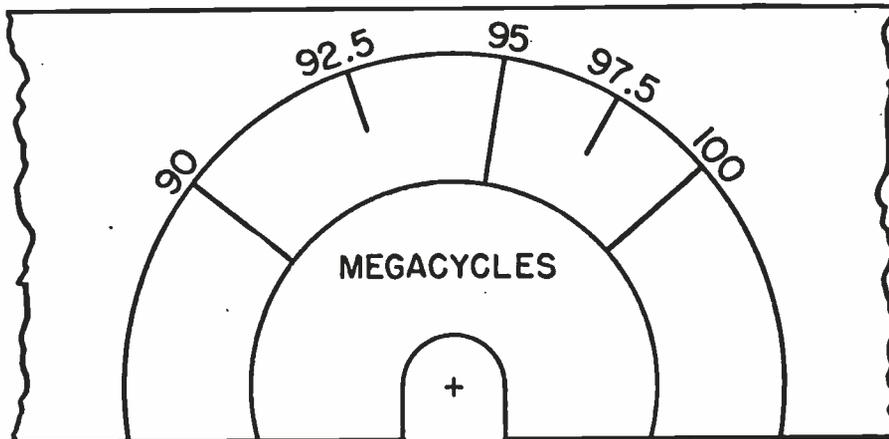


Full scale drawing of recalibrated dial scale for GE tuner.

at several points. Adjustment may be made by trimming the loop which had been left on coil L_2 . If the desired frequency is tuned in, the v.t.v.m. will peak. Next with the oscillator operat-

ing adjust the oscillator padder until 4.3 mc. is obtained at the three arbitrarily chosen points on the dial as tuning progresses through the range. (See tracking chart Fig. 8) The next

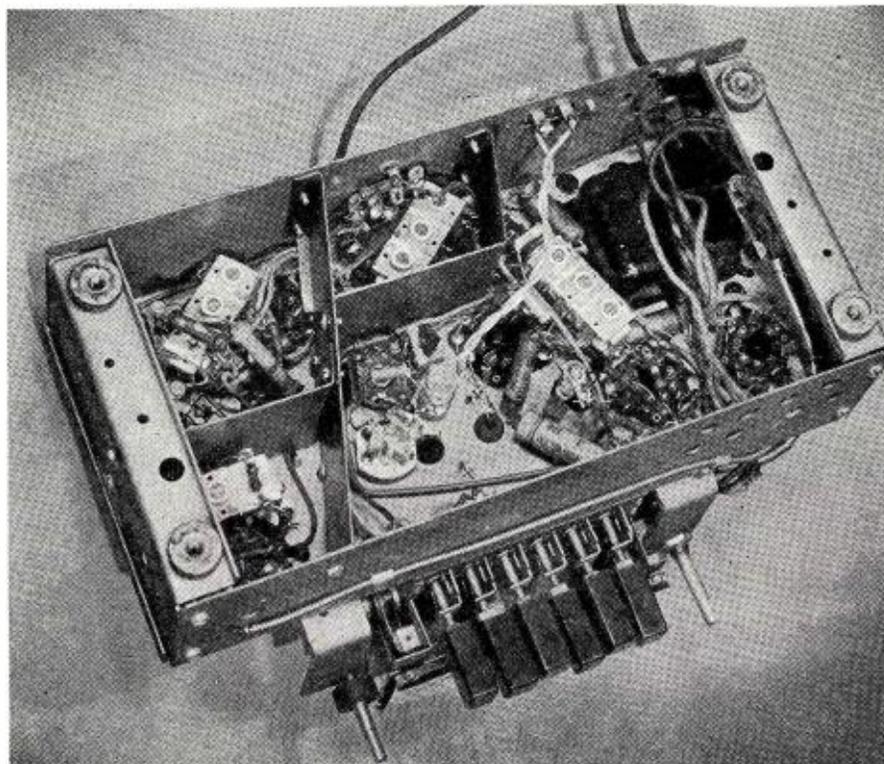
Under chassis view of the converted JFM-90 tuner.





NEW SURPLUS at LOWEST PRICES

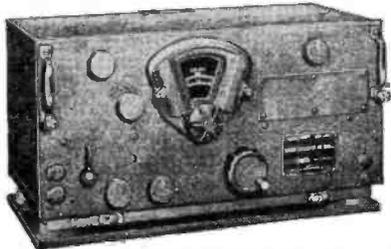When You Buy From Us, You Get The Lowest Prices In U.S.A. Are One Of The Largest Surplus Suppliers.



SENSATIONAL BC-348 RECEIVER

200-500kc and 1.5 to 18mc in six bands! Crystal I.F. Filter, 2 Stages RF, Combined RF and AF Gain Control, High-rate Vernier Tuning dial. Built-in 24v. dc Dynamotor which is easily removable for AC pack installation. Two 'phone jacks on front panel, one for loudspeaker operation. Has 2 stages transformer-coupled audio. BFO. Manual or automatic volume control. This is the most wanted surplus item. Limited stock. First come, first served.

OUR PRICE \$49.50, Complete With 8 Tubes.
• We Can Also Supply This Same Receiver With Built-in 110 v. AC 60 Cycle Power Pack—Ready For Operation \$69.50



372 Ellis St., San Francisco 2, Calif.

SCR-522 VHF XMTR-RCVR.



\$34.95

• 100-156Mc Transmitter-Receiver for Amateur, Civilian, Commercial and Airborne or Mobile Service. One of the most versatile surplus items—can be operated by anyone. 4 crystal-controlled channels, push-button operation, fixed frequencies. Transmitter output 15 watts. Transmitting tubes include 1-6GG6, 1-6SG7, 3-12A6, 2-823. The 4-channel superheterodyne receiver uses 10 tubes, as follows: 1-9002, B-9003, 3-12SG7, 1-12C8, 1-12J5, 1-12AH7G. The dynamotor power supply is included in the purchase price. Control box and other accessories also supplied. Operation is from 28v DC, but can be converted for AC operation, simply and easily. Get one of these SCR-522 sets NOW, while stock lasts. A GREAT BUY!

SCR-274-N COMMAND SET. 2 TRANSMITTERS & 3 RECEIVERS



ALSO INCLUDES MODULATOR

• 6 Units, as illustrated, for less than \$6.00 per unit!!! 4-5.3mc BC-457A and 5.3-7mc BC-458A transmitters, 1 each. 3-6mc BC-454A, 190-550kc BC-453A, 6-9.1mc BC-455A Receivers, 1 each. Also BC-456A Modulator Unit. Our price of \$34.95 includes all of the tubes required, as well as four dynamotors and control box. This is an amazing bargain!

ORIGINAL COST OVER \$600.00. TUBES ALONE WORTH OVER \$40.00
OUR PRICE FOR THE COMPLETE COMBINATION..... ONLY \$34.95

ARN-5A 11-TUBE SUPERHET 332 to 335-MC. Fixed Tune.

• This "Glide Path" Receiver sold for \$150.00 as SURPLUS a month ago. Today you can buy this superhet for \$13.95, complete with 11 tubes. 7-6AJ5, 1-12SR7, 2-12SN7, 1-28D7. Frequencies: 332.6, 333.8, 335.0mc. 6 Relays are included. Requires only 28v. Total "A" & "B" drain only 1.7 amps at 28 volts. Tubes alone worth more than price of complete receiver.

OUR PRICE, COMPLETE WITH TUBES..... ONLY \$13.95

Just RELEASED! RA-105A POWER SUPPLY-COMLETE


• 110 AC Operation. Brand New. Sealed Cartons. A GREAT BUY! 120 pounds of new transformers, chokes, oil condensers, three 5U4G tubes, magnetic circuit breakers for both HV and Fil ckts. Heavy black crackled steel case. READY FOR OPERATION!



OUR PRICE, COMPLETE WITH TUBES..... ONLY \$29.85

TRANSFORMER SPECIFICATIONS.

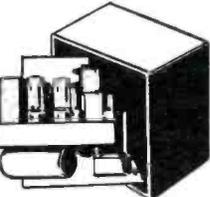355v RMS at 158 MA.
490v RMS at 1.5 MA.
+2000 DC, -2000 DC for scope.
+610 DC, +415 DC, +300 DC, -290 DC, -160 DC and 6.3 ac.
6.4 at 12a., 6.4 at 10a., 5.0 at 3a., 5.0 at 2.5 at 1.75a., 6.3 at 0.6a.
(2100 RMS for 'scope)



6V6 AMPLIFIER

• Three 6V6GT tubes (1 spare). 24v dynamotor, shielded 6V6 output trans., shielded choke and input trans. Oil condensers. Steel cabinet. Parts alone worth \$12.75 NET. Brand new. Sealed Cartons. Our price, \$4.75 with 3 tubes. (Easily converted for audio.)

LOOK AT THESE BARGAINS! STOCK UP NOW!

- TRIUMPH 3" Cathode-Ray Oscilloscope with tube. New. War Surplus \$69.85
- Kit of 100 assorted new resistors, 1/2, 1, 2, 3 watts. All standard values, up to 8 megs. Finest made. 100 for only \$1.95
- 3" Silvered instrument dials, 270°. Marked "AMP." Ideal for volume controls. "Give Away." Price \$1.00 per doz.
- Marion 0-1 MA DC Jumbo Test Meter, 6 1/2" Window, \$12.25
- Webster Model 56 Record Changer with Automatic Stop..... \$27.90
- IRC Volume Control Cabinet with 18 controls, switches, slats, etc. \$16.62
- IRC #1 Resistor Asst. & Cabinet \$9.25
- IRC #2 Resistor Asst. & Cabinet \$8.68
- IRC #3 Resistor Asst. & Cabinet \$8.88
- 25,000 ohm Centralab Pots. \$3.00 per doz.



SUPREME TESTER

• Pocket Model 543-S. 300v AC-DC. Also ohms and MA. scales. NET

ONLY \$12.85



110 A-C Phono Motor and Turntable Alliance \$3.72



12" DeLuxe Alnico-5 PM SPEAKER

Fine for PA use, etc. ONLY \$10.35


I.F.F. XMTR-RCVR.



435-500 MC 15 TUBES!!!

BC-645 \$16.85

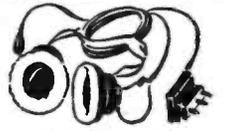• LAST CHANCE! War Surplus Agencies have no more. This 15-tube set will operate on frequencies for Citizens' Radio. Amateur, etc. Tubes alone worth \$28.00 net. Too well known to require description. Be safe. Order yours TODAY!! Our Price..... ONLY \$16.85
12/24V. DYNAMOTOR-PE-101C. SUPPLIES A.L.L. POWER FOR BC-645. 400V. 135MA. DC. ALSO 9V. 1.2a. AC. ONLY \$9.95 NET



Sound-Powered Telephones

• Ultra sensitive dynamic units. Use one as mike, other as receiver, parallel connected. Talk up to 1 mile without batteries or transformer. Fine for intercoms, monitoring, mine, and industrial use. ONLY \$4.95.



51-Pr. TEL. TERMINAL

Standard Cook Electric Co. 102-wire Block with 10-ft. lead-covered stub. NEW WAR SURPLUS. \$4.05 ea.

2-20MC TRANSMITTER

Battery Operated. Makes good signal generator. Calibrated jumbo dial. Metal case. Signal Corp. Item. ONLY \$9.85. ACT QUICKLY!



PUSH-BACK WIRE

• NEW. Stranded. Tinned. 20ga. LENZ made. 1000-ft. spools \$6.25

STEEL TOWERS

• 73-ft. Galvanized sectionalized Alvey Conveyor Co. antenna tower. New. Unused. Surplus. Fine for FM, TV, Hams, Etc. \$175.00 ea.



7-CONDUCTOR CABLE

• Has 1 shielded pair, also 5 color-coded conductors, shielded overall, then rubber-covered. Fine for rotary-beam control, etc. (Direct burial.) NEW. SURPLUS. Only 12c per ft.




McELROY Tape Pullers

• Universal 110 AC-DC motor with rheostat control. War Surplus. No Reels. ONLY \$17.85

DIRECTION-FINDER

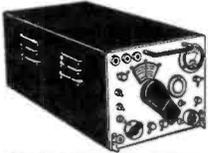
• Marine model. Stewart Warner. 200-18,000kc in 8 bands. 9-tube rcvr. Dual IF super. Perfect Condition. (Without Loop). Net Price \$83.00



HALLCRAFT AR7

• Airborne version of SX-28A. 3 stages RF (one of which is a re-radiation suppressor). BFO. Noise Limiter. AVC. X1 Phasing. Manual or motor tuning. 8-Meter. 550KC-42MC. 12 tubes. Net Price, less speaker. \$152.75

DICTAPHONE Continuous Recording MACHINES

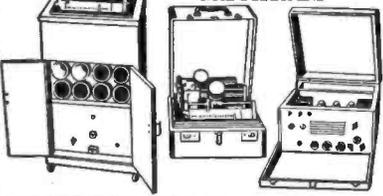

PERFECT CONDITION. WAR SURPLUS AT FRACTION OF REGULAR PRICE.

• Latest Models, selling regularly for \$750.00 per pair, either for the 2 portable units, or both in one steel cabinet, as illustrated. Our net price is only \$175.00 for the portable dual recorder and portable 10-tube Telecord Amplifier, or \$197.50 for the cabinet type, complete with cables, plugs and controls, or the cabinet model of 2 units combined. Universal 110 AC/DC motors, ideal for signal or voice recording, office use, detectives, police departments, etc. IN PERFECT CONDITION. Used slightly by Gov't.



PORTABLE RECORDER

• Edison Telephonograph Portable Recorder with crystal recording head. Universal 110 AC/DC Motor & Governor. Two can be connected together for continuous recording. Heavy airplane luggage case. Used. War Surplus. Motor alone worth more than our price of complete unit. ONLY \$29.50 Net

★ 4-HOUR MAIL-ORDER SERVICE.

• Send 20% Deposit. Balance C.O.D. We Ship Anywhere In The U.S.A.

OFFENBACH & REIMUS CO.

372 Ellis Street, San Francisco 2, Calif. 'Phone: ORdway 8551

(Open Evenings Until 9 P.M.)

"THE HOUSE OF A MILLION RADIO PARTS"



BUD RADIO, INC.

moves forward with the newest in radio transmitting components built on a firm foundation.




VFO-21

An immensely popular new unit at an amateur net of \$52.50.

Features:

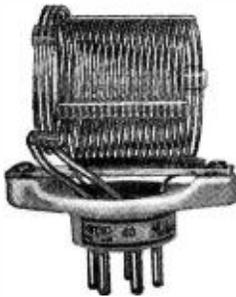1. **PLUG-IN COILS** for flexibility of use and higher efficiency.
2. **COMPACTNESS.** It is entirely self-contained.
3. Provisions for crystal operation.
4. **STABILITY** comparable to crystal.



VARIABLE END-LINKED COILS

A new line of coils that are vital to circuits using single-ended amplifiers. Available in 75 watts, 150 watts and 500 watts.

The entire BUD line is a valuable source of variable condensers, coils, chokes, sheet metal products and many other items familiar to you.

They are on sale at your local distributor and on display at booth 39 at the Radio Parts Show, Hotel Stevens, Chicago, May 13 to May 17.



BUD RADIO, INC.

CLEVELAND 3, OHIO

step is to feed the 88-108 mc. signals into the set and adjust the trimmer on the r.f. tuning section until the tracking follows successfully. It will be a case of adjust and try, using a little patience in changing the adjustments and trimmers and a little lead dressing back and forth.



Practical Radio Course

(Continued from page 67)

but unusually strong interfering image-frequency signals. This was the image-interference prevention method resorted to in most of our early AM broadcast band receivers—especially those which employed low i.f.'s in the neighborhood of 175 kc., 264 kc., etc., since such low i.f.'s resulted in increased image interference troubles. Such tuned r.f. stages are comparatively costly and bulky, for each requires the use of a tuning coil, a variable capacitor section on the signal-tuning capacitor gang, an amplifier tube and socket, associated resistors and bypass capacitors, etc. Consequently, present-day preselectors for AM broadcast band receivers usually consist of a single tuned r.f. stage only.

Choosing I.F. for Prevention of Image Interference

When the receiver designer is unable, because of high signal frequencies to be received, cost, physical size of receiver, or other such limitations, to provide adequate image suppression circuits ahead of the frequency converter by the use of r.f. preselection, it is often possible for him to eliminate the possibility of image interference by properly choosing the i.f. to be employed in the receiver—unless this dictates the use of an i.f. that is undesirable from other viewpoints such as inability to secure sufficient gain per i.f. stage within the allowable limits of cost, stability of the i.f. amplifier, physical size of the receiver, etc. Even if an r.f. preselector is employed in the receiver, proper choice of the i.f. used will help by decreasing the possibility of image interference.

Study of Fig. 2A and Table 1 will show that the i.f. value chosen for use in a receiver has a direct and important bearing on the frequency that a signal must have in order to qualify as an image-frequency signal and thus be able to cause interference, when a desired signal of a particular frequency is being received. Referring specifically to the image-frequency interference example illustrated in Fig. 2A it is evident that if the receiver considered there employed an i.f. value appreciably higher or lower than 455 kc., the 1480 kc. signal labeled as "interfering signal" would no longer qualify as an image-frequency signal for the 570 kc. desired signal. For example, suppose that instead of using an i.f. of 455 kc. in this

Superior!



Electronic Voltmeter Ohmmeter

AT A NEW LOW PRICE **\$59.50**

Vacuum tube meter with stable bridge type circuit. Hand calibration assures constant accuracy and stability. Simple to operate. Positive or negative indications through reversal switch.

Measures D C Volts up to 600 with constant input resistance of 11 megohms.

Meter Ranges: DC 0-3; 0-30; 0-150; 0-300; 0-600. Multiply by 4 with external probe. AC 0-3; 0-30; 0-150; 0-300. Ohms 0-1000; 0-10M; 0-100M; 0-1 Meg.; 0-100 Meg.

ELECTRONIC MANUFACTURING CO.
714 RACE STREET, HARRISBURG, PA.

NEW! "PREMIER" BANDSPREAD DIAL SIGNAL GENERATOR

MODEL 570



Features:


The "Premier" Model 570 is the ONLY low-priced Signal Generator with a MICROMASTER BAND-SPREAD DIAL, equivalent to a scale length of approx. 60"—a major feature for logging, sharp and critical tuning.

- AIR TRIMMERS ON ALL BANDS.
- TRIPLE COPPER PLATED SHIELDING.
- Range 75KC-50MC on fundamental, and 50-150MC on 3rd harmonic, useful for aligning FM and Television Receivers.
- Accuracy better than 1%.
- Special geared straightline frequency tuning condenser provides linear calibration over entire dial range.

Manufactured by Premier Electronic Labs., N. Y. C. PRICE: \$54.75 net, complete with co-axial cable. Overall size: 12"x12 1/2"x5 1/2", shpg. wt. 21 lbs.

JACK GREENE'S RADIO & TELEV. CO.
79 1/2 Courtlandt St., New York 7, N. Y.

Who else would dare to show "the works"?

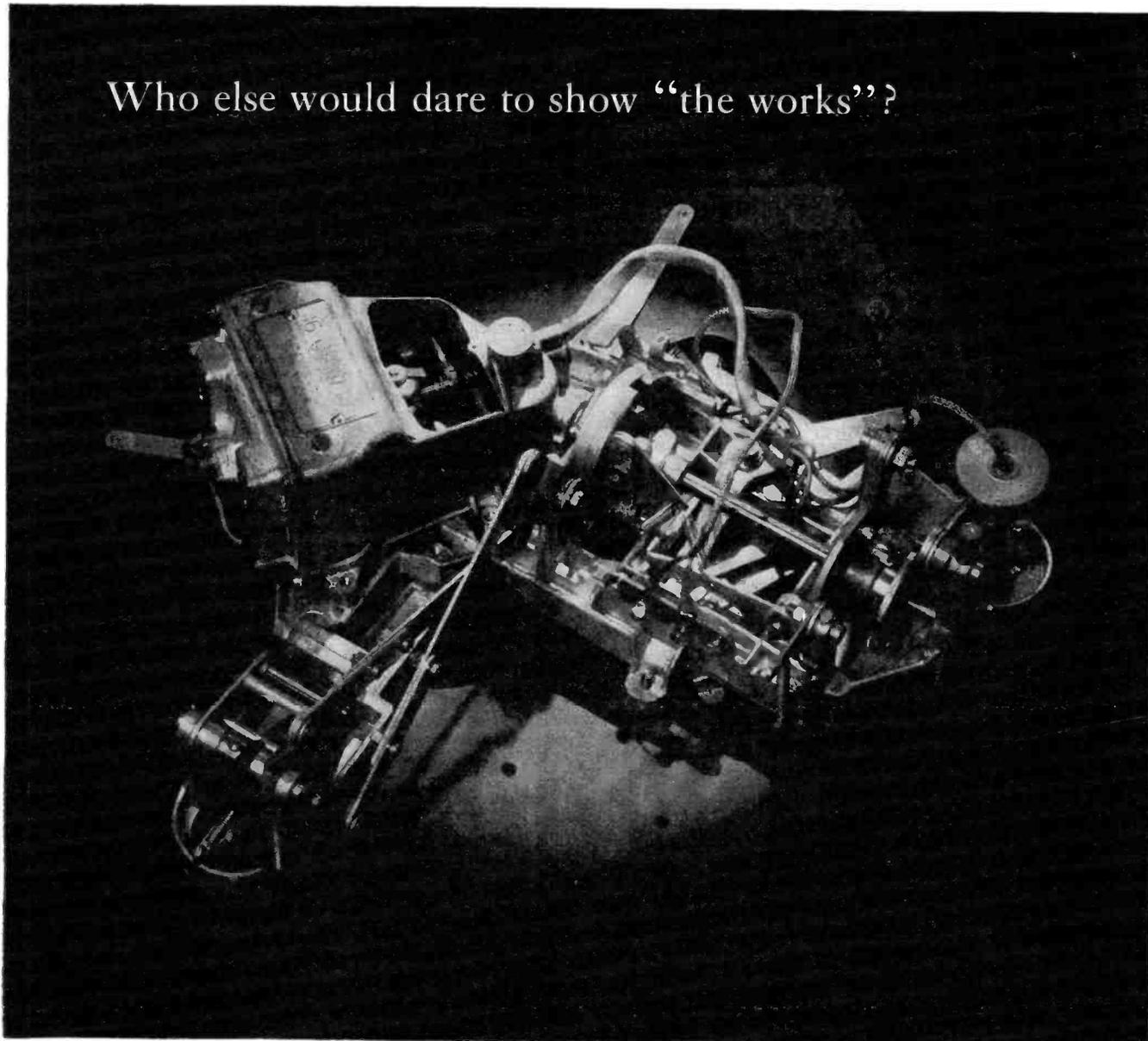

THIS is a Garrard automatic record changer standing on its ear. If we showed it to you right-side-up, you would see a fine record changer, but there would be no convincing proof that Garrard is the world's finest.

For your own satisfaction, turn any other record changer you use in your combinations, "bottoms up" and compare it to the Garrard. Immediately you will see the difference. Where others have little tension springs and stamped out bits and parts, Garrard is completely controlled by fine precision-machined gears and cams.

Obviously, the many exclusive features that make the Garrard changer more precise...more human...than human hands, don't show in a photograph—right-side-up or upside down. Read about them here. Better still, send for a sample changer and put it through your own tests.

Such a record changer as the Garrard cannot be built for so many dollars and cents. It is intended for your finest combinations, where *quality* not *price* is your talking point.




governor-controlled, speed-regulated
motor • completely automatic
mixing • range of pickups
available • true-tangent,
jewelled-pivot pickup •
exclusive non-slip spindle

...the record changer they ask for by name...

GARRARD

SEND FOR "DON'T OVERLOOK THE RECORD CHANGER": GARRARD SALES CORPORATION, 315 BROADWAY, NEW YORK 7

UNIVERSITY REFLEX CONSTRUCTION

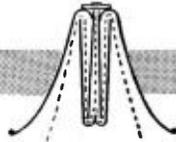

Engineered for efficiency and quality
University Speakers

The conversion efficiency of UNIVERSITY loudspeakers over the useful speech frequency range is 35 to 50 percent! Parallel to this superior sensitivity, is naturalness of tone and a ruggedness which permits every model to be unconditionally guaranteed for one year. Magnets of higher magnetomotive force, greater rigidity and concentricity of voice coils resulting in smaller air-gap clearances, better heat dissipation in the voice coil, diaphragms with a higher fatigue characteristic, and exclusive "rim centering" construction are a tribute to UNIVERSITY design.



UNIVERSITY
LOUDSPEAKERS • INC
225 VARICK STREET
NEW YORK 14, N.Y.

Look for us at Booth No. 16, Radio Parts and Electronic Equipment Show, May 13-16th, Chicago, Ill.



MODEL LH WITH 5AH DRIVER—
High efficiency reflex speaker, best for all-around, high-power P. A. use.

MODEL MM-2TC—
Submergence and explosion proof, may be cleaned with live steam—for ship, railroad or mine.

Pat. Pend.

receiver its i.f. amplifier was designed to employ an i.f. of 480 kc. The new conditions are illustrated in Fig. 4A. For a desired-signal having a frequency of 570 kc. the oscillator frequency is now $570 + 480 = 1050$ kc. With the oscillator operating at 1050 kc., after passing through the frequency converter the 1480 kc. signal would appear as a signal having a carrier frequency of $1480 - 1050 = 430$ kc. Notice that this frequency is 50 kc. removed from the 480 kc. i.f. employed in the receiver, consequently the 1480 kc. incoming signal no longer qualifies as an image-frequency of the 570 kc. desired signal. Since the selective grid and plate circuits of the i.f. amplifier would now be fixed-tuned to the 480 kc. i.f., they would attenuate this 430 kc. signal (which is $480 - 430 = 50$ kc. off resonance) sufficiently so that it would not reach the detector or demodulator tube. This action is illustrated pictorially in Fig. 4B. Observe that we are now depending solely upon the proper choice of i.f. and the selectivity of the tuned circuits in the i.f. amplifier to attenuate the undesired signal.


Radio servicemen often bring about this condition in order to eliminate image-frequency interference that is being caused in an existing receiver by a particular undesired signal. They readjust the i.f. and oscillator tuning circuits so that a slightly different i.f. is employed in the receiver. Consequently the undesired signal no longer qualifies as an image-frequency signal and therefore does not get through the i.f. amplifier. This shifting of the i.f. results in the action illustrated in Figs. 4A and 4B.

Shifting the Image Frequency Outside of Transmitting Band

A study of the foregoing discussion and of Fig. 5 will make clear the fact that if we choose an intermediate frequency value greater (even if only slightly) than half the width of the frequency band in which signals of interfering transmitters are likely to occur, image interference from signals of transmitters within that band is no longer possible. This is so because all possible image frequencies now fall outside of that signal-frequency band. This is a direct consequence of the "twice i.f." relationship between "desired" and corresponding "image-frequency" signals.

To illustrate, let us see how this ap-

Fig. 5. Diagram illustrates how the image frequency for any signal tuned in over tuning range of receiver may be thrown outside of the broadcast band by proper selection of the i.f. frequency.

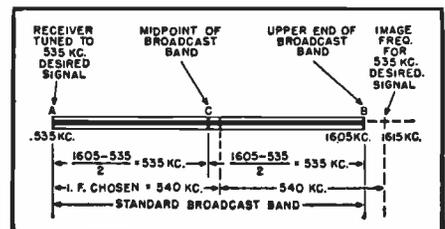

MATHEMATICS FOR RADIO AND COMMUNICATION

by **GEORGE F. MAEDEL, A.B., E.E.**

To master the technicalities of radio—to read engineering literature intelligently—you must have the mathematical ground work covered by these absorbing books prepared for home study. Book I (314 pp.) covers the algebra, arithmetic, and geometry; Book II (329 pp.) covers the advanced algebra, trigonometry, and complex numbers necessary to read technical books and articles on radio.

MAEDEL PUBLISHING HOUSE Room 109
593 East 34th Street, Brooklyn, New York
Send me **MATHEMATICS FOR RADIO AND COMMUNICATION** as checked below I enclose payment therefor with the understanding that I may return the book(s) within 5 days in good condition and my money will be refunded

Name.....
Address.....

- Book I at \$4.00 plus 7c postage.
 - Book II at \$4.25 plus 7c postage.
 - Books I and II at \$8.25 postage prepaid.
- Foreign and Canadian prices 25c per volume higher.

R-L SPECIALS
for IMMEDIATE delivery

PORTABLE AUTOMATIC PHONOGRAPH

Featuring a famous automatic record changer which plays 12-10" or 10-12" records. 3 tube amplifier provides 4 watt power output. Equipped with external on-off switch, volume and tone control and 6" dynamic speaker. Housed in portable carrying case of simulated leather. B6250—Net..... **\$32.95**



WIRELESS PHONOGRAPH WITH AUTOMATIC RECORD CHANGER

No wires to connect. Just plug in and play through radio. 45 minutes of uninterrupted plays of 10 or 12 inch records without reloading. For 110 V. 60 cycle operation. Complete with open type walnut veneer cabinet. Shipping weight 14½ pounds B6200—Net each..... **\$28.50**



Send for **FREE Bargain Bulletin**

R-L Electronic Corp.

731 West Washington Boulevard
Dept. N CHICAGO 6, ILLINOIS

SCR 522 100-156 MC RECEIVER AND TRANSMITTER

Licensed for Railway and Taxicab Use

Transmitter output 12 watts, voice amplitude modulated on any one of four xtal controlled frequencies. Receiver is readily switched to either one of the 4 present xtal controlled channels. Tubes used: 2-832's; 3-12A6's; 1-6G6; 2-6SR7's; 1-12J5GT; 1-12C8; 1-9002; 3-9003's; 1-12A7GT; 3-12SG7's. Super Special. **\$39.95**
*Complete with tubes.

SCR-274-N COMMAND SET

This unit consists of 3 receivers, 2 transmitters, 4 dynamotors, 1 modulator, 2 tuning control boxes, 1 antenna coupling box with RF ammeter, antenna relay and 5000 v., 50 mmfd. W.E. vacuum condenser. Also complete set of 29 tubes with each unit. The receivers cover frequencies of 190-550 kc; 3-6 mc; 6-9.1 mc. Tubes included are: 12SK7—RF amp.; 12K8—mixer; 12SK7—1st IF; 12SK7—2nd IF; 12SR7—diode det. and CW osc.; 12A6 output or AF; Xmters cover freq. of 3-4 mc. and 4-5.3 mc.; tubes included are 1626 master oscillator driving 2 parallel 1625's; a 1629 and a calibrating crystal also included. Each receiver has its own dynamotor and another dynamotor powers the transmitter and modulator. Terrific Value. Complete ready to operate... **\$39.00**

BC 348 RECEIVER

Built for continuous duty, this band switching, six band receiver with a freq. range of 1,500 kc. to 18,000 kc. Has automatic noise compensator—constant sensitivity on all bands—output at 300 or 4000 ohms—xtal filter AVC-MVC-BFO; Smooth vernier tuning; 90 turns of tuning for ea. band. Tubes include: 1st RF—6K7; 2nd RF—6K7; RF Osc.—6C5; 1st Det.—6J7; 1st IF—6K7; 2nd F and CW Osc.—6F7; 3rd IF and 2nd Det.—6B8; Aud. Out.—41. (Conversion kit available for 110 v. operation 60 cy.—price on request.) Conversion instructions and schematics furnished with each unit. **\$49.50**

TELEVISION FOUNDATION KIT

The television foundation kit consists of the most essential (and expensive) parts needed in the construction of a television receiver starting with the high voltage power supply, for the picture tube right through to the antenna. The kit contains the high voltage picture tube transformer (for five or seven inch tube), 2X2 filament transformer, low voltage transformer for the receiver, cathode ray filament transformer, filter choke, 6.3 filament transformer for the 16 six volt tubes along with the five volt transformer for the 5U4. The two high voltage filter condensers, blocking oscillator, transformer all R.F.'s sound and video I.F.'s, peaking coils, discriminator transformer. Rectifier tubes 2X2 and 5U4, the picture tube 5BP4, an all aluminum Elincor dipole antenna are also included. Of course there is the easy-to-follow 28-page instruction book, with a large 12 by 18 schematic diagram. The instructions include television theory, circuit functions, explain scanning, give preliminary voltage measurements, parts layout and final adjustment of the television receiver which facilitates easy alignment without the use of elaborate test equipment. The only knowledge necessary to build this set is the ability to ready a simple schematic diagram. Most radio men will have many or all of the minor parts not included in the foundation kit **\$34.75**

Remaining set of necessary tubes..... **\$14.95**

TRANSVISION TELEVISION KIT

Complete with 7" tube. Thousands of satisfied users..... **\$159.50**

Beautiful mahogany colored plastic cabinet. Fits 5" or 7" tube. Perfect for TRANSVISION Unit. A real jewel at..... **\$44.95**

Available Immediately!

NEW, STANDARD BRAND TUBES

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
1A3	\$.08	37	\$.09	811	\$1.95
1H5	\$.09	38	\$.09	812H	6.90
6AB7/1853	\$.09	39/44	\$.09	813	5.95
6AC7	\$.09	41	\$.09	814	4.49
6AG5	\$.09	45	\$.09	826	2.25
6AG7	\$.09	46	\$.09	828	7.50
6AK5	\$.09	50L6	\$.09	829B	3.95
6AL5	\$.09	70L7	1.59	830B	5.25
6B4	1.29	71A	1.65	832A	3.95
6B6	\$.09	71A	1.65	832A	4.95
6C4	\$.64	954	\$.75	834	2.95
6C5	\$.51	955	\$.75	835	3.00
6C21	12.95	956	\$.75	837	2.50
6F5	\$.51	957	\$.75	838	3.75
6F6	\$.79	958A	\$.75	8193	6.00
6F7	1.25	959	\$.75	7193	4.49
6F8	1.10	9001	1.15	8011	4.95
6G6	1.10	9002	\$.98	0Z4	1.25
6H6	\$.59	9003	\$.98	2X2	\$.84
6H6GT	\$.89	9004	\$.98	3B2A	1.95
6J4	1.50	9005	\$.98	4C35	4.95
6J5	\$.59	9006	\$.98	5R4GY	1.15
6J6	\$.89	10Y	1.50	5T4	\$.98
6J7	\$.80	15E	1.50	5U4	\$.98
6K6	\$.69	HF100	6.95	5Y4	\$.98
6K7	\$.79	HY89	1.65	5Y3	6.00
6K8	1.25	HY615	6.90	5Y4G	\$.98
6L6	1.25	V70D	6.90	5Z3	4.95
6L6G	1.20	100TS/	3.00	6X5	\$.89
6L7	\$.98	VT127A	3.00	2526	\$.98
6R7	\$.98	2C28A	\$.75	35Y4	\$.99
6SA7	\$.90	2C34	1.15	35Z5	\$.99
6SC7	\$.85	2C40	2.60	80	7.50
6SC7	\$.98	2J32	20.00	83V	\$.98
6SH7	\$.65	2J33	20.00	84	\$.90
6SJ7GT	\$.69	2JB51	2.49	117Z3	1.19
6SK7	\$.79	2J56	20.00	250R	3.95
6SL7	\$.89	211	1.25	838	1.50
6SN7GT	\$.69	217C	7.50	865A	2.25
6SO7	\$.89	3E20A/	8.75	872A	2.25
6SR7	\$.89	829B	2.95	884	\$.75
6Q5	\$.98	304TH	9.85	2050	\$.90
6U5	\$.98	307A	6.25	2051	\$.90
6U6	\$.98	4E27/257B	6.49	RK60	1.25
6Y8GT	\$.98	446A	2.65	RK72	3.50
6Y8G	\$.89	6C4	6.4	VF90	\$.75
7F7	1.25	703A	1.49	VR105	\$.75
12SA7GT	\$.99	705A	4.95	VR150	\$.75
12SK7	\$.89	715B	4.95	2225	1.95
12SN7GT	\$.79	800	2.25	2AP1	2.25
12SQ7GT	\$.99	801A	1.75	3AP1	3.45
12K8	1.25	803	8.95	3BP1	2.95
14B6	\$.95	805	3.75	5BP1	3.95
28D7	\$.75	807	\$.95	5BP4	5.45
30	\$.78	808	2.95	5CP1	3.95
34	\$.98	809	1.50	7BP7	7.95
35L6	\$.99	810	1.49	902	2.25
				913	3.00

NO MAIL ORDERS FOR LESS THAN \$5.00
All Tubes are guaranteed with exception of open filaments which are checked before they leave our warehouse. All tubes shipped via Rail Express.

While they last

GENUINE DAMYCO CRYSTAL KIT

"Easy Built" Radio Kits

Give your child a thrill—make him your pal—his own personal radio—place in playroom or by bed. Picks up all local stations with surprising fidelity—scientific—educational—IT REALLY WORKS. Headphone and band, coil, crystal, and special parts, are precisely made to fit the ready cut and drilled mounting base—clear, simple, easy instructions—anyone can assemble this kit and make it work, \$5.00 value. **\$1.45**
Super Special.

SCOOP

FOR BC-348 OWNERS
Converter for Broadcast Band

Convert that BC-348 or other Receivers that tune to long wave bands 200-500 KC without any alteration in your circuit. Our special converter takes power from receiver. Just tune your set to 450 KC and forget it. All tuning is done on converter panel covering 550 to 1600 KC—double conversion means High Sensitivity, Excellent Fidelity, and Higher Selectivity—complete basic kit with schematic and full instructions—less chassis dial and tuning knobs. **\$6.50**
Terrific Buy at.

TELETRON TELEVISION COMPONENTS

Magnetic Deflection Yokes

Cat. No.	Defl. Angle	Horiz. Ind.	Vert. Ind.	Price
DY 18	55°	5 mh	19 mh	\$14.75
DY 2 L	40°	5 mh	22 mh	15.75

BC 375 TRANSMITTER

A complete transmitter giving 150 Watts with a freq. coverage of 200 to 12,000 KC (except for Broadcast Band) in seven tuning units. For alterations refer to Dec. QST for other amateur freq. and AC operations. Also included is the BC 300A antenna tuning unit with variometer and switch, plus PE 73-C dynamotor including relay switches and fuses, etc. Unit comes complete with 5 tubes, 211 oscillator, 211 RF amplifier, 10 speech amplifiers, and 2—211 push-pull modulators. **\$45.00**
A Bargain at.

BC-221 FREQUENCY METER

A superb frequency standard, this stable, heterodyne freq. meter checks up to the 125th harmonic. Fundamental ranges 125-250 and 2000 to 4000 KC. Makes a wonderful VFO accuracy that cannot be beat. Stability better than .005%. Comes complete with tubes, crystal and calibration chart from 125 kc. to 20,000 kc. A simple matter to meet FCC regulations on freq. measurements with this unit. **\$39.50**
Going Fast at.

DYNAMOTOR

Ideal for Summer Use

Attention Hams—12 V. Dynamotor—just the thing for your portable 2 meter rig—low battery drain—235 V. output at 90 mls. No need to worry about hash—filter built in. Can be run at 50% overload and gives up to 150 mls at 215 V. without damage for continuous duty. 6 1/4" x 5 3/4" x 3 1/2" with cover. **\$2.95**
Special.

P.E.-104 POWER CONVERTER

Ideal for Mobile Use

10 Meter—2 Meter Ham Operators—just the item to power that converter for your portable mobile applications in car or aboard boat. This unit has a 6 or 12 V. battery input with switch for easy and quick selection of primary input volt. Excellent volt. reg.—no hash—will power 2 or 3 tubes, output volt, as tested 90 V. D.C. rectified and filtered—50 mls—has octal socket on front to plug in battery power and take out your B+. Volt. available 90 B+, 6 and 14 B+ (Dept. on input volt. either 6 or 12 v. as used) -6 v., -12 v., -51 v., -14 v. Has asynchronous vibrator—well built—compact. 7" x 4" x 3 3/4" complete. **\$3.95**

SELSYN MOTORS

Selsyn II—5 brass housing motors—have a variety of swell uses—ruggedly built—heavy torque and made to rigid Army spec. Made for use on 115 v 60 cy AC. Ideal for remotely controlling your beam ant. and to tell just where it's pointed. Minimize guess work when pinpointing that beam—these motors will not only indicate but will also drive. A steal at \$12.95 pr. Shipping weight Approx. 24 lbs.

JOHNSON COIL

Hams, Experimenters! Just the thing for your antenna tuner—heavy duty hi-volt. insul. coil—ruggedly built—handles up to 750 watts R.F. Turns can be removed to resonate at any of the antenna bands now in use—heavy mycalex insulation, air wound coil made to give lower surface resistance to R.F. by flat winding—complete with 4 mounting lugs. **\$1.49**
Excellent Buy at.

4 mfd V. Oil Filled metal tubular..... **\$ 0.99**
Birnback No. 4175 Feed-through Insulator... **.29**
829 B Socket—Ceramic—Close out—2 for... **.39**
Metal base mike stand with 5 1/2" pipe—will fit any standard mike..... **1.49**
Oil Filled Condensers 1 mfd—1,000 V. 4 for... **1.95**
Beam rotating motor—reversible—3 rpm will rotate 20 meter beam—24 V. AC or DC—a very popular item..... **12.95**
Magnal Scope Socket 14 pin—complete with hi-volt. leads..... **.49**
Carrying case for BC 221 or SCR 211 Freq. Meter complete with canvas cover. Special.. **6.95**

Blocking Osci. Transformers

OT-101H Horiz. Osc.—15,750 Cy..... **\$3.25**
OT-102V Vert. Osc.—60 Cy..... **2.50**

Complete Line of Other Components.
Let Us Know Your Requirements.

NIAGARA RADIO SUPPLY CORP.

160 Greenwich St.

New York City 6, N. Y.

20% Deposit on all orders unless rated. We prepay freight on \$50 orders in U.S.A.

Write for latest Bulletin 5 RN.
All prices F.O.B. New York City.

G&E COLUMN O'BUYS

Immediate Delivery
every item guaranteed!



"Mercury" Electric SOLDERING IRON

Best Quality at bottom prices. 6 ft. (3,000 cycle) approved heater cord with rubber plug. AC/DC. Screw tip. Elements Cartridge Type. Rapid Heating Iron.

No. 4 80-watt 1/2" dia. tip.	Special, ea. \$2.25
	Lots of 6, ea. 1.58
No. 5 100-watt 1/2" dia. tip.	Special, ea. 3.50
	Lots of 6, ea. 2.85
No. 6 150-watt 1" dia. tip.	Special, ea. 4.25
	Lots of 6, ea. 3.60

Handy Radio Shop RATCHET SET

Compact, can be carried in pocket in its sturdy metal container. 1/4" drive tools. Set consists of 4 single hex, 4 double hex and 3 double square sockets, connector, heavy-duty ratchet wrench, Spintite nut driver with plastic handle and Universal driver with cross bar. A high grade set priced amazingly low!



No. 9273 17 pc. set.....only **\$5.50**

2-DAY CLOCK



Westlox Watchman's Clock, an accurate and handy timing device. With slight alterations it can also be used for off-on control of many electrical appliances. Clock is enclosed in an all-metal case, comes with 365 timing faces. Has Hour hand only.

No. 1308 An amazing buy at only **98c ea.**

APPLIANCE CORDS

Ideal for replacements on radios and lamps: 6-ft. 2-wire No. 18 brown rubber cord with plug. No. 9285, lots of 10—20c ea.; lots of 50—18c ea.

RUBBER-HANDLE PLUGS

Heavy duty, top quality, handle grip plugs: fit all appliance cords. Fresh stock. No. 3210. Lots of 10, 12 1/2c ea.—lots of 50, 11 1/2c ea.—lots of 100, 10 1/2c ea.



HI-POWER ELECTRIC DRILL

Heavy duty 3/4 inch capacity drill. Light weight—hand balanced. Three jaw chuck. Oil bronze bearings. Equipped with 6 feet flexible rubber cord and plug. 900 rpm at full load operating at 110V, AC or DC. No. 6202.....\$17.95



AVAILABLE NOW! WHOLESALE ONLY!
Send check or money order—Terms net cash F.O.B. Chicago

Dealers! Write for quantity discounts.

Free! NEW G&E CATALOG

Illustrated. Value-packed with hundreds of other hard-to-get items for Servicemen, Repairmen & Dealers. Send for it now! Coupon brings it fast!



G & E EQUIPMENT SUPPLY CO.

Dept. RN-B, 400 N. Sangamon St., Chicago 23, Ill.

I want your new free Radio & Electrical Repair Parts Catalog.

Name

Address

CityZone.....State.....

plies to the case of a receiver designed for reception of signals over the AM broadcast band (535 to 1605 kc.). This band is illustrated between points A and B of Fig. 5. Let us assume that in a certain locality there is danger of image-frequency interference from other AM broadcast stations assigned to frequencies within this band. Half the width of this frequency band is equal to $(1605-535)/2 = 535$ kc. (point C in Fig. 5 indicates the center of the band). Consequently, if an i.f. higher than this (say 540 kc.) is employed in the receiver, the "image" frequency corresponding to a signal from the lowest-frequency (535 kc.) station in the band will be $535 + (2 \times 540) = 1615$ kc. Since this frequency lies outside of the AM broadcast band, there can be no AM broadcasting station operating on it—hence there is no possibility of image-frequency interference occurring from such a station. The same will be true for any other desired signal of higher frequency tuned in over the AM broadcast band, for its image frequency will lie farther and farther outside of this band. (Of course, this ignores the possibility of image-frequency interference occurring from other types of transmitters of suitable frequency lying outside this band, such as those in the 1700 kc. police band, 2000 kc. amateur band, etc.). Furthermore, the higher the intermediate frequency is made, the further outside the regular broadcasting band will the possible image frequencies be located.

RMA Recommended Standard I.F. for AM Broadcast Band Receivers

It would appear from the foregoing discussion that the problem of image-frequency interference could be easily solved in any receiver design simply by choosing an i.f. high enough so that the frequencies of all possible receivable signals that could qualify as image-frequency signals and thereby cause such interference would lie outside the regular transmitting bands so there would be no transmitters operating on them. Unfortunately, the choice is not a wide-open one for other conflicting considerations in the receiver design may make it impracticable to choose just such an i.f. Some of the more important of these include:

1. The problem of adjacent-channel selectivity. We found that the higher the i.f. employed in the receiver (in order to reduce the possibility of image-frequency interference), the lower will be the adjacent-channel selectivity existing for separation of the wanted signal and any of the possible interfering adjacent-channel signals.

2. The possible danger that other spurious responses, such as harmonic of i.f. direct i.f. response, etc., may occur if too high an i.f. value is employed.

3. The consideration that the higher the i.f. employed in the i.f. amplifier the less the gain per stage realized,

SIMPLIFY YOUR SERVICE WORK

WITH A

DUAL RACK



Holds radio chassis and record changers firmly—any size, any weight, any angle.

- Precision made—sturdily constructed
- Easily assembled and disassembled

NO OTHER SERVICE RACK COMPARABLE

IMMEDIATE DELIVERY

Shipping weight **6 1/2 lbs.**



\$11.85

F.O.B. PHILA.

Friend's 9 North 7th Street
Phila. 6, Pa.

RECORD CHANGER PARTS

Electric Heating Element

FLUX

Repair burned out electric elements of coffee urns, electric stoves, flat irons, toasters, and other electrical appliances. Simply apply Christy Electric Heating Element Flux to the break, turn on the current and PRESTO the job is done and your appliance is ready again for years of satisfactory service. Generous size package (enough to repair 50 elements) sent postpaid for only \$1.00.

ELECTRICAL APPLIANCE REPAIR PARTS

Renual Iron element. Guar. 1 year. Pack- age of 6.....	\$3.12
Toaster element forms. Clear Mica. Fits most toasters. 10 for.....	1.80
Heating element wire. 10 ft. coiled 1/4" O.D. #20.....	2.55
Heating element wire. 10 ft. coiled 3/16" O.D. #22.....	1.77
Hot plate bricks, 5 1/2" diameter. 6 for.....	1.62
Appliance cord. Rubber covered. 20 ft. \$1.00; 100 ft.....	4.50
Ribbon element heating wire. Std. size. 100 ft.....	.75
Percolator elements. Universal. Flat type. 1 yr. guar. 2 for.....	1.20
Element cement. Withstand 3000° F. 1 lb. pkg. \$1.00. 5 lb. pkg.....	3.50
Lead wire. Asbestos covered heater hook- up wire. 10 ft.....	1.00
Iron Cord Sets with complete plug attach- ments. 10 for.....	5.00
Carbon brush set. Assorted. 104 brushes. 15 springs. Complete set.....	3.00

HOW TO FIX IT BOOKS

Modern Electric & Gas Refrigeration... \$5.00
Practical Electricity & House Wiring... 1.50
Armature & Magnet Winding... 1.50
Here is your opportunity to save on repairing your own appliances and to earn extra money repairing appliances for friends and neighbors.

CHRISTY SUPPLY COMPANY

2835 N. Central Ave., Dept. T-156, Chicago 34, Ill.

Sensational Value!

BUILD YOUR OWN

VOLT-OHM-MILLIAMMETER

The model KT 20 kit provides all components, including meter, panel, cabinet, resistors, condensers, tip jacks, control, selector switch, copper oxide rectifier, pre-cut wires—in fact every component and part needed to complete the unit.

THE KIT COMES COMPLETELY ASSEMBLED. Can be wired in 15 minutes. Components and circuit guaranteed to meet the following specifications:

4 A.C. VOLTAGE RANGES: 0-15/75/300/1500 volts.

4 D.C. VOLTAGE RANGES: 0-15/75/300/1500 volts.

2 A.C. CURRENT RANGES: 0-15/150 MA.

2 RESISTANCE RANGES: 0-10,000 ohms; 0-1 Megohm.

Complete kit including all parts assembled and ready for wiring, circuit diagram, easy-to-follow instructions and detailed operating data for the completed instrument.

Only
\$9.50



The New Model B-45 SIGNAL GENERATOR

Self-modulated — provides a highly stable signal. RF frequencies from 150 Kc. to 12.5 Mc. on Fundamentals and from 11 Mc. to 50 Mc. on Harmonics. Modulation is accomplished by grid-

blocking action—equally effective for alignment of amplitude and frequency modulation as well as for television receivers. Self-contained batteries. All calibrations are etched on the front panel. Complete, ready to operate.....

\$27.75

The New Model 670 SUPER-METER

A Combination VOLT-OHM-MILLIAMMETER plus CAPACITY REACTANCE INDUCTANCE and DECIBEL MEASUREMENTS.

D.C. VOLTS: 0 to 7.5/15/75/150/750/1500/7500

A.C. VOLTS: 0 to 15/30/150/300/1500/3000 Volts.

D.C. Current: 0 to 1.5/15/150 Ma. 0 to 1.5 Amp.

Resistance: 0 to 500/100,000 ohms; 0 to 10 Megs.

OUTPUT VOLTS: 0 to 15/30/150/300/1500/3000

CAPACITY: .001 to .2 Mfd. 1 to 4 Mfd. (Quality test for electrolytics).

REACTANCE: 700 to 27,000 Ohms; 13,000 Ohms to 3 Megohms.

INDUCTANCE: 1.75 to 70 Henries; 35 to 8,000 Henries.

DECIBELS: -10 to +18, +10 to +38, +30 to +58.

The Model 670 comes housed in a rugged, crackle-finished steel cabinet complete with test leads and operating instructions. Size 5 1/2"x7 1/2"x3".



\$28.40



The New Model CA-11 SIGNAL TRACER

Simple to operate . . . because signal intensity readings are indicated directly on the meter!

• SIMPLE TO OPERATE—only 1 connecting cable—NO TUNING CONTROLS.

• HIGHLY SENSITIVE—uses an improved Vacuum Tube Voltmeter circuit.

• Tube and resistor-capacity network are built into the Detector Probe.

• COMPLETELY PORTABLE — weighs 5 lbs. and measures 5"x6"x7".

• Comparative Signal Intensity readings

are indicated directly on the meter as the Detector Probe is moved to follow the Signal from Antenna to Speaker.

• Provision is made for insertion of phones.

The Model CA-11 comes housed in a beautiful hand-rubbed wooden cabinet. Complete with Probe, test leads and instructions.....

\$18.75

The New Model 450 TUBE TESTER

Speedy operation—assured by newly designed rotary selector switch which replaces the usual snap toggle or lever action switches.

SPECIFICATIONS:

• Tests all tubes up to 117 volts. • Tests shorts and leakages up to 3 Megohms in all tubes.

• Tests both plates in rectifiers. • New type line voltage adjuster. • Tests individual sections such as diodes, triodes, pentodes, etc., in multi-purpose tubes. • Noise-Test-detects microphonic tubes or noise due to faulty elements and loose internal connections. • Uses a 4 1/2" square rugged meter. • Works on 90 to 125 volts 60 cycles A. C.

EXTRA SERVICE—May be used as an extremely sensitive condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

• Tests shorts and leakages up to 3 Megohms in all tubes.

• Tests both plates in rectifiers. • New type line voltage adjuster. • Tests individual sections such as diodes, triodes, pentodes, etc., in multi-purpose tubes. • Noise-Test-detects microphonic tubes or noise due to faulty elements and loose internal connections. • Uses a 4 1/2" square rugged meter. • Works on 90 to 125 volts 60 cycles A. C.

EXTRA SERVICE—May be used as an extremely sensitive condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

EXTRA SERVICE—May be used as an extremely sensitive condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

EXTRA SERVICE—May be used as an extremely sensitive condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

EXTRA SERVICE—May be used as an extremely sensitive condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

EXTRA SERVICE—May be used as an extremely sensitive condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.



\$39.50

OUR POLICY: • We do not advertise any unit which is not available for immediate shipment from stock. • Less flowery adjectives, more detailed specifications. • All units are sold subject to one year guarantee except when components are damaged through misuse. • We do not solicit orders for any unit that does not meet our requirements for accuracy and honest value. Any item purchased from us is sold with the understanding that it may be returned for full refund after a 10 day trial.

20% Deposit Required
on all C.O.D. Orders.

GENERAL ELECTRONIC DISTRIBUTING CO.
98 PARK PLACE, Dept. RN-5 NEW YORK 7, N. Y.

MONEY-SAVING RESCO THRILLERS



HANDSET SPECIAL!

Ideal for home telephone use. Requires only one 4½-volt battery. Contains single button carbon mike and hi-impedance receiver with built-in push-to-talk switch.

Will Perform up to 500 Ft. Apart!

325 Each Handset 4½-Volt Battery . . . 52c
595 Pair. 3-Conductor Cable in Any Length 2½c Ft. Handsets

Meissner 6-TUBE TWO-BAND KIT

Standard Band: 550-1600 KC
 Shortwave Band: 6-18 MC

Kit includes all parts and tubes. Complete with easy-to-follow step-by-step instructions.

MODEL 10-1199 5-Tube, 1-Band Set **2470**
 MODEL 10-1191 6-Tube, 2-Band Set **2020**

AT LAST! THE BASIC KIT

YOU'VE ALWAYS WANTED!

- All-Metal Cabinet
- Hang on wall—Set on Service Bench
- Individual Compartments

New **IRL** Resistor Kit Contains Complete Variety Needed for Day to Day Work

80¹² Kit Contents

Free! Neat, Handy, Metal Cabinet

- 160 IRC Type BTS New, ½ watt metallized filament Resistors
- 115 IRC Type BTA New, 1 watt metallized filament Resistors
- 35 IRC Type BT-2 2 watt—metallized filament Resistors
- 60 IRC Type BW-½ ½ watt—wire-wound Resistors
- 20 IRC Type BW-1 1 watt—wire-wound Resistors
- 20 IRC Type BW-2 2 watt—wire-wound Resistors
- 22 IRC Type AB 10 watt Power wire-wound Resistors
- 16 IRC Type ABA 10 watt Power wire-wound adjustable Resistors
- 6 IRC Type EPA 50 watt Power wire-wound adjustable Resistors
- 7 IRC Type ESA 80 watt Power wire-wound adjustable Resistors
- 6 IRC Type X-3 Bands—additional bands for adjustable Resistors
- 2 IRC Type MW-2J Bleeder-type Resistors
- 2 IRC Type M-1034 Bleeder-type Resistors

HURRY! JUST A FEW LEFT!

Taylor T-40 RCA 3E29 (829B) **2.95**
 NEVER AGAIN AT THIS PRICE! **4.95**

Write for Big, Value-Packed Bulletin. Include Postage with Cash Orders.

Radio Electric

SERVICE CO. OF PENNA., INC.

7TH AND ARCH STREETS, PHILA. 6, PENNA.
 Branches at 5133 Market St. and 3145 N. Broad St., Phila. Also in Wilmington, Del., Easton, Pa., Allentown, Pa.

although this is not as important as it formerly was since high-gain r.f. pentode amplifier tubes are now available for use in i.f. amplifiers and modern i.f. coupling transformer design has advanced to such a degree that quite acceptable gains may now be realized even at what were formerly considered exceedingly high intermediate frequencies.

Because the many conflicting factors mentioned above make the selection of the i.f. to be used in a receiver under design a more or less arbitrary matter dependent somewhat on the individual preferences of the designer himself, many different i.f. values have been employed in AM broadcast band receivers. Mainly because with the then-existing amplifier tubes and i.f. coupling transformers high-gain could be realized only in i.f. amplifiers employing comparatively low values of i.f., early superheterodynes designed for the AM broadcast band employed comparatively low values of intermediate frequencies, such as 30, 50, 110, 175 and 260 kc. Since there is ample possibility for image interference to occur when such low i.f.'s are used, rather elaborate preselector systems had to be employed to suppress strong and numerous interfering image signals before they could reach the frequency converter (see Fig. 3). Later, (especially with the introduction and popularization of all-wave receivers,) the trend shifted to higher i.f.'s in the neighborhood of 450 kc. and frequencies of 450, 455, 456, 465, 470, etc., became very popular, although 260 kc. still continued to be employed in many auto-radio receivers. It was found that it is possible to use a high intermediate frequency so as to avoid image interference and still retain sufficient adjacent-channel selectivity by employing highly efficient i. f. amplifiers and, at the same time highly effective tuning circuits in the r.f. system. Moreover, by using high-gain r.f. pentode tubes and i.f. coupling transformers of advanced design in the i. f. amplifier, sufficient gain can be obtained.

Finally the RMA made an extensive study of the subject in an attempt to standardize the i.f. value to employ in

receivers designed for the AM standard broadcast band. As a result of this work a standard i.f. value of 455 kc. is recommended and has now been adopted by most manufacturers of these particular receivers.

Observe that when the 455 kc. standard i.f. is employed, the image frequencies (except for a few channels at the upper end of the band) fall above the 535-1605 kc. AM standard broadcast band—on frequencies to which few existing services are assigned for the FCC has pretty well cleared this part of the spectrum to prevent interference. However, in some localities there is still the possibility of image interference from a few stations that happen to be assigned to frequencies at the upper end of the AM broadcast band (see Table 1) if the r.f. signal-tuning circuits of the receiver do not provide a sufficiently high image-rejection ratio to attenuate these signals adequately. Also, the 455 kc. i.f. lies within the 415-510 kc. band used for coastal, marine relay and ship communications, so direct-i.f. interference from them is possible in some localities. However, the use of a suitable wave trap in the antenna circuit, tuned to the intermediate frequency, is effective in minimizing interference from these latter sources. The large majority of AM broadcast band receivers manufactured within the past few years employ the standard 455 kc. i.f.—or some value close to it.

RMA Recommended Standard I.F. for FM and other V.H.F. Receivers

FM broadcasting is now assigned to the very high frequency (v.h.f.) band extending from 88 to 108 mc. Since the image-suppression improvement resulting from the use of each r.f. preselector stage is much less at high frequencies above the standard 535-1605 kc. AM broadcast band (because the selectivity of tuned r.f. circuits decreases as the frequency is increased), a high degree of r.f. preselection at these frequencies becomes rather difficult and expensive to attain. Therefore, most receivers designed for use on the higher-frequency signal bands

ADDITIONAL SUGGESTIONS FOR CONSTRUCTING THE 5" OSCILLOSCOPE

SOME of our readers have experienced difficulty in constructing the unit described in the article "Build this 5" Cathode-Ray Oscilloscope" by Lyman E. Greenlee which appeared in the October, 1946 issue of RADIO NEWS.

Mr. Greenlee has made several suggestions which will simplify the construction process and improve performance. With some tubes, such as the 5CP1, R₂₂ should be 50,000 ohms and R₂₁ should be 300,000 ohms to make the focusing easier. In case ripple from the power transformers is bothersome, try reversing one transformer in its mounting, i.e. turn it around on the chassis. Use large size potentiometers, not midgets. Be sure the cathode-ray tube


socket is wired correctly. Keep grid and plate leads to 6SJ7's as short as possible and shield if necessary. Mount C₃, C₁₄, C₁₇ and C₁₈ as close to the CR tube socket as possible.

The following corrections should be made in the circuit diagram. R₁₃ should be a 10 watt, wire-wound resistor instead of ½ watt. There should be a .1 µfd. condenser between R₃ and R₁ (6SJ7 grid and 884 plate). It is desirable to include a .1 µfd. condenser between the horizontal input and R₃. The line switch, S₁, may be more conveniently incorporated as a part of either R₁ or R₂ and, finally, R₁₁ should be 2 watts in place of a 1 watt resistor.

★ DAVEGA Communications Division ★ ★ ★

★ 68 YEARS OF DEPENDABLE SERVICE TO THE PUBLIC

★ **JUST OUT!** THE NEW NATIONAL NC-173

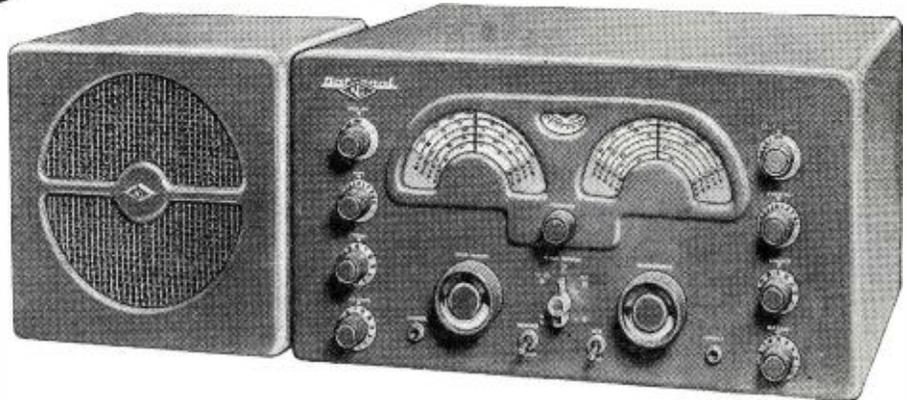

★ Here is a 13-tube circuit, engineered by National to excite any amateur! This NC-173 is the newest in radio technique and exceptional in its frequency scope (6-meter amateur band—0.54 to 31 and 48 to 56 MC). New "Double Diode" noise limiter . . . new AVC system, effective on both phone and CW . . . new high flexible crystal filter . . . voltage-regulated oscillator circuits . . . are but a few of the features to make anyone proud to own this set. Visit any of the nearest Davega stores listed below and judge it for yourself!


**MAIL COUPON FOR
DESCRIPTIVE LITERATURE**

★ The NATIONAL HRO



★ The development of the National HRO-5A1 Radio Receiver brings the famous HRO series to a new high in receiver performance.

★ The NATIONAL NC-2-40D

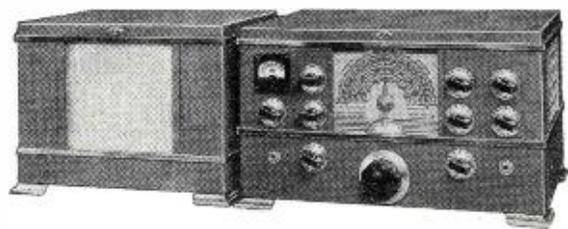

★ This is designed for the radio amateur and for general communications service in the 490 to 30,000 Kc. range.

★ DAVEGA Stores

NEW YORK	NEW JERSEY	LONG ISLAND
Downtown . . . 63 Cortlandt Street	Newark 60 Park Place	Jamaica 163-24 Jamaica Ave.
Hotel Commodore . 111 E. 42nd St.	Jersey City . . . 30 Journal Square	Flushing 39-11 Main Street
	Paterson 185 Main Street	
WESTCHESTER—White Plains		175 Main Street

DAVEGA COMMUNICATIONS DIVISION
63 Cortlandt Street, New York 7, N. Y.
Please send full information on Communication Receivers without obligation.

NAME

ADDRESS

CITY

RN-1




PICK-UP

... AS QUICK AS A WINK... WITH...

Smooth Power

Not a word or a note need be missed when your record players, record-changers or recorders are equipped with *Smooth Power* motors. That's because these units are built for split-second pick-up to full constant speed.

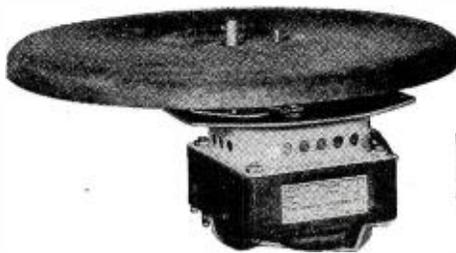Their quietness and freedom from vibration give smooth performance that will delight your customers. From our complete line of *Smooth Power* phonomotors, recorders and combination record-changer recorders, you can select exactly the right units to match your own fine products.



Model GI-RM4 Smooth Power Recording Motor

NOTE TO INDIVIDUAL USERS
Smooth Power Motors are sold only through established trade channels.



DEPT. MR • ELYRIA • OHIO

For the **LATEST** in Test Equipment
at **LOWEST** prices—

... it's **FEDERATED!**



**DUMONT MODEL 274
OSCILLOGRAPH**

Inexpensive yet highly efficient general purpose C.R. instrument for radio servicing and production testing. Uses 5BP1A C.R. tube. Specially adapted for use of colleges, technical and high schools. 7 tubes.
Your Cost... **\$99.50**

**SIMPSON MODEL 260
Set Tester**

20,000 ohms per volt sensitivity, suitable for all servicing jobs. 6 AC and DC ranges to 5000 volts. 6 output ranges, DC Ma 10/100/500, 500 Microamps. Ohms 0-2000/.2 meg/20 megs. Also -10/52 db.
Your Cost... **\$38.95**



RCP 449-P POCKET TESTER

Remarkably accurate and versatile multi-tester, and output vol. for general circuit testing and trouble shooting. DC and AC volts 0-5-50-250-1000. DC Ma .5-10-100-1000. Ohms 0-1000-10,000, -.1 meg -1 meg. Db. -6 to .52 db.
IN HANDSOME STURDY PORTABLE HARDWOOD CASE. Your Cost... \$28.50

OTHER STANDARD TEST EQUIPMENT IN STOCK for Immediate Delivery
MAIL ORDERS: 25% Deposit. Balance C.O.D.

Federated Purchaser
INCORPORATED
distributors of **RADIO - ELECTRONIC**
and **SOUND EQUIPMENT**
80-88 PARK PLACE, N. Y. 7
Phone: WH 4-2080

**PRECISION MOVEMENT
DEPENDABILITY UNLIMITED**

**Burlington
INSTRUMENTS**

Alnico Magnets in all DC Instruments—phosphor bronze control springs—perfectly aligned jewel supports—non-shifting balance weights—added to many other superior construction features enables Burlington to maintain critical characteristics.

All ranges AC or DC available in 2 1/2", 3 1/2", 4 1/2" sizes, rectangular and round.

Inquiries invited for your specific requirements.

BURLINGTON INSTRUMENT COMPANY
914 Fourth Street Burlington, Iowa

such as those used for FM and television broadcasting, depend more upon the use of a high i.f. *especially selected* to throw the image frequencies outside of the frequency band in which there is likelihood of interfering transmitters being assigned, than they do upon the use of r.f. preselectors to attenuate image-frequency signals before they reach the frequency converter.

Receivers for service above 20 mc. should employ higher intermediate frequencies than do those for use on the 535-1605 kc. AM broadcast band, not only for adequate image suppression but also for ease of tuning and alignment. Attempting to tune in signals of this order when a 455 kc. i.f. is employed becomes extremely difficult, even with high-ratio vernier dials and very stable oscillators. Under such conditions, the percentage difference between the signal and oscillator frequencies becomes very small, and even normally stable oscillators have a tendency to "lock in" and to be otherwise influenced by the signal circuit during the tuning process. Even small amounts of coupling between the oscillator and signal circuits (through space-charge coupling within the tube, or from other causes) will sometimes cause appreciable amounts of current at oscillator frequency to flow in the latter and introduce harmful effects. Use of a high i.f. will tend to prevent these difficulties.

With the increasing popularity of FM which results in more and more transmitters in close proximity laying down strong local fields, the use of high values of intermediate frequency in FM receivers has become mandatory in order to reduce the spurious responses even though these higher values of i.f. make the realization of satisfactory gain and stability more difficult and expensive to attain. Hence design engineers have been forced to compromise on values of i.f. which result in acceptable gain and stability with the minimum of spurious responses. This compromise has been aided considerably by the development of better components for the amplifiers.

A few years ago when the assigned standard FM broadcast band extended from only 42 mc. to 45 mc., an i.f. of 2.1 mc. was used in some of the early FM receivers. Later, an i.f. of 3.2 or 3.3 mc. was employed. The FM band was later extended to cover from 42 to 50 mc. To eliminate image response due to FM stations in this band an i.f. greater than 4 mc. had to be used. A value of 4.3 mc. was chosen and became standard. This was satisfactory because, since the oscillator frequency in these receivers was made *lower* than the signal frequency, and the i.f. had to be made more than one-half of the total band, using an i.f. of 4.3 mc. made the first image

⁵ This is contrary to the practice commonly employed in AM broadcast band receivers because it is desirable to reduce the frequencies at which the oscillator must operate.

HERSHEL *Offers*

BETTER BARGAINS . . . BIGGER BUYS

CONDENSERS

Cat. No.	Cap. MFD.	Working Volts	Your Cost
C110	1	5000 Oil	\$3.95
C111	3	4000 Oil	\$4.95
C112	1	1000 Oil	44c
C114	5	600 Oil	95c
C115	2	600 Oil	49c
Westinghouse	1 MFD	6000 volts WVDC	\$7.95
Westinghouse	1 MFD	10,000 volts WVDC	\$12.95

CHOKES

Thordarson 8 HY 150M choke, Cat. No. FC-201	95c
Thordarson 8 HY 175M choke, Cat. No. FC-202	\$1.49
Thordarson 12 HY 25M choke, Cat. No. FC-203	39c
Thordarson 8 HY 350M choke, Cat. No. FC-204	\$4.95

FILAMENT TRANSFORMERS

Thordarson 6.3 V-4 amps., 6.3 V-4.5 amps., 9.7 V-5 amp., pri. 110 V AC 25 or 60 cy.—Cat. No. FT-11	\$1.95
Thordarson pri. 110 V 60 cy.—sec. 6.3 V 6 A, CT—Cat. No. FT-12	\$1.49
Thordarson 110 V 60 cy. pri. sec. #1-2.5 V, 10 A Ct, 3000 V Ins., sec. #2 10 V 3.25 A, Two 5 V 3 A; 6.3 V 1 A—Cat. No. FT-13	\$4.95

MICA CAPACITOR
.002 MFD 3000V VDC. Cat. No. RT-101 **49c**

IF TRANSFORMER
Mounted in aluminum shield can 1500 KC, with air trimmer, impedance coupled type. Cat. No. T-19 **95c**

30MC IF TRANSFORMER
In square aluminum can, silver slug tuned. Cat. No. T-20 **29c**

RECEIVER AND TRANSMITTER

SCR-522. 100-156 MC receiver and transmitter. Used in good condition. Cat. No. RT-10 **\$995**

HALLICRAFTER RECEIVER

R45/ARR7—contains xtal filter, variable I.F. selectivity A.V.C. and A.N.L. B.F.O. patterned after SX28A Hallicrafter, voltage regulator complete with tubes and power supply components for 110V operation. Cat. No. SX28A **\$139.50**

SELSYN MOTORS

The ideal way of indicating the position of rotary beams, wind indicator, etc. (400 cycle). Line cord and instructions for 110 VAC operation furnished.—Cat. No. SM-100 **2 for \$3.95**

R44/ARR-5 HIGH FREQUENCY

receiver. Patterned after S-36A by Hallcrafters. Receives FM and AM signals in the spectrum between 28 and 145 megacycles. Circuit has 14 tubes including voltage regulator for high frequency oscillator. Has two position selectivity control. Contains no internal power supply. Has acorn tubes RF, Osc., and Mixer. Complete with components for power supply including transformer, choke, filter condensers, and rectifier tube **\$100.00**

ALL ORDERS F.O.B. DETROIT

MINIMUM ORDER — \$2.00

Mich. Sales add 3% Sales Tax

Write for **FREE** Bulletin



NEW BC 223 AX TRANSMITTER

801 Oscillator and 801 Power Amplifiers, 2-46 Modulators and 1-46 Speech Amplifier 4 Xtal Frequencies and Master Oscillator on selector switch. 10 to 30 watts output. Tone Voice or C. W. Mod. Ideal for 80 meter band. Comes with 3 coils TU 17A 2000-3000 Kc. TU 18 3000-4500 Kc. TU 25 3500-5250 Kc. Black wrinkle case. Includes 2 separate cases to store extra coils. Frequencies chart and tubes included, packed in original cases, less crystals at this low price. **\$29.95**




BC 654 TRANSMITTER & RECEIVER


Frequencies range 3800-5800 Kc—calibration every 10 Kc.—with crystal oscillated checked every 200 Kc.—power output 17 wat's. voice or CW **\$795**

1 KW MODULATION TRANSFORMER

\$14.95 BUY NOW AND SAVE

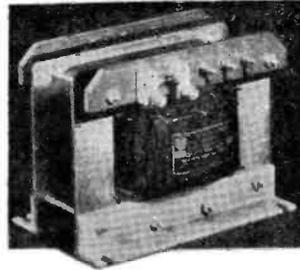

RCA modulation transformer is conservatively rated at 550 Watt audio to modulate that new KW rig. Really rugged construction with protective flashover gaps, which are adjustable. Terminals and gaps are mounted on a "Mylacex" terminal board. The laminations that make up this transformer are of high audio quality and are extremely thin, making it impossible for the core to "chatter or talk." Audio Watts—550 Sec. #1—450 Mils Sec. #2—80 Mils Turns Ratio—Pri. Sec. #1-1:1 Pri. Sec. #2-5:1 Pri. Sec. #2 Top—25:1. Impedance Ratio—Pri. #1-1:1 Sec. #1-1:1 Sec. #2-25:1 Pri. Sec. #2 Top—625:1. DC Resistance—Pri. 135 ohms Sec. #1. 112 ohms; Sec. #2. 99 ohms. Transformers insulation tested. Pri. 8000V.; Sec. #1-11,000V.; Sec. #2-20,000V. to the rest of the coils and core. Primary center-tapped for Class "B" modulators. Secondary #2 will carry 80 Mils to modulate screens of beam power or screen grid tubes. Primary will match any Class "B" tubes up to 10,000 ohms plate to plate, such as 810's, 75T's, 8005's, 2B120's, 203's, HY512's, 211's, 813's, 828's, 805's, 203Z's. Size 9 1/2" wide, 7 1/2" deep, 7 1/4" high. Heavy channel iron mounting brackets. Weight approx. 40 lbs. Catalog number MT-100.

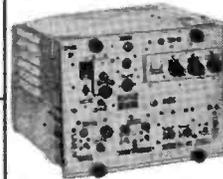

BN-11FF Transmitter & Receiver

Transmitter and receiver. The famous boat anchor, widely used on 1.44 MC band. Shipping weight 100 lbs. Your price, less tubes and power transformer. **\$14.95**



TUNING UNIT

Tuning Unit BC 375. Approx. 65 M.M.F.D. cond., coils, RF chokes, dials, asst'd mica condensers. 2500 WVDC, over \$50.00 in parts. Cat. No. TU-101 **\$375**




BUTTERFLY CONDENSERS

Type B—frequency range 300 to 1000 megacycles to be used with 368AS door knob tube. Cat. No. BC-2. **95c ea.**


DYNAMOTOR

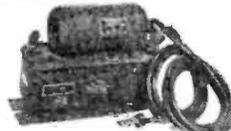Power supply—inputs 6 or 12 V, output 500 VDC at 160 MA, mounted on box with circuit breakers, relays, interference filter and two 10 ft. cables. U. S. Govt. surplus. Cat. No. DM-101. **\$9.95**



TUBES

813	5.45
RK60	1.25
VT127	2.95
VR150	.69
829	2.45
872	1.95
211	1.45
368AS	4.95

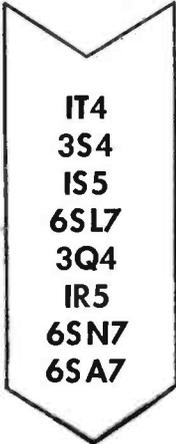

59¢ each

HOT SPOT SPECIALS

Ass't resistors 1/2 watt fully insulated, in popular ohmages. Cat. No. R-5—per 100. \$1.49
Ass't mica condensers, Cat. No. C-12—per 100. \$1.95
Water sockets, 4-5-6-7 and 8 prong. Cat. No. WF-4—per 100. \$2.95
12" Utah P. M. Speaker, Alnico .25 with 6F6 output transformer. Cat. No. ST-100. \$6.95
Ass't knobs push on wood and plastic. Cat. No. KP-100—per 100. \$1.95
6J4. \$1.50
6J6. 95c
Johnson sockets #210-25W. Cat. No. JS-210. 49c
955-9004 tubes. Cat. No. T-99. 65c
Sockets for acorn tubes. Cat. No. AT-10. 19c
8-8 MFD 350 WVDC; 20 MFD 150 WVDC, round can. Cat. No. RC-8B. 69c
Hallicrafter volume knobs—SX 28. 15c
Pots—screw driver shaft, 2 meg., 1 meg., 150M, 50M, 25M, 5M, 2M, 200 ohm—ea. 29c
A 144 MC Radar Osc., uses 15 E or Hy 75. Enclosed silver plated tank with variable coupling. Complete less tube. \$3.95
Jacks PL 55, PL 68. 15c
Powdered iron slug with Isolantite coil form to match, ideal for broad tuning E.C.O. 25c
Powdered iron 3/8 slug. 10c
1 Meg. Shallcross Acra—Ohm wire wound resistors
±1W 89¢

HERSHEL RADIO CO.

5249 GRAND RIVER

DETROIT 8, MICHIGAN

20% DEPOSIT REQUIRED ON ALL C.O.D. ORDERS

Just 3 JFD
ADJUSTABLE BALLASTS

Replace Over **3000** Exact Duplicate AC-DC Resistance Tubes!

New features!

- ✓ 1. Air-Cooled Perforated Shell
- ✓ 2. Larger Insulating Surface
- ✓ 3. Longer Life, Heavier Resistance Wire
- ✓ 4. Exact Adjustments made

List Price \$1.50 each

USE JFD BALLASTS	TO REPLACE AC-DC RESISTANCE TUBES		
	Beginning with	With Numbers	Ending with
"A" Ballasts	K, L, M, BK, BL, or BM	6 through 42	A, B, C, D, F, G, or H
"B" Ballasts	K, L, M, BK, BL, or BM	45 through 105	A, B, C, D, F, G, H, S1, S2, S3
"C" Ballasts	All 4 prongs	80 through 350	R, R4, R8, L, L4, L8

J.F.D. Manufacturing Co.
4111 Ft. Hamilton Parkway Brooklyn 19, N. Y.

JFD
PRECISION
MADE

NOW
The TOWER
You've Been
WANTING!

For Directional Beam Antenna and dozens of other uses.

RUGGED
Aluminum alloy throughout. Guaranteed to support 200 lbs. with an area of 5 sq. ft. in 70 mile wind!

SIMPLE
Triangular, tapered, self-supporting, light weight, 30 ft. tower can be assembled anywhere, using only wrenches, erected by hand. Ladder rungs built into one side.

ECONOMICAL
Buy the height you need: 10, 20 or 30 feet. All fastenings and metal parts of footing furnished. Reasonably priced.

Write immediately for Brochure **FREE!**

FABRICATED LIGHTMETALS CO.
42 W. 15th ST., NEW YORK 11, N. Y.

CLARION SPECIALS

FILTER CHOKES
F-115 50 by @ 370 ma. Hi-Voltage insulation & insulators...\$4.75
(Illustrated)
F-102 Raytheon 25 by @ 65 ma. DC insulated for 1780 R.M.S. volts\$1.15

Oil Filled Transmitting Capacitors
C-123 Cornell-Dubillier 4 mfd. 1500 volts. \$1.75 or 2 for\$3.00
(Illustrated)
C-124 Cornell-Dubillier 1 mfd. 1000 volts. Rectangular can. 50c or 4 for\$1.75
C-120 Rectangular can. 1 mfd. 400 volts. 30c or 6 for\$1.50

M-110 WESTERN ELECTRIC SOUND POWERED MICROPHONE. Complete with chestplate and 20 ft. of high grade mike cable...\$6.50
With 50 ft. length of cable....\$7.50

Altec Lansing Speakers, Amplifiers and Transformers—Magnetic Wire and Tape Recorders—Sound Equipment.
SEND for our BARGAIN FLYER 30% Deposit with COD's Min. Order \$3.00.
Many other items & specialties. Quality sound & recording equipment.

CLARION SOUND ENGINEERING CO.
363 Victory Boulevard
STATEN ISLAND 1, N. Y.
Phone: Gibraltar 7-8975

response occur at 33.4 mc. ($4.3 \times 2 = 8.6$ mc. below the signal frequency)—which was out of (below) the prescribed FM broadcast band of 42-50 mc.

The introduction of the 6SH7 high frequency pentode amplifier tube provided considerable improvement in over-all stability since its plate-to-grid capacitance is very low and separate cathode prongs are provided for the grid and plate return circuits, thus reducing the coupling between these two circuits to a minimum. It aided in improving these 4.3 mc. i.f. amplifiers.

The postwar expansion of the standard FM band to 88-108 mc. has made necessary another upward revision in the i.f. employed in FM receivers. The RMA recommended i.f. value is now 10.7 mc. This frequency has been chosen so that no image-frequency interference from other FM broadcasting stations in the FM band occurs in these receivers. Here again, the same reasoning has been applied for the selection of the standard i.f. to be employed. One-half of the total FM band is $(108-88)/2 = 10$ mc. Therefore in order to throw the first image response outside of this prescribed band, the i.f. had to be made something more than this 10 mc. value. The RMA has settled on a value of 10.7 mc. as the best all-round compromise for the i.f. value to be used in postwar 88-108 mc. FM broadcast and other v.h.f. receivers. (The former prewar 4.3 mc. standard i.f. is now obsolete.)

RMA Recommended Standard I.F. for Television Broadcast Receivers

Three v.h.f. bands, 44-50 mc., 54-72 mc., and 76-88 mc., have been assigned for television broadcasting. Since the total band covers $88 - 44 = 44$ mc., this requires an i.f. in excess of $44/2 = 22$ mc. in order to eliminate the possibility of image-frequency interference from other television broadcasting stations. Television receivers employ two separate i.f. amplifier channels, one for the sound channel and one for the picture (video) channel. The following standard i.f. values have now been recommended by the RMA for use in these receivers:

1. The sound-channel i.f. shall be located in the region 21.25 to 21.9 mc. and oscillator frequency shall be higher than the incoming signal frequency.

2. The video channel i.f. shall be 26.4 mc. (pre-1941 television receivers generally used a sound channel i.f. of 8.25 mc. and video i.f. of 12.75 mc.).

The Final Choice of I.F.

From what has been presented in this discussion it is apparent that choice of the intermediate frequency to be employed in a superheterodyne will depend, in the final analysis, upon the signal frequency band over which the receiver is to operate and the class

PROMPT SERVICE ON
SPEAKER AND PHONO
PICKUP-REPAIRS

MAY LEOTONE SPECIALS

Minimum Order \$2.00—20% Deposit Required
on all orders. Please Add Sufficient Postage.
WRITE DEPT. RN-5.

- DEFLECTION YOKE for 5" cathode ray tube. Fully shielded. 1 1/2" I.D. 3" sq. \$2.49
- DYNAMOTORS (Navy DY-9) DC input: 26V. D.C. output: 360V @ 135MA or 310V @ 355MA. Black crackle finish, with mtg. base 6 1/2"x3 1/2" 3.95
- Co-axial Cable. RG-13/U. 74 ohm, double copper braid, outside vinyl jacket. 420" O.D. With 2 connectors. 20 ft. lengths. 1.69
- Speaker Grille Cloth. Gold or silver weave—sq. ft. #36 D.C.C. enam. wire. Per lb.—1.95; 1/4 lb. spool .89
- SELSYN SYNCHRO-TRANSMITTERS. 115V. 60 cycle. Used in pairs as trans. & follower. 3 1/2" x 5" each 3.75
- SELSYN Control Transformers (#21G1) 57.5-57.5V. 400 cycle. 2 1/4"x4" 1.95
- Wall Toggle Switch (C-3). S.P.D. 3/4" 12V. .39
- RADIOMAN'S HARDWARE TREASURE. Approx. 1000 screws, nuts, washers, etc. .49
- Clear ACETATE for dials, windows etc. (018) 3"x3" .10 7"x7" .45 12"x12" 2.89
- 5"x5" .25 9"x9" .65 sheet 22"x35" 2.89
- EXPERIMENTAL TUBES. 20 asstd. sizes & base types for testing, research, etc. Fil. tested. 1.00
- PHONO MOTORS—110V. AC quiet rim-drive motor and 9" rocked turntable. 8 for \$2.95
- 12" Turntable Felts. Brown or Green. 1.00
- Brand new RCA UX-200 tubes in sealed cartons. Ideal triode detector. 8 for \$2.95
- TUBES: perfect condition, but not in sealed cartons. Guaranteed for 90 days. #26, 27 or 56—29; #24, 42, 45, 75, 77, 80, 5Y3, 6H6 or 6K7 #8A5, 6C5, 6P5, 6J7, 6SA7, 6SK7, 12SA7. .49
- #1A7, 6A3, 6G5, 6U5 or 50. .59
- SPEAKER GRILLES. 5 1/2" sq. Flock musical design on slit perforated metal. .19

ALNICO MAGNETS




- #1—Bar. 1/4"x1/4" (max. length 4") per inch. \$0.12
- #2—Face 1/4"x1/4"x3/8" high. .98
- #3—Heavy duty bar. 2 1/2"x1 3/8"x5/16" .98
- #4—Face 3/4"x5/8"x3/8" high. .39
- #5—Polished. 7/8"x9/16"x5/8" high. .35
- #6—Polished bar. 9/16"x1/4"x3/8"—20 for 1.00
- #7—Face 1/2"x1/2"x3/8" high. .10
- #8—ALNICO V. horseshoe. poles 3/8" sq.; 1 1/2" high. .75
- #9—ALNICO V. horseshoe. poles 9/16" sq.; 1 1/2" high. .98
- #10—ALNICO V. horseshoe. poles 1 1/2"x1/2"x2 3/4" high. 5.95
- #11—Horseshoe. ea. pole 1 1/16" O.D.; 2 1/4" high 1.29
- #12—Similar to #5 3/4"x3/8"x7/16" .35
- #14—Polished by. duty bar. 3"x1 1/4"x7/8" (magnetized lengthwise, wide or narrow sides) 1.29
- #15—Polished Block. 3"x2 3/4"x1 1/2" magnetized wide or narrow sides. (wt. 3 lbs.) 2.49
- #16—Flat Bar. 1 7/8"x15/16"x5/16" thick. 1/4" groove each end. .49

SERVICEMEN'S KITS

- #1—R.F. Antenna & Osc. coils. 10 asstd. \$0.98
- #2—Speaker Cones: 12 asstd. 4" to 12" moulded & free-edge (magnetic incl.). Less voice coils. 2.00
- #3—Bakelite Mica Condensers: 50 asstd. .00001 to .2 mfd., 200-600WV. Clearly marked. 2.95
- #4—Tubular By-Pass Condensers: 50 asstd. .001 to .25 mfd., 200-600WV. Standard brands. 2.49
- #6—Dial Scales: 25 asstd. airplane & slide-rule acetate & glass included. 2.98
- #7—Escutcheon Plates: 25 asstd. airplane, slide-rule & full-vision types. 2.95
- #8—Knobs: 25 asstd. wood & bakelite incl. push-on, set-screw & push-button types. 1.00
- #9—Water Sockets: 12 asstd. 4 to 7 prong .25
- #10—Voltage Dividers: 10 asstd. standard, multi-tapped. Hi-wattages included. 1.98
- #11—Shield Cans: 15 asstd. for coils, tubes, transformers, etc. 1.00
- #12—Mica Padders & Trimmers: 15 asstd. incl. multiple & ceramic base types. .69
- #14—Volume & Tone Controls: 10 asstd. wire-wound & carbon. Less switches. 1.49
- #15—Wire-wound Resistors: 15 asstd. ohmages, 5 to 20 watts; incl. enameled & candohms .98
- #16—F Coils: 6 asstd. including shielded & slug-tuned. Peaks unmarked. 1.95
- #17—Dial Windows: 12 asstd. sizes incl. flat & moulded acetate and convex glass 1.29
- #18—Bakelite Coil Forms: 18 asstd. popular sizes up to 3" diam. .98
- #19—High Resistance Units: 25 asstd. carbon, ferrule-ended. 25000 to 5 meg. ohms. .49
- #20—SPEAKER REPAIR KIT. A real money & time saver. Contains: 20 asstd. paper rings, 10 spiders, 25 asstd. voice coil forms, 3 yds. felt strips, 20 chamois leather segments, kit of 16 shims & tube of spkr. cement. All for 2.49
- #21—Metal Cased By-Pass Condensers: 20 asstd. paper-wound, multi-section: 200-400WV .98
- #22—Resistor Assortments: 20 carton & wire-wound, 1/4 to 3 watts. .49

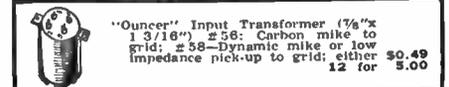- Filter Choke. 15 henry, 1200 ohms DC, 50 ma. 2"x1 5/8"x1 3/8" \$4.49
- 4 TUBE AMPLIFIER (2-7C6, 7F7, 7F4) Used as electronic supercharger control, 110V, 400 cycle. Black crackle finish case & slide-in chassis. Contains: power trans., 7 mica & oil cond., 7 resistors, 4 local sockets plus other components worth several times the price. 8 3/4"x4 1/2"x3 3/4". Less tubes 1.49



- ALUMINUM PANELS (.072"): 8"x8" \$0.39
- 8"x8" .49; 8"x10" .59; 8"x15" .79
- BAKELITE PANELS: 1 1/2" glossy brown, 7"x10" .59
- 7"x14" .59; 7"x18" .79; 9"x14" .85
- 1 1/2" Linen Bakelite Strips, 11"x1 1/2"—3 for. .25
- PRECISION RESISTORS. ± 1% wire-wound. Ohmages: 2.35, 11, 24.5, 100, 840, 7800, 30K. 50K or 400K .35
- Frequency Meter tech. manual (Navy) Theory & operation. 39 illust. & diagrams, 58 pp. .15
- Victor Power Transformer for models R-32, 45, 52 or 75. Unshielded. 5.95

- HEADBANDS (HS-33) with PL-54 plug & cord. \$3.39
- PL-54 Plug & 13" tipped double phone cord .19
- JK-26 ext. Jack for PL-54. Bakelite shell. .23
- HEADPHONES—Army HS-33. 2000 ohms. Leather covered, adj. forks. With PL-54 plug. 1.25
- Rubber phone cushions for above, per pair. 20

MAKERS OF CONES AND FIELD COILS
65-67 DEY STREET, NEW YORK 7, N.Y.
WORTH 2-0284-5
12,000 SQ. FT. OF RADIO PARTS

NOW AVAILABLE FOR IMMEDIATE DELIVERY FROM STOCK!

The New Model 670 SUPER-METER



A Combination VOLT-OHM-MILLIAMMETER plus CAPACITY REACTANCE INDUCTANCE and DECIBEL MEASUREMENTS.

Added Features: The Model 670 includes a special GOOD-BAD scale for checking the quality of electrolytic condensers at a test potential of 150 Volts.

SPECIFICATIONS

- D. C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Vo'ts.
- A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts.
- OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts.
- D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5 Amperes.
- RESISTANCE: 0 to 500/100,000 ohms; 0 to 10 Megohms.
- CAPACITY: .001 to .2 Mfd., .1 to 4 Mfd. (Quality test for electrolytics).
- REACTANCE: 700 to 27,000 Ohms; 13,000 Ohms to 3 Megohms.
- INDUCTANCE: 1.75 to 70 Henries, 35 to 8,000 Henries.
- DECIBELS: -10 to +18, +10 to +38, +30 to +58.

Housed in a rugged, crackle-finished steel cabinet complete with test leads and operating instructions. **\$28.40**
Size 5 1/2" x 7 1/2" x 3"

Please place your order with your regular radio parts jobber. If your local jobber cannot supply you, kindly write for a list of jobbers in your state who do distribute our instruments or send your order directly to us.

SUPERIOR INSTRUMENT CO., 227 Fulton St., Dept. RN-5, New York 7, N. Y.

WAR SURPLUS SALES
RADIO - ELECTRICAL - ELECTRONIC EQUIPMENT - PARTS - SUPPLIES

WILCOX F3 6 Tube Receiver \$13.95



This receiver is equipped with a radio frequency sensitivity control, an audio gain control, automatic volume control and an inter-carrier noise suppressor. The audio amplifier is capable of producing zero level db output across a 500 ohm load.

The F3 Receiver is a crystal controlled super-heterodyne receiver consisting of a single stage radio frequency amplifier, an oscillator-mixer, a single stage intermediate frequency amplifier, a second detector and automatic volume control voltage amplifier, and an inter-carrier noise suppressor and audio output stage.

Brand New, in original carton; complete with set of 3.5 to 6.1 meg. coils and set of spare tubes; 110 VAC 60 cycle. Tubes 2-6K7, 1-6K8, 1-6F7, 1-6C8G, 1-80.



BEEDE METER

Brand New, in black finish bakelite case, 2 3/4 inch square. 0-1000 MA DC. While they last only **\$1.95**

6 TUBE Brand New Receiver with tubes Only \$5.95

Receivers of the SCR-274-N(AN/ARC-5) Series. All-aluminum aircraft receivers 5" wide, 8" high, 12 1/2" long; weight 6 1/2 lbs. Joint Army-Navy nomenclature is R-23/ARC-5, R-26/ARC-5, &c. and these sets are finished in black wrinkle enamel. Signal Corps nomenclature is BC-453-B, BC-454-B, &c. and these sets have no enamel on the sheet-aluminum covers and chassis.

Technical Description

Power required is 250V @ 50MA for B and 25.2V @ 0.45A for the heaters which can easily be rewired for 12.6V @ 0.9A. The output transformer is tapped for either high or low impedance headsets. Voice, MCW, and CW reception. Antenna-tuning trimmer control on front panel. All trimmers and the padder are air-dielectric variable capacitors. The coils and IF cans are plug-ins. Typical tube line-up is: 12SK7 RF, 12K8 Converter, two 12SK7 IF's, 12SR7 Detector and BFO, 12A6 Output, gas-filled antenna-signal voltage limiter, and gas-filled output signal voltage limiter. Each set comes complete with all tubes in sockets. Item 1: 3 to 6 Meg. less dynamotor; Item 2: 6 to 9.1 Meg. less dynamotor

SUPERIOR 2 KVA Power Stats; input 115 volt AC, 50-60 cycle single phase,—output voltage range 0-135 volt; maximum rated output current 15 amp available over entire range of output voltage; weight approx. 20 lbs. **\$29.50**

SUPERIOR 2 KVA 3 1/2 KW power stats, 2 in tandem, each 115 volt AC single phase. Same as the above but twice the input and output voltage. **\$54.50**

HIPOWER quartz Crystal units, type CF5, 5000 KC, complete with holder. **\$1.95**

Prompt Delivery—Write Dept. RNM
25% deposit required on C.O.D. order

Shipped F.O.B. New York. Min. Order \$2.00

MICHAEL STAHL, INC.
39 VESEY ST.
Tel. Cortland 7-5980 New York 7, N. Y.

of service for which it is to be used. The RMA has recommended standard values for the i.f.'s to be employed in AM, FM and television broadcast receivers, and most of the manufacturers of these receivers are now employing these values. Receivers designed for services other than these can be expected to employ other i.f. values, depending upon the designer's preference arrived at after careful study of the existing conditions and all the conflicting factors involved.
(To be continued)

What's New in Radio

(Continued from page 88)

and connections, or for looping wire if it is to be used.


The insulator ends are machined to fit the inside diameter of standard aluminum or dural tubing having 1" o.d. For smaller tubing, the insulator ends can be turned down to fit the required size.

James Knights Company of Sandwich, Illinois will supply additional information upon request.

RESISTOR BALLAST

A new plug-in type resistor ballast is currently in production at the JFD Manufacturing Company's plant.

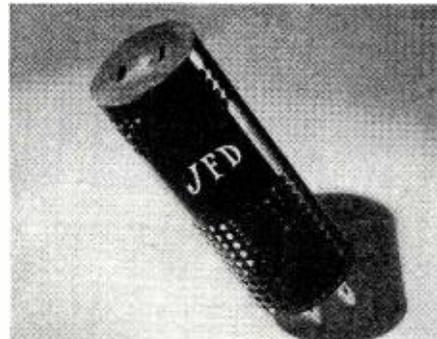This ballast is designed to convert 110 volt radios and electrical appliances for use on 220 volt circuits. The ballasts are available with American, British, and Continental male plugs;



the female sockets are American. This JFD Step-Down Ballast may be used with radios, electric razors, fluorescent fixtures, phono-radio combinations, electric clocks, electric blankets and other electric appliances.

Descriptive literature covering this new ballast will be forwarded upon request to Department RN, JFD Manufacturing Co., 4117 Fort Hamilton Parkway, Brooklyn 19, New York.

BUILT-IN RADIO

Reeves Sound Studios, of New York, has recently announced a new built-in radio and sound system which is engineered to be a functional part of a home.

Known as the Reeves "Soundcraft Radio," the unit consists of four major parts; a portable tuner, an amplifier, a record player, and one or more speakers, plus an antenna and necessary wiring.

ELECTRONIC COMPONENTS

- Socket for 5CP1 & 3BP1 \$0.90
- New 5CP1 shields with bracket & grommets, cad. plated (3-lbs.) 1.25
- NEW TUBES**
- 954 Acorns postpaid. 89c | 957 Acorns postpaid. 89c
- 955 Acorns postpaid. 89c | 9002 Tubes postpaid. 89c
- 956 Acorns postpaid. 89c | 1625 Tubes postpaid. 89c
- New National ceramic acorn sockets 35c each. 1.00
- 4 for Westinghouse 0-1 ma. D.C. grad. in 0-10 output units. 4 1/2" x 4 1/2" wood case. 3.95
- Westinghouse 4 1/4" dia. 0-200 D.C. Microammeter. 6.50
- Westinghouse 4 1/4" dia. 0-150 D.C. Voltmeter. 5.50
- Westinghouse 4 1/4" dia. 0-20 D.C. Milliammeter. 2.95
- Miniature 1/2 wave selenium rect. 18v. 1/2-1 ma. 1.00
- Matched pairs sel. rect. for meters 1/2-1 ma. 2 for .80
- 100 #1 spaghetti 1/4 HV cambric, 1/2 plastic (1-lb.) 1.00
- 12-18v electr. controlled carbon pile voltage regulator postpaid 1.00
- 115/175v-3A, 1.4-2A & 230/30v-3A, 2.8v-2A, 60 cec. 50 watt herm. sealed xformer, black crinkle (4-lbs.) 1.25
- New Dynamotor 24v DC to 250v DC 30 ma (6-lbs.) 2.50
- New Dynamotors 24v DC to 270v DC 120 ma (7-lbs.) 3.25
- New Dynamotors 24v DC to 450v DC 200 ma (11-lbs.) 4.25
- Relays 24v DC DPDT 10 amp. contacts.89
- Heavy duty Sig. Corps telegraph key, sil. cont. & switch 1.00
- Code practice set, excellent key, buzzer, batteries, ready to operate. 2.75
- Ht to low imp. headset xformer with jack & plug49
- Wired Ampl. chassis 3"x7"x2", 2-3 sockets, pot. resistors, condensers75
- Balantine microphone amplifiers less 7#7 & 39 tubes (3-lbs.) 2.80
- Heavy punched Al. chassis 2 1/2" x 4 5/8" x 6 1/2" (3-lbs.) 3 for 1.00
- Heavy punched Al. Chas. 2" x 6 1/4" x 7 1/4" 5 soc. (3-lbs.) 3 for 1.25
- Heavy punched Cad. pla. 2 3/4" x 7" x 1 7/8" 11 soc. (5-lbs.) 2 for 1.00
- Octal ceramic rlnk sockets fits above 2 chas. (1-lb.) 10 for 1.00
- Ex. Heavy punched Cad. pla. Chas. 1 5/8" x 9" x 1 3/4" (7-lbs.) 2 for 1.25
- 200 squeeze-on term. lugs for 18-32 ga. wire (1-lb.) 1.00
- Squeeze-on terminal tool and cutter. (1-lb.) 2.50
- 200 silver plated soldering posts for term. boards (1-lb.) 1.00
- 25 pieces 1/4" x 5/8" x 5/8" linen bakelite 1.25
- 25 pieces 1/4" x 3/8" x 1" bakelite 1.25
- 25 pieces 1/4" x 3/4" x 5/8" x 1" bakelite 2.85
- 5 lb. kit ass. 1 1/2" linen bakelite 2" x 10"; 4" x 5" (8-lbs.) 1.95
- Cardwell 365 mid. single section var. cond. (1-lb.) 1.65
- 2 gang ball bearing. 365 mmfd. per section (1-lb.) 1.75
- Master oscillator heavy duty precision tuning dial 20:1 ratio (5-lbs.) 2 for 2.65
- Selsyn 115v/60cy. transm. & recv. (11-lbs.) 8.50
- RG-34/U 72 ohm Coax 28' lengths handies 2Kw. 6.5 cents per foot. 1.00
- Russell 115v/60cy. phono motors. 9" turntable. 4.95
- Metal tool pouch 7" x 4" x 1 1/4" hooks on belt. 29c (3/4-lb. each) 4 for 1.00
- 20% deposit required on all C.O.D. orders.

OHMEYER ENGINEERING LABS.
Fairview Blvd. Dept. C. Hempstead, N. Y.



HANDY SOLDERING IRON FOR HOME & HOBBY SHOP

Now you can own a home soldering iron which has the same kind of Calrod* heater found in G-E industrial irons, the irons that professionals use. Rated at 85 W, 115 V, G-E Handy irons are perfect for a score of home repair jobs, for building radios, making electrical connections, and for many kinds of metal working and model building.

You'll like the quick way this G-E Handy iron gets down to work with a steady, efficient supply of heat... the high-speed soldering it gives you. You'll appreciate its light weight... its cool easy-to-grip handle.

Ask to see the G-E Handy soldering irons at your dealer's. Price only \$3.95. Or write to Dept. C667-IV, Apparatus Department, General Electric Company, Schenectady 5, N. Y.

FREE: An up-to-the-minute manual on soldering techniques with every purchase of a G-E Handy iron. *Reg. U.S. Pat. Off.

GENERAL ELECTRIC
RADIO NEWS

The portable tuner, which is about the size of a cradle telephone, is the only part of the system which is exposed. All other units are concealed in the walls or other suitable space. The amplifier unit can be placed in a closet, cellar or attic.


Present production calls for standard AM reception units only, but an FM tuner will be provided at a later date. No elaborate conversion process will be required.

Reeves Sound Studios, 10 East 52nd Street, New York, New York, will supply additional information on the "Soundcraft Radio" to those requesting it.

5" OSCILLOGRAPH

The recently developed *Hickok Model 195*, general-purpose 5" oscillograph has several unique features of interest to servicemen.

This new unit provides sinusoidal

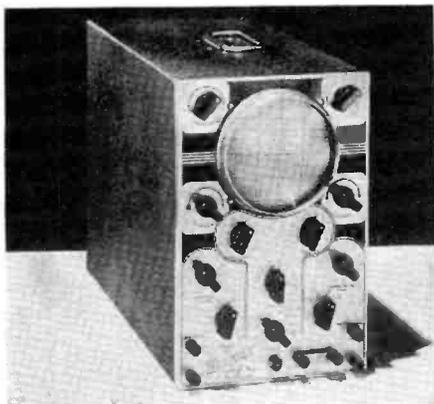

sweep with phasing control and is designed for accurate visual analysis of the wave shapes of television, FM and AM signals. The 5" screen, using the new 5 UP-1 cathode-ray tube, provides easy visibility of all types of radio servicing.

The *Hickok Electrical Instrument Co.*, 10524 Dupont Avenue, Cleveland 8, Ohio, will provide full details regarding this unit upon request.

FLEET CONTROL UNIT

Because of the increasing number of radiotelephone installations, the appearance of *The Hammarlund Manufacturing Company's* new "Fleet Control" selective calling system for two-way service is particularly timely.

Designed with all of the features of previous "Fleet Control" models, the new SCM-26-T includes a bell ringing circuit which provides an audio as well as a visual signal in the mobile unit being called.

In this new unit, the signal light remains lighted until the operator of the mobile unit calls the central office. This feature is advantageous in cases where the operator is absent from the vehicle for varying periods of time.

The *Hammarlund Manufacturing Company* will provide complete details on the Model SCM-26-T to those who write the company at 460 West 34th Street, New York 1, New York.

Lick any **RADIO REPAIR JOB** ... in **LESS TIME** ... with **LESS WORK!** and a lot **MORE PROFITABLY!**

Written by Alfred A. Ghirardi, servicing expert and author of the most widely used books in radio training history.

Ghirardi's **RADIO TROUBLESHOOTER'S HANDBOOK** quickly helps you diagnose and repair common troubles in over 4800 receiver models and automatic record changers of 202 manufacturers.


4 radio repair jobs out of every 5 can be handled as easily as falling off a log—without tedious testing. Try this servicing short cut that really works—the one that pays for itself in time saved on the very first job! There's no magic about it. Just common sense. In this big 4 lb., 744-page manual-size **TROUBLESHOOTER'S HANDBOOK**, Ghirardi supplies you with a carefully tabulated and indexed compilation of the common Troubles (and their Remedies) that occur in over 4800 models of home radios, auto radios and automatic record changers of 202 manufacturers—the sets that account for well over 90% of all service work today! Clear instructions tell you exactly **WHAT** the trouble is likely to be—exactly **HOW** to fix it. No guessing or lost time!

NO OTHER HANDBOOK LIKE IT

This priceless Trouble Case History section of the **HANDBOOK** eliminates the need for all troubleshooting and laborious testing on 4 jobs out of 5. Tells you **HOW** to make the necessary repairs **QUICKLY**, **SIMPLY**, **DIRECTLY!** Ghirardi passes on to you the priceless experience from thousands of hours of tedious troubleshooting so you can save **MORE THAN HALF** your precious time and do your work **Easier, Faster, more Profitably.**

NOT A STUDY BOOK!

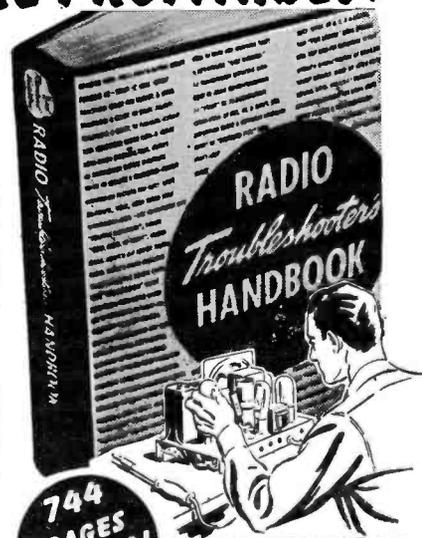Over 300 additional pages contain parts repair data; diagrams, tube charts, tuning alignment and i.f. transformer data for more than 20,000 receivers, complete RMA color codes, and dozens of graphs, diagrams and other service data, all designed to help you repair **ANY RADIO EVER MADE** easier and twice as fast! You get all this for only \$5 complete!



744 PAGES MANUAL SIZE

GOODBYE TO TEDIOUS TESTING ON FOUR JOBS OUT OF 5

Trouble Case History repair instructions on over 4800 models of all these makes:

- | | |
|----------------|-----------------|
| Admiral | Howard |
| Airline | Majestic |
| Arvin | Motorola |
| Belmont | Philco |
| Brunswick | Pilot |
| Capehart | RCA |
| Chevrolet | Silver-Marshall |
| Clarion | Silverstone |
| Colonial | Sonora |
| Crosley | Spartan |
| Emerson | Stewart Warner |
| Fada | Strom.-Carlson |
| Farnsworth | Westinghouse |
| G.E. | Wilcox-Gay |
| General Motors | Zenith |
- ... and 172 more!

Don't BE A HACK!

Learn Professional Servicing by **MODERN, SCIENTIFIC** Methods

MODERN RADIO SERVICING is A. A. Ghirardi's famous illustrated and simplified course in professional radio-electronic service work. 32 big chapters, 1300 pages and over 700 illustrations complete in 1 vol. — sold for only \$5! It explains the construction and operation of all types of test instruments — and how to use each one. Shows how to analyze circuits scientifically; how to test, repair and replace components; how to do every phase of home and auto-radio repair work from A to Z by most expert, time-saving **MODERN** methods. Worth its weight in gold in giving you a real, honest-to-goodness complete course in the **KNOW HOW** of radio - electronic service work!

1300 pages
706 illus.
only

\$5

MONEY-SAVING COMBINATION OFFER!

Let the **HANDBOOK** save you time on common service jobs. Let **MODERN RADIO SERVICING** train you for truly professional work. Get **BOTH** big books at special Money-Saving Combination price of only \$9.50 for the two by mailing coupon today.

HAVE A LOOK AT THEM—NOW!

DEPT. RN-57 MURRAY HILL BOOKS, INC.
232 Madison Ave. New York 16, N. Y., U. S. A.

- Enclosed find \$..... for books checked; or
 send C.O.D. (in U.S.A. only) for this amount plus postage. If not fully satisfied, I may return either or both books within 5 days for full refund of my money.
- RADIO TROUBLESHOOTER'S HANDBOOK**
\$5 (\$5.50 foreign)
- MODERN RADIO SERVICING**
\$5 (\$5.50 foreign)

MONEY-SAVING COMBINATION OFFER:

- Both big books — over 2040 pages total — only \$9.50 for the two (\$10.50 foreign).

Name.....
Address.....
City & Zone..... State.....

**THE NEW
TRANSVISION
TELEVISION
RECEIVER KIT**


Now available for
IMMEDIATE SHIPMENT
from METROPOLITAN



Easy to assemble. No knowledge of television required. Complete easy-to-follow instruction sheet gives you all the knowledge you need. Finished Television Receiver has a picture that is clear and sharp . . . comparable to a moving picture.

All necessary components are included; nothing is required except a screw driver, cutting pliers and a soldering iron. Only the highest quality standard parts are used—the list price value of these parts alone is more than \$300. 110 volts, 60 cycles AC
FACTORY GUARANTEE—set guaranteed to operate satisfactorily if directions are followed exactly. Servicing of component parts and assembled parts will be performed by the factory at factory costs.

\$159⁵⁰

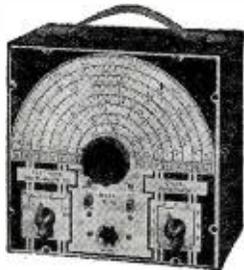

**The New Model B-45
BATTERY OPERATED
SIGNAL GENERATOR**

for servicing AM, FM and Television Receivers
Self-modulated Signal Generator, providing a highly stable signal. Generates R.F. frequencies from 150 Kilocycles to 50 Megacycles (150 Kc. to 12.5 Mc. on Fundamentals and from 11 Mc. to 50 Mc. on Harmonics). R.F. is obtainable separately or modulated by the Audio Frequency.

Direct reading—all calibrations are etched on the front panel. Complete with shielded test lead, self-contained batteries and instructions.
\$2775
Net.

TERMS: 25% deposit, balance C.O.D. or full payment with order.

Send for Free Catalog!

**METROPOLITAN
ELECTRONIC & INSTRUMENT CO.**

6 MURRAY STREET, Dept. RNS, NEW YORK 7, N. Y.

LETTERS from our readers

SERVICE CONVENTIONS?

AT THE February meeting of the Federation of Radio Servicemen's Associations of Pennsylvania held in Harrisburg, the feasibility of holding a State Convention of Radio Servicemen was discussed. I do not believe such a gathering, sponsored by servicemen themselves, has ever been held. We are interested in getting the reaction of individuals and groups to such a suggestion.

"Accordingly, we would appreciate it if you would publish this letter, along with any comments you would care to make. We will welcome any suggestions or ideas from individual servicemen or groups. Please address correspondence to the writer."

A. R. Guild, Secretary
Radio Servicemen's
Association of Pa.
410 Campbell Street
Williamsport 11, Pa.

This would be a good idea if it can be worked out. At least it would give you fellows a chance to thrash out your problems.

* * *

SERVICING AUTO RADIOS

YOUR RADIO NEWS is one of my sources for radio information and I would be very pleased if you would give us an early article on auto radio servicing and installation.

"There is no doubt that the radio serviceman in the near future will have to specialize in a certain type of repair service.

"There is no branch of radio that is expanding like auto radio and there are very few technical articles on this subject.

"An article on how to build a vibrator tester using commercial parts that are readily obtainable would be very helpful."

Preston L. Williams
South Norfolk, Va.

A construction article on the vibrator tester has already been planned and will be run as soon as we can get the material completed.

* * *

SUGGESTIONS

YOU have a swell magazine. However, I believe you should have some articles on television, facsimile and pulse time modulation. A number of your readers are operators and someday they will have use for such information.

"Another item of interest would be a discussion of what makes a good radio trade school. This would be of great value to veterans who are planning to attend a radio school. I have come in contact with some good schools and some not so good.

"I wish to speak in support of a television operator's license, to be issued by the FCC. Television involves principles not encountered in radiotelephony, namely optics and anyone who has a radiotelephone first class license is not necessarily qualified to be a video or FM engineer. Instead of easing the license requirements they should be stiffened to keep pace with the advancement of the art."

Alban Hatzell, WØFIV/6
Hollywood, California

RADIO NEWS is planning to run more and more articles on television, facsimile and pulse time modulation. Watch for them.

* * *

LOOK WHAT MR. DARR STARTED

JACK DARR has covered the question of standardizing methods and procedures on the design of new radio receivers. He has done this so well that I can add little or nothing to his list of suggestions. I think he has something there.

"I believe that it would be well for each receiver manufacturing company executive to read Darr's letter and be inspired."

Walter Demski
Walter's Auto and Radio Supply
McKeesport, Pa.

* * *

JACK DARR'S revealing letter concerning the poor construction of commercial receivers encouraged me to write this letter. Every time I think about repairing radios, I dream a nightmare of rotten rubber hook-up wire, rat's nest wiring, slipping dial cables, and row after row of unmarked trimmers.

"Here are a few suggestions: don't use rubber hook-up wire of poor quality because a serviceman can't make anything on the time spent in rewiring sets in which the wiring has decomposed; avoid the use of rubber mountings on tuning condensers, dials, etc. The rubber dries out and then the tuning mechanism is a loose-jointed mess; mark or color-code the values of the resistors and condensers so that replacement will be simpler. It seems as if the only condensers that go bad are the unmarked ones; eliminate push-button tuning on sets as the contacts get dirty, the coils drift with age, and the temperature coefficient is such that it drifts away from the station as the set warms up.

"Mount electrolytic condensers as far away from the hot tubes as possible. They will last three or four times as long; don't use OZ4 tubes for rectifiers in auto radios, they seldom last any length of time; calibrate dials accurately enough so that one will know



U. S. SIGNAL CORPS 2-WAY TALKING SYSTEM

A Western Electric product. Use them for inter-office communication, house to garage, mother's room to baby's room, on the farm and many other places. Sensitive enough to pick up the slightest whimper. Sturdy all steel construction. Has push-to-talk switch. Speaker is built in. Tube line-up 5Y3, 6SJ7 and 6K6. Can be used as a 4-watt modulator for your ham rig. The small unit is a speaker-receiver. Connect as many as 10 speakers in parallel. Comes ready to operate. Just plug into 110 volt AC line. 100 ft. of speaker cable is supplied. Complete with master and one speaker-receiver.....

Extra speaker-receiver.....



\$3250
\$495

RADIO PARTS ASSORTMENT

Hundreds of valuable and useful radio parts. Transformers, coils, condensers, wire, sockets, escutcheons, lugs, etc., etc.


A Better Buy
10 lbs. \$1.69



HS-30 HEARING AID TYPE HEADSET


Hi-fidelity, flat, from 100 to 10,000 cycles, impedance 128 Ohms, will operate across low impedance voice coil. With matching transformer impedance is 8000 ohms. Brand new, complete with plug and transformer.....

\$1.98

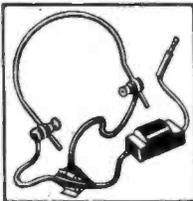

HS-16 HEADSET

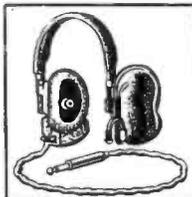Noise-proof, rubber-cushioned, equipped with 2 matching transformers, magnesium earcaps. A superior headset. 8000 ohms impedance. Brand new... **\$2.98**



HOT SPECIALS

1619 Tube. Characteristics same as 6L6 only with a 2½ volt filament. Use as a replacement for a 47 or a 2A5..... **\$.69**

20.7 Megacycle double iron core tuned IF transformers. Four to a complete set. Use them for FM or Video. Can easily be trimmed down to 10 Megs with a single ceramic condenser..... **\$2.98**

Set of four matched coils..... **\$1.79**

6L6 Output transformer..... **\$1.79**

2500 Ohm 100 Watt adjustable resistor.. **\$.49**

Kit of 50-1 and 2 Watt resistors, sizes 25, 150, 1000, 3000, etc..... **\$1.00**

BC-312, 342 I.F. Crystal Transformer, resonant at 470 KC. Replace that 1st I.F. with this unit and separate those crowded ham-bands..... **\$6.49**

Double Button Mike-to-Grid Trans.... **\$.59**

Kit of 10 R.F. & Osc. Coils..... **\$.98**

Pwr.-Trans. 350-0-350, 60Mils, 6.3v @ 3a, 5v @ 2a..... **\$2.15**

RA-20 Power Supply—for Signal Corps Receiver BC-342. Replace battery pack on BC-312 to convert to 110v. AC operation..... **\$14.89**

T-30-V Carbon Throat Mike Brand New..... **\$.79**

10 METER CONVERTER

27 to 30 Megacycles

Designed for Army surplus receivers such as the BC 342, BC 348, BC 312, etc. Uses a single 6SA7 fixed oscillator at 16 megs. Adjust plate output and grid input signal for maximum. Calibrate and tune the entire band on your receiver. The power for the converter comes from the receiver. Our special adapter secures the power from the receiver by a plug-in arrangement. When this is not possible instructions will indicate the correct tapping point. In ordering be sure to mention the model receiver.

Complete Instructions and plans..... **\$1.00**

Kit of parts and plans for complete operation..... **\$12.00**

Complete unit wired and tested... **\$18.00**



BROADCAST BAND CONVERTER

100 KC to 1550 KC

For owners of Army-Navy surplus receivers. Adapter supplied uses a 6SA7 tube mixer-oscillator. Beats BC signal against 3 Megs. Tune in on short wave. An improved feature incorporates an aperiodic tuned antenna circuit for low noise level. Tested with BC-312, 342, NC100-ASD, BC-348 and others. In ordering state model..... **\$15.00**



Cash, Check or M.O. Write Dept. N-M

THOR ELECTRONICS
5051 N. Clark St., Chicago 40, Ill.



The New Home of MELVILLE RADIO INSTITUTE

The Melville Building is ready with facilities for over 2,000 students of

TELEVISION & RADIO

Melville Radio Institute, a well-established, prewar school, is one of New York's outstanding vocational training centers.

Technical know-how, ample equipment and expert faculty have resulted in a satisfied student body that is among New York's largest.

Visit us today without obligation and watch the School in operation. A free brochure may be obtained by mailing the attached coupon.

Licensed by the State of New York.
Approved for Veterans.

MAIL THIS COUPON NOW!

MELVILLE RADIO INSTITUTE
Melville Building
15 West 46th St., New York 19, N. Y.
GENTLEMEN: Send me FREE Information about your school. RN

Name

Address

THE SIX MELVILLE COURSES

- RADIO TECHNICIAN
- TELEVISION TECHNICIAN
- RADIO COMMUNICATIONS
- RADIO & TELEVISION SERVICING
- FUNDAMENTAL RADIO MATH
- SLIP-TAPE TRANSCRIPTION


"The Radio School administered by Radio Men."

MELVILLE RADIO INSTITUTE

Melville Building

15 WEST 46th St., N. Y. 19 • BR 9-5080

UNIVERSAL MODEL 502-C RADIO TUBE TESTER

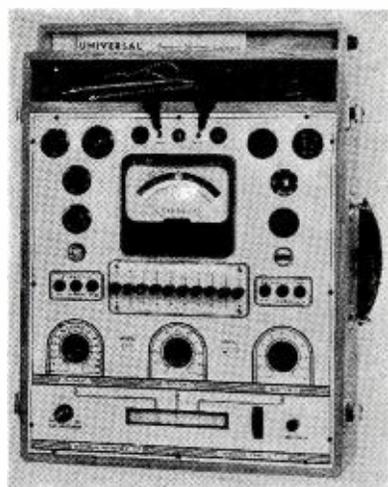

- MODERN DESIGN
- EASY TO OPERATE
- FLEXIBLE CIRCUIT
- HANDSOME OAK CASE
- ROLL CHART
- LEVER ACTION SWITCHES
- 2-RANGE OHMMETER
- 2-RANGE

BATTERY TESTER

Dealer's Net Price

(110 V—60 cycles) **\$49.95**
F.O.B. Factory

Also available as
counter Model 502-C

at same price

Write for catalog

UNIVERSAL INSTRUMENT CO.

306 East McMillan Street
Cincinnati 19, Ohio

Export Department

INTEX COMPANY

303 W. 42nd Street
New York 18, N. Y.

Cable: "INTEXCOM, N. Y."

he has the correct station; incorporate two- or three-position selectivity control on the better sets; incorporate a t.r.f. stage on the better sets; if a set has an r.f. stage, provide sufficient trimmers and permeability tuned coils so that it may be tracked with the mixer and dial; and finally use a simple but good quality coaxial speaker system in larger radios.

"I could rave on and on—but I suppose what I haven't said will be just as effective in correcting conditions as what I have said."

William W. Schriever
Norman, Oklahoma

* * *

THREE cheers for Mr. Darr and his letter. If any of these so-called engineers had to disassemble their product, where the speaker, loop aerial, phono motor, pickup, extension controls and chassis were all wired together without the use of plugs, or other convenient methods of disconnecting the units, perhaps they'd make some drastic changes. And why not some more substantial method of putting on tube locations than paper charts which become torn, lost or obliterated. Equally as bad are inaccessible chassis screws in portable radios which have to be painstakingly removed with an offset screwdriver by half turns, since wooden battery dividers keep you from making a complete revolution."

C. H. Hartwell
Armstrong Radio &
Appliance Store
Chicago, Illinois

* * *

I AM a newcomer to the radio service field so I have held my peace regarding many things I thought were wrong with the design of radios but I do agree 100% with Mr. Jack Darr. My particular gripes concern the lack of accurate dial calibration marks at the limit of pointer travel and at the 1400 kc. and 600 kc. in many sets and the lack of trimmer and padder identification."

William F. Oliver
Plymouth, Wisconsin

* * *

LET'S give three cheers for Jack Darr for expressing his opinion on the new sets coming out now. He voiced the opinion that many of us have been thinking.

"In comment, several of the prewar models had started using his suggesting practice of calibrating the rear of blind dials. I, for one, utter a long low curse when I have to replace a chassis in the cabinet to recheck the dial.

"Another headache is the tiny, ineffective Allen-head set screws in some of the new knobs. Have they run completely out of springs, what was wrong with the split shaft?

"Mr. Darr, without a doubt, is a conscientious worker and like him I never cease to wonder about this deal of the soldering on the new radios. What is the matter with present-day workers?

RADIO AND APPLIANCE DEALERS

LOW PRICES

Fast Delivery



We are in a position to supply you with everything you need in the electrical and radio fields. We can supply many hard-to-get products, such as Plugs, Switches, Sockets, Elements, etc.

FREE—Send for our complete catalog showing Electrical Wiring Devices, Portable Electric Stoves, Fluorescent Equipment, etc.

TRUTONE PRODUCTS COMPANY

Dept. NA

303 West 42nd St., New York 18, N. Y.

20

YES, it was just twenty years ago that Kenyon was first incorporated. For over twenty years Kenyon has served you well... as a reliable source of quality transformers.

May all our future years of business with you be as pleasant as the first twenty.

We are looking forward to seeing all our friends in Chicago during the week of May 13-16 at the Radio Parts and Electronic Equipment Show. Drop in and see us at Booth No. 6

THE MARK OF EXCELLENCE



KENYON

TRANSFORMER CO., Inc.

840 BARRY ST., NEW YORK, N. Y.

"My radio experience has covered about the same number of years as Mr. Darr's and I have a shop that I am proud of and I am proud of my work. How about you manufacturers giving us a product to work on."

Charles C. Gohn
Radio Service Department
Bogle Hardware
Shenandoah, Iowa

RECTIFIER INSTALLATION

READ the article in the November issue of RADIO NEWS in regards to installing a selenium rectifier in a radio.

"Instead of going through all the work of pulling the set apart, I have a Zenith Portable, Model 7G605, I just took the base of an old tube and soldered the lugs to the plate and cathode terminals and plugged it in. It works perfectly. This was on a 117Z6GT.

"Why couldn't these rectifiers be put out this way?"

William P. Dowd
Officers' Quarters
State Farm, Mass.

Nothing is impossible . . . but this suggestion is not too practical as the manufacturers and parts jobbers would have to stock too many different items. It isn't too much trouble hooking up a socket to these rectifiers.

-30-

International Short-Wave
(Continued from page 70)

Smichov—the most distant quarter—took a substantial part in the battle for Broadcasting House and the battle for the transmitter in Strasnice, a different part of Prague. . . . After the building had been hit by a heavy torpedo on Sunday night, which had exploded a few yards from the studio and buried many defenders of Broadcasting House, announcing was taken over by the technicians themselves directly under the transmitting masts in the suburb of Strasnice. In the meantime, workers of the Broadcasting Company, chiefly technical workers, had moved the necessary technical fittings into one of the churches of the Church of Czechoslovakia, with a park, which was about 1 km. from the main building and connected with it by a cable. Here they quickly improvised a new studio and the necessary offices. The announcements were made from the choir and until the revolution was over not a single outsider knew where the studio was. On Tuesday, during the bombardment and shelling of Prague (at the very same time when peace was being solemnly declared in London) the Czechoslovak Broadcasting Company was moving into the shelter of Hus House.

"On the first day after the liberation of Prague—May 9th—at 7 p. m.—normal, though festive, transmissions were begun from the mother house in Prague XII, which although heavily damaged and half destroyed, had been **May, 1947**

FREE send for it now!

VALUE-PACKED

ALLIED'S NEW RADIO CATALOG



EVERYTHING IN RADIO FOR EVERYONE IN RADIO!

Send for your FREE copy of the handiest, most complete Buying Guide for Everything in Radio! Packed with the latest, finest values in radio and electronic supplies . . . parts, tubes, test instruments, communications receivers, Ham gear, Public Address equipment, home radios, tools, books . . . more than 10,000 items of nationally known, guaranteed quality . . . the world's largest and most complete stocks. For fastest service, expert help, lowest prices, depend on ALLIED! Send for FREE Catalog now . . .

MORE THAN 10,000 ITEMS. Everything in radio and electronic supplies to serve the needs of engineers, servicemen, dealers, soundmen, amateurs, and builders. Complete stocks of all the leading makes. Guaranteed quality. Lowest prices. Get everything you need from one dependable source—ALLIED—Radio's Leading Supply House for everyone in Radio!




HAM GEAR

Earliest delivery on latest communications receivers, transmitters and Amateur station equipment. Time payment plan; Ex-trade-ins accepted. Expert Amateur Service.

HOME SETS

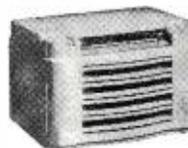New 1947 radios and radio-phonos. Radios for radio men! Handsome styles. Wonderful performance. Outstanding complete line of radio values!



NEW P. A. EQUIPMENT. Entirely new line of complete Packaged Sound Systems for every public address requirement. New styling, new design features. Everything in amplifiers, speakers, microphones, accessories. New intercom systems. New professional-type sound apparatus. Everything for the Soundman!



HANDY RADIO BOOKS

- Radio Formulas and Data10c
- Dictionary of Radio Terms15c
- Radio Circuit Handbook25c
- Radio Builders' Handbook15c
- Simplified Radio Servicing10c
- Radio Data Handbook25c
- ALL 6 BOOKS No. 37-799 \$1.00

HELPFUL CALCULATORS

- These radio reference aids provide valuable data quickly:
- Parallel Resistance and Series Capacitance Calculator. No. 37-960 . . .25c
 - R-F Resonance and Coil Winding Calculator. No. 37-95525c



- **ALLIED RADIO CORP.**
- 833 W. Jackson Blvd., Dept. 1-E-7
- Chicago 7, Illinois
- Send FREE 1947 RADIO CATALOG
- Send Books checked above
- Send 6 Books No. 37-799 } \$.....enclosed
- Send Calculators checked above


Name.....

Address.....


City.....Zone.....State.....

ALLIED RADIO

Everything in Radio and Electronics

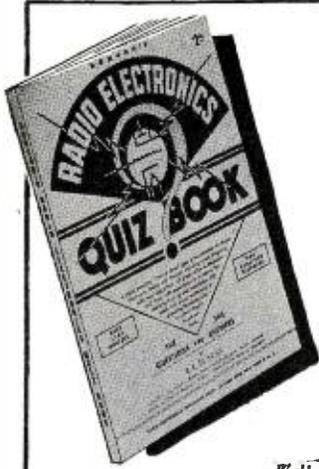

Two New MUST Books

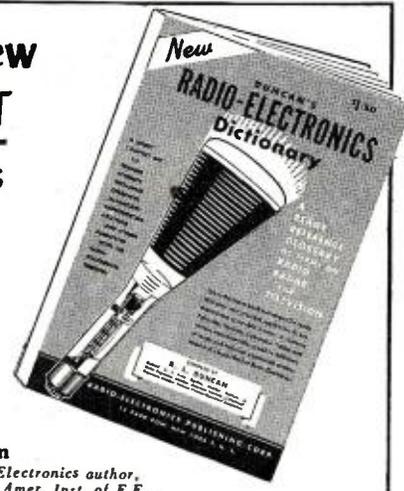

By
R. L. Duncan

Well-known educator and Radio-Electronics author,
Colonel, Sig. Corps Res.; Member, Amer. Inst. of E.E.,
Inst. of Radio Engineers, Veteran Wireless Operators' Assn.

This Quiz Book is of inestimable value to students, trainees and those with experience as a means for checking knowledge and training. It is tops as a pre-examiner for radio license examinations. A highly practical "True or False" type of question and answer treatise containing more than 1200 quizzes, plus the required circuit diagrams. This book points the way... acclaimed as a superior means for determining the scope of your Radio-Electronics "know how"

This Dictionary of Radio-Television-Radar is prepared especially for technicians, students, mechanics, operators, experimenters, trainees, amateurs and others associated with the radio-electronics industry... arranged for ready reference and practical application in one streamlined up-to-date book containing Formulas, Symbols, Conversion Tables and various essential data, as well as definitions of terms and technical expressions encountered in the broad field of Radio-Electronics.

You Need These Books... Order Them NOW!

Only \$2.00 for the Quiz Book and \$1.50 for the Dictionary at your dealer, or if he cannot supply you, order direct. Remit by money order or check—do not send cash.

RADIO-ELECTRONICS PUBLISHING CORP., DEPT. RN-5, 15 PARK ROW, NEW YORK 7, N.Y.

AVAILABLE FROM **RPO**

JENSEN

MODEL	LIST
HNP-51	\$125.00
JAP-60	86.00
JHP-52	65.00
JCP-40	35.00
D-121	62.00
D-151	62.00
H-20	34.05
H-24	41.85
U-20	43.05

SIMPSON

MODEL	LIST
305 Tube Tester.....	\$ 49.50
305 RC Tube Tester.....	59.50
330 Tube Tester.....	98.50
330 RC Tube Tester.....	108.50
315 Signal Gen.....	67.35
260 Meter	38.95

CASH WITH ORDER

RADIO PARTS OUTLET, INC.
4305 LINCOLN AVENUE, CHICAGO 18, ILL.



Clippard ELECTRONIC VOLT- OHMMETER, MODEL 406

We invite comparison of this instrument with any at any price for appearance, ruggedness, accuracy, stability. 0-1 to 1,000 volts From Jobber U.H.F., A.C., D.C. 0-1,000 or F.O.B. Cinti. megohms. Pen-type dual-diode A.C. probe. No extras to buy. Send for details or order today.

\$89.50 NET

CLIPPARD INSTRUMENT LAB., INC.
1125 Bank St., Dept. 6, Cincinnati 14, Ohio

defended until the arrival of the Red Army. The Commanding Officer of the Soviet Troops said that Prague was the only city which had not ceased to transmit throughout her revolution and which had managed to keep all her transmitting stations. This is in the first place due to the efforts of the devoted staff of the Czechoslovak Broadcasting Company, of their comrades from among the broadcasting staff of the Postal Service and hundreds of unknown fighters who came to help the Broadcasting Company. . . .

"Now the Czechoslovak Broadcasting Company is quickly reviving from the heavy wounds which were inflicted on it by the Nazi occupation, the Gestapo terror, and by this war which had in its last phases passed through Czechoslovak towns with transmitters and stations, and had ended in Prague, and from many other wounds which it bore bravely and returned with interest during the Slovak Rising and the Prague revolution.

"Among the questions which are put by friends and kind guests from Allied countries who are interested in the Prague revolution, there are always these: Was it the right moment? Or was the order given before? By which group? Who gave the order to the announcers to call? Was it the Czech National Council? . . . And so on.

"We are sure that it was the entire Czech nation, who in the same moment in places distant from each other, organized and unorganized, simultaneously felt the fatal moment, and unasked, obedient to orders and without orders, armed and without arms, led and without leaders, threw itself against the Nazis, against the occupants! It was the most spontaneous rising of a people, historically related to the spirit of the Hussite revolution, because it originated from the very matter of the national spirit, from the roots of the ideals of liberty, of the national, state and political tradition of that period of humanity, in the midst of which beats the heart of Prague. After seven years once more uplifted heads, after seven years' humiliation, we can again fight for and defend our liberated homeland!"

Czech Schedules

The assertion that the Czech Radio is rapidly recovering is borne out by the expansion of its facilities, especially with regard to "foreign language" broadcasts.

Good to excellent signals are reported from various quarters of the United States during the daily North American beam (in English, Czech, and Slovak), 7-8* p.m., over OLR5A, 15.23; English news is read around 7:35 p.m. In addition, there are cultural reviews, economic talks, Trade Union Bulletins, on various days, and always beautiful music; while the major portion of the program usually originates in Prague, oftentimes relays

*Unless otherwise stated, all time herein is expressed in American Eastern Standard Time—EST—5 hours BEHIND GMT.

are taken from Bratislava and elsewhere. Reception reports are desired and verifications are being sent out promptly. Address, The Czechoslovak Broadcasting Corporation, Prague (Praha), Czechoslovakia.

Additional *English* periods are scheduled daily at 1:45-2 p.m. from OLR3A, 9.55; at 3:45 and 5:45 p.m. from OLR2A, 6.010. (These are usually heard fair to good in the United States.)

The Czech Radio also broadcasts to Austria in German between 2:30-2:45 p.m.; in French, 3-3:15 p.m. and 5:15-5:30 p.m.; in Spanish, 3:30-3:45 and 5:30-5:45 p.m.; to Scandinavia (Swedish, Norwegian, Danish), 4:15-4:30 p.m.; and to Switzerland (French, German, Italian), 4:30-5 p.m.; all these transmissions are from OLR2A, 6.010.

Czechoslovakia lies in the very heart of Europe, and like Switzerland, Austria, and Hungary, is a landlocked country without direct access to the sea. It is bounded on the north by Germany and Poland; on the south by Austria, Hungary, and Rumania; on the west by Germany; and on the east by Poland and Rumania. It lies athwart Europe from west to east, its extreme length being 600 miles and its width varying from 50 to 100 miles. Prague (Praha) is its capital.

The subterranean caverns of Czechoslovakia are among the curiosities of Europe. In the Moravian Kras not far from Brno there stretches an extensive system of caverns, lakes and abysses, all underground. Among the famous sights of Central Europe are the magnificent ice caves in Dobsina in a district known as the "Slovak Paradise." Czechoslovak spas and mineral springs are among the foremost in Europe.

Prague has a wealth of medieval architecture equalled by few other cities on the Continent. It is believed that more than 3500 years back there was a settlement within the territory which is now occupied by present-day Prague, on the site of the castle of Vysehrad.


Czechoslovakia possesses one of the richest territories in Europe—both in natural resources and industrial development.

About 75 per-cent of the population is Roman Catholic, the rest Protestant. Institutions of higher learning are the Czech University in Prague (founded in 1348); the Universities of Brno and of Bratislava; and the German University in Prague.

The Czechoslovak Republic was recreated as the result of World War I. The reestablishment of independence marked the culmination of the struggle of the Czechs and Slovaks for freedom, a struggle the beginning of which went to the Middle Ages, when the ancient independent kingdom of Bohemia was absorbed within the Hapsburg Monarchy.

The Czechs and Slovaks are two closely related branches of Slav ori-

May, 1947

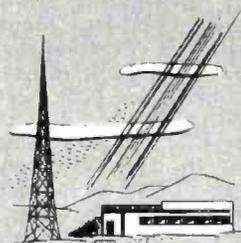


RADIO STATION STANDBY



MOBILE RADIO UNITS




GEOPHYSICAL SURVEY

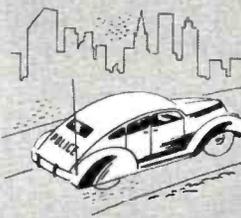

MUNICIPAL SIGNAL STANDBY



RAILROAD RADIO

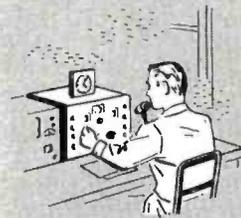

AMATEUR RADIO




"SPOT" RECORDING

A.C. OR D.C.

POWER

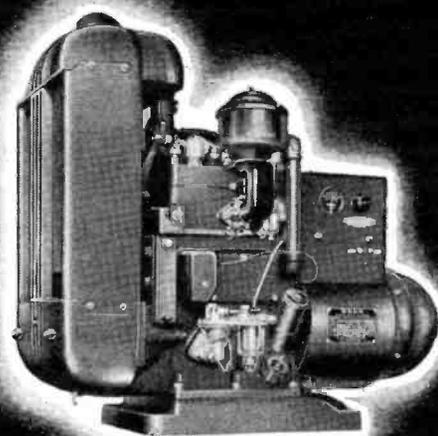PORTABLE, STANDBY
OR STATIONARY
for
Electronics Uses



Onan Electric Plants are completely self-contained, dependable power units built in a wide range of sizes and standard voltages.

Lightweight, one or two-cylinder, air-cooled models offer the maximum in portability for many applications. Portable A.C. models—350 to 3,000 watts; portable D.C. models—600 to 5,000 watts.

Although widely used for intermittent service as standby units, Onan two, four, and six-cylinder water-cooled plants are built for continuous heavy-duty operation . . . stationary or mobile. A.C. models—3 KW to 35 KW; D. C. models—3.5 KW to 10 KW.

WRITE FOR FOLDER

ONAN Electric Plants are available in many sizes and models. ALTERNATING CURRENT: 350 to 35,000 watts in all standard voltages and frequencies. DIRECT CURRENT: 600 to 10,000 watts, 115 and 230 volts. BATTERY CHARGERS: 500 to 3,500 watts; 6, 12, 24 and 32 volts.

D. W. ONAN & SONS INC.

4783 Royalston Ave.

Minneapolis 5, Minn.



MAKE A BEE-LINE TO

KAYLINE!

* * MAY SPECIALS * *

Drills Manufactured by the Van Dorn Electric Tool Co. Div. of Black & Decker

HOME-UTILITY TOOLS

1/4 Inch Drill Delivery Now From Stock



IN U.S.A. \$16.95

In Canada \$21.25

1/2 inch drills also in stock \$31.95 U.S.A. \$39.95 in Canada

OUR OFFER STILL GOES!!

TUBES ALL BRAND NEW, JAN.

5CP1, 2X2A, 2C26, 3E20/820B, 723A, 717A, 417A, 2J32, 6AK5, 6AG5, 6Y8, 6V6, 6SN7GT, 6J5, 6C4, 6E5, 5U4G, 9006, and 3B26.

We will meet any price in this issue for the above (brand new) tubes. We also reserve the right to limit quantities on tubes.

OSCILLOSCOPES • 5 inch 115 V. 60 Cy. BC 412. Mfg. by Western Electric. Complete with All Tubes.. **\$44.95**

Crating Charges \$8.50
 • 5" 5BP4 or 5BP1 • 2500 volt and 400 volt Power supplies 115 V. 60 CY.
 • Cathode Ray Tube • 2x2 and 5T4 rectifiers
 • Vertical & horizontal positioning controls • Intensity control • Focusing control • Sweep control • Horizontal amplitude control • One 6AC7 pulse amplifier • Two 6SJ7 amplifiers • 6L6 amplifiers

ACORN SOCKETS (National) Type XMA—built in bypass copper base.....Each \$0.49

COIL FORMS (Hammarlund) code SWF-5.....Each .25

#44 PILOT BULBS 6-8 volt. Box of 48... 2.00

SCREW DRIVERS (Miller Falls) #853—Six inch35

CONDENSER KIT of 50 Ass't Ceramicons. .1.95

RESISTOR KIT of 100 RMA. Coded Popular Brands 2.50

POTENTIOMETER KIT, 10 Ass't AB Type J, 2 Watt 2.95

SOCKETS—Amphenol Steatite Octal. Each .12

CHOKES—Pie-Wound 2.5 MH. Stand off Ins. TypeEach .25

INTER-LOCK SWITCH—G.E.75

MICRO-SWITCH SPDT35

TOGGLE SWITCHES—SPST, DPST..... .25

SIGNAL CORPS HEAD SETS..... 1.95

PAPER CONDENSER—Electrolytic Aerovox. .1 Mfd. 1000 V15

.0005 Mfd. 500 V. Half Postage Stamp Mica .05

LARGE QUANTITIES LOWER PRICE

MOLDED MICA CONDENSERS

.00075 Mfd. 5000 V. \$1.00

.001 Mfd. 5000 V. 1.00

.002 Mfd. 5000 V. 1.00

.006 Mfd. 3500 V. 1.00

OIL FILLED CONDENSERS—GE, CD Aerovox & Westinghouse.

1 Mfd. 5000 V. \$4.95

8 Mfd. 1500 V. 2.50

2 Mfd. 2000 V. 1.50

2 Mfd. 600 V.75

6 Mfd. 600 V. 1.25

2 Mfd. 1000 V. 1.00

50 Mfd. 330 V.A.C. 3.50

5 Mfd. 330 V.A.C. 1.00

We have a large stock of many still hard-to-get items. Send us a list of your requirements. Large stock of transmitting tubes now on its way. All mail orders filled promptly. Please include postage on parcel post orders. All other orders sent F.O.B. Baltimore Railway Express Collect. We have a stock of relays, all types of amphenol plugs & connectors, Coaxial fittings and cable. Send for new list of real bargains in war surplus items.

KAYLINE DISTRIBUTING CO.
 3523 DOLFIELD AVENUE—DEPT. N5
 BALTIMORE 15, MARYLAND
 LIBERTY 4651
 Cable Address "Kaydisco"

gin; each has its own literary language, but a Czech understands Slovak without any effort and vice versa. In the ninth century they formed a single state, the Great Moravian Empire, which was destroyed during the Magyar invasion of Central Europe in the tenth century. Later the Slovaks lived in the Hungarian and the Czechs in the Austrian half of the Austro-Hungarian Empire. Religious and political persecutions in the sixteenth and seventeenth centuries led to an unsuccessful revolt of the Czechs which resulted in the loss of their freedom at the Battle of the White Mountain near Prague in 1620.

Dr. Eduard Benes has been named President (third time) to serve until a new Constitution has been drafted and another election held.

Looking toward the future, the Czech Parliament has adopted a two-year reconstruction program that sets production goals for most industries and contemplates shifting of workers to achieve the greatest efficiency, and to lay a secure foundation for further progress. In a comprehensive commentary on this plan, "Two Years of Work," Jan Roubal explains:

"The Czechoslovak people have responded to the announcement of the Government program with genuine enthusiasm. The miners were the first to make a solemn promise that they would fulfill the plan, and challenged other workers to compete. The results that have so far been achieved prove that they will really fulfill the plan. Even before the actual proclamation of the plan, output is already rising. Czechoslovak young people willingly assist the peasants. All sections of the nation irrespective of party allegiance are joining in the work for a better future of the Republic and her people. This concerted effort is a guarantee that the plan, whose material factors have been carefully weighed, will really be fulfilled."

Re Sunspots

"Don't worry too much about sunspots," is the advice of the well-known New York DXer, Roger Legge.

"Actually, they are of benefit to DXing," Mr. Legge tells me. "It is during years of high sunspot activity—such as at present—that high-frequency reception is the best. During winter evenings several years ago, when there was very low sunspot activity (bottom of the sunspot cycle), all Europeans of 6 megacycles and above were sometimes inaudible, due to the very low maximum usable frequencies, and the BBC on 2.880 would then be the only European audible; now we are getting good evening reception from Europe on all bands up to 15 megacycles.

"During the few days each month when there is an ionospheric storm, reception is of course poor, but we DXers should be willing to put up with some bad days occasionally in return for improved reception the remainder of the time. (Also DXers

MAY SPECIALS

ALL TUBES 40%—80% OFF!
 Standard Brands New Guaranteed
 Sealed Cartons

1LA6, 117L7, 117M7, 117N7, 117P7 \$1.98;
 2A6, 6AB, 35 \$.92; 6F5, 12Z7, 43, 47, 50Y6,
 84 \$.92; 2AS, 7G7, 32L7, 50A5, 70L7
 \$1.68; 7B7, 7B8, 7C5, 35A5, 35Z3 \$1.09;
 14R7, XXL, 117Z3, 117Z4, 117Z8 \$1.35; 87,
 58, 71A \$.74; 6K8, 7A8 \$1.09
 and many others not listed.

11 SPECIAL OFFERS 11

- 5-Tube "All American" Kit: 50L6, 35Z5, 12SA7, 12SK7, 12SQ7 per kit \$3.25
- 5-Tube "Miniature" Kit: 50B5, 35W4, 12AT6, 12BA6, 12BE6 per kit 3.25
- 25Y5 (same as 25Z5) List price \$3.20. Your cost .69
- 6AK5 Tubes ea. .89
- 6AB6 Tubes ea. .68
- 6J5GT Tubes ea. .59
- 1R5, 1S5, 1T4, 33A Tubes ea. .49
- Acorn Tubes: 954, 955, 956, 957, ea. .45
- Hearing Aid Tubes: 501Z to 509AZ, ea. .49
- 717A Transmitting Tubes: RK-34 and VT-127 ea. .98

CONDENSERS
 Fully guaranteed for 1 year. brand new
 individually boxed. Used by leading radio
 manufacturers at a price you can't beat.

ELECTROLYTICS

20/20 MFD @ 150	45c
20 MFD @ 150	32c
10 MFD @ 450	32c
10 MFD @ 450	45c
20 MFD @ 450	57c
10 MFD @ 25	24c
25 MFD @ 25	27c


BYPASS

400 Volts	600 Volts
.001	12c
.003	12c
.005	12c
.01	12c
.03	12c
.05	12c
.1	14c
.25	24c

Special Discounts on All Large Orders
 Minimum Tube order—1 doz.
 Minimum Condenser order—1 doz.
 All Merchandise fully guaranteed.
 Wire or write for catalog.
 We ship anywhere.
 20% deposit required on all orders.

COMMERCIAL RADIO
 36 BRATTLE ST., BOSTON 8, MASS.
 Department H

Electronics Made Easy!

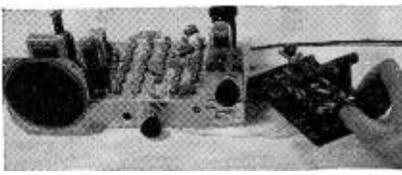

Magi-Klips Kit

Build 18 Experiments at Home—No Tools!

RADIO RECEIVER, HOME BROADCASTER, PHOTOELECTRIC RELAY, CODE PRACTICE OSCILLATOR, SIGNAL TRACER, REMOTE CONTROL RELAY, Phonograph Transmitter, Intercommunication Amplifier, Code Transmitter, Radio Frequency Oscillator, Telephone Line Amplifier, Electronic Switch, Phonograph Amplifier, Temperature Control Relay, Contact Detector, Electronic Metronome, Interval Timer (one-shot), Interval Timer (repeating).

With a Magi-Klips kit you cover the entire field of electronic engineering theory quickly in your spare time. It's simple to arrange the components for each circuit. No soldering. No tedious wiring. Kit operates on 110 v. AC or DC and includes 35Z5 rectifier, 50L6 power amplifier, 12SL7 double triode, powerful 4" speaker-mike, plate relay, broadcast and SW coils, tuning condenser and generous supply of resistors, condensers, chokes, extra wire. Parts worth double the price of kit.

Kit's 48-page manual has complete instructions and diagrams easily followed by the beginner. Remember, you need no tools, except possibly a screwdriver, with a Magi-Klips electronic experimenter's kit. **\$39.95 COMPLETE**

Schools—MAGI-KLIPS kits are excellent equipment for laboratory and classroom. Write for special discounts.
 Dealers—Some territories open. Write for trade discounts.

DEER & TAYLOR COMPANY X
 1340 Milvia St.
 Berkeley 9, Calif.
 Please ship Magi-Klips electronic kit(s).
 I enclose \$.....
 Please mail illustrated folder on the Magi-Klips Kit.
 Name.....
 Street.....
 City..... State.....

should take a few days off once in a while!) Naturally, these ionospheric storms are serious to the communications companies, since they do disrupt their circuits." * * *

Beira Data

We are indebted to Mervyn P. Laubscher, South Africa, for this late information received by him direct from CR7IB, Beira:

"Our station, CR7IB, consists of a HT4 Hallicrafters transmitter, with about 3 kw. power, working on a frequency of 7.255 megacycles. (Note: This is definitely a mistake and should be 7.155 megacycles—M.P.L.) Station CR7IC consists of a Utah transmitter of UAT-1 type, the power of which is approximately .1 kw., operating on a frequency of 3.498 megacycles.

"These stations, which are the sole property of the Aero Clube da Beira, broadcast in conjunction the same program at the following hours—Daily, except Sunday, 4:45-5:45 a.m. and 1-3 p.m.; Sundays, 4-7 a.m. News in Portuguese is read at 5:05 a.m. and 1:05 p.m.

"Our programs consist mainly of recorded music. Owing to the war, we were able to obtain necessary materials for the construction of only studios, one of which is already in use, and the other is now being given the final touches. We hope to be able soon to improve our programs, with variety shows, radio sketches, etc.

"A small number of amateurs enthusiastically maintain the stations in good working condition, hoping to see them grow up more and more as conditions permit."

The letter was signed "For Presidente da Comissao Administrativa das Emissoras do Aero Clube da Beira."
(Continued on page 154)

Bob Ham, manager of the music center at the Downtown Broadway store, Los Angeles, demonstrates the new General Electric television receiver to Mrs. Fay McCarthy, a Los Angeles housewife. Los Angeles recently celebrated Television Week during which time thousands of persons visited the exhibits of television receivers. Two-thirds of the receivers on display were table models while the balance were consoles. Public reaction to the special television programs broadcast during the show was reported to be good.



May, 1947

SILVER EXPERTS CHOOSE



"VOMAX" is the overwhelming choice of experts because it's the finest, perfected v.t.v.m. . . . because greatest demand makes greatest production and lowest cost to you.

"VOMAX" gives you a total of 51 ranges to directly measure d.c., a.c., a.f., i.f. and r.f. volts up through hundreds of megacycles, six resistance ranges covering 2 10ths ohms through 2,000 megohms, three output meter-decibel ranges from -10 through +50 db., six direct current ranges measuring from 50 microamperes through 12 amperes. Most important is the absolute stability, complete freedom from usual grid current errors . . . and its astronomical input resistance . . . an honest 6.6 megohms upon a.c., a.f., i.f. and r.f.; 51 and 126 megohms upon d.c. Voltage ranges measure from .1 through 3000 volts d.c., .1 through 1200 volts a.c.

If you want to guard your meter dollar investment . . . to make it only once for many years to come . . . then "VOMAX" at its present low \$59.85 net price is your logical choice . . . as thousands more wise technicians like yourself have proved to their profit.

Let's look at this matter of what meter you buy seriously . . . for your choice of this, the service technicians basic instrument, can spell either peace and profit . . . or annoyance and loss to you. You must have the best meter to meet "smart" competition. And "smart" competition overwhelmingly uses "VOMAX." The reason is simple. Other manufacturers have had to copy "VOMAX" inventions to try to satisfy your demand for a modern, post-war, obsolescence-proof universal meter. Yet, "VOMAX," the perfected v.t.v.m., stands head and shoulders above all other meters. This is proved by its heavy purchase and use by the Bureau of Standards in Washington, by Western Electric, G. E., Westinghouse, university after university, by top-ranking industrial laboratories, F.C.C., C.A.A., Veterans Administrations, schools, colleges . . .

NEW IMPROVED "SPARX"



Thousands of technicians today rely on "SPARX" dynamic signal tracer to save time . . . increase efficiency . . . cut their costs. It lets you hear and see signals . . . traces signal right an thru every receiver circuit from antenna thru voice-coil . . . is shap test speaker, too. Continuous laboratory research has now improved "SPARX" immensely . . . created the Improved Model . . . tremendously increased sensitivity . . . greatly expanded general usefulness. And the SILVER policy of protecting your dollar investment pays out handsomely . . . a free bulletin tells every user how to convert his "SPARX" into the new, Improved Model in a jiffy . . . goes to prove that for the really serious, profit-conscious technician there's no substitute for SILVER, that "SPARX" costing you only \$39.90 is outstandingly the world's best signal tracer. "SPARX" will earn you, too, more profits in less time than any other instrument you can buy.

906

Thanks for your patience. Model 906 Signal Generator is now flowing to your favorite jobber. And what an instrument . . . 90 kc. through 170 mc. on fundamentals . . . 8 air-trimmed bands . . . variable % 400 ~ amplitude modulation . . . built-in variable electronic FM sweep . . . laboratory triply adjustable attenuator . . . metered microvolts . . . output 1/2 microvolt to over 1 volt . . . multiply shielded . . . strays lower than \$500.00 laboratory generators! Yet all this costs you only \$89.90 net. Better order your 906 now for demand far exceeds production capacity on this precision instrument for months to come.


Send Post Card for Catalog of new measuring equipment, communication receivers, transmitters, kits, parts. See them at your favorite Jobber.

OVER 36 YEARS OF RADIO ENGINEERING ACHIEVEMENT

McMurdo Silver Co., Inc.

1249 MAIN ST., HARTFORD 3, CONNECTICUT

NEW RECEIVERS for Summer Market

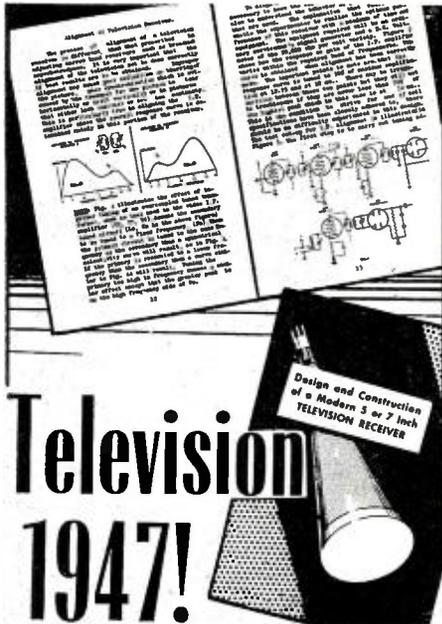

Television 1947!

**Amateurs, Experimenters,
Radio Servicemen...**

Now you have access to the secrets of post-war television. Vision Research Laboratories now brings you in its new series of television booklets complete and detailed plans for the construction of a 5- or 7-inch television-FM receiver! The plans in these books incorporate all of the latest design features plus a detailed parts list. There is no need to wade through textbooks to get this necessary information. These booklets furnish you with all of the information needed for the construction of television receivers, sweep alignment generator, etc.

NOW AVAILABLE At a new low price due to great demand "Design and Construction of a Modern 5- or 7-inch TELEVISION RECEIVER" and "Design and Construction of a Visual Alignment SWEEP SIGNAL GENERATOR."

Each booklet contains: Many pages of theory and practical design information. Detailed sketches, layout photographs and schematic diagrams. In addition, each booklet is furnished with an 11 x 17 inch wall chart working diagram.

SPECIAL TELEVISION COIL KIT including 10 matched coils for above and Television Receiver.
Complete line of TELEVISION and FM COILS—Write for Particulars!

VISION

Research
Laboratories

P. O. BOX #52, Kew Gardens 15, N. Y.

Enclosed is \$..... (Check or Money Order):

Quantity:

.... Television Receiver Booklet at \$1.75 ea.

.... Sweep Generator Booklet at \$1.75 ea.

.... Television Coil Kit \$4.95 ea.

Name.....

Address.....


City.....Zone.....

State.....N5

Order direct or through your local distributor
146

COMBINATION RADIO-INTERCOM
Electronic Laboratories, Inc. is introducing a new radio-intercom which has been designed for the modern executive who wants both radio and intercom service without the use of multiple units.

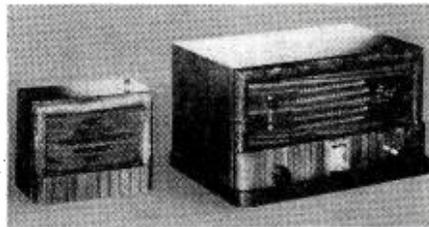The model is housed in a dark mahogany veneer cabinet which holds both master and slave units. The



radio-master unit blends with office furnishings and is fully finished on all sides to permit its use without regard to location.

Known as the Radio-Utiliphone, this unit will cover the standard broadcast band from 540 to 1520 kc. and measures 12 x 9 x 7 inches. The slave unit measures about 7 x 4 x 5 inches. As many as four slave units may be used with the master instrument.

Intercom controls are located on the top half of the front panel with the talk and listen switch on the left and slave station selector on the right. The radio switch and volume control is at the bottom left and the radio station selector at the bottom right of the front panel.

Operational details on this unit will be furnished by *Electronic Laboratories, Inc.*, Indianapolis, Indiana.

SONORA PORTABLE

The Model WDU-233, housed in a buff-colored luggage-type case with blending metal grille and contrasting brown plastic trim, has been added to



Sonora Radio & Television Corporation's line of portable receivers.

This three-way portable receiver tunes the full 535-1620 kc. broadcast band and features a built-in loop which eliminates the necessity for an aerial or ground wire.

The Model WDU-233 carries a tube complement consisting of a 1R5, 1U4, 1S5 and 3V4 plus a selenium rectifier. The unit is 12" wide, 9" high and 6" deep and weighs 7¼ pounds, less batteries.

Sonora Radio & Television Corporation, 325 North Hoyne Avenue, Chicago, Illinois, will supply further details upon request.

PHILCO TABLE MODEL

A new addition to the *Philco* low-priced table model receiver line has been introduced as the Model 204.

This postwar superheterodyne incorporates five tubes, including rectifier, a beam power pentode audio system, and an electrodynamic speaker for improved tonal quality on standard broadcasts.

The cabinet is all plastic and features a leather-grained pattern in



wood plastic with contrasting ivory plastic bezel, ivory knobs with bronze inserts, and a base finished in ivory.

Full details and price on the Model 204 will be furnished upon request by *Philco Corporation*, Philadelphia, Pa.



ECHOPHONE CONSOLE

A new feature has been incorporated in the recently introduced console model home receivers by *Echophone*. These consoles feature a.f.c. on FM. This new development makes feasible push-button tuning on FM stations with electronic correction of any error in mechanical setting of the push buttons.

The EC-403, one of the new units, is a fifteen tube console with separate push button and manual tuning on the broadcast and manual tuning on the short-wave bands. The frequency range is 540 kc. to 18 mc. on 'AM. A special feature of the receiver is two spread bands, one operating from 9 to

RADIO NEWS

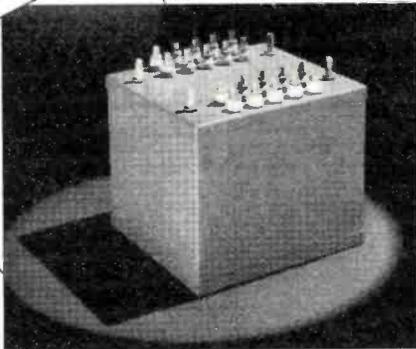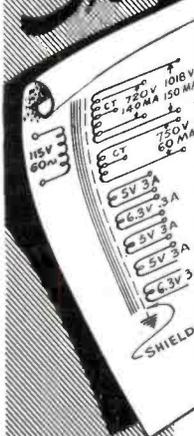SREPCO BRINGS YOU THE Best Transformer Buy THIS YEAR



POWER TRANSFORMER

Operate a complete medium power phone transmitter with this one transformer.

- o 500 Volts at 150 ma.
- o 325 Volts at 140 ma.
- o 350 Volts at 60 ma.
- o 3 - 5 Volt filament windings.
- o 2 - 6.3 Volt filament windings.
- o Static shield.
- o Army-Navy Ratings.
- o 5-3/4" x 6-1/2" x 5-3/8" high.

Net Wt. 22-1/2 lb. - Shipping Wt. 25 lb.

Only
\$3.95

STOCK NO. B-117




Isolation Transformer

115 Volt - 115 Volt with static shield. Operates cool at 40 watts.

- AC-DC set line noise reduction.
- Eliminates hot grounds in AC-DC set service.
- Absolute necessity for Intercoms in noisy electrical locations.
- 2-3/4" x 3-1/4" x 4" high.

Net Wt. 3-3/4lb - Shpg. Wt. 6 lb.

STOCK NO. B-116 Only
\$1.95

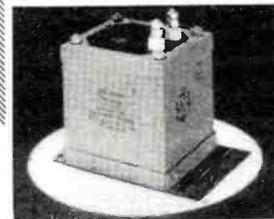

150 MA. Choke

- 150 ma., 5 henry
- 105 ohm DC resistance.
- Upright or thru-chassis mounting.
- Army-Navy Rating.
- 3" x 3-1/2" x 3-1/2" high.

Net Wt. 4-1/2lb - Shpg. Wt. 6 lb.

Only STOCK NO. B-203
\$1.95

TEAR OUT AND MAIL NOW TO:

SREPCO
STANDARD RADIO & ELECTRONIC PRODUCTS CO.
135 East Second Street, Dayton 2, Ohio

Please ship at once:

___ B-117 Power Transformer \$3.95 ea.
___ B-116 Isolation Transformer \$1.95 ea.
___ B-203 150 MA Choke \$1.95 ea.


Name _____ State _____
Address _____
City _____

MAIL ORDERS SHIPPED
WITHIN 24 HOURS
20% DEPOSIT REQUIRED

SREPCO
STANDARD RADIO & ELECTRONIC PRODUCTS CO.
135 E. SECOND ST. DAYTON 2, OHIO

Whether for Auto Radios or Dynamotors...

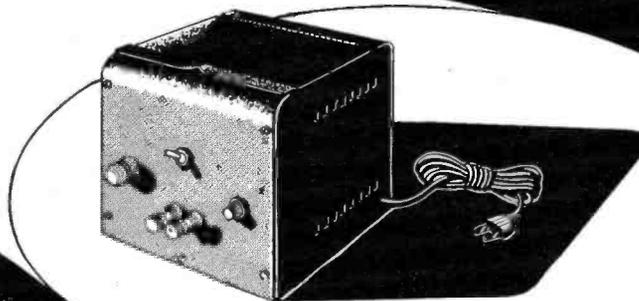...Weber D. C.
Power Supplies
deliver the current



Indispensable for the dealer, to demonstrate auto radios, and for the serviceman, to repair them, WEBER D. C. power supplies are the efficient, practical answer to a pressing need. Utilizing selenium rectifiers as the heart of the unit, WEBER supplies are assured of long, trouble-free operation. All WEBER supplies operate off the standard 115 volt A.C. 50/60 cycle line, are equipped with internal thermal circuit breaker and are housed in attractive crackle painted steel cabinets.

Eliminate the messy bulk of storage batteries and be assured of the accuracy your demonstrations or service need. The WEBER Model No. 6DC4B, as illustrated, delivering 6 volts D.C. at 4 amperes is an excellent value at \$15.75 net to servicemen and amateurs. Model No. 6DC8B, delivering 6 volts at 8 amperes, net \$20.50.

Here are leaders in the WEBER line; look them over and order from your jobber or direct from us. Should you require different specifications, a letter to our engineering department will bring a prompt reply.

Model—12DC4C	12 volts D.C. at 4 amps.....	net \$16.50
Model—12DC12B	12 volts D.C. at 12 amps.....	net 32.50
Model—28DC4B	24-28 volts at 4 amps.....	net 34.50
Model—28DC10B	24-28 volts at 10 amps.....	net 47.50
Model—28DC20B	24-28 volts D.C. at 20 amps.....	net 77.50

Literature on above models available to distributors upon request


WEBER RADIO LABORATORIES

1793 Nostrand Avenue

Brooklyn 26, New York



IT'S NEW

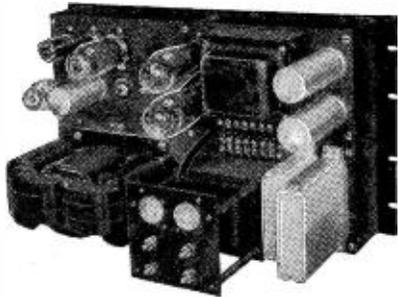

**The STABILINE
Electronic
Voltage Regulator**

Instantaneous in action with a maximum waveform distortion of 3 percent — this new completely-electronic voltage regulator maintains a stable output . . . within $\pm .1$ volt of nominal for line variations from 95 to 135 volts; within $\pm .15$ volt of nominal for any load current change or load power factor change from lagging .5 to leading .9.

Rated — Input: 95-135 volts, 1 phase, 60 cycles. Output: settable between 110-120 volts, 1 KVA. Let us supply you with complete technical and performance data.

**WRITE - - - PHONE - - - WIRE
OR MAIL THIS COUPON TODAY**

**THE SUPERIOR ELECTRIC CO. RA
BRISTOL, CONNECTICUT**

Gentlemen:

Please forward complete engineering and performance data on the new STABILINE electronic voltage regulator.

Company _____

Address _____

City _____ State _____

Name _____ Position _____

12 mc. and the other from 15 to 18 mc. FM broadcast coverage from 88-110 mc. is provided. An automatic record changer and ample record storage space is also included.

This receiver is housed in a Gothic



Chippendale cabinet and contains a single 15" speaker with Alnico V permanent magnets.

The Hallicrafters Company, 4401 West Fifth Avenue, Chicago 24, Illinois, is manufacturing this console and will supply additional data upon request.

PERIOD CONSOLE

In keeping with the West Coast trend toward casual living, the *Magnavox Company* has brought out a new model console radio which is housed in a French Provincial cabinet.

Authentic styling, featuring panelled doors and antique brass exterior fittings, make this radio-phono-



graph suitable for early American or ranch-house decorative schemes.

Distribution has been confined to the West Coast, but *Magnavox Company*, Fort Wayne, Indiana, will supply additional data upon request.

THE "COMMUTER"

A new 6-tube portable receiver which will operate on a.c.-d.c. or batteries has been added to the *National Union Radio Corporation* line of home radios.

Housed in a simulated leather-covered case with the genuine leather carrying handle, the "Commuter" incorporates low drain *National Union* tubes for added battery life. Full broadcast band coverage is provided with tuning by means of a slide rule

RESISTORS

**IS
OUR
BUSINESS**

1/2 WATT—1 WATT—2 WATT

**ANY QUANTITIES
ANY TOLERANCES**

Immediate Delivery

RESISTORS KIT

\$2.05 each

(Assorted and Not Mixed 100 pcs.)
60 pcs. 1/2 watt and 40 pcs. 1 watt


**ELECTRONIC PARTS
AND COMPONENTS**

LEGRI S COMPANY, Inc.

**846-850 Amsterdam Avenue
New York 25, N. Y.**

"SINGER" TUNER!

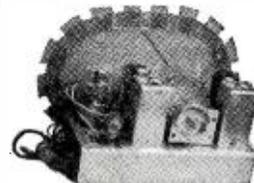Makes any amplifier into a 5 or 6 tube superhet radio



Completely wired
and ready
to operate

\$7.95
(Less Tubes)


Uses 12SA7-12SQ7-12SK7

"SINGER" PHONO AMPLIFIER!

3 tube AC-DC—
completely wired
and ready
to operate

\$2.95
(Less Tubes)

Uses 50L6-35Z5-12SQ7

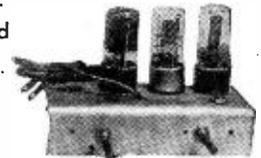

25% Deposit Required With Order

N. J. INDUSTRIAL CO.

309 Elm St. Newark 5, N. J.

RADIO COURSES

Servicing, Broadcast Engineering, Commercial
Operating, Television
INDIVIDUAL LABORATORY WORK—LEARN BY DOING.
DAY AND EVENING CLASSES
Licensed by the State of Maryland
Approved for Veteran Training
FREE TO VETS—TEXTBOOKS, TOOLS, TEST SET
Write for Bulletin

BALTIMORE TECHNICAL INSTITUTE
1425 Eutaw Place—Dept. R, Baltimore 17, Maryland
RADIO NEWS

dial scale. All controls are recessed to minimize damage to the receiver. The "Commuter" Model G-613



weighs 8 pounds, 8 ounces without batteries.


National Union Radio Corporation of Newark, New Jersey, will supply additional details on this receiver upon request.

A MIDGET MIDGET

Sentinel Radio Corporation has recently announced production on their "Treasure Chest" model, a tiny midget receiver measuring 4" high, 4" deep and 8" wide.

This model has five tubes and operates on either a.c., d.c., or batteries. It is available in two-tone plastic cabinets in a variety of colors.

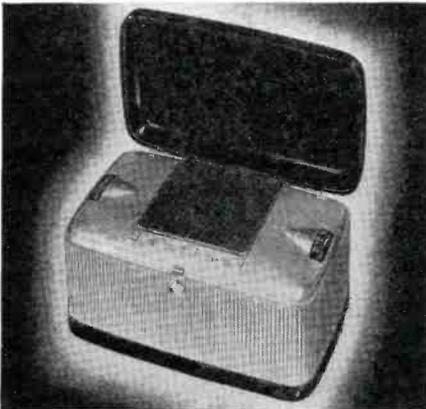The radio has been so designed that the listener may hear a program even when the cover is down by holding the



radio to his ear. This feature makes the set particularly suitable for travel, at ball games, office desks and at home.

Sentinel Radio Corporation of Evanston, Illinois, will supply additional information upon request.

FM-AM COMBINATION

Production has begun on two new FM-AM phonograph-radio combinations which will be known as the Farnsworth Models GK-102 and GK-141.

The Model GK-102 is housed in a modern cabinet which comes in either walnut or blonde "Golden Harvest" finish. The automatic phonograph which will handle twelve 10" or ten 12" records has an automatic play control which stops the mechanism after the last record in a stack has been played. The circuit uses nine tubes and a rectifier and has drift-

May, 1947

"TAB"

• NEW GUARANTEED

That's A Buy

ELECTRONIC PARTS •



VACUUM CONDENSER—100mmf/7500V 24Amp/32mc. List price, \$12. Dimensions 4 1/8" x 1 1/2" Dia. 1/2" D Terminals. "TAB" special \$4.95
Two for 8.95

VACUUM CONDENSER—50mmf/7500V 20Amp/32mc's. List price, \$10. Dimensions 3 1/8" x 1 1/2" Dia. 1/2" D Terminals. "TAB" special \$4.50
Two for 8.40
MFGD. by G.E. or equiv.

OIL CONDENSERS

4mf/50WVDC. Ten for..... \$ 2.00
10mf/800WVDC. Two for..... 2.50
20mf/600WVDC. Two for..... 4.95
4mf/600WVDC. TLA. 2 for 1.25
Tubular 0.1mf/600WVDC. Ten for..... 1.90
Tubular 0.1mf/800WVDC. Ten for..... 2.20
Tubular 0.1mf/1500WVDC. Ten for..... 1.50
3mf/330VAC/1000WVDC. GE Pyranol. 1.25
4mf/330VAC/1000WVDC. CD Dykanol. 2.98
15mf/330VAC/1000WVDC. GE Pyranol..... 2.95
2mf/2000WVDC. Avx&Wst. Two for..... 4.25
3mf/2000WVDC. Avx&Wst. Two for..... 5.00
3mf/5000WVDC. CD. Two for..... 14.50

2mf/5500WVDC. WST INERTEEN..... \$ 7.95
1mf/1250WVDC. WST..... 25.00
1mf/2500WVDC. WST INERTEEN..... 75.00
0.5mf/600WVDC. Bathub. Five for..... .95
2mf/600WVDC. TLA. Two for..... .79
0.5&0.1mf/600WVDC. Bathub. Five for..... .95
0.1&0.1mf/600WVDC. Bathub. Five for..... .95
0.25&0.25&0.25mf/600WVDC. Bathub. Four for..... 1.00
0.3mf/600WVDC. Tubular. Five for..... .95
0.1molded/600WVDC. paper. Ten for..... .99
0.5m/600WVDC. oil. Fifteen for..... 1.15
0.5&0.05mf/300WVDC. oil. Fifteen for..... 1.00
0.1mf/300WVDC. molded paper. Fourteen for..... .98
0.25mf/200WVDC. molded paper. Fourteen for..... .98
0.1mf/400WVDC. molded paper. Ten for..... .75
0.25&0.25&0.25mf/400WVDC. Bathub. Five for 1.00

GR VARIAC 200CU/880Watt. New..... \$14.95
TRANSPAT 880132V/18.2A-110V. New..... 29.50
BLOWERS *L.N. 115V/60cy Dual 200 CU/PM 13.95
DYNAMOTOR 12&24 Vinpt. 275V/110ma & 12V/3A New Navy Pmfld..... 1.95
DYNAMOTOR 12&24 Vinpt. 500V/50ma..... 1.95
RELAY TIME DELAY 115V/10Amp..... 1.49
NEON SIGLITE U4/GT Dual Tel Plug. 8 for..... 1.00
PRECISION 1% Onemex resistor. 3 for..... 2.45
SHALLCROSS TEN POINT DECADE SWITCH @..... .97

0.5mf/1500 TLA. Two for..... \$1.49
0.02mf/800WVDC. Tubular. Ten for..... .98
0.1mf/1000WVDC. Five for..... 1.00
0.03mf/400WVDC. Fifteen for..... 1.00
0.1 & 0.1 & 0.1mf/400WVDC. Five for..... 1.00
.001 & .006mf/1000V/7600WVDC. Twenty for 1.00
2mf/600WVDC TLA OIL. Two for..... .79
25mmf/10000V Wtg. New. Three for..... 75
6mf/1500WVDC. OIL. Two for..... 4.50
0.1mf/2500V. Mica (\$3.40). Two for..... 1.00
0.1mf/5000V. Mica (\$5). Two for..... 1.80
.0003mf/10000V Mica (\$42) SANGAMO G2..... 4.95
.00015mf/20000V EFF AVX1790-404, Mica 7.50
.00095mf/5000V AVX. Mica..... 3.50
CONDENSER KIT. Silver & Mica. Fifty for 2.00
CONTROL KIT ABJ. 50 to 2 Meg Pots. Ten for..... 2.50



SYNCHRONOUS H A Y D O N CLOCKMOTOR 60 cy / 10V 24 R P M S P SWITCH. EXCELLENT FOR AUTOMATIC KE Y E R, EXPERIMENTAL WORK. TIME DELAY. FLASHER. PRODUCTION TESTING. CLOCK 100's of uses. GOVT. Cost (\$7) "TAB" EXTRA SPECIAL \$1. Two for..... \$1.69

★ ANTENNA SECTIONS SC M50..... \$1.00
★ 39 1/4" long. Twelve for..... \$1.00
★ COLLAPSIBLE TELESCOPIC ANT., AN30 12" to 9 feet..... \$1.49
WE Dynamic mike..... 9.95
EDISON TIME DELAY RELAY 115V/10 Amp. 1.49
RF Choke 2.5MH/500ma HAMLUND CH500..... .69
SOCKET OCTAL AMPHENOL 78ST. 25 for..... 1.50
SOCKET MAGNAL CERAMIC 49-SSILL..... .49
RF Choke 1MH/300ma NATIONAL. 3 for..... .89
RF Choke 20MH/500ma HAMLUND..... 1.10

RCA 808 JAN-CRC New Gtd fl. 7.5V/4amp. plate 1500V/200 watts. Rated 140watts. output each "TAB" listed \$7.75) "TAB" price \$2.75 @. Two for \$5, with sockets & caps. \$5.40
Television Pulse Transf for ETO..... \$1.49
Navy Sea Trunks *L.N. 22" x 16" x 12" Fibre..... 3.00
Power Rheostats Assm't. 25& 50V. Six for..... 4.95
WESTON 796 Oak Case 8 1/4" Sq-2 Compart & Locks..... 4.50
Rotary Beam Coupler Const. Impedance..... 3.95
Mica Cond. Kit. 18 pieces 2500 and 5000..... 4.95
NAVY SP3 SYNCHROSCOPE NEW COMPLETE..... 59.50
Ext Cond. Rvy Duty SJ16 & Male & Fem Plug 1.00
WE Crystals boxed New 1N21.22-23. Three for 1.25
WESTGHE Dual AN IND 200microamp..... 4.50
GE METER 2 1/2" B'C OneMillamp..... 2.95
GE METER 2 1/2" B'C Five Amp RF..... 3.50
GE METER 2 1/2" B'C One Amp RF..... 3.95
GE DNI 1 1/2" MTR OneMa/100ohms..... 2.95
MICROPHONE T17 (LN) PB CARBON & CD..... 1.69
DAVEN ATTNTR "T" 600/600ohm 30DB..... 4.95
DAVEN ATTNTR "L" 5000ohm 60DB/10Pos. 1.45
DAVEN ATTNTR "POT" 50000ohm 60DB/30Pos..... 4.95
DAVEN 13CKT Sw 2SPDT/3SPDT/SP3P HV..... .79
VOM ELECTRONIC SC. 1-107-F COMP..... 19.95
WE MIKE DYNAMIC 20' CABLE & STD..... 9.95
GE DOOR INTERLOCK SAFETY SWITCH. Two for..... 2.98
200kc DC-15A STANDARDS 200kc-10cy..... 1.95
SC A27 PHANTOM ANTENNA NEW 6MANUAL 1.00
S.C. TUNING UNIT BC-746A&2XTALS FT243. 1.95
SPRAGUE 10Meg TenKV MEGOMAX MFA1..... 1.75
SPRAGUE 12Meg 12KV MEGOMAX MFA1..... 1.95



Resistor Kit BT 1/2 & 1 Watt 50to2me. 100 for. \$2.50
W.W. Resistor Kit. 20 for..... 1.00
Knob Kit Ass't with Bushings. 25 for..... 1.25
Rotary Switch Kit. Six for..... 1.75
Socket Kit 25 Ass't Ceramic, Mica, B etc..... 2.35
RM-53 Remote Control for Transmitter. Also TL..... 3.49
Transf line to line 500, 333, 250, 200, 125, 50ohms ± 1DB Cased THERMADOR Mfar. 1.95
Micro Switch-MU Leaf SPDT 15A/125V. Two for..... 1.08
Bias Trans 90, 60, 70V LAMP Cased GE..... 2.95
6G4 Boxed New Gtd @ 50c. Five for..... 2.00
6AK5 Boxed New Gtd @ 8c. Ten for..... 8.90
6AG5 Boxed New JAN @ 1c. Ten for..... 7.49
2050, 2X2, RK60/1641, 6SL7, 1E7G @..... 1.25
35L6, 50L6, 35Z5, 12SQ7, 12SH7. Two for... 1.80
WE 717A Door Knob Tube New. Two for... 3.85

RADIO EQUIPMENT RC-148-C—2 Units Power Supply Furnishes all Voltages For Equipment Inpt 343Watts 117.5V 60cy Contains 4Pll&Plate Trans Chokes etc. Trans-Receiver Ant Match Section Pulse Shaper Mod RF Oscillator Range 154-186Mc Superhet RF&IF Stages Video Amp Tuning Eye etc. Freq. can be lowered to 144-148Mc. "TAB" PRICE..... \$49.95

VIBRAPACK & STORAGE BATTERY NEW 4V/40AH-50V Output 156V/30ma, 3V/375ma/1.5V/200ma 7.5V/20ma. NAVY MANUAL NEW COMPLETE. TBY..... \$ 9.95
OSCILLOSCOPE 3" KR 3BP1 includes Transf 115V/60cy Pr 375VCT/110ma 1320V. 5V/3A. 2.5V/3.25A. 6.3V/2.75A. New Tubes 3BP1 C'Ray 5Y3GT Rect 2V3 GRect. Condrs, Choke, Low&HV supply. Complete "TAB" PRICE..... 16.95
FOXORO MECHANICAL RECORDER with 110V/60cy Motor-Mech & Elect Recording (\$200)..... 69.95
VT127A Tube New & Connectors. Two for... 5.98
SELEN IT&T 68AV1 F.W. 85V/2.4A..... 6.95
COPPER OXIDE WST RECTOX F.W. 12V/1.25Amp..... 3.40
MAZDA # 323/3V/190ma (LP \$1.85). Four for..... 1.00
MAZDA # 49 Minbay 2V/60ma (15c) 10 for NE 15&51 Neon Glomamp 1/25Watt. 10 for... 1.80

Brand new gov't sealed and inspected packed in oversize cans synchro-transmitters A.C. 115V-60cy. operation. Continuous heavy duty type—High torque 46 oz. wt.—105% Precision accuracy made for gun fire. Control cost gov't \$80; wt. each 5 lbs. "TAB" special two for \$14.95.
S2 Min. order FOB N.Y.C. Add Postage all orders and 25% deposit. Worth 2-7230. Send for catalogue 99. Specialists in International Export. School, College & Industrial trade. Moneyback "TAB" Guarantee.
TRANSF & CHOKES UTC-115V/60cy3200 VCT & Tap 1560VCT/20ma&Two Chokes & 2 2mf/2000WVDC Condrs&866A'S & Transf..... \$28.95
TRANSF 120VCT/30ma PRI 105-120V/50cy. 6.95
TRANSF 10VCT/8amp 115V60cy indt. 3.50
FRIEZ BAROMETRIC VARIABLE 140000 ohm..... .97



ANTENNA SECTIONS SC M50..... \$1.00
★ 39 1/4" long. Twelve for..... \$1.00
★ COLLAPSIBLE TELESCOPIC ANT., AN30 12" to 9 feet..... \$1.49
WE Dynamic mike..... 9.95
EDISON TIME DELAY RELAY 115V/10 Amp. 1.49
RF Choke 2.5MH/500ma HAMLUND CH500..... .69
SOCKET OCTAL AMPHENOL 78ST. 25 for..... 1.50
SOCKET MAGNAL CERAMIC 49-SSILL..... .49
RF Choke 1MH/300ma NATIONAL. 3 for..... .89
RF Choke 20MH/500ma HAMLUND..... 1.10

"TAB" DEPT. RN-5, 6 CHURCH ST., NEW YORK 6, N. Y., U. S. A. "TAB" CORNER CHURCH AND LIBERTY STS., ROOM 200

TOROIDAL COIL FILTERS


... are the answer to any network problem

- SHARP CUT-OFF
- LOW INSERTION LOSS
- HUM PROOF
- COMPACT
- HIGH STABILITY

Toroidal Coils

Inductance—1 MHY to 3 HYS
 Frequency—300 cy. to 30,000 cy.
 "Q"—55 at 1000 cy.; 150 at 3000 cy.

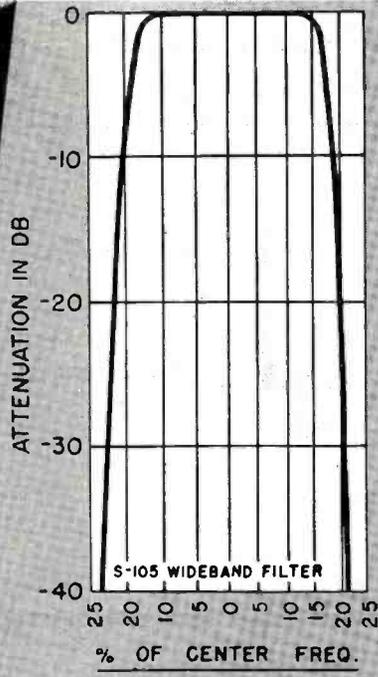Ask to be put on mailing list for complete catalogue of coils and filters.



Actual measurements taken on Toroidal Coil Filter manufactured by Burnell & Co.

Burnell & Co.

Designers and Manufacturers of Electronic Products

45 WARBURTON AVENUE, YONKERS 2, N.Y.

MORE SMASH BUYS at National Radio Distributors

Famous National Radio Kits NOW—Immediate Delivery from Stock

Component Parts Mounted on Chassis for Easy Wiring

All Radio Kits complete, including beautiful plastic cabinet, built-in loop antenna, new Alnico speaker and full instructions for assembly. For 110-125 AC/DC.



White Plastic Cabinets now available—\$1.00 additional.

MODEL N.R.-7—5 Tube Superheterodyne, uses 12SA7, 12SK7, 12SQ7, 50L6 & 35Z5 tubes. Your Net \$11.95
 Kit of 5 Matched Tubes..... Your Net 4.50

MODEL N.R.-5—5 Tube "Two Band" Superheterodyne Tubes as above. Band 1—550/1600 K.C. Band 2—6/18 Megacycles..... Your Net \$13.95
 Kit of 5 Matched Tubes..... Your Net 4.50

MODEL N.R.-6—6 Tube Superheterodyne, uses 2-12SK7, 12SA7, 12SQ7, 35L8 & 35Z5 tubes. Your Net \$13.75
 Kit of 6 Matched Tubes..... Your Net 5.50

MODEL N.R.-1—4 Tube T.R.F., uses 12SK7, 12N17, 50L6, 35Z5 tubes..... Your Net \$10.95
 Kit of 4 Matched Tubes..... Your Net 3.50

NOW! IMMEDIATE DELIVERY

The New TRANSVISION Television Kit

If you can use a soldering iron you can assemble this kit. Step by step instructions include wiring diagrams, schematic and pictorial diagrams. Finished article is guaranteed to operate satisfactorily if directions are followed exactly.

This Kit is complete including 17 tubes, 7" picture tube. Finished front panel. Pretuned R-F unit, all solder & wire, 60' of low loss lead-in and specially designed Television Antenna. **THERE IS NOTHING ELSE TO BUY.** Provisions for six television channels.

Price Complete \$159.50

Please include 25% with order. We will ship balance C.O.D. Cable address: Enardco

Write for New Free Catalog. It's Just Out.

National Radio Distributors

899a Southern Blvd., New York 59, N.Y.

150

Columbia's May Specials!

HOOK-UP WIRE

22 Ga. solid bare copper with plastic insulation. Ideal for alarm systems, inter-com work, Bell wire, etc.

Per 100 ft. \$2.95
 Per 100 ft. coil 34c

RUBBER HAND PLUG

This is a hot item. A large handle cap, screw type connectors.

Per 100 plugs \$7.50
 Per 1000 plugs \$71.90

18 Ga. SOLID PUSH-BACK WIRE

Highest quality, lacquered braid over celanese serve. Easy push-back. Tinned copper conductor. Yellow only.

100 ft. coil 68c
 1000 ft. spool \$6.10

We carry in stock for immediate delivery many types of wire and cable in gauges of from 23 to 2, in addition to various types of multi conductor cable for many uses. We also manufacture cord sets and cables to specifications. Send us your inquiries for prompt attention.


Our new catalog will be ready for distribution shortly. Write for your copy today.

COLUMBIA WIRE & SUPPLY CO.

5740 NO. ELSTON AVE.

CHICAGO 30, ILLINOIS

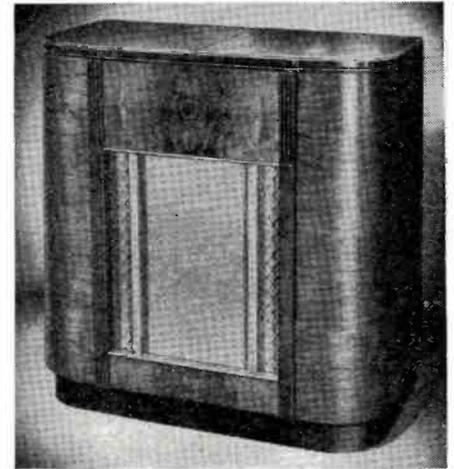corrected, push-button electric tuning, a.v.c., a shielded rotatable built-in antenna for AM reception and a built-in dipole antenna for FM reception, bandspread tuning, push-pull ampli-



fication, and a 12 inch reverberation-insulated PM Alnico speaker.

The companion model to this receiver is the GK-141 which is housed in a mahogany cabinet of traditional Sheraton styling. This 13 tube, (plus rectifier) set has short-wave as well as FM and AM bands, eight push-buttons to tune FM and AM stations, and travelite slide-rule dial.

Further information on either or both of these instruments can be obtained from *Farnsworth Television & Radio Corporation*, Ft. Wayne, Ind.

NEW PORTABLE

Garod Radio Corporation of Brooklyn has entered the low-priced luxury portable field with their new Silver Anniversary Model 5D3.

This radio has a built-in loop antenna hidden in the front-raising plastic cover. Designed especially to appeal to the younger set and the summer vacationer, the Model 5D3 is



available in bright pastels and two-tone combinations.

The receiver weighs less than 6½ pounds with batteries and is designed to play anywhere on a.c., d.c., or batteries.


Additional information on this model portable will be furnished by *Garod Radio Corporation*, 70 Washington Street, Brooklyn 1, New York.

"VIDEORAMA" RECEIVERS

Stewart-Warner Corporation of Chicago has begun shipping the first of their new line of "Videorama" radio-television receivers to dealers.

RADIO NEWS

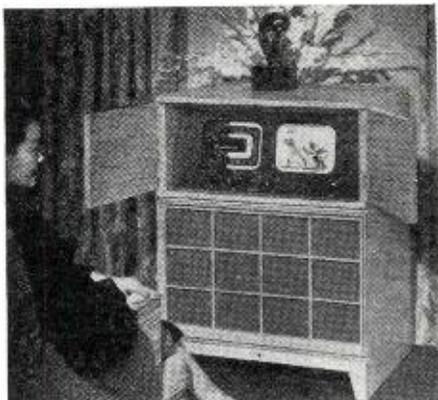Available in custom-built cabinets of either modern bleached walnut or Georgian natural walnut, the set covers all 13 video bands and can be used anywhere in the United States within range of television broadcasting facilities. The set provides standard AM radio reception as well as television sound on FM. The set has a ten-inch, direct-view cathode tube, plus 21 other tubes and two rectifiers.



A 12" superdynamic speaker has been incorporated.

Illustrated is the Model T-711 "Videorama" in a bleached walnut cabinet. Stewart-Warner Corporation, 1828 W. Diversey, Chicago, Illinois, will furnish details on this television line upon request.

TABLE COMBINATION

Andrea Radio Corporation has a new table model automatic radio-phonograph on the market which will cover both standard broadcast and the short-wave bands.

Known as the Model CO-UI15, this a.c. operated receiver is housed in a modern classic cabinet with walnut finish. The full vision illuminated dial



is set into the cabinet at an angle to permit easy tuning on both of the operating bands.

Phono jacks for television sound have been provided on the chassis to meet future requirements.

Andrea Radio Corporation, 27-01 Bridge Plaza North, Long Island City 1, New York, will provide more information on this deluxe table combination unit to those requesting it direct from the company.

—50—

May, 1947

DO You HAVE THESE REPAIR PROBLEMS?



"Just Follow the Signal"

Amazing New STETHOSCOPE Finds ALL Radio Faults Double-Quick!

Do tough service problems waste your valuable time in the shop? Have you been looking for a new kind of test instrument that will save you time and help you earn more? At last there is such an instrument for you! It's the new FEILER ELECTRONIC "STETHOSCOPE" (Registered U.S. Patent Office). It's the *newest, fastest* way to get to the heart of radio trouble in a flash—in minutes instead of hours! Gives you double-quick "know-how" on the toughest jobs—no adjustments required—absolutely simple for anyone to use. Just move the handy Probe and follow the signal right through from antenna to speaker. To isolate and locate trouble, you simply "listen in" on or "look at" the signal as it progresses through the circuit. Finds trouble at First Grid, RF, IF, Audio; tests parts; locates causes of mistracking, intermittence, fading, distortion, etc. Features: 1" dia. shielded probe with 3-ft. cable; Full 5" PM Speaker; Provides for connection of your present V.O.M. as R.F.—V.T.V.M. and output meter; Headphone connection. In brown-finished extra sturdy steel case with handle, 11 1/4"x8"x6". Complete with valuable *Radio Service Guide* . . . You owe it to yourself to own this time-saving, profit-boosting new instrument. Satisfaction Guaranteed. Order your FEILER STETHOSCOPE today! See your local jobber or use the coupon below.

AC MODEL TS-3
Electronic STETHOSCOPE for 105-125 V. 50-60 cycles A.C. Complete with 4 tubes, probe and Service Guide. Wt., 10 1/2 lbs.

ONLY
\$34⁹⁵

Battery Model TS-2
Battery-operated. Complete with 3 tubes and Guide (less batteries). Batteries are low-cost, long-life type; fit in case. Wt., 5 1/2 lbs.

ONLY
\$29⁹⁵

FAMOUS LOW-COST TS-1 FOR EXPERIMENTERS, BUILDERS, AND SMALL RADIO SERVICE SHOPS

Thousands sold and in daily use! An absolutely dependable Signal Tracing Analyzer at the lowest price ever asked for such an instrument. Easy to use—no special skill needed. Just touch the Detector Probe to any portion of the circuit—the signal you hear in the 'phones locates and isolates the trouble for you in just minutes. Works with any magnetic headset, 1000 ohms or higher. Self-contained in compact 6 3/4"x4 3/4" brown metal case; has snap-lock cover and battery compartment. The TS-1 is supplied complete with miniature vacuum tube, less batteries and headphone. Requires only one 22 1/2 v. battery and one No. 2 flashlight cell. Complete with *Radio Service Guide*.

ONLY
\$9⁸⁵



IMMEDIATE DELIVERY!

FEILER

Place your order with your regular parts jobber. If he can't supply you, write for name of the nearest local jobber stocking our instruments—or send your order to the factory.

FEILER ENGINEERING CO., Dept. 1-E-7, 422 S. Dearborn St., Chicago 5, Illinois

- Ship me one TS-3 STETHOSCOPE. Ship me one TS-2 Battery-operated STETHOSCOPE.
 Ship me one TS-1 Analyzer \$ enclosed. Ship C.O.D.
 Send FREE Descriptive Literature covering Models

Name

Address

METERS

COMBINATION OFFER

A.C. VOLTMETER Triplett Model 331-J.P. $3\frac{1}{2}$ " round flush bakelite case, white scale, 0-150 volts. Complete with external wire wound precision resistor to increase range to 300 Volts.
A.C. AMMETER Triplett Model 331-J.P. (same as above) 0-30 Amps A.C.

SPECIAL OFFER

\$8⁹⁵

BOTH METERS

D.C. MICROAMMETERS

W.E., $3\frac{1}{2}$ ", concentric style, 200 microampere \$4.00
G.E., DO-41, $3\frac{1}{2}$ ", 500 microampere scale, 20 K.V. with paper V.O. M.A. scale 4.95

D.C. MILLIAMMETERS

W.H., RX-35, $3\frac{1}{2}$ " Sq. 1 M.A. mvt., 55 Ohms resistance with paper V.O.M.A. scale \$4.95
W.H., NX-35, $3\frac{1}{2}$ ", 50-0-50 M.A. 4.50
Weston, 506, $2\frac{1}{2}$ ", 100 M.A. 3.95
W.H., NX-35, $3\frac{1}{2}$ ", 200 M.A. 4.00

D.C. VOLTMETERS

Weston, 506, $2\frac{1}{2}$ ", 20 Volt. \$3.95
W.H., NX-35, $3\frac{1}{2}$ ", 50 Volt 5 M.A. 4.50
W.H., NX-35, $3\frac{1}{2}$ ", 1.5 K.V. with external 1000 r/v precision resistor 6.95
W.H., NX-35, $3\frac{1}{2}$ ", 2.0 K.V. with two 1 Meg 1000 r/v prec. resistor 7.50

D.C. AMMETERS

G.E., DO-41, $3\frac{1}{2}$ ", 1.5 Amp. Black scale \$3.00
G.E., DW-51, $2\frac{1}{2}$ ", 30-0-30 A. D.C., metal case 3.50

A.C. VOLTMETERS

W.H., NA-35, $3\frac{1}{2}$ ", 15 Volt. \$3.95
W.H., NA-35, $3\frac{1}{2}$ ", 150 Volt. 5.50
G.E., AO-22, $3\frac{1}{2}$ ", 150 Volt. 5.50
Hickok, $2\frac{1}{2}$ ", 150 Volt, metal case. 2.95
Triplett, 332-J.P., $3\frac{1}{2}$ ", 150 Volt, metal case 4.50
Triplett, 232-C, $2\frac{1}{2}$ ", 300 Volt, metal case 4.95

RADIO FREQUENCY AMMETERS

Weston, 425, $3\frac{1}{2}$ ", 120 M.A.R.F. \$8.50
Weston, 507, $2\frac{1}{2}$ ", 1.5 A. R.F. Black scale, metal case. 2.95
W.H., NT-35, $3\frac{1}{2}$ ", 3 A. R.F. 5.50
Simpson, $2\frac{1}{2}$ ", 3 A. R.F., expanded at lower end of scale. 3.50
G.E., DW-44, $2\frac{1}{2}$ ", 6 A. R.F., Black scale 2.50
W.H., NT-33, $2\frac{1}{2}$ ", 9 A. R.F., Black scale 2.50

SPECIAL METER

Running Time Meter, G.E., 8 KT-8, $3\frac{1}{2}$ " Square, 115 volt, 60 cycle, reads to 99,999 hours, Black scale. \$4.50

All meters are in round flush bakelite case, white scale, unless otherwise specified

SURPLUS—NEW GUARANTEED

All orders F.O.B., N.Y., 25% Deposit required on C.O.D.'s. Be sure to include sufficient postage, excess will be refunded.

MARITIME SWITCHBOARD
336 Canal Street - New York 13, New York

BIZ QUIZ

Test Your
Sales Ability

One of a series of sales aptitude tests especially prepared for RADIO NEWS by Mr. George Speer, Director of Institute for Psychological Service, Illinois Institute of Technology.

1. Would you rather read about (a) slum clearance (b) prominent politicians (c) the way our language is changing
2. Do you haggle over prices with junkmen or tradesmen (a) often (b) sometimes (c) never
3. If a salesman calls on you at your home can you get rid of him without purchasing (a) easily (b) with some difficulty (c) considerable difficulty or not at all
4. Within the last five years have you been selected as a leader of a group (a) none (b) one but less than five (c) five or more
5. If you were seeking a new position would you (a) have a friend interview an employer for you (b) write a letter to an employer, applying for a job (c) interview an employer in person to apply for a job
6. Does it make you uncomfortable to have others regard you as different or unconventional? (a) yes (b) no (c) not sure
7. Do you suddenly change from pleasant to unpleasant moods (a) seldom (b) fairly often (c) frequently
8. If you were in a strange town and had some time to spend which would you be more likely to visit? (a) a factory making electric motors (b) a museum of science (c) an advertising agency
9. If others around you are pessimistic or depressed, do you tend to be (a) pessimistic (b) optimistic (c) not affected
10. If income and all other conditions were equal, which would you prefer (a) to be in business with a partner (b) to be in business for yourself (c) to work for a superior whom you greatly respected
11. If it were your job to explain a new invention to a large number of people, how would you prefer to do it? (a) write a description (b) talk to a group to explain it (c) give a demonstration of its operation
12. For your own personal use do you borrow (a) frequently (b) occasionally (c) practically never
13. Which do you prefer to read? (a) about business trends (b) social customs of foreign countries (c) reviews of recent plays
14. If you were dining out with a guest whom you were trying to impress, and the bill was more than you had expected it to be, would you verify the bill (a) surreptitiously (b) not at all (c) openly
15. In a disagreement with an older person whom you respect do you usually (a) maintain your views (b) seem to agree with him, but try to carry your point indirectly (c) agree with him verbally, and let it go at that
16. Would you like to be known as an authority on (a) contract bridge (b) agricultural problems (c) billboard advertising
17. At a social affair would you (a) prefer not to be a leader (b) accept leadership if the others wanted you to (c) enjoy being a leader
18. To ask and receive pay for debts means (a) remit (b) collect (c) exchange
19. Which do you like best (a) people who borrow things (b) thrifty people (c) emotional people
20. When people praise you, do you (a) feel that you are doing well enough (b) feel like doing even better (c) ignore it and remain unaffected
(Answers on page 165)


AT THE RADIO SHOW!

MAY 13th to 16th, INCLUSIVE
HOTEL STEVENS, CHICAGO


Bogen

COMMUNO-PHONES • SYSTEMS
AMPLIFIERS • ACCESSORIES

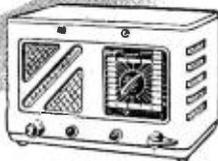The latest BOGEN equipment will be on exhibit at the show. Stop at Booth # 40 and see what's new in this famous line of inter-communication and amplifier equipment. Our engineers will be on hand to answer all technical questions.



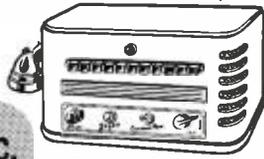Type A Communo-phones are designed for efficient service where economy is essential.



Type I Communo-phones offer exclusive features and flexibility, capable of meeting any requirement.



David Bogen CO. INC.

OFFICES: 663 BROADWAY, NEW YORK 12, N. Y.

BOGEN SOUND SYSTEMS • AMPLIFIERS
COMMUNO-PHONES • ELECTRONIC EQUIPMENT

RADIO TUBES

CONTINENTAL

R.M.A. Guaranteed Top Quality—
For Immediate Shipment

Good Tubes at Good Prices!

01A	.50	6J7G	.90	14A7/12B7	\$1.59
02A	.32	6L6G	1.59	4C7	1.75
1A3GT	.90	6Q7	1.08	25L6GT	.90
1A7GT	1.08	6SN7GT	1.08	25Z3	.81
1C6	1.08	6SR7GT	.81	25Z6GT	.81
1LA4	1.92	6SG7GT	1.08	2E	.63
1LA6	1.92	6SH7	1.08	2F	.57
1L6S	1.92	6SK7GT	1.08	32L7GT	1.59
1LH4	1.92	6SN7GT	1.08	33	1.08
1J4	1.32	6SQ7GT	.90	35L6GT	.81
1LN5	1.92	6SK7GT	1.08	35K4	.90
1N3GT	1.08	6X3GT	.81	35Z3	1.08
1P5	1.32	7A4	1.08	35Z5GT	.89
1Q4	1.32	7C7	1.08	7A	.75
1R5	1.32	7A6	1.08	38	.90
1S5	1.32	7AT	1.08	39 44	.81
1T4	1.32	7AF7	1.08	41	.69
1U4	1.32	7B6	1.08	42	.69
1U5	1.32	7C5	1.08	43	.90
1U6	1.32	7C8	1.08	46	.90
5A4	1.32	7C9	1.08	47	.90
3EP4	1.59	7F7	1.32	50A5	1.59
3EP5	1.32	7H7/1232	1.59	50B5	1.32
3Q5GT	1.32	7HT	1.59	50L6GT	.90
3R4	1.32	7J7	1.59	57	.75
3T4G	.81	7N7	1.08	70L7GT	1.59
5Y3GT	.57	7Y4	1.08	71A	.75
6Y4G	.63	7Z4	1.08	75	.69
6AT	.81	12A6GT	1.59	76	.75
6A8GT	.81	12A7GT	.81	77	.75
6C6	.81	12AT6	1.32	78	.75
6L6	.81	12BA6	1.32	79	1.32
6F5G	.90	12BE6	1.32	80	.87
6I6GT	.69	12C5	1.59	81	1.59
6Q6	1.08	12Q7GT	.75	84	1.08
6R6GT	.81	12R7GT	.90	85	.81
6K7	.90	12S7GT	.90	117L7GT	1.92
6K7GT	.81	12T7GT	.90	117P7GT	1.92
6J5GT	.75	12N7	1.08	117Z3	1.32
		12M7	1.08	117Z6GT	1.32

All tubes individually packed. Each tube carries a standard R.M.A. guarantee. Defective tubes returned during the guarantee period will be replaced.

ADDITIONAL DISCOUNTS:

30%—orders of 250 or more
20%—orders of 100
15%—orders of 50
10%—orders of 25

Telephone Longbeach 4428

Continental Corporation

1800 WINNEMAC AVENUE • CHICAGO 40

The Oldest Radio Tube Company in Chicago • Established 1920

May, 1947

SURPLUS

RADIO SERVICEMEN • EXPERIMENTERS • AMATEURS
SAVE BIG MONEY!
"BUILD YOUR OWN KITS"

If you were to buy this equipment you would have to pay from two to three times more. Here are top values in high priced equipment from which you will get dependable performance and lasting life.

RADIO PARTS

BUILD A HEAVY DUTY AC POWER SUPPLY

3 Outstanding Features:

- 1—270 VDC @ 150 MA 1.5% Ripple
- 2—110 VAC isolated @ 250 Watts
- 3—Bias Voltage, 100 V @ 40 MA

ALL FOR

\$12 PER KIT

Kit Includes:

1 transformer, 2 sockets (octal), 1 dual choke 3 Hy-15 Hy, 1-100 K 1/2 Watt Resistor, 1 toggle switch, 1 line cord, 1 fuse holder, 1 chassis 10 1/2x6 1/2x3, 1 8.5x 8.5 condenser, 1 outlet socket, 2 tubes: 1-5R4GY 1-6X5, 2 condensers; 1-2 MFD 1-10 MFD-150 V resistors; 2-10K-5 W, 1-10K-10 W, 1-1K-1/2 W. Hook-up wire 1 pilot lite assembly, Diagram. Less bias parts: 1-6X5 tube, 2 resistors, 1-10K-5 W 1-1K-1/2 W, 1 octal socket, 1 condenser 2MFD.....\$10 per kit

BUILD AN AC-DC POWER SUPPLY

90 V @ 30 MA. Used to replace 90 V batteries. Diagram included.
COMPLETE, per kit \$3

BUILD AN AC POWER SUPPLY

250 V @ 60 MA. 6.3 @ 2 Amps. Diagram included.
COMPLETE, per kit \$6

BUILD A TOP QUALITY SIGNAL TRACER

This kit would cost more than double our price. Kit includes: sloping panel cabinet 14x8x8, meter on one side—speaker opposite, 4 sockets providing for 4 tube circuit, adaptable for electronic voltmeter, diagram included. Unit can be used as a 3 watt amplifier—requires little rewiring—bench tested.
COMPLETE, per kit \$20

BUILD A 4-TUBE AMPLIFIER WITH 8" JENSEN P.M. SPEAKER

AC, 4-7 Watt, 4 tubes, diagram.
COMPLETE, per kit \$18
Less speaker \$12 per kit

CRYSTAL TUNING UNITS FOR AMATEUR BANDS

..... Each \$2.00

BUILD AN AC 4-TUBE SIGNAL GENERATOR

Kit includes: 2 tube oscillator with 6 band switch and 6 coils, ready wound and center tapped, with all necessary parts to make a complete unit, 1 multi-vibrator circuit included; cabinet size 14x8x8; geared tuning; diagram.
ALL FOR \$15 PER KIT

BUILD AN AMPLIFIER (AC-DC)

Kit includes: 1 chassis 5x 3 1/2x3, 3 octal sockets, 1 1/2 Meg Volume control, 3 10 Watt WW resistors 125 ohm, 1 resistor 5M 1/2 Watt, 3 tubes 1-12SN7, 2-6SL7, 1 toggle switch, 4 mica condensers .003 MFD, 2 filter condensers, hook-up wire and hardware, diagram.
ALL FOR \$5 PER KIT

BUILD A RECEIVER Frequency 2-30 MC

Kit includes: 1 chassis 5x 3 1/2x3, 2 octal sockets, 2 condensers 10 MFD, 1 RF choke 2.5 MH, 4 resistors 1-50 M 1-3 Meg 1-5 M 1-250 M, 1 slug tuned coil, 1 5 M ohm volume control, 2 filter condensers, 1 toggle switch, 1 roll coil wire, 2 mica condensers .003, 2 tubes 1-12SN7, 1-6SL7, 1 condenser 330 MMFD, 3 125 ohm 10 Watt WW resistors, hook-up wire and hardware, diagram.
ALL FOR \$4 PER KIT

BUILD A TRANSMITTER Frequency 2-30 MC

Kit includes: 1 chassis 5x3 1/2x3, 3 octal sockets, 1 toggle switch, 3 10 Watt WW resistors 125 ohm, 2 mica condensers .003, 1 100 M resistor, 1 roll coil wire, 2 tubes 1-12SN7, 1-6SL7, 2 slug tuned coils, 1 filter condenser, 1 RF choke 2.5 MH, 1 100 MMFD mica condenser, 1 key, hook-up wire and hardware, diagram.
ALL FOR \$4 PER KIT

BUILD A CODE OSCILLATOR (Audio)

Kit includes: 2 tubes 1-12SN7, 1-6H6, 2 sockets, 2 resistors 1-100K 1-10K, 3 condensers 1-.001, 1-.01, 1-.005, 1 chassis, 1 oscillator coil, 2 electro condensers, 1 line cord, 1 key, hook-up wire and hardware, diagram.
ALL FOR \$4 PER KIT

BUILD A PHONOGRAPH OSCILLATOR (700 KC, 1400 KC)

Kit includes: 2 tubes 1-6SJ7, 1-6H6, 1 condenser .04, 1 rheostat 5K, 2 octal sockets, 2 condensers, 1 chassis, 1 oscillator coil, 3 resistors 1/2 watt, 1-100K, 1-5K, 1-2K, 2 125 ohm 10 watt WW resistors, 1 line cord, hook-up wire, diagram.
ALL FOR \$4 PER KIT

COMPLETE KITS OF "HARD-TO-GET" CRITICAL ITEMS!

Cat. No.	Quantity	Description	Price Per Kit
122	3 lbs.	Asstd. Radio Parts	\$1.00
123	3 lbs.	Asstd. Screws and Washers	1.00
124	3 lbs.	Asstd. Cables w/Connectors	1.00
125	5 Asstd.	Volume Controls	1.00
126	10 Asstd.	Bath Tub Condensers	1.00
127	300 Asstd.	Terminal Lugs	1.00
128	200 Asstd.	Cable Clamps	1.00
129	2000 Asstd.	Aluminum Rivets (Solid)	1.00
130	200 Asstd.	Spacers and Bushings	1.00
131	1000 Asstd.	Lock Washers	1.00
132	1500 Asstd.	Flat Washers	1.00
133	300 Asstd.	Nuts	1.00
134	500 Asstd.	Eyelets	1.00
135	100 Asstd.	Motor Brushes	1.00
136	100 Asstd.	Brackets	1.00
137	5 Asstd.	Wafer Switches	1.00
138	3 Asstd.	D.C. Relays	1.00
139	20 Asstd.	Knobs	1.00
140	20 Asstd.	Tube Sockets	1.00
141	12 Asstd.	Jewels and 3 Pilot Lights	1.00
142	100 Asstd.	Terminal Strips & Boards	1.00
143	25 Asstd.	Terminal Strips & Boards	1.00
144	100 Asstd.	Fuse Clips	1.00
145	50 Asstd.	Little Fuses 3AG and 4AG	1.00
146	25 Asstd.	Fuse Holders 3AG & 4AG	1.00
147	20 Asstd.	Shock Mounts	1.00
148	5 Asstd.	Fuse Posts	1.00
149	100 Asstd.	Ceramic Stand-off Insulators	1.00
150	10 Asstd.	Phone Plugs	1.00
151	25 Asstd.	Midjet Tube Shields	1.00
152	50 Asstd.	Tube Clamps & Brackets	1.00
153	15 Asstd.	CO-X Connectors	1.00
154	100 Ft.	Asstd. Vinylite, etc. Tubing	1.00
	3 Ft.	Lengths	1.00

CHECK THESE VALUES!

100 asstd. 1/2, 1, 2 watt resistors\$2.00
100 asstd. mica condensers 3.00
100 asstd. ceramic condensers 2.00
50 asstd. w.w. 5, 10, 20 watt resistors 5.00

I.F. TRANSFORMERS SPECIAL!

1600 KC—455 KC—2.5 Meg —30 Meg—10 MC.....Each \$1.00

Buy RELAYS at Low Cost!

115 VAC SPDT; 24 VDC 2 second timing Relay 75 ohm resistance operating point at 10 volts; plate relay 8000 ohm SPDT. Each\$1.00

25 POUNDS OF RADIO—FM—TELEVISION—ELECTRICAL PARTS

Includes: 1 MOTOR, Chassis, cabinet, relay, condensers, resistors, transformers, coils, sub-assemblies, wire, hardware, etc., etc. WORTH AT LEAST \$50.
25 lbs. for \$5.00
10 pound kit same as above \$3.00
10 pound kit less motor..... \$1.50

All items listed above are subject to prior sale. Terms cash with order F.O.B. Chicago, Ill. Please remit postage charges. Attention Manufacturers: Write us for your requirements.

IRVING JOSEPH

220 S. Halsted St. Chicago 6, Ill.

-In New Jersey...
...it's VARIETY-

Variety's Specials for this Month

Limited quantities for immediate shipment. All guaranteed and will be sent in order received while stock lasts.

ASTATIC PHONO PICKUPS
 Complete with L70 crystal & Hardware **\$1.98**

5-INCH PM SPEAKER
 Complete with mounted transformer for 50L6 or 35L6 tubes.
 10 for \$23.00..... **\$2.49 ea.**

I.F. INPUT & OUTPUT TRANSFORMERS
 10 for **\$5.40**
 59 ea.

PHONO KIT
 (Contains motor, turntable, pickup arm complete) **\$5.95**

PLASTIC KNOBS
 (White, Red, Red Mahogany and Tan.) (In lots of 100, \$4.25.) Slip-on type
 1 1/2 in. with 1/4 in. shaft..... **.05 ea.**

ANTENNA LOOPS
 8x5 1/2 Primary and Secondary (10 for \$3.60) **.39 ea.**

PUNCHED RADIO CHASSIS
 (for 6 or less tubes) 10x3 1/4 x 1 1/2. 10 for \$4.20 **.45 ea.**

VARIABLE CONDENSERS
 2 gang, front section cutplate 162 mmf, rear section 420 mmf—2 trimmers long side rotor shaft extension 3/8" dia. x 3/8" long
 —knurled, 10 for \$12.50 **\$1.45 ea.**

R.C.A. CABINETS
 Beautiful inlaid veneer with grill cloth. Inside measurements 13x11 1/2 x 8 1/2" deep. Speaker baffle for 5" speaker. Rubber feet 3 for \$14.00. **\$4.95 ea.**

GUARANTEED VOLUME CONTROLS
 Less Switch..... 48c 10 for \$4.45
 With Switch..... 59c 10 for 5.45
 500,000, 100,000, 50,000, 25,000 ohms; 1/2 meg, 1 meg, 2 megs.

FEDERAL SELENIUM RECTIFIER
 6 or more..... **.99 ea.**
 Less than 6..... **\$1.09 ea.**

RESISTOR CABINETS
 All wood construction, 6 drawers, 24 compartments
 Complete with 100 assorted 1/2 w and 1 w resistors **\$7.95**

Bargain! Guaranteed!
100 Assorted Bypass Condensers 600V
 Value **\$11.00**
Special \$6.95

50L6 OUTPUT TRANSFORMERS **.53 ea.**
 10 for \$4.95

SUPERIOR Model 670
Super-Meter

A Combination Volt-Ohm Milliammeter plus Capacity Reactance Inductance and Decibel Measurements.

Complete with test leads and instructions **\$28.40**



Write Dept. N-5 for our FLYER. 20% Deposit with order required. Please add sufficient postage. Excess will be refunded.

Variety ELECTRIC CO., Inc.
 601 Broad St., Newark 2, N. J.

International Short-Wave
 (Continued from page 145)

Address is, Emissoras do Aero Clube da Beira, P. O. Box 3, Beira, Mocambique (Portuguese East Africa).

Radio Club News

England—One of the most unique radio clubs in the world is the Anglo-American Radio and Television Society. In an airmail letter from Leslie Orton, founder of the organization, come these details:

"I founded this organization well before the war as my contribution towards promoting international goodwill, about which I feel strongly. There are no charges for joining the club. Members are under no obligation. Club news appears in *Entertainment World* which I personally send freely to all overseas members in order to keep them together. To become a member, one should write to me at my home address—15, Hawthorn Drive, Willowbank, Uxbridge, England. If members desire to be put in touch with members in other parts of the world, this will be done.

"I am founder and Hon. Secretary; Arthur Bird, of World Friendship Society of Radio Amateurs, is Vice-President; other officials include Miss Eileen Harris, in charge of Ladies' Section; C. F. Bachman, American representative; Rex C. Gillett, Australian representative; Leonard Wood, French representative; and so on.

Sweden—Hugo Nordqvist, secretary of the Radio Club of Sweden (SRK), informs me that the club now has about 400 members; club plans for 1947 include the printing of a bulletin, "DX-Radio," each month, contests with overseas radio clubs, a radio course to be given in Stockholm to teach members how to repair small faults and how to read wiring diagrams. Present officers are Birger Lundstrom, president; Uno Forsten, deputy president; Hugo Nordqvist, secretary; Bo Svard, deputy secretary; Bertil Dahlstrom, cashier; Sven-Yngve Carlstedt, master-of-ceremonies; Sven Lindhe, Erik Fredriksson, Thore Bostrom, Sture Eriksson, members of the committee. The secretary may be addressed in care of Sveriges Radioklub, Stockholm 5, Sweden (Sverige).


United States—After an absence of some years, the World Wide Dial Club, Chicago, is again in operation, with meetings to be held once a month in a central location. Officers are Frank Anzalone, chairman; Joseph P. Michaski, vice-chairman; Gerard E. Jansen, secretary; and Joseph Seiler, treasurer. Anyone wishing information regarding the WWDC should contact the secretary, Mr. Jansen, at 2551 W. Monroe Street, Chicago.

This Month's Schedules

Alaska—The station reported several weeks ago on 8.860 as either WXFG or WXE is definitely WXFG,

RPO SPECIAL

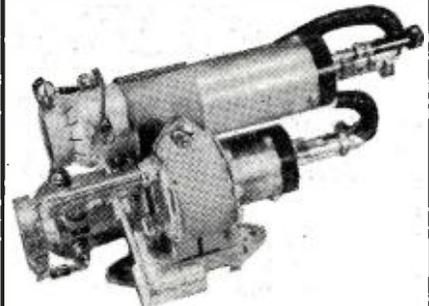12 CM CAVITY OSCILLATOR
 FOR V.H.F. APPLICATION



OVERALL DIM. APPROX. 10x4 1/4 x 1/4

RANGE: 9.5-12.5 CM
TUBES USED: 2C40, 2C43
 (ONLY ONE NECESSARY)

NO COOLING NEEDED IF PLATE CURRENT IS UNDER 20 MA

LESS TUBES & GRID CYLINDER
 With Instructions for Operation .. **\$1.75 Ea.**

2C40 TUBES, \$2.95 Ea.
 100-160 V. plate, Fil. 6.3 volts
 Cash with Order

RADIO PARTS OUTLET, INC.
 4305 LINCOLN AVENUE, CHICAGO 18, ILL.

ATTENTION - at last -
A 25-Watt
High Fidelity Public Address Amplifier



Model PH25 List \$110.00
 Net **\$49.95** inc. tubes

Manufactured by Atomite Electronic & Radio Corp.

IMMEDIATE DELIVERY SPECIFICATIONS

TUBES—2-6SC7, 2-6L6, 1-5U4G.
 CHANNELS (3)—2-Mic High Gain 125DB, 1-Phono 87L/6.
 RESPONSE—40—12000 cycles plus or minus 1DB.
 OUTPUT IMP.—2-4-8-16-500 ohms at both "Speaker Terminals." Strip or sockets. Handles 2 microphones.
 OUTPUT POWER—25 Watts 3% dist. 35 Watts peak. Hum level 57DB below output.
 DUTY—Continuous—PROTECTION—Fused 2 amp. slow blow.
 CASE—Steel two-tone black and silver crackle. Blue panel White letters.
 CAPACITORS—Oil coupling condensers & hermetically sealed electrolytic filter condensers.
 SOCKETS—Output and rectifier sockets seatite.
 DIMENSIONS—8 1/2 x 10 x 14 1/2 inches.
 POWER INPUT—110-125 Volts 60 cycles.
 Available with Phono Top and Tubes
 List \$145.00—Net \$64.95
 TERMS: 10% Deposit with Order Balance C.O.D.—F.O.B. N. Y.

AERCO SALES CO.
 387 Bushwick Ave. Brooklyn 6, N.Y.

RADIO NEWS

Adak, as per verie received by Paul Kary, Pennsylvania.

Albania—ZAA, Radio Tirana, 7.852, is heard in England with *English* news at 3:15 p.m.; usually fades out around 4 p.m. (Boves-Taylor)

Algiers—Current schedules of "The Voice of the United States of America in North Africa," relaying U.S. international programs, are: Algiers I, 9.610, 1-5:45 p.m. to Western Europe; Algiers III, 6.040, 1-5:45 p.m. to Balkans.

Andorra—Radio Andorra, about 5.985, has a program of British music, 4-4:30 p.m.; asks that reports be sent *direct* to Andorra. (Pearce) Although sign-off is scheduled at 8 p.m., was heard recently in Maine signing off at 6:55 p.m. with slogan, "Vive Andorra!"

Angola—Radio Clube de Angola, CR6RC, 9.470, Louanda, heard in England to closedown at 3:45 p.m.; some QRM from TAP, 9.465, Ankara; *no English*. (Pearce)

Arabia—K. G. Frick, Sweden, reports ZNR, 6.765, Aden, heard at 10 a.m.

Argentina—Widely heard throughout the U.S. these days is LPS6, listed on 14.850 but operating on 14.851, Ushuaia, Territory of Tierra del Fuego, heard around 6:45 p.m.; program consists of march, news in Spanish, march sign-off. Appears to be on only weekdays. Also reported used for point-to-point contact work.

Australia—Radio Australia has announced that VLA8, 11.76, has replaced VLA4, 15.32, in the West Coast daily beam, 11:45 p.m.-12:45 a.m.

VLG6, 15.24 (announced, formerly was 15.23), Melbourne, has replaced VLG7, 15.16, to West Coast, 11:45 p.m.-12:45 a.m. The same applies for the beam to New Caledonia, 2:30-3:45 a.m. (Balbi)

ABC National Program is heard in England from 3 to close at 5 p.m. over VLG7, 15.16; at 3 p.m. announces that VLH4, 11.88, and VLR2, 6.15, are in parallel; Saturday sign-off is 5:15 p.m. (Pearce)

VLQ3, 9.66, Brisbane, is again being heard mornings, good signal in West. (Dilg) Weak to fair here in East; probably runs to 9 a.m. Frick, Sweden, reports good signal there at 3 p.m. with *English* news.

Austria—Radio Wien, 12.212, Vienna, logged with good signal but sporadic CWQRM, coming on at 11:45 p.m.; news in German at 12 midnight and 12:45 a.m.; *English* lesson at 12:35 a.m. (by woman). (Kary) The 7.180 frequency is heard in England with strong signal at 2:05 a.m.; *no English*. (Pearce) Heard in Sweden on 11.790 around 1:30 p.m. and with news in German at 2 p.m. (Frick)

Radio Vorarlberg, 6.005, is heard in New York around 1 a.m. (Legge) Also reported heard there 1-1:45 a.m. with good signal. (Ballard)

Azores—Ponta Delgada moved from 4.040 to 4.845; heard, 5-7 p.m. (URDXC) Has "wonderful" signal in District of Columbia. (Howe) Fine

May, 1947

"556" BROADCAST
"55" UNIDYNE

SHURE

MICROPHONES

now made with...

MULTI-IMPEDANCE SWITCH*



- 1 Can be used with amplifiers of any input impedance.
- 2 Insures having the "right" microphone for all types of installations.
- 3 Decreases your stock inventory.
- 4 Switch Lock is tamper-proof. Hidden from view, yet easy to adjust.

*IMPEDANCE TABLE

L—35-50 ohms
M—150-250 ohms
H—High Impedance

SHURE BROTHERS, Inc.

Microphones and Acoustic Devices
225 West Huron Street, Chicago 10, Illinois
Cable Address: SHUREMICRO

SHURE

HEXACON ELECTRIC SOLDERING IRONS

..tagged for
the big jobs!

TYPE P-150
(illustrated)



Follow the leaders—and use HEXACON! For rugged, heavy duty work or for light intricate work . . . here's the answer. One reason is "Balanced Heat"—dissipating excessive element-impairing heat—and minimizing element burn-outs and tip replacements. Another is their lightweight. Literature is available describing the complete HEXACON line of screw tip and plug tip irons from 40 to 700 watts, and with tip diameters ranging from 1/4" to 1 1/4".

HEXACON ELECTRIC CO.
119 W. Clay Ave., Roselle Park, N. J.

HIGH-QUALITY, LONG-LASTING SOLDERING IRONS

HEXACON

CALLING ALL HAMS!
to SCENIC!



First To Feature The New SUPREME AF-100 AMATEUR TRANSMITTER

100 WATTS OUTPUT
AM—FM—CW—ICW

- 6 BANDS—10, 11, 15, 20, 40, 80 meters.
- Highly stable variable frequency oscillator.
- Designed for CONTINUOUS COMMERCIAL SERVICE for AMATEUR USE.
- SIMPLE TO OPERATE! Band changing is easily accomplished in the exciter by a band selector switch, and in the final by a plug-in coil.
- Incorporates the new Frequency Modulation bands—27.185-27.455, 29-29.7 megacycles.
- THIS TRANSMITTER CAN NEVER BECOME OBSOLETE!

For operation on 110-117 volts 50/60 cycles A.C.
Size: 20 1/2 x 11 3/4 x 18 1/2". Wt. 145 lbs. Shpg. wt. 195 lbs.
AMATEUR NET PRICE—\$450.00
Complete Descriptive Literature Sent on Request.

WE SHIP ALL OVER THE WORLD!

25% deposit required with domestic mail orders, balance C.O.D. Foreign orders require full remittance. No Charge for export packing.

We also Stock TEST INSTRUMENTS,
AMPLIFIERS, SPEAKERS, TUBES, etc.

**SCENIC RADIO
AND ELECTRONICS CO.**
53 PARK PLACE • Dept. B • NEW YORK 7, N. Y.

Amsco

MAY SPECIALS

KLYSTRON Osc. Tube 2K25/723AB operates on 3 cm.	\$5.75
PARABOLIC REFLECTORS—15" spun alum. Alzak fin. for 1200 Mc. up. Ea.	2.19
Pr.	3.95
MICRO AMMETER—Beede O-200.....	3.29
METER RECTIFIERS—	
Full Wave95
Half Wave65
VIBRATOR—Syn. 2 Volt 7 prong for G.E. Portables, etc.	1.69
MICROPHONE—T-24 Carbon with Push Switch and Cable.....	1.39
MIKE BUTTONS—1" Carbon contact type T-30.....	1.19
FILTER CHOKES—20 hy. 300 Ma. 2 for	3.95
PLATE TRANSFORMER—Pri. 110 V. 60 cy. Sec. 1500 V.C.T. 250 Ma.	6.95
AIR TRIMMERS—12 assorted.....	1.19
RESISTORS—1/2 and 1 Watt 500 assorted	7.95
MICA CONDENSERS—25 assorted.....	.95
KNOBS—25 assorted	1.95
CAPACITOR Dry Electro. 40-40-150 volt 6 for	1.95

Write for Circular Featuring Radio
Components at Bargain Prices

AMERICAN SALES COMPANY
1811 West 47th Street
CHICAGO, ILLINOIS

signal in England; no English. (Pearce)
Bechuanaland—ZNB, 5.900, Mafeking, heard very weak in Pennsylvania at 6:35 a.m. with music and occasional announcements by man. (Kary)
Belgian Congo—Leopoldville's revised schedules for OTC2, 9.745 (announced), are to British Empire, 10:30 a.m.-12 noon; to Britain, 3:30-4:45 p.m.; and to North America, 9-11 p.m. In latter beam, English news is at 9 p.m., with headline news around 10:45 p.m. (Balbi) Widely heard with good signals throughout United States.

Belgium—Brussels is reported on 9.479, 3:05-4:30 p.m. (URDXC) Heard on 11.89 in Australia at 3:15 p.m. with news in Flemish and music. (Sander-son) Pearson, England, lists this one as ORY3, with schedule of 6-7 a.m., 11 a.m.-12 noon, and 12:25-6 p.m.

British Honduras—In verification just received, it was stated that ZIK-2, Belize, is the Government Radio Station, 10.600, 200 watts. (Kary) Schedule appears to be daily with English news program, 1:30 or 1:35 to 1:45 p.m. (Arthur, McLaughlin)

Brazil—PRA8, 6.016, Recife, identifies with four-note chime. (URDXC) PRL8, 11.72, Rio de Janeiro, was heard recently testing around 9:20 p.m., for the Canadian Broadcasting Corporation (English and Portuguese); good signal. Regular sign-off of PRL7, 9.720, is 9:30 p.m. (Howe) PSL, 7.930, Rio de Janeiro, heard in Pennsylvania recently signing off at 6 p.m. (Kary)

Bulgaria—Radio Sofia, 9.350 and 7.670, according to letter verie, is scheduled 11 p.m.-1 a.m., 5:30-7 a.m., 11 a.m.-1:30 p.m., and 2-3:40 p.m.; has English news at 3:30 p.m. (Pearce)

Canada—CKNC, 17.82, has replaced CKCS, 15.32, to Latin America, 6:20-7:35 p.m. (Balbi) This beam runs to 9:05 p.m. Sundays; CKRA, 11:76, parallels.

Cape Verde Islands—K. G. Frick, Sweden, reports Praia on 6.400, 3:30-5 p.m. with 0.03 kw.

Ceylon—Latest official schedules list Radio SEAC, Colombo, on 15.12, 9.52, and 3.395, 7:30 p.m.-12 noon, for the "main program" in English; 6.075 parallels between 7:30-11 p.m., 11:30 p.m.-5 a.m., 7 a.m.-12 noon; 17.77 parallels irregularly, 11:30 p.m.-5 a.m. Indian Forces programs on 17.77 and 6.075 run 11-11:30 p.m., 5-7 a.m.

Sunday beam to Britain, 1:30-3:30 p.m., is carried on 15.12 and 7.185. (Adey) Widely heard with fine level.

ZOH, 4.900, Colombo, is heard in England with "Epilogue" at 11:45 a.m. just before closedown; has orchestral program of recordings, ending at 11 a.m., and from 11:45 a.m. re-lays BBC; this is for Sundays; other days has dance music from 11:15 a.m. to closedown around 12 noon; very bad CWQRM. (Pearce)

Chile—CE960, Santiago, moved to 9.585 from 9.600; signs off at 12 midnight. (URDXC) This is probably one of the stations that interferes with PCJ, 9.59, Hilversum, Holland.

RADIO NEWS

China—XGOA, Nanking, now uses 9.73, 4-11 a.m. sign-off. (Balbi) Is widely heard, some days with fine signal in East around 7-8:30 a.m.; relays XGOY's *English* news at 9 a.m. The widely reported "new" Chinese outlet on about 11.835 has been definitely identified also as XGOA, Nanking; usually parallels the 9.73 outlet; has fair to good signals in East. (Kary) Announces also several medium-wave calls, probably those of relay stations. Among calls heard are XGRX, XTRA. (Harts, Kary)

XTPA, 11.65, Canton, still carries XGOY *English* news at 9 a.m.; some days is very poor signal. (Kernan, Harts) Good signal in Michigan. (Flanagan)

XORA, 11.698, Shanghai, heard with good signal at 7:30 a.m. in Pennsylvania. (Kary) Heard in Ontario at 8:40 a.m. announcing "end of *English* period," good level. (Harts)

XGOUS, 7.55, Nanking, is now heard 9-9:50 a.m., some days later, with press news to U.S. (Balbi) Some days opens around 8:45 a.m. with music. (Dilg)

XMTA, 12.215, believed Shanghai, has been heard with weak signal in East early mornings; call announced often but location was not heard. (Kary) Heard in Australia at 7 a.m. with western type music and news in Chinese. (Sanderson) Heard in New Zealand as early as 5:30 a.m. (Gray)

A new Chinese station is reported as XRAY, 8.89, Peiping, relaying AFRS programs from around 5:30 a.m. While reports indicate location of Peiping, projected location was Peh-taiho. (Radio Australia) Heard at 5 a.m. in New Zealand, with severe CWQRM, announcing as "AFRS in Peiping." (Gray)

An unidentified Chinese is heard to around 8 a.m. on about 6.04. Heard 4:30 to about 8 a.m. (Baxter) May be XGSA, Nanking.

West Coast DXers report a new Chinese station on about 7.100, mornings; call appears to be XGAF; sometimes alternates western and oriental musical numbers. (Dilg) Probably opens at 5 a.m.; signs off at 9:30 a.m. (Baxter)

XLRA, Hankow, has recently been using about 11.490 to parallel its 6.055 outlet. (Dilg, Baxter)

A much-improved signal is noted from XPSA, 7.010, Kweiyang; lately appears to *not* take XGOY *English* news relay at 9 a.m. (Dilg)

Recently the *English* news at 7 a.m. from XGOY, 6.143, has been QRM'd badly in East by a Latin American transmitter, probably HJDE. (Beck)

XOPD, Hangchow, has moved up to about 9.775 from 9.555; heard signing off at 8 a.m. (Dilg)

XGOE, 9.820, Kweilin (?), was heard again recently on West Coast, early mornings, very weak. (Dilg) Sometimes heard in Australia at 6 a.m. with news in *English*. (Gillett)

XMAG is call of a new AFRS station.
May, 1947

Whether SOUND RECORDER or SEMI-TRAILER

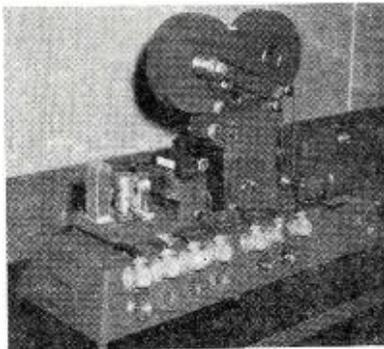


Photo Courtesy Reeves Sound Studios,
New York City.

SOUND RECORDER—Reeves "Sixteen" 16-mm Sound Recorder with cover removed, carries a double row of Type "P" Plugs and Receptacles.

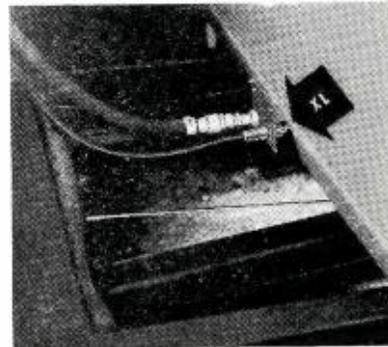


Photo Courtesy Mustang Trailer Co.,
Houston, Texas

SEMI-TRAILER—Hookup between truck and semi-trailer. Top fitting is for air line, lower, Cannon Electric Type XL Plug and Receptacle.

Plug-in with CANNON PLUGS



P-14 Receptacle
(List from \$2.50
to \$2.75)



P-CG-15 Plug
(List from \$5.20
to \$6.40)



XL-3-14 Receptacle
(List \$1.00)



XL-3-11 Plug
(List \$1.25)

TYPE "P"—Made in a variety of shells, Type "P" Series comprises six insert arrangements with 2, 3, 4, 5 and 6 30-amp. contacts for No. 10 B&S stranded wire, and one eight 15-amp. insert for No. 14 B&S stranded wire.

TYPE "XL"—This new series of small general utility connectors is available in one insert of three 15-amp. contacts for No. 14 B&S stranded wire. Originally designed for sound—photo pictures its use on trucks and trailers.

TYPES "P" AND "XL" ARE AVAILABLE DIRECT FROM MORE THAN 125 CANNON ELECTRIC DISTRIBUTORS LOCATED IN ALL PARTS OF THE U. S. A.



NEW EDITION C-46-A CATALOG—For a complete survey of the majority of Cannon Electric products, send for this C-46-A Catalog, containing prices on many items. Also included are the names and addresses of distributors where Types P, O, X, XK, XL and TQ may be purchased directly from stock. Write Department E-228.



CANNON ELECTRIC DEVELOPMENT COMPANY

3209 Humboldt Street, Los Angeles 31, California

Canada & British Empire—Cannon Electric Co., Ltd., Toronto, Ontario • World Export
Agents (excepting British Empire) Frazer & Hansen, 301 Clay St., San Francisco 11, Calif.



TELEVISION KIT...A HIGH QUALITY TELEVISION RECEIVER

ready for Easy, Rapid Assembly

ENGINEERED BY TELEVISION SPECIALISTS



Easy-to-Assemble: No knowledge of television required. COMPLETE easy-to-follow INSTRUCTION SHEET gives you all the knowledge you need.

This Kit INCLUDES SOUND, all component parts, and the following:—

1. Specially designed Television Antenna.
2. A \$30.00 Lectrovision seven-inch Picture Tube . . . plus ALL other tubes.
3. Pre-tuned R-F unit.
4. Finished front panel.
5. All solder, wire, and 60 feet of low loss lead-in cable.

Operates on 110V.; 50-60 cycles A.C.
 Price: complete with ALL tubes, \$159.50. Shipment will be made approximately 2 weeks after receipt of order. \$25.00 deposit required on all orders, balance C.O.D.

Trade Inquiries Invited

We believe that the comparative quality of this set is superior to other available sets. It has been acclaimed by major television schools throughout the country. For full information write to:

TRANSVISION, INC. Dept. R. N.
 385 North Ave. New Rochelle, N. Y.

Enclosed find \$.....deposit. Please ship.....Transvision Television Kits C.O.D. to

Name

Address

City & State.....

tion in Nanking; uses frequency of 4.275 to 11 a.m. sign-off; a further frequency of 7.340 is used irregularly to 11 a.m.; some days seems to have separate program. (Dilg, Baxter)

Colombia—HJCAB, 9.690, Bogota, appears to be off the air. (Howe)

Egypt—The station reported on 20.135 some time ago is SUP, Cairo; reports to NBC and CBS around 8:15 a.m., from correspondents in Cairo and Jerusalem, presumably by landline from latter; excellent signals. (Kary)

El Salvador—YSR, San Salvador, moved from 6.277 to 6.270. (URDXC) In verifying for Paul Kary, Pennsylvania, YSO gave "old" frequency of 7.270, but is actually heard on 7.315.

England—Changes in North American Service include GRP, 18.13, 9:15-10:15 a.m., 1:30-4:15 p.m.; GSJ, 21.53, 10-11:15 a.m., 11:30 a.m.-1:45 p.m.; GSP, 15.31, 4:15-7 p.m.; GWH, 11.80, 4:15-9:45 p.m.; and GRH, 9.825, 7-11 p.m. (Balbi)

H.M.S. Vanguard was heard from Plymouth at commencement of the recent Royal Tour to South Africa, on a frequency of about 7.800, working BBS station on about 8.615, with BBC pick-ups; this is reported to be one of the most powerful transmitters ever installed aboard ship. (Harrison) Was heard in Ontario on a frequency of 13.990 at 5:30 p.m. on the day it crossed the Equator; had clear signal. (Bromley)


Ethiopia—In a letter just received from W. H. Erholm, Technical Director of Radio Services, Ministry of P.T.T., Addis Ababa, Empire of Ethiopia, it was stated: "Thank you very much for your report on the reception of our station, ETA (or Radio Addis Ababa, Ethiopia), frequency 15.074 in the 19-meter band. Your report was exact and complete. We are using a 7-kw. transmitter with a 'diamond' or rhombic antenna. The station at present is off the air on broadcast, but is on the air daily on c.w., working Mackay Radio in New York direct on the hours of 1 a.m., 1 p.m., and 3 p.m. We expect to be on the air daily soon with a voice transmission in various languages, at which time we will advise you of complete details. Thank you again for the valuable information you gave us, and we hope you and your American friends will be a constant listener when we are on the air permanently." Verification was recently received by Kary, Pennsylvania.

France—Paris now uses 9.550 between 12:40-1 a.m. (URDXC)

Paris is heard on 7.240 afternoons in England, but with QRM from Moscow on same frequency. (Harrison) Is heard to 5:15 p.m. in Australia, clear of VLQ. (Gillett)

The Latin American Service from Paris is now heard on 7.280 (new) in parallel with 9.620; former very good, latter poor. The North American transmission continues on 9.550 and 11.845, 8:55-10:45 p.m. (Howe)

LATEST TELEVISION COMPONENTS

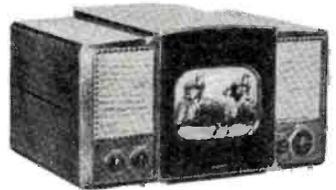

As Used in the New RCA 10" Receiver

	New Prices
50° Deflection Yoke	\$16.25
Focusing Coil	9.13
Ion Trap for 10BP4	6.50
Vertical Output Transformer	9.00
Horizontal Output Transformer with 9000 V. and 1 V. windings for second anode supply.	16.85

Other television parts:

RCA Deflection Yoke for 9" and 12" CR tubes, with special shields for yoke and tube, including brackets	26.75
Rubber Mask, and Frame with Shatterproof glass for 12" CR tubes	5.00
Five band RF Switch and coil assembly	5.60
Cathode Ray Tubes for Television and Oscilloscopes from 1" to 15"	

ALSO

Receiving tubes	Capacitors (Ceramic, oil filled, Mica, etc.)
Sockets for CR tubes	Ceramic trimmers
Sockets with cables	And other television components
Coaxial Cable (72 and 50 ohms)	

Send 50c for complete catalog including diagrams for RCA, GE, DuMont, Stromberg Carlson, Andrea and Viewtone Television Receivers.

World's First Specialized House in Television
TELETRONICS SERVICE AND SUPPLY CORP.
 264 West 40th Street New York 18, N. Y.
 phone PENNSYLVANIA 6-8730

TRANSFORMER

Bargains at Greenwich Sales

115 Volt, 60 Cycle primary

T-1 750VCT @ 100 MA; 6.3V @ 2 amp; 5V @ 3 amp	\$2.50
T-2 1080V @ 15 mils	2.25
T-3 375-0-375V @ 275 mils	3.90
T-4 1020 VCT @ 106 mils; 2.5V @ 5 amp; 6.3V @ 4 amp	3.25
T-5 390-0-390 @ 400 mils	3.25
T-6 5V @ 10 amp; high insulation with 50 watt socket mounted on transformer	1.75

TRANSMITTING TUBES

866 A	\$0.85	805	\$4.00
801	1.75	811	1.95
	813		\$6.25

Brand New, guaranteed. Other tubes in stock. 25% deposit required on all C.O.D. orders. Prompt delivery assured. Write Dept. RNM.

GREENWICH SALES CO.

59 Cortlandt St. Whitehall 3-3052
 NEW YORK CITY 7, N. Y.

RECORDS

LATEST & HARD-TO-GET BACK NUMBERS

Some slightly used and some brand new—Victor, Bluebird, Columbia, Okeh, Decca, Capitol, etc. Such artists as Glenn Miller, Benny Goodman, Harry James, Bing Crosby, Frank Sinatra, Gene Autry, Duke Ellington, Fats Waller, Guy Lombardo, Andrews Sisters, Kate Smith, Ink Spots, Mills Bros., etc.

BIG PROFITS Your opportunity to cash in on this new field that is sweeping the country. Specify the type of music that sells best in your territory such as Swing, Sweet Music, Cow-boy, Hill-billy, Polkas, Blues, etc. Your price \$13.90 per 100 records, f.o.b. Chicago, 2% off for cash with order. All shipments made within 48 hours.

CHAS. HOODWIN CO.
 4419 Broadway, Y15, Chicago 40, Illinois
 World's Largest Dealers in Used Records

Paris is heard daily on 9.560, 2:30-3:30 p.m., with programs in *English*, directed to England. (Laubscher, Pearce)

French Equatorial Africa—Radio Australia recently reported in a DX session that Brazzaville has been assigned a new frequency of 17.84 with 50 kw. power.

On West Coast, 17.53 is excellent some nights, as are 11.97 and 9.44 in parallel; *English* news at 12:30 a.m. (Balbi)

European sources list Brazzaville on 7.000, and Rex Gillett, Australia, airmails me that this frequency is heard in Australia at 3:45 p.m. with *English* news, paralleling other frequencies.

French Guiana—For those who are anxious to log this country, it is reported that Rochambeau Airways, Cayenne, operate irregularly on the 4.220 frequency; schedule is not known; has anyone heard this one?

French Indo-China—Radio Saigon has moved to 6.19 from 4.81; signs off at 10:15 a.m.; signal is much better than when on 4.81, but suffers QRM from AIR, Delhi, on occasion; 11.78 parallels. (Balbi, Dilg, Baxter) *English* news is scheduled for 5, 9 a.m. The 11.78 frequency is still heard fair in the East around 6:15-7 p.m., full schedule is 6-8 p.m., but suffers bad QRM from U.S. stations on 11.79 during most of the period; French news at 6:30, *English* news at 7:45 p.m.

Pnompenh, 12.36, heard in Australia at 7:30 a.m. with news in French and music. (Sanderson) May carry *English* news around 7:45 a.m.

Hanoi, 7.25, was heard recently in Australia at 6 a.m. with *English* news. (Sanderson)

French Morocco—According to verie received by Moss, Ontario, Radio Maroc, Rabat, operates on 9.082 from 1:55 a.m. to 4 a.m. and 12 noon-7:15 p.m.; and on 16.666, 7-10 a.m.; call is CNR3; it was stated that "the antenna-power is about 2½ kw."

Finland—OIX-4, 15.190, Peri, is heard quite well signing on around 7:15 to 7:25 p.m., usually with 10-note chime; *English* news comprises entire program; usually leaves the air around 7:33 p.m.; these times vary from day to day; announces OIX-2, 9.500, in parallel, but this outlet is inaudible. (Kary)

Formosa—XUPA, 9.695, Tai-Pei, has moved to about 7.220; relays XGOY's *English* news from Chungking at 9 a.m. (Dilg)

Germany—Official schedules received from Sudwestfunk, Baden-Baden, French Zone, list the station on 6.321, 12 midnight-6 p.m. (may have short breaks). Relays medium-wave stations located at Freiburg, Sigmaringen, Koblenz, Kaiserslautern, Saarbrücken. Although German is the principal language used, some French programs are relayed from Paris. (Kary)

Official schedules of Munich I, 7.290, are 11 a.m.-4:30 p.m. to Balkans; Munich II, 6.170, 11 a.m.-1 p.m. to Balkans; 1-2 p.m. to U.S.S.R., 2-4:30

May, 1947

Bob Henry calling

CQ QUICK DELIVERY

Models Listed Are in Stock . . .
for Immediate Shipment:

Hallcrafters S38\$ 47.50
Hallcrafters S40A 89.50
Hallcrafters SX42 275.00
Hallcrafters SP44 99.50
Hallcrafters HT9 289.50
Hammarlund HQ129X 161.40
Hammarlund SPC400X 334.05
National NC240DT & NC240DR 225.00
National HR05TA1 & HR05RA1 274.35
National NC46 97.50
National NC176 about 190.00
National NC173 179.50
RME84 98.70
RME45 198.70
RME VHF152 86.60
RME LF90 29.70
Pierson KP-81 367.65
Gon-Set converters 39.95
Collins 30K-1 1250.00
Collins 75A-1 (soon) 375.00
Collins 32V-1 (soon) 475.00
Collins 70E-8 (soon) 40.00
Meissner Signal Shifter 120.00
Bud ECO 52.50
Temco 75GA 495.00
Temco 500GA 1800.00
Supreme AF-100 450.00
Harvey 100T 583.00
Millen 90700ECO 42.50
Millen 90800 exciter 57.50
Millen 90281 power supply 84.50
Millen 90881 500 watt RF unit 89.50
Millen 90902 scope 42.50
Sonar XE-10 39.45
Sonar VFX-680 87.45
Gordon rotary beam 225.00
Direct-O-Beam 117.00
Premax 28MC beam kit 29.40
Work Shop 28MC beam kit 39.50
Ranger 905 Trans-Meter 49.50


In Bob Henry's code of doing business "CQ" means complete stocks, quick delivery. Bob Henry offers the finest, fastest service in the land to all amateurs plus personalized, individual attention to all orders by an amateur who knows what amateurs want. He says:

"The delivery situation is now good. I can ship immediately nearly all items. For fastest service send five dollars and I will ship COD at once at wholesale prices. Or order on my easy time payment plan. I finance the terms myself to give you better service and save you money. Trade-ins welcome. Tell me what you have to trade and we can make a deal. Attached is only partial listing of my complete stocks. I have almost everything an amateur wants. Good bargains in war surplus. Send to me for anything. Orders and inquiries handled with speed and efficiency. Write, phone, wire or visit either of my stores now.

Bob Henry
WØARA

BUTLER, MISSOURI HENRY RADIO STORES Los Angeles 25, Calif.

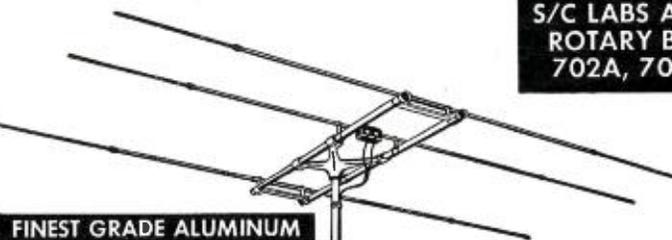"WORLD'S LARGEST DISTRIBUTORS OF SHORT WAVE RECEIVERS"



FINEST GRADE ALUMINUM

Type 702A 27 mc to 29.7 mc (10 and 11 meter band) . . \$44.95
 Type 702B 50 mc to 54 mc (6 meter band) 29.95
 Type 702C 144 mc to 148 mc (2 meter band) 24.50
 Complete with Adjustable "T" Match @ \$6.75 extra.

S/C Labs Three Element Beam Designed for 2, 6 and 10 Meter Band. Weight Less than 15 Lbs.

Also in stock a complete line of FM and television antennae. See your local dealer or write for circular.

S/C LABS ADJUSTABLE ROTARY BEAM KITS 702A, 702B, 702C,

PRECISION AND ADJUSTABLE ANTENNA


Type 701A (28-44 mc) 10 meter amateur \$6.50
 Type 701B (44-88 mc) Television 5 meter amateur. 5.85
 Type 701C (88-148 mc) FM 2 meter amateur 5.75

S/C LABORATORIES, INC., DEPT. R, 20 VAN WAGENEN ST., NEWARK 4, N. J.

NUMBERS 2 and 3 OF THE

WALSCO Hit Parade

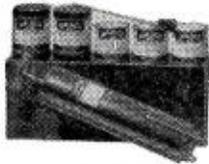IT'S HERE THE NEW, COLORFUL EASY TO APPLY



**FELT
FLOCK
FINISH**

COMPLETE FELT FLOCK SPRAY OUTFIT

Now you can do your own finishing of: Radio cabinets and speaker grilles, phonograph turntables and record cases, novelties, crafts, hobbies and numerous other items

10 brilliant colors available. The kit (as pictured) contains patented WALSCO Felt Flock Spray Gun, together with necessary materials, such as undercoats, ivory and brown felt flocks, brush, instructions, etc.,

CATALOG NO. K-50—List Price \$10.75

Write for full information on these items. Dept. 5A


WALSCO products
Help The Radio Man
WALTER L. SCHOTT CO. BEVERLY HILLS, CALIF. CHICAGO 5, ILL.

WALSCO STAPLE DRIVER

- Pays for itself on the first job
- A sensational tool for installing wires and cables, that saves time and money.
- Used by Radio, Public address and Intercom Technicians.
- Staples into corners and other inaccessible places.
- Staples on hard surfaces such as plaster, hardwood, etc.
- Can be loaded in 10 seconds.



The WalSCO Staple Driver is a real time and trouble saving tool for the radioman. Also extremely useful for general stapling. This device automatically positions the staple after which it is driven to a pre-adjusted depth with one or two strokes of the palm of the hand. A small trigger controls the feeding mechanism. Wires and cables up to 1/4" in diameter can be quickly installed with the WalSCO Staple driver. Price \$4.95 Dealers Net (including box of staples)

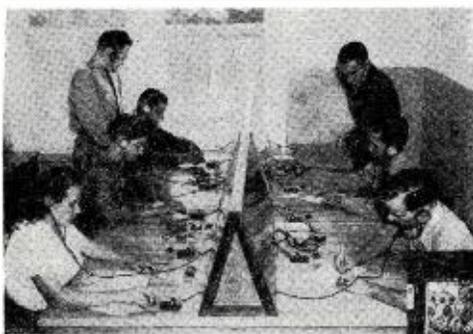

Train for YOUR important Career Job in Beautiful, Cosmopolitan MIAMI

More and more young men and women are preparing to meet the challenge of modern industry with modern training at Embry-Riddle School of Aviation. Years of experience at this U. S. Government approved school have effected the development of a

full year Radio Course that is designed to qualify you for an important position in the Radio industry. A limited number of both civilians and veterans can be accepted for the next class. For complete information fill out the attached Coupon and mail today.



Dean of Enrollments—Dept. 16
Embry-Riddle School of Aviation
Miami 30, Florida

Name.....
Address.....
City..... State.....
Check One Veteran Civilian



MODEL A-2 WITH ADDED SENSITIVITY
For numerous control applications such as burglar alarms, industrial safety controls, automatic counters, or in conjunction with a chime or bell to announce entrance of persons in stores and offices. For A.C. Complete with tubes and built-in SPDT relay. \$11.95
LIGHT SOURCE—Will operate up to 25 feet with above unit. \$5.95
Write to Dept. EN

ADSON RADIO CO.
221 FULTON ST., NEW YORK 7, N. Y.

SERVICE MEN!

- RCA Radiotron
 - Tungsol
 - Tubes, Parts & Equipment
 - Sylvania
 - Raytheon
- Write for our latest Bulletin, Dept. N4

New Astatic CT-J Nylon \$5.24 each.

Distributors of RADIO EQUIPMENT

CHIEF ELECTRONICS

104 MAIN STREET, POUGHKEEPSIE, N. Y.

ELECTRICAL TRAINING

Intensive 82 weeks' residence course in fundamentals of industrial electrical engineering. Including radio, electronics. Prepares for technician, engineering aides. Approved for veteran training. 54th year. Catalog.

BLISS ELECTRICAL SCHOOL
7698 Takoma Ave.
Washington 12, D. C.

p.m. to Balkans; Munich IV, 9.540, same as Munich II. These stations relay U.S. international programs.

"Mitteldeutscher Rundfunk," 9.73, Leipzig, has excellent signals in England, heard before 3:15 a.m. and 5 a.m.-6:30 p.m., no English. (Pearce)

Gold Coast—ZOY, 4.915, Accra, heard in England at 12:45 p.m. with local news; says "Goodnight" and plays few bars of "God Save the King" at 1 p.m. sign-off; heard weekdays; may be off Sundays; has bad CWQRM. (Pearce)

Guadeloupe—Radio Guadeloupe has moved back to 7.445 from 5.986, 11:30 a.m.-1:15 p.m., 6-7:30 p.m. (URDXC)

Guatemala—TGLB, 6.095, Mazatenago, is a new station reported by URDXC, announcing as "Voz de Mazatenago"; heard, 7-10 p.m., relays TGLA.

Hawaii—Relaying U.S. international programs, KRHO, Honolulu, is scheduled 2:45-3:45 a.m. to China (except Monday), 4-11 a.m. to Japan and China, on 9.65; 5-8:15 p.m. to Philippines and Netherlands East Indies, and 8:30 p.m.-1 a.m. to Japan and China, on 17.80.

Holland—Berne list gives calls for Holland stations as PGD, 6.02; PCJ1, 9.59; PHI, 11.730; PCJ2, 15.220; and PHI, 17.776. (URDXC) Due to recent coal shortage, services were curtailed.

Hong Kong—Hong Kong has reverted to standard time—13 hours ahead of EST. (Radio Australia)

ZBW-3 has moved to 9.515, probably to escape QRM from Perth's VLW7, 9.52; heard to 10 a.m. sign-off. (Dilg) Relays BBC news at 6, 8 a.m. Appears to use Chinese to 8 a.m. An airmail report from Rex Gillett, Australia, confirms move to 9.515, "to get away from Perth"; English program heard before 6 a.m. BBC news and after it; also has English program after the 8 a.m. BBC news; medium-wave calls are ZBW, 845 kcs., and ZEK, 640 kcs.

India—VUD2, 3.495, scheduled 8:15 a.m.-12:30 p.m.; VUD11, 4.860, 12 noon-12:40 p.m. (Pearce) "You are listening to Bombay" identifies VUB-2, 3.365, at 12 noon during English program; scheduled closing time is 12:30 p.m. (Gillett)

Iceland—TFJ, 12.235, Reykjavik, scheduled 9-9:30 a.m. on Sunday only, has not been reported lately; may be off the air. Has been heard on c.w., however, with very strong signal in Pennsylvania at 3:25 p.m. (Kary)

Iran—Radio Teheran reported on 11.615 with English news at 6:30 a.m. (URDXC) EPB, 15.100, has good signal in Britain; English news at 6:30 a.m., followed at 6:45 a.m. with news in French. (Pearce)

Iraq—YI5KG, 7.085, Baghdad, is scheduled 9 a.m.-2 p.m. (ISWC) Heard with programs in Arabic to closedown at 2 p.m.; bad QRM. (Pearce) HNU, 6.13, reported heard in England, 8-10 a.m. (ISWC)

Italy—Reported by Per Friis, Denmark, is an AES station in Rome on 6.060, heard 4-4:30 p.m.

Radio Italiana, 11.81 and 9.63, has

an evening program from 6:10-7:20 p.m.; announces in *English* at 6:11 and 7 p.m., and carries *English* news at 7-7:15 p.m., with music to closedown. (Casey) Also scheduled with *English* news for 1.50 p.m.

Jamaica—VRR-4, 11.595 (announced), Stony Hill, is used for special relays; heard with extremely good signals some weeks ago with ZQI's coverage of soccer games at Savannah Parks; verifies. (Kary) Has been heard with good level in South Africa around 5:10 p.m.; asked for reception reports to Cable & Wireless, Ltd., Stony Hill, Jamaica, B.W.I. (Laub-scher)

According to verie received, ZQI, Kingston, operates with 1200 watts, 4-5:30 p.m. on 4.70, and 7:30-10 p.m. on 2.33. (Arthur)

Japan—WLKS, "The Voice of the British Commonwealth Occupation Forces" in Japan, operating on a short-wave frequency of 6.105, is scheduled 4:30-6:30 p.m. and 9 p.m.-4 a.m. (Radio Australia) Is heard in Ohio between 3-4 a.m. (Sutton) Now runs to 5 a.m. (Balbi) Takes relays from Australia and Singapore; on 2.465, appears to run to 8:30 a.m. except Saturdays when continues to 9 a.m. (Dilg) Probably begins at 3 a.m.

WVTR, 9.605, Tokyo, carries AFRS program at 4:50 p.m.; has *English* news at 5 p.m.; bad CWQRM in Pennsylvania. (Kary)

The AFRS station in Tokyo on 6.015 (listed as JLR) was recently heard in New Orleans to announce as JKD; gave the 4.860 outlet as JKE; JLW, 7.825, is also heard mornings in New Orleans. (Crandall)

Java—PMA, 19.350, Batavia, is reported heard in England at 8:30 a.m. with news in Dutch, and at 8:45 a.m. with recordings. (Short Wave News) Heard signing off at 8:58 a.m., some days as late as 9:05 a.m., after *English* dance recordings. (Pearce)

An Indonesian heard on 9.41 from around 5 to 10:30 a.m., except Monday, probably is PLV. (Balbi) Has been heard on West Coast signing off at late as 11 a.m. after playing Ted Lewis' "Good Night Song." (Dilg)

English transmissions of "The Voice of Free Indonesia," 11.000, are officially scheduled for 4-4:30 a.m., 5:30-7:30 a.m., 9-9:30 a.m., and 11-11:30 a.m. (Bachman) Usually signs off with playing of "It's Time to Say Goodnight," and clock chimes for 12 midnight (Indonesian time). (Pearce)

Kenya—VQ7LO, 4.950, Nairobi, heard in England with *English* news at 1 p.m., followed by weather forecast and announcements; announces, "This is Nairobi calling"; signal varies daily from S-3 to S-9. (Harrison) Schedule is 5-6 a.m., 11 a.m.-2 p.m. daily, Sundays has last transmission only; additional, Wednesday and Saturday, 2-3 p.m.; scheduled Tuesdays and Thursdays, 7:30-8:30 a.m., on 6.060. (Levi)

Korea—JODK, 2.510, Seoul, runs to 8:30 a.m. (Dilg)

**your
basic
3R's
for correct
current control**

RELAYS
Ward Leonard

RESISTORS
Ward Leonard

RHEOSTATS
Ward Leonard



RELAYS—provide convenient circuit control, protection, and greater operating efficiency . . . help reduce length of connecting leads. Amateur Relays available from stock: Antenna Change-Over, Antenna Grounding, Keying, Band Switching, RF Break-In, Safety, Overload, Underload, Latch-In, Remote Control, Sensitive, Time Delay. Also Industrial and General-Purpose Relays.

RESISTORS—exclusive features of VITROHM wire-wound resistors insure that *extra* performance needed in critical circuits. Fixed type in 8 stock sizes from 5 to 200 watts. Adjustable type in 7 stock sizes from 10 to 200 watts. Wide range of resistance values. Stripohm, Discohm, and Plaque types also available.

RHEOSTATS—for fixed or variable close control. Protected by tough, acid resistant, crazeless vitreous enamel. Sizes: 25, 50, 100, and 150 watts, in wide range of resistances.

Authorized Distributors Everywhere

WARD LEONARD ELECTRIC COMPANY
Radio and Electronic Distributor Division
53-N West Jackson Blvd., Chicago 4, U. S. A.

WARD LEONARD

RELAYS • RESISTORS • RHEOSTATS

Electric control devices since 1892

SEND FOR
FREE CATALOGS

Write for Amateur Relay Catalog No. D-111, and for Resistor-Rheostat Catalog No. D-2.

U.S.R.S. MONTHLY SPECIAL

CHECK THESE FEATURES
2 OUTPUT CHANNELS • SEPARATE MIKE INPUT, PHONO INPUT AND TONE CONTROL • DUAL OUTPUT SERIES MIXER • LOW DISTORTION

U.S.R.S.

U. S. RADIO SUPPLY
5116 HARPER AVENUE
CHICAGO 15, ILLINOIS
DEPT. NE 5

15 WATT AMPLIFIER



This 15 watt amplifier of special design will cover thousands of people with power to spare. Compact in size, it will outperform many offered at double the price. 5 tubes. 1-6SJ7 input amplifier, 1-6SL7 mixer, 1-5Y3 rectifier, 2-6V6 beam power outputs. Complete with cover less tubes.

Tube kit for above amplifier.
Net \$4.59

60-000 AMPLIFIER—List, \$42.30; Net, **\$25.38**

Write for FREE Buying Guide



COIL KIT

**100 RADIO FREQUENCY COILS ALL NEW!
ALL USABLE! TREMENDOUS VARIETY!
Thousands of Applications in Each Kit**

Frequency ranges from 2 meters to 25 kilocycles. Both iron core types and air types included. Many units have mica condensers which can be salvaged for other purposes.

- CHOKES ● WAVE TRAPS
- ANTENNA COILS
- OSCILLATOR COILS
- R.F. COILS ● TANK COILS
- I.F. TRANSFORMERS

and many other types in kit

With proper trimmers and associated parts every coil can be used. These KITS are perfect for amateurs, experimenters, servicemen, schools, laboratories, etc.

Priced at **\$2.98**

If these coils were to be purchased separately they would cost over \$75.00.

Almost any one of these coils is worth more than the price of the entire kit!

20% Deposit with Order. Balance C.O.D.

PHONO-KIT

**PORTABLE ELECTRIC PHONOGRAPH
A REAL QUALITY 110V AC PHONOGRAPH KIT**

- Handsome leatherette portable case
- High quality motor with 9" turntable
- Light weight crystal pickup
- 5" Alinco speaker with transformer
- Tone tested 2 tube amplifier with tubes
- Tone control and needle cup
- Nothing else to buy. Only 1 hour to assemble for play. Full instructions supplied.

SPECIAL YOUR COST **\$21.50**

LOTS OF TWO OR MORE **\$19.95**

WRITE FOR BARGAIN CATALOG

20% deposit with order. Balance C. O. D.
All materials sold on money back guarantee

BUYERS SYNDICATE

786 CAREW STREET, SPRINGFIELD, MASS.

Lebanon—FXE, *Radio Levant*, 8.036 (actually lower, around 8.020), gives schedule of 12 midnight-1:15 a.m., 5:15-8 a.m., 10:30 a.m.-4 p.m. (Legge) Has been heard in England announcing as "Ici Beirut"; during daily *English* period, 10:45-11:45 a.m. the station carries *English* newscast at 11 a.m. (Pearce)

Macao—According to NNRC, CR9AA, 9.500, operates daily, 4:30-9:30 a.m., with 200 watts; only identification used is "Radio Clube Macao"; call letters are never given over the air; asks for reports and will verify with QSL card; address, Radio Clube Macao, G.P.O., Macao, Portuguese China, Asia; chief engineer is John J. Alvares (CE9AG), who advises that they intend to increase power to 1 kw. soon; Mr. Alvares also advises that these commercial transmitters are in operation in Macao: CRY7, 17.597, 2.5 kw.; CRY6, 14.500, 750 watts; CRY4, 12.250, 1.5 kw.; CRY8, 8.450, 2.5 kw.; and CRY3, 5.900, 300 watts.

CR8AA, 9.254, is reported with schedule of 6-9:20 a.m., mostly in Portuguese and/or Chinese; Portuguese news at 7:30 a.m. and *English* news around 7:50 a.m. (this is read by female announcer); reception is erratic in North America. Peaks on West Coast around 9 a.m.

Madagascar—Tananarive is particularly good on 9.690, fair on 6.065 with identification in French at 11 a.m. (Gillett)

Malaya—Singapore has replaced 4.780 with 4.820; schedule is 5:30-10:35 a.m. (URDXC) *English* news at 9 a.m., headlines around 10:30 a.m. (Dilg) Some days signs off at 10:35 a.m., others at 11 a.m.; signature is "God Save the King"; strong signal in England. (Pearce)

Monaco—*Radio Monte Carlo*, listed on 6.130 but lately reported as high as 6.150, uses 300 watts, but expects to increase power to 25 kw. in July when a new transmitter will come into operation; schedule, 1:30-3:30 a.m., 6-8 a.m., 1-5:15 p.m. (Short Wave News, London) URDXC reports has moved to 6.150. Is heard in Ireland with bad CWQRM. (Levi)

Mozambique—CR7BJ, 9.645 (or 9.650), is heard in England with *English* news at 2:55 p.m.; closes down at

3:30 p.m.; still announces and verifies as on 9.710. CR7BU (listed officially as CR7BF), 4.925, is heard on Sundays between 12 noon and 2 p.m. with sponsored programs; advertisers chiefly in South Africa. (Pearce)

New Caledonia—*Radio Noumea* is now on 6.160 from 6.208, 2-5:15 a.m.; signs off with "La Marseillaise." (Dilg) Heard during the last hour of schedule with weak signal in New York. (Legge)

Nicaragua—YXNW, Managua, previously on 6.275, is now heard on 8.190. (Legge) YNCNN, 6.700, Managua, is heard 6-8 p.m., very weak with heavy QRM. (Howe)

Norway—LLI, Fredrikstad, is correct call and location of the Norwegian station on 6.185, according to verie; relays Oslo Home Service to 5 p.m. (Legge) In verie gave power as 8 kw. (Bromley) LKQ, 11.735, has strong signal in England from 11 a.m.; is heard some days closing at 5:10 p.m.; LLI, 6.185, and LKJ, 9.54, parallel; no *English*. (Pearce)

Philippines—KZRH, 9.64, Manila, has *English* news at 7:30 a.m. (URDXC). I have heard *English* news from KZRH at 5:30 a.m., and it is heard at that time in England by Leslie Holmes. Signals are usually very weak in the East, with considerable QRM from KRHO, Honolulu, 9.650. Fair signal in New York, 6:15-7 a.m. (Ballard)

KZPI, 9.71, Manila, heard weakly in New York around 7 a.m. (Ballard) Usually is covered in East by San Francisco's 9.700 outlet. Good level in New Zealand at 5 a.m., but with CWQRM; announces as "*Radio Philippines*, 800 on your dial"; 800 kcs. is medium-wave outlet. (Gray)


Poland—Warsaw, about 6.10, has good signals in Maine, 3:50-4:10 p.m., with *English* news period. (Beach)

Portugal—CSW7, 9.725, Lisbon, heard 7-8:30 p.m. sign-off. (URDXC) In verifying for Conley, Pennsylvania, listed frequency as 9.726, power of 10 kw., and schedule of 7-8 p.m.

Rumania—Bucharest, 9.252, was heard recently in Massachusetts, signing off at 8:17 p.m. (Harris)

Siam—In verifying, HS8PD, Bangkok, listed frequency of 6.040 (actually appears to be around 5.995) with

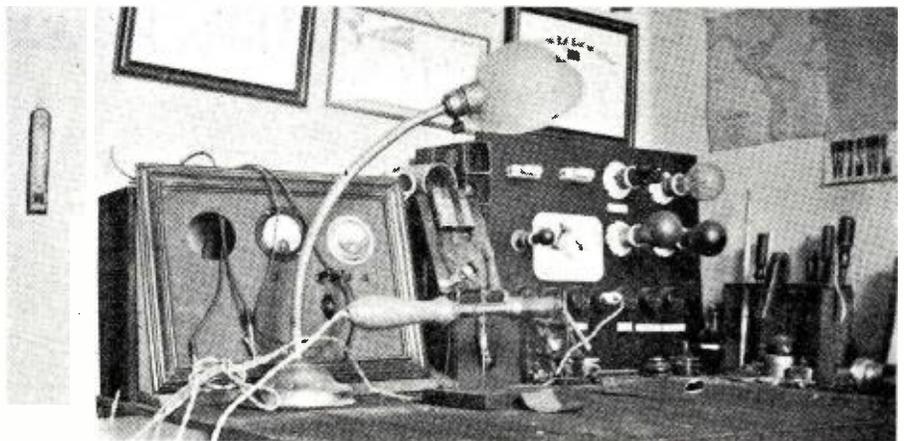
This listening Post is that of Luis Diez Alonso, Santander, Spain.



EXPORT Attention Manufacturers

Are you interested in having your products sold in the foreign markets of the world?

EXPORT

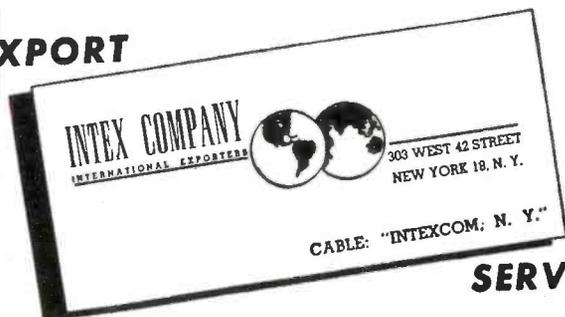

SERVICE

The Intex Company acts as direct factory export representative for a number of allied but non-competitive manufacturers in the Radio, Electronic, Electrical and affiliated fields. We handle all details such as:

- Financing
- Sales Promotion
- Foreign Correspondence
- Permits
- Shipping
- Export Packing

Send us your literature and write us regarding your products. Your letter will bring our prompt response. All inquiries will be kept strictly confidential. References exchanged.

INTEX COMPANY

303 West 42nd St. New York 18, N. Y.
Cable: "Intexcom, N. Y."

JUST OUT! Gov't Surplus BRAND NEW SOLID BRASS 9 FT. PORTABLE RADIO ANTENNAS

Real \$10 value now only \$2.95 ^{POST PAID}

FOR HOMES, BOATS or AUTOS

Same as used on Army tanks. These telescopic RUSTPROOF antenna have a tremendous pick-up and eliminate dangerous wiring. Made of Solid Brass throughout which practically insures

NOISE FREE RECEPTION

9 exceptionally rugged sections
compress into 1 ft. 2 in.

Handy for Camping Trips, also Useful for Transmitting Sets, FM Sets and Television Receivers

Each antenna comes with clamps, nut, lug, & wire. Easy to install anywhere. QUANTITY LIMITED.

MAIL ORDER TODAY. A real \$10 value for only \$2.95 Postpaid. Send check or money order now, or mailed C.O.D. plus postage. Also available 12 ft. Solid Brass Antennas at \$4.95 Postpaid.

Money back in 10 days if not satisfied.

RADIO HOSPITAL

1113 LEXINGTON AVE., DEPT. R5, NEW YORK 21, N.Y.



FOR EXTRA SALES-PROFITS IT'S ATR QUALITY PRODUCTS



ATR "A"

BATTERY ELIMINATORS

For Converting A.C. to D.C.

New Models . . . Designed for Testing D.C. Electrical Apparatus on Regular A.C. lines. Equipped with Full-Wave Dry Disc Type Rectifier, Assuring Noiseless, Interference-Free Operation and Extreme Long Life and Reliability.

- Eliminates Storage Batteries and Battery Chargers.
- Operates the Equipment at Maximum Efficiency at All Times.
- Fully Automatic and Fool-Proof.



ATR


AUTO RADIO

REPLACEMENT VIBRATORS

Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction for Longer Lasting Life.

ATR

STANDARD AND HEAVY DUTY INVERTERS

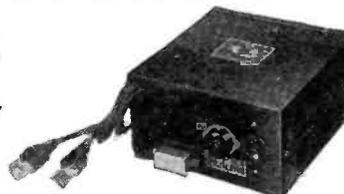

For Inverting D.C. to A.C.

Specially Designed for Operating A.C. Radios, Television Sets, Amplifiers, Address Systems, and Radio Test Equipment from D.C. Voltages in Vehicles, Ships, Trains, Planes, and in D.C. Districts. Write for Our New Catalog—Just Off the Press!

AMERICAN TELEVISION & RADIO CO.

Quality Products Since 1931

ST. PAUL 1, MINN.

U. S. A.

regularly; the morning beam, 7-8:15 a.m., is carried on 11.63, 11.72, 15.18, 17.82. (Cooley)

Vatican—HVJ, 9.660 and 5.970, has English news daily at 10 a.m.; English talks are radiated daily at 1:15 p.m. on these frequencies. On Sundays, commentaries are heard in French, Spanish, English, German, and Polish, at 5:15 a.m., followed at 5:30 a.m. by Holy Mass. On Tuesdays, English news is radiated at 10.30 a.m. on 17.445. (Salmon)

Yugoslavia—Radio Belgrade, 9.42, is being heard again at 12 midnight in New York; very weak. (Beck)

Acknowledgement

Sincere thanks go to all contributors to this issue of ISW. —30—

Deluxe Transmitter

(Continued from page 78)

cated in the accompanying curve (Fig. 6) falls off rapidly below 300 cycles, reaching minus 15 db. at 100 cycles. On the high frequency end the response falls off rapidly after 3000 cycles reaching minus 15 db. at approximately 8500 cycles and is minus 20 db. at 10,000 cycles. The complete schematic diagram of this amplifier is shown in Fig. 7. Because of this lack of linearity very flattering reports are continually being received regarding the speech quality of transmissions.

The apparent improvement in speech fidelity is brought about by a combination of transmitter and receiver characteristics.

A receiver must have a relatively narrow pass band to be very satisfactory for amateur communication purposes. The pass band in most amateur receivers is either limited to 3000 cycles, or is adjusted to approximately that value by the operator. Under these conditions, all frequencies above 3000 cycles represent wasted energy if actually emitted by the transmitter.

If the a.f. response of the transmitter is linear, the effect so far as the listener is concerned is an accentuation of the lower frequencies, since the receiver has eliminated the higher frequency components. It is then apparent that if the lower frequencies are attenuated at the transmitter, the middle range will be accentuated, and the over-all effect as noted at the receiving station will be that of a much higher quality of reproduction than would be possible with a linear audio frequency response at the transmitter.

—30—

ANSWERS TO BIZ QUIZ

- | | | | |
|------|-------|-------|-------|
| 1. b | 6. b | 11. b | 16. c |
| 2. a | 7. a | 12. b | 17. c |
| 3. a | 8. c | 13. a | 18. b |
| 4. c | 9. b | 14. c | 19. c |
| 5. c | 10. b | 15. b | 20. b |

ARE YOU A SALESMAN? Give yourself 5 points for each answer you had checked correctly. A score of 45 is average, and 75 or better is very good indeed.

Yes, it's true!
A Walter Ashe Trade In Deal
Makes your Old Help Pay for New!

TRADE IN ON FINEST TEST EQUIPMENT From

Hickok	McMurdo Silver
Jackson	Radio City Products
Precision	Robson Burgess
Simpson	Chicago Industrial
Triplett	Special Products Co.
Reiner	Industrial Instrument
RCA	Cornell Dubilier
Bliley	Coastwise Electronic
Waterman	Hanlan
Du Mont	Monitor Piezo
Feiler	Weston
Meissner	Sprague

TELL US WHAT YOU HAVE TO TRADE! LIBERAL ALLOWANCES

TRADE IN ON NEWEST RECEIVERS

Halicrafters	National
Hammarlund	RME
Collins	
WOPGI WQJWD WQULH	
WOYD WOGTF WOODF	

Send For Our Free Catalog

Walter Ashe

DYNAMOTOR Power Supply—Few Left
 Brand new, U.S. Army PE 103 operates from 6 or 12 volt battery, will deliver 500 volts DC at 160 **\$995**
 Ma.

MEISSNER KITS WITH TUBES
 6-Tube AC-DC... \$24.70
 3-Tube AC-DC... 8.37

AMPLIFIER CHASSIS
 With covers. De Luxe chrome trim, grayenamel.

No.	Size	Reg. Price	Sale Price
3971	5½x10x9	\$3.69	\$2.77
Standard, with cover, gray			
3980	5½x10x9	\$2.16	\$1.62
3983	10x14x9	3.51	2.64

Astatic R-3 Microphones economy type
 For PA and home recording. Special price... \$4.95

THROAT MIKES
 200 ohm carbon, a real sensation at35c

SHURE HAND MIKES
 Brand new surplus type T-17B, 300 ohm, push-to-talk carbon mikes with cord and plug \$1.47

TYPE H516A HEAD PHONES
 Army surplus, 2000 ohm with 6-ft. cord..... \$2.05

1125 PINE ST. ST. LOUIS, MO.

Become a Radio Amateur In a Few Weeks
No Previous Experience Necessary

Passing the Government Exam made easy by our NEW EASY-TO-LEARN type of instruction. Complete facilities for teaching CODE, Transmitter and Receiver Theory, Code practice W6YSL—3574KCS, Monday through Friday, 5:30 P.M. Day and Evening Classes Starting Now


WITHOUT OBLIGATION SEND FOR FREE CATALOG

I am interested in: AMATEUR RADIO Radio Servicing & General Electronics
 COMMUNICATIONS Home Training
 Television

Name..... Phone..... Hrs. You Work.....
 Address..... City..... Zone.....

ELECTRONIC TECHNICAL INSTITUTE
 771 VENICE BLVD., RN-7 Los Angeles 15, Calif. RICHMOND 9573

WIRE RECORDER

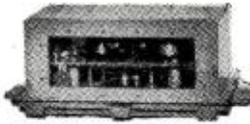

YOUR COST
\$44.50


This precision made wire recording magazine (built by Western Elect) offers you the opportunity to build a complete wire recording machine at less than 1/5 of the average price. Supplied with enough wire for a full 1/2 hour of recording time. Direct reading dials indicate "elapsed" time in minutes and seconds, enabling accurate "spotting" and "cueing". All units complete with recording and "erase" coils in full view case. Driving and take-up reels have splined shafts. Less driving motor and amplifier. Size 14 3/4" L x 7" W x 5-3/4" H. Ship wt. 38 lbs.

IF AMPLIFIER For 36 Megacycles



How long have you waited for a "super-duper" IF strip to come along? Here it is at last. 4 stages of double tuned hi-gain IF. Completely shielded (gain approx. 50,000). Bandwidth 1.4 mc ± 0.4 mc. Uses 4-6AC7 IF tubes, 1-6SJ7 infinite imped. detect. and 2-9002 AVC tubes. Has external cable for connection to 6.3 volt fil. and 250 VDC plate supply. Coax jacks for input and output. Diagram and tech. info. supplied. Units mfg'd by GE and brand new! Dimen. 18 3/8" L x 5 3/4" W x 4 5/8" H. Ship wt. 28 lbs. **\$12.95**
YOUR COST Less Tubes \$3.90
Complete Set of 6 Tubes..... \$3.90

DISCRIMINATOR BC-1270

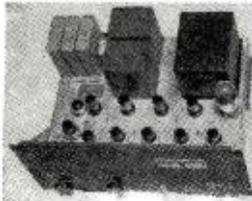

YOUR COST Each Complete With Tubes
\$14.50

Here is your grand opportunity to hit the season's "jackpot" of radio parts value. This discriminator chassis contains the following: a 36 MC IF amp and detect. (3 stages), a video blanking stage, a video discriminator stage and a 115 V 60 AC power supply delivering 6.3 V @ 4.5 amps and 280 VDC @ 170 mls. Filtering—excellent! All mounted on 17" x 15 1/2" x 3 1/2" chassis with standard 19" relay rack panel.

This unit contains the following tubes: 5-6AC7, 1-6H6, 1-6SH7, 1-6SJ7, 2-6SK7, 1-5U4G.

Perfect for rebuilding into a speech amp, television video amp, audio osc, low powered "ham" xmtr or exciter, etc. Hundreds of useful parts such as ceramic switches, resistors, filter condensers, power and IF transformers and chokes. Completely enclosed in metal housing making an ideal unit for table top operation. Diagram and tech manual supplied.

All units including tubes brand new. List price of tubes alone almost twice the selling price! Ship wt. 185 lbs.

TELEVISION SCOPE KIT

Will deliver 2800 VDC @ 15 mls; comprises:
* 1 ea. — Trans. 115 V 60 sec. 3200 V @ 15 mls.

* 1 ea. — Trans. 115 V 60 sec. 6.3 V @ 4 amps and 2.5 V @ 3 amps Hi-insul.

* 1 ea. — Cond. oil — 3 x .2 mfd 4000 VDCW
YOUR COST per kit—special \$14.00

PLATE POWERS SUPPLY

Will deliver 300 VDC @ 150 mls; comprises:

* 1 ea. — plate trans. (pri 115 V 60 sec. 5 V @ 3 amps, 6.3 V @ 4.5 amps 750 VCT @ 150 mls)

* 1 ea. — filter choke 10 H 150 mls.

* 2 ea. — cond. GE Pyranol 10 mfd 400 WV
YOUR COST EACH KIT..... \$5.75

HAND GENERATOR-PORTABLE

Supplies 550 vdc @ 85 mls and 12 vdc @ 2 amps when cranked 60 rpm. Perfect for field days — ham use — emergency boat xmtr. etc. Brand new and complete with chain block for quick and easy mounting on bumper, post, rail fence etc.

YOUR COST \$5.95

ALL MERCHANDISE FULLY GUARANTEED
20% Deposit with Order—Balance C.O.D.
All Orders F.O.B., N. Y.

KELVIN ELECTRONICS

74 Cortlandt St., New York 7, N. Y.

Manufacturers' Literature

Readers are asked to write directly to the manufacturer for the literature. By mentioning RADIO NEWS, the issue and page, and enclosing the proper amount, when indicated, delay will be prevented.

SOLDER BULLETIN

Alpha Metals, Inc. is offering a new bulletin describing their recently developed "Tri-Core" solder.

The folder describes the product as a self-fluxing solder with three cores just beneath the outer surface of the wire.

Application data and full details of this solder are contained in this four-page bulletin which may be secured without charge from Alpha Metals, Inc., 359 Hudson Avenue, Brooklyn 1, New York.

TUBE BROCHURE

A new 156-page receiving-tube brochure entitled "Recommended Types" is currently available for distribution to equipment designers and radio set manufacturers, according to an announcement made by the Tube Division of General Electric Company's Electronics Department.

Covering the complete G.E. and Ken-Rad receiving tube line and associated circuits, the new publication lists tube types in numerical order by sections. Each section includes a typical circuit, complete ratings, curves, and companion technical data for each tube type.

Distribution of this brochure is limited to receiver manufacturers, designers, and engineers who may secure their copy of the book by writing to W. Hayes Clarke, sales manager of receiving tubes, General Electric Company's Electronics Department, Tube Division, Schenectady, New York.

NATIONAL BULLETIN

Information on their new Frequency Shift Diversity Receiving Equipment is contained in a four-page bulletin recently issued by National Company, Inc. of Malden, Massachusetts.

This equipment, which provides frequency shift reception in the 2 to 20 mc. range, is completely described with electrical data and design features on the frequency shift receiver, frequency shift limiter and frequency shift keyer covered.

A copy of this bulletin will be sent to those who make their request to National Company, Inc., Malden, Massachusetts.

"Q" INDICATOR

Descriptive material covering their new Low Frequency "Q" Indicator, Type No. 1030, has just been released for distribution by Freed Transformer Company, Inc.

Complete specifications on this unit are given in this four-page data sheet including range, oscillator frequency range, accuracy, variable impedance

amplifier data, waveform, output impedance and voltage, variable condensers, accuracy of adjustment, temperature coefficient, frequency characteristics, power factor, etc.

A copy of this data sheet will be forwarded to those who request it from Freed Transformer Company, Inc., 72 Spring Street, New York 12, N. Y.

PYRAMID DATA SHEET

Pyramid Electric Company is now offering a one page data sheet which lists electrical and mechanical characteristics for their line of "Twist-Mount" capacitors.

This listing carries part numbers, capacity data, working voltages, can sizes, and prices for almost forty different capacitors in the company's line.

A copy of this data sheet will be forwarded upon request to Pyramid Electric Company, Jersey City 6, New Jersey.

OLSON CATALOGUE

Of interest to radio servicemen is the new Olson Radio Warehouse, Inc., catalogue which has been specially designed to be carried by the serviceman in his pocket.

Listing hundreds of everyday items needed by the serviceman, the new catalogue is reissued every thirty to sixty days in order that items appearing in the booklet are currently in stock.

Radio servicemen may secure their copies of the catalogue by writing direct to Olson Radio Warehouse, Inc., 73 East Mill Street, Akron 8, Ohio.

TEST INSTRUMENTS

Radio City Products Company, Inc., of New York has recently made available a comprehensive listing of their complete line of radio, electrical and electronic test instruments.

This listing, Catalogue 129, contains 24 pages of data covering tube testers, multitestors, v.t.v.m.'s, insulation testers, capacity meters, signal generators, combination tube testers, volt-milliammeters and various accessories for these instruments.

A copy of Catalogue 129 may be secured from the company's authorized jobbers or by writing direct to Radio City Products Company, Inc., 127 West 26th Street, New York, New York.

HAM FLYER

Sun Radio & Electronics Co., Inc., of New York is offering the first of a new series of ham flyers designed specifically for the amateur.

Listing all types of radio components, the flyer is unique in that it is

RADIO NEWS

the first catalogue intended for the use of hams only. All the parts catalogued are designed specifically for amateur construction and were selected by Walt Zuckerman, W2LBF.

Distribution will be made by *Sun Radio & Electronics Co., Inc.*, 122-124 Duane Street, New York 7, New York. Only licensed amateurs will be eligible to receive this catalogue. Call letters must be included with your request.

RHEOSTAT CATALOGUE

Catalogue 3 describing the company's line of slide-contact and rotary drive rheostats has just been issued by *Rex Rheostat Company* of Baldwin, Long Island.

In addition to listing physical characteristics of almost fifty models, this catalogue gives electrical specifications and performance data on many of the units.

A copy of Catalogue 3 will be forwarded to those making their request direct to *Rex Rheostat Company*, 3 Foxhurst Road, Baldwin, L. I., New York.

JK DATA SHEETS

The James Knights Company of Sandwich, Illinois, is currently distributing a new data sheet covering their JK Stabilized 100 kc. Crystal.

Of interest to the radio amateur, the new data sheet provides operation details on this new crystal under different ham applications.

Also available for distribution is an application sheet covering the company's IBC-3 Impedacoupler. This unit provides a universal type antenna insulator-connector for making a weatherproof junction between *Amphenol* "RG" type flexible coaxial line and any current fed antenna or array.

Either or both of these data sheets will be furnished those who write *The James Knights Company*, Sandwich, Illinois.

BOOK CATALOGUE

Chemical Publishing Co., Inc., of Brooklyn, is currently offering copies of their new 1947 book catalogue to those who request it.

Covering the latest books on chemistry, technology, physics, general science, mathematics, engineering, technical dictionaries, etc., this catalogue meets the specific needs of technical and scientific workers as all items are listed by date of publication, price, number of pages, description and full table of contents.

Copies of this catalogue will be forwarded to those making their request to *Chemical Publishing Co., Inc.*, 26 Court Street, Brooklyn 2, New York.

PHILIPS INDEX

A 20-page index listing all articles which have appeared in the "Philips Technical Review" during the period January, 1936 (the first issue), and June, 1942 (the last issue prior to suspension of publication during the German occupation of Holland), is currently available upon request to

May, 1947

HARRISON HAS IT! HARRISON HAS IT!

A WHOLE NEW BUILDING

so we may serve you even more efficiently!

Yep!—we've just added an entire five story building to enlarge our present facilities. More space to display all the fine lines we distribute—more room in which you can shop in comfort—a sparkling new Harrison Select Surplus section—a real Ham Shack where you can meet with the gang—a bigger and better Bargain Counter—larger and more complete stockrooms.

A streamlined Order Department that will get us back to our pre-war speed of *4 Hour Mail Order Shipments*—A special Export Department to expeditiously handle the orders from our good friends in other parts of the world—

HARRISON SELECT SURPLUS SIGNAL CORPS EQUIPMENT

Here are some exceptional bargains in AAF gear that are easily adapted to efficient Ham use.

There are lots of these used units around, but we believe we have been discriminating enough to be able to offer you the very best ones! Carefully reconditioned, checked and crated to come to you in almost new condition—yet our prices are no higher! Order yours from Harrison—in a hurry—and you'll be happy.

SC R-522 VHF Transmitter-Receiver. Complete with 17 tubes, control box, dynamotor, crystals, etc. \$33.95
 SC R-274-N. THREE Receivers. TWO Transmitters, controls, antenna unit, dynamotors, 29 tubes, etc. \$39.00
 BC-375-E Transmitters. Complete with tubes, tuning units, antenna tuner, dynamotor, etc. \$35.00
 BC-348 Receivers. Complete with tubes, crystal filter, dynamotor, etc. less speaker. \$49.50
 BC-221 Frequency Standard. Complete with original crystal and calibration chart, and tubes, in cabinet. \$39.50

RG-8/U

COAXIAL CABLE

52 ohm. FB for feeding beams, etc. Handle a KW. New, perfect cables 110 feet long with two PL-259 coaxial plugs. Total list price is \$39.28. HSS Special!... \$4.98

KW MODULATION TRANSFORMER

Here's the one they're all talking about! RCA broadcast quality. 550 Watt conservative audio rating. 1 to 1 ratio—will match most any tubes. Screen, winding. Safety flash-over gaps. 38 1/4 lbs. \$14.75

Get ready for SUMMER FUN ON 2

Abbott TR-4B, Transmitter-Receiver. Complete with tubes. \$56.78
 Abbott 110 V AC power pack. \$22.50
 EL 6 Volt Vibrator pack. \$14.97
 EL Combination 110, AC/6 V DC input. Delivers 300 Volts DC at 100 Ma. 6.3 at 4.75 A. \$27.00

Abbott BN-2 Five Element Beam

Squirt your sigs where you want 'em! Cut down QRM and have more and better QSOs with this FB beam. Will improve any rig!

Engineered for peak gain—factory pre-tuned 144-148 Mc—all hard aluminum high-Q elements and 75" boom—only 3 lbs.

Accurately machined kit (no drilling or cutting required), complete with insulators, mounting clamp T matching stub (feed with 300 ohm ribbon) and instructions for easy assembly. List \$23.50
 A HARRISON SPECIAL \$8.82

And many more new features—all designed to better enable us to give the friendly service and superior value that have made Harrison's *the Ham Headquarters*—Since 1925!

Business going on as (or even better than) usual during alterations. Drop in now and you'll pick up some exceptional bargains during our E-X-P-A-N-S-I-O-N SALE!

73

Bil Harrison, W2AVA

HAMMARLUND FS-135-C

Crystal controlled frequency standard. Easily connected—zero beat with WWV—and your receiver is an FB Freq. Meter! Complete unit with \$14.25 crystal, tube, and simple instructions...

MILLEN R-9'er

Hop up your receiver with this new antenna matching preamplifier! 27-32 Mc. \$24.75

48-55 Mc plug-in inductor. \$3.25
 18-15 Mc plug-in inductor. \$3.15
 6AK5 Tube. \$3.36



New!

SONAR VFX-680 NBFM, ECO, "Rubber Xtal" Ex. citer Unit. \$87.45
 Harrison Has It!

1947 MEISSNER Signal Shifter. Complete for all \$120 band operation.

SERVICEMEN

HAMS! Earn money for that new rig by selling Intercommunication Systems. Talk-A-Phone and Bogen in stock!

as distributors of COLLINS RECEIVERS and TRANSMITTERS

we are now entering orders for earliest delivery. Literature upon request.

MEISSNER RECEIVER KIT

Build your own 6 tube AC-DC two band BC receiver with this famous 10-1199 kit! Complete with speaker and antenna, less only tubes and cabinet. \$19.75

MECK T-60 TRANSMITTER

Compact! 15" x 11" x 9" metal cabinet contains complete 60 watt input phone-CW Xmitter. 110 Volt AC. With all tubes and 10 meter coils, less only \$150 microphone and crystal.

COMMUNICATION RECEIVERS, AMATEUR TRANSMITTERS, TEST EQUIPMENT—All Makes. All Models. Harrison has the biggest and most complete stock! Lowest Prices! Top Trade-in allowances!



HARRISON RADIO CORPORATION

10 WEST BROADWAY • NEW YORK CITY 7

PHONE—BR 7-9854 • EXPORT DEPT.—CABLE—"HARRISONRAD"

JAMAICA BRANCH—172-31 Hillside Ave.—REpublic 9-4102

RECORDING DISCS

Acetate cellulose recording discs for use on 33 1/2 and 78 R.P.M. machines. 30 and 60 minute recordings. 13 inch discs. 25c EACH

IRVING J. HALPERIN

22 Braemore Rd., Brookline 46, Mass.

FILMGRAPH PAT'D Conference Recorders

UNINTERRUPTED Longtime (up to 12 hours) Conference & Telephone Recordings on Safety Film Models for Dictation "TALKIES"

ECONOMICAL PERMANENT INSTANTANEOUS PLAY-BACK

MILES REPRODUCER CO., INC. 812 BROADWAY, N.Y. 3 RN-5

RADIO-ELECTRONIC TRAINING

"The best job bets for the long pull are those requiring specialized training."

So reports Science Research Associates after completing a survey of postwar opportunities in the U. S. The technical staff and laboratory facilities of WRCI offer you the opportunity to become a specialist in the expanding field of radio-electronics—either in Radio Communications or in Radio-Television Servicing. WRCI graduates now flying with transoceanic airlines, working in broadcast stations, operating their own radio repair shops, etc. Classes convene first Monday in each month. Approved for Veterans. Free copy of "Lifetime Careers in Radio-Electronics" upon request. Write Dept. M—no obligation.

WESTERN RADIO COMMUNICATIONS INSTITUTE

631 W. Ninth St., Los Angeles 15, California

Now Available for
IMMEDIATE DELIVERY
Complete
TELEVISION
COIL KIT

With these Coils, Construction of Your Television Set is Simplified

Instruction Manual for 20 Tube, 7 inch Picture Tube Set, included with each Kit.

Designed by Television Engineers these Coils are able to meet most exacting requirements. This Kit makes it possible

FOR THE HOME CONSTRUCTOR to build a set of excellent quality able to receive six channels of Television Transmission with FM Sound

AT LOW COST
 Look at these
SPECIFICATIONS

IF COILS

- Bandwidth of 4.25 MC that can operate ANY size Picture Tube with Maximum resolution
- Permeability Tuned, All Coupling Coils and all Traps
- Shielded; "CAN" Mounted
- Adjacent Channel and Sound Traps
- Built-in Coupling and Filter networks

***RF ASSEMBLY**

- 6 Channels, No. 1 to No. 6 inclusive
- Permeability Tuned, All Channels
- Maintains Gain and Bandwidth over all Tuning Ranges
- High Sensitivity
- Antenna Coil, RF Tuning Coils, Oscillator Tank Coil, all mounted on Switch Assembly Plate

OUR \$23⁵⁰ OFFER

INCLUDES THE FOLLOWING

1 Oscillator Tank Coil, 1 Antenna Coil, 6 RF Tuning Coils, all mounted on Switch Assembly Plate; 5 Video IF Coils, Shielded, Permeability Tuned; 1 Shielded Discriminator Coil; 3 Video Peaking Coils, and instruction Manual containing Circuit Diagram for 20 Tube Seven Inch Picture Tube Set, together with detailed Assembly Instructions, and Parts list. The design of these Coils makes it possible to obtain satisfactory operation within the ENTIRE service range of ANY Television Station.

If Our Instructions are Followed

SATISFACTION IS GUARANTEED

All Special Coils are in this Kit. Remaining parts are easily obtainable.

TERMS

Shipped Express Prepaid on receipt of check or Money Order. Or Express Collect on receipt of 25 per cent deposit with order, balance C.O.D.

*Patent Applied for.

RAY-LECTRON CO.
 "Television Kit Headquarters"
 BELMAR, N. J.

the Elsevier Book Company, Inc., 215 Fourth Avenue, New York 3, New York.

The index, which is distributed free as a service to readers, catalogues all articles by subject as they appeared during the period covered. This index may also be used as a reference source for technical articles.

PARTS CATALOGUE

A new catalogue of interest to the serviceman and the amateur has just been issued by *E. F. Johnson Company* and is currently available either from the company direct or from its distributors.

Covering well over four hundred items, Catalogue 969 describes the company's line of variable transmitting capacitors, inductors, tube sockets, "Q" antennas, insulators, plugs and jacks, couplings, r.f. chokes, and tube cap connectors. In addition to these items, new products appearing for the first time in the company line included multi-wire connectors, tip plugs and jacks, and pilot dial and panel lights. The catalogue does not include the company's directional antenna equipment or large components for broadcast or industrial use.

A copy of Catalogue 969 may be secured from *E. F. Johnson Company*, Waseca, Minnesota, or any company distributor.

-30-

Spot Radio News

(Continued from page 22)

facturers as this goes to press. From Holland comes word that the Philips Lamp and Radio Works, Nazi-held but comparatively undamaged during the war, is exceeding prewar records in production of radio tubes. Manufacturers in England are well enough along the road back to prewar production levels to have exported 77,586 units last year, as compared with 47,828 units imported. Elsewhere on the Continent, production was in miniature. Germany, for instance, averaged only 246 (two hundred and forty six) receivers per month during the last quarter of 1946, as compared with a monthly average of 12,000 in 1938. (These figures are for the U. S. zone only.)

ELSEWHERE ON THE FOREIGN FRONT, look for significant developments beginning May 15, when the World Telecommunications Conference is scheduled to meet in Atlantic City. FCC and the U. S. delegation will be prepared at that time to submit a plan for worldwide allocation of frequencies for all radio services, but so will a number of other nationals. Some compromises, affecting radio activities in this country, seem inevitable. Final decisions on the whole complicated problem will, in the estimate of FCC chairman Charles R. Denny, take "at least three months." He adds: "We are confident that a basic work-



TELEVISION
BLOCKING OSCILLATOR
TRANSFORMERS

SHIELDED TYPE:—Enclosed in Black Wrinkle Shield cans measuring 1 1/2" x 1 1/2" x 2 1/2". Stud mounting. Lug terminals.

Cat. No. OT-103H. Horizontal Oscillator (15,750 cycles)\$4.75

Cat. No. OT-104V. Vertical Oscillator (60 cycles) 3.95

UNSHIELDED TYPE:—Provided with strap mounting bracket, color-coded leads. Electrically identical to above units.

Cat. No. OT-101H. Horizontal Oscillator \$3.25
 Cat. No. OT-102V. Vertical Oscillator... 2.50

TELETRON Deflection Yokes, Yoke Matching Transformers, and Focus Coils also available.

The TELETRON Television line is now available at many leading jobbers. Write for latest catalog.

THE TELETRON COMPANY
 1988 East 59th Street Cleveland 3, Ohio

TEST OSCILLATOR KIT

Supplies I.F. and broadcast frequencies modulated or unmodulated complete with tubes, chassis and metal cabinet punched and all parts mounted ready to wire. RTO-100N.....\$14.75
 Wired and tested.....\$20.25

RECEIVER SPECIAL

Wilcox type F3 fixed tuned superheterodyne, ideal for use with a high frequency converter. Complete with coils, tubes, 110 volt 60 cycle power supply and complete instructions.....\$14.50

PHONO PLAYER KITS

Table Model, dual tube amp, five-inch speaker, light weight crystal pick-up, attractive two-tone cabinet and quiet rim-drive motor.

Model RNP4, complete.....\$15.95

Wireless Phono Player; tune it in on any radio.

Model IN5W, complete.....\$14.35

Phonograph attachment, plays through any radio.

Model IN5A, complete.....\$9.85

Tubes are supplied with all the above kits.

AMPLIFIER KITS—3-tube RN3, \$3.80; 2-tube RN2, \$2.60; 1-tube RN1, \$2.10; phono oscillator kit RN3W, \$2.60. Tubes extra.

RADIO TUNER KIT, complete with tubes. HRT 150N, \$7.45.

TUBE SPECIALS. 12AT6, \$.65; 32L7, \$1.35; 35W4, \$.60; 50B5, \$.85; 12SA7, \$.65; 35L6, \$.65; 25Z5, \$.65; 50L6, \$.70; 117N7, \$1.45.

TERMS—Cash with order or C.O.D. with 20% deposit. Add postage.

Send for special bargain list.

HALLMARK ELECTRONIC CORP.
 592 Communipaw Ave., Jersey City 4, N. J.

ELECTRONIC VOLT-OHMMETER

\$11.85 110 VOLTS AC 20 RANGES
 0.75/10/50/100/500/1000/5000 volts DC and AC 0-1,000,000,000 ohms in six overlapping ranges. Sensitivity: over MILLION OHMS per VOLT on 5 volt range.

POSTPAID
 Complete kit includes all component parts, tubes, punched and drilled chassis and beautifully enameled panel. Easily assembled and wired.

Special slideback circuit developed during war by scientist at the California Institute of Technology gives amazing sensitivity and flexibility while completely eliminating necessity of batteries and expensive meter. Each instrument is individually calibrated. Dial scale over nine inches long!

In addition to performing the usual volt-ohm functions, this instrument easily measures these voltages: SUPERHET OSCILLATOR, AVC, AFC, TRUE GRID BIAS AT THE GRID, BIAS CELLS without affecting the circuit. Measures the exact leakage resistance of INSULATION, TUBES, CONDENSERS. It can be used with a signal generator for SIGNAL TRACING.

STERLING ELECTRONIC COMPANY
 Dept. 3
 166 N Sierra Bonita Ave., Pasadena 4, California

RADIO ENGINEERING
TELEVISION
ELECTRONICS

Courses in every phase of radio and electronics open to high school graduates. Thorough training, modern courses. Enrollments limited. Approved Veteran Training.

VALPARAISO TECHNICAL INSTITUTE
 Dept. RS Valparaiso, Indiana

Protect Your Future
Buy Extra BONDS Now

able plan can be achieved, but I am sure that what is ultimately adopted will not be the present United States proposal or indeed that of any single nation. It will be a composite plan embodying the best possible way of meeting the requirements of all the nations of the world." He believes that the agreement finally arrived at must provide "not only for the frequencies having long-range propagation characteristics but also for the very high frequencies, the ultra-high frequencies, and even the super-high frequencies where the bands are employed for use on ships or aircraft which travel around the globe." It's going to be a tough, gruelling conference any way you figure it.

DOMESTICALLY, Chairman Denny believes that the two biggest headaches now facing FCC and the industry are the high frequency spectrum and radio heating. The commissioner points to the spectrum between 4 and 25 megacycles as the worst trouble spot. He characterizes it as "a potential bottleneck to the expansion of worldwide communications, worldwide aviation and worldwide shipping." "There is a growing demand," he says, "for additional frequencies from each of these services, but our studies in preparation for the world conference have established that there is no way that any one of these services can be given additional frequencies without

robbing one of the other services." What to do? Mr. Denny offers two solutions, both admittedly temporary—more efficient use of the frequencies between 4 and 25 megacycles by application of all engineering techniques available, including highly directionalized antenna systems; and possible re-assignment of the spectrum "so as to provide blocks of frequencies for a given country or region of the world, thus making possible an even better utilization of the available supply." But supply will continue to lag behind demand—only further scientific development, in FCC's opinion, can ultimately solve the problem. Mr. Denny recently put it up to U.S. radio engineers in the form of a challenge: "If radio is not to impose a ceiling on the expanding communications and commerce of the world, we must have a means for using the microwaves for communicating between continents. I know that this suggestion that you stretch or bend the microwaves is a big assignment but I doubt if there is an informed radio engineer who would venture to say that it cannot be done. The answer may lie in planes circling in the stratosphere, in reflections from the moon, or in some other technique not yet dreamed of—but it is of the greatest importance that an answer be found."

HEADACHE NO. 2, radio heating, is a service which is growing so fast that

FCC believes it "soon may boast a larger investment than radio communications." Chairman Denny points out that it is now being used for such diverse purposes as welding metals, molding plastics, vulcanizing rubber, curing tobacco, fusing glass, drying penicillin, relieving aches and pains, inducing artificial fever and grilling hot dogs. "These radio heating machines," he adds, "must either operate on frequencies assigned to them or some method must be devised for shielding them so that they do not radiate." Best solution yet for the problem is FCC's effort to set up "graveyards" at strategic points in the radio spectrum where all radio heating devices can operate without bothering radio communications. Four graveyards—in the 13, 27, 40 and 2450 megacycle regions—have already been set up. But the radio heating enthusiasts—like everybody else in radio—want more. Where they are going to get it—how they are going to expand in an orderly manner without stepping on the toes of radio communication expansion—is anybody's guess. It is also, to quote FCC's Denny, "going to be one of the biggest headaches of the next decade."

RECOGNITION OF THREE UNSUNG RADIO leaders and their war contributions came recently with Certificate of Merit awards from the U.S. Navy. Two of the recipients were Chi-

Take your choice of these **FREE GIFTS** *from* **OLSON**

100 POPULAR CIGARETTES

Free

with your purchase of \$15 or more in Radio Parts. Lucky Strikes, Comels or Chesterfields—smoke 'em or give 'em away! Make up an order and use the coupon TODAY.



Vacuum-Packed Tin of Planters Peanuts

Free

with your purchase of \$10 in Radio Parts; a \$20 purchase brings you TWO tins, etc. Big 1/2 lb. can of fresh, delicious Salted Jumbo Peanuts of famous quality! Use the coupon TODAY.



NEW, 200-PAGE HANDBOOK

Free

with your purchase of \$10 or more in Radio Parts. A practical guide to help you operate a shop or store successfully. Packed with valuable information! Use the coupon today.



Help yourself to a gift from Olson Radio Warehouse, and get a square deal in Radio Parts too! These gifts are free to our customers—proving that you get MORE for your money when you buy from OLSON. Try it—and see!

Here's how to get your Free Gift: Look through our

catalog (you should have one) and make up an order in the amount specified for the gift you want. Mail this order to us and enclose the coupon below. Do it NOW!

IF YOU DON'T HAVE A COPY OF OUR LATEST CATALOG, SEND FOR IT. NO CHARGE, OF COURSE.



Mail us an order today, and attach this coupon → for your Free Gift!
OLSON RADIO WAREHOUSE, Inc.

73 E. MILL ST., DEPT. 77, AKRON, OHIO

OLSON RADIO WAREHOUSE 73 E. MILL ST., AKRON, OHIO
I enclose an order totalling \$ _____ Send me FREE the gift checked below.

100 CIGARETTES (Luckies Camels Chesterfields)
 PLANTERS JUMBO PEANUTS 200-PAGE HANDBOOK

NAME _____
ADDRESS _____
CITY _____ STATE _____ 77

VERIFIED SPEAKERS

"They speak for themselves"

Distributors Enjoy Selling Them
Because they make friends
and build business.

The VERIFIED GUARANTEE back of the
Distributor enables him to immediately
Replace any defective Speaker with a new one.

Saves Time and Money For The
RADIO SERVICE MAN

WRIGHT

Inc.

2231 University Avenue

St. Paul 4, Minnesota

The HOUSE OF A MILLION RADIO PARTS

BARGAINS for SERVICEMEN AMATEURS, EXPERIMENTERS

No. 01—0 to 1 Standing Wave Meter—used to check Feeder and for Field Strength Meter	\$ 4.95
No. 300—McClintock 0-300 D.C. Milliammeter 3½ inches square	3.93
No. 500—McClintock 0-500 D.C. Milliammeter 3½ inches square	3.93
No. 350—G.E. 3½ inch Foundation Meter—Make Your Own Volt-Ohm Milliammeter Unit	6.95

Thousands of other bargains in stock for immediate shipment—Tubes, Record Changers, Amplifiers, Speakers, etc. Write for Catalog No. 58.

Lifetime SOUND EQUIPMENT CO.
911-913 Jefferson Ave., TOLEDO 2, OHIO

GOVERNMENT SURPLUS

If you cannot get to the Government Sales of War Surplus Radio Equipment, the next best thing to do is to buy our SPECIAL \$25.00 GOVERNMENT RADIO SURPLUS ASSORTMENT. We buy large quantities all over the country, divide those items we don't have in large quantities into choice assortments for which we know you would gladly pay \$25.00 if you could see them.

On a deposit of \$5.00 we will ship you C.O.D. (balance \$20.00) freight collect, a large quantity of Government Surplus Radio Items subject to Your inspection. If, after inspecting, you are not more than satisfied, return to us, freight charges collect, and all it will have cost you will be freight charges. You should be able to dispose of a few of the items that you may not need for the entire cost. This is the cheapest way we can sell you War Surplus Radio Material.

Our warehouses are filled with thousands of choice Government Surplus Radio Items. Lots of them we do not have in sufficient quantity to advertise nationally and the cost of inventorying, itemizing, corresponding, etc., would only increase their cost to you; therefore we make this offer. If you wish to mention a few items you desire, we will endeavor to include them in this assortment. State whether you wish "Ham" or Commercial assortment.

THE ABELL DISTRIBUTING CO.
5 E. BIDDLE STREET, BALTIMORE 2, MD.

cagoans—Leslie F. Muter of the *Muter Company* and Attorney Leonard J. Shapiro. Both got the awards for outstanding contributions to the war effort in expediting Navy electronic production in the industry. Mr. Muter served as president of *Radar-Radio Industries* during the war, and Mr. Shapiro was its executive secretary. Among other things, they recruited 35,000 new workers to meet the vital Navy production schedule. . . . Third man to receive a Certificate for outstanding radio work was Dr. Robert M. Page, superintendent of radio division three of the Naval Research Laboratory, with which Dr. Page has been associated since 1927. He was responsible for many years of fundamental research and development which led directly to the first practical shipboard radar as well as development of the first pulse radar equipment. Dr. Page was head of the special research section, radio division, of the Naval Research Laboratory from 1940 to 1942, and later headed the Laboratory's ship and shore radar research section and fire control section. His home is in Washington, D.C.

—50—

A Sales Control System

(Continued from page 65)


to another salesman with better results. Some salesmen are more adept than others at meeting certain objections or situations.

The Customer Card is an example of the evolution that has taken place in the sales control system since pre-war days. A customer file is exploited as energetically as a prospect file. This prevents salesmen from forgetting old customers, as too many salesmen do. Old customers are first-line prospects for other products and an excellent source of user leads. This card may be filed alphabetically or by date, if the salesman can judge the customer with regard to the next probable purchase and date, in which event, the card is filed to come up for action at that time, similar to the procedure with the prospect card.

The Transcript of Sale is recorded for ready reference in case of misunderstanding regarding settlement, and to give the salesman, when following up the customer for plus business, an idea of the merchandise or service purchased previously and the price paid, also the size of the trade-in allowance. By referring to the Customer Card, the salesman can tell when going after repeat business or plus sales whether he will be able to satisfy the customer with a limited trade-in allowance or whether the customer will demand the limit, whether the customer pays on the dot or is slow pay, whether the financial arrangements were long-term or short-term, etc. The Customer Card also carries valuable information for the statistical build-up of the Sales Analysis Chart.

The Sales Analysis Chart provides

REAL BONAFIDE VALUES

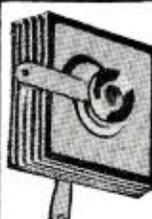	Federal Selenium Rectifier Replaces All Rectifier Tubes Sample \$1.09 92¢ Lots of 12		SHURE CRYSTAL MIKE With Base & Cable Reg. \$18.50 \$6.95		Permoflux Nylon Cone 5" heavy slug Speaker 100 I.R.C. Resistors-Ass't. Sizes & Watts Government Surplus Phones 3525-50L6-12SA7-12SK7-12SQ7 Standard Tube Kits Astatic L-70 Pick-Up Pocket Volt-Ohmmeter 2" PM Speaker Shure T-17B Push Button Carbon 6 Ft. Line Cords & Plug TERMS: 25% Deposit Required with Order. Balance C.O.D. Plus Mailing Charges.	\$1.98 \$2.49 1.98 3.60 2.95 14.75 1.39 2.39 each 15c	
Home Recorder & Playback with Mike. Regular \$99.95	\$79.50	Seeburg 2 Post Changer	\$25.97	Detroit Changers	\$14.75	Government Surplus Special 5½ foot Earphone Ext.—JK26-P.L.54	4.90

BONAFIDE RADIO & ELECTRONICS CO.
89½ CORTLANDT ST. NEW YORK 7, N.Y.

monthly sales statistics to guide the dealer from every angle, including territorial sales analysis. If salesmen are making too few sales, presumably because they are rushing interviews or are weak closers, if selling or advertising expense is too high for sales volume, if window displays have dried up as a source of sales, if too few demonstrations are given in proportion to qualified prospects, the Sales Analysis Chart discloses these facts and others so that the necessary adjustments may be made.

The forms of a well-devised sales control system fit together like a jigsaw puzzle to produce a perfect picture of selling effort versus selling results versus selling possibilities. Forms may be printed, mimeographed, multi-graphed or typewritten in carbon. Prospect Cards and Customer Cards are more adaptable in size 4 x 6 or 5 x 7 for filing in cabinets. The Prospect Register, Daily Report and Sales Analysis Chart are usually kept in looseleaf binders.

Whether you do your own selling or employ one or 21 outside salesmen, you cannot hope to do a topflight job of sales promotion unless you use a systematic method of sales control and this reasoning applies to little business as well as big business.

Salesmanship can only be effective if it is backed by competent business management. An adequate sales control system is essential to this objective. The system outlined here gives the fundamentals of operation and has been devised after analyzing many systems used by dealers in the past. No dealer need use it "as is." Make the necessary changes to conform to your particular business needs.

-30-

TALL CORN HAMFEST

PLANS are now nearing completion for the Tall Corn Hamfest to be held Saturday and Sunday, May 24-25, at Hawkeye Downs, Iowa, the home of the Iowa State Fair.

The program has been planned to provide entertainment for the entire family. Technical sessions for the amateur will be paralleled by special shows for the wives and children of those attending the hamfest.


Saturday evening will be rounded off with a banquet which will be held at the Cedar Rapids Chamber of Commerce Building. The dinner is set for 7 p.m. and will be followed by an address by George Bailey, president of the ARRL and Executive Secretary of the IRE. Dancing will begin at 9:30. Activities for Sunday include tours of the Turner Microphone Company and Collins Radio Company plants and a trip to the Municipal Airport; a picnic type lunch at noon; and a hidden transmitter hunt in the afternoon.

All requests for tickets and complete program details should be made to D. D. Morgan, 430 35th Street, N.E., Cedar Rapids, Iowa. The tariff is \$5.50 for those attending the meeting both days while those attending only the Sunday sessions will be relieved of \$4.50. Check or money order should accompany requests for reservations.

-30-

May, 1947

Available for Immediate Delivery!

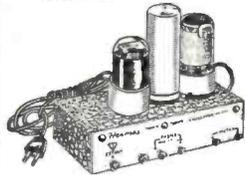

The Hermes Model B5
OSCILLATOR—
PLATE MODULATED

Especially designed and engineered to meet the need for a phono oscillator incorporating all of the features necessary for consistently superior results and ease of installation. The Electronic Engineer will appreciate these features:—broadcast studio type plate modulation thru a new and original circuit design for hi-fidelity and frequency stability. Covers the entire Broadcast Band from 500 to 1750 Kc. Choose the clearest channel in your locality. Plainly marked plastic terminal panel for easy connection of pickup and motor. Terminals provided for high and low output pickup. (No external or internal adjustments required.) Universal mounting. Only two small
a. Electronic (Oscillograph)
b. Aural (Actual Performance)
Complete—Ready to Operate

TUBES \$5.95



AUDIO OSCILLATOR
Sine Wave-Square Wave

"Ferret" Model 610. Frequency range 20 to 24,000 cycles. 3 to 1 vernier planetary drive. No back lash! Sine wave or square wave on same calibration. High impedance output—25 volts. Power: 110-120 volts, 50-60 cycles. Ranges 20-24,000 cycles. Over-All Dimensions: 2" long, 6 1/2" wide, and 9" high. Wgt. 10 lbs. packed. This instrument will enable the serviceman to check frequency response and make various audio checks not possible without this type of generator. . . . EACH, only \$69.95

WEBSTER CHANGERS

Model 50 \$21.17
Model 56 26.66
Model 70 43.50

Terms: F.O.B. Chicago

SPECIAL!

P.M. SPEAKERS

4" ALNICO #5 Net. \$1.19
5" ALNICO #5. Medium Slug. Net. 1.25
5" ALNICO #5. Heavy Slug. Net. 1.45
5" ALNICO #5. Extra Heavy Slug. Net. 1.75
6" ALNICO #5. Net. 1.98
L.A.T.E. SPECIAL 4" LSL Army type P.M. Net. 1.94
Portable phono-record changer with leatherette cabinet. Net. 8.95

SPECIAL

66" 3 Section Auto Antennae Complete with lead and insulators, individually boxed 25 to a carton. \$1.21 ea. In case lots. \$1.00 ea.

MEISSNER 3-5-6 TUBE KITS

3 TUBE KIT—Not a toy! A real midget kit designed for students. Easy to assemble. Detailed printed instructions and diagrams with each kit. Only tools necessary to assemble are a screwdriver and small soldering iron. Complete except for headphones and antenna. Each, Only \$8.25 Complete with Tubes.
5 TUBE KIT—Frequency coverage includes entire broadcast band between 540 kc. and 1600 kc. Operates on 110 volts, 50 to 60 cycles, or DC. Complete with factory wound loop antenna. Each, Only \$22.20 with Tubes.
6 TUBE KIT—Frequency range covers broadcast band from 540 to 1600 kilocycles. Short wave band from 6 to 18 megacycles. Kit contains all needed parts for completion of receiver. Each, Only \$24.76 with Tubes.



SIGNAL CORPS
OUTPUT METER "146"

A war surplus bargain made by Triplet for the U. S. Army. Meter has 5 ranges, 1 1/2v, 6v, 15v, 60v, 150v. Meter resistance 4000 ohms. Can be used on A.C. voltmeter as well as an output meter. Used in conjunction with a signal generator, the "146" is an invaluable aid in "sounding" your alignment jobs by indicating the intensity of the output of the radio. Complete with high quality test leads with clips and black moulded bakelite case measuring 6" x 3".

\$11.95



SOMETHING NEW IN
TEST SPEAKERS

No need to carry the speaker to your shop in servicing any radio from the small midget to the most elaborate console. A ny output tube or tubes can be matched simply by rotating input switch to tube listed on the front panel and rotate field switch for proper impedance and proceed with testing. External voice coil connection permits testing of set speaker to determine if output-transformer is open or shorted. Field impedance: 500, 1000, 1500 and 2500 Ohms.

\$19.95



GUARANTEED
TUBULAR CONDENSERS

8 MFD—450V— 25c ea.
10 or more 27c ea.
Less than 10 28c ea.
20 MFD—150V— 26c ea.
10 or more 28c ea.
Less than 10 28c ea.
20K20 MFD—150V— 45c ea.
10 or more 49c ea.
Less than 10 49c ea.
All fresh stock

Write for FREE Catalog

TUBES

Complete line of all "Hard-to-get critical tubes." Send us your order and we will surprise you with delivery!

AMAZING NEW HI-POWER 1/4" PORTABLE ELECTRIC DRILL

\$17.95

AC/DC Motor

Air-Cooled— Powerful 1/4" capacity in steel. Light weight. Guaranteed against any defect in materials and workmanship for six months. Not a toy—but a fine tool made for maximum service.



The Radio Shack Inc. OF CHICAGO
630 W. RANDOLPH STREET CHICAGO 6, ILL.

Radio Technician and Announcers

A practical nine-month course in First Class Radiotelephone Operation and Announcing is offered by Don Martin School of Radio Arts. Most stations these days require combination men. We specialize in this type of training and maintain a placement bureau for our graduates. Serving the industry for nine years, the School of Radio Arts can train you. Write for our catalogue outlining the courses offered. Classes can be arranged so you can do part time work on the side.

APPROVED FOR VETERANS

DON MARTIN SCHOOL OF RADIO ARTS
1655 North Cherokee St. Hollywood 28, Calif.

LIMITED QUANTITY

RTL TUBE CHECKERS

Model 130—For all standard 4, 5, 6, 7, octal and miniatures. Portable leatherette case. Formerly \$52.45. NOW \$43.00

LIFSEY DIST. CO. 730 N. SAGINAW FLINT, MICHIGAN

NOW!

Vibrators Can Be Rebuilt

Vibrators can be rebuilt under factory methods by skilled technicians. Each vibrator is rebuilt, adjusted and finally tested with an oscillograph. Each vibrator receives the same careful attention. Each vibrator rebuilt is backed by our money back guarantee. Our many repeat orders prove that vibrators can be rebuilt.

Do not send vibrators unless you believe they can be rebuilt. We rebuild any type or kind of vibrator. Enclose remittance and return postage for prompt service. C.O.D. orders accepted also. Synchronous vibrators rebuilt for \$1.25 ea. Others rebuilt for \$1.00 ea. Old vibrators may be rushed to

BEST VIBRATOR CO.
Box 5802-D Cleveland 1, Ohio

A "REEL" BUY!

No.-20-7. Strand Black Plastic Indoor or Outdoor Wiring on 27" reel—15,000 ft. \$270.00 Value. Your Price. \$46.00
Special Discount in Quantities



MALLORY LINE NOISE FILTER
Rating 110-220 V. (AC-DC)
\$10.00 Value. Your Price... \$3.75
In Lots of 10—\$3.25

FREQUENCY METER

Calibrated on Vernier Dial 80- to 500 Meg.
\$25.00 Value. Your Price... \$4.95
In Lots of 10—\$4.60



LATEST PORTABLE RECORD PLAYER

Beautifully finished in simulated alligator. Baffled for console like tone. Heavy duty hinges and snaps.
\$19.95 Value. Your price... \$9.95
In Lots of 10—\$8.95
Dimensions—19 1/2 x 7 1/2 x 13 1/4 in.



BLACK METAL CABINETS

Crackle enamel finish.
Size: 13 1/4 x 15 1/4 x 18.
\$ 7.50 Value. Your price... \$4.00
\$10.00 Value. Your price... \$5.00
Size 7 1/4 x 12 1/4 x 14.
In Lots of 10—\$3.50
In Lots of 10—\$4.60



PHONE PLUG AND JACK

Extension cable standard plug and jack. 66" rubber covered kinkless cable, head phones, extension, speaker cable patch cords.
\$5.00 Value. Your price... \$2 for \$1.00
In Lots of 10—\$0.35 ea.



MASONITE PHONO RADIO COMBINATION CASE

Cabinet stamped ready for assembly with 5 or 6 tube radio or phonograph. Size: 11 1/4 x 8 1/4 x 5 1/4
\$4.95 Value. Your Price... \$2.45
In Lots of 10—\$1.95



SUPREME POCKET MULTIMETER

Meter ranges D.C. Volts—0/150/300 D.C.—M.A. 0/60/120/300/600 A.C. Volts 0/150/300/ Ohms, 0/1000/100 M. Uses D-Arsenval type meter, sensitivity 200 Microamperes.
Exceptional Value. Your Pr. \$24.50
In lots of 10—\$22.50



110 VOLT A. C. MOTOR

Heavy duty construction. Fractional H.P. Ball Bearing Brand New. Ideal for power tools, fans and 100 other uses.
\$15.00 Value. Your Price... \$4.50
In Lots of 10—\$3.50



POWER TRANSFORMERS AND FILTER CHOKES

C-19-Pri. 110-115 Sec. 1 to 60 Volts	\$1.00
C-23-Filter Choke 15 Hen. at .08 amps. Tapped at 5 Hen.	.50
C-25-Filter Choke 15 Hen. at .08 amps	.50
A-93-Output Transformer Primary for Pentode plate, Sec. 600 ohms	1.00
C-26-R.F. Filter Choke 2 Iron core reactors 2 and 12 M.H. . . 1 mid. WV300	.50
X-1-Filter Choke for AC-DC midgets, Iron core	4 for 1.00
Cat. No.	
X-2 10 Wafer and Ceramic Band Switches	\$2.00
X-3 10 Wire wound resistors the best preferred values 10-50 Watt	2.50
X-4 10 Condenser blocks, Shielded, electrolytics paper condensers	2.00
X-5 50 Silver. Yellow, low-loss popular sizes	3.00

Extremely sensitive loop antenna. Can be connected to any receiver without additional wiring. Your price... 12 for \$2.00

HEAD PHONES

Value \$8.00. Your Price... \$1.89

ELECTROLYTIC F.P.COND. 20 MFD. 25V.

15 MFD. 300 V. 10 MFD. 350 V.
\$1.25 Value (ea.). Your price 4 for... \$2.00

SPRAGUE ELECTROLYTIC COND. 20-/20 MFD. 150 V.

Com. Neg. Fresh Stock.
\$1.64 Value (ea.). Your price... .65

VOLUME CONTROLS IRC, Allen Bradley

200 M., 500 M., Dual., 75 M., 25 M., 50 M., 500
\$5.00 Value. Your price 5 for... \$1.00

All merchandise fully guaranteed
All prices F.O.B. New York City.
Remit 20%—Balance C.O.D.

Write for Quantity Prices on Other Items

MANUEL KLEIN
INDUSTRIES CORPORATION

74 Cortlandt St. NEW YORK 7, N. Y.

EXPERIMENTER

For the



Although the recent survey conducted by Radio News indicated a predominance of servicemen and amateur readers, we found that many would like simple "how-to-do-it" articles. Accordingly we present this new department for the benefit of these readers.

AUDIO AMPLIFIER

The one tube receiver described in last month's experimenter's pages, will give greatly improved results and increased volume if an audio amplifier is added. In addition, the bother of wearing headphones is eliminated, and comfortable room volume reception of most stations is possible.


No changes will be required in the receiver to use this added unit. Essentially, the unit consists of a 1Q5GT audio amplifier, which drives a four inch PM speaker. Volume is con-

plus the added drop across a 30 ohm resistor, this bias voltage is obtained.

The speaker used is one of the replacement type sold for use in small receivers. An output transformer to match the 8000 ohm plate load of the 1Q5GT to the 4 ohm voice coil should be chosen. Inasmuch as the power handled is low, the transformer used can be the smallest obtainable.

Wiring is "point to point" for convenience. No particular precautions need be observed in wiring, other than to insure that the polarity of the filament is correct.

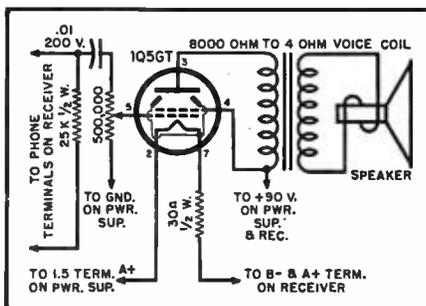The proper connections for the amplifier are shown in the diagram. When these connections are made as shown, the filament voltage and grid bias are automatically obtained.




Wiring diagram of one-tube audio amplifier. This unit, when built, can be used in conjunction with the one-tube receiver covered in last month's issue, page 66.

trolled by means of a 500,000 ohm potentiometer in the grid circuit of the tube.

The 90 volts for the plate and screen of the tube as well as the filament voltage are obtained from the power supply described in last month's pages. The published characteristics for this tube call for a grid bias of -4.5 volts. By using the voltage drop across the filament of the tube in the receiver,

Over-all view of audio amplifier.

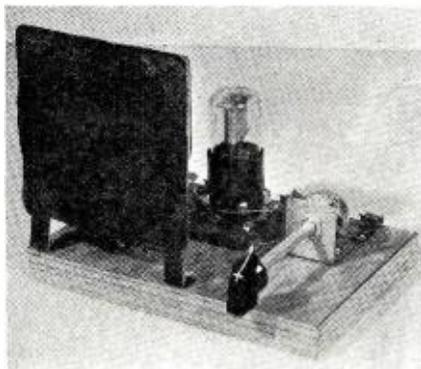

POWER SUPPLY FILTERS

The function of a power supply filter is to reduce the a.c. ripple present in the output of the rectifier to a point where it produces no adverse effects in the equipment fed by the filter. The degree of filtering required varies widely—a microphone preamplifier requires much more filtering than a power amplifier, since any ripple in the preamplifier will be amplified in the successive stages.

Filters may be divided into two general categories—choke input and condenser input. Each has its own good and bad points, and we can take advantage of the good points for certain specific applications. Resistance input filters are occasionally used where the current drain is low and limited filtering is required, but for the most effective filtering, combinations of chokes and condensers are used.

Condenser input filters are most widely used in low power applications. Their principal characteristics are high output voltage and poor regulation. The output voltage of a condenser input filter will closely approach the peak value of the rectified voltage, under no-load conditions, but drops off quite rapidly as the load is increased.

Voltage regulation of a condenser input filter may be improved by increasing the capacity of the input condenser. However, increasing this capacity increases the peak rectifier current, and care must be taken to

see that this peak current does not exceed the rating of the rectifier tube. Usually the tube manual will indicate the maximum capacity which may safely be used with a condenser input filter. Values up to 40 μ fd. are in common use.

The input condenser must have a working voltage rating at least equal to the peak value of the rectified a.c., and preferably a little higher for safety.

Choke input filters are characterized by low output voltage and good voltage regulation. If the input choke inductance is at least the critical value, the output voltage will not exceed .9 of the r.m.s. voltage input to the rectifier. The critical inductance in henries is obtained by dividing the load resistance (in ohms) across the filter output by 1000. The load resistance may be computed by dividing the output voltage from the filter network by the total current drain through the filter. If the input inductance is less than this critical value, the filter begins to take on the characteristics of a condenser input filter. Usually a choke input filter is designed so that the input choke has an inductance of approximately twice the critical value. This is called the optimum value.

Choke input filters are usually used in relatively high power applications where good voltage regulation is important or where the load is variable. With a constant load, condenser input filters are satisfactory, and in general are cheaper.


PHOTOCELL CONTROL UNIT

One of the most interesting pieces of equipment for the experimenter is a photoelectric unit. A device of this type may be used for a wide variety of purposes, such as controlling garage doors, burglar alarms, smoke detectors, and a myriad of similar applications.

There are many different types of photoelectric control circuits, each having its particular advantages and disadvantages. For most uses, though, a simple device consisting of a photocell connected to a single stage of amplification will be satisfactory.




With the unit pictured, the beam

Fig. 1. Schematic diagram of photocell control unit. All parts are readily available.

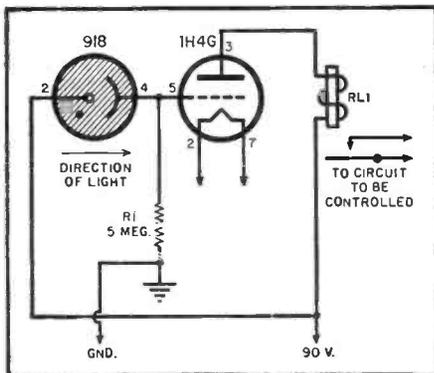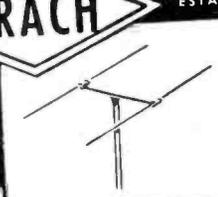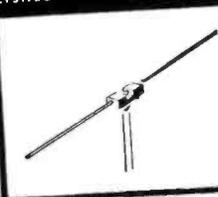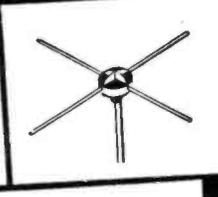

May, 1947

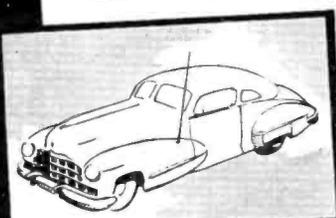
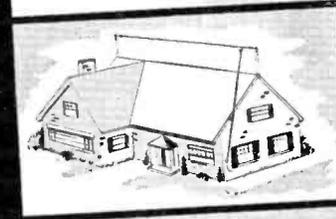
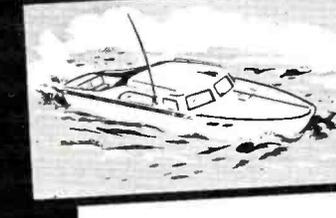

ESTABLISHED 1906

ANTENNA SYSTEMS

for USERS

of PRIVATE BRANDS

We manufacture the following, under private labels and trademarks:

AUTOMOBILE ANTENNAS . . . every variety, including types that can be raised and lowered from inside the car.

RESIDENTIAL ANTENNAS . . . AM and FM, for homes, stores and multi-family buildings. Complete lines of noise-reducing systems incorporating latest patented developments of coupling transformers.

FM, AM and TELEVISION . . . Dipoles with or without reflectors, folded dipoles, turnstile, radiating types and other combinations for roof, sidewall and other mountings.

MARINE ANTENNAS . . . Collapsible and transmitting types for every purpose.

For **POLICE and other mobile units** . . . roof-top antennas for ultra-high frequencies.

WE INVITE INQUIRIES AND CONSULTATIONS.

L. S. BRACH MFG. CORP.

200 CENTRAL AVENUE NEWARK, 4 N. J.



WORLD'S OLDEST AND LARGEST MANUFACTURERS OF RADIO ANTENNAS AND ACCESSORIES



RCA Institutes, Inc.

Offer thorough training courses in all technical phases of Radio and Television

WEEKLY RATES DAYS—EVENINGS

VETERANS: RCA Institutes is approved under G. I. Bill of Rights

For Free Catalog write Dept. RN-47
RCA INSTITUTES, Inc.
A Service of Radio Corporation of America
75 Varick St., New York 13, N. Y.

RADIO SERVICEMEN!

EXPERIMENTERS—INDUSTRIALS

Send today for our new illustrated 1947 CATALOG of RADIO and ELECTRONIC PARTS and SUPPLIES. Just off the press! Write today!

Illustrated Catalog FREE

NATION-WIDE RADIO.

Dept. A, 572 W. Randolph St., Chicago 6, Ill.

WAR SURPLUS

NATIONALLY ADVERTISED—3000 VDC 50 mmfd. type 850, silver Ceramic. 10 for \$1.39

NATIONALLY ADVERTISED—metal-encased, oil impregnated, tubular condensers 600 VDC mfd. 25 for . . . \$2.19 100 for . . . \$8.49

CRYSTALS—Sylvania type 1N21, high frequency, plug-in receiving (makes a fine meter rectifier). 2 for98c

JACKS—Signal Corps type JK34A, short phone jack. 10 for98c

SILVER CERAMIC—Erie type, feed-thru Condenser, 1000 volts 50 mmfd. 100 for . . . \$1.49

NATIONALLY ADVERTISED—10,000 Ohm, 10 Watt, type AB, cement coated. 25 for \$2.19 100 for \$8.49

Write for circular listing many other outstanding values. **SPECIAL DISCOUNTS** on quantities. Shipping extra.

Erie Supply Co. 88 Exchange St. Rochester, N. Y.

DEALERS! SERVICEMEN!
These VALUES mean PROFITS for YOU!

All merchandise offered below is BRAND NEW, and FULLY GUARANTEED. Our enormous stocks and facilities enable us to give you IMMEDIATE DELIVERIES. All merchandise subject to prior sale.

TERRIFIC BUY FOR P.A. MEN!
 Astatic R-3 Crystal Handmade, with 6-ft. R.C. mike cable..... **\$4.50**



WILLARD 2-VOLT STORAGE BATTERY
 Exact replacement for GE portables—brand new. Each..... **\$2.75**
 Willard 6 volt (3-cell) storage battery, brand new..... **\$7.95**
 Magnetic Pickup..... **\$2.20**
 Shure Magnetic Cutting Head Special..... **\$1.95**

TELEGRAPH KEY
 Sig. Corps J-38..... **59c**
7-PRONG 2-VOLT RADIO VIBRATOR for Portable and Farm Sets Replacement for GE LB 530..... **\$1.65**
KIT OF 100 ASSORTED CARBON RESISTORS RMA color coded, 1/4 watt..... **\$1.44**

LOOK AT THESE PM SPEAKER VALUES!
 Alnico 5 4" PM..... **\$1.30**
 Alnico 5 5" PM..... **1.45**
 Alnico 5 6" PM..... **1.95**
 Alnico 5 8" PM..... **3.25**
 450 ohm 4" Dynamic..... **1.59**


MAGNAVOX "FP" FILTER CONDENSERS
 8 mfd 500 volts..... **45c**
 16 mfd 500 volts..... **65c**
 8-8 mfd 500 volts..... **70c**
 40-20-20 mfd 150/150/25 V..... **40c**

MODEL HS23 HEADPHONES
 2000 ohm pair..... **\$1.85**
 600 ohm pair..... **2.25**
ADAPTER, for connecting 600 ohm sets to hi-imp..... **35c**

METER SPECIAL!
 3" Square AC Milliammeter 0-1000 mils..... **\$1.95**

BRAND NEW 6-TUBE SIG. CORPS RECEIVERS BC-453-B series

SEASON'S BEST BUY!
 Tubes alone worth total cost! All-Aluminum Aircraft receivers, 5"x8"x12 1/2". Weight 6 1/2 lbs. Black wrinkle enamel finish.
 Tuning range: 3 to 6 Mc. Tubes: 1-12SK7, 12K8, 12SK7, and 12A6. Power required: 250V @ 50 Ma and 25.2V @ .45A for heaters (easily rewired for 12.6V @ .7A). Hi and Low impedance output. Voice, MCW and CW reception. EACH SET COMPLETE WITH ALL TUBES IN SOCKET, less dynamotor..... **\$5.95**
 Same as above, but tuning range: 6 to 9.1 Megacycles..... **\$5.95**

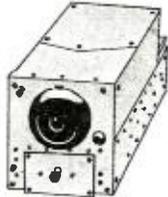

MOTOR AND PICKUP COMBINATION
 Alliance Motor and Astatic curved arm pickup. Specially priced comb. 456 KC IF TRANSFORMERS double tuned, square can..... **\$5.45**

VOLUME CONTROLS
 25M ohm..... **40c**
 50M ohm..... **40c**
 100M ohm With Switch..... **40c**
 250M ohm..... **40c**
 500M ohm..... **40c**
 1 Megohm Less Switch..... **28c**
 2 Megohm..... **28c**

SPDT SLIDE SWITCH, with additional phono-radio name plate..... **15c**

PHONE PLUGS
 PL-55 Standard 2 circ phone plug..... **16c**
 PL-54 same but short barrel..... **16c**
 PL-68 3-circ mike plug..... **16c**
 JK-28 portable jack for PL-54 plug..... **12c**
MIDGET CONNECTORS 4 prong, molded composition, male & female, set..... **12c**
MIDGET TUNING CONDENSERS .00014 mfd, isolantite insulation, long shaft..... **39c**

TOGGLE SWITCHES
 SPDT..... **29c**
 DPDT..... **35c**
1-MFD 1000 VOLT CD OIL-FILLED FILTER CONDENSER in metal case, with porcelain insulation..... **51c**
3-CIRCUIT PANEL JACK, (fits PL68 plug and standard mike plugs)..... **14c**
50 MMFD TUNING CONDENSER, isolantite insulation..... **75c**
22 1/2 VOLT "B" BATTERIES with leads..... **35c**
MIDGET VISE—SPECIAL!..... **\$2.19**
 PLEASE INCLUDE 25% deposit with order—Balance C.O.D.

G & G RADIO PARTS SERVICE
 53 VESEY STREET - NEW YORK 7, N.Y.

"More than 10,000 Satisfied Dealers and Servicemen since 1940!"

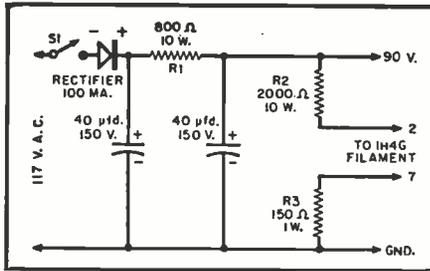


Fig. 2. Schematic diagram of power supply to be used with photocell unit. The power supply covered in last month's issue, page 67, can be easily adapted for this purpose.

from an ordinary two cell focusing flashlight will cause the relay to trip from a distance of over twenty feet. For operation over greater distances, a stronger light may be used. One of the ordinary sealed beam units used for automobile headlights and foglights will permit operation over a distance of several hundred feet.

The entire unit is constructed on a piece of 5 by 7 inch plywood, although any piece of board will serve as well. The sockets for both the 918 photocell, and the 1H4G tube are mounted by means of wood screws and metal spacers, to enable the prongs to clear the base.


The power for the unit is furnished by the power supply described in the April issue of RADIO NEWS, with minor changes. For those who do not have this issue, the revised power supply is shown in Fig. 2.

The relay, RL₁ may be any sensitive relay that will close on a current of two ma. or less. The resistance is not important as several types ranging from 3500 to 9500 ohms give the same results. Many relays of this type are available at reasonable prices from surplus dealers.

Care should be taken in mounting the parts to orient the socket for the 918 tube so that the light will strike the inner curved surface of the plate. It is preferable to shield the phototube from extraneous light, and in this case a shield was made from a defunct electrolytic condenser can. The top of the tube was covered by black masking tape of the type used by photographers.

The unit may be made to operate

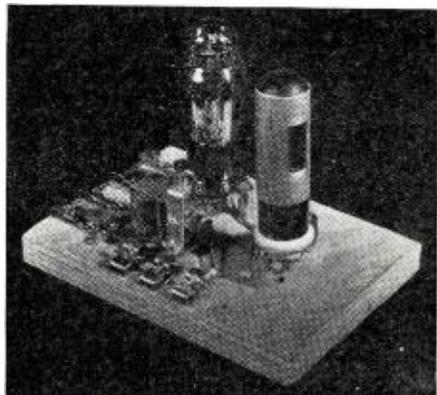Over-all view of completed photocell unit.



STANDARD BRAND TUBES AT MAXIMUM WHOLESALE PRICES

OZ4.....	\$1.04	12SK7.....	\$0.63
1A7GT.....	.83	12SQ7.....	.63
1H5GT.....	.70	24.....	.56
1LA6.....	1.53	25Z5.....	.63
1LN5.....	1.53	25L6GT.....	.70
1N5GT.....	.83	30.....	.63
3Q5GT.....	1.04	32L7GT.....	1.26
5Z3.....	.70	35L6GT.....	.63
6A7.....	.63	35Y4.....	.96
6F6G.....	.56	35Z5GT.....	.53
6N7.....	1.04	42.....	.53
7B7.....	.83	50L6GT.....	.65
7C7.....	.83	75.....	.53
7Z4.....	.83	80.....	.42
12Q7G.....	.56	117Z6.....	.99
12SA7.....	.63		

Many Other Types Available
 Send Us Your Requirements
 Export Tube Inquiries Promptly Acknowledged
 CABLE-ADDRESS-ALRAD



509 Arch Street — Philadelphia 6, Pa.
 Lombard 3-9225

The BUY of a LIFETIME


U. S. SIGNAL CORPS **5 Meter** ONLY \$ **3.49**
SHORT WAVE XMTRS (72.2 Mc)

XMTR and TUBE Only Less mks, Batteries and Antenna
 One 1 1/2 volt dry cell and 87 1/2 volts of B operates it. Just attach di-pole, key or mike, connect the batteries and it's ready to use. Signal Corps spec wired with silvered wire, mica condensers, and precision resistors. Highly stable circuit with Lo-Loss silvered inductance. (Adjustable paddler.) Schematic supplied. Converts easily to walkie-talkie and Ham bands. Weighs less than a pound. Shipped by express only. No C.O.D.'s. No Parcel Post. A sacrifice at only \$3.49. Postal or express money order or certified check.

NEWARK SURPLUS MATERIALS CO.

324 Plane St., Dept. N, Newark 2, N.J.

SEND STAMP FOR GIANT CATALOG!

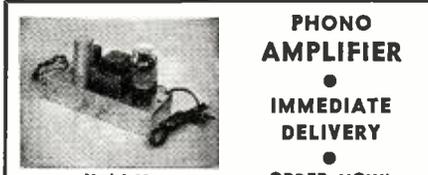

PHONO AMPLIFIER
 IMMEDIATE DELIVERY
 ORDER NOW!
 A SOLUTION TO YOUR AUDIO PROBLEMS
 A.C. Only—4 watts output. Tone and volume control. Wired and tested. Complete with 6J3, 6V6 and 80 type tubes.
 Unit Price **\$10.50**

SOUND PRODUCTS CO.
 80 MAIN STREET, WHITE PLAINS, N. Y.

RADIO

Technician and Radio Service Courses
FM and TELEVISION
 American Radio Institute
 101 West 63rd St., New York 23, N. Y.
 Approved Under GI Bill of Rights
 Licensed by New York State

MAY SPECIALS

100 Assorted Resistors 1/4, 1/2, 1 Watt..... \$ 1.98
 Postage Stamp Molded in Bakelite Mica .000175..... Each..... .05 1/2
 Loop Antennas, Retail for \$1.00..... Each..... .34
 Plastic Antennas 6"x5 1/2"x3 3/4"..... Each..... 1 ea
 Power Transformers: 50 M.A. 750V. C.T. 6.3V; 5V; B Mount Heavy duty..... \$1.98
 each, or 10 for..... 18.50
 Choice of: 6AG7 tubes or 6AC7 tubes..... Each..... 78
 These Net Prices Subject to Prior Sale
 Send for Our Monthly Bulletin Now
G. F. BEARD
 242 W Brookdale Fullerton, Calif.

either when light strikes the photo-tube or when the light is cut off. If operation is desired when the beam is broken, it will be necessary to use a relay that is normally closed with no excitation.

When construction has been completed, the power supply should be connected, and turned on. Care must be taken to observe the correct polarity in the filament connections of the 1H4G tube, or the unit will not operate. A flashlight or some other source of light should be placed close to the photocell tube. The relay will close when the light is turned on if everything is operating satisfactorily. An interruption of the beam should cause the relay to open.

In a brilliantly lighted room it may be necessary to shield the photocell by means of a box to exclude unwanted light. In any case, the only light hitting the photocell should come from the light source.

An interesting application for a unit of this type is the remote flashing of photo-flash bulbs. The relay may be used to control a flash bulb to illuminate unlighted areas, this remote bulb being set off by the flash of the bulb controlled by the camera.

RADIO QUIZ

How's your radio theory? If you miss any of the 10 questions below, you probably need to brush up a bit! Try your hand at answering these questions, then turn to page 183 and see how many you answered correctly. There is only one logical answer to each question. All questions refer to the diagram of a conventional speech amplifier shown on page 72.

The condensers referred to in questions 1, 2, and 3 are (a) coupling, (b) r.f. bypass, (c) filter, (d) a.f. bypass condensers.

1. Condensers C_5 and C_6 are (a), (b), (c), (d).
2. Condensers C_9 , C_{10} , C_{11} , and C_{12} are (a), (b), (c), (d).
3. Condensers C_3 , C_4 , C_7 , and C_8 are (a), (b), (c), (d).

The resistors referred to in questions 4, 5, and 6 are (a) grid, (b) cathode, (c) load, (d) bleeder resistors.

4. Resistors R_1 and R_2 are (a), (b), (c), (d).
5. Resistors R_2 , R_3 and R_4 are (a), (b), (c), (d).
6. Resistors R_1 and R_2 are (a), (b), (c), (d).

The transformers referred to in questions 7, 8, and 9 are (a) power, (b) interstage coupling, (c) r.f., (d) output transformers.

7. Transformer T_1 is (a), (b), (c), (d).
8. Transformer T_2 is (a), (b), (c), (d).
9. Transformer T_3 is (a), (b), (c), (d).
10. The type 80 rectifier is used to provide (a) plate, (b) heater, (c) bias, (d) a.v.c. voltage.



Radionic Equipment Co., Dept. 55RN
170 Nassau Street
New York 7, N. Y.

Please send me a FREE copy of your 1947 Catalog. I understand it has thousands of items illustrated, described and priced and will be a great help to me in my search for hard-to-find radio equipment. CHANCELLOR PORTABLE & PHONO RADIOS.

Name

Address

City State

RADIOS—PARTS & ACCESSORIES
PUBLIC ADDRESS
RECORD CHANGERS
TEST INSTRUMENTS—TUBES
AMATEUR & EXPERIMENTER SUPPLIES

RADIONIC
EQUIPMENT COMPANY

TRIBUNE THEATRE ENTRANCE
170 NASSAU ST., NEW YORK 7, N. Y.
PHONE WO2-0421 CABLE "CHANSLOR"

RADIO ENGINEERING!
COMPLETE Radio Engineering Course. Bachelor of Science Degree. Courses also in Civil, Electrical, Mechanical, Chemical, Aeronautical Engineering, Business Administration, Accounting, Secretarial, Science. 84th year. Enter Mar., June, Sept., Jan. School now filled to capacity. No applications can be accepted until further notice.
TRI-STATE COLLEGE 1657 College Ave. ANGOLA, INDIANA

RADIO TUBES
Most Critical Types in Stock
1LA6, 25Z5, 7A8, etc.
Brand New in Sealed Cartons
100% Guaranteed
Repairmen and Dealers. Write For List at Trade Discounts
RADIO-EXPERTS
178 E. 33rd Street, Dept. R, Paterson 4, N. J.

PREMIER SIGNAL GENERATOR



NEW! EXCLUSIVE! BAND SPREAD DIAL. AWAY OUT IN FRONT AND UP ON TOP . . . this brand-new PREMIER SIGNAL GENERATOR is in demand from COAST to COAST.

CHOCK-FULL of super-features usually found only in the most expensive units. PREMIER is an outstanding value.

NO OTHER low priced signal generator has the famous MICROMASTER BAND SPREAD DIAL. Total scale length approximately 60 inches. Spring loaded drive eliminates all backlash, and the result is split-cycle tuning.

BANDS: 75 Kc to 50 Mc on FUNDAMENTALS. 45 to 150 Mc on powerful 3rd harmonic.

400 CYCLE Pure sine wave Audio Signal. **FOUR STEP**, ladder type, accurately calibrated Attenuator.

COMPLETE LINE FILTER.

TRIPLE SHIELDING throughout. Leakage is reduced to the absolute minimum.

ACCURACY. Better than 1%.

In stock now for immediate delivery.

\$54.50 Complete with coaxial cable.
NET

Manufactured by
Premier Electronic Laboratories

RADIONIC
EQUIPMENT COMPANY

TRIBUNE THEATRE ENTRANCE, DEPT. 55RN
170 NASSAU ST., NEW YORK 7, N. Y.
PHONE WO2-0421 CABLE "CHANSLOR"

AMAZING NEW
Pocket or Purse Size RADIO!

SMALL AS A PACK OF CIGARETTES! Weighs only a few ounces—Beautiful black chrome plastic case. Uses new crystal diode. Hi-Q-slide dial. No tubes, batteries or electric "plugs" required! Receives local broadcasts and

GUARANTEED TO PLAY when used according to instructions sent with each radio! You can use it at home, in many offices, hotels, cabins, in bed, etc.—lots of fun—real entertainment!

SEND ONLY \$1.00 (cash, money order, check) and pay postman \$2.99 plus delivery fees on arrival or send \$3.99 for postpaid delivery. Complete as shown ready to play with self contained personal phone. For gifts—children will love it—grown-ups too! An exceptional value—order yours and enjoy the many good radio programs coming! Don't be without your Pa-Kette Radio another day! (All foreign orders \$5.00 U.S. cash.)
PA-KETTE ELECTRIC CO., Dept. RN-5, Kearney, Neb.

▶ JOBBERS-DEALERS ◀

AND SERVICEMEN

If you need Tubes—We've Got 'Em

Send us a trial order. This will convince you we merit your patronage, based on low prices, quick delivery and fully guaranteed tubes.

The following is a sample of our bargains always in stock:

Type	Each	Lots of 10 Each	Type	Each	Lots of 10 Each
1H5GT	55¢	55¢	7B7	50¢	40¢
1U5	39¢	35¢	7C6	50¢	40¢
1V	50¢	50¢	7Y4	50¢	35¢
5U4G	50¢	40¢	7X7	50¢	40¢
5W4GT	50¢	45¢	7AF7	45¢	40¢
5Y3GT	40¢	37¢	XXL	50¢	40¢
6A7	52¢	50¢	12A9GT	50¢	49¢
6A8GT	52¢	44¢	12J7GT	50¢	42¢
6AB7	59¢	55¢	12Q7GT	53¢	39¢
6AC7	59¢	55¢	12SA7GT	50¢	39¢
6C5	50¢	42¢	12SQ7GT	50¢	39¢
6BA6	75¢	50¢	12SK7GT	50¢	40¢
6F6GT	45¢	40¢	24A	50¢	39¢
6H6	48¢	44¢	25L6GT	68¢	50¢
6J5GT	50¢	50¢	25Z5	63¢	50¢
6K6GT	59¢	39¢	25Z6GT	62¢	51¢
6K7	60¢	50¢	27	42¢	38¢
6K7GT	60¢	44¢	35L6GT	60¢	50¢
6K8	60¢	54¢	35Z3	65¢	60¢
6L5G	65¢	40¢	35Z6GT	65¢	42¢
6SA7GT	60¢	45¢	43	90¢	60¢
6SF7	65¢	55¢	45	66¢	50¢
6S7	50¢	45¢	47	92¢	55¢
6SK7	55¢	48¢	50L6GT	65¢	50¢
6SK7GT	60¢	38¢	56	51¢	45¢
6SL7GT	60¢	52¢	75	67¢	44¢
6SQ7	50¢	45¢	77	45¢	39¢
6SQ7GT	50¢	45¢	80	40¢	38¢
6U7G	60¢	48¢	84/6Z4	58¢	45¢
6V6GT	83¢	50¢	117Z3	85¢	60¢
6X5GT	65¢	45¢	12AT6	75¢	45¢
7A4	69¢	40¢	12BA6	75¢	45¢
7B5	50¢	40¢	12BE6	75¢	45¢
32L7GT	90¢	80¢	50B5	54¢	42¢

ALL TUBES FULLY GUARANTEED

Get Our Special Price List on TRANSMITTING TUBES

EXTRA SPECIAL BUYS

1625 Transmitting beam power, amplifier same as 807 except 12.6 volt filament medium pin base. **19c each**

1629 Tuning indicator — Tri — (Magic eye) Tube **29c each**

829 Push-pull twin-unit beam power amplifier Tube **\$2.25 each**

Buss H.C.M. fuse holder. **15c each**

Western Electric thermistor No. D-163903. **50c each**

Sprague—20 mfd—20 volt FP plug-in type condenser with bracket. . **15c each**

Standard 6 volt 4 prong, auto vibrator. **\$1.19 each**

Complete Assembled & Tested 2 Tube Wireless Phono Oscillator, Less Tubes. . **\$3.95**

Write, Wire, or Phone for our Special Quantity Prices 25% deposit on all orders, balance C.O.D., F.O.B. N. Y.

SENCO RADIO INC.
96 WARREN ST., N. Y. 7, N. Y.
TEL. Cortlandt 7-6065

Within the Industry

(Continued from page 34)

vertising, the sale of radio receiving tubes to equipment manufacturers and to the distributor trade will be under the direction of Ernest Kohler Jr., Sales Manager, while Curtis R. Hammond, newly appointed Distributor Sales Manager, is in charge of all *Raytheon* renewal tube sales activities pertaining to jobber distribution of receiving, transmitting, and special purpose tubes. Mr. Hammond will continue his activities in connection with receiving tube equipment sales and the company's sales engineering service.

RAY R. HUTMACHER has resigned as assistant general sales manager of *Maguire Industries'* Electronics Department to form his own firm of manufacturers' representatives.

The new organization, known as *The Salecrafters, Inc.*, will have its headquarters at 510 North Dearborn Street, Chicago. The company will handle radios and electronic lines on a national or territorial basis.

Mr. Hutmacher has been connected with the radio industry for 21 years and is well known in the trade.

AMALGAMATED RADIO TELEVISION CORP. recently announced the removal of their plant and offices to a new location.

The company will be located in Mount Vernon, New York, at 152-4 MacQuesten Parkway South.

ARCH SAMUELSON is the new Sales Manager of the *Operadio Manufacturing Company's* Commercial Sound Division. Mr. Samuelson was formerly the Mid-West District Manager. His experience in sales, distribution, and engineering will complement *Operadio's* extensive sales program.



Appointment of two new district managers was also announced. J. F. McCraigh, formerly chief of the company's Engineering department, will take the post of West Coast District Manager, while the new Southeastern District Manager for *Operadio* will be Fred H. O'Kelley of Atlanta, Ga.

AUSTIN C. LESCARBOURA, one of radio's old-timers and a publicity and advertising consultant of Croton-on-Hudson, New York, has been awarded the coveted order of "Officier de l'Instruction Publique," according to word recently received from the French Embassy.

The award is made in recognition of the technical services rendered to France in the past.

Mr. Lescarboursa is the former Edi-

Opportunity Knocks

Build Your Own Business NOW!



With TRADIO . . . the radio FUNCTIONALLY DESIGNED for coin operation in Hotels, Motels, Stopovers, Clubs, Hospitals, Stations, etc. Big Earnings . . . Steady Income . . . No Clock To Punch . . . Full or Part Time!

• QUANTITY DELIVERIES DAILY

Get In On The Ground Floor In America's Fastest Growing Industry While It Is Still Young!

• ONLY SMALL INVESTMENT NEEDED

Send For Complete Information Today . . . No Routes Sold.

WRITE **TRADIO, Inc.** Asbury Park, N. J. TO **RIGHT NOW!**

Anyone Can Build Our NEW MODEL S-5C RADIO

Our model S-5C uses the universally accepted superheterodyne circuit containing the following tubes: 12SA7, 12SK7, 12SQ7, 50L6, 35Z5 and tunes from 550 Kc. to 1600 Kc. Model S-5C . . . complete kit less tubes. With Bakelite cabinet and brand new illustrated instruction sheet, showing simple, detailed, step-by-step diagrams.

OUR INSTRUCTION SHEET COVERS EVERYTHING

• Pictorial Diagram • Schematic Diagram • Photographs • Step-by-Step Wiring Instructions Available at your local distributor or write to us for catalog.

Other Models Available

RADIO KITS COMPANY
120 Cedar Street New York 6, N. Y.

REPAIRMEN AND MANUFACTURERS GUARANTEED! RADIO TUBES!

Miniature 3 Way Portable Kits 1R5, 1T4, 1S5, 3Q4, 117Z3.

Miniature 12 Volt Kits
12BE6 Replacing 12SA7
12BA6 Replacing 12SK7
12AT6 Replacing 12SQ7
35W4 Replacing 35Z5
50B5 Replacing 50L6

G.T. 12 Volt Kits
12SA7 12SQ7 12SF7 12A6 or 50L6 35Z5

LARGE QUANTITY OF FOLLOWING TYPES
3Q5 6SK7 6K6 6F6 6G6 6P5 6SJ7 32L7

Send list of requirements of tubes not listed

LE-HI ELECTRICAL COMPANY
660 Broadway Newark 4, N. J.
HUMBOLDT 5-3530 Dept. RN-100 HUMBOLDT 5-3531

PRACTICAL TECHNICAL TRAINING FOR YOU

Specialize in Electronics, Radio, Electricity, Refrigeration, Heating and Air Conditioning, or Welding. Prepare in one year for position as Technician, or in two additional years secure your B.S. Degree in Electrical Engineering with major in Machinery or Electronics.

Write for booklet "Career Building"

MILWAUKEE SCHOOL OF ENGINEERING
"A Technical Institute"

RN-547 N. Broadway and E. State, Milwaukee, Wis.

Send for Our Periodical Bulletins of Real Guaranteed Values

WHOLE-SALE RADIO SUPPLIES

RADIO & TELEVISION EQUIPMENT CO.
207 Oak St. Santa Ana, Calif.
709 Cherry St. Long Beach, Calif.

tor of *Popular Science Monthly*, *Scientific American* and various trade and technicals journals. He is the author of several books and a frequent contributor to technical journals.

EUGENE B. LUCAS was recently appointed Sales Manager of *Air King Products Co., Inc.* Mr. Lucas will head sales of *Air King* radios through the company's nationwide distributor set-up.



Prior to this advancement he was Advertising and Sales Promotion Manager for *Air King Products Co., Inc.*, which is a division of *Hytron Radio and Electronics Corporation*.

Before joining the company in April of 1946 Mr. Lucas was Sales Manager of the Cabinet Division of the *Plymold Corporation* of Lawrence, Mass. and has served with such manufacturers as *General Electric*, *Colonial*, and *Bendix*.

-50-

MIDGET TRANSMITTER-RECEIVER

OF INTEREST to radio amateurs in the United States is a new British-made transmitter-receiver which is only a little larger than a cigarette package.

The inventor, Michael Kasia, is shown using the unit in the top photograph, while comparative size of this midget transmitter-receiver is shown in the lower picture.

Now being manufactured commercially under the tradename "Tele-Radio" this unit utilizes the miniature tubes adapted from those used in radar-controlled shells during the war.

In use the transmitter-receiver can be carried in the breast pocket of a man's suit while the power pack may be slipped into the side pocket. The aerial is sewn inside the lining of the coat. The small microphone can be fastened underneath the lapel of the coat, if so desired.

-50-




May, 1947

Clark AMPLIFIERS Hold Their Audiences!



Men who sell, rent and install public address systems know that failures are costly. So they demand dependability as well as performance.

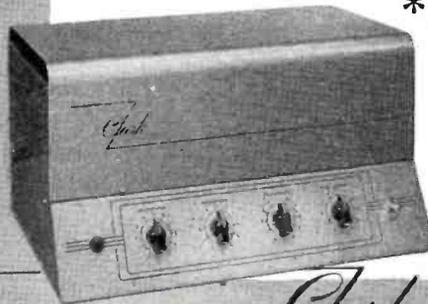The Clark PA series of 10, 20 and 30 watt amplifiers are cleanly engineered with oversize power components and terminal strip mountings as used in broadcast station speech amplifiers. Yet Clark PA'S are so moderately priced they have become the outstanding values in their field.



* The new Clark PA-20a 20 watt Amplifier with stepped-up performance and an attractive new front panel design is now available at your Jobber's. Ask for a demonstration. You will like its crisp, ear-pleasing performance and the built-in safety factor that assures you of dependable service.

For engineering details write for Technical Bulletin No. 137.

Clark Radio Equipment Corp.


4636 RAVENSWOOD AVENUE • CHICAGO 40, ILLINOIS



The sellers' market has become a buyers' market... however, well-established manufacturers are still going strong... we, at HALLDORSON, are proud of our unbroken record of supplying industry with the finest since 1913... our new and more complete line of transformers is worthy of your consideration.

JOBBER: Get on our mailing list today!

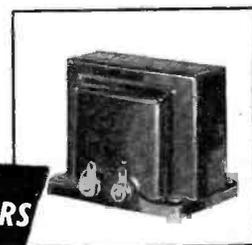THE HALLDORSON COMPANY
4500 Ravenswood Avenue • Chicago 40, Illinois



HALLDORSON Vacuum Sealed TRANSFORMERS

177



Get your hat . . . follow the crowds to Hallicrafters booth at the parts show. Get the details on Hallicrafters advanced developments in high frequency, short wave communications equipment. Hear all about the Gatti-Hallicrafters spectacular radio-equipped expedition to the Mountains of the Moon. This scientific safari, based on Hallicrafters-built mobile radio equipment, will spread the name and fame of "the radio man's radio" around the world. All the dope on this exciting adventure at Hallicrafters show headquarters.

hit the trail!



**hallicrafters
EXHIBIT
BOOTH 86**



hallicrafters

THE HALLICRAFTERS CO., MANUFACTURERS OF RADIO AND ELECTRONIC EQUIPMENT, CHICAGO 16, U. S. A.

Ham Ticket in 30 Days

(Continued from page 56)

times whether you recognized the sound or not. We want to burn this proper association right down into your subconscious so deeply that you can never forget or confuse it.

After you have spent your hour and a quarter a day for three days looking first at the "dit-dah" combination and then at the letter, try three more days of reversing the process. Look first at the letter and see if the proper "dit-dah" combination does not come to you automatically. Check to see if you are right and then continue to say the combination while looking at the letter. By the end of six days you should be able to pick up any card at random, paying no attention to which side was up, and instantly call off what is written on the opposite side before turning it over.

When you reach this point, it is time to call in an assistant. It can be the wife, mother, son, daughter, or anyone else you can persuade to give you a little time. The first evening simply have them keep going through the cards, combination-side up, reading aloud the "dit-dahs." As each is read to you, call aloud the name of the letter, number, or symbol for which the combination stands. At the same time, write that letter down. Do not omit this: *Write that letter down;* and write down every single bit of copying you do from here on in. Never "copy in your head." Write each letter down just as quickly as you are able after hearing the combination.


Spend a half hour of the next evening copying down all the two, three, and four letter words you find in a newspaper column or similar piece of writing. Write the words on separate pieces of paper, and write the correct "dit-dah" combinations on the back of each piece. For example, on one side of one slip would appear the word "and." On the opposite side would appear the following:

Dit-Dah
Dah-Dit
Dah-Dit-Dit

For the remaining forty-five minutes of the period, have your assistant read over the combinations aloud. He should read each group in a single breath, with a slight pause after each combination that makes up a single letter. You should write down each letter as he says it, and then you should say aloud the complete word you have copied so that he can check you.

For the next evening add to this list several common letter groups that you have picked at random from English words. For instance, the word "carton" could be broken down with "car" on one piece of paper and "ton" on the other; or "caution" could be broken into "cau" and "tion." Mix these in with the complete words so that you will never be sure whether

NOW AVAILABLE FROM STOCK!

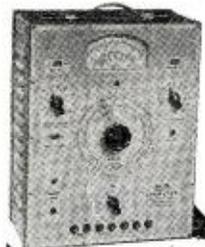

SOLAR

Model CF-1-60

EXAM-ETER

With Exclusive Patented Solar "Quick-Check" Circuit. A sturdy, reliable instrument designed to simplify and speed up electronic servicing.

- Checking of Capacitors Under Actual Operating Conditions.
- Capacitance—10 mmf. to 2000 mf. mfd.
 - Power Factor—0 to 55 per cent.
 - Leakage Current—At Voltages Up to 550 Volts.
 - Insulation Resistance—3 to 10,000 Megs.
 - Resistance—100 Ohms to 7.5 Megs.
 - DC Vacuum Tube V.M.—0-550 Volts
 - AC Vacuum Tube V.M.—10 to 50 Volts.
- Complete with Tubes and Test Leads, Ready to Operate. **\$59.70**

ADSON RADIO CO.
221 FULTON ST., NEW YORK 7, N. Y.

FREE CATALOG

Send for free catalog and prices of hard-to-get Radios, Radio Tubes, Radio Parts, Pickups, Motors, Condensers, Tube Checkers, Volt and Ohm Meters, Signal Generators, Signal Tracers, etc.

FLANAGAN RADIO CORP.

Wholesale Distributors

N. E. Cor. 7th & Chestnut Sts.
Phila. 6, Penna.—U. S. A.

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.



ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY

4711 SHERIDAN ROAD, CHICAGO 40, ILLINOIS

CORRESPONDENCE COURSES IN RADIO and ELECTRICAL ENGINEERING

ELECTRICAL ENGINEERING Get Good Grasp of wide electrical field. Prepare yourself at Low Cost, for secure future. Modern course. So simplified anyone can understand quickly.

RADIO ENGINEERING Extra fine course in radio work. Trains you to be super-service man, real vacuum-tube technician. Servicemen needed badly. Diploma on completion. Many Graduates earning big pay.

WRITE Send postcard for Free Copies of \$25 either school catalog. Full details, all 94 Courses about deferred payment plan, experimental kits, etc. Lincoln Engineering School, Box 931-R1 6, Lincoln 2, Nebr.

LINE VOLTAGE BOOSTER

Protect your equipment against low line voltage. Plug in the new VARI-VOLTER and eliminate loss of power. Handles up to 1000 watts, 115 volts, 50-60 cycles. Complete in cabinet, ready to operate. \$19.95 F.O.B.

GAMMA ELECTRIC COMPANY

1523 41st Street Brooklyn 18, N. Y.

RADIO NEWS

CLEAN ACCURATE HOLES




cut in radio chassis

Greenlee Punches make this tough job easy. No reaming, filing or tedious drilling. Tool has three parts: *punch* cuts through chassis, *die* supports metal to prevent distortion, *cap screw* is turned with wrench to cut holes $\frac{3}{4}$ " to $3\frac{1}{2}$ ". Ask your radio supply or electrical jobber or write for folder and prices. Greenlee Tool Co., 1885 Columbia Ave., Rockford, Illinois.

WRITE FOR FREE FOLDER S-119 

REGISTERED TOOLS
GREENLEE
FOR THE CRAFTSMAN

CRYSTAL SELECTOR

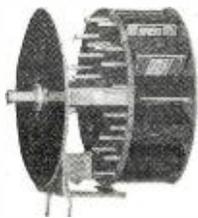

Accommodates one to twelve crystals permitting instant selection of any one.
Designed to hold popular 243 Type crystal.
One-hole mounting.
Sturdy construction gives long life and simple design permits easy replacement of parts.
Can be purchased with or without crystals.
PRICE without crystals **\$4.25**

See this sheet for suggested crystal kits and kit price.

CRYSTAL SETS FOR "VFO" OR CRYSTAL SELECTOR

Sold only in kit form for "VFO" or Crystal Selector

All crystals supplied on fundamental frequencies from 3500 to 9000 KC

KIT A Twelve precision crystals for operation in "VFO" with output on 20 meters but frequencies spotted to fall consecutively 12 KC apart on 10 meter band.

KIT B Twelve precision crystals to double to 20 meter phone band giving complete coverage of band in 8 KC steps.

KIT C Twelve precision crystals spaced consecutively 12 KC apart giving complete coverage of 40 meter band.

KIT D Twelve precision crystals spaced 12 KC apart giving complete coverage of 75 meter band.

KIT E Your choice of any twelve crystals from 3500 to 9000 KC in amateur bands.

KIT PRICE

Price of kit when purchased **\$18.50** for Crystal Selector or "VFO"

Send in your name for our mailing list.

RADIO EQUIPMENT DISTRIBUTORS

312 W. Pico Blvd., Los Angeles 15, California

what you are copying should spell out a complete word or not. Keep going over this list until your errors are few and far between, always urging your assistant to speak the combinations as rapidly as he can do so and still keep proper spacing. *Do not forget to write everything down.*

At the end of the second week you are ready to graduate to your receiver that can be used for code reception, one that produces an audio note with a c.w. signal, that is. Tune across one of the ham bands—probably forty meters would be best in the daytime, eighty at night—until you find a station calling "dah-dit-dah-dit dah-dah-dit-dah." Listen closely, and you will find that he will repeat this several times and then will send "de" or "v" and will next sign his call. In all likelihood, this will consist of the letter "W," then a numeral from 1 through 0, and finally a two-or three-letter combination of letters. He will repeat his call three or more times and then will start calling "CQ" again. This whole process will likely be repeated from three to six times before he finally sends "AR" or "K" and starts listening across the band for an answer. If you like, you can listen with him. The station calling will keep repeating his call for about a half-minute or more and then will send "de" and sign his own call several times.

Try to get each call correctly the first time you hear it. Spend two or three evenings doing nothing but copying calls. They make good practice because they include both letters and numbers, because they are repeated, and because each letter must be copied for itself alone. There is no context to help you. Next, try to find a station sending slowly and clearly and try to copy him solid. Do not worry about it if you miss a letter now and then. Just leave it out and go right on with the next letter. Keep at it, making no attempt to read what you are writing down until you finish. When you do try to read it, do not forget that hams use many abbreviations. For instance, weather is "wx"; signals, "sigs"; crystal, "xtal," etc.

In addition, try to copy W1AW every night Monday through Friday at 10:00 p.m., EST, on 3555, 7145, 14,150, and 28,060 kilocycles. The first ten minutes of these transmissions are sent at fifteen words per minute, the next at twenty, etc. When you can copy fifteen words a minute solid copy, you are ready to take the examination. This allows you a two-word-per-minute leeway for the excitement, strange surroundings, etc., of the examination. Listen to W1AW whenever you can, and spend the remaining part of your hour and a quarter each evening copying on the ham bands, *being sure to write everything down.*

By this time you should find you are having trouble in forgetting the code. By that I mean that you will catch yourself unconsciously translating signs and newspaper headlines into

FREE BOOK SHOWS SHORT CUT TO CODE SPEED



For Amateur or Commercial Radio

ENDORSED BY CHAMPIONS

Qualify at home, in spare time, by easy, simplified system. You can learn code or gain greater speed and skill in sending and receiving by the same system that has made code champions and radio telegraph experts. FREE BOOK OF FACTS explains Course. It's absolutely free. Rush your name for it today.

CANDLER SYSTEM CO.
Dept. 2-E, P. O. Box 528 Denver, Colo.

QSY WITH PRs


TYPE Z-3
PR
QUARTZ CRYSTAL FREQ-KC
PETERSEN COUNCIL BLUFFS IOWA
RADIO CO. MADE IN U.S.A.

Heard on phone bands these days: "Sorry, old man, an S9 plussity-plus is kicking you all over the place. Can you move a few kay-cees lower?" The answer to that is: "Sure can!" You will enjoy all the advantages of having "your spot" with crystal control, and yet dodge QRM if you buy three PRs. Spot your main frequency . . . get PR Precision CRYSTALS, say 7 kcs. each side of your spot. You can get PRs for the EXACT FREQUENCY YOU WANT (INTEGRAL KILOCYCLE) WITHIN AMATEUR BANDS, AT NO EXTRA COST. See your jobber! All PRs are unconditionally guaranteed.—Petersen Radio Company, Inc., 2800 West Broadway, Council Bluffs, Iowa. (Telephone 2760).

10 Meters—PR Type Z-5.....\$5.00
20 Meters—PR Type Z-3..... 3.50
40 and 80 Meters—PR Type Z-2..... 2.65

PR Precision CRYSTALS

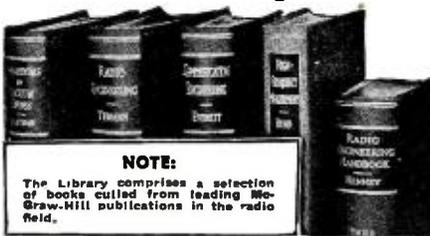**NOW—A REALLY HIGH-POWERED—
Radio Engineering
Library**



NOTE:

The Library comprises a selection of books culled from leading McGraw-Hill publications in the radio field.

- especially selected by radio specialists of McGraw-Hill publications.
- to give most complete, dependable coverage of facts needed by all whose fields are grounded on radio fundamentals.
- available at a special price and on easy terms.

THESE books cover circuit phenomena, tube theory, networks, measurements, and other subjects—give specialized treatments of all fields of practical design and application. They are books of recognized position in the literature—books you will refer to and be referred to often. If you are a practical designer, researcher or engineer in any field based on radio, you want these books for the help they give in hundreds of problems throughout the whole field of radio engineering.

5 VOLUMES, 3559 PAGES, 2558 ILLUSTRATIONS

1. Eastman's FUNDAMENTALS OF VACUUM TUBES
2. Terman's RADIO ENGINEERING
3. Everitt's COMMUNICATION ENGINEERING
4. Hund's HIGH FREQUENCY MEASUREMENTS
5. Henney's RADIO ENGINEERING HANDBOOK

10 days' examination. Easy terms. Special price under this offer—less than books bought separately. Add these standard works to your library now; pay small monthly installments, while you use the books.

10 DAYS' FREE EXAMINATION—SEND COUPON

McGRAW-HILL BOOK CO.
330 W. 42nd Street, New York 18, N. Y.

Send me Radio Engineering Library, 5 vols., for 10 days' examination on approval. In 10 days I will send \$2.50 plus few cents postage, and \$4.00 monthly till \$26.50 is paid, or return books postpaid. (We pay postage on orders accompanied by remittance of first installment.)

Name

Address

City and State

Company

Position

**Come to the Great
SHOPS OF
COYNE**
where you learn by doing™

**RADIO
ELECTRONICS—TELEVISION**
in a Few Short Weeks

**Prepare For A Good Job Now With
A Lifetime Future!**

Trained Radio men needed now. Get Radio training and be ready for a real future. Learn on actual equipment at Coyne. Free employment service to graduates. Many earn while learning. If you are short of money, ask about Student Finance Plan. Now added Training in Electric Refrigeration. We are also equipped to train those who qualify under G. I. Bill. Men with Physical Disabilities may qualify for training at no cost to them for tuition and subsistence.

SEND COUPON FOR FULL DETAILS

B. W. COOKE, Director, Radio Division
COYNE ELECTRICAL SCHOOL
500 S. Paulina St., Dept. 57-1K, Chicago 12, Ill.
Send Big Free Book; also details about Coyne Part-Time Employment and Student Finance Plan.

Send G. I. Bulletin Physical Disability

NAME AGE

ADDRESS

CITY STATE

"dit-dahs." That is good. It shows the old subconscious is beginning to work for you even when you are not sitting at your receiver.

The beginning of the fourth week, and not before, finds you ready to practice sending. You should now know how the code sounds when it is sent right; so you will not be forming a lot of poor sending habits that will have to be broken. Rig up a code-practice oscillator such as you have seen described countless times in issues of RADIO NEWS. Buy a good key, if you do not already have one, and adjust it so that you have a medium spring tension and a vertical movement of the knob of about one-sixteenth of an inch. Grasp it with the thumb on the left, the index finger partly on top and partly on the edge farthest from you, and with the second finger partly on top and partly on the right-hand side. Start sending with a smooth wrist-motion. The whole arm should not be pumped up and down.

At first, practice sending separate letters and numbers. Try to send each letter as a smooth unit, with very small spaces between the "dits" and "dahs." Make the dots as short as you can make them, and make the dashes enough longer that they will not be confused with dots, and no longer. I am deliberately avoiding telling you that a dash "is equal in length to three dots," etc., for I do not think this means anything except in tape transmissions. For your purpose, the length of dots, dashes, letter spaces, and word spaces should be long enough to be correctly recognized for what they are and no longer.

Devote fifteen minutes of each evening of the last few days to sending practice, but keep devoting a full hour to copying. If you want to spend more time sending, do not send for more than fifteen minutes at a stretch, or you will find your muscles tightening up on you making your sending erratic.

You have probably noticed that I said at the beginning that you were to devote an hour and a half each day to this project, but I have been accounting for only an hour and a quarter. The other quarter of an hour is to be devoted to learning the theory and laws necessary for passing the examination.

You should have provided yourself with a copy of "The Radio Amateur's License Manual." This can be obtained from The American Radio Relay League, West Hartford, Conn., for a quarter, postpaid. In it will be found every question that will be asked you on the examination, together with the proper answer.

Take a pair of scissors and cut the sixty-eight questions in the Class B portion from the manual together with their answers. Glue each question on one side of a piece of paper and the answer on the other. Study each question carefully and the answer even more carefully, underlining

ORDER NOW

- Lighthouse Tubes, 2C40; Regular \$12.50
Special \$ 3.95
- Driver Transformer, uncased, Thermador,
pp 6C5 or 6U5 to pp 6L6's \$ 1.95
- Power Transformer 700 V.C.T. @ 140 ma,
6.3 V. @ 5 amp, 5 V. @ 3 amp \$ 4.50
- National ACN Dials \$ 3.00
- 300 Ohm Amphenol Twin Lead,
per 100 ft. \$ 2.90
- 75 Ohm Amphenol Twin Lead,
per 100 ft. \$ 2.00
- Kilowatt 75 Ohm Amphenol Twin Lead,
per 100 ft. \$ 7.20
- 5 Volt, 26 Amp. Trans. (2G,000 V. ins.
uncased) Western Electric \$ 5.95
- 3 Gang 410 Mmfd. Per Sect. Cond.
Excellent quality \$ 2.95
- 2" PM Speaker (Bakelite Cased)
Used in Walkie Talkie \$ 1.95
- Signal Corps Telegraph Key \$ 1.10
- Jan 6 AK5 Tubes \$ 1.95
- #12 Solid Enamel Copperweld Antenna Wire,
per 100 ft. \$ 1.35

Send for Our Special Bulletin of
Government Surplus Items

DOW RADIO

Pasadena Phone—SYcamore 3-1196
Los Angeles Phone—RYan 16683

ATTENTION RECORDISTS

We tentatively offer for sale one complete recording set-up including new Presto equipped rack, 2 new 16" tables and such accessory equipment as needed to operate a commercial recording and transcription studio. All components are of first quality, and the circuits extremely flexible. Upon receipt of your bona fide inquiry, we will send a complete description of this equipment and the price, which will be in the neighborhood of \$2500.

Box No. 445 care of Radio News
185 N. Wabash Ave. Chicago 1, Ill.

*Supplying Every
Electronic Need*

- For the—
- Radio Service Man
 - Amateur
 - Student
 - Experimenter
 - Industrial

Write For Illustrated Price List

**GRABREE'S
WHOLESALE RADIO**

DALLAS 2608 ROSS AVE. TEXAS

ROTA-BASE

NEW HANDY LAB. DIAL actually Gives a "prong" picture of radio tube connections. Simply turn the dial to the tube number desired on the ROTA-BASE and complete correct connections are instantly indicated on the "prong" diagram. No more valuable time lost thumbing pages or on lengthy readings. Filament, grid, plate, cathode, etc., to MORE THAN 300 tube types are given. PRICE NOW ONLY \$1.00 postpaid or sent C.O.D. plus postage. Order NOW, money refunded if you are not delightfully pleased.

REED MFG. CO. 124 W. 4th St.
Los Angeles 13, Calif.

WIRELESS PHONO OSCILLATOR

Transmits recordings from phono pickup or voice from mike to radio without use of wires up to 500 ft. Neatly Designed. NO LICENSE REQUIRED. Complete Kit, less tubes \$3.49
Above Kit assembled and tested \$4.49
A Kit of tubes, 12SA7, 35Z5 \$1.49
Jobbers: Write for quantity discounts on amplifiers and oscillators

Immediate delivery, 10% deposit with C.O.D.
CONSTANT ELECTRIC
112 Cornelia Street Dept. 10 Brooklyn 21, N.Y.

in ink the important phrases, words, etc.

Next, pick a question at random and try to write out the answer. Compare what you have written with the printed answer. If there is any material difference, rewrite your answer. Keep doing this right on through the list of questions; then start over and do it again. Keep right at it, no matter how well you think you know the answers, right up to the time you take the examination. It is very disheartening to pass the code examination and then to flunk out on the written portion.

Let me stress the importance of using the same language the manual uses. Do not try to convert the answers into your own words. Learn them nearly word for word, as a parrot would. The people who grade the papers recognize the clear, straightforward wording of the manual; they may not recognize the same answer when it is cast in altogether different phrasing. *You cannot go wrong in memorizing the wording of the manual.*

Which one of you will be the first to get his license using this method? It can be *you*, you know. Good luck and
73!

Simple FM Converter

(Continued from page 50)

results in the middle range so that generally the operation is good over the entire band. The design of the LC circuits in this unit is such that an extremely wide band is passed. For some sets a very slight adjustment may be required to bring the signals in at maximum efficiency. One capacitor should be tuned to the h.f. band station the other for a station near the same point in the low band.

In most metropolitan areas no new antenna should be required. For the best reception in the range 88-108 mc. a dipole antenna is recommended with a length on either side of center at 30 inches. The new plastic covered parallel transmission line is best for lead-in.

—50—

ERRATUM

The secondary of the discriminator transformers shown in Figs. 2 and 3, page 55, and Fig. 4, page 150, in the March issue should have been shown as a tuned circuit. A trimmer tuning condenser should have been shown across the outside terminals of the secondary winding.

Photo Credits

Pages	Credit
Cover Photo	Arthur Hauk, Staff Photographer
45, 47	Western Electric
48, 49, 66, 172, 174	Arthur Haug, Staff Photographer
50	Daven Company
51, 52, 53, 57, 59, 122, 189	Walter Steinhard, Staff Photographer
56	McElroy Mfg. Corp.
60	Radio News Staff Photographer
61, 102	Miles Reproducer Co., Inc.
62	The Gray Mfg. Co.
63 (top)	Hotpoint, Inc.
65, 118	Newark Electric Co., Inc.
71, 73	The Hammarlund Mfg. Co., Inc.
145	General Electric Co.
162	Luis Diaz Alongo
177	British Information Services

LOOK! COMPARE! BUY!

SPEAKERS
5" P.M. Alnico 5 Magnet, ea... **\$125**
 6 for \$7.00
6" P.M. Alnico 5 Magnet, ea... **179**
 6 for \$10.00

All other sizes in stock, at money-saving prices.

AUTO RADIO SUPPLIES
4 PRONG Universal non-sync. VIBRATORS..... **\$139**
 Minimum order, 6
OZ4 TUBES, ea..... **107**
 Minimum order, 6
SPARK Plug SUPPRESSORS..... **7c**
 See our Catalog for full line of auto aeriels.

Phono Supplies
 Phono Motor & Turntable \$ 3.39
 Crystal Pickup Arms.... 2.49
 Webster No. 50 Changer... 21.17
 Webster No. 56 Changer... 26.66
 Webster No. 70 Changer... 43.20
 Free \$2.50 permanent needle with each changer

VOLUME CONTROLS
1/2 MEG volume control with switch and long shaft, ea.... **59c**
 6 for \$3.25

15 ASSORTED VOLUME and Tone Controls
 (less switches)..... **\$195**

MONEY KITS SAVING
100 Insulated Resistors, 1/2, 1 & 2 Watt **\$1.95**
20 Assorted Wire Wound resistors... **1.95**
50 Popular Assorted Mica Condensers... **2.50**
20 Assorted Tube Sockets..... **1.00**
20 Assorted Trimmers..... **1.00**
I.F.'s 455 KC...... **45c**

WIRE
400 Ft. (approx.) of wire in assorted colors and gauges, solid and stranded in 2 to 4 foot lengths, **99c** per pkg.

CONDENSERS
Tubular Paper (600 V. Test)

Mfg.	Price ea.	Per 100
.01	.08	\$ 6.50
.02	.08	6.50
.05	.10	8.00
.1	.12	9.00
.25	.17	13.50
.001	.08	6.50
.002	.08	6.50
.005	.08	6.50
.006	.08	6.50
.5	.26	22.60

"Illinois" Electrolytics

Mfd. VDC	Price
10	.25v..... \$.25
100	.25v..... .55
12	.50v..... .38
16	.150v..... .35
20	.150v..... .38
24	.150v..... .38
30	.150v..... .40
50	.150v..... .38
8	.450v..... .43
10	.450v..... .55
20	.450v..... .60
40	.450v..... .88
100	.15v..... .49

"Illinois" Duals

16-16	.150v..... .58
20-20	.150v..... .65
30-30	.150v..... .70
40-20	.150v..... .70
50-30	.150v..... .76
8-8	.450v..... .65
10-10	.450v..... .70
20-20-20	.150v..... .99

10% discount on all electrolytics if purchased in lots of 10 or more. Mica Condensers, all sizes, 8c ea.

TEST EQUIPMENT
 Model 670 Superior VoltOhmmeter.....\$28.40
 Model 905 McMurdo Silver "SPARX" Signal Tracer..... 39.90
 Model 900 Vomax..... 59.85
 Model 450 Superior Tube Tester..... 39.50
 Minimum Order, \$3.00—20% with order, Balance C.O.D.—WRITE FOR CATALOG

12 lbs. SURPLUS RADIO PARTS \$2.00

A gold mine of parts for repairmen, amateurs, and experimenters... sockets, condensers, resistors, transformers, coils, hardware, wire, etc., etc. An outstanding bargain in usable parts! Send \$2.00 cash, check or M.O. today! (Pay small express charges on receipt.)

ELECTRONIC PARTS, Inc. Dept. A5 622 W. Randolph St., Chicago 6, Ill.

Built so You Can Read it!

MULTIPLEX
 PER - VOLT - OHM - MILLIAMMETER -



This is your instrument for all day, every day use. The Multiplex Model 458 is a rugged, accurate, portable, bench-type V.O.M. built to high industrial standards by one of America's pioneer makers of test equipment.

Multiplex Features:

Big 5 1/2" d'Arsonval movement meter. 1000 ohms per volt. Multipliers accurate within 1%. Rotary range selector. Copper oxide rectifier for A.C. range accuracy. Priced remarkably low for **\$26.00**—NET an instrument of this quality—only.

See Your Jobber or Write for Bulletin 458

All Popular Ranges

Volts D. C.	0-5/10/50/100/500/2000
Volts A. C.	0-12.5/25/125/250/1250
Milliamperes D. C.	0-1/10/100
Milliamperes A. C.	0-2.5/25/250
Ohms Full Scale	1000/200,000/2,000,000
Ohms Center Scale	50/2250/22,500
Output	-5 to +55 Decibels

CHICAGO INDUSTRIAL INSTRUMENT CO.
 219 West Chicago Avenue CHICAGO 10, ILLINOIS

EXCEPTIONAL → VALUES ←



**DETROLA
AUTO-
MATIC
RECORD
CHANGER**

Plays 10 and 12-inch records. Enjoy almost 30 minutes of uninterrupted music. **Special Low Price \$14.79**

SPEAKER BUYS

4" Alnico 5 Magnet	\$1.40
5" Alnico 5 Magnet	1.55
6" Alnico 5 Magnet	2.35
8" Alnico 5 Magnet	4.15
10" Alnico 3 Magnet	6.25
12" Alnico 5 Magnet	8.95

10% off in lots of 12.

2 TUBE PHONO OSCILLATOR



Complete with tubes, 35z5, 12SK7. Use with record player or carbon mike and tune in on any radio. Range up to 100 feet.

Complete All Wired **\$5.95**

90 MIL POWER TRANSFORMERS

600 Volts 6.3V and 5V Filament transformers \$2.95
50 Assorted Knobs, Push on, screw, etc. 2.65
1/2 Meg volume controls with switch .75
10% off in lots of 12.



HAZELTON INSTRUMENT CO. MODEL 100

Pocket Multimeter 2' Movement, 1000 ohms PV A.C. Volts 0-15, 150, 1500; D.C. Volts 0-15, 150, 300, 1500; Ohms 0-3000, 300,000; Mils 0-15, 150 **\$13.95**

100 Mica Condenser Kit	\$2.95
100 Insulated Resistor Kit in 1/4, 1/2, 1 and 2 Watts	1.95
20-20, 150 VDC	.55
30-20, 150 VDC	.63
40-30, 150 VDC	.70
50-30, 150 VDC	.75

All Electrolytics 10% off in lots of 12 25% with order, balance C.O.D. Include postage, excess returned.

TEL-RAD ELECTRONICS CO.

140 LIBERTY STREET
NEW YORK 6, N. Y.
Barclay 7-4239

Classified

Rate 20c per word. Minimum 10 words.

RADIO ENGINEERING

RADIO Engineering Broadcasting, Aviation and Police Radio, Servicing, Marine Operating and Electronics taught thoroughly. Expenses low. Write for catalog. Valparaiso Technical Institute, Dept. N, Valparaiso, Ind.

FOR SALE

SERVICEMEN: After years of using cigar boxes, etc., have developed in my shop an entirely new Record Changer and Radio Chassis Repair Stand. Can be used on all changers and receivers. Made of steel and semi-steel castings. Price, \$3.50 postpaid. Radio Repair Service, 252 Grant Ave., Jersey City 5, N. J.

SURPLUS radio bargains, free bulletin. Also Electronic Lab., Box 214, Lawrence, Mass.

POWER Mowers. Special deal-sample. Rotacut, M-2063, Ex. Springs, Mo.

MAGNETIC Wire Recorders, 4 lb. pocket model. P.O. Box 363, Hoboken, N. J.

2000 VA SOLA Voltage Regulators. 95-125/190-250v, 50/60 cycles input; 115v @ 17.4a output. Tested and in excellent condition. \$39.50 FOB. McMurray Electric, Grapevine, Texas.

POWER supplies and short wave equipment. Write for bulletins. Spectra Products, 17 E. 42nd St., New York 17, N. Y.

ATTENTION Canadian Radio Amateurs. Just released, new complete transmitter and receiving set for \$89.50. Made in Canada, No. 19, Mark II by RCA lend lease Russia, complete ready to operate. Order now, no duty to pay, FOB Chicoutimi. R. Fong, Box 304, Chicoutimi, Que.

RECEIVER Schematics: BC 224-F, K, H; 312-N, NX; 314 G; 342-N; 344-D; 348-E, J, K, L, M, N, P, Q, R. 75c each. Box 525, Sta. A, Champaign, Illinois.

SERVICEMEN, amateur special, RG59/U, 72ohm coaxial cable, \$.07 per foot. The SCR522, with A.C. power supply, 2-meter band-spread coverage, single RF-OSC. control, other improvements, complete in deluxe metal cabinet, write for information. Television kits, build your own, and a complete line of amateur and servicemen parts. Castle Radio Supply, W2JBM, 677 Euclid Ave., Brooklyn 8, N. Y.

COMPASS for beaming Antennas to Broadcast Stations, determining fields for motor repairs, etc.; brass watch-type case, jeweled bearing, automatic lock, luminous face, sturdy. Price, \$1.39 postpaid. Paramount Products, 67-25 Juno St., Forest Hills, New York.

PANADAPTOR for \$85.00, just about new. Write, M. R. Colliard, Santa Barbara School, Carpinteria, Calif.

ACETATE cellulose recording discs. Use on 3 1/2 and 7 8 R.P.M. machines. 30 and 60 minute recordings 25c each. 13 inch discs. Irving J. Halperin, 102 St. Marys St., Boston, Mass.

SPEAKER Cones and voice Coils, any size. Wholesale Radio & Elec. Service, Orangeburg, S. C.

ROTATORS! Plenty husky for any beam a Ham can dream up! Navy SO-1 Radar type. Beautifully built. Automatic lock-in. Instantaneous reversing. No overswing. Demountable reflector, waveguide nozzle. \$59.50 f.o.b. N.Y. new in original heavy crates. Shipping weight 490 lbs. (stripped for Ham use 150). 110v 60 cycle operation using your parts, or our kit with tapped transformer (permitting 1-2 rpm.), seleniums, condensers, instructions, \$19.50. Further details, photograph, 25 cents. Electrocrafter, Inc., 5 Waverly Place, Tuckahoe 7, N. Y.

MOTOR Alternators. Built by a leading manufacturer to rigid specifications of the U.S. Navy for fire control use. Input: 115 volts D.C. at 14 amps. 3600 rpm. Output: 120 volts A.C. 60 cycles at 10.2 amps. or 1000 watts continuous duty. Splashproof. Fully covered. Centrifugal starter. Brand new in original boxes including spare parts kit. Shipping weight 290 lbs. Net weight 260 lbs. Price f.o.b. N. Y. \$87.50. Electrocrafter, Inc., 5 Waverly Place, Tuckahoe 7, N. Y.

LOWEST Prices. Radio Tubes, parts. Bargain lists 3c. Potter, 1314 McGee, Kansas City 6, Mo.

RADIO Tubes—Dealers, order your needs—be surprised at prices. Address Radio Tubes, Box 108, Elizabeth City, N. C.

SELENIUM Rectifiers, full wave, 1/2 ampere, \$1.85; 1 ampere, \$2.50. Half wave 5 amperes, \$4.50; 2.2 amperes, \$2.25; 1.5 ampere, \$1.85. Bulletin. Bursma Radio, Route 5, Grand Rapids, Mich.

RCA Television Chassis and Power Supply. No tubes or harness, \$90. Meissner Signal Calibrator Mod. No. 9-1006, \$65. Alexander Radio & Electrical Shop, Roy Alexander, Jr., Montezuma, Iowa.

FREE wholesale bulletin, Tubes, parts. Bargain prices. Henshaw Radio Supply, 3313 Delavan, Kansas City, Kansas.

FRESH mailing lists. Trial 1000 radio-servicemen-dealers \$10.00; 600 radio, equip. mfrs. \$8.00; 55 radio amplifiers mfrs. \$3.00; 49 radio tube mfrs. \$3.00. House of Butte, 60 E. 42nd St., New York 17, N. Y.

"RECEIVER Alignment without instruments," 10c. Superheterodynes, TRFs. Electronic Publications, 166 N. Sierra Bonita Ave., Pasadena, Calif.

FIFTY Dials, nameplates, switchplates (paper), 10c. Professional appearance. Electronic Publications, 166 N. Sierra Bonita Ave., Pasadena, Calif.

SIGNAL Generator. \$5.00. All bands, two tubes. 110 volts. Diagram 25c. Electronic Publications, 166 N. Sierra Bonita Ave., Pasadena, Calif.

REPAIRMEN, hams, students! Get needed radio-electronics books by mail. All latest titles. Postcard brings free illustrated catalog N5. D. B. Nephews Publishing Co., 300 Pacific Street, Brooklyn 2, N. Y.

24-28 **VOLT** Transformers to convert ART-13 transmitter or operate other equipment from 115 V.A.C. 250 watts, fully shielded, \$14.50. J. Reidel, W2CRB, 1523 41 St., Brooklyn 18, N. Y.

WANTED

RIDER manuals, give details. G. J. Abbott, Georgetown, Ill.

TYPE BC 610 Transmitters with tubes and accessories, new or used. Box 446, % Radio News.

WIRE Recorders, complete or parts. Give details. Chas. Reich, 415 Walnut, Knoxville, Tenn.

SUB-CONTRACT work on sub-assembly of radio and electronic equipment. Kendall and Kauffman, 25 Woodland Ave., Takoma Park, Md.

CORRESPONDENCE COURSES

CORRESPONDENCE Courses and self-instruction books, slightly used. Sold. Rented. Exchanged. All subjects. Satisfaction guaranteed. Cash paid for used courses. Complete information and 100-page illustrated bargain catalog FREE! Write Nelson Company, Dept. 59, Chicago 5, Ill.

AMATEUR radio licenses. Complete code and theory preparation for passing amateur radio examinations. Home study and resident courses. American Radio Institute, 101 West 63rd Street, New York City.

USED Correspondence Courses and Educational Books sold or rented. Inexpensive. Money-back guarantee. Write for Free Catalog listing 4000 bargains.—(Courses Bought.)—Lee Mountain, Pisgah, Ala.

PATENT ATTORNEYS

PATENTS—U.S. and Foreign Patents Secured. Trade-marks and Copyrights registered. Searches made to determine Patentability and Validity. Patent, Trade-mark and Unfair Competition Causes, Lancaster, Allwine & Rommel, Registered Patent Attorneys, Suite 414, 815 15th St., N.W., Washington 5, D. C.

HELP WANTED

OPENINGS: Instructors, Telegraphers; first phone operators for AM, FM, TV Stations. RRR. Employment Bureau, Box 413, Philadelphia.

SITUATIONS WANTED

AVAILABLE: Veterans trained in Sound Recording, Laboratory and Transmission Engineering. Experienced in the following measurements: Inter-modulation, Distortion, Gain/Frequency, Square Wave. Write, H. M. Tremaine, 1655 N. Cherokee, Hollywood 28, Calif.

MISCELLANEOUS

SPEAKERS reconed by factory trained experts. Cones guaranteed. 3, 4, 5 inch, \$2.15; 6 inch, \$2.70; 7, 8 inch, \$3.15; 10 inch, \$4.25 up; 12 inch, 14 inch, \$4.75 up. Niles Radio Co., 505-14th Ave., Denver, Colo.

RADIO Listeners! "Don't blow your top!" Plug Earsaver remote volume control into your radio; from anywhere in room, fade down loud music, singing commercials, etc. Only \$4.95 with 15-ft. cord. Circular free. Earsaver, 724 E. Elmwood, Dept. 3, Burbank, Calif.

SPEAKER Gauges: Immediate repair for 90% of all dragging voice coils. Ten machined forms to straighten coils. Instructions in packaged unit. \$3.50 complete postpaid. Speaker Service Co., 1038 S. 32nd St., Omaha 5, Nebr.

ELECTRICAL Instruments. All makes and models repaired. Correspondence invited. Haledon Elect. Instrument Co., 319 Belmont Ave. (Haledon), Paterson 2, N. J.

RADIOMEN, servicemen, beginners—make more money, easily, quickly. Methods pulled near \$1000 monthly. We show you how. Write: Merit, 216-32 132nd Ave., Springfield Gardens 13, New York, N. Y.

BUILD radio, phonograph, or combination, complete kits. Catalog. Radion, 6922B 21st Ave., Brooklyn 4, N. Y.

WHOLESALE radio service: Send us radio prepaid, we repair and ship C.O.D. Also auto radios repaired. Reasonable rates, fast service. Your Radio Doctor, 397 Melrose St., Brooklyn 6, N. Y.

RADIO men—Lowest prices in America. Big stock. Write for latest catalogue. McGee Radio, 1330 Broadway, Denver, Colo.

WHOLESALE Radio Service at reasonable rates, quick service, no job too big. Write for full information. Elkins Radio, Elkins, W. Va.

RAILWAY telegraphy. Be a railroad telegrapher. Operators are in great demand. Salaries from \$3,200 up. For information write to Bell Telegraph Ry. Institute, 10 Parker Ave., Suite 9, San Francisco 18, Calif.

CUSTOM Built Equipment for less than "factory-built" prices! How? Write Custom Equipment Laboratories, Box 623, Cedar Rapids, Iowa.

RADIO NEWS

GE Dial Belt Kits
Ruf-Koat
Hell Box
Wire Stripper Kit

G-C SERVICEMEN'S DIAL BELT KITS

Fine woven replacements for all sets. Easy to install. Supplied in kits of various quantities with steel box. No. G-25—Kit of 25 belts List \$6.70

G-C WIRE STRIPPER KIT

Handy, complete with stripper and 7 different size blades in steel box. Strips wire No. 8 to No. 30. No. 733E—standard kit. List \$15.00

G-C HELL BOX

Assortment of thousands of radio parts you use every day, in steel box (screws, washers, nuts, etc.). No. 6500 List \$4.50

G-C RUF-KOAT

Only wrinkle finish that will air dry. Baking not required. Easy to use, gives professional wrinkle finish. No. 60-2— $\frac{1}{8}$ pt. List 45¢
At leading jobbers.
WRITE FOR CATALOG.
See our exhibit—Booth No. 96—Radio Parts Show—May 13-16, Chicago.
RADIO DIVISION DEPT. H

GENERAL CEMENT Mfg. Co., Rockford, Ill., U.S.A.
Manufacturers of over 3,000 products
Sales offices in principal cities

POTTER'S BARGAINS

We still have

80 Meter XTALS
74¢
with holders

3,500 to 4,000 KC. Specify frequency to nearest 10 KC., and first and second choice. Large holders.

OUR NEW LOW PRICED CRYSTALS

80 Meters, Your frequency within 10 KC.	\$0.74
40 Meters, Your frequency within 10 KC.79
20 Meters, 3rd Harmonic Oscillators... 1.49	
1816-1856 KC. for F.M.79

The new crystals are in holders. All are made to your order. Please allow 10 days for delivery.

Crystal Finishing Kit
Consists of the following:
2 blanks to be ground to 80 meters.
2 blanks to be ground to 40 meters.
2 crystal holders for above.
2 grades of lapping compound.
Instructions for finishing.

SPECIAL 79¢

Rough Blank Kit No. 1, 12 rough blanks, well assorted as to thickness so as to finish to various frequencies. Special.....79¢
10 assorted crystal holders. Thousands sold and still going strong. Only 99¢. Postage 3 lbs. extra.

POTTER RADIO CO.
1312-14 McGee St., Kansas City 6, Mo.

Signal Generator
(Continued from page 59)

of a fine pointer on a nine-inch, three-color dial face which is illuminated by two hooded pilot lights. An enlarged view of the dial and vernier drive are shown in Fig. 6.

This signal generator has been designed and constructed to provide accurate signals for radio servicing without the use of elaborate or involved procedures in setting up the instrument. It may be easily adapted to all types of receiver servicing including FM, television, and AM receivers.

Fig. 5. Actual 400 cycle modulated waveform from signal generator described. This trace was taken after signal passed through the r.f. and audio stages of a commercial receiver. Buffer stage modulation is approximately 45%. A pure sine wave is a factor in checking over-all distortion taking place in r.f., converter, detector, and audio systems of receivers.

Fig. 6. Close-up view of vernier and "Micromaster" tuning dial of the signal generator shown in Fig. 1. Calibration reference points of from 0-100 available on the geared vernier provide a precision factor for aligning FM and TV sets.

ANSWERS TO RADIO QUIZ
(see page 175)

1. (a)	5. (b)	9. (a)
2. (c)	6. (c)	10. (c)
3. (d)	7. (b)	
4. (a)	8. (d)	

I'll Train You Quickly—at Home—in Your Spare Time—to Make More Money in the Fastest Growing Industry in the World!

WHO SAID IT COSTS A LOT OF MONEY TO LEARN RADIO ELECTRONICS?

Ghirardi's Famous RADIO PHYSICS COURSE
costs you **only \$5** complete and it is complete!
36 BIG COURSES IN ONE!

FOR BEGINNERS
No Previous Experience Needed

Send coupon today! Examine Ghirardi's big, 972-page RADIO PHYSICS COURSE for five full days. See how this one giant book at ONLY \$5 can give you complete, basic training to pave the way for a brilliant future in Television, Radio, Frequency Modulation, Facsimile, Broadcasting, Communication, Servicing, Industrial Electronics, etc. Prove to yourself that training doesn't need to be expensive to be really good!

9 OUT OF 10 RADIO MEN CAN'T BE WRONG!

Actually, this famous book has given more people their start in Radio-Electronics than any other book or course ever published. On an actual survey among 817 men already in radio, 724 of them—9 OUT OF 10—answered that Ghirardi's RADIO PHYSICS COURSE is their choice as the finest, easiest to understand training on the market—and far better than any other book or course they have ever seen!

LEARN FAST! LEARN RIGHT!
as fast as you can read!

You'll be pleasantly surprised how RADIO PHYSICS COURSE helps you master subjects that other courses make seem very complicated. Starting with Basic Electricity—over 300 pages—it takes you through the entire Radio-Electronics field. Everything is made crystal clear. Nothing is omitted or condensed. You buy it for only \$5 complete—ON OUR MONEY-BACK GUARANTEE. You progress as fast as spare reading time permits. Many students have completed it in a few weeks. 972 pages. 508 illustrations and 856 self-test review questions make study doubly easy. Rush coupon. You cannot lose!

'BORROW' IT FOR 5 FULL DAYS!

MAIL ORDER—Rush Coupon

Dept. RN-57 Murray Hill Books, Inc.,
232 Madison Ave., New York 16, N. Y.

Enclosed find \$5 (\$5.50 foreign) for Ghirardi's 972-page RADIO PHYSICS COURSE book; or send C.O.D. for \$5 plus postage (no foreign C.O.D.'s). In either event, if not satisfied, it is understood I may return book in 5 days for complete refund of my money.

Name.....
Address.....
City & Zone.....State.....

MONEY-BACK GUARANTEE

RADIO PARTS SOUND SYSTEMS ELECTRONIC APPARATUS

Depend on RADOLEK

Radolek's big Free Profit Guide Catalog and Profit Bulletin supplements keep you abreast of the rapidly changing radio situation. Buying from Radolek means greater values, better service and more profits. Make Radolek your buying headquarters.



RADIO PARTS



SOUND SYSTEMS

FREE CATALOG




**Large Stocks
Fast Service**

SEND TODAY!

RADOLEK CO., Dept. B-126
601 W. Randolph St., Chicago 6, Ill.
Please send your FREE Profit Guide Catalog.

Name.....
Address.....

SAVE AT RADOLEK

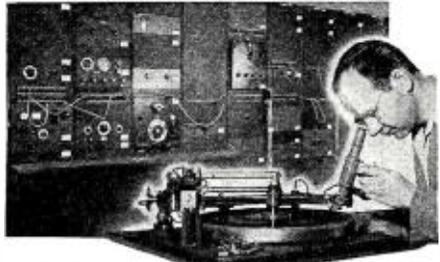

School of SOUND RECORDING and TRANSMISSION ENGINEERING

Learn sound recording and transmission engineering techniques of the professionals, as used in Motion Picture, Broadcast, F-M, Television, and Commercial Recording Studios.

A nine months practical engineering course, devoted exclusively to the technique of sound recording and transmission measurements. Well equipped studios, professional recorders and circuit laboratory containing latest model test equipment installed for student training. A portion of our laboratory is pictured above.



H.M. Tremaine
Director

● New classes admitted the first School day of Jan., Apr., July, Oct.
Affiliated with the Don Martin School of Radio Arts
Approved for Veterans

Write for Literature • Sound Department
Don Martin SCHOOL OF RADIO ARTS
1655 Cherokee • Hollywood 28, California

INDEX OF ADVERTISERS May 1947

Advertiser	Page	Advertiser	Page
Abell Distributing Company, The	108, 170	Halberin, Irving J.	167
Adson Radio Co.	160, 178	Hammarlund Mfg. Co., Inc., The	41
Aerco Sales Company	154	Harrison Radio	167
Air King Radio	17	Harvey Radio Co., Inc.	118
Alliance Manufacturing Company	31	Henry Radio Stores	159
Allied Radio Corp.	9, 141	Herbach & Rademan Co.	185
Almo Radio	174	Hershel Radio Co.	133
American Phenolic Corporation	77	Hexacon Electric Co.	156
American Radio Institute	174	Highbridge Radio-Television & Appliance Company	106
American Sales Company	156	Hollywood Sound Institute	164
American Television Laboratories, Inc.	89	Hoodwin, Chas. Co.	158
American Television & Radio Co.	163	Instructograph Company	178
Amperex Electronic Corporation	18	International Resistance Company	119
Amplifier Corp. of America	164	Interstate Mfg. Co.	96
Arco Electronics, Inc.	40	Intex Company	163
Arrow Sales, Inc.	92, 93	Jensen Manufacturing Company	37
Ashe, Walter, Radio Co.	165	J. F. D. Manufacturing Co.	134
Audel Publishers	122	Joseph, Irving, & Associates	153
Baltimore Technical Institute	148	Kayline Distributing Co.	144
Beard, G. F.	174	Kelvin Electronics	166
Bell Telephone Laboratories	35	Kenyon Transformer Co., Inc.	140
Belltone Radio and Television Corp.	115	Klein, Manuel	172
Best Vibrator Company	171	Lake Radio Sales Co.	185
Bliley Electric Company	121	Legri S Company, Inc.	148
Bliss Electrical School	160	Le-Hi Electrical Company	176
Bogen, David, Company, Inc.	153	Leonard Radio, Inc.	82
Bonafide Radio & Electronics Co.	170	Leotone Radio Co.	135
Brach, L. S., Manufacturing Company	173	Liberty Sales Co.	117
Bradshaw Instruments	185	Lifetime Sound Equipment Co.	170
Bud Radio, Inc.	124	Lifsey Distributing Company	171
Buffalo Radio Supply	100, 101	Lincoln Engineering School	178
Burlington Instrument Company	132	Maedel Publishing House	126
Burnell & Company	150	Maguire Industries, Inc.	109
Burstein-Applebee Company	88	Mallory, P. R. & Co., Inc.	14, 3rd Cover
Buyers Syndicate	162, 164	Maritime Switchboard	152
Candler System Co.	179	Martin, Don, School of Radio Arts	171, 184
Cannon Electric Development Company	157	Melville Radio Institute	139
Capitol Radio Engineering Institute	28	Merit Coil & Transformer Corp.	20
Centralab	13, 99	Metropolitan Electronic & Instrument Co.	29, 138
Chicago Industrial Instrument Co.	181	Mid-America Co., Inc.	116
Chicago Transformer Co.	12	Miles Reproducer Co., Inc.	167
Chief Electronics	160	Milwaukee School of Engineering	176
Christy Supply Company	128	Murray Hill Books, Inc.	83, 137, 183
Clarion Sound Engineering Co.	134	McGee Radio Company	84, 85
Clark Radio Equipment Corp.	177	McGraw-Hill Book Company	180
Cleveland Institute of Radio Electronics	39	McMurdo Silver Company	145
Clippard Instrument Lab., Inc.	142	Nation Wide Radio Company	173
Collins Radio Company	2nd Cover	National Company, Inc.	10
Columbia Wire & Supply Co.	150	National Radio Distributors	150
Commercial Radio	144	National Radio Institute	3
Communications Equipment Co.	97	National Schools	23
Concord Radio Corp.	105	Newark Electric Company	76
Constant Electric Company	180	Newark Surplus Materials Company	174
Continental Corporation	153	New Jersey Industrial Co.	148
Coyne Electrical School	180	New York Technical Institute of N. Y.	80, 81
Coyne Electrical School	32, 114	Niagara Radio Supply Company	127
Crabtree's Wholesale Radio	180	Offenbach-Reimus	123
Croname, Inc.	15	Ohmeyer Engineering Laboratories	136
Davega Stores Corp.	131	Olson Radio Warehouse	169
Deer & Taylor Company	144	Onan, D. W., & Sons, Inc.	143
DeForest's Training, Inc.	19	Pa-Kette Radio	175
Dow Radio Supply Company	180	Petersen Radio Company	179
Editors & Engineers	90, 91	Philco Radio	30
Electro-Voice	26	Potter Radio Company	183
Electronic Development Company	164	Pyramid Electric Company	44
Electronic Manufacturing Co.	124	RCA Institutes, Inc.	173
Electronics Measurements Corp.	104	R-L Electronic Corporation	126
Electronic Parts, Inc.	181	Radio Center	86
Electronic Technical Institute	165	Radio Corporation of America	33
Embry Riddle School of Aviation	160	Radio Dealer Supply	185
Erie Supply Co.	173	Radio Electric Service Co.	130
Ese Radio Company	110, 111, 112	Radio Electronics Publishing Company	142
Fabricated Lightmetals	134	Radio Equipment Distributors	179
Fada Radio & Electric Co., Inc.	6	Radio-Experts	175
Fahnestock Electric Company, Inc.	113	Radio Ham Shack	78, 79
Federal Telephone and Radio Corp.	27	Radio Hospital	163
Federated Purchaser, Inc.	132	Radio Kits	176
Feiler Engineering Co.	151	Radio Maintenance Magazine	75
Flanagan Radio Corp.	178	Radio Parts	120
Friend's	128	Radio Parts Outlet, Inc.	142, 154
G & E Equipment Supply Co.	128	Radio Shack	171
G. & G. Genuine Majestic Radio Parts Service	174	Radio Supply & Engineering Company	24
Gamma Electric Co.	178	Radio & Television Equipment Co.	176
Garrard Sales Corp.	125	Radio Wire Television, Inc.	94
General Cement Mfg. Co.	183	Radionic Equipment Co.	175
General Electric	136	Radolek Company	184
General Electric Company	25	Ray-Ilectron Company	168
General Electronics Distributing Co.	129	Reed Manufacturing Company	180
General Industries, Inc., The	132	Rider, John F., Publisher, Inc.	186
General Test Equipment Co.	164	S/C Laboratories, Inc.	159
Greene, Jack, Radio & Telev. Co.	124	Sams, Howard W. Co., Inc.	11
Greenlee Tool Co.	179	Sangamo Electric Co.	36
Greenwich Sales Co.	158	Scenic Radio & Electronics Co.	156
Guardian Electric Company	87	Schott, Walter L. Company	160
Halldorson Company, The	177	Schuh & Harper	116
Hallcrafters Company, The	5, 22, 116, 178		
Hallmark-Electronics Corp.	168		

Advertiser	Page
Senco Radio, Inc.	176
Shure Bros., Inc.	155
Sigmon's Radio Supply	114
Sound Products Company	174
Sprague Products Company	103
Sprayberry Academy of Radio	7
Stahl, Michael, Inc.	136
Standard Parts Corp.	98
Standard Radio & Electronic Products Co.	147
Standard Transformer Corporation	43
Sterling Electronic Company	168
Stevens Walden, Inc.	8
Stromberg-Carlson Company	34
Sun Radio of Washington, D. C.	38
Superior Electric Company	148
Superior Instrument Co.	135
Supreme Instruments Corporation	96
Supreme Publications	95
Sylvania Electric Products, Inc.	4th Cover
T A B	149
Telectron Company, The	168
Tel-Rad Electronics	182
Telectronics Service & Supply	158
Thor Electronics	139
Tradio, Inc.	176
Transvision, Inc.	158
Tri-State College	175
Trutone Products Company	140
Tyler Commercial College	107
U. S. Radio Supply	161
Ungar Electric Tools, Inc.	104
Universal Instrument	140
Universal Radio Supply Company	114
University Loudspeakers, Inc.	126
Valparaiso Technical Institute	168
Variety Electric Company	154
Vision Research	146
Ward Leonard	161
Ward Products Corporation	21
Weber Radio Labs	147
Webster Electric Company	16
Weller Manufacturing Company	120
Wells Sales, Inc.	42
Western Radio Communications Institute	167
World Radio Laboratories, Inc.	102
Wright, Inc.	170

RADIO KITS

FIVE-TUBE SUPERHETERODYNE KIT

Small Bakelite cabinet, size 9" x 5" x 6", complete parts (except wire and solder) for the construction of a standard superheterodyne receiver using 50L6, 35Z5, 12SA7, 12SQ7, and 12SK7. All parts properly matched to chassis base.

Price, less tubes **\$10.45**

SIX-TUBE, TWO-BAND SUPERHETERODYNE KIT

In a solid color wood cabinet (green, red), contains all parts (except wire and solder) to construct a high grade 2 band superheterodyne receiver covering regular broadcast and short wave bands.

Tubes consisting of 2-6SK7, 1-6SQ7, 1-25Z6, and 25L6 included.

Price **\$16.75**

PORTABLE ELECTRIC PHONO KIT

Contains the following:

- 1-Portable leatherette covered wood cabinet large enough to take 12" records.
- 1-110-120v 60 cycle phono motor.
- 1-Crystal pickup.
- 1-5" P.M. Speaker and output transformer.
- 1-Complete kit of parts including tubes, but excluding wire and solder to construct a 3-tube amplifier using 1-50L6, 1-35Z5, and 1-12SQ7.

Price complete **\$16.95**

3-TUBE PHONO AMPLIFIER

Complete with tone and volume control.

Price **\$2.95**

McGuire Twin Post Record Changer

Suitable for 10" or 12" records.

Price **\$12.95**

PHONO OSCILLATOR

Wireless phono oscillator transmits recordings for crystal pickup or voice from carbon mike to radio without wires. Can also be used as an intercommunication system using a P.M. speaker as a mike.

Price **\$2.95**

INTERCOMMUNICATION SYSTEM

A low priced two-way system for executives, professionals and home use. Consists of a master and one remote. A highly efficient unit, easy to install, and provides a rapid means of communication between two remote points. Its attractive but simple oak appearing cabinet will suit any office installation.

Your Price **\$14.95**

ALL PRICES ARE F.O.B. NEW YORK CITY
Write for our new catalogue showing new test equipment, tubes, and a large variety of new replacement parts. We ship anywhere promptly.

RADIO DEALERS SUPPLY CO.

135 LIBERTY STREET

NEW YORK 6, N. Y.

RANGEMASTER



MODEL 10
BY BRADSHAW
A COMPLETE SERVICE INSTRUMENT

The model 10 RANGE MASTER covers 22 ranges. A unique system of range selection minimizes test lead changes. Three direct reading capacity ranges.

Three A.C. current ranges for checking current drain of electric motors and appliances.
All in One Rugged, Compact, Attractive Unit

COVERS THESE RANGES

A.C. VOLTAGE: 1-10-100-500-1000 Volts
D.C. VOLTAGE: 10-100-500-1000 Volts
A.C. CURRENT: .05-.15 .5-1.5 5-15 Amperes
D.C. CURRENT: 1-10-100-1,000 Milliamps
RESISTANCE: RX10 RX100 RX1,000 Ohms
CAPACITANCE: .001-.1 .01-1 .1-10 Mfd.

Available in Kit Form for Only \$16.95
Factory Assembled. Ready to Use. \$23.50

SEND FOR DESCRIPTIVE LITERATURE

BRADSHAW INSTRUMENTS CO.

942 Kings Highway, Brooklyn 23, New York

NEWS ABOUT

THE LATEST IN RADIO PARTS—EQUIPMENT—ELECTRICAL DEVICES—brought to you in our monthly bulletins. **ABSOLUTELY FREE!** No obligation.


WRITE TO

MANUFACTURING DIVISION
HERBACH & RADEMAN, INC.
ELECTRONICS SPECIALISTS
522 MARKET ST., PHILA. 6, PA. • DEPT. C

May, 1947

SENSATIONAL SELLERS!

LAKE AMPLIFYING SYSTEMS

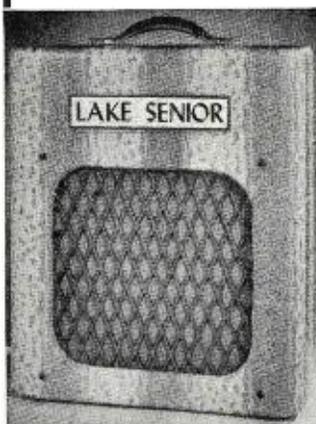

Excellent - designed, compact amplifiers. Ideal for students, professional entertainers, homes, factories, schools, etc. Perfect for voice, musical instruments, pickups and contact microphones: clear, rich tone; heavy plywood in luxurious leatherette-covered streamlined portable cabinets.

As listed below:

No.	Watts	Inputs	List	Your Cost
A16	16	4	\$110.00	\$64.68
A15	15	3	97.50	52.86
A12	12	3	87.50	51.45
A 8	8	3	87.50	51.45
A 6	6	2	75.00	44.10
A 4	4	2	60.00	35.28
A.C.-D.C.	5	3	75.00	44.10
Model				

HAWAIIAN ELECTRIC GUITAR

Beautiful black plastic, trimmed with chrome. 28" scale, 4 1/2 octaves of playing range. List \$50.00. Your Cost **\$29.40**

All types of radio cabinets and parts are available at Lake's Lower prices. A large stock is listed in our catalog.

SERVICEMEN—RETAILERS

Write for our new, illustrated 16-page catalog NR-116, it's free. Get on our mailing list! Write for our Special Catalog on Microphones, Amplifiers and Sound Equipment!



LAKE DELUXE CHANGER

Revolutionizes the Industry!
AN EXCELLENT SELLER

11 Outstanding Features:

- Positive Intermix
- Service Adjustments Eliminated
- Minimizes Record Wear
- Single Knob Control
- Plays All Records
- Pick-up arm may be grasped at any time and changer will not be thrown out of adjustment
- Resonance-free ball bearing tone arm
- Easily operated—any child can do it
- Completely Jam-proof
- Records Gently Lowered on Spindle—not dropped
- Automatic Shut-off on last record

Dimensions: 13 1/8" W x 12 1/4" D x 7 3/4" H
No. 116A YOUR NET **\$28.73**

Lake Radio Sales Co.

615 W. Randolph Street
DEPT. A
Chicago 6, Ill.



A SIGN OF SUCCESSFUL SERVICING



Radio Clinic has all fifteen RIDER MANUALS

The Radio Clinic, with two stores on Broadway in New York City, has long been recognized for the high efficiency of its radio servicing department. Like other successful operators, Radio Clinic has always depended upon the authoritative data in RIDER MANUALS to diagnose the troubles in ailing American-made receivers issued from 1930 to 1947. Also like thousands of others, Radio Clinic is still benefiting from RIDER MANUAL Volume I, bought 17 years ago!

From no other single source is such information available. In no other way can you have at your fingertips the facts you need to locate troubles in any and all receivers that come to your bench; receiver schematics, voltage data, resistance values, chassis layouts and wiring, and trimmer connections.

Volume XV, covering sets issued during 1946, includes the exclusive Rider "clarified-schematics" which

break down the composite diagrams of hundreds of complicated multi-band receivers into individual schematics of each circuit as it exists with each turn of the wave band or equipment switch.

Also with each copy of Volume XV is included the 150 page "How It Works" book, a practical guide to the theory of operation of the new technical features in the latest receivers. These exclusives are but two of the many important features in Volume XV, which also includes all popular "Ham" communication receivers, Scott receivers, Magnavox RA combinations and record player combinations.

RIDER MANUALS provide a systematic, compact, indexed data service, always in order, always ready with the information you must have for efficient, time-saving, profitable servicing. Year after year, after year, RIDER MANUALS keep pouring out profits for servicemen.

In spite of greatly expanded production, demand for RIDER MANUALS still exceeds supply. Place your order today.

JOHN F. RIDER PUBLISHER, INC.

404 FOURTH AVENUE, NEW YORK 16, N. Y.

Export Division, Rocke International Corp., 13 E. 40th St., New York City. Cable ARLAB

RIDER MANUALS

VOLUME XV - JUST OUT!

2000 pages, plus 150 page "How It Works" Book
\$18.00 complete

Volumes XIV to VII (each volume)..... 15.00

Volume VI..... 11.00

Abridged Manuals I to V (one volume).... 17.50

Record Changers and Retorders..... 9.00



OTHER RIDER BOOKS

Inside the Vacuum Tube Solid concept of theory and operation	\$4.50	Vacuum Tube Voltmeters Both theory and practice \$2.50	
Understanding Microwaves Provides foundation for understanding	6.00	Automatic Frequency Control Systems —also automatic tuning systems	1.75
Radar Entertaining, revealing, in lay language	1.00	A-C Calculation Charts Two to five times as fast as slide rule	7.50
The Cathode Ray Tube at Work Accepted authority on subject	4.00	Hour-A-Day-with-Rider Series— On "Alternating Currents in Radio Receivers" On "Resonance & Alignment" On "Automatic Volume Control" On "D-C Voltage Distribution"	\$1.25 each
Frequency Modulation Gives principles of FM radio	2.00		
Servicing by Signal Tracing Basic method of radio servicing	4.00		
The Meter at Work An elementary text on meters	2.00		
The Oscillator at Work How to use, test and repair	2.50		



This new Rider Book, soon to be announced, will be of lasting usefulness to everyone interested in any phase of radio.

RIDER MANUALS

MEAN SUCCESSFUL SERVICING



A section of the huge Indianapolis warehouse, from which thousands of Mallory Approved Precision Products are distributed yearly to all parts of the country.

from coast to coast

**APPROVED PRECISION PRODUCTS
mean Premium Quality,
Dependable Performance**

When you buy and install a Mallory part, you *know* that you won't have service kick-backs. For fifteen years, experience has proved that Mallory means premium quality—that Mallory performance is something you can depend upon. Yet Mallory Approved Precision Products cost you no more.

What's more, these Mallory products are unusually complete. There are no gaps in the lines of vibrators, capacitors, replacement controls. They're easy to order and quickly available, since Mallory distributors are conveniently located.

Then, too, Mallory distributors are especially selected for their ability and desire to serve you. You'll find them equipped to give you prompt, efficient service . . . detailed information on prices, parts and catalog numbers . . . special assistance on problems of management, sales and advertising.

No matter how you look at the service picture, it's true today, as it has always been, that you expect more and get more from Mallory.

See You at the Radio Parts Show in Chicago—Booth 106

P. R. MALLORY & CO. Inc.
MALLORY


VIBRATORS . . . VIBRAPACKS* . . . CAPACITORS . . . VOLUME
CONTROLS . . . SWITCHES . . . RESISTORS . . . FILTERS
. . . RECTIFIERS . . . POWER SUPPLIES.

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA


NOW SYLVANIA TRANSMITTING TUBES

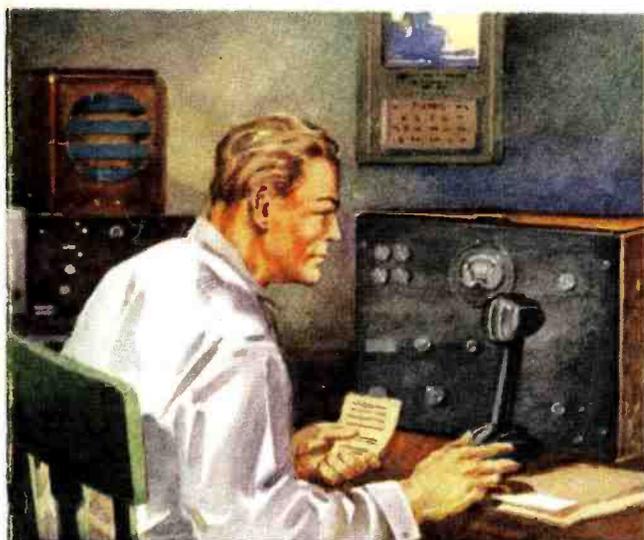

The electronic graphite anode 3D24 is ideal for amateur transmitters.



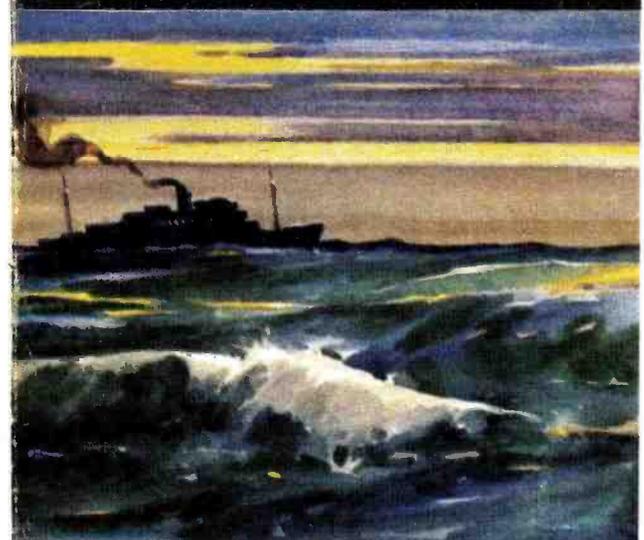Lock-In construction is especially desirable in mobile service.



Rugged construction fits the requirements of marine radio.

A SYLVANIA FIRST— THE ELECTRONIC GRAPHITE ANODE 3D24



Sylvania quality is now available in transmitting tubes too! First of this new Sylvania line, the 3D24—a four-element amplifier and oscillator with 45 watt anode dissipation—features an electronic graphite anode. This outstanding development allows high plate dissipation for a small area . . . maintains constant interelectrode relationship and uniform anode characteristics.

The 3D24 may be used at full input up to 125 Mc—maximum permissible frequency will be announced later upon completion of tests.

Other features of the 3D24: a top cap which provides a short path, greater cooling by radiation and convection. Thoriated tungsten filament. Vertical bar grids. Low interelectrode capacity . . . no neutralizing needed with proper circuit arrangement. Hard glass envelope. *And* the famous Lock-In base!

*A product of the Electronics Division
Direct inquiries to
Radio Tube Division, Emporium, Pa.*

SYLVANIA ELECTRIC

MAKERS OF ELECTRONIC DEVICES; RADIO TUBES; CATHODE RAY TUBES;
FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES; ELECTRIC LIGHT BULBS