

DECEMBER, 1950

# *Radio-Television* **SERVICE DEALER**



The Professional Radio-TVman's Magazine

**IN THIS ISSUE:**

Operation & Service of Keyed AGC Systems  
Sampling Techniques Applied to Television  
Front Ends, Part 6  
Looking For Trouble? No. 2  
Assembling Coaxial Cable Connectors  
Does The Radio-TV Technician Belong In  
The TV Retailing Business?  
High Quality Analyses Series, No. 6

**AM-FM-TV-SOUND**

**Paid Circulation Of This Issue: Over: 25,000**  
**Total Distribution Of This Issue: Over: 30,000**

# Largest Selling Booster

**AT ANY PRICE !**



*Jewels by Cartier  
Photography by Rawlings*



# EDITORIAL

by S. R. COWAN

## Troublesome Days Are Ahead


An "emergency committee" of RTMA has asked National Production Authority to release at once sufficient quantities of materials now restricted, such as cobalt, nickel, copper and aluminum, to prevent imminent stoppage of all TV and radio set production. We commend James D. Secrest, RTMA's general manager, who clearly outlined the industry's position by reasoning that if the Government will want the services of radio plants in 90 days when war contracts are to be issued, unless the factories can be kept in operation in the interim, they face shutdown and the irrevocable loss of their trained manpower to other industries.

The electronics industry committee that coordinates industry—Government war contract relations must also bear in mind that the general public's welfare—meaning the duty of keeping existing receivers in operable use—is of paramount importance too. That our Government is justified in producing radio-electronic equipment for all-out war use, plus the usual 5 to 1 stockpiling, is self-evident. But the fact also remains that now, more than ever before, is it necessary to keep America's home and amateur radios working. The day of atom bombing with its potential vast disruption of other types of communications is the basis for this contention.

Even if all-out war production strains our productive capacity, even if new receiver production must be curtailed to the vanishing point—it must be conceded that a small allocation to the replacement and maintenance fields must be considered worthwhile to the Nation's welfare and economy.
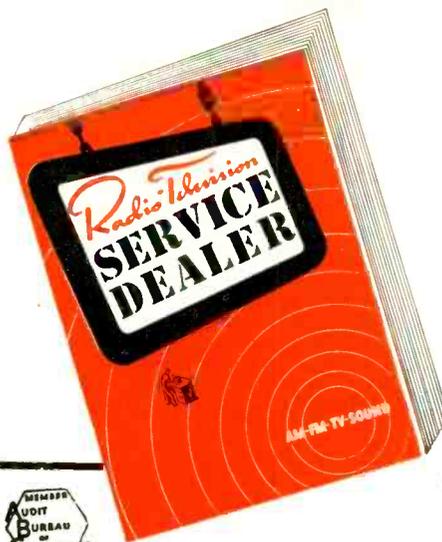
## Color TV Held Back

As predicted, the Courts have enjoined CBS and the FCC on putting a non-compatible method of color videocasting into commercial use until the matter can be given further study. Upwards of 60 days, at least, will be required, and perhaps the matter may drag along in the courts for many months. That's fine! Meanwhile, the proponents of compatible methods can continue their developmental efforts and come up with an acceptable system. We hope so! We are 100% for color TV . . . but, only when it is the right kind of color, completely compatible, and perfected to the Nth degree. Let's have no half-way substitutes in the meanwhile. Of course, there's no reason for getting too excited about color TV right now because the industry itself, due to the war effort, is more than bogged down trying to get necessary tubes and parts needed for ordinary black and white models. As we have stated many times before, all this hubbub about color TV is silly. Anyone who wants a TVset should not hesitate to buy any good brand right now—or when he can get one, because they may become unobtainable or mighty scarce very soon.



**Sanford R. Cowan**  
EDITOR & PUBLISHER

**Samuel L. Marshall**  
MANAGING EDITOR

**COWAN PUBLISHING Corp.**  
342 MADISON AVENUE  
NEW YORK 17, N. Y.

Vol. 11, No. 12

DECEMBER, 1950

Editorial .....	2
Trade Flashes .....	4
Sync Pulses .....	10
Operation & Service of Keyed AGC Systems, by Matthew Mandl .....	15
Why keyed a.g.c. works and how it is applied to various receivers.	
Sampling Techniques Applied to Television, by Edward M. Noll .....	18
Principles of sampling applied to the RCA Color TV system.	
Front Ends, Part 6, by Samuel L. Marshall .....	20
Discussion of alignment precautions and techniques employed in Front Ends.	
Looking For Trouble? No. 2, by Cyrus Glickstein .....	24
A pedagogical trouble-shooting jaunt in the Vertical sweep section of the Hallicrafter Model T-64 receiver.	
Assembling Coaxial Cable Connectors .....	26
Picture story of how to attach connectors to coaxial cable of various sizes.	
Does the Radio-TV Technician Belong In the TV Retailing Business? by Roland D. Payne .....	28
Pros, cons and final conclusions on this interesting question .	
High Quality Analysis Series, No. 6, by C. A. Tuthill .....	29
Analyzing the circuit operation of the Midwest Model JC-16 combination AM-FM receiver.	
Shop Notes .....	32
Philco Models 48-1000, 1001, 1050—Correcting loss of a-g-c action. Philco Model 49-702—Replacement of tuner. Stromberg-Carlson—Pads for connecting Multiple TV-12's to one antenna. G.E. Models 12T3, 1274, 12C107, 12C108, 12C109,—Filament circuit change. G.E.—increased horizontal sweep width. G.E.—removal of 41,25 mc video i-f trap.	
New Products .....	33
Book Reviews .....	36

SANFORD L. CAHN

Advertising Director

SELMA WILE, Circulation Manager

HARRY N. REIZES

Advertising Manager

DAVID SALTMAN, Production Manager

BRANCH: J. C. GALLOWAY 816 W. 5th St., Los Angeles 17, Calif. Mutual 8335  
RADIO-TELEVISION SERVICE DEALER is published Monthly by Cowan Pub. Corp., 342 Madison Ave., N. Y. 17, N. Y. Subscription price: \$2 per year in the United States. U. S. Poss. & Canada: elsewhere \$3. Single copies: 25c. Reentered as second class matter Sept. 25, 1950 at the Post Office at New York, N.Y. under the Act of Mar. 3, 1879. Copyright 1950 by Cowan Pub. Corp.



# No Need To Worry About Moisture When You Use The MALLORY PLASCAP\*

## MALLORY FP CAPACITORS

When you select Mallory FP Capacitors, you can be sure of their performance even in circuits where heat is a problem. Every Mallory FP Capacitor will operate continuously at 85° C. In addition, Mallory FP Capacitors are famous for their long shelf-life... you can depend on them when you need them. Buy the one line that services both AM and TV sets. They are an outstanding example of Mallory Precision Quality at standard prices.

*See your Mallory Distributor right away!*



The Mallory Plascap plastic tubular capacitor exceeds R.M.A. requirements for humidity and immersion tests . . . even for metal-cased capacitors. It's the plastic tubular that's years ahead of the rest of the field.

No oil leakage, no unsoldered leads, no messy wax coating, no insulation problems! Check these four exclusive features which make your service jobs surer and easier:

- **TRISEAL CONSTRUCTION.** Sealed three ways . . . with moisture-free Mollotrol, tough outer plastic shell, exclusive Mallocene!
- **FASTITE LEADS.** Permanently fastened . . . sealed with Mallocene . . . unaffected by soldering-iron heat!
- **DISTORTION-FREE WINDING.** No flattened cartridges due to molding pressures . . . no failures due to "shorts"!
- **TRU-CENTER CARTRIDGES.** Cartridges centered every time . . . uniform insulation guaranteed at all points!

You don't have to handle the Mallory Plascap with kid-gloves . . . it is built to "take it"! See your Mallory Distributor, now. Remember, you pay no more for Mallory Precision Quality!

\*Trade Mark


P. R. MALLORY & CO. Inc.  
**MALLORY**

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS  
• RECTIFIERS • VIBRAPACK\* POWER SUPPLIES • FILTERS

\*Reg. U. S. Pat. Off.

**APPROVED PRECISION PRODUCTS**

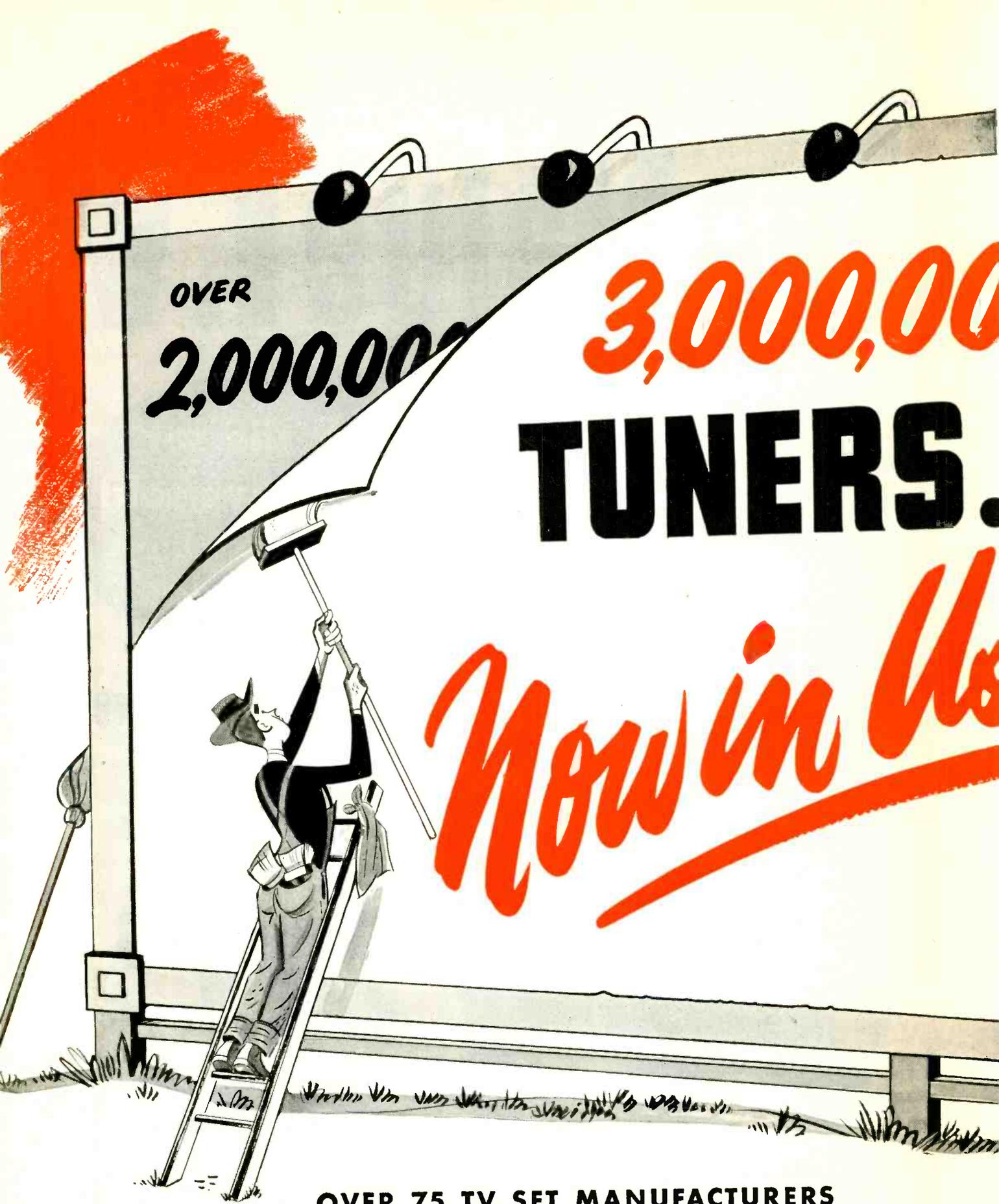**P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA**



OVER  
2,000,000


3,000,000  
TUNERS.

Now in Use



OVER 75 TV SET MANUFACTURERS  
USE "THE STANDARD TUNER"

Standard COIL PRODUCTS CO

10 "Standard"

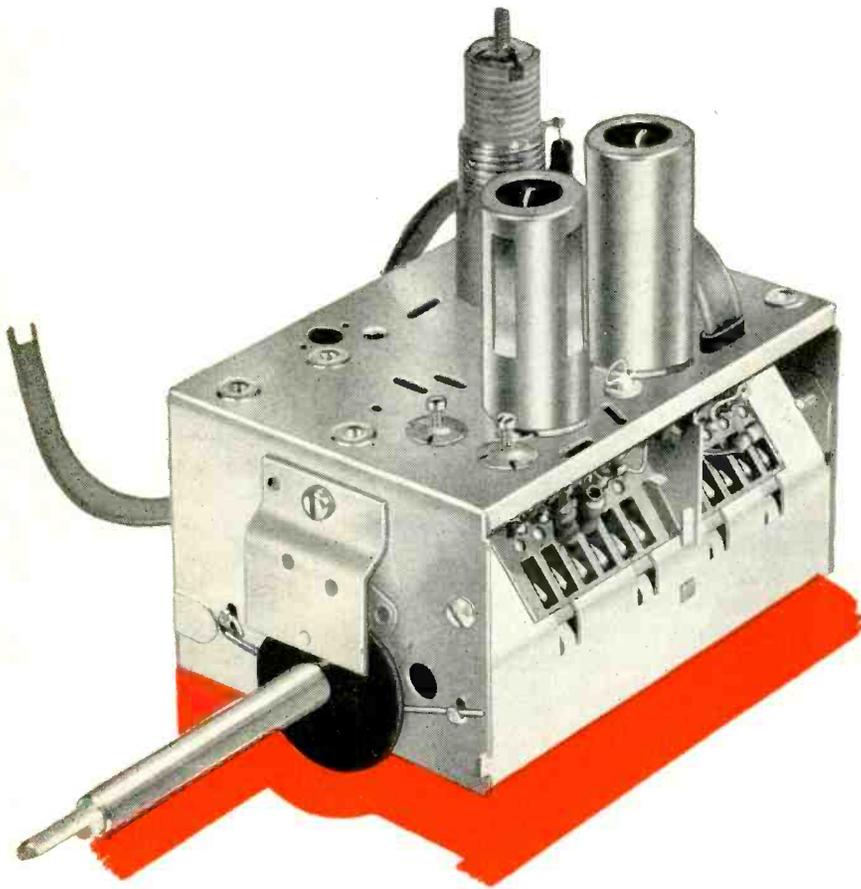


al

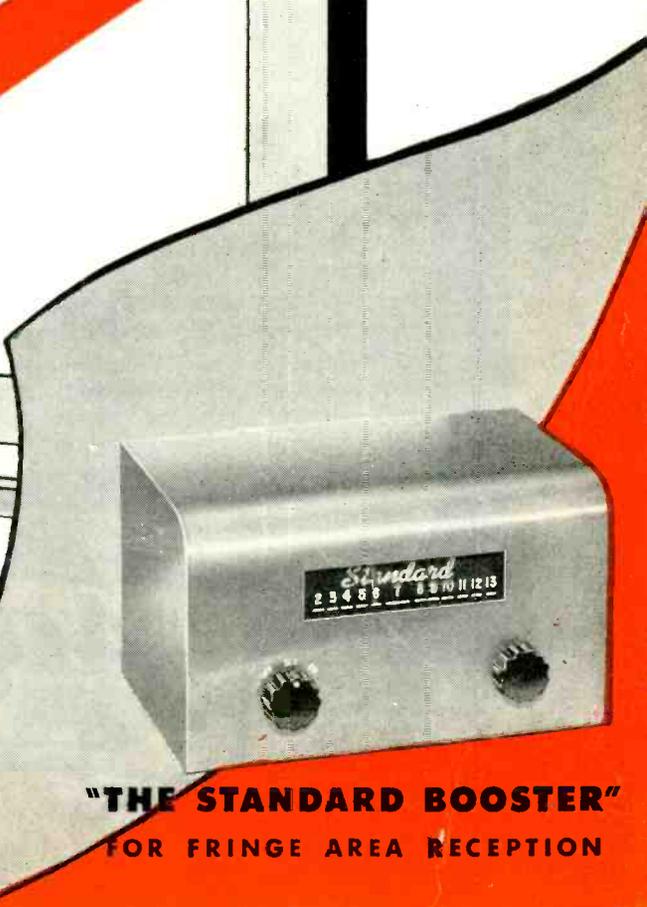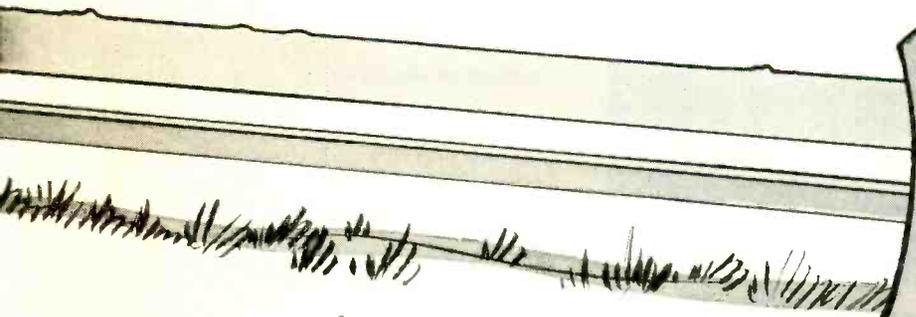

**INC.**  
Chicago  
Los Angeles  
Bangor, Michigan

**"THE STANDARD BOOSTER"**  
FOR FRINGE AREA RECEPTION

# THE EYE IS QUICKER THAN THE EAR

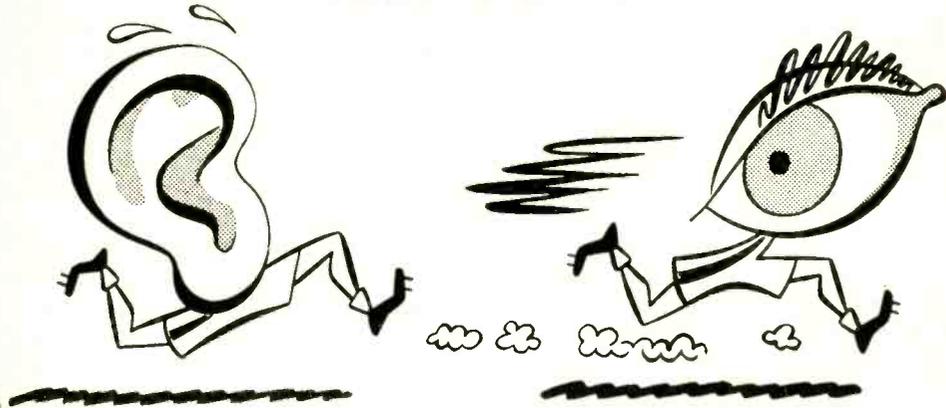

## IF YOU SERVICE TV, YOU KNOW THIS!

Customers are quick to *see* imperfections. Much slower to *hear* them. Therefore *premium-quality* Hytron receiving tubes for the tougher TV jobs. *At no extra cost!* You gain also: Through fewer expensive service call-backs. Better customer satisfaction and confidence. More profits.

How does Hytron do it? By working closely with leading TV set manufacturers. By endless striving

to better already superior performance. By improved design...processing...inspection...testing.

Try Hytron TV receiving tubes: 1X2A, 5U4G, 6AG5, 6AL5, 6AU6, 6BC5, 6BG6G, 6BQ6GT, 6CB6, 6SN7GT, 6V6GT, 6W4GT, 12BH7, 25BQ6GT, etc. Also Hytron rectangular picture tubes: 14BP4, 16RP4, 17BP4A, 20CP4. You pay no more for Hytron. But *see* the difference yourself...on the TV screen...on your cash register.

## THEY COST PENNIES, BUT SAVE DOLLARS!


Order from your Hytron jobber today



**HYTRON SOLDERING AID** — 49¢ net. Fork tip effortlessly, quickly unwraps "mechanically solid" joints. Straddles wire, grips, unwraps, pulls it free. Guides new wire; holds it firm while soldering. Spade tip reams solder from lug hole; pushes other wires aside. Tips are hardened, twist-proof, insulated, hard-chromed to shed solder. Tool handles like pencil. Reaches tight spots. Has dozens of other uses.



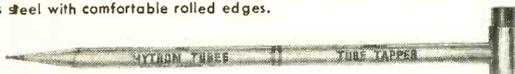**HYTRON TUBE LIFTER** — 15¢ net. Lift 'em all the e-a-s-y prybar way: Tubes (GT, G, standard, lock-in, metal). Vibrators and plugs (Jones, Amphenol) — and knobs. A natural for compact auto radios, etc. Slotted end lifts lock-ins, snap-in trimounts... easily, safely. Of stainless steel with comfortable rolled edges.



**HYTRON TUBE TAPPER** — 5¢ net. Handy combination pencil, eraser and tube tapper. Discovers microphonism, shorts, and opens in tubes, etc. Compact, non-metallic, rugged. Doubles in brass for writing orders, etc.



**HYTRON TUBE PULLER**  
— 75¢ net. Pull or insert 7-pin miniatures the e-a-s-y way. Neoprene rubber puller works by suction and friction on top of tube. Positive grip. Reaches tight spots. Another Hytron time-temper-and-money saver.



**HYTRON PIN STRAIGHTENERS, 7-Pin and 9-Pin** — 55¢ net ea. You merely press tube gently into Hytron Straightener until button base seats squarely. Presto, pins are straight! Fast... safe. Avoiding one broken tube pays for Straightener twice over. Precise, stainless-steel insertion die. Comfortable knurled aluminum holder. For hand, bench or tube tester use.



**HYTRON AUTO RADIO TOOL** — 24¢ net. Substitutes for control cables of universal auto radio. Quickly, precisely turns set on/off, tunes, adjusts volume and tone, re-aligns dial. Square also fits splines. Vee fits spade and other key fittings. Minimum backlash. Compact. Bright-zinc plated. Non-rolling large handle for fine adjustments.




OLDEST MANUFACTURER OF RECEIVING TUBES  
**HYTRON**  
RADIO AND ELECTRONICS CORP.  
MAIN OFFICE:  
SALEM, MASSACHUSETTS



all we can say to you is

# A MERRY CHRISTMAS

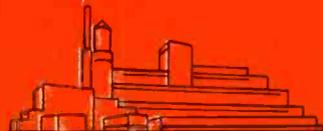

**SNYDER MFG. CO.**



MICA

PAPER

ELECTROLYTIC

CAPACITORS

# The Sangamo Tribe means business




34 little Indians to fill your needs . . .

The Sangamo line offers 34 types of mica, paper, and electrolytic capacitors to take care of practically any replacement requirement in the radio and television field.


For example, the line includes Sangamo Micas, which have enjoyed a reputation for excellence throughout the radio and electronic industry since 1923. It includes the famous "Redskin" . . . the plastic molded paper tubular that is easy to work with because the flexible leads can't pull out. It includes a complete range of Electrolytics that will measure up to the toughest assignments in exacting applications where ordinary electrolytics might cause premature failure.

Sangamo Capacitors are packaged in distinctively designed cartons that you can identify with ease and that make inventory simple.

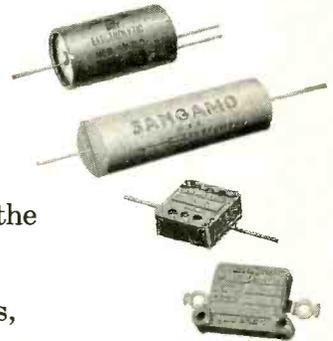A trial of Sangamo Capacitors will convince you. Stock up at your Jobber.



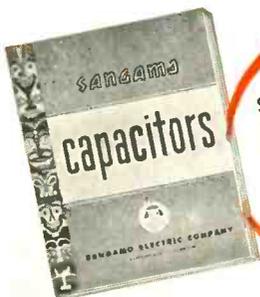*Your Assurance of Dependable Performance*



Send for our new Catalog No. 800. It's the most complete replacement catalog in the industry.

**SANGAMO ELECTRIC COMPANY**  
SPRINGFIELD, ILLINOIS

IN CANADA: SANGAMO COMPANY LIMITED, LEASIDE, ONTARIO

SC60-11A



**SAVE Up to \$1.00 each.**

**Form a Group,  
Service Dealers**

**Subscribe to "RTSD"-**

"The Professional Radio-Television man's Magazine"—published monthly. All articles are exclusive and timely. Practically every issue is worth what an entire 1 year subscription costs.

★ The more in a group the bigger the savings. 6 men in a group save \$1.00 each; 4 men groups save \$ .75 per man. Present "RTSD" subscribers may participate in or form a group with co-workers, or even competitors. Still active subscriptions are automatically extended 1 year. Start a Group today! The timely and exclusive technical data appearing in future issues of "RTSD" will make this the best investment you ever made. The special Group Rate offer may be withdrawn at any time—so hurry.

**Use This Coupon For Convenience**

(The coupon below can be used for from 1 to 6 subscription orders. Use it today!)



**TEAR OUT — MAIL TODAY**

**RADIO-TELEVISION SERVICE DEALER MAGAZINE**  
342 Madison Ave., New York 17, N. Y.

Please enter 1 year subscription orders for the names given below. Our remittance is enclosed.

**NOTE:** If you do not wish to tear this order blank out, just print or type the information on a single sheet of paper, following the style given. Each subscriber's occupation must be clearly described.

	In U.S.A. & Canada	Foreign Rates
<input type="checkbox"/> One 1-year subscription	\$2.00	\$3.00
<input type="checkbox"/> Two 1-year subscriptions, each	1.75	2.75
<input type="checkbox"/> Three 1-year subscriptions, "	1.50	2.50
<input type="checkbox"/> Four 1-year subscriptions, "	1.25	2.25
<input type="checkbox"/> Five 1-year subscriptions, "	1.10	2.00
<input type="checkbox"/> Six 1-year subscriptions, "	1.00	1.50

Name .....

Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

Name .....

Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

Name .....

Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

Name .....

Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

Name .....

Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

Name .....


Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

Smart TV Dealers are

# HITTING THE TENNA-ROTOR JACK-POT!

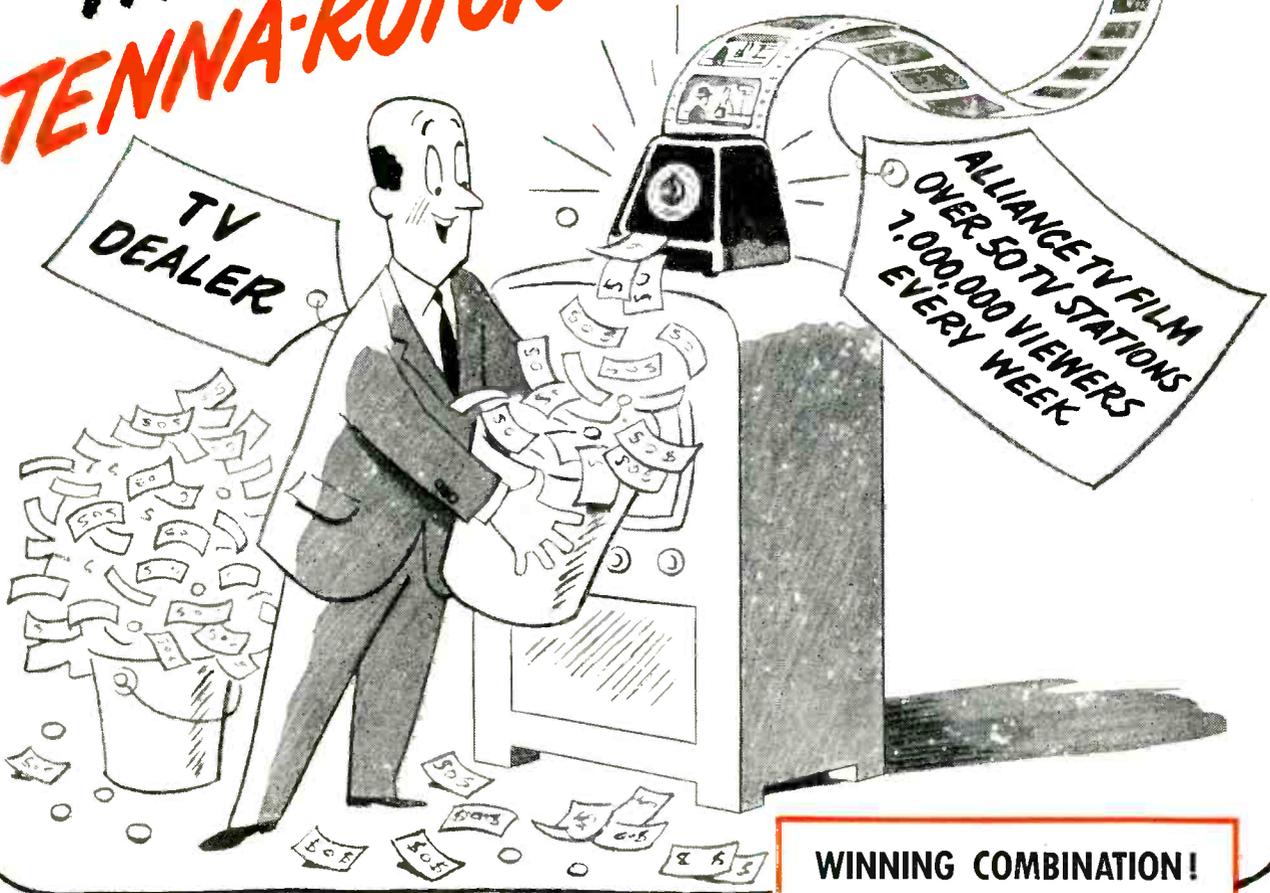

## **PROOF IS IN RESULTS!** Nation-wide TV Advertising Delivers Thousands of Sales—Every Week!

Over 50 key TV stations demonstrate Alliance Tenna-Rotor to 7 million viewers! Tenna-Rotor is the only TV accessory backed by a powerful, sustained television campaign—national in scope! Hundreds of thousands of Alliance Tenna-Rotors are in use!

Alliance Tenna-Rotor offers faster installation with Alliance 4-conductor "Zip" cable—Works in all weather—Guaranteed for one year—Approved by Underwriters' Laboratories.

**NEW DELUXE MODEL HIR IS FULLY AUTOMATIC!**

## **WINNING COMBINATION!** *Just Set It and Forget It!*

The only fully automatic rotator. Set the pointer—antenna turns to that point and stops! North—East—South—West—direction indicator dial shows exact antenna position at all times. Extremely accurate!



MODEL HIR TENNA-ROTOR

## **ALLIANCE TENNA-SCOPE**



—the New TV Booster! Features one simple control. Automatic on-off switch. Gives maximum uniform high gain on all channels—quick to install! An excellent companion item to Tenna-Rotor.

TENNA-SCOPE

**ALLIANCE MANUFACTURING COMPANY • Alliance, Ohio**

THE QUALITY OF RCA TUBES IS UNQUESTIONED



## *Best Sellers*

### **IN PICTURE TUBES...**

Most used . . . by brand  
and by type . . . RCA kinescopes  
are the fast-moving  
profit makers

The largest and most profitable replacement business in television picture tubes comes from the types used in most television receivers . . . the Best Sellers.

RCA's types are Best Sellers. There are more of them in actual use in TV receivers than any other brand. Industry choice of these high-volume types reflects to your advantage. Inventory and stocking problems are simplified . . . and you have the assurance of rapid, profitable turnover.

In addition, when you sell RCA kinescopes, you gain from customer confidence in the RCA brand . . . solidly established by the proved performance of RCA kinescopes in millions of television receivers.

Remember, too, that the quality and dependability of RCA kinescopes mean fewer service failures and fewer costly call-backs. There is, therefore, more profit in every RCA kinescope you sell.


*Always keep in touch with your RCA Tube Distributor*



**RADIO CORPORATION of AMERICA**  
ELECTRON TUBES

HARRISON, N. J.

# THE EYE IS QUICKER THAN THE EAR

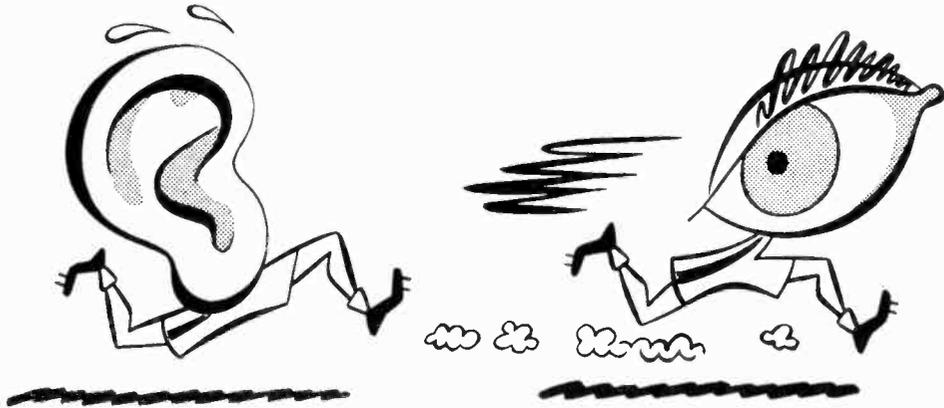

## IF YOU SERVICE TV, YOU KNOW THIS!

Customers are quick to *see* imperfections. Much slower to *hear* them. Therefore *premium-quality* Hytron receiving tubes for the tougher TV jobs. *At no extra cost!* You gain also: Through fewer expensive service call-backs. Better customer satisfaction and confidence. More profits.

How does Hytron do it? By working closely with leading TV set manufacturers. By endless striving

to better already superior performance. By improved design...processing...inspection...testing.

Try Hytron TV receiving tubes: 1X2A, 5U4G, 6AG5, 6AL5, 6AU6, 6BC5, 6BG6G, 6BQ6GT, 6CB6, 6SN7GT, 6V6GT, 6W4GT, 12BH7, 25BQ6GT, etc. Also Hytron rectangular picture tubes: 14BP4, 16RP4, 17BP4A, 20CP4. You pay no more for Hytron. But *see* the difference yourself...on the TV screen...on your cash register.

## THEY COST PENNIES, BUT SAVE DOLLARS!

Order from your Hytron jobber today



**HYTRON SOLDERING AID** — 49¢ net. Fork tip effortlessly, quickly unwraps "mechanically solid" joints. Straddles wire, grips, unwraps, pulls it free. Guides new wire; holds it firm while soldering. Spade tip reams solder from lug hole; pushes other wires aside. Tips are hardened, twist-proof, insulated, hard-chromed to shed solder. Tool handles like pencil. Reaches tight spots. Has dozens of other uses.



**HYTRON TUBE LIFTER** — 15¢ net. Lift 'em all the e-a-s-y prybar way: Tubes (GT, G, standard, lock-in, metal). Vibrators and plugs (Jones, Amphenol) — and knobs. A natural for compact auto radios, etc. Slotted end lifts lock-ins, snap-in trimounts...easily, safely. Of stainless steel with comfortable rolled edges.



**HYTRON TUBE TAPPER** — 5¢ net. Handy combination pencil, eraser and tube tapper. Discovers microphonism, shorts, and opens in tubes, etc. Compact, non-metallic, rugged. Doubles in brass for writing orders, etc.



**HYTRON TUBE PULLER** — 75¢ net. Pull or insert 7-pin miniatures the e-a-s-y way. Neoprene rubber puller works by suction and friction on top of tube. Positive grip. Reaches tight spots. Another Hytron time-temper-and-money saver.



**HYTRON AUTO RADIO TOOL** — 24¢ net. Substitutes for control cables of universal auto radio. Quickly, precisely turns set on/off, tunes, adjusts volume and tone, re-aligns dial. Square also fits splines. Vee fits spade and other key fittings. Minimum backlash. Compact. Bright-zinc plated. Non-rolling large handle for fine adjustments.




**HYTRON PIN STRAIGHTENERS, 7-Pin and 9-Pin** — 55¢ net ea. You merely press tube gently into Hytron Straightener until button base seats squarely. Presto, pins are straight! Fast... safe. Avoiding one broken tube pays for Straightener twice over. Precise, stainless-steel insertion die. Comfortable knurled aluminum holder. For hand, bench or tube tester use.



MAIN OFFICE:  
SALEM, MASSACHUSETTS



**CLEARER PICTURES**

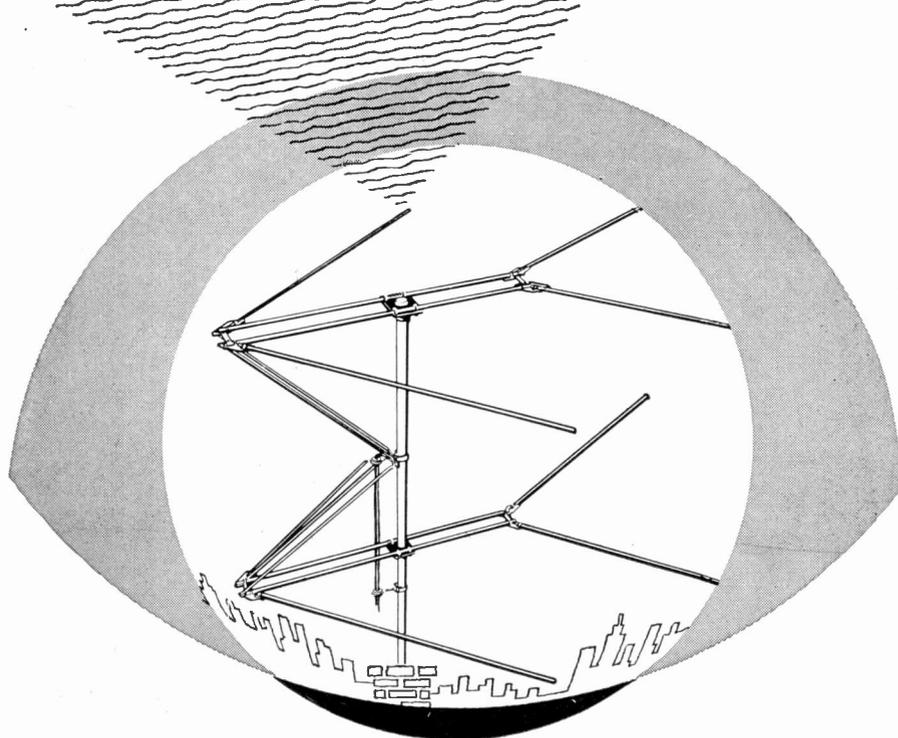

# WORKSHOP

**DUBL - VEE TV ANTENNA**  
PATENT PENDING

By applying the proven "end-fire" principle to TV antennas the WORKSHOP DUBL-VEE set the pace for 1950. Its quick acceptance — over 80,000 installed in three short months — is a testimonial to WORKSHOP'S acknowledged leadership in antenna design and engineering.

The DUBL-VEE is typical of WORKSHOP antennas in other fields — commercial, amateur and aircraft. In every instance, advanced engineering and outstanding performance have established ready acceptance. You know when you specify the DUBL-VEE, or any other WORKSHOP antenna, that you are getting the best.

Write for Bulletin E



**THE WORKSHOP ASSOCIATES, Inc.**

135 CRESCENT ROAD, NEEDHAM 94, MASSACHUSETTS

any serviceman knowing he would be prosecuted for malpractice would cease and desist evildoings pronto. The only catch is that at present ARSNY's treasury is low and if many legal actions were required, it might fast become depleted. To prevent such an event from occurring, it would seem advisable for set distributors and manufacturers to contribute to the ARSNY legal fund, knowing that their money is merely being placed in care of ARSNY to be used only when and if such expenditure becomes necessary. Police action of the TV service industry *by the industry itself* is the surest and quickest way of accomplishing desired results. Manufacturers and dealers have done nothing to protect the public; now it is incumbent upon the servicemen to handle the matter themselves.


### **Injunction Stops Immediate Color TV-casts by Non-Compatible CBS Method**

Judges Major, Sullivan and LaBuy, sitting in the Circuit Court in Chicago on November 14th and 15th, heard RCA and many other TV manufacturers request that FCC and CBS be restrained from beginning color transmission on Nov. 20th. Anyone not legally trained who heard both sides of the case would agree that the Judges' decision to issue a temporary restraining order favoring RCA *et als* was fitting and proper. For example, it seemed to us that FCC's main contention was merely to the effect that "we have studied this matter for a long time and now we want to wind it up, so, having decided in favor of the CBS system, why not let it go at that?" In contrast, RCA *et als* came up with some basically sound points in their argument, outstanding of which were these: 1) - a good, compatible color TV system is not yet available, so why try to foist upon a public (that doesn't care one way or the other about a system's technical makeup) something that will cost the present-day TVset owners 2½ billions of dollars. 2) — why accept a system that will not have for a very long period of time much of an audience, because it is generally conceded that none of the major set makers intended to swing their production from conventional black and white TV models to a mechanical system that would cost vastly more, have but limited sale, look atrocious, and most important, not be able to bring to people the worthwhile TV commercially sponsored programs. 3) — the trend is towards large size picture screens by popular demand, [Continued on page 40]



all we can say to you is

# A MERRY CHRISTMAS

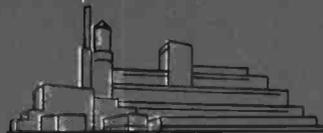


**SNYDER MFG. CO.**

**This article discusses the basic theory of keyed a.g.c. as well as various commercial circuits and their applications.**

Inoperative a.g.c. can cause excessive contrast, weaving of picture and sync instability when a strong station is tuned in.

by Matthew Mandl

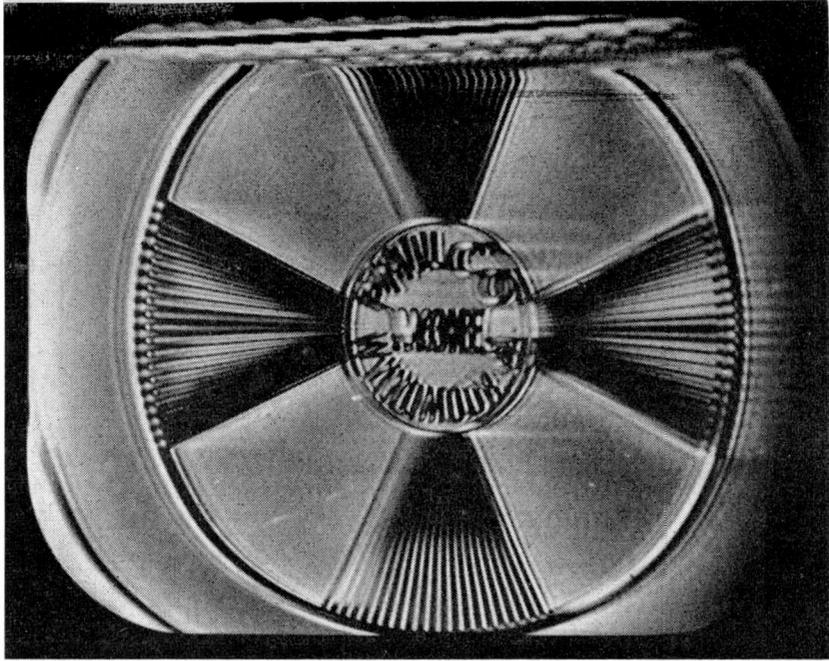

# OPERATION & SERVICE of KEYED AGC SYSTEMS

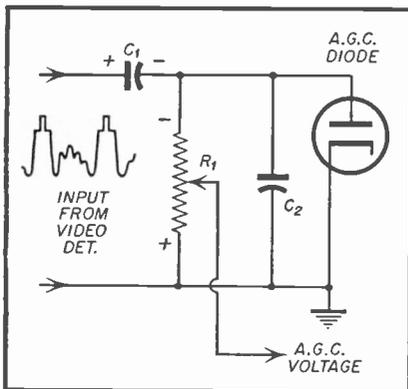


Fig. 1. Basic circuit of conventional a-g-c system.

**I**N their later model television receivers most manufacturers are using keyed AGC circuits instead of the older, more conventional type of automatic gain control. The reason for this is because of the superiority of keyed a.g.c. in terms of noise suppression and the reduction of airplane flutter. Since these advantages are achieved primarily by circuit design rather than by adding a number of extra tubes or parts to the conventional system, the manufacturer is enabled to improve his receiver without material increase in costs.

The keyed a.g.c. process is more easily understood by comparing it with the older, conventional method.

The latter, in its basic form, is illustrated in *Fig. 1*. Here, the detected composite video signal is injected into the circuit in a positive-going polarity. This causes the a-g-c diode to conduct, charging  $C1$  to the peak value of the sync tips. The time constant of  $R1$  and  $C2$  is made quite long so that  $C1$  will remain charged to almost full value between sync tips. The charge across  $C1$  appears across  $R1$  and represents the a-g-c voltage which is used to establish the bias level on the r-f/i-f picture amplifier tubes of the receiver. Potentiometer  $R1$  can be adjusted to get the proper degree of bias control on the amplifier tubes.

While the amplitude of the picture signal varies during transmission, the level of the sync tips is held constant at the transmitter. The bias developed in the a-g-c system, therefore, will also be held at a fixed value unless the station fades. If this occurs, there will be less voltage available at the a-g-c tube and the charge across capacitor  $C1$  will decrease in proportion. This, in turn, decreases the negative bias applied to the amplifier tubes and thereby increases the gain of these stages to compensate for the fading.

Inasmuch as the vertical sync pulses (60 cps) are also present in the composite video signal applied to the

a-g-c circuit, the long time constant is necessary to filter these out. Because of this long time constant, the a-g-c voltage is relatively unaffected for any changes in signal amplitude unless this change occurs over an appreciable time interval. Thus, this system does not respond to the rapid increase and decrease of signal caused by reflections from an airplane.

Besides this, if the signal to noise ratio in the area is poor, the noise impulses may add a sufficient voltage to the a-g-c system to materially decrease the gain of the amplifiers due to the excess bias which is developed. This proves of decided disadvantage, and cannot be corrected by the contrast control, for the latter is usually located in the video amplifier stages when a.g.c. is used.

In some of the earlier receivers an extra tube was employed for noise filtering, but this added to manufacturing costs and still left unsolved the case of airplane flutter. With the advent of *keyed a.g.c.*, however, both problems were solved with a circuit virtually as simple as the conventional a.g.c. but much more ingenious in design principles.

## How Keyed AGC Functions

*Figure 2* shows the basic keyed a-g-c circuit. Here, a small positive voltage is applied to the cathode which, in

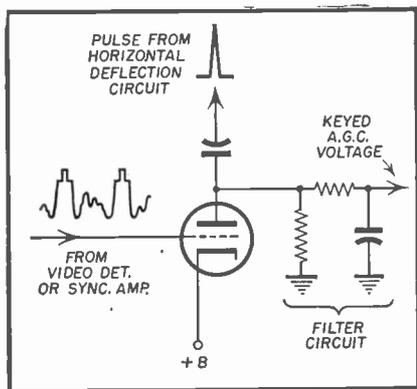


Fig. 2. Basic circuit of keyed a-g-c system.

turn, will make the plate negative with respect to this positive potential. The plate cannot conduct, therefore, unless this negative charge is overcome. A positive going, spike-appearing voltage is procured from the horizontal deflection circuits and applied to the plate of the a-g-c tube. This positive spike is of sufficient amplitude to overcome the negative charge on the plate and cause the tube to conduct. Tube conduction occurs, therefore, at the 15,750 rate of the horizontal sweep circuit, or once every 15,750th second.

The composite video signal from the detector, or the blanking and sync tips from the sync amplifier are applied to the grid of the a-g-c tube. The bias is so arranged that only the sync tips will allow the tube to conduct—that is, the bias is set so far negative that it takes virtually the entire amplitude of the positive blanking—sync tip signal to decrease bias sufficiently to allow current flow through the tube.

We have, therefore, a condition where neither the grid signal alone, or the spiked pulse on the plate alone, will cause conduction of the tube. Both must be present in order for the tube to function. Inasmuch as the sync tips are keeping the horizontal oscillator in proper frequency lock, both sync tips and horizontal pulse will occur at the same time. If the station fades, the sync tips will be lower in amplitude and cause less current flow through the tube, and thus develop less a-g-c bias voltage at the output. Less bias on the amplifier stages will increase their gain and compensate for the decreased signal due to fading.

Inasmuch as the a-g-c tube does not conduct between sync pulses, the video signals or any noise signals riding on them have no influence on the a-g-c voltage. At the same time the filter circuit at the plate need not have a long time constant, for it is

only necessary to filter out the 15,750 ripple frequency. The relatively short-time constant makes the system sensitive to the rapid changes of signal due to airplanes.

#### Typical Commercial Circuits

Figure 3 indicates the type of keyed a-g-c employed by Westinghouse in various models of their receivers using the V-2150 series chassis. The similarity between this and Fig. 2 is readily apparent, the only innovation being the use of a 150 ohm section of twin lead from the horizontal circuits to the plate of the 6BH6

sync amplifier are applied to the grid of the 6BH6 and serve to key the system into operation.

The correct amount of bias for proper operation of the a.g.c. is established by the relationship of the plus voltage at the grid and that at the cathode. The voltage at the grid due to direct coupling from the 1st sync amplifier is approximately 70 volts. The positive potential of approximately 95 volts at the cathode, will make the grid negative with respect to the cathode by the difference between the two voltages, or 25 volts.

Figure 4 shows the type of a-g-c circuit used by Zenith in their 24G20 series TV receivers. Zenith refers to their system as "Gated AGC" and its function is essentially the same as the keyed systems previously discussed. The a-g-c triode is one-half of the 12AT7 which also contains the video detector. The i-f signal from the secondary of the 3rd i-f transformer is applied to the grid of the a-g-c tube through a 200 $\mu$ f coupling capacitor. During the positive half-cycles of this i-f voltage plate conduction occurs because of the presence of 15,750 cps pulses from the horizontal oscillator. Since the frequency of grid and plate signals coincide, the a.g.c. has an "open gate condition" only during the time duration of the applied sync pulses. During the interval between pulses the tube is non-conductive (gate closed) and therefore immune to noise signals present between horizontal sync time. The period of tube conduction can be changed by the potentiometer in the cathode circuit.

Some keyed a-g-c systems utilize more than one tube if additional refinements or greater a-g-c control is desired. An example of this may be found in the DuMont TV receivers and the one employed in their Model RA-105 is shown in Fig. 5.

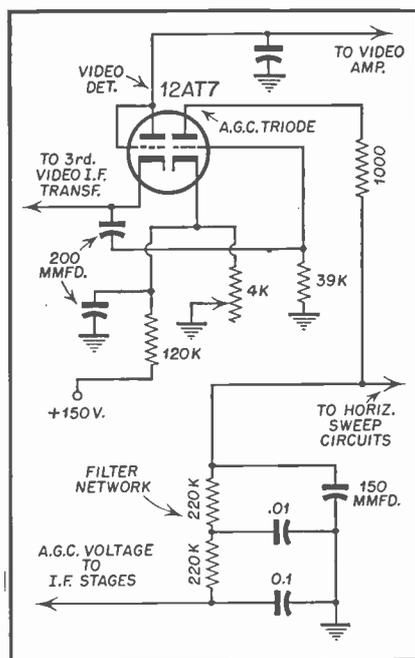


Fig. 4. Zenith a-g-c system.

a-g-c tube. The capacity existing between the two wires of the transmission line is used for coupling the spiked pulse to the plate of the a-g-c tube. The 130 volts screen potential is dropped down to 95 volts for the positive potential necessary at the cathode. Sync pulses from the first

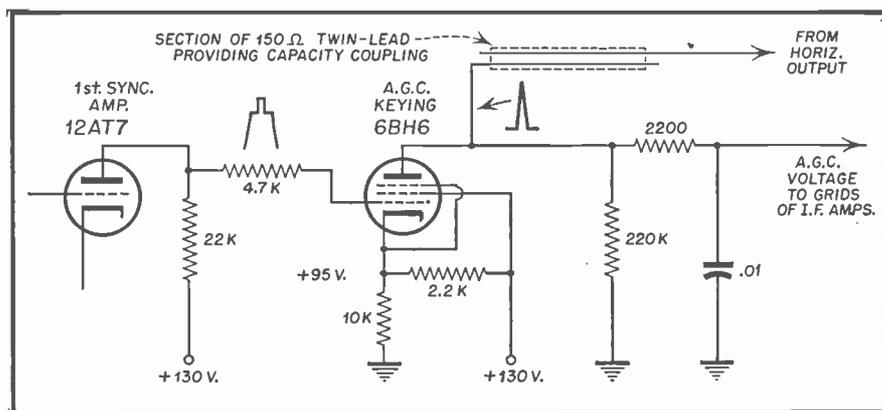


Fig. 3. Basic circuit of keyed a-g-c system used by Westinghouse.

The signal from the output of the video i-f stage is applied to the plate of the a-g-c diode 6AL5 tube. As with the Zenith previously discussed, this tube conducts on the positive half cycle of the input signal sync pulses. An RC filter is used to couple the voltage present in the cathode circuit to the grid of the 6AT6. This means that the grid receives a positive d-c voltage which has an amplitude depending on picture signal, and this d.c. controls the gain of the triode portion of the 6AT6 tube. A 15,750 signal which is primarily a square wave is also applied to the grid of V209 and this is procured from the plate of the horizontal oscillator. This square wave signal is also amplified by the triode, though the gain depends on the d-c signal derived from the 6AL5 a-g-c diode.

The amplified signal appearing in the plate of the triode section is coupled to the upper of two diode plates in the same tube envelope. The diode rectifies this signal and thereby develops a negative potential which appears across R246 and R247. The filter network (R244 and C226) smooths out variations and assures substantially ripple free d.c. for a-g-c bias purposes at the grids of the picture i-f stages. When the incoming signal to the receiver changes in amplitude, the gain of the triode is altered and the resultant bias corrected to compensate for the changes in the received signal.

Circuit variations other than those shown in the foregoing examples will, of course, be encountered in the field. Essentially however, all keyed a-g-c systems function on the same basic principles—bias is developed during tube conduction, and the latter can only occur when both sync tips and horizontal sweep signal are applied to the a-g-c circuit simultaneously.

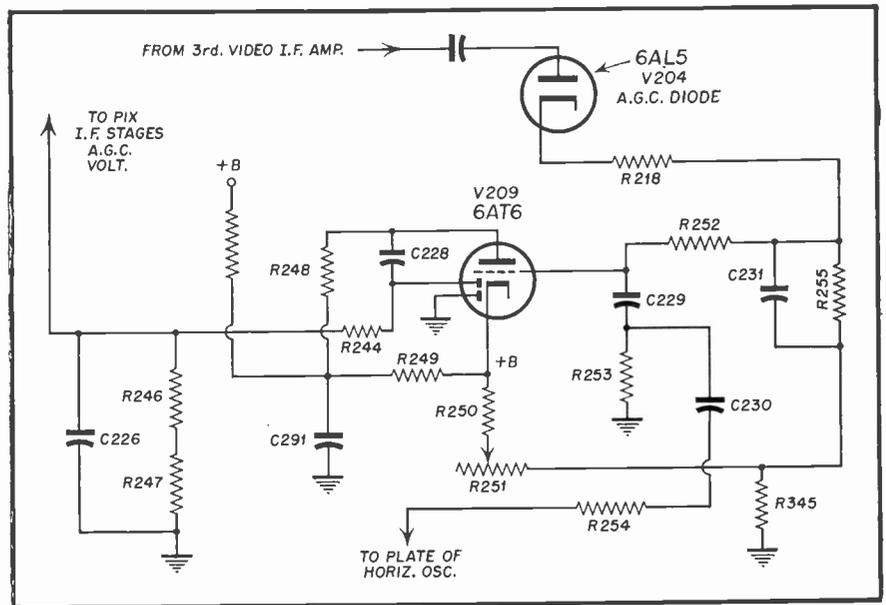


Fig. 5. DuMont a-g-c system.

### Service Notes

Because the purpose of any a-g-c system is to maintain a constant picture signal level by controlling the bits applied to the r-f/i-f stages, the lack of such bias is a positive indication of a-g-c circuit failure. The best method for ascertaining the presence of the a-g-c bias is to tune the receiver to a station and measure the voltage existing at the grid of the first or second video i-f amplifiers. Use only a vacuum tube voltmeter so that the impedance of the measuring device will not materially effect the circuit. The bias should change when the receiver is tuned to other channels. A stronger station should develop greater bias, while a decrease in the a-g-c bias will be noticed for the weaker stations. Figure 6 shows a typical a-g-c filter network usually found in the i-f stages, and method for measuring a-g-c voltage is also

shown. The VTVM should be switched to read *minus* d-c voltage.

A change in tube characteristics or complete failure of the a-g-c tube is a common cause for faulty a-g-c operation. If tube conduction had decreased, sufficient bias will not be available for strong signal inputs, and in consequence the stages are overloaded. Bending and tearing of the signal appearing on the screen will result. This is identical to the condition set up in sets not having a-g.c., where the contrast control is set up too far on a strong local station.

An open circuit in the line feeding the pulse from the horizontal circuits to the plate of the a-g.c will also cause failure of a-g.c., because the tube will no longer conduct. The resultant zero bias will cause excessive gain, and this uncontrolled amplification will again result in picture instability and excess contrast.

Filter capacitors C<sub>2</sub> and C<sub>3</sub> in Fig. 6 usually give little trouble because very little d-c voltage appears across them. When these give trouble, it is usually due to a capacitor which was defective or poorly constructed during manufacture. Occasionally these will be damaged by excessive heat generated by other components which have been placed too close. A shorted C<sub>2</sub> and C<sub>3</sub> will, of course, short out the a-g-c voltage and again the r-f or i-f amplifier tubes will be running with excess gain due to insufficient bias. Opening one side of these capacitors and checking with an ohmmeter will establish whether

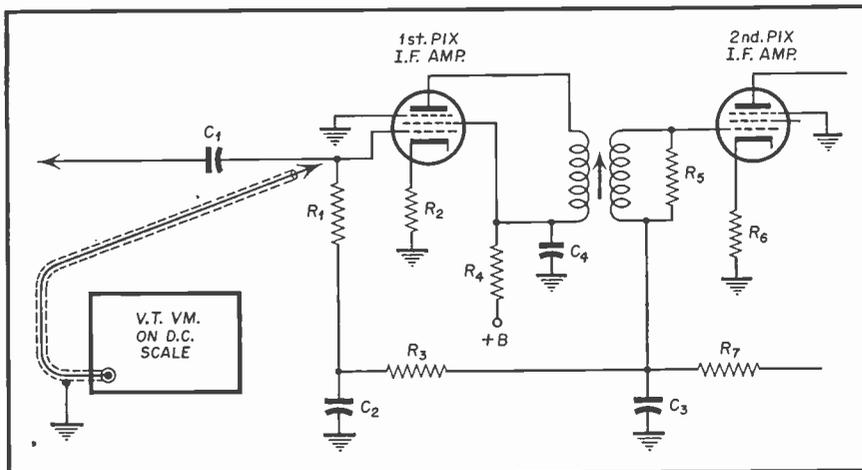


Fig. 6. Method for testing a-g-c voltages.

[Continued on page 44]

# Sampling Techniques APPLIED TO TELEVISION

by EDWARD M. NOLL

(Author of "Television for Radiomen")

In last month's article, sampling & multiplex techniques were introduced. Practical examples of sampling technique have been demonstrated by the RCA color television system and by the high definition black and white experiments conducted by the Philco Corporation. The use of sampling has permitted RCA to produce a color picture with excellent resolution on only a six megacycle channel. Sampling in black and white systems has permitted monochrome resolution figures approximately double that which can be obtained by our present commercial system in a standard 6 megacycle spectrum.

In our present black and white television system a possible maximum of 400 horizontal elements can be conveyed from transmitter to receiver. Frequency response of the system to convey these 400 elements must be in excess of  $3\frac{3}{4}$  megacycles.

## RCA Color TV System

Inasmuch as the frequency components in a video signal extend up to this high frequency, sampling rate must be exceptionally high. In the RCA system a sampling rate of 3.8 megacycles is recommended. This would at first seem to limit the high response to one-half of this frequency rate or 1.9 megacycles. However, in the RCA system a method of mixed highs is employed to obtain an equivalent resolution. Thus a sampling rate of 3.8 megacycles, use of mixed-high transmission, and a method of dot interlacing permit a high resolution color picture to be conveyed.

A color system, Fig. 1, uses three color interpretations—green, red and blue. Each of the color signals feed a low pass video amplifier which has a frequency range up to 2 megacycles. The output of these amplifiers are sampled at a 3.8 megacycle rate, breaking up the individual color video signals, up to a frequency limit of 2 megacycles (approximately one-half the sampling rate frequency). The frequencies in excess of 2 megacycles (from 2 to 4 megacycles) are mixed together in a mixer or added produc-

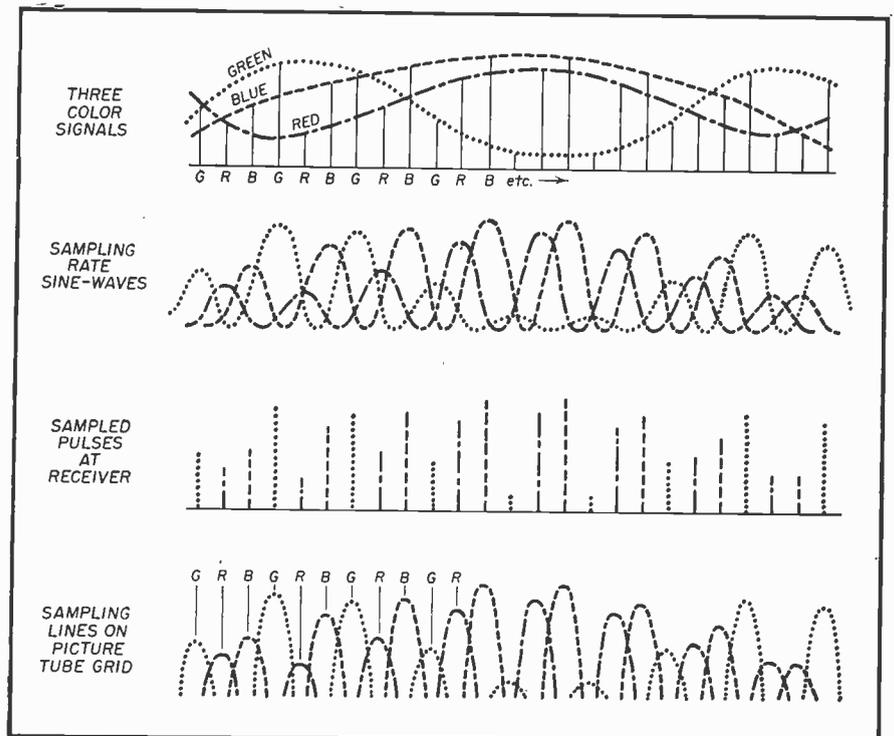


Fig. 2. Method of converting individual color signals into 3.8 mc sine waves. At the receiver a separate sampling circuit separates the colors and impresses them on the picture tube in their proper phase and amplitude relations.

ing a composite signal from the three colors which is representative of the definition of the picture in form of half-tone levels. It has been found that the definition of the picture is represented in the higher frequencies and that they need not be broken

up into individual color elements to reproduce a highly resolved picture. Frequencies below 2 megacycles are apportioned, sampled and broken up into color levels that are a function of the amplitude levels of the three basic colors in the object.

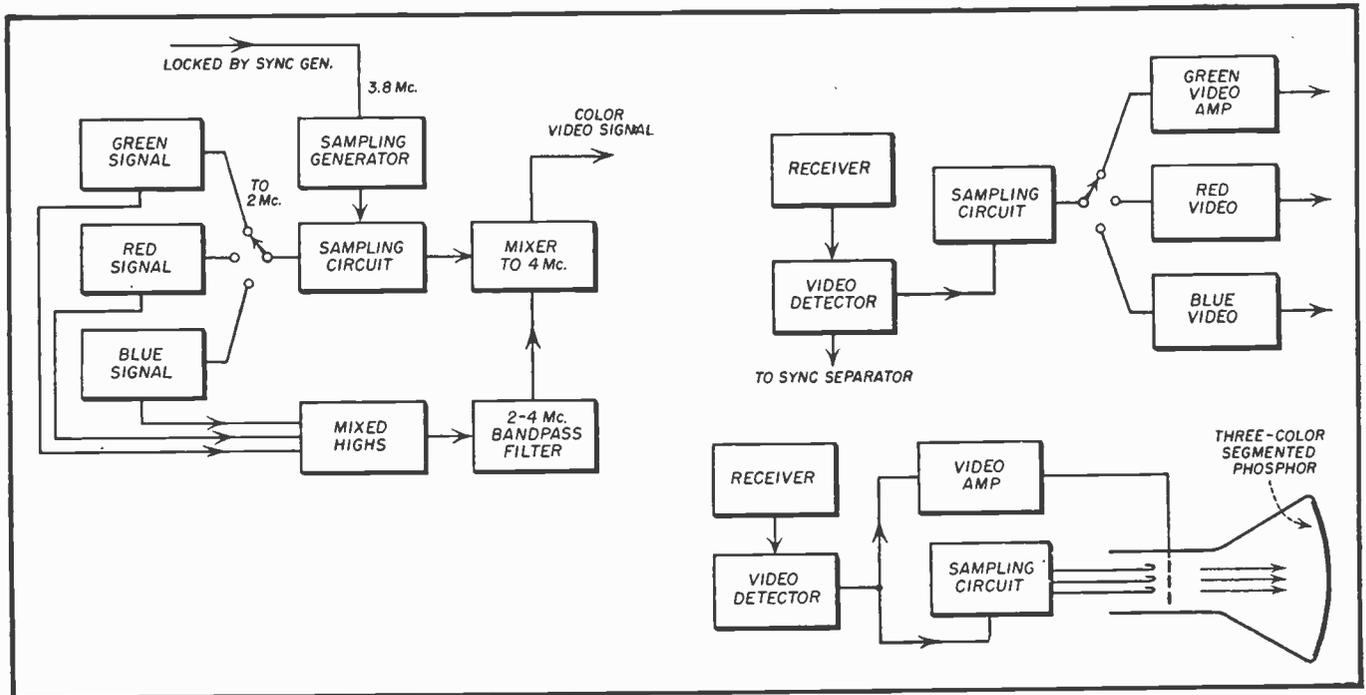


Fig. 1. Block diagrams of RCA color system for transmitter and receiver.

A standard scanning sequence is used for each camera and the output of the sync generator used must not be too different from that used in present commercial practice. A special pulse is used, however, to control the sampling generator which forms a pulse that keys the output of the three color video amplifiers at the proper instant permitting their signals to reach the output mixer video amplifier.

The action of the sampling system can be seen from the waveforms of Fig. 2. Each of the individual colors in accordance with their respective amplitudes and variations are sampled and produce corresponding pulses at the output of the sampling system. Again, the repetition rate of these pulses is the 3.8 megacycles interruption frequency, and as they are passed through the mixer video amplifier, which has a frequency response no

higher than 4 megacycles, the pulses are converted into a 3.8 megacycle sine wave. Again the amplitude of this sine wave is a function of the amplitude of the pulse and, therefore, a function of the individual color intensities.

It is to be observed there is a separate train of 3.8 megacycle sine waves for each color. Relation between these respective sine waves is such that other two sine waves are passing through zero or below at the instant any one sine wave is at its crest value. Thus the crest of the sine wave represents the peak amplitude of the pulse from which it was derived. If these three sine waves are added, a composite sine wave of this same frequency is obtained, amplitude and phase of which is a function of the respective amplitudes of the three sine waves that form it. The average level of this composite is a function of the d-c

components of brightness of these various color signals which make up the composite. As observed from the original color sine waves, the average level of each is a function of the average brightness of that color over a finite time. Thus the instantaneous variation and the average brightness level of each color is conveyed by the sampling system. The color composite video signal is combined with the mixed-highs output of the filter (which only passes the mixed-highs) to produce the complete video signal that is used to modulate (after proper amplification and insertion of pulses) the carrier of the color picture transmitter.

#### Color Receiver

At the receiver this information is picked up in a receiver using a conventional r-f and i-f section. The color video signal at the output of the video detector is applied to a sampler circuit which has been synchronized with the operation of the sampler at the transmitter. Thus the video signal is again broken up into 3.8 megacycle pulse components, one group of pulses for each basic color. The pulses are segregated into three separate color video amplifiers again and will be used to excite three separate picture tube grids. Frequency response of the individual video amplifiers is not much in excess of the 3.8 megacycle sampling rate. Nevertheless, each video amplifier is capable of passing the individual color samples in the form of a 3.8 megacycle sine wave and along

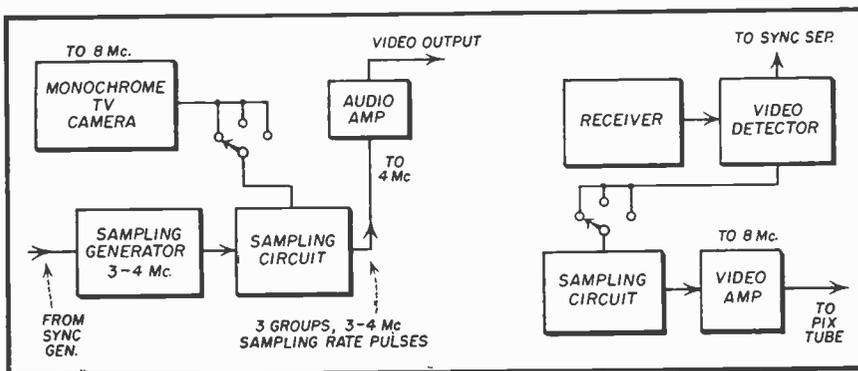


Fig. 3. Sampling principles applied to black and white transmission for high definition transmission and reception.

[Continued on page 42]

# FRONT ENDS

by Samuel L. Marshall

(From a forthcoming book, "Television Installation Techniques")

## Part 6

**T**HE alignment of TV Front Ends consists essentially of two sets of operations. The first is to obtain the required bandwidth and gain, this being accomplished by:

1. Adjusting suitable capacitance trimmers which control the response characteristics over certain frequency limits.

2. Adjusting the circuit inductances for optimum response. The second set of operations consists of adjusting the oscillator trimmers so that the correct i-f response is produced in the plate circuit of the mixer.

In general, Front Ends may be interchanged with slight alterations between split-sound and intercarrier receivers. Basically, all one has to do in order to adapt a Front End designed for split-sound use to intercarrier operation is to remove the sound trap. In some receivers the latter is used to partially attenuate the sound signal as required in intercarrier reception. For purposes of explanation, the block diagrams of intercarrier and split-sound systems are shown in Fig. 3-45.

### Response Curves

A typical set of response curves corresponding to the output obtained at point A in both systems is shown in Fig. 3-46. This set of curves repre-

**In this installment the basic principles of alignment are discussed together with necessary precautions to be followed to insure observation of the proper response curves. A typical alignment procedure is included.**

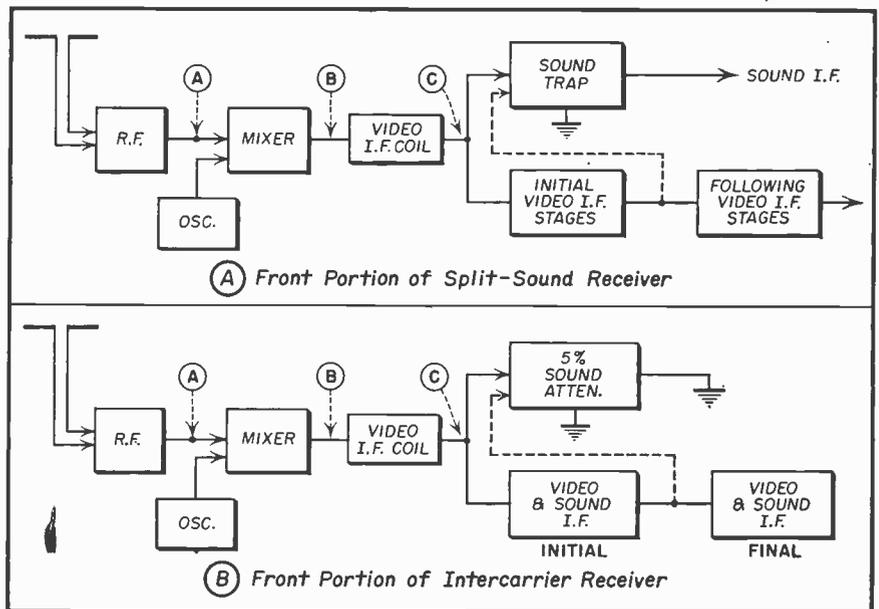


Fig. 3-45: Front portions of split-sound (A) receiver, and intercarrier (B) receiver.

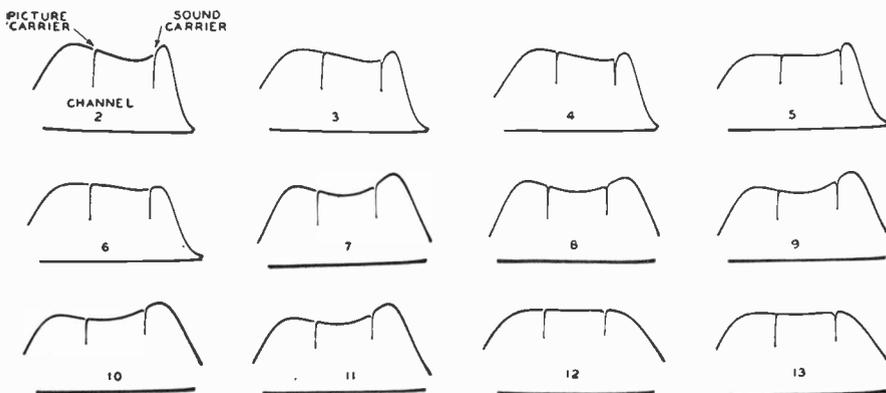


Fig. 3-46: Typical set of r-f response curves obtained in a commercial receiver. (Courtesy RCA)

sents the r-f output for either type of receiver. Notice that in each curve the response is fairly symmetrical around the center frequency of each channel, no attempt being made at this point to favor the sound or video carriers at either end of the channels.

The response at the output of the mixer (point B) is also symmetrical; this time, however, the center frequency is at the center of the i-f band. In all types of receivers a converter transformer is connected at the output of the mixer tube so that the i-f response curve is first influenced by this component. Then, as

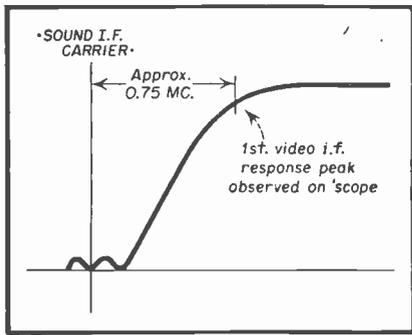


Fig. 3-47A: Correct partial i-f response curve—split sound.

the signal leaves the plate circuit of this transformer and enters the various video and sound i-f stages its response may be further influenced by other circuit components such as sound and adjacent channel traps.

Many split-sound receivers allow the sound signal to be amplified together with the video i-f signal for one or two stages of overall amplification before the sound is diverted to the sound i-f section. This is indicated by the dotted lines shown in Fig. 3-45A. The i-f response after adjustment of the sound trap appears as shown in Fig. 3-47A. This corresponds to the output at point C in Fig. 3-45A.

Proper intercarrier operation requires that the sound i-f carrier level be reduced to about 5% of the corresponding video i-f level. This reduction usually takes place in the converter output or in one of the earlier video i-f stages. Figure 3-47B illustrates the i-f response taken at point C of Fig. 3-45B.

#### Alignment

It will be recalled that symmetrical response curves around the center r-f frequency are called for when align-

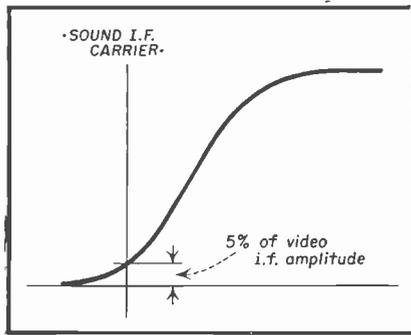


Fig. 3-47B: Correct partial i-f response curve—intercarrier.

ing r-f stages. Because of the wide frequency range of these response curves it is difficult to align these stages with a single frequency and an output meter as is the general practice in AM receivers. Instead, it becomes necessary to employ a sweep generator capable of inserting a wide band of frequencies into the r-f stages, and to adjust the various trimmers so that the required response curve as observed on an oscilloscope is obtained.

A typical test set-up of this type is illustrated in Fig. 3-48. Certain equipment must be used and basic rules observed in hook-ups of this type which apply to all alignments of this nature. These are as follows:

1. *Sweep:* The amount of sweep employed should be more than enough to encompass a complete r-f bandwidth. Because the r-f stage response is generally greater than 6 mc recommended r-f sweep settings are 15 mc.
2. *H-F Probe:* The type of signal at all r-f points except in the grid circuit of the mixer is a modulated r.f. Measurements made at these points, in order to be observed, re-


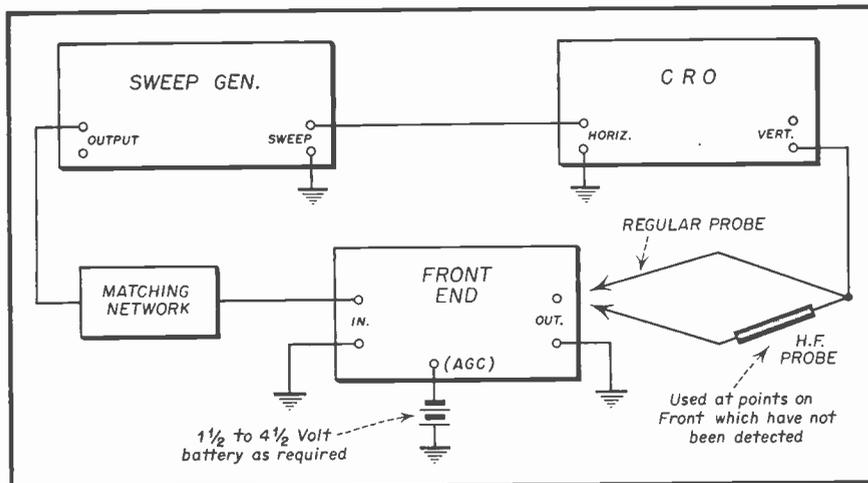


Fig. 3-48: Basic connections between sweep generator, CRO and Front End for observing r-f waveforms. Regular probe is used at grid circuit of mixer which is a point of detection. Crystal or h-f probe is used at other points. Matching network inserted between sweep generator and Front End is necessary to prevent distortion of waveform due to standing waves.

quire that the signal be demodulated. For this reason a h-f detector probe such as is used in an ordinary VTVM must be connected between the scope and the point at which the output signal is observed. A probe of this type is shown schematically in Fig. 3-49.

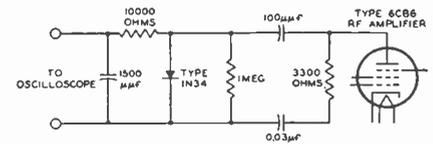
At the grid circuit of the mixer tube the signal is demodulated by virtue of the detector action of the tube. Therefore, no r-f probe is necessary at this point. However, it is customary to isolate the mixer grid from the



(Courtesy RCA)

Fig. 3-49: Typical r-f probe circuit.

probe by inserting a suitable resistor between the grid return and ground. A popular value of this resistor is 100K. The scope probe is then connected across this resistor and ground for measurements of the demodulated waveform present. Commercial Front Ends generally have this point readily accessible at some convenient position on the chassis, and it is referred to variously as a tuner test point, looker

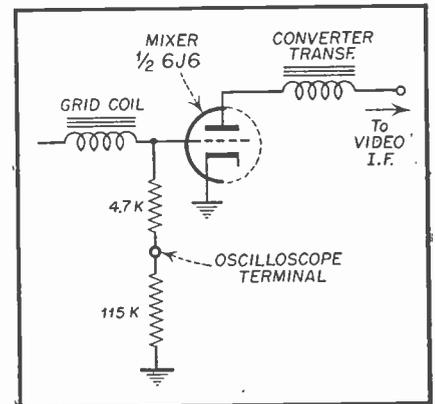

(RCA 206E3 Tuner)

Fig. 3-50: Partial schematic of mixer circuit.

point, oscilloscope point, etc. Figure 3-50 illustrates the partial schematic of a typical mixer circuit showing this connection clearly.

3. *Marker:* It will be recalled that the r-f response curve observed on a 'scope represents the r-f response of the circuit to a wide range of frequencies, the latter being injected into the circuit by the sweep generator. During alignment it often becomes necessary to identify the exact frequency at certain points on the curve. An external oscillator or absorption circuit is therefore provided which in effect provides these exact frequencies, and when combined with the output of the sweep generator results in a slight break in the response curve

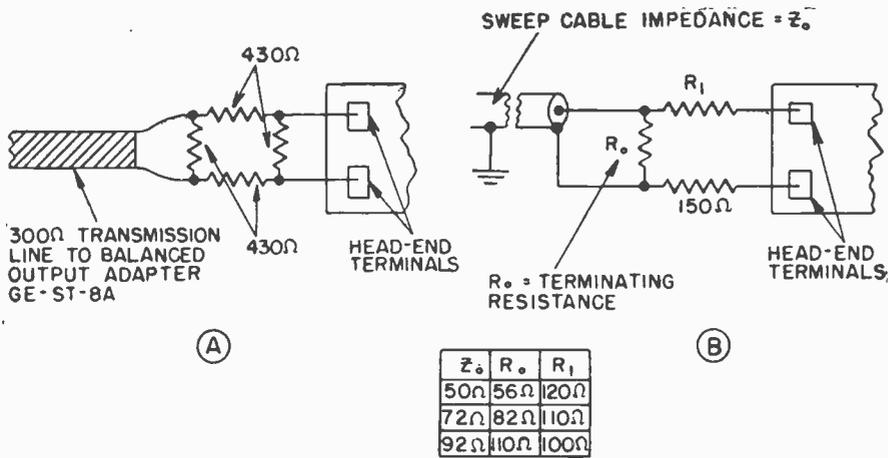


Fig. 3-51: Networks for matching generators with impedances of 50, 75, and 92 ohm output to 300 ohm receiver.

corresponding to the frequency of this oscillator or absorption circuit. The latter may be contained within the sweep generator or may be a separate and external piece of test equipment such as a signal generator. In any event, to be effective, it must have a high degree of accuracy—preferably crystal controlled.

The break in the curve may take on the appearance of a dip or a wiggle (birdie). The first is produced by an absorption device such as a wavemeter, the second by a c-w r-f oscillator. The output of the marker generator must be kept as low as possible; or, if an absorption circuit is used, the coupling must be as loose as possible, otherwise serious disruption of the waveform will result.

4. *Impedance Matching:* At very high frequencies, response curve measurements are valueless unless the sweep generator output terminals are properly terminated at the input terminals of the receiver. The reason for this is that at these frequencies a mismatch of this type results in standing waves which may or may not seriously affect the observed waveform, depending on the amount of mismatch present in the circuit. It is therefore advisable that some sort of matching network be employed between the generator and the input terminals of the Front End being aligned. Data for typical matching networks for connecting generators with 50, 75, and 92 ohm outputs to a 300 ohm input receiver is given in Fig. 3-51.

5. *Connections between units:* All connecting leads should be as short as possible. Shielded leads should be used in the r-f probe, in the 'scope output probe, in the marker output probe, and in the connection between the sweep generator and the horizontal output terminal of the 'scope.

Ground connections should be made with care. Wherever, possible all grounds from the various units should be connected to a single point on the chassis. Sometimes peculiar waveshapes which change as the operator touches various units occur. This is indicative of improper grounding between units. Some manufacturers recommend a metal bench top when aligning Front Ends. While this practice lends itself to excellent grounding it is a little dangerous, being a potential source of high voltage shock.

6. *Vertical Probe Pickup:* Without signal output from the sweep and marker generators the vertical amplitude on the 'scope should be zero. Be sure to make this check, otherwise the observed waveforms will be worth-

less. If any vertical signal does appear even though the sweep and marker generator outputs are set at zero, oscillation or hum is present in the tuner, or external energy is being picked up by the 'scope probe. At full 'scope sensitivity a slight vertical amplitude may be observed. This is permissible because during the actual alignment the 'scope sensitivity is invariably reduced from its full sensitivity range and this pickup will not appear in the final pickup.

7. *Receiver Feedback:* To reduce possible feedback from the video i-f stages it is customary to remove the 1st or 2nd i-f tubes during the Front End alignment. Another possible source of disturbance is the vertical blocking oscillator, which can cause large variations in the "B" plus line. Removal of this tube in many cases will result in smoother alignment of the Front End.

As an example of the principles discussed in this and previous installments the following alignment procedure of the Standard Tuner Model TV 101 Front End is presented. For the convenience of the reader the schematic of this tuner which appeared originally in the Sept. issue, as Fig. 3-24 is presented again as Fig. 3-52.

#### I. F. and Trap Alignment

Connect VTVM in series with 10,000 ohm resistor to 2nd detector video output on main chassis. Remove tube shield on 6J6 on tuner. Capacity couple AM Signal Generator to 6J6


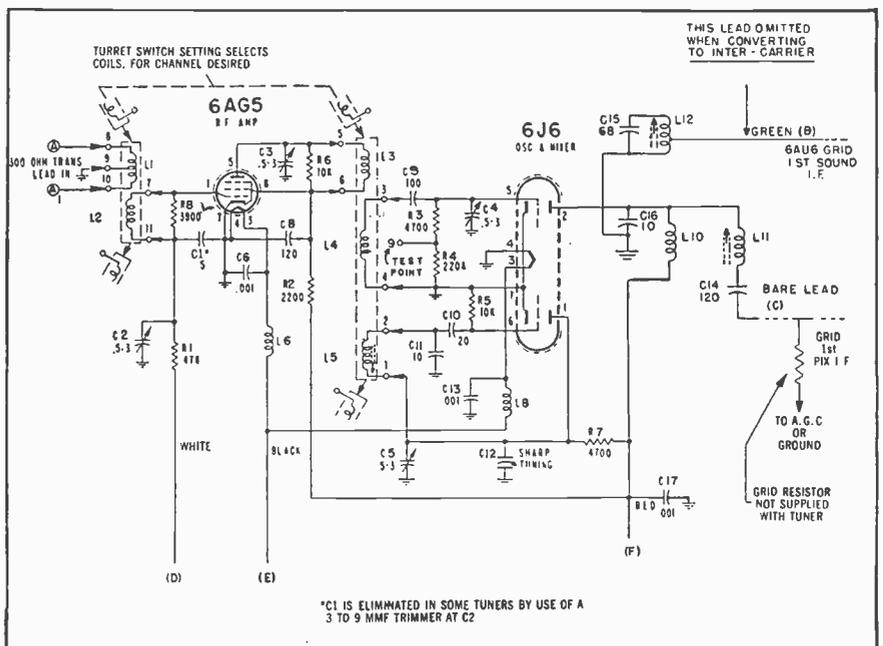


Fig. 3-52: Circuit diagram of Standard Tuner Model TV 101.

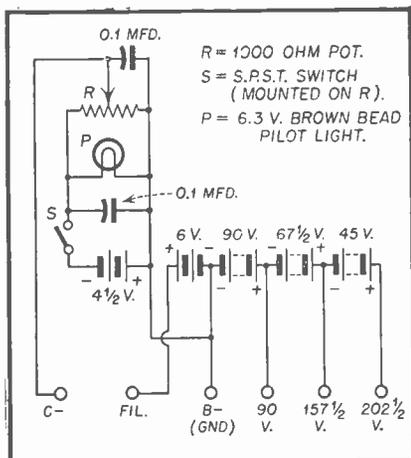

**Fig. 3-53: Circuit details of battery box used to test TV Front Ends.** by slipping tight fitting ungrounded shield over 6J6 and connect generator to ungrounded shield. Set frequency of generator to 21.25 mc. Tune  $L_{12}$  for minimum voltage on VTVM. Set generator to 21.8 mc and tune  $L_{11}$  for maximum voltage VTVM. Use high output signal generator at 21.25 mc and low output on 21.8 mc for above alignment procedure.

**R. F. and Mixer Alignment**

1. Set station selector switch to channel 12.
2. Connect oscilloscope through 10,000 ohms to test point 9 (wire loop on top of tuner).
3. Set bias to 1.5 volts, (a 1.5 volt battery may be used). Set sharp tuning control at approximately midpoint of its tuning range.
4. Feed sweep generator into antenna terminals, sweeping channel 12.

5. Adjust  $C_2$ ,  $C_3$  and  $C_4$  for flat-top response curve and maximum gain. Check markers on all channels. They should fall in automatically on all channels.

**Oscillator Alignment**

1. Turn station selector switch to channel 12.
2. Connect calibrated crystal signal generator to one antenna terminal and ground. Set to sound carrier frequency 209.75 mc.
3. Connect vacuum tube voltmeter to d-c output of ratio detector or discriminator, whichever is used.
4. Adjust  $C_5$  for zero reading on VTVM between a positive and negative peak.
5. Check all channels for zero reading on VTVM. It is usually not necessary to make any further adjustments. If necessary to touch up the oscillator coils, the following procedure is recommended:

**Oscillator Re-check (not usually necessary)**

- a. Center sharp tuning control
- b. Place a non-metallic screwdriver through opening, and adjust oscillator coil on channel 12.
- c. This adjustment can be repeated for all channels or, if necessary, on any single channel.

**Conversion From Split Sound To Inter-Carrier**

1. Disconnect green lead from tap on  $L_{12}$ .

2. If a 21.25 mc trap is not required in first i-f transformer, remove  $C_{15}$  (68 mmf condenser). If a 19.75 mc trap is required, replace  $C_{15}$  with an 80 mmf condenser.
3. The 6AG5 then becomes the 1st inter-carrier i-f amplifier.

**General Procedure**

It must be remembered that there are many different types of Front Ends in use, each requiring an individual alignment sequence. For this reason the manufacturer's specifications and instructions should be followed in detail during the alignment of any one unit. However, it will be found that all alignments follow a general pattern, this being:


1. Adjusting the antenna and r-f stages for proper bandpass and gain.
2. Adjusting the oscillator to the exact frequency required to produce a required i-f bandpass.
3. Adjusting the converter i-f transformer to its required frequency.
4. Adjusting the sound or adjacent channel traps.

**Aligning Front Ends Removed From Receiver**

Very often it becomes necessary to remove the Front End from the receiver proper in order to align it properly or to check it for loose connections. To do this the video output terminals must be terminated in a load equivalent to the input of the succeeding i-f stage. An average value of this load is 10K ohms.

To make tests of this type an external power supply must be used. Such a supply employed by the writer, and utilizing batteries only, which has proven very satisfactory is illustrated in Fig. 3-53 and Fig. 3-54. This battery supply may be used in many other applications such as testing portable receivers. It provides an "A" supply of 6 volts, a variable "C" supply of 4 1/2 volts, and "B" voltage taps of approximately 90, 150 and 200 volts. The pilot light used in conjunction with the "C" supply indicates to the user that the potentiometer is connected across the "C" battery. When not in use the switch is turned off and the pilot light goes out.

Thus far, the writer has been able to test any Front End entirely disconnected from its chassis by connecting it up with this battery supply. Many intermittents and other defects almost impossible to locate with the Front End connected in the receiver have been detected in this manner. To those who have occasion to repair and align many Front Ends a unit of this type will prove invaluable.

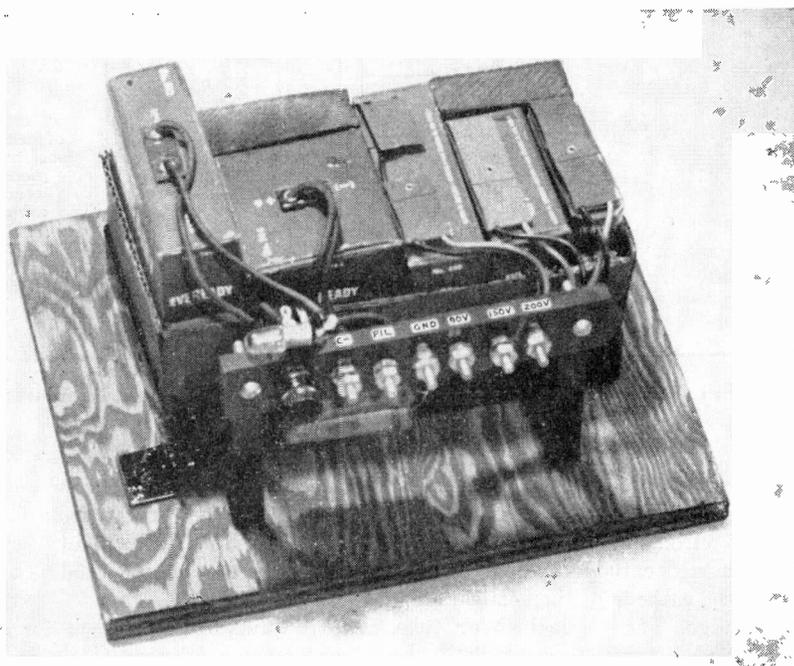

**Fig. 3-54: Batteries used in battery box are Eveready #746-4 1/2v, #744-6v, #490-90v, #467-67v, #455-45v, or their equivalents.**

# LOOKING FOR *Trouble?*

No. 2

by **Cyrus Glickstein**

(Instructor, American Radio Institute)

**H**ERE we go looking for trouble again—this time in Hall-crafter Model #T-64, using transformer low voltage supply, kickback high voltage supply, 10BP4 picture tube, and push-button channel selector. The sound was normal but the picture exhibited a marked foldover at the bottom.

The object of the game is to duplicate as far as possible the general steps in servicing a teletest as might be done on the bench or in the home until the trouble is found. The rules of the game are simple. Answer each question before going on to the next, since the answer is sometimes given in the following question.

1. The first step in trouble-shooting usually consists of checking appropriate controls to make sure there really is a trouble instead of only misadjusted controls. On the basis of the above picture on the screen:

(a) There is definite trouble in the vertical sweep circuit and there is no need wasting time to check vertical controls, since this type of trouble cannot be caused by misadjustment of controls.

(b) Same as (a) except that the trouble is indicated in the horizontal sweep circuit.

(c) Possibly can result from misadjustment of vertical linearity control.

(d) Possibly can result from misadjustment of horizontal drive control.

2. Varying the vertical linearity control varied somewhat the amount of foldover, but manipulating this control and the vertical size control could not take it out. This kind of trouble is caused most usually by a bad tube or a leaky coupling condenser or leaky saw-tooth condenser in

**Continuing this unique type of trouble-shooting article which goes through the actual steps of servicing a TV receiver in quiz fashion. In this installment the Hall-crafter Model T-64 is analyzed for a particular symptom which any radio-TV service dealer might encounter.**

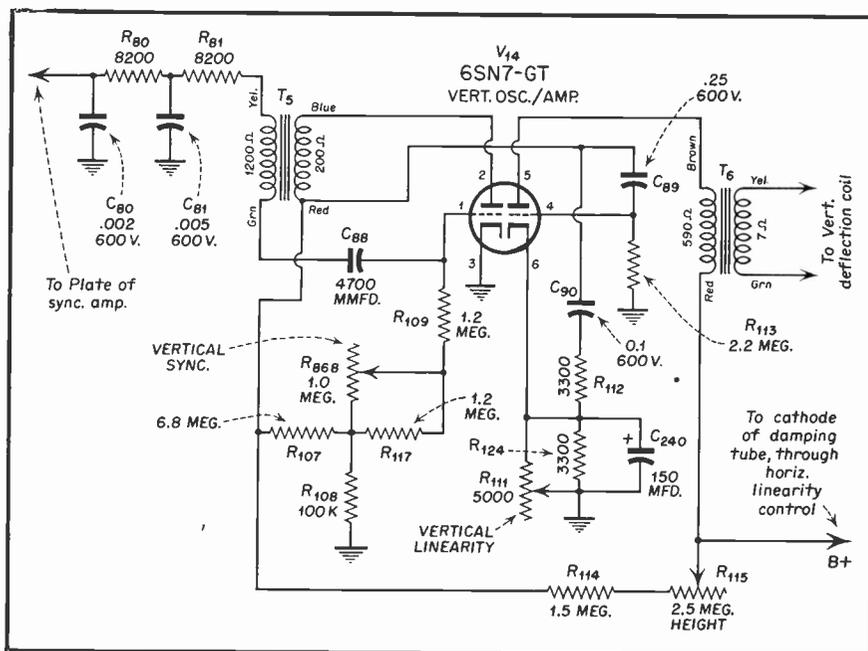


Fig. 1. Vertical sweep section of Hallicrafter Model T-64 receiver. (Partial Schematic).

the vertical sweep circuit, although there are other possibilities. In this type of circuit it can also be caused by a shorted cathode by-pass condenser in the cathode of the vertical amplifier stage. The vertical sweep tube, V-14, 6SN7, consisting of both the oscillator and amplifier stages, was changed. No improvement. The cathode voltage on the amplifier stage was

measured with a voltmeter and found to be normal, varying from 0 to +16 v. as the linearity control was varied, showing that the cathode condenser was not shorted.

A quick way to check for a leaky saw-tooth condenser, C-90 (See Fig. 1) would be to turn set on and to:

(a) Check with VTVM to see if there is a positive voltage from top

of *C-90* to ground with the vertical sweep tube out of socket.

(b) Put VTVM across *C-90* to check if there is a positive voltage with the vertical tube in.

(c) Bridge a known good condenser of the same value across *C-90* and watch picture tube to see if picture or raster returns to normal.

(d) Put VTVM across *R-112* to see if there is a positive voltage with the vertical tube out.

3. Saw-tooth condenser checked O.K. Next check made to see if the coupling condenser, *C-89*, was leaky. Quick check here is:

(a) Check for positive voltage on the grid of the amplifier stage with the set turned on and the vertical tube in the socket.

(b) Same as (a) but with the tube out.

(c) Unsolder one end of the coupling condenser and check across it on the high range of the ohmmeter with the set turned off.

(d) All of the above methods are equally good.

4. Coupling condenser did not check leaky. Resistance check made around the tube socket and all resistance checked normal. Resistance readings of the vertical transformers and vertical section of the yoke were normal. On taking voltage readings, B+ was normal and plate and grid voltages of oscillator were about 20% off, but did not show any conclusive indication of where the trouble might be.

Since it is possible for the saw-tooth to be distorted even if the condensers are not leaky but simply decrease in capacity, the following condensers were changed: sawtooth (*C-90*), coupling (*C-89*) and grid leak (*C-88*). Set turned on. No change in the amount of foldover in picture. A scope was used to check wave-forms at the points shown in *Fig. 2*.

On the basis of the scope information and previous checks, trouble most likely is originating in:

(a) The plate circuit of the amplifier triode.

(b) Grid circuit of the amplifier triode.

(c) Plate section of the oscillator triode

(d) Either the plate section of the oscillator or the grid section of the amplifier.

5. Waveform was rechecked from top of *C-90* to ground after each of the following were done: Coupling condenser *C-89* unsoldered at one end; either side of *R-87* shorted to ground; bottom of *R-112* shorted to ground.

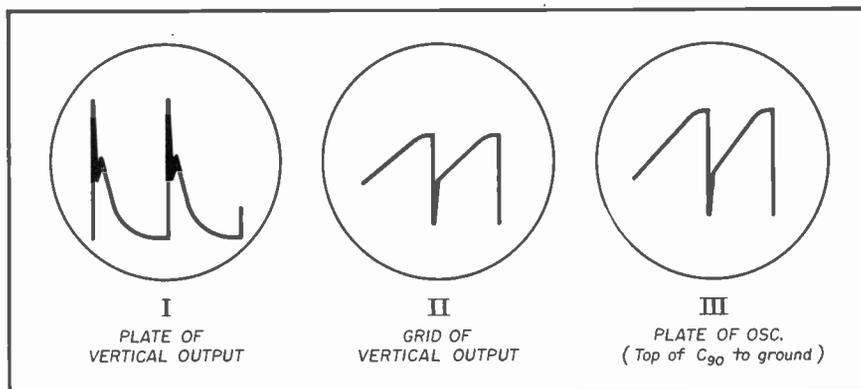


Fig. 2. Waveforms appearing at various points in vertical sweep circuit of a television receiver.

Waveform did not change shape at any time and was the same as before (See *Fig. 2*, III) though shorting each side of *R-87* changed the frequency of the sawtooth somewhat. This indicates the trouble most likely is:

(a) Defective blocking oscillator transformer, *T-5*.

(b) Defective tube socket for vertical sweep tube, *V-14*.

(c) One of the resistors in the vertical oscillator stage must be changing value when voltage is applied.

(d) Shorted *C-87* in integrating network.

## ANSWERS & DISCUSSION

Answer 1—c.

In some receivers, misadjustment of controls can cause vertical foldover. This is true in this receiver because linearity control can reduce vertical amplifier cathode resistance to zero. (See *Fig. 1*) As a result, lack of cathode bias on the amplifier stage will cause top of modified sawtooth wave to be flattened off and so cause foldover. In many sets there is a fixed resistor in series with the linearity potentiometer in the cathode of the vertical amplifier to limit the range the bias can be varied. In such cases, varying the vertical linearity control can correct for (or if set is too far off, cause) vertical non-linearity but not actually foldover.

Trouble definitely is indicated in the vertical rather than the horizontal circuit since it is a fault that is not common to all horizontal lines. Such a fault would be expressed in a vertical direction. That is, trouble in the horizontal sweep generally shows up in the vertical direction, and in the vertical sweep in the horizontal direction.

Answer 2—d.

When the tube is in, the oscillator operates and generates a modified sawtooth voltage. With a sawtooth voltage across *R-112* there may be some d-c reading, especially when the sawtooth is distorted even if the sawtooth condenser is not leaky.

While the sawtooth is an a-c voltage and should give a zero reading when measured with a d-c meter, this would be true only when the positive and negative halves of the signal are equal or symmetrical. When they are unequal, the d-c meter will give a reading in the direction of the larger half of the a-c voltage. However, if the tube is taken out and *C-90* is leaky, there will be a small d-c voltage across *R-112* due to the small amount of current through it and *C-90*. This could usually be measured by a VTVM across *R-112*. However, if the leakage current is very small, it may not show up very well across *R-112* because its low resistance value would give a small voltage drop. A more conclusive check would then be to unsolder one end of *C-90* and put the VTVM in series with it with the power in the set on and the vertical tube out of the socket. Even a small current flow through the VTVM will give a definite reading.

Since this is a transformer a-c set, it is perfectly feasible to take the tube out and the other circuits, including low voltage B+ would continue to operate. In sets where the filaments are in series, the same type of check would have to be made but without taking the tube out. Instead, the oscillator should be immobilized by grounding the grid, the idea being to prevent a sawtooth signal from masking any d-c voltage across the peaking resistor, *R-112*.


[Continued on page 40]

# ASSEMBLING COAXIAL


Reprinted from *Amphenol Engineering News*, June

On these pages we show results of tested work procedures based on extensive experience in assembling connectors for use with RG 55/U, RG 58/U, RG 59/U, RG 62/U and RG 71/U cable. These methods have been adopted as standard on Amphenol assembly lines and are being passed on to our readers in the interest of building toward a higher degree of efficient workmanship. Shown to the right are the first three steps to be taken in processing either of the two assemblies. After these instructions have been followed either of the procedures shown in Figs. 4 to 8 or 9 to 13 may be continued according to the connector type being used.


## OPERATIONS FOR RG 55/U AND 58/U CABLE

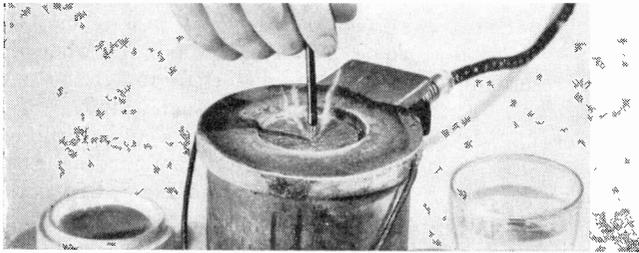

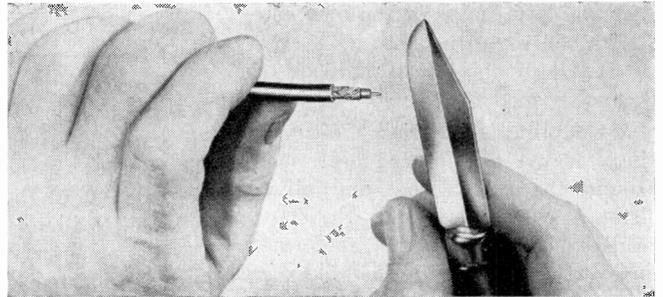
4. Dip exposed shield in rosin-alcohol flux to a depth of 1/8" (Apply a minimum amount of flux for a neat job.) Dip fluxed cable quickly into solder pot and immerse immediately into the alcohol. This cools the dielectric, prevents distortion and removes excess flux.



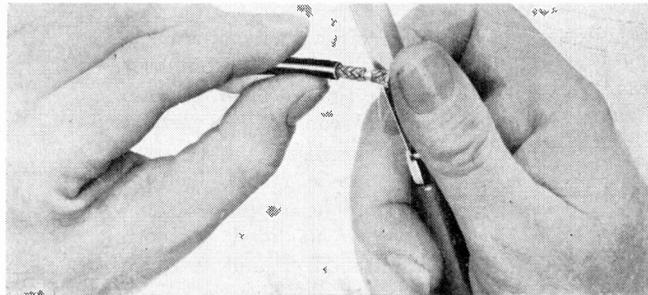
5. The tinned shield is then cut and removed to expose 1/4" of the dielectric.



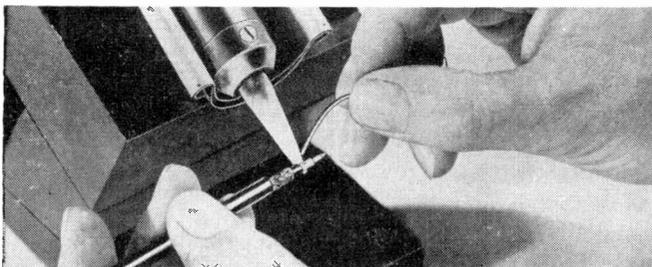6. The dielectric is then cut and removed to expose 1/8" of the center conductor.



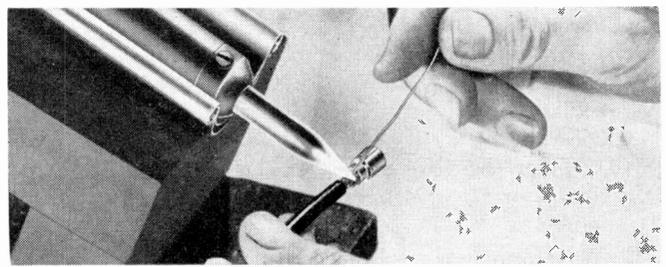
7. Tin the center conductor, slip on the contact and solder through the cross-drilled hole. The rubber or plastic sleeving which protects the external solder connection can now be slipped over the cable.




8. The connector shell is now slipped over the contact and soldered. Be certain the shell is properly located. It is in proper position when the tip of the contact is flush with dielectric and the end of the body shell.
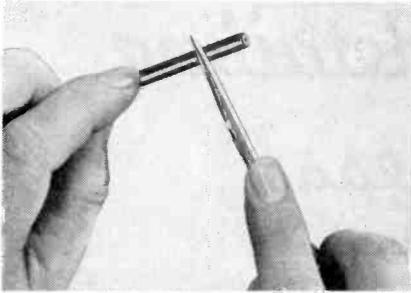
# CABLE CONNECTORS


1950, by permission of the American Phenolic Corp.



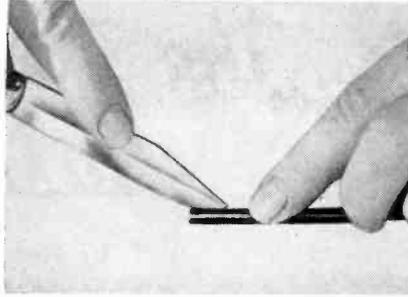1. After the cable is cut to required length, cut and remove vinyl jacket.




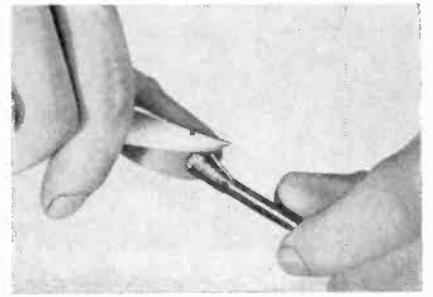2. Slit vinyl jacket laterally to allow easy removal.




3. Remove vinyl jacket, exposing braid to 9/16" on the smaller and 7/16" on the larger cable.

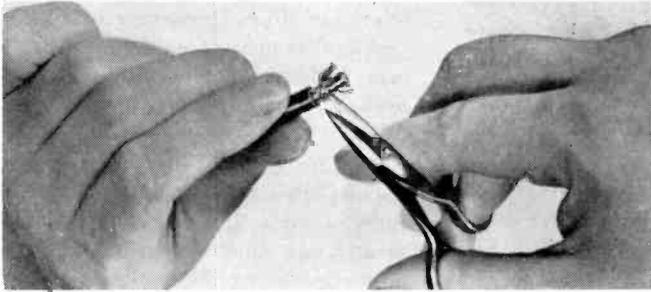
## OPERATIONS FOR RG 59U, 62U AND 71U CABLE



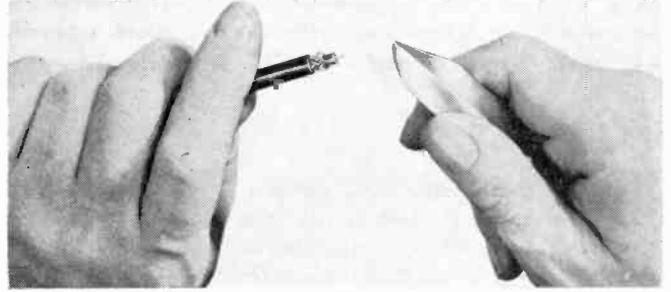
9. Slip the vinyl or rubber sleeving over the cable. Flare the braid slightly to permit trimming and remove 1/4" of shield, leaving 3/16".



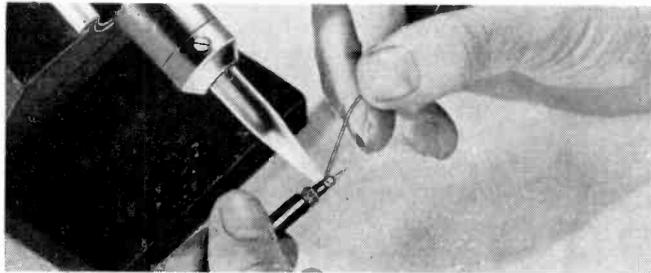
10. Cut the dielectric and remove to expose 1/8" of the center conductor.



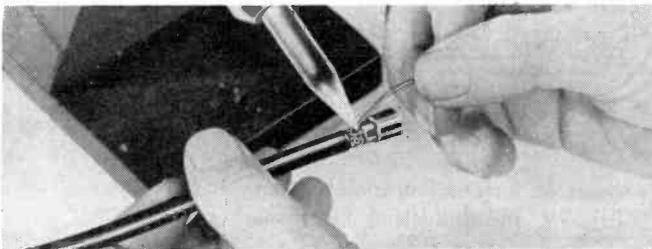11. The conductor is then tinned and the contact slipped in place and solder added through the cross-drilled hole.



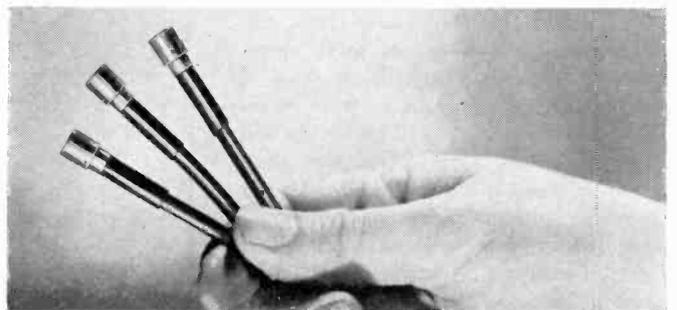12. Flare the braid slightly again and assemble connector shell to the cable. The shell should enter under the braid. The braid is squeezed into position over the shell body and soldered.



13. Slide rubber or plastic sleeving over the solder connection and the job is finished.



Roland D. Payne

# "Does the Radio-TV Technician Belong In The TV Retailing Business?"

by Roland D. Payne

Sales Manager, Air King Prods. Co. Inc.

**Your editor firmly believes that most servicemen can more than double their incomes by assuming an aggressive, rather than "hands-off" approach where potential sales of appliances, receivers, and accessories are concerned. Try it out--you'll be surprised at the results.**

THE above captioned question has oft been asked by both the technician and the television manufacturer. To answer this question let us first establish the facts in the case.

On the negative side, first let us assume that in most cases franchises for the top brand lines of television will not be available to the technician.

Secondly, the main portion of the technician's business is technical know-how and the sale of replacement parts and not merchandising, as is needed to sell television sets.

Third: Most of the secondary television lines available carry very little and, in some cases, no consumer advertising, which makes them hard-to-sell items.

Fourth: Warehouse space being at a premium, most technicians do not have adequate facilities for handling large quantities of television receivers.

To offset the above negatives, the technician will have, in most cases, with a secondary television line, a larger margin of profit to work with. His dealer mark-up will be better and his list prices somewhat lower than those of the top name brands. Larger margins and lower list prices should certainly offset, somewhat, the fact of no consumer advertising. So let us assume for the moment that the selling of television receivers should be profitable.

From a physical equipment point

of view, most technicians are amply prepared. Television must be demonstrated to be sold. Therefore, a display and demonstration corner or room is absolutely necessary. The receivers in this room or space must be in good working order and must be polished or dusted daily. Technicians know all of the idiosyncrasies of receivers and also all of their good qualities. This gives them a decided edge in demonstrating and selling TV receivers.

Most technicians are capable of buying at least one television receiver at a time. They may sell this sample and then immediately reorder. This is a nice lucrative business as the dollar profit is high. Besides, the installation and future servicing of these receivers will provide technicians with additional, regular services of income.

On the servicing side of the ledger, the technician is well equipped. He

has oscilloscopes, signal generators and voltmeters; in fact, all of the equipment necessary for servicing television. Parts inventory creates no problem as most technicians already carry comprehensive inventory of needed standard television parts and tubes.

The technician, in most cases, is not expected by the manufacturer, to carry a large inventory of receivers at any one time. So, in buying what he needs, selling them quickly and re-ordering, the technician is never stuck with obsolete merchandise nor is he caught with a big inventory if and when prices decline.

I particularly emphasize the fact that the radio-TV technician has always been the receiver manufacturer's liaison with the public and undoubtedly is the industry's greatest single factor in the molding of public opinion. Invariably, the serviceman's good or bad opinion of a receiver line is respected by the public, and influences its future purchases.

In conclusion, may I say that the technician definitely belongs in the television receiver business as the affirmative side of the question certainly outweighs the negative considerably.

## WANTED

Technical articles on installation, maintenance, and service of allied Radio-TV and Industrial Electronic equipment.

Attractive prices paid for original manuscripts.

Address replies to: EDITOR, RADIO-TV SERVICE DEALER,  
342 Madison Ave., New York 17, N. Y.

# High Quality Analyses Series

No. 6

by C. A. TUTHILL

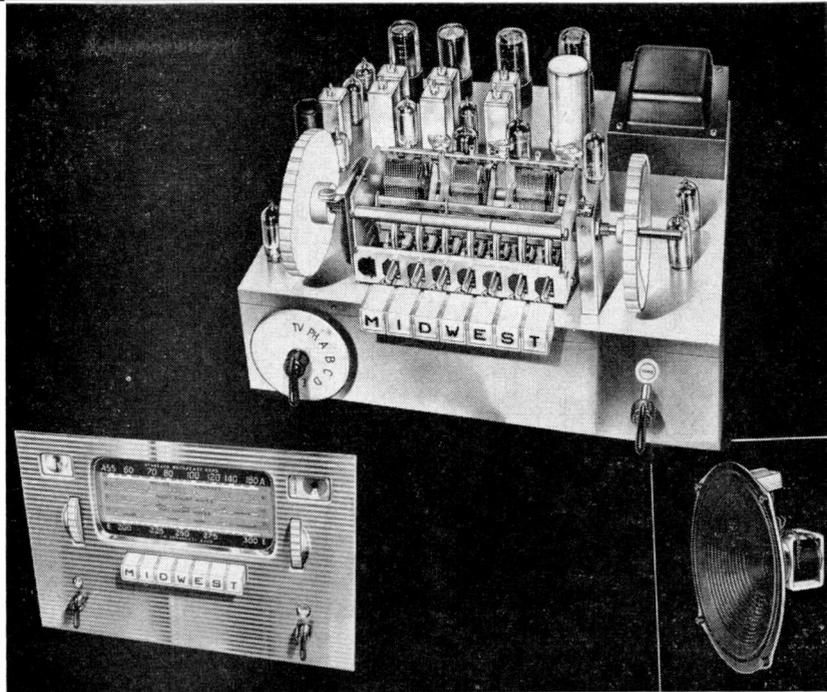


Fig. 1. Midwest Model JC-16 combination AM-FM receiver.

**This is the sixth article on high quality tuners and receivers prepared by the author for our readers. Those who have followed this series are unanimous in their praise of the objective manner in which the various products were handled. In this installment the Midwest Model JC-16 is described.**

IN the interest of high quality reproduction from a combination AM-FM tuner chassis, we find in this model JC-16 by Midwest Radio & Television Corp., Fig. 1, several worthy features. For example, instead of jamming quantitative functions within one envelope, this model provides an independent 6AL5 tube for AM detection while it includes another 6AL5 tube connected as ratio detector for FM translation. There is no shortage of tubes in the straight-forward circuits divulged in the schematic of Fig. 2. The block diagram of Fig. 3 shows the assignment of all tubes.

To the lower left of the schematic (Fig. 2) are shown low capacity jacks and switching facilities for:

(a) inclusion of a video adapter unit which economically employs the contained audio amplifier.

(b) high quality phonograph pickup.

For reception of weaker FM and shortwave AM signals, a properly matched low-loss external dipole antenna should be connected across input terminals "A-A" which offer a 300 ohm balanced input. In many instances a built-in dipole serves adequately for local reception. Terminal "G" should be properly grounded. high impedance loop antenna, provided for this chassis, will answer most standard AM broadcast requirements.

## Tuning Facilities

Simplified band-switching selects individual r-f, mixer and oscillator tuning coils for each of the five channels listed below. Short-cuts are held to a minimum, as proven by the schematic Fig. 2. Twenty-three inductances, twelve trimmer capacitors and sixteen tubes serve the channels below:

Band A - 540 kc to 1600 kc - AM broadcasts.

Band B - 1.6 mc to 4.7 mc. - AM shortwave.

Band C - 4.7 mc to 10.0 mc. - AM shortwave

Band D - 11.2 mc to 22.0 mc. - AM shortwave

Band E - 88.0 to 108 mc - FM broadcasts.

*Note:* Seven International bands are covered by B, C & D above.

Manual tuning control is spur-gearred to six-gang capacitors. This control is augmented by seven push-buttons, each of which may be set mechanically for a station at any point on the dial. These pushbuttons, however, are not recommended for the exacting requirements of shortwave tuning. To minimize noise, and distortion from the cutting of sidebands, a 6U5 tuning indicator is energized through a 1-megohm dropping resistor from the a-v-c bus which is in turn supplied by the detector tube in use. As a signal is properly tuned,

the a-v-c voltage increases and deflection of the 6U5 is reduced to a minimum. This indicator is useful for stronger FM stations but not too accurate for the weaker ones. An auxiliary mechanical device just above the volume control shows visual indication numerically. It serves as a good reference for repeat tuning of a given station and allows volume to be accurately pre-set for local stations prior to *warmup*.

Since oscillator frequencies are changed with band switching the double-tuned i-f stages remain fixed at 10.7 megacycles for FM and at 456 kilocycles for AM reception. Good tracking alignment is accomplished through coil-core and trimmer capacitor adjustments detailed in servicemen's pamphlets.

Input and output r-f channels for all bands are switched to and from one miniature 6BA6 pentode whose high transconductance aids high signal-to-noise ratio.

## Mixer-Oscillator

The 6BA7 pentagrid mixer offers separate grids to amplified r-f and local oscillator signals. Entrance interactions are thus minimized. A high conversion efficiency is derived from the selection of this tube which has a low internal noise content. However, since some hiss will be generated within any mixer tube, it is wise to take

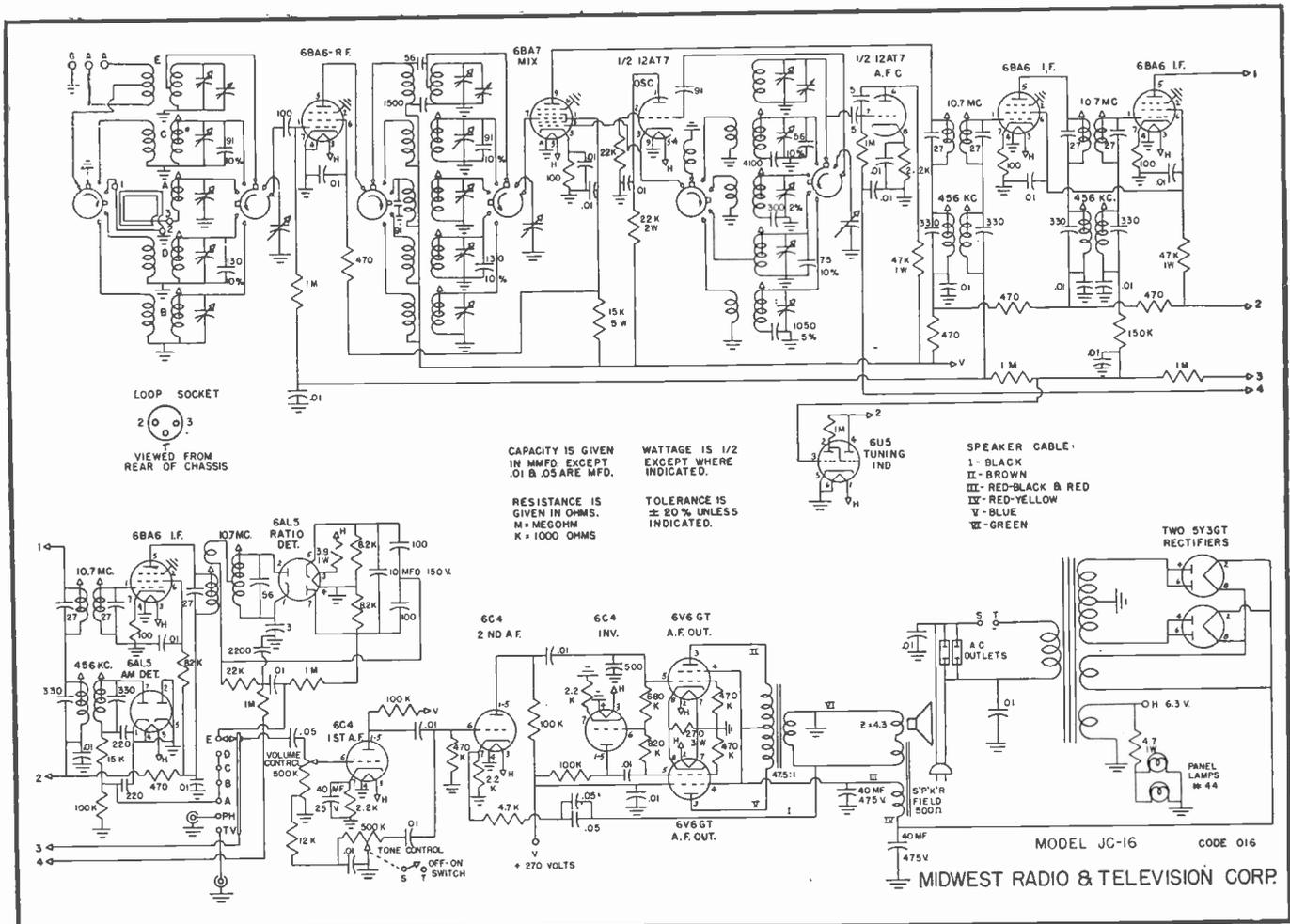


Fig. 2. Circuit diagram of Midwest Model JC-16 combination AM-FM receiver.

every possible step to obtain a healthy signal potential at the grid of the first r-f stage.

As modulated carrier and local oscillator potentials are combined within this tube, the first step in signal translation is effected. Incoming signals from the r-f stage are fed to grid #3 of the 6BA7 mixer via the selector switching system. Output from the 12AT7 oscillator tank is fed directly to its grid #1. Grid #2 screens off spurious interaction prior to desired mixing in the electronic plate stream.

There results in the mixer output circuit a *new* modulated carrier whose *difference* frequency equals the interval between the incoming r-f signal and the r-f of the local oscillator.

Mechanically ganged, the oscillator tank tracks with the tuning of preceding r-f tanks. This results in a fairly constant difference frequency output from the mixer-oscillator. Even casual FM transmitter deviations from normal frequency must be tracked as must aberrations within the tuner itself. Hence a means of

automatic frequency control is applied to the FM channel.

#### AFC-(FM) [Reactance type]

Oscillator stability is highly necessary in high frequency channels. The second half of the 12AT7 (double triode) serves as a reactance-type a-f-c control tube. Plate current in it is made to lag almost 90 degrees behind its plate voltage changes. As witnessed from the schematic, Fig. 2, both the plate and grid of this *reactance* tube, coupled together by a 5  $\mu\text{f}$  capacitor, receive signal from whichever oscillator circuit they are switched to.

An original FM control potential, tapped from the d-c output network of the 6AL5 ratio detector, is fed back through bus #4, (lower left corner of schematic), and through the 1-megohm resistor, directly to the grid of the reactance control tube (12AT7). The more positive this voltage the greater the plate current therein and vice-versa. Then since plate and cathode of this reactance tube are connected directly across the oscillator tank circuit, and since its plate current and plate voltage are

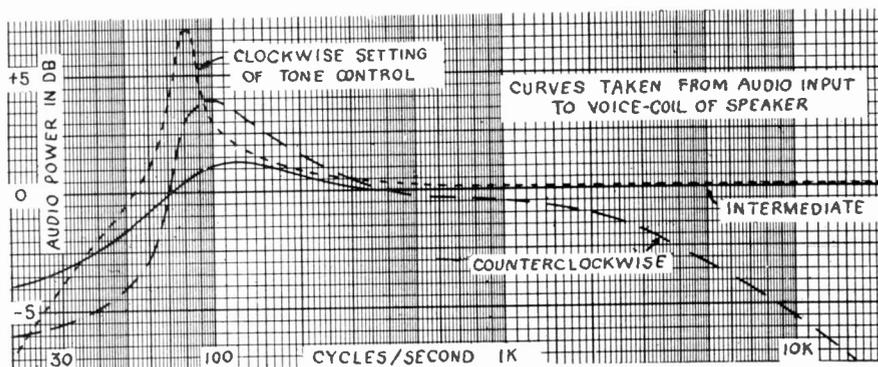


Fig. 4. Compensation effects of tone control at various positions of the latter. Audio output taken at voice coil.

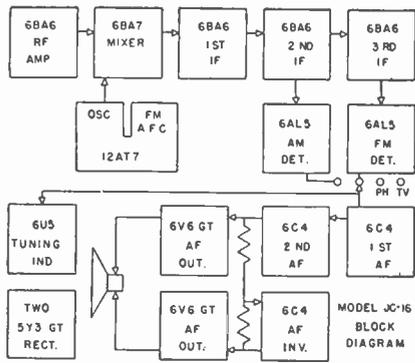


Fig. 3. Block diagram showing assignment of all tubes.

90 degrees out of phase, variations within the tube introduce reactive effects upon the oscillator output.

Should the oscillator frequency become higher than intended, the i-f frequency would naturally rise with it. Such action would indirectly raise the negative potential of the reactance tube grid thereby causing less plate current to flow therein. Resulting directly from this action, the inductive or reactance effect of the control tube adds to the normal inductance value of the oscillator tank circuit. From basic formulae we know that any increase of tank inductance will reduce oscillator frequency. Hence the reactance tube stabilizes oscillator frequency as it responds to plus or minus control potentials supplied to its grid from the ratio detector d-c output. Frequency drift or small tuning errors are therefore compensated.

### Intermediate Stages

Adequate gain must be derived from the i-f section for proper operation of the individual AM diode and FM ratio detectors. This especially holds true for weaker signals and therefore we find a third i-f stage driving the FM detector. The average FM antenna input potential is lower than are those derived from AM transmitters of the standard broadcast band. Some limiting action is advisable prior to the final interpretation of the FM ratio detector. It will be noted from Fig. 2 that the i-f plate and screen voltages are tapped from the supply bus successively lower as the FM detector is approached. The third 6BA6 i-f or driver stage, having low screen and plate voltage, becomes easily saturated and therefore does not respond to a variety of changes in signal amplitude, but, instead produces a fairly constant amplitude output. It remains a frequency-sensitive rather than an amplitude-sensitive device. Amplitude variations are thus smoothed out. They cannot

be amplified beyond the saturation or limiting point of this third i-f tube as pre-determined by the values of its circuit components.

Due to the higher gain of this FM i-f section, regeneration must be guarded against. One of its effects is to peak the i-f response curve to such a degree that amplitude distortion attends higher levels of modulation. The four 10.7 megacycle i-f transformers are overcoupled thus passing the necessary band width and insuring good adjacent channel attenuation.

In the AM channel there are three 456 kc transformers used for intermediate stages. Their coefficient of coupling is adjusted to be slightly less than critical. When properly set there is only one peak.

Only the oscillator section of the 12AT7 serves the AM channels. AFC is applied only to the FM channel. Whereas a.v.c. is derived from the 6AL5 detector and supplied to all four AM channels through the selector switch and has #3 as evidenced in the schematic of Fig. 2.

### FM Ratio Detector

The regulated plate signal output of the third i-f driving stage is supplied to the fixed-tuned primary of the ratio detector. The main center-tapped secondary winding connects to the plate of one diode and to the cathode of the other diode within the 6AL5 envelope, thus effectively connecting the two diodes in series; they conduct on the same i-f half cycle. The rectified voltage across the lower shunt capacitor in the 6AL5 output circuit is proportional to the voltage across the lower diode. The same holds for the upper capacitor and upper diode. Since the voltage across the two diodes differ according to instantaneous carrier frequency, then the voltages across the two capacitors differ proportionately. The voltage across one capacitor is the larger of the two capacitor voltages at carrier frequencies below to intermediate frequency, and the smaller of the two at frequencies above the intermediate. It follows, then, that the voltage across the two capacitors is additive.

Rectified signal current causes a d-c voltage drop across the two 82K shunt resistors. This charges the large 10  $\mu$ f capacitor thus maintaining a steady state d-c value proportional to transmitted signal strength. The resultant stabilizing voltage keeps the summation voltage across the two smaller 100  $\mu$ f capacitors always constant thus minimizing any residual AM component in the detector output.

The tertiary winding, shown above the primary of the driving transform-

er, and common to both diodes, simplifies the signal transfer problem. The transfer from r-f to a-f is not simple. These few tightly coupled tertiary turns aid phase balanced elimination of any undesired AM hangover component. For greater understanding of this transfer problem the reader is referred to literature on ratio detectors.

### Audio Amplifier

To the left of the first 6C4 audio amplifier stage in the schematic Fig. 2 can be seen a multipole selector switch. Inputs of AM or FM radio, phonograph, or television adaptor are chosen and transmitted through the volume control to the grid of the first audio amplifier stage. Beneath this stage a graduated tone control may be seen mechanically linked to the "Off-On" switch. Compensating values derived from the latter are shown by the curves of Fig. 4. Personal tastes in tone are satisfied for any source of input.

The second 6C4 audio stage is connected for negative feedback from the secondary winding of the push-pull output stage. Thereby the amplifier becomes stabilized, distortion is minimized, and dynamic characteristics are made flexible. Expanded ranges of frequency response are amplified practically with equality throughout the workable FM range. The third 6C4 serves as the necessary phase inverter for driving of the lower 6V6 beam-power tube in the pushpull final stage. It must be remembered that no tuner is better than the amplifier and loudspeaker system to which it is connected. An undistorted 10 watt output is claimed for the amplifier.

### Power Supply

Technically this power supply, employing a full wave rectifier, is not unusual despite its simplicity. A 500 ohm loudspeaker field serves as choke-coil in the rectifier output circuit. Initial high voltage is fed from the choke to the screen grids of the 6V6 beam power tubes while plate potential is supplied to these tubes through the mid-tap of the audio output transformer primary winding. Bleeders drop the initial voltage as required for all other potentials except heaters. Heaters are fed from their own 6.3 volt unrectified source.

Ventilation must be considered when this or any chassis is applied to custom-built or special installations. Dissipation of heat from all tubes is provided for in commercial models and must never be neglected elsewhere.

# SHOP NOTES

Write up any "tricks-of-the-trade" in radio servicing that you have discovered. We pay from \$1 to \$5 for such previously unpublished "SHOP NOTES" found acceptable. Send your data to "Shop Notes Editor".

## Philco Models 48-1000 1001-1050- Correcting loss of a-g-c action

An extremely black picture and difficult in synchronizing the picture may be caused by the loss of a-g-c action in the above models. Loss of a-g-c action may be due to the failure of the condenser which is connected between the triode plate and the diode plate of the a-g-c amplifier tube. If this condenser develops a short or a leak, a positive voltage is placed on the a-g-c bus and is fed to the grid of the r-f and i-f amplifiers.

Whenever the symptoms indicate loss of a-g-c action, this condenser should be checked. If it is found defective, replacement should be made with Philco Part No. 61-0120, which has a capacitance of .01  $\mu$ f. and a working voltage of 600 volts, d.c.

## Philco Model 49-702 Replacement of Tuner

The tuner available for replacement for Model 49-702, Code 121, is the one used in Model 50-702. Since there have been some circuit changes in both the latest tuner and the receiver, it will be necessary to make a slight modification to the new tuner to adapt it to Model 49-702, Code 121. This modification consists of removing one turn from the 1st v-i-f coil. The procedure for removing the turn and installing the new tuner is as follows:

1. Remove the chassis from the cabinet, and the picture tube from the chassis.
2. Unsolder the tuner connecting wires, and record the connections.
3. Remove the perforated shield from the bottom of the tuner.
4. Locate the 1st v-i-f coil, which is connected to pin 3 of the 7F8 tube, and disengage the coil mounting clip from the chassis.
5. Unsolder the winding furthest from the chassis, and very carefully peel one turn off.
6. With fine sandpaper, remove the insulation from the wire and solder it to the coil terminal.
7. Secure the coil form.
8. Replace the perforated shield.

9. Install the new tuner in the chassis and rewire the same as the original tuner.


10. Align the i-f and r-f systems of the receiver as described in the service manual for Model 49-702, Code 121.

*Philco Service Dep't.*
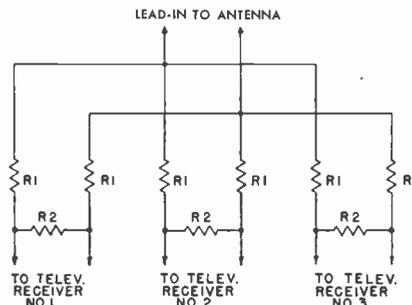
## Stromberg-Carlson-Pads for the purpose of connecting Multiple TV-12's to one antenna

To connect more than one television receiver to one antenna without the use of switches, resistor pads will be necessary to match the impedance of the lead-in to the impedance of the receiver.

Shown below is a chart of the resistors to use with each specified number of receivers. The figures are based on



EXAMPLE FOR THREE RECEIVERS.


Number of Receivers	R <sub>1</sub>	R <sub>2</sub>
2	56	100
3	100	100
4	120	82
5	150	82
6	180	82
7	240	82
8	270	82

a 75 ohm impedance which is the input impedance of the TV-12 and also the characteristic impedance of coaxial lead-in (RG-59U or equivalent). Use Non-inductive carbon resistors and place the pads at the junction point and not at the receiver terminals.

*Stromberg-Carlson Svc. Dep't.*
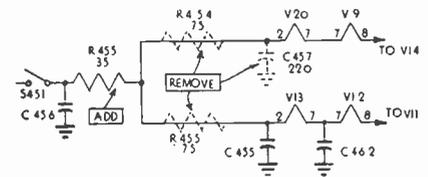
## G.E.-Models 12T3, 12T4, 12C107, 12C108, 12C109-Filament Circuit Change

Late production receivers use a single 0.6 ampere Globar resistor in



the filament circuit to give the same current regulation in this circuit during the warm-up period as was previously accomplished by the two - 0.8 ampere Globar resistors, R454 and R455. The details of the circuit change are shown above.

The new Globar resistor is stocked as:  
RRW-054-35 ohm, 0.6 ampere Globar resistor, (R455) \$1.75

## G. E. Increased Horizontal Sweep Width

Late production receivers incorporated the following changes to increase the horizontal sweep width.

1. Add a 220  $\mu$ f., 1500 v., capacitor (Stock RCU-295) between terminals #6 and #8 of the horizontal sweep output transformer, T351. Either two 390  $\mu$ f. capacitors (Stock UCU-1042) in series or two 470  $\mu$ f. capacitor (Stock UCU-1044) in series may be substituted for the 220  $\mu$ f. capacitor.

2. Change the termination of the high voltage capacitor, C376, from pin #6 to pin #5 of the 25W4GT damper tube, V15.

The above changes will be incorporated in all production receivers from this date.

## G. E. Removal of 41.25 MC Video I-F Trap

Early production receivers made use of a 41.25 mc trap coupled to the 2nd video i-f coil. This caused "buzz" in audio on some receivers when the receiver was properly tuned for best picture detail at low contrast setting or when operating on a rather weak signal. This trap was removed on all late production receivers and was made less effective on receivers in process of fabrication, by shunting the trap by a 5100 ohm, 1/2 watt resistor by connecting it across the trap trimmer C281. If this change is desired in the field, the shunting of C281 by the resistor does not require a realignment of the video i-f.


For replacement purposes the Stock No. RLI-123 2nd video i-f coil with trap will no longer be available. Replace this coil by Stock No. RLI-096. This latter i-f coil has a list price of \$0.85.

*General Electric  
Service Dep't.*

# NEW PRODUCTS
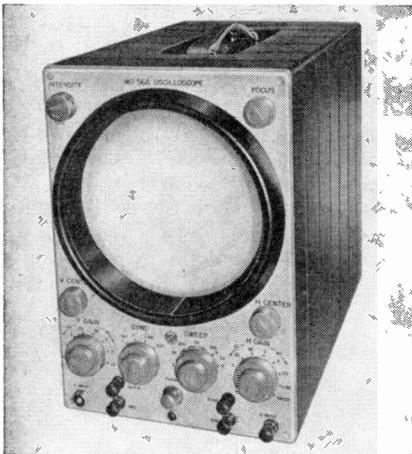
## 7-INCH OSCILLOSCOPE

A new, seven-inch oscilloscope, especially designed to meet the need for a high-quality instrument combining the advantages of large screen size, compactness, portability, and ease and convenience of operation, has been announced by the RCA Tube Department.



The new RCA WO-56A Cathode-Ray Oscilloscope is a precision-engineered instrument having wide application in service shop, laboratory, and factory. It features three push-pull stages of direct-coupled amplification. A wide frequency response, a high deflection sensitivity, and an excellent square-wave response provide waveform reproductions of unusual accuracy and clarity on its seven-inch screen.

## NEW BEAM POWER TUBE

A beam-power amplifier tube, designed for use in the audio output stage of television and radio receivers, has been added to the production lines of the General Electric Tube Divisions.



According to E. F. Peterson, Sales Manager of the Tube Divisions, the new tube (Type 6W6-GT) is capable of delivering relatively large power output and features high


sensitivity. When connected as a triode, the tube may be used as a vertical deflection amplifier in television receivers.

Maximum ratings of the tube include: peak positive pulse plate voltage, 1000 volts; peak negative pulse grid No. 1 voltage 200 volts; plate dissipation, 10 watts. The tube has a heater voltage (A-C or D-C) of 6.3 volts; heater current, 1.2 amperes.
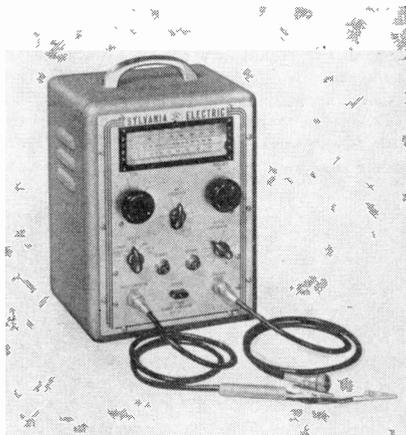
## TV MARKER GENERATOR

A new television marker generator Type 501 designed particularly for use with TV sweep signal generators has been announced by the Radio Tube Division, Sylvania Electric Products Inc., 1740 Broadway, New York 19, New York.

The Sylvania Marker Generator Type 501 provides a means of accurately marking frequencies on the oscilloscope trace of response curves while testing a TV receiver during manufacture or during servicing. Through



the use of the marker generator, which is designed to cover the entire range of TV frequencies, accurate measurements of bandwidth and evaluation of dynamic response at any spot frequency may be made.

## CRYSTAL CARTRIDGE


The Astatic Corporation, Conneaut, Ohio announces its tiny new CAC-J Crystal Cartridge designed for slow speed records.

Ability of the CAC-J to provide high quality performance is attributed to the fact that it is "internally equalized" to follow Columbia Records, Inc., ideal frequency response for the recording characteristics of LP records (30 to 11,000 cycles).

The new cartridge has a small, lightweight aluminum housing with standard 1/2-inch mounting holes to fit most tone arms. It is furnished with an adapter plate to permit mounting in RCA and similar 45 RPM record changers.

Output is listed at approximately six-tenths volt at 1,000 cycles per second on Columbia No. 103 test record and one volt on RCA 12-5-31-V test record.

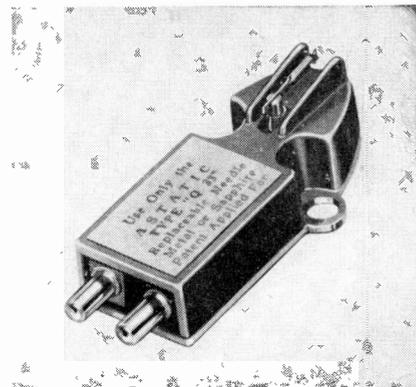The CAC-J is claimed to play both 33-1/3 and 45 RPM records with equal fidelity. Another model, the CAC-78-J, with three-mil needle tip radius for 78 RPM records, is




available.

Both models use the well known Astatic Type Saphire tipped needle, the design of which, in itself, contributes to reduction of needle talk through high lateral and vertical compliance.
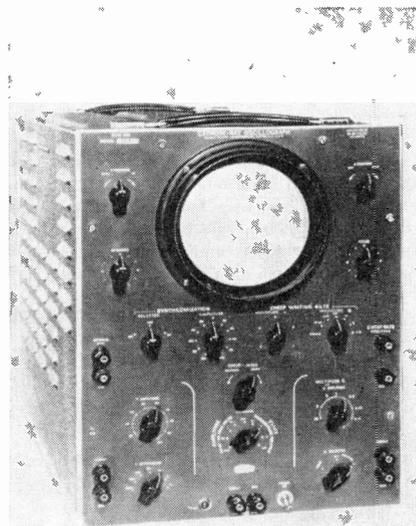
## 10 MC OSCILLOSCOPE

The Instrument Division of Allen B. Du Mont Laboratories, Inc., Clifton, N. J., recently announced a quantitative, 10-megacycle cathode-ray oscillograph, their Type 303. Time calibration is provided for the horizontal sweep of the instrument and regulated voltage calibration for vertical deflection. Both time and voltage calibration are accomplished by substituting a calibrating signal for the input signal.

The Y axis of the instrument, which includes a fixed, signal-delay line, provides a sensitivity of 0.1 volt peak-to-peak per inch. The frequency response of the Type 303 is down 3 db at 10 megacycles with no positive slope in the high-frequency range. Response




falls off slowly past the 10-megacycle point, so that the instrument is usable at frequencies considerably higher than 10 megacycles. The Type 303 will synchronize stably on signals higher than 15 megacycles.
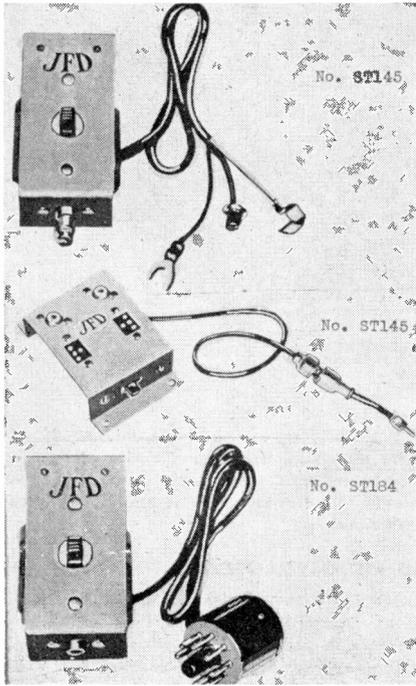
## PHONO-SWITCH ADAPTORS

The popular line of JFD Radio-Phono Switches is being readied for record-breaking sales volume during the fall and winter seasons, according to the JFD Manufacturing Co., Inc. Brooklyn.

The JFD Universal Record Player Selector No. ST144 permits use of a single sound sys-



tem or radio for any 78 rpm, 45 rpm and 33 1/3 rpm record player. Equipped with a special cable adapter, it fits either a 3-pin receptacle or coaxial phono-jack.

JFD Radio-Phono Switches No. ST145 and No. ST184 are designed to connect 78 rpm, 45 rpm and 33 1/3 rpm players to radios not equipped with phono-jacks.

Illustrated literature is available from the manufacturer.

#### LOW R-F IMPEDANCE ELECTROLYTICS


Marked reduction in hum and "hash" often experienced in multi-section electrolytics because of internode coupling and resultant internal cross-modulation, is claimed for currently produced Aerovox Type AFH or twist-prong-base multi-section electrolytics. A special internal construction provides low r.f. impedance and minimum coupling between sections. This desirable feature applies to the exceptionally large selection of capacitance and voltage combinations in the Type AFH electrolytics which are especially suited for



television applications and will withstand temperatures up to 85° C. Manufactured by Aerovox Corporation, New Bedford, Mass.
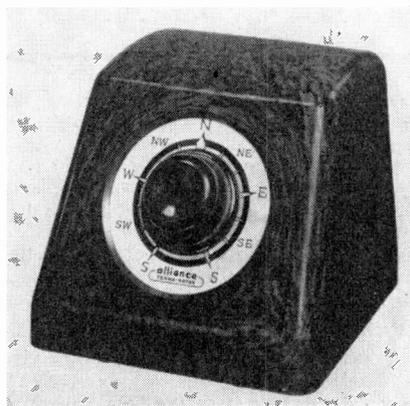
#### DIRECTIONAL DIAL INDICATOR

John Bentia, Sales Manager for The Alliance Manufacturing Company, Alliance, Ohio, announces that the original deluxe model Tenna-Rotor control case, which is fully automatic and which was announced at the NEDA




Show in Cleveland, will be supplied with a NORTH - EAST - SOUTH - WEST direction indicator dial.

The new Model HIR will be advertised in new television films over more than 50 TV stations throughout the country and is available for immediate delivery.
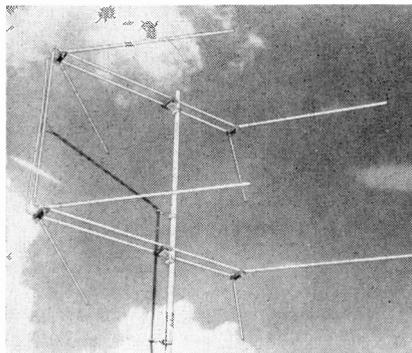
#### TV ANTENNA

A new all-driven-element antenna is announced by Technical Appliance Corporation, Sherburne, N. Y., manufacturers of Taco antenna systems for TV, FM, and AM. This new antenna type has been designed as the 1700 Series and is called the Twin-Driven Corner Antenna.




With all elements driven the directivity of reception has been narrowed, thus minimizing ghosts caused by reflected signals. The front-to-back ratio is extremely high adding to its fine performance. Both high- and low-band lobes coincide due to the phase relationship controlled through feeding.

The antenna elements are merely swung into place and wing nuts tightened to complete the antenna ready for installation. These new antennas are available in single or stacked models, depending upon the requirements of the installation.
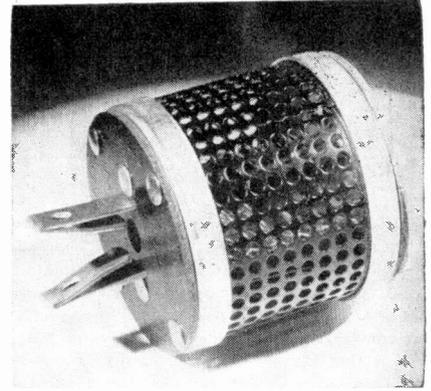
#### TV LINE VOLTAGE REGULATOR

For steadier TV pictures regardless of line-voltage fluctuations, Clarostat Mfg. Co., Inc., Dover, N. H., now offers its Automatic Line-Voltage Regulator to and through its distributors. This aid to still better TV entertainment, particularly in rural districts or areas experiencing line-voltage fluctuations, is really a handy accessory. With male and female Edison connections at either end, it plugs in between the TV set's attachment plug and



the outlet. Two models are available: TV-A rated at 300 watts, for sets consuming 200 to 300 watts, and TV-B rated at 375 watts, for sets consuming 300 to 375 watts.

#### POLICE-TYPE AUTO ANTENNA

A new auto aerial, embodying police and army type construction and mounting features, has been announced by Snyder Manufacturing Company, Philadelphia television, radio and automotive accessory firm. Among its features



are an extra long four-section staff of chrome plated Admiralty brass, shock absorbing spring mount, red ceramic insulators and red tenite static ball.

Complete with 8 feet of UHF polyethylene cable and aircraft fittings, the HOT ROD is the latest addition to the complete line of Snyder Auto Aerials for all types of mounting. Catalog sheets on this aerial may be obtained by writing to Snyder Manufacturing Company, 22nd and Ontario Streets, Philadelphia 40, Pa.


#### CERAMIC DISC CAPACITORS

Centralab, Division of Globe-Union Inc. announces a new line of ceramic disc capacitors. The line includes single, dual and shielded dual capacitors with very high capacities in relation to size, some as small as 1/4 inch diameter. The third dimension—thickness—is virtually eliminated enabling disc capacitors to fit into very narrow spaces. These units are highly efficient as bypass and coupling capacitors in high frequency circuits and the shielded dual discs are especially valuable

[Continued on page 45]



MICA

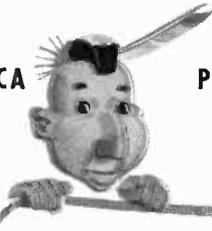

PAPER



ELECTROLYTIC



CAPACITORS


# The Sangamo Tribe means business



34 little Indians to fill your needs . . .

The Sangamo line offers 34 types of mica, paper, and electrolytic capacitors to take care of practically any replacement requirement in the radio and television field.


For example, the line includes Sangamo Micas, which have enjoyed a reputation for excellence throughout the radio and electronic industry since 1923. It includes the famous "Redskin" . . . the plastic molded paper tubular that is easy to work with because the flexible leads can't pull out. It includes a complete range of Electrolytics that will measure up to the toughest assignments in exacting applications where ordinary electrolytics might cause premature failure.

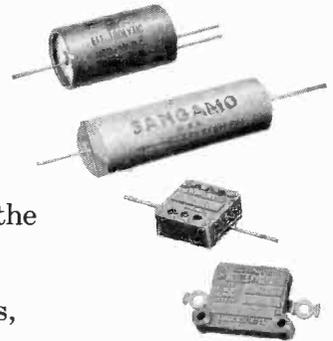

Sangamo Capacitors are packaged in distinctively designed cartons that you can identify with ease and that make inventory simple.

A trial of Sangamo Capacitors will convince you. Stock up at your Jobber.

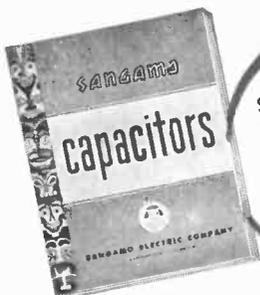*\* Your Assurance of Dependable Performance*



Send for our new Catalog No. 800. It's the most complete replacement catalog in the industry.



**SANGAMO ELECTRIC COMPANY**  
SPRINGFIELD, ILLINOIS


IN CANADA: SANGAMO COMPANY LIMITED, LEASIDE, ONTARIO

SC60-11A
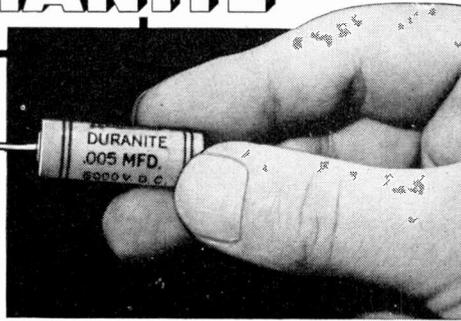
# DURABLE DURANITE

● Durable! That's why Duranite tubulars are so popular. This radically different molded capacitor features Aerolene, the new impregnating methods; new Duranite molded casing.

Drop, bang, scratch—no damage to that durable Duranite casing. Unaffected by high temperatures. Immune to high humidity. Stock them well in advance if you wish—no shelf deterioration. Pigtailed won't



pull out. Definitely, the durable Duranite.

## See Your Jobber...

Insist on Duranites for durable tubulars. Ask your local distributor for latest Aerovox catalog featuring many new capacitor types and extended listings.



CAPACITORS • VIBRATORS • TEST INSTRUMENTS

*For Radio-Electronic and Industrial Applications*

AEROVOX CORPORATION, NEW BEDFORD, MASS., U. S. A. • Sales Offices in All Principal Cities  
Export: 41 E. 42nd St., New York 17, N. Y. • Cable: AEROCAP, N. Y. • In Canada: AEROVOX CANADA LTD., Hamilton, Ont.

## NOW BETTER, BRIGHTER PICTURES

# insuline new "BI-CON" TELEVISION ANTENNA


Single Type and Stacked Array for fringe areas

An engineering triumph by Insuline . . . proved outstanding by actual test. Pre-assembled sections for quick installation.

- Peak ALL-Channel reception.
- Suitable for ANY make TV set.
- Exclusive — separate High Frequency and Low Frequency dipole reflector elements.
- Popularly priced.
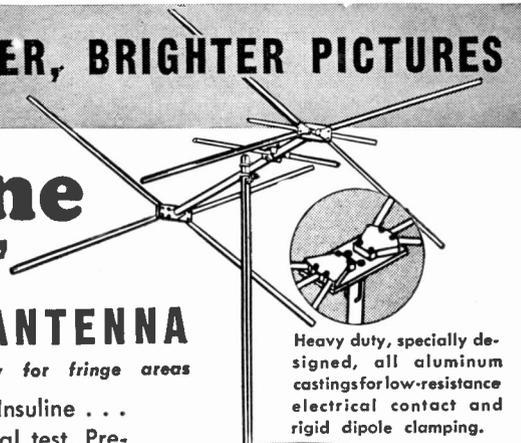
## FREE! New Catalog

Thousands of items including metal goods, radio parts, TV indoor and outdoor antennas and accessories, tools, hardware, etc. Write Dept. RD-12.




Heavy duty, specially designed, all aluminum castings for low-resistance electrical contact and rigid dipole clamping.

## insuline
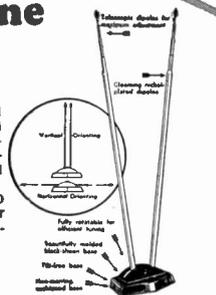
### "molex"

**INDOOR TV ANTENNAS**  
Installed in a jiffy and quickly adjustable to all channels. Supplied complete with 300 ohm connecting lead and open-end mounting lugs.  
**NOTE!** Necessary 300 ohm cable available for all INSULINE TV antennas.



## insuline CORPORATION OF AMERICA

INSULINE BUILDING • 36-02 35th AVENUE • LONG ISLAND CITY, N. Y.  
West Coast Branch and Warehouse: 1335 South Flower Street, Los Angeles, Calif.  
Exclusive Canadian Sales Agents: CANADIAN MARCONI COMPANY, Montreal

## BOOK REVIEWS

Encyclopedia on Cathode-Ray Oscilloscopes and Their Uses, by John F. Rider & Seymour D. Uslan, 992 pages, John F. Rider Publisher, Inc., New York 1950, Price \$9.00.

This is the most complete book on cathode-ray oscilloscopes published to date and, although it covers the subject minutely and includes a vast array of information, every paragraph indicates a careful desire to explain the subject matter simply and clearly.

The first portion of the book deals with the electrical and mechanical theory and application of the 'scope. Also included in this section is an excellent treatment of electrostatic and electromagnetic deflection principles. We particularly enjoyed reading the chapter on Linear Time Bases which is a very complete treatment of this subject.

The second portion of the book deals with the basic oscilloscope and its modifications. This is a single chapter of 130 pages and discusses the various 'scope circuits, their variations and effects, as indicated in the different types of patterns that might be observed.

The third section concerns itself with measurements. This section is described in the chapter headings which are as follows: Phase and Frequency Measurement, Nonlinear Time Bases (measurements utilizing nonlinear sweep systems), Auxiliary Equipment (used in conjunction with measurement), Testing Audio Frequency Circuits, Visual Alignment of AM, FM and TV Receivers, Waveform Observation in TV Receivers, Transmitter Tests, and finally, Electrical Measurement, Scientific and Engineering Applications.

A fourth section (Chapter 20), is devoted to complex waveform patterns. Here we find 82 pages of patterns consisting of fundamentals and harmonics at various combinations of amplitude and phase.

In the fifth and final section, we are treated with a discussion of various special purpose C-R tubes, commercial 'scopes, and related equipment.

A tremendous amount of work and material was evidently entailed in the preparation of this encyclopedia, and any technician who has anything at all to do with the cathode-ray tube



ASSURES YOU the most complete tests of all tubes including television.

ACTUALLY APPLIES 19 separate filament voltages—eliminates usual compromises.

TESTS OVER 700 tubes listed on roll chart—Many thousand tubes used to properly evaluate correct settings.

POSITIVE INDIVIDUAL test of each element.

SPECIAL CIRCUIT feature accurately compensates to provide correct voltages on each tube test.

IMPROVED LEVER switching originated by Triplet for complete control of each tube element.

EACH ELEMENT quickly and conclusively tested for shorts by a flip of the switch.

ILLUMINATED SPEED-ROLL chart with latest tube listings. Kept up-to-date.

LARGE 6" meter—RED-DOT Life-time Guaranteed.

FOR COUNTER or portable use.

**TRIPLET**

MODEL 3413  
TUBE TESTER

*Only*  
**\$69<sup>50</sup>**

COMPLETE WITH ACCESSORIES  
AND INSTRUCTION MANUAL

In Canada: Triplet Instruments of Canada, Georgetown, Ontario

FOR THE MAN WHO TAKES PRIDE IN HIS WORK

**Triplet**

TRIPLET ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO, U.S.A.



# SAVE Up to \$1.00 each. Form a Group, Service Dealers

## Subscribe to "RTSD"-

"The Professional Radio-Television man's Magazine"—published monthly. All articles are exclusive and timely. Practically every issue is worth what an entire 1 year subscription costs.

★ The more in a group the bigger the savings. 6 men in a group save \$1.00 each; 4 men groups save \$ .75 per man. Present "RTSD" subscribers may participate in or form a group with co-workers, or even competitors. Still active subscriptions are automatically extended 1 year. Start a Group today! The timely and exclusive technical data appearing in future issues of "RTSD" will make this the best investment you ever made. The special Group Rate offer may be withdrawn at any time—so hurry.

### Use This Coupon For Convenience

(The coupon below can be used for from 1 to 6 subscription orders. Use it today!)



TEAR OUT — MAIL TODAY

RADIO-TELEVISION SERVICE DEALER MAGAZINE  
342 Madison Ave., New York 17, N. Y.

Please enter 1 year subscription orders for the names given below. Our remittance is enclosed.

NOTE: If you do not wish to tear this order blank out, just print or type the information on a single sheet of paper, following the style given. Each subscriber's occupation must be clearly described.

	In U.S.A. & Canada	Foreign Rates
<input type="checkbox"/> One 1-year subscription	\$2.00	\$3.00
<input type="checkbox"/> Two 1-year subscriptions, each	1.75	2.75
<input type="checkbox"/> Three 1-year subscriptions, "	1.50	2.50
<input type="checkbox"/> Four 1-year subscriptions, "	1.25	2.25
<input type="checkbox"/> Five 1-year subscriptions, "	1.10	2.00
<input type="checkbox"/> Six 1-year subscriptions, "	1.00	1.50

Name .....

Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

Name .....

Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

Name .....

Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

Name .....

Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

Name .....

Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

Name .....

Address .....

Describe Title or Position and Type of Business .....

State whether a New Subscriber  or Renewal Order

and its applications is depriving himself of time-saving and money-making information if he does not obtain this book at once. *S.L.M.*

**Television Servicing** by Walter H. Buchsbaum, 340 pages, Prentice-Hall, Inc., New York 1950, Price \$5.35.

This text is divided into three sections. Part I analyzes receiver circuits, starting with the picture tube and its function and ending with front ends! Other material included in this section deals with the sound system, power supplies and projection units.

In Part II the author discusses alignment and installation. Procedures referring to video and sound alignment are given in the portion devoted to alignment. In the installation section, the author deals with physical location of the receiver, installation procedures and problems and, finally, receiver adjustment.

In the final section, Part III, which deals with trouble shooting, a breakdown of possible receiver symptoms is presented along with corresponding servicing procedures. Thus, inoperative receivers, loss of synchronization, defective deflection systems, poor picture quality, poor sound quality and poor CRT performance are individually analyzed according to effect and cause.

The book is well balanced textwise and is written in a clear and straightforward style. It abounds in illustrations, and coupled with its excellent mechanical makeup (printing, binding, size and layout), it will prove a worthy addition to libraries of those engaged in television servicing. *S.L.M.*

**Second Edition of the Radio and TV Industry Red Book, A Replacement Parts Buyer's Guide**, published by Howard W. Sams & Co., Indianapolis, Ind. Price \$3.95.

This is a truly noteworthy contribution to the industry, providing as it does replacement data on all major receiver components, including AM, FM, TV and radio-phono combinations produced from 1938 to the present.

Replacement components for the receiver of 20 different manufacturers are made available. The manner in which a given part is identified is simple and straightforward; one merely refers to the receiver, and the various replacement components, as catalogued by different manufacturers, are easily identified in their appropriate columns.

The information provided has been divided into eight numerical sections which are as follows:

*Section I* - Component replace listings covering radios and amplifiers produced from 1938 through 1948 (components included are tubes, dial lights, electrolytic capacitors, transformers, chokes, phono-cartridges, IF coils, speakers and controls).

*Section II* - Same components as above covering the period between 1948 to 1950.

*Section III* - Component replacement listings covering postwar television receivers.

*Section IV* - Vibrator replacement listings for the vibrator-powered re-

ceivers produced from 1938 to 1950. *Section V* - Battery replacement listings for battery-power receivers produced from 1938 to 1950.

*Section VI* - Selenium rectifier replacement listings for postwar radios, amplifiers and TV receivers.

*Section VII* - Volume control replacement listings for very popular 1931 through 1938 receivers.

*Section VIII* - Installation notes for applications of Sections 1 through 7 showing references to the specific note required.

For the busy serviceman who wants




**WALSCO**

— in any  
climate,  
anywhere ...


**INSTALL IT  
and FORGET IT**

**new WALSCO SIGNAL-KING**

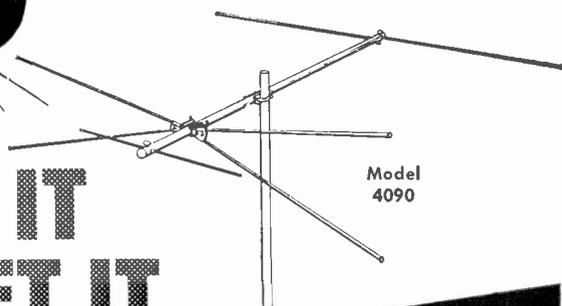


Model 4090

No fear of costly "call backs" that eat up a dealer or installer's profit. In any climate, anywhere ... the new WALSCO Signal King antenna provides sharper, clearer response over entire TV spectrum. Rugged aluminum alloy construction for elements, cross-arm and mast. Corrosion resistant. All steel parts are cadmium plated to AN specifications.

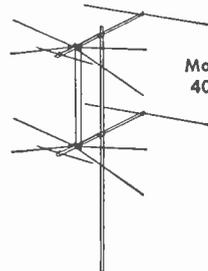

Model 4092

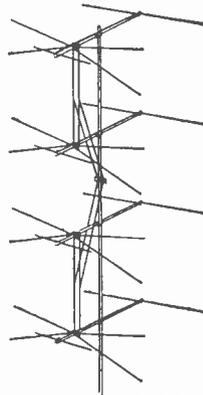

Model 4094

**NOTHING LIKE IT ANYWHERE ...**

- High gain on all channels—no weak spots. Excellent for fringe areas.
- Entirely new insulator guaranteed unbreakable under all operating conditions. Outstanding and lasting dielectric properties.
- Marine type aluminum alloy elements, reinforced and closed ends.
- Assemble in a jiffy (less than 2 minutes).


Write for  
**Information**  
Bulletin No. 51D

**WALTER L. SCHOTT CO.** Beverly Hills, Calif. • Chicago 6, Ill.
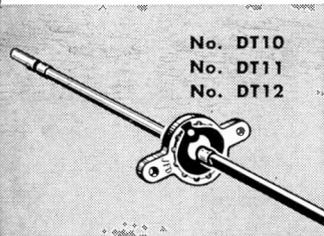
# IT'S **JFD** FOR **DETENT SWITCH CONTROLS**

★ Durable **BRASS** Spring ★ **BRASS** and **PHENOLIC** Shafts.

Look to JFD for the most complete line of Detent Switches on the market! ... exact replacements for RCA, Emerson, Admiral, Teletone and other TV sets. Designed for RCA tuners used in 630, 700 and 721 type chassis. Available with or without locating plates.




No. DT10  
No. DT11  
No. DT12

No. DT10 ... Short shaft, complete with locating plate. (Replaces RCA part No. 71463)  
No. DT20, without locating plate.

No. DT11 ... Long shaft, complete with locating plate. (Replaces RCA part No. 72743)  
No. DT21, without locating plate.


No. DT12 ... Extra long shaft, complete with locating plate. (Replaces Admiral part No. 76B14 used in entire Model Series No. 30A and 8C.)  
No. DT22, without locating plate.

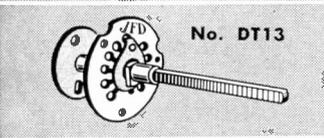[Designed for use with RCA TV Tuner part No. 71531—Replacement type 201E1.]



No. DT13

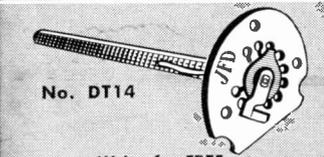No. DT13 ... All phenolic shaft, complete with locating plate. (Replaces RCA part No. 73440.) Designed for use with RCA Tuner Replacement Types No. 74941, 73435, 74571.



No. DT14


No. DT14 ... All phenolic shaft, complete with locating plate, for new RCA TV sets. (Replaces RCA part No. 75162.)

Write for **FREE**  
Replacement Reference Chart



**JFD MANUFACTURING CO., INC.**  
6129 16th Ave. Brooklyn 4, New York  
FIRST in Television Antennas and Accessories
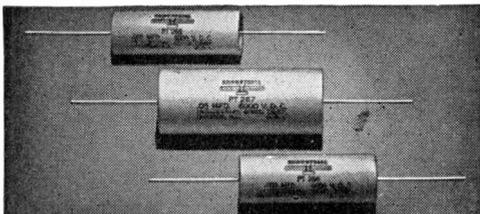
## Insure **BETTER** Television Service to Your Customers! ... *Exclusively Designed*



**HIGH VOLTAGE AND ELECTROLYTIC TUBULAR**

# TELEVISION CAPACITORS

**Especially Engineered for Television Circuits by INDUSTRIAL CONDENSER CORP.**

The economical quality line for replacement. Industrial Condenser Corp., manufacturers of Capacitors exclusively brings you highest quality for the particular requirements of Television as exceptionally attractive prices! Special Capacitors are Pyroteen impregnated for low power factor, high insulation resistance, high operating temperatures. Oil, Pyroteen, Wax and Electrolytic Capacitors. Finest materials throughout.

*Ask Your Jobber for our Attractive Prices Today!*  
Or write for Bulletin 1095. Industrial makes quality Capacitors for Television, Radio, every electronic and industrial application—all types.

Send for Complete Catalog

**INDUSTRIAL CONDENSER CORP.**  
3243 N. CALIFORNIA AVENUE CHICAGO 18, ILLINOIS  
Sales offices in all principal cities.



Modern plant built by Industrial Condenser Corp., for manufacturers of Capacitors only.

*Address*

*Changes ...*

RADIO-TELEVISION SERVICE DEALER, 342 Madison Ave., New York 17, N. Y.

Subscribers to SERVICE DEALER should notify our Circulation Dept. at least 5 weeks in advance regarding any change in address. The Post Office Dept. does not forward magazines sent to a wrong destination unless you pay additional postage. We cannot duplicate copies sent to your old residence. Old and new addresses **MUST** be given.

his replacement part identified in a hurry, this book is a must. *S. L. M.*

## SYNC PULSES

[from page 12]

so why try to impose upon the public a return to small size pictures. 4) — why was an FCC staff engineer who invented a device useable only in the CBS system allowed to influence the commission in favor of adopting a color method that requires use of his brainchild — at least he should have refrained from participating in the making of the decision.

## LOOKING FOR TROUBLE

[from page 25]

The top of *C-90* would always have a positive voltage to ground since that is the side of the condenser going to the plate. In the same manner, a voltmeter across *C-90* would always be positive, whether the condenser is leaky or not. It would show no voltage only if *C-90* were shorted. Bridging a good condenser across a leaky one in this type of circuit would not give any clear-cut indication since it would immediately change the oscillator frequency and throw the picture out of synchronization.

Answer 3—b.

The tube is generally taken out when checking for a leaky coupling condenser and the grid checked for positive voltage because a gassy tube can also cause positive grid voltage. While this possibility was eliminated by changing tubes, it is also possible that a distorted waveform can affect the d-c reading on the grid, as outlined above. With the tube out, the oscillator is not operating and a leaky coupling condenser will give a positive voltage on the grid. This is best checked with a high resistance meter, preferably a VTVM on a low range. There usually is no trouble getting a readable voltage across a high value grid resistor when the coupling condenser is leaky. On the other hand, a low resistance meter is not too reliable for this type of check since it will reduce the total value of resistance in series with the leaky condenser as soon as it is put in parallel with the grid resistor. A small leak-

age current may not give a very large indication on such a meter.

An ohmmeter check across the condenser is not the best method for checking a leaky condenser since it is inconclusive and only shows up when the condenser is very leaky or shorted. On the other hand, the condenser may not check leaky with an ohmmeter and in fact may not become leaky until the voltage is applied and the condenser breaks down again. Besides, why unsolder any connection if there is a quicker and more reliable method which doesn't require unsoldering.

Answer: 4—c

Sawtooth is non-linear on both the plate of the oscillator and grid of the amplifier. Non-linearity is shown by the curve of the waveform along the upper right portion, instead of an angle being formed with straight sides. (See Fig. 3) Non-linearity can originate in the oscillator circuit and be passed on in that form, or the


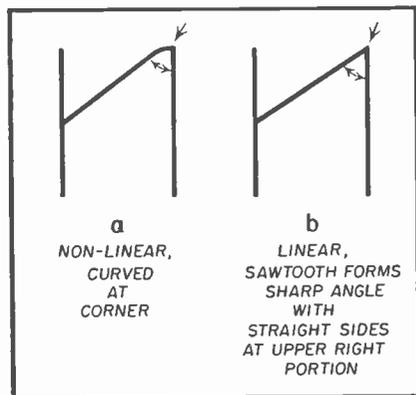


Fig. 3. Non-linear and linear waveforms.

sawtooth can be linear when it is generated and become distorted in the amplifier or output circuits. Where non-linearity is seen at the plate of the oscillator, it may be caused by a fault in the oscillator stage, or the coupling or input to the amplifier stage, which is actually part of the oscillator stage load (leaky coupling condenser, gassy amplifier tube, etc.). However, these last possibilities were fairly well ruled out by the tube and condenser changes already made, unless one of the substituted components was defective.

Resistance values already checked O.K., indicating no resistor had changed value, and so caused the distortion. Condensers were not leaky but it was considered possible that the sawtooth condenser had decreased in value causing it to charge to too great

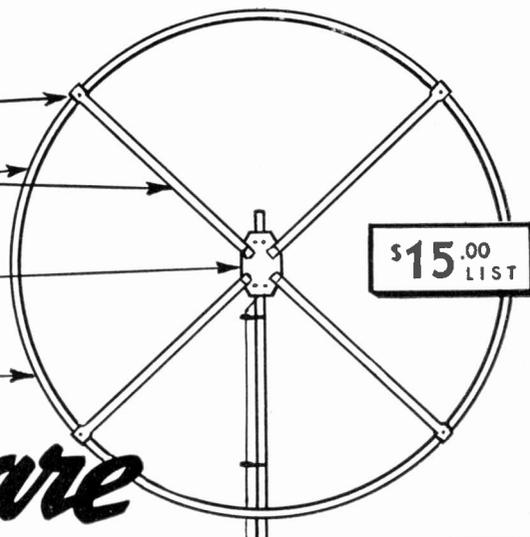- ✓ Bayonet type fitting provides rigid, rapid assembly.
- ✓ High quality corrosion resistant aluminum.
- ✓ High frequency type plastic for superior electrical connection.
- ✓ Circular design — rugged construction — no loose ends.



# Compare

## CIRCLE-X TO ANY OTHER TV ANTENNA

The mechanical and electrical construction of Circle-X is unsurpassed. No other antenna combines all the features that are engineered into the Circle-X. It is perfectly matched to 72, 150 and 300 ohm receiver input circuits.

- One type antenna for all jobs.
- Single lead-in.
- Clear, sharp pictures on all channels.
- Eliminates ghosts.


DEALERS: Air Express or Parcel Post Special Delivery direct from factory to you through your jobber, if he cannot supply you with the Circle-X from his stock.

CIRCLE-X ANTENNA CORP.  
505 MARKET ST., PERTH AMBOY, N. J.



NIAGARA — ONE OF AMERICA'S GREAT ELECTRONICS STORES
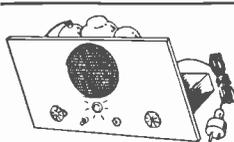
## YOUR MONEY BUYS MORE AT THE NIAGARA STORE!




### 5 WATT AUDIO AMPLIFIER

Complete with speaker and 3 tubes Hi-impedance output for XTAL, mike or Phono-Pickup Volume and tone controls.

5 W. amplif. with 5" speaker ..... \$8.95  
Same as above with 8" speaker ..... \$9.95

### TINIEST V.O.M. IN THE WORLD


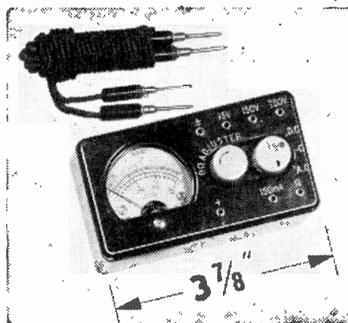


NIAGARA exclusively presents the "Universal Baby Tester," measuring 3 7/8" x 2 1/8" x 1 5/16"! Contains a sensitive 0-240 microammeter with the following ranges.

- 0-15 V AC or DC
  - 0-150V AC or DC
  - 0-100,000 ohms
  - 0-750V AC or DC
  - 0-150V DC MA.
- Ohms adjust and DC-AC-OHMS switch. Includes 1 pair test leads. Will fit into your watch pocket. Fully guaranteed.  
Cat. No. N-258  
SPECIAL ..... \$8.95

### SAVE YOUR FRONT END WITH A

TELEMATIC STURDY-TUNE DETENT

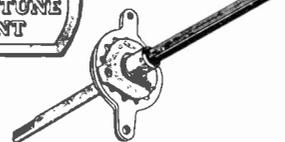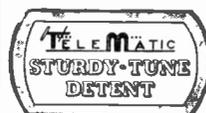

No need to throw out your TV front end tuning assembly — the following listing will repair most types.

Tele Matic #	Replaces	Net Price
1015 short shaft	RCA 71463	\$ .90
1016 long shaft	RCA 727423	.90
1018**	RCA 73440	2.85
1017** long shaft	Admiral 76B14	1.20
1019*	Tele-tone 1/4" shaft	1.20
1039**	" "	1.44
1020*	Tele-tone 3/16" shaft	1.20
1040**	" "	1.44

\* with locating plate      \* less locating plate  
\*\* with locating plate      Write for complete replacement list.



### NEW LOW PRICE NIAGARA'S FAMOUS HIGH PASS FILTER

Banish interference with Niagara's Hi-pass filter! Positive protection against interference from amateur transmitters, diathermy, and all other devices generating radio frequency interference below 40 MCS. Designed for 300 ohm lead-in. No loss in brightness or clarity.  
Wired and tested ..... \$2.50  
Postpaid if full amount is sent with order.  
Write Today for Our Big Free Bargain Bulletin.

Niagara Radio Supply Corp. Dept. D12, 160 Greenwich Street, New York 6, N. Y. Phone Dlgby 9, 1132-34

a value and on the non-linear portion of the charge curve. This could cause foldover. In the same way, change of capacity in the grid leak or coupling condenser would not show up in checks for a leaky condenser but still could distort the waveform. There is no convenient way to check for change in condenser value although it can be done with a capacity checker. However, it is usually more feasible to change condensers for a quick check.

Answer 5—a.

Changing the blocking oscillator transformer eliminated the trouble. This is an unusual reason for foldover. Any possible defect in the integrating circuit or defective cathode condenser (in series with peaking resistor and sawtooth condenser) which could affect the waveform was eliminated from consideration when they were shorted out and the waveform didn't improve. Opening the coupling condenser with the waveform remaining distorted proved trouble was in oscillator circuit. All resistors and condensers in the oscillator circuit had been either checked or changed. Only component left that was likely to cause trouble was the transformer.

Sometimes, in components like a transformer, resistance measurements are inconclusive, since faults like shorted turns may not show up in a resistance reading. However, it can often be found by the principle of exclusion—making certain all other components in the given stage are good, leaving only one component that could be causing the trouble—even though this component may not generally cause that kind of trouble.

Defective tube sockets usually cause intermittent operation rather than this type of distortion. If a resistor has changed value, it generally stays at the new value when the power is shut off. A shorted condenser in the integrating net would have no effect on the oscillator wave-shape but would have some effect on frequency, making it difficult or impossible to keep the picture from rolling vertically.

## COLOR TV

[from page 19]

with this signal is the highest frequency component which is contributed by the mixed highs that are also

sampled at the receiver but were not at the transmitter. However, the mixed-high components in each of the three video channels is approximately the same, but will, nevertheless, produce a high resolution picture. Color levels are, of course, set by the amplitudes of the individual 3.8 megacycle sine waves in each channel and applied to the three grids in timed sequence.

It is interesting to observe that in our basic discussions of sound sampling systems in the previous article, the amplifier which followed the sampler at the receiver only passed information up to the highest frequency of audio to be passed and, therefore, the sampling rate frequency was also filtered, producing only an audio output. However, in the color system the sampling rate is permitted to pass through these receiver video amplifiers and, therefore, the signals as they appear on the grids are in the form of pulsating 3.8 megacycle sinewaves and by properly positioning them on the cut-off characteristics of the picture tube, each can be made to represent a specific group of elements on the television screen. For example, the green 3.8 megacycle sinewave can be at its maximum producing green


## ATTENTION! RADIO SERVICEMEN

THERE ARE THOUSANDS OF OUT-MODED RADIOS IN YOUR "BACK YARD" JUST WAITING TO BE REPLACED . . . AT YOUR SUGGESTION

Here is the custom-built AM-FM chassis that means **BIGGER PROFITS** for you!

THE NEW ESPEY MODEL 511-B FEATURES:

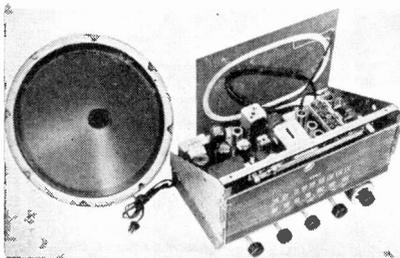1. AC Superheterodyne AM-FM Receiver.
2. Improved Frequency Modulation Circuit, Drift Compensated.
3. 12 tubes plus rectifier, and electronic Tuning Indicator and Pre-Amp. Tubes.
4. 4 dual purpose tubes.
5. Treble Tone control.



6. 6-gang tuning condenser.
7. Full-range bass tone control.
8. High Fidelity AM-FM Reception.
9. Automatic volume control.
10. 16 watts (max.) Push-Full Beam Power Audio Output.
11. 12-inch PM speaker with Alnico V Magnet.
12. Indirectly Illuminated Slide Rule Dial.
13. Smooth, Flywheel tuning.
14. Antenna for AM and folded dipole antenna for FM Reception.
15. Provision for external antennas.
16. Wired for phonograph operation with switch for crystal or reluctance pick-up.
17. Multi-tap output trans. 4-8-500 ohms.
18. Licensed by RCA and Hazeltine.
19. Subject to RMA warranty, registered code symbol #174.

### SPECIFICATIONS

Supplied ready to operate, complete with tubes, antennas, speaker and all necessary hardware for mounting in a table cabinet or console, including escutcheon. Power consumption—105 watts.  
Chassis Dimensions: 13½" wide x 8½" high x 10" deep.  
Cabinet Dimensions: (2 units) 20x14½x10¾ inches  
Net Weight: 17 pounds each.  
Sold through your favorite parts distributor.

Makers of fine radios since 1928.

**ESPEY**  
MANUFACTURING COMPANY, INC.  
529 EAST 72nd STREET, NEW YORK 21, N. Y.

Write Dept. RS-12 for Catalogue and Name of Nearest Distributor.

## THIS IS IT! THE RELAY WITH Interchangeable Coil FOR A WIDE RANGE OF RADIO APPLICATIONS


### GUARDIAN Series 200

Interchangeable

### COIL and CONTACT
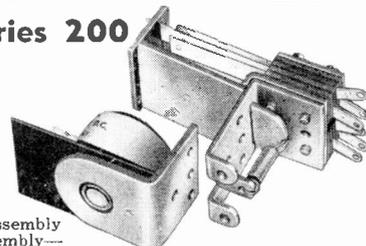
### Switch Assembly

Two basic parts—a coil assembly and a contact switch assembly—comprise this simple, yet versatile relay. The coil assembly consists of the coil and field piece. The contact assembly consists of switch blades, armature, return spring and mounting bracket. The new Guardian Midget Contact Assembly which is interchangeable with the Standard Series 200 coil assembly, is also available in either single pole, double throw; or double pole, double throw.



### CONTACT SWITCH ASSEMBLIES

Cat. No.	Type	Combination	
		Single Pole	Double Throw
200-1	Standard	Double Pole	Double Throw
200-2	Standard	Double Pole	Double Throw
200-3	Contact Switch		
	Parts Kit		
200-4	Standard	Double Pole	Double Throw
200-M1	Midget	Single Pole	Double Throw
200-M2	Midget	Double Pole	Double Throw
200-M3	Midget Contact Switch	Parts Kit	

### 13 COIL ASSEMBLIES


A.C. COILS*		D.C. COILS	
Cat. No.	Volts	Cat. No.	Volts
200-6A	6 A.C.	200-6D	6 D.C.
200-12A	12 A.C.	200-12D	12 D.C.
200-24A	24 A.C.	200-24D	24 D.C.
200-115A	115 A.C.	200-32D	32 D.C.
		200-110D	110 D.C.

\*All A.C. coils available in 25 and 60 cycles

**GUARDIAN ELECTRIC**  
1606-P W. WALNUT STREET CHICAGO 12, ILLINOIS

A COMPLETE LINE OF RELAYS SERVING RADIO AMATEURS

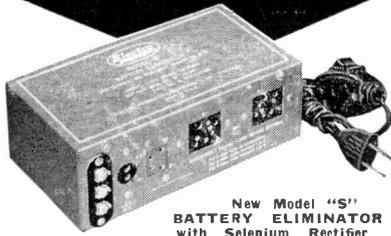**OVER 2 MILLION  
Battery Radios Offer  
Huge PROFIT Market!**




New Model "S"  
BATTERY ELIMINATOR  
with Selenium Rectifier

**CONVERT BATTERY RADIOS  
TO A C ALL-ELECTRIC**

Now is the time your customers want dependable all-electric hum-free performance. Operates any 1.4 volt 4 to 6 tube battery radio from 115 volt 50/60 cycle source. Easily slips into battery space. Guaranteed 3 years. **\$10.65 net**

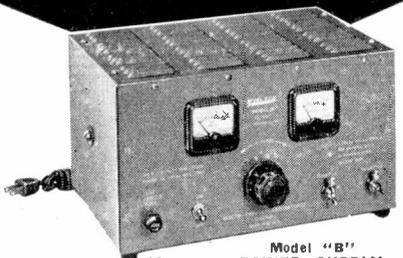**SAVE TIME, MONEY...  
Servicing DC Equipment  
From AC Lines!**



Model "B"  
POWER SUPPLY  
with Conduction Cooling

**DEMONSTRATE AND TEST  
AUTO RADIOS**

... also relays, 'phone circuits, instruments, other low voltage devices. Only filtered power supply with new conduction cooling. Provides lowest cost per ampere output; unequalled power, efficiency, dependability. Costs less than conventional types. 6 Volts, 20 amperes **\$43.50 net**

Ask About New Low Cost  
"BJ" JUNIOR DC POWER SUPPLY  
6 Volts, 12.5 Amperes, **\$32.40 net**

**SEND COUPON NOW!**

ELECTRO PRODUCTS LABORATORIES  
4495-SB Ravenswood Ave., Chicago 40, Ill.

Send new literature and name of nearest jobber.

Name .....

Address .....

City ..... Zone ..... State .....



Pioneer Manufacturers of Battery Eliminators

element illumination. At the same instance, the other two sine waves are beyond cut-off on their respective picture tube grids and that similar elements on the other two grids remain un-illuminated. Just 120 degrees later the red 3.8 megacycle sinewave will reach its crest and light up next element while the other two sines will be below cut-off and the green and the blue grids will be biased off.

Thus, the information is arranging itself on the viewing screen as a series of individual elements, each representing a specific color. If this process continued throughout the individual color pick-up process there would be groups of elements set off on the viewing screen representing just one color. There would be individual groups of green, red and blue elements, each segregated from each other. Such a system, however, would limit the resolution per color and, therefore, the overall definition of the color picture. To improve color operating conditions, however, the sampling pulse circuit is shifted at regular intervals (generally after each frame) so the groups of element which represent one color for a given frame represent still another color for other fields. Thus, each element on a viewing screen is at one time or another representing the light level of each of the three basic colors. Method of transmission is referred to as dot interlace.

In the very latest RCA system using the new single or three-gun color tube only a single video amplifier is needed, video being applied simultaneously to the three grids of a single picture tube gun or to a single grid. In these type tubes there are three separate cathodes which are keyed by sampling pulses, turning on individual color beams in proper order. Each beam strikes its own elements of the three color phosphor and lights it in accordance with amplitude of signal present on the grid at that instant.

**Sampling In Black And White TV**

A similar sampling process can be used to obtain a black and white picture with more elements per line and, therefore, an improvement in apparent resolution. In such a system, the high resolution output of a camera (up to 8-10 mc) is sampled at a high frequency, Fig. 3. Information is again broken up into pulses and then into sampling rate sinewaves. The three sampling rate sinewaves (no frequency in excess of sampling rate) form a composite signal that is the video portion of the television signal which modulates the r-f carrier.

At the receiver this signal is again demodulated into pulses and then

**two rugged  
wirewounds**



**OHMITE**

**BROWN DEVIL**

Vitreous-Enameled Resistors



Provide the utmost dependability and small size. Easily mounted by 1 1/2" tinned wire leads. Three sizes: 5, 10, and 20 watts. Tolerance ± 10%.

**DIVIDOHM**

Adjustable Resistors



Vitreous-enameled resistors, with wire exposed along one side for contact with adjustable lugs. Use for multi-tap resistors or voltage dividers, and for quickly obtaining odd values of resistance.

**NEW OHM'S LAW  
CALCULATOR**

Quickly solves Ohm's Law problems—including parallel resistance. Also has standard slide rule.



**25c**

OHMITE MANUFACTURING CO.  
4846 Flournoy St. Chicago 44, Illinois

Be Right with  
**OHMITE**

Reg. U. S. Pat. Off.

**RHEOSTATS • RESISTORS • TAP SWITCHES**

# 31,475



There are 31,475 models covered completely in RIDER TV—AM—FM—PA MANUALS.

And you may be called upon to service any one of these models . . . today . . . tomorrow . . . next week. Make sure you have the BEST servicing information—when you need it. Complete your RIDER MANUAL Library now. RIDER MANUALS—PROVEN BEST BY 21 YEARS OF TEST.

**In TELEVISION  
5 RIDER TV MANUALS  
★ 10,544 Pages\*  
★ 1,849 Models**  
\* Equivalent of 8 1/2 x 11 ins. size

**RIDER P.A. MANUAL  
★ 2,024 Pages  
★ 1,285 Models**

**In AM-FM-Auto Radio-Phono  
21 RIDER MANUALS  
★ 31,382 Pages  
★ 28,341 Models**

These comprise the world's greatest compilation of ACCURATE — AUTHENTIC — RELIABLE Servicing Information . . . as furnished by the Service Departments of the Manufacturers themselves. And all of it is yours . . . at the astonishingly low cost of LESS THAN 1c PER PAGE!

Plus an **EXTRA**  
feature that is exclusive with  
**RIDER TV MANUALS**

**CIRCUIT ANALYSIS** . . . descriptions of important functions within the receiver . . . pertinent data originating from the manufacturers and presented by RIDER in a manner which makes this added information a valuable aid to the servicing technician—as well as a practical education in the actual design of television receivers.

**John F. Rider Publisher, Inc.**  
480 Canal Street New York 13, N. Y.

See Your Jobber For RIDER MANUALS  
PROVEN BEST BY 21 YEARS OF TEST

back into three sampling pulsating sine waves. These variations (three sampling rate sine waves displaced by 120 degrees are applied to the grid of the picture tube. Each sine wave crest lights up an element on the screen in proportion to the original light intensity. Consequently, sampling forms three complete sets of elements displaced slightly from each other to form a television picture with more elements per line and an improvement in resolution.

#### Synchronizing Of Sampling Generator

A sampling circuit at the receiver must, of course, be synchronized with the sampling frequency and phase at the transmitter. One method of accomplishing synchronization is to utilize the back porch of the horizontal blanking period to transmit a sampling rate sine wave from the transmitter. At the receiver this sampling rate sine wave will be taken off the back porch of the blanking and used to synchronize the generator which forms the sampling rate pulse at the receiver.

To obtain dot interlace it is necessary to shift the sampling pulse in polarity at prescribed intervals. One method is to reverse the polarity of the sampling pulse at the end of each frame and, therefore, a different sequence of sampling will be set up for each frame and dots for element samples will become interlaced. Still another technique is the use of a sampling pulse frequency which is not an interval multiple of the line rate but has a frequency which is an interval and a half times the line frequency. Thus the flip-over of the sampling pulse becomes automatic at the end of each field.

Sampling and multiplex technique open new horizons in the electronic field and may some day, when frequency spectrum becomes too crowded, instigate a major revision of allocations. Possibilities appear unlimited and at present technique is just in its beginning experimental state.

#### KEYED AGC


[from page 17]

or not a short exists. If an ohmmeter gives no reading, and it is suspected that the capacitor is open, it may be bridged with another for a quick check.

With receivers having an adjustable control for proper setting of the a-g-c bias level, poor results may be due to improper adjustment. The
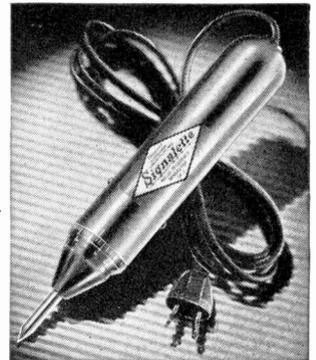
## SHOOTS TROUBLE FASTER!

MAKES MORE MONEY  
FOR YOU ON JOB OR  
AT SERVICE BENCH!



PRICE  
\$9.95 at  
Distrib-  
tor or  
postpaid,  
direct  
No COD's  
please.  
Ohioan's  
add 3%  
State  
Sales Tax

## Signalette

#### MULTI-FREQUENCY GENERATOR

In radio service work, time means money. Locate trouble faster, handle a much greater volume of work with the SIGNALETTE. As a trouble shooting tool, SIGNALETTE has no equal. Merely plug in any 110 V. AC-DC line, start at speaker end of circuit and trace back, stage by stage, listening in set's speaker. Generates RF, IF and AUDIO Frequencies, 2500 cycles to 20 Megacycles. Also used for checks on Sensitivity, Gain, Peaking, Shielding, Tube testing. Wt. 1.3 oz. Fits pocket or tool kit. Satisfaction, or money back! See at your dist. or order direct.

#### CLIPPARD INSTRUMENT LABORATORY, INC.

Dept. F, 1125 Bank Street  
Cincinnati 14, Ohio

Qualified Jobbers write, wire for details.

## TELEVISION WIRE

300 OHM Twin Lead Television Wire, for immediate shipment. 1500 ft. Spools at \$40.00 per 1000 ft. net. Check with order, or 25% deposit required on C.O.D. orders. F.O.B. N.Y.C.

**L and L Products Co.**  
537 Timpson Place  
New York 55, N. Y.

## AD INDEX

Aerovox Corporation .....	36
Air King Products Co., Inc. ....	5
Alliance Manufacturing Co. ....	Cover 3
Astatic Corporation, The .....	8
Circle X Antenna Corp. ....	41
Clippard Instrument Lab, Inc. ....	44
Commercial Trades Institute .....	45
Electro Products Labs .....	43
Espey Manufacturing Co., Inc. ....	42
Guardian Electric Mfg. Co. ....	42
Hallicrafters Co., The .....	1
Heath Company, The .....	13
Hytron Radio & Electronics Corp. ....	11
Industrial Condenser Co. ....	40
Insuline Corp. of America .....	36
Jackson Electrical Instrument Co. ....	10
JFD Manufacturing Co., Inc. ....	40
L & L Products Co. ....	44
Mallory, P. R. & Co., Inc. ....	3
Niagara Radio Supply Corp. ....	41
Ohmite Manufacturing Co. ....	43
Radiart Corporation, The .....	9
RCA Service Company .....	45
RCA Tube Dept. ....	Cover 4
Regency Div., I.D.E.A., Inc. ....	Cover 2
Rider, John F. Publisher, Inc. ....	44
Sangamo Electric Company .....	35
Schott, Walter L. Co. ....	39
Snyder Manufacturing Co. ....	14
Sprague Products Company .....	4
Standard Coil Products Co. ....	6, 7
Triplet Electrical Instrument Co. ....	37
Universal Television System .....	45
Workshop Associates, Inc. ....	12

## JOB CONDITIONED!

### ABLE, ALERT MEN— READY FOR WORK!

Thoroughly trained in TV Installation and Service by UNIVERSAL TV SCHOOL (Est. 1938), Pioneer TV Training School. Screened men, willing to work and eager to demonstrate their skill. Expertly guided on modern TV test equipment, these men have completed 9 months intensive training and are fully groomed for industry. When in need of TV installation or bench man please contact us. This service is FREE. Write or wire

### UNIVERSAL TELEVISION SYSTEM

Wirthman Bldg. Kansas City 3, Mo.  
G. I. APPROVED

## \$1.00 to \$5.00 PAID for "SHOP NOTES"


Write up any "kinks" or "tricks-of-the-trade" in radio servicing that you have discovered. We will pay from \$1 to \$5 for such previously unpublished "SHOP NOTES" found acceptable. Send your data to "Shop Notes Editor," RADIO SERVICE DEALER, 342 Madison Ave., New York 17, N. Y. Unused manuscripts cannot be returned unless accompanied by stamped and addressed return envelope.

control should be set so that the picture is stable for the strongest station in the area. Adjustment should also, however, be made to give the best noise-free reception, and the snow effect on the screen should be studied while making corrections on the adjustable a-g-c control. Check for stability on the strongest station, and the best signal to noise ratio on the weaker stations.

An oscilloscope will facilitate trouble shooting by giving an indication of the composite video signal, blanking and sync tips on the grid of the a-g-c tube, and it will also show the absence or presence of the horizontal pulse on the plate circuit. Not only must both components be present in order for keyed AGC to function properly, but the receiver must be synchronized with the incoming signal so that the horizontal pulses will occur simultaneously with the applied sync tips to the a-g-c tube.

## NEW PRODUCTS

[from page 34]

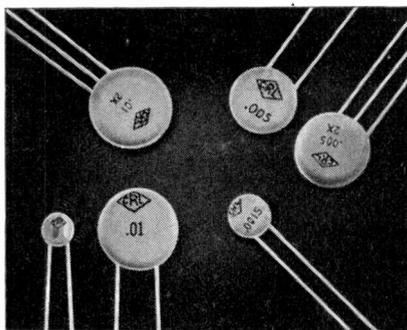


for bypassing in multiple stages because they will function with freedom from feed back.

The ceramic discs use No. 22 tinned soft copper wire radial leads which permit easy, close coupled connections and eliminate tricky bending and fitting. These discs have a low
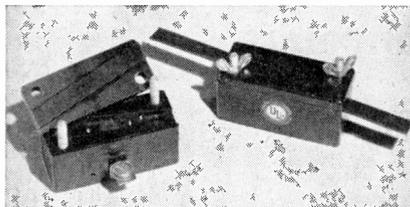
### TV LIGHTNING ARRESTER

Jerome E. Respass, President of LaPointe-Plascomold Corporation (VEE-D-X) Unionville, Connecticut announced that the Vee-D-X 4-wire lightning arrester (RW-204) is now being constructed of high dielectric, double phenolic. This material, he stated, is for



installation in accordance with the National Electric Code and is also approved by Underwriter's Laboratories (UL). He further stated that it is the first and only arrester designed to accommodate 4-wire rotator line as well as regular 300 ohm transmission line.

## ELECTRONICS TECHNICIANS WANTED

The RCA Service Company, Inc., a Radio Corporation of America subsidiary, needs qualified electronics technicians for U. S. and overseas assignments. Candidates must be of good character and qualified in the installation or maintenance of RADAR or COMMUNICATIONS equipment or TELEVISION receivers. No age limits, but must have at least three years of practical experience.

RCA Service Company offers comprehensive Company-paid hospitalization, accident and life insurance programs; paid vacations and holidays; periodic review for salary increases; and opportunity to obtain permanent position in our national and international service organization, engaged in the installation and maintenance of AM, FM, and TV transmitters, electronic inspection devices, electron microscopes, theatre and home television, r-f heating equipment, mobile and microwave communications systems, and similar electronic equipment.

Base pay, overseas bonus, payments for actual living and other expenses, and benefits mentioned above add up to \$7,000 per year to start for overseas assignments, with periodic review of base salary thereafter. Openings also available at proportionately higher salaries for specially qualified technicians with supervisory ability.

Qualified technicians seeking an advantageous connection with a well-established company having a broad-based, permanent peacetime and wartime service program, write to:

Mr. G. H. Metz, Personnel Manager,  
RCA Service Company, Inc.,  
Camden 2, New Jersey.

## HAVE YOU A JOB FOR A TRAINED TECHNICIAN?

We have a number of alert young men who have completed intensive training in Radio and Television Repairing. They learned their trade thoroughly by working on actual equipment under personal, expert supervision. If you need a trained man, we invite you to write for an outline of our course, and for a prospectus of the graduate. No fees, of course. Address:

Placement Manager, Dept. P105-12

COMMERCIAL TRADES INSTITUTE  
1400 Greenleaf Chicago 26

### Address changes . . .

must reach our circulation department 5 weeks in advance if service is to continue without interruption. Old and New addresses MUST be given.

RADIO-TELEVISION SERVICE DEALER  
342 Madison Ave., New York 17, N. Y.

## REPRESENTATIVE

Long Island, New York. One million people (equal to Boston). This vast area requires resident coverage. We cover dealers and jobbers like a blanket. Radio, TV supplies only.

Ten Years Experience — BOX 33R

# 1950 INDEX ★ RADIO-TV SERVICE DEALER

## ANTENNAS & INSTALLATION

All-aluminum TV Mast (New Prods.)	Feb.
All-channel Antenna (New Prods.)	June
All-channel TV Antenna (New Prods.)	July
Antenna Bracket (Trade Flashes)	July
Antenna Rotator (New Prods.)	Jan.
Antenna Rotator (New Prods.)	Mar.
Antenna Switch (New Prods.)	June
Assembling Coaxial Cable Connectors	Apr.
Automatic TV Ant. Rotator (Trade Flashes)	Dec.
Chimney Mount (New Prods.)	Aug.
Clover-V-Beam Ant. (New Prods.)	Apr.
Conical Antennas (New Prods.)	July
Conical-V-Beam Ant. (New Prods.)	June
Directional Dial Indicator (New Prods.)	May
5-Element Yagi Ant. (New Prods.)	Dec.
Erection of TV Tower, by Ransom Beers	Nov.
Indoor TV Antenna (New Prods.)	July
Jack-Up Tower & Rotator (New Prods.)	Feb.
Landlords, Tenants & TV Antennas, by G. I. Nierenberg	June
Lightning Arrestor (New Prods.)	May
Lightning Strikes TV Antenna	Jan.
Master TV Ant. System In Motels, by Ira Kamen	Nov.
Nail Polyethylene Standoff (New Prods.)	Oct.
New Antenna Book (Trade Flashes)	Feb.
New Indoor Antenna (New Prods.)	Nov.
New Indoor TV Ant. (New Prods.)	Apr.
New Insulating Tape (New Prods.)	Aug.
New TV Aerial System (Trade Flashes)	May
New TV Antennas (New Prods.)	Aug.
New Ward Yagi (New Prods.)	Nov.
One Man TV ant. Orientation, by E.M. Noll	Oct.
Philco Antenna Bulletin (Trade Flashes)	May
Police Type Auto Antenna (New Prods.)	Jan.
Profits in TV Installations, by C. Golenpaul	Dec.
Reducing Losses in Transmission Lines, by Norman L. Chalfin	Apr.
TV Ants., Built-in (Editorial)	Oct.
TV Ants., Legal Aspects (Field Finds.)	Mar.
TV Antennas (New Prods.)	Jan.
TV Antenna (New Prods.)	Mar.
TV Antenna (New Prods.)	Apr.
TV Antenna (New Prods.)	Dec.
TV Ant. Accessories (New Prods.)	Apr.
TV Ant. Safety Precautions (Field Findings)	Apr.
TV Antennas Violate Laws (Edit.)	Jan.
TV Installation Book (Trade Flashes)	Sept.
TV Lightning Arrestor (New Prods.)	Sept.
TV Lightning Arrestor (New Prods.)	Feb.
TV Lightning Arrestor (New Prods.)	Apr.
TV Lightning Arrestor (New Prods.)	Dec.
TV Tower (New Prods.)	June
Twin Driven Yagi (New Prods.)	Mar.
Unique Arrestor Idea (New Prods.)	June
Yagi Antennas (New Prods.)	May

## ASSOCIATIONS & COMMITTEES

Keller To Organize New RTMA Group, (Trade Flashes)	Aug.
Phila. Servicemen's Exhibit, (Trade Flashes)	July
PRsMA (Trade Flashes)	Apr.
Town Meeting Committee Named (Trade Flashes)	Nov.
RMA (Trade Flashes)	Apr.
Small TV Tubes Passe (RMA Edit.)	May
RMA (Field Findings)	June
RTMA to Set Ant. Ad. Standards (Trade Flashes)	Oct.

## AUDIO

Admiral Increasing Audio Output On "30 Series" TV Chassis (Shop Notes)	May
Audio Voltage Amplifier (A Comparison of AM-& FM Servicing Problems, by J. Jacobson)	Oct.
Oscillator Injector For Audio Servicing, by Rufus P. Turner	Oct.
Phono-Switch Adaptor (New Prods.)	Dec.
Short-cuts in Audio Servicing, by Matthew Mandl	June
Understdng Push-Pull, by Allan Lytel	Apr.

## BUSINESS MANAGEMENT

Astatic Merchandises Booster Via TV, (Trade Flashes)	Mar.
--	------

Better Business Bureau of NLYL Sets Standards ("Voluntary Fair Practices Code" Trade Flashes)	Aug.
Hal Bersche Firecasts Billion Dollar Market (Trade Flashes)	Oct.
G.E. Tube Campaign (Trade Flashes)	Mar.
How To Estimate Your 1950 Tax, by Betty Lee Gough	Feb.
More TV Statistics (Field Findings)	June
New Merchandising Policy (Trade Flashes)	Nov.
New RCA Contract Plan (Trade Flashes)	Jan.
RCA Service Clinic (Trade Flashes)	June
Small Ad Dollar Savers, by E. W. Fair	Jan.
Summertime TV Slack (Field Findings)	June
TV Legal Aspects (Field Findings)	Jan.
TV Service Advertisement (Field Findings)	June

## CHARTS & GRAPHS

Attenuator Chart	Jan.
Characteristics of Coaxial Cable Twin lead & Shielded Twin Conductor	June
Curves Showing Effect of Demagnetization Upon Frequency Response	July
Frequency Relationships of Pix & Sound Carriers in R-F & I-F Stages (Front Ends)	Sept.
Jensen Needle Replacement Chart	Oct.
New Jensen Freq. Range Rating System (Shop Notes)	Feb.
Philco Universal Pix Tube Test Adapter (Shop Notes)	May
1949 Production Figures (Trade Flashes)	Mar.
Receiver Prod. Figures, 1st Quarter 1950 (Trade Flashes)	June
Receiver Production Figures, 1st Nine Months of 1950 (Sync Pulses)	Nov.
Reducing Losses In Transmission Lines, by Norman L. Chalfin	Oct.
Response/Frequency Characteristics Chart	July
TV Picture Tube Chart	Mar.

## CIRCUIT COURT

Admiral Model 19A1	Mar.
Admiral 6Q1	Oct.
Aircastle Model 211	Nov.
Airline Model 64BR-7810A	Jan.
Airline Model 84GSE3011A	July
Belmont Model 22AZ1	Feb.
Bogen Model PX10	Mar.
Capehart Model 413 P	Nov.
Capehart Models 115P2, 414P, 414P	Oct.
General Electric Co. Model 805	Sept.
General Electric Co. Models 324, 328	May
Hoffman Model CT800	Feb.
Kappler Model 102 T	July
Magnavox Model CT214	Sept.
Philco Model 49-1600	May
Recordio Model 8J10	Sept.
Temple Model TV-1776	July
Truetone Model D4842	July

## COLOR TV

Color TV Fiasco (Editorial)	Nov.
Color TV Servicing (Editorial)	Nov.
Color TV (I Told You So, by San D'Arcy)	Apr.
Color TV (I Told You So, by San D'Arcy)	May
Sampling Techniques Applied to TV, by Ed. M. Noll	Dec.
The CBS System of Color TV	Nov.

## EDITORIALS

The Annual Index	Jan.
Another Parks' Blunder	Oct.
BBB Complaints Increasing	May
Bright Prospects	Apr.
Built-In Antennas—Ha! Ha!	Mar.
Color TV Fiasco	Nov.
Color TV Held Back	Dec.
Copycats	Jan.
Extended TV Lines	Sept.
Industry "Czar"	June
Korean War's Effect	Aug.
Industrial Maintenance	Jan.
Line of Demarcation	Apr.
Nat'l "Fix Your Radio" Month	Feb.
N.Y.'s "Fair Practice Code"	Aug.
"Permanent" Needles	Oct.
Progress Report	Apr.
Radio Reviving	July

Replacement Supply Problem	Feb.
Servicemen's Clinics	July
Servicing Color TV	Nov.
Small TV Tubes Passe	May
The Poor Public	May
Troublesome Days Are Ahead	Dec.
TV Antennas Violate Laws	Sept.
TV A Killer—Beware!	July
TV Manpower Shortage	Feb.
Welcome Students	Mar.

## FEATURE ARTICLES

A Comparison of AM & FM Servicing Problems, by J. Jacobson	Oct.
Auto Radio Drive-In, by Allan Lytel	May
A Studio for Servicemen, by Arthur Lindsey	Nov.
Assembling Coaxial Cable Connectors	Dec.
Automatic Frequency Control For Local Oscillators, by Allan Lytel	Mar.
Build This Winch for Erection of TV Towers, by Ransom Beers	July
Combination Inductance Bridge, by Rufus P. Turner	June
Construction & Operation of A Cable Spinner, by Alfred Czarnecki	Nov.
Conversion of 630TS Chassis to 3 ft by 4 ft Projection, by V. R. Parker	June
Cycle Inventory Control, by Henry Hutchins	Aug.
Does The Radio-TV Technician Belong Dollar Savers, by Ernest W. Fair	Jan.
Electrical Requirements of Tape Recorders, by C. A. Tuthill	Nov.
Elements of TV Signal Distribution, Part 1, by Samuel L. Marshall	May
First Aid to Cabinets, Part 1, by Wm. R. Wellman	Apr.
First Aid to Cabinets, Part 2, by Wm. R. Wellman	May
Front Ends, Part 1, by Samuel L. Marshall	June
Front Ends, Part 2, by Samuel L. Marshall	July
Front Ends, Part 3, by Samuel L. Marshall	Sept.
Front Ends, Part 4, by Samuel L. Marshall	Oct.
Front Ends, Part 5, by Samuel L. Marshall	Nov.
Front Ends, Part 6, by Samuel L. Marshall	Dec.
High Quality Analysis Series No. 4 (Meissner 9-1091-C) by C. A. Tuthill	Feb.
High Quality Analysis Series No. 5 (Hallcrafters S-41) by C. A. Tuthill	Aug.
High Quality Analysis Series No. 6 (Midwest JC-16) by C. A. Tuthill	Dec.
Horizontal A.F.C. Circuits, Part 1, by Walter H. Buchsbaum	July
Horizontal A.F.C. Circuits, Part 2, by Walter H. Buchsbaum	Aug.
Horizontal A.F.C. Circuits, Part 3, by Walter H. Buchsbaum	Sept.
How to Estimate Your 1950 Tax, by Betty Lee Gough	Feb.
Improving Focus in TV Receivers, by Matthew Mandl	Mar.
In The TV Retailing Business?	Dec.
Know The Cathode Ray Tube, Part 1 by Allan Lytel	Oct.
Know The Cathode Ray Tube, Part 2, by Allan Lytel	Nov.
Landlords, Tenants & TV Antennas, by Gerald I. Nierenberg	May
Large Screen Projection, by Allen Lytel	Feb.
Lightning Strikes A TV Antenna	Nov.
Looking For Trouble? No. 1 by Cyrus Glickstein	Sept.
Looking For Trouble? No. 2 by Cyrus Glickstein	Dec.
Master TV Antenna Systems in Motels, by Ira Kamen	Oct.
Mechanical Features of Tape Recorders, by C. A. Tuthill	Sept.
One Man TV Antenna Orientation, by Ed. M. Noll	May
Operation 6 Service of Keyed AGC Systems, by Matthew Mandl	Dec.
Oscillator Injector for Audio Servicing, by Rufus P. Turner	Oct.
Picture Tube Characteristics Chart	Mar.
Reducing Losses In Transmission Lines, by Norman L. Chalfin	Oct.
Repairing Geiger Counters Can Be Profitable, by John L. Parker	Feb.
Sampling Techniques Applied to TV, by Edward M. Noll	Dec.
Shop Overhead Analysis, by Frank H. Russell	Nov.
Short Cuts in Audio Servicing, by Matthew Mandl	June
Servicing FM Detector Systems, by Matthew Mandl	Aug.
Servicing Sync Separators, by Matthew Mandl	Apr.

# RADIO-TV SERVICE DEALER ★ 1950 INDEX

Television Signal Tracing with Lightning Speed, by Marvin Kaplan Jan.  
 Theory of Tape Recorders, by C. A. Tuthill July  
 Theory & Practice of Video Detector Circuits, by Henry A. Schwartz Aug.  
 The CBS System of Color TV Nov.  
 The Serviceman's TV Chassis, by Chas. A. Hobbs, Jr. Sept.  
 The 'Scope as a Modern Service Tool, Part 2, by Matthew Mandl Jan.  
 The Television Waveform & Its Components, Part 1, by Samuel L. Marshall Jan.  
 The Television Waveform & Its Components, Part 2, by Samuel L. Marshall Feb.  
 The Television Waveform & Its Components, Part 3, by Samuel L. Marshall Mar.  
 The Television Waveform & Its Components, Part 4, by Samuel L. Marshall Apr.  
 Time Multiplex Transmission, by Ed. M. Noll Nov.  
 Tube Checkers, by Wm. R. Wellman Jan.  
 TV Sync Sweep Tracing with Lightning Speed, by Marvin Kaplan May  
 U.H.F. Tuning Elements, by Allan Lytel June  
 Understanding Push-Pull, by Allan Lytel Apr.  
 What Have We To Gain Or Lose In TV? by Charles Golenpaul Apr.

## FIELD FINDINGS

More TV Statistics June  
 Phonograph Drive Planned June  
 Record Speed Issue Clarification Jan.  
 Summertime TV Slack June  
 TV Legal Aspect Jan.  
 TV Safety Precautions Jan.  
 TV Service Advertising June  
 TV Wire Links June

## FM

Circuit Court May  
 Comparison of AM & FM Servicing Problems Oct.  
 High Quality Analysis Series, Part 4 Feb.  
 High Quality Analysis Series, Part 5 Aug.  
 High Quality Analysis Series, Part 6 Dec.  
 Servicing FM Detector Systems Feb.

## GENERAL INTEREST

1951 Audio Fair (Trade Flashes) Oct  
 Color TV (Told You So, by Dan D'Aarcy) Apr.  
 Color TV May  
 Cycle Inventory Control, by Henry Hutchins Aug.  
 First Aid To Cabinets, Part 1 Apr.  
 First Aid To Cabinets, Part 2 May  
 "Hal" Bershe Forecasts Billion \$ Market, (Trade Flashes) Oct.  
 Installment Buying Controls (Sync Pulses) Oct.  
 Jensen Replacement Needle Guide Oct.  
 Know The Cathode Ray Tube Oct.  
 Landlords, Tenants & TV Antennas May  
 Licensing Looms Again (Field Findings) June  
 Mass Meet Protest Licensing, (Trade Flashes) July  
 NEDA Exhibit Well Attended (Trade Flashes) Nov.  
 New Merchandising Policies (Trade Flashes) Nov.  
 New RCA Contract Plan (Trade Flashes) Jan.  
 NLY's "Fair Practices Code" (Editorial and Trade Flashes) Aug.  
 Odor 1331 Elected Operating VP (Trade Flashes) Nov.  
 Radio Service Dealer TV Picture Tube Chart Mar.  
 Radio Makers Set Ultimatum (Sync Pulses) Sept.  
 Record-Speed Issue Clarified (Field Finding) Jan.  
 Repairing Geiger Counters May Be Profitable Feb.  
 Shortage (Sync Pulses) Oct  
 TV Antennas Violate Laws (Editorial) Sept.  
 TV Micro-Wave Starts (Sync Pulses) Oct.  
 Town Meeting Committee Named (Trade Flashes) Nov.  
 Understanding Push-Pull Apr.  
 What Have We To Gain Or Lose in TV? Apr.

## HIGH FIDELITY

Front Ends July  
 High Quality Analysis Series (AM-FM Tuner) Feb.

High Quality Analyses Series Aug.  
 High Quality Analyses Series Dec.  
 Jensen Introduces New Speaker (Trade Flashes) July  
 New Blue Cone Speaker (New Prods.) June  
 Servicing FM Detector Systems Aug.  
 The TV Waveform & Its Components 1,000,000 TV Tuners (Trade Flashes) Jan.

## I TOLD YOU SOLD (A Regular Department)

Color TV Apr.  
 Color TV May  
 Coop Radiators Mar.  
 Decca Adds 45 Aug.  
 FM's Second Chance Aug.  
 Get Me Down! Apr.  
 Government Buying Aug.  
 History Repeats Mar.  
 Pay-To-See-TV Mar.  
 Picture Tube Sizes & Shapes May  
 Radioactive Ores Apr.  
 TV Antenna Troubles May  
 Unionization Mar.  
 We Told You So (Re: record speeds) Apr.  
 WJZ-TV Mar.

## NEW PRODUCTS

All Channel Antenna June  
 All-channel TV Antenna July  
 Antenna Rotator Mar.  
 Antenna Rotator June  
 Antenna Switch Apr.  
 Attachable Shaft for Controls Aug.  
 Auto Radio Antenna Oct.  
 Audio Units Apr.  
 Beam Adjuster Sept.  
 Bent-Gun Ion Trap Jan.  
 Blast Filter for Mikes Apr.  
 Boosters-Blonde or Brunette Sept.  
 Capacity Bridge Oct.  
 Ceramic Disc Capacitors Aug.  
 Chimney Mounts Mar.  
 Chimney Mounts Apr.  
 Clover-V-Beam Antenna July  
 Cobra Type Loudspeakers Mar.  
 Concentric Control Assortment June  
 Conical Antenna June  
 Crystal Cartridge Dec.  
 Detent Switch Controls May  
 Directional Dial Indicator Dec.  
 Double Heat Soldering Irons July  
 Dual-Concentric Controls Oct.  
 DuMont Type 12LP4A tube June  
 Dynamic Microphone Feb.  
 Electronic VOM Mar.  
 Electronic VOM Cap. Meter Mar.  
 5-Element Yagi Nov.  
 Grommet & Inserting Tool Aug.  
 Hearing Aid Oct.  
 High Frequency Tweeter Jan.  
 High-Pass Filter Sept.  
 High Voltage Tester Apr.  
 H. V. Coupler Controls July  
 Indoor TV Antenna Feb.  
 Impedance Bridge Kit Jan.  
 Inter-Com Annunciator Apr.  
 Interference Locator May  
 Isolation Transformer July  
 Jack-Up Tower & Rotator June  
 Lab Type VOM Jan.  
 Lightning Arrestor Jan.  
 Locking Shaft Potentiometer Sept.  
 Low Drain Portable Tubes Apr.  
 Low Noise Pentode June  
 Low R-F Impedance Electrolytics June  
 Milner All-Aluminum TV Mast Feb.  
 Miniature Metal-Cased Tubulars Aug.  
 Miniature Resistor Jan.  
 Miniature Tubes Feb.  
 Nail Polyethylene Standoff July  
 New Miniature Tubes June  
 New All-Channel Booster Sept.  
 New Beam Power Tube Sept.  
 New Bent Gun Oct.  
 New Blue Cone Speaker June  
 New Capacitors May  
 New Conical -V-Beam Antenna May  
 New Fuse Holder June  
 New Hytron Tube 1X2A June  
 New Indoor Antenna Apr.  
 New Insulating Tape May  
 New Kit Nov.  
 New Loudspeaker Apr.  
 New L Pad Oct.  
 New Picture Tubes Apr.

New Radio Indoor TV Antenna Aug.  
 New Speaker May  
 New TV Antennas Nov.  
 New TV Antenna Brackets Jan.  
 New TV Booster Nov.  
 New TV-FM Boosters Oct.  
 New Tubes Jan.  
 New Tuner Oct.  
 New Ward Yagi Oct.  
 New 3-Way Portable May  
 New 3-Way Portable Aug.  
 Ohm's Law Calculator Mar.  
 Omi-Directional Microphone Jan.  
 Ore Detector Kit June  
 Panel Instruments Nov.  
 Phono Cartridges Mar.  
 Phono-Switch Adaptors Dec.  
 Police-Type Auto Antenna Dec.  
 Portable TV Service Lab. Aug.  
 Quick-Shot Soldering Iron July  
 RCA 16P4 Mar.  
 RCA 16GP4 Components Feb.  
 Rectangular Tubes 14CP4, 16KP4 June  
 Replacable Stylus Assembly Mar.  
 Servicing Tool Kit July  
 Signal Generator Kit Sept.  
 Slave Projection Unit June  
 Soldering Gun Apr.  
 Steatite Center Jan.  
 Sweep Generators Nov.  
 Tapped Isolation Transformer Apr.  
 Tube Tester June  
 Tube Testers Mar.  
 TV Antenna Mar.  
 TV Antenna Apr.  
 TV Antennas Nov.  
 TV Antenna Dec.  
 TV Antenna Accessories Apr.  
 TV Capacitors Mar.  
 TV Components Jan.  
 TV Components July  
 TV Components Nov.  
 TV Fuse Kit Sept.  
 TV Horizontal Transformers Jan.  
 TV Lightning Arrestors Feb.  
 TV Lightning Arrestor Apr.  
 TV Lightning Arrestor Dec.  
 TV Line Voltage Regulator Dec.  
 TV Marker Generator Dec.  
 TV Sweep Generator May  
 TV Tool Kit July  
 TV Wave Traps Nov.  
 Twin Drive Yagi Mar.  
 Unique Arrestor Idea June  
 Vaco's Screw-Holding Driver Aug.  
 Versatile Concentric Control Feb.  
 Versatile Training Kit May  
 VTVM Kit Feb.  
 Weather-proof Driver Unit July  
 Wide-Band Oscilloscope Sept.  
 Yagi Antennas May  
 3-Inch CRT Feb.  
 3-Inch Speaker Oct.  
 7-Inch Oscilloscope Dec.  
 New 7-Inch 'Scope Nov.  
 10 MC Oscilloscope Dec.  
 14-Inch Rectangular Tube May  
 17-Inch Rectangular Tube July  
 17-Inch Rectangular Tube Oct.  
 New 19-Inch Tube Nov.

## SHOP NOTES

Admiral - Increasing Audio Output on "30" Series TV Chassis May  
 Admiral Models - Sync Buzz in Intercarrier Receivers Oct.  
 Aligning AC-DC Table Models Apr.  
 Belmont BRC18DX21A & 7DX21 - Dynamic Limiter Changes Jan.  
 Bending Tool for Band Switch Contacts Feb.  
 Checking Flyback Transformer June  
 Cleaning Volume Controls Sept.  
 Crosley Horizontal Sweep Sing- Models 10-401; 10-404; 10412; 10-418 Apr.  
 Crosley Models 10-412; 10-418; 10-404 MU; 10-404 MIU - Increase Vertical Size June  
 Damping Tube Trouble Symptom Feb.  
 Dial Cord Stringing Hook June  
 Difficult Bolt & Nut Replacement June  
 Discarded Penlight Carries Speaker Shims June  
 Electronic Growler May  
 Eyelash Curler Picks Up Fine Radio Wire Sept.  
 G.E. Hi-Channel Interference Trap Oct.  
 G.E. Models 12T3, 12T4, 12C107, 12C108, 12C109 - Filament circuit change - Increased horizontal sweep width - Removal of 41.25 mc video trap Dec.  
 G. E. Models 800 Series- Horizontal Sync Adjustment Apr.  
 Handy Test Lead Rack Jan.

# 1950 INDEX ★ RADIO-TV SERVICE DEALER

Heavy Soldering Apr.  
 Intermittent Operation with Microphones in RCA 8-R-71 Oct.  
 Jensen's New System of Rating Speakers Feb.  
 Motorola Model 5A5-Rectifier Lights Up with Switch Turned off Feb.  
 Philco-Intermittent High Volt. Supply Feb.  
 Philco Models 46-1203; 48-1262 -Distortion, Instability, Poor Sensitivity Jan.  
 Philco-Sweep Generator Attenuator Cir. Jan.  
 Philco 46-1203; 48-1262 - Simplified Circ. Feb.  
 Philco Models 48-1000-1001-1050-Correcting loss of a-g-c action. Dec.  
 Philco Model 49-702-Replacement of tuner. Dec.  
 Philco Models 49-1040 etc.- Changes in rating of B+ Protective Fuse June  
 Philco Universal Pix Tube Test Adapter May  
 Pilot Lamp Tool Jan.  
 Poor Brightness Control Oct.  
 RCA 8-R-71- Intermittent Oper. with Mikes Oct.  
 Replacing Bias Cells Apr.  
 Selenium Tester Jan.  
 Sentinel Models 400;401-405;406;411- Tearing and Picture Breakup Feb.  
 Sentinel Models 412; 413; 414; 415; - To improve Horiz. Hold Sept.  
 Sentinel Models- Schematics of Models 412; 413; 414; 415 referred to in Sept.  
 Starting "Stuck" Vibrators Jan.  
 Stromberg-Carlson Model TV125 and TC19-Improved Sig. to Noise Ratio at Sound Detect. for Better Audio Reprod. Nov.  
 Stromberg-Carlson Model TC19- High Voltage Connector Lead Nov.  
 Stromberg-Carlson- Noisy R-F Tuners Sept.  
 Stromberg-Carlson- Pads for connecting multiple TV-12's to one antenna. Dec.  
 Stromberg-Carlson TV Models- Horiz. Picture Instability Nov.  
 Sync Buzz Due to Misalignment Oct.  
 Tele-Tone TV Model 149-B-Fuzzy Picture on Weak Signal Jan.  
 Warm Air Device for Testing Defective Parts Feb.  
 Western Auto Model D2919-Instability & Distortion on FM Sept.  
 Westinghouse- Coupling Sweep & Marker Generators to Receivers Jan.  
 Westinghouse CRT Damage Caused by Incorrect Adjust. of Ion Trap Magnet Feb.  
 Westinghouse Model H-223-Perm. Magnet Type Focus Coil Nov.  
 Westinghouse Model H-223- 4.5 Mc Audio I-F Transformer Nov.  
 Westinghouse Model H-223-Picture Interfer. Nov.  
 Westinghouse Models H-198; H-199; H-203- Oscillation & Poor Sensitivity on FM Band Oct.  
 Westinghouse Model H-216-Picture Distort. Due to Magnetism Sept.  
 Westinghouse Models-Ratio Detect. Alignment May  
 Zenith Model 28-T925R-Repairs (Thick Horizontal Lines) Apr.

## SYNC PULSES (A Regular Department)

Color TV- Ha! Ha! Nov.  
 HoTelevision Sept.  
 Injunction Stops Immediate Color TV costs by Non-Compatible CBS Dec.  
 Installation Buying Controls Oct.  
 Licensing Again Threatened in N.Y.C. Dec.  
 Price Trends Oct.  
 Radiomakers Get Ultimatum Sept.  
 Shortages Oct.  
 Sounds-Too Personal Sept.  
 TV Censorship Negated Oct.  
 TV Microwaving Starts Oct.  
 TV Still Killing Laymen Sept.

## TELEVISION CIRCUITS

Admiral Model 19A1 (Circuit Court) Mar.  
 AFC for Local Oscillators, by Allan Lytel Mar.  
 Front Ends, Part 1 by S. L. Marshall June  
 Front Ends, Part 2, by S. L. Marshall July  
 Front Ends, Part 3, by S. L. Marshall Sept.  
 Front Ends, Part 4, by S. L. Marshall Oct.  
 Front Ends, Part 5, by S. L. Marshall Nov.  
 Front Ends, Part 6, by S. L. Marshall Dec.  
 High Voltage Circuit of National NC7V7 (Circuit Court) Apr.

Horizontal AFC Circuits, Part 1, by Walter H. Buchsbaum July  
 Horizontal AFC Circuits, Part 2, by Walter H. Buchsbaum Aug.  
 Horizontal AFC Circuits, Part 3, by Walter H. Buchsbaum Sept.  
 Improving Focus in TV Receivers, by Matthew Mandl Mar.  
 Kappler Model 102T June  
 Operation 6 Service of Keyed AGC Systems, by Matthew Mandl Dec.  
 Printed Circuit TV Tuner (RCA-Trade) Flashes) May  
 RCA's New TV Line Simplifies Servicing Aug.  
 Servicing Sync Separators, by Matthew Mandl Apr.  
 The Serviceman's TV Chassis Sept.  
 Theory & Practice of Video Detector Circuits, by H. A. Schwartz Aug.

## TELEVISION COMPONENTS

Attachable Shaft for Controls (New Prods.) Aug.  
 Capacitors for TV (New Prods.) Mar.  
 Ceramic Tubulars (New Prods.) Nov.  
 Components for TV (New Prods.) Jan.  
 Components for TV (New Prods.) Nov.  
 Concentric Control Assortment (New Prods.) June  
 Dual-Concentric Control (New Prods.) Oct.  
 Fuse Holder (New Prods.) June  
 Front Ends Sept.  
 Front Ends Oct.  
 Horizontal Transformer (New Prods.) Jan.  
 Isolation Transformer (New Prods.) July  
 Low R-F Impedance Electrolytics (New Prods.) Dec.  
 Miniature Metal-Cased Tubulars (New Prods.) Aug.  
 New Simplified RCA TV Chassis (Trade Flashes) Aug.  
 New Tuner (New Prods.) Oct.  
 Printed TV Tuner (RCA-Trade Flashes) May  
 RCA-16GP4 (New Prods.) Feb.  
 TV Components (New Prods.) July  
 TV Wave Traps (New Prods.) Nov.

## TEST EQUIPMENT

Capacity Bridge (New Prods.) Oct.  
 Combination Induct. Bridge June  
 Electronic Growler (Shop Notes) May  
 Electronic VOM (New Prods.) Mar.  
 Electronic VOM-Cap. Meter Mar.  
 Front Ends, No. 6, by S. L. Marshall Dec.  
 High Voltage Tester (New Prods.) Apr.  
 Imped. Bridge Kit (New Prods.) Jan.  
 Lab Type VOM (New Prods.) Jan.  
 Panel Instrument (New Prods.) May  
 Portable TV Service Lab. (New Prods.) Aug.  
 Philco Sweep Gen Attenuators (Shop Notes) Jan.  
 Plastic Test Prods (Shop Notes) Jan.  
 RCA High Volt. Probes (Trade Flashes) Mar.  
 Repairing Geiger Counters Feb.  
 Selenium Tester (Shop Notes) Jan.  
 Signal Generator Kit (New Prods.) Sept.  
 Sweep Generators (New Prods.) Nov.  
 The 'Scope As A Modern Service Tool Jan.  
 TV Marker Generator (New Prods.) Dec.  
 TV Sweep Generator (New Prods.) May  
 TV Sync-Sweep Tracing with Lightning Speed May  
 TV Signal Tracing with Lightning Speed Jan.  
 TV Test Equipment by G. E. (Trade Flashes) Feb.

Tube Checkers, by Wm. R. Wellman Jan.  
 Tube Testers (New Prods.) Mar.  
 Tube Testers (New Prods.) June  
 VTVM Kit (New Prods.) Feb.  
 Warm Air Device for Testing Defective Parts (Shop Notes) Feb.  
 Wide Band Oscilloscope (New Prods.) Sept.  
 5-Inch Oscilloscope (New Prods.) July  
 7-Inch 'Scope (New Prods.) June  
 7-Inch 'Scope (New Prods.) Nov.  
 7-Inch 'Scope (New Prods.) Dec.  
 10 MC Oscilloscope (New Prods.) Dec.

## TRADE LITERATURE & BOOKS

Aerovox General Catalog Oct.  
 Antenna Booklet by Ward July

Antennaplex Manual Apr.  
 Cone Catalog Mar.  
 Encyclopedia on CRO & Their Uses Oct.  
 Encyclopedia on CRO & their Uses Dec.  
 Filter Facts Oct.  
 "High Quality" Brochure Mar.  
 Hytron's New Reference Guide June  
 Mallory's 2nd TV Book Nov.  
 Microphone Catalog Aug.  
 New Antenna Book Nov.  
 New Catalog DC2S Oct.  
 New Catalog June  
 New Pocket Manual Nov.  
 New Radio Operator's Q & A Manual Feb.  
 New RCA Contract Plan Jan.  
 New RCA Receiver Tubes Booklet Sept.  
 New Rider Manual #20 Mar.  
 New TV Handbook May  
 New 1949 Electronic Index June  
 Philco TV Components Handbook Mar.  
 Radio Service Catalog 27 Centralab June  
 RCA Rec Tubes for AM, FM & TV BC Sept.  
 Rider's TV Manual Vol. 4 May  
 Rider's TV Manual Vol. 5 Oct.  
 Second Edition of the Radio and TV Industry Handbook, Dec.  
 Stancor TV Components Replace. Guide Feb.  
 Sylvania TV Tube Complement Book Mar.  
 TACO Antenna Bulletin Feb.  
 Tele-Clues June  
 Television Servicing by W. H. Buchsbaum Dec.  
 Time For Sound Talk Oct.  
 TV Replacement Guide Mar.  
 TV Installation Techniques Sept.  
 Voluntary "Fair Practice Code" Aug.  
 You Don't Have To Be A Recording Expert Sept.

## TUBES

### Cathode Ray


DuMont "Bent Gun" Oct.  
 DuMont "150" 17" Teletron July  
 DuMont 5BP1-A Nov.  
 DuMont 12LP4 June  
 DuMont 12LPA4 June  
 G.E. 3MP1 Feb.  
 G.E. 14CP4 May  
 G.E.16KP4 Apr.  
 G.E. 19AP4A Apr.  
 Know The Cathode Ray Tube, Part 1, by Allan Lytel Oct.  
 Know The Cathode Ray Tube, Part 2, by Allan Lytel Nov.  
 Picture Tube Size & Shapes (I Told You So) May  
 Sylvania TV Tube Complement Book Mar.  
 Small TV Tubes Passé (Editorial) May  
 TV Picture Tube Chart Mar.  
 National Union 16CP4 June  
 National Union 16KP4 June  
 National Union 16TP4 June  
 Raytheon 16LP4 Jan.  
 RCA 16GP4 Mar.  
 RCA 19AP4-B Nov.  
 5SP11 Nov.  
 7GP1 Nov.  
 7JP4 Oct.  
 12LP4 Oct.

### Receiving

G.E. 6AH6 July  
 G.E. 6S4 July  
 Hytron's 4th Edit. Reference Guide for Miniatures June  
 Hytron 1X2A June  
 Hytron 1B3CT/8016 June  
 Hytron 12BH7 June  
 JFD Ballasts Oct.  
 RCA Receiving Tubes Booklet Sept.  
 RCA Receiving Tubes for AM, FM & TV Broadcast Sept.  
 RCA 5879 June  
 RCA 5915 Oct.  
 RCA 5963 Oct.  
 RCA 5964 Oct.  
 Sylvania 1L6 Jan.  
 Sylvania 3E5 Apr.  
 Sylvania 7X6 Jan.  
 Sylvania 1AF4 Apr.  
 Sylvania 1AF5 Apr.  
 Sylvania 6AD4 Feb.  
 Sylvania 6BA5 Feb.

Smart TV Dealers are

# HITTING THE TENNA-ROTOR JACK-POT!

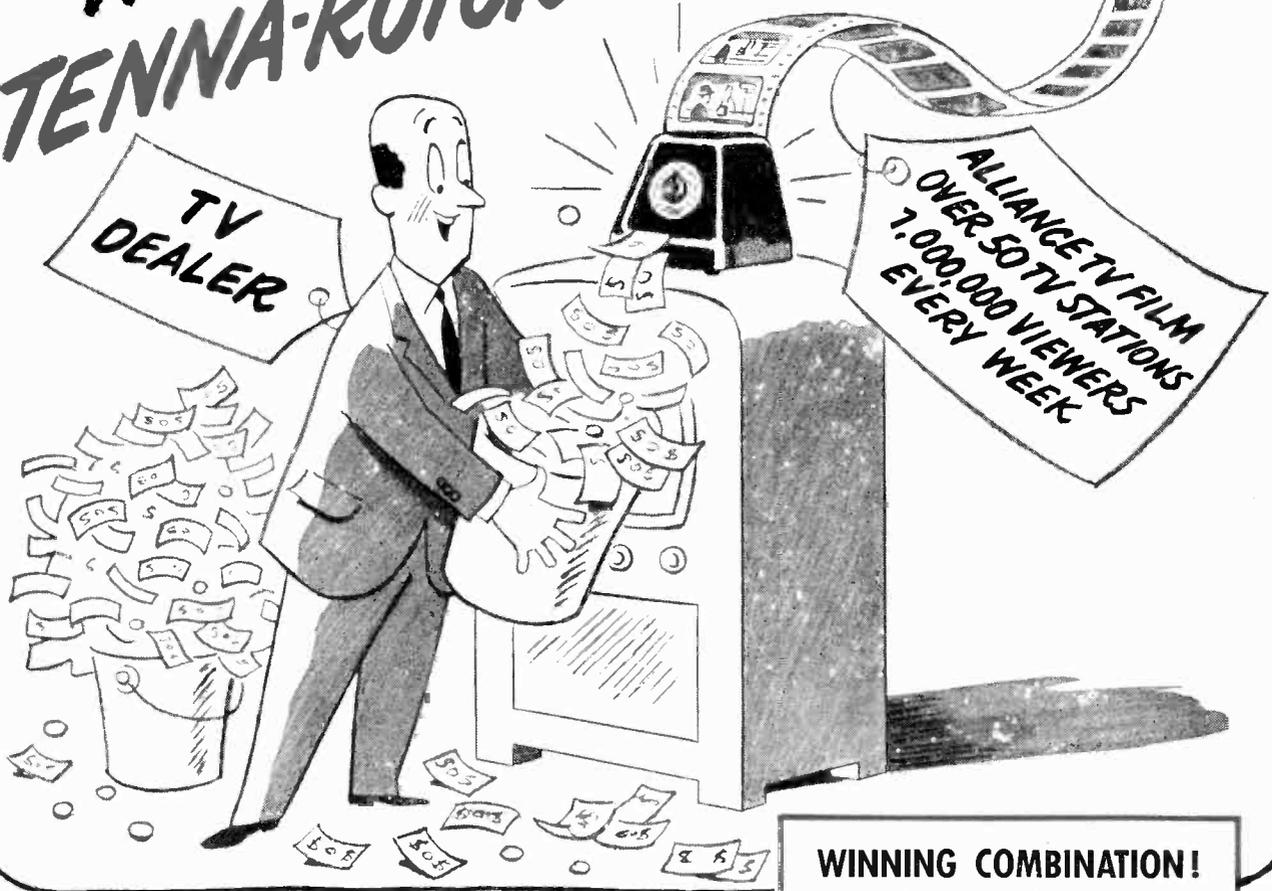

## PROOF IS IN RESULTS! *Nation-wide TV Advertising Delivers Thousands of Sales—Every Week!*

Over 50 key TV stations demonstrate Alliance Tenna-Rotor to 7 million viewers! Tenna-Rotor is the only TV accessory backed by a powerful, sustained television campaign—national in scope! Hundreds of thousands of Alliance Tenna-Rotors are in use!

Alliance Tenna-Rotor offers faster installation with Alliance 4-conductor "Zip" cable—Works in all weather—Guaranteed for one year—Approved by Underwriters' Laboratories.

**NEW DELUXE MODEL HIR IS FULLY AUTOMATIC!**

## WINNING COMBINATION! *Just Set It and Forget It!*

The only fully automatic rotator. Set the painter-antenna turns to that point and stays! North—East—South—West—direction indicator dial shows exact antenna position at all times. Extremely accurate!



MODEL HIR TENNA-ROTOR

## ALLIANCE TENNA-SCOPE




—the New TV Booster! Features one simple control. Automatic on-off switch. Gives maximum uniform high gain on all channels—quick to install! An excellent companion item to Tenno-Rotor.

TENNA-SCOPE

**ALLIANCE MANUFACTURING COMPANY • Alliance, Ohio**

THE QUALITY OF RCA TUBES IS UNQUESTIONED

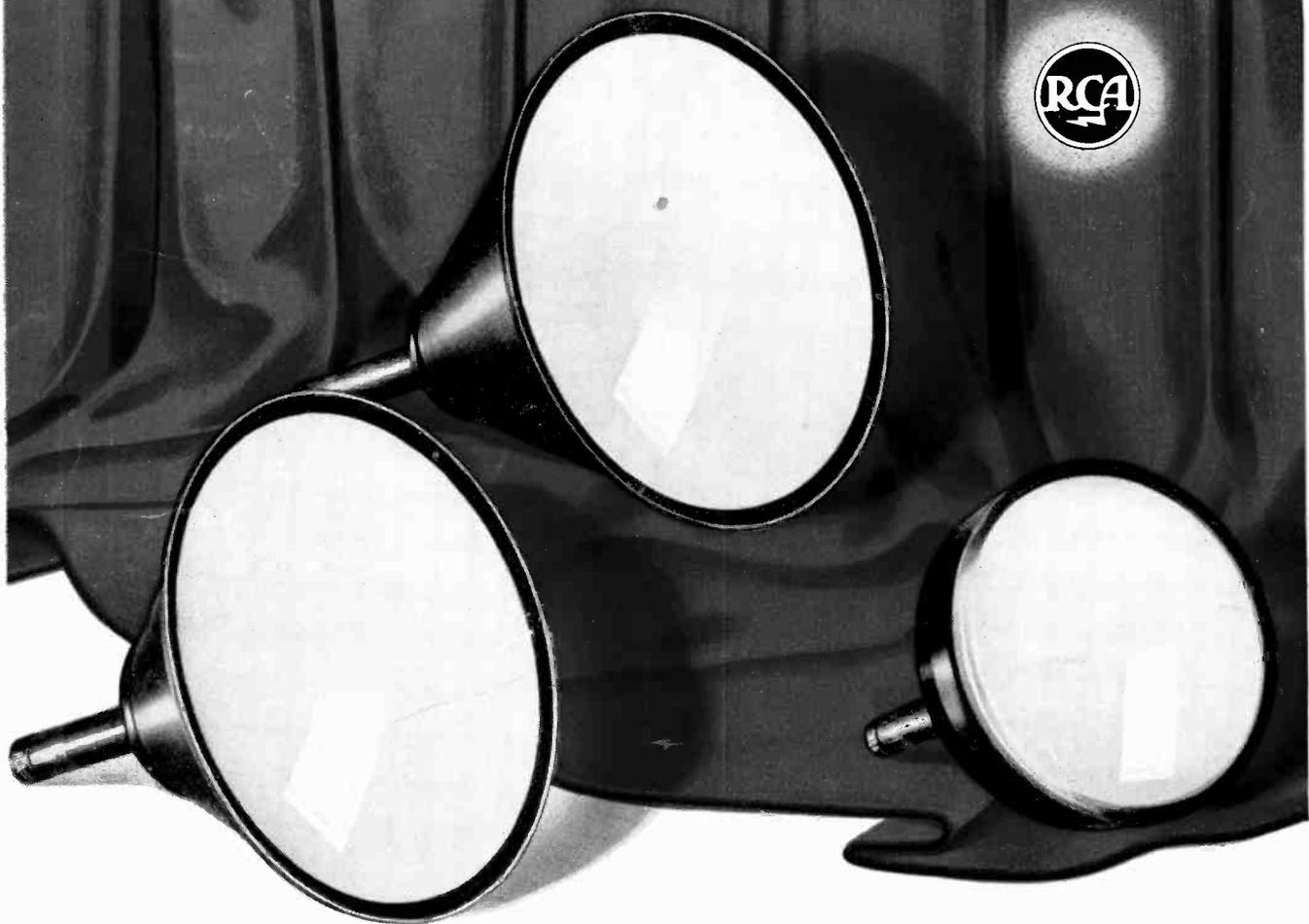

## *Best Sellers*

## **IN PICTURE TUBES...**

Most used . . . by brand  
and by type . . . RCA kinescopes  
are the fast-moving  
profit makers

*The* largest and most profitable replacement business in television picture tubes comes from the types used in most television receivers . . . the Best Sellers.

RCA's types are Best Sellers. There are more of them in actual use in TV receivers than any other brand. Industry choice of these high-volume types reflects to your advantage. Inventory and stocking problems are simplified . . . and you have the assurance of rapid, profitable turnover.

In addition, when you sell RCA kinescopes, you gain from customer confidence in the RCA brand . . . solidly established by the proved performance of RCA kinescopes in millions of television receivers.

Remember, too, that the quality and dependability of RCA kinescopes mean fewer service failures and fewer costly call-backs. There is, therefore, more profit in every RCA kinescope you sell.

*Always keep in touch with your RCA Tube Distributor*



**RADIO CORPORATION of AMERICA**  
ELECTRON TUBES

HARRISON, N. J.