

Page 21

SCHEDULES FOR HEARING EUROPE DURING THE INTERNATIONAL TESTS

JAN. 23

1926

15 CENTS

RADIO WORLD

Title Reg. U.S. Pat. Off.

Vol. 8. No. 18
200


ILLUSTRATED Every Week

THE 4-TUBE DX
ANTENNATROL SET

HOW TO HAVE
B BATTERIES
LAST 6 MONTHS

THE 4-TUBE DIAMOND

IN A HANDSOME
SETTING IN THE HOME

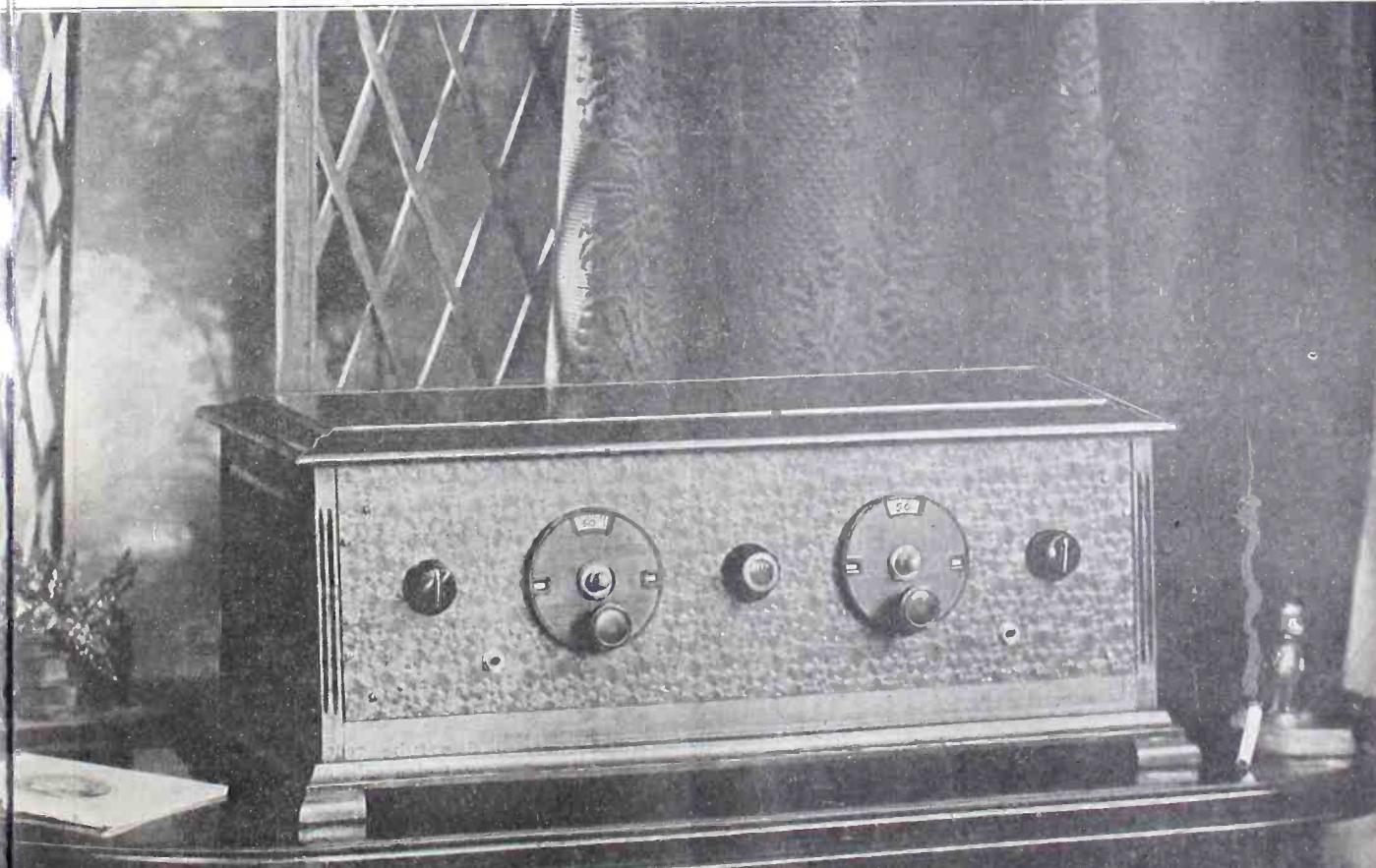

THE 4-TUBE DIAMOND. The tickler knob is at center. (See page 3)

It's Easy to Build A Powerful Set

*Using the New and Improved
FRESHMAN "TRF" Low Loss Kit*



Straight Line Wave Length Condensers With Low Loss Self Balanced Coils

These are the identical units which have made the FRESHMAN MASTERPIECE factory built receivers the World's Greatest Radio Sets

\$ 9⁵⁰

Complete instructions for building this powerful five tube receiver written in plain everyday English, together with actual size schematic wiring diagram are furnished with every FRESHMAN "TRF" Kit.

Sold by Authorized Freshman Dealers Only !

CHAS. FRESHMAN CO., INC.

Freshman Building, New York
2626 W. Washington Blvd., Chicago

RADIO WORLD

[Entered as second-class matter, March, 1922, at the post office at New York, N. Y., under the Act of March 3, 1879.]

A Weekly Paper Published by Hennessy Radio Publications Corporation from Publication Office, 145 West 45th St., New York, N. Y. Just East of Broadway Phones: BRYant 0558 and 0559.

Vol. VIII. No. 18. Whole No. 200

January 23, 1926

15c per copy, \$6.00 a year

The 4-Tube Diamond Set

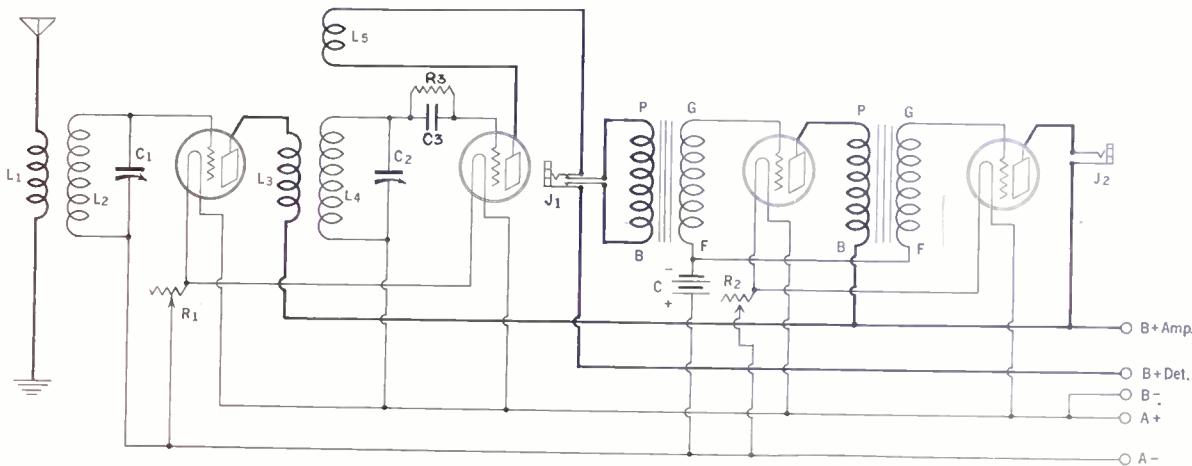


FIG. 1, the wiring diagram of the 4-tube Diamond of the Air. The two rheostats may be replaced by No. 112 Amperites, if —01A tubes are used, in which case two switches should be added, one between A battery plus and the A plus lead that goes to the set, the other between the A plus lead in the set and the F plus posts of the two audio sockets.

By Herman Bernard

Associate, Institute of Radio Engineers

WHILE the 1926 Model Diamond of the Air, employing five tubes, is the reigning favorite with RADIO WORLD readers, quite a few desire to use the 4-tube model, along the lines of the series published last April. The only substantial difference between the two sets is that the 1926 model has an improved audio circuit, consisting of one stage of transformer coupling and two stages of resistance coupling. But no doubt many who have a pair of audio transformers, and who know they will get just as much volume from them, even if the quality is not perhaps so good, want to build the set on the 4-tube basis. Therefore, this article will deal with the circuit substantially as published last April, including rheostats, which were omitted from the 1926 Model and replaced by Amperites. This substitution, which does away with the necessity of tinkering with filament heating, may be applied to the 4-tube model by those who so desire.

On the radio side both models are the same and are equal in detector performance. There is a stage of tuned radio-frequency amplification and a regenerative detector, after which comes the audio. Instead of the RF transformer a loop may be used, or a jack, not shown in Fig. 1, but specially treated in Fig. 2, where it is designated LJ, may be included so that one may have the instantaneous option of loop or outdoor aerial operation. The loop terminals would be connected to a hard rubber jack-plug.

Loop Possibilities

This is a valuable option, since a loop picks up less noise than does an outdoor antenna, hence may be expected to render clearer reception when there is static in the air. Also, the loop has distance pos-

sibilities even on a 2-tube set (considering only the radio side) beyond the expectations of most persons who have had no experience with this pickup method. Moreover, persons living in apartment houses or who are confronted with other obstacles in the way of erecting an outdoor antenna will find that a loop satisfies them quite nicely. Moreover, the selectivity is a little higher with the loop used instead of the outdoor antenna, and this has its virtues for persons living near local stations that otherwise come in over a wide spread of the dial.

Designed for Selectivity

On the score of selectivity, however, it must not be assumed that it is merely meager when an outdoor antenna is employed. The circuit was so designed that even when the outdoor aerial is used the selectivity is all that it dare be without impairing quality. Most fans are familiar with the effect of excessive selectivity upon the quality of the signal, due to the side bands, the resultant modulation of the audio frequencies upon the carrier wave being attenuated or cut off. The great degree of selectivity obtained from the Diamond is due mostly to the coil characteristics, whereby the antenna primary is comparatively loosely coupled to the secondary, by virtue of the number of turns and the distance between primary and secondary; and due also to the similar condition of the primary of the interstage coupler, L3L4L5.

Solenoid Coils Used

The solenoid coils have been used in the Diamond in both models because these are convenient to handle or wind, and are efficient. Other coils also are efficient, and it is not the form of winding that constitutes the exclusive method of determination, hence other models may be employed as the constructor sees fit. It is easier to follow the constructional data,

however, by using the same type of coil and same diameter as specified by an author, and following the directions as to number of turns and spacing, the coupling effect is kept the same, which is one of the important concerns in respect to selectivity.


Use .0005 Mfd. Condensers

As for the inductance, that will depend on the capacity of the tuning condensers used. The .0005 mfd. value is recommended, especially as this facilitates tuning both wavelength controls in step, an item attractive to many fans. If straight-line frequency condensers are used a few more turns should be added, as compared with semi-circular plate condensers. Of course, this would be due to the straight-line frequency condenser not having as high a maximum capacity as the semi-circular plate condenser with which it is compared. But the straight-line frequency condenser normally will have a very low minimum capacity, and there is no danger of failing to tune in the wavelength band. Assuming that band to be from 200 to 550 meters (although its range is not quite so large in fact), a straight-line frequency condenser, with proper coil, will enable you to tune from 175 to 560 meters. As straight-line frequency tuning is very popular no doubt fans who possess or buy semi-circular plate (straight-line capacity) condensers will like to enjoy the convenience of frequency tuning, which they may do simply by using straight-line frequency dials that make any condenser that is not SLF tune as if it were. This is accomplished by an automatically changing vernier arrangement which, in the more skillful types, is smooth, noiseless and velvety, without backlash.

Filament Resistors

The rheostat question is bound to excite some. Granting that a set is properly

Many Use the Small Tubes

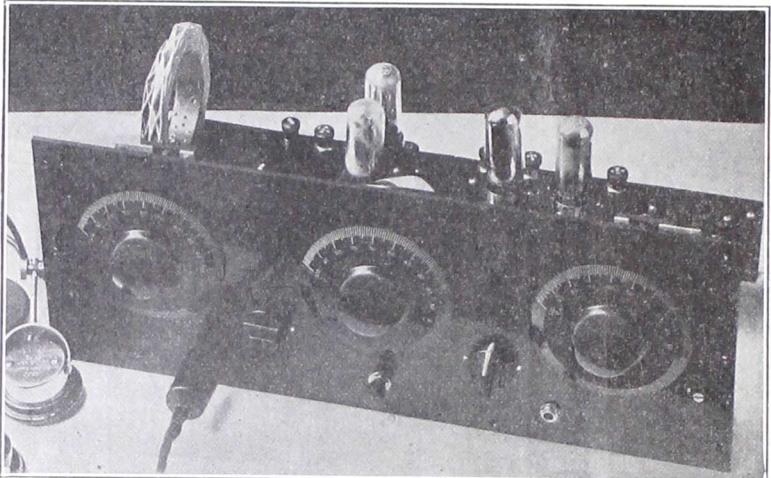


THE PANEL VIEW of the receiver built by E. W. Zimmermann. The plug is in the detector jack. This layout is based on substantially the same circuit wiring as shown in Fig. 1, except that above a switch is included and the RF tube has a rheostat of its own.

designed, without any uncontrolled critical point, there is no absolute need of a rheostat, because a certain type of tube should be heated at a certain temperature, or, as most commonly understood, the filament voltage should be a specified certainty. With the -91A tubes it is five volts, while with the -99 type of tubes it is $3\frac{1}{2}$ volts. The drop in voltage from the source of supply is accomplished either by a rheostat or by a ballast resistor. Constructors may suit themselves about this, but they may rest assured that the ballast suits nicely. It must be remembered, however, that many rheostats are shown in Fig. 1, and may be included with just as good results, the Amperites, if used, would necessitate two switches,

one to turn the set on and off as a unit, the other to turn off only the audio tubes. Thus the connection would be made in the master switch arrangement between the A battery lead where it enters the set, the lead being continued to the RF and detector socket F plus posts, while the branch to the F plus socket posts of the audio tubes would be through the second switch.

Tubes to Use

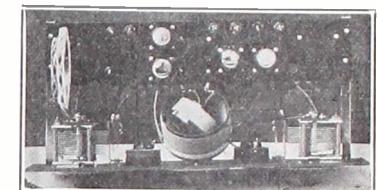If the -99 type of tube is used it is preferable to have an Amperite for each tube. If dry cell batteries are used these Amperites each would be 4v-199, or if a 6-volt storage battery is employed each Amperite would be a 6v-199. If a power



TOP VIEW of E. W. Zimmermann's receiver.

tube is used in the last stage with -99 tube outfit, then it should be the No. 120 Amperite, for the UVI20 tube, the source being a $4\frac{1}{2}$ -volt battery. If the source is 6 volts, then the No. 112 Amperite should be used and a large socket (standard size) employed or a UX socket. The 6-volt source storage battery power tube of the R.C.A. is the UX112, which will fit a standard base or the UX base, while the power tube equivalent to the -99 is the UX120, which needs a special base or adapter. The CX112 and the CX120 are of the same design and may be used instead. Also the general run of high-mu tubes may be used in the last stage, from a 6-volt source, without any rheostat or ballast in the filament circuit of the final tube.

The Coils for the Set

The solenoid having been used in the original model, it is advisable to adhere to that form of coil, which consists of a single layer on a cylindrical form. The cylinder happened to be one formed by quartzite rods, supported by Bakelite rings at either end. A small diameter is preferable, as it sets up a smaller field and there is less danger of magnetic interplay or stray coupling, which would result in difficulty in controlling oscillations. However, for the radio-frequency coil (L1L2) this diameter may be either $2\frac{1}{2}$ " or $3\frac{1}{4}$ " to duplicate the commercial coils employed, which were the Bruno 99 RF for the smaller diameter and the Bruno 55 for the larger (L1L2). In the case of the interstage coupler, or 3-circuit tuning coil, the smaller diameter is preferable, and this is the Bruno 99, a 3-circuit tuner (L3L4L5).

For the $2\frac{1}{2}$ " diameter form the primary consists of 10 turns, $\frac{3}{8}$ " space being left, then the secondary being wound adjacent to the primary and consisting of 53 turns. The wire is No. 24 silk over cotton or No. 24 double cotton covered.

The 3-circuit tuner is wound in the same fashion, as to the stator form, but inside this there revolves the rotary form, which is 1" diameter and 1" high, and on which are wound turns of No. 26 single silk covered wire until the wire almost completely covers the form, which will be about 38 turns.

If straight-line frequency condensers of .0005 mfd. rated capacity are used, instead of having 53-turn secondaries, have these turns number 57. This will bring in the highest receivable wavelength very near the full reading of the dial, but in the case of straight-line frequency condensers this is all right.

If the $3\frac{1}{4}$ " diameter form is used for the RF coil the primary would consist of 8 turns and the secondary of 45 turns, the same kind and insulation of wire being used. The tickler, $2\frac{3}{4}$ " diameter, has 28 turns of No. 26 SSC.

Basket-Weave Coil

Those desiring to wind basket-weave coils may use the same kind of wire, winding a primary of 6 turns and a secondary of 50 turns, the diameter being

How to Use a Loop Jack


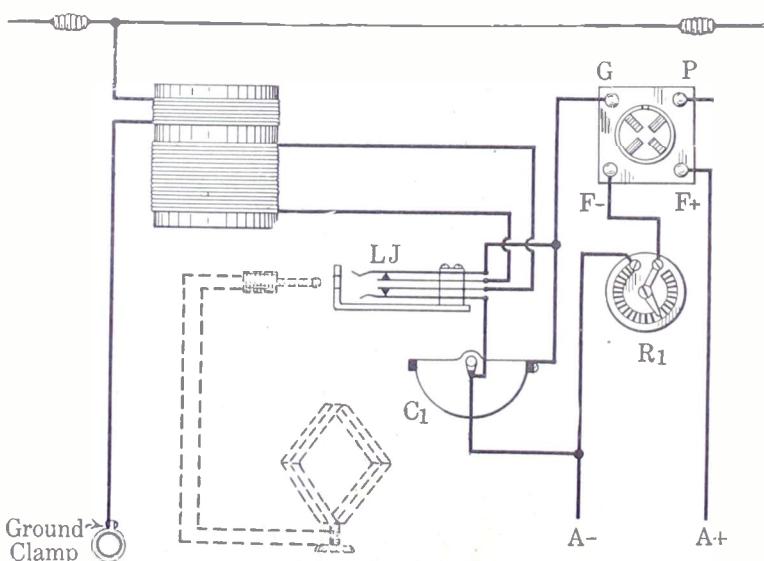


FIG. 2, showing how to include a loop jack, if the constructor desires to incorporate that method. There is no objection to the jack scheme, but see that you get a good plug, preferably one made of hard rubber instead of fiber, otherwise high losses due to resistance will be introduced in this part of the circuit. R1 is shown connected only to the RF tube. This is all right, but in that case connect R2 to the detector and also to both audio tubes.

Set Built in Glass Cabinet

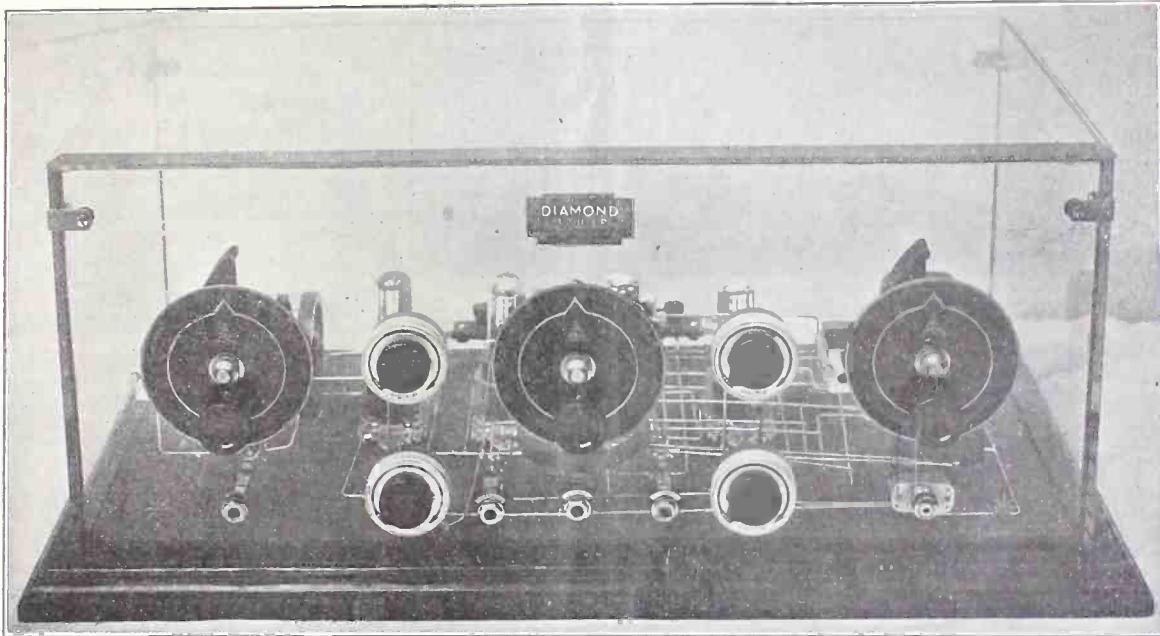

THE 4-TUBE DIAMOND as constructed by L. S. Byrd, of Fort Worth, Tex., in a plate glass cabinet. He used a rheostat for each tube and included a jack for loop, detector, first AF and second AF.

about $3\frac{1}{2}$ ". A circle of this diameter is described and nine equi-distant points located. The circle is thus divided into nine equal parts and the pins are placed in pairs, with diameters about $\frac{1}{8}$ " to left and right of the registered marks. There are 18 pins, i.e., 9 pairs. Wind over one proximate pair and under the next two. The primary winding will stay in place well if it is made near one end of the secondary. Wind a few turns, say 6, for part of the secondary, then pick up enough wire to enable you to continue winding the secondary, with the primary wound with and alongside of the continued secondary. Thus when the primary is completed you will have 12 turns of the secondary and will continue with the secondary for 38 turns more to a total of 50.

The tickler for a basket-weave coil would be wound on a $2\frac{1}{4}$ " diameter and would consist of 18 turns of the same kind of wire (No. 24).

Use of a Binder

As coil security and firmness are a problem with the basket-weave coil where No. 24 wire is used, collodion may be applied sparingly as a binder, and the coil left to dry before being removed from the form. The increased resistance due to this binder is very small and is not important enough to warrant discouragement of the use of collodion. A somewhat lower resistance results when a half-and-half solution of collodion and amyl-acetate is used.

For straight-line frequency condensers use a 54-turn secondary in each of the two cases—RF and 3-circuit coil—where the basket-weave type is employed.

The Spider-Web

A spider-web form would have an outside diameter of $5\frac{1}{2}$ " and a hub diameter of $1\frac{1}{2}$ ". Put on a 12-turn primary at the beginning, then leave a space of $1\frac{1}{8}$ " and wind the secondary, consisting of 47 turns, except that for SLF condensers it should be 51. Leave the spider-web coil on the form. A spider-web tickler

would consist of 16 turns, with the excess of the form cut away, if need be.

As for 4" diameter cylinder, this would require 6-turn primaries and 31-turn secondaries, except that for SLF condensers

put 35 turns on the secondary. The tickler would be on a $2\frac{1}{2}$ " diameter, 2" high and consist of 20 turns. No. 24 wire is used throughout.

For a 3" diameter tubing for the stat-

Diamond Results Delight Fans Who Build the Set

DIAMOND EDITOR:

I am sending photographs of my Diamond of the Air. As these photographs show I have departed slightly from the specifications.

The primary and secondary of the radio-frequency coil are wound on a 3" diameter. The three circuit tuning coil is 180-degree coupler, which is about $3\frac{1}{2}$ " in diameter. The two .0005 condensers are a fairly good make. The odd tube arrangement is due mostly to the position of the audio transformers which are underneath the sub-panel. The left-hand rheostat controls the radio-frequency tube while the right-hand rheostat controls the detector and the two stages of audio. The push-pull switch controls the last audio tube so that the phones may be used on strong stations. I do most of my listening with the phones, using only one stage of audio.

The set is built on a 7x18" panel and is 8" in depth.

I am more than pleased. Here is a log of two hours' listening:

WMBF, Miami, Fla.; WJZ, New York; CZE, Mexico City, Mexico; WTAM, Cleveland; KTHS, Hot Springs, Ark.; WLS, Chicago, Ill.; WJAZ, Chicago, Ill.; WSMB, New Orleans, La.; WGBS, New York; WPG, Atlantic City, N. J.; WGN, Chicago, Ill.; WSM, Nashville, Tenn.; WHBP, Johnstown, Pa.; WOK, Chicago, Ill.; WBBM, Chicago, Ill.; WEBH, Chicago, Ill.; WFAA, Dallas, Tex.; WRC, Washington, D. C.; WJJD, Chicago, Ill.; WSAI, Cincinnati, Ohio; 8BRC, (Ham) Someplace in Penn.; KFI, Los Angeles,

Cal.; KFKX, Hastings, Nebr.; KOA, Denver, Col.; WGHB, Clearwater, Fla.
E. W. ZIMMERMANN.
State College Station, Raleigh, N. C.

DIAMOND EDITOR:

I am enclosing a photograph of my Diamond of the Air, which I built in a plate glass cabinet.

I have been a reader of your magazine for more than a year, and am a subscriber to most of the leading radio magazines, but I find yours to be the best for the home constructor.

I have constructed the Superdyne and many other circuits published in your magazine but I find the Diamond of the Air to be the best. I am not much of a DX fan but I have logged 93 stations, not including the many amateur stations I have heard. All of these stations come in on a speaker with good volume. I am using tubes of the 199 type.

Space will not permit me to give you a list of the 93 stations but I will list just a few.


WEAF, New York; KFI, Los Angeles; KGO, Oakland; WLS, Chicago; KNX, Hollywood, Calif.; WCCO, St. Paul; KDKA, Pittsburgh.

Montreal, Canada, and Mexico City, of which I do not have the call letters, were logged.

The set is super-sensitive and selective; I am using the Bruno coils. Please accept my thanks for the circuit.

L. S. BYRD.
304 E. 15th St., Fort Worth, Texas.

Many Use the Small Tubes

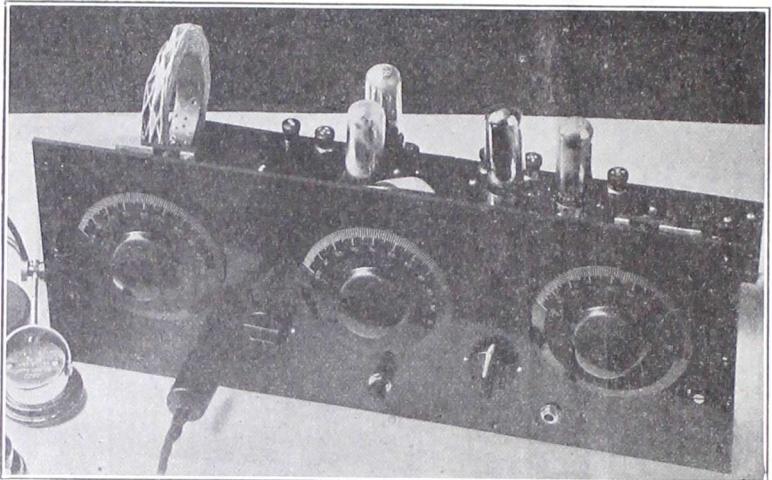


THE PANEL VIEW of the receiver built by E. W. Zimmermann. The plug is in the detector jack. This layout is based on substantially the same circuit wiring as shown in Fig. 1, except that above a switch is included and the RF tube has a rheostat of its own.

designed, without any uncontrolled critical point, there is no absolute need of a rheostat, because a certain type of tube should be heated at a certain temperature, or, as most commonly understood, the filament voltage should be a specified certainty. With the -91A tubes it is five volts, while with the -99 type of tubes it is $3\frac{1}{2}$ volts. The drop in voltage from the source of supply is accomplished either by a rheostat or by a ballast resistor. Constructors may suit themselves about this, but they may rest assured that the ballast suits nicely. It must be remembered, however, that while rheostats are shown in Fig. 1, and may be included with just as good results, the Amperites, if used, would necessitate two switches,

one to turn the set on and off as a unit, the other to turn off only the audio tubes. Thus the connection would be made in the master switch arrangement between the A battery lead where it enters the set, the lead being continued to the RF and detector socket F plus posts, while the branch to the F plus socket posts of the audio tubes would be through the second switch.

Tubes to Use

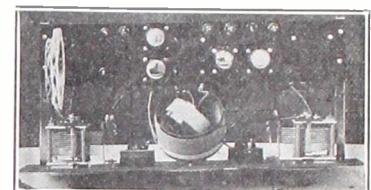If the -99 type of tube is used it is preferable to have an Amperite for each tube. If dry cell batteries are used these Amperites each would be 4v-199, or if a 6-volt storage battery is employed each Amperite would be a 6v-199. If a power



TOP VIEW of E. W. Zimmermann's receiver.

tube is used in the last stage with -99 tube outfit, then it should be the No. 120 Amperite, for the UVI20 tube, the source being a $4\frac{1}{2}$ -volt battery. If the source is 6 volts, then the No. 112 Amperite should be used and a large socket (standard size) employed or a UX socket. The 6-volt source storage battery power tube of the R.C.A. is the UX112, which will fit a standard base or the UX base, while the power tube equivalent to the -99 is the UX120, which needs a special base or adapter. The CX112 and the CX120 are of the same design and may be used instead. Also the general run of high-mu tubes may be used in the last stage, from a 6-volt source, without any rheostat or ballast in the filament circuit of the final tube.

The Coils for the Set

The solenoid having been used in the original model, it is advisable to adhere to that form of coil, which consists of a single layer on a cylindrical form. The cylinder happened to be one formed by quartzite rods, supported by Bakelite rings at either end. A small diameter is preferable, as it sets up a smaller field and there is less danger of magnetic interplay or stray coupling, which would result in difficulty in controlling oscillations. However, for the radio-frequency coil (L1L2) this diameter may be either $2\frac{1}{2}$ " or $3\frac{1}{4}$ " to duplicate the commercial coils employed, which were the Bruno 99 RF for the smaller diameter and the Bruno 55 for the larger (L1L2). In the case of the interstage coupler, or 3-circuit tuning coil, the smaller diameter is preferable, and this is the Bruno 99, a 3-circuit tuner (L3L4L5).

For the $2\frac{1}{2}$ " diameter form the primary consists of 10 turns, $\frac{3}{8}$ " space being left, then the secondary being wound adjacent to the primary and consisting of 53 turns. The wire is No. 24 silk over cotton or No. 24 double cotton covered.

The 3-circuit tuner is wound in the same fashion, as to the stator form, but inside this there revolves the rotary form, which is 1" diameter and 1" high, and on which are wound turns of No. 26 single silk covered wire until the wire almost completely covers the form, which will be about 38 turns.

If straight-line frequency condensers of .0005 mfd. rated capacity are used, instead of having 53-turn secondaries, have these turns number 57. This will bring in the highest receivable wavelength very near the full reading of the dial, but in the case of straight-line frequency condensers this is all right.

If the $3\frac{1}{4}$ " diameter form is used for the RF coil the primary would consist of 8 turns and the secondary of 45 turns, the same kind and insulation of wire being used. The tickler, $2\frac{3}{4}$ " diameter, has 28 turns of No. 26 SSC.

Basket-Weave Coil

Those desiring to wind basket-weave coils may use the same kind of wire, winding a primary of 6 turns and a secondary of 50 turns, the diameter being

How to Use a Loop Jack


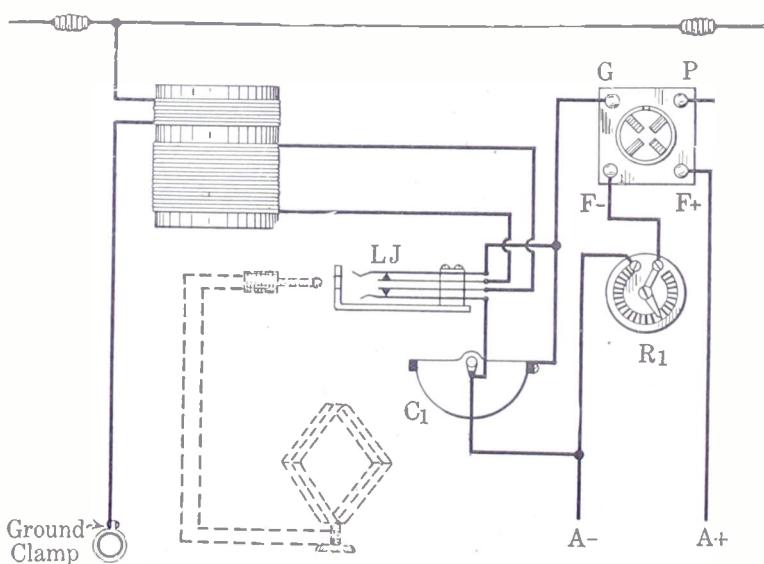


FIG. 2, showing how to include a loop jack, if the constructor desires to incorporate that method. There is no objection to the jack scheme, but see that you get a good plug, preferably one made of hard rubber instead of fiber, otherwise high losses due to resistance will be introduced in this part of the circuit. R1 is shown connected only to the RF tube. This is all right, but in that case connect R2 to the detector and also to both audio tubes.

Set Built in Glass Cabinet

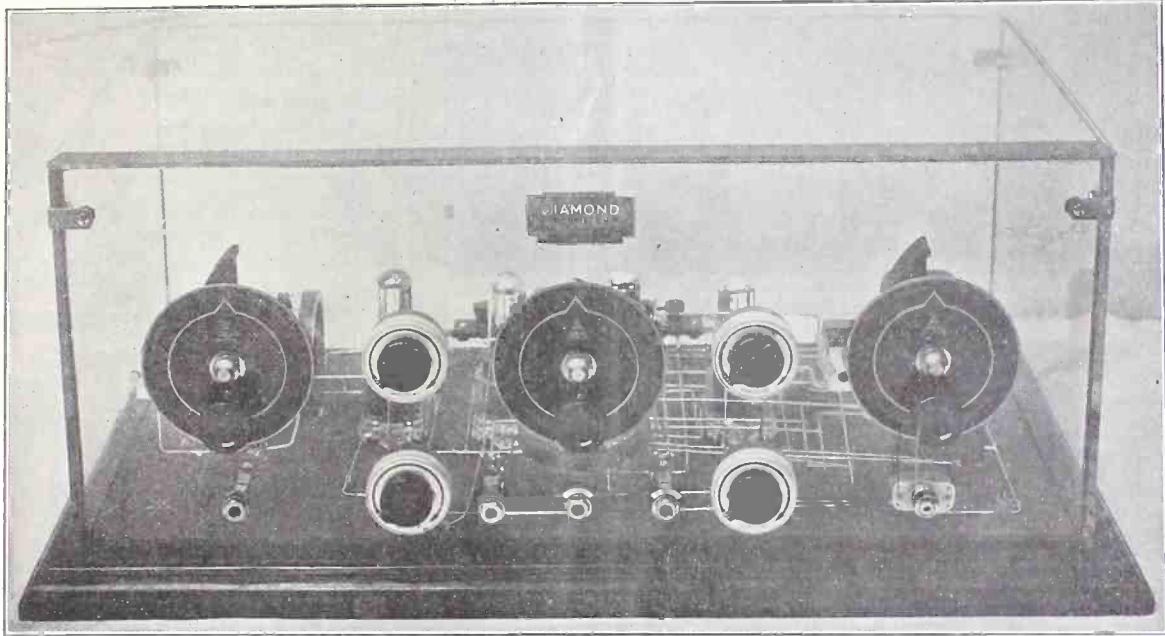

THE 4-TUBE DIAMOND as constructed by L. S. Byrd, of Fort Worth, Tex., in a plate glass cabinet. He used a rheostat for each tube and included a jack for loop, detector, first AF and second AF.

about $3\frac{1}{2}$ ". A circle of this diameter is described and nine equi-distant points located. The circle is thus divided into nine equal parts and the pins are placed in pairs, with diameters about $\frac{1}{4}$ " to left and right of the registered marks. There are 18 pins, i.e., 9 pairs. Wind over one proximate pair and under the next two. The primary winding will stay in place well if it is made near one end of the secondary. Wind a few turns, say 6, for part of the secondary, then pick up enough wire to enable you to continue winding the secondary, with the primary wound with and alongside of the continued secondary. Thus when the primary is completed you will have 12 turns of the secondary and will continue with the secondary for 38 turns more to a total of 50.

The tickler for a basket-weave coil would be wound on a $2\frac{3}{4}$ " diameter and would consist of 18 turns of the same kind of wire (No. 24).

Use of a Binder

As coil security and firmness are a problem with the basket-weave coil where No. 24 wire is used, collodion may be applied sparingly as a binder, and the coil left to dry before being removed from the form. The increased resistance due to this binder is very small and is not important enough to warrant discouragement of the use of collodion. A somewhat lower resistance results when a half-and-half solution of collodion and amylo-acetate is used.

For straight-line frequency condensers use a 54-turn secondary in each of the two cases—RF and 3-circuit coil—where the basket-weave type is employed.

The Spider-Web

A spider-web form would have an outside diameter of $5\frac{1}{2}$ " and a hub diameter of $1\frac{1}{2}$ ". Put on a 12-turn primary at the beginning, then leave a space of $1\frac{1}{4}$ " and wind the secondary, consisting of 47 turns, except that for SLF condensers it should be 51. Leave the spider-web coil on the form. A spider-web tickler

would consist of 16 turns, with the excess of the form cut away, if need be.

As for 4" diameter cylinder, this would require 6-turn primaries and 31-turn secondaries, except that for SLF condensers

put 35 turns on the secondary. The tickler would be on a $2\frac{1}{2}$ " diameter, 2" high and consist of 20 turns. No. 24 wire is used throughout.

For a 3" diameter tubing for the stat-

Diamond Results Delight Fans Who Build the Set

DIAMOND EDITOR:

I am sending photographs of my Diamond of the Air. As these photographs show I have departed slightly from the specifications.

The primary and secondary of the radio-frequency coil are wound on a 3" diameter. The three circuit tuning coil is 180-degree coupler, which is about $3\frac{1}{2}$ " in diameter. The two .0005 condensers are a fairly good make. The odd tube arrangement is due mostly to the position of the audio transformers which are underneath the sub-panel. The left-hand rheostat controls the radio-frequency tube while the right-hand rheostat controls the detector and the two stages of audio. The push-pull switch controls the last audio tube so that the phones may be used on strong stations. I do most of my listening with the phones, using only one stage of audio.

The set is built on a 7x18" panel and is 8" in depth.

I am more than pleased. Here is a log of two hours' listening:

WMBF, Miami, Fla.; WJZ, New York; CZE, Mexico City, Mexico; WTAM, Cleveland; KTHS, Hot Springs, Ark.; WLS, Chicago, Ill.; WJAZ, Chicago, Ill.; WSMB, New Orleans, La.; WGBS, New York; WPG, Atlantic City, N. J.; WGN, Chicago, Ill.; WSM, Nashville, Tenn.; WHBP, Johnstown, Pa.; WOK, Chicago, Ill.; WBBM, Chicago, Ill.; WEBH, Chicago, Ill.; WFIA, Dallas, Tex.; WRC, Washington, D. C.; WJJD, Chicago, Ill.; WSAI, Cincinnati, Ohio; 8BRC, (Ham) Someplace in Penn.; KFI, Los Angeles,

Cal.; KFKX, Hastings, Nebr.; KOA, Denver, Col.; WGHB, Clearwater, Fla.

E. W. ZIMMERMANN.

State College Station, Raleigh, N. C.

* * *

DIAMOND EDITOR:

I am enclosing a photograph of my Diamond of the Air, which I built in a plate glass cabinet.

I have been a reader of your magazine for more than a year, and am a subscriber to most of the leading radio magazines, but I find yours to be the best for the home constructor.

I have constructed the Superdyne and many other circuits published in your magazine but I find the Diamond of the Air to be the best. I am not much of a DX fan but I have logged 93 stations, not including the many amateur stations I have heard. All of these stations come in on a speaker with good volume. I am using tubes of the 199 type.

Space will not permit me to give you a list of the 93 stations but I will list just a few.


WEAF, New York; KFI, Los Angeles; KGO, Oakland; WLS, Chicago; KNX, Hollywood, Calif.; WCCO, St. Paul; KDKA, Pittsburgh.

Montreal, Canada, and Mexico City, of which I do not have the call letters, were logged.

The set is super-sensitive and selective; I am using the Bruno coils. Please accept my thanks for the circuit.

L. S. BYRD.
304 E. 15th St., Fort Worth, Texas.

Wiring Directions for Diamond

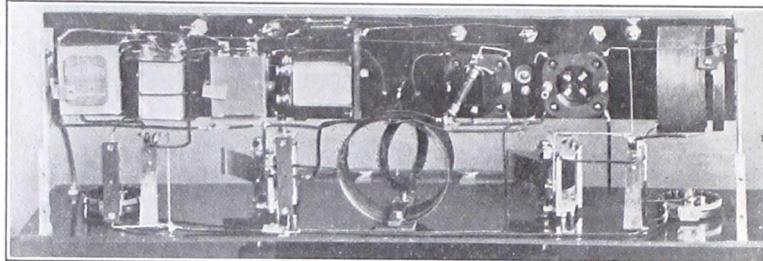

BOTTOM VIEW of the set the panel view of which is published on the front cover.

ors, wind secondaries with 3 more turns than specified for the $3\frac{1}{4}$ " diameter, tickler being the same. For $3\frac{1}{2}$ " diameter, wind 3 turns less on secondaries than for $3\frac{1}{4}$ ", the tickler being the same.

The Panel Layout

The panel for this circuit should be 7×21 ". A socket shelf, supported by brackets, makes a neat wiring job possible, or a baseboard may be used. The socket shelf should be $2\frac{1}{2} \times 20$ " and may be hard rubber or Bakelite. The sockets are mounted thereon, preferably through holes allowing the socket rims to be pushed up through the holes, and the sockets fastened to the strip from underneath. This precaution is advised because of the extra height of the UX tubes, in case such are used, for otherwise the lid of the cabinet might come down on the top of the tubes with costly effect. With a regular baseboard, either wood or hard rubber, this precaution is not necessary, if the supporting brackets, if any, are placed as usual, about $\frac{1}{2}$ " from the above what will be the bottom of the inside of the cabinet. That is the same plane represented by the bottom of the panel.

The photographs of sets others have built will give the proposed constructor an idea of what he may do. The tickler does not require a dial, but, as in one case, a knob may be used. The dial centers may be equi-spaced $3\frac{1}{2}$ " up, which is the center line of the panel, and the two rheostats placed below and between dials 1 and 2 and 2 and 3. Then the detector jack would be at extreme left, on a line with the rheostats, and the speaker jack at extreme right. If a variable leak is used mount the dials $4\frac{1}{2}$ " up, so that the leak may be placed under the central dial (which actuates the tickler).

Mount the panel instruments before wiring. Then wire the filament circuit without panel attached to subpanel. Then do the attaching and wire the set to completion.

Wiring Directions

Connect the filaments first. Following Fig. 1, A plus goes from battery direct to the F plus posts of all four sockets. A minus goes to one side of each of the two rheostats. The open side of R1, the first rheostat, goes to the F minus posts of both the RF and the detector sockets, which sockets appear in that order from left to right in Fig. 1. The open end of R2 goes to the audio socket F+ posts. That completes the filament wiring.

The aerial goes to the beginning of the aperiodic primary, L1. If the coil is standing on a table with primary on top, the beginning is the uppermost lead from the primary, although in the Bruno coils it is fastened to a binding post at the bottom ring, due to the wire being brought through the core for security. The ground goes to the other primary terminal. Thus L1 is disposed of.

Connect that terminal of the winding

L2 which adjoins the primary L1 to the A minus lead and to the rotor of the variable condenser, C1. Thus the ground, in the primary, and the A minus, in the secondary, will be adjoining connections. The other secondary terminal goes to the grid of the RF tube and to the stator plates of C1.

The beginning of the primary of the 3-circuit tuner, L3, goes to plate of the RF tube, the end of that winding to B plus amplifier, normally 90 volts. The secondary is connected in the same fashion as was L2, with the A battery connected to the secondary terminal that adjoins the low potential of the primary, that is, B plus and A plus connections adjoin. Of course these are not connected together. Take note that the A battery end of this secondary goes to A plus, while the RF return was to A minus. Be sure to follow these directions in this respect. The unconnected terminal of the secondary L4 goes to one side of the grid condenser, C3. The other side of this grid condenser is connected to the grid post of the detector socket. The grid leak is placed across the grid condenser, which normally will have mounting clips for that purpose. A variable grid leak, if used, should be on the panel.

The tickler, L5, is connected with plate of the detector tube to one terminal of the tickler and while the other lead goes to B plus detector voltage, normally $22\frac{1}{2}$ to 45. Later reverse tickler connections if regeneration is not obtained throughout the entire broadcast band. The tickler connection to battery is made through a double-circuit jack, hence wire the battery end of the tickler so that it connects to the outside hooked spring of this jack, J1. The frame or right angle of the jack, represented in many types of jacks by an adjoining hooked spring internally connected to the frame, is connected to B plus. Hence if you plug in phones at this point the B plus voltage is obtained through the phones. The inside springs of the jack are so connected that the one that contacts with the B plus or jack frame lead goes to the B plus or P2 post of the first audio transformer, marked B in Fig. 1. The other inside prong goes to the P post, sometimes marked P1 on some transformers. G of the first audio transformer is connected to the G post of the first audio socket, this representing the grid.

The plate of this tube is joined to the P post of the second audio transformer, while B of this AFT goes to B plus amplifier voltage. This is the same lead that went to the end of L3. G of the second AFT is joined to the grid post of the final socket and the plate of the last tube goes to the spring of the single-circuit jack J2, the frame of this jack being connected to B plus amplifier voltage.

Two connections not yet considered are the F posts of the two audio transformers. These are marked Neg. Fil. on some trans-

formers, or S2. The F posts of these two transformers are joined together and connected to C minus, usually $4\frac{1}{2}$ volts, while C plus is connected to A minus. Use flexible leads for these two C battery connections.

That completes the wiring.

Trouble Shooting

Suppose the set is built and you do not receive any signals. This probably will be due to one or more of the following causes:

- (1) A broken connection in the receiver.
- (2) A break in the aerial system.
- (3) One or more tubes being dead.
- (4) Failure to connect wires properly.
- (5) Over-oscillation.

The hookup as shown in Fig. 1 is correct and if the wiring directions are followed, and all the parts, tubes and connections correct, you cannot fail to hear signals, if any are within range. Therefore, lacking them, inspect the receiver for broken connections. These will be easy to find if in any part of the actual wiring that you performed, but if in an audio transformer, for instance, the location of the trouble will not be so easy. Once in a while a primary or a secondary of an audio transformer will burn out or become broken through mishandling, although in my personal experience this never has happened. Use a small dry cell and a pair of phones to test for broken connections at any point, including audio transformers. One phone cord and one battery post go to the test circuit. A sharp click discloses that the connection is all right. In the case of the audio transformer, however, the secondary will click with considerably less perceptibility than will the primary, due to the many more turns of wire on the secondary introducing extra resistance. Also, condensers will give a faint click, even when not shorted, due to charge and discharge, but you will have no difficulty in distinguishing these three points, for the condenser short will show up with abundant certainty and your ear will readily learn to be correctly guided.

A break in the aerial system is best located by the eye. Perhaps the lead-in is not connected to the aerial, or the aerial has fallen and is shorted with the ground, or the ground clamp connection is loose or broken.

Testing the Tubes

The tube test is first performed by changing tubes about. Also you may borrow tubes from a neighbor if need be. If a detector jack is included, as in Fig. 1, it is easy to test tubes to determine whether they are all right, and at the same time find out whether the radio or the audio side is causing the failure of signals to come through. Thus, if you plug in at the detector output and hear nothing, you may take one of the tubes from the audio side and put it in the detector socket. If still no signals are heard, put the other erstwhile audio tube in the RF socket. Thus combinations can be tried out and the result will be that you will hear signals, disclosing which tube or tubes are at fault, or you still will hear nothing, in which case the likelihood will be that you are not suffering from tube trouble. At any rate, you still may borrow a neighbor's tubes and convince yourself. If no signals are heard under any conditions, check up on the wiring up to the audio input, since the trouble has now been confined to the radio side, unless an undisclosed trouble

(Continued on page 28)

The Antennatrol—

*or, Setting the Trap
to Catch DX Signals*

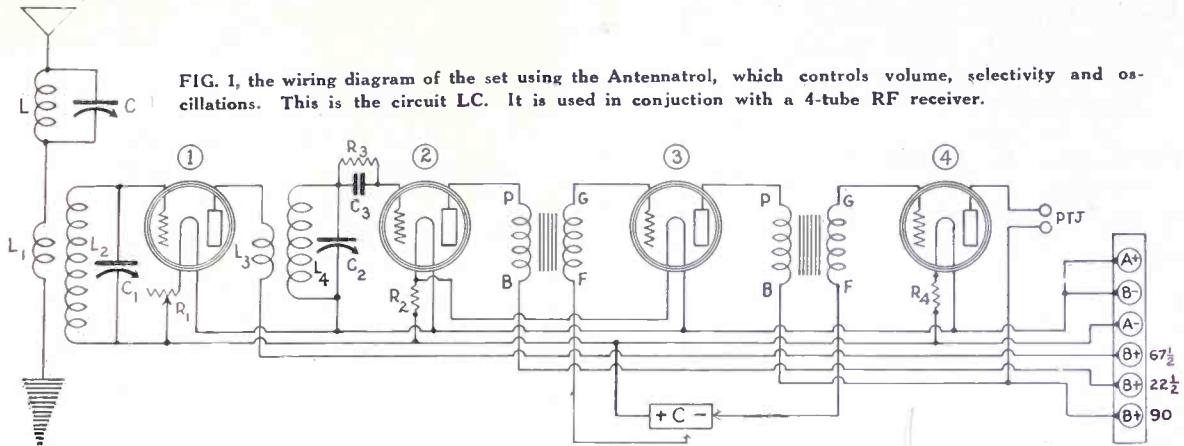


FIG. 1, the wiring diagram of the set using the Antennatrol, which controls volume, selectivity and oscillations. This is the circuit LC. It is used in conjunction with a 4-tube RF receiver.

By Herbert E. Hayden

YOU gain a decided advantage when you tone the aerial, because the whole antenna system is thereby established at a point of highest efficiency for the reception of the desired signals. The reason for the decline in popularity of antenna-tuned systems is not that they are inefficient but because they require an extra control and also because, under most methods of applying this advantage, the tuning of the aerial affects the setting of the condenser across the secondary circuit. As for the extra control, it is of course true that the antenna must have an independent control if it is to be tuned, but the advantage gained is well worth this addition. As for causing the condenser across the secondary to lose its characteristic of "loggability," I avoid this by hooking up the tuned aerial circuit as shown in Fig. 1. In other words, the "untuned" primary, L₁, is retained in all its pristine virtue, and thereby the condenser C₁ has fixed settings for given wave lengths or frequencies, and the detuning argument is fully met.

The Tuned Untuned Coil

L₁ is referred to as untuned because it is the conventional small winding, but it is in effect tuned, because the combination L and C in the antenna circuit is of the acceptor type, hence it favors the desired wave length and causes greater energy transfer for the selected frequency. In that manner the emf communicated to L₁ is maximum for the wave length to which the antenna is tuned, which differs entirely from the conventional untuned primary method, where the coupling is best for some particular frequency, and as well as it can be under the circumstances for all other frequencies.

The L and C combination function as an acceptor wave trap, as distinguished from a rejector circuit, which would exist were L a small winding, connected as shown, while across the condenser C, and in inductive relationship to L, were a large winding of the usual secondary proportions. The difference is that the rejector aids selectivity by absorbing the energy at any given frequency in its range to prevent the energy from being a source of interference to the set which is tuned to a different wave length. But

LIST OF PARTS

- Three Hammarlund low-loss .000375 mfd. straight-line frequency condensers, C, C₁, C₂.
- Three Hammarlund radio-frequency coils, L, L₁L₂, L₃L₄.
- One 20-ohm rheostat, R₁.
- Two No. 112 Amperites, R₂, R₄.
- Four Air-Gap sockets.
- Two Modern Symphony audio transformers.
- One 7x24" panel.
- One 7x23" baseboard, or a 23 1/2x23" socket strip with brackets.
- Two 4" Bruno "Slo-Moshen" Vernier dials.
- One knob, to match rheostat knob, and to be used on C.
- One .00025 mfd. Dubilier fixed grid condenser, C₃.
- One 2-megohm Amsco grid gate, R₃.
- One pair of Na-ald phone tip jacks, PTJ.
- One A battery switch (at broken A plus connection).

L and C in Fig. 1 are tuned to the same wave length as the rest of the circuit.

Effect on Selectivity

Let us see what effect the LC method of Fig. 1, which may be incorporated as a separate unit added to any set that has an untuned primary, has upon selectivity. On strong signals, that is, local stations that ordinarily come with excessive volume, the apparent effect is a loss of selectivity, but this is merely inferential, not actual. In everyday practice selectivity is gauged in respect to volume, so that one measures by a squint at the dial what stretch of that indicators' surface permits the signal to come through. The real test of selectivity is made of course under different conditions, and where the input is uniform. Hence by the everyday method the LC system in some cases seems less selective, but only because the antenna tuning system causes ever so much more energy to be delivered to the receiver, that is, increases volume. When an originally excessively strong station is subjected to further volume amplification, the seeming reduction in selectivity results. In fact it is a case of the volume going up, not the selectivity going down. The system either

adds to selectivity or detracts from it, but it can not do both, therefore let us see whether it adds at all.

Two Tests

The diagram as shown in Fig. 1 was used without the LC system incorporated, and volume was good and so was the reception of distant stations. But the moment the tuned antenna system was included, hereby following Fig. 1 exactly, the volume was increased on all stations, while distant reception was more readily obtained, and stations not otherwise heard were brought in. Moreover, where a faint signal was picked up its volume was brought up to an enjoyably audible point by tuning the LC circuit. Even at the middle and upper parts of the dial that actuated C, stations could be tuned out by a degree or so of the dial, and the selectivity peak was considerably sharpened.

Therefore any one who lives very close to a powerful broadcaster may incorporate a switch which will short-circuit L and C, thus cutting them out of the circuit, and leaving the set of the orthodox type for those special requirements.

A word about the inductive value of L. This will depend upon the capacity of C and of the antenna system. What C is you will know quite readily, for the capacity is stamped on the condenser you buy, or on the box that contains it. The Hammarlund low-loss straight-line frequency condensers and low-loss coils were used all through this circuit and proved most gratifyingly efficient.

The Hammarlund condensers were .000375 and the coils were the radio-frequency transformers that have a neutralizing tap. This enables you to employ the coil with safety, since if the number of turns is insufficient when the condenser C is connected across the secondary alone, added turns may be obtained simply by connecting the small primary winding that is inside the coil in series aiding with the secondary winding, and connecting one end of the primary and one end of the secondary to the respective condenser lines. And if the inductance of the secondary proves too much, you may connect the condenser to the neutralization tap on the coil.

(Part II, the conclusions of this article be published in the January 30 issue of RADIO WORLD, out next week).

B Batteries Last Six Months!

Right Choice Results in Substantial Economies — Tips on How to Gain That End

By Sidney E. Finkelstein

Associate, Institute Radio Engineers

THE life of a B battery can not be foretold in any statement which would apply to every case, but it is perhaps surprising to thousands of B battery users that in many instances a block of B batteries will last six months. In fact, by proper choice and use, it will.

This means six months of efficient service, not merely half-tolerable operation. Recent tests made over long periods showed that, if the proper batteries are used, great economy results. But one must know what to choose.

The Test by Ear

A B battery, or a set of such batteries, is good up to the point where unsatisfactory reception results, due to the impoverished condition of the battery. Therefore, as volume and other considerations enter into this, and as personal taste and preference will be a factor, for the satisfaction of some persons a B battery will last longer than for the satisfaction of others. But a general average, struck after receiving reports from many users of B batteries, showed that 22½-volt batteries were considered still useful after their voltage reading had dropped below 17, and in the case of 45-volt batteries, had gone below 34. This voltage drop was due to use and the voltages given are the "cut-off" voltages. A good way of considering these voltages—17 and 34—is to take for granted that the B battery is not at fault, though reception ceases to be up to snuff, if the voltage readings of a good make of B battery are above the figures cited. The cut-off voltages are not conclusive proof of the battery's deterioration below the point of usefulness.

The Miracle of Difference

Many persons have noted that the same battery will give different voltage readings on different instruments. For instance, when you buy a B battery in a reliable radio store you may see the salesman test the voltage with a rather large round instrument that has a needle indicator which moves on a scale when the terminals are connected to a source of voltage. This is a high resistance voltmeter and is the right kind to use in testing the voltage of a B battery. But if a test is made on a small voltmeter, of the vestpocket variety, the voltage reading sometimes may be the same as under the previously mentioned conditions, but most likely the voltage reading will be lower than the previous one. This is due to the pocket voltmeter having a low resistance, causing the consumption of an excessive amount of current when the battery is tested.

The Gobbling Meter

In one instance a pocket voltmeter with a 0-to-45 scale, actually drew 74 milliamperes while used for testing. The tubes in the set in which the B batteries were used of course were not lighted, nor should they be when B battery voltage is gauged, for then the reading may be still lower, hence failing to show the actual condition of the B batteries. The set, which had six tubes, itself drew only 19 milliamperes B battery current when in full operation

on strong signals. Hence the meter drew nearly three times as much current as the set. Such a frightful drain on the B battery, even for a few seconds, may prove costly, especially if repeated, as it is virtually a form of short-circuiting the B battery, and such tactics soon ruin the condition of any battery.

Eveready's Advice

On this point, the National Carbon Company, makers of Eveready radio batteries, who have done more laboratory work on batteries than any other organization in the world, and who are the undisputed leaders in battery manufacture, give the following advice:

"If you wish to use a voltmeter to obtain accurate voltage readings from your B batteries, the meter should have a resistance of not less than 50 ohms per volt. This means that a voltmeter capable of reading up to 30 volts should have a resistance of not less than 1,500 ohms, or a meter reading up to 60 volts should have a resistance of not less than 3,000 ohms. Such a meter when connected to a B battery will draw from the B battery approximately the same amount of current as is taken by the average receiving set, and, therefore, the voltage which the battery actually delivers to the tubes in your set."

Some radio sets work better than others on low voltages of B battery, hence on some sets B batteries last longer than on others. The hookup has something to do with this, although the trend of receivers today is in the direction of efficient operation on voltages below the cut-off voltages. In reflex sets, due particularly to the method of coupling, the voltage has to be kept fairly high, hence such sets may be deemed to be less inexpensive on the B battery score than most others.

Your ear is as good a test as any as to whether you need new B batteries. As the B battery voltage goes down the signals become weaker. As long as the B battery contains useful energy the drop in voltage from day to day is so slight that it can not be noticed in its effect upon volume. But when the battery nears a state of exhaustion its voltage begins to decline with severity and the weakening of signals is quite noticeable.

Fixing Responsibility

One must not lay every ailment in the set to the B battery. Suppose your set has given good reception from distant stations. Suppose that this delightful service suddenly ends. While it is true that rundown B batteries will cause this, the reason may be in an entirely different direction, and it is unquestionable that many thousands of dollars are wasted each year by radioists who, when some trouble arises, throw away their good B batteries to buy new ones. Maybe the trouble disappears, but it would have done so anyway. Hence some precautions are necessary in the interest of economy.

If distant reception falls off or entirely disappears, or if volume on local stations is less, test your B batteries with a high-resistance voltmeter, if you have one, and find out whether the voltage reading is below that of the cut-off voltage. This is merely an indication. The meter may not be accurate, or the set may be capable of functioning efficiently even below the cutoff voltage, so make some more investigations.

Inspect the A Battery

It is well-known that the same symptoms of lessened volume and decreased reception range attend a rundown condition of the A battery. This may be a

Mistakes Many Make in Attempting to Read Voltages, and in Discarding Good Batteries, Are Revealed

storage battery or a block of dry cells. If a storage battery, test with a hydrometer. No storage battery should be permitted to go below a condition of one-quarter charge and wise radioists operate the storage A battery above the half-charge point, as this is a cheap form of insurance where you have a charger at home. If dry cells are used as the A battery, and you have not a suitable voltmeter, then let the brilliance of the filament heating be your guide. If the brilliance is less than usual for a given rheostat setting, or if it does not increase perceptibly as you turn the rheostat, the dry cell A battery is exhausted. In fact, this test applies to the storage A battery as well.

Enter the Mystery

Do not jump at conclusions, even though tests up to this point may show that the A battery is not at fault. Remember that there are mysterious influences at work in radio, just as in the melodramas, and that poor reception may be due to these. Temporary conditions of shielding, repair operations by lighting or water companies or trolley lines, or unknown causes, as yet unfathomed even by the best minds in radio, may be causing the trouble. Also remember that electrical storms play havoc with distant reception. Fog, rain, sleet or snow may cover your antenna and cause the radio signals entirely or partly to run direct to ground, instead of making entry from your antenna to your set. Even though, from looking out of the window, you note no change in weather, as compared with a previous hour when reception was good, the change may have occurred miles away, or atmospheric conditions, which your senses can not detect, may be different now than they were then.

And then the tubes! How long have you been using them? Many types of tubes are past the useful stage long before their filaments cease to light. Their days end when certain active materials in their composition become exhausted.

Finally, find out what kind of reception some of your neighbors are getting. If they are experiencing trouble, too, you must assume that your set is not to blame, neither your tubes, your antenna, your A battery or your B battery. The untoward conditions are beyond anybody's control and they will pass away. So bide your time.

Another condition often blamed on B batteries, although they are innocent, is the increase and decrease of signal intensity from distant stations, or some weak local stations in rare cases, and accompanied sometimes even by the total disappearance of the signals for spasmodic periods. This is "fading" and is an electrical phenomena wholly dissociated from battery considerations.

With these points in mind, and this advice respected, it is unlikely that you will discard your B batteries too soon.

What B Batteries to Buy

Especially as power tubes are increasingly used, and require higher voltage for best results, it is always safe to purchase three 45-volt B batteries for 3-tube sets,

(Concluded on page 25)

A Study of Battery Types

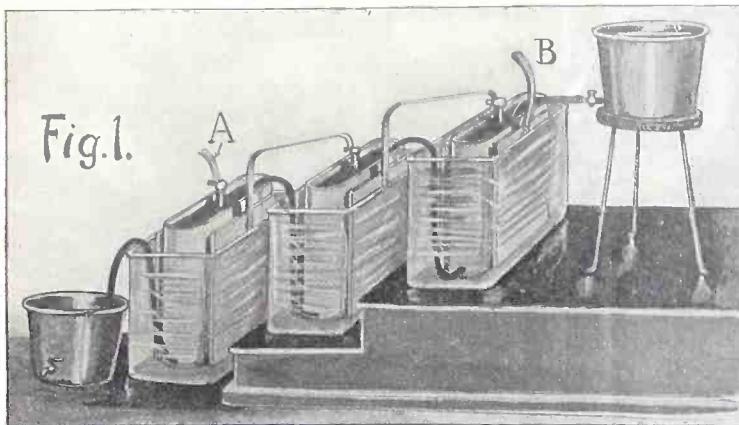


Fig. 1.

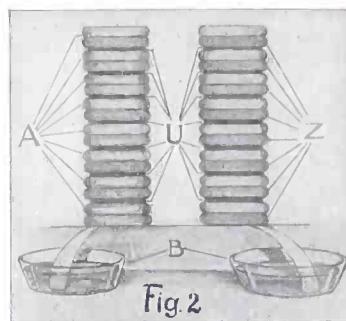


Fig. 2

By Lewis Winner

Associate, Institute of Radio Engineers

A BATTERY is a combination of elements, dissimilar as to property, arranged so as to produce electrical action. There are fundamentally two types of cells, known as the primary cell and the secondary cell.

A primary cell is one in which the making of any electrical current takes place when a diluted solution of some acid or alkali acts upon two elements, dissimilar to each other and connected in electro-chemical series. That is, only when a chemical action takes place between two plates of dissimilar characteristics, which are connected as described, due to the action of an acid solution, will a current be derived. A cell of this type requires no preliminary charging and is commonly known as the dry cell, although the cells really contain a liquid solution absorbed by a blotter, etc.

A secondary cell is one in which an electromotive force will be obtained when an electric current is passed from one set of elements through an acid electrolyte to the other set of elements. The action that results causes the plates to have dissimilar characteristics. At the same time a difference of potential is set up between the plates of the cell. As soon as these elements are joined by a conductor an electric current flows.

Now, there are about 65 types of batteries, all of which are based upon the above two principles.

Many of the batteries to be discussed have been discarded, but it is interesting to note the types that existed before the

two types most commonly used came into favor. At present a great deal of research work is being done on batteries to find out the elements that could be employed in chargers, A and B eliminators, and in A, B and C batteries.

1. The acetic acid type battery is one whose exciting solution is acetic acid or vinegar. Little is known about this type of battery. The only place where this type of battery found its use was in the chemical laboratory to produce feeble currents to actuate medical meters. It is now extinct.

2. The alum battery is one in which a concentrated solution of alum is used as the active liquid. Alum is a much weaker solution than acetic acid. An alum solution in this form will give a more constant current. Automatic electric clocks had this type of battery in the beginning, but magnetic relays, operated by the house line, are used now.

3. The bagration battery is one in which ammonium chloride is the active solution. The electrodes are zinc (positive) and carbon (negative), both of which are immersed in damp earth. The earth is damped by the sal-ammoniac solution (ammonium chloride). With this type of battery the current obtained is very constant.

4. The bichromate battery is one in which the active solutions are sulphuric acid, pure water, and potassium bichromate. The electrodes are composed of zinc (positive) and carbon (negative) plates. To make this solution, any of the following formulae may be carried out: (a) Dissolve about 1 pound (chemical manner to ascertain quantity of liquid)

of potassium bichromate in 10 pounds of water. To this gradually add $2\frac{1}{2}$ pounds of C. P. sulphuric acid. (b) Dissolve six pounds of potassium bichromate in 2 gallons of boiling pure hot water (preferably distilled). Mix 1 gallon C. P. sulphuric acid to 3 gallons of pure water. Then mix the two slowly. (c) Put 3 pints of pure water in a porcelain vessel. Add 5 ounces of C. P. sulphuric acid to this water. Then add 6 ounces of powdered potassium bichromate. Of these three formulae, the second is the best. When using this solution, which is known as Electropoison Fluid, it should be cooled.

4a. The Bunsen battery is one in which the active solution is sulphuric acid or the solution mentioned for the bichromate battery. The plates are composed of carbon and composition zinc. The carbon is the negative plate while the zinc is the positive plate. The substance which is used to take the film of gas bubbles deposited on the plates when the cell is in operation is nitric acid. This is known as the depolarizer. The solution of sulphuric acid which is employed is not concentrated. The carbon plate is placed in the center of a cylindrical vessel (one that will stand the strength of the acids without deteriorating). A metal cap is attached to this carbon plate. The zinc is in a cylindrical fashion and surrounds the porous cup. The nitric acid is in with the carbon compartment. That is, a cup surrounds the carbon plate. Within this cup is this solution. The sulphuric acid

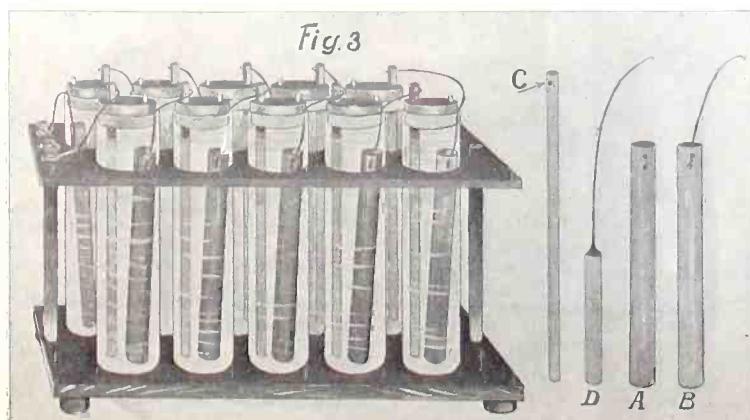


Fig. 3

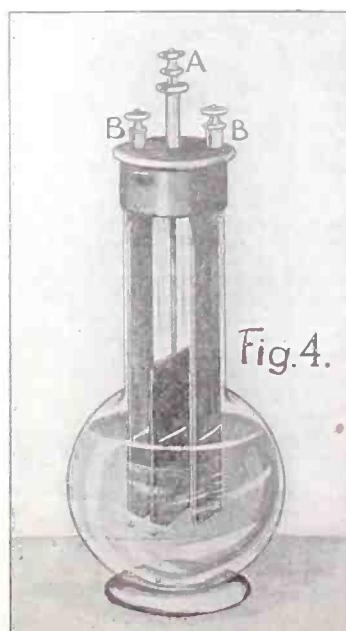


Fig. 4.

How Cells Are Made to Work

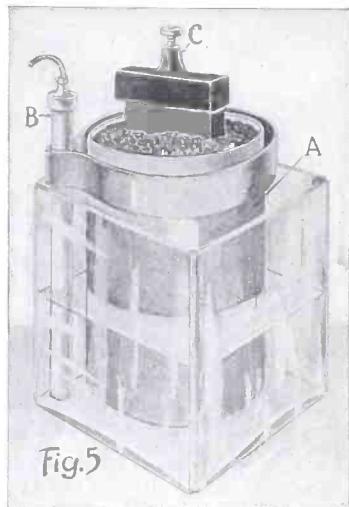


Fig. 5

surrounds the zinc cylindrical plate. This battery is known as the porous cell battery. It is named after the man who invented the Bunsen burner, which is used extensively in the chemical laboratory.

5. The cadmium battery is one in which cadmium sulphate is the active solution. It is also the depolarizer. The cadmium is the negative plate and zinc is the positive plate. The voltage obtained from a battery of this type is about .4. This is a type of the gravity battery, of which more will be said about later.

6. The chloric acid battery is a modified form of the Bunsen battery. An acid solution of potassium chlorate is used as the depolarizer, instead of the nitric acid.

7. The chromic acid battery is a form of the bichromate battery. Chromic acid is used as the depolarizer.

8. The Camacho battery is one in which an Electropoion Fluid is used as the depolarizer and active solution. The carbon plate is negative and the mixed zinc is the positive plate. The carbon as you will notice in Fig. 1, is placed in a cup which is porous, wherein loose carbon granules are packed. A is the carbon plate and B is the zinc plate. Note that the solution is delivered from cell to cell by means of a siphone.

9. The D'Arsonval battery is a form of the Bunsen battery, differing from the bunsen battery only as to solution. As the active solution, the following solution is employed: Twenty glasses (common size) of distilled water; one glass of concentrated sulphuric acid and one glass of concentrated hydrochloric acid. As the depolarizer, in which the carbon plate is surrounded by, one glass of concentrated nitric acid, one glass of concentrated hydrochloric acid, and two glasses of diluted sulphuric acid are used. When mixing these solutions great care should be exercised. Always mix the acids and then add the water.

10. The DeLaRue battery is one in which the active solution is ammonium chloride and is composed of 23 parts of ammonium chloride to 1,000 parts of water. The depolarizing solution is silver chloride. The positive plate is zinc and the negative plate is pure silver. The construction of a type of this battery is shown in Fig. 3. C is the zinc plate punched with a hole at the top so as to pass a wire through for connection with the silver plate, which is next line and


lettered D. The silver is enclosed in a cylindrical form consisting of silver chloride, which naturally makes up the outer coat of the plate. B is a parchment or sheepskin paper cylinder. There are two holes punched at the top, so as to pass the silver wire of the negative plate. This is clearly shown in B. The voltage of each cell is quite great about 1.035. To prevent evaporation of the solution, parafin solution is placed over the ammonium chloride.

11. The ferric chloride battery is another modified form of the Bunsen battery. The only difference lies in the solutions. Ferric chloride is used as the depolarizing solution.

12. The Fuller battery is another form of the Bunsen battery. Here, however, instead of the solutions being changed, the plates used are different. The zinc plate, which is positive, is small and cone shaped. This is placed in a jar, into which mercury is placed. The outer jar is composed of pure carbon and is the negative plate.

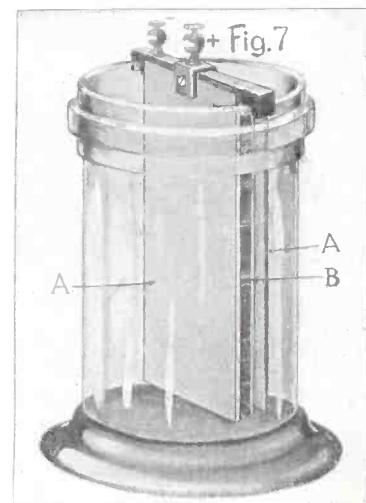13. The gravity battery is one of great importance and takes in quite a number of different forms of batteries.

One of the first forms of this type is the aluminum battery. Aluminum sulphate is used as the active solution. Aluminum is the negative plate. Another form of this type is the balloon battery. A globular flask, such as is used in the chemical laboratory, is filled with crystals of copper sulphate. The flask is then filled with water. This acts as a reserve of the crystals. This flask is inverted into a glass jar containing the elements. Now the original gravity battery is made up as per; a disk shaped copper plate, which is very narrow in thickness, is placed at the bottom of the flask or jar. Near the top of the flask, supported by some means, a zinc plate is placed. This plate is also very thin. The active solution is composed of a very concentrated solution of copper sulphate. This fills only a small portion of the jar. Over this solution is placed a less concentrated solution of zinc sulphate. This must be lighter than the zinc sulphate, otherwise it will sink to the bottom. In order that the jar may be filled up, a solution of zinc sulphate may be mixed with water. This is used as the upper liquid. When the strength of the solution decreases, a few crystals of copper will be dropped into the jar. The zinc plate is cylindrical and is placed at




the top of the jar, about 1/2 the way from the bottom of jar. It is advisable to remove the zinc plates every now and then, as the copper forms a sulphating coat on the zinc. This stops the action of the cell. The voltage of each of these cells is dependant upon the size of the jar, plate and amount of solution.

14. The Grenet battery is one in which a solution of bichromate is used as the depolarizer and active solution. The zinc plate A is the positive plate and is used in plunger fashion. That is, it is plunged into and then taken out of the solution. The carbon plates B are negative. This type of battery is shown in Fig. 4.

15. The Grove battery is a very important type of battery, as it was the first of the storage batteries. It was first made as per: Thin plates of platinum were placed in small vessels of dilute sulphuric acid. They were arranged as if they were zinc and carbon plates. Each one of these plates is surrounded by a glass tube and sealed at the top. Each tube is filled with acid up to the very tops. Naturally through the top, the connections are made. This is what happens inside the battery: A current from an external battery is passed through these cells. This decomposes the water. This also causes the upper portion of one set of plates to be surrounded by an atmosphere of oxygen and the other set by an atmosphere of hydrogen. As soon as the terminals of this battery is connected, a current is delivered in the opposite direction to that of the current delivered to it by the external battery, which is really a charging unit.

The real Grove battery, though, was made as per: Dilute sulphuric acid is the active solution. Nitric acid is the depolarizer. The negative plate is composed of a small band of platinum. The positive plate is composed of mixed aluminum. This battery gives off noxious fumes and therefore is very undesirable.

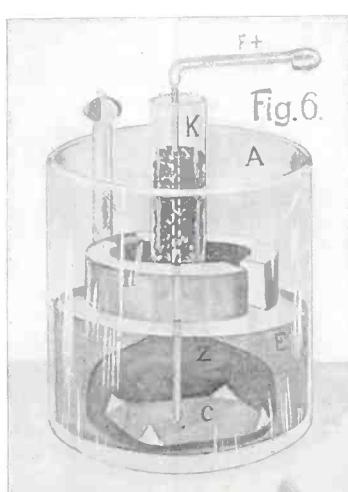16. The Leclanche battery is the most prominent of all the batteries yet discussed. Fig. 5 shows the internal construction of one of these cells. It is, of course, the real dry cell or open circuit battery. In the outer jar, we have a zinc rod, designated as B. C, the carbon rod, is inserted in a cup, containing a mixture pure powdered manganese dioxide (this is the depolarizer) and graphite (lead). These solid substances are put in equal



Solutions Used in Batteries

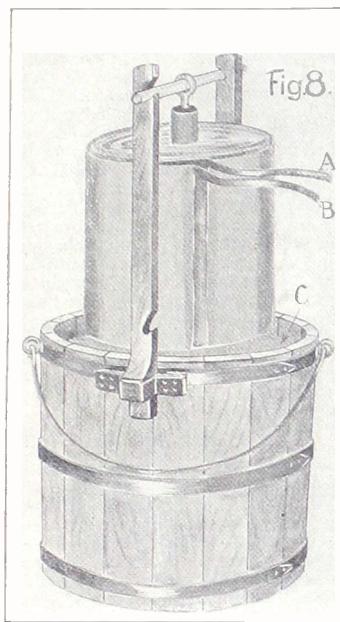


Fig. 8.

20. The Siemen and Halske battery is a very novel type. A copper plate C, which is negative, is placed at the bottom of a large jar, shown in Fig. 6. K, as you will notice, is bell shaped. It contains a large quantity of paper pulp. This pulp is wetted by sulphuric acid, which acts as the excitant. The zinc, which is positive, is put above the paper pulp.

21. The Sir William Thomson battery is another type of the gravity family. Zinc sulphate solution is used as the active solution and depolarizer. The vessels which hold the plates are practically flat and contain a thin lining of lead. Right over this lead a copper plate, which is negative, rests. The zinc plate, which is positive, is shaped as a biscuit mold. That is, the plate is divided into square sections, with each section sunk in. These plates rest on small wooden blocks, which are placed right over the copper plate. In other words, the copper and the zinc plates are parallel to each other. In order to get any pep out of this battery, the charging method has to be resorted to.

22. The Smee battery is a very unique although an expensive battery. This is illustrated in Fig. 7. The active solution consists of diluted sulphuric acid (one to seven). Zinc is the positive plate. The negative plate is composed of a silver plate, which has a black coating of platinum. The voltage obtainable from a battery of this sort is .5. A is the silver plate, while B is the zinc plate.

23. The spiral battery is one which can be easily made at home. Very thin strips of zinc compose the positive plate, while thin strips of copper compose the negative plate. These plates are wound in spiral fashion, as is shown in Fig. 8. A is the copper plate, while the B is the zinc plate. These plates are placed very close to each other, but in no way touching. Sulphuric acid, which has been diluted with about 7 parts of water to one part of acid, is used as the active solution. The plates are dipped into the solution and then taken out. It is a very cumbersome affair, as you will note. It affords, however, an interesting experiment at home.

17. The lead sulphate battery is very similar to the gravity type of battery. However, lead sulphate is used as the active solution and depolarizer. Either tin, copper or lead plates may be used as negative plates. The Marie Davy battery is made on the same style as the lead sulphate. Mercury sulphate is the depolarizer and active material. The carbon plate is negative and the zinc plate is positive. The voltage obtainable from a battery of this type is equal to that of the average dry cell or 1.5.


18. The Meidinger battery is one of the modified forms of the gravity battery. The zinc plate lies against the top of the jar. The copper plate, which is much smaller than the zinc, is placed on the bottom of the jar. A large tubing, with a small gap at the bottom, is supported in the center. This is filled up with pure copper sulphate crystals.

19. The Plante secondary battery is another of the earlier forms of storage batteries. This type of battery has been the most successful as to storage operation. Two pure large lead plates are placed together and immersed in a dilute solution of sulphuric acid. They are "made" by exposing them to a current, which has an electrolyzing property. The current is passed through in one direction only. In this manner, the surface of one plate is changed to a binoxide. The cell is allowed to discharge itself completely, before another charge is put on through plates. This same operation is followed for about 3 days. Then a certain period is allotted for stopping. This sets up a local action on the plate that is oxidized. This action is between the metallic lead of the element and its coating. The resulting action causes the lead to be attacked. Lead sulphate is formed. By charging this plate, it is changed into lead peroxide.

24. The upward battery is a very elaborate affair and is very difficult both to understand the construction and the operation. The positive plate, which is in the center, and called Z in Fig. 9, is solid zinc. B is a cup, which a porous outer layer, and as you see, the zinc is placed in this water. C are the carbon plates, which are solid and pure. Between the outer surfaces of the water cup and the surfaces of the carbon rods, finely powdered carbon is placed. A pipe is inserted into the powdered carbon. Through this pipe chlorine gas is fed. Now this is what happens: the chlorine feed its way through the carbon. It goes through the porous cup and therefore dissolves in the water. Since it dissolves in the water the zinc, which is inserted in this portion, is attacked. When the two combine, zinc chloride is formed. A constant supply of this gas can always be had from a chlorine generating source.

25. The Galvanic battery is a general way of stating an apparatus which causes chemical energy to be changed to electrical energy. Fig. 2, shows a battery column of the Volta or the above type. Here a batch of copper plates (A) are connected in series with a batch of zinc plates (Z). That is, one zinc plate (positive) and one copper plate (negative) are

Fig. 9

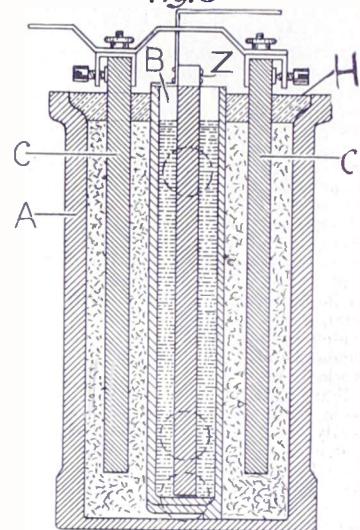

placed together in series in alternate fashion. A piece of soft flannel, covered with diluted sulphuric acid, is placed in between each pair of copper and zinc plates. These pieces of flannels are known as U in the Fig. Across the top of this pile, a metal bar should be placed. This as you will notice has been left out of the Fig. In the small vessels, B, water which has been diluted with sulphuric acid with the plates from the elements are used as the electrodes. Great care should be exercised when making this pile, to see that acid doesn't run from one piece of flannel to the next over the outside of the plates. This will happen if the flannel is too heavily soaked with acid. It is also difficult to keep the flannel soaked with acid and therefore requires frequent attention. Volta invented the first acid battery, which used a copper plate as the negative plate and a zinc plate as the positive acid.

Now in the discussion of all these batteries, we have only found really two types. The primary type is that type from which current can only be obtained when the depolarizer is in an active state, but as soon as the depolarizer is reduced to a lower state of oxidation, the cell starts to discharge. The secondary type of cell, is one in which a current has to be put into the cell, in order that a current may be obtained.

It will be recalled that when the Plante battery was discussed, the forming of lead plates was discussed. These plates after forming are used in the lead storage battery so commonly used now. There are many positive and lead plates in a cell. The active substance in the positive plate is lead peroxide. The negative plates consist of spongy lead. The active solution or as it is called the electrolyte, consists of diluted solution of sulphuric acid (20% pure), which usually has a specific gravity of 1.225. Briefly this is what happens during the charge and discharge of the lead cell style of battery. When the battery is being discharged or in use, the acid combines with the active material of the plate.

As soon as the acid combines with the active material, lead sulphate is formed. As more and more current is drawn from

(Concluded on page 27)

Noise Elimination in Receivers

By E. P. Peck

Vice-President, Utica (N. Y.) Gas & Electric Co.

RADIO is really no more mysterious than any of the natural phenomena, such as light and sound. The only reason for the apparent mystery in connection with radio is that it has become popularized after our ideas and opinions have become adjusted to life without radio, and being new it is not ordinarily accepted as one of the controlled natural forces, such as electricity for use in our homes and factories. Inasmuch as the development of radio broadcasting has been very recent, the engineering has not progressed as far in this line as it has in many other lines, and a good many of the laws governing the operation of radio devices and fundamentals are not yet thoroughly worked out.

Since radio broadcasting and the use of radio receivers in the homes has only recently become general, it is very natural that most of us do not know just what we should expect from a radio receiver. Our ideas have been formed quite largely by articles in the daily press and in magazines and the things that our friends have told us about what they have heard over their receivers. We overlook the fact that the things written up and talked about are nearly always the unusually fine performances, and seldom does anyone brag about the kind of reception he got on a very poor night or on a night when the crashes of static prevented good reception. However, when you install a receiver, or what is commonly called a "radio," in your home you find right away that you cannot get everything that you ever heard of other people getting and that the reception of music, when it is obtained, is sometimes rendered unpleasant by undesired noise from the receiver.

He Wanted a Lot

A little article in a magazine "On The Air" describes a case of too great expectations most interestingly.


"Some time ago an acquaintance called upon me in regard to his new radio receiving set which he claimed did not work right. 'I can't understand it,' he began, 'I get the local stations clear enough but on the distant stations the set seems to fall down.'

"Your difficulty is not unusual," I replied, somewhat bored, for somewhere in the dim recesses of my memory I seemed to have heard the same story before. 'What you desire, I suppose, is greater selectivity.'

"No, that isn't it; the set is selective enough but the signals from the distant stations are not clear. Cincinnati, New Orleans and Denver, for instance, come in fine—clear as a bell and with great volume—but it is with stations like Fargo, N. D., Columbia, Mo. and Atlantic City that I have trouble. They sound scratchy and come in with a lot of crackling sounds. I only use a piece of wire six feet long for an aerial and can't use a ground; as soon as I connect the ground, the crackling becomes so loud I can't use the set."

"What?" I finally cried. "Do you mean to sit there and calmly tell me you consider Cincinnati, Denver, and New Orleans local stations and that you pick up every 50-watt station within a thousand miles at this time of the year on a six-foot aerial and no ground and on top of all that still have the nerve to say your set doesn't work right?" (This was in Chicago and in July).

"Why, sure," he replied, bewildered at

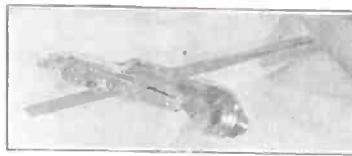

POOR CONTACTS in a jack cause troublesome noise. See that the spring makes firm contact and that the contact point is not corroded. If so, file it slightly.

my amazement, 'but I don't get them clear. I always hear that scratchy noise, they—'

"Enough," I interrupted. You are either plain crazy or you haven't the slightest conception of what a radio set should do."

The latter was the case. He was neither mentally unbalanced nor a disciple of Baron Munchausen, but he actually and honestly believed that he should have no difficulty whatever in picking up 50-watt stations a thousand miles away and that they should come in clear as a bell. It is true, he had what is perhaps the finest and most expensive radio receiving set manufactured and it performed wonderfully, but he had no idea of what to expect. The trouble was not with his set, it was with him in that he expected entirely too much."

Now the trouble with the reception on this particular radio receiver was that the extremely sensitive set was picking up what are commonly called "background noises." The more sensitive the set, the more of these background noises are picked up. On some of the extremely sensitive sets these noises may be heard almost every night in the year.

No Sound Via the Air

We frequently speak of the music or the talk coming over the air. As a matter of fact, in radio reception no sound is carried through the air. What traverses the space between the broadcasting station and your receiver is not sound, but a group of electric waves. Correctly speaking it is no more sound than is the electricity coming over the power wires to drive the industries in the city. The broadcasting station makes the waves of a form such that when they are brought into a correctly made and adjusted radio receiver, they may be converted from electric waves to sound waves, or music, in the receiver. There really is no sound in any part of your receiver except the telephone headset or the loudspeaker.

Since these radio waves are electric waves and your receiver is a very delicate instrument made for the purpose of receiving electric waves, you will necessarily get other sounds in your receiver if other electric waves than those sent out by the broadcasting station are put into the receiver. Now, it is an unfortunate fact that any electric spark produced by any electrical equipment causes electric waves.

Electricity Ever Present

Electricity is always in the air, and any sparks produced in the air, or from cloud to cloud, or from rain drop to rain drop, will produce electric waves. These waves are not of any particular wavelength or frequency and, in general, they may be said to be waves of almost all frequencies. Consequently, these disturbing electric waves, produced by sudden movements of the atmospheric electricity or by sparks produced by electrical apparatus, cause interference to your reception.

The atmosphere always contains elec-

tricity. The amount does not stay constant and it varies between different locations. However, some observers have measured voltages of about 40 volts per foot elevation, which means that a cloud 3,000 feet in the air might have a voltage 120,000 volts above the ground voltage. We know from other studies that lightning strokes are caused by voltages often well over one million volts.

With these large voltage differences in the air, and with particles of moisture and clouds drifting through the air and changing their position constantly, there must be very high voltages produced between different groups of moisture particles and these voltages must cause discharges of electricity through the air at more or less frequent intervals. Every one of these electric discharges may cause interference to your receiver if it is within any reasonable distance.

1/100,000 of a Volt Per Foot!


A good radio receiving set is one of the most sensitive instruments made by man. In the Bureau of Standards in Washington there are some of the most delicate mechanical and electrical devices in the world for measuring weights, lengths and electricity. The most sensitive of these devices, which are operated only by scientists with years of training, is hardly more sensitive than some of the radio receivers. The real wonder of radio broadcast receiving is that it has been possible to make these ultra-sensitive instruments so simple and convenient to use that persons with no scientific knowledge or training are able to get such wonderful results from them. A good radio receiver will give understandable reception if the radio-frequency voltage received on the antenna is around .0001 volt per foot. Is it surprising that your receiver does pick up disturbing noises?

The most sensitive receivers pick up the most noises, and this is one of the reasons why very simple receivers sometimes produce clearer music than do more elaborate receivers. The real point to consider is the difference between the volume of the program being received and the volume of the background noise. Engineers have found that if the background noise is more than 1/30 of the volume of the program, reception is not good. This means that in order to have fairly good reception you should tune in on the louder stations; then if the disturbing noises are loud enough to be troublesome, the volume control on the set should be adjusted to reduce the volume. With a strong signal coming in, it is nearly always possible to adjust the control so that the music is good and clear and the disturbing noises are not prominent. This, of course, is not so when there is any serious electric disturbance in the neighborhood. These disturbances will be taken up later.

No Cure for Static Yet

It is not yet possible to prevent static from interfering with radio reception. Aside from static, there are many causes of noises in your receiver. A large number of these are produced by electric devices of various kinds, some of which may be in good condition and operating as they are supposed to operate. It would be possible, of course, to do away with all these noises, but this would be at the expense of giving up all of your modern electric conveniences, including electric transportation, automobiles, motors, and all household electrical devices. This, of course, is a price no one would consider paying. Another class of noises is caused

An Analysis of Foreign Sounds

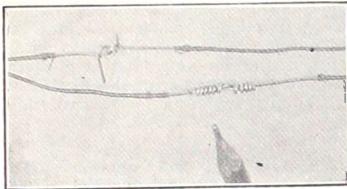

ANOTHER source of noise is a poor contact in the antenna system. Although soldering is highly advisable, many omit it, because when they are ready to erect the aerial they cannot get a hot iron on the roof. A remedy is to measure off the wire and solder in the house. But if twisting is resorted to, avoid the method shown on top. Instead, splice the wire, as shown at the point indicated by the pencil. The two wire ends are separately wound around a small cylinder, like a nail, and the spirals are wound together in screw fashion. Then exert pressure on the wires at opposite directions.

by improperly operated or improperly adjusted receivers.

The interference from radiating receivers is probably the most serious of all broadcast disturbances. This trouble is so general that the Canadian Government has given a series of talks from their broadcasting stations explaining how to use radio receivers to prevent interfering with the reception of your neighbors' radio receivers. They have had this information printed and distributed throughout Canada. These instructions are so good that I am quoting some of them. Their engineers state that approximately 50% of the preventable interference is caused through the incorrect operation of regenerative receiving sets by the broadcast listeners themselves.

Many receivers, particularly of the simpler type, have what is called a feedback or a tickler control. For the purpose of this article, we will agree that your receiving set is made into a transmitting set if you turn the tickler control too far. This tickler control may be marked on your set "regeneration," "tickler," "amplification," "sensitivity," etc. When this control is turned too far, your receiver is sending out radio waves and the wavelengths of your little transmitting station is being changed every time you move your tuning dials. Tests have been made which prove quite definitely that a squeal sent out by a receiver adjusted to produce radiation can be heard fifty miles. Remember, then, that every time you adjust your receiver so that it causes squeals, you are probably interfering with the broadcast reception of a large portion of the broadcast listeners within many miles of your location.

Four Effects of Oscillation

Quoting from the Canadian report:

"When a radio receiving set in a state of oscillation is being tuned to a broadcast station:

(1) It causes whistles in radio receiving sets, of all types, which are tuned to the same station. This interference may be heard up to a distance of several miles.

(2) It distorts the quality of your own music.

(3) It uses more B battery power and therefore the life of the B battery is reduced.

(4) It tends to reduce the life of the detector tube."


When you are tuning your set, you

may get whistles from several causes. The whistle may be caused from improper adjustment of your own set, from interference caused by the receiving sets of some of your neighbors, or by two or more broadcasting stations sending on very nearly the same wavelength. You can tell whether a whistle is being caused in your own set or is coming from the outside by making the tests given in the Canadian instructions, as follows:

"Leave the regeneration control in a fixed position, slowly rotate the tuning dial, and note particularly the change in sound of the whistle. If the whistle rises and lowers in pitch sympathetically with the movement of your tuning dial it indicates that your receiving set is in a state of oscillation and probably causing interference to other sets. On the other hand, if the whistle does not change in pitch corresponding to each movement of your tuning dial, but simply varies in volume, the whistle is not caused by your receiving set, but is interference produced by some other oscillating receiving set in the neighborhood."

The Radioist's Part

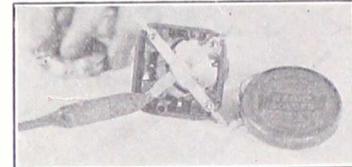You can see that radioists cause themselves about one-half of the preventable interference. Putting this another way,



LOOSE contacts at the socket prongs occasionally develop. It is well to solder the prong to the binding post, as shown.

if each one of you will do your part in preventing radio disturbance, the disturbances will automatically be reduced to at least one-half those you are now getting. Your cooperation should extend much beyond proper operation of your receiver. It is probably entirely safe to say that if each broadcast listener would do his part in the direction of removing interfering sources in his residence, and would cooperate with the power companies in removing disturbances produced by the power lines, preventable radio interference could be reduced to only a small fraction of that you are now having.

Of thirty cases of radio interference
(Concluded on page 24)

53 Interference Sources Make Comprehensive List

Here is a list of 53 sources of radio interference:

In Receiver or Apparatus Connected to It

1. Improperly tuned receiver.
2. Loose connection in receiver or broken wires in headphone or loudspeaker cord.
3. Defective grid leak.
4. Defective tuning condensers—momentary shorting of condenser plates.
5. Fixed condenser with defective insulation.
6. Discharged or weak batteries.
7. Loose connections at batteries.
8. "B" battery eliminators: electrolytic type under certain conditions.
9. Bad socket.
10. Bad tube.

From Apparatus in Same House With Receiver or in Neighbor's House

11. Vacuum cleaners.
12. Sewing machine motors—any commutator motor.
13. Violet-ray machines.
14. Ozonators.
15. Door bells and buzzers.
16. Switching of lamps or other electrical devices.
17. Electrical heating pads with thermostat control.
18. Oil burners using spark ignition—certain types.
19. Washing machines with split-phase type of motor—starting switch defective.
20. Battery chargers; vibrating type.
21. Battery chargers; electrolytic type—under certain conditions.
22. Elevator controllers and motors of the commutator type.
23. Bad contact in switch, fuse, socket, or other device.
24. Hum caused by having radio receiver or its wiring near lighting wires.

From Outside Sources

25. Atmospheric static.
26. Regenerative receivers.
27. Sign flashers.

28. Commercial wireless (code) station.
29. Amateur wireless stations.
30. Induction coils.
31. Electric street cars.
32. Defective rail bonds on street railway systems.
33. Hetrodyming of broadcasting stations.
34. Overlapping of broadcasting stations.
35. Telephone ringers.
36. Induction from telephone and telegraph lines.
37. Motion picture machines using arc lamp.
38. Motors and generators of the commutator type.
39. Electric welding apparatus.
40. X-ray machines.
41. Static machines.
42. Static produced by belts.
43. Electrical manufacturing processes.
44. Induction from high potential circuits.
45. Arcing wire in trees and other grounded objects.
46. Leaking insulators on power circuits.
47. Defective lightning arresters — power circuits.
48. Loose street lamp in socket.
49. Bad contact in switches.
50. Lightning arresters.
51. Smoke or dust precipitators.
52. Defective transformer.
53. Defective street light rectifiers.

This does not cover all possible sources of trouble by a great deal. However, in this list it is seen that there are ten possible kinds of trouble that can be caused by your own receiver or the apparatus connecting to it. There are fourteen kinds of trouble that may occur in the electric equipment in your own house or in the neighbor's house. There are thirty sources of trouble that ordinarily are outside your house, and of these nine may be in the power company's lines or equipment.

RADIO WORLD'S

Laboratory

Reports for the Guidance of Its Readers

Address problems to Laboratory Director, RADIO WORLD, 145 West 45th Street, New York City.

Box Type of Loop Found Most Efficient—Gives Greater Volume with Only Slightly Less Selectivity—Wire Efficiency Studied

WITH the increased popularity of 6- and 7-tube receivers more interest is manifested in the use of loop aerials with these receivers, and since the pick-up is so much less than that obtained with an outdoor aerial the efficiency factor is of greater importance, consequently more attention is being paid to the design and constructional details of these concentrated aerials.

One can very easily comprehend that the efficiency of a loop receiver must be greater than that of an outdoor aerial set if satisfactory reception is to be had. The amount of energy received with a long outdoor aerial is infinitesimal, although the area exposed to the passing wave is large, therefore the pick-up with a unit whose area is only a small fraction of that of the outdoor aerial will be correspondingly smaller, so it is imperative that the losses in the aerial be as small as possible so the greatest amount of signal voltage will be applied to the grid of the input tube.

Box Type Loop Best

The loop constructional design is of importance. That is, whether the loop will be of the box type or the spiral or pancake, the last two mentioned being similar. That the box type is of greater superiority is beyond all discussion, assuming loops whose maximum area is equal. The advantage of the box aerial becomes immediately apparent if fans view the loops as large inductances. This viewpoint is entirely correct, since a loop is nothing but an inductance with a large winding form diameter, and since the single layer solenoid is admittedly superior to the pancake or spiral, the box loop is superior to the other two types. The fact that it is square in form has no great significance upon the usual broadcast band. Very little would be gained if the corners were rounded or the frame made a perfect solenoid. There would be perceptible decrease in resistance as the frequency applied is increased above 1,350 kilocycles, but the increase in efficiency at frequencies lower than this value does not justify the trouble entailed during the construction of a perfect solenoid loop of the correct diameter. Hence the change is not worth while.

All Turns Utilized Fully

Furthermore the box type of loop affords certain other advantages. All of the turns in the loop are being utilized to the fullest extent, since the area is the same for all turns, whereas in the spiral loop the inner turns are not very effective, the operating characteristics of spirals being such as to cause the turns nearest the center to become ineffective. In addition, the distributed capacity of the box loop with spaced turns as compared with a spiral when the electrical constant, that is, inductance, is identical in both, is less and this permits of a greater wavelength ratio with any specific condenser.

There are in addition to the above vari-

ous other items of interest in loop design. Foremost among these is the wire used. While no one goes to great pains to reduce the high-frequency resistance of outdoor aerials by using special wire, the same does not hold true for loops. It is realized that every small gain in efficiency is a manifold gain in receptivity, distance and volume, and all efforts are made to realize upon this knowledge. Relative to the wire used, it must be stressed at the start, that if stranded wire is to be used, it should be Litzendraht.

Stranded wire of the uninsulated type, that is, the turns not insulated, is inferior on certain wavelengths to solid wire of the same diameter or surface area. Tests were conducted upon two loops of identical construction and electrical design, other than the difference in wire used. Loop A was wound with stranded wire (strands not insulated) and Loop B with solid wire of equal surface area. Under these conditions the effective resistance values are indicative of the loop efficiency. The loops were measured on wavelengths between 175 and 500 meters. The following resistance values (Table No. 1) were obtained:

Wavelength	Loop A	Loop B
175 meters.....	42.5 ohms	32.5
200 meters.....	22.5 ohms	17.5
250 meters.....	14.75 ohms	10.
300 meters.....	9.5 ohms	8.75
350 meters.....	7.5 ohms	8.0
400 meters.....	6.75 ohms	7.5
450 meters.....	5.8 ohms	7.0
500 meters.....	5.3 ohms	6.8

The stranded wire, 60/36, is inferior to the solid wire, 24 DSC, on wavelengths below 350 meters (the exact wave upon which both are equal is 325 meters) and the situation reverses itself above that wavelength.

Solid Wire Efficient

However, the difference in effective resistance above 350 meters is much less than that below 350 meters, and it would be perfectly safe to conclude that for general purposes loops should be wound preferably with solid wire, although this wire does not lend itself as well to loop construction, due to its comparative rigidity.

It has been proven quite frequently that wires of 14, 16 and 18 B & S gauge when wound with spacing between turns are superior to coils space wound with thinner wire.

It would be apropos at this time to mention that coils wound with heavy wire without spacing between turns will be found in many instances to be inferior to regular coils using much finer wire, hence it would be well for the fan to bear in mind when winding coils with the heavier gauge wire always to space the turns.

Now, if space wound inductances using heavy wire are superior to coils wound with small diameter wire, why not apply

this advantage to loops? It would be very adaptable, since loops are invariably wound with spaced turns, plenty of winding space being usually available. If this is done, the expected advantage will be realized, as is shown by the accompanying table, No. 2. This is a comparison between two loops of identical inductance value, but wound with dissimilar wire insofar as the wire diameter is concerned. Loop A was wound with No. 18 DSC wire and Loop B with No. 14 DCC wire.

Wavelength	Loop A	Loop B
175 meters.....	20.3 ohms	15.1
200 meters.....	11.75 ohms	9.5
250 meters.....	7.8 ohms	5.9
300 meters.....	6.3 ohms	4.9
350 meters.....	5.3 ohms	3.8
400 meters.....	5.0 ohms	3.5
450 meters.....	4.8 ohms	3.2
500 meters.....	4.65 ohms	3.05

The superiority of the large size wire is easily seen, and a comparison of the two tables will afford at least an idea of the effective resistance difference between loops wound with heavy and fine wire. .

High Resistance on Lower Waves

While the comparisons are not exact, due to the variation in inductance value between the loops used in the two tables, they are sufficiently close because the inductance variations were not radical. The important feature to be stressed is the high-frequency resistance on the lower wavelengths (high frequencies). The gain due to the heavier wire is very discernible.

These tables should not, however, lead one to believe that he can increase the general efficiency of all coils simply by replacing the wire used with heavy wire such as No. 12 or No. 14. There is a definite limit to the wire size, due to the gradual increase of eddy current effects with the increased mass of copper in the wires, until a point is reached where the detrimental effects of the eddy currents induced equal and then overwhelm the beneficial effects of the larger gauge wire, with the final result that the total losses are greater than with the smaller gauge wire. However, heavier wire may be used if the proper precautions are exercised to space the turns; the heavier the wire, that is, the larger the gauge, the greater should be the spacing between turns. For all purposes and reception within the broadcast band, No. 16, spaced, is satisfactory for loops.

Abuse of Tapping

As to the use of a tapped loop, the age-old story is still true. A tapped loop is satisfactory when all of the turns are being used, but when just a portion of the total turns is being used, the overall efficiency takes a heavy drop. This is true regardless of the position of the dead end turns, that is, the unused turns. When the unused turns are at the filament end the effect is not so great as when they are at the grid end, but the bad effect is there, nevertheless. This reference to a tapped loop should not be confused with the loop tapped at the centre and used with certain types of Super-Heterodynes to obtain a regenerative action. The loops referred to as tapped loops are those which purport to cover various wave bands with one condenser.

A loop to afford the best results should be designed to cover one specific wave band. To attempt to use a tapped loop for a certain wave band when all the turns are not utilized is deliberately reducing the output of the receiver. The receiver will not afford the maximum output. To satisfy themselves of this fact let fans who are using a tapless loop tune in any certain station and note the volume. Then

(Concluded on next page)

How to Test Your Set on a Loop

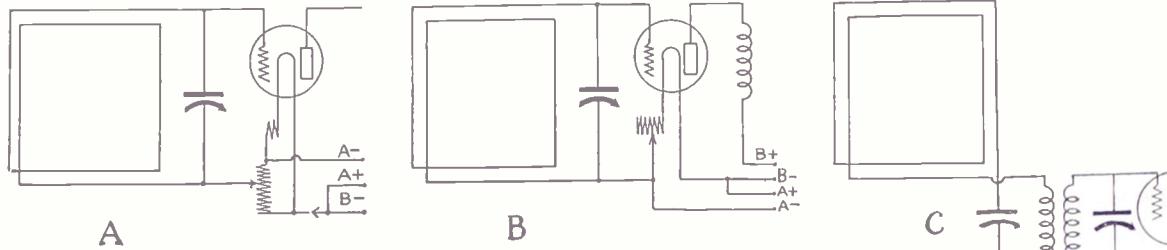


FIG. 1 shows two methods of hooking up a loop, in which A and B are the same method, so far as loop is concerned, the standard and best method. C shows a way to try out a loop on a set that has an untuned primary, otherwise intended for connection to aerial and ground. A shows a potentiometer used to stabilize the tube to which the loop is connected, while in B a rheostat is used as the oscillation control.

MANY persons wonder what sort of results they will obtain on their set if a loop is used instead of an outdoor antenna or a stretch of wire indoors. Often a surprise is in store for them, because the set may not have many tubes, yet its sensitivity may be sufficient to enable loop operation.

The best way to connect the loop is in the standard fashion. One loop terminal goes to the rotary plates of the variable condenser and to the grid return. (A minus or the arm of a potentiometer), while the other loop terminal goes to the stator plates of the tuning condenser and to the grid of the first tube. When that side of the loop which is connected to grid is turned toward the station being received, especially if the signals are not very strong, a noticeable increase in volume will be obtained. Fig. 1, item A, shows this hookup where the grid return is to the movable arm of a potentiometer, just to show what the connection is in a set that uses a potentiometer, while B reveals the hookup where the rheostat is relied on as the oscillation control.

Used in Ordinary Set

But suppose you have a set ordinarily intended for use in conjunction with an outdoor antenna, which most likely will mean that there is a small coil in the set, the leads of which coil are brought out to posts on the set marked "Ant." and "Gnd". This is an untuned Primary. How to hook up the loop in such a set is the problem. One manner of doing this is shown in C of Fig. 1.

Here a tuning condenser has been introduced that is additional to any in your set, which is not true of A and B of Fig. 1, where leads that otherwise went to the

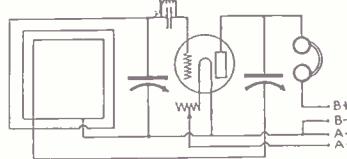


FIG. 2 is the diagram of 1-tube loop set. This will bring in local stations with fair volume. The Hartley method of inducing oscillations is employed for regenerative effect. The loop tuning condenser is .0005 mfd., the loop consisting of 14 turns of No. 24 DCC wire on a 18" square frame, turns spaced $\frac{3}{8}$ " apart. The feedback condenser is .00025 mfd. or .00035 mfd. The tap is at the fourth loop turn from the filament end.

secondary are simply utilized to tune the loop.

In C it will be noticed that the tuning condenser that has been added, and which for the 14-turn loop on a 18" frame is a .0005 mfd. instrument, is not connected directly to the two terminals of the loop. One side of the tuning condenser goes to one terminal of the loop, while the other loop terminal goes to the "Ant." post of the set, the "Gnd" post of the set being connected to the remaining unconnected side of the tuning condenser. Thus the antennal primary coil is in series with the loop, and the distributed capacity of one coil may tend to cut down that of the other.

The method shown in C does not afford maximum volume, but it is an easy ex-

(Concluded from preceding page)
tap a certain portion of the loop, use the turns within that tap and tune in the same station, which action will necessitate a greater value of capacity. The difference, to be more exact, the decrease, will be immediately noted. Hence, always use all the turns of the loop.

About the method of connecting a loop to a receiver, one need not say much; there being only one correct method of connecting a loop. This is via direct leads and binding posts, and not by means of a plug and jack arrangement. In the first place, the contacts between the plug and jack are not always positive and firm, resulting in definite losses. While these contacts are satisfactory in audio amplifiers where the volume and signal voltage are much greater, they are not satisfactory when dealing with the exceedingly small values of signal potential encountered in the input circuit of the receiver. Furthermore, the insulation in the majority of plugs, while satisfactory for audio frequencies, such as found in the audio side of the receiver, are very poor when

high frequency signals are concerned, and since all losses tend to decrease the total output it is essential that all losses in the input side of the receiver be minimized. Also a certain degree of oxidation will take place upon the plug and jack contacts, and minute losses at audio frequency will be increased many times at radio frequencies. And the use of a plug and jack arrangement reduces the wavelength ratio possible with the loop by virtue of the capacity of the plug and jack elements. Measurements upon these units showed that capacity values ranging from 12 to 18 micro-microfarads are found in these units.

These capacitance values are in the majority of cases greater than the minimum capacity of the usual variable condenser, with the result that the minimum wavelength obtainable with the loop, condenser, plug and jack arrangement is never as low as that obtainable when direct lead connections are used and the plug and jack eliminated.

Further measurements conducted to determine the current flow in the loop

experimental method, and the loop possibilities may be gauged on that basis, because the results by the orthodox method will be better. Volume will be improved by the C method if the ground post of the set actually is connected to ground.

The loop has certain advantages over an outdoor aerial, although it does not pick up nearly so much energy. Where interference is suffered, due to stations on wavelengths close together, thus may be tuned out when a loop is used, if the stations are in different directions, due to the directional effect of the loop. This effect is that the energy from the station is picked up when the loop is pointed toward the station, preferably with the grid side of the loop toward the station.

Pointing a Loop

A loop that has its broad side in the direction of the station is pointing at right angles to the station, hence regard one of the lateral angles of the loop as an arrow and point that arrow toward the station. A box loop would be turned with the flat surface of one side toward the station. If you place a loop with flat against a wall, with the back of the loop, left and right, against the wall, the loop will be pointing in the two directions that the wall runs—to your left and to your right, if you are facing the wall. The answer is quickly learnt if you use a loop, due to the absence of results if you try to do the pointing without actually succeeding. With strong local station signals will be heard in many instances no matter which way the loop is turned, although they will be loudest when the loop is correctly pointed, and likewise if incorrectly pointed there is a great tendency to cause whistling.

circuit with various methods of connection showed the superiority of the direct connections. At 1,818 kilocycles the current flow through the loop with a certain input and direct lead connection was 102 microamperes. When the direct leads were replaced by various types of plug and jack arrangements the current flow was reduced from 25 to 35 per cent, with the same input and at the same applied frequency. These statements should not be construed as condemning jacks in general. The regular type of jack is excellent when used for the purpose intended, namely in the audio circuit, but is not conducive to best results when used in circuits carrying radio-frequency currents.

As to the general utility of the loop aerial, it goes without saying that it should be free of all surrounding objects. The loop when in operation should not be contained within the case or cabinet. This method is being used every day, but that does not signify it is correct. That certain concerns encase their loops within the receiver cabinet is no proof of best operating efficiency.

Whole World All Set for Int'l Splendid Co-operation the World Over Marks Plans for Big Event

FOR one full hour during each of the first five nights of tests of the Fourth Annual International Radio Week, beginning next Sunday, every broadcasting station will be silent to the United States, Canada, Cuba and Mexico, to facilitate reception of British and Continental stations. During the last two days three-fourths of the broadcasters in North America will be silent for the first North American DX test.

The week of tests starts Sunday, January 24, at 10 P. M., Eastern Standard Time, when the Americas will broadcast for themselves and for Europe in particular. At 11 P. M. E. S. T. British stations will broadcast (Sunday), while the Americas remain silent.

Announcers at American stations will give their call letters in several foreign languages in this first period, ten to eleven Eastern Time, and listeners will soon grow familiar with the languages used, so that on the entry of the American silence the voices of foreign announcers who will come on the air in special programs for American fans will have a familiar ring.

The First Night

In the first night of the tests, Sunday, January 24, British broadcasters will fill the air with their programs, some of the foremost radio stars of England being scheduled to appear before the microphone in special programs. When it is understood that when it is 11 P. M. in New York it is only 8 P. M. in California, 4 the next morning in London and 5 A. M. in Berlin, American listeners will realize that the foreign stars are inconveniencing themselves considerably to entertain American listeners. In the second night of the tests stations scattered throughout Continental Europe will be heard, while on the three following nights both English and Continental stations will be on the air, with the possible addition of stations in Scandinavian countries as well. Station OAX of Lima, Peru, South America, also will be on the air in the International Tests, transmitting at the same period as the foreign stations.

In view of the late hour at which the broadcasters will face the microphone overseas the Radio Week Committee has arranged to receive from the broadcasters overseas who are active, complete logs of their programs, showing how they differ from the advance programs. These confirmation programs, as they are styled, will be prepared and edited by the committee and published a few days after the tests are completed. They will also be available for checking claims of distant reception by local radio fans.

Fans who wish some official recognition of their feats in logging overseas broadcasts should take special pains to see that their letters citing the stations heard give the particular number listened to, as well as the exact minute of the reception. Be sure to give the call letters correctly. Another important point

is the enclosure of a return addressed envelope, properly stamped, and insuring that the letter containing the claim of reception is postmarked by the local office where mailed before noon of the day following the reception. Letters mailed after this date will be confirmed, but will not be eligible for entry in the various official rosters.

Variation of Plan

On Friday and Saturday of International Radio Week the plan of broadcasting will be varied. In the customary silent hour, instead of hearing the voices of English, French, German or other foreign announcers, the listeners will have an opportunity of hearing stations on the North American continent that have perhaps never come into the listeners' set before because of congestion caused by local transmissions.

Beginning promptly at 11 P. M. Eastern Standard Time on Friday night, January 29, all broadcastes in the United States, Cuba, Mexico and Canada will shut down as usual, except the broadcasters in the Atlantic and Eastern Standard Time zones. These stations will have the North American air free for them for fifteen minutes, when it is expected that many Pacific Coast listeners will log Eastern stations for the first time.

Following the first fifteen-minute period the Eastern stations will shut down with the broadcasters of the Central time zone occupying the air. At promptly 11.30 P. M. Eastern Standard Time the Central time stations will shut down the Mountain stations filling the air with their programs. At 11.45, E. S. T., or 8.45 Pacific Time, the mountain stations will sign off and broadcasters on the Pacific Coast will get busy.

How Idea Was Born

As many broadcasters in widely separated sections of the country operate on the same wavelength it is more than possible that fans will find it possible to set their sets in advance, counting on the wavelength adjustment to bring in the desired distant station the minute the local broadcaster on the same wave has become silent.

Special programs are being arranged by the stations who will participate in the North American tests, with frequent announcements of call letters and station location. In most cases the programs presented will be of the type that has in the past proven itself best for long distance reception to the operator of the station.

International Radio Week, now in its fourth year, has the endorsement of radio trade bodies in every section of the world, the activities in the United States being under the direction of an executive committee composed of representatives of more than fifteen radio trade bodies. The International Week is the outgrowth of National Radio Week, which was inaugurated at the suggestion of RADIO WORLD.

Tabulated Schedule of Events

A DEFINITE plan has been perfected by the casting stations over great distances and an accompanying article which sets forth the effort possible.

The schedule which follows does not include changes, some of which will be made in the course of the week. E.S.T. stands for Eastern Standard Time; M.S.T. for Mountain Standard Time; P.S.T. for Pacific Standard Time.

The following is the schedule of American broadcast stations.

SUNDAY, JANUARY 24
MONDAY, JANUARY 25
TUESDAY, JANUARY 26
WEDNESDAY, JANUARY 27
THURSDAY, JANUARY 28
FRIDAY, JANUARY 29
SATURDAY, JANUARY 30

10 P. M. to 11 P. M., E. S. T.; 9 to 10 M. S. T.; 8 to 9 P. S. T. Stations in the United States, Canada, Cuba, Mexico and Canada will broadcast special programs for the benefit of European listeners. The sending station's call letters and do so many stations expected to be reached.

The following is the schedule for the guidance of listeners in the Americas who seek great DX:

SUNDAY, JANUARY 24

11 to 12 P.M., E.S.T.; 10 to 11, C.S.T.; 9 to 10, M.S.T.; 8 to 9, P.S.T.—British or British and Continental stations will broadcast, while the Americas remain silent.

MONDAY, JANUARY 25

11 to 12 P.M., E.S.T.; 10 to 11, C.S.T.; 9 to 10, M.S.T.; 8 to 9, P.S.T.—British or British and Continental stations will broadcast, while the Americas remain silent.

TUESDAY, JANUARY 26

11 to 12 P.M., E.S.T.; 10 to 11, C.S.T.; 9 to 10, M.S.T.; 8 to 9, P.S.T.—British or British and Continental stations will broadcast, while the Americas remain silent.

WEDNESDAY, JANUARY 27

11 to 12 P.M., E.S.T.; 10 to 11, C.S.T.; 9 to 10, M.S.T.; 8 to 9, P.S.T.—British or British and Continental stations will broadcast, while the Americas remain silent.

THURSDAY, JANUARY 28

11 to 12 P.M., E.S.T.; 10 to 11, C.S.T.; 9 to 10, M.S.T.; 8 to 9, P.S.T.—British or British and Continental stations will broadcast, while the Americas remain silent.

FRIDAY, JANUARY 29

11 to 11:15 E.S.T.; 10 to 10:15 C.S.T.; 9 to 9:15 M.S.T.; 8 to 8:15 P.S.T.—Atlantic (Canadian) and Eastern Standard Time stations will broadcast. Rest of North America and all of South America silent. Good chance for Pacific Coast listeners to pick up Atlantic Coast stations.

11:15 to 11:30 E.S.T.; 10:15 to 10:30 C.S.T.; 9:15 to 9:30 M.S.T.; 8:15 to 8:30 P.S.T.—Central time zone stations in United States will broadcast. Rest of North America silent.

11:30 to 11:45, E.S.T.; 10:30 to 10:45 C.S.T.; 9:30 to 9:45 M.S.T.; 8:30 to 8:45 P.S.T.—Pacific Coast stations will broadcast.

International Tests Next Week

chedule
ours on the Air

which will facilitate the reception of broadcast during the tests. This plan is outlined in the co-operation that makes this joint

ide the actual program, as this is subject purposely, to prevent unjust claims of re-

sential guide.

S.T. for Central Standard Time; M.S.T. for

andard Time.

esting for the benefit of Europe:

JANUARY 24.

JANUARY 25.

JANUARY 26.

JANUARY 27.

JANUARY 28.

JANUARY 29.

JANUARY 30.

T.; 8 to 9, M. S. T.; 7 to 8, P. S. T.—Mexico and South America will send n listeners. Announcers will give the other talking in the tongues of the coun-

P.S.T.—Stations in the Mountain Standard Time Zone of the United States will broadcast. Rest of United States silent.

11:45 to 12, E.S.T.; 10:45 to 11, C.S.T.; 9:45 to 10, M.S.T.; 8:45 to 9, P.S.T.—Pacific Coast stations will broadcast. Rest of North America silent. Good chance for Atlantic Coast fans to pick up Pacific Coast stations.

SATURDAY, JANUARY 30

11 to 11:15, E. S. T. (see conversion to other time zones above).—Broadcasting by Canadian stations. Rest of North America silent.

11:15 to 11:30, E.S.T. (see conversion to other time zones above).—Stations in the northern half of the United States will broadcast. Rest of North America silent.

11:30 to 11:45 E.S.T. (see conversion to other time zones above).—Stations in southern half of the United States will broadcast. Rest of North America silent.


11:45 to 12, E.S.T. (see conversion to other time zones above).—Cuban and Mexican stations will broadcast programs especially prepared in honor of the Canadians. North American stations silent.

Pin Postage Stamps to the Return Envelope

Those who desire confirmation of foreign reception should send a letter to the foreign station heard, giving the call letters and also the exact time that the selection was heard. The selection should be clearly identified. Mail the letter so it will bear a postmark no later than noon of the day following reception. Enclose a self-addressed envelope for reply.

On the question of stamps, it is well to pin the stamps to the return envelope, as the letters, when mailed in a foreign country with American postage stuck on them, probably would not be honored, no more than foreign stamps are acceptable in the United States for purposes of defraying the cost of mailing.

HEAR EUROPE

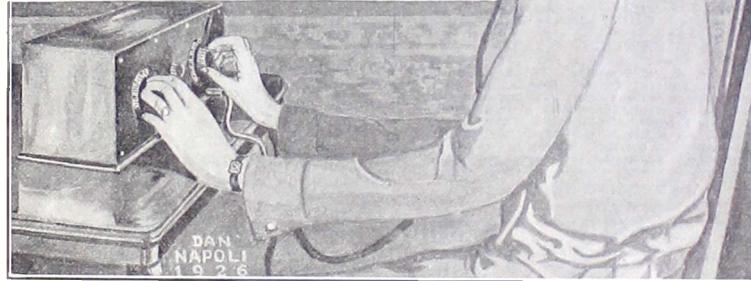

Good Chance to Bring Foreign Stations Direct To Your Radio Receiver

THE Fourth International Tests are about to be made. No doubt many receiving sets in the United States will pick up signals from foreign broadcasters, including stations in England and perhaps on the Continent. Also, listeners in foreign countries have a good chance of hearing programs sent from the United States, Canada, Cuba or Mexico, even perhaps South America.

The New Year tests, still fresh in the minds of most radioists, were unlike the imminent International tests, because in the New year instance the foreign programs were picked up by the American stations, which then re-broadcast them on their own regular wavelength.

Point of Difference

WJZ, New York City, and WGY, Schenectady, played an important part in this. The thrill was there, for to receive programs from the other side of the Atlantic—in that case, programs sent out by the British Broadcasting Co.—appeals to all. But by far the greater thrill will come next week, because then the tests will be different in one very important particular. Instead of a sta-

tion picking up a program and sending it out again, enabling you to receive it on your set as if it were a local or just domestic distance reception, you will have to pick up the original wave of the foreign station, right in your receiver.

Not an Impossibility

This is not an impossibility. While the chances are against success, still the chances are pretty good, because if weather and atmospheric conditions are favorable, the more efficient types of sets in the United States will be able to make a good showing. Receivers as they are designed today are very efficient and are sensitive enough to be favorably ready for the reception of foreign programs. However, there are many uncertainties, and one should not count too heavily on succeeding.

The most sensitive types of sets that operate from a loop may be able to succeed, but their chance would be improved if an antenna coupler were used. This may be of the variety that is used conjunctively with the loop, or the outdoor antenna may be so connected to the set that the loop is cut out altogether.

A THOUGHT FOR THE WEEK

Just think! There need be no shut-ins, in the tragic and literal sense, if only those who have extra sets would contribute them to a general Set Fund for the Alleviation of Loneliness. No shut-in with a radio set is really cut off from the rest of the world. Now, altogether for the S. F. A. L. I.

RADIO WORLD

The Last Connecting Radio Fan Dealer, Jobber, Distributor and Manufacturer

Radio World's Slogan: "A radio set for every home."

TELEPHONES, BRYANT 0558, 0559
PUBLISHED EVERY WEDNESDAY

(Dated Saturday of same week)

FROM PUBLICATION OFFICE

HENNESSY RADIO PUBLICATIONS CORPORATION

145 WEST 45th STREET, NEW YORK, N. Y.

(Just East of Broadway)

ROLAND BURKE HENNESSY, President

M. B. HENNESSY, Vice-President

FRED S. CLARK, Secretary and Manager

European Representatives: The International News Co.

Breams Bldgs., Chancery Lane, London, Eng.

Paris, France: Brentano's, 38 Avenue de l'Opera

Chicago: A. T. Sears & Son, Peoples Gas Bldgs.

Cincinnati Office: Radio World, 304 Provident Bk. Bldg.

7th and Vine Sts. Telephone, Canal 753 and 379.

San Francisco: Lloyd B. Chappell, 636 O'Farrell St.

EDITOR, Roland Burke Hennessy

MANAGING EDITOR, Herman Bernard

SUBSCRIPTION RATES

General Advertising

Fifteen cents a copy \$6.00 a year. \$3.00 for six months. \$1.50 for three months. Add \$1.00 a year extra for foreign postage. Canada, 50 cents.

Receipt by now subscribers of the first copy of RADIO WORLD mailed to them after sending in their order is automatic acknowledgement of their subscription order.

Changes of address should be received at this office two weeks before date of publication. Always give old address also. State whether subscription is new or a renewal.

ADVERTISING RATES

General Advertising

1 Page, 7 1/4" x 11"	462 Lines.....	\$800.00
1/2 Page, 7 1/4" x 25 1/2"	231 Lines.....	150.00
1/2 Page, 8 1/4" D. C.	231 Lines.....	150.00
1/4 Page, 4 1/2" D. C.	115 Lines.....	75.00
1 Column, 2 1/4" x 11"	154 Lines.....	100.00
1 Inch.....		10.00
Per Age Line.....		.75
	Times Discount	
52 consecutive issues.....		10%
26 times consecutively or E. O. W. one year.....		16%
6 consecutive issues.....		10%

WEEKLY, dated each Saturday, published Wednesday. Advertising forms close Tuesday, eleven days in advance of date of issue.

CLASSIFIED ADVERTISEMENTS

Ten cents per word. Minimum, 10 words. Cash with order. Business Opportunities ten cents per word, \$1.00 minimum.

Entered as second-class matter, March 23, 1922, at the Post Office at New York, N. Y., under the act of March 3, 1879.

JANUARY 23, 1926

Program for Children Used as School Adjunct

WASHINGTON

Educational programs by radio for the benefit of school children are being tried out by Radio Station 2FC, Sydney, according to a report to the Department of Commerce. A typical session for primary pupils recently included the singing of Alfred Mill's Maori Song, and an explanation of Mr. Hill's work at the University. Two talks followed, one on nature study by a graduate in science, the other recalling that this year is the 150th anniversary of the Battle of Lexington. The object of these educational sessions is to provide an adjunct to the ordinary school curriculum, the idea being to bring the schools in touch with the present-day thought and artistic movements.

HAVE YOU SEEN RADIO WORLD'S HOOK UP NO. DATED NOV. 27—Full of hookups and picture diagrams, 15c per copy, or start your subscription with that issue. RADIO WORLD, 145 W. 45th St., N. Y. C.

Hearing on Bills Proves "One of the Best Comedies"

By Thomas Stevenson

WASHINGTON.

TWO important facts have been emphasized by the hearings in Congress on the Dill and White bills which would give the Secretary of Commerce additional authority to regulate radio.

The first is that the radio industry, the broadcasters and the public favor the general principles of the regulatory measures. The second is that the average Congressman does not know enough about radio to discuss it intelligently, much less legislate on it.

As pointed out by Secretary Hoover in commenting on the regulatory bills, much time and thought have been given to the form they should take. There have been four annual radio conferences at which representatives of every phase of radio have had a chance to express their views.

The Conference's Ideas

The bills introduced by Senator Dill and Representative White incorporate most of the recommendations of the Fourth National Radio Conference and are fairly representative of the views of those who attended the conference.

Senators and Representatives in Congress frankly admit they do not know anything about radio. For that matter, they cannot be expected to have considerable knowledge of such a highly technical subject.

Congressmen have asked questions which experts can not understand or answer. Some of the questions have provoked considerable amusement on the part of spectators.

A typical example during the House hearings was a question asked by Major Maubourne, of the U. S. Signal Corps, by Representative Frank Reed, of Illinois. Major Maubourne, who has won considerable credit because of his experimental work, did not understand the question and he so informed Mr. Reed.

"Well, you haven't got anything on me," retorted Mr. Reed. "I don't understand it either."

A Long Explanation

At the Senate hearings, it took Acting Secretary Stephen Davis nearly half a morning to explain the difference between a wavelength and a band of wavelengths. The difference between wavelength in meters and frequency in kilocycles was also a hard nut for the Senators to crack.

At the conclusion of the first hearing

in the Senate Interstate Commerce Committee on the Dill radio bill, one of the experts representing a radio company wired an associate as follows:

"Come to Washington immediately. You are missing one of the best comedies I have seen in a long time."

It might be said in passing that W. E. Harkness, expert of the American Telephone and Telegraph Company, has established a record for fortitude during the hearings. Questions that have brought tears to the eyes of others, experts and non-experts, have not caused Mr. Harkness to change countenance. With owlish gravity, he has listened to and answered questions that have made others almost choke with merriment.

What the Situation Is

Of the men on the House Merchant Marine and Fisheries Committee who took an active part in consideration of the White radio bill, only Mr. White himself displayed any intimate knowledge on the subject. On the Senate committee, Senator Dill, author of the Dill radio bill, is the expert.

Congress has never displayed a tendency absolutely to follow the views of Secretary Hoover and others in framing legislation.

If Senators and Representatives take it into their heads that the situation calls for large doses of the amendment medicine the radio bills may emerge in such form as to be wholly unacceptable and actually harmful.

In spite of the urgent necessity for radio legislation, as pointed out by Secretary Hoover, there is danger that the radio bills may not get through this session of Congress. The view of some Senators and Representatives is that Secretary Hoover is merely trying to "pass the buck" to Congress in asking for legislation. If this view becomes general, Congress may very promptly "pass the buck" back to Secretary Hoover by refusing to enact radio legislation during the present session.

In addition, most Senators and Representatives like to have some knowledge of the measures upon which they vote and quite often they are suspicious of anything they do not understand. Due to the fact that there are so few men in Congress who can intelligently explain the radio bills, their progress may be handicapped as a result.

(Copyright, 1926, by Stevenson Radio Syndicate)

Definite Royalty Basis Provided in Copyright Bill

WASHINGTON

An amendment to the copyright law has been introduced in the Senate by C. C. Dill, Washington, which would fix definite royalty payments to authors for the broadcasting of their compositions.

As introduced, the bill does not specify what the payments should be. Senator Dill said he preferred to have the committee which will consider the bill fix the rates rather than attempt to do so himself.

In substance, the bill provides that royalties must be paid to authors for the broadcasting of all copyright matter. The bill would make it necessary for the broadcasting stations to notify the author of the use of the music or other matters

and to make payment therefor within thirty days.

Senator Dill's idea is that the royalty payment should depend on several different factors. One would be the power of the station, and another whether or not the station received compensation for broadcasting the matter for which royalties would be paid. The rate for a small station would, of course, be much less than that which a high power station would be required to pay.

DO YOU WANT TO BUILD ONE OF THE BEST CRYSTAL SETS? See Herbert E. Hayden's article, "One of the Best Crystal Sets," that appeared in our Hookup Number, dated Nov. 7, RADIO WORLD, 145 W. 45th St., New York City.

Radio University

WILL YOU please give me the diagram of a receiver that will reach wavelengths from 75 to 1,100 meters? The radio-frequency tube should be of the non-regenerative type. The detector tube should be regenerative and employ a 3-circuit tuner. The 3 stages of AF amplification should be of the impedance coupled type. A choke coil and a stopping condenser, placed in shunt to the plate of the last tube, so as to obtain greater quality and filament control jacks to control the detector and the amplifier output are also requested to be placed into the diagram. Of course I understand that the coils employed to change from high to low frequency work will be done with the aid of commercial plug-in coils. Please give the constants of the choke coils, resistors, stopping condensers, etc.—H. Blackmer, Jersey City, N. J.

Fig. 253 shows the electrical diagram of such a receiver. C1 and C2 are of the .0005 mfd. variable type. L1 is the an-

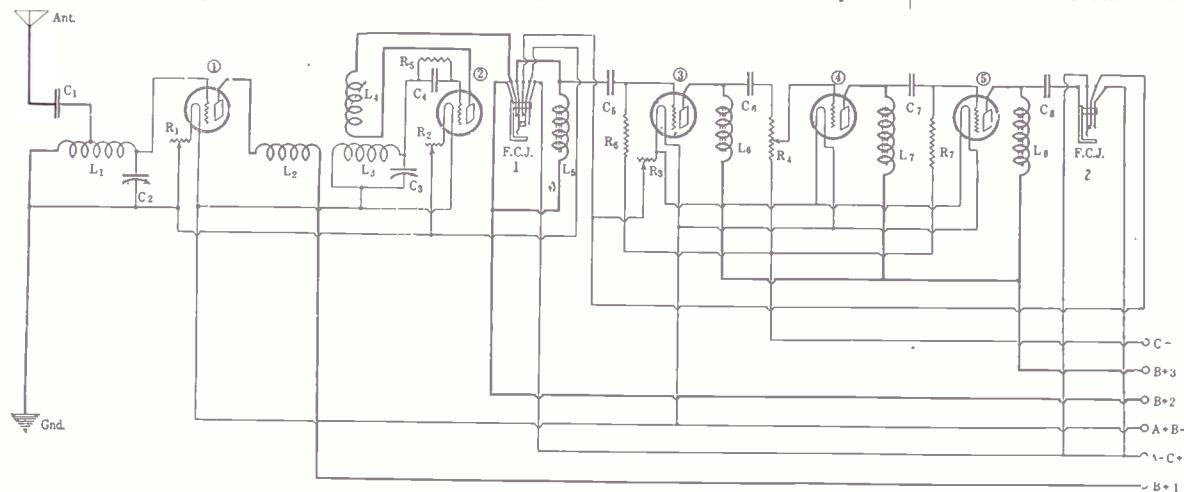


FIG. 253, showing the plug-in receiver.

tenna coil. L2 is the primary, L3 is the secondary, and L4 is the tickler of the 3-circuit tuner. R1 and R2 are both 6 ohm, $\frac{1}{4}$ ampere rheostats. R3 is a 6 ohm, $\frac{1}{4}$ ampere rheostat. L5, L6, L7 and L8 are all 200 henry choke coils. R6 and R7 are 500,000 ohm resistors. R4 is a 500,000 ohm potentiometer. C5, C6, C7 and C8 are of 1 mfd. fixed condenser type. C1 is a .0005 mfd. fixed condenser. Robert Force in the Dec. 5 issue gave a complete description accompanied by pictures of the completed receiver.

* * *

IS THE Lopez Lo-Loss Tuner O. K. to use in the Diamond of the Air?—Harry Canup, 208 North 3rd St., Muskogee, Okla.

Yes. Don't forget to get a radio-frequency transformer to match it.

* * *

I HAVE a Westinghouse 3-Tube RC receiver, which is not selective at all. If I used a SLF variable condenser instead of the 19 plate plain variable condenser would the receiver be more selective?—L. G. Medbery, Eagleville, Conn.

The substitution of the straight line frequency condenser will not make the set more selective at all. It will have a tendency to space the stations on the low waves more equally, that you are now probably receiving close together on the dials. The only thing that will actually make the set more selective is a wave trap, such as that described by

A QUESTION and Answer Department conducted by RADIO WORLD for its Readers by its staff of Experts. Address Radio University, RADIO WORLD, 145 West 45th St., N. Y. C.

John F. Rider in the Dec. 26 issue of RADIO WORLD.

* * *

KINDLY ADVISE me if the Rider Wave Trap described in the Dec. 26 issue of Radio World can be adapted to the Westinghouse R. C. receiver? I have such a receiver and find that I get three and four stations at a time.—William Burke, 1163 Clinton Ave., Irvington, N. Y.

Yes. With this trap and with careful tuning broad tuning will be cured.

* * *

AS TO the Rex Eliminator described in the Dec. 19 issue by Lewis Winner: (1)—Could not No. 30 enameled wire be used instead of No. 26 enameled wire when winding the chokes? I find that I have considerable trouble in placing 8000 turns on the form. This I know, is due to the fact that the small coil winding machine that I am using, does not wind tightly enough.—G. Depew, Atlanta, Ga.

Yes, this type of wire could be used.

Oct. 31 issue of RADIO WORLD. Signals below 400 meters are received with plenty of volume, but above that the volume is very poor. When winding the coils, I used No. 26 double cotton covered wire instead of No. 22 double cotton covered wire. How can my trouble be remedied?—George J. Shuey, Weatherford, Okla.

Add 8 turns to the secondaries, leaving the primaries alone.

* * *

IS IT possible to put a stage of untuned RF amplification ahead of a Reinartz 3-tube circuit, with success? I wish to use a spider-web coil as the fixed RFT. (2)—Where can I obtain full construction details on a satisfactory 4-tube circuit, wherein 1 stage of tuned RF amplification, a regenerative detector, and two stages of transformer coupled AF amplification is used? (3)—Would such a circuit be a marked improvement over the Reinartz. Whatever the improvement be, please note that I wish to use 199 tubes, unless the -01A tubes make a great improvement over the same. (4)—With the present set and with 199 tubes, I get stations 500 miles distant on the loud speaker constantly. If I changed to battery tubes would it increase the volume

of the stations, that I can only receive on the phones, so that I could hear them on the loud speaker?—J. B. Temple, 57 Havelock St., Toronto, Ontario, Canada.

After reading all your queries it seems that you should be satisfied with the set you have at present. A stage of tuned RF amplification will increase the volume of distant stations to a considerable extent. Do not, however, employ a stage of untuned RF amplification. If you use the 201A tubes the signals on those distant stations will also be louder. There is no other set that could be built that will surpass that which you now have as a 3-tube outfit. With the adoption of the 4th tube the same will apply. Any receiver that employs a regenerative detector, with 2 stages of transformer coupled AF, if carefully built, will equal the 5, 6 and even 7 tube receiver, as to distance, volume and quality, unless these receivers employ more than 2 stages of AF amplification.

* * *

MY SET has straight-line capacity (semi-circular plate) condensers. I desire the advantages of straight-line frequency tuning, if it is advisable. Please explain the value of this, if any.—Bertram Reinitz, 127A Clarkson Avenue, Brooklyn, N. Y.

The straight-line frequency dial, such as the Tune-Rite, The Magic Dial and the Rathbun converter, when used in conjunction with a semi-circular plate con-

I HAVE built the Phonograph Cabinet set, described by Lewis Winner in the

denser, affords the tuning ease of a SLF condenser with ordinary dial, an advisable convenience. Thus, as in your case, an existing set gains an advantage of simplicity, due to the wide dial separation between low wave length stations, otherwise crowded. The dials are easily mounted.

* * *

I HAVE built The Set That Thrilled Jack. This was described in the Oct. 10, 17 and 24 issues of RADIO WORLD by Lewis Winner. I am having some trouble with it. Hegehog Audio-Frequency Transformers with 3 to 1 ratios; Micamold and Daven resistors; Dubilier by-pass condensers and an Acme R2 for the first radio-frequency amplifying stage are the parts employed. The nearby stations come in clear and with good volume. The distant stations come in very much distorted. I have tried reversing the A battery leads and changing the connections on the AFT but with no effect.—H. R. Halbass, LaPorte City, Ia.

Disconnect the antenna and the ground. Disconnect the beginning of the primary winding, L3, from the plate post of socket 1 and the end of the winding from the B+ post. Connect the beginning of the primary winding, L3, to the antenna and the end of this winding to the ground. This means that the first tube circuit is out. Take the potentiometer out of the circuit also. Connect the grid return of the new first tube to the F-. Connect the grid return of the detector tube to the F+. Connect the terminal of C6, that now goes to the B+ post on AFT1 to the arm of rheostat R3. Take R8 out. Put a 500,000 ohm potentiometer here, connecting the arm to the G post on socket 5 (really socket 4 now) and the two resistance terminals to one terminal of C4 and the C- post respectively. Change the tubes around. Put 135 volts on the plates of the last three tubes. Put 90 volts on the plate of the RF tube and 67½ volts on the plate of the detector tube.

* * *

I WOULD like to build the 5-tube tuned RF Set, described by Capt. P. V. O'Rourke in the Dec. 26 issue of RADIO WORLD, but I cannot, due to the fact that I have .0005 mfd. variable condensers, instead of the .00035 mfd. variable condensers as specified. Could the coils be wound so that these condensers could be used? If so, please state the number of turns to put on the forms.—John Wahib, 116 Philips Ave., Carick, Pa.

The primaries, L1, L3 and L5 consist of 8 turns. The secondaries, L2, L4 and L6 consist of 45 turns. The wire employed to wind these coils is No. 24 enameled silk covered. The form diameter is 3½". There are 15 rods that this form is composed of. The secondary portion consisting of 18 turns is first wound. The primary winding, consisting of 8 turns is picked up and wound along with the secondary side by side for 8 turns. The primary is of course terminated at the 8th turn, and the rest of the secondary (17 turns) is put on.

* * *


I HAVE constructed a receiver which employs the same principle as that involved in the Fada Neutrodyne. The set works fine with the exception that I cannot pull in stations on the higher wavelengths. The condensers are of the .000375 mfd. type. The coils have 56 turns on the secondaries, using No. 22 silk over cotton covered wire as the conductor. The highest wavelength that I can reach is 520 meters. Any suggestions would be gratefully appreciated.—John Wesing, Oklahoma City, Okla.

Add 3 turns to the secondaries.

* * *

I HAVE built a 3-Tube Roberts Reflex receiver and am having trouble on the second audio-frequency amplification

Rough on Landlord

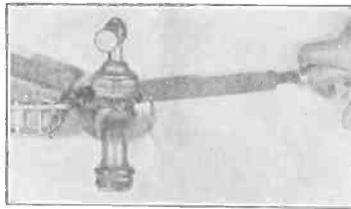

IF you do not own the house you live in, be generous enough not to mutilate the faucet to make a ground connection. Make this contact at the lead cold water pipe below the faucet. Even if you do own the house—well, if you do, the advice is unnecessary.

(Hayden Photo.)

stage. That is, it always howls. I have tried reversing the leads of the primary and the secondary but the volume was decreased. I would like to know if there was something that could be done so that the volume would remain but the howl done away with.—J. Malysak, 531 Brighton St., LaPorte, Ind.

Place a .001 mfd. fixed condenser across the P and the G posts.

* * *

I WOULD like to build the Phonograph Cabinet set described by Lewis Winner in the Oct. 24, 31 and Nov. 7 issues of RADIO WORLD. (1) Are the signals obtainable from this set loud and clear? (2) Is it a good distance getter? (3) Do the signals interfere with each other? (4) Who manufactures the ballast resistances, the AFT, the Autoformers, the rheostats and the stopping condensers, etc.?—W. E. Hicks, 944 Rogers Place, Bx., N. Y. City.

(1 and 2) Yes. (3) No. (4) You may use any of the parts advertised in RADIO WORLD or suggested for other receivers in the various list of parts.

* * *

I WOULD like to have the following queries answered. (1) I am going to change my Thordarson-Wade set to the Duston Special. The primaries and the secondaries are wound on two different size tubings. The primaries are wound on tubing 1½" in diameter. The secondaries are wound on tubing 1¾" in diameter. The primaries consist of 25 turns and the secondaries consist of 150 turns, using No. 22 double cotton covered wire as the conductor. Now I would like to know how many turns to place on the primaries and the secondaries using these same forms, so that I may use .0005 mfd. variable condensers across the secondaries, instead of .00025 mfd. for which the specifications of the secondaries of these coils hold true.—John Bolenbaugh, 173 West Euclid Ave., Jackson, Mich.

The primaries consist of 25 turns. The secondaries consist of 130 turns.

* * *

I WOULD like to have the circuit diagram of a radiophone transmitter, which employs the UV199 as an oscillator and has a transmitting range of ½ mile. The cost of the set should be no more than \$20. (2) Would I need a license to operate a station using such a low amount of power?—Ralph O'Neal, R. D. 4, Everett, Pa.

(1) Such a circuit, with complete data on the coils, condensers, etc., will be published very shortly in RADIO WORLD. (2) Yes. See the June 27 issue of RADIO WORLD.

* * *

IN REFERENCE to the diagram of the Reflexed Neutrodyne which appeared in the Dec. 26 issue of RADIO WORLD. (1) What sized tubing and how many turns are wound so as to make up the coils, L1,

L2, L3, L4 and L5? (2) What are the constants of the condensers, transformers, etc. (3) How large a panel is required to mount the parts (condensers, etc.) that are used in this receiver? (4) With this receiver will I be able to receive the low wavelength stations?—Charles E. Snowhill, 981 Fairbanks Ave., Cincinnati, O.

(1) The primary, which is unmarked, but which is L1 is wound on a tubing 3½" in diameter and 4" high. It consists of 10 turns. The secondary, L2, is wound on the same tubing, with a ¼" separation. It consists of 45 turns. The primary, L3, is wound on a tubing 3½" in diameter and consists of 10 turns. The secondary, L4, is also wound on the same tubing, with a ¼" separation. It consists of 45 turns. The tickler, L5, is wound on a tubing 2½" in diameter and consists of 36 turns. When winding the primaries and the secondaries, No. 22 double cotton covered wire should be used. When winding the tickler No. 26 silk over cotton covered wire should be used. (2) C1 and C2 are both .0005 mfd. variable condensers. C4 is a .00025 mfd. fixed condenser. C3 is .001 mfd. fixed condenser. R4 is a 2 megohm grid leak. R1 and R2 are 6 ohm rheostats. R3 is a ¼ ampere ballast resistor. The -01A tubes should be used if the latter type of rheostats and resistor is to be employed. The ratio of the first audio-frequency transformer is about 6 to 1. The ratio of the secondary audio-frequency transformer is about 3 to 1. The C battery used for the RF tube has a voltage of 4½. The voltage of the second C battery (the one used in the AF stage) is also 4½. However if more than 90 volts is used on the plate of this tube, more C battery should be applied, viz.: 135 volts, 9 volts C battery, etc. (3) A 7x18" panel should be used. (4) Yes.

* * *

KINDLY ADVISE if the B Battery Eliminator described by Lewis Winner in the Dec. 12, 19 and 26 issues of RADIO WORLD, will operate successfully, if constructed with the parts specified on the 110-volt 40-cycle, AC, line?—J. N. Van Dyke, 10 Beekman St., Albany, N. Y.

No, the size of the core for both the transformer and the chokes will have to be made larger. This means that the heads will have to be cut different as per: transformer head, 3" square, width of head 15/16", height of head 1¼"; choke head, 2½" square, width of head, 1¼", height of head, 15/16". The portions on the sides of the heads for the passing of the wire to the terminal lugs, remain the same. Heads of this size can be purchased from the Shore Electric Co., 64 University Place, N. Y. City.

* * *

COULD I have a complete list of the best parts obtainable, so that I may build the Diamond?—E. A. Williams, 555 44th Ave., San Francisco, Cal.

See the advertising columns of this issue. Be sure to get the January 30 issue of RADIO WORLD.


* * *

I WOULD be very glad to know if the Pressley Super is one of the best sets of its type which can be built, wherein a loop is employed. Loud signals from near and far stations should be obtainable. (2) Would the quality of this receiver be improved if 3 stages of autoformer AF amplification were added thereby doing away with the 2 stages of transformer coupling?—Edward Weindl, 404 Urban Building, Louisville, Ky.

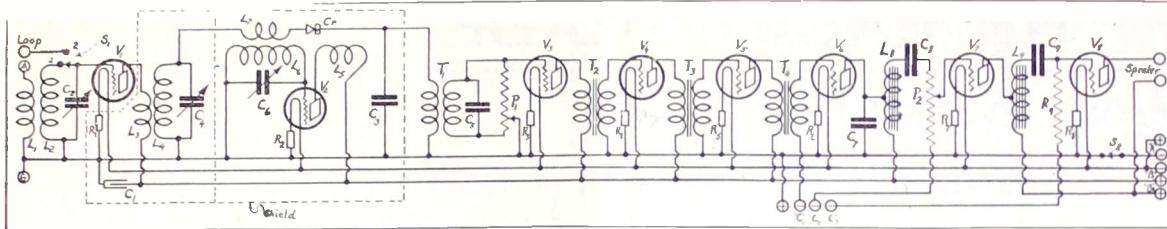(1) The Pressley is a very good receiver for that purpose. (2) Yes, the quality of the signals would be very good.

* * *

I HAVE built the Diamond of the Air and have had very good results with it. However I would like to have these two queries answered. (1) Why is it that at the high wavelengths the readings on the



THE RADIO TRADE

How to Fix List Price; Impatience Often Costly

By Fred W. Mallory

Radio Merchandising Engineer

IMPATIENCE is very costly in manufacturing anything, particularly a product in the radio line, for this is most likely to be something requiring great precision. One of the early signs of impatience is shown by the idea-possessor who, before taking up the factory cost data, rushes into the perilous work of fixing the list price. A likely impulse will prompt him to scan the competitive field, note the list prices, and try his optimistic best to have his own list price under that of everybody else, or at least less than that of any other similar product in the same quality class. This is a mistake.

List Price Important

The list price is a very important thing in radio. On it are based the discounts to the distributor, jobber and retailer. Of course a factory representative will sell the goods to the jobber at the regular jobbing discount for that line, and will receive from the manufacturer the stipulated commission therefor, often 10 per cent. Therefore the list price is the starting point and ultimately everything points back to it, excepting only the actual retail selling price in those markets where cut-throat competition and merchandising ruthlessness rule.

The prospective manufacturer gets an idea for a certain radio product. He has some blueprints made. Perhaps from his own experience he knows the approximate cost of the several items entering into the manufacture of this product. He may even lay the matter before some production concern which he expects will do the actual manufacturing for him. He is not insistent on an adamant price at the moment, but says:

"Let me know what it will cost to produce 50,000 of these. I don't care so much about the exact price, down to a fraction of a cent, but I just want an idea of it—just in a general way."

"Some Sort of Price"

He gets what he thinks he asked for, that is, some sort of price, which the toolmaker, let us say, has been half goaded into giving him, more as encouragement than as anything else, for the actual maker is not bound by what he has said. He has stated merely an opinion, not made a promise. Yet the prospective manufacturer takes this figure more seriously than he should and forthwith fixes the list price. His impatience, although it may

Landlord Removes Aerial, Tenant Sues for \$1,000

A tenant sued his landlord for \$1,000 for removing the tenant's aerial from the roof. The tenant, Norman T. Brenner, then got no reception, and figures his damages are at least \$1,000. He contends that the landlord, Jacob Lowenberg, was not within his rights in removing the aerial without notifying its owner. Brenner charges that Lowenberg had leased a third floor apartment to Fred Marcil, who planned the installation of a transmitter, insisting that there be no other aerials on the roof.

prove costly, has some background of reason, for he has in mind a large advertising campaign in the radio magazines, so he will reach the public that buys radio parts and sets. This campaign can not be undertaken without establishing the list price.

The Solution

The solution, of course, is to exercise just a little less impatience and to wait until the cost is definitely fixed as to all items on which it is possible so to calculate. As to those components which cannot be definitely priced in advance, a liberal estimate should be used, somewhat in excess of the expected price. Thereupon some allowance must be made for unexpected items of expense, which will vary with the nature of the product, but which often will be around 15 per cent. to maintain a safety margin. The actual cost being determined on the basis of written specifications from the owner and written promise from the producer, and the intangible items of expense being generously included, the list price then may be fixed with some feeling of safety.

"Save Your Sorrows"

Then, with the discounts arranged according to the best trade custom, the owner may calculate what he will receive for his product, net, and it is no error to assume that every item will be sold at maximum discount, for that frame of mind, while not picturing the actual condition, bespeaks a conservatism that may relieve future events of much worry and unpleasantness.

The items of cost to be included, of course, will go beyond the actual cost of production of the article and will include boxes, cartons, labels, packing. Usually the overhead, in modern practice in radio, is charged against gross profits, rather than being included in the cost of the article in a delivered state.

The Long Wait

The time of production is another problem. Radio folk are constantly hounding moulders, tool makers, coil winders, etc., for first delivery. Little is promised definitely for a certain date, but indicatory phrases of a non-committal yet encouraging nature are used. Often a much longer time elapses between the giving of the order and the receipt of the first factory shipment than either party imagined. Sometimes the delivery takes two or three times, even five to ten times, as long as both believed it would. This becomes of great importance when it results in a product that was intended for sale in one season being thrown over, very largely, to the next season, due to the slowing up process of the summer months. Those with the most experience do not expect too much. Those with the least experience play hope against likelihood and also pay the price.

Coming Events

JAN. 24 to 30—International Radio Week. Trans-Atlantic tests.

MARCH 8 to 13—6th Annual Radio Show and Convention, Executive Radio Council, 2nd district, Hotel Pennsylvania, N. Y. City.

Literature Wanted

THE names of readers of RADIO WORLD who desire literature from radio jobbers and dealers are published in RADIO WORLD on request of the reader. The blank below may be used, or a post card or letter will do instead.

Trade Service Editor,

RADIO WORLD,
145 West 45th St., N. Y. City.

I desire to receive radio literature.

Name

City or town.....

State

Are you a dealer?.....

If not, who is your dealer?

His Name

His Address

Lawrence Fulton, Muskogee, Okla.

H. M. Hunt, Norwich, Vt. (Dealer.)
L. C. Keck, and Son, 609 Monroe St., Ann Arbor, Mich. (Dealer.)

Wm. Berman, Butts Falls, Ore.

J. Ben. Dake, London, Ind.

Merritt Oberholzer, Mifflintown, Pa.
Charles Runglen, 1008 Avenue K, Brooklyn, N. Y.

Jesse H. Sanders, Greasy Creek, Ky. (Dealer.)
G. W. Ethridge, 153½ N. Church St., Spartanburg, S. C. (Dealer.)

Central Radio Co., Westlake Ave., Seattle, Wash.
John Henderson, 26 Upton St., Cambridge, Mass.

Joseph Hamerman, 403 Hewes St., Brooklyn, N. Y.

L. R. Decker, 930 East 30th St., South Portland, Ore.
Paul Schlek, 4237 Barnes Ave., Bronx, N. Y. City.

Eastern Radio Co., 290 St. Catherine Court, Montreal, Canada. (Dealers.)
B. Gotlieb, P. O. Box 189, Halifax, Nova Scotia, Canada.

P. Curran, Jr., 45 Strathmore Apts., Winnipeg, Manitoba, Canada.

Al D. Romine, 901 T St., Vancouver, Wash.
L. G. Medbury, Eagleville, Conn.

SLEEPER DENIES CONNECTION WITH THE WARE UPHEAVAL

In a statement issued from his Long Island City factory, Gordon C. Sleeper, president of the Sleeper Radio Corporation, emphatically denied that the Sleeper Company was involved in any way in the recent business upheaval centering around the relations of the Ware Radio Corporation, of New York, and the Music Master Corporation, of Philadelphia.

The Sleeper Company is an absolutely independent organization, states Mr. Sleeper, its only connection with Music Master being through a contract which it holds with the latter for the manufacture of one model of a Music Master Receiver, the type 140. It has no connection at all, in any way, with the Ware Corporation.

Business Opportunities Radio and Electrical

Rates: 10c per word; Minimum, \$1.00; Cash with order

FOR SALE—Radio manufacturing plant in operation N. Y. City, Box 1T, Radio World.

MERCHANTISER-EXECUTIVE, widely known; exceptional experience manufacturing, importing, retailing; seeks affiliation with reputable, established business; high character, alert, collegian, 33; possibility investment. Box 2T, Radio World.

RADIO DISTRIBUTOR WANTED—To handle a quality line of radio locally distributed and nationally advertised; New York distributor with Chicago or Western connection preferred. Box OX, RADIO WORLD.

A NATIONALLY KNOWN RADIO MANUFACTURER with a successful record and remarkable growth contemplates putting on the market a radio device of revolutionary character differing from his present line. This is to be done by means of a subsidiary corporation whose stock will be offered to the public based on the past record of the present company. Inquiry is invited from responsible houses prepared to handle such an issue. This is no "get-rich-quick" scheme but will stand investigation. Replies should give complete information as to your responsibility and ability to handle such an issue. P. O. Box P 561, Newark, N. J.

FIRST IN IMPORTANCE

—By Dan Napoli



Radio Leads Electric Field in Exportation

WASHINGTON

As was forecast by the steadily increasing monthly exports of radio equipment, such products show the greatest increase registered by any electrical export class during the first eleven months of 1925. The total value of radio goods exported was \$8,936,565 as compared with \$4,950,746 during the same period of 1924, according to the Department of Commerce.

FIRE ESCAPE IS A VERY GOOD ANTENNA SUBSTITUTE

Where the fire-escape is not attached to the steel framework of the building, it makes a favorite and effective substitute for a regular wire, as it is freely exposed and presents a large surface to radio waves.

Radio Center Opened in New York Office Building

A Radio Center, the newest development in the industry, has been established as a permanent exhibition and market for every known radio part and product. More than two entire floors in the Bush Terminal Sales Building at 130 West Forty-second Street, New York City, and more than 20,000 square feet of space had been leased on a long basis to the Radio Center, Inc., through Col. S. Herbert Mapes, president of the new company.

"The Radio Center is intended as a sort of bourse for manufacturers of radio parts," said Col. Mapes, "and as a service market for buyers. Instead of traveling from one end of the city to another to make comparisons on purchases they intend making, buyers from this and other

cities can see the products of all the manufacturers assembled in one place."

Receiving sets of all makes, all the accessories of the trade and broadcasting equipment will be on permanent display. Sound proof booths have been installed so that each exhibitor may have absolute privacy. A library, reception room and assembly hall are fitted for trade gatherings and conventions.

While radio parts will be demonstrated under actual working conditions all year round, the Radio Center will be open only to accredited representatives of the wholesale trade, Colonel Mapes said. However, a series of special invitation meetings is planned for the general public.

Col. Mapes has been interested and actively engaged in the radio industry for many years. He conducted the first radio fair in New York City in 1920 and later was affiliated with the Federal Telephone and Telegraph Company of Buffalo and with the Jos. W. Jones Radio Company.

Straight-Line Frequency Dial Fulfils Wide Need

While most branches of the radio parts business are highly competitive, only six companies manufacture dials that make semi-circular plate condensers tune on a straight-line frequency basis. Such a condenser is known as straight-line capacity, and it causes the lower wavelength stations to be tuned in on any ordinary dial very close together, while a straight-line frequency condenser affords separation on the lower wavelengths on the same basis as separation exists on the higher wavelengths. The advantage of straight-line frequency tuning, therefore, is that convenience is served. Its contribution to radio's advance is physical ease, as represented mechanically on the tuning dial, whether this be by the process of shaped condenser plates (straight-line frequency condensers) or gears or cams in dials used in conjunction with the semi-circular plate condensers.

Most of the sets in use in the United States today have semi-circular plate condensers as the tuning devices, hence to enjoy the advantage of easy tuning on the straight-line frequency basis it would be necessary to rip the set apart and replace these condensers with straight-line frequency condensers, were it not for the new development, the straight-line frequency dial.

The conversion of the semi-circular plate condenser to straight-line frequency tuning is accomplished by a varying vernier ratio, so that the ratio is highest at the lowest wavelength, say 24-to-1, then grad-

ually declines as the wavelength is increased.

"While gears may be used to accomplish this, there is some danger of back lash or lost motion," said William A. Bruno, well-known radio engineer, president of the Bruno Radio Corporation.

"As the result of nine months of experimenting the Bruno Magic Dial was developed. A system of cam operation is employed with utter simplicity, whereby the turning of the only movable knob on the dial communicates an ever-changing motion to the shaft of the straight-line capacity or straight-line wavelength condenser to which it is attached. No gears are used.

"The Magic Dial functions without backlash or slipping. It requires no screws or bolts for panel mounting. Any condenser that is not straight-line frequency is made to tune as if it were. Thus the Magic Dial uncrowds the air.

"The Magic Dial rotates 340 degrees, while the condenser rotates 180 degrees, and this great spreadout, we believe, helps to put the Magic Dial in front of the class. No extra turns need be added to coils when the straight-line frequency dial is used."

The mechanism is housed in a genuine moulded Bakelite face, which has perpendicular fluted columns, with white Arabian inlay.

The dial is marketed by the Powertone Electric Co., a subsidiary of the Bruno Radio Corporation.

To get the best service out of a radio set in Denmark it is necessary to understand several languages. According to a report to the Department of Commerce, the following stations can be heard regularly in Denmark with sets of two or more tubes:

Daventry, England; Zurich, Switzerland; Munich, Germany, Frankfort, Germany; Königsberg, Prussia; Rome, Italy; Glasgow, Scotland; Breslau, Germany; Münster, Germany; Newcastle, England; Hamburg, Germany; Bournemouth, England; Oslo, Norway, and London, England.

Cotter, Vice-President of Sternfield-Godley

Earl R. Cotter, for three years associated with the sales promotion department of the Sternfield-Godley, Inc., Advertising Agency, 154 Nassau St., New York City, became vice-president of the organization. Sternfield-Godley are widely recognized as radio advertising experts and handle a great many radio manufacturing accounts of national importance and varied in scope.

Among the firm's large national accounts are: Falnestock Electric Co., National Electric Novelty Co., Racon Electric Co., Barbley's Radio Service, Bruno Radio Corp., R. B. Radio Co. and English-Whitman Products Co.

53 Sources of Interferences Discussed by Power Expert

(Concluded from page 13)

investigated by the Utica Gas & Electric Company recently, we find that eight were caused by power lines and equipment of the power company; four were caused by trouble in the receiving sets

themselves; one by a radiating receiver; one by a battery charger; one by a heating pad; one by a motor the customer owned; three by equipment of another utility; the others were found to be either general noises of too small volume to do anything with, or no disturbance was found. The experience of the power company in Utica is about the same as that found by other power companies investigating complaints of radio interference. In general, it may be said that only about one-fourth of the complaints coming in to power companies are found to be caused by trouble in the power company's lines and equipment. Some two or three years ago the power companies found it advisable to start investigating these interference complaints and on account of the importance of the subject, a committee on radio interference was formed in the National Electric Light Association. This committee has been most active in determining the causes of disturbing noises and possible ways of preventing these disturbances. Last year, they made a forty-seven-page report on this subject. The General Electric Company has also been carrying out an exhaustive investigation on different types of apparatus made by electrical manufacturers, to find out which pieces of apparatus cause disturbance and how the disturbances could be prevented. This work is still going on.

How Radioists Can Help

In the work of the power company in Utica on radio interference, we have found that by far the larger portion of interference produced by our lines is caused by tree limbs touching the wires which, of course, results in the production of sparks. Every one of these sparks sends out radio waves which travel the entire length of that circuit, and one of these little arcing tree grounds has caused serious interference to broadcast reception for several miles along a circuit. These tree grounds do not ordinarily stay on the wire, but as the trees are blown by

the wind the limbs touch the wires and move away. Each time the limb touches the wire, a spark is produced and a noise heard in all radio receivers within the affected area. Since the arcing is not continuous, some of these tree grounds are most difficult for the power men to locate. The power company has had men searching for these troubles day and night for weeks. This is not only very expensive, but does not always result in the noise being cleared up promptly.

If any of your trees are touching the wires, it will of course be necessary to get your permission to trim the tree limbs so that they will not touch the wires. If the tree belongs to someone else you would assist greatly if you would explain your trouble to the owner of the tree and get their permission for the power company's men to trim the limbs causing trouble.

RIX

Complete Parts for B Battery

Eliminator with Instructions.....	\$14.75
Blue Tubes 201A and 199 Type.....	1.00
Straight Line Freq. Condensers—	
.0009.....	1.49
.00035.....	1.54
.0006.....	1.65
5 Tube R. F. Radio Sets in Beautiful Mahogany Cabinets	27.50
Apollo Chargers.....	9.75
Fair Wave Chargers.....	12.95
Balkite Chargers.....	12.95
Valley Chargers.....	14.75
Balkite Trickle Chargers.....	7.95
3 Gang Sockets.....	.65
Standard Transformers.....	1.00
Kurz-Kasch Dials.....	.39
3 Circuit Tuners.....	.39
Send No Money. Just Pay the Postman.	.95

\$4.75

APOLLO



A loud speaker of surprising musical quality and volume. In the class with high-priced speakers. Artistically designed. Swan neck type. Adjustable unit where volume and tone are at all times under control. Mail orders filled same day.

RIX RADIO
SUPPLY HOUSE, INC.
5505 FOURTH AVE.
BROOKLYN, N. Y.

5 Tube Radio Set

\$2950

AMERICAN RADYNOLA
5 TUBE SET

The Biggest 5 Tube Value on the Market

Positively the world's greatest 5-tube radio bargain. Regular \$75.00 value, fully built and wired in beautiful mahogany cabinet of latest design, sloping Bakelite panel, Satin finish, hand-wired and tested. Constructed of the finest low-loss condensers, coils and sockets. Bakelite baseboard panel and dials. \$29.50 for set only. Transportation charges extra, shipping weight 25 lbs.

This set with all accessories, includes the famous American Bell loud speaker with adjustable 2-1/2 Volt battery, one guaranteed 100 Ampere Hour, storage "A" battery, cable for battery connection, 5-tube set, aerial and ground equipment, and everything complete ready to set up and operate. Nothing else to buy. Price \$59.75. Transportation charges extra. Shipping weight 100 lbs.

Send For This Radio Book FREE

Contains thousands of bargains in radio sets, semi-finished sets and radio kits of all styles, sizes and approved circuits. Beautiful models, including the new "radio console" cone models with loud speakers built right in cabinets of genuine mahogany and walnut. All sets are built to the highest standard of range. Also contains everything in radio supplies, including batteries, chargers, loud speakers, headphones, etc., and many other parts you may want for improving your set or building a new one. Guaranteed saving to you of 10-30% off the price of the world's largest exclusive radio mail order house.

RANDOLPH RADIO CORPORATION
159 North Union Ave., Dept. 432, CHICAGO



1926 Catalog
Containing
64 Illustrated
pages
of Radio
Bargains
Write for it
Today

Satisfaction
Guaranteed

CLAROSTAT

is the most accurate variable resistance ever placed on the market. It has a continuously variable resistance ranging from practically zero to five million ohms—and all this without a single abrupt step!

\$2.25
American Mechanical Laboratories, Inc.
285 N. 6th St. Brooklyn, N. Y.

LOUD SPEAKER RECEPTION

from either coast on three tubes
Blueprint and instructions..... \$1.00
Necessary low loss coil..... \$2.50
Beautiful finished instrument..... \$35.00

S. A. TWITCHELL CO.
1930 Western Avenue Minneapolis, Minn.

VEBY HIGH-MU TUBES



Especially made
for Resistance
Coupled Amplifiers
to give more
volume of greater
clarity with less
"B" Battery voltage.

A.F.—20 High-Mu..... \$3.00
A.F.—6 Power Tube..... \$4.50

At Good Radio Stores.

VEBY RADIO CO.
47-51 Morris Ave.
Newark, N. J.

CRAM'S INTERNATIONAL RADIO ATLAS

This latest and greatest Radio Atlas has four big maps, a list of all the Radio Stations in the United States, Canada and the entire world, alphabetically arranged by states and cities, latest wave lengths, kilometer and names of operators. Liberal space for your private log. Postpaid on receipt of 50¢, or one cent free with new yearly subscription for Radio World (\$6.00 for \$5.00), but with no other premium.

THE COLUMBIA PRINT
145 W. 45th St.
New York City

Alaska Station Licensed

WASHINGTON


A new Alaskan station has been licensed experimentally by the Department of Commerce. It is KFQD, Chovin Supply Co., Anchorage, Alaska. 227 meters, 100 watts.

**RADIO TUBES
FACTORY PRICES!**

LOW IMPEDANCE, genuine thoriated filament, quarter ampere 201-A type. Silvered and tipless. Will improve any set. GUARANTEED.

79c Each, Postpaid

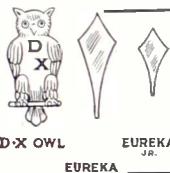TRELLCOTT CO.
2118 Hale Ave. Louisville, Ky.



EAST ORANGE, N. J.
C. W. BUTTS, INC.
40 HEDDEN PLACE
Samples for Standard.

**EUREKA
DIAL POINTERS**
10c EACH
Polished Nickel or Gilt.
D-X Owl Pointer: Nickel 10c
Gold Plated 15c



This is the Norton 3-in-1 Storage B Battery, with Rectifier, and Charger for any house current, whether A. C. or D. C., complete with plug, cord, and necessary binding posts. Made up exactly as your A battery.

Storage Battery Efficiency at Dry Cell cost 100V, only \$18. *135V, only \$23; 150V, only \$25

*Made especially for the Diamond of the Air, and the new R. O. A. power tube. If dealer can't supply, order direct.

REPP-NORTON BATTERY CO., 202 W. 20th, New York

**DX
Quality
Volume
Selectivity**

All that you desire—more than you expect—are at your command if you build

RADIO WORLD'S

1926 Model

**DIAMOND
OF THE
AIR**

The 5-tube set for home construction that works splendidly on either loop or outdoor aerial.

Read Herman Bernard's full exposition of how to build the set that is sweeping the country.

Constructional data, in text and diagrams, appeared in the Sept. 12, 19 and 26 issues; valuable laboratory data in the Nov. 21, 28 and Dec. 5 issues. Any of these issues, 15c a copy.

Send 75c and get all six!

Full-sized blueprint of the wiring, 50c extra.

Send \$6 now for a year's subscription and get these six copies, the blueprint and nameplate FREE!

RADIO WORLD
145 West 45th Street New York City
Send for a free name plate

**Useful Range of Life
Depends on the Drain**

Assuming that a set is operated two hours a day, it has been proven by long experiment that with the proper kind of B batteries the life of those batteries will be about six months. The controlling factor is the consumption rate of the set. This is expressed in milliamperes (one-thousandths of an ampere). It is the current flow or drain.

The smaller B batteries are for sets using three tubes or less and these batteries should last six month if the drain does not exceed 12 or 13 milliamperes. The 4- or 5-tube sets most likely will consume more, say 16 to 20 milliamperes, hence the heavier B batteries should be used, for if the drain is high on a small battery, then the battery life is seriously impaired.

A very small percentage of sets draws more than 24 milliamperes, and for these the heavy duty B batteries should be used. For instance, at that exceedingly high drain the proper size and make of B battery will last five months and 20 days.

These facts are surprising to many, because of the current gossip, not founded on scientific research, that a B battery lasts about three months.

(Concluded from page 8)

and for sets employing four or more tubes, two 45-volt extra large B batteries and one 45-volt large B battery. Note that for sets using four or more tubes there are two 45-volt extra large B batteries and one 45-volt large B battery. Note that for sets using four or more tubes there are two of one type (extra large) and one of another type (large). These should be connected so that the 135-volt tap is taken from the large (not the extra large) battery. The extra large battery may be of layerbuilt construction.

The 135 volts, of course, result from the addition of the voltage (3 batteries, each 45 volts), due to series connection, whereby the plus post of one battery is connected to the minus of the next, in two instances, leaving a free minus post and a free plus post. The voltage taps on the first battery are those designated thereon, while those of the succeeding two batteries represent the labelled voltage plus

the maximum voltage of the preceding battery or batteries.

A PIEZO OSCILLATOR

WASHINGTON

Specifications have been completed by the Bureau of Standards for a portable piezo oscillator, which is used as a frequency standard for the calibration of frequency meters, and as an aid in maintaining constant frequencies for transmitting stations.

FOR CLEAR, QUIET "B" POWER**RADIO Storage "B" Battery**

12 Cells 22 Cells
Lasts Indefinitely—Pays for Itself
Economy and performance unheard of before. Recharged at a negligible cost. Delivers unflinching power that is clear, pure and quiet. Approved as Standard by leading Radio Authorities, including the U. S. Post Office, Post Master General, Radio Broadcast Stations, Lab. Lofax, Inc., and other important institutions. Equipped with solid carbon electrodes and no liquid or gas. Extra heavy glass jar. Heavy rugged plates. Order yours today.


SEND NO MONEY Just state number of batteries required and we will send you a sample and bill of exchange on order received. Extra offer: 4 batteries in series (96 volts), \$10.50. Paid exp. estman after examining batteries. 5 per cent discount for cash with order.

WORLD BATTERY COMPANY

1219 So. Wabash Ave., Dept. 82 Chicago, Ill.
Makers of the Famous World Radio "A" Storage Battery
Prices: 6-volt, 100 Amp. \$11.25; 150 Amp. \$11.25; 160 Amp. \$15.00.
All equipped with Solid Carbon Cells.

World
STORAGE BATTERIES

Set your Radio Dial at 210
meters for the new 100
watt world famous battery
Station, WSHC, Chicago.
Watch for announcements.

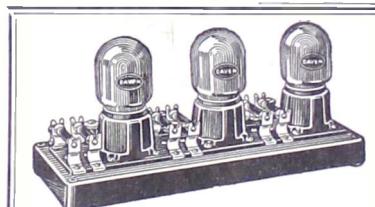**The Daven Super-Amplifier**

for volume and tone quality
3 STAGES RESISTANCE COUPLED
ECONOMICAL DISTORTIONLESS
Easily added to any set.
Saves Several Hours Assembly
For Sale by All Good Dealers

The "ANTENNATROL"

The Remarkable Four-Tube Receiver Described by Herbert E. Hayden in This Issue of RADIO WORLD

Uses**HAMMARLUND CONDENSERS
and SPACE-WOUND COILS**

Which, You Will Agree
With Mr. Hayden, Are

"Most Gratifyingly Efficient"

HAMMARLUND MFG. CO., 424-438 W. 33rd St., New York

For Better Radio

Hammarlund
PRECISION
CONDENSER

Outdoor Wire Gives Biggest Pickup for Aerial Purposes

The Sleeper Radio Corporation, of Long Island City, N. Y., announced the addition of a new 5-tube set known as the "Troubadour" to its line of well-known "Scout" and "Serenader" receivers. It is a lower

priced outfit than the "Serenader." The new "Troubadour" uses an orthodox tuned radio frequency circuit, with two stages of RF, detector, and two stages of transformer audio amplification. It is equipped with a simple two-dial control, with a volume knob and tuning vernier, and is designed to work with a regular outside aerial.

The part the "aerial" plays in the working of a radio receiver is often the subject of inquiry among set owners. As some outfits require the use of outside wires and others get along with short indoor ones, and still others need no lengthy wires at all, radio fans find that their usual conception of the "aerial" as an exposed wire that "picks up" broadcasting out of the air does not cover all receiver installations. To clear the widespread misunderstanding surrounding this subject, J. Louis Reynolds, chief engineer of the Sleeper Radio Corporation, explains the real function of the aerial and corrects a few popular myths surrounding it.

First of all, says Mr. Reynolds, a radio aerial need not be entirely exposed to the atmosphere in order to perform its duties. If, for instance, an indoor type such as the cage-like "loop" is employed, it is not necessary that the windows of the room be kept open, contrary to the amusing belief which many people held at one time and which many in fact still do hold. The radio waves transmitted by a broadcasting station radiate out into space, it seems, and are affected only by large bodies of metal. They travel practically unimpeded through inert materials like wood, brick, stone, non-re-enforced cement, and glass, and lose little of their effectiveness in a passage through structures in which these substances predominate.

A radio aerial is simply a metal body which is excited by a passing radio wave, and which absorbs a little of the electrical energy from the latter; the weak current induced in the aerial in turn actuates the receiving set and is translated into intelligible voice or music by it. Any isolated metal body acts as an aerial, and not

merely copper wires alone. Wires are generally used because they are light, convenient, and easily strung from poles, chimneys, and other exposed supports.



TOROIDS

Measure only $3\frac{1}{2}$ " in diameter. Pri. and Sec. windings are complete toroids. Literature sent on request.

Nolte Mfg. Co.
193 Plainfield Ave.
Jersey City, N. J.

ELIMINATE! STATIC!

Enjoy perfect reception regardless of weather conditions.

The Static Eliminator, the newest and most startling thing in radio, cuts out absolutely all static with lightning speed.

And in addition it will help increase selectivity, tune out local stations, sharpen signals, remove noises, lessen interference and prevent re-radiation.

Use it with any receiving set—simply hook it up between aerial and ground in accordance with our instructions and enjoy perfect reception unmarred by static.

SATISFACTION
ABSOLUTELY
GUARANTEED
Mail order today

\$100
Postpaid

STATIC ELIMINATOR COMPANY
622 United Bank Bldg. Cincinnati, O.

Vacuum Tubes Rebuilt

\$1.00 each

POSITIVELY GUARANTEED equal to new tubes in every respect. Money will be refunded if tubes prove unsatisfactory for any reason other than burn-outs.

Send us your broken and burned out tubes by parcel post. (Not necessary to insure or guard against breakage). We make return shipments by parcel post C.O.D. and try to maintain 24-hour service.

HARVARD RADIO LABORATORIES
200 Old Colony Avenue
South Boston, Mass.

G-K BINDING POSTS

engraved or plain. For engraved ones, specify from following: Ant., Grid, A-, A+, B-, B+ Det., B+ Amp. Binding Post strip complete by mail \$1.25

Ganio-Kramer Company, Inc.
238-R West 53d Street New York, N. Y.

Increased Range and Volume

BETTER SELECTIVITY and QUALITY for YOUR SUPERHETERODYNE if you link it to an Outdoor Aerial with a

SUPERADIO TYPE Q ANTENNA COUPLE R

Tested and Approved by RADIO WORLD Labs.
See January 9th and 16th Issues, or write

THE SUPERADIO CO. 136 Liberty St.
New York City


PANELS

RADIO and HARD RUBBER
RETAIL ANY SIZE WHOLESALE
PRICE LIST MAILED ON REQUEST

HARD RUBBER SHEETS—RODS—TUBING

Special Hard Rubber Parts Made to Order
Send Sample or Sketch for Quotation

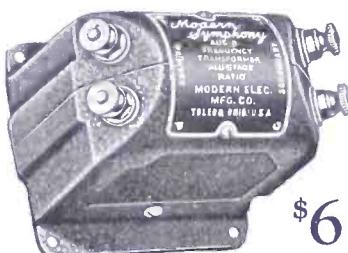NEW YORK HARD RUBBER TURNING CO.
212 CENTRE ST. NEW YORK



\$6

Results Count!

Everyone wants results when they have a radio receiver. You don't get it to look at—you want to hear something. Why not make that listening sooth and pleasant by installing Modern Symphony Transformers? All the original softness and mellowness of music is yours when you replace your old antiquated transformers with new Symphonies.

Modern Electric Mfg. Co., Toledo, O.

Represented by

GRAY SALES CO.

611 Widener Bldg., Philadelphia

S. HAMMER RADIO CO.
303 Atkins Avenue, Brooklyn, N. Y.
Please send me FREE Your NEW
RADIO CATALOG

Name _____
Address _____
City _____ State _____
FILL OUT AND MAIL



The AIRGAP SOCKET

FOR

MAXIMUM RESULTS

Install AIRGAPS. They prevent closed circuit, absorption of current, intercoupling of circuits, feedback and undesirable capacity. They make any circuit more stable and sharpen tuning, resulting in purer and clearer tones with more volume particularly on distant stations.

At all dealers, 75c each.

AIRGAP PRODUCTS CO., Mfr.
188 N. J. R. R. Ave. Newark, N. J.

ULTRA-LOWLOSS CONDENSER

SPECIAL CUTLESS PLATES. DISTRIBUTE THE STATIONS EVENLY OVER THE DIAL. SIMPLIFIES TUNING. CAPACITY 0005 MFD.

\$5.00

PHENIX RADIO CORP., 116-F East 25 St., N.Y.C.

Mailing Lists

Will help you increase sales
Send for FREE catalog giving counts
and prices on thousands of classified
names and addresses—Business, Professions,
National, State and Local—Individuals,
Professionals, Business Concerns.

99% Guaranteed by refund of 5¢ each

ROSS-Gould Co. 313 N. 10th St. St. Louis

"LIBERTY AFLAME" and other verses, by Roland Burke Hennessy. Handsomely bound in cloth; sent postpaid for \$1.00. The Columbia Print, 145 W. 45th St., N. Y. C.

What Action Takes Place When a Battery is Working

(Concluded from page 11)

the cells, the electrolyte becomes weaker, due to the absorption of the acid in the plate, which is forming lead sulphate. As this sulphate increases, the pores, through which the acid formally went through becomes clogged up. This of course stops the free action of the acid. Since the acid cannot get into the plates fast enough to keep the constant normal voltage, the battery loses its "pep." Now, when the plus and minus terminals of the battery are connected to a charging line, an action directly opposite to that which took place during the period of discharge will take place. That is, the acid is driven off the plates and added to the original electrolyte giving it its strength back again.

Therefore the sulphate is also driven off the plates and the pores of the plate are free to allow the current, when the charging ceases, to allow the current to reverse its action. Never during this complete period do we lose any of the acid. That is why every batteryman will tell you when buying a new battery, never to add acid. The only time when acid should be added, is when some acid has accidentally been spilt out or you find after charging a long while, the battery does not come back to its original state. However, always consult a battery man before doing this. You will also note that the hydrometer is always to be used as the voltage can be high, but the specific actual condition of the battery. A voltmeter is not a good testing device to use, as the voltage can be high, but the specific gravity of the acid can below. Usually, a specific gravity of 1150 is obtained and still the voltage is considerably high, about 5½. With this voltage the 6-volt tubes can still be operated, but the battery is in no condition to be used.

Another form of secondary cell is the Edison cell, which uses an alkaline electrolyte. It consists of a 21 per cent. solution of potassium hydrate mixed with a small amount of lithium hydrate. The active metals of this cell are nickel and iron, but are used in the form of nickel hydrate and iron oxide. The negative electrode consists of a nickel-plated steel grid. In the pockets of this grid are placed and hydraulically pressed, perforated corrugated steel pockets which have been filled and packed with iron oxide. A small amount of metallic mercury is added.

The positive electrode consists of a nickel-steel grid to which are secured

perforated steel tubes reinforced by steel seamless springs. These tubes are filled with alternate layers of nickel hydrate and very thin flaked nickel, firmly and carefully packed by a loading machine. The normally fully charged voltage of an Edison cell is 1.2. The cell is said to be discharged when the voltage has dropped to .9 volts. The following action takes place during the charge and discharge of an Edison cell: The first charging of an Edison cell reduces the iron oxide to metallic iron, while converting the nickel hydrate to a very high oxide, black in color. On discharge the metallic iron goes back to iron oxide and the high nickel oxide goes to a lower oxide, but not to its original form of green hydrate.

On every cycle thereafter the negative charges to metallic iron and discharges to iron oxide, while the positive charges to a high nickel oxide. Current passing in the direction of charge or discharge decomposes the potassium hydrate of the electrolyte. An amount of potassium hydrate equal to that decomposed is always reformed at one of the electrodes by a secondary chemical reaction. In consequence there is none of it lost, therefore keeping its density constant.

DEALERS BIG DISCOUNTS

Radio's biggest season is here. Get our new catalog showing huge stocks of radio parts sets, kits at lowest rock-bottom prices. Quick service. Wonderful special offer on best sets, etc., tubes, batteries. Write for free copy.

W. C. Braun Co., 32-60 So. Clinton St., Chicago, U. S. A.

IN RADIO WORLD'S HOOKUP NUMBER dated Nov. 7, appeared a 3-Tube Dry-Cell Circuit, by Capt. P. V. O'Rourke; Measuring Inter-Frequency, by J. E. Anderson; One of the Best Crystal Sets, by Herbert E. Hayden, etc. 15c per copy, or start your subscription with that number. RADIO WORLD, 145 W. 45th St., N. Y. C.

Are You the Man

to be first in your town to sell and demonstrate POWEROLA, the famous 5-tube, NO-BATTERY ELECTRICAL LIGHT SOCKET RADIO RECEIVER (one receiver) universal for D.C. or A.C. (1100-115 v., 40-60 cycle) now sold and demonstrated thru THE NEW YORK EDISON CO., public utility companies and radio, electric and music dealers everywhere. Absolutely dependable, fully guaranteed, powerful, practical, perfect in performance. Tested and endorsed by Popular Radio, Radio Broadcast, Radio News and all leading authorities and engineers of your local electric light company.

Are You the Man Who Sees Opportunities
Ahead for Real Money Making?

Write for literature, terms and prices at once.

You Too Can Make Powerola

Send \$1.00 for wiring diagrams showing how to re-wire any old or new parts, battery sets, or radio circuits (one to eight tubes), and power apparatus used, to operate satisfactorily from A.C. or D.C. Get in at once on wonderful and exclusive business. Thousands of homes are waiting for you now.

POWEROLA RADIO CORP.
Dept. R.W., 1845 Broadway, N. Y. City

TO NEWSDEALERS AND RADIO DEALERS

RADIO WORLD has made arrangements to supply the trade with
**BLUE PRINT AND SCHEMATIC
DIAGRAM
OF RADIO WORLD'S**

1926 Model Diamond of the Air

As designed by Herman Bernard

Questions answered free by RADIO WORLD.

This blue print and schematic diagram is for sale at retail for 50c. Write for discount.

Six copies of Radio World containing Mr. Bernard's complete article on this hookup will be sold to you at the regular dealer's price.

Order direct through this office.
Radio World, 145 W. 45th St., N. Y. City

CHANGES OF ADDRESS

should be sent to Subscription Department at least two weeks in advance of publication in order to insure early and proper attention. RADIO WORLD'S subscription list is so large that it is necessary that changes be sent in as requested. Address, Subscription Department, RADIO WORLD 145 W. 45th St., New York.

Streamline


The Faithful Servant

The Straight-Line Frequency Condenser of Unfailing Performance. Enables tuning from 175 to 560 meters.

Absolute Guarantee of Mechanical and Electrical Efficiency on Every Box!

.0005 mfd. \$2.50 .00035 mfd. \$2.25 .00025 mfd. \$2

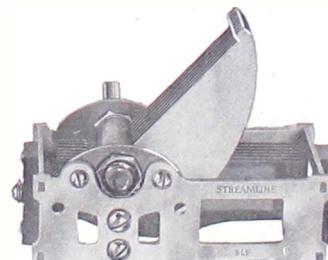(The Streamline is the condenser officially certified for use in RADIO WORLD'S 1926 Model Diamond of the Air.)



Moderate in Price, But Surpassing in Merit

Streamline Radio Co., 223 Fulton St., N. Y. City

Enclosed find \$..... for which send me by return mail Streamline SLF condensers, capacity

NAME

ADDRESS

CITY

STATE

**1926
RADIO
CATALOG
& LOG BOOK**

Get
Our 1926 Beautiful
Illustrated Catalog!

Which contains all latest
Standard Radio Merchandise
AT SLASHED PRICES!!

And Up-to-Date Log Book
IT WILL PAY YOU TO BUY FROM US. We
carry one of the largest lines of Radio in the East.
Don't miss this wonderful opportunity
to participate in this Great Sale.
Rush your request at once.
To cover the cost of mailing Enclose 10c.

ECONOMY RADIO SALES COMPANY
288 6th Ave. Dept. E New York
DEAL DIRECT AND SAVE REAL MONEY
(No Dealers)

STREAMLINE RADIO CO.
223 FULTON STREET
New York City

Diamond Trouble Shooting Discussed in Great Detail

(Continued from page 6)

source also exists in the audio hookup, which you will determine later.

Failure to connect the wires properly extends broadly from the receiver to the batteries and aerial system. To some extent this has been covered already, but the batteries have not been considered. Also,

it often happens that a fan, in the excitement attending the completion of a receiver, tries to get signals without aerial or ground being connected, or omits to connect the B battery. Hence see that the aerial and ground are connected. Sure of that, observe whether the B minus lead has been connected to the A battery (A plus is advisable). If battery cable is used, be sure that you have the high B voltage lead going to the amplifier tubes, and not to the detector tubes, hence try reversing these, for too high a B voltage on the detector, combined with the voltage intended for the detector being placed on the amplifier, may result in absence of signals.

Oscillation Trouble

Another source of no-signal trouble is over-oscillation. This should not be encountered, since the tickler coil is correctly designed and by rotating it it is possible to control oscillations over the entire wavelength band, both for the detector and the RF tubes. Although the tickler coil is primarily in the detector circuit, it is in the RF tube's circuit, also, because the primary of the 3-circuit coupler is connected to the plate of the RF tube, and because there is the common connection of circuits through the batteries.

For over-oscillation as the cause of signal failure, reduce the B plus voltage on the plate of the detector tube.

If oscillations are too strong only on the lower waves, remove turns from the tickler, or if regeneration fails on the higher waves, add turns to the tickler.

We are now in the sphere of trouble shooting that concerns reception of inferior variety, rather than total absence

of reception. If volume falls off perceptibly on the higher waves it is a sign that your aerial is not long enough. Due to the circuit design and the coil construction, the set will stand a long aerial. While a 100-foot aerial should be satisfactory, including leadin in that 100-foot stretch, under some conditions, due to peculiarities attending the location rather than the receiver, a longer aerial will be necessary, and it is safe to go up to an overall length of 200 feet, including leadin. The longer aerial may require more turns on the tickler, or, to gain the same tickler effect, you may place a .001 mfd. fixed condenser across the tickler coil.


It is only natural that the amplification should be somewhat less on the higher waves than on the lower ones, for this is true of all forms of tuned or untuned radio-frequency amplification except intermediate frequency.

After general satisfactory reception has



CONDENSERS
VERNIERS
RHEOSTATS

AMSCO PRODUCTS, Inc. New York City

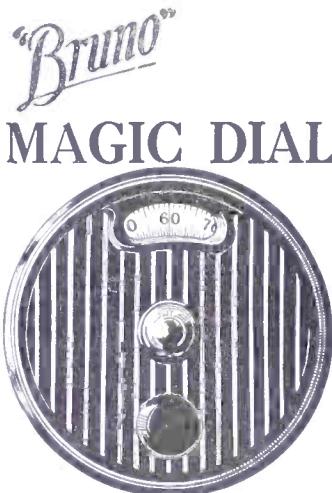

The Newest Wonder in Radio
Makes condensers that are not straight-line frequency tune as if they were. Moulded Bakelite. No gears, no back lash \$2.50

"Bruno Slo-Moshen" Vernier Dial, \$2

POWERTONE KIT

Complete Kit for 5-Tube, 1-Control "Bruno"
Power-tone; Drilled, Engraved Panel; Free Radio World Hookup. FREE CABINET... \$25.00

POWERTONE ELECTRIC CO.
Subsidiary of Bruno Radio Corp.
223 Fulton Street New York City

WE MAKE ANY SET WORK GREAT!

If your set does not bring in enough distant stations, is not selective or sensitive enough, or lacks volume or quality, we can remedy these shortcomings.

receivers and wavemeters calibrated.
Scientific research on all phases of radio reception.

Laboratory of John F. Rider
145 West 45th Street, New York City
Telephone: Bryant 2383

GEM TUBE

A Guaranteed Radio Tube
Within Reach of All

Every tube guaranteed. A tube for a dollar of \$2 value. A trial order will convince you as it has thousands of others. Send your orders at once.

Orders sent C.O.D. parcel post.

Type .199A

Type .199

Type .200

Type .201A

\$1.00

(with standard base) EACH

Dealers. Write for Discounts.

GEM TUBE CO.

Dept. W., 200 B'way., N. Y. C.
220 So. State St., Chicago, Ill.
Lafayette Bldg., Detroit, Mich.



22½ volt
rechargeable
"B"
Storage
Battery

\$2.95

includes
chemical



45 volts, \$5.25; 90 volts, \$10.00; 112½ volts, \$12.50; 135 volts, \$14.75; 157½ volts, \$16.80. Truly, the biggest buy today. Easily charged by current, including 32-volt systems. Avg. special detector plate voltage had. Tested and approved by leading authorities such as Popular Radio Laboratories. Over 3 years sold at a non-red tape, 30-day trial offer with complete refund if not thoroughly satisfied. Further guaranteed 2 years. Knock-down kits at great savings. Complete "Hawley" "B" battery charger, \$2.75. Sample cell, 35c. Order direct—send money and simply pay the expressman cost on delivery. Or write for my free literature, testimonials and guarantees. Same day shipments. B. Hawley Smith, 318 Washington Ave., Danbury, Conn.

RADIO
WORLD'S

PREMIUM SUBSCRIPTION OFFER

For NEW RADIO WORLD Subscribers Ordering NOW

Radio World has made arrangements

—To offer a year's subscription FREE for

any one of the following publications

with one year's subscription for RADIO WORLD:

—RADIO NEWS or

—POPULAR RADIO or

—RADIO BROADCAST or

—SCIENCE AND INVENTION or

—BOYS' LIFE or

—RADIO DEALER or

—RADIO JOURNAL or

—RADIO (San Francisco) or

—THE EXPERIMENTER or

—RADIO AGE or

—COLLIER'S

This is the way to get two publications

—for the price of one:

—Send \$6.00 today for RADIO WORLD

—for one year (regular price

—for \$2 numbers)

—and select any one of the other

—eleven publications for twelve months.

—Add \$1.00 a year extra for

—Canadian or Foreign Postage.

—Present RADIO WORLD subscribers

—can take advantage of this offer by

—extending subscriptions one year

—if they send renewals NOW.

RADIO WORLD'S SPECIAL TWO-FOR-PRICE-OF-ONE SUBSCRIPTION BLANK

RADIO WORLD, 145 West 45th Street, New York City.

Enclosed find \$6.00 for which send me RADIO WORLD for twelve months (\$2 numbers), beginning and also without additional cost, Radio Broadcast, or Popular Radio, or Radio News, or Science and Invention, or Radio Dealer, or Radio (San Francisco), or The Experimenter, or Radio Journal, or Radio Age, or Boys' Life, or Collier's (or \$10.00 for two yearly subscriptions).

Indicate if renewal.

Offer Good Until

February 10, 1926

Name

Street and Address.....

City and State.....

Good Back Numbers of RADIO WORLD

The following illustrated articles have appeared in recent issues of RADIO WORLD:

- 1925:
- July 4—The Handsome Portable, by Herbert E. Hayden. The Freedom Reflex, by Capt. P. V. O'Rourke. 3-Tube Super-Heterodyne, by Abner J. Gejula.
 - July 11—The Baby "Super," by J. E. Anderson. A 1-Dial Portable Receiver, by Capt. P. V. O'Rourke.
 - July 18—Anderson's 6-Tube Super-Heterodyne. The 3-Tube Marconi Receiver, by Percy Warren. A Good Battery Connector, by Herbert E. Hayden.
 - Aug. 1—Enormous Volume on DX Stations, by Sidney E. Finkelstein. The Metropolitan Local Set, by J. E. Anderson. A 2-Tube DX Divider Circuit, by Herbert E. Hayden. Series and Parallel Effects, by Herman Bernard.
 - Aug. 8—The Evolution Reflex, by Capt. P. V. O'Rourke. The Midget—A 3-Tube Set in Sewing Machine Cabinet, by Herbert E. Hayden. How to Build Your First Set, by Herman Bernard. 2-Year-Old Wins DX Stake, by Lewis Winner.
 - Aug. 15—2-Tube Speaker Refit, by Brewster Low. Capt. P. V. O'Rourke's Favorite Audio Amplifier. Set That Taxes Ingenuity, by Lewis Winner. The Loop Jack in The Diamond, by Herman Bernard.
 - Aug. 22—The 5-Tube Diamond, by Sidney E. Finkelstein. A Home-Made Toroidal Coil, by George R. Hostetter. The Electrostatic Regenerator, by Percy Warren. Crystal Sets That You Can Use, by Herman Bernard.
 - Aug. 29—Using 1-Dial Portions, by Herman Bernard. A Simple Baby Can Build, by Herbert E. Hayden. A Fine Meter Switchboard, by Lewis Winner. A Powerful 1-Tube Set, by Percy Warren.
 - Sept. 12—The 1926 Model Diamond of the Air, (Part 1), by Herman Bernard. An Oscillating Wavemeter, by J. E. Anderson. A 25-to-110 Meter Receiver, by Sidney E. Finkelstein.
 - Sept. 19—Diamond of the Air, (Part 2), by Herman Bernard. A 1-Dial 2-Tube Speaker Set, by Percy Warren. A Tube B Battery Eliminator, by Lewis Winner. A Home-Made Volume Control, by Herman Bernard.
 - Sept. 26—The 8-Tube Super-Heterodyne, by Sidney E. Finkelstein. Diamond of the Air (Part 3), by Herman Bernard. The 5-Tube Brown-Inductor Crystal, by Capt. P. V. O'Rourke. A 1-Control Regenerator Set, by Percy Warren.
 - Oct. 3—The Thordarson-Wade Set, (Part 1), by Herman Bernard. A Fired Grid Leak, by Herbert E. Hayden. Trouble Shooting for Diamond of the Air.
 - Oct. 10—Hookup for the Short Waves, by Percy Warren. The 3-Tube, 3-Circuit Tuner, by Capt. P. V. O'Rourke. The DX Set That Thrilled Jack, by Lewis Winner. The Thordarson-Wade Set (Part 3), by Herman Bernard.
 - Oct. 17—The Thoroughbred (1-Tube DX Set), by Herbert Hayden. O'Rourke's Favorite SW Set, by Capt. Peter V. O'Rourke. The Thordarson-Wade Set (Part 3), by Herman Bernard. Trouble Shooting Article.
 - Oct. 24—The 3-In-1 RF Receiver, by Sidney Finkelstein. Phonograph Cabinet Set, by Lewis Winner. The Thoroughbred, by Herbert Hayden (Part 2).
 - Oct. 31—The Pathfinder, by Sidney E. Finkelstein. A Snap-Catch Terminal Strip, by Herbert Erwin. A Simple Loop, by Herbert E. Hayden.
 - Nov. 7—A 3-Tube Dry-Cell Circuit, by Capt. P. V. O'Rourke. One of the Best Crystal Sets, by Herbert E. Hayden. 3-Tube DX Set, by Herman Bernard. Flexible Short-Wave Set, by Percy Warren. The 4-Tube Roberts Receiver, by Neal Fitzalan.
 - Nov. 14—The 4-Tube DX Special, by Herbert E. Hayden. The Set That Water Louderend, by Capt. P. V. O'Rourke. A Receiver for Music Lovers, by Lewis Winner.
 - Nov. 21—A 1-Tube DX Super-Heterodyne, by J. E. Anderson. A Resistance-Controlled Set, by Percy Warren. A 4-Tube A-A Receiver, by Herman E. Hayden.
 - Nov. 28—The Zero Potential Loop, by Frank Freer. The 1-Tube Headset Receiver, by J. E. Anderson.
 - Dec. 5—A Toroid RF Set, Using Crystal, by Lewis Winner. A 70-to-1208 Meter Receiver, by Robert Force. The Diamond of the Air (in Text and Diagram), by Herman Bernard.
 - Dec. 12—A Self-Contained Receiver, by H. E. Hayden (Part 1). B Battery Eliminator, by Lewis Winner (Holiday Gift No.).
 - Dec. 19—The Lemnai Entertainer, by Ed. Spleger. Feldman 5-Tube Set, by Lewis W. Feldman.
 - Dec. 26—The Regenerative Wave Trap, by John F. Rider. The 5-Tube Tuned RF Set, by Capt. P. V. O'Rourke.

- 1926:
- Jan. 2—The 2-C Set for Simplicity, by Capt. P. V. O'Rourke.
 - Jan. 9—The 4-Tube DX Symphony Set, by A. Irving Witz. A Skillfully Made 1-Dial Set, by Herman Bernard.

Any copy, 15¢. Any 2 copies, \$1.00. All these 28 copies for \$3.50, or start subscription with any issue. Radio World, 145 W. 45th St., N. Y.

(Continued from preceding page)

been enjoyed, yet several unsuccessful attempts have been made to receive distant stations, constructors begin to read over results letters to make sure that it is true others got great distance with the same hookup. The problem is what to do to bring in DX on the receiver that seemingly refuses to do this. First make sure that your locality is not at fault, as there are some few places where it is virtually impossible to get distance on any set. You will know quite readily whether this is true in your instance, as you will have tried other sets, and will know what neighbors' experiences have been. Be sure that conditions have not changed since you made tests with another set, such as a big steel building having reared its head and shoulders above your low roof.

Waiving aside location trouble, for which there is no remedy save to move, to try to get distance where it has failed you, resort to the following:

1. Try other tubes in the radio side, i.e., for RF amplifier and detector. This is of general importance, concerning not only distance but local reception, for the object is to have the best radio amplifier in the first tube, and the best detector in the second socket, apportioning the remaining tubes to the audio side as best they serve.

Lengthen the aerial. Use up to 200 feet. The failure to receive distance

may be due not to the fact that the receiver is not sensitive enough to pick it up, but that the incoming impulses are too weak to be made audible by the audio amplifying part of the set, hence instead of mere AF, use the longer aerial, which affords greater signal strength and better possibility of hearing distant stations.

3. Experiment with the coil location. Tilt the RF coil at a different angle than the one at which it is placed, as that is not panel mounted and is the easier one to shift. Stray magnetic feedback

(Concluded on next page)




MAGNATRONS in your set will give sweet purity of tone—clear and complete rendition of all the wealth of overtones. Music and speech come from the loudspeaker of the Magnatron equipped set with rich fidelity and generous volume, recreating in your home the actual performance itself, whether it be ten or a thousand miles away.

Magnatrons are the product of the oldest exclusive makers of vacuum tubes. That, in a large measure, explains their excellence. There's a Magnatron for every purpose. The DC-201A, the DC-199 [large or small base], the DC-120 [for super volume], and the Rex [for B Eliminators]. All list for only \$2.50 each.

Write for your FREE copy of "Pot Pourri"—a snappy review of mirth and music to Department RW

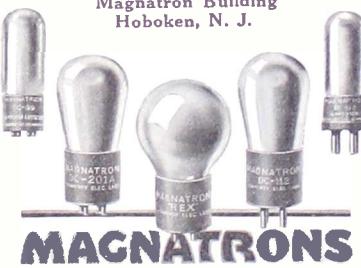CONNEWEY ELECTRIC LABS.
Magnatron Building
Hoboken, N. J.



Complete factory stock for Pacific Coast carried at Pacific Radio Labs., 256 So. Los Angeles St., Los Angeles, Cal.

FILL OUT AND MAIL NOW
SUBSCRIPTION BLANK

RADIO WORLD

RADIO WORLD

145 West 45th Street, New York City
(Just East of Broadway)

Please send me RADIO WORLD for months, for which

please find enclosed \$.....

SUBSCRIPTION RATES

Single Copy	\$.15
Three Months	1.50
Six Months	3.00
One Year, 52 Issues	6.00
Add \$1.00 a Year for Foreign Postage; 50¢ for Canadian Postage.	

(Concluded from preceding page)
will injure DX possibilities very seriously, so avoid that by all means.

4. Put a fixed condenser, about .001 mfd. between the plate of the RF tube and A minus. Be sure that this condenser is not shorted, for if it is the B battery voltage will be delivered to the tube filaments and good-bye tubes. Do not include this .001 mfd. condenser unless

SHORE FOR CHOKE COILS & TRANSFORMERS

For All "B"
Eliminators

PRICES ON REQUEST

SHORE ELECTRIC CO., Inc.
64 University Place N. Y. City

BEAUTY-QUALITY-LOW PRICE

TYPE 555	
5-Tube Tened Radio Frequency.	\$45
TYPE 6RR	
6-Tube Resistance Coupled Audio Tuned	\$50
Radio Frequency	
If your dealer cannot make immediate delivery we will ship direct from factory	

American Interstate Radio Service
183 Greenwich Street, New York City
Distributors, Jobbers, Dealers, write for special trade terms.


FREE!

Our Latest 100 Page
RADIO CATALOG

BEFORE you build be sure to consult our latest 100-page radio catalog. A dependable guide for set-builders. Knock-down sets and kits for all the latest circuits. No finer or more complete assortment to be found anywhere. Latest designed parts—Amer. All-American, Brainer-Tully, Carter, Freshman, Frost, General Instrument, Wallert, etc. And the prices—every one quoted means a big saving for you!

Write for your FREE copy today!

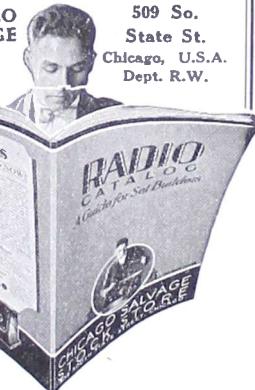CHICAGO SALVAGE STOCK STORE
509 So. State St. Chicago, U.S.A. Dept. R.W.



LIST OF PARTS

One RF coil, L1L2 (Bruno 55 or 99RF).
One 3-circuit tuning coil, L3L4L5 (Bruno 99).
Two SLF .0005 mfd. variable condensers, C1, C2.
One 2-meg. grid leak, R3.
One .00025 mfd. grid condenser, C3.
Two audio transformers, PBGF.
Two 10-ohm rheostats, R1, R2.
One double jack, J1.
One single jack, J2.
Three 4" dials (if condensers are not SLF at least two dials should be).
Battery cable.
One 7x24" panel.
One 7x23" baseboard, or 2½x23" socket shelf, with brackets.

found necessary, as the construction of a considerable number of experimental models of this receiver has proven the unlikelihood of its necessity or desirability.

5. As a last resort, put more turns on the primary of the interstage coupler, even reducing the coupling, if necessary, so that the primary of this 3-circuit coil is right alongside of the secondary, with no spacing between. This will transfer more energy, although slightly reducing selectivity.

6. Experiment with the B plus voltages. Test your B batteries with a high-resistance voltmeter, and see that the A battery is sufficiently strong. If the

batteries are all right, increase the RF tube B plus voltage, even up to 135, while the detector tube may be given experimental plate voltages from 16½ to 45.

7. Put another leak in the set. The wrong value of leak may prevent distant reception. If you do not know what value to use, you can not tell except by the cut and try method, so you may use a variable grid leak, such as the Brewood, to be sure of getting this point settled. Normally the —01A tube requires from 2 to 5 megohms, and this means that if a fixed leak is to be used you should be prepared to try out several, say 2, 3, 4 and 5 megohms. The —99 tube requires somewhat higher grid leak resistors than does the —01A. Also remember that any change in the grid leak may require some adjustment of the B plus voltage of the detector tube.

8. As a final attempt, change the grid return of the detector from plus to minus A. This is contrary to the accepted way of hooking up a detector tube, but in some few instances better results will be obtained, due to the peculiarities of an individual tube. A detector tube, of course, is an amplifier, too, and perhaps by operating your particular detector tube on the best amplification part of the curve you will get better results. There may be some drop in stability at the expense of added sensitivity.

CROSLEY

ILLUSTRATED RADIO CATALOG FREE!
Describes fully the complete Crosley line of radio frequency sets, regenerative sets (licensed under Armstrong U. S. Patent No. 1,113,149) and parts.
THE CROSLEY RADIO CORPORATION
Cincinnati, Ohio

RADIO

BLUE PRINT FOR 1926

Diamond of the Air

A blue print for wiring the circuit that has swept the country may be obtained by sending 50¢ in stamps, money order, cash or check. This blue print is full size and is personally certified by Herman Bernard.

RADIO DIVISION
THE COLUMBIA PRINT
145 West 45th Street New York City



Buy Direct From
Factory, LANES
Guaranteed \$12.50
Products Cash or
C.O.D.

Now, by our method of direct dealing, we actually save you the dealer's discount and give you two powerful, all-class, handsome looking products each in \$12.50 and equal to any at 3 times the cost.
100 Volts Storage B BATTERY
NON-ACID—Wonderful Reception
78 Cells—Wonderful Reception
B ELIMINATOR Best for Sets
Works from either A. C. or D. C.
Each regularly sold for \$25. Now \$12.50

Greatest values. Finest reception.
lowest upkeep costs. We offer
steel crystal case with rubber
foot. We guarantee no disappointments.
Mail your order today.



Lane Mfg. Co.
2941 West Lake Street
Chicago

RADIO WORLD'S QUICK-ACTION CLASSIFIED ADS.

10 Cents a Word. 10 Words Minimum. Cash With Order.

RADIOLA III, \$17.00; TRIRDYN, \$32.00; SUPER-DYNE, \$48.00. Lowest prices on kits. F. J. Terry, Broadalbin, N. Y.

SALESMEN!

MAKE \$100 WEEKLY IN SPARE TIME. Sell what the public wants—long-distance radio receiving sets. Two sales weekly pay \$100 profit. No big investment, no canvassing. Sharpe of Colorado made \$965 in one month. Representatives wanted at once. This plan is sweeping the country—write today before your county is gone. Ozarka, Inc., 126-J, Austin Ave., Chicago, Ill.

THE RESULT OF EXPERIMENTING, IS A SUPER-HET astounding the world. Non-regenerative, no oscillations. Send stamp for free print. Box 32, Station C, Toledo, Ohio.

BULLDOGS BEAUTIFUL REGISTERED BULL PUPS, \$15. Bulldogs, 501 Rockwood, Dallas, Texas.

SELL FIVE-TUBE RADIO SETS. Thirty days free trial. Three sales weekly pays \$90 profit. Experience unnecessary. DIRECT RADIO, 197-D, Fourteenth, Milwaukee, Wis.

SILVER-GILT! THE NEW BUS-WIRE. Silver plate on copper with a light cover plate of gold to prevent tarnish. Low loss, high conductivity, handsome appearance. Price 4¢ per foot, cash or money order. 10 feet C. O. D., 55c. J. A. ARMSTRONG, 124 Pleasant St., Attleboro, Mass.

1926 DIAMOND OF THE AIR. Completely constructed and tested sets in beautiful mahogany cabinet, \$50.00. B. Benson, Orchard Park, N. Y.

MAKE YOUR OWN CONE SPEAKER—Powerful unit, two dollars. Send money order, Box 32, Station C, Toledo, Ohio.

DX SUPER-HETERODYNE, by J. E. Anderson, appeared in RADIO WORLD dated Nov. 21. Sent on receipt of 15¢, or start your subscription with that number. RADIO WORLD, 145 W. 45th St., New York City.

HELP WANTED MALE

EARN \$110 to \$250 monthly, expenses paid as Railway Traffic Inspector. We secure position for you after completion of 3 months' home study course or money refunded. Excellent opportunities. Write for Free Booklet, G-161 Stand. Business Training Inst., Buffalo, N. Y.

KEEP AWARE OF THE LATEST
RADIO DEVELOPMENTS
RADIO WORLD
145 WEST 45th ST. NEW YORK CITY

8 Weeks' Trial Subscription, \$1.00

TEAR OFF AND MAIL TODAY

Thousands of Cooking Students Are Graduated in Our Homes

The other day thousands of women throughout the United States were graduated from a unique school. In place of the usual cap and gown, these graduates wore ordinary house dresses and possibly also kitchen aprons. They received their diplomas not in any college auditorium but in their own homes and instead of having their sheepskins handed to them by some dignified college or university official they received them by radio. The graduates were those who completed the work and passed satisfactory examinations in the Betty Crocker radio cooking school broadcast by the following stations: WHT, Chicago, Ill.; KFI, Los Angeles, Calif.; WFI, Philadelphia, Pa.; WEI, Boston, Mass.; KSD, St. Louis,

Mo.; WEAF, New York, N. Y.; WCAE, Pittsburgh, Pa.; WGR, Buffalo, N. Y.; WEAR, Cleveland, Ohio; WWJ, Detroit, Mich.; WDAF, Kansas City, Mo.; and the Gold Medal Station, Saint Paul-Minneapolis, WCCO.

This cooking school had many thousands of members all over the United States, ranging in age from 14 to 90 years. It was a special feature of the home service talks broadcast by Betty Crocker from these twelve stations three times each week. For six weeks the Friday morning broadcasts in this series were devoted to the cooking lessons. Any woman who cared to enroll might do so without any charge or fee whatever.

Graduation in the school was dependent

upon preparing and reporting on a certain number of recipes as prescribed by Betty Crocker. A large percentage of the women who enrolled qualified for graduation, it was said, including one 80-year-old student who wrote to Betty Crocker and pleaded that she please be allowed to graduate as she had tried so hard and she had never graduated from anything before in her life. She received a diploma.

The graduation exercises consisted of a special talk to the members of the school by Betty Crocker from the twelve stations, and appropriate musical features. Later each graduate received a diploma by mail.

It is believed that this radio cooking school was probably the largest cookery class in history. It opened on November 6, and the final lesson was broadcast on December 18.

The school was the first of three of its kind scheduled to be broadcast by these twelve stations in 1925 and 1926. The second will open on January 29.

*None Better for—Distance and Quality of Tone
than the boxed and sealed 1926*

DIAMOND OF THE AIR KIT—\$35.00

(WITH OFFICIAL BLUEPRINT)

The Fastest Selling Kit on the Market Today. There Is a Reason!



"Bruno 55" matched radio frequency coil for \$99 and used in the Diamond of the Air. \$3.00



"Bruno 99" 3-circuit tuner wound on quartzite glass and specified in the Diamond of the Air. \$5.50



B-C-L Vernier Dial, 20-1 Ratio, 4-inch, Black Face, \$99; Silver Face with Black embossing, 69c.



"It Has a Soul for Music"

We are now able to furnish our patrons with the kit to build the famous Powertone set at this very low price, \$25, Cabinet Free!

DUBILIER BY-PASS CONDENSERS



OUR NEW PRICES
1 MFD.....\$0.25
.25 MFD.....\$.70
.5 MFD.....\$5.00
1 MFD.....\$.90
2 MFD.....\$1.75
4 MFD.....\$3.00

KITS	
Bruno 3-Tube.....	\$18.50
Bruno 4-Tube.....	22.50
Ambassador 3-Tube.....	16.50
Ambassador 4-Tube.....	20.50
Browning Drake.....	19.50
Freshman T. R. F.....	7.95

SETS

Write for our prices on any manufactured set. We have a complete supply, ready for immediate shipment.

CONDENSERS

Bruno No. 18-22 Plate....	\$4.50
Hammarlund 23 P. S. L. F.	4.25
Hammarlund 11-43 Plate Ver.	2.35
General Instrument, Any Size.....	2.40
U. S. Tool — 11-18-23-43 Plate Ver.	1.95
Heath 11-23-43 Plate Ver.	1.95
Murdock Closed 23-43 Plate95
U. S. L. 23-43 Plate Ver.	1.65
Preferred 11-23 Plate....	1.35
Preferred 11-23 Plate Ver.	1.65
General Radio 23 Plate....	2.95
General Radio 11-23 Plate Ver.	3.75
Amsco 17 Plate S. L. F.	2.75
Amsco 23 Plate S. L. F.	3.25
King Cardwell 11-23 Plate.	2.50
Freshman Mercury.95
Manhattan 17-22 Plate Ver.	2.95
Pacent 11-43 Plate.75

TRANSFORMERS

All American 10 to 1.....	\$2.45
Jefferson Star.....	1.50
American.....	3.75
Modern 4 to 1.....	2.75
Modern 10 to 1.....	2.95
Modern Push Pull, per pair	6.50
Thordarson 3 to 1.....	2.95
Thordarson 6 to 1.....	3.10
Thordarson Push Pull, pair	8.50
Thordarson Autoformer.....	3.75
Erla 3 to 1, 6 to 1.....	2.95
Federal No. 65 or 65A.....	2.95
Rauland Lyric.....	6.95

VERNIER DIALS

Marco.....	\$1.65
Erla.....	1.95
Amsco.....	1.50
Universier.....	.75
Gee-Haw.....	2.25
B. M. S.	1.10
Accurateone.....	2.75

LOUD SPEAKER UNITS

Baldwin (Type C).....	\$3.95
Baldwin (Type H).....	4.95
Morrison.....	3.25
Western Electric.....	6.75
Tower Scientific.....	3.95

LOUD SPEAKERS

Brandes Table Talker.....	\$4.50
Farrand Jr.	16.50
Jewett Super.....	19.50

MANHATTAN LARGE

Acme.....	\$11.50
Bezel Sr.	22.50
Thorala Sr.	14.50
Fitlas.....	7.50
Magnavox M4.....	10.95

TUBES

R. C. A. 201-A.....	\$2.25
Cunningham.....	2.25
DeForest.....	2.25
New Venus Blue, 201-A.....	1.50
Schickerling.....	2.25

MISCELLANEOUS

Cutler-Hammer 6-ohm Ver.	\$0.65
Turn-It Grid Leak.....	.75
U. X. Adapter.....	.30
Federal Socket.....	.65
Pacent Plug.....	.25
Soldering Iron.....	.95
"A" Battery Switch.....	.25
Jones Single and Double Jacks.....	.40
Na-alad De Luxe Socket.....	.45
Bruno Binding Post (per pckg. of 12).....	.40
Lightning Arrester.....	.50
Battery Cable.....	.45
Pacent Rheostat.....	.60
Dubilier By-Pass Con., 0.25 mfd.....	.75
D. P. D. T. Switches.....	.50
S. P. D. T. Switches.....	.45
W. L.-11 Adapters.....	.50

PHONE PLUGS

Triple Standard Sockets.....	1.00
Bezel 1" Nickel.....	.05
Bezel 1" Brass.....	.10
Glass Insulator.....	.20
Toggle Switch.....	.20

Bruno Inductance Switch (14 Point).....

.35

Bruno "66"

.225

Hydrometers

.65

Bell Wire (Half Pound).....

.40

Na-alad UX Adapters.....

.35

Aerial Kit (Complete).....

2.50

Crystal Detector.....

.65

Double Jacks.....

.40

Single Jacks.....

.30

Westinghouse R. C. Set (2 only).....

29.50

Neutralizing Cond.....

.35

HARD RUBBER PANELS

7x10.....	\$0.50
7x12.....	.60
7x14.....	.75
7x18.....	.95
7x21.....	1.25
7x24.....	1.35
7x26.....	1.50

Drilled and Engraved for

Diamond of the Air.....

2.65

Powertone, 7x18, Drilled and

Engraved Panel.....

2.15

3-Tube Bruno, 7x18, Drilled

and Engraved Panel.....

1.45

OFFICIAL BLUE PRINTS OF THE DIAMOND OF THE AIR, 50c

WRITE FOR FREE CATALOGUE!


B-C-L RADIO SERVICE CO., 221 FULTON ST., NEW YORK CITY, N. Y.

This Knob Brings in DX

A delightful expression of appreciation lights every countenance when the Bretwood Variable Grid Leak is put in a set and the result is judged *by your own ears!*

The Bretwood Variable Grid Leak may be used in any set employing a tube as detector. The single hole, panel mount enables one to put it in a set in five minutes.

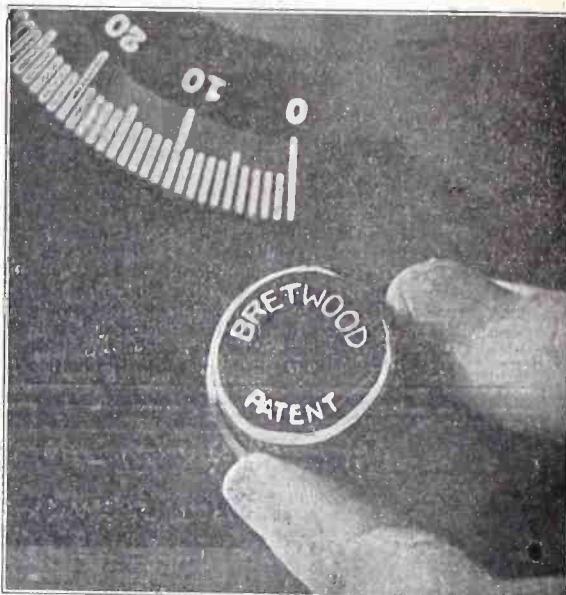*When the King Wanted a Leak He
Commanded Bretwood*



"Send Me Another BRETWOOD Variable Grid Leak

I received the Bretwood Variable Grid Leak last night and it sure did bring in stations. Denver was as far as I could get until last night when, with the Bretwood in my set, I brought in KFI, Los Angeles, and KPO, San Francisco, Calif., clear and fine.

JOS. L. MAIRE,
4026 Grezelia St.,
Pittsburgh, Pa.

I thank you for your letter in relation to the condenser. If this is as good as the Bretwood grid leak, I sure can wait. With your grid leak I was able to bring in with good volume 15 W Stations in one week with a Diamond of the Air set from a city hard to get out of.

Thanking you again,

R. W. Collingwood,
3442 Sacramento St.,
San Francisco, Calif.

Gridleak received and tested out, and find it is the only variable leak I ever used that is really variable.

Enclosed find \$1.50 for which please send me another one.

F. E. STAYTON,
Box 240, Ardmore, Okla.

I think it is about the best grid leak I have ever used. Have made quite a few sets and this beats them all. Get DX very plainly and clearly.

WM. HEBERSON,
2510 N. Franklin St.,
Philadelphia, Pa.

Fit for
a King



$\frac{1}{4}$ to 10
Megohms

Bretwood, Ltd., London, Eng., Sole Patentees and Owners

More DX, Clearer Reception, Smoother Control in Regenerative Sets Assured Price, \$1.50

The Bretwood Variable Grid Leak may be installed in any set in five minutes by single hole panel mounting.

The North American Bretwood Co., 145 W. 45th St., N. Y. City

Sole Distributors for United States

Canadian Representative, Radio, Ltd., Phillips Square, Montreal

NOTE TO RADIO MANUFACTURERS

Write for Wholesale Rates

A set with a FIXED Grid Leak may work perfectly where tested, while it needs a VARIABLE Grid Leak so that set may be adjusted to the locality where used.

THE NORTH AMERICAN BRETWOOD CO., 145 West 45th Street, New York City.

Gentlemen: Enclosed find \$1.50 for which you will please send me one Bretwood Variable Grid Leak prepaid. Satisfaction guaranteed or my money back after trial within ten days of receipt by me.

NAME
STREET CITY
STATE