

COMPLETE LIST OF STATIONS

RADIO

REG. U.S. PAT. OFF.

WORLD

America's First and Only National Radio Weekly

A 3-TUBE LOOP PORTABLE


How to Measure Antenna Capacity

Hookup for AC Tubes

AUGUST 6

15 CENTS

THE 4-TUBE CASH BOX UNITUNE

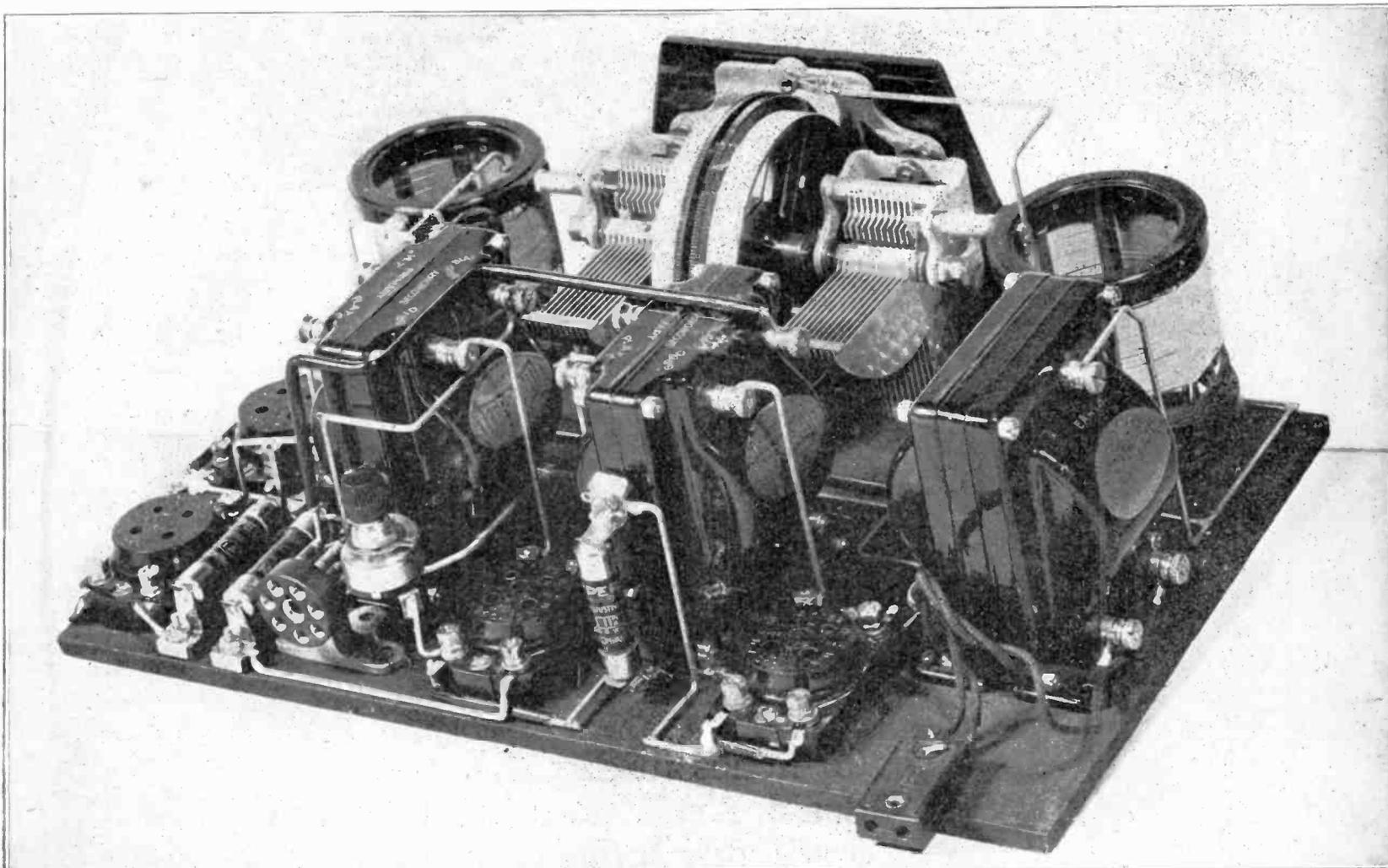

Back view of the Cash Box Set. See article on page 6.

INTERFERENCE

of the Image Variety in Super-Heterodynes

PUSH-PULL OUTPUT

Without Using Coupling Condensers

ARBOR SPEAKER

That You Stick in Garden Soil

THE TOTO WELL

Omits All Batteries, Adds AF

A Great Deal for a Very Little!

Ordinarily This Seems Too Good to Be True, But Here Is An Instance of Complete Verification



The New De Luxe Model Bretwood With Condenser Attached

WHEN you are deciding on what parts are to go into the receiver you are about to build, under no circumstances dismiss the grid leak with only casual consideration. Respect the grid leak as something well worthy of expert choice.

The best course is to select a variable grid leak with an ample resistance range, one that may be mounted on baseboard, sub-panel or front panel, as you prefer.

Such a leak is the **BRETWOOD VARIABLE GRID LEAK**, which is now on the market in new de luxe model, representing improvements in mechanical strength, electrical efficiency and utility.

Higher Efficiency

You should use a variable grid leak like the **North American Bretwood Co., 145 West 45th Street, New York City.**

Gentlemen: Enclosed find \$1.75. Send me at once one De Luxe Model Bretwood Variable Grid Leak on 5-day money-back guarantee. (Or \$2.25 for leak with grid condenser attached.)

NAME
 ADDRESS
 CITYSTATE.....

Inquiries Solicited from the Trade

BRETWOOD VARIABLE GRID LEAK in a set you are about to build, or should put one in your present receiver, because it will enable you to get highest operating efficiency from the detector tube. As nearly all tubes used as detectors draw grid current, the resistance value of the leak is important for biasing and discharge purposes. Not only can exactly the right degree of flow be established to discard excess electrons, but the grid-to-filament impedance is so affected as to afford best selectivity under the circumstances. Only a variable leak gives this precision choice.

You prevent overloading of the detector tube by correct leak setting. This improves tone quality considerably. Often if your set sounds distorted, this is immediately and permanently remedied. Hence you reap greater volume, better selectivity and purer tone quality—all by the simple insertion of a **BRETWOOD DE LUXE MODEL VARIABLE GRID LEAK**.

Selected by Bernard

This efficient instrument so struck Herman Bernard that he prescribed it for his latest and most popular circuit, Radio World's Universal Four-Tube Receiver.


The **BRETWOOD DE LUXE MODEL VARIABLE GRID LEAK** costs \$1.75—a small enough price for so much efficiency. If desired, a .00025 mfd. **BRETWOOD BULLET CONDENSER** is supplied, mounted on the leak, at 50 cents extra.

Note: The Bretwood Leak's range is .25 to 10 meg.

Dealers: Send in your orders direct!

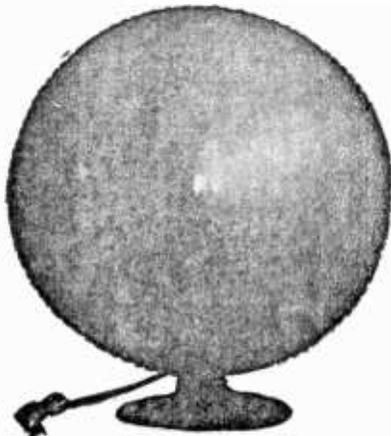B. S. T. CONE SPEAKER

Guaranteed to give Satisfaction in
 Tone, Volume and Appearance
 Adjustable to Volume Desired



18 inches in diameter edged in Gold Braid, Art Metal Base can be placed on highly polished surface without danger of scratching.

Immediate Delivery

\$7.50

Shipped Direct from Factory

Satisfaction Guaranteed or Money Back

GUARANTY RADIO GOODS CO.

145 West 45th St., New York

RADIO WORLD


Vol. XI
No. 20
Whole No. 280
August 6, 1927
15c Per Copy. \$6.00 Per Year

A Weekly Paper Published by Hennessy Radio Publications Corporation
from Publication Office, 145 W. 45th
Street, New York, N. Y.

Phones: BRyant 0558 and 0559

[Entered as second-class matter, March, 1922, at the post office at New York, N. Y., under Act of March, 1879]

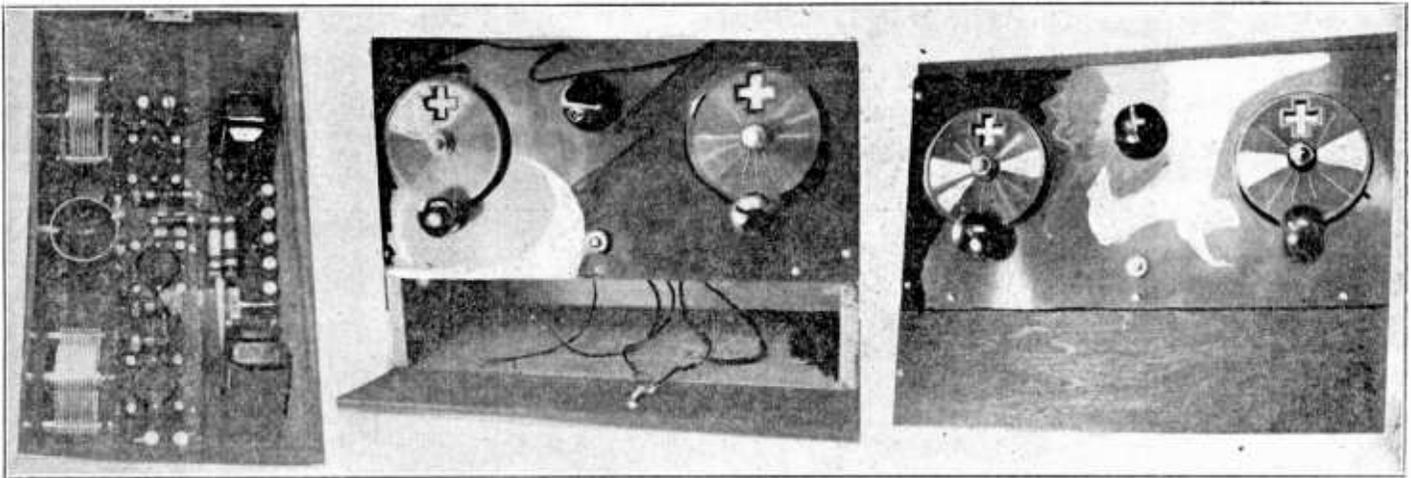A Portable with Novel Speaker Sounding Board is at Rear Cabinet Wall By Michael J. O'Reilly



AT LEFT is shown the layout of the baseboard of the self-contained three-tube reflex portable. The middle photo shows the panel layout and the battery compartment under the set proper. At right is shown the front of the set with the battery compartment closed. Lights and shadows, falling upon the front panel, produced a quaint chiaroscuro effect.

AN important consideration in the construction of a portable receiver is light weight. The lightest possible parts should be used throughout provided that lightness is not gained at a sacrifice of sensitivity and quality. In such a receiver it is also desirable to use as few parts as possible for a given degree of sensitivity.

In view of these requirements the reflex principle, if properly applied, is valuable, as it makes possible discarding one tube without sacrificing any in the sensitivity. With three tubes a receiver having a stage of radio frequency, a regenerative detector and two stages of transformer coupled audio can be built. This represents a popular circuit for home constructors, as it combines sensitivity, volume and low cost.

Let us start the description of the receiver with the loop L. Since the receiver is self-contained, the loop is mounted on the lid of the box containing the set, and the lid is hinged to the box so that it can be placed in a vertical position for use. The size of the lid is $8\frac{1}{2}$ by 14 inches. The loop frame is made of two dowels $14\frac{3}{4}$ inches long and $\frac{3}{8}$ inches in diameter placed diagonally on the lid of the box. The ends of the dowels are slit to a depth of $1\frac{1}{2}$ inches and the wire is placed in these recesses. A total of 19 turns of so-called loop wire is used for a .00025 mfd. condenser. The number of turns in any case would depend on the capacity of the condenser connected across the loop as well as on the value of the distributed capacity.

The tuned loop circuit feeds the radio frequency signal into the first 99 type tube. This tube is also the first audio frequency amplifier and consequently the secondary of the first audio frequency transformer is connected in series with the LC1 tuned circuit.

Between the first tube and the detector is the three circuit tuner L1L2L3, the

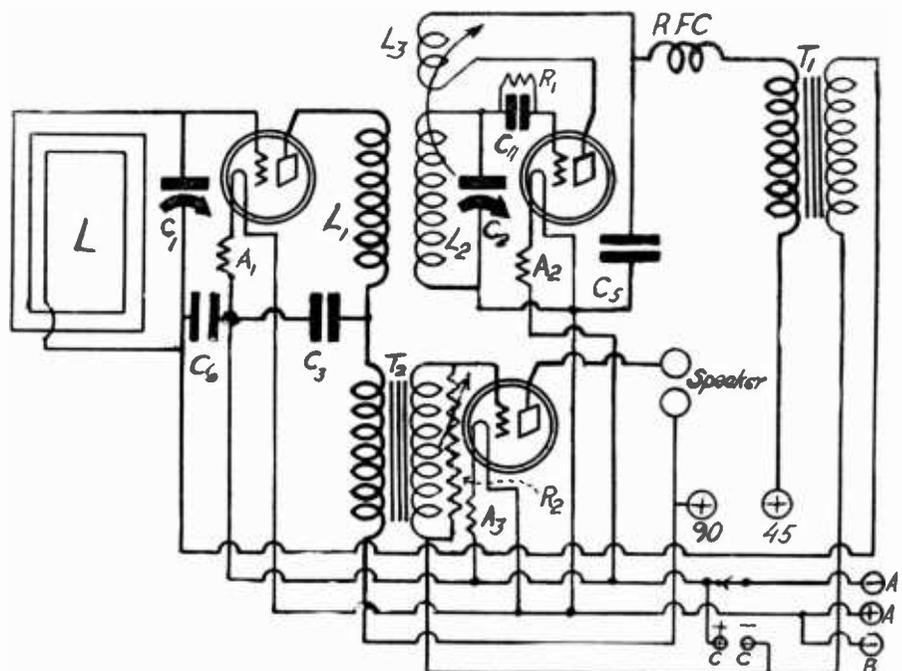


FIG. 1


A portable that gives maximum results from three type 99 tubes is diagrammed above. It is a reflex, the first tube being used as an RF amplifier and as the first stage of audio. This tube is at top, left. The detector tube is at right, top, and is regenerative. Below is the output tube. The set draws only 180 milliamperes filament current, so three No. 6 dry cells in series, as the A battery, should give at least 15 hours' service, if use is not continuous. Condenser C6 and resistor R2 are very important. R2 eliminates a peanut whistle otherwise possibly present.

secondary L2 of which is tuned with a .0005 mfd. condenser C2. The tickler L3 constitutes the volume control.

The grid leak R1 is 5 megohms and the grid condenser C4 is a .00025 mfd.

In the output of the detector tube is a special filter circuit designed to sepa-

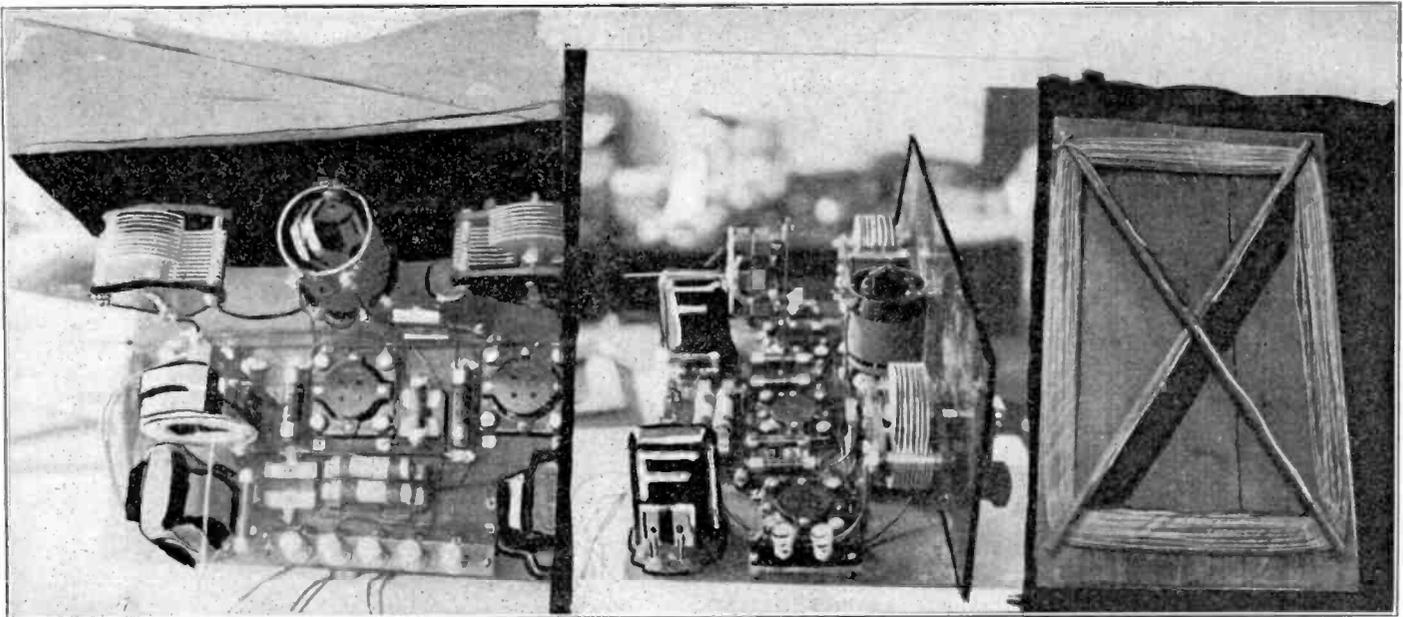rate radio from audio frequency currents. The filter consists of a radio frequency choke coil RFC of 65 Millihenries and the .0005 mfd. condenser C5. The choke coil is the heart of this filter and is indispensable. Its purpose is to prevent the radio frequency current from




A CORNER of the reflex set removed from the containing box is shown at left. The middle photo shows a detailed side view of the set removed from the cabinet. At the right is shown the construction of the loop on the under side of the lid.

passing into the primary of the audio transformer.

If the radio frequency current were not prevented from getting into the audio amplifier, it would be amplified to values large enough to give rise to considerable distortion. It would also give rise to an audio squeal which would ruin reception.

A Wise Choice

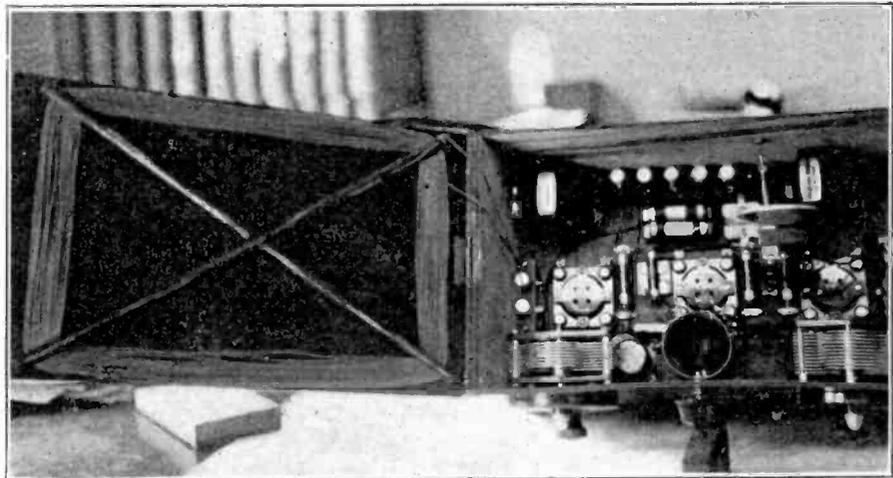The higher value of the inductance in the radio frequency choke the more completely would the radio frequencies be suppressed. However, if the inductance is too high, the higher audio frequencies would also be suppressed noticeably, and this is undesirable. A compromise in the value of inductance has therefore been adopted. The value of 65 millihenries rep-



HOW the loop is fitted into the hinged cover. For directional effect the entire set is turned.

LIST OF PARTS

- L1, L2, L3—One Bruno three circuit tuner, No. 88 midget.
 C1—One .00035 mfd. variable condenser.
 C2—One .0005 mfd. variable condenser.
 C3, C5—Two .0005 mfd. Polymet fixed condensers.
 C4—One .00025 mfd. Polymet fixed condenser.
 C6—One .0001 mfd. Polymet fixed condenser.
 A1, A2, A3—Three No. 4V-199 Amperites.
 T1, T2—Two General Radio audio frequency transformers, No. 285D.
 RFC—One 65 millehenry, General Radio RF choke coil.
 R1—One 5-megohm Lynch grid leak.
 R2—One resistor, preferably variable (Bretwood), or .5 meg. to 1 meg., if fixed.
 Nine X-L binding posts, with markers (Speaker—, Speaker+, A+, A—, B—, B+ Det., B+ Amp., Loop, Loop).
 Three push tube sockets.
 One filament switch.
 Two vernier dials.
 One knob for tickler.
 One 14-inch hard rubber panel (New York Hard Rubber Co.).
 One A battery, consisting of three No. 6 Eveready Columbia ignitor dry cells.
 One B battery, 90 volts, consisting of four No. 763 Eveready midget B batteries.
 One 4½ volt Eveready C battery, No. 771.
 One driving unit for loudspeaker (must have pin or stylus on it).
 A loop specially constructed as per directions.
 A box specially constructed as described.

resents the optimum compromise between suppression of radio frequencies and the transmission of the higher audio frequencies. But just any 65 millihenry choke will not do. It is of prime importance that the coil be so wound as to have a minimum of distributed capacity in its windings and also a minimum resistance. A coil of high resistance is not a choke coil no matter what its inductance may be. Likewise a coil with a large distributed capacity is not a choke coil but may actually be a by-pass condenser.

Condenser C5 not only aids in filtering the radio from the audio currents, but it also aids the regeneration. If the condenser were not connected into the circuit, the tube might oscillate on account of the radio frequency choke and the tickler, but the tickler might not act as a regeneration control. The circuit might oscillate even when the tickler was set a maximum and the leads reversed. But with the condenser the circuit operates normally over the entire tuning range, and still the suppression of the radio frequencies is satisfactory.

Keeping Set From Howling

Condenser C3, .0005 mfd. is connected across the primary of the second audio transformer T2 to keep the radio frequency signal in the first tube out of the third tube. Distortion would result in the last tube if radio frequency currents were allowed to enter it.

Condenser C6, .0001 mfd. is connected essentially across the secondary of the first audio transformer T1, but directly

it is connected from loop tuning condenser to the filament of the first tube. It makes the operation of the circuit more definite in that it furnishes a short path for the radio frequency input to the first tube and eliminates stray pick-up which would creep in by way of the long leads to the transformer T1.

It also serves to eliminate from the input of the first tube any radio frequency energy which has found its way through T1 from the detector tube. It thus serves to prevent undesired and uncontrollable regeneration. Thus C6 is in no small measure responsible for the quietness of operation of the circuit. As is well known, reflex circuits are wont to start squealing of their own accord, and this is due to inadequate by-passing or too high common impedance. Condensers C3 and C6 are largely responsible for confining the radio signal in its proper channel.

Peanut Whistle Eliminated

The two audio frequency transformers T1 and T2 should be chosen with quality of reproduction in mind. Two General Radio type 285D were used in the set.

A variable resistor R2 is connected across the secondary of T2. This suppresses audio frequency oscillations which sometimes interfere with the operation of reflex circuits. The value must be decided by experiment, the object being to suppress a high-pitched squeal. About .5 megohm does it, but a variable leak is preferable. The setting of this variable resistor, once found, is not disturbed,
 (Concluded on page 17)

Measure Your Aerial Capacity!

You Can Do It Without Calibrated Instruments

By Frank P. Sperro

YOU may have a radio installation which is incapable of receiving distant stations when the same set in other locations is capable of receiving real DX. You may have been told that the reason is that you are in a dead spot, that your tubes are dead, or that you are using improper voltages. All of these and countless others may be sufficient causes for lack of reception. But have you ever thought that your antenna may be at fault?

You may not have suspected that, because it is an especially good aerial. The antenna may have the correct length of wire, it may be well insulated, it may be well placed, it may be well-nigh perfect, yet it may be the cause of mediocre reception. Why?

Suppose you couple an antenna rather closely to a tuned circuit and measure the radio frequency resistance of that tuned circuit at different frequencies. In most cases you will find that in one frequency band the effective resistance of the tuned circuit is extremely great, while at other frequencies, either higher or lower, it may be quite low. Now, if that tuned circuit is the first tuner in a radio receiver, the signal intensity will depend on the effective resistance in the tuned circuit, as will the effective selectivity. Where the resistance is high the set will not be at all selective and the volume will not be so good.

Selectivity Up, Volume Down

If the coupling is loosened between the antenna and secondary coils, the selectivity will improve, but the volume will also go down. There will still be a frequency band in which the set will not be selective and where the volume will not be so good, but now the band will be narrower than it was before. If the coupling is reduced very much there will not be enough energy transfer to give any kind of signal strength, hence we are limited in obtaining selectivity in that way.

But why is the effective resistance of the secondary dependent on the primary? Because the antenna circuit absorbs energy from the secondary. It acts as a wave trap at one frequency, and this it does when the inductance and the capacity in the antenna circuit are in resonance with the stated frequency. If a signal is coming in at that frequency and the secondary is tuned to it there is no response, or if there is a feeble response, tuning has no effect on it. If that wave trap effect happens in the middle of the broadcast band, the receiver is of very little use because it will be both insensitive and non-selective over most of the band. Even if it occurs anywhere in the broadcast band the set will be comparatively dead. It is important so to design the antenna circuit as to avoid this condition, and that can only be done if the characteristics of the antenna are known.

Use of Calibrated Condenser

There is a very simple way of measuring the capacity of an antenna, but it requires a calibrated condenser. It can readily be understood by referring to Fig. 1. As will be seen this consists of a simple detector circuit of a single tube. C_0 represents the capacity to be measured, and is the effective capacity of the

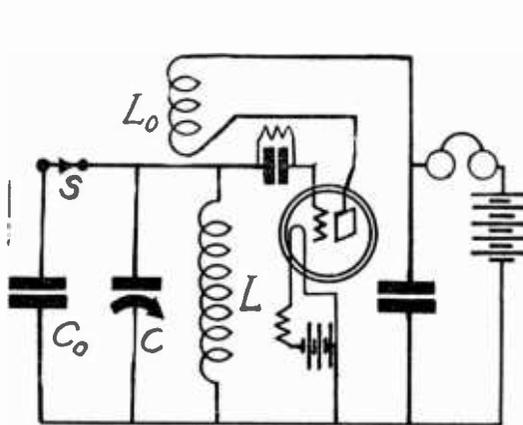


FIG. 1

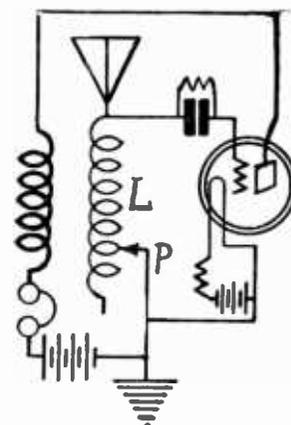


FIG. 2

At left is the circuit arrangement that can be used for measuring the capacity of an antenna by comparing it directly with a calibrated condenser. This is the substitution method. The diagram at right illustrates how the capacity and the distributed inductance of an antenna can be measured without any instruments. The circuit is tuned to two known frequencies by means of a solenoid inductance and the inductance used calculated. Known values can then be substituted in formulas to give the desired values.

antenna. C is a variable and calibrated condenser. L is a tuning coil and L_0 a tickler coil whereby the circuit can be set into oscillation.

Set the circuit into oscillation, with the switch S open. Tune with C until the frequency of the circuit coincides with the frequency of some broadcast station, as evidenced by zero beat. Select the stronger available near the upper end of the band, so that most of C is used, and so that the station can be heard distinctly. Now close switch S and decrease the capacity in C until the same station is tuned in exactly. The difference between the first and second readings of condenser C is the capacity of the antenna. If C is calibrated in micromicrofarads, then the value of C_0 obtained is also in micromicrofarads.

If C is not calibrated but is a straight line capacity condenser, then it can be used to get an approximate value of the capacity of the antenna. Suppose that the dial used has one hundred divisions and the total capacity of the condenser is known to be .0005 mfd. If the first reading on condenser C is 82 divisions and the second is 25 divisions, the difference is 57 divisions. That represents, approximately, 57% of .0005 mfd., or it represents .000285 micromicrofarads, which would be capacity of the antenna in that case.

An Ingenious Method

There is a very simple method of obtaining the capacity of the antenna without the use of any calibrated instruments, and this method should appeal to the student and true amateur because of its ingenuity. It requires the calculation of inductances of solenoids.

Set up the simple circuit shown in Fig. 2. L is a single layer solenoid about three inches in diameter and wound with heavy wire, say No. 20 double cotton covered, to a length of about four inches. Adjust the tickler coil so that the receiver is very sensitive, or so that it oscillates feebly. P is an insulated sharp-pointed probe of steel whereby contact can be made with the turns of the wire through the insulation.

Tune the circuit by means of the

prober to some broadcasting station near the upper end of the broadcast scale. Select one that is loud and the frequency of which is accurately known. The tuning is done by finding the turn at which the signal comes in the loudest, or at which the beat note is the lowest. It may be necessary to estimate fractional turns to make the measurement accurate. When the number of turns has been found for a high wave station, the process is repeated for a station of considerably shorter wavelength, but not one too far down the scale. The smaller the diameter of the coil and the longer it is, the wider may be the separation between the two stations.

Ascertain Distributed Inductance

When the number of turns has been found for each of the known frequency stations, calculate the inductance in the circuit for each case. This can be done quite accurately with the aid of Nagaoka's formula, which can be found in Circular No. 74, Bureau of Standards.

Having found the inductances in the two cases, not only can the capacity of the circuit be determined, but also the distributed inductance of the antenna. Suppose that the frequencies of the two stations used are F_1 and F_2 . Also assume that the values of the two inductances calculated are L_1 and L_2 . Let the true capacity of the antenna be C and let the distributed inductance of the antenna be L .

We first wind the value of the distributed inductance L from the formula $(F_1/F_2)^2 = (L_2+L)/(L_1+L)$. Having found L it can be substituted in $(F_1)^2 (39.48) C (L_1 + L) = 1$ to get C or in the corresponding formula for F_2 . The second of these formulas is simply the ordinary relation between frequency, inductance and capacity. The first formula is simply the ratio between two formulas of the second type.

Example of Determination

The first method of measuring capacity, that is, by means of a calibrated condenser, is suitable for all capacities less
(Concluded on page 15)

The Cash Box Unitone

A Set Worthy of Putting Under Lock and Key

By Wendell Buck

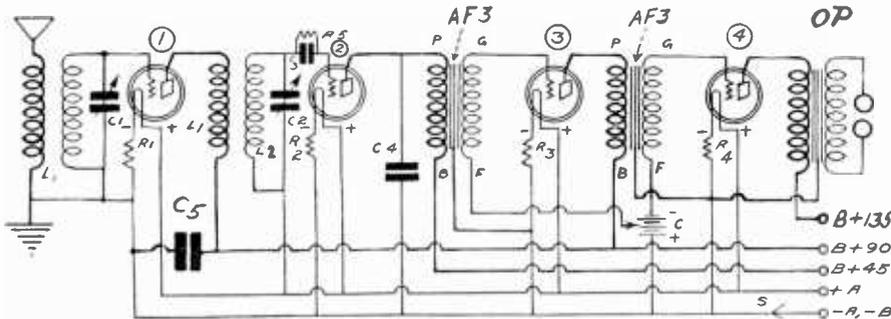


FIG. 2

The wiring diagram of the Cash Box Portable

RUGGEDNESS, sensitivity, selectivity, simplicity, lightness of weight are some of the essential characteristics of a portable receiver, if such a receiver is to meet satisfactorily the demands made on it. If the set is not rugged it may not outlast a single trip to the country; if it is not sensitive it will not bring in any signals to the camp in the country; if it is not selective it will not bring in any desired signal uniquely; if it is not simple it will be a nuisance to tune and operate; if it is not light it will not be portable, though it may be transportable. The set described herein meets requirements satisfactorily.

The demand of ruggedness is met by building the circuit into a metal cash box of dimensions 13 x 9 x 6 inches. This is a very strong case and will withstand a great deal of rough usage. It is adequate in size and it is equipped with a handle so that it can be carried easily. The metallic case for the set also serves as an electric and magnetic shield, thereby cutting out some of the noise in the Summer atmosphere.

The demand of sensitivity is met by using an open circuit antenna, a stage of radio frequency amplification in front of the detector, and by using transformer coupling in the two-stage audio frequency amplifier. The sensitivity is also aided by the use of high plate voltages and the proper use of grid bias voltage.

Set Is Selective Enough

Selectivity is gained by employing sharply tuned circuits in the inputs of the radio frequency and detector tubes, as well as by accurate adjustment of the two tandem tuners. Simplicity of operation is gained by the use of a single tuning control and by the omission of all useless knobs and dials.

Lightness of weight, which is a prime essential in any portable set, has been achieved by employing small parts throughout as well as by making the entire assembly no larger than necessary. While the metal box is heavier than a similar box made of wood or fibre, it does not add enough weight to the assembled set to overcome any of the more desirable features of a metallic container for the set.

As was stated above, the tuning is accomplished by a single dial or rather drum. This double tuning unit is a Bruno Unitone Model RF and consists of two quartzite radio frequency transformers and two .0005 mfd. condensers, all mounted in one unit. In Fig. 2, the two RF transformers are designated by L1L2 and L3L4 while the two condensers are designated C1 and C2.

The grid condenser C3 is of .00025 mfd.

capacity and the grid leak R5 is of two megohms resistance.

Output Transformer Used

There are three transformers used in the receiver, one of which is an output transformer. The two coupling transformers AF3 are Ferranti devices, which have primary windings of very high impedance, and therefore are capable of bringing out the low tones. The output transformer OP is of the same make but is designed to work between a power tube and a loud speaker.

The filament current is entirely controlled by Amperites. Four are used, one for each tube. The first three, R1, R2 and R3 are of the 99 type and R4 is of the 120 type, to match the tubes with which they are used. Of course each amperite is placed in the negative leg of the filament circuits.

The most suitable tubes for use in a portable set are the 99 and the 120, since they do not require much filament current nor a high filament voltage. Three of the 99s and one of the 120 are required for the receiver.

Adequate Plate Voltage

The sockets used in this receiver should be of the UX type so that for home use larger tubes can be substituted. When making the tube substitution it is necessary to change the amperites also. The first three should then be 1A if the tubes have 5-volt filaments and the last Amperite should be a 112 if a 112, or other tube of similar fila-

LIST OF PARTS

C1C2L1L2L3L4—One Bruno Unitone, Model RF, consisting of two .0005 mfd. condensers and two RF transformers, mounted on a frame; two drums, panel plate.

C3—One Electrad .00025 mfd. condenser with leak mounting.

C4—One Electrad .001 mfd. condenser.

C5—One Electrad .01 mfd. condenser.

R1, R2, R3—Three 99 type Amperites.

R4—One 112 amperite.

R5—One 5 meg. Electrad grid leak.

AF3—Two Ferranti audio frequency transformers.

OP—One Ferranti output transformer.

S—One Carter "Imp" filament switch.

Four Patent Cushion Sockets No. 83.

One extension Cord connector.

One Jones Multi-plug and Cable, base mounting type..

One wood baseboard, 12½x8½x¾ in.

Two metal cash boxes, 13x9x6 inches, equipped with handle and lock.

Two ¼ inch rubber bushings.

ment characteristics is used.

The plate voltage on the first audio and the RF tubes is 90 volts. The plate voltage on the detector is the usual 45 volts, and the voltage on the plate of the last tube is 135 volts. If desired the RF tube can be put on the same plate voltage as the detector.

The grid bias for the audio frequency tubes is suited to the plate voltage used and the type of tube employed. Since the first audio tube has a plate voltage of 90 and the tube has a mu of 6.5, the proper grid bias on that tube should be about 7.5 volts.

The grid bias on the last tube, if it is of the 120 type, should be 22½ volts. It should be pointed out that it is a fallacy in a portable set to omit the grid battery to keep the weight down. The use of a very small grid batteries of the proper voltage will save the plate current drain—about 50 per cent.—so that much smaller B batteries can be used. Thus a few ounces of grid batteries will make it possible to dispense with several pounds of B batteries. Of course, it is not recommended that exceedingly small B batteries be used, but they may

(Concluded on page 15)

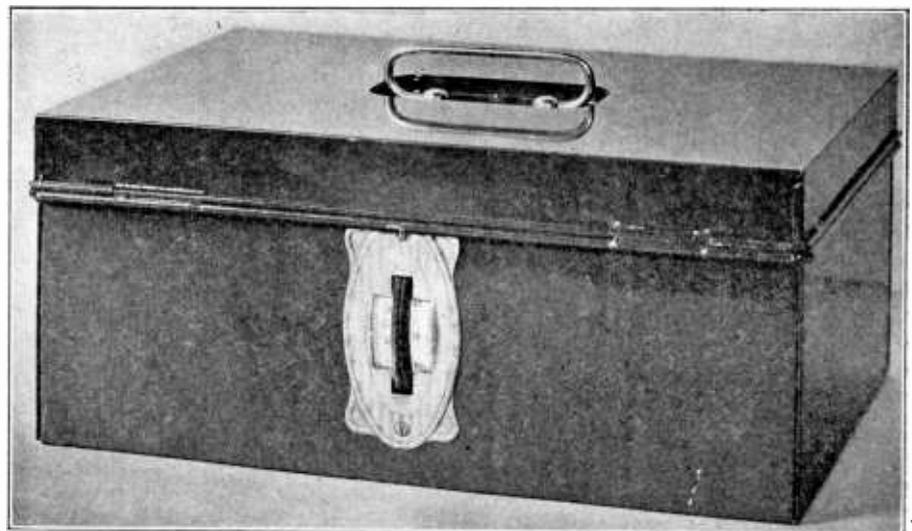


FIG. 3

Front view of the Cash Box Portable Receiver.

How to Use the AC Tubes

Practical and Soon Will Be Rule, Says Expert

By C. T. Burke

Engineering Department, General Radio Co.

THE principal radio trend of the season just past has been toward the elimination of batteries. Many satisfactory plate supplies have been developed, but the problem of filament supply has offered more difficulty.

Larger currents are required for filament than for plate supply, and these mean greatly increased expense in the rectifier and filter circuit. Then too, many of the plans proposed for batteryless filament lighting required rewiring of the tubes in series.

Tubes for alternating current filament supply have been announced by several manufacturers. Many of these tubes will be available in the next few months, and the batteryless receiver will probably be the outstanding development of the coming radio season.

Trend Is Toward AC

This does not imply immediate obsolescence of present receivers. The new tubes will have plate characteristics similar to those now in use, and the present types of tubes will continue to be supplied. The trend will, however, undoubtedly be toward the AC filament tubes.

Two types of AC filament tubes are to be supplied, representing different methods of attack on the problem of AC filament operation.

In the conventional type of tube supplied for direct current operation the filament forms a part of two circuits. The battery circuit through the filament is for the purpose of heating the filament to produce electron emission. This circuit is auxiliary to the main function of the tube, but the filament also forms one side of both input and output circuits of the tube.

Ordinary Tubes Hum

If alternating current is supplied to the filaments of ordinary tubes, a hum will result. Several sources contribute to the hum. As the current through the filament changes during the alternating current cycle, varying from zero to maximum, the temperature of the filament, which depends on the current through it, is also changing. The change in filament temperature results in a cyclic change in the tube characteristics which in turn produces a hum at twice the frequency of the supply. A certain amount of hum is due to capacity effect between the tube elements and to voltage drop along the filament.

Another appreciable source of hum is the grid effect of one side of the filament on the other. The filament of most tubes (except the 199 tube) is triangular in shape (less the base).

It Makes a Difference

When direct current is applied to the filament, conditions are stable, and the grid effect of one end of the filament on the other end introduces no disturbance. When alternating current is applied to the filament, the grid effect is variable. As the current increases through the filament one end of the filament is increasingly negative with respect to the other, and the emission from that end of the filament is reduced, since the other end is more positive and attracts a portion of its emission current. A half cycle later the two ends of the filament are

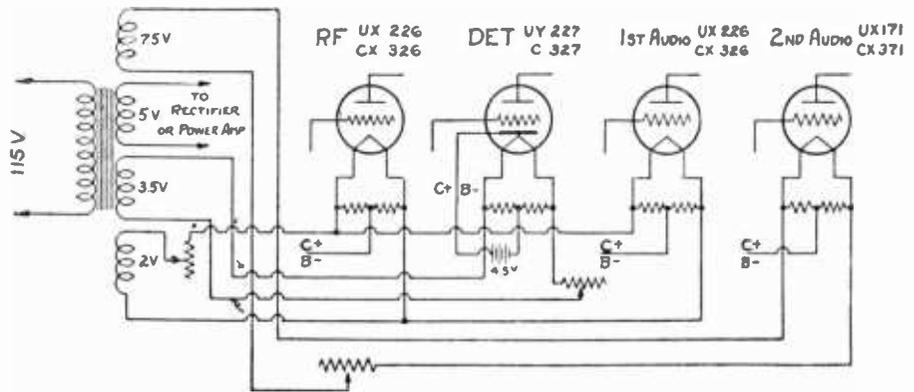


FIG. 1

The AC wiring for a four-tube receiver, with grid return connections shown. AC tubes are used, as identified in the diagram. Note the five-terminal tube used as detector, with the reversed C battery to give positive bias. Mid-tapped resistors across each filament establish the average potential point. Grounding the center makes adjustment critical, particularly in the detector stage, the author observes.

reversed, and the effect repeats. A hum at twice the supply frequency results.

In one type of alternating current filament tube, the design is similar to the direct current type except for the construction of the filament, which is short and heavy, taking materially more current than the modern direct current tubes and operating at a low voltage.

An advantage of the heavy filament is that it retains heat longer than the present type, i.e., there is less heating and cooling as the current goes through its cycle, the heat carrying over from one cycle to another. In fact, sufficient heat remains to produce audible signals for a few seconds after shutting off the current.

There's an Appreciable Wait

It might be expected that such a filament would take longer to reach its operating temperature. This proves to be the case, and there is an appreciable wait between the turning on of the current and the appearance of the signals. It may be noted in passing that some of the direct current tubes have the characteristics of slow heating and cooling of the filament. The WX 12 type can in fact be used with fair results, with low AC on the filament in radio frequency stages, provided care is used. It is also interesting to note that the 199 type of tube, with a straight filament, shows little grid effect.

The filament of the AC tubes is short and straight, which greatly reduces the grid effect. The low voltage across the filament also tends to reduce the hum due to grid effect.

Returns to Average Potential

In order to eliminate hum due to the voltage drop through the filament the grid and plate returns must be connected at the average potential of the filament, i.e., the potential of the center point. Unless this is done a pronounced hum having the same frequency as the source of current will be produced by a periodic fluctuation of both the grid bias and plate voltage. The most satisfactory means of obtaining this connection is by means of a center-tapped resistance across the filament terminals of the tube. The

center of the resistance is necessarily at the same potential as the center of the filament.

Tubes of the heavy filament type are generally made to fit the standard UX type of socket. This type of tube is suitable for either radio or audio frequency amplifier work. Some manufacturers do not, however, recommend tubes of this type for use as a detector.

The Fifth-Terminal Tube

In another type of tube for alternating current operation the two circuits which use the filament of the direct current tubes are separated. The cathode is heated from a separate heating element inside the cylindrical electrode, while an additional terminal is provided for the C+ and B- connection and the tube has therefore a five-prong base, requiring a special socket. This type of tube also requires a center-tapped resistance across the heating element.

The center point of the resistance may be grounded in this case. When the mid-point of the potentiometer is grounded, the setting is rather critical for best results. Another less critical method is to connect a 4.5 volt battery between the center tap and the cathode terminal. The negative of the battery is joined to the center tap. This type of tube is particularly recommended for use as a detector.

No power tubes are listed among the new alternating current filament tubes since raw AC can be used with perfect satisfaction on the filaments of present last stage tubes. The output tube should always be the 112, 171 or 210 type. These tubes are connected in the same manner as the AC tubes which use the standard UX base, i.e. with a center-tapped resistance across the filament.

Needs Wire That Suits

Due to the heavy currents drawn by the alternating current types of tube, it may prove necessary to replace the filament wiring in some multi-tube sets with heavier wire, No. 18 wire, for example, should not be required to carry more than three amperes. Portions of the filament bus through which greater current

(Concluded on page 15)

Curing Image Interference

Analysis of An Ailment of Super-Heterodynes

By Brunsten Brunn

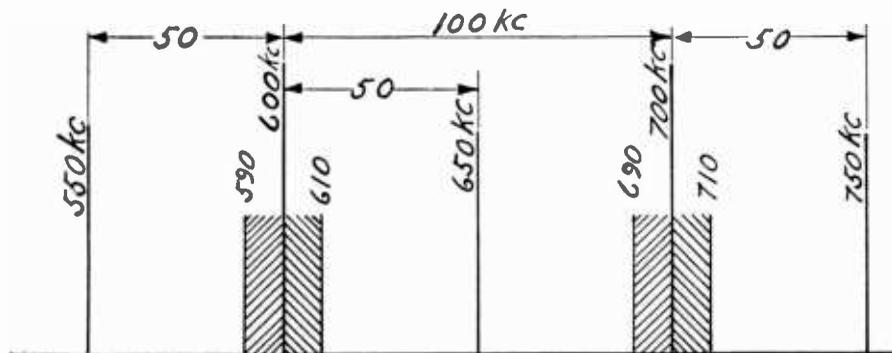


FIG. 1

The production of image interference. When the oscillator is set at 550 kc, a 50 kc frequency is produced with the 600 kc signal and it gets through the filter. When the oscillator is set at 750 kc, a 50 kc frequency is produced with the 700 kc signal and it gets through the filter. When the oscillator is set at 650, a 50 kc signal is made with the 600 kc signal and also with the 700 signal, and both get through the filter at the same time. A squeal is produced.

EVERY system of reception has its ills. The Super-Heterodyne system is no exception. The Super-Heterodyne is immensely popular, which proves its value, but experts are trying to free it from all troubles.

The principal reason the Super-Heterodyne is popular is that it is the "Rolls Royce" of reception. Ownership of a Super is a mark of distinction, of affluence, just as the ownership of a Rolls Royce or a yacht is. Ownership of a Super-Heterodyne is not always a sign of radio satisfaction, of radio tranquility.

Notwithstanding defects of the Super-Heterodyne, it has always been a pet with most technical writers, engineers and advanced radio experimenters. Despite ills to which it is subject it is the non-plus-ultra of receivers.

Time and thought spent in overcoming the shortcomings of the Super-Heterodyne should be regarded as legacies to posterity, because unquestionably the Super-Heterodyne embodies the principles of the receiver of tomorrow, or the day after.

Some Troubles Listed

What are some of the troubles with the Super-Heterodyne? It may be too selective, and many examples of Super-Heterodynes are too selective.

The Super is subject to more interference than any other receiver, with the possible exception of the single circuit crystal receiver.

The Super-Heterodyne also will pick up more noise from the atmosphere and it will develop more noise of its own than any other set.

The greatest trouble with the Super-Heterodyne is that which has been called image interference, which gives rise to most of the squeals heard in the Super-Heterodyne. Indirectly, it is also the cause of over-selectivity, because in an endeavor to get rid of the squealing, designers have increased the selectivity.

It may be well to discuss image interference and tell what it is. Suppose that the intermediate frequency used in the Super-Heterodyne is 50,000 cycles and that it is desired to receive a station operating on a frequency of 600 kilocycles. A local oscillator is started and its frequency is adjusted to differ from the desired fre-

quency of 600 kilocycles by the value of the intermediate frequency, that is, 50 kilocycles. The frequency of the local oscillator can either be 50 kc above 600 or it can be 50 kc below it. That is, the desired station can be received either when the local oscillator is set to 550 kc or to 650 kc.

Image of One, Object of Other

One of these frequencies is just as far below the 600 as the other is above it, or the two bear the same relationship to the 600 kc frequency as the object and the image bear to the plane mirror. It is for this reason that the term image interference is used. We can regard the position of the 600 kc frequency in the scale as a mirror and then the 650 kc frequency can be regarded as image and the 550 as the object, or vice versa. The term image interference is not a very appropriate one, but it is rather widely used.

It should be pointed out that the image can never interfere with the object of the same station. It is the image of one station that interferes with the object of another. For example, suppose that there is another station operating on a frequency of 700 kc, and that this is close enough to the receiver to make itself heard. This station can be received on our 50 kc Super-Heterodyne if we set the local oscillator on either 750 or 650 kc. Therefore both the 600 and the 700 kc station can be received if the local oscillator is set on 650 kilocycles. Therefore, there is a clash between the image of one and the object of the other.

Little damage would be experienced from this clashing if the two stations were really on 600 and 700 and if the 50 kc Super were set on exactly 650 kc, unless the two signals were of about the same intensity at the first detector. The trouble arises when there is enough divergence in frequency so that the clashing image and the object produce a squeal.

Arrives Weak, Interferes Strongly

The Super-Heterodyne is extremely sensitive to this type of interference. The interfering image may be exceedingly weak yet be strong enough to ruin the reception of a strong local station. The reason for this is that the strength of

the interference is proportional to the intensity of the local oscillation, which is the same for both the strong local station and for the weak interfering station. It does not take much of a squeal to render reception intolerable.

So far we have seen that the 50 kc Super-Heterodyne cannot receive without interference a 700 or a 600 kc signal when stations of both of these frequencies are operating. It will be noted that the separation between these stations is equal to twice the intermediate frequency. It requires no further demonstration to show that any two stations operating simultaneously on frequencies separated by twice the intermediate frequency will interfere no matter what the absolute values of the station frequencies may be or what the value of the intermediate frequency may be, just so one of the station frequencies lies within the range of the local oscillator. For example, two stations operating on 950 and 1050 kc can be received when the local oscillator is set at 1000 kc on our 50 kc Super-Heterodyne, and therefore these stations will interfere with each other.

Since the broadcast stations are separated by multiples of 10 kc, it appears that if the intermediate frequency is 50 kc no stations would be free from image interference except those operating on frequencies less than 600 kc, that is, 550 plus 50 kc. These long wave stations could be received free of broadcast interference on one point each only. Stations operating near the upper limit of the broadcast scale could not be received without interference because of harmonics of lower frequency stations. If we choose another intermediate frequency which is a smaller multiple of 10 kc, the situation is simply aggravated, because there will be a greater number of chances for interference, and the fact that the selectivity can be made much greater on the lower frequencies will not aid in preventing the interference.

Applies All Over

It is not only the whole multiples of 10 kc which are subject to interference but practically every other frequency that can be selected. Suppose the intermediate frequency is 45 kc. Stations separated by 90 kc will interfere. Suppose again that the intermediate frequency 42,500 cycles. Stations separated by 85 kc would interfere. But there are no stations in this country or Canada which are separated by such an interval, since 85 is not a whole multiple of 10 kc. But that does not prevent interference. In this case there would be much more interference, because neither the 90 nor the 80 kc separations would be exempt. There is nothing to be gained by splitting up the intermediate frequency into fractional multiples of the 10 kc interval.

What can be gained by tuning the intermediate frequency filter? Selectivity and nothing else. No relief from image interference to speak of can be gained, unless the interfering noises are so high in frequency as to be cut off together with the higher frequencies in the side bands. The remedy is worse than the malady.


What then can be done to minimize image interference in a Super-Heterodyne? One thing that can be done is to
(Continued on next page)

An Arbor Speaker

Handy Indeed for Enlivening Garden Parties

By Herbert E. Hayden

Photographs by the Author

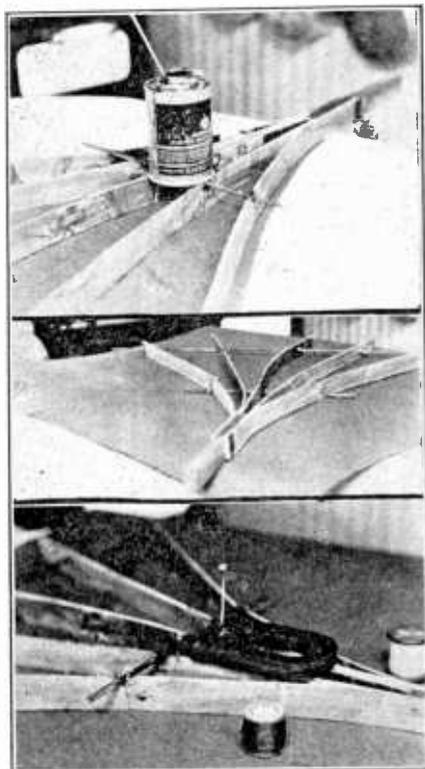

FIGS. 1, 2 AND 3

The top photo shows the construction of the fan-shaped trellis or arbor for holding the sounding surface. It also shows the manner in which the paper is placed and trimmed. Fig. 2 shows the fans and the paper which is to be the sounding surface. At bottom (Fig. 1) is the driving unit of the speaker.

WE have heard of the welkin ringing, of brooks murmuring, of boughs sighing, of the wind howling. But we have never heard a vine covered trellis singing and speaking, though we have heard whisperings and cooings inside the arbor formed of the trellis. But now we have a trellis that not only transmits the whisperings and cooings from the lovers inside, but we have a trellis that sings and speaks of its own accord.

This singing trellis is a loudspeaker. It is basically of the cone type. It consists of a trellis arrangement, called an arbor, and sold as garden equipment, which you cover with a sheet of Alhambra Phonotex paper. The trellis or arbor is the form of a fan with a substantial handle at the apex. The construction can be seen from the photographs. First we have the wooden handle and then five radiating strips of wood placed on edge. The fan is spread by means of a couple of wood dowels suitably placed.

In assembling the fan-shaped trellis the work can be facilitated by binding it together with thread. Then glue is applied and the assembly is left to dry, after which the threads can be removed.

In Figs. 1 and 3, the top and bottom photos, you see the structure of the fan, in case you want to make it yourself. After the glue is dry the fan is placed on top of a sheet of Alhambra paper and secured by means of more glue. Then excess paper is trimmed off with a pair of shears and the sound part of the speaker is finished.

But the speaker will not sing without a driving unit. How this is mounted is shown in Fig. 3 in the bottom photograph. This photo merely shows the position. The coupling pin should, of course, be turned toward the sounding paper. The Enesco unit may be used.



FIG. 4

This shows the finished trellis speaker and a girl entertained by it.

Fig. 4 shows the finished speaker. Its base is pointed and the speaker may be stuck into the earth anywhere in the garden, while extension cords connect to the set in the house. Thus garden parties are enlivened by broadcast music.

RESTAURANT USES AC SET

As a means of entertaining its patrons, Thomas's Restaurant in Newark, N. J., has installed an AC operated receiver. This is used in conjunction with a 36-inch cone speaker. The set is kept going from noon to 1 A. M.

Trapping and Balancing Out Interference

(Concluded from preceding page)

increase the intermediate frequency. It might be made 100 or even 250 kilocycles. Increasing the intermediate frequency militates against selectivity as well as the sensitivity.

Safety Factor in Higher Frequency

Vacuum tubes and circuits are not so effective at high frequencies as at low, so that using high intermediate frequencies nullifies one of the main objects of the Super-Heterodyne, and it does so in direct proportion to the increase in frequency. But the loss in amplification can always be offset by a little regeneration. This would also offset some of the loss in selectivity.

The higher the intermediate frequency the fewer chances there will be for image interference. The advantage will mainly be noticeable at the lower end of the scale, but there will also be some advantage at the upper. If the intermediate frequency is fairly high it will represent a considerable part of the total range and there will only be a small band in the middle of the range which will be subject to interference. But this is not the only advantage to be gained from using a high intermediate frequency.

The most effective way of minimizing

image interference is to operate on the radio frequency end of the circuit. It might be said that it is the only way of reducing the trouble. The radio frequency tuner must be made so selective that the signal which causes the image interference is reduced to zero as far as its effect on the output is concerned. This elimination of the interfering carrier can be done by making the radio frequency tuner very selective irrespective of the value of the intermediate frequency. But if the intermediate frequency is low, the radio frequency tuner would have to be very much more selective than it has to be when the intermediate frequency is higher, to gain the same suppression of the interfering carrier.

Other Means Suggested

Making the radio frequency tuner selective enough to cut out the interference when the intermediate frequency is low would result in cutting off the side band frequencies in the signal to such a point as to reduce the intelligibility of the signal received. If the intermediate frequency is high the interfering carrier can be nullified without making the tuner so sharp as to interfere appreciably with the quality of the reproduced signal. For this reason a high intermediate frequency

is desirable. Recent practice favors intermediate frequencies ranging from 100 to 250 kc, with a few still clinging to the 50 kc frequency.

There are other means of suppressing an interfering carrier which do not necessitate making the radio frequency tuner very selective or without making the intermediate frequency excessively high. One is based on trapping out the interfering carrier by means of a tuned circuit, and another is based on balancing it out. When the trap method is employed a tuned circuit is incorporated in the receiver and coupled loosely to the input. If there is a squeal caused by image interference the trap is set on the carrier which causes the trouble, and the squeal either disappears or is reduced to tolerable intensity. If the balancing method is used the circuit is so arranged that no signal can be received from the direction of the interfering carrier. The simplest way of balancing is merely to turn the loop so that its plane is at right angles to the direction from which the interference comes. This is effective provided that it does not also cut out the station desired. There are other methods of balancing out interference of this type but they are not suitable for broadcast reception.

A Push-Pull Output

Condenser Folly Avoided in This Hookup

By Gen. T. C. H. Branon

WHEN it is desirable to have considerable undistorted power for the loudspeaker and neither power tubes nor high voltages are available, a push-pull amplifier can be rigged up, usually out of parts that are already at hand. Fig. 1 shows such an amplifier. T1 is an audio frequency transformer. It must be one of high grade and preferably of high ratio, say 6 to 1. R1 and R2 are two resistors or about .5 megohm each. R3 is a high resistance potentiometer about .5 megohm. This potentiometer is connected between the two fixed resistors and it is used for the purpose of dividing the secondary voltage equally between the two tubes. It is difficult to find two resistors of exactly equal ohmage to make the potentiometer unnecessary. Of course, if a potentiometer of about one megohm is available, R1 and R2 need not be used, R3 alone being sufficient.

The grid battery is put in the lead which runs to the slider on the potentiometer, with the minus terminal pointing toward the slider.

No Condensers Used

In the output side two choke coils L1 and L2 are used in place of an output transformer. These choke coils can be the secondary windings of audio frequency transformers. Cheap transformers, which should not be used in any high quality amplifier, can be used here to good advantage. The two choke coils are connected in series between the two plates of the two windings, is connected to the positive of the plate battery.

The loudspeaker is connected from plate to plate across the two choke coils. Note that no condensers are used in series with the speaker. Similar circuits have been recommended in which a 2 mfd. condenser has been placed on each side of the speaker, with the admonition that each must stand the voltage of the plate battery. When two condensers of 2 mfd. each are used in series the effective capacity in series with the speaker is only one microfarad, and this is so low that it seriously cuts down the lower notes in the signal. The loss of the low notes is too heavy a price to pay for a habit which serves no purpose. It is apparent that there is no DC voltage across the loudspeaker, and no direct current will flow through the loudspeaker when the condensers are omitted. Hence the condensers should be omitted.

Tubes to Use

Since the loudspeaker is connected from plate to plate without a step-down transformer, the loudspeaker should have a very high impedance to take full advantage of the power delivered by the tubes. The internal resistances of the tubes are in series with the speaker, and therefore the speaker should have twice the usual impedance. We cannot change the impedance of the speaker at will to match the series connection, but we can use two speakers in series. But using two speakers is not a practical solution.

It is better to use two tubes which have a low output impedance, e. g., two 371 tubes, the impedance of which is around 2,000 ohms each, requiring a load impedance of 4,000 ohms each. The impedance of the speaker when connected

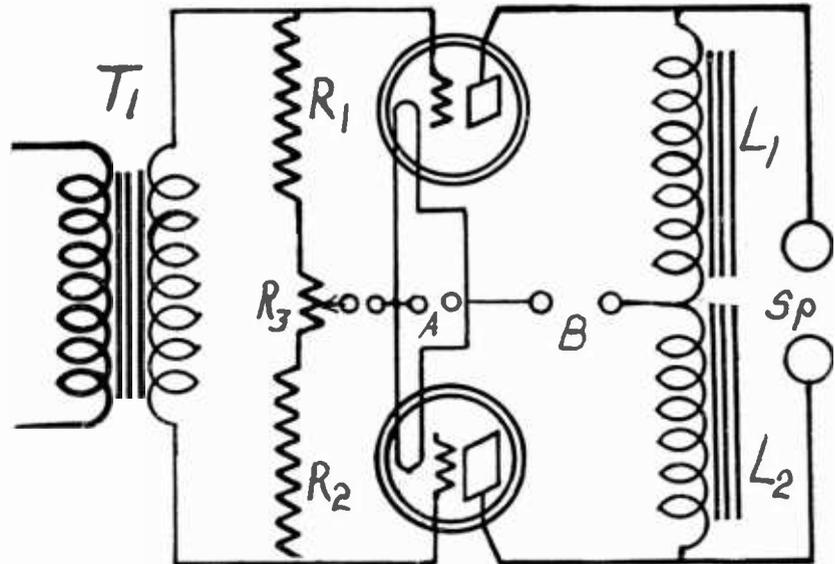


FIG. 1

A push-pull amplifier without the regular input and output transformers. A potentiometer is used to divide the secondary voltage of transformer between the two tubes. Two choke coils are used in the output and the loudspeaker is connected directly across the coils without any stopping condensers.

LIST OF PARTS

- T1—One good audio transformer, ratio 6 to 1.
- R1, R2—Two .5 megohm grid leaks (Lynch).
- R3—One .5 megohm potentiometer.
- L1, L2—Two audio frequency choke coils or transformers.
- One double mounting (Lynch).
- Two UX sockets.
- Two amplifier tubes of low output resistance.
- Ten XL binding posts.
- One baseboard 4x7 inches.

across two such tubes should therefore be 8,000 ohms. Most good speakers are suitable. Such tubes as the 220 and 112 may be used.

Hammarlund Has Two RF Chokes

Two radio frequency choke coils are the latest additions to the line of Hammarlund radio products. A specially developed method of winding, and impregnating with low dielectric compound, produces a coil of minimum distributed capacity and extremely high impedance to currents at radio frequencies. Due to the resistance of the coils and the method of winding, there is no point within the broadcast band at which they become self-resonant and their action is the same throughout this range of frequencies.

The case is 1½ inches in diameter by 1¾ inches high, and the coils are made in two values of inductance for the broadcast band.

R.F.C. No. 85 has an inductance of 85 millihenrys, a capacity of 3 mmfd. and a resistance of 215 ohms.

R.F.C. No. 250 has an inductance of 250 millihenrys, a capacity of 2 mmfd. and a resistance of 420 ohms.

Literature Wanted

THE names and addresses of readers of RADIO WORLD who desire literature on parts and sets from radio manufacturers, jobbers, dealers and mail order houses are published in RADIO WORLD on request of the reader. The blank below may be used, or a post card or letter will do instead.

RADIO WORLD,
145 West 45th St., N. Y. City.

I desire to receive radio literature

Name

Address

City or town

State

C. A. Roeper, 341 Orchard Place, Pittsburgh, Pa.
R. Arthur Heiser, 1517 Olivewood Ave., Cleveland, Ohio.

Adolf Sauter, 486 Park Ave., West New York, N. J.

Lee Henderson, R. F. D. No. 2, Jewett, Ohio.

Mr. Jno. Lucas, Box 75, Jewett, Ohio.

Geo. H. Keller, Jr., 254 Delaware Ave., Albany, N. Y.

B. R. Farris, General Delivery, West Palm Beach, Florida.

Chester L. Davis, Ph.D., School of Engineering of Milwaukee, 163 East Wells Street, Milwaukee, Wisc.

Daven Retains Baron; New Circuit on Way

Baron von Ardenne, 20-year-old German scientist, who recently visited the United States, has been retained by the Daven Radio Corporation, of Newark, N. J., prominent resistor and high and low mu tube manufacturers, as consulting engineer.

The Baron's special anode (plate) bend method of detection will be used in a specially designed receiver.

The Toto Power Well

Dispenses With All Batteries, Provides AF Stage

By Capt. Peter V. O'Rourke

Contributing Editor

PART I

ELIMINATORS in which all the three voltages, A, B and C, are obtained are now rapidly gaining in popularity. Such eliminators should incorporate a stage of power amplification. This the Toto power well does.

The rapid gain in the popularity in these devices is due to the cleanliness and ease of operation as well as to the enormous amount of power or undistorted quality that is available in the output circuit.

It is customary to connect the filaments of most of the tubes in series in such eliminators and to filter the filament current so that all ripple is removed from it. It is this filtering which makes it possible to eliminate not only the B battery but also the A and the C batteries.

The C battery is eliminated by making use of voltage drop in a resistance. The grid bias voltages for most of the tubes can be obtained from the voltage drops in the filaments of the tubes.

May Use Drop in Filament

If 01A tubes are employed the drop in each filament is 5 volts, and therefore grid bias potentials can be obtained in steps of 5 volts. However, in series connected circuits there will always be one tube, and sometimes two, which cannot get bias from a drop in another filament. This tube can often be made the detector, which does not require a negative bias. If the detector cannot be placed in this unique position, it is often possible to place the first radio frequency amplifier there, since such a tube can be operated without any negative bias.

However, it is always best to adjust the grid bias for every amplifier to the proper value. Hence it is customary to introduce a resistance in series with the filament circuit and utilize the voltage drop in that resistance for the bias of the tube which is in the unfavorable position. The voltage for the bias on the power tube is obtained in a similar manner, although in this case the current utilized is only the plate current from the power tube rather than the filament current for the other tubes.

One of the essential things in the eliminator is the filter, as was stated above, and the most important parts in the filter are the by-pass condensers. Without them no satisfactory operation could be obtained.

Good Condensers Spare Trouble

Condensers should be used generously both in size and number.

For example, there should be a by-pass condenser of large value across every filament heated with direct current as a means of reducing the effect of residual hum. This is important because the ripple in the filament current not only affects the heating current but it also affects both the plate and the grid voltages. Since it affects the grid voltages it also affects the input voltages to the amplifier tubes and the detector. The hum is amplified just as the signal is amplified, and what at first was a minute and inaudible ripple is likely to become an audible hum. The by-pass condensers prevent the hum from entering the signal and thus keep the output hum-free.

Another important reason for by-passing generously is that it reduces the

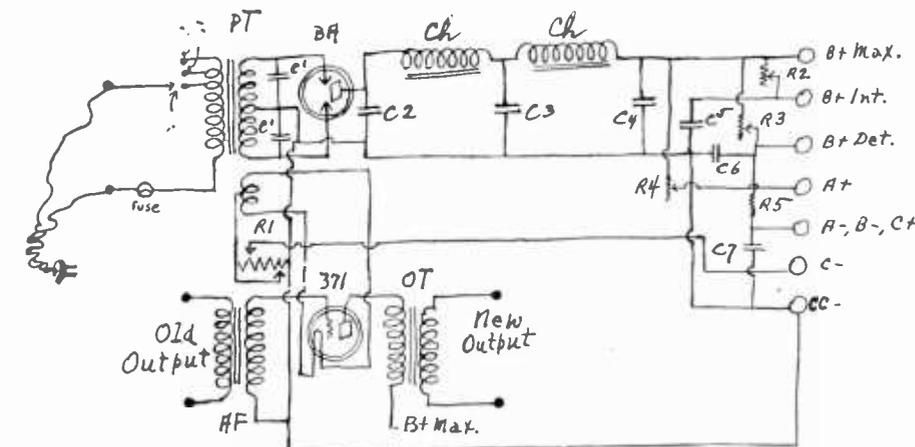


FIG. 1

The circuit diagram of an ABC eliminator and a one-stage power amplifier.

tendency to motorboat. Condensers furnish the only means of reducing the cause of motorboating, although there are other means of stopping the oscillation. Another place where condensers must be used is in the voltage divider in the plate supply part of the eliminator.

Need of By-passing

Every section of the resistance should be by-passed with a good sized condenser, and the by-passing should always be from the high potential side of the resistor to the lowest potential point in the circuit.

In an eliminator in which A, B and C voltages are to be obtained the voltage at the output of the filter must be higher than when only the B voltage is to be

obtained. This requires that the condensers used in by-passing be able to stand a higher voltage. Sometimes the voltage will be as high as 600 volts. The condensers used must then be able to stand continuously at least 1,000 volts. This high limit is set as a matter of safety, not only for the condenser but also for the circuit as a whole and the operator. Short-circuits and break-downs never do any good.

A direct current voltmeter placed in the output of the filter may show a steady reading of 350 volts, but that does not mean that that is the highest voltage to which the condensers will be subjected.

Surges Are High

There are surges in the line which may rise to several times the value of the indicated voltage. These surges do not last long enough to affect the reading of the meter but they may last long enough to break down the condensers or insulation of the leads. A 200% margin of safety in the condensers is not excessive.

A condenser might resist a high voltage for an instant yet break down on a somewhat lower voltage sustained for a considerable period, if not enough margin is left. This will more likely occur when the condensers are carrying an alternating current of some intensity than when the current is feeble. The current heats the insulation and weakens its dielectric strength. So good condensers are necessary, and on the BA circuit are doubly necessary, since here the current drain is heavy.

[Part II, dealing with the construction, will be published next week. The biasing problem will receive special attention then.]

ENSCO OPENS TORONTO OFFICE

Increasing demand in Canada for the Ensko three-foot cone speaker kit, manufactured and marketed by the Engineers' Service Co., 25 Church street, New York City, has caused the opening of the first of a chain of Canadian studios in Toronto. This studio opening was arranged by D. B. Tilson, New England manager for Ensko, and is located at 331 Bay street, Toronto, Canada.

LIST OF PARTS

- BA—One Raytheon Type BA tube.
- PT—One Acme power transformer for BA tube (2kw).
- AF—One Acme Apparatus audio transformer.
- OT—One Acme output transformer.
- C1, C1—Two 1,000-volt Flechtheim buffer condensers, each .1 mfd.
- C2—One 4 mfd. 1,000-volt Flechtheim condenser.
- C3, C4—8 mfd. each, made up of four each of C2 type.
- R1—One Amsco Duostat, 2,000 ohms.
- R2—One Electrad 5,000-ohm 5-watt Truvolt variable resistor.
- R3—One Electrad 10,000-ohm 5-watt Truvolt variable resistor.
- R4—One Power Clarostat.
- R—One Electrad 1,500-ohm 5-watt Truvolt fixed resistor.
- C5, C6, C7—Three Flechtheim 1 mfd. 250-volt by-pass condensers.
- Two Acme Apparatus Co. choke coils for BA tube (BA2).
- Eleven binding posts.
- One fuse and one porcelain fuse socket.
- One extension cord and lamp socket plug.
- Two vacuum tube sockets.
- One CX-371 tube.
- One 20x10-inch asbestos board.
- One shielded case (optional).

Precautions Assure Fine Summer Reception

(From Information Bureau, Radio Corporation of America)

Just as the family car must be prepared for the Winter driving season by undergoing a thorough overhauling, so must the family radio set be groomed for Summer use. In either event the preparations are simple enough, and should not stand in the way of enjoying to the utmost both these one-time hobbies which have now become such everyday necessities in American family life.

Many things have been done during the past few summers to ameliorate conditions in warm weather radio reception. Transmitting power has been enormously increased. Network station operation has placed the best programs in most parts of the country with the loudspeaker volume of local stations. Receiving equipment has been developed with an eye—or shall we say an ear?—to lessening the static effect while increasing the apparent signal strength. In all, remarkable advances have been scored against Summer-time obstacles. A large field for improvement still lies in the homes of the set owner.

Satisfactory radio reception depends primarily upon what radio engineers call the signal-static ratio. In other words, static is present, in varying degree to the signal strength from the broadcasting station.

Question of Signal Strength

With the advent of warm weather, particularly in humid, uncomfortable weather that presages the thunderstorm, the static level rises and becomes evident in as a raspy background to broadcast music or speech. Fortunately, however, it is very rare that the static is sufficiently powerful to interfere with the signals of present-day broadcasting stations within their service range.

It is obvious, then, that the signal must be of sufficient strength to override static interference by a fair margin. Broadcasters have long recognized this fact. Transmitting power has been steadily increased from the early days, when a 500-watt rating was considered ample for broadcasting over a wide area. Today, the 500-watt rating is recognized only for purely local service, with a limited service range throughout the year. Many times that power must and is being employed in Summer for a service range of about 100 miles and over, reaching out into the rural districts.

What is more, the rapid development of network broadcasting, making the best programs available in many parts of the country through local broadcasting stations, has had the greatest influence on popularizing summertime radio not only by providing sufficiently powerful signals, but also in maintaining the highest quality of entertainment.

The first essential in Summertime radio, then, is to tune in the most powerful signals available when conditions are least favorable.

Shorter Antenna

Give a sufficient ratio between signal and static levels, the radio listener can reduce the undesirable background by being satisfied with smaller volume from his loudspeaker.

Another effective method is to employ a smaller antenna. The antenna, nor-

mally 60 to 100 feet in length, may be cut down to 30 or 40 feet with sufficient pick-up to intercept powerful local signals during the Summer months. Or an indoor antenna may be substituted, consisting of 20 or 30 feet of wire stretched about the room behind the picture moulding, or otherwise placed about the house. A small fixed condenser of .0005 mfd. capacity, should be placed between the antenna and the ground binding posts of the receiver, to compensate for the reduced wavelength of the antenna, without causing material change in the dial settings of the receiver.

Interesting experiments may be performed with underground antennas, which are less subject to static pick-up. No. 14 rubber covered wire, such as is used for exposed wiring, may be buried several feet deep in a straight trench, and then covered over, with the end brought to the antenna binding post. Sometimes the ordinary gas pipe of the home will serve as a satisfactory Summertime antenna.

Loop Operation Excellent

In the early days of radio communication, two ground connections made at different depths underground so as to tap two different strata, were employed with fair results. The loop-operated receiver provides an almost ideal means of favoring signal as against static interference, because of its sensitive directional pick-up, enabling the operator to swing away from undesirable noises.

Aside from altering the receiving conditions, the volume of the loudspeaker rendition may be lowered so as to make the static background less conspicuous. In fact, most radio listeners do employ too much volume, and this is especially true in Summer reception. The average radio receiver has a satisfactory volume control that may be employed in reducing the loudspeaker volume to the desired degree, to drop out the static background. If the receiver is not provided with a volume control, then a variable high resistance of from zero to least 250,000 ohm range may be connected across the secondary of the first audio transformer as an effective and non-distorting volume control.

Filament Control Attacked

Turning the filaments of the receiver up or down does not constitute an efficient volume control. It should be noted that filaments must be operated at the proper voltage at all times, irrespective of the volume desired. Dimmed filaments may result in severe distortion, while excessively lighted filaments lead to greatly shortened life of tubes.

Distance never fails to add greater realism and maximum enchantment. If we may take this hint with our Summertime radio, do not fail to experiment in loudspeaker placement. The loudspeaker should be tried out in different rooms, with the listeners sitting at various distances. A marked improvement will be noted when the distance between loudspeaker and listeners is increased. Or, if weather permits, the loudspeaker may be brought outdoors, on the porch or even placed on the lawn of the country home. There is a positive thrill of freshness which never fails to arouse even the most blasé radio listener-in when the radio is brought outdoors for the first time.

Among the radio listener's Summertime

GERMANY TODAY



(Henry Miller)

A TYPICAL German radio installa-
single tuner serves to select the stat-
a multiplex tube amplifier steps up t-
speaker. Except for the cone the
radi-

equipment, then, should be an extension cord or at least some wire whereby the loudspeaker may be moved about the home and brought outdoors, if possible. Of course the purpose of the outdoor rendition is for the enjoyment of the immediate family and guests. The volume should be just sufficient for proper enjoyment, and at no time should it be so low as to disturb the neighborhood, for that is not the purpose of radio entertainment.

These suggestions will help greatly but it is taken for granted that the receiver is in good operating order. After the long and steady use over the indoor season, it is obvious that the receiver should be gone over and put into first-class condition.


First of all, the batteries, if the receiver operates on this form of power supply should be checked over. It is well to remember that dry batteries dry out quicker in Summer than in Winter, and if the batteries have already been in use for many months, the warm weather of Sum-

A Phonograph with Ser-

If you contemplate using an electrical pickup with your phonograph the audio amplifier of your radio receiver may be used to advantage and it will not be necessary to build a separate amplifier. As most of the electrical pickups on the market are supplied with a volume control it will not be necessary to alter the set in any way.

If the filaments of the tubes in the set are wired in series, the tube socket plug-in arrangement supplied with some of these units cannot be used, for if you remove one of the tubes from its socket all the others would go out. It would be best to connect the pickup across the primary of the first audio transformer.

Y LIKE U. S. IN 1922

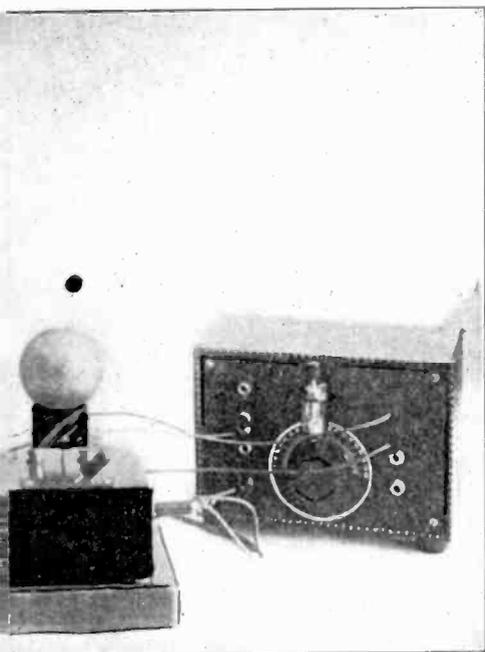

tion of today. A crystal receiver with a ion desired and to make it audible. Then he volume to make it loud enough for the installation is reminiscent of American in 1922.

Chopin First in Poll; Herbert Second Choice

Baltimore. Jazz devotees are growing fewer every day and the musical celebrities are once again ascending to the throne of public favor, according to a recent survey conducted by WBAL, Baltimore.

S. Broughton Tall, head of WBAL's literary and musical research department, has discovered that the works of Frederic Chopin are the most popular compositions on the air, records at this station showing this celebrated Polish composer has "appeared" before WBAL's microphone more frequently than any other musical writer in the world.

Last season, when a similar survey was made by Mr. Tall, it was discovered that the most popular composer at that time was Victor Herbert, one of the most distinguished of all American composers.

This season, however, it is found that Herbert has been displaced by Chopin, whose music breathes the delicacy of a poetic fancy, tinged with a glittering satire and a passionate melancholy, wrought, no doubt, from the deep emotions that stirred his being during his unfortunate romance with the domineering George Sand, famous novelist.

The next two most popular composers, according to WBAL's records, are both Americans—these are Victor Herbert and Edward MacDowell, the former being slightly more popular than the latter. This "musical survey" revealed a number of other interesting facts; for instance, Liszt

and Schubert rank equally in popularity, while Tschaikowski and Schumann rank together and Mozart and Brahms are in equal favor. Schumann, however, is far more popular than Schubert, while Tschaikowski leads all other Russian composers by a long way.

Following is a list of the most popular composers in the order of their popularity:

- | | |
|-----------------|-----------------|
| 1. Chopin | 12. Handel |
| 2. Herbert | 13. Mendelssohn |
| 3. MacDowell | 14. Massenet |
| 4. Beethoven | 15. Mozart |
| 5. Grieg | 16. Brahms |
| 6. Debussy | 17. Friml |
| 7. Tschaikowski | 18. Nevin |
| 8. Schumann | 19. Cadman |
| 9. Verdi | 20. Wagner |
| 10. Liszt | 21. Chaminade |
| 11. Schubert | 22. Puccini |

These are, of course, just a few of the 510 composers whose works have been heard over WBAL. Among other popular musical writers are: Bizet, Dvorak, Delibes, Hayden, Weber, Gounod, and the modern writers: Campbell Tipton, Teresa del Riego, Carrie Jacobs Bond, Horatio Parker, George Chadwick, A. Walter Kramer, Irving Berlin, and others. Of all the various types of music the negro spirituals seem to be decidedly the most popular, WBAL being one of the few stations on the air to exploit this particular form of American folk music.

Blows Sharkey Got K. O.'d McNamee Also

When Jack Dempsey, the Manassa Mauler, fought Jack Sharkey, the gabby gob from Boston, in the Yankee Stadium, New York City, more than 80,000 persons saw the fight from the ringside and 50,000,000 more heard it at their own firesides, or wherever they happened to be at the time. Radio brought Graham McNamee's blow-by-blow description of the fight to millions more persons than ever before focused their attention on any single event. The story sped with the velocity of light to every State in the Union and to many foreign countries. It went to ships at sea, to moving trains, to remote camps at the seashore and to the hearts of forests.

The 50,000,000 or more persons who heard the description of the fight as related by Mr. McNamee are indebted to the New York Telegram and 25 other Scripps-Howard newspapers throughout the country. Altogether 51 broadcast stations were connected up in this broadcast undertaking sponsored by Scripps-Howard interests. This is one more than was connected up on the occasion of Col. Lindbergh's reception in Washington and

constituted a new world's record.

Estelle Taylor, Dempsey's wife, sat in her home in Los Angeles and listened to McNamee's blow-by-blow description of the fight, and thus learned immediately the good news of victory which her husband scored. Mrs. Dempsey, the fighter's mother, listened in on a radio set back stage of a theatre in Salt Lake City.

On the other hand, Sharkey's wife had locked herself in a room in Hotel Bretton Hall in New York City, without the benefit of radio or telephone communication. By prearrangement a message carrying the news of the result was delivered to her immediately after the fight.

Had the vitally interested women known the outcome by intuition?

That there was a knockout is certain. Whether it was by fair means or foul the radio audience could not determine. McNamee, by the way, never gave any hint of a foul. Of one thing listeners were certain, and that was that Jack Sharkey was not the only individual knocked out in the excitement. McNamee was befuddled by the sudden turn of events long enough to be counted out.

WEIL IS SELECTED AGAIN

All advertising for the Fourth Annual Radio World's Fair, Madison Square Garden, New York, September 19-24, will again be handled by Paul S. Weil of Albert Frank & Co., advertising agency, Metropolitan newspapers, radio and allied trade papers will be used, Mr. Weil announced.

KOW SEEKS 1,500 WATTS

Washington. An error in an announcement by the Commission stipulated 2,500 watts as the power to be sought by KOW, Denver, which has asked for a public hearing August 4. The power it seeks is 1,500 watts in lieu of its present power of 200 watts on a frequency of 630 kilocycles.

oh Pickup ries Filaments

If you want to use the socket plug arrangement connect to it a fixed resistance of about 25 ohms. The resistance is connected across the two filament terminals of the plug. This will complete the circuit which would otherwise be broken.

When using the phonograph the radio frequency stages should be detuned to prevent any external interference. A scratch filter, such as manufactured by National, may be employed to remove the phonograph scratch from the music coming from the loudspeaker. Of course, this will not prevent hearing the scratch directly from the record, and for this reason the lid of the phonograph should be kept closed when playing.

Tip or Two to Aid You-All with the All-in-One Set

By Robert Frank Goodwin and Stuart Bruno

Consulting Engineers

Regarding the All-in-One Receiver, consisting of a 5-tube TRF set and a Q.R.S. ABC eliminator, published in the previous issue (July 30), the RF amplifier depends upon the design of the variable condensers, coils and tubes used. There are condensers and coils of many designs, both efficient and inefficient, and discretion must be used when purchasing the parts.

The construction of the receiver is greatly simplified by the elimination of rheostats and wiring the filaments in series. The series-wired set possibly possesses better stability than the battery operated receiver. Wiring the tubes in series may account for some of this, but the absolutely correct biasing of the grids of each tube and the steady voltage applied to the filaments supplied by the power unit can be credited with the superior performance of the All-in-One batteryless radio receiver. It is, of course, for installation on premises having AC.

During the first tests we noticed that the set was quite simple to tune and that it lacked the violent oscillations present in some battery types. Regeneration was noted in the higher waves. There was an absence of the hum generally inherent in sets employing the ordinary B eliminator. This is due to the proper design of the filter system.

Leads Go Through Bottom

The different leads coming from the supply unit and going to the receiver are brought through the holes at the bottom of the shield. It would be well to mark these holes so as to make it easy to trace the wires when checking. The wires connecting to the resistance bank and those nearby should be No. 18 asbestos covered. The lamps in the Mar-co illuminated control dials may be wired in parallel and a 50-ohm resistance shunted across; this is then to be wired in series with the filaments of the receiving tubes, negative end. The illumination of the dials is an added feature and may be disregarded if the fan so wishes.

After the set is placed in the cabinet the antenna and the ground wires may be brought from underneath and soldered to two Fahnestock clips placed on the back of the cabinet. The two leads from the transformer are brought from underneath the cabinet directly to the control box. The leads to the milliammeter in the control box are also brought through a small hole in the bottom of the cabinet. These may be drilled while the set is in the cabinet.

Where Voltmeter Comes in Handy

Before connecting the wires to the house current check the wiring carefully and make sure that everything is correct. Then turn the rheostat in the control box all the way to the right, insert the rectifier tube in its socket and all the other tubes. Connect to house current and turn the rheostat in the control box to the left until the milliammeter reads approximately 250 mils.

Before proceeding farther check all B and C voltages with the 0-500 voltmeter. This is done by connecting the negative lead of the meter to the negative terminal of the resistance bank. With the red or positive lead make contact to the various B terminals on the resistance bank and

determine whether each portion of the receiver is receiving its proper voltage.

The lead coming from the power tube should check 180 volts; if this should read less, due to line variations, we advise placing an additional 200-ohm resistance in series with the positive end of the top resistance unit and placing the leads formerly going to the large bank to the end of the additional resistance.

Do not make any voltage measurements unless the tubes are in the circuit with their filaments turned on. If the filaments of the tubes are turned off and the readings taken of the B voltages it will be noticed that the values are away off. To check the C voltages connect the positive end of the meter to A minus and the negative end of the meter to C-40; this should read 40 volts.

Insulating the Cabinet Lid

To insulate the cover of the cabinet from heat radiated by the tube and chokes it would be advisable to put a small piece of tin directly over these and raised from

the surface of the cover with washers. This will allow for the circulation of air. The heat will never rise to any dangerous points. A 1-ampere fuse may be placed in the primary circuit of the power transformer; this can be a cartridge type fuse and may be concealed in the control box. In the writers' set a metal cash box was used.

We have been advised by the manufacturer of the condensers [Dubilier] that the type PL-543 condenser block which contained two 5 mfd. condensers is now made up in two units and will occupy the same space.

The transformers T-2 and T-3 are mounted bottom to bottom and secured together by screws through the holes of their bases and supported to the base-board with two brackets. T-3 is placed on the top of T-2. The terminals P and G of T-2 are to face the front panel, while P and B of T-3 face the condenser C-1. Care should be taken to allow as much space between the transformer and condenser as possible. Two leads are brought from the output of T-3 and go to two Fahnestock clips on the back of the cabinet. These are for the loud speaker.

WTMJ TO JOIN CHAINS

WTMJ, owned and operated by the Milwaukee "Journal," will become a member of both the Red and Blue Networks maintained by the National Broadcasting Company at some date between August 15 and September 1.

Higher Plate Voltage Cuts Plate Impedance

It is generally understood that to get a flat amplification characteristic of the musical scale—that is, the bass notes are amplified as much as the high notes—the primary impedance of an audio transformer must be higher than the plate impedance of the tube. It is particularly important that we select a transformer of low ratio in the first stage.

Since the voltage used on the plate of the detector tube is in the neighborhood of 22½ to 40 volts, the plate impedance of this tube is very high. Since the inductance of a low ratio transformer is higher because of the greater number of primary turns, we also have a greater impedance.

Both May Be Low Ratio

The tube used in the first audio stage need not be a power tube, since this tube very seldom overloads. The second stage transformer can be of the same ratio as that of the first stage. This transformer will have a lower impedance when operated at a higher current in the plate circuit of the first stage amplifier tube. This is due to the fact that feeding a higher current in the primary of this

transformer has a tendency to lower the inductance and, as a consequence, the impedance (due to the D-C saturation of the core).

Now, since a high voltage is being applied to the plate of the first amplifier tube, the plate impedance of this tube is lower than that of the detector tube. It is plain that the impedance characteristic of the two transformers nearly match the operating impedances of the tubes with which they work.

Power Tube for Quality

The tube in the last stage is usually a power tube. When one hears the term "power tube" he immediately is inclined to think that this tube has a greater amplification constant than the ordinary amplifying tube. This is not so, for, as a matter of fact, the amplification factor of the -01A tube is eight while that of the 71 power tube is three.

The power tube is really used to handle power without distortion, rather than to amplify signals to any great extent. The 71 power tube has a maximum undistorted power output of fifty times that of the 01A tube.—R. F. G.

Murdock Licensed Under Group Patents

Announcement was made by D. R. W. Murdock, treasurer of the Wm. J. Murdock Company, 347 Washington Avenue, Chelsea, Mass., that the Murdock Company has signed a license agreement with the Radio Corporation of America which gives the manufacturers of Murdock Radio full right to manufacture under one hundred and forty or more radio patents held and controlled by the Radio Corporation of America, the General Electric Co., the Westinghouse

Electric & Mfg. Co., and the American Telephone & Telegraph Co.

The issuance of this license by the Radio Corporation of America places the Murdock Company in that select group of radio set manufacturers whose products are now licensed not only under these patents held by the Radio Corporation of America, and associated companies, but likewise under the patents controlled by the Hazeltine Corporation and the Latour Corporation.

Examples of Capacity of Receiving Antenna

(Continued from page 5)

than the range of the calibrated condenser, and it is particularly suitable for the measurement of small capacities. The second method is particularly suitable for measuring capacities between 100 and 1,000 micromicrofarads.

An example of the determination of the capacity and distributed inductance of an antenna by this method will help to make the method clear. The stations used in the determination were WEA and WGBS, operating respectively on 610 and 950 kilocycles. Thus F1 was 610 and F2 was 950 kilocycles. The inductances in the two cases as calculated from the turns used and the dimensions of the coil were respectively 255 and 95.3 microhenrys. The square of the ratio 610-950 is .4125, which according to the first formula is equal to the ratio $(95.3+L)/(255+L)$. Therefore the value of L is 17 microhenrys. When this value of L is substituted in the second formula together with the other known values, the capacity is found to be 250 micromicrofarads.

The capacity thus found includes the capacity of the coil and of the leads to the detecting circuit. The assumption is made that the capacity of the coil does not change when the number of turns is changed. This is allowable.

Use of Series Condenser

Since the capacity of this antenna is .00025 mfd. and the distributed inductance is 17 microhenrys, the natural frequency of the antenna is 2.44 megacycles. However, there will always be a loading coil in the antenna circuit which will lower the frequency at which the antenna might act as a wave trap, and this loading coil is the primary of the input transformer. Suppose that this is 20 microhenrys. The total inductance in the antenna is therefore 37 microhenrys, and

the frequency of oscillation or absorption is 1.65 megacycles. This is very close to the upper frequency limit of the broadcast range, which is 1.5 megacycles. Hence in this antenna the primary should not be made larger than 20 microhenrys, and in the interest of selectivity it should not be more than 15 microhenrys.

Another way of preventing the antenna circuit from being resonant in the broadcast range is to put a condenser in series with the primary. If this condenser is small the natural frequency of the antenna circuit will be so far removed from the broadcast range that no wave trap effect will be met. Still another way of overcoming the difficulty if it occurs is to put in a very large inductance in series with the antenna, so that the frequency of it will be much below the lowest frequency in the broadcast range. The inductance of this coil should be more than 3 millihenrys.

Turns—Inductance Table

As an aid in obtaining the inductance of a solenoid of 3-inch diameter when wound with No. 20 D. C. C. wire the following table is appended:

N	L	N	L
10	13.8	55	186.7
15	26.75	60	210.0
20	42.20	65	234.0
25	60.50	70	258
30	78.30	75	282
35	98.40	80	307
40	119.3	85	332
45	141.1	90	368
50	163.5	95	407

Intermediate values can be obtained from the tabular values by plotting a curve on a large scale and reading off the inductances opposite the given number of turns.

Watch Wire to Filaments of AC Tubes

(Continued from page 7)

than this would flow should be replaced if No. 18 had been used in the original wiring. As some of the new tubes draw two amperes each, quite large currents may flow in parts of the filament wiring carrying current for several tubes.

Another change which is necessary in all cases where a set is altered to accommodate the new tubes is the shifting of the plate and grid return connections. In the direct current types of tube the C+ and B- connections are made to one side of the filament.

Uses Step-Down Transformer

When using the five-prong type of AC tube, the C+ and B- connections are made to the fifth prong. In the other type of tube, using the UX base, the center of the resistance across the filament is used for the C+ and B- connections.

All the new tubes operate on low voltage and a transformer is required between the line and the tube. The transformer should be designed to provide a higher voltage than the tube requires, to allow for voltage drops in the wiring. Rheostats will be required, but once set no further adjustment will be necessary, so that rheostats may be placed behind the panel.

While variations may be necessary to meet the requirements of individual receivers, the diagram of filament wiring for a typical four-tube receiver (Fig. 1) will be a useful guide in changing over a receiver for the new tubes. No other changes will be required than in the circuits shown.

Wire Sizes and Current

These data will be found helpful in determining the size of wire to use in rewiring filament circuits for AC operation:

Size	Diameter (Mils)*	Current
12	80	20 amperes
14	64	11 amperes
16	51	6 amperes
18	40	3 amperes
20	32	1.5 amperes

*Mil=0.001 inch.

THE NEW AC TUBES

Everybody should have on hand for ready reference full data on the new AC tubes. The filaments of these tubes are heated by alternating current from a step-down transformer and anybody having AC can put these tubes into a set by making some wiring changes. Those who have AC and who are about to build a set also should possess this full information. Send 15c for the June 4 issue that contains the data on the AC tubes and also on two new rectifier tubes for B eliminators. Radio World, 145 W. 45th St., N. Y. C.

NEW CORPORATIONS

Atwater Kent, Wilmington, Del. (Corporation Trust of America), 10,000 shares no par.

Standard Telephone Co., Philadelphia, Pa. (Corporation Guarantee & Trust Co.), \$100,000.

J. A. Zavorski, Wilmington, Del., Electrical equipment (Corporation Trust Co. of America), \$5,000.

Grid Battery Is Called Vital in Portable Sets

(Continued from page 6)

be when low weight is absolutely necessary. A grid battery must be used at all times because it not only saves the B battery but it also saves the quality of reproduction of the receiver.

Stability is Excellent

One by-pass condenser C4 of .001 mfd. is connected across the primary of the first audio transformer and another by-pass condenser C5 of .01 mfd. is connected across that portion of the B battery which is serving the R. F. tube.

Stability of operation of the receiver is aided by grounding the cores of the three audio transformers and also by grounding the metallic box in which the receiver is built.

THE 5-TUBE DIAMOND

Fully described by Herman Bernard in a booklet, with diagrams, including blueprint, and sent on receipt of 25 cents. The Diamond is automatically adaptable to phonograph pickup. RADIO WORLD, 145 West 45th St., N. Y. City.

All the batteries are placed in a metal cash box of exactly the same specifications as the receiver box. The battery leads are cabled and brought from one box to the other through holes lined with hard rubber bushings to prevent short-circuits. The antenna and loud speaker leads are similar brought out of the receiver case through rubber lined holes.

In laying out the parts on the baseboard due regard should be given to balance of the set, in view of the fact that the set is to be carried. If the parts are suitably placed the weight of the set will be distributed evenly and no difficulty will be experienced in carrying the box.

(Other Photo on Front Cover)

CONNECTION FOR -00A TUBE

When inserting an -00A type detector tube, in place of the -01A tube, it is advisable that the grid return be changed. Instead of the return being made to plus A or plus filament, it is brought to the minus filament post on the socket. Unless this is done sensitivity is sacrificed.

SIXTH YEAR

RADIO WORLD

The First and Only National Radio Weekly

Member, Radio Publishers Association

Radio World's Slogan: "A radio set for every home."

TELEPHONES: BRYANT 0558, 0559
 PUBLISHED EVERY WEDNESDAY
 (Dated Saturday of same week)
 FROM PUBLICATION OFFICE
 HENNESSY RADIO PUBLICATIONS CORPORATION
 145 WEST 45TH STREET, NEW YORK, N. Y.
 (Just East of Broadway)
 ROLAND BURKE HENNESSY, President
 M. B. HENNESSY, Vice-President
 HERMAN BERNARD, Secretary
 European Representatives: The International News Co.
 Breems Bldgs., Chancery Lane, London, Eng.
 Paris, France; Brentano's, 8 Avenue de l'Opera

EDITOR, Roland Burke Hennessy
 MANAGING EDITOR, Herman Bernard
 TECHNICAL EDITOR, Lewis Winnar

CONTRIBUTING EDITORS:
 J. E. Anderson, Capt. Peter V. O'Rourke, and
 James H. Carroll

SUBSCRIPTION RATES

Fifteen cents a copy, \$6.00 a year, \$3.00 for six months, \$1.50 for three months. Add \$1.00 a year extra for foreign postage. Canada, 50 cents.

Receipt by new subscribers of the first copy of RADIO WORLD mailed to them after sending in their order is automatic acknowledgment of their subscription order. Changes of address should be received at this office two weeks before date of publication. Always give old address; also state whether subscription is new or a renewal.

ADVERTISING RATES

General Advertising

1 Page, 7 1/2" x 11"	462 lines.....	\$300.00
1/2 Page, 7 1/2" x 5 1/2"	231 lines.....	150.00
1/2 Page, 8 1/2" D. C.	231 lines.....	150.00
1/2 Page, 4 1/2" D. C.	115 lines.....	75.00
1 Column, 2 1/2" x 11"	154 lines.....	100.00
1 Inch.....		10.00
Per Ad Line.....		.75

Time Discount

52 consecutive issues.....	20%
28 times consecutively or E. O. W. one year.....	15%
4 consecutive issues.....	10%

WEEKLY, dated each Saturday, published Wednesday.
 Advertising forms close Tuesday, eleven days in advance of date of issue.

CLASSIFIED ADVERTISEMENTS

Ten cents per word. Minimum 10 words. Cash with order. Business Opportunities ten cents per word, \$1.00 minimum

Entered as second-class matter March 23, 1922, at the Post Office at New York, N. Y., under the Act of March 3, 1879.

National Radio Day Proposed for Sept. 21

The Radio Industries Banquet Committee, regulating and operating the Fourth Annual Radio Industries Banquet, after three months of active work in planning the program for the banquet has decided that the broadcasting of this program will be of sufficient interest to justify the designation of Wednesday, September 21, as National Radio Day for the United States.

The banquet program, as in the past, will be broadcast by a tremendous chain of stations. On the occasion of the third annual banquet last year the record of 42 stations operating on the same program at the same time was established. This was not beaten until Lindbergh Day. The broadcasting committee for the Fourth Annual Banquet announces the intention of lining up at least sixty broadcasters for this year's program.

L. A. Nixon and Associates will handle the management and publicity of the Radio Industries Banquet and National Radio Day.

FITZNER APPOINTED

The International Resistance Company, Philadelphia, announced the appointment of B. J. Fitzner, 159 E. Elizabeth Street, Detroit, Mich., as sales representative.

Board Explores Air, Hands Self Bouquets

Washington.

General satisfactory conditions in both the third and fourth radio zones of the United States are reported by the respective members of the Federal Radio Commission from those districts, Eugene O. Sykes and H. A. Bellows, who have just returned from inspection trips lasting about one month.

With the exception of scattered complaints, broadcasting and reception throughout the South and Middle West, embraced in these zones, were described as good. Listeners were reported to be well satisfied with Summer reception, which they generally agreed has improved, and most of the broadcasters are raising no objections to the frequencies assigned them by the Federal Radio Commission under the June 15 allocations.

The Commissioners returned in time to join with Admiral W. H. G. Bullard, chairman, and Commissioner O. H. Caldwell, of New York, to conduct public hearings on 19 applications filed by as many stations for changes in wavelength or power.

South Fares Well

Judge Sykes, in an oral statement, asserted that both broadcasting and reception in the South are quite good, although static is bad on account of the season. He said he spent a large part of his time away from Washington at his home in Jackson, Miss., where many broadcasters conferred with him on broadcasting problems.

"Everybody says we have improved conditions very much," said Judge Sykes. "There are some problems left to us down there, but in general everything is quite satisfactory and listeners are satisfied."

In the 11 States which his district embraces, said Judge Sykes, there are from 75 to 100 applicants who would like to build new stations, and some were said to have good claims to right to build such stations in order to furnish local programs. However, the Commission has taken the stand that no construction permits for new stations will be issued.

The states in Judge Sykes' zone are North Carolina, South Carolina, Georgia, Florida, Alabama, Tennessee, Mississippi, Arkansas, Louisiana, Texas and Oklahoma.

Middle West Has Problems

Mr. Bellows' zone comprises the States of Indiana, Illinois, Wisconsin, Minnesota, North Dakota, Iowa, Nebraska, Kansas and Missouri. With Chicago, it includes a large share of the program stations of the country and many of the large broadcasters.

There are a number of problems which must be faced in the Middle West, said Commissioner Bellows. Notably, these are matters of interference between stations, constancy of frequency, and dissatisfaction with assigned wavelengths. Public hearings before the Commission

will settle many of these difficulties, in Mr. Bellows' opinion.

The schedule of hearings was augmented by the application of WSEA, Virginia Beach, Va., which seeks a frequency of 680 kilocycles in lieu of its assignment to 1,370. Stations that have been notified to appear at the hearing because they are on or near the frequency applied for are: WJR and WCX, Pontiac, Mich., and WEEI, Boston. NAA, Arlington, operated by the United States Navy, was also notified.

Opening the docket of hearings before the Commission are the applications of WFRL, New York City, and WFBE, Cincinnati.

WFRL seeks a frequency of 1,170 kilocycles instead of its assigned frequency of 1,370 kilocycles, 500 watts. The following stations were notified to appear: WBBR, Rossville, N. Y.; WJBI, Red Bank, N. J., and WEBJ, New York.

WFBE seeks an increase in power from 250 to 500 watts on a frequency of 1,220 kilocycles. Notified to appear were WGBB, Freeport, N. Y.; WAAT, Jersey City; WSOM, New York; KFH, Wichita, Kan.; WHDI and WLB, Minneapolis, and WDOD, Chattanooga, Tenn.

Some News from First District

Orestes H. Caldwell, of New York, reported for his district:

"Local conditions in the cities I visited are much better. It is still difficult to determine how far some of the stations cover. Strange to say, several of the more powerful transmitters up-State, which we might think would cover at least 100 miles, only get out about forty to sixty miles. Reception in Buffalo is in fine shape and every one seems to be well pleased.

"Although Canadian stations are not far distant from several broadcasters in Western New York, there is only one complaint, and that is against one station within ten kilocycles of a New York State transmitter. However, I think we can straighten it out easily."

WGR Not Faring So Well

Mr. Caldwell said that station WGR of Buffalo has received reports that the waves do not get out as well on the present wave of 303 meters. It was formerly on 319 meters. He said that the Summer weather, which reduces the range of stations, might be responsible.

"We plan to hold more public hearings in Washington," said Mr. Caldwell. "Most of the hearings will deal with power outputs rather than requests for wavelength changes.

"Judge Rutherford of WBBR on Staten Island has applied to the District Court in Washington to get part time on WJZ's wave. He is not contesting the law but following it. The Commission ruled that WBBR should not share WJZ's channel, but under the Radio act of 1927 a station can appeal to the court in an effort to reverse the Commission's decision."

Klemm Dedicates Song to His Station's Tenor

Baltimore.

A new song that bids fair to be one of the popular hits of the late summer, has just been written by Gustav Klemm, program supervisor at WBAL, Baltimore's super power station. This song, entitled "A Vagabond Am I," was dedicated to John Wilbourn, WBAL staff tenor, who sang it over the air for the first time a few weeks ago. The song will be published this month, Mr. Klemm advised friends.

Klemm has been program supervisor

of WBAL ever since this station first went on the air in November, 1925. Prior to joining the staff of this station, Mr. Klemm was conductor of the City Park Band, and his composition work had already given him a very definite place among the American composers. Mr. Klemm studied composition with Victor Herbert and also with Gustav Strube at the Peabody Conservatory of Music. Mr. Klemm's song, "It's Me," a negro spiritual, is now being featured by Roland Hayes in programs abroad.

Many Stations Far Off Wave

Washington.

Preliminary reports received by the Radio Division of the Department of Commerce and transmitted to the Federal Radio Commission indicate that a large percentage of the broadcasting stations of the United States are transmitting their programs off their assigned frequencies. Lack of frequency control apparatus in the transmitters is ascribed as the reason for the deviations, which, it was stated at headquarters of the Commission, are causing much needless interference in the ether.

Radio inspectors of the Department of Commerce have submitted reports which point out specific cases of deviation from assigned frequencies, involving some of the largest broadcasting stations in the country. The order of the Federal Radio Commission is to the effect that stations may not deviate more than 500 cycles, (one-half kilocycle above or below their assignments).

Wide Deviation

Reported deviations indicate many stations as far off their frequencies as five kilocycles, some as high as 10 and 15 and at least one station is reported to have gone 25 kilocycles away on account of an unstable antenna.

It is the intention of the Commission, it was stated, to enforce its order when consistent violations are detected. The Commission has recommended the installation in all stations of crystal controls or meters which measure the frequency and maintain it at standard. Up to now, the manufacturers have reported to Washington that they have been unable to meet their orders for crystals, which maintain practically an absolute frequency, but a leading Boston firm has advised Commissioner Caldwell that it is now able to fill several hundred orders which it has on hand.

Will Act Soon

Installation of these controls is not expensive for broadcasting stations, but requires considerable adjustment of apparatus. When the controls are installed, it is anticipated that much of the hetro-dyning now being checked against stations will have been eliminated.

From Commission headquarters, however, it is announced that the Commission intends to enforce its order permitting no more than one kilocycle leeway to broadcasters. As soon as the entire Commission returns to Washington from the field survey now being conducted, this matter will be taken up. The revocation of licenses may be ordered under the law by stations violating the Commission's order.

Victoreen Moves To Bigger Factory

The Victoreen Radio Co., and their merchandising company, the George W. Walker Co., have moved to 2825 Chester Ave., Cleveland, Ohio. Their former factory became entirely inadequate to meet production demands for the coming season.

The new factory has approximately three times the floor space of the other and is so arranged that additional space may be used when necessary. The Walker Co., from reports of their jobbers and dealers, will have a very successful radio season and every effort is being made in advance to anticipate the early season demand.

WBBR Sues for Right To Choose Own Wave

Washington.

Notice of appeal from the decision of the Federal Radio Commission, denying the applications of WBBR, of Rossville, N. Y., for change in its assignment of frequency, was filed in the Court of Appeals of the District of Columbia. The notice, entered by Frederick W. Sparks, of Brooklyn, attorney for the Peoples Pulpit Association, owners and operators of the broadcasting station, asked for a temporary injunction restraining the Commission from interfering with WBBR's use of the frequency of 660 kilocycles (454.3 meters) or 720 kilocycles (416.4 meters), to either of which channels, it maintains, it is entitled under the Communications Act of 1912.

Constitutionality of the Radio Act of 1927 is not questioned in the WBBR case, which was the subject of recent public hearings before the full Commission which decided against its applications for a different wave length and ordered it to remain on its assigned frequency of 1,170 kilocycles (256.3 meters) under the June 15 allocations.

The appeal denies the power of the

Commission to shift it from the frequencies it formerly used, stating that it was entitled to one of them by virtue of "pre-emption right and user." It is also stated that the act of the Federal Radio Commission in assigning it to a different wave length amounted to a confiscation of property rights in violation of the Constitution. The value of WBBR is given as \$140,000.

The appellants further argue that no order or proceeding has ever been made by the Commission to show that a change in the wavelength of WBBR would promote the public convenience or interest, stating that the appellant's license under the Communications Act of 1912, under which it was permitted to operate on 720 kilocycles, has never been revoked.

This phase of the suit is expected to be one of the tests of the validity of the Radio Act of 1927, which in effect superseded the Communication Law of 1912, after the Attorney General in July, 1926, decided that the Department of Commerce was powerless to regulate radio under the 1912 laws.

Fans are greatly interested.

A Portable with a Novel Speaker

(Concluded from page 4)

hence it is not necessary to place the control on the panel.

The high-pitched squeal in the set is due to feedback of energy through the batteries, leads, and mutual coupling between the transformers. Usually the feedback is not sufficient to cause oscillation at more than one frequency where phase relations are right. If the amount of energy fed back can be controlled by varying the amplification or otherwise the squeal can be stopped.

By means of the variable resistor across the secondary of T2 the amplification can be reduced until the squealing stops. Only a small reduction is necessary in most cases to stop the oscillation.

The reason the amplification is reduced by connecting a resistance across the secondary is found in the regulation of the transformer. Most audio frequency transformers are designed to work into an infinite impedance. For that reason it does not matter how high the resistance of the secondary winding is. Often the resistance is around 5,000 ohms. When a resistance is connected across the secondary a current flows. The voltage in the transformer is then divided between the resistance of the transformer winding and the resistance connected across the terminals. It is only such part of the total voltage which drops in the external resistance which is effective on the grid, and this is always less than the total as long as any current flows. When no resistance is connected across the terminals, no current flows, and then there is no voltage drop in the transformer winding, and all the voltage induced in the secondary is effective on the grid. It should be pointed out that the resistance slightly improves the quality of reproduction of the amplifier.

Small Drain

The filament current is limited by Amperites A1, A2, A3. Each of these is a No. 4V-199, suitable for 99 type tubes when the voltage source is 4 to 4½ volts. This voltage is supplied by three No. 6 dry cells, series-connected. The filament current consumption is only .018 ampere.

A grid bias battery is required to give the grids of the two amplifier tubes the

correct bias. Since both of these tubes have the same effective plate voltage and they are both the same type, they may have the same grid bias. Hence the grid return leads from these tubes have been joined to the negative terminal of the C battery. This battery should preferably be small type 4½ volt battery, but one of the 6-volt units can be used, for it takes up less width, though it is slightly longer.

The panel is 7x14 inches and is of hard rubber. On this are mounted the two tuning condensers C1 and C2, the three-circuit tuner and the filament switch, together with the appropriate knobs and dials.

Optional Type C Battery

The radio frequency choke coil is near the panel, between first tuning condenser and the three-circuit tuner. By-pass condensers are placed in various suitable positions.

A two-cell battery of small dry cells can be seen mounted in clips in the middle of the baseboard. This constitutes a three-volt C battery, which may replace the C battery previously discussed, if there is no room in the regular battery compartment underneath. But you will find sufficient room indeed if you follow directions.

A unique feature of this receiver is the manner in which the loudspeaker has been built in. The double magnet driver unit can be seen near the right end of the box secured by a stiff brass mounting. A coupling rod runs from the unit to the back wall of the set, which is used as the sound radiating surface. Since the sounding surface must be very thin, the back of the set will not be strong.

This can be remedied in the following way:

May Use Balsa Wood

First a substantial back wall is put in place and a small hole cut in it opposite the driving rod. Two ¼-inch strips of wood are glued at left and right, to this board, inside the box. Then a sheet of Lata Balsa wood is mounted to the strips and the coupling unit fastened to the Balsa wood. Of course, this leaves full protection for the sounding surface, i. e., the outer wall.

LIST OF STATIONS

With new wavelengths, frequencies, location and power, corrected to July 27. Time sharers in parentheses.

Table listing radio stations with columns for Station, Kc, M, Watts, and Station, Kc, M, Watts. Includes entries like WDRS-New Haven, Conn. (WCAC), WJAZ-Mt. Prospect, Ill. (WMBI), and WOD-Chatanooga, Tenn.

Station	Kc	M	Watts	Station	Kc	M	Watts	Station	Kc	M	Watts
WNBH—New Bedford, Mass.	1150	260.7	250	KELW—Burbank, Calif. (KPPC)	1310	228.9	250	KGDR—San Antonio, Texas	1480	202.6	15
WNBJ—Knoxville, Tenn.	1450	206.8	50	KEX—Portland, Ore.	1250	239.9	2500	KGDW—Humboldt, Nebr.	1450	206.8	100
WNBL—Bloomington, Ill. (WMBY)	1500	199.9	15	KFAB—Lincoln, Nebr. (5000 before 7 p. m.)	970	309.1	2000	KGDY—Shreveport, La.	1410	216.6	250
WNBO—Washington, Pa.	1420	211.1	15	KFAD—Phoenix, Ariz.	1100	272.6	500	KGEF—Los Angeles, Calif.	1450	206.8	15
WNBQ—Rochester, N. Y.	1480	202.6	15	KFAU—Boise, Idaho (4,000 watts daytime)	1050	285.5	2000	KGEH—Eugene, Ore.	1490	201.6	50
WNBW—Memphis, Tenn.	1310	228.9	20	KFBB—Havre, Mont.	1090	275.1	50	KGEK—Yuma, Colo.	1470	204.8	10
WNBZ—Newark, N. J. (WGCP)	1070	256.3	500	KFCB—San Diego, Calif.	1210	247.8	100	KGEN—El Centro, Calif.	1330	225.4	15
WNOX—Knoxville, Tenn.	1130	265.3	1000	KFBK—Sacramento, Calif.	560	535.4	100	KGEQ—Grand Island, Nebr.	1460	208.4	100
WNRC—Greensboro, N. C.	1340	223.7	500	KFBL—Everett, Wash.	1340	223.7	50	KGER—Long Beach, Calif. (KRLO)	1390	218.7	100
WNYC—New York, N. Y.	1050	302.8	2000	KFBS—Trinidad, Colo.	1260	238.0	15	KGES—Central City, Nebr.	1470	204.4	10
WOAI—San Antonio, Texas	1060	260.7	250	KFBW—Laramie, Wyo.	700	428.3	500	KGEU—Lower Lake, Calif.	1320	227.1	50
WOAN—Lawrenceburg, Tenn.	1250	239.9	500	KFCB—Phoenix, Ariz.	1230	243.8	125	KGEW—Fort Morgan, Colo.	1370	218.1	10
WOAX—Trenton, N. J. (WEAM)	850	352.7	5000	KFCR—Santa Barbara, Calif.	1420	211.1	50	KGEY—Denver, Colo.	1490	201.6	15
WOC—Davenport, Iowa	1340	223.7	25	KFDM—Beaumont, Texas	800	374.8	500	KGEZ—Kalispell, Mont.	1460	205.4	100
WOCJ—Jamestown, N. Y.	1020	293.9	1000	KFDK—Shreveport, La.	1270	236.1	250	KGFB—Iowa City, Iowa	1340	223.7	10
WODA—Paterson, N. J. (WGL)	1130	265.3	2500	KFDY—Brookings, S. Dak.	760	394.5	500	KGFF—Ava, Okla.	1460	205.4	25
WOI—Amaes, Iowa; 5000, daytime, 6 to 6 (WSUI)	1130	252.0	5000	KFDZ—Minneapolis, Minn.	1300	215.7	10	KGFG—Oklahoma City, Okla. (KGCB)	1390	215.7	50
WOK—Chicago, Ill. (WMBB)	1190	252.0	250	KFEC—Portland, Ore. (KFIF)	1400	214.2	50	KGFH—La Crescenta, Cal. (KMIC)	1340	223.7	100
WOKO—Peekskill, N. Y.	1390	215.7	250	KFEL—Denver, Colo.	1210	247.8	250	KGFI—Ft. Stockton, Tex.	1360	220.4	15
WOKT—Rochester, N. Y.	1430	209.7	500	KFEQ—St. Joseph, Mo.	1300	230.6	1000	KGFJ—Los Angeles, Calif. (KFVD)	1440	208.2	100
WOMT—Manitowoc, Wis.	1350	221.1	50	KFEY—Kelllogg, Idaho	1290	232.4	100	KGFK—Haltom, Minn.	1340	223.7	50
WOO—Philadelphia, Pa. (WIP)	590	508.2	500	KFEZ—St. Joseph, Mo.	1300	230.6	1000	KGFL—Trinidad, Colo.	1350	222.1	50
WOOD—Furnwood, Mich.	1150	260.7	500	KFH—Wichita, Kansas	1220	245.8	500	KGFM—Yuba City, Calif.	1420	211.1	15
WOQ—Kansas City, Mo. (WHB)	890	336.9	250	KFHA—Gunnison, Colo.	1180	254.1	500	KGFN—Aneta, N. Dak.	1500	199.9	15
WOR—Newark, N. J.	710	422.3	500	KFHL—Oskaloosa, Iowa	1410	212.6	100	KGFO—Terra Haute, Ind.	1470	204.0	100
WORD—Batavia, Ill. (WTAS)	1090	275.1	5000	KFI—Los Angeles, Calif.	640	468.5	5000	KGFP—Mitchell, So. Dak.	1410	212.6	10
WOS—Jefferson City, Mo.	760	394.5	500	KFIF—Portland, Ore. (KPEC)	1400	214.2	50	KGO—Oakland, Calif.	1780	384.6	5000
WOW—Omaha, Nebr.	590	508.2	1000	KFIO—Spokane, Wash. (KEPY)	1220	245.8	100	KGRC—San Antonio, Texas (KGCI)	1360	220.4	50
WOWO—Ft. Wayne, Ind. (WCWK)	1310	228.9	1000	KFIQ—Yakima, Wash.	1440	208.2	100	KGRS—Amarillo, Texas	1230	243.8	150
WPAB—Norfolk, Va.	1430	209.7	100	KFIU—Juneau, Alaska	1330	225.4	100	KGTT—San Francisco, Calif.	1450	206.8	50
WPCC—Chicago, Ill. (WFEB, WCRW)	1340	223.7	500	KFIZ—Fond du Lac, Wisc.	1120	267.7	100	KGU—Honolulu, T. H.	1110	270.1	600
WPCH—New York, N. Y. (WRNY)	970	309.1	500	KFJB—Marshalltown, Iowa	1210	247.8	150	KGW—Portland, Ore.	610	491.5	1000
WPDQ—Buffalo, N. Y. (WSVS)	1460	205.4	50	KFJF—Oklahoma, Okla.	1100	272.6	750	KGY—Lacey, Wash.	1230	243.8	50
WPEP—Waukegan, Ill.	1390	215.7	250	KFJI—Astoria, Ore.	1200	249.9	15	KHJ—Los Angeles, Calif.	740	405.2	500
WPG—Atlantic City, N. J. (WHAR)	1100	272.6	2500	KFJM—Grand Forks, N. Dak.	900	333.1	100	KHO—Spokane, Wash.	810	370.2	1000
WPRC—Harrisburg, Pa.	1430	209.7	100	KFJR—Portland, Ore. (KTBR)	1060	282.8	100	KIK—Anita, Iowa	650	461.3	100
WPSC—State College, Pa. (WBAK)	1000	299.8	500	KFJY—Ft. Dodge, Iowa	1250	239.9	100	KJBS—San Francisco, Calif.	1360	220.4	50
WPSW—Philadelphia, Pa.	1480	202.6	50	KFJZ—Fort Worth, Texas	1200	249.9	50	KJR—Seattle, Wash.	860	348.6	2500
WQAA—Parkersburg, Pa.	1390	215.7	500	KFKA—Greeley, Colo.	750	399.8	200	KKP—Seattle, Wash.	1130	265.3	15
WQAE—Springfield, Vt.	1200	249.9	50	KFKB—Milford, Kansas	1240	241.8	1000	KLDS—Independence, Mo.	1260	238.0	150
WQAM—Miami, Fla.	930	322.4	750	KFKU—Lawrence, Kansas (WREN)	1180	254.1	500	KLIT—Portland, Oregon	1450	206.8	10
WQAN—Scranton, Pa. (WGBI)	1300	230.6	100	KFKX—Hastings, Nebr. (KYW)	570	526.0	2500	KLS—Oakland, Calif. (KZM)	1220	245.8	250
WQAO—WPA—Cliffside, N. J. (WHN)	760	394.5	500	KFKZ—Kirkville, Mo.	1330	225.4	15	KLX—Oakland, Calif.	590	508.2	500
WQJ—Chicago, Ill. (WMAQ)	670	447.5	500	KFLR—Albuquerque, N. M.	720	416.4	100	KLZ—Denver, Colo.	1120	267.7	250
WRAF—La Porte, Ind.	1400	208.2	100	KFLU—San Benito, Texas	1270	236.1	15	KMA—Shenandoah, Iowa (KFNF)	1110	270.1	500
WRAH—Providence, R. I.	1500	199.9	250	KFLV—Rockford, Ill.	1120	267.7	100	KMED—Medford, Oregon	1120	267.7	50
WRAC—Escabana, Mich.	1050	282.8	50	KFLX—Galveston, Texas	1110	270.1	100	KMIC—Inglewood, Calif. (KGFH)	1340	223.7	250
WRAM—Galesburg, Ill. (WFZ)	1210	247.8	50	KFMR—Sioux City, Iowa	680	440.9	100	KMJ—Fresno, Calif.	820	365.6	50
WRAY—Yellow Springs, Ohio	880	340.7	100	KFMX—Northfield, Minn. (WCAL)	1270	236.1	500	KMMJ—Clay City, Neb. (WCAJ)	790	379.5	500
WRAX—Reading, Pa.	1260	238.0	50	KFNE—Shenandoah, Iowa (KMA)	1110	270.1	1000	KMO—Tacoma, Wash.	1180	254.1	250
WRAY—Philadelphia, Pa. (WNAT)	1040	283.5	250	KFOA—Seattle, Wash.	670	447.5	1000	KMOX—St. Louis, Mo.	1000	269.8	5000
WRBC—Valparaiso, Ind.	1260	238.0	50	KFOR—Long Beach, Calif.	1240	241.8	500	KMTR—Los Angeles, Calif.	570	526.0	500
WRD—Washington, D. C.	640	468.5	500	KFOR—Lincoln, Nebr.	1380	217.3	100	KNRC—Santa Monica, Calif.	800	374.8	500
WRD—Raleigh, N. C.	1380	217.3	250	KFOX—Omaha, Nebraska (KOCH, WNAL)	1160	258.5	100	KNX—Los Angeles, Calif.	890	336.9	500
WRD—Memphis, Tenn.	1180	254.1	50	KFOY—St. Paul, Minn.	1050	285.5	100	KOA—Denver, Colo. (10,000 until 7 p. m.)	920	325.9	5000
WRE—Lawrence, Kans. (KFKU)	1180	254.1	750	KFPL—Dublin, Texas	1090	275.1	15	KOAC—Corvallis, Ore.	1110	270.1	500
WRE—Lansing, Mich.	1300	230.6	500	KFPM—Greenville, Texas	1300	230.6	15	KOB—State College, N. M. (KWSC, KTW)	760	394.5	5000
WRE—Quincy, Mass.	1380	217.3	50	KFPR—Los Angeles, Calif. (KFQZ)	1290	232.4	250	KOCH—Omaha, Nebr. (WNAL, KFOX)	1160	258.5	250
WRHF—Washington, D. C. (Daytime only)	940	319.0	50	KFPW—Carterville, Mo.	1140	263.0	50	KOCW—Chickasha, Okla.	1190	252.0	250
WRHM—Minneapolis, Minn. (WDGY)	1150	260.7	1000	KFPY—Spokane, Wash. (KFIO)	1220	245.8	250	KOIL—Council Bluffs, Iowa	1080	277.6	1500
WRM—Urbana, Ill.; 1000 watts before 6 p. m. (WBAA)	1100	272.6	500	KFQA—St. Louis, Mo.	930	322.4	50	KOIN—Portland, Ore.	940	319.0	1000
WRMU—New York, N. Y. (Portable)	1490	201.6	100	KFQB—Ft. Worth, Texas	1150	260.7	1000	KOLO—Durango, Colo.	1500	199.9	5
WRNY—New York, N. Y. (WPCH)	970	309.1	500	KFQD—Anchorage, Alaska	870	344.6	100	KOMO—Seattle, Wash.	980	305.9	1000
WRPI—Terre Haute, Ind.	1440	208.2	100	KFQW—Holy City, Calif.	1200	249.9	100	KOWW—Walla Walla, Wash.	1000	299.8	500
WRR—Dallas, Texas	850	352.7	500	KFQZ—Hollywood, Calif. (KFPR)	1290	232.4	100	KPCB—Seattle, Wash. (KGCL)	1300	230.6	50
WRRS—Racine, Wis.	930	322.4	50	KFRC—San Francisco, Calif.	660	454.3	500	KPJM—Prescott, Ariz.	1400	214.2	15
WRSC—Chelsea, Mass.	1460	205.4	15	KFRU—Columbia, Mo.	1200	249.9	500	KPNP—Muscatine, Iowa	1420	211.1	100
WRST—Bay Shore, N. Y. (WCDA, WBRS, WCGU)	1420	211.1	250	KFSD—San Diego, Calif.	680	440.9	500	KPO—San Francisco, Calif.	710	422.3	1000
WRVA—Richmond, Va.	1420	211.1	250	KFSG—Los Angeles, Calif.	1090	275.1	500	KPPC—Pasadena, Calif. (KELW)	1310	228.9	50
WSAI—Cincinnati, O.	830	361.2	5000	KFUL—Galveston, Texas	1160	258.5	500	KPRC—Houston, Texas	1020	293.9	500
WSAJ—Grove City, Pa.	1340	223.7	250	KFUM—Colorado Springs, Colo.	1270	236.1	100	KPSN—Pasadena, Calif.	950	315.6	1000
WSAN—Allentown, Pa. (WCBA)	1350	222.1	100	KFUO—St. Louis, Mo. (KSD)	550	545.1	500	KQV—Pittsburgh, Pa. (WJAS)	1110	270.1	500
WSAR—Fall River, Mass.	1190	252.0	100	KFUP—Denver, Colo.	1320	227.1	100	KQW—San Jose, Calif.	1010	296.9	500
WSAX—Chicago, Ill.	1470	204.0	100	KFUS—Ogden, Utah	1330	225.4	50	KRAC—Shreveport, La.	1360	220.4	50
WSAZ—Huntington, W. Va.	1240	241.8	100	KFUT—Salt Lake City, Utah	600	497.7	50	KRE—Berkeley, Calif. (KFUS)	1170	256.3	100
WSB—Atlanta, Ga.	630	475.9	1000	KFV—Venice, Calif. (KGFJ)	1440	208.2	250	KRLD—Dallas, Texas	1350	222.1	500
WSBC—Chicago, Ill. (WWAE)	1290	232.4	500	KFVD—St. Louis, Mo.	1280	234.2	1000	KRLO—Los Angeles, Calif. (KGER)	1390	217.3	250
WSBT—New Bend, Ind. (WEMC)	1350	222.1	250	KFVG—Independence, Kans.	1330	225.4	50	KROX—Seattle, Wash. (KRSC)	1420	211.1	50
WSDA—New York, N. Y. (WARS, WBBC)	1320	227.1	250	KFVI—Houston, Texas	1260	238.0	50	KRSC—Seattle, Wash. (KROX)	1420	211.1	50
WSEA—Virginia Beach, Va.	1370	218.8	250	KFVR—Denver, Colo.	630	475.9	250	KSAC—Manhattan, Kans.	900	333.1	500
WSIX—Springfield, Tenn.	1410	212.6	150	KFVS—Cape Girardeau, Mo.	1340	223.7	50	KSBA—Shreveport, La.	1120	267.7	1000
WSKC—Bay City, Mich.	610	491.5	250	KFWB—Los Angeles, Calif.	830	361.2	500	KSCJ—Sioux City, Ia. (KWUC)	1230	243.8	500
WSM—Nashville, Tenn.	940	319.0	2000	KFWC—San Bernardino, Calif.	1350	222.1	100	KSD—St. Louis, Mo. (KFUC)	550	545.1	500
WSMB—New Orleans, La.	930	322.4	500	KFWF—St. Louis, Mo.	1400	214.2	250	KSEI—Pocatello, Idaho	900	333.1	250
WSMK—Dayton, O.	1010	296.9	200	KFWH—Eureka, Calif.	1180	254.1	100	KSL—Salt Lake City, Utah	990	302.8	1000
WSOE—Milwaukee, Wis.	1100	270.1	500	KFWI—San Francisco, Calif.	1120	267.7	500	KSMR—Santa Maria, Calif.	1100	272.6	100
WSOM—New York, N. Y. (WGBB, WSR											

FLECHTHEIM

Superior Condensers for Socket Power Circuits Are

UNCONDITIONALLY GUARANTEED
Not to Break Down in Use If Operated At or Below Their Rated Voltages



1,000 Volts D.C. Working Voltage

600 Volts D.C. Working Voltage

(Working Voltage is the voltage at which the condenser can be safely used in continuous operation.)

Flechtheim Quality Condensers

In compact aluminum cases, are designed for Socket Power Sets and Power Amplifiers, with a working voltage up to 600 volts D.C., and in Filter Circuits for plate supply. Accurate when made and remain accurate within 5% of their rated capacities.

Capacity	Bi-Pass 250 Volts	Filter 450 Volts
.10 mfd.	.60	.70
.25	.70	.75
.50	.75	.85
1	.90	1.20
2	1.50	1.65
4	3.00	3.25

14 Mfd. Block Condenser.....\$10.00
2-2-4-4-0-1-1 Mfd.

01-0.1 mfd. H. V. Buffer Condenser.....\$1.50

We also make 1,000-volt D.C. working voltage condensers and 2,000 D.C. working voltage transmitting condensers in 1, 2 and 4 mfd. capacities.

Inquiries from the Trade Solicited
Manufacturers Supplied

A. M. FLECHTHEIM & CO., Inc.
275 BROADWAY NEW YORK
Telephone: WORTH 7150

A DC Galvanometer You Can Make at Home

THERE is nothing mysterious or complicated about a galvanometer. The two essentials are a coil of wire and a magnet, one of which must be suspended so as to be capable of rotation. If the coil is suspended in the field of the magnet the type of galvanometer is known as the D'Arsonval, or the moving coil type. If the magnet is suspended in the field of the coil, it is called a moving magnet type. The first of these is the more common. It is used in many electrical voltmeters, ammeters, galvanometers and other instruments. The moving magnet type is not used so extensively, though it is much easier to make.

Interesting Work

For those who are experimentally inclined it is both interesting and useful to make one of the moving magnet type. First obtain a small magnetic needle of the type used in pocket compasses, or make one out of a steel needle by stroking it with a larger horseshoe magnet. Now make a coil. This should be preferably in the form of a rectangle considerably longer than it is wide. The length should be such that the needle may swing inside it lengthwise. Say for the sake of definiteness that the length of the needle is 1 3/4 inches. The inside dimension of the coil should then be about 2 inches. The coil should be wound in a compact form and covered with collo-

dion to hold it together and make it self-supporting. As to the number of turns and size of wire a wide latitude is allowable since there is no definite requirement to be met. One hundred turns of No. 28 silk covered wire are suggested. The mounting may be made very simply. Use a small piece of wood cut from a cigar box as a base. Then glue a cork to the center of this. Then mount the finished coil on top of the cork, likewise using glue for the purpose. The coil should be mounted with its plane vertical and its long axis horizontal.

For an indicator scale cut out a circle of cardboard and inscribe on it a scale similar to that used on radio dials. Mount this cardboard inside the rectangular coil on the side next to the cork, making its plane as nearly horizontal as practicable.

Now we come to the mounting of the needle. This should be placed in the exact center of the coil measured both in the short and in the long directions. The matter of suspension of the needle is important. If the object is merely to indicate the passage of a current through the coil it may be placed on a pivot without any elastic reactance, that is, without the use of any spring to resist the motion. If an attempt is made to get a value of the current flowing it will be necessary to use a spring of some sort. One of the simplest springs is a fine wire. The needle is then merely suspended over the center of the indicator scale and no supporting pivot is used. A No. 40 copper wire may be used for suspension. The current is then measured by the amount of twist in the wire.

May Get Definite Reading

In some cases a definite reading may be obtained by using the earth's magnetic field as the restoring force instead of the supporting wire. The lower pivot may then be used. If the earth's magnetic field is used the coil should be placed so that the earth's field is at right angles to the field set up by the current. The direction of the field set up by the current is at right angles to the plane of the coil. The direction of the earth's field is shown by the magnet when no current is flowing through the coil. The coil should be turned so that the plane of the coil is parallel with the magnet when no current is flowing. Then when the current is turned on the needle will deviate from the north and south alignment and will try to swing around to a direction of east and west. The needle will come to rest at an intermediate direction, depending on the strengths of the two opposing forces.

FLECHTHEIM CONDENSERS

BEST BY TEST

Dealers! Write for Attractive Proposition!

VENUS RADIO CORP.

142 LIBERTY STREET, NEW YORK CITY

Telephone: Rector 7190-7191

Sole distributors for these states:
New York, New Jersey and Connecticut

Take Your Choice of 7 Other Publications!

For NEW RADIO WORLD Subscribers Ordering NOW

Radio World has made arrangements

-To offer a year's subscription for any one of the following publications with one year's subscription for RADIO WORLD

RADIO NEWS or POPULAR RADIO or SCIENCE AND INVENTION or BOYS' LIFE or RADIO DEALER or RADIO (San Francisco) or RADIO AGE.

This is the way to get two publications

- for the price of one
- Send \$6.00 today for RADIO WORLD
- for one year (regular price)
- for 52 numbers)
- and select any one of the other
- nine publications for twelve months.
- Add \$1.00 a year extra for
- Canadian or Foreign Postage.
- Present RADIO WORLD subscribers
- can take advantage of this offer by
- extending subscriptions one year
- if they send renewals NOW!

Radio World's Special Two-for-Price-of-One Subscription Blank

RADIO WORLD, 145 West 45th Street, New York City.
Enclosed find \$6.00, for which send me RADIO WORLD for twelve months (52 numbers), beginning..... and also without additional cost, Popular Radio, or Radio News, or Science and Invention, or Radio Dealer, or Radio (San Francisco), or Radio Age or Boys' Life (or \$10.00 for a two-year subscription to one address). No other premium with this offer.

Indicate if renewal. Name

Offer Good Until Street Address

Sept. 10, 1927 City and State.....



In B ELIMINATORS, in T. R.' F. sets; in all circuits, CLAROSTAT, the greatest variable resistor, is indispensable. Don't experiment - use CLAROSTAT. "THE GATEWAY TO BETTER RADIO." 32 pages covering the latest angles in radio. Send 25c to Dept. R.W., American Mechanical Labs., Inc., 285 N. 6th St., B'klyn.

World "A" Power Unit--\$12.75

Automatically provides even, unvarying "A" current from your light socket. Absolutely noiseless. Assures full tone quality from your set and wider D. X. range. Famous WORLD quality--at less than half of the cost of any similar equipment. Shipped complete, subject to inspection on receipt of price, or C.O.D. If you wish, 25 amp. unit for sets of 4 tubes or less, \$12.75. 60 Amp. unit for sets of 5 tubes or more, \$15.75. 5% discount if cash in full is sent with order. Send order today. World Battery Co., 1219 So. Wabash Ave., Dept. 82, Chicago, Ill.


THE RADIO TRADE

New Set Tester Made by Weston

What may be aptly termed as the "Serviceman's Delight" has just been placed on the market by the Weston Electrical Instrument Corporation, Newark, N. J., one of the oldest and foremost electrical houses in the country. It is known as the Weston Model 519 Radio Set Tester. It is very light in weight and compact. Various voltages in either a battery or a battery eliminator operated set, both at the battery terminals and at the tube sockets, as well as the continuity and actual condition of all circuits, regardless of intricacy, may be determined with this device. No additional batteries are required for any of these tests. The instrument which forms a part of this tester is a special Weston model, having three voltage ranges, e.g., 200, 80 and 8, as well as a 20 milliamperere range. The voltage ranges have a sensitivity of 1,000 volts ohms per volt, which means that full scale deflection is produced with only one milliamperere of current. A plug and socket of the UX type, as well as two adapters are furnished. One adapter is used to change the socket and one to change the plug on the tester from the UX type to the UV type. Adapters for the UV 199 tubes are also obtainable.



Upright Leak Mount

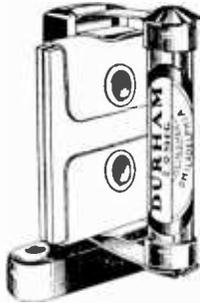

The International Resistance Co. announced an upright mounting base for grid leaks, especially designed for "tight places." This is part of the Durham line, which includes the metallized resistors.


Make any Good Receiver BETTER.

CEC TUBES

C. E. MFG. CO.
Providence R. I.




Remler 2-in-Line Among New Parts

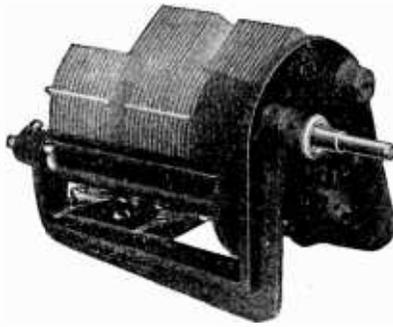

Two-in-line Remler Condenser, of the familiar and efficient twin rotor design

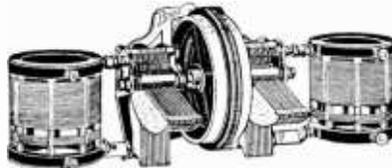Besides having a three-in-line condenser, Remler has a two-in-line model. This also is in straight wave and frequency models and embodies the twin rotor design. Gray and Danielson, Remler Division, are the manufacturers. Pat Kiley, 30 Church Street, New York City, is the Eastern representative.



THE BRUNO "RF" UNITUNE, illustrated in an article in this issue on the Cash Box Portable, is only one of several models adaptable to various circuits. List price - - - - - \$17.00

The basic unit "2C," from which all other UNITUNES are built, consists of two bakelite shaft condensers, mounted on an aluminum frame; a pair of moulded bakelite drums; a bronze escutcheon plate and two mounting screws. It can be bought in all capacities for - - - - - \$11.00

All other UNITUNES assembled with one or more quartzite coils, for all popular circuits, range from - - \$12.00 to \$21.00


Get them at your dealer or send 25 cents to us for NEW 36-page booklet about our complete line.

BRUNO RADIO CORPORATION
Long Island City New York

THE 5-TUBE DIAMOND

Fully described by Herman Bernard in a booklet, with diagrams, including blueprint, and sent on receipt of 25 cents. The Diamond is automatically adaptable to phonograph pickup. RADIO WORLD, 145 West 45th St., N. Y. City

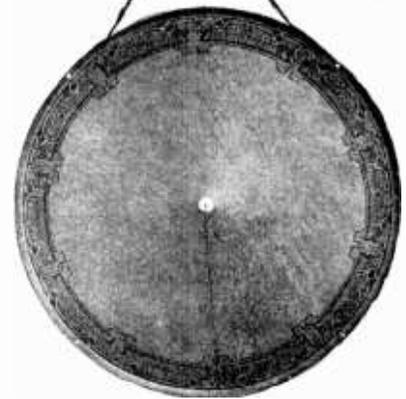The NEW "ENSCO" 3 Ft. Cone Loud Wall Type Speaker



Complete "ENSCO" Kit

\$10.00 With Hardwood Wall Frame, \$11.00

It contains "ENSCO" Direct-drive unit, designed and patented by Clyde J. Fitch. Beautifully decorated Alhambra FON-O-TEX Cone Material; Metal Apexes; Extension Cord and 12-page illustrated Book of Instructions for easy assembly of any of six sizes of Cone or Roll shape, Wall, Pedestal or Console speaker. You can build it in less than an hour. Static materially reduced—winter results all summer.

The "World's Finest Loud Speaker"

Now within the means of every one. At your dealer's or direct from any of the offices listed below. Send check, money order or C.O.D. Shipping charges paid. Absolute (money-back) guarantee

Engineers' Service Company

25 Church Street, New York
73 Cornhill, Boston
28 E. Jackson Blvd., Chicago
331 Bay Street, Toronto

New and Improved FRESHMAN MASTERPIECE

AT AUTHORIZED
FRESHMAN DEALERS ONLY

**RADIO WORLD'S
QUICK-ACTION
CLASSIFIED ADS
10 CENTS A WORD
10 WORDS MINIMUM
CASH WITH ORDER**

SHIELDED 30H, 60 MA chokes—\$2.25. Write us for quotations on your requirements. Lists on request. Radio Parts Sales Co., Orange, N. J.

THOUSANDS OF RADIO BARGAINS. Write, OMAN, 156 Concord, St. Paul, Minn.

NEW DE LUXE BST RECEIVER—5-Tube Set, resistance coupled audio, built-in C eliminator, genuine mahogany cabinet. Price, \$60. Five-day money-back guarantee. GUARANTY RADIO GOODS CO., 145 W. 45th St., N. Y. City.

VALET AUTOSTROP RAZOR—The only razor that sharpens its own blades. Highly polished, nickel-plated, self-stropping Valet AUTOSTROP Razor, with one blade, in velvet lined metal case. Leather strop especially prepared, and complete outfit in neat, lithographed carton. Mailed post-paid on receipt of 50c. SPECIAL: Send \$2 for one-third of a year subscription for Radio World (yearly price \$6), mention this particular ad, and complete "Pal" set will be sent as a premium. If already a subscriber, your subscription will be extended three months. THE COLUMBIA PRINT, 145 West 45th Street, New York City.

LINDBERGH PLANE SPEAKER. Pictures and explanatory article appeared in Radio World dated June 25, 1927. Sent on receipt of 15 cents or start your subscription with that number. Radio World, 145 W. 45th St., N. Y. C.

WATCH EXPIRATION OF YOUR SUBSCRIPTION

Subscribers will note that the end of their subscriptions is indicated on the labels on wrappers. If your wrapper shows a date earlier than the current issue, please send payment for renewal. Changes in expiration dates on wrappers appear two weeks after receipt of renewal. PLEASE ALWAYS INDICATE WHEN SUBSCRIPTION IS A RENEWAL.

RADIO WORLD, 145 West 45th Street, New York City (Phones: Bryant 0558-0559)

Good Back Numbers of RADIO WORLD

The following illustrated articles have appeared in back issues of RADIO WORLD, 1924-1927:

1926

- Oct. 9—A Practical "A" Eliminator, by Arthur H. Lynch. Building the Equisatic, by Capt. P. V. O'Rourke.
- Oct. 16—The Bernard, by Herman Bernard. How to Box an "A" Supply, by Herbert E. Hayden.
- Oct. 23—The 5-tube P. C. Samson, by Capt. P. V. O'Rourke. Getting DX on the Bernard by Lewis Winner.
- Oct. 30—The Electro Receiver, by Herbert E. Hayden. How to Get Rid of Squeals, by Herman Bernard.
- Nov. 6—Reduction of Interference, by A. N. Goldsmith. Variations of Impedance, by J. E. Anderson.
- Nov. 13—The 4-tube HD-Power Set, by Herbert E. Hayden. A Study of Eliminators, by Herman Bernard.
- Nov. 20—Vital Points About Tubes, by Capt. P. V. O'Rourke. The 4-tube Diamond of the Air, by Herman Bernard.
- Dec. 4—The regenerative 5-tube Set, by Capt. P. V. O'Rourke. The 8-tube Lincoln Super, by Sidney Stack. Winner's DC Eliminator, by Lewis Winner.
- Dec. 18—Selectivity on One Tube, by Edgar Speare. Eliminating Interference, by J. E. Anderson.
- Dec. 25—A New Coupling Device, by J. E. Anderson. Function of Eliminators, by Herman Bernard.
- Jan. 1, 1927—The 2 Tube DeLuxe Receiver, by Arthur H. Lynch. The Twin-Choke Amplifier, by Kenneth Harkness.
- Jan. 8—Tuning Out Powerful Locals, by J. E. Anderson. A Choice Superheterodyne, by Brunton Brunel. The 2-Tube De Luxe Receiver, by Arthur H. Lynch (Part 2).
- Jan. 15—The DeLuxe Receiver, by Arthur H. Lynch (Part 3). The Simple Meter Test Circuit by Herbert E. Hayden. The Superheterodyne Modulator Analyzed, by J. E. Anderson.
- Jan. 22—The Atlantic Radiophone feat, by Lewis Rand. An Insight Into Resistors, by J. E. Anderson. A Circuit for Great Power, by Sidney Stack.
- Jan. 29—The Harkness KH-27 Receiver (Part 1), by Kenneth Harkness. Use of Biasing Resistors, by J. E. Anderson.
- Feb. 5—3-Tube, 1 Dial Set, by Capt. P. V. O'Rourke. The Harkness KH-27 (Part 2), by Kenneth Harkness. What Produces Tone Quality, by J. E. Anderson.
- Feb. 12—Phone Talk Put On Speaker, by Herbert E. Hayden. All Batteries Eliminated, by Herman Bernard. The Harkness KH-27 Receiver, by Kenneth Harkness (Part 3). Conclusion.
- Feb. 19—The 6-Tube Victoreen, by Herman Bernard (Part 1). The Big Six Receiver, by Wentworth Wood. "E" Eliminator Problem, by Wm. F. Lear. The Phasmatron Circuit, by Capt. P. V. O'Rourke. The 5-Tube Victoreen, by Herman Bernard (Part 2). Conclusion.
- Feb. 26—The 5-tube Diamond in a Phonograph, by Hood Astrakan. How To Read Curves, by John F. Rider. Proper Tubes for 5-Valve Receiver, by J. E. Anderson.
- Mar. 5—Introduction of 4-tube Universal, by Herman Bernard. Discussion on DX, by Capt. P. V. O'Rourke. Sensible Volume Control, by Chas. Gribben.
- Mar. 12—Ten Tell-Tale Points, by J. E. Anderson. How To Figure Resistors, by Frank Logan. The 4-tube Universal, by Herman Bernard, (Part 1).
- Mar. 19—Psycho-Analyzing Circuits by Thomas L. McKay. The Universal, by Herman Bernard (Part 2). How To Use a Wave Trap, by James H. Carroll.
- Mar. 26—The Universal, by Herman Bernard, (Part 3). Flow of Current in a Vacuum Tube, by Badelife Parker. Broadcasting Hypnotism.
- April 2—Facts Every Experimenter Should Know, by J. E. Anderson. A Ship Model Speaker, by Herbert E. Hayden. The 8-tube Compact, by Jasper Henry. The Nine-in-Line Receiver, by Lewis Rand (Part 1.)
- April 9—A 5-tube Shielded Set, by Herbert E. Hayden. The Power Compact, by Lewis Winner. The Nine-in-Line Receiver, by Lewis Rand, (Part 2).
- April 16—The Schoolboy's Set, by Wally Frost. The Melo-Heald 11-tube Set, by Herbert E. Hayden. The Nine-in-Line Circuit (Part 3), by Lewis Rand.
- April 23—The Melo-Heald Set, by Herbert E. Hayden (Part 2). The Nine-in-Line, by Lewis Rand. (Conclusion). How Frequencies Are Cut-off, by J. E. Anderson.
- April 30—A 1-tube Portable, by Jasper Jellicoe. A Ship Model Receiver, by Smedley Farnsworth. A Double Three Foot Cone, by W. H. Sinclair.
- May 7—The Adams-Griffin 6-tube Set, by Dana Adams-Griffin (Part 1). A 3-tube Portable, by Hood Astrakan. How to Improve Superheterodyne Sets, by John L. Barrett.
- May 14—A 3-tube Portable, by Herbert E. Hayden. The Adams-Griffin Receiver, by Dana Adams-Griffin. (Conclusion).
- May 21—The Victoreen Portable Receiver, by Capt. P. V. O'Rourke. A Low-Pass Filter, by J. E. Anderson.
- May 28—The Console Cone, by Thorvald Larson. The 3-tube Reflex by Edgar E. Francis. The Victoreen Portable Receiver, by Capt. P. V. O'Rourke. (Part 2).

Any copy, 15c. Any 7 copies, \$1.00. All these 32 copies for \$4.00, or start subscription with any issue. Any 7 of these numbers sent as premium with NEW yearly subscription. No other premiums allowed. RADIO WORLD, 145 West 45th Street, New York City.

Radio University

FREE Question and Answer Department conducted by RADIO WORLD for its yearly subscribers only, by its staff of Experts. Address Radio University, RADIO WORLD, 145 West 45th ST., New York City.

When writing for information give your Radio University subscription number

I HAVE BEEN GIVEN a five tube tuned radio frequency set, and been told to stop it from squealing when tuned. I don't know where to tap the coils to neutralize it. Can you tell me of any other way that will work?—John R. Stritt.

You can connect a 50,000 ohm-maximum variable resistance in the B battery lead to the primaries of the RF transformers (not the antenna coupler), and use this to cut down their plate potential to the proper value. Also, you can connect the grid returns of the first two tubes to the arm of a non-inductive potentiometer, and connect its outside terminals across the A battery leads in the set, to give a control of RF grid bias. If you decide to use the latter method, be sure that the filament switch is between the potentiometer and the A battery, to avoid a constant current drain. Use a potentiometer that has a resistance of 400 ohms, and the current passed through it will be only .015 ampere.

* * *

I WISH to install a set in a hotel room, where I have no facilities for erecting an aerial. I have tried to make the set work on a loop, but without succeeding. It is a regenerative set, using three tubes. How can I get along without an aerial, or if this cannot be done, how can I change the set?—W. Hall.

There are several acceptable antenna substitutes on the market. Some attach

in an electric light socket. Examples are the "Antenella" and the "Ducon." There is also a metal plate which may be placed under a telephone. Its name, I believe, is the "Antennaphone." Another way that usually works well is to use the steam pipe or gas-pipe as an aerial. In all cases use the cold water pipe as the ground.

* * *

MY SET has a rather raspy tone, that I would like to overcome. Tubes and batteries are new, so I assume that they are all right and the loud speaker sounded fine when the dealer demonstrated it to me. Do you think that if I added a stage of resistance coupled amplification it might help?—Irving Hendon.

No. If you were to remove the second audio transformer and replace it with a better one or with two stages of resistance coupling, the tone would probably be improved. Before doing this, try connecting a 1/4 to 5 megohm variable resistance across the primary of the first transformer. Then try it across the primary of the second transformer. It is likely that you will find that this will remove the rasp without necessitating rebuilding.

* * *


CAN YOU TELL me an easy way to determine the primary to secondary ratio of an audio transformer?—Ira Hoff.

An approximate idea can be had by connecting first the primary and then the secondary in series with a 0-50 milliammeter and a 22 1/2 volt B battery. Suppose that the reading shows a current of 2 mils through the secondary and 10 mils through the primary. Then the transformer has a 5-1 ratio, as 10 divided by 2 equals 5. This test holds good only if the primary and secondary are wound with the same size wire, as is almost always the case.

HELPFUL HINT

In soldering, use good flux, because it assures clean contact.

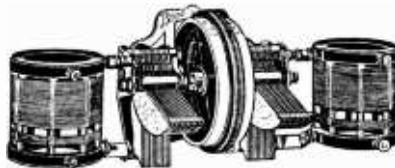B. C. L. RADIO SERVICE CO., INC.
220 Fulton St., N. Y. City
Phone, Cortlandt 6209



Bruno Unitone, Model RF, specified for the Cash Box Portable by Wendell Buck. Order from us. Immediate shipment.

NEW Improved Kit \$37.50
Diamond of the Air

Send for Free Catalog

COMPLETE DETAILS on what ohmage resistances may be used with B eliminators to also obtain C bias, were given by Frank Logan in the March 12 issue of RADIO WORLD. Either send 15c for his issue or begin your subscription with this issue. RADIO WORLD, 145 West 45th St., New York City.

Be sure to take RADIO WORLD along with you on your vacation, or read it while you are at your summer home so that you will not miss a copy; send \$1.50 for three months subscription and RADIO WORLD will be sent to you all summer. RADIO WORLD, 145 W. 45th St., N. Y. C.

FILL OUT AND MAIL NOW SUBSCRIPTION BLANK

RADIO WORLD

RADIO WORLD

145 West 45th Street, New York City
(Just East of Broadway)

Please send me RADIO WORLD for months, for which please find enclosed

SUBSCRIPTION RATES:

- Single Copy \$.15
- Three Months 1.50
- Six Months 3.00
- One Year, 52 Issues 6.00
- Add \$1.00 a Year for Foreign Postage; 50c for Canadian Postage.



VICTOREEN

Super Coils

Send for Folder

Geo. W. Walker Co.
6522 Carnegie Avenue
Dept. B Cleveland, O.

How the Service Man Peps Up Weak Sets

Quite frequently, the service man is called in to give his views on the failure of a home-built tuned radio frequency set to afford volume and selectivity. Often this can be traced to the grid returns of one or more of the RF coils or the detector coil secondary being run to the wrong filament lead. There is a quick way to check up on the former, if the set is the usual type, using 90 volts of B battery potential on the plates of all amplifier tubes and 45 volts on the detector tube, with a 4½ volt negative bias on the audio amplifier grids. It is to insert a 0-50 scale milliammeter in the wire running from the negative terminal of the B battery to the common A and B battery connection. If all is well, the deflection of the needle on the meter will indicate that a current of 17 mils or less is flowing. When a greater amount of current is being consumed, first see that the polarity of the C battery is correct, and that its positive terminal is connected to the negative A lead. Next, inspect the set and make sure that the RF amplifier grid returns are connected to the negative side of the lamemfit circuit and that those of the audio tubes are run to the negative C battery terminal. If a 201-A type tube is being used as detector, it should have a positive grid return, and if the detector is of the 200 or 200-A type, the grid return should be negative.

The milliammeter reading of about 17 mils, as mentioned above, will hold good for storage battery operated sets that do not use power tubes, as these tubes will require higher B and C voltages and draw a greater amount of plate current. Sets using various types of dry-cell tubes will draw slightly less.

Many owners of factory-made sets are replacing their type 201-A tubes with the type 200-A in the detector stage—and are neglecting to change the grid return. This is a point that must be watched, if the new tubes are to function properly. If ever you hear a set owner complaining that a special detector is not performing as it should, check up on the grid return before going to any further trouble.

INTERESTING FACTS

A hissing noise in the loud speaker is due often to a defective conductor or contact. Carbon resistors are most frequently to blame. The trouble may be

Why is the Karas Equamatic the Most Efficient Receiver Ever Designed?

Write us for Full Information

KARAS ELECTRIC CO.
4039-HA. No. Rockwell St., Chicago, Ill.

**25 Cents
Brings ALL THIS!**

One Official Blueprint of the Five-Tube Diamond of the Air

One official booklet describing in detail how to build this famous set, wind coils, etc.

Act Now! Send That Quarter to

RADIO WORLD

145 West 45th Street, New York City

traced to the transmitting microphone, to a grid leak, or to a plate coupling resistor. Sometimes the cause is a corroded contact and most frequently occurs at the positive terminal of the storage battery.

If the A battery has been accidentally reversed it will produce a very noisy signal, characterized by scratches and hisses.

A run down dry cell will cause a similar noise, but it will be more severe.

All sets radiate unless they have been completely shielded.

Most of the whistles heard at this time in a radio set are not due to faults in the set. The true cause is double in nature.

Do not worry about the quality of a tuning condenser.

LIFE OF A C BATTERY

If the grid is correctly biased no current flows in the grid circuit, and the C battery will last as long in the set as it will on the shelf.

BUY
NATIONAL
RADIO PRODUCTS
For
Satisfactory and Lasting Results
NATIONAL COMPANY, INC.
Engineers and Manufacturers
W. A. READY, Pres. Cambridge, Mass.

**HOW TO BUILD THE
BALSA SPEAKER**
With genuine Lata Balsa Wood, fully described, including acoustical theory, by H. B. Herman in the June 11 issue. Send 15c for copy.
RADIO WORLD
145 West 45th Street, New York City

2100 intelligent questions
2100 correct answers
Ratings of 62 celebrities
and
THE SUPER-TEST
Ask Me Another
2
Series
The second question book
THE VIKING PRESS

Sent, postpaid, for \$1.60
THE COLUMBIA PRINT
145 West 45th St., New York

KEEP FILAMENTS NORMAL

Do not burn the filaments in the radio set brighter than normal. Nothing is gained and the life is unduly shortened. If more power is required, use a larger tube.

Lata Balsa Wood Reproducer

Nature's Sounding Board

Radio's Sensation


Real Tone Reproducer at Last

The full story of this wonderful vibrating wood that reproduces the missing element lacking in every other means of Sound Reproduction for radio is told by

H. B. HERMAN

in the June Eleventh Issue of

RADIO WORLD

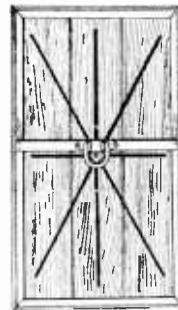

THE BALSA SPEAKER (back view) brings the artist into your home. Lends itself to any scheme of decoration. Chintzes, cretonnes, tapestries, even wall papers may be used.

Our kits are of genuine Lata Balsa Wood, especially treated for radio use by our own process. Made in three sizes for any good unit or with special Lata Balsa Reproducer Unit created by acoustic engineers solely for the LATA BALSA DIAPHRAGM.

Patented
Lata Balsa Reproducer Kits are available in three sizes:
24" x 13"..... \$5.50
36" x 21"..... \$8.00
43" x 24"..... \$10.00
Express Charges Collect

Easily and quickly built. Look for the name "Lata," the only genuine Balsa Wood kit. Completely Built Speakers, with unit attached, may also be had. Send for price list.

Beware of Imitations

Our reproducers are protected by Patent No. 1,492,982, which covers a sound-reproducer diaphragm made of Balsa wood, however constructed.

Information now ready on the new Lata Balsa Unit priced at \$8.00. Made especially for use with the Lata Balsa Reproducer. It, however, is sold separately and makes an excellent unit for any loud speaker.

Balsa Wood Reproducer Corp.
331 Madison Avenue New York City

BALSA SPEAKERS

Genuine Lata Balsa Wood Kits
Special Units to drive Balsa Speakers with fine results from \$3 to \$17. We will build a Balsa Speaker to your specifications or size. Shipped anywhere. Get
SPECIAL HEAVY DUTY "B" BATTERIES \$1.85
Anything in Radio
BLAN—the Radio Man
145 East 42nd Street New York City

TELEVISION

Picture Transmission—the Marvel of the Century

Newest and greatest authority, just published, gives History, facts and complete instruction to build a home television set

THE marvel of Radio Broadcasting, the transmission of the voice and music over the air is no longer the greatest achievement of this precocious 20th century.

We now have TELEVISION—the transmission of events over land wires or by radio. A tremendous step ahead of even Radio.

For many years experiments on television have been diligently made by many famous inventors and engineers. Step by step machines have been corrected, improved and simplified—until today—practical machines

are in constant operation, annihilating distances in picturing events to the eager public.

Here is the first and only book in print that gives you the complete story of television from earliest experiments to the present day machines.


The book is the most complete publication of its kind. It gives you *the history, the facts* and the full instructions on how to build, in your own home, an up-to-date model Television apparatus.

Like Radio in 1921

Television is ready for the world. Like Radio in 1921, it waits only for you experimenters to invent, develop and perfect the apparatus. You may be fortunate enough to develop an idea that will be worth many dollars—start now with a copy of this book.

Great Future for practical Experimenters

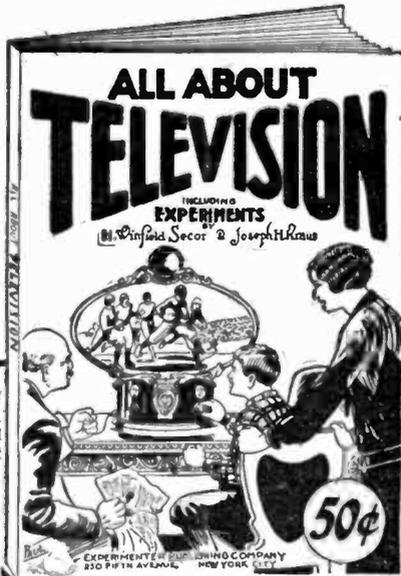Television will be as popular as Radio. Even now the public is showing great interest in telephoto pictures from Europe and elsewhere. Get your apparatus together. You are in for many days of fascinating experiments that beat anything you've ever tried. 4 special chapters in this book deal exclusively with how to construct an experimental set.



**COPIES 50¢ EACH
AT ALL
NEWSSTANDS**


*If Your Newsdealer Cannot
Supply You - Order Direct*
EXPERIMENTER PUBLISHING CO., Inc.
230 Fifth Ave., New York, N.Y.

1000 Hours of Fun with SAM LOYD

THERE are more than one thousand hours of truly amazing fun and frolic—in Sam Loyd's "Tricks and Puzzles." There is only one Sam Loyd, the Puzzle King, the incomparable, a true master mind, and he has crowded in this new volume, "Tricks and Puzzles," the best work of his lifetime.

In this book are thousands of puzzles of every conceivable nature, games, tricks, conundrums. Hundreds of illustrations. Scores of real brain-teasing puzzle stories, dozens of humorous anecdotes.

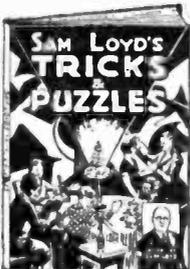With this inexhaustible gold mine of lively entertainment at hand you need never be at loss for an evening's party program or a rainy day's delight.



It's a book for young and old folks alike—Riddles for the youngsters—Brain teasers for the grown-ups.

The kind of a book every home should have in its book-rack. 116 pages, 100 or more illustrations, large size, 9 x 12 inches with beautiful 2-color cover.

**50c THE COPY
EVERYWHERE**

or you can order direct

EXPERIMENTER PUBLISHING CO., Inc.
230 Fifth Ave. New York, N. Y.

SECRETS of your HANDS

*96 page Book on the revelation of
character, fortune, etc.--in Hands*

FINGERPRINTS are used throughout the world as a means of apprehending criminals—but fingerprints are but a small portion of the secrets of your character that your fingers, your palm, even your handshake reveals.

Every inch of your hand has been charted by the experts of this highly developed science, and so simply and accurately that anyone can learn the telltale signs by heart.

Here is a brand new book with all the latest information—written in such a way that you can quickly master "Palmistry."

Everything is simplified, easy to understand, the book contains 96 pages, hundreds of illustrations and is the large size 9x12 inches.

**50c THE COPY
EVERYWHERE**

or you can order direct

EXPERIMENTER PUBLISHING CO., Inc.
230 Fifth Ave., New York, N. Y.