

Patent applied for




Perfect Smooth Taper.



Pure Silver Shortcuts for Switch Action.



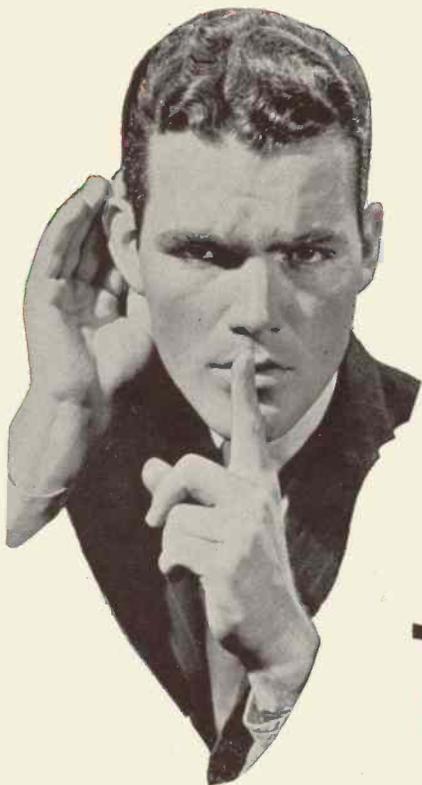New Spring Wedge Prevents Loose Terminals.



At Last!

a really

SILENT

Volume Control
of course... It's a

YAXLEY

"No foolin'" — it's really here. They said it couldn't be done. But here it is — a triumph of Mallory-Yaxley engineers — the new SILENT Yaxley Replacement Volume Control.

Here is silent operation with a capital "S". You Can't Hear It! There's not the slightest sound — not even a whisper.

Consider these features (and there are many more):

- 1 Perfect Smooth Tapers, feather edged to insure electrical smoothness, and applied to promote mechanical smoothness — and silent operation.
- 2 Pure Silver Shortcuts for Switch Action — and silent operation.
- 3 Silver to Silver Contacts. No corrosion — but silent operation.
- 4 Highest current carrying capacity; uniform characteristics, long life — and silent operation.
- 5 Perfect Contact between moving arm and carbon element through the special Yaxley "M" roller (that doesn't roll). Perfect contact for silent operation.
- 6 Low humidity and low temperature coefficients. Never fear "damp spots" or "hot spots." Depend on Yaxley for silent operation.
- 7 Universal Application — equipped with the famous Yaxley attachable switch — and other exclusive universal features.

Here's a golden opportunity for you! Take the lead in your locality! The Yaxley "Silent" Volume Control builds reputation and builds business. Get in touch with your distributor today and place your order.

YAXLEY MANUFACTURING DIVISION

P. R. MALLORY & CO. INC.
MALLORY

of P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA
Cable Address — PELMALLO

YAXLEY

RESEARCH KEEPS GENERAL ELECTRIC YEARS AHEAD

General Electric Announces

THE 5TH OF A SERIES OF FIELD SERVICE MEETINGS

DURING SEPTEMBER

Admission Free!

EVERYBODY IS INVITED

We'll advise you in advance regarding the date and meeting place of the 5th of a series of General Electric Field Service Meetings in your locality. This educational course is FREE. Your interest in radio sales and service is the only requirement for admission.



MAIL COUPON OR
PHONE G-E RADIO
DISTRIBUTOR FOR DATE
OF LOCAL MEETING

GENERAL ELECTRIC COMPANY
BRIDGEPORT, CONNECTICUT

Attention: Section R-999

Please send me the date and address of the next Field Service Meeting in my locality.

Name.....

Firm Name.....

Street Address.....

City..... State.....

RADIO'S NEWEST MARVEL



Focused Tone

COME, SEE AND LEARN ABOUT THIS AMAZING NEW DEVELOPMENT!

AUTOMATIC FREQUENCY CONTROL — A device which will automatically and instantly compensate for any reasonable error in tuning, bring the station signal into perfect tune, and thus assure the best possible quality of reproduction.

COLORAMA DIAL — A revolutionary tuning indicator which automatically flashes the whole dial from red to brilliant green when the signal is hair-line tuned for perfect tone.

ILLUSTRATED LECTURES
SERVICE NOTES

COMPETENT SPEAKERS
OPEN DISCUSSIONS


Illustrated Copies of Literature Will Be Distributed

FOR METAL TUBE RENEWALS, SPECIFY G-E METAL TUBES

GENERAL ELECTRIC

Focused Tone Radio

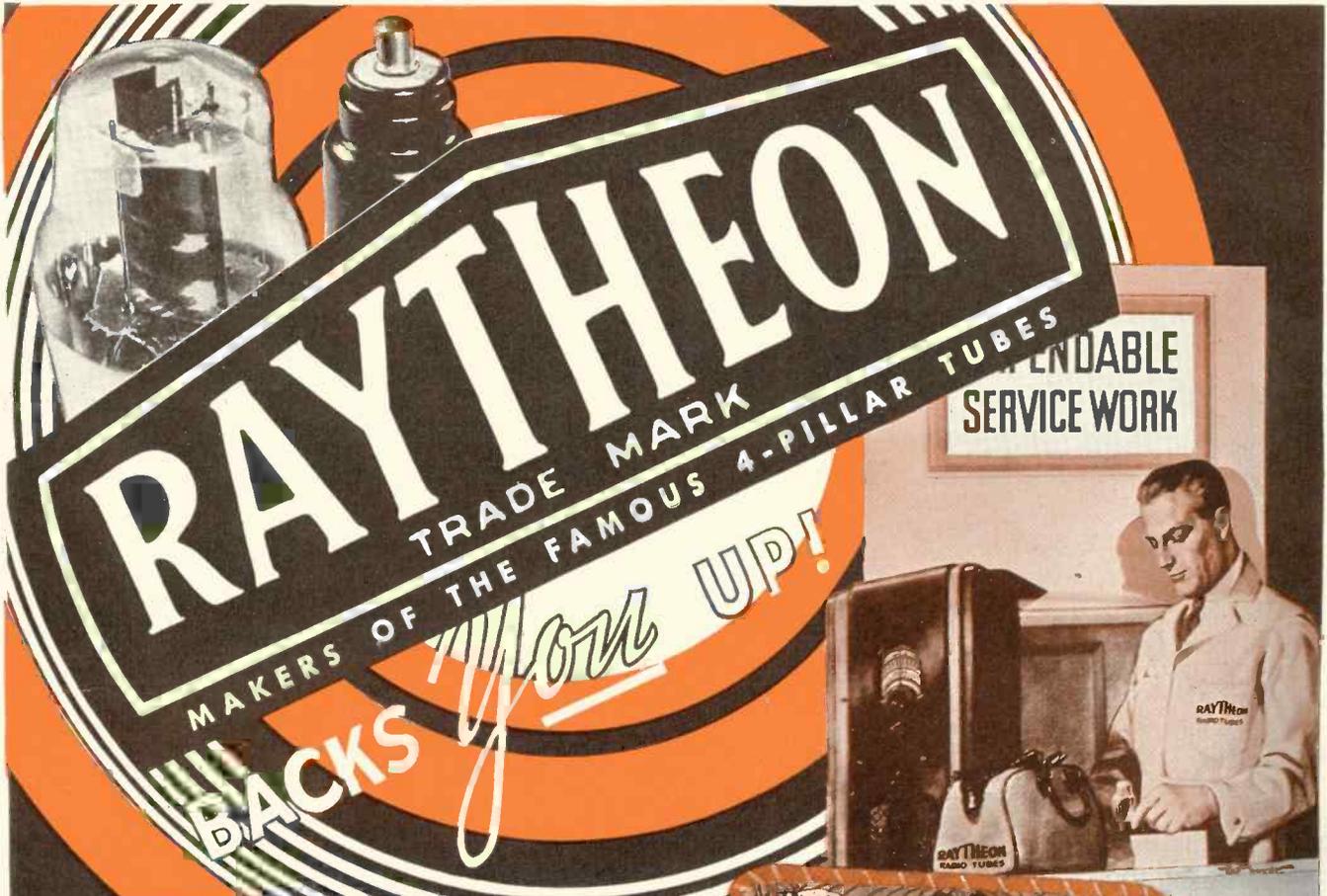APPLIANCE AND MERCHANDISE DEPARTMENT, GENERAL ELECTRIC COMPANY, BRIDGEPORT, CONN.




DEPENDABLE
SERVICE WORK



THROUGH THE YEARS IT HAS ALWAYS BEEN RAYTHEON'S POLICY TO PROTECT ITS DEALERS AND JOBBERS THROUGH A RIGID RETAIL PRICE SETUP. RAYTHEON'S TUBES ARE FAIRLY PRICED TO GIVE RAYTHEON DEALERS REAL PROFIT PER TUBE OVER OTHER TUBE LINES. BECAUSE OF RAYTHEON'S UNUSUALLY HEALTHY GROWTH, THE SALE OF RAYTHEON TUBES HAS NEVER BEEN "FORCED". RAYTHEON TUBES ARE NOT ADVERTISED AT CUT PRICES.

TO AID RAYTHEON DEALERS IN FULLY CAPITALIZING ON THE TREMENDOUS PUBLIC ACCEPTANCE OF RAYTHEON'S QUALITY AND NAME, OUTSTANDING SELLING HELPS ARE SUPPLIED RAYTHEON DEALERS, INCLUDING SIGNS, POSTERS, BANNERS, COUNTER CARDS, WINDOW DISPLAYS, NEWSPAPER MATS, REPLACEMENT CHARTS, TECHNICAL DATA SHEETS, ETC.

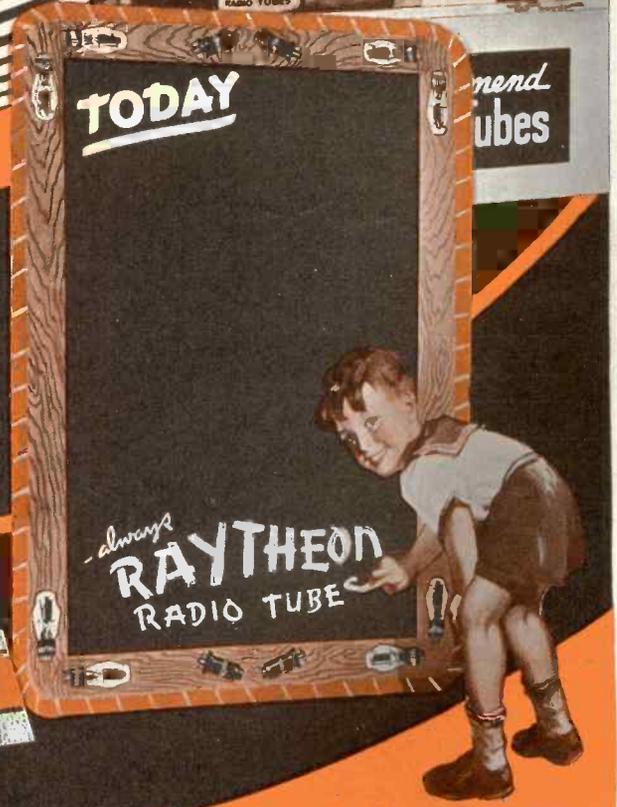WRITE RAYTHEON TODAY FOR YOUR SUPPLY OF THESE AIDS TO GREATER TUBE PROFITS.




THE MOST COMPLETE LINE—ALL TYPES OF GLASS, OCTAL BASE, METAL AND AMATEUR TRANSMITTER TUBES

RAYTHEON PRODUCTION CORPORATION

420 Lexington Ave., New York, N. Y. 55 Chapel Street, Newton, Mass.
 445 Lake Shore Drive, Chicago, Illinois 555 Howard Street, San Francisco, Calif.
 415 Peachtree Street, N. E., Atlanta, Ga.

radio and "man-made" static

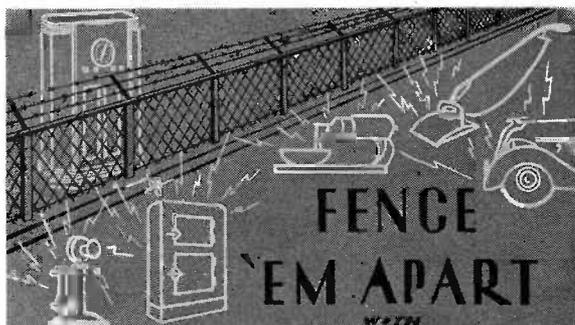

This trademark is your guarantee of the very finest in antennas and radio wire products . . . an acknowledged standard in the field.

THE "man-made" static caused by household appliances can be completely divorced from radio by installing "NOISE-MASTER", the modern antenna. Licensed by Amy, Aceves & King, this fine product improves radio reception on broadcast as well as shortwave bands. There is a model for every set and location. Servicemen interested in giving their customers the best—in really building up permanent good will—should investigate "NOISE-MASTER".

"NOISE-MASTER" No. 14 . . . \$6.75 list price

Amy, Aceves & King patented. Brings in overseas signals stronger, and eliminates "man-made" static on broadcast as well as shortwave band. For better reception in EVERY location.

"NOISE-MASTER" No. 18 . . . \$3.40 list price

First time at this popular price; licensed Amy, Aceves & King antenna of simple doublet type, SELF-SELECTING, recommended for clarifying shortwave reception.

"NOISE-MASTER" No. 19 . . . \$4.30 list price

SELF-SELECTING doublet type, Amy, Aceves and King licensed, with junction-box in the antenna line. Assures excellent all-wave reception.

Send for full particulars

CORNISH WIRE CO., Inc.

30 CHURCH STREET, NEW YORK CITY

SERVICE

A Monthly Digest of Radio and Allied Maintenance
Reg. U. S. Patent Office. Member, Audit Bureau of Circulations

EDITOR

Robert G. Herzog

SEPTEMBER, 1936

VOL. 5, NO. 9

EDITORIAL CONTENTS

FEATURES

An Impact Excitation Generator <i>By Alfred E. Teachman</i>	407
A Practical A-C, D-C Amplifier.....	432
Automatic Volume Control.....	412
Calibrated Condenser for the Service Bench <i>By Robert C. Moody</i>	442
Locating Intermittent Condensers <i>By Harvey Schock</i>	434
Pentode Used as High-Mu Triode.....	414
RCA Universal A-C Bridge.....	436

ANTENNA	398
---------------	-----

ASSOCIATION NEWS	444
------------------------	-----

AUTO RADIO

Antenna Shield Ground.....	430
Cadillac and LaSalle 6Q.....	428
Crosley A-266.....	426

CIRCUITS

Cadillac and LaSalle 6Q.....	430
Circuit Diagram of A-C, D-C Amplifier.....	432
Circuit for Condenser Calibration.....	442
Crosley A-266.....	426
Fairbanks-Morse 72.....	421
G.E. E-61, E-62, E-68.....	422
Intermittent Condenser Tester.....	434
Pentode Used as Diode and High-Mu Triode Front Cover	416
RCA 7T, 7K, 8T and 8K.....	418
RCA Speaker Connections.....	436
RCA Universal A-C Bridge.....	434
Signal-Divider Circuit.....	408
The Circuit Diagram of the Impact Excitation Generator.....	413
Typical Automatic Volume Control Circuit..	438
Wheatstone Bridge Circuit.....	438

GENERAL DATA

An Impact Excitation Generator <i>By Alfred E. Teachman</i>	407
Automatic Volume Control.....	412
Fairbanks-Morse 72.....	418
G.E. E-61, E-62, E-68.....	422
Locating Intermittent Condensers <i>By Harvey Schock</i>	434
Pentode Used as Diode and High-Mu Triode.....	414
RCA 7T, 7K, 8T and 8K.....	416
Technical Features of 1937 Zenith Radio Receivers	423

HIGHLIGHTS	446
------------------	-----

MANUFACTURERS	448
---------------------	-----

ON THE JOB

Calibrated Condenser for the Service Bench <i>By Robert C. Moody</i>	442
Condenser Trouble.....	442
Detecting Faded Colors <i>By Harvey Schock</i>	442
Locating Intermittent Condensers <i>By Harvey Schock</i>	434
Removing Knobs.....	442

PUBLIC ADDRESS

A Practical A-C, D-C Amplifier.....	432
-------------------------------------	-----

TEST EQUIPMENT

An Impact Excitation Generator <i>By Alfred E. Teachman</i>	407
Calibrated Condenser for the Service Bench <i>By Robert C. Moody</i>	442
Locating Intermittent Condensers <i>By Harvey Schock</i>	434
RCA Universal A-C Bridge.....	436

Copyright 1936—Bryan Davis Publishing Co., Inc.

BRYAN S. DAVIS
President

JAS. A. WALKER
Secretary

Published Monthly by the

Bryan Davis Publishing Co., Inc.

19 East 47th Street

New York City

Telephone: Plaza 3-0483

SANFORD R. COWAN
Advertising Manager

PAUL S. WEIL
Eastern Advertising
Manager

A. B. CARLSEN
Circulation Manager

Chicago Office—608 S. Dearborn St.—C. O. Stimpson, Mgr.
Telephone: Wabash 1903

Wellington, New Zealand—Tearo Book Depot.

Cleveland Office—10515 Wilbur Ave.—J. C. Munn, Mgr.
Telephone: Republic 0905-J

Melbourne, Australia—McGill's Agency.



Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

PICK A WINNER THIS YEAR

NEW

"PRECISION"

ELECTRONOMETER SERIES 600

A MODERN TUBE ANALYZER

COMBINED WITH

- ★ 4 VOLTMETER RANGES...
- ★ 3 OHMMETER RANGES...
- ★ 3 MILLIAMMETER RANGES...
- ★ CONDENSER LEAKAGE TESTS

"PRECISION" engineers developed the "600" to provide the radio technician with an instrument of compact size that will enable the obtaining of modern radio tube analyses and set analyses and many important radio analyses; eliminating the inconvenience of carrying or the expense of purchasing several test units.

A COMBINATION test instrument... A modern tube analyzer with many adequate radio set analyses features... Flexible for future releases... Built to withstand "rough" usage...



PRECISION

Apparatus Corporation

821 EAST NEW YORK AVENUE
BROOKLYN • NEW YORK

LET us RUSH full information on the NEW ELECTRONOMETER, Series 600; including the name and address of your local distributor.

THE ANTENNA . . .

IN THIS ISSUE

PADDING THE LOW-FREQUENCY end of each band has always presented some difficulty. Not only is considerable time spent trying to accomplish three things at once but there is no assurance as to the accuracy of the adjustment, if the present accepted method of padding is used. The Service Man usually hopes that the adjustment finally selected is the one giving the "maximum output from the combined operations," but he cannot be sure.

In the May issue of SERVICE, Mr. G. F. Devine described a method designed to accomplish accurate padding condenser adjustment without rocking the tuning control during the adjustment. This method is used successfully at the General Electric Company, and has since been adopted by other receiver manufacturers for their production lines.

In this issue Mr. Alfred Teachman, in presenting his "Impact Excitation Generator," a similar broad-band generator, goes further by giving complete constructional details. In addition the many uses for his inexpensive device are discussed and complete instructions presented.

The use of either the multi-vibrator described in the May issue of SERVICE or the impact excitation generator covered in this issue gives the Service Man a method of completing the padding condenser adjustment easily and accurately. He will find himself well repaid for the expense and time entailed in the purchasing or building of the impact excitation generator, especially if he learns to use it for the many purposes set forth in this issue of SERVICE.

• • •

INCREASED FALL BUSINESS

WITH THE PASSING OF LABOR DAY the season of vacations is over. The annual wanderlust that invades the body must be put aside as we buckle down to business again. People returning home in September have always

brought increased business to the Service Man—he should be prepared to meet this increase.

New tubes, new parts, new antennas and other new accessories will be in demand. The Service Man should stock up and then make a concerted effort toward encouraging this business. Complete check-ups should be suggested to his customers at an attractive price in his window advertising, direct mail advertising and in all other advertising. The time to act is now—tomorrow may be too late!

• • •

FREE SERVICE INSPECTIONS

MUCH HAS BEEN SAID BY Service Men and editors both for and against free service inspections—mostly against. Without taking sides in the matter permit us to mention that although these calls have been used as a come-on racket there *are* two sides to the question.

• • •

FREE ADMISSION TO THE TRADE SHOW

COINCIDENTALLY WITH THE APPEARANCE of this issue the Fourth Annual New York IRSM Convention and Trade Show opens on the mezzanine floor at the Hotel Pennsylvania in New York City. A list of the exhibitors and their booth numbers is included in this issue on page 444.

The Institute of Radio Service Men invites the public as well as the entire radio trade to visit the show and listen to the attending lectures. No admission fee is charged.

SERVICE also invites you to visit booth number 48.

TUNG-SOL DEALERS

make money

**WITHOUT INVESTING
A CENT**

The Tung-Sol plan was the first and is today the only nation-wide consignment plan for selling radio tubes. It has been successful because Tung-Sol dealers carry adequate stocks of tubes which build customer satisfaction, and make full profits on their sales.

There are still desirable locations where independent service organizations who can meet requirements may be appointed as agents. Ask your nearest Tung-Sol wholesaler.



TUNG-SOL LAMP WORKS, INC. *Radio Tube Division*

SALES OFFICES: Atlanta, Boston, Charlotte, Chicago, Dallas, Detroit, Kansas City, Los Angeles, New York. . . . General Office: Newark, N. J.

TUNG-SOL
Tone-flow radio Tubes

Announcing

IRC
REG. U.S. PAT. OFF.

Metallized

VOLUME CONTROLS

for Radio Service and Amateur Use

1. "Knee Action" Contact

Made by 5 separate silver plated phosphor bronze springs.

2. No "Jumping"

No jumping or shifting of points of contact. Each contactor invariably follows the same smooth "path" across the resistance element.

3. No Obstructions


IRC contact method on tapped controls eliminates obstructions in path of contactor. Smoother adjustment—no noise.

4. Dust-Proof Case

No openings or slots in covers.

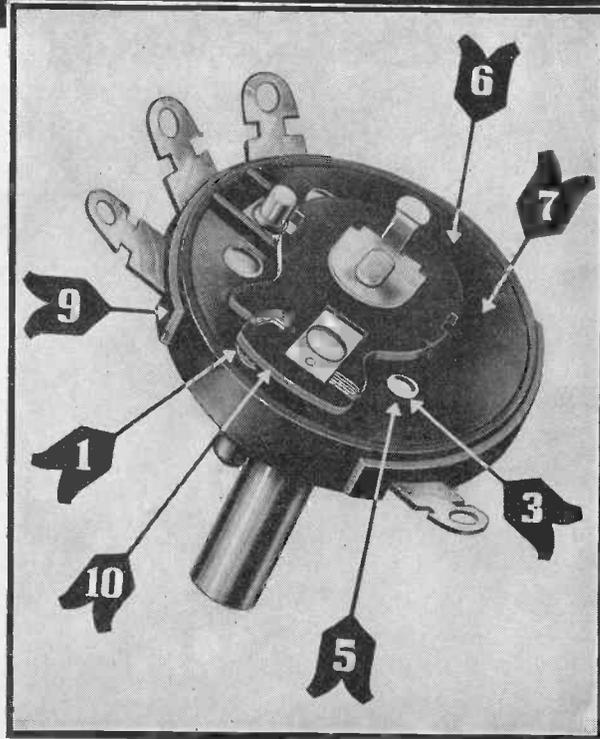5. Corrosion-Proof

All electrical contacts are proofed against corrosion and oxidation.



6. Metallized Type Resistance Element

Permanently BONDED to moisture-proof Bakelite base.

7. Moisture-Proof

The Bakelite base of the resistance element CANNOT absorb moisture—nor will moisture damage the Metallized type resistance coating.

8. Small—But Not Too Small

Minimum size for universal application and maximum performance.

9. Protected Terminals


Deeply set in molded Bakelite casing.

10. Amazingly Smooth

Smoothly, yet firmly, the 5 contactors glide over the hard wear-proof surface.

with the **10** MOST IMPORTANT FEATURES EVER OFFERED IN A VOLUME CONTROL

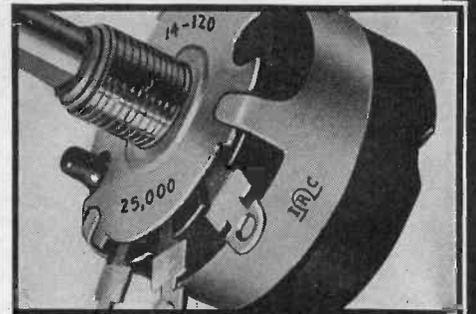The world's best known maker of fine resistance units scores again! For several years IRC Volume Controls have been supplied to leading radio and electrical manufacturers. Now, in a complete range of types, they are offered for service and amateur use as the outstanding replacement control development in the history of radio! Featured by leading jobbers. See them—try them—write today for catalog.



Actual size illustration of IRC Type "C" Volume Control with switch.

INTERNATIONAL RESISTANCE COMPANY
401 NORTH BROAD STREET • PHILADELPHIA


FLASH—MORE BIG NEWS!

NEW Type BT-2 (2-watt) INSULATED Metallized Resistors now ready
List Price 30c

NEW LOW PRICES on both ½-watt and 1-watt
INSULATED Metallized Resistors effective Sept. 1

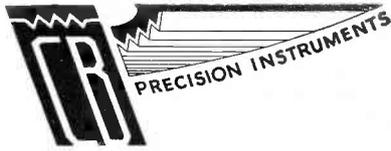½-watt (Type BT-½) List 17c 1-watt (Type BT-1) List 20c






are easy to buy on THIS liberal plan!


Lower down payment—Easy monthly payments

Study these specifications

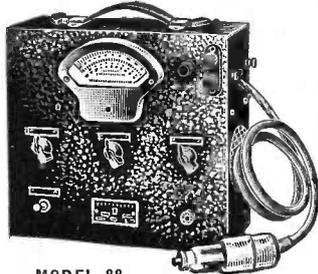

MODEL 88

MODEL 88 Combination Vacuum Tube Voltmeter and Peak Voltmeter is a logical companion for the MODEL 99 Signal Generator. With this sensitive instrument, stage by stage gain is accurately measured. New application bulletin now ready. Net cash.....\$42.50 (Only \$5.00 down and ten monthly payments of \$4.29.)

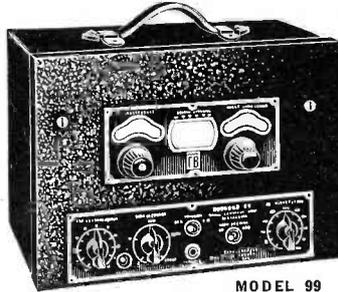

MODEL 99

MODEL 99 Signal Generator, net cash.....\$43.90
(Only \$5.00 down and ten monthly payments of \$4.44.)


Complete Service Laboratories! Rack and panel style foundation cabinet for bench use may be purchased in any of the combinations listed below. All C-B instruments are now offered optionally in 19" rack mounting style. Series 1000 as illustrated at right, net cash \$299.50 complete, down payment \$33.70. Series 1010, same less MODEL 95, net cash \$249.50, down payment \$28.00. Series 1040 includes MODEL OC-A R-F Signal Generator and MODEL 95 Super-Unimeter in Laboratory Cabinet Rack with Lumaline Floodlight, net cash \$104.50, down payment only \$12.00.




MODEL 79-A

MODEL 79-A Beat Frequency Audio Oscillator for precision study of audio wave form and Cathode-ray analysis, P. A. tests, etc. Net cash price..\$53.75 (Only \$6.00 down and ten monthly payments of \$5.45.)

MODEL OM-A R-F Signal Generator with the new "INDUCTOR-SWEEP" wobbulator. Provides accurate selectivity curves on Cathode-ray oscillograph screen. Fundamental range of 100 kc to 30 mc with accuracy to 1/2 of 1% with fixed-width plus and minus 20 kc sweep. Hand calibrated against Arlington checked precision crystal frequency standard. Wobbulator has plus or minus 20 kc "INDUCTOR-SWEEP" at all test frequencies. Metal tubes included. (Only \$6.50 down and ten monthly payments of \$5.85.)

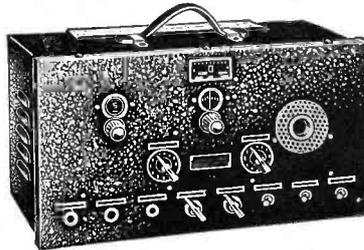

MODEL OM-A
Net cash \$57.75

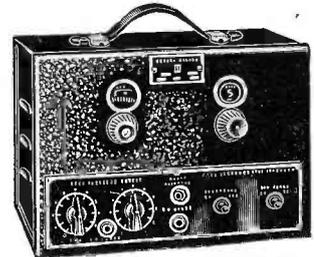

MODEL OC

This popular all-wave signal generator is continuously variable on fundamental frequencies from 100 kc to 30 mc through five tuning bands. Calibrated against Arlington time checked crystal frequency standard, guaranteed within 1/2 of 1% frequency accuracy. These new improved models are rugged, dependable sources of r-f signal energy for all types of alignment tests on radio receivers. MODELS OC-A and OC-B have metal tubes. Compare these precision hand-calibrated models with any similarly priced instruments. Compare the fine engineering, performance, and value of the OC MODELS. You can rely on C-B equipment.



MODEL 95

MODEL 95 Super-Unimeter measures all a-c and d-c volts and d-c milliamps, resistance, and capacity (.00025 to 16 mfd.) encountered in radio. Twenty ranges! Net cash.....\$47.75 (Only \$5.50 down and ten monthly payments of \$4.83.)



MODEL CRA

MODEL CRA Cathode-Ray Oscillograph consists of the power supply, controls, and wide range sensitivity amplifiers for the two pair of plates, the linear "saw-tooth" sweep voltage generator, and all tubes, including the 3-inch Cathode-ray tube. Everything necessary for scientific receiver analysis. The C-B oscillograph is simple to operate and its stability assures dependable results. It opens new avenues of profit and experience for servicemen. With the coming of television, these servicemen familiar with the Cathode-ray will be leaders. MODEL CRA, net cash \$84.50. (Only \$9.50 down and ten monthly payments of \$8.36.)

"PAY-AS-YOU-EARN"

The NEW liberal plan for easy time payments permits you to immediately start earning. Note the lower down payments. Let these business building instruments start paying for themselves in the added profits which result from the use of modern laboratory type equipment. See your nearest C-B jobber today and learn how you, too, can enjoy this fine modern equipment in your own service shop, or mail the coupon for complete catalog and time payment application blank.



MODEL 85-A Uni-meter. A 4 1/2-inch fan-type meter with ranges of 5, 50, 500, 1000 v. d-c; 5, 50, 500 m. d-c; 15, 150, 750 v. a-c. Ohms range 100, 20,000, and 2 megs. Rotary selector switch principle. Net cash \$24.95.

(Only \$4.00 down and seven monthly payments of \$3.44.)

MODEL OC-A R-F Signal Generator for operation from 110 volt 50-60 cycle lines, complete with tubes and calibration curves. Net cash \$29.95.

MODEL OC-B same as OC-A but for 110 volt ac-dc operation. Net cash \$29.95.

MODEL OD-A same as above but for operation from self-contained battery supply. Less batteries. Net cash \$29.95. (Only \$4.50 down and seven monthly payments of \$4.20.)

The CLOUGH-BREngle CO.

2817 W. 19th St., Chicago, Illinois.

Rush us full details (no obligation) on all instruments in the new C-B SUPER SERVICE line and "Pay-As-You-Earn" application blank.

NAME

ADDRESS

THE ULTIMATE IN SUPER-SENSITIVITY

- ① [★] NO CURRENT DRAIN
PLUS
- ② ^{★★} SELF CALIBRATION

MODEL
1250

TRIPLET VACUUM TUBE VOLTMETER

★ Means accuracy cannot be affected by the current drain of the instrument itself. Permanent accuracy of Triplet Vacuum Tube Voltmeter is assured by the self calibrating bridge circuit used.

★★ The most important advancement in circuit design for precision electrical instruments in recent years.

Laboratories and engineers will use and immediately appreciate the significance of this remarkable instrument. Indispensable also in the servicing field for measuring electrical impulses either A.C. or D.C. of low magnitude such as the carrier wave of signal circuits, and particularly for television work.

The self-calibrating feature is automatic with the tube bridge circuit developed by Triplet engineers (Pat. Pending). The initial operation of adjusting the bridge at the zero level insures

THIS IS A TRIPLETT MASTER UNIT
See your jobber—write for more information

THE TRIPLETT ELECTRICAL INSTRUMENT CO.
179 Harmon Drive, Bluffton, Ohio

- Without obligation please send me complete information on Triplet Vacuum Tube Voltmeter.
- I am also interested in

Name

St. Address

City State



DEALER PRICE
\$33.34

exact calibration independent of tube emission values or when replacing tubes.

Model 1250 is furnished with Triplet Tilting type twin instrument. One instrument indicates when bridge is in balance. The other is a three range voltmeter with scales reading in peak A.C. and D.C. voltages. Ranges are 2.5, 10 and 50 volts. Other ranges to order.

Model 1250 is complete with all necessary accessories including 1-84, 1-6C6, 1-76. Case is metal with black wrinkle finish, panels are silver and black. Dealer Price.....\$33.34



The BIG CONDENSER FIGHT Begins!



WATCH THAT TOBE FLEXIDON! HE'S LIKE TWO CONDENSERS IN ONE!

G'WAN THE UP-AND-COMER IS TOBE TUBIDON.. AND HE WORKS FOR LESS MONEY!



"TOBE" TUBIDON vs "TOBE" FLEXIDON

We consider TOBE TUBIDON and TOBE FLEXIDON such ultra-fine condensers that we just can't imagine how either can lose in this big fight for condenser supremacy. But the answer is up to you... compare their advantages: TOBE TUBIDON is tubular-shaped, up to 525 volts, self-supporting, easier to install, and *lower in cost*. TOBE FLEXIDON is rectangular-shaped, up to 525 volts, space-saving design... with the big feature of *flexibility* (the fact that if one section breaks down, it is necessary to replace *only* the broken section.)


Which do you favor in this big battle? Note how they shape up... read the exact specifications. Remember that both are *topnotchers*... thoroughly moisture-proof, double-jacketed, asphalt impregnation and heavy wax seal, added protection against developing open circuit or high resistance contact... all the features born of skillful manufacture and long experience.

SEE THE CONTESTANTS IN PERSON AT ALL GOOD RADIO JOBBERS

Ask for them by their nicknames, TOBE TUBIDON and TOBE FLEXIDON. And, if you wish to receive our complete illustrated TOBE CATALOG fill in the coupon below, and mail today.

HOW THEY SHAPE UP...

	TUBIDON	FLEXIDON
VOLTS	35-50-200-525	200-525
MFD.	35v.—5 to 50 50v.—5 to 25 200-525v.—1 to 16	1 to 16 (single) (multiplies up to triple eight)
MAXIMUM SIZE	2-1/4" x 1"	3-1/4" x 1 5/8" x 1 5/8"
MINIMUM SIZE	2-1/4" x 1/2"	2-1/8" x 7/8" x 7/8"
TYPE LEADS	solid bare tinned copper wire	insulated tinned copper wire
LEAD LENGTHS	2-1/2"	6"
MOUNTING	self supporting by leads	metal eyeletted tabs
PRICE (typical 8 mfd.-475v.)	\$.75	\$.95

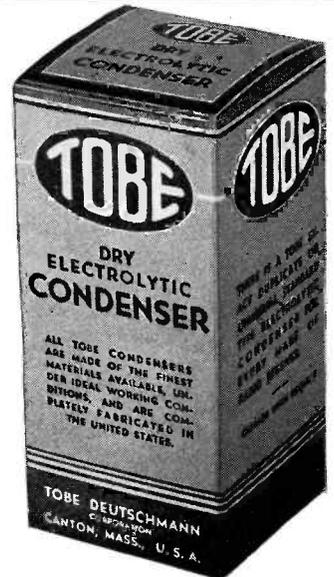

ELECTROLYTIC CONDENSERS

Skillfully Manufactured at Canton, Mass.

TOBE DEUTSCHMANN CORP.
Dept. J-10; Canton, Massachusetts


Please send FREE OF CHARGE full technical description of TOBE TUBIDON and TOBE FLEXIDON, including your complete TOBE catalog.

Name

Street

Town..... State.....

HIGH PRESSURE is out!

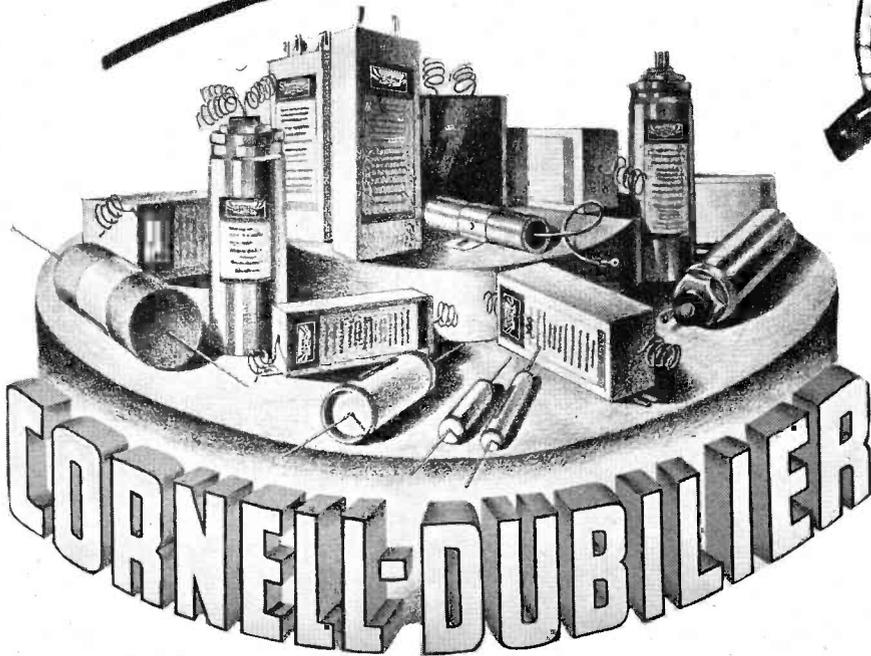

THOUSANDS of Servicemen throughout the world have learned that it pays to standardize on Cornell-Dubilier condensers. They know that the use of Quality condensers means the elimination of those expensive FREE repeat calls—that C-D condensers mean customer satisfaction. Use C-D's on your next service job and build your reputation.

IT required no "high pressure" sales campaign to put Cornell-Dubilier condensers "across." Our success formula is simple: "Make a BETTER product—price it RIGHT—tell 'em about it."

C-D products have always been built UP to a standard—never down to a price, yet, C-D production is so enormous that C-D price schedules are in line with modern day requirements.

Cornell-Dubilier Dry Electrolytics, utilizing the "High Formation" process of manufacturing, are triply sealed in their containers by a special method, assuring maximum efficiency in operation—indefinite shelf life

and unfailing, dependable service. C-D Electrolytics are available in a complete line of aluminum containers and cardboard cartons. All electrolytics are supplied with either lug or lead terminal assembly.

For the light service jobs the "Handy Mike" series fill the bill. Constructed in handsome silver cartons, they are convenient for mounting and simple to hook into the circuit.

Look for the C-D display featuring the entire condenser line for the servicing fraternity. Descriptive catalogue No. 128 sent on request.

MICA • DYKANOL • WET AND DRY ELECTROLYTIC • PAPER

CORNELL DUBILIER

1026 HAMILTON BOULEVARD

SOUTH PLAINFIELD, N. J.

TWO PRECISION TESTERS


FOR THE PRICE OF ONE

Each Ranger-Examiner Combination puts together in one case two (2) units of test equipment every serviceman needs in his everyday work. The savings effected in design and in using this exclusive Ranger-Examiner grouping permits offering these combinations of two Precision Testers at prices you would normally expect to pay for one.

Each item is precision built throughout by the oldest company in the service equipment field. Their past contacts with the trade as well as with every advancement in the field of radio make them fully acquainted with the needs of the service profession. From the standpoint of sheer merit Ranger-Examiner testers are becoming popular favorites with radio servicemen.



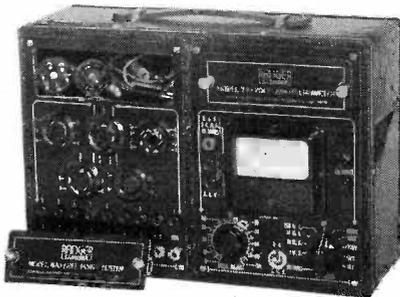COMBINATION FREE POINT TESTER AND VOLT-OHM-MILLIAMMETER MODEL 640-740



Model 640 Free Point Tester has five (5) sockets. Panel includes automatic switch type and single action jacks.

Model 740 VOLT-OHM-MILLIAMMETER Unit has a Triplett Precision Instrument scale reading 10-50-250-500-1000 A.C. and D.C. volts at 1000 ohms per volt. 1-10-50-250 M.A.; low ohms 0-300; high ohms to 250,000 at 1.5 volts. Rheostat adjustment.

Model 640-740 is contained in the standard size metal carrying case above described.

Dealer Price \$27.00

ADDITIONAL COMBINATIONS

Using the same standard size metal carrying case the following additional combinations may be had; the testers in all cases being identical with foregoing descriptions and complete with necessary accessories.

MODEL 540-740 Signal Generator and Multimeter — DEALER PRICE \$36.00

MODEL 440-740 Tube Tester and Multimeter — DEALER PRICE \$37.50

DIRECT READING SIGNAL GENERATOR MODEL 557



Model 557 has the same features as described for Signal Generator Model 540 except that it is installed in a black leatherette carrying case and is an integral part of the case. The five individually calibrated coils are nested on the side as shown, handy for instant use. The attractive panel is silver and black.

Dealer Price \$18.00

Model 557-A is the same as Model 557, but not direct reading. Calibrated graphs included for accuracies under 1% on any band.

Dealer Price \$14.40

COMBINATION TUBE TESTER AND SIGNAL GENERATOR 440-540



Model 440-540 has the two separate testers installed in a sturdy metal carrying case for shop or field use.

COMPLETE DEALER PRICE \$33.60

Model 440 Tube Tester checks all type tubes. Condition of tubes is read directly on GOOD-BAD instrument scale while load values are applied. Circuit designed to indicate inter element shorts and leakages. Illuminated dial A.C. instrument for line volts adjustment, also shows when tester is connected to power supply.

Model 540 Signal Generator uses plug-in type coils. Five frequency bands cover 110 to 20,000 K.C. All readings are direct on fundamentals. Each coil is individually calibrated by peaking with trimmer condensers. Accuracy, within one percent (1%) from 110-3000 K.C.—2% for higher readings. Completely shielded. Attenuation and stability are outstanding features. Complete with coils, two type 30 tubes, batteries and necessary accessories.

Model 440-540 consists of these two instruments installed in a sturdy metal case with built-in compartment having snap on cover for accessories, finished in electro black baked enamel, panels in silver and black. Every essential feature is incorporated in these outstanding instruments. No extravagance. No added unnecessary cost. To see one—to use one—means you will be glad to own this outstanding tester.

D.C. POCKET VOLT-OHM-MILLIAMMETER MODEL 735

D. C. Pocket Volt-Ohm-Milliammeter-Model 735. Contained in sturdy black molded case with silver and black panel, rounded corners. Ranges are 15-150-750 volts; 1.5-15-150 M.A.; 1/2-1,000 low ohms; 0-100,000 high ohms at 1.5 volts. Provision for external batteries to be used for higher resistance measurements.

Has Triplett D'Arsonval precision instrument accurate to 2%. Selector switch for all ranges. Provides for all D.C. measurement requirements of the serviceman.

Size 3 1/8" x 5 7/8" x 2 3/8" deep—is easily carried in the pocket, and handy for the laboratory complete with battery, test leads and alligator clips.



DEALER PRICE \$10.80

See them at your Jobber—Write



READRITE METER WORKS,
917 College St., Bluffton, Ohio.


Without obligation please send me more information on
..... Ranger-Examiner Combination

Name

Address

City State

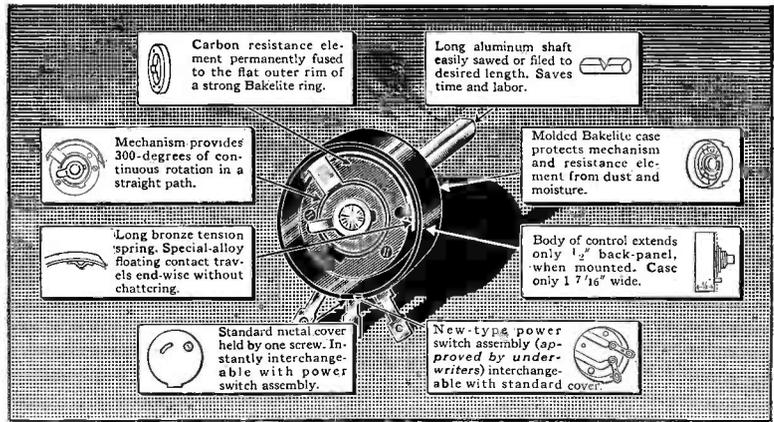The direct friction contact principle used in the Electrad Carbon Volume Control is the basic reason for its smooth, electrically quiet operation. Every Electrad control is noise tested at the factory and fully guaranteed.



Whatever the Replacement calls for...

ELECTRAD Has the Right Control for the Job!

Electrad's specialty is replacement volume controls. Electrad's policy is "a control that is mechanically and electrically right for any receiver model."

To make that policy good, Electrad spends thousands and thousands of dollars every year for engineering development.

That is why you can always find the *right* Electrad control for a quick, accurate and lastingly satisfactory replacement. And that is the kind of replacement that puts *real* profit into your pocket!

Use an Electrad on your next replacement job—and you'll have no kick back! Long aluminum shaft easily cut to required length, standard end covers instantly interchangeable with power switch assembly.



A Service "Tool" You Really Need

The Electrad Volume Control Guide is a real *guide* to quick, accurate replacements. It puts at your fingertips volume control facts that can't be found anywhere else in such handy form. Contains approximately 150 pages of information. You can get it FREE if you will send one complete Electrad Volume Control carton, with your business card or letterhead to Dept. S9.

ELECTRAD, INC.

175 Varick Street

New York, N. Y.

ELECTRAD

RESISTOR SPECIALISTS IN RADIO AND ELECTRICAL INDUSTRY SINCE 1923

SERVICE

A Monthly Digest of Radio and Allied Maintenance

FOR SEPTEMBER, 1936

AN IMPACT EXCITATION GENERATOR

By ALFRED E. TEACHMAN

AT one time or another it has probably been the dream of every Service Man to own a flock of calibrated crystal oscillators with enough separate oscillators to cover the entire radio spectrum. Barring the expense of such a layout, there are some very practical possibilities in the idea. If a number of test oscillators were spaced 10 kc apart over the entire radio spectrum, all having the same output intensity and fed through a master attenuator, we would at once have a rapid and easy method of testing receivers for regions of low sensitivity by merely sweeping the tuning dial over the range. Improper tracking could be quickly detected since it is the most common cause of low sensitivity when confined to a portion of the band.

A single oscillator rich in harmonics might be used having a base frequency of 10 kc and therefore a harmonic every 10 kc. The difficulty here is that the harmonics do not have the same intensity and grow rapidly weaker at the higher frequencies. Some success might be had in using a motor to drive the tuning condenser of a regular generator and thus keep the spectrum alive. In fact, something of this nature is now widely recommended for locating the optimum adjustment of 600-kc padding condensers. The procedure is to use an oscilloscope signal wobbulator attached to the signal generator for providing a band of frequencies in the region of 600 kc. The point of maximum output is located without reference to the exact frequency at which it occurs. Even at first glance the idea seems worthy of further investigation as a new method of attack since anything which will speed analysis and adjustment and assure accuracy in service work is greatly needed.

The idea of the harmonic generator seems to be the most practical approach to the development of a generator satisfactory for the purpose. In effect, what is required is an essentially con-

tinuous spectrum of radio frequencies of equal amplitude, thus obviating the need for a tuning control on the signal generator. If a harmonic generator is to be used, it must have harmonics of practically equal strength. The strength of the harmonics is governed by the wave shape of the plate circuit impulses, but in common r-f oscillators these impulses cannot be developed into a form sufficiently rich in harmonics suitable for the purpose.

To have uniform harmonic strength, it is essential that the waveform be very steep. In fact, it is because of the steep waveform produced by X-ray machines and various other electrical devices that they create radio interference troubles over wide bands of frequencies. The spark coil and buzzer were used to impart radio oscillations in the tuned circuits of early radio transmitters and wavemeters. The buzzer in particular was widely used to

excite wavemeters into oscillation. Its waveform output (see Fig. 3) contains harmonics of sufficient strength to excite tuned circuits from the lowest radio frequencies to well up in the short wavelengths. Although the harmonics are not strictly uniform in strength, the falling off is very gradual with frequency being most noticeable toward the high-frequency end. The trend is so gradual as to be hardly noticeable over the range covered by a single band in a home receiver.

THE IMPACT GENERATOR

The small size and convenience of the buzzer leads to its choice as a most suitable generator of the desired harmonic waveform. Considered from the viewpoint of harmonic theory, it is capable of furnishing harmonics of less than 1 kc apart since its fundamental frequency will generally be somewhere below this figure. Actually it will ex-

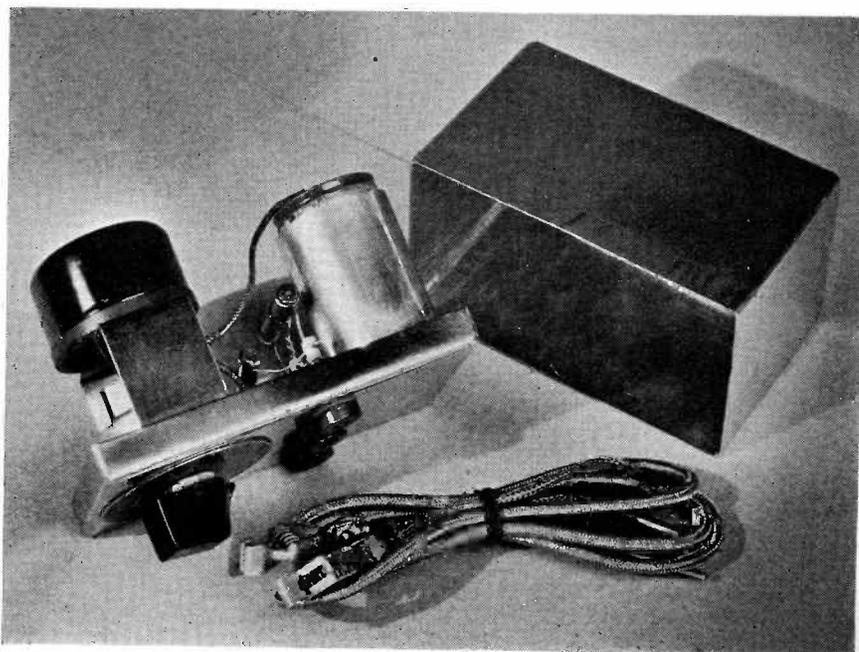


Fig. 1. The impact excitation generator.

cite any r-f circuit regardless of its harmonic relation, for at such high harmonic ratios the r-f oscillations of the tuned circuit will cease before the next impulse. Such a generator might well be called an impact generator and the system impact excitation.

The high steep part of the buzzer waveform illustrated in Fig. 3a is caused by the sudden interruption of the current when the contacts open. The energy stored in magnetic lines of force about the magnet instantly collapse and if there were no escape for the resultant reverse voltage it would rise to infinite value. This cannot happen because the contacts cannot open faster than the voltage builds up and as a result a small arc dissipates some of the energy at the contacts. It is the erratic nature of this arc which causes poor tone when the buzzer is used to generate r-f oscillations. To overcome this difficulty, a resistor is placed in shunt to the buzzer magnet coil and serves to dissipate some of the energy, thus controlling the rise of inductive voltage to a point where the contacts can properly interrupt the current and produce a recurring wave pattern.

A practical circuit for an impact excitation generator is shown in Fig. 2. The output control serves both as a load resistor to shunt the magnet coil and as a variable output control. When the generator is connected to the antenna posts of a receiver it permits a rapid check of the sensitivity conditions existing throughout the various bands.

Figs. 3a, 3b and 3c show a stage-by-stage development from the waveform output of the buzzer to the audio output voltage at the speaker. The sketches are from observations made with an oscilloscope.

Fig. 4 shows graphically the results obtained when a standard multiband receiver was tested with a laboratory type signal generator and with the impact generator. Because of technical difficulties involved, it was found best to take the test with constant attenuator settings and plotting the output meter readings. The AVC action had been disconnected and the input signal strength set at a minimum.

USING THE IMPACT GENERATOR

From the foregoing discussion it is evident that the impact generator is a radically different approach to the test generator problem and in effect it generates a test signal which has no tuning characteristic. This is quite contrary to the accepted type of signal generator which makes use of a single frequency or one of its related harmonics.

Although it may be easily understood that such a generator could be used to explore the tuning range of a receiver for locating "holes" and low sensitivity

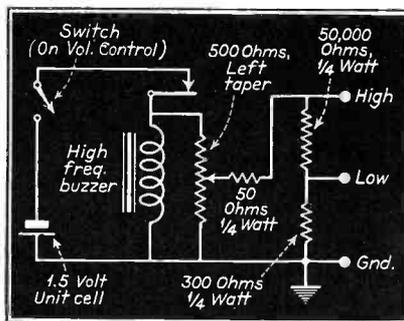


Fig. 2. Circuit diagram of the generator.

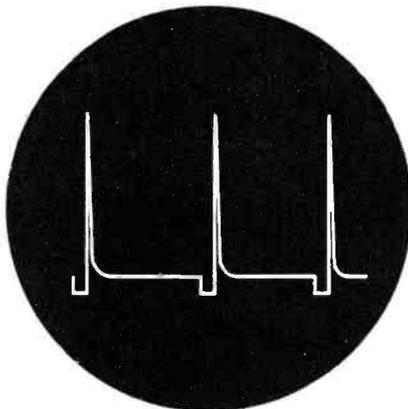


Fig. 3a. Buzzer wave.

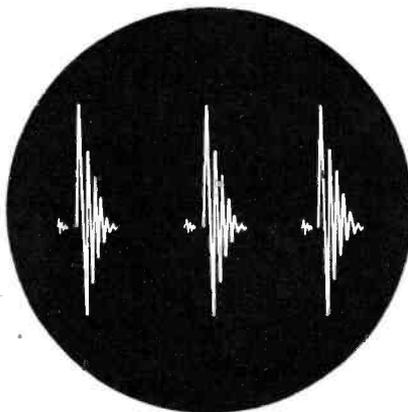


Fig. 3b. R-F oscillations.

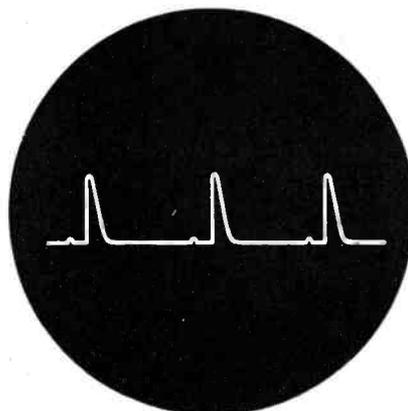


Fig. 3c. Audio wave.

regions, it may not be so apparent that it can be very successfully used in tuning-up processes. The question is—how can tuning or resonating be accomplished to a signal that has no tuning characteristic? The answer to this is simple and brings out an interesting fact. If the impact generator is connected to the antenna posts of a receiver it will shock the first tuned circuit into oscillation. The oscillations which follow each impulse will take on the frequency of resonance in the first tuned circuit. Thereafter as the signal passes on through the remaining tuned circuits it will be more sharply filtered or tuned. The fact that the first tuned circuit takes on its own frequency of oscillation is an interesting point since it means that at no time can the signal generator be out of tune with the receiver. The importance of this fact when making certain tests will later be shown. The frequency generated in the first tuned circuit will have broad resonance, and in general it will be somewhat broader than the natural selectivity of the circuit. The reason for this will be seen from a study of Fig. 5 in which the short vertical lines represent the harmonic frequencies present in the generator output. If the buzzer is tuned to 1,000 cycles, then the harmonics will fall 1,000 cycles apart over the entire spectrum and their effect on the resonant rise of voltage in a tuned circuit is illustrated by the curved line. The maximum rise in voltage will take place exactly at resonance, but the additive components of the adjacent frequencies will cause the resonance curve to be more rounded than the natural selectivity curve of the circuit. It is worth noting that there will be only one resonant rise of voltage in the spectrum and, if the tuned circuit is resonant at 1,500 kc, there will be no resonant rise at 3,000 kc or any other harmonic relation.

While practical tests indicate that the output of the impact generator falls off very slowly up into the region of 30 meters, there are some theoretical considerations which would seem to indicate that it should be much more rapid. It seems reasonable to suspect that the superheterodyne circuit has much to do with the results obtained since the greater amplification takes place at one fixed frequency.

In using the impact generator, it should be understood that there are certain service procedures which cannot be accomplished without a tuned type signal generator. However, the impact generator has a field of usefulness untouched by any other method.

SIGNAL INJECTION TEST

The difficulties of running down an

No Headaches over

HIGH SURGE

P. R. MALLORY & CO. Inc.

MALLORY

Replacement Condensers are Surge-Proof

Surge-Proof — because an exclusive Mallory development makes use of the "Constant Wattage" characteristic of radio power packs to keep surge voltage well below the danger point.

That's a big help! You will never "get a pain in the neck" from high surge troubles when you use Mallory for replacements.

"Surge-Proof" is only one of the many features of Mallory Replacement Condensers — they have greater efficiency; are humidity-proof; built to meet high temperatures; easy to install because of smaller sizes and the exclusive Mallory Universal Mountings — a combination of advantages that only Mallory can offer.




Twenty Minutes Reading Saves You Hours of Servicing

Read the Mallory Replacement Condenser Manual! A 94-page book — but only twelve reading pages (reading time: 20 minutes) gives you the complete story, — shows you just how the Mallory Universal Replacement idea saves you hours of servicing and insures real profits from the finest servicing any man can do. You owe it to yourself to study this manual.

Everywhere service men are saying — "a swell help — the Mallory Manual and Mallory Parts" . . . "Invaluable for the best service" . . . "Worth its weight in gold" . . . "Mallory Condensers can really take it" . . . "I can depend on Mallory" . . . We receive thousands of such letters from satisfied service men. It is proof positive that Mallory Replacement Condensers for universal replacement service have what it takes to produce quality service, solid profits and satisfied customers.

Use Mallory Replacement Condensers — ask your distributor now!

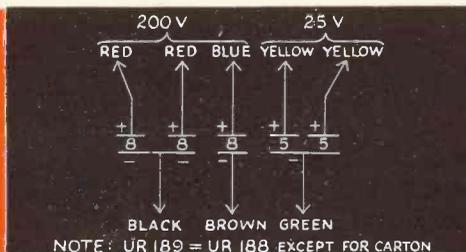Two Examples of New Mallory Universal Replacements



P. R. MALLORY & CO. Inc.

MALLORY

P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA
Cable Address—PELMALLO

YAXLEY

OVER WITH A

BANG


THE WESTON

MODEL 772

Super-Sensitive Analyzer

PRICE \$ **46** ⁵⁰/_{NET}

TO DEALERS
IN U.S.A.

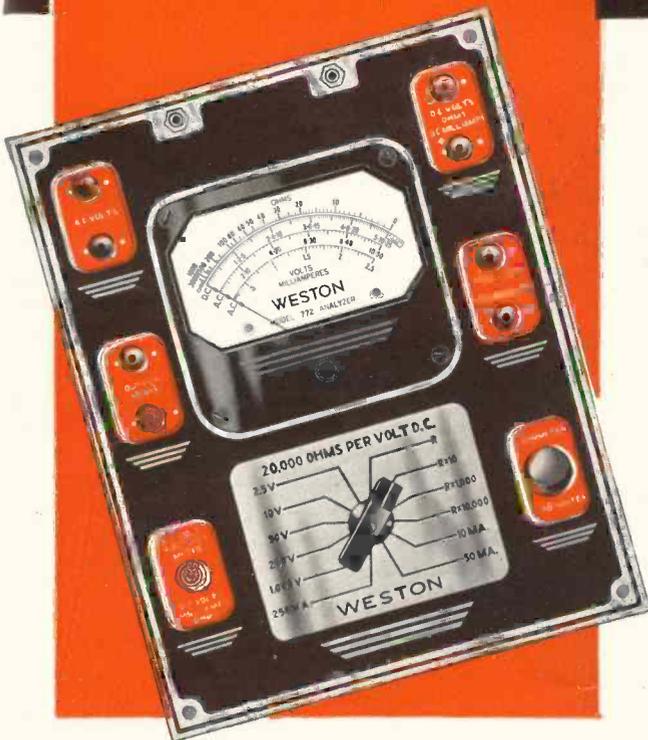

THE NEW WESTON ANALYZER . . . WITH
SENSITIVITY OF 20,000 OHMS PER VOLT,
MEETS WITH OVERWHELMING RESPONSE—
servicemen won't take less!

Announced but one month ago, the new WESTON Model 772 Super-Sensitive Analyzer is sweeping the service field. With sensitivity of 20,000 ohms per volt . . . with resistance ranges usable up to 30 megohms . . . with current measurements as low as ½ microampere . . . with a wide range of usefulness, including *all* radio receivers, old or new; television sets, amplifiers, sound movies, P.A. systems and photo-cell circuits . . . with a big, super-sensitive WESTON Meter . . . and, above all, being WESTON built throughout, it's no wonder that servicemen, everywhere, are equipping with this new device. For there is nothing that compares with Model 772, except in laboratory instruments, and at laboratory prices.

Be sure you get full particulars on Model 772 before you buy any set tester. Also, be sure to get complete information on the WESTON Model 771 Checkmaster, the portable tube checker equipped for quick and dependable trouble shooting. Return the coupon today . . . Weston Electrical Instrument Corporation, 604 Frelinghuysen Ave., Newark, N. J.

THE WESTON MODEL 771 CHECKMASTER

PRICE \$ **45** ⁰⁰/_{NET}

TO DEALERS
IN U.S.A.

Compact . . . attractive . . . tests all present tubes—neon short check—voltage ranges for point-to-point testing—resistance ranges for continuity testing, etc. For counter and portable use.



WESTON
Instruments

Weston Electrical Instrument Corp.,
604 Frelinghuysen Ave.,
Newark, N. J.

Rush me bulletin on the new Super-Sensitive Analyzer,
and the Checkmaster.

NAME

ADDRESS

CITY STATE

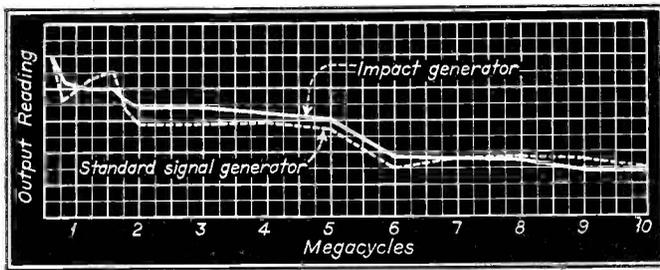


Fig. 4. Comparison test showing generator outputs over the tuning range.

off and on condition need no elaboration, but when this condition is due to a defect in the r-f stages the impact generator provides an excellent means of locating the dead stage in short order, and then the hardest part of the battle is over. The signal injection method is used, which is simply to bring the exposed tip of the shielded test lead close to the tube cap on the successive tuned stages beginning with the last i-f and working towards the first stage. The attenuator is adjusted to suit the conditions and it should be possible to decrease the generator output as more stages come into play. If a stage shows no gain or no signal, it is evident that the trouble has been localized. No generator tuning is involved and no additional consideration need be given to r-f or i-f stages. If the fading be of short duration, the impact generator permits a quick search by the injection method and, due to the fact that no physical contact is made with the chassis, the likelihood of "healing" due to a static surge is completely eliminated. The method is also a useful expedient in locating dead or weak stages affected by less fickle conditions.

PADDING CONDENSER ADJUSTMENTS

The common procedure in the adjustment of padding condensers has always been a little awkward and uncertain since it involved the trial by error method of juggling two adjustments—rocking the rotor and manipulation of the padding condenser screw. In all cases, the object has been to find the oscillator frequency which beats with the resonant frequency of the first circuits at a rate equal to the i-f peak. The fact that the impact generator will excite the first circuits into natural oscillation simplifies the matter greatly since it is then only necessary to adjust the padding condenser for maximum response. If the padding condenser be of the fixed type, a new one can be selected by using a calibrated variable condenser in substitution and noting the capacity required to obtain maximum response. If no more than an assortment of fixed condensers is at hand, they can be tried separately or in combination to find the correct value.

FINDING BEST I-F PEAK

It frequently happens that an i-f dif-

fering from the manufacturer's specification will improve the performance of the set. This is especially so with sets having corrected or shaped plates for the oscillator section of the tuning gang. These sets have no padding condenser and the proper performance of the beat oscillator is dependent on the original design and its permanence. The beat frequency may not be correct, but since it cannot be changed it must be offset by shifting the i-f transformer tuning to a new beat frequency. Using the impact generator, this can be accomplished in a straightforward manner by simply adjusting the i-f tuners for maximum output. For this adjust-

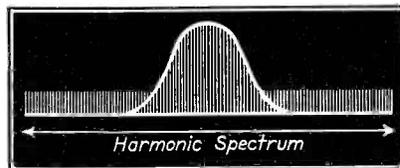


Fig. 5. Resonance response of a tuned circuit.

ment the generator is connected to the Ant and Gnd post with the tuning set at the low-frequency end of the band.

COMPROMISE ADJUSTMENTS

Very frequently, from poor design or ageing, it becomes impossible to achieve perfect tuning and a large part of the tuning range cannot be brought into line without sacrifice elsewhere. Consequently, it becomes necessary to select some compromise adjustment which will give the best possible performance under the circumstances. In

this work the impact generator permits a fairly rapid trial-by-error method of juggling the tuning elements for the best sensitivity curve. Though no specific procedure for accomplishing this can be laid down, the principal aim is to try the various i-f and r-f adjustments noting, the while, those adjustments which tend toward raising the general sensitivity level without adversely affecting any other part of the band. At each step of the work, the tuning dial of the receiver is swept across the range to observe the affect of the adjustment. The fact that no generator tuning is involved greatly facilitates the work.

In Fig. 6 an attempt has been made to sketch an illustrative analogy which may help in visualizing the mechanics of tuning. In this sketch, the impact generator might be supplanted by a broad light beam a part of which passes through the selector hole in blade 1. With the proper line-up of all holes and the reflector, the light will emerge full strength from the last hole. If the cams in the sketch are properly adjusted, the selected light beams will pass through unimpeded at each blade. In many respects this parallels the requisits of a properly tuned receiver in which the light acceptance hole is replaced by the frequency acceptance circuit.

A further study of the sketch shows that in most receivers the low-frequency end of the r-f stages are without means of adjusting resonance lineup. When the oscillator is also without adjustment at this end of the band, i.e. no padding condenser, it may happen that the frequency difference does not correspond to the setting of the i-f amplifier. Eliminating any serious fault, this can best be taken care of by shifting the i-f tuning to a new frequency giving maximum response. This done, the dial scales reading may be corrected for the low-frequency end by slipping it to read correctly while tuned to a known station. Alignment of the high-frequency trimmers can practically always be ac-

(Continued on page 440)

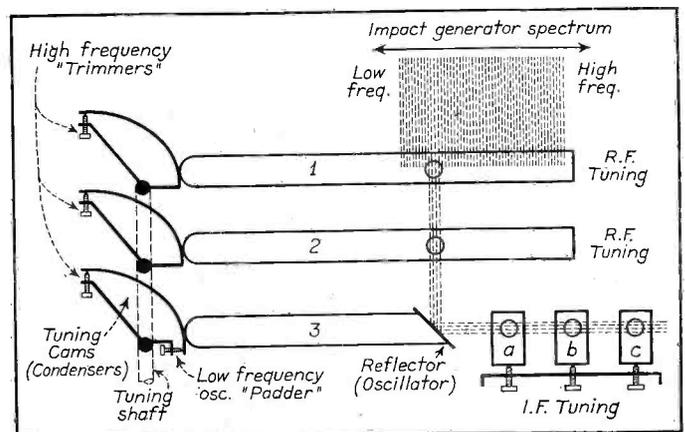


Fig. 6. Mechanical analogy of the impact generator.

AUTOMATIC VOLUME CONTROL*

AUTOMATIC volume control, normally identified as avc, has become an integral part of practically all present-day commercial radio receivers. It is true that a few t-r-f receivers, employing possibly three or four tubes in all, do not incorporate such control systems, but on the whole it is safe to say that every commercial superheterodyne is equipped with avc.

NEED FOR AVC

When we stop to consider the conditions of signal input which are encountered in practice, and the consequent effects—it is not difficult to see why avc is essential. There are a number of factors which contribute to the presence of an extremely wide range of signal intensities at the antenna systems of any one radio receiving installation; this range may be as great as a million to one. As to the reasons for this wide range—we find first the fact that the power rating of different transmitting stations varies widely. Some stations may employ a power output as low as 100 w, whereas others may be 5,000 w, 50 kw and even 500 kw. Then again the variation in the distance between any one receiver and the various transmitting stations which are within its range, cannot help but result in reception of signals which may be as weak as 2 or 3 microvolts or as strong as a volt—such as exists across an antenna system located in close proximity to a very powerful broadcast station. The phenomenon of fading due to a change in the transmitting medium located between the transmitter and the receiver, contributes a received signal of fluctuating strength. All in all, these various influences are very undesirable and up to the time when automatic control systems were introduced, represented some of the objectionable characteristics of everyday radio reception.

Supplementary to signal strength fluctuation is the introduction of distortion as the consequence of overloading due to excessively strong signals or the attempts to reduce manually these signals to the required levels.

The desirability of some automatic control system which would eliminate or minimize these difficulties and which would keep the output of the receiver constant in spite of this tremendous variation of signal strength was extremely obvious. The result was the development of avc.

In his "Hour-a-Day" series on avc John Rider discusses numerous avc systems, describing the operation of each.

AVC AS AUTOMATIC CONTROL OF SENSITIVITY

As to sensitivity, each and every receiver is very definitely limited, which means that while avc. may be a part of the receiver system, it does not increase the sensitivity of the receiver over and above that which would exist if the receiver were not equipped with avc. It is a well-known fact that a prescribed input signal is required in order that a certain output signal be available from a receiver. This condition holds true with or without avc. If, during a fade, the received signal falls below the required minimum, no output signal will be heard. This is quite natural, because the maximum sensitivity which can be built up in a receiver is definitely limited and if the signal input falls below the required minimum, as established by the maximum sensitivity of the receiver, then there is not sufficient signal strength to actuate the various tubes.

The action of avc eliminates what has been often identified as *blasting when tuning*, which means that it is possible to tune a receiver equipped with avc over a tuning band and to shift from a weak to a strong station without being annoyed with a sudden blast of sound when passing over the strong stations. While it is true that the manual audio volume control can be used to minimize such blasting in a radio receiver, it is a customary thing to maintain this control at a reasonably high-level setting in order to be able to tune in a weak station properly, or at least to recognize the presence of a weak station. If the manual audio volume control is maintained at a low-level setting in order to prevent the excessively loud bursts of sound when passing over strong stations, then it is possible to pass right over or miss the desired weak station.

Another excellent and beneficial effect of avc is the *reduction of distortion*. In days gone by some receivers not equipped with avc and which employed a sensitivity control located in the r-f portion of the receiver, distorted signals badly as the result of overloading and as the consequence of the effect produced when the sensitivity control was so adjusted to reduce a strong input signal to a suitable level as it passed through the receiver. While

it is true that this was not really the fault of the sensitivity control, but rather a limitation imposed by the design of the tubes then in use, the disadvantage of a variable control which required continual manipulation when tuning, still existed.

In order to comprehend the function of avc properly it is necessary to divorce the avc system from the manual volume control located in the audio system. Of course, the volume level of the receiver output is indirectly controlled, but this is not the essential point. The important thing to recognize is that the sensitivity of the receiver up to the second detector in a superheterodyne receiver, is automatically varied so as to insure constant output from the second detector. Expressed in another manner, we can say that the function of avc is to insure constant input to the a-f amplifiers, irrespective of the variation in intensity of the received signal across the antenna system of the receiver. The last named condition should be understood as to be within reasonable limits.

The development of avc systems has progressed over a period of time and, as a result, a number of different types of systems are in use. It is basically true that all of these systems are alike—but from the practical angle, some systems are simple,—some more complex, and still others very elaborately interlocked with the different parts of a radio receiving system.

VARIOUS TYPES OF AVC SYSTEMS

To what extent do the various types of avc systems now in use provide a constant output signal from the second detector tube—an output signal which is independent of the strength, intensity or level of the received signal? . . . In order that we have a basis of comparison, it might be well to show the relation between the input signal level and the output of the second detector tube

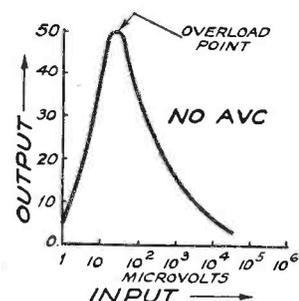


Fig. 1. Input-output relationship of receiver without avc.

*Much of the material for this article was gathered from John Rider's book on avc.

in a superheterodyne receiver not equipped with any form of avc. Such a relation is illustrated in Fig. 1. If you examine this curve closely, you will note certain very significant details. First is the fact that a continual increase in input does not necessarily result in a continual increase in output. This is indicated by the fact that the curve representing output does not continue rising. Instead it reaches a certain maximum and then starts to decrease. This means that every receiver not equipped with avc is very definitely limited in the output which it can supply (for a given setting of the manual gain control). Input signals greater than that required to produce this maximum do not result in greater output. . . . As a matter of fact, as is evident in Fig. 1, they result in weaker output, and, in addition, produce distortion. . . . This is the second important detail. The reason why such receivers cannot be operated with input signals greater than a certain level is that if the input signal is greater than the value permitted by design—the tubes in the r-f and i-f amplifiers begin to draw grid current and load or damp the tuned circuits. This has the twofold effect of reducing the amplification and introducing distortion.

SIMPLE AVC

How is this output-input characteristic modified in the case of a receiver which incorporates a simple avc system? At the present time it is not necessary to describe this system. Let it suffice if we say that the simplest possible avc system is employed. The output signal for various values of input for such a receiver is illustrated in Fig. 2. Certain significant details are evident in this illustration, which you should compare with Fig. 1. Note that in Fig. 2 the output for comparable values of input signals is substantially less than in the case of the receiver which does not incorporate any avc system. In other words, the output from the receiver with simple avc for small values of input signal is substantially less than in the case of the receiver without any avc. As the input signal is increased, there is a further marked difference in the output characteristic. Instead of increasing at a uniform rate until the overload point

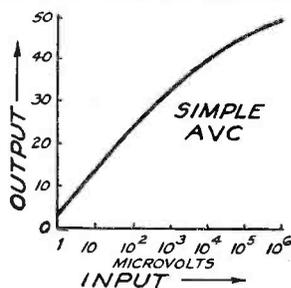


Fig. 2. Input-output relationship of receiver with avc.

is reached, the output climbs slowly and then gradually tapers off.

Figs. 1 and 2 should not be construed as definitely signifying that all receivers which are equipped with avc possess less sensitivity than receivers which do not employ avc. This is a matter of design. As a matter of fact, the modern receivers equipped with avc are more sensitive than the older receivers which were not so equipped.

Referring again to Figs. 1 and 2, it is significant to note that in Fig. 2 there is an absence of an overload point. Whereas the receiver without avc, shown in Fig. 1, overloads considerably with an input signal of 100 microvolts, the receiver equipped with simple avc does not overload when the input signal is as much as 1 volt. An idea of the uniformity of output, which can be obtained with a simple type of avc, can be seen from the fact that a change in input signal from 10 microvolts to 1 volt changes the output of a receiver from 10 units to 50 units. In other words, a change of 100,000 to 1 in the input signal voltage is effective in changing the output of the receiver in the ratio of only 5 to 1.

DELAYED AVC

A close examination of Figs. 1 and 2 shows that a receiver which is equipped with simple avc, has a lower sensitivity for very small input signals than one which does not have avc. The reason for this condition is that the avc acts to cut down the sensitivity of the receiver as soon as a signal is received, and this happens no matter how weak the incoming signal may be. This is a great disadvantage, because it is with weak signals that the maximum sensitivity of the set is desired. From a practical viewpoint, this would mean that weak signals would be difficult to receive or, at least, hear, because during the time when maximum sensitivity is needed, the presence of the avc lowers the sensitivity. Various remedies for this disadvantage are used in present day avc systems. These are discussed in Rider's book on avc.

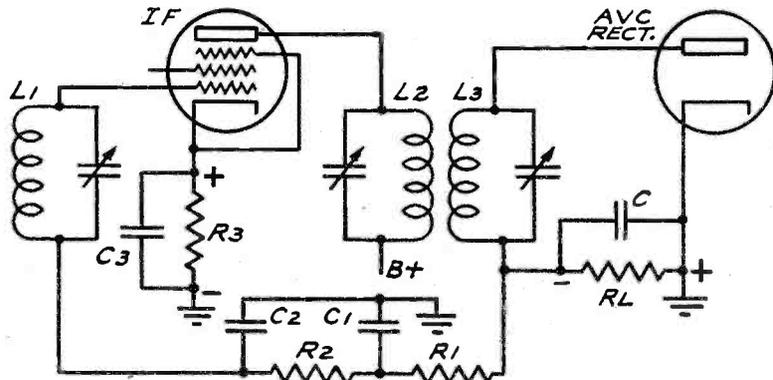


Fig. 3. Typical avc circuit.

THE BASIC CONTROL CIRCUIT

The function of the control voltage is to vary the gain of the r-f and i-f amplifier tubes in accordance with the strength of the signal impressed on the antenna. By distributing this voltage to the control grids of the several controlled tubes, the desired degree of control over the amplification in the r-f and i-f systems is obtained.

A typical simple circuit illustrating the coordination of all of the basic elements, which have been discussed so far in the preceding pages, is shown in Fig. 3. This circuit contains an i-f tube, which is controlled by the avc voltage, the avc rectifier, and the resistance-capacity filter. This is the simplest possible illustration and is by no means offered as an example of what would represent a complete circuit. However, it does illustrate the relation between the source of control voltage, the filter network and the tube being controlled. . . . What happens in such a circuit?

If we examine this circuit, we find certain significant details present. To start with, the i-f signal is transferred from the plate circuit of the i-f tube to the input circuit of the avc rectifier. Rectification takes place and the pulsating voltage is developed across the load resistor, R_L . The input to the filter circuit is connected to the most negative point along the control voltage supply resistor, which means that the control grid of the i-f tube is joined to this point. The filter circuit, consisting of R_1 , R_2 , C_1 and C_2 , removes the alternating component of the pulsating voltage, so that a steady voltage is available for bias.

Speaking about the bias for the i-f tube, we note that the cathode of the i-f tube contains its own biasing resistor. . . . But why should this biasing resistor be in the circuit if we can secure an automatic bias from the avc rectifier?

The purpose of the i-f cathode bias resistor is to supply a fixed minimum bias, which sets the operating point of that amplifier stage for its maximum sensitivity position. If we depended

solely upon the avc circuit to supply the entire bias, the i-f tube would be operating without bias during those moments when the receiver was being tuned between stations and no signal was passing through the receiver so as to develop the automatic bias. By providing a fixed minimum bias, safe operation of the i-f tube is at all times assured. Such an arrangement is not limited to the i-f amplifier only—but can also be used in r-f systems.

Now the polarity of the fixed minimum bias applied to the i-f tube and the control bias developed by the avc rectifier when a signal is passing through the receiver, is such that these two voltages are effectively in series—so that the avc bias is additive to the fixed minimum bias.

Let us now analyze in a qualitative way the exact manner in which this simplified circuit functions. We start off with the assumption that a weak signal is being picked up by the antenna. Under this condition the signal

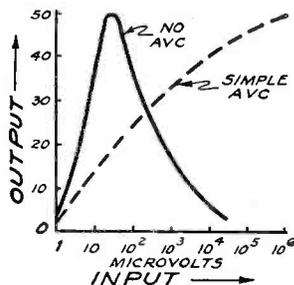


Fig. 4. Input-output relationship of same receiver with and without avc.

voltage is passed on to the i-f tube and across the secondary winding of the i-f transformer, which feeds the avc rectifier, there will be a moderate signal and consequently the control voltage produced across R_p will likewise be moderate in value. This in turn means that the control bias on the i-f amplifier will be of moderate value and the sensitivity of the receiver will be moderately great. As the input signal to the receiver is increased, the magnitude of the control voltage likewise increases in the same ratio. The effect of this increasing control voltage is to level out the response, because the greater the control voltage, the greater the bias applied to the i-f tube, and the less its mutual conductance, which can be interpreted in terms of the gain or amplification of the system. This action tends to make the output uniform regardless of the strength of the signal voltage fed to the input of the receiver. The output characteristic which such a system would have if it did not incorporate avc as against the output characteristic with avc is shown in Fig. 4. Note that the output characteristic, even with avc, is far from ideal in that the output is not the same for all values of input, but on the

contrary does increase to a certain extent with increasing values of signal input. While it is true that the performance with avc is not ideal, it is still far superior to the action when the avc system is absent. . . .

TIME DELAY CONSIDERATIONS

The function of an avc system is to provide substantially constant output irrespective of changes in the signal input. As far as changes of received signal intensity are concerned, they may be either rapid or slow. Whatever the condition, the fact remains that the control voltage must be capable of following the fluctuations in intensity of the applied signal. In other words, the control voltage must be able to increase or decrease as rapidly as the occasion demands.

The filter network displays a great deal of influence upon the ability of the

control voltage to follow rapid changes in the input signal. However, before we can really understand the nature of the action which takes place in the filter network consisting of R_1 , C_1 , R_2 and C_2 in Fig. 3, we must investigate some of the fundamental facts relating to the charge and discharge of a condenser through a resistor. As a rule we think of circuits in such a way that if the voltage is changed at one point in a circuit,—then the voltage instantaneously changes in every other part of the circuit in conformity with the initial change. In general this is quite true, but where the circuit involves large values of resistance and capacity, there is a definite appreciable time lag between the instant that the initial voltage change is made at one point in the circuit and the instant at which the corresponding effect is felt at other points in the circuit.

PENTODE USED AS DIODE AND HIGH-MU TRIODE

(See Front Cover)

THE circuit given on the front cover shows a 6J7G used as a combination second-detector diode with avc and as a high- μ triode first-audio stage. The particular values indicated on the cover diagram are those used in the 1937 Crosley model 526.

THE CIRCUIT

The signal from the i-f tube is fed through the doubly-tuned second i-f transformer the secondary of which feeds the plate of the 6J7G. The return leg of secondary is connected, through a 400,000-ohm (diode) load resistor, to the suppressor grid of the 6J7G. The suppressor is connected to the cathode which is suitably biased, for the tubes action as the first audio stage, by proper connection to the voltage divider (+4 volts). The secondary return leg of the second i-f transformer is also connected, through the 1.5-meg, 0.05-mfd resistor-condenser r-f filter to the grid returns of the r-f and i-f stages. The a-f signal developed at the second i-f return leg is fed through the 0.006-mfd coupling condenser and the 100,000-ohm filter resistor to the volume control. Any desired portion of this a-f signal is fed from the arm of this section of the control to the grid of the 6J7G. The screen of the 6J7G with a 300,000-ohm load resistor is coupled through the 0.03-mfd condenser to the second section of the a-f volume control. Any desired portion of the signal across this control is fed to the grid of the output stage, a 6N6

for the circuit shown. The two volume controls work from the same shaft.

FUNCTIONING OF THE TUBE

The plate and suppressor of the 6J7G act as a diode and rectify the r-f signal delivered by the i-f transformer secondary. The rectified (d-c) voltage is developed across the 400,000-ohm load resistor; it is, however, still modulated by the a-f signal present on the original station carrier. This varying d-c across the load resistor, none the less, has a definite negative value with respect to the cathode at the end away from the cathode. This negative voltage is used for automatic volume control. The portion of the tube in which the plate and suppressor are located is sufficiently hot to enable rectification of the small amount of current required for detection and avc action.

The variations or a-f signals developed across the 400,000-ohm load resistor are passed on to the control grid of the 6J7G by means of the 0.006-mfd coupling condenser, the 100,000-ohm r-f filter and the first a-f volume control. This section of the dual volume control is used as the 6J7G grid load resistor. The screen of the 6J7G is used as the high- μ triode plate and collects the (amplified) signals. The screen receives full plate voltage through its 300,000-ohm load resistor. The signal is collected by the screen because it has the highest (+) potential and the suppressor and plate which surround it are at a much lower potential.

**True facts
about the radio
replacement field
*are yours for
the asking***

- How many full time service men are there today?
- How many part time service men are there today?
- How many service men own their own business?
- How many service men are also dealers?
- How many service men own their own tube checkers?
- How many service men own their own set analyzers?
- How many service men own their own voltmeter-ohmmeters?
- How many service men own their own RF-IF oscillators?
- How many service men own their own cathode ray oscillographs?
- How many service men own their own automobiles?
- How many service men carry a stock of radio receivers?
- How many service men carry a stock of parts?
- How many service men carry a stock of tubes?
- Whom do service men buy from?
- What type of advertising influences a service man?
- In dollars and cents, what is the radio replacement market?

The Answers to all these questions . . . and many others . . . are now available to advertisers and advertising agencies . . .

The SERVICE SURVEY is accurate and timely. You cannot afford to be without it.

Communicate with

SERVICE

**19 EAST 47th STREET
NEW YORK N. Y.**

"The Magazine for Professional Service Men and Parts Jobbers."

General Data . . .

RCA 7T, 7K, 8T and 8K

The model 7T is a 7-tube, table-type superheterodyne with an 8-inch dynamic speaker. The 7K is of the console type and has a 12-inch speaker. The 8T and 8K are similar to the models 7T and 7K, respectively, except for the addition of a 6E5 and different cabinet designs.

THE CIRCUIT

Design features incorporated in these receivers include: built-in doublet antenna coupler; improved plunger-type air-dielectric adjustable trimmer condensers in the antenna and oscillator coil circuits; high-efficiency first-detector-converter with separate oscillator; magnetite core adjusted i-f transformers; low-frequency oscillator compensation; wave trap; aural compensated volume control with music-voice switch; avc; phonograph terminal board, and a dust-proof speaker.

The tuning range is continuous through the standard-broadcast, medium-wave and short-wave bands. This range includes the 49, 31, 19, 16 and 13 meter broadcasts in addition to the channels assigned for police, amateur and aviation communication.

The 6F6 output tube provides an undistorted power output of 2 watts. The

total a-c power consumption is (approximately) 80 watts.

ALIGNMENT PROCEDURE

Connect the output indicator to the voice coil or to the primary of the output transformer (see Fig. 4). Advance the receiver volume control to its maximum position allowing it to remain in this position throughout the alignment procedure. For each adjusting operation regulate the test oscillator output so that the signal level is as low as possible and still observable at the receiver output. Use of a small signal will obviate broadness of tuning that would otherwise result from the use of a stronger one.

I-F ALIGNMENT

(a) Connect the output of the test oscillator to the grid cap of the 6L7 (with grid lead in place) through a 0.001-mfd capacitor and to receiver chassis. Tune the test oscillator to 460 kc.

(b) Adjust the two magnetite core screws of the second i-f transformer (one on top and one on bottom) to produce maximum (peak) output.

(c) The two first i-f transformer magnetite core screws (one on top and one on bottom) should be adjusted to

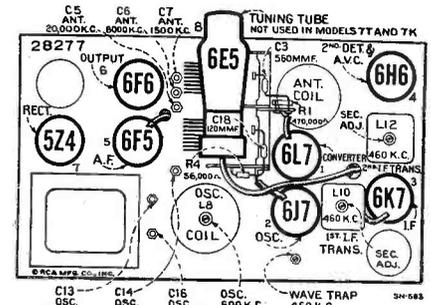


Fig. 2. Tube and trimmer locations.

produce maximum (peak) output. It is advisable to repeat the adjustment of all i-f magnetite core screws to assure that the interaction between them has not disturbed the original adjustments.

R-F ALIGNMENT

Calibrate the pointer of the tuning dial by adjusting it to the extreme low-frequency end of dial scale (beyond 55 on dial) with the plates of the gang tuning condenser in full mesh. Alignment must be made in sequence of short-wave band, medium-wave band, wave-trap and standard-broadcast band.

Short-wave band

(d) Connect the output of the test oscillator to the antenna terminal "A1" through a 300-ohm resistor, leaving the ground of the oscillator connected to the receiver chassis.

(e) Turn range selector to its short-wave position. Set receiver dial pointer to 20,000 kc. Adjust test oscillator to 20,000 kc. Set oscillator air trimmer

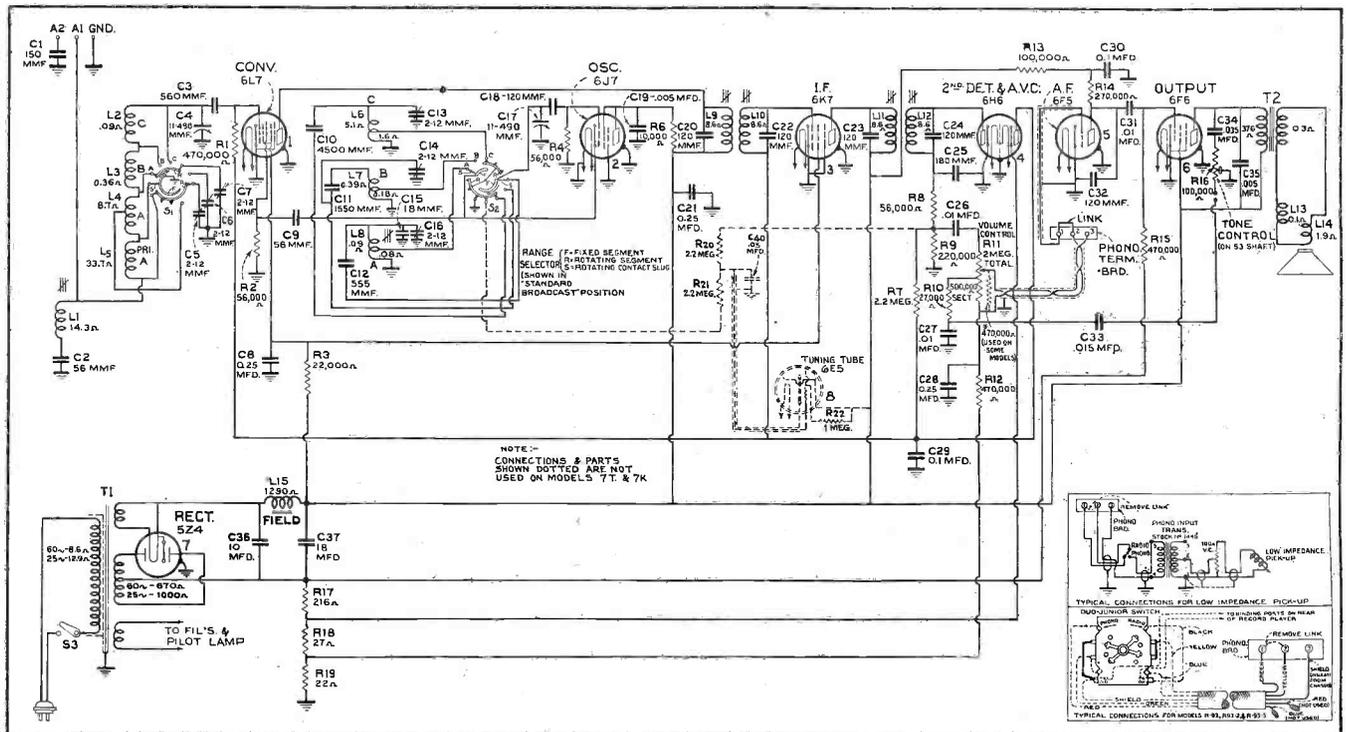


Fig. 1. RCA 7T, 7K, 8T and 8K circuit diagram.

Boy it's a Honey

**THE NEW
"BLUE RIBBON"
RADIO CATALOG**
And it's Free!



ATTENTION, SERVICERS

ATTENTION SERVICERS!

It will be four long years before another Presidential campaign comes along. From now until Election Day, you have a swell chance to improve your financial standing by renting out portable P.A. systems to the local political organizations—and often SELLING an installation. WHOLESAL RADIO SERVICE CO., INC., will show you how—will help you with technical advice—and will guarantee to furnish you with equipment which will STAY sold!

Shop at Home with the Wholesale Blue Ribbon Catalog! Special New York-Chicago-Atlanta Inter-communicating teletype system makes possible prompt, efficient service, for your most exacting requirements.

**EVERYTHING
YOU NEED IN
RADIO—FROM
THIS ONE SOURCE**



Let us make you a present of this mastodonic catalog—without any obligation on your part—clip the coupon, paste it on a post card and mail it—TODAY!

WHOLESAL RADIO SERVICE CO., INC.

CHICAGO, ILL.
901 W. JACKSON BLVD.

NEW YORK, N.Y.
100 SIXTH AVENUE

ATLANTA, GA.
430 W. PEACHTREE ST. N.W.

BRONX, N.Y.
542 E. FORDHAM RD.

NEWARK, N.J.
219 CENTRAL AVE.

WHOLESAL RADIO SERVICE CO., Inc.
100 Sixth Avenue, New York, N. Y.

Rush FREE BLUE RIBBON CATALOG NO. 65-J5.


NAME

ADDRESS

CITY STATE

Watch

FOR NEW 1937
SUPREME
TESTING EQUIPMENT!

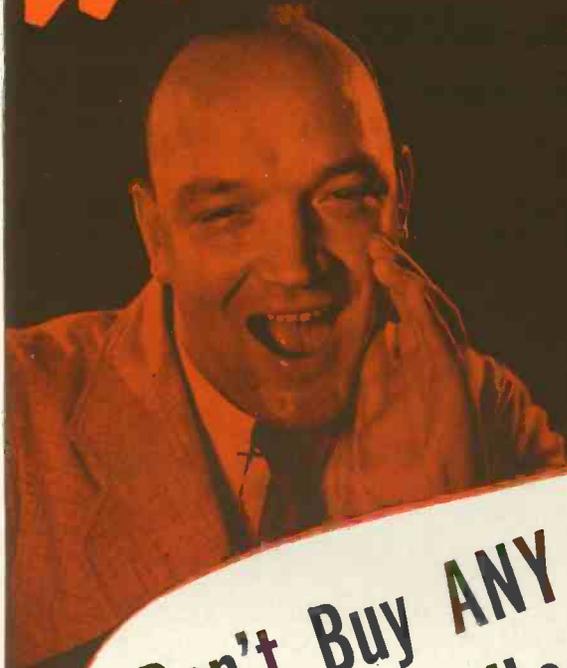

“Don't Buy ANY Radio Test Equipment
Until You Have Seen the NEW
1937 SUPREME LINE.”

Your Parts Jobber

NEW INSTRUMENTS

NEW FEATURES

A NEW IDEA IN METERS

You can buy any SUPREME
Instrument on S.I.C. easy terms!

SUPREME INSTRUMENTS CORP. GREENWOOD
MISS., U. S. A.

EXPORT DEPT., ASSOCIATED EXPORTERS CO., 145 W. 45th STREET, NEW YORK, N. Y., CABLE ADDRESS: LOPREN, N. Y.

SEE THE NEW SUPREME MODELS ON DISPLAY AT THE IRSM SHOW IN NEW YORK CITY!



*Most Complete Transformer
Line in the World*

QUALITY · RELIABILITY

UTC Leads the Field Again . . .

ALL PRICES ARE NET TO SERVICEMEN OPEN CHANNEL FRAME AUDIO TRANSFORMERS

Horizontal Mounting Centers 2 13/16" — L 3 5/16"
W 1 1/2" H 2"

S-31	1 plate to 1 grid 3:1 ratio, Vertical mount.....	\$1.65
U-31	1 plate to 1 grid 3:1 ratio.....	1.05
S-32	1 plate to 2 grids 2:1 ratio, Vertical mount.....	1.11
U-32	1 plate to 2 grids 2:1 ratio.....	1.11
U-32X	1 plate to 2 grids 2:1 ratio split secondary.....	1.14
U-33	2 plates to 2 grids 1.75:1 ratio.....	1.20
U-47	Single power pentode to single voice coil.....	.90
U-247	Push pull power pentodes to single voice coil.....	.96
U-45	Single power triode to single voice coil.....	.90
U-245	Push pull power triodes to single voice coil.....	.96

UNCASED UTC MIGHTY MITE AUDIO TRANSFORMERS

For Transceivers. For compact head amplifiers. For Pee Wee and aeroplane receivers.

Horizontal Mounting Centers 2 3/8" — L 2 7/8" W 1 3/8"
H 1 11/16"

S-41	Interstage audio 4:1 ratio, Vertical mount.....	\$.90
U-41	Interstage audio 4:1 ratio.....	.90
S-51	Single plate to 2 grids 2 1/2:1 ratio, Vertical mount.....	.93
U-51	Single plate to 2 grids 2 1/2:1 ratio.....	.97
UPM	Single pentode 18, 20, 33, 41, 32, 2A5 plate to 4000 and 2000 ohms.....	1.05
UTM	Single triode 71, 45, 59 plate to 4000 and 2000 ohms.....	1.05
UMG	Single or double button mike to 1 grid.....	.96
UTG	Single plate and carbon mike to single grid.....	.99
UHO	Single 56, 27, or 864 plate to 500 and 200 ohms.....	1.20
UPPM	Push pull triodes 71, 45, 59 to 4000 and 2000 ohms.....	1.05
UTTM	Push pull pentodes 18, 20, 33, 41, 32, 42, 2A5, 47 to 4000 and 2000 ohms.....	1.05
U30B	Driver 30 plate to Class B 19, 49, 79, 89 grids.....	1.05
U19B	Class B 19, 49, 79 or 89 plates to 5000 or 3500 ohms.....	1.05

PEE WEE DYNAMIC SPEAKER OUTPUTS

Horizontal Mounting Centers 2 13/16" — L 3 5/16"
W 1 1/2" H 2"

MA-1	Single power pentode to voice coil.....	\$.75
MA-2	Push pull power pentodes to voice coil.....	.81
MA-3	Single power triode to voice coil.....	.75
MA-4	Push pull power triodes to voice coil.....	.81

UTC ALL-PURPOSE REPLACEMENT OUTPUT TRANSFORMERS

Due to their ingenious mounting arrangement, these transformers will easily fit Rola, Wright DeCoster, Jensen, Utah, Magnovox, and other small dynamic speakers.

These units are compact. The mounting centers are from 3/4" to 2 3/8"; the height 1 5/8". A fine grade of silicon core material is used and each unit has a high degree of efficiency. A tapped secondary winding will match voice coils from two to eight ohms. A top lug terminal bracket is supplied so that field coil leads may be soldered directly to each unit.

US-47	Single power pentode like 18, 20, 33, 41, 32, 57, 2A5 to single voice coil.....	\$.90
UPP-47	Push pull power pentodes like 18, 20, 33, 41, 32, 47, 2A5 to single voice coil.....	.90
US-45	Single power triode like 71, 45, or 59 to single voice coil.....	.90
UPPO	Push pull power triodes like 71, 45, or 59 to single voice coil.....	.90
UPP-45	Push pull 48's to single voice coil.....	.90
UPP-48	Compact type Universal output for single and push pull triodes or pentodes to any voice coil.....	.90

NEW SILCHROME



REPLACEMENT AUDIO, FILAMENT and FILTER COMPONENTS designed according to the best of modern standards. These units employ the finest high permeability silicon steel and the best insulating materials. The coils are fully vacuum impregnated and precision machine wound to assure long lasting service under the most adverse humidity conditions encountered.

The new UTC SILCHROME units have non-tarnishing chromium plated channel frames that completely enclose the core structures. New silver wrappers used on the coils complete the appearance of these distinctive units. While SILCHROME components represent the greatest forward step in replacement material of high quality, THERE IS NO INCREASE IN COST.

See these new SILCHROME units at your favorite distributor.

UNITED TRANSFORMER CORP.

72 SPRING STREET

NEW YORK, N. Y.

EXPORT DIVISION: 100 VARICK STREET NEW YORK, N. Y. CABLES: "ARLAB"

GENERAL DATA—continued

kc. Make any adjustments that are necessary to obtain satisfactory calibration.
Short wave band:

1. Turn the band-selector switch to the short-wave (clockwise) position.
2. Tune the receiver to 20 megacycles.

3. Supply a 20-megacycle signal from the signal generator to the antenna lead of the receiver through a 400-ohm carbon resistor (dummy antenna) connected in series with the signal generator lead.

4. Adjust the short-wave band oscillator trimmer condenser (Fig. 1) for maximum output with minimum input from the signal generator. Then adjust the short-wave band antenna and radio-frequency stage trimmers for maximum output at the same time rocking the tuning condenser back and forth across the signal to insure the peak of greatest intensity.

5. The 8-megacycle signal should be received near 8 megacycles on the dial. If this is not the case check the oscillator tube, switch connections, the fixed padding condenser and the coils. No adjustment is required at this point.

Warning:

The image signal should be received at approximately 19 megacycles on the dial. If not, the oscillator has been aligned to the image frequency and the oscillator trimmer condenser must be

backed out until the correct signal is received at 20 megacycles and the image at approximately 19 megacycles. If readjustment is found necessary the antenna and radio-frequency stage trimmers should be checked again.

G. E. E-61, E-62, E-68

Models E-61, E-62 and E-68 employ six metal envelope tubes in a superheterodyne circuit giving the selectivity and sensitivity inherent in this type circuit. Two-watts undistorted output is obtained through diode detection and two high-gain audio amplifier stages.

The frequency range of the broadcast band is from 540 to 1750 kc; of the short-wave band, from 2.2 to 7.0 mc. The approximate power consumption is 70 watts.

THE CIRCUIT

The signal from the antenna is applied to the control grid of the 6A8 tube through the r-f coil, the secondary of which is tuned to the incoming signal by the rear section of the main tuning condenser. In the 6A8 tube the incoming signal is combined with the local oscillator signal which is 465 kc higher in frequency. The local signal is generated by the oscillator elements of this tube, and the proper frequency difference is maintained throughout the

tuning range by the front section of the main tuning condenser in conjunction with the oscillator coil and padding capacitors.

The combination of the two signals produces the i-f of 465 kc. The i-f amplifier consists of a 6K7 tube and two i-f transformers, each with two tuned circuits. An i-f wave trap is provided across the antenna and ground terminals to eliminate interfering signals.

The output of the i-f amplifier is applied to one plate of the 6H6 diode rectifier, which is a combined detector, initial bias and avc tube. The direct-current component of the rectified signal, through one diode of the 6H6, produces a voltage drop across R-3. This voltage drop provides automatic bias for the converter and i-f amplifier tubes and so gives avc action. The other diode of the 6H6 provides an initial bias for the tubes on the avc circuit under conditions of little or no signal. This initial bias diode, under conditions of small signal, draws current which flows through resistors R-2 and R-3. The resulting voltage is the required minimum operating bias for the controlled tubes. Upon receiving signals above the level of the initial bias, the initial bias diode stops drawing current and the avc diode takes over the controlling bias.

The manual volume control, R-5, selects the amount of audio signal applied

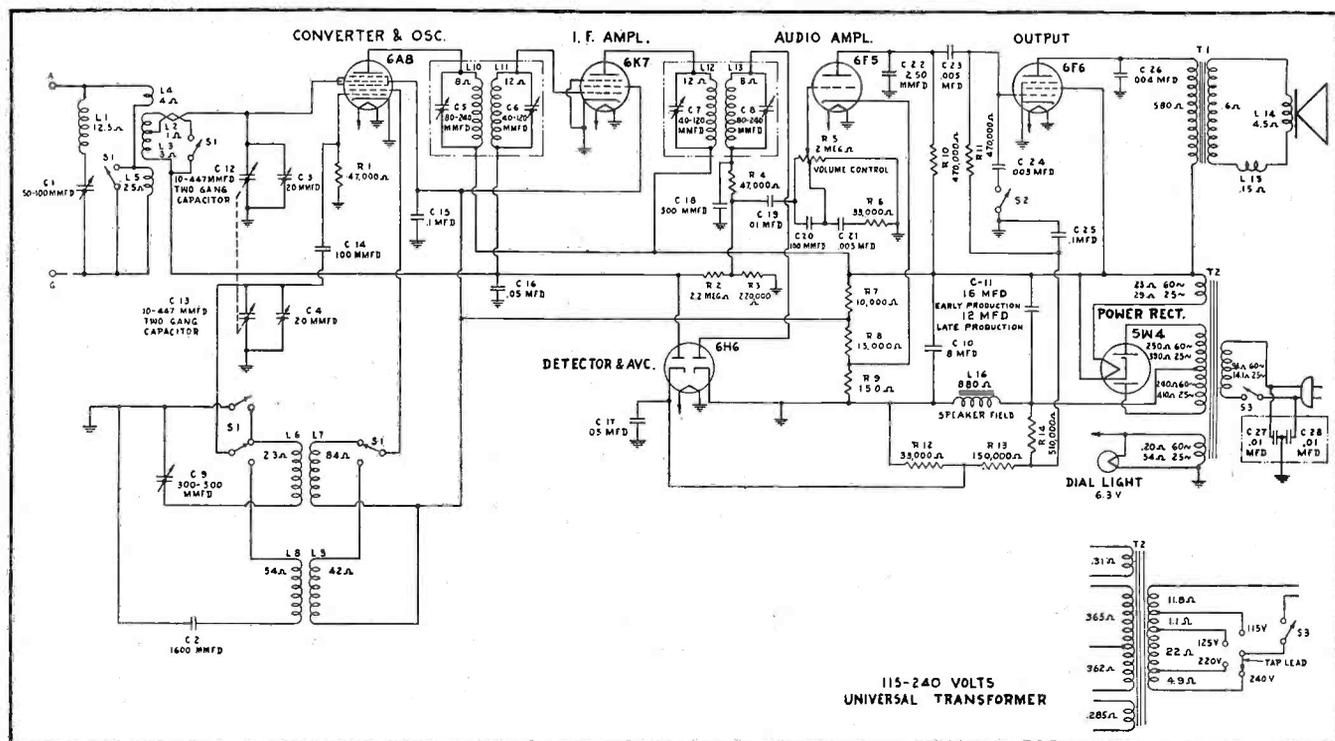


Fig. 1. G.E. E-61, E-62 and E-68 circuit diagram.

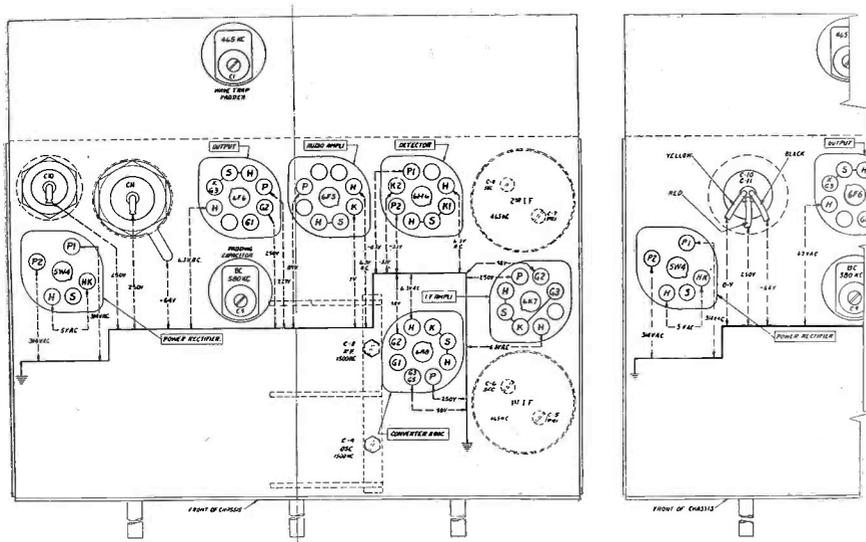


Fig. 2. Chassis views showing socket layout and trimmer locations.

to the grid of the 6F5 audio amplifier tube, and this regulates the output of the receiver. The output of the 6F5 tube is resistance coupled to the grid of the 6F6 power amplifier pentode. The plate circuit of the 6F6 is suitably matched to the loudspeaker by means of a step-down output transformer.

The tone control circuit consists of a 0.003-mfd capacitor, connected in series with a two-point grounding switch, S-2, in the grid circuit of the 6F6 power pentode. When it is desired to reduce the high-frequency output of the receiver, the switch, S-2, is turned to its counterclockwise grounding position.

Plate and grid voltages for all tubes are supplied by the power supply system employing a 5W4 full-wave rectifier tube which, together with a suitable network of resistors and capacitors, supplies the required voltages and filtering action.

ALIGNMENT PROCEDURE

The receiver should first be allowed to run for fifteen minutes in order to reach its approximately normal operating temperature. Before making any adjustments, it is wise to determine the correctness of the existing alignment.

Set the frequency band switch of the receiver to the broadcast position and turn the volume control to the extreme clockwise position. Tune the receiver to some point above 1500 kc so that no signal is heard, short-circuiting the antenna and ground terminals if necessary, and ground the chassis.

I-F ALIGNMENT

Remove the control grid clip from the 6A8 tube and connect the test oscillator

output between the chassis and the dome terminal of the 6A8 tube. The i-f amplifier is tuned to 465 kc; set the oscillator dial at this frequency. Make sure that a d-c path exists between the output terminals of the test oscillator; if an ohmmeter does not show continuity between the test oscillator terminals, connect a resistor of fairly high resistance between the 6A8 dome terminal and chassis to provide a d-c grid return path.

Connect the output meter across the cone coil of the speaker and adjust the test oscillator output control so that, with the volume control at maximum, a small indication is observed on the output indicator.

Adjust the secondary trimmer of the second i-f transformer until a peak output reading is obtained. Maintaining a small output indication, adjust next the primary trimmer of the second i-f transformer for maximum output. Continue this procedure, adjusting the secondary trimmer of the first i-f transformer, and lastly, the primary trimmer of the first i-f transformer. After completing this procedure, repeat it a second time for final alignment. The i-f alignment will then be complete.

During both i-f and r-f alignments, the test oscillator signal would be maintained at the lowest level that will give a good output indication, keeping the receiver volume control at maximum and adjusting the test oscillator output control to give the required indication.

WAVE TRAP ALIGNMENT

After completion of the i-f alignment, with the test oscillator still set on 465 kc, apply this frequency to the antenna

post of the receiver through a dummy antenna. This dummy antenna consists of a 400-ohm resistor in series with a 250-mmfd capacitor and should be connected in series between the test oscillator output and the receiver antenna post. With the 465-kc signal applied to the receiver antenna post, adjust the wave trap trimmer for minimum output indication.

R-F ALIGNMENT

The r-f and oscillator trimmers are aligned at 580 and 1500 kc. First of all, check the position of the dial pointer. To do this, rotate the gang condenser to the maximum capacity position, i. e., plates fully meshed. While in this position, align the pointer with the last black line on the scale by loosening the dial drum set screws and rotating the drum on the gang shaft. Make sure the antenna and ground terminals of the receiver are not short-circuited and connect to them the output of the test oscillator, preferably using the dummy antenna described between the test oscillator and the receiver antenna terminal. Connect the output indicator across the speaker cone coil.

Broadcast 540-1750 kc

Set the frequency band switch to the broadcast position. Tune the test oscillator to 1500 kc and set the dial pointer on the receiver to this frequency. Adjust the broadcast oscillator trimmer on the front section of the gang condenser for maximum output, keeping the receiver volume control at its extreme clockwise position and adjusting the test oscillator output to maintain a small reading on the output indicator. When optimum adjustment on the broadcast oscillator trimmer is obtained, adjust the broadcast r-f trimmer on the rear section of the gang for maximum output.


Now set the test oscillator at 580 kc and tune the receiver to that frequency. Slowly, rocking the tuning condenser back and forth through the signal, adjust the 580 kc padding capacitor for maximum output. When this has been done, return to 1500 kc on the receiver and test oscillator and recheck the alignment at that frequency for maximum output. The broadcast band should now be in alignment.

Short Wave 2.2—7.0 mc (2200-7000 kc)

No separate short wave trimmers are provided on this receiver. The correct adjustment of the broadcast band at 580 and 1500 kc automatically aligns the short-wave band.

Resistors

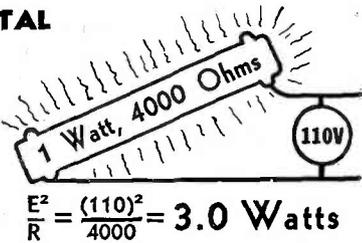**CONTINENTAL
Insulated
Carbon
Resistors
Withstand
300%
Overload**



Resistors are not supposed to be operated at a 300% overload, but it is a satisfaction to know that 300% overloads can be carried by dependable CONTINENTAL Carbon resistors. Standard types, list price: 1/4, 1/2-watt, 17 cents; 1-watt, 20 cents. Semi-precision insulated resistors are supplied only in 1-watt size within 5% of rated value for meter multipliers. List, 30 cents. Complete listing, including 3 and 5-watt sizes, in Bulletin 104-A.

Free Cabinet




Dial Color Code, Wattage Chart

Offered with the purchase of 35 standard insulated CONTINENTAL Carbon resistors—this convenient cabinet saves time in locating resistors and in calculating the correct size to use. The resistor bins are supplied with 35 selected values most frequently required.

- Code 135D, 1-watt, list price \$7.00
- Code 135G, 1/2-watt, list price 5.95

Filtercons

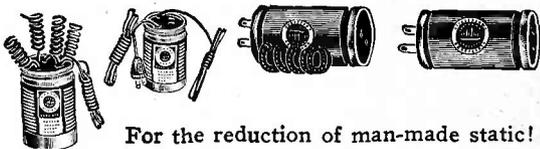

For the reduction of man-made static! CONTINENTAL Filtercons are designed in three major types—interference rejection, interference diverting, and noise suppression Filtercons. The application of Filtercon F1005DH in blocking line noise out of the house wiring eliminates much of the interference picked up by antenna lead-ins. Bulletin 104-A describes applications for Filtercons.



13912 Lorain Avenue Cleveland, Ohio
Toronto, Ontario

CONTINENTAL CARBON INC.

WHAT SINGLE P. A. SYSTEM

**Will Serve 98% of
Dealer Demands?**

FOR RENTALS


110 V. or 8 V.

FOR SALES

110 V. or 6 V.



SYSTEM MP-420

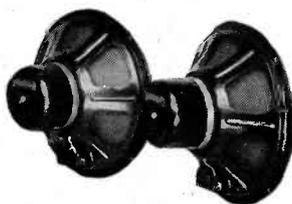

WEBSTER-CHICAGO

Operates on either 110 V. A.C. or 6 V. D.C. 20 watts output . . . amplifiers and turn table built in 1 unit . . . two 12" Permanent Magnet Speakers . . . Hand Type dual diaphragm crystal microphone.

The "ONE" sound system that the dealer should own. Just the system for rentals or for demonstration. Because of flexibility many consumers prefer this system.

System MP-420 can be used on either 110 V. A.C. or 6 V. D.C. by plugging in the right power pack. It is thus equivalent to two complete systems. The plug-in type power pack is an exclusive Webster-Chicago development (Pat. Pending).

All equipment, including tubes, furnished with system. Complete price surprisingly low. See this system at your nearest jobber. Write for more complete information.

Webster-Chicago are old established manufacturers of P. A. Systems Sound Equipment and Accessories of all kinds. A full line of carefully engineered merchandise, priced right. The Sound line that all dealers should handle.



**STRICT DEALER POLICY—
FULLY LICENSED
TIME PAYMENT PLAN**

WEBSTER-CHICAGO
Section S-5, 3826 West Lake St., Chicago, Ill.

Please send me more information on Model MP-420.

I am also interested in sound systems for Rentals . . . ; Portables . . . ; Fixed Systems . . . ; Low Power . . . ; High Power . . . ; Institutional Systems . . . ; Hotels . . . ; Schools . . . ; Inter-Office Communicating Systems . . . ; Factory Call Systems . . .

Name
St. Address
City State

Auto-Radio . . .

Crosley A-266

The Crosley model A-266 is a single unit auto-radio six-tube superheterodyne receiver. The power supply unit is built into a completely shielded compartment and is an integral part of the receiver chassis.

A circuit diagram is shown in Fig. 1 with the tubes used and with the various voltages encountered on the socket prongs lettered on the diagram. These readings were taken with a 1000-ohm-per-volt voltmeter with the receiver in operating condition and no signal input. The filament voltages were measured with a low range d-c voltmeter. Voltages taken in the field may vary 10 percent from those given.

ALIGNMENT PROCEDURE

All the circuits in this receiver are very accurately adjusted at the factory and normally should need no further adjustment. However, if it is definitely known that an adjustment is necessary the circuits can best be properly aligned

with the use of a modulated signal generator and an output meter.

Connect one terminal of the output meter to the plate and the other terminal

to the screen of the 42 output tube. Be sure the meter is protected from d-c by connecting a condenser (0.1 mfd or larger—not electrolytic) in series with one of the leads.

Note: The receiver chassis must be in its case and a speaker similar to one used with the receiver must be connected to the chassis before making any adjustments. It is also advisable to use a spare control unit for making adjust-

PARTS LIST (SEE FIG. 1)

Condensers		Resistors	
No.	Capacity	No.	Ohmage
11A	0.1 mfd 160 v	23	300,000 ohm ¼ w
11B	0.1 mfd 160 v	24	750 ohm ½ w
11C	0.05 mfd 160 v	25	60,000 ohm ¼ w
11D	0.05 mfd 160 v	26	20,000 ohm ¼ w
12	0.02 mfd 200 v	27	1 meg ¼ w
13	0.00025 mfd moulded	28	100 ohm ½ w
14	0.00025 mfd moulded	29	100 ohm ½ w
15A	0.5 mfd 160 v	30	55,000 ohm 1 w
15B	0.5 mfd 160 v	31	20,000 ohm ¼ w
16	0.0005 mfd moulded	32	450 ohm ½ w
17	0.1 mfd 200 v	33	350 ohm ½ w
18	0.0001 mfd moulded	34	750,000 ohm ¼ w
19	0.02 mfd 200 v	35	150,000 ohm ¼ w
20	0.006 mfd 400 v	36	500,000 ohm ¼ w
21	0.005 mfd 1000 v	37	300,000 ohm ¼ w
22A	6 mfd 350 v	41	300,000 ohm volume control
22B	6 mfd 350 v		
43	M.N. plate riveted to chassis		
51	0.1 mfd 200 v		


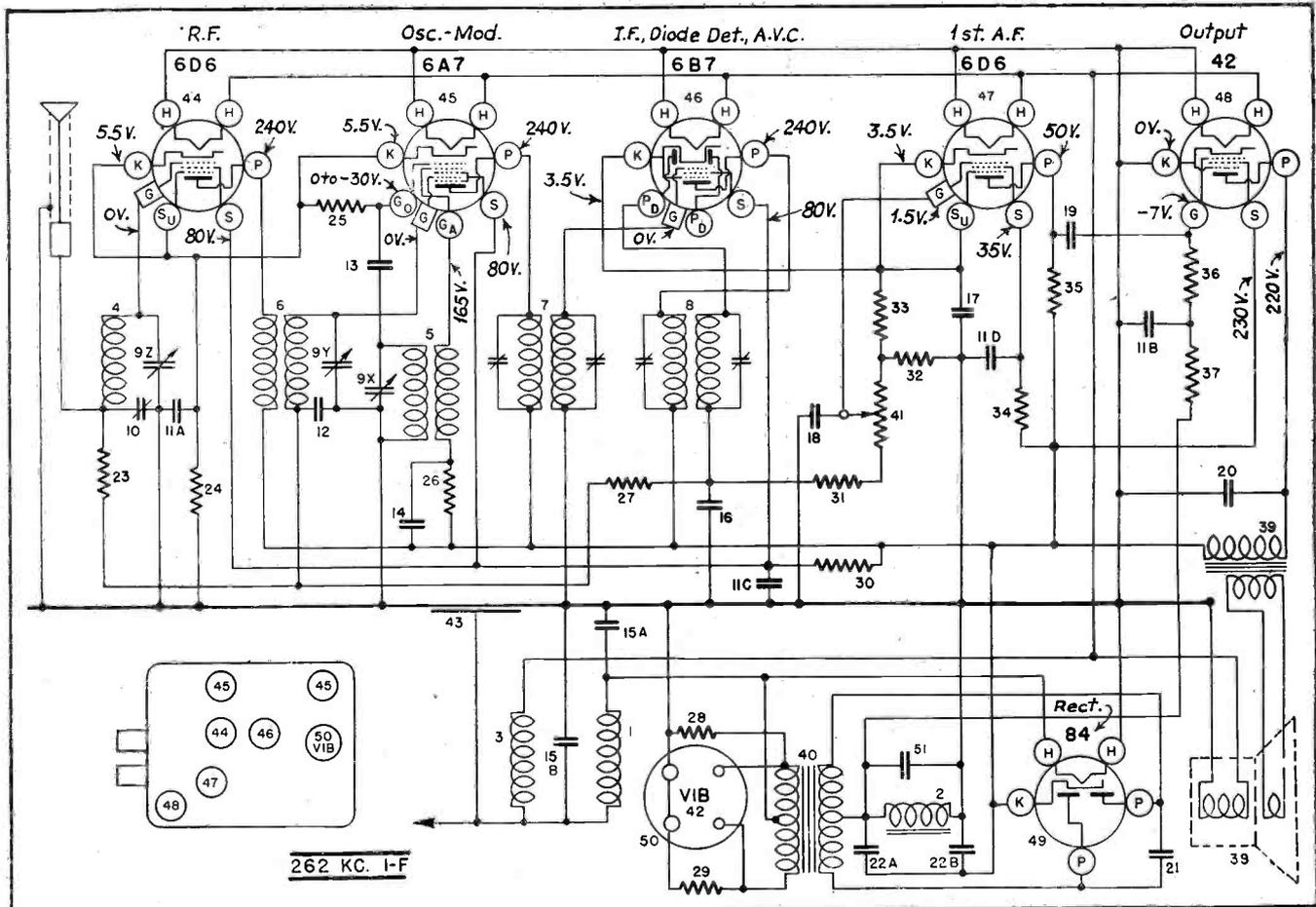


Fig. 1. Crosley A-266 circuit diagram.

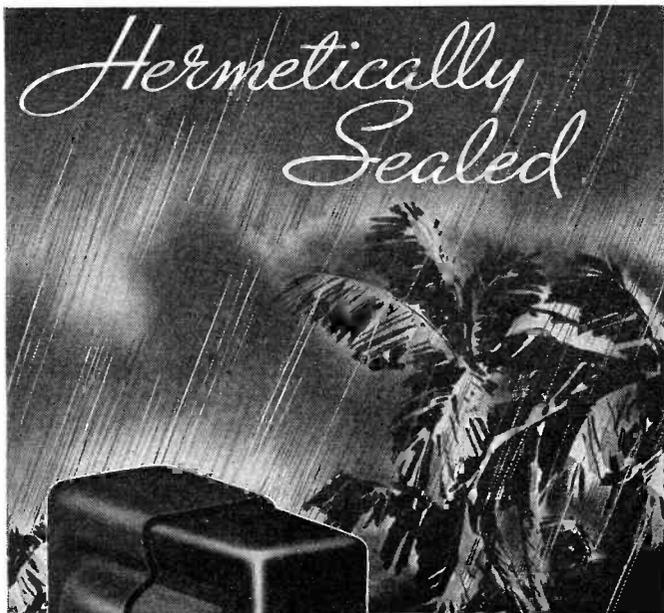

The NEW
JEFFERSON
Plastic-Sealed
Line
Audio and Output Transformers
and Chokes

● THE PLASTIC COATING of high melting point, black, moisture-proof compound, expertly applied, permanently adheres to and seals all exposed surfaces and assures positive protection from adverse climatic conditions.

● MOISTURE CANNOT PENETRATE this tough elastic jacket. The delicate windings are completely protected at all times and electrolysis or deterioration prevented. The coating is not brittle and therefore will not chip or crack to allow absorption and condensation of moisture to endanger the useful life of the windings.

The construction and design are up to the well-known Jefferson standard,—with precision machine-wound coils, vacuum-dried and impregnated,—cores of Jefferson specification silicon steel laminations annealed after stamping . . . JEFFERSON ELECTRIC COMPANY, Bellwood (Suburb of Chicago), Illinois. Canadian Factory: 535 College Street, Toronto, Can.

**SELECT
 FROM LIST
 BELOW**

ASK YOUR RADIO PARTS JOBBER

JEFFERSON *Radio* **Transformers**

AUDIO TRANSFORMERS

CAT. NO.	SIZE	PRICE
467-501 1 to 2 Audio	2-7/8 x 1-5/8 x 1-7/8"	\$1.25
467-502 1 to 2 P. P. Input	2-7/8 x 1-5/8 x 1-7/8"	1.30
467-503 1 to 3 Audio	3-1/4 x 1-7/8 x 2-1/8"	1.50
467-504 1 to 3 P. P. Input	3-1/4 x 1-7/8 x 2-1/8"	1.60

OUTPUT TRANSFORMERS

for Single or P. P. Output Tubes—71A, 45, 33, 42, 47, etc.

467-509 2 Watt-7000-4/6 Ohms	2-7/8 x 1-5/8 x 1-7/8"	\$1.20
467-510 3-1/2 Watt-7000-6/8 Ohms	3-1/4 x 1-7/8 x 2-1/8"	1.35

CHOKES

Small filter and plate chokes

466-(590) 20 Hen.-50MA.-425 Ohms	3-1/4 x 1-7/8 x 2-1/8"	\$1.50
466-(540) 250 Hen.-10MA.-5000 Ohms	2-7/8 x 2 x 2-1/2"	1.30

YOURS FOR THE ASKING!



The latest Sylvania service booklet is off the press. Send for your FREE copy Now!

Have you an auto radio installation or servicing business? Then you can't afford to be without this latest Sylvania Service Manual. This handy little booklet is chock-full of valuable information compiled by one of the most expert engineering research staffs in the business. And it's written in your language!

Here are just a few of the important subjects covered: Elimination of motor interference for every make of 1936 car. . . . Tube complement chart for practically all models of automobile radio sets, with I.F. peak frequencies. . . . Set and Antenna installation hints. . . . Power Supply hints, etc. These and hundreds of other problems you will meet in auto-radio installation and servicing are covered in this amazing book.

If this book cost a dollar, you'd pay it willingly. *But it doesn't cost a cent!* It's yours absolutely free. All you have to do is fill out the coupon below and send it to us. You'll receive your free copy in a few days.

Hygrade Sylvania Corporation. Makers of Sylvania Radio Tubes and Hygrade Lamps. Factories at Emporium, Pa., Salem, Mass., and St. Mary's, Pa.

SYLVANIA

The Set-Tested Radio Tube

HYGRADE SYLVANIA CORPORATION S-96
 Emporium, Pa.

Please send without obligation your new service book, "Auto-Radio Installation and Servicing."

Experimenter Amateur Call
 Serviceman Employed by dealer Independent

Member Service Organization


Name

Address

City State

Name of jobber

Address

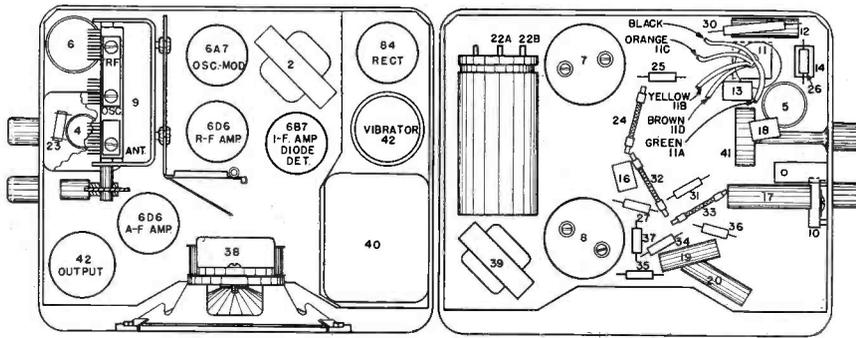

Figs. 2 and 3. Chassis views Crosley A-266.

ments of the volume control and tuning condenser. A standard control unit with short cables (6 inches to 8 inches) makes a very convenient and useful tool. If it is desired to shorten a pair of long cables it will be absolutely necessary to heavily tin the cables before cutting them.

I-F ALIGNMENT

(a) Connect the output of the signal generator through a 0.02-mfd condenser to the top cap of the 6A7 osc-mod tube, leaving the tube's grid clip in place. Connect the ground lead from the signal generator to the receiver chassis frame. Keep the generator leads as far as possible from the grid leads of the other screen grid tubes.

(b) Adjust the station selector so that the rotor plates of the tuning condenser are completely in mesh.

(c) Turn the volume control of the receiver full on and turn the tone control to the treble position.

(d) Set the signal generator to 262 kilocycles.

(e) Adjust both trimmers located on the second i-f transformer for maximum output.

(f) Adjust both trimmers located on the first i-f transformer for maximum output.

(g) Repeat operations (e) and (f) for more accurate adjustments.

Always use the lowest signal generator output that will give a reasonable output meter reading.

R-F ALIGNMENT

(a) Connect the output lead from the signal generator through a 0.00025-mfd condenser to the antenna connection of the receiver.

(b) Set the signal generator to 1400 kilocycles.

(c) Adjust the station selector to 140 on the dial.

(d) Adjust the trimmer on the oscillator section of the tuning condenser for maximum output.

(e) Adjust the trimmer on the r-f

section of the tuning condenser for maximum output.

(f) Adjust the trimmer on the antenna section of the tuning condenser for maximum output.

(g) Readjust the station selector for maximum output. Do not readjust the oscillator trimmer.

(h) Repeat operations (e) and (f) for more accurate adjustments.

ADJUSTING ANTENNA COMPENSATOR

(a) Set the signal generator to 600 kilocycles.

(b) Tune in the 600-kilocycle signal with the station selector for maximum output.

(c) Adjust the antenna compensating condenser, Illustration No. 10, Fig. 2, for maximum output.

(d) Repeat operations (b) and (c) alternately until no further improvement can be obtained.

(e) Set the signal generator at 1400 kilocycles again.

(f) Tune in the 1400 kilocycle signal with the station selector for maximum output.

(g) Readjust the trimmer on the antenna section of the tuning condenser for maximum output.

It will be necessary to adjust the antenna compensating condenser to the car antenna after the receiver has been installed in the car.

(a) After the installation is complete, tune in a weak station between 55 and 65 on the dial.

(b) Adjust the antenna compensating condenser for maximum volume in the speaker.

Cadillac and La Salle 6Q

This model is a six-tube automobile receiver using glass tubes in a conventional superheterodyne circuit. The tuning range is from 530 to 1650 kc. The power consumption at 6 volts is 9.0 amperes. The power output is 5.5 watts. A circuit diagram is shown in Fig. 1, with the tubes used, their functions, and

the various voltages encountered on the socket prongs lettered on the diagram. The values given were measured with a 1000-ohm-per-volt voltmeter with the volume control on maximum and the antenna shorted to the chassis. The grid bias of the driver and output tubes were measured at the genemotor cable socket.

Referring to the first i-f transformer, T4 in Fig. 1, it will be noted that there is a coupling winding shown below the primary.

When the expander (selectivity control) is in the sharp position, the coupling winding is open circuited and the loose coupling which exists between the primary and secondary of this transformer results in high selectivity.

When the expander is in the broad position, the coupling winding which is wound under the primary is connected in series with the secondary. This provides overcoupling which results in a greatly widened resonance curve. Passage of a wide range of audio frequencies is thus obtained.

ALIGNMENT PROCEDURE

Misalignment of condensers generally manifests itself as broad tuning and lack of volume at portions or all of the standard waveband. The receivers are all properly aligned at the factory with precision instruments and realignment should not be attempted unless all other possible causes of the faulty operation have first been investigated and unless the service technician has the proper equipment.

A signal generator that will provide accurately calibrated signals over the standard waveband and at the intermediate frequency, and an output meter are required for indicating the effect of adjustments.

I-F ALIGNMENT

Set the signal generator for a signal of 175 kc.

Connect the output of the signal generator through a 0.1-mfd condenser to the stator of the interstage section of the tuning condenser—see Fig. 2 for the location of this condenser. This can be done by connecting a lead to the lug on the top of this stator.

Connect the ground lead of the signal generator to the chassis ground.

Short out the oscillator section of the tuning condenser.

Turn the expander to the sharp position and keep it in this position for all adjustments.

Set the volume control at the maximum position.

Attenuate the signal from the signal

A WORD TO THOSE



WHO SERVICE



BATTERY RECEIVERS

Plug-in Terminals

The cells in these batteries are accurately sized and carefully compounded especially for "C" battery work. This makes the capacity bear the correct relation to "B" battery capacity, so that on modern battery receivers, practically all of which bleed the "C" battery during periods of operation, the "C" voltage goes down in step with the "B" voltage, thus preserving the ideal relationship between grid and plate voltage for best receiver performance throughout the entire life of the batteries.

Because the voltage of the "C" Battery is thus reduced, it is essential that new "C" batteries be installed with each new set of "B" batteries. Otherwise, the tubes will be considerably under-biased and the "B" battery current excessively high, so that the life of new "B" batteries will be seriously shortened if they are used with old, run-down "C" batteries.

Always replace the "C" battery with each new set of "B" batteries.


NATIONAL CARBON COMPANY, INC.
 General Offices: New York City
 Branches: San Francisco, Chicago
 Unit of Union Carbide **UCC** and Carbon Corporation
 The word "EVEREADY" is the trade-mark of
 National Carbon Co., Inc.

EVERY RADIO SERVICEMAN SHOULD OWN

FREE

RANGER EXAMINER

THE NATIONAL UNION ★WAY

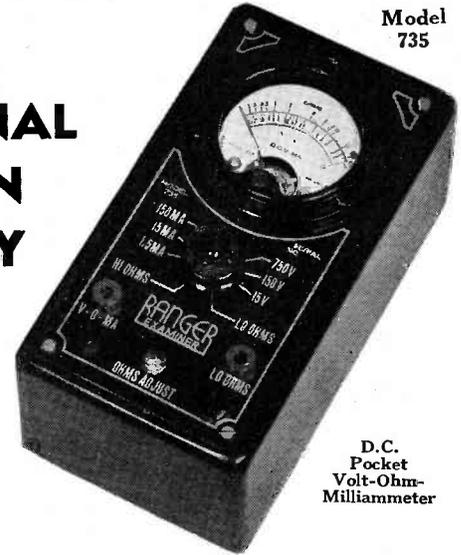

Model 735

D.C. Pocket Volt-Ohm-Milliammeter

Reads D.C. 15-150-750 volts at 1000 ohms per volt; 1.5-15-150 Milliamperes; 1/2-1000 low ohms; 0-100,000 high ohms at 1.5 volts.

★ The National Union Way makes the purchase of National Union radio tubes doubly profitable. Besides full protection on the highest quality radio tubes, each National Union tube purchased helps to earn free equipment. But, possession of the equipment is obtained at once with just a nominal cash deposit. (Deposit is rebated when required number of tubes have been purchased). Over 50,000 completed deals with progressive radio dealers. Don't be misled. See your National Union jobber and get all the facts.

OTHER NATIONAL UNION OFFERS

In **SOUND EQUIPMENT** items available include 17-watt portable system, 10-watt portable system, 6-watt portable system, phonograph pickup and turntable, etc.

In **SERVICE EQUIPMENT** items available include tube testers, analyzers, oscillographs, signal generators, modulators, meters, etc.

In **SHOP EQUIPMENT** items available include stock cabinets, coats, display signs, etc. All items absolutely free the National Union Way.

NATIONAL UNION RADIO TUBES

National Union manufactures a complete line of radio tubes in glass, metal and G-type. National Union's high quality has made them the outstanding favorite in the radio service profession. All sales policies have been formulated with the idea of making National Union radio tubes the ideal replacement tube for the radio dealer. This has been backed up with a selling program that means real support and help to the wide-awake dealer. Dealers and jobbers handling National Union radio tubes are the leaders in repair parts and service.

Let National Union Help You

Write for Information

THE ROAD TO BETTER BUSINESS

1. Full guarantee on highest quality radio tubes. 4. N. U. jobber stocks are complete...No hunting for odd types.

2. Cut price business not solicited. 5. Timely business building aids.

3. Price Protection.

NATIONAL UNION RADIO CORPORATION
 570 Lexington Ave., New York City

S-936

Please send me more information on Ranger-Examiner New Pocket D.C. Volt-Ohm-Milliammeter.

Dealer Name

Address

City

AUTO-RADIO—continued

generator to prevent the leveling-off action of the avc.

Then adjust the three i-f trimmers until maximum output is obtained. The location of these trimmers is shown in Fig. 2.

1650 kc adjustment:

Set the signal generator for 1650 kc. Turn the rotor of the tuning condenser to the full open position.

Connect the shielded antenna lead from the chassis through a 110-mmf condenser to the antenna post of the signal generator.

For this and all subsequent adjustments keep the volume control at the maximum position and attenuate the signal from the signal generator to prevent avc action.

Adjust the trimmer of the oscillator section of the three-gang condenser until maximum output is obtained—see Fig. 2 for location of this trimmer.

1400 kc Adjustment:

Set the signal generator for 1400 kc.

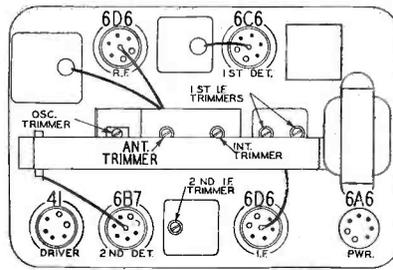


Fig. 2. Chassis view showing tube and trimmer locations.

Turn the rotor of the tuning condenser carefully until maximum output is obtained.

Adjust the interstage and antenna trimmers for maximum output—see Fig. 2.

Do not change the setting of the oscillator trimmer.

ADJUSTING ANTENNA TRIMMER

After the receiver is installed and the

car antenna is connected it will be necessary to adjust the antenna trimmer. Tune in a weak signal between 1200 and 1400 kc with the volume control about three-fourths on. Remove the cover of the chassis case. The antenna trimmer is on the center tuning condenser section—see Fig. 2. Turn the adjusting screw of this condenser up or down until maximum output is obtained. Caution—Do not turn any of the other trimmer adjusting screws for this adjustment.

Antenna Shield Ground

It is often necessary to ground the shielded antenna casing every foot or two. In these cases it is advisable to run a heavy bare copper wire (about No. 12) along the shield wrapping the two together every foot or so and grounding the copper wire at each end.

Hygrade Sylvania Auto-Radio Hints


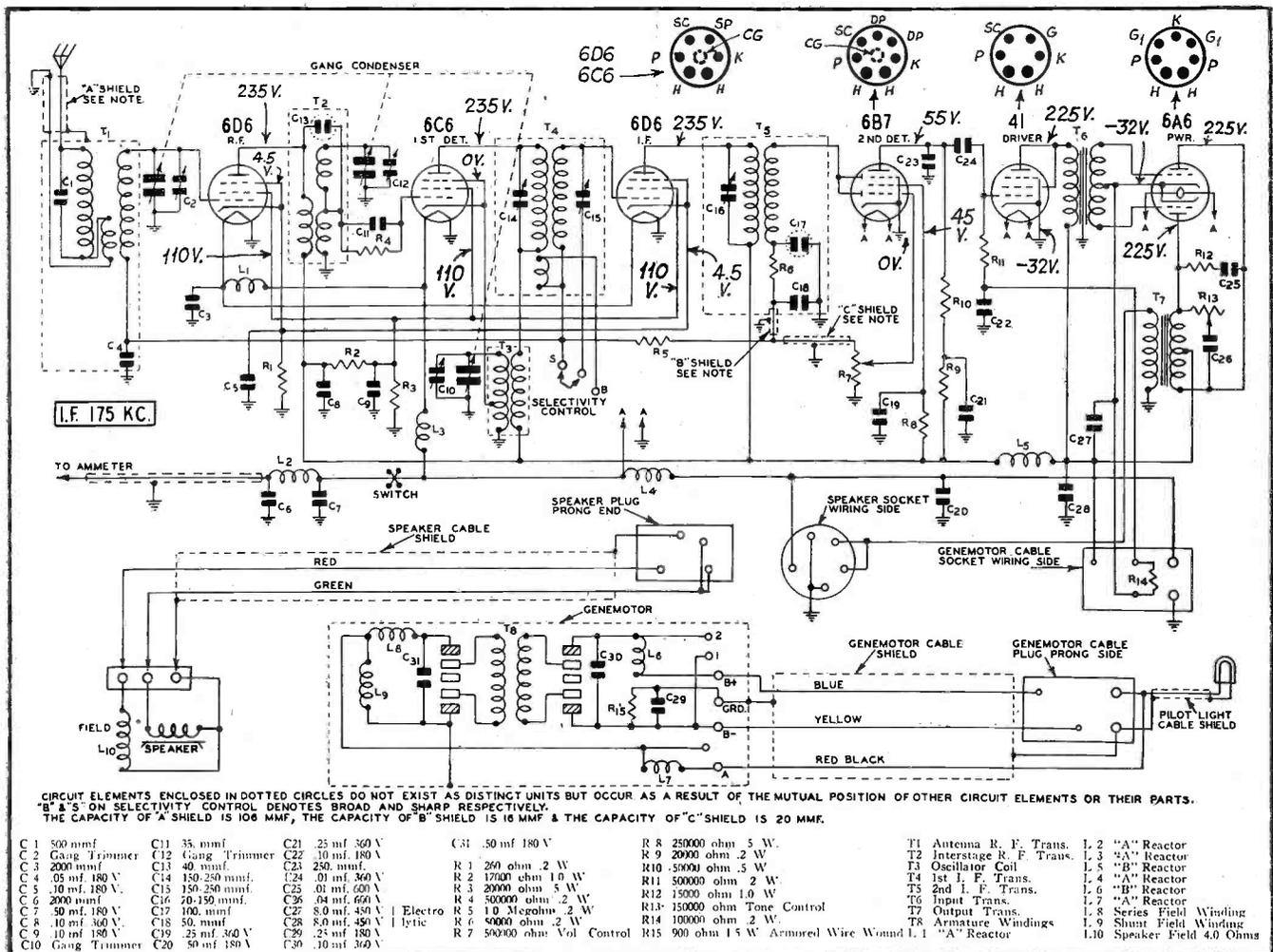


Fig. 1. Cadillac and LaSalle auto-radio circuit diagram.

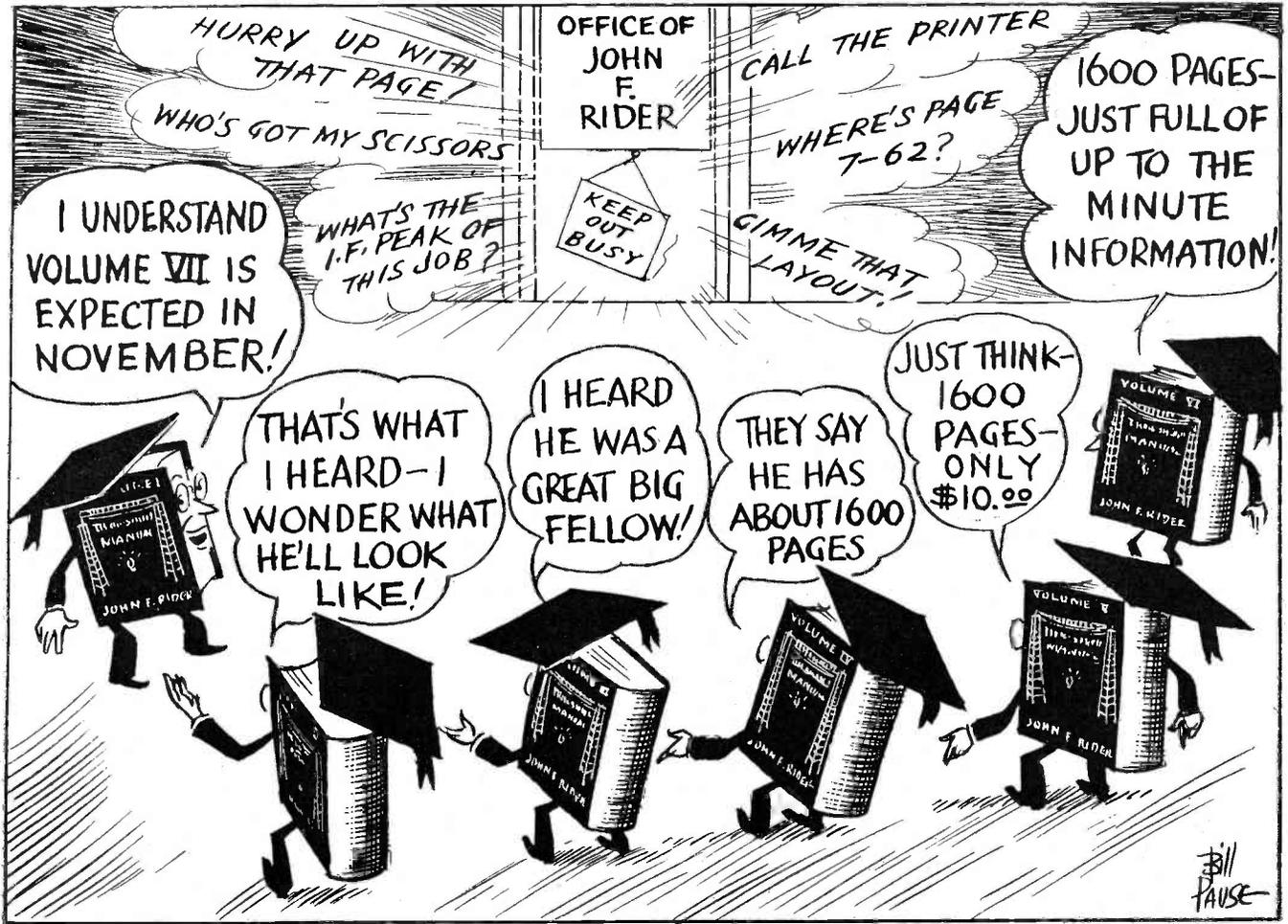



FREE!

REPLACEMENT TRANSFORMER GUIDE

DON'T hunt through page after page of catalogs for the right transformer for any receiver. It's FREE to users of Stancor Transformers. Mail the coupon.

SEE OUR EXHIBITS
Booth 2, IRSM Show
Sept. 18-20
Hotel Penna., New York

Booth 34,
Amateur Radio Show
Hotel Sherman, Chicago
Sept. 5-7

MAIL THIS COUPON

STANDARD TRANSFORMER CORPORATION
866 BLACKHAWK STREET, CHICAGO, ILLINOIS

Please send me STANCOR Replacement Guide.
I am enclosing Stancor Box Top or
I am enclosing 25 cents to cover mailing cost.

Name _____ Address _____

Public Address . . .

A PRACTICAL A-C, D-C AMPLIFIER

THE practicability of a p-a amplifier capable of operating from either a-c or d-c mains need not be stressed. In large cities, such as New York, Philadelphia and Chicago, d-c is often encountered. In some areas 25-cycle a-c is the only current available. Many hotels and theatres generate their own d-c. In all these instances a good portable a-c, d-c amplifier can be used to advantage. The circuit diagram given in Fig. 1 is applicable for such service.

THE INPUT CIRCUIT

The circuit is of the high-gain type with separate, independent low-gain input terminals.

The high-gain terminals feed directly into a 6C6 (or 6J7) pentode grid with a 5.0-megohm load resistor. This is the specified load for satisfactory operation of a crystal microphone. The return leg of the microphone, usually fed through the shield portion of the microphone cable, must be rubber covered since it is connected to the power line (through the two filter chokes).

The plate of the input pentode is fed through a 0.1-mfd coupling condenser to the 250,000-ohm high-gain stage volume control. The arm of this control is fed through a 1-megohm resistor to

the grid of the second stage, a 6C6 (or 6J7) pentode. A low-gain input circuit such as a phonograph pickup or a radio tuner, with its own volume control can be plugged into the closed circuit jack which feeds the second stage 6C6 (or 6J7) through a 500,000-ohm resistor.

By use of the special input circuit shown for the second stage suitable mixing of the two stages is accomplished with independent control of volume for either or both circuits.

The arrangement is such that when the first stage volume control is on maximum about one-third of the output of the first stage is fed to the grid of the second stage. This condition is altered only slightly by the position of the second stage control.

The grid of the second stage is tapped off between the 1-megohm and the 500,000-ohm resistors. These resistors are in effect in series (together with the second-stage volume control) across the output voltage from the first stage. Thus the second stage receives

$$\frac{500,000}{1,000,000 + 500,000} \text{ or } \frac{1}{3}$$

of that output.

Examination of the low-gain input

circuit will show that about two-thirds of the voltage delivered to the input to this stage is fed to the second 6C6 grid. In this stage the 500,000-ohm resistor, connected in series with the input jack and the 6C6 grid, and the 1-megohm resistor are in effect across the voltage input to this stage. However, in this case the 1-megohm resistor is in the ground leg; the ratio will therefore read

$$\frac{1,000,000}{500,000 + 1,000,000} \text{ or } \frac{2}{3}$$

of the signal.

Enough gain is provided in the remaining stages of the amplifier to offset this apparent loss. Full excitation of the four 43's is obtained with the output of a crystal microphone, a phonograph pickup, or a radio tuner connected to their respective inputs.

The position of the first stage volume control will have little effect on the signal from the second-stage input because the fraction of the 250,000-ohm resistance over which the knob is adjusted during any change in volume is negligible as compared to the total 1,000,000 ohms or more across the second-stage circuit.

THE SIGNAL-DIVIDER STAGE

The output of the second stage is resistance coupled to a 76 (or 6C5)


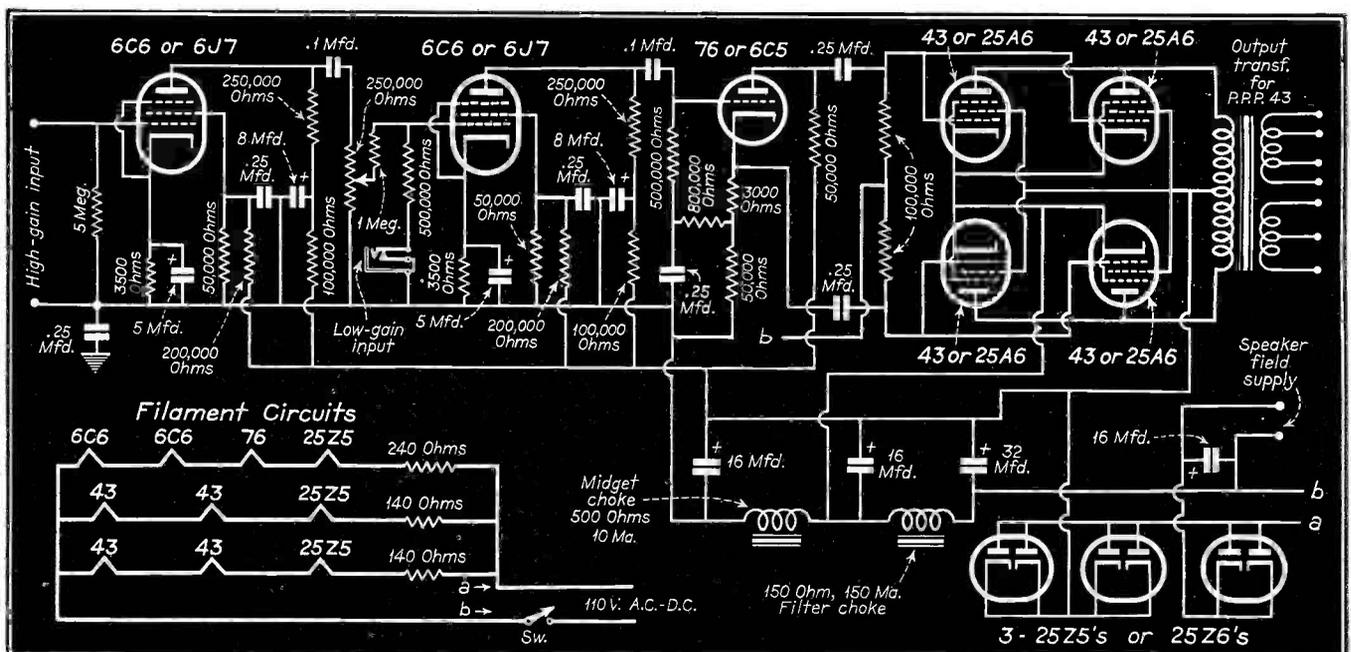


Fig. 1. Circuit diagram of a-c, d-c amplifier.

A NEW DEAL IN P. A.

(plus a new deck of cards!)

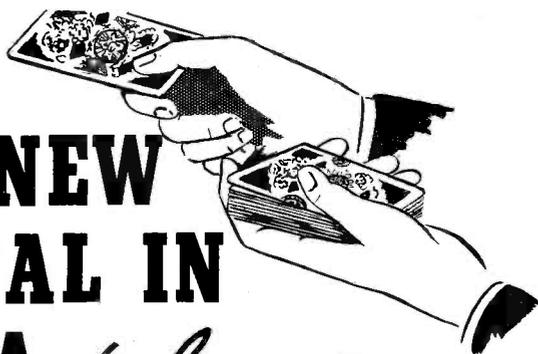

OUT of the chaos which has enveloped the Public Address market, CLARION emerges with a new deal in distribution, and a new deck in the form of a complete line of sound equipment which is a full year ahead of the rest.

Now—for the first time—sound engineers will be able to centralize their source of P.A. equipment. Distribution will be effected through franchised jobbers in each territory—Johnny Q. Public cannot buy CLARION direct—list prices will be maintained for the protection of the Serviceman or Engineer who makes the installation—a comprehensive advertising campaign will intensify the demand for CLARION P.A. equipment. That's CLARION'S NEW DEAL. And it's a FAIR and SQUARE deal!

SHOW VISITORS: We cordially invite you to inspect the new CLARION line at our Showrooms. Demonstrations at your convenience.



CLARION MODEL C17

Here's one of the new deck of cards. It's an ACE—portable, rugged, well designed, PRICED RIGHT. Send for catalogue describing the entire CLARION line.


TRANSFORMER CORPORATION OF AMERICA

DEPT. J15

69 WOOSTER ST., NEW YORK, N. Y.



Clarion
AMPLIFIERS

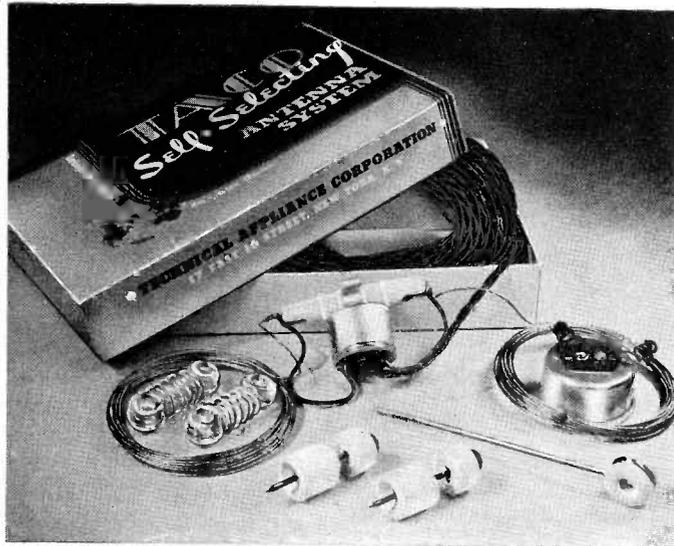

ANTENNA SYSTEMS that make money for you!

WHY? Because folks today want the best to be had in radio entertainment. That fellow with the latest all-wave set, and the other fellow with the old set, both are ready to spend a few dollars for *demonstrably better* results. And that means the sale of either one of these two TACO jobs:

* Popular-Priced TACO No. 500 System

All-Wave, self-selecting, noise-reducing system; factory assembled, wired, soldered.

Readily installed. Just string up Built to last. Trouble-proof.

Complete kit—no extras to buy. Attractively boxed. Instructions. Shown above.

Priced at only \$4.50 list. A fast seller both over the counter and on service calls.

* DeLuxe TACO No. 200 System



A product of years of specialized engineering, thousands of tests, and present demand for superlative results.

All-wave, self-selecting, noiseless. Provides new conception of any set's performance.

Complete kit—no extras to buy. Factory assembled, wired, soldered (ant-corrosion wire and joints).

Neatly packaged. Complete instructions. Only \$6.75 list—and a real big value!

* TACO Master Antenna Systems

Single aerial and downlead serves up to 25 sets. All-wave. Maximum efficiency. Noiseless. Concealed wiring for new buildings, exposed for old. Ideal for apartment houses, hotels, hospitals, clubs, etc. Also for private dwellings.

*** Let Us Tell You How . . .

Just write for technical and merchandising facts on all three of these popular antenna systems. Better still, order one No. 200 and one No. 500 from your TACO jobber, try them out, and you'll sell many of them. And ask him about the Master System.

TACO

• TECHNICAL APPLIANCE CORP.

Pioneers in Noiseless Antenna Systems


17 EAST 16th STREET

NEW YORK CITY

signal-divider stage. The operation of this type of circuit was fully described in SERVICE for June on pages 260 and 263. The general details of this circuit are repeated in Fig. 2.

An ordinary triode has a resistor (R1) connected between plate and B plus and a resistor (R2) between the cathode return and B minus. Each resistor is approximately half the value of the plate resistor that would ordinarily be used with this tube in a typical resistance coupled stage. R4 is the self-biasing resistor of the usual value for the type of tube used and C1 is a high-capacity by-pass condenser of the low voltage electrolytic type. If a signal is now applied between the grid and cathode it will be amplified and appear across each of the load resistors R1 and R2 with equal amplitude and opposite phase. All that is necessary is to couple the plate and cathode to the next or push-pull stage through coupling condensers.

The signal-divider circuit used in the

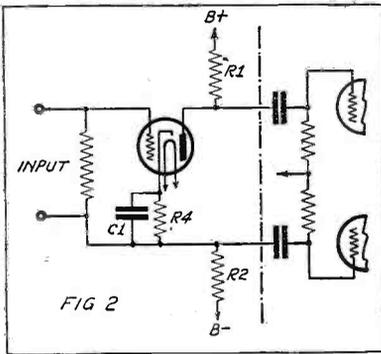

amplifier is similar to that pictured in Fig. 2. Bias is provided for the 76 (or 6C5) signal-divider stage by the 3,000-ohm resistor in series with the 50,000-ohm cathode load resistor. The grid return is led to the proper potential by means of the 800,000-ohm resistor which also serves to isolate the grid circuit from the cathode circuit. This resistor, which is in parallel with the 50,000-ohm cathode load resistor as far as the signal is concerned, is of such value that its shunting effect offsets the series effect of the 3,000-ohm bias resistor. Thus the cathode load is kept at the same value as the plate load.

THE OUTPUT STAGE

The output stage consists of four 43's in a push-pull parallel arrangement. A low value (100,000 ohms) of resistance is chosen to suitably load the grid circuit of this stage. The small value of this grid load makes the use of 0.25-mfd coupling condensers necessary for faithful transmis-

sion of the low-frequency signals. The grid return for this push-pull parallel stage is connected to the a-c, d-c line ahead of the two filter chokes. A resistance filter (not exceeding 100,000 ohms) may be used with a by-pass condenser of about 1-mfd returned to the common cathode connection of the 43 tubes. Should any hum feed through to the circuit at this point then the resistance capacity filter must be employed.

The bias for this stage is obtained from the d-c drop across the first (150 ohm) choke in the filter circuit. Because of this use of the filter choke its value is critical. Any small choke may be used in the second position.

The output of the amplifier is fed to a transformer and from the secondary to a suitable speaker voice coil or to a universal line. If an exact matching transformer for push-pull parallel 43's is not available a transformer designed for a single pair of 48's to the desired load, from a practical standpoint, is a suitable match for the push-pull parallel 43's.

POWER SUPPLY CIRCUITS

Power for the operation of the heaters is taken directly from the a-c, d-c line through the use of dropping resistors. Three separate circuits are employed to minimize the hum pickup from this source.

Two 25Z5's (or 25Z6's) are used in a parallel half wave circuit to rectify the current needed for plate supply. The plate and screen current for the 43 tubes is filtered by means of the 150-ohm choke in the negative return of the power supply circuit. A 32-mfd condenser across the rectifier output and a 16-mfd condenser at the output of the choke are used to assist the rectifier and filter circuit. A second choke is used in conjunction with another 16-mfd condenser to further assure smooth d-c for the plate circuits of the earlier stages of the amplifier.

A third 25Z5 (or 25Z6) is used with a 16-mfd condenser to supply the d-c necessary for the excitation of the speaker field. To assure humless operation the speaker should be equipped with a bucking coil or similar hum filtering arrangement. A permanent magnet type dynamic speaker may be used; in this event the third 25Z5 may be omitted.


The layout of parts aside from following general practice is not critical. The absence of input and power transformers which might cause hum pickup contributes to this flexibility. The

filament supply resistors should be mounted in such a manner so as to allow sufficient radiation of the heat generated. The electrolytic condensers should not be near these resistors nor near any other part or tube that radiates considerable heat.

Locating Intermittent Condensers

Probably the most difficult problem presented in the repair of radio receivers is the detection of open or intermittently open condensers. To definitely test a condenser unit for such condition is possible through the use of the apparatus described below.

An r-f oscillator capable of delivering about 10 watts to a linked circuit is required. A complete home-made circuit was described in the Philco Service Broadcast for July, 1935. The linked circuit is coupled to another tuned circuit as shown in the accompanying diagram. With the test leads shorted the circuit is tuned to resonance with the oscillator. The resonance condition will be indicated by the flickering of the pilot light. The by-pass condenser to be tested need not be disconnected from the receiver since the impedance of a condenser of say 0.01 mfd or larger is negligible at that frequency and will short circuit any resistance which may be connected across it in the receiver. With the circuit in resonance the test leads are then connected across the condenser to be tested. A slight retuning

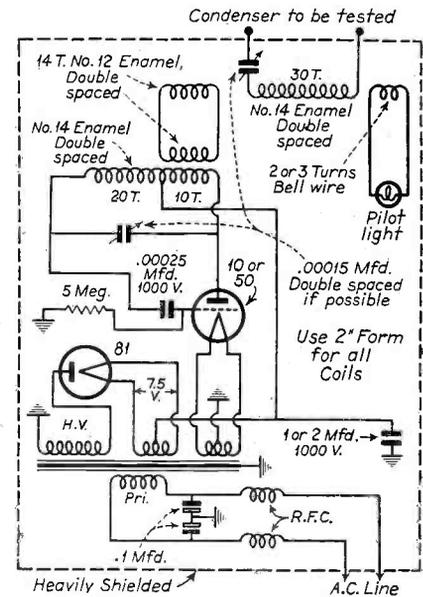

of the resonant circuit may be necessary. An intermittent condenser will be completely burned out by the large current in the resonant circuit, whereas a good condenser will not be affected.


Harvey Schock



OL' MAN CENTRALAB 'TAKES IT' EITHER WAY

blistering heat, or excessive humidity
... it's all the same to a CENTRALAB
Control ... Millions of these Controls
are "standing up" under unbelievably
severe conditions ... so the next time

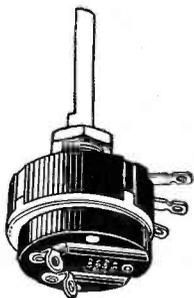a control goes "hay-
wire" change to
CENTRALAB ... and
play safe.



Every Radio Service Man
should be a member of the
Institute of Radio Service Men

Centralab

MILWAUKEE, WIS.

British Centralab, Ltd.


Canterbury Rd., Kilburn, London, N. W. 6, England

Centralab, 68-70 Rue Amelot, Paris, France

VOLUME CONTROLS
FIXED RESISTORS

THE 4 WAY ARCTURUS LINE IS N . E . W . S


GLASS

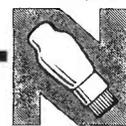

CORONET



THE PERFECTED
METAL TUBE

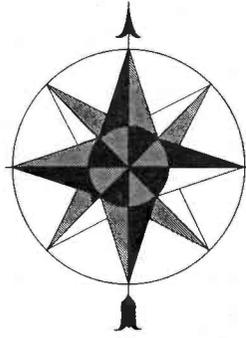

"G"



CORONET
TO REPLACE
OLD GLASS TUBES

Millions of Arcturus Glass Tubes, used initially in radio receivers, create a *natural* replacement market for Arcturus Dealers and Servicemen.

More "G" Tubes of Arcturus manufacture are in use today than any other make. Pioneered by Arcturus more than a year ago, and now used by the entire industry, Arcturus "G" Tubes have the advantage of tested and proved performance.

Arcturus Coronets—the *perfected Metal Tubes*—are being used as initial equipment by a number of set manufacturers. The active demand for Arcturus Coronets indicate the preference of the trade and consumers for a tube they *know* will give the same efficient service as other Arcturus Tubes.

Arcturus Coronets for replacing glass tubes is the *biggest* sales idea that has hit dealers and servicemen in years. Made to order for you to increase your sales and profits. Owners of old sets like this modernization idea; want to incorporate radio's latest development in their receivers.

ARCTURUS

alone provides a 4-way sales and profit set-up; has designed its prices to give the trade a better opportunity for profits; pioneered 7 of the 8 fundamental developments in a.c. tubes. (Arcturus Dealers and Servicemen are kept always ahead.)

ARCTURUS RADIO TUBE CO., NEWARK, N. J.

At the Show!

Be sure to see the ARCTURUS EXHIBIT Booth No. 12, New York Retail Trade Show, September 18th, 19th and 20th.

Get on the band-wagon. More sales and greater profits with Arcturus. See your Arcturus Jobber, or write us today for details of this 4-way profit line.



ARCTURUS
GLASS—"G"
CORONET The Perfected Metal
RADIO TUBES

TEST EQUIPMENT...

RCA Universal A-C Bridge

This Universal Bridge consists of a variable-ratio-arm Wheatstone Bridge having three standards each of inductance, capacity and resistance. A vacuum tube 1,000-cycle oscillator and a two-stage amplifier, together with their power supply, make up the major part of the equipment. The only additional equipment required is a "null" indicator for which the usual high impedance headphones suffice. Power is obtained from a 110- to 120-volt, 25- to 60-cycle supply.

The two terminal posts in the upper left-hand corner of the panel, marked "X," are the points to which the component to be measured is connected. Beneath are the two phasing controls, used for balancing out the resistance component always present in inductors or capacitors. The upper control graduated from 1 to 100 is for coarse adjustment. The lower control, graduated from 1 to 10, is used when fine adjustment is required. The control, "Capacity Balance for Resistance, 100M-1 Meg.," in the lower right-hand corner

is a phasing control necessary for obtaining balance in this range. Above this phasing control is the "Range" selector switch, which determines the type and range of measurement, i. e., whether it is resistance, capacity or inductance, and in conjunction with the "Low-High" switch, the bracket of measurement is indicated. The main dial (calibrated from 1 to 10), located in the center of the panel, is used for obtaining balance on all measurements. The switch marked "R in X Arm" and "R in Std. Arm" shifts the "phase" controls from the "X" arm to the "Std." arm of the bridge.

With the phones plugged in and with no external connections to the "X" terminals, make the 110-volt connection to the line and turn the "110-Volt A. C." switch "On." After a short interval, during which the tubes are warming up, a 1,000-cycle tone will be heard in the phones. The bridge is now ready for operation.

Caution: Do not connect the case or any part of this instrument to ground. The unknown unit being measured must not be grounded. This is necessary for

the protection, operation and accuracy of this bridge.

The unit to be measured may now be connected to the binding posts marked "X" with its low terminal connected to the "X" terminal to the left. By low terminal it is meant that terminal nearest ground potential. The bridge may now be balanced (see specific instruction under Resistance, Capacity and Inductance measurements). Remember that the balance is indicated by *minimum 1,000-cycle* tone in the headphones. When this condition exists, the second harmonic, 2,000 cycles, often becomes quite loud in the phones. This, however, does not indicate an unbalance. The 1,000-cycle tone is always the tone to adjust to a minimum.

If it is found impossible to obtain a null point on the bridge, the unit under test is either defective or outside the range of the bridge. Note, however, that it is impossible to measure with the bridge the resistance of an inductor. This does not indicate a faulty inductor or bridge, but is simply a characteristic of this type of bridge circuit.

RESISTANCE MEASUREMENTS

Connect the resistance to be measured to the binding posts marked "X." The low side of the resistor should be connected to the terminal to the left. The two phasing controls should be set so that each is at its counterclockwise posi-


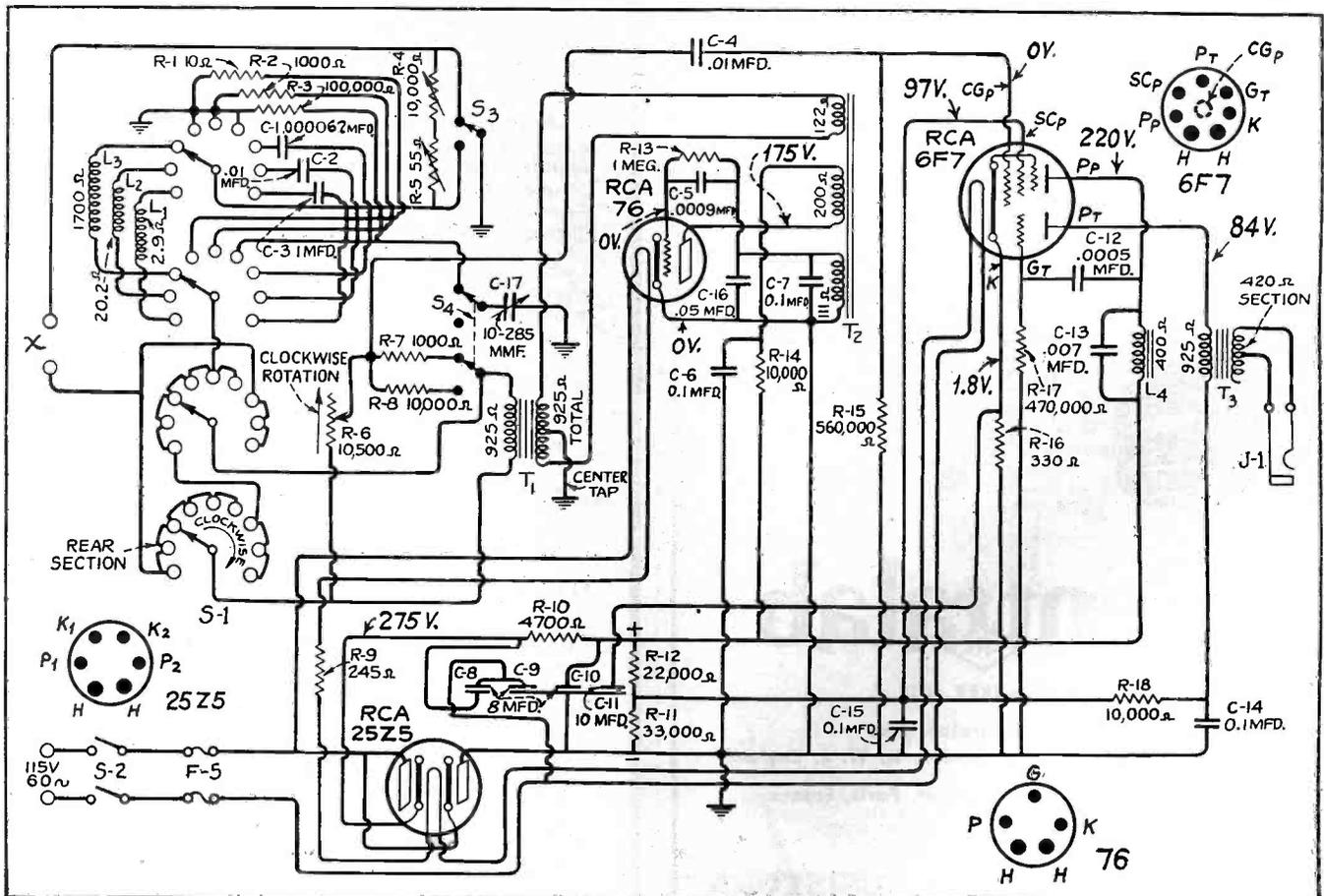


Fig. 1. RCA TMV-132A universal a-c bridge.

ELECTRO-VOICE

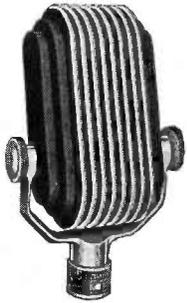TWO BRILLIANT SERIES VELOCITY MICROPHONES



THE "K" SERIES

Entirely new performance, appearance and value. You can now have velocity performance and quality on your lowest priced installations. Shock-absorber, 8' cable, locking cradle all included. High impedance output.

Model K-20. America's lowest priced Velocity Microphone. Output: -68 DB. Finished in black with chromium trim. List Price: \$19.50

Model K-21. An excellent microphone for music or voice. Finished in black with chromium bars. Output: -66 DB. List Price: \$24.50

Model K-22. The finest in the "K" series. Beautifully finished in chromium with black trim. Output: -64 DB. List Price: \$29.50

THE "V" SERIES

The established standard for high-fidelity reproduction. Widely used throughout the World in Broadcast, Recording and Public Address. Thoroughly shielded against inductive hum. Frequency response 40-14,000 c.p.s. Two year guarantee. Complete with 20' cable, locking cradle and internal shock-absorber.

Model V-2. One of America's most popular microphones. Finished in black and chromium. Output: -68 DB. List Price: \$35.00

Model V-3. Designed for ultra-quality Broadcast or Sound work. Finished in black and chromium. Output: -66 DB. List Price: \$50.00

Model V-4. One of the finest microphones that research can evolve. Finished in black and chromium. Output: -64 DB. List Price: \$75.00




See your distributor or write for literature.

ELECTRO-VOICE MFG. CO., INC.

332 E. Colfax Ave., South Bend, Ind.

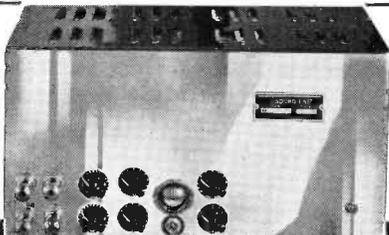Export Office: 100 Varick Street, New York, N. Y.



THE SENSATIONAL "30-60" 28 SOUND SYSTEMS IN ONE!

- The MASTERPIECE "30-60" is the only truly universal sound system being built today. It will cover an outdoor audience of 50,000 people—or 1,500 pairs of headphones in a hospital. It is the most flexible sound system ever designed in terms of inputs, outputs and power output of anything from one watt up to sixty-four honest man-sized watts at 2½ times less than customary total harmonic distortion. It has a dozen entirely new technical features—and such mechanical advantages as rack mounting, wall mounting and portable operation all in one unit.

- Any MASTERPIECE amplifier may be purchased on Easy Terms with a 5-Year Guarantee and a Free Trial under your own conditions. Send the coupon for full details.

McMURDO SILVER

MASTERPIECE AMPLIFIERS

FULL DETAILS FREE — MAIL THIS COUPON!

McMURDO SILVER CORP.

3356 N. Paulina St., Chicago, Ill., U. S. A.


Please RUSH me full details on MASTERPIECE amplifiers.

Name

Address

WHAT THIS CARTON ON YOUR JOBBER'S SHELF

TO YOU!

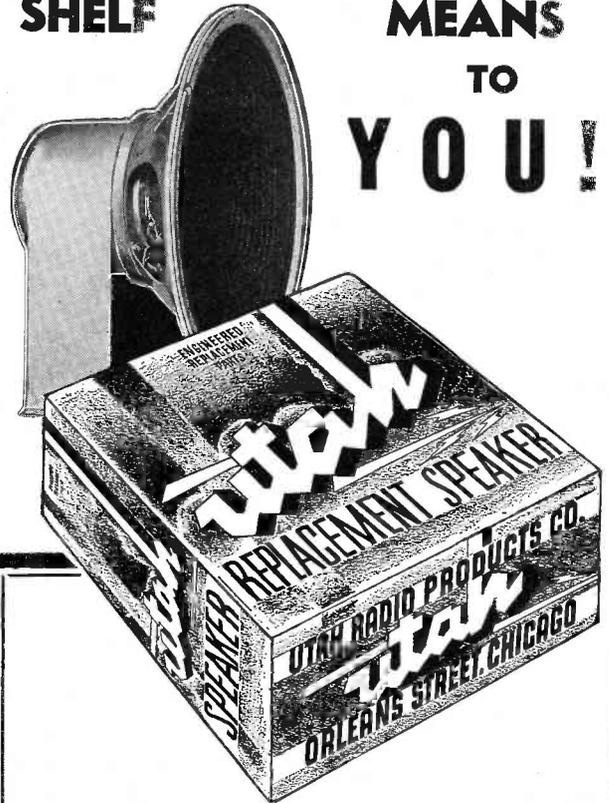

It means *instant service* on replacement speakers because your jobber stocks only twenty scientifically designed models which give you perfect replacement for *any set you will ever be called upon to service.*

The UTAH carton also means that behind the product it contains there is fifteen years' experience in building quality replacement parts.

UTAH also makes the best in replacement Vibrators, Transformers, Chokes, Volume Controls, Tone Controls, Resistors, Jacks, Jack Switches, Push Button Switches and Plugs.

UTAH RADIO PRODUCTS COMPANY

ORLEANS STREET, CHICAGO

"15 YEARS OF LEADERSHIP"

tion, since they are not used in resistance measurements. More conveniently, they may be cut out of the circuit by throwing the phasing toggle switch to the down, "R in Std. Arm" position. Now select the lowest resistance scale. This is done by throwing the range toggle switch to "Low" and by turning the Range Switch to the first resistance position (1-10 ohm). Now turn the large centrally located knob so that the pointer moves over the main scale from 1 to 10. If the resistance we have selected to measure lies anywhere between 1 and 10 ohms, a null point (balance) will occur and moving the pointer in either direction will *increase* the signal in the phones. If the null point is exactly at 5 on the scale, the resistance of the unknown is 5 ohms. If it occurs between 5 and 6 and exactly on the first small division to the right of 5, the resistance is 5.1 ohms. If no null point is found on this scale, throw the toggle switch to "High." The main scale now reads from 10 to 100 ohms. If still no null point is found, set the toggle switch on "Low" again and move the Range Switch one position to the right, so that just under ohms we read 100-1M. Since M represents 1,000, the scale now reads 100 to 1,000 ohms. In a like manner, by throwing the toggle switch to "High" the main scale becomes 1M to 10M; that is 1,000 to 10,000 ohms. On this latter scale, a null point at 5 means that the unknown resistance is somewhere between 1,000 and 10,000 ohms, then the range switch and the "Low-High" switch are set to select this range and the resistance reading obtained from the main scale after locating the null point. With this control set at approximately mid scale obtain an initial resistance balance. Then vary the capacitor for a null point.

CAPACITY MEASUREMENTS

Set the bar pointer knob so that it is pointing to mmfarads, which is an abbreviation for the familiar micro-micro-

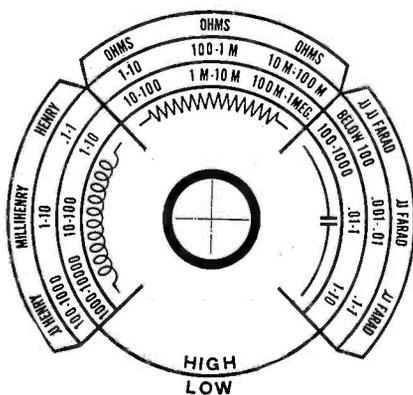


Fig. 3. Dial scale.

farads. Set the toggle switch to "Low" so that the range in use is "below 100." Now move the pointer over the main scale and at somewhere near 30 (scale division 3) a null point will be found. This is the balance point with no capacity across the "X" terminals. For convenience, we will refer to this reading as the capacity constant "K." If a small capacity is connected across the "X" terminals, say 20 mmfd, a new null point will be found at the capacity constant plus 20. Therefore when making measurements with the range switch in the lowest capacity position, the null point is found, the scale is read and "K" is subtracted from the reading.

At this point the two variable resistor phasing controls should be considered. For the very small capacitors treated above, their setting does not affect the null point appreciably. The reason for the inclusion of these controls in this bridge is that all capacitors and inductances have some resistance. The amount of this resistance is an indication of power loss. Ordinarily we are not interested in the exact power loss, but in order to secure a null point the effect of this resistance must be balanced out.

To continue with capacity measurements, leaving the range switch (pointer) at "Mmfad," throw the toggle switch to "High." The scale is now from 100 to 1,000 mmfd. In this range, the phasing controls have more effect on the null point. Set the phasing controls at their minimum positions and with the main control secure a tentative null point. Then increase the upper (coarse) control to see if the signal increases or decreases. If the signal decreases, adjust the phasing control for a minimum signal. Then readjust the main control for minimum. The true null point is obtained by successive adjustments as outlined above.

If increasing the phasing control causes an increase in signal instead of a decrease, then the toggle switch to the right of the lower control should be thrown to the opposite position and successive adjustments made until the null point is obtained. In this capacity range (100 to 1,000 mmfd) the lower (fine) phasing control will have little effect. In this range also the capacity constant "K" is subtracted from the null point reading. If the null is at 500 mmfd and "K" is 30, then the true capacity is 500 minus 30 equals 470 mmfd. For all higher capacity ranges, this correction need not be made as it will be a negligible portion of the capacity.

INDUCTANCE MEASUREMENTS

Connect the inductance to be meas-

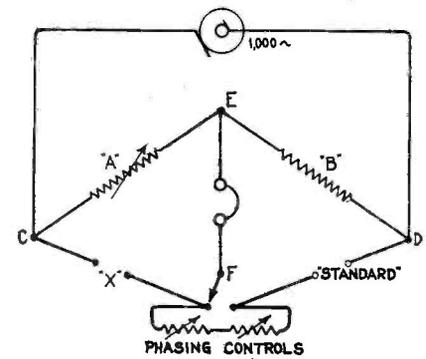


Fig. 2. Wheatstone bridge circuit.

ured to the "X" terminals and with its low side connected to the left terminal, a preliminary null point is obtained on the main scale. Then the phasing controls should be adjusted to reduce the signal in the phones to a new low point. Successive adjustments of the main control and phasing controls should be made until the lowest signal can be obtained. The inductance is read directly from the main scale. For illustration, suppose the range switch is set to "millihenry," the range toggle switch is on "Low" and the main scale reads 6, then the inductance is 6 millihenries. The setting of the phasing controls is not taken into consideration at all. The two phasing controls are in series and in measuring inductance it will usually be necessary to find the resistance component balance roughly on the "coarse" control and then adjust the "fine" control for the final balance. Facility in successively manipulating the phase control and ratio comes readily with practice. On the lowest inductance scales, the resistance balance is quite critical and some care will be required to secure the correct null point. This same care is necessary with a laboratory bridge as well.

CIRCUIT DESCRIPTION

A simplified a-c Wheatstone bridge is shown in Fig. 2 to illustrate the principles of measurement involved, whereby, the value of an unknown resistance, capacitance, or inductance may be measured by comparison with a known standard resistance, capacitance, or inductance. This diagram shows an impedance network into which an unknown "X" may be connected in series with a known "Standard," a variable ratio arm "A," and a fixed arm "B." An a-c voltage of 1,000 cycles is connected across the bridge elements between points C and XD. An indicating device (headphones) is connected between points E and F to detect balance. Such a balance is indicated when a minimum signal is heard in the headphones, thus indicating that

Curtis

Electrolytic CONDENSERS

Announcing— NEW CATALOG

with a complete listing of
condensers

"STANDARD"
6 volt to 550 volt

"SUPER"
550 volts plus

"BLUE RIBBON"
630 volts

EXACT DUPLICATES

You can depend on
CURTIS CONDENSERS

*They Are Tested in Millions of Installations.
Satisfaction Guaranteed.*



Patent
No. 1950352

CURTIS CONDENSER CORPORATION

3088 WEST 106TH ST. CLEVELAND, OHIO


BRUSH *General Purpose* MICROPHONE

The Brush G2S2P sound cell microphone—an all around general purpose microphone for program—remote pickup and announcing work. Widely used in high grade public address installations. A typical sound cell microphone built to Brush's traditionally high mechanical and electrical standards. Non-directional. No diaphragms. No distortion from close speaking. Trouble-free operation. No button current or input transformer to cause hum.

Beautifully finished in dull chromium. Output level minus 70 D.B. Size 3 inches by 1 1/4 x 1 1/8 inches. Furnished complete, at no extra cost, with a Brush S-1 socket that facilitates easy installation. Full details will be found in Data Sheet No. 4 Free. Send for one.



BRUSH *Headphones*

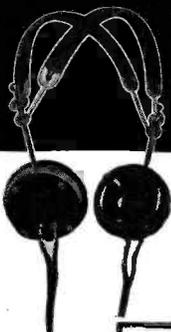

Meet every headphone requirement. Response 60 to 10,000 cycles. No magnets to cause diaphragm chatter. Specially designed cases minimize breakage. Light in weight. Only 6 oz., complete with headband and cords. A quality product at a low price. Details, Data Sheet No. 10. Copies on request. Send for one.

The **BRUSH** DEVELOPMENT COMPANY
PIEZO ELECTRIC CLEVELAND, O.

1882 E. 40th St.

MICROPHONES • MIKE STANDS • TWEETERS • HEAD PHONES • LOUD SPEAKERS



CLAROSTAT EXACT-DUPLICATE Volume Controls

FOR that fussy trade that insists on repairs that look as well as they work, you can bank on CLAROSTAT Exact Duplicate Controls obtainable through your local jobber, because:


★ EXACT DATA

New Guide contains most complete listing of exact duplicate controls covering requirements of all standard sets. No improvisations. No substitutes. No makeshifts. True replacements in each case.

★ EXACT UNITS

And that comprehensive data is backed by the largest line of exact duplicate controls, positively matching the initial equipment electrically and mechanically. The finished job looks right and acts right.

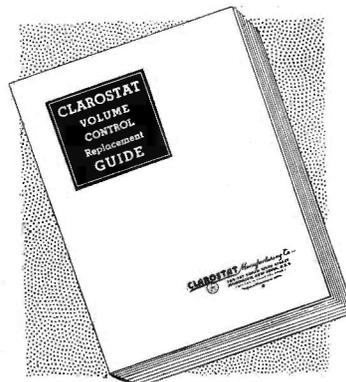Thousands of service men have recently tested and compared CLAROSTAT volume controls at our expense. Their reports enthusiastically endorse our products. Would you care to test a CLAROSTAT at our expense? If so, just say the word.



Write for Your Copy!

This big 80-Page Volume Control Replacement Guide will be sent free of charge. Listed units can be obtained through local jobber.

Or Meet us . . .

at the I.R.S.M. Show, in Booth 25, where we shall have an interesting display and story to tell.



**CLAROSTAT
MANUFACTURING CO., Inc.**

285-7 N. SIXTH ST. :: BROOKLYN, N. Y.

the ratio of arm "A" to arm "B" is identical to the ratio of the unknown "X" to the "Standard." By calibrating arm "A" the value of the unknown may be read direct. By properly choosing the values of the standards, the various ranges may be made multiples of the basic range of 1 to 10.

In the schematic circuit of the TMV-132-A bridge (Fig. 1) the 1,000-cycle energy is delivered to the bridge elements through the transformer (T-1) which is balanced capacitively to ground. This transformer isolates the bridge elements from the auxiliary equipment; that is, the power supply and oscillator, and insures the desired capacity-to-ground of the "known" and "standard" arms of the bridge.

The differential voltage, which indicates unbalance, is fed from the bridge elements through condenser C-4 to the pentode-grid of the 6F7. This unbalance-voltage is amplified in both sections of the tube and then made audible by headphones connected to the secondary of the output transformer (T-3), the primary of which is connected in the plate circuit of the triode section.

Three standards each of capacitance, inductance and resistance contained in the bridge elements are so arranged as to be selected by the range switch (S-1). Two ranges for each standard are obtained by means of the "High-Low" switch (S-4).

Arm "A" is the "Main Linear Control" (R-6) calibrated over the range from 1,000 to 10,000 ohms. Arm "B" is 10,000 ohms (R-8) for the low position and 1,000 ohms (R-7) for the high position of the "High-Low" switch. This arrangement, for a given standard, gives ratios of 0.1 to 1 for the low position and 1 to 10 for the high position. An overall range for one standard is, therefore, 1 to 100. By this arrangement the ratio of the bridge arm is never greater than 10, thus preserving sensitivity.

For inductance and resistance measurements, the "X" arm is the unknown element being measured, and the standard is selectable by the range switch. The ratio of the unknown resistance or inductance is to the standard resistance or inductance as arm "A" is to arm "B." The two phasing controls R-4 and R-5 can be placed in either the "X" arm or standard arm by means of the "R in X arm—R in Std. Arm" switch (S-3). The two rear sections of the range switch act as a double-throw switch to reverse arms "X" and the standard for capacity measurements, since the reactance of a condenser decreases as its capacity value increases. This per-

mits the use of the same linear scale for all measurements.

The oscillator which supplies the 1,000-cycle energy to the bridge elements consists of a type 76 tube and a transformer (T-2). The grid winding of the transformer is tuned to 1,000 cycles by the condensers C-7 and C-16 (Fig. 1). Self bias is obtained by the grid leak and condenser combination R-13 and C-5. A separate winding is provided to feed the energy to the bridge elements through transformer T-1.

A 6F7 triode pentode is used as a two-stage amplifier to provide adequate 1,000-cycle energy to the headphones for detecting balance. The signal from the bridge elements is amplified in the pentode section and then fed to the triode section through condenser C-12. The plate impedance of the pentode section is tuned to 1,000 cycles by L-4 and C-13, which permits maximum signal voltage

to appear on the triode grid. This arrangement provides high sensitivity, giving a sharp balance. The energy is then transferred to the headphones through transformer T-3.

The rectifier, a 25Z5, comprises two separate diodes of the heater-cathode type. It is employed in a voltage-doubler circuit and acts as a full-wave rectifier with one-half of the tube passing current to the load on each half of the a-c input cycle. During the period that one-half of the 25Z5 is rectifying the condenser across the other half is discharging through the conducting diode and the load. The voltage across the load is the sum of the d-c output voltage of the conducting diode and the discharge voltage of the condenser. C-8 and C-9 are the condensers which are alternately charging and discharging. C-10 and R-11 constitute a resistance-capacity filter. R-11 and R-12 form a bleeder circuit.

IMPACT EXCITATION GENERATOR

(Continued from page 411)

complished, but it should be noted that this can occur at several levels. The trimmer blades may all be down tight or at some higher position. Their relative position affects the high-frequency tuning range of the receiver and to obtain correct scale reading the proper level must be struck as well as alignment.

In passing it should be noted that misalignment of one of the i-f tuning stages will cause a loss of sensitivity which will appear as a uniform drop throughout the band. Inversely a receiver which has adequate sensitivity at some point in the band must have very good i-f tuning and will probably require only tracking of the r-f and oscillator circuits.

MISCELLANEOUS USES

Sometimes with multiband receivers one band only may be dead and the trouble may quite likely be caused by poor contact on the band switch. This can be checked by connecting the impact generator to the antenna and ground posts and rocking the band switch over the troubled position. If the defect is due to poor contacts, it will be evident because at some critical position all the contacts in circuit will "carry through." The impact generator, because it requires no tuning, eliminates any guess work about a signal coming through when the critical position of the contact switch is reached.

One common procedure used in running down off and on conditions is to prod the wiring and elements of the

receiver while it is in operation. Confusion often times results from inadvertent detuning of the incoming signal. The impact generator adequately solves this problem.

The same output posts and attenuation control of the impact generator supply an a-f signal which may be used in testing audio systems for gain, fading, etc. The maximum output is just sufficient to actuate a magnetic speaker directly.

The impact generator is an adequate demonstrator to show when a set is in need of tuning service. While repairing auto radios its small size and battery operation make it very useful for testing sensitivity, checking antennas and antenna tuning by the signal injection method.

AN INEXPENSIVE IMPACT GENERATOR


In Fig. 2 are given the circuit details of a practical impact generator designed around a high frequency buzzer. This buzzer consumes about 30 ma at 1.5 volts giving a battery life of several months. When using other buzzers it will be necessary to do some experimenting to find the correct value of battery voltage and the value of the shunt resistor. A smooth operating buzzer for which the correct values of battery voltage and shunt resistor have been chosen will yield a musical steady tone. A buzzer which makes slight mechanical sound is preferred. Shielding requirements are very adequately met by enclosing the components in a simple metal case as shown in Fig. 1.

INSURE LARGE RADIO PROFITS

WITH THE NEW 1937

Freed-Eisemann

FAMOUS SINCE BROADCASTING BEGAN

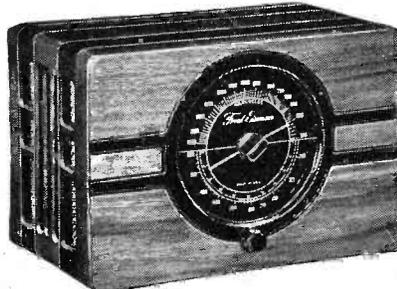

ONE OF
OUR MANY
OUTSTAND-
ING
VALUES—
LIST PRICE
\$17.95

STUDY THESE REMARKABLE FEATURES

- Model 50—Powerful 5 Tube Set
- 5 1/2", 4 color, illuminated Airplane Dial
- Handsome Rubbed Walnut finish 2 tone Cabinet
- Width 12", height 8", depth 7"
- Natural Tone Dynamic Speaker
- Works on either AC or DC current
- Self-contained aerial; no ground needed

AN EXCEPTIONAL VALUE FOR QUICK, PROFITABLE SALES

This model also available with extra band for shortwave police and amateur calls—List Price \$18.95

Other FREED-EISEMANN models are priced from \$12.50 to \$49.95

Prices on Export Models, for higher voltages and with long wave band on application
DISTRIBUTORS AND DEALERS—Write for catalog and wholesale prices on complete line.

FREED MANUFACTURING CO., INC.
44 West 18th Street, New York, N. Y.

Free Ticket
TO DETAILS ON THE BEST MONEY-
MAKING PROPOSITION OF THE YEAR

Yes, Sir! We would like to have full details on Belfone for Restaurants, Factories, Offices and the many other places it will sell on demonstration.

Name _____

Address _____

City _____

State _____

BELphone

A Complete Intra-
Department Com-
municating Sys-
tem for as little as

\$39.50

Mail Today!

Think of the places it can be used! Just flip a key and give orders—talk back and forth with other departments without wasted steps. No waiting for switchboard connection. No expensive rentals. Conversation clear and distinct. Units plug into light socket. Compact, neat, foolproof and simple to install. Costs remarkably little for multiple station systems. Belfone is so convenient—efficient—that a demonstration sells it.

Mr. Jobber: Here's a real proposition. Your Dealers are quick to see the profit possibility.

BELL Sound Systems, Inc.
61-62 East Goodale St.
Columbus, Ohio




**THERE'S
DOLLARS IN
DIVIDOHMS**

*says
Bill Fixit*

"I can't charge my customer for all the extra time it takes to shop around for an odd resistance value or a bleeder for a discontinued model. But I've solved that problem by always carrying a few OHMITE Dividohms. They save my time, and guarantee my customer a good job. Everybody wins!"

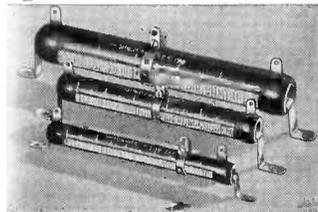Dividohm semi-variable resistors are made in all practical sizes and resistance values. Approximate values easily determined with patented "percentage-of-resistance" scale. Famous OHMITE Vitreous Enamel coated. Ask your jobber or get Catalog 14—FREE!




OHMITE
MANUFACTURING CO.

Makers of Resistors of
All Types

4827 Flourney Street
CHICAGO ILLINOIS

Hot off the Press

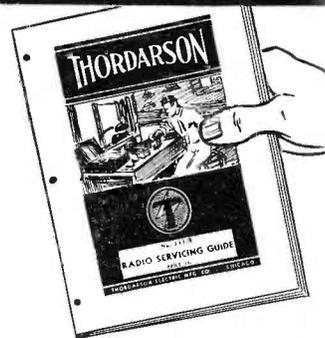THORDARSON'S BIG 1937 Radio Servicing Guide. Here are a few features which make this new — profusely illustrated guide, the **Biggest Bargain** you have seen. 52 pages of



tested ideas and suggestions. How to build a direct reading voltmeter. 4 pages of truly worthwhile auto installation hints. Hundreds of ideas—suggestions and helpful articles. Buy your copy from your parts distributor or write direct to the factory **today**. Only 15c post paid.

FREE — NEW FALL CATALOGS — FREE

Catalog No. 400—Complete line of Thordarson Transformers.
Catalog No. 500—Tru-Fidelity by THORDARSON.

THORDARSON ELECTRIC MFG. CO.
500 W. HURON ST., CHICAGO, ILL.
Demand 'Power by Thordarson'

ON THE JOB . . .

Calibrated Condenser for the Service Bench

A calibrated variable air condenser can be a very useful item of equipment on the Service Man's bench. Such a condenser can be used to match r-f coils, to determine the exact size of padding condenser required to make an oscillator track or to check the variable condensers in a set. These and a great number of other cases will come to the mind of the Service Man.

Such a condenser can be calibrated in terms of a known standard very accurately and easily. A calibrated standard is almost always a part of the laboratory equipment of a technical school or college. Usually it may be rented or borrowed.

The condenser to be calibrated must be of good mechanical construction and especially with good bearings. A transmitting condenser with double spaced plates and about 0.0005-mfd capacity is excellent. A wiping contact between rotor and frame is preferred to the pig-tail type. A good dial with an easy to read scale is essential. The condenser must be mounted in a shielded box or can. Tin cans such as are used in the kitchen for tea, sugar, etc., may be used to good advantage if they are sturdy. In any event, it is most necessary the mounting arrangement be such that the condenser cannot move with respect to the shielding or the dial. The writer used a wooden box lined with copper

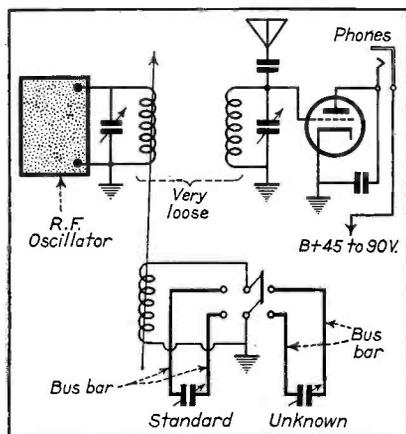


Fig. 1. Equipment layout.

and with a 1/4-inch thick aluminum panel on top. Mount a pair of good husky binding posts on the panel and ground the rotor to the shielding. The condenser is ready for calibration.

In calibrating the condenser by far

the best results will be obtained by using the substitution method. The writer used a modification of the usual substitution method which gave excellent results and was most accurate. The equipment layout is shown in Fig. 1. The r-f oscillator is tuned to zero beat with a convenient broadcasting station. This beat is heard in a detector, of the non-oscillating type, coupled just enough to easily hear the beat note. Normally a short piece of wire for an antenna will pick up enough of both oscillator and broadcasting station to be satisfactory. The oscillator should warm up for an hour or so to reach an equilibrium condition where it will not drift in frequency. It should, incidentally, be *unmodulated* and sufficiently strong so as not to lock into step with the broadcasting station near zero beat. Couple another coil to the oscillator tank and tune it with the *calibrated standard*. As this circuit comes into resonance a change in the pitch of the beat note will be observed. Adjust the coupling between this circuit and the oscillator so that, say, the beat changes about 20 cycles per division of the standard near the resonant point. When this condition obtains it will be easy to set the oscillator to zero beat with the broadcasting station by means of this separate circuit. If the circuits are judiciously placed and well grounded there will be little or no hand capacity. A little experimentation will provide this condition. To substitute the condenser to be calibrated for the standard a double pole double throw knife switch is used. It should be mounted solidly and the leads to both condensers be of the same length and of rigid wire such as bus bar.

To calibrate, merely introduce the standard into the circuit, tune to zero beat, note the capacity, substitute the condenser to be calibrated, retune to zero beat and note the dial setting. The capacity value of the standard will be the capacity of the condenser being calibrated for that dial setting. Calibrate about every ten divisions of the dial. More points will be necessary at the dial ends as the dial setting vs. capacity curve bends at each end. For most accurate results in using such a condenser only the range between 10 and 90 on a 100 division dial is used.

Some cautions are in order. Check and recheck your points. Do not disturb the detector tuning once it has been set. See that the headphone cord does

not change the beat note when moved around.

Plot the points you have taken on rectangular coordinate paper and draw a line through them. If the condenser

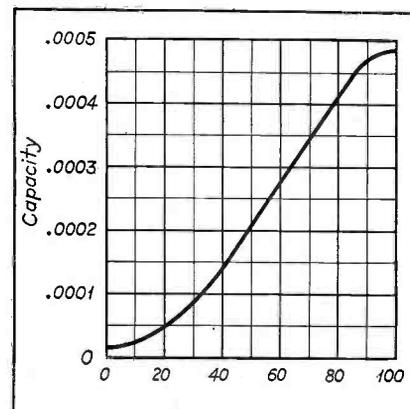


Fig. 2. Typical calibration curve.

is of the straight line capacity type this will be a straight line with a slight curve at each end. When these instructions are observed and reasonable care taken with the calibration the condenser will be within one percent or less of the standard and will hold this calibration to an exceptional degree for several years.

Robert C. Moody

Condenser Trouble

If you experience difficulty in having newly installed cartridge-type by-pass condensers open try giving the pigtails a little slack next time. Usually if pulled up snug while soldering the heat expands the wire and on cooling there is a tension on the wire which will more than likely cause the pigtail to pull apart from the foil in due time.

Hygrade Sylvania Service Hints

Removing Knobs

To remove spring-type knobs without marring the cabinet panel slip a length of shoe-string behind the knob. Pull the knob off slowly with the string, pressing against the panel with the thumbs for leverage if it sticks. The use of the string gives an even pull on the shafts.

Hygrade Sylvania Service Hints

Detecting Faded Colors

To assist in determining the color of a condenser or transformer lead that has been faded or is covered with pitch a hot soldering iron may be used. Rubbing the wire with the iron will cause the color to stand out more clearly.

Harvey Shock

ASSOCIATION NEWS . . .

INSTITUTE OF RADIO SERVICE MEN REPORTS

IRSM Board Meeting

The Board of Trustees of the Institute of Radio Service Men will hold its second regular meeting for 1936 on September 18 at the Hotel Pennsylvania, New York City.

At this time the Board will decide upon the next major activity for the Institute to engage upon, now that the Qualification Project for Service Men has been placed into capable hands.

It is anticipated, too, that the Board will take action at its New York meeting on the matter of changing the rules governing admission to the Institute, and that very shortly it will be necessary for an applicant for membership in the Institute to first have fulfilled the requirements of the Qualification Project.

New York Trade Show

The 1936 New York Radio Trade Show, conducted by the Institute of Radio Service Men, and staged on the Mezzanine Floor of the Hotel Pennsylvania, will be one of the largest displays of radio parts and accessories shown in the eastern metropolis. Between 60 and 70 booths will be occupied (as of August 31).

The opening hour of the show is 2:00 o'clock, Friday, September 18, and the entire afternoon will be devoted to exhibits—no lectures are scheduled for the afternoon period of the first day.

Entrance to the exhibition hall will be by way of the stairway at the east end of the hotel lobby. Elevator service to the Mezzanine—or at least to the Trade Show—will not be available, except for service purposes.

On Saturday and also on Sunday the Trade Show doors will be open at noon, which will give the registrants plenty of time to view the exhibits before the technical lectures begin.

Although no complete program of events is available at this time, it is understood that Mr. C. Herbst, RCA service engineer, will describe technical receiver advances on September 18. Drs. V. K. Zworykin and G. A. Morton will demonstrate the electron multiplier the same evening. On Sunday evening Mr. R. G. Herzog, editor of *SERVICE*, will discuss noise reducing antennas.

The Trade Show will close at 11:00 p.m., Sunday, September 20.

Forest Arnold, Prog. Com.

IRSM Qualification Project

Marked interest has been shown in the Qualification Project developed by the Institute of Radio Service Men and placed into the hands of especially formed bodies for effectuation. The National Board of Radio Service Standards reports that the applications to take the examinations have been coming into the office at the rate of between 30 and 40 a day, from a relatively small preliminary mailing of the details of the Project.

The returns from the restricted mailing mentioned above have given the office staff of the National Board of Radio Service Standards an opportunity to devise methods

IRSM INVITATION

THE entire radio trade is cordially invited to attend the Fourth Annual New York Convention of the Institute of Radio Service Men to be held on the Mezzanine Floor of the Hotel Pennsylvania in New York City, September 18, 19, 20, 1936.

NO ADMISSION CHARGE!

of handling the routine in an efficient manner.

A general announcement of the entire Project was being prepared for putting into the mail beginning September 4 and continuing until more than 14,000 had been sent forward.

Cleveland Chapter

As per schedule the Cleveland chapter of the IRSM held their annual picnic on August 23. Both the Akron and Cleveland chapters attended with their wives and children.

The Cleveland chapter won the ball

game 13 to 0. Seven and a half barrels of beer, eighteen cases of pop, ten gallons of ice cream and oodles of scotch were consumed during the frolic which lasted till well after midnight.

The dates of the Cleveland Trade Show have been changed to November 1 and 2, to be held at the Hotel Cleveland in the grand ballroom.

A special feature of the show will be a telephoto demonstration arranged through the courtesy of the Acme News Service and the N.E.A. Service.

L. Vangunten, Secretary

SOUTHERN MINNESOTA RADIO ASSN.

The annual convention of the Southern Minnesota Radio Association will be held in Rochester, Minn., September 26 and 27. All radio Service Men, dealers and amateurs are invited. Numerous prizes have been donated and will be distributed among those attending the convention.

RADIO SERVICE ASSN. OF CALIFORNIA

Dr. Lester Reukema was the guest speaker at the August 17 meeting of the Radio Service Association of California. The meeting was held at the headquarters of the association, 921 Harrison St., Oakland, Cal. Mr. H. A. Schmidt, the association's president opened the meeting.

LIST OF EXHIBITORS

Fourth Annual IRSM N. Y. Convention, September 18, 19, 20, 1936

<i>Exhibitor</i>	<i>Booth No.</i>	<i>Exhibitor</i>	<i>Booth No.</i>
Aerovox Corp.	56	National Union Radio Corp. of N. Y.	15
All-Wave Radio	58	Ohmite Manufacturing Co.	33
American Microphone Co.	32-R	Operadio Manufacturing Co.	13
American Phenolic Corp.	32-L	RCA Manufacturing Co., Inc.	70 & 71
American Radio Hardware Co., Inc.	57	The Radiart Corp.	24
Amperite Corp.	50	Radio City Products Co., Inc.	34
Arcturus Radio Tube Co.	12	Radio Retailing	66
Astatic Microphone Laboratory, Inc.	47	The Radiotechnic Laboratory	5-R
Atlas Resistor Co.	69	Radio Today	54
Bendix Products Corp.	43 & 44	Radio Weekly	—
D. R. Bittan Sales Co., Inc.	31-33	Raytheon Production Corp.	36
The Brush Development Co.	45	Readrite Meter Works	39
BRYAN DAVIS PUBLISHING Co., Inc.	48	John F. Rider	6
B. O. Burlingame	30	Roye Sales Agency	2-4
Centralab	42	W. S. Scharp	42-47
Cinaudagraph Corp.	21	F. Edwin Schmitt	61
Clarostat Manufacturing Co., Inc.	25	SERVICE	48
Clough-Brengle Co.	14	Shure Brothers	68
Cooper-DiBlasi	10	Simpson Electric Co.	18 & 19
Cornell-Dubilier Corp.	7	Paul C. Smalley	16 & 17
Dale Parts, Inc.	51	Solar Manufacturing Corp.	9
The Dale Radio Co., Inc.	52	Sprague Products Co.	49
Tobe Deutschmann Corp.	28 & 29	Standard Transformer Corp.	2
Electrad, Inc.	41	H. A. Steinberg	7
Electronic Laboratories, Inc.	4	Supreme Instruments Corp.	30
John M. Forshay	1	Technical Appliance Corp.	5-L
Sam Harper	5-R & 14	Thordarson Electric Manufacturing Co.	10
General Transformer Corp.	31	Tilton Electric Corp.	65
The Hickok Electrical Instrument Co.	1	Transducer Corp.	55
Hygrade Sylvania Corp.	37 & 38	The Triplett Electrical Instrument Co.	20
International Resistance Co.	11	United Transformer Corp.	53
Jefferson Electric Co.	40	Utah Radio Products Co.	35
J. F. Distributing Co.	23	Ward Leonard Electric Co.	22
P. R. Mallory & Co., Inc.	16 & 17	The Webster Co.	46
Meissner Manufacturing Co.	3	Weston Electrical Instrument Corp.	8
Micamold Products Co., Inc.	67	Wholesale Radio Service Co., Inc.	26 & 27



THE Group Subscription Plan for SERVICE enables a group of service men, dealers or jobbers to subscribe at one-half the usual yearly rate. The regular individual rate is \$2.00 a year. In groups of 4 or more, the subscription rate is \$1.00 a year. (In foreign countries, \$2.00.)

The service departments of thousands of radio dealers, independent service men, etc., have used this Group Plan for years, in renewing their subscriptions to SERVICE.

Each subscriber should print his name and address clearly and state his occupation—whether a dealer, jobber, independent service man, service organization, etc.

Remember this
when *Your* Subscription Expires

(Service)

BRYAN DAVIS PUBLISHING CO., Inc.
19 East 47th Street, New York, N. Y.

HIGHLIGHTS . . .

RCA SERVICE MEETINGS

Announcement of a series of Service Men's meetings was made by F. B. Ostman, RCA Victor Service Manager. Beginning Sept. 14 the lecture meetings will take place in over 150 cities throughout the country and come to a close on Oct. 23.

As in the past the meetings will be conducted under the joint auspices of the RCA Victor Service Department and the radio parts wholesalers who will announce the date and meeting place for each locality.

BRIGGS AND STRATTON MANUAL

Briggs & Stratton Corp., Milwaukee, Wis. manufacturers of gasoline motors, have just issued a sales manual and instruction book on the company's new 6-volt, 200-watt "Power-Charger" battery charging unit and lighting plant. The story of the advantages of electricity provided by gasoline motors in the home and on the farm has been told in a series of cartoons, leading into an analysis of the portable power and light plant and the possible markets into which it will go. Operating instructions and repair information and parts lists are included in a separate section illustrated with line drawings.

RAYTHEON SALES MANAGER

Mr. D. T. Schultz, vice-president and treasurer of Raytheon Production Corp., announces the appointment of Mr. E. S. Dietrich as manager of distributors' sales. Mr. Dietrich's headquarters will be at the New York Office 420 Lexington Ave. He will operate under the general supervision of the general sales-manager, Mr. E. S. Riedel, of the Chicago office 445 Lake Shore Dr., Chicago.

CORNELL-DUBILIER CATALOG

A special catalog has been issued by the Cornell-Dubilier Corp. covering the reduced prices recently announced for their line of "Dwarf-Tiger" condensers.

This catalog lists the entire line of this series, together with catalog numbers, and shows both the old and new price schedules. This catalog, No. 132A, will be mailed to those requesting it from the Cornell-Dubilier Corporation, 1000 Hamilton Blvd., South Plainfield, N. J.

NATIONAL UNION RADIO LOG

A sixteen page radio log has been released by National Union Radio Corp. for use as promotional material by radio Service Men and retail radio dealers.

Contents include listings of all broadcasting stations in the United States and throughout the World, more than fifty photos of radio stars, world distance charts for the short-wave enthusiast, information as to where to write for short-wave verifications of interest to the DX fan and a wave length frequency chart.

A feature of particular interest to radio retailers and Service Men is the fact that the log provides for a choice of complete outside back cover advertisements for the dealer, thus making the publication appear to be his own log.

Complete details may be obtained from the National Union Radio Corp., 570 Lexington Ave., New York City.

ATLAS RESISTOR CATALOG

The Atlas Resistor Co. have published their 1937 catalog, No. 7, describing their line of wire-wound resistors and voltage dividers. Very attractively prepared, it will prove of definite value and interest to all service men.

Copies of the catalog may be had by writing to the Atlas Resistor Co., 423 Broome St., New York City.

AMPERITE DECALCOMANIA

Amperite Co. offers the Service Man a useful help in the form of a decalcomania. Measuring over 9" by 5" and finished in brilliant gold, red, black and white this



window sign should attract business during the coming active season.

The decalcomanias may be obtained directly from Amperite Co., 561 Broadway, New York City.

WEBSTER CATALOG

The Webster Co., 3825 W. Lake St., Chicago, have their catalog, No. 736, describing their line of synchronized sound systems and accessories, ready for distribution among the trade.

RADIO RECEPTOR BULLETIN

The Radio Receptor Co., 106 Seventh Ave., New York City, have released their latest bulletin, No. 3013. The bulletin, which may be obtained upon request, describes their series 7 dynamic microphones and contains much material of interest for everyone engaged in public address sales and installations.

HYGRADE SYLVANIA ENLARGES

The new Salem, Mass. plant of the Hygrade Sylvania Corp., is 400 feet long and 80 feet wide aside from the wings containing quarters for engineering research, restaurant and recreation rooms. The total floor space is 91,000 square feet.

TRANSMITTER GUIDE FOR AMATEURS

The Amateur Press, 1300 W. Harrison St., Chicago, have released a pamphlet called "Progressive II." This pamphlet is intended to be a supplement to the Progressive Transmitter Guide for Amateurs recently published.

Copies of the guide or supplement may be obtained from the Amateur Press or from the General Transformer Corp., 500 Throop St., Chicago.

FRANKLIN SALES MANAGER

Franklin Transformer Mfg. Co., 607-22nd Ave. N. E., Minneapolis, Minn., announces the appointment of H. Lawrence Mills as sales manager of their transformer division. Mr. Mills has had a varied experience in radio and allied fields.

There will be no great change in the sales policies of the company for the present. However, there will be numerous additions and improvements in the Franklin transformer line.

STANCOR TRANSFORMER GUIDE

The Standard Transformer Corp., 866 Blackhawk St., Chicago, Ill., is offering the Service Man a card file replacement guide. The guide consists of a set of printed cards, filed in alphabetical order according to the name of the receiver, giving replacement data on practically every commercial receiver ever built. Information on audio transformers and chokes is also included.

The card file may be obtained by any Service Man for 25c or by returning a Stancor box top to the manufacturer.

SPRAYBERRY BOOKLETS

The Sprayberry Academy of Radio is offering several booklets extolling the advantages of enrolling in the Academy. The booklets explain the Sprayberry course and give a summary of each lesson. Numerous testimonials from former students as well as letters of praise from successful men in the industry are included.

The booklets may be obtained by writing to the Sprayberry Academy of Radio, 2548 University Pl., N. W., Washington, D. C.


ALADDIN DATA SHEET

Aladdin Polyiron Data Sheet 536 is available to Service Men and dealers who write to the Aladdin Radio Industries, Inc., 466 W. Superior St., Chicago. The 8-page bulletin enumerates representative products produced in the Aladdin Radio Industries line during the last few years.

UNIT REPRODUCERS N. Y. OFFICE

In order to better handle the demands of New York and nearby manufacturers, jobbers, dealers and Service Men the Unit Reproducers Manufacturing Co., 999 E. Main St., Rochester, N. Y., have established a New York City office at 1472 Broadway.

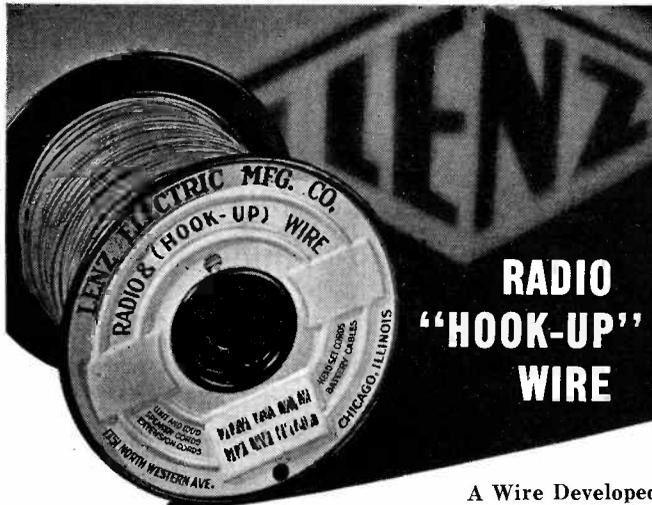The Unit Reproducers Co. manufactures a complete line of magnetic pickups and permanent magnet dynamic speakers.



RADIO "HOOK-UP" WIRE

LENZ R.F. Hookup Wire Dielectric Characteristics At 70 F. 50% RH.

Power Factor—One-half of one per cent at 25 meters (12 megacycles), completely immersed in mercury.

Phase Angle—18 degrees and seven minutes.

Insulation Resistance—33,000 megohms per foot at 400 volts DC, completely immersed in mercury.

Capacity (to ground)—22 MMF. per foot at 25 meters (12 megacycles).

AC voltage breakdown—1600 volts per foot, completely immersed in mercury.

At 120 F. 90% RH.
Power Factor—1% at 25 meters (12 megacycles), completely immersed in mercury.

Capacity (to ground)—28 MMF. per foot at 25 meters (12 megacycles).
Moisture Absorption—less than 1% by weight.


A Wire Developed Especially for
LOW LOSSES at High Frequencies!

Conductors supplied in several sizes either solid or stranded. Insulation pushes back easily without adhering to the conductor. Insulation impregnated in a high-resistant, low-loss, moisture resisting compound. Specifically designed for RF circuit.

Handled by Dealers and Jobbers
All Over the Country



1751 NORTH WESTERN AV.
CHICAGO ILLINOIS

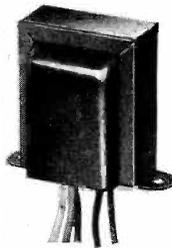

At What Voltage does it Break Down



You can make your own check test . . . but you can be just as safe if you tell your jobber, I want

HALLDORSON TRANSFORMERS Vacuum Sealed

Halldorson transformers are stocked by leading part distributors everywhere. It is no longer necessary for radio service dealers to take chances with transformers. For the same price you can get the quality transformer that for years has been used as standard equipment in leading American made radio sets.

The vacuum-seal safeguards against failure due to moisture.

See Your Jobber. Write

THE HALLDORSON COMPANY,
4500 Ravenswood Ave., Chicago, Ill. S-9

Please send me your new Catalogue.

(Name)

(Street)

(City)

(State)



MORE EXPENSIVE TO MANUFACTURE

LESS FAILURES

NO INCREASE IN PRICE

Get a Political Job It's Easy Money

STENTORIAN SOUND AMPLIFIER NUCLEUS



The hottest political campaign in years is directly ahead! Political organizations of all parties will need public address systems with a "Stentorian" tone. Dealers and Sound engineers can make good quick profit in selling or renting sound amplifiers built the "Stentorian" way.

G.T.C. Nuclei furnished for stationary and mobile outfits. Easy to understand directions for wiring supplied with each Nucleus. Power supply units are the HEART—the very nucleus of Sound Amplifiers. Each "Stentorian" NUCLEUS includes matched power transformer, chokes, audios, outputs with neat black wrinkle finished chassis, lettered terminal strips, marked tube sockets. "Stentorian" Sound Amplifiers provide wide tone range and good clear sound coverage for convention halls, auditoriums, stadiums, refectories, athletic fields, ballrooms, night clubs, taverns, lodge halls, banquet programs, political rallies, office and factory call systems, truck or auto advertising for concession barkers, race track announcements, depot train call systems, and the like.

The "Stentorian" way is the most economical way for Quality Sound Amplifiers.

GENERAL TRANSFORMER CORPORATION
(Manufacturer of Replacement Units)
502 S. Throop Street
Chicago, Ill.

Free for the Asking!

Interesting illustrated bulletin on "STENTORIAN" Sound Amplifier. Nuclei and name of distributor nearest you.

Mr. Service Man, can you fix my--er--er RADIO



Yes, indeed you can and because you do good work and use dependable Ward Leonard replacement resistors, you give satisfaction, and she will call on you again for your services. That is how a permanent profitable radio business is built. The Radio Service Bulletin 507A shows the Ward Leonard Line and gives prices. Be ready when she calls. Send for it today.



WARD LEONARD ELECTRIC CO.

South Street, Mount Vernon, N. Y.

Please send me FREE Bulletin 507A.

Name
Street
City State
Jobber

THE MANUFACTURERS . . .

MALLORY CONDENSER REPLACEMENTS

P. R. Mallory and Co., Inc., Indianapolis, Ind., feature a line of 69 general replacement condensers which they claim will cover complete replacement requirements in all of the commercial receivers now in use. The new units are small in size, surge-proof, oven-tested and are sealed in metal (humidity-proofed).

Complete information concerning this line may be obtained from the manufacturers.

ACOUSTI-REFLEX SPEAKER CABINET

The Acousti-Reflex speaker cabinet, an Operadio development, is designed to reduce feedback, increase the efficiency of the speaker, reinforce bass response and present a neat appearance.

The cabinet accommodates only 12" speakers and contains a built-in exponential chamber which takes the sound from the rear of the speaker cone, expands it in the normal manner and projects it out in front to augment the sound generated at the front of the cone.

The cabinet is built of seasoned plywood




heavy enough to eliminate vibrations.

Catalog 10-E, giving full particulars, is obtainable by writing to the Operadio Manufacturing Co., St. Charles, Ill.

FREED-EISEMAN FE-60

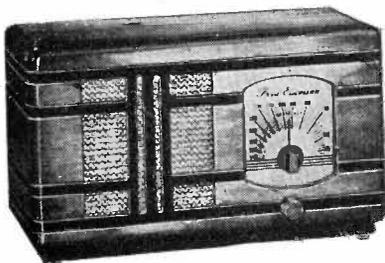The Freed-Eiseman Model FE-60 is an a-c, d-c, 6-tube superheterodyne covering the American broadcast band and the police calls within the tuning range from 540 to 1740 kc. The set has a multi-colored illuminated tuning scale and is mounted in a hand-polished, two-tone, walnut-veneered and gumwood cabinet.



The FE-60 is manufactured by the Freed Manufacturing Co., Inc., 44 W. 18 St., New York City.

TRIAD 25B5 AND 25N6G

The Triad Manufacturing Co., Inc., Pawtucket, R. I., have added a new member to the Triadyne family with the announcement of the 25B5 and its octal base counterpart the 25N6G. The new tube is intended for use as an output for a-c, d-c and transformerless a-c receivers. A somewhat greater output is afforded than was



previously obtainable with the type 43 tube.

Characteristics and other information can be obtained from the manufacturer.

SUPREME 1937 LINE

The Supreme Instruments Corp., Greenwood, Miss., have announced their series 500 line of test apparatus for 1937. Included in the new line are a model 545 "Cathoray Oscilloscope," a model 555 "Diagnomoscope" and a model 565 "Carrier Shift Indicator."

Additional information can be obtained directly from the manufacturer.

NEW SPRAGUE CONDENSERS

Working on the premise that condenser failures caused by humidity could be eliminated, the Sprague Products Co., North Adams, Mass., announces a specially treated tube and sealing compound. This humidity-proof tube construction is used in the manufacture of the entire Sprague line of paper, foil and gauze condensers.

Since the change is internal, the new Sprague units may be identified by a red dot imprinted upon the base to differentiate them from former Sprague units of the same general type and rating.

MICAMOLD JOBBERS LINE

Micamold Products Corp., Brooklyn, N. Y., will shortly announce a jobbers' line of paper, mica and dry electrolytic condensers and an assorted line of carbon and wire-wound resistors. Included in the line will be the Micamold patented bakelite-molded paper condensers and the Micamold patented bakelite-molded resistors.

Mr. E. B. Tyler, formerly with Polymet Mfg. Co., is in charge of the new line as general sales manager. He will be assisted by Mr. Nat Pomeranz.

FOUR-WAY MICROPHONE

Shure Brothers, 215 W. Huron St., Chicago, Ill., announce a new type microphone unit available in the general purpose crystal, in the communications type crystal, and in the carbon types.


A single unit provides 4-way utility. By means of an adapter on the base of the unit, the handle and the microphone may be removed to become a hand microphone or replaced on to the base to become a desk microphone again. A slot is provided in the adapter to accommodate the cable. The microphone may be removed from the handle and mounted directly on to a floor-stand or spring suspended in a carbon ring.

TRIPLETT VACUUM-TUBE VOLTMETER

The Triplett Model 1250 is a self-calibrating vacuum-tube voltmeter with accuracy independent of changing tube values.

The instrument will answer many purposes in measuring low voltages, both in a-c and d-c, without current drain.

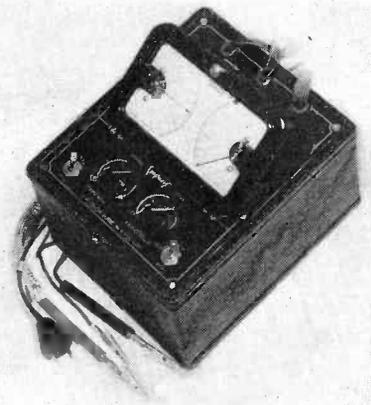Model 1250 has a twin instrument (tilting type); one of the instruments is a



sensitive galvanometer that indicates when the bridge is in balance; the other is a three-range voltmeter with linear scales reading peak voltages. Ranges are 2.5, 10 and 50 volts.


CORNISH NOISE-MASTER ANTENNAS

Cornish Wire Co., 30 Church St., New York City, announces material advances in their Amy, Aceves and King licensed



"Noise-Master" antenna. Several models are available to suit all sets and locations. Dealers and Service Men are invited to request information covering the 1937 Cornish wire products.

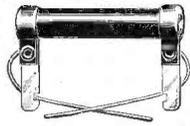
ATLAS PRODUCTS
TOLERANCE 2%
LONG LIFE
ACCURATE
SAFE WATTAGE RATING



ATLAS RESISTOR CO.
423 Broome St., New York, N. Y.

WRITE FOR NEW 1937 CATALOG

SELECTED for DISTINCTIVENESS

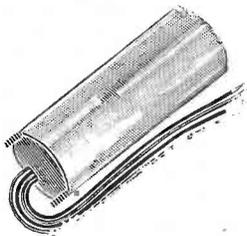

Illinois Electrolytic
 Condensers.
 Hermetically Sealed.
 Assured of Quality and
 long life. . . . Guarantee.
 The Condenser with a
 reputation.
 We invite your inquiries.
 Write today.

ILLINOIS CONDENSER CO.

Dept. B, 3252 NORTH AVENUE, CHICAGO, ILL.



**Ken-Rad
 Radio Tubes**


Ken-Rad Radio Tubes are made to give clear, dependable reception. They satisfy customers and build good will for dealers. Write for full information.

Genuine Glass or All-Metal Radio Tubes

KEN-RAD TUBE & LAMP CORPORATION, Inc.
 Owensboro, Ky.

Also Mfrs. of Ken-Rad Incandescent Electric Lamps

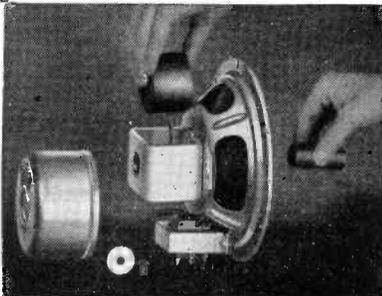**PERFORMANCE PLUS THIS
 "CHANGEABLE"
 FEATURE!**



Hear these new OXFORD "Changeable Field" Dynamic Replacement Speakers! Then see how easily and economically you can change the field to fit the job. Universal transformer matches any tube. Voice coil remains centered. Ideal for Service Men and Amateurs! Available in 5", 6", 8" and 11" models.

Ask your Jobber or write for Bulletin 361A.

EXPORT DIV.
 15 Laight St.
 New York, N. Y.
 Cable: 'ARLAB'


OXFORD-TARTAK
 RADIO CORPORATION

915 W. VAN BUREN ST. • CHICAGO, U. S. A.



AMPERITE presents...

The NEW RBHn VELOCITIES

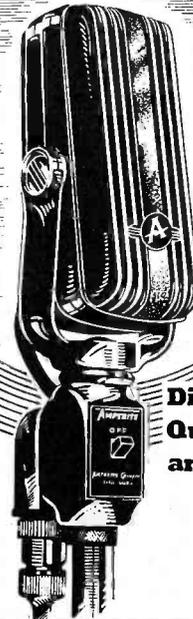

**Distinguished in
 Quality, Design,
 and Construction**

Embodies the latest technique in microphone design.

Compact. Streamline. Modern. All cast case achieves maximum ruggedness. Fitted with Switch, and new Cable Clamp.

Models RBHn (High Impedance); RBMn (200 ohms).

\$42.00 List

With built-in Cable Connector having locking device. \$44.00 List.

featuring...

NEW! Models RBSn, RSHn — EXCELLENT ALL-AROUND MICROPHONES FOR SPEECH and MUSIC. Slightly lower output and frequency range than above. APPEARANCE SAME AS ABOVE.

\$32.00 List

For switch, add \$1.00 list. For cable connector, add \$2.00 list.

1. Output increased 6 DB.
2. Triple shielded — against all RF or magnetic fields, entirely eliminating hum pickup.
3. Eliminates feedback troubles.
4. Excellent for close talking and distant pickup.
5. Acoustically designed to eliminate any possibility of cavity resonance.

(Finishes: All microphones have the new Standard Gunmetal Finish. Chrome finish, extra, \$1.00 list.)

FREE!

TO DEALERS AND SERVICE MEN:
 A Striking Window Decal, advertising your SOUND SERVICE, and displaying the New AMPERITE VELOCITY. Write for it now!



Now! An Amperite Velocity within the means of everybody!

A specially designed microphone built to Amperite standards, which can be used for both speech and music. No peaks. Flat response. Triple shielded. Shock absorber. Swivel bracket.

Models RAL (200 ohms); RAH (2000 ohms)

\$22.00 List

AMPERITE Co. 561 BROADWAY NEW YORK

Cable Address: Alkem, New York

AMPERITE Velocity MICROPHONE

FOR LOWER PRICES, GREATER VALUE, FASTER SERVICE ORDER FROM ALLIED



**YOU NEED THIS
 NEW 1937 CATALOG**

Radio's newest, most complete supply guide, 152 pages packed with thousands of exact duplicate and replacement parts; dozens of new test instruments; All-Wave, Dual-Wave, and Short-Wave sets and kits; Sound equipment; books; tools, etc.—at lowest prices. Fast, reliable service. Avoid costly delays—save time and money at ALLIED. Send coupon for Free Catalog.

ALLIED RADIO
 833 W. Jackson Blvd.
 Chicago, Ill.

Send me Free 1937 ALLIED Catalog.

Name: _____
 Address: _____

Dept. 19-J



TRIAD




THE QUALITY NAME IN RADIO TUBES


TRIAD MANUFACTURING CO., Inc.

PAWTUCKET, RHODE ISLAND

SERVICEMEN!

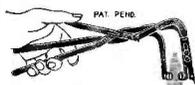

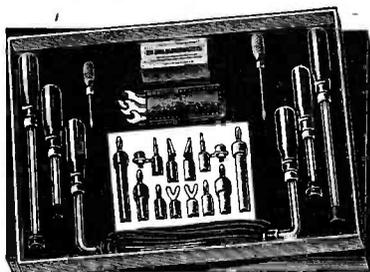A special kit of tools and accessories, including the famous ARHCO metal tube extractor! No more burns from hot tubes or struggling in tight corners. Net \$3.75 complete to servicemen only during special introductory offer. Regular price \$8.50. Order from your dealer, distributor or direct. Offer expires Nov. 1st, 1936. Order your kit now!



Visit Booth 57—New York IRSM Show
AMERICAN RADIO HARDWARE CO., INC.
 476 BROADWAY NEW YORK CITY

LOW WHOLESALE PRICES GET THIS FREE CATALOG!



• Over 10,000 items in this big catalog including radio receivers, nationally known radio parts and broadcasting equipment. A catalog of great value to dealers and service men offering the best in radio at low wholesale prices. Write today for your FREE copy of this big catalog. Get on the list to receive monthly "Hot Shot" Bulletins.

BURSTEIN-APPLEBEE CO.

1012-14 McGee St.

Kansas City, Mo.


INDEX TO ADVERTISERS

A	G	R
Aerovox Corp. 443	General Distributing Corp. 452	RCA Mfg. Co., Inc. Fourth Cover
Allied Radio Corp. 449	General Electric Co. 393	Racon Elec. Co. 451
American Radio Hdwe. Co. 450	General Transformer Corp. 447	Radiart Corp., The. 443
American Television & Radio Co. 452	Gernsback Publications, Inc. 451	Radolek Co. 451
Amperite Co. 449	H	Raytheon Production Corp. 394
Arcturus Radio Tube Co. 435	Halldorson Co., The. 447	Readrite Meter Works. 405
Atlas Resistor Co. 449	Hickok Elec. Instrument Co. 452	Rider, John F. 431
B	Hygrade Sylvania Corp. 427	S
Bell Sound Systems, Inc. 441	I	Solar Mfg. Corp. Third Cover
Brush Development Co., The. 439	Illinois Condenser Co. 449	Standard Transformer Corp. 431
Burstein-Applebee Co. 450	International Resistance Co. 400	Supreme Instruments Corp. 419
Burton-Rogers Co., The. 443	J	T
C	Jefferson Elec. Co. 427	Technical Appliance Corp. 433
Centralab 435	K	Thordarson Elec. Mfg. Co. 441
Cinaudagraph Corp. 451	Ken-Rad Tube & Lamp Corp., Inc. 449	Tobe Deutschmann Corp. 403
Clarostat Mfg. Co., Inc. 439	L	Transformer Corp. of America. 433
Clough-Brengle Co., The. 401	Lenz Elec. Mfg. Co. 447	Triad Mfg. Co., Inc. 450
Continental Carbon, Inc. 425	Mc	Triplett Elec. Inst. Co. 402
Cornell-Dubilier Corp. 404	McMurdo Silver Corp. 437	Tung-Sol Lamp Works, Inc. 399
Cornish Wire Co., Inc. 395	M	U
Curtis Condenser Corp. 439	Mallory & Co., Inc., P. R. Second Cover, 409	United Transformer Corp. 420
E	N	Utah Radio Products Co. 437
Electrad, Inc. 406	National Carbon Co., Inc. 429	W
Electro-Voice Mfg. Co., Inc., The. 437	National Union Radio Corp. 429	Ward Leonard Elec. Co. 447
F	O	Ward Products Corp. 451
Fox Sound Equip. Corp. 451	Ohmite Mfg. Co. 441	Webster-Chicago 425
Freed Mfg. Co. 441	Operadio Mfg. Co. 452	Weston Elec. Inst. Corp. 410
	Oxford-Tartak Radio Corp. 449	Wholesale Radio Service Co. 417
	P	Wright-DeCoster, Inc. 443
	Precision Apparatus Corp. 397	Y
		Yaxley Manufacturing Division Second Cover, 409

THE FOX ONE-PIECE

METAL DIAPHRAGM

The Standard A, only .002 inches thick (H.D. .003"), combines extreme hardness with great elasticity and is unaffected by temperature or humidity so that its performance is constant and dependable. Withstands extreme wattage, and special processing prevents internal strains and stresses. The voice coil is wound directly on the diaphragm, eliminating broken wires and distortion caused by loose diaphragm coils. Write for catalog sheets and prices.

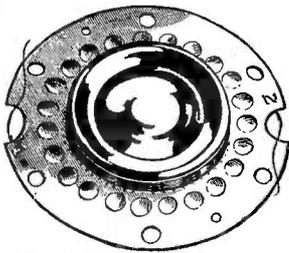

FOX SOUND EQUIPMENT
CORP.

3121 Monroe St. Toledo, O.

GET ON THE P. A. BAND WAGON
TO MORE BUSINESS AND
GREATER PROFITS WITH THE
CINAUDAGRAPH
Magic Magnet Speaker

CINAUDAGRAPH CORPORATION

Speaker Division—Dept. A.
STAMFORD, CONNECTICUT, U. S. A.

RACON

6 FOOT
UNBREAKABLE
TRUMPETS

"The World's Finest"

Demountable into three sections. Made of RACON Acoustic Storm Proof material, reinforced throughout, and guaranteed unbreakable. The ultimate in trumpet design, highly efficient and able to stand the roughest treatment.

Send for RACON catalog S-9 describing the complete line of RACON Horns, Electro-dynamic Units, and Acoustical Sound Projectors.

RACON ELECTRIC COMPANY, INC.
52 EAST 19TH STREET NEW YORK CITY



AMERICA'S NEWEST
AERIAL IDEA!

THE BUGGY-WHIP

Most Practical
No Drilling
Quick Installation
Chrome Finish


NEW WARD PRODUCTS

Fish-Pole Antenna
Improved Running Board Aerials
Microphone Stands
Sound Systems—Auto Radio Aids

Displayed at IRSM Show


WARD
PRODUCTS CORP.

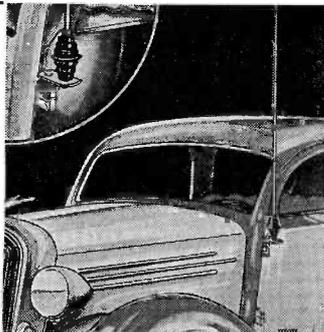In Canada Atlas Radio Corp.
Toronto, Ontario



To WARD PRODUCTS CORP.
WARD BLDG., Cleveland, Ohio
Please send new catalog

Name
Address

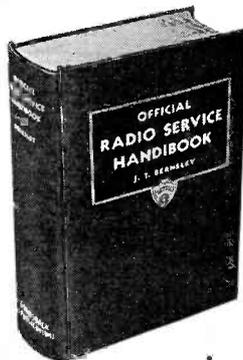

JUST OUT

OFFICIAL RADIO SERVICE HANDBOOK

OVER 1,000 PAGES

OVER 1,000 ILLUSTRATIONS

Published only a few weeks ago, the OFFICIAL RADIO SERVICE HANDBOOK by Bernsley, is the most modern, up-to-the-minute volume on radio servicing. Contains over 1,000 PAGES filled with vitally important service data—over 1,000 illustrations.

OVER 250 PAGES OF OPERATING NOTES

The section on Operating Notes contains valuable information supplied from personal notes of hundreds of Service Men for over a thousand manufactured receivers. This section alone should be priced more than the entire volume.

Here are other highlights of the OFFICIAL RADIO SERVICE HANDBOOK: **CIRCUIT THEORY AND ANALYSIS**—Circuit Fundamentals, Tuning Circuits and Aligning Data, Volume Control, Tone Control, A.V.C., Resonance-Indicator Circuits, A. F. Amplifier Systems and Power Supplies, Speakers, Pickups, Phono-equipment, Commercial Receivers; **SERVICING EQUIPMENT**—Fundamentals of Test Instruments, Commercial Equipment, Cathode-Ray Oscillograph, Building Test Instruments, Localizing Trouble, Short Cuts, Unusual Servicing Experiences; **STANDARD AND SPECIALIZED RECEIVER AND INSTALLATION DATA**—All-Wave Receivers, Auto-Radios, Noise Interference; **MODERNIZATION AND CONVERSION DATA**—Receiver Conversion Work; **SOCIAL AND ECONOMIC PROBLEMS OF THE SERVICEMAN**—Improving Knowledge and Technique, Uplifting the Profession; **OPERATING NOTES FOR STANDARD RECEIVERS**.

Order your HANDBOOK today—use the coupon for convenience.

GERNSBACK PUBLICATIONS, Inc., 99 Hudson Street, New York, N. Y.

GERNSBACK PUBLICATIONS, Inc.
99 Hudson Street, New York, N. Y.

SV-96

Gentlemen: Enclosed please find my remittance of \$4.00, for which send me immediately, POSTPAID, one copy of the OFFICIAL RADIO SERVICE HANDBOOK by Bernsley—just published.

Please send HANDBOOK to me C.O.D.

Name

Address

City

State

Please send complete literature on HANDBOOK.
(Send remittance by check or money-order. Register letter if you send cash or currency.)

This is it!

Entirely New!

"The Most Complete Radio Buying Guide"

● The Radolek New 1937 Radio Profit Guide is the most complete Radio Parts Catalog ever published. Completely revised—right up to the minute, bringing you everything in Radio—and Public Address—at the right prices. Every page brings you extra profits! Contains over 10,000 Individual Radio Repair Parts—hundreds of new items—a complete new selection of Radio Receivers, P. A. Amplifiers, Tools, Tubes, Books and Test Instruments. Everything you need—always in stock... ready for prompt shipment to you. You need this Big Radio Parts Catalog—its FREE!

Send for It!

RADOLEK

625 W. Randolph Street, Chicago, Illinois

Name

Address

Serviceman? Dealer? Experimenter?

HOW TO GET IT



UNIT-MATCHED P.A. EQUIPMENT *The Bunk?*

Sounded like a selling idea when I first heard it . . . but after checking with other service men who do lots of Public Address work

I'm not so sure NOW

. . . in fact I *know* it isn't the bunk. If other manufacturers have the same thing, it may be just "follow the leader," but boys, if you're not buying Portable P. A. Units, amplifiers, microphones and speakers from OPERADIO then you don't know what smooth, swell working, profitable P. A. installations are.

Give that Operadio outfit a try like I did. You won't regret sending for their Catalog No. 10 . . . be sure and address Dept. S.

Ask about our convenient time payment plan.

OPERADIO

MANUFACTURING COMPANY

Unit-Matched P. A. Equipment at Its Finest
ST. CHARLES, ILLINOIS



NOW—YOU CAN PURCHASE

HICKOK

RADIO INSTRUMENTS on our NEW EASY PAYMENT PLAN

Thru arrangements with The Specialty Finance Co., Cleveland, Ohio, we are now able to furnish a reasonable, low cost, easy payment plan on all HICKOK RADIO TESTING INSTRUMENTS—Oscillographs, Oscillators, Tube Testers, Set Testers, etc. You can get details from your Jobber.

Send for latest catalog and details of all Hickok Instruments and bring your equipment up-to-date with only a small cash outlay.

THE HICKOK ELECTRICAL
INSTRUMENT COMPANY

10514 DUPONT AVE.


CLEVELAND, OHIO

ATR

Automatic
Tapering

BATTERY CHARGER

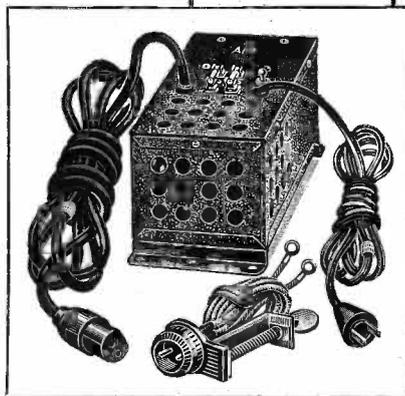Keeps Auto Batteries fully charged. An automotive necessity—needed more now than ever before — makes cold weather starting easy.



Big Fall and Winter Seller

High in efficiency but low in price. Operates noiselessly and economically. Ruggedly made to last many years. Simple to operate and fool-proof. Operates from any 110 volt 50-60 cycle A.C. line. Tapers off in charging current rate to approximately one-half as battery becomes charged. Completely equipped as illustrated.

Other ATR Products

ATR Auto Radio "A" Battery Eliminator. Specially designed for demonstrating and testing auto radio sets on regular A.C. lines 105-125 volts, 50 to 60 cycles.
ATR D.C.-A.C. Inverters. Produces A.C. Current Anywhere—in Cars—on Farms—in D.C. Districts. 16 different types for D.C. inputs from 6 to 220 volts having A.C. output of 110 or 220 volts.

Send for description and prices of money-making Battery Chargers, Eliminators, Inverters, etc. and name of nearest Jobber.

Manufactured by


AMERICAN TELEVISION & RADIO CO.
St. Paul, Minnesota, U. S. A. Cable Address: "LIKEX," New York

3 Sizes
STANDARD DIS-
COUNTS APPLY
Standard Charger,
Model 450. Maximum
charging rate, 4½ am.
List..... **\$9.67**
DeLuxe Charger, Model
600. Maximum charging
rate, 6 amp.
List..... **\$11.45**
Master Charger, Model
1000. Maximum charging
rate, 10 amp.
List..... **\$14.25**

**NOISE-LEVEL
GOES**

DOWN

and Volume
comes UP when you
install

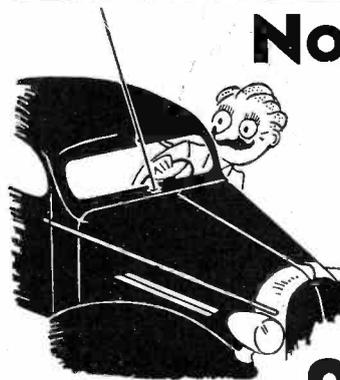

The Solution to the
Car Aerial Problem!

**MAGIC
ROD**


Honestly, fellows, MAGIC ROD is the answer to the service man's prayer! It can be installed in half an hour without getting mud in your eyes. It's up out of the way of road hazards, and its location *absolutely minimizes* ignition noise, wheel static, and other interference caused by the car itself. It's non-directional reducing fading, and its height makes it an AERIAL—receiving signals from the AIR. It is NOT affected by changing ground characteristics.

Simple, neat, trim in appearance. It flexes readily to give clearance, yet holds its position. You'll thank us for telling you about it if you'll only try it!

LIST Black Baked Enamel **3.50**
PRICES Chromium Plate 4.50

If you're an independent, write us for nearest distributor. If you're a dealers' or distributors' man—have your buyer get a sample MAGIC ROD. Show him this ad!

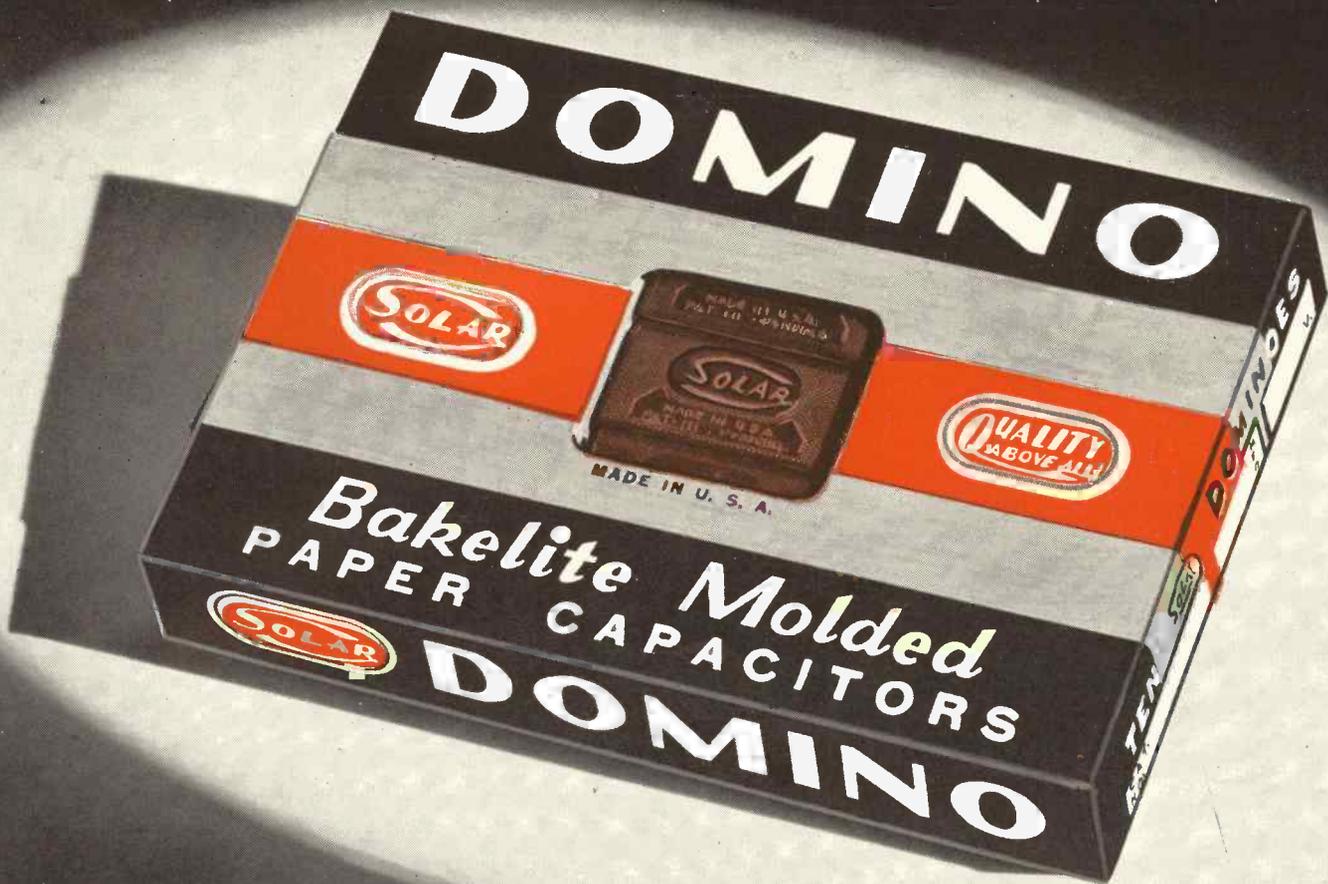MAGIC ROD DIVISION General Distributing Corp.
BOX S-9 SAGINAW, MICHIGAN




AN old favorite in a radically new form . . . attracting universal interest! Solar Dominoes are non-inductive paper condensers molded in Bakelite. They resist heat and moisture . . . offer permanent capacity and full voltage protection. Small, flat, easy to use. Dominoes combine all the quality features of Solar tubular paper condensers . . . plus the obvious advantages of protective and attractive molding in Bakelite. Compare their appearance and performance with ordinary paper tubulars. You will find Dominoes the better value.

Solar Dominoes are available in standard cartons of 10. A wide range of capacities may be obtained, up to .25 mfd. 200 volts, .1 mfd. 400 volts, .05 mfd. 600 volts. Complete listing furnished on request.


SOLAR MFG. CORP.

599-601 BROADWAY, NEW YORK CITY

SOLD BY LEADING JOBBERS EVERYWHERE

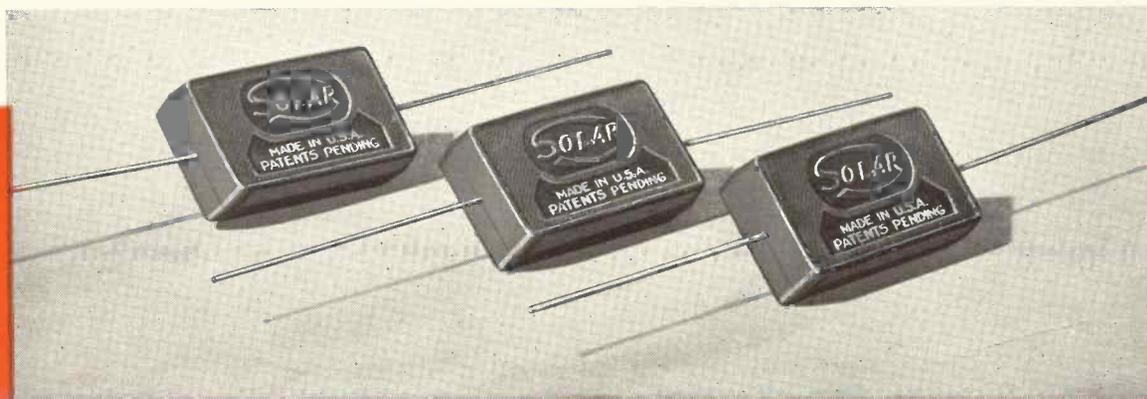

NOW READY TO HELP YOU MAKE MORE MONEY

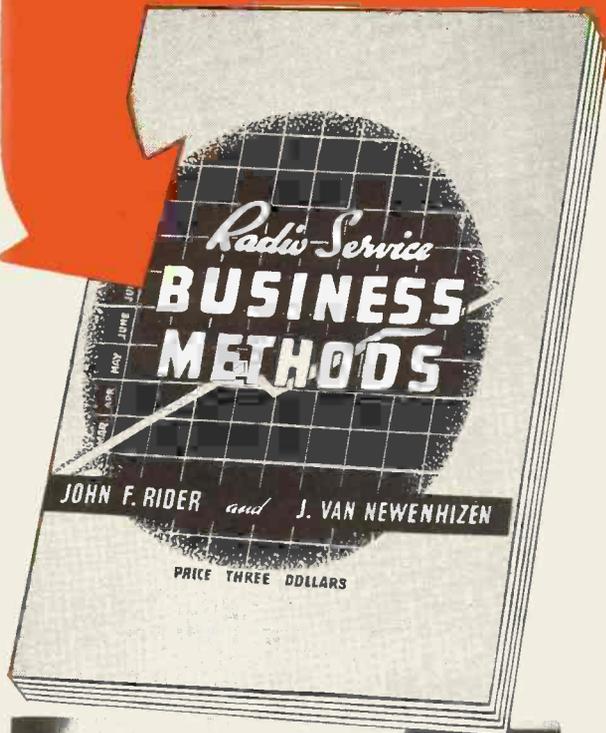

Here is the Third Point of the RCA 3-Point Service System—"Radio Service Business Methods," by John F. Rider and J. Van Newenhizen, just out. Tells in detail how to make your business ability match your technical expertness, so you can make the money you are justly entitled to make.

Learn how to calculate your costs, so you can put a fair and proper price on every job. Book explains how to keep simple records, as the basis not only for charging, but for credit. Shows the forms needed, and how to get them. This section of the book is simple. Follow it, and just a few minutes a day will provide you with the figures that will show whether you are making money on your volume of business.

220-page book, price \$3.00—but your RCA Parts Distributor or your RCA Tube Distributor will make you a deal so the book costs almost nothing. Ask him for details.

RCA 3-POINT SERVICE SYSTEM

Tells how to get more work, how to handle it more quickly, how to organize your business for profit.

1 "101 Sales Ideas for Service Men." Every idea tested, tried and proved, capable of increasing your volume of service business.

2 "The RCA Radio Service Tip File." A high quality steel

card file, with 200 cards, each bearing a practical servicing tip. Indexed by make and model. New tips being constantly released in packets of 20 cards.

3 "Radio Service Business Methods." Just out.

These Three Points should be used together for best results, but can be had separately. Ask your RCA Parts Distributor or RCA Tube Distributor to explain how you can get the complete System, or any part of it, for less than actual cost.



Parts for PROFIT

Parts Division, RCA MANUFACTURING COMPANY, Inc., Camden, N. J.

A Service of Radio Corporation of America