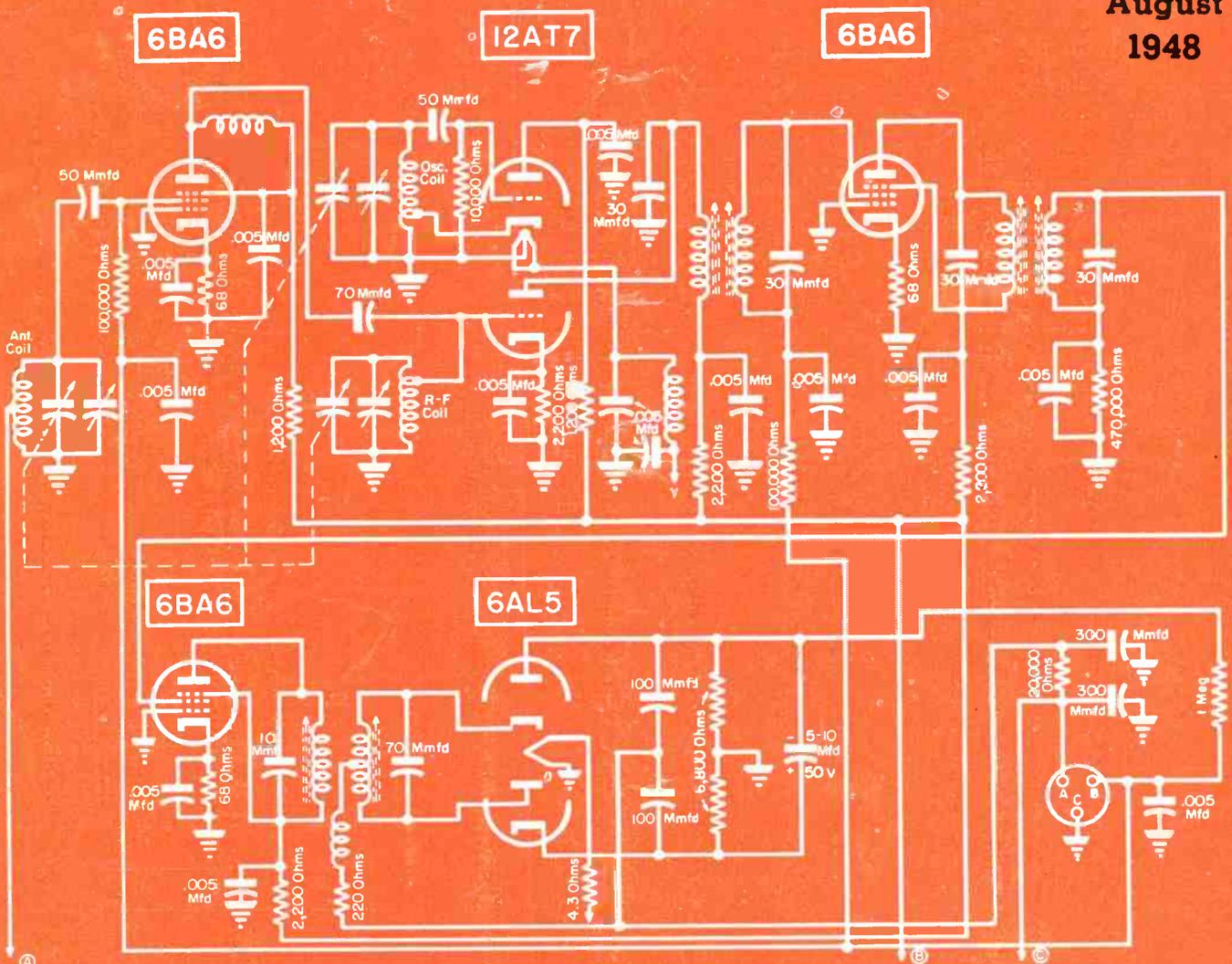


SERVICE


August
1948



Self-powered seven-tube f-m tuner featuring a dual-diode converter and oscillator (12AT7), ratio detector (6AL5) and an audio booster (6J5).

[See page 2]

**NEW PROFITS
FOR
SERVICEMEN**

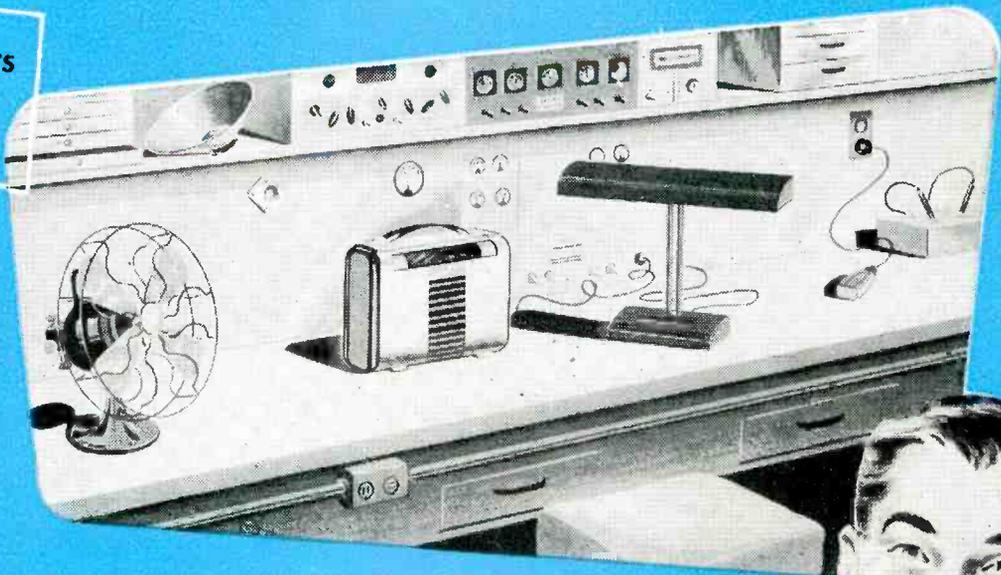


here's how one serviceman makes more money with C-D quietones...

Along with the finest test equipment, Frank Viscardi of Glen Rock, New Jersey, includes on his bench an electric shaver, an old-fashioned brush-type fan, and a fluorescent lamp. These articles — together with four popular types of C-D Quietone Radio Noise Filters — make up a potent demonstration. Every service customer is shown — *with his own set being used as guinea pig* — how the radio noises he thought had to be tolerated — can easily be eliminated. *Three out of four customers buy the filter recommended.*

Most of *your* customers need one or more C-D Quietones — *but they don't know it. Tell them — better yet show them, like Frank Viscardi does — and you'll discover the quickest-selling, fastest-moving accessories in the entire service field.*

Start cashing in on this big profit opportunity NOW! Mail coupon below for free copy of Catalog No. 195A. Cornell-Dubilier Electric Corporation, Dept. S8, South Plainfield, New Jersey. Other large plants in New Bedford, Brookline, and Worcester, Mass., and Providence, R. I.

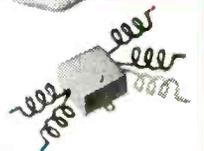

IF54



IF21



IF18



IF6



SEE YOUR LOCAL CLASSIFIED TELEPHONE DIRECTORY FOR NEAREST AUTHORIZED C-D DISTRIBUTOR

FREE!
profit building ideas in capsule form within the two covers of "THE CAPACITOR"



This remarkable magazine — published for servicemen — makes it easier for you to service any set ever made. Also, every month it brings you a fresh supply of hints for bringing more customers to your shop — boosting your profits. Mail coupon NOW — your free subscription will start at once!

CORNELL-DUBILIER
WORLD'S LARGEST MANUFACTURER OF
CAPACITORS

MICA • DYKANOL • PAPER • ELECTROLYTIC

CORNELL-DUBILIER ELECTRIC CORPORATION,
Dept. S8, South Plainfield, New Jersey

I can use those ideas for servicemen.

- Start The Capacitor coming my way at once — FREE.
 Please send copy of Catalog No. 195A.

Name.....

Address.....

City..... Zone..... State.....

I am a serviceman amateur experimenter

Other classification.....

"YOU CAN'T BEAT KEN-RAD TUBES!"



"You can't beat Ken-Rad tubes—I found that out long ago!

"Ever since 1935, when I started in business, I've been using Ken-Rad tubes.

"And believe me, they hold up—never let me down!

"I found Ken-Rad tubes dependable. So I sold them to my customers. They like them, too. I never receive a complaint.

"In fact, I think a good part of the big repeat business I do is the result of Ken-Rad tubes.

"Quality pays off!"



JOHN F. BERANICH, 4439 West Madison St., Chicago, Ill., does a big business servicing radios, and like thousands of other servicemen he uses Ken-Rad tubes. He likes their dependable quality!

"HERE'S WHY YOU CAN'T BEAT KEN-RAD TUBES!"


"From start to finish, Ken-Rad tubes undergo strictest inspections and tests.

"I know, because I help test them!

"They're made to stand up, satisfy customers, increase your business.

"You can depend on Ken-Rad tubes because they're tested for noise, microphatics, static, life, shorts, appearance, gas, air and hum.

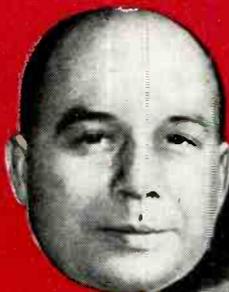"Your customers can depend on Ken-Rad tubes because they're built, throughout, to the highest standards of quality, stamina, and endurance."



WALTER DOWNING, Foreman, Raw Materials Inspection Department, is in charge of comprehensive testing of all materials used in making Ken-Rad tubes. Here cathode sleeves are being tested for breaking strength.



KEN-RAD *Radio Tubes*

PRODUCT OF GENERAL ELECTRIC COMPANY

Schenectady 5, New York

**The
Serviceman's
Tube**



RADIO · TELEVISION · ELECTRONIC
SERVICE

LEWIS WINNER
Editorial Director

F. WALEN
Assistant Editor

ALFRED A. GHIRARDI
Advisory Editor

	Page
Association News	32
Electronic Baby Light. By Jack Najork	10
F-M Tuner (Cover)	38
Ser-Cuits (Complete Analysis of Stromberg-Carlson, G.E. and Philco Projection Television Circuits)	24
Servicing Helps. By P. M. Randolph	22
Ten Years Ago in Associations	33
Tube News (Miniature Tube Basing Circuits)	12
TV Signal and Voltage Picture Tube Circuits. By Edward M. Noll	18
Use of Math in 12-Channel TV Antenna Installations. By Ira Kamen	14
Views and News. By Lewis Winner	9
CIRCUITS	
Auto Test Setup	23
Capacitor Check Circuit	22
Code Practice Oscillator Circuit	22
Diode Filter Circuit	35
Farnsworth 6V240 (TV Picture Tube Circuit)	19
G.E. 801 (TV Picture Tube Circuit)	18
G.E. 803 (TV Receiver Block Diagram)	28
(TV and F-M R-F Amplifier, Converter and Oscillator Circuit)	28
(Broadcast Converter and Oscillator Circuit)	28
(Video and Audio I-F Circuit)	28
(Horizontal Sweep Circuit)	30
(Horizontal Multivibrator and Sync Circuit)	30
(Vertical Multivibrator and Sweep Output Circuit)	30
(Video Detector and Amplifier Circuit)	30
Howard 482 (Cover)	38
Philco 48-2500 (Block Diagram of TV Projection Receiver)	31
RCA 641 (Signal-Voltage TV Circuit)	18
R-F Circuit of A-C/D-C Receiver Using 12BA6 and 12BE6	34
Stromberg-Carlson TV-12 (Block Diagram)	24
Stromberg-Carlson TV-12 (Complete Circuit)	26
Sound-Light Amplifier (Electronic Baby Light)	11
COVER	
F-M Tuner (Howard 482)	38
SERVICING HELPS	
Remedy for Fogging Dials	23
Service Notes on Admiral 7T01 C, E, M and 7C64W-UL; Chevrolet 985255 and 985284; Philco 47-1226/1227/1230, 48-1264 and 48-200	23
Using A Signal Tracer for Capacity Checkup, Code Practice and Auto Set Testing	22
Index to Advertisers	48
Manufacturers	
New Products	42
News	46
Jots and Flashes	48

Entire contents Copyright 1948, Bryan Davis Publishing Co., Inc.



Published monthly by Bryan Davis Publishing Co., Inc.
52 Vanderbilt Avenue, New York 17, N. Y. Telephone MURray Hill 4-0170



Bryan S. Davis, President Paul S. Weil, Vice Pres.-Gen. Mgr. F. Walen, Secretary A. Goebel, Circulation Manager

Cleveland Representative: James C. Munn, 2253 Delaware Dr., Cleveland 6, Ohio. Telephone: Erieview 1726

Pacific Coast Representative: Brand & Brand, 1052 W. Sixth St., Los Angeles 14, Calif. Telephone: Michigan 1732
Suite 1204, Russ Building, San Francisco 4, Calif. Telephone: SUTter 1-2251

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.


"We show customers we're equipped with Factory Information"

Says: H. A. WENZEL

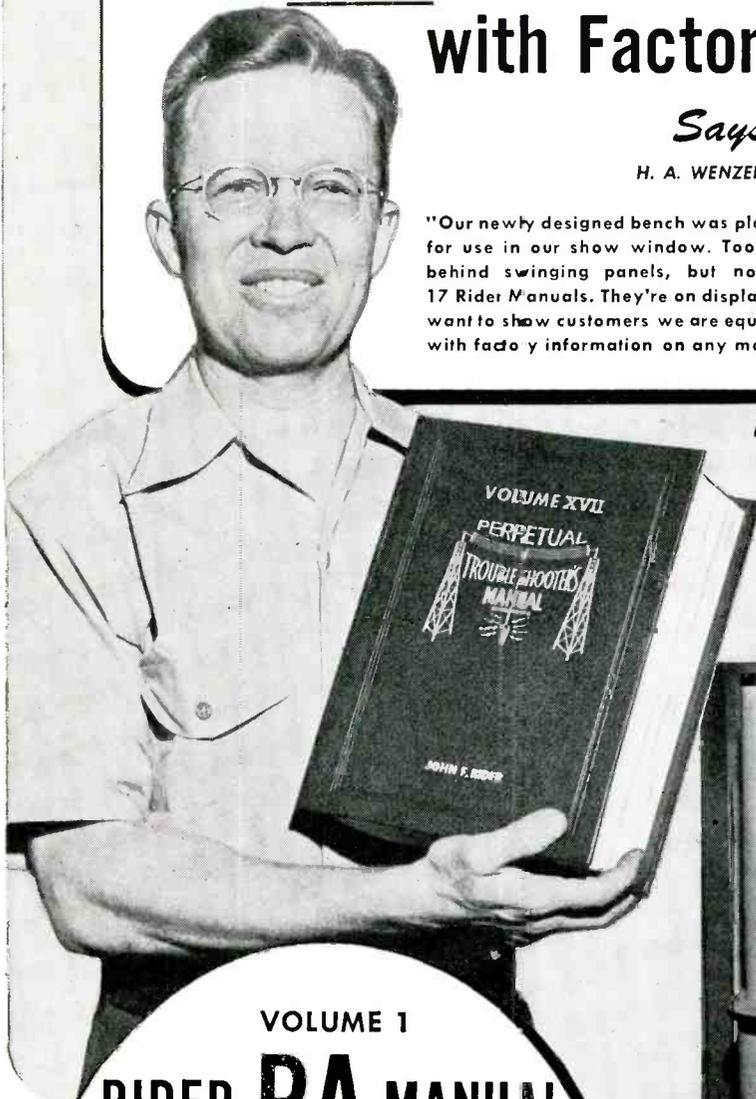H. A. WENZEL RADIO SERVICE, Quincy, Ill.

"Our newly designed bench was planned for use in our show window. Tools are behind swinging panels, but not our 17 Rider Manuals. They're on display. We want to show customers we are equipped with factory information on any make or

model receiver they bring us for repair. "We keep our Rider Manuals at our fingertips as they are an important part of our servicing procedure. Speeding up diagnosis, they're important to our servicing profits too."



You NEED ALL 17 RIDER MANUALS

Volume XVII . . .	\$16.50	Abridged Manuals I to V (one vol.) . . .	\$19.80
Volume XVI . . .	8.40	Record Changers and Recorders . . .	9.00
Volume XV . . .	19.80	Master Index, covering Manuals, Vols. I to XV, 1.50	
Volume XIV to VII (ea. vol.) . . .	16.50		
Volume VI . . .	12.50		

ORDER - FROM YOUR JOBBER - TODAY!



VOLUME 1
RIDER PA MANUAL

OUT IN SEPTEMBER

The first industry-wide service manual covering amplifying systems produced from 1938 to date, by more than 135 manufacturers. Schematics voltage data, resistance values, capacity values, parts lists, etc. Separate "HOW IT WORKS" book explains the theory of various designs employed in different types of amplifier systems, the servicing of PA systems, using sine wave and square wave means of checking, methods of rapidly locating faults. Everything you need.

Approx. 2000 Pages . . . \$18.00

ORDER YOURS TODAY!

VOL. 1 JUST OUT
RIDER

Television MANUAL

Establishing Sales Records!

Contains circuit descriptions, adjustment of various trimmers, traps, transformers, etc., voltage and resistance readings, alignment instructions, parts lists, schematics, patterns, chassis views, wave forms. Everything needed.

208-page "How It Works" book covers underlying theory of television. Transmission and reception, frequency standards, antennas, various portions of television receivers.



OVER 1400 PAGES
(but the equivalent of 2000 pages)

PLUS, 2 Separate Books, "HOW IT WORKS" & INDEX Complete \$18.00

Television "HOW IT WORKS" Available Separately

If television is not yet in your area, it will be soon. Here is theory you want. 208 pages . . . \$2.70

RIDER MANUALS Mean SUCCESSFUL SERVICING

JOHN F. RIDER PUBLISHER, Inc., 404 Fourth Avenue, New York 16 Export Agent: Rock International Corp., 13 E. 40th St., N.Y.C. Cable ARLAB.

NOTE: The Mallory Radio Service Encyclopedia, 6th Edition, makes reference to only one source of Radio Receiver Schematics—Rider Manuals.

IT'S HERE! WEBSTER-CHICAGO AUTOMATIC MICROGROOVE RECORD CHANGER

**"MICROGROOVE" IS HEADLINE NEWS—
MODEL 133 IS "CASH REGISTER" NEWS!**

Model 133 • the famous Webster-Chicago *foolproof* record-changer mechanism • New balanced tone arm and nylon knee action needle • magnificent reproduction from microgroove records • 33 RPM turntable speed — plays 10 twelve inch or 12 ten inch microgroove records *automatically* at one loading • 4 hours of continuous record play with fast change cycle.

THE *Matinee*

First of the Webster-Chicago line of automatic record changers for microgroove recordings • Phone your Webster-Chicago distributor for details. Don't delay! Be ready for the microgroove records. **\$38⁷⁵** Retail
\$39.95 West of the Rockies

WEBSTER - CHICAGO



5610 West Bloomingdale Ave.
Chicago 39, Ill.





Safety

The cop on the beat that protects your home . . . guides children across the street — he offers an important factor of safety in community life! And so it is with the patented construction feature of the RADIART VIBRATOR — the mica stacks! Because of this mica detail, sudden shifts in load peaks to high voltages are taken in stride, because they are designed to carry an overload! The resulting longer life and more dependable, longer performance means more satisfied customers for you . . . and yet this expensive feature costs no more! Just another factor that has helped build RADIART VIBRATOR superiority, and made them the fastest selling in the field.

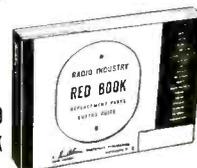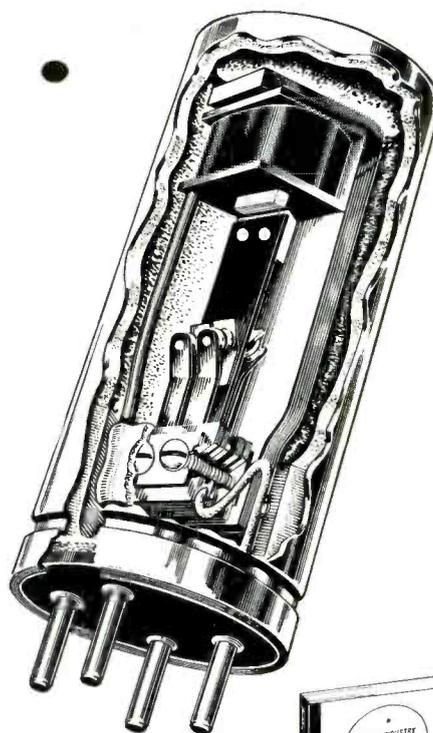


THE ONLY VIBRATOR LINE TO
BE LISTED IN SAMS RED BOOK



The Radiart Corp.

CLEVELAND 2, OHIO

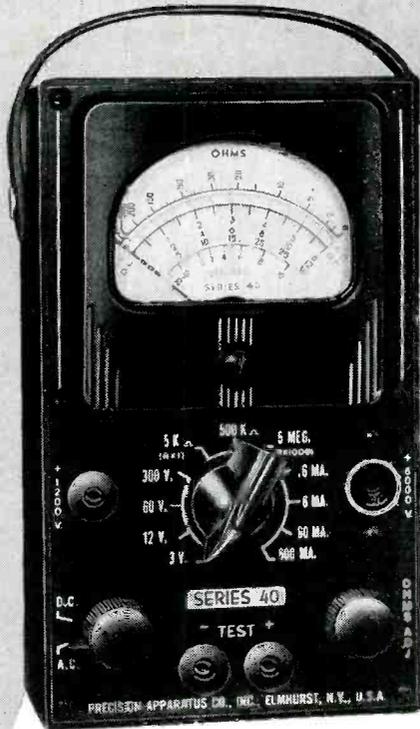Export-Scheel International Inc., 4237 N. Lincoln Ave., Chicago 18, Ill.



... a Pocketful of
PRECISION
Series 40
 Compact Wide-Range Circuit Tester

**Self-Contained to 6000 Volts AC & DC
 5 Megohms, 600 MA, + 70 DB,
 with full size 3" Rectangular Meter**


In a custom molded bakelite carrying case, the series 40 is an unparalleled instrument of its type and size. Ideally dimensioned and engineered to meet the need for a portable, compact, yet rugged, accurate test set to withstand hard, long term usage as is imposed by the service technician, maintenance engineer, production inspector, trouble-shooter, radio amateur, etc.

The Series 40 offers every advanced design feature and full-bodied components as are regularly incorporated in "Precision's" larger multi-range test sets, including: Rotary Range Selection—1% shunts and multipliers—heavy duty insulated pin jacks—Large numeralled, easy reading meter.

ALL RANGES, including 6000 volts and 5 Megohms, are SELF-CONTAINED and ready to operate. NO EXTERNAL BATTERIES OR MULTIPLIERS ARE REQUIRED.

RANGE SPECIFICATIONS

- ★ 6 A.C.-D.C. & Output Voltage Ranges: all at 1000 ohms per volt. 0-3-12-60-300-1200-6000 volts.
- ★ 4 D.C. Current Ranges: 0-6-60-600 MA.
- ★ 3 Resistance Ranges: with self-contained batteries. 0-5000-500,000 and 0-5 megohms.
- ★ 6 Decibel Ranges from -22 to +70 DB.
- ★ Full Size 3" Rectangular Meter: 400 microamperes ± 2% accuracy.
- ★ 1% Wirewound & Metallized Resistors.
- ★ Only 2 Pin Jacks serve all standard functions.
- ★ Recessed 6000 volt safety jack.
- ★ Anodized, etched aluminum panel: resistant to moisture and wear.

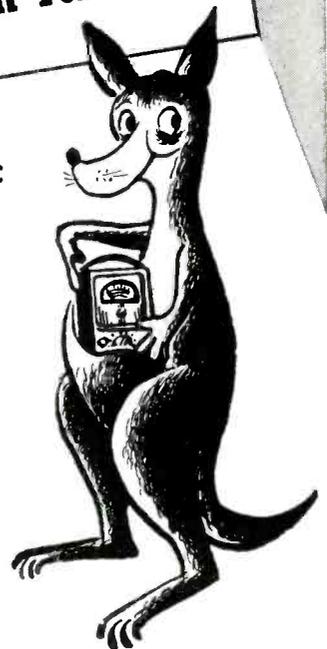

See this new "Precision" Test Set now on display at all leading radio parts and equipment distributors, or write directly for the Precision 1948 catalog describing the complete Precision line of quality Electronic Test Instruments for all phases of modern radio-electronics—A.M., F.M. and TV.

Series 40 (illustrated) In custom molded bakelite case with plastic handle. 3 3/4" x 6 1/4" x 2 1/2". Complete with ohmmeter batteries and test leads.

NET PRICE **\$24.75**



PRECISION
 TEST EQUIPMENT
Standard of Accuracy

PRECISION
 APPARATUS COMPANY INC.
 92-27 HORACE HARDING BOULEVARD
 ELMHURST 6, NEW YORK


Export Division: 458 BROADWAY, NEW YORK CITY, U.S.A.

Cables: MORHANEY
 SERVICE, AUGUST, 1948 • 7

Electrolytics by Sangamo

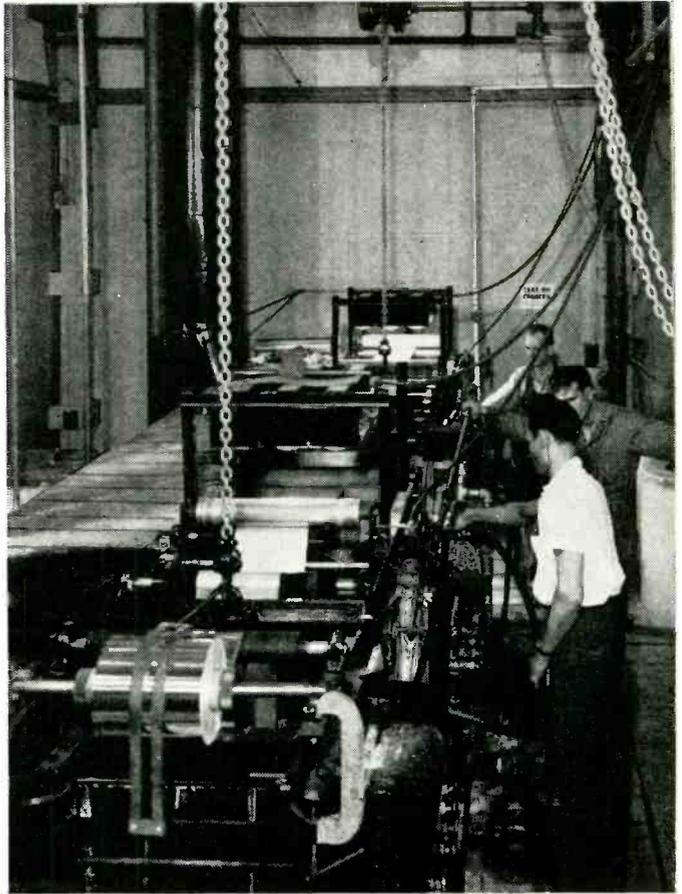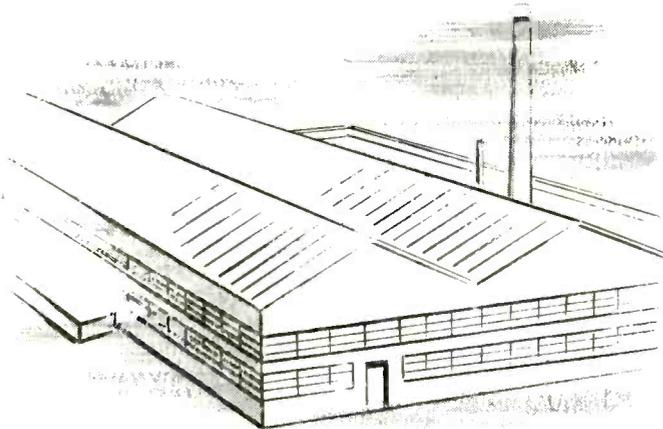

a New plant for Electrolytic Capacitors

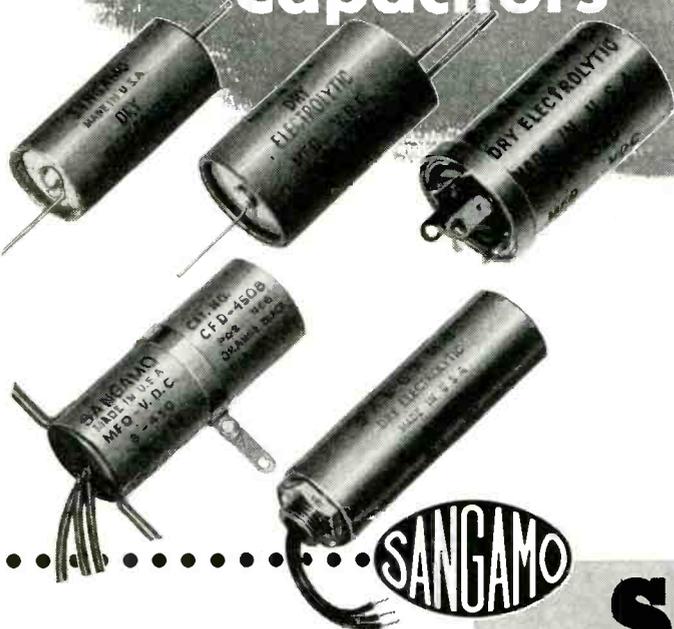

A complete line of capacitors for every electronic application—write for information today.

5C487

Sangamo is manufacturing electrolytic capacitors in a completely new plant, with the latest equipment, and with the most modern techniques. The plant is completely conditioned with filtered air to conform with Sangamo standards of cleanliness. Humidity is carefully regulated to accurately control moisture absorption. Stainless steel or aluminum is used on all surfaces which may be touched by the capacitors, and all operators wear rubber gloves in order to avoid contamination of foil.

The fine aluminum foil used in Sangamo Electrolytics is given particular attention. The equipment pictured above washes the foil in hot chemicals to remove any trace of surface impurity and etches the foil in one continuous operation.

Every capacitor is aged and tested at voltages in excess of the working voltage, and is heat-treated in temperature-controlled ovens. Only after these tests and repeated individual inspections, are Sangamo Electrolytics ready for you.

CAPACITORS:
PAPER • MICA • SILVER • ELECTROLYTIC

SANGAMO

ELECTRIC COMPANY

SPRINGFIELD • ILLINOIS

RADIO · TELEVISION · ELECTRONIC
SERVICE

The New Long-Playing Records

THE RECENTLY ANNOUNCED MICRO-GROOVE long-playing records requiring the use of slow-speed $33\frac{1}{3}$ rpm motors offers an unusual installation-service opportunity to every Service Man. The long-playing idea is unique and is rapidly winning over not only those who now have phono systems, but those with standard receivers.

It won't be long before there will be a substantial demand for either complete slow-speed phono setups, or the slow-speed motor alone, or complete high-fidelity phono setups with a slow-speed motor. In each instance, the Service Man can play a significant installation and servicing role. In many cases, it will be necessary to remove the 78 rpm motor setup and install the new system or provide for dual high and low-speed service. Where no phono system exists at present, connection to the audio-frequency circuit will be required, new switching may be necessary, and in many instances it will be necessary to provide a housing for the receiver, phono and speaker. Where the a-f system has a normal audio range, there'll be the opportunity of providing a wide range amplifier with, perhaps, a high-fidelity speaker in a custom-built setup.

Some alert Service Men have begun to sell the long-playing record idea by demonstrating a l-p phono unit during their service calls. The look, listen and try-it-yourself tests are quite convincing and usually quite productive.

Some Service Men have also been called on by furniture and music shops to conduct these demonstrations during their calls and then, perhaps, make an installation, with a sales commission-service charge arrangement in force. In New York City the tieup proved quite profitable to many.

The p-a field has also begun to show interest in the l-p system. Several Service Men having already installed the necessary slow-speed motors and lightweight pickups and revamped the

amplifiers to provide the required high-fidelity reproduction.

As indicated last month, SERVICE will soon publish a special report on l-p systems covering the features of the equipment and accessories, and detailing installation and servicing procedures, from the lab and the field.

Watch for this important report!

The Ideal F-M/A-M/Phono System

THE ADVANCED TECHNICAL KNOWLEDGE possessed by the Service Man enables him to serve as an accurate guide in the choice of receivers and accessories. Many consumers have been aware of this important factor and have come to rely completely on the judgment of the Service Man before buying.

Discussing this point with Harry Burnett of Hytron, recently, it was learned that Service Men are not only links in the complete receiver sale, but particularly combination affairs involving tuners, amplifiers, speakers, phonos, etc. He pointed out that Service Men are invariably questioned when the purchase of tuners are in mind, the consumer requesting information on the *best* or *ideal* system with often no ceiling on price. Here's a situation where general design and circuit familiarity become particularly helpful, and many interesting and effective combinations of equipment can be assembled, Burnett declared.

The Service Man can really go to town in *service* in this instance, we were told. And interviews with a number of Service Men revealed this fact to be quite true, with numerous successful tuner-amplifier projects recorded. Many interesting combinations of equipment seem to have been used because of many variables such as size, receiver location, cabinetry, outputs required, etc.

In each instance, the Service Man had assembled what he believed to be the ideal setup.

We believe that these *ideal* setups would be of interest to all Service Men and are thus preparing a series of articles describing these arrange-

ments. Undoubtedly, many SERVICE readers have their ideal setups, too. If you have one you feel would be of interest to the professional Service Man, send in a brief description, and every effort will be made to weave it into our articles. If you have photos, send them along, too. Feature article rate payments will be made for all material published.

Hope we'll be hearing from you soon.

New York Servicing Clinic

DATES FOR THE long awaited New York servicing clinic sessions have been set; there will be a three day series of meetings at the Hotel Astor in New York City on September 27, 28 and 29, with meetings being held in the afternoon and evening.

The New York meeting will be followed by one in Boston at the Hotel Bradford, November 15, 16 and 17, and others are scheduled for Atlanta in January, Los Angeles in March, and Chicago in April.

The sessions, which will be known as Town Meetings, will be conducted under the sponsorship of the Radio Parts Industry Coordinating Committee, composed of RMA, EPEM, WCEMA and Sales Managers Club (Eastern Division).

Walter W. Jablon, vice president in charge of sales for Espey, will be in charge of the New York meeting preparations and William P. Ready, radio parts sales manager of the National Company, will service similarly for the Boston meeting.

The Associated Radio Service Men of New York Inc., is cooperating in program development for the New York meeting. The sessions will feature 40 minute talks, with 20 minute *q* and *a* periods. To illustrate servicing techniques, typical lab equipment will be employed.

Every Service Man is urged to attend these all-important sessions at the Astor.

A complete report on the meetings will appear in SERVICE. Watch for it.—L. W.



Fig. 2. Interior view of Baby Light.

Fig. 3. Baby Andrea Jane Baxter of Syracuse activating the *Electronic Baby Light*, causing a lamp in the living room to flash and warn her parents that she wants attention.



The Electronic Baby Light

Unique Light-Sound Converter-Amplifier Designed For The Deaf Uses Sounds, Such As From A Crying Baby, To Actuate A Warning Light.

by **JACK NAJORK**

*Specialty Division
General Electric*

A FEW MONTHS ago, we received a request for a unit which would turn a remotely-located light on and off in response to sounds. This unusual device was wanted by deaf parents who were living in constant apprehension over the welfare of their baby girl because they could not hear the infant cry.

What was needed was a simple, reliable system of amplifying and converting sound into light. Simplicity and reliability go hand-in-hand, since the simpler the unit, the less likelihood of component failure. Therefore, these two features influenced the final design more than any other factors.

Simplicity was achieved by using only two active tubes, plus two other tubes for voltage regulation and rectification. The test of reliability will be answered after the unit has been in operation for a year or more. However, by using quality parts and allowing large safety factors, the possibility of component failure can be reduced to a minimum.

The Circuit

Basically, the system comprises a high gain audio amplifier which drives

a relay instead of a loudspeaker. The relay turns a remotely located light on and off through an extension cord which can be almost any length. A conventional four-inch p-m loudspeaker is used as a microphone and this is coupled to the amplifier stages through the output transformer originally designed for the speaker. A two stage resistance-coupled voltage amplifier using a dual triode 6SC7 develops sufficient audio gain to drive a 6J5 triode. The 6J5 is operated in class B; that is, it is biased almost to plate current cut-off in the absence of signal. When the amplified signal is applied to the grid of the 6J5, plate current flows, and this current flows through the relay and closes the contacts. The relay contacts remain closed only for the duration of the sound.

For the remotely-located light 117 v a-c is used since most relays have contacts rugged enough to handle ap-

proximately one-half an ampere or so. A 60-watt lamp was specified as the largest which should be used with the unit because tests showed that this resistive load caused almost no sparking at the relay contacts. Since the relay was considered the most vulnerable component from the standpoint of failure due to sticking contacts, it was given an accelerated test by connecting a 120-watt resistive load to the test model. This test model was then run continuously for several days in a noisy laboratory. Inspection of the relay contacts at the end of this period showed no apparent pitting or wear and the relay was therefore considered capable of breaking the current taken by a 60-watt lamp.

The possibility of using a universal (a-c/d-c) power supply was considered and rejected, primarily for safety reasons. Since the unit would, of necessity, be within reach of infants and small children, it had to be as

TUBE News

Improved Circuit Arrangements Available With The New Base-Pin Connections of 35C5, 50C5, 6BH6, 12AW6 And 6BJ6 Miniatures. Diode Filters.

by L. E. STEWART

RECENTLY SEVERAL miniatures with new basing arrangements, to facilitate circuit design, were announced; beam power amplifiers 35C5 and 50C5, sharp-cutoff pentodes 6BH6 and 12AW6, and remote-cutoff pentode 6BJ6.

Types 35C5 and 50C5 were designed for use in the output stages of a-c/d-c receivers. They are performance equivalents of miniature types 35B5 and 50B5, respectively, differing in basing connections only.

The use of two connections to grid 1 in beam-power amplifiers has been found very desirable because of the additional cooling effect of the second lead. If the temperature of grid 1 becomes too high, current flows in the grid circuit because of electron emission from the grid. This current causes loss of bias and, consequently, signal distortion.

However, because of this double grid connection, the basing arrangement used with types 35B5 and 50B5 (Fig. 1) has a tube-interchange disadvantage; for instance, if the 35B5 or 50B5 is accidentally inserted into a socket wired for a 12BA6. When the

12BA6 is used as an r-f amplifier without a coupling capacitor in the grid-1 circuit, which is often the case, a low resistance connection is made between the cathode terminal (socket pin 7) and the terminal connected to the loop antenna and the stator of the tuning capacitor (socket pin 1). In an a-c/d-c receiver, the cathode terminal of the r-f amplifier socket is generally connected to one side of the power line, either directly or through a small biasing resistor (Fig. 2). Consequently, the accidental insertion of a 35B5 or 50B5 into the 12BA6 socket connects one side of the power line to the tuning capacitor and loop antenna.

A similar situation can occur if a 35B5 or 50B5 is accidentally substituted for a 12BA6, when the latter is used as an i-f amplifier, in a circuit having the signal grid of the converter connected as in Fig. 3. In this case, one side of the power line is connected from the cathode of the i-f amplifier through the i-f grid, the avc line, and the loop antenna to the signal grid of the converter.

Mistakes of this kind result in inoperative receivers and a possible fire and shock hazard, when a plugged-in receiver is handled or serviced with

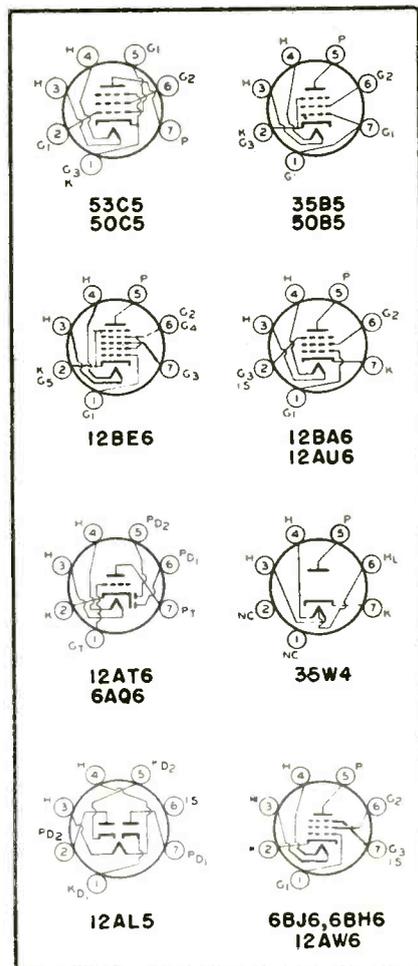


Fig. 1. Basing connections of new miniatures (35C5, 50C5, 6BH6, 12AW6 and 6BJ6) and comparable types.

(Continued on page 34)

Lightest
Most Efficient
Crystal Pickup
Cartridge
Ever Conceived!

NEW
SERIES 12



ACTUAL SIZE →



← WEIGHS ONLY $\frac{1}{5}$ OZ.



HANDY NEW KIT MAKES SALES AND SERVICE EASY!

Enables you to service most replacements *immediately*—helps you seal more replacement jobs to old and new customers—cuts overhead and inventory—increases turnover and profit! Contains 6 cartridges, 4 needles, mounting plates, literature, replacement chart and full instructions. Available in KIT "A" (Osmium) or KIT "B" (Sapphire).

ONLY TORQUE DRIVE GIVES YOU ALL THESE FEATURES!

Low mass drive system—Light weight—No bearings or bushings—Multiplied needle-force-to-crystal—High lateral and vertical compliance—Low distortion—Record matched frequency response—Triple voltage output—Zero output for vertical movement—Moisture-proofed crystal—Easy mounting—Replaceable osmium or sapphire tip whisker needle.

BETTER COUPLING OF RECORD GROOVE TO CRYSTAL

Exclusive Electro-Voice development now brings amazing improvement in record playing . . . *outmodes existing crystal pickup cartridges* . . . opens up vast new replacement opportunities. Fully tested and proved . . . the new Series 12 TORQUE DRIVE provides a more rugged cartridge for everyday use in home phonographs, booth demonstrators, and coin-operated machines. Assures finer reproduction, less surface noise, less needle talk, less record wear, longer record life, more needle plays!

3 BASIC MODELS REPLACE OVER 100 STANDARD TYPES

Comes in low, medium and high voltage outputs to provide universal replacement. Speeds servicing, steps up your profit. Installation is simple. Each cartridge is furnished with replaceable Osmium-tip or Sapphire-tip long-life whisker needle. It is available individually or in kits.

Series 12 with Osmium-tip needle. List price, \$7.50

Series 12 with Sapphire-tip needle. List price, \$8.50

It's the talk of the industry! Ask your E-V Distributor, or send now for Bulletins 141 and 142.

ELECTRO-VOICE, INC., BUCHANAN, MICH.


Export: 13 East 40th St., New York 16, U.S.A.
Cables: Arlab



ANOTHER FIRST BY

Electro-Voice

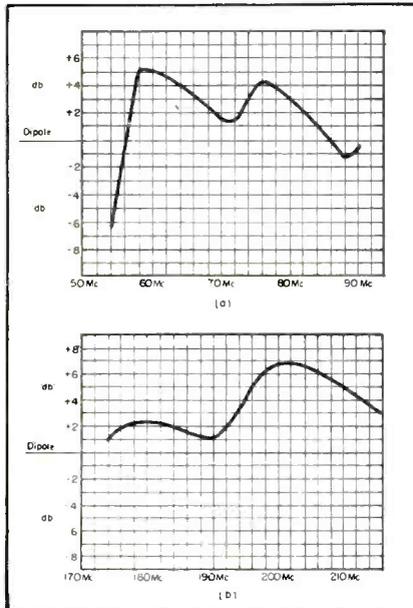Use of Math In 12-Channel TV Antenna Installations



ONE OF THE most important factors in tv installation work is the antenna's decibel gain, or db.

The db term is applied as an r-f function, expressing the ratio between any two electrical powers. In itself db is not an absolute measurement unless it is referred to some specific reference levels.

In the audio field, there have been several reference levels.

Broadcast engineers have selected a one milliwatt reference level; and replaced the db with a term called *volume unit* or *vu*. This means that a ten-watt broadcast amplifier has a power ratio of 10 w/.001 w or 10,000. Referring to a db table we find that this amplifier has an absolute value of 40 db or 40 vu, with respect to the one-milliwatt reference level.

Public-address amplifier manufacturers use a six milliwatt reference level in rating their amplifier equipment. A 10-watt p-a amplifier has a power ratio of 10 w/.006 w or 1666 with respect to the 6-milliwatt reference level. The db table will show that the 10-watt amplifier has an output rating of 32.2 db at this reference level.

Television antennas are rated in db antenna power gain, which is a measurement of the power ratio between the tv antenna under test and a standard dipole antenna having a gain of *one*; therefore, *one* is the reference level.

A tv antenna, rated as having an average gain of 3 db, will have a power gain ratio of 2:1 and a voltage

gain ratio of 1.4:1 (1.4 is the square root of 2), with respect to a dipole antenna with a gain of one.

Gain of Broadband Antennas

In Fig. 1 appears a 12-channel curve which shows the effect of frequency on gain. It will be noted that the gain of the broadband antenna plotted varies from one to almost 7 db. Fig. 2 shows the high front-to-back and front-to-side ratios of the antenna, which is illustrated in Fig. 3. The minor rear lobes (from 90° to 270°) are of low level and have a very small influence on the overall operating pattern.

The radiation pattern information must be coupled with the db antenna gain specification, as a highly directional pickup pattern (Fig. 2) raises the signal-to-noise level, a vital characteristic in weak signal areas.

Single channel 3-element antennas have a 5-db gain and a high front-to-side ratio at the specific channel (Fig. 4) and can be adjusted to match 73-ohm transmission line as shown in Fig. 5. The gain and directivity of a single-channel array can be further increased by piling the arrays which raises the forward gain to 7.6 db.

In interpreting the design features and specifications of any antenna, the following *rule of thumb* information will be found helpful:

(a) Three db is a power gain of 2:1 and a voltage gain of 1.4:1.

(b) Six db is a power gain of 4:1 and a voltage gain of 2:1.

(c) A 1-db increase in gain is negligible and does not provide a noticeable improvement on a tv picture unless the antenna also has a


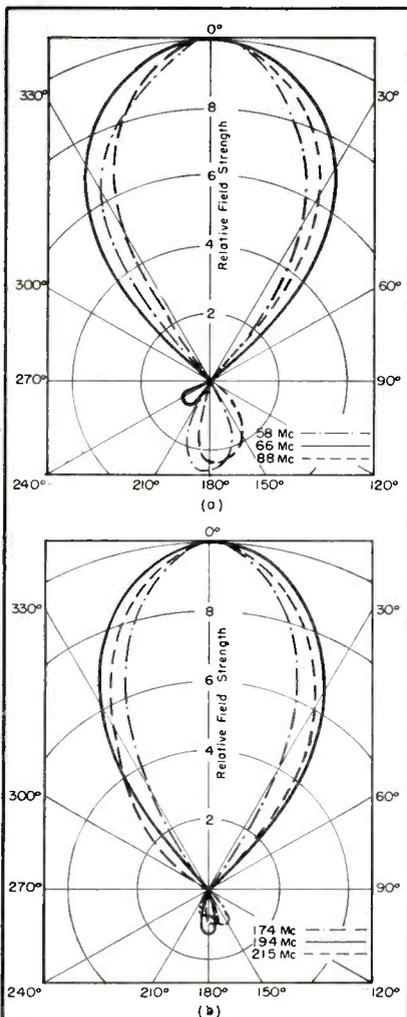


Fig. 1 (top, left). Effect of frequency on gain of broadband antenna with respect to a dipole antenna having a gain of one. (Courtesy Amphenol)

Fig. 2. Effect of frequency on front-to-side and front-to-back ratio of broadband antenna. (Courtesy Amphenol)

Fig. 3. Broadband antenna with gain and pattern characteristics indicated in Figs. 1 and 2. (Courtesy Amphenol)

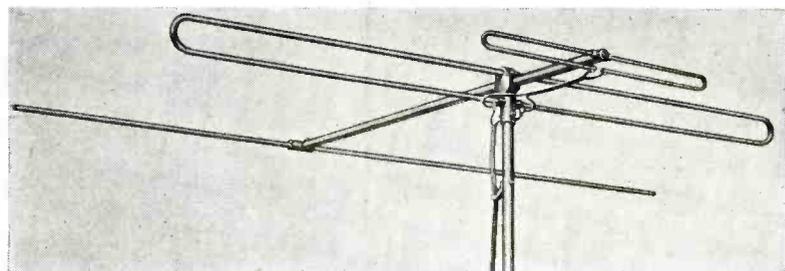

Simplified Explanation Of The Major Mathematical Factors With Which Service Men Must Be Familiar To Accurately And Successfully Install TV Antennas For Full Band Coverage. Typical Problems Analyzed.

by **IRA KAMEN**

*Manager, Television Antenna Dept.
Commercial Radio Sound Corp.
New York City*

radiation pattern which raises the signal-to-noise ratio.

(d) Broadband antennas should be analyzed and chosen on the basis of their gain characteristic with respect to the signal level problem in the area. For example, some broadband antennas favor the high channels more than the lower channels and should be used in those areas where there is less signal available from the higher channels, and conversely broadband antennas favoring the low frequency channels, should be employed where the signals are weaker from those stations in that section of the tv band.

(e) Broadband antennas with directional patterns should be used when all the stations are in the same direction with respect to the antenna.

(f) The tv channel favored by any dipole or folded dipole antenna can be readily checked by reference to Fig. 7.

(g) When a single tuned dipole has to be matched to a 300-ohm line, it is possible to increase the gain on a single tv channel by inserting a matching section between the two impedances.

$$\begin{aligned} \text{Impedance } (Z) \text{ of matching section} \\ &= \sqrt{Z_{\text{of dipole}} \times Z_{\text{of line}}} \\ &= \sqrt{72 \times 300} \\ &= \sqrt{21600} \\ Z &= 140 \text{ (approx.) ohms} \end{aligned}$$

As 140 ohms is not commercially available a 150-ohm piece of balanced line may be selected as the matching section. The length of the matching section should be approximately .9 times the length of the dipole rod. For example, for a channel 5 rod whose length is approximately 36", the matching section would be .9 x 36" or 32.4". The reason the matching section is shorter than $\lambda/4$ rod length, is that the velocity of wave propagation is different in transmission line than in air.

Typical Problems

The best way to understand 12-channel tv antenna engineering is to

apply the fundamentals to some specific problems.

Problem 1: Fig. 8 shows an antenna located from 1 to 15 miles from low and high-frequency tv stations, which are all in one direction with respect to the receiving antenna.

Assuming that a 15-mile maximum radius is still in a primary signal area of at least five millivolts and that no reflection problem exists, a simple straight or folded dipole, or dipole and reflector, will have sufficient gain to energize the tv receiver on the low and high frequency channels. Even if a dipole adjusted for the lower channels had a 12-db loss at the higher channels, the signal would still be adequate. As indicated in our *rule of thumb* notes, a 6-db gain or loss is a voltage gain or loss of 2:1. Therefore 12 db is a voltage loss of 4:1 and in a five millivolt area, there would still be 5/4 or 1¼ millivolts of signal

available for the tv receiver. This is more than twice the FCC minimum requirement for a satisfactory picture. If the signal-to-noise ratio in the area is low, a wideband antenna array with reflector assembly is preferred.


Problem 2: Fig. 9 shows a tv receiving antenna located with high and low-frequency tv stations on both sides of its position.

When the tv signals are 180° apart, an antenna without reflectors should be selected. While a wideband array is preferred a simple straight or folded dipole will be satisfactory in areas where the signal-to-noise ratio is high.

Problem 3: Fig. 10 illustrates a single high-frequency station at approximately right angles to a group of high and low-frequency tv stations.

A straight or folded dipole adjusted for the mean frequency of the lower tv channels will operate on the third harmonic for the high-frequency channels and will pick up adequate signal strength for channels 2, 4, 5 and 11, when matched into a 300-ohm line. A high frequency antenna attachment (Fig. 11) which consists of a straight

Fig. 4. Plot of horizontal pattern in power indicating the high front-to-side ratio of dipole, director, and reflector. (Courtesy Workshop Associates)

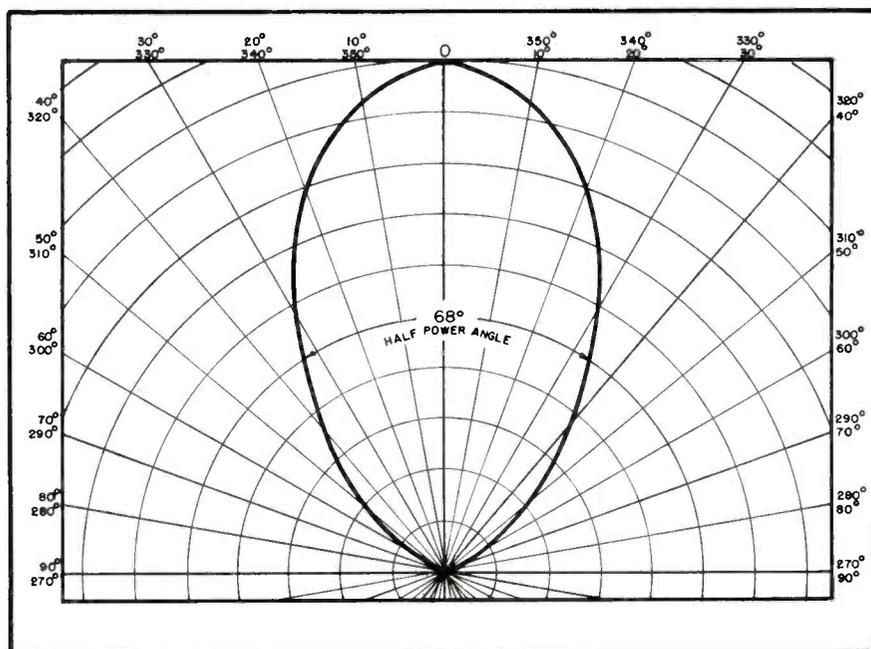


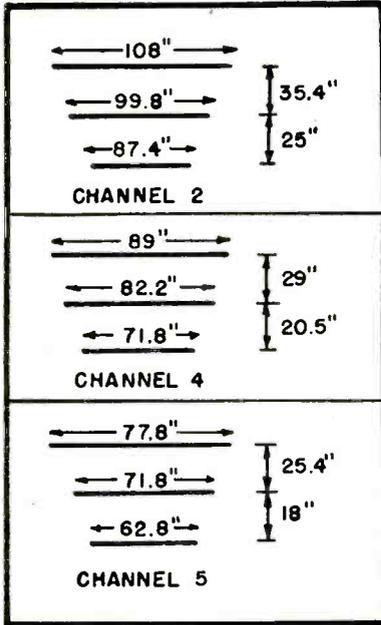


Fig. 5. Dimensions and spacing of antenna elements of three-element array to realize approximately 73 ohms at the dipole terminals for one specific tv channel.

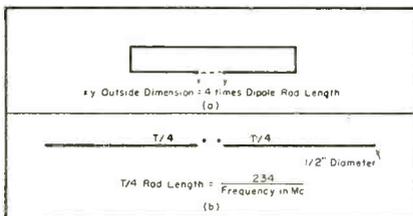

Fig. 6. A double stack of three element arrays, which serves to increase the forward gain of a specific tv channel. (Courtesy Workshop Associates)

Fig. 7. Tables for determining resonant frequency of dipoles shown below. Distance between the elements in the folded dipole can vary from .54 to .145.



or folded dipole cut approximately for channel 13 may be added to the larger array and adjusted at right angles to pick up channel 13 and transfer its signal into the transmission line. The best way to adjust this composite array is:

(a) Install larger array and adjust for best reception on channels 2, 4, 5 and 11.

(b) Add high-frequency attachment and adjust for best reception of channel 13.

(c) Recheck channel 2, 4, 5 and 11 pictures to determine if they have been affected by the addition of the high-frequency attachment.

(d) If the channel-13 attachment mars reception on the other channels (2, 4, 5 and 11), a separate transmission line may be installed for the high-frequency antenna attachment, and an antenna transfer switch mounted adjacent to the tv receiver.

High-frequency antenna attachments may affect low-frequency or broadband arrays under the following conditions:

(a) When the low-frequency array picks up a strong reflected signal on a high-frequency channel, which differs in time and phase delay with respect to the direct signal picked up by the high frequency attachment on the same high-frequency channel.

(b) When the larger antenna array picks up a ghost-free reflection on a low-frequency tv station and the high-frequency attachment induces a direct pickup tv signal on the same low fre-




(Continued on page 36)

TV Channel	Approximate Dipole Rod Length
2	4.1'
3	3.6'
4	3.4'
5	3'
6	2.8'
7	1.32'
8	1.28'
9	1.24'
10	1.2'
11	1.16'
12	1.13'
13	1.18'

Fig. 7b. Dipole rod table.

TV Channel	xy Outside Dimension
2	16.4'
3	14.4'
4	13.6'
5	12.0'
6	11.2'
7	5.28'
8	5.12'
9	4.96'
10	4.8'
11	4.64'
12	4.52'
13	4.4'

Fig. 7a. Folded dipole table.

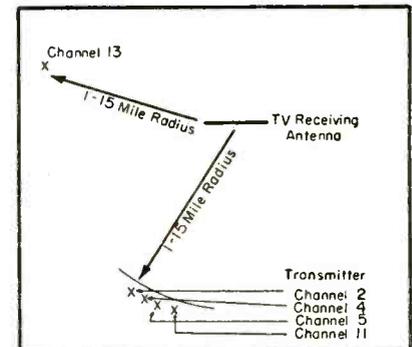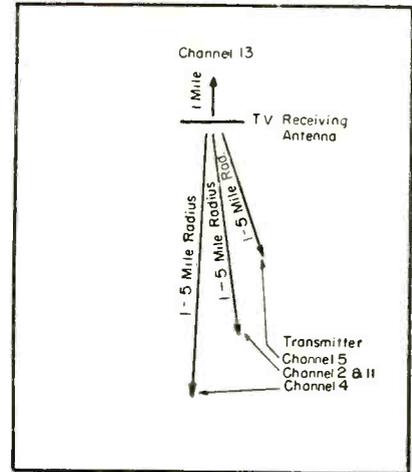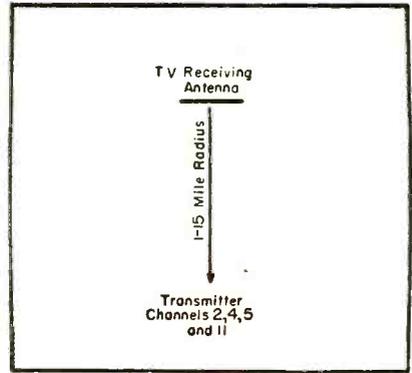

Figs. 8, 9 and 10 (top to bottom). Illustrations of typical antenna location problems encountered in the field.

Fig. 11. High channel (7 to 13) tv antenna attachment to low channel (2 to 6) tv antenna array. (Courtesy Camburn)



Now Available!

STANCOR QUALITY

midget REPLACEMENT TRANSFORMERS



DESIGNED FOR PERSONAL PORTABLE TYPE RADIOS

SINGLE PLATE TO VOICE COIL . . . Two primary impedance ratings are offered in the STANCOR A-3328 and A-3329 output transformers. These will match the majority of output tubes commonly used in personal portable-type radios.

The A-3328 is interchangeable with RCA Part Number 37806. It is designed to match a single tube 4,000 ohm plate impedance to a 3.5 ohm voice coil for use with tubes such as the 1S4 and 3S4. It has 1 3/4" mounting centers and a small depth dimension to insure a fit in all cases. Overall dimensions are 1 3/16" H. x 2 1/8" W. x 1" D.

List Price . . . \$1.45


The A-3329 is similar to the A-3328 in all respects with the exception that it matches a single tube plate impedance of 8,000 ohms to a 3.5 ohm voice coil and is used with such tubes as the 1C5-GT, 1G5-G, 1Q5-GT/G, 1S4 and 3S4.

List Price . . . \$1.45

DESIGNED FOR SPECIALIZED SERVICE APPLICATIONS

HUM-REDUCING TYPE . . . The STANCOR A-3330 is a special output transformer with an extra tap on the primary winding for use in hum-reduction circuits. The primary matches a single 2,000 ohm plate and the secondary is designed for use with a 3.5 ohm voice coil. Maximum allowable primary D.C. is 50 milliamperes. Used with such tubes as the 25B5, 25B6, 25L6, 35A5, 35L6 and 50L6. Maximum audio power is rated at five watts. Overall dimensions are 1 3/8" H. x 2 3/8" W. x 1 3/8" D. Mounting centers are 2".

List Price . . . \$2.10

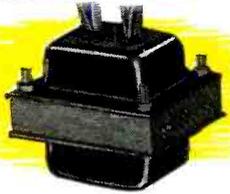

**Combination Plate and Filament
ULTRA-COMPACT SIZE**

The STANCOR P-6348 is a special, midget size plate and filament transformer for small four- or five-tube receivers using either a type 6X4 or 6X5 rectifier tube. Primary operates from 117 volts, 60 cycles; high voltage winding delivers 480 volts CT at 60 ma.; 6.3 volts center tap winding delivers 2.75 amperes. Mounting area is 2 3/16" x 2 11/16". Mounts in a STANCOR type "M" mounting by two bolts with 1 29/32" between centers. Overall depth is 2 3/4".

List Price . . . \$5.95



FREE! GET STANCOR'S NEW CATALOG TODAY!

Stancor's new catalog 140H contains important technical data and approximately 400 catalog items. Contact your authorized Stancor distributor or write direct.




standardize on **STANCOR** **TRANSFORMERS**

STANDARD TRANSFORMER CORPORATION • 3584 ELSTON AVENUE • CHICAGO 18, ILLINOIS

SERVICE, AUGUST, 1948 • 17

Howard W. Sams

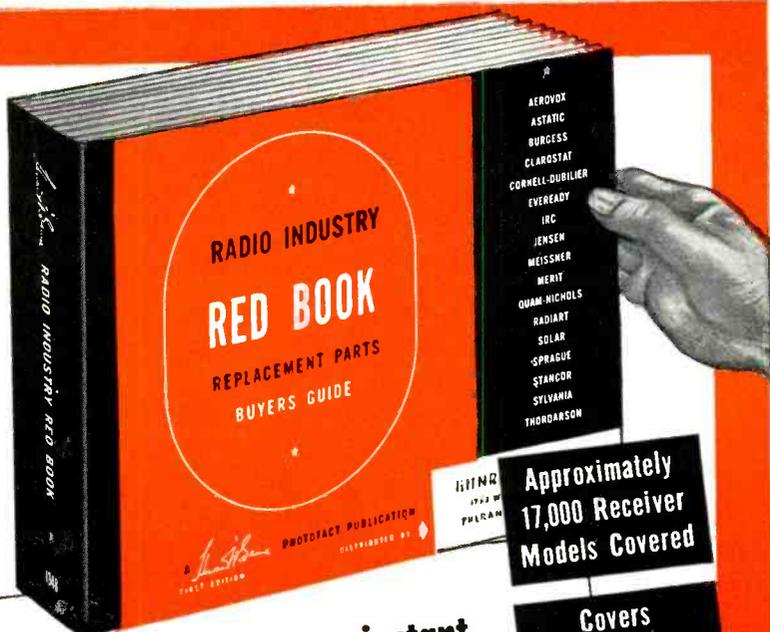presents the amazing
**RADIO INDUSTRY
 RED BOOK**
 REPLACEMENT PARTS
 BUYER'S GUIDE



NOW — a SINGLE authoritative volume that gives you instant reliable data on ALL replacement parts for thousands of popular radio receivers . . . more useful data than in all other replacement parts guides and manuals COMBINED . . .

COMPLETE!

The First Cooperative Industry Effort in Behalf of the Radio Service Technician

FOR THE FIRST TIME IN RADIO HISTORY!

All 9 Major Replacement Components Listed
(not just 1 or 2 components)

17 Leading Parts Manufacturers Represented
(not just 1 manufacturer)

Approximately
 17,000 Receiver
 Models Covered

Covers
 Ten Years:
 1938 to 1948

Easy to Use:
 All Data
 Quick to Find

440 Pages
 Smyth-bound
 Opens Flat

COMPLETE DATA ON ALL RECEIVER REPLACEMENT PARTS — ALL IN THIS ONE GREAT BOOK!

Save time! Stop wasteful hunting! Get ALL the parts data you need—quickly—from this single book. NOW—for the first time—have all the replacement parts data you need—ALL in one single, authoritative volume. No more waste of valuable time searching through dozens of incomplete manuals and catalogs. The RED BOOK, first and only complete parts guide ever produced, covers approximately 17,000 radio models made from 1938 through 1947—10 full years. Lists parts made by 17 leading manufacturers—not just one! Gives you complete, accurate data on all 9 major replacement components—not just one or two! Clear, concise, easy-to-use—over 440 pages (8½" x 11") bound in a sturdy sewed cover, arranged alphabetically by manufacturer and model number for quick reference. Does away with confused collections of separate books and manuals—gives you complete information—PLUS data that cannot be found in any other source—at a fraction of the price you'd pay for the books it replaces. There's never been anything like it—absolutely indispensable for every service shop!

Only the RED BOOK gives you ALL this invaluable data. Here's everything you need to know about the replacement parts for the receivers you service daily. The RED BOOK gives you original manufacturers' parts numbers, proper replacement parts numbers and valuable installation notes on *Capacitors, Transformers, Controls, IF Coils* (including Peak Frequencies), *Speakers, Vibrators and Phono Cartridges, Tube and Dial Light* data includes number of tubes in each chassis, with type number for each tube, plus dial light numbers. *Battery* data includes replacement numbers on A, B, and AB packs. The following leading replacement parts manufacturers are represented in the RED BOOK:

- | | |
|------------------|------------|
| AEROVOX | ASTATIC |
| BURGESS | CLAROSTAT |
| CORNELL-DUBILIER | IRC |
| EVEREADY | JENSEN |
| MEISSNER | MERIT |
| QUAM-NICHOLS | RADIART |
| SOLAR | SPRAGUE |
| STANCOR | SYLVANIA |
| | THORDARSON |

18 months in preparation—over \$90,000 to produce. The RED BOOK is the product of thousands of man-hours spent in laboratory research and in cooperation with 17 participating manufacturers to produce the most complete, accurate, authoritative parts replacement guide ever published. Every bit of information in this amazing book has been painstakingly checked to insure maximum accuracy and usefulness. Over \$90,000 was spent to prepare the RED BOOK—the only book that brings you everything you need to know—every bit of replacement parts data you want to make your work easier and more profitable. You can't afford to be without the RED BOOK. It's the indispensable guide you'll use profitably every single day. Stop hunting for the right answers now—order your copy today.

**THE INDISPENSABLE
 RED BOOK . . . ONLY . . . \$3.95**

BE SURE TO ORDER YOUR RED BOOK TODAY →

HOWARD W. **SAMS** & CO., INC.
 INDIANAPOLIS 7, INDIANA

Mail This Order Form to Your Parts Jobber Today or send directly to HOWARD W. SAMS & CO., INC., 2924 E. Washington St., Indianapolis 7, Ind.

My (check) (money order) for \$..... enclosed.
 Send RED BOOK (S) at \$3.95 per copy.
 (I understand that delivery will be made to me in September.)

Name

Address

City.....State.....

Servicing Helps

Using A Signal Tracer For Capacity Checking, Code Practice And Auto Set Testing. Service Notes on Philco, Admiral And Chevrolet Receivers.

IN THE FEBRUARY ISSUE OF SERVICE appeared several interesting applications of a signal generator originally described in the May, 1947, issue of SERVICE.


Franklin H. Stewart, who sent in the May issue circuit, reports that he has included a few innovations which have amplified the circuit's uses. In Fig. 1 appears one of the circuit changes.

Considerably more gain was obtained by using a 6AC7 instead of the 6SK7 in the r-f stage. Other alterations include an r-f choke used in place of the plate load resistor.

In checking capacitors Stewart says he inserts the unit under test in series with the high voltage supply, and the potentiometer and neon-lamp combination; Fig. 2. If the capacitor is good, there will be an initial flash of the lamp and no further indication. An open capacitor will not cause the flash. A leaky capacitor will cause a series of flashes and a shorted one will cause a continual glow. For replacement purposes capacitors of at least 600-volt ratings are used, each one being checked before installing, with 250 volts applied from the voltage divider.

Capacitors in the receiver, says Stewart, may be tested by discon-

Fig. 2. Circuit of capacitor checker in the signal tracer.

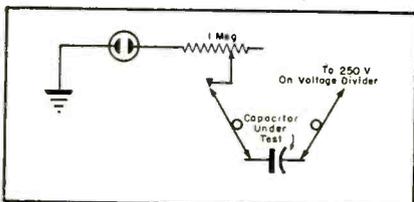


by P. M. RANDOLPH

necting one lead. This circuit may also be used as an aid in locating shorts in variable capacitors. Plates are straightened until rotor may be turned all the way in or out without neon glow at any position.

The tracer can also be used as a code-practice oscillator, by making the changes noted in Fig. 3. A key is inserted in series with the connection to the plate coupling capacitor on the 6K6 and the connection to the diode detector section of the 6SQ7. Audio gain control must be reduced to minimum before inserting key. Then the volume can be increased to desired level with key closed.

Another interesting modification and application is shown in Fig. 4. The 6.3-volt a-c filament secondary of the power transformer may be used to op-

Fig. 1. Revision of signal tracer using a 6AC7 instead of a 6SK7 in the r-f stage.

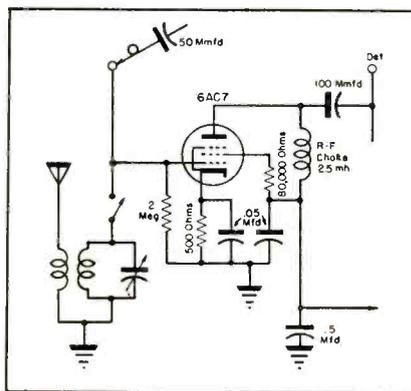

erate an automobile receiver, if the receiver has a rectifier tube. One side of this 6.3-volt a-c is connected to the lead which ordinarily goes to the ammeter or other source of supply. A two-lead connection is made to the other side of the 6.3 terminal. One of these has a clip on it and clips to the chassis. The other of this pair has one prong of an old battery plug on the end. Vibrator should be removed and pin inserted into either of the small terminals.

We now have 6.3 volts on all filaments and 6.3 volts a-c from one side of the primary winding to center tap on the power transformer.


Service Notes

JOHN W. FINDARLE of Modesto, Calif., has forwarded an assortment of very useful services notes on Admiral, Philco and Chevrolet receivers.

On the Admiral 7TO1C, E, M models, Findarle states there are several troubles common to this series.

Set dead: If pilot light flickers when the set is tuned to a point on the dial

Fig. 3. How to hook up a code practice oscillator in the signal tracer.

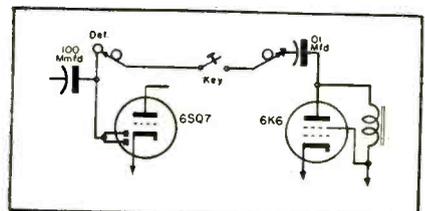

where a powerful local is normally heard, the set is probably okeh up to the secondary winding of the output transformer. (This is a rapid and positive method of determining the same trouble on other a-c/d-c sets having the conventional pilot light hookup.) The cure is a rather odd one; application of a soldering iron to the voice coil terminals on the speaker frame. It seems that no flux was used on the original joint, and the leads from the secondary of the output transformer do not make good contact.

Set dead, pilot light does not flicker: The resistance of the i-f transformer windings should be checked, especially the secondaries. It should be about 15 ohms. Comparing the value of one winding with that of the others will disclose the correct value.

Chevrolet Auto Radio, Model 985255

A common complaint on this model is the lack of sensitivity over part of the dial. A preliminary check will usually indicate improper alignment. However, when alignment of the i-f transformers is attempted, it may be found impossible to peak at the 262.5 kc i-f specified for this receiver. In fact the lowest possible frequency at which the i-fs can be peaked may be 310 kc.

Normally this would indicate shorted windings on the transformers, but the possibility of all the coils being shorted is seldom the case. In one receiver under test, a resistance check proved the i-f transformers and associated trimmers to be okeh. The set was therefore peaked at 315 kc and on the completion of the alignment, found to not only play normally throughout the dial, but be less subject to ignition interference.

Philco Models 47-1226, 1227, 1230 and 48-1264

It has been found that most complaints in these models are caused by the original tubes in them. Replacements have cured intermittents, frequency drift noise, etc.

Intermittent, comes back on only after turning set off and allowing to cool: Replacing the 7R7 tube will

remedy this every time. A tube checker will not disclose a defective tube and neither will tube tapping every time.

Intermittent, cutting on and off is periodic: The 6BA6 should be tested. These tubes seem to develop an intermittent open after being in service for awhile. Tapping the tube while the set is in operation will readily disclose if this tube is at fault.

Frequency drift accompanied by mushiness: This is another tube replacement item, with the 7F8 at fault. No amount of tube tapping nor a tube test will disclose a defective tube. After replacing the tube, the set should be kept on for a couple of hours. Old tubes usually do not act sick until they have been used for an hour or so either, and some new tubes will act the same way.

Intermittent noise: If the noise sounds like bursts of static, the 7F8 should be tapped. In seven out of eight cases the tube was found to be at fault.

Mushiness and noise: In some cases this can be traced to one of the 6V6GT or 6K6GT output tubes. The best way to locate the bad tube is to find a quiet spot on the dial, then turn the volume control full on and tapping and listening; tapping each of the output tubes in turn and listening for a change in noise level and a click each time that the defective tube is tapped.

Philco Model 48-200

Set dead: If the dial light flickers with the volume control wide open and the set tuned to a point on the dial where a powerful local is normally heard, the speaker voice coil can be suspected. A check with a low reading ohmmeter will invariably disclose it to be shorted. Replace it with a

5" p-m Alnico V (1 ounce) speaker having a 3.2-ohm voice coil. This defect occurs before the sets are sold or very soon after.

Chevrolet Model 985284 Auto Radio

Weak or no reception: This was traced to the lugs of the antenna coil which were found to be shorting to the shield can under vibration. This also causes an intermittent condition in some cases. The remedy is to bend the lugs in.

Admiral Model 7C64W-UL

Set dead: On checking it was noticed that the following tubes and the pilot lamps were cold: 6BA6 i-f, 6BA6 i-f/a-m detector, 6AL5 discriminator, 6SJ7 a-f and 6V6GT output. This was caused by a snap in the lead of the capacitor-choke combination at lug 4 of the 6BA6 i-f tube socket due to vibration. To repair, it is best to drill a hole in the chassis and mount a single lug tie-point strip and use this as a terminal for the capacitor-choke wire and then run a wire to the socket lug.

Remedy for Fogging Dials


THE DIAL WINDOWS of the Admiral 8B1, 9A1 and 9B1 chassis build up a small electrostatic charge, thus causing the plastic to attract fine dust particles. These are so fine that the dial windows appear milky or foggy. This often occurs within a few days.


A solution called Hexco Dust-Ded^d, has been found to be an effective remedy. This solution is used on television magnifying lenses to reduce their affinity for dust. When testing this solution, it was found that it will materially reduce the amount of fine dust collecting on the dial windows, thus preventing the foggy appearance. Admiral service engineers report that one application will last indefinitely. However, it is possible that reapplication may be necessary. At the present time, Admiral is treating all dial windows in production with this solution.

To apply the solution, the dial window will have to be removed from the cabinet. The window should be cleaned by wiping off the dust thoroughly on both sides, with a damp (not wet) cloth or chamois skin.

^dSolution available from Admiral Corp. Service Department; part number 98A11-2.

Fig. 4. Use of the 6.3 volt a-c filament secondary of the power transformer for operation of an auto receiver.

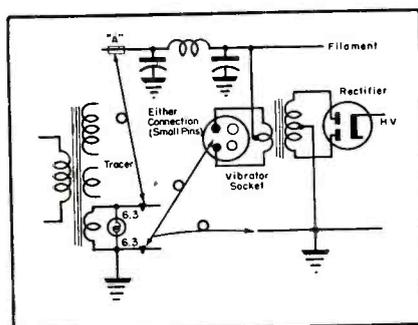

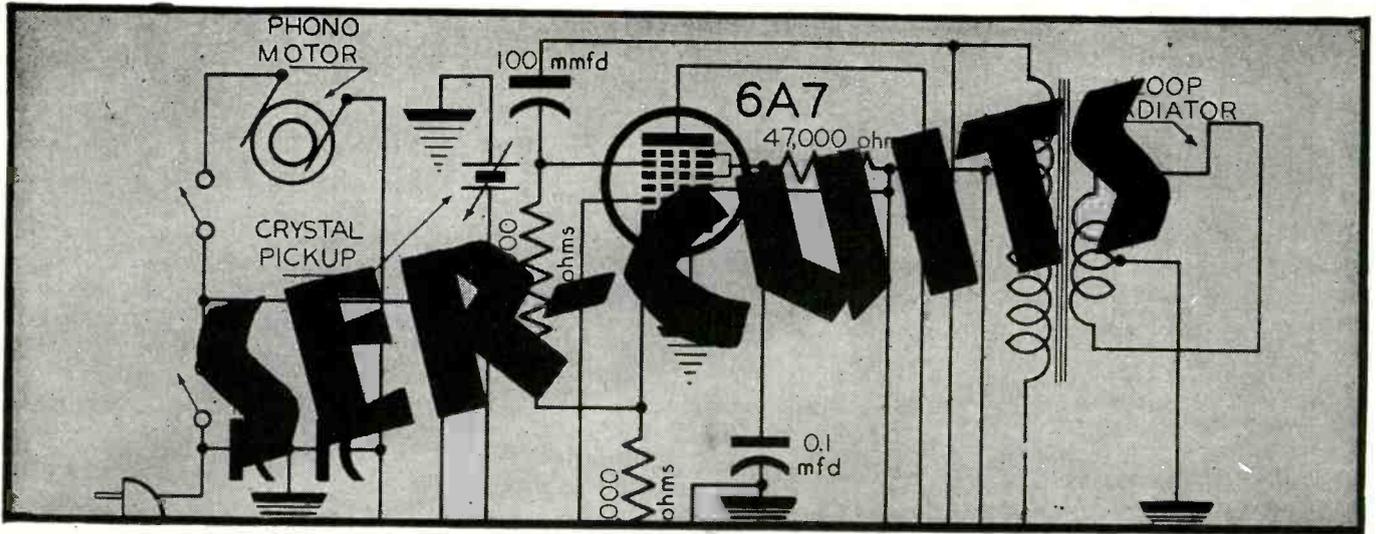

TV Circuit Features of Stromberg-Carlson TV-12, G. E. 803 and Philco 48-2500 (Projection Model).

DURING THE PAST few months many new types of tv receivers have appeared featuring a variety of circuit innovations.

The Stromberg-Carlson TV-12 model is an excellent example of the recently-announced receivers with quite a few advanced circuit features.

In this receiver twenty-eight tubes are used:

6J6 r-f amplifier; 6AK5 converter; 6J6 r-f oscillator; three 6AG5s for


first, second and third video i-fs; 6AL5 video detector and d-c restorer and sync takeoff; 6AC7 video amplifier; 12JP4 picture tube (providing a 7½" x 10" picture); 6AU6 first sound i-f; 6AU6 f-m sound limiter; 6AL5 f-m sound detector; 6SJ7 first sound amplifier; 6V6GT/G sound power amplifier; 6SN7GT sync clipper and horizontal saw generator; 6SJ7 sync clipper; 6AL5 sync discriminator; 6K6GT/G horizontal oscillator;

6SN7GT vertical buffer and vertical saw generator; 6SN7GT vertical deflection amplifier; two 5U4Gs as low-voltage rectifiers; 6AC7 reactance tube; 6BG6G horizontal deflection amplifier; 1B3GT/8016 high-voltage rectifier; 5V4G for horizontal damping; 6AL5 time delay relay and 6AL7GT tuning eye.

R-F Tuner

A 75-ohm low-loss transmission line (coax) used between antenna and in-

Fig. 1a. Block diagram of the Stromberg-Carlson TV-12 (Series 10-11). This circuit is similar to the DuMont RA-103.

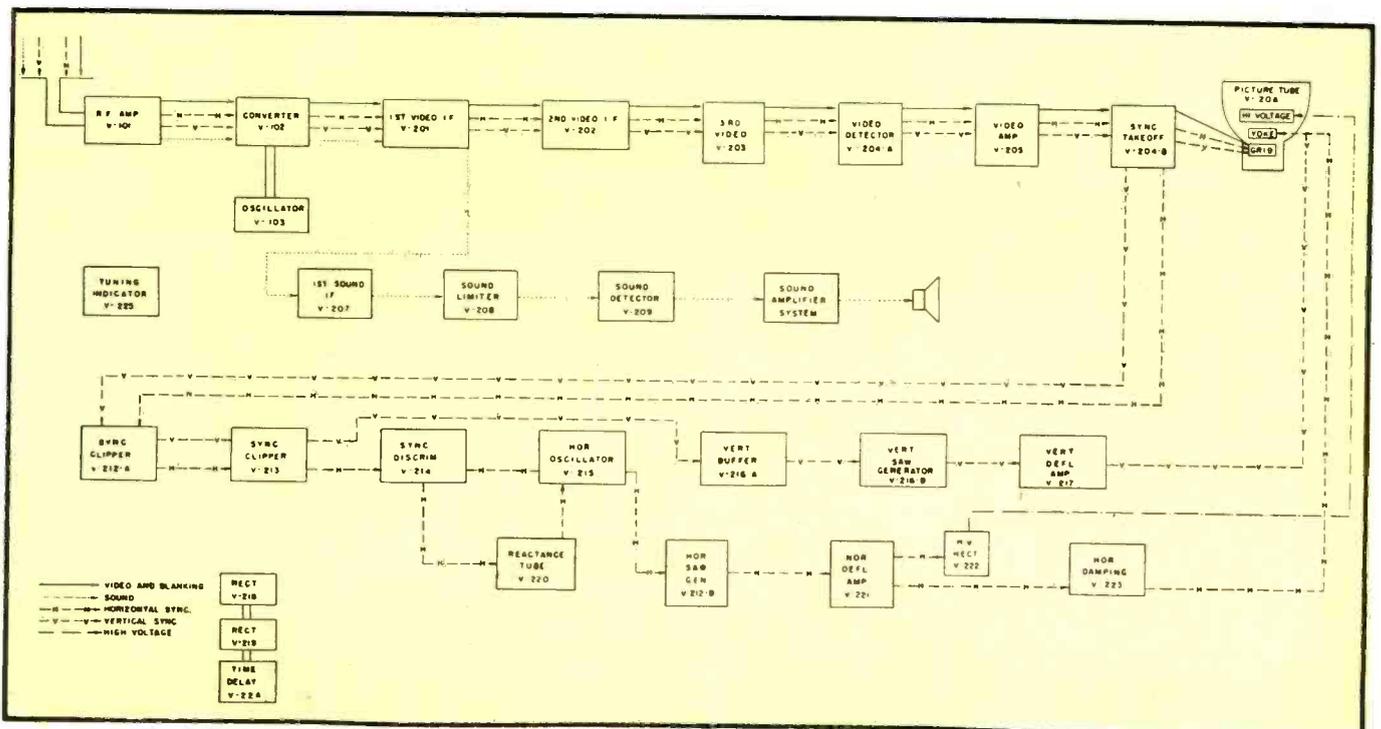


Specify the



1201


**DELUXE ALNICO 5
LOUDSPEAKER**

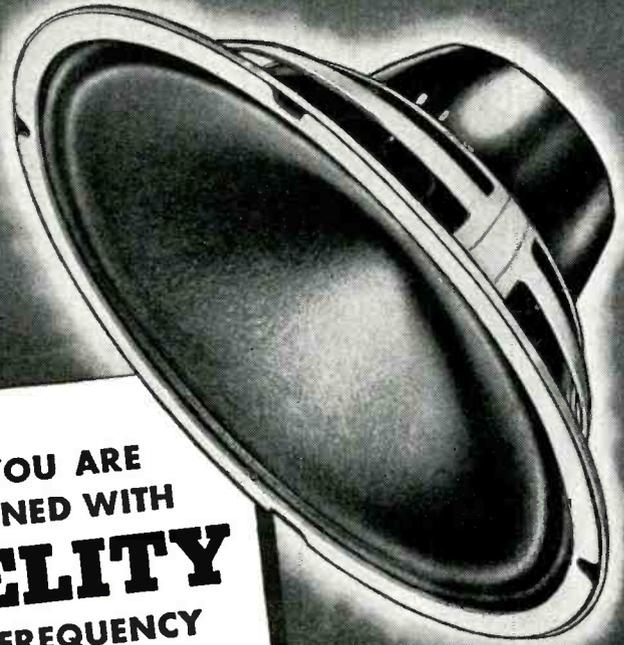

WHEN YOUR
JOB DEMANDS
POWER
25 WATTS
POWER HANDLING
CAPACITY

WHEN YOU ARE
CONCERNED WITH
FIDELITY
BROAD FREQUENCY
CHARACTERISTIC
50-13,000 CYCLES

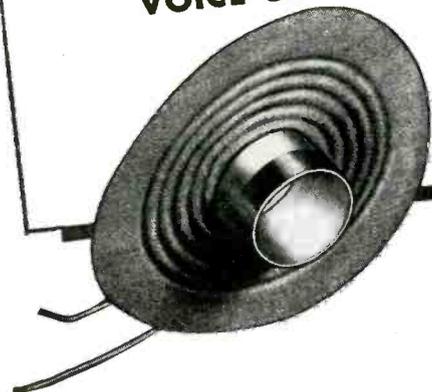EQUIPPED WITH
THE FAMOUS
GENERAL ELECTRIC
ALUMINUM FOIL BASE
VOICE COIL



POWER, fidelity and a price that will amaze you for a speaker of this exceptionally high quality—it's the G-E 1201.

It's a wide range speaker with the frequency response stretched out at both ends of the curve to give intense realism, smooth, full lows and "high fidelity." A curvilinear cone is employed to provide this extended frequency response. Alnico 5, 14½ ounces of it, gives high sensitivity and smooth response.

The moving parts in the speaker assembly are ruggedly designed to take high power without damage to the speaker in any way.

Note: Frequency response 50-13,000 cycles.

For complete information on this outstanding speaker write: *General Electric Company, Electronics Park, Syracuse, New York.*

GENERAL  **ELECTRIC**

169-GB

put is terminated by the cathode input circuit of a grounded-grid 6J6 r-f amplifier. This input circuit is capacity coupled to the transmission line by means of a 470-mmfd capacitor. The inductance in parallel with the antenna input provides a high-pass r-f filter to suppress broadcast-band or other low-frequency, cross-modulation interference which may arise when the receiver is located in an extremely intense field of an a-m broadcast station or other radiator.

The plates of the 6J6 r-f amplifier are coupled to the grid of the 6AK5 converter by means of a 6-mc wide coupling network. A variable series coil combination tunes to the desired signal frequency in conjunction with the associated tube capacities and a coupling network. A pair of 12,000-ohm resistors are used to reduce the Q of the respective coils considerably so that the coupling network can maintain the very wide pass band.

The r-f oscillator utilizes one section of the twin triode 6J6 in a modified Colpitts oscillator circuit, and its frequency is on the high side of the signal. The feedback voltage of the oscillator is accomplished by means of the interelectrode capacity of the tube. The oscillator frequency is tuned by movement of a tap on the coil which short circuits a portion of the coil.

The oscillator output is coupled to the grid of the converter by means of a 1-mmfd capacitor. The incoming signal is also fed into the grid of the converter tube and the resulting i-f signal appearing on the plate is fed into the first video i-f transformer.

Video I-F Amplifier

The video i-f amplifier chain consists of three stages, using the type 6AG5 sharp cutoff high-gain pentode. Each video i-f coupling network consists of two adjustable coils which are resonant with their respective tube capacities and coupling networks. The first video i-f coupling network utilizes shunt inductive coupling. The second, third and fourth video i-f coupling networks use the series type of inductive coupling. The two parallel resonant traps in the series arm of the π network in the third coupling network provide a high degree of attenuation to the associated sound carrier and to the sound carrier of the adjacent channel.

The grids of the first and second video i-f stages are returned to a variable negative bias provided by the

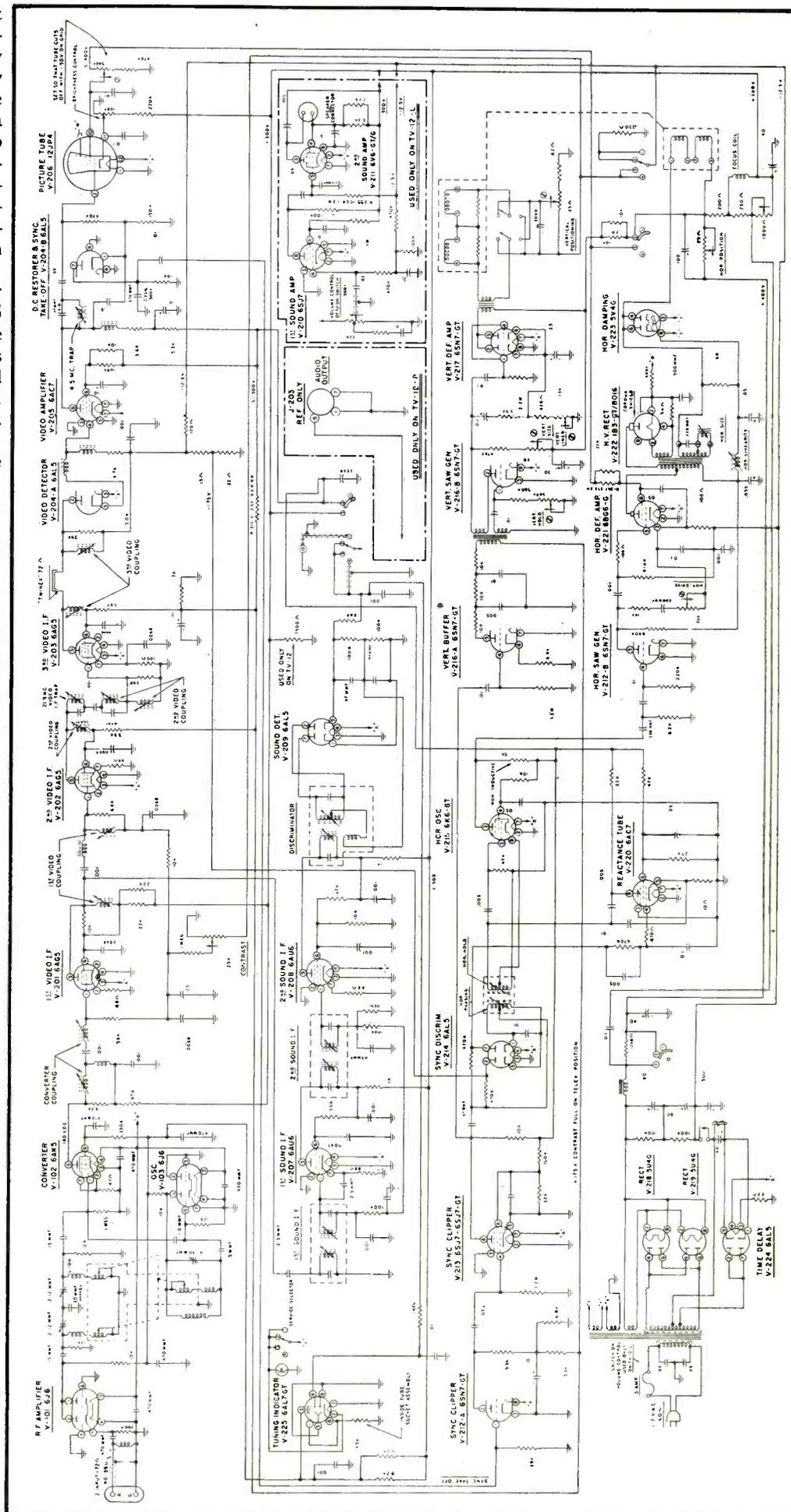


Fig. 1b. Circuit diagram of the Stromberg-Carlson TV-12 receiver.

contrast control, which thus varies the gain of the i-f amplifier. The third video i-f amplifier stage is operated at maximum gain. The input to the f-m sound i-f amplifier system is taken from the plate of the first video i-f amplifier.

The output of the fourth video i-f coupling network is fed into one diode section of the 6AL5 video detector and the diode load which consists of a 4,700-ohm resistor and a pair of peaking coils.

Video Amplifier

The grid of the 6AC7 video amplifier is directly connected to the diode load. A fixed bias of -3 volts (when no signal is present) is maintained on the grid of the video amplifier by returning the low-potential end of the diode load resistor (4,700 ohms) to the -3 volt point of the bleeder resistor network consisting of 120-ohm, 15-ohm and 22-ohm resistors.

The plate of the video amplifier is coupled to the 12JP4 picture tube by means of a resonant trap, consisting of an iron-cored coil and a 47-mmfd capacitor and a .05-mfd unit. This resonant trap provides the video amplifier section with an extremely sharp cutoff characteristic at 4.5 mc and thus attenuates the beat of the sound carrier and video carrier to prevent it from interfering with the picture.

D-C Restorer and Sync Separator

The plate of the video amplifier is also coupled to the second section of the 6AL5 diode and its associated circuit containing a 150,000-ohm and 10,000-ohm resistor and a 270-mmfd capacitor. This circuit rectifies the composite video signal and reinserts its d-c component on to the grid of the picture tube. This diode also serves as a sync separator, only negative sync pulses appearing across the 10,000-ohm output resistor.

Picture Tube Controls

The brightness control, a 100,000-ohm pot, varies the positive d-c bias on the cathode of the picture tube so as to vary the picture background brightness. The bias control, a 500,000-ohm unit, varies the positive voltage on the second grid of the picture tube. The purpose of this control is to adjust the second grid voltage of each picture tube so that they all will have a standard grid-control characteristic.

Sync Clippers

The sync pulses developed across

the 10,000-ohm output resistor and 270-mmfd capacitor are coupled into the two sync clipper stages. The clipper stages amplify and clip both top and bottom of the sync pulses. The sync pulses developed on the plate of the second stage remain substantially constant in amplitude over a wide range of input signal levels.

Vertical Deflection

The output of the second sync clipper is fed into the 6SN7 vertical buffer with an integrating network used as the plate load. The integrating network adds the six vertical pulses into one pulse which is then fed into the primary of a vertical sawtooth generator transformer. The 6SN7 vertical sawtooth generator then can be locked into synchronization with this pulse by adjusting a vertical hold control. A vertical size control varies the *B* supply voltage to the sawtooth generator and thus varies the vertical size.

The vertical deflection amplifier amplifies the incoming signal so that it will have the power to deflect the picture tube to the correct height. A vertical linearity control varies the cathode bias of the vertical deflection amplifier. This control interacts with the vertical size control, so that when changing either the vertical size or the linearity, both controls will have to be adjusted.

The signal coming from the vertical deflection amplifier is fed into the vertical deflection coils by means of a vertical output transformer. A vertical positioning control, in conjunction with a vertical positioning switch adjusts the amount and polarity of d-c current so the picture can be centered in the vertical direction on the screen of the picture tube.

Horizontal Sync and Deflection

The output of the sync clippers is also fed into a 6AL5 horizontal sync discriminator through a pair of 470,000-ohm resistors and a 47-mmfd capacitor. The time constant of this combination is such that if either a wide vertical pulse or a narrow horizontal pulse is applied from the sync clipper plate, only sharp pips will result.

The resulting pulse is fed into a horizontal sync transformer. At the same time the sine wave 6K6 horizontal oscillator impresses a sine wave on the secondary of the sync transformer, making one end of the transformer primary have a sine wave 180° out of

phase with the sine wave at the other end. The combination pulse and sine wave causes current to flow in each diode, the resultant being 0 at pin 7 of the 6AL5 sync discriminator if the currents are equal. If the frequency of the oscillator tries to change, the pulse will ride at a different point on the sine wave, causing a change of current in each diode resulting in a change of potential at pin 7. This voltage is then applied to the grid of the 6AC7 reactance tube through a resistor-capacitor network (.005 and .1-mfd capacitors and 470,000-ohm resistor) which filters the voltage. The change of voltage on the grid causes a change of plate current which changes the inductive reactance of the tube (which is connected across the tuned circuit of the oscillator) in such a way as to bring the tuned circuit resonance back to where it was. This automatically keeps the oscillator at the horizontal sync or line frequency rate.

Sync Phase Control

The phase control on the sync transformer adjusts the phase of the pulse with respect to the sine wave. This is adjusted so that the picture tube will have its horizontal sweep at the correct moment in order to place all the picture information on the screen and one in the blanking interval. The hold control on the transformer adjusts the frequency of the oscillator.

The output from the plate of the horizontal oscillator is fed into a differentiating network consisting of 330-mmfd capacitor and 6,800-ohm resistor. The tips of the differentiated pulses shown cause the horizontal sawtooth generator to discharge a sweep generating capacitor, a 680-mmfd unit, in the plate circuit. A discharge network, consisting of the 680-ohm resistor, 10,000-ohm resistor and the 20,000-ohm horizontal drive control, is returned to the most negative point in the power supply through a 100-ohm cathode bias resistor. The horizontal drive control adjusts the shape of the wave being applied to the grid of the horizontal deflection amplifier and therefore affects the horizontal linearity and size. This wave applied to the grid causes the tube to be conducting except for the time the negative pip of the wave is present. Current is made to flow in the horizontal yoke when the tube is conducting. When the tube is cut off, the current in the yoke collapses in a very short time, resulting in a very high negative voltage pulse across the yoke. This high voltage pulse becomes opposite in polarity and therefore positive on the priming of the output transformer

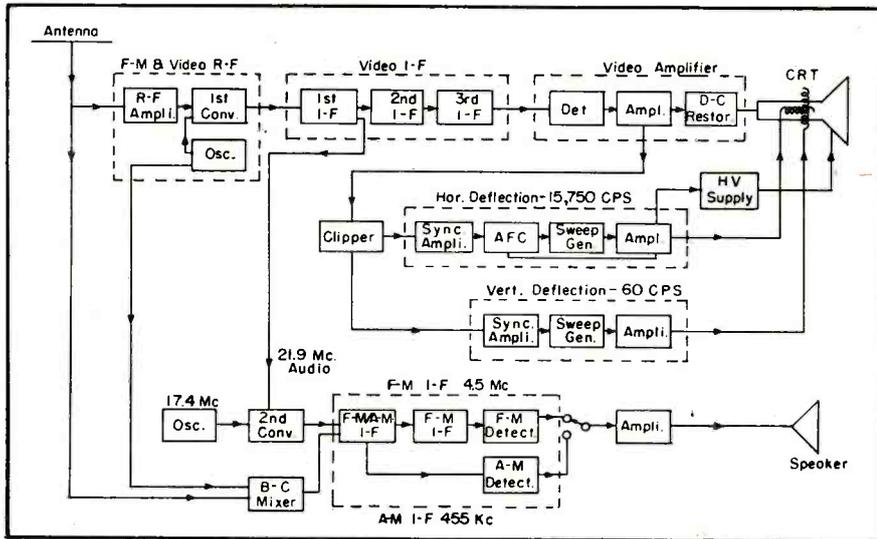


Fig. 2. Block diagram of the G.E. receiver, model 803.

all tubes have heated up and the capacitors are thereby protected from the initial high surge voltage.

Focus Coil and Control

A focus coil is in series with the section of the power supply which delivers 300 volts to most of the circuits, the current drain of these circuits thus providing the focus current. The focus current is adjusted to bring the picture tube to precise focus by means of a 1,000-ohm focus control, which is variable shunted, together with a 250-ohm unit across the focus coil.

and reaches an amplitude of about 4,000 volts.

high voltage rectifier is obtained from the energy in the transformer.

Horizontal Damping and High Voltage Power Supply

The 5V4 horizontal damping tube and a 6,000-ohm damping resistor critically damp the overshoot of the horizontal deflection yoke, which takes place as a result of energy storage in the yoke.

A horizontal linearity network is used to set the time at which the damper will start conducting. By so doing the waveform of the current in the deflection coil is governed to give good linearity. The horizontal positioning control controls the d-c current through the horizontal deflection coils and thus the position of the picture in the horizontal direction.

The high voltage is obtained by first applying a pulse of 4,000 volts at the plate of the horizontal deflection amplifier. By adding more turns to the primary of the transformer feeding the h-v rectifier, the voltage of this pulse can be increased. Then, this high voltage pulse is rectified by the h-v rectifier and then filtered by a 500-mmfd capacitor and applied to the picture tube anode. The heater for the

Sound I-F Channel

The sound is taken off at the plate of the first video i-f and fed into the first sound i-f through a small coupling capacitor. The transformer is tuned to 21.9 mc which is the sound carrier frequency. After the sound signal is amplified in it is limited in the second sound i-f and detected. A 68,000-ohm resistor and .001-mfd capacitor are used in a deemphasis network.

Power Supply

The low-voltage power supply of the receiver is obtained from a pair of 5U4G rectifiers connected for full wave, high current rectification, with conventional filtering.

The low voltage power is applied to the receiver by the closing of a time delay relay. This relay is energized by the diode current of the 6AL5. The relay circuit has been designed so that the relay is energized approximately ten seconds after the power is applied to the television receiver. In this way

G.E. 803

Another interesting new tv model is the G. E. 803. The circuits in this receiver are divided into nine sections: (1) R-f amplifier, converter and oscillator; (2) video and audio i-f amplifier; (3) video detector and amplifier; (4) sync pulse clipper-amplifier; (5) horizontal multivibrator and afc sync; (6) horizontal sweep output; (7) vertical multivibrator and sweep output; (8) high voltage power supply; and (9) low voltage power supply.

R-F Amplifier, Converter and Oscillator (Fig. 3)

The television and f-m r-f amplifier use a 6AU6 connected as a triode grounded-grid amplifier. The antenna is connected into the cathode circuit so as to provide a substantially constant input impedance of 300 ohms to the antenna at all frequencies. With a 300-ohm antenna and transmission line system, this coupling arrangement permits 13 channels and also prevents reflections from being set up on the transmission line. R_2 , a 200-ohm resistor, is used for normal bias. A

Fig. 3. The television and f-m r-f amplifier, converter and oscillator circuits of the G.E. 803.

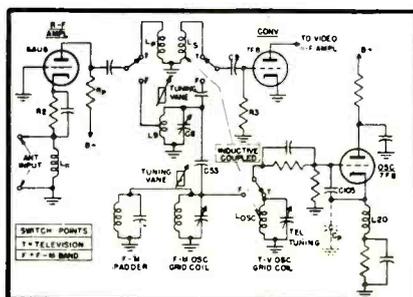


Fig. 4. Broadcast converter and oscillator circuits used in the G.E. 803.


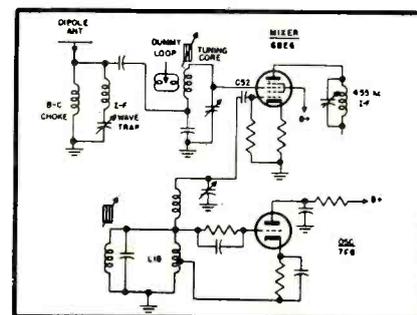


Fig. 5. Video and audio i-f amplifier of the G.E. 803

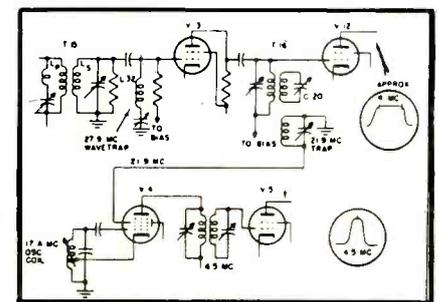

TUBES ARE KNOWN BY

THE COMPANY THEY KEEP



A smart serviceman, you are mighty careful to pick the best in tubes. That's only natural. You have a reputation to protect. Just so does Motorola guard jealously its well-earned reputation as tops in auto radio by selecting only the best components.

Ever notice how often you find Hytron tubes in Motorola auto sets? To rate as one of Motorola's major tube suppliers, Hytron just naturally makes tubes a lot better than good.

Take a tip from leading radio set manufacturers like Motorola. They make it their business to know and use the best in tubes. You, too, can bid goodbye to your tube troubles, and safeguard your reputation by "going steady" with Hytron.

SERVICEMEN—Win These Monthly Prizes!



FIRST PRIZE, AUG.

McMurdo Silver 900A "Varnax," 904 C/R Tester, and 905A "Sparx."



FIRST PRIZE, SEPT.

Jackson 641 Universal Signal Generator.



FIRST PRIZE, OCT.

Weston 769 H-F Electronic Analyzer.



Want one of these deluxe first prizes? Perhaps a \$200 U. S. Savings Bond grand prize? Or one of three \$50 and three \$25 U. S. Savings Bond second and third prizes? Try your hand at any or all of Hytron's monthly contests exclusively for radio servicemen. It's easy. Here's how. Get entry blank

with complete details from your Hytron jobber, or write us. Describe your proposal for a simple, economical shop tool like the Hytron Tube Tapper or Miniature Pin Straighteners. Mail entry to Hytron Contest Editor. Then hold your breath. The finger of the judges may point at you.

SPECIALISTS IN RADIO RECEIVING TUBES SINCE 1921



HYTRON
RADIO AND ELECTRONICS CORP.

MAIN OFFICE: SALEM, MASSACHUSETTS

NEW 9-PIN
Miniature Pin Straightener



Only 49¢ at Hytron jobbers

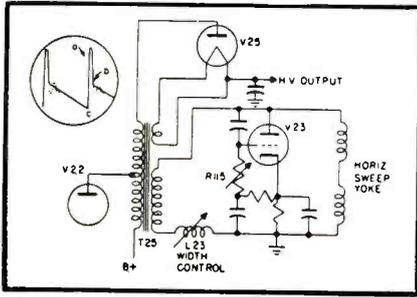


Fig. 8. Horizontal sweep circuit in the 803.

choke, L_x , is placed in series with this cathode resistor to prevent the input impedance from being lowered by the shunting effect of the total stray capacity to ground of the cathode of the tube. The choke value is changed for different channels.

For television operation, the r-f amplifier is coupled to the converter tube by a wide-band transformer consisting of windings L_p and L_s . The windings are overcoupled and self-tuned by the distributed and tube capacities to provide optimum gain and bandwidth. On channel 2, the transformer is triple tuned to prevent the image frequencies of the 88- to 108-mc f-m band from interfering with this channel. For f-m reception in the 88- to 108-mc band, the r-f amplifier is coupled to the converter through the guillotine tuner unit, L_9 .

The triode converter is one section of a 7F8 dual triode. Bias for this tube section is provided by the oscillator voltage appearing in the grid of the converter tube, causing grid rectification charging the grid resistor-capacitor combination, R_3 and C_6 (220,000 ohms and ceramic 47 mmfd).

The oscillator uses the remaining half of the 7F8, and for tv operation, the oscillator voltage is coupled inductively to the converter grid by locating the oscillator grid coil, adjacent to the converter grid coil. For f-m operation, the oscillator voltage is coupled through capacitor C_{53} (3 mmfd ceramic) into the grid circuit tuning circuit, L_6 . The oscillator is a modified Colpits oscillator, oscillation being produced by the cathode-to-grid and cathode-to-plate interelectrode capacities of the oscillator tube. C_{105} (ceramic 6 mmfd) shunts the cathode-to-grid capacity to provide uniform operation. The choke, L_{20} , provides a d-c ground to the cathode of the oscillator tube, but maintains the cathode off-ground at the r-f frequencies. The oscillator operates on the high-frequency side of the r-f signal on all bands.

For broadcast reception (Fig. 4) no r-f amplifier stage is used, the r-f sig-

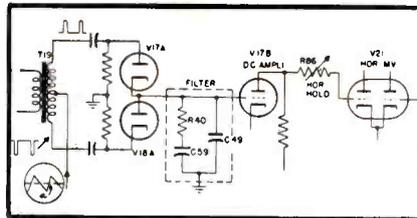


Fig. 7. The horizontal multivibrator and sync circuits of the G.E. 803.

nal being applied directly to a 6BE6 mixer. Here the broadcast signal is converted to 455 kc in the plate circuit. The oscillator section of V_2 operates as the local oscillator for broadcast, operating on the high-frequency side of the incoming signal. The oscillator is connected in a Hartley circuit by taking off the cathode tap on L_{18} which forms part of the grid tank circuit. The oscillator voltage is capacity coupled to mixer grid through C_{52} (ceramic 3-mmfd).

Video and Audio I-F Amplifiers (Fig. 5)

The video i-f amplifier consists of a three-stage band-pass amplifier using three 6AC7 tubes. The transformers are overcoupled and then loaded with resistance to give adequate (approx. 4 mc) band-pass frequency characteristic. A series tuned trap tuned to 27.9 mc is connected in the first i-f amplifier grid circuit to provide rejection of the adjacent channel sound. T_{11} is a broad-band, single-tuned inductance with two 21.9-mc traps coupled to it, which are used to provide rejection of the channel audio. A series tuned 21.9-mc trap is used at the diode stage.

Bias for the video i-f is taken from the horizontal multivibrator. This bias is shorted out on f-m to prevent positive voltage from appearing on the grid of V_8 . The horizontal multivibrator does not operate on f-m so that the bias circuit is returned to B+.

The audio i-f frequency is developed by taking the 21.9-mc sound i-f signal from across one of the traps at T_{16} and applying it to the second converter tube, V_4 . At this tube, the 17.4-mc local oscillator combines with the 21.9-

Fig. 6. Video detector and amplifier of the G.E. tv receiver.

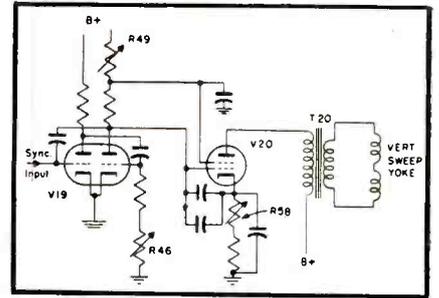
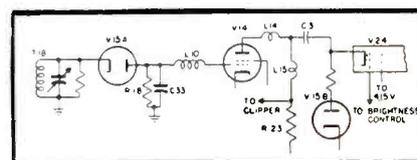


Fig. 9. The vertical multivibrator and sweep output circuit of the G.E. 803.

mc to form a difference frequency of 4.5 mc. At this frequency it is amplified by V_6 , applied to the limiter tube V_6 and then detected.

Video Detector and Amplifier (Fig. 6)

The video i-f amplifier output is applied to a diode rectifier, V_{15A} , and the diode load, R_{18} (15,000 ohms) is connected so as to develop a negative-going signal at this point. This signal is amplified by pentode amplifier, V_{15B} , and then applied to the cathode of the picture tube, V_{24} , through a coupling capacitor, C_3 (1 mfd). The remaining diode section of V_{15} is used to provide d-c reinjection to the picture at the picture tube.

The chokes L_{10} and L_{14} are series-peaking chokes, while L_{16} is a shunt-peaking choke. These are used to obtain good-high-frequency response. L_{10} in combination with C_{33} (10 mmfd) also prevents harmonics of the i-f frequency from being passed through the video amplifier. R_{23} (3,300 ohms) is the V_{14} tube plate-load resistor.

Since the cathode of the picture tube is normally at a positive voltage, by the fact that it is returned to a B+ source, a variable positive voltage is also applied to the grid of V_{24} for control of the brightness or beam current. As long as this grid voltage is less positive than the cathode voltage, the tube beam current will be within its rating. This positive voltage on the grid is controlled by brilliance control potentiometer, R_{108B} (500,000 ohms).

Clipper and Sync Amplifier

The triode section of a 6SN7GT is used to separate the sync pulses from the composite video signal taken off at a 3,300-ohm load resistor. The clipper tube is operated at a very low plate voltage and its bias is derived by grid rectification of the positive polarity video signal applied to the grid. Thus, conduction will occur only during the

sync pulse intervals which are the most positive component of the video signal.

Another portion of the 6SN7GT is used as a horizontal synchronizing amplifier which operates into an afc input transformer. This transformer by virtue of its low inductance acts as a differentiator; that is, in the secondary, the original sync signals become positive and negative pips. Only the pip that is representative of the leading edge of the synchronizing pulse is used.

The vertical synchronizing amplifier tube receives the sync pulse at its grid circuit through an integrator circuit. This integrating circuit accepts the wide vertical pulses and further amplifies them, while the horizontal pulses do not have sufficient energy to charge the integrating circuits and are, therefore, attenuated. The tube is operated as a cathode follower and further integration of the sync signal is provided in its cathode circuit.

Horizontal Multivibrator and AFC Sync (Fig. 7)

In the horizontal sawtooth oscillator there is a 6SN7GT in a conventional cathode-coupled multivibrator circuit. Instead of its frequency being controlled directly by the horizontal sync pulses, it is controlled by a d-c voltage on its controlling grid, the d-c voltage being a resultant of the phase error between the incoming sync signal and a sawtooth voltage derived from the output of the horizontal sweep amplifier. This voltage is the automatic frequency control (afc) voltage.

The afc voltage is developed by the diode-connected triodes by mixing the horizontal sync pulses at the transformer secondary with a sawtooth voltage waveform derived at the output of the sweep amplifier tube. When the sync pulse occurs at the time *a*, shown in the sawtooth waveform drawing in Fig. 7, no voltage will be developed at the output of the filter. However, if the multivibrator runs faster or slower so that the pulse falls at a point other than at *a*, a positive or negative voltage will appear at the filter, which will be amplified by the d-c amplifier V_{17B} and then applied to the grid of the multivibrator. This change in d-c voltage on the grid of the multivibrator will cause it to speed up or slow down so as to cause the sawtooth wave to combine with the incoming sync pulses until the correction voltage becomes zero. With the filter consisting of R_{40} , C_{58} and C_{10} (470 ohms, 1 mfd and .05 mfd), the change

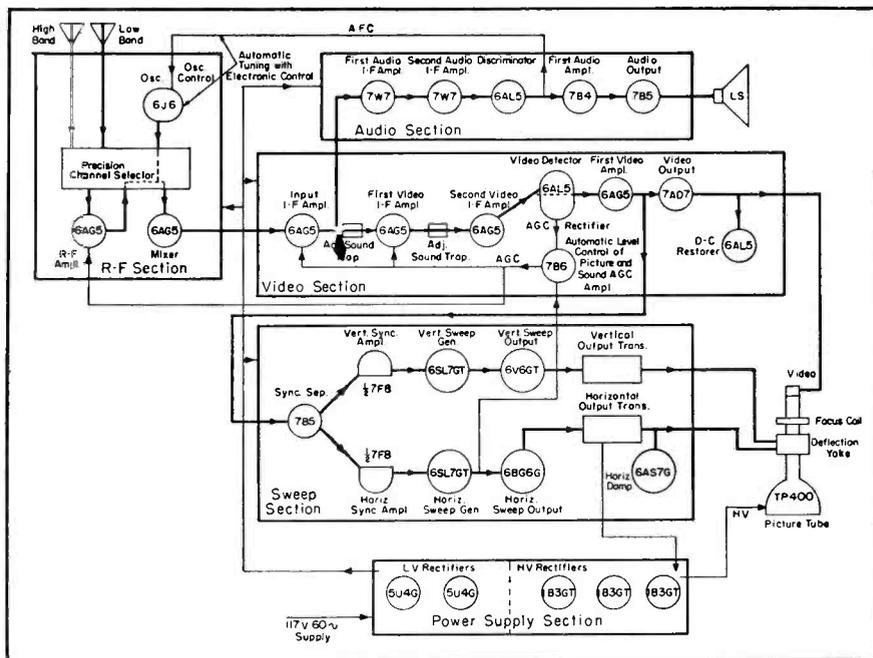


Fig. 10. Block diagram of the Philco projection tv receiver, model 48-2500. (Courtesy Philco)

is relatively slow in controlling the speed, permitting the equivalent of individual frame synchronization instead of each component line. This gives a picture characterized by greater detail than is possible where random noise triggers the directly synchronized sweep generator. The horizontal hold control, R_{80} (100,000 ohms), in conjunction with the cathode-tuned circuit, C_{90} (.05 mfd) and L_{23} , control the free-running speed of the multivibrator. They are adjusted near to the correct frequency during the time when no sync pulses are available.

Horizontal Sweep Output (Fig. 8)

The horizontal sawtooth voltage generated by the multivibrator is shaped and then amplified by a 6BG6G. The output of this tube is coupled to horizontal deflection coils through an impedance-matching transformer, T_{25} . An oscillatory voltage, as shown in the dotted line in the waveshape at the upper left of Fig. 8, which results from the rapid retrace in the transformer T_{25} , is removed by the damping tube, V_{23} . This tube is a dual triode, 6AS7G, and by its use the transient may be dampened, linearity controlled, and the positive overshoot voltage retained for use in the high voltage supply. The linearity of the horizontal trace is controlled by varying the voltage waveshape applied to the grid of V_{23} by potentiometer, R_{115} (250,000 ohms). The horizontal size is controlled by the adjustable iron core in-

ductance, L_{23} , which is in series with the output to the yoke.

Vertical Multivibrator and Sweep Output (Fig. 9)

The vertical sawtooth voltage is generated by a 6SN7GT, V_{19} , connected as a multivibrator. This voltage is coupled directly to a 6V6G vertical sweep output tube, V_{20} , and then to the vertical sweep coils through a impedance-matching transformer, T_{20} . Vertical speed is controlled by changing the time constant of the multivibrator grid circuit by the potentiometer, R_{40} (250,000 ohms). Sweep size is changed by a 100,000-ohm potentiometer, R_{10} , which changes $B+$ voltage applied to the charging network of V_{19} simultaneously with the screen voltage on V_{20} . Vertical linearity is controlled by a correction voltage developed in the cathode of V_{20} being fed back through a capacitor to the grid of the output tube.

Philco 48-2500


Many novel circuit developments are also used in the Philco 48-2500 tv projection model. For instance, channel tuning is used, with an eight-position channel selector supplied with snap-in coils for channels allocated to area in which receiver is to be used.

The video i-f is 26.6 mc, adjacent-channel sound trap 28.1 and the audio i-f 22.1 mc.

In the sound portion, the detector is a ratio-type f-m, 500-kc peak-to-peak
(Continued on page 39)

New Book makes AUTO RADIO REPAIR *twice* as easy!

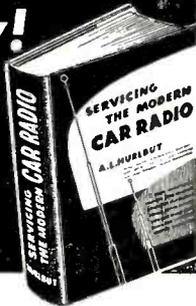Covers all auto
Radio types from
mid-1930's to
present, includ-
ing mobile FM.



Just Out!

SERVICING THE MODERN CAR RADIO

by
A. L. Hurlbut

Second edition, 702 pages,
8½ x 11, 222 illus., over
500 circuit diagrams, \$7.50

Here—written by a practical auto radio expert of 20 years' standing—is everything to help the beginner or experienced serviceman gain profitable skill in the fast-growing field of car radio servicing. A complete guide to the work. Book not only describes installation, testing, and repair methods fully, but also gives needed special facts of car radio circuits, differences between car and home radio servicing problems, shop set-up and business-getting ideas, etc. And invaluable for all jobs is the big gallery of circuit diagrams on hundreds of models, old and new.

Practical facts and methods on:

- getting into the car radio business
- differences between mobile and home radios
- antennas and input circuits
- power supplies
- circuit features
- auto electrical systems
- setting up shop
- car set installations
- antenna installation
- loudspeaker installation
- remedying interference
- servicing procedure
- vibrator maintenance
- loudspeaker servicing
- car-radio alignment
- push-button tuning, etc.

OPPORTUNITY OF A LIFETIME

for alert servicemen, says A. A. Ghirardi,
author of famous radio servicing
books and articles



ALFRED A.
GHIRARDI

"I believe **SERVICING THE MODERN CAR RADIO** represents an opportunity no wide awake serviceman can afford to miss. There are over 9,000,000 car radios—approximately 16 out of every 100 radio receivers in use today—a wonderful field for increasing servicing business; increasing profits, stepping ahead of competition! Good auto radio men are scarce, and this book gives you a gold mine of information you need to cash in on this profitable, fast-growing business."

10 DAYS' FREE EXAMINATION

MURRAY HILL BOOKS, Inc.
(Division of Rinehart & Co.)

Dept. S-88, 232 Madison Ave., New York 16, N. Y.

Send me Hurlbut's *Servicing the Modern Car Radio* for 10 days' examination on approval. In 10 days I will send \$7.50, plus few cents postage, or return book postpaid. Postage paid on cash orders; same return privilege. (Books sent on approval in U. S. only. Price outside U. S., \$8.00, postpaid.)

Name

Address

City (Zone) and State

Occupation

ASSOCIATIONS



RTSEA, Anderson, Indiana

W. D. RENNER and W. W. Hensler of Howard W. Sams & Co., Inc., addressed a recent meeting of the Radio and Television Service Engineers Association, Inc., of Anderson, Indiana, on tv installation and signal distortion. Basing his talk on data developed in the *Photofact* program of tv receiver installation and servicing analysis, Renner pointed out that successful reception of a usable signal at points as far as 150 miles from the telecasting antenna may bring about a modification of the previously considered requisite of line-of-sight limitations for satisfactory television receiver installations. Hensler spoke on the technical aspects of some of the present receivers and apparent trends in design.

At the conclusion of the meeting, honorary memberships in the association were presented to Howard W. Sams, W. D. Renner and W. W. Hensler.

RTSEA officers are Roy Shepherd, president; John Hart, vice president; Vernal Layton, recording and corresponding secretary; John Jones, sergeant-at-arms; William Stevenson and Clyde Nottingham, three-year trustees; Dawson Lewis and Charles Mahoney, two-year trustees; and Myron Seybert and Walter Goodwin, one-year trustees.

Roy Shepherd, president of the Radio and Television Service Engineers Association, Inc., of Anderson, Indiana, presenting honorary memberships in the association to Charles H. Hartley, Indiana State Representative; J. Cromer Aldridge, Indiana State Deputy Attorney General and W. W. Hensler and W. D. Renner of Howard W. Sams & Co., Inc., at a recent meeting during which Hensler and Renner discussed television installation techniques. An honorary membership was also awarded to Howard W. Sams at this meeting.



MSRSA, Harrisburg, Pa.

GEORGE E. HARDY, secretary of the Mid-State Radio Servicemen's Association of Pennsylvania, reports that the nomination of officers took place at the July meeting, and an election was scheduled for August.

At the July meeting Willie Fleicher of Friends Radio of Philadelphia spoke on *record changers*.

At the August session, Robert Miller of D & H Distributing Company of Harrisburg was scheduled to talk on *oscilloscopes* and their use to the Service Man.

In September the installation of officers will take place. And at this meeting Russell Knerr of Knerr's, Inc., of Harrisburg will speak on *multivibrators* and their use in television.

REAW, Waco, Texas

THE FIRST MEETING of the recently organized Radio Electronic Association of Waco was held recently.

The association was formed because of a projected licensing law, which O. B. Howell, REAW treasurer, reports was planned only to add income to the city treasury.

At one of the meetings two sound films were shown: One on transmitters, the other on television.

TEN YEARS AGO

From the Association News Page of **SERVICE, August, 1938**

RSA REPORTED that six more associations voted to affiliate with them: Green Bay, Wisconsin; Danville, Illinois; Decatur, Illinois; Pittsburgh, Pa.; Fargo, North Dakota and Minneapolis, Minnesota. . . . An extension course for the professional Service Man announced by RSA, was available to members at a nominal charge. . . . A National Speakers Bureau was announced by RSA. . . . WGN, WMAQ, WENR and WLS of Chicago concluded a very successful *Better Radio Reception Week* in cooperation with RSA. Some 30 spot announcements, commenting on the abilities of RSA men and mentioning a central 'phone number for membership contact, were heard over these stations during the week. . . . The Duluth Chapter voted to have one meeting a month during the summer. . . . H. B. Eilers delivered a talk on facsimile before the boys. . . . The National Radio Service Association of Houston had its name changed to the Houston Chapter of RSA. . . . The Lansing Chapter held its third regular meeting and elected a vice chairman, Clarence Kachelski to preside in the place of the chairman. . . . Harry P. Bridge, president of the Harry P. Bridge Company, delivered a talk before the Philadelphia Radio Servicemen's Association urging Service Men to spend not less than 5% of their gross receipts for some form of advertising or promotional activity. . . . A television course had been planned by the Radio Service Association of California. Dave Atkins of Atkins and Brown delivered a talk on r-f amplifier and transmitter design at one meeting. . . . Officers of the Fremont Chapter were announced: John Mutschler, chairman; Harold Kelsey, vice chairman; Don Daymon, secretary; Frank Marx, treasurer; and Gilbert Anderson, sergeant-at-arms. . . . A report on the excellent response to the RSA display at the June Trade Show was issued.

RTG, Rochester, N. Y.

THE ANNUAL RADIO TECHNICIANS GUILD picnic was held in July at Durand Eastman Park.

The membership committee is planning a drive for early in the fall.

According to Ed Fisk, chairman of the publicity committee, each member is being asked to get at least one petition in an attempt to double membership.

TRANSVISION


BIGGEST VALUES in TELEVISION! Large-Image, Direct-View TV Kits at Low Cost!

Kits Engineered for EASE of ASSEMBLY and Top Performance.
Cabinets designed and built for Beauty, Utility, Durability.


NO TECHNICAL KNOWLEDGE REQUIRED for ASSEMBLY



Console Model 7CL

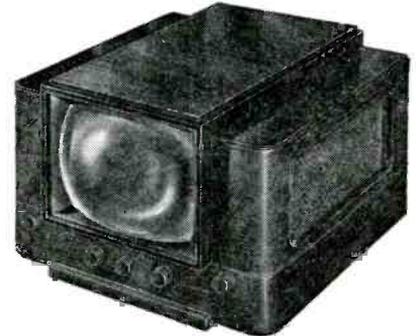

MODEL 10BL
Gives 115 Sq. In. Picture

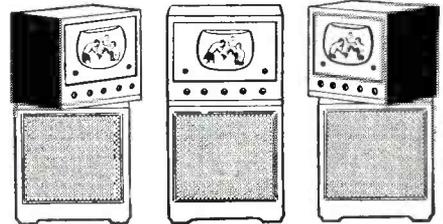

Roto-Table for full 180° Visibility

TRANSVISION manufactures the most extensive line of high quality *Television Kits, Cabinets, and Components*. Models illustrated and listed here are only representative of Transvision's leading values. See your distributor.

MODEL 10BL, TV/FM Kit, gives 115 sq. in. picture; complete FM Radio; receives all channels; streamlined cabinet.....NET \$299.00
Roto-Table for Model 10BL, gives full 180° visibility.....NET \$ 24.95

MODEL 7CL, TV Kit, gives 60 sq. in. picture; console cabinet complete with Roto-Table; streamlined design. NET \$199.00

MODEL 7BL, same as 7CL except that it is a table model. NET \$189.00

All prices include cabinets, tubes, antenna, and 60 ft. of lead-in wire. (Models 7CL and 7BL can be supplied with complete FM Radio for small additional cost.)



**FREE—
Fascinating
BOOKLET
On Television**

Illustrated 20-page 2-color booklet gives you excellent basic information on television. Call at your distributor's for a FREE COPY; or write to us for names of distributors.

"SERVICE NOTES"

by Transvision . . . the Key to Successful Television Servicing . . . Confidential Television Notes and Information, product of experience with over 20,000 television sets. Complete with photos, diagrams. Worth a small fortune. Cost is only . . . \$1.95 NET



All prices 5% higher west of Mississippi; all prices fair traded.
For further information see your distributor, or write to:


TRANSVISION, INC. Dept. 5 **NEW ROCHELLE, N. Y.**
In Calif.: Transvision of California, 8572 Santa Monica Blvd., Hollywood 46

For TELEVISION, it's TRANSVISION—the complete line of High Quality Kits, Cabinets, Antennas, Lenses, Filters, Boosters, Components—Ask your distributor!

THE FASTEST TV ANTENNA ASSEMBLY

YOU + JFD "QUIK-RIG" = 30 SECONDS!

*As Simple
As Opening
An Umbrella*

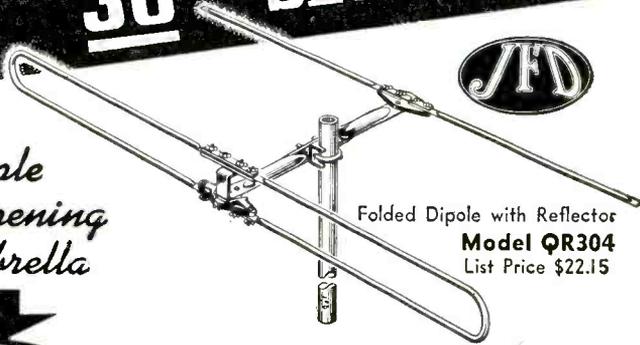

Folded Dipole with Reflector
Model QR304
List Price \$22.15

- ★ The simplest — fastest — easiest antenna assembly on the market today!
- ★ Completely pre-assembled.
- ★ No special tools or knowledge required.
- ★ Cuts installation time to the bone.

JFD Super-Beam Quik-Rig Antennas are available in a wide range of models to fit all requirements. Write for complete Quik-Rig catalog.

Ask your jobber to show you the new JFD Quik-Rig Antenna line.

JFD MANUFACTURING CO. Inc.

4111 FORT HAMILTON PARKWAY, BROOKLYN 19, N. Y.

KEEP POSTED ON ELECTRON TUBES

Use this convenient coupon for obtaining the RCA tube reference data you need.

RCA, Commercial Engineering, Section HW62, Harrison, N. J.
Send me the RCA publications checked below. I am enclosing \$..... to cover cost of the books for which there is a charge.

Name _____
Address _____
City _____ Zone _____ State _____

- Quick-Reference Chart, Miniature Tubes (Free). [A]
- HB-3 Tube Handbook (\$10.00)*. [B]
- RC-15 Receiving Tube Manual (35 cents). [C]
- Receiving Tubes for AM, FM, and Television Broadcast (10 cents). [D]
- Radiotron Designers Handbook (\$1.25). [E]
- Quick Selection Guide, Non-Receiving Types (Free). [F]
- Power and Gas Tubes for Radio and Industry (10 cents). [G]
- Phototubes, Cathode-Ray and Special Types (10 cents). [H]
- RCA Preferred Types List (Free). [I]
- Headliners for Hams (Free). [J]


*Price applies to U. S. and possessions only.

TUBE DEPARTMENT

RADIO CORPORATION OF AMERICA
HARRISON, N. J.



Fig. 2. In this circuit of an a-c/d-c receiver, we see how the cathode terminal of the r-f amplifier socket is generally connected to one side of the power line either directly or through a small biasing resistor. The accidental insertion of a 35B5 or 50B5 into the 12BA6 socket would connect one side of the power line to the tuning capacitor and loop antenna.

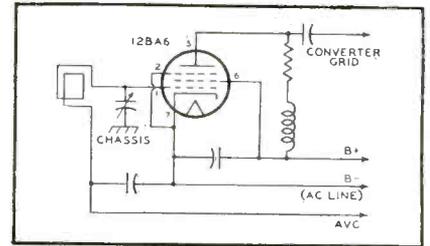

Tube News

(Continued from page 12)

the wrong tube in the socket. The hazard can be eliminated by the use of blocking capacitors between the 12BA6 grid 1 and the tuning capacitor, and shunt-feed resistors between the avc line and the signal or control grid of the first stage (r-f or converter).


With either the 35C5 or the 50C5, a possible, but easily avoidable hazard exists in a circuit similar to that of Fig. 4. In such a circuit, insertion of either tube into the 12AT6 socket can result in a connection of the power line to the loop antenna and tuning-capacitor terminal, if the diode plate connected to pin 5 is used to keep the avc line from going positive in case of a gassy tube (gas-gate diode). This possibility, however, can be easily avoided by using diode D₁ connected to pin 6 as the gas-gate diode and diode D₂ connected to pin 5 as the detector diode, as shown in Fig. 4.

Types 6BJ6, 6BH6 and 12AW6

At high frequencies, the inductances of the lead wires and the mutual inductances between the lead wires of a tube can cause feedback currents and voltages of appreciable magnitude. It has been discovered that the mutual inductance between the control-grid leads and the suppressor-grid leads in types 6BA6 and 6AU6, in combination with the plate-to-suppressor capaci-

Insertion of a 35W4 in a 12AT6 socket can also cause a shock hazard. In this instance the gas-gate diode should be eliminated.

Fig. 3. Here we note how the accidental insertion of a 35B5 or 50B5 would also cause damage to the receiver, with one side of the power line being connected from the cathode of the i-f amplifier through the i-f grid, avc line and loop antenna to the signal grid of the converter.

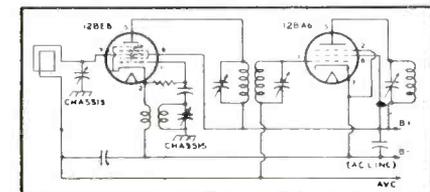

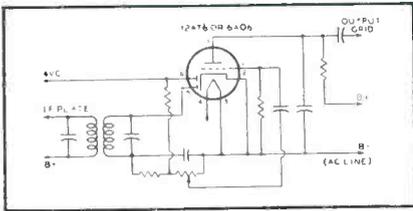


Fig. 4. Avoiding the Figs. 2 and 3 hazards by using diode D1 connected to pin 6 as the gas gate diode and diode D2 connected to pin 5 as the detector diode. The 35C5 or 50C5 could be used in this type of circuit without any fear of damage.


tance and the control-grid-to-suppressor capacitance, causes feedback. This feedback, though negligible at the normal operating frequencies of these tubes, is equivalent to an increase in control grid-to-plate capacitance at high frequencies. At high frequencies, alternating voltage at the plate causes an appreciable current to flow through the plate-to-suppressor capacitance and the suppressor-grid lead. This current induces voltage in the control-grid lead because of the mutual inductance between these two leads, and the induced voltage causes a current to flow in the control-grid circuit through the grid-to-cathode capacitance of the tube.

In the 6BA6, 12BA6, 6AU6, and 12AU6 r-f pentodes the control grids and suppressor grids are connected to adjacent pins. In the newer types, 6BJ6, 6BH6, and 12AW6, pin 2 is used for the cathode connection and pin 7 is used for the suppressor-grid connection (Fig. 1), providing a low feedback capacitance at 20 mc or higher.

The increase in feedback capacitance for the 6BA6 is negligible at 10.7 mc, the usual i-f for f-m receivers. However, the increase may be significant at tv sound intermediate frequencies in the vicinity of 20 mc when a narrow bandwidth is used. At frequencies of 20 mc or higher, the use of the 6BJ6, 6BH6, and 12AW6 will prove beneficial where the gain is limited by

(Continued on page 36)

Fig. 5. A diode filter circuit. C1, C2 and R1 are contained in a three-terminal unit.

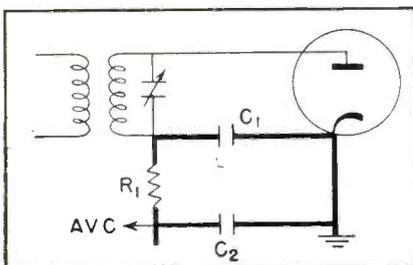

Everybody agrees
ATR AUTO RADIO VIBRATORS
are TOPS



AUTO RADIO VIBRATORS
have Ceramic Stack Spacers



A Complete Line of Vibrators . . .

Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction, featuring Ceramic Stack Spacers for Longer Lasting Life.

Backed by more than 17 years of experience in Vibrator Design, Development, and Manufacturing--

ATR PIONEERED IN THE VIBRATOR FIELD.



ATR New Models

"A" BATTERY ELIMINATORS

For DEMONSTRATING AND TESTING AUTO RADIOS

New Models . . . Designed for Testing D. C. Electrical Apparatus on Regular A. C. Lines. Equipped with Full-Wave Dry Disc Type Rectifier, Assuring Noiseless, Interference-Free Operation and Extreme Long Life and Reliability.

ATR New Models

STANDARD AND HEAVY DUTY INVERTERS

For Inverting D. C. to A. C. . . . Specially Designed for operating A. C. Radios, Television Sets, Amplifiers, Address Systems, and Radio Test Equipment from D. C. Voltages in Vehicles, Ships, Trains, Planes and in D.C. Districts.

NEW MODELS
NEW DESIGNS
NEW LITERATURE
See your jobber or write factory

AMERICAN TELEVISION & RADIO Co.
Quality Products Since 1931
 SAINT PAUL 1, MINNESOTA-U.S.A.

**QUALITY, FIDELITY
FOR FM, MONITORING,
RECORDING, AND
OTHER SOUND USES**

**WIDE RANGE and
PA SPEAKERS**

GET HIGH quality sound reproduction throughout the tonal range with Utah Wide Range Speakers. These Wide Range Speakers assure exceptionally brilliant response in the middle range plus extension of the higher frequencies to 10,000 cps. Unusual sound requirements in FM, laboratory, monitoring, or recording work, often can be met with Utah Speakers. Ask about the SP8JW and SP12LW.

WHEN YOU have a public address job use SP8K, SP12M, SP12P. Utah Speakers are quality built and severely tested. They are completely dust proofed and have pot covers. Write for catalog today!



UTAH RADIO PRODUCTS
HUNTINGTON, INDIANA
 DIVISION OF INTERNATIONAL DETROLA CORPORATION
 EXPORT DIVISION: MORHAN EXPORTING CORPORATION
 NEW YORK, NEW YORK

BUILT STRONGER TO LAST LONGER

Tube News

(Continued from page 35)

feedback considerations rather than by bandwidth requirements.

[Data based on copyrighted material prepared by RCA.]

Diode Filters

THE ERC¹ DIODE FILTER is a π section filter circuit whose function is to filter the carrier frequency from the demod-

ulated signal at the detector stage; Fig. 5. The diode filter is made in two types, tubular and flat. The tubular has a maximum o.d. of .250" and length of .725". The flat diode is .250" square. The flat diode filter normally is made of two equal 100-mmfd capacitors and a 47,000 ohm resistor. The tubular diode filter is furnished in capacities ranging from double 50 mmfd to double 100 mmfd and resistances from 200 ohms to 22 megohms.

¹Electrical Reactance Corp.

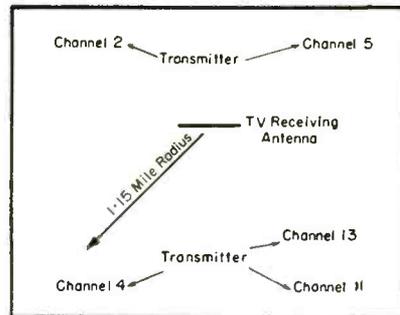


Fig. 12. Another typical problem of antenna spotting for reception of channels 2, 5, 4, 11 and 13.

TV Antennas

(Continued from page 16)


quency tv station, when the high-frequency attachment is properly positioned for best high-frequency channel reception. This condition manifests itself by a *leading ghost* appearing on the tv pattern of the low-frequency tv station, when the high-frequency attachment is installed.

(A separate transmission line for the high-frequency attachment will alleviate this interaction, provided a 200-mc anti-capacity switch is used at the set end of the transmission line, so that the signal cannot combine through the antenna switch. Some switches used successfully on the low-frequency tv channels (54-88 mc) are inadequate for high-frequency channel (174-216 mc) isolation. In selecting antenna switches it is important to remember that a switch capacity of 10 mmfd has a reactance of less than 100 ohms at 200 mc.)

(c) When the loading effect of the high-frequency attachment reduces the signal strength on any of the tv stations, picked up by the larger antenna array.

Problem: Fig. 12 shows an antenna located at a point with high and low-frequency tv stations in all directions.

Fig. 13. Problem encountered for antenna location when 45 miles from transmitters.

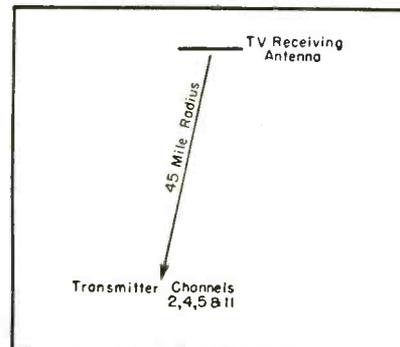

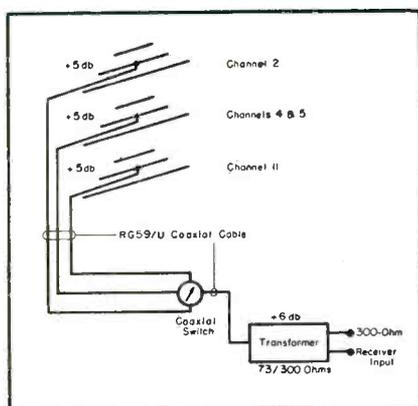


Fig. 14. Three-array system for channels 2, 4, 5 and 11 fed to coaxial switch and a trifilar transformer (RCA).

This is currently a problem in the Baltimore-Washington area and will shortly be as serious a problem in the New York and N. J. area when WOR-TV installs its tv station in New Jersey.

A simple rotating dual dipole assembly which is remotely controlled at the tv receiver is a favorite solution to this problem. The longer dipole arms are cut to the mean frequency of the low tv channel band (2-6) and the shorter dipole arms are set for the mean frequency of the high tv channel band (7-13). The high and low channel dipoles, being at right angles to each other, have no interaction.

A simple wide-band array without reflectors may pick up sufficient signal on all tv channels if the tv stations are close enough and of sufficient signal strength to withstand a compromise antenna adjustment. The wideband antenna array (selected in accordance with *Rule of Thumb* item *d*) should be directed toward the stations transmitting the weakest signals into the area. High-frequency attachments with reflectors may also be installed on top of a low-frequency array (without reflectors) with the considerations described under *problem 3*.

Problem 5: Fig. 14 shows a tv receiver located in a secondary signal area for all tv stations.

When a relatively expensive installation can be made to solve this type of installation problem, a stacked array should be used. In this setup there should be one dipole, director and reflector for channel 2, a second for channels 4 and 5 and a third for channel 11 which may be circuited as shown in Fig. 14. It will be possible to secure a gain of approximately 11 db for each channel with this arrangement.

Flexibility makes

"the Service Man's Line"

Brach antennas . . . long known for dependability . . . maximum reception . . . trouble-free operation . . . durability and ease of installation . . . now feature an added extra . . . Flexibility. Unique construction features aid the service man in making a more rapid installation to which future additions or modifications can be easily made.

1. FLEXIBILITY A complete line designed with basic antenna parts which are convertible to more complex arrays as required by location and reception problems.

2. COMPLETE KITS Each antenna model is independently designed and furnished in a completely packaged kit containing all necessary hardware, download (when desired) and the Universal Base Mount . . . ready for installation.

3. PRE-ASSEMBLY Each antenna is factory pre-assembled as far as possible, ready to erect. Complete and simple installation instructions. Saves valuable man-hours on the roof.

4. MECHANICAL STRENGTH Weather - tested for durability, Brach Antennas feature a husky steel mast, rigid connections, sturdy base mount, neat appearance. All parts corrosion resistant.


5. SUPERIOR RECEPTION Designed with engineering "know-how". All Brach antennas are factory pre-tuned, matched for 300 ohm transmission line with large diameter aluminum elements for better signal pick-up. Directivity patterns and standing wave ratios available upon request.

New! Tops in TV! HI-LO ROTATABLE Antenna

Here it is! A rotatable antenna to provide peak performance with any station at any time. Brach introduces the new "Superview" Rotatable, covering both high (174 MC to 216 MC) and low (88 MC to 108 MC) TV bands. High band extension available for easy addition to standard dipole array for separate orientation. No more multiple images. No more "weak" stations. Brach's Superview HI-LO assures television reception that's tops. Make sure and investigate the new Superview line today.

Write for Free Brach catalog showing complete line of TV and FM antennas and accessories.


SEND FOR CATALOG No. S304

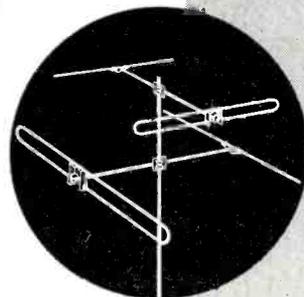

L. S. BRACH MFG. CORP.

200 CENTRAL AVENUE, NEWARK, N. J.

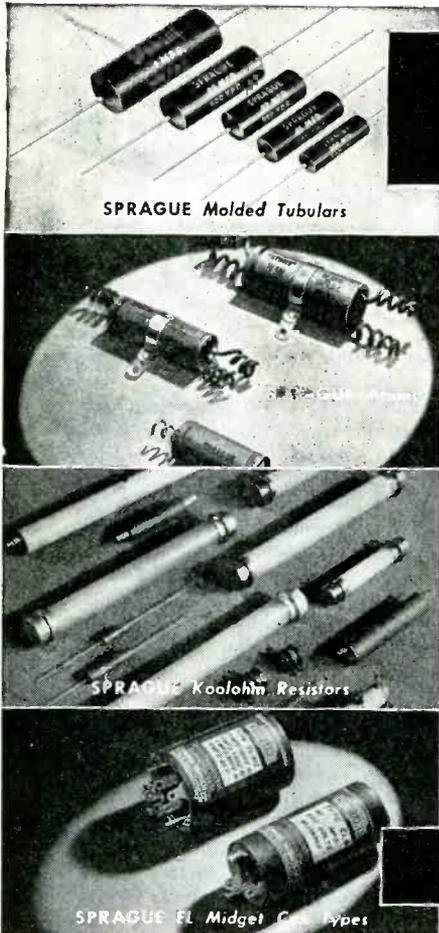WORLD'S OLDEST AND LARGEST MANUFACTURERS OF RADIO ANTENNAS AND ACCESSORIES



YOUR REPUTATION...

and your customers deserve the best!

SPRAGUE

These are but a few of the many capacitor and resistor types in the complete SPRAGUE Line. "Specify SPRAGUE" in all your repair work. Build a reputation for a quality job while you are building a more profitable business!

WRITE FOR THE COMPLETE CATALOG

SPRAGUE PRODUCTS COMPANY, North Adams, Mass.

JOBGING AND DISTRIBUTING ORGANIZATION FOR THE PRODUCTS OF THE SPRAGUE ELECTRIC COMPANY

F-M Tuner

[See Front Cover]

THE SEVEN TUBE a-c f-m tuner, shown on the cover (Howard Radio, model 482) features a 6J5 audio booster stage and volume control system.

There is one stage of r-f in the


tuner, a 6BA6, feeding into a 12AT7 dual diode which is used as a converter and oscillator. This is followed by two stages of iron core i-f with a pair of 6BA6s. Then we have an iron-

core discriminator transformer, feeding a 6AL5 in a ratio-detector stage.

A heavy duty three-section capacitor is used in the power supply filter system; 50 x 30 x 30 mfd at 130 volts.

The tuning drive has a 14:1 ratio. Sensitivity of the tuner is less than 5 microvolts.

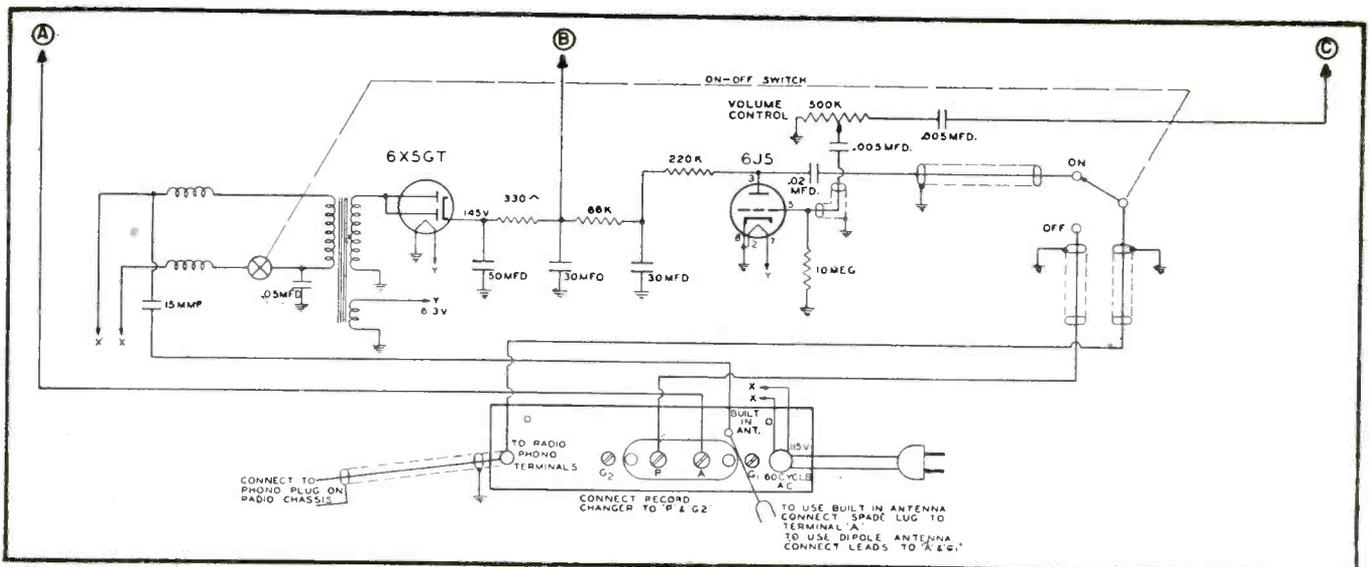Circuit of the audio booster stage and power system for the f-m tuner.



Ser-Cuits

(Continued from page 31)

bandwidth. A diode-type a-m is used as a video detector.

The projection system is a modified, wide-aperture, Schmidt optical, using a 12" spherical mirror and 7" corrector lens. Throw is 33.5". A 4" projection tube, TP400, is used with magnetic deflection and combined electro and permanent-magnet focus.

The transmission line is a non-resonant, 300-ohm, balanced type.

There are 29 tubes in this model: Eight loktals (1-7AD7, 1-7B4, 2-7B5, 1-7B6, 1-7F8, 2-7W7); ten octals (3-1B3GT, 2-5U4G, 1-6AS7G, 1-6BG6G, 2-6SL7GT, 1-6V6GT); ten miniatures (6-6AG5, 3-6AL5 and 1-6J6).

R-F Section

The entire r-f assembly is contained on a separate sub-chassis, which is shock-mounted onto the main chassis.


The output of the r-f amplifier is impedance-coupled to the mixer. The mixer and oscillator coils are wound on the same snap-in coil form, and are inductively coupled on channels 2 to 6 and capacitively coupled on channels 7 to 13 to secure the proper amount of oscillator injection. The triode oscillator, which is of the Colpitts type, is shunted by a reactance tube (oscillator control), which is controlled by the d-c voltage obtained from the output of the f-m ratio detector. When a positive voltage is applied to the grid of the reactance tube, the oscillator frequency is decreased; conversely, with a negative voltage the frequency is increased. Since the output of the f-m detector, at the point from which the control voltage is taken, varies in polarity from a negative maximum through zero to a positive maximum in accordance with the frequency of the signal, any change in oscillator frequency changes the frequency of the sound carrier i-f and produces a correction voltage. In this manner, the oscillator is maintained constantly at the correct frequency, and a maximum of stability is obtained, regardless of the aging of tubes or other components.

The output of the mixer is applied to input i-f impedance coupler.

Video Section

The i-f signals present in the plate circuit of the mixer are selected by the input i-f impedance coupler and applied to the grid of the input i-f amplifier. The amplified i-f signal


(Continued on page 40)

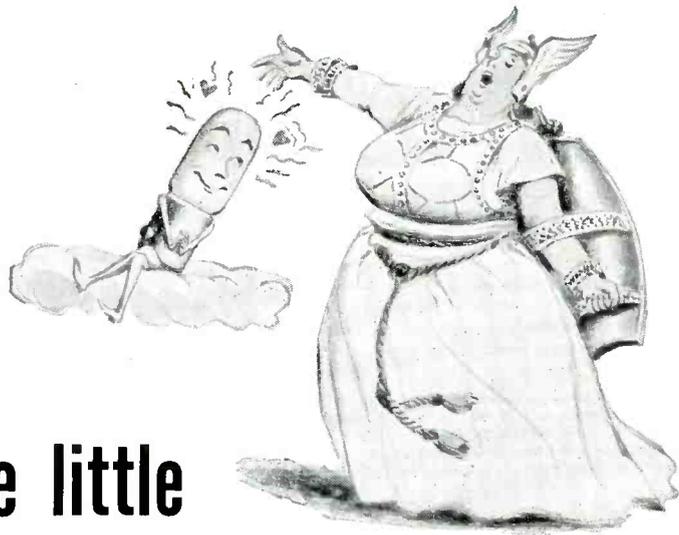

The little lamp that learned to love sopranos

TIME was when certain high notes played havoc with radio panel lamps. A soprano's "high C" often caused vibrations severe enough to tear the filament apart. G-E research engineers investigated. By making the filament supports longer and moving the base closer to the coil, they greatly reduced the effects of vibration. Now G-E dial lamps can take the shrillest soprano in stride!

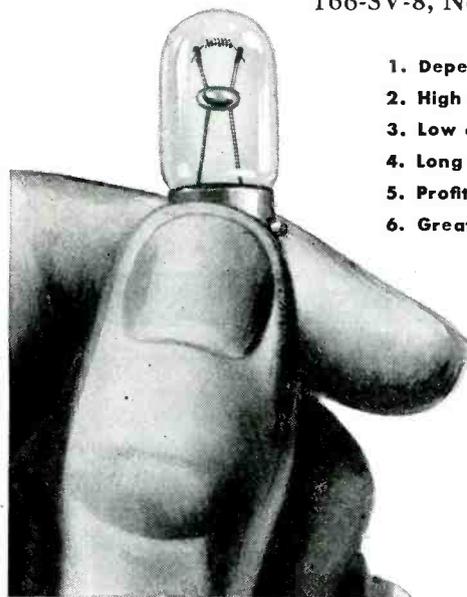For information on prices and types of G-E miniature lamps, see your nearby G-E Lamp Office. Or write to General Electric Company, Division 166-SV-8, Nela Park, Cleveland 12, Ohio.



1. Dependable, trouble-free performance.
2. High level of maintained light output.
3. Low current consumption.
4. Long life.
5. Profitable to handle.
6. Greater dealer acceptance.



G-E LAMPS

GENERAL ELECTRIC

THE NEW E-SERIES BY NEWCOMB

A LOW-PRICED LINE OF SUPERIOR UTILITY AMPLIFIERS

In addition to the incomparable Deluxe K-Series and Standard H-Series Amplifiers, Newcomb now offers the new, economy E-Series. Phono-tops, portable assemblies and mobile units are included in this new line designed to fill the needs of those who want a superior utility amplifier but must confine their purchase to the lower price range.

Model E-10: An outstanding value in the public address market, the E-10 delivers a full 10 watts from push-pull 6V6 tubes in a multistage inverse feedback circuit... has inputs for microphone and phonograph and a full range tone control. With tubes less cover, retail **49.50**

Model E-17: 17 watts of undistorted audio from push-pull 6L6 tubes. Inputs for a microphone and phonograph... full range tone control... multistage inverse feedback. With tubes and cover, retail... **79.50**

Model E-25: A really fine utility amplifier for better performance, more dependable operation. Full range tone control, 25 watts of undistorted power and inputs for 2 mikes and a phonograph make the E-25 easily applicable to most sound jobs. Inverse feedback assures lowest distortion. With tubes and cover, retail... **99.50**

Model E-25MP: Mobile unit with phono top. Ruggedly built with best materials and workmanship. An achievement in functional simplicity, dependability, performance and economy. A full 25 watts at less than 5% distortion from either 117 volts a.c. or a 6 volt storage battery. Inputs for two mikes, one phono; multistage inverse feedback. With tubes and cover, retail... **169.50**

Model E-50: 50 watt performance leader in its price class. Multi-stage inverse feedback and push-pull parallel 6L6 tubes assure low distortion. Two mikes mixed, or one mike, one phono. Impedance selector simplifies speaker matching. With tubes and cover, retail **154.50**

All models Underwriters Approved.


Send for complete details!



NEWCOMB AUDIO PRODUCTS CO.

Dept. E, 6824 Lexington Ave., Hollywood 38, Calif.

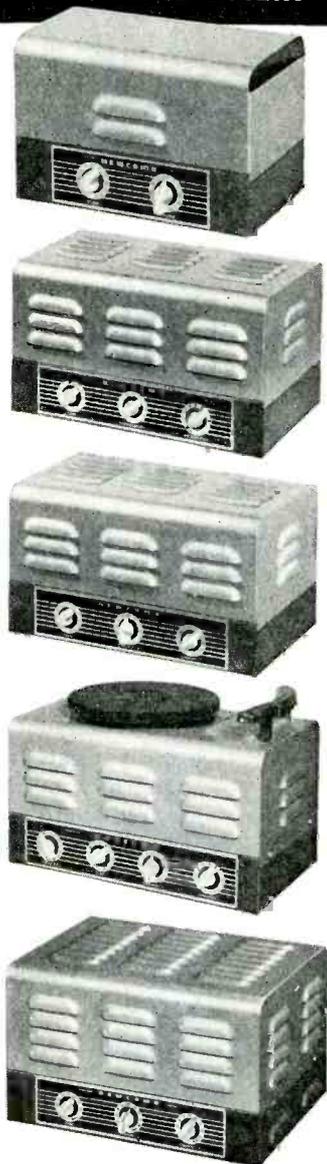NOT MERELY AS GOOD AS THE OTHERS... BUT BETTER THAN ALL OTHERS



to the adjacent-channel audio-i-f signal (28.1 mc), and offers a high impedance to the adjacent-channel audio-i-f signal, if present. (Because of channel allocation, the adjacent-channel sound appears on some channels as a 32-mc i-f. Since this frequency is not within the pass band of the receiver, no interference results.) The amplified video i-f signal is applied to the third video i-f impedance coupler, which is tuned to slightly different frequencies. (In later receivers, an additional sound trap has been included. The trap is tuned to 22.1 mc to afford further protection against any audio-i-f signal which may have passed the first sound trap.)

The video detector rectifies the negative portion of the video i-f signal. The resultant negative video signal is amplified by the first video amplifier and the video output tube, and is applied to the grid of the picture tube. The first video-amplifier circuit contains a sharply tuned rejector trap, adjusted for 4.5 mc. This trap is placed in the plate circuit of the first video amplifier to eliminate interference that might be produced by the beating together of the sound and picture carriers, which on all channels are 4.5 mc apart. High and low-frequency compensation is employed to provide a video response from approximately 30 cycles to 4 mc. D-c restoration is accomplished by using a diode to establish a d-c bias according to picture content on the grid of the picture tube, thus insuring that the picture brightness changes only with each change of scene, not with each frame.

Automatic control of picture and sound (agc) is achieved by using the sync tips to provide a control voltage. Since the sync tips are always at the same modulation level but vary in amplitude with the strength of the signal, they provide a suitable reference for agc. One half-section of the video-detector diode is used to rectify the sync tips and to furnish the control voltage for the agc amplifier tube. The agc amplifier is supplied with a portion of the horizontal-sweep-generator voltage, which it amplifies and rectifies under control of the agc voltage output from the agc rectifier. Enough agc voltage is available at all times to regulate the gain of the r-f amplifier, input i-f amplifier, and first video i-f amplifier stages, so that any fading or change in strength of the incoming signal is compensated for by a change in the gain of these stages.

Sweep Section

A portion of the video signal is taken from the screen of the first video

signal (22.1 mc). Since the plate supply to the input i-f amplifier is connected through the first audio-i-f transformer, the audio i-f signal is transferred to the first audio-i-f stage, and very little, if any, of the audio-i-f signal remains in the video section.


The video-i-f signal is amplified by the first video-i-f amplifier stage, and passed through the second video i-f impedance coupler. This transformer is tuned to pass the video signal, but is peaked at different frequencies to achieve the desired pass band. The adjacent-channel-sound trap is tuned

Ser-Cuits
(Continued from page 39)

in the plate circuit of the input i-f amplifier consists of both video and audio i-f signals, together with adjacent-channel and audio i-f signals, if present (adjacent-channel video i-f signals, when present, are not within the receiver pass band). The plate and grid windings of the first video i-f impedance coupler are adjusted to accept the video i-f signal, while the sound trap is adjusted to reject the audio-i-f

CHECK!

the GREENOHM JR.

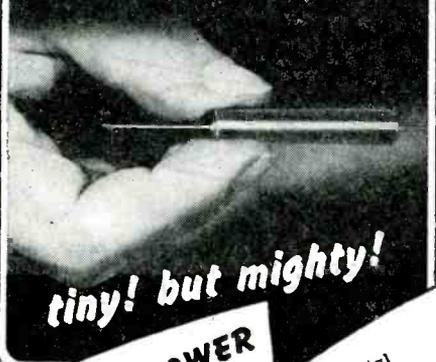

tiny! but mighty!

A REAL POWER RESISTOR!

Wire winding on fibre-glass core. Axial bare pigtail leads clinched to ends. Encased in ceramic tube and sealed with exclusive Greenohm inorganic cement.

STAY-PUT -- TROUBLE-PROOF!

Won't blister, crack, change shape. Don't confuse the Greenohm Jr. with usual plastic-molded resistors. This is a real power resistor, ceramic-cased, in miniature form.

FITS IN TIGHT SPOTS!

Type C7GJ—1-3/4" long x 5/16" dia. 2" leads. 7 watts. Practically zero to 5000 ohms. Smaller Type C4GJ—1" long x 5/16" dia. 4 watts. Up to 1000 ohms.

CLAROSTAT



Ask your Clarostat jobber for latest catalog. Or write us.

Controls and Resistors

CLAROSTAT MFG. CO., Inc. · 285-7 N. 6th St., Brooklyn, N. Y.

In Canada: CANADIAN MARCONI CO., Ltd. Montreal, P.Q., and branches

amplifier and applied to the grid of the sync-separator tube so that the synchronizing-pulse portion of the video signal may be used to control the horizontal and vertical-sweep generators. The sync-separator-tube potentials are such that the video portion of the composite video signal applied to its input circuit is insufficient to operate the tube, and only the *blacker-than-black* portion of the tv signal is passed. This blacker-than-black portion contains the horizontal and vertical synchronizing and blanking signals, each of which is greatly different in duration and recurrence rate from the others. The output of the sync separator is applied to the vertical-sync amplifier and the horizontal-sync amplifier through separate *r-c* coupling circuits, each with a different time constant.

The sweep generator is a blocking oscillator operating at a free-running frequency slightly lower than the horizontal-sweep rate of 15,750 cps. When the pips are applied to the grid, the blocking oscillator operates in synchronism with the horizontal sync pulses.

The Micro-Lens Projection System

A TP400 projection-type picture tube is mounted at a slight angle to the axis of the spherical mirror to provide proper optical positioning. The mounting of the tube is such that for correct optical focusing it can be moved through three axes: The *Z* axis (in and out), the *Y* axis (top and bottom) and the *X* axis (side to side). This projection tube produces an image which is approximately fifteen times more brilliant than that of a direct-viewing picture tube, an extreme brilliance required because of unavoidable reduction of light intensity in the optical system.

[Data based on copyrighted material prepared by Philco.]

[To Be Continued]

Rig-Fast TV & FM Antennas

For clear, sharp signals — sell the Rig - Fast line. All aluminum, strong and easy to install. All models are interchangeable and are packed with complete accessories. Write for details!

OAK RIDGE ANTENNAS

239 East 127th St., New York 35, N. Y. Dept. C

Built for Service



Servicemen's choice!
in . . .

MISSOURI

● Cunninghams draw more votes of confidence in the "show me" State . . . because Cunningham tubes have demonstrated their long life and top performance over a period of 32 years. That's why Cunninghams draw more customers when renewal tubes are needed...and that's why *you* should make Cunningham tubes your leading brand.

See your
CUNNINGHAM DISTRIBUTOR

McGee Radio & Elec. Co. . . . Kansas City
Ebinger Radio & Supply Co. . . . St. Louis

Cunningham Tubes

A product of
RADIO CORPORATION OF AMERICA
Harrison, N. J.

THE FIRST AND ONLY ONE OF ITS KIND!

DE LUXE COMBINATION

Tube Tester

Set Tester

Signal Generator

RCP Model 8573

\$99.⁹⁵

at this record-smashing price . . . only

Every square inch solid-packed with value! Look what you get in this phenomenally low-priced tester: (1) A complete tube tester with over 800 listings in its famous Rollindex roll chart, (2) A battery tester, (3) A capacitor tester, (4) An AM-FM signal generator, (5) An audio oscillator; and a dozen additional features.



Readable scale divisions on the ohmmeter start at 0.05 ohm to 25 megohms

DC Volts: 0, 2.5, 10, 50, 250, 1000, 5000
AC Volts: 0, 10, 50, 250, 1000, 5000
DC Milliamps: 0, .5, 2.5, 10, 50, 260, 1000
DC Amps: 0, 10
Ohms: 0, 250, 2500, 25000

Megohms: 0, 2.5, 25
Decibels: -8 to +15, 15 to 29, 29 to 49, 32 to 55
Output Voltmeter: 0, 10, 50, 250, 1000, 5000

Complete with tubes, batteries and test leads, output leads, etc., housed in natural finish oak case; hammertone gray panel. See this outstanding buy at your jobber today—or write for full details.

RCP INSTRUMENTS—BEST FOR EVERY TEST

RADIO CITY PRODUCTS CO., INC.

152 West 25th Street,



New York 1, N. Y.

AMPERITE

Studio Microphones
at P.A. Prices

Ideal for BROADCASTING

- RECORDING
- PUBLIC ADDRESS

"The ultimate in microphone quality," says Evan Rushing, sound engineer of the Hotel New Yorker.

- Shout right into the new Amperite Microphone—or stand 2 feet away—reproduction is always perfect.
- The only type microphone that is not affected by any climatic conditions.
- Guaranteed to withstand more "knocking around" than any other type mike.

Special Offer: Write for Special Introductory Offer, and 4-page illustrated folder.

AMPERITE Company, Inc.

561 BROADWAY • NEW YORK 12, N. Y.

In Canada: Atlas Radio Corp., Ltd., 560 King St. W., Toronto



Models
RBLG—200 ohms
RBHG—Hi-imp.
List \$42.00



"Kontak" Mikes
Model SKH, list \$12.00
Model KKH, list \$18.00

New Products


MUELLER ELECTRIC TWIN-CLIP

A clip, No. 22 Twin Clip, with jaws on both ends has been announced by the Mueller Electric Company, 1583 E. 31st St., Cleveland 14, Ohio.

Both jaws may be opened at the same time by pressing at the center of the clip or either jaw may be opened separately without disturbing the grip of the other.

Clip made of cadmium steel is 2" long and has a screw connection.

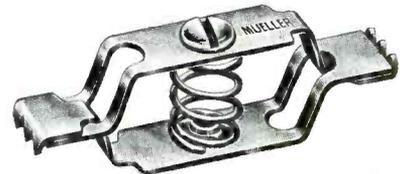Free samples may be had by writing the manufacturer.




* * *

AEROVOX RADIO NOISE FILTER SETUP

An interference filter with provision for choosing the proper combination of circuit elements for the job, has been announced by the Aerovox Corp., New Bedford, Mass.

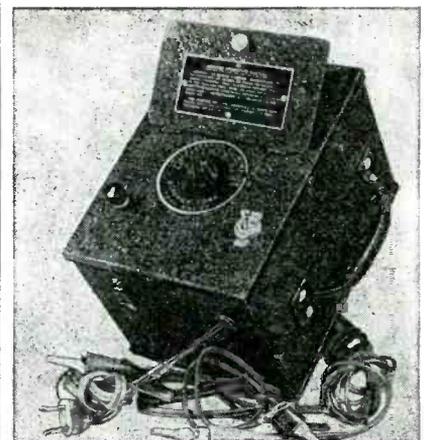Supplied in a metal cabinet with hinged-cover compartment holding assortment of connecting cords, plugs, receptacles and clips. Knob turned through the series of different settings brings into circuit the same circuit elements as found in Aerovox interference filters of corresponding type numbers.



* * *


E-V DYNAMIC MICROPHONES

Two high output dynamic broadcast microphones, models 650 and 645, have been announced by Electro-Voice, Inc., Buchanan, Michigan.

Models are equipped with a shock mount. It incorporates dual Lord shear type mountings which are said to eliminate undesirable vibrations transmitted from the stand, and reduce side sway of the microphone without reducing the efficiency of the isolation unit. The microphone head may be tilted through an angle of 45°.

Model 650 frequency response is said to be flat from 40 to 15,000 cps.

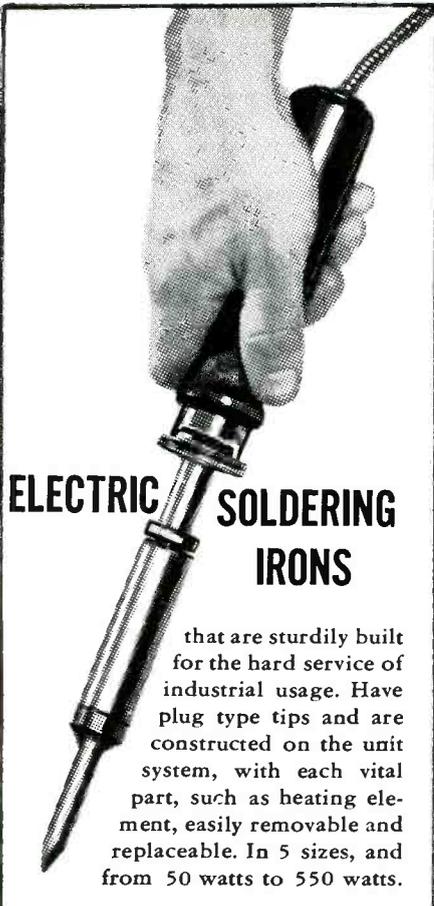Model 645 frequency response is said to be flat from 50 to 15,000 cps.




ELECTRIC SOLDERING IRONS

that are sturdily built for the hard service of industrial usage. Have plug type tips and are constructed on the unit system, with each vital part, such as heating element, easily removable and replaceable. In 5 sizes, and from 50 watts to 550 watts.

American Beauty

TEMPERATURE REGULATING STAND

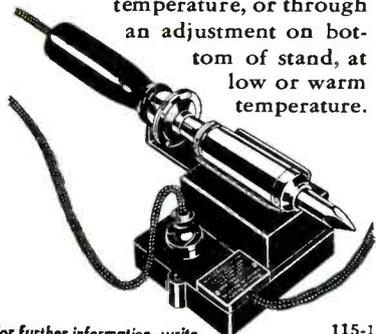This is a thermostatically controlled device for the regulation of the temperature of an electric soldering iron. When placed on and connected to this stand, iron may be maintained at working temperature, or through an adjustment on bottom of stand, at low or warm temperature.




For further information, write

115-1

AMERICAN ELECTRICAL HEATER COMPANY
DETROIT 2, MICHIGAN
 established 1894

SOLAR CAPACITOR ANALYZER

A capacitor analyzer, model CBC, which measures capacitances from 10 mmfd to 800 mfd, using a magic eye indicator for capacitance bridge balancing, has been announced by Solar Manufacturing Corporation, 1445 Hudson Blvd., North Bergen, N. J. Power factor measurements on electrolytic capacitors are made by the bridge method. Also incorporates simplified neon lamp test circuits for visual checks of the insulation resistance of paper and mica capacitors and of the leakage current of electrolytic capacitors. The instrument also has a line frequency resistance bridge covering a range of 100 ohms to 7 megohms. Complete description of the analyzer appears in catalog IN-3, available upon request.

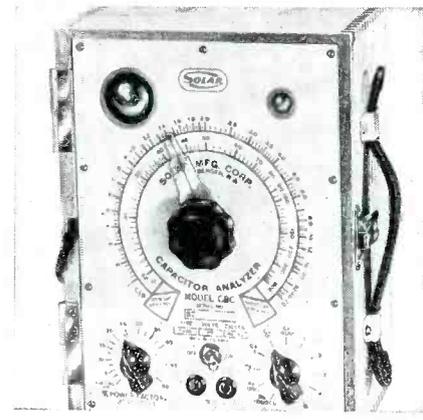

* * *

RUF SADL ANTENNA MOUNTING

A tv or f-m antenna mount adjustable to any pitch of roof and any width of metallic capping has been announced by Crums, Inc., Manufacturing Division, Wooster, Ohio.

* * *


WRIGHT FLUSH MOUNTING GRILLE

A 10" chrome-plated 18-gauge steel disc, model 10-P, for speaker flush-mounting installations has been announced by Wright, Inc., 2233 University Avenue, St. Paul 4, Minn.

SAVE 50% ON KITS!

25 WATT P.P. 6L6 HI GAIN AMP. KIT

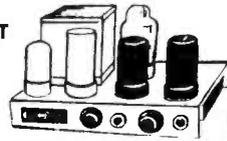A wonderful buy! Make up an amplifier worth \$50 to you. Powerful enough for auditoriums seating 1500 people. Separately controlled Mike & Phono inputs. All parts incl. drilled chassis, hdware, solder, circ. dia., etc.



LESS TUBES **\$11.95**




UNIVERSAL TROUBLE SHOOTER KIT

Locates every service trouble. Guaranteed to do everything we say. Aligns paddler. Locates dead spots, weak spots, defective parts. Checks gain. All parts incl. case, test leads, plug. 2 1/4" x 6" x 3"..... **\$3.95**

Phono Oscillator 2 Tube Kit. Hi-gain with microphone jack and all parts including Tubes, **\$2.95**
 Phone-Amplifier Kits. All parts incl. tubes. 3 Tubes **\$4.25** 2 Tubes **\$2.95**
 Free data, circuits designed by ROBERT G. HERZOG.

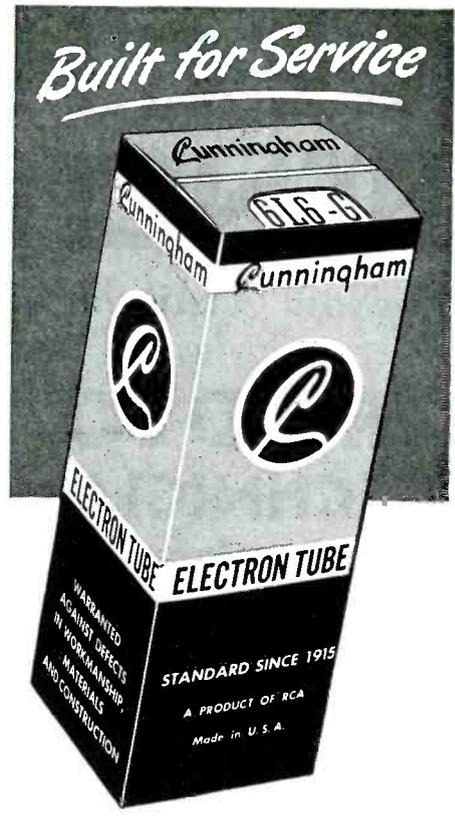Universal/general corp.
 365 CANAL STREET. DEPT. K
 N. Y. 13, N. Y. WALKER 5-9642



Servicemen's choice!

in ...



• Thousands of set owners in New Mexico rely on Cunningham Tubes. Their top quality and performance make them the favored tubes when replacements are called for. You'll sell more customers if you campaign for Cunningham.

See your **CUNNINGHAM DISTRIBUTOR**

L. B. Walker Radio Co. Albuquerque



TECH BENCH

Now Available
for the

RADIO TECHNICIAN



"Everything in its place, and a place for everything . . ." Engineered for convenience and workability . . . designed to give 100% working efficiency and sturdily built for long and practical use.

CHECK THESE OUTSTANDING TECH-BENCH FEATURES . . .

- Eighteen well proportioned drawers, eight of which can be used for complete material systems or small tools.
- Stops on all drawers to prevent spilling.
- Hardwood finished top with durable, lustrous finish.
- Two conveniently located internally wired electric sockets for electrical tools and equipment.
- Handy catalog and chart space.
- Reinforced canvas apron of generous size.
- Top surrounded three sides with guard rail and has grooved slot.
- Made of corrosion resistant non-magnetic aluminum.
- Foot rest placed for comfortable working position.
- Either left-handed or right-handed model.

STANDARD SPECIFICATIONS

Length 40", Depth 20", Height 38"
Shipping Weight, 90 Lbs.

only **\$74.95** F.O.B.
HOUSTON

Order from your Radio Supply Dealer or for further information write directly to

The DE MARIA COMPANY
711 Main Street Houston, Texas

WEBSTER-CHICAGO MICROGROOVE RECORD CHANGER

An automatic microgroove record changer, model 133, has been announced by Webster-Chicago Corp.

Changer features a carefully-balanced tone arm which applies no lateral pressure on the thin walls. Has a nylon knee-action needle.

The drive is said to have the same single-speed torque characteristics and wow-less performance of the standard Webster-Chicago record changer models. Changer unit is mounted in an all metal base which is finished to blend with home furnishings and may be used on table top or in radio console compartment for amplification through the receiver.



EICO VTVM KIT


A vtvm kit, 221-k, has been announced by Electronic Instrument Co., 377 Blake Ave., Brooklyn 12, N. Y.

Kit is the Eico model 221 vtvm in disassembled form.

ASTATIC PICKUP CARTRIDGE

A phonograph pickup cartridge with ceramic elements has been announced by The Astatic Corporation, Conneaut, Ohio.

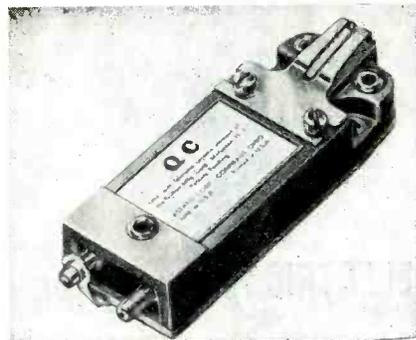Model QC pickup cartridge, with ceramic element, is said to have a frequency range of 50 to 10,000 cps and a needle pressure of one ounce.



OLSON AKRAD CAPACITORS

Four new values of Akrad capacitors have been announced by Olson Radio Warehouse, Inc., 73 E. Mill Street, Akron 8, Ohio: 20 mfd, 450 volts; 30 mfd, 450 volts; 40 mfd, 450 volts, and a 50-30 mfd, 150-volt tubular.




REVOLUTIONARY SOLDERING IRON

TRANSVISION Soldetron

Tr. Mark Reg., Pat. Pend.

For Easier, Better Soldering—on Any Job!

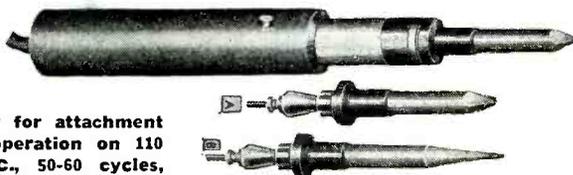- Weighs only 3 ozs., yet can do the job of a 200 watt iron.
- Heats up in 20 seconds from a cold start; saves time.
- Fingertip control; permits soldering without fatigue.



Ready for attachment and operation on 110 V A.C., 50-60 cycles, through transformer supplied with iron, or 6-8 volt A.C. or D.C. without transformer (from an automobile battery).

Overall size of iron 9 1/4" x 15/16"; shipping weight approx. 4 lbs.

- Ideal for fine precision work in "hard-to-reach" places.
- Readily interchangeable tip-heads; no cleaning or filing.
- Retains heat with switch off up to 1 minute; efficient.
- Bakelite handle, cork covering, for comfortable cool grip.

PRICE: including transformer and Tip-Head "A", \$13.95
5% higher west of Mississippi; fair traded

Ask your distributor, or for further information write to:

TRANSVISION, INC., Dept. S, NEW ROCHELLE, N. Y.

IN CALIF.: Transvision of Cal., 8572 Santa Monica Blvd., Hollywood 46

Television Installers

HERE'S WHAT YOU NEED!

The NEW

Easy-Up

Self-Supporting
TOWER for
Your Antenna

Here, for the first time, is a quick, simple way to elevate your TV antenna for best reception. Just tip it up—no more struggling with wobbly pipe-masts and their maze of guy wires. Mounts either on flat or peaked roof. Light, sturdy, attractive, dependable. Gives you an installation to be proud of.

Height of tower proper is 32 ft. (providing a height of 40 ft. above roof top when used with 10 ft. antenna pole.) Pre-assembled in four easily joined sections. Pays for itself. Complete installation takes two men less than an hour; tower can then be lowered and raised anytime in just a few minutes.

Write for full details

Easy-Up Tower Co.
3800 Kinzie Ave.
Racine, Wis.

TELEVISION ASSEMBLY CO. PROJECTION TELEVISION UNITS

A projection television assembly has been announced by Television Assembly Company, 540 Bushwick Avenue, Brooklyn 6, New York. Projects 520 square-inch picture onto an Eastman Kodak projection screen. Optical-electronic system consists of a Bausch & Lomb F/1.9 projection lens, RCA 5TP4 projection tube, tripler 30 kv power supply, and an aluminum-top coated mirror.

The 30 kv power supply is pre-wired.

Projection television assembly consists of 36 tubes (including the projection tube) and features a 13-tube pre-wired, pre-tuned i-f picture and sound strip (pat. pend.) having 5 stages of i-f picture amplification, with a 4.25-mc bandwidth; Dumont inputuner, with three continuously tunable circuits, tuning from 44 to 216 mc; ratio-detector f-m circuit; three-stage audio amplifier, with two 6V6GTs in push-pull, class AB1, delivering approximately 8 watts undistorted output.

* * *

DEMARIA TECH-BENCH

A Tech-Bench in both right and left-handed models, has been announced by The DeMaria Co., 711 Main St., Houston 2, Texas. The entire bench is constructed of corrosion resistant non-magnetic aluminum.

Has a durable hardwood replaceable top surrounded by guard rails on three sides with a grooved slot in front, and eighteen well proportioned drawers, eight of which can be used for small tools and materials are made spill proof by individual stops.

The overall specifications are length 40", depth 20", height 38" and weight 90 pounds.



GREYLOCK

A Dependable Name in
RADIO TUBES

GT, Glass, and Miniature Types
ALL TUBES IN INDIVIDUAL CARTONS

39¢	39¢	39¢	49¢	49¢	49¢	59¢
6A8GT	12A7G	25L8GT	1R5	6AK5	6X4	6L6GA
6K7GT	12BA6	25Z6GT	1T4	6AC5	25Z5	6U5
6Q7GT	12BE6	35W4	1U4	6AQ5	6A7	43
6SA7GT	12K7GT	45	1S5	6BE6	6C6	70L7
6SK7GT	12Q7GT	46	3S4	6BA6	6D6	84
6SQ7GT	12SA7	47	3Q4	6AU6	75	117L7
6V6GT	12SK7	50B5	3V4	6BJ6	117Z3	32L7
12A8GT	12SQ7	50L8				

Webster A11 Pickup, plastic arm..... \$1.49
TERMS: Net C.O.D. No order accepted for less than \$5.00

Write for Bargain Catalog S-8

GREYLOCK ELECTRONIC SUPPLY CO.
30 CHURCH STREET NEW YORK 7, N. Y.

Built for Service



Servicemen's choice!
in ...



● As the Governor of North Carolina might have said to the Governor of South Carolina... "It's a long time between complaints with Cunninghams." No wonder... Cunninghams tubes are built for service—which is good reason why Cunninghams should be your choice.

See your
CUNNINGHAM DISTRIBUTOR

Long's Distributing Co. Asheville
Glasgow Supply Co. Charlotte
Carolina Radio Equipment Co., Inc. ... Raleigh
Dalton-Hege Radio Sup. Co. ... Winston-Salem

Cunningham Tubes

A product of
RADIO CORPORATION OF AMERICA
Harrison, N. J.

For the Sharpest, Clearest Pictures
INSTALL A
WORKSHOP
RECEIVING SYSTEM

In many locations, the ordinary television antenna does not provide enough "signal strength" for even the finest receivers. Workshop custom-designed Receiving Systems, because of their "high gain," will bring you pictures with brilliant clarity — even at places far beyond the normal range.

Here's what users say:—
 —"My WORKSHOP 6-element high-gain antenna brings in Chicago stations 225 miles away."
 —"Ghosts and noise have completely disappeared since I installed your Television Receiving System." — New York City
 —"The tough winter brought down a lot of antennas in my neighborhood, but my rugged Workshop antenna stood up beautifully." — White Plains
 —"I get wonderful reception on baseball games 125 miles from Cleveland with your antenna system."
 Many new television stations will come on the air soon. Play safe with a Workshop Receiving System — it is designed to take care of them.
 Write for Free Television Catalog.




THE WORKSHOP ASSOCIATES, INCORPORATED
 67 Needham Street, Newton Highlands 61, Mass.

RCA TUBE DEPT. APPOINTS
J. R. MEAGHER TV SPECIALIST

John R. Meagher has been named television specialist in the Renewal Sales Section of the RCA Tube Department. Meagher was previously training coordinator on television for the RCA Service Company. He developed the RCA *Dynamic Demonstrator* radio-instruction panels, and is the author of *Television Troubleshooting and Alignment*. His lectures include appearances before such Service Men's groups as the RMA-sponsored television clinic held recently in Philadelphia.



* * *

ROSE KORSGREN NOW ALASKA
RADIO SALES MANAGER

Rose Buss Korsgren has been appointed sales manager of Alaska Radio Supply, Box 84, Anchorage, Alaska. Mrs. Korsgren was formerly sales promotion director of the Hallicraeters Company. The firm has branch offices in Juneau and Ketchikan.



* * *

J. K. POFF HEADS ERIE RESISTOR
DISTRIBUTOR SALES DEPARTMENT

J. K. Poff has been appointed to head a new Distributor Sales Department at Erie Resistor Corporation, Erie, Pa. Department will handle parts jobbers sales of tubular ceramic bypass and coupling capacitors, high voltage television capacitors, ceramic trimmers, temperature compensating ceramic capacitors, button silver micas, insulated and non-insulated carbon resistors, etc. Poff was formerly sales-service engineer with the Astatic Corp., Comenaut, Ohio. During World War II he was a Chief Specialist in the U. S. Navy.




TINIT makes TOUGH JOBS EASY!

TINIT flows into crevices—and you're sure it's tinned with TINIT because you can see it! Contains enough tin for small jobs without additional solder. Cleans, tins and fluxes all metals including sheet aluminum, penetrates rust, grease and dirt in one easy operation! Twenty years on the market. Sold by automotive, refrigeration, tinning supply and other jobbers.

TINIT MFG. CO., INC.
 P. O. Box 794, Denver, Colo.

BUY FROM YOUR JOBBER


Permoflux SPEAKERS

YOUR JOBBER CAN SUPPLY YOU!

Permoflux quality and dependability—the same as supplied to the major set manufacturers—is your assurance of complete customer satisfaction. You'll find Permoflux Speakers easy to install and readily available in both PM and Electrodynamic types. You'll find too, that it pays to give your customers "tops in tone" with a Permoflux Replacement Speaker.

TWO COMPLETE FACTORIES TO SERVE YOU **PERMOFLUX** WRITE FOR FREE BULLETIN
 PIONEER MANUFACTURERS OF PERMANENT MAGNET DYNAMIC TRANSDUCERS

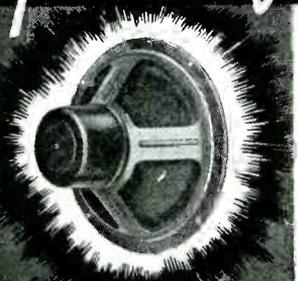PERMOFLUX CORPORATION
 4900 WEST GRAND AVE., CHICAGO 39, ILLINOIS
 236 SOUTH VERDUGO ROAD, GLENDALE 5, CALIFORNIA



SHOOTS TROUBLE FASTER!

Makes more money
for you on job or
at service bench!



PRICE
\$9.95

at distributor
or postpaid,
direct. Sorry,
no COD's.
Ohioans add
3% State Sales
Tax.

Signallette

MULTI-FREQUENCY GENERATOR

In radio service work, time means money. Locate trouble faster, handle a much greater volume of work with the SIGNALLETTE. As a trouble shooting tool, SIGNALLETTE has no equal. Merely plug in any 110V. AC-DC line, start at speaker end of circuit and trace back, stage by stage, listening in set's speaker. Generates RF, IF and AUDIO Frequencies, 2500 cycles to 20 Megacycles. Also used for checks on Sensitivity, Gain, Peaking, Shielding, Tube Testing. Wt. 13 oz. Fits pocket or tool kit. See at your distributor or order direct.

Clippard INSTRUMENT
LABORATORY
Inc.

DEPT. S, 1125 BANK STREET
CINCINNATI 14, OHIO

**QUALIFIED JOBBERS WRITE,
WIRE FOR DETAILS.**

**T.V. RADIO
SYSTEMS
ELECTRONICS**

**NEW
1948
Complete
RADIO CATALOG
FREE**

28 Years to Develop
160 Bargain Packed
Pages.

32,210 Radio and TV
Items.

Absolutely FREE . . . this gigantic, all inclusive radio and electronics Catalog with sets, parts, systems, newest developments. It's practically a power-packed reference library of vital needs and information. Every one of the illustrated 160 pages is crammed with amazing bargains much too good to miss! No matter WHAT your interest in Radio or Radio-Electronics, you MUST have this FREE Catalog. Write at ONCE . . . NOW!

FREE ENGINEERING SERVICE

Bring us your problem or question about Radio, TV, or Radio-Electronics. Write to Concord. No charge for this service.


CONCORD RADIO CORPORATION
527-K 901 W. Jackson Blvd., Chicago 7, Ill.

265 Peachtree St., Atlanta, Ga.

FIRST WINNER IN HYTRON SIX-MONTH SERVICEMEN'S CONTEST

Harry L. Smith of 25-26 Steinway St., Long Island City, New York, won first prize, a DuMont type 274 five-inch oscillograph, in the first contest of the six-month Hytron Service Men's contest.

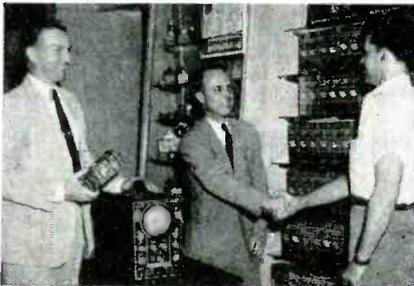There are still many first prizes to be won and a \$200 U. S. Savings Bond as the grand prize in the contest. All Service Men have to do is get an entry blank with complete details from Hytron jobber or write Hytron direct. Wanted are designs for a simple, economical shop tool like the Hytron tube tapper or miniature pin straighteners.




Left to right: Bill Harrison of Harrison Radio Corp., New York; Everett B. Boise, Hytron commercial engineer in New York area, and Harry L. Smith, who was prize winner for May in the Hytron contest.

* * *

HOWARD W. SAMS' RADIO INDUSTRY RED BOOK

The *Radio Industry Red Book* with listings on nine major replacement components for approximately 17,000 models made during the ten year period 1938 to 1948 will be published in September by Howard W. Sams & Co., Inc., 2924 East Washington St., Indianapolis 6, Indiana. Lists original parts, together with numbers for proper replacement parts made by 17 leading manufacturers, covering capacitors, transformers, controls, i-t coils (including peak frequencies), speakers, vibrators, phono cartridges, tubes and dial lights, batteries.

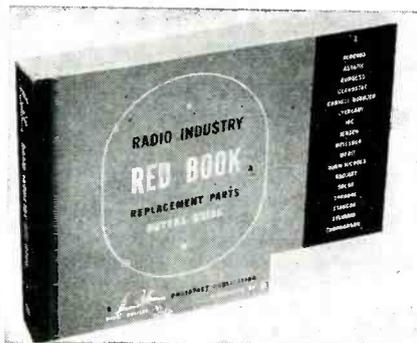Parts manufacturers represented include Aerovox, Astatic, Burgess, Clorostat, Cornell-Dubilier, Eveready, IRC, Jensen, Meissner, Merit, Quan-Nichols, Radiart, Solar, Sprague, Stancor, Sylvania and Thordarson. All data are arranged alphabetically and by model numbers for quick reference. Price, \$3.95.




* * *

WALSCO CATALOG

A 16-page catalog listing hardware, chemicals, tools, finishing materials and service items has been prepared by Walter L. Schott Co., 9306 Santa Monica Blvd., Beverly Hills, Calif.

Built for Service

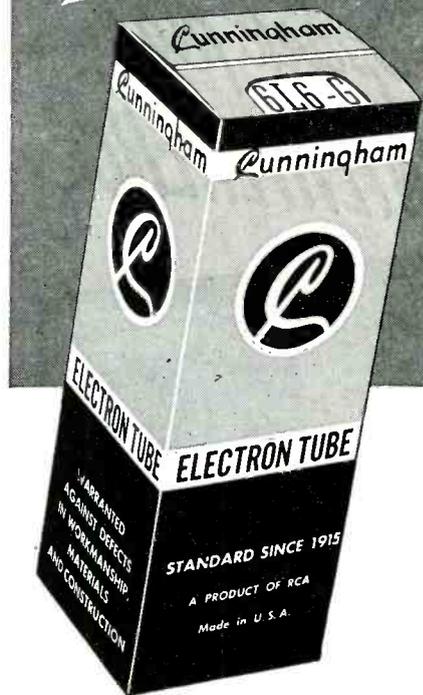

**Servicemen's choice!
in . . .**

NEW JERSEY

● Cunninghams are natives of New Jersey—and proud of it. And the natives of New Jersey are proud of Cunninghams—because Cunningham tubes are built to give quality service and long life. You'll be proud of the way Cunningham tubes will boost your business by using them when renewal tubes are called for.

See your

CUNNINGHAM DISTRIBUTOR

Radio Elec. Service Co. of Pa., Inc., Camden

Barclay-New York, Inc.

Cunningham Tubes

A product of

RADIO CORPORATION OF AMERICA

Harrison, N. J.

...Help end spark plug INTERFERENCE




Spark Plugs are miniature broadcasting stations, send signals that interfere with radio reception, distort television. The New Auto-Lite "Resistor" Spark Plug reduces this interference.*



Recommend NEW AUTO-LITE Resistor SPARK PLUG

Here's How It Works to End Interference

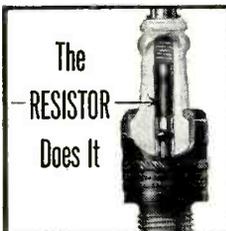The "Resistor" acts to dampen the spark plug radio signal to an acceptable level* while still delivering the full high voltage discharge required to ignite the fuel.



Auto-Lite Ignition Engineers, working with leading automotive manufacturers, have developed the new Auto-Lite "Resistor" Spark Plug with this built-in resistor that reduces spark plug interference.* Remember, the "Resistor" also helps deliver smoother idling, improved economy, longer electrode life. Dealers are being supplied as rapidly as possible. Write for Booklet M-1186 for full information.

THE ELECTRIC AUTO-LITE COMPANY
Toronto, Ontario Toledo 1, Ohio

*Under 35mv/m from 540 k.c. to 150 m.c. at 50 ft.

Tune In "Suspense," Thursdays, 9:00 P. M., E. T., CBS

JOTS AND FLASHES

CHICAGO will be the scene of a gigantic tv show in September during which eighteen set makers will display and demonstrate their receivers and accessories. The show, to be known as the National Television and Electrical Living Show, will be held at the Chicago Coliseum, September 18th through 26th. Among the manufacturers who will be represented are G.E., Westinghouse, RCA Victor, Crosley, Motorola, Sylvania, Philco, Bendix, Hallicrafters, Farnsworth, Admiral, Magnavox, Garod and Stewart-Warner. . . . William A. Browne is now merchandising supervisor for the Radio Division of Sylvania Electric . . . Dave M. Lee Co., of Seattle, Washington, and Portland, Oregon, has been named northwest representative of Solar Manufacturing Corp. . . . Wes Alderson of the W. Bert Knight Co., Los Angeles rep for Taco, is lecturing to jobbers on television antenna techniques . . . John J. Moran has been named special television representative for Philco . . . Admiral Corp. has purchased the domestic appliance division of Pressed Steel Car Co., Inc., to permit expansion into the electric range business . . . Morhan Exporting Corp., New York, now have the exclusive export sales rights for Utah Radio Products Division of International Detrola Corp. in every country throughout the world except Canada and Mexico. . . . The radio receiving tube warehouse of Raytheon is now located in a new streamlined building at Newton, Mass. . . . The RCA projector model (TLS-86) on view in the lobbies of the Philadelphia hotels during the recent national conventions, is now being produced on a quantity basis. The unit provides pictures from 3 x 4 feet to approximately 7 x 9 feet . . . Edlie Electronics is now located at 154 Greenwich Street, N. Y. C. . . . The April-June issue of the "Oscillographer" prepared by DuMont, features articles on the servicing of DuMont instruments . . . Tore Lundahl of Taco, is now visiting in Sweden . . . Ed Berliant has been named general manager of Fada of New Jersey, Inc., which will distribute Fada radio and tv receivers exclusively in N. J. . . . Tv and radio receiver manufacturers displayed their equipment at the recent World's Fair of Music at the Grand Central Palace in New York City . . . National Radio Week will be held from November 14th to 20th and will be sponsored by RMA and NAB. W. B. McGill is chairman of the RMA-NAB National Radio Week Committee. . . . R. I. Parker has been elected a commercial vice president of G.E. . . . RCA recently held three tv meetings for 800 dealers in Dallas, Fort Worth and Memphis. Henry G. Baker, general sales manager of the Home Instrument Dept., headed the delegation, which also included Dan Halpin, tv receiver sales manager and Jack M. Williams, advertising and sales promotion manager . . . James M. Skinner, Jr., is now vice president of the service and parts division of Philco . . . The Lund-Hansen Co., 549 W. Washington Blvd., Chicago 6, Illinois, has been formed to succeed the Ralph T. Brengle Sales Co., and represent Precision Apparatus, University Loudspeakers, Marion Electrical Instrument, Premax, Special Products Co. and Potter & Brumfield.

ADVERTISERS IN THIS ISSUE

SERVICE INDEX—AUGUST, 1948

AMERICAN ELECTRICAL HEATER CO.	43
Agency: Dudgeon, Taylor & Bruska, Inc.	
AMERICAN TELEVISION & RADIO CO.	35
Agency: Firestone-Goodman Adv. Agency	
AMPERITE CO.	42
Agency: H. J. Gold Co.	
L. S. BRACH MFG. CORP.	37
Agency: A. W. Lewin Co.	
CLAROSTAT MFG. CO., INC.	41
Agency: Austin C. Lescauroua & Staff	
CLIPPARD INSTRUMENT LABORATORY	47
Agency: The S. C. Baer Co.	
CONCORD RADIO CORP.	47
Agency: O'Neil, Larson & McMahon	
CORNELL-DUBILIER ELECTRIC CORP.	Inside Front Cover
Agency: Reiss Advertising	
THE DeMARIA CO.	44
Agency: A. R. Hersk	
EASY-UP TOWER CO.	45
ELECTRIC AUTO-LITE CO.	48
Agency: Ruthrauff & Ryan, Inc.	
ELECTRO-VOICE INC.	13
Agency: Henry H. Teplitz, Advertising	
GENERAL ELECTRIC LAMP DEPT.	39
Agency: Batten, Barton, Durstine & Osborn, Inc.	
GENERAL ELECTRIC CO.	25
Agency: Maxon, Inc.	
GREYLOCK ELECTRONIC SUPPLY CO.	45
Agency: Bergman-Jarrett Co.	
HYTRON RADIO & ELECTRONICS CORP.	29
Agency: Henry A. Loudon, Advertising	
JFD MFG. CO., INC.	34
Agency: Bergman-Jarrett Co.	
KEN-RAD DIV. GENERAL ELECTRIC CO.	1
Agency: Maxon, Inc.	
P. R. MALLORY & CO., INC.	Inside Back Cover
Agency: The Aitkin-Kynett Co.	
MURRAY HILL BOOKS, INC.	32
Agency: The Harry P. Bridge Co.	
NEWCOMB AUDIO PRODUCTS CO.	40
Agency: Gail Hall Advertising	
OAK RIDGE ANTENNAS	41
Agency: Knapp-Shepard, Inc.	
PERMOFLUX CORPORATION	46
Agency: Turner Adv. Agency	
PRECISION APPARATUS CO., INC.	7
Agency: Shappe-Wilkes, Inc.	
RADIART CORP.	6
Agency: Ohio Adv. Agency	
RADIO CITY PRODUCTS CO., INC.	42
Agency: Reiss Advertising	
RADIO CORPORATION OF AMERICA	34, 41, 43, 45, 47, Back Cover
Agency: J. Walter Thompson Co.	
JOHN F. RIDER PUBLISHER, INC.	3
Agency: Lansford F. King, Advertising	
HOWARD W. SAMS & CO., INC.	21
Agency: George Brodsky	
SANGAMO ELECTRIC CO.	8
Agency: Arthur R. Morgo, Inc.	
SPRAGUE PRODUCTS CO.	38
Agency: The Harry P. Bridge Co.	
STANDARD TRANSFORMER CORP.	17
Agency: Burnet-Kuhn Adv. Co.	
TINIT MFG. CO.	46
Agency: Bill Bonsib Adv. Agency	
TRANVISION, INC.	33, 44
Agency: H. J. Gold Co.	
UNIVERSAL GENERAL CORP.	43
Agency: Gelles Adv. Agency, Inc.	
UTAH RADIO PRODUCTS DIV. INTERNATIONAL DETROLA	36
Agency: Bonsib Adv. Agency	
WEBSTER-CHICAGO	4, 8
Agency: Fuller & Smith & Ross, Inc.	
THE WORKSHOP ASSOCIATES, INC.	48
Agency: Larcom Randall, Advertising	

All New!


Mallory Midgetrol

Revolutionary

The
First

15
/ 16

Replacement
Control
Line

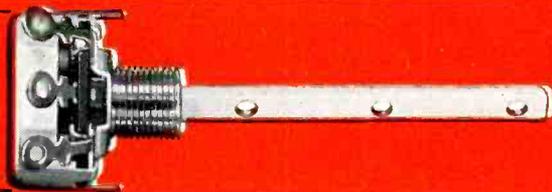

Quietest and Smoothest . . . by Test!

THE SIZE IS NEW

Only 15/16" in diameter, it easily services the increasingly popular small sets where ordinary controls will not fit.

THE SWITCH IS NEW

No chance of failure—it's Mallory engineered and Mallory manufactured. Pushes on—stays on—and works.

THE DESIGN IS NEW

Brand new shaft style saves valuable time in installation—reduces inventory since one shaft fits all knobs.

THE ELEMENT IS NEW

More accurate over-all resistance, smoother tapers, ample power dissipation.

THE CONSTRUCTION IS NEW

Extra quiet—no metal-to-metal contact between shaft and cover or bushing. Special Mallory contact material.

THE CONTACT IS NEW

Laboratory tests prove that the Mallory Midgetrol is the quietest control on the market.

THE SHAFT IS NEW

Unique—two simple fittings—for all type knobs. No need for extra controls for different knobs.

THE TERMINAL IS NEW


Won't break—twist 'em all you want in close working space. Away from panel to avoid shorting.

THE EXTENSION IS NEW


Easy to apply with self-tapping screws. Supplementary shafts available for installations which require them.

THE SUSPENSION IS NEW

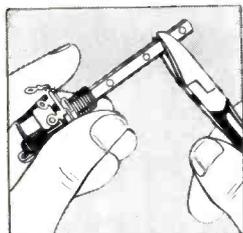
Two-point—insures even contact pressure at all points of rotation. Larger bushing area—added support—no wobble.



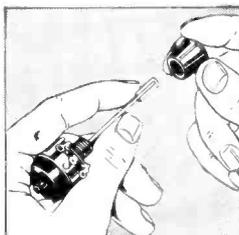
Side snips neatly cut shaft to length desired.



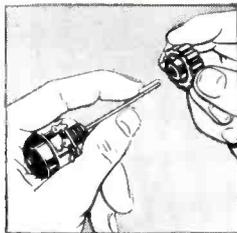
U-clip furnished to slide over end of shaft—holds set-screw knobs.



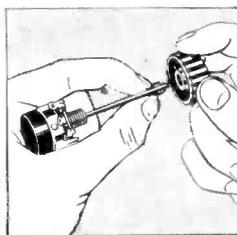Use half the U-clip to hold push-on type knobs.



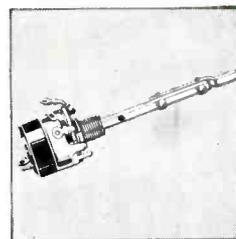Spring steel clip included for use with knurled knobs.



Extension shafts with two self-tapping screws available when needed.

It's the NEW Standard in Carbon Controls. See your Mallory distributor.

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA



You can sell more RCA Batteries



Get the complete catalog of RCA Battery Sales Promotion Material from your RCA Distributor

Powerful Sellers . . . all geared to the radio trade!

Greatest Radio Battery Promotion Program in the Field! . . .

- ✓ Banners ✓ Streamers ✓ Cartoons ✓ Counter Displays ✓ Counter Merchandisers ✓ Direct Mail Post Cards ✓ Advertising Mats
- ✓ Battery Guides ✓ Dealer Price Lists ✓ Battery Cartons


Again RCA leads the battery field in progressive merchandising with a *complete* line of powerful selling aids specifically designed for the *radio trade*!

Now you can get everything you need to sell *more* RCA Batteries than ever before . . . compelling full-

color displays to lead more customers your way . . . self-serving counter merchandisers that sell batteries on sight . . . banners and seasonal window streamers to let all radio owners know you're headquarters for RCA Radio Batteries.

Don't miss the *extra* business these new sales aids will bring you. Ask your RCA Battery Distributor for Bulletin No. 2F406 that contains the complete story on the most comprehensive *sales promotion plan* in the radio battery industry today!

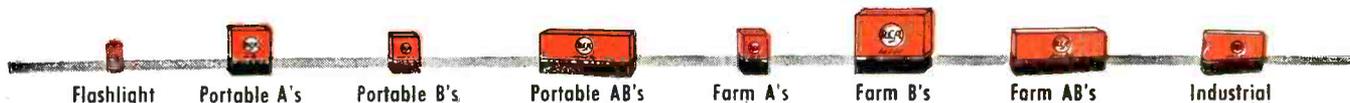SELL RCA BATTERIES—THE COMPLETE LINE FOR THE RADIO AND ELECTRONIC TRADE



RADIO CORPORATION OF AMERICA

HARRISON, N. J.