

B

January  
1934

# SHORT WAVE RADIO



Edited by

Robert Hertzberg and Louis Martin

## IN THIS ISSUE:

**A Correctly Designed  
2-Tube Receiver**

*by J. A. Worcester, Jr.*

**The "Hg-7"—A 7-Tube  
Superheterodyne**

**Revamping the A. K. 20  
for Short-Wave Use**

**A Really Portable 2-Tube  
Receiver**

*by Frank Lester*

**Satisfactory Short-Wave  
Reception**


*by Arthur H. Lynch*

**Day and Night Waves**

*by Capt. H. L. Hall*

**Amateur 5-Meter Phone**

*by Robert S. Kruse*

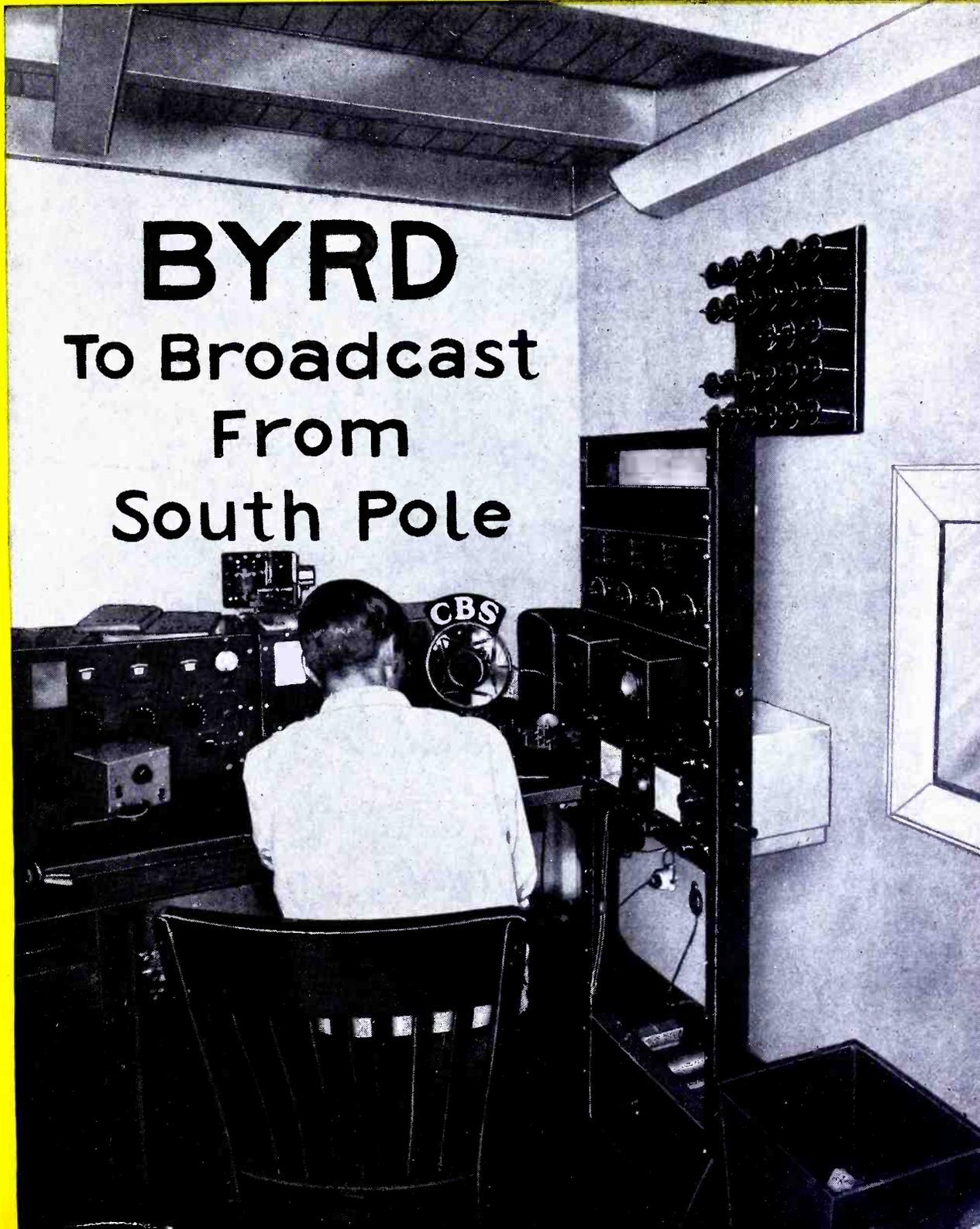

## BYRD To Broadcast From South Pole



---

# FOR YOUR PROTECTION

THE readers of a radio magazine who support it by patronizing its advertisers are entitled to all possible protection against misrepresented merchandise, unauthorized substitutions, exaggerated claims, and delayed deliveries. Toward this end, the publishers of SHORT WAVE RADIO are accepting advertising only from firms whose business ethics and general reputations are known to be above reproach, and they are rejecting advertising from firms of doubtful or questionable standing. This means an annual loss of thousands of dollars of advertising revenue, but the protection which this policy affords both readers and advertisers more than compensates us. Furthermore, SHORT WAVE RADIO is a legitimate magazine, not a disguised house organ for a subsidiary business, and has no hidden sales or manufacturing affiliations to influence its editorial activities.

Experienced short-wave fans will recognize the advertisers in SHORT WAVE RADIO as established, well-known firms. New radio fans just getting into the highly interesting short-wave field can patronize them with the utmost confidence.

Another thing: SHORT WAVE RADIO offers no premiums or free goods in an effort to build up spurious circulation. It subscribes to the belief that a magazine should sell itself on the basis of its reading matter alone, and not on irrelevant inducements.

## SHORT WAVE RADIO



# I will train you at home



**Here's Proof**

## to fill a **GOOD PAY Radio Job!**

If you are dissatisfied with your present job, if you are struggling along in a rut with little or no prospect of anything better than a skimpy pay envelope—clip the coupon NOW. Get my big FREE book on the opportunities in Radio. Read how quickly you can learn at home in your spare time to be a Radio Expert—what good jobs my graduates have been getting—real jobs with real futures.

**Free Book  
Tells How  
Mail Coupon!**

### Many Radio Experts Make \$40, \$60, \$75 a Week

In less than 15 years the Radio Industry has grown from a few million to hundreds of millions of dollars in business a year. Over 300,000 jobs have been created by this growth, and thousands more will be created by its continued development. Many men and young men with the right training—the kind of training I give you through the N. R. I. method—have stepped into Radio at two and three times their former salaries.

### Get Ready Now for Jobs Like These

Broadcasting stations use engineers, operators, station managers and pay up to \$5,000 a year. Manufacturers continually employ testers, inspectors, foremen, engineers, servicemen, buyers, for jobs paying up to \$7,500 a year. Radio operators on ships enjoy life, see the world, with board and lodging free and get good pay besides. Dealers and jobbers employ servicemen, salesmen, buyers, managers, and pay up to \$100 a week. My book tells you about these and many other interesting Radio jobs.

### Many Make \$5, \$10, \$15 a Week Extra in Spare Time Almost at Once

The day you enroll with me, I send you instructions, which you should master quickly, for doing 28 Radio Jobs common in most every neighborhood, for spare-time money. Throughout your training I send you information on servicing popular makes of sets. I give you the plans and ideas that have made \$200 to \$1,000 a year for N. R. I. men in their spare time. My course is famous as the Course that pays for itself.

### Television, Short Wave, Loud Speaker Systems Included

There's opportunity for you in Radio. Its future is certain. Television, short wave, loud speaker systems, police Radio, automobile Radio, aircraft Radio—in every branch, developments and improvements are taking place. Here is a real future for thousands and thousands of men who really know Radio—men with N. R. I. training. Get the training that opens the road to good pay and success.

### You Get a Money-Back Agreement

I am so sure that N. R. I. can train you satisfactorily that I will agree in writing to refund every penny of your tuition if you are not satisfied with my Lessons and Instruction Service upon completion.



### FREE 64-page Book of Facts

Get your copy today. It's free to any ambitious fellow over 15 years old. It tells you about the opportunities in Radio; about my course; what others who have taken it are doing and making. Find out what Radio offers you without the slightest obligation. ACT NOW!

**J. E. SMITH, President  
National Radio Institute Dept., 4 A S 8  
Washington, D. C.**

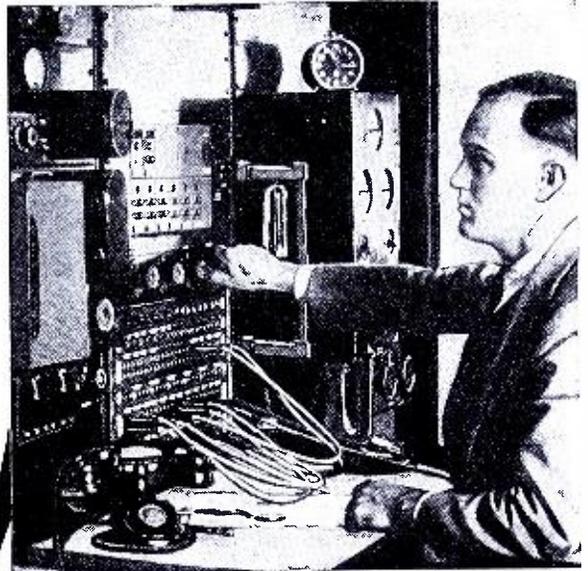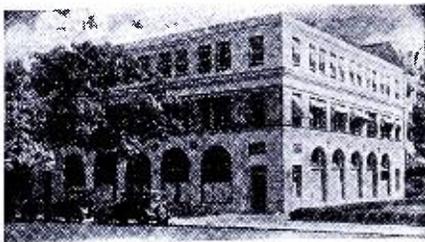
### Our Own Home

Pioneer and World's Largest Home-Study Radio training organization devoted entirely to training men and young men for good jobs in the Radio industry. Our growth has paralleled Radio's growth. We occupy three hundred times as much floor space now as we did when organized in 1914.


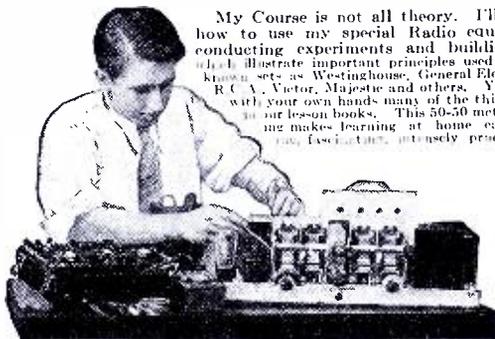
### SPECIAL Radio Equipment for Broad Practical Experience Given Without Extra Charge

My Course is not all theory. I'll show you how to use my special Radio equipment for conducting experiments and building circuits. I'll illustrate important principles used in such well-known sets as Westinghouse, General Electric, Philco, RCA, Victor, Majestic and others. You work out with your own hands many of the things you read in our lesson books. This 50-50 method of training makes learning at home easy, interesting, fascinating, intensely practical.



### \$50 to \$75 a Week

"The National Radio Institute put me in a position to make more money than I ever made in good times. I am in the Radio service business for myself, where it is possible for me to make from \$50 to \$75 a week. Service work has increased because people who in normal times would buy a new Radio, now are contented to have the old one 'pepped up'."  
BERNARD COSTA,  
150 Franklin St.,  
Brooklyn, N. Y.



### Runs Successful Radio Business

"I am a member of the firm of South Grand Radio & Appliance Co., which runs a very successful business. The greater part of my success I owe to N. R. I. Without your training, I could never have been successful in Radio."  
J. A. VAUGHN,  
Grand Radio & App. Co.,  
3107 S. Grand Blvd.,  
St. Louis, Mo.



### Does Radio Work In Spare Time

"I am operating a 120-acre farm. Three nights a week I teach a Radio class. On the other nights I make service calls. Words cannot express my gratitude to N. R. I. Your training prepared me to earn nice sums of cash in spare time."  
HOYT MOORE,  
R. R. No. 3, Box 919,  
Indianapolis, Ind.

### 28 MONEY- MAKING HINTS FREE



Mail the coupon. I'll send you one copy of my valuable 56-page Reference Book "28 Tested Methods for Making Extra Money." I'll do it to prove that my training is easy to understand and use—that it is practical—that it is full of money-making information right from the start. This book shows you how to do 28 Radio jobs common in every neighborhood—tells you how to get these jobs. Hundreds of my students have made \$5, \$10, \$15 a week in spare time while learning. Prove to yourself that you can do it, too. Mail coupon.

I have doubled  
and tripled the  
salaries of many.  
Find out about  
this tested way  
to **BIGGER  
PAY**



**FILL OUT AND MAIL  
THIS COUPON TODAY**

**J. E. SMITH, President  
National Radio Institute, Dept. 4A88  
Washington, D. C.**

Dear Mr. Smith, I want to take advantage of your Special Free Offer. Send me your two books, "28 Tested Methods for Making Extra Money" and "Rich Rewards in Radio." This request does not obligate me. (Please print plainly)

Name..... Age.....

Address.....

City..... State..... **J**

**The Famous Course That Pays For Itself**

# SHORT WAVE RADIO

January, 1934  
Vol. 1, No. 3

*devoted to short-wave transmission and reception in all their phases*

Robert Hertzberg, *Editor*

Louis Martin, B.S., *Technical Director*

General Advertising and Editorial Offices, 1123 Broadway, New York, N. Y.

## IN THIS ISSUE:

Byrd to Broadcast from South Pole by Robert Hertzberg	4
Graphite Anode Transmitting Tubes by D. E. Replogle	7
The Hg-7—A Super. . . . . by L. van der Mel	8
Satisfactory Short-Wave Reception (Part 3) by Arthur H. Lynch	12
Revamping the AK-20 for Short-Wave Use	14
This, Believe It or Not, Is an Amateur Station! . . . . .	18
Correct Design Applied to a Two-Tube Receiver . . . . . by J. A. Worcester, Jr.	20
All-Wave Reception With Short-Wave Sets	23
Replacing Obsolete Five-Meter Modulated Oscillators . . . . . by Robert S. Kruse	24
A Portable Set That Is Portable by Frank Lester	26
Lyric All-Wave Receiver . . . . .	29
Book Review . . . . .	29
Capt. Hall's Department on Foreign Stations	30
Short-Wave Station List . . . . .	34

## IN FUTURE ISSUES:

**A NEW TYPE OF SET CONSTRUCTION**—Although the necessity for shielding is fully recognized by short-wave experimenters, comparatively few have the facilities or ability to cut large holes in aluminum or perform other machine operations. Realizing this situation, an enterprising manufacturer is bringing out a series of cleverly designed unit panels with a variety of holes already drilled in them. In a forthcoming issue we expect to describe a very fine receiver built around this idea—and with the coils entering from the *front* of the panel. This innovation will undoubtedly be enthusiastically received.

**USING THE NEW TUBES**—The characteristics and applications of many of the new tubes that deluged the radio market during the past year are still not very well understood by experimenters. We expect to run a number of authoritative articles on this subject, written in simple, understandable language.

**SOLDERING THAT STAYS PUT**—We thought that everyone knew how to solder, but the surprisingly large number of letters we receive on the subject indicates that many people have not been properly instructed on this very important operation. We have prepared a well illustrated article that tells just how to use the iron and its accessories in radio work.

**SUPER-REGENERATION**—Super-regenerative circuits are coming back into their own and are enjoying particular popularity for ultra high frequency reception. As the principles of this highly interesting and remarkable circuit are not well known, we have commissioned Mr. J. A. Worcester, well known radio writer, to tell you all about it.

**A SIMPLE RADIOPHONE FOR THE BEGINNER**—The present generation of new amateurs takes to the microphone rather than to the key. For the benefit of advanced short-wave broadcast listeners who want to get into the "ham" game, John B. Brennan, Jr., has prepared a whole series of articles describing the construction and operation of an inexpensive but highly effective short-wave phone transmitter.

**CHARLES H. FARRELL, Advertising Manager**

The entire contents of SHORT WAVE RADIO is copyrighted by Standard Publications, Inc., and must not be reproduced without permission of the copyright owners.  
SHORT WAVE RADIO—Monthly. Entered as second-class matter September 15, 1933, at the post office at Chicago, Illinois, under the Act of March 3, 1879.  
SHORT WAVE RADIO is published on the first of every month preceding date of issue. Subscription price is \$2.50 a year in the United States and possessions; Canada and foreign countries, \$3.00 a year. Individual copies, \$ .25 in the United States and possessions; Canada and foreign countries, \$ .30. Published by Standard Publications, Inc., 4600 Diversey Avenue, Chicago, Illinois. Editorial and advertising offices, 1123 Broadway, New York, N. Y. Louis Martin, President, Robert Hertzberg, Secretary-Treasurer. Send all manuscripts to SHORT WAVE RADIO, 1123 Broadway, New York, N. Y.  
Distributed by Mutual Magazine Distributors, Inc., 53 Park Place, New York, N. Y.

Why the

# SCOTT ALL-WAVE Deluxe

## Excels all Other RADIOS



*E. H. Scott*  
Pioneer designer and custom-builder of superheterodyne all-wave radio receivers of superior quality.

# Performance!

After all, the supreme test performance is made in the hands of owners. Here are a few of hundreds of letters on file in our laboratories:

### Venezuela and Germany in Minnesota

The following foreign stations being received at present: FYA, Pontoise; GSA, Daventry, England; EAQ, Madrid, Spain; YVIBC, Caracas, Venezuela; VK2ME, Sydney, Australia; DJB, Germany and CMCI, Cuba.  
L. C. Melville,  
Minneapolis, Minn.

### A Real DXer Reports!

My Scott DeLuxe Allwave Receiver has certainly pulled in the stations. I have only had the set a little while and have pulled in 225 stations on the broadcast band from all over the North American Continent. I have received 86 stations on the short waves of which 62 have been foreign stations. On February 12 and 13 I received 27 foreign stations (short waves) of which nearly all were regular broadcasts with good loud speaker volume. In all I have received 20 different countries to date. The tonal qualities are the best. The sensitivity and selectivity cannot be beaten.

J. F. Luttmann,  
Milltown, N. J.

### Gets Sweden on West Coast

My set brings in stations other sets don't even show are in the air. I have a log of over 750 in all states and around 15 foreign countries. On my log I have Motala, Sweden, which I think is extremely good from the West Coast.

Charles Maylone,  
Placerville, Calif.

### England and Spain Every Night

Have received both England and Spain every night for two weeks. I get them with plenty of volume.

Solomon Ford,  
Toledo, Ohio.

### Results in Bad Location

\* I made it my point to try for VK3ME Australia and picked them up at 7:45 and held them to 9:00 A.M. Sunday morning April 2, 1933. I certainly am more than convinced that your receiver is the only one that I have seen that will do as you said. Also tuned in the following stations with good results, considering the cloudy and unsettled weather conditions, and my locality in which I am surrounded by all kinds of electrical machinery. The stations I have received are VK3ME, Australia; Rabat, Morocco; Pontoise, France; Germany, England, and I2RO, Italy.

Mr. Fred L. Roenbeck,  
Chester, Pa.

This receiver gives clear, loud-speaker reception from stations 10,000 miles or more distant. It covers the entire wave band between 15 and 4,000 meters.

But this is no longer a distinction. Many receivers are able to tune in, with more or less regularity, short wave stations from foreign lands. Now it is not what an all-wave receiver can do . . . but how it can do it!

All automobiles have motors, wheels, frames, fenders, etc., regardless of price. Practically all radios have the same general line-up of component parts. The factors that make for superiority in motor cars or radios are scientific precision, highest quality parts, rigid inspections and tests and careful hand workmanship by highly skilled technicians. When quantity-production demands speed and more speed there must be a sacrifice of these qualities. You can get them only in a custom-built receiver.

The SCOTT ALL-WAVE Deluxe is quality custom-built in one of the most  
**E. H. SCOTT RADIO LABORATORIES, INC.**  
4450 Ravenswood Ave. Department SW 14 Chicago, Ill.

completely and modernly-equipped radio engineering laboratories in the land. Constant and gruelling tests, both in the laboratory by scientific instruments and by reception tests carried on in various parts of the world, maintain its quality.

The ultimate result is a vastly superior instrument. It demonstrates its ability not only by startling reception of far-away foreign stations on both the broadcast and short wave bands, but by consistently finer reproduction of programs from domestic broadcasting stations. Tone fidelity in the SCOTT ALL-WAVE Deluxe convinces the ear of actuality . . . laboratory tests prove its variance from actuality undetectable by the human ear.

No claim for SCOTT superiority is made without positive supporting evidence. It will be a pleasure to furnish you with these PROOFS, its moderate price and all other information regarding this radio that has won the title of "The World's Finest Receiver." Simply mail the coupon below.



"The Fine Things are Always Hand Made"



A super-fine receiver deserves housing in a cabinet of comparable merit. Here is one of the many distinctive and exclusive designs in consoles created for the SCOTT ALL-WAVE Deluxe. This is the Westery Grande Model, in rare and exotic woods patterned in a theme moderne.

## MAIL THIS COUPON NOW!


E. H. SCOTT LABORATORIES, INC.  
4450 RAVENSWOOD AVE., DEPT SW 14, CHICAGO, ILL

Send me, without obligation, PROOFS of the superiority of SCOTT ALL-WAVE Deluxe performance and tone together with price and complete details regarding its laboratory-construction, etc.

Name .....

Address .....

City ..... State .....

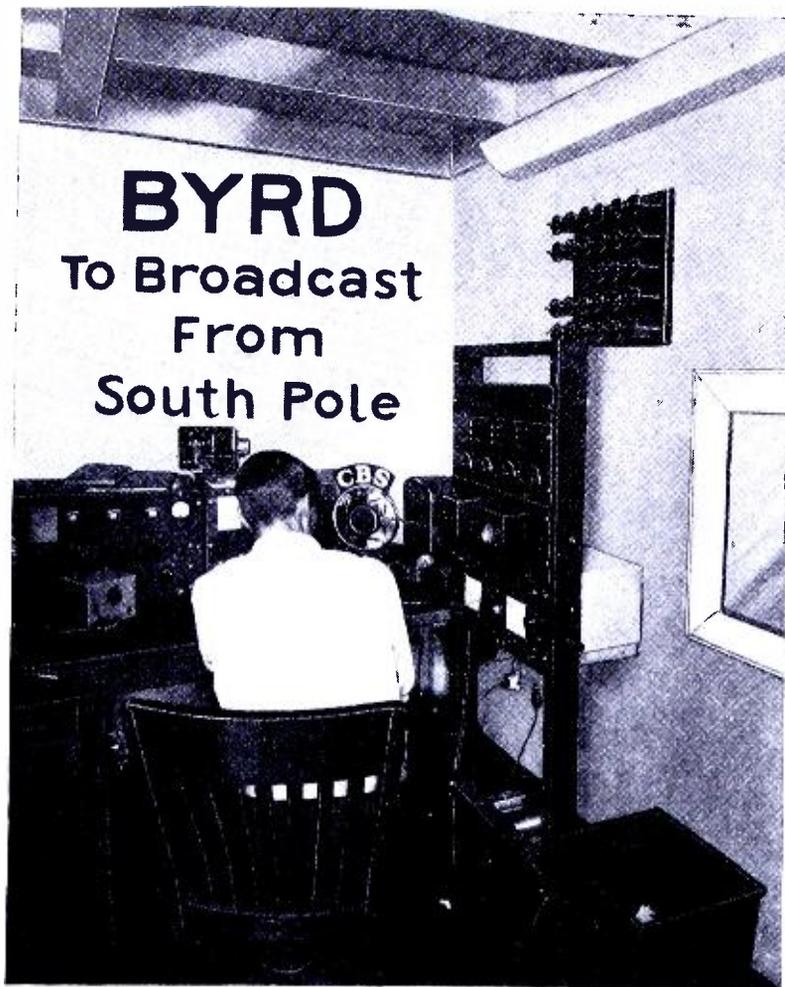

The radio room of the S.S. Jacob Ruppert, showing Operator Dyer at the control panel of KJTY, the short-wave transmitter that is being used for the Byrd broadcasts. The receiver on the lower section of the rack is a regulation National AGS.

By Robert Hertzberg

**T**HE second Byrd Antarctic Expedition promises to provide short-wave fans everywhere with extremely interesting reception. Although, of course, the previous Arctic and Antarctic Expeditions of Byrd carried considerable radio equipment and maintained very successful contact with civilization, all this communication was accomplished by radio-telegraph, voice transmission not being employed at all. The present Expedition is noteworthy from the radio standpoint because of the very considerable use that will be made of *radio-telephone* transmitters. Whereas in previous years only amateurs or other listeners with a knowledge of the code could follow the progress of the explorers, now all short-wave fans will be able to listen in *directly* on the special transmissions from the South Polar wastes, reception conditions permitting. Special equipment has been provided by the Columbia Broadcast System for what is probably the most unusual broadcasting stunt ever attempted.

The *Jacob Ruppert*, Admiral Byrd's main supply vessel, in which he, himself, is sailing, carries very elab-

orate radio equipment. Many amateurs have already reported hearing the one kilowatt radio-telephone transmitter, which has the call letters KJTY. According to the October 1st, 1933, issue of the Radio Service Bulletin, issued by the Federal Radio Commission, KJTY is licensed for telephone transmission on a whole mess of frequencies. These are as follows:

6650	kilocycles	(45.11 m.)
6660	"	(45.05 m.)
6670	"	(44.98 m.)
8820	"	(34.01 m.)
8840	"	(33.94 m.)
13185	"	(22.75 m.)
13200	"	(22.68 m.)
13245	"	(22.65 m.)
13260	"	(22.62 m.)
17600	"	(17.045 m.)
17620	"	(17.026 m.)
21575	"	(13.905 m.)
21600	"	(13.889 m.)
21625	"	(13.873 m.)

#### Regular Weekly Broadcasts

A series of regular broadcasts from the icy wastes of Antarctica will be heard over the Columbia

Broadcasting System's nation-wide network. The programs, in addition to their value as a means of keeping the civilized world in touch with the progress of this vast scientific enterprise, will gain added interest from the fact that they will be the first series ever to be broadcast from a point so far from any humanly inhabited portion of the world.

#### CBS Sends Announcer

A CBS engineer and a combination production man and announcer are accompanying the expedition on its two-year sojourn in the bleak South Pole territory. Although separated from network headquarters by more than 10,000 miles, both men will carry on the same duties which are the lot of engineers and production men on less remote broadcasts. They will supervise each week's program, checking voice levels, writing continuity and arranging technical details.

An elaborate technical set-up has been worked out for the Antarctic broadcasts. Great care was taken in the planning of facilities, since the broadcasts are looked forward to as being more than mere technical stunts. Valuable information of a scientific nature is expected to be sent over the air-waves from Admiral Byrd's base as new discoveries are made concerning the nature of the ice-bound Antarctic.

The broadcasting arrangements call for the use of three transmitters. One is to be a Collins 1,000-watt crystal controlled 100 per cent modulated radio-telephone transmitter installed on the supply ship of the Expedition during the trip to Little America. This will later be set up at the Expedition's permanent base, where it will operate through a directional antenna to one of the directional receiving antennas at Buenos Aires, Argentina. The signals will be relayed from there by short waves to the Columbia key station in New York, and then rebroadcast. Of course, there is no



Dr. Thomas S. McCaleb of Harvard University, radio adviser to Rear Admiral Byrd on his second Antarctic Expedition.

doubt that short-wave listeners in the United States will be able to hear many programs *direct*.

The second sending apparatus is a 200-watt crystal controlled radio-telephone transmitter located at Admiral Byrd's sub-base at the foot of the polar barrier, about three hundred miles closer to the South Pole than the main base.

A portable 100-watt short-wave radio-telephone transmitter will be installed in the bi-motor plane in which Byrd will fly across the South Pole and from which an attempt will be made to broadcast the flight while it is in progress.

Edwin K. Cohan, technical director of the Columbia Broadcasting System, worked out the arrangements with Dr. T. S. McCaleb, of Harvard University, Byrd's counselor on radio; A. Y. Tuel, vice president of the International Telephone and Telegraph Corporation; Harry Young, of Western Electric; William Thompson, of the American Telephone and Telegraph Corporation; and S. H. Simpson of the Radio Corporation of America.

#### 5000 Pounds of Equipment

Five thousand pounds of broadcasting equipment were loaded on board the *S.S. Jacob Ruppert*, flagship of the Second Byrd Antarctic Expedition. Five miles of wire, 9000 feet of it for antennas alone; 300 tubes for transmitting and receiving apparatus; three major transmitting units; ninety-foot wooden poles for antenna structure; dozens of microphones of various types, and power generators are among the items making up the broadcasting cargo.

The heaviest single item of the broadcasting equipment is a 1000-pound gas-driven generator. On the way down to Little America this device will not be employed, but once the ice-party is settled on the Ross




Rear Admiral Richard E. Byrd, photographed in Norfolk, Va., on the occasion of his last broadcast on American soil. His talk was carried over the Columbia Broadcasting System network.

Barrier, it will be the only reliable source of electrical energy. This generator will have to be transferred from the *Ruppert* to the *S.S. Bear*, the ice-breaker, at sea at a point just outside of the ice-pack.

Charles J. V. Murphy, newspaperman, author, and radio announcer, has been chosen as production manager and announcer of the weekly programs to be broadcast from the base of the Byrd Antarctic Expedition in Little America over the Columbia Broadcasting System's nationwide network.

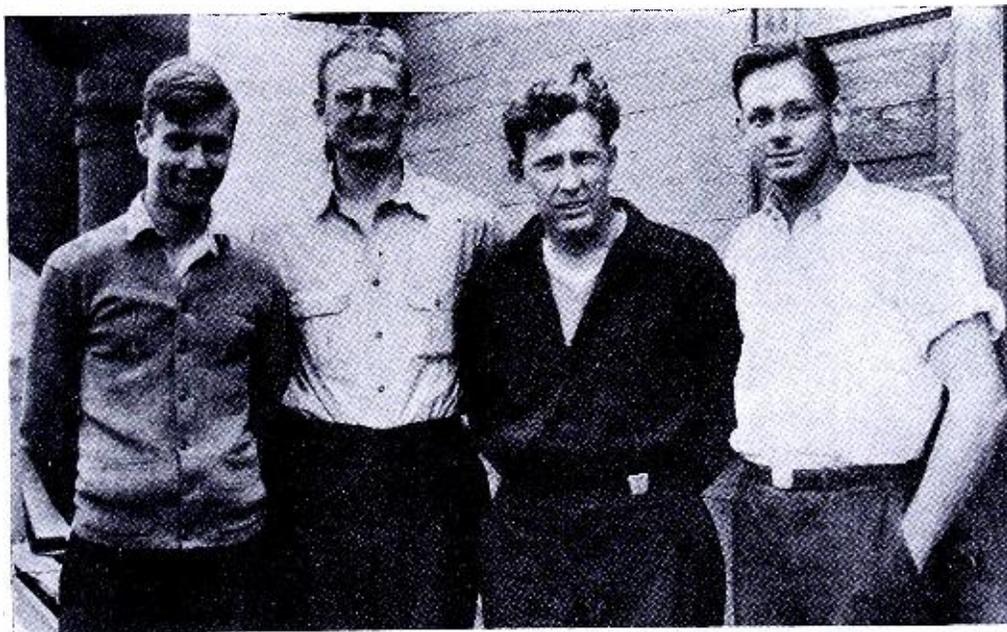As station manager of the most remote unit of any network, Murphy's duties will consist of preparing scripts, introducing speakers or any of the Expedition's potential amateur talent, arranging special programs and coaching all in microphone technique.



The radio men aboard the *S.S. Jacob Ruppert*. Left to right: John N. Dyer, CBS engineer; Stanley Pierce, operator; Clay Bailey, chief operator, and Guy Hutcheson, operator.

Murphy is a native of Boston and a close friend of Rear Admiral Byrd. He is 29 years old and attended Harvard.

John Newton Dyer, of the Columbia Broadcasting System's field engineering department, has been chosen to accompany the Byrd Expedition as technical supervisor of the program series to be broadcast from Little America over the CBS network. In addition to his broadcasting duties, the engineer will also be in complete charge of all Admiral Byrd's communication facilities.

Dyer is 23 and a resident of Haverhill, Massachusetts. He is six feet tall and passed the physical examination, to which all who are going on the expedition are subjected, with a rating of 98.2 per cent.

Among the qualities for which Dyer was selected is his wide knowledge of short-wave transmission, especially in connection with directional work. He studied radio engineering, among other courses, at Massachusetts Institute of Technology, and graduated with a B.S. degree in 1931. He did post-graduate work there for two years. He is well known in New England amateur radio circles as W1BJD.

#### Special W2XAF Programs

From the short-wave transmitting station of the General Electric Company at Schenectady, N. Y., W2XAF, special radio programs will be sent to Rear Admiral Richard E. Byrd's base on the Bay of Whales. This is one of the stations that continually "talked" to Byrd and his men during their previous Antarctic expedition, from 1928 to 1930, and it is the station which they picked up more frequently than any other. The station sends on a wavelength of 31.48 meters. It is still equipped with the directional antenna successfully employed in the broadcasts to the earlier Byrd expedition. This antenna was designed by Dr. E. F. W. Alexanderson, radio consulting engineer of the General Electric Company. Its effect is to increase the signal volume in one direction about twenty times. The normal power of this station is 20 kilowatts. During the previous expedition Admiral Byrd heard every program which W2XAF sent out.

Saturday nights from 11 to 12 o'clock (E.S.T.) will again be the time when the radio programs will be transmitted in the direction of the South Pole for the Byrd expedition to pick up. These programs may start even before the expedition reaches Little America. It is planned to inaugurate the series as soon as Byrd's second ship, the *Jacob Ruppert*, clears from the Panama Canal.

The hour from 11 to 12 o'clock will consist of radio entertainment. After 12 o'clock the station will read letters addressed to members of the expedition from relatives and friends. This "radio mail" will be the only mail service which the ex-

pedition will possess. It is also planned to invite, on occasion, relatives and friends to talk before the microphone. The entertainment programs will originate not only at Schenectady but also in various centers of the east, such as Boston, New York, Washington, Richmond, Va. (Byrd's home city), Albany, Rochester, and other points.

### Standard Equipment Taken

One of the odd things about the radio equipment is that all the fixed receivers and transmitters will be entirely a.c. operated, the aforementioned gas-driven generator supplying all the necessary "juice."

Some widely published and misleading advertising notwithstanding, all the short-wave communication receivers taken on the expedition are standard National units. Included in the lot are two each of the AGS, FB7 and SW-58 models, and a number of SW-3's for use in the expedition's planes. The plane transmitters are all Western Electric. For the sled parties, Harvey transceivers, tiny combination transmitter-receivers working on the ultra-high frequencies, will be used. A Hammarlund broadcast receiver is also being taken.

### Marconi Believes Broadcasts from Antarctic Feasible

The proposed series of broadcasts from the Little America base of the Byrd Antarctic Expedition are entirely feasible, Senatore Guglielmo

### Dressed for the Job



Charles J. V. Murphy, CBS announcer and continuity writer, who will stage the weekly Byrd broadcasts from Little America.

Marconi informed Edwin K. Cohan, technical director of the Columbia Broadcasting System, in an interview at the Hotel Ritz-Carlton, New York, during September. At the same time, Senatore Marconi accepted membership on an honorary advisory committee on radio for the expedition.

Marconi, after discussing the frequencies to be used in the broadcasts and the radio equipment to be taken to the Antarctic, told Cohan:

"I think the project is entirely feasible and the manner of carrying it out is very sound."

Learning that the frequencies to be used range from the eight to the twenty-three megacycle band, Marconi pointed out that it is possible for signals transmitted in the twenty-three megacycle end of the spectrum to be heard around the world, and that, therefore, it may be possible some time during the expedition's stay in the Antarctic to transmit voice direct to New York, instead of relaying it through a short-wave station at Buenos Aires, as will be done with their weekly broadcasts.

Marconi signified his interest in the outcome of the broadcasts by saying he will establish a listening post either aboard his yacht *Electra*, or somewhere in Italy to keep in touch with transmission from Little America. Cohan offered to collate all technical data accumulated during the period of the broadcasts, and Marconi, in turn, said he would be glad to supply Cohan with his findings in connection with the work.

## A High-Gain Resistance Coupled A. F. Amplifier

**T**HE 37, 56, 57 and 77 type tubes may be operated as resistance-coupled amplifiers with high plate-supply voltages, of the order of 500 volts, to provide high audio input voltage for the operation of large power output tubes.

In the design of power amplifiers, the tubes, the coupling devices, and the operating voltages to obtain the highest output levels with the least amount of distortion must be carefully selected.


For representative tubes operated with a plate supply of 500 volts, a plate load of 250,000 ohms, and a grid leak of 500,000 ohms for the following tube, the voltages developed across the a.c. load of 167,000 ohms are:

Tube Type	Grid-Bias Volts	Screen Volts	Peak-Output Volts	Distortion Per Cent
37	-22.5	..	172	3.5
56	-16.0	..	180	5.9
57	-3.5	92	180	5.0
57	-3.5	90	200	7.0
77	-4.5	100	200	9.5

From the standpoint of distortion, the 37 is the most satisfactory. The 37, however, requires 6.5 times as great an input voltage as the 57 to yield the same output. From the

standpoint of gain, therefore, the 57 is to be preferred to the 37.

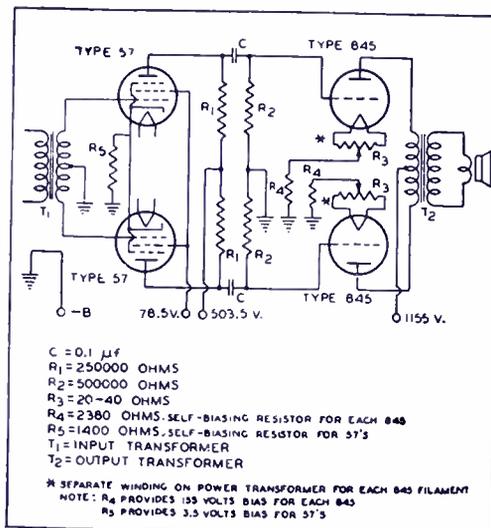An excellent output tube for providing very large audio output of high quality is the 845. This tube, operated as a self-biased audio amplifier with a peak-input voltage of 150 volts, is capable of an a.f. output of 21 watts. Any of the tubes shown in the table (the 37, 56, 57, and 77) can be used to provide the necessary grid excitation for the 845.



From the plate characteristics of the 57 and 77, one might expect that low distortion at high output voltages would be obtained from these tubes when the plate supply is 500 volts, plate load is 250,000 ohms, and grid resistor is 500,000 ohms for following tube. However, distortion increases rapidly with output at high plate-supply voltages and, although large outputs can be obtained, they may not be sufficiently free from distortion. This relationship is indicated in Table I. Distortion, incidentally, is somewhat critically dependent upon screen voltage.

Operation of any of these tubes in push-pull will provide greater output at lower percentages of distortion. The accompanying tabulation shows self-biased push-pull operation for pairs of the same tubes as in Table I with the same conditions, i.e., plate supply voltage of 500 volts with plate and a.c. loads of 250,000 and 167,000 ohms respectively per tube. Screen voltage is given for minimum distortion.


Considering both output voltage and distortion, the 57 provides the most satisfactory performance.

(Continued on page 40)
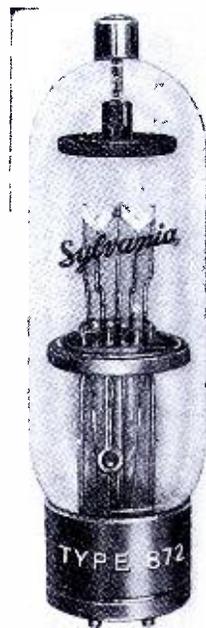
# Graphite Anode Transmitting Tubes

**SUMMARY:** *The use of graphite as material for plates of high power tubes has long been a dream of tube engineers. Graphite, when pure, allows greater heat dissipation, more uniform characteristics, and freedom from secondary emission effects which ordinarily hamper tube operation.*

*In the discussion below, Mr. Replogle gives some interesting data regarding the construction and operation of graphite anode tubes used for transmitting, although the same principles apply to receiving tubes as well.*



A "graphite" 872.

practice has been to mount the carbon anode and seal it in the tube, followed by bombardment and exhaust. Under bombardment, commercial carbon gives off its impurities, as well as sheds its amorphous carbon or loose surface layer. One result is a deposit of carbon dust on the inside of the glass bulb, actually cutting down heat radiation and consequently defeating the very purpose of the carbon anode. Another result is the spattering of loose carbon and impurities on the glass press, the spacers and other insulating parts of the tube, causing troublesome leakage at the high potentials impressed on transmitting tubes. Still another result is incomplete gas cleanup, perhaps not so obvious during production, but certainly noticeable after the tube has been in use for some time. The impurities in the carbon are bound to be distilled or boiled out during the heat of actual operation.

## History of the Graphite Anode

When we first contemplated the use of carbon anodes in our tubes as a justification for an entirely new line of tubes at this rather late date, we were not unmindful of the many technical difficulties in the way of successful realization. It was decided from the start that the anode or plate would have to be in one piece, and that the commercial carbon stock would have to be purified, or reduced to graphite, prior to mounting in the tube.

The task of evolving a pure carbon or graphite anode was assigned to our assistant chief engineer, Victor O. Allen, who has long specialized in filaments, oxide coatings, getters, and other phases of tube chemistry. The research began shortly before March, 1933. Already conversant with the chemical factors involved, it was not long before Mr. Allen announced a unique process for refining commercial carbon. Experimental tubes were built and tested. His claim of a pure carbon, or graphite, was borne out by performance and accelerated life tests. Soon tubes were in production, employing graphite anodes in place of the former nickel or molybdenum plates. One type after another was redesigned for the graphite anode.

The graphite anode begins with a solid block of commercial carbon. This is machined to the ultimate size and shape with a precision of one one-thousandth of an inch tolerance. The finished anode, with its excavated center, thin walls, reinforcement, mounting fins, and long holes, is then chemically treated to remove the binder, hydro-carbons, and amorphous carbon. The resulting graphite anode is then mounted in the tube assembly by means of screws and nuts and rods, in a rigid manner, yet with noticeably less metal support than it required when using metal plates which must be

(Continued on page 40)

## By D. E. Replogle \*

considered as carbon plates because of the retention of a metal base or support for the thin coating.


Also, there have been carbon plates or anodes of solid carbon, usually made up of several sections, or segments. These carbon plates have generally failed to realize the theoretical advantages of the carbon anode. To begin with, the use of several sections, or segments, has introduced high contact resistance within the plate itself. Again, the usual commercial carbon contains a binder, hydro-carbons and other impurities, as well as sheds its amorphous carbon, or a loose surface layer. The

**B**ECAUSE short-wave radio, particularly ultra-short-wave radio, stands for utmost precision, the graphite anode transmitting tube must prove of more than ordinary interest to radio amateurs. Here is a tube development which, in the opinion of many familiar with the history of transmitting tube engineering, is comparable with the introduction of the thoriated tungsten filament several years ago. In matters of greater heat dissipation or ability to withstand heavy overloads, the prevention of primary and secondary grid emission, the elimination of troublesome leakage within the tube, the positive clean-up of gases during production, and a continued getter action during an exceptionally long life, and, what is of cardinal importance, the rigid maintenance of tube characteristics at all times because of a non-warping anode—these and other features attach particular significance to the graphite anode transmitting tube in short-wave work.

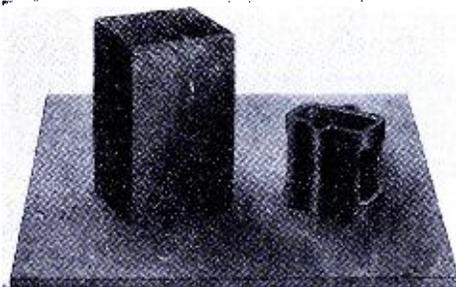
## What Is a Graphite Anode?

It may be well to explain what a graphite anode is, and then proceed to an analysis of its actual worth in short-wave transmission. By a graphite anode is meant a one-piece anode or plate of pure carbon. There are several theoretical reasons why carbon—this term being used here to indicate the unrefined form, as distinguished from the pure form termed graphite—should be considered for the anode or plate of transmitting tubes. First and foremost is the fact that carbon quite closely approaches the perfect black body which is the ideal heat radiator. Tube makers have long sought to take advantage of carbon. Carbonized plates, or metal plates coated with graphite, have been employed in large and small tubes alike with some success, but could hardly be

\* Chief Engineer, Electronics Dept., Hygrade Sylvania Corporation.




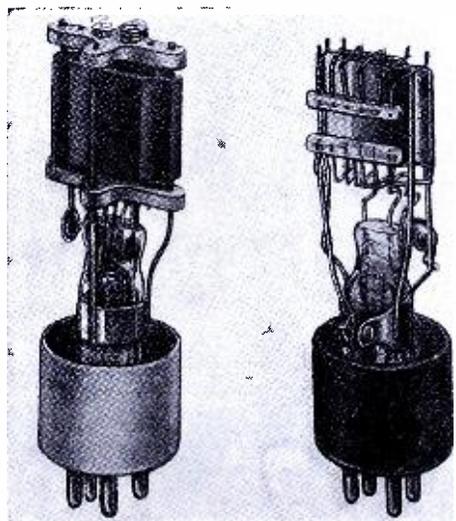Left, a block of amorphous carbon before machining; right, the plate after machining.



Left, the stem mount of a new 210; right, the stem mount of an old type 210 tube.

# The "Hg-7"-A Super

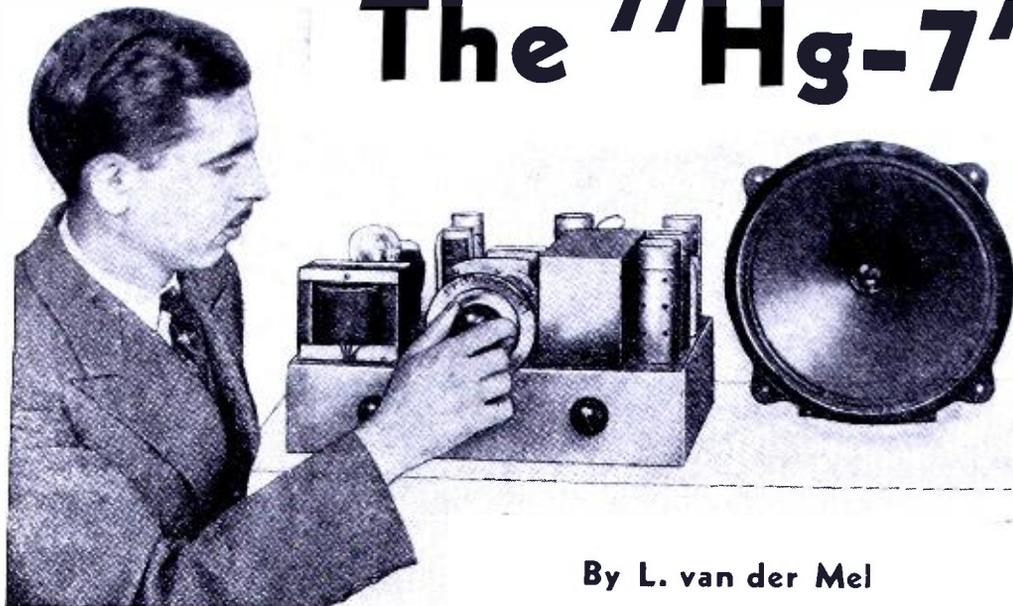

By L. van der Mel

**SUMMARY:** Here is a complete description of a modern superheterodyne with a really novel coil-changing arrangement. This arrangement permits plug-in efficiency without changing individual coils.

It uses seven tubes, has a.v.c., a pre-selector stage, single dial control, and a host of other new details which should make this set the last word in short-wave receiver design.

**T**HE usual procedure for a person interested in radio is to start constructing simple receivers and then gradually promote himself to the more complex types. During the course of this promotion, he gains a certain critical viewpoint regarding what a radio set should or should not do, and no receiver which, in his opinion, does not satisfy his personal requirements is a good one. Only too often have authors expounded their theories as to why *their* sets are the last word in radio; but it seems to the writer that not a few of these authors entirely underestimate the intelligence of the average set-builder. During the author's fifteen years of experience in radio, he has seen many a set-builder unknowingly make a receiver work, which, even during the loftiest peaks of the designer's imagination, could produce nothing but a wide variety of tube noise. In fact, I dare say that our experimental psychologists would do well to use some of our present schematic diagrams as intelligence tests. The results, I am sure, would be surprising.

The receiver to be described was designed for the man with some knowledge of radio, preferably with superheterodyne experience. I don't maintain that anyone with a screwdriver, a pair of pliers, and a lot of nerve can assemble this receiver in twenty minutes and hear China ten minutes later; I do maintain, though, that with the proper attention to details and with the proper apparatus, this receiver will satisfy the most critical listener.

The receiver is modern in every respect. It contains all of the improvements that the author has found necessary for good reception; it does not contain any unnecessary complications that would not improve performance, but that would only be good sales talk. I am trying to explain that this set contains no mysterious gadgets, but is a straightforward, well designed superheterodyne using six tubes and a rectifier, gives excellent qual-


ity and has more than enough sensitivity for the comfortable reception of most foreign programs. By "comfortable" I mean enough volume for a listener to really sit back and enjoy the foreign programs with volume to spare. With this preliminary qualitative description over, let us turn to a more quantitative consideration of the receiver.

## Electrical Characteristics

Study the schematic circuit and the photographs until you have a general idea as to the placement of parts and the symbols used to designate the main units. You will notice, first off, that the antenna is inductively coupled to a preselector r.f. stage using a type 78 tube. This tube, while it is of the variable mu

type, was selected for two reasons: first, because of its variable mu characteristics it is not very critical as to grid bias, so that slight variations in the value of its bias will not cause this tube to detect and defeat its very purpose—to increase selectivity; second, it has a high amplification factor, higher, in fact, than any other similar amplifier tube.

The output of the first r.f. tube, V1, feeds into a 6A7 combination oscillator and first detector. This tube was selected, not only because it has a higher translation gain (ratio of i.f. voltage output to r.f. voltage input) than any other detector tube, but because it obviates the necessity of using a separate oscillator. I don't believe that any saving in cost is effected by the use of the 6A7 over the cost of a sep-

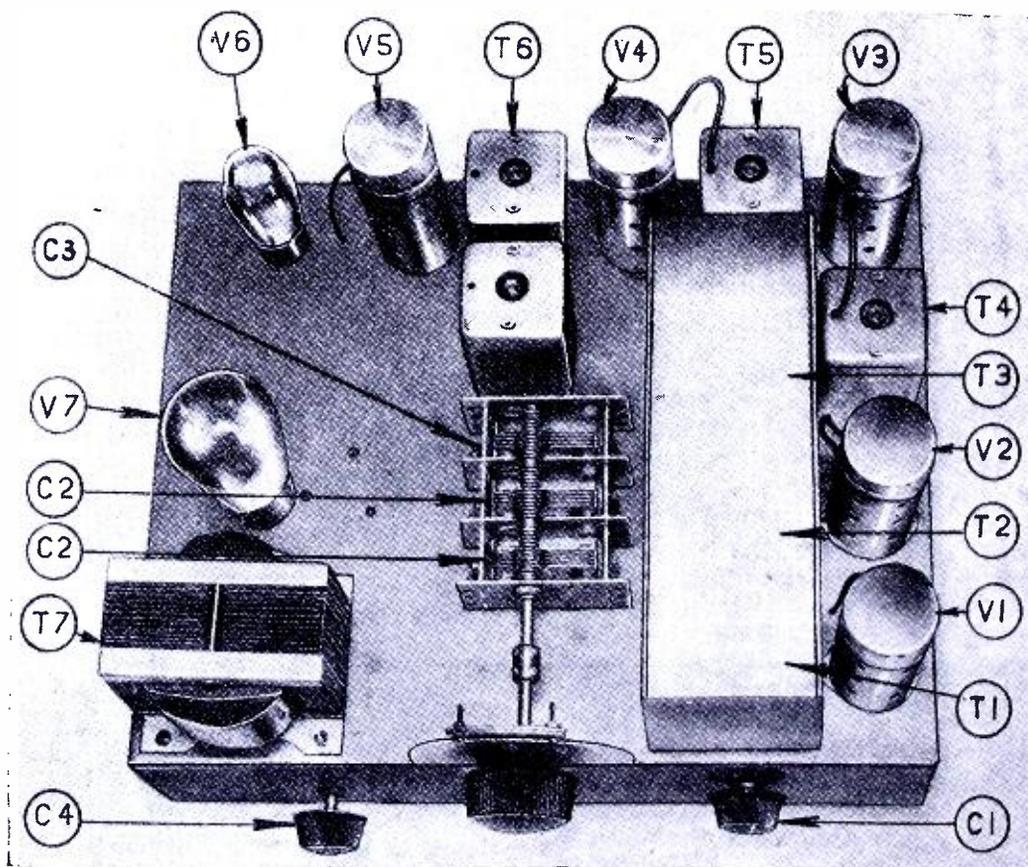

TOP VIEW OF THE "Hg-7" WITH ALL PARTS LABELED  
The transformer in front of T6 is for c.w. reception.


arate oscillator and first detector, but the increase in efficiency certainly justifies the use of this tube.

The output of the 6A7, which is i.f., feeds into V3, the first i.f. stage, which, in turn, feeds into a second i.f. stage and, finally, into the second detector. This second detector uses a type 75 duo-diode triode. This tube performs three separate and distinct functions: first, it rectifies the incoming signal using one of the diode plates; second, it provides delayed automatic volume control by virtue of its second diode plate; and third, it amplifies the a.f. output and resistance-couples it to a type 41 output tube.

The power unit is very conventional and needs no further comment. The voltages at the important points along the bleeder resistor are specified in the diagram. These voltages, however, are only approximate, and may vary 5 volts at the highest point, about 3 volts at the intermediate point, and about a one-half volt at the lowest point. These voltages are measured with respect

to the B— end of the power unit, which is *not* at chassis potential.

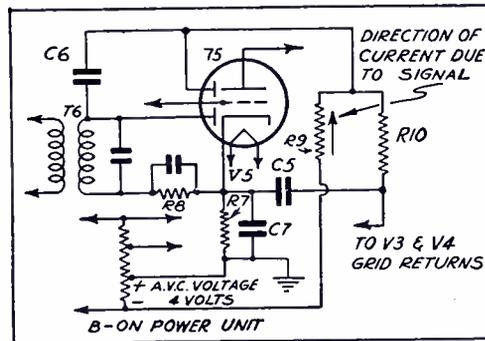
The sensitivity of this receiver was measured by the writer using a standard signal generator and was found to have a sensitivity of 3 microvolts absolute, or  $\frac{3}{4}$  microvolt per meter, at 30 meters, and a sensitivity of 1 microvolt absolute, or  $\frac{1}{4}$  microvolt per meter, at 60 meters. Those familiar with sensitivities will find that these figures are more than satisfactory.



**DETAILS OF THE A.V.C. CIRCUIT**  
Detailed schematic of the a.v.c. circuit, showing how delayed a.v.c. is obtained.
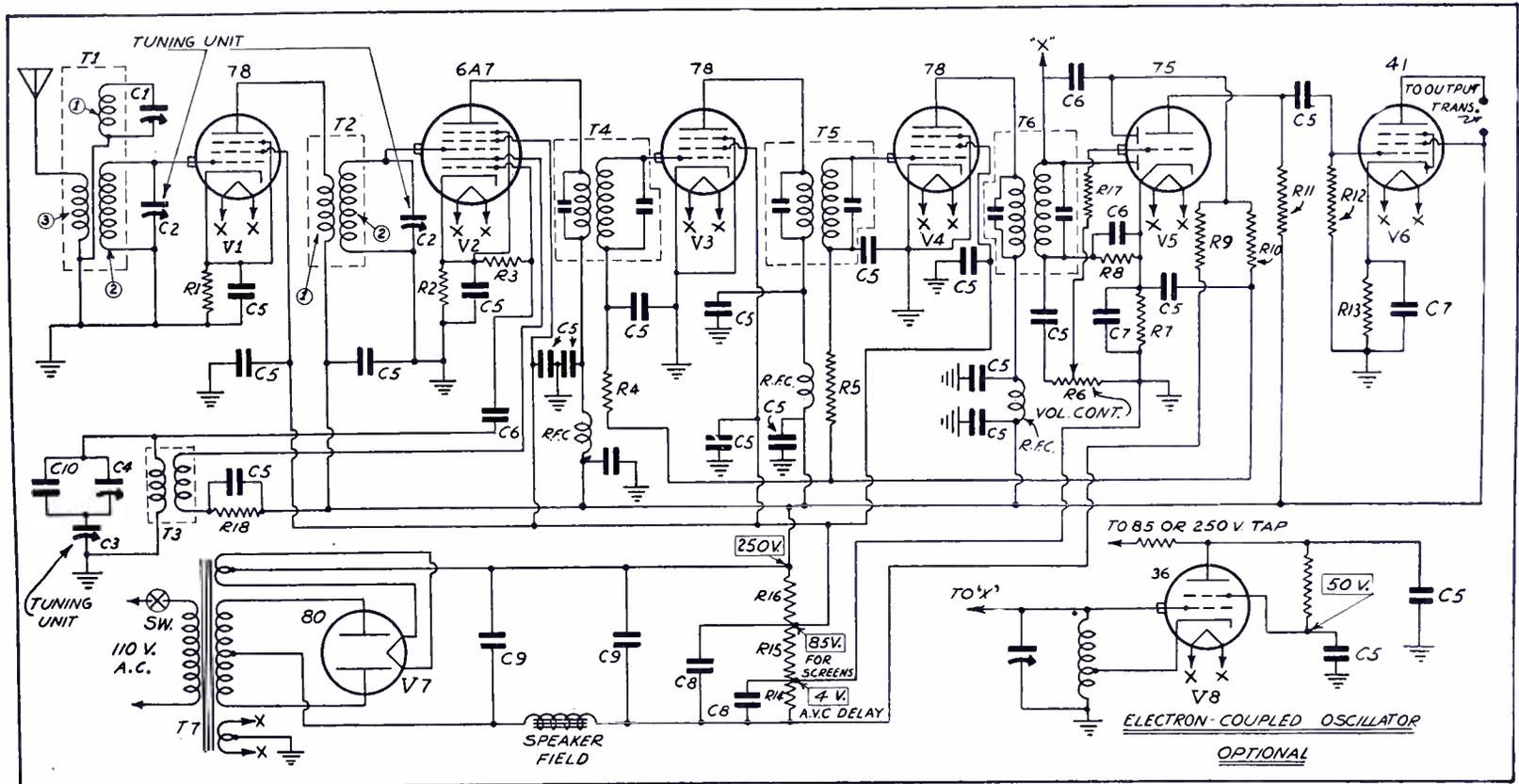
## The Delayed A.V.C. System

In one of the preceding paragraphs I mentioned that the chassis is not connected directly to the B— end of the power unit. The reason for this becomes apparent when the A.V.C. system is considered. Refer to the detailed schematic of this system. It will be seen that the left diode plate is used for rectification and produces a voltage across resistor R8, which is audio. This voltage is applied through a coupling condenser to the grid of its triode section, and volume is controlled by means of potentiometer R6. The right-hand diode plate connects to two resistors, R9 and R10. One end of R9 connects to the low point of the bleeder resistor, while the corresponding end of R10 supplies C bias to tubes V3 and V4. Note, also, that a small fixed condenser having a capacity of .00025 mf. and designated C6 is connected directly across the two diode plates. It should also be noticed that the cathodes of V3 and V4 connect directly to ground.




**COMPLETE SCHEMATIC CIRCUIT OF THE "Hg-7" AND LIST OF PARTS FOR IT**

- C1—35 mf. variable condenser, Hammarlund Midline.
- C2, C3—three gang 140 mmf. tuning condenser, General Instrument type 1450, counterclockwise rotation.
- C4—100 mmf. Hammarlund variable condenser, S.L.C.
- C5—.01 mf. fixed condensers, Aerovox, twenty-one required (twenty-three required with local oscillator for A.V.C.).
- C6—.00025 mf. fixed condensers, Aerovox, three required.
- C7—25 mf. tubular electrolytic condensers, 25-volt rating, two required.
- C8—4 mf. metal-cased condensers, Flechtheim, 200-volt rating, two required.
- C9—8 mf. electrolytic condensers, Aerovox, 600-volt rating, two required, insulated type.
- C10—.003 mf. fixed condenser, Aerovox.

- R1—350-ohm,  $\frac{1}{2}$ -watt resistor, Lynch.
- R2—300-ohm  $\frac{1}{2}$ -watt resistor, Lynch.
- R3—50,000-ohm resistor, 1 watt, Lynch.
- R4, R5, R10, R11, R17—1-megohm resistors.
- R6—5-megohm potentiometer and line switch, Frost.
- R7—2500-ohm resistor, 1 watt.
- R8, R9, R12—5-megohm resistors.
- R13—600-ohm resistor, 1 watt.
- R14—50-ohm, 5-watt resistor, Acra-test.
- R15, R16—10,000-ohm 5-watt resistors, Acra-test.
- T1, T2, T3—coils as specified in the article, Mercury.
- T4, T5, T6—465 kc. i.f. transformers, Meissner, Litz wound.
- T7—power transformer: high-voltage secondary, 850 volts with center tap to supply 100 ma. d.c.; one 5-volt, 3 ampere filament winding for 80 rectifier; one 6.3-volt, 3

- ampere filament winding for remainder of tubes, Mercury.
- 9—six-prong sockets for antenna coil, first-detector coil, for tubes V1, V3, V4, V5, and V6, and two for the coil shields without contacts on them.
- 4—four-prong sockets for the oscillator coil, speaker plug, for V-7, and for oscillator coil in shield can.
- 1—seven-prong socket for the 6A7 tube.
- 1—spot welded steel chassis as specified in mechanical drawing, also four coil shields, Mercury.
- 3—2 millihenry r.f. chokes.
- 1—power cord and a.c. plug.
- 1—dial and cabinet (a National vernier dial was used on the model shown).
- 7—Sylvania tubes: 1—80; 1—41; 1—75; 1—6A7; and 3—78.
- 5—tube shields.

Now, with no signal applied, the voltage of the A.V.C. diode is -5 volts with respect to ground, 4 volts due to the bleeder resistor and 1 volt due to resistor R7, which supplies grid bias for the triode section. This plate, therefore, cannot draw current, since it is negative with respect to the cathode. The potential on the grids of the two i.f. tubes equals 4 volts, since the grid return leads travel through R10, R9, and the 4-volt section of the bleeder to ground. There is no voltage loss in R9 and R10 simply because there is no current flowing through them with no signal. Now, when the carrier voltage of a station reaching the detector is strong enough so that the voltage across C6 (connected between the two diode plates) is greater than 5 volts, the right-hand diode plate starts to draw current because, by virtue of the signal, it begins to become positive. The only place from which this current can be obtained is the bleeder circuit, so that current starts to flow through R9 in the direction indicated by the arrow. This results in one end of resistor R9 becoming negative because of the signal. This negative voltage is carried through R10 to the grid circuits of the i.f. tubes. Hence, the bias on these i.f. tubes increases and decreases in direct proportion to the signal strength, since the diode rectifier is a linear rectifier. This increase in bias lowers the sensitivity of the receiver, and it is in this manner that A.V.C. is obtained. The 5 volts constitutes the delay section of the A.V.C. In plain English, the A.V.C. system is delayed until the carrier voltage causes the A.V.C. plate to become positive before A.V.C. action starts.

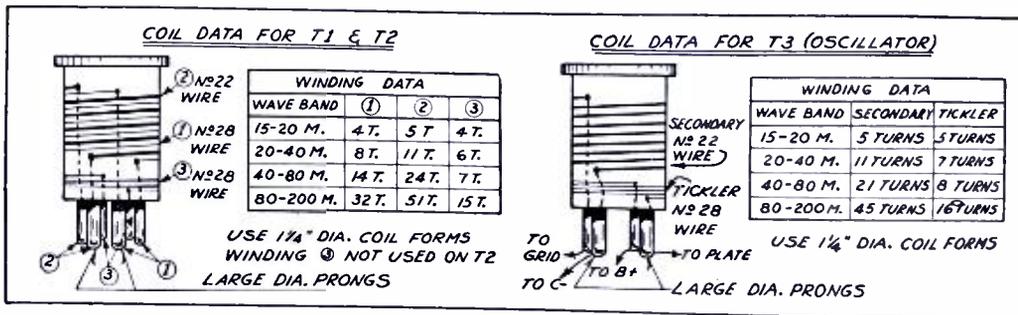

COIL DATA FOR T1, T2, AND T3 FOR THE "Hg-7"

This system has proved very effective in operation, and we found no necessity to amplify this A.V.C. voltage. A further increase in A.V.C. action would only tend to reduce the sensitivity of the receiver to a point where noise would have sufficient magnitude to lower the sensitivity and blanket the signal entirely.

### The Oscillator Padding Circuit

One of the major problems in designing a short-wave superheterodyne is obtaining and maintaining the proper i.f. It is not sufficient to merely remove turns from the oscillator coils in order to secure the i.f. of 465 kc.; this i.f. must be maintained over the entire short-wave band. For this reason, the padding circuit composed of C4 and C10 is used; the main oscillator tuning unit is C3. C4 is a variable 100 mmf. condenser, which is tunable from the front panel. When the coils are properly adjusted, the i.f. may easily be maintained constant, and any slight misadjustments compensated by varying C4.

The coils used in this receiver may easily be wound at home in accord-


ance with the data given in a separate sketch. The antenna transformer, T1, uses 3 coils: a primary, a secondary, and a third winding across which is connected a 35 mmf. condenser, C1. This coil is wound on a six-prong form and has its coils numbered 1, 2 and 3, respectively. Coil 2 is the secondary. Coil 1 is an interwound primary having the condenser C1 shunted across it. Coil 3 is wound near the base of the form and connects to the antenna and ground.

Transformer T2, although it has but two coils, is also wound on a six-prong form. The reason for this becomes apparent when one attempts to buy coils for use in this set. For some unaccountable reason, four-prong coils are not made with high impedance primaries suitable for use with type 78 tubes. To obtain such primaries, it is necessary to buy six-prong coils, and since the third winding on these coils is unused in this part of the circuit, we have the anomalous condition of a two-winding transformer on a six-prong form.


The coils comprising C3 are of the four-prong type simply because the primary is used as the tickler, and the ticklers on these four-prong coils are very satisfactory.

There is nothing unusual about the power unit. It is standard in every respect and is economical because no choke is used—the speaker field, which should have a d.c. resistance of 1000 ohms, acts as the choke. Two 8-mf. electrolytic condensers provide sufficient filter action. A glance at the underview of the receiver will show that there are two large paper condensers used in the filter system; a top view of the receiver shows an electrolytic condenser used in the filter circuit. These condensers happen to be present in the model photographed although they have been eliminated in later models, and two 8 mf. electrolytics as shown in the schematic circuit are used instead. It might be well to mention here that the detailed drawing of the chassis layout makes provision for these electrolytic filter condensers.

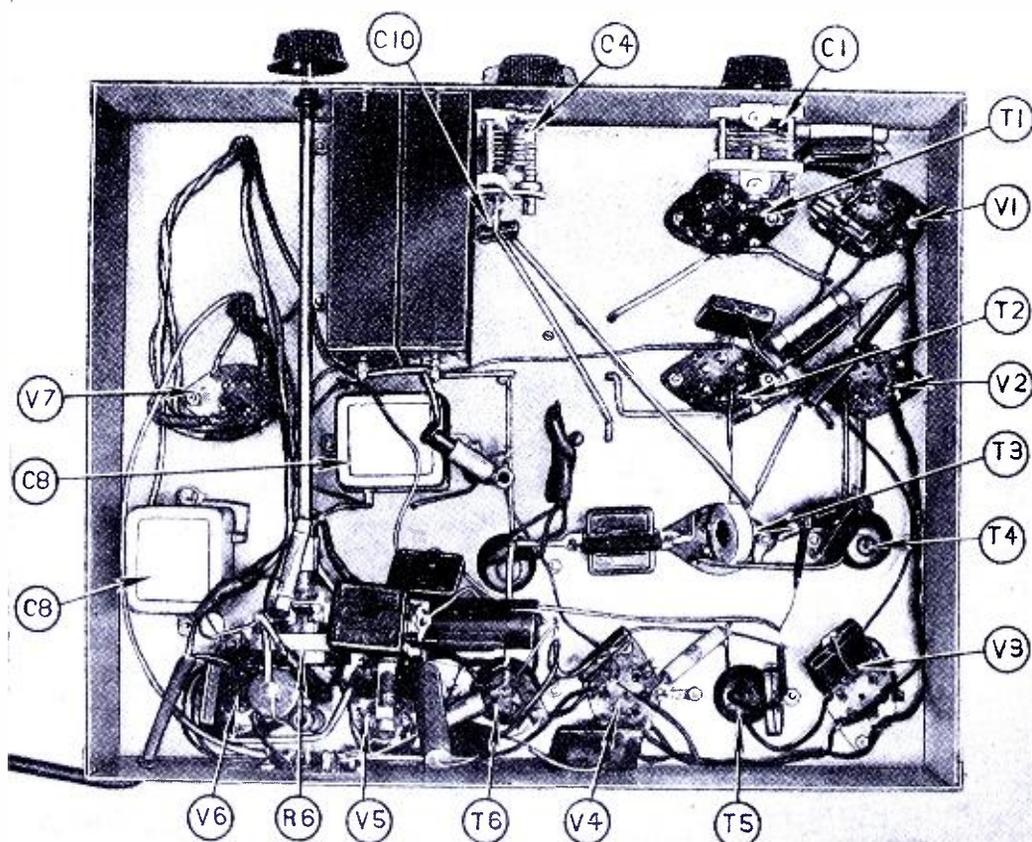Although the receiver was not designed for the reception of c.w. signals, a local oscillator may be incorporated for such purpose if so desired. It is best to use an electron-coupled oscillator, the circuit of which is shown in the schematic diagram.



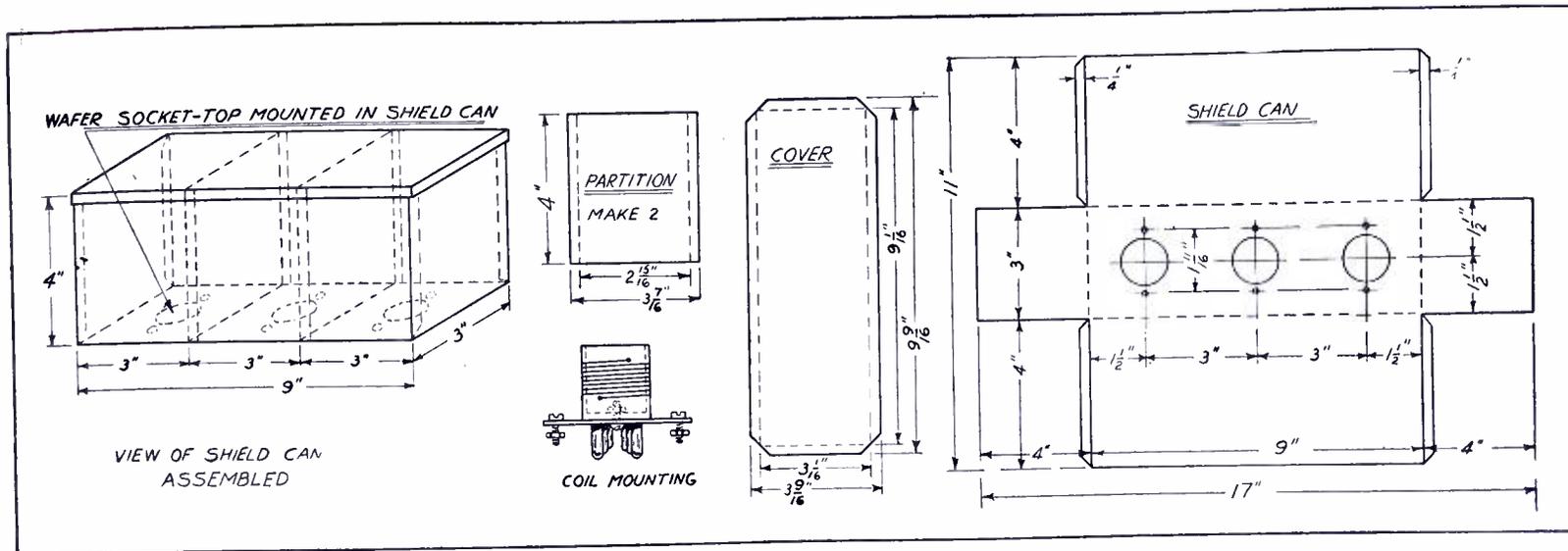UNDER-VIEW OF THE RECEIVER WITH MAJOR PARTS LABELED  
The two large condensers may be replaced by electrolytics.



DETAILS OF MOUNTING THE COILS IN THE SHIELD CAN—FOUR CANS ARE NEEDED

In view of the fact that this receiver was intended mainly for broadcast reception, this local oscillator was omitted in later models, but sufficient room had been left in the chassis for its incorporation at any time. Thus, one of the i.f. transformers, which is not labeled and which is shown in the top view of the receiver, is the electron-coupled oscillator.

### Constructing the Receiver

There is very little to say regarding the mounting and wiring of the receiver itself. Those readers who have built sets before realize the essential details of wiring, and it would be a waste of space to repeat these fundamentals. There are, however, a few points which should be enlarged upon if this superheterodyne is to function properly. The first requirement is that all plate leads be kept as short as possible. Although you probably have heard this statement many times in the past and are possibly fed up with hearing it now, I would like to relate how one of the problems in the design of this superhet was overcome.

In one of the earlier models, uncontrollable oscillation in the i.f. amplifier prevented us from obtaining maximum sensitivity. Every time we lined up the i.f. transformers, the oscillation, of course, would drown out everything. We tried choking and bypassing every single lead in the r.f. and i.f. portions of the receiver, but to no avail. After considerable experimentation, it was found that the plate and B+ leads of both i.f. stages had to be shortened. When this was done, oscillation stopped and stability was obtained. A glance at the schematic circuit will also show the very complete filtering in the plate-return circuits.


Mount the apparatus as shown in the photographs and wire accordingly. Please take your time at this stage of the game if you want to have a receiver that you can be proud of.

### Coil Shields

The problem of what coil arrangement to use had been given considerable thought. Switching arrangements, while they are excellent, did not suit us, simply because suitable switches could not be purchased in the open market. The only other efficient arrangement left was plug-in coils, but here again the necessity for changing three coils every time the wave band had to be changed did not seem highly desirable. This problem was solved by Mr. Clifford E. Denton, who suggested that the coils for a given wave band be placed in one box, so that all that need be done to shift wave bands is to change one box. Furthermore, the coils would automatically be shielded and be kept out of the way of the operator.

The arrangement as finally decided upon is shown in a sketch. A metal box, preferably of copper, aluminum, or copper-plated steel, 9" long, 3" wide and 4" high, is divided into three compartments as shown. The usual socket mounting holes are drilled in the center of each compartment and a wafer type socket *with the contacts removed* is mounted in each compartment. The coil is then plugged in and a hole is drilled through this wafer socket through the coil form. A nut and bolt thus fastens the coil form to the socket. This construction is shown in a separate sketch. Thus, when finished, each compartment has a coil in it, the coil being fastened to the upper part of the wafer socket by means of the nut and bolt, and the wafer socket, in turn, is mounted


(Continued on page 47)

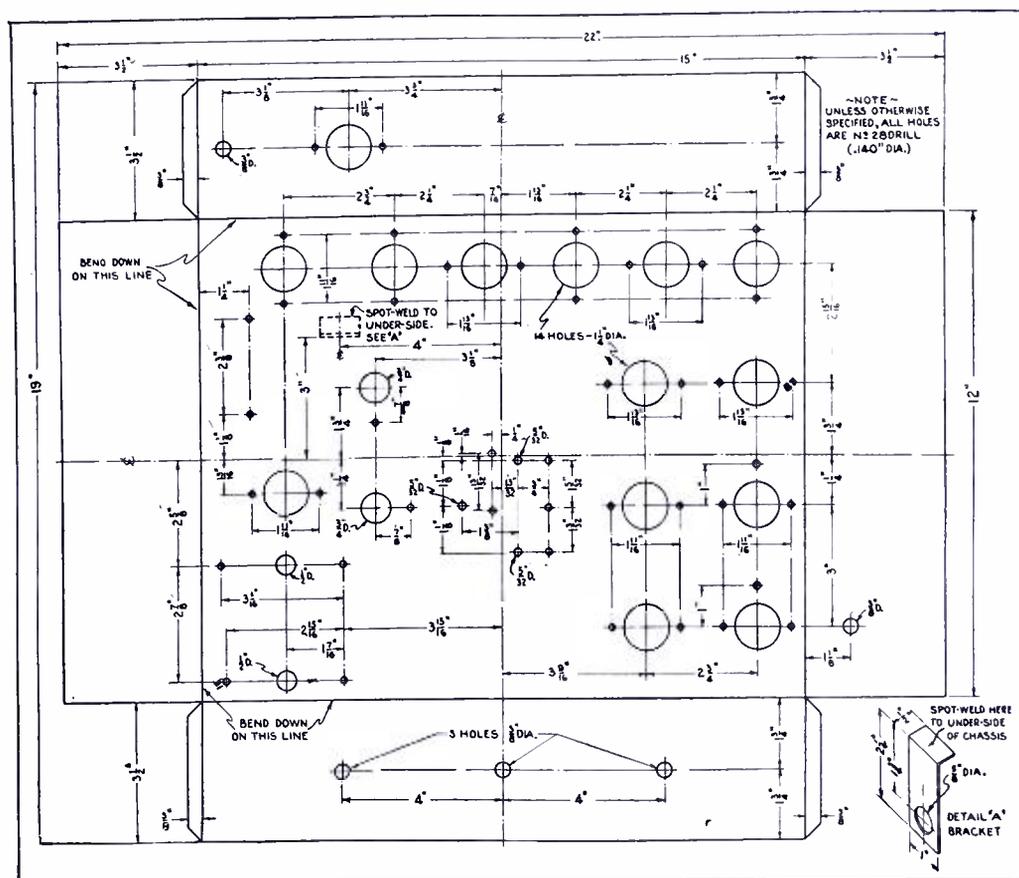

MECHANICAL DRAWING OF THE CHASSIS OF THE SET  
This drawing is for the actual parts specified in the list of parts.

# Satisfactory Short Wave Reception

by  
Arthur H. Lynch

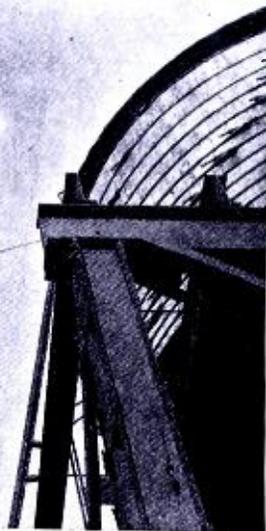

A Lynch antenna system installed on the roof of the American Sales Co. building in New York.

**H**OW best to get rid of background noise becomes a more and more important question as we go up in frequency and down in wavelength. In the old days when, with tall, pillar inductances or concentrated honeycomb coils, we listened to "over-the-pond" stations, it was possible to locate the receiver in a veritable hot bed of electrical devices of one type and another and it was rarely that the interference they kicked up caused us any real concern. Why, for a number of months we stood a regular twenty-four hour watch, with three eight-hour shifts, in the tower of the N. Y. Times Building, at Broadway and 42nd Street, New York City, where we copied regular schedules from most of the then important foreign stations. There was plenty of ordinary static, to be sure, but there was very little of the man-made variety. Or, to put it more correctly, there was plenty of both, but the man-made variety did not bother us above four thousand meters, where most long-distance communication was being carried on at that time.


The first time that the serious trouble which background noise or man-made static causes became generally recognized was during the first International Radio Broadcast Tests in 1923. At that time, with every broadcasting station on the North American Continent shut down for an hour each night for a whole week, and with every receiver cranked up to the limit of its sensitivity in the attempt to hear the foreigners, radio fans became cognizant of the effect of local interference. And the waves used at that time were the ordinary broadcast waves, most of them being between 400 and 500 meters. The problem has become aggravated as the trend

in waves has been down-hill—the frequency up.
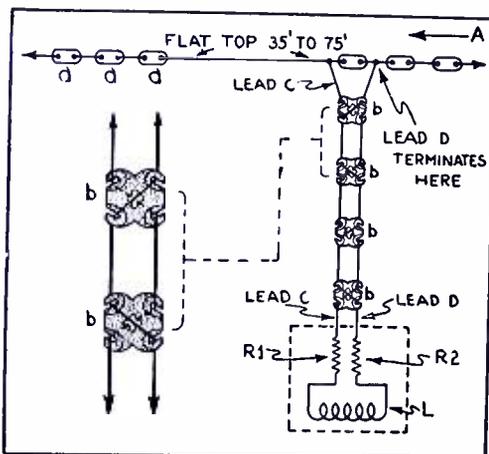
## Beam Arrays and Transmission Lines

The publicity which followed some of the recent tests on short waves and ultra short waves has brought a number of rather intricate and very expensive, as well as very effective, receiving systems to the attention of the serious investigator; and a natural demand for additional information on the part of the hams learning of the improvement has followed. The publicity, valuable as it is, has been just a little misleading. It would seem that the present tests and improvements have been worked out with some new sets of fundamentals; that the engineer has waved his magic wand, and out of his trick hat has popped a new rabbit in the form of a receiving antenna which cuts out interference, but which costs thousands of dollars to erect.

In his classic presentation of this important subject in the latter part of 1930 before the Institution of Electrical Engineers, London, T.



Method of connecting a transposed lead-in to an "L" type antenna.

Walmsley, reviews the art in this way:

"Although as early as 1899 Brown had taken out a patent for a type of aerial which utilized the principle of interference, it was not until 1927 that the first commercially successful 'beam' high-speed telegraph service was inaugurated at Bodmin, Cornwall. . . .

"Since the establishment of the fact that short-wave beam telegraphy is a highly successful commercial proposition, many different types of beam arrays have been developed. *The principle in all is the same; by means of wires correctly spaced, and currents correctly phased, an increase in field strength in the desired direction and a decrease in the other direction is produced.*" (Italics are present author's.)

Some idea of the complexity and the expense involved in the erection of the arrays which are being used for commercial point-to-point purposes may be had from the following considerations.

While a number of these arrays have been designed for transmission purposes, the same principles are involved when it comes to receiving. Remember the ads you have seen from time to time in the newspapers telling you that you can now hear all the foreign broadcasting stations at any and all times with this or that new gadget, which can be hitched to your present receiver, which costs little or nothing, and which only requires a wire under the rug? Keeping such statements in mind, a certain amount of humor may be had from pondering a few more paragraphs from Mr. Walmsley's interesting treatise, under a heading which he is pleased to call "Economic Size of Array." Here they are; read 'em and weep:

"In the case of an array consisting of exciting and reflecting panels for a wavelength of 16 meters, a convenient span is eight wavelengths, which, allowing for attachments and clearance between supporting structures and end radiators, would necessitate two towers separated by 500 feet.

"An array having two rows of vertical radiators, one above the other, would require towers  $2\frac{1}{4}$  wavelengths, or 120 feet in height. This figure, taken from an actual design by the author, allows one quarter of a wavelength clearance from the ground, three quarters of a wavelength for dip of the supporting cables, and one quarter of a wavelength for insulators and attachments. Again, the towers would be required to resist a total top pull of four tons, viz., two tons for the exciter panels and two tons for the reflectors. An array having four vertical rows of half-wave radiators would require twice the dip allowed for the two row array to ensure a four ton top pull. The height of the towers required would thus be about four wavelengths, i.e., 210 feet. . . . Assuming an approximate cost of

fabricated steel of \$200.00 per ton inclusive of foundations and erection, or a total of \$3,800 and \$8,000 respectively for the two towers for each array, and estimating the cost of the arrays complete with insulators as \$1,750 and \$3,250 respectively, the grand totals are \$5,550 and \$11,250 respectively. The field-strength gain of the four vertical half-wave aerial over the two vertical half-wave aerial has been shown to be 2.8 decibels, and this gain might be well worth the extra expenditure involved."

My purpose in bringing these facts and figures to your attention is two-fold. Firstly, it will indicate that serious attempts to improve short-wave communication are not new, and they are engaging the attention of an increasing number of the greatest minds in the communications field. They indicate that great care and great expense are being incurred with a view toward making slight improvements in the efficiency of the radiating and pick-up systems, and that the expense is considered worth while. Secondly, it is obvious from the few examples which space permits calling to your attention here that this is a fertile field for the serious investigator, and that, in more modest forms, some of the advantages of these elaborate systems may be employed by the radio enthusiast to whom radio communication of one form or another is an avocation rather than a vocation.

### Transmission Lines for Ham Radio

In the locating of a transmitting aerial, and even more generally in the locating of a receiving aerial, it is desirable to have the equipment itself some distance from the aerial proper; receiving conditions in metropolitan centers impose this restriction in nearly every case. As a matter of fact, this is more of an asset than a liability, since it enables us to place the receiving antenna system a considerable distance from the receiver itself and well out of the field of man-made interference.

In order to get from the antenna proper to the transmitting or receiving apparatus, it is generally desirable to use some feeder system which has no effect upon the antenna system itself and which does not form any portion of the radiating or pick-up system, as such. The leads used for this purpose are called "transmission lines." They are usually designed to have several very important properties and their design determines the degree to which these various properties may be obtained.

The principal difference between the schemes used for short-wave reception and the systems used for the broadcast waves lies in the selection of the transmission line and the method of coupling it to the antenna and the receiver. The systems which

### This Series of Articles

*The article is the third of a series of articles by Mr. Lynch on "Satisfactory Short-Wave Reception".*

*The first of the series outlined, in general, the problems involved in short-wave reception; the second part gave specific directions on the installation of transposed lead-ins; and this, the final article, illustrates the problem from the economic angle—an important one for the average radio listener.*

*Any questions pertaining to this subject should be addressed to Mr. Lynch, care of SHORT WAVE RADIO.*

work well for the broadcast wavelengths introduce rather severe losses when we attempt to use them on short waves. The shorter the waves the greater the losses. The reason is very simple to understand.

In most of the really effective noise-free systems for broadcast reception we have one lead or a pair of twisted leads running from the antenna to the receiver through a metallic sheathing; the sheathing is grounded. The distance between the lead and the sheathing is not very great, and therefore we have a condenser effect. The puny signal voltage picked up on our antenna for use in a suitable building-up process in our receiver is thus bypassed right through the condenser formed by our lead and is shot into the ground without getting to our receiver at all, or in a very greatly weakened condition.

In order to cut down this loss as far as possible, elaborate systems have been put in operation in several of the important commercial stations as well as at those stations where short-wave broadcast signals are picked up for retransmission. In cases of this character, an improvement of a few tenths of a percent is generally worth while, because the

result is made to benefit a great many listeners; but the benefits derived from such a system are beyond the engineering and the financial limits of the average short-wave operator. Suitable systems for home use on short waves are available, and they are giving a very favorable account of themselves in actual use. Before this year is out, the average performance of the short-wave receiver—and therefore the effectiveness of the short-wave transmitter—will have improved materially.

### Analysis of Losses


The losses in transmission lines may be classified under three headings: (1) ohmic loss, (2) dielectric hysteresis and eddy-current losses, and (3) radiation losses.

Ohmic losses are appreciable at high frequencies. This resistance loss may be reduced by using several insulated wires of small diameter instead of one large wire for each of the two members of the transmission line. For example, a No. 5 wire has only twice the high-frequency resistance of No. 00 wire of equal length. Thus, assuming that the proximity of other wires does not change the resistance values of individual wires, four No. 5 wires would have half the resistance of one No. 00 wire of equal length. To test the truth of this contention a 16.1-meter array was fed by a group of transmission lines running along the same poles. Three insulated open lines, two of which were used normally for two other arrays, were bonded at the transmitter and the array ends. From the current values of both ends of the lines the efficiency of transmission was calculated. The result showed that the reduction in loss, namely 16 per cent, was approximately the same as the estimated reduction due to less ohmic resistance.


No method is known of estimating dielectric hysteresis losses with any degree of accuracy. To reduce insulator losses the best type of ceramic or other insulation should be used. Subject to mechanical requirements, the insulator should be as long as possible and the cross-section as small as possible to minimize leakage and reduce local capacity at the points of attachment to transmission poles. The latter precaution is necessary to lessen small reflections due to changes in the constants of the line.

Obviously, we cannot avail ourselves of the elaborate short wave systems which are used commercially, so as to receive with the same satisfaction with which we now receive our local broadcast stations. However, a few intelligent applications of the same fundamental principles in a less elaborate degree, and a few intelligent compromises, make it possible, at very slight expense, to get very much better results on the

(Continued on page 38)

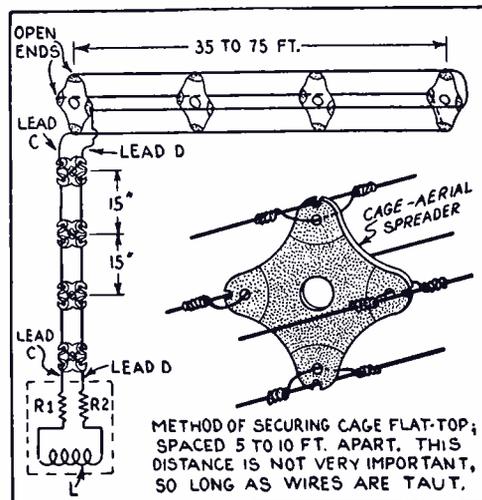

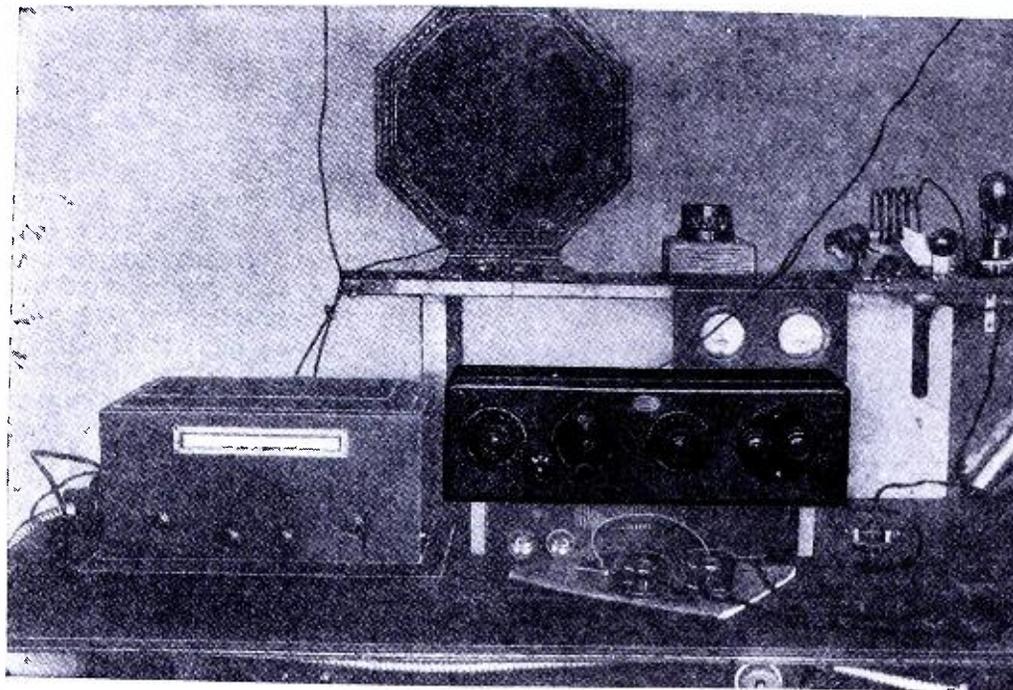The transposed lead-in connected to a cage aerial. See text.



THE REVAMPED A.K. 20 ALONGSIDE A NATIONAL SW-58

## Revamping the A. K. 20 for Short-Wave Use

**A** GREAT many of the people who are getting into the short-wave game are ex-broadcast experimenters and set-builders from the 1920-1928 broadcast era, people who bought a lot of radio apparatus at a time when sockets cost \$1.50 apiece, variable condensers \$7.00, and tubes, \$12.00. They have a fairly good foundation of practical radio experience, but simply are not "up" on present day short-wave practice.

Many of these people do not want to buy modern receivers immediately, but prefer to renew their contact with the radio game by first experimenting with simple and inexpensive outfits built up out of old parts they have on hand or rebuilt from old broadcast receivers.

A very good way for these people to get started is to pick up some ancient broadcast receiver and to revamp it. There must be thousands and thousands of obsolete t.r.f. receivers kicking around in radio dealers' back rooms. These can be purchased for next to nothing, in most cases the dealers being delighted to get rid of the junk. The type of set that is most suitable for short-wave conversion is the old 5-tube, 3-dial battery model. There were probably more sets of this type made and sold than of all other types put together to date. Who does not remember the old Fada, Freed-Eisman, Garod and Eagle neotrodynes, and a host of other similar t.r.f. sets? Even today, some of the radio surplus houses list these sets for sale at prices that would not even have paid for the shipping cases at

the time they were first produced.

Just to show what could be done along these lines, the writer visited a number of radio dealers in his own community, which is in Long Island, and without any trouble at all picked up an old Atwater Kent model 20 receiver for the munificent sum of \$1.25. He does not doubt that he could have cut this down to the sum of an even dollar if he had cared to bargain! He deliberately avoided visiting New York's famous Radio Row, along Cortlandt Street, because there is only one such place in the United States, and any experience he had there could not be duplicated very well in other cities.

### THE "WHY" OF THIS ARTICLE

The editors of this magazine have received so many inquiries of late regarding the use of old broadcast receivers for short-wave work that they decided to go out, buy a cheap broadcast set of the vintage of 1925, rebuild it for s.w. use, and let you have the dope.

The investment was so small, and the results so satisfactory, that the complete story is presented herewith in detail.

### Why the A.K. 20?

This Atwater Kent model 20 was a fortunate selection because it is certainly a typical t.r.f. set of the pre-a.c. period. It contains three variable condensers, to the back of each of which is fitted an r.f. tuning coil, two individual sockets for the r.f. tubes, a triple socket block for the detector and a.f. tubes, and two encased audio transformers. Each condenser has its individual dial on the front panel, which also holds an on-off switch and two filament rheostats. This same description can be applied very accurately to any number of sets of other makes. The sockets are all of the four-prong type, the set probably having been designed to use 201A's in the r.f., detector and a.f. positions, and a 112A or 171A in the output position. Front and back views of the set before it was "given the works" are shown herewith.

Although the cabinet is of wood, the front panel is either iron or steel. The sockets and audio transformers are mounted to an iron shelf welded to the back of the panel.


First of all, the set was torn completely to pieces, a job that required only a soldering iron, a screw driver, and a pair of pliers. The old fixed condensers and resistors were discarded, as they were not marked in any way. The r.f. coils were thrown into the junk box, as their forms might prove useful some time. The variable condensers were thoroughly cleaned up, as they are very beautiful instruments, with conical bearings, accurately adjustable tension plates, and moulded bakelite end-pieces.
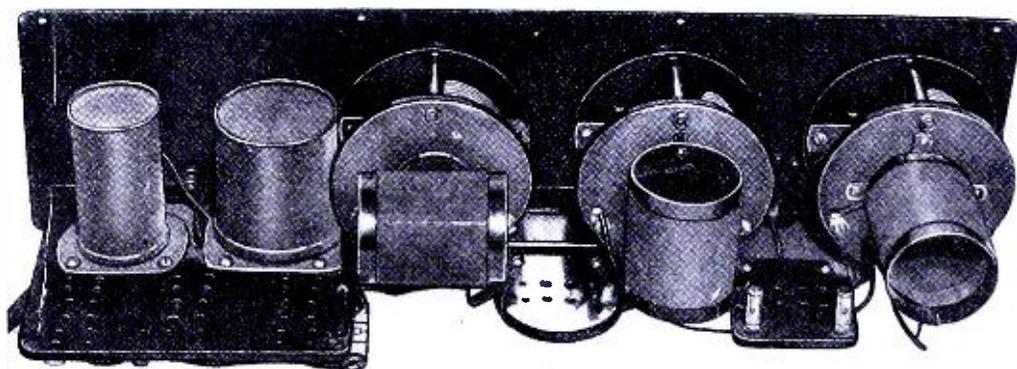
### Designing the New A.K.

In view of the straight-in-line arrangement of the parts, with the r.f. tube sockets between the condensers, it was decided to make the new short-wave set consist of one untuned r.f. stage using a type 34 tube, a regenerative detector using another 34, and a single audio output stage using a 33 pentode. These tubes work very satisfactorily with ordinary No. 6 dry cells for filament supply and three small 45-volt B batteries for plate supply. A.c. operation was decided against because it was felt that the cost of a power pack would be too high for a mere "junk" set; besides, if a.c. operation were adopted, it would have been just as cheap to buy or build a set of new and modern design. Batteries are cheap and will last long enough to familiarize the builder with the many tricks of short-wave operation that he should know before he buys himself a modern tuned t.r.f. or superhet set. The surprising "wallop" that the set developed when it was finished more than justified the choice of these tubes.

The socket that formerly held the first r.f. tube in the original broadcast circuit now holds the untuned r.f. amplifier tube, V1. Since the 34





REAR VIEW OF THE ORIGINAL SET EXACTLY AS PURCHASED

alone. The values of these rheostats are unknown, but they seem to be just right when three volts of dry cells are used for filament supply. The correct filament voltage of two volts was obtained with the rheostats turned about half way up. The original six-wire battery cable supplied with the set was again used.

### Screen Switch Useful


The AK model 20 happened to be fitted with a three-point switch which was used originally as a selectivity control of the primary of the first r.f. transformer. As long as this was available, it was connected in the position marked SW2. With this switch open, the potentiometer R6 does not draw current from the "B" batteries, which would be the case if no such switch were used. With battery type tubes, it is a good idea in all cases to use a switch of this kind. Incidentally, this switch

proved to be very useful when the receiver was used in an amateur station. During periods of transmission this switch was simply opened to prevent the signals from thumping in the ears of the operator.

The revamped receiver worked perfectly the first time it was turned on. It was only necessary to experiment with a few different grid leaks, R4, to obtain smooth regeneration.

Rough tuning is done with condenser C1 and fine tuning with C2. A National type B midget vernier dial was attached to C2 to facilitate fine adjustment. Incidentally, this arrangement produced a most excellent band-spreading receiver for amateur purposes.

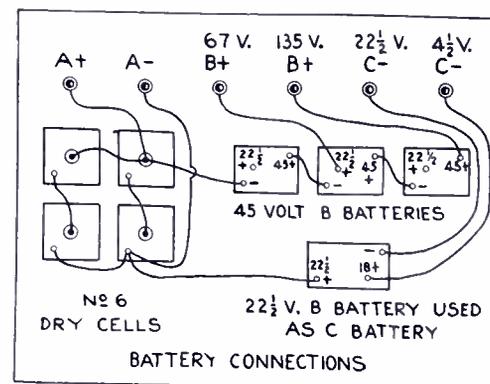The set was never intended for anything more than ear phone operation, but many signals are received with such strength they work a small magnetic speaker quite comfortably. This is with an antenna



BATTERY CONNECTIONS  
Hook-up of the batteries for the A.K.

only about 40 feet long and about 10 feet off the ground. The four plug-in coils, for which complete winding data are given, tune from about 13 to 200 meters and are providing no end of interesting reception. The absence of background noise and the smoothness of the regenerative action make tuning a real pleasure.

As four No. 6 dry cells were available, these were connected in series—parallel, as shown. They maintain a surprisingly steady voltage at the terminals of the tube sockets. In fact, it is unnecessary to change the rheostats at all, once the correct adjustments have been determined by means of a small d.c. voltmeter. The total filament drain is only .38 ampere, which is a very comfortable load on these batteries. The same four dry cells, after more than three weeks of pretty steady use, showed no appreciable drop in voltage. The measured plate current drain is only about 15 ma., which means that the B batteries will outlast the set.


For filament supply it is also possible to use a single cell of a storage battery, which gives a little more than two volts. In this case the rheostats should be turned all the way up. It is desirable to check the filament voltage by means of a small d.c. voltmeter; maintain the value as closely as possible to two volts.

Complete coil winding data are given in the lower right hand corner of page 17, directly opposite. The 20-40, 40-80 and 80-200 meter coils are all that are really necessary.
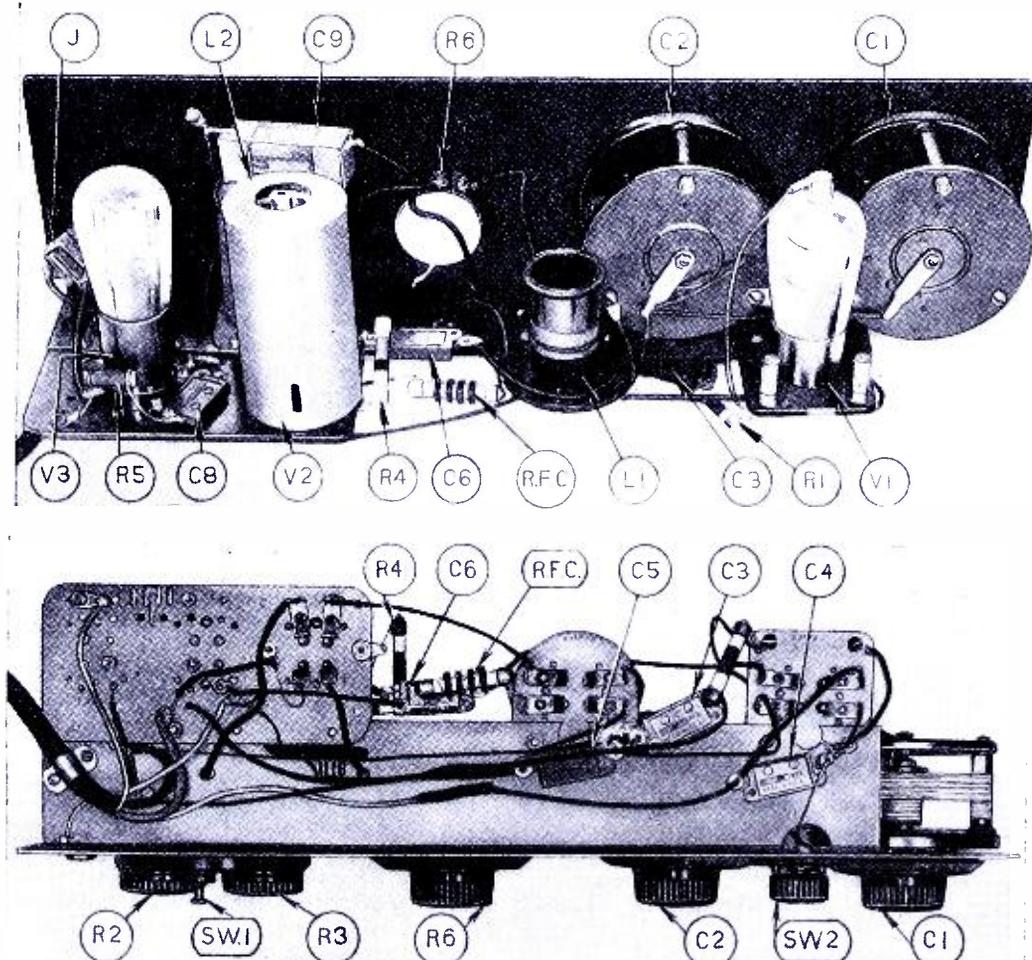
### What We Received

Although no particular attempt was made to log foreign stations, programs from EAQ, Madrid; Radio Coloniale, Paris; and the various Daventry and Berlin transmitters have been received quite regularly. Daventry and Berlin can even be heard on the loudspeaker quite comfortably through a sensitive magnetic speaker. And code stations! No attempt is even made to even count them, as they drop in by the hundred.

While not all new short-wave enthusiasts will be able to obtain Atwater Kent model 20's, the general directions given in this article can be applied just as readily to other sets.



TOP AND BOTTOM VIEWS OF THE REVISED A.K. 20  
Compare the designations with those given in the schematic circuit.


# Problems in S.W. Super Design

EVERY so often we hear some one say, "Why not more s.w. supers?" And just as often the answer is, "Aw, they're too hard to adjust." The strange part of the situation is that supers are hard to adjust—if you go about it haphazardly. Suppose we build a super—on paper—make it squeal and howl; in fact, let this hypothetical super do everything but deliver signals. O.K.? Let's go.

This super will consist of a tuned r.f. stage; a first detector, also tuned, an oscillator, two stages of i.f., a second detector and one or two stages of audio. We have just finished wiring it—on paper—but the thing won't perk. Where do we start and when do we finish?

The first thing to do is to break the plate circuit of the first detector and insert a pair of phones, connect an aerial and ground and tune carefully. Still no sigs. Set the trimmer on the tuned r.f. stage about half-way in, and gradually adjust the first-detector trimmer; after each adjustment, turn the tuning dial over the complete range. This procedure is tiresome; but if you

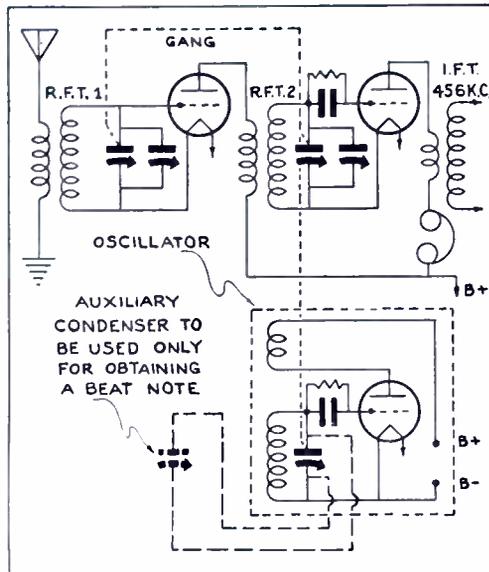are patient and if the apparatus is good, you will eventually hear something—provided, of course, that a fairly strong station is on the air. We may safely assume that eventually some station will be heard. Once a station is tuned in, hold him, and keep adjusting the r.f. and first detector trimmer until maximum signal strength is obtained.



The r.f. and first detector stages that we just adjusted comprise a standard, garden-variety two-stage receiver with which most experimenters are familiar. If the r.f. stage should oscillate, then the usual precautions should be taken: shield the tube, coil, and perhaps some of the wiring; reduce primary turns on the second r.f. coil; insert grid suppressors. One or all of these measures may have to be taken to insure stability. In any event, there should be no oscillation when the phones are connected in the plate circuit of the first detector. Of course, as an added precaution, be sure to remove all the other tubes in the set from their sockets.

## The Oscillator Circuit

With the signal still coming in, insert the oscillator tube in its socket and adjust its trimmer until the familiar beat squeal is heard. Now, here an important point arises. In the usual run of supers intended for s.w. reception, the i.f. is about 456 kc. To obtain this i.f., the oscillator inductance may be made smaller  
(Continued on page 41)

# The Eagle Short-Wave Receiver

A SIMPLE but very effective short-wave receiver that is finding great favor with both short-wave broadcast listeners and amateurs is Jerry Gross' "Eagle." This is a three-tube job using a 32 untuned r.f. amplifier, a 32 regenerative detector, a 33 pentode output tube. For power supply, dry cells are used exclusively. Two ordinary No. 6 dry cells (or better still, four, connected in series parallel) light the filaments. For plate supply 135 volts of "B" battery is needed; for grid bias, 22½ volts.


Since the antenna stage is untuned, only one plug-in coil is necessary for each wavelength range. Five standard Alden coils give the set a range of 10 to 350 meters. The complete coil details are given in the accompanying diagram.

Continuous band-spreading is provided by means of a 3-plate midget condenser C2, connected directly across the regular tuning condenser C1, which has a maximum capacity of .0001 mf. Rough tuning is done by means of C1, and then band-spreading over any section of the


coil range obtained by means of C2. Regeneration is controlled by means of another .0001 mf. variable condenser, C3.

Plate voltage for the r.f. tube is fed through the grid winding of the detector plug-in coil. The .004 mf. condenser connected between C2 and the bottom end of the coil closes the r.f. circuit.

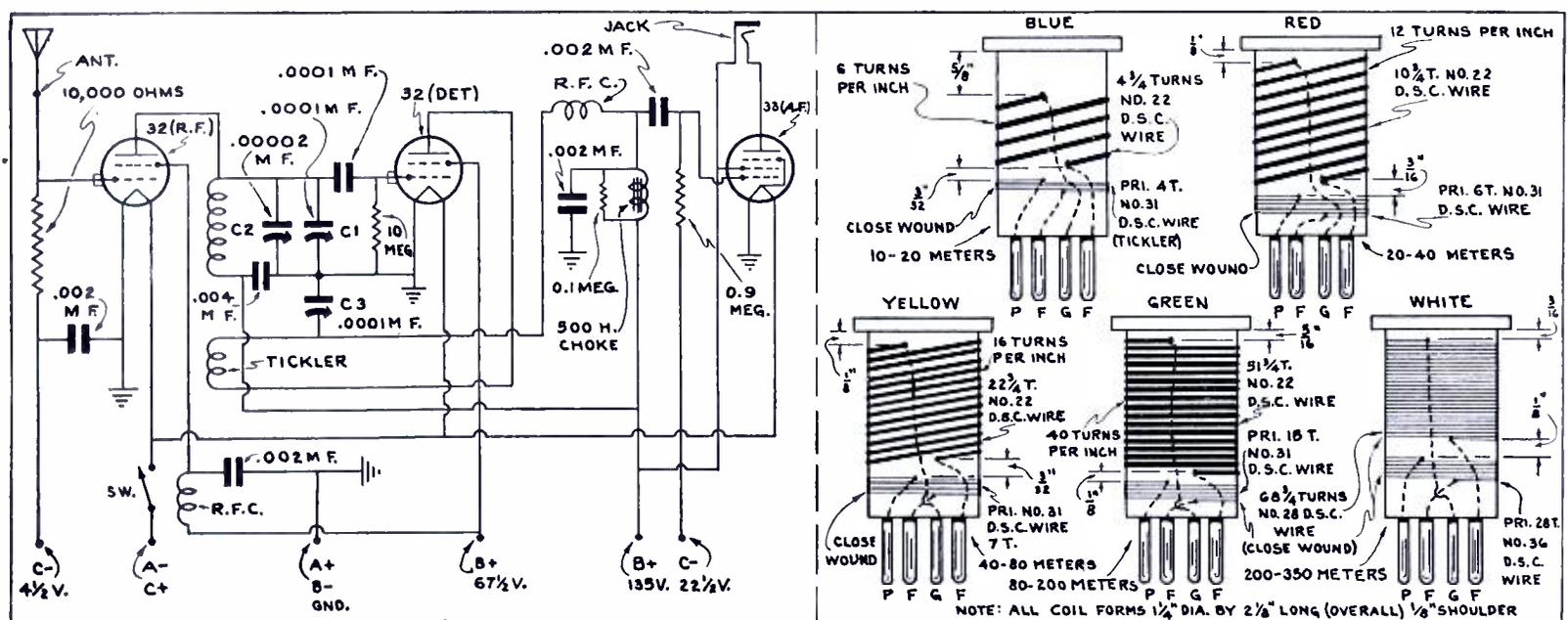With a normal antenna about 50 feet in length, this set provides excellent signals. Many stations can be heard quite well on a magnetic speaker.



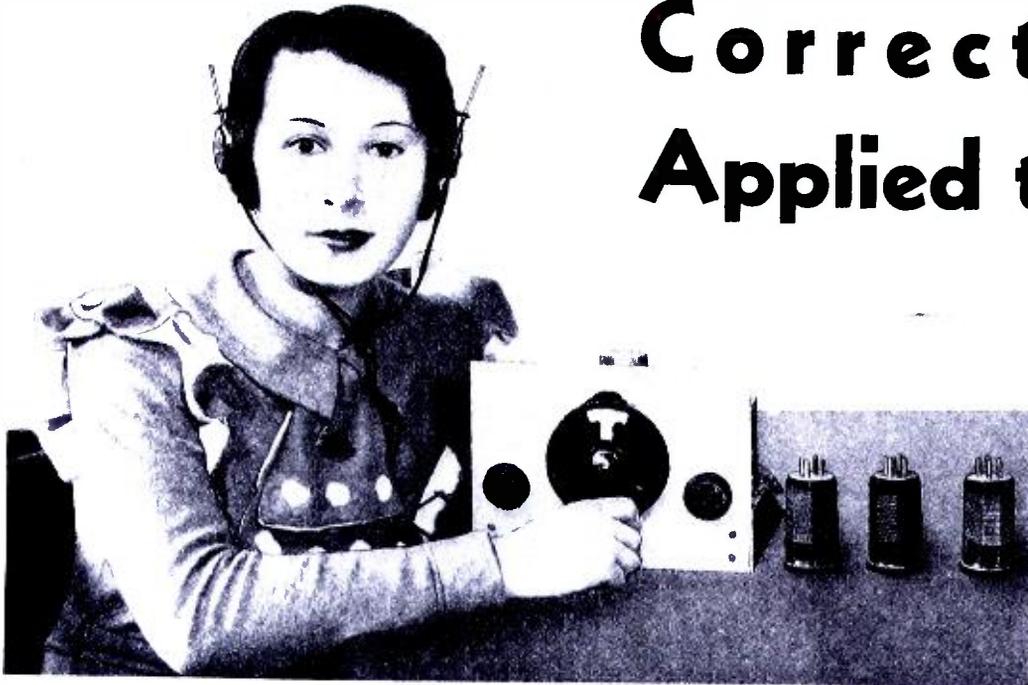SCHEMATIC CIRCUIT AND COIL DATA OF THE EAGLE SHORT-WAVE RECEIVER



THE RELATIVE SIZE OF THE SET AND COILS IS ILLUSTRATED HERE

# Correct Design Applied to a 2-Tube Short Wave Receiver

By J. A. Worcester, Jr.

**A**LTHOUGH it may appear to the casual reader that all two-tube short-wave receivers are practically identical as far as circuit diagrams are concerned, the fact remains that some work better than others, while some can scarcely be said to work at all. The explanation lies in the fact that in short-wave receiver design the circuit diagram means very little as far as determining whether a receiver will be a success or a failure. It is the attention to seemingly trivial details, such as smooth regeneration control, hum-free output, noiseless tuning, etc., that makes for successful operation. The method of obtaining the above characteristics in the receiver to be described will be discussed in the following paragraphs.

In order to obtain smooth regeneration control, it is necessary, first of all, to employ a low resistance tuning circuit. In this receiver, this is accomplished by employing a high-grade variable condenser in conjunction with a set of manufactured plug-in coils employing strip-wound, silver-plated secondaries. The strip construction is designed to reduce eddy current losses, while silver plating increases the surface conductivity.

## Regeneration

It has been pointed out on numerous occasions that as long as regeneration is used, the effective circuit resistance can be reduced to practically zero, and, hence, there is no object in reducing the actual circuit resistance to as low a value as possible. As a matter of fact, however, the value to which the effective circuit resistance can be reduced by regeneration is proportional to the initial circuit resistance. The reason for this is not difficult to comprehend. As the feedback is increased the signal strength builds up to a

certain critical value; any further increase in feedback will cause the circuit to break into oscillation. This can be explained by the fact that the feedback at any setting of the regeneration control is not constant, but varies slightly due to irregular electron emission, etc. When the feedback is increased to a point beyond the critical value, these uncontrollable variations in the feedback are sufficient to make the circuit resistance negative at some point, thus causing the production of sustained oscillations. Now, if the resistance of the tuned circuit is increased, say by the use of less efficient coils, it will be necessary to increase the feedback over the value previously required before the critical adjustment is obtained. Due to the increased feedback, which magnifies the effect of the uncontrollable feedback variations, the value to which the effective circuit resistance can be reduced before continuous oscillations are produced is diminished.

**SUMMARY:** *The essential points in good receiver design are as follows: (1) a low resistance tuning circuit, in order to secure uniform and smooth control of regeneration; (2) a high amplification-factor tube of the screen-grid type, which permits regeneration to be controlled by varying the screen-grid voltage; (3) impedance coupling in the detector plate circuit to permit of high gain because of high plate voltage; and (4) a heater-type output tube to reduce the hum level to a minimum.*

The above discussion, of course, only applies to the reception of modulated carriers. Any receiver that will work at all is capable of receiving continuous wave signals from any part of the globe. There are two reasons why this should be so. In the first place, the circuit resistance when using the beat method of reception is always negative, since the detector is in an oscillating condition. Secondly, the audio-frequency output from such a detector is directly proportional to the radio-frequency input, instead of being proportional to the square of the input as is the case with an ordinary detector. Consequently, the effectiveness of a receiver must be determined by its performance on modulated signals.

## 57 Used as Detector

For a detector, a type 57 tube is used and regeneration is controlled by varying the voltage applied to the screen grid. This combination was chosen for its sensitivity and freedom from reaction between the tuning and regeneration controls. Incidentally, the 57 tube is appreciably superior as a detector to the type 58, as can be readily proved by comparative tests on a weak signal.

It was found that with the above detector tube, the number of tickler turns on the plug-in coils was several times too great for obtaining satisfactory regeneration control. As a matter of fact, the circuit in most instances went into oscillation so violently that irregular oscillations were produced almost immediately; these manifest themselves by anything from a continuous squeal to an almost inaudible hiss, depending on the values of the grid condenser and leak employed.

This state of affairs cannot be regarded as faulty coil design, however, since in order to make the coils applicable to all types of tubes, it is

## List of Parts

- C1, C3—Hammarlund adjustable padding condensers, 10-70 mmf., type MICS-70.  
 C2—Cardwell 140 mmf. Midway variable condenser, type "C" plates, type 405C.  
 C4—Aerovox .0001 mf. molded mica condenser.  
 C5—Cornell .5 mf. tubular bypass condenser, type BB-2050.  
 C6—Solar .0005 mf. molded mica condenser, pigtail leads.  
 C7—Solar 25 mf., 25-volt dry electrolytic condenser.  
 L1, L2—One set Bruno short-wave plug-in coils, 15-228 meters.  
 L3—Hammarlund isolantite 8 mh. r.f. choke, type CH-8.  
 R1—Lynch 3 megohm grid leak.  
 R2—Acratest 50,000-ohm potentiometer.  
 R3—Acratest 250,000-ohm potentiometer.  
 R4—Electrad 400-ohm wire wound pigtail resistor.  
 T1—National impedance coupling unit, type S-101.  
 1—National type B vernier dial.

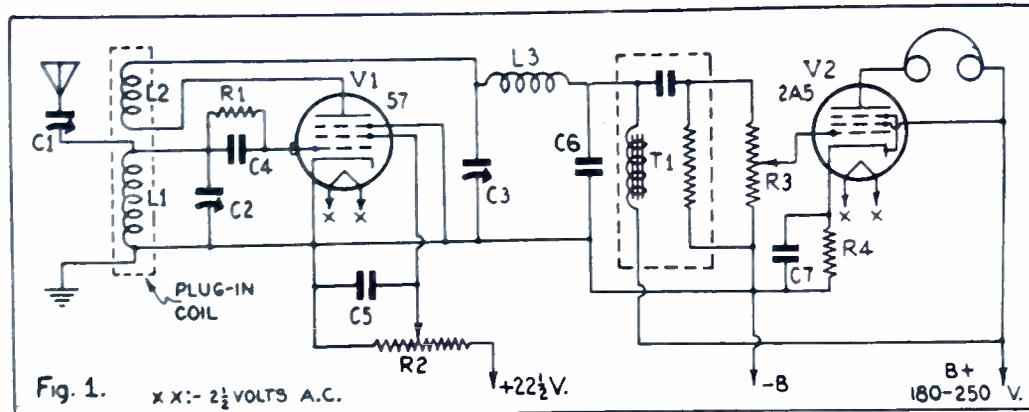


Fig. 1. x x: - 2½ VOLTS A.C.

SCHEMATIC CIRCUIT OF THE CORRECTLY DESIGNED SET

- 1—Eby 4-prong isolantite socket.  
 2—Alden 6-prong wafer sockets.  
 1—Alden 5-prong type 435 socket.  
 1—Alden type 95 Connectoral plug.  
 1—Eby twin binding post assembly.  
 1—Eby twin speaker jack.  
 3—feet Belden 5-conductor cable.

- 1—roll Belden hookup wire.  
 2—Aluminum panels 6½" x 9" x 1/16" and 8¾" x 8½" x 1/16".  
 1—Type 57 tube.  
 1—Type 2A5 tube.  
 1—Hammarlund aluminum tube shield, type TS-50.

necessary to put on sufficient tickler turns to provide satisfactory operation from the least efficient. As is well known, the older type triodes require several times more turns than the present tetrodes and pentodes.

Of course, an obvious solution to this difficulty would be to remove turns until satisfactory operation is obtained. However, it was not desired to mutilate the coils unless necessary; hence, the more convenient and satisfactory solution shown in the wiring diagram was adopted. A small padding condenser, C3, is used as a variable bypass in the detector plate circuit, and is so adjusted that the circuit just oscillates over the whole dial when the potentiometer control is about three-quarters advanced. For satisfactory operation the voltage across the potentiometer should not exceed 22½ volts.

### Impedance Coupling Unit

Another feature designed to improve the smoothness of regeneration control is the use of an impedance coupling unit, T1, instead of the usual resistance coupling in the detector plate circuit. This results in smoother regeneration by allowing a respectable voltage to be impressed on the detector plate, and, also, provides a substantial increase

in volume over that obtainable with resistance coupling.

### The Output Tube

In order to obtain a low hum level, a heater-cathode type output tube is employed, which practically eliminates hum from the audio stage. This tube is the 2A5 pentode, and is quite similar to the filament type 47 in operating characteristics. With this tube combination, it is entirely feasible to operate a small magnetic loudspeaker on most stations. If headphone reception only is desired, it is advisable to employ a plate voltage of 180 volts or less in order to reduce the plate current to a satisfactory value. The volume can be readily adjusted for satisfactory headphone reception by means of the 250,000 ohm potentiometer, R3.

To reduce the hum originating in the detector tube to a satisfactory level, it was found necessary to enclose the detector tube in an aluminum shield. It was also found advisable to locate the grid leak and condenser so that the tube shield isolated them as much as possible from the field of the impedance unit. The proper location of these units can be noted from the photographs.


In addition to these precautions, it is also necessary to have a well filtered power supply containing at least two chokes and plenty of capacity. For best results, this supply

should be located three feet or more from the set if at all possible.


Noiseless operation requires, first of all, a well built variable condenser designed especially for short-wave reception. Condensers with coiled brass pigtailed should be avoided. They invariably introduce all sorts of grating noises when used for reception below 50 meters. If pigtailed are used, be sure that they are of the non-inductive variety designed especially for short-wave use.
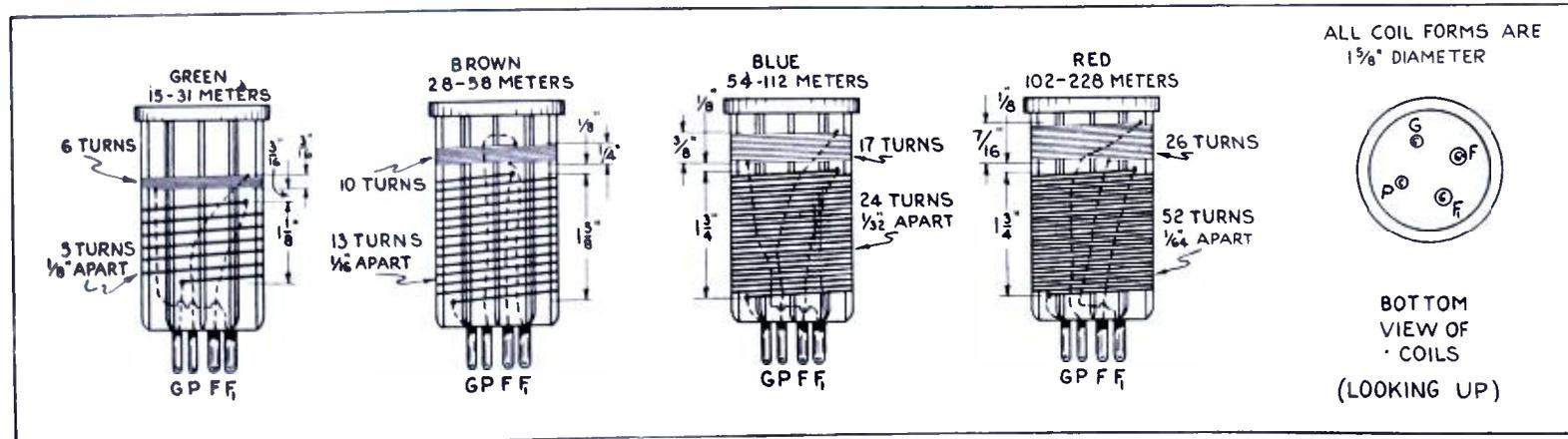
### Factors Affecting Noise

Other factors tending to produce smooth and noiseless tuning are a well designed, high ratio vernier dial and a composition type potentiometer for regeneration control. If a potentiometer having a grounded slider is used, it will be necessary to insulate the shaft from the panel. This can be done by cutting a hole in the panel sufficiently large to enable the threaded bushing of the potentiometer to clear the panel. By employing fibre washers between the nuts and panel and between the potentiometer casing and panel, it is possible to completely insulate the potentiometer. An alternative method would be to first mount the potentiometer on a bakelite strip which, in turn, is mounted to the panel. If this is done, it is, of course, necessary to drill a large enough hole to provide



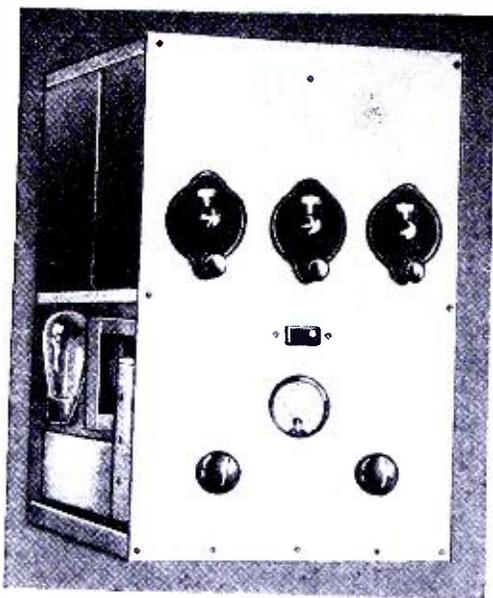COMPLETE COIL CONNECTIONS AND WINDING DATA FOR ALL BANDS



# Replacing Obsolete 5-Meter Modulated Oscillators


**SUMMARY:** Part II of a series of three articles by Mr. Kruse on the why and wherefore of replacing obsolete 5-meter modulated oscillators. The first part gave a general outline of the problem; this, the second, gives a rigid technical discussion of "why"; and the third, the last part, will describe an actual transmitter using the principles discussed.

The illustration to the left is a front view of a modern 5-meter transmitter built along the lines suggested by the author. It uses an oscillator, screen-grid buffer, and a modulated output amplifier.

In Part I of this paper the almost incredible frequency instability of the primitive modulated-oscillator type of five-meter voice transmitter, with which the amateur world has been struggling these past two years, was pointed out. It was suggested that such low-grade performance was hardly in line with the results demanded in other bands, and that there exists no reason why it should be tolerated—or permitted—at five meters, or why such equipment should be described.

Some experimental 1929 equipment was shown in order to emphasize the fact that for at least four years we have had both the apparatus and the information with which to make a decent 5-meter radiophone. It is, incidentally, interesting to note that since I somewhat forcibly called attention to these shortcomings some months ago, there have begun to appear really proper 5-meter rigs showing that inertia alone was causing the delay. Of course, others, too, have been objecting to modulated-oscillator operation; many months ago Messrs. James Millen and Dana Bacon built and described a magnetron transmitter of good frequency stability, and used it to demonstrate that with a stable signal, reception was better with something other than a "zero-selectivity" receiver such as are now current. Five-meter rigs under crystal control have been built by many experimenters, usually for c.w. work.

\* Consulting Engineer.

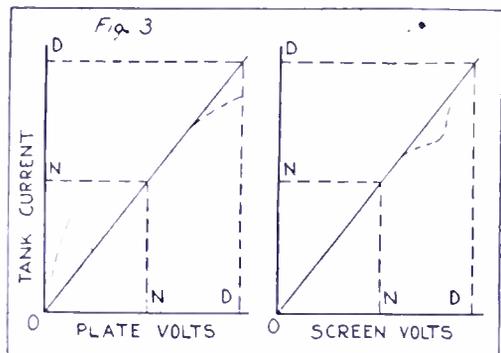

Showing why neither plate modulation (left) or screen modulation (right) can alone give good fidelity from a tetrode used as a modulatee, that is, a modulated r.f. amplifier.

By Robert S. Kruse, E. E.\*

Taking for granted that our transmitter will be of the oscillator-buffer-modulatee type, just as on any other waveband, let us see what else is necessary. As a first requirement toward something modern, let us forget all desires to put the transmitter into a spectacle case until we bring the circuit up to date. During this business of getting up to date, we shall be better off in a frame-and-panel rig, without any model-builder's problems to complicate our electrical work. As a concession to portability—if necessary

we shall make the frame of aluminum and aluminum alloys, and keep its size down to what is really necessary for a rig whose output is but a few watts. The photograph shows this plainly enough.

Now, what tubes? For the oscillator, the 10 is beautiful; but its 7.5-volt filament is an infernal nuisance. The 45 does not last too long as a 5-meter oscillator, nor do some makes of 2A3. A number of other tubes are inferior 5-meter oscillators, so that the problem gradually simmers down to a choice of the 71A, 46, or 12A, of which I prefer the last; my only regret is that the somewhat sturdier 12, with the 1/2-amp. filament, is no longer made.

For the buffer, we shall, of course, use a screen-grid tube, and for this small set it may as well be a receive-

ing tube. The 24, 51, 35, 57, and 58 all serve very decently, as do their 6-volt relatives. The life is not always long, but until we get that intermediate-size transmitting tetrode, we can well feed a few, cheap 24 tubes to the set in order to escape the nuisance of neutralization.

For the modulatee—that is, the tube-to-be-modulated—we may use several kinds of the more capable output tubes, including the 10, 46, and 59, but not the 50, 2A3, 45, or 53—either because they do not work well or because they are too hard to drive adequately.

For no reason whatever, it seems to have been assumed that a 5-meter transmitter must depend on plate modulation. While it is perfectly o.k. to modulate in this manner, we shall show several other schemes that are not new, but useful in these small sets.

Before getting into details, we suggest consideration of the following useful combinations:

12A oscillator, 24 buffer, 59 modulatee (or push-pull pair) with plate modulation from an amplifier using two stages of 56 and a p.p. output stage with 2A3 tubes. The catch in this arrangement is that the output transformer has to be specially made.

The same, with plate modulation effected by a stage of 58 and one of 47, or better, a 2A5. The coupling transformer is one intended to work out of 45's in p.p. into the grids of class B tubes. The center taps on both sides are ignored, and the primary as a whole put into the 2A5 plate circuit while the secondary is put into the B+ lead of the 59. This doesn't give 100 per cent modulation, it merely gives about 30 per cent more than you can secure by modulating an oscillator—and it isn't "all over the dial." The 59 is adjusted to draw 25 to 30 ma. All tubes are working with 250 volts on the plate in this and in the preceding arrangement.

The same as in the foregoing two paragraphs, but with grid modulation of the 59, which is now operated at 400 volts with a plate current of 20 ma., giving a carrier of about

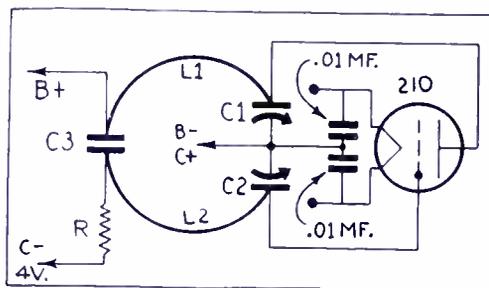


Fig. 4: The oscillator circuit repeated for those who came in after the picture started. It is the familiar Hoffman-Colpitts circuit with a very small inductance and high capacity. C1 and C2 are the sections of a 2-part Cardwell receiving condenser, with about .0005 mf. per section; C3 is about .01 mica; L1 and L2 are parts of the same single 2-inch turn of heavy wire; or 3-inch turn of heavy strap. R is 5,000 to 15,000 ohms.

4½ watts, the bias being —125 volts with enough r.f. grid input to produce the plate current just mentioned. One hundred percent modulation can now be produced if audio swings with peak values of 40 volts are fed to the grid, and *no* audio power is necessary. A 58 and a 56 stage suffice—believe it or not! Incidentally—you can modulate a p.p. output stage just as easily, getting 9 watts of carrier, which is ample for the present-day short-distance 5-meter work.

If more "hop" is desired than in the above combinations, use type 10 tubes in the output stage—how we need that new screen-grid tube! Run it with 700 volts on the plate with a bias of —135 volts, and feed in enough r.f. to produce a plate current of 15 ma., which will produce a carrier of some 6.3 watts. Or, use two tubes in p.p. and make it 13 watts. The same modulator rig suffices, a 58 and a 56. In all these grid-modulated rigs adjust the speech level to *just* draw grid current on loud sound peaks—I mean grid current in the modulatee.

If *that* isn't power enough, take a crack at a pair of 800 tubes in p.p. with a bias of 200 volts, plate voltage of 2000, and r.f. input such as to show a per-tube plate current of 20 ma., total 40 ma., carrier around 40 or 50 watts. This requires a buffer with more authority,—again we certainly need that successor-to-the-865—so we will reluctantly let neutralization creep in and use a second buffer consisting of a single 800 working at 1000 volts, with a grid leak of about 3000 ohms to supply its bias. The oscillator and first buffer might stay as they were, but we are now into 7.5-volt filaments anyway, and the whole thing has become costly, so one might as well jump off the dock and use a 10 oscillator and an 865 buffer.

### Tetrode Output Stages

Having thrown rocks at the idea of neutralizing, it seems inconsistent to describe triode output stages—and so it is. If you can afford it, by all means use 865 tubes (for a while) or Western Electric 282s.

When modulating them, we remember that—as this chap Kruse has said in nearly every radio magazine—mere plate modulation will not give us a linear modulation like the slanting straight line in the first (left) chart of Figure 3; but will produce the dynatron bump (dotted) of uncontrolled oscillation on the downswing, and the screen-droop (also dotted) on the upswing. Dynatron action is reputed not to take place at 5 meters. Maybe not, but hitch a tetrode up to a cathode-ray tube and try to use it at 5 meters with plate modulation. The dynatron bump appears—though I will not testify as to its frequency. The fidelity is awful.

On the other hand, if we use screen-modulation alone, we have the effect shown in the right-hand

chart of Figure 3. Up to about 70 percent modulation things are good enough, then the curve goes haywire, as they say at the University of Borneo. Of course, 70 percent is still more than twice as much modulation as we can get on the present crop of modulated oscillator dingbats—but let's get into step with the other bands!

To do this, we modulate both the screen and the plate or else we screen-modulate in two stages.

(Chorus from gallery—"Aw, you said that before." All right—why lot do it? I'll say no more and let you read it up for yourself—and tell you where to find the dope if you don't know.)


Now, our triode stages are of two distinct sorts—the plate-modulated ones, which require some neutralization, and our grid-modulated ones which don't require it. This sounds silly, but the explanation is that the grid-modulated ones require very little r.f. input, hence are very loosely coupled to the buffer-tanks. This leaves the grids without much in the way of a reactance across which feedback voltages can build up; hence the stability is really quite good, especially if adequate antenna coupling is used. Neutralization, if used at all, is uncritical.

Now, then, we can start doing something definite.


Since there are to be three tubes in the r.f. system, we shall place a transverse wall half way back, putting the oscillator and buffer ahead of it—just behind the front panel—and leaving the entire back compartment for the output stage, or modulatee. Since this output stage will sooner or later be tried in push-pull, we may as well begin by keeping both sides of the tuning condenser "off-ground." It is, accordingly, mounted on a small bakelite sub-panel, and turned by a ¼ inch bakelite shaft extending forward through the division wall and the front panel to one of National's "velvet" dials—the central one on the panel. This location not only misses both early stages nicely, but allows symmetrical p.p. stages to occupy the back compartment.

In the forward compartment we have the oscillator, which uses the circuit shown once more in Figure 4, and the buffer, which is nothing more than a straightforward 24, r.f. amplifier stage. Push-pull isn't ordinarily needed here, hence the tuning condenser is "off-ground" by only a small amount, which is to say we insulate it for d.c., but ground it via a bypass condenser, generally a .01 mf. mica condenser. This permits us to use series feed and dodge one r.f. choke. At five meters this means something, and with care a voltage gain of four or better can be obtained. This isn't very good compared to the 90 we easily achieve in the i.f. stages of a broadcast receiver, or the 35 that we find in the r.f. stages of the same receiver, or


(Continued on page 44)

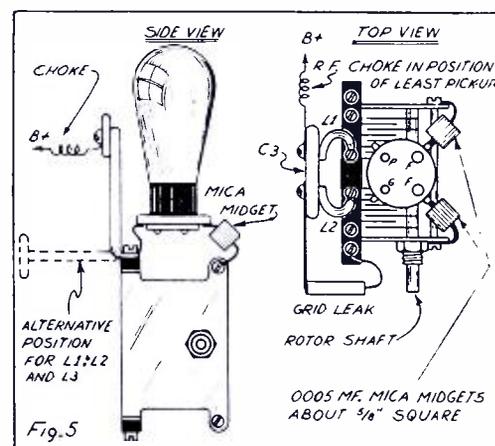

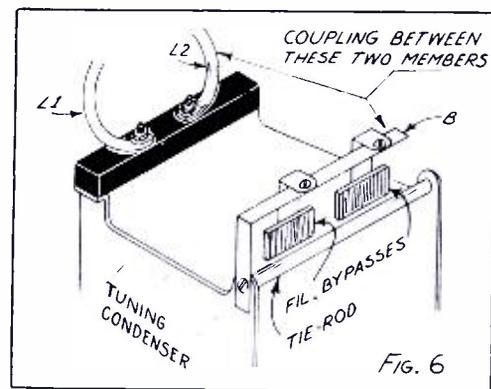
An oscillator construction. Compare with Fig. 2 in Part I of this paper.



A bad oscillator, see text.

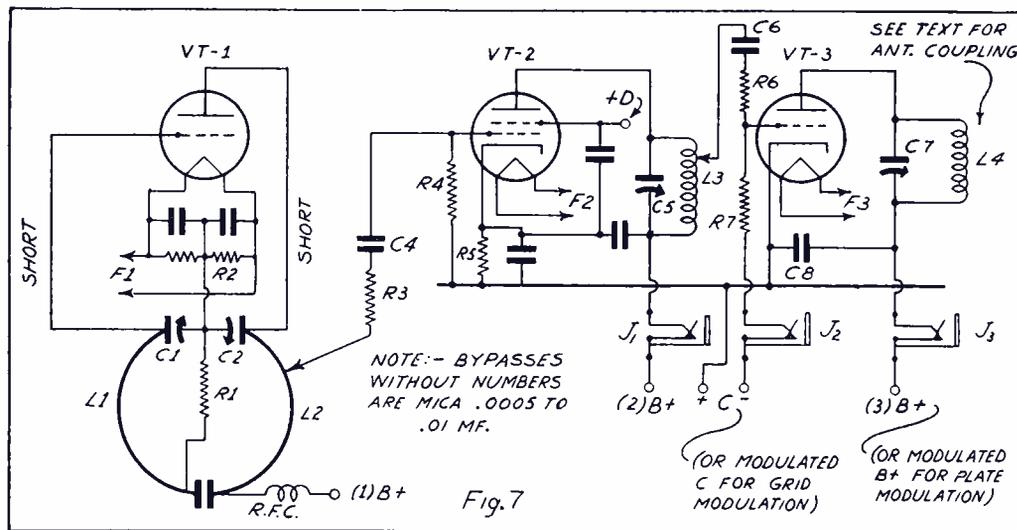

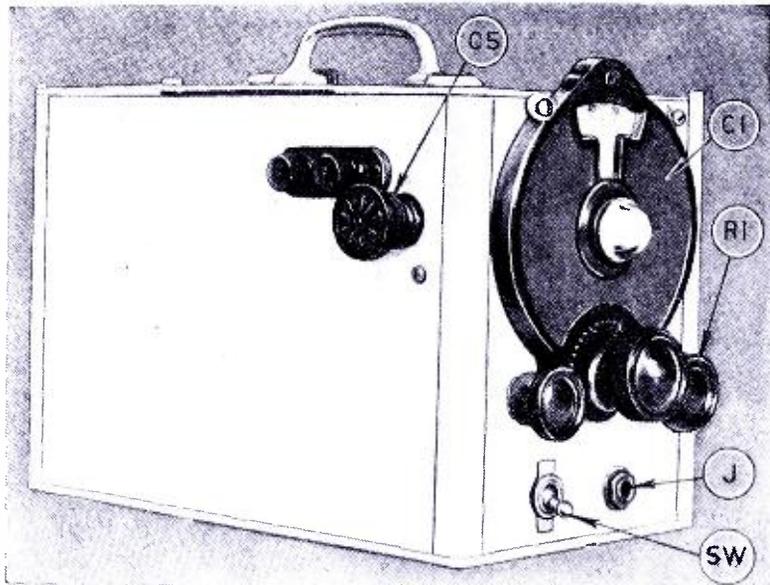Type-diagram, with constants temporarily omitted to concentrate attention on the entirely normal nature of the circuit. We have known this for many years; why use obsolete modulated oscillators?



THE COMPLETE PORTABLE RECEIVER

# A Portable Set That Is Portable

**SUMMARY:** Here is a real portable receiver that does not require six men to carry it around. Here is a real portable short-wave receiver that may be used in the home as well as in the field with equal efficiency.

There is no doubt about the fact that portable short-wave receivers have appeared before; but we believe that the results obtained with the one described here, considering its extreme portability, are such as to bring it into first place. We take pleasure in presenting this description.

By Frank Lester\*

**M**OST portable radio receivers are about as portable as baby grand pianos with handles attached to them. Although it is a very simple matter to make up a compact tuner-amplifier, the weight of the required batteries or other power equipment invariably is enough to discourage even the strongest and most rabid radio bug. All the enjoyment that the portable receiver is supposed to give disappears quickly after the perspiring owner has massaged his aching shoulder muscles for the twentieth time!

Of course, if you have an automobile, you really do not need a set belonging in the portable class, as you can use the car's storage battery for filament supply, and even carry a small dynamotor or vibrator type B power unit for plate supply.

Realizing this situation, the writer undertook the construction of a portable receiver so that he could have something to listen with when he

\*In charge of Short Wave Dept., Wholesale Radio Service Co., Inc.

visited the World's Fair in Chicago this summer. Never having been farther west than the Atlantic seaboard, he wanted to get an idea of short-wave receiving conditions in the Middle West. As he was traveling by train, compactness, lightness, and true portability were essential requirements. That he succeeded pretty well is indicated by the fact that his two-lunger survived 2000 miles of train, taxi, and elevated travel, and that he is more enthusiastic about short-wave radio now than ever before.

## Batteries Self-Contained

It was decided in advance that all A and B batteries must be built into the same container as the receiver itself. There were to be no outside accessories, except, of course, a pair of very light earphones and an aerial of thin, flexible wire. The phones were readily stowed away in a traveling bag, while the aerial wire, when not in use, was simply stuffed into the set cabinet itself.

The receiver proper is a straightforward, trustworthy two-tube outfit, comprising a regenerative detector and one stage of transformer-coupled audio amplification. The tubes used were 30's. For filament supply, a large size 4½ volt C battery was used. This is the size measuring 4" wide, 1¼" thick, and 3" high. For plate supply, a single 45-volt B battery is employed. This measures 4¼" wide, 2½" thick, and 6" high. The case for the set is a standard aluminum shield can 9" long, 5" wide, and 6½" high. This can has four corner posts, and the sides, bottom, and top are quickly removable.

On one of the ends of can are mounted the tuning condenser C1, the regeneration controls C2 and R1, the filament switch SW, and the earphone jack J. As the can is grounded and forms the B—A+ side

of the circuit, the jack is insulated from the aluminum by means of two fibre washers. The hole for the jack stud is drilled out extra large to provide comfortable clearance.


The vernier dial shown in the illustrations sticks above the top of the can about half an inch. This was used only because a smaller dial was not available at the time the set was taken to Chicago. A three-inch dial was used originally, but this was broken by one of the writer's friends during a preliminary trial.

On the bottom of the shield can are mounted two tube sockets; an audio transformer, T1; a bypass condenser, C3; and a small r.f. choke. These are compactly arranged to cover exactly half of the base area. Another tube socket, to accommodate a plug-in coil, is mounted between the two tube sockets 3" above the base. It is supported by two ¼" brass rods, which are drilled and tapped at each end for 6/32 screws.

On the left side of the cabinet are mounted a two-plate variable midget condenser, C5, which is the antenna-



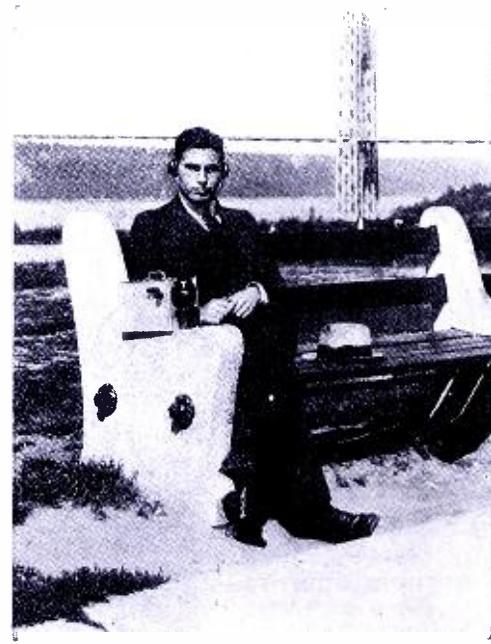
THE RECEIVER IN ACTION  
Taken in Central Park, New York, a notoriously bad location.



IN THE WIDE OPEN SPACES!  
On Riverside Drive, with the George Washington Bridge in the background.

- C1—50 mf. variable tuning condenser (National No. ES-50).
- C2—50 mmf. midget variable condenser (Cardwell Balancet was used for size).
- C3—1 mf. bypass condenser (Trutest).
- C4—.0001 mf. mica grid condenser (Solar).
- C5—two-plate midget variable condenser, made by cutting down five- or seven-plate midget (Trutest).
- C6—.001 mf. mica condenser (Solar).
- R1—50,000 ohm potentiometer regeneration control (CRL).
- R2—5 megohm grid leak (Trutest).
- R3—8 ohms fixed resistor (Trutest).
- R4—1 megohm grid leak (Trutest).
- T1—3½ to 1 ratio uncased audio transformer (Trutest).
- SW—Single pole snap switch (Trutest).
- J—Single open circuit earphone jack (Trutest).

- 3—four-prong bakelite base tube sockets, one for plug-in coil L, the other two for tubes V1 and V2 (Na-Ald).
- V1, V2—Type 30 tubes.
- 1—double binding post strip marked ANT. and GND. (Eby).
- 1—Vernier dial, National midget type B.
- 1—aluminum shield can 9" x 5" x 6¼".
- L—short-wave plug-in coils, any standard four-prong, two-winding coils are satisfactory, such as Octo or Trutest, etc., or home-wound according to directions given.
- 1—pair of light earphone with plug attached.
- 1—4½-volt C battery used for filament supply (Burgess No. 2370).
- 1—45-volt B battery (Burgess No. 5308).
- Incidental hardware such as bakelite strip for mounting of C5, brass rods for mounting of coil socket, insulated push-back wire, etc.

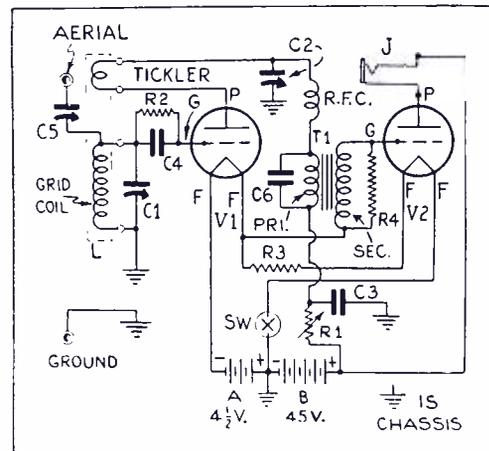


SCHEMATIC CIRCUIT OF THE PORTABLE

coupling condenser, and a double binding post strip. C5 is actually mounted on a piece of bakelite measuring 1¼" x 2". A large hole is drilled in the aluminum to clear the mounting stud. The bakelite piece is then fastened by one of the same screws that holds the binding post strip and by one extra 6/32 screw. This bakelite mounting is necessary, of course, to insulate the condenser from the grounded can. The two-plate condenser was made by cutting down an ordinary five-plate midget.
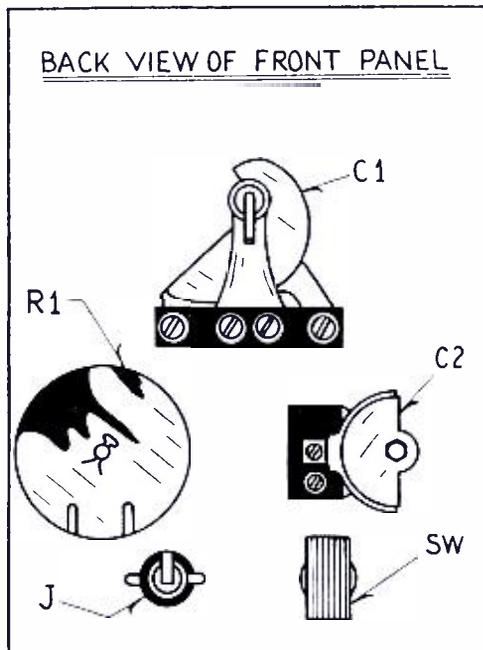
#### The Circuit

The hookup is very simple and the wiring should not take more than 30 or 40 minutes. Note carefully that the tube filaments are wired in series and are connected directly across the A battery, with an 8 ohm fixed resistor, R3, also in series. The filament battery has given remarkably good service. The same unit was used continually for 3½ weeks during the very hottest part of the summer, and lasted another 2½ weeks when the portable receiver was later used as a station monitor. The drain on the B battery is, of course, very light, and a life of 9 to 12 months is expected.



PLACEMENT OF PARTS ON FRONT PANEL



The cover of the shield can is fitted with a 10c door-handle and simply screws in place. To change coils, it is necessary to unscrew the cover. This sounds like a nuisance, but actually the 40-meter coil is used most of the time. If coil-changing is contemplated, the cover is simply

left off and not replaced until another move is made.



In Chicago this receiver brought in amateurs from every district in United States and Canada and numerous foreign amateurs as well, with nothing more than 10 feet of flexible Christmas-tree wire for an aerial and a steam radiator for the ground. The wire was simply dropped from a hotel window. On the 49-meter broadcast channel, short-wave broadcast stations in Central America, England, and Germany were heard. Of course the volume with a two-tube set is not very great, but the absolute absence of background noise of any kind makes reception of even weak signals very easy.
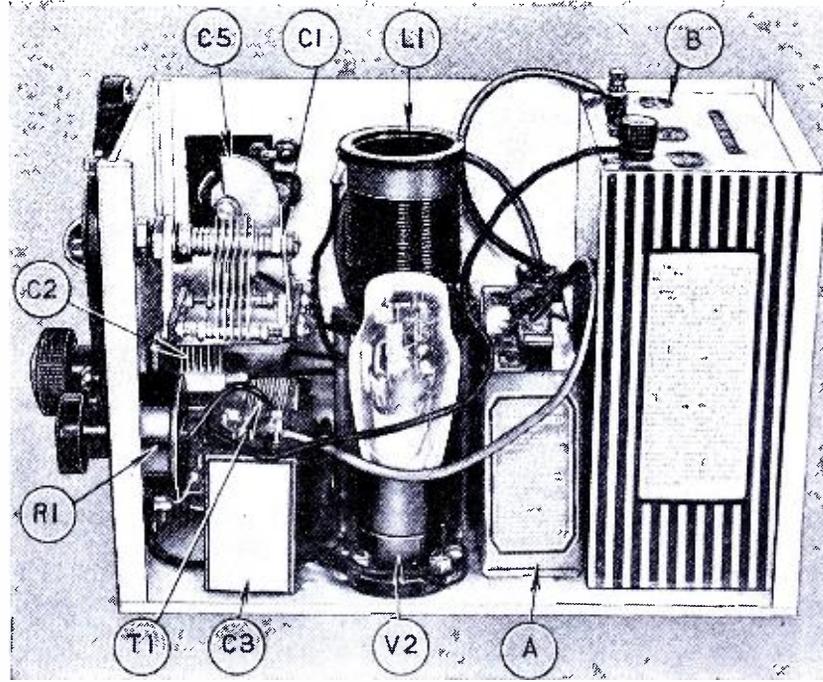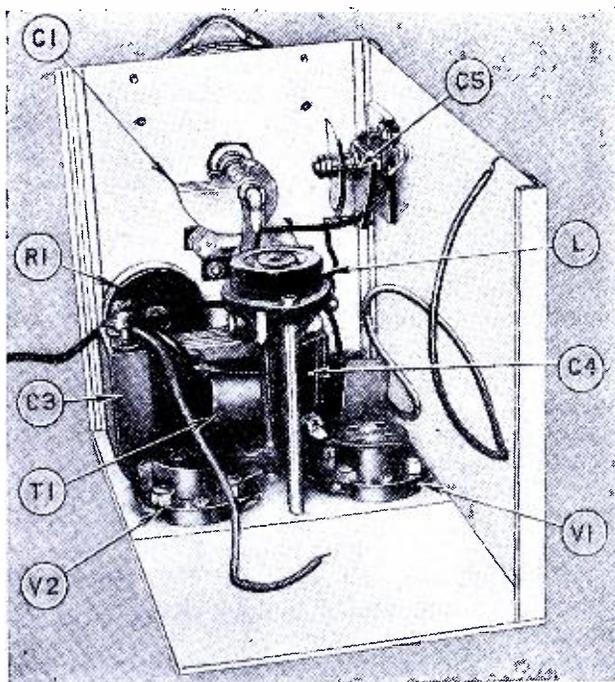
#### May Be Used as Monitor

Since it is completely self-contained and also pretty thoroughly shielded, this little receiver makes a very simple and reliable monitor for an amateur transmitting station. It may be calibrated quite easily by using it first as a regular receiver and spotting the positions of marker stations of known frequency on any particular frequency band. In this connection, it is important to take



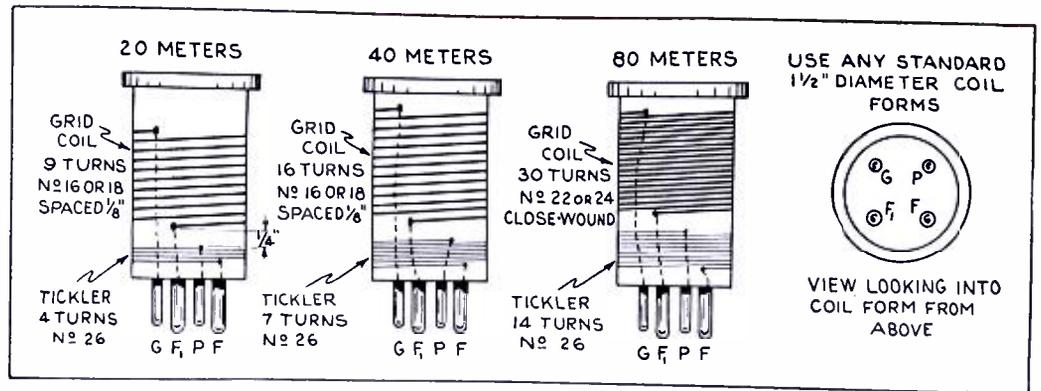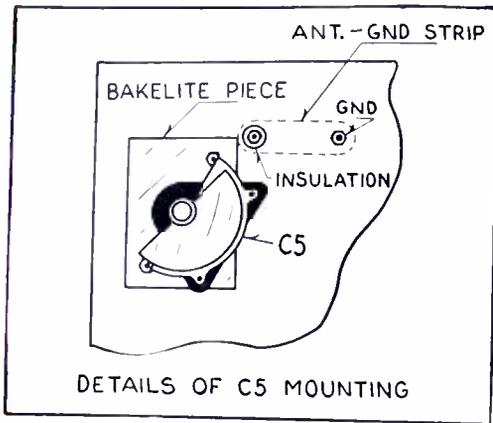TWO INSIDE VIEWS OF THE PORTABLE RECEIVER MARKED FOR CONVENIENCE




CONSTRUCTION DETAILS OF THE COILS USED IN THE PORTABLE RECEIVER

into account the detuning effect of the antenna. To insure accuracy for monitoring purposes, calibrate the dial with an extremely short antenna—say, three or five feet in length. Fix the antenna condenser C5 in one spot and leave it there, and then use this entire setup for monitoring. If a three- or five-foot antenna picks up too strong a signal from the transmitter being monitored, cut it down a foot at a time. Even with a wire only a foot or so long, good recognizable signals can be picked up from amateur and commercial stations for calibration purposes.
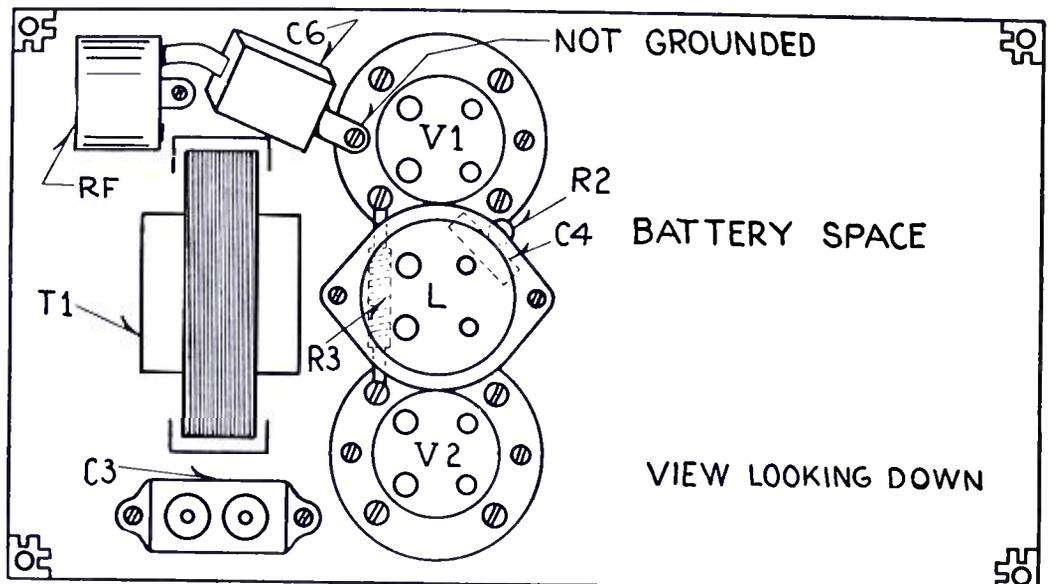
#### Editor's Note

The editors of *SHORT WAVE RADIO* had an opportunity to play with Mr. Lester's receiver for several days. It was carried by hand in the New York subway during rush hours and was tried in a number of different locations, some noticeably good and some noticeably bad. One of the good spots, for instance, was upper Riverside Drive, just south of the George Washington Bridge across the Hudson River, which is shown in one of the accompanying illustrations. A ten-foot length of wire hung between a bench and a small tree brought in hundreds of ama-



TOP VIEW, LOOKING DOWN, SHOWING PARTS PLACEMENT

teurs on the 40-meter band and a number of domestic short-wave broadcasting stations.

In Central Park, which is one of the poorest radio locations in New York, the results were not as good, but were still very interesting. Because it could be gotten into operation in less than a minute, this little outfit provided some extremely inter-

esting experimentation. The shielding effects of large buildings were readily noticeable, as signals could be received quite well from one direction, but not another. By walking around with the set in one hand, the phones clamped on and the aerial trailing along on the ground, it was possible to determine the limits of the dead spot areas quite accurately.

## A Codeless Amateur License? No!

**A**LTHOUGH we doubt if anyone in Government circles is giving the matter any serious thought, there seems to be a lot of noise at the present time about creating a special class of amateur license that will not involve a code test. Considering the numerous and unmatched privileges already enjoyed by the American amateur, it seems to us that any demands for a license class of this kind are ridiculous. Many honest amateurs admit that even the present test is too easy, and is bringing many irresponsible persons on the air. Of course, everyone has to begin some time, so we must forgive the beginner his rotten fist or his hoarse modulation, as long as he stays within band, uses d.c. for plate supply and otherwise conforms to the spirit, as well as the letter, of the Federal Radio Commission regulations.

When you stop to consider that the American amateur is not even required to pay a cent in the way of license fees, that he is permitted to operate absolutely unhampered, and that the Army and the Navy defend him at international conferences while the highly military governments of other nations try to wipe him off the map, we think it is time to stop biting the hand that feeds us, so to speak.

The recent federal economy wave was responsible for a serious reduction in the technical administrative staff of the F.R.C. You can just about imagine the mess that would be created by a lot of unchecked so-called "amateurs" who are willing to jeopardize their own freedom by their unwillingness to learn the code, which, after all, is the real language of radio.

Why do some people consider the


code a stumbling-block? It is really very easy to learn, as 10-year old children and 75-year old patriarchs have discovered. Besides, a knowledge of the code greatly increases the enjoyment that you can obtain from a short-wave receiver, even if you have no intention of applying for an amateur license.

To many people not familiar with the code, the host of mysterious dots and dashes that sometimes interrupts music are things which should be eliminated by law; but to those with even a slight knowledge of the code, these mysterious interruptions are highly interesting.

Airplane, coastal and naval stations, all transmitting information that really makes sense, may easily provide hours and hours of entertainment, especially when you want to get away from the beaten path.

—R. H.

# Diagram of New Lyric All-Wave Receiver

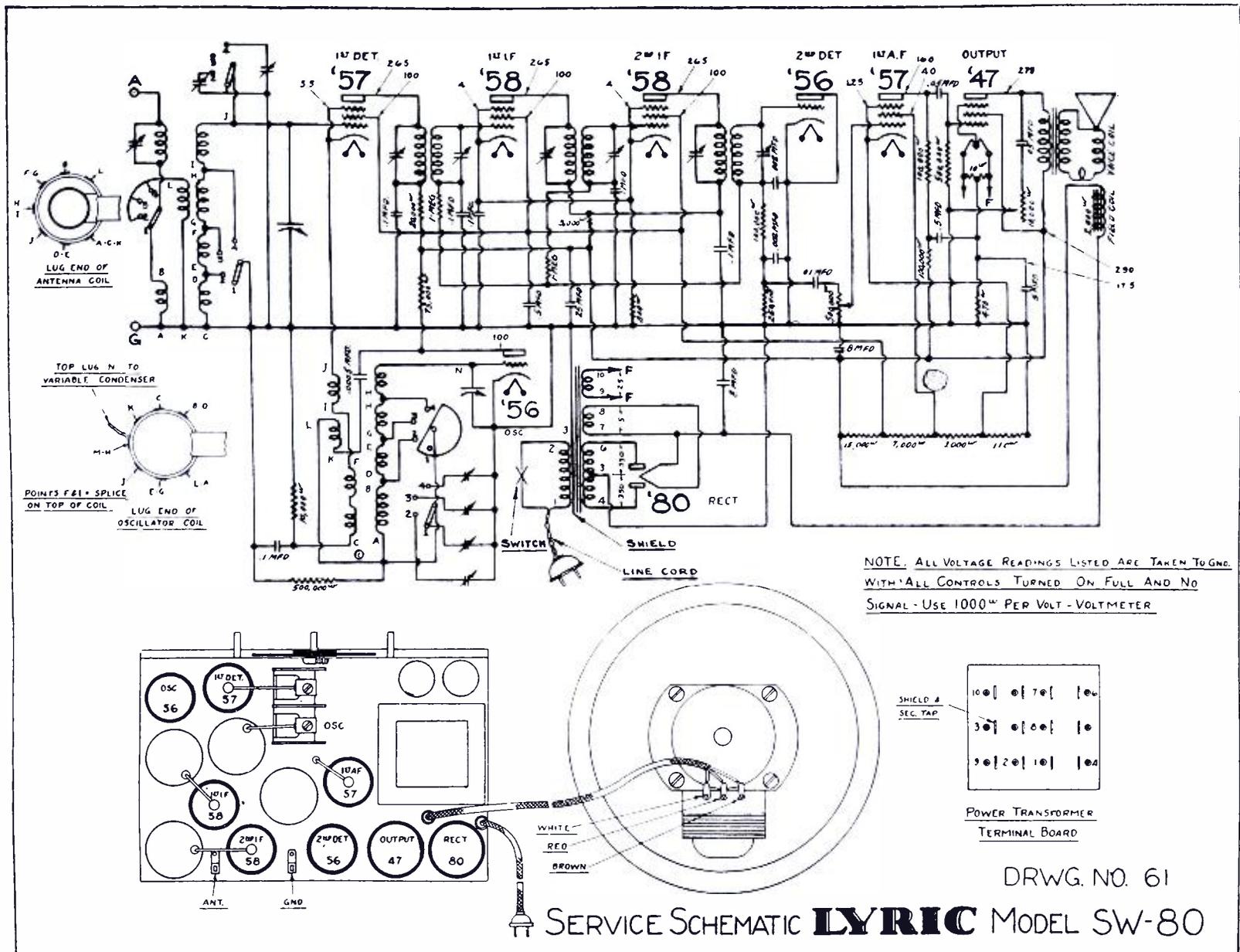

**T**HE growing interest in short-wave reception is reflected in the appearance of a number of excellent all-wave receivers, produced by firms that heretofore have specialized exclusively in straight broadcast sets. One of the latest receivers of this type is the Lyric model SW88, which uses a chassis designated as SW80. A complete schematic diagram and

service sheet, with the values of all parts indicated, appears herewith. This was furnished through the courtesy of E. Wesselman, of the Engineering Department of the Rudolph Wurlitzer Mfg. Company, the manufacturers.

This receiver is designed for the reception of broadcast signals on all frequencies between 550 kilo-

cycles and 22 megacycles, or between 546 and 13.64 meters. The selection of any desired band is made by means of a four-position change-over switch. The intermediate frequency is 485 kc. No provision is made for the reception of continuous wave (telegraph) signals, as the set is intended primarily for use on broadcast stations.

## Book Review—"The Inductance Authority"

**THE INDUCTANCE AUTHORITY** by Edward M. Shiepe, B.S., M.E.E., published by Herman Bernard, New York, N. Y., 9 by 12 inches, 50 pages, practically all illustrations, leatherette cover. Price, \$2.00.

Probably the greatest factor that tends to confuse the mind of the average set constructor is that of coil information. The question, "How many turns shall I wind on that coil?" is asked by the same experimenters over and over again, for it seems that every set requires just a little different coil design than the preceding one. This holds true regardless of whether coils

are used for the short waves or for the broadcast band.


The author of this book has made, in the opinion of your reviewer, a very excellent and practical contribution to the field of radio. One of the most significant factors is that of the 50 pages in the book, over 40 are completely filled with charts; about 10 pages are devoted to explanations of the use of the charts.

Although the information available from these is valid for close-wound coils, the author, nevertheless, gives good data on how to calculate space-wound coils specially suitable for short-wave work.

Another valuable feature of the book is the numerous numerical examples

which serve to illustrate the principles set forth. These examples not only aid in interpreting the curves, but more than that, they represent actual figures usually found in practice. Complete coil winding data for various diameter forms and for frequencies between 160 and 20,000 kilocycles (1875 to 15 meters) are included. Data are also given for various sizes of wire between No. 14 and No. 32 for enameled, single cotton covered, double silk covered, single silk covered, and double cotton covered insulation.

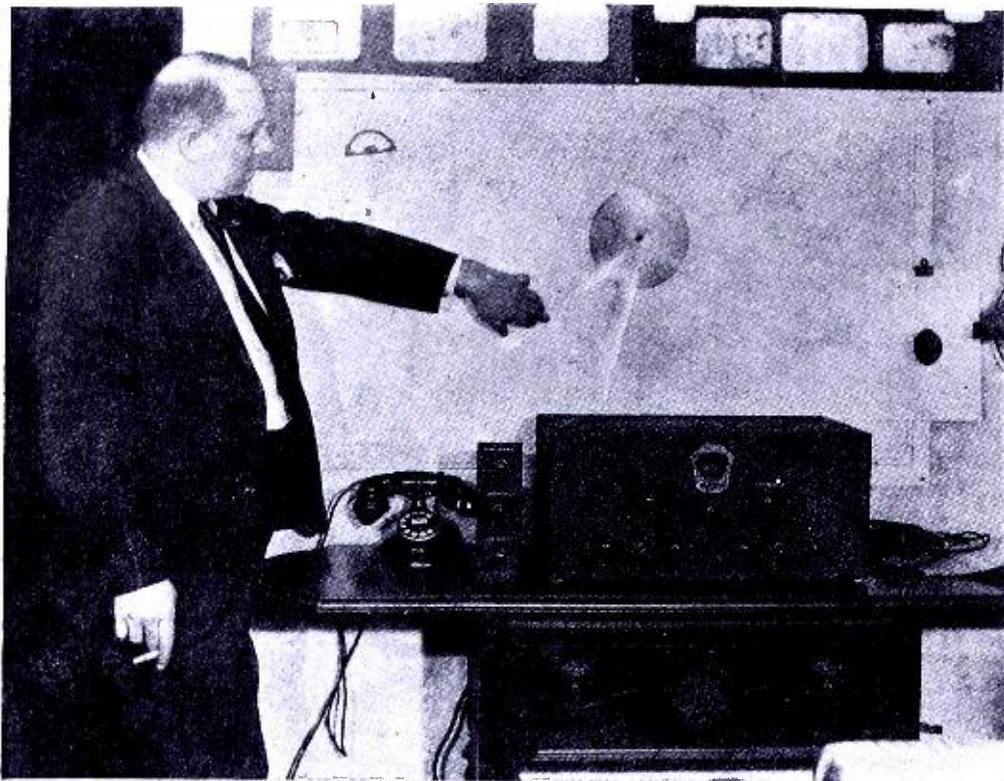This book should prove an excellent standby for those who find the need for quickly determining the size of inductance and number of turns for radio work. L. M.



The Captain with his charts, distance finders, and a new Postal "International" receiver.

# Capt. Hall's Department on Foreign Stations

## Day Waves and Night Waves

**W**HEN reading magazines which devote space to the short waves, I have seen many articles about tuning receivers. The chief point that interests me and all up-to-date short-wave fans is the writers' beliefs that for good tuning results it is rather a waste of time to fish on the low wavelengths after dark. By the "low wavelengths" we must naturally take into consideration the nineteen-meter band, as that band is a very interesting one for all fans.

Now to go back to 1928, my own first short-wave tuning days. Everything that was told me about "don'ts" and "do's" in tuning I listened to, thought over, and then tried out for myself. Fellow fans always used to tell me that my coils that took in the nineteen-meter band were known as the "daylight coils" and that the other extreme end, the forty-nine-meter band coils, were known as the "night time" coils. Not sure that these advisers really knew what they were talking about, and with nothing else to do, I fished many a time with "daylight" coils in the night time and vice versa. The results were startling even to my friends, who, not wanting to be proven wrong by a beginner in the game, and still holding to their antiquated views about night and day wavelengths, used to pass over the subject of my results with, "Well, that was just an accident!"

To the short-wave fans who believe in these ideas, the report that Pontoise, France, was going to broadcast on 25.60 meters until midnight came as a decided shock. They really seemed to resent the idea of any station daring to attempt to operate on a "daytime" wavelength in the night time. Days passed and these fans were just beginning to rejoice in the idea that France could

### This Department

*In this department, which is conducted exclusively by Capt. Hall, the latest "meat" on foreign stations is given. The photographs which appear here have been collected by the Captain and are reproduced to illustrate what can be received from foreign stations aside from programs.*

*The Captain wants you listeners to write to him about your own results. If any of your comments are printed, you get full credit. Write your letters to the editors, attention of Captain Hall. They will be forwarded immediately.*

not be heard here because of the wave they were using, when the true reason was that Pontoise had not started to put across their programs. One night over came the transmissions from Pontoise, loud and clear, with tremendous volume—and on 25.60 meters!

The foundation under my short-wave friends' feet was weakening. Their pet theory was nearly overthrown, but not quite. Then, like a bombshell exploding at their feet, we heard that Daventry was starting to send test programs on 19.82 meters *at night*. This was too much for these loyal "day" and "night" band believers. No one need ask any tuner how Daventry came over on that wave! They were clearer and far more satisfactory than when they were among the "forty niners."

Germany has since followed suit, and shoots programs over to her listeners here in the states on 25.51 meters until after seven o'clock, and then jumps to 31.38 meters, where they continue to transmit enjoyable programs.

### More on "Veries"

Swapping stories on verifications is a topic of conversation among fan friends, and when three or four ardent tuners get together, much information and misinformation fills the air.

When fellow short-wave fans view my collection of verifications, which I have gathered from thirty countries, they invariably ask the following questions: "Just how do you know what language to write in?" Secondly: "How do you know what they are talking about when they answer you?" And thirdly: "What is the secret of your success in getting answers from these foreign stations?"

In my opinion, answering the last question is the most important and probably by far the one that will benefit other prospective collectors of "veries." Now to detour slightly from the subject, I know that these few remarks will be found to have bearing on the answer. In my mail bag there are always letters from fans asking questions, giving station data, etc. Sometimes I have real difficulty reading these otherwise interesting letters, simply because the writing is so poor. Now, I sometimes think of how difficult it is for the officials in charge of foreign stations to read these illegible letters. How can a director of a station verify a program when he cannot even understand what has been written to him? To put this paragraph into one sentence: typewritten letters are the best, almost a necessity when writing for verifications. If you haven't a typewriter yourself, find a fellow fan or a friendly neighbor with one, who will type your letter.

Now we will go back to the first question. Although I recognize many languages when I hear them on the air, which probably benefits

me by helping me to identify stations I have not heard before, I cannot write in these foreign languages, being limited in that respect to our own English. Being so "language bound," it is an impossibility for me to write to these foreign stations in their own language. Very few fans are linguists, and, therefore, they are in exactly the same predicament as I am in. I always write in English, and ninety percent of the answers are written in the same language.

The answer to the second question is longer and more complicated, but very interesting. In 1928 I received my first short-wave "veri." That was from VK2ME, which acknowledged on a card. This naturally was written in English, as we all know that it is the language used in Australia. From 1928 to 1931 my interest in the short waves lagged, due to lack of capable receivers and the absence of information on the short-wave stations as to their schedule of time on the air, etc.

In the later part of 1931, I reentered this game and started collecting veries on a large scale. The next one was from F3ICD, Saigon, Indo-China. There was quite some difficulty attached to getting a response from this distant country. I had been receiving this station daily, although the program I was hearing was only of fifteen minutes duration, due to the fact that the scheduled time on the air of W2XE, New York, was such that they came on the air and completely blanketed Saigon. After hearing several programs from this Asiatic station, I decided to take a chance and write them and see if and when they would answer my communication. I addressed the letter to "Radio Station F3ICD, Saigon, French, Indo-China." I waited what seemed an endless time, and then, receiving no answer, I wrote again, enclosing another program. Still no answer. Again I wrote and enclosed still another program.

#### A Real "Veri"

After three months I received a letter written in perfect English, from "L'Ingenieur chef de Station," in which he acknowledged receipt of my letter and informed me that enclosed I would find several articles: (1) A notice of our broadcasting station; (2) a copy of our weekly publication "Radio Saigon," subscription five dollars in Indo-China dollars; (3) a subscription form for a Listeners Assistance to the development and the improvement of our transmissions. The yearly subscription is \$25 (Indo-China dollars, also). There followed a paragraph or two on whom to make checks payable to and the ordinary forms of sending a letter followed. Within a day or two I received a heavy magazine from the station with pictures of the interior of the station and letters or testimonials from other listeners; also reception results of individual tuners from one




A SECTION OF THE WALL OF DX CARDS IN THE CAPTAIN'S DEN

corner of the globe to the other. This book was very interesting and still is my star veri.

While waiting for Saigon to answer I had been sending out letters to foreign stations which included Germany, England, France, etc. Germany did send and still sends a stereotyped letter to all listeners who send in reports of reception. The "D" stations are very thankful for these reports. Letters are in German and very long. They include no scheduled time on the air, but the wavelength and call letters are mentioned, and also, details on power, etc.

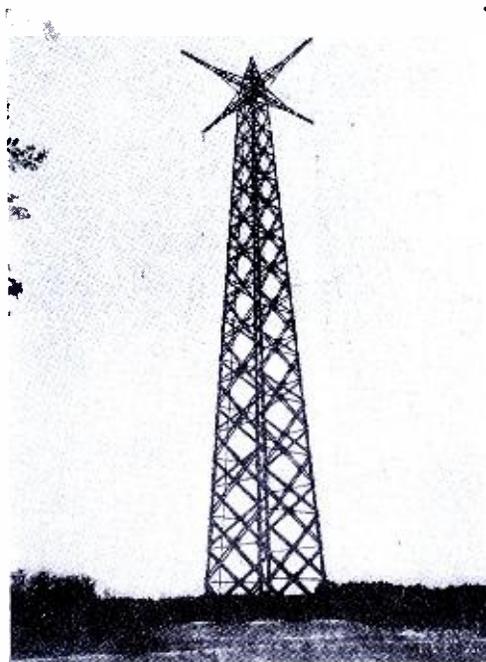France sends a card written in French with blank spaces on it for the "Directeur du Service de la Radiodiffusion" to fill in. This country takes a long time to answer, if ever.



PHOTOGRAPH OF THE DIRECTIONAL AERIAL USED AT BERLIN

Daventry sends a card acknowledging receipt of your letter, but cannot verify specific reports due to more than one wavelength being used simultaneously.

2RO, Rome, Italy, is another station that is easy to hear, but hard to hear from. When they answer, they send a card written in Italian. The card is printed in three colors: red, white, and black. The letters 1RO and 2RO take in the entire length of the station card.

The most interesting and thrilling veries come from the Far East. On the envelope are letters in Siamese which are printed in a heavy ink, resembling paint. Under these characters are the words in English, "Post and Telegraph Department." On the flap of the envelope is the official crest, which resembles an idol, or Buddah, with spread double wings and a head.

This same crest is printed in the upper left-hand corner of the letter with "Telepost Bangkok" printed in this same heavy ink. The letter is numbered for future reference and the body of this message is written in perfect English and signed by the "Superintending Engineer of Radio." This is a veri well worth the necessary three months to get.

From Java we also get a letter of interest, not so truly Oriental as the one from Siam, but just as "rare" a catch. The letter is written on a very heavy paper with no water mark. The firm name and address are written in Dutch. The communication sent by the listener has been numbered and the answer is written in English.

Now a certain station in Japan, not J1AA, sends out a very pretty post card picture of its antenna system. This card is enclosed in an envelope of transparent paper. On this envelope is a sketch of the volcanic mountain Fujiyama and also



MALABAR TRANSMITTING STATION NEAR BANDOENG, JAVA  
The vertical fan antenna is strung between two mountain peaks!

some Japanese lettering. Under this in the same language is the time schedule and other information concerning the station.

A station in the Far East that does not QSL with a card or letter is VUC, Calcutta, India. An official magazine printed by the station devotes several pages to letters from listeners who report reception of this "rare" one. The magazine has many pictures in it and much information. One paragraph in this booklet says, "Those desirous of a reply to their correspondence must always send a stamped addressed envelope for a reply. No replies will be sent otherwise. Also please remember to write legibly or in block letters if typewriter is not used. We do not keep hand writing experts to decipher unintelligible writings and signatures." In the July 7th issue only two Americans have received recognition.

A station that verifies in French is the Indo-China phone, FZS. The mother station is in Paris, and controls FTE and FTA, St. Assisse, France. This veri is in French and is one that is difficult to understand

#### British Amateur Regulations

In the mail bag was a very interesting letter from a British short-wave fan who has just become an amateur. The rules and regulations of the Government of Great Britain for amateurs are very exacting. Amateurs here in the States may be interested in knowing some of them.


All sending stations must be equipped for reception. Applicant for a license must be of British birth. For those who want a radiating aerial the examination requires that he have an adequate knowledge of the adjustment and operation of the apparatus and an operating speed of at least twelve

Morse words a minute, sending and receiving. A fee of five shillings is charged for this examination.

For each station authorized to use power up to ten watts the initial licensing fee is ten shillings plus an annual fee of one pound. Higher fees are charged for more powerful stations. If apparatus is also used for receiving broadcast programs for entertainment, a wireless receiving license must also be held.

Amateurs are limited to the following wavelengths:

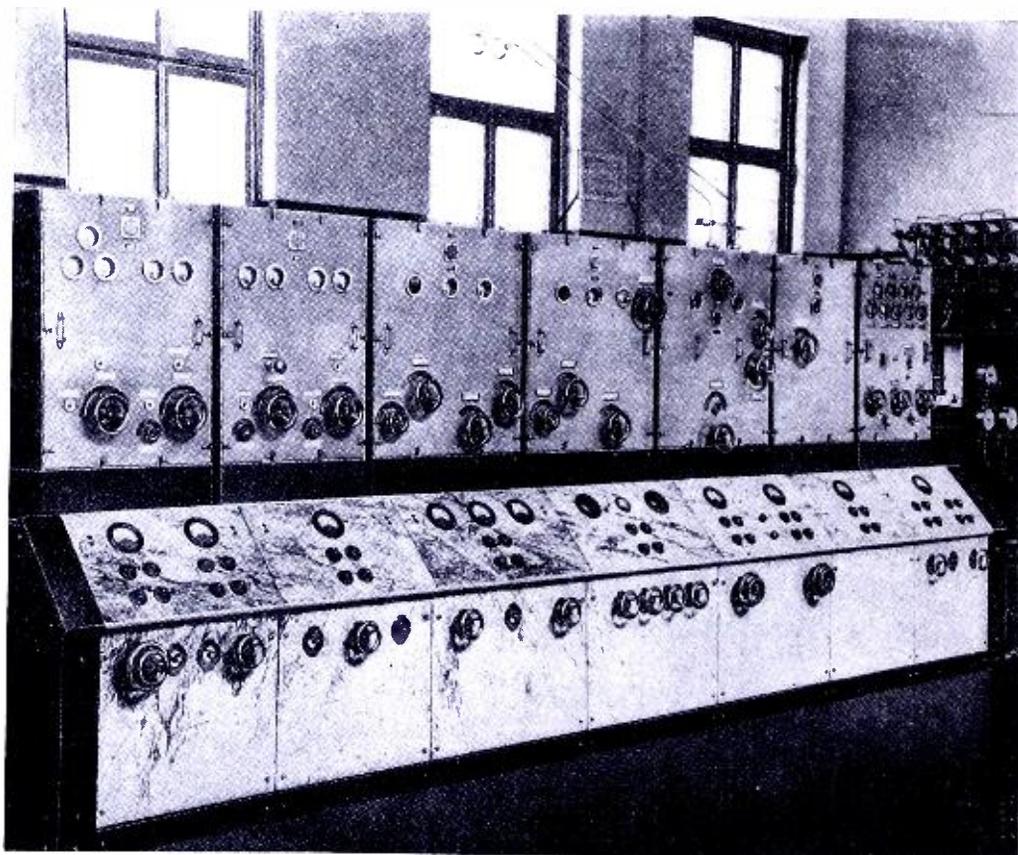- 173.4 to 151.1 meters.
- 42.7 to 41.24 meters.
- 31.33 to 20.88 meters.



THE MAIN TRANSMITTER USED AT THE BERLIN STATION  
The fancy sloping panels are characteristic of German radio apparatus.

If special justification is shown the licensing officials, the following meters may be permitted:

- 10.7 to 10.02 meters.
- 5.35 to 5.005 meters.

Ordinary transmission will be limited to code work and telephony.

Aerials are limited to the following dimensions: combined height and length not to exceed one hundred feet.

Licenses are also given to chaps who desire to transmit with an "artificial aerial," that is a non-radiating aerial. No Morse qualifications are necessary.

The last mentioned license is the type my friend has obtained.

An "artificial aerial" means a closed, no ground, oscillator circuit possessing inductance, capacity, and resistance, and functioning in place of the usual aerial-earth system. It must be as near non-radiating as possible. The inductance should be in one piece and of small dimensions, as distinct from an inductance of large dimensions, such as a frame aerial. The maximum area formed by the turns of the inductance shall not exceed one square foot, and any lateral dimension or, in the case of a circular or oval inductance, shall not exceed one linear foot.

The "artificial" aerial circuit must be so arranged as to reduce radiation to a point at which signals from it will not be perceptible outside the building in which the apparatus is installed, and no attempt shall be made to send signals to other stations. It is intended that the effects produced by the sending apparatus shall be ascertained by means of suitable detecting or measuring devices coupled with or used within a few feet of the inductance of the "artificial" area.

**For the Station List**

With the help of our innumerable correspondents we were able to greatly improve our list of stations heard.

PSH, 29.35 meters, Rio de Janeiro, Brazil, sending programs for the Radio Club of Brazil.

LSX, 28.98 meters, Buenos Aires, sending tests programs to America.

XETE, Mexico City, Mexico, roaming all over the dials from 29 to 31.25 meters; most irregular.

RV59, 50.00 meters, Moscow, U. S. S. R. This station will be heard now that the winter is approaching.

JAVA, 48.3 and 49.15 meters, testing and using a speech scrambler.

VE9JR, 25.60 meters, Winnipeg, Canada.


VE9HX, 49.10 meters, Halifax, Nova-Scotia, Canada.

PRADO, 45.31 meters, Rio Bamba, Ecuador. Thursdays from 9 to 11.30 p. m., sending very fine programs.

EAQ, Madrid, Spain, 30.00 meters, always coming in with an R-9 signal.

HI1A, 49.89 meters, Santa Domingo, Dominican Republic, has been sending some wonderful programs.

YV3BC, 48.95 meters, Caracas,

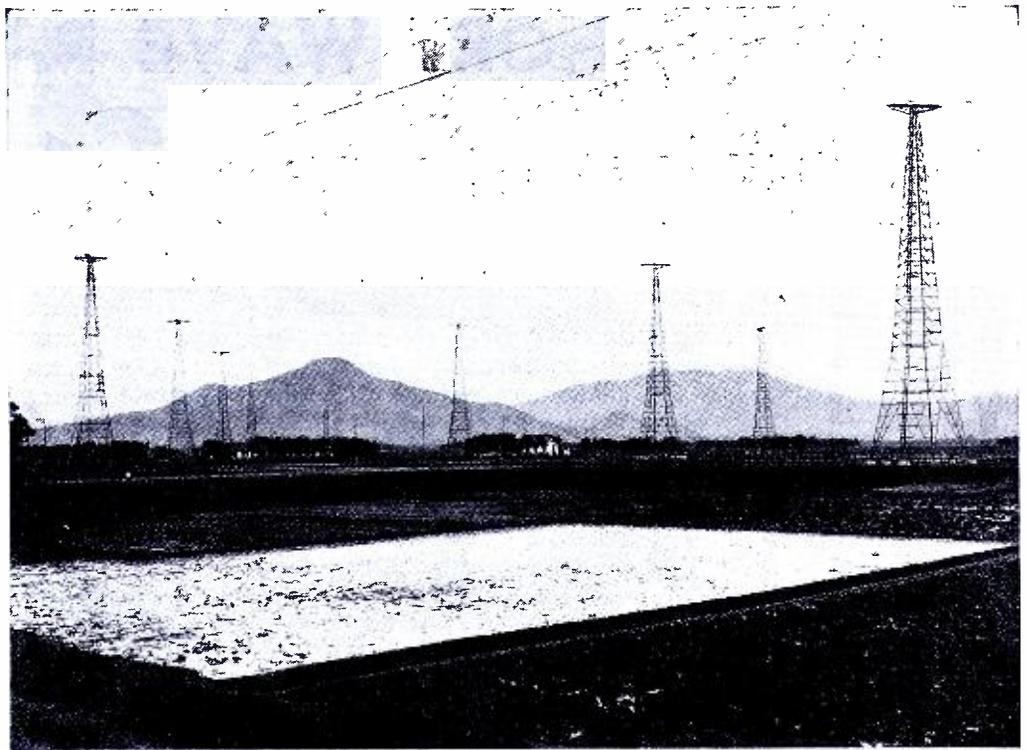

THE RANBJA EKEK RECEIVING STATION NEAR BANDOENG, JAVA  
The antenna consists of wires—usually two—strung between the towers.

Venezuela, has been sending programs received here with fine volume and clarity.

YV1BC, 49.1 meters, Caracas, Venezuela, hard to pull in when band is busy.

**RADIO CENTRE, SOLIANKA 12, MOSCOW  
U. S. S. R.**

**PROGRAMME FOR OCTOBER, 1933**

PART 1				HOURS OF BROADCASTS			
DAYS	23-24 Moscow Time 21-22 Cen. Europe T. 20-21 Greenwich T.		0-1 Moscow Time 22-23 Cen. Europe T. 21-22 Greenwich T.		1-2 Moscow Time 23-24 Cent. Europe Time 22-23 Greenwich Time		
	Language and Wavelength		Language and Wavelength		Language and Wavelength		
Mon.	German 1481 and 50 m.	English 1481 m. 50 m.	Hungary 424.3 m. and 45.38 m.	German 1481 and 50 m.			
Tues.	German 1481 and 50 m.	French 1481 m. 50 m.	Dutch 424.3 m. and 45.38 m.	English 424.3 m. and 45.38 m.	German 1481 and 50 m.		
Wed.	German 1481 and 50 m.	English 1481 m. 50 m.	Czech. 424.3 m. and 45.38 m.	German 1481 and 50 m.			
Thurs.	German 1481 and 50 m.	French 1481 m. 50 m.	Swedish 424.3 m. and 45.38 m.	English 424.3 m. and 45.38 m.	Spanish 1481 and 50 m.		
Fri.	German 1481 and 50 m.	English 1481 m. 50 m.	Czech. 424.3 m. and 45.38 m.	German 1481 and 50 m.			
Sat.	German 1481 and 50 m.	French 1481 m. 50 m.	Czech. 424.3 m. and 45.38 m.	English 424.3 m. and 45.38 m.	Spanish 1481 and 50 m.		
Sun.	German 1481 and 50 m.	English 1481 m. and 50 m.	Swedish 424.3 m. and 45.38 m.	German 1481 and 50 m.			
Sun.	4-5, 6-7 Moscow T. 2-3, 4-5 Cent. E. T. 1-2, 3-4 Greenw. T.		English 50 m. News Bulletin				

A typical program issued by the U. S. S. R.

**The Jamestown N. Y., Amateur Radio Association**

President, Harry Stewart, W8CQW, 143 Fairview Ave.; Vice-President, Waldemer Jaderstrom, W8HJN, R. F. D. No. 3; Secretary-Treasurer and Publicity Manager, Norman W. Smith, P. O. Box 273.

Club meetings are held on alternate Friday evenings in Room 2 of the Central High School at 7:30 p. m. The club conducts a class in code for beginners on Wednesday and alternate Friday evenings at the Central High School. Twenty-three registered for this class. Carl Ornehaug, W8CDK, is the instructor, and rapid progress is being made.

The club is affiliated with the A. R. R. L., and a large number of its members are also members of the League.

We boast of over fifty members, of whom, perhaps, thirty are really active. Hamfests, treasure hunts, and picnics are held from time to time. QSO contests, etc., create much interest. Lectures on radio fundamentals are part of the club meetings during the winter season.

(The editors would be pleased to receive descriptions of local radio clubs for publication. The descriptions do not, necessarily, have to be lengthy; in fact, the shorter the better. Include, though, the names of the officers as well as their call letters—it helps, you know.

If possible, get hold of some good pictures; small snapshots, if they are clear, will do the trick.

# SHORT WAVE RADIO'S

# Short-Wave Station List

**T**HE following list, conveniently arranged alphabetically according to call letters, represents practically all the short-wave stations of the world, except amateur, that use voice transmission and are therefore recognizable by listeners who do not know the code. In most cases the frequency in kilocycles, the corresponding wavelength in meters, and the location by city are given; the country of origin, where it is not obvious, may quickly be determined from the preliminary list of international call letter assignments. Amateur and some special experimental calls consist of the assigned prefix, followed by a number and usually two or three more letters.

Stations listed as "experimental" change around a great deal and may use code or voice; definite frequen-

cies cannot be given for them.

No attempt has been made to include operating schedules in this list, as a great majority of the stations are experimental in nature, and have the habit of changing announced programs without warning. Up-to-the-minute information on the best stations of the month is contained in another department in this issue.

For the sake of brevity, a number of abbreviations of operating company names are used. These are RCA, Radio Corporation of America; GPO, General Post Office; BBC, British Broadcasting Corporation; CBS, Columbia Broadcasting System; NBC, National Broadcasting Company; GE, General Electric Company; ATT, American Telegraph & Telephone Co.; MRT, Mackay Radio Telegraph Co.

## List of International Call Assignments

Block of Calls	Country	Amateur Prefix	Block of Calls	Country	Amateur Prefix	Block of Calls	Country	Amateur Prefix
CAA-CEZ	Chile	CE	J	Japan	J	VOA-VOZ	Newfoundland	VO
CFA-CKZ	Canada	VE	K	United States of America:		VPA-VSZ	British colonies and protectorates	
CLA-CMZ	Cuba	CM		Continental United States	W		British Guiana	VP
CNA-CNZ	Morocco	CN		Philippine Ids.	KA		Fiji, Ellice Ids., Zanzibar	VPI
CPA-CPZ	Bolivia	CP		Porto Rico and Virgin Ids.	K4		Bahamas, Barbados,	
CQA-CRZ	Portuguese colonies:			Territory of Hawaii	K6		Jamaica	VP2
	Cape Verde Ids	CR4	LAA-LNZ	Norway	LA		Bermuda	VP9
	Portuguese Guinea	CR5	LOA-LVZ	Argentine Republic	LU		Fanning Id.	VQ1
	Angola	CR6	LZA-LZZ	Bulgaria	LZ		Northern Rhodesia	VQ2
	Mozambique	CR7	M	Great Britain	G		Tanganyika	VQ3
	Portuguese India	CR8	N	United States of America	W		Kenya Colony	VQ4
	Macao	CR9	OAA-OCZ	Peru	OA		Uganda	VQ5
	Timor	CR10	OFA-OHZ	Finland	OH		Malaya (including Straits Settlements)	VS1-2-3
CSA-CUZ	Portugal:		OKA-OKZ	Czechoslovakia	OK		Hongkong	VS6
	Portugal proper	CT1	ONA-OTZ	Belgium and colonies	ON		Ceylon	VS7
	Azores	CT2	OUA-OZZ	Denmark	OZ	VTA-VWZ	British India	VU
	Madeira	CT3	PAA-PIZ	The Netherlands	PA	W	United States of America:	
CA-CVZ	Rumania	CV	PJA-PJZ	Curacao	PJ		Continental United States	W
CWA-CXZ	Uruguay	CX	PKA-POZ	Dutch East Indies	PK		(for others, see under K.)	
CZA-CZZ	Monaco	CZ	PPA-PYZ	Brazil	PY	XAA-XFZ	Mexico	X
D	Germany	D	PZA-PZZ	Surinam	PZ	XGA-XUZ	China	AC
EAA-EIHZ	Spain	EAR	RAA-RQZ	U. S. S. R. ("Russia")	RA	YAA-YAZ	Afghanistan	YA
EIA-EIZ	Irish Free State	EI	RVA-RVZ	Persia	RV	YHA-YHZ	New Hebrides	YH
ELA-ELZ	Liberia	EL	RXA-RXZ	Republic of Panama	RX	YIA-YIZ	Iraq	YI
ESA-ESZ	Esthonia	ES	RYA-RYZ	Lithuania	RY	YLA-YLZ	Latvia	YL
ETA-ETZ	Ethiopia (Abyssinia)	ET	SAA-SMZ	Sweden	SM	YMA-YMZ	Danzig	YM
F	France (including colonies):		SPA-SRZ	Poland	SP	YNA-YNZ	Nicaragua	YN
	France proper	F	STA-SUZ	Egypt:		YSA-YSZ	Republic of El Salvador	YS
	French Indo-China	F1		Sudan	ST	YVA-YVZ	Venezuela	YV
	Tunis	FM4		Egypt proper	SU	ZAA-ZAZ	Albania	ZA
	Algeria	FM8	SVA-SZZ	Greece	SV	ZBA-ZHZ	British colonies and protectorates	
G	United Kingdom:		TAA-TCZ	Turkey	TA		Transjordan	ZC1
	Great Britain except Ireland	G	TFA-TFZ	Iceland	TF		Palestine	ZC6
	Northern Ireland	GI	TGA-TGZ	Guatemala	TG		Nigeria	ZD
HAA-HAZ	Hungary	HA	TIA-TIZ	Costa Rica	TI		Southern Rhodesia	ZE1
HBA-HBZ	Switzerland	HB	TSA-TSZ	Territory of the Saar Basin	TS	ZKA-ZMZ	New Zealand:	
HCA-HCZ	Ecuador	HC	UHA-UHZ	Hedjaz	UH		Cook Ids.	ZK
HHA-HHZ	Haiti	HH	UIA-UKZ	Dutch East Indies	PK		New Zealand proper	ZL
HIA-HIZ	Dominican Republic	HI	ULA-ULZ	Luxemburg	UL		British Samoa	ZM
IJA-HKZ	Colombia	HJ	UNA-UNZ	Yugoslavia	UN	ZPA-ZPZ	Paraguay	ZP
IRA-HRZ	Honduras	HR	UOA-UOZ	Austria	UO			ZS
ISA-HSZ	Siam	HS	UWA-VGZ	Canada	VE	ZSA-ZUZ	Union of South Africa	ZT
I	Italy and colonies	I	VHA-VMZ	Australia	VK			ZU

# STATIONS ALPHABETICALLY BY CALL LETTERS

## —C—

<b>CEC</b>	10,670 kc., 28.12 m.
	15,860 kc., 18.91 m.
	19,690 kc., 15.24 m.
	Santiago, Chile
<b>CFA</b>	6,840 kc., 43.8 m.
<b>CDM</b>	Drummondville, Quebec, Canada
<b>CGA</b>	4,780 kc., 62.7 m.
	13,340 kc., 22.55 m.
	13,750 kc., 21.82 m.
	9,330 kc., 32.15 m.
	18,170 kc., 16.5 m.
	Quebec, Canada
<b>CM6XJ</b>	15,000 kc., 19.99 m.
	Central Tuinucu, Cuba
<b>CMCI</b>	6,060 kc., 49.5 m.
	Havana, Cuba
<b>CN8MC</b>	6,250 kc., 48 m.
	Casablanca, Morocco
<b>CNR</b>	8,050 kc., 37.33 m.
	9,300 kc., 32.26 m.
	12,880 kc., 23.38 m.
	Rabat, Morocco, Africa
<b>CT1AA</b>	6,990 kc., 42.9 m.
	9,600 kc., 31.25 m.
	Lisbon, Portugal
<b>CT3AQ</b>	11,181 kc., 26.33 m.
	Funchal, Madeira

## —D—

<b>DAF</b>	8,470 kc., 35.42 m.
	12,400 kc., 24.19 m.
	17,270 kc., 17.37 m.
	Norden, Germany
<b>DAN</b>	11,340 kc., 26.44 m.
	Nordeich, Germany
<b>DFA</b>	4,400 kc., 68.17 m.
	19,240 kc., 15.58 m.
<b>DFB</b>	18,520 kc., 17.12 m.
<b>DGK</b>	6,680 kc., 44.91 m.
<b>DGU</b>	9,620 kc., 31.2 m.
<b>DHC</b>	11,435 kc., 26.22 m.
<b>DHO</b>	20,040 kc., 14.97 m.
<b>DIH</b>	19,950 kc., 15.03 m.
<b>DIQ</b>	10,290 kc., 29.15 m.
<b>DIS</b>	10,150 kc., 29.54 m.
	Nauen, Germany
<b>DJA</b>	9,560 kc., 31.38 m.
	Konigswusterhausen, Germany
<b>DJB</b>	15,200 kc., 19.73 m.
<b>DJC</b>	6,020 kc., 49.83 m.
<b>DJD</b>	11,760 kc., 25.51 m.
	Zeesen, Germany
<b>DOA</b>	7,230 kc., 41.46 m.
	7,390 kc., 37.8 m.
	4,430 kc., 67.5 m.
	3,620 kc., 82.9 m.
	Doberitz, Germany

## —E—

<b>EAJ25</b>	6,000 kc., 50 m.
	Barcelona, Spain
<b>EAR110</b>	6,980 kc., 43.0 m.
	Madrid, Spain
<b>EAQ</b>	19,700 kc., 15.23 m.
	10,000 kc., 30 m.
	Alcaida 43—Madrid, Spain
<b>EHY</b>	10,100 kc., 29.7 m.
	Madrid, Spain

## —F—

<b>F8KR</b>	3,750 kc., 80 m.
<b>F8KR</b>	6,660 kc., 45 m.
	Constantine, Algeria
<b>F8MC</b>	6,875 kc., 43.6 m.
	Casablanca, Morocco
<b>FIGA</b>	6,000 kc., 49.97 m.
	Tananarive, Madagascar
<b>FL</b>	6,120 kc., 49.02 m.
<b>FLJ</b>	9,230 kc., 32.5 m.
	Paris, France
<b>FOE</b>	12,150 kc., 24.68 m.
<b>FOO</b>	12,150 kc., 24.68 m.
<b>FRE</b>	18,240 kc., 16.44 m.
<b>FRE</b>	19,400 kc., 15.45 m.
<b>FRO</b>	18,240 kc., 16.44 m.
	St. Assise, France
<b>FSR</b>	20,680 kc., 14.5 m.
	Paris, France
<b>FTA</b>	11,950 kc., 25.12 m.
<b>FTD</b>	19,830 kc., 15.12 m.
<b>FTF</b>	7,770 kc., 38.6 m.
<b>FTK</b>	15,690 kc., 19.12 m.
<b>FTK</b>	15,860 kc., 18.9 m.
	St. Assise, France

<b>FYA</b>	11,705 kc., 25.6 m.
<b>FYA</b>	11,905 kc., 25.16 m.
<b>FYA</b>	15,240 kc., 19.68 m.
	Pontoise (Paris) France
<b>FZG</b>	12,000 kc., 24.98 m.
<b>FZR</b>	16,200 kc., 18.5 m.
<b>FZS</b>	11,900 kc., 25.02 m.
<b>FZS</b>	18,310 kc., 16.38 m.
	Saigon, Indo-China

## —G—

<b>GAA</b>	20,380 kc., 14.72 m.
<b>GAG</b>	18,970 kc., 15.81 m.
<b>GAS</b>	18,410 kc., 16.38 m.
<b>GAU</b>	18,620 kc., 16.11 m.
<b>GBB</b>	13,580 kc., 22.09 m.
<b>GBC</b>	17,080 kc., 17.55 m.
<b>GBC</b>	12,780 kc., 23.46 m.
<b>GBC</b>	9,310 kc., 32.22 m.
<b>GBC</b>	8,680 kc., 34.56 m.
<b>GBC</b>	4,980 kc., 60.26 m.
	Rugby, England
<b>GBJ</b>	18,620 kc., 16.1 m.
<b>GBK</b>	16,100 kc., 16.57 m.
	9,250 kc., 32.4 m.
	11,490 kc., 26.1 m.
	Bodmin, England
<b>GBP</b>	10,770 kc., 28.04 m.
<b>GBS</b>	18,310 kc., 16.38 m.
	12,250 kc., 24.46 m.
	12,150 kc., 24.68 m.
<b>GBU</b>	18,620 kc., 16.11 m.
	22,300 kc., 13.45 m.
	12,290 kc., 24.41 m.
	9,950 kc., 30.15 m.
<b>GBW</b>	14,480 kc., 20.7 m.
	9,790 kc., 30.64 m.
	GPO, Rugby, Eng.
<b>GBX</b>	16,150 kc., 18.56 m.
	10,390 kc., 28.86 m.
	9,710 kc., 30.9 m.
<b>GCA</b>	9,280 kc., 32.33 m.
<b>GCB</b>	9,020 kc., 33.26 m.
<b>GCS</b>	9,950 kc., 30.15 m.
<b>GCU</b>	9,800 kc., 30.60 m.
<b>GCW</b>	6,900 kc., 43.45 m.
<b>GDS</b>	4,840 kc., 62.0 m.
	Rugby, England
<b>GSA</b>	6,050 kc., 49.58 m.
<b>GSB</b>	9,510 kc., 31.55 m.
<b>GSC</b>	9,585 kc., 31.29 m.
<b>GSD</b>	11,750 kc., 25.53 m.
<b>GSE</b>	11,865 kc., 25.28 m.
<b>GSF</b>	15,140 kc., 19.81 m.
<b>GSG</b>	17,770 kc., 16.88 m.
<b>GSH</b>	21,470 kc., 13.97 m.
	BBC, Daventry, Eng.
<b>G6RX</b>	4,320 kc., 69.44 m.
	Rugby, England

## —H—

<b>HB9D</b>	7,200 kc., 41.5 m.
	Zurich, Switzerland
<b>HBF</b>	18,900 kc., 15.78 m.
<b>HBJ</b>	14,560 kc., 20.6 m.
	Pragins, Switzerland
<b>HBL</b>	9,595 kc., 31.27 m.
<b>HBP</b>	7,800 kc., 38.47 m.
	Geneva, Switzerland
<b>HC1DR</b>	6,382 kc., 47 m.
	Quito, Ecuador
<b>HC2JSB</b>	8,000 kc., 37.5 m.
	Guayaquil, Ecuador
<b>HCJB</b>	8,110 kc., 37.0 m.
	5,714 kc., 52.5 m.
	Quito, Ecuador, S. A.
<b>HJ1ABB</b>	5,800 kc., 51.75 m.
	Barranquilla, Colombia
<b>HJ2ABA</b>	5,880 kc., 51.49 m.
	Tunja, Colombia
<b>HJ3ABD</b>	7,400 kc., 40.55 m.
<b>HJ3ABF</b>	6,250 kc., 48.0 m.
	Bogota, Colombia
<b>HJ4ABB</b>	7,150 kc., 41.6 m.
	Manizales, Colombia
<b>HJ4ABE</b>	5,930 kc., 5.06 m.
	Medellin, Colombia
<b>HJ5ABD</b>	6,380 kc., 47.0 m.
	Cali, Colombia
<b>HJB</b>	7,470 kc., 40.16 m.
<b>HJY</b>	9,930 kc., 30.2 m.
	18,460 kc., 16.25 m.
<b>HKC</b>	6,270 kc., 47.81 m.
	Bogota, Colombia
<b>HKF</b>	7,612 kc., 39.14 m.
<b>HKM</b>	6,660 kc., 45 m.
	Bogota, Colombia

<b>HKO</b>	5,900 kc., 50.8 m.
	Medellin, Colombia
<b>HKX</b>	7,140 kc., 42.02 m.
	Bogota, Colombia
<b>HSP2</b>	9,640 kc., 31.1 m.
<b>HSP</b>	17,750 kc., 16.92 m.
	Bangkok, Siam
<b>HVJ</b>	5,970 kc., 50.26 m.
	75,110 kc., 19.84 m.
	15,120 kc., 19.83 m.
	Vatican City, Rome, Italy

## —I—

<b>I2RO</b>	11,810 kc., 25.4 m.
	Rome, Italy
<b>I3RO</b>	3,750 kc., 80 m.
	Rome, Italy
<b>IAC</b>	8,380 kc., 35.8 m.
	6,650 kc., 45.1 m.
	12,800 kc., 23.45 m.
	Pisa, Italy
<b>IBDK</b>	11,470 kc., 26.15 m.
<b>IRW</b>	19,540 kc., 15.25 m.
	Italy
	<b>J</b>
<b>JB</b>	6,069 kc., 49.43 m.
	Johannesburg, South Africa
<b>J1AA</b>	7,880 kc., 38.07 m.
	13,090 kc., 22.93 m.
	9,870 kc., 30.4 m.
	15,490 kc., 19.36 m.
	Tokio, Japan

## —K—

<b>K6XQ</b>	Experimental
	S. S. Lake Miraflores
<b>KAZ</b>	9,970 kc., 30.09 m.
	Manila, P. I.
<b>KDK</b>	7,520 kc., 39.89 m.
<b>KEJ</b>	9,020 kc., 33.27 m.
	Kauhuku, T. H.
<b>KEL</b>	6,860 kc., 43.7 m.
	Bolinas, Cal.
<b>KEQ</b>	7,370 kc., 40.71 m.
	Kauhuku, T. H.
<b>KES</b>	10,410 kc., 28.80 m.
<b>KEZ</b>	10,410 kc., 28.80 m.
	Bolinas, Cal.
<b>KGHO</b>	1,534 kc., 191.1 m.
	Des Moines, Iowa
<b>KGJX</b>	1,712 kc., 175.15 m.
	Pasadena, Cal.
<b>KGOZ</b>	2,470 kc., 121.5 m.
	Cedar Rapids, Iowa
<b>KGPA</b>	2,414 kc., 124.2 m.
	Seattle, Wash.
<b>KGPB</b>	2,416 kc., 124.1 m.
	Minneapolis, Minn.
<b>KGPC</b>	1,712 kc., 175.15 m.
	St. Louis, Mo.
<b>KGPD</b>	2,470 kc., 121.5 m.
	San Francisco, Cal.
<b>KGPE</b>	2,422 kc., 123.8 m.
	Kansas City, Mo.
<b>KGPG</b>	2,422 kc., 123.8 m.
	Vallejo, Cal.
<b>KGPH</b>	2,450 kc., 122.4 m.
	Oklahoma City, Okla.
<b>KGPI</b>	2,470 kc., 121.5 m.
	Omaha, Neb.
<b>KGPJ</b>	1,712 kc., 175.15 m.
	Beaumont, Tex.
<b>KGPL</b>	1,712 kc., 175.15 m.
	Los Angeles, Cal.
<b>KGPM</b>	2,470 kc., 121.5 m.
	San Jose, Cal.
<b>KGPN</b>	2,470 kc., 121.5 m.
	Davenport, Iowa
<b>KGPO</b>	2,450 kc., 122.4 m.
	Tulsa, Okla.
<b>KGPP</b>	2,442 kc., 122.8 m.
	Portland, Ore.
<b>KGPO</b>	2,450 kc., 122.4 m.
	Honolulu, T. H.
<b>KGPS</b>	2,414 kc., 124.2 m.
	Bakersfield, Cal.
<b>KGPW</b>	2,470 kc., 121.5 m.
	Salt Lake City, Utah
<b>KGPX</b>	2,442 kc., 122.8 m.
	Denver, Colo.
<b>KGPY</b>	1,574 kc., 189.5 m.
	Shreveport, La.
<b>KGPZ</b>	2,450 kc., 122.4 m.
	Wichita, Kans.
<b>KGTP</b>	Various aero frequencies

<b>KGZB</b>	1,712 kc., 175.15 m.
	Houston, Tex.
<b>KGZD</b>	2,430 kc., 123.4 m.
	San Diego, Cal.
<b>KGZE</b>	2,506 kc., 120 m.
	San Antonio, Tex.
<b>KGZF</b>	2,450 kc., 122.4 m.
	Chanute, Kans.
<b>KGZII</b>	2,442 kc., 122.8 m.
	Klamath Falls, Ore.
<b>KGZI</b>	1,712 kc., 175.15 m.
	Wichita Falls, Tex.
<b>KGZL</b>	1,712 kc., 175.15 m.
	Shreveport, La.
<b>KGZM</b>	2,414 kc., 124.2 m.
	El Paso, Tex.
<b>KGZN</b>	2,414 kc., 124.2 m.
	Tacoma, Wash.
<b>KGZP</b>	2,450 kc., 122.4 m.
	Coffeyville, Kans.
<b>KGZO</b>	1,712 kc., 175.15 m.
	Waco, Tex.
<b>KGZR</b>	2,442 kc., 122.8 m.
	Salem, Ore.
<b>KGZX</b>	2,414 kc., 124.2 m.
	Albuquerque, N. M.
<b>KIO</b>	11,670 kc., 25.68 m.
<b>KKH</b>	7,520 kc., 39.89 m.
<b>KKP</b>	16,040 kc., 18.71 m.
	Kauhuku, T. H.
<b>KKO</b>	11,945 kc., 25.1 m.
<b>KKW</b>	13,780 kc., 21.77 m.
<b>KKZ</b>	14,150 kc., 21.17 m.
<b>KQJ</b>	18,050 kc., 16.61 m.
	Bolinas, Cal.
<b>KSW</b>	1,658 kc., 180.7 m.
	Berkeley, Cal.
<b>KVP</b>	1,712 kc., 175.15 m.
	Dallas, Tex.
<b>KWN</b>	21,000 kc., 14.24 m.
<b>KWO</b>	15,420 kc., 19.46 m.
<b>KWU</b>	15,350 kc., 19.54 m.
<b>KWV</b>	10,840 kc., 27.67 m.
<b>KWX</b>	7,610 kc., 39.42 m.
<b>KWY</b>	7,560 kc., 39.65 m.
<b>KWZ</b>	10,400 kc., 28.8 m.
	Dixon, Cal.

## —L—

<b>LGN</b>	9,600 kc., 31.23 m.
	Bergen, Norway
<b>LQA</b>	9,600 kc., 31.25 m.
<b>LSA</b>	9,890 kc., 30.3 m.
<b>LSA</b>	14,530 kc., 20.65 m.
<b>LSG</b>	19,950 kc., 15.03 m.
<b>LSG</b>	19,906 kc., 15.07 m.
<b>LSL</b>	10,300 kc., 29.12 m.
<b>LSL</b>	21,160 kc., 14.17 m.
	Buenos Aires
<b>LSM</b>	21,130 kc., 14.15 m.
	Monte Grande, Argentina (Buenos Aires)
<b>LSN</b>	14,530 kc., 20.65 m.
<b>LSN</b>	21,020 kc., 14.27 m.
<b>LSN</b>	20,680 kc., 14.5 m.
<b>LSR</b>	18,960 kc., 15.82 m.
<b>LSX</b>	10,350 kc., 28.98 m.
<b>LSY</b>	20,730 kc., 14.47 m.
<b>LSY</b>	10,410 kc., 28.8 m.
<b>LSY</b>	18,130 kc., 16.55 m.
	Buenos Aires

## —N—

<b>NAA</b>	16,060 kc., 18.68 m.
<b>NAA</b>	12,045 kc., 24.89 m.
<b>NAA</b>	4,105 kc., 74.72 m.</

OXY 15,300 kc., 19.6 m.  
Lyngby, Denmark  
OXY 6,075 kc., 49.4 m.  
OXY 9,520 kc., 31.51 m.  
Skamleback, Denmark  
OZ7RI 3,560 kc., 84.24 m.  
Copenhagen, Denmark

—P—

PCK 7,770 kc., 38.6 m.  
18,400 kc., 16.3 m.  
PCL 16,300 kc., 18.4 m.  
PCV 17,830 kc., 16.82 m.  
PDK 10,410 kc., 28.8 m.  
PDU 7,830 kc., 38.3 m.  
PDV 12,060 kc., 24.88 m.  
Kootwijk, Holland  
PHI 17,770 kc., 16.88 m.  
11,730 kc., 25.57 m.  
Huizen, Holland  
PK2AG 3,156 kc., 95 m.  
Samarang, Java  
PK3AN 6,040 kc., 49.67 m.  
Sourabaya, Java  
PLE 18,200 kc., 15.94 m.  
PLF 17,850 kc., 16.8 m.  
PLG 15,950 kc., 18.8 m.  
PLM 12,250 kc., 24.46 m.  
PLR 10,630 kc., 28.2 m.  
PLV 9,420 kc., 31.86 m.  
PLW 8,120 kc., 36.92 m.  
9,480 kc., 31.63 m.  
PMB 20,620 kc., 14.54 m.  
5,170 kc., 58 m.  
PMC 18,370 kc., 16.33 m.  
PMN 10,360 kc., 29.25 m.  
PMY 5,170 kc., 58.0 m.  
Bandoeng, Java  
PPG 11,660 kc., 27.73 m.  
PPU 19,270 kc., 15.57 m.  
Rio de Janeiro  
PRADO 6,620 kc., 45.31 m.  
Riobamba, Ecuador  
PRAG 8,450 kc., 35.5 m.  
Porto Algero, Brazil  
PSA 21,080 kc., 14.23 m.  
PSII 10,220 kc., 29.35 m.  
PSK 8,190 kc., 36.65 m.  
Rio de Janeiro

—R—

RABAT 12,830 kc., 23.38 m.  
8,035 kc., 37.33 m.  
Morocco  
RAU 15,100 kc., 19.85 m.  
Tachkent, Turkestan  
REN 6,610 kc., 45.38 m.  
RIM 7,630 kc., 39.34 m.  
RKI 7,500 kc., 39.97 m.  
U. S. S. R.  
RV15 4,273 kc., 70.2 m.  
Khabarovsk, Siberia  
RV59 6,000 kc., 50 m.  
Radio Moscow, U.S.S.R.  
RXF 14,500 kc., 20.69 m.  
Panama City, Panama

—S—

SAJ 6,065 kc., 49.46 m.  
Motola, Sweden  
SRI 9,570 kc., 31.35 m.  
Poznan, Poland  
SUV 10,050 kc., 29.83 m.  
Cairo, Egypt

—T—

TI4NRH 9,675 kc., 31 m.  
Heredia, Costa Rica, C. A.  
TIR 8,790 kc., 34.13 m.  
14,500 kc., 20.69 m.  
Cartago, Costa Rica  
TGA 14,500 kc., 20.69 m.  
6,660 kc., 45 m.  
6,180 kc., 48.5 m.  
TGX 5,940 kc., 50.5 m.  
Guatemala City, C. A.

—U—

UIG 10,400 kc., 28.8 m.  
Medan, Sumatra  
UOR2 6,072 kc., 49.41 m.  
Vienna, Austria

—V—

VE9AP 6,335 kc., 47.35 m.  
Drummondville, Canada  
VE9BJ 6,090 kc., 49.29 m.  
St. John's, N. B., Canada

VE9BY 4,795 kc., 62.56 m.  
6,425 kc., 46.7 m.  
8,650 kc., 34.68 m.  
London, Ontario, Canada  
VE9CA 6,030 kc., 49.75 m.  
Calgary, Alta., Canada  
VE9CF 6,050 kc., 49.59 m.  
6,100 kc., 49.15 m.  
Halifax, N. S., Canada  
VE9CG 6,110 kc., 49.1 m.  
Calgary, Alta., Canada  
VE9CL 5,710 kc., 52.5 m.  
6,147 kc., 48.8 m.  
Winnipeg, Canada  
VE9CS 6,069 kc., 49.43 m.  
Vancouver, B. C., Canada  
VE9CU 6,005 kc., 49.99 m.  
Calgary, Alta., Canada  
VE9DR 11,780 kc., 25.47 m.  
6,005 kc., 49.96 m.  
Drummondville, Quebec, Canada  
VE9GW 6,095 kc., 49.17 m.  
11,800 kc., 25.42 m.  
Bowmanville, Ontario, Canada  
VE9HK 6,120 kc., 48.98 m.  
VE9HX 6,125 kc., 48.98 m.  
Halifax, N. S., Canada  
VE9JR 11,720 kc., 25.6 m.  
Winnipeg, Canada  
VK2ME 9,760 kc., 30.75 m.  
10,520 kc., 28.51 m.  
Sydney, Australia  
VK3LR 9,510 kc., 31.55 m.  
5,680 kc., 52.8 m.  
Melbourne, Australia  
VLJ 9,980 kc., 37.59 m.  
VLK 9,760 kc., 30.75 m.  
10,520 kc., 28.51 m.  
Sydney, Australia  
VPD 7,890 kc., 38.0 m.  
Suva, Fiji Islands  
VPN 4,510 kc., 66.5 m.  
Nassau, Bahamas  
VQ7LO 6,000 kc., 49.5 m.  
Nairobi, Kenya, Africa  
VRT 5,050 kc., 59.42 m.  
10,070 kc., 29.8 m.  
Hamilton, Bermuda  
VSIAB 7,195 kc., 41.67 m.  
Singapore, S. S.  
VUC 6,110 kc., 49.1 m.  
Calcutta, India  
VWY 18,540 kc., 17.1 m.  
Poona, India

—W—

W1XAB 4,700 kc., 63.79 m.  
Portland, Me.  
W1XAL 11,790 kc., 25.45 m.  
6,040 kc., 49.67 m.  
W1XAU 1,560 kc., 199.35 m.  
W1XAV 1,600 kc., 187.5 m.  
Boston, Mass.  
W1XAZ 9,570 kc., 31.35 m.  
Westinghouse, Springfield, Mass.  
W1XG 43,000 kc., 6.52 m.  
W1XL 6,040 kc., 49.67 m.  
Boston, Mass.  
W2XAA Experimental  
Bell Labs., Port. & Mob.  
W2XAB 2,750 kc., 109.1 m.  
CBS, New York, N. Y.  
W2XAC 8,690 kc., 34.5 m.  
W2XAD 15,340 kc., 19.56 m.  
W2XAF 9,530 kc., 31.48 m.  
GE, Schenectady, N. Y.  
W2XAK 43,000 kc., 6.52 m.  
W2XAK 48,500 kc., 6.18 m.  
W2XAK 60,000 kc., 5.00 m.  
CBS, New York, N. Y.  
W2XAO 17,850 kc., 16.8 m.  
W2XAR Experimental  
Long Island City, N. Y.  
W2XAV Experimental  
Bell Labs., Port. & Mob.  
W2XAW Experimental  
GE, Schenectady, N. Y.  
W2XBB Experimental  
RCA, New York, N. Y.  
W2XBC 25,700 kc., 11.67 m.  
RCA, New Brunswick, N. J.  
W2XBG Experimental  
Radio Marine, New York, N. Y.  
W2XBI Experimental  
RCA, Rocky Point, N. Y.  
W2XBJ 14,700 kc., 20.27 m.  
Rocky Point, N. Y.  
W2XBL Experimental  
RCA, Port. & Mob.  
W2XBS 2,100 kc., 136.4 m.  
W2XBT 43,000 kc., 6.52 m.  
W2XBT 48,500 kc., 6.18 m.  
W2XBT 60,000 kc., 5.00 m.  
NBC, Portable

W2XBW Experimental  
Globe Wireless, Garden City, N. Y.  
W2XBX Plane, Experimental  
Bell Labs.  
W2XCJ Experimental  
Police, Bayonne, N. J.  
W2XCS Experimental  
W2XCT Experimental  
Police, Eastchester, N. Y.  
W2XCU 12,850 kc., 23.35 m.  
W2XCU 8,650 kc., 34.68 m.  
Rocky Point, N. Y.  
W2XDC Experimental  
RCA, Portable & Mobile  
W2XDJ 21,420 kc., 14 m.  
ATT, Deal, N. J.  
W2XDK Experimental  
Polin, Inc., Port. & Mob.  
W2XDO 17,110 kc., 17.52 m.  
W2XDO 8,630 kc., 34.74 m.  
ATT, Ocean Gate, N. J.  
W2XDT Experimental  
Press Wireless, Port. & Mob.  
W2XDV Experimental  
CBS, New York, N. Y.  
W2XDY Experimental  
W2XDZ Experimental  
Central Hudson Gas & Electric Co.  
Portable  
W2XE 15,270 kc., 19.65 m.  
W2XE 11,830 kc., 25.36 m.  
W2XE 6,120 kc., 49.02 m.  
CBS, Wayne, N. J.  
W2XEA Experimental  
W2XEB Experimental  
W2XEC Experimental  
W2XED Experimental  
W2XEE Experimental  
W2XEF Experimental  
W2XEG Experimental  
W2XEH Experimental  
Police, Bayonne, N. J.  
W2XEI Experimental  
P. J. Golhofer, Port. & Mob.  
W2XEJ Experimental  
D. B. Whittemore, Yonkers, N. Y.  
W2XEK Experimental  
Knickerbocker Broad. Co., Port.  
& Mob.  
W2XEL Experimental  
Police, Eastchester, N. Y.  
W2XER Experimental  
D. B. Whittemore, Yonkers, N. Y.  
W2XF 43,000 kc., 6.52 m.  
W2XF 48,500 kc., 6.18 m.  
W2XF 60,000 kc., 5.00 m.  
NBC, New York  
W2XG Experimental  
Bell Labs., Ocean Township, N. J.  
W2XGG Experimental  
Police, Bayonne, N. J.  
W2XJ Experimental  
Bell Labs., Ocean Township, N. J.  
W2XK Experimental  
NBC, New York, N. Y.  
W2XL Experimental  
Bell Labs., Port & Mobile  
W2XM Experimental  
W2XN Experimental  
Bell Labs., Holmdel, N. J.  
W2XO 12,850 kc., 23.35 m.  
GE, Schenectady, N. Y.  
W2XP Experimental  
RCA, Riverhead, N. Y.  
W2XR 1,600 kc., 176.5 m.  
W2XR 43,000 kc., 6.97 m.  
W2XR 48,500 kc., 6.18 m.  
W2XR 60,000 kc., 5.00 m.  
W2XS Experimental  
W2XT Experimental  
RCA, Rocky Point, N. Y.  
W2XU Experimental  
Bell Labs., Portable  
W2XV 8,650 kc., 34.68 m.  
W2XV 4,975 kc., 60.30 m.  
Long Island City, N. Y.  
W2XW Experimental  
W2XY Experimental  
Bell Labs., Portable  
W3XAB Experimental  
RCA, Camden, N. J.  
W3XAD 43,000 kc., 6.97 m.  
W3XAD 48,500 kc., 6.18 m.  
W3XAD 60,000 kc., 5.00 m.  
RCA, Camden, N. J.  
W3XAJ Experimental  
RCA, Camden, N. J.  
W3XAK 2,100 kc., 136.4 m.  
NBC, Portable  
W3XAL 17,780 kc., 16.87 m.  
W3XAL 6,100 kc., 49.15 m.  
NBC, Bound Brook, N. J.  
W3XAM Experimental  
RCA, Port. & Mob.

W3XAN Experimental  
Harrisburg, Pa.  
W3XAU 9,580 kc., 31.32 m.  
W3XAU 6,060 kc., 49.5 m.  
CBS, Philadelphia, Pa.  
W3XAW Experimental  
W3XAX Experimental  
M. & H. Sporting Goods Co., Port.  
W3XB Experimental  
College Park, Md.  
W3XE 9,580 kc., 31.32 m.  
W3XE 43,000 kc., 6.52 m.  
W3XE 48,500 kc., 6.00 m.  
W3XE 60,000 kc., 3.75 m.  
Philco, Philadelphia, Pa.  
W3XE 8,650 kc., 34.68 m.  
Baltimore, Md.  
W3XI Experimental  
NBC, Bound Brook, N. J.  
W3XN Experimental  
Bell Labs., Whippany, N. J.  
W3XR Experimental  
Bell Labs., Mendham Township,  
N. J.  
W3XV Experimental  
RCA, Arneys-Mount, N. J.  
W3XW Experimental  
Boonton, N. J.  
W3XX 8,650 kc., 34.68 m.  
W3XZ 4,795 kc., 62.56 m.  
Washington, D. C.  
W4XB 6,040 kc., 49.67 m.  
Miami Beach, Fla.  
W4XC Experimental  
Portable  
W4XD Experimental  
Port. & Mob.  
W4XG 8,650 kc., 34.68 m.  
Miami, Fla.  
W5XC Experimental  
Shreveport, La.  
W6XAC Experimental  
Fred W. Christian, Jr., Portable  
W6XAD Experimental  
San Francisco, Calif.  
W6XAH 2,000 kc., 150 m.  
Bakersfield, Cal.  
W6XAJ Experimental  
Portable  
W6XAO 43,000 kc., 6.97 m.  
W6XAO 48,500 kc., 6.18 m.  
W6XAO 60,000 kc., 5.00 m.  
Los Angeles, Cal.  
W6XAP Experimental  
Port. & Mob.  
W6XAR Experimental  
W6XAS Experimental  
Julius Brunton & Sons Co.,  
Port. & Mob.  
W6XBB Experimental  
Port. in Calif.  
W6XD 27,800 kc., 10.79 m.  
MRT, Palo Alto, Cal.  
W6XF Experimental  
Port. in Calif.  
W6XJ Experimental  
Port. in Calif.  
W6XP Experimental  
Press Wireless, Portable and  
Mobile  
W6XQ 24,000 kc., 12.48 m.  
San Mateo, Cal.  
W6XR Experimental  
San Francisco, Calif.  
W6XS 2,100 kc., 136.4 m.  
Los Angeles, Calif.  
W7XAW 2,342 kc., 128.09 m.  
Seattle, Wash.  
W7XC Experimental  
Edmonds, Wash.  
W7XL Experimental  
Northern Radio Co., Portable  
W8XAG 8,650 kc., 34.68 m.  
Dayton, Ohio  
W8XAL 6,060 kc., 49.5 m.  
Crosley, Cincinnati, O.  
W8XAN 43,000 kc., 6.97 m.  
W8XAN 48,500 kc., 6.18 m.  
W8XAN 60,000 kc., 5.00 m.  
W8XAN 1,600 kc., 176.5 m.  
Jackson, Mich.  
W8XF 43,000 kc., 6.97 m.  
W8XF 48,500 kc., 6.18 m.  
W8XF 60,000 kc., 5.00 m.  
Pontiac, Mich.  
W8XI 31,000 kc., 9.68 m.  
W8XJ 5,550 kc., 54.02 m.  
Columbus, O.  
W8XK 21,540 kc., 13.93 m.  
W8XK 17,780 kc., 16.87 m.  
W8XK 15,210 kc., 19.72 m.  
W8XK 11,870 kc., 25.26 m.  
W8XK 6,140 kc., 48.86 m.  
Westinghouse, E. Pittsburgh, Pa.

<b>W8XL</b> 17,300 kc., 17.34 m. Dayton, O.	<b>W10XJ</b> Experimental Bell Labs., Portable	<b>WOA</b> 6,750 kc., 44.41 m.	<b>WPFA</b> 1,712 kc., 175.15 m. Newton, Mass.
<b>W8XL</b> 43,000 kc., 6.97 m.	<b>W10XN</b> Experimental NBC, Portable and Mobile	<b>WOB</b> 5,850 kc., 51.26 m.	<b>WPFC</b> 2,442 kc., 122.8 m. Muskegon, Mich.
<b>W8XL</b> 48,500 kc., 6.18 m.	<b>W10XT</b> Experimental RCA, Portable and Mobile	<b>WOF</b> 9,750 kc., 30.77 m.	<b>WPFD</b> 2,430 kc., 123.4 m. Highland Park, Ill.
<b>W8XL</b> 60,000 kc., 5.00 m. Cuyahoga Hts., Ohio	<b>W10XX</b> 43,000 kc., 6.97 m.	<b>WOK</b> 10,550 kc., 28.44 m.	<b>WPFE</b> 2,442 kc., 122.8 m. Reading, Pa.
<b>W8XN</b> 1,600 kc., 176.5 m. Jackson, Mich.	<b>W10XX</b> 48,500 kc., 6.18 m.	<b>WON</b> 9,870 kc., 30.40 m. Lawrenceville, N. J.	<b>WPFH</b> 2,430 kc., 123.4 m. Toms River, N. J.
<b>W9XAA</b> 6,080 kc., 49.31 m. Chicago, Ill.	<b>W10XX</b> 60,000 kc., 5.00 m.	<b>WOO</b> 17,110 kc., 17.52 m.	<b>WPFJ</b> 1,712 kc., 175.15 m. Hammond, Ind.
<b>W9XAI</b> Experimental	<b>W10XY</b> Experimental NBC, Portable and Mobile	<b>WOO</b> 8,550 kc., 35.09 m.	<b>WPFK</b> 2,430 kc., 123.4 m. Hackensack, N. J.
<b>W9XAJ</b> Experimental	<b>W10XZ</b> Experimental CBS, Portable and Mobile	<b>WOO</b> 6,515 kc., 46.05 m.	<b>WPFL</b> 2,470 kc., 121.5 m. Gary, Ind.
<b>W9XAK</b> 2,100 kc., 142.9 m. Manhattan, Kans.	<b>WAEQ</b> Various aero frequencies Elmira, N. Y.	<b>WOO</b> 8,630 kc., 34.74 m.	<b>WPFM</b> 2,414 kc., 124.2 m. Birmingham, Ala.
<b>W9XAL</b> 2,200 kc., 136.4 m. Kansas City, Mo.	<b>WAJ</b> 13,480 kc., 22.26 m.	<b>WOO</b> 4,750 kc., 63.13 m.	<b>WPFN</b> 1,712 kc., 175.15 m. Fairhaven, Mass.
<b>W9XAM</b> 4,795 kc., 62.56 m. Elgin, Ill.	<b>WBA</b> 257 kc., 1,123 m. Rocky Point, N. Y.	<b>WOO</b> 4,116 kc., 72.87 m.	<b>WPFO</b> 2,470 kc., 121.5 m. Knoxville, Tenn.
<b>W9XAO</b> 11,840 kc., 25.34 m.	<b>WBR</b> 257 kc., 1,123 m. Harrisburg, Pa.	<b>WOO</b> 3,124 kc., 96.03 m.	<b>WFPF</b> 2,414 kc., 124.2 m. Clarksville, W. Va.
<b>W9XAO</b> 2,000 kc., 150 m.	<b>WCK</b> 2,414 kc., 124.2 m. Butler, Pa.	<b>WOP</b> 19,380 kc., 15.48 m. Ocean Gate, N. J.	<b>WPFQ</b> 2,470 kc., 121.5 m. Swarthmore, Pa.
<b>W9XAP</b> 2,100 kc., 142.9 m. Chicago, Ill.	<b>WCN</b> 5,070 kc., 59.08 m. Belle Island, Mich.	<b>WOU</b> 2,590 kc., 115.8 m. Green Harbor, Mass.	<b>WPI</b> 2,430 kc., 123.4 m. Columbus, Ohio
<b>W9XAT</b> 43,000 kc., 6.97 m.	<b>WDX</b> 257 kc., 1,123 m. Wyoming, Pa.	<b>WOX</b> 2,540 kc., 118.06 m. New York, N. Y.	<b>WPDR</b> 2,458 kc., 122 m. Philadelphia, Pa.
<b>W9XAT</b> 48,500 kc., 6.18 m.	<b>WEA</b> 10,610 kc., 28.28 m.	<b>WPA</b> 2,414 kc., 124.2 m. Tulare, Cal.	<b>WPDS</b> 2,416 kc., 124.1 m. St. Paul, Minn.
<b>W9XAT</b> 60,000 kc., 5.00 m.	<b>WEB</b> 6,940 kc., 43.23 m.	<b>WPB</b> 1,712 kc., 175.15 m.	<b>WPDT</b> 2,470 kc., 121.5 m. Kokomo, Ind.
<b>W9XD</b> 43,000 kc., 6.97 m.	<b>WEC</b> 8,930 kc., 33.59 m.	<b>WPC</b> 1,712 kc., 175.15 m.	<b>WPDU</b> 1,712 kc., 175.15 m. Pittsburgh, Pa.
<b>W9XD</b> 48,500 kc., 6.18 m.	<b>WEF</b> 9,590 kc., 31.6 m.	<b>WPD</b> 1,712 kc., 175.15 m.	<b>WPDV</b> 2,458 kc., 122 m. Charlotte, N. C.
<b>W9XD</b> 60,000 kc., 5.00 m.	<b>WEL</b> 8,950 kc., 33.52 m.	<b>WPE</b> 2,442 kc., 122.8 m.	<b>WPDW</b> 2,422 kc., 123.8 m. Washington, D. C.
<b>W9XE</b> 43,000 kc., 6.97 m.	<b>WEM</b> 7,400 kc., 40.54 m.	<b>WPF</b> 2,442 kc., 122.8 m.	<b>WPDY</b> 2,414 kc., 124.2 m. Detroit, Mich.
<b>W9XE</b> 48,500 kc., 6.18 m.	<b>WES</b> 9,450 kc., 31.74 m.	<b>WPG</b> 2,442 kc., 122.8 m.	<b>WPEH</b> 1,712 kc., 175.15 m. Atlanta, Ga.
<b>W9XE</b> 60,000 kc., 5.00 m.	<b>WGN</b> 5,260 kc., 57.03 m.	<b>WPH</b> 2,442 kc., 122.8 m.	<b>WPEI</b> 1,712 kc., 175.15 m. E. Providence, R. I.
<b>W9XF</b> 17,780 kc., 16.87 m.	<b>WGY</b> 13,870 kc., 21.63 m.	<b>WPI</b> 2,442 kc., 122.8 m.	<b>WPEK</b> 2,422 kc., 123.8 m. New Orleans, La.
<b>W9XF</b> 11,880 kc., 25.24 m.	<b>WJL</b> 257 kc., 1,123 m. Rocky Point, N. Y.	<b>WPK</b> 2,430 kc., 123.4 m.	<b>WPEL</b> 1,574 kc., 189.5 m. W. Bridgewater, Mass.
<b>W9XF</b> 6,100 kc., 49.18 m.	<b>WKA</b> 21,060 kc., 14.25 m. Greensburg, Pa.	<b>WPL</b> 2,470 kc., 121.5 m.	<b>WPEP</b> 1,712 kc., 175.15 m. Arlington, Mass.
<b>W9XG</b> 2,750 kc., 109.1 m. NBC, Chicago, Ill.	<b>WKD</b> 1,712 kc., 175.15 m. Lawrenceville, N. J.	<b>WPM</b> 2,470 kc., 121.5 m.	<b>WPET</b> 1,712 kc., 175.15 m. Lexington, Mass.
<b>W9XK</b> 2,000 kc., 150 m. W. Lafayette, Ind.	<b>WKF</b> 19,220 kc., 15.61 m.	<b>WPN</b> 2,458 kc., 122 m.	<b>WPEV</b> 1,574 kc., 189.5 m. Portable, Mass.
<b>W9XL</b> 17,300 kc., 17.34 m.	<b>WKF</b> 4,750 kc., 63.21 m.	<b>WPO</b> 2,458 kc., 122 m.	<b>WPEW</b> 1,574 kc., 189.5 m. Northampton, Mass.
<b>W9XL</b> 12,850 kc., 23.35 m.	<b>WKJ</b> 9,590 kc., 31.6 m. Lawrenceville, N. J.	<b>WPD</b> 2,470 kc., 121.5 m.	<b>WPEZ</b> 1,574 kc., 189.5 m. Miami, Fla.
<b>W9XL</b> 6,425 kc., 46.70 m.	<b>WKK</b> 21,410 kc., 14.01 m.	<b>WPE</b> 2,470 kc., 121.5 m.	
<b>W10XAA</b> Plane, Experimental Anoka, Minn.	<b>WKN</b> 19,830 kc., 15.13 m. Rocky Point, N. Y.	<b>WPF</b> 2,416 kc., 124.1 m.	
<b>W10XAC</b> Experimental Bell Labs.	<b>WKU</b> 14,700 kc., 20.27 m.	<b>WPG</b> 2,442 kc., 122.8 m.	
<b>W10XAC</b> Experimental Milwaukee, Wis., Port. & Mobile	<b>WKW</b> 19,020 kc., 15.77 m. Rocky Point, N. Y.	<b>WPH</b> 2,458 kc., 122 m.	
<b>W10XAF</b> Experimental Larry L. Smith, Portable	<b>WLA</b> 18,350 kc., 16.35 m.	<b>WPI</b> 2,458 kc., 122 m.	
<b>W10XAG</b> Experimental N. Y. Conservation Dept., Port. and Mobile	<b>WLK</b> 16,330 kc., 18.44 m.	<b>WPK</b> 2,430 kc., 123.4 m.	
<b>W10XAH</b> Experimental	<b>WLO</b> 21,400 kc., 14.01 m.	<b>WPL</b> 2,470 kc., 121.5 m.	
<b>W10XAI</b> Experimental NBC, Portable and Mobile	<b>WLO</b> 16,300 kc., 18.4 m.	<b>WPM</b> 2,470 kc., 121.5 m.	
<b>W10XAJ</b> Experimental N. Y. Conservation Dept., Port. and Mobile	<b>WLO</b> 10,540 kc., 28.44 m.	<b>WPN</b> 2,458 kc., 122 m.	
<b>W10XAK</b> Experimental NBC, Portable and Mobile	<b>ATT, Lawrence, N. J.</b>	<b>WPO</b> 2,458 kc., 122 m.	
<b>W10XAL</b> Experimental CBS, Portable and Mobile	<b>WMA</b> 13,390 kc., 22.4 m. Lawrenceville, N. J.	<b>WPD</b> 2,470 kc., 121.5 m.	
<b>W10XAM</b> Experimental	<b>WMB</b> 267 kc., 1,123 m. West Reading, Pa.	<b>WPE</b> 2,416 kc., 124.1 m.	
<b>W10XAN</b> Experimental	<b>WMDZ</b> 2,442 kc., 122.8 m. Indianapolis, Ind.	<b>WPF</b> 2,442 kc., 122.8 m.	
<b>W10XAP</b> Experimental NBC, Portable and Mobile	<b>WMF</b> 14,470 kc., 20.73 m. Lawrenceville, N. J.	<b>WPG</b> 2,470 kc., 121.5 m.	
<b>W10XAQ</b> Experimental Westinghouse, Portable & Mobile	<b>WMI</b> 19,850 kc., 15.1 m.	<b>WPH</b> 2,458 kc., 122 m.	
<b>W10XAY</b> Experimental Polin, Inc., Portable and Mobile	<b>WMI</b> 9,700 kc., 30.9 m. ATT, Deal, N. J.	<b>WPI</b> 2,442 kc., 122.8 m.	
<b>W10XBA</b> Plane, Experimental	<b>WMJ</b> 2,422 kc., 123.8 m. Buffalo, N. J.	<b>WPK</b> 2,430 kc., 123.4 m.	
<b>W10XBB</b> Plane, Experimental	<b>WMN</b> 14,590 kc., 20.56 m. Lawrenceville, N. J.	<b>WPL</b> 2,470 kc., 121.5 m.	
<b>W10XBC</b> Plane, Experimental Aeronautical Radio Inc.	<b>WMO</b> 2,414 kc., 124.2 m. Highland Park, Mich.	<b>WPM</b> 2,470 kc., 121.5 m.	
<b>W10XBE</b> Experimental N. Y. Conservation Dept., Port. and Mobile	<b>WMP</b> 1,574 kc., 189.5 m. Framingham, Mass.	<b>WPN</b> 2,458 kc., 122 m.	
<b>W10XBF</b> Experimental	<b>WNA</b> 9,170 kc., 32.72 m.	<b>WPO</b> 2,458 kc., 122 m.	
<b>W10XBG</b> Experimental W. G. H. Finch, Portable & Mob.	<b>WNB</b> 10,680 kc., 28.09 m. Lawrenceville, N. J.	<b>WPD</b> 2,470 kc., 121.5 m.	
<b>W10XBI</b> Plane, Experimental Roland Reed	<b>WNC</b> 19,200 kc., 15.6 m.	<b>WPE</b> 2,416 kc., 124.1 m.	
<b>W10XBK</b> Experimental W. G. H. Finch, Portable & Mob.	<b>WNC</b> 14,480 kc., 20.7 m.	<b>WPF</b> 2,442 kc., 122.8 m.	
<b>W10XE</b> Experimental RCA, Portable and Mobile	<b>WNC</b> 9,750 kc., 30.75 m.	<b>WPG</b> 2,470 kc., 121.5 m.	
<b>W10XI</b> Plane, Experimental Aircraft Radio Corp.	<b>WND</b> 18,350 kc., 16.35 m.	<b>WPH</b> 2,442 kc., 122.8 m.	
	<b>WND</b> 13,400 kc., 22.38 m.	<b>WPI</b> 2,442 kc., 122.8 m.	
	<b>WND</b> 6,753 kc., 44.4 m. ATT, Deal, N. J.	<b>WPK</b> 2,430 kc., 123.4 m.	
		<b>WPL</b> 2,470 kc., 121.5 m.	
		<b>WPM</b> 2,470 kc., 121.5 m.	
		<b>WPN</b> 2,458 kc., 122 m.	
		<b>WPO</b> 2,458 kc., 122 m.	
		<b>WPD</b> 2,470 kc., 121.5 m.	
		<b>WPE</b> 2,416 kc., 124.1 m.	
		<b>WPF</b> 2,442 kc., 122.8 m.	
		<b>WPG</b> 2,470 kc., 121.5 m.	
		<b>WPH</b> 2,442 kc., 122.8 m.	
		<b>WPI</b> 2,442 kc., 122.8 m.	
		<b>WPK</b> 2,430 kc., 123.4 m.	
		<b>WPL</b> 2,470 kc., 121.5 m.	
		<b>WPM</b> 2,470 kc., 121.5 m.	
		<b>WPN</b> 2,458 kc., 122 m.	
		<b>WPO</b> 2,458 kc., 122 m.	
		<b>WPD</b> 2,470 kc., 121.5 m.	
		<b>WPE</b> 2,416 kc., 124.1 m.	
		<b>WPF</b> 2,442 kc., 122.8 m.	
		<b>WPG</b> 2,470 kc., 121.5 m.	
		<b>WPH</b> 2,442 kc., 122.8 m.	
		<b>WPI</b> 2,442 kc., 122.8 m.	
		<b>WPK</b> 2,430 kc., 123.4 m.	
		<b>WPL</b> 2,470 kc., 121.5 m.	
		<b>WPM</b> 2,470 kc., 121.5 m.	
		<b>WPN</b> 2,458 kc., 122 m.	
		<b>WPO</b> 2,458 kc., 122 m.	
		<b>WPD</b> 2,470 kc., 121.5 m.	
		<b>WPE</b> 2,416 kc., 124.1 m.	
		<b>WPF</b> 2,442 kc., 122.8 m.	
		<b>WPG</b> 2,470 kc., 121.5 m.	
		<b>WPH</b> 2,442 kc., 122.8 m.	
		<b>WPI</b> 2,442 kc., 122.8 m.	
		<b>WPK</b> 2,430 kc., 123.4 m.	
		<b>WPL</b> 2,470 kc., 121.5 m.	
		<b>WPM</b> 2,470 kc., 121.5 m.	
		<b>WPN</b> 2,458 kc., 122 m.	
		<b>WPO</b> 2,458 kc., 122 m.	
		<b>WPD</b> 2,470 kc., 121.5 m.	
		<b>WPE</b> 2,416 kc., 124.1 m.	
		<b>WPF</b> 2,442 kc., 122.8 m.	
		<b>WPG</b> 2,470 kc., 121.5 m.	
		<b>WPH</b> 2,442 kc., 122.8 m.	
		<b>WPI</b> 2,442 kc., 122.8 m.	
		<b>WPK</b> 2,430 kc., 123.4 m.	
		<b>WPL</b> 2,470 kc., 121.5 m.	
		<b>WPM</b> 2,470 kc., 121.5 m.	
		<b>WPN</b> 2,458 kc., 122 m.	
		<b>WPO</b> 2,458 kc., 122 m.	

# NATIONAL SHORT WAVE PRODUCTS

## Precision Type N Dial

The National Type N Dial has the mechanical smoothness and accuracy so essential for Short Wave use. It is of solid German Silver, engine-divided and equipped with a Vernier reading to 1/10 division. The planetary reduction has a ratio of 5 to 1.

List Price, \$6.75



## Short Wave Condensers

Fifty-two models! All embody the basic National features of insulated bearings, constant impedance pigtails, Isolantite insulation and non-resonant aluminum plates.

## National R39 Coil Forms

Made of the ultra low-loss material R-39, National Coil Forms insure stability, maintain calibration. Both sizes are designed for best form factor and lowest R.F. Resistance. The Standard Coil Form (4, 5 or 6 prong) is 1 1/2" in diameter, 2 1/4" long. List Price is \$.75 each. The Midget Coil Form (4 prong only) is 1" in diameter, 1 1/2" long and lists for \$.50.



## Low-Loss Coil and Tube Sockets




A point which is often overlooked in ultra high-frequency receiver and transmitter design is the efficiency of coil and tube sockets. Suitable for either standard sub-panel or base-board mounting. Made in standard 4-, 5-, 6- and 7-prong styles as well as in special 6-prong for National coils. List Price, \$.60.

## National Short Wave Choke Type R-100

Isolantite mounting, continuous universal winding in four sections. For pigtail connections or standard resistor mountings. For low powered transmitters and all types of high frequency receivers.

List Price, \$.75

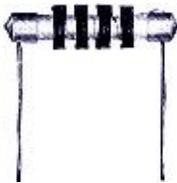

## National Transmitting Choke, Type R-152

Isolantite insulation on metal base—10,000 v. insulation; continuous universal winding in 5 tapered sections. For both high and low powered transmitters and laboratory oscillators.

List Price, \$2.25



## National Grid Grip

This remarkably convenient little Grid-Grip is easy to operate, never works loose, makes continuous electrical contact. Eliminates possibility of loosening cap on tube when removing lead. Two sizes, for broadcast tubes (List Price \$.05) and for large tubes, such as the 872 (List Price \$.10).



## Send for the Free National Catalogue No. 220

Mail the coupon below for the National General Catalogue No. 220. Its sixteen pages describe a complete line of quality parts for the amateur and constructor.

NATIONAL COMPANY, INC.  
61 Sherman Street  
Malden, Massachusetts

Gentlemen: I enclose 6c in stamps to cover mailing costs of your General Catalogue No. 220. Please mail it at once to the address below.

Name.....

Address.....

## Satisfactory S. W. Reception

(Continued from page 13)

than a year ago.

### The Directional Doublet

A study of the various types of antennas which can be erected in congested areas with the least expense and with the best possible results for the particular service required has led to the selection of one of three fundamental types, with possible variations to suit special requirements.

Where the space permits, the use of the horizontal doublet, with a transposed transmission line lead, is just about the ideal type.

This antenna is made of two single wires of equal length, run in a straight line, or 180 degrees apart, separated from each other by a suitable insulator, thoroughly insulated from their supporting elements, and as thoroughly isolated from all surrounding objects as possible. The dimensions and the general instructions for the erection of an antenna of this type are now quite generally known. The outer ends of the antenna should not come closer than twenty feet from the sides of the building which supports them. If masts are used to raise the whole system above the level of the roof, so much the better. In any event, it is safe to figure on permitting the antenna to come no nearer than twenty feet from the roof or any grounded object over which it must pass, such as barns, trees (especially in the summer, when the foliage is heavy), tin roofs, etc. If moving the antenna to one side or the other a slight amount will avoid the necessity of having it pass over some object, it is desirable to do so. There is a theoretical difference in its performance, but it will be so much better than the ordinary type of antenna that you will never miss the slight loss which the change will produce.

An antenna of this variety is quite directional. The directional properties of such a system has confused a number of old timers who have it fairly well rooted in their minds that an inverted L antenna will receive best in the direction opposite the free end. They cannot understand, if that is true—and it is—why the use of the doublet should bring in signals best in the direction at right angles to the flat-top portion of the antenna. But a doublet of this variety, whether it is a tuned or untuned, will receive best in just that manner. *In other words, if you want to receive from stations in Australia and in Europe, consulting a mercatorial map or looking at a globe will indicate that the direction from almost any portion of the United States will put Australia to the southwest and Europe to the northeast.* The best direction for the running of the antenna is, therefore, southeast and

northwest, or at right angles to a line drawn on a globe from Australia to Europe.

### Unilateral Directional Antenna

Where it is desirable to receive from a single direction, we can generally rely upon the unilateral directional properties of the inverted L type antenna, but the modern version is provided with a suitable transposed transmission-line lead. The lead is, of course, taken from the end of the flat-top from which we wish to receive. For instance, if we wish to receive from Europe, our flat-top should run in a general northeast and southwesterly direction, with the transposed transmission line lead taken from the northeasterly end. In general, the same precautions regarding the insulation and the isolation of the antenna itself should be followed as have been outlined as a guide in the erection of the directional doublet.

Some confusion exists concerning the method of applying the transposed transmission line lead to the ordinary inverted L type of antenna. It is easy enough to understand the connections when such a symmetrical system as the horizontal doublet is used, but the method of using the two wires with a single wire in the flat-top part of the system could cause mystification. As shown in Fig. 1, the antenna end of the second wire in the transposed transmission line lead goes nowhere—that is, it goes nowhere electrically. Physically, it is terminated at the opposite end of the antenna insulator, which is also the terminal for the lead-in end of the flat-top. Of course, another insulator is used to break the path from the second lead to the supporting element.

It is but natural that a rather long flat-top and its down lead, is balanced by nothing but the down lead itself. The system is partially unbalanced, but the greater part of the effect of this unsymmetrical condition is reduced by the simple process of placing a suitable resistance in each of the base positions of the two wires which go to make up the transposed transmission line lead-in, as shown in Fig. 1. In this connection, it will be found that the value of the resistance for optimum results on given frequencies will vary. It is a simple matter to incorporate a suitable resistor mount in each lead and make the necessary changes by having a suitable supply of fixed resistors on hand. Precision wire-wound resistors are not required for this purpose, and the range of resistance required is from two hundred to about one thousand ohms. Steps of one hundred ohms are usually sufficiently accurate for all practical purposes.

In many instances it will be found that there will be plenty of signal,

especially if the length and the height of the flat-top portion of the antenna system are great, so that adjustment of the resistance in series with the coupling coil is unnecessary. This is particularly true when it is possible to adjust the coupling between the transposed transmission line lead-in and the tuned circuit of the receiver to which it is coupled. In such cases, the value of the resistors which seem to function satisfactorily is in the neighborhood of 400 ohms. A very simple method of coupling a transposed lead to any sort of receiver, other than those in which the antenna coil is in a shielded can, has been treated in this series previously.

Many modern receivers are so thoroughly shielded that the use of any special coupling device is out of the question. While it is impossible to say what degree of satisfaction is to be derived from using receivers of this nature, it may be said with certainty that, while one such receiver may work better than another under identical operating conditions, it is positive that even with the poorest performer there will be a noticeable improvement in the ratio of desired signal to background noise if the following precautions are taken. It is possible, however, in some few instances, in territories which are particularly free from the noises which are produced by man-made static, and where the ground is especially good, that the advantages gained by the systems we are considering are less evident.

In any event, the changes necessary for trying the system are very simple.

The third fundamental type of antenna is one which is recommended for use in areas where the space available will not admit of the use of the horizontal doublet and where reception from all directions is desired. The mechanical details for such a system are given in the drawing, Fig. 2. The length of a flat-top of this nature does not need to be as great as the length of a single wire for picking up the the same signal voltage, but, for all practical purposes, especially where it is desirable to receive a fairly dependable signal from given stations at almost any hour, the flat tops for any of the three systems described should not be less than thirty-five feet in length.

#### Conclusions

- 1—Noise-free reception on short waves is possible and economical.
- 2—Transmission lines for broadcast and short waves are simple and inexpensive, but differ in form.
- 3—There are three general types of antennas best suited for short waves.
- 4—Stranded, insulated copper wire is better for antennas and transmission lines than solid copper or stranded alloys, such as phosphor bronze.

# Short Wave World-Wide RADIO TOURS




Natives in Bogota cheer a victory of Colombian aviators over Peruvian airmen. (Acme)



Hollanders en route to church on a Sunday morning. (Keystone View)



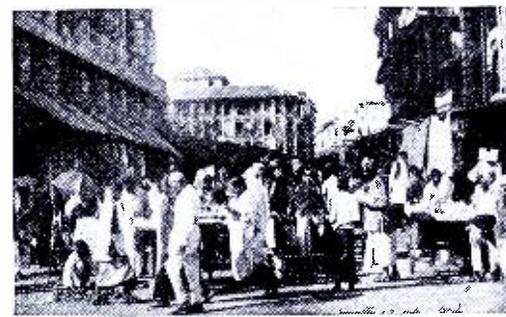A German band serenades Hitler on his birthday. (Keystone View)



Thieves' Market in Bombay, India. No questions asked as to the origin of the goods. (Keystone View)

Throw out old, worn-out radio tubes... re-tube with new Cunninghams or RCA Radiotrons—and start traveling!

GET the most out of that short-wave set of yours... you don't have to be held down to a few stations... a turn of the dial and you're traveling around the world!

Land in London for a dinner dance... hop over to Australia... or tour South America, hear tangos from the Argentine, rhumbas from Buenos Aires... hear Hitler speaking in Germany

... Mussolini receiving the Fascist salute in Rome... the whole world is yours and here's all you need to start tonight on a world-wide radio tour: a good short wave radio set with a good antenna system—plus a new set of



Cunningham Radio Tubes or RCA Radiotrons. Don't be held back by worn "stick-in-the-mud" tubes. Start a world cruise tonight with the world's finest radio tubes—the *only* tubes guaranteed by RCA. Cunningham Radio Tubes and RCA Radiotrons come to you today with five great new improvements undreamed of when most people bought their tubes.

To make your world-wide radio tour more thrilling, we'll send you a large 4-color "Radio Tours" folder with a map of the world showing all short wave stations, their kilocycles, call letters and the *actual times* when the best broadcasts are put on.

Get this exciting "Short Wave World-Wide Radio Tours" folder from your dealer or send 10c in stamps to cover handling and mailing, to RCA Radiotron Company, Camden, New Jersey.

## Cunningham Radiotron

Here's Where I Start a World-Wide Cruise via Short Wave Radio!

Please send me your 4-color illustrated folder "Short Wave, World-Wide Radio Tours". I enclose 10c in stamps for postage and handling.

Name   
Address

(Coupon must be sent to RCA Radiotron Co., Camden, N. J.)

# At Last!


## A TRULY PORTABLE 2 TUBE RECEIVER

### COMPLETE KIT OF PARTS

Here is a compact, light weight, portable, short wave receiver of real efficiency! It is entirely self-contained, including batteries and requires no outside accessories except earphones and 10 ft. aerial wire. Uses  $4\frac{1}{2}$  V. "C" battery for filament supply and a single 45 V. "B" battery for plate supply. Size overall 9" x 5" x  $6\frac{1}{2}$ ".

Complete kit of parts including easy to follow wiring diagrams less coils, tubes and batteries **\$9.84**

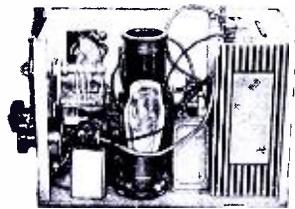Set of batteries for above **\$1.85**  
2 Lafayette No. 30 tubes **\$1.18**



### LOOK AT THESE BARGAINS



#### RCA—Victor Speaker

Equipped with channel selection switch and volume control. 2-toned walnut panel. Ornamental grille. **1.85**  
Plenty of volume.



#### Variable Air Condenser

Precision built; suited for S. W. work. 26 plates; max. cap. 500 mmf. No "skidding". Clockwise rotation  $180^\circ$ . **1.45**



#### Western Electric Headphones

One of the finest, very sensitive, adjustable, padded headband. Concealed terminals. 2000 ohms D. C. resistance. **3.95**

## BIG FREE CATALOG

We carry the world's largest stock of replacement parts for every known radio set. Buy from this great catalog which lists everything in radio. Big special section on Short-wave equipment, receivers, kits, coils, converters, condensers, antenna systems, etc., by the foremost manufacturers — always at the lowest wholesale prices!

**NOTE:— Mail orders filled from New York Office only!**

WHOLESALE RADIO SERVICE CO  
100 Sixth Avenue, Dept. S. W. R.-14  
New York, N. Y.

Send me your new free catalog No. 55.

Name .....

Address .....

City ..... State .....

**WHOLESALE RADIO SERVICE CO.**  
100 Sixth Avenue, New York, N.Y.  
New Branch  
219 Central Avenue, Newark, N.J.

## Graphite Anode Transmitting Tubes

(Continued from page 7)

reinforced against excessive warpage. A minimum of supporting metal is highly desirable from the standpoint of less occluded gases to be cleaned up during bombardment and exhaust.

Since the graphite anode has been previously purified, it gives off little or no foreign matter during bombardment. The mass is heated to incandescence or hotter than it will ever get in actual use, assuring the expulsion of occluded gases and water vapor residing in its pores. The volatilization point of pure graphite is too high to be attained in production bombardment, so that there is no sputtering or spattering of conducting particles about the tube, as is frequently the case with metal. When cooled, the graphite mass acts as a getter, having great affinity for whatever gases may still remain in the evacuated tube.

Mechanically, the graphite anode is stronger than the usual metal plates. It is rigidly mounted and supported in place by means of screws, nuts and rods. With the roughest handling, the glass and metal parts will break before the graphite anode. The contact resistance between this one-piece anode and adjacent metal is practically zero, because of the low contact resistance of pure graphite.

In operation, the advantages of the graphite anode immediately become obvious. The outstanding feature is, of course, the realization of that perfect black body as a heat radiator. The graphite anode offers 50 per cent greater heat dissipation than the usual metal plate. The glass bulb may run hotter, because the heat is radiated by the anode to the surrounding glass envelope; but the latter can withstand the heat since its function is to impart that heat to the surrounding air. The graphite anode never attains the incandescent state, as contrasted with glowing molybdenum plates even under normal operating conditions.

Due to the exceptional heat dissipation, graphite anode tubes are capable of handling higher outputs for a given rating. If desired, the tubes may be made smaller and provided with more compact glass envelopes. If operated at the indicated rating, the tubes are under comparatively little strain and can function satisfactorily for long periods. Long life is anticipated for these tubes, because (1) the tubes can be processed and aged more critically than is common practice with metallic plate tubes; (2) the tubes can be made "harder," or more highly evacuated, because of the getter action of the graphite; and (3) with harder tubes the positive ion bombardment of the filament is reduced to a minimum, which means that the thorium in thoriated filaments is consumed

at a far slower rate, resulting in longer filament life.

The operation of the graphite anode at a lower temperature than is the case in tubes heretofore available prevents primary and secondary emission from the grid, because this element is not heated excessively.

The non-warping characteristic of the graphite anode is of considerable interest to the short-wave enthusiast, engineer, and operator. With the precisely controlled frequencies in present-day short-wave amateur and commercial communications, the matter of precisely stabilized tube characteristics is of prime importance. The precision is even more marked in the ultra-short-wave band, for which the graphite anode tube appears particularly well adapted.

Reports from the field indicate the realization of the several outstanding advantages anticipated for the graphite anode tube, not only in theoretical speculation, but also in laboratory tests on our experimental tubes. Indeed, the results are sufficiently encouraging to encourage us to essay other elements of graphite in transmitting tubes, replacing still more metal. It is difficult to predict just what may be the further gain by introducing more graphite components, but it is safe to state emphatically that the graphite anode at least is here to stay.

## High Gain A. F. Amplifier

(Continued from page 6)

Tube Type	Grid-Bias Volts	Screen Volts	Peak-Output Volts†	Distortion Per Cent
37	-22.5	275	275	0.7
56	-16.5	275	255	1.1
57	-3.5	75	300	1.0
57	-3.5	75	350*	2.5*
77	-3.5	70	293	1.5

† The peak-output voltage is that measured between plates.

\* For the 350-volt output condition in the above table, the input to the 57 tubes is sufficient to cause some grid current.

In cases where the grid leak of the power tubes is limited to 100,000 ohms, the maximum output of two 57's in push-pull with plate load of 250,000 ohms is 315 volts peak with distortion of 1.8 per cent. Screen voltage of 75 volts is used. The input signal is that which will just start grid current.

Thus, if it is desired to operate two 845's in push-pull with a plate voltage of 1000 volts and grid voltage of 155 volts to provide approximately 45 watts of power, very satisfactory results would be obtained by using a pre-amplifier stage of two 57's in push-pull with a plate-supply voltage of 500 volts and a control-grid voltage of 3.5 volts. Where an amplifier is to be used in conjunction with low voltage inputs, the high gain of the 57 is a distinct advantage.—RCA Radiotron Co.

## Problems in S. W. Super Design

(Continued from page 17)

than the r.f. coils, or the oscillator tuning condenser may have a smaller capacity than the other condensers. In any case, the point is that the difference frequency is 456 k.c., which is so far beyond audibility that a beat cannot be heard. To obtain the beat therefore, connect a small external condenser across the oscillator tuning condenser and adjust it until a beat is heard. The only reason we want a beat is to be sure that the oscillator is oscillating. We could tell, of course, by means of a wavemeter; but not all experimenters are gifted with such equipment.

If we find that a beat is heard, then remove any of the auxiliary equipment used in the oscillator circuit and proceed; but, on the other hand, if you find that you cannot get a beat, then reverse the connections of the plate or grid coil in the oscillator circuit; check the coupling system between the oscillator and first detector; check all voltages and currents; be sure that there are no shorted turns on the oscillator coil; and, finally, watch those high-resistance joints. Oscillator circuits are fairly well understood, so that no trouble should be experienced on that score.

With the r.f., first-detector, and oscillator functioning normally, our next job is to line up the i.f.'s. It is well to point out at the outset that it is absolutely necessary that an oscillator be used here; you can't get by successfully without one. To adjust the i.f. stages, remove the r.f. and oscillator tubes from their sockets, and insert the two i.f. and the second detector tubes in their sockets. Change the connection of the phones from the plate circuit of the first detector to the plate circuit of the second detector.

The external oscillator should, of course, be capable of generating a reasonably strong signal at 456 k.c., our intermediate frequency. One side of the oscillator output should be grounded and the other side connected to the control grid of the first-detector tube. Set the oscillator to 456 k.c. and listen. Adjust the trimmers of the i.f. transformers until the oscillator is fairly strong, and then disconnect the lead from the oscillator to the control grid. The signal should disappear entirely. If the signal does not disappear, then the i.f. stages are picking up the oscillator externally. The remedy is to completely shield the oscillator proper and its "hot" lead going to the control grid of the first detector. Ground the shield. After the signal can be made to disappear entirely, reconnect the hot lead to the grid and tune the i.f. trimmers very carefully for maximum response.

It's a good idea to connect a milliammeter in the plate circuit of the second detector in series with the

phones; watch the meter as well as listen. If the second detector is of the power type, the meter reading will increase with signal strength; in this case a 0—10 ma. meter will do the trick. If the second detector is of the grid-leak—grid-condenser type, then use a 0—1 ma. meter; in this case, the meter reading will decrease with increasing signal strength. The advantage of using a meter is that its indications of variations are more accurate than those of the human ear, and a better adjustment is possible. The phones are desirable because the usual experimenter feels better when he's listening.

After the i.f.'s are lined up, we must go back to the oscillator again; for we haven't adjusted its tuning condenser so that the difference frequency is 456 kc. We know that the i.f. stages are all right, and we know that the r.f. stages are tuned properly; but we know nothing about the oscillator, except that it is oscillating.

Insert the r.f., first detector, and oscillator tubes in their respective sockets and, keeping the phones and the meter—if one is used—in the second-detector plate circuit, tune in the signal. Of course, if the oscillator tuning condenser is too far off, you will not hear it; but by carefully adjusting the trimmer, tuning the set after each small adjustment until maximum response is again obtained, you can tune in a signal. Remember, whether the plate milliammeter in the second-detector circuit increases or decreases depends upon the type of circuit used, as discussed previously.

When these adjustments are completed, the entire procedure should be gone over once again to insure accuracy, as sometimes a change in one circuit may affect the adjustment of another, allied circuit.

Perhaps it would be best to summarize the procedure outlined above for convenience.

- (1) Line up the r.f. and first-detector tuning circuits;
- (2) Be sure that the oscillator is working. Test by the beat method;
- (3) Line up the i.f. stages using an external oscillator;
- (4) Adjust the oscillator tuning condenser for maximum output response.

We will not discuss the audio end of the set, as audio amplifiers are so well understood that any brief discussion could only be a repetition of already published material.

When the adjustments are completed, there should be no squeals, howls or other internal disturbances to mar reception. But what if there are squeals and howls? What to do then?

The answer to that question is simple. With squeals and howls

# IMPROVE Your Radio with HAMMARLUND PARTS



**E**XPERIENCED builders don't have to be told that radio efficiency can be only as good as the parts used.

That is why Hammarlund parts have been first choice of experts since the beginning of broadcasting. They perform better and cost less in the long run.

Mail coupon for  
General Catalog "34."
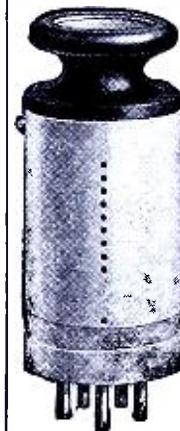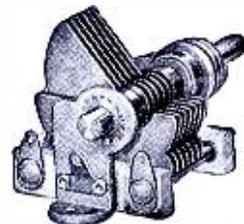
## S-W CONDENSERS

Special designs for receiving, transmitting, band-spread tuning, balancing. All types for short-wave, ultra short-wave and broadcast work. Built with watch-like precision.




## COIL FORMS & SOCKETS

Sockets have Isolantite base and perfect spring contacts, for 4, 5 and 6 prongs. Isolantite Coil Forms for Short and Ultra Short Waves. No drilling. 4, 5 and 6 prongs.


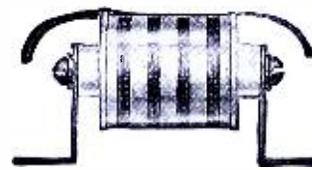
## R-F CHOKES

Compact. Low loss. All types for short-wave, ultra short-wave and broadcast receivers and transmitters.



HAMMARLUND MANUFACTURING CO.  
424-438 W. 33rd St., New York, N. Y.

Check here for General Catalog "34."  Check here for folder on "Air-Tuned" I. F. Transformers.  Check here for details of COMET "PRO" 8 to 550 meter receiver with Crystal Filter and Automatic Volume Control.

Name .....

Address .....

SR-1

There **IS** Something New

Under the Sun

# LYNCH

ANTENNA SYSTEMS  
Cut Out All Noise  
on the SHORT WAVE  
and BROADCAST Bands

WILLIAM F. BUHL

600 Bergen St., Newark, N. J.

Mr. Arthur H. Lynch, Lynch Manufacturing Co. Inc., 51 Vesey Street, New York City

August 4th, 1933

Dear Mr. Lynch:

I am just writing a few lines to tell you of the success of the installation of your doublet antenna system which I installed a few months ago, in connection with a short wave receiver.

As the location of this installation was on a highway, upon which a continuous stream of automobiles was passing in addition to street cars, the interference encountered was terrific, and at most times short wave reception was an impossibility. I may further add that not only were there street cars in front of this location, but also on each side, and it was located close to the business district. It was impossible to run an antenna at right angles to the source which is generally recognized as the best interference eliminator. Then it was decided to install the Lynch Antenna System. The results received after its installation were more than satisfactory, and it was worth far more than its purchase price. Now, a program may be listened to with ease.

Assuring you that I am fully satisfied, I am  
Yours very truly,  
(Signed) WILLIAM F. BUHL


AT ALL LYNCH JOBBERS AND DEALERS  
If your Jobber, Dealer or Serviceman cannot supply you, order direct from us. Sent postpaid, with instruction Booklet

COMPLETE KIT \$6.00

Free Descriptive Folder Upon Request

LYNCH MANUFACTURING CO. Inc.  
51 Vesey Street, New York, N. Y.  
Makers of Famous Lynch Resistors

## It Satisfies Capt. Hall!

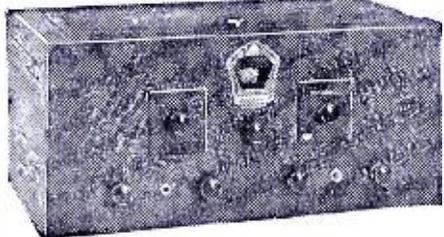

A short-wave receiver that satisfies the critical ear of Captain H. L. Hall must be a darned good set—and that set is the **POSTAL INTERNATIONAL**.

The International is a specially designed professional custom built a.c. operated or battery superheterodyne that meets the exacting demands of the most advanced short-wave enthusiasts. Consistent foreign reception is an every-day occurrence with the International, not merely an occasional accident.

The new drawer coils make wave changing quick and easy. Regular tuning or band-spreading is instantly available with the same coils by simply pulling them out or pushing them in a half inch. Four units cover the entire short-wave channels from 15 to 200 meters. Accurate single dial tuning.

### EFFICIENT CIRCUIT

Circuit uses a 58 tuned r.f. preselector stage, 58 electron-coupled oscillator, 57 first detector, two 58 i.f. amplifiers—57 second detector, 58 electron-coupled audio beat oscillator for c.w. reception, 2A5 output tube and 280 rectifier. (THE T.R.F. AMPLIFIER STAGE IS A FEATURE HITHERTO FOUND IN SETS COSTING TWO OR THREE TIMES AS MUCH.)

No straining your ears to hear foreign broadcast stations with the Postal International! This set drags them in with a volume that you never heard before. Why be satisfied with a converter or a weak set when the Postal International costs so little? Sold direct from laboratory to you.

### FREE CIRCULAR

Do not hesitate, write now for complete details and special price offer to *Short Wave Radio* readers. Just say "I'm interested," and in a day or two you will receive a pamphlet describing the Postal International, as used by Capt. H. L. Hall. There isn't any obligation whatsoever.

**Postal Radio** 135 H. LIBERTY ST.  
NEW YORK, N. Y.

present, you could not adjust the set to maximum sensitivity. Each individual squeal and howl must be eliminated one at a time; and the proper time is when making individual adjustments of the set. For instance, when adjusting the i.f. stages, be sure that when peak sensitivity is reached, none of the i.f. amplifiers is oscillating. Many men, when reaching maximum response, find a persistent oscillation. They serenely "put salt on the bird's tail" by detuning one of the transformers. Why throw away sensitivity? Eliminate the oscillation by reversing either the primary or secondary, or both, leads of one of the transformers; place i.f. filters in the plate circuit of each i.f. stage; shield the transformers or leads or tubes; or do all of these things. But don't leave the i.f. stages without eliminating the oscillation.

Another thing. Nearly all s.w. supers are equipped with a second

oscillator for c.w. reception. Of course, this same oscillator may also be used to locate carriers of phone stations. The important thing about this oscillator is that it must not disturb the adjustment of the set when turned on or off. For this reason, this oscillator is so connected that its output feeds into the i.f. stages, preferably the second. This oscillator should be thoroughly shielded, and only a small voltage removed and fed to the amplifier. In this manner, the effect of the oscillator will be nil.

Bear in mind that 456 kc. is small compared to 20,000 kc. (corresponding to 15 meters). We all know the trouble in getting broadcast supers to work, so imagine the trouble getting a super to work at 20,000 kc.

The usual precautions for s.w. work holds: shield all parts; make the leads as short as humanly possible; take your time when adjusting it; and last but not least, keep your shirt on when tuning it.

## Quartz Crystals in S. W. Supers

**B**ECAUSE of the publicity that has been given certain superheterodynes using quartz crystal filters in their intermediate-frequency amplifier circuits, many short-wave broadcast listeners have obtained an erroneous idea as to the purpose of this novel arrangement. Let us get this business straightened out and prevent further confusion.

### Idea Is Old

The idea of using a quartz crystal to sharpen the selectivity of a tuning circuit was suggested more than 10 years ago, but because of the high cost of satisfactory crystals and the fact that simpler circuit combinations were quite satisfactory for current conditions, the scheme never achieved any widespread use. Credit for the present application of the idea must be given to James J. Lamb, technical editor of QST. The congestion in the amateur transmitting channels was becoming so great that super-selective receivers were becoming a necessity. Mr. Lamb designed a remarkable short-wave superheterodyne, using a crystal filter, which possesses such enormous selectivity (expressed in cycles rather than in kilocycles), that it became known popularly as the "single signal" receiver. This set clearly separates amateur telegraph signals that in ordinary receivers are merely a hopeless jumble of noise. In some of the superheterodynes using the single signal principle, the selectivity is hundreds of times greater than in the best previous types of short-wave receivers.

The very needlepoint selectivity that makes these single signal supers so valuable for amateur telegraph reception is just what makes them undesirable for broadcast reception. The exceedingly sharp cut-off effect

on an ordinary voice or music signal removes most of the side-bands and renders the transmission wholly unintelligible. The selectivity effect may be broadened out to a point that will permit intelligible reception of at least voice, the frequency range of which is less extended than that of music, but interference on the short-wave broadcast channels has by no means reached the same point that it has on the crowded amateur bands and extreme selectivity of this kind is neither desirable nor necessary, at least at the present time.

To sum things up, it can be said that the single signal receiver is primarily an amateur communication receiver. The listener who is interested mostly in foreign short-wave broadcast reception need not concern himself about its complex technicalities.

### Used in Stenode

As a matter of fact, the late lamented Stenode receiver, which was given considerable attention in American radio publications about three years ago, was a superheterodyne using a crystal filter in much the same manner that the present amateur single signal outfits do. Of course, the great selectivity provided by the crystal filter in the i.f. amplifier lopped off a good deal of the high-frequency portion of the received signal. To compensate for this loss, the set employed a special audio amplifier which emphasized the high frequencies and which thus tended to restore a natural balance to the final music as reproduced by the loud speaker. Most American radio engineers who heard the set in operation were not greatly impressed by the tone quality, although admittedly the r.f. selectivity was of a very high order.



45 Vesey Street, New York City  
New York Headquarters for Short Wave and  
Experimental Apparatus

### NATIONAL FB-7A



**\$34.20**

FBXA \$47.70

All coil ranges,  
each \$6.00  
SW-3 All  
models \$17.70

All band spread and short wave coil  
ranges **\$3.00**

We carry a complete stock of National parts.

### The New HAMMARLUND "PRO"

with crystal filter (less tubes) **\$111.72**

with automatic volume control **\$118.86 extra**

We carry complete stock of Hammarlund  
parts.



### Navy Type Telegraph Key

List \$3.60. Navy knob— $\frac{1}{8}$ " Tung-  
sten contacts. While they last. **\$1.25**

With regular knob ..... **1.10**

Practice key on wood base ..... **.75**

LYNCH short wave antenna kit. .... **3.53**

The Radio Amateur has found it convenient  
to shop at LEEDS. Only quality mer-  
chandise at wholesale prices.

We do not publish a catalog; quotations  
on all short wave equipment furnished by  
return mail.

## 600 questions and answers covering all radio operator license examinations

This new edition of Nilson and  
Hornung's well-known book will  
help you pass examinations and  
to know your stuff better in any  
field of practical radio. Brought  
completely up to date. Enlarged  
to cover more amateur work;  
also police, aeronautical and other  
radio.



Recently Published  
1933 Fifth Edition  
Nilson and Hornung's

## RADIO OPERATING QUESTIONS & ANSWERS

389 pages,  $5\frac{1}{2} \times 8$ , Illustrated, \$2.50

EVERY question is typical of those you meet on ex-  
aminations; answers are complete, illustrated, and  
give the information essential to meet every situation.  
For amateurs, short wave fans, men who are preparing  
for operator examinations or technical positions. Users  
say, "Best of anything I have read on the subject." "One  
of the best on preparing for an operator's license that I  
have seen." "Wouldn't take \$5.00 for it now." etc.

See it on approval—Send the coupon

McGRAW-HILL ON-APPROVAL COUPON  
McGRAW-HILL BOOK CO.  
330 West 42nd Street, New York City

Send me Nilson and Hornung's Radio Operating Questions  
and Answers for 10 days' examination on approval. In 10 days  
I will send \$2.50, plus few cents postage or return book postpaid.  
(We pay postage on orders accompanied by remittance.)

Name.....

Address.....

City and State.....

Position.....


Name of Company..... SWR-12-33  
(Books sent on approval in U. S. and Canada only)

## New Raytheon RK-18 Transmitting Tube

The new Raytheon RK18 is an  
oscillator-amplifier tube designed  
particularly for use in the amateur  
high-frequency bands. It is intended  
for use in Class B modulator service  
also.

The RK-18 provides r.f. power  
output and Class B modulator per-  
formance which cannot be secured  
from the 210, although it requires  
only 750 volts for normal operation.  
Having capacities lower than the  
210, it is more suitable for use on the  
ten- and five-meter bands.

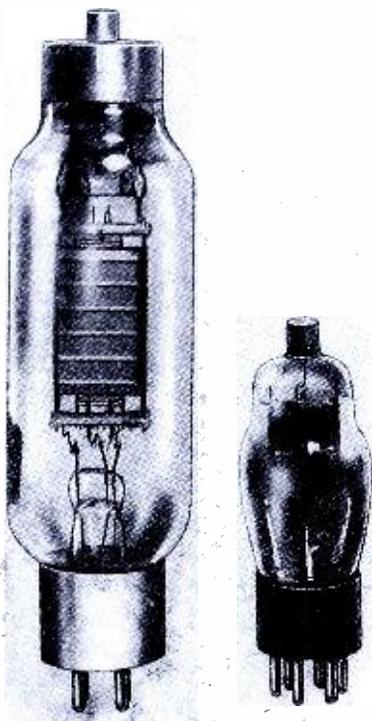The plate connection is made at  
the top of the bulb and the grid and  
filament connections through the  
usual prongs on a standard four-  
prong Isolantite base. The maximum  
diameter is  $2\frac{1}{16}$ " and maximum  
overall length  $8\frac{1}{2}$ ".



The new RK-18 (left), compared with  
a 58.

#### Operating Data and Characteristics

Filament Voltage		7.5 volts
Filament Current		1.40 amperes
Class "A" Service		
Plate Voltage	750 nominal	1,000 maximum
Grid Bias Volt.	-30	-40 volts
Amplification Factor	18	18
Plate Resistance	6,300	6,000 ohms
Mutual Conductance	2,850	3,000 ohms
Plate Current	34	36 ma.
Load Resistance	9,300	13,500 ohms
Undistorted		
Pr. Output	5.4	8.5 watts
Class "B" Service		
Plate Voltage	750 nominal	1,000 maximum
Grid Bias Volt.	-40	-50 volts
Load Resist.*	2,500	3,000 ohms
Power Output (2 tubes)	55	70 watts
Plate Dissipation per tube	25	35 watts
Max. Plate Current (peak)	210	220 ma.
Max. Eg. AC	64 RMS	70 rms.
*For two tubes, multiply by four.		
Class "C" Service		
Plate Voltage	750 max. mod.	900 unmod.
Grid Bias Volt.	-150	-150 volts
DC Plate Current	85	85 ma.
Grid Leak Resistor	15,000	15,000 ohms
RF Grid Current	5 max.	5 amps. (max.)
Plate Dissipation (per tube)	35	40 watts
Watts Output	30	35 watts

## NEW SENSATIONAL OFFER

# Learn RADIO PAY FOR TRAINING AFTER YOU GRADUATE



To a few honest fellows I am offering an  
opportunity to get a training and pay for  
it after they graduate in easy monthly  
payments. You get Free Employment Ser-  
vice for life. And if you need part-time  
work while at school to help pay expenses,  
we'll help you get it. Coyne is 33 years  
old. Coyne Training is tested—You can  
find out everything absolutely free. Just  
mail the Coupon for My Big Free Book.

## Jobs Leading to Salaries of \$50 a Week and Up

Jobs as Designer, Inspector and Tester—  
as Radio Salesman and in Service and In-  
stallation—as Operator or Manager of a  
Broadcasting Station—as Wireless Oper-  
ator on a Ship or Airplane, as a Talking  
Picture or Sound Expert—Hundreds of  
Opportunities for fascinating Big Pay  
Jobs!

## 10 Weeks' Shop Training AT COYNE IN CHICAGO

We don't teach you from books. We teach  
you by Actual Work on a great outlay of  
Radio, Broadcasting, Television, Talking  
Picture and Code equipment. And because  
we cut out useless theory, you get a prac-  
tical training in 10 weeks.

## TELEVISION Is Now Here!

And Television is already here! Soon there  
will be a demand for Television Experts!  
The man who gets in on the ground floor  
of Television can have dozens of opportu-  
nities in this new field! Learn Television  
at Coyne on the very latest Television  
equipment.

## Talking Pictures A Big Field

Talking Pictures, and Public Address Sys-  
tems offer golden opportunities to the  
Trained Radio Man. Learn at Coyne on  
actual Talking Picture and Sound Repro-  
duction equipment.

## Get the Facts

Don't spend your life slaving away in some  
dull, hopeless job! Don't be satisfied to  
Work for a mere \$20 or \$30 a week. Let  
me show you how to make Real Money in  
Radio—the fastest-growing, biggest money-  
making game on earth! Get my big Free  
book and all details of my pay after grad-  
uation offer. Mail the coupon today.

H. C. LEWIS, President  
Radio Division, Coyne Electrical School  
500 S. Paulina St., Dept. 14-5K, Chicago, Ill.


Dear Mr. Lewis:  
Send me your big Free Book; details of your Free  
Employment Service; and tell me all about your spe-  
cial offer of allowing me to pay for training on easy  
monthly terms after graduation.

Name .....

Address .....

City..... State.....
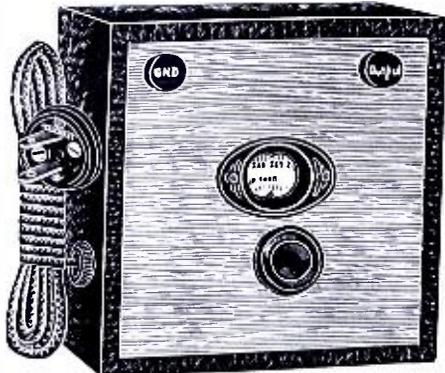
## New High Accuracy in a Commercial Oscillator



**A** NEW improvement in the Bernard Test Oscillator for intermediate, broadcast and short-wave frequencies results in an accuracy of 1%! And the dial scale is direct reading! The fundamental is 135 to 380 kc. with 1 kc. separation on the scale from 135 to 140; 2 kc. from 140 to 180, and 5 kc. from 180 to 380 kc. All the other popular intermediate frequencies are registered on the scale, including 400, 450, 456 and 465 kc. The broadcast band has divisions 10 kc. apart from 540 to 800 kc. and 20 kc. apart from 800 to 1500 kc. By harmonics, lining-up of short-wave sets can be performed. The oscillator works on a.c., d.c. or batteries and is only 5 x 5 x 3 inches (3 times size of illustration). Send \$7.50 and order Cat. 30. Sent express collect (shipping weight 5 lbs.). Price includes tube.


### "The Inductance Authority"

Wind solenoids for any radio frequency—from the fringe of audio to ultra frequencies—without any computation whatever. "The Inductance Authority," by Edward M. Shiepe, consists of complete curve-sheets for direct reading of numbers of turns for all popular form diameters and wire sizes. Accuracy 1%. Send \$2.00 for Cat. 1A (postpaid).

**HERMAN BERNARD**  
135-S Liberty St., New York, N. Y.

## The "Hg-7"

"The International Messenger"

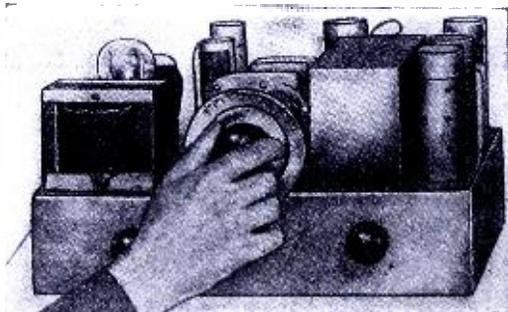

Designed and produced by men who are specialists in their fields, this strictly short-wave receiver is the last word in short-wave performance.

It is designed for those who want quality reproduction. A local oscillator for c.w. reception may be secured at slight additional cost.

May be obtained completely wired or in kit form. Either way, the receiver is complete with tubes and speaker—there is nothing additional to buy. Act now before inevitable price increases result.

The "Hg-7" in complete kit form \$57.50  
The "Hg-7" completely wired ... \$72.50

**MERCURY RADIO CO.**  
48 West Broadway, New York, N. Y.

MERCURY RADIO CO.  
48 West Broadway, New York, N. Y.

Gentlemen:  
Please send me complete data about the "Hg-7"

Name.....

Address.....

City..... State..... 1-34

## Replacing Obsolete Modulated Oscillators

(Continued from page 25)

even the 20 attained in a really good short-wave receiver r.f. stage, but it is adequate for the job. And if the 24 runs at 250 volts on the plate, we are o.k.; 180 volts is frequently enough, and to spare.

The oscillator condenser, like that of the old 1929 model shown in Part I, is solidly grounded on the front panel, via its mounting bushing. It should not be grounded elsewhere, other supports being of an insulating nature. The mechanical arrangement may be as shown in Part I, or this may be modified in various ways, one of which is suggested in Figure 5. The main idea is always to provide quite short paths and to avoid loops which look as if they might tune to five meters and/or be coupled to the tuned coil, or rather loop. As an illustration of what is meant, an oscillator arranged as shown in Figure 6 showed a bad "jump" at five meters when tuned back and fourth. The fault was found to lie in the loop consisting of the bus B, the filament bypasses C1 and C2, and portions of the tube and the tuning condenser. When the loop was turned down horizontally to decrease coupling with the tuned coil, the "jump" almost stopped. Rebuilt as in Figure 5, it worked quite well.

Again—the C and B feed leads have little r.f. voltage on them inherently; but what is to prevent their picking up voltage by induction? They run near the tuned coil, and cannot be shielded without inducing bad losses in the shielding. If they could be led off at right angles to the plane of the tuned coil, the coupling would be small. The usual test of touching the B lead and watching the plate meter for a jump is good if—and only if—we are not being deluded by having an accidental high-loss capacity between the B plus lead and chassis acting as a bypass. This will prevent the appearance of r.f. voltages (so will a bypass in the plate supply filter), but the performance is poor none the less.

### Getting Started

Start by placing a good r.f. choke in the B plus lead quite close to the stopping condenser in the tuned coil and bend it around until you find the "least coupling" location. During this stage of the proceedings, use a B plus lead that does not lie on the chassis and that is from 10 to 20 inches long before reaching a bypass to chassis. Now, any r.f. at the "back" end of the choke will be shown up very nicely by a jump of the plate-supply meter when the supposedly cold end of the choke is touched. (Look out for the d.c. and don't touch the chassis with the other hand.) Having, by means of

neon lamps, finger-touch, and plate-meter tests established the fact that the oscillator oscillates well across the five-meter band, and a comfortable distance to both sides, we are ready to advance from 1924 to 1934 by adding the buffer-stage.

This stage is coupled to the oscillator in the manner made manifest by the type-diagram, Fig 7, noting that not all of the coupling gadgets shown there are well used in all cases. The proper combinations for various tube arrays will be shown in later paragraphs. Whereas the oscillator circuit was an extreme example of the so-called "high C" type of circuit, we should use a very low-C circuit in the buffer tank if this were possible. The tuning capacity should be, perhaps, a micromike. This is not very practical, for one must waste too much time in clipping sixteenths of an inch from the coil and every change in the tube or in the position of a coupling clip would then demand another coil rebuilding. Thus, we throw the ideals clean overboard and use a 25 micromike midget tuning condenser across a single 1 $\frac{3}{4}$ " or 2" turn of a fairly heavy wire or small copper tubing, taking care of the tuning-spread in the dial by using another "velvet" microdrive dial.

### Adjusting the Set

The adjustment is simple to the last degree. The input clip is put on the "plate" side of the coil near the B plus end, the 24 operated at 90 volts screen and 180 to 250 volts plate, then the tank condenser is turned slowly while plate meter and neon lamp are watched. If nothing happens move the input clip a little closer to the "plate" end of the coil and it will shortly happen. The tuning is very sharp. Do not expect much output; it isn't needed or wanted. The amplification in the buffer is between four, as a maximum, and less than one, as a minimum. The latter should not happen, but in most tube combinations some de-amplification in this stage is harmless as there is ample "push" to start with and a de-amplifier is a perfectly splendid buffer since the coupling from input to output is obviously low.

The excitation of the final stage is a repetition of the above with the minor difference that we must adjust for a particular plate current. For plate modulation this is done by using ample grid r.f. input and changing the plate-to-load coupling until the required plate current appears. For grid modulation the coupling to the load is made rather close, and the r.f. input is carefully adjusted until the plate current has the specified value.

When it comes to modulation by

**New Raytheon Tube and New Acratest Transformers for The Amateur and Public Address Field**



**RAYTHEON RK-18**  
An oscillator-Amplifier designed particularly for use in the amateur high frequency bands. It is intended for use in Class B modulator service also. Provides RF power output and class B modulator performance which cannot be secured from the 210, although it requires only 750 volts for normal operation. Having capacities lower than the 210 it is more suitable for use on the ten and five meter bands. Standard four prong Isolantite base. Plate connection is made at the top of the bulb.  
Net Price ..... **\$10.95**



**'ACRATEST Filament Transformer**  
Heavy Duty Filament Transformer, Primary 115 v. 60 cycle. Filament windings: 25 volt—10 ampere; 10 volt—7 ampere; both center-tapped. Fully enclosed. Size, 4 1/4" x 3 3/4" x 3 1/4". Cat. No. 8312.  
Net Price ..... **\$3.90**



**ACRATEST Filter Choke**  
An extra heavy duty filter choke, for all types of power amplifiers and small transmitters. 15 Henry—300 M.A.—100 ohms, d.c. resistance. Size, 4" x 3" x 4 1/2". Universal mounting brackets. Cat. No. 8313.  
Net Price ..... **\$4.50**



**ACRATEST Plate Transformer**  
Designed especially for use with the new Raytheon RK-18 tube or type 845 tube. Heavy duty plate transformers for power amplifiers and amateur transmitters. 2400 volts c.t. at 200 mils. 115 volt, 60 cycle primary. Size, 6 1/2" x 5" x 5 1/2".  
Cat. No. 8311—Net Price **\$12.75**

**Federated Purchaser, Inc.**  
NATIONAL DISTRIBUTORS OF RADIO PARTS & EQUIPMENT  
NEW YORK CITY 75 PARK PLACE CHICAGO ILL. 1311 MICHIGAN AV.  
ATLANTA GA. PHILADELPHIA PA. JAMAICA NY. BROOKLYN N.Y. NEWARK N.J. PITTSBURGH PA.  
RICHMOND VA. ST. LOUIS MO. ST. PETERSBURG FL. ST. PAUL MINN. ST. CINCINNATI OH.  
INDIANAPOLIS IND. CLEVELAND OH. COLUMBUS OH. CINCINNATI OH. DAYTON OH.  
CINCINNATI OH. CINCINNATI OH. CINCINNATI OH. CINCINNATI OH.

**SHORT WAVE EXCHANGE**

Have you some apparatus to sell or swap, or some special service to offer to other short-wave fans? Take advantage of the low rates of this department to reach other "hams". Only 5 cents per word for amateurs, 8 cents per word for manufacturers or dealers. Name, initial and address each count as one word. Not less than 10 words accepted. Cash, money order or U. S. postage stamps must accompany all advertisements. Please write clearly.

**THE ANSWER FACTORY** has unsnarled many puzzles of amateur and commercial operators. Prompt quotations, reasonable prices. Robert S. Kruse, RFD No. 2, Guilford, Connecticut.

**FOR SALE:** Jensen 8" P.M. dynamic, for P.P. 38's, no baffle, new, \$3.00. Weston Model 301, 0-15 v. D. C. voltmeter, perfect, \$1.50. A. Bachner, 3970—48th Street, Long Island City, N. Y.

**FOR SALE:** Weston Model 617 exposure meter. Two cell, high sensitivity type. Only few months old. Condition spotless and perfect. Complete with leather carrying case and neck strap. A real bargain for some photo fan. Cost \$33. Sell \$18. Marlin Model 39 lever action .22 calibre repeating rifle, take down type. Beautiful walnut stock. Fired less than 100 times; in gun crank condition. With canvas case, complete, \$14. R. Hertzberg, c/o **SHORT WAVE RADIO**, 1123 Broadway, New York, N. Y.

the plate method, the procedure is familiar, with the difference that for once there isn't any antenna or tank meter to lie about the percentage—one must watch the d.c. plate meter and modulate until it just moves a very little on loud sounds. This is the right method on ordinary waves, too.

For grid modulation we plug the milliammeter into the grid of the final r.f. tube just discussed, and modulate by such an amount as will occasionally cause a faint movement of the meter, i.e., a twinge of grid current.

The only thing about the whole business that is the least unusual is that the set happens to be working at five meters, and is of low power.

So far we have intentionally gone light on structural details. In the next part of this story the construction of a specific set will be described.

**"Supers" in Favor**

It took the short-wave fraternity a long time to accept the superheterodyne circuit, in spite of its admitted superiority over straight regenerative circuits on the general points of sensitivity and selectivity. An enormous amount of signal amplification can be squeezed out of a regenerative tube, but the comparatively poor selectivity of single tuning circuits apparently is what finally forced short-wave fans into the complexities of the super. Now that they have been using supers for a while, they admit, rather begrudgingly, that they are really good sets after all. With short-wave stations crowding the air in increasing numbers, it certainly is desirable, if not necessary, to employ three or four tuned circuits, as the super does, in order to separate powerful stations on nearby channels.

One of the factors contributing greatly toward the increasing popularity of the super is the general improvement that has been made in the circuit itself. Instability, the curse of early short-wave supers, has been eliminated almost entirely by the design of electron-coupled oscillators and quartz crystal resonators, the latter being responsible for the "single signal" type of "ham" set.

Incidentally, the popular acceptance of the short-wave superheterodyne has also brought coil-switching arrangements back into favor. The flimsy, unreliable switches that were perpetrated two or three years ago have given way to sturdy, absolutely dependable devices that isolate the individual coils and make wave changing really easier than using plug-in coils. For certain purposes, of course, plug-in coils are still preferable, either in t.r.f. or superheterodyne sets. In some of the more advanced supers, however, the switches are so well made that no operator need ever worry about their getting out of order.




Announcing  
The New 1934  
Improved  
Prizewinner  
A.C.-D.C. S.W.  
Receiver

\$12.95  
complete with four coils

**Verified Worldwide Reception**

Completely Self Powered Latest Type 77-43 and 25Z5 Tubes—15-200 meters

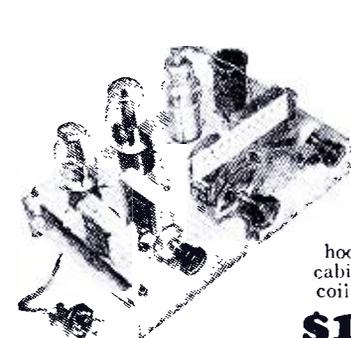**PROVISION FOR HEAD PHONES AND SPEAKER**



Complete Kit of Improved Prize winner parts, identical with those used in built-up models, including hardware hook-up, wire cabinet, dial, 4 coils.

**\$10.55**

Assembled, wired, tested and enclosed in beautiful, crackle finish cabinet, hinged cover ready to plug into your line ..... **\$12.95**  
Kit of RCA or Arcturus tubes to match ..... **3.75**  
Broadcast coil for covering from 200 to 500 meter ..... **0.90**  
220 V. A. C. or D. C. Adaptor ..... **1.75**  
Send for full particulars

**ALAN RADIO CORP.**  
83 W. Cortlandt St. New York City

**When Seeking a Radio School**

Consider RCA Institutes . . . 24 years old . . . an institution recognized as an important factor in the radio industry.

The beginner who seeks instruction in any branch of radio will find courses designed for him . . . either at the Resident Schools in New York and Chicago or the RCA Institutes Home Study courses.

Resident Schools are fully equipped—conveniently located—low weekly tuition rates.

**FEATURES OF RCA INSTITUTES HOME STUDY**

Extension courses for home study on convenient "no obligation" plan. Examination and tutorial advisory services. Free post-graduate practical training at resident school with modern equipment under instructing engineers.




Write for Catalog

**RCA Institutes, Inc.**

Dept. SR-1  
75 Varick Street, New York  
1154 Merchandise Mart, Chicago

**ALUMINUM BOXES AND CHASSIS**

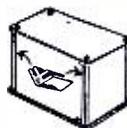

Pioneers in furnishing experimenters with special aluminum boxes, chassis and panels. Cut and made to any imaginable size. See

back issues of any radio publication for last 10 years. We can supply any chassis described in this issue of *Short Wave Radio*. Prices? Lower than anyone else! **SATISFACTION GUARANTEED.**

**Radio Amateur's Handbook**

200 pages of short wave hookups and information. Coil winding, antennas, rules, short cuts, hints, etc. Published Sept., 1932, by the American Radio Relay League at \$1.00. Now **45 cents.**

**BLAN, THE RADIO MAN, INC.**  
177 Greenwich Street New York, N. Y.



No. 651, \$2.50



No. 982, \$6.00

## Get a Globe!

A globe makes a stunning decoration for your radio table, and is very useful in tracing the path of long distance radio signals. Treat yourself to either of these two fine Hammond globes, or use them as Christmas gifts that your friends will really appreciate.

The No. 651 is six inches in diameter and stands 10 $\frac{1}{4}$  inches high overall on a graceful walnut finished stand. Sphere is of unbreakable composition, with hand mounted map. Price, only \$2.50. Add parcel post for 3 lbs.

The No. 982 is nine inches in diameter, and is mounted on a beautiful black bakelite stand, striped with silver. Map is hand mounted and is very detailed. Price, \$6.00. Add parcel post for 5 lbs.

order by number directly from

**STANDARD PUBLICATIONS, Inc.**  
1123 Broadway, New York

## Station X1G

(Continued from page 19)

This can also be used as a monitor for checking purposes. Next in line is a Hammerlund Comet "Pro" receiver. This is mostly used for the reception of short-wave broadcasting stations from the U. S. A. For all amateur reception, a Hendricks and Harvey Single Signal Super is used and it sure does pull them in. Next to the S.S. receiver is a four stage a.c. operated speech amplifier that consists of a 57 impedance coupled to a push-pull stage of 27's, followed by another stage of push-pull 27's followed by a pair of 50's in push-pull. A 500-ohm line couples this unit to the Class B modulators for 20 and 75 meters and to the Class A modulators for 160-meter operation. A Western Electric moving coil microphone is normally used.

The power supply unit for the 20- and 75-meter transmitters is located on the opposite side of the room from the operating desk and is remotely controlled by means of push buttons which actuate time delayed relays. It consists of a sturdily built rack made of one-inch channel iron divided into three shelves. The top shelf contains the power supply for the crystal oscillator and buffer stages and voltages from 300 to 900 volts are obtained. The four relays which control the various plate and filament voltages are mounted in the rear of this shelf. The 2000-volt supply for the 852's is mounted on the center shelf and consists of a pair of 872 mercury vapor tubes in a full-wave circuit. The bottom shelf contains the 1000-volt supply for the class B modulators. This whole unit is switched from the 20-meter set to the 75-meter set by means of the two multi-poled double throw switches on the front panel. An auto transformer in the primary circuit enables the operator to regulate the line voltage to compensate for the changes that are quite severe in Mexico.

A cathode ray oscillograph is mounted on the mantle above the fireplace and is used for checking up the frequency response of all the transmitters and amplifiers. An Esco motor generator unit supplies the 1200 volts for the 160-meter set and is located in an adjoining room.

With this arrangement, a complete coverage of all bands may be had and changing from one band to another can be accomplished almost instantaneously. All the above transmitting equipment was built and installed by Morton B. Kahn, who owns and operates W2KR in New York City. The frequencies of the various transmitters are 1995 kc., 3896 kc. and 14140 kc. Phone is used exclusively and as the handling of messages is prohibited by the Mexican Government the main enjoyment derived by the operation of this station is rag chewing.

## Amateur Station LOG SHEETS

Paragraph 386 of the "Rules and Regulations Governing Amateur Radio Stations," issued by the Federal Radio Commission, reads as follows: "Each licensee of an amateur station shall keep an accurate log of station operation in which shall be recorded: (a) the date and time of each transmission; (b) the name of the person manipulating the transmitting key of a radio telegraph transmitter, or the name of the person operating a transmitter of any other type, with statement as to nature of transmission; (c) the station called; (d) the input power to the oscillator, or to the final amplifier stage, whether an oscillator-amplifier transmitter is employed; (e) the frequency band used; (f) the location of each transmission by a portable station.

"This information shall be made available upon request by authorized government representatives."


Be prepared! Lay in a supply of the new and simplified log sheets, as prepared by SHORT WAVE RADIO. These are the most sensible sheets brought out to date for ham use. Plenty of space to write in all the dope required by the F. R. C. Quick and easy to use, and can be filled-in in a hurry while you are "pounding brass." Also very useful for the short-wave broadcast listener.

These new log sheets measure full 8 $\frac{1}{2}$  by 11 inches, are printed on high grade white paper that will take ink without smudging, are ready punched to fit any standard 3-ring note book binder, and are handier than bound books. You can make rough entries on one sheet, and then typewrite them on another for permanent record. This will make up a really swell log book that you will be proud to show. Nothing like these loose-leaf sheets for convenience.

Loose-leaf log sheets, package of 50, \$.50

Postpaid anywhere in U. S. A. United States stamps, Post Office and Express Money Orders accepted. Do not send coins through the mail. These log sheets are carried in stock. Your order sent out same day it is received.

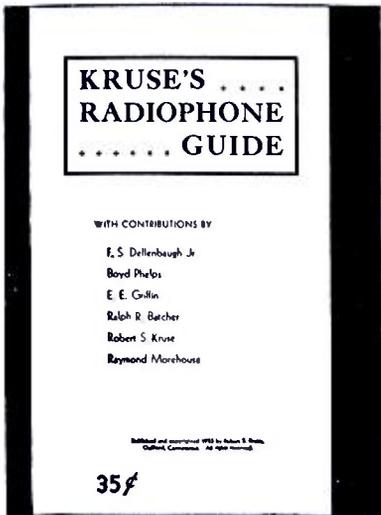Standard Publications, Inc., 1123 Broadway, New York, N. Y.



# KRUSE'S RADIOPHONE GUIDE

has been well received  
because it  
**TELLS HOW to**  
Build, Adjust, Improve,  
Economize

IN STOCK AT—

Thompson Holmes, San Francisco  
Walter Ashe Radio Co., St. Louis  
G. M. & C. Radio Sup. Co., Oakland  
Zack Radio Sup. Co., San Francisco  
Radio Specialties Co., Detroit  
Warner Bros., San Francisco  
E. C. Wenger Co., Oakland  
Leeds, New York  
Offenbach Elect. Co., San Francisco  
I. S. Cohen's Sons, San Francisco  
Neilsner Bros., Inc., Boston  
J. C. Hobrecht Co., Sacramento  
Portland Radio Sup. Co., Portland  
Griffith Sales Co., Tacoma, Wash.  
Wedel Co., Inc., Portland  
Wedel Co., Inc., Seattle  
Seattle Radio Sup., Inc., Seattle  
Lou Bonn Co., St. Paul  
Chicago Radio Apparatus Co., Chicago  
Spokane Radio Co., Inc., Spokane  
Midwest Radio Mart, Chicago  
Gross Radio, Inc., New York

35 cents at your dealer's or  
postpaid from

**Robert S. Kruse**  
RFD No. 2, Guilford, Conn.

## The Hg-7

(Continued from page 11)

on the bottom of the copper can in its usual fashion. The prongs of the coil, therefore, protrude through the wafer socket-top and shield can and slide into regular sockets mounted on the chassis. The top of the can should be removable for inspection whenever necessary. Four such cans are required, one for each wave band.


All that is necessary, then, to change wave bands is to remove the entire can and substitute another one. Another feature of this arrangement is that the front panel is not cluttered up with coil knobs, which may be used, perhaps, once or twice an evening. Also, we believe the cost of this method of construction is lower than any other equally successful coil-changing method.

The procedure used to line up the superheterodyne is not different from that of any other super. Obtain an oscillator and adjust the i.f.s. to 465 kc. Since the three-gang tuning condenser has no trimmers on it, there is no necessity for making any other adjustments. Individual antenna adjustments or individual antenna compensations are made by means of C1. The oscillator coil should have several turns removed from its secondary on the two longest wave coils. This information is given in the coil data. Although the photographs show condenser C4, the oscillator-compensator, mounted directly on the front panel, it should be pointed out that a better location, and one that has been used in the final model, is directly underneath the three-gang tuning condenser. The mechanical drawing of the chassis takes care of this. Any insulated type of bracket may be used for this purpose. A scheme used by the writer is shown in the same sketch as for the coil shield.

The proportions and directions given here should enable anyone with a working knowledge of radio to build this receiver in a few nights and have it work "right off the bat."

Announcing the
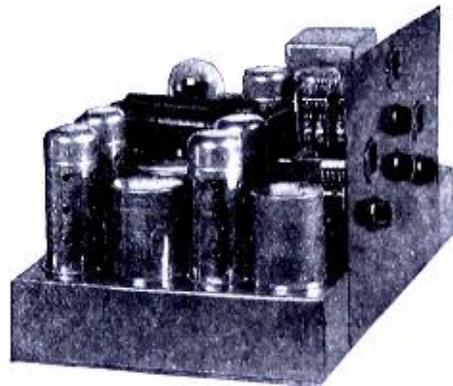
## R R L - 7 B - X Custombuilt S. W. Super 1/2 the Price!



BAND SPREAD WITHOUT PLUG-IN COILS

Before buying *any* receiver you will want to get complete particulars on the RRL-7B-X Custombuilt S. W. receiver developed by R. H. Liedtke and Associates. The RRL-7B-X Custombuilt Super was designed for the serious student of short waves who will never be satisfied with anything less than the ultimate in reception. The fan who has become weary of promises, controversial data, and extravagant advertising claims will find in the RRL-7B-X the answer to his prayers—real outstanding performance—at about *one-half the Price*. NOW, R. H. Liedtke and Associates, again pioneer with the LABORATORY "AIR TEST" PERFORMANCE RECORD. Each receiver sold is accompanied by a laboratory checked performance card, giving for all S. W. bands the actual dial settings for that particular receiver. Thus, VK3ME, Australia; DJR, Germany; a host of others and all the amateur bands, are brought in with extraordinary ease using this guaranteed method. Sold subject to refund after ten days if not satisfactory. You owe it to yourself to find out all about this remarkable new short wave set. Use the coupon.

### RADIO RESEARCH LABORATORIES

Manufacturers, Designers, Consulting and  
Experimental Engineers

2019 California Ave., Ft. Wayne, Ind.

20 Years in the Radio Electrical and Mechanical Field

RADIO RESEARCH LABORATORIES  
2019 California Ave., Ft. Wayne, Ind.

Send me complete information on the RRL-7B-X Custombuilt S. W. Receiver. (We supply all postage.)

Name.....  
Street.....  
Town..... State.....



### "KEY KLIX" IS OUT!

● Thousands of amateur radio items at the lowest prices are contained in this immense FREE book, together with many interesting articles by people well known in amateur radio circles.

Get your copy NOW!

### AMERICAN SALES COMPANY

Wholesale Radio Distributors

S-44, W. 18th Street, - New York, N. Y.

The Oldest "HAM" Supply House  
Established 1919



graphs contain statements embracing affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner; and this affiant has no reason to believe that any other person, association, or corporation has any interest direct or indirect in the said stock, bonds, or other securities than as so state by him.

LOUIS MARTIN.

Sworn to and subscribed before me this 5th day of October, 1933.

MAURICE COYNE, Notary Public.

(My commission expires March 30, 1934.)

STATEMENT OF THE OWNERSHIP, MANAGEMENT, CIRCULATION, ETC., REQUIRED BY THE ACT OF CONGRESS OF AUGUST 24, 1912,

Of SHORT WAVE RADIO, published monthly at Chicago, Illinois, for October 1, 1933.  
State of New York }  
County of New York } ss.

Before me, a Notary Public in and for the State and county aforesaid, personally appeared Louis Martin, who, having been duly sworn according to law, deposes and says that he is the business manager of the SHORT WAVE RADIO and that the following is, to the best of his knowledge and belief, a true statement of the ownership, management (and if a daily paper, the circulation), etc., of the aforesaid publication for the date shown in the above caption, required by the Act of August 24, 1912, embodied in section 411, Postal Laws and Regulations, printed on the reverse of this form, to wit:

1. That the names and addresses of the publisher, editor, managing editor, and business manager are: Publisher, Standard Publications, Inc., 4600 Diversey Ave., Chicago, Ill.; Editor, Robert Hertzberg, 1123 Broadway, New York, N. Y.; Managing Editor, Louis Martin, 1123 Broadway, New York, N. Y.; Business Manager, Louis Martin, 1123 Broadway, New York, N. Y.

2. That the owner is: (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding one per cent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a firm, or company, or other unincorporated concern, its name and address, as well as those of each individual member, must be given.) Standard Publications, Inc., 4600 Diversey Ave., Chicago, Ill.; Louis Martin, 1123 Broadway, New York, N. Y.; Robert Hertzberg, 1123 Broadway, New York, N. Y.; Irene Levine, 1123 Broadway, New York, N. Y.

3. That the known bondholders, mortgagees, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.) None.

4. That the two paragraphs next above, giving the names of the owners, stockholders, and security holders, if any, contain not only the list of stockholders and security holders as they appear upon the books of the company but also, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, is given; also that the said two para-

# why not SUBSCRIBE?

Why take the chance of missing the meaty "dope" that will be published in forthcoming issues of **SHORT WAVE RADIO**? Enter a subscription and have the magazines mailed direct to your home or office. Only \$2.50 per year for 12 issues in the United States and possessions; \$3.00 in Canada and foreign countries.

The best authors in the short-wave field will be regular contributors. Among these are Clifford E. Denton, Robert S. Kruse, Arthur H. Lynch, Capt. H. L. Hall, H. G. Cisin, and Alfred A. Ghirardi. Keep up with short-wave radio by reading **SHORT WAVE RADIO**!

## SHORT WAVE RADIO

STANDARD PUBLICATIONS, INC.  
1123 Broadway, New York, N. Y.

Here is a man-sized coupon that doesn't require a magnifying glass

Enclosed is \$..... for one year's subscription to **Short Wave Radio**. My full name and address are given at the right. (\$2.50 in U. S. and possessions; \$3.00 in Canada and foreign countries.)

Name \_\_\_\_\_

No. and Street \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Kind of Receiver \_\_\_\_\_

1-34


you must see the new

# RADIO PHYSICS COURSE

Including Short Waves, Television and Sound Pictures

(Second Enlarged and Revised Edition)

by ALFRED A. GHIRARDI

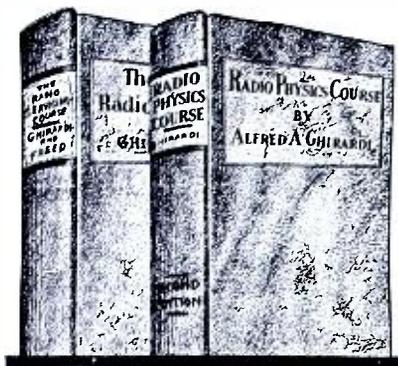

The Radio Physics Course  
contains 992 pages and  
over 500 illustrations.

Two Inches Thick!

Cloth Bound

Price

**\$4.00**

Postpaid anywhere in U. S. A.

Haven't you often felt that you would like to get hold of a book that would explain very carefully, step by step, and in a really interesting manner, everything there is to know about modern radio?

The new, revised second edition of the RADIO PHYSICS COURSE does just that—and more! It now contains, in addition to the most popular radio course ever written, a complete course in sound and electricity as applied to radio. Written in the same clear, simple style which has won the author great popularity as a writer for technical and radio magazines, and as a teacher of radio and electricity, this part of the new edition will be welcomed as a refreshing departure from the old electrical texts now in use. Free use of the modern electron theory has been made without going beyond the grasp of even the most non-technical student. You will be surprised at the ease and simplicity with which this modern tool of science, in the hands of so capable a writer as Mr. Ghirardi, has been utilized to clear up the many mysteries of electricity which have always troubled students. Electricity has not been treated as a "mysterious flow of something or other," but as a definite movement of vibrant electrons which have been skillfully made to create an absorbing interest in the subject.

Nothing is taken for granted, everything is explained simply, clearly and completely, with the aid of hundreds of carefully prepared diagrams and illustrations which the author has found invaluable in his practical experience in teaching this subject.

All chapters, including those on Vacuum Tubes, Superheterodynes, Electric Receivers, Short Waves, Television and the Talkies, have been brought right up to the minute, with complete descriptions of all the new developments brought out during the past year. We feel the chapter on Television to be the most sensible, complete and up-to-date explanation of this latest marvel of radio ever published. Even the new Cathode-ray television system is explained!

The Radio Servicing Course

192 pages, 121 illustrations.

Cloth Bound

Price

**\$2.00**

Postpaid anywhere in U. S. A.

## THE RADIO SERVICING COURSE

by Alfred A. Ghirardi & Bertram M. Freed

This new book, by both the author of the famous "Radio Physics Course" and Mr. Bertram M. Freed, should be in the hands of every Service Man, Radio Student, Teacher and Technician, for it is the most comprehensive, up-to-date book on Radio Servicing ever written. It will show you how to make money by doing radio servicing scientifically, in a logical, rapid way with proper test equipment.

*Please do not send cash through the mail. Remit by post office money order or bank check to*

*(Be sure to address your letter to the exact address given below)*

Radio Technical Publishing Co., 45-R Astor Place, New York, N. Y.

Announcing the

# Short Wave Radio HANDBOOK

By

CLIFFORD E. DENTON

*Ready this Month*

**Special price \$1.00 postpaid**

• The new SHORT WAVE RADIO HANDBOOK is the answer to the short-wave fan's prayer for a readable, understandable book that explains the mysteries of high-frequency radio without adding any mysteries of its own because of obscure technical wording. This book is not a long and exhaustive volume, but rather a concise work from which you will receive immediate enlightenment on many confusing phenomena that you encounter in your everyday radio experimenting.

• One half of the book contains explanatory text and much useful data; the other half is devoted to descriptions of a variety of new and representative short-wave receivers, designed by Mr. Denton, never before shown in print.

• Clifford E. Denton, well known to all readers of radio publications, is one of

those rarities of the publishing business—an accomplished engineer who can write on highly technical subjects in simple, lucid language, thoroughly understandable to the layman. A graduate of both Stevens and Columbia, and the holder of four degrees, his high standing as a technician is universally acknowledged, while his ability as a writer has made him widely popular with the people who find short-wave radio such a fascinating hobby.

• The book contains 128 pages and is worth its cost many times over to every radio fan. Order now and save yourself money later, as printing and paper costs are going up, and we may have to raise the price of the book.

• United States stamps, money orders and bank checks accepted. Use the handy coupon and please write clearly.

Standard Publications, Inc.  
1123 Broadway, New York, N. Y.

Gentlemen:

Enclosed is \$1.00 in U. S. stamps—bank check—postal or express money order (check form of remittance). Reserve a copy of The Short Wave Radio HANDBOOK by Denton for me and mail when ready. It is understood that I am protected against a price increase by ordering before January 1st, 1934.

Name.....

Street and Number.....

City and State.....



**Standard Publications, Inc.,**

**1123 Broadway**

**New York, N. Y.**