

THE RADIO EXPERIMENTER'S MAGAZINE

HUGO GERNSBACK Editor

SHORT WAVE CRAFT

January 1936

**WORLD'S
LARGEST
SHORT WAVE
CIRCULATION**

Jan
1936

Eng 5pm to
6 pm 1020 on



Pg 538 Transmitter very good
and easy to build little expense
Pg 546 coil data for almost all
SW sets including S. C. Doshell and
as Doshell

Pg 5-21 is the set which
I will build and add
2 stages of 3F ahead of
Pcl-





**World
Globe
No. P-100**

This beautiful floor model globe fills the demand for a globe of this type at a popular price. The 12" standard ball shows 67 prominent international short-wave stations—steamship routes, ocean currents, mountain peaks with heights, principal railroads, Lindbergh's flight and other important data will be found clearly printed on the globe.

The ball is mounted in a fully graduated, semi-meridian. The solid walnut base has been gracefully patterned to harmonize with the interior of home or office. The base is sturdy constructed.

A beautifully illustrated, 32-page book, "The Story of the Globe" is included with this model. It is full of interesting facts, including the question and answer globe-game. Height of stand, including 12" globe—34". Shipping weight—12 lbs. **\$3.95**
PRICE



**World
Globe
No. P-75**

This beautiful 7" Radio Globe, with 55 principal international short-wave stations and call letters, is attractively mounted in a half ring, with a sturdy spun steel base. The stand is finished in statuary bronze.

The highly glazed surface of this ball is scratch-proof as well as water-proof. It shows 2,500 place names; it is printed in seven, rich, beautiful colors. Important geographic information such as: Lindbergh's flight, Byrd's travels through Little America, etc., will be found on the map. Height—10". Shipping weight—2½ lbs. **85c**
PRICE

ORDER YOUR GLOBE TODAY!

SHORT WAVE CRAFT
99 Hudson St., New York, N.Y.

SWC-1-36

Gentlemen: Enclosed you will find my remittance of \$..... for which please ship me the following World Globe.

- () World Globe No. P-75 @ \$.85
- () World Globe No. P-88 @ 1.75
- () World Globe No. P-212 @ 2.95
- () World Globe No. P-100 @ 3.95

Name
Address

City State
Send remittance in check or money order—register letter if it contains cash, stamps or currency. GLOBES ARE SHIPPED FROM OUR WAREHOUSE IN CHICAGO. F.O.B. FROM THAT CITY.

Best and lowest priced **WORLD GLOBES** FOR SHORT WAVE LISTENERS

THESE remarkable, new globes printed in a variety of popular colors are indispensable to short-wave fans. Notable among the many features of these world globes, is that they give life-time service. Short-wave fans are enabled to determine correct time in various centers of the world with the aid of these globes; distances from city to city can be accurately established.

There is a graduated "Meridian" scale on many of the globes. Another feature is the moreable hour scale found at the north pole—this facilitates determining the hour in any part of the world.

You will be thrilled when you put the globe to actual use—measuring distances from New York to Moscow; from Cape Town to Tokio; from Los Angeles to Rio de Janeiro; etc. A flat map is deceptive for measuring, but take a small string and stretch it across the globe, from city to city, and you have the correct distance.

Each globe contains a listing of several thousand cities in nations all over the world—spellings conform to International geographic standards—all globes are of 1933 production. They contain such important features as: tracks of Admiral Byrd's recent voyage to Little America; Lindbergh's Paris flight; the new Japanese Empire; principal railroads; principal international short-wave radio stations and call letters; steamship routes; and other equally important data.

The colors on our fine handmade or Library globe maps are refined and delicate. Nevertheless, the two types have an essential characteristic in common—their rich color harmony, in which each color of equal strength blends into a harmonious color unit.

The map surface of all models is protected by a high, glazed, water and scratch proof finish which can easily be kept fresh and new with a damp cloth. This finish will not fade, crack or become yellow with age. The colors are sun-proof.

These globes add dignity to home, office, studio or laboratory—they are globes that everyone will be proud to own.



World Globe No. P-212

The 12" standard globe was the first to list principal international short-wave stations and call letters. On this map are printed 67 prominent short-wave stations—quickly recognized since they are printed in red. They are accurate and up-to-date.

Such data as: steamship routes, ocean currents, mountain peaks, principal railroads, Lindbergh's flight, and other useful information will be found on the globe. There are over 5,000 place names shown.

This attractive globe is highly suitable for home, studio, school or office. It is extremely low in price when compared to its beauty and utility value.

A 32-page booklet, well illustrated, entitled "The Story of the Globe" is included with this world globe. Height—16¾". Shipping weight—6 lbs. **\$2.95**
PRICE



**U. S. Army Airplane.
Dixie, Texas.**
Gentlemen:
Receipt is acknowledged of the "Short Wave World Globe" which arrived okay today and am very well pleased with same. The writer desires to thank you for attention to this.
The globe was received at our local express office this morning, in good condition. The agent had never seen one of this type, so upon demonstrating the globe to him, he fell in love with it immediately and asked for your address, saying that he would order one immediately.
(S) E. H. Buchanan,
Radio Operator.



All globes are carefully packed in original corrugated protected cartons, assuring safe delivery. ORDER BY NUMBER. Send check or money order, plus sufficient postage for delivery by parcel post. Globes are shipped from our Chicago warehouse. Register letter if it contains cash, currency or stamps. Specify if shipment is to be sent express collect. ALL ORDERS ARE FILLED PROMPTLY.

SHORT WAVE CRAFT

99 HUDSON STREET,
NEW YORK, N.Y.



I will Train You at Home in Spare Time for a GOOD JOB IN RADIO

These two fellows had the same chance. They each clipped and sent me a coupon, like the one in this ad. They got my book on Radio's opportunities.

S. J. Ebert, 104-B Quadrangle, University of Iowa, Iowa City, Iowa, saw that Radio offered him a real chance. He enrolled. The other fellow, whom we will call John Doe, wrote that he wasn't interested. He was just one of those fellows who wants a better job and better pay, but never does anything about it. One of the many who spend their lives in a low-pay, no-future job, because they haven't the ambition, the determination, the action it takes to succeed.

But read what S. J. Ebert wrote me and remember that John Doe had the same chance: "Upon graduation I accepted a job as serviceman, and within three weeks was made Service Manager. This job paid me \$40 to \$50 a week compared with \$18 I earned in a shoe factory before. Eight months later I went with Station KWCR as operator. From there I went to KTNT. Now I am Radio Engineer with WSUI. I certainly recommend the N.R.I. to all interested in the greatest field of all, Radio."

Get ready for Jobs like these. Many Radio Experts make \$30, \$50, \$75 a week

Spare time and full time set servicing; installing, operating, maintaining broadcast, aviation, commercial, police, ship and television stations. Opportunities with Radio dealers and jobbers. A service shop or re-



"I want to help you. If you are earning less than \$35 a week I believe I can raise your pay. However, I will let you decide that. Let me show you what I have done for others, what I am prepared to do for you. Get my book, read it over, and decide one way or another." *J. E. Smith.*

tail Radio business of your own. I'll train you for these and other good jobs in connection with the manufacture, sale and service of Radio sending and receiving sets, auto Radios, loud speaker systems, short wave sets, etc.

Save Money—Learn at Home. Money Back Agreement Protects You

Hold your job. I'll train you quickly and inexpensively right at home in your spare time to be a Radio Expert. You don't need a high school or college education. My 50-50 method of training—half with lessons, half with Radio equipment—gives you broad practical experience—makes learning at home easy, fascinating, practical. I will

agree in writing to refund your money if you are not satisfied with my Lesson and Instruction Service when you graduate.

Many Earn \$5, \$10, \$15 a Week in Spare Time While Learning

That's what many of my students earn in spare time while taking my course. I send you Extra Money Job Sheets containing tested plans and ideas to help you do it. Many students have made \$200 to \$1,000 in spare time while learning. Nearly every neighborhood offers a spare time serviceman an opportunity to make good money. I'll show you how to "cash in"—show you why my Course is famous as "the Course that pays for itself."

Find Out What Radio Offers You

Mail the coupon. My book is free to any ambitious fellow over fifteen years of age. It tells you about Radio's spare time and full time opportunities—about my Course, what I give you, what my students and graduates do and earn. There is no obligation. Act today. Mail coupon in an envelope or paste on a 1c postal card. Do it right now.

**J. E. SMITH, President
National Radio Institute, Dept. 6AB3
Washington, D. C.**

FOR FREE BOOK OF FACTS ABOUT RADIO

**J. E. SMITH, President, Dept. 6AB3
National Radio Institute, Washington, D. C.**

Dear Mr. Smith: Without obligation, send me in the Sample Lesson and your free book about spare time and full time Radio opportunities, and how I can train for them at home in spare time. (Please write plainly.)

NAME	AGE
ADDRESS	STATE
CITY	14X1

Get my FREE LESSON on Radio Servicing Tips

I'll prove that my training is practical, money-making information, that it is easy to understand—that it is just what you need to master Radio. My sample lesson text, "Radio Receiving Troubles—the Cause and Remedy" covers a long list of Radio receiver troubles in A.C., D.C., battery, universal, autot. T.R.F., super-heterodyne, all-wave, and other types of sets. And a cross reference system gives you the probable cause and a quick way to locate and remedy these set troubles. A special section is devoted to receiver check-up, alignment, balancing, neutralizing and testing. Get this lesson Free. No obligation. Just mail coupon.



Please mention SHORT WAVE CRAFT when writing advertisers

IN THIS ISSUE: PROMINENT SHORT-WAVE AUTHORS

Vette • Cisin • Gregor • Shuart • Palmer

HUGO GERNSBACK
Editor



Contents for January, 1936

Editorial—The Glories of Short Waves, by Hugo Gernsback	517
New S-W Sets at the German Radio Show.....	518
Solar Phenomena and Their Effect on Short Waves.....	519
How Waves Are Propagated from Different Antennas, by H. W. Secor.....	520
Improved 3-Tube DOERLE for Battery Operation.....	521
5-Meter TRANSCEIVER Uses "Midget" Tubes, by Art Gregor	522
World-Wide Short-Wave Review, edited by C. W. Palmer	524
Talking on One-Half Meter! By George W. Shuart, W2AMN	526
Short Waves and Long Raves—Our Readers' Forum.....	528
Short Wave Scouts—"Silver Trophy" Award.....	530
New Circuit Testing Unit, by William J. Vette	531
An All-Electric Amplifier and Power Supply, for small S-W Receivers, by H. G. Cisin, M. E.....	532
What's New in S-W Apparatus—2.5 and 5-Meter Super- HET	533
11-Tube "Communications" Receiver, with a Range of 1.5 to 25 mc.....	534
Practical 5-Meter Antenna Design, by Arthur H. Lynch.....	535
Radio Amateur Course, by George W. Shuart, W2AMN.....	536
The "SG3" Transmitter—Made from "Receiver" Parts, by George W. Shuart, W2AMN.....	538
\$5.00 for Best Short-Wave "Kink".....	540
Short-Wave Stations of the World, edited by M. Harvey Gernsback	541
Short Wave League—Keeping the S-W Club "Alive"!....	545
Short Wave QUESTION BOX.....	546
Short Wave Scout "NEWS".....	548
When to Listen in, edited by M. Harvey Gernsback	575
Latest Tube Developments.....	564

Features in the February Issue

- Another S-W Receiver for the Beginner, by Walter C. Doerle.
Metal Tube T.R.F. Receiver, by M. Harvey Gernsback.
5-Meter M. O. P. A. Transmitter using Three 89 Receiver-Type Tubes, by George W. Shuart, W2AMN.
Universal "Tester" for the Ham and S-W Experimenter—Measures A.C. and D.C. Voltage, Current and Resistance.
Latest Television News—including a New Mechanical Scanning System.
Talking on an "Infra-Red" Light Beam.

H. WINFIELD SECOR

Managing Editor

GEORGE W. SHUART,
W2AMN

Associate Editor



Certified Circuits

• SHORT WAVE CRAFT goes to a large expense in verifying new circuits. When you see this seal it is your guarantee that such sets have been tested in our laboratories, as well as privately, in different parts of

the country. Only "Constructional-Experimental" circuits are certified by us.

When you see our certified seal on any set described, you need not hesitate to spend money for parts, because you are assured in advance that the set and circuit are bona fide and that this magazine stands behind them.

SHORT WAVE CRAFT is the only magazine that certifies circuits and sets.

OUR COVER

"Merry DX-mas" is the title of this month's cover illustration. It incorporates the two principal Xmas thoughts uppermost in the mind of every short wave Fan and Ham—a new radio receiver for Xmas; one that can "step out" and bring in that "DX"!

COPYRIGHT, 1935, BY H. GERNSBACK

Published by POPULAR BOOK CORPORATION

HUGO GERNSBACK, President - - - H. W. SECOR, Vice-President
EMIL GROSSMAN - - - Director of Advertising
Chicago Adv. Office - - - L. F. McClure, 919 No. Michigan Ave.
Los Angeles Adv. Office - - - J. A. Kendall, Box 176, Arcade Annex
Publication Office - - - 404 N. Wesley Avenue, Mount Morris, Ill.
Editorial and General Offices - - - 99-101 Hudson St., New York, N. Y.
European Agent: Gorringe's American News Agency, 9A Green St.,
Leicester Square, London W. C. 2
Australian Agents: McGill's AGENCY, 179 Elizabeth St., Melbourne

SHORT WAVE CRAFT—Monthly. Entered as second class matter May 7, 1930, at the post office at Mount Morris, Illinois, under the act of March 3, 1879. Trademarks and copyrights by permission of H. Gernsback, 99-101 Hudson St., N. Y. C. Text and illustrations of this magazine are copyrighted and must not be reproduced without permission. SHORT WAVE CRAFT is published on the 1st of every month. Twelve numbers per year. Subscription price is \$2.50 a year in the United States and possessions. Canada and foreign countries, \$3.00 a year. Single copies 25c. Address all contributions for publication to Editor. SHORT WAVE CRAFT, 99-101 Hudson St., New York, N. Y. Publishers are not responsible for lost manuscripts. Contributions cannot be returned unless authors remit full postage. SHORT WAVE CRAFT is for sale at all principal newsstands in the United States and Canada. European agents: Brentano's, London and Paris. Printed in U. S. A. Make all subscription checks payable to Popular Book Corporation.



STUDENTS BUSY AT WORK IN LARGE COYNE SHOPS

Learn RADIO

**SEND TODAY FOR DETAILS OF MY
Pay-Tuition-after-
Graduation Plan!**

Train for Radio in 90 days, right here in the big Coyne Shops—not by correspondence—but on real Radio, Sound and Television equipment. Mail the coupon below. If you are short of money I'll send you all details of my finance plan and consider your application. If accepted, you won't have to start paying tuition back until five months from the date you start school, and then you'll have over a year to complete your payments.

Tremendous Developments Ahead in Radio and Television!

HERE is YOUR opportunity to cash in. Every day brings news of new developments in every branch of Radio and Television, with more opportunities, more jobs, and a greater future for the trained man than ever before. I consider the fellow who is ambitious enough to want to get ahead by taking my Training, worthy of my help. MAIL THE COUPON BELOW and you can prove to me that you are willing to spend just 12 weeks in the Coyne Training Shops learning Radio. Then, I'll tell you about my finance plan which has enabled many to get complete Training and pay tuition back later.

Learn By Doing In 90 Days

I don't care whether you are 16 or 45. It makes no difference to me if you don't know an oscillator from a spark coil. You don't need any previous experience or advanced education to master my Shop Training. Don't let lack of money hold you back from getting all details of my amazing plan.

MANY EARN WHILE LEARNING

If you need part-time work to help pay your living expenses and will tell us your problems we may be able to help you as we have thousands of others. Then, in 12 brief weeks, in the great Training shops of Coyne, you will learn on a wide variety of modern, up-to-date A. C. Superheterodyne sets, oscillators, analyzers and test instruments. Prepare for Amateur Broadcast, or Telegraph Radio Operator's License and to know all code and Dept. of Commerce rules for government License Examination.

TRAINING

By Actual Work

No dull books...you get individual training...real actual work with only the theory you will need. Building real radio sets,



Auto Radio Instruction

Prepare For Jobs
Like These

Here are a few of hundreds of positions in the Radio field. My free employment bureau gives you life-time employment service.

AIRCRAFT RADIO OPERATOR
SHIP RADIO OPERATOR
RADIO SERVICING
PUBLIC ADDRESS SYSTEMS
BROADCAST STATION OPERATOR
TALKING PICTURE STUDIOS
TELEVISION LABORATORY MAN

doing radio wiring and testing, trouble-shooting, repairing and servicing. That's a glimpse of how we help to make you a Radio expert, and fit you to qualify for jobs leading to the biggest pay.

Jobs - Pay - Future

"I got my present job two days after graduation, at shorter hours, and wages increased 60% over my old job," reports Arne Wiklem of Minnesota. "I have my own shop, own a real car and make fine money in the radio business," writes E. Allen of Montana. "All this is possible because I came to Coyne." And I could go on quoting from hundreds of letters of successful Coyne Trained men. What they have done, you should be able to do.

Electric Refrigeration Air Conditioning

Right now I'm including my new Electric Refrigeration and Air Conditioning course at no extra cost.



Home of Coyne Shops

This is our fireproof modern Building wherein is installed thousands of dollars' worth of Radio equipment of all kinds. Every comfort and convenience has been arranged to make you happy and contented during your Training.

GET THE FACTS

Coyne is your one great chance to get into Radio. This school is 36 years old—Coyne training is tested—proven beyond all doubt—endorsed by many large concerns. You can find out everything absolutely free. Simply mail the coupon and let me send you the big, free Coyne Book with photographs... facts... jobs... salaries... opportunities. Tells you how many earn expenses while training and how we assist our graduates in the field. This does not obligate you. So act at once.

MAIL Coupon Today for FREE! BOOK!



H. C. LEWIS, President
Coyne Radio & Electrical School
500 S. Paulina St. Dept. 16-2K, Chicago

Dear Mr. Lewis: Without obligation send me your big free catalog and all details; also tell me all about your "Pay-Tuition-After-Graduation" Plan.

Name.....Age.....

Address.....

City.....State.....

COYNE H. C. LEWIS, President
RADIO & ELECTRICAL SCHOOL
Dept. 16-2K
500 South Paulina Street Chicago, Ill.

IT IS always the well-trained man who wins out over the hordes of thousands of superficially trained and incompetent men. You are reading this magazine because you are interested in radio. Sooner or later, the time will come when you will wish to cash in on your knowledge. Your chance may come over night, and then the big and vital question will be, "How well equipped am I to fill the job?" You are in radio because you like it. You also realize that, at the present time, there are many branches of the radio art which you do not know as thoroughly as you should. Knowledge, these days, can be gotten cheaper than ever before. It isn't necessary

CUT PRICES ON RADIO BOOKS

for you to go to college to become proficient in radio. Start today, to build a REAL radio library and become acquainted with all branches of this great and growing art. In this page are listed the world's best radio books. We have combed the market for the really important books in radio; so that, no matter what branch you are interested in, you can pick out the best books that are now printed. Start now, to build a complete radio library. You do not have to get all the books at once, but make up your mind to get one book a month; so that, when your chance comes, you will be fully equipped to win out over the others not so well equipped.

IMPORTANT—All prices have been drastically reduced—many new books.

SHORT WAVE WIRELESS COMMUNICATION, by A. W. Lander and C. R. Stoner. Cloth covers, size 6½" x 9", 348 pages, 200 illustrations, 12 plates. **\$3.46**

Short wave experimenters who have grown out of 1-tube sets will revel in this book, which tells the "inner corner" of short-wave operation. A good portion of the volume is devoted to the amateur and commercial aspects of S. W. transmission.

SHORT WAVES, by C. B. Leutz and R. B. Gable. Cloth covers, size 6½" x 9", 384 pages, 258 illustrations. Price was formerly \$2.98. **NEW PRICE NOW. \$1.15**

prepaid. The biggest and most complete book on short waves covers every imaginable phase, including S. W. Superheterodynes, Television, Aircraft Radio, Ultra Short Waves, Directional Antennae, etc. The authors are famous short-wave authorities. This is the best book on Short-Wave in print today.

PRACTICAL TELEVISION, by E. T. Larmer. Cloth covers, size 5½" x 8½", 223 pages. **\$3.69**

This book explains television in full, including elementary principles, photo-electric cells, and all important types of television sets as well as basic principles of optics, images, mirrors, lenses, etc.

OFFICIAL SHORT-WAVE RADIO MANUAL, Volume 1, by Hugo Gernsbach and H. W. Seur. with 352 pages, illustrations. Flexible, looseleaf leatherette binder. Size 9x12". **\$2.00**

The one and only short-wave manual published. Contains constructional information on the most important Short-Wave Receivers, sections on S.W. Transmitters, Ultra Short Waves, S.W. Beginner's section, coil winding, A.C.-S.W. Power Packs, kinks, etc., for S.W. Experimenters, sections on S.W. Converters, Antennae, Superheterodynes, Amateur Phone Transmitters, Super Regeneration in S.W. Receivers, S.W. Therapy, S.W. Physics, etc.

ELEMENTS OF RADIO COMMUNICATION (Second Edition), by John H. Morecroft. Cloth covers, size 6 x 9¾", 286 pages, 211 illustrations. **\$2.98**

An introductory volume, written in easily understandable style, to the more comprehensive, "Principles of Radio Communication."

AUDELS RADIONIC'S GUIDE, by Frank D. Graham. Cloth covers, size 5½" x 8", 220 pages, 300 illustrations. **.89**

A practical, concise book presenting the theoretical and practical information for the proper operation, maintenance and service as applied to modern radio practice.

EXPERIMENTAL RADIO, by R. R. Ramsey, Prof. of Physics, Indiana University. Cloth covers, size 7½" x 9¾", 256 pages, 168 illustrations. Price **\$2.69**

A marvelous book for the experimenter. Experiments galore in easy comprehensible language.

THE RADIO AMATEUR'S HANDBOOK, (New Revised Edition), by A. Frederick Collins. Cloth covers, size 5¾" x 7¾", 394 pages, 116 illustrations. **\$1.97**

If you wish to become a radio amateur (radio ham) this book tells you how. Everything in receiving and transmitter sets and how to build them.

RADIO THEORY AND OPERATING, by M. T. Loomis. 5th revised Edition. Cloth-bound; size 5¾" x 8½", thick; 1,000 pages; over 800 illus.; 450 review questions and answers. **\$4.38**

Written in textbook style, a tremendous amount of useful information has been crammed into this thin-paper, compact reference work. Radio transmission and reception have been covered, "from soul to nuts." A truly great book.

SHORT WAVE RADIO HANDBOOK, by Clifford E. Denton. Paper covers, size 6½" x 8½", 128 pages, 150 illustrations. **\$1.00**

Coll data, circuit data, testing data, I.F. and A.F. amplifier data—in fact, let us say, "data of every imaginable sort"—in connection with short-wave radio reception.

DRAKE'S CYCLOPEDIA OF RADIO AND ELECTRONICS, by H. P. Manly. Cloth covers, size 6½", 1950 pages, 1950 illustrations. **\$4.88**

The largest work of its kind ever put between two covers. New and up-to-date; a standby for every radio man.

FUNDAMENTALS OF RADIO, by R. R. Ramsey, Professor of Physics, Indiana University. Cloth covers, size 9¾" x 6", 372 pages, illustrated. **\$3.46**

Price prepaid. **\$3.46**

The backbone of the radio art. This book gives you the foundation on radio from A to Z.

OFFICIAL RADIO SERVICE MANUAL, Volume 4, by Hugo Gernsbach and C. Walter Palmer. Flexible, looseleaf leatherette cover, size 9x12", over 3,000 illustrations, over 1,000 pages. Printed on thin Bible paper. Price prepaid. **\$5.86**

This 1935 Manual is the most authentic and elaborate service guide ever used in the radio field. There has never appeared such a complete radio manual as this one.

OFFICIAL RADIO SERVICE MANUAL, Volume 5, by Hugo Gernsbach and C. Walter Palmer. Flexible, looseleaf leatherette cover, size 9x12", over 3,000 illustrations, over 1,000 pages. Printed on thin Bible paper. Price Prepaid. **\$5.86**

This 1935 Manual is the most authentic and elaborate service guide ever used in the radio field. There has never appeared such a complete radio manual as this one.

EXPERIMENTAL RADIO ENGINEERING, by John H. Morecroft. Cloth covers, size 5¾" x 8", 246 pages, 145 illustrations. Numerous tables. Price **\$2.47**

This textbook gives you the fundamentals of electricity as applied to radio. It equips you for further study in the field of radio.

RADIO CONSTRUCTION AND REPAIRING, by James A. Moyer and John F. Wostrel. Cloth covers, size 5¾" x 7¾", well illustrated, new revised fourth edition, containing 444 pages, still remaining at the same price. **\$2.50**

A handbook that every radio set tester and general student must have. The diagrams alone are worth the price of the book.

THEORY OF VACUUM TUBE CIRCUITS, by Leo James Peters. Cloth covers, size 6½" x 9", 226 illustrations, 226 pages. **\$2.98**

It is one thing to "connect green lead No. 1 to pink lead No. 4," but it is another to know why the connections are made. Read this book and learn the design factors in tube circuits.

PRINCIPLES OF RADIO COMMUNICATION, by J. H. Morecroft, Prof. of Electrical Engineering, Columbia University. Cloth covers, size 9¾" x 6", 988 pages, profusely illustrated. **\$7.35**

THE radio classic, by the dean of radio. Covers entire radio art as does no other book.

We herewith present the most complete collection of recent important radio books. We have, after an exhaustive study, selected these volumes because they represent the foremost radio books of their kind in print today. There is such a great variety that we are sure it will satisfy any taste as well as any requirement that the student of radio might have.

We publish no catalog and ask you to be kind enough to order direct from this page. Prompt

shipments will be made to you direct from the publishers. We merely act as a clearing house for a number of radio publishers and OUR PRICES ARE AS LOW OR LOWER THAN WILL BE FOUND ANYWHERE. Remit by money order or certified check. Register all cash.

RADIO ENGINEERING HANDBOOK, by Keith Henney. Flexible leatherette, size 4½" x 7", 581 pages, 482 illustrations. Price **\$4.88**

Each of the 23 sections has been written by a specialist. Includes valuable data on talkies and short waves.

RADIO SERVICE MAN'S HANDBOOK WITH ADDENDA DATA SHEETS. Flexible covers, size 9x12", 200 pages, 400 illustrations. Price **\$1.49**

The Service Man's standby. Contains the latest practical information on radio servicing.

HOW TO PASS U. S. GOVERNMENT RADIOS LICENSE EXAMINATIONS, by R. L. Duncan and C. E. Drew. Flexible covers, size 9¾" x 6", 170 pages, 92 illustrations, appendix. Price **\$1.89**

The most important book on the subject ever published. Gives every conceivable angle which will help you to pass a radio license examination successfully.

RADIO RECEIVING TUBES, by Moyer and Wostrel. Cloth covers, size 7½" x 5¾", 298 pages, 181 illustrations. Price **\$2.47**

One of the finest books on vacuum tubes. Everything worthwhile on the subject treated in a masterful manner.

PHOTOCELLS AND THEIR APPLICATION, (Second Edition), by V. K. Zworykin and E. D. Wilson. Cloth covers, size 5½" x 8", 332 pages, 180 illustrations. Price **\$2.88**

Does this book tell you why and how to use light-sensitive cells? The answer is that the first edition was a "sell out," and the second edition brought right up to date, is even a better volume. Enough said.

ELECTRONICS, by R. C. Hudspeth. Cloth covers, size 6½", 131 pages, 45 illustrations. Price **\$1.95**

"This book is written for the reader who may wish to know something about what is going on and who has not heretofore given the matter much attention," says the author. Read it and learn how dry rectifiers, vacuum tubes, batteries, television tubes, and other apparatus work; get the "low down" on electrons and atoms.

MODERN RADIO SERVICING (2nd Revised and Greatly Enlarged Edition of Radio Servicing Course) by Alfred A. Ghirardi. Cloth covers, size 8 x 6", 1300 pages, over 700 illustrations. Price **\$4.00**

One of the greatest text books on radio servicing. Contains hundreds of facts on up-to-date servicing methods—construction and operation of latest test equipment, auto radios, all-wave receivers, etc.

RADIO ENGINEERING, by George E. Sterling and Robt. N. Russel, E.E. 2nd enlarged edition. Cloth covers, size 6½", 700 pages, 425 illustrations. Price **\$5.88**

Not a book for the beginner in radio, but a reference volume for the technician who wants modern information on the design and use of hand-selectors, automatic volume control, diode detectors, and circuit arrangements which have been recently developed.

RADIO OPERATING QUESTIONS AND ANSWERS, (Revised Fifth Edition), by Nilson and Hornung. Cloth covers, size 5½" x 8", 390 pages, 96 illustrations. Price **\$2.47**

Contains over 600 questions and answers covering all phases of licensed radio operation. Revised to contain much new material. Nothing better in print.

RADIO PHYSICS COURSE (2nd enlarged edition), by Alfred A. Ghirardi. Cloth covers, size 7½" x 9¾", 992 pages, 510 illustrations, numerous tables. Price **\$3.89**

The finest and most popular book on electricity and radio. Each subject is clearly discussed, with the aid of dozens of excellent drawings. Chapters on talkies, television, electronics and service work, etc. Biggest buy in radio.

5 METER RADIODTELEPHONY, by Frank Jones. 52 pages, 89 illustrations. Price **.25**

Here you learn to construct a variety of 5 meter transceivers and antennas. Written by the designer of the 5 meter equipment for the San Francisco Bay Bridge.

PRINCIPLES OF RADIO, by Keith Henney. M. A. Cloth covers, size 8½" x 5¾", 478 pages, 306 illustrations. Price **\$3.46**

A marvelously written textbook with the latest radio principles, including screen grid and pentode, amplifiers, etc.

NEW LOW PRICE RADIO BOOKS

Here are 14 new, up-to-date books on every conceivable radio subject, just published. Modern in every sense. ALL BOOKS UNIFORM from 64 to 72 pages; 50 to 120 illustrations. All books written by well-known radio authors. Order by Number.

No. 1 **RADIO SET ANALYZERS**
No. 2 **MODERN RADIO VACUUM TUBES**

No. 3 **THE SUPERHETERO-DYNE BOOK**

No. 4 **MODERN RADIO HOOK-UPS**, by R. D. Washburne

No. 5 **HOW TO BECOME A RADIO SERVICE MAN**

No. 6 **BRINGING ELECTRIC (RADIO) SETS UP TO DATE**, by C. E. Denton

No. 7 **RADIO KINKS & WRINKLES** (for Experimenters)

No. 8 **RADIO QUESTIONS & ANSWERS**, by R. D. Washburne

No. 9 **AUTOMOBILE RADIO & SERVICING**

No. 10 **HOME RECORDING AND ALL ABOUT IT**, by Geo. J. Saliba

No. 11 **POINT-TO-POINT RESISTANCE MEASUREMENTS** by C. E. Denton

No. 12 **PUBLIC ADDRESS INSTALLATION AND SERVICE**

No. 13 **HOW TO BUILD AND OPERATE SHORT WAVE RECEIVERS**, by the Editors of SHORT WAVE CRAFT

No. 14 **HOW TO BECOME AN AMATEUR RADIO OPERATOR**, by M. F. Eddy

PRICE PREPAID EACH BOOK **.45**

PRICE PREPAID FOR ALL 14 BOOKS **\$6.00**

HOW TO ORDER We cannot ship C. O. D. Our prices are net, as shown. Some of the books sent prepaid (In U. S. only). Those that are not thus listed will be shipped by express collect if sufficient postage is not included by you.

FOUNDATIONS OF RADIO, by Rudolph L. Duncan. Cloth covers, size 5½" x 8", 246 pages, 145 illustrations. Numerous tables. Price **\$2.47**

This textbook gives you the fundamentals of electricity as applied to radio. It equips you for further study in the field of radio.

EXPERIMENTAL RADIO ENGINEERING, by John H. Morecroft. Cloth covers, size 5¾" x 8", 346 pages, 250 illustrations. Price **\$3.46**

A student's book; devoted to the principles of radio apparatus; intended to accompany a course in electricity. The best of its kind.

RADIO PUBLICATIONS

97 Hudson St.

New York, N. Y.

Please mention SHORT WAVE CRAFT when writing advertisers



The Glories of Short Waves

An Editorial By HUGO GERNSBACK

● EVER since the beginning of radio, there has been woven about this art a particular romance which has kept increasing as the years went by. The thrills that humanity got when the first important SOS was flashed from mid-ocean and heralded the rescue of many lives, fired the popular imagination as very few events had done heretofore. Then, the very idea of communication through free space without even wires, made for romance in itself. Finally, the spoken word hurled across hundreds of miles, and lately over thousands of miles regularly by short waves—all this has helped to bring glory to the art of radio and, particularly, to short waves.

But then, it should never be forgotten that we are still at the very beginning of radio in general. Our instruments and apparatus are still very crude. We are still groping around in the dark. Most of the basic facts in radio we do not know.

David Sarnoff, president of the Radio Corporation of America—easily the most dynamic figure in radio today—is one who holds these views.

In mid-ocean last month, while Mr. Sarnoff and the writer were discussing radio, Mr. Sarnoff proposed the question, "What," said he, "is radio's biggest asset?" I ventured the opinion that perhaps radio's greatest asset lay in short waves.

"No," replied Mr. Sarnoff. "RADIO'S GREATEST ASSET LIES IN OUR IGNORANCE OF ITS FUTURE."

You have to let this statement sink into your consciousness for a while, to appreciate its real importance. Mr. Sarnoff, of course, means that, since we are ignorant of what the future holds for radio, we cannot tamper with it and work mischief with something yet unknown. He also means that the future of radio holds much more than the past, a thing on which probably all of us agree with him. Further Mr. Sarnoff believes that some day in the future you will be enabled, by means of a wrist-watch short-wave radio, to talk with your wife in China; if she does not answer, it will mean that she is not wearing her wrist-watch radio, or that she is incapacitated.

Mr. Sarnoff is quite serious when he talks in this fashion and, while our present-day radio engineers may not be able to conceive the instrumentalities by which this will all come about, there is no question that we are headed exactly toward this goal.

Consider the fact that, when Marconi in 1901 sent his first letter "S" across the Atlantic, it required 10 kilowatts, or over 13 horsepower to do it. Machines weighing many

tons were necessary to generate this power. In addition to this, it required a fearful array of radio masts, with tons of copper wire, to send the signal across the Atlantic. Then, in Newfoundland, the Marconi operators picked the weak signal from the air on a 400-ft. wire suspended from a kite.

This performance makes any 14-year-old radio experimenter smile today because, with a little transmitter requiring a few dry cells, and an aerial strung around his own living room, he can now call up his friends at the Antipodes and get back an answer in a few seconds. The entire equipment need not weigh more than ten pounds, and the power is less than that of a 60-watt electric light bulb. In other words, in 34 years we have achieved the result whereby instead of using hundreds of tons of equipment, a few pounds give us much better results, so far as radio is concerned.

What will the resulting picture be in the future, when we have Mr. Sarnoff's wrist-watch radio? Here we will have a little instrument, small enough to actually slip onto your wrist, containing a few tubes, the battery perhaps being carried in your pocket. The tiny loudspeaker is also the "microphone." When you wish to talk, you

press one button; when you wish to hear, you press another button. The wavelength adjustment will be done automatically. Yes, and it probably will be crystal-operated too, in order that you shall "stay on your frequency," so that you will not clash with Tom Jones, who a half mile away from you, is talking to his wife—who may be in mid-ocean on a pleasure trip. The transmitting and receiving antenna for the wrist-watch radio will be concealed, right on your own person, it being only a strip of flexible wire sewed into your suit—or dress if you are a lady—when the suit or dress is first made by the tailor.

Will you be talking directly to your wife in China? Perhaps not at first. You will be sitting in your automobile, talking with the nearest telephone central, who will make the direct connection to China, and thence, by short waves, to your wife. The parallel to this is when you are on a steamship in mid-ocean today, and call up your home in Chicago. You do not talk by short waves direct to Chicago. The ship operator makes connection to a receiving station at some point on the Atlantic seaboard, and then your voice impulses go by wire to Chicago.

Perhaps it will be possible some day for all human beings to communicate with each other directly, without intervening telephone wires, but that will come much later.

Radio's Greatest Asset:

"Our ignorance of its future."

—David Sarnoff

SHORT WAVE CRAFT IS PUBLISHED ON THE 1st OF EVERY MONTH

This is the January 1936 Issue—Vol. VI, No. 9. The Next Issue Comes Out January 1.

Editorial and Advertising Offices, 99-101 Hudson Street, New York City

New S-W Sets at the German Radio Show


A number of interesting new S-W apparatus, including television sets were exhibited at the German Radio show. An S-W converter, also new tubes with "wing" contacts were exhibited, and a new type of flywheel dial.



An Interesting 4-tube German superhet


The tuning knob of this set, a great hit at the recent Berlin Radio Show (see right side of the cabinet below), drives a heavy flywheel, which is connected with a gearing system with the large ratio of 1 to 150. The knob on the left side operates the tone and volume control. In case the radio listener wants to switch over to a station to be found on a distant part of the tuning scale, he puts the flywheel in full swing, and a small blue ball is used as an indicator, the ball moving very fast over the scale.

If the blue ball is near the desired scale division, the flywheel is stopped and the final exact tuning is done by means of the gearing which moves the ball very slowly over the scale. It might be of interest to note that the manufacturer of this 4-tube superhet claims that this set has nine tuned circuits. That means, according to the German advertising custom, not nine tuned circuits in a band-filter manner, but involves all the primary and secondary windings of the I.F. transformers.

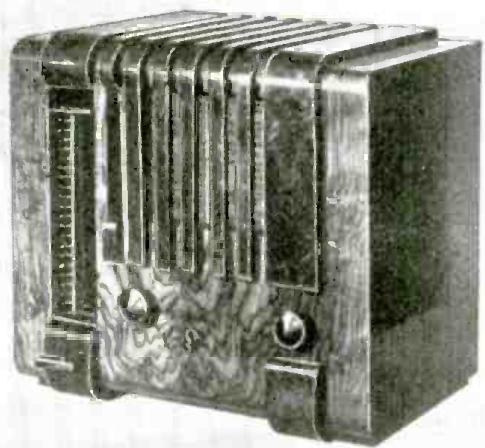


German short-wave converter: One of the new short-wave converters, furnished with an autodyne circuit. These converters are to be used for the reception of television signals by means of the regular short-wave receiver.

Below: Newest Telefunken S-W receiver.


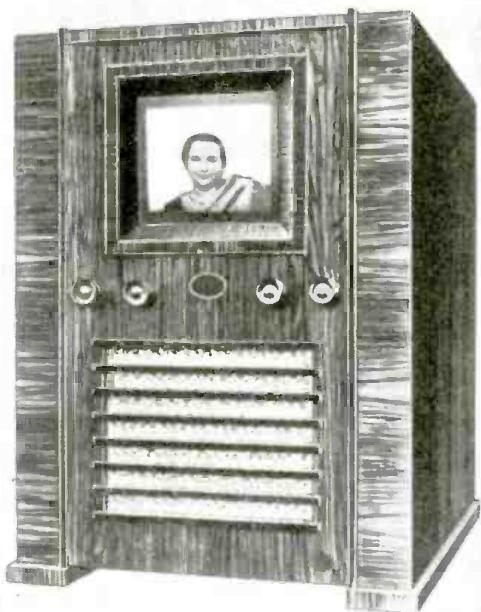


Above: Modern German television set. The new television receiver as produced by C. Lorenz, A.G., operates with a cathode ray tube. The screen size is about 8 inches.

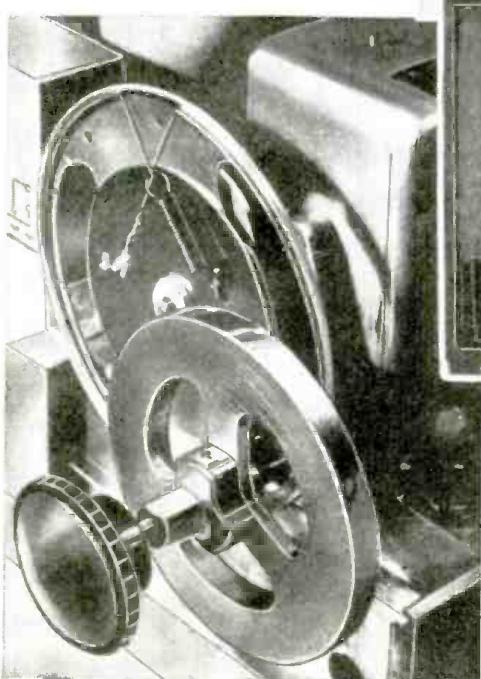
The image shown is not faked as is often done, through the incorporation of a photo in the receiver screen window, but is an actual image received by television, showing the announcer of the Berlin television station, Miss Ursula Patzke.



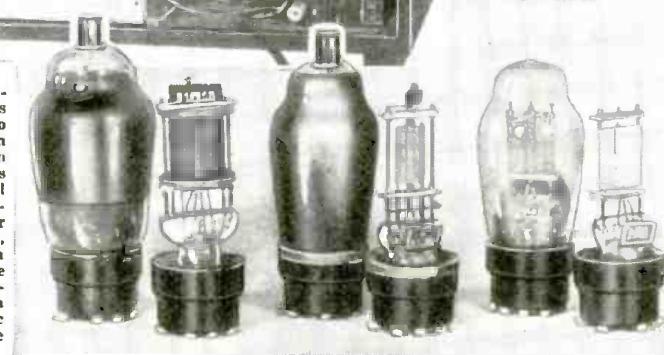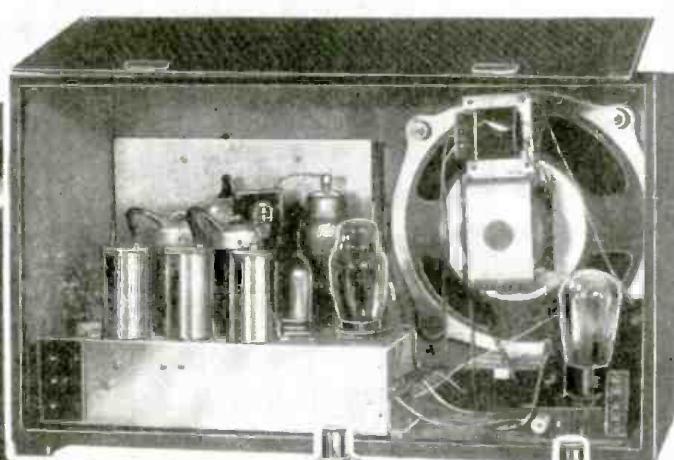Left: The heavy flywheel in front drives a gear having a ratio of 1 to 150, which in turn is connected with tuning condensers closed by the metal box in the background. The indicator of the tuning scale, which cannot be seen since it is fixed on the left side of the chassis, is operated by a cable drive. This cable lies in a groove around the wheel.



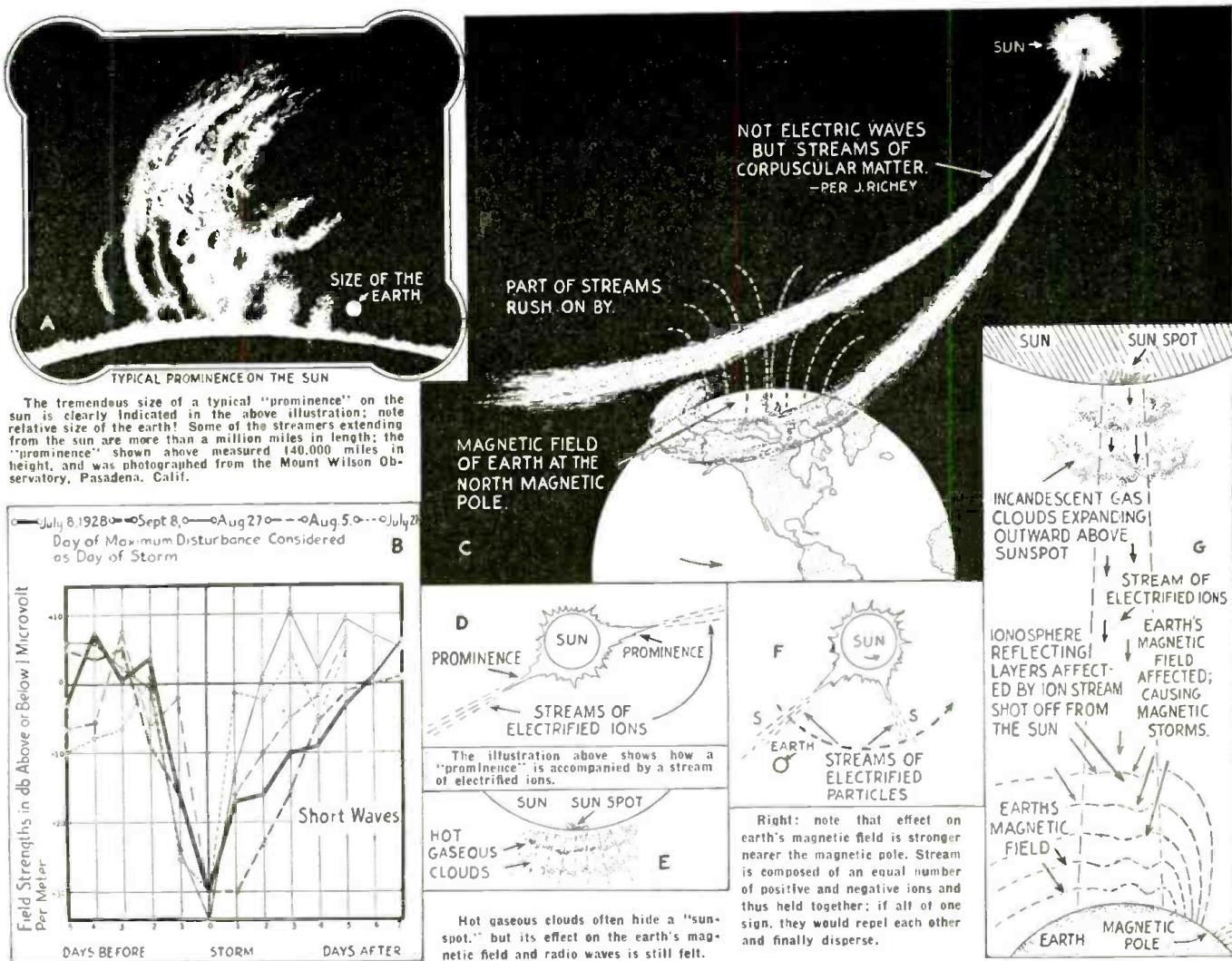Below: The new German tubes with wing contacts instead of pins.



Streams of electrified particles shot off by the sun, in the region of the spots, sweep across the earth and cause "magnetic storms." These storms markedly reduce short-wave transmission ranges.

Solar Phenomena and Their Effect On Short Waves

● SUNSPOTS, which are the most conspicuous of solar phenomena, have a far-reaching influence on radio transmission, especially short-wave propagation, and the technical people in charge of the short-wave telephone circuits in daily operation across the ocean, between the United States and Europe as well as other parts of the world, have made a special study of solar disturbances and their periods of recurrence. It is somewhat difficult to believe that the sun, some 93,000,000 miles distant from the earth, can cause magnetic disturbances on the earth of such magnitude that during periods of strong sunspot activity, short-wave transmission across the Atlantic, for example, may be entirely disrupted. At the same time, long wave transmission, such as that employing 5,000 meter waves, usually improves in the daytime, so far as transmission is concerned. One of the accompanying graphic charts illustrates an actual case of high sunspot activity when the short-wave transmission fell off markedly, while the long-wave transmission actu-

ally improved during this period. What effect do Sunspots have on Short-Wave transmission—and why? Is the range of Long Waves increased? What is the length of the average sunspot cycle? These and other questions are answered in this article.

A great deal of special study regarding the effect of sunspots, their cycle of recurrence, and the probable method whereby they affect short-wave transmission so markedly, has been made by Joseph L. Richey, chief technical operator of the Trans-Atlantic Control Room of the A. T. & T. Co., in New York. Elaborate records of solar activities and their day-to-day effects on short as well as long waves

are kept and studied carefully.

The rotation period of that part of the sun in which sunspots most frequently appear, is about 27 days. This rotation frequently causes a variation in short-wave transmission efficiency on the earth, for the reason that the electrified particles radiated from the sun in the region of high sunspot activity, will sweep across the earth every time the sun makes one revolution. If the activity producing a certain spot or spots on the sun should subside while the sun is making one rotation, then the next time the spot comes around into a position where it faces the earth, there may not be much of a terrestrial effect noticed. Another peculiar thing about the effect of sunspots and the radiations of electrified particles shot out from the sun, which cause magnetic disturbances in the earth's field, and markedly affect the transmission of radio waves, particularly the short ones, is the fact that effects of this nature have been observed when apparently very few or no spots have

(Continued on page 559)

How Waves are Propagated

From Different Antennas

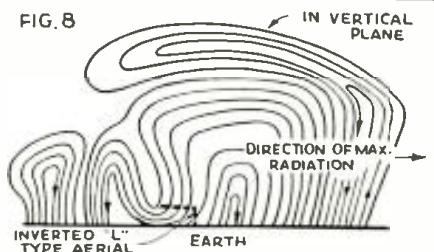
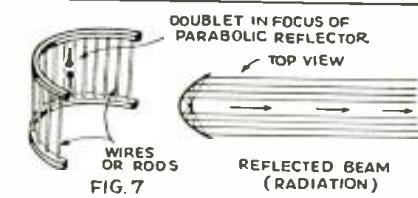
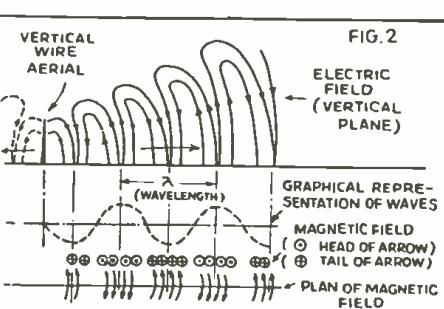
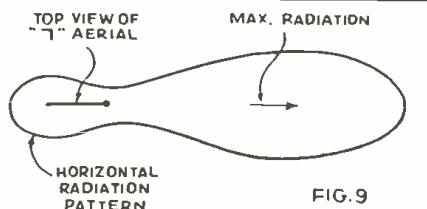
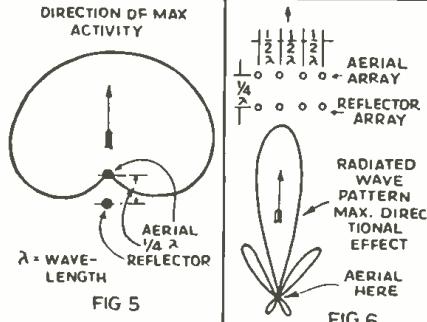
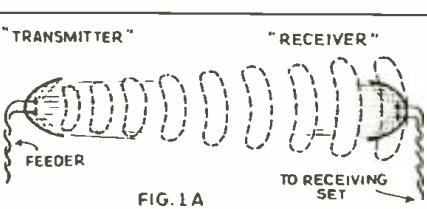
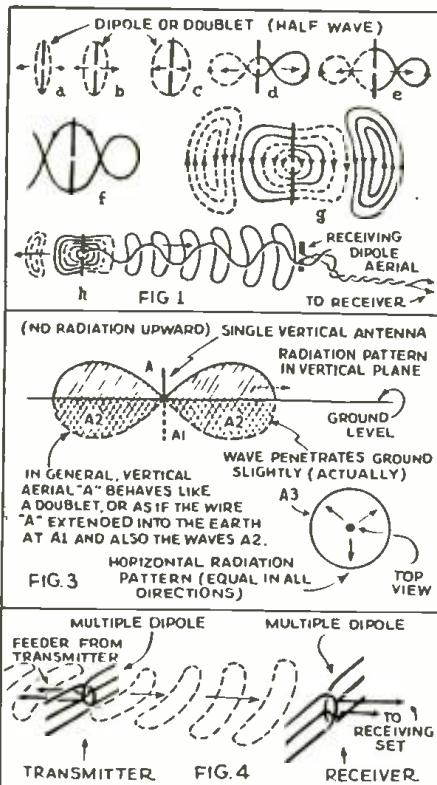


Fig. 1 shows progressive development of electric field about a half-wave doublet. 1A shows waves passing from doublet placed in a reflector to a receiving doublet also mounted in a reflector. Fig. 2 shows formation of waves about a vertical antenna. Fig. 3 shows vertical and horizontal radiation patterns for a vertical grounded antenna. Fig. 4 shows radiation from multiple dipole aerial. Fig. 5 illustrates horizontal radiation from aerial with a reflector one-quarter wave behind it. Fig. 6—Directive horizontal radiation from aerial array with reflector one-quarter wave behind it. Fig. 7—Concentrated beam from a reflector made of wires. Fig. 8—Vertical and horizontal radiation patterns about an inverted "L" aerial.

THE wide popularity of short waves today has caused many students of the subject to ponder the subject of short-wave propagation and the accompanying drawings have been prepared to provide the layman with a possible explanation of the mystery.

While the doublet antenna, commonly comprising two equally balanced arms or radiator elements, as shown in Fig. 1, (a half-wave doublet is illustrated) is mostly used in short-wave work for receiving the signals, (usually each arm is one-fourth wave long) it has also been employed for transmitting purposes, especially in the case of ultra-short waves a fraction of a meter long. In some of these applications, where waves only 1.3 meters long are employed, (a 56-mile link is in daily operation between two islands of the Hawaiian group) the transmitting and receiving aerials used until recently were small dipoles or doublets, placed in the focus of reflectors. The doublets were so-called half-wave units, each half of the doublet being one-fourth wave long. Recently a multiple dipole aerial has been substituted for the dipoles and parabolic reflectors. It is interesting to study the progressive development of a wave, as shown at A, B, C, D, etc., in Fig. 1 and to note how a detached loop or free space wave is finally whipped off the antenna, which phenomena occurs as the electro-static waves and their magnetic components continually form and expand on the doublet, similar to the effect of dropping a pebble into smooth pool of water.

(Refer to the October issue for charts showing simple explanation of how waves are formed.)

In Fig. 2 we see a number of interesting factors concerned with the production of radio waves about a vertical antenna. The first striking thing that will be noted from the diagram is that it has no radiation directly overhead. The waves spread progressively outward from the vertical antenna wire. As explained by several different authorities in a discussion of aerials, it is best to consider the vertical grounded aerial as a doublet, the wave generation and propagation being similar to Fig. 1, excepting that in the case of Figs. 2 and 3 the lower half of the wave, shown by dotted lines at A2, A2 does not penetrate into the ground as shown, but theoretically it can be considered that it does so. In this way a clearer conception of the shape of the wave radiated from the antenna is obtained. The diagram A3 in Fig. 3 shows the horizontal radiation, equal in all directions, looking down at the top of a vertical antenna.

The same rule holds for the vertical antenna where it is employed for reception, i.e., it receives equally well from all directions and manifests no directional characteristics in the horizontal plane.


Looking at Fig. 2 for the moment, we see that the electro-static waves move along horizontally outward from the antenna, the magnetic components of each wave being at right-angles to the electro-static field. The meaning of wavelength is also shown in Fig. 2, and the circles indicating the magnetic field are shown with dots and crosses, the dots within the circles indicating the heads of arrows and the crosses the tails of arrows. Note the changing polarity of the magnetic fields as well as the electro-static waves as we move progressively from one wave to the next. It must be remembered that these waves are circular like the rings or ripples on a pool of water when a pebble is dropped into it, as explained in the first article on antennas in the October issue.

Also, the waves expand spherically or in three dimensions, the same as if you repeatedly deflated and expanded a toy balloon.

One of the newest short-wave aerials is that known as the *multiple-dipole* shown at Fig. 4. The maximum directional activity of this antenna is at right-angles to the array, as shown in the diagram, and unless a set of reflection wires or rods spaced say a quarter of a wavelength from it are

(Continued on page 558)

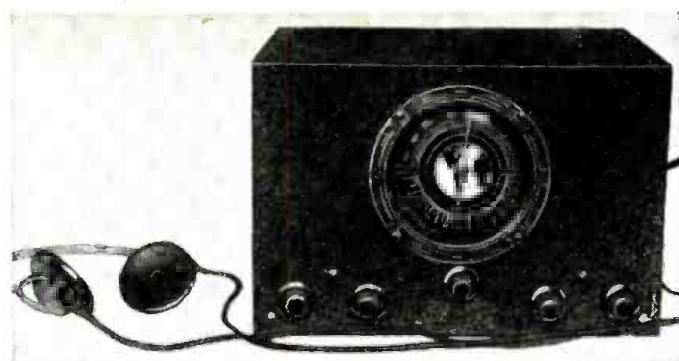The next article will cover radiation and wavelength relations of short-wave aerials of the directive type.



Front view of the 3-tube battery-operated receiver, which gives 4-tube performance.




• WHILE electrified receivers, i. e., receivers operated directly from the A. C. house circuit, have become the standard in performance, there are still many short-wave "fans" who either are not equipped to build and operate an A. C. receiver, or prefer battery-operated sets because of their quiet operation.

With the present-day tubes, a very satisfactory battery-operated receiver can be constructed at an extremely low cost. It can be built in the old bread-board fashion, with remodeled broadcast receiver parts. However, if the results obtained with the modern electrified sets are to be duplicated, the battery-operated receiver should be constructed, with the same high-quality parts and using the conventional A.C. receiver design.


The battery-operated receiver, or any receiver for that matter, using more than one or two tubes, should, by all means, employ a tuned radio frequency amplifier. This amplifier, while it does not increase the selectivity, does increase the sensitivity tremendously, and allows more efficiency and stable operation of the regenerative detector. The receiver shown in the photographs, and outlined in the accompanying circuit diagram, employs three tubes, although 4-tube performance is obtained. Glancing at the diagram, we find that a type 34 R.F. pentode is used in the T.R.F. stage; inductive coupling is used, to increase gain and stability, between the R.F. stage and the detector. This detector is a type 30 triode. (Continued on page 550)

Improved 3-Tube DOERLE For Battery Operation

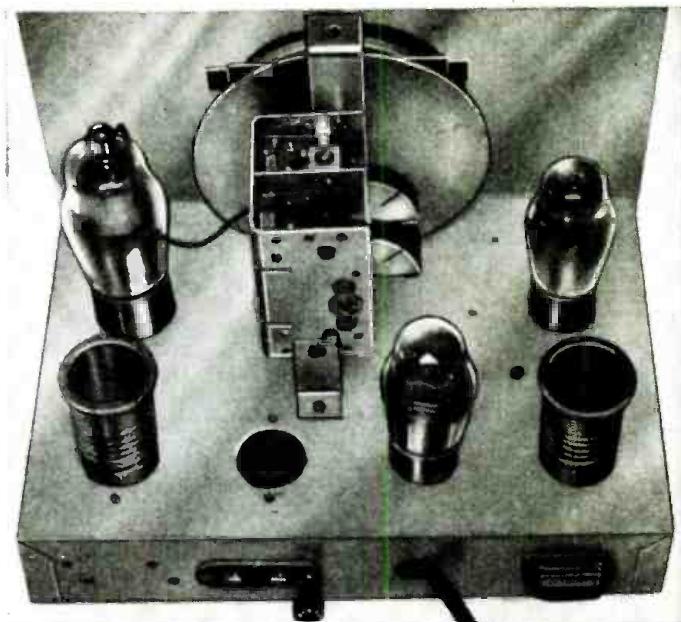Here is a 3-tube receiver that actually gives 4-tube performance! It operates directly from dry batteries and gives the utmost in simplicity, sensitivity and signal strength.



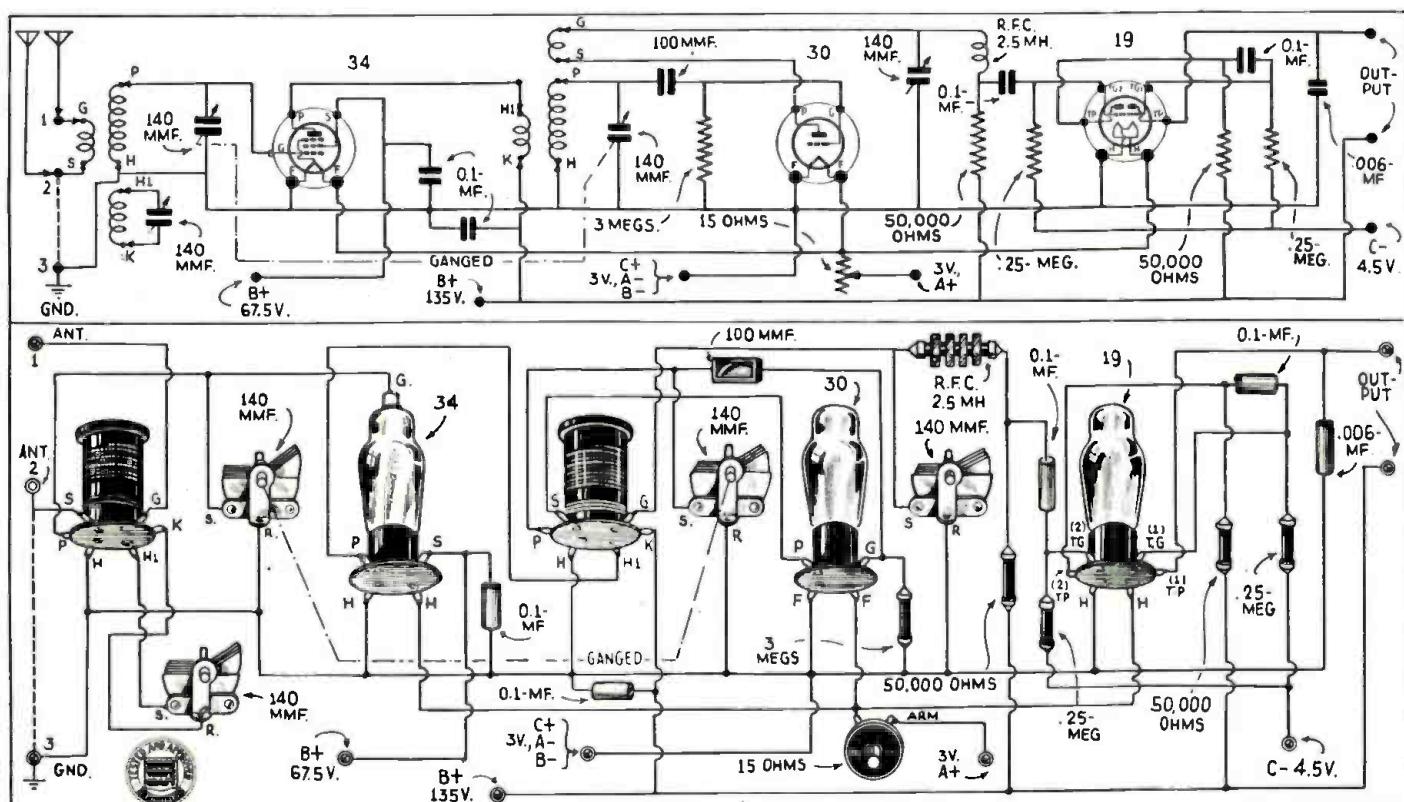
Rear view showing placement of the various parts.



This diagram very clearly shows how to wire the improved battery-operated Doerle receiver described above.



5-Meter Transceiver

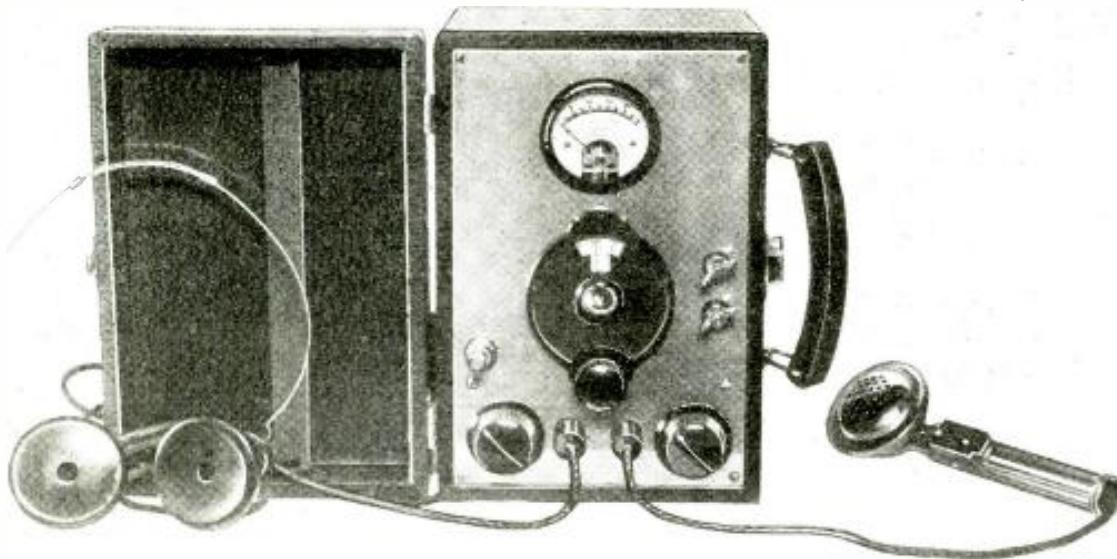

The battery-operated Transceiver ready for a QSO.

NEARLY every amateur, who is interested in the 5-meter band, has at some time, like ourselves, wanted a really portable transmitter and receiver. The logical solution of course is a *transceiver*. Even considering the few "nasty things" certain people have said of them. We agree that a transceiver, if not in the hands of a discreet person can kick up more noise and fuss than two Model-T Fords. But, there is no reason why the receiving position of the switch should create as much noise as the transmitting position. Most transceivers do not employ separate low-frequency oscillation coils and depend upon very high plate voltage and a small grid-leak to produce super-regeneration. This type of detector will no doubt radiate a strong signal and interfere with other near-by receivers.

In this receiver we use a regular *interruption-frequency*

is not so good for small batteries and for this reason the 30 is the better of the two.

Until just recently the transceiver was handicapped by large batteries. But this past year has seen astounding development in the manufacture of small batteries. The two 45-volt B batteries used in this rig furnish 90 volts and each measures $2\frac{7}{8} \times 1\frac{3}{16} \times 4\frac{5}{8}$ inches and weighs only $\frac{3}{4}$ of a pound. Each unit is a full-fledged 45-volt battery with a 22.5-volt tap. The "A" battery is a 3-volt affair and measures $2\frac{1}{8} \times 3\frac{3}{4} \times 1\frac{1}{8}$ inches and this only weighs $\frac{1}{2}$ pound. Quite an advantage, these small batteries especially in small portable receivers and transmitters such as this one.

The entire transmitter-receiver unit is built into a wooden box which is covered with black paper, a sort of instrument box readily obtainable from radio stores. The particular box used is $6\frac{1}{4} \times 9\frac{1}{4} \times 5\frac{3}{4}$ inches outside dimensions, although any convenient size may be used. The panel is aluminum $5\frac{5}{8} \times 8\frac{5}{8}$ inches and has a shelf $5\frac{1}{8} \times 4$ inches.

All of the apparatus is mounted above that shelf excepting the three winding transformer, the modulation choke and a few by-pass condensers.


In the photos of the rig, we have three views, one front, one back, and one of the underneath side of the shelf. In

Here is a 5-meter Transceiver that can be carried on hikes or any similar excursion into areas where no electricity is available. It is extremely light in weight and entirely self-powered; the batteries are contained in the carrying case, and it is capable of working a distance of 15 or 20 miles. It uses midget tubes manufactured in England, but which are available in the United States.

transformer to obtain super-regeneration, thus allowing the detector to be operated at lower plate voltages during reception and consequently causing much less interference. A separate tube could have been used for the low-frequency oscillator, but would not have helped in the least. So much for the arguments against transceivers.

The most important features of any transceiver are the weight, size, and serviceability. We can build transceivers that are much lighter and more compact than this one, but if the "rig" only operates a half hour or so, what good is it?

The tubes used in this set are manufactured in England by the High Vacuum Valve Co., Ltd., and are obtainable in the United States. These tubes are about the size of our American *peanut* tubes, but have the advantages of a type 30 in that the filament only draws .06 ampere at two volts. The 30's may be used if there is space in the box used to house the "rig." The *peanut* tubes require $\frac{1}{4}$ ampere which

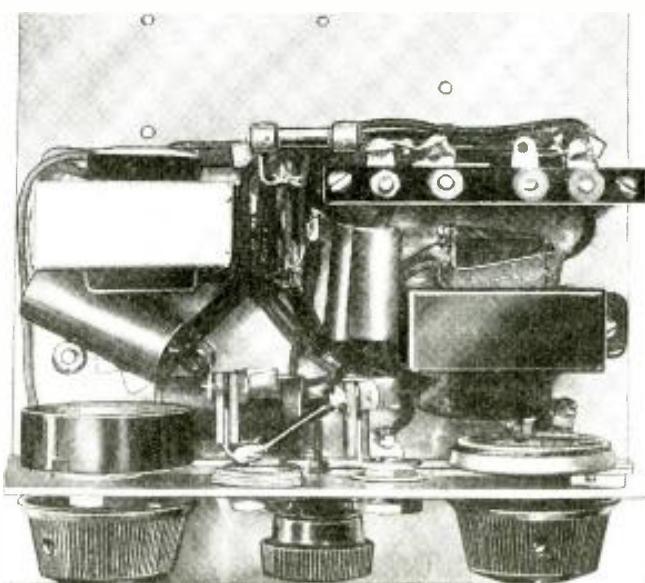

This view clearly shows how the parts are mounted.

Uses MIDGET TUBES

By Arthur Gregor

In the front view we see the 0-25 milliammeter at the top, the main dial in the center, the two antenna posts to the right and the "send-receive" switch at the left. The two knobs are the regeneration control and the filament rheostat. The two jacks are for the earphones and the microphone. These last two items fit in the cover when not in use making it completely self-contained.


The rear view shows the detector tube in the center of the shelf and the audio tube to the left of it. Behind the audio tube is the interruption-frequency transformer. The split coil and the antenna coil are on the right of the detector. The double-pole-double-throw switch is also shown. This switch has an extra single circuit switch which controls the microphone. This switch happens to be an old one used on battery sets of a few years back, however, a modern toggle type would serve.

Referring to the diagram we see that the same battery is used for the filaments, "mike" current, and bias on the audio stage. This was done to preserve space but the builder may use separate units. In switching from receiving to transmitting the grid-leak of the detector is changed, the plate circuit is cut loose from the transformer and connected to the plate of the audio tube, which is then a modulator. This puts the full "B" voltage on the detector which is now the power oscillator and feeds R.F. into the antenna coupling coil. The microphone circuit is also closed.

The transformer is a common transceiver type which has two primaries, one for the mike and another for the output of the detector. The modulation choke is a midget affair designed for A.C.-D.C. radios. There is no change in the plate of the modulator as the choke, together with the .1 mf. condenser, serves as the output filter for the phones.

One warning—do not allow the plate current of the oscillator to exceed 5 or 6 mills (M.A.) or the tube life will be materially shortened; the meter is used for that reason.

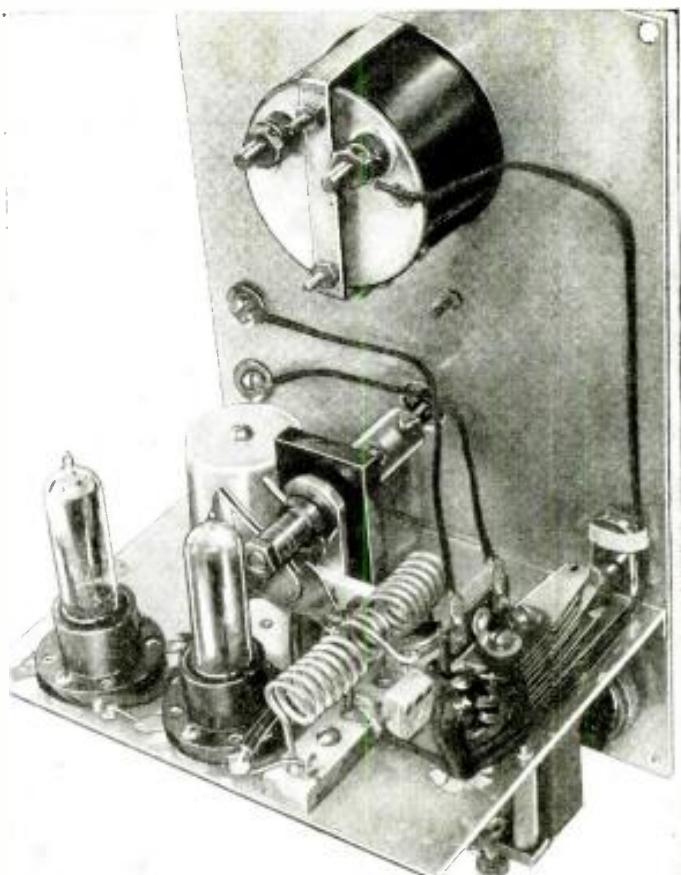In the detector-oscillator circuit we show a 1 meg. grid-leak for receiving. This value may have to be changed to



Rear view of the Transceiver; note the small size tubes.

suit different types of tubes. The transmitting grid-leak may also have to be changed although 50,000 ohms seemed to be just right.

In operation, the detector should produce a strong hissing sound as do all super-regenerators. The regeneration control should be adjusted to a point of lowest plate voltage
(Continued on page 562)


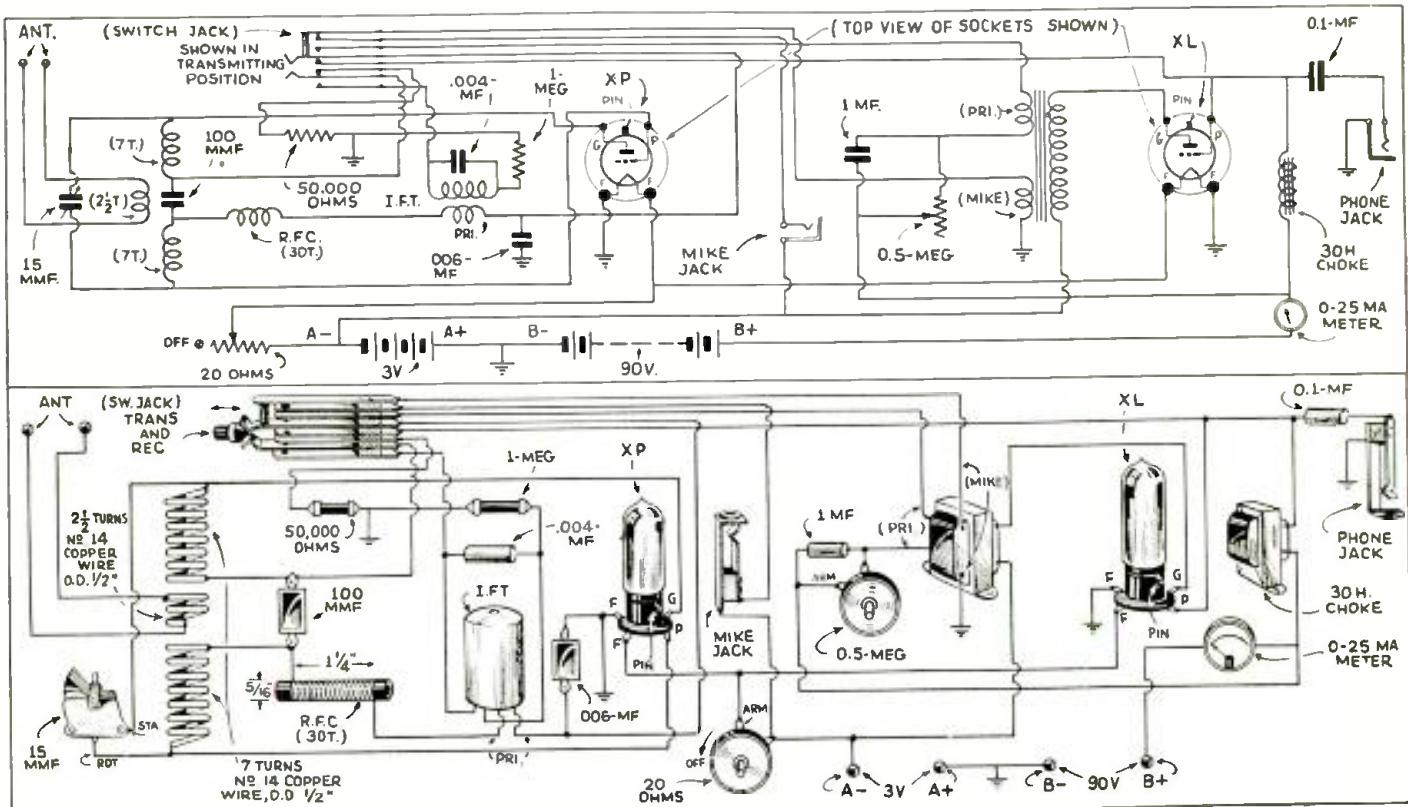


Diagram of the 2-tube battery-operated portable Transceiver.

WORLD-WIDE SHORT-

A French Automatic Set

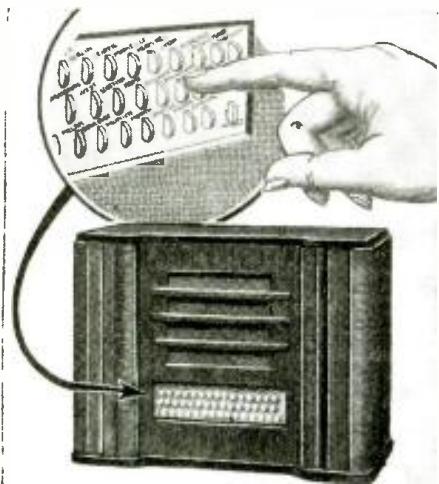● IN THE new issue of *Documentez-Vous*, a French magazine for the trade, a picture of a new receiver covering both the broadcast and short-waves was shown. This receiver is novel in that small buttons permit stations to be tuned in, without the usual procedure of turning a dial. Forty-eight of these buttons are placed on the



Tripping one of the 48 buttons shown on this French automatic receiver causes the station corresponding to that "tuner setting" to roll in. No dialing is necessary.

panel at the front of the receiver, permitting 48 different stations to be brought in.

This novelty in receiver design will, without doubt, create much interest, as did the new German receiver which is equipped with a dial similar to the dial telephone, so that it is only necessary to dial a number to tune the set.

It seems that Europe is going in quite strongly for these novelties in receiver design.

A New Short-Wave Converter

● IN A RECENT issue of *Wireless World*, a description appeared for a short-wave converter of the self-powered type.

It uses a triode-pentode type of frequency changer with a coil arrangement covering the band from 13.5 to 200 meters in three steps.

The dial used for the unit is a two-ratio affair, providing 12-1 or 150-1 reduction.



An English short-wave converter which has its own power supply. When used with a "broadcast" band receiver, it permits reception of wavelengths from 13.5 to 200 meters.


● The Editors have endeavored to review the more important foreign magazines covering short-wave developments, for the benefit of the thousands of readers of this magazine who do not have the opportunity of seeing these magazines firsthand. The circuits shown are for the most part self-explanatory to the radio student, and wherever possible the constants or values of various condensers, coils, etc., are given. Please do not write to us asking for further data, picture-diagrams or lists of parts for these foreign circuits, as we do not have any further specific information other than that given. If the reader will remember that wherever a tuned circuit is shown, for instance, he may use any short-wave coil and the appropriate corresponding tuning condenser, data for which are given dozens of times in each issue of this magazine, he will have no difficulty in reconstructing these foreign circuits to try them out.

An A.C.-D.C. type of power supply is included, so that the unit may be self-powered on any type of power line.

The output of the frequency changer is coupled to a tuned coil output, preadjusted to a frequency of 1,800 kc. This makes it possible to track the two tuning condensers in the converter and at the same time allow sufficient I.F. selectivity for use with small broadcast sets, without introducing the annoyance of image or other forms of interference.

A test by the above magazine produced some fine results from so simple a device.

An English 4-Band Coil Unit

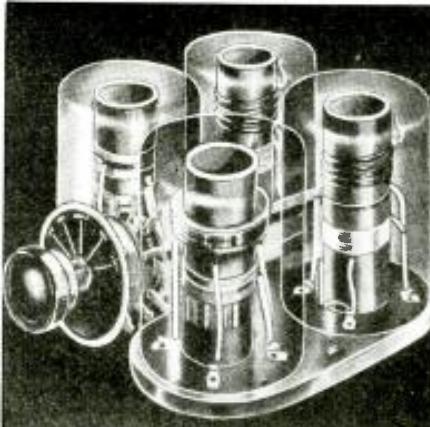

Novel 4-band coil unit recently introduced in England. Both the aerial and the oscillator coils are included in each of the four shield cans.

● A RATHER interesting form of tuner for all-wave superheterodynes was introduced recently, in England, according to *The Broadcaster and Wireless Retailer* (London).

The unit is shown in phantom form in the accompanying illustration. It will be noted that both the aerial and oscillator coils are included in each of the four shield cans. The coils are designed to cover 15 to 35, 35 to 85, 200 to 575 and 1,000 to 2,000 meters, which include the frequencies of practically all European broadcast stations on short, medium, and long waves.

The coils are designed to feed into a 465 kc. intermediate frequency amplifier. The features are high efficiency; ease of installation in new and modernized receivers; and reasonable price. The method of mounting the coils keeps the connecting leads extremely short, and still allows the coils to be completely and effectively shielded.

Cathode-Ray Frequency Doubler

● CATHODE-RAY tubes have been so closely allied to television scanning and A.C. wave-form analysis that some of the more obscure applications of the cathode-ray principle are apt to be neglected.


For example, a very ingenious frequency doubler for ultra-short-wave communication was described in the latest issue of *Wireless World* (London).

The ordinary fluorescent screen is replaced by an annular electrode, P, formed of a strip of insulating material bounded by inner and outer conducting wires, which are connected respectively to the two arms of a Lecher-wire system coupling to a dipole aerial. Inserted at intervals along the insulating strip are a series of small "targets," connected alternately to the inner and outer conductors, so as to feed intermittent pulses of energy from the cathode-ray stream to the aerial.

The discharge stream through the tube is focused, as usual, by a negatively biased cylinder, C, so as to pass through the center of the accelerator plate, A. Once past the plate, the stream comes under the influence of a pair of deflecting plates which cause it to trace out a circular path over the annular target.

High-frequency oscillations from a source, O, are applied directly to the first pair of deflecting plates. Owing to the distance separating the first pair of deflecting plates from the second it is necessary to introduce a definite phase difference in the voltages applied to the second pair of plates, to cause the stream to follow the required circular track. For this reason, the upper pair of plates is fed from the lower through a Lecher-wire system fitted with a "trombone" section for fine adjustment.

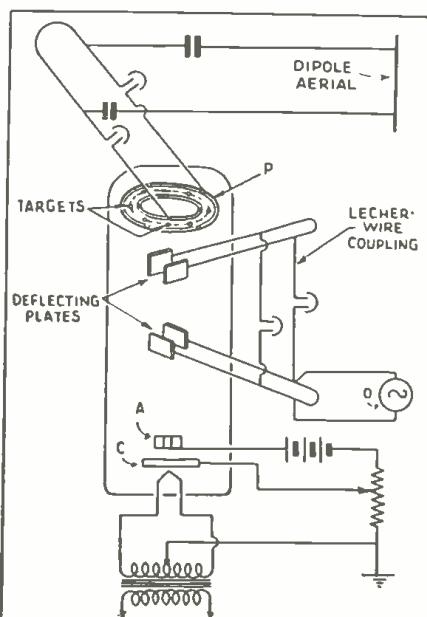The speed at which the cathode-ray traverses the annular strip is, of course, determined by the frequency of the oscillations from the source, O, while the multiplied frequency fed to the aerial depends upon the number of pairs of "targets" inserted in the annular strip. Using eight targets, as shown, the frequency emitted from the tube is four times that fed into it from the source O.



Using eight targets, the frequency emitted from this cathode ray tube is four times that fed into it from source "O."

WAVE REVIEW.

Edited by
C. W. PALMER

Short-Wave Aerials

- IN A discussion on short-wave aerials in a recent issue of *Popular Wireless* (London), a well-known author brings out some interesting facts concerning dead spots and the effect of tight coupling on reception over a wide frequency range.


An interesting sidelight to his article is a short description and sketch of several trick aerials that have proved to give unusual results for their constructors, despite the fact that they are, theoretically, all wrong. The first of these is a short dipole in which the feeders are tuned. The builder finds that he can get good performance on practically any wavelength.

Obviously this aerial is incorrect theoretically, as it cannot be operating as a true dipole at more than one, or possibly two frequencies.

The second aerial is even more strange than the first, consisting of a kind of sideways "T" aerial, but the top of the "T" is supported on a slant. The builder has tried sliding this part of the aerial about at all angles and finds an inclination of 60 degrees to the horizontal to be best.

How on earth this "thing" works is beyond all conception, but the results claimed for it are certainly unusual!

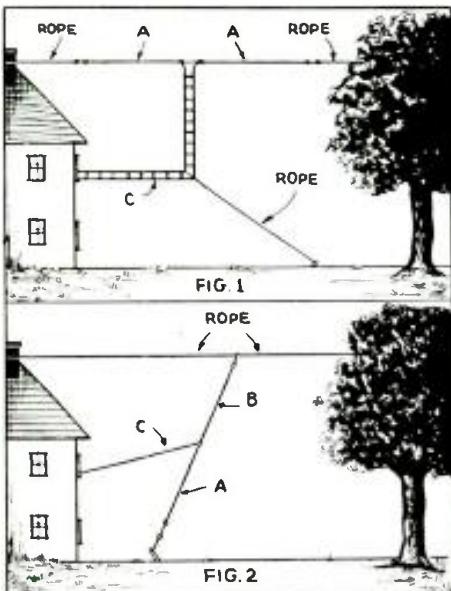While these two "freak" aerials work in spite of, rather than because of, any particular theory, our experimentally inclined readers might like to try them out. We will be interested to hear from anyone who tries either or both of them.



Two unusual aerials; theoretically they may look all wrong, but they are reputed to "bring home the bacon."

An Austrian A.C.-D.C. Set


- THE A.C.-D.C. form of receiver which has become so popular for both long- and short-wave receivers has also found much attraction among European radio fans.

In the latest issue of *Radio-Amateur* (Vienna), a typical universally operated set was described for the set-builder. The circuit of this set is shown here, as a means for comparison.

It will be seen that the set uses plug-in coils of the common four-pin type. The aerial is coupled to the grid circuit of the detector tube, through condensers attached to taps on the sides of the tuning coils, to permit the greatest selectivity

(Continued on page 555)

Special Antennas for Short Waves

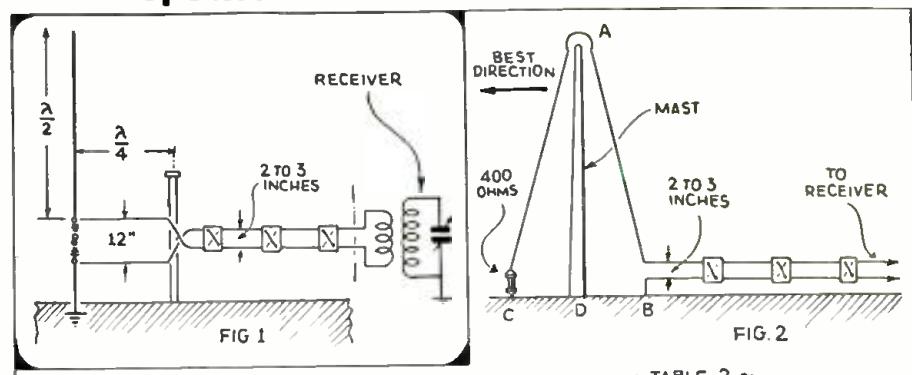

~ TABLE 1 ~
WHERE LENGTH OF SIDE = 3/4 WAVELENGTH

WAVELENGTH IN METERS	HEIGHT OF MAST (A-D)	LENGTH OF BASE (C-B)	TOTAL LENGTH OF WIRE (C-A-B)	WAVELENGTH IN METERS	HEIGHT OF MAST (A-D)	LENGTH OF BASE (C-B)	TOTAL LENGTH OF WIRE (C-B)
17	39.5 FT	28.2 FT.	83.6 FT.	17	54.1 FT	83.6 FT.	139.5 FT.
20	43.3 "	32.8 "	98.3 "	20	65.6 "	98.3 "	164.0 "
25	59.1 "	41.3 "	123.0 "	25	82.0 "	124.8 "	205.0 "

~ TABLE 2 ~

WAVELENGTH IN METERS	HEIGHT OF MAST (A-D)	LENGTH OF BASE (C-B)	TOTAL LENGTH OF WIRE (C-B)
17	39.5 FT	28.2 FT.	83.6 FT.
20	43.3 "	32.8 "	98.3 "
25	59.1 "	41.3 "	123.0 "

While not so new to the more advanced short-wave "fan" perhaps, these designs of S-W antennas are very excellent ones and if you have not tried them, you should do so at the earliest opportunity.

- IN A recent issue of *La T.S.F. pour Tous* (Paris) two short-wave aerials for special purposes were described, being translated into French from a paper published by the British Broadcasting Corp.

The first of these aerials consists of a half-wave vertical antenna, fed into a scientifically designed transmission line. The latter consists of a section, half as long as the aerial, of two wires supported in a horizontal position and parallel to each other. This is followed by a section coupling the actual aerial to the receiver which is transposed into two sections with three transposition blocks. This transposed line is fed into a coupling transformer in the receiver.

This aerial can be used in places where the local "man-made" static is bad, and still feed a strong signal into the re-

ceiver, because of the efficient lead-in arrangement.

The second antenna is known as the inverted "V" aerial. It consists of a wire supported in the form of an inverted "V" by a tall pole, one end of which is grounded through a noninductive resistor of 400 ohms, while the other is fed to a transmission line, ostensibly the same as that described for the first aerial above. This aerial is sharply directional from the direction C in the sketch, and is particularly useful for directional reception from a given station or direction.

The length of the "V" portion of the aerial determines the wavelength at which greatest signal strength is obtained. The length of the various parts of the aerial for different wavelengths is given in the accompanying chart for 3/4-wave and 5/4-wave units.

A Simple Short-Wave Superhet

- FOR the radio man who wants a simple yet efficient receiver for short waves, a 4-tube superheterodyne which was described in a late issue of *Practical and Amateur Wireless* (London) bids for consideration.


It contains only one tuning condenser, as the aerial circuit is entirely aperiodic. A pentagrid type of frequency converter feed the signals to the I.F. amplifier, after selection by the oscillator.

The I.F. amplifier contains one stage

having an input and an output I.F. transformer feeding into a triode second detector and a pentode A.F. tube.


The values of the parts are indicated on the circuit for anyone who may wish to try it.

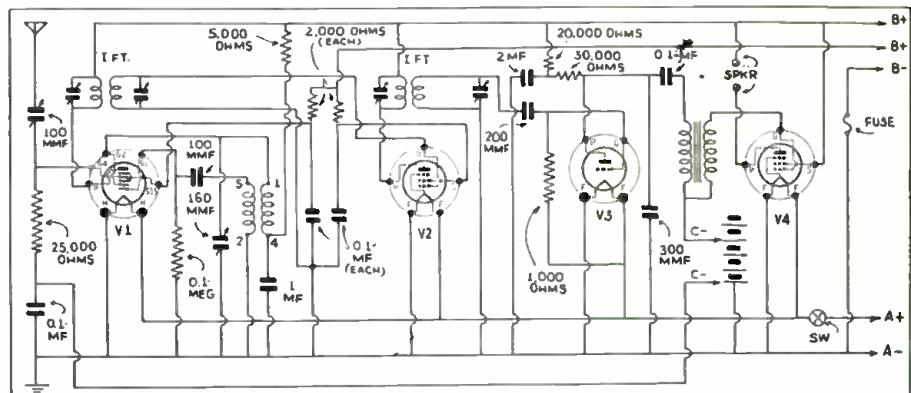While a set such as this is not ideal from the standpoint of image-frequency interference, cross talk, and birdies, it has advantages in the line of simplicity of construction and operation.



A simple superhet is in great demand by S-W "fans" and "hams." Here's a nifty one from the other side of the "big pond." It uses but one tuning condenser, the aerial circuit being entirely aperiodic. The experimenter can easily try out this circuit as the values of the parts are given.

Talking On One-Half

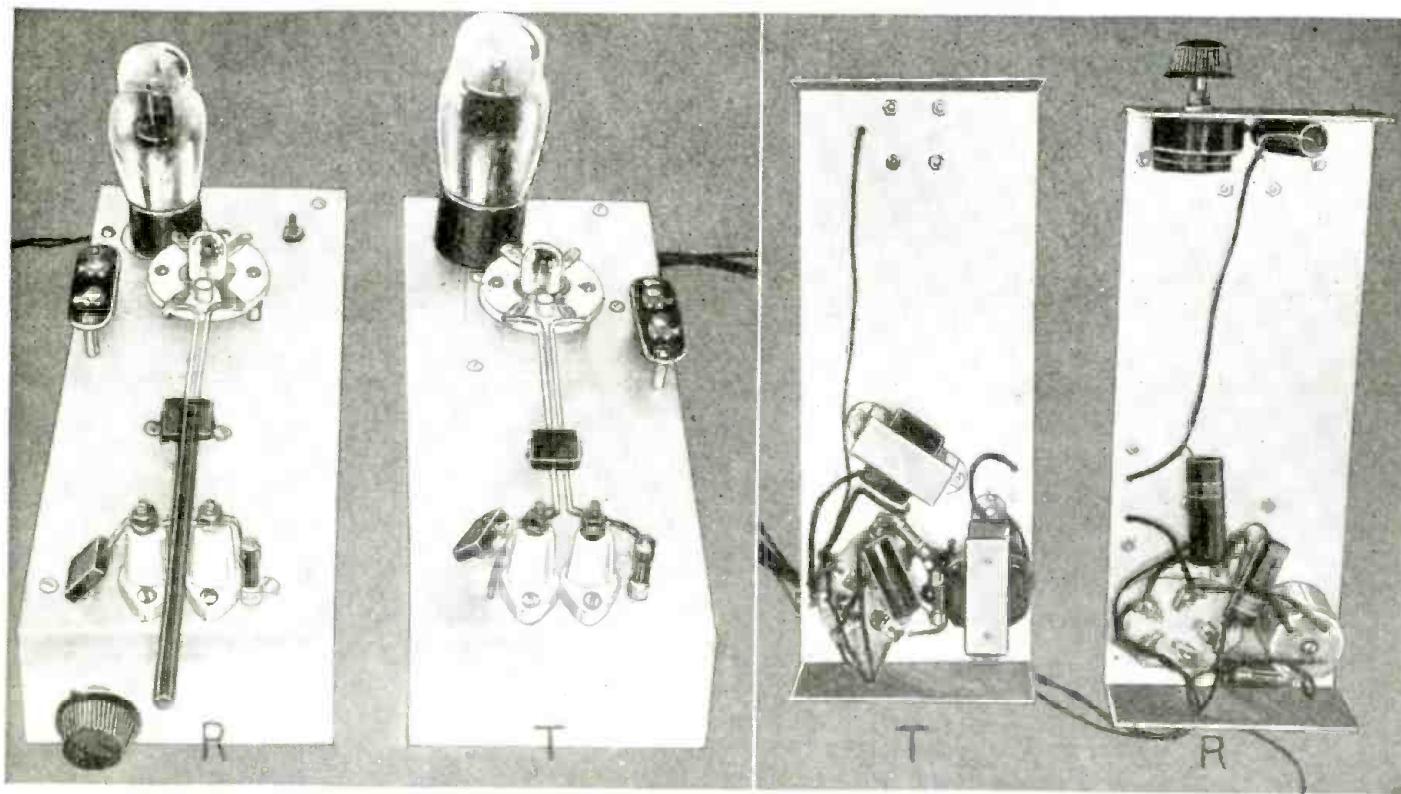

Left—Top views of receiver and transmitter. Right—Bottom views of transmitter and receiver. "T" is the transmitter, and "R" is the receiver.

• MANY times it has been said that in the days of the *crystal set* and the *loose-coupler* there were real thrills and a certain romance to radio. But today this is all gone, because radio has become so fully commercialized, what with the two and three thousand dollar Ham transmitting stations and Ham receivers selling as high as \$500.00! All we can say is—maybe!


Just as mysterious as radio was in

the days of the galena detector are these new *ultra-short waves*. Because they are few if any who know more than a little bit about them. Radio in the old days was fascinating because of its newness. Today we have something just as new and far more mysterious in the waves below one meter!

Some time ago we were told that ultra-short waves were quasi-optical. This has been proven false to a con-

siderable extent in many recent instances. Who can say that new discoveries may not prove it true in all? The dyed-in-the-wool experimenter of today, as of old, has a very great opportunity for interesting and valuable experimentation and research.

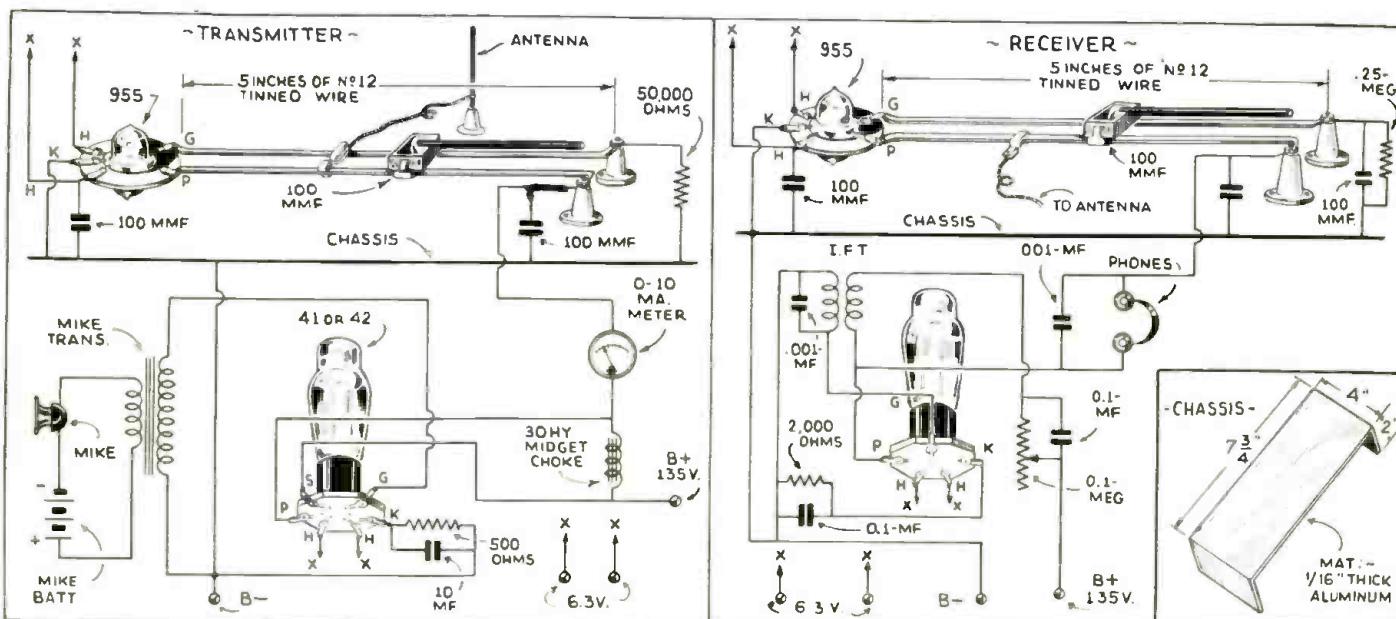Many weird ultra-high-frequency transmitters and receivers have been built and experimented with under the roof of W2AMN's "shack." A good



Complete diagrams of the half-meter transmitter and receiver.


Meter



By George W. Shuart, W2AMN

Fans, Experimenters, and Hams alike have long desired information on a simple and effective transmitter and receiver to operate below one meter. The transmitter and receiver described in this article is built around the Acorn tubes and tunes between one-half and one meter; of course, for transmitting, an amateur license is absolutely essential. The dimensions of the antenna and the low cost of the apparatus offer the experimenter a wonderful opportunity of performing many interesting experiments.

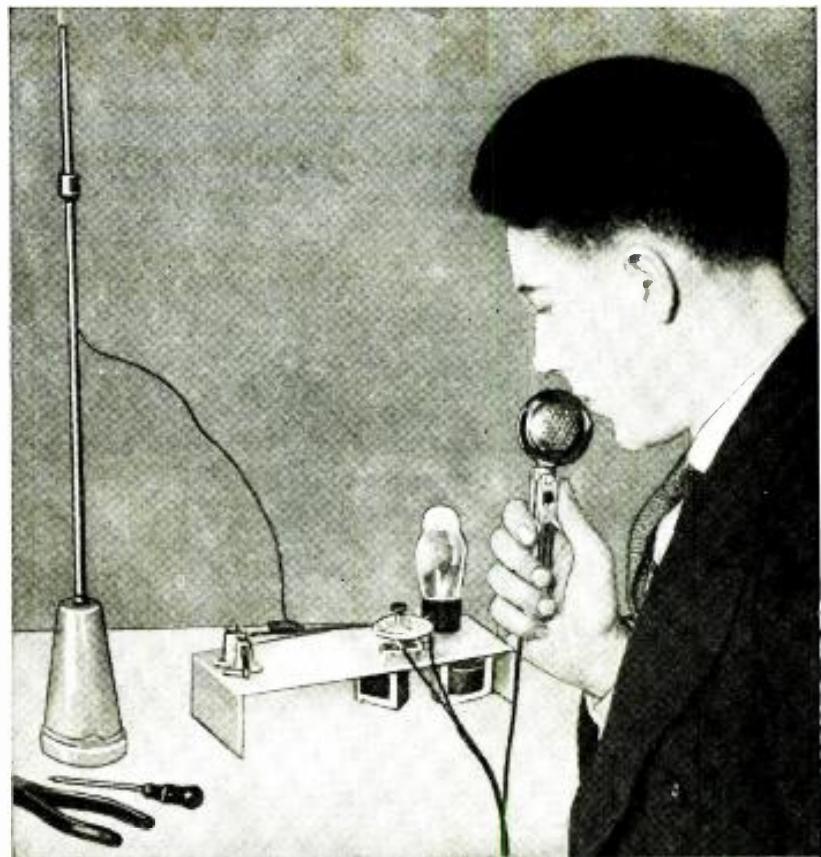Mr. Shuart demonstrating his half-meter transmitter.



many worked and just as many were failures. But we still say that we had a lot of fun and there's lots of it left for you boys. Probably the most interesting part of it is the comparative small cost of the apparatus used. Most of it is homemade as in the days of old.

Range 0.5 to 1 Meter

The transmitter and receiver shown in the photos are the acme in low cost and simplicity. They both operate in a range of from less than one-half meter up to slightly less than one meter. Although very low power apparatus they provide plenty of opportunity for experiment. Don't forget that the transmitter must only be operated by or in charge of a licensed operator. Anyone can talk over it as long as the operator is present. The tuned circuits are an adaptation of the now famous "long lines" oscillators previously described by the writer. The detector tube in the receiver and the oscillator tube in the transmitter are 955 "Acorn" tubes, the only ones that can be successfully used on waves below one meter, at this writing.

Receiver Is a Super-Regenerator

The receiver is a super-regenerator and uses a type 37 as the low frequency oscillator. In the transmitter we have a type 41 connected as a pentode and used to modulate the 955 oscillator. The microphone is connected directly to the pentode and provides plenty of modulation for the 955.

Both sets are alike in construction, therefore it will be necessary to describe only one in detail. The tuning is done by sliding a fixed capacity condenser along the two wires making up the—should we say—"very short lines."

In constructing this very short line, place the wires as close together as possible without danger of "shorting" them by contact with each other. If

these wires were farther apart they would have less length per given wavelength. This is a peculiarity of this type of circuit. If they were placed say an inch apart and gradually brought closer together, the wavelength would become shorter or the frequency higher. This is because even though the capacity increases, the inductance decreases. The inductance decreases more

the line there is the grid-leak connected between the grid wire and the chassis. At the end of the plate wire is fed the plate voltage for the tube.

Tuning Adjustments

When the "shorting" condenser is placed at the extreme end of the line, the circuit is resonant at its lowest frequency. As this condenser is pushed nearer to the 955 tube, the frequency becomes higher until it is placed as near to the tube as it will go, when the circuit is resonant at the highest frequency to which it will tune.

On the transmitter the adjustment of the tuning condenser is not changed as often as on the receiver, therefore a handle is attached to the receiver condenser. This is a $\frac{1}{4}$ -inch bakelite rod which has been filed flat on one side and cemented to the condenser with household cement.

For calibration and aid in tuning, a scale of numbers may be marked on the chassis directly under the two wires. This will serve in returning to a given wavelength.

At the end of the plate wire on both the receiver and transmitter, there is a .0001 mf. by-pass condenser connected between it and the chassis. R.F. (radio frequency) chokes of various sizes were tried and proved of no particular value. Also there is a .0001 mf. condenser bypassing one of the heater leads to the chassis. This aids considerably in obtaining stable operation of both the transmitter and receiver. Cathode R.F. chokes were also tried and were of no benefit. It seems the more gadgets one puts on one of these very short-wave outfits, the poorer they perform.

The grid-leak for the receiver which provided maximum sensitivity with the particular tubes available was 250,000 ohms. The transmitting grid-leak depends a great deal upon the plate voltage applied (Continued on page 557)


- Parts List**
- 4—Small stand-off insulators, I.C.A.
 - 2—Acorn Tube Isolantite Sockets, Hammarlund.
 - 1—6-Prong Isolantite Socket, Hammarlund.
 - 1—5-Prong Isolantite Socket, Hammarlund.
 - 1—50,000-ohm one-half watt Resistor, I.R.C.
 - 1—250,000-ohm one-half watt resistor, I.R.C.
 - 1—500-ohm Resistor, I.R.C.
 - 7—.0001 mf. Mica Condensers, Aerovox.
 - 1—100,000-ohm Potentiometer, Electrad.
 - 1—2,000-ohm one-half watt Resistor, I.R.C.
 - 1—Interruption Frequency Transformer, I.C.A.
 - 2—.001 mf. Condensers, Aerovox.
 - 2—.1 mf. Condensers, Aerovox.
 - 1—10 mf. Electrolytic Condenser, Aerovox.
 - 1—Midget Microphone Transformer, Stancor.
 - 1—Midget Filter Choke, A.C.-D.C. type, Stancor.
 - 2—Chassis (see drawing), Blan.
 - 2—955 Acorn Tubes.
 - 1—37 Tube.
 - 1—41 Tube.
 - 1—Hand-mike—Universal Microphone Co.
 - 1—Pair Headphones—Trimm Radio Mfg. Co.

rapidly than the capacity increases. Number 12 tinned bus-bar was used and the spacing between the wires is about equal to the diameter of the conductors.

Each wire is 5 inches long; one connects directly to the grid and the other to the plate of the tube. At the end of

SHORT WAVES and

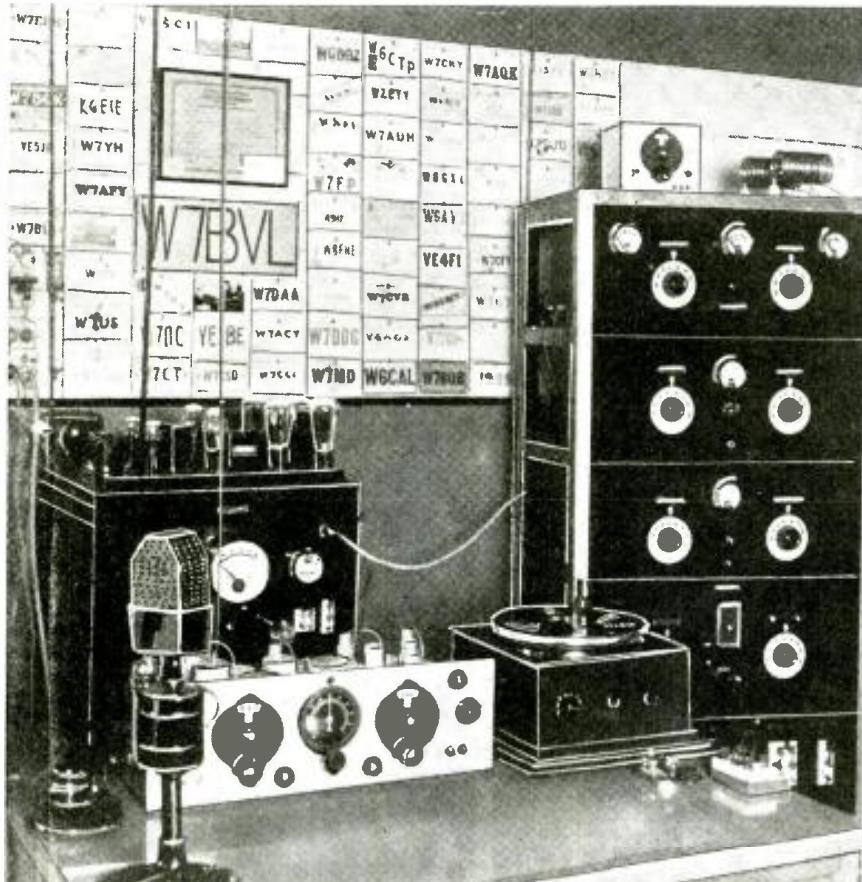**Howard L. Dull Built This High-Quality Amateur Station
Awarded This Month's Prize**



Howard L. Dull of Seattle, Wash., is the lucky winner of this month's prize—one year's subscription to this Magazine, for the photo of his very fine home-built amateur station. The receiver is a 9-tube homemade superhet with A.V.C. and an "R" meter.

Editor, SHORT WAVE CRAFT:

• THIS photograph gives a general view of radio station W7BVL, owned by Howard L. Dull, 7214 Palatine Ave., Seattle, Wash. The station has not been designed for the maximum power, but rather for good quality transmission. Most of the operating is done on 20- and 75-meter phone with a power input of 150 watts. W7BVL has been "on the air" since January, 1932.

The rack and panel on the right contains a complete four-stage R.F. unit, consisting of a 59 crystal oscillator, a 59 buffer doubler exciting two type 10's in push-pull which are link-coupled to a single 211 as a final amplifier. Grid-leak bias is used in the final amplifier, and the coils of the R.F. exciting units are shielded to eliminate feed-back. The high-voltage and low-voltage power supplies are at the bottom of the rack; next above are the low-power stages, followed by the final stage and antenna matching network. The antenna used at the present time is a 75-meter current-fed zepp with 45-foot feeders and 120-foot flat-top.

The audio equipment includes an Amperite velocity microphone, with a four-stage resistance-coupled pre-amplifier employing a 75 high-gain triode, a 76, and two 37's. The pre-amplifier is not shown in the picture, but is one completely shielded unit. The output of the pre-amplifier feeds into two 56's in push-pull, which "kick" two 2A3's as push-pull drivers, which in turn excite four type 250's in push-pull parallel as Class-A-Prime modulators—making

a total of seven stages of audio. The modulator and high-level audio equipment are in the rack on the left—the large meter shown in the picture is in the plate circuit of the modulator and provides a check on modulation. The additional equipment includes a vacuum tube voltmeter and a special two-stage amplifier in the phonograph box on the desk. It is utilized for the phonograph pickup, and as an emergency pre-amplifier. A "fading" system is also used, making it possible to mix both voice and music.



Charles B. Cox of York, Pa., sports an "up-and-going" short-wave listening post.

The receiver at W7BVL is a nine tube homemade superheterodyne which incorporates A.V.C. and an "R" meter. A separate matched-impedance "doublet" receiving antenna is used, making possible duplex operation. All districts in the United States and Canada, Cuba, Mexico, and the Hawaiian Islands have been worked on phone, and SWL verifications have been received from beyond these limits. This station is operated in the interest of "world-wide friendship."

(We are glad to award this month's prize for the photo of your homemade transmitter and receiver "rig," Howard. You certainly deserve a lot of credit for building up this excellent transmitter and receiver, and anyone who has ever tried to build a 9-tube superhet of the type you have, will quite agree, we are sure.—Editor)

C. B. COX HAS LIVE LISTENING POST

Editor, SHORT WAVE CRAFT:

My receiver is homemade and A.C. operated. It uses 58 TRF, 57 Detector, 57 and 2A5 audio stages. I have heard a total of 123 stations (no Hams or CW), with stations on all continents. I have received 38 verities, some of which are shown in the photo. My aerial is about 75 feet long. At the highest end it is 30 feet high. The aerial runs east and west, the free end pointing to the west. The ground is made on a radiator pipe.

I am assistant vice-president of the International 6000-to-12500-Mile Short Wave Club, of which Mr. Oliver Amlie is president. How about some more of you DX-ers joining up? It's a fine club to belong to, one must do some work to become a member.

In closing I will say that *Short Wave Craft* is the best magazine I have ever seen for the "SWL." I have been reading it for several years and hope to do so for many more. My receiver was built from plans in *Short Wave Craft*, it has always worked fine.

CHARLES B. COX,
526 Madison Ave.,
York, Pa.

One Year's Subscription to SHORT WAVE CRAFT FREE

for the "Best" Station Photo
Closing date for each contest—75 days preceding date of issue; Dec. 15 for March issue, etc. The editors will act as judges and their opinions will be final. In the event of a tie a subscription will be given to each contestant so tying.

LONG RAVES . . .

OUR
READERS' FORUM

(Thanks for your expressions of opinion on Short-Wave Craft, Charles, and also for your courtesy in sending us the very nice photo of your short-wave "listening post." The set-up looks like "real business."—Editor)

A "KINK" THAT DID WONDERS!

Editor, Short Wave Craft:

I wish to compliment Mr. Seiko Yakabi on his fine "kink" in the October *Short Wave Craft*. He described how to change an ordinary two-circuit detector into an electron-coupled one. I tried his circuit out on my "Doerle A.C. Two," which heretofore had worked fairly well. Within an hour after I had made the required changes I had picked up EAQ, Madrid, with enough volume to be heard all over the upstairs and part of the downstairs rooms of our house. The tonal quality was almost equal to that of any U.S. station. The sensitivity and "pep" were about doubled. It is my opinion that Mr. Yakabi had the best "kink" on the page. Every "fan" who has a set similar to a "Doerle" should at least give Mr. Yakabi's "kink" a trial, as there are only four wires to change.

I hope that the sets in *Short Wave Craft* do not all start using metal tubes, as most of us still have quite a few glass tubes left that are still usable.

Yours truly,
LOUIS E. KELSEY.
420 North Lincoln Avenue,
Wilmington, Ohio.

(Will give you plenty of glass-tube sets.
O. M.—Editor.)

W7AHQ HAS FIVE STATIONS

Editor, Short Wave Craft:


Having been a reader of *Short Wave Craft* for quite some time, I have been interested in reading about all the amateur stations which you have published. I used to spend a lot of time during the winter working Eastern stations and I thought this would be a good way to show them what I have.

I have been active in amateur radio ever since 1920 and am about the only "old-timer" left in the northwest I believe.

The receiver is a National FB7 with antenna for BK-JN. The transmitter is a MOPA, using a 210 to drive a pair of 210's. With about 750 volts, a pair of 866's, with a large filter, keep the note clear. Separate filament transformers are used for rectifier and main tubes, and during transmission the tubes are run steady, instead of being turned off after each time.

Your editorials on radio, particularly the last one, have been quite interesting, and

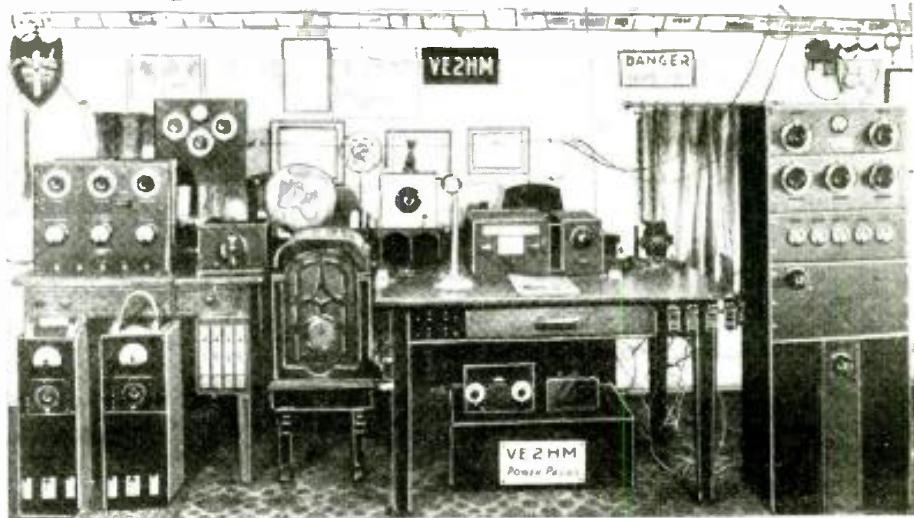VE2HM—Corking Station operated by W. C. J. Meredith at 1228 Pine Ave. Montreal, Canada.



Speaking of short-wave Ham stations—here is a corker, operated by W. C. J. Meredith at Montreal, Canada.

I have been hoping that some editor would write on this subject.

I'll be glad to exchange photos with other amateurs.

R. C. NASER, W7AHQ,
1119 9th St.,
Anacortes, Wash.

Glad to hear from you, R. C. N., together with the excellent photo of your Ham station, particularly as we have not heard from many of our friends in the state of Washington. You ought to obtain some very fine long-distance contacts with this excellent station, and with the FB7 receiver, your reception should be right up to par. Editor)

Editor, Short Wave Craft:

The transmitter on the left of the photo is capable of a fully modulated carrier output of 25 watts and is used principally on 160-meter phone over medium distances, and on regular schedules, with the OM's shack in the country. On the right is a Collins 30 FNB transmitter, which is run with an average input of 200 watts to the final stage and is employed mostly for 20-meter phone work. Its signals have been reported fairly consistently in many parts of the world, but probably owing to directional effects the best DX reports are usually had

from Europe. Recent successful 2-way phone contacts include EA4AO Spain, CT1BY Portugal, G6XR England, VP3BG British Guiana, LU9PA Argentina, etc. On April 20 and 22 last, under good conditions, reports of QSA 5, R9 "local strength and quality" were obtained from G5VL, Cornwall, England, in 2-way QSO's.

Four transmitting antennas are available: a 268-foot single-wire-fed Hertz for 160-meter work, a 20-meter current-fed antenna, a 40- and a 20-meter Zeppelin. Both transmitters are fitted with the well-known Collins impedance matching system which greatly simplifies a change over from one antenna to another and also reduces harmonic radiation to a minimum.


The principal receiver is a National FBX, with one stage of pre-selection, coupled to a doublet antenna via a variable "all-wave coupler." This receiver is transformer-coupled to a dynamic speaker seen in the background. A National SW3 and a 3-tube battery set (seen under operating table) are available as stand-by receivers and a General Electric K80 is used for broadcast reception. On the left, under the smaller transmitter, are two self-contained portable 56 mc. transceivers used for experimental work on the 5-meter band. On the right of the principal receiver are the keys and key-click filter system—a combination of choke, condenser and resistance.

The station mascot, a black cat, presides over the monitor, wishing DX to every CQ. W. C. J. MEREDITH,
1228 Pine Ave.,
Montreal, Canada.

(Some station! And we don't mean maybe! With this elaborate transmitting and receiving station, you should be able to contact stations just about anywhere "round the world," under good operating conditions, of course. The idea of using a series of antennas for the different wavelengths is a very good one, and we have often wished for a large tract of ground, way out in the open country, away from high-tension lines, railroads, and other electrical or mechanical structures, so that we could erect a veritable "flock" of S-W antennas; then select, by means of switches, the one best suited for the particular transmission or reception frequency in use at the time.—Editor)

D.C. 2-TUBE DOERLE WORKS FINE

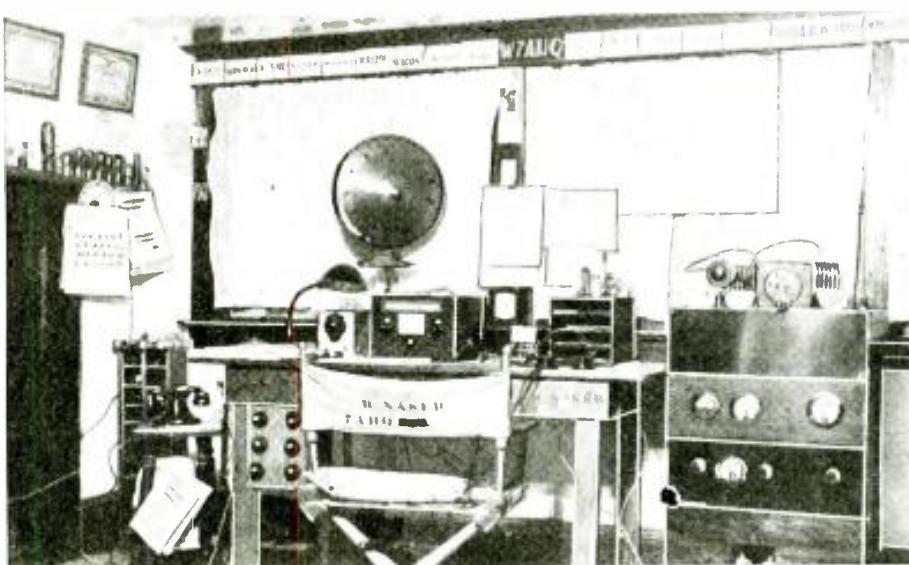Editor, Short Wave Craft:
Having built the 2-tube Doerle D.C. set,
(Continued on page 571)



R. C. Naser of Anacortes, Wash., owner and operator of Station W7AHQ.

TWENTY-SECOND "TROPHY CUP"

Presented to

SHORT WAVE SCOUT

FLETCHER W. HARTMAN

SOUTH AMBOY, N.J.

For his contribution toward the advancement of the art of Radio

by



Magazine

22nd TROPHY WINNER

62 veries; 47 foreign

● IT IS with pleasure that we award the 22nd Short Wave Scout Trophy to Fletcher W. Hartman of 365 John St., South Amboy, N.J., for his contribution to the art of short-wave radio. Mr. Hartman had a total of 62 stations, all of which were verified; 15 were located in the United States, and 47 in foreign countries.

Mr. Hartman built his own receiver, and has been using it for the past two years. It is a 6-tube superheterodyne and has a switch arrangement for changing bands, and tunes from 9 meters to 26 meters in one position, 24 to 52 meters in the other, and from 200 to 550 meters in the third position of the switch. The antenna was a 60-foot wire with a 20-foot leadin and 20 feet high. It seems, from his letter, that he had considerable difficulty with several stations in getting them to send verification cards, which would conform with the rules of our Contest. However, after much correspondence, he was able to win his point and submit the excellent total of 62 stations. You other fellows, who are complaining that the verifications received do not conform with our Contest rules, should take a hint from Mr. Hartman, and you will obtain the right kind of veries.


UNITED STATES STATIONS

W1XK—9,570 kc.—Westinghouse Elec. & Mfg. Co., Boston, Mass.
W2XAD—15,330 kc.—General Elec. Co., Schenectady, N. Y.
W2XAF—9,530 kc.—General Elec. Co., Schenectady, N. Y.
W2XE—6,120 kc.—Atlantic Broadcasting Co., 485 Madison Ave., New York City.
W3XAL—17,780 kc.—National Broadcasting Co., New York City.
W3XAL—6,100 kc.—Nat'l Broadcasting Co., N. Y. C.
W3XAU—6,060 kc.—1622 Chestnut St., Philadelphia, Pa.
W3XL—6,425 kc.—National Broadcasting Co., New York City.
W8XAI—6,060 kc.—The Crosley Radio Corp., Cincinnati, Ohio.
W8XK—15,210 kc.—Westinghouse Elec. & Mfg. Co., Pittsburgh, Pa.
W8XK—6,140 kc.—Westinghouse Elec. & Mfg. Co., Pittsburgh, Pa.
W8XK—11,870 kc.—Westinghouse Elec. & Mfg. Co., Pittsburgh, Pa.
W9XAA—6,080 kc.—Northeast Tower, Navy Pier, Chicago, Ill.
W9XF—6,100 kc.—National Broadcasting Co., Chicago, Ill.
W10XV—3,100 kc.—Nat'l Broadcasting Co., N. Y. C., Mobile transmitter testing with Empire State Bldg.

FOREIGN STATIONS

CJRO—6,150 kc.—Jas. Richardson & Sons, Winnipeg, Manitoba.
CIRX—11,720 kc.—Same as above.
VE9GW—6,090 kc.—Canadian Radio Comm., R. R. 4, Bowmanville, Ont.

(Continued on page 573)

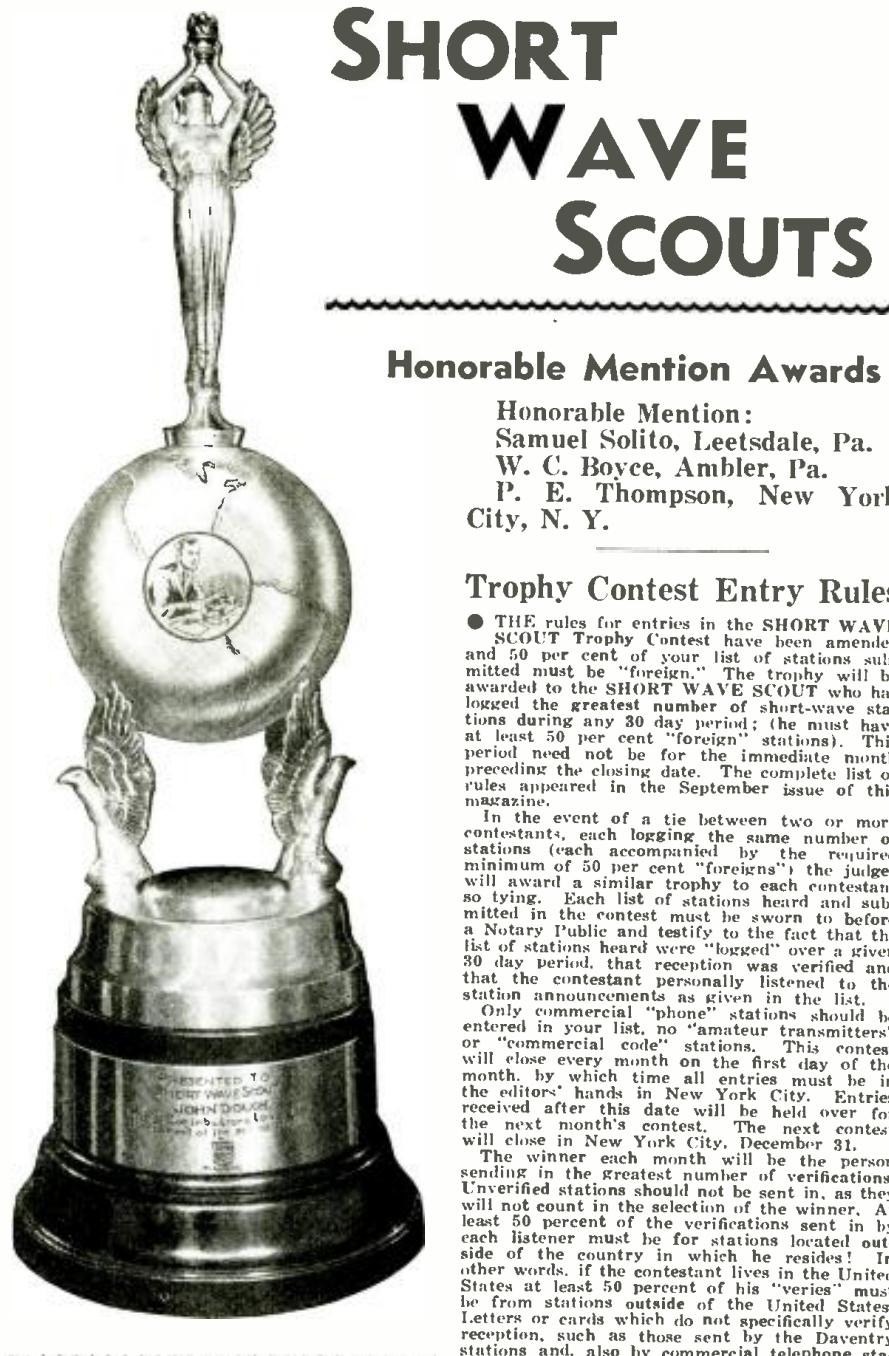

● ON this page is illustrated the handsome trophy which was designed by one of New York's leading silversmiths. It is made of metal throughout, except the base, which is made of handsome black Bakelite. The metal itself is quadruple silver-plated, in the usual manner of all trophies today.

It is a most imposing piece of work, and stands from tip to base 22½". The diameter of the base is 7½". The diameter of the globe is 5¾". The work throughout is first-class, and no money has been spared in its execution. It will enhance any home, and will be admired by everyone who sees it.

The trophy will be awarded every month, and the winner will be announced in the following issue of SHORT WAVE CRAFT. The winner's name will be hand engraved on the trophy.

The purpose of this contest is to advance the art of radio by "logging" as many short-wave phone stations, amateurs excluded, in a period not exceeding 30 days, as possible by any one contestant. The trophy will be awarded to that SHORT WAVE SCOUT who has logged the greatest number of short-wave stations during any 30-day period.

SHORT WAVE SCOUTS

Honorable Mention Awards

Honorable Mention:

Samuel Solito, Leetsdale, Pa.

W. C. Boyce, Ambler, Pa.

P. E. Thompson, New York City, N. Y.

Trophy Contest Entry Rules

● THE rules for entries in the SHORT WAVE SCOUT Trophy Contest have been amended and 50 per cent of your list of stations submitted must be "foreign." The trophy will be awarded to the SHORT WAVE SCOUT who has logged the greatest number of short-wave stations during any 30 day period; (he must have at least 50 per cent "foreign" stations). This period need not be for the immediate month preceding the closing date. The complete list of rules appeared in the September issue of this magazine.

In the event of a tie between two or more contestants, each logging the same number of stations (each accompanied by the required minimum of 50 per cent "foreign") the judges will award a similar trophy to each contestant so tying. Each list of stations heard and submitted in the contest must be sworn to before a Notary Public and testify to the fact that the list of stations heard were "logged" over a given 30 day period, that reception was verified and that the contestant personally listened to the station announcements as given in the list.

Only commercial "phone" stations should be entered in your list, no "amateur transmitters" or "commercial code" stations. This contest will close every month on the first day of the month, by which time all entries must be in the editors' hands in New York City. Entries received after this date will be held over for the next month's contest. The next contest will close in New York City, December 31.


The winner each month will be the person sending in the greatest number of verifications. Unverified stations should not be sent in, as they will not count in the selection of the winner. At least 50 percent of the verifications sent in by each listener must be for stations located outside of the country in which he resides! In other words, if the contestant lives in the United States at least 50 percent of his "veries" must be from stations outside of the United States. Letters or cards which do not specifically verify reception, such as those sent by the Daventry stations and also by commercial telephone stations, will not be accepted as verifications. Only letters or cards which "specifically" verify reception of a "given station," on a given wave length and on a given day, will be accepted! In other words it is useless to send in cards from commercial telephone stations or the Daventry stations, which state that specific verifications will not be given. Therefore do not put such stations on your list for entry in the trophy contest!

SHORT WAVE SCOUTS are allowed the use of any receiving set, from a one-tube up to one of sixteen tubes or upwards, if they so desire.

When sending in entries, note the following few simple instructions: Type your list, or write in ink, pencilled matter is not allowed. Send verification cards, letters and the list all in one package, either by mail or by express prepaid; do not split up the package. Verification cards and letters will be returned, at the end of the contest, to their owners; the expense to be borne by SHORT WAVE CRAFT magazine.

In order to have uniformity of the entries, when writing or typing your list, observe the following routine: USE A SINGLE LINE FOR EACH STATION; type or write the entries IN THE FOLLOWING ORDER: Station call letters; frequency station transmits at; schedule of transmission, if known (all time should be reduced to Eastern Standard which is five hours behind Greenwich Meridian Time); name of station, city, country; identification signal if any. Sign your name at the bottom of the list and furthermore state the type of set used by you to receive these stations.

(Continued on page 573)

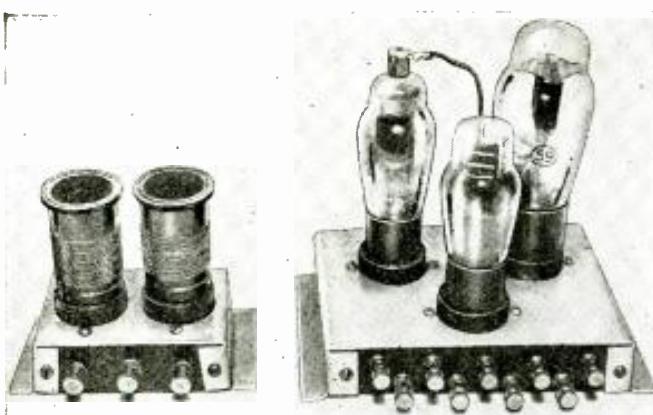

In the scheme here described by Mr. Vette, a set of "coil" and "tube" units are provided, the various wires from the socket terminals leading to numbered binding posts, all sorts of connections being quickly arranged.

• HOW many times have hundreds of you readers of SHORT WAVE CRAFT, having good little sets working in tip-top shape, read the praises of hundreds of other experimenters using the "XYZ" circuit, which was a later circuit than yours, and wished that you could try out that circuit, without tearing up the set you already had, and without spending another five to twenty dollars. We all like to try out new circuits and improvements, of which the pages of this magazine are full. But about eight-tenths of us cannot afford a complete new outlay of parts, nor do we wish to spoil the performance of the set already operating so sweetly. Even so, I have found from experience that it doesn't take much soldering, unsoldering, and resoldering, along with unmounting and remounting parts to make them noisy and unfit for use in the modern hi-gain S.W. circuits. Well, it is to the above-mentioned eight-tenths that this article is dedicated. And I'm willing to bet a goodly number of the other twenty percent will perk up their ears, too.

A few words here about what the two units about to be described will do:

You will remember the famous "Doerle" two-tube receiver—you read its praises in every issue of SHORT WAVE CRAFT. And the more recent "Oscillidyne", in all its phases. And the "Pentaflex", another of Worcester's brain-children (or Storms?) And the "Twiflex", also by Worcester. And dozens of other circuits. Just look back over a few issues of SHORT WAVE CRAFT, and see how many circuits strike you as being worth a whirl, due to their novelty, or the writer's claims as to their DX abilities.

And how many more of these circuits are going to appear next month—and each month after that? Super-regenerative circuits by the dozen, and dozens of different regeneration schemes. It would cost a fortune to buy new parts and try them all out—but that's not necessary. You can, for an expenditure of between two and three dollars experiment with each and every one of these experiments, without damaging parts, or destroying the receiver already in use. In fact you may experiment with a dozen or so of them in a day's time; and you don't even need a soldering iron. This latter article, I believe, takes most of the job out of experimenting, if one makes very many changes. But this is not a necessity, after once building the about-to-be described gadgets. You can, by changing a few wires

to various binding posts on the units, try any regeneration control scheme with any coil, and with any ordinary tube on the market. And change from one to half a dozen others in just a few moment's time. It sounds fantastic, and even impossible—yet the two units making it not only absolutely possible, but practical as well, are constructed so simply that anyone without the slightest knowledge of radio can put them together and build them into a workable set in a very short while. These two units consist of merely two chosen groups of sockets, paralleled in such a manner as to receive any coil form in use today, and any common tube now in use by the average experimenter, their terminals brought out to metal binding posts arranged so that any tube may be used in any circuit, merely by connecting associated apparatus to the proper binding posts.

The photograph reproduced elsewhere shows two aluminum shelves, one holding two sockets and six binding posts; the other three sockets and nine binding posts.

These five sockets are of the type that will permit the use of any tube or coil form, due to their novel construction.

Reference to the parts list will show that of these five sockets, two of them are four-prong UX sockets, two of them "Universal" small and large base seven-prong socket. With the exception of the antique and ancient WD, WX and UV bases, these sockets will accommodate any type, size or make of tube, and as tubes will probably run to no more than seven prongs for a short while at least, will accommodate any that will be brought out in months to come. In addition to these five sockets, all else that is necessary is fifteen of the old style metal binding posts, with a hole and clamping screw, three strips of bakelite, dimensions shown in drawings, and two pieces of aluminum, dimensions also shown. The only substitution possible is the binding posts, and as such a substitution would be more expensive than the specified part, such is not advised. For quick and easy change, these binding posts should have a hole in them, and the metal post specified is the cheapest obtainable. There is, however, a similar post having two holes, and this would be an extremely worthy substitution, as will become apparent when you start adapting the E-Z Change units to different circuits. Auxiliary and external apparatus, of

(Continued on page 556)

It's a Cinch to Try Out The NEW CIRCUITS With These Units

By WILLIAM J. VETTE

Here's a simple idea which will make it easy to try out the various new circuits. The author provides "coil" and "tube" units fitted with numbered binding post terminals leading from all the socket contact springs. Connections can be made by means of flexible insulated wire.

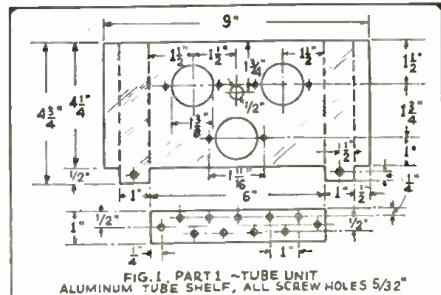


FIG. 1, PART 1 - TUBE UNIT
ALUMINUM TUBE SHELF, ALL SCREW HOLES 5/32"

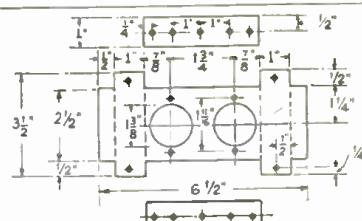


FIG. 1, PART 2 - COIL UNIT

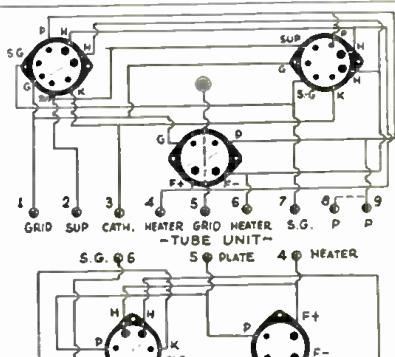


FIG. 2 - TUBE SOCKET GUIDE

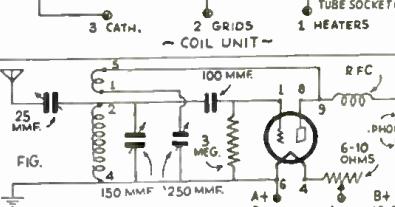


FIG. 3


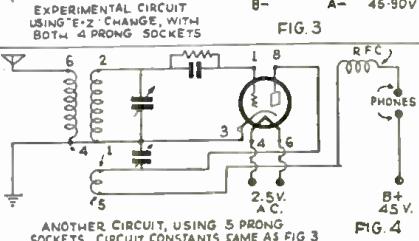


FIG. 4

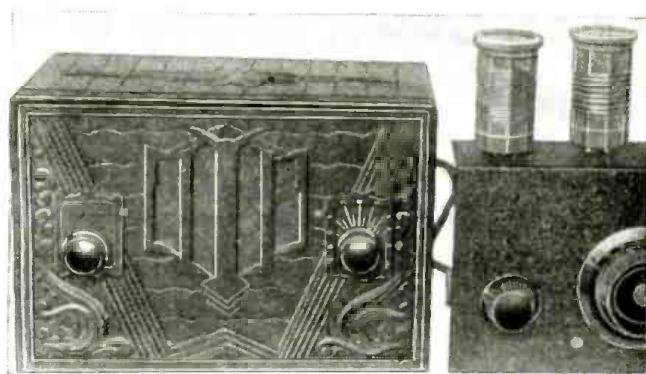Above: Dimensions for making the "coil" and "tube" units. Also, two hook-ups for "E-Z" receivers are shown, the numbers referring to the binding posts on the units.



Above—Appearance of the amplifier and power-supply unit with built-in speaker, connected to 2-tube S-W receiver. Photo at right shows rear view of amplifier and power-supply unit.

• IN the article in the November issue, a schematic diagram was given showing how to add a second stage to the "two-tube all-electric" receiver. No doubt the reader will recollect that this merely involved the addition of a 38 tube together with a few fixed resistors and fixed condensers. The actual physical appearance of this set is shown in the accompanying illustration.


Actually a set having two audio stages is powerful enough to operate a loudspeaker. In fact, this set is strong enough to operate a dynamic speaker, the only difficulty being that the 37 rectifier cannot pass enough current to supply both the set and the speaker field. Consequently, this set is restricted to magnetic speaker operation, except where a dynamic speaker is available which has a *separate source* of field supply. Where the set is to be operated on *direct current*, it is a simple matter to rig up a small filter and thus supply the speaker field independently. On alternating current, however, an A.C. type speaker would be necessary and this would involve an unwarranted expenditure.

In using this receiver on alternating current, the hum may be annoying when earphones are used instead of a speaker, due to the increased amplification. If such trouble manifests itself, the remedy is to increase the filtering action by adding electrolytic condensers on either side of the

An All-Electric Amplifier and Power Supply


By H. G. Cisin, M.E.

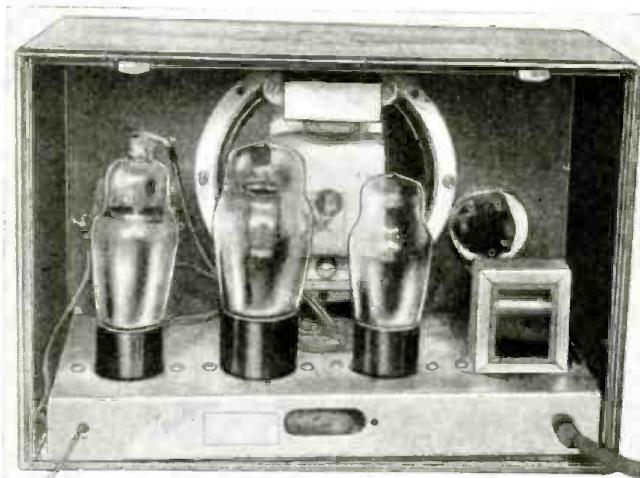An amplifier for the 1 - 2 and 3 tube All-Electric sets—Part 3 of "standardized radio for the short-wave constructor."



choke. The best values can readily be determined by a little experimentation.

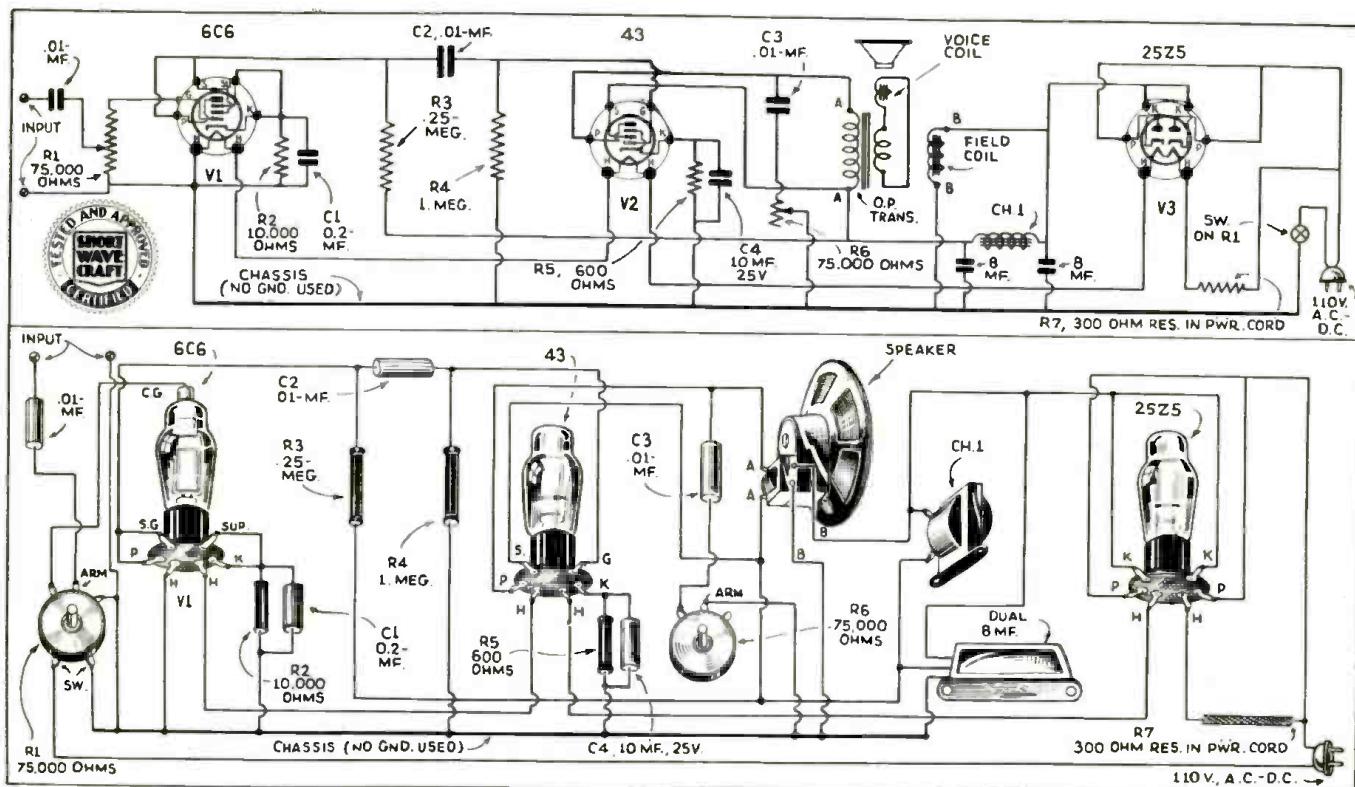
Now we come to the description of a device which can be used in conjunction with any of the sets described in this or previous articles. This is an inexpensive *all-electric amplifier*. The writer has received many requests for information regarding this amplifier (*Continued on page 566*)



Here we have the wiring diagram for the All-Electric amplifier and power-supply unit described by Mr. Cisin. This amplifier will work out of the detector stage of practically any short-wave receiver.

WHAT'S NEW

In Short-Wave Apparatus

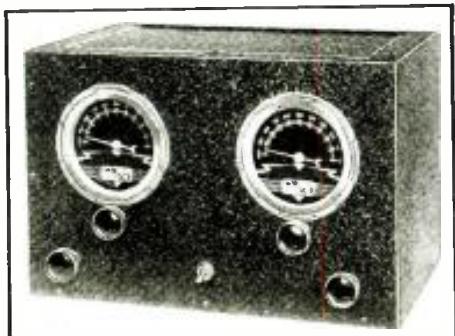

Front view of the Lafayette 2.5 and 5-meter superhet receiver.

● FULL advantage is taken of the excellent characteristics of the type 954 "Acorn" tube in the new two and a half and five-meter "Lafayette" superheterodyne receiver, recently brought out.

Examination of the accompanying diagram reveals that this receiver employs a type 954 "Acorn" pentode in a tuned R.F. stage, followed by another 954 as a tuned autodyne detector. Two 6D6 I.F. stages, a 41 second detector and semi-automatic volume control tube and a 42 output tube com-

2.5 and 5-Meter Superhet.

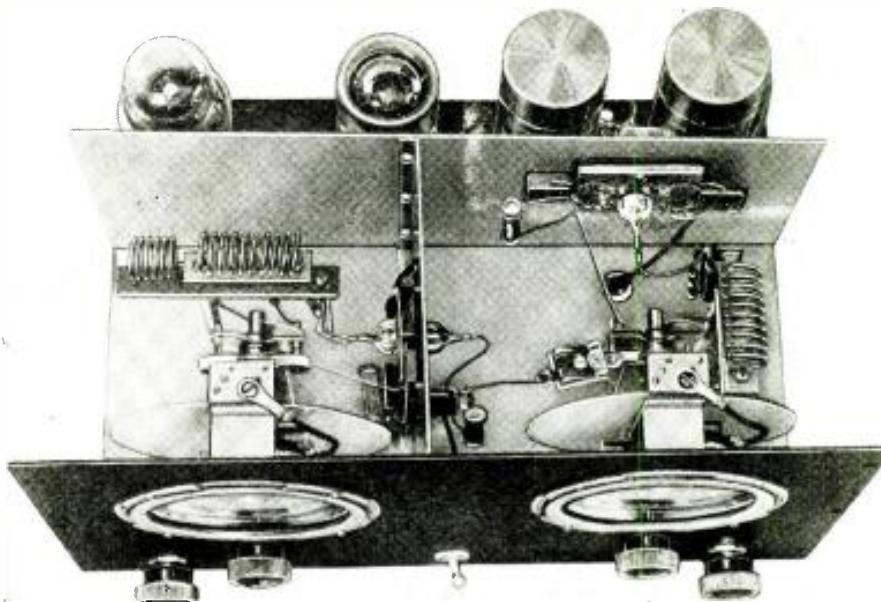


Photo above shows combination front and top view of 2.5 and 5-meter superhet, while diagram of the receiver appears at the left.

plete the circuit. The action of the autodyne detector is controlled by a 50,000-ohm potentiometer in the screen circuit, while audio volume is regulated by a one-half megohm potentiometer between the 41 and 42 tubes.

Due to the internal construction and design of the 954's, very little noise that is due to thermal agitation is heard in this set. Although the overall gain is much higher than in conventional superregenerative receivers, the background noise is at a very much lower level.

Although six tubes are used, the entire


(Continued on page 571)

Noise-Reducing Aerial

● THE All-Wave Aerial shown is a noise-reducing, high-efficiency system for reception of both broadcast and short wave. The system comprises a group of resonant circuits which are responsive to various frequency bands within the short-wave ranges, as well as complete frequency re-

sponse in the broadcast band. For example, the 17-foot section is resonant to a quarter wave length of the 15-megacycle band. The entire length of 60 feet is resonant to a half wave length in the 6-megacycle band. The 43-foot section is resonant to a quarter wave length somewhat below 6 megacycles. The combination of condensers, transformers and transmission line affords various other resonant points throughout the short-wave range. The result is that the antenna system is completely or partially resonant at almost any frequency within the short-wave broadcast transmission band. It likewise affords the high efficiency that a carefully installed antenna of the untuned type would for the other frequencies. When the set switch is placed in the broadcast position instead of the short-wave position, the system is then resonant to all frequencies within the broadcast band.

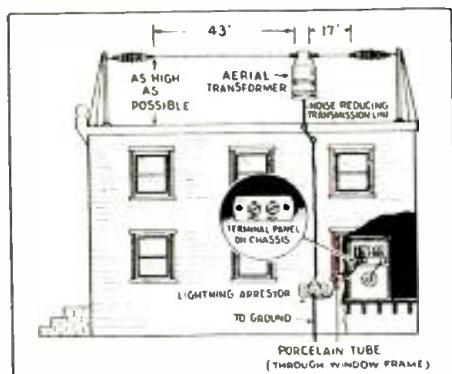The set transformer is equipped with a switch having two positions—one for short waves and the other for standard broadcast. By adjusting the antenna system in this way for short-wave reception or for broadcast reception, the utmost efficiency is thus obtained. In the new All-wave An-



Arrangement of short and broadcast wave aerial supplied by one of the leading set manufacturers. (No. 328.)

(Continued on page 558)

New Line Filter

● THE new service line filter has a brand-new feature, in that it is adjustable for each individual installation, by means of a small set-screw provided on the front of the filter. The filter is very easy to install, the plug from the set being inserted in the outlet on the filter box, while the rubber-

(Continued on page 560)



A new "adjustable" Line-Filter or balancer which is connected between the A.C. line and the receiver itself. (No. 513)



Front view showing the control panel of the new RCA AR-60-S Communications Receiver.

In the photo herewith we see the new RCA AR-60-S Communications Receiver which represents the last word in radio design. This receiver uses 11 tubes. The functions of the various tubes are as follows: Two 6DG's are used as R.F. amplifiers ahead of the first detector, which is a 6C6; another 6C6 is used as a high-frequency oscillator, and the voltage of this tube is regulated by an RCA 991 Regulator Tube; two more 6DG's are used as I.F. amplifiers, feeding into a 6B7, which functions as the third stage of I.F. second detector and AVC.


From this, we go into a 6F7 which is used as a combination audio frequency amplifier and CW beat oscillator. The audio output tube is a "41," and the rectifier is an indirectly heated cathode tube, type 84.

Glancing at the diagram it appears that the 11 tubes actually perform the duty of 14. The manufacturers claim that the sensitivity of the receiver is limited only by tube noise originating in the first tube and


11-Tube Communications Receiver—Range 1.5 to 25 mc.

its associated circuits. A large part of this noise is due to thermal agitation in the first tuned circuit. Being designed for communication purposes, the set naturally has band-spread, and this is of the type which allows full coverage and band-spread at any frequency within the range of the receiver. It is also equipped with a crystal filter, thus allowing extremely high selectivity, together with "single-signal" reception. Band switching is arranging so that all one needs to do, when changing from one band to another, is to "flip the switch," located directly under the tuning dials, to anyone of the six bands which the set takes in. The tuning range incidentally is from 1,500 to 25,000 kilocycles in the following steps: 1.5-2.29 megs., 2.29-3.63 megs., 3.63-5.65 megs., 5.65-9.25 megs., 9.25-15.2 megs., and 15.2-25 megs. As can be seen from the photograph, a great many switches and knobs are located on the panel. Every circuit that needs adjustment has a knob or control on the front panel, greatly simplifying the operation of the receiver.

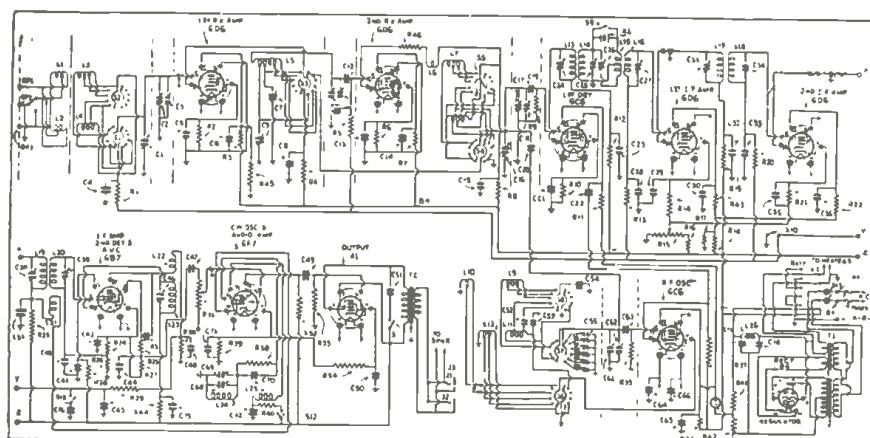This receiver can be operated from a 110-volt or 240-volt 60-cycle alternating current supply or from batteries, as explained in the instruction book supplied by its sponsors, the RCA (Continued on page 551)



Wiring diagram of the new RCA Receiver.

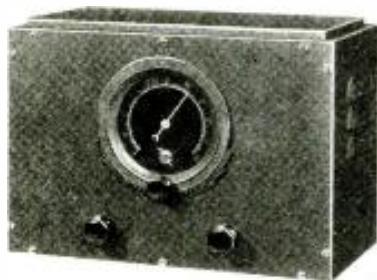

Front view of the Miller preselector.

of either 1800 or 2200 kc. The higher frequency setting of the oscillator is usually used. The 2200 kc. oscillator will also beat with any signal at 2400 kc. unless we take precautions against allowing frequencies of 2400 kc. to reach the oscillator. The undesired response is sometimes called the *image*.

In receivers where the signal circuit tuner consists of a single-tuned circuit connected to an antenna, the selectivity of such a setup is very broad and signals far off resonance will be passed. In the above example a signal of 2400 kc. would be heard along with the desired 2000 kc. signal. This is why we hear a lot of interference on signals, that is not due to the supposition that the signals are near each other in frequency but that they are *twice the intermediate frequency* apart. Many listeners suffer along, listening to short-wave broadcasts that are all smeared with code signals, thinking that the code is on the same frequency, when the fault is in their receiver and could be corrected by the use of a good *preselector*.

All superheterodynes that have no preselection suffer from this sort of interference, especially on the *short waves*.

It can be seen that no matter how good the selectivity of the intermediate ampli-


A 3-Tube Preselector

IN all superheterodynes the local oscillator can be tuned to either of two frequencies that are an intermediate frequency higher or lower than the signal frequency. For example, we have an intermediate amplifier of 200 kc. and a signal of 2000 kc., so we must use an oscillator frequency

fier, the image response will come through, without *preselection*.

Modern receivers have increased the intermediate frequency to a point just outside the broadcast band about 500 kc. and this makes the image response 1000 kc. away from the signal. This improves the situation at comparatively low signal frequencies, but when we tune in signals in the high-frequency spectrum the image is comparatively close to the signal. For instance, with a signal of 20,000 kc., the image, with a 500 kc. intermediate, is 21,000 kc. and the detector circuit cannot eliminate it, so that in modern receivers preselection is absolutely necessary. If the modern receiver did not have to tune continuously through the broadcast band up to the neighborhood of 25,000 or 30,000 kc., a higher intermediate frequency could be used, which would put the image farther away from the signal. Receivers that are made to receive high frequencies, only, take advantage of this point, but an all-wave receiver cannot.

(Continued on page 565)

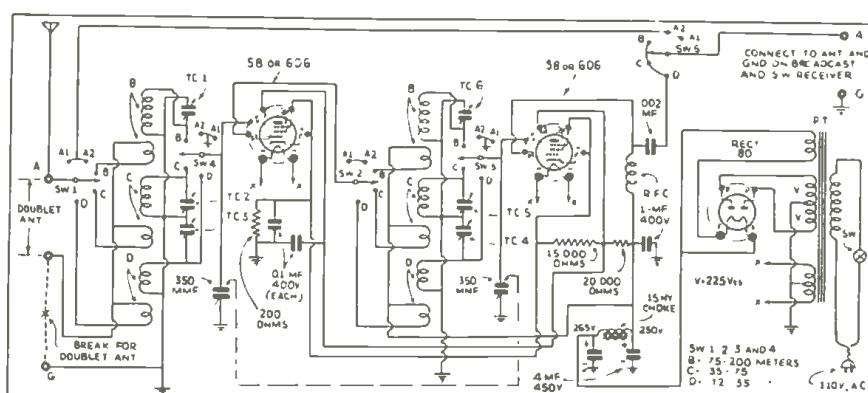

Wiring diagram of the 3-tube preselector.

Names and addresses of manufacturers of apparatus described on this and following pages furnished upon receipt of 3 cent stamp; mention No. of article.

NEW APPARATUS FOR THE HAM



5-Meter Antennas (H-25)

Adjustable U.H.F. Antennas H-25


Here is a complete set of adjustable ultra high-frequency antennas which should prove very interesting to the amateur. As can be seen in the photograph, several different types are manufactured. They are constructed of aluminum and are telescoped, with a hard metal locking sleeve to insure good contact at the joint. Lying horizontally at the base of the photo is a partial view of a complete doublet with the central insulating block clearly shown.

Dial and Knob for Ham Set H-26

These dials will beautify any Ham transmitter or similar apparatus. They are of attractive satin finish, with black numbers and graduation marks on a chrome silver background. The knob is a large type with a flange, providing a very comfortable grip. These are available in 2", 3½" and 4" diameters with various scale readings.

The readings are 0 to 100 with a 180-degree swing and 0 to 100 with a 325-degree swing. Bar type bakelite pointer knobs and the usual round finger-grip knob with pointer are also available to take the place of the flange-type knob shown in the photograph.

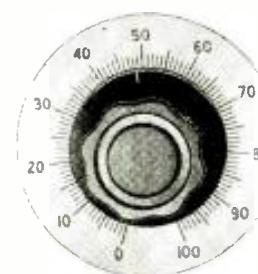They are made with several different mounting arrangements.



New dial. (H-26)

Practical 5-Meter Antenna Design

IT IS DOUBTFUL that any group of radio amateurs in the country has been more active, during the past year and a half, than the Garden City Radio Club. This organization has made a very definite study of ultra-high-frequency operation and it has gone to considerable expense to prove certain theories by working them out practically. Members of the Club have been very active in arranging ultra-high-frequency tests between ground and aircraft and between fixed and mobile stations.

It has long been recognized by the Club that 5-meter operation in a large city is vastly different from such operation in flat unobstructed areas. The Club's urban activities have been placed in charge of the present author and in order to draw satisfactory conclusions, good and poor 5-meter locations have been chosen and the following interesting results have been obtained, with receiving antennas.

It may be that the work we have done

Various Types of Aerials Used at W2DLG and W2DKJ and the Results Obtained


By Arthur H. Lynch

will be of some benefit to others who contemplate 5-meter activity. We have discovered no new principles. In fact, a recent rereading of "Below Ten Meters" prepared by James Millen and S. Kruse, some time ago, indicates that nearly all of the present ultra-high-frequency operation is along lines which were fairly well understood many years ago. It is, rather, with the idea of enabling the beginner on five meters to eliminate much of the guesswork, that we recount our own activities.

It has been our belief that fair distances can be covered with moderate power, provided aerials of suitable design were used. We have never looked upon the method of getting long distances by the expedient of using high power as being very intelligent when, with moderate power and careful attention to antenna design, the same result can be accomplished, at a much lower cost. Much cutting and trying will be eliminated if the newcomer to five meters will first read "Below Ten Meters" because there is more real dope packed into that one little publication, than can be dug up from a whole group of texts.


For our receiving antenna, after observing 5-meter performance in various sections of New York City, we realized that for suitable metropolitan coverage, it would be desirable to secure a location having reasonably good altitude.

Through the good offices of Eli M. Lurie, (Continued on page 552)

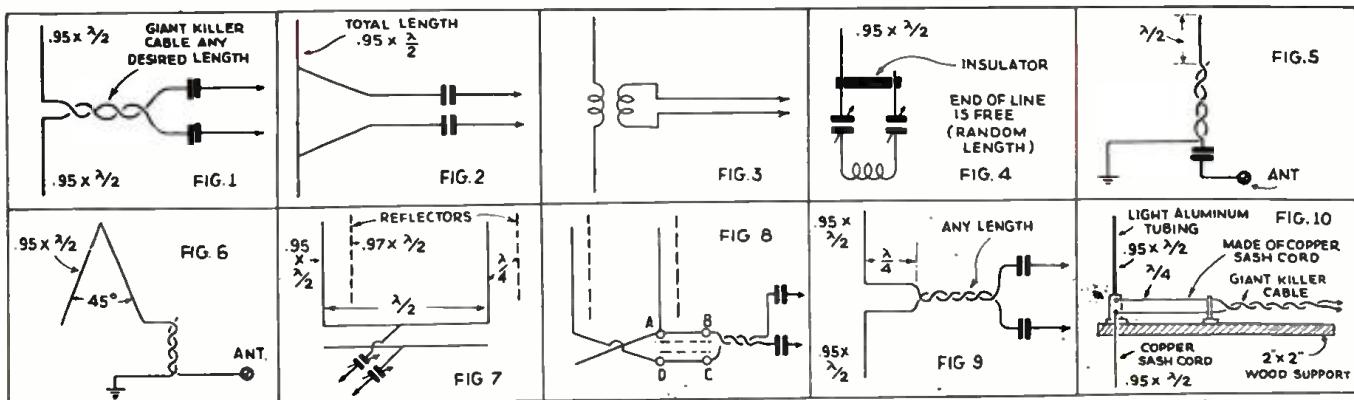

Various 5-meter aerials described by the author.

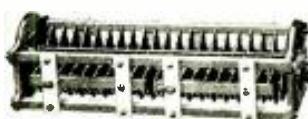Names and addresses of manufacturers of apparatus described on this and following pages furnished upon receipt of 3 cent stamp; mention No. of article.




Transmitting Condenser H-27

This is a really rugged and well-designed dual-transmitting condenser. The frame is made of heavy cast aluminum with plates of extremely high polish and with rounded edges. This new Hammarlund product can be obtained in capacities ranging from 50 to 500 mmf. per section. With the two sections in series the breakdown voltage is 13,000 volts.

With a split-stator condenser of the type shown, R. F. burns and body-capacity effects are eliminated when the two sections are connected across the coil and the rotor grounded to the "B" negative side of the circuit, thus permitting precise adjustment.

Flexible Shaft Coupling H-28

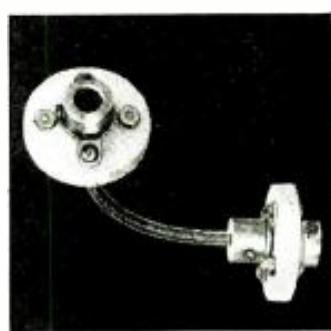This new National flexible shaft coupling unit is ideally suited to cases where the driving adjustment and instrument shafts are offset up to angles of 90 degrees. This virtually eliminates all aligning problems.



Flexible coupling. (H-28)



Transceiver hand-set. (H-29)

THE RADIO AMATEUR

Conducted by Geo.W.Shuart

Radio Amateur Course

● THIS is the fifth lesson in our *Radio Amateur Course*, and will deal with radio and audio frequency, class "A" and "B" amplifiers, and radio frequencies, class "B" and "C" amplifiers, together with frequency multipliers. The first type of amplifier that the average radio experimenter comes in contact with is the well-known *Class "A" audio amplifier*. In our previous lessons discussing the vacuum tube action, we clearly explained the functions of the cathode grid and plate, also just how the changes in grid potential effect changes in plate current, thus amplifying the signal.

When reading the following descriptions of amplifiers, it is well to review the previously described actions of the various elements in tubes because these will not be taken up again in detail, and a perusal of the lesson on tubes will greatly aid in obtaining a clear mental picture of various types of amplifiers.

In Figure 1-A, the tube is operated under conditions so that the output is an exact replica of the input signal. It can, therefore, be said that the tube is operated on the flat portion of its grid-voltage plate-current curve. By examining the drawing at Figure 1-A, we see that the grid never goes sufficiently negative to reduce the plate current to zero, and it is also not allowed to go positive; if it were, the grid would draw current on the positive peaks, and this is not desirable in the usual Class "A" amplifier.

Class "A" Amplifiers

Class "A" amplifiers are capable of really faithful amplification, but are quite inefficient, insofar as power conservation is concerned. Usually these

In this, the fifth lesson of the Radio Amateur Course, Class "A", "B" and "C" amplifiers are discussed. Also frequency multipliers and modulated Class "C" amplifiers are explained.


amplifiers are about 50 per cent efficient. In Figure 2-A we have in a 1-tube audio frequency Class "A" amplifier circuit. In figure 2-B we have an amplifier of the push-pull variety wherein two tubes are used, each operating on alternate half cycles of the input signal. In Figure 1-B we have a diagram of the characteristics of a Class "B" radio frequency amplifier. The operating characteristics are essentially the same as a Class "B" audio amplifier, only in the R.F. amplifier, as indicated, the frequency is constant and the amplitude of it is varied by modulation. This is said to be a *Linear amplifier*.

In a Class "B" audio amplifier, the frequency would vary. However, the essential functions are the same. We find that the bias is such that it allows the grid to become positive on one-half of the incoming signal, running the plate current way up. On the negative half of the cycle in the R.F. amplifier, we find that the plate current is zero and remains zero through the entire 180 degrees of the negative grid swing, and then it begins to rise as the grid again goes positive. It can thus be seen that plate current flows over the 360 degrees of the grid swing in Class "A" amplifier, and only


180 degrees of the grid swing in a Class "B" amplifier. Now, in an audio system, it is essential that we reproduce an exact replica of the incoming signal; that is why in Class "B" amplifiers intended for audio frequency use, we use push-pull in order to reproduce *both halves* of the incoming signal.

Class "B" Amplifiers

In R.F. amplifiers wherein the variations in amplitude of a constant frequency carrier constitutes our audio frequency signal, we do not need push-pull, because if we refer to Figure 1-D, we will see that a complete A.F. variation is present on the one-half, although two tubes are often used in the Class "B" R.F. amplifier. This is only done to increase the power output. We can very easily see why only one-half of the modulated R.F. signal is needed; because of the action of our detector, really only one-half of it is used anyway. In Class "B" amplifiers of all descriptions, the grid-bias is adjusted so that the plate current is zero or nearly zero with no signal present in the grid circuit. In the now popular Class "AB" or "A" prime, audio frequency amplifiers, plate current flows throughout more than 180 degrees of the input cycle but less than 360. This means that the plate current may fall to zero and remain zero for just a small portion of the input cycle. In Figures 1-E, F and G, we clearly show how in the Class "A" amplifier, the plate current is continually flowing, and in the Class "B" amplifier, it only flows through 180 degrees of the input cycle, while on Class "C" amplifier, which is next to be discussed, on less than 180 degrees of the input cycle.

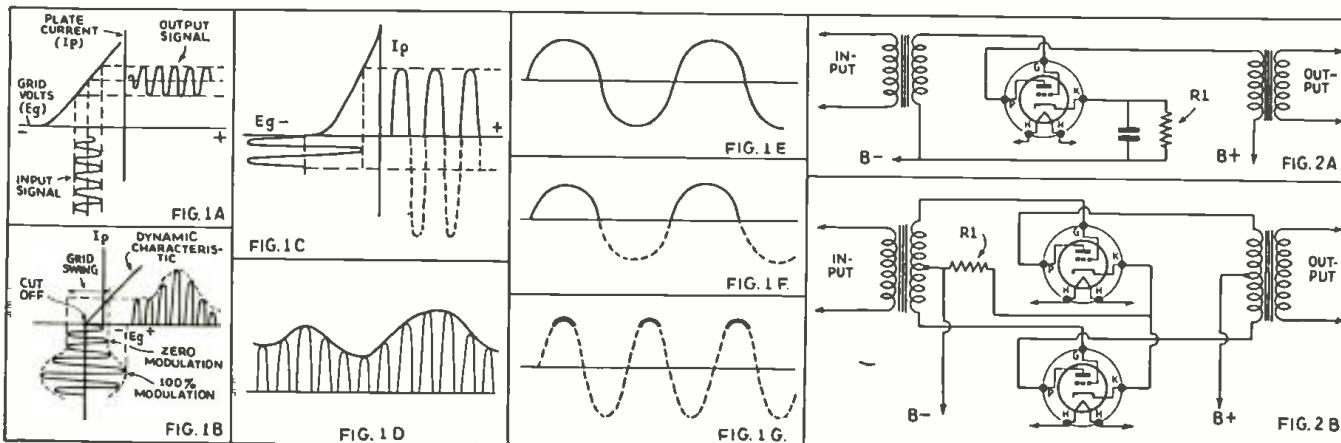

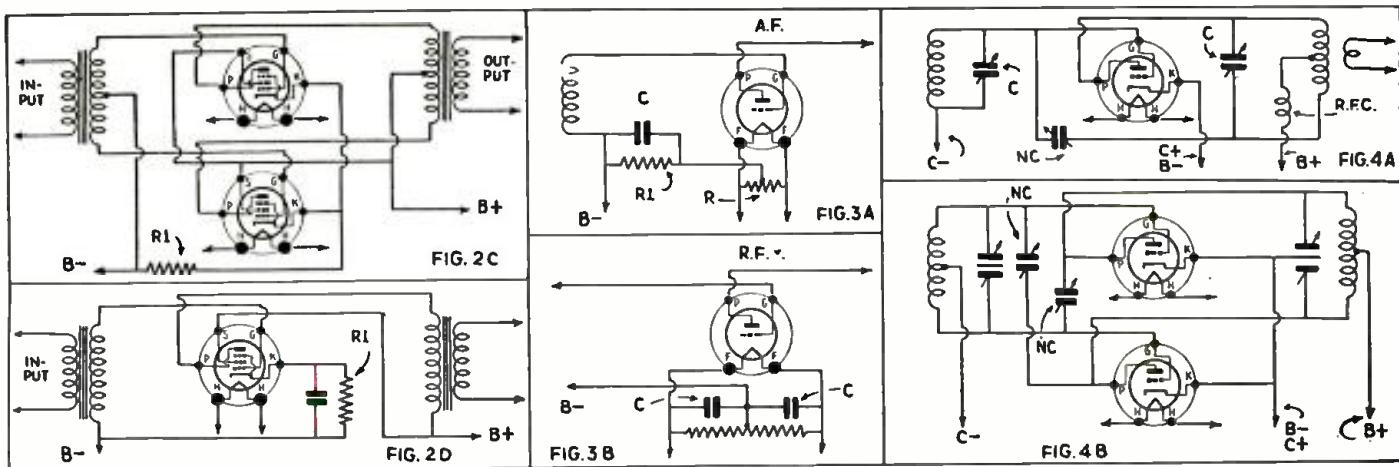The above drawings show characteristics of Class "A," "B," and "C" amplifiers, together with amplifier diagrams.



Diagrams of pentode A.F. amplifiers, single and push-pull, together with neutralizing single and push-pull R.F. amplifiers.

Class "C" Amplifiers

Class "C" amplifiers are usually used only for radio frequency amplification because of the tremendous amount of distortion which is present in the output wave. In Class "C" amplifiers, the bias is increased to about two times the value necessary to bring the plate current to zero. This means that a greater amount of excitation is required in order to make the plate current flow. This requires, of course, that the grid be driven considerably positive. Vacuum tubes operated in the Class "C" category are capable of tremendous power output as compared to a Class "A" or "B" amplifier, and are usually quite a bit more efficient, insofar as plate-power conversion is concerned. Efficiencies as high as 85 per cent are quite easily obtained. Of course, the ratio of power amplification is reduced considerably in a Class "C" amplifier, because of the fact that plate current only flows on a small portion of the input cycle and because a Class "C" amplifier requires a good deal more excitation.

A class "C" amplifier in a radio frequency phone transmitter is modulated directly, i.e., a powerful modulator is used to vary the plate input to the tube at audio frequencies, while a Class "B" amplifier used in a phone transmitter is not modulated directly, but a low-power, class "C" amplifier which is modulated at voice frequencies, is used to drive the Class "B" linear R.F. amplifier. While the Class "B" amplifier is not

as efficient as the Class "C" amplifier, it introduces a considerable saving in the cost of modulator equipment, because a fairly low-power stage is modulated, and the Class "B" amplifier is merely used to amplify the modulated output of this low-power stage.

The next lesson will describe a M.O.P.A. (Master Oscillator-Power Amplifier) transmitter—using a crystal oscillator, a frequency multiplier, a buffer and a power amplifier. Thorough outline of the tuning and operative procedure will be given.

Efficiency in Power Output


Efficiencies of around 70 per cent may be secured from a Class "B" amplifier with 100 per cent modulation on the driver stage, although an unmodulated Class "B" amplifier would be only about 35 per cent efficient. Speaking of plate efficiency or power conversion in the plate circuit of the vacuum tube, we mean the "power" output divided by the power input,

times 100. For instance, if we have an amplifier with a power input of 100 watts and an output of 75 watts, we would have an amplifier which was 75 per cent efficient, the output being 75 per cent of the total plate input.

In figures 1-C and 1-G, we have illustrations of the operation of a Class "C" amplifier. To the lay reader, Figure, 1-G would probably be the clearest, because herein we find a clearer picture, showing that the plate current flows on a very small portion of the input cycle. In Figures 2-C and 2-D, we have pentodes used as audio frequency amplifiers. Bias for these is obtained by inserting the resistor in series with the cathode, or if it is a filament type tube, a center-tapped resistor is needed, as shown in Figures 2-A and 3-A. In an R.F. amplifier, usually the center-tapped resistor is bypassed with two condensers, as in Figure 3-B. Resistors "R" in Figure 2-C, 2-D, and 3-A, are the self-biasing resistors.

Neutralizing

With a triode used as a radio frequency amplifier and where the input and output circuits are tuned to the same frequency, a method of overcoming self-oscillation is required. This is accomplished by neutralizing as shown in Figure 4-A. What we have done here is to center-tap the plate coil, making the two ends out of phase 180 degrees. Then a small condenser is connected between the grid of the tube and the end (Continued on page 561)

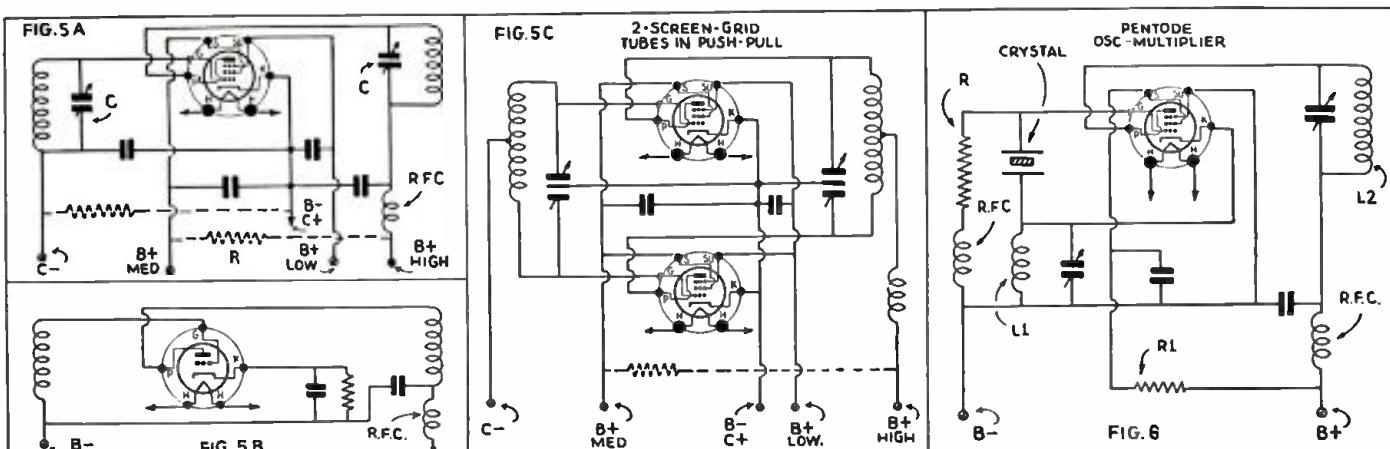

Pentode single and push-pull R.F. amplifiers and crystal oscillator-frequency multiplier diagrams.



Front view of 20-watt transmitter using all receiving parts

- LOW cost and high efficiency is the cry of the young Ham. Still, when building his transmitter he should have a quality piece of apparatus capable of putting out a fairly strong signal of the highest quality—a signal that meets with the present Government requirements. The first thought is toward receiving type tubes. Of these we have built plenty of transmitters and obtained excellent results. In most cases though, we have not had the latest in quality and simplicity. Most low-power transmitters use triodes or pentodes which require neutralizing and this makes a messy job of shifting bands.

The "89" Tube a Daisy!

There is one tube which is comparatively unknown amongst the amateurs and this is the type 89 intended for audio frequency amplification either as a pentode, triode, or class A and B amplifier. The tube is almost an exact duplicate of the type 59, well known as a crystal oscillator and frequency multiplier. The 89 differs from the 59 in that the control-grid connection is brought out the top of the bulb much

the same as screen-grid tubes. The 89 is rated at somewhat lower-power input than the 59, but tests have shown that it will do just about all a 59 will, and besides has many advantages not found in the 59. In the first place the 89 can be used as a screen-grid R.F. amplifier on all frequencies up to 125 megacycles! And by good authority we have been informed that it will stand up to 8 watts plate dissipation and 1.4 watts for the screen-grid! This makes it a rather "husky" tube for low-power transmitters and exciter units.

Three type 89's are used in this transmitter, one as a crystal-controlled "tritet" oscillator and two in push-pull as screen-grid R.F. amplifiers. No neutralizing whatsoever is necessary and the amplifier operates as "stable" as any we have ever come in contact with; there is not the slightest trace of a tendency toward self-oscillation. The transmitter will work on any two bands with one crystal. For 80 and 40 meters an 80-meter crystal is used; on 40, the plate circuit of the oscillator takes care of the frequency doubling and the amplifier is provided with plenty of

excitation. The 89 is the *berries* for tritet oscillators and frequency multipliers!


Actual Tests Showed Superior Results

It might be well to "take time out" and say that two of these transmitters were built; one to operate on the low-frequency bands and one for the 5-meter band. And with the push-pull amplifier running on 5 meters with 500 volts on the plates and a total of 50 mills plate current, 14 watts output was obtained and the tubes showed no signs of being overloaded. In fact, this is still within the plate dissipation value previously given. This 5-meter transmitter will be described in an early issue.

The low-frequency transmitter herein described gave an output of approximately 20 watts with 35 watts input—500 volts at 70 mills (M.A.); higher inputs gave little increase in output and would materially shorten the tube life. Neither of the transmitters required any shielding, not even tube shields. By all means do not employ tube shields, because the tubes become very warm in operation and the shield would only hinder heat radiation and cause trouble.

The Hook-Up

Looking at the circuit diagram, we find a conventional tritet oscillator, inductively coupled to the amplifier. The values of condensers and resistors indicated in the diagram, have proved optimum and should not be changed. The same power supply is used for both the oscillator and amplifier; the oscillator voltage being reduced slightly with a series resistor. There is also a separate voltage-dropping resistor for the screen voltages of the two stages. The screen voltages are kept quite low in order not to shorten the tube life.

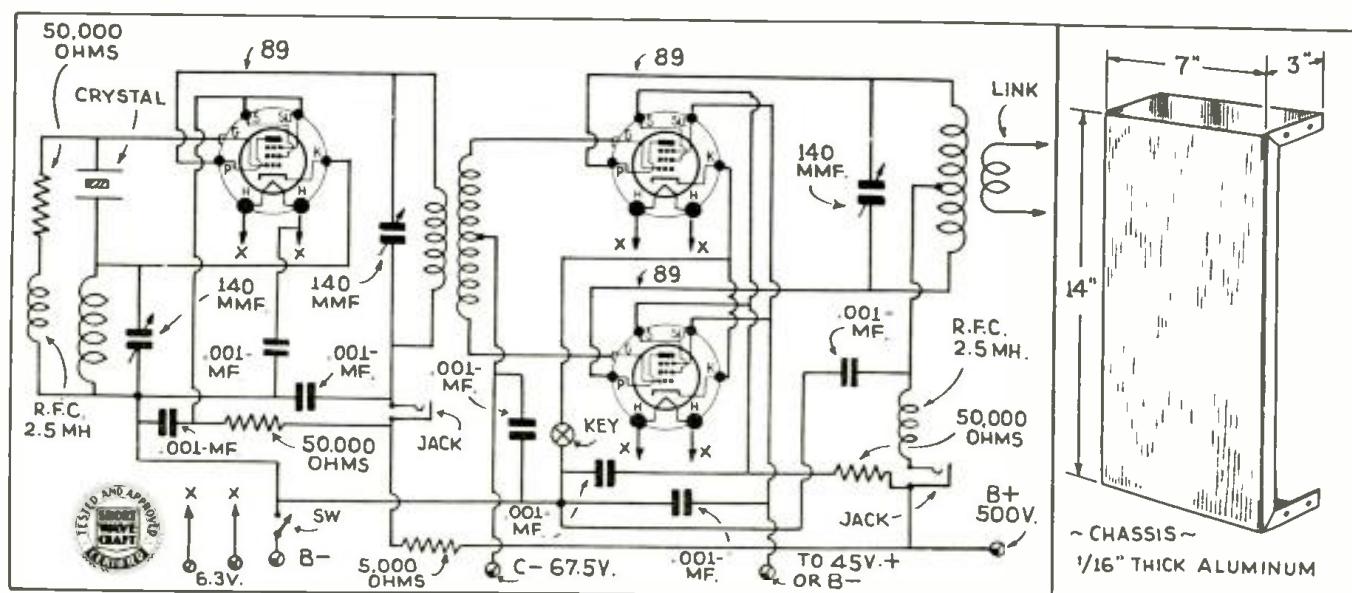

Circuit diagram and chassis details of 20-watt transmitter.

TRANSMITTER

Made from Receiver Parts

It is at last possible, thanks to W2AMN, to build a transmitter almost entirely of receiving parts and one which is not really "flea power." This one uses 3 type "89" tubes, one as a crystal-control oscillator, and two in a push-pull, screen-grid amplifier circuit. It is capable of transmitting a high-quality signal, and has an output of 20 watts! It operates on 80, 40 and 20 meters. Believe it or not, it can be built for less than a dollar a watt.

Oscillator

In the oscillator we find that the suppressor grid is connected to the screen while in the amplifier the suppressors are either connected to the cathodes (B negative) or a positive potential of from 22.5 to 45 volts. This positive potential gave a slight increase in output but probably not enough to warrant its application.

The three plug-in coils are wound on small National type NR20 isolantite forms, having five prongs. The plate coil of the oscillator is wound on the outside of the form while the grid coil of the amplifier is wound on a short length of one-inch tubing and placed inside of the coil form. This coil is wound with fine wire and is untuned much the same as in TNT circuits. The tuning condensers are all midget receiving condensers, having 140 mmf. capacity.


Aluminum Chassis Used

The entire transmitter is mounted on an aluminum chassis 7 inches wide, 14 inches long, and 3 inches high; along one side of the chassis is mounted a bakelite strip to accommodate the 0-100 scale milliammeter and the various jacks and power switch. By this plug arrangement only one meter is needed, thus lowering the cost of the parts. All by-pass condensers are mounted under the chassis and the leads feeding it are by-passed right at the point where they come through the chassis.


Looking at the photo of the top view we have the oscillator grid-coil and the crystal on the extreme left, and the es-

cillator tube behind the tuning condenser. The oscillator plate coil and its tuning condenser are in the center with the two amplifiers next, and the plate tuning condenser between them and the plate coil. The output link which is supported around the plate coil with standoff insulators, serves to couple the antenna or another amplifier stage. With the plate voltage reduced on the oscillator the plate current will be low. The plate current when operating on the crystal frequency will be around 20 mills (M. A.) and slightly higher when operating on the second harmonic of the crystal fre-

quency. The plate condenser of the oscillator should be adjusted for minimum plate current. The plate condenser of the amplifier should also be tuned for lowest plate current, this will be around 20 or 25 mills, when no antenna load is present. With the antenna coupled, the current will rise. The coupling should not be adjusted to load the plate circuit up to more than 60 mills (M.A.). With this input (30) watts, the output should be around 20 watts. Tuning is very simple especially as there is no neutralizing required. The key jack is in series with the two cathodes of the amplifier

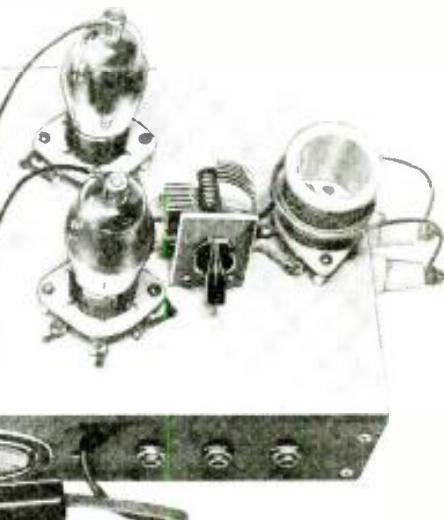

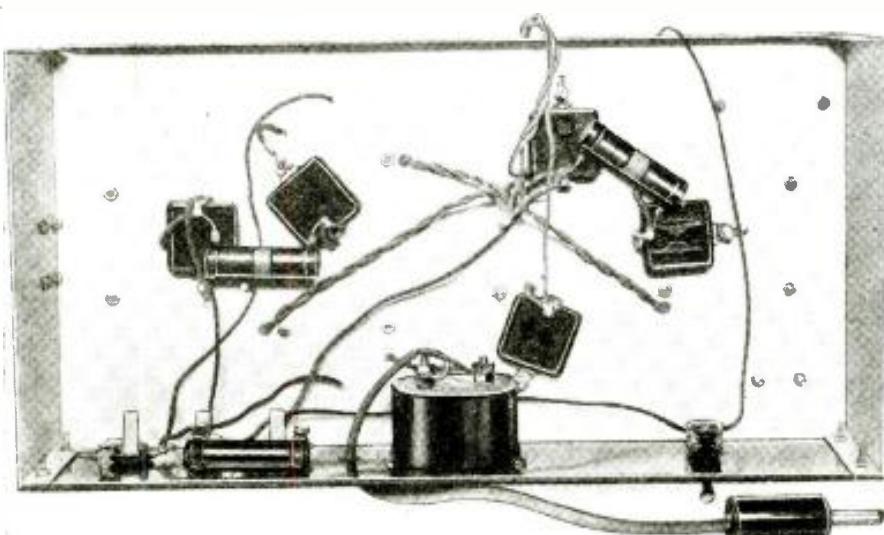Above: Top view showing the placement of parts; note its extreme simplicity.
Left: Bottom View. Only condensers and resistors are placed underneath.



providing very smooth keying.

During a month of operation and testing this little transmitter proved positively practical as a transmitter of high quality and also as a very efficient exciter unit for a higher power stage. In the very near future we will describe an amplifier, antenna network, and power supply which will provide a combination hard to beat.

Parts List for Transmitter

- 1—Aluminum chassis (see drawing), Blan.
- 1—Bakelite panel (see drawing).
- 3—6-prong isolantite sockets; National.
- 4—5-prong isolantite sockets; National.
- 3—110 mmf. condensers; National, type EX.
- 6—.001 mf. 1,000 volt mica condensers; Aerovox.
- 3—50,000-ohm resistors, 20 watt; Aerovox.
- 1—5,000-ohm resistor, 20-watt; Aerovox.
- 2—R.F. chokes, National R100.


(Continued on page 564)

By George W. Shuart,

W2AMN




\$5.00 Prize

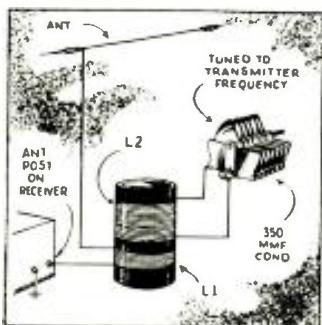


AID FOR DUPLEX

Duplex operation may be greatly aided by means of an inductively-coupled wave-trap as shown in the diagram. The coupling between L1 and L2 may be varied to increase the selectivity of the circuit or to increase the effect of the trap, so that the trap will weaken the transmitter signal without seriously affecting the strength of the incoming signal. L1 should generally be about $\frac{1}{4}$ the number of turns of L2. Approximate dimensions of L2 are: For 160 meters, 25 turns; for 80 meters, 10 turns; for 40 meters, 5 turns; for 20 meters, 3 turns—all on 3" diameter form and wound with No. 20 or larger wire.—Roger E. Farmer.

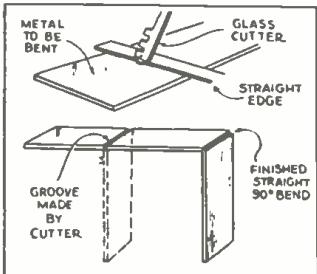

HOME-MADE SHIELD CANS

Here's how to use a glass-cutter to very good advantage in making "commuter-looking" square shield cans for that superhet you're building, or for any other purpose—all from aluminum 3-32" or under. First get a straight edge and place against line to be bent, then glass cutter with plenty of pressure run back and forth against straight edge, until an impression of about one-third the thickness of the aluminum is obtained. Then with the cut side on the outside of the square can, put in line or in between two blocks of wood and bend as per sketch. You will be surprised to see what a perfectly square and straight corner you have. That will make a fine commercial-looking job.—Geo. Kusinich.

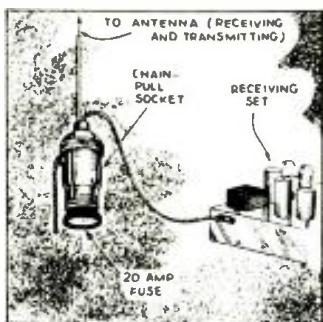

ANTENNA SWITCH


My kink is to use an ordinary lamp socket that has a pull chain device for turning on and off the current. Screw a 20 amp. fuse in the socket to complete the circuit when the switch is pulled to the on position. This device may be mounted alongside the feeder where it enters the room, and ordinary strong twine run from the chain of the socket through eyelets to near the receiving position. All the operator has to do is to pull the twine and he breaks the receiving antenna in order to transmit.—B. S. Krebs-W3EZY.

EARPHONE AS MIKE

I have found that by connecting a 2,000-ohm earphone to the input circuit of the

\$5.00 FOR BEST SHORT-WAVE KINK


The Editor will award a five dollar prize each month for the best short-wave kink submitted by our readers. All other kinks accepted and published will be awarded eight months' subscription to SHORT WAVE CRAFT. Look over these "kinks" and they will give you some idea of what the editors are looking for. Send a typewritten or ink description, with sketch, of your favorite short-wave kink to the "Kink" Editor, SHORT WAVE CRAFT.

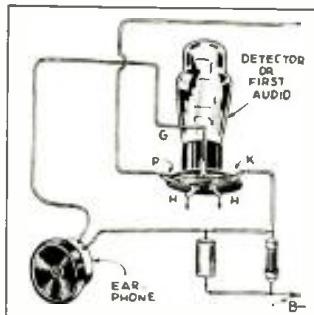

detector or first audio amplifier of my broadcast receiver. It served as an excellent microphone. The diagram clearly shows how it is connected.—Tom Davis.

PLUG-IN SOLDERING IRON

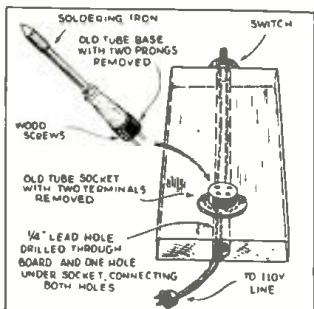
Here is a kink which should find favor among the short-wave experimenters and mechanics. I fastened an old tube-base to the handle of my soldering iron. Then connect the terminals of the socket in series



with the A. C. line and a switch. The drawing clearly shows how the job is done. Be sure the socket will carry the current requirements of the iron.—Clarence Teter.

NOVEL ANTENNA CONDENSER

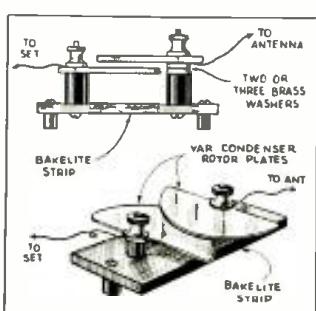As is shown in the drawing, I used two condenser plates from a discarded bridge condenser as an antenna tuner. One is fastened to a bakelite strip, while the other can be moved, thus varying the capacity. A knob attached to the shaft of the movable plate, will be of considerable aid.—Edward Whiges.





Short-Wave Stations of the World

Complete List of Broadcast, Police and Television Stations

We present herewith a revised list of the short-wave broadcasting, experimental and commercial radiophone stations of the world. This is arranged by frequency, but the wavelength figures are also given for the benefit of readers who are more accustomed to working with "meters."

All the stations in this list use telephone transmission of one kind or another

and can therefore be identified by the average listener.

Herewith is also presented a very fine list of police as well as television stations. Note: Stations marked with a star ★ are the most active and easily heard stations and transmit at fairly regular times.

Please write to us about any new stations or other important data that you

learn through announcements over the air or correspondence with the stations themselves. A post card will be sufficient. We will safely return to you any verifications that you send in to us. Communications of this kind are a big help.

Stations are classified as follows: C—Commercial phone. B—Broadcast service. X—Experimental transmissions.

Around-the-Clock Listening Guide

Although short-wave reception is notorious for its irregularity and seeming inconsistency (wherein lies its greatest appeal to the sporting listener), it is a good idea to follow a general schedule as far as wavelength in relation to the time of the day is concerned. The observ-

ance of these simple rules will save time.

From daybreak till 3 p.m. and particularly during bright daylight, listen between 13 and 19 meters (21540 to 15800 kc.).

To the east of the listener, from about 1 p.m.-8 p.m., the 25-35 meter will be found very pro-

ductive. To the west of the listener this same band is generally found best from about 8 p.m. until 9 a.m. (After dark, results above 35 meters are usually much better than during daylight.) These general rules hold for any location in the Northern Hemisphere.

Short-Wave Broadcasting, Experimental and Commercial Radiophone Stations

NOTE: To convert kc. to megacycles (mc.) shift decimal point 3 places to left: Thus, read 21540 kc. as 21.540 mc.

21540 kc. W8XK -B. 13.83 meters WESTINGHOUSE ELECTRIC PITTSBURGH, PA. 7-9 a.m.; relays KDKA	19345 kc. ★PMA -B.C. 15.51 meters BANDOENG, JAVA Calls Holland early a.m. Broadcasts Tues., Thur., Sat. 10:00-10:30 a.m.	17790 kc. GSG -B. 16.86 meters DAVENTRY, B.B.C. BROADCASTING HOUSE, LONDON, ENGLAND 6-8:45 a.m.	15880 kc. FTK -C. 16.90 meters ST. ASSISE, FRANCE Phones Saigon, morning	15250 kc. W1XAL -B. 19.67 meters BOSTON, MASS. Irregular, in morning
21420 kc. WKK -C. 14.01 meters A. T. & T. CO. LAWRENCEVILLE, N. J. Calls Argentina, Brazil and Peru, daytime	19220 kc. WKF -C. 15.60 meters LAWRENCEVILLE, N. J. Calls England, daytime	17780 kc. ★W3XAL -B. 16.87 meters NATIONAL BROAD. CO. BOUND BROOK, N. J. Relays WJZ, Daily exc. Sun. 9 a.m.-1 p.m.	15810 kc. LSL -C. 18.98 meters HURLINGHAM, ARGENTINA Calls Brazil and Europe, daytime	15245 kc. ★ -B. 19.88 meters "RADIO COLONIAL" PARIS, FRANCE Service de la Radiodiffusion 103 Rue de Grenelle, Paris 7-11 a.m.
21080 kc. PSA -C. 14.23 meters RIO DE JANEIRO, BRAZIL Works WKK Daytime	19160 kc. GAP -C. 15.66 meters RUGBY, ENGLAND Calls Australia, early a.m.	17775 kc. PHI -B. 16.88 meters HUIZEN, HOLLAND Used irregularly	15760 kc. JYT -X. 19.04 meters KEMIKWA-CHO, CHIBA-KEN, JAPAN Irregular in late afternoon and early morning	15220 kc. ★PCJ -B. 19.71 meters N.V. PHILIPS' RADIO EINDHOVEN, HOLLAND Sun. 8:30-11:30 a.m. Also Tues. 3-6 a.m., Wed. 7-11 a.m.
21060 kc. WKA -C. 14.25 meters LAWRENCEVILLE, N. J. Calls England noon	18970 kc. GAQ -C. 15.81 meters RUGBY, ENGLAND Calls S. Africa, mornings	17760 kc. DJE -B. 16.89 meters BROADCASTING HOUSE BERLIN, GERMANY 6-11:30 a.m.	15660 kc. JVE -C. 19.16 meters NAZAKI, JAPAN Phones Java 3-5 a.m.	15210 kc. ★W8XK -B. 19.72 meters WESTINGHOUSE ELECTRIC & MFG. CO. PITTSBURGH, PA. 9 a.m.-7 p.m. Relays KDKA
21020 kc. LSN6 -C. 14.27 meters HURLINGHAM, ARG. Calls N. Y. C. 8 a.m.-3 p.m.	18830 kc. PLE -C. 15.93 meters BANDOENG, JAVA Calls Holland, early a.m.	17760 kc. IAC -C. 16.89 meters PIASA, ITALY Calls ships, 6:30-7:30 a.m.	15620 kc. JVF -C. 19.2 meters NAZAKI, JAPAN Phones U.S. 5 a.m. & 4 p.m.	15200 kc. ★DJB -B. 19.74 meters BROADCASTING HOUSE BERLIN, GERMANY 3:45-7:15 a.m., 8-11:30 a.m.
20700 kc. LSY -C. 14.49 meters MONTE GRANDE, ARGENTINA Tests irregularly	18345 kc. FZS -C. 18.35 meters SAIGON, INDO-CHINA Phones Paris, early morning	17310 kc. W3XL -X. 17.33 meters NATIONAL BROAD. CO. BOUND BROOK, N. J. Tests irregularly	15415 kc. KWO -C. 19.46 meters DIXON, CAL. Phones Hawaii 2-7 p.m.	15140 kc. ★GSF -B. 19.82 meters DAVENTRY, B.B.C. BROADCASTING HOUSE, LONDON, ENGLAND 3:30-5:30, 6-8:45, 9-10:30 a.m.
20380 kc. GAA -C. 14.72 meters RUGBY, ENGLAND Calls Argentina, Brazil, mornings	18340 kc. WLA -C. 16.38 meters LAWRENCEVILLE, N. J. Calls England, daytime	17120 kc. WOO -C. 17.52 meters A. T. & T. CO. OCEAN GATE, N. J. Calls ships	15370 kc. ★HAS3 -B. 19.52 meters BUDAPEST, HUNGARY Broadcasts Sundays, 9-10 a.m.	15120 kc. ★HVJ -B. 19.83 meters VATICAN CITY ROMA, ITALY 10:30 to 10:45 a.m., except Sunday Sat. 10-10:45 a.m.
19900 kc. LSG -C. 15.08 meters MONTE GRANDE, ARGENTINA Tests irregularly, daytime	18310 kc. GAS -C. 16.38 meters RUGBY, ENGLAND Calls N. Y., daytime	17080 kc. GBC -C. 17.56 meters RUGBY, ENGLAND Calls Ships	15355 kc. KWU -C. 19.53 meters DIXON, CAL. Phones Pacific Isles and Japan	15090 kc. RKI -C. 19.88 meters MOSCOW, U.S.S.R. Phones Tashkent near 7 a.m. and relays RNE on Sundays irregularly
19820 kc. WKN -C. 15.14 meters LAWRENCEVILLE, N. J. Calls England, daytime	18250 kc. FTO -C. 16.43 meters ST. ASSISE, FRANCE Calls S. America, daytime	16270 kc. WLK -C. 18.44 meters LAWRENCEVILLE, N. J. Phones	15330 kc. ★W2XAD -B. 19.58 meters GENERAL ELECTRIC CO. SCHENECTADY, N. Y. Relays	15070 kc. PSD -C. 19.91 meters RIO DE JANEIRO, BRAZIL Calls N.Y., Buenos Aires and Europe, daytime
19650 kc. LSN5 -C. 15.27 meters HURLINGHAM, ARGENTINA Calls Europe, daytime	18200 kc. GAW -C. 16.48 meters RUGBY, ENGLAND Calls N. Y., daytime	16270 kc. WOG -C. 18.44 meters OCEAN GATE, N. J. Calls England, morning and early afternoon	15280 kc. DJQ -B. 19.63 meters BROADCASTING HOUSE BERLIN, GERMANY 12:30-2 a.m.	15055 kc. WNC -C. 19.92 meters HAILEAH, FLORIDA Calls Central America, daytime
19600 kc. LSF -C. 15.31 meters MONTE GRANDE, ARGENTINA Tests irregularly, daytime	18135 kc. PMC -C. 16.54 meters BANDOENG, JAVA Phones Holland, early a.m.	16240 kc. KTO -C. 18.47 meters MANILLA, P. I. Calls Cal., Tokio and ships 8-11:30 a.m.	15270 kc. ★W2XE -B. 19.65 meters ATLANTIC BROADCASTING CORP. 485 Madison Av., N.Y.C. Relays WABC daily, 11 a.m.-6 p.m.	14980 kc. KAY -C. 20.03 meters MANILA, P. I. Phones Pacific Isles
19355 kc. FTM -C. 15.50 meters ST. ASSISE, FRANCE Calls Argentine, morning	18040 kc. GAB -C. 16.63 meters RUGBY, ENGLAND Calls Canada, morn. and early aftn.	16233 kc. FZR3 -C. 18.54 meters SAIGON, INDO-CHINA Calls Paris and Pacific Isles	15260 kc. GSI -B. 19.66 meters DAVENTRY, B.B.C. BROADCASTING HOUSE, LONDON, ENGLAND 12:15-2:15 p.m.	14950 kc. HJB -C. 20.07 meters BOGOTA, COL. Calls WNC, daytime

(All Schedules Eastern Standard Time)

14600 kc. JVH	12396 kc. CT1GO	11710 kc. ★HJ4ABA	10260 kc. PMN	9580 kc. ★ GSC
-B.C. 20.55 meters NAZAKI, JAPAN Broadcasts Mon. and Thurs. 4-5 p.m. Phones Europe 4-8 a.m.	-B. 24.2 meters PAREDE, PORTUGAL Sun. 10-11:30 a.m., Tues. Thurs., Fri. 11:00-2:15 p.m.	-B. 25.62 meters P. O. BOX 50, MEDELLIN, COLOMBIA 11:30 a.m.-1 p.m., 6:30-10:30 p.m.	-C. 29.24 meters BANDOENG, JAVA Calls Australia 5 a.m.	-B. 31.32 meters DAVENTRY, B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 4:15-5:45, 6-8, 10-11 p.m.
14590 kc. WMN	12290 kc. GBU	11680 kc. KIO	10250 kc. LSK3	9580 kc. ★ VK3LR
-C. 20.56 meters LAWRENCEVILLE, N. J. Phones England morning and afternoon	-C. 24.41 meters RUGBY, ENGLAND Calls N.Y.C., afternoon	-X. 25.68 meters KAHUKU, HAWAII Tests in the evening	-C. 29.27 meters HURLINGHAM, ARGENTINA Calls Europe and U.S., after- noon and evening	-B. 31.32 meters Research Section, Postmaster Gen's. Dept., 61 Little Collins St., MELBOURNE, AUSTRALIA 3-7:30 a.m. except Sun. also Fri. 10:30 p.m.-2 a.m.
14535 kc. HBJ	12235 kc. TFJ	11560 kc. VIZ3	10220 kc. PSH	9570 kc. ★ W1XK
-B. 20.64 meters RADIO NATIONS, GENEVA, SWITZERLAND Broadcasts irregularly	-C. 24.52 meters REYKJAVIK, ICELAND Phones England mornings, Broadcasts irregularly	-X. 25.95 meters AMALGAMATED WIRELESS OF AUSTRALASIA FISKVILLE, AUSTRALIA Calls Canada, evening and early a.m.	-C. 29.35 meters RIO DE JANEIRO, BRAZIL	-B. 31.35 meters WESTINGHOUSE ELECTRIC & MFG. CO., SPRINGFIELD, MASS. Relays WBZ, 7 a.m.-1 a.m. Sun. 8 a.m.-1 a.m.
14530 kc. LSN	12150 kc. GBS	11413 kc. CJA4	10140 kc. OPM	9568 kc. LKJ1
-C. 20.65 meters HURLINGHAM, ARGENTINA Calls N.Y.C., afternoons	-C. 24.69 meters RUGBY, ENGLAND Calls N.Y.C., afternoon	-C. 26.20 meters DRUMMONDVILLE, QUE., CAN. Tests with Australia irregularly in evening	-C. 29.59 meters LEDPOLDVILLE, BELGIAN CONGO Phones around 3 a.m.	-B. 31.35 meters JELOV, NORWAY 5-8 a.m., 11 a.m.-6 p.m.
14500 kc. LSM2	12000 kc. ★RNE	11200 kc. XBJQ	10055 kc. ZFB	9565 kc. VUB
-C. 20.69 meters HURLINGHAM, ARGENTINA Calls Rio and Europe daytime	-B. 25 meters MOSCOW, U. S. S. R. Sun. 6-9, 10-11 a.m., 12:30 p.m. Wed. 5-6 a.m.	-B. 26.79 meters BOX 2825, MEXICO CITY, MEX. Daily 5:30-6:30 p.m., 10 p.m.- 12 m. Relays XEW.	-C. 29.84 meters HAMILTON, BERMUDA Phones N. Y. C., daytime	-B. 31.36 meters BOMBAY, INDIA 11 a.m.-12:30 p.m., Wed., Thurs., Sat.
14485 kc. TIR	11991 kc. FZS2	11050 kc. ZLT4	9950 kc. GCU	9560 kc. ★ DJA
-C. 20.71 meters CARTAGO, COSTA RICA Phones Cen. Amer. & U.S.A. Daytime	-C. 25.02 meters SAIGON, INDO-CHINA Phones Paris, morning	-C. 27.15 meters WELLINGTON, N. ZEALAND Phones Australia and England early a.m. Also broadcasts ir- regularly on Sunday, 9-10 a.m.	-C. 30.15 meters RUGBY, ENGLAND Calls N.Y.C., evening	-B. 31.38 meters BROADCASTING HOUSE, BERLIN 5:05-9:15 p.m. 12:30-2 a.m. 8-11:30 a.m.
14485 kc. HPF	11950 kc. KKQ	11000 kc. PLP	9870 kc. WON	9540 kc. ★ DJN
-C. 20.71 meters PANAMA CITY, PAN. Phones WNC daytime	-X. 25.10 meters BOLINAS, CALIF. Tests, irregularly, evenings	-B.C. 27.27 meters STE. ASSISE, FRANCE Phones CNR morning, Hurlingham, Arge., nights	-C. 30.4 meters LAWRENCEVILLE, N. J. Phones England, evening	-B. 31.45 meters BROADCASTING HOUSE BERLIN, GERMANY 12:30-2 a.m. 3:45-7:15 a.m. 8-11:30 a.m. 5:05-10:45 p.m.
14485 kc. TGF	11940 kc. FTA	10770 kc. GBP	9860 kc. ★ EAQ	9530 kc. ★ W2XAF
-C. 20.71 meters GUATEMALA CITY, GUAT. Phones WNC daytime	-C. 25.13 meters STE. ASSISE, FRANCE Phones CNR morning, Hurlingham, Arge., nights	-C. 27.85 meters RUGBY, ENGLAND Calls Sydney, Austral. early a.m.	-B. 30.43 meters P. O. Box 951, MADRID, SPAIN Daily 5:15-9:30 p.m.; Saturday also 12 n.-2 p.m.	-B. 31.48 meters GENERAL ELECTRIC CO. SCHENECTADY, N. Y. Relays WGY 4 p.m.-12 m. Sun. 4:15 p.m.-12 m.
14485 kc. YNA	11890 kc. ★	10740 kc. ★JVM	9840 kc. JYS	9518 kc. ★ VK3ME
-C. 20.71 meters MANAGUA, NICARAGUA Phones WNC daytime	-B. 25.23 meters "RADIO COLONIAL" PARIS, FRANCE 11:50 a.m.-6 p.m. 3-4 a.m.	-B.C. 27.93 meters NAZAKI, JAPAN Daily 12 m.-1 a.m., Tues. and Fri. 2-3 p.m., Mon. and Thur. 4-5 p.m.	-X. 30.49 meters KEMIKAWA-CHO, CHIBA- KEN, JAPAN Irregular, 4-7 a.m.	-B. 31.54 meters AMALGAMATED WIRELESS, LTD., G. P. O. Box 1272L, MELBOURNE, AUSTRALIA Wed. to Sat. 5:00-7:00 a.m.
14470 kc. WMF	11870 kc. ★W8XK	10675 kc. WNB	9800 kc. LSE	9510 kc. ★ GSB
-C. 20.73 meters LAWRENCEVILLE, N. J. Phones England morning and afternoon	-B. 25.26 meters WESTINGHOUSE ELECTRIC & MFG. CO., PITTSBURGH, PA. 5-9 p.m. Fri. till 12 m. Relays KDKA	-C. 28.1 meters LAWRENCEVILLE, N. J. Calls Bermuda, daytime	-C. 30.61 meters MONTE GRANDE, ARGENTINA Tests irregularly	-B. 31.55 meters DAVENTRY, B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 10:30 a.m.-12 n. 12:15-4, 4:15-5:45 p.m.
14440 kc. GBW	11860 kc. GSE	10670 kc. ★CEC	9790 kc. GCW	9501 kc. ★ PRF5
-C. 20.78 meters RUGBY, ENGLAND Calls U.S.A., afternoon	-B. 25.29 meters DAVENTRY, B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND	-C. 28.12 meters SANTIAGO, CHILE Broadcasts Thurs., Sun. 6:30-9 p.m.	-C. 30.64 meters RUGBY, ENGLAND Calls N.Y.C., evening	-B. 31.58 meters RIO DE JANEIRO, BRAZIL Irregularly 4:45-5:45 p.m.
13990 kc. GBA	11830 kc. W2XE	10660 kc. JVN	9760 kc. VLJ-VLZ2	9428 kc. ★ COCH
-C. 21.44 meters RUGBY, ENGLAND Calls Buenos Aires, late afternoon	-B. 25.36 meters ATLANTIC BROADCASTING CORP., 485 MADISON AVE., N. Y. C. Relays WABC 6-8 p.m.	-C. 28.14 meters NAZAKI, JAPAN Phones Europe 3-8 a.m.	-C. 30.74 meters AMALGAMATED WIRELESS OF AUSTRALIA SYDNEY, AUSTRALIA Phones Java and N. Zealand early a.m.	-B. 31.6 meters 2 B ST., VEDADO, HAVANA, CUBA 10 a.m.-12 n., 4-6:30, 8-10 p.m. also 11 a.m.-12 N. Thurs.
13635 kc. SPW	11810 kc. ★2RO	10550 kc. WOK	9750 kc. WOF	9415 kc. ★ PLV
-B. 22 meters WARSAW, POLAND Sundays 11:30 a.m.-12:30 p.m.	-B. 25.4 meters E.I.A.R. Via Montello 5 ROME, ITALY 8:15-9 a.m.-9:15-10:15 a.m., 12 n.-1 p.m.	-C. 28.44 meters LAWRENCEVILLE, N. J. Phones Arge., Peru, nights	-C. 30.77 meters LAWRENCEVILLE, N. J. Phones England, evening	-C. 31.67 meters BANDOENG, JAVA Phones Holland around 9:45 a.m. Broadcasts Tues. and Thurs., Sat. at 10:30 a.m.
13610 kc. JYK	11800 kc. CO9WR	10520 kc. VLK	9710 kc. GCA	9330 kc. CJA2
-C. 22.04 meters KEMIKAWA-CHO, CHIBA- KEN, JAPAN Phones California 1111 11 p. m.	-B. 25.42 meters P. O. Box 85 SANCTI SPIRITUS, CUBA Testing in early evening and 9 a.m.-12 n.	-C. 28.51 meters SYDNEY, AUSTRALIA Calls Rugby, early a.m.	-C. 30.89 meters RUGBY, ENGLAND Calls Arge. & Brazil, evenings	-C. 31.65 meters DRUMMONDVILLE, CANADA Phones England irregularly
13585 kc. GBB	11790 kc. W1XAL	10430 kc. YBG	9635 kc. ★2RO	9280 kc. GCB
-C. 22.08 meters RUGBY, ENGLAND Calls Egypt & Canada, afternoons	-B. 25.45 meters BOSTON, MASS. Sun. 5-7 p.m.	-C. 28.76 meters MEDAN, SUMATRA 5:30-6:30 a.m., 7:30-8:30 p.m.	-B. 31.13 meters E.I.A.R., ROME, ITALY M. W. F. 7:45-9 p.m. Daily 2:30-5 p.m.	-C. 32.33 meters RUGBY, ENGLAND Calls Can. & Egypt, evenings
13415 kc. GCJ	11770 kc. DJD	10420 kc. XGW	9625 kc. ★ CT1AA	9170 kc. WNA
-C. 22.36 meters RUGBY, ENGLAND Calls Japan & China early morning	-B. 25.49 meters BROADCASTING HOUSE, BERLIN, GERMANY 12-4:30 p.m.	-C. 28.79 meters SHANGHAI, CHINA Calls Manila and England, 6-9 a.m. and California late evening	-B. 31.17 meters LISBON, PORTUGAL Tues., Thurs., Sat. 4:30-7 p.m.	-C. 32.72 meters LAWRENCEVILLE, N. J. Phones England, evening
13390 kc. WMA	11750 kc. ★GSD	10410 kc. PDK	9600 kc. XEFT	9125 kc. HAT4
-C. 22.40 meters LAWRENCEVILLE, N. J. Phones England morning and afternoon	-B. 25.53 meters DAVENTRY, B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 3:30-5:30 a.m., 9 a.m.-12n; 12:15-4 p.m.	-C. 28.80 meters BOLINAS, CALIF. Tests evenings	-B. 31.25 meters AVE. INDEPENDENCIA, 28, VERA CRUZ, MEXICO Daily 11 a.m.-4 p.m., 7:30 p.m.- 12 m., Sat. 11 a.m.-4 p.m., 6:30 p.m.-12 m., Sun. 11 a.m.- 4 p.m., 9 p.m.-12 m. Relays XEFT.	-B. 32.88 meters "RADIODABOR," GYALI-UT, 22 BUDAPEST, HUNGARY Sunday 6-7 p.m.
13345 kc. YVC	11730 kc. PH1	10350 kc. LSX	9595 kc. ★ HBL	9060 kc. TFK
-C. 22.48 meters MARACAY, VENEZUELA Calls Hialeah daytime	-B. 25.57 meters HUIZEN, HOLLAND Daily exc. Tues. and Wed. 8:30- 10:30 a.m., Sun. 8:30-11:30 a.m.	-C. 28.98 meters MONTE GRANDE, ARGENTINA Tests irregularly 8 p.m.-12 mid- night.	-B. 31.27 meters LEAGUE OF NATIONS GENEVA, SWITZERLAND Saturdays 5:30-6:15 p. m. Mon. at 1:45 a.m.	-B. 33.11 meters REYKJAVIK, ICELAND Phones London afternoons. Broadcasts irregularly.
13075 kc. VPD	11720 kc. ★CJRX	10330 kc. ★ORK	9590 kc. ★ VK2ME	9020 kc. GCS
-X. 22.94 meters SUVA, FIJI ISLANDS Daily exc. Sun. 12:30-1:30 a.m.	-B. 25.6 meters WINNIPEG, CANADA Daily, 9 p. m.-12 m.	-B.C. 29.04 meters RUYSSELEDE, BELGIUM Broadcasts 2:30-4 p.m.	-B. 31.28 meters AMALGAMATED WIRELESS, LTD., 47 YORK ST. SYDNEY, AUSTRALIA Sun. 1-3, 5-11 a.m.	-C. 33.26 meters RUGBY, ENGLAND Calls N.Y.C., evenings
12840 kc. WOO	11715 kc.	10300 kc. LSL2	9590 kc. HP5J	
-C. 23.36 meters OCEAN GATE, N. J. Calls ships	-B. 25.61 meters "RADIO COLONIAL" PARIS, FRANCE 7-10:10 p.m. 11 p.m.-1 a.m.	-C. 29.13 meters HURLINGHAM, ARGENTINA Calls Europe, evenings	-B. 31.28 meters APARTADO 867 PANAMA CITY, PANAMA 11:45 a.m.-1 p.m., 7:30-10 p.m.	
12825 kc. CNR		10290 kc. DIQ	9590 kc. W3XAU	
-B. C. 23.39 meters DIRECTOR GENERAL Telegraph and Telephone Stations, Rabat, Morocco Broadcasts, Sunday, 7:30-9 a.m.		-X. 29.16 meters KONIGSWUSTERHAUSEN, GERMANY Broadcasts irregularly	-B. 31.28 meters NEWTOWN SQUARE, PA. Relays WCAU 12 N-7:50 p.m.	
12800 kc. IAC				
-C. 23.45 meters PISTA, ITALY Calls Italian ships, mornings				
12780 kc. GBC				
-C. 23.47 meters RUGBY, ENGLAND Calls ships				

(All Schedules Eastern Standard Time)

9010 kc. KEJ	7281 kc. HJ1ABD	6520 kc. YV6RV	6130 kc. HJ1ABE	6070 kc. HJ4ABC
-C- 33.3 meters BOLINAS, CAL. Relays NBC & CBS Programs in evening irregularly	-B- 41.04 meters CARTAGENA, COLO. Irregularly, evenings	-B- 46.01 meters VALENCIA, VENEZUELA 12 n.-I p.m.-6-10 p.m.	-B- 48.92 meters CARTAGENA, COL. P. O. Box 31	-B- 49.42 meters PERIERA, COL. 9:30-11:30 a.m.-7-8 or 9 p.m.
8795 kc. HKV	7100 kc. HKE	6500 kc. HJ5ABD	6130 kc. ZGE	6070 kc. VE9CS
-B- 34.09 meters BOGOTA, COLOMBIA Irregular: 6:30 p.m.-12 m.	-B- 42.25 meters Tues. and Sat. 8-9 p.m.; Mon. & Thurs. 6:30-7 p.m.	-B- 45.15 meters MANIZALES, COL. 12-1:30 p.m., 7-10 p.m.	-B- 48.92 meters KUALA LUMPUR, FED. MALAY STATES Sun., Tue. and Fri. 6:40-8:40 a.m.	-B- 49.42 meters VANCOUVER, B.C., CANADA Sun. 1:45-9 p.m.; 10:30 p.m. 1 a.m.; Tues. 6-7:30 p.m. 11:30 p.m.; Wed. 6-7:30 a.m.; Daily 6-7:30 p.m.
8775 kc. PNI	7080 kc. VP3MR	6482 kc. H14D	6130 kc. XEFT	6065 kc. HJ4ABL
-C- 34.19 meters MAKASSER, CELEBES, N.I. Phones Java around 4 a.m. M.	-B- 42.68 meters GEORGETOWN, BRIT. GUI- ANA, S.A. Sun. 7:45-10:15 a.m. Mon. 3:45-4:45; 6:45-7:45 p.m. Wed. 6:45-7:45 p.m. Thur. 5-6:45 p.m. Sat. 6:45-7:45 p.m.	-B- 46.28 meters SANTO DOMINGO, DOMINI- CAN REPUBLIC Except Sun. 11:55 a.m.-1:40 p.m.; 4:40-7:40 p.m.	-B- 49.02 meters ATLANTIC BROADCASTING CORP. 485 MADISON AVE., N.Y.C. Relays WABC, 8-11 p.m.	-B- 49.46 meters MANIZALES, COL. Daily 11 a.m.-12 m., 5:30-7:30 p.m.; Sat. 10:30-11:30 p.m.
8760 kc. GCQ	7030 kc. HRP1	6450 kc. HJ4ABJ	6120 kc. W2XE	6060 kc. OXY
-C- 34.25 meters RUGBY, ENGLAND Calls S. Africa, afternoon	-B- 42.67 meters SAN PEDRO SULA, HONDURAS Reported on this and other waves irregularly in evening	-B- 46.51 meters "LA VOZ de CAMBEPE," IBAQUE, COLOMBIA 6-9 p.m.	-B- 49.02 meters VERA CRUZ, MEX. II a.m.-4 p.m.; 7:30 p.m.-12 m. Sat. also 6:30-7:30 p.m. Sun. II a.m.-4 p.m.; 9 p.m.-12 m. Relays XETF	-B- 49.50 meters SKAMLEBOAEK, DENMARK 1-6:30 p.m.; also II a.m.-12 n. Sunday
8750 kc. ZEK	7000 kc. HJ1ABK	6447 kc. HJ1ABB	6110 kc. GSL	6060 kc. W8XAL
-B- 34.29 meters HONGKONG, CHINA Relays ZBW Daily 11:30 p.m.-15 a.m. Mon. and Thurs. 3-7 a.m. Tues., Wed., Fri. 6-10 a.m. Sat. 6-11 a.m.	-B- 42 meters CALLE, BOLIVIA, PROGRESO-IGUALAD BARRANQUILLA, COLOMBIA Testing in evening	-B- 46.53 meters BARRANQUILLA, COL., S.A. P. O. BOX 715 II:30 a.m.-1 p.m.; 5-10 p.m.	-B- 49.10 meters DAVENTRY, B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 2:15-4, 10-11 p.m.	-B- 49.50 meters CROSLEY RADIO CORP. CINCINNATI, OHIO 6:30 a.m.-8 p.m.; II 5-1 a.m. Relays WLW
8730 kc. GCI	6996 kc. PZH	6425 kc. W9XBS	6110 kc. VUC	6060 kc. W3XAU
-C- 34.36 meters RUGBY, ENGLAND Calls India, 8 a.m.	-B- 42.88 meters P. O. BOX 18, PARAMARIBO, DUTCH GUIANA Sun. 9:36-11:36 a.m. Mon. and Fri. 5:36-9:36 p.m. Tues. and Thur. 8:36-10:36 a.m. 2:36-4:36 p.m. Wed. 3:36-4:36, 5:36-9:36 p.m. Sat. 2:36-4:36 p.m.	-X- 46.7 meters DAILY NEWS BUILDING, CHICAGO, ILL. Operates irregularly in afternoon	-B- 49.10 meters CALCUTTA, INDIA Daily except Sat. 3:50 a.m., 9:30 a.m.-noon; Sat. 11:45 a.m.-3 p.m.	-B- 49.50 meters NEWTOWN SQUARE, PA. Relays WCAU, Philadelphia 8 p.m.-11 p.m.
8680 kc. GBC	6905 kc. GDS	6375 kc. YV4RC	6110 kc. HJ4ABB	6050 kc. GSA
-C- 34.58 meters RUGBY, ENGLAND Calls ships	-C- 43.45 meters RUGBY, ENGLAND Calls India, 8 a.m.	-B- 47.06 meters CARACAS, VENEZUELA 4:30-10:30 p.m.	-B- 49.14 meters MANIZALES, COL., S.A. P. O. Box 175 Mon. to Fri. 12:15-1 p.m.; Tues. & Fri. 7:30-10 p.m.; Sun. 2:30-5 p.m.	-B- 49.50 meters DAVENTRY, B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 10:45 a.m.-12 n., 4:5-4:5 p.m. 6-8 p.m.
8560 kc. WOO	6860 kc. KEL	6316 kc. HIZ	6105 kc. HJ4ABB	6045 kc. HJ3ABI
-C- 35.05 meters OCEAN GATE, N.J. Calls ships irregular	-X- 43.70 meters BOLINAS, CALIF. Tests irregularly II a.m.-12 n.; 6-9 p.m.	-B- 47.5 meters SANTO DOMINGO DOMINICAN REPUBLIC Daily except Sat. and Sun. 4:40-5:40 p.m.; Sat. 9:40- 11:40 p.m.; Sun. 11:40 p.m.- 1:40 p.m.	-B- 49.16 meters NATIONAL BROADCASTING CO. BOUND BROOK, N.J. Relays WJZ Monday, Wednesday, Saturday, 5-6 p.m.; Sun. 12 m-1 a.m.	-B- 49.63 meters BOGOTA, COLO. Irregular in evening
8380 kc. IAC	6814 kc. HIH	6230 kc. OAX4G	6100 kc. W3XAL	6042 kc. HJ1ABG
-C- 35.8 meters Pisa, Italy	-B- 44.03 meters SAN PEDRO DE MACORIS DOMINICAN REP. 12-10:1 a.m.; 7:30-9 p.m. Sun. 3-4 a.m.; 4:15-6 p.m.	-B- 48 meters Apartado 1242 LIMA, PERU Wed. 7-11:30 p.m.	-B- 49.16 meters NATIONAL BROADCASTING CO. BOUNDED BROOK, N.J. Relays WJZ Monday, Wednesday, Saturday, 5-6 p.m.; Sun. 12 m-1 a.m.	-B- 49.65 meters BARRANQUILLA, COLO. 12 n.-I p.m., 6-10 p.m. Sun. 1-6 p.m.
8220 kc. ZP10	6755 kc. WOA	6198 kc. CT1GO	6040 kc. W4XB	6040 kc. PRA8
-B- 36.4 meters ASUNCION, PARAGUAY 7-9 p.m.	-C- 44.41 meters LAWRENCEVILLE, N.J. Phones England, evening	-B- 48.4 meters Portuguese Radio Club, PAREDE, PORTUGAL Sun. 11:30 a.m.-1 p.m. Daily exc. Tues. 7:20-8:30 p.m.	-B- 49.67 meters MIAMI BEACH, FLA. Relays WIOB, 12 n.-2 p.m., 5:30 p.m.-12 m.	-B- 49.67 meters RADIO CLUB OF PERNAMBUCO, BRAZIL 1-3 p.m., 4-7:30 p.m., daily
8214 kc. HCJB	6750 kc. ★JVT	6185 kc. HI1A	6040 kc. ★W1XAL	6040 kc. YDA
-B- 36.5 meters QUITO, ECUADOR 7-11 p.m., except Monday Sun. 11 a.m.-12 n.; 4-10 p.m.	-B-C- 44.43 meters NAZAKI, JAPAN KOKUSAI-DENWA KAISHA, LTD., TOKIO Broadcasts 12 m-1 a.m. 4-8 a.m.	-B- 48.5 meters P. O. BOX 423, SANTIAGO, DOMINICAN REP. 11:40 a.m.-1:40 p.m. 7:40-9:40 p.m.	-B- 49.68 meters DOWNERS GROVE, ILL. Relays WENR, Chicago	-B- 49.67 meters BOSTON, MASS. Tues., Thurs. 7:15-9:5 p.m.
8185 kc. PSK	6710 kc. ★TIEP	6175 kc. HJ2ABA	6040 kc. ★CRCX	6040 kc. ★W1XAL
-C- 36.65 meters RIO DE JANEIRO, BRAZIL Irregularly	-B- 44.71 meters LA-VOZ DEL TROPICO SAN JOSE, COSTA RICA APARTADO 257, Daily 7-10 p.m.	-B- 48.58 meters TUNJA, COLOMBIA 1-2; 7:30-9:30 p.m.	-B- 49.26 meters TORONTO, CANADA Daily 6 p.m.-12 m., Sun. 12 n.-12 m.	-B- 49.67 meters N.I.R.O.M. TANDJONGPRIOK, JAVA Testing 5:30-11 a.m.
8170 kc. CO9JQ	6672 kc. YVQ	6170 kc. HJ3ABF	6090 kc. ★CRCX	6030 kc. ★HP5B
-X- 36.72 meters CAMAGUEY, CUBA Broadcast 8-9 p.m., daily except Sat. and Sun.	-C- 44.81 meters MARACAY, VENEZUELA Broadcasts Sat. 8-9 p.m.	-B- 48.62 meters BOGOTA, COLOMBIA 6-11 p.m.	-B- 49.26 meters SAINT JOHN, N.B., CAN. 7-8:30 p.m.	-B- 49.75 meters P. O. BOX 910 PANAMA CITY, PAN. 12 N.-I p.m., 8-10:30 p.m.
8036 kc. CNR	6660 kc. ★HC2RL	6160 kc. ★YV3RC	6090 kc. VE9BJ	6030 kc. VE9CA
-B- 37.33 meters RABAT, MOROCCO Sunday, 2:30-5 p.m.	-B- 45.05 meters P. O. BOX 509, GUAYAQUIL, ECUADOR, S.A. Sunday, 5:45-7:45 p.m. Tues., 9:15-11:15 p.m.	-B- 48.7 meters CARACAS, VENEZUELA 11 a.m.-2 p.m., 4-10:30 p.m.	-B- 49.28 meters SAINT JOHN, N.B., CAN. 7-8:30 p.m.	-B- 49.75 meters CALGARY, ALBERTA, CAN. Thurs. 9 a.m.-2 a.m. (Fri.); Sun. 12 n.-12 m. Irregular on other days from 9 a.m.-12 m.
7901 kc. LSL	6650 kc. IAC	6155 kc. CO9GC	6085 kc. 2RO	6020 kc. CQN
-C- 37.97 meters HURLINGHAM, ARGENTINA Calls Brazil, night	-C- 45.11 meters PIASA, ITALY Calls ships, evenings	-B- 48.74 meters GRAU & CAMENEROS LABS., BOX 137, SANTIAGO, CUBA 9-10 a.m., 11:30 a.m.-1:30 p.m., 3-4:30 p.m., 10-11 p.m., 12 m.- 2 a.m.	-B- 49.3 meters E.I.A.R. ROME, ITALY Mon., Wed., Fri. 6:15-7:30 p.m. Daily 6-6:15 p.m.	-B- 49.83 meters MACAO, CHINA Mon. and Fri. 3-5 a.m.
7880 kc. JYR	6620 kc. ★PRADO	6150 kc. CSL	6083 kc. VQ7LO	6020 kc. ★DJC
-B- 38.07 meters KEMIKAWA-CHO, CHIBA- KEN, JAPAN 4-7:40 a.m.	-B- 45.30 meters RIOABAMBA, ECUADOR Thurs. 9:11-11:45 p.m.	-B- 48.78 meters LISBON, PORTUGAL 7-8:30 a.m.-2.7 p.m.	-B- 49.31 meters NAIROBI, KENYA, AFRICA Mon.-Fri. 5:45-6:15 a.m., 11:30 a.m.-2:30 p.m., Also 8:30-9:30 a.m. on Tues. and Thurs., Sat. 11:30 a.m.-3:30 p.m., Sun. 11 a.m.-2 p.m.	-B- 49.83 meters BROADCASTING HOUSE, BERLIN 12 n.-4:30 p.m., 5:05-10:45 p.m.
7860 kc. HC2JSB	6611 kc. RV72	6150 kc. ★CJRO	6080 kc. CP5	6020 kc. HJ3ABH
-B- 38.17 meters GUAYAQUIL, ECUADOR 8:15-11:15 p.m.	-B- 45.38 meters MOSCOW, U.S.S.R. 1-6 p.m.	-B- 48.78 meters WINNIPEG, MAN., CANADA 6 p.m.-12 m. Sun. 3-10:30 p.m.	-B- 49.34 meters LAPAZ, BOLIVIA 7-10:30 p.m.	-B- 49.83 meters BOGOTA, COLO. APARTADO 565 7-11 p.m.
7799 kc. ★HBP	6600 kc. YV5AM	6150 kc. HJ5ABC	6080 kc. W9XAA	6018 kc. ZHI
-B- 38.47 meters LEAGUE OF NATIONS, GENEVA, SWITZERLAND 5:30-6:15 p.m., Saturday	-B- 45.45 meters "ECOS DE LLANO" SAN JUAN DE LOS MORROS, VENEZUELA Testing in evening	-B- 48.78 meters CALI, COLOMBIA M.W., F., 7-8 p.m.	-B- 49.34 meters CHICAGO FEDERATION OF LABOR CHICAGO, ILL. Relays WCFL Sunday 11:30 a.m.-9 p.m. and Tues., Thurs., Sat. 4 p.m.-12 m.	-B- 49.8 meters RADIO SERVICE CO., 20 ORCHARD RD., SINGAPORE, MALAYA Mon., Wed., and Thurs. 5:40-8:10 a.m., Sat. 10:40 p.m.-1:10 a.m. (Sun.) Every other Sunday 5:10- 6:40 a.m.
7715 kc. KEE	6600 kc. ★TIRCC	6140 kc. ★W8XK	6072 kc. OER2	6010 kc. ★COCO
-C- 38.89 meters BOLINAS, CAL. Relays NBC & CBS Programs in evening irregularly	-B- 45.77 meters RADIOEMISORA CATOLICA COSTARRICENSE SAN JOSE, COSTA RICA Sun. 12:45-2:30, 6-7, 8-9 p.m.	-B- 48.86 meters WESTINGHOUSE ELECTRIC & MFG. CO. PITTSBURGH, PA. Relays KDKA 9 p.m.-1 a.m.	-B- 49.41 meters VIENNA, AUSTRIA 9 a.m.-5 p.m.	-B- 49.82 meters P.O. BDX 98 HAVANA, CUBA Daily 9:30-11 a.m., 4-7 p.m. and 8-10 p.m. Sat. also 11:30 p.m.-1:30 a.m.
7630 kc. ZHJ	6528 kc. HIL	6130 kc. COCD	6070 kc. HP5H	
-B- 39.32 meters PENANG, MALAYA Daily 7-9 a.m. also Sat. 11 p.m.-1 A.M. (Sun.)	-B- 45.95 meters SANTO DOMINGO, D.R. Sat., 8-10 p.m.	-B- 48.92 meters "La Voz del Aire" CALLE G y 25, VEDADO, HAVANA, CUBA Relays CMCD 8 p.m.-12 m.	-B- 49.42 meters COLON, PANAMA Testing in evening.	
7510 kc. JVP				
-C- 39.95 meters NAZAKI, JAPAN Heard irregularly				
7400 kc. HJ3ABD				
-B- 40.54 meters P. O. Box 509 BOGOTA, COLOMBIA Daily 12-2 p.m.; 7-11 p.m. Sunday, 5-9 p.m.				
7380 kc. XECR				
-B- 40.65 meters FOREIGN OFFICE, MEXICO CITY, MEX. Sun. 6-7 p.m.				

6000 kc. TGWA	5950 kc. HJ1ABJ	5800 kc. ★YV2RC	5077 kc. WCN	4320 kc. GDB
-B- 50 meters GUATEMALA CITY, GUAT. 12 a.m.-1 p.m. 6:30-7:30 p.m. 10-11 p.m. Sat. also from 12 m. 6 a.m. (Sun.)	-B- 50.42 meters SANTA MARTA, COLO. 11 a.m.-1 p.m. 7-9 p.m.	-B- 51.72 meters BROADCASTING CARACAS CARACAS, VENEZUELA Sun. 8:30 a.m.-10:30 p.m. Daily 11 a.m.-1:30 p.m., 9:30 p.m.	-C- 59.08 meters LAWRENCEVILLE, N. J. Phones England irregularly	-C- 69.44 meters RUGBY, ENGLAND Tests, 8-11 p.m.
6000 kc. RV59	5950 kc. HJ4ABE	5790 kc. JVU	5025 kc. ZFA	4273 kc. RV15
-B- 50 meters MOSCOW, U. S. S. R. Daily 3-6 p.m.	-B- 50.42 meters MEDELLIN, COLO. Daily 11 a.m.-12 p.m., 6-10:30 p.m.	-C- 51.81 meters NAZAKI, JAPAN Broadcasts 2-7:45 a.m.	-C- 59.7 meters HAMILTON, BERMUDA Calls U.S.A., nights	-B- 70.20 meters KHABAROVSK, SIBERIA, U. S. S. R. Daily, 3-9 a.m.
5990 kc. ★XEBT	5940 kc. TG2X	5780 kc. HI1J	5000 kc. TFL	4272 kc. WOO
-B- 50.08 meters MEXICO CITY, MEX. P. O. Box 79-44 8 a.m.-1 a.m.	-B- 50.5 meters GUATEMALA CITY, GUAT. 4-6, 9-11 p.m.	-B- 51.9 meters SAN PEDRO de MACORIS, DOM. REP. 7-8:30 p.m.	-C- 60 meters REYKJAVIK, ICELAND Calls London at night. Also broadcasts irregularly	-C- 70.22 meters OCEAN GATE, N. J. Calls ships irregularly
5985 kc. HJ2ABC	5880 kc. YV8RB	5780 kc. OAX4D	4975 kc. GBC	4098 kc. WND
-B- 50.13 meters CUCUTA, COLOMBIA Irreg. in evening	-B- 51.02 meters "LA VOZ de LARA" BARQUISIMETO, COLOMBIA 6-10 p.m.	-B- 51.9 meters P.O. Box 853 LIMA, PERU Mon., Wed. & Sat. 9-11:30 p.m.	-C- 60.30 meters RUGBY, ENGLAND Calls Ships, late at night	-C- 73.21 meters HIALEAH, FLORIDA Calls Bahama Isles
5980 kc. XECW	5875 kc. HRN	5720 kc. YV10RSC	4820 kc. GDW	4002 kc. CT2AJ
-B- 50.17 meters CALLE del BAJIO 120 MEXICO CITY, MEX. 4-4:30 p.m., 10:30 p.m., 12 m.	-B- 51.06 meters TEGUCIGALPA, HONDURAS 7-9 p.m.	-B- 52.45 meters "LA VOZ de TACHIRA," SAN CRISTOBAL, COLOMBIA Testing near 12 m.	-C- 62.24 meters RUGBY, ENGLAND Calls N.Y.C., late at night	-B- 74.95 meters PONTA DELGADA, SAO MIGUEL, AZORES Wed. and Sat. 5-7 p.m.
5980 kc. HIX	5853 kc. WOB	5714 kc. HCK	4752 kc. WOO	3543 kc. CR7AA
-B- 50.17 meters SANTO DOMINGO, DOMINI- CAN REP. Sun. 7:10 a.m.; Tues. and Fri. 11:10 a.m., 4:40 and 8:10 p.m.; Mon., Wed., Thurs. and Sat. 11:10 a.m. and 4:40 p.m.	-C- 51.26 meters LAWRENCEVILLE, N. J. Calls Bermuda, nights	-B- 52.5 meters QUITO, ECUADOR, S. A.	-C- 63.1 meters OCEAN GATE, N. J. Calls ships irregularly	-B- 84.67 meters P. O. BOX 594 LOURENCO MARQUES, MO- ZAMBIQUE, E. AFRICA 1:30-3:30 p.m., Mon., Thurs., and Sat.
5968 kc. HVJ	5850 kc. ★YV5RMO	5713 kc. TGS	4600 kc. HC2ET	3490 kc. YDH3
-B- 50.27 meters VATICAN CITY (ROME) 2-2:15 p.m., daily, Sun. 5-5:30 a.m.	CALLE REGISTROS LAS DE- LICIAS APARTADO de COR- RES 214 MARACAIBO, VENEZUELA 11 a.m.-1 p.m., 5:30-10 p.m.	-B- 52.51 meters GAUTEMALA CITY, GUAT. Tues., Thurs., and Sun. 6-8 p.m.	-B- 65.22 meters Apartado 249 GUAYAQUIL, ECUADOR Wed., Sat. 9-11:30 p.m.	-B- 85.96 meters BANDOENG, JAVA Daily except Fri., 4:30-5:30 a.m.
5825 kc. TIGPH	5500 kc. T15HH	4470 kc. YDB	3040 kc. YDA	
-B- 51.5 meters SAN JOSE, COSTA RICA 6:15-11 p.m.	-B- 54.55 meters SAN RAMON, COSTA RICA Irregularly around 9:45 p.m.	-B- 67.11 meters N.I.R.O.M. SOERABAIA, JAVA 10:30 p.m.-1:30 a.m., 5:30- 11 a.m., 3:45-6:45 p.m.	-B- 98.68 meters N.I.R.O.M. TANDJONGPRIOK, JAVA 10:30 p.m.-1:30 a.m., 5:30-11 a.m.	

(All Schedules Eastern Standard Time)

Police Radio Alarm Stations

CGZ	Vancouver, B.C.	KGZT	Santa Cruz, Cal.	KSW	Berkeley, Cal.
CJW	St. John's, N.B.	KGZU	Lincoln, Neb.	KVP	Dallas, Tex.
CJZ	Verdeen, Que.	KGZV	Aberdeen, Wash.	VDM	Halifax, N.S.
KGHA	Portable-Mobile	KGZW	Lubbock, Tex.	YVR	Montreal, Can.
KGBH	In State of Wash.	KGZX	Albuquerque, N.Mex.	VYV	Winnipeg, Man.
KGHG	Las Vegas, Nev.	KIUK	San Bernardino, Cal.	WCK	Belle Island, Mich.
KGHK	Palo Alto, Cal.	KNFA	Jefferson City, Mo.	WEY	Boston, Mass.
KGHM	Reno, Nev.	KNFB	Clovis, N.Mex.	WKDT	Detroit, Mich.
KGHN	Hutchinson, Kans.	KNFC	Idaho Falls, Idaho	WKDU	Cincinnati, Ohio.
KGHO	Iowa Moines, Iowa	KNFD	SS Gov. Stevens, (Wash.)	WMDZ	Indianapolis, Ind.
KGHP	Lawton, Okla.	KNFE	SS Gov. J. Rogers, (Wash.)	WMJ	Buffalo, N.Y.
KGHQ	Chinook Pass, W.	KNFF	Duluth, Minn.	WMO	Highland Park, Mich.
KGHR	(Mobile) in Wash.	KNFG	Leavenworth, Kans.	WMP	Framingham, Mass.
KGHS	Spokane, Wash.	KNFH	Olympia, Wash.	WNFP	Niagara Falls, N.Y.
KGHT	Brownsville, Tex.	KNFI	Garden City, Kans.	WPDA	Tulare, Cal.
KGHU	Austin, Tex.	KNFJ	Mt. Vernon, Wash.	WPDB	Chicago, Ill.
KGHV	Corpus Christi, Tex.	KNFK	Pomona, Cal.	WPDC	Chicago, Ill.
KGHW	Centralia, Wash.	KNFL	Bellingham, Wash.	WPDD	Chicago, Ill.
KGHX	Santa Ana, Cal.	KNFM	Shuksan, Wash.	WPDE	Louisville, Ky.
KGHY	Whittier, Cal.	KNFN	Compton, Cal.	WPDF	Flint, Mich.
KGHZ	Little Rock, Ark.	KNFO	Waterloo, Iowa	WPDG	Youngstown, Ohio.
KGJX	Pasadena, Cal.	KNFP	Storm Lake, Iowa	WPDH	Richmond, Ind.
KGLX	Albuquerque, N.M.	KNFQ	Everett, Wash.	WPDI	Columbus, Ohio.
KGOZ	Cedar Rapids, Iowa	KNFR	Skykomish, Wash.	WPDK	Milwaukee, Wis.
KGPA	Seattle, Wash.	KNFS	Mobile in State of Wash.	WPDL	Lansing, Mich.
KGPB	Minneapolis, Minn.	KNFT	Alpowa Camp, Wash.	WPDM	Dayton, Ohio.
KGPC	St. Louis, Mo.	KNFU	Hells Crossing Camp, Wash.	WPDN	Auburn, N.Y.
KGPD	San Francisco, Cal.	KNFV	Satus Pass Camp, Wash.	WPDO	Akron, Ohio.
KGPE	Kansas City, Mo.	KNFW	Yakima, Wash.	WPDP	Philadelphia, Pa.
KGPF	Santa Fe, N.Mex.	KNFX	Vancouver, Wash.	WPDR	Rochester, N.Y.
KGPG	Vallejo, Cal.	KNFY	Walla Walla, Wash.	WPDS	St. Paul, Minn.
KGPH	Oklahoma City, Okla.	KNFZ	Cleburne, Tex.	WPDT	Kokomo, Ind.
KGPI	Omaha, Neb.	KNGA	Sacramento, Cal.	WPDU	Pittsburgh, Pa.
KGPJ	Beaumont, Tex.	KNGB	Dodge City, Kans.	WPDV	Charlotte, N.C.
KGPK	Sioux City, Iowa	KNGM	El Centro, Cal.	WPDW	Washington, D.C.
KGPL	Los Angeles, Cal.	KNGN	Duncan, Okla.	WPDX	Detroit, Mich.
KGPM	San Jose, Cal.	KNGO	Rapid City, S. Dak.	WPDY	Atlanta, Ga.
KGPN	Davenport, Iowa	KNGP	Norfolk, Nebr.	WPDZ	Fort Wayne, Ind.
KGPO	Tulsa, Okla.	KNHQ	Portable, Okla.	WPEA	Syracuse, N.Y.
KGPP	Portland, Ore.	KNJR	Shreveport, Pa.	WPEB	Grand Rapids, Mich.
KGPQ	Honolulu, T.H.	KNJK	Wenatchee, Wash.	WPEC	Memphis, Tenn.
KGPR	Minneapolis, Minn.	KNKL	Spokane, Wash.	WPED	Arlington, Mass.
KGPS	Bakersfield, Cal.	KNKM	Muskogee, Okla.	WPEE	New York, N.Y.
KGPW	Salt Lake City, Utah	KNKN	Yakima, Wash.	WPEF	New York, N.Y.
KGPX	Denver, Colo.	KNKO	Salina, Kans.	WPEG	New York, N.Y.
KGPZ	Wichita, Kans.	KNKP	Portable, Los Angeles	WPEH	Somerville, Mass.
KGZA	Fresno, Cal.	KNKQ	Lodi, Calif.	WPEI	E. Providence, R.I.
KGZB	Houston, Tex.	KNKR	Ephrata, Wash.	WPEK	New Orleans, La.
KGZC	Topeka, Kans.	KNKT	Mobile, Wash.	WPEL	W. Bridgewater, Mass.
KGZD	San Diego, Cal.	KNKU	El Paso, Tex.	WPEM	Newton, Mass.
KGZE	San Antonio, Tex.	KNKV	Green Bay, Wis.	WPEP	Kenosha, Wis.
KGZF	Chanute, Kans.	KNKW	Ada, Okla.	WPES	Saginaw, Mich.
KGZG	Des Moines, Iowa	KNKX	Redwood Falls, Minn.	WPET	Lexington, Ky.
KGZH	Klamath Falls, Ore.	KNKY	Port Smith, Ark.	WPEW	Portable (in Mass.)
KGZI	Wichita Falls, Tex.	KNKZ	Denton, Tex.	WPFA	Northampton, Mass.
KGZJ	Phoenix, Ariz.	KNHA	Prescott, Ark.	WPFC	Newton, Mass.
KGZM	El Paso, Tex.	KNHB	Fargo, N. Dak.	WPFE	Muskegon, Mich.
KGZN	Tacoma, Wash.	KNHC		WPFG	Reading, Pa.
KGZO	Santa Barbara, Cal.	KNHD		WPFI	Jacksonville, Fla.
KGZP	Coffeyville, Kans.	KNHE		WPFJ	Baltimore, Md.
KGZQ	Waco, Tex.	KNHF		WPFK	Columbus, Ga.
KGZR	Salem, Ore.	KNHG			Hammond, Ind.
		KNHM			Hackensack, N.J.

"WHEN TO LISTEN IN"
Appears on page 575

For Television Stations see Page 570

SHORT WAVE LEAGUE



HONORARY MEMBERS

Dr. Lee de Forest
John L. Reinartz
D. E. Replogle
Hollis Baird
E. T. Somerset
Baron Manfred von Ardenne
Hugo Gernsback

Executive Secretary

Keeping the Short Wave Club "Alive"

● IN the last two articles, we have discussed the essential details which those about to start a club will find valuable, while the second article in the December issue covered the teaching of code to club members, lectures, the club transmitting and receiving station, etc.

In the present discussion, we will confine our thoughts to such important factors as keeping the club *alive*, and what the club's officers can do to promote this spirit.

The old saying, "All work and no play makes Jack a dull boy," is quite applicable to short-wave clubs—and if you are really interested in having a good, wide-awake club, you will have to add a dash of pleasure to the club's activities now and then.

The club may be so fortunate as to

have a dramatic coach among its members, and not only a lot of fun, but also financial aid for the club can be obtained by staging a play occasionally. In some cases, the manager of the local movie theater will be glad to cooperate with the club and arrange matters so that the club members can sell specially printed tickets for the performance on a certain night. The percentage of profits and other details will have to be worked out in each case with the local theater manager.

In some cases, dramatic organizations in adjacent towns have staged a particularly successful play, and you can arrange with them to produce the play in your town. The club can share in the profits in return for their work in publicizing the show, and other assistance which they may render, such as transporting the scenery and costumes, etc.

Several times during the year, arrangements can be made to transport the club's members by bus or otherwise, to visit some commercial radio station, particularly a short-wave station. In other cases, a prominent Ham may have a particularly fine station in operation, and by pre-arrangement with the owner, he will invariably be very glad to receive a visit from the club's members.

As mentioned in the previous articles, do not forget the club's members like to hear an out-of-town speaker once in a while, and an effort should be made by the officers of the club to contact an expert on short waves to give a talk before the club. Sometimes you may have to send a car for the speaker, even a distance of fifteen miles or so, but it will repay you handsomely in renewed spirit among the club members, as experience has richly proved.

A novelty feature, which has apparently received much more recognition in

Here's Your Button

The illustration here-with shows the beautiful design of the "Official" Short Wave League button, which is available to everyone who becomes a member of the Short Wave League.

The requirements for joining the League are explained in a booklet, copies of which will be mailed upon request. The button measures $\frac{3}{4}$ inch in diameter and is inlaid in enamel—3 colors—red, white, and blue.

Please note that you can order your button AT ONCE—SHORT WAVE LEAGUE supplies it at cost, the price, including the mailing, being 35 cents. A solid gold button is furnished for \$2.00 prepaid. Address all communications to SHORT WAVE LEAGUE, 99-101 Hudson St., New York.



Europe than it has in America, is the "hidden" transmitter hunt. For this stunt, a certain short-wave transmitter is put into operation at a given time, and those participating in the "hunt," use special sets fitted with loop or other directive aerials, and eventually, of course, they succeed in locating the transmitter. There are many other variations of this interesting short-wave "stunt," which live club directors will be able to develop themselves. For instance, in addition to the "hidden" transmitter hunt, other complications may be added, such as trick code combinations, rapid changes in wavelength, and other wrinkles which will help to arouse and sustain the interest of the short-wave "hunters."

Experience with clubs in general has shown that advantage should be taken of all of the important holidays, when theater parties (and dances) held in the club's quarters can be arranged, and do not forget to notify the Y.L.'s (young lady operator) as well as potential Y.L.'s—and that field, of course, is as broad as a house, and includes all the "eligible" young ladies in town—or as many as the club can provide cake and coffee for.

One thing that the writer has noted about short-wave clubs in general is that the organizations tend to be too clannish at times—not intentionally, of course. In other words, if the club

(Continued on page 562)



At a Directors Meeting held in New York City, New York, in the United States of America, the Short Wave League has elected

John F. Müller

a member of this League.


In witness whereof, this certificate has been officially signed and presented to the above.

H. Winfield Sear
Cert. Secretary

This is the handsome certificate that is presented FREE to all members of the SHORT WAVE LEAGUE. The full size is $7\frac{1}{4}'' \times 9\frac{1}{2}''$.

See page 576 how to obtain certificate.

Short Wave

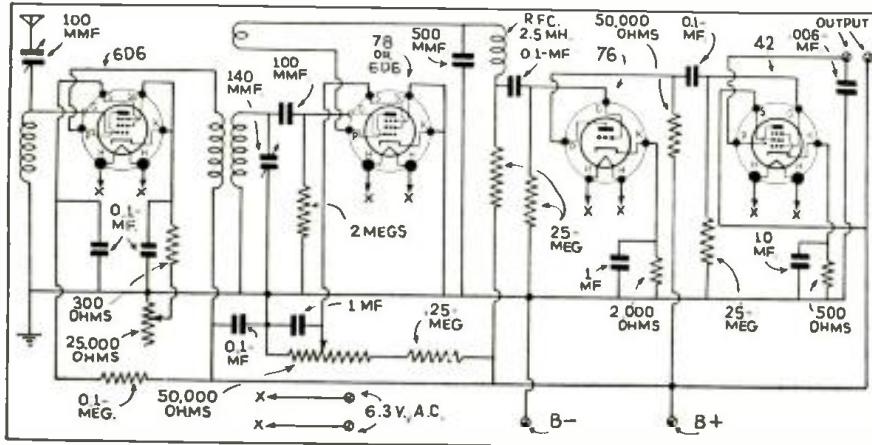


4-tube 6.3 volt receiver.

4-TUBE T.R.F. RECEIVER

James Kiggin, Lynchburg, Va.

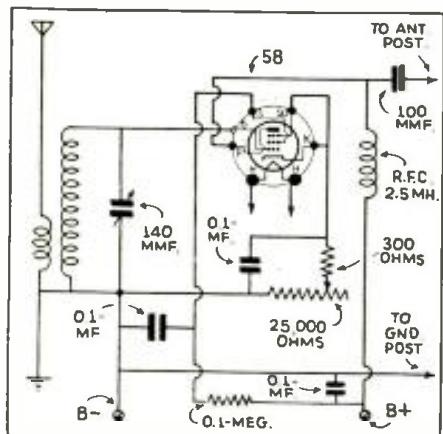(Q) Kindly print a diagram of a 4-tube regenerative receiver, using a 6D6, a 78, and a 42. Also show how 3:1 ratio transformers may be used. Also employ only one plug-in coil. I would also like to



T.R.F. stage diagram.

have you supply me with coil data.

(A) The 4-tube diagram shown comprises an untuned R.F. stage inductively coupled to a regenerative detector with two stages of resistance-coupled audio amplification, resistance-coupling being preferred to transformer-coupling. The

antenna coil is a 2.5 mh. R.F. choke commonly used in S-W receivers.

T.R.F. STAGE FOR DOERLE RECEIVER

Chas. Yorker, Salem, Mass.

(Q) I would greatly appreciate your printing a diagram of a T.R.F. stage which can be added to the 2-tube Doerle band-spread receiver described in the May, 1934 issue.

(A) The tuned R.F. diagram is shown, using standard 4-prong 2-winding coils and a 140 mmf. condenser for tuning. Band-spread is really not necessary because a nonregenerative R.F. stage tunes rather broadly. The output terminals will connect directly to the antenna and ground posts of your receiver.

25-CYCLE POWER SUPPLY

D. Gluch, Crowland, Ont.


(Q) I would like to know whether or not a 25Z5 tube will work in receivers on 25-cycle power, as well as on 60-cycle.

(A) The results would be approximately the same on either 25 or 60 cycles, except for the amount of hum experienced. A 25-cycle supply will require considerably greater filtering than the 60-cycle supply.

COIL DATA

Ralph Peer, Syracuse, N.Y.

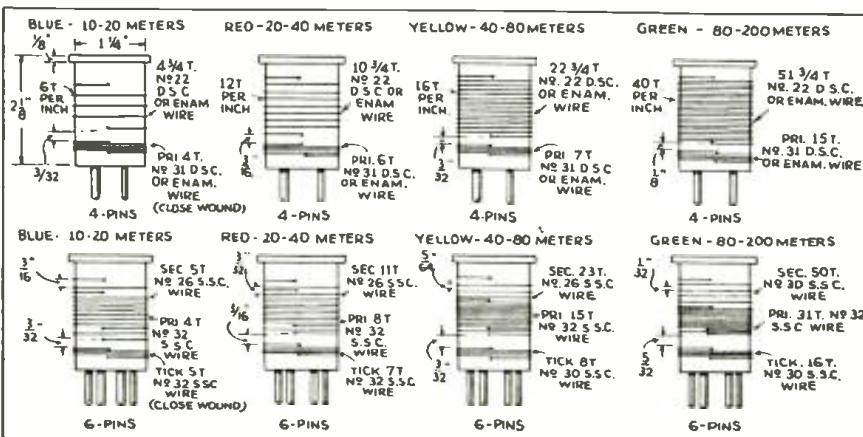(Q) I have built the 3-tube "electrified" Doerle receiver which was described in the May, 1935 issue. All I need is the coil data; would you be kind enough to give



Complete coil data for 2 and 3 winding coils.

EDITED BY GEORGE

Because the amount of work involved in the drawing of diagrams and the compilation of data, we are forced to charge 25c each for letters that are answered directly through the mail. This fee includes only hand-drawn schematic drawings. We cannot furnish "picture-layouts" or "full-sized" working drawings. Letters not accompanied by 25c will be answered in turn on this page. The 25c remittance may be made in


me this information in the next issue of the *Question Box*!

(A) Once again we print the coil data for 2- and 3-winding coils, covering a range of from 15 to 200 meters. It is given in pictorial form, and we suggest that our readers save this data because it can be used in just about every set described in *Short Wave Craft*.

POWER SUPPLY DIAGRAM

David K. McNish, Jr., Huntington, West Va.

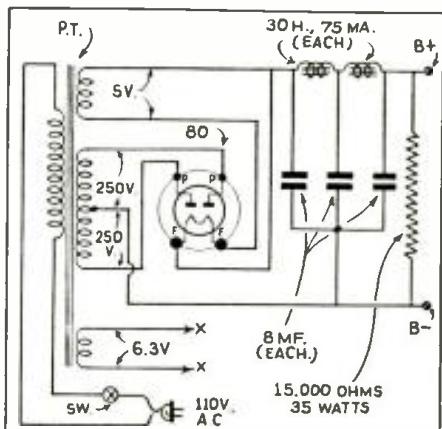(Q) I would appreciate it if you would publish a diagram of a "power supply" unit delivering 300 volts, with a 6.3 volt filament winding for the tubes.



Power supply for Short-Wave receivers.

(A) The power supply diagram will be found on this page. If you wish to obtain various "B" voltages, the 15,000-ohm bleeder should have four or five sliders which may be adjusted to the desired voltages. Each tap on the divider should be by-passed to the "B" negative with a condenser ranging from $\frac{1}{4}$ to 1 mf.

OBTAINING VERIS

Arthur Anderson, St. Paul, Minn.

(Q) I am very much interested in your "Trophy Contest" and have had considerable trouble in obtaining verification cards. I have written to a number of stations and have received no reply. Please outline the correct procedure in obtaining veris, and where can I purchase an International Postal Reply Coupon.

(A) There is no reason why you should not obtain "verification" cards, provided you go about the thing properly. When receiving a station, make a note of the following: The time, date, frequency or wavelength, the character of the program received, together with any other data which may be the result of your observation. Send this, together with an International Postal Reply Coupon to the address of the station; this is given in each issue of *Short Wave Craft*. Make your report interesting and complete, and of some value to the station management.

QUESTION BOX

W. SHUART, W2AMN

the form of stamps or coin.

Special problems involving considerable research will be quoted upon request. We cannot offer opinions as to the relative merits of commercial instruments.


Correspondents are requested to write or print their names and addresses clearly. Hundreds of letters remain unanswered because of incomplete or illegible addresses.

2-TUBE CONVERTER

L. C. Browning, Newark, N.J.

(Q) I have a broadcast receiver which is very sensitive, and I would like to add a converter to it in order to receive short-wave programs. This converter should use a "57" detector and a "56" oscillator. The coils should be 2-winding, 4-prong affairs, and the output of the converter should connect to the antenna and ground posts.

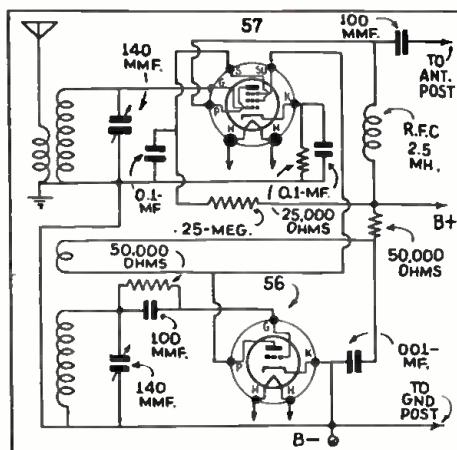(A) We are pleased to print the diagram, and you should obtain excellent results with it, providing your receiver really is *sensitive*. The diagram shown is one in which the two 140 mmf. variable



2-tube short-wave converter.

condensers are operated individually, and not ganged.

WHAT TYPE AUDIO TRANSFORMER?

Roy C. Foss, Chicago, Ill.

(Q) In an article in the July, 1935 issue of *Short Wave Craft* there was a self-powered amplifier with an input transformer not designated. Could this be a 3½ to 1 Thordarson standard amplifier transformer? If not, please give the characteristics.


(A) Any good make of transformer between 2:1 and 5:1 ratio will serve as the input transformer.

2-TUBE E. C. RECEIVER

William C. Baker.

(Q) Would you please show a diagram in the *Question Box* of a short-wave receiver using Na-Ald band-spread coils? This set should use a "58" electron-coupled detector, and a "56" resistance-coupled audio amplifier. The coils are of the 5-prong variety.

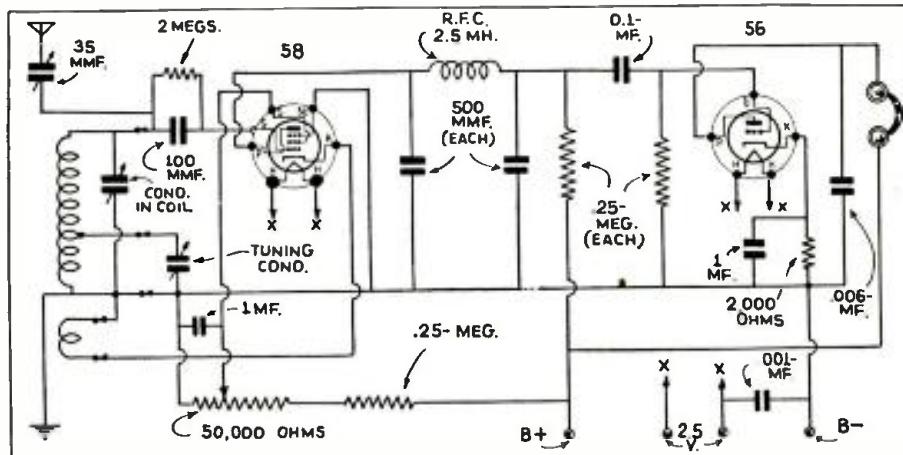(A) We are pleased to print the 5-prong band-spread coil connections in a 2-tube receiver using a "58" and a "56." The conventional tickler or small winding, is con-



Electron-coupled detector and one stage of resistance-coupled audio amplification.

nected in the cathode circuit. The cathode of the tube is connected to the end of the tickler which is nearest to the grid coil.

ANTENNA TRANSFORMER

Paul Davis, Racine, Wis.

(Q) I have recently constructed a doublet antenna having a length of 40 feet in each half. The lead-in and transformer have been quite a puzzle to me. I am told that a suitable transformer can be constructed to match a given lead-in or feeder system to the antenna; also a transformer should be used to couple the lead-in to the receiver. Please let me have your suggestions.

(A) It is impossible to build a transformer which will match any feeder to your antenna, unless you wish to receive on *one particular frequency*. For general reception, no transformer is needed. The transformer which couples the lead-in to the receiver will depend upon the type of lead-in. These can be purchased more cheaply than they can be built.

AUDIO AMPLIFIER DIAGRAM

S. Boorshstein, Detroit, Mich.


(Q) Please publish a diagram of an amplifier using a "57" and a 2A5 tube, and which has its own power supply. This power supply should be capable of running a receiver as well as the amplifier.

(A) The "57" and 2A5 amplifier is quite a high-gain affair, and we have shown the circuit with sufficient decoupling to render the amplifier stable in operation. The power supply will also furnish voltages for a receiver.

1-TUBE POCKET SET

James Shivel, Hendersonville, Tenn.

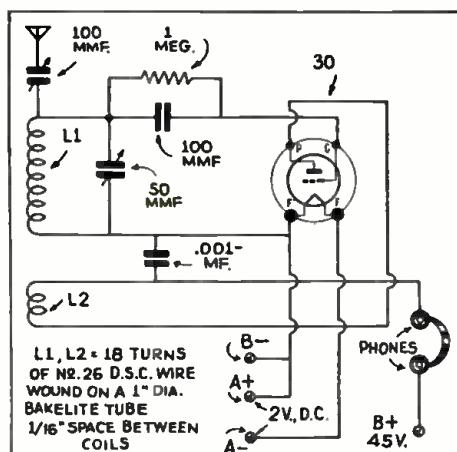
(Q) Please print a diagram in your *Question Box* of the 1-tube pocket set which was described in the December, 1934, issue of *Short Wave Craft*. This was a



The famous "1-tube Pocket Set."

super-regenerative set.

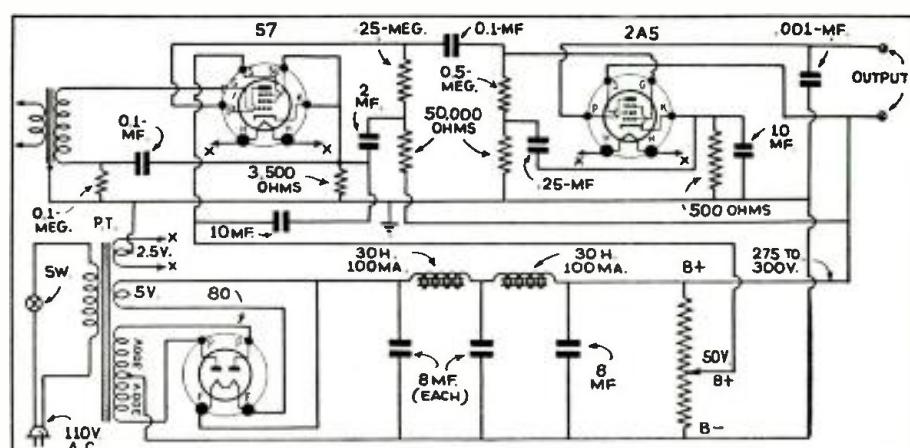(A) The 1-tube pocket set sure did become famous, because nearly every one that built this set received foreign stations without an antenna! We are pleased to print the diagram again, and wish you success with it.



High-gain audio-frequency amplifier having 3 watts output.

Short Wave SCOUT NEWS

Dr. Alan Smith, Reports From Chester, Vt.

- NEW stations heard and logged here in the last month include:

YNDA, Managua, Nicaragua. Heard several evenings on 8590 kc., around 9 p.m. XEFT, Vera Cruz, Mexico. Heard on 6120 kc., best after W2XE and COCD sign off. I have their veri and they say they have a special DX program on Saturdays from 6:30 to 7:30 p.m.

TG2X, Quatamala City, "The Voice of the National Police," heard on 5940 kc. around 9 p.m.

HRN, Tegucigalpa, Honduras, on 5875 kc., heard with good signal. They have a daily schedule of 8-10 p.m., with program of appreciation to listeners who report to them, every Sunday night.

YV4RC, 6375 kc., Caracas, is on daily "sked" with good signal and announces as "Ecos de Avila."

TIPG, 6410 kc., San Jose, Costa Rica, is on daily every evening.

SPW, Warsaw, Poland, 13,635 kc., tested from Oct. 1 to Oct. 15, being heard here on two days around noon, signing off at 12:30 p.m. They usually use telegraphy on same frequency.

TFJ, Reykjavik, Iceland, 12,235 kc., was heard one Sunday, originating a program for CBS.

YV8RB, 5880 kc., located at Barquisimeto, Venezuela, is heard every evening.

Veris received this month: XEFT, TIPG, HJ4ABA, W10XF (the ground station of the stratosphere balloon), DOAI (S.S. Europa), FNSK (S.S. Normandie), HI1J.

Charles Guadagnino, Detroit, Mich., Reports

- HERE are some of the stations heard: YVQ, Maracay, Venezuela, 6.67 meg., broadcasting every Saturday night from 8:00 to 8:30 p.m. E.S.T.

PRADO, Rio Bamba, Ecuador, 6.62 meg., broadcasts on Thursday 9:00 to 11:30 p.m.

HICK, Quito, Ecuador, 5.89 meg., heard between 8 p.m. and 11 p.m. E.S.T.

LSX, Buenos Aires, Argentina, 10.35 meg., heard testing with New York between 6 p.m. and 11:30 p.m., E.S.T.

PRF5, Rio de Janeiro, Brazil, 905 meg., broadcasting from 4:45 p.m. to 5:45 p.m. Address: Postoffice Box 709, Rio de Janeiro, Brazil.


CEC, Santiago, Chile, 10.6 meg., broadcasts Thursday and Sunday 8:30 to 9 p.m.

XBJQ, Mexico City, Mexico, 11 meg., heard broadcasting 8 p.m. to 11 p.m., E.S.T.

COCD, Havana, Cuba, 6.13 meg., heard irregularly 7 p.m. to midnight.

TYA, Paris, France, 12.2 meg. heard working the "Normandie."

A Neat "QSL" Card

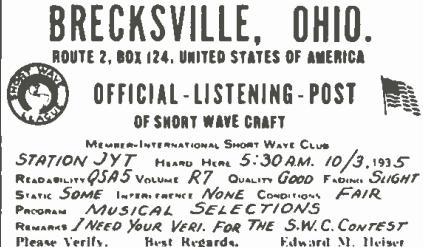

One of our trophy winners, Edward N. Heiser of Brecksville, Ohio, has designed this interesting "QSL" card, on which he has incorporated the insignia of the Short Wave League, and also the fact that his station is an "Official Listening Post" of Short-Wave Craft.

A. B. Rice of Richmond, Va., and his trophy



Above—A. B. Rice of Richmond, Va., and the Short Wave Scout Trophy which was recently awarded him. Mr. Rice in a recent letter says: "It was with much pleasure that I received the beautiful trophy awarded by your magazine. . . . The trophy has been greatly admired, and I will always prize it very highly. . . . I am very pleased to know that I have been appointed 'Official Listening Post' for Richmond, and will endeavor to furnish you with reports at regular intervals as to the results obtained on short-wave reception."

J. C. Storer's Listening Post Report

• I SURELY want to thank all those nice fellows who sent me their SWL cards. We are again enjoying Boundbrook's 16-meter programs, as DJE has faded out in this season. IHI and GSG still come in very good in this band.

19 meters has not been very good; only W8XK coming in as usual.

PMA and SUV have been heard early in the morning; quite good.

On the 25 meters the best has been 2RO at all times. The English and German stations on this wavelength were poor. CEC is coming in R9 for the last few days and it seems that they give daily broadcasts, except Sundays, at 7:00 p.m. E.S.T.

TFK, the new station in Iceland, has been heard for about ten consecutive nights, testing phone with England.

The new station XBJQ in Mexico is "pounding in" fine every evening. The same with W4XB of Miami Beach, Fla.

New stations heard are:

YVNA—8620—Managua, Nicaragua.
HI3C—Voz de Rio Dulce—La Romana, D.R. on 6900 kcs.

YV4RC—6375—Ecos Avila—Caracas.
HJ1ABK—7150—Barranquilla, Colombia. Just inaugurated.

YV5AM—7100—Ecos del Llano—San Juan de los Morros, Venezuela, just received today their verification. Will officially inaugurate this month.

YV8RB—5880—La Voz de Lara—Barquisimeto, Venezuela, has already inaugurated and is coming in R9 at all times. V13RG—7200—Georgetown, British Guiana. Broadcasts commercial programs of the Empire Bar every Tuesday at 8 p.m. E.S.T.

T18W—7550—Ecos del Pacifico—Punta Arenas, Costa Rica. Every evening from 7 to 10 p.m., E.S.T.

I am using a G. E. "V" doublet antenna.

Juan Cloquell Storer,
José de Diego St., No. 1,
P. O. Box 194, Arecibo, Puerto Rico.

Report from Our "Ace" Dial-Twister in Illinois, Edward G. Schmeichel, 12th Trophy Winner

• RECEPTION at this "Post" during the past month has been excellent on all frequencies. Stations from the four corners of the earth have been received with good volume, and very fine programs. I am enclosing a few tips which may be of aid to all listeners. These tips are up to the minute and will be of benefit to all listeners.

PMA—Bandoeng, Java, 19.35 megs., is now operating on a regular schedule Tuesday, Thursday, and Saturday mornings from 10—10:30 a.m., E.S.T. They have a loud, clear signal and are heard very nicely. For a real treat, try for them on the above schedule.

YV2RC—Caracas, Venezuela, 5.80 megs., has moved to this frequency and are heard daily from 6—10 p.m., E.S.T., with tremendous volume, and crystal-clear signals. They announce in English, and use a 6-note chime at every 15-minute interval. They previously were on 6.11 megs.

DJ1—Berlin, Germany, is a new German station operating daily from 12—2 p.m., E.S.T., on a frequency of 14.41 megs. They are heard very clear, and no difficulty should be experienced in hearing them.

DJB—Berlin, Germany, 15.20 megs., has again returned to the fold, and are now operating daily from 9—11:30 a.m., E.S.T. They have a strong signal since their aerial is "beamed" toward North America. They request reports and send very attractive QSL cards.

RIM—Tashkent, U.S.S.R., is heard every Saturday morning at 8:30 a.m., E.S.T., and earlier phoning RKI Moscow. They are heard very loud and clear, and reports of reception should be sent to Comite de Radiodiffusion et Radiofication, Petrova 12, Moscow, U.S.S.R. As a matter of fact all stations heard from the U.S.S.R. provinces, including Siberia, should be sent to this address. They verify all reports.

(Continued on page 567)

Hi! Special Xmas Greetings to S.W.C. from Australia

All readers of Short Wave Craft are cordially invited to listen-in to a farewell program from VK2ME-3ME-3LR given to this post as follows: Dec. 29, 1935. VK2ME will give a Farewell Program to Oliver Amlie, members of the International 6000-12,500 Mile Club, and greetings to all Short Wave Craft readers, time 6:45 to 7:15 a.m., Eastern Standard Time. VK3ME will give the same Farewell Program of a different nature to the same party on Dec. 26, 1935, time 6:45 to 7 a.m., Eastern Standard Time. VK3LR will also give a Farewell Program to same party on Dec. 30, 1935, time 6:45 to 7:15 a.m., Eastern Standard Time, and greetings to Short Wave Craft readers.

Both the writer and each station would appreciate a report of reception on these transmissions. This post will finish his work in this zone of Australia on the three main Australian stations December, 1935; from January to October 23, 1935, this post has cleared 260 reports, or veris on these three Australian stations, or 360 hours. Hope to get 365 veris, and 500 hours in this zone, ending December, 1935, and hope to win the first Australian Trophy for this work with only a "three-tube" receiver. If the trophy is received, readers of Short Wave Craft will be able to see it as a photo will be sent to the Editor of Short Wave Craft.

The Australian "farewell" programs will be heard in every country in the world, it is hoped. I wish all readers of Short Wave Craft a Merry Christmas and a Happy New Year.

Oliver Amlie,
Philadelphia, Pa.

Keep An
Allied Catalog
By Your Side-
It Pays !

"We're doing our Radio Buying"



100% from ALLIED's catalog

1

"We're tough customers. We know what we want, the kind of service we want and what price we want to pay. That means we know real value when we see it."

2

We've been around—we've done plenty of shopping—and we're through experimenting. Now we've found the right answer for every single one of our radio needs.

3

We're doing our radio buying 100 per cent from ALLIED. We know that only ALLIED can give us the quality, the low prices and the real service that we want. That's why we keep an ALLIED Catalog handy—It pays!"

**WRITE
FOR**

**YOUR
COPY**

FREE

Send this coupon now!

ALLIED RADIO CORPORATION
833 W. Jackson Blvd.
Chicago, Ill.

Dept. E


Send me your FREE 1936 Catalog—Radio's
Leading Supply Guide

Name.....

Address.....

City..... State.....

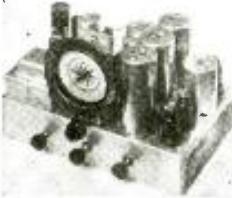Allied Radio
CORPORATION
833 W. JACKSON BLVD., CHICAGO
“EVERYTHING IN RADIO UNDER ONE GREAT ROOF”



ALL-WAVE PATHFINDER
6 TUBE SUPER HETERODYNE
Featuring ALL METAL TUBES

With glass tubes if specified

Uses 1—6A8, 2—6K7, 1—6J7, 1—6F6, 1—5Z4. Individual Coils for each Band. Positive Contact Band on all Bands. Crowe Micro Master Band Spread Dial. Covers complete spectrum from 16 to 550 meters.

Selector Switch, with Monel metal contacts. Pre-selector Stage on all Bands. Crowe Micro Master Band Spread Dial. Covers complete spectrum from 16 to 550 meters.

\$2150
8-inch Dynamic Speaker \$2.95

MAIL ORDERS FILLED



Dept. S-12

FREE CIRCUIT ON REQUEST

167 GREENWICH ST.

NEW YORK, N. Y.

MUTER DE LUXE TUNING SELECTOR

"BIG AJAX"

FOR QUIET FOREIGN RECEPTION

Big Ajax—reduces static and interference. Ends forever the nuisance of mangled, noise-ridden short wave reception—install Big Ajax between your antenna and receiver.

Here's an accurate, impedance-matching, tuning selector for coupling a doublet antenna to any receiver. Its easily adjusted switches correct many reception troubles, greatly increasing volume and improving selectivity.

It's got a noise reduction shield that takes out man-made static, like an All-American Half Back takes out an opposing End. Hook it up between your antenna and your set and learn what quiet foreign reception is really like.

Your jobber has them—get one today. Or mail the coupon NOW and we'll send it postpaid for \$2.50. It's guaranteed to improve reception or your money will be refunded. PRICE \$2.50.

MAIL THIS COUPON!

THE MUTER COMPANY
 1255-P South Michigan Ave, Chicago, Ill.

Please RUSH me one of your "BIG AJAX" I am enclosing \$2.50
 I will pay mailman \$2.56. It must be satisfactory in every way.

Name

Address

City, State

Improved 3-Tube "Doerle"

(Continued from page 521)

In the audio portion of the receiver, we have two stages of resistance-capacity coupled amplification; a single 19, which is a twin triode, serves for the two stages. Tremendous amplification is obtained with this tube lineup, and even the weakest stations can be brought in with full earphone volume. The stronger stations will operate a magnetic speaker. However, no power output stage is used, and the best results would be obtained with the use of earphones, rather than a speaker.

Has R.F. Stage

The radio frequency and detector stages are tuned with a two-gang 140 nmf. condenser assembly, allowing single dial tuning. Padding in the R.F. stage is accomplished through the loading effect obtained by adjusting the small condenser connected across the interwound winding of the antenna coil. This is the same winding that is used as primary or R.F. plate coil in the detector circuit. The entire receiver is built on a commercially available, stamped and drilled chassis. This chassis has six tube holes, but only five of them are used.

Looking at the front of the receiver, we see the large airplane type tuning dial in the center. This dial can be of the "dual-ratio" type if band-spread is desired. The small knobs along the bottom of the panel are used as follows: From left to right, on-and-off switch, antenna trimmer, throttle condenser for regeneration control, and filament rheostat. In the rear view, we have the two six prong-3 winding plug-in coils on either side of the chassis. Behind the left-hand plug-in coil is the 34-R.F. amplifier. Behind the right-hand coil, is the regenerative detector; the "19" is between the two plug-in coils. For smoothness in operation, regeneration is controlled through the use of a "throttle" condenser.

The underneath view of the receiver shows the various resistors and by-pass condensers. Note the absence of transformers. Through the use of resistance coupling, quite a saving is brought about in the cost of construction, and the tone quality is all that could be expected of any good short-wave receiver. The particular chassis used, measures 10½ inches long, 7 inches deep, and it fits into a cabinet which is finished in black crackle enamel, to match the front panel. Building receivers on metal chassis, and using metal cabinets, not only enhances the appearance of the receiver, but increases the efficiency considerably. It also simplifies tuning because serious body capacity effects are eliminated.

Standard plug-in coils are used. These have three windings, and cover a range from 15 to 200 meters. On the plug-in coils, the small winding at the base of the coil is used as the antenna coupling coil in the RF stage, and as the tickler or feedback coil in the detector stage. The largest winding is used as the grid coil in both cases. The interwound winding is used in the R.F. stage as the trimming coil, and in the detector stage, as the plate coupling coil of the R.F. stage. In connecting up these coils, remember that the top of the largest winding always connects to the grids. The top of the interwound winding in the detector coil connects to the plate of the R.F. tube, and the bottom of the tickler winding goes to the plate of the detector tube.


Any antenna having a length approximating 75 feet, or over, will give satisfactory results. The length of the antenna should be considered directly from the receiver to its farthest end. If a doublet is used, the one set of the antenna coil indicated by the dotted line, is not grounded. In other words, the connections marked "1," "2," and "3," are connected as follows: No. 1 to the antenna, and Nos. 2 and 3, shorted, i.e., with an antenna and ground combination. With a doublet, the connection between "2" and "3" is eliminated, and the two leads of the feeders or lead-in's connect to the terminals "1" and "2." For

MUTER
 The MUTER COMPANY
 1255-P S. Michigan Av.
 CHICAGO, ILL.
 U.S.A.

complete coil data, see the Question Box.

Parts List for "3 Tubes Equal 4"

- 1—2-gang 140 mmf. condenser.
- 2—140 mmf. variable condensers, Hammarlund.
- 4—1 mf. by-pass condensers, Cornell-Dubilier.
- 1—100 mmf. mica condenser, Cornell-Dubilier.
- 1—.006 mf. mica condenser, Cornell-Dubilier.
- 1—3 meg., $\frac{1}{2}$ watt resistor, I.R.C.
- 2—50,000 ohm resistors, $\frac{1}{2}$ watt, I.R.C.
- 2—250,000 ohm resistors, I.R.C.
- 1—2.5 mh. R.F. choke, Hammarlund.
- 2 sets of 4, 6 prong plug-in coils, Na-Ald.
- 2—4-prong wafer sockets, Na-Ald.
- 2—6-prong wafer sockets, Na-Ald.
- 1—15 ohm rheostat.
- 1—4 inch airplane type dial.
- 1 metal Chassis and Cabinet, Radio Trading Co.
- 1—type 34 tube, Aro.
- 1—type 30 tube, Aro.
- 1—type 19 tube, Aro.
- 3—45 volt "B" batteries, Burgess.
- 2—1 $\frac{1}{2}$ volt dry cells, Burgess.

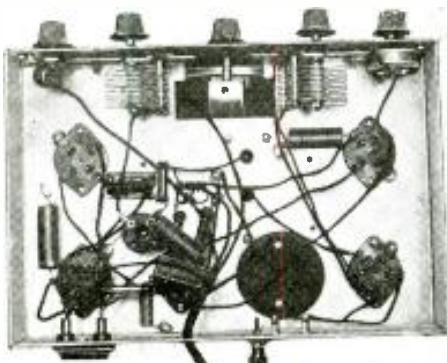


Bottom-view of 3-Tube Doerle.

11 Tube Receiver

(Continued from page 534)

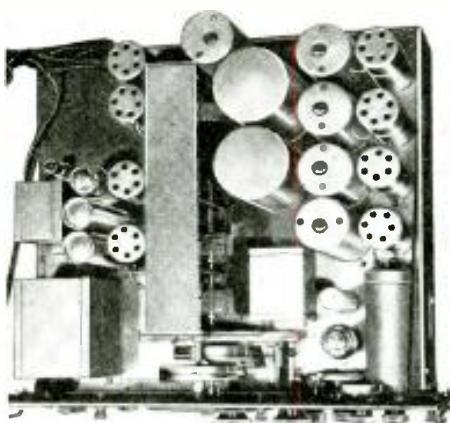Victor Division, RCA Mfg. Co. Inside the receiver, a terminal strip with jumpers is provided in order to change for operation either from batteries or A.C. power line.



This view shows the chassis.

New 1936 Allied Radio Catalog

THE new "Streamlined" Allied Radio Catalog for 1936 is "packed full" of data on the latest radio apparatus of interest to every amateur and set-builder. The main sections of this snappy new catalog are devoted to metal tubes, all-wave, short-wave, battery and auto sets; also new public-address sound equipment, new service test equipment and tools, short-wave receiving and transmitting apparatus, together with thousands of standard replacement and set-building parts. Every "Ham" and "Fan," will want a copy of this valuable book. Ask for Catalog No. 510, Service Department, Short Wave Craft, 99-101 Hudson St., New York City.

*A gift that will bring joy
to any man or boy*

For a Merry Christmas

SEND FOR EITHER OF THESE EXCELLENT RECEIVERS TODAY!

IMMEDIATE DELIVERY GUARANTEED!

FULTONE V

3-Tube Set

NEW FIVE - IN - THREE SET
6D6—6F7—12A7
ALL-ELECTRIC



BUILT - IN LOUD SPEAKER
ENTIRELY SELF-CONTAINED

**1936 MODEL
NOW!! WITH FULL
B-A-N-D-S-P-R-E-A-D**

OF ALL HAM BANDS AND
FOREIGN STATION
BANDS AT NO EXTRA
COST!!

Screen grid RF stage—Screen grid regenerative detector—High gain first audio tube—Power pentode output—Voltage rectifier. FIVE tube performance from THREE new type tubes! Self contained, builtless power supply—operates on 110 volts AC or DC—Triple winding coils—Velvet smooth, large alnico vernier dial—Pull loud speaker volume—Tuning range $5\frac{1}{2}$ to 625 meters.

We're proud of it—and we know you will be too! Order your 1936 Fultone V today and enjoy real reception. Try it yourself for five days—full cash refund if you want it.

COMPLETE FULTONE V THREE TUBE RECEIVER KIT of all necessary parts including large airplane dial, crystal finished metal chassis and panel with all holes, four coils $5\frac{1}{2}$ to 200 meters, and complete easily followed wiring and tuning instructions. (Not wired, less tubes, cabinet, loud speaker and broadcast coils). Three matched guaranteed tubes. Metal Cabinet for above. Loudspeaker to fit in set. 200 to 625 meter Broadcast and Long Wave coils. Two coils. Laboratory wired and tested.

\$6.95
\$2.20
1.25
1.45
1.25
1.50

ISOLATED REGENERATOR TUBE

This sensational new feature alone makes Royal's new professional receiver the outstanding Communications Type receiver of today! Twenty other ROYAL features will convince you that this is the only set for you! Read pages 406 and 125 of the November issue of Short Wave Craft for complete description. Available with either metal or glass tubes. Please state your choice when ordering.

Complete "PR-SIX" Receiver

With built-in power supply and large dynamic speaker. Complete with SIX real STEEL Tubes, all coils $5\frac{1}{2}$ to 625 meters, and \$31.45 attractively finished heavy steel cabinet. Laboratory wired and tested, ready to plug in and operate!

31-45

SPECIAL COMBINATION OFFER

Complete Fultone V 3-Tube receiver kit, not wired, but with 3 tubes, Two Broadcast band coils, Loudspeaker and Cabinet net. Laboratory wired and tested \$1.50 extra

1145
1.25
1.45
1.25
1.50

**Order direct for immediate shipment by mail,
or if in New York—**

Call At Our New Large Salesroom

12 West Broadway (Between Barclay and Vesey Streets)

LARGE STOCK

(We are one of the few with enough confidence in our products to cheerfully demonstrate)

Send for new large catalog

Dept. C-1, New York City
142 Liberty Street

HARRISON RADIO CO.

ROLAND'S 100% 5 Tube Bandspread Receiver

Our Engineering Dept. has now perfected our short wave receiver to provide 100% band-spreading on all bands from 15-200 meters. This has been accomplished with the new dual ratio airplane dial with its 125-1 ratio band-spread pointer.

You may now use this receiver for your daily communication work and log your stations accurately for repeat tuning. For the short wave fan these new features will aid in separation of the foreign and domestic stations on all congested bands.

Phone jacks with speaker cutout switch are mounted on front panel for easy accessibility. Complete shielding of all stages to eliminate R.F. and audio feedback. A highly sensitive regenerative circuit using a tuned R.F. stage with a newly perfected system for equalizing both stages, makes this an ideal short wave receiver for both ham and short wave fan.

Tubes employed are the newly developed 6.3 volt types: 6D6, 6F7, 76,

42 and 80. Set is mounted on a black wrinkled heavy steel chassis.

Chassis wired and tested with 8 coils without cabinet, speaker, power supply, and tubes.

Cabinet for above

Five Sylvania set tested tubes.


6" short wave dynamic speaker

Short wave hum free power supply

Complete kit of parts for set and power supply, less speaker and tubes.

No. R 2000, same receiver as No. R 1000, but complete with Pack and Speaker in Cabinet, wired and tested, with 5 tubes, ready to operate.....\$23.25

Can also be obtained A.C.-D.C.

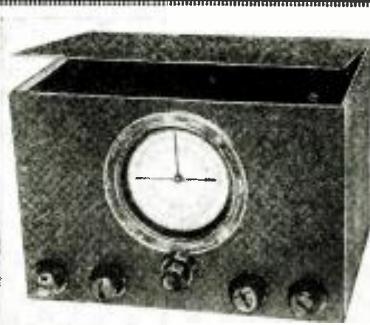

MODEL R 1000

\$11 75

\$ 1.75
3.50
2.00
4.95
14.75

No. R 2000, same receiver as No. R 1000, but complete with Pack and Speaker in Cabinet, wired and tested, with 5 tubes, ready to operate.....\$23.25

Can also be obtained A.C.-D.C.

ROLAND RADIO CO.

1340 E. 9th St.,

Dept. S-1-36,

Brooklyn, N. Y.



PR-16, complete with 16 tubes, metal cabinet, speaker, less crystal.....\$ 95.70
PR-16C, same as PR-16 above, but with crystal.....\$101.70

W M A R I N E R G O T R A D I O C O M P A N Y Q

124-11 101st Avenue
Richmond Hill, N. Y.

HERE At Last! THE PATTERSON PR-16

16 TUBE SUPER HET

The patience of the many thousands of amateurs—experimenters—and professional operators who have been waiting for this model—is gratefully acknowledged. In case you haven't seen the specs on this most advanced all-wave receiver—check some of these.

*Three stage push-pull audio.

*18½ watts audio output. Less than 2% distortion.

*Beat frequency oscillator for CW reception.

*16 tube superhet.

*Crystal filter can be cut in as a series or parallel filter.

Write for descriptive catalog material on this and other models. Also a complete group of amateur transmitters.

We are also making immediate delivery on Sargent, RME-69, Silver, Hammarlund, RCA, Hallicrafters Super Skyriders, Brettling, etc.

*Five band range. Full 8 to 550 meters.

*Dial shutter—Patterson camera type.

*Audio channel flat=2 db from 50 to 10000 cycles.

*12" dynamic speaker.

*AVC and manual volume control.

*Six months guarantee—you can't go wrong.

FACTORY TO YOU

LATEST MODEL REMINGTON TYPEWRITERS

BRAND NEW, latest model Remington Portable for only 10¢ a day! Here is your opportunity to get a perfect writing machine at an amazingly low price direct from the factory. Every essential feature of large office typewriters—standard 4-row keyboard, standard width carriage, margin release, back spacer, automatic ribbon reverse. Act now, while this special opportunity holds good. Send coupon TODAY for details.

You Don't RISK a Penny

We send you the Remington Portable, Model 5, direct from the factory with 10 days' free trial. If you are not satisfied, send it back. We pay shipping charges both ways.

FREE Typing Course and Carrying Case

With your new Remington you will receive FREE a complete simplified home course in Touch Typing. Follow instructions during



your 10-day trial period and see how easy expert typing can be. We also will send you FREE a sturdy carrying case of 3-ply wood covered with heavy Du Pont fabric. Mail coupon for full details—NOW.

Remington Rand Inc., Dept. 214-1

205 East 42nd St., New York, N. Y.

Please tell me, without obligation, how I can get a New Remington Portable, plus Free Typing Course and Carrying Case, for 10¢ a day. Send Catalogue.

Name

Address

City State

Please mention SHORT WAVE CRAFT when writing advertisers

Practical 5-Meter Antenna Design


(Continued from page 535)

chief radio man for all of the hotels under the management of Ralph Hitz, we were able to secure free access to the roof of the Hotel New Yorker. This roof is some forty-four stories, or approximately six hundred feet above the street. Our receiving and transmitting equipment was placed in a large motor room on the forty-third floor and the antennas, themselves, were approximately one hundred twenty-five feet above this point. It is difficult to imagine any place where local interference would be quite as bad as in this location. For the purpose of studying the means for reducing local noise, resulting from the use of noise-reducing antenna systems, it is doubtful that a better location could be found.

Our first antenna was a simple half-wave dipole, as shown in Fig. 1. This antenna was tied to the end of an 8-foot stick and it was stuck out from one of the

FR. MC.	W.L. MET	O1	D2	D3
56	5.357	8' 3"	430	440
57	5.263	8' 0"	13.068	13.167
58	5.172	7' 11"	12.67	12.768
59	5.085	7' 10"	12.54	12.635
60	5.0	7' 8 1/2"	12.418	12.5
			12.21	12.3
			475	13.8
				29.7
				28.8
				28.5
				28.2
				27.75

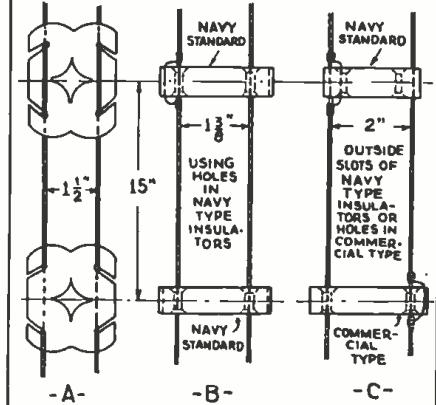HI-MHO WIRE IN ALL LINES (LIGHT WEIGHT FOR LESS THAN SOFT, HEAVY WEIGHT FOR LONGER LINES)




Correct dimensions for various radiators and reflectors.

supporting members of the hotel's huge Neon sign. The antenna proper was approximately level with the window and the room where our receiver was installed; and the lead from the antenna to the receiver was approximately twenty-five feet long. In order to determine the effect of introducing long lengths of transmission line, the antenna circuit was opened and various additional lengths were introduced. No variation in signal intensity was noticed.

Our next move was to the matched impedance type of antenna, shown in Fig. 2. No particular difference was noticed between this antenna and the arrangement shown in Fig. 1, so far as signal strength was concerned, but the system shown in Fig. 1 was a very much better system for eliminating interference.

SELECT YOUR HOLIDAY GIFTS from this LIST of REAL SHORT WAVE VALUES

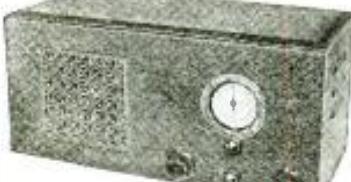WE GUARANTEE SATISFACTORY RESULTS ON ALL OF OUR PRODUCTS



pentode output
stage-high voltage rectifier and built-in power supply. Operates entirely from 105 to 130 volt AC lighting socket. Entirely self-contained. Dimensions 14x7x28".

Uses 6DG-6CG-7G-12-81 hi-gain tubes as Tuned RF amplifier-Tuned screen-grid regenerative detector-powerful 2 stage audio frequency amplifier with pentode output stage, rectifier & built-in power supply. Hum-free. Completely self-contained. Operates entirely from 105 to 130 volt AC lighting socket.

Uses special dual ratio, double scale, multi-colored, bandspread, illuminated airplane type dial of great beauty. Positively no backlash. Continuous bandspread from 9½ to 600 meters. Any of the AMATEUR BANDS or foreign SW bands may be spread over from 80 to 100% of the bandspread scale.

Automatic jack for phones—volume control—built-in high fidelity dynamic speaker—hum free—connections for doublet or single wire antenna—beautiful, black shrivel finish metal chassis and cabinet—selectivity, sensitivity, and tonal qualities that will amaze you.

HG-36 KIT of all necessary parts, unired, 4 coils for 9½-200 meters, & instructions (less tubes, cabinet, & BC coils)	\$14.95
Beautiful metal cabinet82.50
5 Matched Arcturus tubes.....	2.85
SPECIAL: Complete kit, cabinet & 5 tubes, less BC coils & unired	\$17.95
Labor for wiring & testing, ready to use, extra	2.00
2 Broadcast band coils, if desired	1.25

EILEN HG-36 5-Tube Bandspread Receiver

A POWERFUL, CUSTOM-BUILT, TUNED RADIO FREQUENCY regenerative short wave receiver that WILL PRODUCE RESULTS. See editorial description pages 471 and 488 December issue of SWC.


Uses 6DG-6CG-7G-12-81 hi-gain tubes as Tuned RF amplifier-Tuned screen-grid regenerative detector-powerful 2 stage audio frequency amplifier with pentode output stage, rectifier & built-in power supply. Hum-free. Completely self-contained. Operates entirely from 105 to 130 volt AC lighting socket.

Uses special dual ratio, double scale, multi-colored, bandspread, illuminated airplane type dial of great beauty. Positively no backlash. Continuous bandspread from 9½ to 600 meters. Any of the AMATEUR BANDS or foreign SW bands may be spread over from 80 to 100% of the bandspread scale.

Automatic jack for phones—volume control—built-in high fidelity dynamic speaker—hum free—connections for doublet or single wire antenna—beautiful, black shrivel finish metal chassis and cabinet—selectivity, sensitivity, and tonal qualities that will amaze you.

An unusual value for the SW fan or the AMATEUR who wishes a REALABLE COMMUNICATIONS RECEIVER. Send for literature.	
HF METAL GLASS TUBES (OK7 - GJ7 - 6C5 - 6F6 - Z11) are preferred over the glass type, add \$1.00.	

HF METAL GLASS TUBES (OK7 - GJ7 - 6C5 - 6F6 - Z11) are preferred over the glass type, add \$1.00.	
---	--

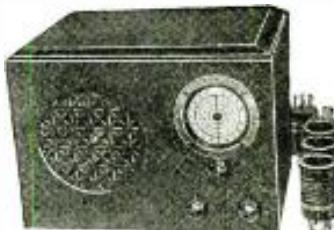

EILEN 6A SHORT WAVE 4-TUBE RECEIVER


A midgetin size—A giant in performance The new, sensational, 1936 Eilen 6A receiver is truly a masterpiece in design. Its unusual design, conforming to the best in modern engineering theory, has all of the latest up-to-the-minute features. FULL 6 TUBE PERFORMANCE.

Uses 6K7 (metal-glass)—6F7 (twin 2 in 1)—6C5 (metal-glass)—12A7 (twin 2 in 1) hi-gain tubes as aperiodic RF amplifier, screen grid regenerative detector, POWERFUL 3 stage audio amplifier with pentode output stage, rectifier & built-in power supply. Hum-free. Completely self-contained. Operates entirely from 105 to 130 volt AC or DC light socket.

BAND SPREAD TUNING TRIMMER—in hi-quality loudspeaker—automatic headphone jack—large, airplane vernier tuning dial—large 3 winding low-loss inductances—selectivity, sensitivity, and volume that will amaze you. Heavy, black shrivel finish metal chassis and cabinet. Foreign speaker reception under fair conditions.

ORDER YOURS TODAY! YOU'LL NEVER REGRET IT!

EILEN 6A KIT of all necessary parts, unired, with 4 coils for 10-200 meters & instructions (less tubes, batteries, cabinet, & BC coils)	\$7.75
Beautiful cabinet	1.25
4 Matched Arcturus tubes	3.15
Special loudspeaker	1.45
2 Broadcast band coils	1.25
SPECIAL: Complete kit, cabinet, tubes, BC coil & instructions (less speaker, unired)	\$12.75
Labor for wiring & testing, ready to use, extra	1.50

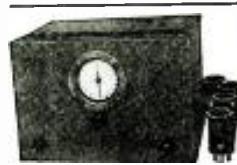

EILEN 5A SHORT WAVE 4-tube RECEIVER

The finest, low-priced, SW receiver on the market. The sensitivity, volume, unusual beauty, and hum-free reception obtainable from this set make it an outstanding value. Uses 6DG-6CG-7G-12-81 (twin 2 in 1) tubes as aperiodic amplifier, screen grid regenerative detector, 2 stage audio amplifier with pentode output tube, rectifier and built-in power supply. Operates entirely from the 105 to 130 volt AC or DC light socket. Hum-free.

See article p. 343 October issue of SWC.

BAND SPREAD TRIMMER —Large, airplane type vernier dial—tremendous headphone volume—operates a speaker on many stations—large 3 winding coils for selectivity and efficiency—so simple that even a beginner can operate it—heavy, black shrivel finish metal chassis and cabinet.	
“So simple that even a beginner can operate it. Owners report dozens of foreign SW stations with loudspeaker volume. You can do the same under fair conditions.”	

HF METAL GLASS TUBES are preferred over the glass type, add \$1.00.	
AMATEURS: Model 5A-AB same as 5A except designed especially for 10-10-80-160 M bands. \$1.00 extra.	

HF METAL GLASS TUBES are preferred over the glass type, add \$1.00.	
AMATEURS: Model 5A-AB same as 5A except designed especially for 10-10-80-160 M bands. \$1.00 extra.	

Cannonball phones \$1.35. Magnetic speaker, unmounted \$1.45 (In beautiful cabinet \$2.75).


FREE Catalogue of SW receivers, transmitters, transceivers, and accessories. Send for your copy. Prompt Shipment. 36 hour service. Telegraph orders rushed to you. 20% deposit on COD orders. QUALITY—HONESTY—SERVICE.

EILEN RADIO LABORATORIES,

Coupling to the Receiver

Wherever the low impedance Giant Killer Cable type of transmission line was employed, the coupling to the receiver was in the form of a two-turn coupling coil. With receivers in which the regular National Midget Coil Forms support the tuning winding, the making of such a coupling coil is a very simple matter. Number 14, solid, enamel wire is wound into a self-supporting coil, with its two ends projecting. The diameter is such as to permit it to fit snugly into the coil form. The turns may be spaced the same distance as the diameter of the wire. When such a coupler is employed, the coupling between the line is variable and it permits the operator to control both the sensitivity and the selectivity. It requires no changing, after finding the optimum position, unless more than ordinary sensitivity and selectivity are required for a specific purpose. Such a coil forms a fairly close match for the low impedance transmission line of G-K cable, used in our work.

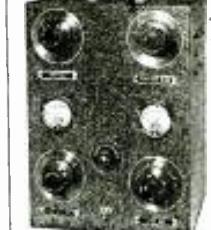The third type of vertical dipole was the system employing the so-called Picard type of antenna shown in Fig. 3. This type of antenna has been designed to provide a suitable impedance match between the low impedance, current-fed dipole and a high



EILEN HF-35 SW 3-tube TRANSMITTER

SEE FEATURE ARTICLE pages 474 and 475 of Dec. issue of SWC. A POWERFUL and well designed amateur band transmitter that you can be proud to own.

CRYSTAL CONTROL—TRI-TET OSCILLATOR—DOUBLER—CLASS C RF POWER AMPLIFIER—TRIPLETT METERS—EILEN TRANSMITTING DIALS—BUILT-IN AN-

35 WATTS OUTPUT ON 20-10-80-160 meter bands.

Extremely beautiful appearance. Heavy, black shrivel finish metal shelving and cabinet. Highest quality of parts used.

TENNA TUNING SYSTEM—20-10-80-160 meter bands.

Very fine, built-in antenna tuner.

Very fine,

NEW Sets for OLD! AT $\frac{1}{3}$ THE COST

A sensational new idea now makes it possible for you to own a custom built radio at a fraction of the cost of a factory built model of equal performance! Why discard your present radio when the cabinet and much of the equipment can be utilized in an up-to-the-minute circuit which brings you superlative world-wide all-wave reception? Other features include: automatic volume control, highest sensitivity and selectivity, etc. Your own radio serviceman is undoubtedly a Tobe Modernization Engineer. Tear out this ad and ask him about it. You'll be amazed when he gives you a price for modernizing your receiver. If he cannot—write for name of the nearest Tobe Modernization Engineer.

SERVICEMEN! DEALERS!

If you have not already done so, get a copy of Zeh Bouck's book on this new phase of radio Servicing. Nearly 1000 servicemen have already entered this field. Write today for Book and Free Merchandising Plan and Sales Promotion Kit.

Tobe Deutschmann Corp., Dept. SW-16
Canton, Massachusetts

I am a customer serviceman
 Send me name of nearest Tobe Modernization
Engineer. I own a receiver.
 I enclose 25c for Zeh Bouck's Book and Free
Sales Promotion Kit.

Name _____
Address _____
City..... State.....

CABINETS
for ALL STAR SR. & JR.
with hinge cover
finished to match
the ALL STAR
SET.



Our Low Price
\$3.95

We do not supply panel, dial or knobs
for ANY MAKE RECEIVER. Send drawing, blue print
or give complete description for estimate.
Dealers and Jobbers: Write for special prices.
KORROL MFG. CO., Inc. Dept. S-1
232 GREENWICH ST. NEW YORK CITY



ACME PHONES PROVIDE

Superior performance at remarkably low cost. Sturdy construction—Lightweight—The most phone for the money.

ACME SPECIALTY CO.
2000 MENDEL ST. CHICAGO, ILL.

LEARN RADIO

225 Graduates Placed in the Last Four Years
At the oldest, largest and best equipped privately owned
radio operating school in the East. Western Electric and
RCA tube transmitters; 225 licensed graduates placed in
past four years in broadcasting, shipping, police radio,
aviation, service work, etc. Course prepares for all U.S.
Government Telegraph and Telephone licenses. Send for
40-page catalog, investigate. New classes every eight
weeks from Sept. 9th. Open all year around.
MASS. RADIO SCHOOL 18 Boylston St., BOSTON
R. F. Trop, Pres.—EST. 1899—G. R. Entwistle, Pres.
One of America's leading Radio Schools

spaced a half wavelength apart and the radiators are spaced a quarter of a wavelength from the reflectors. The high impedance transmission line employed, in this case, was tuned with a pair of variable condensers, as shown. A very much simpler arrangement which accomplishes the same result is illustrated in Fig. 8. Here the same general dimensions for the radiator and reflector portions are employed and the quarter-wave matching section is made up of two pieces of regular stranded enamel antenna wire, spaced two and a quarter inches apart.

One very important point in the construction of antennas such as shown in Fig. 8, is the quarter-wave matching section. The total distance ABCD must be exactly half of a wavelength.

The Latest Antenna

Since moving from the Hotel New Yorker, to the Forty Wall Street Building, where our equipment is located more than nine hundred feet above the street, we have run into several problems which our experience at the Hotel New Yorker did not cover. The tower in which we now have our station is a very ornate affair and we find ourselves in a position where there is practically no roof space. Therefore, we cannot avail ourselves of the advantages of beams and all of our antenna activity must be conducted with comparatively simple units. The arrangement shown in Fig. 9. is, if we forget about the reflectors indicated by the dotted line, essentially the same as Fig. 8, except for the fact that the half-wave radiators are disposed one above the other, instead of being parallel and a half a wave apart.

This type of antenna is two half-wave vertical elements, with a quarter-wave matching arrangement, fed by a low impedance transmission line. In this case, each of the radiators, themselves, are actually ninety-five percent of a half wavelength long and they are about two and a half inches apart at the center.

The arrangement it is necessary for us to make for using an antenna of this nature, is to provide ourselves with several 8-foot lengths of two by two inch sticks. The antenna and its supporting members are attached to these sticks, as shown in Fig. 10 and then the sticks, themselves, are pushed out the window, for a distance of at least nine feet, which is more than a half wavelength away from the building itself, which is copper-covered.

For simplicity of construction, we arranged to use a very light aluminum tube for the upper radiator and a length of copper sash cord for the lower radiator and the matching section. The insulators for supporting the matching section, are permanently fastened to the outside two by two, as is the 8-foot sash cord, which forms the lower half of the antenna. The outside antenna insulator is provided with a suitable length of aluminum tubing, into which the 8-foot section may be slid. This type of antenna has resulted in a very marked increase in our signal strength and because the transmission line used with it is a twisted pair, the reduction in noise is very apparent and its simplicity would seem to suggest that it will become very popular among 5-meter station owners.

All-Wave Set Modernization Book

• **ZEH BOUCK**, whose name is known to short-wave Fans and Hams up and down the land, is the author of a popular new book entitled, "8,000,000 Jobs for the Service Man," this book being sponsored by the Tobe Deutschmann Corp. It gives detailed information on the changes necessary for converting the average broadcast receiver into a modern "all-wave" set. This book also tells how you can make money by modernizing old broadcast receivers, and includes photos, diagrams and methods of getting business, etc. The complete merchandising plan, including Zeh Bouck's book is obtainable at 25c. Ask for book and plan No. 511, Service Department. Short Wave Craft, 99-101 Hudson St., New York City.

Guaranteed RADIO TUBES at New LOW PRICES!

Complete Stock Ready for Immediate Shipment

Order from this page—Remit 20% with order, balance C. O. D. All prices are F. O. B. FACTORY, Newark. Shipments go forward express or parcel post. No order for less than \$3.00 accepted.

DEALER'S NET PRICE LIST

Guaranteed for 6 Months		Licensed by R.C.A.	
METAL SHIELDED TUBES			
Type	Net Price	Type	Net Price
6K7	\$.85	6H6	\$.75
GA8	.98	5Z1	.98
6J7	.85	6F6	.85
6C5	.73	6L7	.98
		Balast Unit	.65

REGULAR TUBES

Type	Net Price	Type	Net Price	Type	Net Price
00A	.56	46	.44	99X	.11
01A	.26	47	.40	99Std	.56
1V	.56	48	1.13	WD111	.56
10	.90	49	.44	WD112	.56
12A	.31	50	1.13	1A6	.56
19	.44	53	.56	166	.68
20	.44	55	.44	2A3	.56
22	.56	56	.31	2A5	.44
24A	.40	57	.40	2A6	.44
26	.26	58	.10	2B6	1.13
27	.31	59	.56	2A7	.56
30	.31	71A	.31	2B7	.56
31	.31	75	.44	5Z3	.40
32	.56	76	.31	6A1 (1a)	.56
33	.41	77	.44	6A6	.56
34	.56	78	.44	6A7	.56
37/51	.40	79	.56	6B7	.56
36	.40	80	.26	6B6	.44
37	.31	81	.30	616	.10
38	.40	82	.30	6F7	.68
39/14	.40	83	.10	6Z1 (81)	.56
40	.31	83V	.68	12A5	.90
41	.40	84	.56	12A7	.90
42	.44	85	.44	12Z3	.44
43	.41	89	.11	2Z5	.11
45	.31	99V	.11	PZII	.68

MAJESTIC TYPE TUBES

Type	Net Price	Type	Net Price	Type	Net Price
2A78	\$ 1.01	778	\$.77	358-518	\$.63
2B78	1.01	6P78	.86	558	.77
2B-48	1.19	6Y5	.86	568	.50
2Z2-G84	.83	6Z1	.58	578	.79
6A78	1.01	6Z5	.86	588	.79
6B78	.95	248	.79	6B7	.79
6C7	.86	25-258	1.22	858	.77
6D7	.79	278	.36		

SPECIAL PURPOSE TUBES

Type	Description	Net Price	Type	Description	Net Price
1B2B	Sparton type	\$.68	1B1	Raytheon type	125
1B3	Sparton type	.68	1B1	full rect.	\$ 1.13
4B4	Sparton type	.68	213	Full wave rectifier	.26
4B5	Sparton type	.68	216B	Half wave rectifier	.90
5B6	Sparton type	1.13	Neon Tuning Lamps		
401	Kellogg type	.90	(single contact)		
403	Kellogg type	1.13	Neon Tuning Lamps		
6B6	Sparton type	.68	866	Heavy Duty	1.70

CHARGER BULBS

Type	Net Price
6/10 amp trickle charger bulb (tungar type)	\$ 1.65
2 amp charger bulb with wire (tungar type)	1.80
2 amp charger bulb without wire (tungar type)	1.80
5 and 6 amp charger bulbs (tungar type)	3.75
15 amp charger bulbs (tungar type)	7.50

TELEVISION TUBES, PHOTO ELECTRIC CELLS, CRATER TUBES, CATHODE RAY TUBES

1" sq. cathode television tube	\$ 2.85
1½" sq. cathode television tube	3.85
1" sq. cathode reflectron window type 50-60 mils	2.85
Cold cathode crater tube crater size .010 to .250	5.75
Photo electric cells (potassium type) 2½" length overall 1.75	
Photo electric cells (potassium type) 4" length overall 5.90	
Photo electric cells (caesium type) 3½" length overall 3.90	
Photo electric cells (caesium type) 4½" length overall 5.90	
Photo electric cells (caesium type) 868 type	3.00

Specifications and quotations on TRANSMITTER TUBES, CRATER TUBES, GLOW LAMPS, HIGH VACUUM TYPE CATHODE RAY TUBES, suitable for television and standard oscillographic uses. SUBMITTED ON REQUEST.

ARCO TUBE COMPANY
227 Central Avenue Newark, N. J.


Please mention SHORT WAVE CRAFT when writing advertisers

World-Wide S-W Review

(Continued from page 525)

and volume possible to be realized. An unusual feature of this set is the way in which the grid-leak is connected. Instead of returning the grid-leak to the cathode circuit in the usual way, it is connected to the screen-grid, at a high positive potential.

While this gives the required positive bias to the grid circuit, for grid-detection, the bias is unusually high, even though a 5 meg. grid-leak is employed. This method of connecting the detector is an interesting wrinkle for experimentally inclined readers to try. The remainder of the circuit is quite normal, except for the group of power line jacks for 110, 150 and 220 volt lines. A 5-prong plug inserted into one of these jacks changes the circuit for that particular voltage by changing filament connections.

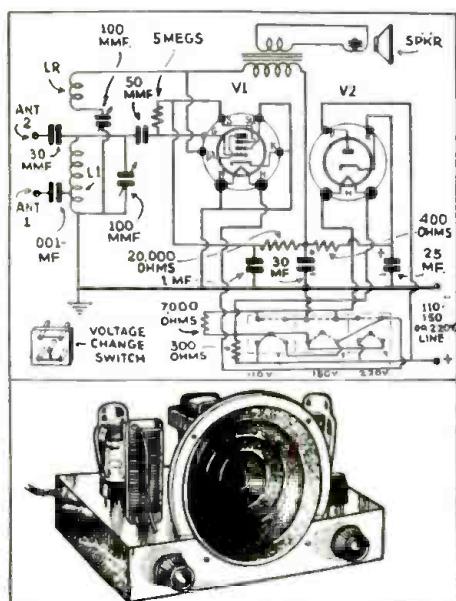

Circuit and appearance of A.C.-D.C. set.

Call Letters for Your Transmitter Panel

THE Tri-Dot metal call letters provide distinction to the appearance of your transmitter. As can be seen in the photograph, these letters are heavy, sharp-face Gothic style with a bright metal finish. The overall height is 5"; width, 10½"; width of 5 letters, 8½"; letter height, 1¾", furnished with a drilled bracket for mounting on top of transmitter. A wall model is also made, which is equipped with a chain arranged for convenient hanging. (No. 330.)




Dandy "Call Letter" sign for your panel.

Correction

Inadvertently, credit was not given to the manufacturers of the earphones shown in the photograph on Page 462 of the December issue of Short Wave Craft. This was "The Ham and Fan Band-Spread 2." These phones were the new crystal type manufactured by the Brush Development Company.

BEST BY TEST IN 5 & 10 METER EQUIPMENT

Universal 5 & 10 Meter 2 Tube Receiver

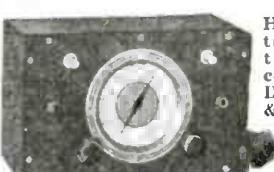

Here again Raco triumphs in introducing a complete A.C.-D.C. operated 5 & 10 meter receiver only. This extremely efficient receiver is recommended to the amateur beginner as well as the professional ham. The super regenerative circuit consists of 1-12A7 Audio & Rectifier 1-76 Detector Tubes. Due to perfect layout and circuit design absolutely no hum is encountered when listening in on the latest dope and signals.

Complete Kit of parts, not wired, less cabinet and tubes.....	7.95
Wired and Assembled.....	2.00
Crystallized Cabinet.....	1.00
Kit of 2 Matched tubes.....	1.25
Wiring diagram with each Kit.	


3 Tube (Battery Operated) Transceiver Raco Presents



This powerful portable unity coupled combination super regenerative Transceiver for the 56 to 60 m.c. This unit is capable of maintaining communication up to 100 miles depending on localities. Tubes used are 1-19 Det. and Class B Oscillator, 1-30 Amplifier, and 1-19 Class B Modulator and Output. Batteries required are 2 No. 6 dry cells and 3.45 volt battery for 12 volt O. G. meter. The result of years of experience in circuit and layout design have been incorporated in this go-getter rig.

Complete Kit of parts not wired, less cabinet, tubes and batteries.....	10.95
Wired and Assembled.....	\$3.00
Crystallized Cabinet.....	1.50
Kit of 3 Tubes.....	1.65
Wiring Diagrams with each Kit.	

All Electric 2 Tube Transceiver

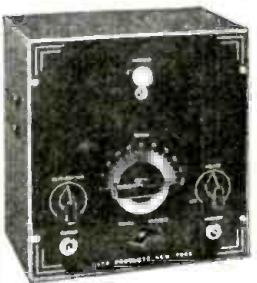


For the ham or beginner looking for a permanent installation, completely A.C. operated, we recommend this 3-in-1 balanced combination transmitter and receiver. The tubes used are 1-6A6 dual purpose and 1-80 rectifier tube. Absolutely humless when working on 5 or ten meter bands. Extremely sensitive, and extraordinary long range tuning and receiving. Range on 5 meters, 25-50 miles on 10 meters, 50-75 miles.

Complete Kit of parts (including both 5 & 10 meter coils). Not wired, less cabinet and tubes.....	8.95
Wired and Assembled.....	2.00
Black Crystallized Cabinet.....	1.50
Kit of 2 Tubes.....	1.10

RACO
PRODUCTS
136 Liberty St.
New York, N.Y.
Dept. S-1

1 Tube (No. 19 Tube) Transceiver

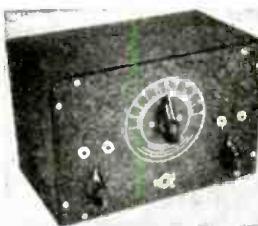

An inexpensive 1 tube 5 and 10 meter transceiver. This extremely efficient transceiver is recommended for the short-wave enthusiast who is interested in exploring the fascinating 5 & 10 meter bands. This circuit utilizes the type 19 two-volt twin tube, and is exceedingly

sensitive since the super regenerative principle is employed when the receiving position is switched on. Batteries required are two 1½ volt dry cells and 90 to 135 B supply. Tuning ranges are on 5 meters, one to 20 miles, on ten meters, 20 to 50 miles, depending on locality.

Complete Kit with 5 meter coils. Not wired, less cabinet, 10 meter coils, tubes and batteries.....	\$4.75
Shielded Crystallized Cabinet.....	.75
1-10 meter coils.....	.50
I-R. C.A.D.C. matched tube.....	.65
Wired and tested.....	.65
Wiring diagrams with each Kit.	

LEARN TO SEND AND RECEIVE CODE



Whether you want to enter radio as a career, seriously add another valuable and fascinating ability to your amateur repertoire, TELEPLEX will help you!

Learn to send and receive code signals, like operators on ships at sea and at commercial and amateur land stations. Intercept distress signals, news flashes, bulletins, and dozens of other kinds of interesting radio communications.

TELEPLEX teaches you to receive code exactly the way the world's best operators do—by sound. Copper tape, running through a machine, operates an automatic key which sends messages to you, at any speed you desire. As you improve in speed, the machine sends faster, gradually preparing you for ten-speed amateur and commercial signals. With the MASTER TELEPLEX you learn to send by sending, and the signals you send are repeated back to you, exactly as you sent them, thus enabling you to correct your own errors. We furnish a complete course, lend you the improved MASTER TELEPLEX and give you personal instruction with a MONEY BACK GUARANTEE. Send for our new TELEPLEX FOLDER SI today. IT'S FREE!

TELEPLEX CO., 76 Cortlandt St., New York

Good Results Demand Good Instruments

TRIPLETT manufactures a complete line of electrical instruments for radio, electrical and general industrial purposes both standard and custom built—for better short wave work, write for catalogue.

TRIPLETT ELECTRICAL INSTRUMENT CO.
281 Harmon Drive
Bluffton, Ohio

Model 325 Voltmeter Portable
A.C. or D.C.
TRIPLETT
Precision
ELECTRICAL INSTRUMENTS

Please mention SHORT WAVE CRAFT when writing advertisers

A.C.-D.C.-5 BAND-SWITCH— 15-550 METER—4-METAL-TUBE RECEIVER

Only RACO can give you such value. No more plug in coils. No more groping for that elusive coil socket. Easy to make, easy to tune. All band switching done by the new RACO all wave unit. Covers all broadcast, police, amateur, and foreign short wave bands. The new all metal tubes used are 2-6K7, the new metal-glass tubes used are 1-MG13 1-MG25Z5 in a perfectly symmetrical layout for high efficiency. The latest in laboratory design—switched coils—metal tubes—built in dynamic speaker—phone jack.

Complete Kit of parts. Not wired, less tubes, including dynamic speaker and crystallized cabinet.....	\$10.95
Wired and assembled.....	\$2.50
Kit of 2 All-Metal Tubes and 2 metal-glass tubes.....	\$2.35
Wiring diagram and instructions with each kit.	

RADIO CONSTRUCTORS LABS

136 Liberty St., Dept. 2-1, New York

Mail us your order for the world's most reliable and accurate Balancing or Grid Condenser

X L VARIO DENSER In 4 ranges

Mod. N. Cap. 1.2 to 20 MMF

Mod. G. Cap. 20 to 100 MMF

Mod. G5.

Cap. 100 to 500 MMF

Mod. G10.

Cap. 500 to 1000 MMF

and the

XL PUSH POST

that's spring type Binding Post

Mod. N \$1.00 ea.

Mod. G \$1.50 ea.

No Corrod. Navy Type (Brass Base Bak. Top) 28¢ ea.

Type B (Aluminum Base) Bakelite insulated Top 15¢.

Type M (All Aluminum Body) at 10¢ each.

For quick connections and positive contact at all times.

X. L. RADIO LABORATORIES

Dept. S.W.1., 1224 Belmont Ave., Chicago, USA.



YOU CAN BUILD IT AND SAVE MORE THAN 50%

Join the hundreds of DXers who have already seized this exceptional opportunity to own the most sensational communication receiver of the year—at a tremendous saving!

If you want real proof of what it has done in actual short wave contacts, listen to the W.A.C. Boys sing its praises over the air . . . and read this letter which is typical of scores that are pouring in from the four corners:

"All contacts, with very few exceptions, have been 100% on phone on the 20 meter band . . . South America, Cuba, Haiti, all on Indies, Mexico, Canada, East, West and South coasts of the U.S. have been made within the past three days. The permanent logging has been excellent, and performance has been excellent. The parallel crystal works perfectly in cutting QRM and background noise level is negligible. Have tried receiver on all bands and find it works perfectly, and with more than enough volume on all stations. Foreign broadcasts are through the roof with beautiful quality. Notice absolutely no image (repeat) signal when listening. Great, after the performance of my former receiver. Congratulations on the perfect engineering design, beautiful appearance and marvelous performance." —Charles F. Grover (W9FJ), Engineer WFDD, Police Dept., Chicago Ill.

START FOR AS LITTLE AS \$7.30! BUY THE PARTS AS YOU BUILD!

The 32-page "HOW TO BUILD IT" Book (sent for 10c) tells the whole story of this amazing 10-Tube Superhet. You can build and align it in a few hours . . . or you can buy its standard parts from your local jobber as you build, if you haven't already got many of them.

SEND 10c

(stamps or coin)

for 32-page Book

"HOW TO

BUILD IT"

Address:

R-S MERCHANTISING COMMITTEE
1711 Roscoe St., Chicago, Ill., U.S.A.

SPONSORED BY:

Billey Plesio Electric Co., Crowe Name Plate and Mfg. Co., Hammarlund Mfg. Co., Chicago Trans. & Mfg. Co., Jensen Radio Mfg. Co., Sprague Products Co., Continental Carbon Co., Ohmite Mfg. Co., General Electric, Raytheon Production Corp., Aladdin Radio Industries, Inc., Steel Box & Display Co., Filtermatic Mfg. Co., McMurdo Silver Corp.

YOUR RADIO

WITHOUT A HEADPHONE ATTACHMENT

frequently becomes a nuisance because it keeps the family and neighbors awake. You can easily correct this condition by using

CANNONBALL HEADSETS

Write for illustrated circular S-1

C. F. CANNON COMPANY
SPRINGWATER, N.Y.

INSTRUCTOGRAPH

THE PRACTICAL CODE TEACHER

To learn the code or increase speed, you want to study the most practical way. With the Instructograph, you can study more easily than at a school or by listening to Short Wave. You can practice when and where you like—regardless of schedules or interference. Book of Instructions, showing how to study to best advantage, comes with each Instructograph sold or rented. Write today for free folder and price list.

INSTRUCTOGRAPH COMPANY, Dept. SW-1
912 Lakeside Place, Chicago, Ill.

Representatives for Canada

Radio College of Canada, Ltd., 863 Bay St., Toronto



RADIO COURSES

RADIO OPERATING: Prepare for Gov't License Exam. • **RADIO SERVICING:** Including Short Wave • **AMATEUR CODE:** New Course in ELECTRONICS: Day and Evening Classes. Booklet Upon Request

NEW YORK YMCA SCHOOLS 4 W. 64th St.
N.Y. City

It's a Cinch to Try Out the New Circuits

(Continued from page 531)

course, is at the option of the builder; while the experimenter is naturally expected to use what he has on hand, experimental apparatus is usually of a high degree of perfection. In hooking up circuits, stranded wire is a nuisance, due to its becoming frayed, and I find the handiest possible wire to use is solid "push-back". So much for that part of it.

No technical drawing of connections is possible, as this would involve a specific tube, but a picture-drawing is given, along with a detailed explanation to follow, so no slip-up should occur in wiring.

The four and five six-prong sockets are marked, but the seven-prong socket bears no marking at all. But examination of the socket will show you that there are two holes in one end, larger than the rest. By turning the socket over, and locating the two terminals directly connected with these two holes, which are the HEATER connections, you will be able, by following the directions given here, to mark the other terminals so as to be able to wire it into the unit. In order to make the wiring easier, all three sockets are shown in Fig. 2. These drawings show the TOPS of the sockets—and the following explanation applies to the BOTTOMS of the sockets, as, of course, the wiring is done from the bottom.

Turning the seven-prong socket over, as above, you will "read" from left to right, or clockwise. The first terminal immediately to the left of the left heater prong is the plate, and following towards the right in immediate sequence are: Suppression grid, Control grid, Screen grid and Cathode.

There are on the five-six prong socket two unmarked terminals. One of these, to the immediate right of the plate terminal, is the screen-grid, and the other, immediately adjacent to the Grid, is the Suppressor Grid. The four-prong socket is plainly marked, and with the aid of Fig. 2, no difficulty in wiring should be met with.

Assuming that the sockets and binding posts have all been properly mounted, and the correct terminals located, the actual wiring may now be done. The first wire to be laid is the control grid cap, from the tip jack in the center to binding post number 5. This is a direct and straight connection. Binding posts 4 and 6 are connected to the filament-heater prongs, all wires in parallel. Binding post number 9 connected to the three plates. Number 2 terminates the two suppressors. Number 1, connected to the three control-grid terminals, marked "G", serves as grid connection, as well as screen-grid for 24's, 30's, etc. No. 3 is soldered to the "K" (Cathode) prongs of the two sockets bearing such markings. The pentode screens, on the six and seven-prong sockets, are connected to binding post No. 7. Number 8 may be connected to Number 3, to serve as a double connection for resistor and condenser individual connection, or to number 9, to give double connection to the plate circuits. In the event that double posts are used, and such is highly recommended, only eight in all will be necessary for this one unit.

Wiring of the coil unit is practically identical with that of the forementioned, except that three binding posts are omitted, as there is no control grid cap to be considered, nor any seven-prong sockets. Binding post No. 1 goes to one side of the heater and filament circuit, the side adjacent to its corresponding post, and the opposite side of the heater circuit goes to No. 4. No. 2 is connected to the grid terminals, and the suppressor grid terminal of the five-six-prong socket, which is the terminal immediately adjacent to the grid prong, is also connected to this post. Post No. 3 goes to "K" on the five-prong socket; post No. 5 to the two plate terminals; and No. 6 connects with the screen-grid terminal. Double posts here would be especially beneficial. You now have two units which, with a few

MOTOR DRIVEN Craftsman Tools

COMPLETE—READY TO RUN

ELECTRIC HANDY-LATHE

PRICE

\$757

Ship. weight
10 lbs.

WITH BUILT-IN MOTOR

Length of Bed, 15 inches; height to spindle, 2 inches, is supplied with face plate as well as spur center for handling all types of work. This lathe is furnished with a built-in Induction Motor, mounted on the head-stock, so that the drive wheel acts directly on the three-speed pulley. NO BELT REQUIRED. In shifting to the various speeds it is only necessary to lift the motor with the left hand and slide it forward or back as desired. A finger-tip switch is located conveniently on top of the motor. Finished in gray and green enamel and comes complete with motor, cord and plug cap, and special wrench. Operates on alternating current only, 110 volts, 60 cycles.

ELECTRIC GRINDER

PRICE

\$349

Ship. weight
4 lbs.

Comes supplied with 2 genuine Aloxite grinding wheels, one coarse grinder, and one fine grinder. It is driven with a dependable induction type high speed inner fan cooled motor with the grinding wheels mounted at opposite ends of the motor shaft. This motor does not interfere with radio reception, and has a heavy ground steel shaft and large bronze bearings, having thick felt oil-retaining washers behind them, constantly lubricating the shaft and bearings and provided with oil holes for re-oiling. Complete with cord and plug cap. Operates on alternating current only, 110 volts, 60 cycles.

ELECTRIC SCROLL AND JIG SAW

PRICE

\$469

Ship. weight 10
lbs.

This is an entirely new type of saw, powered by a fan-cooled, induction motor geared directly to a saw blade for maximum power.

Blade stroke $\frac{3}{4}$ ". Made of channelled steel, has 12" throat that handles work up to 24" long, $\frac{6}{5}$ " round work table, adjustable hold down shoe with guide roller to support and steady saw blade. Cord, plug and 1 blade included. Built-in motor operates on alternating current only, 110 volts, 60 cycles.

Our Old Customers Know That
Our Merchandise Is Sold on a
Strict Money-Back Guarantee

All Shipments will be forwarded by Express
Collect if not sufficient postage included
with your order.

WELLWORTH TRADING CO.
506 Palmolive Bldg., Dept. S. W. 136, Chicago, Ill.

fixed condensers and resistors, a tuning condenser or two, scrap panels and a couple of potentiometers, along with some good wire, will enable you to experiment with any R.F. or A.F. amplifier, detector, wavemeter, frequency meter or rectifier making use of, either singly or in combination, any coil, condenser or tube. All of the technical points of construction of the actual units have been given due consideration, and I believe I have made everything clear. The business-like appearance of the aluminum shelves as shown in the photos may be duplicated by yourself, or do as I did—turn it over to the wife. Due credit should here be given to her for her good work with a pencil eraser, in giving it the much desired "whorl", or chased, effect, and with a scribe in scratching in the "V". The whole unit, minus the sockets, was given a coat of clear lacquer, to prevent marring and fingerprinting.

You will find in Fig 4 the circuits of two "time-tried and true" one-tube receiving sets. The numbers of the binding posts are given on coils, and tubes, and the values of external parts are marked, so no confusion will arise. These two sets will give you an idea as to how the unit is used.

Parts List

- 1 Piece Aluminum 4 $\frac{3}{4}$ x 9.
- 1 piece Aluminum 6 $\frac{1}{2}$ x 3 $\frac{1}{2}$.
- 1 piece Bakelite 1 x 6.
- 1 piece Bakelite 1 x 3 $\frac{1}{2}$.
- 15 Old style Metal Binding Posts.
- 2 UX (four-prong) Sockets.
- 2 "Universal" 5-6 prong Sockets.
- 1 "Universal" Short and Long Prong Socket.
- 1 Insulated Tip Jack for Grid Cap Lead.
- Mounting Screws, Wire, etc.

Talking On One-Half Meter

(Continued from page 527)

to the oscillator. The plate current of the oscillator should not be allowed to exceed 5 milliamperes. Remember these 955 Acorn tubes are not 210's! Don't try to light flashlight bulbs with the output. When the antenna is connected to the oscillator there should be only the slightest sign of increase in the plate current. If the coupling is too close, the tube will stop oscillating and the plate current will rise to a value far too high and the plate of the tube will become red hot. This condition should be carefully avoided!

Antenna Details

The antenna used in experiments was a single wire as shown in the photo; this proved to work very fine. The feeder was a single wire tapped on to the antenna slightly "off center"; for complete details see the antenna table. Probably the most interesting part of this ultra short-wave business is the antenna. Many types of directional antennas may be used. With a sharply concentrated beam antenna, this transmitter and receiver covered distances up to over one-half mile. And under favorable conditions communication probably could be held over even greater distances. For best results the receiving and transmitting antennas should be identical.

This apparatus has been operated successfully and affords an opportunity for the experimenter to build and operate a really practical transmitter and receiver operating between one-half and one meter.

Antenna Data

Antenna length	Tapped off center
1 meter, 20 inches	2.8 inches
3/4 meter, 15 inches	2.1 inches
1/2 meter, 10 inches	1.4 inches

New Sets for the S-W "Fan."

In the next and following issues new receivers for general S-W "broadcast" reception will be described, with full "constructional" details.

FOR BETTER RADIO
use

Hammarlund
I.F. TRANSFORMERS
AIR-TUNED • VARIABLE COUPLING



1 CONTINUOUS VARIATION
OF BAND WIDTH — EXTREME
SELECTIVITY TO HIGH
FIDELITY

2 PANEL OR INDIVIDUAL
CONTROL — POSITIVE
COIL SPRING ACTION

3 IMPREGNATED THREE PIE
LITZ COILS - ISOLANTITE
CORES — HIGH GAIN

4 FOR ANY I.F. AMPLIFIER
WITH SCREEN GRID TUBES —
175 AND 465 KC TYPES

5 ONLY 2" x 2" x 5"

6 GUARANTEED STABILITY

For Better Radio
Hammarlund
PRECISION
PRODUCTS

Write Dept. SW-1 for FREE NEW
CATALOG of Condensers, Transformers,
Chokes, Sockets, Coils and technical data
on receiving and transmitting equipment.

Attach 10¢ for New 32-page Manual of
most popular Short-Wave Receivers, with
illustrations, diagrams and parts lists.

Hammarlund Manufacturing Co.
424-438 W. 33rd St., New York

Attention-

Amateurs and Radio Experimenters!

At last the dream of thousands has been realized. W.2-C.V.E. Experimental Laboratory is introducing to the radio amateur fraternity a new plug-in coil known as the *Uno All-Wave Coil*.

This unit alone will take the place of all the necessary coils required to cover the entire amateur bands. No switches, no soldering, and no alteration to your present receiver is required to adapt this unit. It is plugged-in, in the ordinary way, and by turning the dial it is equipped with, you are ready to tune in, any particular frequency required. The *Uno All-Wave Coil* will permit you to monitor your signals, or to work duplex, by listening in to the second harmonic of your transmission; it will also enable you to listen in to commercial stations and broadcasting abroad. All the tuning is done with your own tuning condenser in your set, while the unit will furnish the frequency required for each set of the tuning knob.

It is also provided with padding condensers to make up for any minor off-tolerance from time to time, and is available with 4, 5, or 6 prongs. It has many advantages over the ordinary plug-in coils now on the market, for economy and efficiency, and above all is available for Super-het with 465 K.C. intermediate, also for all-wave sets covering continuous frequency from 15,000 to 550 K.C. List Price.....

Watch following issues for list of distributing houses.

UNO ALL-WAVE COIL CO.

Dept. S-1

Roosevelt, N.Y., U.S.A.



**IDEAL! THE FIRST FULLY
SEALED AND
INSULATED RESISTORS**

IRC INSULATED Resistors bring you EVERY advantage of the famous Metallized resistance principle PLUS full, high voltage insulation. No danger of shorts or opens. Smaller—lighter—vibration-proof—moisture-proof—BOTH color coded AND marked with range and value. Featured by leading jobbers.

International Resistance Co.
Philadelphia, Pa. — Toronto, Canada

Metalized IRC INSULATED

OIL
MICA
PAPER
ELECTROLYTIC
THE BEST CONDENSERS
MONEY CAN BUY

Write for general catalog No. 128
on complete line today.

CORNELL-DUBILIER
CORPORATION
4376 BRONX BOULEVARD
NEW YORK

*The cream
of Radio Books*

Principles of Radio

By KEITH HENNEY

Considered "the best combination of theory and application for all radio experimenters that has yet appeared."

Second Edition, \$3.50

Short Wave Wireless Communication

By A. W. LADNER and C. R. STONER

A self-contained treatise, not restricted to short waves alone, but including wherever necessary principles common both to short and long waves.

Second Edition, \$3.75

Elements of Radio Communication

By the late JOHN H. MORECROFT

"The whole story of radio, simply as well as accurately treated."

Second Edition, \$3.00

ON APPROVAL COUPON

John Wiley & Sons, Inc.
440 Fourth Ave., New York City

Kindly send me the following books. I agree to return their price within 10 days after their receipt or return the books postpaid.

Henney Ladner-Stoner Morecroft

Name _____

Address _____

Employed by _____ SWC-36

The SENSATION of the Short Wave Field the 1936 SUPER

SKYRIDER

- All Metal Tubes
- Iron Core I.F.'s
- Controlled Crystal Filter
- Duo - Micro Band Spread



WRITE FOR FULL DETAILS

the Hallicrafters
3001-U Southport Ave., Chicago

DON'T READ THIS IF YOU ARE A MILLIONAIRE

HUNDREDS OF AMATEURS AND SHORT WAVE LISTENERS ARE PURCHASING ON OUR

EASY PAYMENT PLAN

WE ARE MAKING IMMEDIATE DELIVERY ON

NATIONAL—HAMMARLUND
PATTERSON—RCA—BRETING
SKYRIDER—RME—SILVER

AND OTHER CUSTOM BUILT RECEIVERS

DOWN PAYMENTS AS LOW AS \$15.00

SEND 5c FOR COMPLETE DETAILS

DELAWARE RADIO SALES CO.

403 DELAWARE AVE., WILMINGTON, DEL.

ATTN.: WILLARD WILSON-W3DQ EST. 1920

Be a TELEVISION EXPERT

LEARN TELEVISION WITH RADIO NOW!

Here's opportunity! Get ready for the best paid jobs in Radio as Television sweeps the country. Train at big-time broadcasting stations. Get actual experience over our "Television Station W9XAL and commercial station W9XB1". Write today for free folder and literature showing actual photos of Television broadcasting opportunities, etc.

FIRST NATIONAL TELEVISION, INC.
Dept. B-1, Power & Light Bldg., Kansas City, Mo.

How Waves Are Propagated

(Continued from page 520)

used, the multiple-dipole transmits equally well along an axis at right angles to the point of the array, i.e., it transmits in front of and behind the array, as shown by the full line and dotted arrows in Fig. 4.

Fig. 5 shows one of the simplest reflector-antenna arrays which utilizes one aerial wire or rod and one similar size reflector rod, space one-fourth wavelength behind it. The radiation is shown for this simple reflector type. Fig. 6 shows how greater directional activity is obtained by using an aerial array of four wires or rods, using a reflector system spaced one-fourth wavelength behind it. The individual rods or wires comprising the antenna are spaced one-half wavelength apart, as shown in the diagram. As the wave pattern in Fig. 6 shows, most of the energy is concentrated in the elongated lobe and only a small fraction of the total energy radiated from this highly directive antenna is wasted in the four auxiliary lobes, as shown. By using various arrangements of the aerial and reflector arrays, and by suitably phasing or staggering the phased relation of the currents in the antennas and the reflectors also, or by spacing them in suitably spaced groups, as shown in a paper prepared by G. C. Southworth of the American Telephone & Telegraph Co., the predominating lobe or directive wave pattern may be caused to become much sharper. In other words, by using this principle, antenna patterns can be arranged so that the wave may be sharply beamed or directed toward Europe, etc.

Fig. 7 shows one form of directive aerial in which a doublet is placed at the focus of a parabolic reflector made from a series of wires or rods held in an insulated frame made in the shape of a parabola. The direction of the concentrated beam or wave is indicated in Fig. 7.

The inverted "L" aerial and the peculiar vertical wave pattern around a transmitting aerial of this type are shown in Fig. 8.

It should be mentioned at this point, perhaps, that very little of the wave energy penetrates into the ground and the more conducting the ground happens to be, the more it acts like a true reflector. The horizontal radiation pattern for the inverted "L" aerial is also shown in Fig. 8.

(To be concluded)

Noise-Reducing Aerial

(Continued from page 533)

tenna System here illustrated the switch serves to throw into the circuit, in the same way that a wave change switch on a short-wave receiver would do, another section of the set transformer which is matched for short waves.


The length of transmission line between the antenna transformer and the set transformer is not critical and can be extended up to 300 feet without loss of efficiency and without noise pick-up.

The antenna should be as high as possible. If it is feasible to run the antenna from the end of the building out to a pole or tree beyond, such an arrangement would be more desirable than having the antenna run over the roof of the building, because of the greater effective height. The full length of the antenna should be employed whenever possible, and best reception in all cases will result. If the distance between the two supports is greater than 60 feet, the 60-foot antenna should be used with insulators at each end and a length of regular antenna wire or guy wire employed to make up the additional distance required. In no case should either the 17-foot section or the 43-foot section be increased in length. If it is impossible to install the entire 60 feet of antenna, the reduction in length should be made from the 43-foot section and not the 17-foot section.

Best reception is obtained when the lead-in does not exceed 150 feet.

DATA PRINTS

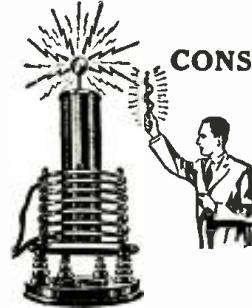Just the CONSTRUCTION Information You Need To Build Electrical Apparatus



TESLA OR OUDIN COILS

Dataprint containing data for constructing this 3 ft. spark Oudin-Tesla coil. Requires 1 K.W. 20,000 volt transformer as "exciter"; see list below. Includes condenser data. \$.75

8 inch spark, data for building, including condenser data; requires 1/2 K. W. 15,000 volt transformer; see list below. \$.50

Violetta type, high frequency coil data: 110 volt A.C. or D.C. type; 1" spark; used for "violet ray" treatments and "Experiments". \$.50

How to operate Oudin coil from a vacuum tube oscillator. \$.50

3 inch spark Tesla coil; operates on Ford ignition coil; 110 volt A.C. "Kick-Coll". \$.50

3 inch spark Oudin coil; 110 volt A.C. "Kick-Coll". \$.50

20 Tricks with Tools and Oudin Coils. \$.50

TRANSFORMER DATA

1 k.w. 20,000-volt transformer data, 110-volt, 60-cycle primary. Suitable for operating 3 ft. Oudin coil. \$.50

1/2 k.w. 15,000-volt transformer data, 110-volt, 60-cycle primary. Suitable for operating 8-inch Oudin coil. \$.50

Electric Welding Transf. (2 K.W. 110 Vt. Prim. 18 Vt. Sec. Other Sec. Vt. data given). \$.50

Induction Coils—1 to 12 inch spark data. \$.50

ARTIFICIAL FEVER APPARATUS. \$.75

(Low, Medium & High Power Data Given)



SLIDE RULE

MIDGET

Metal 4" Dia.

Price \$1.50.

Case 50c extra

This rule solves any problem in multiplication, division, addition, subtraction, and proportion; it also gives roots and powers of numbers, sines, cosines, tangents and cotangents of all angles; also logs of numbers. Adds and subtracts fractions. Approved by colleges.

10" Dia. 27" Scale "Special" Rule. \$2.75.

Multiplication and Division, but has no "Trig" Scales.

TELEGRAPHONE — Records Voice or "Code" signals on steel wire by magnetism. Code can be recorded "fast" and translated "slow." Construction data (special)	\$.50
---	--------

MAGNET COIL DATA

Powerful battery electro-magnet; lifts 46 lbs... \$.50

110 Volt D.C. magnet to lift 25 lbs. \$.50

110 Volt D.C. 300 lb. Lift electromagnet. \$.50

110 Volt D.C. solenoid; lifts 2 lb. through 1 in. \$.50

110 Volt D.C. solenoid; lifts 6 lb. through 1 in. \$.50

12 Volt D.C. solenoid, lifts 2 lb. through 1 in. \$.50

A.C. Solenoid, powerful. 110-volt, 60-cycle. \$.50

MOTOR—1/16 H.P., 110 volt A.C., 60 cycle (suitable for driving 12" fan, etc.)—Data. \$.50

60 or 1,200 cycle Synchronous motor Data. \$.50

MISCELLANEOUS DATAPRINTS

Electric Furnace Regulator. \$.50

Treasure Locator. \$.50

Water Turbines. \$.50

20 motor circuits—book-ups. \$.35

20 practical telephone hook-ups. \$.35

100 mechanical movements for inventors. \$.50

Polarized Relay—Ultra Sensitive. \$.50

Electro-medical coil (shocking coil). \$.50

Water-Wheels—How to Build and Light your house. \$.50

20 Electric Bell circuits. \$.50

Public Address System. \$.50

Electric chime ringer; fits any clock. \$.50

20 "Electrical Tricks" for LODGES and PARTIES \$.50

How to Fry Eggs on Cake of Ice Electrically.. \$.50

"Rewinding" Small Motor Armatures. \$.50

"ENGINEERING SERVICE BY MAIL"

(20% off on orders for \$3.00 or more. No C.O.D.)

The DATAPRINT COMPANY

Box 322 RAMSEY, N. J.

Please mention SHORT WAVE CRAFT when writing advertisers

Solar Phenomena and Their Effects on S-W's

(Continued from page 519)


been seen on the sun. This may account for the fact that invisible sunspots and activity surrounding them may be causing the strong terrestrial effect, the spots themselves being hidden underneath clouds of hydrogen and calcium gases, which in themselves are also a manifestation of solar activity. These clouds are called flocculi, and some of them are prominent in an eruptive state. During periods when disturbed radio conditions obtained and where it was possible to observe the sun through a device called the spectrohelioscope, these flocculi were always in evidence.

The sunspots move across the surface of the sun by virtue of its rotation, as pointed out by Mr. Richey, and in some of his research work, as well as that made by many astronomers, successive photos have been taken, showing the movement of a spot or a group of spots across the surface of the sun as it rotates. As mentioned previously, a strong sunspot disturbance, which resembles a veritable whirlpool of incandescent gases in the sun's surface, causes streamers to be shot forth from the sun in the region surrounding these sunspots, some of the streamers extending more than a million miles in length, as recorded by the camera. These streamers can be likened to the jets of water caused by a revolving lawn spray, and it will be seen that as the sun rotates, and providing the streamers are pointed at the right angle to intercept the earth, the earth will be swept by one of these streamers and the speed of the sun's rotation is such that the streamer, would sweep across the earth's disc in about thirty seconds.

Sunspots, in many cases, last for only a day or two, but every once in a while one will persist as long as two hundred days. In one case, in 1840-41, one lasted eighteen months. To see a sunspot with the naked eye, it must measure approximately thirty thousand miles across, and the largest sunspot ever recorded, measured one hundred and fifty thousand miles in breadth. The birth of a sunspot is generally preceded and accompanied by eruptive prominences composed mostly of sheets of hydrogen and calcium flames, extending up to high altitudes, ranging from a few thousand to millions of miles. These activities apparently give rise to streams of electrified gas particles which are shot off from the sunspot region and are expelled or driven away from the sun by the pressure of light radiation. Calculations and observations of the commencement of magnetic storms with the incidence of the passage of spots across a vertical line in the center at the sun show that these streams of electrified particles may reach an average velocity of about one thousand miles per second. In other words, in about twenty-six hours such a stream of particles could traverse the ninety-three million miles, separating the earth and sun.

So far as the effect of the sunspots on short-wave transmission is concerned, these seem to recur on about a twenty-seven-day cycle. Recently solar activity of this nature has been noticed to be on the increase. The effect or presence of severe magnetic storms on the earth have been noted for many years, and the conclusion that practically all magnetic storms are caused by some change in solar activity or the presence of sunspots has been believed for some time. Even though the spot or spots are not always visible, due to being hidden under clouds of incandescent gases, still the effect and relation between them and magnetic storms, is quite positive and measurable.

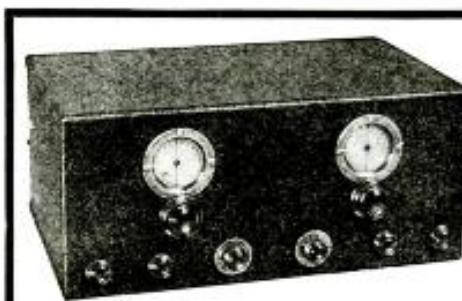With regard to the effect of streams of electrified particles radiated by the sun, and in addition to its effect on the earth's magnetic field as it sweeps across the earth, it also appears to increase the ionization of the "E" layer in the ionosphere and decreases the ionization in the "F" layers. It apparently raises the temperature of the gases at great heights, which increases the



**Sargent Model 20
9 Tube Receiver**

- One Stage Pre-Selection
- A.V.C. and Manual Volume Control
- Continuous Band Spread, Calibrated for Amateur Bands
- Coil Switching—No Plug-in Coils
- Built-in, Hum-free Power Supply
- Headphone Jack
- Excellent Broadcast Band Reception
- Ideal for Shipboard Work
- Razor-edge Selectivity
- Fractional Microvolt Sensitivity
- Outperforms Receivers selling for 3 times its price.

Radio Operators, Amateurs — Look at This One!

15 to 1500 Meters Not a "Skip Band" Receiver

MARINE TUNING RANGE

A true communication-type super-het that covers all of the wavelengths that you really want. Has all of the popular short wave features such as band spread, local oscillator, etc., that are absolutely necessary to efficient short wave reception. In addition it covers the ship telegraph wavelengths as they should be covered. The 5th tuning band of the receiver, 510 to 1500 meters, is peaked near 600 meters, giving the highest efficiency possible. This receiver also covers the 800 meter compass wave and the airplane beacons from 900 to 1500 meters.

Due to special design of our coil unit, this extension of wave coverage is obtained without any reduced efficiency at short waves, and if we were to design the set for short waves only, we could not improve it. For those not wanting the ship telegraph wavelengths, this same receiver is also put out with a tuning range of 15-550 meters.

Model 20 prices given below include an 8" Jensen speaker unit and a complete set of tubes. For speaker cabinet, finished to match receiver add \$3.25 net to these prices.

This will be the outstanding receiver of the 1936 season. ORDER YOURS TODAY.

Amateur Net Prices

Prices Include Tubes

Model 20-MA, 15-1500 Meters, complete,	\$67.50
less speaker cabinet	

Model 20-SA, 15-550 Meters, complete,	\$59.50
less speaker cabinet	

IMMEDIATE DELIVERY

E. M. SARGENT CO.

212 Ninth St. Dept. S Oakland, Calif.

Good News!

Your order for the Patterson PR-16 shipped promptly \$95.70 complete or with crystal filter \$101.70. Shipped prepaid on ten day trial. You need send but \$5 with order. Write for full information.

IN STOCK too:

SUPER-SEVENS complete prepaid	\$ 49.50
METAL TUBE SUPER SKYRIDERS complete prepaid	79.50
SILVER 5Ds complete prepaid	109.80
BRETIG 12s complete prepaid	93.00
RCA ACR-136s complete	69.50
RME-69s	118.80
HROS	167.70

All receivers shipped on ten day trial. You can trade in your receiver or buy on time payments.

HENRY RADIO SHOP

211-215 North Main St. Butler, Missouri

You cannot make a better investment than to have in your home a GOLD SHIELD PROFESSIONAL MODEL Carbon Sun Lamp SAVES DOCTOR'S BILLS Everyone in your family needs the health giving VIOLET RAYS. This is a large CHROMIUM plated lamp with a carbon bulb emitting rays of ultra violet and infra red. If SUN TAN is desired, order accordingly CURES COLDS, RHEUMATISM AND MANY OTHER AILMENTS.

Complete with screen and google. \$5.50

WONDERFUL VALUE!
GOLD SHIELD PRODUCTS CO.,
17 W. 60th St. N. Y. City

Size 18" high, 7" wide, 5" deep.
Weight 12 pounds.

SEND FOR THE LATEST

and complete authorized information on testing the new Octal Metal tube, the new Octal analyzer plug with Dial grid cap and 9 wire cable, and socket and associate adapters, the new Octal sockets, the new Octal grid caps, etc.

NOW the new "Tuning Fork" clip is available in every type of socket including the new Octal types. Life tests are now approaching 2,000,000 perfect contacts without failure.

ALDEN PRODUCTS CO.
Dept. SW-1 715 Centre St.
BROCKTON, MASS.

BLAN CLASSIS

Have you noticed BLAN equipment mentioned in various radio magazine articles lately? Most of the leading authors and research engineers use BLAN parts, because BLAN is dependable and can furnish anything from a setscrew to a speaker.

BLAN THE RADIO MAN
175 GREENWICH ST. NEW YORK, N.Y.

BUD TUNING DIALS

For EVERY Amateur Purpose



A large moulded bakelite fluted knob with skirt mounted on a nickel silver dial plate with circular finish. Numerals and divisions etched in black enamel. Made in clockwise and counter clockwise rotation.

No. 711—1 3/4" Dia. 0-100 in 180° Price \$1.00
No. 712—1 3/4" Dia. 100-0 in 180° Price \$1.00
No. 713—2 3/8" Dia. 0-100 in 180° Price \$1.25
No. 714—2 3/8" Dia. 100-0 in 180° Price \$1.25
No. 715—4" Dia. 0-100 in 180° Price \$1.75
No. 716—4" Dia. 100-0 in 180° Price \$1.75

40% DISCOUNT TO AMATEURS

NEW 1936 Catalog describing numerous new items for the amateur sent to you upon receipt of 3c postage stamp.

BUD RADIO, Inc.

1937 E. 55th St., Cleveland, Ohio

Brush Type A'Phones

meet every headphone requirement. Response 60 to 10,000 cycles. Brush phones operate from any normal source . . . give greater volume from weak signals. No magnets to cause diaphragm chatter. Will handle excessive volume without overloading. Specially designed cases minimize breakage. Weight . . . 6 ounces. Now available at the new low price . . . only \$9.00 plus postage.

Data Sheet No. 10 gives full headphone information and circuit diagrams. Free on request. Send for your copy today.

BRUSH
PHOTO ELECTRIC DEVELOPMENT COMPANY CLEVELAND, O.

HEADPHONES • MIKE STANDS • TWISTERS • HEAD PHONES • LOUD SPEAKERS

ELECTRICAL BOOKS
shipped
FREE

A-C-RADIO
TELEVISION
EVERY ELECTRICAL SUBJECT COVERED

10 BIG BOOKS

Here's great news for anybody interested in Electricity. BRAND NEW 10 volume set of Applied Electricity brought right down to date with every NEW Electrical subject fully covered in big volumes and all shipped FREE for examination. See special offer below.

For
Beginners
and Experts

Over 3000 pages—
hundreds of illustrations—the most complete work of its kind ever published. Dynamos, motors, power stations, radios, television, everything electrical explained clearly so anyone can understand them.

BIG FIELD! Big Demand!

Big Pay! Men who understand electricity are urgently needed right now in thousands of industries. Autos, airplanes, machine shops—practically every industry depends on electricity and men who know this subject make big money. Pleasant, fascinating work, easy to learn and do. Send coupon for a set of these books for FREE examination.

FREE [S. Geraback's famous Radio Encyclopedia (latest edition) given free with these electrical books if you send NOW. Available in any Radio work. Covers whole Radio field.]

American Technical Society, Drexel at 58th St., Dept. E 145, Chicago

Send for 10 days free use, BRAND NEW 10 volume set of Electrical Engineering. Include free membership in the American Technical Society and S. Geraback's Encyclopedia. I will pay the few cents delivery charge on the books. If I wish I may return them in 10 days and owe you nothing, but if I keep them I will send \$2.00 after 10 days, then \$3.00 a month until the special price of only \$29.50 is paid.

Name.....

Address.....

City.....State.....

Attach letter stating age, occupation and name and address of employer and at least one business man as reference.

Newark's ★★ Program

Deferred Payment plan on all Short-Wave sets. Write for Catalog No. 101.

★ ★ ★ THORDARSON No. T6878 Plate and Fil. Transformer. 600-0-600 V. at 200 M. A. 2½ V. at 10 amp., 5 V. at 3 amp., 7½ V. at 3 amp. \$2.45

★ ★ ★ THORDARSON No. T6877 Heavy Duty choke, 15 henries at 250 M. A. \$1.95

★ ★ ★ THORDARSON No. T1998B Choke, 18 henries at 200 M. A. 190 Ohms —2200 Volt insulation \$1.25

★ ★ ★ NEWARK Oil filled—Oil impregnated Filter Condensers.


2 mfd. 2000 V. DC	\$1.50
4 mfd. 2000 V. DC	\$2.25
8 mfd. 2000 V. DC	\$2.75
9 mfd. 3000 V. DC	\$7.25

★ ★ ★ NEW LOW PRICES ON RCA TUBES 852 \$16.40 866 \$2.25

NEWARK ELECTRIC COMPANY
“Faster Service—Better Bargains”
226 W. Madison St. Dept. S., Chicago, Ill.

A NEW BOOK—Second Edition of FUNDAMENTALS OF RADIO

(426 pages 6"x9", 430 figures)

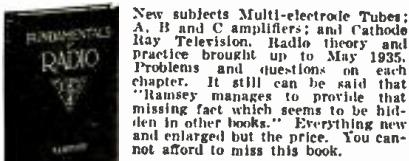By Professor R. R. RAMSEY, Ind. Univ.
Revised, enlarged, repaged, reprinted, New cover.**EXPERIMENTAL RADIO**

By the same author. You have heard of the original radio manual of experiments. Get it. Price: Fundamentals \$3.50; Experimental \$2.75 post paid.

Your check, postal order or C.O.D. brings 'em
RAMSEY PUBLISHING CO. Bloomington, Indiana

Low Prices On Short Wave Parts

4-prong S.W. Coils 12 to 180 meters, 4 coils to set.....	\$.98
6-prong S.W. Coils 12 to 180 meters, 6 coils to set.....	1.18
2½ m. h. R. F. Chokes, 4 ples wound on ceramic mica film forms.....	.25
Plot 30 hys. 45 mfa. bakelite cased filter chokes.....	.49
1 P. P. input for 1.0. Output 47 case filter each.....	.45
Giant View Power Transistor, 1000 m.a. 100 v.w. Guaranteed.....	1.00
5 mfd. Elec condenser-cardboard 450 V.W. Guaranteed.....	.25

Write for bargain bulletin. Distributors of all nationally known radio parts and test equipment for amateur and servicemen. No order too small to ship. We ship to all parts of the world.

M. SCHWARTZ & SON
710-712 Broadway Schenectady, N. Y.

collision frequency and serves to reduce the ionic density. Layer height measurements point to great turbulence existing at these heights. The increase in the ionization of the "E" layer apparently increases the daylight intensity of the long waves, while the general turbulence and reduced ionization, together with increased collisions in the "F" layers, probably explains the increase in attenuation of the short waves, as pointed out by Mr. Richey.

One of the most interesting and valuable observations about sunspot activity is that they occur in fairly regular cycles, the average cycle being 11.13 years, sunspot activity obtaining its maximum at this period, after which it slowly declines for a little more than five years, then slowly works back toward its maximum. Since 1788, the interval between the major maxima has varied from 7.3 to 17.1 years. Sometimes, for periods as long as two hundred days, no sunspots will be observed, but at other times, there may be whole years during which the sun is never without them. The maximum number of sunspots, observed per day, under the same conditions, may vary from twenty-five to fifty, or more, depending upon the magnifying properties of the observing instrument.

Other phenomena have been observed which show a close connection with the occurrence of severe magnetic storms and high sunspot activity. Two interesting correlating phenomena are the occurrence of polar aurora and large electric currents oscillating back and forth in the earth's crust.

So important is the effect of sunspot activity on short-wave transmission, that the engineers of the Bell Telephone Laboratories have made a special study of these effects and also have an instrument known as a Spectrohelioscope located at Deal, N.J., for making observations of the sun. These observations, plus a careful study of past records of sunspot and magnetic storm activity, make it possible to predict possible future occurrences of such disturbances. While not much can be done about a really violent storm, steps can often be taken to minimize their effect. The origin of the majority of the disturbances causing a change in the normal behavior of terrestrial magnetism and radio transmission, therefore, lies in the sun and sunspot activity, and not in some cosmic agency affecting simultaneously both the sun and the earth. This is borne out by the fact that so many disturbances have occurred on a synodic rotation period (a rotation period as seen from the earth) and not a sidereal period (a period of rotation as would be seen from a fixed point in space) of the sun.

New Line Filter

(Continued from page 533)

covered cord and terminal plug coming out of the filter, is placed in the 110-volt A.C. supply. The cord from the set is coiled up and tied with a piece of twine, and this acts as an extra choke in the circuit.

The filter can be installed in a few minutes by anyone, and complete instructions and simple hook-up diagram come with it. A ground clip on the Lynch Filteradio is connected to the ground post of the receiving set, or to any convenient part of the chassis, by means of a short piece of wire. At the same time, another piece of wire is run from the ground post on the set to a water pipe or other good ground. The receiver is turned on and a program tuned in, keeping the volume well down. Then the line balancer is adjusted to a spot where the least interference noise is found. Changing from one station to another, or even shifting from one band to another, should have no effect on the setting of the line balancer.

The improvement produced by the use of the device can be checked by switching an electric light on and off rapidly, with the device first in the circuit, and then cut out. In some cases, a further improvement may be noted by reversing the attachment plug from the receiver where it is plugged into the filter.

Why gamble?—

INVEST in a genuine

DOERLE

**2-TUBE BATTERY RECEIVER**

15 to 200 Meters

One of the most popular members of the Doerle Set family. Employs but two tubes, yet gives the performance of a set having three tubes. Uses a type 30 as regenerative detector and a type 19 twin triode (actually 2 tubes in one) as two stages of resistance-coupled audio. The world-famous reputation of the entire Doerle line, is behind this remarkable set. Requires two No. 6 dry cells and two 45 volt "B" batteries for operation. All parts and workmanship fully guaranteed. Employs a set of four 5-prong ribbed plug-in coils. These coils are interchangeable with the new 5-prong bandspread coils. Ship. wt., 10 lbs. List Price \$15.75.

\$7.66
KIT
Less Tubes, Cabinet, and Batteries

No. 5009-K Doerle 2-tube Battery Receiver Kit, not wired, but including Coils, less Tubes, Batteries and cabinet. YOUR PRICE \$7.66

Set of 2 Matched Tubes.....\$1.00
Metal Cabinet for above90
Set of 4 Bandspread Coils.....2.35

No. 5006-K Doerle 3-tube Battery Receiver Kit, no wires, but with 4 Coils and Metal Cabinet, less Tubes and Batteries. Ship. wt., 10 lbs. List Price \$23.75
YOUR PRICE \$12.46

Set of 3 Matched Tubes.....\$1.80

We will wire and test any of these kits at an additional charge of \$1.50.

125 to 1 Bandspread Dial for the 3-tube set \$1.75 extra

RADIO TRADING CO.
101-A Hudson St. N. Y. C.

STOPPANI COMPASS

A Precision Instrument made in Belgium. Purchased by the U. S. Government at more than \$30.00 each. Ideal for Radio Experimenters Laboratory, also may be used as a Galvanometer for detecting electric currents in radio circuits. Ruby, jeweled, solid bronze. 4 inches square, fitted in a hardwood case. Also used by hunters and surveyors. Our price prepaid \$4.50 each

Gold Shield Products Co., 17 West 60th St., N. Y. City

Radio Amateur Course

(Continued from page 537)

of the coil which is not connected to the plate. The condenser "NC," which is the neutralizing condenser, is then adjusted to feed an amount of R.F. from the plate circuit back to the grid, equal to the amount of R.F. fed from grid to plate, due to the internal capacity of the tube. This external feed-back method of feeding back R.F. 180 degrees out of phase, cancels the plate-to-grid feed-back within the tube.

Push-Pull With Triodes

In figure 4-B, we have *push-pull* amplification, using triodes, each operating 180 degrees out of phase, making neutralizing possible by just connecting small, variable condensers between the plate of one tube and the grid of the other. In other words, one tube furnishes the neutralizing voltage for the other.

In Figures 5-A and 5-B, we have R.F. amplifiers using screen grid tubes which require no neutralizing. One is a *push-pull* circuit, and the other is a *single-ended* affair. As we said before, in Class "B" and "C" amplifiers, both audio and radio frequency grid current flows during either a portion or all the positive half-cycle of the exciting voltage. Now, this grid current can be utilized for biasing R.F. amplifiers by inserting a resistor in series with the grid return, the same as we have in an oscillator where bias is obtained with a grid leak. We can also obtain bias by the cathode method as shown in Figure 5-B. Grid-leak bias is never used in audio frequency, Class "B" amplifiers. Screen-grid voltage in amplifiers, such as shown in Figures 5-D and 5-C, can either be obtained directly from a separate power supply or obtained through a voltage-dropping resistor as indicated at "R," dropping the plate voltage to a sufficient value for the screen.

Frequency Multipliers


Radio frequency amplifiers can be used for frequency multiplication. For instance, we can feed a 3500 kc. signal into the grid of any one of the "single-ended," Class "B" or "C" R.F. amplifiers shown in the various diagrams; then by tuning the plate circuit to 7,000 kc. and taking power out of this circuit, we have doubled the frequency of the original exciting signal. Class "B" amplifiers are not well suited for frequency doubling, because there is less second harmonic present in the output circuit. A Class "C" amplifier is a very fine frequency multiplier where the even order of harmonics are to be obtained. A *push-pull* amplifier does not make a good second harmonic amplifier or frequency doubler because the *push-pull* output circuit tends to cancel out the even order of harmonics. The *push-pull* amplifier can be used as a frequency multiplier where the odd order of harmonics are desired. For instance, the 3rd, 5th, etc.

Push-pull amplifiers are generally used where *frequency tripling* is required. Through the use of the new pentode tubes, such as the 2A5, 42, 802, and 23, an oscillator and frequency multiplier can be combined within a single tube. In Figure 6, we have a pentode oscillator and multiplier. The crystal is connected between the cathode and the grid. A tuned circuit is inserted between the cathode and the "B" negative and is tuned to a frequency about midway between the crystal frequency and its second harmonic. This will cause the crystal to oscillate; then the plate circuit can be tuned to twice or even three times the crystal frequency, with a fair amount of power output. It can also be tuned to four times the crystal frequency, but the power output and plate efficiency are so low that it is of no particular value.

For the HAM!

In the next issue—All about the 5 meter M.O.P.A. that's now making history—"on the air"! It uses 3 type 89 Receiver tubes. W2AMN describes its construction.

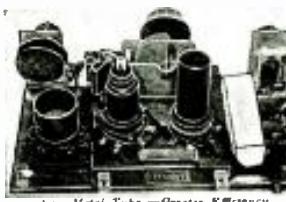H. G. Cisin's 2-Tube Metal Tube AIR SCOUT All Electric ALL WAVE



Only Set
of its kind
in
the world

Pat. Pending U.S.
Serial No. 302,586.
Operates on A.C.
or D.C. Self-Contained
Power Supply.

New Metal Tubes—Greater Efficiency

POWERFUL—W. C. Ansell, Jr., of Providence, R.I., logged 12 foreign stations the first week. Many Air Scout owners report reception from Spain, England, Germany, Rome and even Australia and Japan. Broadcast reception on indoor aerial. Police calls, amateurs, code, weather reports, airplane and Trans-Atlantic phone conversations. Speaker on strong stations.

COMPLETE ASSEMBLED KIT, all necessary parts, instructions, picture diagram and all four short wave coils, less tubes, long wave unit, broadcast coils and earphone, ready to wire.

Set of 2 Matched Metal Tubes, \$2.50 Broadcast Coils..... 1.45
Special Long Wave Unit W. Coil, .95 Earphone (Single)..... .85
Total..... \$3.95

SPECIAL COMBINATION OFFER—Assembled Kit, not wired, \$3.40
2 metal tubes, 6 coils, including Long Wave Unit, earphone,..... \$3.40
Above, Custom-Built, Wired and Laboratory Tested, ready to use, \$1 extra

H. G. CISIN'S AIR SCOUT SIGNAL SET

"THE IDEAL X'MAS GIFT FOR THE BOY"
THREE ENTERTAINING AND INSTRUCTIVE INSTRUMENTS IN ONE!

In this set, giving same signals used in wireless.

In Pictures, like a railroad telegraph sounder.

In Clues, like a crossword puzzle.

In Flags, like blinker signaling as used in Navy.


The Air Scout Signal Set comes in a compact, portable black crystalline metal case with suitable key. International Code Signals are printed on plate alongside key. Convenient switch changes from button to flag or code. Can be connected to similar instrument for code communication between friends. Ideal practicing code or for sending messages. Full instructions included. Uses two ordinary flashlight batteries.

COMPLETE READY TO USE (less batteries) \$1.25 (Two for \$2.)

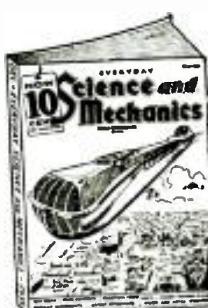H. G. CISIN, Chief Engineer, Allied Engineering Institute, Dept. S-23, 98 Park Place, New York, N.Y.

Over 130,000 People
Find Each Issue of
**EVERYDAY SCIENCE
AND MECHANICS**
of Intense Interest!

EVERYDAY SCIENCE AND MECHANICS is the finest scientific—technical—mechanical—construction magazine in the field. Up-to-the-minute with news flashes of scientific events. Dozens of instructional articles and many popular experiments. Ideas from which you can make things to sell.



Over 150 Illustrations

10c the copy

A HOST OF
INTERESTING SUBJECTS
COVERED
Woodworking—Photography—
Music—Patents and Inventions—Book Reviews—
Metal-Working—Chemistry—
Engineering—Microscopy—
Electrical Experiments—
Household Helps—Astronomy—Prize Contests—and other subjects.

Edited by
HUGO
GERNSBACK

Get your copy today!
On all newsstands
Everyday Science and
Mechanics
99-C Hudson St.,
New York, N.Y.



Instrument, with tapes prepared
by expert and complete course
of lessons: all for \$11.55

"HAM" SPECIAL Standard
Teleplex
A highly efficient code teacher
using heavy specially prepared
waxed paper tape, having two
rows of perforations. Write for
Free folder "S.W." DEALERS
Correspondence invited with dealers
in protected territories.

We are the originators of
this type instrument.
TELEPLEX CO.,
76 Cortlandt St., New York City

Reduce Noise On ALL Waves

LYNCH HI-FI ASSEMBLED ALL- WAVE ANTENNA

All ready to hang.
Saves 50% of installation time.
Amazing re-
sults.

\$6.75
List

Write
for folder

If dealer
cannot supply
order direct

\$5.00
List

LYNCH FILTERADIO

Cuts out objectionable
noise from the light
line. Easy to
install; simple to
adjust.

\$5.00
List

Arthur H. Lynch, Inc., 227 Fulton St., N.Y.
PIONEER OF NOISE-REDUCING AERIALS

NEW METAL TUBE PROFESSIONAL THREE-TUBE



All Electric

ALL WAVE

AIR
SCOUT

Superlative
Performance

- Foreign, Short Wave and Regular Broadcast Tubes
- 10 to 550 Meters
- Loud Speaker Operation
- Band Spread
- Self-Contained Power Supply

COMPLETE ASSEMBLED KIT, all parts, 4 coils 10 to 200 meters, diagram, less speaker, tubes, Broadcast Coil, and Earphone, ready to wire. \$6.95

Kit of 3 Matched All Metal Tubes..... \$3.50
Broadcast Coil (single)..... .95
Earphone..... .85

Total..... \$6.95

SPECIAL COMBINATION OFFER—Assembled Kit, not wired, 3 parts, 4 coils, including broadcast, earphone, less speaker..... \$10.95

Above Custom-Built, Wired and Laboratory Tested, ready to use \$1.75 extra. Loud Speaker (extra), \$1.65.

\$12.25

\$12.25

\$12.25

\$12.25

SA, OM!!**HARRISON HAS SUM FB XMAS BARGAINS!**

Grab yourself a few of these before they're all gone! There won't be any more shortly at anywhere near our special price!

Western Electric
211-D — \$4.90

Brand new, genuine, first grade, Western Electric Fifty Watters. Standard characteristics. Over 100 Watts output! An FB tube for any Ham! Regular selling price is \$17.50. Harrison offers them at the sensational price of only \$4.90. Unconditionally Guaranteed for 30 Days (broken glass or burnt out filament the only exceptions)! Safe, prompt shipment to any part of the world. Broadcast Stations supplied.



HEAVY DUTY
866 Mercury Vapor Rectifier Tubes
Fil. 2.5 Volts, 5 Amps.
Inverse Peak—7500 Volts
DC Current 600 MA.
A fully guaranteed tube at a low price
98c

New Low Prices
RCA—De Forest
Xmitting Tubes
866—\$2.25
8520—16.40
All other types in stock

VISIT OUR NEW
LARGE SALESROOM
AT
12 WEST BROADWAY
(Between Barclay and Vesey St.)
Send for FREE HAM BULLETIN

HARRISON RADIO CO.
12 West Broadway Dept. C-1 New York City

UNCONDITIONAL GUARANTEE ON ALL OUR RADIO SUPPLIES

UNCLE DAVE'S
SERVICE, RADIO SHACK
336 BROADWAY, ALBANY, N.Y.

Just a few left GENUINE SPRAGUE AMPLIFIERS, uses 3 tubes, 3½ watts output, less tubes, speaker and mike \$2.95
PEERLESS 3-tube Professional AC receiver, wired and tested, with tubes, power supply and 2 sets of coils for 15 to 200 meters \$15.75
PEERLESS 2-tube LOUDSPEAKER AC receiver, wired and tested with tubes, power supply and 1 set of coils for 15 to 200 meters \$12.75
Weston 1 Meters with volt-ohm-ma scale, net special early \$6.00
Weston 0-150 ohm AC meters, special \$6.75
Cable Address "UncleDave"
Long Distance Phone 4-5746
Include 20% deposit with o.d. orders
Prices F.O.B. Albany Foreign Trade Solicited
Send for new Ham Catalog—just out!

ELIMINATE Line Noise
with the
NEW MILLER LINE FILTER
J. W. MILLER COMPANY
5917 So. Main St. • Los Angeles, Calif.

RADIOS..SAVE UP TO 50%
DEAL DIRECT. Factory Price
Many models to select from
AC and DC sets, and
new metal Tube Models.
Your name and address on
postcard brings you NEW 1936
catalog. Get details of
30-DAY TRIAL plan and
Agent-User proposition.
Goldentone Radio Co., Dept. 222
8780 Grand River, Detroit, Mich.

RADIO ENGINEERING
RCA Institutes offers an intensive course of high standard embracing all phases of Radio. Practical training with modern equipment at New York and Chicago schools. Also specialized courses and Home Study Courses under "No obligation" plan. Catalog. Dept. SW-36.

RCA INSTITUTES, Inc.75 Varick St., New York. 1154 Merchandise Mart, Chicago
Recognized Standard in Radio Instruction Since 1909**Keeping the Short Wave League Club "Alive"**

(Continued from page 545)

wishes to attract new members and really grow into a flourishing organization, it would be a very good idea to publicize the club's activities in the local newspapers, bulletin boards about town, etc. Why not stage a short-wave "DX" performance, for the benefit of the laymen or those who are unfamiliar with what short waves are really doing today.

The technical experts of the club should hook up a first-class receiver, or at least the best the club can afford, together with a good-size amplifier, and let the folks hear some foreign stations roll in! In connection with such a demonstration now and then, a popular lecture could be very well given by one of the club's members qualified to do so. Lantern slides may be used to illustrate the lecture or pictures clipped from magazines, such as *Short Wave Craft* for example, can be very nicely projected on a screen by means of the well-known Reflectoscope or post-card projector.

Even though the club is small at the beginning, it will always prove a very good asset to have a library. Magazines, as well as the latest books on short waves and radio in general can be purchased through the club's funds, and magazine subscriptions may often be contributed as gifts by some of the club's members or friends of the club. If the club is in a small town and where the mayor is not so busy, he might appreciate being invited to one or more of the club's meetings. And do not forget the local M.D.—many physicians, through their thorough college training, which includes physics and mathematics, have become regular radio enthusiasts, and some of the liveliest clubs we know of have several M. D.'s and other professional men as regular members, and they often own and enjoy Ham stations in the bargain.

5-Meter Transceiver Uses Midget Tubes

(Continued from page 523)

on the tube, compatible with good sensitivity, in order that you will cause no undue interference with other 5-meter receivers.

The antenna which gave best results was a "doublet," measuring eight feet long, with a "twisted pair" feeder about three and a half feet long. The length of the feeder is determined by watching the plate current of the oscillator. For a given frequency the plate current should show a slight increase when the feeders are connected. The feeders can be tuned with a condenser if the proper length cannot be readily determined.

During tests we worked over distances of seven to eight miles and under favorable conditions ten to twenty miles may be covered with little difficulty.

Parts List for Transceiver

- 1—50,000-ohm 1/2-watt resistor, I.R.C.
- 1—1-meg. 1/2-watt resistor, I.R.C.
- 1—.5 meg. variable resistor (Pot.), Electrad.
- 1—.0001 mfd. mica condenser, Aerovox.
- 1—.004 mfd. mica condenser, Aerovox.
- 1—.006 mfd. mica condenser, Aerovox.
- 1—1mf. by-pass condenser, Sprague.
- 1—.1 mf. by-pass condenser, Sprague.
- 1—shield interruption-frequency transformer, National.
- 2—Isolantite coil assemblies (5-meter), National.
- 1—15 mmf. Isolantite variable condenser, National.
- 1—transceiver transformer; 3 windings.
- 1—midget choke, 30 henry A.C.-D.C. type.
- 1—0.25 MA meter, Triplett.
- 1—panel and shelf; see text, Blan.
- 1—carrying case; see text, Blan.
- 2—type XL "midget" tubes, Hivac.
(Types 30's may be used as substitutes.)
- 1—double-pole, double-throw, send-receiving switch.
- 1—3-volt midget battery, Burgess type T2FL.
- 2 midget 45-volt batteries, Burgess type X30FL.

"COSMAN 4" 5-Band 4-Tube Receiver

The year's outstanding inexpensive short-wave receiver. Provides Band Spread tuning of any signal. Uses two of the new Metal tubes; Built-in 15-Watt Speaker; 15-550 meter tuning range; 5-Band switch coil assembly—no plug-in coils; 1" Airplane Dial; Harmonic Tuning condenser; Built-in power supply and numerous other features found only in higher priced receivers. Uses four tubes; 2-6K7's; 1-13 and 1-25Z. A.C.-D.C. Operation.

Complete kit of parts and instructions. Not wired, less tubes and cabinet. \$10.50
Wired and tested, Extra. \$2.50
4 Matched Sylvania tubes. 2.25
All Metal Crystallized Cabinet for "Cosman 4". 1.50

Send for Our New 1936 Catalogue.

TRY-MO RADIO CO., INC.
85 CORTLAND ST. NEW YORK CITY**What more useful HOLIDAY GIFT**

can you give your relatives or friends than a large and good looking
SPORTS BINOCULAR

A real high-power field glass that enables you to enjoy such sporting events as Football, Prize Fights, Wrestling Matches, Horse Racing, Baseball-Games, etc. Most useful on Auto Trips, Hunting, Outings, Beaches, etc. It's a real buy at a fraction of its worth.



PARCEL \$1.50
POST
PREPAID 5 1/4" long, extended to 6 1/4", lenses nearly two inches in diameter. Black crackle finish. Carrying strap.

Supply limited—ORDER NOW!
Money back guarantee. You can't lose!

GOLD SHIELD PRODUCTS CORP.
17 West 60th St. Dept. S. New York City

**RADIO'S LIVEST MAGAZINE**

Edited by HUGO GERNSBACK

RADIO-CRAFT is devoted to general Radio in all its phases, to Studio Servicing and to the advanced set builder and Radio Technician. Kinks show simple ways out of difficult problems. The latest radio equipment is illustrated and described.

8
Months for
\$1.00

RADIO-CRAFT
99C Hudson Street
New York, N. Y.

Short Wave League Members

IDENTIFY THEMSELVES WITH THE ORGANIZATION

In order that fellow members of the LEAGUE may be able to recognize each other when they meet, we have designed this button, which is sold only to members and which will give you a professional appearance.

If you are a member of the LEAGUE, you cannot afford to be without this insignia of your membership. It is sold only to those belonging to the LEAGUE and when you see it on another, you can be certain that he is a member. See Page 576.

Lapel Button, made in bronze, gold filled, not plated, prepaid..... 35c
Lapel Button, like one described above, but in solid gold, prepaid..... \$2.00

FREE S-W DATA SERVICE

Joseph Calcaterra, Director

Short Wave Craft Data Service,
99 Hudson Street,
New York City, N. Y. SWC-136

Please send to me, without charge or obligation, the catalogs, booklets, etc., the numbers of which I have circled below.

2	3	4	5	25	
28	57	73	74	75	76

My radio connection is checked below:

- () Short-Wave Set Builder
- () Short-Wave Experimenter
- () Short-Wave Listener
- () Service Man operating own business
- () Service Man for manufacturer
- () Service Man for jobber
- () Service Man for dealer
- () Service Man for servicing company
- () Dealer
- () Jobber
- () Experimenter
- () Professional Set Builder
- () Amateur Set Builder
- () Licensed Amateur
- () Station Operator
- () Radio Engineer
- () Laboratory Technician
- () Public Address Worker
- () Manufacturer's Executive
- () Student

My age is years.

I have been interested in radio for years.

I buy approximately \$.00 of radio material a month. (Please answer this question without exaggeration or not at all.)

(Please Print Name and Address)

Name.....

Address.....

City..... State.....

AVOID DELAY. The catalogs and booklets listed are now in stock and will be sent promptly as long as the supply lasts. Only the items listed are available. Please make your selection from the current issue of *Short Wave Craft*, and use the coupon in ordering the items.

● THE catalogs, booklets, and folders listed in this department contain a wealth of information and data which will help you in your short-wave work.

These catalogs, booklets, and folders may be obtained by *Short Wave Craft* readers (without the trouble and expense usually involved in writing individual letters to the various organizations which publish them) through arrangements which have been made by *Short Wave Craft* magazine with the publishers of the literature listed.

To obtain any of the material listed in this department, simply draw a circle around each Booklet Number on the coupon, corresponding to the numbers of the items you would like to have, fill in the rest of the coupon and mail it to the *Short Wave Craft* Data Service.

A complete stock of these catalogs and other literature is kept on hand and will be sent to you promptly, as long as the supply lasts. There is no limitation on the number of items you may ask for, but to avoid waste, please do not ask for material in which you are not interested or of which you already have a copy.

Only the literature listed in this issue is available. Please do not ask for catalogs which are not listed. Do not include letters asking for information from other departments with your request for catalogs as that will cause delay in answering your inquiries.

2. HAMMARLUND 1936 CATALOG. Short wave fans and set builders will find a flock of

new low-loss parts such as variable condensers, coil forms, sockets, transformers, chokes, shields, and other precision products especially designed for short-wave and ultra-short-wave work described in this catalog. Information on short-wave sets is included.

3. THE HAMMARLUND SHORT-WAVE MANUAL. No short-wave fan who is interested in short-wave set design should be without this 16-page manual, which contains constructional details, wiring diagrams and lists of parts of the day. A circular giving a description and 12 of the most popular short-wave receivers of list of contents of this manual is available free of charge to *Short Wave Craft* readers.

4. THE HAMMARLUND "COMET PRO" SHORT-WAVE SUPERHETERODYNE. This receiver is still holding its own as one of the leading short-wave receivers available for professional operators and advanced amateurs, for work on 15- to 250-meter code and phone reception. It is especially adapted for laboratory, press, police, airport and steamship use.

5. ELECTRAD 1936 VOLUME CONTROL AND RESISTOR CATALOG. No short-wave set can function properly unless the volume controls and resistors are of the best. This catalog of resistors features the latest developments in the resistor art. Fundamental volume and tone control circuit diagrams are given.

25. LYNCH NOISE-REDUCING ANTENNA SYSTEMS. No use trying to get world-wide short-wave reception if your aerial picks up more noise than signals. This folder, by Arthur H. Lynch, gives complete instructions on how to build noise-reducing antenna systems for short-wave reception and contains a special supplement covering Ham Antenna Design for transmitting and receiving on the amateur bands as well as the ultra-high frequencies.

28. LYNCH SUPER-FILTASTATS FOR AUTO RADIO INSTALLATIONS. It isn't necessary to put up with ignition noise in auto radio installations. The new Lynch Super-Filtastats eliminate ignition noise without the necessity of using the conventional suppressors.

57. RIBBON MICROPHONES AND HOW TO USE THEM. How do your phone signals sound to the fellow at the receiving end? If they sound as though you're talking with a bunch of marbles in your mouth, the chances are a good microphone, properly hooked up, would help "to beat the band." This folder describes the Amperite Velocity Ribbon Microphone and gives information and circuit diagrams on how to connect up the microphone.

73. HOW TO ELIMINATE RADIO INTERFERENCE. You'll get much more enjoyment out of short-wave programs if you cut out the noise interference. This handy folder gives complete information on the Sprague Interference Analyzer and how to use it to locate and eliminate radio interference.


74. SPRAGUE ELECTROLYTIC AND PER CONDENSER CATALOG. You can't very well build a short-wave set without fixed condensers for filtering and bypassing. You'll find complete specifications of all the condensers you'll need for building or improving your short-wave set in this catalog. A description of the Sprague Capacity Indicator, for making tests on condensers, is included.

75. SPRAGUE TEL-U-HOW CONDENSER GUIDE. If you are ever puzzled regarding the proper kind, capacity and voltage of condenser to use in any given place, you should have a copy of this free chart which gives data on just that very subject. This folder also gives valuable hints on how to locate radio troubles due to defective condensers and includes helpful data on condenser calculations.

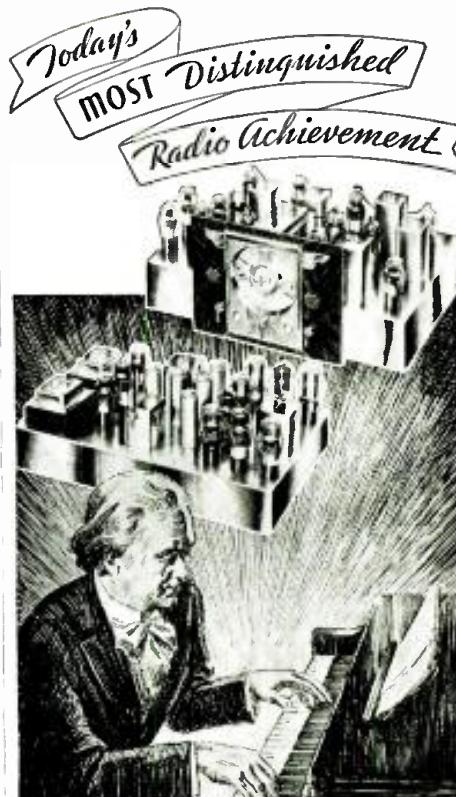76. FACTS YOU SHOULD KNOW ABOUT CONDENSERS. If you have any wrong ideas or notions as to the effect of certain condenser characteristics on the filtering efficiency or suitability of a condenser for a given application, this little folder will straighten you out.



Cannot Be Obtained Under One Cover Elsewhere!
Complete Symbols used in Radio Circuits. Frequently used for
Complete Grid-bias for 28 Standard Tubes. Complete R.M.A.
Color Code. International Morse Code. Diagrams and Technical
Data for building 4 FAMOUS EAGLE ALL-WAVE SETS and
AC-DC MIDGET HOOK-UP. Dictionary of Radio Definitions
All Radio Terms defined and explained. Characteristic chart of
New Metal Tubes, etc.
DON'T HESITATE—WRITE NOW!
Enclose 10¢ in stamps or coin, which only covers the cost of handling
and mailing this valuable technical data.
EAGLE RADIO Dept. S-1, 84 Cortlandt St., New York City



CUSTOM BUILT ROYALE 24-TUBE Radio

THIS super radio-musical instrument was created for those discriminating and exacting few who insist on the finest, most beautiful, most precisely built radio obtainable. A set of rare distinction, musically and artistically perfect, the Royale offers over 100 features... assuring a luxurious and idealized type of brilliant, sparkling, guaranteed world-wide performance... heretofore unattainable. It is today's only "aged" radio... offers 6 tuning ranges... 4 1/2 to 2400 meters... etc.

This 24-tube achievement outperforms other receivers. Assures Unlimited Scope Full Fidelity. Audio range is 20 to 16,000 cycles per second... 40 watts undistorted output. Fully guaranteed for 5 years... absolute satisfaction assured.

The 30-day FREE Trial Offer enables you to try the Royale in your own home, without obligation. Write for literature now or mail coupon TODAY.

ROYALE RADIO CRAFTERS
(Division Midwest Radio Corporation)
Dept. 205G, Cincinnati, Ohio.

Without obligation, send me literature describing Custom-Built 24-Tube 6-Tuning Range, Royale Radio... and details of your 30-day Free Trial Plan.

Name.....
Street.....
Town..... State.....

Learn Code RIGHT With The SYSTEM That Made The Champion



TED McELROY
World's Champion Radio Operator. Speed 69 wpm.

CHAMPION McELROY says: "My speed is the result of CANOLER training. It taught me to read code as easily as I read print. Beginners who wish to learn code **RIGHT**; and those who want real speed, will save themselves much time and discouragement by taking The CANOLER SYSTEM."

FREE—Copy of article by Champion McElroy: "HOW I LEARNED TO HANDLE CODE," also BOOK OF FACTS containing valuable help if you want to learn code **RIGHT**. A card will do. No Obligation.

Candler System Co. Dept. S-1, Asheville, N.C.

ANNOUNCING!!

OUR "EASY PAYMENT PLAN"

NOW Radio Amateurs and Shortwave listeners, living in any part of the U. S. A., may buy modern, standard shortwave receivers on extremely easy terms. We now offer our really "EASY PAYMENT" Plan for the Radio Amateur and Experimenter, so you and your friends may purchase a really good receiver out of your budget. Our plan enables you to equip your station with the latest type receivers, thus greatly increasing your interest and pleasure in Amateur Radio.

JUST THINK payment, you may have your choice of the finest receivers on the market. You can equip your station with that fine new receiver you thought you couldn't afford. Really, OM, you can't afford NOT to buy your new set—our plan works so well for you.

WHY WAIT? Every day you put off ordering, you are without good reception that much longer. If you're buying it—buying up-to-date equipment. Get "On The Air" OM. Write for further information on our really "EASY PAYMENT PLAN".

HINDS and EDGARTON
19 S. Wells St., Chicago, Illinois
W5APY R5D08 W5WR

Regent 5-Tube 5 Band 15-550 Meter Switch Receiver

This new improved "Regent" completely eliminates the use of plug-in coils. Independent tuning of the five separate bands is accomplished by means of a five-band switch. No more groping around for the proper coils. A great distance getter that will fulfill the requirements of every radio experimenter or amateur. Uses 2-58's, 1-80 and 2-245's. All controls on front of cabinet. Complete kit of parts includes: 5 band control, dial, blue prints, and all accessories unwired, less cabinet and tubes. Cabinet \$12.50
Cabinet for wiring and testing (extra) \$1.50
Set of 5 Matched Sylvania or R.C.A. Tubes 2.50
Write for our latest catalog or circular



TRY-MO RADIO CO., INC.
85 Cortlandt St. New York City
This is our only address

QUALITY RADIO SUPPLIES

1936 Catalog featuring hundreds of new items—xmitting and transceiver parts—television and short wave equipment, apparatus and items of interest to all in the radio industry. Send 10c in stamps or coins to cover the cost of handling and mailing.

INSULINE CORP. OF AMERICA
25 Park Place Dept. S-1 New York, N.Y.

SPECIAL

FOR THIS MONTH
Send \$1.00 (\$1.25 Canada and foreign) and we will send you SHORT-WAVE CRAFT for Eight months. DO IT NOW.

SHORT WAVE CRAFT
99-101 Hudson Street New York

Latest TUBE DEVELOPMENTS

New 6A3 Audio Amplifier



The New 6A3 Au-
dio Amplifier Tube

and the two grids are connected together, with a single grid and plate terminal in the base of the tube.

These tubes are said to be more uniform than the older type of 2A3.

THE 6A3 is the latest addition to the tube family and it is designed to replace the 2A3 in high fidelity audio amplifiers. The new tube requires 6.3 volts for the heater instead of the 2½ which the 2A3 required.

The elements of the tubes are duplicated; in other words, there are two triodes within the envelope and they are connected in parallel internally. The two plates are connected together,

and the two grids are connected together, with a single grid and plate terminal in the base of the tube.

These tubes are said to be more uniform than the older type of 2A3.

Sylvania Type 6A3 Output Triode CHARACTERISTICS

Filament Voltage A.C. or D.C.	6.3 Volts
Filament Current	1.0 Ampere
Maximum Overall Length	5¾"
Maximum Diameter	2 1/16"
Bulb	ST-16
Base	Medium 4-Pin

Operating Conditions and Characteristics: Class A Amplifier (One Tube)

Filament Voltage	6.3 Volts
Plate Voltage	250 Volts Max.
Grid Voltage	-45 Volts
Plate Current	60 Ma.
Plate Resistance	800 Ohms
Mutual Conductance	5250 micro-mhos
Amplification Factor	4.2
Load Resistance	2500 Ohms
Power Output (with 5% 2nd Harmonic)	3.3 Watts

Push-Pull Class A Amplifier (Two Tubes) Fixed Bias

Filament Voltage	6.3	6.3 Volts
Plate Voltage	325	325 Volts Max.
Grid Voltage	-68	-68 Volts
Plate Current per Tube	35	35 Ma.
Plate to Plate Load Resistance	3000	5000 Ohms
Power Output	15	10 Watts
Total Harmonic Distortion	2.5%	5%

The "SG3" Transmitter

(Continued from page 539)

- 8—Isolantite coil forms (5-prong); National.
- 1—Crystal, 80 or 40 meters or one for each.
- 2—Small standoff insulators; National.
- 3—Closed circuit jacks.
- 1—0-100 MA meter Triplett.
- 3—Type "89" tubes.

Coil Data Receiving Parts Transmitter

xtal	80 meters	osc. plate	amp. grid	amp. plate
20T.	27-T.		54-T.	26-T.
xtal	40 meters	osc. plate	amp. grid	amp. plate
9T.	12-T.		26-T.	12-T.
xtal	20 meters	osc. plate	amp. grid	amp. plate
Use	6-T.		16-T.	6-T.
40m				
coil				

All coils close-wound with No. 22 D. C. C. wire. Amp. grid coil No. 30 D. C. C. wire. Amplifier coils are both center-tapped.

Please mention SHORT WAVE CRAFT when writing advertisers

Copies of
6 SHORT WAVE CRAFT
70c PREPAID

For a limited time only, and as long as they last, we will send you six back numbers of SHORT WAVE CRAFT assorted, your choice, for 70 cents.

The usual price for six copies would be \$1.50 and most publishers charge a higher price for back numbers over one year old.

We can supply all copies except the following: June-July, Aug.-Sept., Oct.-Nov., 1930; Dec.-Jan., 1931; May, June, Sept., Nov., 1932; Jan., Feb., March, May, June, July, 1933; Dec., 1934.

If you do not specify copies we will use our own judgment in sending assorted numbers to fill your order. Note we cannot exchange the copies for ones that have been sent to you.

Practically every copy of SHORT WAVE CRAFT contains important information that you should have. Here is a chance to get those copies.

As we have only a small supply of back numbers on hand, this offer will be withdrawn as soon as they have been sold.

We accept U.S. stamps, U.S. coin, or money order. Rush your order today.

SHORT WAVE CRAFT
99-101 Hudson Street New York, N.Y.

SHORT WAVE CRAFT 1-36
99-101 Hudson Street, New York, N.Y.

Gentlemen: I enclose herewith 70c. for which you are to send me six back number copies of SHORT

WAVE CRAFT as follows:

Name _____

Address _____

City..... State.....

ELECTRIC DRILL

CAPACITY
1/4" DRILL



Weight 4 1/2 lbs.

PRICE
\$5.97

This Utility Drill is built for intermittent service, always ready for instant use, and will accommodate straight shank drills up to 1/4 inch. Weighs only 4 1/2 pounds, and has a convenient on-and-off switch mounted on the motor body. The three-jaw chuck has a capacity up to 1/4 inch. Furnished complete with 10 feet of heavy duty rubber covered cord, and plug cap. Operates on alternating current only, 110 volts, 60 cycles. Ship. weight 5 lbs.

Shipped by Express Collect if not sufficient postage included.

MONEY-BACK GUARANTEE

WELLWORTH TRADING CO.
506 Palmolive Bldg. DEPT. SWC 136
CHICAGO, ILLINOIS

PATENTS — TRADE MARKS

All inventions submitted held confidential and given personal attention by members of the firm.

Form "Evidence of Conception" and instructions

"How to Establish Your Rights"—Free
LANCASTER, ALLWINE & ROMMEL
PATENT LAW OFFICES
475 Bowen Bldg. Washington, D. C.

A 3-Tube Preselector

(Continued from page 534)

In the design of a preselector several factors must be considered. It should have sufficient selectivity to completely eliminate image response at high signal frequencies as well as have noticeable gain at those same frequencies. Two stages of radio frequency amplification are necessary to accomplish this. Quick change from one band to another makes coil switching, rather than plug-in coils, desirable but the coils and the coil switch must be of low loss design with short leads from coils to switch, if any gain is to be realized at high frequencies.

Proper shielding as well as the correct layout of parts must be considered to prevent oscillation or unstable operation without resort to critical sensitivity controls or adjustments.

The unit should contain its own power supply so that it can be used with any type of receiver, by simply connecting it to the antenna post of the receiver and connecting the antenna to the preselector. If the unit were to receive its power from the receiver, more or less complicated connections would be necessary, which in some cases would disturb the balance and sensitivity of the receiver.

The Miller Preselector is shown as an

example of good design and fills all the requirements of an ideal preselector. It should have sufficient selectivity to completely eliminate image response at high signal frequencies as well as have noticeable gain at those same frequencies. Two stages of radio frequency amplification are necessary to accomplish this. Quick change from one band to another makes coil switching, rather than plug-in coils, desirable but the coils and the coil switch must be of low loss design with short leads from coils to switch, if any gain is to be realized at high frequencies.

The coils are mounted one above and one below the chassis at right angles to each other, providing good shielding as well as short leads to the switch and tuning condensers, which are two-gang .0035 mfd. The trimmers originally mounted on the tuning condensers are not used and are bent wide open to provide as low a minimum capacity as possible. Separate trimmers are used on each coil and are mounted close to the coil switch. These trimmers are 50 mmf. maximum capacity and are adjusted to as low a capacity as possible to make the circuits track.


A shield is shown in the bottom view of the chassis, between the R.F. coil and the band-change switch, and is bent so that it also shields the trimmers TC3 and TC4 from each other. Without this shield, the unit may oscillate at some positions on the dial.

The resistors shown in the circuit diagram are all one-watt carbon and the bypass condensers have a 400-volt rating. The .002 mfd. condenser from plate of second R.F. tube to the receiver antenna post must be a good mica condenser.

The power supply provides full 250 volts to the plates of the tubes and uses a type 80 rectifier tube. A single 15 henry choke and two 4 mfd. condensers in the same can, adequately filter the output. The power transformer can have either a 2½-volt or a 6.3-volt winding for the heaters, depending on which type of tubes are used.

The wiring to the various parts is not critical, states Ralph O. Gordon of the J. W. Miller Co., except for the coil to switch and trimmer condenser connections, which should be as short and direct as possible, keeping the wires well separated. The preselector antenna lead from the binding post to the coil switch should be a stiff piece of bus bar kept well away from the second R.F. coil circuits.

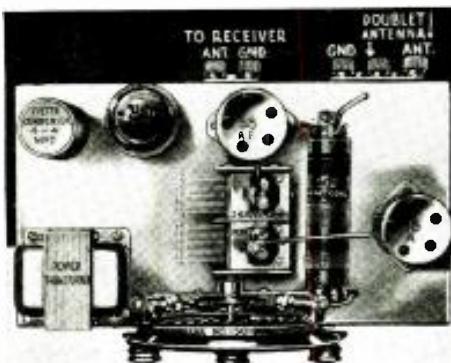The unit is mounted on a metal chassis 10½ inches wide, 6 inches deep, and 2½ inches high. A 4-inch airplane-type dial gives plenty of band-spread and the tuning is sharp but not at all critical.



Top view of the preselector chassis.

example of good design and fills all the requirements of an ideal preselector. The circuit diagram is given here. Three sets of coils are used to cover the range of frequencies from 1500 to 25,000 kc. As most all-wave receivers operate satisfactorily on the broadcast band of 550 to 1500 kc., coils for those frequencies are not provided, but provision is made for the inclusion of broadcast or other long-wave coils by an extra contact on the coil switch.

A five-contact three-circuit switch is used. The (A) contact or position cuts out the preselector by connecting the antenna direct to the receiver. This position is used when working on the broadcast band. It can also be used to check the gain in both volume and selectivity when the preselector is in circuit. A signal tuned in on the receiver that is barely audible, can be brought up to full room volume when the preselector is switched and tuned to the signal frequency. Also a reduction of noise in relation to signal is noticed, due to the increase in selectivity. If, when the signal was tuned in on the receiver, it had interference due to image response, this interference will be completely eliminated when the preselector is switched on.

The (B) position connects the coils for the 75- to 200-meter band, the (C) position the 35- to 75-meter coils, and the (D) position the 12- to 35-meter coils. The extra position is either connected to the (A) contact or used for a set of coils on some other frequency.

The coils have been designed to provide high and uniform gain throughout their range. The antenna coils are inductively coupled to the first grid coil and are not grounded so that a doublet antenna can be used. The plate of the first R.F. tube, which can be either a type 58 or 6D6, de-

\$200.00 "Cover Title" Contest Winners in Next Issue.

THE prize awards to the successful contestants in our *Cover Title* Contest will be published in the February issue. Thousands of titles were submitted to the judges, and the editors were agreeably surprised by the large number of entries received, and we know that all of our readers will be on "tiptoe" until they learn the name of the first prize winner. The first prize is the magnificent, new 18-tube Midwest receiver, as announced in the previous issue of this magazine. If you like this contest and have some suggestions for a future contest in *Short Wave Craft*, send them to the Editor, care of this publication.

WANTED —Fully experienced Radio Service Expert, "Screw driver mechanics" need not apply. Must be fast, accurate and thoroughly familiar with all types of modern radio work. A real opportunity for the right man. State qualifications in detail. Box 101, c/o Bulletin.

Could You Fill This Service Job?

Under improved business conditions, dozens of good-paying opportunities will soon be popping up in radio. Your future depends on whether or not you are qualified to grasp them. Will they go to other fellows—or will you MAKE them come to you!

Sprayberry Training is designed NOT for beginners but for men already in the service business who recognize the need for keeping up-to-date. It is for men who know that, to get better-than-average jobs, they have to be better-than-average workmen. It is sound, practical business and technical training—at a price within the reach of all. Investigate!

LET ME HELP YOU BUILD A REAL SERVICE BUSINESS



F. L. SPRAYBERRY 2548 University Place, N.W.
Washington, D.C.
Without obligation, send me details on your advanced
Service Training.

Name.....

Street.....

City SW1-36

SPRAYBERRY'S PRACTICAL MECHANICS OF RADIO SERVICE

Radio's Latest Developments ... WHOLESALE RADIO'S New 1936 CATALOG!



196 Pages Crammed With Bargains at Lowest Wholesale Prices

Get your copy now! Over 50,000 items! Every latest radio development, every last minute improvement. Newest sets from 2-24 tubes, parts, tubes, kits, tools and accessories; Short Wave and X-Mitting Equipment; Nationally known lines. Quality approved parts for all radio construction kits. Buy from the World's Largest Stock at Lowest WHOLESALE Prices and save Money. Send coupon for your FREE copy of radio's latest, greatest Bargain Book.

Parts can be supplied for any kit described in this magazine

Wholesale Radio Service Company
100 Sixth Ave., Dept. SW-16, New York, N.Y.

Please rush FREE copy of your new 196 Page Catalog for 1936, listing over 50,000 items

Name.....

Address.....

City State


AMERICAN MICROPHONE CO. A California Corporation

Microphones of Quality


Condenser, Carbon, & Crystal Microphones.

New catalogue available upon request.

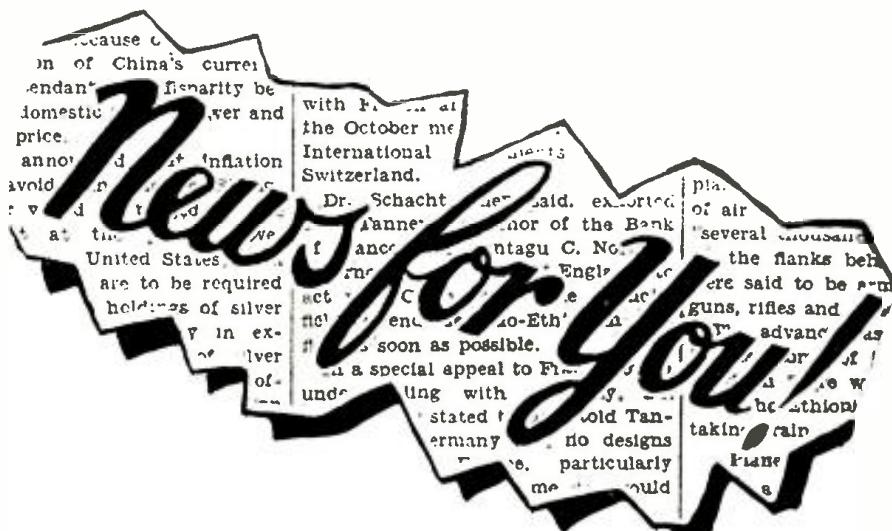1915 South Western Avenue, Los Angeles, Calif.



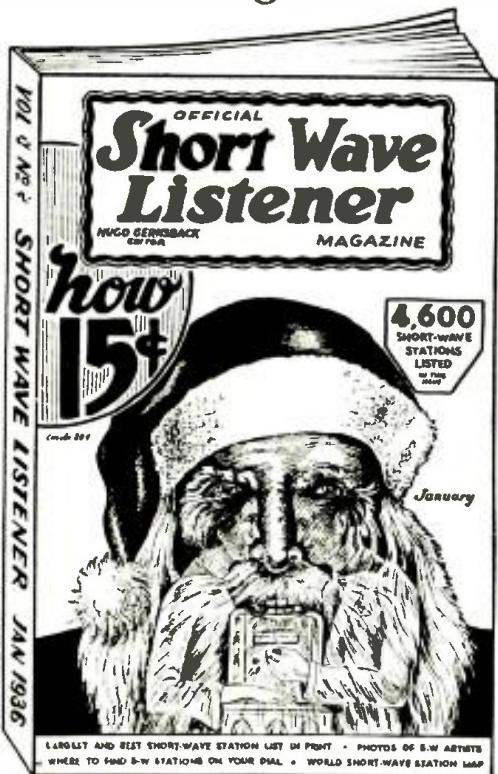the new price of 15¢ makes SHORT WAVE LISTENER the leading short-wave fan magazine



P. S. —If you cannot get the magazine at your newsstand due to sell-out, send 15¢ in cash, stamps, or money order, and we will send the magazine to you direct, prepaid.

Features in the January Issue

How to Obtain Verifications. Short Wave "Map" of the World. Latin-American S-W Stations by H. S. Bradley. Latest Reports from Short-Wave Listeners. How to Listen to Police Calls. New "Catches" Among S-W "Foreigns". Hints for Improving S-W Listening. "Grand List" S-W Stations of the World. The Listener Asks—"Questions and Answers". "Best" S-W Station List. Silvery Trophy Cup for "Best Listening Post" Photo. Up-to-date List of "Police Calls."

From this you will see that the magazine has been designated as a companion magazine to SHORT WAVE CRAFT.

If you are now a reader of SHORT WAVE CRAFT magazine, you will not wish to be without THE OFFICIAL SHORT WAVE LISTENER MAGAZINE. It will help you tremendously in your short wave logging at all times. This invaluable information, such as you cannot get anywhere else, THE OFFICIAL SHORT WAVE LISTENER MAGAZINE, in other words, is a necessity.

OFFICIAL SHORT WAVE LISTENER MAGAZINE
99 HUDSON STREET

An All-Electric Amplifier and Power Supply

(Continued from page 532)

and can recommend its operation most highly. As a matter of fact, it can be used with almost any earphone receiver, including the small battery sets and it gives excellent volume and tone quality. It can also be used for many other purposes where a small but effective amplifier is required.

Actually it adds two powerful (self-contained power supply) audio stages to the original receiver. In the first stage, the 6C6 tube is coupled to the receiver by resistance-coupling. The 75,000-ohm grid resistor is replaced by a 75,000-ohm potentiometer which serves as a *volume control*. The 6C6 tube is also coupled to the output stage by resistance-coupling. The 43 type pentode tube is used in the output stage. The rectifier is a 2Z5Z tube which provides rectified current for the 6C6 and the 43 tubes and also for the dynamic speaker field. A small choke bypassed at either end by electrolytic condensers provides more than sufficient filtering to eliminate hum when the amplifier is used on A.C. The standard Universal A.C.-D.C. circuit is employed so that the amplifier will work just as well on alternating current as on direct current. The filaments of the three tubes are connected in series and the 300-ohm limiting resistor is contained in the line cord. By connecting the .01 mf. cartridge condenser and the 75,000-ohm variable resistor in series between the plate of the 43 and ground, an excellent *tone control* is obtained.

In constructing the *all-electric* amplifier a metal chassis is used similar to the one used in making the sets previously described. The only component mounted on top of the chassis is the choke, CH-1. The three six-prong sockets are secured to the chassis and the small fixed resistors and fixed condensers are soldered in place beneath the chassis during the wiring. In the amplifier illustrated, the entire outfit has been mounted in a small cabinet with the volume control, tone control, and dynamic speaker fastened to the front panel of the cabinet.

The wiring is so easy to do that it is hardly necessary to go into any detail regarding this. It is suggested, however, that the filaments be wired in first with the other wiring following in natural sequence. All ground returns may be connected directly to any portion of the metal chassis. This eliminates the use of a single ground return wire reducing the amount of wiring and resulting in a better-looking job.

The *all-electric* amplifier is the easiest thing in the world to connect up and use. First of all, the line cord is plugged into an A.C. or D.C. source. If used on direct current, it may be necessary to reverse the plug before the amplifier will operate as it only works in the one way on direct current. After the tubes have had a chance to warm up, place a hand on the flexible input wire and a distinct audio hiss will be heard. Now, put the receiver into operation and attach the input wire to one of the earphone jacks. Experiment will show which is the correct wire; as soon as the right one is attached, the amplifier works.

List of Parts for Amplifier

- C1—.01 mf. cartridge condenser
- C2—.01 mf. cartridge condenser
- C3—.01 mf. cartridge condenser
- C4—10 mf. 25 volt cartridge electrolytic condenser
- C5, C6—dual electrolytic condenser, 8 mf. each section
- C7—2 mf. cartridge condenser
- R1—75,000-ohm Electrad potentiometer with switch
- R2—10,000-ohm, 1-watt IRC Resistor
- R3— $\frac{1}{4}$ meg., $\frac{1}{2}$ watt IRC Resistor
- R4—1 meg., $\frac{1}{2}$ watt
- R5—600-ohm wire-wound resistor
- R6—75,000-ohm Electrad rheostat
- R7—300-ohm, 50-watt line cord
- CH1—300-ohm, 20-henry choke
- V1—6C6 tube
- V2—43 tube
- V3—2Z5Z tube
- 3—6-prong sockets
- 1—screen grid clip
- 1—5" Dynamic speaker output transformer for 43 tube
- 1—metal chassis, hardware

Please mention SHORT WAVE CRAFT when writing advertisers

Short Wave Scout News

(Continued from page 548)

HRN—Tegucigalpa, Honduras, 5.87 megs. is a new Honduras station heard in the evenings with strong signals. Every Sunday evening at 8:30 p.m., E.S.T.

XBJQ—Mexico City, Mexico, D.F., 11.00 megs. This is a new station which is putting a very strong signal into this part of the country. They are heard from 5—12 p.m., E.S.T. daily. They request reports to be sent to P.O. 2825, Mexico, D.F.

OPL—Leopoldville, Belgian Congo, can be heard daily at 11:45 a.m., E.S.T., calling station ORG at Brussels. OPL is on 20.04 megs, and is heard well when conditions prevail. A man with a low gruff voice calls out "Allo Bruxelles," and then converses in Belgian.

VWY—Poona, India, 17.54 megs. This station calls London daily between 7:30 and 8:00 a.m., E.S.T., every day, and when no calls are ready for them they immediately close down. They are heard very well in this part of the country, and are very clear. They use English entirely, and when closing down they announce as "V.W.Y."

JVT—Tokio, Japan, 6.75 megs. is now heard on mornings from 5—8 a.m., E.S.T., with very good volume. This station replaced the famous JVM. However, JVM is used to broadcast the "Overseas" program which is broadcast every Monday and Thursday from 4—5 p.m., E.S.T. on 10.74 megs.

TG2X—Guatemala City, Central America, 5.94 megs., is a new station heard in Guatemala. They are slightly higher in frequency than HJ4ABE and are heard in the evenings from 8—12 p.m., E.S.T. They identify themselves as "Los Voz del Nacional Policiano," or in English, Voice of the National Police.

TYA—Paris, France, 12.22 megs., can be heard calling the ship Normandie daily from 1—3 p.m., E.S.T. Call Normandie in English.

YVQ—Maracay, Venezuela, 6.67 megs. This station which is a phone station is now broadcasting musical programs every Saturday night from 8—9 p.m., E.S.T. They announce in English after every selection.

PHI—Huizen, Holland, 11.74 megs. This station is now operating on this frequency, and is heard with very good volume and excellent program merit. This station was previously on 17.77 megs. They will verify all reports, and English is used freely. They broadcast from Wednesday to Monday inclusive from 8—10:30 a.m., E.S.T.

LSN-3—Buenos Aires, Argentina, is a new station which was heard on 9.88 megs., re-broadcasting station LR1. They are at Buenos Aires, and reports should be sent to LR1. They broadcast an English program.

ZBW—Hong Kong, China, 8.75 megs. This station is heard quite well when conditions prevail from 5—7 a.m., E.S.T. They will be heard much better as winter pushes in. Reports of reception should be sent to Miss Betty Billing, Hong Kong Broadcasting Service, Post Office Box 200, Hong Kong, China.

PLP—Bandoeng, Java, 11.00 megs., is heard every Sunday morning from 5—9 a.m., E.S.T., broadcasting music, and announcing in English. They are the best-heard station on Sunday morning, and broadcast in parallel with PMN also at Bandoeng, on 10.26 megs.

ETB—Addis Ababa, 12.27 megs., was heard on Sunday, Oct. 13, 1935, at 1:00 p.m., E.S.T., calling the United States. They were heard until 1:35 p.m., E.S.T., frequency 12.275 kilocycles.

ZLT—Wellington, New Zealand, can be heard on 11.05 megs., calling and speaking to VLZ of Australia at 12:30 a.m., E.S.T. in the mornings.

Edward G. Schmeichel,
2939 South Luomis St.
Chicago, Ill.

Official Listening Post, Richmond, Va., Reports

Call	Location	K.C.	Remarks
COCH	Havana, Cuba	9.428	Very good
EAQ	Madrid, Spain	9.860	Loud and clear
DIQ	Germany	10.400	Special for Denmark
HBP	Geneva, Switzerland	7.799	Very good
HBL	Geneva, Switzerland	9.595	Fading at times
RNE	Moscow, Russia	12.000	Fair-to-Good— QRN
CT1GO	Paredes, Portugal	6.198	Very poor
HAT4	Budapest, Hungary	9.125	Talk and Music
HKY	Bogota, Colombia	8.795	Music—good
HIIH	Dominican Republic	6.800	Good—QRN times
RNE	Moscow, Russia	12.000	Very good
RADIO	Colonial Paris, France	11.890	Very weak
2RO	Rome, Italy	11.810	Fair
2RO	Rome, Italy	9.635	Good
DJD	Berlin, Germany	11.770	Good
TIEP	San Jose, Costa Rica	6.710	Very good
W7BCI	Washington State	20 Mts.	W6BJ
TI2RC	Costa Rica	20 Mts.	CQ
HBL	Geneva, Switzerland	9.595	Good
HBP	Geneva, Switzerland	7.799	Good
CRCX	Bowmanville, Ont., Can.	6.090	Very good
WMA	Lawrenceville, N.J.	Working England	
LU6AP	Argentina	20 Mts.	Working W3BPII
EAQ	Madrid, Spain	9.860	Very good

Please mention SHORT WAVE CRAFT when writing advertisers

WCG	New York	10,500	Testing
HPF	Panama City	Calling WNC
WQP
WCG	New York	Testing HBJ
HBJ	Geneva, Switzerland	Testing WCG
HP5J	Panama City, Panama	9,590	Very good
ORK	Brussels, Belgium	10,330	Very good
WEN	Special to DIQ
WEA	New York	A. B. Rice,
		3432 Hanover Ave., Richmond, Va.	

Ohio Report from E. M. Heiser Brecksville, Ohio—Time is E.S.T.

Date	Time	Call	K.C.	Location	Remarks
Sept. 1935					
Sept. 21	p.m.	HJ4ABA	11,700	Colombia, S.A.	Very loud and clear
21	7:30	EAQ	9,860	Spain	Very loud. Some noise
21	7:35	GSC	9,580	England	Very loud
22	8:45	LSL	21,160	Argentina, S.A.	Very loud
22	8:50	PH1	17,775	Holland	Very loud, clear and steady
22	9:00	DJD	11,770	Germany	Very, very loud
22	9:15	GBS	12,150	England	Very loud. Working WMA
22	7:20	GSC	9,580	England	Very, very loud and clear
22	7:25	DJA	9,560	Germany	Very loud
22	7:25	DJN	9,540	Germany	Louder than DJA
Oct. 17	7:10	EAQ	9,860	Spain	Very, very loud
17	7:20	W1XAL	6,040	U.S.	Steady, but weak
18	7:20	2RO	9,635	Italy	Very, very loud
21	7:50	CRCX	6,090	Canada	Fair, faded
					Very loud and clear

Edward M. Heiser,
Route 2, Box 124, Brecksville, Ohio.

Report From Walter A. Jasiorowski, 964 West Manitoba St., Milwaukee, Wis.

ALTHOUGH conditions during the month of October were not exactly excellent, 140 short-wave broadcasters were logged.

Europe

SPW, Warsaw, Poland, 13.635 megs.; a new 10-kilowatt station heard testing the first two weeks of October from 11:30 a.m. to 12:30 p.m. with music. Announcements were made by a man, who spoke in Polish, and a woman, who announced in French, English, and German. Reports were requested sent to "Polskie Radio," Warszawa (Warsaw), Poland.

Central America

XEFT, Vera Cruz, Mexico, 6.121 megs.; "La Voz de Vera Cruz." This 20-watter will dedicate a special program to us and the Milwaukee Journal, Nov. 15, 11:30 p.m., since ours was the first report the station had received regarding their short-wave transmissions. They relay XETF daily 7:30 p.m., to 12:30 a.m.

XEUW, Vera Cruz, Mexico, 6.028 megs.: although they announce their frequency as 6.02 megs., the station is actually heard on 6.028 megs. relaying XEU, and both stations at times relay XEW, 7 p.m. to 12:30 a.m.

XIQJ, Mexico City, Mexico, 11.00 megs.: owned and operated by the Bank of Mexico, this 50-watter is heard daily 4 p.m. to 1 a.m. re-broadcasting various long-wave stations. Ricardo Bravo of the old XETE, and operator of Amateur Station XIQ, is chief engineer.

YNL, Managua, Nicaragua, 5.91 megs.; this 100-watter can't make up its mind; heard irregularly 7 to 11:30 p.m. anywhere between 5.88 and 5.99 megs., but lately has settled on 5.91 mc.

TG2X, Guatemala City, Guatemala, 5.94 megs.; "La Voz de Policia Nacional," heard irregularly between 7 and 12 midnight.

TGW, Guatemala City, Guatemala, 6.00 megs.; "Radiodifusora Nacional"; power 200 watts, heard Sundays 2 to 4 a.m.

HRN, Tegucigalpa, Honduras, 5.875 megs.; "La Voz de Honduras" is a new one heard daily 8-10 p.m. and Sundays with an English program 10-10:30 p.m.

HRP1, San Pedro Sula, Honduras, 6.038 megs.; this station was heard once on that frequency calling various Latin stations at midnight. Their broadcast schedule is irregular, 7 to 9 p.m.

TIPG, San Jose, Costa Rica, 6.41 megs.; "La Voz de La Victor"; broadcasts daily 6 to 11:15 p.m. with 1 kw. power.

HP5J, Panama City, Panama, 9.61 megs.; "La Voz de Panama"; this station is poor here and is not received on its announced frequency of 9.59 megs. Broadcasts daily 7 to 10:30 p.m.

Lafayette 5 METER Superhet Receiver



6 Tubes

- ★ Using New 954 Acorn Pentode Tubes in R.F. and Autodyne Detector stages.
- ★ Reduced Thermal Noises, Low Noise Level, Increased Sensitivity.

Lafayette engineers offer another scoop in presenting this 5 meter receiver in which the noise level is practically negligible due to the use of the acorn pentode type 954 tubes. Ample gain is provided for reception of all but the weakest signals on loud speaker, while new type high-reduction, noiseless dials are used. Here is a job that will appeal to every amateur, particularly those accustomed to the use of super-regenerative receivers in which "rush" is an outstanding and annoying noise characteristic.

SWYY 21934—Lafayette 5 meter "Acorn" Superhet receiver complete in cabinet less tubes, power supply \$26.50

BRANCHES AT

CHICAGO—901 W. Jackson Blvd.
ATLANTA—430 W. Peachtree St.
NEWARK, N.J.—219 Central Ave.
BRONX, N.Y.—542 E. Fordham Rd.

CLIP & MAIL TODAY

Wholesale Radio Service Co., Inc.
100 Sixth Ave., Dept. SWX-16, N.Y. City

I enclose \$_____ for order described in attached letter. Check here if interested in our Special New Ham Catalog. It's FREE

Name _____

Address _____

City _____ State _____

30-15,000 CYCLES
±1 DB
Alloy Core
MULTIPLE COIL
Hum-Free Construction
AUDIO TRANSFORMERS \$3.75

In Hum-Free Alloy Cases
Single or Push-Pull High and Low Equalizers in Alloy Case
Each net \$1.50
Hum-Proof Alloy Cases75
Filament Transformers. Modulation, Special Coils wound to order. 24 Hour Service.

ALLOY TRANSFORMER CO.
1355 Liberty St., New York City

ARE YOU AN AMATEUR A DEALER SERVICEMAN OR EXPERIMENTER

WE STOCK A COMPLETE LINE OF STANDARD

RADIO EQUIPMENT

1936 catalog on request to those living in Ohio, Pennsylvania, W. Virginia only


CAMERADIO

601-3 GRANT ST., PITTSBURGH, PA. □ 30 TWELFTH ST., WHEELING, W.VA.
Established 1919

RADIO ENGINEERING,

broadcasting, aviation and police radio, servicing, marine radio telegraphy and telephony, Morse telegraph and railway accounting taught thoroughly. Engineering course of nine months' duration equivalent to three years of college radio work. All expenses low. Catalog free. Dodge's Institute, Turner St., Valparaiso, Ind.

Stop!— GREATEST

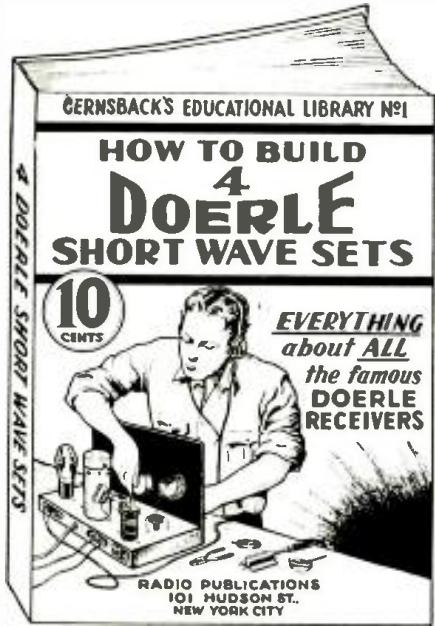

LITERALLY thousands of readers have built the now famous DOERLE Short Wave Radio Receivers. So insistent has been the demand for these receivers that all available literature, including back numbers of SHORT WAVE CRAFT, have long been exhausted.

For the thousands of readers who wish to build any, or all of the many approved DOERLE Short Wave sets, this book has been specially created.

HOW TO MAKE FOUR DOERLE SHORT WAVE SETS

Contains EVERYTHING that has ever been printed on these famous receivers. Four of the most popular sets are described herein. These are the famous sets that appeared in the following issues of SHORT WAVE CRAFT: "A 2-Tube Receiver that Reaches the 12,500 Mile Mark," by Walter C. Doerle (Dec., 1931-Jan., 1932), "A 3-Tube 'Signal Gripper," by Walter C. Doerle (November 1932), "Doerle 2-Tube," Adapted to A. C. Operation," (July 1933), "The Doerle 3-Tube 'Signal-Gripper' Electrified," (August 1933) and "The Doerle Goes Band-Spread," (May, 1934).

Due to a special arrangement with SHORT WAVE CRAFT, we now present complete, as well as compact 32-page book with stiff covers, printed on an extra heavy grade of paper, with numerous illustrations. Nothing has been left out. Not only are all the DOERLE sets in this book, but an excellent power pack if you wish to electrify any of the DOERLE sets, is also described. A wealth of detail is presented in this book despite its ridiculously low price—and, believe it or not, it contains over 15,000 words of legible new type. Everything has been brought up to date; it isn't merely a reprint of what was printed originally, but any improvements on the original sets that were made by readers and various laboratories have been incorporated in this most up-to-date book.

And at the extraordinary price of 10c you cannot possibly go wrong. Despite its low cost, our usual guarantee goes with this book as well.

IF YOU DO NOT THINK THAT THIS BOOK IS WORTH THE MONEY ASKED FOR IT, RETURN IT WITHIN TWENTY-FOUR HOURS AND YOUR MONEY WILL BE INSTANTLY REFUNDED.

There has never been such a wealth of data published in a low-priced radio book of this type in the history of the radio publishing business.

Take advantage of the special offer we are making and use the coupon below.

**RADIO PUBLICATIONS
101 Hudson Street
New York, N. Y.**



RADIO PUBLICATIONS (No. 1) SW-1-36
101 Hudson Street
New York, N. Y.

Please send immediately your book HOW TO MAKE FOUR DOERLE SHORT WAVE SETS, for which I enclose 10c (coin or U. S. stamps acceptable). Book is to be sent prepaid to me.

Name _____
Address _____
City _____ State _____

West Indies

CO9JQ, Camaguey, Cuba, 8.10 mgs.; broadcasts irregularly 8 to 10 p.m. with 150 watts power, should be on 8.665 mgs.

CO9GC, Santiago de Cuba, 6.15 mgs.; this station not often heard because of its wavelength, which coincides with that of W8XK. Heard here 6 to 8:30 p.m.

HJ1J, San Pedro Macoris, D.R., 5.865 mgs.; heard irregularly between 6 and 9 p.m. on its normal frequency; this station was formerly on 5.78 and gives its power as 42 watts.

HJ1A, Santiago de los Caballeros, 6.16 mgs.; another one of those Latins with the ethereal wanderlust has settled on 6.16 mgs. but should be on 6.188 mgs.; this 50-watt heard here irregularly 5:10 to 10:40 p.m.

South America

HJ1ABC, Quibdo, Colombia, 6.008 mgs.; "La Voz de Choco"; heard irregularly 8 to 11 p.m. HJ1ABJ, Santa Marta, Colombia, 6.006 mgs.; "La Voz de Santa Marta"; daily except Sundays 6 to 11 p.m. Announced power as 600 watts.

HJ4ABC, Pereira, Colombia, 6.08 mgs.; this station is now heard daily 7 to 9:30 p.m. but interference is noted from W9XAA.

HJ4ABD, Medellin, Colombia, 5.76 mgs.; originally on 6.06 mgs. this station shifted to 5.76 and is heard daily 6 to 11 p.m.

HJ4ABJ, Ibagué, Colombia, 6.46 mgs.; "Ecos del Combeime," heard daily 8 to 10:30 p.m.

HJ2ABD, Bucaramanga, Colombia, 5.98 mgs.; this is a new station heard testing between 10 p.m. and 1 a.m.

HJ5ABC, Cali, Colombia, 6.155 mgs.; daily 7 to 10 p.m.; styled "La Voz de Colombia," uses chimes similar to those used by NBC.

YV2RC, Caracas, Venezuela, 5.80 mgs.; a change from 6.112 mgs. was made early in October.

YV8RB, Barquisimeto, Venezuela, 5.88 mgs.; "La Voz de Lara"; this one is heard daily now, 6 to 10:30 p.m.

HCTD, Ambato, Ecuador, 7.27 mgs.; heard broadcasting irregularly at 10 p.m.

HC2CW, Guayaquil, Ecuador, 8.30 mgs.; "Ondas del Pacifico"; this station was originally heard on 8.62 mgs. but slipped down to 8.30 and is heard daily 8 to 11 p.m.

HICB, Quito, Ecuador, 8.46 mgs.; "La Voz de los Andes" also got the "bug" and shifted to 8.16 mgs. from 8.214; heard daily ex. Mondays 7:30 to 11 p.m.

PRA8, Pernambuco, Brazil, 6.05 mgs.; "A Voz do Norte" which is supposed to be on 6.04 is now on 6.05 daily 4:30 to 8:30 p.m.

CEC, Santiago de Chile, 10.67 mgs.; this 2-kilowatt now broadcasts daily 7:15 p.m. and also Thursdays and Sundays 8:30 to 9 p.m.

Asia

JVN, Tokio, Japan, 10.66 mgs.; now broadcasts daily 12 to 1 a.m. with English announcements; fairly good here.

JVM, Tokio, Japan, 10.74 mgs.; broadcasts Thursdays and Mondays 4 to 5 p.m. simultaneously with JVP, 7.51 mgs.; received here well.

JVT, Tokio, Japan, 6.75 mgs.; now broadcasting mornings 2:15 to 7:40 a.m. in place of JVM; fairly good here.

JVI, Tokio, Japan, 14.60 mgs.; heard testing several times at 9 p.m. but very weak.

PLP, Bandung, Java, 11.00 mgs.; and PMN, Bandung, 10.26 mgs., are both heard Sunday mornings 4:30 to 8 a.m.

ZBW, Hongkong, China, 8.75 mgs.; extremely weak here, this station shows signs of improving as winter approaches; heard irregularly 5 to 8 a.m.

North America

KIO, 11.68 mgs., and KKH, 7.52 mgs., Kauai, Hawaii; these stations were as strong as "locals," relaying special programs to CBS Monday nights.

Frank Hogler, Brooklyn, N.Y., Reports
HAS3—15.370 and HAT4—9.125 kc., Budapest, Hungary, is heard fine lately. Sundays 9 to 10 a.m. and 6 to 7 p.m. E.S.T. respectively.

HBL—955 kc., Geneva, Switzerland, is heard broadcasting to Australia around midnight, Sundays.

KTO—18.450 kc., Manila, Phillipines, was heard calling and testing with Tokyo, Japan, around 6:15 to 7 p.m. E.S.T.

Most South American stations are coming in fine, as soon as it gets dark; that's around 5.500 kc. to 7.400 kc.

Frank Hogler,
222 Wyckoff Ave.,
Brooklyn, N.Y.

"Listening In" at Freeport, Pa.

TIGP, 6.40 meg., puts in a very nice signal schedule, 8:30 p.m. to 11:30 p.m., E.S.T.

DJC, 6.02 meg., and HJ3ABH, 6.01 meg., cause heterodyne whistles on each other. At times neither one can be heard on account of their wave-lengths being about the same.

YVQ, 6.67 meg., is heard very well Saturdays; schedule is 8 to 8:30 p.m. Saturdays, but they may be heard before, and after the said time.

HHI, 6.81 meg., is operating on a new schedule. Daily 7:30 to 9:00 p.m. Sundays 3 to 4 a.m. and 4:15 to 6:00 p.m.

TIRCC, the only Catholic stations in Costa

Look!! 10c BOOKS



There has been a continuous demand right along for a low-priced book for the radio experimenter, radio fan, radio Service Man, etc., who wishes to build 1- and 2-tube all-wave sets powerful enough to operate a loudspeaker. Sets of this type are always intensely popular with all classes of people who not only wish to amuse themselves to see how good a set they can build with a single or two tubes, but frequently such sets are important for special purposes, particularly where space is at a premium. For the thousands of readers who wish to build such sets, this book has been especially published.

HOW TO MAKE THE MOST POPULAR ALL-WAVE 1. and 2-TUBE RECEIVERS

This book contains a number of excellent sets some of which have appeared in past issues of RADIO-CRAFT, and have been highly successful. These sets are not toys but have been carefully engineered. They are not experiments. To mention only a few of the sets the following will give you an idea.

• The Megadyne 1-Tube Pentode Loud-speaker Set, by Hugo Gernsback. • Electrifying the Megadyne. • How to Make a 1-Tube Loud-speaker Set, by W. P. Chesney. • How to Make a Simple 1-Tube All-Wave Electric Set, by W. Green. • How to Build a Four-In-Two All-Wave Electric Set, by J. T. Bernsley, and others. Not only are all of these sets described in this book, but it contains all of the illustrations, hookups, etc.—the book, in fact, contains everything. Nothing at all has been left out. A wealth of important detail is presented in this book that will make you wonder how we can do it at the price.

Believe it or not, the book contains over 15,000 words of new legible type. The book is thoroughly modern and up-to-date. It isn't just a reprint of what was printed before. All the latest improvements have been incorporated into the sets.

Remember that this book sells at the extraordinary low price of ten cents; you can not possibly go wrong in buying it. Despite its low cost, our usual guarantee goes with this book as well!

IF YOU DO NOT THINK THAT THIS BOOK IS WORTH THE MONEY ASKED FOR IT, RETURN IT WITHIN TWENTY-FOUR HOURS AND YOUR MONEY WILL BE INSTANTLY REFUNDED.

There has never been such a wealth of data published in a low-priced radio book of this type in the history of the radio publishing business.

Take advantage of the special offer we are making and use the coupon below.

**RADIO PUBLICATIONS
101 Hudson Street
New York, N. Y.**

RADIO PUBLICATIONS (No. 2) SW-1-36
101 Hudson Street
New York, N. Y.

Please send immediately your book "HOW TO MAKE THE MOST POPULAR ALL-WAVE 1- AND 2-TUBE RECEIVERS," for which I enclose 10c (coin or U. S. stamps, acceptable). Book is to be sent prepaid to me.

Name _____
Address _____
City _____ State _____

Save \$1.98

Just as Long as the Supply
Of This Book Lasts!

THE ONE AND ONLY ENCYCLOPEDIA on SHORT WAVES

By C. R. Leutz and R. B. Gable

384 Pages — Over 345 Illustrations
Bound handsomely in red linen. Stiff covers. Size 6x9"

"**SHORT WAVES**" is written by Leutz and Gable, two foremost radio authorities. You will remember Charles R. Leutz as one of the pioneers in radio, also designer and manufacturer of the famous LEUTZ Transoceanic Receivers. Mr. Robert Gable owned and operated one of the finest low power broadcasting stations in the country. He is well known as an experimenter and research worker in scientific fields.


Considering the value of this book for data alone, its cost should really be more than originally asked. But when you see the illustrations in the book you will marvel at how this book could be sold for **ONE DOLLAR**. It originally sold for \$2.98.

The book is printed on a very expensive super-calendared paper. It contains 384 pages with over 345 photoreducible illustrations and diagrams. The supply of these books is not expected to last long. Once they are gone no additional copies will be available. ORDER NOW—be sure to tell your friends about this remarkable book value. Send the coupon today for your copy of "**SHORT WAVES**" by Leutz and Gable.

**345 Photographic
Illustrations**

384 Pages

This book
originally sold
for \$2.98

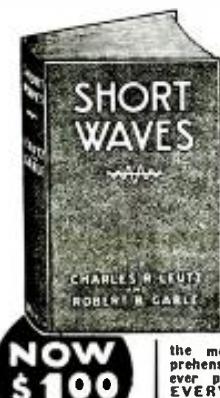

NOW
\$1.98

The most important and comprehensive volume of short-waves ever published. This book has EVERYTHING on short-waves—it literally contains a complete education on short-waves.

Partial Contents of
"SHORT WAVES"

HISTORICAL REVIEW
SHORT WAVE PROPAGATION
COMMERCIAL RADIO TELEPHONY
AND TELEGRAPHY
SHIP TO SHORE RADIO TELEPHONY
DIRECTIONAL ANTENNAE
TELEVISION
AIRCRAFT RADIO EQUIPMENT
SHORT WAVE BROADCAST RECEIVERS
ULTRA SHORT WAVES (Medical and Surgical Applications)
AMATEUR SHORT-WAVE EQUIPMENT

Don't forget that this comprehensive volume is sold on a MONEY-BACK GUARANTEE. If you are not satisfied with it, return it within three days for refund. Use the coupon below for ordering your copy of "**SHORT WAVES**" by Leutz and Gable.

RADIO PUBLICATIONS
103 Hudson St. New York, N. Y.

MAIL COUPON TODAY!

RADIO PUBLICATIONS, Dept. SWC-1-36
103 Hudson Street, New York, N.Y.

Gentlemen: Enclosed you will find my remittance of One Dollar (\$1) (cash, money order or cashier's check, U. S. money) for which send me one copy of "**SHORT WAVES**". I understand that if I am not completely satisfied and my money refunded.

NAME _____

ADDRESS _____

CITY _____ STATE _____
(Include 15c extra to cover mailing charges; 25c foreign countries)

Rica, on 6.55 meg., and HII4D, 6.61 meg. interfere with each other very much.

CO9GC, 6.15 meg., is always heard very good. HJ4ABD, 6.05 meg., and W8XA1, 6.06 meg., interfere with each other sometimes, mostly at from 6 to 7 p.m. 2V8XAL cannot be heard; covered up entirely by HJ4ABD.

HIZ, on 6.31 meg., is heard very well. Tune for them on Saturdays, 10:40 to 11:10 p.m.

YV2RC is operating on 5.80 meg. The change is for the better; their old wavelength was pretty crowded; the new wavelength is heard fine.

IQ4, Italy, on 14.6 meg. may be heard around 3 p.m. sending music for Buenos Aires.

A new Mexican station, XBJQ, is operating on about 11.12 meg.

Radio Colonial on 15.25 meg. is now coming in fine.

HAS3, 15.37 meg., and HAT4, are heard fairly well on Sundays.

ZRO, Rome, Italy, on 9.61 meg., now broadcasts a "news" bulletin every night at 6 p.m.. except Sundays.

RIM, 15.25 meg., has been phoning almost every morning until 7 a.m.

RKI, 15.04 meg., has been relaying programs to N.B.C. on Sundays, irregular.

YVR, 18.30 meg., may be heard phoning DFB, 17.52 meg., at about 10 a.m., nearly every morning.

DJE on 17.76 meg., is being heard better now that the weather is getting colder.

VK2ME, 9.59 meg., is very fine till 8:30 a.m. Sundays.

Angelo Centanino,
Box 516,
Freeport, Pa.

Report from Rhode Island

● THE stations heard on 19 meter band are: PCJ, Holland; GSF, England; HVJ, Vatican City, Italy; ZRO, Rome, Italy; DJB, Germany; WNC, Hialeah, Fla.

On 25 meters, RNE, Russia; W8XK, Pittsburgh, Pa.; W2XE, New Jersey; GSE, and GSD, England.

On 31 meters, EAQ, Madrid, Spain; W3XAU, Philadelphia, Pa.; ZRO, Rome, Italy; DJA, Germany; GSB, England; VK2ME, Sydney, Australia; CTIAA, Lisbon, Portugal; HBL, Switzerland; T1RA, Costa Rica.

On 49 meters, CJRO, Winnipeg, Can.; VE9HX, Halifax, Nova Scotia; W9XF, Illinois; W9XAA, Chicago, Ill.; H54ACB, Colombia, S.A.; HJ4ABB, Colombia, S.A.

Spencer E. Lawton,
15 Hillside Ave.,
Westerly, R.I.

News from Tulsa, Okla.

● LISTENING here at this post has been very good for the past month. All of the European "locals" heard daily if tuned for. I wish to say in particular that GSB 9.51 mc. and GSD 11.75 mc. may be heard extra good here at 2:15 a.m., E.S.T. for an hour or two, especially GSB. Also DJA at 1:30 a.m., E.S.T., may be heard fairly good sometimes. ORK Brussels, heard a number of times on 10.33 mc. at 2:30 p.m., good signal. HAT4, Budapest, heard on Sundays at 6 to 7:00 p.m., E.S.T. EAQ, Madrid, Spain, is now heard on the air as late as 9:30 p.m., E.S.T. RIO, Bakou, U.S.S.R., phone heard at 11:00 p.m. to 12:00 midnight. They call Moscow at this time. TYA, Paris, 12.22 mc. irregular during the day, calling the S.S. Normandie.

Asia

JVF, Nazaki, Japan, 15.61 mc., 9:00 p.m., E.S.T.—Good signal.

JVM, Nazaki, Japan, 10.74 mc., 11:30 p.m., E.S.T.—Good signal.

JVN, Nazaki, Japan, 10.66 mc., 12:05 a.m., E.S.T.—Good signal.

KTO, Manila, P.I., 16.24 mc., 6:55 p.m., E.S.T.—Fair signal.

PLE, Bandoeng, Java, 18.83 mc., 7:30 p.m., E.S.T.—Fair signal.

Australia

VK2ME, Sydney, on 9.59 mc. Sunday morning 12:00 to 2:00 a.m., E.S.T.

VLK, Sydney, on 10.52 mc. heard most any time after 1:00 a.m., E.S.T.

VK3LR, Melbourne, 2:00 a.m. and irregular after 12:00 a.m., E.S.T.

Africa

SUV, Cairo, Egypt, 10.04 mc. irregular during the afternoon.

North America

WVD, Seattle, Wash., irregular during the evenings and early a.m. It is on 8.66 mc. Strong signal. This station is a U.S. Army signal station. XBJQ, a new station in Mexico City, heard on 11.00 mc. The address of this station is P.O. Box 2825.

W10XL, ground station of "stratosphere" flight, was picked up here on about 47 meters at 5:45 p.m., E.S.T., one afternoon.

CO9JQ, Camaguey, Cuba, on 8.65 mc. A new Cuban station, received very good.

South America

HP5J, Panama City, 5.59 mc.; YV5RMO, Maracaibo, Ven.

HJ4ABE, Medellin, Colombia.

CEC, Santiago, Chile.

LSN-LSX, IIJB and others received O.K.

Wade Chambers,
Tulsa, Okla.

"Pleased"

with the Hi-Fidelity
of the Model 1750—the
Reproducer with the New



It's What OTHERS say
that COUNTS!

Read the following letter:

Pass Christian, Miss., Oct. 14, 1935

"Gentlemen:

Recently I received one of your new No. 1750 Para-Curve Reproducers and I am more than pleased with its Hi-Fidelity performance. Please rush 1 Model 1750 to match a new Philco Model 650X."

Eldridge A. Helwick.

\$17.50
LIST

Write for complete catalog, dealer's discount and name of nearest distributor. Wright - DeCoster distributors are always anxious to cooperate with you.

**WRIGHT-
DECOSTER,
Inc.**

Model 1750
12" Reproducer
2257 University Ave.,
St. Paul, Minn.

PHILA.'S SHORT WAVE HEADQUARTERS

We carry a complete line of parts for all the new short wave circuits appearing in this magazine and other periodicals.



IN STOCK
THE NEW

PATTER-
SON
PR-16

16-TUBE
SUPERHET

— ALSO —

National HRO
Sargent Marine
All Wave Model
New Silver
9 to 200 meter super.
All Star Jr. & Sr.
Service Instruments

Browning 35

Hammarlund

Thordarson

Triplett & Dayrad

Service Instruments

M & H Sporting Goods Co.
512 MARKET ST. PHILADELPHIA

ASTATIC

THE QUALITY CRYSTAL MICROPHONE



Noted for quality, dependability, ruggedness and performance. A professional microphone at an amateur price and fully guaranteed. Modernize your transmitter. See your jobber today!

Licensed under Brush Development Co. patents.

ASTATIC MICROPHONE LAB., INC.
YOUNGSTOWN, OHIO

"Pioneer Manufacturers of Quality Crystal Devices"

Please mention SHORT WAVE CRAFT when writing advertisers

Police Radio Alarm Stations

(Continued from page 544)

WPFL	Gary, Ind.	2470 kc.
WPFM	Birmingham, Ala.	2382 kc.
WPFN	New Bedford Mass.	1712 kc.
WPFO	Knoxville, Tenn.	2474 kc.
WPFP	Clarksburg, W. Va.	2490 kc.
WPFQ	Swarthmore, Pa.	2474 kc.
WPFR	Johnson City, Tenn.	2470 kc.
WPFS	Asheville, N.C.	2474 kc.
WPFT	Lakeland, Fla.	2442 kc.
WPFU	Portland, Me.	2422 kc.
WPFV	Pawtucket, R.I.	2466 kc.
WPFW	Bridgeport, Conn.	2466 kc.
WPFX	Palm Beach, Fla.	2442 kc.
WPFY	Yonkers, N.Y.	2442 kc.
WPFZ	Miami, Fla.	2442 kc.
WPGA	Bay City, Mich.	2466 kc.
WPGB	Port Huron, Mich.	2466 kc.
WPGC	S. Schenectady, N.Y.	1658 kc.
WPGD	Rockford, Ill.	2458 kc.
WPGF	Providence, R.I.	1712 kc.
WPGG	Findlay, Ohio	1596 kc.
WPGH	Albany, N.Y.	2414 kc.
WPGI	Portsmouth, Ohio	2430 kc.
WPGJ	Utica, N.Y.	2414 kc.
WPGK	Cranston, R.I.	2466 kc.
WPLG	Binghamton, N.Y.	2442 kc.
WPGN	South Bend, Ind.	2490 kc.
WPGO	Huntington, N.Y.	2490 kc.
WPGP	Muncie, Ind.	2442 kc.
WPGQ	Columbus, Ohio	1596 kc.
WPGS	Mineola, N.Y.	2490 kc.
WPGT	New Castle, Pa.	2482 kc.
WPGU	Cohasset, Mass.	1712 kc.
WPGV	Boston, Mass.	1712 kc.
WPGW	Mobile, Ala.	2382 kc.
WPGX	Worcester, Mass.	2466 kc.
WPGZ	Johnson City, Tenn.	2474 kc.
WPHA	Fitchburg, Mass.	2466 kc.
WPHB	Nashua, N.H.	2422 kc.

WPHC	Massillon, Ohio	1596 kc.
WPHD	Steubenville, Ohio	2458 kc.
WPHE	Culver, Ind.	1634 kc.
WPHF	Richmond, Va.	2150 kc.
WPHG	Medford, Mass.	1712 kc.
WPHI	Charleston, W. Va.	2190 kc.
WPHJ	Fairmont, W. Va.	2490 kc.
WPHK	Wilmington, Ohio	1596 kc.
WPHL	Portable in Ohio	1682 kc.
WPHM	Orlando, Fla.	2442 kc.
WPHN	Tampa, Fla.	2466 kc.
WPHO	Zanesville, Ohio	2430 kc.
WPHP	Jackson, Mich.	2466 kc.
WPHQ	Parkersburg, W. Va.	2190 kc.
WPHS	Culver, Ind.	1634 kc.
WPHT	Cambridge, Ohio	1596 kc.
WPHU	Jasper, Ind.	1634 kc.
WPHV	Bristol, Va.	2450 kc.
WPHY	Elizabethhton, Tenn.	2174 kc.
WPHZ	Oil City, Pa.	2482 kc.
WPSP	Harrisburg, Pa.	1674 kc.
WQFA	New Haven, Conn.	2496 kc.
WQFB	Macon, Ga.	2414 kc.
WQFC	Gainesville, Fla.	2466 kc.
WQFD	Columbia City, Ind.	1534 kc.
WQFE	Seymour, Ind.	1634 kc.
WQFF	Monessen, Pa.	2482 kc.
WQFG	Roanoke, Va.	2450 kc.
WQFH	Lynchburg, Va.	2450 kc.
WQFI	Petersburg, Va.	2450 kc.
WQFJ	Oneonta, N. Y.	2414 kc.
WQFK	Clearwater, Fla.	2466 kc.
WQFM	Wilkes-Barre, Pa.	2442 kc.
WQFN	Winter Haven, Fla.	2442 kc.
WQFO	Lancaster, Ohio	2430 kc.
WQFP	Springfield, Ill.	1610 kc.
WQFQ	Lafayette, Ind.	2442 kc.
WQFR	Portable, N. Y.	1658 kc.
WQFS	Hibbing, Minn.	2382 kc.
WQFT	Portable, Ohio	1596 kc.
WQFU	Sharon, Pa.	2482 kc.
WQFV	Augusta, Ga.	2414 kc.
WRBH	Cleveland, Ohio	2458 kc.
WRDQ	Toledo, Ohio	2474 kc.
WRDR	Grosse Pt. Village, Mich.	2414 kc.
WRDS	E. Lansing, Mich.	1642 kc.
W1XAO	Boston, Mass.	1712 kc.

Television Stations

(Continued from page 544)

VE9AU	2000-2100 kc.
VE9DS	London, Ont., Can.
W2XDR	Montreal, Que.
W8XAN	Long Island City, N.Y.
W9XK	Jackson, Mich.
W9XAK	Iowa City, Iowa
W9XAO	Manhattan, Kans.
W6XAH	Chicago, Ill.
	71 PM Tues. 1/26
	Bakersfield, Calif.
	2750-2850 kc.
W3XAK	Portable
W9XAP	Chicago, Ill.
W2XBS	Bellmore, N.Y.
W9XAL	Kansas City, Mo.
W9XG	W. Lafayette, Ind.
W2XAB	New York, N.Y.
VE9AR	Saskatoon, Sask., Can.
VE9ED	Mt. Joli, Que., Can.
	42000-56000, 60000-86000 kc.
W2XAX	New York, N.Y.
W6XAO	Los Angeles, Calif.
W9XD	Milwaukee, Wis.
W2XBT	Portable
W2XF	New York, N.Y.
W3XE	Philadelphia, Pa.
W3XAD	Camden, N.J.
W10XX	Portable & Mobile (Vicinity of Camden)
W2XDR	Long Island City, N.Y.
W8XAN	Jackson, Mich.
W9XAT	Portable
W2XD	New York, N.Y.
W2XAG	Portable
W1XG	Boston, Mass.
W9XK	Iowa City, Iowa
VE9BZ	Vancouver, B.C., Can.
VE9DS	Montreal, Que., Can.
VE9AU	London, Ont., Can.
VE9RC	Quebec, Que., Can.
VE9AG	Walkerville, Ont., Can.

NOW READY!



\$2.50

SHORT WAVE CRAFT
99 Hudson Street
New York, N. Y.

SWC-1-36

Gentlemen: I enclose herewith my remittance of \$2.50 for which please send me one copy of the 1935 OFFICIAL SHORT WAVE RADIO MANUAL. (Send remittance, check or money order. Register letter if it contains cash or currency.)

Name _____
Address _____
City _____ State _____

Volume Two (1935 Edition) of the Official Short-Wave Radio Manual

There has been tremendous progress and a great boom in short waves in the past year, and the art has made such rapid progress that no single book, up to now, has been able to keep up with this progress. The 1935 OFFICIAL SHORT WAVE RADIO MANUAL fills this need, and it fills it completely. All the progress made in short waves, whether it is in set building, whether it is in radio servicing, whether it is in new models, whether it is in new short wave discoveries, all are faithfully reported and chronicled in this great 1935 volume. Similar to last year's volume, the new book has been edited by Hugo Gernsback, Editor of SHORT WAVE CRAFT and H. W. Secor, Managing Editor.

Here are the star features of the book:

29 ★ FEATURES

- ★ 1—Short-Wave Beginners' Section—Illustrations of new simplified circuits for 1-2 and 3-tube receivers, including famous "Dooley" and "Oscillodynes," etc.
- ★ 2—Short Wave Receivers—All types discussed with diagrams, new and improved. The best types only, which have "stood the test" of actual operating service. Full details for constructing them, etc.—"Broad-Spread" the Dooley, 8-tube T.R.F. Receiver, etc.
- ★ 3—Battery Short-Wave Receivers—1-2 & 3 tube sets—The way up to special 5-tube superheterodyne, designed especially for battery sets.
- ★ 4—"5-Meter" Department—All the latest "dope"—including newest transmitters, "Long Line" oscillators, improved "high sensitivity" receivers, 5-meter transceivers, hook-ups, etc.
- ★ 5—grids—New circuits, new types—The best types only, which have "stood the test" of actual operating service. Full details for constructing them, etc.—"Broad-Spread" the Dooley, 8-tube T.R.F. Receiver, etc.
- ★ 6—Short-Wave "Artificial Fever" Apparatus—Alps, newest therapeutic and other allied applications of ultra short waves.
- ★ 7—Short-Wave Experimenter's Section—Filled with Short-Wave Kinks, Short-cuts, etc., of interest to every experimenter.
- ★ 8—Ultra Short Waves—Newest circuits, apparatus, and results obtained in this field.
- ★ 9—Commercial "Short-Wave" and "All-Wave" Receivers—New Servicing Data for "Set-Owners" and "Servicemen."
- ★ 10—How to build "Power Supply" Units for Short-Wave Receivers.
- ★ 11—Latest Short-Wave Converters—With servicing data on Commercial Models.
- ★ 12—The Short-Wave Antenna—Including latest "Noise Reduction" types, Transposed Lead-in systems, shielded cable, Double-wire, etc.
- ★ 13—Short-Wave Superheterodynes—From 3 to 11 tubes—Latest descriptions and diagrams including commercial all-wave superhet.
- ★ 14—Phone Transmitters for Amateur Stations—How to build them.
- ★ 15—"Skip" Distance—Heaviside layer, etc.—Explained, physics of short waves.
- ★ 16—Recording "Foreign" and "Domestic" Short-Wave programs—All systems in use.
- ★ 17—"High Fidelity"—How to obtain it in Short-Wave Receivers.
- ★ 18—The best Short-Wave Questions and answers of the year.
- ★ 19—The best Short-Wave "Kinks" of the year.
- ★ 20—"Foreign" Short-Wave Review—Novel circuits, apparatus, etc.
- ★ 21—Tubes for Short-Wave purposes—Including tables of latest tubes for Short-Wave transmitters and Receivers.
- ★ 22—Short-Wave Transmitters—All about the new "Long Line" Oscillators and others.
- ★ 23—Multi-Power Receivers—How to use them on Short-Wave Sets in which 2 tubes equal 4, etc.
- ★ 24—"Audio Amplifiers" for Short-Wave Receivers. Circuits, etc.
- ★ 25—"Band-Spread"—How to spread the stations over the dial for easier tuning.
- ★ 26—"Plug-less "Mono-Coll" Receivers—How to build them, how to use them, how to eliminate plug-in coils, "Clip-Coll" Receivers, etc.
- ★ 27—"Boosters, Pre-amplifiers and Beat Oscillators—How they work, with constructional data, diagrams, etc.
- ★ 28—"Portable Short-Wave Receivers and Transmitters—Transmitter Power supply from Ford Coils, etc.

AND FOR SERVICE MEN

★ 29—Every short-wave diagram, every short-wave set, whether it is an all-wave set, whether it is an all-short wave set, EVERYTHING, in other words, that has been manufactured in the commercial set line, will be found in this special enlarged section.

OVER 1000 ILLUSTRATIONS

Size 9x12 inches—Flexible Looseleaf Leatherette Binder


SHORT WAVE CRAFT

NEW YORK, N.Y.

MAIL COUPON AT LEFT FOR YOUR COPY

Please mention SHORT WAVE CRAFT when writing advertisers

INVALUABLE

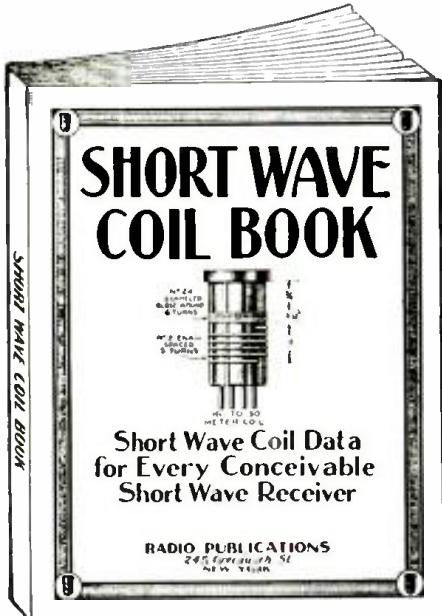

SHORTWAVE SET BUILDERS MUST HAVE THIS BOOK

FOR the first time, it is now possible for the experimenter and short wave enthusiast to obtain the most exhaustive data on short wave coil winding information that has ever appeared in print.

As every experimenter who has ever tried to build a short wave set knows only too well by experience, the difference between a good and a poor receiver is usually found in the short wave coils. Very often you have to hunt through copies of magazines, books, etc., to find the information you require. The present data has been gotten up to obviate all these difficulties.

Between the two covers of this book you now find every possible bit of information on coil winding that has appeared in print during the past two years. Only the most modern "dope" has been published here.

No duplication. Illustrations galore, giving not only full instructions how to wind coils, but dimensions, sizes of wire, curves, how to plot them, by means of which any coil for any particular short wave set can be figured in advance, as to number of turns, size of wire, spacing, etc.

There has never been such data published in such easy accessible form as this.

Take advantage of the special offer we are making today, as due to increasing costs, there is no question that the price will increase soon.

RADIO PUBLICATIONS
97 HUDSON STREET
NEW YORK, N.Y.

Radio Publications
97 Hudson Street.
New York, N.Y.

Please send immediately your Short Wave Coil Book, for which I enclose 25c herewith (coin, U. S. stamps or money order acceptable). Book is to be sent prepaid to me.

Name _____

Address _____

City and State _____

Short Waves and Long Raves

(Continued from page 529)

I wish to advise you of the results I have received with it.

The first station I received with it was COC, Havana, Cuba; DJC, Berlin, Germany; 12RO, Rome, Italy; HI5B, Panama City, Panama; GSA, Daventry, England; YV2RC, Caracas, Venezuela; CJRX, Winnipeg, Canada; YV5RMO, Maracibo, Venezuela; XEBT, Mexico City, Mexico; WOB, Lawrenceville, N.J.; W1XAL, Boston, Mass.; W2XE, New York; W9XAA, Chicago, Ill.; CRCX, Bowmanville, Canada; W3XAL, Bound Brook, N.J.; W8XK, Pittsburgh, Pa. on two bands, W2XAF, W3XAU on two bands, W9XF, Chicago, Ill.; and many Spanish stations which I could not identify.

Not bad, eh? More luck to your magazine, and wish you would have more like it. And thanks for printing descriptions of such excellent sets as the Doerle.

AMBROSE McMULLEN,
567 Querbes Ave.,
Montreal, Quebec, Canada.

(Fine business, Ambrose, and your Doerle D.C. 2-tuber is certainly performing in fine shape. We presume that by this time you have rolled up quite an astonishing "log" of foreign as well as home stations.—Editor)

2.5 and 5-Meter Superhet


(Continued from page 533)

receiver unit is built onto a copper-plated chassis measuring only 11x7½x9 inches. No power supply is included, as the same receiver chassis is designed for operation either on a 6-volt storage battery and dry "B" batteries or an A.C. power supply unit delivering 6.3 volts for the filament and up to 300 volts for the plate.

To simplify the arrangement of the parts and to eliminate trimming and aligning troubles, separate controls are provided for the radio frequency and detector stages, according to its designer, Frank Lester, W2AMJ, engineer of the Wholesale Radio Service Co. While the R.F. stage does not provide a great deal of amplification, it does decidedly improve the signal to noise ratio, and more important, it eliminates receiver radiation and dead-spots in the detector tuning due to antenna absorption. Tiny plug-in coils, only one-half inch in diameter, are provided for the two and one-half and five-meter bands.

Long Distance on 7.5 Meter Waves

IT has recently been reported that communications have been held between Washington, D.C. and battleships off the coast of California on 7.5 meters. This is probably the longest ultra high-frequency actual QSO (contact) that has taken place. This only goes to show that one never can tell just what is going to happen on these ultra short waves. It seems that each day brings new developments, tending to outlaw the quasi-optical theory, i.e., the rule that ultra short wave transmitting and receiving stations should be erected so as to be within sight of one another. It is reported that the 7 meter television station in Berlin has been picked up in America. The 7 meter harmonic of the B.B.C. 14 meter wave station in England was heard in Buenos Aires, S.A., a distance of about 7000 miles, according to one report. Just how far these ultra short waves can be relied upon for regular long distance transmission can only be ascertained after more extensive tests.

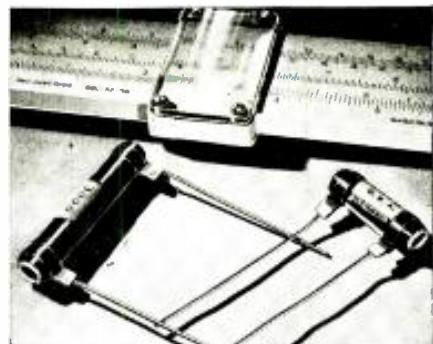

PYROHM Jr. RESISTORS



Genuine wire-wound vitreous-enamel resistors. Most compact. 5, 10, 15 and 20 watt ratings. All resistance values. For midget sets and crowded assemblies. For stay-put servicing.

Crack-proof refractory Wire ends brazed to tubing. Adequate heat dissipation.

Quality resistance wire. Heavy vitreous enamel coating. Permanent seal Space wound under against moisture and damage.

DATA Send for new catalog covering complete condenser and resistor line. Also largest listing of exact duplicate replacements. Sample copy of Research Worker included.



72 Washington St. Brooklyn, N.Y.

"CHI-RAD"

More for your old S.W. receiver in a trade at Chi-Rad
Panels, Racks, Chasses and Cabinets. We specialize in S.W. Supplies of every description

Get a copy of "The Morse Code" free on request at our store.

CHICAGO RADIO APPARATUS COMPANY, Inc.

Amateur Sta. W9RA-W9PST
415 South Dearborn Street
(Near Van Buren Street)

Est. 1921 CHICAGO



Write for CHART CV.


AMPERITE Co. 561 BROADWAY NEW YORK

QUICK WAY to make money in RADIO

Modern receivers are demanding men with modern training for service work. New training method and service equipment offer starts you earning almost at once. Up to \$3 an hour easy in a short time. Write today for FREE book of details.

Radio Training Association of America
Dept. S.W.C.-61
4525 Ravenswood Ave., Chicago

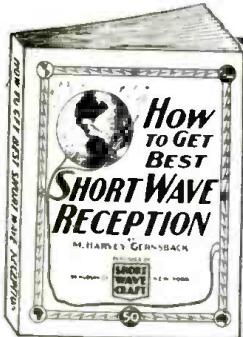Without doubt you will have to go a long way to buy better books on short waves than you find on this page. Each book is written by a well-known authority on short waves . . . each book has been carefully illustrated with photographs and diagrams to



How to Get Best Short-Wave Reception

By M. HARVEY GERNSBACK

This book tells you everything you ever wanted to know about short-wave reception.

The author, a professional radio listener and radio fan for many years, gives us his long experience in radio reception and tells that goes with it.

Why is one radio listener enabled to pull in stations from all over the globe, even small 100 watters, 10,000 miles away, and why is it that the next fellow with a much better and more expensive equipment can hardly receive the powerful stations that any child can get without much idea?

The reason is intimate knowledge of short waves and how they behave. Here are the chapters of this new book:

1. What Waves and what can the Listener hear on a short-wave receiver.
2. How to tune and when to listen in on the short waves.
3. How to identify short-wave stations.
4. Seasonal changes in short-wave reception.
5. Types of receivers for short-wave reception.
6. Aerial systems for short-wave receivers.
7. Verifications from short-wave stations.

The book makes excellent reading matter. There are many tricks in short-wave reception that even some of the "old-timers" do not know. Be sure to get it.

40 Illustrations, 72 Pages.
Stiff, flexible covers

50c

HOW TO BUILD AND OPERATE SHORT-WAVE RECEIVERS

THIS is the best and most up-to-date book on the subject. It is edited and prepared by the editors of SHORT WAVE CRAFT, and contains a wealth of material on the building and operation, not only of typical short-wave receivers, but short-wave converters as well. Dozens of short-wave sets are found in this book, which contains hundreds of illustrations; actual photographs of sets built, hookups and diagrams galore.


This book is sold only at a ridiculously low price because it is our aim to put this valuable work into the hands of every short-wave enthusiast.

We know that if you are at all interested in short waves you will not wish to do without this book. It is a most important and timely radio publication.

150 Illustrations, 72 Pages.
Stiff, flexible covers

50c

THE SHORT-WAVE BEGINNER'S BOOK

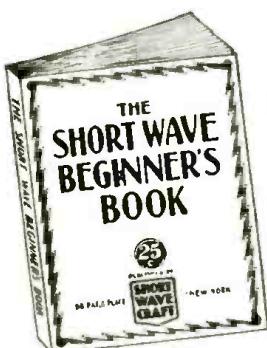

Partial List of Contents

Getting Started in Short Waves—the fundamentals of electricity. Symbols, the Short Hand of Radio—how to read schematic diagrams. Short Wave Coils—various types and kinds in making them. Short Wave Aerials—the points that determine a good aerial from an inefficient one. The Transistor Lead-in for reducing static. The Beginner's Short-Wave Receiver—a simple one tube set that anyone can build. How to Tune the Short-Wave Set—telling the important points to get good results. Audio Amplifiers for S.W. Receivers. Lengths of Wires for greater enjoyment with the S.W. set. Wave length to Kilometers Chart. Wire Chart—to assist in the construction of coils.

**25c 75 Illustrations, 40 Pages.
Stiff, flexible covers**

All the books shown on this page are published exclusively by

SHORT WAVE CRAFT

99-101 Hudson Street,
New York, N. Y.

CLIP-MAIL

make the study of this field of radio much simpler. The volumes on this page are the finest books on short-waves which are published anywhere today. Order one or more copies today . . . find out for yourself how fine they are. Prices are postpaid.

101 SHORT-WAVE HOOKUPS


Compiled by the Editors of SHORT WAVE CRAFT

EACH and every hook-up and diagram illustrated is also accompanied by a thorough explanation of what this particular hook-up does. All parts are required, coil-winding information, values of resistors, etc., in fact, everything you want to know in order to build the set or to look up the data required.

The book is the result of a popular note which have appeared in print during the past five years in the column booklets such as the Doerle, Diagonal, the 19-Tube, 10-Tube, Oscillodrome, Denton "Stand-by," Magadine Triplex 2-Tube, Superhet, Mindyne, "Loop" Receiver, "Dove" 2-Tube A.C. Detector, Doerle 3-tube Battery, "Doerte" 2-tube A.C. Detector, Doerle "Signal Gripper," Duo R.F. 4-tube Receiver, The Sargent 9-33 Tapped Coil Receiver, Globe-Girdler 7, The 2-Tube "Giant," Twin Equal 3, Ham-Band "2-Tube Peewee," Wythe All-Around 2-Tube, Economy 2-Tube "Regenerative-Oscillodrome" will be found here, with full descriptions. In many cases we have also included a picture hook-up for those who do not wish to follow the regular symbolic drawing. This book will have a regular wiring diagram.

This is a very handy volume, especially for those "fans" who wish to study the beat sets in the short-wave art, from one tube up to ten tubes.

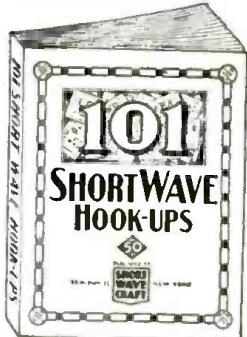**100 Illustrations, 72 Pages, 50c
Stiff, flexible covers**




HOW TO BECOME AN AMATEUR RADIO OPERATOR

We chose Lieut. Myron F. Eddy to write this book because his experience and field work make him pre-eminently qualified in this line. For many years he was instructor of radio telegraphy at the R.C.A. Institute. He is a member of the I.R.E. (Institute of Radio Engineers), also the Veteran Wireless Operators Association.

If you intend to become a licensed code operator, if you wish to take up phone work eventually—this is the book you must get.

Partial List of Contents

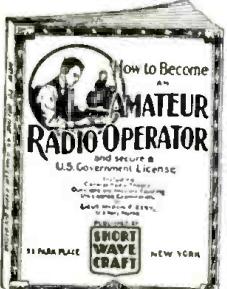

50c 150 Illustrations, 72 Pages, Stiff, flexible covers

TEN MOST POPULAR SHORT-WAVE RECEIVERS

—HOW TO MAKE AND WORK THEM

THE editors of SHORT WAVE CRAFT have selected ten outstanding short-wave receivers and there are described in detail the parts required, the parts required, the complete layout, pictorial representation, photographs of the set complete, hookup and all workable specifications. Everything from the simplest one-tube set to the 10-tube "Giant" is represented. Complete lists of parts are given to make each set complete. You are shown how to operate the receiver to its maximum efficiency.

CONTENTS

The Doerle 2-Tube Receiver that Reaches the 12,500 Mile Mark, by Walter C. Doerle.

The R.F. Pentode S.W. Receiver, having two stages of Tuned Radio Frequency, by Clifford E. Denton and H. W. Secor.

The Myron F. Eddy Receiver, by Edward G. Ingraham.

The Biowave 2-Tube 12,000 M.Hz DX Receiver, by A. Binneweg, Jr.


The Short-Wave Receiver in your "Brief-Case," by Hugo Gernsback.

The Denton "Stand-by," by Clifford E. Denton.

The "COAT-POCKET" Short-Wave Receiver, by Hugo Gernsback and Clifford E. Denton.

The S.W. PENTODE-4, by H. G. Cisner, M. E. Louis Martin's Idea of a GOOD S.W. RECEIVER, by Louis Martin.

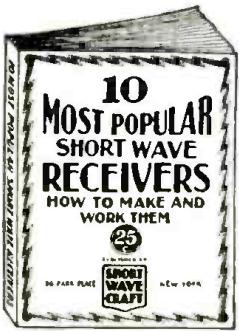**75 Illustrations, 40 Pages, 25c
Stiff, flexible covers**



OVERSEAS READERS!

These books can be obtained from the following houses:

GREAT BRITAIN
Gorring's
9a. Green Street, Leicester
Square
London, England

FRANCE
Editions Radio
42 Rue Jacob
Paris

AUSTRALIA
McGill's
183-195, 218 Elizabeth St.
Melbourne, C. I.

Please mention SHORT WAVE CRAFT when writing advertisers

Short Wave Scouts

(Continued from page 530)

WEST INDIES AND CENTRAL AMERICA

COH—9,428 kc.—Short Wave Station COH, Calle B No. 2 Vedado, Havana, Cuba.
COC—6,010 kc.—Short Wave Station COC, Box 98, Havana, Cuba.
COCD—6,130 kc.—La Voz Del Aire, S. A., Box 2291, Havana, Cuba.
XECR—7,380 kc.—Secretaria de Relaciones Exteriores, Mexico City, D. F. Mexico.
HIID—6,482—La Voz de Quisqueya, Santo Domingo, Dominican Republic.
HIH—6,814 kc.—Radiodifusora HIH, San Pedro de Macoris, Dominican Republic.
HIX—5,980 kc.—Santo Domingo, Dominican Republic.
CEC—10,630 kc.—Compania Internacional de Radio S. A., Santiago, Chile.
HJ1ABE—6,115 kc.—Station HJ1ABE, Laboratorios Fuentes, Cartagena, Colombia.
HJ2ABC—5,890 kc.—Estacion La Voz de Cucuta, Cucuta, Colombia.
HJ4ABA—11,710 kc.—Ecos de la Montana, Medellin, Colombia.
HJ4ABE—5,925 kc.—La Voz de Antioquia, Medellin, Colombia.
HJ5ABE—14,480 kc.—Cia Radiodifusora Colombiana, Apartado 50, Cali, Colombia.
HP5B—6,030 kc.—Estacion Radiodifusora, Miramar, Apartado 919, Panama City, Panama.
HP5J—9,590 kc.—Servicio Publico de Radio, S. A., Panama City, Panama.
OAXD—5,780 kc.—All American Cables, Inc., Casilla 2336, Lima, Peru.
PRADO—6,619 kc.—Apartado 98, Riobamba, Ecuador.
YV2RC—6,112 kc.—Broadcasting Caracas, Caracas, Venezuela.
YV3RC—6,150 kc.—Caracas, Venezuela.
YV5RMO—5,650 kc.—Apartado de Correos 214, Maracaibo, Venezuela.
YV6RV—6,520 kc.—Por Radiodifusora La Voz de Carabobo, Valencia, Venezuela.
HJIABG—6,042 kc.—Barranquilla, Colombia.
TIPG—6,410 kc.—Estaciones La Voz de la Victor, Apartado 225, San Jose, Costa Rica.
EAQ—9,860 kc.—Box 951, Madrid, Spain.
DJD—11,760 kc.—Berlin, Germany.
DJB—15,200 kc.—Same as above.
DJC—6,546 kc.—Same as above.
DJN—9,540 kc.—Same as above.
DJE—17,760 kc.—Same as above.
HAT4—9,125 kc.—Budapest Radiolabor, Budapest, Hungary.
HBL—9,595 kc.—League of Nations, Geneva, Switzerland.
HBP—7,799 kc.—Same as above.
2RO—9,635 kc.—Ente Italiano Avdizioni Radiofoniche, Via Montello 5, Rome, Italy.
2RO—11,810 kc.—Same as above.
ORK—10,330 kc.—I.N.R., 1A, Rue de Baston, Bruxelles, Belgium.
PHI—17,770 kc.—Eindhoven, Holland.
RNE—12,000 kc.—Radio Centre, Solyanka 12, Moscow, U. S. S. R.
Radio-Coloniale—11,715 kc.—98 bis Blvd. Haussmann, Paris, France.
DQJ—15,280 kc.—Berlin, Germany.
DJA—9,560 kc.—Berlin, Germany.
HBJ—14,535 kc.—Radio-Suisse S.A. 12, Quai de la Poste, Geneva, Switzerland.
VK2ME—9,590 kc.—Amalgamated Wireless Ltd., Sydney.
3LR—9,580 kc.—Postmaster-General's Dept., Lyndhurst, Victoria.
OPM—10,140 kc.—Leopoldville, Belgian Congo.

TROPHY CONTEST RULES

(Continued from page 530)

The judges of the contest will be the editors of SHORT WAVE CRAFT, and their findings will be final. Trophy awards will be made every month, at which time the trophy will be sent to the winner. Names of the contesting SCOUTS not winning a trophy will be listed in Honorable Mention each month. From this contest are excluded all employees and their families of SHORT WAVE CRAFT magazine. Address all entries to SHORT WAVE SCOUT AWARD, 99-101 Hudson St., New York City.

\$20.00 Prize Monthly for Best Set

THE editors are looking for "new" receiving circuits—from 1 to 5 tubes preferably. A \$20.00 monthly prize will be awarded to the best short-wave receiver submitted. The closing date for each contest is 75 days preceding date of issue (Dec. 15 for the March issue, etc.). In the event of a tie, an equal prize will be given to each contestant so tying. Address all entries to: Editor, SHORT WAVE CRAFT, 99 Hudson St., New York City.

CLASSIFIED

Advertisements are inserted at 5c per word to strictly amateurs, or 10c a word to manufacturers or dealers. Each word in a name and address is counted. Cash should accompany all orders. Copy for the February issue should reach us not later than December 5th.

BOOKS

ARMY-NAVY GIVES FREE
radio operators' training for service on aircrafts. Salary, expenses paid. Information pamphlet, how to apply, 20c. Continental, Box 311, Dept. 4, Indianapolis, Ind.

GENERATORS

TWENTY PRACTICAL AND LOW cost changes converting old generators into new generators and motors 100-500 watt capacity, d c or a current, with 6 to 100 volts, for radio operation, power, light, or welding. Also instructions for rewinding armatures, 350 definitions of electrical terms, etc. All in new, revised book with simplified instructions and illustrations. Endorsed by thousands. Only \$1.00 postpaid. Autopower, 411 S. Hoyne Ave., Chicago.

"HAM" OFFERS AND WANTS

SALE TRADE READWRITE MODEL 710 Tester \$8.50. New Allstar Jr. tubes speaker \$19.75. Sears Roebuck 1935 World's Fair model 2 band box battery Radio \$12.75. Crosley Banbox Jr. Bat. Radio \$3.50. All Good. Maynard Ogle, Gallatinburg, Tenn.

FOR SALE SILVER MARSHALL all-wave superhetrodyne, also National power pack, Gross Eagle receiver, two fifty power amplifier. Want National, Patterson, Skyridger, Hallertraiter or Scott receiver. Glenn Watt, Chanute, Kas.

BUY, SELL OR TRADE HIGH quality short wave receivers, public address equipment, cameras, lenses, binoculars, etc. Wells-Smith Radio Corp., 26 N. Wells St., Chicago.

FOR SALE GROSS TWENTY- five watt transmitter, Denton six-tube superhetrodyne receiver used three months. Inquire WABVZ, Needham Crow, New Bern, North Carolina.

300035 VARIABLE CONDENSERS 3 for \$1.00. W8RW, Bluffton, Ohio.

SW3 COMPLETE SACRIFICE E. T. Blanchard, Gunnison, Mississipi.

INSTRUCTION

RADIO ENGINEERING, BROADCASTING, AVIATION AND POLICE RADIO Serving Marine and Morse Telegraphy taught thoroughly. All expenses low. Catalog free. Dodge's Institute, Coll St., Valparaiso, Ind.

COMPLETE TRAINING AMATEUR Radio Operators' Licenses. License guaranteed. \$1.50 weekly. New York Wireless School, 1123 Broadway, Watkins 9-2667.

MISCELLANEOUS

OHM'S LAW CALCULATOR—Lightning Slide Rule; solves all problems of Voltage, Current and Resistance. Power, Wire Sizes, etc. Range: 1 micro-amp. to 1000 amps.; 1 micro-volt to 10,000 volts; 1 micro-ohm to 10 meg-ohms; 1 micro-watt to 10 megawatts; wire sizes 0 to 30 B. & S. gauge. Introductory price \$1.00 prepaid. The Dataprint Co., Box 322, Ramsey, N.J.

PATENTS & INVENTIONS

PRACTICAL USEFUL INVENTIONS may now be safely marketed without patenting expense. Complete information free. Chartered Institute of American Inventors, Dept. 92, Washington, D. C.

PATENTS, REASONABLE TERMS, Book and adviser free. L. F. Randolph, Dept. 711, Washington, D. C.

QSL-CARDS—SWL

QSLs, SWLs, DIFFERENT PHOTOTYPE Attractive. Very Reasonable. Samples? (Stamps). W8ESN—1827 Cone, Toledo, Ohio.

QSL CARDS, NEAT, ATTRACTIVE, reasonably priced, samples free. Miller, Printer, Ambler, Pa.

QSLs! SWLs! SNAPIA! 200 TWO colors \$1.00. W5ACB, Tupelo, Miss.

SNAPPY QSL'S SAMPLES? W8SF, Spring Road, Hinsdale, Ill.

RADIO ENGINEERING

CUSTOMBUILDERS OFFERS YOU a new service. Any radio equipment built to your specifications. Write for details—no obligation. Custombuilders, Dept. A, 113 West 57th, New York City.

SHORT WAVE COMPONENTS

4 BAKELITE PLUG-IN COILS, wound on tube bases .30, tall forms .30, six prong .75. Noel, 728 Birch, Scranton, Pa.

SHORT WAVE RECEIVERS

BUILD IT TUBE SHORT WAVE Superhetrodyne, Automatic Volume Control, Boat oscillator, Crystal filter, 20 watts output. Diagram, coil winding data and instructions. Price 25 cents. Link Laboratories, Box 437, Kirksville, Mo.

BLUEPRINT "HOW TO BUILD 18 Long Distance Crystal Receivers—record 2100 miles; "Seibuilders Data" year; 25¢. Laboratories, 151-A Liberty, San Francisco.

FREE—Just Out!

NEW 1936 BARGAIN BUYING GUIDE


64 Illustrated Pages—Two Colors

For Radio Servicemen, Dealers, Experimenters and Short-Wave Fans.

Contains modern glass and metal-tube receivers at unbeatable prices. Complete Public Address Systems from 6 watts up to 10 watts—all high quality, guaranteed systems—at prices which will amaze you. Latest type all-metal and glass tube testers and other test equipment. Complete information on the famous 5-Tube Doerle DeLuxe A.C. Short-Wave Receiver and many other interesting short-wave equipment. This catalog carries a large array of modern radio equipment of interest to all classes of radio servicemen, experimenters and fans. Many items found in no other catalog are listed and illustrated in this Radio Bargain Guide.

You can increase the value of your dollar by buying at the low prices contained in this buying guide. This bargain catalog will show you how to save money by buying economically. Why not start saving now? Don't delay. Write today for your free copy. You are not obligated in any way.

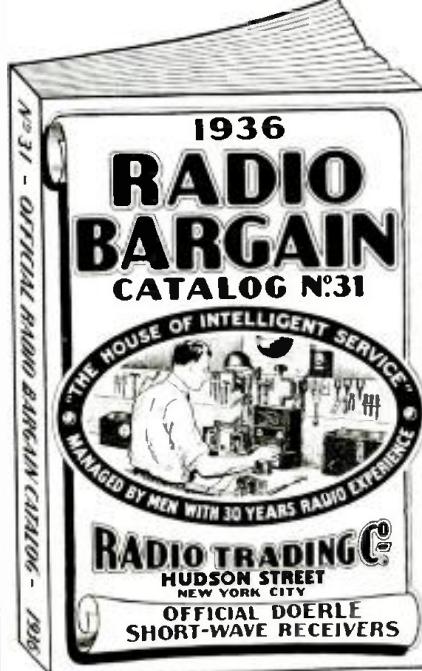WRITE TODAY—send postcard or letter. Buying guide sent by return mail. IT'S ABSOLUTELY FREE.



See pages 560 and 574 for our other "ads."

101A Hudson St.

New York, N. Y.

RADIO TRADING CO.

101A Hudson St.

New York, N. Y.

New D. C. Multiple Meter

0-.1-1-10-100-1,000 VOLTS
0-.001-.01-1-10 AMPERES
0-50,000-5,000,000 OHMS

A beautiful wall-mounted, decimal scale, precision meter for the ENGINEER, EXPERIMENTER and SERVICE MAN, ONLY \$1.95. For details write.

SCHOOLEY ENGINEERING CO., Terrell, Texas

OXFORD SPEAKERS

—give you ALL there is in radio. High piccolo, low organ, pure tones, no distortion. And they're durable. Write for price.

OXFORD-TARTAK RADIO CORP., 350 "D" W. HURON ST., CHICAGO, ILL.


Please mention SHORT WAVE CRAFT when writing advertisers

The DOERLE

5-TUBE DELUXE

A.C. SHORT WAVE RECEIVER

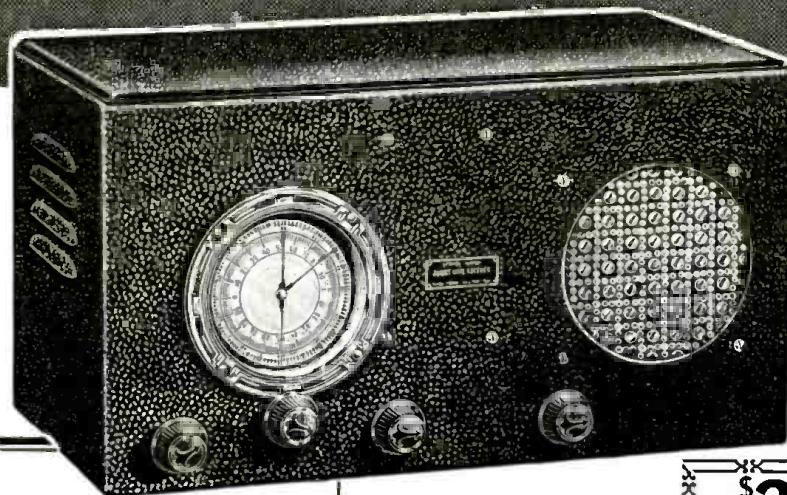*features CONTINUOUS BANDSPREAD
on All Bands!*



NATION-WIDE TESTIMONIALS PRAISE THIS SET!

Dear Sirs:

Just a line or so to give you an idea of what my Doerle A.C. 5 I bought in during a 2 weeks listening test. All of the G and D stations were received also TIEP, WSE, PRADO, HJIAABE, WSNAL, W2XE, WSNK, CIRO, YU2RC, CIRX, COC, HJIAABB, UYRMO, YP2BC, WCRCT, CTIAA, WIXAL, W9XAA, WIXAZ, EAQ, WE6FW, HC2BL, HJ3ABD, KEJ, HAB, HP5B, HJIAAD, WNB, YUHRC, HIZ, JVK, FYA, YU4BC, OA4AD, RNE, PHZ, RKL, WNC, YBA, COH, PRF5, WON, XEPT, W2XAEP, LSL, I2RO, IRM, JYS, UK3LR. All stations come in with strong carriers with a QSA-5 plus.

FRANCES KMETZ,
213 Linden St., Allentown, Pa.

Gentlemen:

Here is a list of Short-Wave stations I have received in a short time with my "Doerle AC5," with a very poor aerial for short-wave work. EAQ-MAD-11D, SPAIN; WIXAZ—Springfield, Mass.; W2XAF—Schenectady, N.Y.; COH—Havana, Cuba; COU—Havana, Cuba; VE9GW—Bowmanville, Ontario, Canada; CTIA—Lisbon, Portugal; PRF5—Rio De Janeiro, Brazil; HJIAABB—Barraquilla, Colombia; PRADO—Riobamba, Ecuador, S.A.; DJU—Berlin, Germany; XEPT—Mexico City, Mexico; YV5RMO—Maracaibo, Venezuela, S.A.; HAB—Winnipeg, Canada; W2XFP—New York, N.Y.; W8XK—Pittsburgh, Pa.; HJ5B—Panama City, Panama; YVA—Paris, France; GSC-GSI—Daventry, England.

EAQ—Madrid, Spain, and COH—Havana, Cuba, come in every night on the loud speaker regardless of weather conditions. This is the third and best receiver I have owned in the short time I have been interested in Short Waves.

EMERALD H. DELRUECGE,
Rose-Mary Dahlia Gardens,
Martins Ferry, Ohio.

Original Letters Plus Others May Be
Seen At Our Office

EVERYBODY'S talking about the new 5-Tube Doerle Deluxe Short-Wave Receiver. If you are interested in short-waves, avail yourself of this opportunity to listen to this remarkable set with no obligation to buy it unless you are absolutely satisfied with its performance. Use the coupon below for fast service.

USES ANY TYPE AERIAL

Regardless of what type aerial you have, this receiver makes provisions for using it. Either the standard inverted-L type or noise-free doublet type may be utilized. This means that this receiver can be used in ALL localities.

SENSITIVE REGENERATIVE CIRCUIT

Two tuned stages, regenerative detector, three A.F. stages with powerful '41 pentode output and perfectly matched dynamic speaker—all these features contribute to the great power and fine performance of this receiver. A special antenna-trimming scheme permits perfect alignment of both antenna and detector tuning circuits without affecting the setting of the tuning dial.

CONTINUOUS BAND-SPREAD

Continuous bandspread on the entire range from 15 to 200 meters is ob-

F R E E

64 page Buying Guide
for the Radio Serviceman, Dealer and Experimenter. Contains thousands of well-illustrated diagrams, valuable address equipment short-wave receivers, standard American and European broadcast receivers, Automobile, radio parts, etc., etc.

DO NOT DELAY
WRITE TODAY

Send post card or letter buying guide
by return mail. It's Free.



\$27.51
READY TO OPERATE
Less 2 Broadcast coils—
\$1.75 extra

- ★ USES DOUBLET OR STANDARD ANTENNA.
- ★ 8 LOW-LOSS PLUG-IN COILS.
- ★ RANGE 15 to 200 METERS.
- ★ MICROMASTER BANDSPREAD DIAL.
- ★ MAGNAVOX DYNAMIC SPEAKER.
- ★ BEAUTIFUL CRACKLE CABINET
- ★ HEADPHONE RECEPTION IF DESIRED.
- ★ SENSITIVE REGENERATIVE CIRCUIT.
- ★ TONE CONTROL.

tained through the use of a very ingenious dial having a ratio of 125 to 1 and two pointers. Furthermore, two knobs are provided, making possible fast and slow tuning. No longer are the foreign broadcast stations crowded on two or three scale divisions of the dial. They are now spread out over a goodly portion of the dial thereby greatly simplifying tuning.

8-LOW-LOSS PLUG-IN COILS

The use of plug-in coils is still the most efficient method of changing from one band to another. That is why they are used in this Doerle receiver. 8 coils are provided to cover the range of from 15 to 200 meters in 4 bands, viz.: 20, 40, 80 and 160 meter bands. These coils are of the 3-winding 6-prong type and are used 2 at a time. Wound on ribbed bakelite forms and designed especially for the Doerle receiver, they are highly efficient.

EXQUISITE WORKMANSHIP

All parts are mounted on a single, cadmium-plated chassis and contained in a large, handsomely-finished black crackle cabinet. The dial and speaker grill are practically the same diameter and are symmetrically centered on the front panel of the cabinet thereby presenting a professional and dignified appearance.

Provisions are made for using headphones if desired with switch to cut out the dynamic speaker. A tone control is provided which not only varies the tone but helps materially to reduce back ground hiss.

FAMOUS FOR DX RECEPTION

Hundreds of testimonials in our files attest to the superlative performance of this world-famous receiver. Several of these testimonials are printed on this page. Set measures 17 1/4" x 8 1/2" x 8 1/2" high. Net weight 23 lbs., shipping weight 35 lbs. Designed for 110-120 volt 50-60 cycle A.C. operation. No. 5000—Doerle 5-Tube DeLuxe A.C. Short-Wave Receiver complete with matched tubes and 8 coils. Completely wired and tested (NOT SOLD IN KIT FORM). Your p/c. \$27.51. Set of 2 broadcast coils \$1.75 additional. Add \$2.50 for 110 volt 25 cycle model or 220 volt 60 cycle model.

**Send
COUPON
TODAY**

5-DAY FREE TRIAL

RADIO TRADING CO., 101A HUDSON ST., NEW YORK

Gentlemen:
I enclose _____ dollars, for your new Doerle 5-tube Deluxe Short-Wave receiver on a five day free trial basis. If, at the end of five days after receipt of radio, I am not perfectly satisfied, I will write you for return shipping instructions. Upon receipt of the radio, you will refund me the full purchase price. I agree to pay express charges one way, and you the other.

C.O.D. SHIPMENT. I enclose _____ dollars, balance of _____ dollars, _____ cents deposit, _____ cents C.O.D.

PRINT Name _____
Address _____
Town _____ State _____

RADIO TRADING CO., 101A Hudson St., New York City

● Index to Advertisers ●

	A	561
Ace Radio Laboratories	561	
Acme Specialty Co.	554	
Aerovox Corporation	571	
Alden Products Co.	559	
Allied Engineering Institute	561	
Allied Radio Corp.	549	
Alloy Transformer Co.	567	
American Microphone Co.	565	
American Technical Society	560	
Amperite Co.	571	
Arco Tube Company	554	
Astatic Microphone Laboratory	569	
B		
Blan, the Radio Man	559	
Brush Development Co., The	559	
Bud Radio Inc.	559	
Burstein-Applebee Co.	575	
C		
Cameradio Co.	567	
Candler System Co.	564	
Cannon, C. F., Company	556	
Chicago Radio Apparatus Co., Inc.	571	
Classified Advertisements	573	
Cornell-Dubilier Corporation	557	
Coyne Radio & Electrical School	515	
D		
Dataprint Company	558	
Delaware Radio Sales Co.	558	
Deutschmann, Toile, Corp.	554	
Dodge's Institute	567	
E		
Eagle Radio Co.	563	
Eilen Radio Laboratories	553	
Everyday Science & Mechanics	561	
Experimental Radio Labs.	561	
F		
First National Television, Inc.	558	
G		
General Winding Co.	575	
Goldentone Radio Co.	562	
Gold Shield Products Co.	559, 560, 562	
H		
Hallcrafters, The	558	
Hammarlund Manufacturing Co.	557	
Harrison Radio Company	551, 562	
Henry Radio Shop	559	
Hinds & Edgerton	564	
I		
Instructograph Company	556	
Insuline Corp. of America	564	
International Correspondence Schools	575	
International Resistance Co.	557	
K		
Korrol Mfg. Co., Inc.	554	
L		
Lancaster Allwine & Rommel	564	
Lynch, Arthur H., Inc.	561	
M		
M. & H. Sporting Goods Co.	569	
Marine Radio Company	552	
Massachusetts Radio School	554	
Midwest Radio Corp.	Back Cover	
Miller, J. W., Co.	562	
Muter Company, The	550	
N		
National Company, Inc.	Inside Back Cover	
National Radio Institute	513	
Newark Electric Co.	560	
New York Y.M.C.A. Schools	556	
O		
Oxford-Tartak Radio Corp.	573	
R		
Radio Constructors Labs.	555	
Radio Craft	562	
Radio Publications	516, 568	
Radio Trading Co.	560, 573, 574	
Radio Training Assn. of America	571	
Ramsey Publishing Co.	560	
RCA Institutes, Inc.	562	
Remington-Rand, Inc.	552	
Roland Radio Co.	552	
Royale Radio Crafters	563	
R-S Merchandising Committee	556	
S		
Sargent, E. M., Co.	559	
Schwartz, M. & Son	560	
Schooley Engineering Co.	573	
Short Wave Coil Book	571	
Short Wave League	562, 576	

Short Wave Listener Magazine	566
Short Wave Manual	570
Short Waves	569
Sprayberry, F. L.	565

T

Teleplex Co.	555, 561
Thor Radio Corp.	550
Triplet Electrical Instrument Co.	555
Try-Mo Radio Co., Inc.	562, 564

U

Uncle Dave's Radio Shack	562
Uno All-Wave Coil Co.	557

W

Wellworth Trading Company	556, 561
Wholesale Radio Service Co., Inc.	565, 567
Wiley, John, & Sons, Inc.	558

Wright-DeCoster, Inc.	569
-----------------------	-----

X

X.L., Radio Laboratories	555
--------------------------	-----

When To Listen In

by M. HARVEY GERNSBACK

(All Schedules Eastern Standard Time)

ETHIOPIA

The station at Addis Ababa in Ethiopia is now the center of attention for S-W fans. This station originally built for telegraphy is now employed to send special "broadcasts" of news, etc., using telephony. The power of the transmitter is 12 kw. (It was raised to this figure from 3.5 kw. a year ago.) The call letters are ETA and ETB. The station operates normally on 18270 and 11955 kc. using the call ETA and on 7620 kc. using the call ETB. The 11955 kc. channel has been heard up to 7 p.m.

CARACAS

YV2RC at Caracas, Venezuela has now settled down on 5800 kc., now being heard very well indeed and we thank the management for the special broadcast dedicated to the SHORT WAVE LEAGUE.

POLAND

SPW at Warsaw, a commercial phone and telegraph station has been heard since Oct. 1st, sending a special Sunday broadcast from 11:30 a.m.-12:30 p.m. Announcements are in Polish and English. There are 2 announcers, one a man, the other a woman. The frequency employed is 13635 kc. (22 meters); SPW is rated at 20 kw. power.

ROME

In addition to its regular broadcasts, 2RO is now sending out a daily news bulletin in English from 6-6:15 p.m. on its 49 meter band transmitter. This is followed by one in Spanish on 9635 kc.

MEXICO

There is a new Mexican station at Vera Cruz. It is XEFT. Address is 28 Ave., Independencia, Vera Cruz. The frequencies used are either 9600 or 6120 kc. XBJQ at Mexico City on 11200 kc (approximate) is operated by the National Bank, P.O. Box 2825. It is supposed to be on daily from 5:30-6:30 p.m. and 10:30 p.m.-12 m.

JAVA

PMA (19345 kc. and PLV (9415 kc.) are still broadcasting from 10-10:30 a.m. on Tues., Thur. and Sat.

YDA at Tandjongpriok is expected back on the air on either 6010 or 6120 kc. by the time this appears in print. YDA may also operate in the 19 and 25 meter bands.

DAVENTRY

The English stations will be operating as follows in December. The stations used are subject to sudden change however so listen to the announcer for the waves being used. Trans. 1, 5:30-6:30 am on GSD and GSB; 6:30-7:30 am on GSD and either GSF or GSB. Trans. 2, 6-8:45 a.m. (Sun. 6:30-8:45 a.m.) on GSF and either GSG or GSE. Trans. 3, 9-10:30 a.m. on GSD and GSB; 10:30 a.m.-12 noon on GSD and either GSD or GSA. Trans. 4, 12:15-2:15 p.m. on GSI, GSD and GSB; 2:15-4 p.m. on GSD, GSB and GSL; 4:15-5:45 p.m. on GSB and GSA. Trans. 5, 6-8 pm. on GSC and GSA. Trans. 6, 10-11 pm. on GSL and either GSC or GSA.

QUALITY APPARATUS FOR

Short Waves

GEN-WIN POLICE AND SHORT WAVE ADAPTER

Convert your broadcast set into a short-wave set tuning from 80 to 200 meters. Get exciting police alarms from stations thousands of miles away. Airplane communications while planes are in flight. Amateur phone and international code communications. The biggest thrill and fun for so little money. Installed in your set. Plugs directly into the detector tube socket. Specify the detector tube in your set, or if uncertain as to detector tube advise make and model number of set when ordering.

No. 190—for 30-, 40-, 50-, 12A, 200, or '201A Detector Tube	\$1.39
No. 191—for 34-, 36-, 38-, 1814-, 18	

• • • SHORT WAVE ESSENTIALS FOR MEMBERS OF THE SHORT WAVE LEAGUE • • •

Application for Membership SHORT WAVE LEAGUE

1-36
SHORT WAVE LEAGUE
99-101 Hudson Street, New York, N. Y.

I, the undersigned, herewith desire to apply for membership in the SHORT WAVE LEAGUE. In joining the LEAGUE I understand that I am not assessed for membership and that there are no dues and no fees of any kind. I pledge myself to abide by all the rules and regulations of the SHORT WAVE LEAGUE, which rules you are to send to me on receipt of this application.

I consider myself belonging to the following class (put an X in correct space): Short Wave Experimenter Radio Engineer Student
I own the following radio equipment:

Transmitting _____

Call Letters _____

Receiving _____

Name _____

Address _____

City and State _____

Country _____

I enclose 10c for postage and handling for my Membership Certificate.

A FEW WORDS AS TO THE PURPOSE OF THE LEAGUE

The SHORT WAVE LEAGUE was founded in 1930. Honorary Directors are as follows:

Dr. Lee de Forest, John L. Reinartz, D. E. Replolie, Hollis Baird, E. T. Somerset, Baron Manfred von Ardenne, Hugo Gernsback, Executive Secretary.

The SHORT WAVE LEAGUE is a scientific membership organization for the promotion of the short wave art. There are no dues, no fees, no initiations, in connection with the LEAGUE. No one makes any money from it; no one derives any salary. The only income which the LEAGUE has is from its short wave essentials. A pamphlet setting forth the LEAGUE's numerous aspirations and purposes will be sent to anyone on receipt of a 3c stamp to cover postage.

FREE MEMBERSHIP CERTIFICATE

As soon as you are enrolled as a member, a beautiful certificate with the LEAGUE's seal will be sent to you, providing 10c in stamps or coin is sent for mailing charges.

Members are entitled to preferential discounts when buying radio merchandise from numerous firms who have agreed to allow lower prices to all SHORT WAVE LEAGUE members.

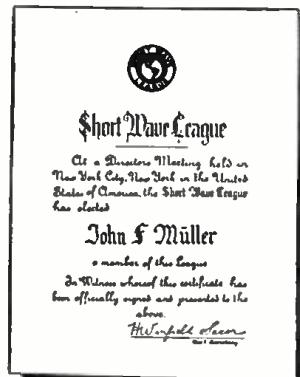


Illustration of engraved free membership certificate

SHORT WAVE ESSENTIALS LISTED HERE SOLD ONLY TO SHORT WAVE LEAGUE MEMBERS


They cannot be bought by anyone unless he has already enrolled as one of the members of the SHORT WAVE LEAGUE or signs the blank on this page (which automatically enrolls him as a member), always provided that he is a short wave experimenter, a short wave fun. radio engineer, radio student, etc.).

Inasmuch as the LEAGUE is international, it makes no difference whether you are a citizen of the United States or any other country. The LEAGUE is open to all.

SHORT WAVE LEAGUE LETTERHEADS

A beautiful letterhead has been designed for members' correspondence. It is the official letterhead for all members. The letterhead is invaluable when it becomes necessary to deal with the radio industry, mail order houses, radio manufacturers, and the like; as many houses have offered to give members who write on the LEAGUE's letterhead a preferential discount. The letterhead is also absolutely essential when writing for verification to radio stations either here or abroad. It automatically gives you professional standing.

50c

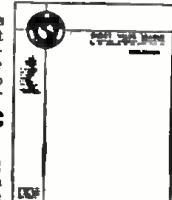

A—50c per 100

OFFICIAL SHORT WAVE LISTENER MAGAZINE

The finest magazine of its kind ever published—totally different in get-up and contents from any other. Contains the largest listing of short wave stations in the world, up-to-the-minute, including "Police," "Television" and short-wave stations, as well as a special list of the star short-wave stations with their frequencies and call letters. Also contains photos and descriptions of short-wave broadcasting stations in various parts of the world with photos of short wave studio artists—How to locate "weak" distance stations, and other hints for the "short-wave listener"—Question and Answer Department for the "listener"—Silver Cup Trophy for best photo of readers' listening "Posts," etc.

B—Official Short Wave Listener Magazine.....Prepaid 15c

RADIO MAP OF THE WORLD AND STATION FINDER

The finest device of its kind published. The world's map on heavy board is divided into 23 sections, while the rotary disc shows you immediately the exact time in any foreign country. Invaluable in logging foreign stations. Also gives call letters assigned to all nations. Size 11"x22".

C—Radio Map of the World and Station Finder.....Prepaid 25c

GLOBE OF THE WORLD AND MAGNETIC COMPASS

This highly important essential is an ornament for every den or study. It is a globe, 6 in. in diameter, printed in fifteen colors, glazed in such a way that it can be washed. This globe helps you to intelligently log your foreign stations. Frame is of metal. Entire device substantially made, and will give an attractive appearance to every station, emphasizing the long-distance work of the operator.

D—Globe of the World.....Prepaid \$1.25

SHORT WAVE LEAGUE LAPEL BUTTON

This beautiful button is made in hard enamel in four colors, red, white, blue and gold. It measures three quarters of an inch in diameter. By wearing this button, other members will recognize you and it will give you a professional air. Made in bronze, gold filled, not plated. Must be seen to be appreciated.

E—SHORT WAVE LEAGUE lapel button.....Prepaid 35c

EE—SHORT WAVE LEAGUE lapel button, like the one described above but in solid gold.....Prepaid \$2.00

SHORT WAVE LEAGUE SEALS

These seals or stickers are executed in three colors and measure 1 1/4 in. in diameter, and are gummed on one side. They are used by members to affix to stationery, letterheads, envelopes, postal cards and the like. The seal signifies that you are a member of the SHORT WAVE LEAGUE. Sold in 25 lots or multiples only.

G—SHORT WAVE LEAGUE seals.....per 25, Prepaid 15c

SHORT WAVE MAP OF THE WORLD

This beautiful map, measuring 18x26 in. and printed in 18 colors is indispensable when hung in sight or placed "under the glass" on the table or wall of the short wave enthusiast. It contains a wealth of information such as distances to all parts of the world, political nature of the country in which a broadcast station is located, etc., and from the manner in which the map is blocked off gives the time in different parts of the world at a glance.

F—SHORT WAVE Map of the World.....Prepaid 25c

PLEASE NOTE THAT ABOVE ESSENTIALS ARE SOLD ONLY TO MEMBERS OF THE LEAGUE—NOT TO NON-MEMBERS WITH EXCEPTION OF ITEM B.

Send all orders for short wave essentials to SHORT WAVE LEAGUE, 99-101 Hudson Street, New York City.

If you do not wish to mutilate the magazine, you may copy either or both coupons on a sheet of paper.

SHORT WAVE LEAGUE 99-101 Hudson St., New York, N. Y.



G—15c for 25



SHORT WAVE LEAGUE, 99-101 Hudson Street, New York, N. Y.

Gentlemen:

I am already an enrolled member in the SHORT WAVE LEAGUE

I am a new member and attach my application to this coupon


Please send me the following short wave essentials as listed in this advertisement:

for which I enclose \$ herewith.

(The LEAGUE accepts money order, cash or new U. S. Stamps in any denomination. Register cash and stamps.)

Name
Address
City and State
Country

1-36

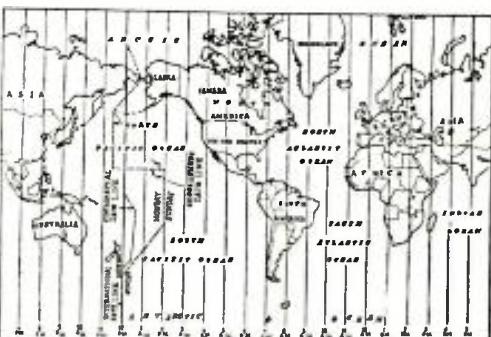

F—25c each




C—25c each



D—\$1.25 each



E—35c each

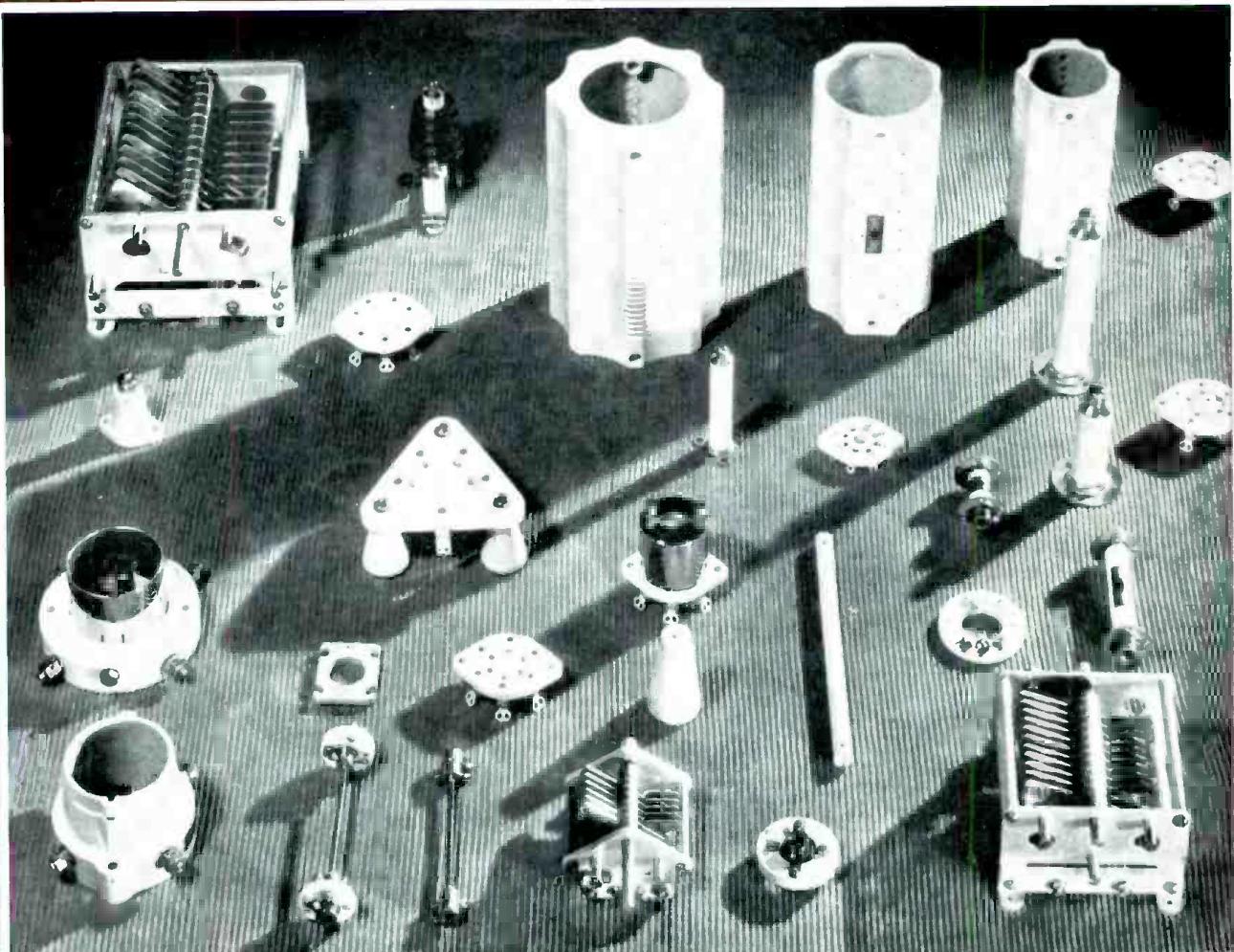

National offers a thoroughly engineered part for nearly every radio purpose. The entire line cannot be compressed into our twenty-page catalogue, much less a single page. But look over the group above. Transmitting condensers from the little 1000 volt TMS in the foreground to the 12,000 volt TMA at the rear. Low loss ceramic coil forms for every amateur band. Low loss sockets for nearly every tube type, from acorns to power pentodes. Flexible couplings from the little TX-12, which will work around a corner, to the big fellows for heavy condensers, high voltages, and low-losses. Strain insulators, spreaders, lead-ins for the antenna: stand-offs, chokes, dials for the rig. National has what it takes.

NATIONAL
61 SHERMAN STREET



COMPANY
MALDEN, MASS.

only
MIDWEST
Gives You an
18-TUBE Radio
(for Metal or Glass Tubes)

SIX TUNING RANGES
4½ to 2400 METERS
FULL SCOPE
HIGH FIDELITY
PUSH BUTTON TUNING

ROBOT EAR
and Scores of Other
Features for

\$59⁵⁰
with New
GIANT
THEATRE-
SONIC
SPEAKER

TERMS AS LOW AS \$5⁰⁰ down

ONCE again Midwest demonstrates its leadership by offering the world's most powerful Super De Luxe 18-METAL Tube 6-Tuning Range radio. It is a master achievement . . . today's most highly perfected, precisely built, laboratory adjusted set. It is a radio-musical instrument that will thrill you with its marvelous super performance . . . glorious new acousti-tone . . . crystal-clear "concert" realism . . . and magnificent foreign reception. Before you buy any radio, write for FREE 40-page 1936 catalog. Learn about the successful Midwest Laboratory-To-You policy that saves you 30% to 50% . . . that gives you 30 days FREE trial.



Send for FREE 40-page four-color catalog. It pictures the complete line of beautiful 1936 Midwest Acousti-Tone V-Spread consoles...and chassis...in four colors.

SIX TUNING RANGES
This exclusive engineering triumph puts Midwest radio years ahead of ordinary sets and makes them the "World's Greatest Radio Values." Now, it is easy to make the nations of the world parade before you. You can switch instantly from American programs to Canadian, police, amateur, commercial, "secret," experimental, airplane and ship broadcasts . . . to the finest and most fascinating programs from Europe, Africa, Asia, Australia, South America . . . 12,000 miles away.

ACOUSTI-TONE V-SPREAD DESIGN
(U. S. Patent No. 96750)

The V-Front Dispensing Vanes established a new radio style overnight. They spread the beautiful lace-work of the "highs" throughout the room in a scientific manner . . . directing the High Fidelity waves uniformly to the ear. Now, get complete range of audible frequencies from 50 to 16,000 cycles . . . achieving glorious new acousti-tone . . . assuring life-like crystal-clear "concert" realism.

MIDWEST RADIO CORP.
DEPT. 14P CINCINNATI, OHIO U.S.A.
Established 1920 Cable Address MIRACO All Codes

SAVE UP TO 50%
Direct FROM MIDWEST LABORATORIES

No middlemen's profits to pay. You buy at wholesale price, direct from Laboratories . . . saving 30% to 50%. You can order your 1936 Midwest radio from the new 40-page catalog with as much certainty of satisfaction as if you were to come yourself to our great laboratories.

You save 30% to 50% . . . you get 30 days FREE trial . . . as little as \$5.00 down puts a Midwest radio in your home. You are triply protected with a One-Year Guarantee, Foreign Reception Guarantee and Money-Back Guarantee.



**30 Days
FREE Trial!**

GUARANTEED FOREIGN RECEPTION


This super radio will out-perform \$200 and \$300 sets on a side by side test. It is so powerful, so amazingly selective, so delicately sensitive that it brings in distant foreign stations with full loud speaker volume, on channels adjacent to powerful locals. The 18 tubes permit of advanced circuits, make it possible to use the tremendous reserve power, and to exert the sustained maximum output of the powerful new tubes.

80 SENSATIONAL ADVANCEMENTS

Scores of marvelous Midwest features, many of them exclusive, explain Midwest glorious tone realism, super performance and thrilling worldwide 6-band reception. They prove why nationally known orchestra leaders like Fred Waring, George Olsen, Jack Denny, etc., use a Midwest in preference to more costly makes. Pages 12 to 21 in FREE catalog illustrate the new Midwest features. Study them before you make up your mind.

PUSH BUTTON TUNING

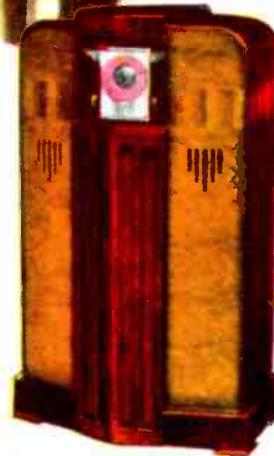Simply pushing Silence Button silences set between stations. Beautiful tuning lights automatically indicate when station is properly tuned. Release button . . . and station comes in perfectly. Pressing Station Finder Button (Midwest's exclusive ROBOT EAR) automatically determines proper dial position for bringing in extremely weak stations.



GINGER ROGERS AMAZED
AT MIDWEST PERFORMANCE

Hollywood, California.
"Your Midwest is a wonderful instrument. The tone quality is delightful and it surpasses any set I have ever owned. I have heard stations from all over the world. I got a thrill the first time I tuned in on the boomerang of 'Big Ben.'"

GINGER ROGERS

MAIL COUPON TODAY!

**FOR
FREE 30-DAY TRIAL OFFER and 40-PAGE FOUR-COLOR FREE CATALOG**

**MIDWEST RADIO CORP.,
Dept. 14P, Cincinnati, Ohio**

User-Agents
Make Easy
Extra Money
Check Here
for details

Without obligation on my part, send me your new FREE catalog, complete details of your liberal 30-day FREE trial offer, and FREE Miniature Rotating 18-tube Dial. This is NOT an order.

Name _____

Address _____

Town _____ State _____

Check here if interested in a Midwest All-Wave Battery Radio