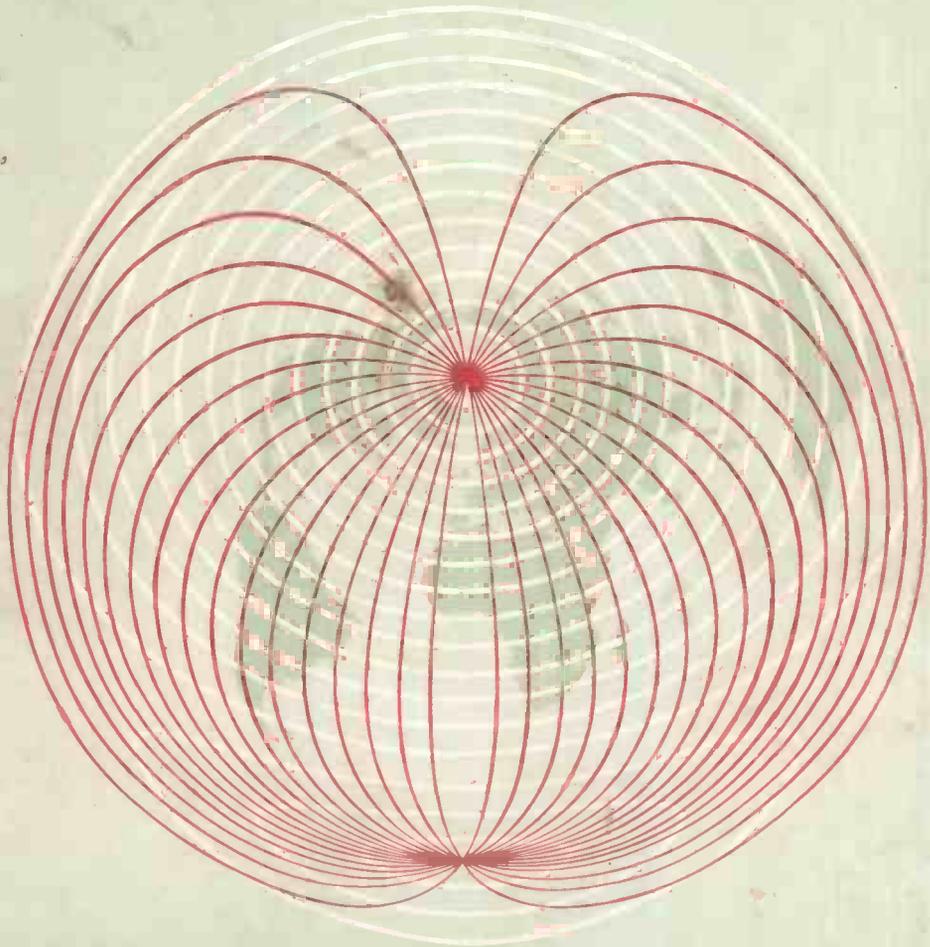


C. J. Smith

Wireless World

MARCH 1954

TWO SHILLINGS



RADIO, TELEVISION AND ELECTRONICS

VALVES**For
SPECIAL
PURPOSES**

We are now able
to give prompt deliveries of

EDISWAN
MAZDA

*27M1 & 27M2 HIGH-VACUUM PHOTO MULTIPLIERS

Complete details and
prices of Ediswan Mazda
photo-multipliers will be
supplied on request.

*These valves are plug-in replacements
for the American type 931A.

EDISWAN

MAZDA

VALVES AND CATHODE RAY TUBES

THE EDISON SWAN ELECTRIC CO. LTD., 155 CHARING CROSS ROAD, LONDON, W.C.2
Member of the A.E.I. Group of Companies.

Telephone: Gerrard 8660

Wireless World

RADIO, TELEVISION
AND ELECTRONICS

43rd YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK, M.I.E.E.


Editor: H. F. SMITH

MARCH 1954

In This Issue

EDITORIAL COMMENT	101
SQUANDERED V.H.F. CHANNELS. By <i>J. R. Brinkley</i> ..	103
CATHODE FOLLOWER OSCILLATOR. By <i>Thomas Roddam</i>	106
MEASUREMENT OF HARMONIC DISTORTION. By <i>T. D. Conway</i>	110
ELECTRONIC ANALOGUE COMPUTING. By <i>Raymond B. Quarmby</i>	113
BOOKS RECEIVED	118
SURFACE-BARRIER TRANSISTORS	119
TRANSISTORIZED MEGOHMMETER. By <i>P. B. Helsdon</i> ..	121
WORLD OF WIRELESS	124
LETTERS TO THE EDITOR	127
SHORT-WAVE CONDITIONS	128
FREQUENCY SHIFT RADIO TELEGRAPHY. By <i>D. H. C. Scholes</i>	129
FOCUSING CATHODE RAYS. By " <i>Cathode Ray</i> "	133
AWARDS FOR TECHNICAL AUTHORS	137
IMPROVED RADIO ALTIMETER. By <i>A. Bloch, K. E. Buecks</i> and <i>A. G. Heaton</i>	138
ATTENUATORS FOR HIGH FREQUENCIES. By <i>R. F. Privett</i>	141
MULTIPLEX F.M. BROADCASTING	145
VIBRATORY GYROSCOPE	146
MOBILE FLIGHT SIMULATOR	147
MANUFACTURERS' PRODUCTS	148
RANDOM RADIATIONS. By " <i>Diallist</i> "	150
UNBIASED. By " <i>Free Grid</i> "	152

PUBLISHED MONTHLY (last Monday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. Telephone: Waterloo 3333 (60 lines). Telegrams: "Ethaworld, Sedist, London." Annual Subscription: Home and Overseas, £1 7s. 0d. U.S.A. \$4.50. Canada \$4.00. BRANCH OFFICES: Birmingham: King Edward House, New Street, 2. Coventry: 8-10 Corporation Street. Glasgow: 26B Renfield Street, C.2. Manchester: 260. Deansgate, 3.

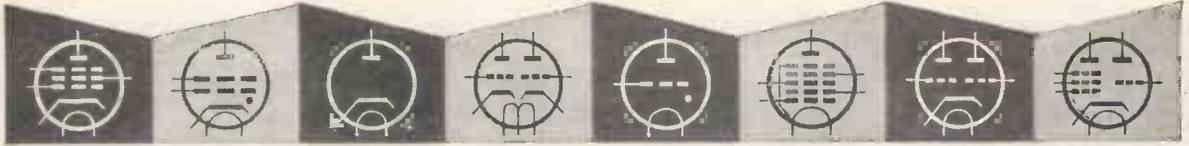

VALVES, TUBES & CIRCUITS

15. VALVES FOR V.H.F. TELEVISION RECEPTION

The advent of television transmissions in the frequency range of 174 to 216 Mc/s (Band III) will mean that receivers must be capable of receiving signals radiated at these frequencies in addition to those already transmitted in the range 41 to 68 Mc/s (Band I).

Reception of signals at the higher frequencies involves changes in the input and frequency changer stages of present-day superheterodyne receiver designs. To meet these requirements the Mullard "World Series" of television valves has been augmented by the introduction of two new types:—

PCC84—Double triode for use as a cascode amplifier in V.H.F. input stages.


PCF80—Triode pentode for use in frequency-changer stages.

As with most of the other "World Series" valves, these new types use the B9A (noval) miniature nine-pin base, have heaters suitable for inclusion in a 300 mA series chain, and can operate with a receiver h.t. supply of 180 volts.

PCC84. The double triode is designed for use as a cascode amplifier, i.e. one triode section operates as a neutralised grounded-cathode amplifier and the other section as a grounded-grid amplifier. The two sections are then connected in series across the h.t. supply, the anode of the first section having a direct connection to the cathode of the second section. The cascode arrangement results in a low noise level for the input stage being achieved in the first section, combined with high gain resulting from use of the grounded-grid connection in the second section.

PCF80. The triode pentode, having separate electrode systems for triode and pentode sections, is used in the frequency changer stage. The triode section, connected as a local oscillator, is in a Colpitts circuit. The oscillator voltage and the input signal from the PCC84 are mixed either inductively or capacitively on the control grid of the pentode section. This section functions as the mixer stage, its performance depending considerably upon the choice of circuit components to give optimum values of conversion conductance and input damping.

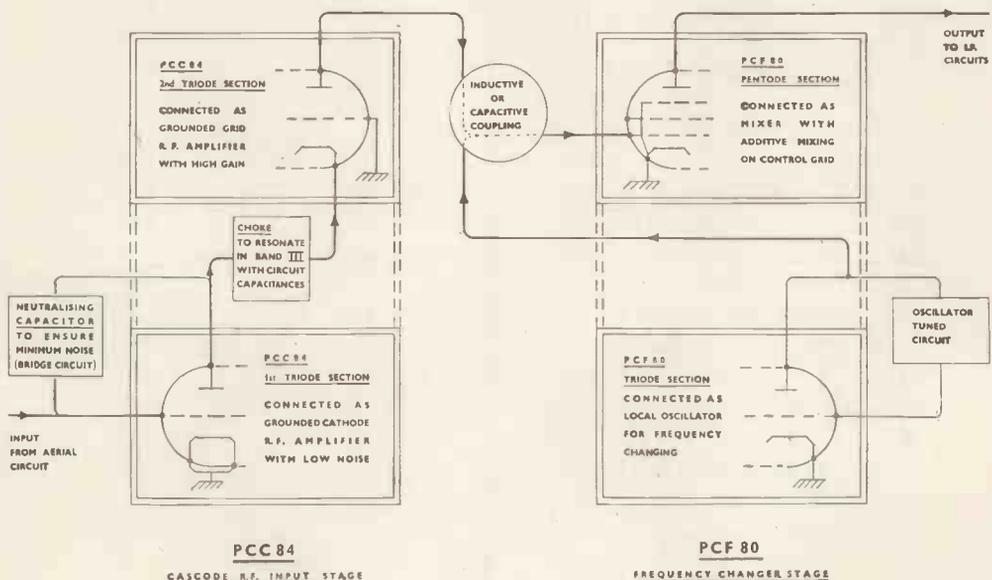The accompanying functional diagram illustrates the basic mode of operation of these valves when used in the "front-end" circuit of a television receiver for use in Bands I and III.



Reprints of this advertisement, together with additional data, may be obtained free of charge from the address below



MULLARD LTD., Technical Publications Department, Century House, Shaftesbury Avenue, W.C.2.

Wireless World

MARCH 1954

VOL. 60 No. 3

A.M. versus F.M.: End of a Controversy

INTEREST in proposals for the setting up of a v.h.f. broadcasting system may be stimulated by the announcement, made in Parliament on February 18th, that the Postmaster-General has accepted the recommendation of the Television Advisory Committee that frequency modulation should be used. Acceptance of this recommendation was accompanied by a statement that B.B.C. proposals for making a start on an initial group of stations are now under discussion with the Corporation and "further developments will be considered in due course."

This somewhat lukewarm acceptance of the T.A.C.'s Report* is perhaps on a par with the slightly unenthusiastic nature of the Report itself, which has provoked surprisingly little comment in radio circles since it was published on January 18th. The Report starts off on a rather doleful note by saying that the introduction of v.h.f. broadcasting is an "unwelcome complication." In addition to the question of modulation already mentioned, the main recommendations are that the service should be conducted in the band 88-95 Mc/s and that a start should be made on a fairly large scale. The Committee points out the radio industry should be given encouragement to embark on the production of suitable receivers in reasonable volume. This recommendation, if accepted, is a matter for some satisfaction, and is in welcome contrast to the Government's proposals for starting competitive television on a severely restricted basis.

It should be added that the Committee's recommendations apply either to a scheme designed to give national coverage of three programmes or to a network of stations planned to give merely "a substantial reinforcement" of the services at present provided by the B.B.C. on long and medium waves.

A lengthy report from the Technical Sub-Committee is appended to the document, and in it the relative merits of frequency and amplitude modulation are discussed from the point of view both of transmission and reception. As the main point at

issue has now been finally decided by the P.M.G.'s acceptance of the Committee's recommendation, there is little value in commenting on these arguments in detail. Considerable stress is laid on the greater capital and upkeep cost of a.m. transmitters, and also on the economics of receivers for the two modulation systems. The conclusions reached are, however, simple and straightforward: "The a.m. wide-band system has specific disadvantages and no advantages relative to the f.m. system. For the a.m. narrow-band system the only advantage is a possible saving in the frequency spectrum required."

Perhaps the most interesting part of the Technical Sub-Committee's report, now that the a.m./f.m. issue is settled, is that dealing with some of the details of f.m. receiver and convertor design. We are pleased to see a recommendation (which is endorsed by B.R.E.M.A.) that standards of good practice should be set up from the start in order to minimize harmful radiation from v.h.f. broadcast receivers. These problems should be studied jointly by the Post Office and Industry.

In general, the discussion on f.m. is based on the acceptance of the almost universal standards of a maximum deviation of ± 75 kc/s and a modulation bandwidth of 15 kc/s.

Just as the Report opens on a rather doleful note, it ends in similar vein. There is a minority statement signed by C. O. Stanley, who considers that adequate attention has not been given by his colleagues to the broader questions of fundamental policy. Mr. Stanley says v.h.f. broadcasting has been a failure in practically every country in which it has been introduced, and casts strong doubts on its advantages in general. He also makes a point of the "incompatibility" of f.m., as recommended for the new service, with a.m. as used for all existing broadcast sound, and which, presumably, will be used for the proposed competitive television service. This last is a provocative point, and in this matter at least Mr. Stanley will probably find some supporters among those who believe that television and sound broadcasting may ultimately be merged into a more-or-less integrated service.

* Second Report of the Television Advisory Committee, H.M.S.O. 1s

EDWIN H. ARMSTRONG

The following appreciation of Major Armstrong, whose tragic death is recorded on page 124, has been received from Capt. H. J. Round, who has been responsible for many radio developments in parallel fields.

The tragic death of Armstrong has given a sincere shock to all his friends, many of whom are on this side of the Atlantic.

The writer first met him in 1917 during the later stages of the war when he was a Major in the U.S. forces then going into Europe, and the friendship then established has been maintained throughout the years.

I had the good fortune to be given a very early demonstration of his superheterodyne in the Paris laboratory he had established, and, as the world knows, this basic invention was followed first by super-regeneration and in 1935 by wide-band frequency modulation.

This, as with some of his other inventions, involved him in very prolonged and expensive litigation, a good deal of which his closest acquaintances thought could have been avoided. However, the intensity with which he attacked technical problems he also applied to his legal problems and there is not much doubt in my mind that this double load clouded his very great intellect in the end.

Since those early years I have met him a few times and have been in constant correspondence with him, and I am happy to think that only a year ago I was able to spend considerable time with him in New York. A sentence of Armstrong's own in his recent paper on "The Spirit of Discovery," in which he eulogizes the work of Marconi, I think applies very

well to Armstrong himself: "It is seldom that a man makes two basic discoveries. When a man makes three, his attitude towards problems and his method of work merit close analysis and study." Armstrong should go down in American history as one of her great sons, worthy to be classed with Edison, Bell and Westinghouse.

INTERFERENCE LIMITS

THE publication by the British Standards Institution of a revision of the Standard specifying the limits of radio interference is of particular interest in view of the announcement that the two committees appointed to advise the P.M.G. on interference from small electric motors and refrigerators have now submitted their reports and, too, that he hopes shortly to lay regulations before Parliament.

The revised BS 800:1954* now covers Band 1 in addition to the long- and medium-wave bands. The limits of magnitude of noise voltages measured from each line terminal to earth are laid down as 750 μ V (40-70 Mc/s) and 1,500 μ V (200-1,605 kc/s) and the limits of noise fields at a distance of 10 metres are 50 μ V/m and 100 μ V/m for the respective frequency ranges. Measuring apparatus and methods of measuring are specified in BS 727:1954,† which has been revised and now covers the range 150 kc/s to 150 Mc/s.

* "Limits of Radio Interference," price 4s.

† "Characteristics and Performance of Apparatus for Measurement of Radio Interference," price 4s.

LAMP INTERFERENCE



THERE was some mild controversy in our correspondence columns last year over the question of radio interference from electric lamps. The writers of most of the letters contended that radiation was restricted to vacuum lamps, but others stated that trouble was also caused by gas-filled types.


The facts seem to be that neither kind is entirely free of blame, though the vacuum lamp is by far the most serious source of trouble, as it can radiate interference throughout its life and when in apparently perfect condition. Radiation from the gas-filled lamp,

on the other hand, usually occurs when the bulb is coming to the end of its life, and is produced by arcing across a minute break in the filament.

So far as television receivers are concerned, interference from vacuum lamps is generally of the nature shown in the accompanying illustrations (by John Cura). The double line of interference, as in the middle picture, is perhaps the most typical, though the single line on the left is not uncommon. The right-hand picture is an enlargement which shows (at top) the broken nature of a typical interference line.

Characteristic interference patterns produced on a television receiver by a nearby 60-watt vacuum (traction type) lamp.

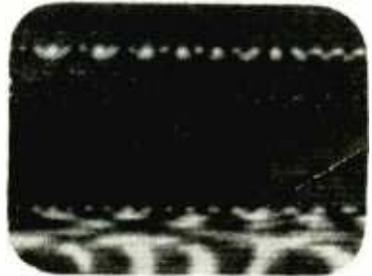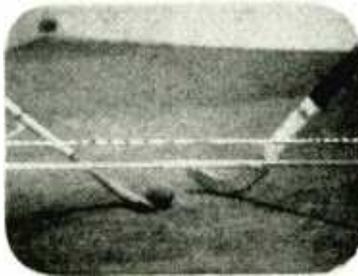

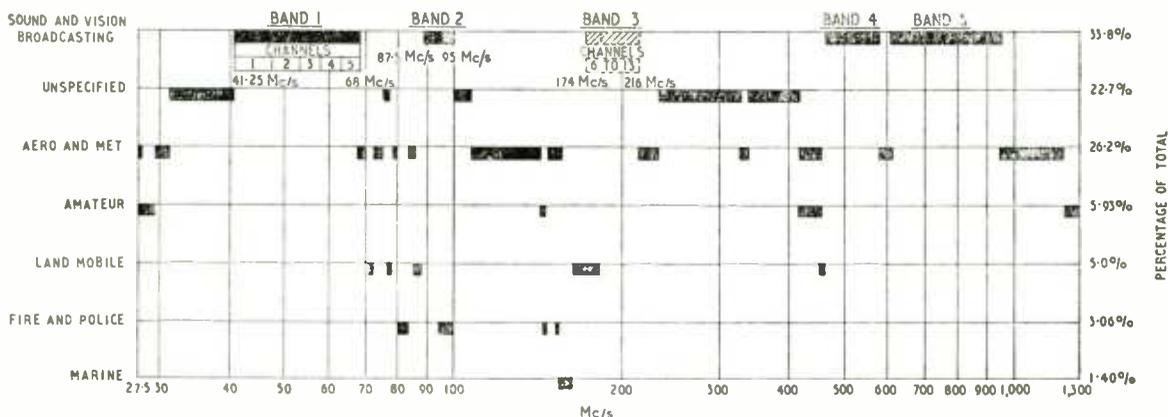

Squandered V.H.F. Channels

Why There is a Lack of Space for Television and Mobile Radio Developments

By J. R. BRINKLEY*

IT has been suggested in these columns and elsewhere that the administration of radio frequencies in this country is not working satisfactorily. The situation which has come to light as a result of the pressure for frequencies in Band 3 for additional television services is certainly disturbing and this article has been written in an attempt to clarify as far as possible in a short article what has become a very complicated situation.

The block allocation of the very high frequencies in the United Kingdom is shown at the head of this article and, in conjunction with the diagram, the following three points should be noted:—

1. The "single programme" service of the B.B.C. operating in the band 40-68 Mc/s has room for five 405-line TV channels. This block is probably more than adequate for nation-wide coverage with one programme.

2. The desire for competitive television in this country no doubt stems greatly from the example to be found in the U.S.A. where most large cities have a choice of two or three programmes and where New York has six and Los Angeles seven programmes, all operating on the *immediately practicable* frequencies below 216 Mc/s.

3. If the total frequency spectrum available below 216 Mc/s to sound and TV broadcasting in the U.S.A. (a total bandwidth of 92 Mc/s) were currently available in Britain, there would be no difficulty in providing multi-programme TV. It would, in fact, be rather easier, since a British TV channel requires only 5 Mc/s as against the American 6 Mc/s.

Why is it that instead of a total of 92 Mc/s, as in the United States, probably something less than

10 Mc/s can be found in this country for the immediate expansion of television? The answer is, that unlike the U.S.A. and most of the rest of Europe, the U.K. did not reserve adequate frequencies for television at the last International Conference (Atlantic City, 1947) and that subsequently, some of the frequencies which were reserved for television have been given to or taken by other services. Under the Atlantic City agreement, the world is divided into three regions and the U.K. and Europe are in Region 1. The Region 1 allocations to broadcasting (below 216 Mc/s) are 41-68 Mc/s, 87.5-100 Mc/s and 174-216 Mc/s—a total of 81.5 Mc/s. If these bands were available in the U.K., they would be adequate for immediate broadcasting requirements.

Of these three bands, however, it is now apparent that only the "B.B.C." block (Band 1) is available intact. There are two reasons for this: first, Atlantic City footnotes inserted by the British delegation which allocated parts of them to other services, and second, subsequent "national" allocations made in this country to other services. As a result, frequencies have been "lost" on the 87.5-100 Mc/s band to the police and fire services (95-100 Mc/s). Further frequencies have been "lost" in the 174-216 Mc/s to mobile and "fixed" services (174-184 Mc/s) and, in the band 200-216 Mc/s, to aeronautical navigation services (Distance Measuring Equipment—DME). Since the band 87.5-95 Mc/s is intended for sound v.h.f. broadcasting, the outcome of all this is that the only frequencies at present available for TV expansion lie between 184 and 200 Mc/s. But it is important to

* Pyc Telecommunications, Ltd.

note that when guard bands and other factors are considered, even this small band is probably not available intact.

We shall now examine the "intruding" services to see how they got where they are.

Aeronautical Navigation Services—200-216 Mc/s

The authority for operating these services is drawn from footnote 89 to the Atlantic City agreement which states—"In the U.K. DME will be operated on the band 200-235 Mc/s until such time as world standardization (of DME) on 1,000 Mc/s has been accomplished." This footnote precludes the use of TV in this band since it is obviously incompatible with DME. On the other hand, continental Europe plans TV stations in this band authorized by the agreement, which would make 200-Mc/s DME unworkable in the U.K. It will be observed in passing that world standardization of DME on 1,000 Mc/s was an even more remote possibility in 1947 than it is at this moment.

It is unfortunate, therefore, that these frequencies were earmarked for a service which is prejudiced by Continental TV planning, and yet at the same time could only be used by British TV stations by closing down such services and ignoring the Atlantic City provisions. (Footnote 87 states categorically—"the band 200-216 Mc/s is allocated for the aeronautical radio navigation service.")

Fixed Services—174-200 Mc/s.—These are point-to-point G.P.O.-type telephone links (e.g., between islands in the Channel Isles). International authority for them is obtained under footnote No. 87 which states "In the U.K., the band 174-200 Mc/s is also allocated for the fixed service." This footnote was not very realistic since with anything but exclusive band allocations, the planning of broadcasting services will prove unnecessarily difficult.

Mobile Services—174-184 Mc/s.—The occupiers of these frequencies include mobile services operated by

ambulances, railways, the Press, industrial users, electricity, gas and oil undertakings and the majority of radio taxi services. These services have been operating in this band since 1948-9. Such services were first allocated frequencies in the 70-Mc/s band, but in 1948 the G.P.O. made it known to manufacturers that all future allocations would be in the 156-184-Mc/s band which would be the "permanent and secure band for such services." This was a great embarrassment at the time since no suitable apparatus or valves were available for these frequencies. After 12 months development, fitting in the new band began and has been proceeding ever since. It was not realized, and the G.P.O. did not point out, that this allocation was not in accordance with Atlantic City. The recent official statement by the Postmaster-General that these frequencies will be cleared for TV has created a situation in which manufacturers and users, who have invested heavily in this band, have lost confidence in all official statements regarding the allocation of mobile frequencies. Their confidence will only be restored by adequate compensation for loss of frequencies and capital investments and written Government undertakings giving long-term security in any new arrangements made for them.

One of the outstanding shortcomings of the Atlantic City agreement and most of the subsequent planning provisions is that virtually no account is taken of guard bands. Thus, for example, in continental Europe one country may operate mobile stations up to the limits of the International allocation; for example, up to 174 Mc/s, and an adjacent country may operate TV down to 174 Mc/s. In the border areas, the two types of transmission will experience serious mutual interference, but both countries will be operating within their rights. A very substantial guard band will be required to obviate such interference, but no agreed assessment exists as to the extent of such guard bands or as to how their provision will be shared between the adjacent services.

This problem is equally important within the borders of any one country. In the U.K. it has a most significant bearing on the present Band 3 problems. The interference suffered will be two-way. It will be caused to the mobile service because as can be seen from Fig. 1, TV transmitters radiate appreciable power several megacycles beyond their allocated channels. Likewise, interference will be caused to the TV service because of the very poor selectivity employed in most TV receivers. An example of sound

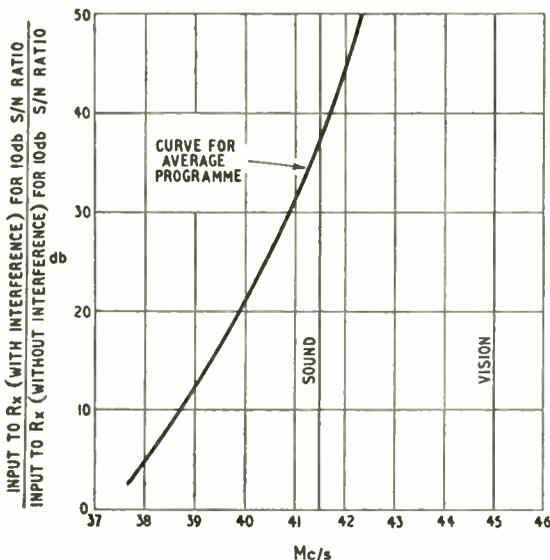


Fig. 1. This diagram shows the increase of wanted signal level required to restore the signal-to-noise ratio after the Alexandra Palace TV transmitter has been switched on. The out-of-band radiation was measured at 1½ miles from the television station.

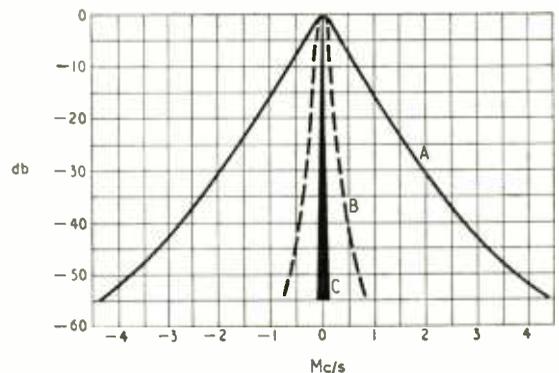


Fig. 2. Comparisons of the selectivity of different receivers. A, sound channel of typical television receiver; B, German domestic v.h.f. receiver; C, typical mobile v.h.f. receiver.

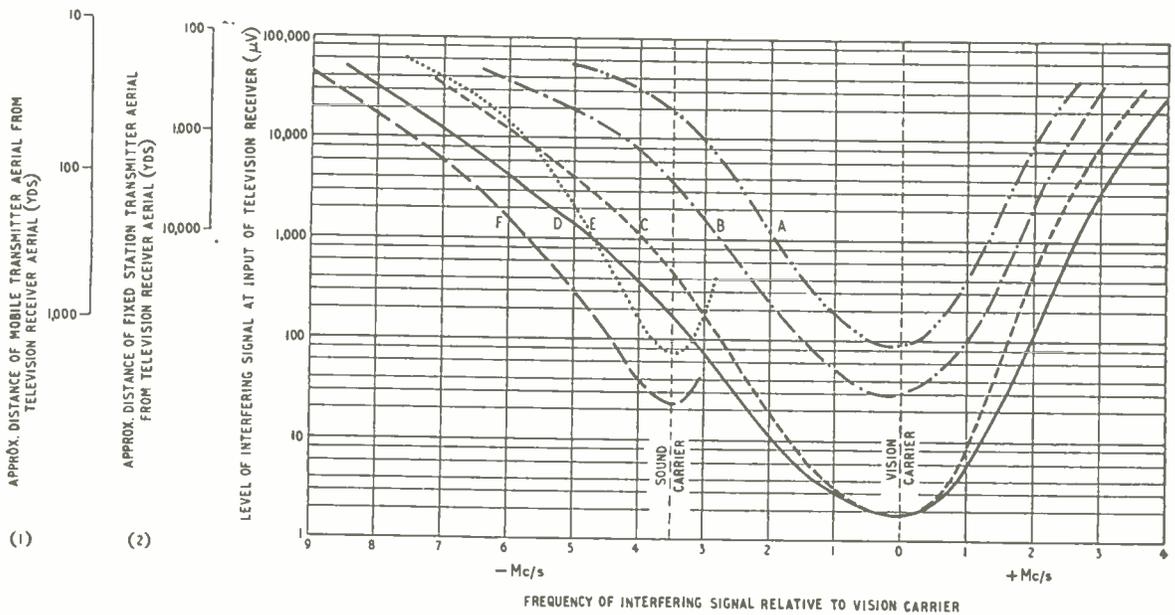


Fig. 3. Estimated interference from mobile services to TV receivers. The curves show the input of interference needed at the television receiver and frequency separation from the vision carrier for various conditions of interference. Curves A ($300\mu\text{V}$) and B ($30\mu\text{V}$) are for interference just sufficient to cause picture tearing, while C ($300\mu\text{V}$) and D ($30\mu\text{V}$) are for just discernible interference. Curves E ($170\mu\text{V}$) and F ($25\mu\text{V}$) are for just audible interference on the sound channel. The curves are for the TV signal levels shown in brackets. Scales are added to relate the interference input to distance in yards between the TV aerial and the aerial of a mobile transmitter (1) and a fixed transmitter (2), in both cases for a power of 15W.

channel selectivity characteristics is shown on Fig. 2. Television receivers have so far been designed without any serious attention being paid to providing adjacent-channel selectivity, and the effect of this is shown in Fig. 3, in which interference to a TV receiver from a mobile transmitter is estimated for various ranges.

This article is not necessarily a plea for adopting American methods of frequency allocation which have their own shortcomings and are being currently criticised. It is to be noted, however, that the present U.S. methods have made multi-programme TV widely available in that country, while "frequency shortage" is making it more than difficult in this country. Direct comparisons are not easy, but the U.S. achievement does not appear to have been at the expense of mobile radio development. There are estimated to be more than 300,000 radio equipped mobiles operating in the U.S. as against fewer than 10,000 in the U.K.

In America, the Federal Communications Commission has been able to publish a great deal of documentation on the subject of frequencies, much of which is well conceived. It is specific in matters of policy and detail in a way in which it is of the greatest possible value to manufacturers and operators alike. No such documentation is available in this country.

It is suggested that three preliminary steps are necessary to put frequency allocation on a sound basis. First, there must be a clear legal basis for frequency allocation. The only existing legislation relating to frequencies is the Wireless Telegraphy Act. This gives the P.M.G. the widest possible powers relating to the establishment of transmitting stations. But it has been stated that the P.M.G. does not regard himself as responsible for "overall" frequency allocation which is carried out by an "Inter-departmental Committee." This vital function is, therefore, apparently carried out by an anonymous committee for which

the writer can discover no legislative authority. Such an arrangement is not likely, in the writer's opinion, to produce the best results.

Secondly, there must be a clear declared policy in matters relating to frequency allocation. As an initial step in establishing a policy, the Government must make up its mind whether or not it intends to stand by the international frequency agreements to which it is signatory.

Thirdly, there must be adequate independent machinery to administer the policy laid down in an equitable manner. The writer suggests that the American F.C.C. is by far the most advanced example of such machinery to be found anywhere in the world to-day.

"Introduction to Valves"

MOST radio textbooks either take it for granted that the reader knows all about valves or deal with the subject rather sketchily. On the other hand, books written about valves specifically are often too highbrow and specialized, not to mention expensive. Where, then, is the radio man with only a nodding acquaintance of the subject to get the sort of information he wants? The answer is to be found in "Introduction to Valves" by R. W. Hallows, M.A.Cantab., M.I.E.E., and H. K. Milward, B.Sc.Lond., A.M.I.E.E. This is a comparatively small book, but a careful selection of material has ensured that its 152 pages and 107 illustrations provide just the right kind of information for everyday radio work.

An important feature of the book is that it explains the operation of the valves in typical circuits—they are not just left in mid-air, so to speak. Beginning with an exposition of fundamental principles, there are chapters on diodes as rectifiers and detectors; triodes; tetrodes and pentodes; multiple-grid valves for frequency changing; power-output valves; and valves for v.h.f. and e.h.f.

The book can be obtained from any bookseller, price 8s 6d, or direct from our publishers at 9s by post.

Cathode Follower Oscillator

Using RC Networks with a Voltage Step-up

By THOMAS RODDAM

IN an article in last month's issue I described an oscillator circuit in which the valve was connected as a cathode follower. The valve in this circuit really uses a cathode follower, too, with a sufficiently high cathode load for the negative feedback to dominate the system completely. The circuit was analysed as a particular circuit, but it was mentioned that it could be regarded as a member of a class of oscillators, those using over-balanced rejector circuits. In fact I had overlooked one variant, which is not a rejector circuit at all, so that the classification becomes just that of a cathode-follower oscillator. Most of these use only resistances and capacitances (or inductances), although last month's variant included all three types of element, and it is of some interest to survey the properties of the group as a whole.

The feature of the cathode-follower oscillators which makes them especially interesting is that most of them use a resistance-capacitance network to give a voltage step-up. When we think of an RC network we always see ourselves carrying out a lot of voltage divider calculations, and getting out less than we put

in: it isn't necessarily so, however, and the way in which these circuits provide the step-up is so simple that it seems incredible that no one should have spotted it before 1947.* We need a step-up, of course, if we want to use a cathode follower, because we can never get quite as much at the cathode as we put in at the grid. The step-up need not be very large.

First of all, let us look at the basic feedback oscillator. This is one way of looking at the general idea of an oscillator, a way which happens to be very convenient for purposes of analysis. The circuit is shown in Fig. 1 and it looks, indeed, just our old friend the feedback amplifier. As you will remember, the basic equations for this take the form:

$$\begin{aligned} V_2 &= A(V_1 - V_3) \\ V_3 &= \beta V_2 \\ \text{so } V_2(1 + A\beta) &= AV_1 \\ \frac{V_2}{V_1} &= \frac{A}{1 + A\beta} \end{aligned}$$

These are the equations in the form most convenient for amplifier working, with no minus signs to think about: some people prefer to put in a minus sign in the appropriate place, and with the gain as $m = \mu(1 - \mu\beta)$. It boils down to the same thing in the end.

As you can see, if $A\beta = -1$, the gain will be infinite, so that if we close the input terminals through a finite but very small resistance, the noise in this resistance will still be amplified up to the overload point of the circuit. In fact, it will oscillate, and that bit about noise was just to show how the oscillation starts. A practical oscillator will always have $A\beta = -k$, where $k > 1$, with very low level conditions, and the amplitude of oscillation will grow until something in the circuit alters A or β to reduce $A\beta$ to unity. It is perfectly possible for such a circuit, with $-A\beta > 1$, to be stable, and amplifiers which are "conditionally stable" have in fact been used. One of the advantages of the feedback amplifier approach to oscillator theory is that it helps to clarify the behaviour in these special cases, which are often associated with "mode jumping" and other awkwardnesses.

The other way of treating oscillators is to lump some components with the valve into a package which gives a negative resistance across two terminals. Transistors, with their built-in positive feedback, are easily considered in this way. Again we have two boxes, but the way the elements are split between them is different. The final answer must, of course, be exactly the same.

It will be clear that the problem which confronts us in designing a cathode-follower oscillator is that of obtaining a suitable network for the β box, remember-

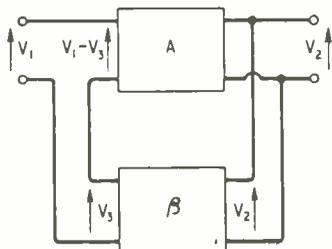


Fig. 1. The basic feedback amplifier or oscillator consists of the amplifier A and the feedback β .

Fig. 2. A passive quadripole with two input terminals, 1,2 and two output terminals, 3,4.

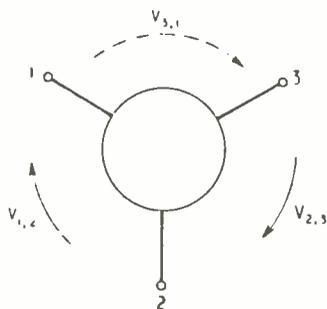
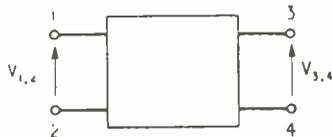


Fig. 3. If terminals 2 and 4 have an internal connection in Fig. 2, the system can be drawn like this. The input terminals are still 1,2, but the output can be taken from 3,2 or 3,1.

* "An RC Circuit Giving Over-Unity Gain", C.L. Longmire, *Tele-Tech*, April 1947

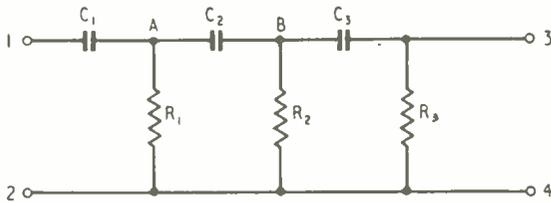


Fig. 4. Resistance-capacitance circuit used in the phase-shift oscillator.

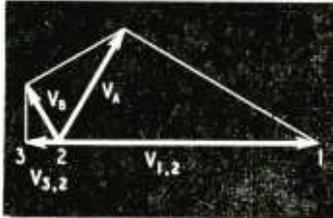


Fig. 5. Vector diagram for the voltages in Fig. 4.

ing that in the box marked A we have a gain of about 0.9 - 0.95 and no phase shift.

Let us consider the "passive quadripole" shown in Fig. 2. Just a box, with four terminals, of which two are called inputs (1, 2) and two called output (3, 4), looking unpleasantly like the introduction to some heavy mathematics. We can simplify matters by joining 2 and 4 together, because all the systems we want to discuss actually have got an internal connection here, which we usually think of as earth. This is the trap into which we must not fall. Let us re-draw the circuit in a more non-committal form (Fig. 3). The voltage arrows now run clockwise between each pair of terminals, and a new one, $V_{3,1}$, has been dotted in. When we apply a voltage $V_{1,2}$ across the input terminals 1, 2, we can now say that we get an output of $V_{3,4}$ across 3, 4 in Fig. 2, or outputs of $V_{2,3}$ ($= -V_{3,4}$ of Fig. 2) across 2, 3 in Fig. 3 or an output of $V_{3,1}$ across 3, 1 in Fig. 3. Quite clearly we must have $V_{3,1} = -(V_{1,2} + V_{2,3})$, and looking at Fig. 2 again this means $V_{1,3} = V_{1,2} - V_{3,4}$.

Suppose that the network inside the box in Fig. 2 produces a loss of n times, with a phase shift of 180 degrees. Then we shall have $V_{3,4} = -n V_{1,2}$, when n , of course, is a proper fraction. Obviously $V_{1,3} = (1 + n) V_{1,2}$. We can consider terminals 1, 2 as input, and 1, 3 as output, and we have got a step-up of $1 : (1 + n)$ in this network, which we thought was just attenuating and shifting phase.

So far we have been discussing the rather depressing "passive quadripole" but it may make things rather clearer if we consider a specific circuit. The circuit shown in Fig. 4 is the one we associate with the phase-shift oscillator. The limiting case of this network is when $C_1 R_1 = C_2 R_2 = C_3 R_3$ and $R_1 \ll R_2 \ll R_3$, and this limiting form

is particularly easy to analyse. At one frequency each RC section produces 60 degrees phase shift, so that the vector diagram shown in Fig. 5 is obtained, with V_A , the voltage across R_1 , equal to one-half $V_{1,2}$ and rotated 60 degrees. The following RC circuits each divide the voltage by 2, giving $V_{3,4} = -\frac{1}{8} V_{1,2}$.

As we have already shown, $V_{1,3} = (1 + n) V_{1,2}$, where n is here equal to $\frac{1}{8}$. Redrawing the circuit in the way shown in Fig. 6(a) we have a rather odd-looking network which provides a step-up ratio of 9 : 8 although it uses only resistance and capacitance elements. The network shown in Fig. 6(b) is the step-up version of the other phase-shift oscillator circuit, the one with the C's and R's interchanged, but this time it has been arranged rather differently to bring out two features of the circuit, the common connection at one side of the capacitances and the d.c. path on the output side.

These two circuits are often constructed with equal values of C's and R's, and the output voltage from the basic network is then only 1.29 times the input. This means that when twisted round we get only 30/29 times the input, which is very tight indeed for use with a cathode follower. There are various compromise solutions, all of which are inconvenient in one way or another.

Choice of Circuit

If we want to make the collection of diagrams more impressive, we can consider the 4-stage RC networks and also the corresponding 3- and 4-stage RL networks. There is a great deal of tedious algebra already published about these networks. Some of it can be replaced by common sense: for example, it needs no mathematics to see that the arrangement of Fig. 6(b) lets harmonics through easily, while if it were an RL network the harmonics would be attenuated. It needs no algebra to show that the input impedance of the Fig. 6(b) network is more than R_1 , and in the


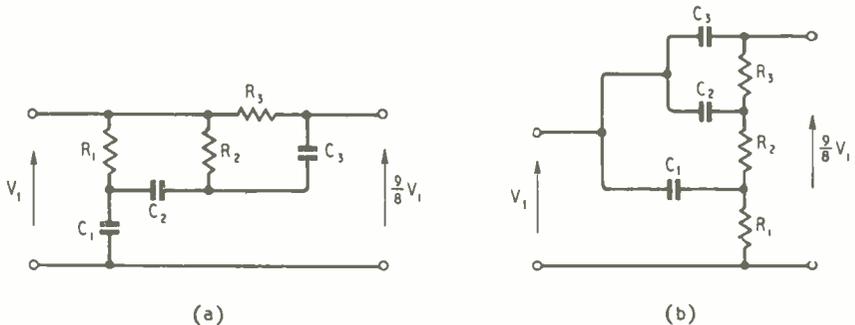


Fig. 6. The circuit of Fig. 4 can be redrawn either as in (a) or, if we take the output across 3,1, as in (b).

Fig. 7. The parallel-T on the left transforms to that on the right in its step-up form.

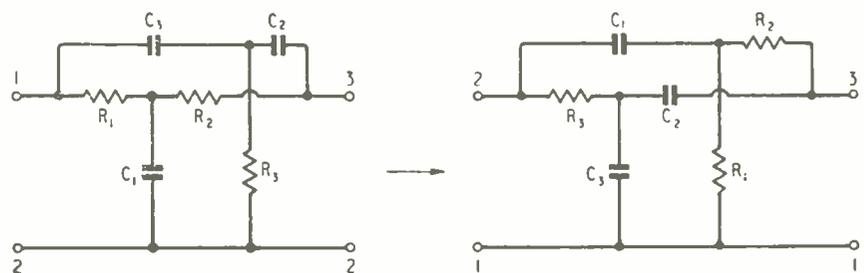

limiting graded case is $2R_1(R_1 + j\sqrt{3}R_1)$. In a practical design this input impedance will be part of the cathode load of the cathode follower, and the value of R_1 must, therefore, be high enough to provide the proper gain conditions.

The networks we have been considering so far have been phase-shift networks with some attenuation, but the attenuation has been of the smoothly falling kind: monotonic, the mathematicians call it. The only condition is that the network must be complicated enough to give more than 180 degrees phase shift.

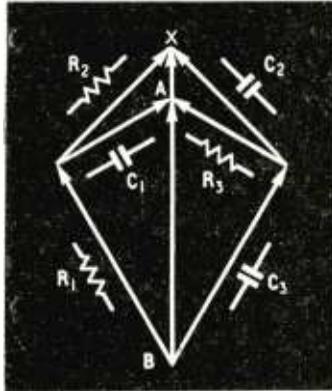
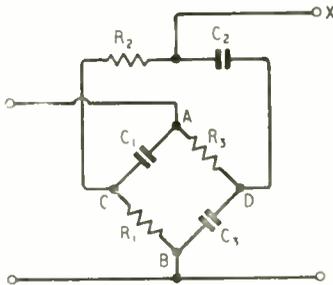


Fig. 8. Another way of drawing the transformed parallel-T circuit, and (right), a vector diagram of the network voltages.

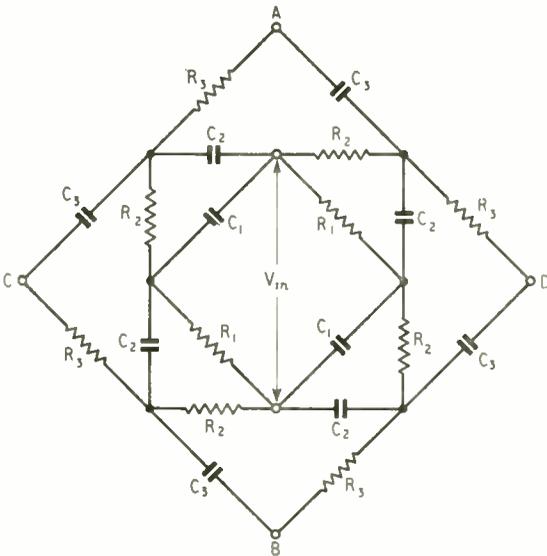


Fig. 9. Four-phase step-up network giving a measured gain of 1.67 at 640 c s. $R_1 = 100\Omega$, $R_2 = 1k\Omega$, $R_3 = 50k\Omega$, $C_1 = 2.5\mu F$, $C_2 = 0.25\mu F$, $C_3 = 0.005\mu F$.

We must now turn to the other sort of RC network, of which the parallel-T is the most familiar example. This network, in its basic form and its twisted round form, is shown in Fig. 7. We could write down the network equations and find out what happens: the answer, in the particular case, when $R_2/R_1 = C_3/C_2 = m \rightarrow \infty$, and $R_3/R_1 = C_3/C_1 = n = 0.41$, gives a step-up of 1.207 under zero phase conditions. A simpler way of seeing what happens is to draw the network in the form shown in Fig. 8 and build up a vector diagram on the assumption that the R_2C_2 arm does not load the rest of the network at all. This is, of course, exactly what the algebraists have done in taking $m \rightarrow \infty$. The resulting vector-diagram is shown in Fig. 9, and gives a clear indication of how the voltage step-up occurs.

You can have a busy time extending Fig. 8 too, and Fig. 9 (*Wireless Engineer* Jan. 1953, Fig. 6, p.21) shows how Bacon and Salmon have done this. Their network, with the values shown, was calculated to give a step-up of 1.98 times, and actually gave 1.68 times at 640 c s.

Just as the parallel-T network gives, in its twisted-round form, a desirable step-up, so does the series- π , its dual. As you would expect, the series- π gives a current step-up, but by working it back to front the wanted voltage step-up is obtained. A large collection

of these arrangements is given by S. C. Dunn in *Wireless Engineer* Jan. 1953 (Figs. 2 3), from which Fig. 10 has been taken (2c, 3e loc. cit.).

It is, I think, unnecessary to add the two variants of the bridged-T LCR circuit to this figure: the relationship between bridged-T and parallel-T is well known, and the advantage of the bridged-T, the very much higher Q, is another of those things which can be regarded as self-evident.

The circuit of Fig. 10 is obviously a very useful one for oscillators. The basic oscillator circuit is shown in Fig. 11, from which you can see that there is a convenient capacitance C/n^2 , across the grid-earth circuit to absorb some of the valve capacitances, and a d.c. path back for the grid to enable the bias conditions to be fixed. The resistance R_4 is rather inconvenient, because if it is large enough to make the cathode follower work properly it will upset the bias conditions. One way out of this difficulty is to replace R_4 by a transformer, the solution adopted in the oscillator described last month. The other easy way out is to split the bottom resistance R into two parts, R_1 and R_2 , which in parallel equal R, but are connected as in Fig. 11(b) to lift the grid positive. Provided that the supply voltage is sufficiently high, this arrangement should be very stable indeed because of the very large amount of d.c. feedback applied to the valve in such a way as to keep the cathode current constant.

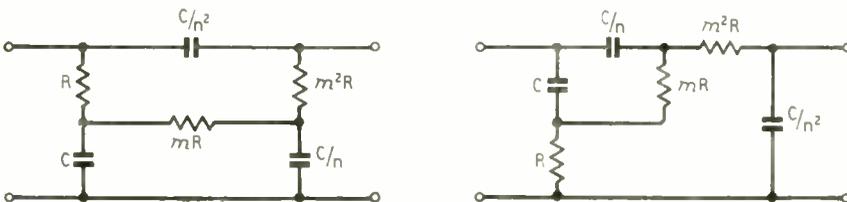


Fig. 10. The series- π network on the left can be twisted round to give the step-up network on the right. This form is especially convenient for use with valve circuits.

These oscillators which use the balanced type of network must not be confused with the parallel-T oscillators which are already well known. The common form of the parallel-T network applies negative feedback through the parallel-T, and some positive feedback through a separate resistive network. The negative feedback keeps the amplifier from oscillating except at the frequency at which the network is balanced. Here the only feedback is through the network, which does not operate at the normal balance point, but at what may be termed a special over-balanced point.

There is not much more to be said about these oscillator circuits, unless we settle down to calculate particular values. A great deal of the analysis has already been published by Dunn, and anyone who wishes to study the matter in more detail is recommended to refer to his paper and to the references

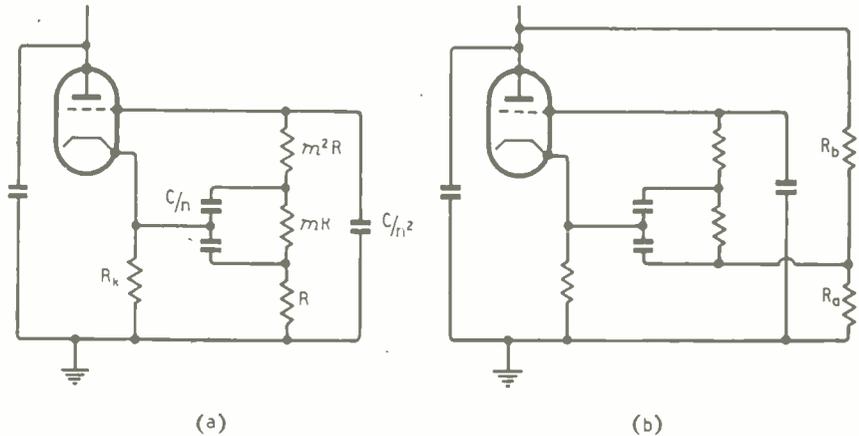


Fig. 11. (a) Basic oscillator derived from the circuit of Fig. 10, together with, (b) a modification, R_b and R_a replacing R , to get suitable bias conditions.

given at the end of it. This paper also discusses the use of the system under non-oscillatory conditions, as a selective amplifier. Feedback amplifiers incorporating RC networks are extremely useful for very low frequencies, where high values of Q cannot be obtained easily with LC networks, but this is outside the scope of this article.

CLUB NEWS

Birmingham.—The March 5th meeting of the Slade Radio Society will be held at the Imperial Hotel, Temple Street, Birmingham, at 7.30, when a film-illustrated talk on valve manufacture will be given by a representative of Mullard's. Sec.: C. N. Smart, 110, Woolmore Road, Erdington, Birmingham, 23.

Brighton.—Meetings of the Brighton and District Radio Club continue to be held at the Eagle Inn, Gloucester Road, Brighton, every Tuesday at 7.30. The club transmitter (G3EVE) is on the air on the second Tuesday of each month on 80 metres using both 'phone and c.w. Sec.: T. J. Huggett, 15, Waverley Crescent, Brighton.

Cleckheaton.—"Crystal Microphones and Pickups" is the subject of the talk by N. G. Newman, of Rothermel, Ltd., to be given at the meeting of the Spen Valley and District Radio and Television Society on March 24th. Meetings are held on alternate Wednesdays at 7.30 at the club headquarters in the Temperance Hall, Cleckheaton. Sec.: N. Pride, 100, Raikes Lane, Birstall, Nr. Leeds.

Romford.—"Television Interference and Transmitter Design" is the subject of the talk to be given by Louis Varney, A.M.I.E.E. (G5RV), to members of the Romford and District Amateur Radio Society on March 30th. Meetings are held each Tuesday at 8.15 at R.A.F.A. House, 18, Carlton Road, Romford. Sec.: N. Miller, 10, Rom Crescent, Romford.

S.E. London.—Meetings of the Clifton Amateur Radio Society (G3GHN) are held every Friday evening at the society's headquarters, 225, New Cross Road, S.E.14. Sec.: C. H. Bullivant (G3DIC), 25, St. Fillans Road, Catford, S.E.6.

Southend.—At the meeting of the Southend and District Radio Society on March 19th, G. T. Peck, of Ernest Turners, High Wycombe, will speak on the radio control of models. The society meets at the Municipal College Laboratories, Queens Road, Southend-on-Sea, on alternate Fridays. Morse and theory classes are again being held at 27, Park Road, on Tuesdays and Thursdays at 8.0. Sec.: J. H. Barrance, 49, Swanage Road, Southend-on-Sea.

Wellingborough.—A talk on television aerials will be given by J. W. Hobley at the March 18th meeting of the Wellingborough and District Radio and Television Society. The club meets each Thursday at 7.30 at the C.W.S., Silver Street, Wellingborough. Sec.: R. J. Henty, 6B, Silver Street, Wellingborough.

Wolverhampton. Amateur Radio Society recently moved to new headquarters at Stockwell End, Tettenhall, where the club transmitter (G8TA) is being installed. The club meets fortnightly on Mondays with Morse classes on the alternate Mondays. Sec.: H. Porter (G2YM), Applegarth, 221, Park Lane, Wolverhampton.

QRP.—Readers interested in the low-power operation of transmitters, whether it be for communication or the control of models, are invited by the QRP Research Society to send for details of membership and a specimen copy of the Society's journal. Contests for both transmitters and short-wave listeners are held throughout the year and a QRP net is organized each Sunday at 2.30 on 1.9 Mc/s. Sec.: J. Whitehead, The Retreat, 92, Rydens Avenue, Walton-on-Thames, Surrey.

Radio Control.—At the meeting of the Birmingham group of the International Radio Controlled Models Society on March 6th at 2.30 at the International Centre, Suffolk Street, Birmingham, J. Merrick will speak on "A Reliable Receiver." A demonstration of a radio-controlled model land vehicle will be given by R. F. Stock at the meeting of the London group on March 14th at 2.0 at the Horseshoe Hotel, Tottenham Court Road, London, W.1. Sec.: C. H. Lindsey, 55, Tenison Road, Cambridge.

Standard Valve Symbols

ADDITIONAL symbols for electronic tubes and valves, including gas switches, are given in Supplement No. 3 (1953) to B. S. 530:1948 (Graphical Symbols for Telecommunications). The basic electrode symbols are given, together with examples of their assembly to represent complete valves. The emphasis is on cold-cathode discharge valves and many of the symbols are unfamiliar ones. Travelling-wave valves, cavity magnetrons, velocity-modulation valves and photo-voltaic cells are included, as well as TR cells or gas switches. The Supplement is issued by the British Standards Institution, 2, Park St., London, W.1, price 2s 6d.

Measurement of Harmonic Distortion

Self-contained Direct-reading Instrument for Works Testing and Servicing

By T. D. CONWAY,* B.Sc.(Eng.), A.C.G.I., A.M.I.E.E.

NUMEROUS articles have been written on the general aspects of audio distortion, its detection, and cure, but these notes are intended to cover the specifically practical problem of measuring distortion on a mass production flow-line, and objectively assessing distortion in a service department handling audio equipments. Many methods of distortion measurements are already available, but on examination they were all found to require skill and time to give accurate results, whereas what was wanted was a direct-reading instrument capable of giving accurate repeatable measurements with unskilled labour.

This type of measurement is becoming of great importance in the manufacture of tape recorders, where it is usual to set the maximum recording level to correspond to a definite amount of distortion, which is a compromise between dynamic range and quality. The increasing emphasis on fidelity in amplifiers makes it necessary to check quickly performance figures of output against distortion to verify that the equipment meets the published specification.

In this article it is proposed to deal only with harmonic distortion, that is to say harmonics produced in the output of a system when a single frequency is applied to it: normally the amount of harmonics produced will depend upon the input signal and hence it may often be necessary to plot a curve relating input to distortion in the output. The distortion factor of a periodic voltage is the ratio of the total r.m.s. voltage of the harmonics (i.e., the square root of the sum of their squares) to the total r.m.s. voltage. When this figure is multiplied by 100 it gives what is known as the percentage of total harmonic distortion, or more simply percentage of total distortion.

In some cases where we know that a certain harmonic is more pronounced than others we may consider only its ratio to the total r.m.s. voltage, and this we will call the percentage of second or third, etc., harmonic distortion. In tape recorders the third

harmonic is dominant and of chief interest, as it is in push-pull amplifiers. In Class A triodes the second harmonic is dominant, and in pentodes all harmonics up to the fifth are usually significant.


When the percentage of total distortion is small (i.e., less than 10 per cent), it may be more simply expressed as the square root of the sum of the squares of the individual harmonic percentages. The calculated error of such a simplification is less than one part in two hundred,

i.e., $D_{total} = \sqrt{(k_2)^2 + (k_3)^2 + \dots}$ where $k_2 =$ percentage 2nd harmonic, $k_3 =$ percentage 3rd harmonic, etc.


In order to make a comprehensive assessment of distortion on a piece of equipment, measurements should be carried out over the whole of the working frequency range, due regard being paid to neglect those harmonics which lie outside the audible range. The test procedure is lengthy and considerable skill is needed to give the correct results. A simple system should be usable by unskilled labour, involve no calculation or charts, and preferably be direct reading.

Since we are more concerned here with the testing of distortion, the first simplification to suggest itself is the use of a single frequency, and to provide that frequency with the distortion-measuring circuit in a

Fig. 1 Colpitts oscillator and cathode follower with less than 0.25 per cent distortion.

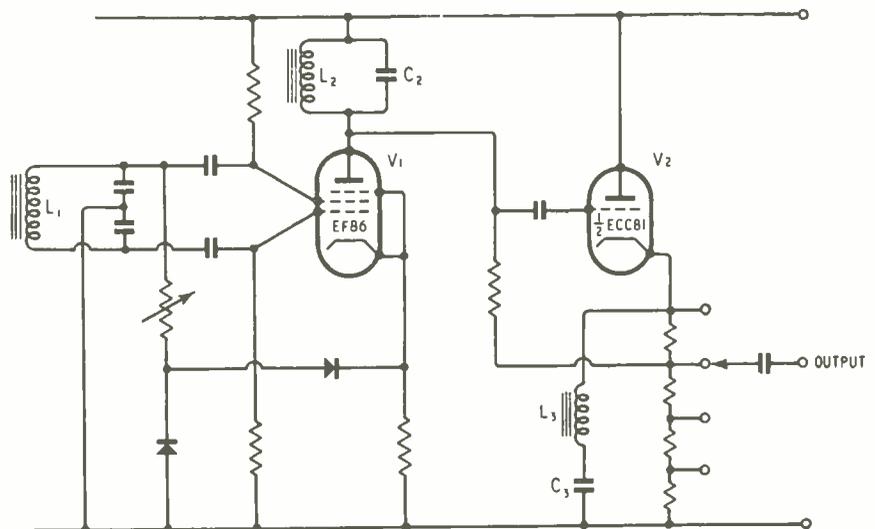

*Grundig (Gt. Britain) Ltd.

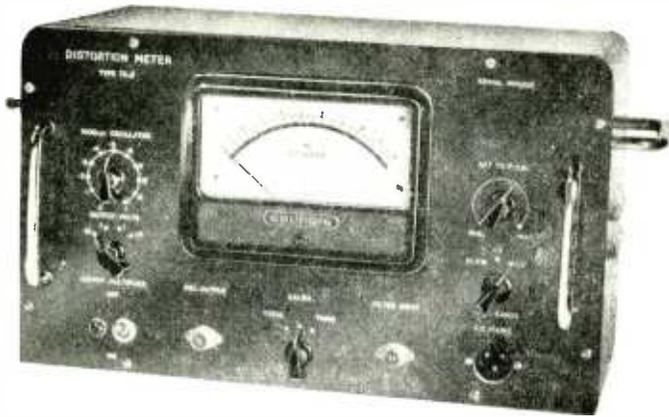

In the Grundig Type TGS distortion meter, controls associated with the 1,000-c/s oscillator are on the left and those for range selection and calibration on the right.

single self-contained unit. The next problem is to decide which individual harmonics are of interest, or alternatively whether the total harmonic distortion is to be measured. For our particular problems a frequency of 1,000 c/s was chosen, and it was decided to provide facilities for measuring either the percentage of total distortion or that of third harmonic distortion.

As explained previously a true measurement of total distortion involves the r.m.s. summation of all harmonics, and this can only be carried out by using either a thermal instrument, square-law valve voltmeter or a suitable dynamometer. For practical purposes these all have to be ruled out, and it was decided to carry out some tests on a "1-milliamp" full-wave bridge instrument rectifier, in conjunction with a 100-microamp meter. First, it was found that the superimposition of 10 per cent of second or third harmonic on the fundamental only affected the reading by less than ± 1 per cent as its phase was changed, hence as an indicator of the r.m.s. value of a distorted wave it is sufficiently accurate. Secondly, 5 volts of 2,000 c/s and 5 volts of 3,000 c/s fed together gave a deflection of 6.8 volts, which is within reasonable limits of the calculated value of 7.07; again phase variation between the two can cause a difference, but since all harmonics will be generated

from the original signal the phase relationship on any equipment should be constant.


An equipment was developed on the above lines, provision being made to measure up to 10 per cent of third or total harmonic distortion by direct reading, for a 1,000-c/s oscillator of low harmonic content having an output continuously variable up to 10 volts, and for the accommodation of inputs between 10 millivolts and 100 volts.


Oscillator Unit. The oscillator needs to be stable in operation and to have as low a harmonic content as possible. A Colpitts circuit was chosen and arranged as an electron-coupled oscillator to buffer the tuned circuit, with a tuned anode to reduce the output of harmonics. In order to maintain the minimum of harmonic content the amplitude of such an oscillator must be closely controlled, and as a first approach the h.t. supply was regulated by a neon type stabilizer. Next some attempts were made to limit the amplitude by negative feedback, but although this produced excellent results, satisfactory starting could not be guaranteed.

Finally a germanium diode was used between the anode of the oscillator and the cathode via a variable feed resistor which gave perfect control of amplitude. When oscillation starts the diode acts as a high impedance across the tuned circuit, biased by the cathode-to-earth voltage, and does not conduct. As the amplitude of oscillation increases the diode begins to conduct and increases the cathode potential of the oscillator, thus automatically controlling its amplitude. A high-impedance d.c. return for this current is provided by a second diode.

The final arrangement as shown in Fig. 1 was extremely stable and had a harmonic content of less than 1 per cent. A cathode follower was used for the output stage to give complete isolation and to provide a simple form of output attenuator. Since

Fig. 2. A three-section filter, with toroidally wound inductances, is used to suppress the fundamental.

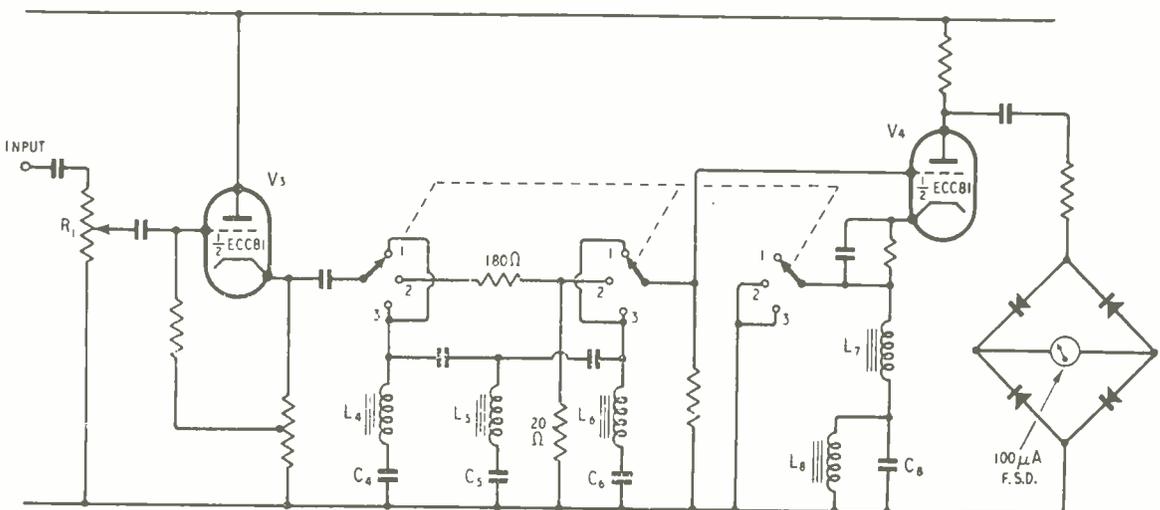

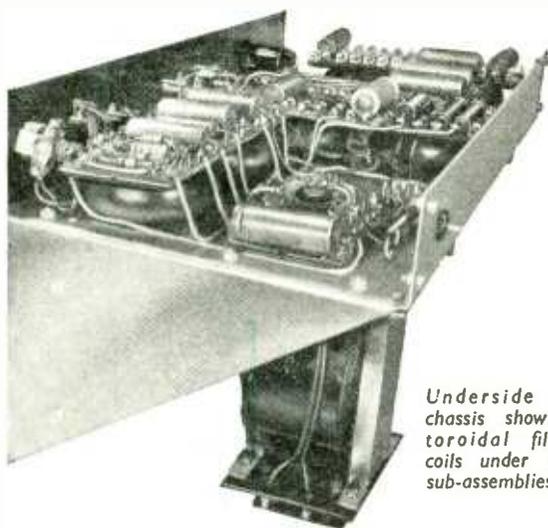

Underside of chassis showing toroidal filter coils under RC sub-assemblies.

a trace of second harmonic was introduced by the cathode follower, a simple acceptor circuit was added across the cathode load, bringing the total distortion content of the output down to less than $\frac{1}{4}$ per cent.

Distortion Measuring Unit. The design of filter units is greatly simplified by the use of low-impedance values, and this in turn limits the dangers of stray pick-up and removes the necessity for shielding. For the inductances toroidal windings were used, since high Q's can be readily obtained and the stray field is virtually negligible.

To remove the fundamental 1,000 c/s a three-section *m*-derived high-pass filter was employed, fed from a cathode follower input of approximately 200 ohms output impedance. Attenuating ranges were fitted both in the grid and cathode circuits so that a range of inputs between 100 millivolts and 100 volts could be accommodated.

The general circuit layout is shown in Fig. 2. In the central position (2) the signal passes straight from cathode follower input via a 10/1 attenuator to the output stage which has a full-wave bridge rectifier meter in its anode circuit. In the final arrangement an additional RC-coupled stage was added before the output valve in order to give sufficient gain to work at inputs down to 100 millivolts. A conventional "1-milliamp" full-wave bridge rectifier is employed with a 100-microamp movement meter. The incoming wave is adjusted by the input control R_1 to give full-scale deflection of the meter, and the instrument is now "calibrated" to measure the distortion of the incoming signal.

To measure the third harmonic percentage the switch is placed in position 1 when the signal passes first through the high-pass filter which attenuates the fundamental by 40 db. At the same time, since the 10/1 attenuator is now out of circuit, the gain has been increased by that amount and the full-scale deflection of the meter corresponds to only 10 per cent of the original signal. The cathode of the output valve, V4, now introduces two inductances L_7 and L_8 , and a condenser C_8 . L_8 and C_8 are tuned to 2,000 c/s and introduce very considerable negative feedback at this frequency, thereby eliminating the second harmonic from the output. At 3,000 c/s the L_8 - C_8 combination is capacitive, and L_7 is therefore added in series to resonate with it and give virtually

zero impedance: thus the third harmonic is amplified with low loss. In practice the amplifier gain is fractionally increased in the switching to make up the loss, which is about 2 db. All higher harmonics i.e., fourth, fifth, etc., suffer considerable attenuation due to negative feedback, and the output is the percentage of third harmonic distortion, the full-scale reading being 10 per cent.

For the measurement of percentage total harmonic distortion the switch is placed in position 3, when the 1,000-c/s fundamental is removed as before, but all harmonics are amplified equally and summated into the rectifier meter.

Mechanical Construction and Layout. The simplicity of the switching arrangements permits an easy and symmetrical layout of the front panel, as may be seen in Fig. 3. On the left is the oscillator unit with its output control and multiplier, and on the right the attenuator and input control to the distortion measuring unit. In the centre is a spring loaded switch, normally resting in the second position, for selection of the distortion measurement.

A normal folded chassis is employed, and, to avoid the necessity for special screening, the toroidal coils are placed underneath the chassis and clamped by the various tag panels; this form of coil is used throughout the equipment. The oscillator second harmonic rejector alone was screened.

Two double triodes ECC81 (12AT7) are used to provide the two cathode followers and the two RC stages; an EF86 is employed as oscillator with a 150B2 to stabilize its h.t. supply. No further h.t. stabilization was found necessary, but since the h.t. supply is derived from a full-wave bridge metal rectifier, a relay was added with its coil in series with the two cathode follower anodes. This normally shorts out the sensitive meter and prevents the series of bumps which occur as the valves warm up: it is also a useful transit protection.

Performance. Two of these instruments have been in continuous use for six months for setting the programme level meters of tape recorders. An endless tape is employed and recording is made at a standard input level and adjusted to correspond to maximum indicated recording level. It is immediately played back through the distortion meter. The programme level meter is successively adjusted till the required value of distortion is obtained, and it is found that with semi-skilled operators the whole of the adjustment and measurement may be completed in some two to three minutes.

For measuring distortion on audio amplifiers readings may be obtained immediately and quickly over a wide range of inputs; it is only necessary to adjust the input attenuators to full-scale deflection and then turn the switch for a direct reading. In conjunction with an output power meter a curve of distortion against output watts may be readily obtained.

The overall accuracy obtained on third harmonic measurement is ± 0.3 per cent distortion and on total harmonic distortion measurement ± 0.5 per cent distortion. These figures relate to the full scale of 10 per cent and are better on the lower half of the scale. Allowance can be made for the oscillator distortion if required, but since this is normally less than $\frac{1}{4}$ per cent for all measurements over half scale it may be neglected.

The author wishes to thank Mr. O. E. Dzierzynski for his assistance in carrying out the experimental work involved in developing this equipment.

Electronic Analogue Computing

Survey of Modern Techniques

SO much has been written recently about the truly wonderful achievements in the field of digital computing that there has been a tendency to forget about analogue computers and to overlook the progress they have been making. Indeed there are those who would say that the analogue computer is outdated and dispute the need to improve it further. It is hoped in this article to show that the need still exists, and further that the digital computer as it stands, in spite of its undoubted superiority in many cases, still has a long way to go before it can surpass the analogue device in all applications.

A useful distinction between the two classes of computer may be drawn by referring to analogue *instruments* on the one hand and digital *machines* on the other. The instrument handles continuously varying quantities, but to an accuracy limited by the attainable perfection of its manufacture: this is not easily made better than about one part in 10,000. The machine handles numbers expressed in finite digital form and is thus incapable of handling continuously variable quantities, but within this restriction is theoretically capable of any required finite degree of accuracy; in practice, accuracies of one part in a million are being achieved with machines of the size now available.

From what has been said, it will be clear generally that if problems of an essentially arithmetic nature are posed, and exact answers required, the digital machine is called for, but that if continuously variable quantities are to be dealt with the analogue device is more suitable. The precise nature of the difference between the two classes of computer will be evident if we consider the way in which the digital machine handles its input data. First of all, it samples its data at particular instants of time. Secondly, at each sample, it recognizes only a finite number of magnitude levels, i.e., it quantizes each sample of the data. In digital computer programming, it is good practice to try to equalize the errors due to sampling and quantizing. In the analogue instrument, the counterparts of quantizing and sampling errors are respectively the imperfections in the computing components, or the static errors, and the finite response times of the computing servos, or the dynamic errors. Again, the best design requires these errors to be of equal magnitude.

Optimum balancing of the computing errors is not the only factor to be taken into account, however, in the choice of a computing system. It is sometimes essential for a natural time scale to be used in the computation, for example in certain classes of simulator.

In a simulator the system to be studied is represented by the circuits of the instrument, and the

behaviour of these circuits is studied under representative working conditions. A natural time scale is essential when actual components are to be inserted, as is done sometimes to allow a check on their performance during design. These component tests may be carried out not only under representative circuit performance conditions but also under representative operating conditions of temperature, humidity, vibration and the like. It is also possible to reproduce the conditions under which a human operator is included in the servo loop.

In problems of any degree of complexity, where operation in natural time scale is desired, digital computers are sometimes too slow. Since limitation in speed of response is a characteristic of digital computers that is not always appreciated, it may be of interest to illustrate it by means of an example. In some work on the behaviour of a controlled missile, a problem was posed which involved the time de-

pendence of the missile's position and attitude in space, as well as the behaviour of certain important parts of the control system. A simplified mathematical description of the problem involved over twenty first-order simultaneous differential equations, and these were solved on the Manchester University digital computer using a step-by-step method of integration in which the step interval was adjusted according to the shortest time constant of interest in each part of the solution.

It was found that, in a range of interest where a time interval of an eighth of a second was adequate, investigation of each ten seconds of the solution took just over an hour of computing time, i.e., the ratio of machine time to natural time was about 400. In another range, where step intervals of 1/32 second were used, the ratio worked out to 1,800. Time ratios of this order of magnitude appear to be typical for problems of this degree of complexity. In many cases, as in the example given, such a change of time scale is unimportant because the time is available, but in other cases, as we have seen in connection with the simulator, operation in the natural time scale is often essential. In some applications, where the analogue simulator or computer is used purely for design purposes and high accuracy is not the primary requirement, it is convenient to arrange for the computer time scale to be much less than natural and to display the response of the system to a repetitive square wave on the screen of a cathode ray tube. The results of any changes in system parameters may then be observed directly with consequent saving of a great deal of the designer's time.

By

RAYMOND B. QUARMBY*

M.Sc., M.I.E.E.

* Ferranti, Ltd

In other problems where the data provided are continuous and high accuracy answers are required continuously, either in the natural time scale or faster than this, neither the digital nor the analogue computer may be capable of dealing with the situation adequately. It is evident that there is a need for faster digital machines, of the order of 100 to 1,000 times faster than the present Manchester machine, and also a need for electronic analogue devices of 100 to 1,000 times the accuracy at present attainable. It may be that the solution will lie in the development of a machine using a combination of both computing techniques.

D.C. Amplifier Networks

Most of the accurate analogue computing being carried out in this country at the present time is done on electro-mechanical analogue computing instruments which use techniques developed during the war for anti-aircraft predictors and component production facilities set up at that time. While computers of this type have been considerably improved in recent years, a new and interesting field is now being opened up by the use of all-electronic devices, which require no moving parts.

In these electronic techniques the basic computing procedures of scale changing, adding, subtracting, integrating and differentiating may be carried out by d.c. amplifier networks, as shown in Fig. 1. Though balanced amplifiers have some advantages, mainly in reduced h.t. smoothing demands, a form of d.c.

amplifier often used is the unbalanced one shown in Fig. 2. It is a three-stage amplifier with resistive interstage coupling; the odd number of stages ensures an overall sign reversal and permits feedback, while the direct coupling between stages permits operation at frequencies down to zero. As the overall gain of such a three-stage amplifier may be several tens of thousands, a small grid-to-cathode input potential suffices to produce the full output. In this case, the amplifier gain is about 50,000 and the output varies over a range of ± 150 volts, so that the required grid-to-cathode voltage variation is only ± 3 millivolts. Thus, in the normal operating state the input grid may be considered as being at earth potential.

A circuit incorporating a d.c. amplifier of this type which can be used either for scale changing or for sign reversing is shown in Fig. 1(a). The input voltage, E_1 , is applied to the input grid through a resistor, R_1 . Neglecting the feedback resistor, R_0 , for the time being, it will be seen that since the input grid is virtually at earth potential the input current, I_1 , is given by Ohm's law as:

$$I_1 = \text{input current} = \frac{\text{input voltage}}{\text{input resistance}} = \frac{E_1}{R_1}$$

This flow of current drives the input grid (Fig. 2) positive in potential and the amplifier responds by driving the output anode voltage down. Considering now the action of the feedback resistor, R_0 , it is evident that it draws from the input a current of magnitude $I_0 = E_0/R_0$ and that this current increases until it equals the current I_1 , when the amplifier settles down to steady state operation. Equating the expressions for the currents I_1 and I_0 gives:

$$(E_1/R_1) + (E_0/R_0) = 0$$

or $E_0 = -E_1(R_0/R_1)$, while if the input and feedback resistors are equal in value $E_0 = -E_1$, i.e., the output is equal in magnitude to the input but has opposite polarity.

Since a large current may be taken from the output without causing a drop in the output voltage, these amplifiers are often used as buffer stages between high output-impedance circuits and their loads.

If two input resistors are provided, as shown in Fig. 1(b), then the current drawn off from the grid through the feedback resistor equals the sum of the input currents, i.e., the output voltage is equal to minus the sum of the input voltages. The accuracy of the summation depends, of course, on the accuracy with which the resistors can be matched;

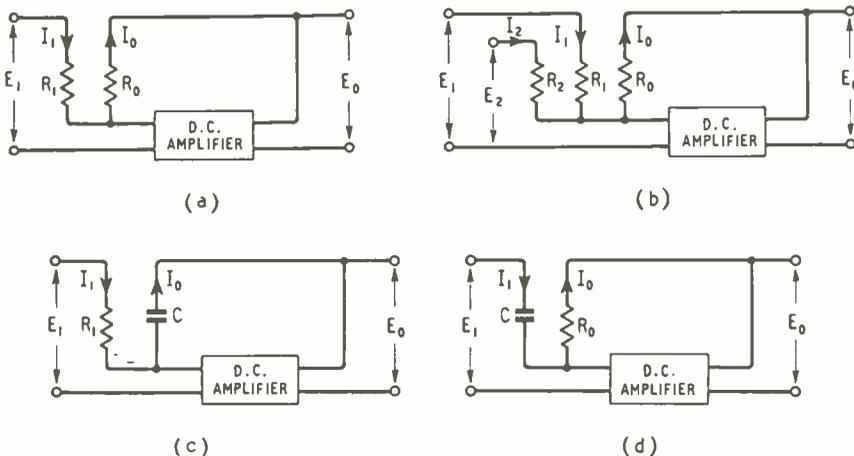


Fig. 1. D.C. amplifiers used for (a) sign reversing, (b) summation, (c) integration and (d) differentiation.


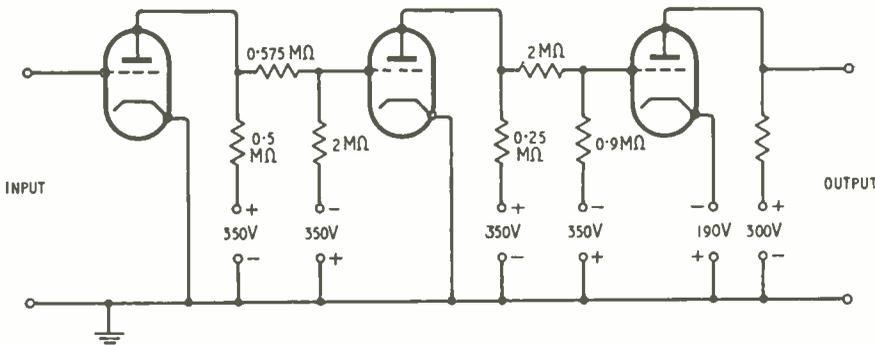


Fig. 2. Unbalanced d.c. amplifier suitable for circuits such as those in Fig. 1.

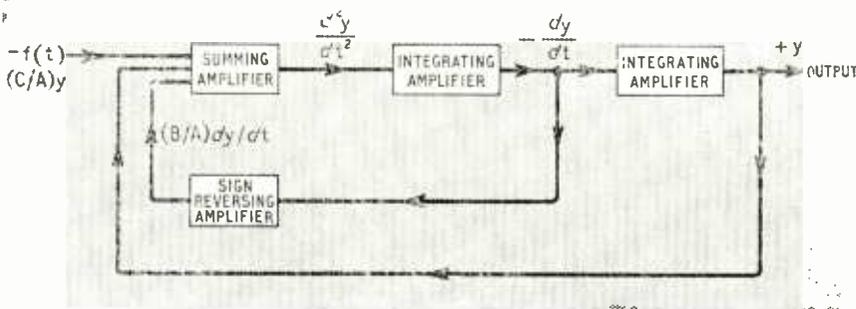

Left: Fig. 3. Four d.c. amplifiers arranged as a differential analyser.

high stability wire-wound resistors are normally used. Subtraction is achieved by the addition of a voltage of opposite polarity.

Incorporating a capacitor in the feedback loop in place of the resistor, as shown in Fig. 1(c), converts the arrangement into an integrator. Since the current passed by the capacitor is proportional to the rate of change of the voltage across it, we have

$$E_1/R_1 + C dE_0/dt = 0 \text{ or } E_0 = -(1/CR_1) \int E_1 dt$$

Polythene capacitors are usually employed because of their high leakage resistance.

With the capacitor in the input, as shown in Fig. 1(d), the arrangement becomes a differentiating circuit, and $E_0 = -CR_0 dE_1/dt$. One drawback to differentiating amplifiers is their tendency to accentuate any irregularities in the input voltage. When a computer is being set up for the solution of a differential equation, however, it is always possible to rearrange this in the form of an integral equation. The solution then allows the use of integrators in place of differentiators.

Differential Analyser

An arrangement of four d.c. amplifiers for solving a second-order differential equation is shown in Fig. 3. The equation solved is:


$$Ad^2y/dt^2 + Bdy/dt + Cy = f(t)$$

and its solution is a time function, $y(t)$, representing the response of a system with two energy storage components, A and C, and an energy dissipating component, B, to a forcing function of time, $f(t)$. When the system is linear, A, B and C are constant and this is assumed in this case.

The first amplifier is connected for summing and the quantity d^2y/dt^2 is assumed to exist at its output. This is then fed to the second amplifier, connected as an integrator, in which $-dy/dt$ is evaluated. The third amplifier is also an integrator and gives y . In the first amplifier, d^2y/dt^2 is evaluated by summing the three terms $(B/A)dy/dt$, $(C/A)y$ and $-f(t)$, the various proportions in which they are summed being obtained by a suitable choice of the input resistors. The fourth amplifier is needed to give a sign reversal to the quantity $-dy/dt$. Initial conditions, representing the levels in the two energy stores, are set into the two integrators before the forcing function is applied. This forcing function is sometimes just a step function; at other times, however, a repetitive solution is required and then a continuous square wave is applied. This enables the solution for y to be presented as a steady trace on a cathode ray tube provided the frequency of the square wave is high enough to avoid flicker.

Usually it is convenient for the repetition frequency

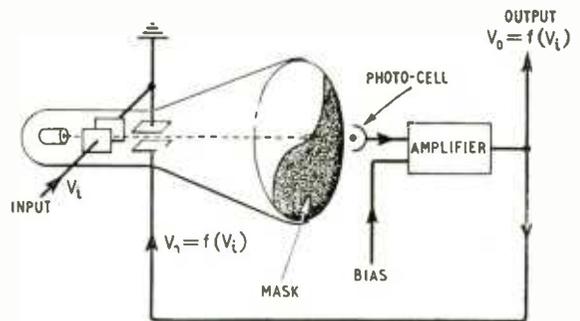Below: Fig. 4. Electronic function generator in which the required function of the input voltage is represented by the profile of a mask.



to be that of the mains. The time scale will then be chosen to allow the whole output transient to occur in less than 1/50th second, and also to allow enough time for the flyback and reset of initial conditions.

If a plot of the response is required, inaccuracies are introduced in trying to obtain this from the cathode ray tube screen directly. It is better to use a pen recorder, in which the accuracy is comparable with that of the computing network and in which the paper drive mechanism can have a greater speed constancy than the cathode ray tube time base. One way of doing this is by sampling the output waveform with a pulse of repetition frequency slightly different from the 50 c/s, so obtaining from each successive transient a portion slightly displaced from the last. The pen recorder, being unresponsive to frequencies as high as 50 c/s, will draw a smoothed version of the required response, though taking the whole of a beat period to do so.

Function Generators

With the aid of a multiplying device, or a non-linear function generator, it is possible to solve more complicated equations in which the coefficients A, B and C are no longer constants but functions of time. The circuits used do not differ radically from that of Fig. 3, and the method of getting the answer is very similar. The same cannot be said of the analytical solutions, as the modified equations are much more difficult to solve than the linear.

An all-electronic non-linear function generator developed recently is shown in Fig. 4. It consists of an opaque mask, having a profile representing the required function, placed on the screen of a cathode ray tube. A photocell receives light from the fluorescent spot on the screen when this is not obscured by the mask, and the output of this photocell controls the voltage applied to the vertical deflecting plates, through an amplifier. The input voltage is applied to the horizontal deflecting plates and causes the spot

to move horizontally. A bias voltage is applied through the amplifier to the vertical deflecting plates in such a sense as to cause the spot to rise until it reaches the edge of the mask. As the spot becomes unmasked, the photocell input to the amplifier opposes the bias increasingly until the amplifier output attains

a value at which the spot is prevented from rising further. The spot is thus forced to follow the mask profile, and the required function of the input voltage is generated at the output terminals of the amplifier. This device has been used in an aerial simulator to represent the functional relationship between aerial gain and offset angle, and can be used to simulate any empirical relationship of this kind.

Arrangements of biased diodes allow the representation of various non-linear saturation characteristics, such as occur in the simulation of mechanical systems. Fig 5 (a) shows two diodes arranged to limit the output of an amplifier and the full lines in Fig. 5(b) show the resulting output characteristic. Diode V_1 conducts when the output voltage, E_o , exceeds the bias voltage, E_1 , so E_1 corresponds to the maximum value of E_o which can be passed. Conversely, V_2 conducts when E_o is less than E_2 , so this voltage corresponds to the minimum value of E_o . The circuit thus gives a characteristic typical of a system with position, rate or torque limits.

When a characteristic representing friction torque as a function of speed is to be generated, a circuit similar to that in Fig. 5(a) is used, but without the feedback connection to the amplifier input. The amplifier then drives its output to the limiting value for any slight departure of its input voltage from zero, in either the positive or negative direction. The resulting characteristic, which is of the desired form, is shown dotted in Fig. 5(b).

A dead zone often exists in mechanical instruments and this may be represented, in a computer, by the arrangement of Fig. 6(a). If the input signal θ_1 is positive, it must exceed $+E$ for the diode V_1 to conduct or, if negative, be less than $-E$ for the diode V_2 to conduct. A positive or negative threshold of value E is thus introduced into the output θ_o as shown in Fig. 6(b).

The inclusion of a capacitor at the output, as shown in Fig. 7(a), somewhat modifies the behaviour of the circuit. The diode V_1 now conducts when $\theta_1 - \theta_o > E$, and V_2 when $\theta_1 - \theta_o < -E$. This results in the characteristic of Fig. 7(b), which represents the backlash in a system of gears. If a limiter is combined with this arrangement a hysteresis characteristic results.

Approximating Characteristics

The method may be extended to the approximation of any non-linear function to within specified limits of accuracy by a number of straight-line sections, provided the slope of the characteristic remains of the same sign throughout. If the slope of the required function varies in sign then the characteristic is obtained as the sum of a number of simpler characteristics. A high-speed electronic differential analyser at the University of Bologna has function generators of this type which permit any function to

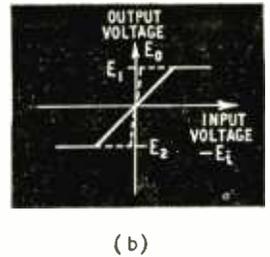
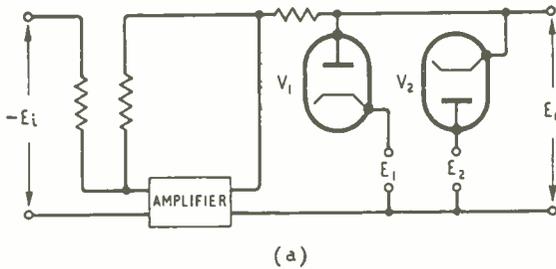


Fig. 5. Arrangement of biased diodes to simulate a mechanical system with limits on displacement, rate or torque.

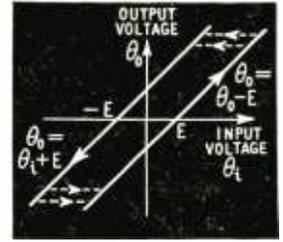
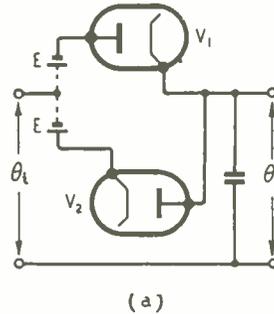


Fig. 6. Biased diodes simulating a dead zone in a mechanical system, as shown by $-E$ to E in (b).

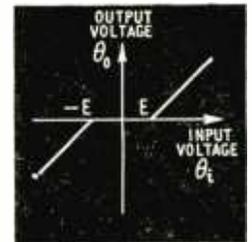
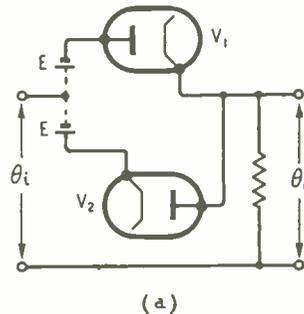


Fig. 7. Including a capacitor in the Fig. 6 circuit modifies the characteristic to represent backlash in a system of gears.

be set up as a combination of ten connected line sections whose slope and length can be adjusted independently.

An application of the method is shown in Fig. 8. At low input voltages, when the diodes are all biased off, the circuit acts as a simple potential divider, but as the input voltage increases the diodes become conducting one after the other and make the effective potential divider ratio progressively less. With the circuit values and bias voltages shown, the arrangement gives a logarithmic law over a wide range, and this particular circuit has been used as an attenuator for compressing voltages from one to 1,000 volts, so allowing the voltage values in both low- and high-level regions of the signal to be read on a meter to the same percentage accuracy.

A good deal of attention has been given recently to the development of fast multipliers. Some work has been done on improving the speeds of response

of electromechanical devices, but purely electronic devices are more common.

One form of electronic multiplier uses a cathode ray tube and photocells, as shown in Fig. 9. There are the usual vertical and horizontal deflection plates in the neck of the tube and a coil is fitted round the tube in the vicinity of the horizontal deflection plates. One of the input voltages, V_1 , is applied to this coil and produces a magnetic field along the axis of the tube of magnitude proportional to V_1 . So long as the electron beam is undeflected, the electron beam current acts in the same direction as this magnetic field and does not interact with it. When, however, the second voltage, V_2 , is applied to the vertical deflection plates it imparts a vertical velocity to the electron beam so that the beam current now has a component in the vertical direction of magnitude proportional to V_2 . This component of the beam current interacts with the axial magnetic field and produces a force on the electron beam, in the horizontal sense, of magnitude proportional to the product $V_1 V_2$.

The tube face is divided by a vertically placed knife edge having a photocell on either side. This enables any horizontal deflection of the beam to be detected as a difference signal, which is amplified and applied to the horizontal deflection plates in a restoring sense. The resultant behaviour of the system is to produce a voltage across the horizontal deflection plates proportional to the product of the two input voltages.

In another electronic multiplier, the mark space ratio of a repetitive square wave is made to depend on one voltage, and its peak-to-peak amplitude on another. The detected and smoothed output then varies as the product of the inputs. A multiplier

width and adequate suppression of side lobes. Since high accuracy is not demanded, an electronic computer may be used, and the computed radiation patterns presented on the screen of a cathode ray tube. This allows the designer to see at once the effect of changing any design parameter and speeds up what is essentially a trial and error process.

Synthetic Radiation Pattern

The voltage which produces the synthetic radiation pattern on the c.r.t. screen is an analogue of what would be measured by a field-strength measuring set moving in a circle round the real aerial array. In the real array the waves emitted from the elements would combine to produce various maxima and minima which would be detected by the revolving measuring set. The same effect is obtained in the computer by combining a number of 450-kc/s r.f. carriers, corresponding to the emissions from the elements, after modulating their respective amplitudes and phases in different ways corresponding both to the amplitudes and phases of the currents fed to them, and to the transmission lags between them and the rotating measuring set. Thus at various points on the modulating cycle the resultant carrier output goes through maxima and minima analogous to the maxima and minima detected by the measuring set at corresponding points on its circle of rotation. Fig. 10(a) shows the apparatus for simulating the contribution of a single element, while (b) shows the combining and display system.

In order to obtain a continuous presentation of the maxima and minima on the c.r.t. screen the modulating

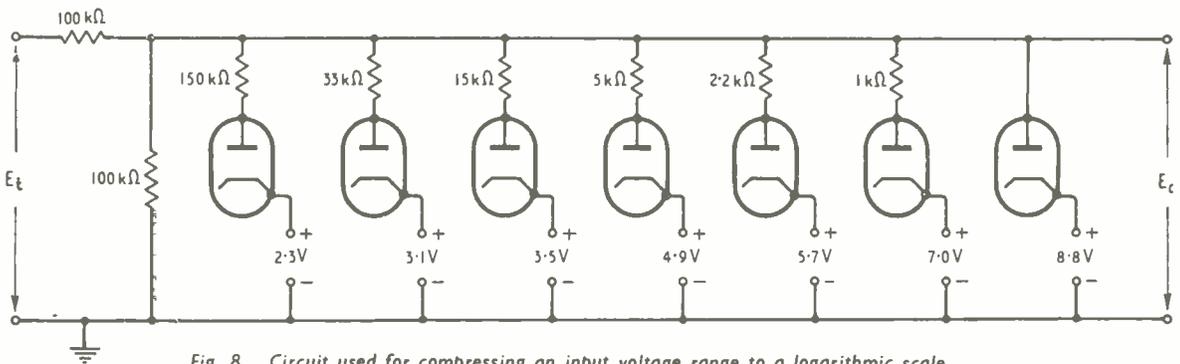


Fig. 8. Circuit used for compressing an input voltage range to a logarithmic scale.

may also be made from function generators arranged to give square law responses. If two such generators are arranged to evaluate $(A+B)^2$ and $(A-B)^2$, their difference, when scaled down by a factor of four, is equal to the product AB .

Large computing assemblies, being expensive, are rarely justified when suited only to the solution of a special problem. The exceptions to this rule are when the problem has to be solved quickly, as in an anti-aircraft predictor, or frequently, in which case substantial savings in computing effort may rapidly outweigh the initial cost. An example in this latter class is the aerial radiation pattern computer constructed recently at the Telephone Manufacturing Company.

Aerial array design involves computing a great variety of radiation patterns until one of suitable form is found, which has the right compromise between the conflicting requirements of narrow main lobe

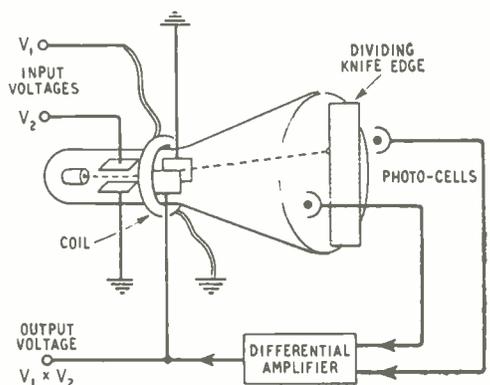


Fig. 9. Electronic multiplier using a cathode ray tube and two photo-cells.

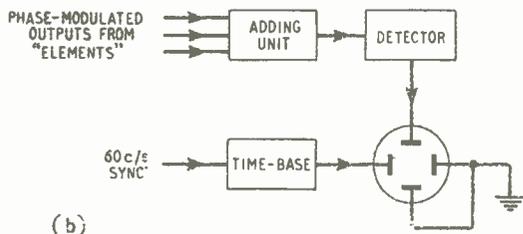
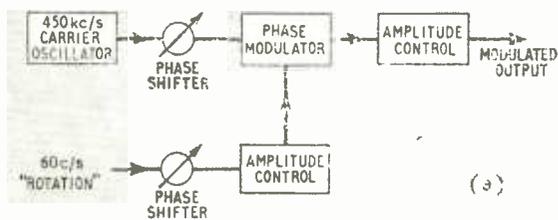


Fig. 10. Aerial radiation pattern computer with (a) apparatus for simulating contribution of a single element, and (b) combining and display system.

cycle is chosen to be 60 c/s and the time base is synchronized with this frequency. (This being equivalent to a rotation of the hypothetical measuring set round the array sixty times in every second.) Thus, with the azimuth angle represented along the time base and the combined carriers applied to the Y plates, the radiation pattern is presented in rectangular co-ordinates. Manual adjustment of the amplitudes and phases of the 450-kc/s carriers gives the effect of

similar adjustments to the currents in the elements of the real array, while alteration of the amplitudes and phases of the 60-c/s modulating signals gives the effect of changing the positions of these elements.

Very often the problem to be solved does not justify the building of such a large special-purpose computer. In this event it is sometimes possible to arrange for the problem to be solved on a general-purpose computer, which can be used in the solution of a large variety of problems and so be more economical. General-purpose electronic analogue computers have been built at the National Physical Laboratory, Teddington, and also at the Royal Aircraft Establishment, Farnborough.

The N.P.L. computer is intended mainly for use in the design of servo systems and comprises exponential time delays, pure time delay or distance velocity lag, balanced d.c. amplifiers, mixers, integrators, square-wave and pulse generator working at 1,600 c/s, phase advancers, resonant circuits, and an on-off controller. Combinations of these elements allow most types of servo to be studied.

By contrast, the R.A.E. computer is arranged as a differential analyser, similar to those discussed previously but more complex. It comprises 16 integrators, 15 summing amplifiers, 12 curve followers or function generators, 15 multipliers, and 30 units for scaling and inserting initial conditions. The multipliers are of the variable mark/space ratio type previously described; all the other units are based on unbalanced d.c. amplifiers.

One very large use of differential analysers of this type is in the solution of flutter and vibration problems in airframe design. Since the data on which designers work are very rarely accurate to better than a few per cent, highly accurate computers are out of place, and the purely electronic type with repetitive solutions presented on the screen of a cathode tube is ideal.

BOOKS RECEIVED

Radio Receiver Design, by K. R. Sturley, Ph.D., B.Sc., M.I.E.E. Revised second edition of Part 1 dealing with radio-frequency amplification and detection. Pp. 667+xx; Figs. 260. Price 56s. Chapman and Hall, 37, Essex Street, London, W.C.2.

Low-frequency Amplification, by Dr. N. A. J. Voorhoeve. Philips Technical Library treatise on the principles of a.f. amplifier design, with chapters on auxiliary apparatus and acoustics as applied in sound reinforcing systems. Pp. 495+ xv; Figs. 479. Price 50s. Cleaver Hume Press, Wright's Lane, Kensington, London, W.8.

Ultra High-frequency Radio Engineering, by S. A. Knight. Elements of the theory of transmission lines, wave guides, magnetron and klystron valves, etc., with chapters on propagation and aerial systems. Pp. 256+ viii; Figs. 202. Price 21s. Sir Isaac Pitman and Sons, Parker Street, London, W.C.2.

Microwave Spectroscopy, by M. W. P. Strandberg. Theory of molecular rotational states and their measurement by interaction with microwave fields. Pp. 140; Figs. 15. Price 9s 6d. Methuen and Company, 36, Essex Street, London, W.C.2.

World Radio Handbook for Listeners (1954). Compendium of information on broadcasting and television stations, their wavelengths, interval signals, times of transmission, etc. Pp. 136 with numerous illustrations. Price 8s 6d. Edited and published by O. Lund Johansen, English edition distributed by W. Dawson and Sons, Cannon House, Macklin Street, London, W.C.2.

Electrical Engineering Progress Series, Editor M. G. Say, Ph.D., M.Sc., M.I.E.E. Collections of articles on recent developments by specialist contributors.

Cathode Ray Tubes. Radar, television, instrument and camera tubes. Pp. 216+ vii; Figs. 113. Price 25s.

Rotating Amplifiers. Amplidyne, Metadyne Magnicon and Magnavolt machines and their applications. Pp. 125+ vii; Figs. 74. Price 17s 6d.

Electrical Earthing and Accident Prevention. Current practice in domestic, industrial, mining and ship installations. Pp. 248+ viii; Figs. 116. Price 25s.

The above three books are published by George Newnes, Tower House, Southampton Street, London, W.C.2.

Mechanism of Economic Systems, by Arnold Tustin, M.Sc., M.I.E.E. Application of control system engineering methods, feedback and stabilization, to the problems of economic fluctuations. Pp. 161; Figs. 57. Price 25s. W. Heinemann, 99, Great Russell Street, London, W.C.1.

Technique de la Télévision, by A. V. J. Martin, A.M.Brit.I.R.E. Outline of television receiving technique with special reference to Continental standards. Pp. 295; Figs. 358. Société des Editions Radio, 9 Rue Jacob, Paris 6.

Gears for Small Mechanisms, by W. O. Davis. Theory and practice of designing small gears for instruments, clocks and automatic control mechanisms. Pp. 157+ ix; Figs. 76. Price 25s. N.A.G. Press, 226, Latymer Court, Hammersmith, London, W.6.

Surface-Barrier Transistors

New Technique for Making High-frequency Junction Types

ARTICLES in this journal have already described the point transistor and the junction transistor: variants, like the analogue transistor which is now reported to be approaching the practical stage, have not passed unnoticed. It is a feature of both these basic types of transistor that they are all of the *a-b-a* type, the junction transistors either *n-p-n* or *p-n-p*, and the point transistors actually having small areas of *p*-germanium under the points, so that internally they are *p-n-p* systems.

The technological problems of constructing the germanium sandwich are, like the problem of getting the jam into the doughnut, extremely difficult. The central layer must, like the jam, be extremely thin and methods used so far have not been very successful in achieving the required uniformity except for relatively thick base layers, with the corresponding limitation to low frequency operation.

A new type of junction transistor has now been announced by Philco in America, in which many of the difficulties are overcome. In some ways this new transistor reminds us of the coaxial point transistor described by Kock and Wallace¹. The coaxial transistor consisted of a disc of germanium one-eighth of an inch in diameter and 0.02in thick, in the faces of which two concave depressions were ground. The point contacts were applied coaxially, one fitting in each hollow. It seemed quite a good idea, but no more has been heard of it. The surface-barrier transistor is also made from a small plate of germanium, cut from a single crystal of *n*-germanium and initially 0.05 × 0.10in in area and 0.006in thick. Since the cutting operation damages the crystal structure, the small blanks are etched to a thickness of 0.003in, and a nickel contact tab is then soldered to one end.


This slab of germanium is still far too thick, and the working section must

be reduced in thickness. Here we meet Part I of the new invention. Jet electrolytic etching is used to dissolve away some of the germanium. Fig. 1 shows how two jets are played on opposite sides of the germanium blank from glass nozzles about 0.005in in diameter. The jets are a solution of an indium salt, and a current of about 1.5 mA is passed along the jets and through the germanium, the circuit being closed through the nickel tab. Light must fall on the jet-germanium junction during the etching process, because the current is flowing through the back resistance of the jet-germanium diode, and it turns out that the effect of these combined conditions is to make the window flatten out as it gets thinner. This helps to give good high-frequency performance.


A hole is first drilled right through, to find out how long it takes on the particular blank being processed. Then the blank is moved, and the etching process carried out, stopping when calculations show it must have left a window about 0.0002in thick. This takes rather under two minutes.

The current through the jet-germanium diode is now reversed, so that the system becomes an electroplating unit. Indium is deposited on the surface of the germanium, and the layer is built up to give an electrode thickness of 0.0005in. Wires are fastened to these two electrodes and the unit is mounted and sealed. The etched wafer is shown in Fig. 2, and the method of mounting in Fig. 3.

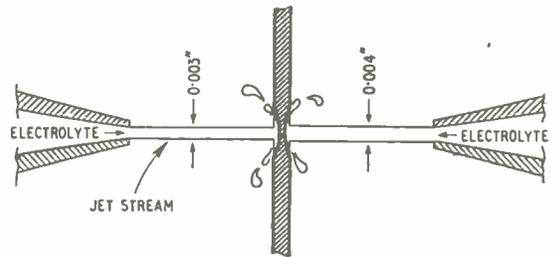
There is no forming action, no heating to produce



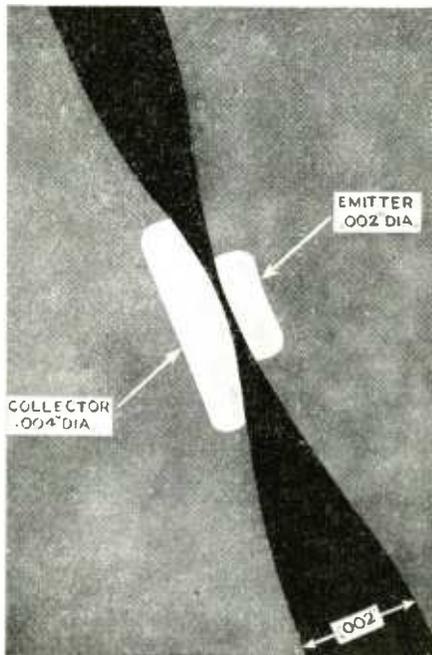Above: Fig. 1. Etching of germanium wafer by jets of electrolyte.



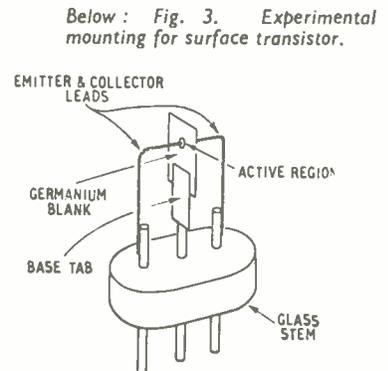Left: Fig. 2. Photomicrograph of section of etched wafer. The white areas show the relative sizes of the indium electrodes.



Below: Fig. 3. Experimental mounting for surface transistor.

¹ *Elect. Engng.*, N.Y. March 1949.

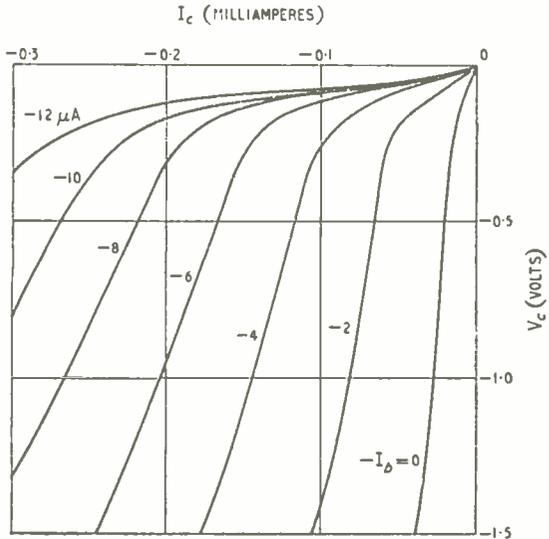


Fig. 4. Earthed-emitter characteristic of the surface-barrier transistor.

Fig. 5. Circuit of video amplifier using surface-barrier transistors.

diffusion. Here we see the fundamental difference between the transistor which results from this method of manufacture and the transistors we have encountered before. The junction with which we are concerned is that between the germanium and the indium, at the actual surface of the germanium. This is, of course, much more clearly defined than the *n-p* junction in either a grown type or a diffused type of junction unit.


A typical set of characteristics is shown in Fig. 4. These are measured using the base current as parameter. It can easily be seen that for very small signal working the point $I_c = -0.06\text{mA}$,

$V_c = -0.5\text{V}$ and $I_b = -2\mu\text{A}$ is quite satisfactory. Amplifiers giving a power gain of 18db at 30 Mc/s and using only a 3-volt supply have been made. The values of α cut-off published for 10 units range from 36 to 49 Mc/s, and the values of α from 0.905 to 0.962.

The circuit shown in Fig. 5 shows a video amplifier having a gain of 28 db and a bandwidth of 9 Mc/s. It will be noticed that the collector supply is only -3 volts. The alternative junction tetrodes, which also have good high-frequency characteristics, require much high supply voltages, usually over 15 volts.

The surface-barrier transistor appears to be a stage nearer the solution of the problem of reproducible high-frequency transistors.

Acknowledgments. Figs. 1, 2 and 3 are based on Figs. 1, 3 and 4 of "Electrochemical Techniques for Fabrication of Surface-Barrier Transistors," by J. W. Tiley and R. A. Williams, *Proc. I.R.E.*, Dec., 1953, p. 1706; Fig. 4 on Fig. 4 of "Principles of the Surface-Barrier Transistor," by W. E. Bradley, *Proc. I.R.E.*, Dec., 1953, p. 1702; and Fig. 5 on Fig. 2 of "Circuit Applications of Surface-Barrier Transistors," by J. B. Angell and A. P. Keiper, *Proc. I.R.E.*, Dec., 1953, p. 1709.

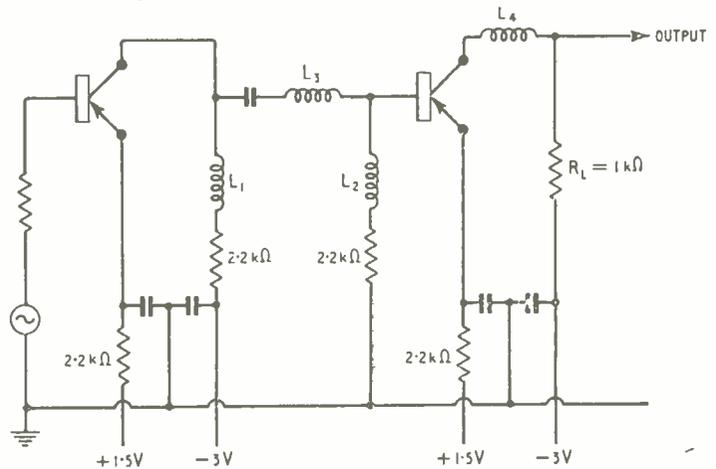

COMMERCIAL LITERATURE

Tubular Ceramic Capacitors for handling high pulse voltages (up to 5kV peak) in radar and television. Technical bulletin No. 43, Series 2, from The Telegraph Condenser Company (Radio Division), North Acton, London, W.3.

Radio Books to be published in the first half of 1954 included in a spring list from Sir Isaac Pitman & Sons, Parker Street, London, W.C.2.

Eddystone short-wave components and accessories for transmitting and receiving described in a 28-page catalogue, with illustrations and technical data, from Stratton and Co., Alvechurch Road, West Heath, Birmingham, 31.

Connectors for coaxial and balanced twin cables for general-purpose use, including television. Also, details of special microwave, v.h.f. and miniature types. Leaflets from Trans-radio, 138A, Cromwell Road, London, S.W.7.

Portable Electric Gramophones with Collaro pickups and motors (or record-changers). Range of four types described in a leaflet from Electric Audio Reproducers, 17, Little St. Leonard's, Mortlake, London, S.W.14.

Resistance Boxes, calibrating potentiometers, Wheatstone and plug bridges, resistance standards and other measuring instruments listed on a leaflet from the Croydon Precision Instrument Company, 116, Windmill Road, Croydon, Surrey.

Tape Recorder with Truvox tape deck, crystal microphone

and 10-in elliptical loudspeaker. Specification on a leaflet from Unitelex (London), Deptford Bridge, London, S.E.8.

Instrument Cases of welded steel construction and chassis to fit (also in aluminium). Range of sizes given on leaflets from Phillips & Bonson, Pond Works, 8, Millfields Road, Hackney, London, E.5.

Television Aerial Outlet Boxes.—Instructions for wiring extensions to other rooms given on a leaflet from Aerialite, Castle Works, Stalybridge, Cheshire.

U.H.F. Turret Attenuator (0-3,000 Mc/s) with six tubular pads which, in turn, are brought in line with the coaxial input and output sockets. Characteristic impedance is 50Ω and attenuation steps can be from 0.1 db to 60 db. Full description on a leaflet from Stoddart Aircraft Radio Company, 6644, Santa Monica Boulevard, Hollywood, 38, California, U.S.A.

"**Transistor Research Bulletin**," a new publication covering progress in the field of transistors, crystal diodes and other semi-conductor devices. The December, 1953, issue contains information about developments in Germany and a semi-conductor bibliography. From National Scientific Laboratories, 2010, Massachusetts Avenue, N.W. Washington, 6, D.C., U.S.A.

Transistorized Megohmmeter

Compact Two-range Instrument Using a Transistor E.H.T. Generator

By P. B. HELSDON, A.M.Brit.I.R.E.

THE small size and low power consumption of a transistor e.h.t. generator makes the electrostatic type of megohmmeter an attractive proposition. The complete unit to be described measures 6in × 4in × 3in and operates from a small hearing-aid type battery. There are two ranges, 3 to 1,500 megohms and 35 to 22,000 megohms.

In principle, the electrostatic megohmmeter is the dual of the well known milliohmmeter or bonding meter. The basic circuit of the bonding meter is shown in Fig. 1. Its dual in Fig. 2 is the basis of the electrostatic megohmmeter. The constant voltage source equals the full-scale deflection (f.s.d.) of the meter. The voltmeter is connected across the standard resistor and is calibrated in terms of the unknown resistance. To measure very high resistances the meter must be electrostatic.


Electrostatic meters have a modified square law of deflection, so that greater sensitivity is obtained near full-scale reading. With the arrangement of Fig. 2, large values of the unknown give low voltage reading. But when the standard and unknown are interchanged as in Fig. 3, large values of the unknown give readings near full scale, so that the meter is used to best advantage. In practice the meter is switched according to the range in use. One is used for unknowns less than the standard and the other for those greater. The meter reads half-scale voltage on each range when the unknown equals the standard.

In theory, the value of the standard can be as high as desired, but in practice it is limited by considerations of leakage. Meters can be obtained with leakage resistance greater than one million megohms, so that with care and a suitable standard, resistances of this order can be measured. The 750-volt electrostatic meter used by the writer is of war surplus stock and unfortunately has a leakage of 1,750 megohms. This value has been measured on several different occasions and is assumed to be fairly stable. For the standard resistor (R_{STD}) a value of 25 megohms is used.

Source Impedance

Power requirements are modest. Allowing for the leakage, the low range requires up to 3.4 μ A at 750 V and the high range up to 3.25 μ A at 815 V. Regulation must be such that the effective source impedance obtained is small compared with the standard. No serious attempt has been made to analyse the regulating properties of the e.h.t. generator. Measurement shows the effective source impedance to be 14 M Ω .

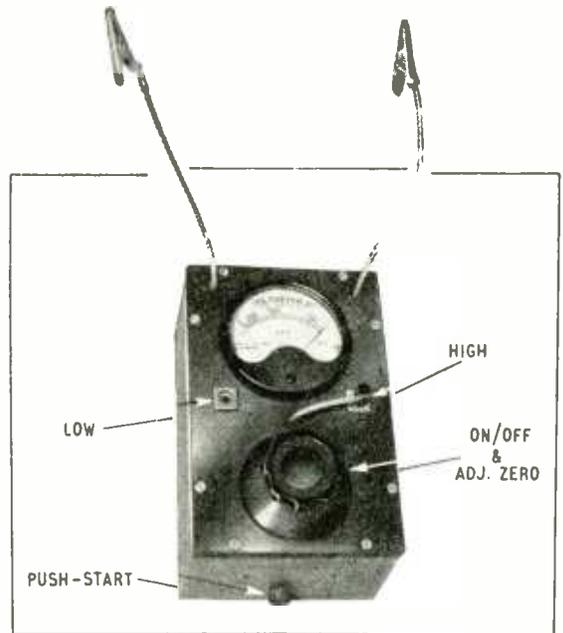After adding elements for leakage and source impedance the circuit of Fig. 2 becomes as shown in



Polythene-insulated leads and wander-plug switching are employed. The meter is of the electrostatic type.

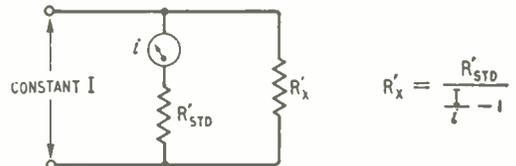


Fig. 1. Basic circuit of milliohmmeter.

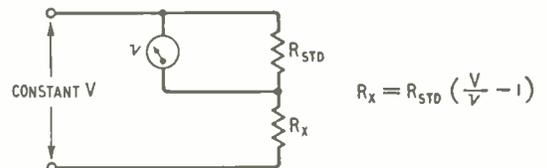


Fig. 2. Basic circuit of electrostatic megohmmeter ($R_x < R_{STD}$)

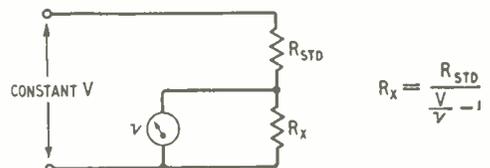


Fig. 3. Circuit of Fig. 2 altered to give readings near full-scale deflection when $R_x > R_{STD}$

Fig. 4, with an effective standard resistance (1,750 and 250 in parallel) of 220 MΩ.

So when $v=100$, $R_x=1,526$ MΩ; and when $v=740$, $R_x=3$ MΩ.

The same procedure changes Fig. 3 into Fig. 5. Applying Thévenin's theorem, the complex resistance network seen from the R_x terminals can be reduced to a single (standard) resistance of approximately 228 ohms, in series with an open-circuit generator voltage of 750.

From the formula in Fig. 5, when $v=100$, $R_x=35$ MΩ; and when $v=740$, $R_x=22,800$ MΩ.

Oscillator Circuit

A battery driven transistor oscillator with a step-up transformer to a selenium rectifier system is used to supply the high voltage. In this oscillator circuit the transistor acts more like an astable switch, rather than as an amplifier with positive feedback. This triggering mode of oscillation is desirable since the collector dissipation is low, both during the conducting and non-conducting parts of the cycle. During the transition, however, the dissipation is high, so the switch should be as fast as possible. The Class "C" mode of operation would seem desirable for high efficiency, but every attempt at this failed because of "squegging." The peak instantaneous collector dissipation under "squegging" conditions is very high and soon damages the transistor. Satisfactory results are obtained when Class "B" operation is adopted.

The switching capabilities of a transistor can be demonstrated by the circuit of Fig. 6. The ohm-

meter should have an internal 9-V battery and a half-scale reading of about 5,000 ohms. If the bias resistor has the right value the collector-emitter resistance indicated with base floating can be either high or low.

If the base is momentarily connected to the emitter, the transistor triggers to high resistance (off), but if the base is momentarily connected to the collector the transistor triggers to low resistance (on.) This constitutes a bistable switch. A pair of headphones added as in Fig. 7 makes a simple astable switch.

A better oscillator circuit is shown in Fig. 8. The base bias resistance R_2 should be increased until oscillations just start and then the emitter series resistance R_1 adjusted for maximum output. The tap on the inductor should be about $\frac{1}{3}$ of the total down from the base.

The transistor can be regarded as a switch which connects the tuned circuit to the battery throughout each negative half cycle. The peak-to-peak voltage developed across the tuned circuit is then twice the battery voltage. The collector has to withstand this double battery voltage at the peak of the non-conducting half cycle. As 33V seems a safe peak collector voltage, the battery must be limited to 16½V.


In practice the 16½ V to the transistor is obtained from a 30-V battery (Type B105) through a decoupled series resistance. This resistance is provided by a fixed safety resistor and a variable resistor ganged to the on-off switch. The variable resistor compensates for battery ageing and gives a precise control of the e.h.t. voltage. In addition it reduces the current to a low value before switching off, so that dangerous inductive surges are avoided. The complete circuit is shown in Fig. 9.

The oscillator is sometimes reluctant to start in cold weather. A transistor, unlike a valve, has no gain at zero bias. The emitter is biased only by the small collector leakage current passing through the base bias resistor R_2 . When the crystal is cold this current is small, due to the negative coefficient of resistance with temperature of high-purity germanium. After switching on, the collector current slowly rises as the crystal warms up. Seconds or even minutes may pass before the circuit bursts into oscillation. Quick starting can be obtained by connecting a fixed resistor of about 39 kΩ from collector to base. This is wasteful of current and also loads the tuned circuit. The method adopted is to connect this resistance by way of a push-button starting switch. Lightly loaded oscillators can be made to start by suitably phasing the switching-on surge, but the rectifier load in the present case initially constitutes a virtual short circuit on the tuned circuit and prevents "kick" starting.

Auto Transformer Design


To obtain 830 volts d.c. from the peak-to-peak rectifier system, the inductance must be made into an auto transformer with a step-up ratio of $830/33 = 25/1$ approx. The battery voltage adds in series giving the required total output of 860 volts on no load.

The auto transformer is wound on a four-section polystyrene former with a small pair of "Ferroxcube" E cores (FX 1105/A4) un-gapped. A total of 1250 turns of 42 s.w.g. vinyl acetal enamelled grade M (medium thickness) wire is tapped at 5 turns for the emitter and 50 turns for the battery positive. Total inductance is 4.25 H with a Q of 50 at the self-resonant frequency of 32 kc/s. The extra stray capacitance of

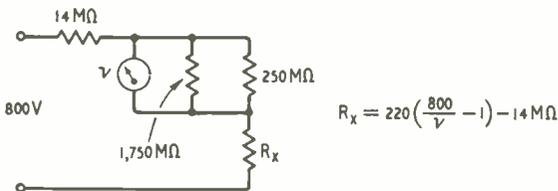


$$R_x = 220 \left(\frac{800}{v} - 1 \right) - 14 \text{ M}\Omega$$

Fig. 4. Practical equivalent circuit of Fig. 2 for low resistance range.

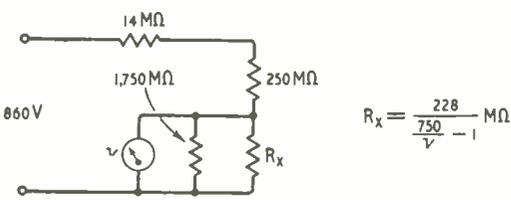

$$R_x = \frac{228}{\frac{v}{750} - 1} \text{ M}\Omega$$

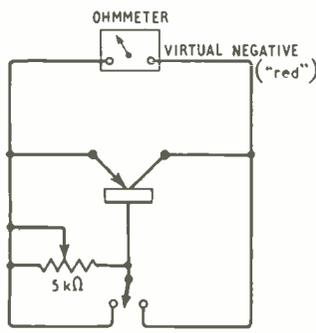Above: Fig. 5. Practical equivalent circuit of Fig. 3 for high resistance range.



Left: Fig. 6. Circuit for demonstrating the function of a transistor as a bistable switch.

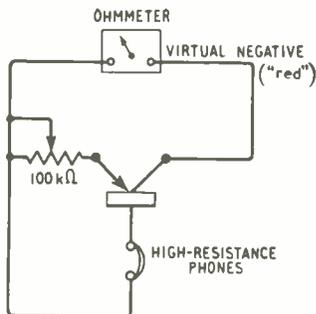


Fig. 7. High resistance headphones in the base circuit demonstrate the astable switching function of the transistor.

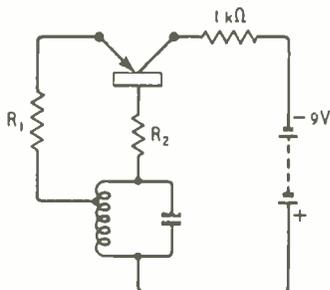


Fig. 8. Sine-wave oscillator using the astable switching circuit.


the rectifier system reduces the frequency of oscillation to about 20 kc/s. The waveform is a distorted sine wave on which is superimposed damped oscillations at a higher frequency. These high-frequency ripples are produced during the switching transitions and are caused by the several leakage inductances resonating with stray capacitance. It is important to keep leakage inductance to a minimum, so that the switching transients do not over-dissipate the collector.

Reduced Current Consumption

A large percentage of the power loss is due to collector-to-base leakage within the transistor. The low current consumption of 2.2 mA was obtained by forming a transistor to an I_{c0} (collector current for zero emitter current) of 0.6 mA at 30 volts. The average commercial point-contact transistor has an I_{c0} of 1 to 2 mA at $E_c = 30$ volts.

The complete unit is contained in a wooden box with high-grade insulation where necessary. The polythene test leads are brought out to crocodile clips to avoid the use of terminals. Meter switching is by plug and socket, since few switches have sufficiently good insulation.

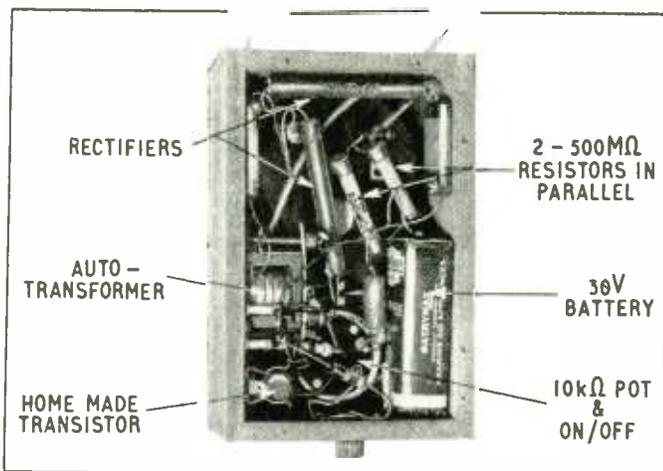On the low range the zero is set by shorting the test leads together and adjusting the vari-



Underside showing single hearing-aid battery and general arrangement of components.

able resistor to give f.s.d. on the meter. Infinity on the high range is set by separating the test leads and adjusting the variable resistor to f.s.d. as before.


The meter has a high internal impedance and no shock can be felt when handling the test leads.

One inconvenience is the time taken to measure large low-leakage capacitors. For example, a $1\text{-}\mu\text{F}$ capacitor takes over 15 minutes to test. This time could be reduced to about 1 minute by temporarily short-circuiting the standard resistance. Once a large capacitor is charged, however, it is highly dangerous and should be carefully discharged after testing.

The transistor megohmmeter appears to be quite reliable. One has been in use for three months, at the time of writing, without any loss of efficiency or output, even after transport by bicycle on several occasions.

The e.h.t. generator itself has several applications apart from the megohmmeter; it could supply e.h.t. for Geiger-Muller radiation counters, image-converter tubes, flash-tubes or small cathode-ray tubes, to name a few.

Fig. 9. Complete circuit diagram of two-range megohmmeter with transistor e.h.t. generator.

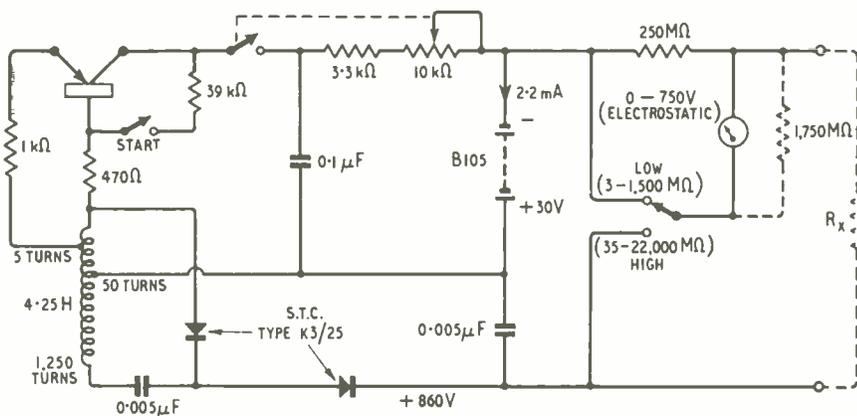

WORLD OF WIRELESS

Death of Major Armstrong

Radio Fuse Awards

More Band 1 Stations

F.M. Broadcasting in U.S.

RADIO INSTALLATION on the floating whaling factory "Abraham Larsen" which is the headquarters vessel for a whaling fleet operating in the Antarctic. The equipment was supplied by Redifon.



F.M. Pioneer's Death

WITH REGRET we record the death in tragic circumstances in New York on February 1st of Major Edwin H. Armstrong, the f.m. pioneer. Born in December, 1890, Edwin Armstrong graduated in electrical engineering from Columbia University at the age of 23 and had worked there ever since, becoming Professor of Electrical Engineering in 1934.

Professor Armstrong will be remembered not only for his work on f.m. but for his earlier work on the regenerative and super-regenerative receiving circuits and also the principle of the super-heterodyne. He contributed a letter on the significance of regeneration to our January issue. His latest work was concerned with a multiplex system of f.m. transmission, a brief description of which will be found elsewhere in this issue.

More Radio Fuse Awards

IN ADDITION to the £20,000 awarded by the Ministry of Supply to Pye, Ltd., for the development during the war of the proximity fuse and the No. 19 tank set (see our January issue), recommendations of awards to seven claimants have been made by the Royal Commission on Awards to Inventors. Four of the claimants—H. Cobden-Turner, G. M. Tomlin and L. Rollin, all of Salford Electrical Instruments, Ltd., and W. H. B. Lord, late of that company—have been awarded jointly £11,500. Individual awards have also been made to A. Stratton (£2,000), N. Coles (£750) and G. A. Whitfield (£750), who are at R.A.E., Farnborough.

New TV Stations

AMENDED PLANS for the completion of the B.B.C.'s single-programme chain of television stations were recently announced by the Assistant P.M.G. in the House. Whereas it was originally planned for eight of the twenty stations to go into Band 3, six of them will now be accommodated in Band 1, although this is contrary to the plan drawn up at Stockholm.

The two channels in Band 3 (186-191 and 191-196 Mc/s) to be made available for television will now be used for the proposed competitive stations. Channel 9 (191-196 Mc/s) will be assigned to London.

The six B.B.C. stations referred to above will be at, or near, Norwich, Dover, Inverness, Londonderry, Towyn and Carlisle. They will each use horizontal polarization. The site for the Norwich station, where it is hoped to have a temporary 0.5-kW transmitter working within

twelve months, is at Tacolneston, some 10 miles south west of the city.

A temporary station is also to be brought into service this year at Redmoss to serve Aberdeen until the permanent transmitter is installed at Core Hill.

The much-debated North Hessary Tor site for the Devon-Cornwall television transmitter has now been approved by the Minister of Housing. This 5-kW station will operate in Channel 2.

Mobile Radio

A WRIT has been served on the Post Office by the Colchester engineering firm, Davey, Paxman & Company, alleging that the fees collected for licences for the operation of their mobile radio transmitters are not lawfully chargeable. They also claim that some of the conditions regarding frequencies and power, etc., laid down in the licence, are contrary to the provisions of the Wireless Telegraphy Act.

The outcome of the action will be of interest to all civil users of mobile radio.

Whither F.M. Broadcasting?

IN AMERICA, the home of f.m. broadcasting, there are indications that all is not well in the f.m. camp. A member of the Federal Communications Commission recently stated that "if the broadcast industry does not take some steps to increase the utilization of the f.m. frequencies" he had no hesitancy in saying that in the public interest he would have difficulty in retaining the whole of the 88-108-Mc/s band for f.m. broadcasting should the Commission be asked to make use of part of it to relieve congestion in other services.

According to the latest returns available from the F.C.C., the number of f.m. broadcasting stations has decreased from some 750 to 560 during the past four years.

Radio Exports Up

A RECORD YEAR for radio exports was reported in the Board of Trade returns for 1953. The total value of exports of radio equipment of all kinds was £25,761,818, compared with the 1952 figure of £24,495,950.

The contributions by the four sections of the industry are given below in £M, together with (in parentheses) the 1952 figure:—

Transmitters and radio navigational aids	11.001	(7.963)
Components and sound reproducing equipment	9.042	(8.481)
Domestic receivers	3.517	(4.435)
Valves and cathode-ray tubes	2.200	(3.615)

PERSONALITIES

H. O. Sampson, who has been appointed head of technical operations, B.B.C. Television Studios, joined the Alexandra Palace staff in 1936 and remained there until the television service was suspended at the outbreak of the war. During the war he served at several of the Corporation's high-power transmitting stations and with the London Recording Unit. He returned to the television service in 1946.

Eric E. Jones, who was for some years in charge of the Telecommunications Division of the Philips group of companies in this country and has, since 1949, been commercial manager of Savage and Parsons, Ltd., recording equipment manufacturers of Watford, has taken over the direction of the commercial activities of the Solartron Electronic group of companies.

In our note in the last issue recording the appointment of Rear-Admiral (L) C. P. Clarke, C.B., D.S.O., R.N. (ret.), as a Knight Commander of the British Empire (K.B.E.) in the New Year Honours, we omitted to mention his position at the Admiralty and his radio associations. At present director of the Naval Electrical Department, Rear-Admiral Clarke has been a vice-president of the Brit.I.R.E. since October, 1952.

Hugo Gernsback, editor of our New York contemporary *Radio-Electronics*, has been appointed Officer of the Oaken Crown by H.R.H. The Grand Duchess Charlotte of Luxembourg. The award was made to Mr. Gernsback, who was born in Luxembourg, "for his meritorious service to science."

OUR AUTHORS

J. R. Brinkley, who has been technical director of Pyc Telecommunications, Ltd., since 1949, writes on the problems of frequency planning on page 103 of this issue. He received his early technical training in the Telephone Department of the Post Office, and after a year as inspector in the Engineer-in-Chief's Office went to the Radio Branch at Dollis Hill in 1939. He was later seconded to the Home Office, where he was responsible for the development of police v.h.f. radio systems and in particular for the introduction of the multi-carrier mobile radio system.



J. R. BRINKLEY



T. D. CONWAY

T. David Conway, author of the article on the measurement of harmonic distortion, has been chief engineer of Grundig (Gt. Britain), Ltd., since its formation in 1952. He joined Grundig from the Ministry of Supply, where he had been an instrument engineer for two years. Throughout the war he was with Ultra Electric as a radar engineer and from 1945 to 1947 he was concerned with the development and testing of ceramic and mica condensers at the United Insulator Company's works. Mr. Conway was with Standard Telephones and Cables as a factory valve engineer from 1947-1950.

R. B. Quarmby, contributor of the analogue computing article in this issue, became a probationary college apprentice at Metropolitan Vickers in 1936. A year later he went to Manchester University, where he graduated in 1940, and then spent some time on extra-mural research on the properties of polythene dielectrics, etc., for the Ministry of Supply. Wartime work at the Royal Military College of Science was followed by a year's lectureship in electrical engineering and electronics at the University of Capetown and in 1950 he joined the staff of Ferranti, Ltd., where he has been working on the design and construction of analogue computers and simulators for use in the design of guided weapons.

D. H. C. Scholes, who contributes an article on frequency-shift radio telegraphy in this issue, has been with the Plessey Company since 1946, where he is now chief engineer and sales manager of the Telecommunications Division. For a short while at the beginning of the war he worked at the Royal Aircraft Establishment, Farnborough; then, in 1941, joined the Royal Navy as an air engineering officer and was engaged in various theatres of war on engineering duties concerned with airborne radio and radar equipment. Lt. Cdr. Scholes was at the Admiralty for a year after the war. For seven years before his war service he was with the Marconi Company.

IN BRIEF

Broadcast Receiving Licences current in the United Kingdom at the end of December totalled 13,268,270, including 2,956,846 for television and 206,348 for car radio sets. The month's increase in television licences was 110,619.

French Components Show.—The annual Paris exhibition of radio components, valves, accessories and measuring equipment will be held in the Parc des Expositions, Port de Versailles, from March 12th to 16th.

A course on **Point-to-Point Radio Services**, which is open to overseas senior planning and operating engineers and telecommunications administrators, is being conducted in London from June 27th to July 10th by the British Council in conjunction with the Engineering Department of the Post Office. Information on the course, for which there is a limited number of vacancies, can be obtained from overseas offices of the British Council, or from 65, Davies Street, London, W.1. The fee is £38.

Quick Work.—At the time of the Comet airliner crash near Elba, Pyc engineers were developing a new underwater television camera for operation at a depth of 500 fathoms. Although the equipment had hardly gone beyond the drawing-board stage, the camera, in a case for operation at the estimated depth of the Comet (some 40 fathoms), was ready within six days. It was then learned that the wreck was probably 100 fathoms below the surface. A new case was designed and completed within seven days and flown to Italy for use by the Admiralty in the search for the wreck.

Bronze Medallist.—The City and Guilds' Bronze Medal for the best student in Great Britain in the 1953 Intermediate Radio Servicing Examination has been awarded to John McCubbin, a Glaswegian, who is employed by James Anderson & Son (Glasgow), Ltd. He is a fourth-year student at Allan Glen's Further Education Centre, Glasgow, studying for the R.T.E.B. final certificate.

F.M. for Marine V.H.F.—On the question of the proposed change to f.m. for international maritime mobile radio services, the Radio Communication and Electronic Engineering Association states in its annual report that it has advised the Post Office that the majority of its members favour the change provided there are suitable safeguards to minimize dislocation of services, especially during the changeover.

R.C.E.E.A. Council.—The following member-firms of the Radio Communication and Electronic Engineering Association were elected to the Council of the organization for 1954 (the names of the companies' representatives are given in parentheses): B.T.-H. (V. M. Roberts), Decca Radio (C. H. T. Johnson), E.M.I. (S. J. Preston), G.E.C. (M. M. Macqueen), Kelvin & Hughes (C. G. White), Marconi's (F. S. Mockford), Metrovick (L. H. J. Phillips), Mullard (T. E. Goldup), Murphy (K. S. Davies), Plessey (P. D. Canning), Redifon (B. St. J. Sadler) and S.T.C. (L. T. Hinton). C. G. White, general sales manager and director of Kelvin Hughes (Marine), Ltd., who has been vice-chairman of the Association for the past two years, has been elected chairman in succession to T. E. Goldup.

INDUSTRIAL NEWS

Moroccan Television.—The first television station in North Africa, established by a private company at Casablanca, has been equipped with Pyc, a camera chain, teletext camera and vision and sound transmitters. The station operates on the French 819-line standards.

Hi-Fi Agencies.—Enquiries from Hollywood and Hong Kong to act as representatives of U.K. manufacturers of high-fidelity sound recording and reproducing equipment have been received through the Export Services Branch of the Board of Trade. Interested firms should write direct to Gordon Agencies, 1506, North-Western Avenue, Hollywood 27, U.S.A..

and Scientific Service Company, 447, Alexandra House, Hong Kong. The Board of Trade, Lacon House, Theobalds Road, London, W.C.1, should also be notified, quoting references ESB/1614/54 (Hollywood) and ESB/1897/54 (Hong Kong). An enquiry has also been received from Long Island, New York, for the agency for a tape recorder. The firm concerned is Rek-O-Kut Company, Inc., 38-01, Queens Boulevard, Long Island City 1, New York. The B.o.T. reference is ESB/1103/54.

A contract for the supply of a quantity of airfield control radar equipment has been awarded to Decca Radar by the Ministry of Supply. The equipment, which is the air-transportable version of the Decca 424 described in our November issue, will be used by the R.A.F.

"The Ship of the Year," as the new P. & O. liner *Arcadia* was described at her launching last May, is being fitted with radio communication and navigational equipment by the Marconi Marine Company. In addition, a comprehensive sound-reproducing system, including 156 loudspeakers fed by seven power amplifiers, each having an output of 60 watts, has been installed. Four sources of programmes—microphones, broadcast receiver, wire recorder and record player—are available and switching permits selected groups of loudspeakers to be fed simultaneously from the four separate sources.

Sound amplifying equipment provided by Hadley Sound Equipments, Ltd., of Smethwick, Birmingham, has been installed in the Roman Catholic cathedral in Calabar, Southern Nigeria.

W. F. Randall, B.Sc.(Eng.), M.I.E.E., director of the Telegraph Construction and Maintenance Company, is on a two months' visit to the company's branches and representatives in the Far East and Australasia.

New premises have been opened by the G.E.C. at Magnet House, Mincing Lane, Blackburn. The depot is equipped for the supply and servicing of the company's radio and television equipment.

British Insulated Callender's Construction Company, manufacturers of radio masts and the like, recently moved to 30, Leicester Square, London, W.C.2 (Tel.: Trafalgar 7777). The central administrative offices of the parent company, British Insulated Callender's Cables, remain at 21, Bloomsbury Street, London, W.C.1 (Tel.: Museum 1600).

Goldring Manufacturing Company (Gt. Britain), Ltd., is the name of the company recently formed to conduct the business of Erwin Scharf, manufacturer of the Goldring pickup, and associated concerns. The company will operate from the present address: 49-51a, de Beauvoir Road, Kingsland Road, London, N.1 (Tel.: Clissold 3434).

Excel Sound Services, Ltd., tape-recorder and amplifier manufacturers, of Shipley, Yorks, have moved to Celsonic Works, Garfield Avenue, Bradford, 8, Yorks (Tel.: Bradford 45027).

MEETINGS

Institution of Electrical Engineers

Radio Section.—"A Study of some of the Properties of Matter affecting Valve Reliability" by E. A. O'Donnell Roberts, M.Sc., Ph.D., on March 10th.

"Colour Television" by C. J. Hirsch on March 22nd.

Both the Radio Section meetings will be held at 5.30 at Savoy Place, London, W.C.2.

Cambridge Radio Group.—"Computing Machines" by T. Kilburn, M.A., Ph.D., at 8.15 on March 9th at the Cavendish Laboratory, Cambridge.

Mersey and North Wales Centre.—Faraday Lecture "Electro-Heat and Prosperity" by O. W. Humphreys, B.Sc., at 6.45 on March 25th at the Philharmonic Hall, Liverpool.

North-Eastern Radio and Measurements Group.—"A Study of some of the Properties of Matter affecting Valve Reliability" by E. A. O'Donnell Roberts, M.Sc., Ph.D., at 6.15 on March 15th at King's College, Newcastle-upon-Tyne.

North-Western Centre.—Faraday Lecture "Electro-Heat and Prosperity" by O. W. Humphreys, B.Sc., at 7.30 on March 23rd at the Free Trade Hall, Manchester.

North-Western Radio Group.—"Distributed Amplifiers" by W. S. Percival, B.Sc., at 6.30 on March 17th at the Engineers' Club, Albert Square, Manchester.

North Lancashire Sub-Centre.—"Some Aspects of the Design of V.H.F. Mobile Radio Systems" by E. P. Fairbairn, B.Sc., at 7.15 on March 10th at the N.W. Electricity Board, North Road, Lancaster.

South-East Scotland Sub-Centre.—"Some Aspects of the Design of V.H.F. Mobile Radio Systems" by E. P. Fairbairn, B.Sc., at 7.0 on March 16th at the Heriot-Watt College, Edinburgh.

South Midland Radio Group.—"Some Aspects of the Design of V.H.F. Mobile Radio Systems" by E. P. Fairbairn, B.Sc., at 6.0 on March 22nd at the James Watt Memorial Institute, Great Charles Street, Birmingham.

Southern Centre.—"Technical Arrangements for the Sound and Television Broadcasts of the Coronation Ceremonies" at 6.30 on March 3rd at the S.E.E.B. Headquarters, Hove, by W. S. Proctor, M. J. L. Pulling, M.A., and F. Williams, B.Sc. "Demonstrations of Synthetic Speech" by W. Lawrence, M.A., and R. A. Eades, B.Sc., at 6.30 on March 5th at the South Dorset Technical College, Weymouth.

Western Centre.—"Telemetering for System Operation" by R. H. Dunn, B.Sc., and C. H. Chambers at 6.0 on March 8th at the Electricity Offices, Colston Avenue, Bristol.

South-Western Sub-Centre.—"Colour Television: Some Subjective and Objective Aspects of Colour Rendering" by G. T. Winch at 3.0 on March 10th at the Rougemont Hotel, Exeter.

Oxford District.—"Modern Trends in Television" by G. G. Gouriet, B.Sc., at 7.0 on March 17th at the Southern Electricity Board, 37, George Street, Oxford.

London Students' Section.—Visit to G.P.O. Research Station, Dollis Hill, N.W.2, at 2.15 on March 3rd.

"Metallic Resistance at High Frequency" by A. D. Stevens at 7.0 on March 3rd at the Public Library, Chelmsford.

"Servo Mechanisms" by Capt. R. A. Middleton, R.E.M.E., at 7.0 on March 30th at the Drill Hall, 185, London Road, Chelmsford.

British Institution of Radio Engineers

London Section.—"Radio Astronomy" by R. Hanbury Brown (Jodrell Bank Experimental Station) at 6.30 on March 31st at the London School of Hygiene and Tropical Medicine, Keppel Street, London, W.C.1.

Scottish Section.—"The Acoustic Design and Measurement of Buildings" by H. C. Watson (Newall's Insulation Co.) at 7.0 on March 11th at the Institution of Engineers and Ship-builders, 39 Elmbank Crescent, Glasgow, C.2, and at 7.0 on March 12th in the Department of Natural Philosophy, The University, Edinburgh.

North-Western Section.—"Colour Television" by G. B. Townsend (G.E.C. Research Laboratories) at 7.0 on March 11th at the College of Technology, Manchester.

West Midlands Section.—"Industrial Applications of Electronic Instruments" by A. G. Wray, M.A., (Marconi Instruments) at 7.15 on March 23rd at the Wolverhampton and Staffordshire Technical College, Wulfruna Street, Wolverhampton.

British Sound Recording Association

London.—"High Quality Microphones: The Assessment of Performance" by D. E. L. Shorter, B.Sc., at 7.0 on March 19th at the Royal Society of Arts, John Adam Street, London, W.C.2.

Manchester Centre.—"Disc Recording with special reference to Long Playing" by A. R. Sugden at 7.30 on March 15th at the Engineers' Club, Albert Square, Manchester.

Television Society

London.—"Trick Effects in Television Production" by D. R. Campbell (B.B.C.) on March 12th

"An Industrial Television Channel" by R. J. Boddy and C. D. Gardner (E.M.I.) on March 25th.

Both the London meetings of the Television Society will be held at 7.0 at the Cinematograph Exhibitors' Association, 164, Shaftesbury Avenue, London, W.C.2.

Leicester Centre.—"Transistors and Other Crystal Valves" by D. D. Jones (G.E.C. Research Labs.) at 7.0 on March 29th in Room 45, The College of Art and Technology, The Newarkes, Leicester.

Institution of Electronics

North-Western Branch.—"Semi-conductors" by R. Cooper, Ph.D., M.Sc. (Liverpool University), at 7.0 on March 26th in the Reynolds Hall, College of Technology, Manchester.

Radio Society of Great Britain

"Trustworthy Valves and Their Manufacture" by G. P. Thwaites, B.Sc.(Eng.), at 6.30 on March 26th at the I.E.E., Savoy Place, London, W.C.2.

Engineers' Guild

Metropolitan Branch.—"Television Broadcasting and the Engineer" by M. J. L. Pulling, M.A., (B.B.C.) at 6.0 on March 4th at Caxton Hall, Westminster, S.W.1.

Institution of Production Engineers

Liverpool.—"Induction Hardening" by R. H. Barfield, D.Sc., at 7.30 on March 24th at the Adelphi Hotel, Lime Street, Liverpool.

LETTERS TO THE EDITOR


The Editor does not necessarily endorse the opinions expressed by his correspondents

Regenerative Single-Transistor Receiver

WE read with great interest the article on transistor receiving circuits by B. R. Bettridge in your January issue, having been experimenting in the same field with the GETI for some time. We cannot add to his useful information on 2-stage circuits for local station loud-speaker reception, but some of your readers who may be able to afford only one of these treasures to begin with, and are interested in getting the greatest sensitivity with a single stage, may find Mr. Bettridge's warning against positive feedback in the base circuit unduly discouraging. With the circuit shown in the accompanying diagram, controllable bias and r.f. feedback are combined, and the danger of destructive oscillation is avoided by the limiting resistor in the emitter circuit.

In operation with a very poor "tree aerial" the circuit brings in continental stations at good signal strength, once you get used to co-ordinating the three variable controls. Moreover, with patient resolution of carriers, in which the variable base resistance is critical, many American stations can be received at stable listening volume. New York and New Orleans are particularly easy; both are in what seems to be the most favourable frequency band, around 870kc/s, though others between 600 and 1,200kc/s come in well; talks and plays can be comfortably followed between 2 and 3 a.m. The total consumption is only 18 mW.

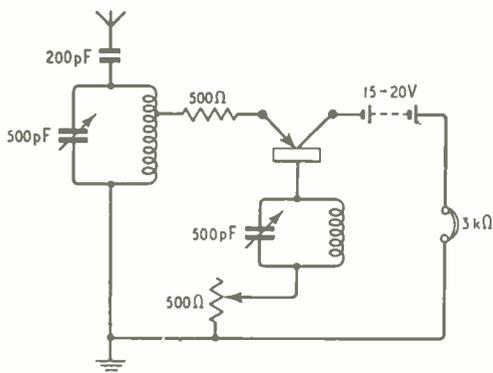Youngsters who have the patience to experiment with transistors in this way may thus get a taste of the thrills



which two of your earliest readers recall, sitting up at night with one of the wonder sets of the period to get the first whisper from across the Atlantic.


W. GREY WALTER, KARL WALTER.

Bristol, 9.

Symbols

THE symbol for the current source in the technical literature is usually chosen to be an arrow as shown at (a) in the accompanying diagram. I would suggest that the symbol (b) should be adopted, this being more logical as well as exactly analogous to the symbol for a voltage source commonly used and shown at (c).

The ideal constant-current generator is assumed to have no shunt admittance, just as the ideal constant-voltage generator has no series impedance. In practical circuits internal shunt admittance and internal series impedance appear connected in their appropriate places. For example, the equivalent circuit for a transistor shown at (b) can easily be correlated with that at (c). There is the additional

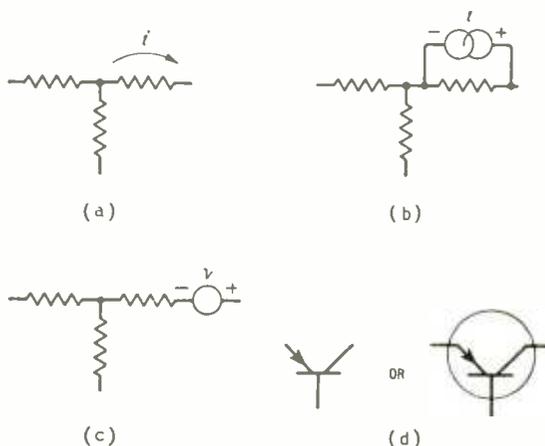

advantage that the current source appears *connected* to the rest of the circuit which is not the case with the arrow symbol of (a).

In this connection, it is felt that the introduction of new symbols for the triode transistor is rather superfluous, bearing in mind that the symbol originally introduced by W. Shockley and shown at (d) is quite adequate.


F. OAKES.

Ferguson Radio Corporation,
Enfield, Middx.

"C.R. Tube Safety"

THE article in your January issue considers the importance of correctly choosing the time constants associated with the cathode and grid of a television tube in order to prevent the bias going positive immediately after the receiver is switched on or off. I cannot however, altogether agree with W. Tusting's approach to this matter. In modern television receivers in which the e.h.t. potential for the tube is derived from an overwind on the line transformer and no e.h.t. bleeder resistor is used, the time constants in question are normally chosen so that the tube passes beam current immediately after switch-off. This ensures that the e.h.t. smoothing capacitor is discharged via the tube whilst the time bases are collapsing. If in a receiver which has a permanent magnet focussing unit the grid potential of the tube decays more quickly than that of the cathode, the tube will be biased off immediately the set is switched off. Then as both potentials approach zero the cathode may still be emitting and a bright focused spot will appear at the centre of the screen. To obviate this possibility many receiver designers prefer to arrange the grid and cathode circuit time constants so that the tube bias decreases immediately after the set is switched off.

However, if in meeting this requirement or because of some other circuit condition there is a danger of the tube grid becoming positive with respect to the cathode, the positive bias may be limited by means of a series grid resistor. The value of this resistor will depend upon the grid-cathode characteristic of the tube in the positive grid region and the extent to which the source of bias voltage travels positively. In general a resistor of 22 kΩ will serve to limit the positive grid excursion to +1 volt, a value which is generally accepted by tube manufacturers as being allowable for a short period immediately after switch-off. The general circuit arrangement is shown in

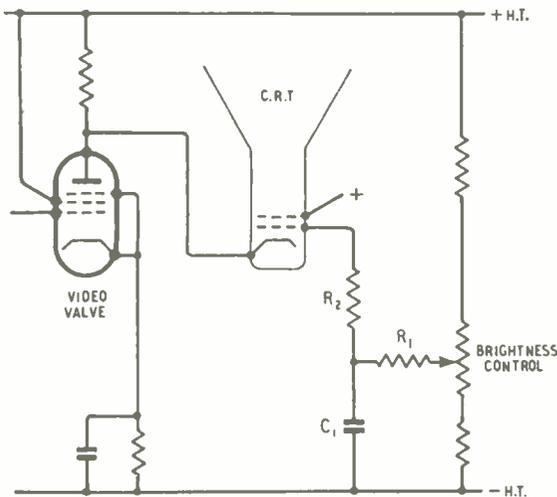

the accompanying diagram, the time constant $C1R1$ serving to hold the grid voltage up to ensure that the e.h.t. capacitor is discharged through the tube. The grid limiting resistor is $R2$.

D. A. WARD.

Mullard, Ltd., London, W.C.2.

"Weathering of Polythene"

I HAVE read with interest the short note in your December issue (page 570) which is a *précis* of a Ministry of Supply document "Reports on Plastics in the Tropics: 2—Polythene."

Neither your note nor the report itself brings out the point that the addition of 0.1 per cent of carbon black is intended only to provide identification of the cores and is not intended to provide protection against ultra-violet light. The approved practice, for this use, established over a number of years, is to include 2 per cent of carbon black of suitable grade and well dispersed in the polythene. This material would be found to possess resistance against the effect of ultra-violet light adequate for commercial use and immeasurably superior to most natural or synthetic cable materials. The addition of this quantity of carbon black does, of course, impair the initial power factor of the material at all frequencies, but it will be found that the power factor is quite stable on exposure to tropical sunshine. Observation of power factor during the course of testing is valuable as a sensitive method of revealing physical or chemical changes in the material.

Our tests indicate that the power factor of polythene with 2 per cent carbon black is not higher than 30×10^{-4} at frequencies up to 3000 Mc/s. except in the band 3-15 Mc/s. where it rises to a maximum of about 65×10^{-4} at 5 Mc/s. The commonest application where polythene is exposed to sunlight is when used as a cable sheath and here the power-factor is rarely of direct interest.

It would perhaps be unwise to deduce firm estimates of the life of this material from accelerated ageing tests, but it may be mentioned that exposure tests in India for periods which have so far attained four years have failed to reveal any change whatsoever in its electrical or physical properties.

One further characteristic of polythene is its resistance to oxidation and this matter is not considered in great detail in the Ministry of Supply report. The antioxidant most generally used with polythene is not well suited to continued operation at high temperatures on account of its volatility. However, other suitable antioxidants are available for use where the polythene is to be used as a black cable sheath exposed to tropical sun.

In view of your conclusion in the penultimate paragraph that polythene cables are unsuitable for desert conditions, I should be grateful if you would give this contrary opinion adequate publicity.

Although the work reported in the M.o.S. document is

extremely valuable and no doubt correct in its facts, it was realized in many quarters that it was open to misunderstanding, and representations have already been made to the Department concerned.

R. C. MILDNER.

The Telegraph Construction and Maintenance Co., London, S.E.10.

"Measuring Non-linearity"

IN my article in the February *Wireless World* I find that Appendix 1 is full of mistakes which I overlooked because the final equation (5) gives a correct numerical answer. For my gross carelessness in this matter I hope readers will accept my apology. The equations in Appendix 1 should read as follows:—

$$(v_1 - v_2) R_3 (v_1 - v_2) R_1 + (v_2 - v_1) R_2 \dots (1)$$

$$v_1 A v_2 \dots (2)$$

$$v_1 - (v_1 + v_2) R_3 R_1 : v_2 (1 - 2R_3 R_1) \dots (3)$$

$$v_1 (v_1 + v_2) (2A + R R_3 - R A R_3) \dots (4)$$

$$v_1 - (v_1 + v_2) (1 - 3A) \dots (5)$$

$$R_3 R (A - 1) (A - 2) \dots (6)$$

The above equation (6) also appears in the main text as equation (5). Fortunately, these mistakes do not effect the body of the argument. There is also one misprint in Appendix 2—a redundant capital "I" has been inserted at the end of the last term in equation (7).

Camberley, Surrey.


D. C. PRESSEY

Short-wave Conditions

Predictions for March

THE full-line curves given here indicate the highest frequencies likely to be usable at any time of the day or night for reliable communications over four long-distance paths from this country during March.

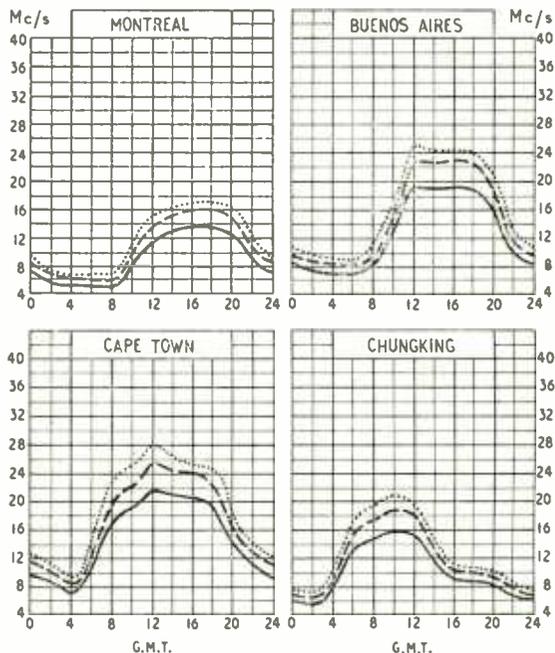Broken-line curves give the highest frequencies that will sustain a partial service throughout the same period.



— FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE ON ALL UNDISTURBED DAYS
 - - - PREDICTED AVERAGE MAXIMUM USABLE FREQUENCY
 FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE FOR 25% OF THE TOTAL TIME

Frequency Shift Radio Telegraphy

Modifying Radio Equipment for Teleprinter Operation

By D. H. C. SCHOLLES*

READERS have already been given a very adequate introduction to this subject in an article by Thomas Roddam,† and it will consequently be possible to devote our present attention to considering in rather more detail some of the problems and latest developments, particularly in connection with the receiving end of the circuit.

The various techniques for f.s.k. (frequency shift keying) reception seem to be surrounded by as much controversy as the f.m.-a.m. question, and many systems which seem theoretically sound are discredited by at least a proportion of the practical results. The whole question is complicated by the many factors which enter into long-distance radio working, and it is not possible with present experience to draw any firm conclusions as to the best system. However, some of the main advantages and shortcomings of the two principal reception systems are fairly firmly established and these will be discussed in the appropriate place.

Whatever system of resolving the teleprinter signal is employed, it is now firmly established that while for on-off c.w. operation, of either auto-morse or teleprinter, triple space-diversity reception is desirable, in the case of f.s.k. triple diversity shows no improvement over dual. It now appears that the most effective receiver is a dual diversity system where the channel giving the poorer signal is completely suppressed. The switching system should have a very rapid response and should be operated by very small level differences even during deep fades on both channels.


Teleprinter Characteristics

In discussing radio teleprinter systems, in radio publications generally little consideration is given to the characteristics of the machine itself. The writer feels that this is unfortunate, in that the whole design of such systems is directed to the one end of producing a signal which will enable the teleprinter to operate without error. For this reason the electronics is inextricably bound up with the peculiarities of the machine itself, which must be understood before the problems connected with the radio side can be appreciated. As the teleprinter is a specialized machine it seems probable that many readers, while knowledgeable in the electronic field, may not be so well informed regarding the teleprinter, and the writer asks the indulgence of those skilled in the art during a brief digression on the operation of the machine.

Operation of any key on the sending machine causes it to produce a signal of varying polarity consisting of marks and spaces lasting for 150 milliseconds. This comprises a "start" signal followed by a 100-msec. period during which the polarity may be any combina-

tion of marks and spaces, the change-over from mark to space (if any) taking place at 20-msec. intervals. These five 20-msec. periods are the five units of the "five unit" code, and each letter or symbol on the keyboard has a corresponding combination of marks and spaces. The complete signal is terminated by a 30-msec. "stop" signal of opposite polarity to the "start" signal. The purpose of the start and stop signals is to control the mechanism of the receiving teleprinter. The timing of the transmitted signals is controlled by a closely speed-controlled motor. There are no pauses between the signal elements and the transitions between mark and space are as nearly instantaneous as the transit-time of the mechanisms and relays will allow. The signal may, therefore, be regarded for all practical purposes as a square wave.

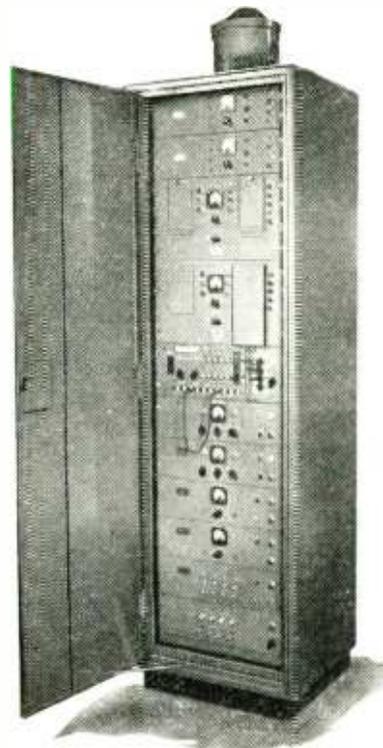Reception of a start signal causes the selecting mechanism of the receiving teleprinter to be connected to a motor whose speed is regulated to within 0.5% of that of the sending motor. The purpose of the selecting mechanism is to investigate the position of the receiving relay at intervals corresponding to the



F.S.K. transmitter drive unit, Model PVT, made by Plessey.

* The Plessey Company.

† "Frequency Shift Keying"; *Wireless World*, November, 1948.

middle of the five 20-msec. code elements to determine whether the incoming signals are mark or space. As each element is interrogated in turn the mechanism in the machine is progressively set until finally the type head is positioned and the letter is printed.

For reasons connected with the operation of the machine which we need not go into here, the receiving teleprinter needs 6 msec. of each code element to carry out its interrogation, thus, in the case of characters involving changes between mark and space, the change-over point cannot be advanced or retarded more than 7 msec. without danger of wrong selection and misprinting. Temporal displacement of the change-over points is called telegraph distortion and is expressed as the percentage of the 20-msec. element length by which the change-over is early or late. The maximum distortion the teleprinter will tolerate without danger of misprinting is 35%.

Waveform Distortion

Bias distortion is another phenomenon which may prove troublesome, and this arises when the receiving relay is not driven symmetrically in both directions by the incoming signal. Although bias distortion is not particularly serious when the incoming signals are perfect steep-sided square waves, if the pulses are rounded, sloped or otherwise distorted in transmission (as they may well be in a long radio link) the effect of bias distortion may be to alter the apparent time of change-over with consequent telegraph distortion. In "single-current" working such as on-off c.w. or single tone m.c.w., where a d.c. bias of half the signal level has to be introduced to polarize the receiving relay, not only is half the signal wasted but, in the case of varying signal strength, bias distortion arises if the signal departs from twice the bias value (as it may do with fading). Automatic bias control can mitigate this effect but has practical difficulties. F.S.K., being a true "double-current" system in which signals are sent equally for mark as for space, has considerable advantages in this respect. It will further be seen that as distortion of the shape of the signal is detrimental any system should have as its aim preservation of the signal shape. F.S.K., being a c.w. double-current system, furthers this end by making more efficient use of the transmitted signal than either c.w. on-off or single or two-tone m.c.w. It is further thought that certain effects of the f.m. nature of the signal have advantages in the presence of certain types of fading.

Having reviewed the method of reception of the radio signal and some of the problems connected with the teleprinter, we can now pass on to consider the

resolution of the teleprinter signal from the radio signal. Only the two main methods will be considered here, these being the linear and non-linear discriminator systems, usually referred to as the "discriminator" and "two-filter" methods.


In considering this phase of the operation we must bear in mind that we are conveying intelligence by varying a signal, whose frequency may be as high as 30 Mc/s, by 850 c/s or less. Consequently, frequency stability is of more than secondary importance whatever system of reception is used.

In the discriminator system, Fig. 1, the r.f. signal is converted to a fairly low i.f. and passed through a limiter to a linear discriminator of the conventional f.m. type. The frequency-shifted signal will thus produce at the discriminator output a d.c. signal of positive or negative sign (polarized) which can be passed through a low-pass filter and further amplifiers, shaping circuits, etc., to the teleprinter. At first sight, it would appear that provided the discriminator be made with a sufficiently long linear characteristic, this system should be very tolerant of frequency drift, but in practice any drift causes a standing d.c. component to appear at the discriminator output resulting in bias distortion. Various methods of eliminating this bias have been evolved but they all involve other difficulties. The discriminator system is, however, much more tolerant of varying values of shift than the two-filter system and this is an advantage in some types of service as shift values are not yet by any means standardized.

The two-filter system, Fig. 2, involves the use of a heterodyne oscillator at i.f. to produce an audio note of 2,000 to 3,000 c/s whose frequency depends obviously on whether the transmitter is sending mark or space.

This audio signal is passed through a bandpass filter and limiters to two further filters tuned to the mark and space frequencies respectively. The outputs of these filters are rectified, filtered and dealt with as before to produce the polarized d.c. signal for the teleprinter. With the two-filter system in the case of small drifts the bias distortion per cycle of drift is very much lower than with the discriminator system. As long as the mark and space frequencies stay within the pass-bands of their respective filters there will be virtually no bias distortion. However, as these filters should for other considerations be made as narrow as possible it could be that the discriminator method would produce some signal from a carrier which had drifted too far to work with the two-filter system, but for many commercial applications, where accuracy is all-important, this might be a doubtful advantage.

Fig. 1. Simplified diagram of a f.s.k. dual-diversity discriminator receiving system.

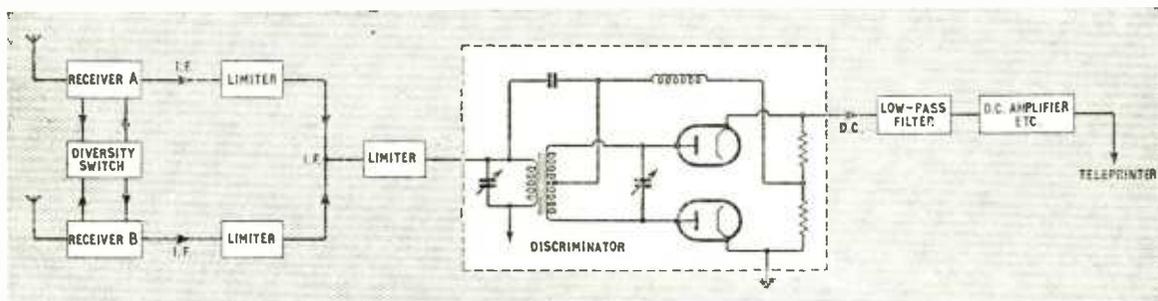

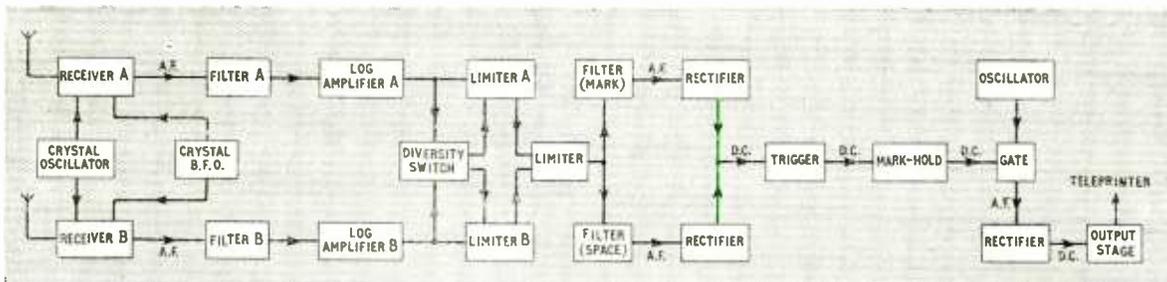


Fig. 2. Schematic diagram of a two-filter dual-diversity f.s.k. system.

It appears, therefore, that while the discriminator system may produce polarized signals under worse conditions than the other, the bias distortion in such circumstances would probably be excessive and at lower values of drift there is reason to believe that the two-filter system would produce lower distortion.

Work has been done in connection with both systems on the application of a.f.c. (automatic frequency control) and automatic bias adjustment at various points in the system but in the present congested condition of the short-wave bands, there is always a grave danger of the a.f.c. locking on to a strong interfering signal and causing a complete breakdown of communication.

It will be appreciated that in f.s.k. systems, the effects of level changes at the receiving aerial are less important than with some other systems since the continuous carrier simplifies a.g.c. problems and the ability to use a.f. or i.f. limiters further helps to reduce the effects of fading.

Holding Signal

A further feature which has to be introduced into the telegraph converter arises from the arrangement whereby the sending teleprinter, when not sending traffic, transmits a continuous mark signal. This prevents the receiving machine from being operated by noise and also after a continuous mark has been received for a given time the motor of the receiving machine is stopped until a further start signal is received. Because an interruption of the carrier would result in the mark signal not being received, with a consequent chance of the receiving machine being started by noise, it is usual to incorporate in a radio teleprinter system a "mark-hold" device which automatically produces a mark signal locally at a fixed time after the last space pulse, in the absence of any further signal.

It is not proposed to deal in detail with transmitting systems as these were covered at some length in the article by Roddam already referred to. Two points are worth noting, however; first, that compared with the c.w. on-off system f.s.k. is much less likely to distort the signal elements in the transmitter. In the case of c.w. on-off (which is for all practical purposes a 100% square wave amplitude modulation) the keying, being usually carried out in an early stage, may be subject to considerable distortion by the succeeding non-linear amplifiers. As there is a constant level of carrier in f.s.k., this trouble is avoided. The second point to be noted is that it is most important that the transition between mark and space be as smooth as possible; an abrupt and discontinuous change between mark and space will give rise to

spurious radiations and other undesirable effects.

Now to consider the question of frequency stability in relation to practical conditions. First, the comparatively small clear space allocated to each radio telegraph circuit makes it essential, no matter what system of telegraph conversion is used, to have the highest selectivity in the receiver compatible with conveying the intelligence. (In the case of an 850-c/s shift the bandwidth cannot safely be much less than 1,500 c/s). The skirts of the i.f. response curve should be as steep as possible. With such selectivities the stability of both transmitter and receiver must be high and crystal control of the transmitter and of the receiver change-frequency oscillator is really essential if the system is not to fail by simple inability to convey any signal at all.

Stability of shift must next be considered. If the mark and space frequencies drift in opposite direction by the same amount no bias distortion will be introduced but if both drift in the same direction, or if only one drifts (both of which effects are more likely in practice) bias distortion will be introduced, particularly in the discriminator system and in the two-filter case excessive drift of any type may overstep the pass-band of the filters.

It will be seen that a fairly high degree of frequency stability at all points in the system is essential, but if the station is to be continuously attended by a skilled operator who can devote most of his attention to a single radio channel it is possible (having made sure that neither shift, carrier nor receiver c.f.o. frequency are subject to violent and random changes) to provide monitoring devices and fine controls so that the operator may at all times keep the circuit at peak efficiency. A drawback of this system is that before a new circuit can be brought into service, some time must be wasted in lining up before traffic can be accepted as such a system cannot be adjusted in the absence of a signal from the corresponding transmitter.

Unattended Operation

For certain types of service (such as aeronautical) the teleprinters may be located remotely from the radio station and many circuits may be in use at once under the control of operators whose accomplishments do not in any case lie in the direction of skilled adjustment of radio equipment. Similarly, it may be necessary to make many changes of frequency during a 24-hour period under circumstances which allow no time to be wasted in preliminary lining up. This problem has been the subject of some years' investigation by the writer's company in collaboration with International Aeradio and it is now believed

that field test data has been collected on a scale sufficient to show that given stabilities of mean transmitted carrier, shift and receiver change-frequency oscillator and b.f.o. of the order of 1 part in 10^6 (which is quite practicable) a system can be built which is capable of virtually unattended operation and in which new channels may be brought into use without preliminary lining up. A typical receiving equipment might have four dual-diversity channels and any one of four radio circuits can be selected remotely, but it is only necessary in this account to describe one channel.

A pair of receivers operating from spaced aerials has its c.f.o. signal provided by a separate unit using a temperature-controlled crystal oscillator in an oven stabilized by a temperature-sensitive resistance bridge.

B.F.O. signals to each receiver are supplied from another temperature-controlled unit which has alternative crystal-controlled and variable oscillators. The stability of all the above crystal oscillators is of the order of 1 part in 10^6 . Alarm circuits on all the ovens give warning should the temperature control fail.

A.F. signals from both receivers are passed to a converter unit via an input band-pass filter whence they pass through logarithmic amplifiers and limiters to the mark and space filters. The outputs from these filters are rectified and combined to produce a low-level polarized d.c. signal.

The converter unit also accomplishes the diversity switching. The signals from the receivers are made to operate an electronic switching device which selects the stronger of the two signals and suppresses the other. The characteristics of the switch are such that with the signals on both aerials subjected to a 20-db fade the stronger signal is still selected as

long as there is a difference of 3 db. The output level of the converter is arranged to vary not more than 1 db for a 60-db change in input.

The converter output is fed to a keyer amplifier unit where the signal is re-shaped and amplified to a level sufficient to work three teleprinters. The ability of the keyer amplifier to re-shape the signals to some extent is an important factor in operation under adverse conditions.

Various built-in test and measuring devices enable the apparatus to be set up in the absence of a signal. The variable b.f.o. facilities enable some degree of compensation to be carried out under local-control conditions when working against an unstable transmitter, but full realization of the benefits of the precise frequency control system necessitates the use of a very stable transmitting system and the drive equipment illustrated was designed to provide such a facility although there are many transmitters already in service of adequate performance.

The drive equipment uses h.f. oscillators and keyer amplifiers identical with those already described, together with shifter units giving crystal control of mean carrier and shift frequencies. These shifter units enable a number of preset channel frequencies to be selected by remote control and on each channel the shift is automatically adjusted to allow for the multiplication in use in the transmitter. A drive guard unit ensures that power cannot be applied to a transmitter unless drive is available. Warning devices operate should any of the ovens fail.

Using the two equipments described it is possible to set up a communications system on a number of frequencies between two points and to switch from one channel to another as propagation conditions dictate without any lining up or other attention and without interruption of the service.

MOBILE RADIO

Compact Sets Intended for Unskilled Operation

A RANGE of compact radio-telephone sets for use in motor cars, taxi cabs and various kinds of commercial vehicles and at the communicating fixed stations is now made by Hudson Electronic Devices, Ltd., Appach Road, London, S.W.2.

The sets are intended for unskilled operation and ease of servicing, and work on fixed frequencies controlled by close-tolerance quartz crystals in the band 60 to 185 Mc/s. While the same basic-circuit is used throughout, slight


differences are found in the sets for the high and the low part of the band; for design purposes it is divided into two parts, low covering 60 to 100 Mc/s and high 101 to 185 Mc/s. In general the high-band sets have one or two valves more than the low.

Transmitters follow well-tried practice, using a crystal-controlled oscillator and frequency multipliers to give the working frequency and an r.f. power amplifier which is normally anode modulated. The r.f. output is about 5 watts for mobile and 6 watts for fixed sets.

Receivers are a little different to the usual in that they employ a double superheterodyne circuit with one oscillator only. This is crystal stabilized and different harmonics are selected for the two frequency changers.

Installation costs of such equipment must inevitably vary according to circumstances, but a typical mobile equipment complete works out at about £85 and a fixed station at £120, plus cost of aerial.

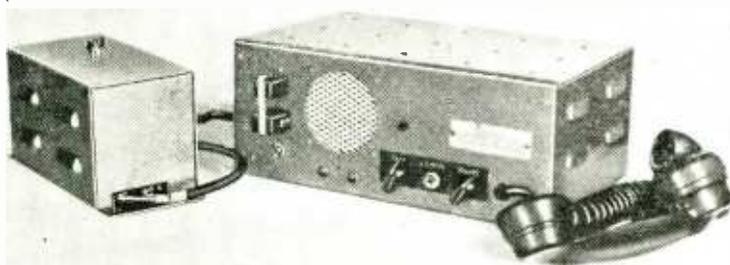Alternative models are available for f.m. or a.m. and for rotary generator or vibrator operation.



Hudson v.h.f. mobile radio-telephone installation. The unit on the left is the power supply.

Focusing Cathode Rays

How Electron Lenses are Arranged in C.R. Tubes

By "CATHODE RAY"

THIS is really a continuation of last month's issue ("Electron Optics") on the principles of electric deflection and focusing. So first will come a summary of the findings; then examples of how they are applied in cathode-ray tubes; and lastly something about magnetic focusing.

Here, then, is the summary. Cathode rays are streams of electrons in a vacuum. Each electron conforms very closely to Newton's laws of motion; that is to say, so long as it is not acted upon by any force it stays where it is or moves at constant speed in a straight line, and when a force acts on it in any direction it accelerates in that direction at a rate proportional to the force. An electron is so light that the force of gravity on it is negligible, but it responds smartly to electric and magnetic fields. An electric field is usually measured in volts per metre (or cm), and an electron placed in such a field accelerates positive-wards along the imaginary lines of electric force. These lines are at right angles to the equipotential lines, i.e., lines joining all points at the same potential. If the electric field is curved, or the electron already has some velocity in a different direction, its track does not coincide with any line of force, but bends in towards it as the acceleration in that direction increases; just as a ball thrown out of a top-floor window does not immediately follow the lines of gravitational force downwards but curves gradually towards that direction. Consequently an electron's track can be bent more sharply by a given electric field when the electron is travelling slowly than when it is fast. Its speed depends on the field strength multiplied by the distance through which it has acted, and this product is the total potential difference; if it is denoted by V volts the speed reached by the electron from a standing start is $593\sqrt{V}$ kilometres per second. The track of an electron in a given electric field pattern can be calculated from these principles, but the practical problem, which is the reverse—to find the shapes and voltages of electrodes needed to produce a field pattern that will make the electrons in a cathode ray follow a desired pattern of tracks—is more difficult, and is largely a matter of cut and try. A help towards visualizing the relationship between electric field patterns and electron tracks is the analogy in which electrons are represented by little balls, electric field by gravity, intensity of field by gradient of the surface along which the balls roll, p.d. by difference in height, and equipotential lines by contour lines.

The problem in any cathode-ray tube is to persuade the electrons, which tend to fly off in all directions by mutual repulsion, to converge to a particular point somewhere on the fluorescent screen. If they were sent towards this point slowly, their mutual repulsion would again have time to work and they could not be crowded together to produce a sufficiently small and intense spot. But if they are shot towards it at many

thousands of miles per second they are there before they have time to realize that they hate one another's faces. So that is why a high voltage is applied between cathode and anode—which is sometimes very appropriately called the accelerator.

The converging, or focusing, can be done by either electric or magnetic fields, or of course both. In most oscilloscope tubes focusing is done by electric fields. In most television tubes it is done magnetically, but there is a tendency now to revert to electric focusing in order to save the cost of the magnet.

Before we tackle a complete c.r. tube it may help to clarify our mental pictures if we review the simple process of making a broad stream of marbles converge towards a point. Suppose they are being delivered uniformly along the front AB in Fig. 1 and that we want them to arrive at C. To get them moving in that direction it is of course necessary to make the surface slope down towards it. The speed they develop (friction neglected) is $8\sqrt{H}$, where H is the total height in feet they lose in the process; this formula is analogous to $593\sqrt{V}$ for electrons. To obtain, in addition, convergence towards C the obvious method is to channel the slope into a sort of valley. The marbles respond best to this treatment near the

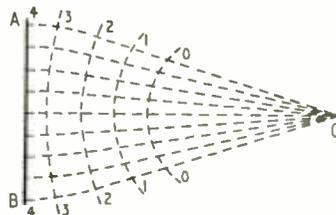


Fig. 1. Contour map of a valley slope (Fig. 2) for making marbles roll from AB to C. The numbers attached to the contour lines are in inches above C level. The other dotted lines are the tracks of the marbles: note that by the time they have reached the last (zero) contour their momentum prevents them from rolling down exactly at right angles to the contour lines.

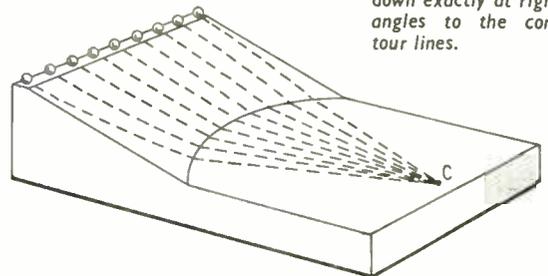


Fig. 2. Model, of which Fig. 1 is the contour map. An electric field having equipotential lines of the same pattern as the contour lines of the model would make electrons follow similar tracks.

start, before they have got up enough speed for their momentum to have much effect. Once their tracks have been directed towards C, it doesn't matter if the rest of the ground is flat. One procedure would be to make a model as in Fig. 2 and vary the shape of the channel until the balls actually did all arrive at C. Fig. 1 could then be derived from it, as a contour map of the model, the numbers on the contour lines being "inches above C level." Note that at first the tracks are almost at right angles to the contour, but nearer the foot the marble's momentum (neglected in the similar diagram last month) makes them swing out slightly.

Alternatively, if one were better at maths than at modelling, the contour lines required to obtain the converging tracks could be calculated and plotted as in Fig. 1, and these contour lines used to form an experimental model as in Fig. 2, by which the calculation could be checked. If now an electrode system were designed to produce equipotential lines shaped exactly like the contour lines in Fig. 1, electrons released along AB ought to converge on C, provided that their speed was sufficient for their mutual repulsion to be negligible. Of course the potentials of the equipotential lines must be proportional to *minus* the heights of the contours.

Gravity models have actually been used in the practical development of electron lenses, but a more usual device is the electrolytic tank, mentioned last month.

Typical Focusing System

Let us now follow the evolution of a typical electric focusing system or lens in a c.r. tube. To show what happens in the small holes through which the beam passes it is necessary to draw these parts larger than life, and if the whole tube were drawn on the same scale—well, the Editor would disapprove! So the diagrams that follow, which are longitudinal sections, are *not* accurately to scale.

The first requirement in the vacuum tube is a heated cathode, for emitting the electrons; and next, an anode for accelerating them in the desired direction. If the anode were simply a plate, the electrons would all crash into it and there would be no beam to light up the screen. So a hole is made in the centre of the anode, as in Fig. 3. Removing this bit of metal does not much affect the potential of the space it leaves, for that space is surrounded by metal at the

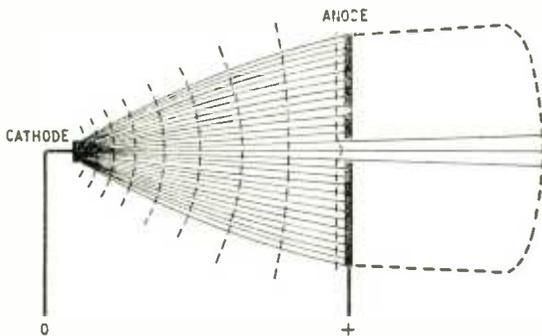


Fig. 3. Equipotential lines (dotted) and electron tracks in a tube having only a cathode and perforated anode. The space enclosed by the dotted boundary on the right is supposed to be all at the same potential as the anode.

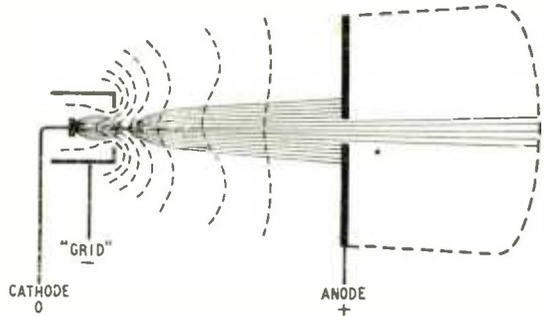


Fig. 4. The addition of a cylindrical control electrode ("grid") at a slightly negative potential provides a more highly concentrated and controllable electron beam.

anode potential. So electrons starting off from the cathode scarcely notice the difference. As we saw last month, the equipotential lines are closer together where the lines of force diverge from a relatively small electrode, which means that the electrical slope is steepest near the start, and the electrons accelerate very rapidly.

Electrons right on the axis go clean through the hole, for although the anode attraction becomes increasingly sideways as they approach it, the sideways pulls are equal all round and cancel out. Even electrons slightly off the axis are travelling so fast by the time they are near the hole that only those very close to the edge would be deflected sufficiently to hit the anode. In Fig. 3 a contour line has been drawn very close to the anode to show how the field tends to follow the shape of the anode into the hole. The tendency for the electron tracks to be attracted towards the lines of force at right-angles to this line is small, and does little more than cause the beam that goes through the hole to spread out slightly. To prevent it from being spread out more by positive surroundings beyond the anode, or being repelled back to the anode by negative surroundings, the space beyond the anode is kept at or near anode potential so that the electrons that get through continue on in straight lines.

An obvious disadvantage of the system so far is that most of the electrons go to waste by colliding with the anode, leaving only a feeble beam to light the screen. One step towards remedying this is to start the electrons off on the right lines by making them run the gauntlet of a negatively charged cylinder, as in Fig. 4. If this is made too negative it neutralizes the strong but distant attraction of the anode and prevents any electrons from getting out, so it serves the double purpose of beam-forming and controlling the amount of beam current, and by analogy with a valve (rather than any physical resemblance) is usually called the grid. One of its effects is to focus the beam at a point just beyond where the beam emerges from the grid. In a well-designed tube the diameter of the beam at this point (called the cross-over) is smaller than the emitting surface of the cathode, so in effect the electrons are coming from a close approximation to the ideal point source, to the benefit of subsequent focusing.

If the screen were just beyond the anode the spot of light would be little bigger than the hole in the anode. But to leave room for deflecting the beam over a reasonable area the screen has to be a considerable distance beyond the anode, and even if the hole

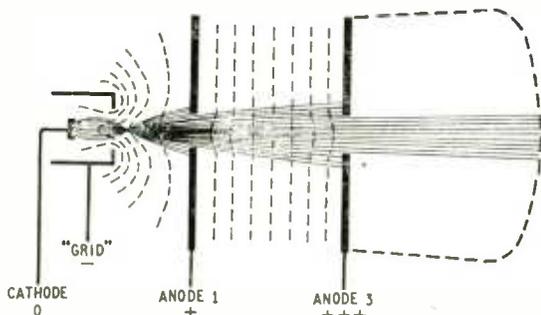


Fig. 5. Although the addition of another disk anode at a higher potential does not improve the focusing it is a step towards an effective electron lens—Fig. 6.

were extremely small the beam would spread too much to give fine definition, and, moreover (having come through such a small hole) it would be very weak. So the hole is made relatively large and the wide beam going through it is made to converge. The arrangement that does this is the electron lens proper. There are innumerable varieties, but many of them comprise three anodes; in some, these anodes are kept at progressively higher potentials; in others, the first and third are highly positive and the second is less so, or even at or near cathode potential. Fig. 5 shows the sort of thing that would happen if the first and third anodes were disks with relatively large holes and the middle anode were omitted. The field between the anodes would be fairly uniform and would accelerate the beam but have little or no focusing effect.

Now put in a middle anode of cylindrical shape, as in Fig. 6. The metal wall of the cylinder short-circuits the electric field, for obviously it is all at the same potential, and so the equipotential lines are crowded together at the edges of the cylinder but are free to spread out in the center. Remembering that the electrons tend to take the shortest cut from one equipotential line to another (but at the speed they are now doing they only *tend* to do so) we see that this pattern will make them converge. If it is found that the point to which they converge is, say, short of the screen, then by raising the potential of the middle anode some of the equipotential lines are transferred from the converging region to the diverging region, and the point of convergence is pushed farther away from the lens. This adjustment alone does not ensure that all rays converge on the *same* point to give a sharp focus; that depends to some extent on the voltages applied to the other anodes, but mainly on the shapes of all the anodes.

Reversing Potential Gradient

A system basically like that just described is quite usual in oscilloscope tubes. The requirements for television are more exacting, and in a recent design there are four anodes: the first at only about +250 V, to attract the electrons gently through the grid orifice; the second and fourth forming a long cylinder with one section removed; and the third, between them, at about zero volts. The second and fourth are at about +10,000 V. One important thing to note about this and many other electric lenses is that the potential gradient reverses (in this example between the second and third anodes). After having fallen rapidly down a steep slope, the electrons have to go uphill

for a short distance, like a switchback. If they strike this upward slope head-on, at right angles to the equipotential lines, all that happens is that they are decelerated. The final velocity corresponds to the net difference of potential between start and finish. But if they strike the upward slope at an angle, that angle is *increased* by the slope (instead of being diminished, as it would be if the slope were downward). One can easily check this by rolling balls up a slope. Of course, if the slope rises to a greater height than the original starting point, it fails to clear the summit and rolls back; but in the electron lens with the zero-potential third anode this condition is avoided by placing it so that it is largely screened by the 10 kV anodes.

I hope that by the time of the next Radio Show someone will have made a gravitational model for the educational stand. A better method than messing around with plaster of Paris is to mount a sheet of rubber in a horizontal frame and clamp portions of it (corresponding to sections of electrodes) at heights representing the potentials of those electrodes. It could be a simple matter for the heights to be variable, showing the effects of focusing adjustments and also of deflecting potentials, about which I have said nothing, because their principle ought by now to be obvious.

Of course, it must be realized that although such a model is three-dimensional it represents the electric field pattern in only two dimensions—a cross-section of the electron lens, as in Figs. 1-6 here. The lens is (or should be) symmetrical around its axis, so that the same diagrams or models hold good for all longitudinal sections. Equipotentials are always *surfaces*; it is only in section that they appear as lines.

The reason why this three-dimensional situation can be discussed on two-dimensional paper is that the direction in which electrons are accelerated by an electric field is the same as the direction of the field (lines of force). And the reason why the effects of magnetic fields are so much more difficult to visualize is that the direction of acceleration is at right angles both to the direction of the electron's movement and the direction of the field, so even when the problem is presented in its simplest form it still involves three dimensions. And in a solemn session of the Institution of Electrical Engineers I once heard one learned gentleman after another confess that visualizing anything in three dimensions was quite a headache. (Viewers of "3D" films will doubtless heartily agree.) However, it is a difficulty that is basic to electro-magnetism. In

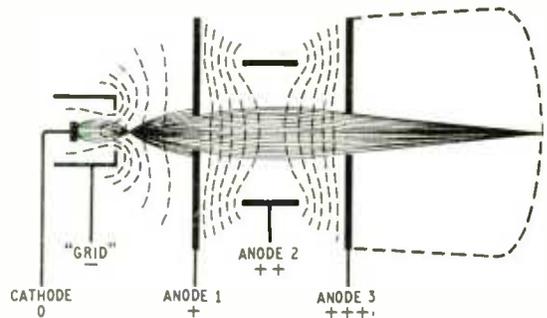


Fig. 6. An intermediate anode of cylindrical shape bends the equipotential lines (which are actually sections of equipotential surfaces) as here, making the beam converge to a point on the fluorescent screen.

ordinary electrical engineering—dynamors, motors, etc.—the problem is often a little easier because the electrons are confined to conductors, which are usually not free to move just anywhere. Electrons in a vacuum are not so bound. Their gyrations under the influence of combined electric and magnetic fields are the mathematicians' delight—but the non-mathematicians' despair.

However. Suppose we start with an electron gun something like that shown in Fig. 4, but with a larger hole, through which a slightly diverging beam of electrons is shot at high speed towards the screen. And suppose now that we wind a long coil around the beam, as in Fig. 7, producing a magnetic field pointing the same way as the electrons. What happens? To those electrons right at the centre of the beam, along its axis, nothing; for their path coincides exactly with the axial magnetic line of force, so they do not cut across the field, even slightly. So far as they are concerned there might not be a field. But those that are diverging do cut across the field, and so come under the law that makes electric motors motor. The appropriate memory-aider is the Left Hand Rule: if the thumb and first two fingers are stuck out all at right angles to one another, and the First finger is pointed in the direction of the magnetic Flux, and the seCond finger in the direction of the Current (which is opposite to the direction of the electrons) across the flux, the thuMb shows the direction in which the electrons tend to Move because of the electromagnetic force.

Cathode's-eye View

Now in our c.r. tube the movement of the electrons, in so far as it is straight down the tube, parallel to its axis, is not across the flux at all, so merely confuses the issue; the proper viewpoint for seeing the movement across the flux without the axial movement is from the cathode. So here, Fig. 8, is a cathode's-eye view of the electron beam. Electrons along the axis remain at the centre all the time so do not appear to be moving at all; all others appear to be radiating outwards. Let us fix our attention on one particular electron just leaving the cross-over and diverging to the right. Since, for purposes of the left-hand rule, that is equivalent to a current in the opposite direction, the second finger should point to the left. The forefinger is pointing away, along the flux line, so the thumb shows that the force acting on the electron will make it accelerate downwards. If for simplicity we assumed (what in a real tube is not likely to be true) that the speed of divergence was constant, and also (what is certainly not true) that the direction of

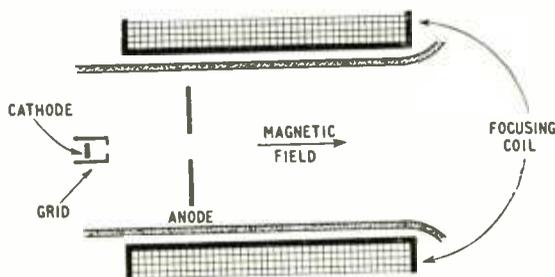


Fig. 7. Section of electron gun, surrounded by a long coil designed to produce a nearly uniform magnetic field down the tube in the same direction as the electron beam.


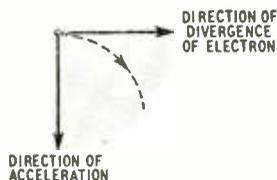


Fig. 8. Cathode's-eye view of the beam, showing the effect of the magnetic field on an electron diverging to the right.

Fig. 9. The divergent paths of electrons, as seen from the cathode, are curled round into circles by the magnetic field. The time taken to do a complete circle is the same for all electrons, slow or fast.

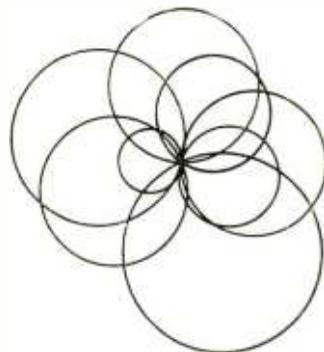

acceleration continued to be downwards, then the path of the electron would be a curve as shown dotted. This is the same kind of curve as that traced by a ball thrown horizontally, and for the same reason—that the ball is given a constant speed horizontally, combined with a steadily growing speed downwards.

In practice, during the first stage of the electron's flight, from cross-over to anode, it is not going at uniform speed but is being accelerated by an electric field; it is only from the anode onwards that its horizontal motion is at constant speed. However, this complication is largely offset by the fact that the electromagnet force causing the electron to accelerate downward is proportional to the speed of the electron as well as to the strength of the magnetic field. The real complication is the second one—that the downward acceleration doesn't keep on being downward. It is always at right angles to the electron, so directly the electron starts curving downward as in Fig. 8 the magnetic acceleration veers round to the leftwards. This makes the electron curve all the quicker, which keeps the acceleration veering, and so on. When the ordinary mind tries to follow the electron it is therefore likely to become very dizzy. Even the chap who rather fancies his proficiency with the calculus and tackles the thing mathematically may quite possibly get himself into a mess.

But the situation is exactly similar to a very familiar one—a weight being whirled round at the end of a string, or, if you prefer, the earth revolving round the sun. The weight, let us suppose, is given a constant speed in a certain direction—say the original direction of the electron in Fig. 8. But being attached to the string it cannot go out in a straight line; it goes round in a circle centred at the point where the other end of the string is fixed. To keep it in this orbit, the string has to exert a tensional force. This force is obviously always at right angles to the direc-

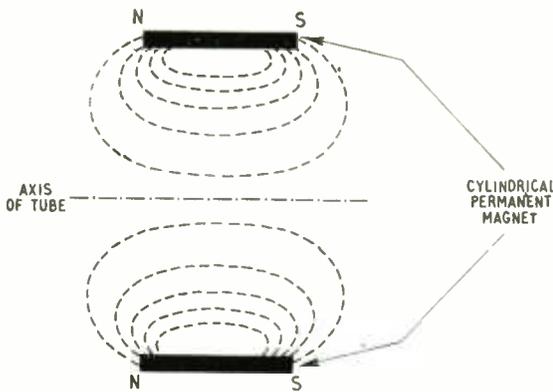


Fig. 10. In practice a short magnet is used, and the effect on the electrons is more complicated.



Fig. 11. One effect of shortening the magnet is to change the circles of Fig. 9 into shapes more like this. The final result can still be satisfactory, and much more conveniently obtained.

tion the weight is going. And if the speed of the weight is constant, so too is the force. Since these are exactly the conditions that govern the movement of the electron, it is reasonable to suppose (and it can be confirmed mathematically) that the electron whirls round in a circle.

Corkscrew Electron Tracks

All electrons have the same mass and charge, and we are assuming that the magnetic field is the same for all, so for a given speed they all experience the same force. Actually, of course, the speeds with which they cross the field are different; those only just off the axis diverge much more slowly than those on the outside of the beam. But if the equation for centrifugal force is applied to weights that are all the same, and force proportional to speed, it shows that the time for one complete revolution is the same for all, regardless of speed. The faster speeds are handicapped by having to take bigger circles. The same applies to electrons. So after a certain time all electrons that started off from the centre together, whether fast or slow, have done one revolution and arrive back on the axis again simultaneously. In the meantime, of course, they have been travelling down the tube, so the electron tracks are actually like a corkscrew—or a helix, to be more scientific. Fig. 9 shows one curl each of a few electron tracks as seen from the cathode. The small circles are made by slowly diverging electrons; the larger circles by the faster ones.

Increasing the strength of the magnetic field increases the centre-wards force on all the electrons, so tightens their curls and reduces the time they take to execute each complete turn. To get a well-focused spot it is obvious that the strength of the magnet must be adjusted so that one of the times when all the

electrons meet again is the moment they reach the fluorescent screen—which is a grand place for a reunion; they all get beautifully lit up.

Obvious it may be, but quite unpractical. To keep the electrons corkscrewing all the way to the screen it would be necessary to maintain the uniform magnetic field all the way there—a point that seems to have been overlooked in some of the drawings I have seen, purporting to explain magnetic focusing. Even to provide a magnet as long as the one in Fig. 7, extending as far as where the tube begins to open out, is too expensive and inconvenient, let alone one enveloping the entire tube, screen and all! So in practice a very short magnet is used, producing a curved field pattern something like Fig. 10. If you have been thinking that the theory of magnetic focusing has already been complicated enough, even with our beautifully uniform but quite unpractical field, you (and I) may well quail at the prospect of having to trace precisely what happens to diverging electrons in a field that varies rapidly both in strength and direction. But the operative word is “precisely.” We can make a guess at roughly what happens.

At first, before an electron gets into the magnetic field, it is diverging quite happily in a straight line. But before it has had time to go too far, at the comparatively slow speed of this first stage of the journey, it finds itself going through the magnet ring, with a strong magnetic pull making it wheel round sharply. The magnet has been made of such a strength that by the time the electron is beyond its influence it has done an about-turn and is converging towards the axis again, as in the view from the cathode in Fig. 11. It is now also shooting towards the screen at really high speed, and, if everything has been done right, hits it just as it (and all its mates that left the cathode at the same moment) are on the axis again. Of course this is assuming the beam is not being deflected. If it is, then they meet elsewhere, but as all are equally deflected they do meet.

But don't ask me to produce a mechanical analogy to demonstrate all this! The proof of the thing is on your TV screen.

Awards for Technical Authors

THE Radio Industry Council's premiums for technical writers for the year 1953 are now announced; as will be recalled, these awards are made with the object of encouraging the publication of clearly written expositions of British achievements in radio and electronics.

Premiums of 25 guineas each are awarded to the authors of the following articles:—

“Spectrum Equalization,” by G. G. Gouriet (*Wireless Engineer*, May).

“Triode Transformation Groups,” by A. W. Keen (*Wireless Engineer*, October).

“A Cylindrical Magnetron Ionization Gauge,” by A. H. Beck and A. D. Brisbane (*Vacuum*, April).

“The Scanning Electron Microscope and the Electron-Optical Examination of Surfaces,” by D. McMullan (*Electronic Engineering*, February).

“A Linear Sweep Cathode-Ray Polarograph,” by H. M. Davis and Miss J. E. Seaborn (*Electronic Engineering*, August).

“Selective Calling for Radio-Telephone Systems,” by J. R. Pollard (*Electronic Engineering*, December).

Improved Radio Altimeter

Servo Principle Giving Greater Freedom From Noise

By A. BLOCH,* K. E. BUECKS† and A. G. HEATON‡

THE radio altimeter has now become quite a well-known instrument for giving the pilot of an aircraft an indication of his clearance height above the terrain. Like many distance-measuring devices it works on the echo or radar principle, only instead of pulses it makes use of frequency modulation to obtain the actual measurement. A frequency-modulated continuous wave is transmitted downwards from the aircraft and is reflected back from the ground. By the time it reaches the aircraft again the transmitter frequency has changed, so there is a difference between the frequency of the received wave and that of the transmitted wave. This frequency difference is, of course, proportional to the time delay experienced by the returning wave, and so to the height of the aircraft above ground, and in the instrument it is obtained simply by heterodyning the two waves and taking the resultant difference frequency.

A new instrument has now been designed which works on this familiar principle but has improved sensitivity. It will give a reliable indication of height up to 5,000ft with an accuracy of $\pm 3\%$ ± 5 ft and over all types of ground—including dry desert which reflects only 3% of the incident power. At the same time the new instrument avoids certain complications, such as range-switching, which were necessary in previous designs. It uses a continuous-wave transmission, the frequency of which is varied linearly with time between 1,605 and 1,655 Mc/s.

One method of obtaining the greater sensitivity has been by the use of the superheterodyne principle. This achieves the required large amplification of the received signal without introducing difficulties brought about by microphonic noise created in the amplifier by the vibration of the aircraft. The wave returned from the ground may have an amplitude of only one millionth or less of the amplitude of the wave transmitted and may thus require an amplification of 10^7 times in order to operate a robust indicator.

Instead of the returned wave being heterodyned with the transmitted wave, it is heterodyned with an auxiliary wave, the frequency of which is always 110 Mc/s higher than the transmitted wave. This auxiliary frequency is created by mixing part of the output of the transmitting oscillator with the output of a 110-Mc/s oscillator and filtering out the desired component. If the returned wave had been heterodyned with the transmitted wave directly the resultant beat frequency would have been an audio frequency. Here, however, it is 110 Mc/s plus or minus this audio frequency, which is, of course, quite low compared with 110 Mc/s, so that for brevity we can still speak


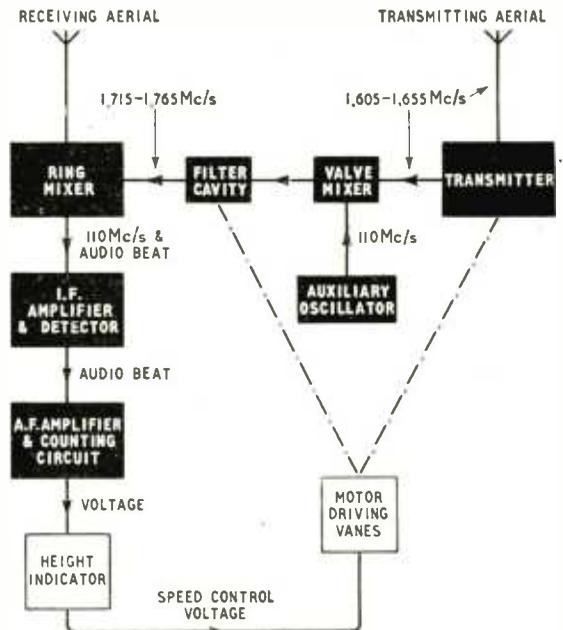


Fig. 1. Simplified block schematic illustrating the principle of the altimeter.

Fig. 2. The cavity resonator of the transmitting oscillator, showing the small rotating capacitor vane.

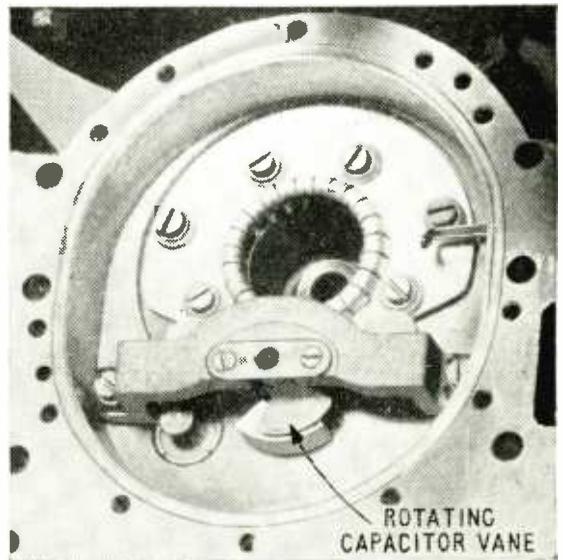

* Research Laboratories, General Electric Company.

† Royal Aircraft Establishment.

‡ Salford Electrical Instruments.

of an intermediate frequency of 110 Mc/s. This intermediate frequency is amplified about a thousand times and then mixed with the output of the auxiliary 110-Mc/s oscillator. As a result, beats are produced of the same audio frequency as if the returned wave had been heterodyned directly with the transmitted wave. These beats are subsequently amplified and sent to an indicating mechanism, which will be described below. The exact frequency of the 110-Mc/s oscillator is immaterial, as long as it stays within the pass band of the i.f. amplifier.

Additional protection against noise is obtained by an application of the principles of servo mechanisms to keep the bandwidth of the amplifier smaller than it would be normally. In order to get a sufficiently accurate indication of heights below 900ft the constants of the altimeter are chosen so that for this height a beat frequency of just 10 kc/s is produced. Under the same conditions at 5,000ft a beat frequency of over 50 kc/s would be produced, so that an amplifier of this bandwidth would be required, which would pass five times as much noise as an amplifier with a bandwidth of only 10 kc/s. In order to avoid this the following scheme has been adopted. The frequency variation of the transmitting oscillator is produced by a rotating capacitor vane driven by a small motor. Once a height of 900ft has been reached, any further increase in height is arranged to cause a reduction of the voltage supplied to the driving motor, slowing down the motor until a beat frequency of 10 kc/s is restored. Obviously, the amount of slowing down of the motor is just as much a measure of the height reached as is the frequency attained with constant motor speed. The additional advantage of this scheme is that from a height of 900ft upwards the beat frequency produced is always 10 kc/s, and it is possible to make the audio amplifier most sensitive to this particular frequency. Thus the weaker signals, i.e., signals received at heights greater than 900ft, get maximum amplification.

Circuit Arrangement

Fig. 1 shows the layout of the instrument and the relation of its various parts. The transmitting oscillator consists of a triode operating in a cavity resonator (Fig. 2). This resonator is modulated through the range 1,605-1,655 Mc/s by a small rotating capacitor vane driven by a special d.c. motor. (In this motor the speed of rotation is an accurate measure of the voltage applied to the terminals of the motor, a property required in the operation of the servo mechanism.) The larger part of the oscillator output is fed to the transmitting aerial. A small part is fed to the valve mixer, where it is mixed with the output of an auxiliary 110-Mc/s oscillator. This mixer valve, a triode, also operates in a cavity resonator which is of similar dimensions to the transmitting oscillator cavity and is always kept in tune with the required frequency (110 Mc/s above the transmitter frequency) by a rotating capacitor vane mounted on the same shaft as the vane of the transmitting cavity. The output of this filter cavity is used as the "local oscillation" and is mixed with the received signal in the ring mixer.

The ring mixer is a so-called balanced mixer, i.e., a type in which two mixing elements (here silicon crystals) are operated simultaneously in such a way that the effect of any amplitude modulation of the local oscillator frequency is cancelled in their com-

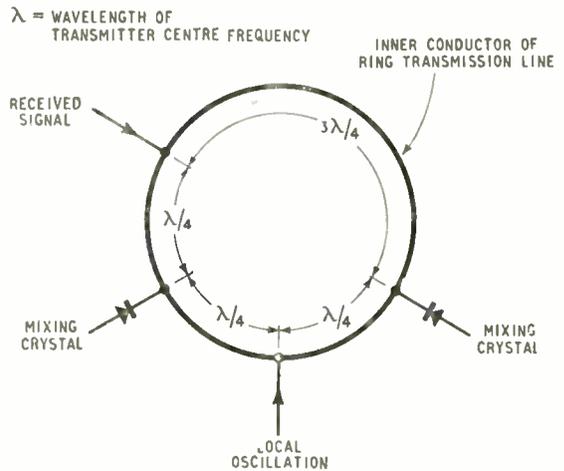


Fig. 3. Principle of the ring mixer. The local oscillation is fed to the crystals in phase while the returned signal is fed to them 180 out of phase. The i.f. outputs from the crystals are then in opposite phase and as they are combined by subtraction any unwanted amplitude modulation of the local oscillation is cancelled out.


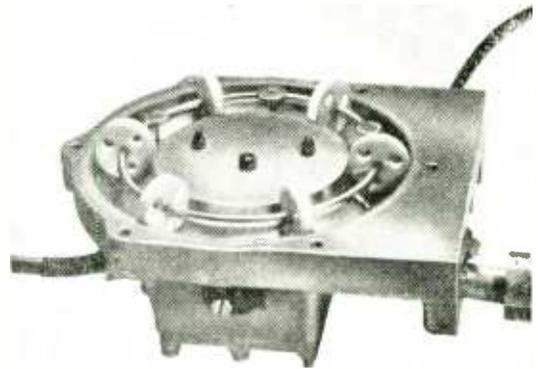


Fig. 4. The ring mixer consists of a coaxial transmission line, 1.5 wavelengths long, formed into a circle. This is an opened-up view.

bined output as far as possible (Figs. 3 and 4). The output of the ring mixer consists of a 110-Mc/s intermediate frequency with a superimposed audio beat corresponding to the height of the aircraft. This is passed through an i.f. amplifier, which has a bandwidth of 1.5 Mc/s, and then on to a detector where the audio beat frequency is obtained. After amplification the audio beat goes to a counting circuit which produces an output voltage proportional to the rate of the beat.

It has already been mentioned that the altimeter has two different modes of operation: one, below 900ft, where the modulating motor is run at constant speed and the frequency of the beats is taken as a measure of height; and another one, for heights above 900ft, where the beat frequency is kept constant at 10 kc/s and the motor speed is taken as a measure of height. The altimeter must therefore include some mechanism which will automatically change from one mode of operation to the other one without an external switching operation.

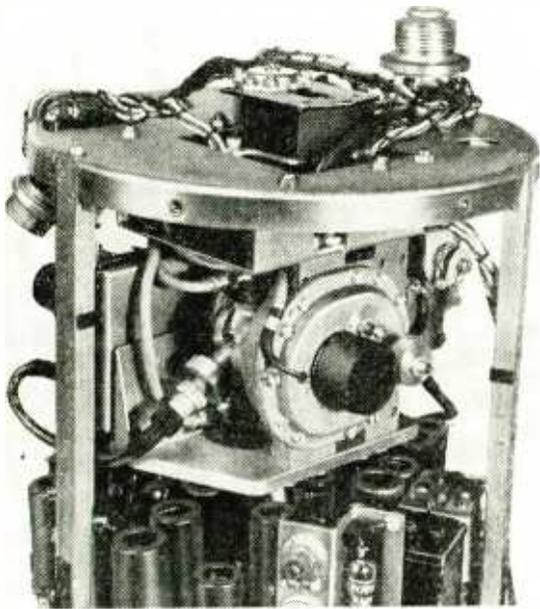

One end of the chassis showing the cavity resonator of the valve mixer and the capacitor-vane driving wheels.

The voltage from the counting circuit is compared with a voltage derived from a potentiometer that is mechanically coupled to the height indicator. Any unbalance detected is used to control the motor which sets the potentiometer and indicator in such a way as to eliminate the unbalance. For heights below 900ft the voltage derived from the counter is (because of the constant speed of the modulating motor) proportional to the height of the aircraft. The voltage derived from the potentiometer is proportional to the height shown by the indicator. Thus the position of the indicator will always reflect the rate at which the beats are produced and therefore show the correct height (Fig. 5).

Second Mode of Operation

The potentiometer is constructed in such a way, however, that once the indicator setting exceeds 900ft it provides constant output, irrespective of height. Evidently its output can then only be balanced if the modulating motor is slowed down. For this purpose there is mechanically coupled to the first potentiometer a second potentiometer which supplies the voltage for the modulating motor. If the indicator shows a height of less than 900ft this second potentiometer is in a "flat" portion of its range and thus supplies the required constant voltage for the modulating motor. But if the indicator goes to a height of more than 900ft the potentiometer is in an appropriately graded part of its range and supplies to the motor a voltage which decreases with the height shown by the indicator. Hence, when the aircraft rises to a height of more than 900ft the indicator motor—not being able to establish a balance on any setting of the indicator of less than 900ft—will run on, drive the first potentiometer on to its "flat" portion and the second potentiometer on to its graded portion. It will thereby reduce the speed of the modulating motor until there is again



Fig. 5. Face of the height indicator. The full scale represents 1,000 ft, so the pointer makes five revolutions for 5,000 ft. Integral thousands are clocked-up in the window at the bottom.

a balance between the output of the counter and the voltage supplied by the first potentiometer (now constant, corresponding to a beat frequency of 10 kc/s). With proper grading of the second potentiometer the setting of the indicator at which balance is obtained and the indicator motor stops corresponds again to the height of the aircraft.

This second mode of operation continues for heights up to 5,000ft. For heights exceeding this figure the motor speed stays constant and an indication is given that the aircraft is above the limiting height. This "hold off" presentation continues above 5,000ft, even if the signal should fade into noise, as sufficient gain is provided before the counting circuit for this to be operated by noise. Such noise represents a signal above 10 kc/s, since the audio amplifier characteristic extends beyond 20 kc/s. It will be apparent that if an output corresponding to a frequency greater than 10 kc/s is produced by the counter, the indicator will run up beyond 5,000ft in an endeavour to find a balance point.

Automatic Change of Characteristics

An additional feature of the altimeter is a system which indicates to the pilot that he is flying at a pre-selected height and warns him if he drops below this height.

An interesting point about the audio amplifier which magnifies the beat frequency is that it has a system for automatically changing its frequency characteristic to suit the mode of operation of the altimeter. Two input channels are provided. The first is in operation when the signal strength is below a certain level and its characteristic is of the peaked form referred to already. As the signal strength increases a bias is produced which closes this channel and the signal is now transferred to the second channel, which has a flatter characteristic. This arrangement has been chosen because when working at low altitudes; i.e., at low beat frequencies, a peak in the frequency response characteristic at 10 kc/s would cause an undesirable deterioration in the signal/noise ratio.

The aerials used are identical for receiver and transmitter. They are arranged on the aircraft in such a position that the direct transfer of energy from transmitter to receiver is kept at a minimum. An installation on either side of a tail plane is usually sufficient for this purpose. The directivity of these aerials is prescribed by operational requirements such as angles of bank, dive, or climb during which the reflected signal must be received.

Attenuators for High Frequencies

By R. F. PRIVETT,* M.Sc.

Basis for a Design Using Standard Components

MANY r.f. measurements, such as the measurement of receiver gain, require that a known voltage be produced at the input terminals of the unit under test. The input voltage may be too low to permit it to be measured directly, and it is then usual to generate the signal at a level convenient for measurement, to attenuate it to the required level and to transmit it via a screened conductor to the unit under test. The combination of oscillator, monitor, attenuator and coaxial cable is called a standard signal generator. This article is intended to give the reader an understanding of that part of a signal generator which is in general the least understood—the output system.

"Cathode Ray"† has given an introduction to the subject in which he stresses the importance of matching and illustrates "ladder" attenuators and attenuators which contain "T-section" pads of fixed attenuation, which are selected by the operation of two-pole, two-way, changeover switches. The latter system is the one described in this article, and, as designed, the attenuator can provide any attenuation variable in increments of 1 db, up to a total of 80 db, by the combination of pads of 1, 2, 5 and 10 db loss.

To appreciate the importance of each factor involved in attenuator design it is necessary to consider the following topics: (1) Precautions required in the transmission of r.f. energy and in particular propagation along coaxial cables. (2) The r.f. behaviour of resistors, and the variation of pad attenuation with changes of resistance. (3) The effects of switch capacitance and lead inductance.

In a signal generator one must also consider how best to measure the attenuator input.

The R.F. Transmission Circuit

An output system is illustrated in Fig. 1. The open circuit voltage E of the generator may be measured and held constant and the voltage presented to the unit under test is the voltage e developed across the cable termination Z_T . This diagram has been simplified and shows the generator as a source of open-circuit voltage E and internal impedance Z_S , the attenuator as comprising one "T-section" and the termination as an impedance Z_T separate from the unit under test (in practice this unit may provide a part, or all of this terminating impedance).

We will now concern ourselves solely with the requirements placed by the cable on Z_T and Z_S . The physical form of the generator and the behaviour of the attenuator will be discussed later. So let us

connect the generator directly to the cable by putting $R_1 = R_3 = 0$ and $R_2 = \infty$.

The characteristic impedance Z_0 of a cable may be defined as the input impedance presented by an infinite length. A lossless cable has a Z_0 which is purely resistive and can be calculated in terms of the geometry of the conductors and the dielectric constant of the insulation. Conductor resistance and dielectric loss cause Z_0 to have a reactive component and cause attenuation along the length of the cable, which, however, can be minimized by the choice of an optimum value for Z_0 . The standard polythene-insulated cable is designed for this optimum and has a Z_0 which may be taken as resistive, and is nominally 75 ohms with a manufacturing tolerance of a few ohms. For our purpose the cable will be considered lossless.

A length of cable can nevertheless affect the output by introducing impedance transformations; for example a cable of length one quarter of a wavelength ($l = \frac{\lambda}{4}$) can behave as a transformer causing our generator of impedance Z_S to appear at the other end of the cable as a generator of impedance $Z' = \frac{Z_0^2}{Z_S}$.

The open circuit voltage E would be transformed as the square root of the impedance, i.e. $E' = E \sqrt{\frac{Z'}{Z_S}}$.

From the above it follows that the variations of the output voltage e due to changes with frequency in the electrical length of the cable (defined as $\frac{2\pi l}{\lambda}$) can be

reduced to zero by making $Z_S = Z_0$. The generator is then matched to the cable and the value of the load Z_T is unimportant. By a similar process one may show that the generator impedance Z_S is unimportant if $Z_T = Z_0$.

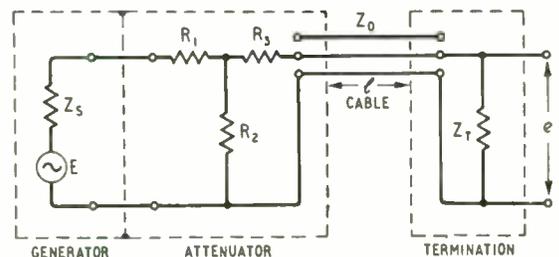


Fig. 1. Simplified circuit of the output system of a signal generator.

* General Electric Company (Research Laboratories).
 † "Wireless World," March 1953, p. 131.

In practice the cable may not be uniform and the source or generator may not be perfectly matched. Then it is best to have the cable approximately matched at *both* ends.

It is possible to design the generator impedance to match the cable, and imperfections are more likely to be present at the termination. Part or all of the terminating impedance may be provided by the unit under test, and the effects of mismatches introduced by the unit must be minimized.

As an example of the use of a matched generator in minimizing the effects, consider the problem of providing a constant voltage at the input terminals of an amplifier which has a small input capacitance C . If these terminals are shunted by a resistor the cable can be terminated correctly at low frequencies, but the capacitance will introduce a moderate mismatch at high frequencies. The voltage developed across the terminals has been calculated, by methods outlined in the Appendix, for the case of a matched generator, and for that of a zero impedance or constant-voltage generator. The results for the particular values of $C = 10\text{pF}$, cable $Z_0 = 75\text{ ohms}$ and length $l = 1\text{ metre}$ are plotted on Fig. 2. The dotted curve, calculated for a generator of 75 ohms output impedance, shows a loss increasing with frequency to a value of 0.86 db at 200 Mc/s, whereas the full curve, calculated for a zero impedance source, shows large fluctuations with frequency; even at 30 Mc/s the output has risen by 0.5 db.

We may conclude that a generator of the correct output impedance is essential, unless measurement is restricted to frequencies at which the cable has a length less than one-eighth of a wavelength, or to frequencies at which the unit under test can be assumed to match the impedance of the cable.

R.F. Behaviour of Resistors and Resistance Networks.

The low-frequency accuracy of an attenuator using resistance networks is limited by the stability of the component resistors. D.c. measurements of resistance and successive adjustments may be employed to approximate to the required value of resistance with any accuracy likely to be desired, until the error remaining is of the order of the errors expected to arise with age, temperature, humidity, etc.

Unfortunately the resistors of the higher stability generally become extremely reactive at high frequencies, and attenuator design has shown signs of division into two classes. The first class is exemplified by the precision instrument accurate to a hundredth of one db which contains wire-wound resistors, and the second by the instrument of medium d.c. accuracy which is maintained at high frequencies. Research is in progress to improve the high-frequency performance of the former class and the accuracy of the latter. The attenuator described falls into the latter class and employs the "cracked"

carbon high-stability type of resistor. As a useful attenuator can be constructed using the familiar resin-bonded carbon type of resistor both types will be considered.

The resistance values required for attenuator pads of 75 ohms characteristic impedance are given in Table I. Each pad is symmetrical so that, in the nomenclature of Fig. 1, $R_1 = R_3$.

A pad in which all the resistances are the same has attractions economically and, as will be shown later, electrically. This pad gives an attenuation of 11.44 db. The values are calculated from the formulae:—

$$R_1 = Z_0 \left(\frac{N-1}{N+1} \right)$$

$$R_2 = Z_0 \left(\frac{2N}{N^2-1} \right)$$

where N is the ratio of input current to output current, which in the case of a 3 db pad is $\sqrt{2}$.

The resin-bonded carbon resistor can be obtained in miniature form with ample dissipation for attenuator inputs of a few volts r.m.s., and the required value of resistor can be approximated to within ± 5 per cent by selection from the preferred standard values of the 5-per cent tolerance range.

For example, half the resistors nominally 20 ohms or 22 ohms should be within 5 per cent of the 21-ohm value required by the 5db pad. With a temperature coefficient averaging 0.05 per cent per degree C and a shelf-life stability of ± 2 per cent, selection to ± 3 per cent would be profitable.

The errors in attenuation between correct values of source and load impedance due to pad resistances of 90 per cent of the correct values are given in Table II.

The values in brackets are those obtained with a

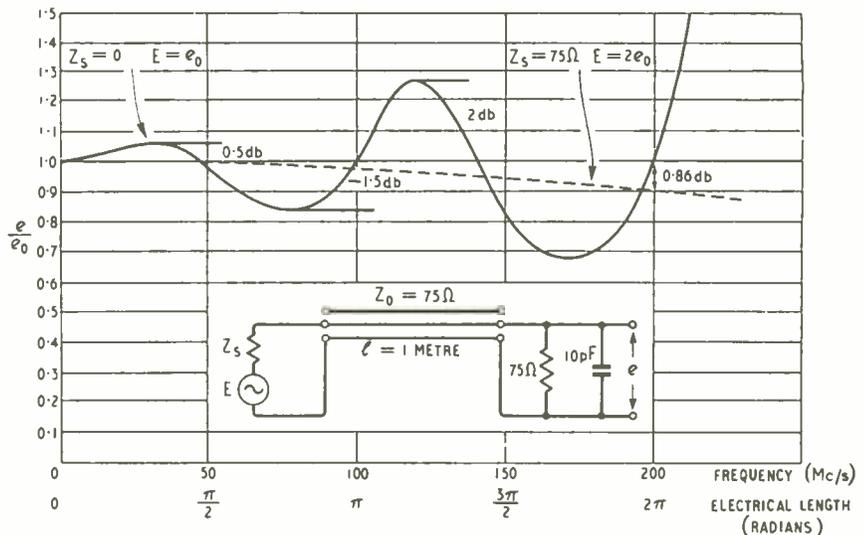


Fig. 2. Effect of source impedance on output voltage from a 1-metre coaxial cable feeding a resistance equal to the characteristic impedance shunted by 10pF.

zero-impedance source and it can be seen that a correct source impedance is important in reducing the effect of errors. The change in attenuation due to a proportionate change in all resistances is then low, and this has a bearing on high-frequency response (as will be shown).

"High-stability" resistors, stable to ± 1 per cent,


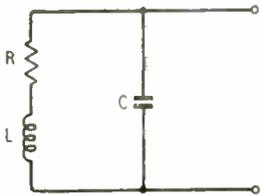


Fig. 3. Equivalent circuit of a carbon resistor.

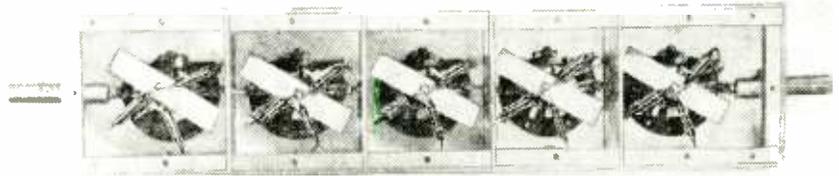

Right: Fig. 4. Underside of attenuator using wafer switches. Foil instead of wire is used for cross leads to reduce inductance.

TABLE I

Attenuation (db)	20	11.44	10	5	3	2	1
R_1 ..	61.36	43.30	38.96	21.01	12.8	8.66	4.31
R_2 ..	15.15	43.30	52.71	123.4	212	323	650

TABLE II

Nominal attenuation (db)	Increase in attenuation (db) due to -10 per cent resistance change			
	R_1 only	R_1 and R_2	R_2 only	R_1, R_2 and R_3
3	-0.05	-0.15	+0.17	+0.02
11.44	-0.26	-0.51	+0.54	+0.02
20	-0.38	(-0.8)	(+0.4)	(-0.28)
		-0.72	+0.76	+0.02

can be obtained with a nominal dissipation of $\frac{1}{2}$ W. They are slightly larger than the conventional resistors described, but in spite of this, and the spiralling of the resistive track which is necessary to control the value of resistance, they have high-frequency properties which are very similar. An equivalent circuit which approximates to both types of resistor in the resistance range of 10 to 1,000 Ω is shown in Fig. 3.

The shunt capacitance C is usually below 1 pF and the series inductance will vary with lead length, but should be under 0.02 μ H. It thus appears that the behaviour of a resistor will vary with its resistance value R and it is found that the impedance of a 1,000- Ω resistor will fall at high frequency and that of a 10- Ω resistor will rise. Resistors in the range 40 to 200 Ω can be expected to retain a resistance close to their d.c. value.

Reference to Tables I and II will now show why it is advisable to avoid low values of resistance, especially when included in a pad of high attenuation, e.g. the 15- Ω resistor in the 20-db pad. The advantages of using pads with equal resistors, having the same behaviour of high frequencies, are now obvious. This suggests that the bulk of the attenuation should be provided by pads of 11.44 db attenuation and to approximate to this value it was decided to standardize on a 10-db pad.

Switches and Interconnections.—Two-pole two-way switches are required to control the insertion of the pads and many varieties of toggle and wafer switches are available. The wafer type has the lowest capacitances to earth and across the contacts, but its use leads to a large attenuator compartment. Fig. 4 gives an underneath view of an attenuator using wafer switches and containing 20, 10 and 5 db pads, giving a total attenuation of 75 db variable in increments of 5 db. Such a design using pads of 10 db maximum attenuation and giving increments of one db would result in a very bulky unit, but it is possible that 20 db pads in which the 15- Ω resistor is replaced by 3 resistors each of 45 Ω , would be satisfactory when used in conjunction with wafer switches. Space could be saved by using toggle switches to control the insertion of the pads of lower attenuation.

Some attention was given to the performance of the attenuator at its zero attenuation setting, as heavy losses due to the switches and connecting leads would render the attenuator useless for incorporation in a signal generator. Measurements were made of the input impedance Z_i of the wafer-switch type of attenuator at its zero setting with a 75- Ω load across the output terminals. The results of these measurements together with the equivalent circuit of a switch and its connections are shown in Fig. 5.

The reduction of the inductance L of the connection across the switches, which was achieved by replacing

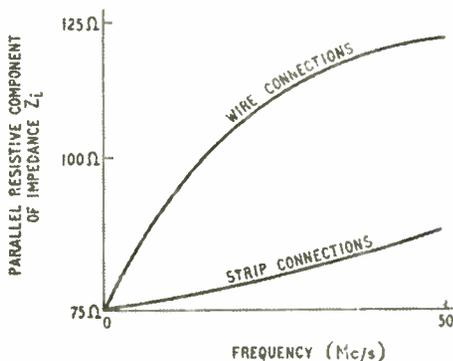
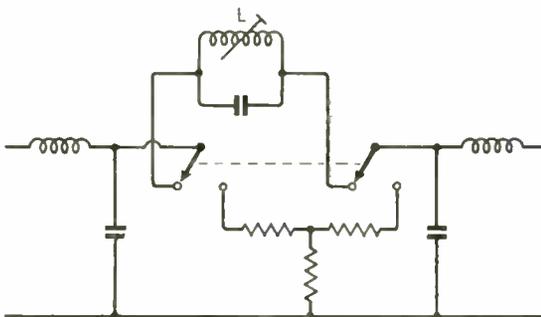


Fig. 5. Equivalent circuit of switch and wiring and variation of losses with frequency.

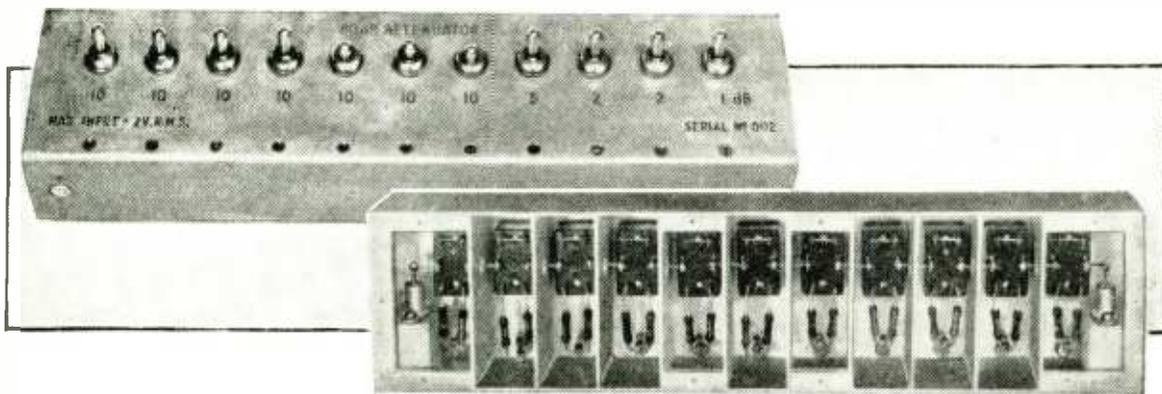


Fig. 6. Attenuator unit for frequencies up to 100 Mc/s using standard toggle switches.

the original copper wires by strips of copper foil, resulted in an input impedance which varied slowly with frequency. These strips can be seen in Fig. 4 and the theoretical explanation of this behaviour is that the series inductances and shunt capacitances form a low-pass filter which by the reduction of inductance has been brought to a characteristic impedance, analogous to that of a cable, of approximately 75 Ω . The cut-off frequency of this filter is of the order of 500 Mc/s so that at frequencies up to 100 Mc/s the attenuator at zero setting

behaves very much as a length of 75- Ω cable.

With the application of these principles attenuators were constructed using "Arrow," "Bulgin" and "N.S.F." toggle switches, and the type produced in small quantities is that illustrated in Fig. 6. The resistors used were supplied by special arrangement to be within ± 1 per cent of the required values and are high-stability components. Standard P.O. type connectors were used while the box was fabricated from sheet brass.

One of the units was sent to the National Physical

APPENDIX

A generator of impedance Z_s is connected by a cable of characteristic impedance Z_0 , and length l , to a termination consisting of a resistance Z_0 shunted by a capacitance C . If the generator impedance $Z_s = Z_0$ the output voltage e developed across the termination will be independent of l and the circuit has the simple equivalent form shown in Fig. A1.

We then have $\frac{e}{e_0} = \frac{1}{1 + j\omega C Z_0/2}$ and taking the modulus or "amplitude of e "

$$\left| \frac{e}{e_0} \right| = \frac{2}{\sqrt{4 + \omega^2 C^2 Z_0^2}}$$

If the generator impedance $Z_s = 0$ we have the equivalent circuit of Fig. A2.

The equivalent output impedance is reactive and the open-circuit voltage is transformed in the ratio $\sqrt{1 + y^2} : 1$

where $y = \tan \frac{2\pi l}{\lambda}$. The term $\frac{2\pi l}{\lambda}$ is called the electrical length of the cable and the wavelength in the cable is $\lambda = \frac{\lambda_0}{\kappa}$ where λ_0 is the wavelength in air and κ is the dielectric constant of the insulation. (For polythene $\kappa = 2.23$ and $\lambda \approx \frac{2\lambda_0}{3}$)

From the above circuit

$$\left| \frac{e}{e_0} \right| = \frac{\sqrt{1 + y^2}}{\sqrt{(1 - y Z_0 \omega C)^2 + y^2}}$$

When $y = 0$ ($l = \frac{n\lambda}{2}$) $\frac{e}{e_0} = 1$, and for a cable of length one metre this occurs at 0, 100, 200, 300 Mc/s etc. Note that $e = e_0$ at all frequencies if $l = 0$, and that $e = e_0$ for all l if $C = 0$.

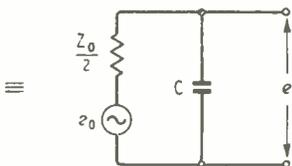
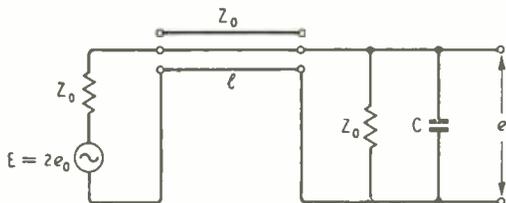


Fig. A1.


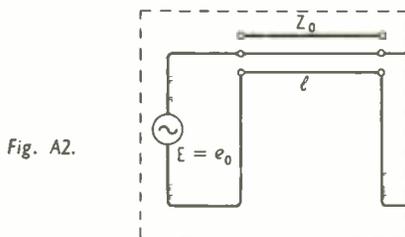


Fig. A2.

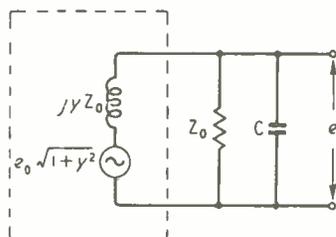

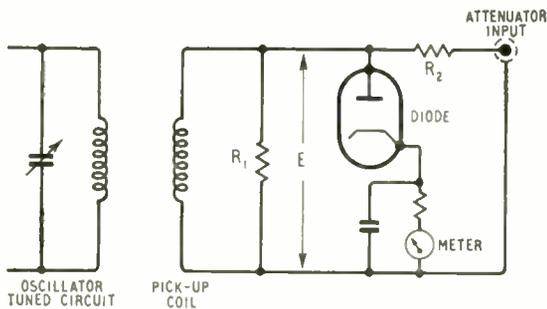


Fig. 7. Typical coupling circuit between oscillator and attenuator.

Laboratory for calibration at high frequencies and the results are summarized in Table III. The change in attenuation relative to the value measured at 1 Mc/s is given for various combinations of pads at frequencies of 25, 50, 75 and 100 Mc/s. At the higher frequencies the measurements were limited to a maximum attenuation of 50 db. Also the attenuation introduced by the presence of the attenuator at its zero setting was measured.

Measurement of Attenuator Input.—Consider the circuit coupling an oscillator to the input of the attenuator and in particular the arrangement in Fig. 7. Here a pick-up coil, which is lightly coupled to the oscillator, and is damped by resistance R_1 , develops a voltage across a diode voltmeter. It is normal practice

TABLE III

Pads in circuit	Nominal attenuation (db)	Attenuation in db relative to 1-Mc/s value at frequencies of :			
		25 Mc/s	50 Mc/s	75 Mc/s	100 Mc/s
1 × 10	10	0	0.05	0.025	0.05
1 + 2 + 2 + 5	10	0	0.05	0.10	0.125
5 × 10	50	0	0.10	0.25	0.10
1 + 2 + 2 + 5 + (4 × 10) . . .	50	-0.05	+0.075	0.3	0.2
All	80	-0.15	-0.125	—	—
"Zero level" insertion loss . .	0	0.15	0.25	0.45	0.65

to hold this voltage to a constant value at all frequencies, either by an operator who corrects errors shown on a meter by the adjustment of manual controls, or by a feedback network.

Whether the servo system is automatic or is completed by human agency it results in a constant voltage E being maintained across R_1 . At the attenuator input the terminals yield an open-circuit voltage E and a short-circuit current E/R_2 and by Thévenin's theorem must appear as a source of resistance R_2 . Thus to suit the attenuator described R_2 would be made 75 Ω . A low value of R_1 will minimize the adjustment necessary to compensate for changes of load presented by the attenuator, but too low a value will cause excessive loading of the oscillator circuit.

MULTIPLEX F.M. BROADCASTING

Two Programmes in a Standard Channel

With frequency modulation very much in the air as a result of the Television Advisory Committee's recent report on v.h.f. broadcasting, it is interesting to hear from America about a system of f.m. multiplexing whereby a standard 200-kc/s channel can be used for carrying two programmes simultaneously. It is the work of the late Maj. E. H. Armstrong, the pioneer of f.m. transmission, and J. Bose of Columbia University, and has been undergoing tests for several years at Maj. Armstrong's experimental f.m. station in New Jersey. The auxiliary channel is provided by a 27.5-kc/s sub-carrier, which frequency modulates the main carrier and is itself frequency modulated by the auxiliary programme.

Previous attempts have been made at f.m. multiplexing for broadcasting but have not been very successful, mainly because of cross-modulation between the main and auxiliary channels and the transfer of noise from one to the other. Armstrong and Bose have published claims to have overcome this trouble by arranging for the modulation processes of the two channels to be performed in separate parts of the transmission system, so that they are protected from each other. The phase-shift method of modulation is used, with frequency multipliers to increase the small deviation obtained from it to the required value. A crystal oscillator providing the drive is followed by a phase-shift modulator into which is fed the a.f. modulating signal of the main programme.

The resulting modulated carrier then passes through a chain of three frequency multipliers and interposed band-pass filters to a power amplifier and the aerial, where the final maximum deviation is about 50 kc/s. Between the second and third multipliers is inserted a second phase-shift modulator and here the 27.5-kc/s sub-carrier with its auxiliary programme is superimposed on the main carrier. The deviation produced by this sub-carrier is of the order of ± 20 kc/s, while its own deviation by the modulation is about ± 5 kc/s.

The phase-shift modulation system is also used within the auxiliary channel for impressing the audio input on the sub-carrier. To obtain the necessary deviation, however, the frequency multipliers have to increase the modulated sub-carrier to something like 11 Mc/s, so a frequency converter is used to bring this down to the required 27.5 kc/s.

Demonstrations of the system have been given with different programmes on the two channels, and in spite of the fact that the modulation in the auxiliary channel is limited to 7.5 kc/s, compared with the main channel's 15 kc/s, listeners at the receiving end have reported "no audible difference in quality between the two programmes." Other demonstrations have been given with the two channels carrying the same programme; with binaural audio inputs; and with the receiving loudspeaker listening to the silent auxiliary channel to show the absence of cross-modulation from the main channel.

Vibratory Gyroscope

Electronic Indicating System

THE familiar tuning-fork, once used for controlling the frequency of wireless transmitters, now figures as the stabilizing element in a new kind of gyroscope devised by the Sperry company. It performs the same function as the spinning flywheel of an ordinary gyroscope, but in rather a different way. Actually it operates on much the same principle as the physiological balancing mechanism of the common housefly, which has club-shaped vibrating rods situated just behind the wings. The main advantage of this type of instrument is, of course, that it has no rotating parts or bearings to cause trouble. In addition, its sensitivity to different rates of turn is claimed to cover a very wide range—from as slow as the earth's rotation to as fast as 100 r.p.m.

In operation the two prongs of the tuning fork (Fig. 1) can be regarded as segments of two ordinary gyro flywheels pivoted at somewhere near the heel of the fork. Since the prongs are vibrating towards and away from each other, the imaginary flywheels would be continually reversing their direction of rotation in a similar manner, one going clockwise to the other's anti-clockwise. If the "flywheels" were rotating continuously as in an ordinary gyroscope they would provide a steady reaction against any external force that tried to turn the tuning fork about its vertical centre line. Since, however, their motion is actually alternating, the reaction to an applied turning force is also alternating, and it appears as a vibratory twisting

motion in the shaft of the fork. The greater the rate of turn applied to the fork the greater the amplitude of this torsional vibration. As for the direction of turn, clockwise or anti-clockwise, this is indicated by the phase of the torsional vibration. With clockwise turning, an inward swing of the vibrating prongs causes the torsion blade to approach the left-hand pick-up coil, while with anti-clockwise turning an inward swing sends it

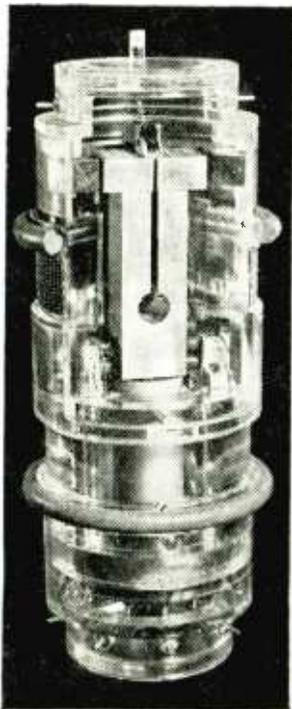


Fig. 2. Cut-away model showing the actual form of the instrument. Underneath the prongs is the tuned torsion shaft, and at the base of this are the torsion pick-up coils.

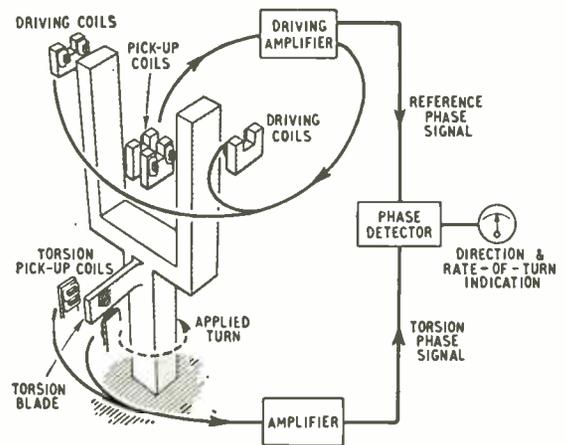


Fig. 1. Essentials of the experimental vibratory gyroscope.

towards the right-hand coil. In the actual instrument the shaft of the fork is mechanically tuned so that it resonates torsionally at the natural vibration frequency.

As can be seen from the diagram, the prongs of the fork are kept in vibration (actually at 1,850 c/s) by a feedback arrangement comprising driving coils, pick-up coils and an amplifier. The resultant torsional vibration is detected by a blade on the shaft and two more pick-up coils. The electrical signal from these is amplified and applied to a phase detector, which also has an input signal from the vibrating prongs to provide a reference phase. Thus the phase detector gives the phase of the torsional vibration relative to the prong vibration and hence the direction of turn, as already explained. Its output is in the form of a d.c. signal which indicates by its polarity the direction of turn and by its amplitude the rate of turn. These indications are shown by appropriate pointer movements on a centre-zero meter.

POWER TRANSISTOR

ACCORDING to a description in the December, 1953, *Electronics* a 20-watt transistor, which exceeds the normal power level by about 100 times, is being produced by the Minneapolis-Honeywell Regulator Company. It is a diffused-junction germanium transistor hermetically sealed in glass and metal and having a screw mounting for direct connection to a metal chassis, or other support, which will act as a conduction cooling medium.

For the present they are being used in aircraft fuel gauges only but some may become available for commercial use later. No mention is made of their frequency characteristics but a 20-watt transistor excites the imagination and conjures up visions of economical and compact power amplifiers.


Ionosphere Review—1953

A Correction

THE two graphs on page 67 in last month's issue were unfortunately transposed. The lower graph is Fig. 1 (twelve-month running averages of sunspot numbers, etc.), while the upper is Fig. 2 (monthly mean sunspot numbers, etc.).

Mobile Flight Simulator

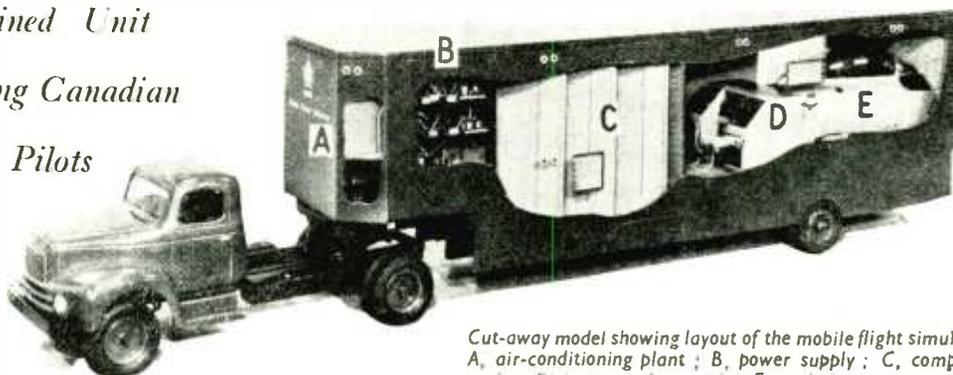*Self-contained Unit
for Training Canadian
"Sabre" Pilots*




Cut-away model showing layout of the mobile flight simulator. A, air-conditioning plant; B, power supply; C, computer racks; D, instructor's console; E, cockpit.

THE first of the ten flight simulators ordered by the Canadian Department of Defence Production was handed over at a ceremony in London recently by the designers and makers, Redifon, Ltd., Broomhill Road, London, S.W.18.

This equipment is for the training of "Sabre" jet fighter pilots, and can reproduce all the effects of flight on instrument readings and the "feel" of the controls, with appropriate sound effects. In everything but the accelerations resulting from change of course and speed the pilot feels that he is airborne, and can be set problems in navigation, artificial emergencies due to such causes as icing, engine defects, etc., any of which might have serious consequences for an inexperienced trainee if he were in actual flight. The instructor can watch the pupil's reactions and correct errors in safety, and, last but not least, at low cost. Taking everything into account the simulator costs about £3 per hour to run, whereas the overall cost of flight training would be £50 per hour. Not the least of the advantages of flight simulators is the saving of training time which might otherwise be lost through bad flying weather. They can also be used to re-examine qualified pilots periodically, and tests can be devised which are far more searching

On the right are shown recorders for plotting simulated flight path. These also generate long-range d.f. signals.

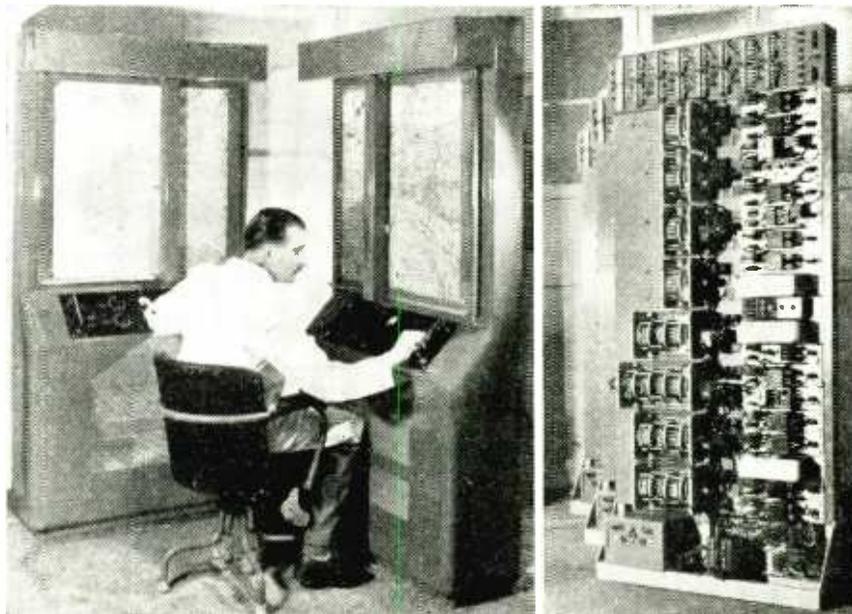One of the computer-amplifier racks is shown in the photograph on the extreme right. Six of these are mounted "herring bone" fashion in the middle section of the van.




Manufacturers' Products

NEW EQUIPMENT AND ACCESSORIES FOR RADIO AND ELECTRONICS

Tuner Unit

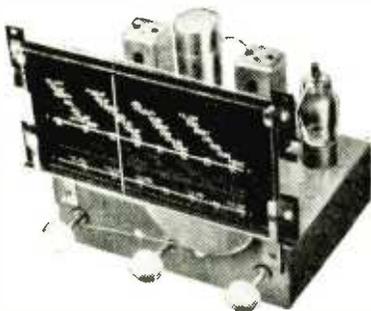THE detector circuit in the "Elpico" Model RF/716 superheterodyne tuner unit makes use of a double triode, the first half of which



"Elpico" Model RF/716 tuner unit.

functions as a diode and the second as a cathode follower. By this means capacitive couplings and shunts have been eliminated and the d.c. and a.c. load conditions are the same. It is claimed that the circuit will accept, without adding distortion, the maximum modulation level used by the B.B.C. Diodes for a.g.c. are combined with the pentode i.f. valve.

Long, medium and short wavelengths are covered and the unit, which is made by Lee Products, 63, Great Eastern Street, London, E.C.2, costs £14 14s.

Sapphire Needles

THE installation of automatic grinding and polishing machines has enabled the makers of "Windsor" sapphire-tipped needles to produce a range retailing at 2s 6d each. These are all of 0.0025in tip radius for 78 r.p.m. records and are available in standard diameter or "midget" shanks, or in the "trailer" type for use with older heavy magnetic pickups.

The makers, Sapphire Bearings, Ltd., 16, Catherine Place, London, S.W.1, state that every needle is inspected by shadowgraph for sphericity and radius of point, and surface polish.

Miniature Trimmers

COMPRESSION capacitors of the "postage stamp" variety for circuit trimming are now obtainable from the British Distributing Company, 591, Green Lanes, London, N.8, in capacitances ranging from 5/60 pF (min and max) to 150/400 pF. They are assembled on ceramic bases designed for use separately or in banks

of any number and mixture of capacitances. The dielectric is mica. Individual units measure $\frac{1}{4} \times \frac{1}{8} \times \frac{1}{8}$ in and the test voltage is 300 d.c.

Germanium Crystal Coil

AMONG the small r.f. coils made by The Teletron Company, 266, Nightingale Road, Edmonton, London, N.9, is one designed especially for a germanium crystal receiver. Described as the Type HAX it has three separate windings on a 0.45-in moulded former with an adjustable dust-iron core. The tuned winding is Litz-wound and covers the medium broadcast waveband with a 0.0003-mfd variable capacitor.

The other windings are for aerial and crystal respectively, the couplings being set for optimum performance with an average aerial. The coil costs 3s.

Potted Transformers

A HARD-SETTING resin compound is used for casing a new range of miniature audio transformers introduced by John Bell and Croyden, 117, High Street, Oxford. With this type of finish fixing screws can be moulded into the block where required and become an integral part of the component. Rigid tags or pins can replace loose connecting wires and be inserted where required for particular purposes. Non-standard shapes and sizes are more easily provided by potting than by most other types of finish.

Electrostatic "Tweeter"

THE introduction of new materials and methods has brought about a revival of interest in the electrostatic loudspeaker, particularly in Germany. The two outstanding advantages of this type are the simplicity of application (it is connected across the output transformer primary with a simple filter to keep out low frequencies), and the virtual absence of directional properties through 180 degrees in the horizontal plane.

One example, the Körting, is now available in this country through

Körting electrostatic high-frequency loudspeaker.




E. D. Parchment, 69, Clapham Road, London, S.W.9. It consists of a curved perforated back-plate with a stretched diaphragm of plastic film, coated on the outside with a metallic film. The whole is housed in a moulded plastic frame measuring approximately $4\frac{1}{4}$ in \times $3\frac{1}{4}$ in \times $\frac{1}{2}$ in.

The normal polarizing voltage is 250 (test 1,000V) and the capacitance 0.001 μ F. The frequency response, according to the makers' published curve, is 7,000-15,000 c/s, \pm 5db.

Transistors

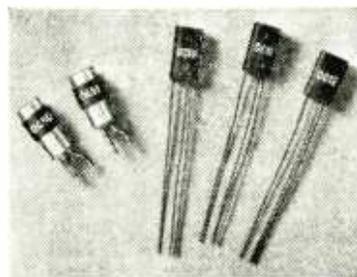A RANGE of transistors is now available from Mullard to equipment designers who wish to carry out experimental work. These are two-point contact types, the OC50 and



New transistors from Mullard.

OC51, and three junction types, the OC10, OC11 and OC12.

The point-contact types are readily available at a price comparable with that of mains subminiature valves. Their point spacings have been made different so that the two transistors have markedly different characteristics. The OC51 has a better high frequency characteristic than the OC50. The OC50, however, operates more satisfactorily than the OC51 in the "collector bottomed" condition.

The junction transistors, OC10, OC11 and OC12 are designed for economy in power supplies and, in

both amplifier and oscillator circuits, they will operate from h.t. supplies as low as 1.5 volts, with current consumptions of a similarly low order. Under suitable conditions they will work with h.t. supplies of only a fraction of a volt.

The OC11 is a general-purpose amplifier which, in an earthed emitter circuit, gives a current amplification factor of 17. Under similar conditions, the OC12 gives a current amplification factor of 30, and is intended primarily as an output transistor, although it can also be used in amplifier circuits. The OC10 is a low-noise version of the OC11 and is intended for use in the early stages of high-gain amplifiers.

Mullard's address is Century House, Shaftesbury Avenue, London, W.C.2.

Nickel for Valves

TWO new grades of nickel in wrought form are now available for valve manufacturers from Henry Wiggin & Co., Birmingham, 16. Both grades have a minimum nickel content of 99.5 per cent and are low in the volatile elements such as magnesium. Grade H.P.A., which has a low silicon content (0.03 per cent max.), is useful for the cathodes of valves which must have a very long life with low emission current. In Grade H.P.B. the silicon content is 0.15 to 0.25 per cent with the object of increasing activation and emission. The makers warn that care must be used with H.P.B. nickel, as under certain conditions high interface impedances may build up between the cathode sleeve and the coating material.


Element	H.P.A. (per cent)	H.P.B. (per cent)
C	0.10 max	0.10 max
Cu	0.04 max	0.04 max
Fe	0.05 max	0.05-1.0
Mn	0.02 max	0.10 max
Mg	0.01 max	0.01 max
Si	0.03 max	0.15-0.25
Al	0.01-0.05	0.02 max
S	0.005 max	0.005 max
Ni		
and Co	99.5 min	99.5 min

Miniature Attenuator

THE illustration shows a miniature stud-type attenuator no larger than a two-shilling piece (1½ in) and measuring 1½ in in depth behind the panel.

It is described as the Type M and is intended primarily for audio applications in portable equipment and where space is at a premium. In certain circumstances it could be employed in medium- or carrier-frequency circuits up to about 4 Mc/s.

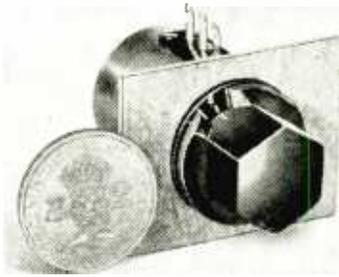Painton ¼-W high-stability carbon resistors are fitted and the attenuator can be arranged as either a 10-step twin-arm network (bridge T) or a



Painton miniature stud attenuator, Type M.

20-step single-arm network (unbalanced potentiometer). Alternatively, it can be arranged as a fader control.

The knob and dial are so designed that only the portion of the network in circuit is indicated by the figures uncovered by the skirt of the knob.


The makers are Painton & Co., Ltd., Kingsthorpe, Northampton.

Hearing Aid with Transistor

CONSIDERABLE saving in h.t. battery consumption has been effected in the Amplivox Model J2 hearing aid by the use of a junction transistor in the output stage. Low-consumption valves are used in the voltage-amplifying stages, but the greater part of the normal h.t. current is saved by using the transistor; actually a reduction from 0.35mA in the all-valve Model J to 0.04mA in the J2, or a ratio of 120/1,000 hours life. A single Mallory mercury cell (1.3V) is used for 1.t. and here the economy is useful, but less spectacular, 20mA to 12.5mA or 50 to 80 hours. The air-to-air gain of the J2 is 47db with E9L high-sensitivity earphone, compared with 53db in the all-valve J hearing aid.

The price of the J2 is £44 2s and the makers are Amplivox, Ltd., 2, Bentinck Street, London, W.1.

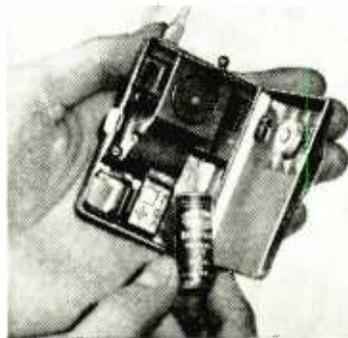Amplivox Model J2 hearing aid with junction transistor output stage.



SOUND

Versatility in

In TRIX Sound Equipment, versatility is allied to quality. Quality of design, of workmanship and materials, outstanding quality of performance. TRIX continues to lead the way in the development of sound reproduction. Our range of standard units is the widest available, for we place at your disposal the complete service in sound



Model RE48. A heavy duty reflex type weather-proof horn speaker with exceptional range and performance. Very suitable for all public address work.

The NEW Model T.635 Amplifier



This outstanding 30 watt high fidelity amplifier provides all the features needed to cover the large majority of Sound installations. It is designed for A.C. operation and can also be used on batteries with a 6 volt adaptor unit. Inputs for 2 Microphones, and one Gramophone pickup, with individual mixing controls. Separate controls for Bass and Treble boost.

The amplifier is a 4 stage, high-gain type suitable for use with ribbon microphones, without additional pre-amplification. Special anti-microphonic features incorporated. High and low impedance inputs.

Push-pull output circuit with inverse feed-back. High and low impedance tapings, including 100 volt line matching.

SERVICE IN SOUND BY



The TRIX ELECTRICAL CO. LTD.
1-5 MAPLE PLACE, TOTTENHAM CT. ROAD,
LONDON, W.1 Phone: MUSeum 5817
Telegrams and Cables: TRIXADIO, WESDO, LONDON

RANDOM RADIATIONS

By "DIALLIST"

At Long Last!

UNLESS ANYTHING so entirely monstrous as the shelving of the Television Advisory Committee's all-but-unanimous report should take place, f.m. is at long last recognized as the victor in the great (and far too protracted) controversy over the best modulation system for v.h.f. broadcasting. No one who had been receiving the Wrotham broadcasts, as no doubt all members of the technical sub-committee had, could have failed to realize the vast superiority of frequency modulation as a defence against motor-car-ignition interference, which is the only really important kind of interference on the v.h. frequencies. Given a receiver so arranged that a quick switch-over from one system of modulation to another can be made, two or three short periods of listening should convince most people that a.m. with limiter is a bad second to f.m., with plain a.m. very much an also-ran. Since it has been shown that a nation-wide f.m. service could be installed at little more than one-third the cost of a similar a.m. service, and that the latter would call for 44 per cent more stations, with a power output more than $3\frac{1}{2}$ times as great and costing $2\frac{1}{2}$ times as much to run, I can't help feeling very much in sympathy with the Committee's majority report.

Shaggy Dog Story

UNLIKE MOST of the others, this Shaggy Dog Story is true, cross my heart; see that wet, see that dry. Hailing me as I was passing her house the other day, my friend Mrs. X wafted me into her drawing room. "Have you ever heard," she asked, "of a dog that was radio-active or something?"

??????

"Well, I think Wuffles must be." Wuffles is an Old English Bobtail. "Yesterday afternoon, when the children and I were watching Muffin, he just gave himself a shake over there and the television set immediately went mad."

"What happened?"

"First, the picture shrank to half-size; then it blacked right out. I tried twiddling knobs and things,

but that didn't do any good. There were so many flashes and crackles that I switched off and 'phoned the serviceman. He took the set away this morning, saying that its innards looked as if it had been struck by lightning."

I asked whether by any chance Wuffles was wet when he performed that devastating shake. He was! He'd been brought in at the back door by her husband, after a walk in the rain, and had escaped and made his way into the drawing room before he could be dried off. Most of him was behind the television set when he shook himself. One could picture large drops of water being propelled through the louvres while a mist of droplets was borne in by convection currents. Wet dogs, it seems, should be kept far from TV receivers; the shaggier the farther.

A C.R.T. Weak Spot

A CAUSE of television c.r. tube breakdown which seems to be growing increasingly common is the development of a "short" between heater and cathode. The fault is often intermittent—and that kind is the most exasperating of all. It can be cleared in suitable cases by the use of an isolating transformer; and

the fact that special transformers are readily available shows that these shorts are not exactly rarities. When one considers the cost, including purchase tax and labour charges, of replacing one of the large tubes so popular today, one can't help feeling that a very special effort should be made to overcome any known weaknesses in them. Here is one which calls urgently for attention. For it is clearly not always possible to use an isolating transformer; and even when it is possible there are dealers here and there who can't, or won't, undertake the job.

But We Liked it

IF YOU WANT some fun, get some friends who are old hands at wireless to ransack their junk boxes and lumber rooms and join with them in building a receiver as nearly as possible like those used to reproduce broadcasting in its early days in this country. Then, having made the set, you may spend entertaining hours in listening to its performances and in wondering how people in those days could possibly have thought them enduring, let alone beautiful. Some friends and I did just that a year or two ago. We were able between us to bring together a fine collection of period-piece components. My own contribution was three typical triodes, which had actually had very little use. The triode was in those days the most complex valve available; and when I say typical I mean that r_{ii} was of the order of



"WIRELESS WORLD" PUBLICATIONS

	Net Price	By Post
GUIDE TO BROADCASTING STATIONS. Compiled by "Wireless World," 7th Edition ...	2/-	2/2
INTRODUCTION TO VALVES. R. W. Hallows, M.A. Cantab., M.I.E.E., and H. K. Milward, B.Sc., Lond. A.M.I.E.E. ...	8/6	8/10
TELEVISION ENGINEERING: Principles and Practice. VOLUME ONE: Fundamentals, Camera Tubes, Television Optics, Electron Optics. A. B.B.C. Engineering Training Manual. S. W. Amos, B.Sc. (Hons.), A.M.I.E.E. and D. C. Birkinshaw, M.B.E., M.A., M.I.E.E., in collaboration with J. L. Bliss, A.M.I.E.E. ...	30/-	30/8
WIRELESS WORLD TELEVISION RECEIVER MODEL II: Complete constructional details with notes on modernizing the original design ...	3/6	3/9
F. M. FEEDER UNIT. S. W. Amos, B.Sc. (Hons.), A.M.I.E.E. and G. G. Johnstone, B.Sc. (Hons.) ...	2/-	2/2
RADIO INTERFERENCE SUPPRESSION as Applied to Radio and Television Reception. G. L. Stephens, A.M.I.E.E. ...	10/6	10/11
SOUND RECORDING AND REPRODUCTION. A B.B.C. Engineering Training Manual. J. W. Godfrey and S. W. Amos, B.Sc. (Hons.), A.M.I.E.E. ...	30/-	30/8
ADVANCED THEORY OF WAVEGUIDES. L. Lewin ...	30/-	30/7
FOUNDATIONS OF WIRELESS. M. G. Scroggie, B.Sc., M.I.E.E. 5th Edition ...	12/6	13/-
TELEVISION RECEIVING EQUIPMENT. W. T. Cocking, M.I.E.E. 3rd Edition ...	18/-	18/8

A complete list of books is available on application.

Obtainable from all leading booksellers or from

ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1.

40,000Ω and g_m round about 0.225 mA/V. One man proudly produced a loudspeaker famous in its day for the quality of its reproduction: an Amplion "Lion," with a conical metal horn, about 12in long and 4in in diameter at the output end, fixed to the case of a rather large telephone receiver. Others contributed an assortment of coils, transformers, condensers and resistances (to call the last two capacitors and resistors would be an anachronism) and we were all set to go.

Loud and Clear!

The circuit, selected from a handbook of the period, consisted of a tuned-grid, tuned-anode r.f. amplifier, held down by the application of positive grid bias *via* a potentiometer; a leaky-grid detector, with reaction of the variably coupled coil type; and an a.f. stage, coupled to the detector by a 5:1 transformer and working with about 2 volts negative grid bias, which was as much as it would stand with the historically correct 90-V h.t. But, younger readers may exclaim, what about the output stage? Dear younger readers, that a.f. stage *was* the output stage! The small power valve didn't come along until broadcasting had been going on for some time. The same Marconi "R," or Mullard "Ora" or Cossor "Tin-hat" valves had to serve in each and every stage of early broadcast receivers. Also included in our collection were several numbers of the popular radio magazines of the early 1920s. These confirmed our recollection that the two qualities then most esteemed in a broadcast receiver were the number of stations that it would "get" and the volume with which it would bring in the local station: "Even at 50 yards from the speaker," wrote one enthusiast in the correspondence columns, "every note is clear and free from all distortion!" Bearing in mind the conditions prevailing in that output stage—and indeed in all those stages—you may feel that this writer had been a little over-enthusiastic. Make up a set on the lines suggested and you'd wonder how anyone could have endured its output for a moment, even with the volume turned right down. Will my successor in the *Wireless World* of thirty years hence, I wonder, make similar experiments by reconstituting a 1954 wireless or television set? And, if he does, will he marvel in the same way at the crudities which our eyes and ears must have accepted without protest?

INTRODUCING THE NEW

SILVER-DIAL

RANGE OF CONTROL-KNOBS



A NEW Range of Instrument Knobs and Dials. Manufactured in the finest-grade polished Bakelite, with frosted aluminium "Silver-Dial" dials.

List No.	Item	Dimensions, etc.
K.400	Knob	$1\frac{1}{2}$ " (23.8 mm.) ϕ \times $\frac{3}{8}$ " (15.9 mm.) high
K.410	Dial*	$1\frac{1}{2}$ " (38.1 mm.) ϕ \times 21 S.W.G., engraved 0-10 over 270°
K.410/P	Dial*	ditto, not engraved


* Rivets to Knob; we will fit and rivet, if requested.



List No.	Item	Dimensions, etc.
K.401	Knob	$1\frac{1}{2}$ " (29.4 mm.) ϕ \times $\frac{1}{4}$ " (17.5 mm.) high
K.405	Skirt	$1\frac{1}{2}$ " (38.1 mm.) ϕ \times $\frac{5}{16}$ " (5.9 mm.) thick
K.411	Dial*	2" (50.8 mm.) ϕ \times 21 S.W.G., engraved 0-10 over 270°
K.411/P	Dial	ditto, not engraved



List No.	Item	Dimensions, etc.
K.402	Knob	$1\frac{1}{2}$ " (41.3 mm.) ϕ \times $\frac{3}{16}$ " (19.9 mm.) high
K.406	Skirt	$2\frac{1}{4}$ " (52.4 mm.) ϕ \times $\frac{3}{16}$ " (5.9 mm.) thick
K.412	Dial*	$2\frac{1}{2}$ " (69.9 mm.) ϕ \times 21 S.W.G., engraved 0-100 over 180°
K.412/P	Dial	ditto, not engraved

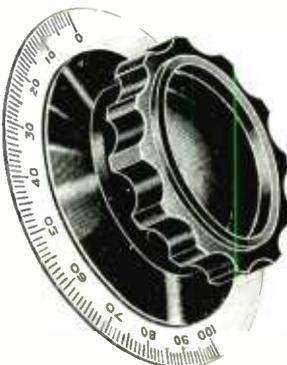

List No.	Item	Dimensions, etc.
K.403	Knob	2 $\frac{3}{4}$ " (60.3 mm.) ϕ \times $\frac{3}{16}$ " (24.6 mm.) high
K.407	Skirt	3" (76.2 mm.) ϕ \times $\frac{3}{16}$ " (5.9 mm.) thick
K.413	Dial*	4" (101.6 mm.) ϕ \times 21 S.W.G., engraved 0-100 over 180°
K.413/P	Dial	ditto, not engraved

Further details available in the NEW 114 page Catalogue. Price 1/- post free. Ref. 192/WW.



MANUFACTURERS OF RADIO AND ELECTRONIC COMPONENTS

A. F. BULGIN & CO. LTD., BYE-PASS RD., BARKING, ESSEX

Telephone: RIPPleway 3474 (5 lines)

Alice in Solidconductorland

"A current of electricity from A to B consists of electrons moving from B to A and/or positive ions moving from A to B. If the current is flowing in solid material, the ions are the fixed material itself, so cannot move and the current consists wholly of electrons."

THE ABOVE definition of an electric current in a solid conductor, which is quoted from the article in the January issue of *W.W.* dealing with the speed of electricity is accurate beyond the shadow of a doubt. It does, however, have a seeming oddness if considered carefully and my warped mind has sometimes wondered if this is not due to the fact that in pre-electronic days an unlucky guess was made about the direction of electric current flow and we still cling stubbornly to it.

"What is going on?" said Alice to the Red Duchess as she pointed to a rather disorderly mob of soldiers streaming out of one of the castle towers which had a big B over the gate and entering another tower labelled A. "Oh," said the Duchess, "just troop movements; I have decided to evacuate tower A and house all the troops in tower B." "But," protested Alice, "They're not obeying your orders; they are evacuating B and marching over to A." "Nonsense, child," said the Duchess following the direction of Alice's pointing finger. "What you see are merely soldiers; the troops which are moving in the opposite direction are not really moving at all."

"Then do troop movements from tower A to tower B consist of soldiers marching from B to A and nothing moving from A to B?" asked Alice. "Certainly" said the Duchess. "What a strange thing" commented Alice. "Wouldn't it make things easier to call the soldiers troops, and then troops and soldiers would always be marching in the same direction because they would, in fact, be one and the same thing?"

"Maybe to your simple mind it would make things easier" said the Duchess with some asperity, "but you have no respect for tradition; a century or more ago when troops were first discovered my great-grand-

father, who, being blind, mistook the directions in which they were marching and gave orders that the castle entrances were to be labelled exits and vice-versa. As everybody else was blind too" continued the Duchess, "it didn't matter much and the troops didn't care anyway as they knew the way in and the way out by the same sort of natural law or homing instinct which enables a male hippopotamus, even when he is blindfolded, to distinguish a female hippopotamus from another male hippopotamus."

"But nobody is blind now" protested Alice. "Of course not, child," said the Duchess chidingly, "but out of respect for my great-grandfather's



"What is going on?"

memory we still like to pretend he was right even though it gets us into all sorts of difficulties, so when soldiers are moving from B to A we always pretend that troops are moving from A to B even though troops don't really move; at any rate not in Solidconductorland in which we live.

"Well" said Alice "I call it silly; we have nothing like it in our country." "Rubbish" snapped the Duchess beckoning to her executioner, "What about your summer time? What is obviously midday you pretend it is one hour past midday although everybody knows full well that it really isn't." "Off with her head," she shouted to the executioner.

A Unique Opportunity

NOBODY SEEMS to have pointed out what a magnificent opportunity the proposed introduction of competitive television would offer for

starting the higher definition of which we have heard so much from those who criticize the B.B.C.'s 405-line system. Now at last a unique opportunity arises for confounding these critics or justifying their views.


Before any competitive service could start we would all, in any case, have to buy adaptors or new sets if we want to receive the programmes. Those who could not or would not go to the expense of this would be no worse off than they are at present, for they would still be able to receive the B.B.C. programmes. But if people were willing to go to the expense of buying an adaptor or a new set to receive the alternative programmes, then why not give them full value for their money in the shape of a picture of the highest definition which modern technique can provide?

Naturally this would be very hard lines on the B.B.C.—about 625 of them, I suppose—and the Corporation would be torn between its desire to radiate a picture of equally high definition and the necessity of keeping faith with owners of existing sets who didn't want to spend money on new receiving gear. But I feel that owners of existing sets would be so jealous of the technically better picture of "competitive" viewers that they would soon alter their views and their viewing apparatus, thus freeing the B.B.C. from its obligations and enabling it to compete on equal technical terms with, or even to go one better than, its competitor by radiating stereoscopic TV, to say nothing of colour.

No Suppressors Needed

AT THIS TIME of the year the big toy shops in all our large towns usually make an intensive drive to sell model electrically-operated railways, which they show in operation. These are prolific sources of interference to neighbouring TV sets as, so far as I can see, no attempt is made to fit suppressors.

It may be argued, of course, that these trains are not being demonstrated in normal television hours, but one cannot expect the average modern child to discontinue the use of his model railway when TV starts. At least, such was my opinion until recently, when I was discussing the problem with a specimen of the 1963 National Service class. To my surprise he pointed out with withering contempt that he and others of his age group were the backbone of the B.B.C.'s TV audience and would not fob their own nest. I felt completely silenced and suppressed.

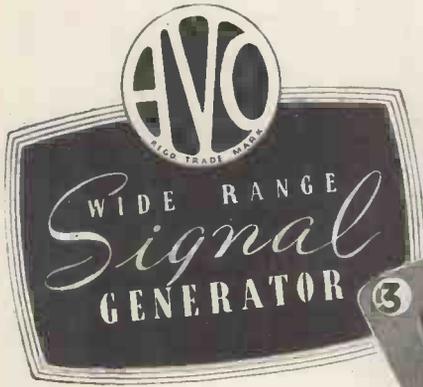

An inexpensive yet precision instrument designed especially to meet the exacting needs of the modern service engineer and laboratory technician. With six frequency ranges covering 50 Kc/s. to 80 Mc/s., its accuracy is better than $\pm 1\%$ of the scale reading.

- | | |
|-------------------|-------------------|
| 50Kc/s.-150Kc/s. | 1.5Mc/s.-5.5Mc/s. |
| 150Kc/s.-500Kc/s. | 5.5Mc/s.-20Mc/s. |
| 500Kc/s.-1.5Mc/s. | 20Mc/s.-80Mc/s. |

Scale sub-divisions provide more than adequate discrimination for use in television circuits. Note the starred features below, which combine to maintain a minimum signal of less than $1\mu\text{V}$ up to 20 Mc/s. and less than $3\mu\text{V}$ between 20 Mc/s. and 80 Mc/s.

- ★ **OUTPUT** 1
Co-axial socket for attenuated output. Force socket located totally within H.F. compartment.
- MAINS TRANSFORMER** 2
Marked tagboard for inputs of 100-130 V. and 200-260 V., A.C. 50/60 c/s.
- ★ **H.F. COMPARTMENT and CHASSIS** 3
Large number of fixing holes for H.F. compartment cover ensures excellent electrical bonding and good screening.
- FUSE** 4
Easily accessible when replacement is necessary.
- VALVES** 5
Standard types run at a rating to ensure long life.
- TURRET COIL SWITCHING** 6
Standard "AVO" practice.
- ★ **ATTENUATOR SYSTEM** 7
Employs close tolerance, high stability midget carbon resistors, low reactance rotary potentiometer modified for H.F. operation with carefully designed screening.

- Other features include:
- ILLUMINATED SPOT RANGE SELECTOR**
Gives rapid identification of operational band with intensified lighting round precise frequency. Fine hair line gives close discrimination, particularly on high frequencies.
 - STOPS**
Separate stops prevent turning of dial with respect to condenser.
 - ★ **MAINS FILTER SYSTEM**
This is screened from main electrical assembly.
 - BUSHING PLATES**
Provide additional rigidity for rotary controls.
 - SLOW MOTION DRIVE**
Substantially free from backlash.

MAINS MODEL 100—130 V. and 200—260 V. A.C., 50—60 c/s. £30
OR BATTERY MODEL

Sole Proprietors and Manufacturers:

THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.

WINDER HOUSE · DOUGLAS STREET · LONDON S.W.1 Telephone VICTORIA 3404-9



S. G. 2

Come Again



Radio - Electronic Men!

Just as you have been coming since 1945 to the IRE National Convention and Radio Engineering Show — coming by the thousands, 35,642 in '53 — so come again to see and hear all that is new in the engineering advances of your industry.

▲ Fifty-four in '54!

— 243 scientific and engineering papers will be presented, skillfully grouped by related interests into 54 technical sessions. More than half these sessions are organized by IRE Professional Groups, thus making the IRE National a federation of 21 conferences in one. The whole provides a practical summary of radio-electronic progress.


▲ **600 Exhibitors "spotlight the new!"** — A mile and a half of exhibits line the avenues of this show, intriguingly named for the elements of radio — such as "Instruments," "Components," "Airborne," "Radar," "Transistor," "Audio," "Microwave," etc., filling the four acres of the great Kingsbridge Armory to capacity. An expanding radio industry shows why it is growing by proving how engineering research pays out in new products. The exhibits themselves are an education, condensed to one place — reviewed in four days.

▲ Kingsbridge is the solution!

Only the combined facilities of the Waldorf-Astoria Hotel, plus the three great halls in the Kingsbridge Armory, seating 906, 720, and 500 respectively, are able to keep pace with the increased technical papers program of the IRE Convention. The show had to move because the U. S. Treasury took over Grand Central Palace. The immense Kingsbridge Armory, connected to the very satisfactory Lexington Avenue Hotel area by direct express subway, serves well to expand the already outgrown exhibit facilities of the Palace and pro-

vide space for 200 new firms to exhibit, as well as seat greater audiences at the high-interest sessions. In addition to the subways, free busses leave the Waldorf every ten minutes in which you may travel in the congenial company of fellow engineers, direct to Kingsbridge.

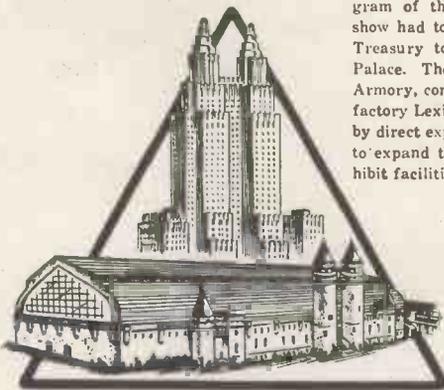▲ **Admission by registration only!** Registration serves for the four day period. It is \$1. for IRE members, \$3. for non-members, covering sessions and exhibits. Social events priced separately




Waldorf-Astoria and Kingsbridge Armory

March 22-25, 1954

**The IRE National Convention
and
Radio Engineering Show**
THE INSTITUTE OF RADIO ENGINEERS
1 East 79th Street, New York City

EUROPEAN VISITORS — are invited to write immediately to Mr. William C. Copp, Advertising Manager, 1475 Broadway, New York 36, New York, U.S.A. giving your arrival dates and hotel requirements so that we may render you preferred service in obtaining accommodations.

TESTED TO SPECIFIED EXTREMES

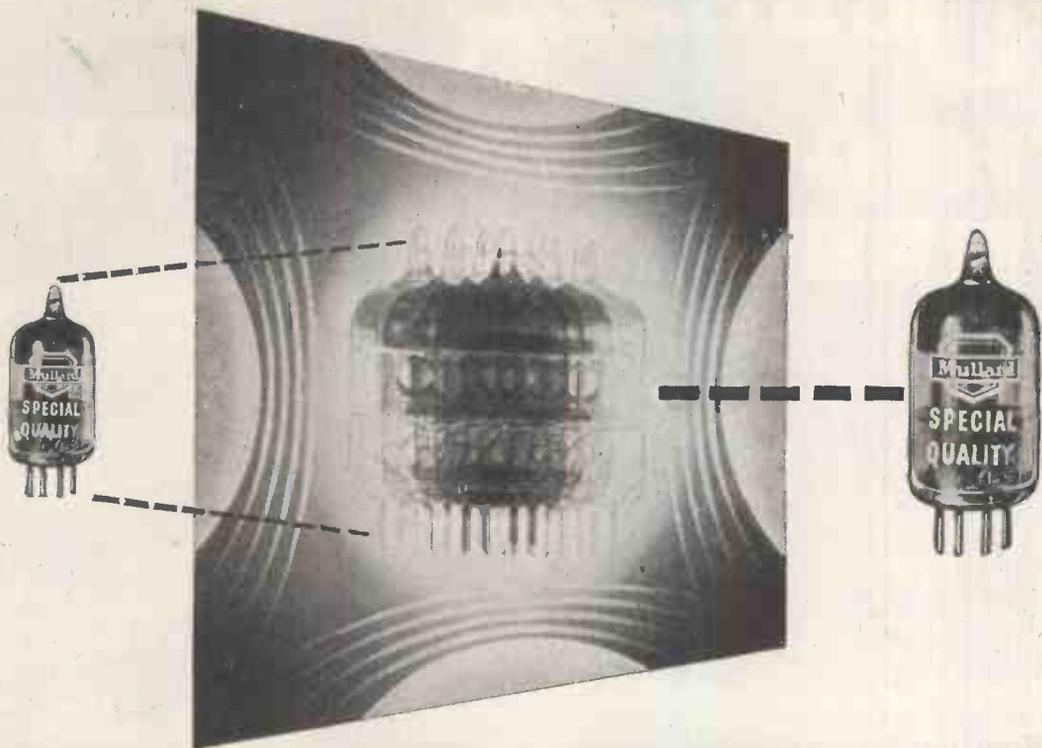

SHOCK • VIBRATION FATIGUE • MECHANICAL RESONANCE GLASS STRAIN • RELIABLE LIFE

New production methods and exhaustive tests assure users of Mullard Special Quality Valves of the definite standard of reliability laid down in Ministry of Supply (Air) Specifications.

Large-scale production of valves which are capable of withstanding such arduous conditions of shock and vibration presents obvious difficulties. These problems have been vigorously investigated over the past five years by Mullard who have now evolved techniques which make Special Quality Valves an economic reality for a wide variety of electronic equipment.

The first types in a comprehensive Mullard range are now generally available and are listed below. Details of the availability of types at present under advanced development will be announced soon.

Mullard Special Quality Type No.	Description	Electrical Equivalent		
		Mullard	American	British Services
M8079	Double Diode with separate cathodes	EB91	6AL5	CV140
M8081	Double Triode for use as R.F. amplifier or oscillator	ECC91	6J6	CV858
M8082	Output Pentode	EL91	—	CV136
M8083	High-slope R.F. Pentode	EF91	—	CV138
M8100	Low-noise high-slope R.F. Pentode	EF95	6AK5	CV850

Mullard
SPECIAL  **QUALITY**
VALVES
TESTED TO SPECIFIED EXTREMES


DUBILIER

HIGH STABILITY RESISTORS

Some outstanding features :

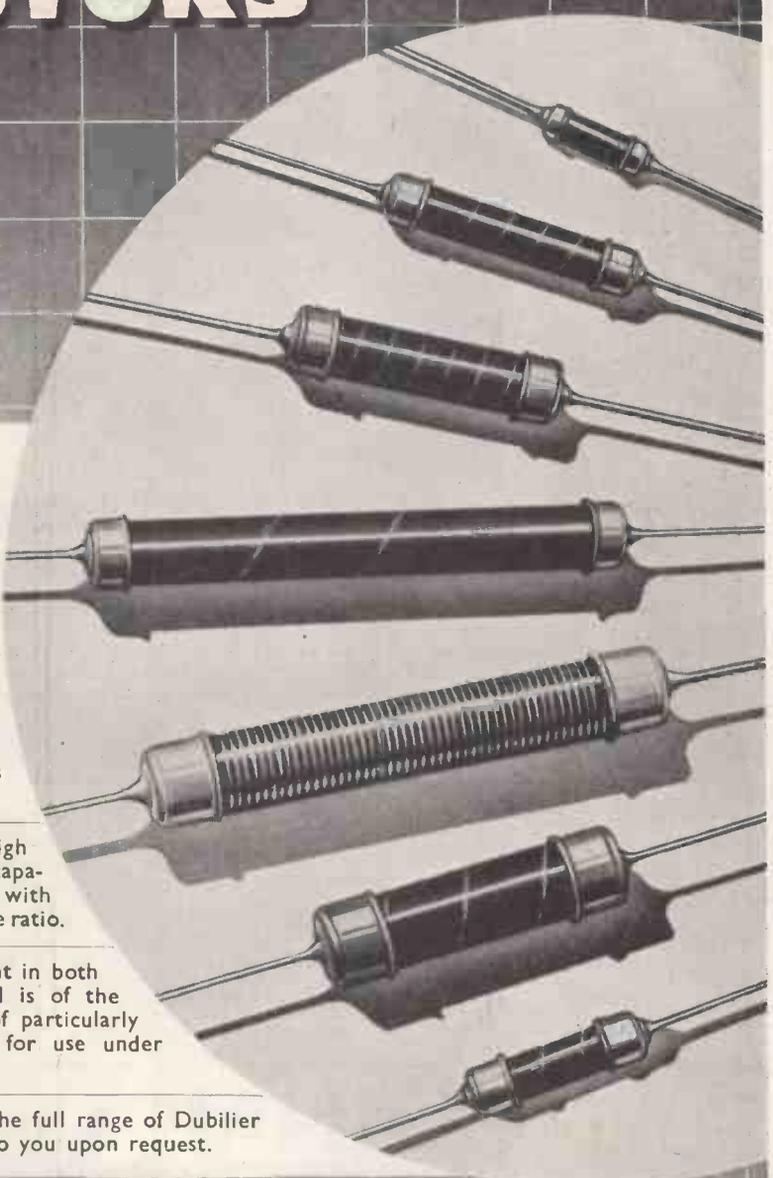1. Dubilier High Stability Resistors have a low temperature coefficient of resistance not exceeding minus 0.03% for values up to 100K Ω and not exceeding minus 0.04% per $^{\circ}$ C for values above 100 K to 1 M Ω .
2. The voltage coefficient is low and does not exceed 0.002% per volt applied. The noise level is very low and is less than 0.5 μ V per volt applied and in most instances is less than 75% of this value.
3. The resistors have excellent high frequency characteristics with low capacitance of the order of 0.5 pF and with an excellent inductance to resistance ratio.
4. The long term stability is excellent in both working and idling conditions and is of the order of 1%. The resistors are of particularly robust construction and suitable for use under the most stringent conditions.

Catalogue HSR 753 giving details of the full range of Dubilier High Stability Resistors will be sent to you upon request.



DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, NORTH ACTON, LONDON, W.3

Phone: Acorn 2241 (5 lines)

Cables: Hivoltcon, London.

Grams: Hivoltcon, Wesphone, London

Marconi International Code


Wearite & Ferrograph

TAPE RECORDING EQUIPMENT



**FERROGRAPH
MODEL 2A**

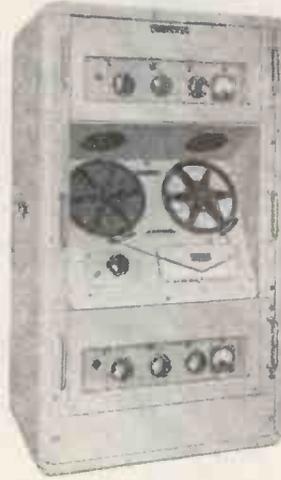Model 2A provides at a reasonable cost an instrument approaching professional standards — its specification commending it especially to those engaged in educational and cultural pursuits.



**WEARITE
EQUIPMENT
TYPE YDC**

Equipment Type YDC is a simultaneous dual-channel Recorder/Reproducer offering special facilities to those engaged in analysis problems in the medical, aeronautical and scientific fields.



**FERROGRAPH
MODEL YD**

Ferrograph Model YD. An instrument version of the famous 2A having balanced 600 ohm inputs and outputs, a tropicalised amplifier, and a performance up to professional standards. It can be rack mounted.



**SIGNAL
OPERATED
SWITCHING
UNIT**

A switching unit developed for use with recorders type YD and YDC. It switches on the recorder only when a signal is present and enables the traffic of many hours to be recorded on a normal length reel.

Ferrotape is now freely available in the following sizes:—


200ft.	600ft.	1,200ft.	1,750ft.
12/6	£1-6-9	£2-5-0	£3-3-0

WRIGHT & WEAIRE LTD.

British Ferrograph Recorder Co. Ltd.

Please note address of new offices and showrooms :

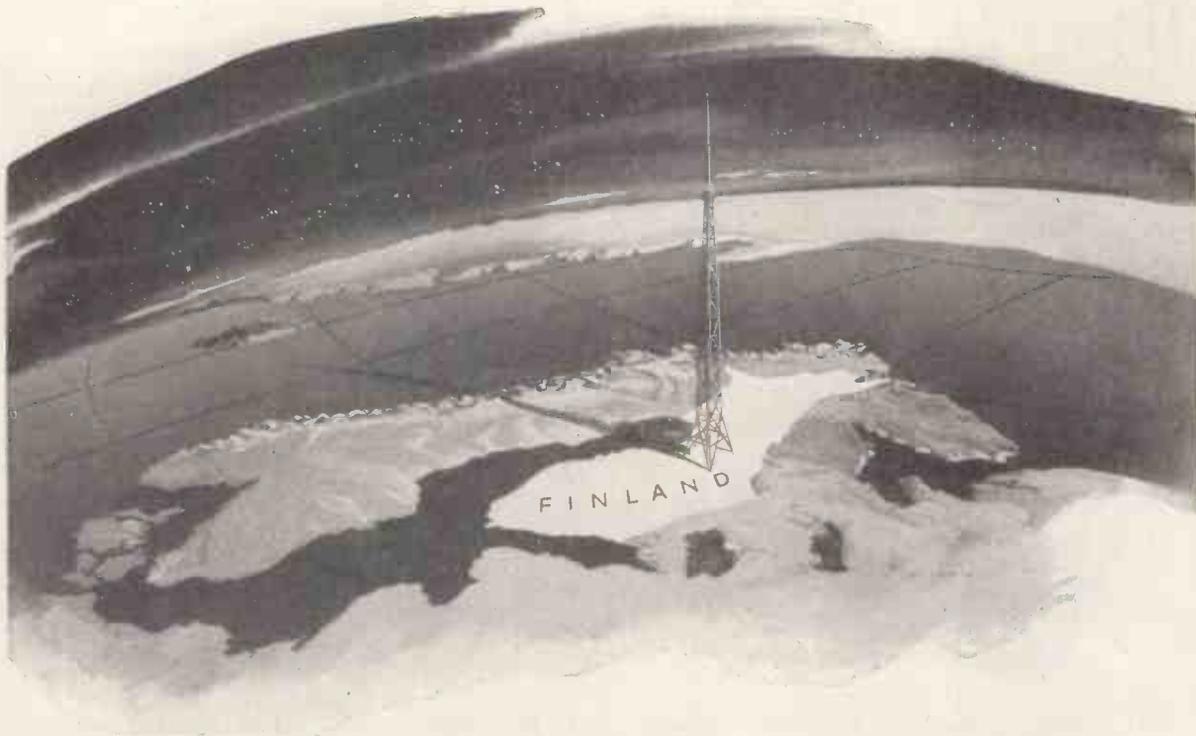131 SLOANE STREET · LONDON · S.W.1 Telephone: SLOANE 2214/5 & 1510



Finland expands her radio services with 19 RCA Transmitters

Frequency Modulation Network Broadcasting aids her people

ONCE AGAIN, Finland's traditional foresight has carried her people forward in the march of progress.

From Lahti—where Finland's new broadcast center is growing toward completion—a *Frequency Modulation* network will reach out to all parts of the land. The network's nineteen RCA FM transmitters will carry the benefits of modern radio to Finnish people from Helsinki on the Gulf of

Finland to Utsjoki in the far North.

. . .

The Radio Corporation of America is proud of the opportunity to have cooperated in this significant achievement and joins Havulinna Oy, its distributor in Finland, in saluting the Government of Finland, and the Finnish Broadcasting Company . . . a pioneer in FM networking on the European continent.



RCA INTERNATIONAL DIVISION

RADIO CORPORATION of AMERICA

RCA BUILDING

30 ROCKEFELLER PLAZA, NEW YORK, N.Y., U.S.A.


"Marca Registrada"

Sealed *with 'Araldite'*

Outstanding adhesion to metals and excellent electrical and mechanical properties combine to make 'Araldite' "the resin of choice" for sealing electrical components. Exceptionally low shrinkage on setting plus resistance to high temperatures,

humidity and corrosive agents contribute further to the success of this new epoxy resin for potting or casting applications. 'Araldite' complies with the requirements stipulated for the sealing of Service equipment. Our illustration of a transformer potted in 'Araldite' is published by courtesy of the makers, Messrs. Evershed & Vignoles Ltd., who also use the same resin for sealing resistances and valve assemblies.

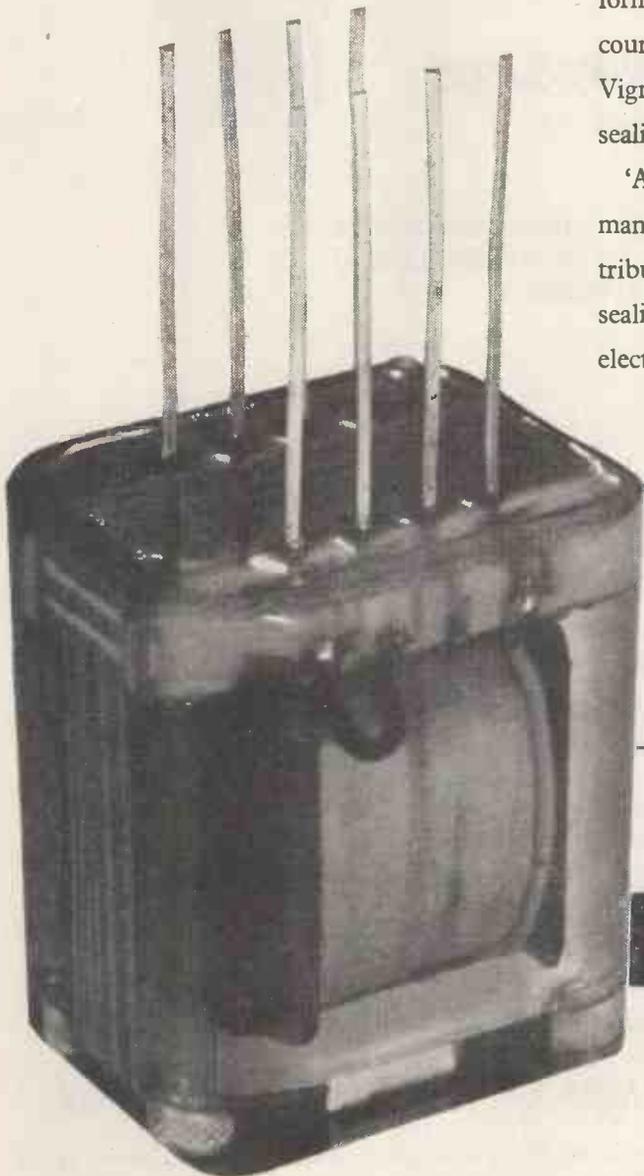'Araldite' epoxies are simplifying production in many industries. Nowhere, however, is their contribution more important than in the potting and sealing of components for radio, electronics and electrical engineering generally.



THESE ARE THE NEW EPOXIES !

'Araldite' (regd.) epoxy resins are obtainable in the following forms:—

Hot and Cold setting adhesives for metals, and most other materials in common use.

Casting Resins for the electrical, mechanical and chemical engineering industries.

Surface Coating Resins for the paint industry and for the protection of metal surfaces.

Full details will be sent gladly on request

'Araldite'

casting resins

Aero Research Limited

A Ciba Company

DUXFORD, CAMBRIDGE. Telephone: Sawston 187

Standard
 microphones
 maintain the highest standards in
design and performance
 for every purpose




Type 4021

A GENERAL PURPOSE STUDIO MICROPHONE FOR RADIO, TV., SOUND-REINFORCEMENT AND RECORDING

This well-known moving-coil microphone has been the subject of continuous research and improvement since 1937. It continues to satisfy a universal demand for an instrument which combines a very high fidelity of response with a mechanically robust design, at a reasonable cost. Extensively used as a calibrated standard for acoustic measurements, each microphone is individually manufactured to very fine limits and is tested after manufacture to conform with the highest laboratory standards.

The microphone as normally supplied is omni-directional. An alternative front baffle is available to give a directional response.

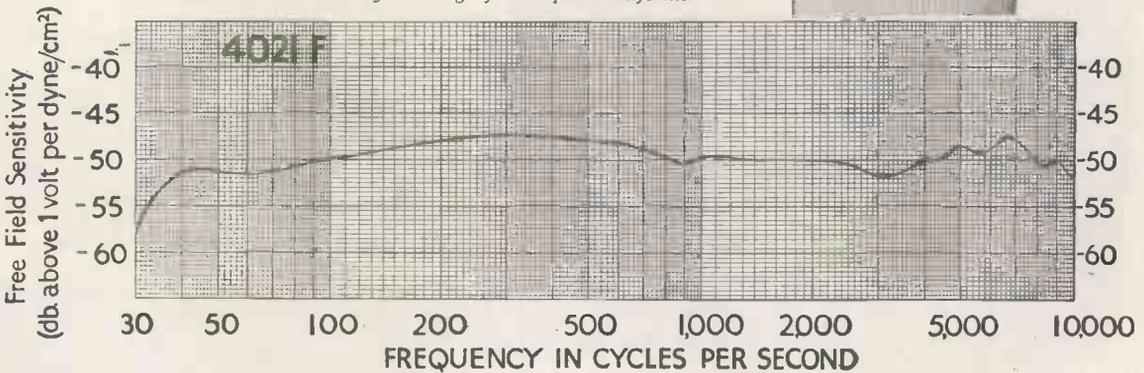Approved extract from National Physical Laboratory report. Typical 4021-F microphone showing frequency response characteristics at secondary winding of an input transformer



Bulletins and prices of all Standard microphones are available on request to



Standard Telephones and Cables Limited

PUBLIC ADDRESS DEPARTMENT, Connaught House, Aldwych, London W.C.2

New RECTIFIER DEVELOPMENTS

for TELEVISION ANODE SUPPLIES

and at less cost



HT 57
Price 24/3
AC Input 240 volts.

HT 59
Price 26/3
AC Input 250 volts.




WESTALITE METAL RECTIFIERS

These new "Westalite" rectifiers are the answer to every problem confronting the amateur television constructor, either for building into new sets or as replacements. Everything about them is right—price—size—output—efficiency—and, of course, reliability; their generous ratings enabling them to withstand the exceptional conditions experienced in modern television receivers. They are for use in conventional half-wave circuits, outputs being dependent upon the ventilation provided, and are available EX STOCK.

Address all enquiries to

DEPT. W.W.3, WESTINGHOUSE BRAKE & SIGNAL CO. LTD.
82 York Way, King's Cross, London, N.1

**AUTOMATIC
FREQUENCY
MONITOR (1 Mc/s)**

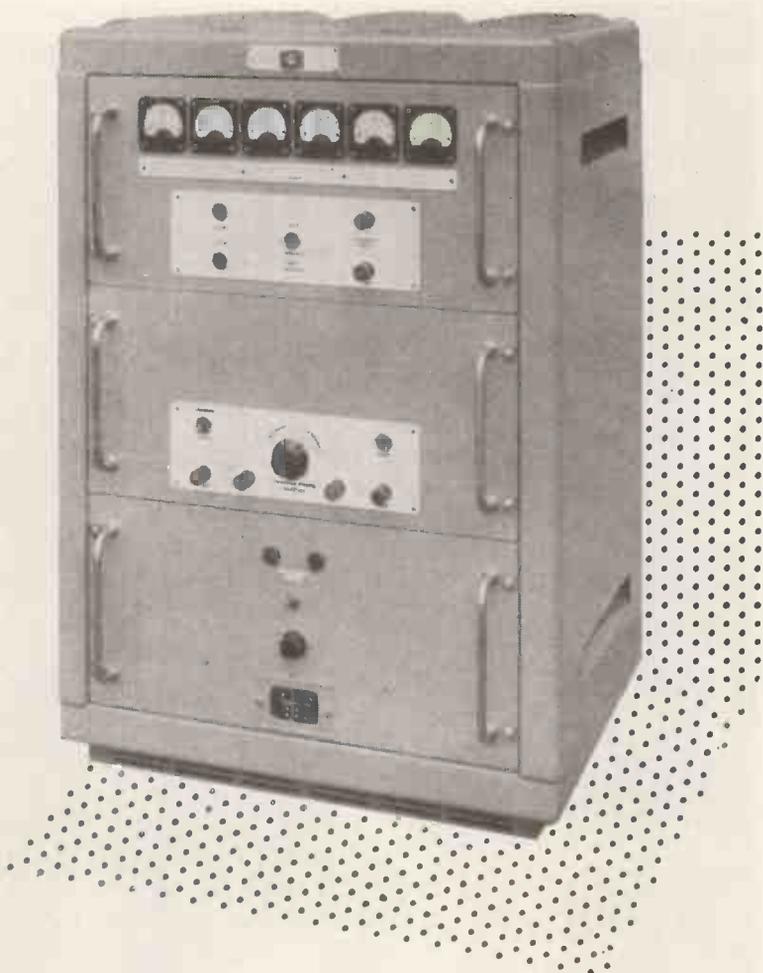

Designed for the measurement of any frequency in the range 10 c/s to 1 Mc/s with a basic accuracy of $\pm 0.005\% \pm 0.1, 1.0, \text{ or } 10 \text{ c/s}$.

Higher accuracies available if required. The unknown frequency is determined by counting the number of cycles that pass through a 'gate' open for a selectable time interval of 0.1, 1.0, or 10 seconds. The result is presented on six panel mounted meters each scaled 0 to 9 and is in decimal notation. Full information available on request.

CINEMA-TELEVISION LIMITED

A Company within the J. Arthur Rank Organisation

WORSLEY BRIDGE ROAD · LONDON · SE26

Telephone Hither Green 4600

SALES AND
SERVICING AGENTS

F. C. Robinson & Partners Ltd.,
287 Deansgate, Manchester, 3

Hawnt & Co. Ltd.,
59 Moor St. Birmingham, 4

Atkins, Robertson & Whiteford Ltd.,
100 Torrisdale Street, Glasgow, S.2

for all Good Instruments **S·E·I**
COPPER OXIDE RECTIFIERS

A range of rectifiers designed to suit all types of instrument movements.

The performance data and details of the types available are given in our publication No. C.O.R. 5305/2.

Please apply to the following address:—

SALFORD ELECTRICAL INSTRUMENTS
LIMITED
PEEL WORKS · SILK STREET · SALFORD 3 · LANCASHIRE
A Subsidiary of THE GENERAL ELECTRIC CO. LTD. OF ENGLAND.



Prompt delivery

Competitive Prices

**LOW LOSS
CERAMICS**
for the Electronic Industry

*Write for full
particulars from*

TAYLOR TUNNICLIFF (REFRACTORIES) LTD.

ALBION WORKS · LONGTON · STOKE-ON-TRENT

Telephone: Longton 33122

London Office : 125 HIGH HOLBORN, W.C.1

Telephone : Holborn 1951/2



A New Portable Wave Analyser

THE WAYNE KERR MODEL A.321

An audio frequency analyser of the heterodyne type to measure the relative levels of the components of a complex waveform down to -75 db below fundamental.

It is light, compact and simple to operate and can be supplied either in a transportable case or for standard 19" rack mounting.



Specification

FREQUENCY COVERAGE: 50—20,000 c/s in two ranges

FREQUENCY STABILITY: Better than $\pm 1\%$

INPUT LEVEL: Between -20 and +20 db relative to 1mV into 600 ohms adjusted by a 5 step attenuator and fine control of 0—10 db

FREQUENCY RESPONSE: Flat to within ± 1 db over the whole working range.

LEVEL STABILITY: ± 1 db if mains supply voltage remains within $\pm 5\%$

ACCURACY OF HARMONIC MEASUREMENTS: Harmonics below fundamental

to -55 db $\pm 5\%$
to -75 db $\pm 10\%$
or ± 1 db whichever is the greater.

INPUT IMPEDANCE: 100,000 ohm unbalanced (greater than 25,000 ohm, balanced, can be supplied to order)

SELECTIVITY: Constant over the frequency range. 2 stage crystal filter, mid band frequency 100 Kc/s. Flat top (± 1 db) pass band extending over 10 c/s ± 1 c/s. -55 db

HUM LEVEL: 110/115 and 200/250 volts 40/60 c/s

POWER SUPPLY: Approx. 60 watts

POWER CONSUMPTION: In case 20" \times 9" \times 8 $\frac{1}{2}$ "

DIMENSIONS: 31 lbs. approx.

WEIGHT:





1 kW Channelised Transmitter

THE GFT.560 is a 1-kW channelised transmitter with a frequency range of 1.5—30 Mc/s. It consists of three basic cabinets—r.f. unit, modulator unit, and power supply unit—combinations of which can be used to provide multi-frequency working as well as a number of different types of emission. The wave change facilities of the transmitter are both rapid and reliable—a valuable asset when the operating frequency is changed many times each day.

The GFT.560 is fully tropicalised, and its unit construction facilitates future expansion of the initial installation, should the need arise.

For use in conjunction with the GFT.560 there are ancillary units that enable the transmitter to be remotely controlled over a two wire telephone circuit: operational adjustments are dialled to the transmitter.

The versatility and reliability of this new Mullard transmitter make it particularly suitable for h.f. en-route, ground-to-air services and point-to-point communication networks. A team of Mullard communication engineers is available to advise on the use of the GFT.560 in such applications. They will also assist in planning complete communication systems, if required.

ABRIDGED DATA

Frequency Range 1.5—30 Mc/s
Frequency Stability To Atlantic City, 1947, standards
Power Output 1 kW
Types of Emission c.w., m.c.w., telephony, frequency shift, single and independent sideband. (A1, A2, A3, F1, A3a and A3b)
Output Impedance 600 ohms balanced twin feeder
Power Supply 400V, 50-60 c/s, 3-phase

Mullard



SPECIALISED ELECTRONIC EQUIPMENT



Loud-speaker Manufacturers to the radio industry since 1930

We do everything

... possible in the design and production of R. & A. Reproducers to ensure that initial performance is maintained over long periods of use. A typical example is the patented method of moulding phosphor-bronze strip voice-coil leads between the two layers of Bakelised linen which form the centring member.

We don't suggest that this works miracles, but it does avoid the buzzes and rattles commonly caused by flexible leads anchored to the cone; and it prevents both distortion of the cone when eyelets are inserted, and the effects of localised heat during the subsequent soldering operation.

**REPRODUCERS AND AMPLIFIERS LIMITED
WOLVERHAMPTON ENGLAND**


Telephone: Wolverhampton 22241 (5 lines)

Telegrams: Audio Wolverhampton


When Fidelity Really Matters
 then the **MUSICMASTER**
TAPE RECORDERS

will be your choice

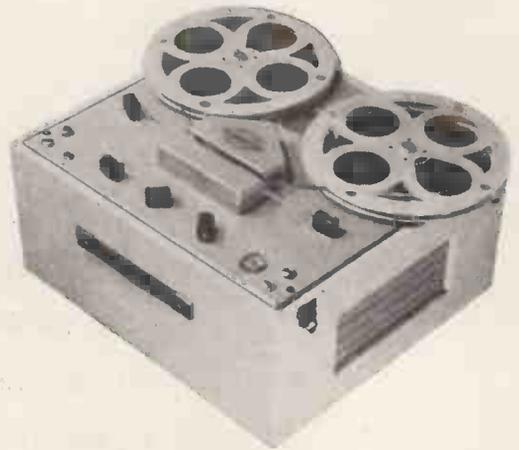These 'quality first' tape recorders have been exported to over forty countries throughout the world and are in regular use by Industrial Organisations and Government Services. Price for price they offer unequalled performance. Unsolicited testimonies on file prove conclusively that the Musicmaster Tape Recorders are among the finest tape recorders available.



MODEL 2250B £52

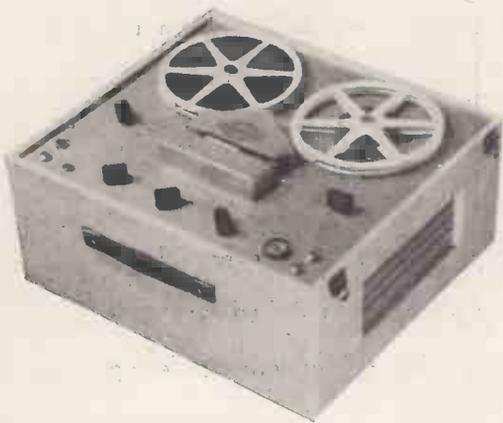

MODEL 1200B £45

H.P. TERMS AVAILABLE

WRITE TODAY FOR FULL DETAILS


DESIGNED FOR CRITICS

Trusound Ltd.

BY CRITICAL DESIGNERS

Showroom open daily for demonstrations

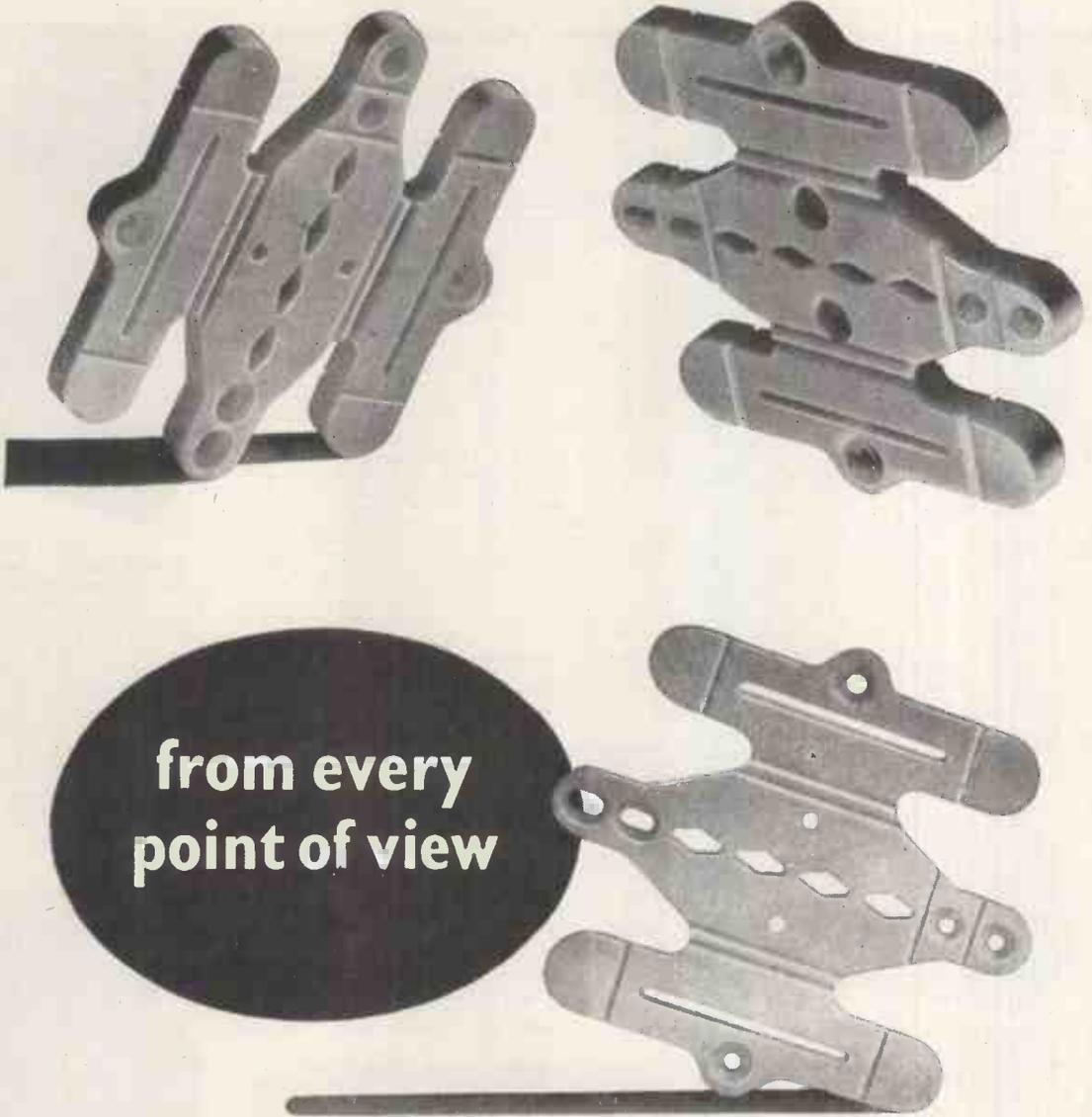OFFICES & SHOWROOM: 196 KINGSLEY ROAD, HOUNSLOW, MIDDX. (HOUNSLOW 7947) WORKS: TWICKENHAM, MIDDX.



from every
point of view

'Frequentite' is the most suitable insulating material for all high frequency applications. Seventeen years ago we introduced the first British-made low-loss ceramic, and consultation with us before finalising the design of new components is a wise precaution.

STEATITE & PORCELAIN PRODUCTS LTD.

Head Office: Stourport-on-Severn, Worcestershire. Telephone: Stourport 111. Telegrams: Steatoin, Stourport



S.P.66


REAL HIGH FIDELITY at modest cost . . .

• Manufacturer-to-Consumer policy saves you one-third cost!!

You may have already extended your record reproducer to include the now firmly established L.P. Records. You may be considering doing so. In either case, for real high fidelity at modest cost, it will pay you to consult us. Our aim is not just to sell you equipment but to save you money and to ensure that you get the apparatus most suited to your needs. Discuss

your problem with our Chief Engineer (available daily including Saturdays 11 a.m. to 6 p.m.). Or write enclosing 2d. stamp. This Technical Guidance Service will cost you nothing and save you pounds.

NOTE: Regarding Pick-up heads to take standard or miniature thorns for 78 r.p.m., these can be supplied with any of the single-record Gram Units or Auto-changers sold by us, if desired.

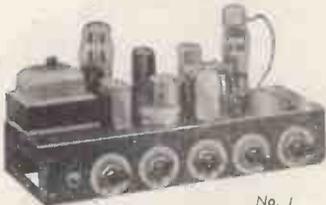

No. 1

No. 1 "SYMPHONY" AMPLIFIER is a 3-channel 5-watt Gram/Radio Amplifier with astonishingly flexible tone-control. You can lift the treble, the bass, or—and here is the unique feature—the middle frequencies to suit your own ear characteristics and the record or radio programme being heard. It is thus possible to arrange the frequency-response of the amplifier to a curve equal and opposite to the resultant curve of the other items in the chain so that what finally registers in the brain is as per original. This flexibility of control is far more important than mere nominal linear response of the amplifier, as the pick-up, speaker, etc., are not linear. Independent Scratch-Cut is also fitted and special negative-feedback circuit employed. The amplifier can accommodate a wide variety of records from old 78's to new L.P.'s. Input is for all types of pick-up of 0.2v. output or more and there is full provision (and power) for Radio Tuner. It is available to match 2/3 or 15 ohms speakers. Price: 10 gns. (carriage 5/-). Fitted in Portable Steel Cabinet 35/- extra.



No. 2

No. 2 "SYMPHONY" AMPLIFIER as No. 1 but with 10-watt Push-Pull triode output and triodes throughout. Wooden mains and output transformers and choke. Full provision and power for Tuner. Output tapped 3, 7.5 and 15 ohms. Competes with the most expensive amplifiers on the market yet costs only 15 gns. (carriage 5/-). Fitted in portable Steel Cabinet 2 gns. extra.



"SYMPHONY" AMPLIFIERS with REMOTE CONTROL. Both the above model Amplifiers are available with all controls on a separate Control panel with up to 4 feet flexible cable which simply plugs into the amplifier. Enables the Amplifier proper to be sat in the bottom of a cabinet whilst the controls are mounted conveniently higher up. Extra cost 2 gns.



GOODMANS CORNER CABINETS (right) for the AXIOM 150 Mark 2, manufactured by us to Messrs. Goodmans own design. Price: complete kit in plain board with felt, 8 gns. Price ready built, 10 gns. Finished in figured walnut, 16 gns. Other veneers to order. Carriage extra according to area.

GARRARD 3-SPEED GRAM UNIT MODEL "T." With turnover Magnetic Pick-up Head or Turnover Astatic Crystal Head, £10, post and pack., 2/6.

MODEL "TA," as above, but fitted with the latest Radio Show High-Fidelity Acos HGP35 Pick-up Heads (one for Std. and one for L.P.). Price £12/3/9, post and pack. 2/6. Heads only, 43/- each, post 1/-.

Model "TB," as above, but with two separate Decca XMS Heads, £13/7/6, post and pack., 2/6. Or with two separate Acos HGP39 Heads, £12/16/-. Or with Garrard Head for fibres (78) and Acos HGP39 for L.P., £12/5/-.

GARRARD 3-SPEED AUTO-CHANGERS, Model RC80, plays up to ten records 7in., 10in. or 12in. at 78, 45 and 33½ r.p.m. Stylus pressure on L.P. 10 grammes (adjustable). New ultra-sensitive auto-trip mechanism and heavy loaded turntable to eliminate "wow." Price £15/1/6 or with Garrard Magnetic or Astatic Crystal Turnover Pick-up Head, £17/3/6. With two separate Acos Hi-fi Heads, £19/12/6. With two separate Decca XMS Heads, £20/18/-. Carriage 5/-. Optional Extras: A.C./D.C. Operation £7/14/-. Fitting in de luxe rexine-covered Portable Cabinet, £5. Pick-up Head to take Fibre Needles, 25/-.

GARRARD 3-SPEED AUTO-CHANGERS, MODEL RC90 in de luxe rexine-covered Portable Case, £23/1/- Or fitted with Garrard Magnetic Turnover Head, £25/3/5. Or fitted with two separate Acos high-fidelity HGP35 Heads, £27/7/-. Carriage in all cases 7/6.

GARRARD 3-pin plug-in MAGNETIC PICK-UP HEADS for Fibre or Steel Needles fit Garrard and Decca Arms. Prices: Standard 25/-; Miniature low impedance 25/-; Postage 1/-; Garrard Arm 35/-; Decca XMS Arm, 23/6. Post 1/- Advice re matching if required.

COLLARO latest model A.C.3/534 3-SPEED GRAM UNIT with new "STUDIO" Pick-up type "O" or "P," £10/6/1, post 2/6.

COLLARO latest model 3RC531 AUTOCHANGER with "STUDIO" PICK-UP type "O" or "P" £15/3/10, carr. 5/-. DITTO but Mixer (3RC532), £17/9/6.

COLLARO "STUDIO" PICK-UP (Arm and Head) type "O" or "P" 74/8, post 2/-.

NEW TYPE ACOS PICKUPS. Arm with one HGP39 head (Standard or L.P.) £3/8/9 or with both heads £5/11/- Post 1/6d. Heads separately 42/3d each. Immediate delivery.

RECORD PLAYER CASES, rexine-covered with hinged lid and carrying handle and fasteners and uncut motorboard. Standard model to spring-mount any Garrard, Collaro or B.S.R./Decca Gram Unit, 57/6, post 2/6. Ditto autochanger size 90/-, carriage 5/-. As Standard but extra large for Connoisseur Motor and one or two Pickups 67/6, carr. 5/-.

TAPE DECKS. We stock and recommend the latest TRUVOX Mark 3. Price 22 gns., carriage free.

ILLUSTRATED CATALOGUE AND SUPPLEMENT. Our new catalogue just published will save all those considering the purchase of radio or record-reproducing equipment much time, trouble and money. Send two 2d stamps for your copy now! Our CHIEF ENGINEER will be pleased to afford TECHNICAL ADVICE where required.

HIRE PURCHASE FACILITIES

NOW AVAILABLE on orders of £15 or over.


Send one-third deposit with order, balance over 6 or 12 monthly instalments. State which required.

NORTHERN RADIO SERVICES

16 KINGS COLLEGE RD., ADELAIDE RD., LONDON, N.W.3. Phone: PR1mrose 8314

Tubes: Swiss Cottage and Chalk Farm.

Buses: 2, 13, 31, 113, 187.

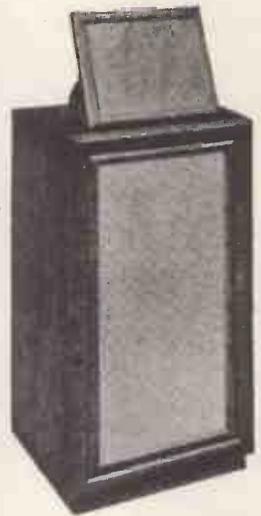

REGD. DESIGN

"SYMPHONY" BASS REFLEX CABINET KITS.


Regd. Design to match our Console Amplifier Cabinet illustrated below. 30in. high, consist of fully-cut 3in. thick, heavy, inert, non-resonant patent acoustic board, deflector plate, felt, all screws, etc., and full instructions. 8in. speaker model, 85/-; 10in. speaker model, 97/6; 12in. speaker model, £57/6. The design is the final result of extensive research in our own laboratory and is your safeguard of optimum acoustic results. Carriage 7/6. Ready built, 10/6 extra.



CONSOLE AMPLIFIER CABINETS (above), 33in. high, lift-up lid, take Gram Unit or Auto-changer, Amplifier, Pre-amplifier, and Radio Feeder Unit, finished medium walnut veneer. De Luxe version, 10 gns., carriage according to area. Bass Reflex Cabinets to match available. Details 2½d.




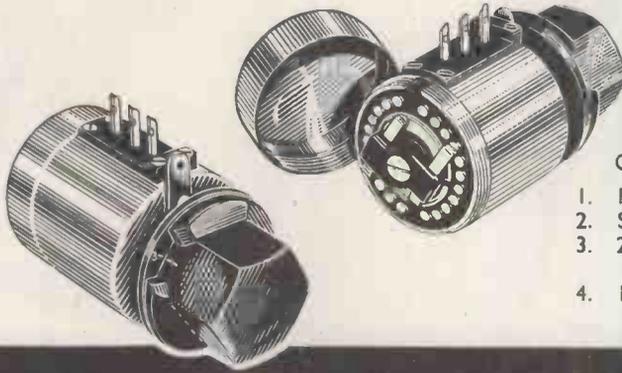
By Appointment to the Professional Engineer



INSTRUMENT "TYPE M"

GENERAL DESIGN FEATURES

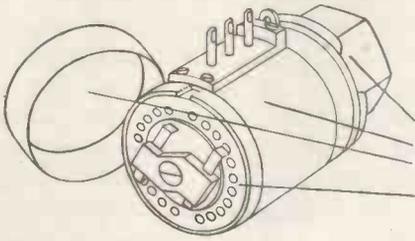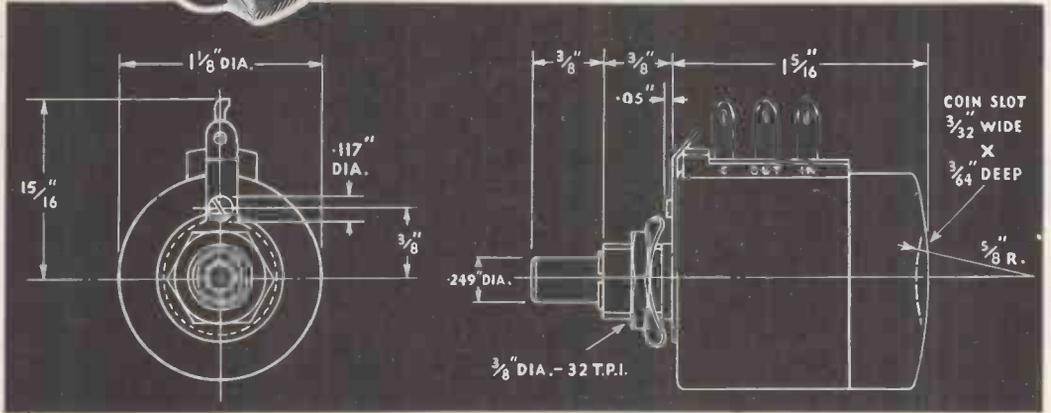1. Precision-made Midget Instrument.
2. Supplied as Attenuator or Fader.
3. 20-step Unbalanced Potentiometer or
or
4. 10-step Twin-arm Networks.



MECHANICAL CONSTRUCTION FEATURES


1. Entirely new and space-saving design Knob and Dial.
2. Contains Painton 1/4-watt High Stability Carbon Resistors.
3. Removable cover for easy access to stud panel.
4. Beryllium-Copper Studs and Contact Arms.

PAINTON
Northampton England

**ATTENUATORS AND FADERS • STUD SWITCHES • FIXED AND ADJUSTABLE WIREWOUND RESISTORS
WIREWOUND POTENTIOMETERS • MIDGET R.F. CHOKES • HIGH STABILITY CARBON RESISTORS • TERMINALS
PLUGS AND SOCKETS • KNOBS, DIALS AND POINTERS • TOGGLE SWITCHES • PUSH BUTTON SWITCHES**

SOMERFORD TRANSFORMERS AND CHOKES

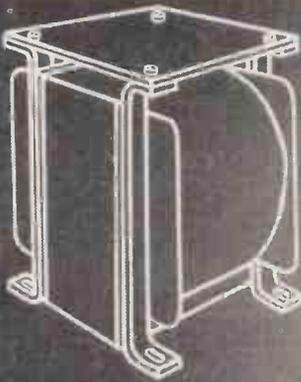A range of 360 standard types available for "off the shelf" delivery in several different mounting styles including both open and hermetically sealed "C" cores.



Fully descriptive Catalogue upon request

GARDNERS RADIO *Ltd*



SOMERFORD CHRISTCHURCH HANTS

Tel: 1024/5

ONLY the LAB unit has all these features...

★ Continuous storage ★ 700 resistors in a space 12" x 4" x 4"

★ Ohmic values separately carded ★ Finger-tip selection



BRITISH
PATENT
No. 680632

Designed to provide a complete range of resistors for research and experimental laboratories and small production units. As easy to use as a card index. Rapid selection from 700 sorted and carded resistors. Continuous storage — empty cards merely replaced with full ones available from stock. The Lab Continuous Storage

Unit is supplied FREE with initial purchase of 180 Type R Resistors (Order LSUC 1/2) or 240 Type T " (Order LSUC 1/4)

THE **LAB**
TESTED
CONTINUOUS
STORAGE UNIT

RESISTOR SPECIFICATION					
Ref.	Type	Loading	Max. Volts	Range	Dimensions
T	1-watt	1/2-watt	250	10 ohms to 10 megohms	1 1/2" x 1 1/2"
R	1-watt	1-watt	500		1 1/2" x 1 1/2"

Tolerance available ±20%, ±10%, ±5%

The Lab Continuous Storage Units are available from your normal source of supply but more detailed information can be obtained from

THE RADIO RESISTOR COMPANY LTD.
50 ABBEY GARDENS, LONDON, N.W.8 Telephone: Maida Vale 5522

Announcing the **NEW**



OHMMETER *Type 861*

1 ohm to 10 Megohms



THE AIRMEC OHMMETER is intended for production and laboratory continuity testing, and enables the value of any resistance between 1 ohm and 10 Megohms to be rapidly determined. A large meter, having a scale length of approximately 7 inches, is employed, thus enabling excellent reading accuracy to be obtained.

- **Resistance Range:** 1 ohm to 10 Megohms in 6 ranges.
- **Range selection:** By push-button switching
- **Accuracy:** $\pm 2\frac{1}{2}\%$.
- **Test Voltage:** The instrument operates from the normal A.C. mains supply, the D.C. test voltage being obtained from an internal stabilised source.
- **Dimensions:** The instrument, which is suitable for both bench and rack mounting, is 19 ins. wide, 12 ins. high, 10 ins. deep over projections.

Full details of this instrument which is available for immediate delivery will be forwarded on request.

AIRMEC
L I M I T E D

HIGH WYCOMBE — BUCKINGHAMSHIRE — ENGLAND

Telephone: High Wycombe 2060.

Cables: Airmec, High Wycombe

for

SELENIUM RECTIFIERS

consult



WHETHER the need is for a single unit or a supply running into thousands . . . if it's a Selenium Rectifier that must fulfil critical requirements and maintain its characteristics over long periods . . . the answer is to be found with Electrix.

- Electrix Rectifiers are characterised by their cool running and consistent long-life conformity to stated specification
- Manufacturers, Traders and Electronic Engineers, send us your specific requirements.
- Your needs may possibly be met from "standard" types, or
- "To specification" models can be quickly prepared.
- Quotations by return . . . and deliveries a matter of days only.
- We welcome export enquiries.

Here are some typical "standard" full-wave types

	each
Output 12/15 Volts D.C. 1 Ampere. List Price	9/-
Output 12/15 Volts D.C. 2.5 Ampere. „	13/6
Output 12/15 Volts D.C. 4 Ampere. „	22/6
Output 12/15 Volts D.C. 6 Ampere. „	35/-

Trade Supplied

- Heavy duty rectifiers with say 230/250 volts A.C. input and 220 volts D.C. output a speciality.
- We use only freshly manufactured selenium plates and components, no ex-W.D. materials whatsoever.

HOUSEHOLD ELECTRIX LTD
47-49 HIGH ST., KINGSTON-ON-THAMES
Telephone: KINGston 4585

In the Winter Number of the

BBC QUARTERLY

—NOW ON SALE—

Proposals for a Programme Fading Circuit

by *R. C. Whitehead, A.M.I.E.E.*

*Planning and Installation Dept.,
B.B.C. Engineering Division*

The author points out several disadvantages of conventional methods employed for fading sound and vision signals. He then proceeds to describe several alternative circuits designed to overcome these disadvantages and based on the use of combinations of resistive elements having positive and negative temperature coefficients.

The use of such elements in the circuits described is shown to eliminate many of the difficulties commonly encountered in programme fading networks.

Standardisation of Magnetic Tape Recording Systems

by *E. D. Daniel, M.A., A.M.I.E.E.*

and

*P. E. Axon, O.B.E., M.Sc., Ph.D., A.M.I.E.E.
Research Department, B.B.C. Engineering Division*

The recording characteristic of a magnetic tape system can be defined in terms of the magnetic induction at the tape surface. A method of measuring surface induction is described which employs a non-magnetic conducting loop as a reproducing head. Using tapes calibrated by means of this device, the action of conventional magnetic-core reproducing heads is examined and various empirical expressions are deduced for their response. It is shown that if suitable corrections are applied conventional heads having either short or very long gaps may be also used for standardisation. Finally, the effects of various common imperfections and maladjustments in all types of reproducing heads are examined in detail.

Technical Training for Broadcasting

by *K. R. Sturley, Ph.D., M.I.E.E.*


*Head of Engineering Training Department,
B.B.C. Engineering Division*

Is technical training in broadcasting worthwhile? This problem is examined and details of the B.B.C.'s views on the matter and some of the methods employed by the Department, are stated. Information on the types of courses which have been formulated for particular categories of staff under training for specific reasons, together with a chart showing the courses and the proportion of time spent on the various aspects of the work, is given.

Other contributors to this number discuss broadcast talks, drama, music and farm radio.


—PRICE 2/6—

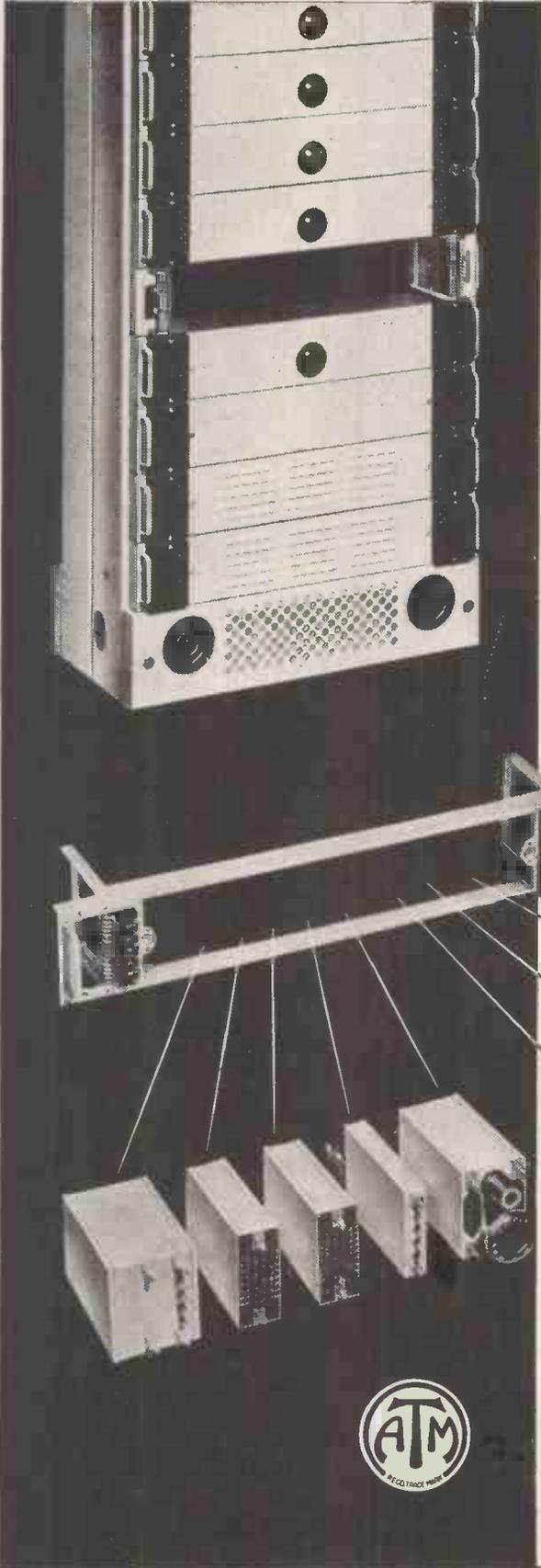Obtainable through bookstalls or news-agents or post free from B.B.C. Publications, 35, Marylebone High Street, London, W.1. Yearly Subscription 10/-.



Designed for Continuous Service

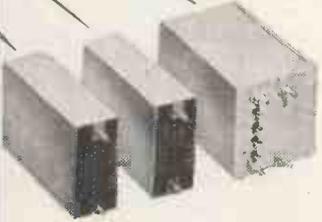ATE/TMC Transmission equipment is designed to offer an operating administration the maximum facility in the performance of maintenance routines. Jack-in panel frames fitted with quickly detachable functional units ensure the most rapid form of servicing yet devised. You are invited to apply for a copy of "Unit Construction Practice" which describes the technique employed.






AUTOMATIC TELEPHONE & ELECTRIC CO. LTD.

Radio and Transmission Division, Strowger House, Arundel Street, London, W.C.2. Telephone: TEMple Bar 9262. Cablegrams: Strowgerex London. Manufacturers:—AUTOMATIC TELEPHONE & ELECTRIC CO. LTD., Ljverpool and London. TELEPHONE MANUFACTURING Co. LTD., St. Mary Cray, Kent.



Bullers CERAMICS FOR INDUSTRY

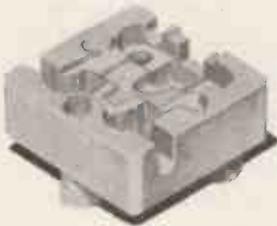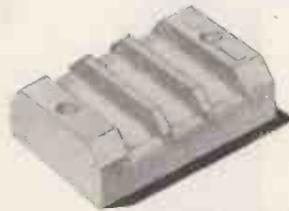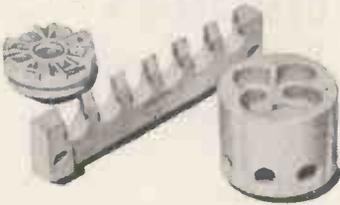High quality material and dimensional precision are attributes of Bullers die-pressed products. Prompt delivery at competitive prices.



We specialise in the manufacture of

PORCELAIN
for general insulation

FREQUELEX
for high-frequency insulation

REFRACTORIES
for high temperature insulation

PERMALEX & TEMPLEX
for capacitors

BULLERS LIMITED

Porcelain Works :
MILTON,
STOKE-ON-TRENT
Stoke-on-Trent S164

Sales Office :
6, LAURENCE POUNTNEY HILL,
LONDON, E.C.4
Mansion House 9971

Iron Works :
TIPTON,
STAFFORDSHIRE
Tipton 1691

ELL08

NEW ARCOLECTRIC SIGNAL LAMPS

For Low Voltage or Mains

Illustrated are a few signal lamps taken from our wide range. The insulation of every Arcoelectric signal lamp will resist a flash test of 1,500 volts A.C.

The S.L.90 illustrated here is a typical Arcoelectric low voltage signal lampholder. It is designed to accept popular M.E.S. bulbs. The bulb is accessible from front or rear of panel. The domed plastic lens surrounded by a polished chrome bezel gives a most attractive panel appearance. This holder can be fixed in a single $\frac{3}{8}$ " hole.

The mains voltage signal lamp S.L.88/N is supplied complete with an M.E.S. neon tube and a suitable series resistance.

Write for Catalogue No. 128



S.L.88/N



S.L.90



S.L.86



S.L.82



S.L.92


ARCOLECTRIC
SWITCHES · LTD

CENTRAL AVENUE, WEST MOLESEY, SURREY · TELEPHONE: MOLESEY 4336 (3 LINES)



Pointers for Designers

AND CONSTRUCTORS
NUMBER TWELVE

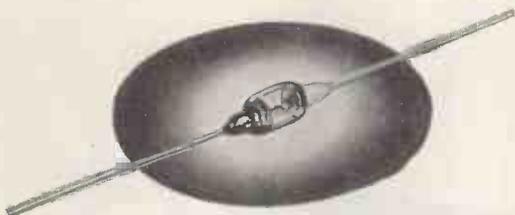

G.E.C.


GERMANIUM DIODE

GEX 34

The use of the Germanium Diode with its attendant advantages of robustness—small size—long life—high efficiency—freedom from hum and general circuit manoeuvrability is rapidly becoming standard practice in modern television receiver design.

The GEX 34 has been specially developed as a high level vision detector to meet the increased drive voltage requirements of modern cathode ray tubes operating at high E.H.T. voltages. During manufacture the GEX 34 is subjected to special functional tests at the typical intermediate frequency of 35 Mc/s to ensure a satisfactory R.F. performance.

It is also an efficient sound detector and sound noise limiter. In the former application it is capable of driving a high efficiency output pentode directly, thus enabling the designer to eliminate the customary intermediate audio stage and its ancillary components. This typical television sound detector and noise limiter circuit uses two GEX 34 germanium diodes. The saving in space possible using germanium diodes compared with conventional thermionic diodes is obvious from the full size illustration of the GEX 34.

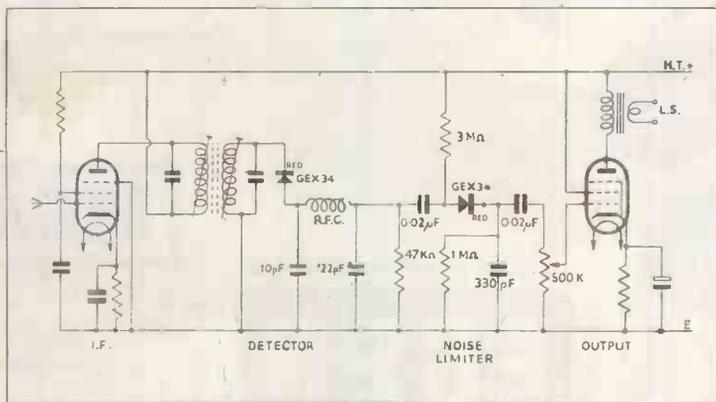

Write to Osram Valve and Electronics Dept. for full technical data on the GEX 34 and the complete range of G.E.C. Germanium Diodes.

EGEN


MINIATURE POTENTIOMETERS

Designed to meet the demand for Egen reliability within the smallest possible compass, these exceptionally small carbon potentiometers ($\frac{1}{2}$ " diameter) retain all the desirable features of their standard-size counterparts. The special Egen carbon deposition process ensures a highly stable resistance element of extreme durability. Double-contact rotor provides firm balanced contact with exceptional freedom from wear and noise. Positively located soldering tags, silver plated for easy soldering. All steel parts rustproofed. Standard resistance values available, from 5000 ohms to 2 megohms.

Type 105 is identical to Type 115 except that a 2-pole Q.M.B. switch is incorporated.



TYPE 105

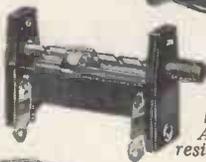

PRE-SET RESISTORS
A wire-wound pre-set resistor for panel or chassis mounting



SUB-MINIATURE VOLUME CONTROLS
For use in Deaf Aids and other miniature electronic apparatus

Export enquiries welcomed




EGEN ELECTRIC LTD.,
CHARFLEET INDUSTRIAL
ESTATE, CANVEY ISLAND, ESSEX • PHONE: CANVEY 691-2



For
Quality in
the Core

*Electrical
STAMPINGS
and Magnetic
SCREENS
by MEA
remain
unequaled*

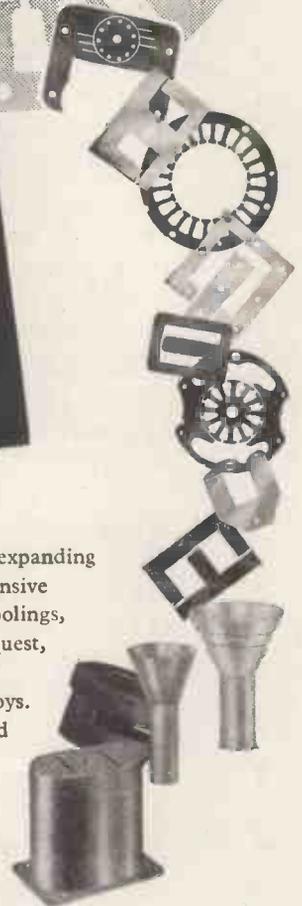Pacing progress in the ever expanding field of Electronics, the extensive M.E.A. range of standard toolings, plus special patterns on request, are available in all grades of Silicon and Nickel Iron Alloys. Your requirements, standard or special, will receive immediate attention.




The following catalogues are available: Transformers and Choke Stampings, F.h.p. Motor Stampings, Magnetic Screening Tubes and Cases, Nickel Iron Alloys Data, on request to our Head Office, Dep. F.H.M.

*For Service to Science and Industry
throughout the field of Electronics*

MAGNETIC & ELECTRICAL ALLOYS LTD.

HEAD OFFICE: 101-103, BAKER ST., LONDON, W.1. Tel.: Welbeck 3381/2.
WORKS: BURNBANK, HAMILTON, LANARKSHIRE. Tel.: Hamilton, 932/3/4.
MANCHESTER: 33, BYROM STREET, DEANSGATE. Tel.: Blackfriars 5223.
BIRMINGHAM: 12, WESTWOOD RD., SUTTON COLDFIELD. Tel.: Streetly 78586.


THIS

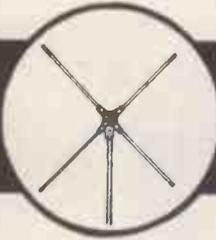

MARKS THE SPOT...

FOR AERIAL NEWS AND VIEWS

They are all **"5 STAR AERIALS"**

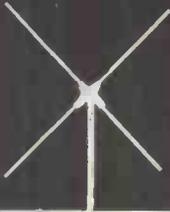	"ANTEX" 6 MODELS
	DIPOLE 3 MODELS
	DIPOLE AND REFLECTOR 4 MODELS
	MULTI-ELEMENT 4 MODELS

The entirely new and patented "SNAPACITOR" principle, exclusive to Antiference, provides an aerial that is :



CORROSION PROOF

There are no metal-to-metal connections.



PRE-ASSEMBLED AND ALIGNED

Rods and insulator are factory assembled as a complete unit.



QUICKER TO INSTALL

Factory built as a unit, packed complete in one carton, is instantly ready for mounting—no loose parts to go astray.



LIGHTER IN WEIGHT

Construction is of highest grade aluminium tubing of aircraft specification which provides maximum strength with minimum weight, to withstand the severest of weather conditions.



TRULY COMPETITIVE IN PRICE

MODELS FROM **27'6** TO **231'-**

AVAILABLE FROM ANTIFERENCE APPOINTED DISTRIBUTORS.

Fully descriptive leaflets on request :
 Leaflet No. E3/W. "Antex" Series.
 Leaflet No. A3/W. Single Dipole, and Dipole and Reflector.
 Leaflet No. P3/W. Multi-Element Arrays.

ANTIFERENCE
Aerials

ANTIFERENCE LIMITED, BICESTER ROAD, AYLESBURY, BUCKS.

BK

CORDIALLY INVITE ALL HIGH-FIDELITY ENTHUSIASTS TO
visit our new REGENT ST. showroom

★ For the first time we can offer direct, comparative demonstrations—under identical conditions—of the accepted best in high quality audio amplifiers and loud-speakers.



★ We are demonstrating tape reproduction to truly high fidelity standards.

Mon. to Fri. 10.30-5.30.
 Sat. 10.30-12.30. Phone REG 7363

H.P. terms on all
 equipment available

B. K. PARTNERS LTD.

229 Regent St., London, W.1.

(Entrance Hanover St.)



Facsimile in Sound



3-SPEED MOTOR

Identify each instrument in the orchestra with "Connoisseur" High Fidelity Equipment. Records seem to live when played.

The 3-speed motor (33 $\frac{1}{3}$, 45, 78 r.p.m.) with 12in. turntable is priced (without pickup) at £21/17/3.

The 3-head pickup (if required with one head £5/19/3) extra heads £3/6/3. Spare Armature System with sapphire 13/7.

All prices stated include Tax.

3-HEAD PICKUP

Connoisseur
 High Quality Equipment
A. R. SUGDEN & CO.
 (ENGINEERS) LTD.

WELL GREEN LANE, BRIGHOUSE, YORKSHIRE
 Telephone: Halifax 69169

OVERSEAS AGENTS: S. Africa: W. L. Procter (Pty.) Ltd., 63 Strand Street, Cape Town. Australia: J. H. McGrath & Co. Pty., Ltd., 208 Little Lonsdale Street, Melbourne. Canada: The Astral Electric Co. Ltd., 44 Danforth Road, Toronto 13, Ontario. New Zealand: Turnbull & Jones Ltd., Head Office 12/14 Courtenay Place, Wellington. Hong Kong: The Radio People, Ltd., 31 Nathan Road, Hong Kong. Malaya: (Main Distributors) Eastland Trading Co., 1 Prince Street, Singapore.

OC10
OC11
OC12

3

JUNCTION TRANSISTORS

for circuit experiments

Three types of junction transistor, the Mullard OC10, OC11 and OC12 are now available for circuit experiments.

In the past, the lack of supplies has prevented circuit designers in this country from gaining direct experience of junction transistors in their own laboratories. Now, however, the availability of the first junction types invites practical investigation into their many possible applications.


As junction transistors provide no current gain when connected with grounded base, they are more usually employed in grounded emitter circuits, where they function well as A.F. amplifiers. In both amplifier and oscillator circuits these transistors will operate with supply voltages as low as 1.5 V and with current consumptions of the same remarkably low order.

The OC11 is a general-purpose amplifier, while the OC12 is intended for operation in an output stage, although it can, of course, be used otherwise. A low-noise version of the OC11 is provided by the OC10, a special transistor for early stages in high-gain amplifiers.

Junction transistor type		OC10	OC11	OC12
Max. D.C. negative collector-to-emitter voltage (V)		4	4	4
Typical D.C. collector voltage (V)		2	2	2
Typical collector current (mA)		-0.5	-0.5	-2
Current amplification factor (α') with grounded emitter		17	17	30
Output resistance with infinite A.C. source impedance (grounded base) (K Ω)		700	700	500
Special low-noise characteristics		★	—	—
★ Superior type for these characteristics.				

Information on these junction transistors and the point-contact types in the Mullard range of semi-conducting devices will be gladly supplied by the Industrial Technical Service Department at the address below.

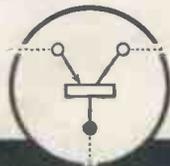- The OC10, OC11 and OC12 are readily available for experimental purposes at a price comparable with that of mains subminiature valves.



Mullard

MULLARD LIMITED, COMMUNICATIONS & INDUSTRIAL VALVE DEPT., CENTURY HOUSE, SHAFTESBURY AVE., LONDON, W.C.2

EDDYSTONE

MODEL '840'

AC/DC COMMUNICATIONS RECEIVER



The New Model '840', illustrated above, possesses full Communication facilities and operates from either A.C. or D.C. mains 100/110 and 220/250 volts.

- Seven valve superheterodyne with R.F. stage.
- Frequency coverage 30 Mc/s. to 480 kc/s.
- Gear driven tuning with 140/1 reduction.
- Mechanical bandspread. Accurate re-setting.
- B.F.O. and noise limiter.
- Internal loud-speaker. Headphones jack.
- Robust diecast construction. Rustproofed steel case.
- Suitable for tropical service.
- Weight 30 lbs. Size 16 $\frac{3}{4}$ " x 10 $\frac{1}{2}$ " x 8 $\frac{3}{4}$ " high.

List Price (in U.K.) £45

Exempt from Purchase Tax

PLEASE WRITE FOR FULL SPECIFICATION TO THE MANUFACTURERS:

STRATTON & CO. LTD., EDDYSTONE WORKS, BIRMINGHAM, 31

A THREEFOLD INSTRUMENTATION SERVICE ...

F. C. Robinson & Partners Ltd. offer a unique threefold service to users of electronic instruments in the North of England. Enquiries are invited and will receive prompt attention.

- 1** We are agents for the leading makes of radio and television test equipment, electronic instruments and industrial control apparatus and stocks are constantly maintained at our showroom in Manchester.
- 2** Our factory at Cheadle, Cheshire is specially equipped and staffed for the design, development and manufacture of specialized non-standard electronic apparatus.
- 3** Prompt and skilled maintenance facilities are always available. Our specially trained engineers are ready to carry out repairs to electronic instruments, either in our own workshops or on your own premises.

F. C. ROBINSON & PARTNERS LIMITED
ELECTRONIC ENGINEERS

Sales & Service: 287, DEANS GATE, MANCHESTER, 3.

Phone: DEAnsgate 6601

Factory: COUNCILLOR LANE, CHEADLE, CHESHIRE.

To start you talking —and listening



Those who have followed the growth of high quality reproduction in recent years may wonder how it is possible to improve still further the amplifier part of the system. Yet, like its predecessor, the QUAD II introduces entirely new features of importance to the final objective—features anticipating trends in design of both amplifier and associated equipment.

Engineers will readily appreciate among the many salient points of design of this amplifier, the complete stability under all load conditions. They will delight too in the unique low noise pickup matching system and in the new wide range filter developments.

The gramophone enthusiast will be pleased to find that his moving coil pickup no longer requires a transformer; that each of the seven playback characteristics is accurately provided at the touch of a button; that the logical system of filter control gives him low distortion without the sacrifice of correct musical balance.

Above all, the musician will find that the QUAD II gives the closest approach to the original sound. . . . The QUAD II booklet will tell you why.


A booklet
describing the
QUAD II
is available
on request from

 **ACOUSTICAL**
MANUFACTURING CO LTD
HUNTINGDON • HUNTS • TEL: 361



PRICE £42.0.0 RETAIL

4 mmf/ft

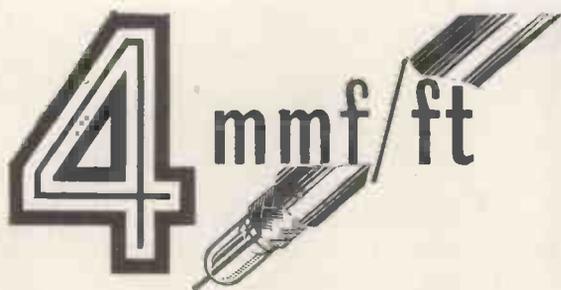

AIR-SPACED ARTICULATED

CO-AX CABLES

offer a unique combination of

- ✓ FRACTIONAL CAPACITANCE
 - ✓ HIGH IMPEDANCE
 - ✓ MINIMUM ATTENUATION
- ALONG WITH
- ✓ EXCEPTIONAL FLEXIBILITY
 - ✓ LIGHT WEIGHT

38 STOCK TYPES

FOR ANY OF YOUR STANDARD
OR SPECIAL APPLICATIONS

A few of the very low capacitance types are:

Type No.	Capacit. μ F/ft.	Impedance ohms	O.D.
C.44	4.1	252	1.03"
C.4	4.6	229	1.03"
C.33	4.8	220	0.64"
C.3	5.4	197	0.64"
C.22	5.5	184	0.44"
C.2	6.3	171	0.44"
C.11	6.3	173	0.36"
C.1	7.3	150	0.36"

TRANSRADIO
CONTRACTORS TO
H.M. GOVERNMENT
LTD.


138a CROMWELL ROAD, LONDON, S.W.7

AERIALITE AERIALS
are designed for
HIGH PERFORMANCE




AERFRINGE—For long-distance reception this range has the high electrical performance which is essential. The robust construction ensures long service even in the most exposed conditions. The range is available with 10ft. or 14ft. alloy mast and double chimney lashings or arrays only. Prices from £12/15/- complete (Model 63).

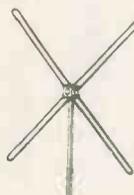Model 63A
Forward Gain
8 dB
Front/back Ratio
21.6 dB
Acceptance
Angle 55°




DUBLEX—Special folded dipole construction plus driven array connections make the Dublex the highest gain aerial in this price bracket. The Dublex (as supplied to the B.B.C.) is available with 7ft., 10ft. or 14ft. mast versions or as an array only. The Dublex 77S (7ft. mast single lashing bracket) is £4/8/6 complete. (Mast and array is only 3.2 lbs.)

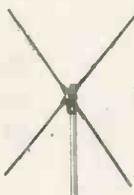Model 77
Forward Gain
6 dB
Max/min Ratio
25 dB
Acceptance
Angle 96°



UNEX—Light in weight, high in performance, the Unex combines excellent forward gain with robust construction at a low price. The cross-connected elements give a driven array which is extremely easy to erect. The Unex 83S (with 6ft. alloy mast, single lashing chimney bracket) is only £3/19/6 complete.

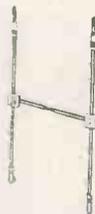Model 83
Forward Gain
3 dB
Front/back Ratio
25 dB
Acceptance
Angle 176°



AERFOLD—Where conditions do not allow an outdoor aerial to be fitted, the AERfold provides a high gain aerial which has excellent directivity. It is easy to fit and by rotation will eliminate or substantially reduce interference. Price £15/-.

Model 71
Forward Gain
3.75 dB
Max/min Ratio
40 dB
Acceptance
Angle 120°

ACCESSORIES

The range covers coaxial plugs, sockets, connector boxes, matching boxes, gutter brackets, tile clips, lightning arrestors.

H.F. CABLES

All types are manufactured, including co-axials, twin feeders and screened balanced twin. Applications cover T/V and radio downloads etc.

CONNECTOR WIRES

P.V.C. insulated single conductor and multi-strand types. Also, screened and sheathed electronic cables and H.T. connecting wires.

THE AERIAL'S RIGHT
IF IT'S AN AERIALITE

'AERIALITE Aerials

AERIALITE LTD · STALYBRIDGE · CHESHIRE

Photograph: by courtesy of Handley Page Ltd.



with **GOODMANS VIBRATORS**

The flight characteristics of a newly designed aeroplane are the subject of lengthy calculations before the first prototype is built. Whilst the mathematical calculations are themselves accurate, they are based, as in all design work, on several assumptions which have to be verified by a series of pre-flight tests.

One of these essential investigations is the Ground Resonance test, the purpose of which is to determine the various complex modes of vibration of the airframe structure. The frequency of the mode and the dynamic response at remote parts of the aircraft must be accurately determined. The information obtained together with the aerodynamic derivatives is used in predicting the critical 'flutter' speed of the aircraft. The illustration shows one of the two Goodmans Model 8/600 Vibration Generators which were used to excite the Handley Page "Victor" for this very important test.

For wide frequency range vibration testing and dynamic response investigations, Goodmans Vibration Generators are an obvious choice. These units require no field excitation and provide a faithful reproduction of the input wave form. Industrial applications of controlled vibration are continually increasing; maybe it can serve you—in which case our unique experience is at your service.

The range includes models from the 8/600 shown, developing a force of ± 300 lb., to the midget model, with a force of ± 2 lb., for optical cell research and hairspring torque testing, etc.

Just another of the wide applications of Goodmans Vibration Generators. Full technical data available from Vibration Division "W"



GOODMANS INDUSTRIES LIMITED, Axiom Works · Wembley · Middx · Wembley 1200 (8 lines)
GD

EVERYTHING

YOU HAVE ALWAYS WANTED

now available in this chassis 'de luxe' model


The **BURGOYNE 8 VALVE** Superhet — Custom Built — Radiogram Chassis

With a push-pull output giving 8 watts of undistorted quality reproduction and using negative feed-back, this fine chassis is supplied for those connoisseurs wanting only the best, at a price within their means!

- ★ Extra large fully illuminated coloured tuning scale 11in. x 6in.
- ★ Wavebands 16-50; 190-550; 1,000-2,000 metres.
- ★ Bass and treble controls for cut and lift.
- ★ Magic eye tuning indicator.
- ★ Precision flywheel tuning.
- ★ Chassis size 12in. x 7in.
- ★ Overall height 9in.
- ★ Chassis height 2in.
- ★ 8 Mazda valves 6C9, 6F15, 6L1, 6LD20, 6U7, 6M1 and 2 6P25.

Come to the "Radio Centre" to see and hear this exceptional unit or order in confidence by mail.

- ★ Speech coil impedance 3 OR 15 ohms.
- ★ Extension speaker sockets.
- ★ Smoothed power supply 200-250 v. A.C. incorporated on chassis.
- ★ Specially designed for perfect reproduction of the **LONG PLAYING** as well as the standard record.
- ★ Brilliant reproduction on radio.
- ★ Long distance reception as clear as local stations.
- ★ **TWO YEARS' GUARANTEE.**
- ★ See our Loudspeaker list for suitable types of units.

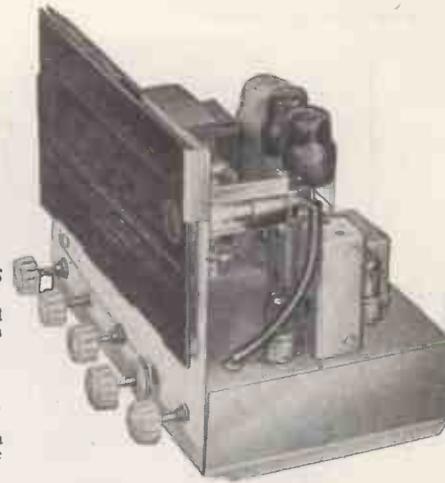


PRICE ONLY **22 GNS.**

H.P. TERMS £7/14/- deposit, 12 monthly payments of 29/-, CREDIT TERMS. Send 59/- to secure and eight monthly instalments of 59/-.
Carr. and pkg. 7/6.

Sole distributors of the
BURGOYNE
SOLDER GUN
79/6 Spare bits — 10 for 7/6

This 4 watt Amplifier...

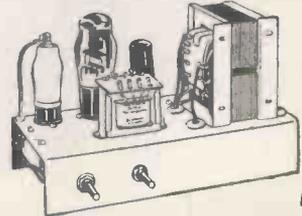complete with 3 valves, for use on A.C. mains, giving brilliant reproduction has been produced in very large quantities. Because of this we have a surplus quantity this month only, which we can offer at 79/6, carr. paid.



ONLY
79/6
Carr. Paid.

Ready to use

THE **BURGOYNE TONE CONTROL**

This unit provides a wide range of bass and treble control, without the need to re-adjust the main volume control when bass or treble are altered. The use of continuously variable controls is most necessary when dealing with unknown characteristics, for compensation of these can only be done by ear. As the characteristics of the human ear vary with intensity, the compensation required is a function of the loudness of reproduction.



70/- Complete and ready to use
Or nine monthly inst. of 11/-

PRE AMPLIFIER — A.7.


With a badly designed tone-control amplifier, the critical listener will find himself indulging in an orgy of knob twiddling which cannot be rationalised. This unit not only avoids introducing distortion into the reproduction, but precisely and easily overcomes the defects of the signal fed into it. The unit is supplied completely assembled and tested. A three-position input switch is incorporated:—
RADIO-78-33/45.

THE R.F.I. RADIO FEEDER UNIT

An inexpensive tuning unit using "straight" T.R.F. circuit tuning the Medium Wave Band only. It can be used with any amplifier. The unit is exceptionally sensitive and can be used in areas of only moderate signal strength.

By use of a T.R.F. circuit the bandpass is such that the output fed into an amplifier is of very high fidelity, and full advantage can be taken of the transmitted quality. The unit is provided with only two controls—Tuning and Sensitivity—and consequently is very simple to operate. No tuning scale is provided as it is thought that the great majority of constructors will prefer to fit the unit into a cabinet and so be able to choose an assembly to suit the housing. Adequate spindle length is provided in all cases.

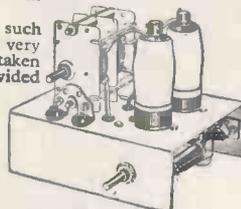The kit is complete in every detail, and the instruction manual fully detailed and illustrated.



COMPLETE KIT WITH
VALVES
£2.12.6
Instruction Manual only 2/-

Complete ready to use
Carr. and pkg. 3/6 **£3.12.6**


The **BURGOYNE HIGH FIDELITY**

CRYSTAL MICROPHONE
for Desk or Table use made by

RONETTE

only **55/-** post free

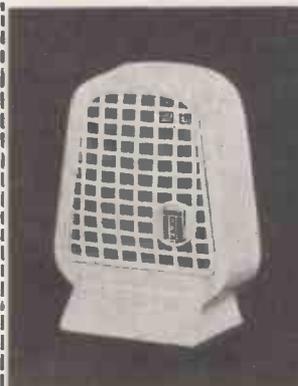This attractive microphone is housed in a cream plastic case with gold background as illustrated. Fitted with type DX12 crystal insert as used on the famous "CORONATION" microphone, the frequency response is 30-13,000 c/s, and the output level at 1,000 c/s, 1.3 mv. μ Bar in 5 Megohms.



E. & G.

MAIL ORDER

Telephone: MUSeum 6667.

THE RADIO CENTRE.

The M.O.S. PERSONAL CREDIT PLAN

★ Two methods of purchase are available:—CREDIT SALE OR HIRE PURCHASE. The first allows you to own your equipment on payment of a first instalment of nine which are spread over 9 months. We quote the first instalment as one-ninth of the total purchase price, but if you so desire the first instalment can be any sum you please (within reasonable limits).

★ The second method secures delivery on payment of one-third of the cash price and the balance plus charges spread over any period up to 18 months. Again, we quote payments spread over 12 months but this may be varied.

★ Our range of electronic equipment is unequalled by any other firm, and can be inspected at your leisure in our spacious modern showrooms. Here is a selection listed below.

★ Your enquiries and orders will be dealt with confidentially whether by mail or personal shopping. We have years of experience behind us to advise and help you on your choice of goods. Carriage and packing is extra, all prices quoted being ex warehouse and subject to market fluctuations. Comprehensive lists are available upon request.

★ We specialise in export and, having a world-wide market for our merchandise, we have had to create a special export packing department, which, having had long experience of all types of packing for all markets, will ensure that your order reaches you safely wherever you are.

★ Satisfaction is always guaranteed to our customers, no matter how small the order, it will be valued by us.

ITEM	CREDIT SALE OR H.P. TERMS			
	CASH PRICE	9 Mthly. Inst.	DEPOSIT	12 Mthly. Inst.
AMPLIFIERS AND ACCESSORIES				
Acoustical Quad II	£42 0 0	106/6	£14 0 0	53/6
Burgoyne A7 Pre-amp.	£3 10 0	11/-	£1 3 4	7/-
EMG steep cut filter	£4 10 0	14/2	£1 10 0	8/-
Leak point one	£28 7 0	72/-	£9 9 0	36/2
Leak varislope	£12 12 0	32/4	£4 4 0	17/4
Leak steep cut filter	£5 10 0	14/-	£1 16 8	9/3
Lowther A15F	£45 0 0	115/-	£15 0 0	58/4
Lowther master control	£20 0 0	51/-	£6 13 4	25/6
Rogers baby de Luxe	£14 0 0	35/6	£4 13 4	19/-
Rogers Junior pre-amp.	£9 0 0	24/6	£3 0 0	13/4
Grampian ENSA	£46 0 0	117/-	£15 6 8	59/6
TAPE RECORDERS AND ACCESSORIES				
Baird "Sound Master" Recorder	£68 5 0	171/-	£22 15 0	86/6
Editor Recorder	£47 5 0	120/-	£15 15 0	60/-
Ferrograph Recorder	£79 16 0	—	£26 12 0	100/-
Grundig Recorder	£84 0 0	213/-	£28 0 0	106/9
Grundig Console Recorder	£99 15 0	254/-	£33 5 0	126/3
Emicord	£94 10 0	242/-	£31 10 0	120/9
Sund PMR/3 Recorder	£99 15 0	254/-	£33 5 0	126/3
Sound Master KIT	£60 0 0	152/-	£20 0 0	79/-
Vortexion Recorder (Wearite Deck)	£84 0 0	213/-	£28 0 0	106/9
Lane Tape Desk	£17 10 0	42/10	£5 16 8	22/-
Truvox Tape Desk	£23 2 0	59/-	£7 14 0	29/-
Wearite Tape Desk 2A	£35 0 0	89/-	£11 13 4	46/6
Wearite Tape Desk 2B	£40 0 0	102/-	£13 6 8	51/1
Burgoyne Oscillator Unit	£1 17 6	7/-	£0 12 6	4/-
Lane Amplifier Kit.	£13 0 0	33/2	£4 6 8	17/9
Lane Amplifier	£15 10 0	39/6	£5 3 4	20/6
LOUDSPEAKERS				
WHARFEDALE				
W15CS	£16 0 0	41/-	£5 6 8	21/2
W15	£15 10 0	39/4	£5 3 4	20/7
Super 12CSAL	£16 0 0	41/-	£5 6 8	21/2
W12CS	£9 15 0	26/2	£3 5 0	14/2
W12	£9 5 0	24/8	£3 5 0	13/4
W10CS (B)	£12 6 6	31/10	£4 2 6	16/11
Golden 10	£7 13 3	21/8	£2 11 0	11/10
Bronze 10	£4 12 8	14/6	£1 10 11	8/2
Supr. 8CSAL	£6 13 3	19/5	£2 4 5	10/9
Super 8CS	£6 6 7	18/9	£2 2 2	10/1
Bronze 8	£3 3 11	11/5	£1 1 4	6/6
Super 5	£6 13 3	19/5	£2 4 5	10/9
W5	£2 0 0	8/6	£0 16 8	5/-
W.B.				
12in. Concentric Duplex (less transformer)	£22 11 0	57/11	£7 10 4	29/6
Ditto (with transformer)	£23 16 0	60/-	£7 19 0	30/9
10in. Concentric Duplex (less transformer)	£9 7 6	24/11	£3 2 6	13/9
Ditto (with transformer)	£10 15 6	28/-	£3 12 0	15/4
Tweeter Unit	£3 15 6	12/-	£1 5 0	7/6
HF610 High Fidelity	£2 10 6	9/-	£0 16 10	6/-
HF810 High Fidelity	£3 0 6	10/-	£1 0 2	6/6
HF912 High Fidelity	£3 7 0	11/-	£1 2 4	6/11
HF1012 High Fidelity	£3 13 6	12/-	£1 4 6	7/3
GOODMANS				
Axiom 22	£14 14 0	37/6	£5 4 0	19/2
Axiom 101	£6 12 1	19/2	£2 4 0	10/7
Axiom 102	£9 18 0	26/5	£3 6 0	14/4
Axiom 150	£10 5 6	27/-	£3 8 6	14/9
Axiom 60	£8 12 6	23/6	£2 17 6	12/11

ITEM	CREDIT SALE OR H.P. TERMS			
	CASH PRICE	9 Mthly. Inst.	DEPOSIT	12 Mthly. Inst.
TEST EQUIPMENT				
AVO				
Heavy Duty Meter	£15 0 0	38/-	£5 0 0	20/6
Model 7 or 40 Meter	£19 10 0	49/-	£6 10 0	26/6
Universal Minor	£10 10 0	27/6	£3 10 0	15/-
Signal Generator, Mains or Battery	£30 0 0	74/6	£10 0 0	39/-
Universal Bridge	£34 0 0	86/-	£12 0 0	42/-
Electronic Test Meter	£40 0 0	102/-	£13 6 8	50/-
Valve Characteristic Meter	£60 0 0	153/-	£20 0 0	75/-
D.C. Minor	£5 5 0	16/-	£1 15 0	9/2
Model 8 Meter	£23 10 0	60/-	£7 16 8	30/4
Leather cases for 7, 8, 40 and heavy duty meters	£3 0 0	9/6	£1 0 0	5/-
ADVANCE				
Audio Generator H.I.	£25 0 0	63/-	£8 6 8	33/-
Signal Generator E.2	£28 0 0	70/-	£9 6 8	36/6
Signal Generator J.I.	£35 12 0	90/-	£11 17 4	45/6
Signal Generator P.I.	£19 19 0	51/-	£6 13 0	25/6
TAYLOR				
20B Circuit Analyser	£15 15 0	40/-	£5 5 0	21/6
44A Montrose Meter	£2 10 0	8/9	£0 16 8	5/-
45B Valve Tester	£25 10 0	64/-	£8 10 0	32/6
66A Signal Generator	£22 10 0	58/-	£7 10 0	30/-
70A Universal Meter, 1,000 o.p.v.	£12 10 0	32/2	£4 3 4	17/3
71A Universal Meter, 1,000 o.p.v.	£12 10 0	32/2	£4 3 4	17/3
72A Universal Meter, 1,000 o.p.v.	£16 0 0	40/6	£5 6 8	21/2
75A Universal Meter, 20,000 o.p.v.	£15 0 0	38/-	£5 0 0	20/6
77A Universal Meter, 20,000 o.p.v.	£15 0 0	38/-	£5 0 0	20/6
85A/P Universal Meter, 20,000 o.p.v.	£19 10 0	49/-	£6 10 0	26/-
88A Universal Meter	£22 0 0	55/6	£7 6 8	27/11
90A Universal Meter	£15 15 0	40/-	£5 5 0	21/6
110C Bridge	£14 10 0	37/-	£4 10 0	20/-
120A Universal Meter, 20,000 o.p.v.	£9 0 0	24/6	£3 0 0	13/4
130A Insulation Circuit Tester	£15 0 0	38/-	£5 0 0	20/6
170A Electronic Test Meter	£24 0 0	61/-	£8 0 0	31/6
190A Audio Oscillator	£22 10 0	58/-	£7 10 0	29/-
240A Pattern Generator	£14 0 0	36/-	£4 13 4	19/-
260A T.V. Wobulator	£36 15 0	93/-	£12 5 0	46/-
COSSOR Tele-Check	£27 0 0	68/-	£9 0 0	35/-
Portable Oscillograph 1039	£29 0 0	72/3	£9 13 4	39/-
EVERSHED Wee-Megger	£20 14 0	52/-	£6 18 0	26/8
PULLIN Universal Test Meter Series 100				
RC Bridge/Valve Voltmeter	£40 0 0	102/-	£10 0 0	57/6
AMPLION D.C. Test meter	£5 0 0	15/-	£1 0 0	10/-
B.P.L. Foundation Meter 1m/a F.S.D. 3 1/2in.				
0-500 Microamps 3 1/2in. Meter (Flush Mfg.)	£3 10 0	11/9	£1 3 4	7/-
Universal Meter	£5 10 0	16/6	£1 10 0	10/-
Radar Kilovoltmeter	£3 17 6	12/9	£1 6 0	7/6
Denco Modulated Test oscilator MTO1	£3 15 0	12/9	£1 5 0	7/6

Carriage and packing extra
All prices are ex warehouse

SUPPLY COMPANY

33 Tottenham Court Rd., London, W.1 Telephone: MUSeum 6667



The
smallest
precision
soldering
instrument
you've
ever
seen!



(ACTUAL
SIZE)

- No fatigue . . . as light and easy to use as a pencil ($\frac{1}{2}$ oz.)
- Speeds production . . . heats up in 30 seconds.
- Safety first . . . for 6, 12 or 24 volts.
- Prevents damage . . . pin-point heat concentration for small assemblies.
- Robust construction . . . no ceramic or mica formers to break or flake.
- Fully reliable . . . in constant demand by the world's most famous manufacturers.
- Bit sizes: 3/16in., 5/32in., 3/32in. (interchangeable) and 1/16in.
- Consumption : 6, 8.3 or 12 watts.


ORYX

**MINIATURE
SOLDERING
INSTRUMENTS**

Sole Distributors:

ANTEX · 3 Tower Hill · London · E.C.3
Telephone: ROYal 4439

**Smith's
for
current
"know how"**

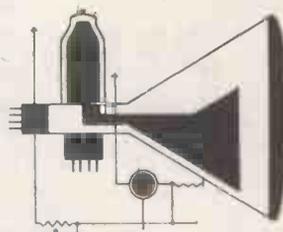

From Smith's shops and bookstalls you can quickly obtain technical books on the latest developments in circuit design, new components, methods and new theories. Books not actually in stock can usually be supplied within a day or so. Smith's Postal Service can send books to any address at Home or Overseas. Lists of the standard works on any subject gladly supplied upon request.

W. H. Smith & Son
FOR TECHNICAL BOOKS

HEAD OFFICE: STRAND HOUSE, LONDON, W.C.2



THE **EDDYSTONE** MODEL "608X"
PRICE £106


The 608X is a fifteen-valve superheterodyne receiver of advanced technique. 110/240 v. A.C. Continuous coverage from 30 M/cs. to 480 K/cs. 2 R.F. stages. Crystal filter. "S" meter. Noise limiter. Stabilised H.T. supply. Variable selectivity. Push-pull output. Accurately calibrated dial. Sensitivity better than 5 microvolts on all ranges. Numerous other features. Full specification gladly sent. This and all other models available on our convenient H.P. terms. Latest Eddystone Component Catalogue now ready, 1/-.



The
Eddystone
Specialists

RADIO SERVICES LTD.,
55 COUNTY ROAD, LIVERPOOL, 4
Telephone: AINTREE 1445 ESTAB. 1935

S.L.I.

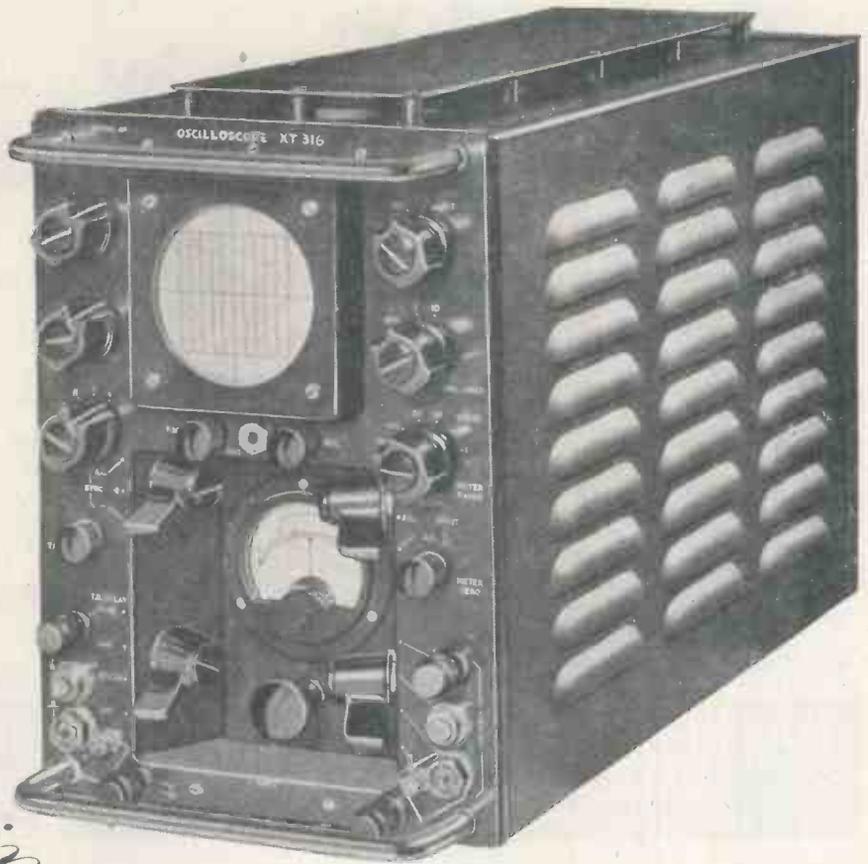

Now in quantity production

The New R.R.E./
Solartron Oscilloscope XT316 Model D300

Outstanding features:

- D.C. to 6 Mc/s.
- 1 μ sec. maximum sweep speed.
- Built-in calibrator.
- Video and T.B. delays.
- Y shift meter.
- Fully tropicalised.
- Weighs under 50 lbs.

Designed at the Radar Research Establishment this new oscilloscope incorporates the latest advances in circuit technique and construction. It is eminently suited to the display and accurate measurement of the velocity and amplitude of pulse waveforms encountered in radar and communications equipment. **£145**

Full Technical details sent gladly on request.

ORDER NOW FOR EARLY DELIVERY

SOLARTRON LABORATORY INSTRUMENTS LIMITED

SOLARTRON WORKS, QUEENS ROAD, THAMES DITTON. Tel: Emberbrook 5611 PBX



14 reasons why those concerned
with recorded sound choose

FERROVOICE

MAGNETIC RECORDING TAPE


- 1 Does not curl—lies flat on the transducer head, giving better frequency response, and smooth tracking.
- 2 Has the lowest possible surface friction—reducing wear on transducer heads, and guide pillars.
- 3 Has the best possible dispersion of oxide particles, free from coagulation, and flocculation ensuring low noise level.
- 4 Is correctly heat-dried to preclude "blocking" and sticking, layer-to-layer, under storage conditions.
- 5 The Lacquer is formulated to attain the maximum adhesion to the base material.

- 6 Gives the highest possible signal-to-noise ratio—excelling in high-frequency response.
- 7 Has a superlative dimensional stability—negligible stretch, and the highest possible tensile strength.
- 8 Discourages static collection during fast-forward, and fast re-wind operations.
- 9 The Kraft Paper base has been selected after careful development with the paper manufacturers—flexibility, and supercalendering being prime considerations.
- 10 The Lacquers are pigmented with the highest grade powder. The individual particle size is less than one micron (0.000039 inch).

- 11 The pigment is dispersed and milled, with the highest degree of control, thus ensuring a uniform dispersion of the oxide particles within the binder.
- 12 The spools were designed to incorporate the "universal" hub, perfect balance, and negligible rotation noise.
- 13 "FERROVOICE" products are subject to continuous development by our technical staff.
- 14 "FERROVOICE" has a Coercivity of 270 oersteds (BHC) remanence = 730 gauss, when subjected initially to a magnetising force of H = 2,000 oersteds.

Suitable for Single or Double Track Recording. Length 1,200ft. on 7in. Diameter Spool—Frequency response 50 C.P.S. to 10 kc/s. at 7.5 in. per sec. Breaking strain exceeds 4lb.

22/6 PRICE RETAIL

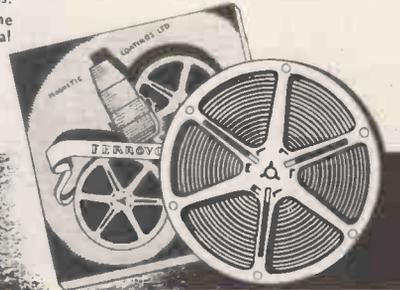

MAGNETIC COATINGS LIMITED

38 GROSVENOR GARDENS LONDON SW1 Telephone: SLOANE 9129
WORKS & LABORATORY: 25 DASHWOOD TRADING ESTATE
LARCH ROAD · LONDON · SW12 BALHAM 5579


REDUCE YOUR PRESS TOOL COSTS

**THE HUNTON UNIVERSAL BOLSTER OUTFIT
FOR SHEET METAL PIERCING AND
BLANKING ON FLY PRESSES**

Bolster Frame with 2 adjustable gauges and insertable steel Holders for Dies 1/2 in. to 3 1/2 in. bore diameter.



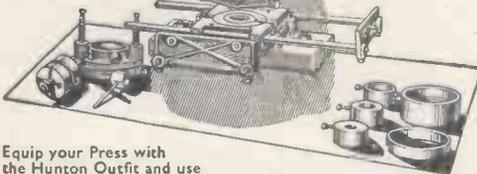Two Punch Holders with detachable positive-action Strippers take the complete range of Punches 1/2 in. to 3 1/2 in. diameter.



Equip your Press with the Hunton Outfit and use inexpensive standardised Punches and Dies 1/2 in. to 3 1/2 in. diameter, obtainable from stock—in 1/2 in. sizes—when required.

Standardised Tools also available at short notice for Square, Oblong and other shapes, Louvre Forming (up to 8in. long), Corner Notching, Corner Radiusing, Angle Iron Notching and Piercing, etc.

Get the Outfit now—Buy Punches, Dies and Tools as you need them.

Descriptive brochure and prices on request.

HUNTON LIMITED

Phoenix Works, 114-116, Euston Road, London, N.W.1
Telephone: EUSTON 1477-8-9 Telegrams: Untonexh, London



INSULATED SLEEVING

Heat, shock and moisture proof. Diameters from 0.5 mm. to 30 mm. in 36" lengths. It is manufactured in all colours and bi-colours.

SPICERS LIMITED

19 New Bridge St., London, E.C.4. Tel.: CENTral 4211

...more than you BARGAIN FOR!



In point of fact the reception you get when you fit one of these really powerful units in compact form is more proof that OSMOR "Q" Range Coilpacks provide quality and performance right out of proportion to their midget size and modest cost. They have everything that only the highest degree of long practised technical skill can ensure—extra selectivity, super sensitivity, adaptability. Size only 1½ x 3½ x 2½, with variable iron-dust cores and Polystyrene formers. Built-in trimmers. Tropicalised. Pre-aligned, receiver-tested and guaranteed. Only 5 connections to make. All types for Mains and Battery superhets, and T.R.F. receivers. Ideal for the reliable construction of new sets, also for conversion of the 21 Receiver, TR.1196, Type 18, Wartime Utility and others. Send today for particulars!

SEPARATE COILS: A full range is available for all popular wavebands and purposes. Fully descriptive leaflet and connection data available. Just note these "plus points":

- Only 1in. high
- Packed in damp-proof containers.
- Variable iron-dust cores
- Fitted tags for easy connection.
- Low loss Polystyrene formers.



With OSMOR

Lines—you're on the right lines!

A spotlight on another of the "specials" in the OSMOR "Q" Coil Range

45 K/C Tape Recorder
Oscillator Coil

TYPE QT8.

A centre tapped wave-wound coil as illustrated for TRUVOX and similar tape-decks. Single screw fixing. Fitted tags.

7/6 each



TWO for the Price of ONE

The NEW OSMOR CHASSIS CUTTER

An inexpensive but invaluable tool of entirely new design. Cuts two hole sizes with any one reversible punch and die; and can be operated with a spanner or tommy-bar. Blanks easily removed. For use on steel up to 18 s.w.g. Brass and Dural up to 16 s.w.g. Aluminium and Copper up to 14 s.w.g.



P. Pat.
11325/53

Type	Hole Sizes	} Illust. price list on request.
1	1in. x 1½in.	
2	¾in. x 1½in.	
3	¾in. x 1½in.	
4	1½in. x 2in.	

Tommy-bars available.

The OSMOR "JIFFY PUNCH"

For cutting smaller holes neatly and quickly with one blow of a light hammer.



P. Pat.
11324/53

Type	Hole Size	} Illust. price list on request.
A	¾in.	
B	¾in.	
C	¾in.	

For use on Steel up to 20 s.w.g. Brass and Dural up to 18 s.w.g. Aluminium and Copper up to 16 s.w.g.

DIALS

Type A. Glass DIAL ASSEMBLY (as illus.) measuring 7in. x 7in. (9½in. x 9½in. overall) mounts in any position on or above the chassis and works with any type of drive. Choice of two 3-colour scales—G1 (L.M.S.) or G2 (M.S.S.). Price complete 24/6. P. & P. 1/6. Pulley assembly for right angle drive if required 1/9. Escutcheon 4/-.



METAL DIALS

Overall size 5½in. sq. Printed area 4in. sq., as illustrated. Cream background, 3-colour. Type M1, L.M.S. waves. M2, L. & M. waves. M3, M. & 2/S. waves. Price 3/6 each. Pointer, 1/6. Drum, Drive, Spring and Cord for use with both types of dial, 3/2.



FREE!

Send 5d. (stamps) for fully descriptive literature including The really efficient 5-valve Superhet Circuit and practical Drawings, 6-valve ditto, 3-valve (plus rectifier) T.R.F. circuit, Battery portable superhet circuit, Coil and Coilpack leaflets, Chassis Cutter leaflet, and full radio and component lists, etc., etc.

We keep stocks of many radio components for use in published circuits, including:—

"WIRELESS WORLD" "No compromise" TRF Tuner. "Midget Mains Receiver." Sensitive 2-Valve Receiver. Television Converter (special coils in cans available), etc., etc.

"PRACTICAL WIRELESS"

Coronet Four; Beginners' Superhet; Modern High Power Amplifier 2; Attache Case Portable; R1155 Converter; A.C. Bandpass 3; Modern 1-Valver; 3-speed Autogram, etc.

Dear Reader,

We can't mention all our products here but shall be glad to receive your enquiries for Chassis, Tuning Condensers, Switches, Volume Controls and all other Radio Components. If it's top-quality components and a speedy, courteous service you are looking for—try Osmor. We really shall do our best for you.




Keep those small components—resistors, condensers, etc., neatly stored yet visible by using an

OSMOR "JAR-RACK"

(If you're a generous husband you'll buy one or two for your wife's larder, too—she will appreciate the extra space they make.) Holds any 1 lb. jam jars, with or without lids. Easily removed, cannot fall out. Just the thing for the tidy "HAM" or Radio Dealer. Type 1 for wall-fixing, 6/9 each, holds 8 jars. (Jars are not supplied but are easily obtained.) Length 24in. enamelled olive green. Type 2 (as illustrated) for screwing under a shelf, 5/9 each, holds 6 jars. Length 18in., enamelled green. Post and packing 1/- (either type).

OSMOR STATION SEPARATOR

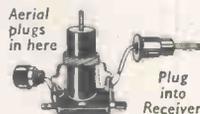

TYPE METRES

- 1 — 141-250
- 2 — 218-283
- 3 — 267-341
- 4 — 319-405
- 5 — 395-492
- 6 — 455-567
- 7 — 1450-1550
- 8 — 410-550 k/c

This is a device on the well-known "wave-trap" principle, which will reject an undesired signal when inserted in the aerial lead. The Separator may easily be tuned to eliminate any one Station within the ranges stated and fitting takes only a few seconds. Sharp tuning is effected by adjusting the brass screw provided. Complete with plug, socket and full instructions—nothing to add.

7/6 POST FREE Satisfaction guaranteed.

I.F.s. 465 k/c. Permeability-tuned with flying leads. Standard size 1½in. x 1½in. x 3½in. For use with OSMOR coilpacks and others, 14/6 pair. PREALIGNED, 1/6 extra.

OSMOR radio products ltd.

(Dept. W.51) 418, BRIGHTON ROAD, SOUTH CROYDON, SURREY.

Telephone : Croydon 5148/9

(Trade Enquiries Invited)



Series 20
2" Dial
Instrument

accuracy on a small scale

Pullin Miniature Instruments are of unique and robust construction. A new die-cast frame, integral with top bearing bridge-piece and centre iron, permits precision boring of the jewel mounting holes thus ensuring exact alignment of the coil. This gives an evenly balanced scale and a very high standard of accuracy is maintained.



INSTRUMENTATION BY

PULLIN

DYNAMOMETER TESTING SETS MULTIRANGE TEST SETS
MEASURING INSTRUMENTS PORTABLE TESTING INSTRUMENTS
INDUSTRIAL SWITCHBOARD INSTRUMENTS


MEASURING INSTRUMENTS (PULLIN) LTD.
ELECTRIN WKS., WINCHESTER ST., ACTON, LONDON, W.3
Telephone: Acorn 4651 & 4995. Telegrams: Mipulco. Ea'ux, London.

For your OWN-STYLED Cabinet!

'TELEMAX' (4ft. x 3ft.) PICTURE

PROJECTION
TELEVISION

CHASSIS

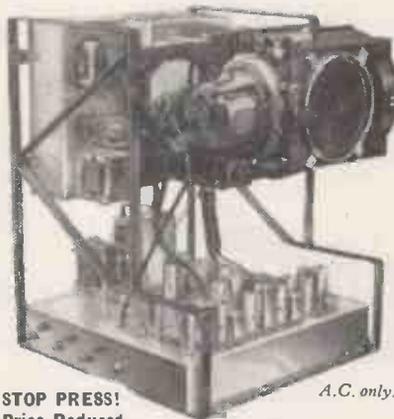

★ 23-valve s/h circuit.

★ Sensitivity better than 50 microvolts.

★ Full bandwidth.

★ 5-channel facility.

★ Complete with valves, c.r.t. and optical unit.

★ Ready for fitting.

★ Chassis size approx. 19" x 17" x 15".

STOP PRESS!
Price Reduced

A.C. only.

★ Detailed Specification from the Manufacturers :

TELEMECHANICS LTD

3 NEWMAN YARD, NEWMAN ST., LONDON, W.1. LAngham 7965

MANUFACTURERS OF

AUTOMATIC, HAND & STRIP WINDING MACHINES

SOLE AGENTS ABROAD

K. G. Khosla & Co., 1 Original Road (Opp. Paharganj Police Station), New Delhi 1, India.

Etablts Octave Houart, 14 Quai de L'Industrie, Sclessin-loz-Liege.

R. H. Cunningham, Pty., Ltd., 118 Wattletree Road, Armadale, S.E.3, Victoria, Australia.

Heitje & Frogg, Oslo, Norway, Storgaten, 15.

Technical & Industrial Services, P.O. Box 60, Claremont Cape Town.

YOUR ENQUIRIES ARE INVITED


ETA TOOL CO

(LEICESTER) LTD

29A WELFORD ROAD, LEICESTER

Phone 5386

for every type of coil

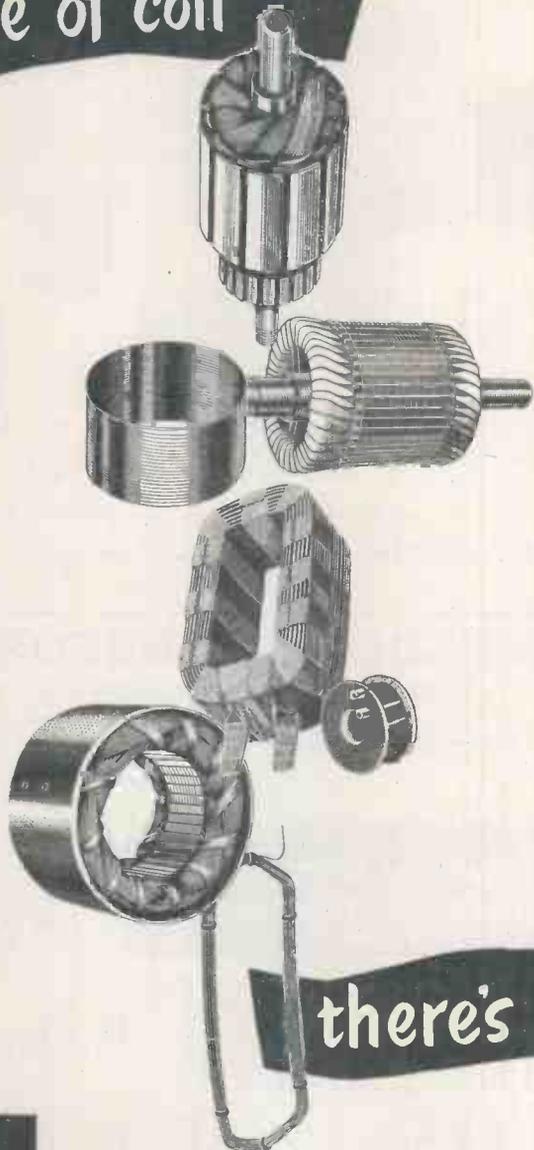

there's a

BICC

WINDING WIRE

USE OUR TECHNICAL ADVISORY SERVICE

If you are faced with a winding problem please ask for assistance; BICC technicians are always willing to give you the benefit of their experience. For most winding wire jobs the Publications listed will provide the data you require. They are available on request.

- No. 266 *Insulated Winding Wires and Strips.*
- No. 296 *"Bicaloc" Winding Wires (Self Bonding).*
- No. 303 *Enamelled Oil Base Winding Wires.*
- No. 322 *"Bicalex" Winding Wires (Synthetic Enamel).*
- No. 328 *"Fifty-Three" Enamelled Winding Wires.*

BRITISH INSULATED CALLENDER'S CABLES LIMITED



21 Bloomsbury St., London, W.C.1



*Several more good reasons
why our circle of friends keeps enlarging*

Air Cooled, Compound Filled and Oil Immersed Transformers for every requirement

A.I.D. Authority Ref. No. : 6489/53

WILLESDEN TRANSFORMER CO., LTD.,

2a FRITHVILLE GARDENS, SHEPHERDS BUSH, LONDON, W.12.

Telephone : SHEpherds Bush 5819

THE BRITISH NATIONAL RADIO SCHOOL

ESTD. 1940

**NOW IN OUR FOURTEENTH YEAR
AND STILL**

NO B.N.R.S. STUDENT HAS EVER FAILED

to pass his examination(s) after completing
our appropriate study course.

... and now
TELEVISION!

A.M.Brit.I.R.E. and CITY and GUILDS Radio and
Telecommunications Exams., etc., etc.

NOTE NEW ADDRESS :

PRINCIPAL
BRITISH NATIONAL RADIO SCHOOL
2, CANYNGE ROAD, CLIFTON, BRISTOL, 8
Tel. BRISTOL 34755

IF YOUR PROBLEM IS COIL IMPREGNATION

The BLICKVAC HIGH VACUUM IMPREGNATOR meets the rapidly growing demand for high-vacuum impregnation.



Full range of models available to meet the needs of

- ★ The large-scale Producer.
- ★ The Research Laboratory.
- ★ The small Rewind Shop.

**BLICKVAC UNITS MEET THE
MOST STRINGENT SPECIFI-
CATIONS.**

Outstanding features:

- ★ Ease-in Control.
- ★ Simple attachment of auxillary autoclaves.
- ★ Best quality fittings.
- ★ Fully demountable to facilitate cleaning.

UNEQUALLED FLEXIBILITY AND PERFORMANCE.

Units available for:

VARNISH
WAX

BITUMEN
POTTING RESINS

If your problem is Coil Impregnation

CONSULT BLICKVAC

Write today to

HAMILTON ROAD WORKS, HAMILTON ROAD, S.E.27

Associated with Blick Time Recorders Ltd., Blick Engineering Ltd.

NO EXTERNAL CHANNELLING EQUIPMENT !

Standard
six channel


V H F
ery igh frequency

radio link

type

FP11

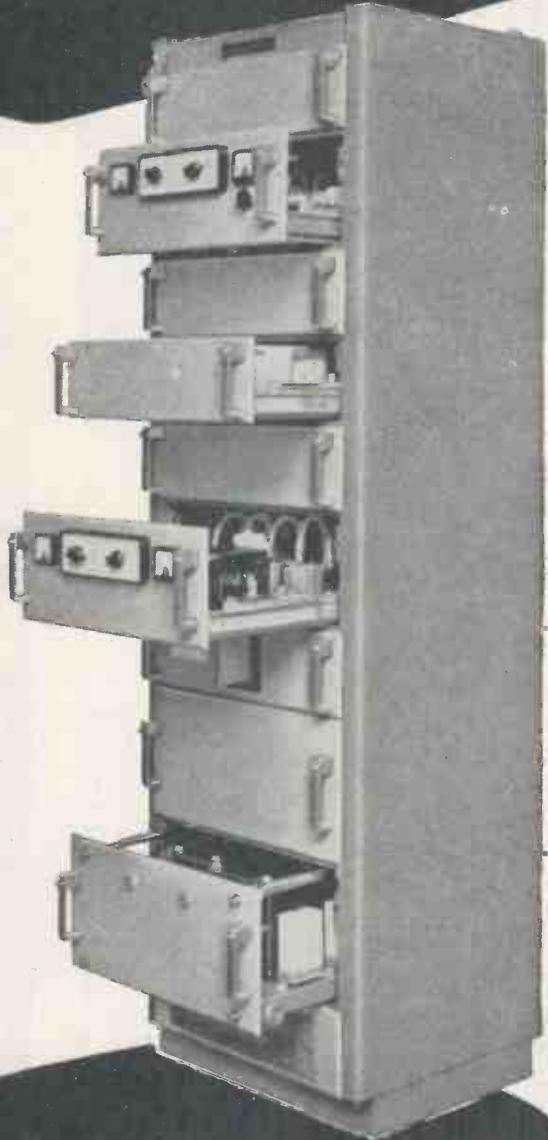Six Telephone or Teleprinter Channels,
plus Independent Order Wire Circuit.
Full Supervisory and Control Facilities.
Alternative Radio Frequency Band.



complete in one cabinet

available for
early delivery

Write for leaflet No. 198/6.



Standard Telephones and Cables Limited


Registered Office: Connaught House, Aldwych, London, W.C.2

RADIO DIVISION • Oakleigh Road • New Southgate • London • N.11

THE NEW



for
cheaper
radio listening

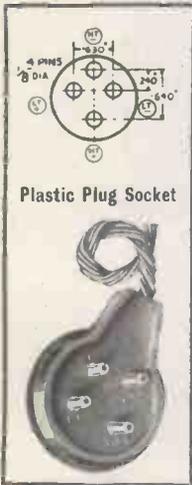

This new Ever Ready Battery, combining a 90 volt high tension unit and a 1.5v low tension section, has been designed for use with the latest Ever Ready low consumption valves, type DK96, DF96, DAF96 and DL96, which use only half the filament current (25mA) of the older series valves (50mA).

A balanced service life of 300 hours is obtained when the high tension current is 10.5 mA at 90 volts and the low tension current 125 mA at 1.4 volts; the respective cut-off voltages being 40v and 1.0v on load.

The maximum battery dimensions are 7 1/8" x 3 7/8" x 4" and the weight is 5 lbs. 10 oz. Price 16/-.


BATTERY PLUG

The new Ever Ready plastic 4 pin battery plug has been specially designed to ensure correct and easy battery connections. Plugs are fitted with four staggered metal pins, also four coloured wires 18" in length. List Price 2/- complete. Suitable for use with BSS. 1766-1951.



**EVER READY DRY BATTERIES FOR RADIOS
TORCHES · HEARING AIDS · CYCLE LAMPS**

HIGH FIDELITY REPRODUCTION

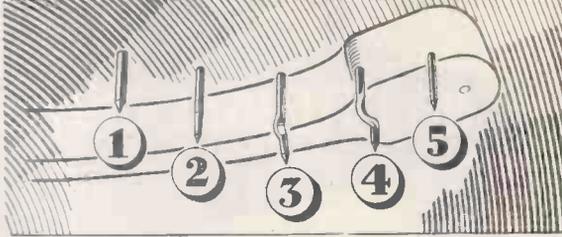

WITH A MINIMUM OF WEAR

Calls for the use of

S. G. BROWN PRECISION SAPPHIRE NEEDLES

- No. 1 "Miniature" Jewel-tipped needle for *Lightweight* pick-ups.
- No. 2 "Straight" Jewel-tipped needle for *Crystal* pick-ups.
- No. 3 "Trailer" Jewel-tipped needle for *Medium weight* pick-ups.
- No. 4 "Knee Bend Trailer" Jewel-tipped needle for *older type Heavy weight* pick-ups.
- No. 5 "Miniature Solid Sapphire" needle for *Lightweight* pick-ups.

PRICES (Subject to full Trade Discount)
Nos. 1-4, 7/-, plus 2/4 P.T. Post 6d.

No. 5, 9/3, plus 3/1 P.T. Post 6d.

There's an S. G. BROWN PRECISION SAPPHIRE NEEDLE for every type of PICK-UP

All S. G. Brown Precision Sapphire Needles are protectively mounted on a useful double-sided stroboscope (78 & 33-1/3 r.p.m.). An instructive and interesting Brochure with many useful hints on obtaining better reproduction gladly sent on request. Write to Dept. W.

S. G. Brown Ltd. SHAKESPEARE ST., WATFORD, HERTS.
Telephone: Watford 7241.

ACE
THE LAST WORD IN
TAPES RECORDERS

MODELS 10 & 12 HAVE EVERYTHING

- 10 WATTS PUSH-PULL HIGH FIDELITY AMPLIFIER
- 3 INPUTS; CRYSTAL & M/C. MICS. & GRAM.
- 3 TAPE SPEEDS; 3 3/4, 7 1/2 & 15 INCHES PER SECOND
- 2 TRACKS PER TAPE - 2 HRS. RECORDING
- 2 SEPARATE INPUT CONTROLS FOR MIXING
- COMPLETELY AUTOMATIC ERASE (ELECTRONIC)
- DETACHABLE SPEAKER UNIT MODEL 12
- FAST REWIND & FORWARD WIND
- MONITORED & DIRECT INPUTS
- VERY COMPACT MODEL 10 15 1/2" x 10" x 7 1/4"

SEND STAMP FOR FULLY ILLUSTRATED BROCHURE

MODEL 10 £65
MODEL 12 £66-10-0

Associated Cine Equipments Ltd.
353, BEXLEY ROAD, ERITH, KENT. Phone: Erith 2543.

A PRECISION SIGNAL GENERATOR BY ADVANCE

For the

**SERVICE
ENGINEER**



A high grade generator, in the Advance tradition, at a price that puts it within reach of every service engineer.

Employing standard signal generator technique, the P.I incorporates an up-to-the-minute oscillatory circuit with special screening and filtering so that even at 100 Mc/s leakage is less than 3 microvolts. The accurate attenuator system embodies a non-inductive slide wire followed by a five-position 75-ohm ladder network, and the correctly terminated 75-ohm cable obviates mis-match reflections and provides dummy aerial output voltages substantially those indicated by the attenuators.

The instrument is covered by the usual Advance guarantee. Write for fully descriptive leaflet No. W22.

LIGHTER
Weighs only 10 lb.

SMALLER
12 in. wide x 9 in. high x 6 in. deep.

COVERS
100 kc/s to 100 Mc/s
ON FUNDAMENTALS IN
SIX RANGES.

COMPLETE
with T.P. Pad and Dummy
Aerial, etc.
For 105-125, 210-250 V 40-
100 c/s.

The Advance
SIGNAL GENERATOR

TYPE PI

**COSTS
ONLY
19 GNS
(LIST)**

Special models available:

PI/M for 105-125 volts, 140-160 volts,
210-250 volts, 40-100 c/s.

PI/NA for 117 volts, 25-60 c/s.

The best of Tape Recorders – and an INDEPENDENT P.A. AMPLIFIER *as well!*

★ **TO THE TRADE:**
Ask for details of special Dealer facilities and Information Sheet T1/6

One of the many features of the SIMON Portable Tape Recorder is the provision of facilities for entirely independent use of the amplifier for public address, record reproduction, etc. at 10 watts output power.

This versatile and brilliant Recorder was designed for the user who expects—and appreciates—the best.

Two hours' recording time. Twin tracks, two speeds. Frequency response: 50-12,000 c/s at 7½ in./sec. and 50-7,000 c/s at 3½ in./sec. Bass and treble independently variable.



-
- SIZE 18 in. x 15 in. x 10 in.
 - LOUDSPEAKER 6½ in. built-in monitor
 - POWER SUPPLY 200/250v. 50 Cycles A.C.
 - INPUT CHANNELS ... High impedance for microphone; low or high impedance for radio
 - POWER CONSUMPTION 100 watts approx.



Portable TAPE RECORDER

Ask for
"THE GENTLE ART OF TAPESMANSHIP"
and Information Sheet T1/6
SIMON SOUND SERVICE LTD. (Dept. W)
48-50 GEORGE ST., LONDON, W.1. Phone: WELbeck 2371

- ★ Monomaster "Finger-tip" Control
- ★ Separate capstans
- ★ Three motor drive
- ★ Fast rewind and wind-on.
- ★ Provision for Remote Control.
- ★ Drop-in loading.

SIMON for
Sound Recording
at a
Sensible Price

TWO AND SIX!

This small sum will bring you on 50 glossy art pages* full information enabling you to build ALL of the following high-class equipment.

- ★ 3-VALVE 3-BAND SUPERHET. FEEDER UNIT.
- ★ 4-VALVE 3-BAND SUPERHET. "NORM./HI-FI/GRAM." FEEDER UNIT.
- ★ 4-VALVE 3-BAND A.C. SUPERHET. ("CORONET.")
- ★ 5-VALVE 3-BAND A.C. SUPER. (with Gram.)
- ★ 5-VALVE 3-BAND A.C./D.C. SUPERHET.
- ★ 6-VALVE 3-BAND A.C. SUPER. (with Gram.)
- ★ 6-VALVE 3-BAND A.C./D.C. SUPER. (with Gram.)
- ★ 3-VALVE 2-BAND "LOCAL STATION" T.R.F. SUPER QUALITY FEEDER UNIT, ETC.
- ★ FEEDER AMPLIFIER AND POWER PACK.
- ★ MAGIC EYE TUNING INDICATOR UNIT.
- ★ SIGNAL TRACER A.C.
- ★ 5-WATT QUALITY AMPLIFIER A.C. with NFB.
- ★ 10-WATT P-P QUALITY AMP., A.C. with VAR. NFB.
- ★ SIGNAL GENERATOR, A.C. ETC., ETC.

Our completely NEW 1954 HOME CONSTRUCTORS HANDBOOK contains constructional details, large blueprint circuits, complete parts lists and technical descriptions of these famous outfits, as well as Set Building Hints, Servicing Hints, Facts and Formulae, Resistance Colour Code, Symbols, etc., etc. AND our current Catalogue. **WHAT MORE COULD YOU WANT FOR ONLY HALF-A-CROWN? SO DON'T DELAY, SEND FOR YOUR COPY TO-DAY!!**

* Printed on glossy art paper, and now enlarged to 50 9in. x 5½in. pages, this latest issue of our famous book is packed solid from cover to cover with information YOU want!

OVER 60,000 COPIES NOW SOLD!

RODING LABORATORIES
(Dept. WW3), BOURNEMOUTH AIRPORT, CHRISTCHURCH.

URGENT "PER RETURN" ATTENTION, IS A NORMAL PART OF OUR SERVICE TO ALL RADIO DEALERS AND TRADE SERVICE ENGINEERS

AT TO-DAY'S KEENEST TRADE PRICES we are comprehensive stockists of quality condensers, resistors, potentiometers, transformers, valves and engineers' sundries of all kinds.

STOCKISTS OF "HOME CONSTRUCTOR" KITS

"Sound Master" Tape deck and amplifier. "Truvox Mark III Tape Deck" and amplifier components. "View Master" and Tele-King Televisor Kits, etc.

FAST TRADE SERVICE GIVEN ON REPAIRS to loudspeakers and transformers. Special Transformers to own specs.

A.W.F. CONE ASSEMBLIES

for L/S repairs in your own workshops at economical rates

BUYERS OF SURPLUS STOCKS OF BRAND NEW COMPONENTS & VALVES. SEND US YOUR OFFERS.

TRADE LISTS for 3d. stamp (2/- overseas air mail) "We know the export business".

A.W.F. RADIO PRODUCTS
TATLER CHAMBERS, BRADFORD I.

Phone 24008.

Cables "Testube"



MAGNETIC MATERIALS

Extensive research and manufacturing facilities have established Mullard as the leading producers of magnetic materials. They were the first, for example, to introduce Ferroxcube, the world's most efficient magnetic ferrite; 'Ticonal' anisotropic permanent magnets, renowned for their high stability and high energy output; and Magnadur, an entirely new type of permanent magnet with the insulating properties of a ceramic.

The wealth of experience gained from these developments is available to all users of magnetic materials through the Mullard advisory service. An enquiry to the address below will put a team of specialised engineers at your disposal.



Mullard

· 'TICONAL' PERMANENT MAGNETS · MAGNADUR (Formerly Ferroxdure)
 PERMANENT MAGNETS · FERROXCUBE MAGNETIC CORE MATERIAL

MULLARD LTD., COMPONENT DIVISION, CENTURY HOUSE, SHAPTESBURY AVENUE, LONDON, W.C.2.


Mullard Ferroxcube being extruded into rods for H.F. cores.

ADCOLA

PRODUCTS LIMITED
(Regd. Trade Mark)


**SOLDERING INSTRUMENTS
& ALLIED EQUIPMENT FOR
THE PRODUCTION LINE
& HOME CONSTRUCTOR**

**S
O
U
N
D
J
O
I
N
T
S**

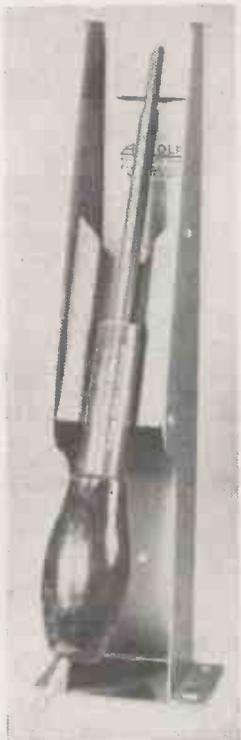

$\frac{3}{16}$ " Bit.

**F
O
R
S
O
U
N
D
E
Q
U
I
P
M
E
N
T**

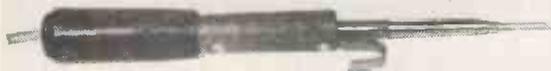

$\frac{1}{8}$ " Bit Instrument Model


**SUPPLIED IN ALL VOLT RANGES
STANDARD VOLTAGES STOCKED
6/7, 12/13, 22/24, 50/55, 100/110, 200/20,
230/50**

**"ADCOLA" PVC & POLYTHENE
ELECTRICAL CABLE
STRIPPERS ALSO AVAILABLE
IN ALL VOLT RANGES.**

WRITE FOR CATALOGUES

ADCOLA PRODUCTS LTD.

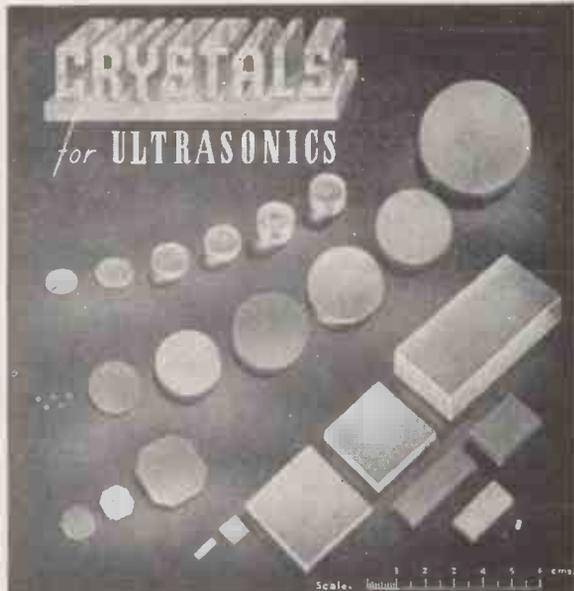Sales Offices & Works: CRANMER COURT, CLAPHAM
HIGH ST., LONDON, S.W.4. MA Caulay 4272



Quartz Crystals of any shape and size cut and ground precisely to specification and coated, if required, with Gold, Silver, Aluminium or Rhodium, etc.

BROOKES CRYSTALS LTD.


Suppliers to Ministry of Supply, Home Office, B.B.C., etc.

EARLSWOOD STREET, GREENWICH, LONDON, S.E.10
Phone: Greenwich 1828

Grams: Xtals Green, London.

Cables: Xtals, London.

SCREENED CONNECTORS

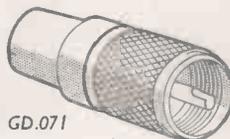

GD.071


for cables of 0.2" to 1.03" O.D.

Single and multi-way types.


Special types fitted with coupling rings.

Cable joining connectors.


U.S. Type Connectors
as illustrated.

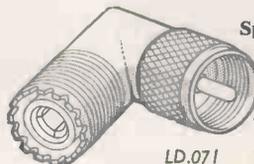

LD.071

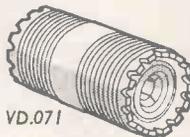

VD.071

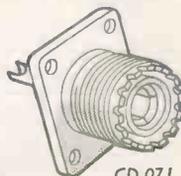

CD.071



RD.07/05

CABLE O.D.	TYPE	CODE NO.
0.41"	Straight plug	GD.071
0.25"	Reducing adaptor	RD.07/05
0.2"	Reducing adaptor	RD.07/03
fits on GD.071, CD.071, VD.071	Elbow plug adaptor	LD.071
fits on GD.071, LD.071	Bulkhead (Junction) adaptor	VD.071
fits on GD.071, LD.071	Chassis receptacle	CD.071

Other Transradio specialised products:


CO-AX air-spaced articulated

Very Low Loss Cables.

Microdual Two-speed Precision Drives.

TRANSRADIO LTD

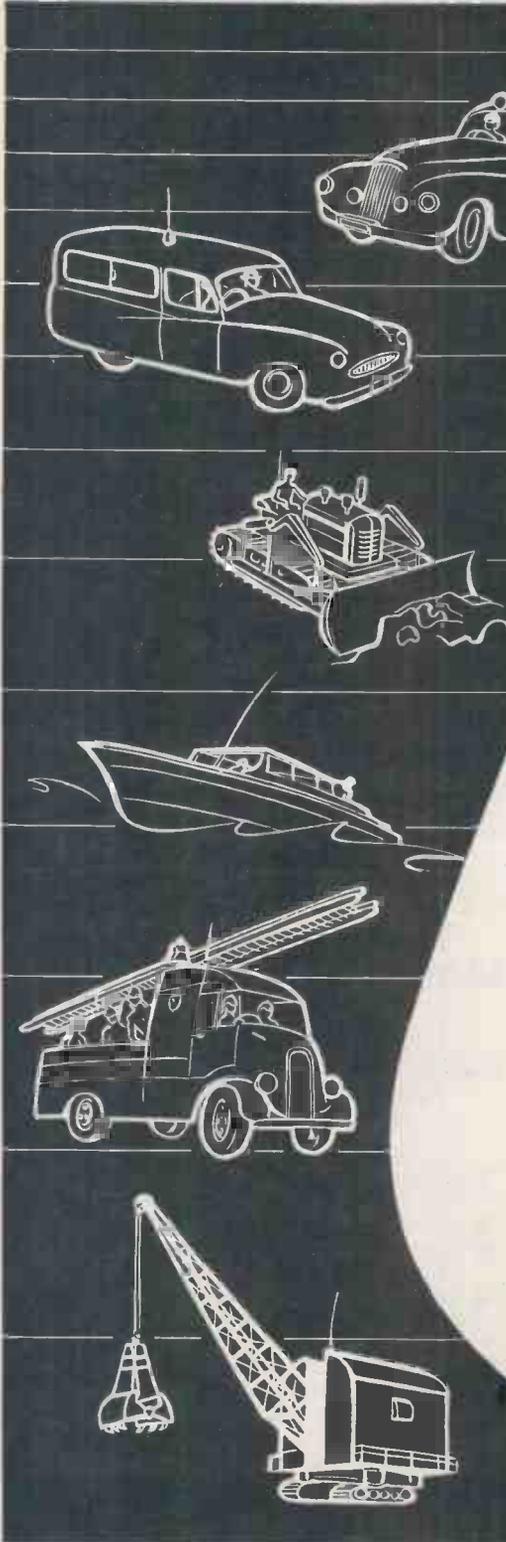138A CROMWELL ROAD, LONDON, SW7,
ENGLAND Telephone: FREmantle 4421 (P.B.X.)



B.C.C.

MOBILE EQUIPMENT


combines the unmatched performance and reliability with ease of maintenance and simplicity of operation.

VERSATILE IN USE

has many applications where central control, unrestricted mobility and immediate action are important.

Once again B.C.C. sets the standard for reliability and efficiency.

WE PRESENT

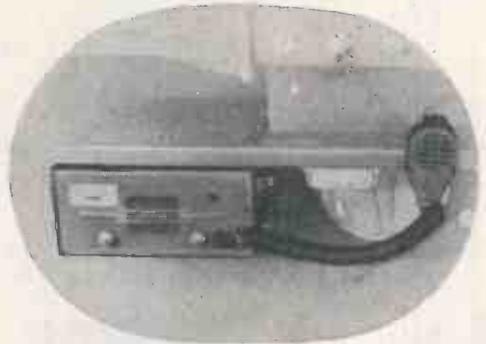

**THE NEW VHF
TRANSMITTER RECEIVER
TYPE 68**

Frequency Ranges : L75—100 Mc/s.
LH100—135 Mc/s.
H115—156 Mc/s.
HH156—186 Mc/s.

Transmitter Power Output : 5 watts

Receiver Sensitivity : 1 microvolt for 12 db.

Spurious Response : Better than —80 db.



BRITISH COMMUNICATIONS CORPORATION LIMITED

Second Way, Exhibition Grounds, Wembley, Middlesex. Telephone : Wembley 1212

LONGEST SCALE - SMALLEST SPACE



This compact, robust D.C. Milliammeter is flush mounting and is ideal for use in restricted space.

SCALE LENGTH : 9"

RANGE FROM 0-500 μ A

**The meter with the
dead beat movement**

The meter measures only 5" across and the depth behind the panel is only 2" yet it retains a scale length of 9". It is available with spade or knife-edge pointer and special scales can be supplied to customers' specification if required. Send for prices and full details.

BRITISH PHYSICAL LABORATORIES

Radlett, Herts



Tel : Radlett 5674/5/6

LONDON STOCKIST : M. R. SUPPLIES LTD., 68 NEW OXFORD STREET, LONDON, W.C.1

dm BP.19



This BLUEPRINT
is Morane^{*}
PROTECTED

Cut your cost by protecting Blueprints, Notices, Documents, Bookcovers, Charts, Drawings and all printed matter with Morane Transparent Heatsealing Plastic Skin.

Plastic material now available for lamination of identification cards, Calendars, Price tickets, etc.

- Washable high gloss surface.
- Instantaneous firm bond to paper, cardboard, etc.
- Can be fixed by unskilled labour.


SEND NOW FOR FULL DETAILS OF

*** Morane Transparent
HEATSEALING PLASTIC SKIN**

21 WOODTHORPE RD. - ASHFORD - MIDDLESEX

Tel.: Ashford Mddx. 2727 and 3391

THE GOLDRING MAGNA CARTRIDGE

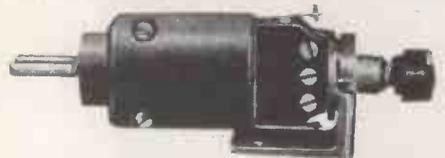

- A magnetic Turnover Cartridge with high output and cantilever styli.
- Entirely new principle. (Pat. app. for.)
- Output comparable to crystal pickups.
- Cantilever styli give minimum record wear and eliminate needle-talk.
- Styli easily replaceable.
- Smooth extended frequency response on both standard and L-P. records.
- The ideal replacement Cartridge for 3-speed record changers and units.

Of special interest to the designer of new equipment.

Write for full technical information to:—

**THE GOLDRING MANUFACTURING CO.
(Great Britain) Ltd.**

49-51a. DE BEAUVOIR ROAD, N.1

Telephone: CLIssold 3434-5-6

The specification

OUTPUT IMPEDANCE

Standard Model 20 ohms

SENSITIVITY

(20 ohms imp) -87db with respect to 1v/microbar (HI-Z) -55db ditto.

FREQUENCY RESPONSE 50-10,000 c/s, ± 5 db.

DIMENSIONS Overall length $3\frac{3}{8}$ " ; Max. dia. 3".

WEIGHT (incl. 10ft. screened cable) 14 ozs., with transformer 16 ozs.

FINISH Polychromatic Old Gold, Front cover and base anodised, dyed gold. Or grey crackle and chromium.

Incorporating recessed 'ON/OFF' switch.



The presentation

The price

£7·7·0

with built-in matching transformer providing 200 ohms, 600 ohms and Hi-Z impedances 30/- extra.

The outstanding characteristics of the Z33—its high sensitivity, its wide range and even response, combine to make this microphone unique in its many applications. It is essentially an instrument suited to obtain the very best possible reproduction from any commercial or home-built tape or disc recorder. By the same token it is ideal for P.A. work and for sound dubbing on cine film. And its attractive appearance is an added claim for its use in office and works 'intercom' systems. Full details in Folder W/M gladly sent on request.

GOODMANS *The masters of HI-FI*



GOODMANS INDUSTRIES LTD., AXIOM WORKS, WEMBLEY, MIDDX.

Telephone : Wembley 1200 (8 lines)

MAINS TRANSFORMERS

**FULLY INTERLEAVED
SCREENED AND IMPREGNATED, ALL GUARANTEED.
ALL PRIMARIES ARE 200/250 v. Half Shrouded.**

HSM63 (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps.	16/3
HS63 . Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps.	16/6
HS40 . Windings as above. 4 v. at 4 amps., 4 v. at 2 amps.	16/6
Output	
HS2 . 250-0-250 v. 80 m/a.	19/-
HS3 . 350-0-350 v. 80 m/a., 19/-.	19/-
HS2X . 250-0-250 v. 100 m/a., 21/-.	21/-
HS75 . 275-0-275 v. 100 m/a.	21/-
HS30X . 300-0-300 v. 100 m/a., 21/-.	21/-
HS3X . 350-0-350 v. 100 m/a.	21/-

Fully Shrouded

FSM63 (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. 2 amps.	26/9
Output	
FS2 . 250-0-250 v. 80 m/a.	21/-
FS30 . 300-0-300 v. 80 m/a., 21/-.	21/-
FS2X . 250-0-250 v. 100 m/a., 23/-.	23/-
FS75 . 275-0-275 v. 100 m/a.	23/-
FS30X . 300-0-300 v. 100 m/a., 23/-.	23/-
FS3X . 350-0-350 v. 100 m/a.	23/-
All the above have 6.3 4.0 v. at 4 amps., 5.4-0 v. at 2 amps.	
FS43 . Output 425-0-425 v. 200 m/a., 6.3 v. 4 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded	47/6
FS50 . Output 450-0-450 v. 250 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded	67/6
F35X . Output 350-0-350 v. 250 m/a., 6.3 v. 6 amps., 4 v. 8 amps., 4 v. 3 amps., 0.2-6.3 v. 2 amps. Fully shrouded	65/-
FS160X . Output 350-0-350 v. 160 m/a., 6.3 v. 6 amps., 6.3 v. 3 amps., 5 v. 3 amps. Fully shrouded	44/-
FS43X . Output 425-0-425 v. 250 m/a., 6.3 v. 6 amps., 6.3 v. 6 amps., 5 v. 3 amps. Fully shrouded	63/6
HS6 . Output 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. For receiver R1355. Half shrouded	26/6
HS150 . Output 350-0-350 v. 150 m/a., 6.3 v. 3 amps., C.T. 5 v. 3 amps. Half shrouded	27/9
F36 . Output 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. Fully shrouded	29/6
FS120 . Output 350-0-350 v. 120 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 2 amps., C.T. 5 v. 3 amps. Fully shrouded	29/9
FS256 . Output 250-0-250 v. 80 m/a., 6.3 v. at 6 amps., 5 v. at 3 amps. Fully shrouded	28/6
PR1/J1 . Output 230 v. at 30 m/a., 6.3 v. at 1.5/2 amps.	21/-
FS150 . 350-0-350 v. 150 m/a., 6.3 v. 4 amps., 5 v. 3 amps.	31/6
FS150X . Output 350-0-350 v. at 150 m/a., 6.3 v. at 2 amps., C.T. 6.3 v. at 2 amps., C.T. 5 v. at 3 amps. Fully shrouded...	31/6

The above have inputs of 200/250 v.

OUTPUT TRANSFORMERS

MIDGET OP . 5,000Ω to 3Ω	3/9
8,000Ω to 3Ω	3/9
MOP1 . Ratios, 26, 46, 56, 66, 90, 120-150 m/a. max. current. C.T. for Q.P.P. Class B, etc. Secondary 2/4 ohms. Top panel, and clamped, each	5/6
OP10 . 10/15 watts output, 20 ratios on Full and Half Primary	17/9
OP30 . 30 watts output, 20 ratios on Full and Half Primary	25/9
Williamson's O.P. Transformer to Author's specification...	£4/4/-
Chokes for Williamson's Amplifier, 30 H. at 20 m/a.	16/6
10 H. at 150 m/a.	32/-

FILAMENT TRANSFORMERS

All 200/250 v. Input.

F3 . 6.3 v. @ 3 amps.	9/6
F4 . 4 v. @ 2 amps., 7/6.	7/6
F6X . 6.3 v. @ 0.3 amps., 5/6.	8/-
F12X . 12 v. @ 1 amp.	8/-
FU6 . 0-2-4-5-6.3 v. @ 2 amps., 10/-.	16/6
F12 . 12.6 v. tapped 6.3 v. @ 3 amps.	16/6
F24 . 24 v. tapped 12 v. @ 3 amps.	23/6
F29 . 0-2-4-5-6.3 v. @ 4 amps., 18/9.	17/6
FU12 . 0-4-6.3 v. @ 3 amps.	17/6
FU24 . 0-12-24 v. @ 1 amp.	17/6
FS . 6.3 v. @ 10 amps. or 5 v. @ 10 amps., or 12.6 v. @ 5 amps., or 10 v. @ 5 amps.	34/-
F6/4 . Four windings at 6.3 v. tapped 5 v. @ 5 amps. each, giving by suitable series and parallel connections up to 6.3 v. @ 20 amps.	51/6

Quotations, etc.—stamped addressed envelope, please

C.W.O. (add 1/6 in £ for carriage).

Export enquiries invited.

**H. ASHWORTH (Dept. WW),
676, Gt. Horton Road, Bradford, Yorks.**

**Accepted as
the Standard..**

... by leading manufacturers, the trade and the aircraft industry.




**DC/AC
CONVERTERS**

Units Complete and ready for use

Specialists in Converters since 1937

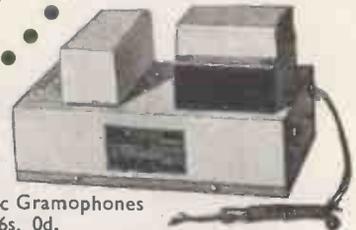Please ask for our descriptive folder W.W.



- for Electric Gramophones from £8 16s. 0d.
- for Radios, Radiograms, and Autochange Radiograms (Inc. 3-speed motors) from £11 16s. 6d.
- for Television, Tape Recorders, and for operation of TV from Country House lighting plants, price according to instrument.
- Inputs, 6, 12, 24, 32, 50, 110 or 200/250V. D.C.
- Outputs, 110V. or 230V. 50 or 60 c/s.

VALRADIO LTD. NEW CHAPEL ROAD, HIGH STREET
FELTHAM, MIDD.X. Tel.: FELtham 4242
Service Dept.: 57 Fortress Road, London, N.W.5. GULliver 5164 and 7202
Scottish Depot: 257 Gorbals Street, Glasgow, C.5 Tel.: South 1326
Overseas enquiries to nearest E.M.I. Organisation Depot

ASK ARTHURS FIRST

Send your enquiries for all Radio and Electrical goods, especially those in short supply.

★ **NEW VALVES**

We have probably the largest variety of valves in the country. Let us know your requirements.

AVO METERS IN STOCK

Avo Model 7.....	£19 10 0
Avo Model 8.....	£23 10 0
Signal Generator, Mains and Battery Models	£30 0 0
Electronic Test Meter.....	£40 0 0
Valve Characteristics Meter.....	£60 0 0

Also full range **TAYLOR METERS**. List on request.

VALVE MANUALS

Mullard	5 0
Osram	5 0
Brimar Nos. 4 & 5	5 0
each	
Mazda, Part 2.....	2 0
Mullard Valve Replacement Guide	3 6
Art and Science in Sound Reproduction by F. H. Brittain, D.F.H.	2 6
Postage 6d. each extra.	

Leak Point I Amplifiers	£28 7 0
Leak Pre-Amplifiers	£9 9 0
Leak Tuning Unit	£35 6 3
Wearite Tape Deck ...	£35 0 0
Grundig Tape Recorder two-speed	£84 0 0
Recording Tapes: E.M.I., G.E.C. and Scotch Boy, 35/- each.	
Ferrovoice Tape, 1,200ft. on 7in. spool 22/6 (plus 9d. postage).	
Terms C.O.D. or Cash with order. Goods offered subject to being unsold and to price alteration.	

Arthur's
EST. 1919

PROPS: ARTHUR GRAY, LTD.

GRAY HOUSE, 150-152 CHARING CROSS ROAD, LONDON, W.C.2
TEMPLE Bar 5833/4 and 4765. Cables: TELEGRAY, LONDON

THE ELAC "DUOMAG" FOCALISER



THE SENSATIONAL NEW ELAC T/V COMPONENT

The DUOMAG focaliser gives precision beam focus and complete picture positioning with minimum effect on scan coils and ion trap assemblies. It is designed for use with magnetically focused tubes having 38 m/m diameter necks.

DUOMAG is a permanent magnet type unit using two concentrically mounted Sintered Oxide ring magnets arranged with opposed magnetic fields.

- Minimum stray magnetic field. Symmetrical, uniform and very low external field.
- Magnets of high electrical resistivity enable the unit to be placed in close proximity to high efficiency scan coils.
- All insulated construction—No risk of high voltage shock.
- Wide range picture shift.

RETAIL PRICES IN U.K.

Low Flux, 37/6 ; Med. Flux, 39/6 ; High Flux, 42/-.

*Leading the
field in TV
components*



ELECTRO ACOUSTIC INDUSTRIES LTD

STAMFORD WORKS. BROAD LANE. TOTTENHAM. N.15 TEL: STAMford Hill 5606-8

Extract of letter from Sumatra

SOUND REPRODUCTION by G. A. Briggs

Enlarged and Revised 3rd Edition. 368 pages, 315 illustrations. Many new chapters; up-to-the minute advice and information. 17/6 (plus 1/- for postage). De Luxe Edition 25/- (plus 1/- for postage).

LOUDSPEAKERS by G. A. Briggs

3rd Edition 9th impression. 88 pages, 36 illustrations 7/6 (plus 3d. postage).

AMPLIFIERS by G. A. Briggs & H. H. Garner

Fine Art paper. Bound full rexine. 216 pages. 174 illustrations. 15/6 (plus 6d. for postage). De Luxe edition 21/- (plus 9d. postage).

PIANOS, PIANISTS & SONICS by G. A. Briggs

192 pages, 162 illustrations. 10/6 (plus 6d. post.)

Sold by leading Radio Dealers and Booksellers. Published by

Wharfedale

WIRELESS WORKS LTD.

BRADFORD RD., IDLE, BRADFORD, YORKS. 'Phone: Idle 1235/6. 'Grams: Wharfdel Idle, Bradford.

H. MULLER
B.P.M.
Pladju—Sumatra
Indonesia 11.12.53

Dear Mr. Briggs,

Although a chemical engineer by profession and as such completely unfamiliar with radio whenever it gets more complicated than Ohm's Law, I have nevertheless dabbled in High Fidelity. As a result of the circulation of your books ("Loudspeakers"—"Sound Reproduction" and "Amplifiers") we in Pladju have been making scores of sandfilled panels and those of my friends with an old-fashioned authority over their wives have even managed to knock holes in the walls of their, or rather the Company's houses. I have already a very good Wharfedale Golden in the proper sand-filled corner panel. I hope I am not bothering you too much with some further questions



METERS

LARGE AND VARIED STOCKS AVAILABLE FOR IMMEDIATE DELIVERY

EXAMPLES FROM OUR RANGE OF 2½ inch FLUSH PATTERN (as illustrated)

50-0-50	Microamps	Moving Coil
100-0-100	"	" "
250-0-250	"	" "
500-0-500	"	" "
1-0-1	Millamps	" "
0-100	Microamps	" "
0-200	"	" "
0-300	"	" "
0-400	"	" "
0-500	"	" "
0-1	Millamps	" "
0-25	"	Moving Iron
0-50	"	" "
0-100	"	" "


We can supply meters with NON-STANDARD, CURRENT and VOLTAGE RANGES to any specification. DELIVERY 7-14 days.

ANDERS ELECTRONICS LTD.
91, HAMPSTEAD ROAD, LONDON, N.W.1.

Telephone: EUSton 1639

Suppliers to Government Departments, B.B.C.,
Leading Manufacturers & Research Laboratories

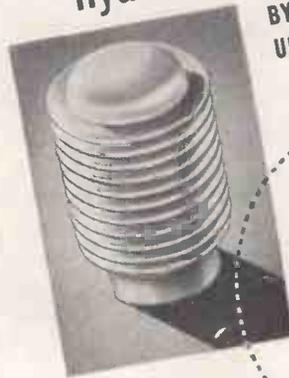hydraulically formed
BY A PROCESS
UNIQUE IN THIS COUNTRY



COMBINING THE PROPERTIES OF

1. A compression spring capable of repeated flexing
2. A container which can be hermetically sealed
3. A packless gland

for Automatic coolant regulation: Movement for pressure change: Packless gland to seal spindle in high vacua: Reservoir to accept liquid expansion: Dashpot or delay device: Barometric measurement or control: Pressurised couplings where vibration or movement is present: Dust seal to prevent ingress of dirt: Pressure reducing valves: Hydraulic transmission: Distance thermostatic control: Low torque flexible coupling: Pressure sealed rocking movement: Pressurised rotating shaft seals: Aircraft pressurised cabin control: Refrigeration expansion valves: Thermostatic Steam Traps: Pressure amplifiers: Differential pressure measurements: Thermostatic operation of louvre or damper.

Write for List No. N.800-1

B13

DRAYTON metal bellows

The Drayton Regulator and Instrument Co. Ltd., West Drayton, Middlesex

STRICTLY EXPORT ONLY



Leading Exporters of all types of Radio Receiving and Transmitting Tubes. Current Production and Ex-Government Surplus Special Purpose Tubes. Over 900 types in large quantities, available Ex-stock, Contractors to British Commonwealth and Foreign Governments for Army, Navy and Air-Forces, Post Offices, Civil Air Lines, etc. Ask for Export List.

SOME OF THE TYPES CARRIED IN STOCK

1A3	4THA	6D7	8S7	12K7GT	50C5	715B	1825	CV22	H30	PE285	VCR97
1A5GT	4TPB	6E5	8S7	12K8 (metal)	30CD6/G	717A	1826	CV415	H63	PE286	VCR140
1A7/G	5A21	6E8	8T7	12K8/GT	50L6GT	721A	1829	CV967	HF300	PE2820A	VCR140A
1A7GT	5A24	6F5	8T7	12Q7/GT	50Y6GT	723A/B	1833	CV980/8431	HL2	PM4DX	VCR511B
1B24	5B4G	6F5GT	8U4GT	12SA7	53A	724A	1835	CV1481	HL4	PM202	VCR516
1C6G	5A102D	6F5GT	8U6G	12SA7GT	53KU	725A	1842	CV1583	HL41	PP225	VCR516A
1C6GT	5B102A	6F6/1013	8U6/8G5	12SC7	54	726A	1848	CV6008	HP210	PT15	VCR517A
1D5	5B1	6F6G	8U7G	12SG7	57	800	1815	CV31	HP4101/5	PT5	VCR517B
1D8GT	5B4	6F6/GT	8V6	12SH7	58	801	1851	CV32	HR120	PT4	VCR517C
1E7G	5C1	6F7	8V6/G	12SJ7	59	801A	1860	DL	HT1	PT25	VCR517E
1G4GT	5C7	6F8G	8V6GT	12SJ7GT	61P	802	2050	D41	KR3	QP21	VCR528
1G5G	5C146 (A)	6F8GT	8X4	12SK7	72	803	2051	D63	KT2	R1	VCR528
1G6GT	5F7	6G5/G	8X5	12SK7GT	73	805	4005A	DA50	KTS	R2	VCR528
1H5G	5J4	6G6G	8X5G	12SL7GT	75	807	4019A	DA100	KT4	R3	VCR528
1H5/GT	5L35	6H6	8X5/GT	12SN7GT	76	808	4019B	DE75	KT33C	R10	VCR528
1L4	5L1	6H6G	8Y6G	12SQ7	77	810	4021A	DE79	KT44/VT75A	R12	VCR528
1LA6	5R4GY	6H6GT	8Y7G	12SQ7GT	78	811	4032A	DE712	KT61	RC3/522	VCR528
1L6	5T4	6J5	8Z5	12SR7	80	813	4045A	DE716	KT66	RE21	VCR528
1LD5	5U4/G	6J5G	7A4	12U5G	80S	814	4048A	DE719	KTW61	RG1/125	VP4A
1LE4	5V4G	6J5GT	7A6	12X3	81	915	4080A	DE725	KTW62	RG6/45	VP23
1LN5	5X4G	6J8	7A7	12Y4	82	816	4094A	DH63	KTW63	RK20A	VE21
1N5/G	5Y3G	6J7	7B6	1447/12B7	83V	828	4313C	DL63	KT241	RK28A	VE32
1N5GT	5Y3GT	6J7G	7B7	1488	83	828	4325D	E4448	KT263	RK34	VE33
1P5GT	5Y6G	6J7GT	7C2	1487	84/6Z4	829	4378	E1148	KT273	RK39	VE34 (EB34)
1Q5GT	5Z3	6K6G	7C4	14H7	89	829A	5783	E1155	L2	RK47	VE34
1R4/1294	5Z4	6K6GT	7C5	14K7	100TH	829B	7193	E1190	L30	RK48A	VE30/30
1R5	5Z4/G	6K7	7C8	14S7	117L7/GT	830B	7475	E1191	L63	RK73	VE105/30
1R4	5Z4GT	6K7/G	7O7	15E	117N7/GT	832	8011	E1192	L610	RK75	VE150/30
1R5	6A1	6K7GT	7D3	15B	117Z6/GT	832A	8012A	E1231	LD210	RK73	VE24
1T4	6A7	6K8	7D8	19A05	205F	833/833A	8013	E1248	LD410	RK33A	VE24
1U5	6A8G	6K8/G	7D8	23D	210HL	834	8016	E1254	LL2	RX235 (72)	VE110A
2A3	6A8GT	6K8/GT	7E7	24G	220RC	836	9001	E1265	LL4	825A	VT4C (211)
2A5	6A87/1853	6L5G	7E6	25A6G	210SPG	837	9002	E1266	LP2	827A	VT13B
2A6	6A87/1852	6L6 (metal)	7G7	25L6	210SPT	838	9003	E1271	L85	828A	VT46
2A7	6A8G	6L6/G	7H7	25L6GT	210VPT	841	9004	E1320	M125H	S130P	VT58A
2B7	6A88/G	6L6/GA	7K7	25V5	212E	843	9006	E1323	NH4	S130	VT60A
2C26	6A7	6L7	7N7	25Z4G	215P	850	AC4/PEN	E1369	MH41	SP2	VT94
2C34	6A35	6L7G	7R7	25Z5	217C	860	ACR13	E1388	MH4105	SP4	VT98
2E22	6AK5	6N7	7Q7	25Z6G	220B	861	APP4B	E1456	MH45D	SP22	VT501A
2J21A	6AK5	6N7/B	7S7	25Z6GT	231D	863	APP4C	E1469	ML4/TT4	SP41	VT510
2J21	6AL5	6N7GT	7E5	28D7	250TH	864	APP4G	E1474	ML6	SP42 (ARP20)	VT510
2J34	6AM5	6P7G	7W7	30	282B	865	AR12	E1496	MR10	SP61	VT29
2J36	6AM6	6Q7	7Y4	32	282A	866A	AR13	E1516	MS/PEN	SP210	VU33
2J39	6AQ5	6Q7/G	7Z4	33	204TH	866JR	AR300	E1509	MS/PEN/B	STV/280/40	VU39A/39
2J48	6AT6	6Q7GT	8D2	35A5	307A	869B	AR101	EAC51	MS/P4/NR65	STV/280/80	VU72
2J54	6AU6	6R7	9D2	35L066	318A	872/872A	AR34	EP34 (VR54)	MS/P4	SU150A	VU120A
2J54B	6B4G	6R7/G	9D6	35T	310B	874	ARF13	EB33	MU12/14	TP22	VU133A
2X2/879	6B5	6R7/GT	10	35TG	311A	875A	AR56	EC54	MS/PEN/3	TT4/NR57/ML4	VU508
2X2A	6B7	6SA7	10D1	35W4	3130	878	AT4	ECH22	NC11/12	TV05/13	VX7056
3A4	6B8	6SA7GT	11D3	35Z3	323A	878/804	AT5	ECH35	NC13	TV1/50-DET12	VY22
3A71	6B8G	6SC7	11D5	35Z4GT	327A	884	AT40	EF22	NG1	TT20	VY2
3B7/129	6BA6	6SD7/GT	12A8	35Z5GT	328A/4328A	902	ATP4	EF38	NG75	TT240	VY21
3B24	6BE6	6SF5	12A6GT	36	337A	923	AU5 (VU111)	EF39	NS2	U10	W31
3B26	6BG6G	6SF7	12A8/GT	37	354V	931A	AZ1	EF50	NS5	U12/1U14	W232
3BP1	6BE7	6S07	12A7H/GT	38	357A	934	AZ31	EF64	NT577/CV1234	U15	WD30
3CP1	6BW6	6S7	12A7	39/44	380A	955	B21	EHT1	NT63A/CV1238	U17	WE3A (IP21)
3D4/1299	6B7	6S7GT	12AT7	40	388A	956	B30	EK32 (VR57)	NT98/CV1249	U18/AU1	X21
3DP1	6C4	6S7	12AU6	41	394A	957	BL63	EL3	NT98B	U19	X24
3FP7	6C5	6S7GT	12AU7	41MP	405TL	958A	BT45 (CV22)	EL22	NU4	UC0	X31
3L4	6C5G	6S7Y	12AX7	41MPL	705A	959	C5B	EL32	OSGLIMS	U23	X41
3Q4	6C6GT	6S7GT	12B6	41MXP	705A	961	CL33	EL38	OZ4	U600	X61
3R7/G	6C8G	6S7GT	12BE6	41MXP	707A/B	961/1005	CM925	FG17	OZ4A	V226	X63
3C8G	6C8G	6S7	12C8	42	708A	1299A	CV3	GD74B	OZ4G	V1120	X63
3S4	6C21	6SL7GT	12C8GT	43	713A	1616	CV83	GL451	P2	V1808	X65
3V4	6CD8-G	6SN7/GT	12E6	45	714AY	1619	CV101/2	GTIC/GT2	P41	V2023	X66
4D21	6CH6	6SQ7	12J5GT	46	715	1622	CV193	GU20	P215	V1/132	X67/61
4C7	6D8	6SQ7GT	12J7GT	46	715A	1624	CV210	GU21	P25	VCR85	Z62


HALL ELECTRIC LTD

HALTRON HOUSE, 49-55 LISSON GROVE,
LONDON N.W.1.

Tel.: Ambassador 1041 (5 lines) Cables: Hallelectric, London

HALTRON

HALTRON

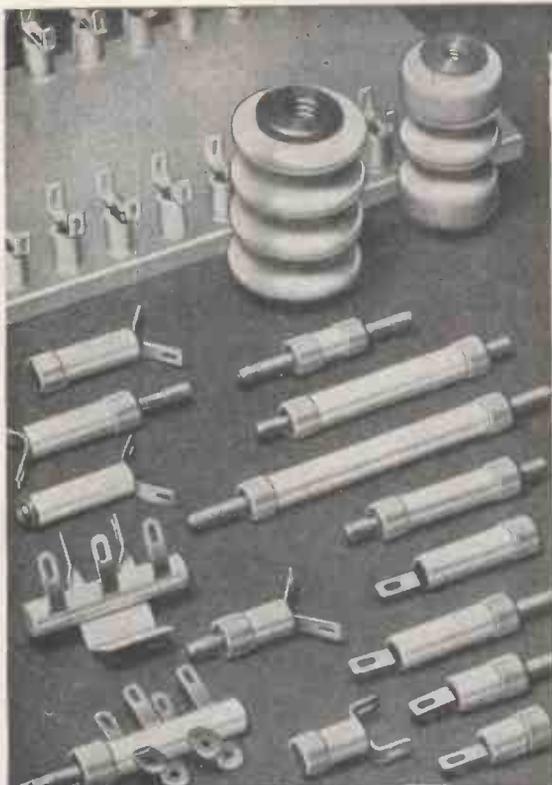

Here's quick, safe anchorage!

U.I.C. "Cactus" and "Porcupine" Tags and the almost limitless variety of Stand-Off Insulators will solve all your anchorage problems quickly, easily and efficiently.

These latest aids to neat and economical wiring and component assembly are tough, fireproof, and constructed entirely without solder. Only low-loss ceramics and electro-plated brass are used in the manufacture of these best of all anchorages.

Unique design
Insulation perfection
Competitive prices

U.I.C.

Write for Catalogue Section 3a

UNITED INSULATOR COMPANY LIMITED
OAKCROFT ROAD, TOLWORTH, SURBITON, SURREY
Telephone : Elmbridge 5241-2-3-4

SPECIALISTS IN ELECTRO TECHNICAL CERAMICS & COMPONENTS · SPECIALISTS IN ELECTRO TECHNICAL CERAMICS & COMPONENTS



CONSOLES

For Major Film Mixer Suites to Individual requirements.

"VIEWMASTER" CONSOLES

AS SHOWN

Beautifully designed and finished in Walnut, Oak, Mahogany and Teak, to customers' requirements



Standard "VIEWMASTER" model as shown £13.0.0

With Full Length Doors £14.0.0

Universal Model for all 16" tubes now in preparation.

Carriage and Packing 15/- extra

Fitted with shelf for easy mounting. These are NOT mass produced and dimensions can be altered to suit personal requirements.

Individual and Trade Enquiries to

H. ASHDOWN
CABINET MAKER

98 HERTFORD ROAD, EDMONTON, N.9

Phone: TOT. 2621

M. R. SUPPLIES Ltd.

for high-quality material at the most attractive prices. The diligent and enthusiastic service. Established 1835. Prices nett.

GARAGE HEATERS (black heat) 220/250 v. 500 watts. Efficient units also suitable for greenhouse, loft, workroom, etc. Robustly made in all-metal housing 10 1/2 in. x 4 in. with feet for vertical or horizontal use. Good tax-free bargain. 29/6 (despatch 2/6).

THERMOSTATS for heat control. Ex-A.M. small model, switching on at 32 deg. F., and off at 49 deg. F. (with considerable range adjustment). Capacity 5 amps., new, 4/6 (des. 6d.). Extremely useful instrument.

ELECTRICITY CHECK METERS (Kilowatt hour). 220/240 v. 50 c. Indicating up to 99,999 kw. hours. Capacity 10 amps. Second hand, in fine condition, perfect electrically. Exceptional offer, 16/6 (des. 1/6).

MAINS VOLTMETERS. First-grade m/iron by reputable makers. 0/300 volts 50 c. 5in. proj. type. Brand new, 47/6 (des. 2/-). **AMMETERS**, 0/5 amps., D.O. 2 1/2 in. square, ideal for chargers, model railways, etc., 9/6 (des. 9d.).

DECADE RESISTANCE BOXES, total resistance 210 ohms in 1-ohm steps on two radial arms and additional 100 ohms (which can be made into multiplier). Fitted m/coil galvo. In first-class condition in teak case 16in. x 7 1/2 in. x 6 1/2 in., 65/- (des. 2/-).

CRESSALL TOROIDAL REHEOSTATS, 20 ohms 2 amps. For series or potentiometer use. Brand new and half price, 22/6 (des. 1/6). Also G.E.C. **SLIDING RESISTANCES**, fully enclosed "safety-first" pattern, 40 ohms 2 amps., length 10in., under half price, 22/6. Two useful and brand new units.

SELENIUM RECTIFIERS. Bank of two units to give a D.C. supply up to 200 volts 1.2 amp. full wave. The bank of two rectifiers, 65/- (des. 2/-).

SEWING MACHINE MOTORS. Really high quality job at about half usual price. 200/250 v. A.C./D.C., complete and new equipment including motor, foot control, needle-light, belt, etc., ready for easy installation (instructions included), 28/15/- (des. 2/-). Complete satisfaction is guaranteed.

G.E.C. 1/3rd H.P. MOTORS. Very finest spec. Capacitor/Induction (with correct condenser). Ball-bearing, 1,440 r.p.m. cont. rated. For vertical or horizontal use. Silent running. Last few, brand new, in maker's wood packing cases, 25/17/6 (des. 6/-). Also very large selection of F.H.P. **GEARED MOTORS** from stock. Universal A.C./D.C., reversible. 220/250v. Average overall length 8in. Final speed, 100 or 50 r.p.m., either 25/17/6 (des. 2/6). Final speed, 10 or 1 r.p.m., either 26/18/6 (des. 2/6). Also Cap./Ind. type, 230/250 v. 50 c. reversible. Choice of final speeds: 17, 33, 46 or 92 r.p.m., any one, 25/17/6 (des. 2/6). All brand new.

SHADED POLE INDUCTION MOTORS, 200/250 v. A.C., torque 400 grms./cms. Size 3in. dia., 3in. long, shaft proj. 1in. Silent running and ideal for recorders, gram. motors, fans, stirrers, etc., 27/6 (des. 1/-).

SELF-PRIMING IMMERSION ELECTRIC PUMPS. New—ex-A.M. Fitted 24 v. D.C. Motor (operating well on 12 v. D.C. or 24/30 v. A.C.). Handy short model, 12 1/2 in. overall length—Immersion 9 1/2 in. Delivery 200/300 g.p.h. Ideal for use in laboratories, caravans, boats, etc., 25/6 (des. 2/6).

G.E.C. MINIATURE CRYSTAL CALIBRATORS. Operation 200/250 v. A.C. For frequency calibration in 100 Kc. steps from 100 Kc. to 40 Mc/s. Modulation at 400 c/s switched in if desired. With vacuum mounted crystal, basic 100 Kc/s, in cabinet 3 1/2 in. x 6 1/2 in. x 2 1/2 in. Last few at 25/5/- (des. 2/6).

LONDEX MINIATURE MAINS RELAYS. 250 v. A.C. coil, 2 pole "make," 5 amps. Size: 2 1/2 in. x 1 1/2 in. x 1 1/2 in. Silent in operation, 12/6 (des. 9d.).

We are stockists of **STUART TURNER PUMPS**, **B.P.L. MEASURING INSTRUMENTS**, **PHILIPS VARIABLE TRANSFORMERS**, **TEDDINGTON THERMOSTATS**, lists on request.

M. R. SUPPLIES, Ltd., 68 New Oxford St., London, W.C.1

Telephone : MUSeum 2958


Marconi Wavemeter



TF975

For the checking of transmitters

THIS supremely portable absorption-type instrument is directly calibrated in eight bands between 100 kc/s and 100 Mc/s. A primary use is harmonic identification in the case of transmitters having a crystal drive followed by harmonic multiplication. The wavemeter requires no power supply and may be easily held in one hand whilst adjustments are being made. The instrument itself, which measures only 5 in. x 3½ in. x 3½ in. over projections without tuning inductor, comprises a tuned

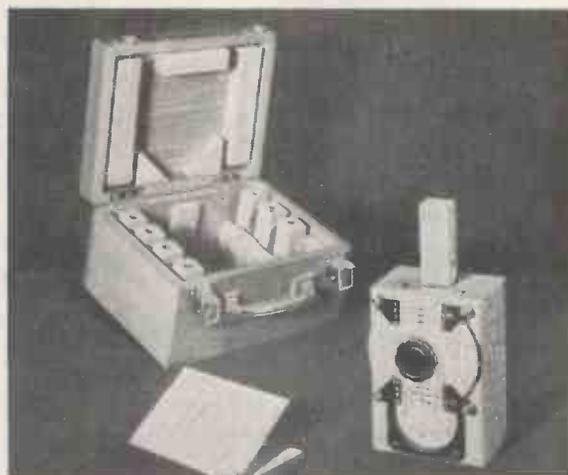

circuit in which resonance is indicated by a sensitive moving-coil micro-ammeter with crystal rectifier. It has an accuracy of $\pm 3\%$. For carrying purposes, a polished hardwood case accommodates the instrument and its eight plug-in coils.

MARCONI INSTRUMENTS

SIGNAL GENERATORS · VALVE VOLTMETERS · FREQUENCY STANDARDS
BRIDGES · WAVEMETERS · WAVE ANALYSERS · BEAT FREQUENCY OSCILLATORS


MARCONI INSTRUMENTS LTD · ST. ALBANS · HERTS · Telephone: St. Albans 6161/7

Midland Office: 19 The Parade, Leamington Spa

Northern Office: 30 Ablon Street, Kingston-upon-Hull

Export Office: Marconi House, Strand, W.C.2.

INTRODUCING . . .

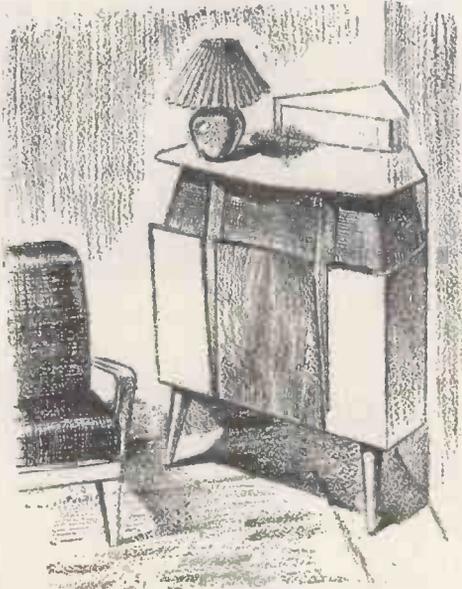

Walnut finish £96
(as illustrated Ex-works)

THE LOWTHER CORNER REPRODUCER

The greatest step yet taken

-towards perfection-

ENTIRELY NEW DESIGN THROUGHOUT incorporating THE LOWTHER P.M.3 pressure Drive unit.

MAIN FEATURES:- The design sets a new standard of reproduction of speech and music, transient frequencies, air column loaded; mid frequencies, wide angle directional baffle (short horn); low frequencies, pressurised exponential folded horn; high flux; high acoustical damping and high efficiency throughout.

INDISPENSABLE:- For Studio and Monitoring or when faithful reproduction of speech and music is required.

THE LOWTHER MANUFACTURING COMPANY, ST. MARKS ROAD, BROMLEY, KENT
Telephone: RAVensbourne 5225

- T/V TECHNOLOGY
- RADIO ENGINEERING
- ELECTRONICS
- RADIO SERVICING

There's a big future in T/V and Radio. Act now! Increase your knowledge. Back up experience with a sound theoretical background. I.C.S. offer courses of instruction in—

T/V TECHNOLOGY ● ADVANCED SHORT-WAVE RADIO ● RADIO ENGINEERING ● RADIO SERVICE ENGINEERING ● RADAR ● ELEMENTARY ELECTRONICS

I.C.S. will also coach you for the following examinations:—
B.I.R.E.; P.M.G. Certificate for Wireless Operators; Radio Servicing Certificate (R.T.E.B.); C. & G. Telecommunications, etc., etc.

DON'T DELAY—SEND COUPON TODAY for free descriptive booklet, stating which subject or examination interests you. Fees include all books needed. Examination students coached until successful.

Reduced terms for H.M. Forces.
Dept. 223D, I.C.S., 71 Kingsway, W.C.2


INTERNATIONAL CORRESPONDENCE SCHOOLS.
Dept. 223D, International Buildings, Kingsway, London, W.C.2.

Please send Booklet on subject.....

Name Age

(Block letters please)

Address.....

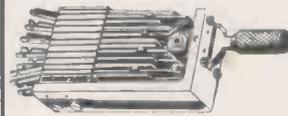

Also Suppliers of
RELAYS
UNISELECTORS
P.O. EQUIPMENT
PLUGS & SOCKETS

THE

KEYSWITCH CO.

P.O. TYPE RELAYS TO YOUR SPECIFICATION
SWITCHBOARD EQUIPMENT

SEND ALL YOUR ENQUIRIES TO
191 KENSAL ROAD, LONDON, W.10
LAD. 0666

LeeRaser

The original ultra rapid tape de-magnetiser as supplied to the leading recording studios, the B.B.C., and many Government departments including the Admiralty, R.A.F. and War Dept.



FOR
A.C. MAINS

MODEL B (up to 7" spool capacity) **£9. 10. 0.**

MODEL C (up to 12" spool capacity) **£15. 0. 0.**

Tropical
Specification

LEEVERS-RICH EQUIPMENT LTD.,

Manufacturers of high quality magnetic recorders
37, WARDOUR STREET, LONDON, W.1. GER. 4502

RADIO BULLS VALVES

246, HIGH ST. HARLESDEN, N.W.10.



SERVICE SHEETS

The one you require enclosed if available in a dozen assorted of our best choice. **10/6**

Please mark envelope (WW3)

A SELECTION FROM OUR MICROPHONES

Acos	35/1	£1 5 0	ROTHERMEL 2AD56	£3 3 0	RESLO RVA	£9 0 0	
"	33/1	£2 10 0	LUSTRAPHONE LX55	£2 10 0	" URA	£7 5 0	
"	MIC 30	£2 10 0	"	CS1/2 H.I.	£5 15 6	" VMC	£6 0 0
"	22/1	£4 4 0	"	CH51/2 H.I.	£6 6 0	GOODMAN Z33	
"	22/2	£4 4 0	GRAMPIAN MCR.		HIFI L.I.	£7 10 0	
"	16/2	£12 12 0	(MOVING COIL)	£4 12 6	HIFI H.I.	£9 0 0	

PIFCO

All-in-one Radio-meter A.C./D.C. Tests everything in Radio. Complete with Test prods.



29/6
Post 1/6.

Ex Gov. Guar. "DEMOBBED"



double-headphones for undisturbed listening on Crystal, Battery and Mains Sets. 7/6. Post 1/6.

Instantaneous! SOLDERING GUN 63/-

Note these special features
Instant Heating
Ample Capacity for one-tenth fuel cost
Temperature Control At the finger-tip
Slender Bit Can be bent to shape to reach corners
Automatic Feed Of molten solder by magnetic induction
Fully guar. for 12 months.


Deposit **10/-** monthly



Electric Paint Stripper Tax Free Post 2/-



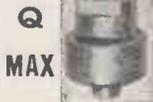A "BURNING" Question Blowlamp or Electropstrip? Unique Electric Paint Stripper outdates and outstrips Blowlamp. No smell, no mess, cost 1/6d. per hour. One year guarantee. Unique. **37/6** Post 1/3



Chassis Cutters with Keys

The easiest and quickest way of cutting holes in sheet metal. The cutter consists of three parts: A die, a punch and an Allen screw. The operation is quite simple. Prices, incl. Key:

1/8" B7G	12/4
1/8" B9A	12/4
1/8" B8A	13/4
1" Octal and Loctal	16/-
1 1/2" Engl. 4/5 pin	16/-
1 1/2" Engl. 7-pin	16/-
1 1/2" EF50	18/-
1 1/2" Conduit	18/-
1 1/2" Meter Size	19/9
2 1/2" Meter Size	31/9
2 1/2" Meter Size	36/9
1" Square	24/3

Postage 1/-.

Special price for complete set of 12 cutters and 3 keys, £10.

SIX TOOLS IN ONE

Punches, Bends, and Shears Metal Strip, Rod and Angle. Every Handyman, Mechanic and Service Engineer needs one! 10,000 used! Unique!

Post 1/-.



10/-

Reduced from 20/-

TRUVOX TAPE DECK MARK III.

Incorporating high impedance mu-metal twin-track heads. Two-speed capstan for tape speeds of 7 1/2 and 3 1/2 inches per second. Three heavy-duty motors allowing for fast forward and rewind facilities without tape handling. All controls operated by electrically and mechanically interlocked push buttons.

CASH PRICE £23. 2. 0



12 Payments of

29/-

monthly and

Deposit

£7. 14. 0

ELPICO TAPE AMPLIFIER Model AC/54

Cash Price £16. 16. 0 or Deposit £5/12/- and 12 monthly payments of 22/-. Can be used for recording/play-back and erase with any tape unit. Case to fit, 24/15/-.

A COMPLETE RECORDER

INCORPORATING THE FAMOUS

TRUVOX TAPE DECK for only £44.13.0

AMPLIFIER—TRUVOX TAPE DECK in LIZZARD type carrying case.

LOUDSPEAKERS

(Plus 1/6 postage)

2 1/2" P.M. 15 ohm Voice Coil, less Transformer	16/-
3" P.M. 3 ohm Voice Coil, less Transformer	14/6
5" P.M. 3 ohm Voice Coil, less Transformer	17/-
6 1/2" P.M. 3 ohm Voice Coil, less Transformer	18/-
6 1/2" P.M. 3 ohm Voice Coil, with Transformer	21/-
8" P.M. 3 ohm Voice Coil, less Transformer	22/-
8" P.M. 3 ohm Voice Coil, with Transformer	25/-
10" P.M. 3 ohm Voice Coil, less Transformer	25/-
8" P.M. 3 ohm "Celestion" Type C 80, less Transformer	40/3
8" P.M. 3 ohm "Stentorian" Type S808, less Transformer	33/6
10" P.M. 3 ohm "Stentorian" Type S1012, less Transformer	69/-
10" P.M. 15 ohm "Stentorian" Type S1012, less Transformer	69/-
10" P.M. 3 ohm "Stentorian" Type HF1012, less Transformer	73/6
10" P.M. 15 ohm "Stentorian" Type HF1012, less Transformer	73/6
12" P.M. 3 ohm "Truvox" Type BX11, less Transformer	60/-

EXTENSION LOUDSPEAKER CABINETS

6 1/2" Speaker Unit, size 7 1/2" x 7 1/2" x 3 1/2" deep in polished Walnut	16/-
6 1/2" Speaker Unit in Two-tone High polished Walnut Veneer	17/6
6 1/2" Speaker Unit in high polished Walnut Veneer, Baffle	17/6
8" Speaker Unit in Two-tone high polished Walnut Veneer	24/6
6 1/2" P.M. EXTENSION SPEAKER, TYPE R.M.3815 Housed in a Plastic Walnut Cabinet with W/W Volume Control	50/-

CATHODE RAY TUBES

BRIMAR	£ s. d.	ELAC ION TRAPS	G.E.C.	(Carriage free)
C12F 12"	16 13 8	*Type IT/6	5 0	3/31 12"
C14BM 14"	20 10 10	*Type IT/9	5 0	3/32 15"
C17BM 17"	24 13 6	FERRANTI		TA10/10"
COSSOR and EMITRON		T9/3 9"	12 10	TA15 15"
*ICI Indus	1 17 6	T9/5 9"	12 10	TA15/3 15"
12X P4 12"	16 13 8	T12/4 12"	16 13	MAZDA as available
12X P4A 12"	16 13 8	T12/8 12"	16 13	MULLARD
14K P4 14"	19 9 3	T12/5/8 12"	16 13	MW/2 9" pro-
18EP 15"	20 17 0	T12/14 14"	20 10	jection
17AS P4 17"	23 12 8			MW/22 18 9"
65K 15"	20 17 0			MW/31 74 12"
171K 17"	23 12 8			MW/36 22 14"
ENGLISH ELECTRIC				MW/36/24 14"
T900 16"	22 4 10			MW/41 11 16"
T901 16"	22 4 10			*Moulded B12A bases ea.

Easy terms on Taylor meters up to 10 mths, very near cash price. Ask for catalogue & proposal form.



Rod antennas 1" section interlocking extending copper plated steel, bargain 2/6 dos.

SPECIAL OFFER of

from 2/- VALVES

01A	2/-	2A7	3/-	EF6	17/6
1B4	3/-	2B7	2/-	KTZ41	3/-
1LN5	7/-	12A5	2/-	P215	2/-
2A6	2/-	12SF5	6/-		

Postage 9d.

DEMOBBED Valves "Manual" 2/3

Giving equivalents of British and American Service and Cross Reference of Commercial Types with an Appendix of B.V.A. Equivalents and Comprehensive Price List. We have still have some Valves left at very old Budget Rates (33 1/3%) which are actually sold at the o.d price. (1951 rate.)

—Lower Prices

AZ1	13/3	EK32	22/8
AZ31	13/3	EL3(N)	20/2
AZ50(DW4)		EL33	16/5
		EL37	22/2
CB1	13/3	EL38	25/2
CL4	20/2	EL41	18/5
CY1	13/3	EM1	16/5
EB41	11/4	EM4	16/5
EB91(6AL5)		EM34	16/5
		GZ34(GZ32)	
EB33	15/4		18/6
EB1	22/1	EY51	25/2
EBF80	18/11	EZ40	13/3
ECC40	22/1	EZ41	13/3
ECH3	22/8	PY80	15/9
ECH25	20/2	PY81	18/11
ECH42	20/2	PY82	13/3
ECL80	23/4	PL81	18/5
EP9	19/6	PL82	16/5
EP37A	22/1	UBC41	15/1
EP39	18/5	UBL21	20/2
EP40	22/1	UCH21	20/2
EP41	18/5	UF41	18/5
EP50	22/1	UL41	16/5
EP80	22/1	UY41	13/3
EP91	22/1		

Great Britain's Valve Mail-Order House

The Ideal Receiver for Point-to-Point
and Ground-to-Air Channels

✦ A Fixed Frequency, Single Channel Receiver covering 2 to 20 Mc/s.


The crystal-controlled R.93 is an important receiver which has been designed to operate over long periods under either temperate, arctic or tropical conditions at unattended sites. A number of R.93's may be stacked in standard 19" racks for multi-channel working on R.T. or W.T. Double or triple diversity racks can also be supplied with suitable terminal equipment for direct teleprinter operation from frequency shift transmission. Enquiries will receive immediate attention.

REDIFON LIMITED
RADIO COMMUNICATIONS DIVISION

BROOMHILL ROAD
LONDON, S.W.18

Phone: VANDYKE 7281

Redifon

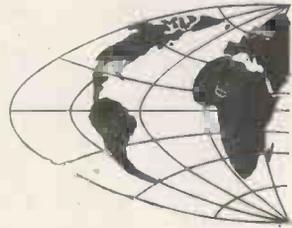

DESIGNERS AND MANUFACTURERS OF RADIO COMMUNICATIONS AND INDUSTRIAL ELECTRONIC EQUIPMENT

"WEYRAD"

ANNOUNCING A NEW MINIATURE I.F. TRANSFORMER OF PARTICULAR INTEREST TO MANUFACTURERS

THE
TYPE P.6.

SIZE = $1\frac{7}{8}$ " \times $\frac{3}{4}$ " \times $\frac{3}{4}$ "

"Q" = 85 (in can)

FREQUENCY = 455 - 495 Kc/s.

Large scale production enables us to quote very attractive prices. For applications where even higher performance is required special versions can be produced against quantity orders.

The P.6 will be among the very comprehensive range of components which we shall be showing at the R.E.C.M.F. Exhibition in April. A visit to Stand Number 115 will be well repaid.

WEYMOUTH RADIO MFG. CO., LTD.,
CRESCENT ST., WEYMOUTH, DORSET.

Television • Radio • Record
CABINETS MADE TO ORDER

ANY SIZE OR FINISH

CALL OR SEND DRAWINGS FOR QUOTATION

B. KOSKIE (DEPT. E.)

72-76 Leather Lane, Holborn, E.C.1

Phone: CHAncery 6791/2

**MINIATURE MAGNETIC
LIGHTWEIGHT EARPHONES**



The AMPLIVOX E.4, E.5 and E.6 provide a range of highly sensitive lightweight miniature receivers. Ideal for many applications, the inserts have been incorporated in lightweight headsets, stethoscope devices and small microphones. The E.6 is the smallest of the range, the diameter is 0.835", depth 0.332" and weight 1/2 oz. D.C. resistance E.4 & E.5 2-2,000 Ω , E.6 1-600 Ω .

AMPLIVOX LTD.
2 Bentinck Street, London, W.1.

PREMIER RADIO CO.

B. H. MORRIS & CO. (RADIO) LTD. EST. 40 YRS.

(Dept. W.W.) 207 EDGWARE RD., LONDON, W.2. Tel.: AMBassador 4033 & PADddington 3271



The NEW PREMIER T.R.F. RECEIVER design

You can build the Receivers illustrated for **£5.15.0**


The circuit is the latest type TRF using 3 Valves and Metal Rectifiers for operation on 200/250 volt A.C. mains. Waveband coverage is 180/550 metres on medium wave and 800/2,000 metres on long wave. The Dial is illuminated and the Valve line up is: 6K7—H.F. Pentode, 6J7—Detector and 6V6—Output. The attractive Cabinets to house the Receiver, size 12in. long 6½in. high, 5½in. deep, can be supplied in either walnut or ivory Bakelite or wood.

Below are examples of the excellent values we offer

SECTION 1	
1 Cabinet and Back (choice of Bakelite in either Ivory or Walnut, or Wood)	17 6
1 Chassis TRF	3 9
2 Chassis Brackets	9 9
1 Drive Spindle (Rear Drive)	1 6
1 Drive Drum	1 6
1 Drive Spring	3
1 Drive Pointer	4
1 2-band Dial	1 6
1 Front Plate	2 6
2 Dial Clips L.H.	6
2 Dial Clips R.H.	6
1 Length Drive Cord 15in.	3
TOTAL COST	£1 10 10
SPECIAL PRICE FOR COMPLETE SECTION £1/5/6 plus packing and postage 2/6.	

SECTION 2	
1 Aerial Coil (Green Spot) with Fixing Bar	2 9
1 Anode Coil (Red Spot) with Fixing Bar	2 9
1 Wavechange Switch	2 6
1 2-gang Variable Condenser with Trimmers	8 6
TOTAL COST	16 6
SPECIAL PRICE FOR COMPLETE SECTION 12/6 plus packing & postage 1/6.	

SECTION 3	
1 Choke	6 6
1 Heater Transformer T/LT3 PRY. 200/250 Volts SECY. 6.3 Volt 2 Amps Tapped at 5 volts	7 0
1 Output Transformer Ratio 45/1	5 6
1 Volume Control 10 K ohm with Switch	4 6
TOTAL COST	£1 3 6
SPECIAL PRICE FOR COMPLETE SECTION 17/9 plus packing & postage 1/6.	

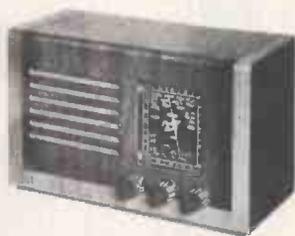

Send 1/- for Instruction Booklet which includes layout, circuit diagram and point-to-point wiring instructions, also included is a complete stock list of individually priced components.

The PREMIER De Luxe PORTABLE MAGNETIC TAPE RECORDING KIT

Including ALL parts, Valves, Portable Cabinet, 8in. Loudspeaker, Tape-Table, Reel of 'Scotch Boy' Tape and Rewind Spool, and Microphone. **PRICE £37.4.0** (Plus 15/- Pkg., Carr. & Ins.)

THE 7-VALVE AMPLIFIER IS SPECIALLY DESIGNED FOR HIGH QUALITY REPRODUCTION

Brief Specification: VALVE LINE-UP: EP37A First Stage, 6SL7 Second Stage and Tone Control; 6V6 Output 6X5 Rectifier; VT501 Bias and Erase Oscillator; 7193 Record Level Amplifier; 6U5 Magic Eye Record Level Indicator. OUTPUT: 4 Watts. FREQUENCY RANGE: 50 c.p.s. to 9,000 c.p.s. CONTROLS: Volume; Record/Playback Switch; Treble Boost; Bass Boost—on/off.

A VISUAL MAGIC EYE Record Level Indicator. The unit is housed in a superbly finished resin covered portable cabinet which incorporates a compartment for the Microphone when not in use. Weight complete 35lb. Dimensions: 2in. long, 12½in. deep, 9½in. high.

THE RECORDER incorporates an entirely NEW VERSION of the famous LANE TAPE TABLE.

Brief Specification: Made to high standards and incorporating features ensuring low level of "Wow" and "Flutter" throughout the full length of tape.

FAST REWIND. Provision for fast rewind and forward runs less than 1 min. in either direction. WIND AND REWIND WITHOUT UNLACING OF TAPE. INSTANTANEOUS BRAKING. THREE MOTORS obviating friction drive.

HIGH FIDELITY RECORD PLAYBACK (1 HOUR APPROX. PLAYING). The Table is fitted with high fidelity record playback head of new design wound to high impedance and a separate A.C. Erase Head. The Heads are half-track size allowing approx. 1 hr. playing from standard 1,200ft. Reel of Tape.


TAPE SPEED: 7½in. sec. For use on A.C. 200/250, 50 cycles mains only.

MICROPHONE: Crystal—specially designed for Premier by famous manufacturer.

SEPARATE UNITS CAN BE SUPPLIED AS LISTED BELOW

AMPLIFIER KIT (including 8in. Speaker)	£11 0 0 plus 5/- pkg./carr.
AMPLIFIER (already built, wired and tested)	£14 15 0 plus 7/6 pkg./carr.
LANE TAPE TABLE & REWIND SPOOL	£17 10 0 plus 7/6 pkg./carr.
PORTABLE CABINET (resin covered)	£4 19 6 plus 5/- pkg./carr.
MICROPHONE	£2 19 6 plus 1/- pkg./carr.
REEL OF NEW M.C.-2-III "SCOTCH BOY" TAPE (1,200ft.)	£1 15 0 plus 1/- pkg./carr.

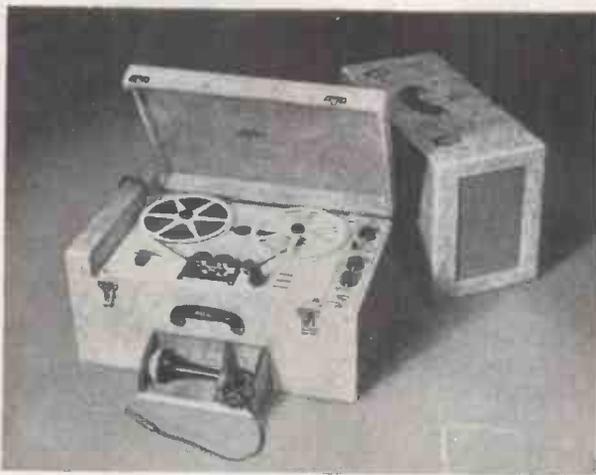★ INSTRUCTIONAL BOOKLET 2/6
This is credited if a complete kit of the Tape Recorder is ordered.



This Recording Outfit has been designed for use with M.C.-2-III "SCOTCH-BOY" Magnetic Tape. With this new and improved high-quality tape a frequency of 50 c.p.s. to 9,000 c.p.s. at tape speed of 7½ in./sec. can be readily achieved. Additional reels of 1,200ft. can be supplied at 35/-.

As is usual in all PREMIER KITS every single item down to the last nut and bolt is supplied. The Chassis is punched and layout diagrams and theoretical circuits are included. When completed the PREMIER PORTABLE TAPE RECORDER compares MORE than favourably with any other make at double the price.

Supplied completely assembled **39 GNS.** Plus 1 gn. Pkg. & Carr.

TERMS OF BUSINESS: Cash with order or C.O.D. over £1. Please add 1/- for Post Orders under 10/-, 1/6 under 40/-, unless otherwise stated.

PREMIER RADIO COMPANY

MAY BE BUILT FOR


£31 · 19 · 7

including all valves.
(plus cost of CRT)



THE COMPLETE TELEVISOR IS SAFE TO HANDLE, BEING COMPLETELY ISOLATED FROM THE MAINS BY A DOUBLE WOUND MAINS TRANSFORMER. ALL PRESET CONTROLS CAN BE ADJUSTED FROM THE FRONT. MAKING SETTING UP VERY SIMPLE.

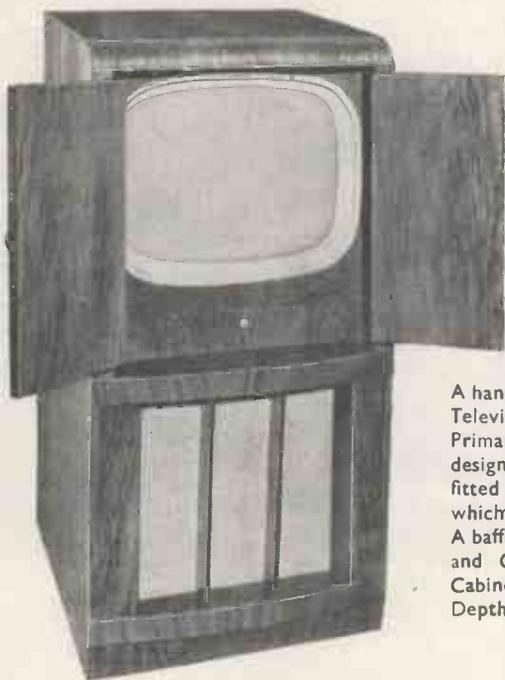The Televisor may be constructed in 5 easy stages: (1) Vision, (2) Time Base, (3) Sound, (4) Power Pack, (5) Final Assembly. Each stage is fully covered in the Instruction Book, which includes layout, circuit diagrams and point-to-point wiring instructions.



PRICE **£13 · 10 · 0**

plus 2/- packing & carriage.

The NEW

PREMIER TELEVISOR

Three years ago we gave you the 6in., 9in. and 12in. Televisors which achieved tremendous popularity. Now after a considerable period of research our Technical Staff have designed a very worthy successor to these original Models.

Brief Technical Details are as follows:

20 valves (plus tube) Superhet Receiver, tunable from 40-68 Mc/s without coil or core changing. Wide Angle scanning Flyback EHT giving 14 kV, Duomag Focalsiser permanent magnet focussing with simple picture centring adjustments, suitable for any 17in. or 14in. wide angle Tube, may also be used with a 12in. Tube with very minor modifications.

VISION CIRCUIT. Common RF Amplifier, single valve frequency changer, two IF stages, Video Detector and Noise Limiter followed by special type of Video Output Valve. ALL COILS PRE-TUNED ASSURING ACCURATE ALIGNMENT AND EXCELLENT BANDWIDTH.

SOUND CIRCUIT. Coupling from anode of frequency changer, two IF stages, Double Diode Triode detector and first LF Amplifier, Diode Noise Limiter and Beam type Output Valve, feeding a 10in. Speaker. ALL COILS PRE-TUNED.

TIME BASES. 2 valve sync. Separator, giving very firm lock and excellent interlace.

LINE TIME BASE. Blocking Oscillator using a pentode driving a high efficiency output stage comprising Ferroxcube Cored Output Transformer with Booster Diode.

FRAME TIME BASE. Blocking Oscillator driving a Beam Output Valve coupled through a Transformer to the high efficiency FERROXCUBE Cored Scanning Coils.

POWER PACK. Double wound Mains Transformer supplying all L.T. and H.T. using two full-wave Rectifiers.

The Instruction Book also includes full details for converting existing Premier Magnetic Televisors for use with modern wide angle tubes. All components are individually priced.

Instruction book 3/6, Post Free.

PREMIER TELEVISOR CONSOLE CABINETS For 14" and 17" Televisors

A handsome Walnut Cabinet that will be a fitting housing for a first-class Televisor.

Primarily designed for our own Televisor, they are quite suitable for most designs published in the various Radio Periodicals. Folding doors are fitted to cover the Cathode Ray Tube when not in use. A flap is provided which gives access to any preset controls on the front edge of the Chassis. A baffle board suitable for a 10in. Loudspeaker and all the necessary Tube and Chassis bearers are included. The overall dimensions of both Cabinets are the same: Height 38½in. Width 19in. Depth Top 19in. Depth Bottom 21in.

TUBE ESCUTCHEONS

17in. White Moulded	21/-	(packing and postage 1/6)
17in. Bronze Moulded, Complete with Protective Glass	48/-	(packing and postage 2/6)
14in. Black Moulded	7/6	(packing and postage 1/-)
Dark Screen Filter suitable for 14in. or 17in. Tubes	19/6	(plus 1/6 packing and postage).

PREMIER RADIO COMPANY

ONLY A FEW LEFT!


THE FAMOUS 'SOBELL' 4-VALVE SUPERHET TABLE RECEIVER

M. & L. WAVEBANDS
 Valve line-up: 12Z7, 35L6, 1487, 35Z4.
 Entirely transportable and unusually sensitive owing to special feed-back circuit employed. Housed in attractive plastic cabinet. Choice of 2 colours—Brown and Cream.



Carrying handle incorporated in design. For use on 200/250 A.C./D.C. mains. **£8.5.0**
 Plus 6/- Pkg./carr./Ins.
Fully covered by Manufacturer's Guarantee

1124 RECEIVER UNITS

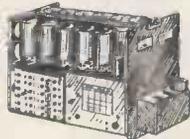

Range 30 to 40 Mc/s. Contains six new Valves 3-9D2, 1-8D3, 1-16D3 (frequency changer), 1-4D1, 24 ceramic trimmers, 6 ceramic valveholders, 6 valve screening cans, 30 resistors, 1-W/W Pot. Meter Mica Tubular and Block Components, 2 Westcoaster WX6 and 1 Westcoater WX4, 5-way 4-bank switch with long spindle, I.F. transformers, etc. New in transit case. Solved 17/8 plus 3/6 postage and packing. **24/0**

1155 RECEIVER UNIT

SIGHTLY SOILED

In original cases complete with 10 valves. Frequency range 18.5 Mc/s. 75 Kc/s. in 5 wavebands. **£7/19/6**. Plus 10/6 packing and carriage.



POWER SUPPLY UNIT

for above, incorporating output stage. Supplies an output of 250 volts at 80 mA. which is ample for the R1155 with the output stage. Jones plugs for connecting the Power Pack to the Receiver are included. The 6V6 output stage complete with Output Transformer and 6in. speaker is built into the unit. Price **£25/5/-**, plus 5/- packing and carriage.



We have a few Brand new R1155 Receivers in original cases, complete with 10 valves. Frequency range 18.5 Mc/s.—75 Kc/s in 5 wavebands. PRICE £11/19/6. Plus 10/6 pkg. and carr.

As a special offer, power supply unit including speaker together with R1155 receiver. PRICE £16.19.6. Plus 15/- pkg. & carr.

R1355 RECEIVER AMPLIFIER
 with 5 I.F. Stages for T.V. conversion. Contains 7 VBE5's, 1-3U4, 1-VU120, 1-EA50, 39/6. Brand new 55/- Plus pkg. and carriage 5/-.

RF 24 UNITS

Frequencies covered 30-20 Mc/s (10-15 metres). Switched tuning. 5 pre-tuned spot freq. 3/VBE5 (RP61). 12/6.

RF 25 UNITS

Frequencies covered 40-50 Mc/s (6-7.5 metres), switched tuning. 5 Pre-set positions complete with 3 VBE5's, 17/6.

RF 26 UNITS

The ideal short-wave converter for T.V., variable tuning, contains 2—EF64, 1—VR137, 37/6.

RF 27 UNITS

Frequencies covered 85-65 Mc/s (3.5-5 metres). Otherwise as RF 26, 37/6.

CORRECT ASPECT WHITE Rubber Mask—Round or Flat

6in. 8/6 9in. 9/8
 12in. 16/11 15in. 27/8

T.V. PRE-AMPLIFIER

Amplifier Unit Type 208A using 2-VBE1 valves suitable for operation on London frequency. Brand **19/6** new. Plus 1/6 pkg. and carr.

ACCUMULATORS

Lead Acid Celluloid Non-Spill, 2 v. 7 amps. 8/6
 3 volt 10 amp. (by famous maker) 4/11
 3 volt 16 amp. 5/11

METERS

Large stocks available, a few of which are enumerated below:—

Full Scale Deflection	Scale Length	External Dimensions	Movement	
25 A	1 1/2"	2 1/2" round	R.F. Thermo	7/6
3.5 A	1 1/2"	2 1/2" x 2 1/2"	R.F. Thermo	7/6
4 A	1 1/2"	2 1/2" x 2 1/2"	R.F. Thermo	7/6
20 A	1 1/2"	2 1/2" round	M/C	8/6
40 A	1 1/2"	2 1/2" round	M/C	8/6
1.5 mA	1 1/2"	2 1/2" round		12/6
3 mA	2"	3 1/2" round		7/6
6 mA	2"	3 1/2" round		16/9
50 mA	1 1/2"	2 1/2" x 2 1/2"	M/C	7/6
20 V	2"	2 1/2" x 2 1/2"	M/C	8/6
40 V	1 1/2"	2 1/2" x 2 1/2"	M/C	8/6

MANUFACTURER'S SURPLUS STOCK

5-VALVE SUPERHET RADIO RECEIVER CHASSIS, built to high standards ensuring quality reception. **SPECIFICATION:—**
VALVE LINE-UP:— 757, 7B7, 7C8, 7C5, 774. **3 WAVEBANDS**. Long, medium and short. **CONTROLS:—** Tuning, wave change, volume tone control on/off Gram Position on Switch, Pick-up and Extension Speaker Socket Incorporated. For use on 200/250 v. A.C. mains. **DIMENSIONS:—** Length 14 1/2 in., height 11 1/2 in., width 6 1/2 in. Distance between controls, left to right from edge of chassis: 1in. 3in., 6 1/2 in., 3in. Plus 5/- pkg./carr./ins. **£7.19.6**
 The above Receiver less Speaker and Output Transformer. A suitable 10in. Moving Coil Speaker and Output Transformer can be supplied at 29/- extra.

LIMITED QUANTITY 1132A RECEIVER UNITS COMPLETE WITH CIRCUIT

11-valve Superhet Receiver, covering 100 to 124 Mc/s., using four VR55, two VR56 and VR66, VR67, VR54 and VR57 valves. Fitted with Tuning Meter, slow motion drive, R.F. and L.F. Gain. Control, etc. Circuit: R.F. amp, frequency changer, oscillator and stab., 3-I.F. amps., R.F.O. Det., first audio and output. Brand new, with circuit diagram.



Price **59/6** plus 7/6 carriage.
POWER PACK for above completely wired and tested, will fit on Receiver chassis. Price 50/- plus 2/6 pkg. and carr.

C.R. TUBES

VCR516
 9in. Blue picture, Heater volts 4 Anode 4 Kv. In manufacturer's original carton. **£3/19/6**. Plus 5/- pkg., carr., ins.
VCR517C
 6 1/2 in. picture. This tube is a replacement for the VCR97 and **Price 35/-**
VCR517. Guaranteed full size picture. Plus 2/6 pkg. carr. ins.



ALL BRAND NEW

LOUDSPEAKERS

ELAC—2 1/2 in. dia., Moving Coil, 15 ohms imp. 15/-
 ELESSEY—3 in. dia., Moving Coil, 3 ohms imp. 9/11
 ELAC—3 1/2 in. dia., Moving Coil, 3 ohms imp. 15/-
 GOODMANS—5 in. dia., Moving Coil, 3 ohms imp. 15/6
 ELAC—5 in. dia., Moving Coil, 3 ohms imp. 19/6
 PLESSEY—9 in. dia., Mains Energised, 3 ohms imp. (600 ohms field), with Pentode Transformer 22/6
 PLESSEY—8 in. dia., Mains Energised, 3 ohms imp. (600 ohms field) 12/6
 PLESSEY—10 in. dia., Moving Coil, 3 ohms imp. 23/6
 GOODMANS—12 in. dia., Moving Coil, 15 ohms imp. Plus 5/- packing and carriage. **£8/8**
VITAVOX—E12/20 12 in. dia., Moving Coil, 15 ohms imp. **£11/11**
 Plus 5/- packing and carriage.

SPECIAL OFFER A 12in. TRUVOX P.M. SPEAKER

(2-3 ohm Voice Coil) For only **47/6**
 These are brand new in Maker's Cartons Plus 2/6 Pkg. and Carr.

"MASTERADIO" VIBRATOR PACK

3 v. Input 180 v. 35 mA. output complete with valve rectifier and leads. **39/6**. Plus 5/- pkg., carr.



WHY PAY MORE?

WILLIAMSON AMPLIFIER KIT 15gns.
 plus 7/6 post, pkg. & ins.
 This kit is absolutely complete and all components are guaranteed exactly to author's specification.

WILLIAMSON OUTPUT TRANSFORMER
 (author's spec.), 3.6 ohms sec. **£4.4.0**

MAINS TRANSFORMER 8P425A (with additional 6.3 v. 3 a. and capable of supplying an extra 50 mA. for Pre-amp. or Feeder Unit) **£3.7.6**

PREMIER MAINS TRANSFORMERS

All primaries are tapped for 200-230-250 v. mains 40-100 cycles. All primaries are screened. All LTs are centre tapped.
 SP175B, 175-0-175, 50 mA., 4 v. @ 1 a., 4 v. @ 2-3 a. 4 v. @ 3-6 a. 25/-
 SP350A, 250-0-250, 100 mA., 5 v. @ 2-3 a. 6.3 v. @ 2-3 a. 4 v. @ 3-6 a. 29/-
 SP351, 350-0-350, 150 mA., 4 v. @ 1-2 a. 4 v. @ 2-3 a. 4 v. @ 3-6 a. 36/-
 SP352, 350-0-350, 150 mA., 5 v. 2-3 a. 6.3 v. 2-3 a. 6.3 v. 2-3 a. 36/-
 SP375A, 375-0-375, 250 mA., 6.3 v. @ 2-3 a. 6.3 v. @ 3-5 a. 5 v. @ 2-3 a. 55/-
 SP501, 500-0-500, 150 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 2-2 a. 4 v. @ 3-5 a. 47/-
 SP501A, 500-0-500, 150 mA., 5 v. @ 2-3 a. 6.3 v. @ 2-3 a. 6.3 v. @ 2-3 a. 50/-
 SP425A, 425-0-425, 200 mA., 6.3 v. @ 2-3 a. 6.3 v. @ 3-5 a. 5 v. @ 2-5 a. 67/6
 250-0-250, 80 mA., 6.3 v. @ 4 a. 5 v. @ 2 a. 19/6
 350-0-350, 80 mA., 6.3 v. @ 4 a. 5 v. @ 2 a. 19/6
 200-230-250, output 3 v. 30 v. @ 2 a. 17/6

AUTO TRANSFORMERS 50 WATTS

Input/Output 0-110-210-220-230-240-250 volts. Plus 1/- p. & p. **7/6**

PREMIER VARIABLE IMPEDANCE "MATCHMAKER" M.O.15 OUTPUT TRANSFORMER

Designed to meet the demand for an efficient variable ratio Output Transformer. 11 ratios from 13:1 to 80:1 all centre tapped and can be used to match any output valves at either single or push-pull Class "A" or "AB1" "AB2" or "B" to any low impedance speech coil or combination thereof. Primary Inductance 60 henries 15 watts audio 100 mA. Price 45/-.

WEYMOUTH MINIATURE I.F. TRANSFORMERS

465 Kc/s., Iron cored, permeability tuned, 10/6 pair

WEYMOUTH MINIATURE COIL PACK.

Covering Med./Long/Short wavebands. Iron cored coils, gram position on switch. Dimens.: Height, 1 1/2 in. Length, 3 1/2 in. Width 2 1/2 in. Spindle length 2 in. Price 19/6.

MINIATURE TUNING CONDENSERS

2 gang .0005 mfd. with trimmers 8/9

FILAMENT TRANSFORMERS

Input 230 v. A.C. Output 12 v. at 1 amp. Completely shrouded. Price 9/11.

BATTERY CHARGERS

200-250 v. A.C. Will charge 2 v., 6 v. and 12 v. Car Battery at 1 amp. Housed in strong metal casing. Finished in Green hammered enamel. Size: 6in. long, 3 1/2 in. wide, 3 1/2 in. high. Guaranteed 12 months. The above unit is manufactured by PREMIER and does not contain ex-Govt. components. Plus 3/6 post and pkg. **39/6**



BATTERY CHARGER KITS

All incorporate metal rectifiers. Transformers are suitable for 200/250 v. A.C. cycle mains. Cat. No. 2002 Charges 6 volt accumulator at 1 amp. Resistance, supplied to charge 2 v. accumulator 21/-
 2004 Charges 2,6 and 12 v. accumulators at 1 amp. **24/6**

MICROPHONES

LUSTRAPHONE: Moving Coil; High Impedance. Stand Type: £5/15/6—Hand Mike £6/6/6—RONETTE—Crystal Mike; Incorporates the Filter Cell Insert; High Imped. Ball Type: £3/10/6.
CRYSTAL MICROPHONE—Rothenel 2AD36. Especially recommended. £2/19/6. Table stands for all the above 10/6 and 17/8.

CRYSTAL HAND MICROPHONE

High impedance. Excellent frequency response, light weight. Gives very high quality results when used with tape recorder, amplified for any type of P.A. equipment. Complete with screen lead and plug plus 1/6 Pkg. & Carr. Price 29/6.

CRYSTAL MICROPHONE

An entirely insulated crystal microphone which can be safely used on A.C./D.C. amplifiers. High impedance. No background noise, really natural tone. The ideal Mike for tape, wire and sound projectors. Price 23/6.

PREMIER RADIO COMPANY

SPECIAL OFFER

THE FAMOUS "CHANCERY" HIGH FIDELITY MICROCELL PICK-UP TYPE GPX for Standard and Long Playing

The Chancery Light Weight GPX Pick-up which has a sapphire stylus which is precision ground and semi-permanent. With two cartridges 1 L.P. and 1 Standard Price 52/6. Additional L.P. or Standard Cartridges can be supplied from stock at 19/6 each.

★ **QUALITY CRYSTAL PICK-UP ROTHERMEL TYPE U48 26/-**
Plus 1/6 Pkg. and Carr.

GRAMOPHONE CABINETS—Portable

By famous manufacturers Substantial Wooden Case, Resine covered, including wooden motor board. Outside dimensions: Hgt. (when closed) 5 1/2 in., length 15 in., depth 13 1/2 in. Clearance space, under motor board when closed 2 1/2 in.

Price 29/6, plus 2/6 pkg. carr

SPECIAL OFFER—at Almost Half Price PLESSEY GRAMOPHONE UNITS



The Motor, Tone arm, and Magnetic Pick-up is in one Unit, with Automatic stop and start. For use on 200/250 v. A.C. mains 50 cycles. Limited quantity only. £3/19/6, plus 2/6 packing and carriage.

RECTIFIERS

Type	E.H.T. Pencil Type S.T.C.	1 mA.	4/7
K3/25	650 v.	1 mA.	8/2
K3/40	3.2 kV.	1 mA.	8/2
K3/45	3.6 kV.	1 mA.	8/8
K3/50	4 kV.	1 mA.	8/8
N3/160	12 kV.	1 mA.	21/6
Type	H.T. Type S.T.C.	60 mA.	4/-
RM1	125 v.	60 mA.	4/6
RM2	125 v.	100 mA.	5/6
RM3	125 v.	125 mA.	5/6
RM4	250 v.	250 mA.	18/-
L.T. Type Full Wave			
6 v. 1 amp. 4/-			
12 v. 1 amp. 8/-			
12 v. 2 amp. 10/9			
12 v. 4 amp. 15/-			

A.C.R.I. C.R. TUBES

5 1/2 in. screen. 4 volt Heater. This Electrostatic Tube is recommended as eminently suitable for Television. 15/- plus 2/6 Pkg., carr. and ins. Data sheets supplied.

SUPER QUALITY TELEVISION MAGNIFYING LENS

5in. lens suitable for 6in.	18/6
6in. lens	25/-
10in. lens	£2/10/-
12in. lens	£3/10/-

ALUMINIUM CHASSIS 18 s.w.g.

Substantially made from Bright Aluminium, with four sides			
7 x 5 1/2 x 2in.	4/-	10 x 9 x 3in.	7/-
7 x 3 1/2 x 2in.	3/9	12 x 10 x 3in.	7/9
9 1/2 x 4 1/2 x 2in.	4/3	14 x 10 x 3in.	7/11
10 x 8 x 2 1/2 in.	5/6	16 x 10 x 3in.	8/3
12 x 9 x 2 1/2 in.	7/-	16 x 8 x 2 1/2 in.	8/-
14 x 9 x 2 1/2 in.	7/6		

ALUMINIUM PANELS 18 s.w.g.

7 x 6in.	1/3	7 x 4in.	1/-
9 1/2 x 6in.	1/8	9 1/2 x 4in.	1/5
10 x 9in.	2/2	10 x 7in.	1/11
12 x 9in.	2/8	12 x 7in.	2/5
14 x 9in.	3/2	14 x 7in.	2/11
16 x 9in.	3/8	16 x 7in.	3/5
20 x 9in.	4/8	20 x 7in.	4/5
22 x 9in.	5/2	22 x 7in.	4/11

H.T. ELIMINATOR AND TRICKLE CHARGER KIT

All parts to construct an eliminator to give an output of 120 volts at 20 mA., and 2 volts to charge an accumulator. Uses metal rectifier, 37/6.

Famous Manufacturer's Surplus of **ANTI-INTERFERENCE AERIALS** offered at a fraction of original cost



The aerial is designed for reception of long, medium and short waves, with any ordinary or communications receiver, having an input impedance greater than 1,000 ohms long/medium waves and 150 ohms short waves. The installation discriminates against locally generated electrical interference, especially on the short wave bands. The equipment enables the installation of an 8.3 Mc/s. fully-tuned dipole which operates as a "T" aerial on medium and long waves. The aerial and receiver transformers are intended to be interconnected with a 70 ohms co-axial cable.

COMPONENT PARTS

Aluminium Aerial Transformer Assembly. Comprising one each: Aluminium transformer, Transformer clip, Rubber sucker, 1/2 in. x 1/2 in. brass screw, 4AB x 1/2 in. brass bolt, 4BA nut. Receiver Transformer. Complete with Insulators, clips, etc.; Porcelain Insulators, 2 each, 60ft. Insulated Aerial Wire, 60ft. Screened Co-Axial Down Lead. Installation instruction leaflet included. LESS CO-AXIAL CABLE & AERIAL WIRE, 15/-, plus 1/6 pkg. and carr. COMPLETE 35/-, plus 1/6 pkg. and carr.

GARRARD Rlm Drive 78 r.p.m., complete **£5.19.6**
Packing and carriage on the above unit 2/6

MAINS NOISE ELIMINATOR KIT

Two specially designed chokes with three smoothing condensers with circuit diagrams. Cuts out all mains noise. Can be assembled inside existing receiver, 5/6, complete.

Germanium Crystal Diodes. G.E.C. wire ended, 2/8, 24/- doz.



"Minor"

INSULATION TEST SET

The Minor, although small, possesses all features of the large models and no mechanical or electrical point essential to efficiency has been omitted.

Among other fine instruments manufactured by:—

THE RECORD ELECTRICAL CO LTD BROADHEATH - ALTRINCHAM - CHESHIRE

Phone: Altrincham 3221 (4 lines) Cables and Grams: "Circscale" Altrincham
London Office: 28 Victoria Street, S.W.1. Phone: Abbey 5148 & 2783
Grams: "Circscale" Sowest, London. Cables: "Circscale" London

TRANSFORMERS COILS CHOKES LARGE OR SMALL QUANTITIES TRADE ENQUIRIES WELCOMED

SPECIALISTS IN

FINE WIRE WINDINGS

MINIATURE TRANSFORMERS, PICK-UP, CLOCK AND INSTRUMENT COILS, ETC. VACUUM IMPREGNATION TO APPROVED STANDARDS

ELECTRO-WINDS LTD.

CONTRACTORS TO G.P.O., M.O.S., L.E.B., ETC

123-5-7 PARCHMORE ROAD, THORNTON HEATH, SURREY LIVINGSTONE 2261 EST. 1933

TELEVISION

for "Fringe" and "Long distance" viewers is vastly improved with the SPENCER-WEST type AC/3 Pre-Amplifier. The specification includes a first stage neutralised triode cathode coupled to a grounded grid triode. The optimum arrangement for best "noise factor." Self-contained power supply unit complete with correctly adjusted interference filter. Price complete, 10 gns. from your dealer or direct. Leaflets, etc., on request.

RECEIVER CONVERSION TO NEW CHANNELS. The type AC/4 Converter units for perfect simple conversion. Price complete with 5 valves and self-contained power unit, etc. 15 gns. Available for Brighton booster on London receivers (type AC/4KL) and all other conversions. Leaflets on request.

SPENCER-WEST QUAY WORKS, GT. YARMOUTH

Phone: Gt. Yarmouth 3009.

Taylor Model 88A multirange universal meter



Five inch moving coil meter with knife-edge pointer and anti-parallax mirror. Instantaneous overload protection. Buzzer for continuity testing.
Sensitivity: 20,000 o.p.v. D.C. 2,000 o.p.v. A.C.
Accuracy: D.C. mA. D.C. Volts ranges 2% of F.S.D.; A.C. V. & A.C.M.A. ranges (except for 5 kV A.C.) 3% of F.S.D. 5 kV ranges 6% of F.S.D.

RANGES

Volts D.C.: 0-1-25-1-2.5-5-10-25-50-100-250-500-1,000-5,000.
Volts A.C.: 0-1-2.5-5-10-25-50-100-250-500-1,000-5,000.

Price £22 . 0 . 0

or £3 . 6 . 0 deposit and 10 monthly payments of £2 . 2 . 1.

Milliamperes D.C.: 0-.05-1-.25-1-2.5-5-10-25-50-100-250-500-1,000.
Milliamperes A.C.: 0-.25-1-2.5-5-10-25-50-100-250-500-1,000.
Amperes A.C./D.C.: 0-2.5-10.
Resistance: 1 ohm to 5 megohms in 4 ranges (can be extended up to 50 Megohms).
Decibels: -20 to + 69 in 9 ranges. Zero reference level is 6 mW into 500 ohms.
Output: As A.C. volt ranges (except 5,000 volts) via a condenser.
Inductance: 0.2 to 200 henries in 2 ranges*
Capacitance: 1,000 pF to 100µF in 4 ranges*

*External adaptor, Model 313D, required.

PROMPT DELIVERY

Taylor Model 110C capacity-resistance bridge

An A.C. mains operated bridge designed to give quick and accurate measurements of capacity or resistance at mains frequencies, covering all practical requirements.
Eight Capacity Ranges: 0-0.00012-0.0012-0.012-0.12-1.2-12-120-1,200 µF.
Eight Resistance Ranges: 0-12-120-1,200-12,000-120,000 ohms and 0-1.2-12-120 megohms.
The accuracy of all resistance ranges except the highest is 2% of full scale, on the highest range it is 3% of full scale. On all capacity ranges except the lowest it is 3% of full scale. On the lowest range it is 4% of full scale.



Price £14 . 10 . 0

or £2 . 3 . 6 deposit and 10 monthly payments of £1 . 7 . 9.

PROMPT DELIVERY

Other Taylor Products:
A selection of Multirange A.C./D.C. Testmeters; Signal Generators; A.C. Bridges; Circuit Analysers; Cathode Ray Oscilloscopes; High and Low Range Ohmmeters; Output Meters; Valve Testers; Moving Coil Instruments; T.V. Test Gear.
WRITE FOR CATALOGUE

Taylor

ELECTRICAL INSTRUMENTS LTD

Montrose Avenue, Slough, Bucks. Slough 21381

A *NEW* WIDE-BAND A.F. OSCILLATOR

that really "gets down to it"....(1.4 CYCLES)

TYPE G.420. This Furzehill instrument delivers a constant sinusoidal output of up to 1 volt into 600 ohms over the wide frequency range of 1.4 c/s. to 15 kc/s.

Frequency Range: 1.4 to 15 c/s.
1.4 to 150 c/s. 140 c/s. to 1.5 kc/s.
1.4 kc/s. to 15 kc/s. Accuracy
2.5%: Scale arc 280°.

Output: 1 V r.m.s. into 600 ohms
or 10 V r.m.s. into high impedance,
substantially constant over entire
frequency range.

Attenuator: 600 ohm, continuously
variable, T-pad.

NOTE:—This instrument is also available to the above specification,
but including the addition of square wave output at a small additional
charge, (Type G.420A).

Write for full particulars of this and other Laboratory instruments to:—

Harmonic Content: Less than 2%
over most of the range.

Hum Level: Better than 40 dB
below any signal level.

Stability: Less than 0.1 dB change
in output volts and less than 0.1%
change in frequency for 10%
change in supply voltage.

Delivery: 7/14 days.



Price, Ex-Works: £50.0.0

Furzehill

AN UNUSUALLY LOW PRICE FOR AN UNUSUALLY VERSATILE PERFORMANCE

Furzehill Laboratories Ltd.

SHENLEY ROAD · BOREHAM WOOD · HERTS. Cables: FURZLAB, LONDON. Tel: ELStree 3940

C. MARKS & CO.

THE ELECTRONIC INSULATION TEST SET AND NULL INDICATOR. This instrument incorporates the use of a cathode ray visual indicator. High sensitivity is achieved by an input impedance of 3.6 megohms. This permits a wide range of applications, amongst which are: (1) Testing the insulation of capacitors, windings on transformers, E.H.T. circuits, i.e., lag boards, valve bases, any valve resistors that are suspected of being open circuit, giving visual indication with values of resistors from 0-500 megohm, a test which normally calls for expensive apparatus. Ideally suitable for testing motor vehicle wiring systems and spark plugs, sensitivity better than 500 megohms. (2) Null indicating for bridge circuits, etc. (3) If connected to A.V.C. (A.C.) line of receivers it will serve as a sensitive visual indication for receiver alignment. Operates from 200-240-volt A.C. 40-60 cycles supply. Power consumption 5 watts. Completely assembled and ready for use in a handy portable steel case, size 6 1/2 in. x 5 1/2 in. x 5 in. Price 37/6 each, plus 2/6 post and packing.

BOMB-SIGHT COMPUTOR, MARK XIV, with two 24 v. A.C./D.C. motors, a 24-v. repeater motor, Gyro unit, dozens of gear wheels and aneroids, etc. Ideal for model makers, etc. Brand new in cases (the cases are worth at least 15/-). Price 37/6, each, plus 7/6 carriage.

INFRA-RED RECEIVER, TYPE 50/280L. As advertised by us in January issue of "Wireless World." We have received a further small supply (in working order) and we offer these receivers at 23/10/- each.

SANGAMO MOTOR UNITS. These are brand new pre-paid meter movements with dozens of gears and a Sangamo-Weston 200-250 v. A.C. 50 cycles motor (silent running), has numerous applications (clockmaking, etc.). Price 10/6 each, plus 1/3 post.

RELAY UNIT BY LONDEX. Containing 2,000 Ω relay (2 makes, 1 break, heavy duty contacts), with a slight delay chain of 50 Ω wirewound resistor, 1,500 Ω slider resistor and a 200 mfd. 12 v. condenser, mounted on a bakelite base. Will operate on 24-30 v. D.C. Brand new in original cartons. Price 8/6 each, plus 1/6 post.

SPECIAL OFFER OF CURRENT STOCK CONDENSERS. NOT GOVT. SURPLUS. 20 mfd. 500 v. Electrolytic, at 2/6 each; 10 for £1. 3.3. pf. and 1.5 pf. Ceramicons at 3/- doz.; 30/- per gross.

COAXIAL CABLE. 75 to 30 Ω impedance. Brand new current stock, 1/2 in. dia. Available in following lengths 18 yds., 19 yds. and 20 yds. Price 6d. per yd., plus 1/- postage.

HIGH-INDUCTANCE R.F. CHOKE. Suitable for use in RINGING CHOKE, E.H.T. UNIT, as described in "W.W.," December, 1953 (page 603). This choke used with 807 Valve gives 4 kv. 350 mA. Brand new, a 5/- each, post paid.

VCR159A G.B. TUBE. Complete with base and metal screen, 25/- each, plus 2/- post and packing.

ROMAC VACUUM PUMP (Rotary Vane Type). Ideal where air pressure is required, viz., paint sprayers, etc. Brand new at 15/- each, plus 2/- post.

AMPLIFIER UNIT, TYPE A1271 Containing EF36 valve, 400 Ω Relay (4 makes 2 breaks), 10,000 Ω Pot., resistors, condensers, etc. In black metal case, 5 1/2 in. x 5 1/2 in. Brand new at 7/6 each, plus 1/6 post.

HALF-WAVE TRANSFORMERS. Input 230 v. output 200 v. 60 mA. 6.3 v. 1.5 amp. Price 7/6 each, plus 1/6 post.

POLYTHENE RODS. 5/16 in. dia., 1 1/2 in. long, at 6/- doz.
TRANSLUCENT PROJECTION SCREENS (size 15 1/2 in. x 12 1/2 in.). As used in Projection Television and Epidiascopes. Price 7/6 each.

90 COMMERCIAL ST., NEWPORT, MON. Tel. 4711
Also at 15 Wyndham Arcade, Cardiff

All mail orders and enquiries to Newport branch please

SOLE IMPORTERS

of

RONETTE MICROPHONES

Trianon-Electric Limited

95 Cobbold Road, London, N.W.10

Telephone: WILlesden 2116

Enquiries from Industry invited

POLYTHENE

H. F. EQUIPMENT

(AMBYTHENE BRAND)

COIL FORMERS

CHOKES

STAND-OFFS

FEED-THROUGHS

Send for particulars and Samples

AMPLEX APPLIANCES (KENT) LTD.

19, PARTMOUTH ROAD, HAYES, BROMLEY, KENT.

(RAVensbourne 5531)

All export enquiries to

ANTEX LTD., 3, TOWER HILL, LONDON, E.C.3

***Attractive Opportunity
for***
TECHNICAL ENGINEERS

in New Acoustic and Vibration
 Research Laboratories

FOR more than twenty-five years we have given to the trade and the enthusiast the service most suited to their individual needs. This policy has been justified by the increasing demand for our loudspeakers and equipment.

To assist us in our future endeavours we are building a new and much larger Laboratory which will be on the most up-to-date lines, and will give even greater facilities than our present Laboratory. This will include an anechoic chamber which has been designed to meet a larger number of exacting requirements including the measurement of transient performance of loudspeakers under any desired conditions, as well as all

standard measurements encountered in acoustic design. The chamber itself is resiliently mounted to isolate structurally-borne vibration. Among the facilities being provided is an audio theatre whose reverberation characteristics will be sufficiently variable to enable it to simulate a wide variety of domestic listening conditions. The new Laboratory will be installed with apparatus necessary for the thorough investigations of all magnetic and electro acoustic phenomena.

The scope of this new enterprise covers not only our work in the acoustic field but also extends to our activities in controlled vibration applications and transformer design.

In consequence of this project, vacancies arise for additional engineers having good qualifications and experience in either of the following spheres:—



***Loudspeaker
Engineers***




***Vibrator
Engineers***

Applicants should state age and qualifications. All replies should be in writing, will be treated as confidential, and should be addressed to the Managing Director.



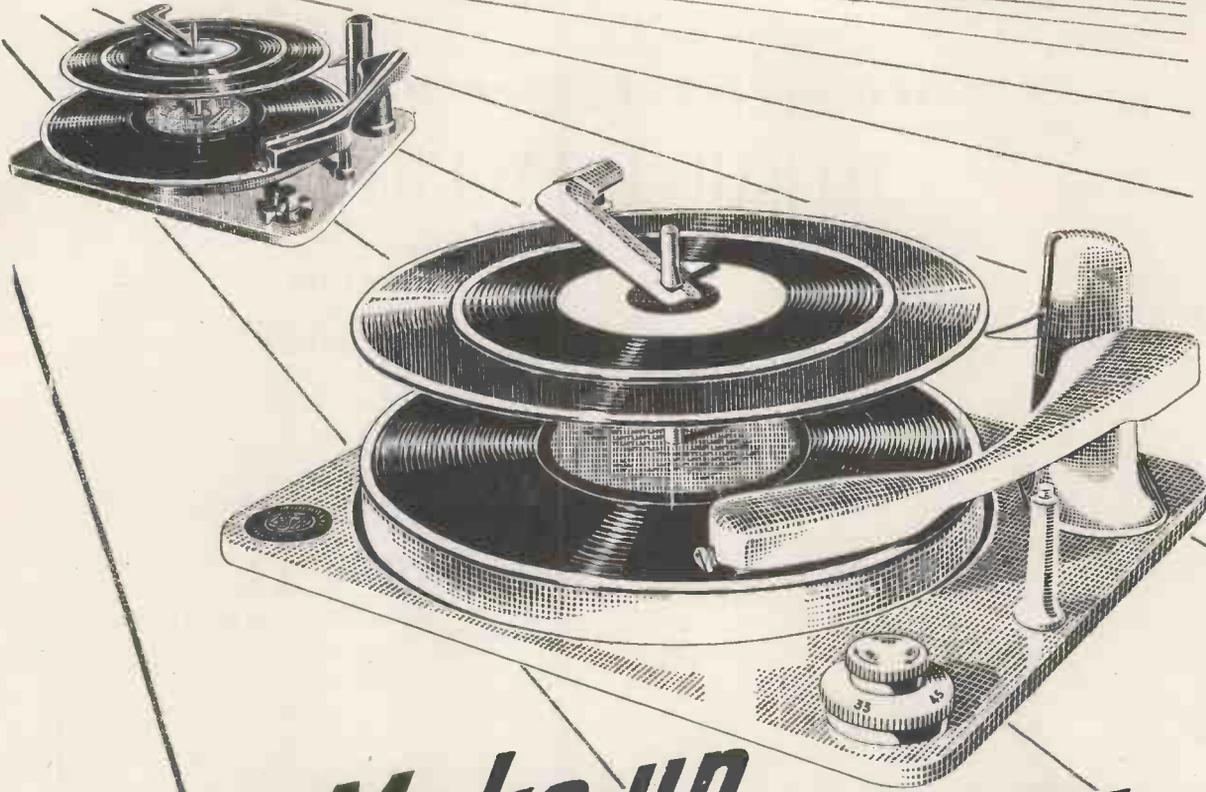GOODMANS INDUSTRIES LTD., AXIOM WORKS, WEMBLEY, MIDDX.



New Make-up for famous features

Everyone knows the Monarch couldn't be better, but the universally acclaimed features have been given a new-look. It's fresher—smoother looking—superfinely finished. In fact it's a new conception that still stars—

- ★The 'Magidisk'—that exclusive feature of the Monarch that selects any record, any size, in any order.
- ★The quickest changeover that gives uninterrupted pleasure.
- ★The hidden music discovered by the BSR dual stylus cartridge.
- ★The control—so simple—so handy.

That is why it is agreed that the Monarch is the World's Finest and most wanted Auto-changer.



WORLD'S FINEST AND MOST WANTED AUTOCHANGER

BIRMINGHAM SOUND REPRODUCERS LTD. OLD HILL, STAFFS. ENGLAND

Wireless World

RADIO, TELEVISION
AND ELECTRONICS

43rd YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK, M.I.E.E.


Editor: H. F. SMITH

MARCH 1954

In This Issue

EDITORIAL COMMENT	101
SQUANDERED V.H.F. CHANNELS. By <i>J. R. Brinkley</i> ..	103
CATHODE FOLLOWER OSCILLATOR. By <i>Thomas Roddam</i>	106
MEASUREMENT OF HARMONIC DISTORTION. By <i>T. D. Conway</i>	110
ELECTRONIC ANALOGUE COMPUTING. By <i>Raymond B. Quarmby</i>	113
BOOKS RECEIVED	118
SURFACE-BARRIER TRANSISTORS	119
TRANSISTORIZED MEGOHMMETER. By <i>P. B. Helsdon</i> ..	121
WORLD OF WIRELESS	124
LETTERS TO THE EDITOR	127
SHORT-WAVE CONDITIONS	128
FREQUENCY SHIFT RADIO TELEGRAPHY. By <i>D. H. C. Scholes</i>	129
FOCUSING CATHODE RAYS. By " <i>Cathode Ray</i> "	133
AWARDS FOR TECHNICAL AUTHORS	137
IMPROVED RADIO ALTIMETER. By <i>A. Bloch, K. E. Buecks</i> and <i>A. G. Heaton</i>	138
ATTENUATORS FOR HIGH FREQUENCIES. By <i>R. F. Privett</i>	141
MULTIPLEX F.M. BROADCASTING	145
VIBRATORY GYROSCOPE	146
MOBILE FLIGHT SIMULATOR	147
MANUFACTURERS' PRODUCTS	148
RANDOM RADIATIONS. By " <i>Diallist</i> "	150
UNBIASED. By " <i>Free Grid</i> "	152

PUBLISHED MONTHLY (last Monday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. Telephone: Waterloo 3333 (60 lines). Telegrams: "Ethaworld, Sedist, London." Annual Subscription: Home and Overseas, £1 7s. 0d. U.S.A. \$4.50. Canada \$4.00. BRANCH OFFICES: Birmingham: King Edward House, New Street, 2. Coventry: 8-10 Corporation Street. Glasgow: 26B Renfield Street, C.2. Manchester: 260, Deansgate, 3.

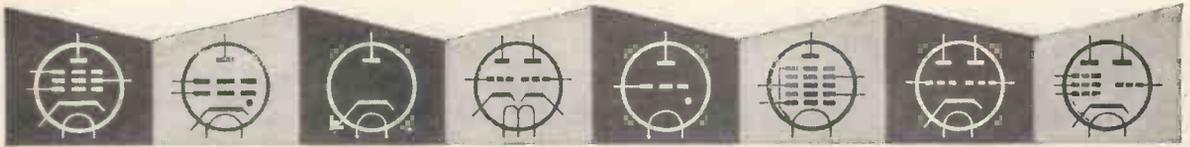

VALVES, TUBES & CIRCUITS

15. VALVES FOR V.H.F. TELEVISION RECEPTION

The advent of television transmissions in the frequency range of 174 to 216 Mc/s (Band III) will mean that receivers must be capable of receiving signals radiated at these frequencies in addition to those already transmitted in the range 41 to 68 Mc/s (Band I).

Reception of signals at the higher frequencies involves changes in the input and frequency changer stages of present-day superheterodyne receiver designs. To meet these requirements the Mullard "World Series" of television valves has been augmented by the introduction of two new types:—

PCC84—Double triode for use as a cascode amplifier in V.H.F. input stages.


PCF80—Triode pentode for use in frequency-changer stages.

As with most of the other "World Series" valves, these new types use the B9A (noval) miniature nine-pin base, have heaters suitable for inclusion in a 300 mA series chain, and can operate with a receiver h.t. supply of 180 volts.

PCC84. The double triode is designed for use as a cascode amplifier, i.e. one triode section operates as a neutralised grounded-cathode amplifier and the other section as a grounded-grid amplifier. The two sections are then connected in series across the h.t. supply, the anode of the first section having a direct connection to the cathode of the second section. The cascode arrangement results in a low noise level for the input stage being achieved in the first section, combined with high gain resulting from use of the grounded-grid connection in the second section.

PCF80. The triode pentode, having separate electrode systems for triode and pentode sections, is used in the frequency changer stage. The triode section, connected as a local oscillator, is in a Colpitts circuit. The oscillator voltage and the input signal from the PCC84 are mixed either inductively or capacitively on the control grid of the pentode section. This section functions as the mixer stage, its performance depending considerably upon the choice of circuit components to give optimum values of conversion conductance and input damping.

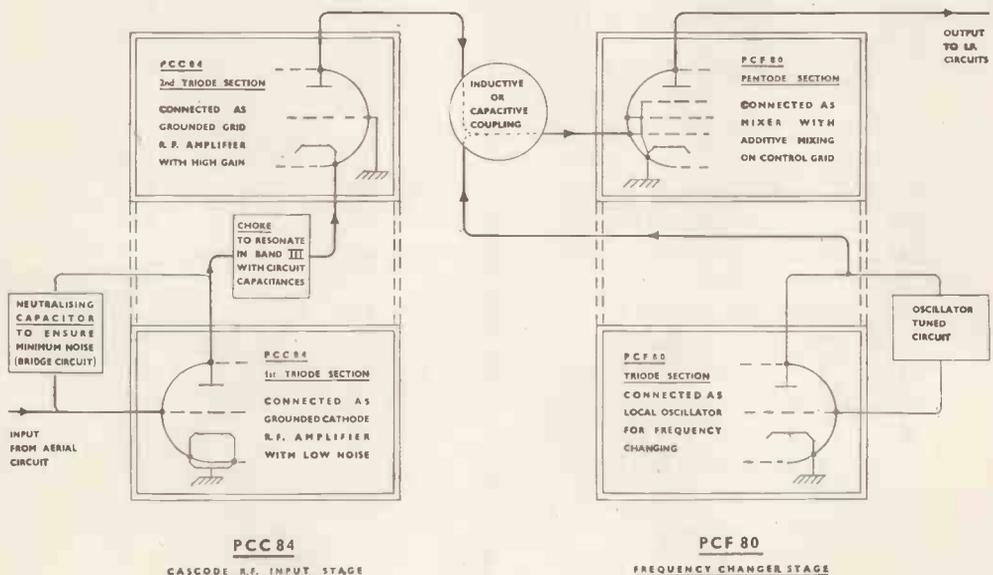The accompanying functional diagram illustrates the basic mode of operation of these valves when used in the "front-end" circuit of a television receiver for use in Bands I and III.



Reprints of this advertisement, together with additional data, may be obtained free of charge from the address below



MULLARD LTD., Technical Publications Department, Century House, Shaftesbury Avenue, W.C.2.

Build your own MODERN

5-CHANNEL large screen TV

The MAGNAVUE receiver, incorporating the latest techniques, gives excellent performance and its large-screen, flat-faced, aluminium-backed Brimar Teletube gives extra bright pictures.

EASY to BUILD



and reduces home construction to the simplest possible proportions. Anyone with previous experience in the construction of radio receivers, and an elementary knowledge of the principles of TV circuitry, can build it.

Ask for this booklet

—its popularity has necessitated the issue of a

THIRD EDITION

A number of circuit modifications have been introduced to give improved performance. The text has been re-written and new drawings and photographs have been prepared. The first step towards building this outstandingly modern TV Receiver is to fill in the application form and post it NOW.



BRITISH MADE

BRIMAR

VALVES and TELETUBES

Please send me constructional details for the LARGE SCREEN TV. I enclose 6d. Postal Order to cover packing and postage.

NAME

ADDRESS

.....
.....

Standard Telephones and Cables Limited FOOTSCRAY, SIDCUP, KENT


2 New

MODELS

~~acos~~ quality crystal microphones at a reasonable price

MIC 33-1: A crystal hand or desk omni-directional microphone for the high quality public address and tape recording field, incorporating a specially designed acoustic filter giving a response flat from 30 to 7,000 c.p.s.

RETAIL PRICE £2-10-0d.

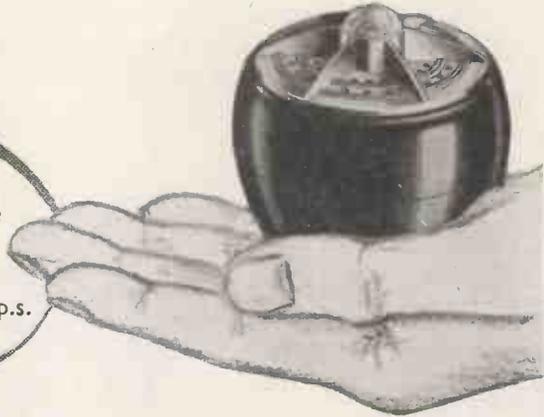

Ideal for tape and disc recording, P.A. and amateur radio.

MIC 35-1: A general purpose hand microphone of robust construction with substantially flat response from 50 to 5,000 c.p.s. Suitable for recording apparatus, Public Address equipment etc.

RETAIL PRICE £1-5-0d.



always well ahead

ACOS devices are protected by patents, patent applications and registered designs in Great Britain and abroad.

THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products and the suppression of electrical interference


Measurement of the Characteristics of Television Aerials

It is necessary to measure the performance of television aerials to enable the relative merits of different installations to be compared. The measurements must be related to the performance of an average aerial installation and it is well known that the presence of objects near to an aerial will change its characteristics. It is impossible, however, to define an average house on which the measurements should be carried out, and it would be extremely laborious to measure the characteristics on a large number of houses, and average the results. It is for this reason that all measurements of the characteristics of aerials should be carried out above flat ground, well away from surrounding objects. It must be assumed that in a practical installation there will be an equal chance of surrounding objects enhancing or reducing the performance of the aerial. Measurements on an open site will then simulate the conditions on an average house.

It is possible to make a direct measurement of the gain of an aerial, i.e., to measure the amplitude of the signal delivered by the aerial to the receiver, and in particular to make a comparison between any aerial and a half-wave dipole. A half-wave dipole is chosen as a reference for gain measurements for several reasons. It is simple to construct and the relation between the strength of the incident signal and the voltage across its terminals can be determined from theoretical considerations. It is ideal for horizontally polarized signals, but in the case of vertically polarized waves, as in the majority of television transmissions in this country, there is a complication from the influence of the mast supporting the dipole. This can be overcome, however, by using either a "sleeve" dipole in which the supporting mast is inside the lower element, or a unipole above a horizontal reflecting plane. In practice misleading results are sometimes obtained when aerials are compared with a normal dipole, due to the influence of the mast. So as to overcome this without resorting to a special dipole, measurements are often made relative to "H" type aerial.

The gain measurement of an aerial can be carried out as follows. An open site on flat ground is chosen well away from trees, houses, telephone wires and other

objects which might cause reflections of the signal. An ideal site is a disused airfield, but unfortunately this is often not available in a given area. The dipole aerial is now erected to a height of about 50ft. and moved horizontally over a short distance to determine if there is a standing wave pattern present. The aerial under test is now raised in place of the dipole and the direct comparison made of the signal.

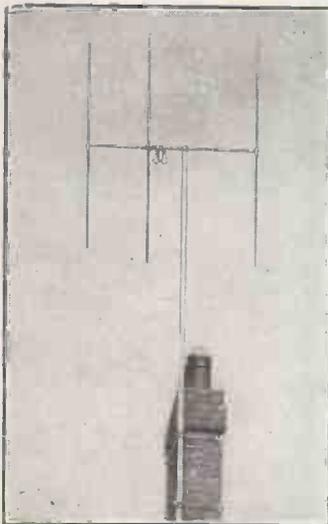

"Junior Multirod"
Band 1 3-Element Array.

Two methods are available for measuring the signal amplitude. In the first, either the mean or the peak white level of the television signal is measured, the measurements always being carried out when Test Card "C" or some steady picture is being transmitted. In the second method the amplitude of the black level is measured, and observations can be made at any time during transmissions. In the latter method the black level is determined by displaying the half line pulses occurring during the frame synchronising signal on an oscilloscope. With this it is often possible to separate the main signal from any ghost that may be present.

The gain measurements described above include not only the intrinsic gain of the aerial but also any mismatch loss between the aerial and the feeder and losses in the feeder itself. Error due to losses in the feeder can be eliminated by using the same length of cable for the dipole and for the aerial being tested. Mismatch losses can only

be evaluated from measurements of the impedance of the aerial. It is possible, however, to deduce the intrinsic gain of an aerial compared with that of a dipole from measurements of its directional characteristics. Experimental measurements of aerial gain by the two methods are in close agreement.

Another important measurement that is required on an aerial is its directional characteristics or its ability to reject signals arriving at the aerial in a direction different from that of the wanted signal.

Here again the measurements must be carried out on an open site, and it is essential that there is no standing wave pattern. In fact the most sensitive method of detecting a standing wave field is to measure the apparent polar diagram of an aerial which is known to have a very deep minima. If a standing wave field is present then the measured polar diagram will be distorted and the depth of the minima will be reduced. The supporting pole should always be included when aerial measurements are made, as removal of this will change many of the aerial's characteristics.

Two other factors must also be determined in order to anticipate the overall performance of an aerial. These are its impedance and band width. The various methods available for the measurement of impedance will not be discussed here. It can be pointed out, however, that the matching requirements for a receiving aerial are far less stringent than those required for a transmitting system. As regards band width, an estimation of the ability of an aerial to accept the required range of frequencies can be ascertained both from impedance measurements and from visual observations on Test Card "C."


Measurement of the above properties of aerials give a very useful yardstick for the comparison of aerials. They are, moreover, usually in agreement with comparisons made over a large number of practical aerial installations.

Band I Aerials

In this and future announcements, we will refer to the T.V. aerials in our present range, which are designed for the reception of existing B.B.C. transmissions, as band I aerials.

Written 24th January, 1954.

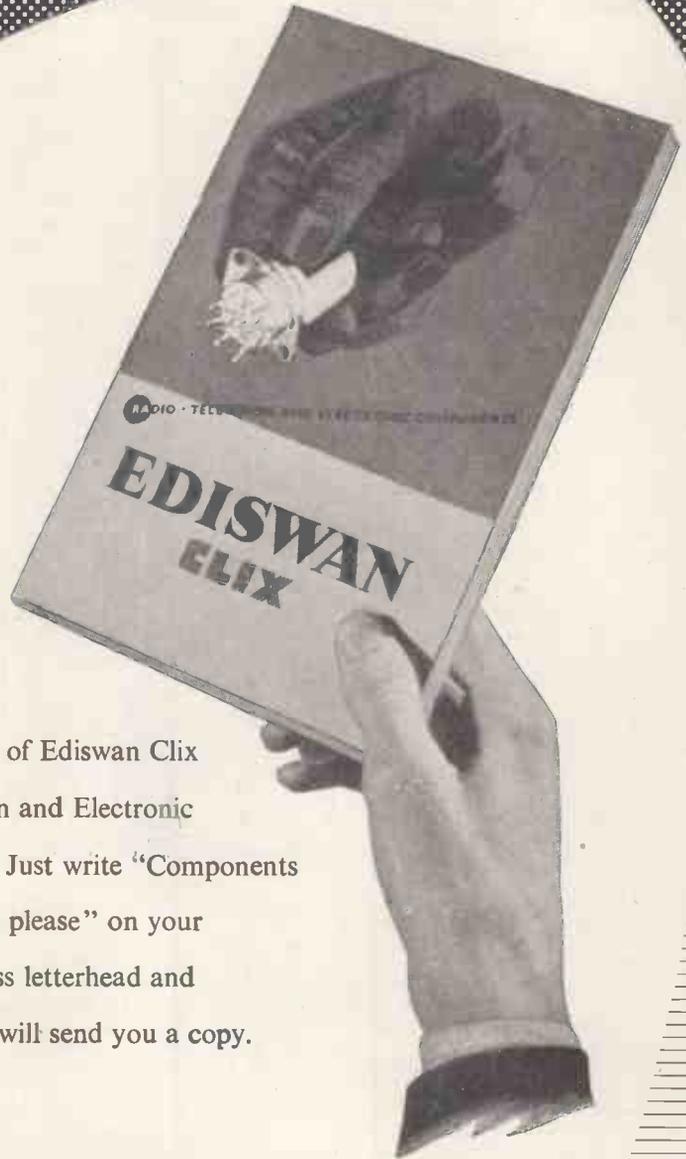BELLING & LEE LTD
GREAT CAMBRIDGE ROAD, ENFIELD, MIDDLESEX, ENGLAND



MANUFACTURERS OF
EQUIPMENT, and
DEVELOPMENT GROUPS
are invited to send
today for this NEW


complete catalogue of Ediswan Clix
Radio, Television and Electronic
Components. Just write "Components
Catalogue please" on your
business letterhead and
we will send you a copy.

EDISWAN

CLIX

RADIO COMPONENTS

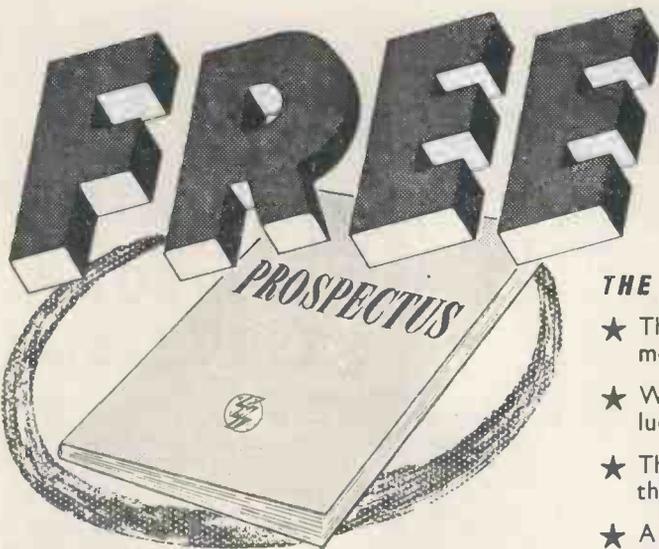THE EDISON SWAN ELECTRIC COMPANY LIMITED, *Member of the A.E.I. Group of Companies*
155 Charing Cross Road, London, W.C.2 and Branches. Telephone: Gerrard 8660. Telegrams: Ediswan, Westcent, London.
C.R.1. Radio Components Sales Office: 21 Bruton Street, London, W.1 Telephone: Mayfair 5543



**POST THE COUPON TODAY
FOR OUR BROCHURE ON THE
LATEST METHODS OF HOME
TRAINING FOR OVER
150 CAREERS AND HOBBIES**

THE ADVANTAGES OF E.M.I. TRAINING

★ Your training is provided by the only Postal College which is part of a world-wide Industrial Organisation.

- ★ The teaching methods are planned to meet modern industrial requirements.
- ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies.
- ★ The student is taken carefully and thoroughly through his chosen subject.
- ★ A tutor is personally allotted by name to ensure private and individual tuition.
- ★ Free advice covering all aspects of training is given to students before and after enrolment with us.

NEW

LEARN THE PRACTICAL WAY

With many courses we supply actual equipment thus combining theory and practice in the correct educational sequence. The equipment, specially prepared and designed, remains your property. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography and Commercial Art, Amateur S.W. Radio, Electricity, Languages, Mechanics, etc.



PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME

Accountancy	Customs & Excise Officer	M.C.A. Licences	Secretaryship
Advertising	Draughtsmanship	Mechanical Engineering	Sheet Metal Work
Aeronautical Engineering	Economics	Motor Engineering	Shorthand & Typing
Automobile Engineering	Electrical Engineering	Photography	Sound Recording
Banking	Electronics	P.M.G. Licences	Structural Engineering
Book-keeping	Fashion Drawing	Police Production	Telecommunications
Building	Heating & Ventilating Engineering	Public Speaking	Television
Business Management	Industrial Administration	Radar	Time & Motion Study
Carpentry	Journalism	Radio & Television Servicing	Tracing
Chemistry	Languages	Radio Engineering	Welding
Civil Service	Marine Engineering	Refrigeration	Writing
Civil Engineering	Mathematics	Retail Shop Management	Workshop Practice
Commercial Subjects		Salesmanship	Works Management
Commercial Art & Drawing		Sanitation	and many others.

Also courses for University Degrees, General Certificate of Education, B.Sc.Eng., A.M.I.Mech.E., L.I.O.B., A.C.C.A., A.C.I.S., A.M.Brit.I.R.E., A.M.I.I.A., City & Guilds Examinations, R.S.A. Certificates, etc.

Courses from £1 per month

EMI

INSTITUTES

THE ONLY POSTAL COLLEGE WHICH IS PART OF A WORLD-WIDE INDUSTRIAL ORGANISATION

POST THIS COUPON TODAY

Please send without obligation your FREE book.

E.M.I. INSTITUTES Dept. 127k,

43 Grove Park Road, London, W.4. Phone: Chiswick 4417/8.

NAME

ADDRESS

SUBJECT(S) OF INTEREST

SenTerCel H.T. rectifiers

from **125V 30 mA**
to **250V 325 mA**

Specially designed for use in domestic Radio & Television receivers, these miniature rectifier stacks have an established position with manufacturers to whom reliability, small dimensions and low costs are important.

FEATURES

- Instant starting — no warming-up period
- Unlimited instantaneous overload
- No limit to size of reservoir capacitor
- Simple mounting—no valve holder
- Withstand overloads such as charging current of de-formed electrolytic capacitors
- Low heat dissipation
- Practically indestructible in service
- Simple wiring—two connectors only
- Small size . . . low weight
- Low cost

TYPE	RM0	RM1	RM2	RM3	RM4	*RM5
Maximum ambient temperature	35°C	55°C	55°C	35°C	55°C	35°C
Maximum output current (mean)	30mA	5mA	60mA	100mA	90mA	325mA
Maximum input voltage (r.m.s.)	125V	125V	125V	125V	250V	250V
Maximum peak inverse voltage	350V	350V	350V	350V	700V	700V
Max. instantaneous peak current	Unlimited	Unlimited	Unlimited	Unlimited	Unlimited	Unlimited
Weight	0.82 oz.	1 oz.	1.4 oz.	2 oz.	4.5 oz.	4.75 oz.

* For use in voltage doubler circuits the peak inverse and maximum input voltages are halved, current output being as for half wave operation.




Standard Telephones and Cables Limited

Registered Office: Connaught House, Aldwych, London, W.C.2

RECTIFIER DIVISION: Warwick Road, Boreham Wood, Hertfordshire. Telephone: Elstree 2401

One Way only . . .

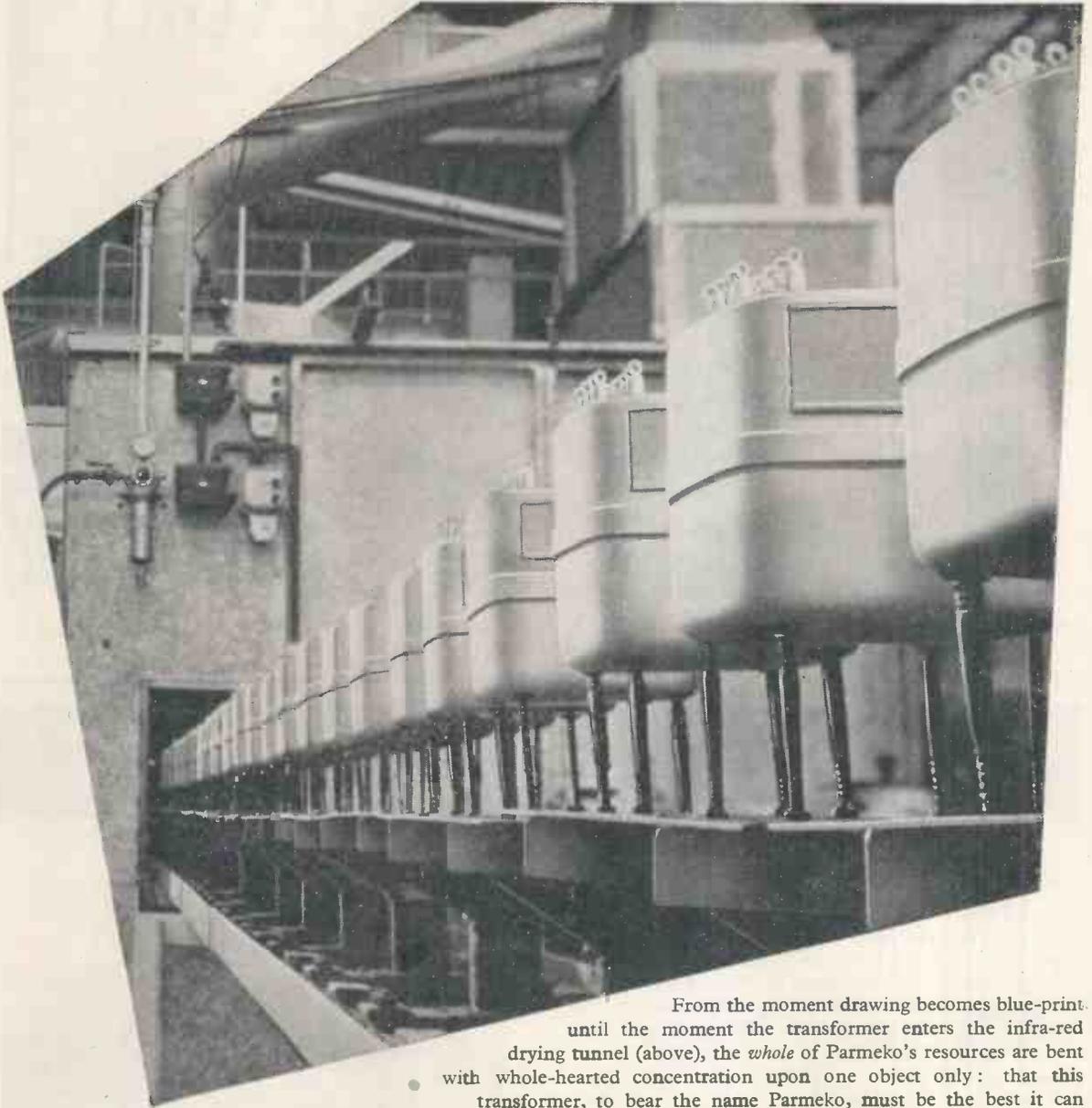


From the moment drawing becomes blue-print until the moment the transformer enters the infra-red drying tunnel (above), the *whole* of Parmeko's resources are bent with whole-hearted concentration upon one object only: that this transformer, to bear the name Parmeko, must be the best it can possibly be. To this end there is an unswerving single-mindedness on the part of everyone in the company. There are many men in the organisation who could lend their skill to the production of other products for the electrical and electronic industries but Parmeko insist that they shall be "master of one." How well they succeed is most strikingly shown in the orders that are repeatedly given by some of the largest manufacturers in the world to . . .

The firm with the one-track mind

PARMEKO of LEICESTER

MAKERS OF TRANSFORMERS for the *Electronic and Electrical Industries*

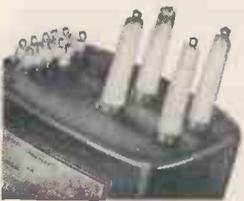


ENDORISING 3-D RADIO

We are indebted to Mr. C. E. Herbert, a musician and great lover of music who has one of our Radiograms, for the following comments:—

“ May I add that I have a Radiogram of yours which is giving wonderful service and I would not part with it, as it is without question the finest reproduction, I feel sure, that one can possibly obtain from any radio to-day.”

D.X. PLUS FOUR RADIOGRAM ..	£62.1.0 (including purchase tax)
3-speed Model	£64.1.5 (including purchase tax)

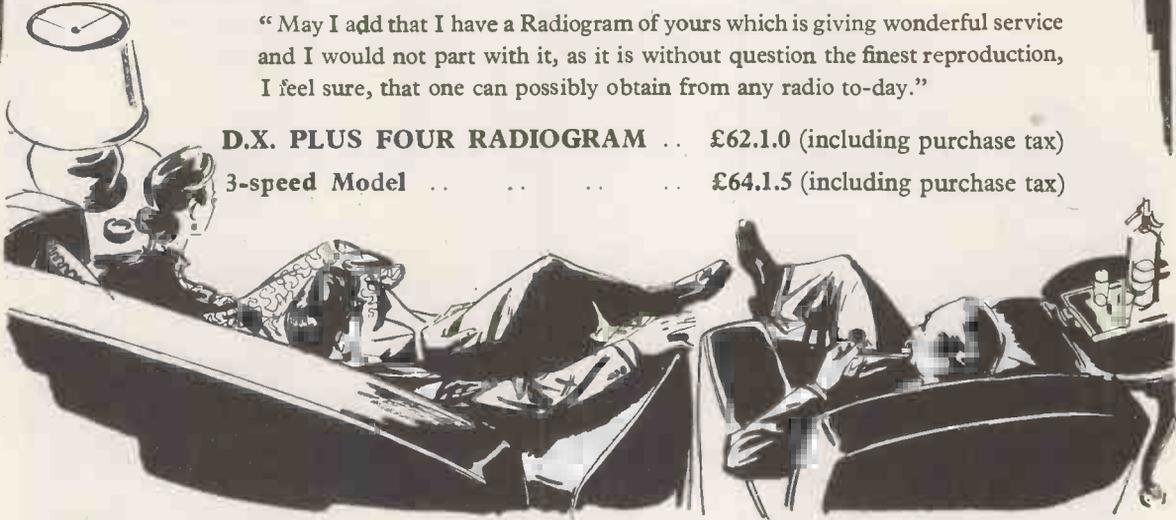

SOUND SALES LTD., WEST STREET, FARNHAM, SURREY Farnham 6461-2-3
LONDON AGENTS: WEBB'S RADIO—HOLLEY'S RADIO

NEW!


EXPERIMENTAL OUTFITS

LEARN THE PRACTICAL WAY

Specially prepared sets of radio parts (which you receive upon enrolment) with which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at very moderate cost.

EASY TERMS FROM £1 A MONTH

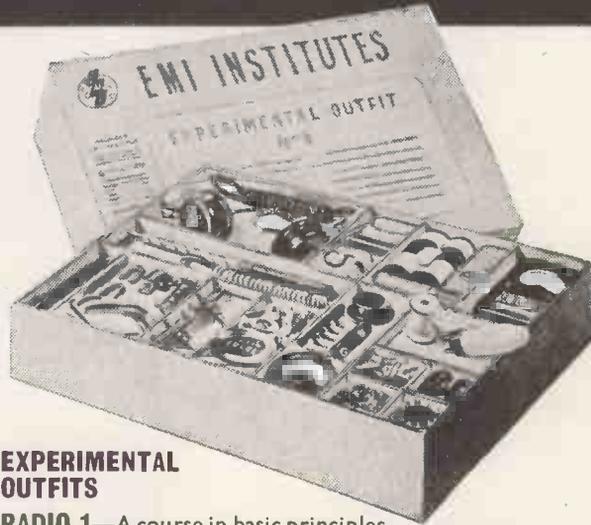A tutor is available to give individual help and guidance throughout the Course.



POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses:
To: E.M.I. INSTITUTES, Dept. 16X, 43 Grove Park Rd.,
Chiswick, London, W.

NAME

ADDRESS

SUBJECT(S) OF INTEREST

EXPERIMENTAL OUTFITS

RADIO 1—A course in basic principles.

RADIO 2 — Instruction and equipment from which you build a Radio Receiver.

TELEVISION — Instruction and equipment for building a Television Receiver.


Also for Mechanics, Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages.

E.M.I. INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation.

VORTEXION TAPE RECORDER

Type 2A

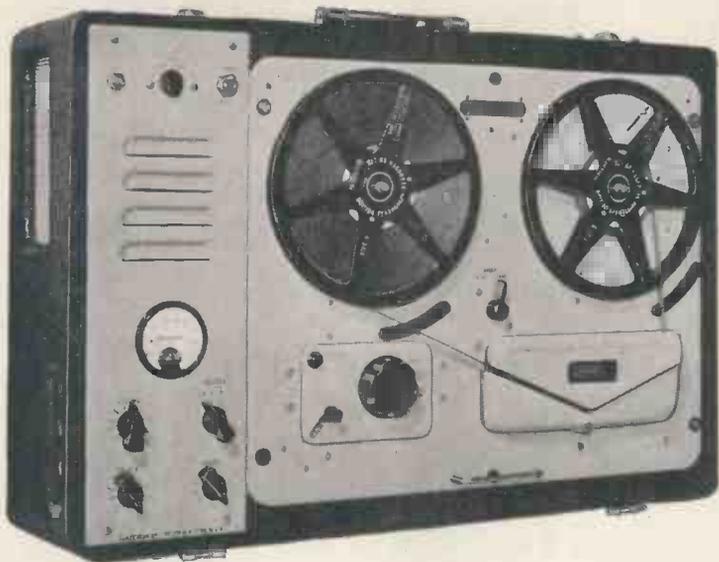

THE FOLLOWING
TECHNICAL REPORT
by
P. WILSON, M.A.
APPEARED IN THE JANUARY
ISSUE OF
"THE GRAMOPHONE"

Vortexion Tape Recorder, Type 2A
Vortexion Ltd., 257, The Broadway,
Wimbledon, S.W.19. (Price £84)

Specification :

Twin Track Recording Speed: 7½ in. and 3½ in. per sec.

Spools: Normally 1,200ft., but can take up to 1,750ft.

Recording Time: 1,200ft. spools—½ hr. per track at 7½ in., 1 hr. per track at 3½ in. 1,750ft. spools—¾ hr. per track at 7½ in., 1½ hrs. at 3½ in.

Frequency Range from 50 to 10,000 c.p.s.: Amplifier response is within 1½ db.

Input: (1) Microphone (preferably Ribbon) 15 to 30 ohms with full loading on 8 microvolts. Balanced or not, so that 100ft. unscreened cable can be used if desired. Model for Crystal microphone with input of 1 millivolt can be supplied. (2) For Radio feeder unit or Gramophone p/u or even crystal set. Fully loaded by 17 millivolts on ½ megohm. Unbalanced.

Output: 3½ watts at 15 ohms, i.e. up to 7 volts. Internal speaker. Jack for external speaker or to feed any other amplifier of any impedance greater than 15 ohms.

Monitoring: Internal loudspeaker may be used to monitor during recording and there is also a meter to monitor recording level. This meter may also be used for setting bias level to suit different makes of tape. Best settings for different makes are specified.

Cabinet: Flat rexine case with carrying handle and detachable lid. All controls on tape deck or extension. Input and output connections inset in side of case.

Dimensions: 8½ in. by 22½ in. by 15½ in.

Weight: 48 lb.

This instrument, though on the heavy side as portable tape recorders go, is so nicely balanced as to be fairly easily carried. It is certainly very convenient.

I collected a sample myself from the factory, took it home and started a test straightaway. It gave no trouble at all during the whole fortnight I had it in operation. During the period, I recorded test frequencies, radio and record performances and also made direct recordings of speech and music through a Reslo Ribbon Microphone.

I paid particular attention to detect "wow" or "flutter," since these were not mentioned in the makers' specification. I was aware that the Wearite Tape Deck which is used in this model has a good reputation in this respect, but my sample was even better than the standard: by ear I detected nothing at all at any part of the test.

In my frequency test on 7½ in. I found that the range of response was as specified, though from input to output (i.e. through the tape twice, once in recording and once in replay) the response was falling above 9 kc. and below about 100 cps. The amplifier has, for playback but not for recording, both bass and treble controls. The treble control can either attenuate or boost; the bass control only attenuates. In playback I found it best to have full bass response and a slight treble boost.


At these settings with my external loudspeaker system the response was very satisfactory, and even with the internal speaker it was quite good. Indeed I found myself more than once listening with delight to the reproduced music rather than getting on with my testing. The makers' claim that the reproduction is "equal to orchestral recording" is fully borne out. For speech, of course, it is practically perfect.

For a medium-priced recorder I consider this instrument to be wonderful value, and I can thoroughly recommend it.

VORTEXION LIMITED, 257-263, The Broadway, Wimbledon, London, S.W.19

Telephones: LIBerty 2814 and 6242-3

Telegrams: "Vortexion, Wimble, London."

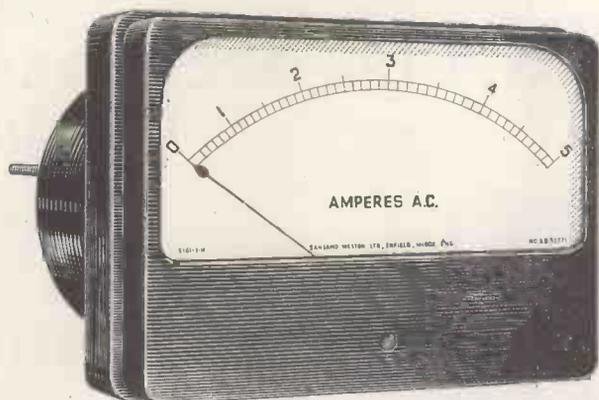

WESTON ELECTRICAL INSTRUMENTS INCLUDE :—
 LABORATORY STANDARDS · SUB STANDARDS ·
 FIRST GRADE PORTABLE INSTRUMENTS · ROUND,
 RECTANGULAR AND EDGEWISE SWITCHBOARD AND
 PANEL INSTRUMENTS · PORTABLE TEST SETS ·
 RELAYS · AIRCRAFT INSTRUMENTS

SANGAMO WESTON LIMITED

Enfield, Middlesex. Tel: Enfield 3434 (6 lines) & 1242 (6 lines) Grams: Sanwest, Enfield

Scottish Factory: Port Glasgow, Renfrewshire. Port Glasgow 41151.
 Branches: London, CHAncery 4971 · Glasgow, Central 6208 · Manchester, Central 7904 · Newcastle-on-Tyne,
 Newcastle 26867 · Leeds, Leeds 30867 · Liverpool, Central 0230 · Wolverhampton, Wolverhampton 21912
 Nottingham, Nottingham 42403 · Bristol, Bristol 21781 · Southampton, Soton 3328 · Brighton, Brighton 28497

THE WESTON RANGE OF RECTANGULAR INSTRUMENTS

Supplied as D.C. moving coil, A.C. rectifier and H.F. thermocouple types; also A.C./D.C. moving iron types. Four sizes are available with scale lengths of 2.5in., 3.2in., 4.2in. and 6.25in.

Front of panel or back of panel mounting may be adopted as desired, and if the former method is used there is complete interchangeability with existing round models. The 3.2in. and 4.2in. scale instruments are available with either illuminated or non-illuminated dials; the 2.5in. and 6.25in. scale instruments being available only with non-illuminated dials.

WESTON Measuring Instruments

Tune in with

Delanco

REGD.

COIL FORMERS



Wind your coils on "Delanco" S.R.B.P. formers, and improve the performance of your set. "Delanco" formers have been developed after years of research in this field, and in practically every well-known radio or T.V. set, "Delanco" formers are giving trouble-free service. We have a large number of standard types, but maybe your Design Department wants something new? Contact us, giving details, and we will produce their "brain-child" with the minimum of trouble or delay.

ANGLO-AMERICAN VULCANIZED FIBRE CO. LTD.

Cayton Works, Bath Street, London, E.C.1
 CLE 3271.

VHF TELEVISION AND THE RECEIVER I.F.

WITH the possible introduction of another band for Television in this country, bringing with it several alternative programmes, the choice of receiver I.F. becomes even more vital than it now is.

For Band 1 reception, it has been known for many years that the receiver I.F. must be clear of amateur transmitter frequencies to avoid interference from these transmissions.

The receiver should also be inherently clear of internally generated whistles and patterns arising from beats between the signal and harmonics of the I.F. and local oscillator. The practice of re-tuning the I.F. for different channels, or inserting tunable filters to avoid patterns that would otherwise occur, reduces the flexibility of the superheterodyne principle, and is likely to lead to difficulty should the owner move, or additional stations come into operation.

At the time of the erection of the Sutton Coldfield Station, a 34 Mc/s I.F. was decided upon by "His Master's Voice" Engineers as the best means of overcoming all the difficulties at that time envisaged, two of which are indicated above. With a choice of programmes, two other problems arise. Their solutions underline the wisdom of the original decision.

Firstly, the local oscillator of the television receiver must not radiate on the channel of another television station in the same area. This has already occurred in the Brighton district, where receivers tuned to Truleigh Hill on 56.75 Mc/s and employing a low oscillator and I.F. of 11-12 Mc/s created havoc on receivers still tuned to 45 Mc/s.

By very careful screening, and by use of filters it might be possible on Band 1 to reduce oscillator radiation to such proportions that only in fringe areas will serious trouble arise. On Band 3, however, the efficiency of the R.F. valve as a buffer to prevent radiation is seriously reduced due to the low reactance of the stray and inter-electrode capacities.

Furthermore, aerial filters are of no avail as they would effectively remove other transmissions to which the receiver may be tuned. The 34 Mc/s I.F. gives complete freedom from radiating oscillator interference over at least the seven adjacent channels

which it is hoped will be made available for T/V. And hence while it is highly desirable that television designers should reduce oscillator radiation to a minimum, if a 34 Mc/s I.F. is chosen, at least the residual radiation will not put a neighbour's receiver out of action. The 34 Mc/s I.F. receiver may well be styled then a "Good Neighbour Receiver."

A further difficulty arises from the fact that the band-width of the aerial circuit at 200 Mc/s is likely to be of the order of 8 Mc/s, and hence the rejection of the second channel interference on receivers employing a low I.F. is likely to be poor.

It is self evident that with 68 Mc/s separation second channel selectivity is easily obtained with 34 Mc/s I.F.

These problems must be of intense concern to the Television receiver manufacturer and to the dealer interested in his future reputation, because although the customer may initially have no trouble in receiving the first Band 3 programme, buying a receiver in good faith, when an alternative network comes into being, possibly of greater power, his reception may be considerably marred by second channel interference from that network or oscillator radiation from a neighbour's set also tuned to that network.

Adaptors and Converters

Many existing receivers will require an adaptor to receive Band 3 transmissions, and it is obvious that as little modification as possible to the receiver is desirable.

From the considerations indicated above if an existing receiver employs a 34 Mc/s I.F., it will not only be more easily modified, but will be better placed to receive interference free transmissions, and not to disturb other receivers.

ALL THE "HIS MASTER'S VOICE" super-heterodyne receivers manufactured since the opening of the Sutton Coldfield station have employed the 34 Mc/s I.F.

"HIS MASTER'S VOICE"

THE GRAMOPHONE COMPANY LIMITED · HAYES · MIDDLESEX



SHORTAGE OF RADIO and T/V ENGINEERS

There is an assured well-paid future for those trained and willing to train in electronics, radar and radio. Modern industrial techniques demand more and more highly trained personnel and the gap between demand and supply is still widening.

This is your opportunity — write for our free brochures giving full details of courses to:

E.M.I. INSTITUTES

DEPT. 16R, 10 PEMBRIDGE SQUARE, LONDON, W.2.

Telephone: Bayswater 5131/2.

The College associated with a world-wide electronics industry.

IA9

1 YEAR COURSE

We offer full-time day course for one year in the Principles and Practice of Radio and Television.

Next course commences

1st April, 1954.

3 YEAR COURSE

This course in Telecommunication Engineering includes one year's Factory attachment.

Next course commences

30th August, 1954.

Associated with

'H.M.V.'

MARCONIPHONE

COLUMBIA

etc.

CLEARLY the Best of P.A. Speakers



LIST PRICE

£7 Less
Transformer
(No P.T.)

RA 13 REFLEX SPEAKER

Ideal for critical installations where clear speech reproduction is of first importance. Gives three or four times the coverage of conventional cabinet speakers. Excellent as a local intensifier. Handles up to 3 watts.

TRUVOX

*Robust, Reliable,
Really Weatherproof*

The world-famous range of Truvox Public Address loudspeakers includes many models designed for widely varying applications. But all have in common the clarity of reproduction, absolute dependability and magnificent performance under the most exacting conditions which are characteristic of Truvox loudspeakers. The model illustrated is just one example from an infinitely varied range. Write to-day for descriptive folder and price list.

Manufactured by:

ROLA CELESTION LTD.

Ferry Works, Thames Ditton, Surrey.


Phone: Emberbrook 3402-6.

LEAK equipment is unique—

It is acceptable to professional communications engineers for recording and broadcasting. The B.B.C. use several hundreds of the TL/12 Amplifier, and 1,000 are used by other Broadcasting Corporations.



The Vari-Slope

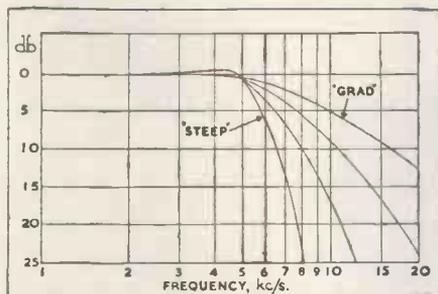

Representing a unique feedback circuit development, the "Vari-Slope" pre-amplifier gives audibly better reproduction. This advance consists of variable slope "electronic" low-pass filters operating on negative voltage feedback principles. No Inductors ("Chokes") are used, and their disadvantages are completely eliminated. The turnover frequencies are 5kc/s, 7kc/s, and 9kc/s, and the slopes of attenuation are continuously variable over the range 5db to 50db per octave.

The filters consist essentially of Twin-T resistor-capacity networks inserted in the return circuit of a single-loop feedback amplifier. The more obvious advantages of this electronic feedback method over conventional choke filters include:—

(a) Improved transient response characteristics (due to absence of chokes having self-capacitance) and the consequent reduction of "ringing."

- (b) Extremely low harmonic and inter-modulation distortion due to negative voltage feedback action.
- (c) No discontinuities in the rates of slope when the slope control is operated, and no change in signal level at frequencies below turnover (Both these faults occur in variable-slope choke filters due to the slope control altering the terminating impedance and the insertion loss.)
- (d) No chokes to cause magnetic hum pickup.
- (e) Smaller size, lighter weight, greater uniformity in production

Frequency amplitude curves for the "TREBLE-3" position (5 kc/s turn-over). Curves of the same slopes are obtained on the other two positions turning over at 7Kc/s and 9Kc/s ("—2" and "—1" positions).

Point-One TL/12 Triple Loop Feedback Amplifier

Used with the "Vari-Slope" pre-amplifier and the best available complementary equipment, the TL/12 power amplifier gives to the music-lover a quality of reproduction unsurpassed by any equipment at any price.

For laboratory use as a stabilised-gain audio frequency power amplifier. For the highest possible standard of disc recording. For the highest possible quality of reproduction from Pickup, Radio, Microphone, Film and Magnetic Tape. For use as a driver amplifier in the speech modulator chain of broadcast transmitters.

27 Gns.

The "Point-One" TL/12 Amplifier is built to a tropical specification and used throughout the world, including:

- The British Broadcasting Corporation.
- The South African Broadcasting Corporation.
- The Swedish Broadcasting Corporation.
- The Swiss Broadcasting Corporation.
- The Italian Broadcasting Corporation.

LIST PRICE IN BRITAIN 12 Gns.



£5. 10s.

Write for fully descriptive literature.

Steep-Cutting Filter

For use with the TL/12 power amplifier and pre-amplifiers preceding the Vari-Slope. This filter unit is of particular interest to the record enthusiast.

H. J. LEAK & CO., LTD., BRUNEL ROAD. WESTWAY FACTORY ESTATE, ACTON, W.3

Phone : SHEpherds Bush 1173/4.

Telegrams : Sinusoidal, Ealux, London.

Cables : Sinusoidal, London.

ELECTRONIC PRECISION EQUIPMENT LTD


A RADIO UNIT FOR SUPERIOR 15

A circuit for a suitable radio unit to fit into our Coronation Console Cabinet has now been completed and thoroughly tested. All the parts are available. The total cost is £5/19/6. Data is included free with orders for parts, or can be supplied separately; Price 2/6.

Note: This radio unit incorporates T.V. control and is also highly suitable for fitting into other televisors. The addition of a radio unit to a televisor is not only worthwhile but is essential where the televisor is kept in a room away from the main radio.

The Superior 15 Corner Cabinet is also available now in light oak, or medium oak to suit your furnishings, and it really does look impressive. The price is £18, plus carriage. H.P. terms £6 deposit, balance over twelve months.


About the Superior 15 itself, if you have not already ordered your set of parts for this, be advised and do so immediately. We are definitely getting down to the last batch of the 15in tubes and once these are gone the Super 15 T.V. cannot be repeated. At £37/10/- for all the parts (including 15in. Cossor Tube) this represents the finest value ever offered to the home constructor. If you doubt your ability to make it then send 7/6 for the data and study this first. Don't forget, we guarantee to help you to get perfect results and, if necessary, for nominal charge, will take in your televisor, completely check over your work, and return it to you in perfect order.

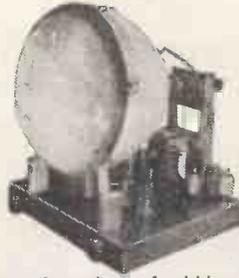

22 1/2 WATT FLUORESCENT LIGHTING

Complete kit comprises Hi-craft 40 watt control unit, starter lamp, lamp holders, clips and wiring diagram. Price, less tube, 22/6, plus 1/6 post. With tube, 30/-, plus 3/6 carriage.

NEW 5 AMP. THERMOSTAT (MINIATURE)

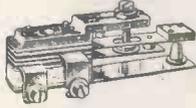

Useful for the control of appliances such as convectors, gluepots, vulcanisers, hot plates, etc. This thermostat is adjustable to operate over the temperature range 50-550 deg. F, fitted with heavy (5 amp. A.C.) silver contacts size 1 1/2in. long x 3/8in. wide, price 8/6, post 6d.; 1 amp. type, 3/6, 2 amp. type, 5/6.

FLEXIBLE COUPLINGS


These are sometimes known as bellows couplings because they will extend as well as bend. They are ideal for joining shafts which are out of alignment and for slug tuning controls where the core has to come in and out. Price 1/9 each.

With one pair of wires and a simple push button you can select any one of four stations without leaving your armchair. This is just one of the many applications of our impulse relay. There are many other purposes to which it can be put. Note they are somewhat soiled, due to storage but mechanically O.K. Price 2/6.

RE-MOTE CONTROL



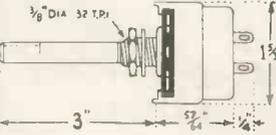TELEPHONE JACK PLUGS
As illustrated 7d. each. Sockets to suit, 10d. each.



VOLUME CONTROLS
We carry a full range of standard size volume controls from 2K to 2 meg. Prices are: less switch, 3/-; Single pole switch, 4/-; double pole switch, 5/- . We can also supply midget-type controls, less switch, 4/-; single pole switch, 5/9; double pole switch, 6/6. Each of these midget controls has a serial number and carries a 12-month guarantee by the makers; they are made on the new moulded track principle and really do perform well.

MAKING TRANSISTORS

Six wire-ended, glass sealed Germanium Diodes. Manufactured approximately two years ago which should therefore be quite suitable for making transistors, as per last month's article. Offered at the very low price of 10/- the six.


T.V. SIGNAL AND PATTERN GENERATOR

Cost of all components, valves, etc., only 29/6. Although this generator can be built and used by any beginner it is at the same time a most useful instrument for the more advanced worker.

It can be tuned to the vision channel and will produce a pattern on the face of the C.R. tube. Alternatively if tuned to the sound channel it will produce an audible signal in the loudspeaker.

Thus, its owner will become independent of B.B.C. transmissions and can fault-find or test at any time. It operates entirely from A.C. mains and is quite suitable for use with superhet or straight receivers.

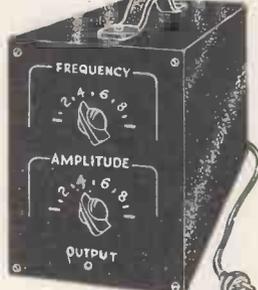A complete kit of parts (in fact everything except the cabinet) with full constructional and operational data will be supplied for 29/6, plus 2/6 post and insurance, alternatively, data is available separately, price 2/6 (credited if you buy the kit later). NOTE. Cabinets as per the illustrated prototype are available price 15/-, plus 1/6 post and packing.




SCAN COILS


Perfectly made by a very famous maker for standard type tubes, we have a limited number only, the price is 12/6 and cannot be repeated once these are cleared, so please act quickly.

THE ELPREQ E.H.T. GENERATOR

This is a made up unit working on the blocking oscillator/overwound amplifying stage principle. It is of moderate power consumption (6.3 volt .8 amp. filament and approx. 59 mA. H.T.) and contains three of the latest BVA all glass valves. Output obtainable ranges from 6 kv. to 9 kv. with normal H.T. rail input but somewhat higher outputs can be obtained with higher H.T. supply. Valve rectification is employed in the output stage. The core of the overwound transformer is kept insulated from chassis in order to give additional protection against possible flashovers. This unit is particularly suitable for those who during the course of their T.V. construction have come to appreciate the advantages of separate E.H.T. supply, but should also prove invaluable as experimental or stand-by high voltage source. Effective screening (not shown in the illustration) is provided, and the dimensions are 6 1/2 x 4 1/2 x 7in. Price 69/6, post, packing, etc., 5/-.

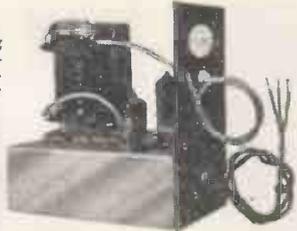


CRYSTAL SET

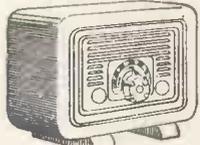

Two waves, uses latest crystal valve—good results without batteries or mains 18/-. Headphones, high resistance, 15/6 per pair.

RELAYS

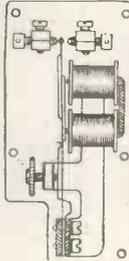

Extra light weight, extra sensitive for high speed or radio control work, weight only 1 1/2 oz., closes on 2 mA., solid platinum changeover contacts, adjustable pressure. Price. 13/6.



12 CELL ACCUMULATOR

This accumulator can be coupled up to give 24 v. with all cells connected in series or 12, 6 or 2 volts in series parallel arrangements. They were originally made for the Admiralty by a leading manufacturer, have never been filled, and are in excellent condition. Each is contained in a wooden crate as illustrated. To clear 10/- each. Post and insurance 2/6.

PYREX AERIAL INSULATORS



Ideal for aerial connections through cabin wall or through panels. Consists of glass dome with threaded rod and terminal ends, and metal fixing flange Price 2/- each.



VIBRATOR UNIT

This unit gives 150 v. at 50 mA. from 4 or 6 v. car battery, also gives L.T. supply, suitable for all dry valves. IT4, IR5, etc. Ex-W.D. Price 15/-, plus 2/6 post.

LAMP HOLDERS

Bakelite, 1/- each or 10/6 doz. Bakelite skirted Batten holder, 1/6 or 15/- doz. Bakelite type threaded for 1/4in. with HO skirt, 1/6. 10 per cent. discount if bought in dozens.


ELECTRONIC PRECISION EQUIPMENT LTD.

7 VALVE 5 WAVEBAND RADIO CHASSIS

GIVE AWAY PRICE

only
**£7 or
47/-**
deposit.

Less valves and power pack

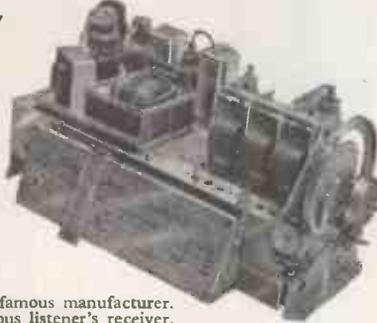

A famous set by a famous manufacturer. Undoubtedly a special listener's receiver. Among many special features are an H.F. stage and tuning indicator. Tunes up to 11 metre band. Price complete with valves but less speaker, £14/19/6. H.P. terms £5 deposit and 12 monthly payments of £1. We have a few left, less valves and power pack, otherwise in good condition; they definitely have never been used. Price £6/19/6, or £2/7/- deposit and 11 monthly payments of 10/9, plus 15/- carriage.

THE INFRAY LAMP

Means real comfort in bed or in workroom or other place where air temperature is low as it emits Infra-Red Rays which not only warm you but relieve pain, if you have any, and keep you healthy.

- Economical because its rays warm you and not the room.
- Costs only 4d. per hour to run (electricity at 1d. per unit).
- Works off lighting circuit (full instructions supplied).
- Absolutely safe for continuous burning, no health or fire risk.
- Ideal for many other uses:—over pet's basket—rearing pup, chicks—over desk—work bench, etc.
- Completely and unconditionally guaranteed for five years.
- All complete and ready to work. Price 36/-, post & pkg. 2/-. Money refunded in full if after seven days' trial you are not completely satisfied.



CARBON RESISTORS
These will now be supplied in individual packets, with the value and wattage clearly indicated.
Prices:
1/4-watt, 5d. each; 1 watt, 6d. each.

L.P. RECORD PLAYER
Made by Decca. Contains B.S.R. motor and Decca pick-up. Although we offer this at approximately half price, it carries same manufacturer's guarantee as if the correct price of £9/9/- were paid. Price £4/19/6, plus 7/6 postage and insurance.

GRAMOPHONE UNIT
BSR 3-speed motor Type MU14 with Chancery pick-up and two crystal heads, one for long playing and one for normal records. £7/7/- plus 3/6 carriage and insurance.

AMERICAN POWER PACK
Built to operate H.R.O. receiver from British mains. Gives 80-100 m/a. smoothed D.C. at 200 volts, also 5 volts and 6.3 volts. Totally enclosed in metal case. An extremely nice unit. Price £2/17/6, plus 5/- postage and insurance.



TOGGLE SWITCHES
Metal body standard size, made by a leading maker. Available with round dolly or with special V cut dolly. State which type when ordering. Price while stocks last only 2/3.

MOVING COIL METER
0-5 m/a. 2in. flush mounting, Bakelite cased, can easily be made into multi-range test meter. Price 7/6 plus 6d. postage.

MINIATURE 7-PIN PLUG AND SOCKET
With non-breakable plastic rubber shroud. Overall size 1 1/2in. long, diameter approximately 3/4in. Price 2/- pair.



CO-AXIAL CABLE
70 to 80 ohms for T.V. by one of our leading manufacturers, medium thickness. Price 8d. yd. cut to your length.

L.F. CHOKES

50 H 30 mA.	6/6
50 H 20 mA.	6/6
30 H 20 mA.	6/6
20 H 10 mA.	5/6
15 H 80 mA., fully shrouded	15/-
10 H 150 mA.	18/-
10 H 100 mA.	15/-
10 H 75 mA.	4/9
10 H 60 mA.	4/9
5 H 250 mA., fully shrouded	20/6

Please add 1/- post. & pkg.

COILS
T.R.F. Long and medium wave, complete with circuit diagram, 5/6 pr. Superhet, long wave 900-2,000 metres, medium wave 185-550 metres, short wave 16-50 metres with aerial and oscillator coils that is set of six. Coils with circuit diagram, price 10/6.

GLASS INSULATOR
Complete with iron bracket for mounting on pole, wall, tree, etc. Also suitable as aerial insulator. Price 3/6 each.




BEDROOM-NURSERY MAINS MIDGET RADIO

All the parts, bakelite cabinet, valves, knobs, back—in fact everything will cost you only £3/15/- (plus 2/6 postage) which, we think you will agree, is not too much to spend on your dear ones. The set is economical to run, too, for it uses only three valves in a special reflex T.R.F. circuit which gives ample power combined with good tone. Incidentally if you wish to give the sets to young children who not decorate the cabinet with a few suitable transfers? These can usually be obtained from local handicraft shops. Circulating and construction data free with the parts or available separately at 1/6.




THE ELPREQ "SELECTIVE FEED-BACK" AMPLIFIER

The amplifier is fitted with independent bass and treble control, both connected through different feed-back loops so that no "cut" at all in the ordinary sense is applied. The variation which can be achieved, by applying various degrees of negative feedback in the higher and lower ranges of the sound strata will accommodate all individual tastes. We strongly recommend a 12in. speaker in order to make the fullest use of the instrument's of components available at once at £2/19/6, post, etc., 2/6. Booklet separate 1/6. 12in. speaker to suit £3, post free if bought with amplifier.

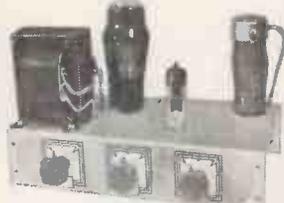

LAST FEW

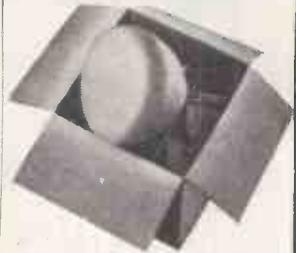

15in. MAGNETIC TELEVISION TUBE

By famous maker. Specification Blue/White screen 9 Kv. ion trap triode, heater 6.3 v. at .55 amp., 50° deflection. New, with written guarantee, offered at approximately half price, £13/10/- each, plus 10/- carriage and insurance. H.P. terms £4/10/- deposit and 12 monthly payments of 18/3. Limited quantity, so order immediately.

SLIDER RESISTORS

Heavy Duty Type.
Size 7in. x 1 1/2in. 11 ohms 4.5 amp., 22/-; Size 9in. x 1 1/2in. 1.2 ohms .15 amp., 15/-; size 13 1/2in. x 1 1/2in. 3 ohms 10 amp., 15/-.



LECTROSS TOWEL AIRER, £3/19/6



The Lectross warms room as it dries clothes, bathing costumes, towels, etc. Size 3ft. wide, 3ft. high and 5in. deep. Works off A.C. or D.C. mains, consuming 650 watts. Fully guaranteed. Price £3/19/6 plus 7/6 carriage.

40 VOLT 2 1/2 AMP. STEP DOWN TRANSFORMER

Totally enclosed in metal box—primary 200-240 50 c.p.s.; secondary easily rewindable to other voltages—ideal safety unit for operating children's toys or domestic gadgets, 17/6 each.



CHASSIS ASSEMBLY


3 colour, 3 waveband scale covering standard Long, Medium, and short wavebands, scale pan, chassis punched for standard 5 valve superhet, pulley driving head, springs, etc., to suit. Scale size 14 1/2in. x 3 1/2in. Chassis size, 15in. x 5in. x 2in. deep. Price 15/-, plus 1/6 post. Note: This is the one that fits our 37/6 table cabinet.



DEMOBBED VALVES

Gives the commercial equivalents of many thousands of Service Valves, an invaluable publication recently revised. Price 2/3.

ELECTRONIC PRECISION EQUIPMENT LTD

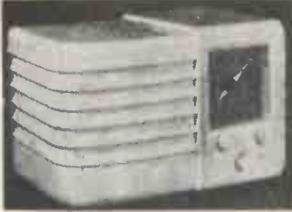

THE WHITE LADY
Moulded in expensive pure white bakelite, this cabinet is ideal for T.R.F. or Superhet alike. It is supplied with holes for two controls only. Size approx. 11in. x 6in. x 5in. Price 22/6, plus 3/6 post and ins.




THE PROJECTOR
An impressive cabinet, originally designed for T.V. but slight modification makes it into an unusual, but most dignified, radio-gram or amplifier. Size 23in. wide, 22in. deep, 37in. high. Price £8/15/-, or £2/18/4 deposit. Carriage and ins. £1.

THE PORTA-PLAYER


This is a robust, handsome carrying case, finished in two-tone leather cloth with foldaway carrying handle and clasps. Approximate dimensions 19in. x 14in. x 10in., ample for 8in. speaker, mains or battery driven amplifier, and tape deck or other record-playing mechanism. Price £3, carr. and ins. 10/-.



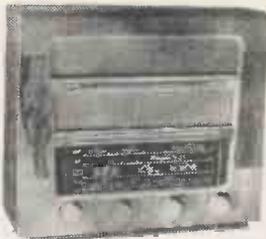THE MIDGETRONIC
Yet another bankrupt bargain. This pleasing little cabinet (size approx. 8in. x 7in. x 3in.), moulded in bakelite is supplied complete with dial ring and special pointer as illustrated. Price 15/-, plus 2/6 post. Or complete with all the valves and parts to make an excellent T.R.F. set, price £3/15/- plus 2/6 post. Note: A few suitable transfers make this an ideal nursery cabinet.



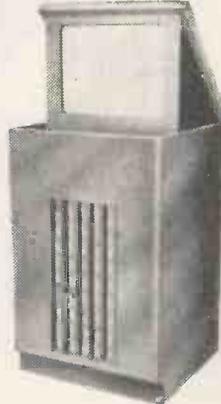THE WINDSOR DE LUXE
This takes our Windsor 5 chassis and 8in. Speaker, is undoubtedly a fine cabinet, well-made and pleasantly finished. Approximate dimensions 19in. x 16in. x 8in. Price 49/6, plus 3/6 post and ins.



THE REGINA
High polished, nicely figured, two-tone walnut finish, developed for the home constructor and supplied with component parts for a shelf that can be fitted in at any desired height. Suitable for most constructor sets, "Viewmaster," "Supervisor," "Magnevisor," "Teeking," etc., etc. Size 18in. wide, 18in. deep, 34in. high. Cut for 12in. tube, but not drilled. Price £7/17/6, or £3/12/6 deposit.



THE OCCASIONAL
Available in cream or brown bakelite, this is probably our most popular cabinet. Approximate size 11in. x 6in. x 5in. The price 17/6, plus 3/6 carriage and ins. Or with all parts, including four B.V.A. valves, to make a T.R.F. receiver of proved design, price £6/1/6, or if req., £2/1/6 deposit and ten monthly payments of 10/6. Postage and ins. is 3/6.

THE PORTA-RADIO




This is ultra-modern, two-tone, bakelite with integral moulded handle. We can supply, where required, the metal chassis, dial, and all other parts necessary to make a Mains or Battery portable. Note: All of these cabinets have slight imperfections; these are hardly noticeable, however, and will not impair the performance or safety of the set. Price 10/- each, post and ins. 3/6.



THE TABLE-TELE
Another cabinet which through the misfortunes of a manufacturer we are able to offer at below cost. Designed to take a 12in. tube, we supply this complete with armoured plate glass at £3/17/6, plus 7/6 post. Metal work, punched chassis, outrigger, etc., available as a parcel. Price 17/6, plus 2/6 post.



THE NON-REPEATABLE
Through a manufacturer ceasing production we are able to offer this really handsome cabinet at well below cost. It was originally made for a very expensive television so its quality is beyond question. Size 1ft. 10in. wide, 1ft. 4in. deep and 3ft. 5in. high. Complete with plywood back, fitted "Bowler Hat." Price £7/5/-, or £3/8/4 deposit. Note: The cutout is for 12in. tube but holes for the controls are not drilled.

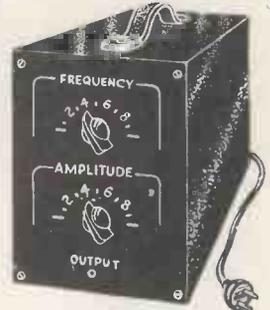

THE SMALL INSTRUMENT
This is of sheet metal finished black crackle with lanule front left ready for lettering with white paint or transfers. Approx. size 8in. x 4in. x 6in. high. Price 15/-, plus 1/6 post and packing.

THE MINI-RADIO



Internal dimensions of this are 6in. x 5in. x 3in. Two models are available, one has the new plastic "open crackle" finish. Price 15/9, plus 1/6 post. The De Luxe model is covered with brown and grey leather cloth. Price 22/6, plus 1/6 post. Either model has fitted carrying handle.



THE MINI-MIKE
A brown bakelite cabinet with metal grille. Size 4in. x 4in. x 2in. Will take 3in. moving coil speaker or other type of microphone. Price 6/6, post and packing 1/-.



THE WINDSOR STANDARD
This takes our Windsor 5 chassis and 6in. speaker. It is a very nice job, walnut veneered and pleasantly polished. Size approximately 16in. x 16in. x 7in. Offered at the particularly low price of 39/6, plus 3/6 post.


ELECTRONIC PRECISION EQUIPMENT LTD

THE EMPRESS



A cabinet to delight the eye of any discerning connoisseur, beautifully styled and elegantly veneered medium full-grained walnut. High polish finish. The amply sized control board is raised to a convenient level, but is not cut or drilled. Motor board, again uncut, measures 16in. x 14in. deep and has a clearance of 5in. To the extreme left is a space for recordings storage. Size 3ft. wide, 2ft. 8in. high, 1ft. 4in. deep. Price £15/15/- or £5/5/- deposit.

THE CONSORT

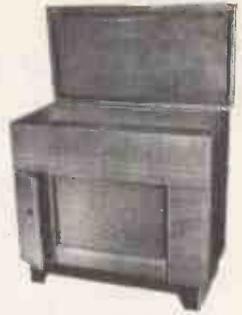

In two-tone, highly polished walnut veneer, with contrasting inlaid bands. Lift-up lid and storage compartments. Uncut motor board. Size 2ft. 6in. wide, 2ft. 5in. high, 1ft. 2in. deep. Clearance to motor board is 6in. Price £12/10/- or £4/3/4 deposit.

THE STANDARD

A well-proved design, solidly constructed and pleasantly finished in medium-toned veneer, highly polished, uncut motor and control board. Size 30in. wide, 30in. high, 15in. deep. Price £11/10/- or £3/16/8 deposit.



THE GUILDFORD

Finished French walnut and eucalyptus veneer, highly polished. Twin doors open outwards displaying shelves for amplifier, radio unit etc., also leaving ample storage space. Motor drawer has uncut platform. 16in. x 13in. with ample clearance. Overall dimensions 3ft. 4in. wide, 2ft. 5in. high, 1ft. 5in. deep. Price £18/18/- or £6/6/- deposit.



THE SUPERIOR 15 CONSOLE

Undoubtedly a very fine cabinet designed to house a very fine set. Handsome two-toned walnut finished and distinctive design, its modern lines blend with all furnishings. Cut out for 15in. tube and drilled to take the standard Superior 15 chassis. Price £11/10/- or £3/16/8 deposit.

THE SUPERIOR 15 CORNER

Designed for the man who wants something really impressive. A massive cabinet but being corner fitting is not out of place even in the modern small living room. Voted by one of our leading magazines as one of the finest pieces of furniture at the 1953 National Radio Show, Earls Court. Overall dimensions of this cabinet are 47in. wide, 31in. deep (to corner), 50in. high. Note that in addition to the Superior 15 Televisor this cabinet will accommodate a radio unit with controls on the sloping panel at the top and a tape recorder, or a record player under the lid in the top. Price £18 or £6 deposit.



Note 1. The carriage and Insurance charge on all cabinets on this page is £1, which covers a distance up to 200 miles. For distances beyond this there will be an additional charge.

Note 2. H.P. charges are normally 1/3rd deposit balance plus charges being payable by 12 equal monthly instalments.

ELECTRONIC PRECISION EQUIPMENT LTD.

Post orders should be addressed to :—

ELPREQ HOUSE (Ref 2.), HIGH STREET, WEALDSTONE, MIDDX.

Personal shoppers however must call at :—

42-46, WINDMILL HILL, RUISLIP, MIDDX.
Phone: RUISLIP 5780. Half-day, Wednesday.

152-153, FLEET STREET, E.C.4.
Phone: CENTRAL 2833. Half-day, Saturday.

29, STROUD GREEN RD., FINSBURY PARK.
Half-day, Thursday.



Top Sellers!

ALL-WAVE CAR RADIO

MODEL D.3



- Complete coverage on all international short wavebands from 16 metres.
- Daylight and powerful overseas reception
- Higher sensitivity—6 latest type, high performance valves.
- Slow-motion control for easier short-wave tuning.
- Self-contained large loudspeaker with power-pack.
- Attractively housed.
- Greater volume through push-pull output.
- Tropicalised, shock-proof

ALL-WAVE PORTABLE

MODEL D.4—'COMPANION'



(Battery Model only or as a Combined Battery/A.C. Mains.)

- Coverage from 13 metres on 3 bands.
- 7 V. oversea and local reception.
- Telescopic Aerial extending to 60 inches.
- Longer Battery Life assured by latest type of low-consumption valves.
- Magic Eye—the only portable today with Cathode-ray visual tuning
- Rejuvenator trebles usual battery life. (operates in Battery/A.C. Mains Model only).

Supersonic

REG. TRADE MARK

**SOLE DISTRIBUTORS WANTED
IN ALL PARTS OF THE WORLD**

Enquiries to: Export Manager, **CHASSAY BROS. (Pvt.) LTD.**,
Ingutsheni Road, **BULAWAYO**, Southern Rhodesia.

MAINTAINING A REPUTATION.....



Deflector Coils type DC300/C. As specified for the "Teleking," "Supervisor" and "Magnaview."

Conversion circuits for 14in. and 17in. C.R. Tubes available. Send 9d. and S.A.E.

Every day we read the words: "I am ordering Allen Components because they are so highly recommended by my friends".

We are proud of our reputation. Since we pioneered Wide Angle scanning some years ago we naturally carried on our policy of producing components designed to the highest specification and engineered to the closest tolerance. In these days of shortages and lowered standards such a policy is not easy to carry out and it has necessitated unrelaxed attention to detail in all our departments. The result of this care is apparent in all our products, in which good workmanship is combined with high reliability.

May we suggest you ask your friends?

From all Leading Stockists.


ALLEN COMPONENTS LIMITED

Crown Works, Lower Richmond Rd., Richmond, Surrey

Telephone: Prospect 9013

Send 9d. and S.A.E. for Circuit Diagram

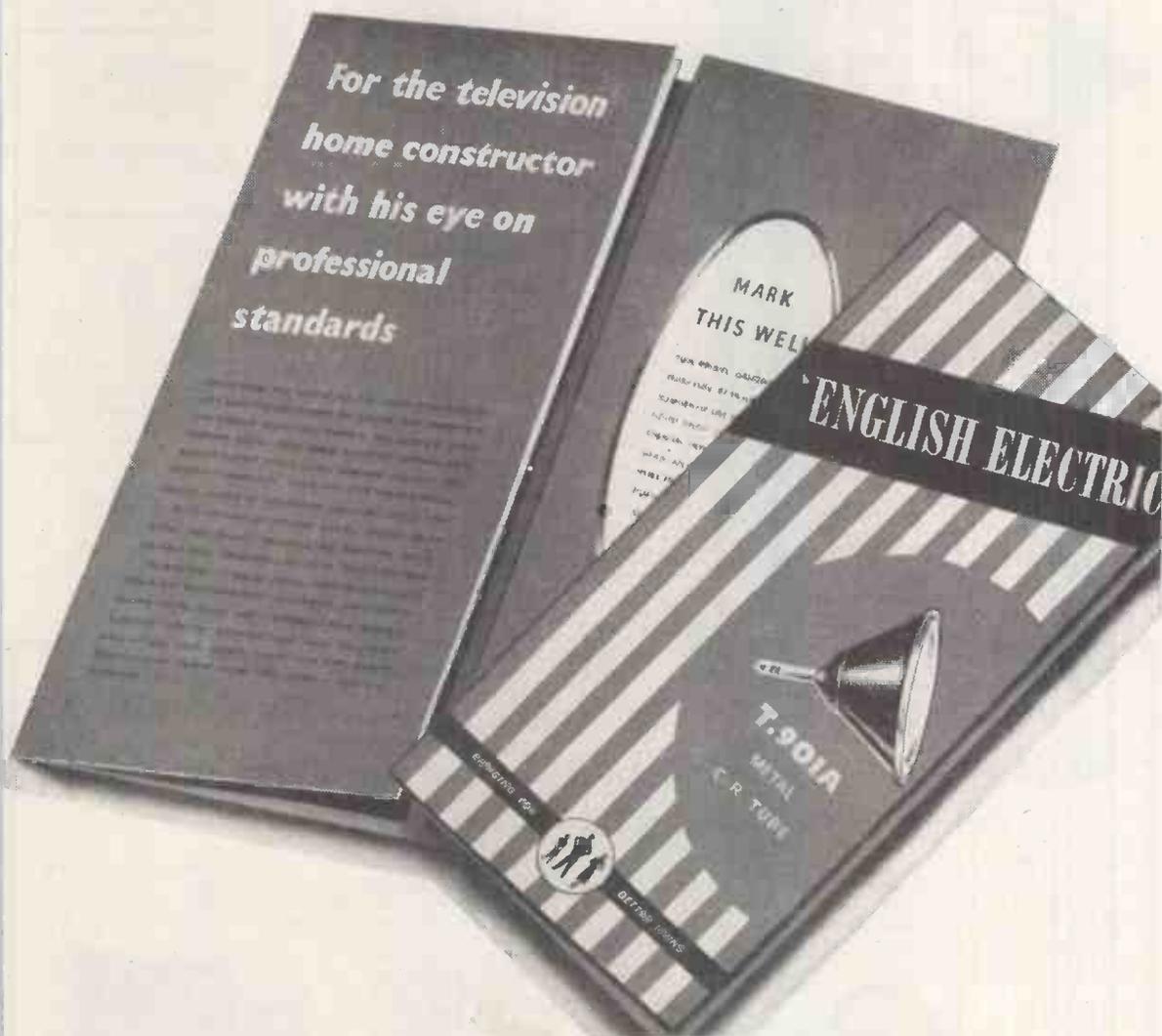Line and frame scanning All information required by the home-
 constructor has been put together in this leaflet. If you are building a new set or
 converting with an 'ENGLISH ELECTRIC' metal C.R. tube, please let us know and we
 will gladly send you a copy.



'ENGLISH ELECTRIC' T901A

BRITISH MADE LONG LIFE 16-INCH METAL C.R. TUBE

The tube around which the 'Tele-King,'
 'Magnaview' and 'Super-Visor' circuits and
 'View Master' conversion circuits were designed.


* The T901A is a suitable replacement for
 16in. wide angle metal C.R. tubes used in
 A.C. and D.C. sets, without modification.

The Editor scoops the Tape Recorder market


because its features, its price and performance have a wide appeal.



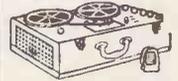● Unique lightweight custom built chassis!



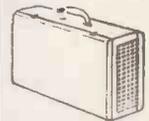● Compact—easy to control, fully automatic!



● The smallest lightweight all mains portable recorder!

SPECIFICATION

★ Tape speed, 7½ in. per second. ★ Mullard miniature valves. ★ Twin track heads. ★ Three high-grade specially designed recording motors provide fast forward run and 50 sec. rewind without unloading tape. ★ Independent Bass and Treble Controls for recording and playback. ★ Negligible wow and flutter. ★ Overall negative feedback. ★ 1,200ft. reel of tape will provide ONE hour playing time. ★ Amplifier may be used independently for high quality record reproduction and public address. ★ High fidelity Record head. ★ Special high-grade speaker. ★ Provision for external speaker. ★ Speaker muting switch. ★ 4 watts output and brilliant reproduction. ★ Positive servo braking on all functions. ★ Compact size for ease of handling, only 16½ in. x 12 in. x 7 in. (with lid). ★ Operating height only just

over 5 inches. ★ Magic eye recording indicator. ★ Weight only approx. 33 lbs. ★ 200-250 v. A.C. Mains.

ACCESSORIES

The "Editor" is supplied ready for use, with a crystal desk microphone made specially for this equipment by RONETTE. The Coronation microphone can be supplied as an alternative.

A 1,200ft. reel of high coercivity BURGOYNE tape is issued with every recorder. This especially recommended tape is available at 35/- per 1,200ft. reel, or 21/- per 600ft. reel.

Write for details and outstandingly attractive leaflet to:—

TAPE RECORDERS (ELECTRONICS) LTD.

3 FITZROY STREET, LONDON, W.1
Telephone: MUSEum 5563.

CITY SALE & EXCHANGE

THE HI-FI SPECIALISTS

LIMITED

90-94 Fleet Street, London, E.C.4

Phone: Central 9391/2

Offer the following from stock:—

AMPLIFIERS. Leak TL/12 and Varislope pre-amplifier, 39 gns. Acoustical QUAD II complete, £42. R. D. Baby de Luxe Mark II, £23. R. D. Minor £11/10/-. Reconditioned QUAD I and pre-amplifier, £25. QUAD with preamp. attached, £17/10/-. Nusound push pull, £10.




SPEAKERS. Wharfedale 3 speaker system, £72. Lowther PW1 horn PM2 unit, £60. Wharfedale 15 and 5 in. units, crossover sandfilled baffle, £42. Salex 12 in. reflex cabinet with Axiom 150 Mark II unit, £20. Salex 10 in. reflex with Golden 10 unit, £17.

Hire Purchase terms can be arranged on all new apparatus over £10—third deposit, and the balance over 6, 12 or 18 months. Write for order forms.

GRAM. UNITS. B.S.R. Mon-arch 3 speed auto, turnover crystal pick up, £16/10/-. Garrard RC72 as new, 6 gns. Collaro cream 3R531 with studio pick up, £15/3/-. Collaro 3R531 with mixed autochange, £17/10/-. Garrard T unit, 3 speed non-auto, less heads, £7/14/9. Connoisseur 78 motor with Leak ruby pick up, £15/15/-. Collaro 3-speed non-auto orthodynamic head, transformer, £6/19/6. B.S.R. Regent turnover crystal, £9/5/-. B.S.R. 78 or 33 motors only, 49/6. Collaro A.C./D.C. motor only, adjustable speed, £4/10/-. Collaro A.C./D.C. motor with pick up and auto stop, £7/10/-. Decca 3 speed transcription motor with 2 XMS heads, £22/18/3. Decca 2 speed portable record player, crystal P.U., £6/10/-. Columbia record player, 78 only, £4/10/-. Philips Disc Jockey, £10/13/8.

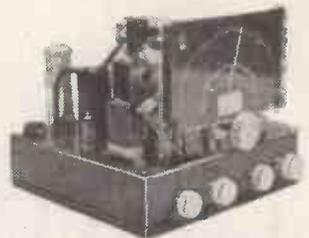TUNERS. Leak variable selectivity £35/1/3. Lowther 7 valve DT4, £37/6/3. Lowther LE1, £22/7/8. 3 Station 3 valve preset, £7.



Why not
PART EXCHANGE
your present equipment
for the latest type?

Write with details.

WE PAY TOP PRICES

FOR

**AMERICAN SURPLUS
ELECTRONIC EQUIPMENT**

Any Quantity or Condition

LOOK AT THESE EXAMPLES

for equipment in good condition

SCR291, complete	£350
R54/APR4 Receiver with all tuning units	£135
ET4336 Transmitter	£110
BC348R Receiver	£25
TS175/U Frequency Meter	£80
TS67 Test Set	£25
RC94 Scanner	£100
TS13 Test Set	£100

We pay similar remarkable prices for:—

SCANNERS. Any U.S.A. type.
RECEIVERS. R111/APR5, R89/ARN5, R5/ARN7, R65/APN9, R15/APN3, R15/CPN2, BC1147A, BC348.

TRANSMITTERS. CPN2, APN3, ART13, BC1149, TDQ, TDE.

TRANSCIEVERS. ARCI, ARC3, SCR-522, TCS, BC800 RT1/APN2.

INDICATORS. ID6B/APN4, ID17/APN3, ID18/CPN2, BC1151, BC1152, BC1159, MC412, I-81A, I-82A.

TEST SETS. Any unit with prefix "TS." IE19, BC638, I-208.

MODULATORS. BC1091, BC1142, CM3.

SYNCHRONISER. BC1148.

POWER UNITS. RA34, RA42, RA59, TA2, RA88, RA90, MG149, PE98, PE158, DM28.

TUNING UNITS. TN17, TN18, TN19, TN54, TU57, TU58, TU59.

CONTROL GEAR. BC1150, BC1145, JB91, JB95, JB98, JB102, PN31, PN32.

ANTENNA GEAR. BC223A, RC94, AS27, AT4, AN104.

MOUNTINGS. FT237, FT247A.

And almost every American made unit even if not mentioned above.

Phone us immediately, transfer charge.

Deal with the firm that has been established for twenty-five years and which is by far the largest buyer of Ham Equipment.

ALTHAM RADIO CO.

JERSEY HOUSE, JERSEY ST.

MANCHESTER 4

Telephone : Central 7834/5/6

EASY L.R.S. TERMS

Estd.

1925

LEAK QUALITY EQUIPMENT for the Connoisseur

**POINT-ONE TL/12 12-WATT
Triple Loop Feedback Amplifier**



For the highest possible quality of reproduction from Pick-up, Radio, Microphone, Film and Magnetic Tape this amplifier has won world-wide recognition. As used by the B.B.C. and many overseas Broadcasting Corporations.

Cash Price £28/7/0.

THE NEW VARI-SLOPE PRE-AMPLIFIER

Gives audibly better reproduction. No chokes to cause magnetic hum pick-up. Extremely low harmonic and intermodulation distortion.

Cash Price £12/12/0.



For fuller details see maker's advertisement on p. 83.

TERMS for these TWO UNITS

£9 deposit with order and 18 monthly instalments of 40/-.
Passenger carriage 10/- extra, payable with deposit.

LEAK V.S. TUNER AND DYNAMIC P.U. also supplied on similar terms. All the above available separately

Armstrong Chassis

Two new models incorporating many new features including Bass and Treble lift controls and improved tuning scales with flywheel action.
MODEL FC38. 3 wavebands 16-50 m., 190-500m., 1,000-2,000m. 8-watt P.P. Output. Cash Price £23/13/0 (incl. P.T.).
MODEL RF41. 10 valves, 4 wavebands, 12-35, 35-90, 190-550, 800-2,000m. 10-watt P.P. output. Cash Price £31/19/8 (incl. P.T.).

See maker's advertisement on pp. 105 & 131.

Connoisseur 3-speed GRAM UNITS and LIGHTWEIGHT PICK-UPS to match, can be supplied from stock.

Wharfedale & Goodmans LOUDSPEAKERS. Complete range available.

Illustrated lists of any item and details of our EASY TERMS will be sent upon request by return.

HAVE YOU TRIED?

the amazing ALL-NEW

REMINGTON '60'
ELECTRIC DRY SHAVER




OUR 14 DAYS FREE TRIAL OFFER
WILL CONVINCE YOU

that it really does shave every type of beard quicker and closer than any other method.

SEND ONLY 20/- DEPOSIT for 14 DAYS FREE TRIAL
DEPOSIT RETURNED IN FULL IF NOT SATISFIED. Balance by 9 monthly payments of 24/-. Cash Price £9/19/0. A.C./D.C. 200/250v. Brand new, dispatched by return in silk-lined case, post paid. 12 months maker's guarantee.

THE L.R. SUPPLY COMPANY LTD.
(LONDON RADIO SUPPLY COMPANY)

BALCOMBE Telephone : Balcombe 254 SUSSEX

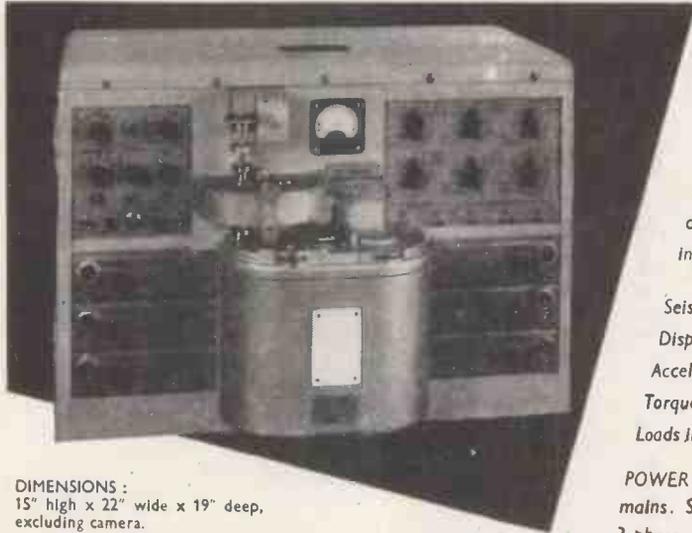

Six channel C.R.T. Continuous film Recorder Type P.76

This is a versatile instrument developed to fill an ever growing need in engineering research for the recording and measurement of physical variables under dynamic conditions. It is being used to record simultaneously information concerning the following physical effects:—

Seismic Vibration (for mining and geological survey)
 Displacement . . . Time/Frequency . . . Velocity
 Acceleration . . . Force . . . Pressure (Liquid or Gas)
 Torque . . . Temperature . . . Vibration Analysis
 Loads in compression and tension . . . Phase measurement

POWER SUPPLIES : 200-250 V., 50 C.P.S., Single-Phase mains. Special model for above and 115 V., 400 C.P.S., 3-phase supply, for airborne use, to order.

DIMENSIONS :
 15" high x 22" wide x 19" deep,
 excluding camera.

Full details of these or any other
 Boulton Paul Electronic Instruments
 will gladly be forwarded on request.



BOULTON PAUL ELECTRONICS


BOULTON PAUL AIRCRAFT LTD. WOLVERHAMPTON

Telephone : Fordhouses 3191 Telegrams : Aircraft, W'ton

Garrard

THE NAME WHICH HELPS TO SELL
 THE WORLD'S FINEST RADIOGRAMS

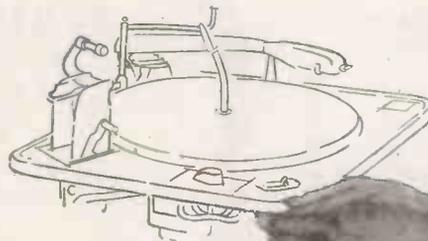Garrard Gramophone Equipment is world famous for its reliability and its excellent design, and is acclaimed throughout the world for its superb performance.



THE GARRARD ENGINEERING AND MANUFACTURING CO. LTD.

CLASSIC EXAMPLES of

HIGH-FIDELITY EQUIPMENT and COMPONENTS

CUSTOM-BUILT REPRODUCTION

Everyone has his idea as to what constitutes the right equipment to give the ultimate in sound reproduction. Here at Classic we have evolved a plan to suit your personal preferences in this highly personal field. The starting point is the handsome Classic cabinet, to which can be added the necessary amplifier, gramophone motor or tape deck, pick-up or what you will to give you just the sort of reproduction you want. No dearer than commercial radiograms, these "custom-built" specifications stand comparison with anything available. Recently, a customer of considerable discernment told us "I have waited twenty years to buy a gramophone—I have never heard such superb reproduction." The Classic cabinet will house Connoisseur or Garrard motors, or a Tape Deck in place of a motor; Quad Mark II, Leak Point-One, Rogers, Goodsell, Lowther, Pye or Pamphonic amplifiers; Quad, Lowther, Leak, Goodsell or Rogers Radio Feeder Units; Radio Feeder Units for Wrotham A.M. and F.M. Transmissions. Below are given a few typical combinations made up under this scheme. If there are any other combinations you prefer, why not come along and see us—we have these various equipments available for demonstration at Croydon, and, after all, there's nothing like hearing them for yourself.

1

CLASSIC CABINET.....	£27 10 0
QUAD RADIO UNIT.....	£24 0 0
QUAD MARK II AMPLIFIER.....	£42 0 0
CONNOISSEUR MOTOR WITH TWO PICK-UPS	£27 10 0
CASH PRICE	£121 0 0

Or deposit £40/6/8, balance by 12 monthly payments of **£7/14/6**

SPEAKER TO CHOICE—EXTRA.



2

CLASSIC CABINET.....	£27 10 0
LEAK RADIO UNIT.....	£34 19 0
LEAK POINT-ONE AMPLIFIER.....	£40 9 0
(With Vari-slope pre-amp.)	
GARRARD RC90 A.C. AUTO-CHANGER	£19 15 3
CASH PRICE	£122 13 3

Or deposit £41/13/3, balance by 12 monthly payments of **£7/15/0**

SPEAKER TO CHOICE—EXTRA.

3

CLASSIC CABINET.....	£27 10 0
GOODSELL "WILLIAMSON" AMPLIFIER	£33 0 0
GOODSELL PRE-AMPLIFIER.....	£18 18 0
LOWTHER AM/FM UNIT.....	£22 0 0
CONNOISSEUR MOTOR.....	£21 17 3
2 LOWTHER PICK-UPS.....	£21 10 0
CASH PRICE	£144 15 3

Or deposit £48/15/3, balance by 12 monthly payments of **£9/2/9**

SPEAKER TO CHOICE—EXTRA.

The Classic "Hi-Fi" cabinet is a handsome cabinet in a rich straight-grained or figured walnut. It has a slightly sloped front, lined lid, fully ventilated back, and heavy motor board, size 30in. x 20in. x 20in. Price from £22/10/-.

4

CLASSIC CABINET.....	£22 10 0
ROGERS BABY-DE-LUXE AMPLIFIER.....	£14 0 0
ROGERS JUNIOR PRE-AMP.....	£9 0 0
ROGERS FEEDER UNIT.....	£25 0 0
GARRARD T.A. 3-SPEED MOTORS WITH 2 DECCA HEADS.....	£11 6 8
CASH PRICE	£81 16 8

Or deposit £27/16/8, balance by 12 monthly payments of **£5/3/6**

SPEAKER TO CHOICE—EXTRA.

The prices quoted are for individual units only, not assembled in cabinets. We despatch equipment to all parts of the world—your orders for "custom-built" specifications can safely be left to us. No purchase tax on overseas orders—exact transport rates only are charged. Wherever you are, you can rely on The Classic Service.

CLASSIC ELECTRICAL CO LTD

352-364 LOWER ADDISCOMBE ROAD · CROYDON · SURREY TEL · ADDISCOMBE 6061-2

TWO JOBS IN ONE.....



The McMurdo X3/UA crystal holder is a dual purpose quartz crystal socket designed to take either 10X or 10XJ service type crystals. It is made of nylon loaded bakelite and fitted with the well known McMurdo Valveholder contacts ensuring a remarkably low and stable contact resistance.



Wholesale Enquiries:—

CYRIL FRENCH HOLDINGS LTD., Hampton Wick, Middlesex. KIN. 2240

Manufacturers' Enquiries: THE McMURDO INSTRUMENT CO. LTD., VICTORIA WORKS, ASHTEAD, SURREY. ASHTEAD 3401



THE "RD MINOR MK II"

A SMALL HIGH PERFORMANCE GRAMOPHONE AMPLIFIER

NOTE THESE EXCEPTIONAL IMPROVEMENTS:

- ★ Increased Power Output.
- ★ Lower Distortion.
- ★ Exceptionally low hum level.
- ★ Improved output transformer.
- ★ All transformers now totally enclosed.

BRIEF SPECIFICATION:

Input Sensitivity : LP 80 m/V,
78 100 m/V. } for 3.5 watts.
AES 120 m/V.

Frequency Response : $\pm .5$ DB. 30-15,000 c.p.s.

Power Output : 4.5 watts, maximum.


Distortion : Less than .35% at 1 kc/s. for 3.5 watts.

Hum : —80DB below 3.5 watts.

N.F.B. : Main loop, including O.T. 15DB.

Retail Price : £12. 17. 6d. Ex. works.

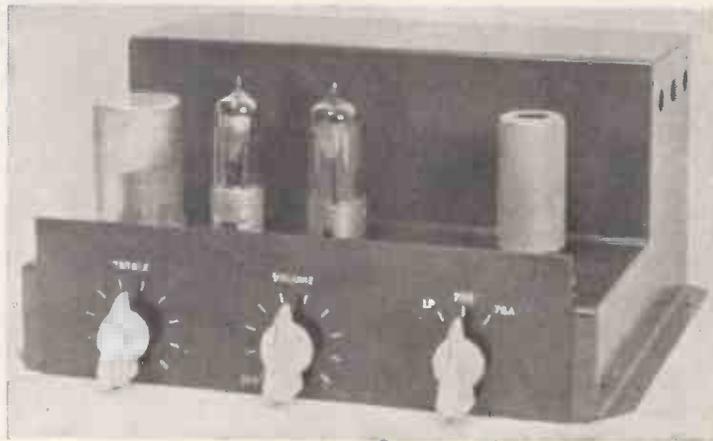An illustrated leaflet will gladly be forwarded post free on request. Available from leading dealers in London and the Provinces, or if in any difficulty, please apply direct.



Trade and Export enquiries invited.

ROGERS DEVELOPMENTS CO.


MANUFACTURERS OF PRECISION BUILT SOUND EQUIPMENT

"RODEVCO HOUSE," 116, BLACKHEATH ROAD, GREENWICH, S.E.10. TIDeway 1723.

TRUVOX

TAPE DECK MK III

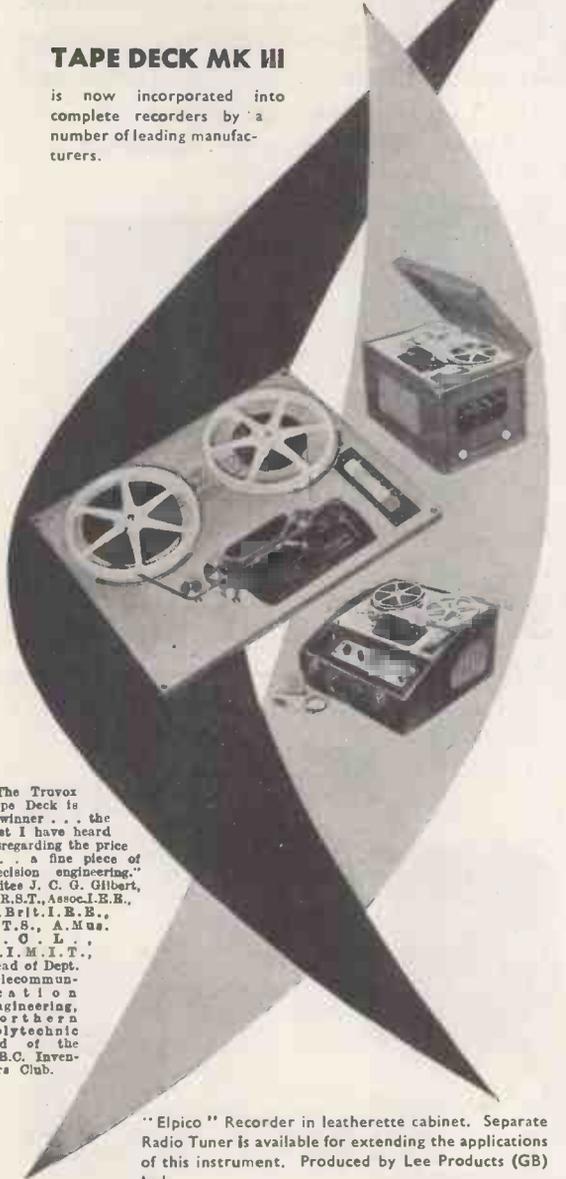is now incorporated into complete recorders by a number of leading manufacturers.



"The Truvox Tape Deck is a winner... the best I have heard disregarding the price... a fine piece of precision engineering." writes J. C. G. Gilbert, M.R.S.T., Assoc.I.E.E., M.Brit.I.R.E., F.T.S., A.Mus. T.O.L., M.I.M.I.T., Head of Dept. Telecommunication Engineering, Northern Polytechnic and of the B.B.C. Inventors Club.

"Elpico" Recorder in leatherette cabinet. Separate Radio Tuner is available for extending the applications of this instrument. Produced by Lee Products (GB) Ltd.

"Prima" general purpose recorder in streamlined carrying case by Unitolex Ltd. 4 watts output.

WE SHALL BE PLEASED TO PUT INTERESTED ENQUIRERS IN TOUCH WITH THESE MANUFACTURERS.




TRUVOX LIMITED
HARROW, MIDDLESEX

Sales Office: 15 Lyon Road, Harrow, Middx. Phone: Harrow 9282. Service and Technical Depts., 328 The Broadway, Harrow Road, Harrow, Middx. Phone: Harrow 4455.

SUB-MINIATURISATION

HIVAC

FIRST TO GET DOWN TO IT!

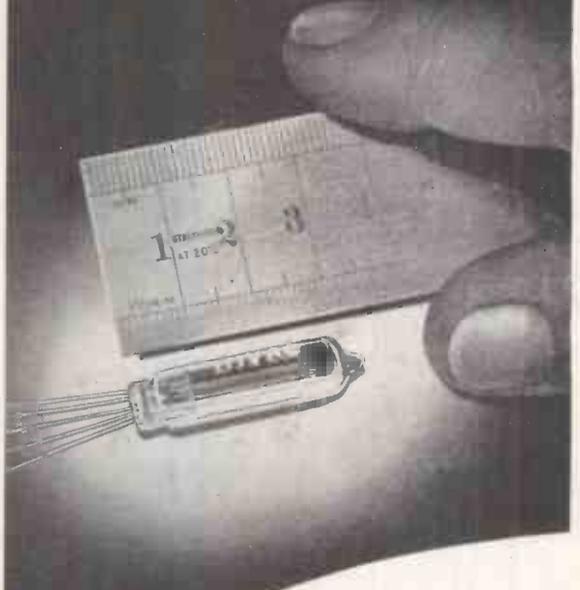

ACTUAL SIZE

XFY 42

Beam Tetrode Sub-miniature Output Valve with still lower filament current

TYPICAL OPERATION

Filament Voltage	1.25	1.25	1.25 V.
Filament Current	10	10	10 mA.
H.T. Voltage	16.25	22.5	30 V.
Control Grid Voltage	0	-1.5	-2.75 V.
Power Output	1.1	2.7	6.0mW.

The maximum cross-section is only 8 mm. x 6 mm. with a maximum glass length of 35 mm.

A small flat sub-miniature output tetrode with still lower filament current and improved performance at reduced battery voltages.



Hivac Ltd. Telephone: HARrow 2655
GREENHILL CRESCENT, HARROW-ON-THE-HILL, MIDDLESEX

**High grade
Laboratory
Equipment**


REBUILT & GUARANTEED AS NEW!

We have a comprehensive range of electronic equipment by well known makers, including *Microwave Receivers, Signal Generators and Cavity Wavemeters.*

A small selection of other equipment is shown below.

★ 3 cm. Signal Generators type TS.13/AP ★ 10 cm. Signal Generator type TS.14/AP ★ Millivoltmeters, Valve Voltmeters, Audio Oscillators by Hewlett Packard, Ferris Noisemeters ★ Transmitter Output Meters 3-10 W Max. 100/200 Mc/s ★ Frequency Meters type BC.221, TE.149 and TS.69/AP ★ F.M. Signal Generators by Boonton.

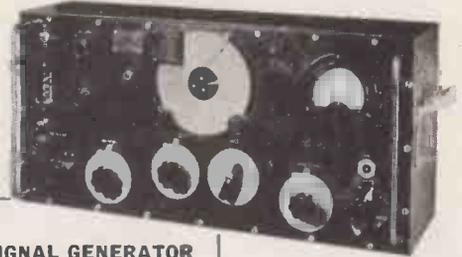Microphotometers, Chart recorders to your specification.



**SIGNAL GENERATOR
TYPE TF.144G**

WE CAN ALSO UNDERTAKE TO RECALIBRATE OR REBUILD YOUR LABORATORY EQUIPMENT.

For further particulars of these and other high grade electronic instruments, write to:—

HATFIELD INSTRUMENTS LTD. 175, UXBRIDGE ROAD
HANWELL, LONDON, W.7

Telephone: EALing 0779, 9857

**VIEW MASTER, SOUND MASTER
FROM STOCK**

SMOOTHING CHOKES, 10 H. 50 mA., 6/-; 15 H. 60 mA., 5/11; 10 H. 100 mA., 8/3; 20 H. 30 mA., 6/-; 40 H. 50 mA., 6/-; 20 H. 120 mA., 15/6; 50 H. 30 mA., 10/9; 10 H. 150 mA., 16/6; 15 H. 150 mA., 18/-; **PANEL** Black Crackle Paint, 3/6. **WIRE-WOUND RESISTORS**, 5 w. 1/3, 10 w. 1/6. **SILVER MICA CONDENSERS** up to 100 pf., 9d., 100-1,000 pf., 1/-; **CARBON RESISTORS**, 1/2, 1/4 and 1 w., 4d. **PENTODE OUTPUT TRANSFORMERS**, 5/11. **METAL RECTIFIERS RMO**, 5/-; RM1 5/3; RM2 5/9; RM3 7/-; RM4 21/-; DRM1B 11/6; DRM2B 12/6; DRM3B 15/-; K3/45 8/2; K3/50 8/8; K3/100 14/8.

MINIATURE MAINS TRANSFORMERS

for PRE-AMPLIFIERS, TESTGEAR, etc. PRIMARY 230/240 v. SECONDARIES 0-250 v. 30 mA. (for 250 v. from a half-wave rectifier), and 6.3 v. 1 a. New and guaranteed. Price 14/9.

ELECTROLYTICS, 450 v. wkg. (Gtd. New Stock), 4 mfd., 1/6; 8 mfd., 2/-; 16 mfd., 3/-; 8-8 mfd., 3/6; 8-16 mfd., 4/-; 16-16 mfd. 4/6. **PM LOUDSPEAKERS** (3 ohms), 3in., 13/6; 5in., 14/6; 6in., 15/6; 8in., 18/6; 10in., 22/6. **GERMANIUM CRYSTAL DIODES**, 2/-. **B.I.C.**, 0.1 mfd. 3 kv. TV Condensers, 10/6. **ROTARY SWITCHES**, 3-bank, total of 5 p. 6 w., 3/9. **H.R. HEADPHONES**, 18/6. **SOLO** Miniature SOLDERING IRONS, 19/6. 6in. ENLARGERS (for VCR97), 17/6. **WEARITE "P" COILS**, 3/-. **ALI CHASSIS**, 2 1/2 in. deep, 6in. x 4in., 4/6; 8in. x 6in., 6/-; 10in. x 7in., 7/-; 12in. x 8in., 9/-; 14in. x 8 1/2 in., 13/-; 16in. x 9in., 14/-. **TRANSFORMERS** (Mains input Standard Primaries), 250-0-250 v. 80 mA., 0-4-6.3 v. 4 a., 0-4-5 v. 2 a., 19/6; Ditto, but 350-0-350 v., 19/6; 250-0-250 v. 100 mA. 6.3 v. 2.5 a., 5 v. 2 a., 26/6; Ditto, but 350-0-350 v., 26/6. **ORDERS UNDER £1** please add 1/- p. and p. **ORDERS £1** and over add 1/9.

FOR INSTANT SERVICE—WRITE:

CITY & RURAL RADIO,
101 HIGH STREET, SWANSEA, GLAM.

Telephone: Swansea 4677

**SCALAMP
ELECTROSTATIC
VOLTMETER**



Cat. No. W.W. 11310

This instrument introduces a completely new conception of electrostatic voltmeter. It is compact, portable and robust, and does not require critical levelling or special mounting. The movement has a taut suspension, is critically damped, and readings can be taken with rapidity and ease.

- Three models are available:
- Cat. No. W.W. 11308
1 - 5 kV A.C. D.C.
 - Cat. No. W.W. 11309
3 - 10 kV A.C. D.C.
 - Cat. No. W.W. 11310
5 - 18 kV D.C. and
5 - 12 kV A.C. R.M.S.

- DIRECT READING.**
- ZERO CURRENT DRAIN.**
- THREE SECONDS PERIOD.**
- LAMP OPERATES FROM MAINS OR 4 VOLT BATTERY.**
- BRIGHT SPOT-AND-HAIRLINE INDICATOR.**

Please write for illustrated leaflet.

SCIENTIFIC  INSTRUMENTS

W. G. PYE & CO. LTD. GRANTA WORKS, CAMBRIDGE



The *LIGHTEST* and *smallest re-chargeable accumulator*

Full details of this amazing accumulator will be sent **FREE** on request



VENNER ACCUMULATORS LTD. KINGSTON BY-PASS, NEW MALDEN, SURREY. Tel.: MALden 2442


Associated Companies: **VENNER LIMITED · VENNER ELECTRONICS LIMITED**

WILLIAMSON AMPLIFIER KITS

KIT 1
WITH ELLISON
MAINS
TRANSFORMER
AND CHOKES

19 GNS.

READY BUILT
and tested
23½ Gns.

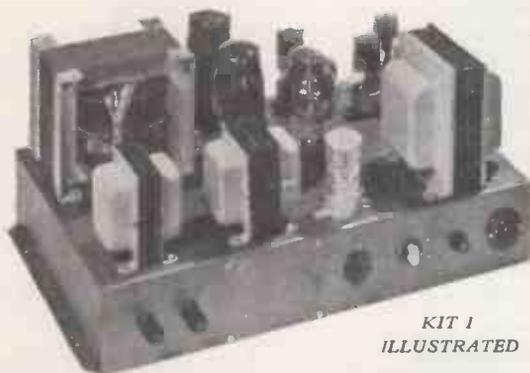

*KIT 1
ILLUSTRATED*

KIT 2
WITH
PARTRIDGE
TRANSFORMER
AND CHOKES

21 GNS.

READY BUILT
and tested
25½ Gns.

BOTH Kits have PARTRIDGE OUTPUT TRANSFORMERS

Fully drilled and enamelled chassis, T.C.C. and G.E.C. Condensers, Marconi-Osram-Cossor valves, sundries by Colvern, Belling-Lee, Eric, Bulgin, Welwyn, etc., complete to the last nut and bolt, with wiring instructions and layout drawings. *Packing and Carriage £1 extra, 10/- refunded on return of case carriage paid. C.W.O.*

PA1 PRE-AMPLIFIER

In response to numerous requests for a simple, inexpensive pre-amplifier for use with Tele-Radio Williamson Kits we have introduced our PA1. Specification includes full control of Bass and Treble, radio input and switched compensation for standard and long playing records. Recommended for use with ACOS GP20 and GP30, Decca C. & D. heads and Connoisseur Pick-ups. With wiring instructions and lay-out drawings.

KIT OF PARTS 6½ gns. READY BUILT 8½ gns. Postage and Packing 2/- extra. C.W.O. or C.O.D.

TELE-RADIO (1943) LTD.

189 EDGWARE ROAD, LONDON, W.2.

Phone: PAD 4455/6

SHOP HOURS: MON.-SAT. 9 a.m. to 6 p.m.

THURSDAY 9 a.m. to 1 p.m.

THE WORLD'S LOWEST PRICED TEST GEAR

SUPPLIED IN KIT FORM READY CALIBRATED

NEW THIS MONTH AUDIO FREQUENCY BRIDGE

THREE RANGES DIRECTLY CALIBRATED IN CYCLES PER SECOND, MEASURING ALL A.F. FREQUENCIES FROM 40 C.P.S. TO 16,000 C.P.S.

38/6

NO CALIBRATING NO METAL WORK
JUST ASSEMBLE AND USE

P & P 1/6


RES/CAP. BRIDGE

31/6

P & P 1/6


SIX RANGES

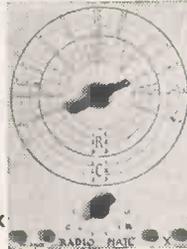- 10 to 1,000 ohms.
- 1,000 to 100,000 ohms.
- 50,000 to 5 megs.
- 500pf. to .01mfd.
- .01mfd. to 1mfd.
- .2mfd. to 50mfd.



NO CALIBRATING NO METAL WORK
JUST ASSEMBLE AND USE

INDUCTANCE BRIDGE

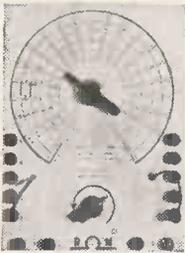

FIVE RANGES

- 50μHy to 1,000μHy
- 1,000 μHy to 20 MHy
- 20 MHy to 400 MHy
- 400 MHy to 8 Hy
- 5 Hy to 100 Hy

42/6

P & P 1/6


NO CALIBRATING NO METAL WORK
JUST ASSEMBLE AND USE

R.M. TWIN MULTI-OHMER

25/-


P & P 1/6

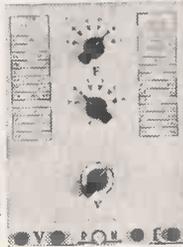A Heavy Duty 2,000 Ω w/w variable, calibrated in 50 ohm steps, plus all useful fixed resistance values up to 7 megs., switched. Separate outlets for each function.



NO CALIBRATING NO METAL WORK
JUST ASSEMBLE AND USE

I.F. ALIGNER

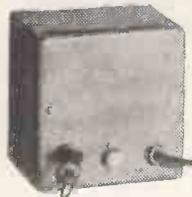

Fully screened. Tunes over the 465 kc/s range of I.F. frequencies.

17/6

P & P 1/6

PRE-TUNED. NO METAL WORK
JUST ASSEMBLE AND USE

SIMPLE AND COMPREHENSIVE INSTRUCTIONS AND DIAGRAMS FOR ASSEMBLY AND USE WITH EACH OF THESE FAMOUS KITS.


CASH WITH ORDER OR C.O.D.

STAMP FOR ILLUSTRATED LEAFLETS.

RADIO MAIL

DEPT. D,
RALEIGH ST.,
NOTTINGHAM

MOTEK

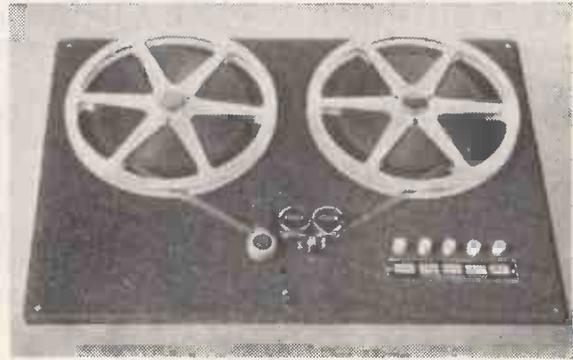

K4 UNIT (shown above)17 guineas

Motek—The name for tape units.

Illustrated leaflet available on request.

MODERN TECHNIQUES

138-144 Petherton Road, London, N.5

Tel.: Canonbury 5896



REPLACEMENTS

134-136 LEWISHAM WAY, NEW X, S.E.14.

Tel.: TIDeway 3696-2330.

E.H.T. WINDINGS. These are supplied to overcome sending heavy mains type T.V. transformers for rewind. Keep one for each model in stock. New Reduced Price 24/- each plus 1/- packing and postage.

LOW CAPACITY ISOLATOR TRANSFORMERS. These are high quality transformers for C.R.T.s having a cathode to heater short. The capacity is low enough to give a 2.5 mc/s. response on the tube. State voltages and if mains input or 1:1 is required. 17/3 plus 1/- packing and postage.

HEATER BOOSTERS. For use with low emission C.R.T.s. Tapped to provide a range of boost voltages. Auto wound, state voltage required. 15/9 plus 1/- packing and postage.

BACK PROJECTION SCREENS, 14in. x 17in. For T.V. or movies. 24/-, plus 3/6 packing and postage.

Send today for

NEW REPLACEMENT AND REWIND MANUAL

- ★ Covers hundreds of models. ★ Helpful Hints and Modifications.
- ★ MOST COMPLETE T.V. REPLACEMENT MANUAL EVER ISSUED IN THIS COUNTRY.

To DIRECT T.V. REPLACEMENTS, 134-136 LEWISHAM WAY, S.E.14.

Please send me new manual. I enclose 9d. stamps.

NAME

ADDRESS

DEALERS PLEASE ENCLOSE TRADE HEADING.



We manufacture
a wide range of metal cabinets
cases, racks and desks
for use in many branches of industry
Please write
for new 1954 catalogue
fully illustrated and detailed
to Department A

IMHOFS

ALFRED IMHOF LIMITED, 112-116 NEW OXFORD STREET, LONDON, W.C.1. MUSEum 7878

FOR BRILLIANT SOUND RECORDING

GET A
GRUNDIG
TAPE RECORDER



THE NEW TK9

A masterpiece of compactness and engineering. Push-button control and magic eye tuning give instant mastery of both recording and reproduction. Sound frequency range: 50-9,000 c/s. Tape Speed 3½ in. per second. Recording Time 1½ hours.

NEW FEATURES INCLUDE:

PRECISION PLACE INDICATOR. A unique clock device for instant selection of any particular recording.

AUTOMATIC TRACK SWITCH. Enables operator to switch from one Sound-Track to another in less than one second.

AUTOMATIC STOP. At end of spool. Also prevents tape "running off" at end of spool.

SAFETY BUTTON. To prevent accidental erasure.

GRUNDIG "Reporter" TK9 Price 65 Gns. Less microphone.

GRUNDIG "Golden Voice" moving coil microphone (GDM.5). 6 Gns.

GRUNDIG "Silver Voice" crystal microphone (GXM.1). 4½ Gns.



THE FAMOUS 700L

Two speeds, giving TWO HOURS perfect speech recording, or ONE HOUR high-fidelity music recording. Unique Grundig microphone, as sensitive as the human ear, faithfully reproduces all tone characteristics. Push-button control and


magic eye tuning give instant mastery of both recording and reproduction. Sound Frequency Range: 50-10,000 c/s at 7½ in. per second. 50-6,000 c/s at 3½ in. per second.

GRUNDIG "Reporter" 700L

Price 80 Gns. including Condenser Microphone.
Hire Purchase Terms Available.

Most Radio and Photographic Dealers stock Grundig. Ask for a demonstration today, or write for illustrated Folder to: Dept. WW., Grundig (Great Britain) Ltd., Kidbrooke Park Road, London, S.E.3.

knobs

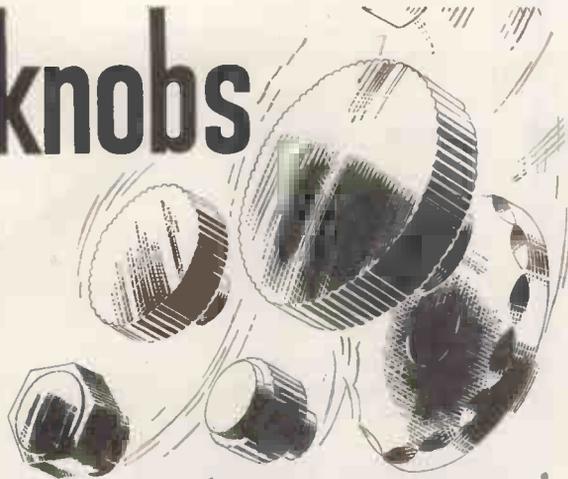

AND know-how


Although radio amateurs the world over have always been fond of knobs, the scientist and research worker likes his instruments to be efficient and functional and to perform their ancillary tasks as accurately and unobtrusively as possible. Nagard Oscilloscopes are designed with just these points in mind.

When the capacity and accuracy of Nagard instruments are considered, the controls are astonishingly few in number. Those that are present are clearly marked and perform specific and essential functions free from interaction with other controls. In addition, the six inch flat screen, well placed to avoid distracting ambient light and provided with a clearly marked and internally illuminated graticule, allows comfortable viewing together with accurate trace measurement. The instruments are of unit construction and cover a very wide band with exceptionally high gain.

A further aid to the operational efficiency of Nagard Oscilloscopes is provided by the Nagard Floor Trolley. This is carefully designed for mobility and enables the viewing angle of the screen to be easily adjusted. The trolley has three point support for stability on uneven floor surfaces, occupies very little floor space and is robustly constructed.

The Nagard Organisation exists to aid research, where accurate measurement of dynamic phenomena is involved. If you would like details of Nagard Wide Range Calibrated Oscilloscopes or Amplifiers, or would be glad of the co-operation of Nagard technicians to solve a definite problem, please communicate with the manufacturers.

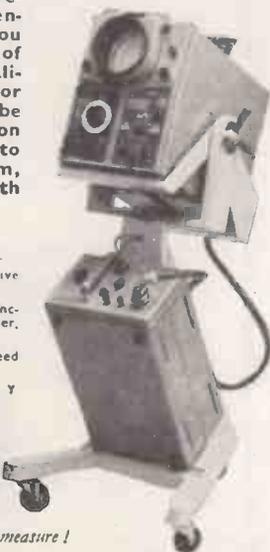- MODEL L 103 For High Speed Transients.
- MODEL A 103 For Pulse Work and Repetitive Signals up to 10 Mc/s.
- MODEL F 103 For General Work at Frequencies up to 1 Mc/s, High Gain D.C. Y Amplifier, Excellent Triggering.
- MODEL G 103 As above but with Slow Speed Time Base.
- MODEL H 103 Extra High Gain D.C. Y Amplifier up to 200 Kc/s.



NAGARD
LTD

See what you measure!

18, Avenue Road, Belmont, Surrey

VIGILANT 0345

MAGNETIC RELAYS

Built to Specification

TYPES 3000 and 600
HIGH SPEED and A.C. to 400 VOLTS
TROPICALISING—IMPREGNATING



UNISELECTOR




SWITCHES

From 3 to 8 Bank—All Resistances

KEY SWITCHES

Several types
in stock

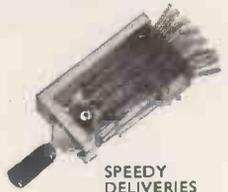

GOVERNMENT CONTRACTORS

SPEEDY DELIVERIES

JACK DAVIS (RELAYS) LTD.

36 PERCY STREET · LONDON · W.1
MUSEUM 7960 LANGHAM 4921

A SELECTION from our GENERAL LIST

MIKES. Acco Mic. 22-2, 84/-; Mic. 30, 50/-; Rothermel 2.AD/56, 63/-; Lustraphone C.51/Z, 25/15/-, base extra 10/6.
LOUDSPEAKERS. Goodman Audio 60, 28/12/6; Axiom 150 Mk. II, £10/5/6.
W.B. HIGH FIDELITY, 3 ohm coil, HF. 610, 61inch, 50/6; HF.810, 8in., 80/6; HF.912, 9in., 87/-; HF.1012, 10in., 73/6; (150 available at 73/6).
COILS. (State range required). Osmor Q, 4/-; Weymouth H. 3/9; Wearite P, 3/-; Denco C.T.F. 3/- pr.; Denco Maxi-Q std. or miniature, 2/11, with reaction 4/9. R.E.P. dual range high gain 4/-. OSMOR Q Coilpacks, Type HO 48/-; I.M. 40/-; Batt. 50/-; TRF, 40/-; ETA 4 Station Tuning pack, 43/8.
I.F. TRANS. (465 K/c.s.) Denco I.P.T. 11, 12/- pr.; I.P.T. 6, 18/4 pr.; Wearite M.800, 21/- pr.; Weymouth P.4, 15/- pr.; P.5, 8/6 each; P.5A, 10/- each.
OUTPUT TRANSFORMERS. 50 Watt. FOTTEE de Luxe type to suit single or push-pull PK4, 6V, 6L8 & KT66 valves. Optimum loads 4,000 to 10,000 ohms. Elevations 131: 1 to 78: 1, 47/8. Elstone M.B.T 4 w. multi-ratio, 8/9; Elstone MR7, 7-10 w. multi-ratio, 18/9; MR.16, 15 w. multi, 41/6; MR.30, 30 w. multi, 49/6. Woden Williamson, Potted. WOT.26, 1.7Ω sec., 28/10/-; WOT.26, 3.8 ohm. sec., 26/18/6.
RECTIFIERS. Brimar 75 T. & C. RM.1, 5/3; RM.2, 5/9; RM.3, 7/-; RM.4, 21/-; DRM.1B, 11/6; DRM.2B, 12/6; DRM.3B, 15/-; K3/45, 8/3; K3/50, 8/9; K3/100, 14/8; Westinghouse 14A86, 20/4; 14A100, 26/-; 36EHT45, 23/8; 36EHT50, 26/1; 36EHT100, 29/5; 14D36, 11/7; WX.3 & WX.6, 4/- each.
TAPE DECKS. Truxor Mark III, 223/2/-; Motek type K.4 with super sensitive heads, 217/17/-; TAPE. Emirate and Scotch Boy 1,200ft., 35/-; 600ft., 21/-; Ferrovoice, 1,200ft., 22/6; 600ft., 15/-; 300ft., 8/6. Spare REELS, 1,200ft., 4/6; 600ft., 2/6; 300ft., 2/3.
WIDE ANGLE COMPONENTS. ALLEN. Teleking Chassis, 50/-; Coilets, (TK & Super-Visor), 44/6; LO.308, 40/-; FG.305, 21/-; DC.306c., 39/6; FC.302, 21/-; GL.16 & 18, 7/6 each; SC.312, 21/-; AT.310, 30/-; OF.11, 9/-; BT.314, 15/-; DENCO Chassis Magnaview, 37/6; Chassis Super-Visor, 51/6; Coilets, Magnaview, 41/2; WA/DCAL, 43/-; WA/FCAL, 31/-; WA/LCI & WCL, 7/6 each; WA/FMAL, 21/-; WA/LOTL, 42/-; WA/FBTL, 16/-.
ELAC Duo-mag Focallers, Low Flux, 37/6; Medium, 39/6; High, 42/-; Ion traps, all types, 5/- each.
SUNDRIES. Denco MTO.1 test oscillator, 75/-; AVO Universal AC-DC Minor, £10/10/-; DECALs, standard, 4/9, post free. Amateur, 3/9, post free; J.E. Dial assemblies, 8L.5, 28/6; 8L.8, 27/6; TYANA Std. Irons, 16/9; ERIE RESISTORS, type 8, 1 w., 6d.; Type 2, 2 w., 10d., all listed values 10Ω to 10 meg. ERIE Silertex 10 watt w/w resistors, 25Ω to 10k., 2/- each.
Send 6d. stamps for our General List of components for Viewmaster, Soundmaster, Williamson Amplifier, Teleking, Magnaview (Brimar & English Electric large screen TV), Super-visor; Close tolerance Silver Micacs etc., etc. Please add 1/- postage to orders under 21.

L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH

Tel.: 3811

HELICAL MEMBRANE COAXIAL CABLES

The Helical Membrane cable was developed primarily for radio-frequency applications to provide a highly efficient construction which would not have the same frequency limitations as disc-spaced cables. The insulation is comprised of a thin Telcothene* tape spirally wound edge-on around the inner conductor. A practical method of achieving this basic form of the insulation was sought unsuccessfully for many years until Telcon succeeded in overcoming the difficulties involved. In the practical form which has been realised, the effective permittivity is as low as that of any commercial form of disc-spaced cable whilst tests indicate that an extremely high degree of uniformity has been achieved. In combination with an aluminium sheath as an outer conductor and a watertight covering, it has electrical characteristics closely approaching the optimum and yet is mechanically robust and reliable.

Please ask for publication HM/2

*Telcothene (Regd.) is polythene processed by Telcon to provide specific characteristics.

TELCON cables



THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD

Works: Telcon Works, Greenwich, S.E.10. Tel: GREENWICH 3291

Branch Office: 43 Fountain Street, Manchester 2. Tel: CENTRAL 0758

Manufactured in accordance
with Patent No. 627815

THE



'IMPRESARIO' COMPLETE ENTERTAINER TAPE RECORDER

The "Impresario" is a combination instrument that will make high quality tape recordings of live speech or music, gramophone or radio and telephone conversations, etc.

- DUAL SPEED: 3 $\frac{3}{4}$ in./7 $\frac{1}{2}$ in. per sec.
- TWIN TRACK: Up to 2 hrs. recording.
- SEPARATE BASS AND TREBLE CONTROLS.
- 4 WATTS OUTPUT: Neg. F/B.
- INTERNAL MIKE RECORDING SYSTEM.

The "Impresario" can also be used as a high quality radio, gramophone or microphone amplifier.

PRICE **49 $\frac{1}{2}$ GNS.**
(EXCLUDING TAPE)

RADIO RECEIVER


The "Impresario" is the first transportable tape recorder in Great Britain to provide power supply and internal space for a radio tuner unit with optional listening and/or recording.

DISTORTIONLESS SUPERHET 3-WAVE RADIO TUNER UNIT
May be fitted in a few minutes.

PRICE **14 GNS.**
(TAX PAID)

PIEZO-ELECTRIC MICROPHONES

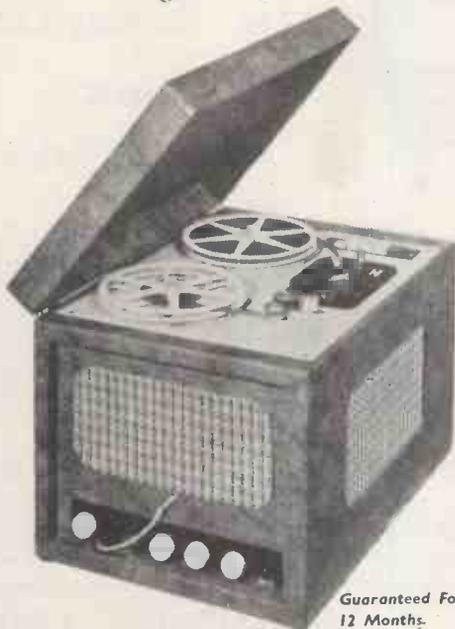Hand unit in rubber grip...3 gns. Studio Floor-stand Pattern...6 gns.
Telephone Pick-up Stand...3 gns.



Guaranteed For
12 Months.

Send for "Impresario" Illustrated Brochure which also contains details of Radio Tuner Unit, Telephone Pick-up, Suitable Microphones and Recording Tape.
LEE PRODUCTS (GREAT BRITAIN), LTD., ELPICO HOUSE, GT. EASTERN ST., LONDON, E.C.2.

MODERN ELECTRICS LTD.,

164, Charing Cross Road, London, W.C.2.

Tel.: TEMple Bar 7587.

Cables: Modcharex, London.

Export enquiries welcomed.

Immediate delivery from stock.

Prompt attention to post orders.

TAPE RECORDERS

GRUNDIG 700L	£84	0	0
BAIRD Soundmaster	£68	5	0
BAIRD Mk. II	£61	19	0
FERROGRAPH 2A	£79	16	0
VORTEXION	£84	0	0
SOUNDMIRROR Twin Track			
Table	£69	10	0
Portable	£74	10	0
WEARITE TAPE DECK	£35	0	0
TRUVOX TAPE DECK	£23	2	0

RECORDING TAPES

GRUNDIG L.G.S. 1,200ft.	£2	0	0
FERROVOICE Spare Spools.....	4	6	
E.M.I. H60, 1,200ft.	£1	15	0
E.M.I. H60, 600ft.	£1	1	0
E.M.I. H65, 1,200ft.	£1	15	0
E.M.I. H50, 1,200ft.	£2	8	0
SCOTCH BOY 1,200ft.	£1	15	0
600ft.	£1	1	0
Spare Spools 1,200ft.	4	3	
Spare Spools 600ft.	3	3	
FERROGRAPH 1,200ft.	£2	5	0
1,750ft.	£3	3	0
8 1/2 in. Spools	9	6	
AGFA 1,200ft.	£1	17	6
600ft.	£1	2	6

RECORD REPRODUCING EQUIPMENT

COLLARO 3-sp. Unit complete with studio P/U.....	£10	6	1
GARRARD R.C.80.....	£17	1	3
R.C.90.....	£17	16	6
R.C.80 A.C./D.C.	£24	14	4
TA/A.C.	£9	10	10
TA/B Decca	£13	7	1

SPEAKERS

TRUVOX 12 in. 3Ω.....	£2	5	0
WB STENTORIAN HF. 610	£2	10	6
HF. 912	£3	7	0
HF. 1012	£3	13	6
GOODMANS Axiom 150 Mk. 2 ...	£10	5	6
Axiom 102	£9	18	2
Axiom 101	£6	12	1
Audiom 60	£8	12	6

WHARFEDALE W15 CS	£16	0	0
Super 12 CS/AL	£16	0	0
W12 CS	£9	15	0
Golden 10 CSB	£8	6	7
Super 5 and 8 CS/AL	£6	13	3
Bronze 10in.	£4	12	9
Bronze 8in.	£3	4	0
W.B. Crossover Unit	£1	6	6
W.B. Tweeter Unit ...	£3	15	6

TEST GEAR

AVO Model 8	£23	10	0
Model 7 (latest)	£19	10	0
Unimior Mk. II	£10	10	0
Electronic Meter.....	£40	0	0
Wide Band Sig/Gen... ..	£30	0	0
Valve Characteristic Meter.....	£60	0	0
D.C. Minor	£5	5	0
10kV Multiplier for Model 8	£3	5	0
Carrying Cases for Models 7, 8 and 40 ...	£3	0	0
ADVANCE H.1 (Sig/Gen)	£25	0	0
E.2 (Sig/Gen)	£28	0	0
J.1 New Model.....	£35	12	0
P.1	£19	19	0

COSSOR Oscilloscope 1049	£150	0	0
Oscilloscope 1052	£104	0	0
Volt: Adaptor 1433	£18	5	0

TAYLOR All new Taylor Test Gear in stock.

PICK-UPS

ACOS GP.20 (Std. or L.P.)...	£3	6	1
Spare heads for above	£2	0	0

DECCA X.M.S. Magnetic	£6	9	5
-----------------------------	----	---	---

CONNOISSEUR Super 2 Hds.	£9	5	6
Spare Heads.....	£3	6	3

COLLARO STUDIO Type O or P.....	£3	14	4
---------------------------------	----	----	---

VALVES

We are one of London's largest stockists—Please write for requirements.

MICROPHONES

ACOS Mic 22 (Crystal)	£4	4	0
Mic Inserts for above	£1	0	0
Mic 16 (Crystal)	£12	12	0
Mic 35-1 (Crystal).....	£1	5	0

LUSTRAPHONE M/C with T/F.C. 51... ..	£5	15	6
Heavy Table Base for above	£1	1	0

RESLO M/C (Low Imp.) Ribbon High Fidelity	£7	5	0
Mumetal Transformer	£1	15	0

MICROPHONE STANDS Floor, 3 extensions... ..	£3	12	6
Table Stand	£1	1	0

LEAK AMPLIFIERS

Point 1, TL.12	£28	7	0
Point 2, TL 25	£34	7	0
Vari-slope pre-amp... ..	£12	12	0
Type VS R.F. Tuner Unit	£35	1	3


SOLON. New Instrument Iron 200-250 v. 25 w.	19	8	
--	----	---	--

ALL GARRARD, CONNOISSEUR, DECCA and COLLARO HEADS AND STYLIS IN STOCK.

H.P. Terms available on all items over £10.0.0.

High Sensitivity

DOUBLE PURPOSE METER

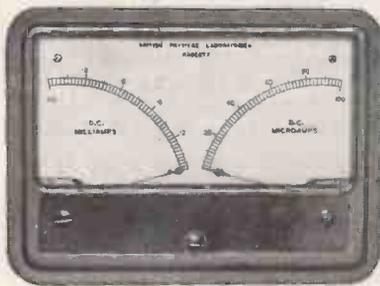

★ PANEL MOUNTING

MOVING COIL RANGES FROM 15μA
MOVING IRON RANGES FROM 5 MILLIAMPS

Movements are independent of each other and any two ranges may be incorporated. Panel space is saved and it enables more convenient observation of interdependent electrical quantities. Send for prices and full specification.

BRITISH PHYSICAL LABORATORIES



RADLETT, HERTS. Tel.: Radlett 5674/5/6
LONDON STOCKIST: M. R. SUPPLIES LTD.,
68 NEW OXFORD STREET, W.C.1

dm BP.2J



Actual Size

NEW!

The Manning-Carr Miniature Polarised Relay

DATA—A Sensitivity of 25 milli-watts and capable of handling mains voltage on the contacts with alternating currents up to 0.25 amps. Being polarised it has the advantage that the Armature contact can be biased to lock in either direction by suitable adjustment of the contact screws, which provides a useful facility where pulse operation is required. Speed of operation is also high and the Relay will follow A.C. frequency of 50 c.p.s. Resistance 7,000 ohms, which is acceptable for Anode circuits. Alternatives to specification if required. Sole Concessionaires.


POST OFFICE TYPES 3,000 AND 600 RELAYS

to specification. Tropicalising, impregnating and Services jungle finish if required. Delivery 3-4 weeks. Manufacturers to H.M. Govt. Depts. and leading contractors.

L. E. SIMMONDS LTD.
5, BYRON ROAD, HARROW, MIDDXX.

Telephone: Harrow 2524-0315.

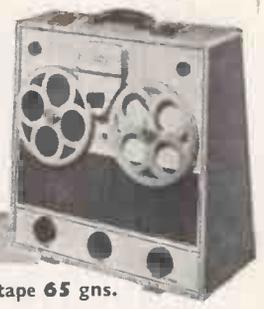A Service in Sound
 “—from the finest of
 portable tape recorders”
 says **BRIAN RIX**, Actor-Manager—
 Producer of “Reluctant Heroes.”



Brian Rix, G2DQU, successful impresario with a keen interest in Amateur Radio, has a trained ear for the technical merits of the Baird Soundmaster. “Here is a portable instrument”, he says, “with a performance equal to that of costly professional equipment. Its distortion-free, true-to-life recordings are the result of many new and impressive advances in high fidelity technique. The finest of all portable recording instruments, it’s invaluable at rehearsals.”

Complete with microphone and tape 65 gns.

**BAIRD
 SOUNDMASTER**

ALL-BRITISH
 TAPE
 RECORDER

BAIRD TELEVISION LIMITED
 LANCELOT ROAD · WEMBLEY · MIDDLESEX

NOW!

Fill in and post this coupon

TO BAIRD TELEVISION LTD. WEMBLEY MIDDX.

Please send me illustrated folder on the Baird Soundmaster

NAME

ADDRESS

AGENTS FOR THE
Astronic
 RANGE OF AMPLIFIERS



- A 1254 12 Watts High Fidelity AC Mains.
 (As illustrated.)
- A 1258 Tone Corrector unit for A 1254.
 (As illustrated.)
- A 1261 30 Watts Portable AC Mains.
- A 1262 12 Volt Power unit for A 1261.
- A 1263 40 Watts Portable AC Mains or Battery.

SOUTHERN ENGLAND AGENTS
 for
**Birmingham Sound
 Reproducers Ltd.**



The Monarch and Regent Gramophone Units, Styli, Matching Transformers and Spares.

Special Amplifiers, Transformers, Chokes and Laboratory Apparatus. A full range of Microphones and Loudspeakers available. For superb reproduction of gramophone records use the Monarch or Regent and A 1254. Obtain details from your local retailer or wholesaler. In case of difficulty and all overseas enquiries, write to “Dept. AB” at the address below.

N. MIERS & CO. LTD., 115 Gower Street, London, W.C.1
 Telephone: EUSton 7515. Cables: MIERSCO.

Reflectograph

MAGNETIC TAPE RECORDERS

Reflectograph Development provides a high performance Scientific and Industrial Recorder with the following features

SCIENTIFIC and INDUSTRIAL RECORDER

Frequency response at 7.5in. p.s. = $\begin{cases} 70 \text{ to } 15,000 \text{ c/s } \pm 3 \text{ DB} \\ 50 \text{ to } 15,000 \text{ c/s } \pm 6 \text{ DB} \end{cases}$
 Signal to noise ratio in excess of 55 DB, with less than 3 per cent harmonic distortion
 Synchronizing frequency injection control (Ratio of record to playback tape velocity may be synchronised at any tape speed to an accuracy of less than .01%)
 Continuously variable speeds from 15in./7½in. per second, or 7½in./3½in. per second
 Heavy duty synchronous capstan motor
 "Inching" control on rewind
 Fast forward and fast rewind. 10½in. or 7½in. spools
 Separate record and playback amplifiers
 Input and output impedances to order
 Audio output to order (normal 6 watts)
 Built into console type steel cabinets mounted on castors or in standard Post Office type racks

For full information on the Reflectograph range write to the Manufacturers

RUDMAN DARLINGTON (ELECTRONICS) LTD

Wednesfield, Staffs. Tel: *Wolverhampton 31704*

See us at the B.I.F. Olympia. Stand No. B.44

WhiteAd 2728R

STL

TRANSFORMERS for POWER SUPPLIES and AUDIO FREQUENCY CHOKES for A.C. and D.C.

Suitable for use in all electrical and electronic equipment, to Ministry, B.S.S. or commercial standards. Tropical or standard finish.



Enquiries from manufacturers and the trade only.

Quotations sent upon receipt of specifications or drawings.

STEWART TRANSFORMERS Ltd.
75 KILBURN LANE, LONDON, W.10

Tel.: LADbroke 2296/7

SHIP-TO-SHORE RADIO TELEPHONE FOR THE SMALL CRAFT

Here is an inexpensive Radio Telephone for the voluntarily equipped small ship. Low power but efficient for ship-to-shore and ship-to-ship conversations. Conforms to Post Office requirements. Simple to install and operate.

- PUSH-BUTTON SELECTION OF FOUR CHANNELS
- VERY LOW BATTERY CONSUMPTION
- SMALL AND LIGHT
Size: 18 in. x 11 in. x 7½ in.
Weight: 36 lb.
- FREQUENCY COVERAGE 1.5 to 4 mcs. (200 to 75 metres)



Price **£45** complete

MARINE RADIO COMMUNICATIONS CO.

Head Office:

46 GREYHOUND ROAD, LONDON, W.6

Phone: FULHAM 1138-9 Cables: Hallicraft, London

INTRODUCING — THE *Armstrong*

Specialists in High Quality Reproduction for over 20 years.




“SPECIAL” RADIOGRAM

AN OUTSTANDING RADIOGRAM WITH INDEPENDENT BASS AND TREBLE COMPENSATION GIVING PERFECT REPRODUCTION

Following the success of the “Standard” and “Super” Radiograms, Armstrong are proud to announce their latest Model. The “Special” combines years of experience in high quality reproduction and gives truly AMAZING reproduction from both records and radio. The cabinet is finished in a beautifully polished walnut.

BRIEF SPECIFICATION : — 8 valve, 3 wave-band superheterodyne chassis, giving 8 watts push-pull output with negative feedback. Independent BASS and TREBLE lift and cut controls. High flux 10in. Permanent Magnet Loudspeaker with rigid die cast frame, in special adjustable reflexing sound chamber. Collaro 3-speed autochanger for 7in., 10in. and 12in. records with turnover crystal pick-up head. Cabinet dimensions 36in. × 18in. × 36in. high, with two large record storage cupboards.

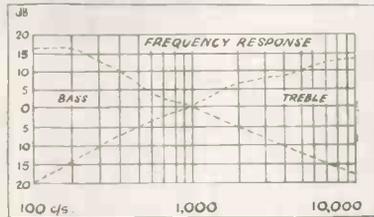
★ **FOR FULL DETAILS OR DEMONSTRATION**
Please write or call. Our Warlters Road Showrooms are open daily from 9 a.m. to 6 p.m. (Saturdays until 5 p.m.)



79 GUINEAS (TAX PAID)

ARMSTRONG WIRELESS & TELEVISION CO. LTD., WARLTERS ROAD, HOLLOWAY, LONDON, N.7. Tel. NOR 3213/4

Instruments for Research & Industry

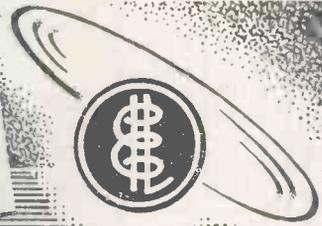

MODEL 29

Twenty Million Megohmmeter

The Model 29 Megohmmeter is a direct reading instrument covering a range of 0.3 to 2×10^6 megohms. Internal test voltages of 85 and 500 are provided, but up to 1000 v. may be used from an external source. The instrument is extremely simple to operate and is being widely used for testing cables, condensers and dielectrics of all types.



ELECTRONIC INSTRUMENTS LTD
RICHMOND · SURREY · ENGLAND

GUYNE RADIO LTD.

18, TOTTENHAM COURT ROAD, LONDON, W.1

MUSEUM 5929/0095.

All goods specially selected for quality and value. Prompt service—Money-back guarantee—It will pay you to visit our new rebuilt shop premises. Situated 50 yds. only from Tottenham Court Road Tube! (Genuine)

P.M. SPEAKERS. Elac 2 1/2 in., 15/-; Elac 3 1/2 in., 15/-; Plessey 3 in., 9/11; Plessey 5 in., 14/-; 5 in. Goodmans at 15/-; 6 1/2 in. Goodmans at 16/6; 8 in. Elac at 17/6; 10 in. Plessey at 16/6; 10 in. Elac at 22/6; 10 in. Lectrona at 17/6; 10 in. Rola with Transformer, 22/6; 12 in. Truvox, 47/6. All 3 ohm speech coil. Also the new Baker, 12 in., 16 ohms 15 watt. A quality speaker at 115/-. Also 2 1/2 in. Elac 15 ohm at 15/-. In addition to the above, we can definitely supply from stock the complete range of new W.B. "Hi-Fi" Speakers, Wharfedale and Goodmans. Also W. Harterdale Cross-over units, Transformers, etc. Limited quantity only of mains engrafted Plessey 8 in. 1,500 ohm. field at 27/6 each.

EX-W.D. CATHODE RAY TUBES. Guaranteed full picture. VCR97 at 40/-. VCR5170 at 35/-. Also VCR139A—ideal for oscilloscope 2 1/2 in. screen at 35/-. We also have VCR97 with slight cut-off, very suitable for oscilloscope, testing purposes, etc., at 16/6 only. All these tubes are brand new, in original packing, and tested before despatch. Please add 2/6 packing and carriage for any of the above tubes.

INTRODUCING L.T. RECTIFIERS TYPE R.K. A newly manufactured range, fully guaranteed for 12 months. 6 v. 1 A. Centre Tapped, 5/- each. 6 or 12 v. 1 A. F.W. bridge type ... 7/6 6 or 12 v. 2 A. F.W. bridge type ... 12/3 6 or 12 v. 3 A. F.W. bridge type ... 11/6 6 or 12 v. 4 A. F.W. bridge type ... 15/- 6 or 12 v. 6 A. F.W. bridge type ... 23/6 6 or 12 v. 10 A. F.W. bridge type ... 37/6

CHARGER TRANSFORMER. High grade wax-dipped, 220/240 v. input, 6/12 v. 2 A. at 11/8 only. Also 6/12 v. 4 A. at 17/6.

COLLARO RECORD CHANGERS TYPE RC/521. Complete with two GP27 Crystal Plug-in heads—One for standard and one for Long-playing records. Brand new in sealed cartons at very low prices. £9/19/6—Or the same changer with orthodynamic turn-over head, at £10/9/6, carriage free. Tax Paid.

VERY SPECIAL HIGH-QUALITY RADIOGRAM CHASSIS. We have purchased a limited quantity of these chassis by Britain's leading manufacturers of quality radiograms. Circuit is a 3-waveband five-valve superhet with A.V.C. Valves 6K90 frequency-changer 6B80 I.F. amplifier, detector and A.V.C. 6B17GT. Combined pick-up amplifier and A.F. Amplifier on Radio and Gram. 6V60, beam-power output tube; 5Z4G full-wave rectifier—Employing a special circuit for gramophone pre-amplification—A continuously variable tone-control provides ample treble control without accentuating the bass. Large glass dial, horizontal tuning measuring 1 1/2 in. x 3 1/2 in. Chassis measurement: 1 1/4 in. x 9 in. x 8 in. This is a superior chassis designed to sell originally in a Radiogram costing £79. Our price is £13/19/6 only, tax paid, plus 5/- packing and carriage. We will gladly demonstrate this chassis or any other working item from our stocks to personal callers!

CONSOLE RADIOGRAM CABINETS. This is an attractive figured walnut cabinet, originally intended for the above superhet chassis. It is constructed to take the chassis in the top part, dial being permanently visible through sloping front. Underneath the gramophone unit is housed in a drawer which slides forward on steel runners—when required for use—Total Cabinet measurement is 36 in. high, by 20 in. wide, by 16 in. deep—Our price for the cabinet only is £9/17/6, plus 10/- packing and carriage.

● The Collaro changer listed above fits neatly in drawer of this cabinet! ● We can supply the three units, cabinet, chassis and changer, if purchased together at one time, at a price of £32/10/- plus 20/- packing and carriage. May we suggest an 8 in. Elac P.M. Speaker at 17/6? Fully assembled model being demonstrated at our shop premises.

THE "SUPERIOR" FOUR KIT
Our new four-valve receiver. A.C. mains. 200/250 v. M. and Long Waves. As with our very successful "Economy Four" all required components are supplied. Valve line-up 2-6BGT, 6X5GT and 6V6GT. Chassis ready-drilled: Cabinet size—10 1/2 in. high x 10 in. wide. Maximum depth at Base—5 in., tapering to 3 1/2 in. at top. Sloping front. Very attractively finished in light walnut and peach. Each component brand new and tested prior to packing. Complete Instruction Booklet with practical and theoretical diagrams is provided. Booklet available at 1/6—post free. Our price for complete kit—£6/9/6!!! Please add 2/6 packing and carriage.

If preferred, we can supply Cabinet Assembly only, comprising Cabinet and back, Drilled chassis and bracket, wave change switch, dial, pointer drum, pulleys, drive spindle, drive spring and knobs—at 45/-. plus 2/6 packing and carriage.

N.B.—Our Kits are even supplied with sufficient solder for the job!



		METERS		
F.S.D.	Size	Type	Fitting	Price
250 microamp	D.C. 2 1/2 in.	M.C.	F.R.	40/-
500 microamp	D.C. 2 in.	M.C.	F.R.	18/6
500 microamp	D.C. 2 1/2 in.	M.C.	F.R.	35/-
1 mA.	D.O. 2 in.	M.C.	F.S.Q.	17/6
1 mA.	D.O. 2 in.	M.C.	F.S.Q. (Scale Calib. 1.5kV)	15/-
1 mA.	D.C. 2 1/2 in.	M.C.	F.S.Q.	27/6
5 mA.	D.C. 2 in.	M.C.	F.R.	7/6
10 mA.	D.C. 2 1/2 in.	M.C.	F.R.	10/-
15 mA.	D.O. 2 in.	M.C.	F.R.	7/6
20 mA.	D.C. 2 in.	M.C.	F.R.	7/6
30 mA.	D.C. 2 in.	M.C.	F.S.Q.	8/6
200 mA.	D.C. 2 1/2 in.	M.C.	F.R.	10/-
500 mA.	D.C. 2 in.	M.C.	F.R.	6/6
5 amp.	R.F. 2 in.	Thermo	F.S.Q.	4/6
2.5 amp.	AC/DC 2 in.	M.I.	F.R.	12/6
3 amp.	R.F. 2 in.	Thermo	F.S.Q.	7/6
5 amp.	D.C. 2 in.	M.C.	F.R.	13/6
20 amp.	D.C. 2 in.	M.C.	R.F. (with shunt)	10/6
10 v.	D.C. 2 in.	M.C.	R.F.	8/6
150 v.	D.C. 2 1/2 in.	M.C.	F.R.	15/-
500 microamp	D.C. 2 in.	M.C.	R.F.	13/6
500 mA.	D.C. 2 1/2 in.	M.C.	F.R.	8/-
6 amp.	R.F. 2 1/2 in.	Thermo	F.R.	7/6

PORTABLE RECORD PLAYER CABINETS. Manufacturer's surplus, brand new. External dimensions 15 in. x 16 1/2 in. x 8 in. deep. Finished attractively in dark brown veneer. Motor board cut for B.B.R. Monarch Changer, but will take any standard single player; also room for amplifier. Front view shows attractive grill for speaker. Leather carrying handle, two snap locks. Price 45/- only, plus 2/6 packing and carriage. Also available to take any standard single player—brown leatherette covered. Complete with locks and carrying handle. Size 15 in. x 15 1/2 in. x 6 1/2 in., 22/6 only, plus 2/6 packing and carriage.

45 Mc/s PVE STRIP—Brand new complete with 6 valves type EF60 and one EA50, 70/- only.



THE "ECONOMY FOUR" T.R.F. KIT.

A three valve plus metal rectifier receiver. A.C. mains 200/250 v. Medium and Long waves. We can supply all required components right down to the last nut and bolt. Valve line-up, 6K7, 6J7 and 6V6. Chassis ready drilled—Cabinet size 12 in. long by 6 in. high by 8 in. deep—Choice of Ivory or brown bakelite, or wooden, walnut finish cabinet. Complete instruction booklet with practical and theoretical diagrams. Each component brand new and tested prior to packing. Our price £5/15/- complete—Remember this set is being demonstrated at our shop premises! We proudly claim that our fully shop receiver—Booklet available at 1/6 post free—This is allowed if kit is purchased later—Please, 2/6 packing and carriage for complete kit.

CABINETS. We can supply a cabinet for every requirement, Table Model, Extension Speaker, Portable Player, Console, even for Projection T.V! Why not call and see us?

SPECIAL OFFER—Garrard A.C./D.C. model "E" centre drive motor—Auto-stop and special for 78 r.p.m.—Speed regulator—Few only at £7/19/6, plus 2/6 packing and carriage. We also have in stock—Connaisseur 3-speed motors, pick-ups, and heads, by Garrard, Decca, Collaro, Aco, Chancery, etc., etc., all at current prices!

BRAND NEW R1155A RECEIVERS guaranteed serviceable in original packing cases £11/19/6. Fully assembled Power Pack and output stage, to plug straight in to R1155 for A.C. 200/250 volts, at 79/6—Deduct 10/- if purchasing receiver and power pack at the same time.

DECCA RECORD PLAYERS. MODEL 93A. A complete playing-desk, brand new, ready to plug in. Can be supplied with either standard or long-playing crystal heads, at £4/19/6, or complete with both heads at £5/19/6. Also available from stock at current list prices, Collaro A.C. 3/534, RC/531, RC/532, etc. Garrard RC75, Garrard RC76, A.C./D.C. RC80A, and perhaps by time of appearance of this advert. RC1101 Also, ex-stock, Connaisseur 3-speed motors, Pick-ups by Collaro, Decca, Connaisseur, Rothermel, Aco, Chancery, etc.

TAPE RECORDER CABINETS. We can offer a well-constructed cabinet, handsomely finished in grey or brown redine, made specifically to take Truvox or Wearite Tape Decks, Measur 22 in. x 14 in. x 9 in. deep. Completely portable, shows attractive speaker grille at end, and made to take up to 8 in. Speaker. We guarantee satisfaction and will be pleased to refund cash if dissatisfied. Ample room for suitable amplifier. Price 79/6, plus 2/6 packing and carriage. N.B. We can supply from stock the latest Truvox and Wearite Tape Decks at 22 guineas and £35 respectively. Reduction of 20/- on cabinet if purchased at the same time as either of these tape decks!!!

RADIOGRAM CHASSIS

3 Wave-band Superhet. Med., long and short.
6 Latest Type MULLARD Valves.
4 Position Switching Gram., med., long and short.
Provision for A.C. Mains.
Extension Speaker. 110/250 v. Chassis 1 1/2 in. x 7 in. x 2 1/2 in. Scale 8 in. Square.
Or Chassis 1 1/2 in. x 6 1/2 in. x 2 1/2 in. Dial 10 in. x 5 1/2 in.

PRICE £10/5/-

BRAND NEW AND GUARANTEED. CAB. PACKING AND INS. 10/-

We can also supply and demonstrate any of the "Dulci" well-known Radio-Gram Chassis advertised elsewhere in this issue—at list prices.

R.F. UNITS. All new condition and complete. Case size 9 1/2 in. x 5 in. Type 24—20-30 Mc/s, 15/- Switched Tuning. Type 26—40-80 Mc/s, 19/6 Switched Tuning. Type 27—64-88 Mc/s, 45/- Variable Tuning. We have a limited supply of RF97 new condition and complete, but tuning dial damaged. Price 30/- each only. ALL these units Post Free!!

ELPICO 4-WATT AMPLIFIER, AC/34. A small 3-valve 3-stage audio amplifier. AC 200/250 v. Output 4 watts. 2 1/2 ohm. Suitable for Radio, Microphone or Gramophone input. Volume and Tone Controls—Valve line up. 6B17, 6V6, 5Z4—Engraved front panel. Size of chassis only—7 in. x 5 in. x 2 in. Overall height—5 1/2 in. Price £7/10/-. Each amplifier guaranteed for 12 months.

H.T. RECTIFIERS BY S.T.C. TYPE RM1 at 4/6, RM2 at 5/-, RM3 at 6/-, RM4 at 12/6, DRMB1 at 9/6, DRMB2 at 10/6. E.H.T. Rectifiers Type K3/25 at 5/3, K3/40 at 7/6, K3/45 at 2/6, K3/50 at 8/6, K3/100 at 14/8, K3/130 at 8/6, and K3/200 at 26/-. New Surplus 300 v. 60 mA, 8/6.

METER RECTIFIERS. 1 mA. by G.E.C., at 11/6, also 6 mA. by Westinghouse at 8/6. I.P. TRANSFORMERS. SPECIAL OFFER. All iron-core 465 K/C/S. By Weymouth, Size 3 1/2 in. x 1 1/2 in. x 1 in., 8/6, or Philips, size 2 1/2 in. x 1 1/2 in. diameter (cylindrical), 7/6 pair. By Invicta—Cylindrical, 2 1/2 in. x 1 1/2 in. diameter, 8/6 pair. Also, our own special ultra-midget, size 1 1/2 in. x 1 1/2 in. x 1 1/2 in. Only 9/6 per pair.

K.B. WIRE RECORDER AMPLIFIERS. Limited supply of wire-recorder amplifiers complete, by Kolster-Brandes. Chassis measurements: 10 1/2 in. x 4 1/2 in. x 2 in., plus power pack chassis, measuring 8 in. x 4 1/2 in. x 3 in. Valve line-up, 6X5, 6V6, 2-6J5, 2-6J7, and 6U5 magic-eye. Incorporates built-in erase oscillator. These amplifiers are brand new, absolutely complete, but may require very slight attention. However, each amplifier carries a small tag listing any faults, and a complete circuit diagram is provided. Limited quantity only at £5/19/6, plus 5/- packing and carriage.

MAINS TRANSFORMER MANUFACTURERS' SURPLUS. Black tropical finish. Size 3 1/2 in. x 3 1/2 in. x 2 in. 250-250, 60 mA. 6.3 v. 3 A. (Centre Tapped) 5 v. 2 A., 10/6 each, plus 1/6 packing and postage.

VALVES. We have a very comprehensive stock of special purpose surplus valves at competitive prices. A stamp will bring Valve Price List.

You're SURE to get it at
STERN'S
 ESTABLISHED 25 YEARS

**FOR HOME CONSTRUCTORS
 A 5 VALVE 3 WAVEBAND SUPERHET RECEIVER
 for £10/10/-**

For use on A.C. Mains 200 to 250 volts. The following are outstanding features:

- A superhet circuit designed for high efficiency on all three wavebands.
- A 3 1/2 in. P.M. speaker accurately matched for good quality reproduction.
- The latest range of new 6-volt B.V.A. miniature valves.
- Built-in frame aerial with provision for external aerial for distant stations.
- A white plastic cabinet of very attractive appearance, overall size 7 1/2 in. x 5 1/2 in. x 5 1/2 in.

Send 2/6 for the fully descriptive stage by stage assembly and wiring diagrams, with which complete price details are given.



Ex W.D. TESTMETER

Complete with case and carrying strap.

23/6 Post and Ins. 1/3.

Provides direct readings of
 (a) 1.5 volt and 3 volts D.C.
 (b) 6 mA. and 60 mA.
 D.C. current
 (c) 500 ohm and 5,000 ohm resistance ranges.
 600 ohm and 600 D.C. at 6mA.
 F.S.D. by an external series resistor arrangement for 6/-.


A SPECIAL BARGAIN

Genuine Quality Equipment at a Greatly Reduced Price.

- A 4 stage superhet feeder unit, incorporating an R.F. stage and covering Long, Medium and Short wavebands, fully assembled, aligned and ready for use and
- A quality push pull amplifier also fully assembled and ready for use and
- A matched high fidelity 10in. W.B. S'tentorian "Cambridge Coned" P.M. Speaker.

Can be bought separately.
**Tuning Unit 12 gns.
 Amplifier £7.15.0**

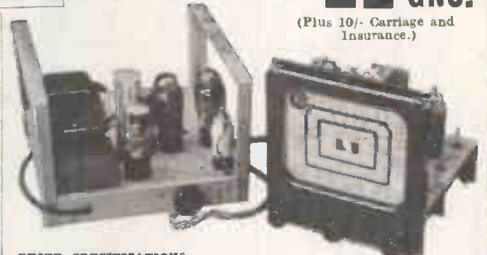FOR ONLY 22 GNS.
 (Plus 10/- Carriage and Insurance.)



BRIEF SPECIFICATIONS:

(A) FEEDER UNIT. Complete up to and including Audio stage, A.V.C. being applied to both I.F. and R.F. stage. Incorporates a "Magic Eye" tuning indicator and a Gram position on the wavechange switch. A separate Tone Control is provided on a "Flying Lead." Valve line up, 3F39, ECH35, EF39 and EBC33. Overall size of unit 8in. x 8in. x 9 1/2 in. high. Glass dial 8in. x 6in. (aperture required 6in. x 5 1/2 in.). An acetone is supplied.
 (B) A quality PUSH PULL AMPLIFIER designed and matched for use with the above feeder unit. Has two EL33's in push pull to produce maximum 8 watts, and an EBC33 as phase inverter. Incorporates power supplies for both units, and provides for high impedance Pick Ups. Overall size 11in. wide x 1 1/2 in. x 7in. high. THIS EQUIPMENT IS ABSOLUTELY NEW and is supplied ready for immediate use.




**CONSTRUCTORS SAY
 "IT'S STILL THE BEST MAINS OR
 BATTERY PORTABLE SET"**

chassis, etc. Overall size of assembled chassis 8in. x 4in. x 2 1/2 in. This receiver, as illustrated, can be completely built for approx. £10 (plus Mains Unit if required). Send 1/9 for the fully descriptive Assembly Book which includes Practical Layouts and complete Price list of Components. Attache case available separately 37/6.

A Midget 4-valve Superhet Portable covering medium and long wavebands. Designed to operate on A.C. mains 200/240 volts or by an "Alldry" battery. The set is designed so that the main section can be supplied as a separate unit, and can be added at any time. The Set supplied as an "Alldry" battery Superhet can be accommodated in the attache case illustrated (size 9 1/2 in. x 4 1/2 in. x 7in.). This is attractively finished in lizard, maroon, dark green or blue rexine. As a combined Mains/Battery Superhet Portable a polished cabinet is available to accommodate both Mains Unit and Batteries. Circuit incorporates delayed A.V.C. and pre-selective Audio Feedback. The Set is complete in every detail and includes ready-wound frame aernals, fully aligned I.F. transf. and drilled chassis, etc.

WIRELESS WORLD 3 VALVE SET

A Midget 3-valve T.R.F. Receiver for operation on A.C. mains, covering long and medium wavebands. We are able to supply all the components to build this set, as designed and specified in the Feb. 1950 issue, including the drilled chassis. Valves and moving coil speaker etc., at the following prices—
 To construct complete chassis less dial and drive assembly, £5/5/-. Ditto including dial and drive assembly £6. To construct the complete set, including dial and drive assembly and cabinet, £7/3/6. Overall size of cabinet is 7 1/2 in. x 3 1/2 in. x 1 1/2 in. A reprint of the designer's article, giving circuit and assembly instructions (this is available separately for 9d.) together with a practical component layout is included with each of above assemblies.

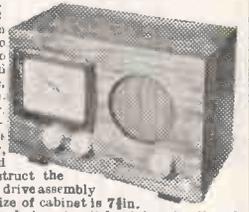

TWO BATTERY PORTABLES

(a) THE "MINI TWO-THREE"

An "Alldry" Battery Portable of midget size, 6 1/2 in. x 4 1/2 in. x 3 1/2 in., designed to cover medium waveband 190-555 metres, with use of short trailer aerial.

The simple design of this Receiver is so arranged that either a 3-valve set or a 2-valve (afterwards easily converted to the 3-valve) can be made.

Consists of a T.R.F. circuit using a regenerative detector with H.F. stage and a high gain output pentode. Valve line up 1T4-1T4-DL94.

The 2-valve set can be completely built for £4/3/6 (less case), and the 3-valve for £5/3/- (less case). Each price includes valves, speaker and drilled chassis.

Send 2/- for the assembly instructions: they include simple and complete practical component layouts and diagrams which enable the most inexperienced constructor to successfully build either set. All components are available for separate sale, a price list being supplied with assembly instructions.

(b) THE "MINI-FOUR"

As 4-valve Battery Superhet Receiver designed to receive 4 pre-set stations, three on medium waveband and one on long wave to suit local conditions. Each station is obtained on the set by the turn of a rotary switch. No tunings necessary.

It is of midget size, being only 4 1/2 in. x 6 1/2 in. x 4 1/2 in. when completely built and is very easily assembled from diagram supplied.

Cost of all components to build this set in accordance with the design, including a drilled and cut chassis and panel and new valves, is £9/10/- (or less valves for £6/7/6). Attractive carrying case finished in blue leatherette, 16/9. Complete constructional data with a blue print, which shows the practical component layout and wiring diagram, together with an individual component price list are available separately, 1/6. Our battery eliminators (illustrated above) available in kit form are suitable for use with this set.

When submitting orders, please include post and packing.

STERN RADIO LTD.
 109 & 115, FLEET STREET, E.C.4
 Tel.: CENTRAL 5812-3-4



**AN AMAZING OFFER!
 A COMPLETELY ASSEMBLED**


4 VALVE T.R.F. CHASSIS

Including a 5in. P.M. SPEAKER and VALVES FOR ONLY

£6/9/6

(Plus 7/6 carr. and ins.)

This receiver is of the very latest design and is for use on A.C. or D.C. Mains. It covers both Long and Medium Wavebands, and includes the modern B.V.A. miniature valves. The line up being 12 BA6-12AT6-12A6-35W4. It incorporates Permeability Tuned Coils, thus ensuring excellent selectivity and sensitivity. The overall size of the complete chassis including speaker is 10 1/2 in. x 4 1/2 in. x 6 1/2 in. An attractive Bakelite Ivory finished Cabinet size 11 1/2 in. x 5 1/2 in. x 6 1/2 in. is available for 16/6 (plus 2/6 carriage and insurance).

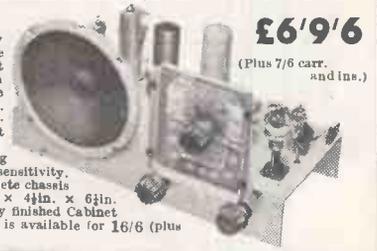

The DENCO M.T.O.I. Modulated Test Oscillator £3/15/-

(Plus 2/- carr. and ins.). Has Frequency range continuously variable from 170-475 Kc/s and 550-1,600 Kc/s. Battery operated and thereby completely self-contained.

"PERSONAL SET" BATTERY ELIMINATOR

A complete Kit of parts to build Midget "Alldry" Battery Eliminator, giving approx. 69 volts and 1.4 volts. This eliminator is for use on A.C. mains and is suitable for any 4-valve Superhet Receiver requiring H.T. and L.T. voltage as above, or approx. to 69 volts.

The Kit is quite easily and quickly assembled and is housed in a light aluminium case size 4 1/2 in. x 1 1/2 in. x 3 1/2 in. Price of complete Kit with easy-to-follow assembly instructions, 42/6. In addition we can offer a similar COMPLETE KIT to provide approx. 90 volts and 1.4 volts. Size of assembled unit 7in. x 2 1/2 in. x 1 1/2 in. Price 47/6.



THIS IS A STERN'S ADVERTISEMENT

Constructors everywhere are amazed!

AT THE EXCELLENCE OF

The "TELE-VIEWER"

5 CHANNEL TELEVISOR
DESIGN OF A COMPLETE 12" SUPERHET T.V. RECEIVER

HUNDREDS SOLD IN 4 MONTHS
SIMPLE DIAGRAMS MAKE
CONSTRUCTION EASY

PERFECT FRINGE AREA RECEPTION
BETTER RECEPTION AT HALF
COMMERCIAL COST



This complete TELEVISOR including all Valves, can be built for only
(Plus cost of C.R.T.)

£28-16-4

£12-19-6

We can supply a New 12in. C.R.T. at specially reduced price of

Here are some of the features which combine to make this such a fine receiver.

- The Superhet circuit easily tuned to any of the five channels, i.e., LONDON, SUTTON COLDFIELD, HOLME MOSS, WENVOE and KIRK-O-SHOTT. (The extreme ease of tuning is accomplished by the provision of pre-aligned I.F.T.s.)
- A lifelike, almost stereoscopic, picture quality made possible by the following factors:
 - a. Excellent band width of I.F. circuits.
 - b. A really efficient video amplifier.
 - c. C.R.T. Grid modulated from low impedance source.
 - d. High E.H.T. voltage (approx. 10 kV).
- The picture brilliance is also much above the average and enables comfortable viewing with normal room lighting or daylight.
- FIRM picture "HOLD" circuits (Frame-Line) ensures a steady picture, free from bounce or flicker even under the most adverse conditions met with in "fringe" areas and excellent "interlace" ensures the absence of "liney effect."
- Negative feedback is used in the audio frequency circuits which provide 2/3 watts of High Quality Sound.
- Entire receiver built on two chassis units each measuring 14½" x 6½" x 3½".

- Rigid C.R.T. mounting enables entire receiver to be safely handled with tube in position.
 - All pre-set controls are mounted on side of chassis enabling all adjustments to be carried out whilst facing the C.R. Tube.
- As no hire purchase terms are available the receiver can be bought in five separate stages (practical diagrams and circuits are provided for each stage) thus enabling hire purchase interest rates to be avoided. The complete set of ASSEMBLY INSTRUCTIONS is now available, price 5/-. The instructions include really detailed PRACTICAL LAYOUTS, WIRING DATA and COMPONENT PRICE LIST. ALL COMPONENTS ARE AVAILABLE FOR INDIVIDUAL PURCHASE. A CABINET WILL ALSO BE AVAILABLE.

NOW available at Stern's The "WIDE ANGLE" TELE-VIEWER

- A design that retains all the distinctive features of the 12in. Televisor but with increased Time Base efficiency, producing 15 to 16 kV. E.H.T., with ample scanning power for C.R. Tubes up to 17in.

It can be completely built including supply of all valves for **£34** (plus cost of C.R.T.) and is as simple to construct as the 12in. model.

- This is the most efficient "WIDE ANGLE" large screen design yet offered to constructors, and yet it can be built for almost half the cost of similar designs.
- Complete assembly instructions, diagram, etc., available for 5/-.

BATTERY CHARGER KITS

All Kits are for A.C. Mains 200-250 Volts. They comprise a Metal Rectifier and Transformer, tapped for 6 or 12 volt charging, and a tapped Resistor, with Selector Switch, to enable the charging rate to be varied.

For 6 or 12 volt batteries at max. 1 amp. £1/17/6
For 6 or 12 volt batteries at max. 2½ amp. £2/5/3
For 6 or 12 volt batteries at max. 4 amp. £3/2/8
An easily followed Wiring Diagram is included with each kit.

THE DENCO ULTRA MIDGET SUPERHET COIL TURRETS WITH A ROTARY TURRET ACTION

Type CT9 consists of a four-station "pre-set" unit from which any three stations on medium waveband and one on long wave can be received by a turn of the turret switch. Price 39/6.

Type CT10, is a 3 waveband coil pack incorporating a fourth switch position for Gram. Complete coverage is: long waveband 700-2,000 metres, medium waveband 190-570 and short wave 15-50 metres. Price £2/8/-. A complete receiver circuit and all necessary data are included with each turret. These can be supplied separately for 6d.

VARLEY HEATER TRANSFORMER

Input 200-250 volts. Output 4 **14/9** (1/- postage).
volts (centre tapped) 5 amps

A COMPLETE "CAR RADIO" FOR THE HOME CONSTRUCTOR



11½" x 4½" x 3½"

A design of a complete 5-VALVE SUPERHET RECEIVER employing an B.F. Stage and incorporating a separate VIBRATOR PACK size 4½" x 2½" x 6½in. for use on 6 or 12 volt D.C. supplies. We can supply all components to build this complete Receiver and Vibrator Pack including a Metal Case, Valve, Drilled Chassis and 5in. P.M. Speaker for £12/19/6. (Carr. and Ins. 5/6 extra). Or the receiver Components for £9/19/6 and the Vibrator Components for £3. This is NOT an EX-GOV'T. Receiver, it is a new design employing new Components. Send 2/8 for the complete set of ASSEMBLY INSTRUCTIONS, CIRCUITS and PRACTICAL LAYOUTS, including a complete individual Component Price List.

!! AMPLIFIERS !! EASY TO BUILD COMPLETE KITS OF PARTS

A 4-VALVE QUALITY "PUSH-PULL" 8-8 watt AMPLIFIER for A.C. mains. Incorporating Negative Feedback. Filter Input Circuit and employing 6V6s in Push-Pull. A simple arrangement is provided to enable either a magnetic-crystal or lightweight pick-up to be used, and is suitable for use with Standard or long-playing records. A tone control is incorporated, and the 10-watt output transformer is designed to match 2 to 16 ohm speakers. The overall size of the assembled chassis is 10in. x 8in. x 7½in. high, and full practical diagrams are supplied. Price, including drilled chassis and valves, of complete kit, £6/17/6. Price of assembled chassis, supplied ready for use, £8/12/6. Plus 5/- Carr. & Ins. Full descriptive leaflets are available separately for 1/-.



A 12-watt HIGH FIDELITY "PUSH-PULL" AMPLIFIER designed for A.C. mains 200 to 250 volts employs 6 valves plus rectifier with negative feedback, and comprises a main amplifier chassis and a remote controlled Pre-amplifier and Tone Control Unit, incorporating four controls—bass, treble, main volume or mixing control, and a radio, gram, microphone, selector switch. This control unit measures only 7 x 4 x 2½in. The measured frequency range of the amplifier with this unit shows an excellent response from 14,000 cycles down to 20 cycles—the bass and treble controls allowing independent control of gain at both ends of the frequency range from zero to a gain of 50. It can be seen, therefore that ample correction is provided to suit any type of pick-up with any type of recording. Input voltage for maximum output is 70 mV. 6.3 volts at 2 amps. and 30 mA. H.T. is provided for tuning unit, etc. Price of complete kit, including drilled chassis and valves, £14. Complete specification and layout, 2/-. We can also supply completely assembled and ready for use at £17. Plus 7/6 Carr. and Ins. THIS AMPLIFIER COMPARES WELL WITH THE WILLIAMSON AND SIMILAR DESIGNS AT A FRACTION OF THEIR COST.



Modernise your old Radiogram for only £25


THREE COMPLETELY ASSEMBLED ALL-WAVE SUPERHET CHASSIS

- Model B.3. A 5-valve 3-waveband Receiver.
- Model B.3.P.P. A 6-valve 3-waveband Receiver with PUSH-PULL OUTPUT.
- Model B.3.P.P./R.F. A 7-valve 3-waveband Receiver incorporating an R.F. stage with PUSH-PULL OUTPUT.

The three Receivers are for operation on A.C. mains 100/200 volts and 200/250 volts, and employ the very latest miniature valves. They are designed to the most modern specification, great attention having been given to the quality of reproduction which gives excellent clarity of speech and music on both gram. and radio, making them the ideal replacement chassis for that "old Radiogram," etc.

Brief specifications: Model B.3.—Valve line-up, 6BE6, 6BA6, 6AT6. 6BW6, 6X4—waveband coverage short 16-50 medium 187-550 long 900-2,000 metres. Controls: (1) volume with on/off; (2) tuning (flywheel type); (3) wave-change and gram.; (4) tone (3-position switch operative on gram. and radio). Negative feedback is employed over the entire audio stages. Chassis size: 11 x 7½ x 8¼in. high. Dial size 9¼in. x 4¼in.

Price complete and READY FOR USE, excluding speaker, £12/12/- (carr. and Ins. 7/6 extra). Model B.3. P.P. This model is the B.3 Receiver but incorporates two 6BW6 VALVES in PUSH-PULL, resulting in really excellent quality reproduction up to approximately 6 watts. Price £15/15/- (plus 7/6 carr. and ins.). Model B.3. P.P./R.F. This model is similar in appearance and has same waveband coverage as the Model B.3, but in addition it incorporates an R.F. STAGE together with PUSH-PULL OUTPUT, employing a total of 7 valves with two type 6BW6 in Push-Pull. This makes for a really sensitive receiver with genuine quality reproduction. Price £18/18/- (plus 7/6 carr. and ins.).

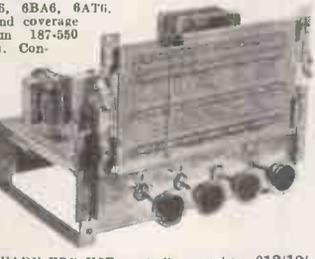

"MINI-TWIN" 1-VALVE BATTERY SET



A design of a simple 1-valve 2-stage Battery Receiver, giving excellent results on medium and long wavebands and having exceptionally low battery consumption. Drilled chassis and practical diagrams make it the ideal set for the beginner to build.

The complete chassis, including valve, can be built for 37/6 plus 8/11 P/Tax. The attractive plastic case is 8/6, and suitable headphones, 14/9. The complete assembly instructions, layouts and a component price list are available for 1/6. This Receiver also performs excellently, without modification, as a tuning unit, and, in addition, with simple modifications for which a complete diagram is provided, makes a first-class pre-amplifier for pick-up or microphone.

Speaker Bargains!

PLESSEY, 10in. 3 ohm V/coil.....	£1 5 0
TRUVOX, 12in. 3 ohm V/coil.....	£2 9 6
ROLA, 12in. 3 ohm V/coil.....	£3 19 6
BAKERS, 12in. 15 ohm V/coil.....	£4 12 6

(Carriage & Ins. 1/6 extra).

WE ALSO HAVE THE NEW W. B. "STENTORIAN"

HIGH FIDELITY SPEAKERS IN STOCK

Model H.F. 6-inch.....	£2 10 6
Model H.F. 9-inch.....	£3 7 0
Model H.F. 8-inch.....	£3 0 6
Model H.F. 10-inch.....	£3 13 6

These speakers are of the very latest design and provide quality reproduction for the lower-price range. 3 or 15 ohm models are available.

THE VIEWMASTER TELEVISOR

We have had very considerable experience in assisting customers to build this TV and can supply SPECIFIED COMPONENTS EX STOCK. The assembly instructions showing practical layouts and price list are available for 7/6 for London, Sutton Coldfield, Holme Moss, Kirk-o-Shotts and Wenvoe.

This AUTOCHANGE UNIT by a Famous Manufacturer is offered for £11/14/6

We will supply this 3 speed Autochanger and the Model B.3 Chassis on the left together with a 10in. (or 8in.) P.M. Speaker for £25 or with the B.3 P.P. for £28/7/6 or with the Model B.3 P.P. / R.F. for £31/5/- Carr. and Ins. 10/-.

(Plus 7/6 Carr. and Ins.) (Normal price is £16/10/-)

- These units will auto-change on all three speeds 7in., 10in. and 12in.
- They play MIXED 7in. 10in. and 12in. records.
- They have separate sapphires for L.P. and 78 r.p.m., which are moved into position by a simple switch.
- Minimum baseboard size required 15in. x 12¼in. with height above 5¼in. and height below baseboard 2¼in. A bulk purchase enables us to offer these BRAND NEW UNITS at this exceptional price.



The COLLARO 3RC/521 3-Speed AUTO CHANGE UNIT £9/17/6

We will supply this 3 speed Autochanger and the Model B.3 Chassis on the left together with a 10in. (or 8in.) P.M. speaker for £23 with the B.3.P.P. for £25/5/- or with the Model B.3.P.P./R.F. for £29 Carr. and Ins. 7/6 extra.

(Including Carr. and Ins.) (Normal price is £18/10/-)

- With separate crystal heads for standard and L.P. records.
- Incorporating pick-up weight adjustment.
- Will autochange on 7in., 10in. and 12in. records not intermixed.
- Minimum Base plate size 15in. x 12¼in., with height above 4¼in. and below baseplate 3in.



● Brand new in Maker's Cartons, complete with Mounting Instructions.

In addition to the Record Players advertised we have a FEW ONLY—NEW MANUFACTURER'S SURPLUS

COLLARO MODEL 3RC/522 This is the same type of unit as the 3RC/521 but it plays MIXED 10in. and 12in. records. Price £10/19/6 (plus 7/6 carr. and ins.).


LATEST COLLARO 3-SPEED AUTOCHANGER Incorporating the new STUDIO "O" PICK-UP. This is a NON-MIXER TYPE and is attractively finished CREAM. Price £11/19/6 (plus 7/6 carr. and insurance).

HIGH-FIDELITY PICK-UP Incorporating the famous CONNOISSEUR Light Weight Moving Iron Head and including the Connoisseur matching Transformer (plus 1/- carriage weight) Price 39/6

THE LATEST "ACOS" MODEL GP 20 H.G. PICK-UP incorporating the new "High G" Crystal Head. Price £3/8/8

DUAL-CHANNEL PRE-AMPLIFIER and TONE CONTROL UNIT

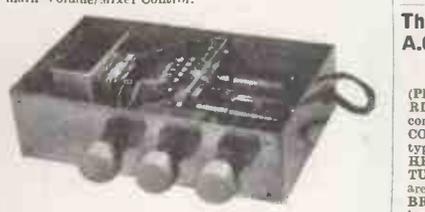This comprehensive PRE-AMPLIFIER and TONE CONTROL UNIT provides a full control of bass and treble in conjunction with a main Volume/Mixer Control.



The unit can be used with any amplifier and with any pick-up, the range of frequency control provided by the unit affording ample compensation for all types of pick-up and all natures of recordings, i.e., English, American and long-playing, without recourse to pick-up correction. The extreme flexibility of the bass and treble controls is such that the level of bass and treble can be set to suit any conditions irrespective of the volume output of the amplifier. Response characteristics are given in 12-watt amplifier advt. The unit measures only 7in. x 4in. x 2in., including self-contained power supply and can be accommodated either on or away from the main amplifier, i.e., on the front panel of a cabinet or any other position. Price, including drilled chassis, valves (6SN7 and 6J5), £3/16/9. Complete assembly data are available separately for 1/-. Completely assembled and ready for use, £5/5/-.

The GARRARD Model RC75A

A 3-speed non-mixer AUTOCHANGE UNIT complete with the TWIN STYLUS CRYSTAL PICK-UP. Separate sapphires for L.P. and 78 R.P.M. moved into position by a switch on the pick-up head. Price £13/15/0 (plus 7/6 carr. and Ins.).



The COLLARO Model A.C. 514 Record Player £3/19/6

(Plus 5/- carr. and ins.) RIM DRIVE 78 r.p.m. complete with the COLLARO Plug in type MAGNETIC HEAD and 10 inch TURNABLE. These are COMPLETE BRAND NEW UNITS for A.C. Mains 200-250 Volts.

A Famous Manufacturer's SHADED POLE RIM DRIVE 10/6 GRAM MOTORS

(Plus 1/- carr. and Ins.) Clockwise rotations and incorporates a Mains Adjustment Panel. Could also be used as Recording Take Up or Rewind Motor.

The "REGENT" HALF-WAVE H.T. RECTIFIERS

Crystal Hand Microphone 25/6 Plus 1/- carr & Ins. Complete with screened lead List Price £2/2/-



SELENIUM RECTIFIERS

6 or 12 Volt 1 amp. rating 7/6
6 or 12 Volt 2½ amp rating 12/6
6 or 12 Volt 4 amp. rating 17/6
6 or 12 Volt 6 amp rating £17/9

!! The TRUVOX TAPE UNIT !!

We can now offer this very successful Unit ex stock. Price (Plus 5/- carr. and Ins.)... £23/2/0 A really good-class TAPE AMPLIFIER is also available. Price (Plus 5/- carr. and ins.). 16/10/0 The combination of these two Units provides a really first-class complete TAPE RECORDER. Send S.A.E. for complete details.

When submitting orders, please include post and packing


STERN RADIO Ltd.

109 & 115, FLEET STREET, E.C.4

Tel.: CENTRAL 5812-3-4

Prices slashed at Clydesdale

TI154B TRANSMITTER UNITS

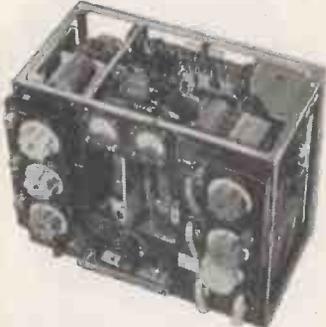

Medium/high powered for C.W.-M.C.W. R/T, 3 ranges 10-5.5 Mc/s. 5.5-3 Mc/s. 500-200 kc/s. Complete with 4 valves, etc., in metal case 14in. x 16 1/2in. x 8 1/2in. External Power Supply required. ASK FOR **39/6** each CARRIAGE X/E5A **7/6 EXTRA**
 ALSO AVAILABLE
 TI154B as above, but less valves. ASK FOR **15/-** each CARRIAGE X/E5B **7/6 EXTRA**

MONITOR CRYSTAL TYPE 2, 10T/11390
 As used with the R1116 or R1082. Less valves and Crystals, but otherwise complete, dim. 7 1/2in. x 5 1/2in. x 3 1/2in. Plastic constructions, in transit case. ASK FOR **5/-** each POST X/H872. **1/- EXTRA**

MAGNETIC MARCHING COMPASS MK. I
 Small hand compass. Can be used day or night. Complete with instructions, in plastic case, size 3in. x 2 1/2in. x 1 1/2in. ASK FOR **12/6** each POST X/H406. **3/6 EXTRA**

INDICATOR UNIT TYPE 6
 In original wood case. Containing VCR.97 tube and valves, etc., in metal case 18in. x 8 1/2in. x 7 1/2in. New condition. ASK FOR **79/6** each CARRIAGE X/H524. **3/6 EXTRA**

MIDGET MOTOR, Ref. 5U/2705
 Input 24 v. D.C. 2 a., R.P.M. 2,800 drive pulley each end. Overall dim. 2in. x 2in. x 5 1/2in. ASK FOR **7/6** each POST X/H98. **3/6 EXTRA**

MALLORY SYNCHRONOUS VIBRAPACK
 Input: 12 v. D.C. Output approx. 120 v. D.C. 70 mA. unsmoothed, dim. 5 1/2in. x 2 1/2in. x 5in. Unused, but soiled and vibrator contacts stuck due to long storage. ASK FOR **10/-** each POST X/E954. **3/6 EXTRA**

MICROPHONE REF. 10A/14381
 (Flying Helmet Type.) Electro Magnetic 500 ohms with switch, lead and 2 way sockets. ASK FOR **3/11** each POST X/E16. **6d. EXTRA**

26 WATT OUTPUT TRANSFORMER
 Parmeko type AF5084/1A. (Mfg. Surplus). Primary: 6,600 ohms. C.T. Sec's, 3.5, 5, 7.5 or 10 ohms. Dim. 3 1/2in. x 2 1/2in. x 3in. Fully shrouded Weight 3 lbs. ASK FOR **19/6** each POST X/H565. **3/6 EXTRA**

CABLE
 2 core Metal braided X/H541, 4d. per yard, post 3d. extra.

HALF MILE REELS (880 YARDS)
 23 SWG P.V.C. covered signal corps wire, X/H855, 25/- per reel.

CERAMIC WAFER ROTARY WAVE-CHANGE SWITCH
 3 bank each, single pole, 5 ways. Overall length 8in. x 2 1/2in. wide. ASK FOR **3/-** each POST X/E120. **3d. EXTRA**

VALVEHOLDERS

Ceramic B9G (EF50), British Octal (SP61), Int. Octal (5Z4), 7UX (RK34). 1/- each, post 1 1/2d. extra. Dozen lots 10/6. Moulded, British Octal, B7G (6AM6), B8A (EAF42), B8G (ILN5). Int. Octal, B9A (12AU7), 7UX (6A7). 9d. each, post 1 1/2d. extra. Dozen lots 7/6. Paxolin, B9G (EF50), B9, B7G, B8G. 6d. each, post 1 1/2d. extra. Dozen lots 5/-.

CONDENSERS

Mansbridge Metal cased type, dim. 5 1/2in. x 4in. x 1 1/2in. XRN. Capacity 6 mfd. wkg. vtg. 1,000 volts. ASK FOR **5/6** each POST X/H359. **9d. EXTRA**
 Electrolytic Tubular. Aluminium cased, wxd. cardboard cover. U.S.A. made. Capacity 32 mfd. wkg. vtg. 450 v. D.C. Dia. 2in., length 4 1/2in. with mtg. plate. ASK FOR **1/9** each POST X/H852. **9d. EXTRA**

Or 3 Condensers (32/450) as above, in original sealed carton. ASK FOR **4/6** each POST X/H852X. **9d. EXTRA**

Electrolytic Tubular. Aluminium case, clip mtg. Capacity 8-16 mfd. wkg. vtg. 450 v. D.C. Dia. 1 1/2in. x 2 1/2in. Mfg. surplus. ASK FOR **3/-** each POST X/H918. **3d. EXTRA**
 Clip 4d. extra.

Electrolytic Tubular. Aluminium case. Capacity 8 mfd. wkg. vtg. 450 v. D.C. Dia. 1in. x 2 1/2in. Tag ends. Mfg. surplus. ASK FOR **1/9** each POST X/H598. **3d. EXTRA**

Ceramic Tubular. Mfg. Surplus. Capacity PF 1,100, 1,000, 504, 200, 180, 150, 120, 82, 68, 56, 39, 33, 15, 12, 8.2, 6.8. Price 6d. each, post 1 1/2d. extra. Dozen lots 5/- post paid.

Silver Mica. (w) waxed. (p) pitched. Mfg. Surplus. Capacity PF 5,000 (w), 4,550 (w), 4,000 (w), 432 (w), 432 (p), 350 (p), 135 (p), 47 (w), 20 (w), 10 (w), 8 (w), 5 (w). Price 6d. each, post 1 1/2d. extra. Dozen lots 5/- post paid. Tubular Paper (pitch covered) 400 v. D.C. wkg. Mfg. surplus. Capacity mfd. 0.068, 0.039, 0.022, 0.018, 0.015, 0.0082, 0.00668, 0.0056, 0.0039, 0.0027, 0.0022, 0.0018, 0.00082, 0.00068. Price 4d. each, post 1 1/2d. extra. Dozen lots 3/6 post paid.

Tubular Paper (pitch covered) 600 v. D.C. wkg. Capacity mfd. 0.012, 0.0082, 0.0033, 0.00082. Price 6d. each, post 1 1/2d. extra. Dozen lots 5/- post paid.

VOLUME CONTROLS. Potentiometers, Carbon Track. 1/2 meg. (500,000 ohms.), long spindle fitted DP/ST Switch and mtg. plate. ASK FOR **3/11** each POST X/E189. **3d. EXTRA**

With DP Switch 3/4in. Spindle, 100,000 ohms. Ref. 3U/100M. PAC X/H415, 500,000 ohms., ref. 3U/500M PAC X/H655. Price 3/9 each, post 3d. extra.

With SP Switch 3in. spindle, 2 meg. ohm. ref. 187-Z-2169. ASK FOR **3/3** each POST X/H427. **3d. EXTRA**

Less Switch. 3in. spindle 1/2 meg. (250,000 ohms). ASK FOR **2/3** each POST X/H705. **3d. EXTRA**

Preset Types, less switch. (M) Metal type, (T) Tropicalised. 10,000 ohms. Ref. 10W/8655, X/H434 (T), 25,000 ohms. Ref. 10W/9230 X/H433 (T) 100,000 ohms. Ref. 10W/7457 X/H414 (M) 200,000 ohms. X/H956 (M) 250,000 ohms. Ref. 10W/9188 X/H431 (T). Price 1/6 each, post 3d. extra.

Short Spindle Types, less switch. 100,000 ohms. Ref. 10W/8741 1/2in. sp. X/E924 (T). 500,000 ohms. Ref. 10W/8777 1/2in. sp. X/H699 (T). 500,000 ohms. Ref. 10W/7856 1/2in. sp. X/H700 (T). 1 meg. ohm. Ref. ZA.2809. 1/2in. sp. X/H733 (M). Price 1/9 each, post 3d. extra.

Midget Types, less switch. 500 ohms. Ref. 10W/8990. 1/2in. sp. X/H428. 25,000 ohms. Ref. 10W/17403, Preset, X/H657. 100,000 ohms. 1 1/2in. sp. X/E928. 250,000 ohms. Linear. 1 1/2in. sp. X/H896. 500,000 ohms. Log. 1 1/2in. sp. X/H895. Price 2/3 each, post 3d. extra.

W.W. POTENTIOMETERS

2 watt by Clarostat U.S.A. 10,000 ohms. Ref. CMC-63532 Preset. ASK FOR **2/6** each POST X/H957. **3d. EXTRA**

3 Watt Type. 500 ohms. Ref. DB1307/12. 1/2in. sp. X/H661. 1,000 ohms. Ref. 10W/8924. Preset. X/E936. 2,000 ohms. Ref. 10W/8843. 1/2in. sp. X/H904. 5,000 ohms. Ref. 10W/7796. 1/2in. sp. X/H423. 5,000 ohms. Ref. 10C/8925. 1/2in. sp. X/H663. 10,000 ohms. Ref. 10C/8926. Preset, X/E568. 20,000 ohms. Ref. CLR4037/175. 1in. sp. X/H421. 25,000 ohms. Ref. 10C/8927. Preset, X/H665. 25,000 ohms. Ref. 10C/538. 1/2in. sp. X/H422. 25,000 ohms. Ref. 10W/8573. 1/2in. sp. X/H522A. 50,000 ohms. Ref. CLR4001/85. Preset, X/E943. Price 3/- each, post 3d. extra.

5 watt, 2 hole fixing type. 270 ohms. Ref. CLR/6003/12. W9259. 1in. Spindle. ASK FOR **2/-** each POST X/H905. **3d. EXTRA**

5 watt type. 400 ohms. Ref. 10W/8534. 1/2in. sp. X/H571. 5,000 ohms. Ref. 10H/6524. 1/2in. sp. X/H666. 2,000 ohms. 1/2in. sp. X/H425. 25,000 ohms. Ref. 10W/8572. 1/2in. sp. X/H667. Price 3/- each, post 3d. extra.

10 watt Toroidal Type. 200 ohms. Ref. W1363, wound on porcelain. ASK FOR **3/-** each POST X/E172. **6d. EXTRA**

FIXED RESISTORS, Wire Wound. 25 watt, 26 ohms. Vitreous finish, wire ends. Ref. 10W/15688. Type AW3192. 3/- each, post 3d. extra. Dozen lots 30/- post paid.

18 watt, 2,000 ohms. Vitreous finish Contact ends. 2/- each, post 3d. extra. Dozen lots 19/6 post paid.

15 watt 50 ohms. Vitreous finish. Tag ends. 2/- each, post 3d. extra. Dozen lots 19/6 post paid.

10 watt Vitreous finish Wire ends. Resistances, ohms: 6,800, 270, 25, 10. 2/6 each, post 3d. extra. Dozen lots 25/- post paid.

5 watts. Cemented (C), Enamelled (E), Resistance, ohms: 1,200 (E), 220 (C). 2/- each, post 3d. extra. Dozen lots 21/- post paid.

4 watt 100 ohms. Vitreous finish Wire ends. 2/- each, post 3d. extra. Dozen lots 19/6 post paid.

3 watts Enamelled Wire Ends. Resistance, ohms: 2,200, 1,800, 1,500, 1,000, 150, 33, 18. 9d. each, post 3d. extra. Dozen lots 7/6 post paid.

1.5 watts, Enamelled Wire Ends. Resistance, ohms 1,500, 1,200, 1,000, 200, 1.7. 4d. each, post 1 1/2d. extra. Dozen lots 3/6 post paid.

Resistance type 849, 10W/767. Heavy Duty type W.W. or bakelite mtg. Panel 5 1/2in. x 2 1/2in. x 3/16in. 0.3 ohms, tapped every 0.05 ohms. ASK FOR **3/-** each POST X/H686. **6d. EXTRA**
 Dozen lots 30/- post paid.

RESISTANCE TYPE 243
 10W/9305 W.W. on mica panel 43 x 18-mm. with fixing holders. 1.3 ohms. ASK FOR **3/-** each POST X/H687. **6d. EXTRA**
 Dozen Lots 30/- post paid.

RESISTANCE ELEMENT TYPE 4773
 10W/16125. Heavy Duty. 1 ohm. element NO former or mtg. ASK FOR **3/-** each POST X/H688. **6d. EXTRA**
 Dozen lots 30/- post paid.

RESISTANCE TYPE 150 10W/8524
 W.W. bobbin type on former 10.5 cm. long, 18 mm. dia. with fixg. holders. 40,000 ohms. tapped every 5,000 ohms. ASK FOR **3/6** each POST X/H689. **6d. EXTRA**
 Dozen lots 32/6 post paid.

Order direct from:-

CLYDESDALE SUPPLY CO LTD. 2, BRIDGE STREET, GLASGOW. C.5

Phone: South 2706/9 Branches in Scotland, England and Northern Ireland.

CAR RADIO SPECIAL—Partly assembled car radios.



Small size case 12 x 4 x 6in. Will fit most cars. For either 6 or 12 volts, depending on vibrator. Chassis supplied with 5 octal valve holders, medium wave aerial and oscillator coils, output transformer, volume control, sundry resistances and condensers, dial and knobs. Case finished in brown crackle. Dial calibrated 150-550 metres. 5 valves to suit. One each, either GT or metal: 6SA7, 6R7, 6V6, 6K7, OZ4.

LASKY'S PRICE £5/5/-. Carriage 5/- extra.
Or less valves, 69/6. Carriage 5/- extra.
Other chassis in various conditions of completion are available for personal callers only.
CIRCUIT for 5 valve car radio, using above chassis.
PRICE 1/6.

CONDENSERS. Electrolytics.

Cans		Tubular	
16 mfd. 500 v.w.	3/8	1 mfd. 200 v.w.	1/-
20 mfd. 500 v.w.	3/6	1 mfd. 250 v.w.	9d.
24 mfd. 450 v.w.	3/11	2 mfd. 150 v.w.	1/-
32 mfd. 500 v.w.	5/11	2 mfd. 350 v.w.	1/6
60 mfd. 350 v.w.	2/11	4 mfd. 350 v.w.	1/3
64 mfd. 450 v.w.	3/11	4 mfd. 450 v.w.	1/8
8+8 mfd. 450 v.w.	3/11	8 mfd. 150 v.w.	1/6
8+16 mfd. 450 v.w.	3/11	8 mfd. 350 v.w.	1/3
8+32 mfd. 475 v.w.	3/11	8 mfd. 450 v.w.	1/3
16+8 mfd. 500 v.w.	4/6	15 mfd. 200 v.w.	2/-
16+16 mfd. 500 v.w.	4/6	16 mfd. 350 v.w.	2/3
16+32 mfd. 450 v.w.	4/9	16 mfd. 450 v.w.	2/9
20+20 mfd. 275 v.w.	2/-	16 mfd. 500 v.w.	3/3
32+32 mfd. 500 v.w.	4/11	32 mfd. 350 v.w.	3/3
32+32 mfd. 350 v.w.	3/11	32 mfd. 450 v.w.	4/9
60+100 mfd. 350 v.w.	7/6	50 mfd. 350 v.w.	4/6
250 mfd. 350 v.w.	4/11	250 mfd. 12 v.w.	2/-
8000 mfd. 3 v.w.	6/11	8+8 mfd. 350 v.w.	3/-
		8+8 mfd. 450 v.w.	3/11
		12+12 mfd. 350 v.w.	2/6

MANY OTHER TYPES IN STOCK

SPECIAL T.V. CONDENSERS

32+100 mfd. 450 v.w., 7/6 .04 mfd. 12.5 Kv. 7/6

Bias		High Voltage	
10 mfd. 25 v.w.	1/3	.1 mfd. 10 Kv.	12/6
12 mfd. 50 v.w.	1/3	.25 mfd. 2.5 Kv.	5/6
25 mfd. 50 v.w.	1/6	.1+1 mfd. 3.5 Kv.	5/11
25 mfd. 50 v.w.	1/6		
50 mfd. 12 v.w.	1/3		
50 mfd. 25 v.w.	1/6		
50 mfd. 50 v.w.	1/9		
75 mfd. 12 v.w.	1/-		
100 mfd. 25 v.w.	2/-		
100 mfd. 50 v.w.	2/6		

Tubular Waxed
500 v.w., .01, .02, .05, .001, .002, .005, etc. From 6d. each, 5/- doz. .1 mfd. 9d. each.

Miniature Mica
100, 200, 300, 500 PF., 5d. each, 4/- doz.

T.C.C. VISCONOL HIGH VOLTAGE CONDENSERS

(Cathodray)
.001 mfd. 12.5 Kv. ... 7/6
.001 mfd. 15 Kv. ... 10/-
.001 mfd. 25 Kv. ... 18/-
.0005 mfd. 25 Kv. ... 18/-
.0005 mfd. 12.5 Kv. ... 10/-
Plastic case, single bolt fixing. Other h.v. types.
.1 mfd. 7 kv. 15/-
.04 mfd. 12.5 kv. 7/6

We have a large range of ceramic tube condensers now available.

12 VOLT D.C. MOTOR GENERATORS

Output 300 volts at 150 mA. D.C. 7,500 r.p.m. Size: 2 1/2 in. diam. 6 in. long. **LASKY'S PRICE 17/6**

I.F. TRANSFORMERS

465 Kc/s Iron dust cores in cans, midget type. Size 1 1/2 in. x 1 in. x 2 1/2 in. By Plessey. Price 8/6 per pair. **WEARITE TYPE 550. 445-520 Kc/s. 8/6 per pair. WEARITE TYPE 500. 450-470 Kc/s. 8/6 per pair.**

SOLON SOLDERING IRONS

220-250 volts
Latest model instrument iron 19/8
Standard model 19/-

PRESS BUTTON COIL UNITS

5 Preset stations—3 M.W. and 2 L.W. For use in superhet circuit, with 445-520 Kc/s. I.F. Size: 3 1/2 in. x 5 1/2 in. 2 1/2 in. deep. By famous manufacturer, complete with circuit and knobs. **LASKY'S PRICE 21/-.** Postage 2/6.

R.1132.A RECEIVERS

Supplied in maker's original wood transit case. Frequency coverage 100-124 Mc/s. 11 valves: 1 VR65, 1 VR66, 4 VR53, 2 VR54, 1 6J5, 1 VS70, 1 VR57. Large tuning scale with slow motion drive. 0-5 mA. tuning meter. R.F. and L.F. gain controls, jack sockets for line and 'phone. Totally enclosed in metal case, grey enamelled with plated handles. Size: 18 x 10 x 1 1/2 in. Supplied with all valves, also circuit and calibration chart.

GRADE 1. Brand New, 79/6. **GRADE 2.** Soiled, 49/6. **GRADE 3.** Secondhand, 39/6. Carriage 10/- per unit extra.



In metal case, black crackle finish, 12 x 6 x 8 1/2 inches. Without handles. This unit is ideal for breaking down and rebuilding as another type of instrument.

LASKY'S PRICE 45/-
Carriage 3/6 extra.

HUGE PURCHASE OF STAINLESS STEEL RECORDING WIRE. STANDARD REELS.

By B. & H.

15 mins.	7/6
30 mins.	12/6
60 mins.	25/-

GARRARD RECORD PLAYERS

For 6 and 12 v. operation, complete with magnetic pick-up and volume control. In metal cabinet size: 17 in. x 14 in. x 1 1/2 in. Very limited quantity.

LASKY'S PRICE £5.19.6
Carriage 10/- extra.

R.1155 RECEIVERS

BRAND NEW AERIAL TESTED BEFORE DESPATCH

These well-known ex-Air Ministry Receivers need no further introduction. Supplied complete with 10 valves, and full circuit data.

LASKY'S PRICE £11.19.6
USED MODELS £7.19.6

A Few Only. Model R1155.N Covering the shipping band of 1.5-3.0 Mc/s. Price £17.

Carriage 12/6 per unit extra, including 10/- returnable on packing case. 10s. 0d. rebate will be given on power packs for the R.1155 when purchased with the receiver.



Fully Assembled Power Pack and Output Stage, for R1155 Receiver. For use on 200-250 volts A.C. mains. **LASKY'S PRICE 79/6**
Carriage 5/- extra.

GRAM MOTORS Shaded Pole



Rim drive, synchronous. For 200-250v. 50 c.p.s. Many uses. **LASKY'S PRICE 9/6**

METAL RECTIFIERS

6 and 12 volt F.W. Bridge.

2a.	9/-
3a.	9/11
4a.	12/-
6a.	17/6

HEARING AIDS

By well-known Manufacturer. In metal case, size: 2 1/2 in. x 4 1/2 in. x 1 in. Complete with batteries and 3 sub-miniature valves, earpiece and cord. Only two controls: volume and on/off. Fitted with internal crystal microphone.

Suitable for reconstruction into midget radio receiver.

MADE TO SELL FOR 22 GNS. LASKY'S PRICE 99/6
Postage 3/6 extra.

Ready for use. Perfect working order. Slightly soiled, but new and unused. A few hearing aids available, less earpiece, cord and batteries. **PRICE 50/-.** Carriage 2/6 extra.

TANNOY PRESSURE UNITS

10 watts. 7.5 ohms impedance. Last few only. **PRICE 59/6**
Carriage 4/6 extra.

TWO-GANG TUNING CONDENSERS .0005MFD.

No. 1. Miniature. With trimmers. Size: 2 1/2 in. x 1 1/2 in. x 1 1/2 in. spindle. **LASKY'S PRICE 6/6**
No. 2. Midget. With trimmers. Size: 2 1/2 in. x 1 1/2 in. x 1 1/2 in. spindle. **LASKY'S PRICE 7/6**
No. 3. Midget. Less trimmers. Size: 2 in. x 1 1/2 in. x 1 1/2 in. spindle. **LASKY'S PRICE 6/6**
No. 4. Standard type. Size: 2 1/2 in. x 2 1/2 in. x 1 1/2 in. spindle. **LASKY'S PRICE 6/6**

THREE GANG. .0005mfd. Less trimmers. Size: 3 1/2 x 2 1/2 in. LASKY'S PRICE 6/6.

BAFFLE RADIO CABINETS



Pleasing design, complete with knobs, drilled chassis, dial, drum drive and back. Finish in satin mahogany veneer, natural colour polish. Outside dimensions: 17 1/2 in. wide, 11 1/2 in. high, 5 in. deep.

Circuit and component list for valve T.R.F. set available.

LASKY'S PRICE

36/6

Carriage 2/- extra.

A LASKY'S RADIO ADVERTISEMENT SEE OVER.



LINE TRANSFORMERS FOR "ETRONIC" T.V. RECEIVERS

No. 1. For models 1536 and 1637. Complete with EY51 rectifier, 39/6.
No. 2. 7Kv. type, 35/-.

POT/METERS. All values. Wire Wound from 3/6. Depending on wattage and length of spindle. Carbon. Less switch 2/11 each. With s.p. switch 4/3 each. With d.p. switch 5/6 each.

VCR97 C.R. TUBES, new unused. Carriage 5/-.

Screen Enlarger for VCR97. Filter or clear, 17/6. Postage 2/6.

C.R.T. Neck Protectors, 2/6.

10 K.V. METROSIL E.H.T. REGULATORS. By Metrovick. Pencil type, 5/- each.

S.T.C. SENTERCELL RECTIFIERS

RM.1.. 3/10	K3/40, 3.2 kV. 6/-
	K3/45, 3.6 kV. 8/2
RM.2.. 4/3	K3/50, 4.0 kV. 8/8
	K3/100, 8.0 kV. 14/8
RM.3.. 5/-	
RM.4.. 18/-	K3/160, 12.8 kV. 21/6

6- AND 12-VOLT VIBRATORS

4-Pin type. Soiled. S/H.	4/6
New	9/6
W/W	12/6

State voltage required.

8-PIN JONES SOCKETS. For 1155 Receiver, etc., 1/9 each.

WESTINGHOUSE RECTIFIERS

250 v. R.M.S.	
14A976. 80 m/a.	8/6
14A86. 200 m/a.	20/4
14A100. 270 v. R.M.S.	
200 m/a.	21/6

TRIPLEX DARK SCREEN FILTERS

14 x 12 1/2 x 1/8 in.	7/6
15 1/2 x 13 1/2 x 1/8 in.	9/6

Postage and packing 5/- per piece extra. (This charge is necessary owing to extra packing required.)

DARK SCREEN PERSEPEX FILTERS

18in. x 14in.	25/-
14in. x 12in.	19/6
13in. x 11in.	14/11

PERSPEX. 13in. x 10in. x 1/8 in. Neutral shade slightly marked, 4/11 per piece.

BRANDENBURG R.F. E.H.T. UNITS

6-9 Kv.	£5 19 6
13-16 Kv	£8 19 6

TEST PRODS

Fully fused, with retractable points, 4/11 per pair (1 red, 1 black).

TOGGLE SWITCHES. BULGIN.

S.P.S.T.	1/6
D.P.S.T.	2/6
D.P. Change over	3/6

SPECIAL C.R.T. OFFER

Brand new and unused 12in. ion trap cathode ray tubes. 6.3 volt heater, 7-9 Kv. E.H.T. 35 mm. neck. Black and white picture. By famous manufacturer.

PERFECT £12/19/6
Carriage and insurance 15/- per tube extra.

MANUFACTURERS' SURPLUS T.V. COMPONENTS

Wide Angle Scanning Coils. Low imp. line and frame	19/6
Scanning Coils. 35 mm. Low imp. line and frame	12/6
Frame output transformer. Standard	10/6
Focus Coil. 35 mm. electro magnetic	12/6
Line or Frame B.O. transformer. Auto	4/6
Wide Angle Frame B.O. trans.	10/6
P.M. Focus Magnets. With vernier. 35 mm.	
Tetrode	15/-
Triode	17/6
Wide Angle P.M. Focus Unit. For all 38 mm. tubes. With vernier and picture shift, Ferroxdure	25/-

PLESSEY

Scan soils per pair	25/-
Width Control	6/6
P.M. Focus magnet	12/6

Co-Axial Cable. 70-80 ohms impedance. Single core, 8/- doz. yards. Twin core, 12/- doz. yards. Twin feeder, 6/- doz. yards. Co-Axial Connectors. For standard 1/4 in. cable, 1/6.

WX6. WESTINGHOUSE MINIATURE RECTIFIERS

Wire ends. 1/6 each.

C.R.T. MASKS Brand New LATEST ASPECT RATIO

9in.	7/-
10in.	7/6
12in.	15/-
12in. Flat Face	15/-
12in. Old ratio	9/6
14in. Rectangular	12/6
15in. Cream rubber	17/6
15in. With fitted safety glass	22/6
16in. Plastic, white	12/6
16in. Double D	31/6
17in. Rectangular	21/-

PLASTIC ESCUTCHEON SAFETY MASKS

Incorporating dark screen filter.

12in. Round Face	12/6
12in. Double D.	
Round Face	15/-
16in. for metal tubes	25/-

SOILED. NEW ASPECT RATIO MASKS

9in.	5/-
12in.	7/6
12in. with fitted armour plate glass, cream	11/6
12in. do. Black	8/6

ARMOUR PLATE GLASS

16in. Actual size 17 1/2 x 15 1/2 x 1/8 inch	7/11
15in. Actual size 16 1/2 in. x 13 in. x 1/8 in.	6/11
12in. Actual size 13 in. x 10 1/2 in. x 1/8 in.	4/-
9in. Actual size 9 in. x 8 in. x 1/8 in.	3/-

DE LUXE T.V. CABINETS

Our new 12 inch model. Mark II

This cabinet is now supplied complete with mask, glass, castors, shelf, bearers, c.r.t. neck end protector, back, speaker fret and baffle board. Finished in beautiful figured medium, light or dark walnut veneer, with high polish. Suitable for most home constructor T.V. receivers, including the "Viewmaster," "Practical Television," "Tele King," "Magnivision," "Wireless World," etc. Can be supplied with cut-out for 16in. c.r. tube at no extra cost.



An allowance of 4s. 6d. will be made if the mask is not required. Mask and glass extra when cabinet is ordered with cut out for 14, 16, or 17in. C.R.T.'s.

Inside Dimensions: Depth 16 1/2 in.; width 17 1/2 in.; height 28 in. Overall height 32 in. and width 18 1/2 in.

WHY NOT CONVERT YOUR TABLE RECEIVER TO A CONSOLE MODEL.

Adaptor frames for fitting 9in. or 10in. c.r. tubes can be supplied if required.

LASKY'S PRICE Carriage 12/6 extra. **£8.10.0**

THE VIEW MASTER

Construction envelope 7/6. POST FREE
Wide Angle Conversion 3/6. POST FREE

All components in stock. Write for price list.

R.F. E.H.T. OSC. COILS
For use with 6V6 Heater winding for EY51. Circuit and full data supplied. 6-10 Kv. PRICE 19/6
6-18 kv. PRICE 25/-

COLLARO 3-SPEED AUTOMATIC RECORD CHANGERS

MODEL 3RC/521.

Brand new and unused in maker's original carton.

Pleasing cream or fawn finish. Complete with hi-fidelity studio crystal turnover head. Type GP. 29.



LASKY'S PRICE Carriage Free. **£9.19.6**

THE "UNIVERSAL" LARGE SCREEN AC/DC TELEVISOR

By A. S. Torrance, A.M.I.P.R.E., A.M.T.S.

A 28-page booklet giving full instructions for building a large 17-inch screen televisior.

- ★ A.C. and D.C. mains
- ★ P.M. focussing.
- ★ Mullard valves and c.r. tube.
- ★ 5-channel superhet.
- ★ Table model.
- ★ Convertible into radiogram console.
- ★ Incorporates all latest developments.

3d. POST FREE.

TYPE AT/9 T.V. MAINS AUTO-TRANSFORMER

200, 220, 250 and 375 volt tappings. 250 mA. Also 5 v. 3 a.; 6.3 v. 7 a.; and 6.3 v. 3 a. secondaries. Price 25/-.

ION TRAPS All types. Price 3/-.

INTERCOM UNITS

4-station operation. For use on A.C./D.C. mains 200-250 volts. Supplied complete, with 3 new valves, ready for immediate installation. Fitted in attractive plastic cabinet. Suitable for use as baby alarm. **MASTER UNIT £5/19/6.** Carr. 5/- extra.

Extension Units. Price 21/- each complete. Carriage 2/- each extra.

LASKY'S LINE TRANSFORMER

RF/EHT for line flyback. 6-8Kv, with EY51 heater winding. Suitable for home construction T/V 19/6 each.

POSTAGE STAMP TRIMMERS

Paxolin. Up to 100pF. 6d. each. 5/- per doz. Ceramic. Up to 100pF. 9d. each. 7/6 per doz.

Duodecal (B12A) bases. VCR139 c.r.t. bases. 1/- each. 10/6 dozen.

ELAC DUOMAG FOCALISERS. For wide angle c.r. tubes. Low, medium and high flux, 37/6 each.

THE TELE-KING

A practical 5-channel

SUPERHET TELEVISION RECEIVER

Using the new 16 and 17 inch cathode ray tubes and wide angle components for the home constructor.

Complete instructions, wiring diagrams and 32-page descriptive booklet.

6/- POST FREE

ALL COMPONENTS IN STOCK
WRITE FOR LIST

ALLEN WIDE ANGLE COMPONENTS

D.C. 300 latest type Ferroxcube Coils 39/6
GL. 16 Coil 7/6
GL. 18 Coil 7/6
Focus Coil 31/-
FO.305 trans. 21/-
Frame B.O. transformer 15/-
Line EHT. transformer 40/-

CHASSIS

Power pack Sound-vision and Scan chassis.
PRICE 11/- each. All other metal work available from stock.
CONDENSERS
All condensers as specified. Manufacturers' surplus. £3/16/-.
COILS 13 all exactly as specified. Price 44/6.

RESISTANCES. 72 Resistances, all exactly as specified, 18/-.

CABINET

As illustrated here. £8/10/-.
Carriage 12/6 extra.

WIDE ANGLE CATHODE RAY TUBES

14in. MW36-22 £19 9 3
14in. C14B £20 10 1
16in. MW41-1 £22 4 10
16in. T901 £22 4 10
17in. MW43-64 £23 12 8
17in. C17BM £24 13 0
Carriage and insurance extra.

OUTPUT TRANSFORMERS

40 mA Multi ratio 4/11
80 mA Multi ratio 14/11
80 mA Pentode 12/6
60 mA Plessey, 6,000 ohms 5/11
Standard Pentode 4/11
Pentode 3/6
Midget Pentode 3/6
Miniature Pentode, 3S4, 1S4 3/6
PX4 Intervalve 8/6
5:1 Intervalve 5/11

MUIRHEAD SLOW MOTION DRIVES

Standard size 3/11 per pair.

P.M. LOUDSPEAKERS

All with 8 ohm speech coil
2 1/2in. 15/- din. 9/6 8in. 15/-
3in. 14/6 5in. 14/6 8in. 15/-
10in. 17/6

NEW AVAILABLE 12-inch Goodmans heavy duty speaker. Capacity 15 watts, 15 ohms speech coil impedance.

LASKY'S PRICE £5/19/6.

Car. 3/6 ex. All loudsprs. offered are first grade and of highest quality construction. Many other types in stock. Send us your reqts. Special offer. 12in. Truvox, 3 ohms. **LASKY'S PRICE** 49/6.

Alexandra Palace,
Sutton Coldfield,
Holme Moss,
Wenvoe,
Pontop Pike,
Belfast,
Kirk o'Shotts.



NOTICE TO ALL PURCHASERS OF THE ENGLISH ELECTRIC 16 inch C.R.T. TYPE T.901

The first and only reconditioning service. By English Electric. A reconditioned 16in. metal tube costs £12 and carries maker's full guarantee. Write for further details.

MAINS TRANSFORMERS

All 200-250 v. 50 c.p.s. primary. Finest quality, fully guaranteed. M.B.A./3 350-0-350 v. 80 mA., 6.3 v. 4 a., 5 v. 2 a. Both filaments tapped at 4 volts. An ideal replacement trans. Price 18/-.

MBA/6. 325-0-325 v. 100 mA. 6.3 v. 3 a., 5 v. 2 a. With mains tapping board. Price 22/6.

MBA/7. 250-0-250 v. 80 mA., 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts. Price 18/-.

MBA/8. 235-0-235 v. 60 mA., and 6.3 v. 3 a. Price 12/6.

AT/3. Auto transformer. 0-10-120, 200-230-240 volts 100 watt. Price 17/6.

SPEAKER FRET

Expanded Metal.	Silver Finish.	Price
12in. x 12in.	3/11
12in. x 18in.	5/11
Plastic, White, 12in. x 5in.	2/-
Wire, Bronze, 11in. x 8in.	2/-

SMOOTHING CHOKES

20 mA. 40 H	3/6
40 mA. 8 H	3/6
40 mA. 10 H	4/3
100 mA. 10-20 H	7/3
250 mA. 10 H	18/6

J/RA/3 AMPLIFIER

6 VALVES 12-15WATTS OUTPUT
Originally made for talkie film projectors. In carrying case. Chassis size: 14 1/2 x 10 x 4in. For use on 100-250 volts A.C. mains. Grey crackle finish. Fitted with volume and tone controls. Resistance capacity coupled circuit. Output 2 KT66 in push-pull.



High quality components used throughout. In black rexine covered wood case, size 15 1/2 x 13 1/2 x 9 1/2 in. giving plenty of room for speaker, etc. Circuit diagram available. Complete with 6 valves, fully assembled and wired.

LASKY'S £9.19.6 COMPLETE
Carriage 15/- e xtra.

R.F. OSC. COIL KITS

Consisting of R.F. oscillator E.H.T. coil with EY51 heater winding, EY51 rectifier, 6V6 valve and base. All necessary condensers and resistances. Including full circuit and data.

6-9Kv. **LASKY'S PRICE** 47/6d.
9-15Kv. **LASKY'S PRICE** 53/6d.

FILAMENT TRANSFORMERS

6.3 v. 1.5 a., 5/9. 6.3 v. 3 a., 9/6.
6.3 v. tapped at 4 v. 2 amps., 7/9.
Special Transformer. 2 amps. with the following tappings: 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volts. Price 17/6.


COIL PACKS

Medium and 2 short wave bands. Price 16/-.
Long, medium and short wave bands, 29/6.

RF25 UNITS. New with valves, 19/11.
Carriage 2/6.

LASKY'S T.V. CONSTRUCTORS' PARCELS

No. 1. All brand new components by Igranic. Comprises E.H.T. flyback line transformer, 7-10Kv. with ferroxcube core and rectifier heater winding; scanning coils; frame output transformer; Elac focus unit with vernier adjuster, U37 E.H.T. rectifier and brand new 12-inch cathode ray tube with ion trap, mask and glass. **LASKY'S PRICE FOR THE COMPLETE PARCEL** £15/19/6. Carriage and insurance, 15/- extra.

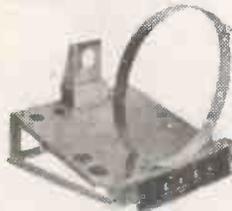

No. 2. The Constructors' Parcel as above, but less the cathode ray tube and ion trap. **LASKY'S PRICE** 79/6. Carr. 3/6 extra.

No. 3. Condenser Parcel. 1 of each:—.04mfd. 12.5Kv.; 32 + 32mfd. 350 v.w.; 32 + 100mfd. 450 v.w. AND 24 1,000pf. ceramic tubes; 6 .1mfd. 500 v.w.; .01mfd. 500 v.w. ALSO 12 assorted "pf" condensers of your own choice. **PRICE** 45/- POST FREE.

No. 4. Complete set of metal-work, as illustrated here. Un-assembled. Comprising main chassis, tube supports and valve-holders. (Less sound-vision chassis.) **PRICE** 25/- Carriage 3/6 extra.

No. 5. **RESISTANCES.** 4 Watt. 85 resistances your choice. **PRICE** 18/- POST FREE.

No. 6. One of each of the following:—Ion trap IT6; Duodecal tube holder; low impedance line and frame scanning coils. **PRICE** 15/- Postage 1/6 extra.

LASKY'S RADIO

Lasky's (Harrow Road) Ltd.,

370 HARROW ROAD, PADDINGTON, LONDON, W.9

(Opposite Paddington Hospital)

MAIL ORDER AND DESPATCH DEPARTMENTS, 485/487 HARROW ROAD, PADDINGTON, LONDON, W.10

Telephones: CUNningham 1979 and 7214. ALL DEPTS. Hours: Mon. to Sat. 9.30 a.m. to 6 p.m. Thurs. half day 1 p.m.

TERMS: Pro forma, Cash With Order or C.O.D. on post items only. Postage and packing on orders value £1—1/- extra

£5—2/- extra; £10—3/6 extra. Over £10 carriage free, unless specifically stated otherwise.

BARTON'S (Radio) LIMITED

RADIO

TELEVISION

OUR MOTTO IS—

**"GOODS OF QUALITY
SERVED WITH CIVILITY"**

**42: TOTTENHAM COURT ROAD,
LONDON: W.1.**

Telephones: LANGHAM 1151/2

TERMS OF BUSINESS: Cash with order (or C.O.D. Post items only); all orders for small items totalling over £2 post free unless otherwise stated.

THE FAMOUS RANGE OF

'DULCI'

RADIO/DIAGRAM CHASSIS

Allchassis 11in. x 7in. x 3in. high. Latest type valves 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Flywheel tuning. Negative feedback over entire audio section. Engraved knobs. 3 tone positions for radio and gram.

Model B3.—Long, Medium Short	5 Valves. Output 3½ watt	£12 12 0
Model B3.—Plus Push Full Stage	5 Valves. Output 6 watt	£15 15 0
Model B3.—Double Feature with P/Pull & R.F. Stage. 7 Valves. Output 6 watt		£18 18 0
Model B6.—Six Wavebands. Med., Long, 4 Short. (3 Band spread).	5 valves. Output 3½ w.	£15 15 0
Model B6.—Plus Push Full Stage	6 Valves. Output 6 watt	£18 18 0
Model B6.—Double Feature with P/Pull & R.F. Stage. 7 Valves. Output 6 watt		£23 2 0

FULLY GUARANTEED. TAX PAID. For A.C. Mains 100/120 and 200/250 volts. The Double Feature chassis are supplied with separate Power Packs.

BATTERY CHARGER KIT

Incorporates metal rectifier. Transformer is suitable for A.C. mains 200/250 volts. Charges either 12, 6 or 2 volt accumulator at 1 amp. Complete with circuit diagram. Price 22/6, plus 1/6 post and packing.

CHARGER TRANSFORMERS

Primaries tapped 200/250 v. Type MT5B. To charge 12, 6, and 2v. at 2½ amps. 18/- Type MT5. To charge 12, 6 and 2v. at 4 amps. 22/- Plus 1/6 post and packing.

METAL RECTIFIERS (FULL WAVE)

12 v. 1 amp. (Bridge Type), 7/6; 12 v. 2 amp., 11/3; 12 v. 3 amp., 12/-; 12 v. 4 amp., 15/- Suitable for use with the above transformers.

MAINS NOISE SUPPRESSOR KIT

Consisting of 2 specially designed chokes and 3 condensers. Extremely effective, cuts out all mains noise. Can be assembled in existing receiver or separately as desired. Complete with circuit diagram, 4/11, plus 1/- P.C.

1 mA METER

D.C., 2in. sq., panel mounting, 16/6, plus 1/- post and packing.

FILAMENT TRANSFORMERS

6.3 v. 1½ amp., 5/11; 6.3 v. 3 amp., 8/11; 6.3 v. (with 4 v. and 2 v. tappings), 1½ amp., 7/6. All plus 1/- P.P.

CONDENSERS

Silver Mica; Moulded Mica; Wax Tubular; Paper Black Types. Huge Stocks carried—please state your requirements.

ELECTROLYTIC CONDENSERS—NEW!

2 mfd., 150 v. 1/6	25 mfd., 50 v. 1/6
8 mfd., 450 v. 2/6	20-20 mfd., 275 v. 2/3
8-8 mfd., 450 v. 3/6	25 mfd., 25 v. 1/3
8-16 mfd., 450 v. 3/11	50 mfd., 50 v. 2/-
16 mfd., 450 v. 3/6	8-16 mfd., 350 v. 3/11
32 mfd., 500 v. 4/11	4 mfd., 450 v. 1/6
50 mfd., 12 v. 1/8	32-32 mfd., 350 v. 3/11

RESISTORS (CARBON)

± and ½ watt, 3d. each. 1 watt, 5d. each. All preferred values from 10 ohms to 10 meg.

LARGE STOCKS OF B.V.A. VALVES

and Ex-Govt. Special purpose valves. Your enquiries invited.

METAL RECTIFIERS

S.T.C.		
R.M.1. 125 v. 60 mA.	4/6	
R.M.2. 125 v. 100 mA.	5/-	
R.M.3. 125 v. 125 mA.	6/-	
R.M.4. 250 v. 250 mA.	18/-	

E.H.T. PENCIL RECTIFIERS—	
K3/50. 4 kV.	8/8
K3/100. 8.5 Kv.	14/8

METAL RECTIFIERS—BRAND NEW! 300 v. 75 mA., may be used in series or voltage doubling to give any required voltage, 7/11, plus 6d. post/pkg.

VIBRATORS

WEARITE, Type QFA/12, 12 v. 7-pin Sync. (Self Rectifying). BRAND NEW, in orig. cartons, 15/-. MALLORY, Type C45, 12 v. 5-pin (Non-Sync.), 7/6. Pkg., carr. on either of above 1/-.

LOUDSPEAKERS (2-3 ohms imp.)

ELAC, 2½in. dia. ... 15/-	ELAC, 6½in. dia. ... 18/6
ELAC, 3½in. dia. ... 15/-	ELAC, 8in. dia. ... 17/6
PLESSEY, 10in. dia. 18/9	

All the above plus 1/6 pkg., carr., ins.

GOODMANS 10in., H.F. 15 ohms 5 w. peak A.O.	28 12 0
Axiom 101	28 12 0
GOODMANS 8in., H.F. 15 ohms 5 w. peak A.O.	28 12 0
Axiom 102	28 12 0
ELAC 10in., 2-8 ohms	21 2 6

TRUVOX 12in., 2-3 ohms. SPECIAL OFFER, 47/6.

THE LATEST RANGE OF W.B. H.F. SPEAKERS

Incorporating the NEW Composite Cone

W.B. 8in. H.F., 10,000 lines, 3 ohms	£2 10 6
W.B. 8in. H.F., 10,000 lines, 3 ohms	£3 0 6
W.B. 9in. H.F., 12,000 lines, 3 ohms	£3 7 0
W.B. 10in. H.F., 12,000 lines, 3 ohms	£3 13 6

(Also available 15 ohms imp.)

WEARFEDALE BRONZE 10in. Flux

Density, 10,000 lines 6 w. 15 ohms	£4 12 8
WEARFEDALE GOLDEN 10in. Flux	
Density 13,000 lines, 8 w. 15 ohms	£7 13 3
WEARFEDALE GOLDEN/CSB 10in. Flux	
Density 13,000 lines, 5 w. 15 ohms	£8 6 7
WEARFEDALE SUPER 8in./CS/AL 8in. Cloth	
Suspension, Flux Density 13,000 lines, 40 w. 10 ohms	£6 13 3
WEARFEDALE SUPER 5in./CS/AL 5in. Cloth	
Suspension, Flux Density 13,000 lines, 10 ohms	£6 13 3
WEARFEDALE W12/CS 12in. Cloth Suspension.	
Flux Density 13,000 lines, 10 w. 15 ohms	£9 15 0
WEARFEDALE W12 12in. Flux Density	
13,000 lines, 15 w. 15 ohms	£9 5 0
GOODMANS 12in. Axiom 150 twin cone H.F., 15 ohms 16 w. peak A.O.	£10 5 6
GOODMANS 12in. Audiom 60 H.F. 15 ohms 15 w. Peak A.O.	£8 12 6

All the above plus 2/6 pkg., carr., ins.

MAINS TRANSFORMERS

Type LPL. 250-0-250, 60 mA. 5.3 v. 3 amp., 5 v. 2 amp. Fully shrouded	22/9
LP4. 275-0-275 v. at 80 mA., 0/4/6.3 v. at 4 amps., 0/4/5v. at 2 amp.	22/6
LP6. 350-0-350, 80 mA. 5.3 v. 5 amp., 5 v. 3 amp. Halshrouded	28/-
LP6. Fully shrouded as above	29/6
LP7. 350-0-350 120 mA. 6.3 v. 5 amp., 5 v. 3 amp. Fully shrouded	37/6
LP8. 425-0-425 150 mA. 3 v. 4 amp. C/T 8 v. 2 amp. Fully shrouded	52/8
LP10. 430-0-430 200 mA. 6.3 v. 4 amp., 6.3 v. 4 amp., 5 v. 3 amp. P/F.S.	55/-
LP11. 350-0-350 150 mA. 5.3 v. 5 amp., 5 v. 3 amp. Fully shrouded	44/6
E12. 350-0-350 150 mA. 6 v. 3 amp., 4 v. 3 amp., 30 v. 0.5 amp. Incorporates voltage adjustment panel tapped 200/210 v., 220/230 v., 240/250 v. Semi-shrouded drop through type	21/-
E13. 250-0-250 80 mA. 6.3 v. 4 amp., 5 v. 2 amp. Universal upright mounting	23/6
E14. 350-0-350 80 mA., 6.3 v. 4 amp., 5 v. 2 amp. Universal upright mounting	23/6
E15. General Purpose Step-down Transformer. Tapped 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v., 30 v. Total output 30 w. at 2 amps.	22/-

AUTO TRANSFORMERS

Tapped 10 v., 120 v., 200 v., 230 v., 250 v. 100 w., 22/- All the above are plus 1/6 post & pkg.

MICROPHONE TRANSFORMERS

Ratio 100:1, Mu metal. Has innumerable uses, 1/11 plus 6d. post/packing.

MICROPHONES

ACOS Mic. 22 (Crystal)	£4 4 0
Mic. 16 (Crystal)	£12 12 0
LUSTRAPHONE	
M.O. with T/F/CS1	25 15 6
Heavy Table Base for above	£1 1 0
RESLO (M/C Low Imp.)	
Ribbon High Fidelity	£7 5 0
Mumetal Transformer	£1 15 0

THE NEW ACOS 33-1

Crystal Mike., Output level—55 db. Ref. 1 v./dyne/cm., 50/- plus 6d. post/pkg.

ACOS 35-1

Crystal Mike., Output level—55 db. Ref. 1 v./dyne/cm., 25/- plus 6d. post/pkg.

REGENT HAND MICROPHONE

A high impedance crystal microphone complete with screened lead and jack plug. (Normal list price £22/-). Plus 1/6 post/packing. 22/6

BUILD YOUR OWN

HIGH FIDELITY

TAPE RECORDER

THE SENSATIONAL

'SOUND MASTER'

BY THE CREATORS OF THE FAMOUS

"VIEW MASTER"

Precision machined parts and standard radio components. Easily wired and assembled without previous experience. KITs can be purchased separately as follows:—

Tape Desk Kit	£13 13 0
3 Collaro Motors	25 15 0
Bulgin Component Kit	£3 10 0
Lab. Resistor Kit	£2 8 6
T.C.C. Condenser Kit	24 3 0
N.S.F. Switches	£1 15 6
Wearite Components	27 0 0
Whitley Components	£11 13 2
Cabinet	24 19 6

EASY STEP BY STEP INSTRUCTION ENVELOPE, 6/6. Working model may be heard at our shop.

TRUVOX TAPE DECK MARK III

Incorporating high impedance mu-metal twin-track heads. Two-speed capstan, for tape speeds of 7½ and 3½ inches per second. Three heavy-duty motors allowing for fast forward and rewind facilities without tape handling. All controls operated by electrically and mechanically interlocked push buttons. Price £23/2/- carriage free.

LANE TAPE DECK MARK IV

Made to high standards and incorporating features ensuring low level of "Wow" and "Flutter" throughout the full length of tape. Provision for fast rewind and forward run in less than 1 min. in either direction. WIND AND REWIND WITHOUT UNLACING OF TAPE. INSTANTANEOUS BRAKING. THESE MOTORS obtaining friction drive. The Table is fitted with high fidelity record playback head of new design wound to high impedance and a separate A.C. Erase Head. The Heads are half-track size allowing approx. 1 hr. playing from standard 1,200ft. Reel of Tape.

TAPE DECKS AND TABLES

WEARITE 2A TAPE DECK	£35 0 0
MOTEK K4 TAPE TABLE. Push button operation	£17 17 0

TAPE RECORDER

The Famous "GRUNDIG" 2 Speed. £84 0 0

RECORDING TAPE

FERROGRAPH, 1,200ft.	£2 5 0
GRUNDIG, 1,200ft.	£3 0 0
SCOTCH BOY, 1,200ft.	£1 15 0
EMITAPE, 1,200ft.	£1 15 0
FERRVOICE, 1,200ft.	£2 6 6
GRUNDIG, 600ft.	£1 4 0
SCOTCH BOY, 600ft.	£1 0 0
EMITAPE, 600ft.	£1 1 0
FERRVOICE, 600ft.	15 0 0
FERRVOICE, 300ft.	8 6

THE NEW COLLARO STUDIO PICK-UP

Type "O" or "P" £3 14 8

THE FAMOUS 4-VALVE

"SOBELL"

SUPERHET TABLE RECEIVER MEDIUM/LONG WAVES

Valve line up 12T7, 35L6, 148T, 35Z4. This very sensitive receiver, incorporates a carrying handle making it entirely transportable. Housed in an attractive plastic cabinet of modern design, it can be used on either A.C. or D.C. 200/250 v. mains.



£8.5.0

Plug 3/6 Packing carr., ins.

AVAILABLE IN ONE COLOUR ONLY: WALNUT BROWN.

GUARANTEED FOR TWELVE MONTHS

"TYANA" SOLDERING IRON

Weight 4 ozs.; Adjustable Bit; heating time 3 mins. Length 10½in., 14½ plus 1/- post.

"TYANA" ELECTRIC SOLDER GUN

Instant heating, low voltage, bit which can be bent to shape to reach corners, balanced grip. A.C. 220/250 v. Guaranteed 12 months. Complete with 6 Bits 63/-

RADIO

BARTON'S (Radio) LIMITED

TELEVISION

**MONEY BACK GUARANTEE
PROMPT DESPATCH
GOODS OF QUALITY**

42 · TOTTENHAM COURT ROAD,

LONDON · W.1.


Telephones: LANGHAM 1151/2

TERMS OF BUSINESS: Cash with order (or C.O.D. Post-tickets only); all orders for small items totalling over £2 post free unless otherwise stated.

BUILD YOUR OWN RADIO!



We can supply all the parts (including valves, 5in. moving coil speaker, cabinet, chassis, and everything down to the last nut and bolt) to enable YOU to build a professional-looking radio. The chassis is punched and drilled ready to mount the components. There is a choice of any of three attractive cabinets 12in. long 5in. wide by 6in. high, as follows; either Ivory or brown bakelite, or wood, finished in walnut. Complete and easy-to-follow point-to-point and circuit wiring diagrams supplied.

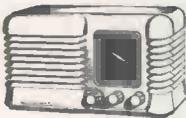

MODEL 1 T.R.F. RECEIVER

This is a 3 valve plus metal rectifier TRF receiver with a valve line-up as follows: 6K7 (HF), 6J7 (Det) and 6V6 (Output). The dial is illuminated and when assembled the receiver presents a very attractive appearance. Coverage is for the Medium and Long Wave bands. Operates on 200/250 volts AC Mains.

Plus 2/6 Packing, Carriage, Insur.

£5.15.0

MODEL 2. SUPERHET RECEIVER

This is a powerful midget 4 valve plus metal rectifier Superhet Receiver with a valve-line-up as follows: 6X8, 6K7, 6Q7, 6V6. The dial is illuminated and coverage is for the Short Wave bands between 15-50 metres, the Medium Wave bands between 190-540 metres, and the Long Wave bands between 1,000-2,000 metres. Operates on 200/250 volts AC mains.

Plus 2/6 Packing, Carriage and Insur.

£7.19.6

T.R.F. RECEIVER We can supply this Receiver ready built at £8 19s. 6d. plus 3/6 p.c.

ALL COMPONENTS SUPPLIED ARE GUARANTEED FOR ONE YEAR

NOTE: We would respectfully suggest to those interested in building this receiver that they send for OUR Instruction Booklet. Intending constructors can then judge for THEMSELVES how comprehensive this Booklet is.

Instruction Booklet and priced Parts List, for either of the above, available separately at 1/-. This money will be refunded if circuit diagram is returned as a NEW within 7 days. When ordering please state Model No.

IT'S SENSATIONAL!

NOW BEING DEMONSTRATED AT OUR SHOP

THE 'IMPRESARIO' TAPE RECORDER

The 'Impresario' is a combination instrument that will make high quality tape recordings of live speech or music, gramophone or radio and telephone conversation, etc.

- Dual speed 3 3/7 in. per sec.
- Twin track : up to 2 hrs. recording.
- Separate bass and treble controls.
- 4 watts output : neg. F/B.
- Internal mike recording system.

The 'Impresario' can also be used as a high quality radio, gramophone or microphone amplifier.

PRICE **49 1/2 GNS.**

(Excluding tape and microphone)

GUARANTEED FOR 12 MONTHS

RADIO RECEIVER

The 'Impresario' is the first transportable tape recorder in Great Britain to provide power supply and internal space for a Radio Tuner unit with optional listening and/or recording

DISTORTIONLESS SUPERHET 3-WAVE RADIO TUNER UNIT

PRICE (Tax Paid) **14 GNS.** May be fitted in a few minutes.

The 'Impresario' combined instrument will not only provide tape recordings from microphone, gramophone, radio, telephone, etc., but can be used independently as a high-quality amplifier. It also provides internal space with H.T. and L.T. supplies for a radio tuner unit.

The conventional switching of record/playback is supplemented by a neutral position which enables the unit to be operated as a straight amplifier when recording facilities are not required. An internal input terminal is provided for connection to a radio feeder unit output (where this is incorporated) and, whilst operated in the neutral position, the 'Impresario' then becomes a radio receiver. Should it be required to record any part of a radio programme, it is necessary only to switch to "record" and start the tape deck.

The input jack for "mike", gram, etc., automatically mutes the radio. The speaker jack is so arranged that any programmes may be monitored or an extension speaker used if required. A system is employed whereby the internal speaker may be used as an occasional microphone for recording.

The 4W amplifier incorporates generous negative feedback over each of its five stages. The use of independent bass and treble lift and cut tone controls, operative on all inputs, ensures correct equalization. A recording level indicator is provided and bias and erase voltages are obtained from a separate oscillator valve stage.


The latest Truvox 3-motor, dual-speed (3 1/2 in. per second) twin track, electrically and mechanically interlocked push-button control, Tape Deck is used, and the Impresario is housed in an attractive light brown imitation lizard skin cabinet, measuring 19 by 13 1/2 by 13 1/2 in. high. It is for operation on 200-250 v. A.C.

The radio tuner unit can be fitted very easily; the right side panel of the cabinet is conveniently detachable, being held by four screws. The tuner, is a modified version of the Elpico RF/716 3-way superhet unit.

Announcing a NEW 4 watt AMPLIFIER KIT

This is a 3 valve 3 stage Amplifier for use with Gramophone, Microphone or Radio. Valve line-up is as follows: 6BL7; 6V6; 5Z4. Negative feed-back. Tone control. Voltage adjustment panel incorporated. 4 watts output. For operation on A.C. Mains 200/250 volts. The complete Kit, includes every item down to the last nut and bolt, drilled and punched chassis, and comprehensive point-to-point wiring circuit diagram. Chassis dimensions: 8in. x 6in. x 3 1/2in.

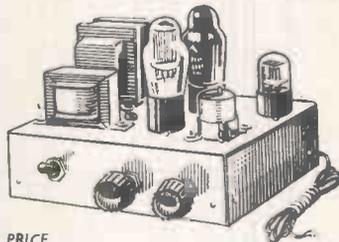ALL COMPONENTS SUPPLIED ARE GUARANTEED FOR ONE YEAR



PRICE

£4.19.6

Plus 2/6 PACKING CARRIAGE & INSUR.

The Output Transformer supplied is for use with a loud-speaker of 3 ohms impedance and we would suggest that the output of the completed amplifier justifies the use of one of the latest W.B. H.F. Speakers which can be supplied as follows: 8in., 60/6; 9in., 67/-; 10in., 73/6. All plus 2/6 pkg., carr., ins.

Circuit Diagram only, available separately at 1/-. To those who require this Amplifier ready-built we can supply it at £5/19/6, plus 3/6 pkg., carr., ins.

RADIO CABINET

Superb highly polished walnut cabinet, strongly constructed. Dimensions:—Height 17 1/2 in.; Width 17 1/2 in.; Depth 9 in. Shown with dial of chassis below.



£3.15.0

Plus 7/6 Carr & Ins.

5 VALVE SUPERHET CHASSIS



Fitted with Valve Holders, Aerial, Earth and Gram Socket; Full Vision 3 Wave band Dial and Drive Assembly 2 gang Tuning Condenser. Chassis dimensions:—13 1/2 in. long, 5 1/2 in. wide, 2 1/2 in. deep.

42/6 Plus 1/6 Pkg, Carr. & Ins.

AS A SPECIAL OFFER WE CAN SUPPLY BOTH THE ABOVE, IF PURCHASED TOGETHER, FOR **£5.7.6** Plus 7/6 Carr. & Ins.

R.S.C. MAINS AND OUTPUT TRANSFORMERS

Fully Guaranteed, Interleaved and Impregnated

FILAMENT TRANSFORMERS

Primaries 200 250 v. 50 c/s.	
6.3 v. 1.5 a.	5/9
6.3 v. 2 a.	7/6
6.3 v. 3 a.	9/6
0-4-6.3 v. 2 a.	7/9
12 v. 1 a.	7/11
6.3 v. 6 a.	17/6
0-2-4-5-6.3 v. 4 a.	16/9
12 v. 3 a. or 24 v. 1.5 a.	17/6

CHARGED TRANSFORMERS

All with 200-230-250 v. 50 c/s. Primaries: 0-9-15 v. 1.5 a., 12/9; 0-9-15 v. 3 a., 16/9; 0-9-15 v. 6 a., 22/9; 0-4-9-15-24 v. 3 a., 22/9; 0-9-15-30 v. 3 a., 23/9.

TOP SHROUDED DROP THROUGH TYPE

Primaries 200-230-250 v. 50 c/s.	
250-0-250 v. 70 mA., 6.3 v. 2.5 a.	12/11
250-0-250 v. 70 mA., 6.3 v. 3 a., 5 v. 2 a.	14/11
350-0-350 v. 80 mA., 6.3 v. 2 a., 5 v. 2 a.	16/9
350-0-350 v. 80 mA., 6.3 v. 3 a., 4 v. 2.5 a.	14/11
200-0-250 v. 100 mA., 6.3 v. 4 a., 5 v. 3 a.	23/9
300-0-350 v. 100 mA., 6.3 v. 4 v. 4 a., c.t., 0-4-5 v. 3 a.	23/9
350-0-350 v. 100 mA., 6.3 v. 4 v. 4 a., c.t., 0-4-5 v. 3 a.	23/9
350-0-350 v. 150 mA., 6.3 v. 4 a., 5 v. 3 a.	29/11
350-0-350 v. 150 mA., 6.3 v. 2 a., 6.3 v. 2 a., 5 v. 3 a.	29/11

E.H.T. TRANSFORMERS. 2,500 v. 5 mA.,

2-0-2 v. 1.1 a., 2-0-2 v. 1.1 a., for VCR97, VCR517 or ACR2X 35/-
5,000 v. 5 mA. 2 v. 2 a. 39/6

SILVER MICA CONDENSERS. 5, 10, 15,

20, 25, 30, 35, 50, 100, 120, 150, 180, 200, 230, 300, 330, 400, 470, 500, 1,000 pfd. (.001µF), .002 mfd. (2,000 pfd.). All at 5d. each; 3/9 dozen one type.

DIAL BULBS, M.E.S., 8 v. 0.15 a., 6/9 doz.

6.5 v. 0.15 a., 6/9 doz. 3.5 v. 0.3 a., 6/6 doz.

VOLUME CONTROLS with long spindles,

all values less switch, 2/9; with S.P. switch, 3/9.

WIRE WOUND POTS: 30 ohms, 500 ohms

1,000 ohms, 5K, 20K, 50K (medium length spindles), 2/9. 220 ohms, 2K, 10K, 20K, 50K Preset type, 1/9 ea.

AMMETERS. Moving coil. G.E.C. 0-5 amps,

2in. scale, 11/9.

ELECTROLYTICS (Current production.)

NOT ex-Govt.

Tubular Types		Can Types	
8µF 450 v.	1/11	16µF 450 v.	2/9
8µF 500 v.	2/9	24µF 350 v.	2/11
16µF 350 v.	2/3	32µF 350 v.	2/11
16µF 450 v.	2/9	32 mfd. 450 v.	4/9
16µF 500 v.	3/9	64 mfd. 450 v.	4/9
24µF 350 v.	3/3	8-8µF 350 v.	3/9
32µF 350 v.	3/9	8-8µF 450 v.	3/11
32 mfd. 500 v.	5/9	8-8mfd. 500 v.	4/9
8-16µF 500 v.	4/11	8-16µF 450 v.	2/11
25µF 25 v.	1/3	16-16µF 450 v.	4/11
50µF 12 v.	1/3	16-32µF 350 v.	4/9
50µF 5 v.	2/3	16-32 mfd. 450 v.	4/9
Can Types			
8 mfd. 450 v.	2/3	32-32µF 350 v.	4/9
8 mfd. 500 v.	2/11	32-32µF 450 v.	5/11
16 mfd. 350 v.	1/11	60-100 mfd. 450 v.	7/9
		64-120 mfd. 350 v.	7/6

MISCELLANEOUS EX-GOVT. ITEMS

Slydlock Fuses, 15 amp, 1/9. Bulgin octal type moulded Bakelite, 5-pin or 7-pin Plugs and Sockets, 1/11 pair. Earphones (Single), low resistance, 1/3.

EX-GOVT. ACCUMULATORS with non-spill vents.

Unused and guaranteed. 2 v. 16 A.H., 5/9 each, or 3 in wood carrying case 9-7-5in., 14/9, plus 2/6 Carr.

P.M. SPEAKERS. All 2-3 ohms 3½in. Goodmans

(Ex New Units), 10/9. 6½in. Goodmans, 16/9. 8in. Plessey, 15/9. 8in R.A. Heavy duty, 18/9. 10in. Rola, 27/9. 10in. Plessey, 18/6. 10in. Rola with Trans, 29/6. 12in. Truvox, 49/9.

M.E. SPEAKERS. All 2-3 ohms 6½in. Rola

field 700 ohms, 11/9. 10in. R.A. field 600 ohms, 23/9. 10in R.A. field 1,500 ohms, 23/9. 10in. R.A. field 1,000 ohms, 23/9.

FULLY SHROUDED UPRIGHT MOUNTING

Primaries 200-230-250 v. 50 c/s.	
250-0-250 v. 60 mA., 6.3 v. 2 a., 5 v. 2 a., Midget type 2½-3-8in.	16/9
350-0-350 v. 70 mA., 6.3 v. 2 a., 5 v. 2 a.	18/9
300-0-300 v. 60 mA., 12 v. 1.5 a., c.t.	18/11
250-0-250 v. 100 mA., 6.3 v. 4 v. 4 a. c.t., 0-4-5 v. 3 a.	25/9
250-0-250 v. 100 mA., 6.3 v. 6 a., 5 v. 3 a., for R1355 conversion	29/9
300-0-300 v. 100 mA., 6.3 v. 4 v. 4 a. c.t., 0-4-5 v. 3 a.	25/9
350-0-350 v. 100 mA., 6.3 v. 4 v. 4 a. c.t., 0-4-5 v. 3 a.	25/9
350-0-350 v. 150 mA., 6.3 v. 4 a., 5 v. 3 a.	33/9
350-0-350 v. 150 mA. 6.3 v. 2 a., 6.3 v. 2 a., 5 v. 3 a.	33/9
350-0-350 v. 160 mA., 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a.	45/9
350-0-350 v. 250 mA., 6.3 v. 6 a., 4 v. 8 a., 0-2-6 v. 2 a., 4 v. 3 a., for Electronic Eng. Television	67/6
425-0-425 v. 200 mA., 6.3 v. 4 v. 4 a., c.t., 6.3-4 v. 4 a., c.t., 0-4-5 v. 3 a. suitable Williamson Amplifier, etc.	49/9
425-0-425 v. 250 mA., 6.3 v. 6 a., 6.3 v. 6 a., 5 v. 3 a.	65/6

EX-GOVT. E.H.T. SMOOTHING CONDENSERS

.02 mfd. 5,000 v. Bakelite Tubulars	1/6
.02 mfd. 8,000 v. Cans	1/11
.1 mfd. 2,000 v. Blocks	2/9
.25 mfd. 5,000 v. Blocks	4/9
.5 mfd. 3,500 v. Cans	3/3
1 mfd. plus 1 mfd. 8,000 v., large blocks (common negative isolated)	9/6

BAKELITE AND WALNUT VENEERED CABINETS



Size approximately 12in. x 6½in. x 5in. Bakelite type available in Brown or Cream. Price of Cabinets, 17/6 ea., carr. 2/6.

Suitable fully punched T.R.F. 3-valve and rectifier chassis	3/9
Suitable fully punched superhet chassis (4 valves and rect.)	4/9
Dial Scales, 2 colour, 2 waveband, station named, glass	1/6
Dial Scales, 3 colour, 3 waveband, station named, glass	1/9
Suitable coloured Metal Backplates	1/3
Pointers, Double ended	4d.
T.R.F. Coils, 2 waveband with circuit	4d.
Drum Drives, complete	2/6

THE SKY CHIEF T.R.F. RECEIVER

A design of a 4-stage, 3 valve 200-250 v. A.C. Mains receiver with selenium rectifier. For inclusion in any of cabinets illustrated above. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally comes the output stage consisting of a parallel connected double triode giving ample output at an extraordinary low level of distortion. Point to point wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/16/- including cabinet.

SELENIUM RECTIFIERS

L.T. Types	H.T. Types H.W.
2/6 v. ½ a.h.w.	1/9
F.W. Bridge Types	
6/12 v. 1 a.	5/9
6/12 v. 2 a.	9/9
6/12 v. 4 a.	14/9
6/12 v. 6 a.	19/9
70 v. 20 mA.	2/11
90 v. 20 mA.	3/6
120 v. 40 mA.	3/11
250 v. 50 mA.	5/9
350 v. 50 mA.	7/9
250/350v. 80 mA.	8/9

SPECIAL OFFERS. Germanium Crystal Diodes

1/11. Midget Mains Transformers (size approx. 2½ x 3 x 2½in.). Screened Primary 220/240 v. 50 c/s. Output, 220-0-220 v. 40 mA. 6-3 v. 1.5 a., 9/9.

EX-GOVT. CATHODE ISOLATING FILAMENT

TRANSFORMERS. 6.3 v. to 6.3 v. c.t., 3/9 ea.

SMOOTHING CHOKES

250 mA., 7-10 H. 200 ohms Shrouded	16/9
250 mA., 3 H. 50 ohms	11/9
100 mA., 15 H. 350 ohms	7/6
80 mA., 10 H. 350 ohms	5/6
60 mA., 10 H. 400 ohms	4/11
50 mA., 40 H. 1,000 ohms Potted	10/9

ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c/s. 120 v. 40 mA.	7/11
120 v. 40 mA. 5-0-5 v. 1 a.	14/9

OUTPUT TRANSFORMERS

Midget Battery Pentode 66: 1 for 3S4, etc.	3/6
Small Pentode, 5,000Ω to 3Ω	3/9
Standard Pentode, 5,000Ω to 3Ω	4/9
Standard Pentode, 8,000Ω to 3Ω	4/9
Standard Pentode, 10,000 ohms to 3 ohms	4/9
Multi-ratio 40 mA. 50:1, 45:1, 60:1, 90:1, Class B Push-Pull	5/6
Push-Pull 8 Watts 6V6 to 3 ohms	8/9
Push-Pull 10-12 Watts 6V6 to 3Ω or 15Ω	15/9
Push-Pull 10-12 Watts to match 6V6 to 3-5-8 or 15Ω	16/9
Push-Pull 15-18 Watts to match 6L6, etc., to 3Ω or 15Ω Speaker	22/9
Push-Pull 20 Watts high-quality sectionally wound, 6L6, KT66, etc., to 3 or 15Ω	47/9
Williamson type, exact to author's specification	85/-

MICROPHONE TRANSFORMERS

100:1	5/9
-------	-----

EX-GOVT. AUTO TRANSFORMERS 50c/s.

Double Wound 100 watts, 5-0-115-125 v. to 10-0-10-210-230 v. or reverse	18/9
15-10-5-0-215-235 v. 200 watts	25/9
Double wound 10-0-200-220-240 v. input, 10-0-270-290-310 v. output 200 watts	27/9
Double Wound 220/240 v. input. Output 51 v. to 250 v. 21 amps. in steps of 11 v.	85/-

EX-GOVT. MAINS TRANSFORMERS

All 230 v. 50 c/s. input 48 v. 1 a. output	9/6
Outputs 250-0-250v. 40 mA., 6.3v. 2 a., 5v. 2 a.	10/9
350-0-350 v. 150 mA. 5 v. 3 a.	17/6

VALVE SCREENING CANS. International Octal

3 piece, 10/6 doz., 1/3 each.

EX-GOVT. SMOOTHING CHOKES

250 mA., 10 H. 50 ohms	14/9
250 mA. 20 H. 250 ohms. Tropicalised	13/9
250 mA. 10 H. 100 ohms	14/9
250 mA. 3 H. 50 ohms Potted	7/6
150 mA. 10 H. 50 ohms	10/11
100 mA. 10 H. 100 ohms. Tropicalised	6/9
100 mA. 5 H. 100 ohms. Tropicalised	4/8
90/100 mA. 10 H. 100 ohms. Potted	8/9
70 mA. 5-10 H.	3/9
50 mA. 5-10 H.	2/9
L.T. type 1 amp.	2/9

EX-GOVT. T.V. TYPE TRANSFORMERS. All

230 v. 50 c/s. input	
1250-0-1250 v. 250 mA., 4 v. 3 a.	25/-
6.3 v. 6 a., 6.3 v. 6 a., 5 v. 3 a., 5 v. 3 a., 4 v. 3 a.	
400 v. C.T. 150 mA., 4 v. 6 a., 6.3 v. 6 a., 6.3 v. 0-6 a., 4 v. 6 a., 4 v. 3 a., 4 v. 3 a., 5 v. 2 a.	22/6

EX-GOVT. BLOCK PAPER CONDENSERS

4 mfd. 500 v.	2/9	4 mfd. 1500 v.	4/9
4 mfd. 750 v.	3/3	10 mfd. 1500 v.	7/9
4 mfd. 400 v. plus 2 mfd. 250 v.	4/11.		

EX-GOVT. CATHODE RAY TUBES

VCR517 (guaranteed full picture) (carr. 5/-) 29/6 ea. ACR2X (guaranteed full picture) (carr. 5/-) 12/6 ea.

EX-GOVT. TRANSMITTER-RECEIVER TYPE

TR9D, complete with all valves, only 47/9, plus carr. 5/-.

CO-AXIAL CABLE. 75 ohms ½in., 8d. yard.

SPECIAL PURPOSE EX-GOVT. VALVES


(GUARANTEED) VR91, 5/9, SP61 (VR65), 3/9, VR56 3/11, 807 6/11, 0J6 10/6, 6SH7Met 6/11, 12SC7GT 6/11, VU120A 2/9, VS1101/9.

R.S.C. 25 WATT "PUSH PULL" AMPLIFIER


Now firmly established and proving extremely popular, our AII Quality Amplifier we consider to be the best value in amplifiers offered to-day. The volume of its high fidelity reproduction is completely controllable, from the sound of a quiet intimate conversation to the full glorious volume of a great orchestra. Its sensitivity is so high that in areas of fair signal strength it can be operated straight from a crystal receiver. Entirely suitable for standard or long playing records in small homes or in large auditoriums. For electronic organ or guitar or for garden parties or dance bands.

The kit is complete to the last detail, and includes easy to follow point-to-point wiring diagrams.

Twin volume controls with twin input sockets allow SIMULTANEOUS INPUTS for BOTH MICROPHONE and GRAM, or TAPE and RADIO. SEPARATE BASS and TREBLE CONTROLS giving both LIFT and CUT. FOUR NEGATIVE FEEDBACK LOOPS with 15 db in the main loop from output transformer to voltage amplifier. Frequency response ± 3 db. 50-20,000 c.p.s. Hum and distortion LESS THAN 0.5 per cent. measured at 10 watts. This is comparable with some of the highest priced amplifiers. Six B.V.A. valves, Marconi/Osram KT series output valves. A.C. only, 200-230-250 v. 50 c/s. input. 420 v. H.T. LINE. Paper reservoir condenser. Compact chassis. Matched components. OVERALL SIZE 12x10x9in. approx. Output impedances for 3 and 15 ohms speakers.

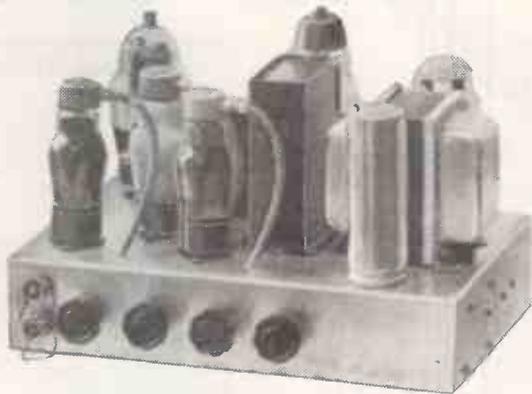

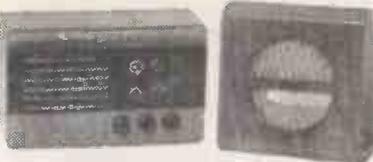Available in kit form at **9 gns.** Plus the amazingly low price of **5/-** carriage 5/-
Or ready for use 50/- extra.



R.S.C. MASTER INTERCOMM. UNIT, with provision for up to 4 "Listen-Talk Back Units" individually switched. A high gain amplifier enables speech and other sounds emanating from the rooms containing remote control units to be heard at the master control. The unit is in kit form and point-to-point wiring diagrams are supplied. A walnut veneered wood or Brown Bakelite cabinet is included. Mains input is 200-250 v. 50 c/s. H.T. line 300 v. CHASSIS IS NOT "ALIVE." Ideal also for use as "Baby Alarm." Sound amplification 4 watts. Price only **25/19/6**. "Listen-Talk Back Unit" as illustration can be supplied at 30/- each. Full descriptive leaflet 10d. The Master Unit can be supplied assembled and tested for 30/- extra.


R.S.C. BATTERY CHARGER KITS. For mains input 200-250 v. 50 c/s. To charge 6 v. accumulator at 2 amps., 25/9.



To charge 6 v. or 12 v. accumulator at 2 amps., 31/6.
To charge 6 v. or 12 v. accumulator at 4 amps., 49/9.

ABOVE KITS CONSIST OF BLACK CRACKLE LOUVRED STEEL CASE, MAINS TRANSFORMER, FULL WAVE METAL RECTIFIER, FUSES, FUSE-HOLDERS AND CIRCUIT. The mean charging rates are as indicated above, and complete safety is ensured by fusing of both input and output. Chargers supplied assembled and tested for 6/9 extra.

A PUSH-PULL 3-4 WATT HIGH-GAIN AMPLIFIER FOR **23/12/6**, plus carr. 2/6. For mains input 200-250 v. 50 c/s. Complete kit of parts including point-to-point wiring diagrams and instructions. Amplifier can be used with any type of feeder unit or pick-up. Output is for 2-3 ohm speaker. (We can supply a very suitable 10in. unit by Rola at 27/9.) The amplifier can be supplied ready for use for 25/- extra. Full descriptive leaflet 7d.

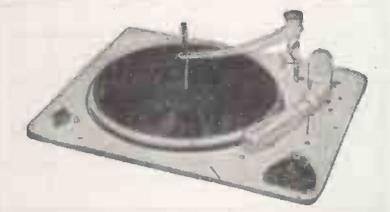

COLLARO 3-SPEED AUTOMATIC RECORD CHANGERS (brand new), type RC3521, complete with 2 plug-in Crystal P.U. heads for long playing or standard records 7, 10 or 12in. Not intermixed. Mains input 200-250 v. Limited number available at only **29/15/-**, plus carr. 5/-.

COLLARO 3-SPEED RECORD PLAYER UNIT. Type RC3/514, complete with Orthodynamic Pick-up, and matching transformer. Separate Stylus for long playing or standard records are moved into position by a switch which also makes necessary weight adjustment. Mains input 200-250 v. A.C. Brand new in Makers cartons, **26/19/6**, plus 5/- carr.

COLLARO RECORD PLAYER UNIT. Type AC/514. Standard 10in. turntable. Speed normal 78 r.p.m. Crystal pick-up. Mains input 200-250 v. A.C. Brand new cartoned **23/19/6**, plus 5/- carr.

COLLARO TAPE DESK MOTORS. Shaded pole type. Clockwise or anti-clockwise. Mains input 110-200-250 v., 31/6.

R.S.C. 8-10-watt "Push-Pull" HIGH-FIDELITY AMPLIFIER A3. Complete with integral pre-amp. Tone control stage (as AII amplifier), using negative feedback, giving humproof individual bass and treble lift and cut tone control. Six Negative Feedback Loops. Completely negligible hum and distortion. Frequency response ± 3 db. 30-20,000 c.p.s. Two independently controlled inputs. Six B.V.A. valves. A.C. mains 200-230-250 v. input only. Outputs for 3 or 16 ohm speakers. Kit of parts complete in every detail. **27/19/6**, plus 5/- carriage, or ready for use, 45/- extra.

R.S.C. TONE CONTROL-PRE-AMP. UNIT. A complete set of parts for the construction of a very efficient but simple pre-amplifier and tone control unit. Suitable for use with any amplifier and pick-up. Fil. supply is self-contained. Size is 7 1/2-5 1/2in. approx. Full descriptive leaflet 9d. Price, including wiring diagrams, 37/6. Or ready for use, 15/- ex ra.

CHASSIS
18 s.w.g. undrilled aluminium amplifier type (4-sided)
12in. x 6in. x 2 1/2in. ... 6/11
14in. x 6in. x 2 1/2in. ... 6/11
14in. x 10in. x 3in. ... 7/11
16in. x 10in. x 3in. ... 8/3
18 s.w.g. aluminium receiver type, 4-sided.
16in. x 8in. x 2 1/2in. ... 5/3
16in. x 8in. x 2 1/2in. ... 7/6
20in. x 8in. x 2 1/2in. ... 8/11

H.T. ELIMINATOR AND TRICKLE CHARGER KIT. Consists of H.T. and L.T. transformer, H.T. and L.T. rectifiers, smoothing electrolytic choke, and steel case. For mains input of 200-250 v. Output 120 v. 40 mA. and 2 v. 1/2 a. Price with circuit 29/6. Or in working order, 37/6.

PERSONAL SET BATTERY SUPERSEDER KIT. All parts for an "All Dry" Battery Eliminator. Complete with case. Supplies 90 v. 10 mA. and 1.4 v. 250 mA. fully smoothed, from normal. 200-250 v. 50 c/s. mains. For 4-valve superhet receivers. Price with circuit 35/9. Or ready for use, 42/6. Size of unit 5 1/2-4-1 1/2in.

BATTERY SET CONVERTER KITS. All parts for converting any type of battery receiver to all mains. A.C. 200-250 v. 50 c/s. Kit will supply fully smoothed H.T. of 120 v. 90 v. or 60 v. at up to 40 mA., and fully smoothed L.T. of 2 v. at 0.4 a. to 1 a. Price complete with circuit and instructions only 48/9. Supplied ready for use for 7/9 extra.

RADIO SUPPLY CO. (LEEDS) LTD.

32 THE CALLS, LEEDS, 2

Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/1 extra under £1, 1/9 extra under £3. Full Price List 6d. Trade List 5d.
Open to Callers: 9 a.m. to 5.30 p.m. Saturdays until 1 p.m.

"MUST HAVE" BARGAINS

RECEIVER R3118, ideal for conversion to TV, having a built-in A.C. mains Power Pack or 180-240 volts, is tremendously powerful employing 7 I.F. stages of 12 Mc/s with 4 Mc/s Bandwidth and has 16 valves as follows: 6 of SP61, 4 of EA50, 2 of VR136, 1 each VR137, P61, 5Z4, and Y63 "MAGIC EYE" IN NEW CONDITION, only 97/6 (carriage, etc., 7/6).

"**PYE**" 45 Mc/s I.F. STRIP. Ready made for the London Vblon Channel. Complete with 6 valves EF50 and 1 EA50. BRAND NEW. ONLY 70/- (postage, etc., 2/6).

I.F. STRIP 194. An easily modified strip recommended for TV constructors who want good results at moderate cost, or for those who have built televisions but are having trouble in the sound or vision receivers. Size 18in. x 5in. x 5in., it is complete with 6 valves VR65, 1 of VR92, and 1 of VR56 or VR53. Mod. data supplied. ONLY 45/- (postage, etc., 2/6). Less valves, 19/6 (post, etc., 2/6).

TELESCOPIC AERIAL. Pulls out of metal tube 15in. long to extend to 73in. BRAND NEW. ONLY 7/6 (postage 10d.).

AMPLIFIER 208 Ideal for conversion into a high-gain TV pre-amp. Complete with 2 valves EF50. ONLY 15/- (postage, etc., 1/6).

CHOKES. 3H 40 mA., 3/6. 5H 200 mA., 7/6. 10H 60 mA., 4/- 30H 100/150 mA., 12/6. (Postage 1/-).

CHASSIS OF POWER UNIT 529. An ideal unit for component value or for building an amplifier, etc. Contains valveholders, resistors, potentiometer chokes, and block and tubular condensers. Housed in grey metal case, size 12in. x 8jin. x 7jin. BRAND NEW. ONLY 10/- (carriage, etc., 3/6).

AMERICAN 12 v. DYNAMOTORS. Output 255 v. 60 mA. ONLY 22/6.
24 v. BLOWER MOTORS. ONLY 17/6.

C.R. TUBE VCR97. Tested full screen. BRAND NEW IN MAKER'S CRATES. ONLY 42/6.

6 v. VIBRATOR UNITS. Made by the National Co. of America for use with H.R.O. Communications Receivers, supplying 165 v. at 85 mA. fully smoothed D.C. Complete with vibrator and 6X5 rectifier in black crackle cabinet size 7in. x 7jin. x 6in. ONLY 29/6 (postage, etc., 2/6).

METAL RECTIFIERS. Selenium full wave bridge 6 or 12 volts; 1 amp 7/6; 2 amp 11/3; 3 amp 12/6; 4 amp 15/-

CHARGER TRANSFORMERS. Normal primaries, output 0.9-15 volts; 1 amp 10/6; 2 amp 16/6; 3 amp 18/6; 4 amp 20/-.

COMMUNICATIONS RECEIVER R.1155

The famous ex-Bomber Command Receiver known the world over to be supreme in its class. Covers 5 wave ranges: 18.5-7.5 Mc/s, 7.5-3.0 Mc/s, 1,500-600 kc/s, 500-200 kc/s, 200-75 kc/s, and is easily and simply adapted for normal mains use, full details being supplied. Aerial tested before despatch. BRAND NEW AND UNUSED IN MAKER'S TRANSIT CASES. ONLY £11/19/6.

USED RECEIVERS, also tested working before despatch, £7/19/6.

R.1155 "N" Model. This is the latest version which covers the Trawler Band and in addition has ultra-slow motion tuning. Used, in good condition, and tested working before despatch £17/19/6.

A Factory-made Power Pack, Output Stage and Speaker, contained in a black crackle cabinet to match the receiver, can be supplied for ONLY £5/10/-. Plugs on to the receiver, and operates it immediately.

DEDUCT 10/- IF PURCHASING RECEIVER AND POWER PACK TOGETHER.

Please add carriage costs of 10/6 for receiver, and 5/- for Power Pack.

INDICATOR UNIT TYPE 62A

Built on a two-deck chassis, this contains VCR97 Cathode Ray Tube with mu-metal screen, 12 valves EF50, 4 of SP61, 3 of EA50, and 2 of EB34. An economical way of buying a VCR97 and EF50s. IN NEW CONDITION IN MAKER'S TRANSIT CASES. ONLY 99/6 (carriage, etc., 10/6).

ROTARY POWER UNITS TYPE 104

Input 12 v., Output 230 volts 65 mA. and 6.3 volts 2.5 amp. Fully filtered and smoothed and noise suppressed. Ideal for car radio, etc. BRAND NEW. ONLY 15/- (postage, etc., 2/6).

100 MICROAMPS METERS

2jin. circular flush mounting. Widely calibrated scale of 15 divisions marked "yards" which can be rewritten to suit requirements. These movements are almost unobtainable to-day and being BRAND NEW IN MAKER'S CARTONS are a snip at ONLY 42/6.

METERS

BRAND NEW, MOVING COIL, FLUSH MOUNTING
1 mA. 2jin. square, 15/-; 5 mA. 2in. square, 7/6; 100 mA. 2jin. round, 12/6; 500 mA. 2jin. round, 12/6; 20 amp. 2in. round, 7/6; 40 amp. 2in. round, 7/6; 500 mA. thermo couple 2in. square or round, 5/-, or 3 for 13/6; 30-0-30 amp. moving iron, car type, 5/-.

POWER UNIT TYPE 3

Made for use with the R.1132A, this is a standard rack mounting job to match the receiver, and is for 200/250 v. 50-cycle mains with outputs of 250 v. D.C. 100 mA., and 6.3 v. 4 amp. Fitted with H.T. current meter and voltmeter, this is a first-class unit, and can be used for a variety of receivers. Used, but tested working before despatch, ONLY 90/- (carriage, etc., 5/-). Connecting Cable with Jones Plugs for receiver and power unit, 10/-.

AMPLIFIER A1135A Complete with 3 valves, 1 each EL32, EK32, EBC33. A handy little unit for conversion or breakdown. ONLY 17/6 (postage etc., 2/6).

TR1196 TRANSMITTER SECTION. In perfect condition, less valves. ONLY 12/6 (postage, etc., 2/6).

OSMOR H.O. COIL PACK. The 3 wave superhet pack recommended for the TR1196 Receiver conversion. ONLY 48/- 1196 conversion data supplied with coil pack, or separately 1/-, post paid

500 KCS. CRYSTALS. Standard 2-pin mounting. Ex. new equipment and perfect. ONLY 15/- (postage, etc., 1/-)

159 RECEIVER UNIT. Contains 1 each valve, types EF50, EA50, SP61, RL37 and 24 v. selector switch. ONLY 12/6.

VACUUM PUMPS. For Handymen and Model Makers. Ex-R.A.F. Type B3-Mk. III, made by Romec. BRAND NEW IN MAKER'S CARTONS, ONLY 15/- (post 2/-).

TRANSFORMERS. Manufactured to our specification and fully guaranteed. Upright mounting, fully shrouded, normal primaries.

425 v.-0-425 v. 250 mA., 6.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a., 50/-.

350 v.-0-350 v. 160 mA., 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a., 42/6.

350 v.-0-350 v. 150 mA., 6.3 v. 5 a., 5 v. 3 a., 32/6.

250 v.-0-250 v. 100 mA., 6.3 v. 6 a., 5 v. 3 a., 32/6.

Please add 2/- per transformer postage.

TRANSFORMERS, FILAMENT. 6.3 v. 2 a., 7/6; 6.3 v. 3 a., 10/6 (postage 1/-).

TRANSFORMERS, EHT. Upright mounting.

EHT for VCR97 Tube 2,500 v. 5 mA. 2 v.-0-2 v. 1.1 a., 2 v.-0-2 v. 2 a., 37/6.

EHT 5,500 v. 5 mA., 2 v. 1 a., 72/6.

EHT 7,000 v. 5 mA., 2 v. 1 a., 82/6.

EHT 7,000 v. 5 mA., 4 v. 1 a., 82/6.

Please add 2/- per transformer postage.

TRANSFORMERS, EX-W.D. AND ADMIRALTY, built to more than 50 per cent. safety factor with normal A.C. mains primaries. All brand new and unused, 330-0-330 v. 100 mA. 4 v. 3 a., 22/6.

E.H.T., 1,400 v. 2 mA., 520 v. 10 mA. 300 v. 10 mA., 2 v. 1.5 amp., 21/-.

L.T. 6.3 v. 7.7 amp., 4.2 v. 2.5 amp., 4 v. 1 amp., 19/6.

L.T. 4 v. 20 amp. C.T., 30/-.

Please add 2/6 per transformer postage.

INTERNATIONAL OCTAL PLUG Fits into I.O. valveholder, 2/- (post 3d.).

GANGED POTENTIOMETERS. Double 50K and double 1 meg., 7/6 each.

CERAMIC 2-WAY 3-BANK SWITCHES, 7/6 each.

P.M. SPEAKERS. 6jin. ROLA with transformer 17/6, 10in. LECTRONA with transformer 27/6.

GOODMANS, less transformer, 15 ohms speech coil, 99/6. ALL SPEAKERS BRAND NEW IN MAKER'S CARTONS.

Postage 2/- each please.

U.E.I. CORPORATION

Cash with order please, and print name and address clearly

Radio Corner, 138 Gray's Inn Road, London, W.C.1. Phone: TERMINUS 7937

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross;

AMOUNTS GIVEN FOR CARRIAGE REFER TO MAINLAND ONLY.

ENAMELLED COPPER WIRE **ØB REELS.**
 14 S.W.G./1/4 30 S.W.G./2/2
 16 S.W.G./1/4 32 S.W.G./2/3
 18 S.W.G./1/6 34 S.W.G./2/4
 20 S.W.G./1/7 36 S.W.G./2/6
 22 S.W.G./1/8 38 S.W.G./2/8
 24 S.W.G./1/10 40 S.W.G./2/11
 26 S.W.G./1/10 44 S.W.G./3/3
 28 S.W.G./2/-

J.B. DRIVES, ETC.
 SLS Spin Wheel Drive, 27/6.
 Airplane Drive, 13/-.
 Full Vision Drive, 13/-.
 Square Plane Drive, 12/9.
 SLS RV Drive, 26/6.
 Send for catalogue of drives, condensers, etc.

SPECIAL PURPOSE VALVES.
 EF8, 6/6; 6G6G, 6/6; 9004, 6/3;
 VR136, 7/-; VR66, 3/9; VU120A,
 3/6; 9002, 6/3; VR53, 7/6; VR91,
 6/-; 807, 8/-; 5Z3, 8/6; 6Y6G,
 8/-; 955, 4/-; TTL1, 6/6; VR116,
 4/-; VR56, 7/-; 954, 2/-; CV71,
 1/-; VR137, 5/-; VR55, 7/3;
 VT105, 4/-; PT16, 10/-; 6SA7,
 9/-; ATP4, 6/9; VU111, 3/6;
 9001, 6/3; VU39, 8/6; VR65A,
 3/6; 956, 3/6; 9003, 6/3; 2X3,
 5/8; VR65, 3/9; 6BS7, 8/-;
 1ASGT, 7/6; 6ST7, 8/-; 7Q7, 8/6.
 220V8G, 6/9.

BURGESS MICRO SWITCH.
 Ball type switch. Type 60/1910.
 Price 3/6 each.

VARNISHED COTTON SLEEVING
 1 M.M. 1/6 doz. yds.

INDICATOR UNIT, 63/-.
 Type 255, Case size 17 1/2 x 13 1/2 x 1 1/2 in.
 Complete with VOR5170.
 Brand new, latest type panels,
 dozens of resistors and condensers.
 Less valves. Carriage 7/6.

LOUDSPEAKER UNITS
 3in. Plessey Round Type for
 Portables..... 12/9
 Elac 3 1/2 in. square type. 2 to
 3 Ω..... 13/6
 5in. Units by Elac..... 12/3
 Truvox 6 1/2 in. Water Speaker,
 only 1 1/2 in. deep..... 20/-
 8in. Units by Plessey and B. &
 A..... 15/-
 Lectra 10 in., 2 to 3 Ω..... 16/6
 Rola/Celestion, 10 in..... 25/6
 12 in. Truvox BX11 Light-
 weight..... 49/6
 Extension Loudspeaker in
 mottled bakelite case, suitable
 for bedrooms or kitchen-
 ettes..... 19/6
 Plessey Mains Energised 8in.
 Unit, 1,500 Field..... 21/-

SOLDERING IRONS
 964 Solon oval bit type, 19/- each.
 968 Solon pencil bit type, 19/- each.

GOLDENING PICKUP HEADS
 Pickup head Type No. 112 (2,000
 ohms), complete with lead. Price,
 20/- each.

**FOR BUILDING—T.R.F. OR SUPERHET,
 THIS IS THE
 MOST
 POPULAR
 CABINET ON
 SALE TODAY.**



Complete with drilled
 chassis, dial, back plate,
 pointer, dial drive and
 drum, etc. Price 27/6.
 Post 2/-.

VCR97 6 1/2 in. CATHODE RAY TUBE
 Complete with case and screen, 29/9
 each. Packing and post 3/-.

MTL Primary 0-210-230-250 v.
 Secondary. 250-0-250 v. 80 m.a.
 6.3 v. 4 amps., 5 v. 2 amps., with
 taps at 4 v. on filament winding.
 Price, 17/6 each.

MT2. Primary 0-210-230-250 v.
 Secondary. 250-0-250 v. 80 m.a.
 6.3 v. 4 amps., 5 v. 2 amps. Both
 filament windings tapped 4 v.
 Price, 17/6 each.

MT3. 30 volt 2 amp. tappings as
 follows: 3, 4, 5, 6, 8, 9, 10, 12, 15, 18,
 20, 24 v. 17/6 each.

MOULDED MICA CONDENSERS
 All wire ends. .0001, .0003, .0004,
 .0005, .01, .001, .005, .0027, .0008,
 .00005, .003, 4/6 each.

EK-GOVERNMENT VOL. CONTROLS
 500 600 Double 1500 10K 20K 25K
 50K 100K 150K 200K, 1 meg.
 1/2 meg. 1 meg. 2 meg., all 1/2 ea.

**HALF WAVE 1 M/A PENCIL
 RECTIFIERS**
 K3/25 665V..... 5/8
 K3/40 1KV..... 7/6
 K3/45 1.140KV..... 8/2
 K3/50 1.260KV..... 8/8
 K3/60 1.5KV..... 9/8
 K3/100 2.550 KV..... 14/8

STANDARD S.T.C. RECTIFIERS
 RM1 125V 60 m/a 3/11 each
 RM2 125V 80 m/a 4/3 each
 RM3 125V 100 m/a 6/- each
 RM4 250V 250 m/a 16/- each
 Standard cartridge fuses, 1 amp.,
 1 amp., 1 1/2 amp., 2 amp. and 3 amp.,
 3d. each.
 Bulgin Toggle Switch DPDT, 2/- ea.
 Bulgin Toggle Switch DPST, 2/3 ea.
 Extension Speaker Vol. Control,
 1/3 each.
 44 Variable Resistors suitable for
 train sets, etc., 5/- each.
 Welwyn 50K Pre-Set Carbon Con-
 trols, 1/9 each.
 Throat Microphones, 2 in a box, 1/8
 box.
 G.P.O. Jack Plugs, 1/3 each.
 Block Condenser 4 mfd. 500 v.
 Flying Leads, 1/6 each.
 T.V. Coil Formers, 1 in., 9d. each;
 1 1/2 in., 7d. each.

Microphone Transformer, 60 to 1
 Ratio, 1/6 each.
 Intervalve Transformer, 1/- each.
 WHANDA wire and cable stripper
 Retail price 15/- each. Our price
 5/- each.
 T.R.F. Switch, 1/- each.
 Crystal Diodes, wire ends, 1/8 each.
 10 x 16 mfd. 350 v. Can type, 2/9
 each.
 Octal Rectifiers 12 v. 3 A., 13/9 ea.
 Octal and British screened valve
 caps, 3d. each.
 Standard Iron Elements, 450 watts,
 1/8 each.
 H.M.V. Elements, 3/- each.
 Hydrometers, brand new in wooden
 case, 3/6 each.

FILAMENT TRANSFORMERS. All
 220 to 240 v. input.
 2 volts 1 amp. 4/6
 2 volts 3 amps. 7/9
 4 volts 1 amp. 5/-
 4 volts 3 amps. 10/-
 5 volts 2 amps. 10/-
 6.3 volts 1 1/2 amps. 6/-
 6.3 volts 1 amp. 5/-
 6.3 volts 3 amps. 9/-



LOUDSPEAKER CABINETS

Available for 6 1/2 in. and 8 in. speaker units. Polished walnut
 finish. A very attractive cabinet at quarter of today's prices
 Price 6 1/2 in. Type Cabinet, 15/6 each.
 Price 8 in. Type Cabinet, 19/6 each.

**★ REPAIR YOUR OWN
 LOUDSPEAKERS**

Speaker Cone replacements available as follows.
 CASEZ 6in. Rola 5Z types, and other midgets with
 1/2 in. pole pieces..... 4/- each
 CASEP 8in. Philco R & A..... 4/6 each
 CASEZ. Rola 8Z New Plessey. This cone will suit
 most modern receivers with an 8in. Speaker.... 5/- each
 CASEZ 6 1/2 in. Rola 6Z..... 4/6 each
 CASEP, Philco, R & A..... 5/- each

RECEIVER 1132A
 Contains EK32; 4 EF39; 6H6; 6J5;
 3 SP61; P61 in good condition. Fitted with
 tuning meter. Slow motion drive calibrated
 dial complete with circuit diagram. 49/6
 each. Carriage and packing 7/6.



“SWAN” RADIO CABINET

Build a Radio in this up-to-date Cabinet.
 A modern looking Radio Cabinet complete with drilled
 chassis; dial drive and drum; back plate; dial; spring
 pointer; size 16 1/2 in. x 11 1/2 in. x 6 in. Price £1/16/6.
 Post and Packing 2/-.

We can supply a circuit diagram with all instructions for
 constructing a 3 valve plus metal rectifier T.R.F. receiver to
 operate on Long and Medium wavebands for 1/6.
 The complete kit can be supplied for 28/6/- Plus Packing
 and Post 2/6.

HAND MICROPHONE BY “REGENT”
 complete with screened lead and plug—Crystal
 insert, nickel chrome plated head, listed at
 2 gns. Our price, 21/- each.

ENGRAVED KNOBS
 1 1/2 in. dia. for 1/2 in. spindles, available Cream or Brown as
 follows:—“Focus,” “Contrast,” “Brilliance,” “Brightness,”
 “Brilliance On/Off,” “Wavechange,” “On/Off,” “Tuning,”
 “Volume,” “S.M.L. Gram,” “Tone,” “Vol On/Off,” “Radio-
 Gram,” “Bass,” “Treble,” “Record-Play.” Price 1/6 each.
 Plain knobs to match 1/- each.

BULLDOG CHARGER CLIPS. 8in
 long, 6d. each.

**MOULDED BAKELITE CASE CON-
 DENSERS.**
 .001 mfd. 4 Kv..... 1/- ea.
 .01 mfd. 4 Kv..... 1/6 ea.
 .25 mfd. 800 v..... 1/3 ea.
 .1 mfd. 1,000 v..... 1/- ea.

SCREENED MICROPHONE CABLE,
 with outer P.V.C., 7/0076, 1/- yd.
 .00035 MFD. 2-GANG CONDENSER,
 complete with trimmers and dust
 cover, 8/3 ea.

DIAL BULBS.
 M.H.S. Types.
 6.3 v. 15 A..... 6d. ea.
 6.3 v. 3 A..... 8d. ea.
 M.B.O.T. Types.
 6 v. 3 A..... 5d. ea.
 6.5 v. 3 A..... 5d. ea.

30 AMP. ROTARY SWITCH, 4
 position, complete with knob, 4/-
 each.

HEADPHONES. Type CLR Low
 Resistance Headphones, 120 ohms
 7/6 pair. Type DHB A. Super
 Q-60 or 2-61 in. Pans-Pull, 13/9 pair.
 Headbands, Wide type, 1/9 ea.

ELECTRON TRANSFORMERS.
 Type LV9.
 Ratio 1/1.25 giving 25% boost on
 tube heater. Capacity between
 windings 16 pF. Secondary to frame,
 6 pF. Suitable for High Definition
 Receivers.
 LV9A 2 volts..... 12/6 ea.
 LV9C 6.3 volts..... 13/6 ea.
 LV12. A low capacity Heater
 Transformer with mains input and
 universal output, Suitable for use
 with all C.R.K. Tubes, in medium
 definition receivers. Input 0-220-240
 volts, Boost 1-Boost 2. Output
 0, 2, 4, 6.3, 7.3, 10, 13 volts Price
 22/9.
 O.P.4. Dual purpose 12-watt output
 Transformer. Primary tapped for
 240/6 or 2-61 in. Pans-Pull, 3
 Secondary, 3, 8, 15 ohms. 23/6 ea.

TUNGAR RECTIFIERS.
 Cat. No. 189048, 6 amps., 10/- ea.

AMERICAN CONDENSERS.
 1 mfd., 350 v., .01 mfd. 1,000 v.
 .01 mfd. 1,000 v., .02 mfd. 750 v.
 .05 mfd. 500 v. All 9/- doz.

MIDGET CAN CONDENSERS.
 8 mfd. 450 v., 1/11 ea.; 8 mfd.
 350 v., 1/11 ea.; 16 mfd. 350 v., 2/9
 ea.; 24 mfd. 350 v., 3/- ea.; 32 mfd.
 350v., 1/9 ea.; 32 mfd. 450v., 2/1ea.;
 16 x 16 mfd. 450 v., 4/6 ea.; 8-8 mfd.
 450 v., 4/- ea.; 250 mfd. 12 v., 2/3
 each.

WIRE END TYPE CONDENSERS.
 25 mfd. 25 v., 1/4 ea.; 50 mfd. 50 v.,
 1/9 ea.; 50 mfd. 12 v., 1/8 ea.;
 8 mfd. 450 v., 2/- ea.; 8 mfd. 500 v.,
 2/3 ea.; 16 mfd. 500 v., 3/3 ea.;
 20 mfd. 500 v., 3/6 ea.

STANDARD CAN CONDENSERS.
 16 x 8 x 8 mfd. 500 v. plug in type.
 4/9 ea.; 8 x 24 mfd. 350 v., 2/- ea.;
 32 x 8 mfd. 350 v., 3/9 ea.; 24 x 16
 mfd. 350 v., 4/6 ea.; 32 x 32 mfd
 450v., 6/9 ea.; 16 mfd. 400v., 3/3ea.;
 8 x 8 mfd. 350 v., 2/9 ea.; 52 x 32
 mfd. 350 v., 25 mfd. 25 v., 5/9 ea.;
 32 x 16 mfd. 350 v., 3/9 ea.; 20 x 20
 mfd. 500 v., 4/6; 16 x 8 mfd. 350 v.
 3/11 ea.; 12 x 4 mfd., 450v., 2/- ea.



CATALOGUE
 IS A MUST FOR EVERY
 CONSTRUCTOR.
 SEND FOR YOURS TO-DAY.

ALPHA RADIO SUPPLY CO.
 5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.

WHEN ORDERING PLEASE QUOTE “DEPT. W.W.”

FERGUSON RADIO CORPORATION LTD., requires ENGINEERS :-

ENFIELD FACTORY

Senior Engineers with initiative and sound technical background for work on a wide range of projects covering the Television, Radio and Communications field. Permanent posts for men able to carry responsibility in rapidly expanding departments offering exceptional promotion and long-term prospects.

Junior Engineers of ability for work on Development Projects offering a wide experience in Communications and Test Equipment Development with excellent prospects for advancement.

SPENNYMOOR FACTORY (County Durham)

Engineers with initiative and sound technical background to work on the development of Radio Receivers. Permanent posts for men able to carry responsibility in a rapidly expanding department offering good prospects.

Laboratories are well equipped and working conditions excellent. Successful applicants eligible for Company's Pension Scheme. Housing assistance considered in appropriate cases.

Applications specifying the post for which application is made and giving full particulars as to age, qualifications and experience, etc., to:—

**Employment Manager, FERGUSON RADIO CORPORATION LTD.
GREAT CAMBRIDGE ROAD, ENFIELD, MIDDLESEX**

G2AK

*This Month's
Bargains*

G2AK

TRIPLETT 400 Micro Amp. Basic Meter Unit, sealed for 8 ranges. New, boxed 32/6, post free.

GERMANIUM DIODES, B.T.H. 2/-; G.E.C., 2/6.

METERS. 2½in. Flush mounting M.C. 100 mA., 12/6 each; 2in. Flush Square 5 mA., 10/-; 4 amp. thermo., 5/-; 2½in. thermo. 0.2 a., 7/6; 2½in. 2in. Flush 0.15 a. thermo. Proj. 2½in., 7/6 each. 0.9 a. Hot wire, 5/-.

TEST METER. 7 ranges as follows: 1.5 v. 3 v. 150 v. 6 mA., 60 mA., 5,000 ohms, 25,000 ohms. 2½in. Dia. scale M.C. meter. Rotary selector switch. Black bakelite case, 6 x 4½ x 4½, fitted with removable lid, also provision for internal batts, ranges can be easily extended. Bargain Price 30/- plus 1/6 post.

SPECIAL OFFER, AR88 SPARES. Cabinets complete with base, feet and side strips, £4/15/- each. Pkg. and Carr. 5/- Set of 14 valves for "D" or "LF" model receivers, £5/10/-. Panel escutcheons 22/6 each. "D" type I.F.S., 12/6 each. Matching Speakers by R.C.A., fitted rubber feet and 6ft. lead, 65/-.

DEAF AID CRYSTAL MIKE UNITS 12/6 each, post 9d.

CRYSTAL HAND MICROPHONES. Complete with lead and plug. High Quality, very sensitive, chrome finish. List price 2 gns. Our price 25/-, few only.

CERAMIC SWITCHES, 2 bank, 2 pole, 4 way each bank, 6/-, post 9d.

SPECIAL TRANSFORMER OFFER. PRI. 115, 210, 240 v. SEC., 260/260 v. 100 mA., 6.3 v. 3 a., 6.3 v. 1 a. (for 6X5 Rec.) Universal Mounting. Limited Quantity, 17/6 each, post free.

SPECIAL VALVE OFFER. 83 MV Rectifiers, 10/-, 866A, 17/6 each, or 30/- pair. 807's, 10/- each or 17/6 pr. 931A, 45/-, 832, 35/-, 829B, 80/-, 813, £5.

NOISE LIMITERS. Plug-in type, no re-wiring required. 3 positions. Brand new in cartons. 15/- each, post 1/-. Carriage paid on all orders over £1 except where stated. Please include small amount for orders under £1.

Please print your name and address.

CHAS. H. YOUNG, G2AK

Mail orders to 102 HOLLOWAY HEAD, BIRMINGHAM I
Phone: MIDLAND 3254

All callers to 110 DALE END, BIRMINGHAM, 4
Phone: CENTRAL 1635

1 KW TELEGRAPH TRANSMITTERS. Two HF 300's output. Operation 3.5 mc. to 16 mc.

BC610 TRANSMITTERS with speech amplifier, aerial tuning unit, etc. Brand new.

RCA TRANSMITTERS. Type ET-4336. Complete with original speech amplifier, crystal multiplier and VFO units. Unused and re-conditioned. Can be supplied with very large quantity of spares.

RCA TRANSMITTERS. Type ET-4332 modified by R.A.F. for use on crystal or master oscillator. Complete with speech amplifier.

MAGNETO 10 LINE U.C. TELEPHONE SWITCH-BOARDS (complete).

NO. 33 TRANSMITTERS.

A.R.88D's, A.R.88LF's, A.R.77's, S27's, HRO, R.109 and others.

SCR510's complete with Power Pack and telescopic aerial.

All above items in excellent working condition. Working demonstration upon request.

SPARES A large selection available for SCR399 (BC610), ET4336, SCR610, EE8 Telephones, and Teleprinters type 7B.

TX VALVES 805, 807, 813, 861, 866A, DET-16, 100TH and many others.

Large stock of Tx condensers, crystals and other components. Alignment and repair of communication receivers and all other short-wave equipment undertaken.

P.C.A. RADIO

New Address, Offices and Works:

BEAVOR LANE, HAMMERSMITH, LONDON, W.6

Telephone: RIV 8006

Best Buy at Britain's

BAND III TEST SET

TEST SET TYPE B.G.3 is a wavemeter made by R.F. Equipment for the Ministry and covers 160-220 Mc/s., having a 5 $\frac{1}{2}$ in. instrument type directly calibrated dial with vernier. A 5 Mc/s. crystal oscillator is incorporated for checking purposes. The instruction booklet states that the accuracy is better than 200 kc/s. (1/10th of 1 per cent). The instrument employs 4-VR91's (EF50) and 1-VR135 (UHF-triode). It is housed in a strongly made, handsome wooden case, size 9in. x 13in. x 12 $\frac{1}{2}$ in. high, with hinged lid, which when opened reveals a black crackle instrument panel with controls, terminals, indicating lamp, etc. The oscillator itself is contained in a completely screened compartment. The circuit diagram, giving full component values, is engraved on a metal plate fixed to the base of the chassis: The instrument requires a power supply of 6.3 volts at 1.5 Amps, and 120 volts H.T. at 12 mA. which may be provided either from batteries (not provided) or from mains power pack which can be housed in the cabinet. Supplied complete with five valves, 5 Mc/s. crystal, circuit diagram and instruction booklet, in tip-top condition for only 59/6 plus 5/6 carriage.

COMMUNICATION RECEIVERS

CALLERS—PLEASE NOTE that we have a good selection of American and other types of communication receivers, including Hallcrafters, HRO, R.M.E., etc. in stock. All thoroughly reconditioned, re-aligned and in perfect working order, which we will be pleased to demonstrate at any time.

COMMUNICATION RECEIVER RI155 for world-wide reception. Can be heard at any time during shop hours. Air tested prior to despatch. Brand new at £11/19/6. A few slightly used at £7/19/6.

TRAWLER BAND. RI155N, with super slow motion drive, available at £17/19/6. Carriage in original transit cases 10/6 extra on all models. Send 1/3 for full details and circuit.

A.C. MAINS POWER PACK OUTPUT STAGE enables the RI155 to be used to operate speaker from 200/250 volts A.C. without ANY MODIFICATIONS WHATSOEVER. All our Power Packs have heavy duty transformers, are complete with leads and Jones plugs and are guaranteed for 6 months.

TYPE A in smart black metal case size 8 $\frac{1}{2}$ in. x 4 $\frac{1}{2}$ in. x 6 $\frac{1}{2}$ in. Less speaker. Price £4/10/- plus 3/6 carr.

TYPE B with built in speaker in black metal case size 13 $\frac{1}{2}$ in. x 5 $\frac{1}{2}$ in. x 7 $\frac{1}{2}$ in. Price £5/5/- plus 3/6 carr.

TYPE C with an 8in. R. & A. speaker in specially designed, beautiful black crackle cabinet to match the receiver. Size 11 $\frac{1}{2}$ in. x 10 $\frac{1}{2}$ in. x 6in. A de Luxe job. Price £6/10/- plus 3/6 carr.

U.S.A. DYNAMOTOR. 12 volts D.C. input, 250 volts 60 mA. output. Weight 2 $\frac{1}{2}$ lbs. Size 4 $\frac{1}{2}$ in. x 3in. diameter. Ideal for car radio, mobile amplifiers, small transmitters, etc. All tested prior to despatch. ONLY 22/6, post paid.

POLICE, FIRE, WROTHAM

THE RI132A receiver covers 100-124 Mc/s with variable tuning. Very easily altered to other frequencies. Complete with all 11 valves. Requires only 250 volts and 6.3 volts when it is ready to operate. Complete circuit supplied. Only 45/- plus 7/6 carriage. **BRAND NEW.** Will operate from our standard RI155 power pack using special lead, price 10/- extra.

POWER PACK NO. 3. Standard 19in. rack-mounted power packs for 200/250 volts mains operation. Paper smoothing, two heavy duty chokes, VU39 rectifier. Output 250 volts D.C. 100 mA., 6.3 volts 4 amps. Two types: Mark I with H.T. current meter at £4/4/-; Mark II with H.T. current and voltmeters at £4/10/-, carriage 5/-. Suitable for use with P48, RI132, RI481, RI392, RI155, etc. Lead for any specified set with Jones plugs, 10/- extra. All power packs guaranteed in working order.

TRANSFORMER BARGAINS. 350-5-350 volts at 180 mA., 6.3 v. 5 Amps and 5 v. 3 Amps. Standard 200/250 volt 50 cycle screened primary. Size 4in. x 4in. x 5in. Brand new and unused 29/6 plus 2/6 post. Filament Transformers—Standard tapped primary, two types—Type "A" 12 volts 1 $\frac{1}{2}$ Amps., 6.3 volts 1 $\frac{1}{2}$ Amps. Type "B" 12 volts 1 $\frac{1}{2}$ Amps., 4 volts 1 $\frac{1}{2}$ Amps. Either type 7/6 each.

H.R.O. 6 VOLT VIBRATOR PACK gives 165 volts 80 mA. smoothed D.C. Uses Mallory vibrator, 6X5, heavy duty smoothing choke, etc. In black crackle cabinet size 7in. x 7in. x 6in. Brand new only 29/6.

C.R. TUBES for G.E.C. "Miniscope" price 35/- each. New and Boxed.

VARIACS. semi-variable. Rated .8 kVA, oil filled. Adjustable for 30 volts above and below the mains input. Price £5.

METER BARGAINS

UNIVERSAL AVOMETERS MODEL 40—very little used, thoroughly checked and tested. First-class multi-range test meter for ONLY £9/19/6.

1 Milli-amp. 2 $\frac{1}{2}$ in. square panel mtg., 15/-.
5 Milli-amp. M/C. 2 $\frac{1}{2}$ in. square panel mtg., 7/6
200 Milli-amp. M/C. 2 $\frac{1}{2}$ in. diameter flush panel mtg., 10/6.

20 Amps. 2 $\frac{1}{2}$ in. diameter M/coil, 7/6.
20 Volts 2in. square panel mtg., M/coil, 7/6.
500 Milli-amps. Thermo-couple 2in. square panel mtg., 5/-.

All the above meters are brand new and boxed. **G.E.C. 1 mA. METER RECTIFIERS, BRAND NEW AT ONLY 11/6.**

3,500 volt moving coil 3 $\frac{1}{2}$ in. projection type at the **SPECIAL BARGAIN** price of 15/-.

MICRO-AMP. METERS

100 MICRO-AMP. METER. 2 $\frac{1}{2}$ in. barrel, 3 $\frac{1}{2}$ in. flange, panel mounting. Scaled 0-1500 in 15 clear divisions. These meters have just arrived and are **BRAND NEW** in original maker's cartons. Now in short supply, they are a real bargain at 42/6 each.

50 MICRO-AMP. METER. 2 $\frac{1}{2}$ in. barrel, 3 $\frac{1}{2}$ in. flange, panel mounting. Scaled 0-100 in 50 equal divisions. Price ONLY £3/10/- each.

VALVE BARGAINS

New and in original boxes. At 7/6: 6AG5, VR53, VR56, 6CSMet, TT11, 6SH7Met; At 5/-: 2X2; At 2/6: RK34, EI148, 954.

New Ex unfts. VR91Sylvania, 8/6; VR91, 6/-; VR65, 3/6; VR65A, 3/6; VR65A, 3/6; VT501 (TT11), 5/-; VR52, 7/6; 807, 7/6; CV6, VR78, VR92 at 1/6 each or 15/- per dozen. Soiled, tested. VR65, VR65A at 2/6; VR91 at 3/3.

METAL RECTIFIERS

Selenium 230 volts 60 mA. at 5/-; 300 volts 100 mA. at 7/6; RM2 at 4/3 or two for 8/-; RM4 at 17/-; Selenium Full Wave Bridge 6 or 12 volts—1 amp. at 7/6; 2 amp. at 11/3; 3 amp. at 12/6; 4 amp. at 15/-. Heavy duty selenium rectifier, square fins, size 8 $\frac{1}{2}$ in. x 4in. x 4in. Two units in full wave bridge give 48 volts 10 Amps. D.C. Brand new at £4 per pair.

COLLARD THREE SPEED AUTO CHANGER 3RC521 complete with two separate crystal heads. **BRAND NEW AND BOXED.** Only £9/19/6.


GOODMANS AND B.T.H. 12in. 15 watt 15 ohm heavy duty speakers in stock. Brand new and boxed at bargain prices for callers.

PUSH PULL OUTPUT TRANSFORMERS 15 watts, push-pull 6V6's to 15 ohms. A bargain for ONLY 7/6 each.

HEAVY DUTY CHOKES. 5 Hy 300 mA., 50 ohms, size 3in. x 4in. x 4 $\frac{1}{2}$ in. Potted type, chassis mtd. Price 12/6. 30 Hy. 150 mA., 300 ohms, universal mounting, size 4in. x 3in. x 2 $\frac{1}{2}$ in. Price 10/6. 5 Hy. 200 mA. 120 ohms, chassis mounting, size 2 $\frac{1}{2}$ in. x 2 $\frac{1}{2}$ in. x 3in. Price 7/6. These chokes are all brand new and boxed.

INDICATOR UNIT 182A

contains 3 EF50, 1 5U4G, 4 SP61 and a 6 $\frac{1}{2}$ in. C.R.T. type VCR517. This tube will replace the VCR97 without any alteration, is completely free from cut-off and has a more pleasant tube colour. Contains in addition a very large assortment of pots, resistors, condensers, etc. Tubes demonstrated. Supplied **BRAND NEW** (less relay) for only 67/6, plus 7/6 carriage in original transit cases. **Original circuit supplied FREE** with each order, or 1/6 separately.

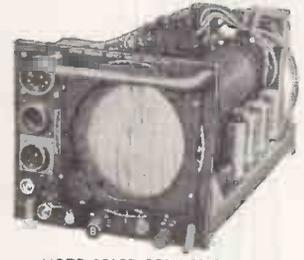

NOTE PRICE REDUCTION

45 Mc/s **PYE STRIP.** Vision unit for London frequency, complete with 6 EF50 and 1 EA50. Circuit provided. Price £3/10/-, plus 2/6 carriage. **TV PRE-AMP.** Uses 2 EF50's and tunes to 45 Mc/s. Easily altered to other frequencies. With valves, 19/6, less valves, 10/-, post 1/- extra. **E.H.T. TRANSFORMER** for the VCR97, etc. Mains input. Output 2,500 volts, 4 volts 2 amps. 2-0-2 volts 2 amps. Fully guaranteed at 35/- each, plus 1/- post.

CO-AXIAL CABLE. Brand new 70/80 ohm. with STRANDED inner conductor. Not ex-Govt. Price 9d. per yard. Minimum per post, 7/6 per doz. yards.

HEAVY DUTY twin circular polythene cable, weatherproof, suitable for extension mains lead, etc. Price 9d. per yard. Minimum per post 8/6 per doz. yards. **SPECIAL OFFER** of 100 yard coil for 50/-, plus 3/6 carriage.

TELEVISION RECTIFIERS 3 $\frac{1}{2}$ in. dia., 235 volts A.C. input. Type A—Output 300 mA., price 13/6. Type B—Output 380 mA., price 14/6. These are **BRAND NEW.** Either type plus 1/- postage.

COIL PACKS. We have a bargain line in S. M. and L. wave packs for 465 kc. I.F. Single hole fixing. Price 14/6, BUT regret **CALLERS ONLY** this item.

I.F. TRANSFORMERS iron dust core, 465 kc/s. brand new, manufacturer's surplus, ONLY 6/9 per pair.

TYPE 12 TRANSMITTER. Mains operated transmitter covering 1.2-17.5 Mc/s in four bands, crystal or V.F.O. Size 24in. x 12 $\frac{1}{2}$ in. x 17 $\frac{1}{2}$ in., weight 134 lbs. Complete with all valves, ready for operation. In first class condition and tested before despatch, with circuit and instructions ONLY £16/16/-, plus 14/- carr. A few, soiled, for callers only at bargain prices.

STANDARD TRANSFORMERS

Transformers of current manufacture. Two types, both standard tapped primaries. Universal mounting. (1) 350-0-350 volts 80 mA., 0-4-6.3 volts 4 amps., 0-4-5 volts 2 amps. (2) 250-0-250 volts 80 mA., 0-4-6.3 volts 4 amps., 0-4-5 volts 2 amps. Both these transformers are new and boxed, fully guaranteed at 18/- each, post paid.

30 VOLT TRANSFORMER standard primary. Secondary 30 volts 2 amps., tapped to give 3, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 volts. Has countless uses. Price 17/6.

METAL RECTIFIER, 12 volt 2 amp. full wave bridge type. Suitable for use with the above transformer. Price 11/3.

CHARLES BRITAIN (Radio) Ltd.

11 UPPER SAINT MARTIN'S LANE,
LONDON, W.C.2

One minute from Leicester Sq. Sta. (up Cranbourn St.) TEMple Bar 0545
Shop Hours: 9-6 p.m. (9-1 p.m. Thursday) Open all day Saturday



G.W. SMITH & CO.

(RADIO) LIMITED

V.H.F. Wavemeters. Type 4. Ref. AM.107/534, Cavity Tuned, complete with VU39 4 volt rectifier, SP61, VR92, C.V.51 Magic Eye Tuner, Brand New in sealed boxes. 39/6 each.

Power Packs, Type S441, B, Input voltage 200/250, 50 cycles A.C. Outputs 300 volts 200 mA., L.T. 12 Volt 3 Amp., also separate 12 volt 1 amp. supply operating built in Londex overload relay, with 5U4G valve. Supplied in grey mottled cabinet size 13½ in. x 7½ in. x 6½ in., 62/6 each.

Vibrator Power Supply Units, 6 volt input, Output 180 volt 40 mA., using Metal rectifier, size 7½ in. x 5½ in. x 3 in., 22/6 each. P24 Camera Control Boxes. Type 35 No. 20, Brand new, 27/6 each.

A.C. Mains Transformers, Ex-Admiralty, input voltage 100/250 A.C. at 50 cycles, Outputs 670 x 670 volt at 200 mA., 6.3 volt 4 amp., 5 volt 3 amp. 49/6 each.

P.O. Automatic Telephone Circuit Diallers, Type 1, 25 bank, Type 2, 50 bank, 12/6 each. These precision built units have hundreds of potential uses each one being fitted with clockwork control motor.

2 Volt Accumulators, Brand New. Capacity 3 Amp. Hours, size 4½ in. x 1½ in. x 1½ in. 3/6 each.

R.1155 2 Speed Slow Motion Motor Drives. "A" type with double knobs, 4/6 each.

Amplifier Cabinets, Ex-Well Known Manufacturer, sloping desk type, well constructed with ventilated cover, chassis drilled for 5, 1/0 holders, size 13 in. x 9 in. x 7 in. Sprayed attractive yellow. 15/6 each.

R.1155 Receivers, used models, aerial tested, and in perfect working order, complete with valves. 27/19/6 each.

A.C. Voltmeters. BSI Grade, reading 0-300 volts at 50 cycles, 3½ in. panel mounting, supplied complete with leads and case. 39/6 each.

Transmitter Units, Type 39. Covering V.H.F. frequencies, complete with A.C. mains 230 volt 50 cycle E.H.T. and L.T. supply, condition as new at 25/19/6 each.

Uniselector Switches. 4 Bank double wiper 32/6 each; ditto 8 Bank 45/6 each.

Handsets. Standard P.O. telephone type 12/6 each. **Ceramic Switches.** 3 pole 4 way 4 bank, standard size wafer, 10/6 each.

American Rotary Transformers. 12 volts D.C. input. Output 255 volt at 65 M/A. Size 4½ in. x 2½ in. For Car Radio Operation. Also suitable for running Electric Shavers from your car supply, 22/6 each. Brand new.

Muirhead Switches. Precision built. 8 pole 2 way. Key switch action, brand new, boxed, heavy contacts, 4/6 each.

Ceramic Transmitter Switches. With extra heavy duty silver-plated contacts, 3 bank single pole 6 way, spacing between contacts 1 in. spacing between wafers 1½ in. and 5 in., 9/6 each.

Venner Hour Meters for Time Recording, capacity zero-10,000 hours, incorporating synchronous 200/250 volt 50 cycle motor. For component and instrument life check. Brand new, 69/6 each. **Mains Isolation Transformers for industrial purposes.** 230 volt A.C. 50 cycles input. Output 230 volt 50 cycle 1,000 watts, supplied complete in heavy duty metal case, size 13 in. x 10½ in. x 8 in. Price 26/10/6.

Smoothing Chokes. Heavy duty. 20 Henry 300 M/A., 2,000 volt insulation test. Admiralty rating will pass 500 M/A., 17/6 each.

Mains Transformers. 230 volt Primary, Secondary 500 x 500 at 170 M/A., 4 volt 4 amp. C.T. W.D. rating insulation test 3,000 volts. Ample space for additional 6.3 winding if required, 22/6.

H.R.O. 6 volt Vibrator Power Packs. Output 165 volt 80 M/A., 6.3 volt at 3 amps., 6 x 5 rectifier. Choke condensers smoothed, complete in self-contained crackle cabinet size 7 in. x 7½ in. x 6 in., battery leads with croc. clips supplied. Brand new, 29/6.

Ceramic Switches. Standard spacing, 4 pole 3 way 3 bank. Special price 6/6 each. Brand new and boxed.

Smoothing Chokes. Ex-W.D. 15 Henries at 275 M/A. Ministry rating, resistance 25 ohms, 10/6 each.

Meter Switches. Standard Yaxley Wafer Type, 8 bank, single pole 9 way, 11 way or 12 way. Size 2½ in. diameter, switch length 5½ in. plus spindle, 2½ in. Price 7/6 each.

A.C. Mains Transformers, 0/230 to 250 volt 50 cycle input. Outputs 250 volts h/w 60 M/A., 6.3 volt 1½ amps. Size 3 in. x 2½ in. x 2½ in., with fly leads, brand new, 8/6 each.

Microamp Meters. 0-100 Microamps. 2½ in. Flush Panel Mounting scaled 0-1,500 yards. Brand new and boxed. 42/6 each

Rotary Convertors. 24 volt D.C. input. Output 230 volt A.C. mains 50 cycle at 100 watts. 92/6 each, ditto 12 volt input, 102/6.

Mains Transformers. Input: voltages 200/250 at 50 cycle. Output 350 x 350 volt 180 M/A. Lt. Windings 6.3 volt, 5 amp., 5 volt 3 amp. Brand new. Ex-W.D. 29/6 each.

Charging Transformers. 200/250 volt at 50 cycle. Outputs 14 volt 1½ amps also 4 volt 1½ amps. Brand new, 7/6 each.

Chokes. Heavy Duty Ex-W.D. 20 Henry 120 M/A., size 3 in. x 4 in. x 2½ in., 10/6 each.

Please print your name and address clearly, also include postage or carriage on all items.
Hours of Business: 9 a.m.-6 p.m., excluding Thursday, 1 p.m. Open all day Saturday.

G. W. SMITH & CO., (RADIO) LTD.
3-34 Lisle Street, London, W.C.2

Telephone: Gerrard 8204/9155

Nearest Tube Stations: Piccadilly or Leicester Square.

MIDLAND INSTRUMENT CO.

VENNER 24-VOLT TIME DELAY SWITCHES, consists of a high-grade clockwork motor with external wind, 2 electro-magnets, 5-pole cam operated contacts, in smart metal cases size 3½ in. x 2½ in. x 2½ in., fitted 4-way terminal block, brand new boxed, cost 22s, our price 10/6, post 1/6.

PROJECTION UNITS, consist of an enclosed lamphouse, fitted 24-v. 15-watt lamp, highly polished reflector, attached mount containing 2 lenses, one a concave/convex, the other a Dallmeier bloomed "Achromatic" 40 mm. dia., 3½ in. focal length lens, taken from new equipment, 10/6, post and packing 1/6.

CHARGER KITS, consists of a G.E.C. 12-v. 1½-amp. full-wave bridge rectifier, with a Douglas 200/250-v. transformer, specially designed for this rectifier, giving the correct A.C. input voltages, to charge a 2, 6 or 12-v. battery at 1½ amps., 2 brand new components, complete with circuit diagram, and Instructions, 25/6, post 1/6.

AIR COMPRESSORS, or vacuum pumps, Romec rotary vane type, develops constant 40/50-lb. sq. in. pressure, fitted 2 in. long ½ in. dia. splined shaft, size (less shaft) 6 in. long, 4 in. by 4 in. dia., brand new in sealed cartons, 20/6, post 2/6.

TELEPHONE SETS, consists of 2 combined receivers and microphones, provides perfect 2-way communication (up to 1-mile with extra flex) self-energised, no battery required, 20-ft. connecting flex, complete ready for use, brand new boxed, 12/6, post 1/6.

VARIABLE REOSTATS, wire wound on ceramic, laminated wiper, 50-ohms at 1-amp., easily altered to 12.5-ohms at 2-amps, new boxed, 5/6, post 1/6.

PLESSEY MOTORS, 200/250-v. A.C. mains shaded pole, as fitted to the 3-speed gram. units, size 3 in. x 3 in. x 2½ in., brand new boxed, 12/6, post 1/2.

BUZZERS, 3 to 6-v. high note, platinum contacts, knob note control, fraction of original cost, new, unused, 5/6, post 1/6.

ELECTRIC REV. COUNTERS, dial scaled 0-4,000 r.p.m., contains A.C. motor, permanent magnet slip drive to the hairpin loaded pointer, bakelite cases, flush panel mounting, new, unused, 5/6, post 1/2.

CROMPTON PARKINSON METERS, 4 in. scale, graduated 40-45-50-55-60 cycles, with sub-division, incorporates Westinghouse metal rectifier, flush panel mounting, brand new, boxed, 30/6, post and packing 2/6.

DETECTOR UNITS TYPE 66, a self-contained unit, fitted CV-271 (IT4 type) valve, various components, compartment to take a U2 cell, switch, etc., 7 in. long, 1½ in. dia., new, unused in rubber waterproof cases, 5/6, post 1/6.

SUPPRESSORS, car plug fitting, standard 15,000 ohms, for easier starting, T.V. and car radio suppression, brand new stock, current price 2/6 each, our price, set of 4, 3/6, post 3d., sealed cartons of 100, 62/6, post 1/6.

THERMOSTATS, close at low temperatures, adjust. 30-80 deg. F., ideal for green-houses, car heaters, frost warning, etc. 2/6, post 4d.

SWITCHBOXES, black mat finish alloy, size 3½ in. x 2½ in. x 2 in., fitted 2 Wylex 250 v. 10 amp. A.C. on/off toggle switches, new unused, 2/6, post 9d.

G.P.O. TYPE 3000 RELAYS, 100 plus 100-ohm balanced, 4-pole, 1-make, 2-break and changeover contacts, new, unused, 5/6, post 9d.

H.S. RELAYS, 145-ohm s.p.c.o. 2/6, post 6d. **IMPULSING MECHANISMS,** actuating switch, 22/24-v., 1/6, post 1/6. **BOSTIE CEMENT,** 1-lb. tubes, 1/6, post 7d.

EMPIRE TAPE, 1 in. wide, 50-yd. rolls, 2/6, post 9d. **SLYDLOCK FUSES,** 250 v. 15 amp., 1/6, post 3d. **TEST PRODS,** 6 in. long, fitted red and black flexible, 1/6 pair, post 4d.

THROAT MICROPHONES, electro-magnetic, boxes of 2 microphones, 1/6, post 4d. **TOGGLE SWITCHES,** 24-v. 20-amp. on/off, 1/6, post 3d.

GERMANIUM CRYSTALS, 2/-, post 3d. **CRYSTAL SET COILS,** med. and l-wave, with circuit, 2/6, post 3d. **BOMB COMPUTERS,** 40/-, carriage 10/-, Scott., 12/6, N.I.

UNIVERSAL SWITCHES, twin press-button, 250 v. 5 amp. A.C. boxed with circuits, 1/6, post 4d. **WIRE STRIPPERS,** usual tool shop price 15/-, our price, new, boxed, 5/6, post 6d. **ARROW SWITCHES,** 250 v. 25 amps., 4-way rotary, 3-heat and off, series parallel, 2/6, post 1/6. **PNEUMATIC DASHPOTS,** 3 in. long, ½ in. dia., plunger movement 2 in., 1/6, post 6d.

Many other bargains to offer - send 6d. for lists.
MIDLAND INSTRUMENT CO., MOORPOOL CIRCLE, BIRMINGHAM 17
Tel.: HAR 1308

PROOPS of KINGSTON



The only "walk-around" radio shop in Surrey

ACCUMULATOR CAPACITY TEST SETS

A.M. No. 5A/2181

For discharging at a controlled rate 2, 6, 12 and 24 volt batteries. Containing ammeter, voltmeter, watt/hour meter, variable resistance. Assembled in heavy cast case for wall fixing.

A vital necessity for any battery room. In fully guaranteed condition, plus carriage £15.

PROOPS BROS. LTD.

39, Cambridge Road, Kingston-on-Thames, Surrey
Tel.: KINGston 4614

CLOSED—1 O'CLOCK WEDNESDAY. OPEN—ALL DAY SATURDAY
Correspondence to: 119, Charlotte Street, London, W.1.

GARLAND BROS., Ltd.



The "Unitelex Prima" Tape Recorder

57 OR ON HIRE PURCHASE
GNS.

(£19/19/- Deposit. Balance by 6 monthly instalments of £7/3/- or 12 monthly instalments of £3/13/2.)

TAPE DECK: Truvox Mk. III. 3-motor Twin Track Two Speed (3½ in. per second and 7½ in. per second). **AMPLIFIER:** Unitelex PR3A. Valves EF40, 12AX7, EL41, EL41, EM34. Separate power pack with full-wave metal rectifier system for robustness and instantaneous brake operation. **CONTROLS:** Bass control (boost) operative on both record and playback; treble control (boost and cut) operative on playback; volume control. **INPUTS:** Low Gain 20mv. across 1 megohm, used for recording from Radio, Television and Gramophone. High Gain 100µV across 2 megohm, used for recording from microphone. **FREQUENCY RESPONSE:** 50 Cycles—10 Kc/s ± 3 db on recording. 30 Cycles—14 Kc/s ± 1 db on direct playback. **OUTPUT:** 4 watts. **L/SPEAKER:** High—Flux 10in. elliptical speaker—provision for feeding up to 2 extension speakers; switch for muting internal speaker if desired. **RECORD LEVEL INDICATION:** Magic eye. Direct Playback available for playing records from Gramophone unit or as direct microphone amplifier. A.C. Mains only, 200/250, 50 cycles. Supplied complete with microphone and tape. Weight 35 lbs. Dimensions: Height 18½ in., Width 17½ in., Maximum Depth 10 in. Send 2½d. stamp for illustrated brochure.

EXAMPLES OF OUR "EASY PAYMENTS" TERMS

ARTICLE	Cash Price	Deposit	6 monthly payments	12 monthly payments
T.V. Enlargers. 9in.	£2 10 0	16 8	6 2	—
T.V. Enlargers. 12in.	£3 10 0	£1 3 4	8 8	—
De Luxe T.V. Enlargers. 12in.	£3 15 0	£1 5 0	9 2	—
Bremi Microphone 7D	£3 15 0	£1 5 0	9 2	—
Tamsa R/P & Erase Head	£4 10 0	£1 10 0	10 9	—
Amplion Testmeter. 10 ranges A.C.-D.C.	£5 0 0	£1 13 4	12 3	—
Bremi Microphones IIA	£5 5 0	£1 15 0	12 10	—
Three 1,200ft. reels Scotch Boy Tape ...	£5 5 0	£1 15 0	12 10	—
Black & Decker ½ in. Universal Drill ...	£5 19 6	£2 0 0	14 3	7 4
Collaro AC514	£6 5 11	£2 2 0	15 1	7 10
Bremi Microphone 13U	£6 6 0	£2 2 0	15 1	7 10
Goodmans Axiom 101. Bin. L/Spkr.	£6 12 1	£2 4 1	15 9	8 1
Garland Amplifier AC11A	£6 12 6	£2 4 2	15 9	8 1
Collaro AC47	£6 13 4	£2 4 6	15 11	8 2
Wharfedale Golden CBS. 10in. Speaker	£8 6 7	£2 15 7	19 11	10 2
Goodmans Audiom 60 Speaker	£8 12 6	£2 17 6	£1 0 8	10 7
B.S.R. 3-speed single player. GU4	£9 5 0	£3 1 8	£1 2 2	11 4
Connoisseur Pick Up, 2 heads	£9 5 6	£3 1 10	£1 2 2	11 4
Leak Pre-amplifier	£9 9 0	£3 3 0	£1 2 7	11 7
Wharfedale W12/cs. 12in.	£9 15 0	£3 5 0	£1 3 4	11 11
Goodmans Axiom 150, Mk II	£10 5 6	£3 8 6	£1 4 7	12 7
Leak "Varislope" Pre-amplifier	£12 12 0	£4 4 0	£1 10 2	15 6
Garrard 3-speed Auto-changer. R.C.75A	£15 8 1	£5 2 8	£1 16 10	18 10
Garland Amplifier AC IV	£15 15 0	£5 5 0	£1 17 8	19 3
B.S.R. "Monarch" 3-speed Auto-change	£16 10 3	£5 10 1	£1 19 6	£1 0 3
Garrard 3-speed Auto-change. R.C.80	£17 1 3	£5 13 9	£2 0 10	£1 0 11
Lane Tape Desk, Mk. IV	£17 10 0	£5 16 8	£2 1 10	£1 1 5
"Unitelex" Record/Playback Amplifier. PR3A	£20 0 0	£6 13 4	£2 7 10	£1 4 6
Connoisseur 3-speed unit	£21 17 3	£7 5 9	£2 12 3	£1 6 9
Truvox Tape Deck, Mk. III	£23 2 0	£7 14 0	£2 15 3	£1 8 3
Leak "Point One" Amplifier	£28 7 0	£9 9 0	£3 7 9	£1 14 8
Q.U.A.D. Amplifier with pre-amplifier	£35 0 0	£11 13 4	£4 3 8	£2 2 9
Herald Tape Recorder	£50 0 0	£16 16 0	£5 17 8	£3 1 8
Unitelex "Prima" Tape Recorder. (Described above)	£59 17 0	£19 19 0	£7 3 0	£3 13 2

This list is not exhaustive—if your requirements are not here, ask us for H.P. quotation.

ALL GOODS NEW AND UNUSED (except where otherwise stated).

PLEASE ADD POST OR CARRIAGE ON ALL ITEMS. KINDLY PRINT NAME AND ADDRESS. POST ORDERS TO OUR DEPTFORD ADDRESS. EARLY CLOSING THURSDAY. OPEN ALL DAY SATURDAY.

SHOP HOURS: Mon: Tues: Wed: and Sat: 9 a.m.—6 p.m. Thurs: 9 a.m.—1 p.m. Fri: 9 a.m.—7 p.m.

GARLAND BROS. LTD.

CHESHAM HOUSE, DEPTFORD BROADWAY, S.E.8.

5 OBELISK PARADE, LEWISHAM, S.E.13.

TEL: TIDEWAY 4412/3

TEL: LEE GREEN 4038



RECEIVERS • TEST EQUIPMENT • AMPLIFIERS • RECORDERS, ETC.

Britain's most comprehensive Suppliers of Electronic Equipment for "Hams" and Industry.

All readers are cordially invited to call and inspect our stocks.

AMPLIFIERS • RECORDERS • SOUND EQUIPMENT

The latest Webster Tape Recorder in case (1953), £75. TRIXETTE 3-speed player as NEW £25. Baird type 2 tape recorder, £45. Microphones. Lustraphone, STC, Ronnette, Tannoy, etc. Rogers Amplifiers, £20. Disc cutting gear MSS, BSR, U.S.A. 2-speed motors and cutting gear 110 v., £11. Loudspeakers in stock. Goodmans, Wharfedale, Vitavox, etc.

BRITISH TEST EQUIPMENT

AVO Model 7 as NEW, £15. Model 40, £12. AC/DC mInor, £6/15/-. Roller panel valve testers, £12. Electronic test meter by AVO, £30. Wide range signal generator, £22. AVO valve characteristic meter, £50. AVO signal generator £9. Taylor 65C signal generator, £13. 90A test meter, £10. 260A TV Wobbulator, as NEW £30. Evershed Wee Meggers 500 v., £14. Bridge type and others in stock. Marconi: Signal generator types TF144G, TF517, TF390/G. Valve voltmeters, output meters. Marconi BFO type L8000A, etc. Cossor Double Beam oscilloscopes, type 3339, 339 from £35.

TRANSMITTERS

U.S.A. 1953 Harvey Wells, type TB550. Phone CW, 80, 40, 20, 15, 10, 6 and 2 metres. Crystal Oscillator VFO switching. AS NEW. Less power supply, £45. ELMAC transmitter 50 w. Phone or CW. VFO or crystal control, 75, 20, 11, 10 bands. Dual scale meter, less power supply mobile or fixed, £50. Latest Job. £55 NEW. Hallcrafters HT17's, £25.

RECEIVERS

All receivers are in good working order and condition unless stated. SX28, 550 kc/s-42 Mc/s., £45. SX24, 550-42 Mc/s., £28. SX42 540 kc/s-108 Mc/s. S20R, 550-42 Mc/s., £25. S20, £20. S29, AC/DC portable, battery 550-32 Mc/s., £25. S38 AC/DC 110-250 v. 550-30 Mc/s., £25. Also in

★ OUR ONLY ADDRESS IS WE ARE ALWAYS PREPARED TO PURCHASE EQUIPMENT SIMILAR TO THE RANGE NOW OFFERED

UNIVERSAL ELECTRONICS

★27 LISLE STREET, LEICESTER SQ., LONDON, W.C.2

Shop hours, 9.30 a.m. to 6 p.m.

stock S27, 30 Mc/s-150 Mc/s., S27CA, 150-230 Mc/s., HT11 A Marine 12 v. radiotelephones. HRO receivers junior and senior types with all coils and power supplies from £27, complete. National NC44, NR100, NC81X, NC200. Marconi CR100. 60 kc/s-30 Mc/s., £32. RME 69, £35. Eddystone receivers: Types 640, £22/10/-; 740, £35; 750, £50; 680, £65; 670, £35; 504, £25. RCA receivers, AR88D and LF from £55. Set of three dials for model D, £1/10/-.

MANUALS for the following receivers: AR88D-LF, AR77E, Marconi CR100, S20, S20R, B2 Transmitter/Receiver, H.R.O.s. Photostatic copies of originals £1/7/6.

Also in stock. Receivers by many other makers. MCRI receivers, £8. B2 Transmitter/Receiver, £20.

U.S.A. MICROWAVE TEST GEAR

No technical manuals for sale. Please write for prices. TS3. S band power frequency meter. TS10. APNI Test set. TS13. AP. X band signal generator. TS14. S band signal generator. TS34. Radar Synoscscope. TS36. X band power meter. TS62. X band echo box. TS69. 300-100 Mc/s. frequency meter. TS127. 300-700 Mc/s. frequency meter. TS226. 300-1,000 Mc/s. power meter. BC221. Frequency meter (Bendix). BC1277. S band signal generator. TS45/AP. 3 cm. signal generator. I-222A. 8-15 Mc/s. 150-230 Mc/s. signal generator. IE-19 signal generator. TS89. Pulse voltage divider. TS47. 40-500 Mc/s. signal generator. TS174. 20-250 Mc/s. FERRIS. 22A signal generator. Dumont scope, type 224A. GENERAL RADIO 804B. 30-300 Mc/s. signal generator.

RECEIVERS • KLYSTRONS • MAGNETRONS

American Receivers. APR4 and tuning units. 30-1,000 Mc/s., APR5, 1,000-6,000 Mc/s. Klystrons 723/AB, 707A, 707B, CV129. Magnetrons 725A, 2J32, 2K33, 2K25. TR cells 1B24, and many other items of equipment covering HF, VHF, UHF and centimetric bands.

Write, Call or Telephone
GERard 8410 (Day)
MEAdway 3145 (Night)

Thursday, 9.30 a.m. to 1 p.m.

• HAVE YOU A TYPE 18-19-21 OR 22 TRANS./RECEIVER— if so buy these brand new and boxed ARPI2 Valves at 4 for £1, or 5/6 each—while they last.

NEW TYPE 6H OR 182A OSCILLOSCOPE UNITS. Containing YCR97 or 517—with mu metal screen and rubber mask. EF50s or VR65s, 3 EB34s. Dozens of H.V. condensers, resistors and pots. Now is the time to buy these units before they are gone. Price £3/10/-, including "W./W." T.V. Scope Circuit.

LABORATORY TEST EQUIPMENT. For aligning and checking Trans./Receivers covering 150 to 234 Mc/s. comprising: Type BC906. Frequency Dip Grid Meter. 145-235 Mc/s. Type I-196-B. Signal Generator. 150-234 Mc/s.

Type BC1066-R. Radio Receiver. 150-234 Mc/s. Price £12 the set. Carriage extra. Just right for aligning and checking the new T.V. and F.M. bands.

VALVES. 15A, 8/6; 6AG5, 10/6; 117Z6, 12/6; 6SH7, 5/6; EF50, 6/6; 955, 954, 6/-; SG215, 6/6; Pen 220A, 6/6; TT11, 8/6; 42, 10/6; 9001, 9002, 9003, 7/6; 954-955, 6/6.

MAINS TRANSFORMERS. Input 200/240 v. Output 350-0-350 or 250-0-250 volt 80 mA. and 4 and 6.3 v. 4 a. and 4 and 5 v. 2 a. Price 21/6. Input 200/240 v. Output tapped 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30 volts, 2 amps., 21/6. All with one year's guarantee. D.P.D.T. RELAYS. Operate at 200/300 volts D.C., 8/6. We can supply any type of voltage and contacts at varying prices.

NEW SELENIUM RECTIFIERS. F.W. 12/6 volt 3 amp., 14/6; 4 amp., 22/6; 6 amp., 30/-; 1 amp., 8/6; 12 v. 100 mA., 3/-; H.W., 250 v. 100 mA., 9/-; 80 mA., 6/6; 250 v. 275 mA., 17/6.

GERMANIUM CRYSTAL DIODES, 3/9. NEW P.M. SPEAKERS. By leading manufacturers. Sin., 15/-; 6in., 16/6; 8in., 20/-; 10in., 26/6.

M/C MICROPHONES with matched Trans., 15/6. FL5 FILTER UNITS, 8/6. Same as FL8 but less switch. FL8, 12/6. TYPE FT243 FREQUENCY CRYSTALS. 5.8 to 8.6 Mc/s. In 25 Kc. steps, 8/-.

6 VOLT VIBRATOR PACK. Output 250 v. 60 mA. Complete in steel case, 22/6.

TRI196 TRANSMITTER SECTION. New and complete but less valves. 4.6-6.8 Mc/s. Easily converted, 15/-.

L.R. ARMY HEADPHONES, 8/6. TIME DELAY RELAYS. We specialise in units giving varying time constants. Please send us your requirements or problems.

FISHING ROD AERIALS. Set 3—12ft., 7/6. Screw type, 9/6. RUBBER MOUNTING BASES, 3/6.

All Carriage paid in the U.K. from Dept. W.W.,

The RADIO & ELECTRICAL MART

253B PORTOBELLO ROAD, LONDON, W.11

Phone: PARK 6026

CABINETS—RADIO CHASSIS

—OUTSTANDING BARGAINS—

Console Tape-Recorder; Radiogram; Radio and Television. Also many varied Table Model Cabinets. In polished walnut.

- 12in. or 16in. C.R.T. CONSOLE TELEVISION CABINET in high polished veneer, size 3ft. 5in. x 1ft. 4in. x 1ft. 16in. wide. PRICE 110/-.
 - CONSOLE TAPE RECORDER CABINETS, from 170/-.
 - ULTRA MODERN DESIGN RADIOGRAM, complete with latest MODEL "COLLARO" 3-speed autochange unit, £31/10/- net trade and CHANGERS, LOUDSPEAKERS, MAGNETIC TAPE RECORDING EQUIPMENT, MICROPHONES, RESISTORS, CONDENSERS AND TUNING COILS, ETC.
- DE-LUXE RADIOGRAM CHASSIS
R.L. A 5-valve 3 W/B Superhet Receiver. A.C. mains 200/250 volt. Latest Mullard miniature valves; ECH42, EL41, EBL41, EF41 and EZ40 rectifier. Large edge-lit scale with printed English and Continental Station names. 4 controls, Volume off-on, Tone, Wavechange and Tuning. Chassis size 13 1/2in. x 6in. x 2 1/2in. vertical/or horizontal, dial size 10 x 4 1/2in. PRICE £9/19/6. E.2. A 5-valve 3W/B Superhet Receiver. Specification as for R.L. but size of chassis 11in. x 7in. x 2 1/2in., scale 8in. square. Price £9/19/6.

TRADE ONLY SUPPLIED. EXPORT ENQUIRIES WELCOMED.
V.E.S. WHOLESALE SERVICES LTD.
11 GUNNERSBURY LANE, ACTON, W.3. Telephone: ACO rn 5027

WILL BUY any U.S. surplus radio parts, equipment

* APN-9, TS-67, R-89B/ARN-5, ARC-1, ARC-3, ART-13, BC-221, BC-348, SCR-522, MN-53, MN-61, RA-1, MN-31, MI-32, ARN-7, Headsets, Mikes, Cannon Amphelhol plugs, 274-N, ARC-5, Dynamotors, Test sets, "TS." or "1." prefixes.

State condition and Best Price

Aircraft Radio Industries, Inc.

85 St. John Street, New Haven, Conn., U.S.A.



5 Harrow Road, Paddington, W.2

PADDINGTON 1008/9 and 0401

OPEN MONDAY to Sat. 9-6. THURS. 1 o'clock.

★ TAPE-DECK AMPLIFIER AND POWER UNIT ★

This unit is specially designed for the "Truvox" unit and we believe this quality amplifier lifts tape recording from the novelty, into the quality class.

AMPLIFIER SPECIFICATION :

★ 2-6BR7, 2-V6GT, 1-6J5, 1-6U5G ★ Variable selective negative feed back circuits ★ Variable tone control ★ Magic eye level indicator ★ Four watts undistorted output ★ Amplifier complete with valves, £13/5/-.
Chassis size 10in. x 6in. x 2½in.

POWER UNIT (AC200/250 volts)
Chassis size 9in. x 5in. x 2½in., complete with 5Z4 £4 15 0
Amplifier and Power Unit complete £16 16 0
COMPLETE KIT OF PARTS for Amplifier and Power Unit £13 10 0

CALL FOR DEMONSTRATION OR SEND FOR FULL DETAILS

TRUVOX TAPE DECK MARK III

Incorporating high impedance mu-metal twin-track heads. Two-speed capstan, for tape speeds of 7½ and 3½ inches per second. Three heavy-duty motors allowing for fast forward and rewind facilities without tape handling. All controls operated by electrically and mechanically interlocked push buttons.

Price £23/2/-, carriage free.
(Available from stock.)

CRYSTAL MICROPHONE INSERTS

8'6 POST FREE  **8'6** POST FREE

Ideal for tape recording and amplifiers. No matching transformer required.

RADIO-GRAM CHASSIS

3 Wave-band Superhet. Med., long and short. 5 Latest Type MULLARD Valves.
4 Position Switching. Gram., med., long and short.
Provision for A.C. Mains. Extension Speaker. 110/250 volts.
Chassis 11in. x 7in. x 2½in. Scale 8in. Square. Or Chassis 13½in. x 6½in. x 2½in. Dial 10in. x 5½in. PRICE £10/5/-.
BRAND NEW AND GUARANTEED CARR. PACKING AND INS. 10/-.

SEND STAMPS FOR NEW 1954 28-PAGE CATALOGUE

6 WATT AMPLIFIER (UNDISTORTED)

Manufactured by Parmeko and Sound Sales for Admiralty. 4 valves, PX25, MS/PEN, AC/HL, MU14. Output Matching and 3Ω and 15Ω, 100/250 v. A.C. COMPLETE IN STEEL GREY AMPLIFIER CASE. £12/10/-.
CALL FOR DEMONSTRATION


62A INDICATOR UNIT

Complete with VCR517 or 517C, 12-EF50, 4-SP61, 3-EA50, 2-EB34.
Built on double-deck chassis. Absolute new condition.
8/6. Carr. 7/6.

R.F. UNITS

Type 24
20-30 Mc/s. Switched Tuning. With 3-SP61
15/- EACH
BRAND NEW.

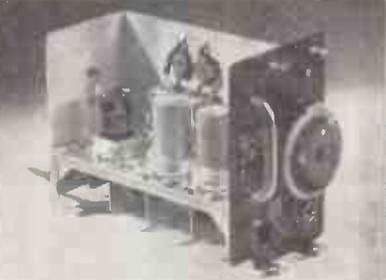Type 25
40-50 Mc/s. Switched Tuning. With 3-SP61.
19/6 EACH
BRAND NEW.



R.F. UNITS

Type 26
50-65 Mc/s. Variable Tuning. 2-VR136. 1-VR137
45/- EACH
BRAND NEW.

Type 27
65-85 Mc/s. Variable Tuning. 2-VR136. 1-VR137
45/- EACH
BRAND NEW.

R.F. OSCILLATOR UNIT

6-18 kV., including rectifier winding.
25/-.

PYE 45 M/CS. STRIP, TYPE 3583 UNITS

Size 15in. x 8in. x 2in. Complete with 45 Mc/s. Pye Strip, 12 valves, 10 EF50, EB34 and EA50, volume controls and hosts of Resistors and Condensers. Sound and vision can be incorporated on this chassis with minimum space. New condition. Modification data supplied. Price 25. Carriage paid.

T.V. PRE-AMPLIFIER FOR LONDON AND BIRMINGHAM. Complete with 6AM6. Ready to plug in to your set, 2/7/6. P.P. 2/6.

BOWTHORPE CONTINUITY METER

Dual scale 0-500 ohms and 100-200,000 ohms moving coil operated from 4½-volt internal battery. Size 6in. x 3in. x 4in. Original price 28/8/-. Our price, brand new, 23/5/-.

RECORDING TAPE

G.E.C.

600ft. Reels 10/-
1,200ft. Reels 17/6

BUY NOW—UNREPEATABLE BARGAIN.

INDICATOR UNIT TYPE 182A

Unit contains VCR517 Cathode Ray 6in. tube, complete with Mu-metal screen, 3 EF50, 4 SP61 and 1 5U4G valves, 9 wire-wound volume controls and quantity of resistors and condensers. Suitable either for basis of television (full picture guaranteed) or Oscilloscope. Offered BRAND NEW (less relay) in original packing case at 67/6. Plus 7/6 carr.

RECEIVER R1355. As specified for "Inexpensive Television." Complete with 8 valves VR85 and 1 ea. 5U4G, VU120, VR92. Only 29/6, carriage 5/-. Or brand new in original packing cases 55/- carriage 5/-.

VCR138A. 2½in. C/R Tube. Brand new in original cartons 35/-, carr. free.

VOLTMETERS

15 v. (50 c.) A.C. M.I. 2½in. flush panel mounting 10/-
20 v. M.C. 2in. square panel mounting 7/6
150 v. M.C. 2½in. flush panel mounting 10/-
3,000 v. M.C. 2½in. flush panel mounting 21/-
4,000 v. M.C. 2½in. flush panel mounting 21/-
3,500 v. M.C. 3½in. Projection 21/-

No. 38 "WALKIE TALKIE" TRANSMITTER-RECEIVER, complete with Throat Mike, phones. Junction Box and Aerial Rods in canvas bag. Freq. range 7.4 to 9 Mc/s. Range approx. 5 miles. All units are as new and tested before despatch, £410/-.

INDICATOR UNIT TYPE SLC5

This unit is ideal for conversion for a 'Scope Unit or basis for Midget Television. It contains C/R Tube type ACR10 (VCR193A) complete with holder and cradle, also earthing clip. 1-VR66, 2-VR66, 24 mid. 550 v. wkg. condenser, potentiometers and a varied assortment of resistors and condensers. These Units are in new condition and packed in wooden transit cases. The C/R Tube will be tested before despatch. Dimensions: 8½in. x 6½in. x 11½in. 45/-.

MILLIAMMETERS

500 Microamp M.C. 2in. round panel mounting 15/-
1 mA. M.C. 2½in. flush panel mounting 22/6
5 mA. M.C. 2in. square panel mounting 7/6
10 mA. M.C. 2½in. flush panel mounting 10/-
30 mA. M.C. 2in. round panel mounting 7/6
30 mA. M.C. 2½in. flush panel mounting 10/-
50 mA. M.C. 2in. square panel mounting 7/6
200 mA. M.C. 2½in. flush panel mounting 10/-
300 mA. M.C. 2in. flush panel mounting 10/-
500 mA. M.C. 2½in. flush panel mounting 12/6

WALKIE-TALKIE TYPE "46."

Complete with 6 valves, 2VP23, HL23 DD, QP25, TP23 and ATP4, aerial rods, I.P. trans., 1.6 Mc/s. mike trans. in new condition, but less transmitting components and coils removed by M.o.S., 30/-, carr. paid. (Less valves, 10/-)

ROTARY POWER UNIT TYPE 104

Input 12 v., Output 230 volts 65 mA. and 6.3 volts 2.5 amps. Fully filtered and smoothed and noise suppressed. Ideal for car radio, etc. BRAND NEW. ONLY 15/- (postage, etc., 2/6). ALSO 24 v. type 15/-.

AMP-METERS

1 amp. T.C. 2½ Projection 6/-
3 amp. T.C. 2in. square panel mounting 6/-
6 amp. T.C. 2½in. flush mounting 7/6
20 amp. M.I. 2½in. round 10/-
15 amp. M.I. (50 c.) Projection 35/-
30 amp. M.C. 2in. square panel mounting 7/6
300 volts 50 cy. A.C. 5in. dial projection type. 50/-
M.C. = Moving Coll. M.I. = Moving Iron. T.C. = Thermo-Coupled.
All Meters are Brand New and in original cartons.

CATHODE RAY TUBES

VCR97. Guaranteed full T/V picture £2 0 0 (carr. 2/-)
VCR517 or 517C. Guaranteed full T/V picture £1 15 0
VCR136 £1 10 0
3BP1, with shield suitable for 2½V or scope (carr. 1/6) £1 5 0
MU-METAL SCREENS for VCR97 or 517. P.P. 1/6 10 0
6in. ENLARGER for VCR97 or 517. P.P. 1/6 17 6

AMERICAN 12 v. DYNAMOTOR

Output 250 volts. 60 mA. Weight 5 lb. Suitable for Car Radio or Electric Razors, 22/6.

PHOTO CELLS CMG25. Brand new, 25/-.

WANTED
723 A/B. Top prices paid.

PLEASE ADD POSTAGE. ARTICLES UP TO 10/-, 1/-, £1, 1/6. £2, 2/-.

RADIO TRADERS LTD.

23 WARDOUR ST., LONDON, W.1. (Coventry Street end)

Phone No. GERrard 3977/8 Grams: "Radiotrade"

Component Specialists for 20 years.
The Largest Selection of Radio and Electronic Components in the Country.

SPECIAL OFFER

MILLIAMPER METERS, 0-500, 0-300, 0-30, 2½ in. round, flush panel mounting 10/6 each

CONDENSERS

	Per doz.
16 x 8 Mfd. Metal Cans Electrolytic, 350 v.	15/-
32 Mfd. Metal Cans Electrolytic, 350 v.	15/-
32 x 8 Mfd. Metal Cans Electrolytic, 275 v.	18/-
64 Mfd. Metal Cans Electrolytic, 350 v.	30/-
2 Mfd. 150 v. Tubular Paper (aluminium tubes)	18/-
100 Mfd. 50 v. Metal Cans. 15/- doz. 25 Mfd. 50 v. Tubular Cardboard	12/-
12 Mfd. 50 v. Tubular Paper (aluminium tubes)	12/-
100 Mfd. 6 v. Tubular Paper (aluminium tubes)	12/-
.0005 Tubular Miniature ... 3/6 .02 Tubular 500 v.	4/6
.001 Tubular 350 v. 4/6 .05 Tubular 350 v.	4/6
.005 Tubular 200 v. 3/6 .05 Tubular 500 v.	10/-
MIDGET MICA CONDENSERS : .0001, .0002, .0003, .0004, .0005	4/-
200 Assorted Moulded Micas. Popular Values	£2 10 0
200 Assorted Silver Micas. Popular Values	£2 10 0
200 Assorted Carbon Resistors : ¼, ½ and 1 watt. Good selection	£10 0 0
CARBON RESISTORS : ¼ watt 2/6; ½ watt 3/-; 1 watt 4/-; 2 watt 6/-; 5 watt 9/- per doz.	

HIGH STABILITY RESISTORS :

Tolerance :	1%	2%	5%	each
¼ watt	1/-	9d.	6d.	each
½ watt	1/3	1/-	9d.	each
1 watt	1/9	1/3	1/-	each

8-13 MEG 2 watt 2/6 each

W/W AND VITREOUS RESISTORS. 5 watt, 1/6; 10 watt, 2/6; 15 watt, 3/-; 20/30 watt, 3/6 each.

V/CONTROLS. COLVERN and B-NSF. 5K PRESET and other values, 2-3 watt, 2/- each. 10K Isolated Spindle..... 2/- ..

500 ohms, 1K, 20K, 25K, 50K, with spindle 3/- ..

V/CONTROLS WITH SWITCH : 50K, 500K, B-NSF..... 2/6 ..

V/CONTROLS : Less Switch, Preset and Spindle. MOST VALUES TWIN MIDGET GANGS, .0005, with trimmers, PERSPEX COVER 1/9 ..

4-WAY PUSH BUTTON UNITS 5/6 ..

PUSH BUTTON KNOBS 15/- doz.

TAG STRIPS : 3-way, 2/- doz.; 4-way, 2/6 doz.; 5-way, 3/- doz.; 7-way 4/- doz.; 28-way 10/- doz.

ASSORTED PILOT LAMP HOLDERS 4/- ..

FUSES 1½ in. Most values from 750 mA. to 10 amp. 2/- ..

POINTER KNOBS. Small black, with line, ½ in. hole..... 7/6 ..

STANDARD ROUND KNOBS : Small, ½ in. hole, 6/-; Large, ¾ in. hole, 7/6; with spring clip, ½ in. hole 4/6 ..

CLIX WANDER PLUGS. Type MP2. Red, black, blue... 2/- ..

PHILIPS TRIMMER TOOLS 9/- ..

BELLING & LEE. P/M FUSE HOLDERS, Type L356..... 2/6 each

WEARITE COILS : Types PA4, PO4, PA5, PO5 12/- doz.

VALVE HOLDERS : Moulded, B9A, 7/6; B7G, 6/-; EF50, 6/-; ENGLISH OCTAL, 3/- per doz. **SCREEN CANZ** for B9A, B7G, 6/- doz.; **PAXOLIN**—B7G MAZDA 4-pin UX 3/- ..

BELLING & LEE. PLUGS AND SOCKETS. Ex-Govt. BRAND NEW. 5-pin, Chassis and Cable, 7-pin..... 1/6 pair

BULGIN. P.73, Plug and Socket, 2/9 each; P74, Plug and Socket, 2/6; P200, Plug and Socket, 2/-; Rotary Switches, S.255, 2/-; Dolly Switches, S.267, 2/-; Dolly Switches, S.259, 1/6; Standard Switches, Ex-Govt., On-off 1/6 each

POST OFFICE LAMP JACKS, No. 10 9/- doz.

Lamp Covers for same 3/- ..

L.F. CHOKES. 300 w., 60 mA. CH5 4/6 each

OUTPUT TRANSFORMERS. Multi Ratio, 5/-; Pentode or Power 4/- ..

VALVE SCREEN CANS for Standard Valves 10/6 doz.

DRUM DRIVES. 4 in. 1/- each

WESTECTORS. WX6, WX12, W1, W12, W4 9/- doz.

ARCOLECTRIC (Whitney Lamps). Red, green, clear 15/- ..

SIGNAL LAMP HOLDERS P/M, complete with adjusting lamp holders 18/- ..

AIR SPACE TRIMMERS. Preset and spindle types, 5PL, 10PF, 15PF, 20PF, 25PF, 50PF, 75PF, 15/-; 100PF Preset 18/- ..

JONES PLUG AND SOCKETS. 4-pin, 2/6; 6-pin, 3/-; 8-pin, 3/6; 10-pin, 4/-; 12-pin..... 6/- pair

NUTS. 8BA, 3/-; 6BA, 2/6; 4BA, 3/-; 2BA 4/- gross

SOLDER TAGS 1/6 gross **SHAKEPROOF WASHERS** 1/- ..

WASHERS. 2, 4 and 6BA 1/- ..

SHAKEPROOF SOLDER TAGS, 4BA and 6BA, 2/-; 2BA 2/3 ..

REDUCED PRICES FOR LARGE QUANTITIES

ALL CINCH COMPONENTS IN STOCK

CASH WITH ORDER OR C.O.D. ALL ORDERS FOR LESS THAN £2 ADD POSTAGE

Trade Counter open 9.30 to 5.30 Mondays to Fridays.

Callers Welcomed.

WHOLESALE, MANUFACTURERS' AND EXPORT ENQUIRIES INVITED

★ SEND FOR LISTS ★

H.R.O. SENIOR RECEIVERS. With A.C. P.P., 5 coils, £37/10/-.
D.S.T. 100 RECEIVERS, as new. Coverage is 7 bands from 30 Mc/s. to 50 Kc/s., £30 each.
HAMMERLUND BC779B. Mint condition, rack mtg., £42/10/-.
HALLICRAFTERS SX28, S27, S41, S38, etc. All in perfect condition.

AR88LF, AR85D, CR100, from stock. **RI155 RECEIVERS,** new. A.C./D.C. MOTORS, suitable for sewing machines, 47/6 each.

A.C./D.C. 12 v.-15 v. MOTORS, long spindle for models, 15/- each.
20 WATT P.A. RACK MOUNTING AMPLIFIERS, complete with power pack, 200/250 v. A.C., less valves, £6/10/-.

Valves—2 type PX25, 1 MH4 and 1 MUI4, £2/15/- per set.
NEW M/C MICROPHONES, hand type, with 12 yds. heavy duty screened cable, £3/15/- each.

B.C.221 FREQUENCY METER, from stock. Many items of American equipment available.

TEST EQUIPMENT. We hold a comprehensive stock. Multi-range meters at 1,000 and 20,000 o.p.v., valve testers, signal genes.

4,000Ω **EARPHONES,** 11/6 pr.
10,000Ω POTENTIOMETERS, large size, by Colvern, enclosed, 8/6 each. 100k, 15w, 9/6 each.

C.R.100 RECEIVERS, perfect order, £27/10/-.
MAINS TRANSFORMERS. Special offer, not ex-W.D., 200/250 v. input tapped. Output 250-0-250 v. at 100 mA., 5 v., 3 a., 6.3 v., 4 a., 2/6 each.

350-0-350 v. Ellison at 120 mA., 6.3 v., 5 a., C.T. 5 v., 3 a., 37/6. All types in stock.

EVERSHED BRIDGE MEGGERS, 250 v. Special price, £17/10/- each.

COSSOR DOUBLE BEAM OSCILLOSCOPE, perfect, £33.
G.E.C. 7 WATT V.H.F. MOBILE TX/RX. Complete with 12 v. rotary p/ack, 80.9, 81.1 and 81.3 Mc/s., special offer, £30.

EDDYSTONE 640 RECEIVER. Perfect, at £22.
6 VOLT (3 at 2 v.) BOXED ACCUMULATORS, 24/-.

1μF350 v. **METAL CASED TUBULARS, U.S.A.** at 4/6 doz. (minimum 2 doz.).

H.R.O. COILS. 46-96 Mc/s. etc., at £2/5/- per coil.
LARGE STOCKS OF MOTORS. A.C./D.C. and A.C., 1/16, 1/12, ½, ½ h.p.

EDDYSTONE "750," as new, £45/10/-.
 Your post enquiries welcomed. S.A.E. for reply, please. Orders, C.W.O. or Pro-forma Invoice, no C.O.D. Prices quoted do not include carriage and packing.

All types of equipment purchased. Top prices paid.

SERVICE RADIO SPARES

4, LISE STREET, LONDON, W.C.2

Telephone: GERrard 1734.

Good Investments

LIGHTING PLANTS for house lighting where mains supply is not obtainable. We have in stock plants both A.C. and D.C. by leading manufacturers, surplus stocks which have been completely rebuilt in our works and every plant is guaranteed.

D.C. PLANTS. 12/18 volts Alco Lyon 360 watts with S/bd. £22/10/-.
 12/18 volts J.A.P. 550 watts, £30. Switchboard, £8/10/-, 36 volts Lyon Norman 1,260 watts, £40. Switchboard, £10.

A.C. PLANTS. 2.75 K.W. 130 volts 3-phase J.A.P. with switchboard. 1.5 K.W. 230 volts 50 cycles S.P. Pether Higgs. 300 watt 110 volts 50 cy. S.P. and 12/18 volts D.C. for charging. Choroehorse with switchboard, £32/10/-, 300 watt 220 volt A.C. 50 cy. S.P. and 12/18 volts D.C. Briggs & Stratton with S/bd., £35. 250 V.A. 230 volts 50 cy. Lyon Alco with S/bd., £32/10/-.

All prices nett, packing and carriage at cost.
RECTIFIER UNITS. Westinghouse metal rectifiers, double wound transformers. Output 50 volt ½ amp., 50 volts 1½ amps., 50 volts 3½ amps., 110 volts 2 amp., 230 volts ½ amp., 24 volts 6 amp., 22 volts 10 amps., 24 volts 26 amps., 11/48 cells 20 amps. All for prompt delivery. Write for special leaflet.

ELECTRADIX RADIOS

DEPT. A, 214 QUEENSTOWN ROAD, LONDON, S.W.8

Telephone: MACaulay 2159

LYONS RADIO Ltd.

INVERTERS. Known as Motor Generator type 7. Input 22/29 v. D.C. Output 80 v. A.C. at 1,600 cycles, 240 vA at unity power factor. Complete with carbon pile voltage regulator and filter unit mounted beside generator on the same base plate. Overall dimensions approx. 9 x 8 x 9 in. and weighs only 15½ lb. In new and unused condition. PRICE 55/10/-.

POWER UNITS type 87. Rotary converter units for 24 v. D.C. input and having a twin D.C. output of 6.5 v. at 2.5 a. and 250 v. at 50 mA. Can be operated in reverse from D.C. mains or 6 v. accumulator. Totally enclosed in neat metal cases 8½ x 6½ x 4½ in. In good condition and working order. PRICE 9/6, post 2/6. Rotary Converter only (less case). PRICE 5/-, post 2/-.

SUB-STANDARD VARIABLE CONDENSERS. Fitted in glass containers with heavy brass frame. Calibrated 0.05 jars to 0.95 jars. Approx. size 7 x 7 x 6 in. Front panel fitted with brass terminals and shorting switch. In good condition. PRICE 25/- or less glass container, 15/6, carriage 3/6.

CABINET SPEAKERS. 8 in. moving coil P.M. speaker fitted in wooden cabinet—less back, 18 in. sq. x 8 in. deep with small carrying handle at top. In used condition but speaker tested to ensure in good working order. BARGAIN PRICE. Only 17/6, carriage 3/6.

SCREENED WIRE. Copper conductor 1/048, permaloid insulated. Bargain clearance 12 yards, 5/9; 25 yards, 10/9; 50 yards, 17/9; 100 yards, 25/-.

3 GOLDHAWK ROAD, (Dept. M.W.)

SHEPHERD'S BUSH, LONDON, W.12

Telephone: Shepherd's Bush 1729

MAINS TRANSFORMERS

Primary, 200-250 v. P. & P. 2/-
 300-0-300 100 mA., 6 volt 3 amp.
 5 volt 2 amp., 22/6.

Drop thro' 350-0-350 v. 70 mA., 6 v.
 2.5 amp., 5 v. 2 amp., 14/6.

Drop thro' 250-0-250 v. 140 mA., 6 v. 3
 amp., 5 v. 2 amp., 14/6.

Drop thro' 110-110 60 mA., 6 v. 0.5
 amp., 8/6.

280-0-280, drop through, 80 mA.,
 6 v. 3 amp., 5 v. 2 amp., 14/6.

250-0-250 80 mA., 6 v. 4 amp., 14/-
 Pri. 230 v. Sec. 200-0-200 35 mA.,
 6 v. 1 amp., 8/6.

Pri. 200/250 v., secondary 3, 4, 5, 6,
 8, 9, 10, 12, 15, 18, 20, 24 and 30 volt
 at 2 amps., 13/-.

Drop thro' 280-0-280, 200 mA., 6 v.
 5 amps., 5 v. 3 amps., 27/6.

Drop thro' 270-0-270 80 mA., 6 v.
 3 amp., 4 v. 1.5 amp., 13/6.

Drop thro' 270-0-270 60 mA., 6 v.
 3 amp., 11/6.

Heater Transformer. Pri. 230-250 v.
 6 v. 1 amp., 0/-; 2 v. 2 1/2 amps., 5/-
 2 v. 2 1/2 amp. and 6 v. 0.6 amp. E.H.T.
 Insulated, 8/6. P. & P. each 1/-.
 Input 200/250 sec., v. 3, 5, 6 amp., 4 v.
 4 amp., 2 v., 2 amp., 14/6. P. & P. 1/6.
 1000-0-1000 v. 250 mA. 4 v. 3 amp.
 37/6. P. & P. 6/-.

P.M. SPEAKERS (closed field)

	with trans.	less trans.
2 1/2 in.	—	15/6
3 in.	—	13/6
5 in.	16/6	12/6
6 in.	16/6	12/6
8 in.	18/6	15/-

P. & P. on the above 1/- each.
 10W less trans., 19/6. P. & P. 1/6.

Truxor BX11. 12in. P.M. 3 ohm speak
 coil, 45/- P. & P. 3/6.

6 1/2 in. M.E. Speaker, 1,000 ohm field
 15/- P. & P. 1/6.

R. & A. T.V. Energised 6 1/2 in. speaker
 with O.P. trans. 6V matching, field
 coil 175 ohms. Requires a minimum
 150 mA. to energise, maximum current
 250 mA. 15/- P. & P. 2/-.

Extension Speaker Cabinet, in contrast-
 ing walnut veneer, size 15x10 1/2 in.
 Will take 6 1/2 in. speaker 17/6.
 P. & P. 2/-.

Completely built All-dry Mains Unit
 with O.P. trans. 6V matching, field
 coil size 5x5x3in., incorporating
 Westinghouse metal rectifiers, 3 500
 mfd., 16x24 mfd., mains trans., 3
 smoothing chokes, output 90 v., 10
 mA., 1.4 v., .25 amp., 39/6. P. & P.
 2/6.

Volume Controls, Long spindle less
 switch, 50K, 600K, 1 meg., 2/6 each.
 P. & P. 3d. each.

Volume Controls, Long spindle and
 switch 1/2, 1 and 2 meg., 4/- each:
 10K, 50K, 3/6 each. 1/2 and 1 meg.,
 long spindle double pole switch, mini-
 gauge, 5/- P. & P. 3d. each.

Trimmers, 5-40 pf., 5d.; 10-110, 10-250.
 10-450 pf., 10d.

Twin-gang .0005 Tuning Condenser,
 5/- With trimmers, 7/6. P. & P. 1/-.
 Line Cord, 2-way 0.3 amp., 60 ohms,
 per foot, 1/3 per yard.

Twin-gang .0005 with feet, size
 3 1/2 x 1 1/2 in., 6/6.

3-gang .0005, with feet, size 4 1/2 x 3 1/2 in.
 7/6.

Hoover Variable Speed 600-1,200
 revs. Tape Recording Motor. Silent
 running, 200/250 v. A.C. Shaded pole
 with timing. Weight 5 lb., 27/6.
 Plus P. & P. 2/6.

PERSONAL SHOPPERS ONLY. 9in.
 Enlarger 17/6, 12in., 27/6.

Germanium Crystal Diode, 2/3 post
 paid.

Television Masks, White Rubber 9in.
 with glass, 7/6. Cream Rubber, 12in.,
 with armour-plate glass, 15/-, 15in.
 Cream, 17/6 plus 1/6 P. & P.

T.V. Width Controls, 3/6.

T.V. Sub Assembly, all-chassis, 12in. x
 3 1/2 in. with frame osc. line osc., 12 mfd.
 275 wkg. Metrolin 3s. condensers, 4
 resistors and tag panel 15/-, p. & p. 1/6.

CRYSTAL PICK-UP by famous manu-
 facturer complete with sapphire
 trailer needle and volume control
 23/- P. & P. on each 1/-.

Amplifier case, black rexine covered,
 leather carrying handle, chrome plated
 corners, rubber feet, felt lined, detach-
 able 1 1/2 in. External dimensions, 13 1/2
 x 13 1/2 x 9 1/2 in., 21. P. & P. 2/6.

Mains Droppers, 0.3 amp., 460 ohms.
 tapped 280 and 410, 1/6; 0.2 amp.,
 717 ohms, tapped at 100 ohms,
 vitreous, 1/6; 0.3 amps., 850
 ohms, tapped 700 and 525, 2/6;
 0.2 amp., 1,000 ohms, vitreous, tapped,
 2/6; Vitreous 3 amp. 700 tapped
 680, 640, 600, 3/6. P. & P. on each 3d.

D. COHEN RADIO AND TELEVISION COMPONENTS


Terms of Business: Cash with order. Despatch of goods within 3 days from receipt of order. Where post and packing charge is not stated please add 1/- up to 10/-, 1/6 up to £1, and 2/- up to £2. All enquires and lists, S.A.E.

SPECIAL NOTE: NO GOODS SENT WHERE CUSTOMS DECLARATION IS APPLICABLE.

23 HIGH STREET (Uxbridge Road) ACTON, W.3 Telephone: ACOrrn 5901

Hours of Business: Saturday 9—6 p.m. Wednesday 9—1 p.m. Other days 9—4.30 p.m.

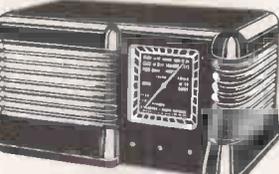HIGH-IMPEDANCE PLASTIC RECORDING TAPE, by famous manufacturer. 600 ft. on aluminium spool, 8/-, 1,200 ft. on aluminium spool 17/6, post paid.



CABINET, as illustrated, 1 1/2 x 6 1/2 x 5 1/2 in. in walnut or cream complete with TRF chassis, 2 waveband scale, station names, new waveband, backplate, drum pointer, spring, drive spindle, 3 knobs and back, 22/6. P. & P. 3/6.

AS ABOVE, with superhet chassis, 23/6. P. & P. 3/6.

AS ABOVE, complete with new speaker to fit, and O.P.trans., 35/-, P. & P. 3/6, with superhet chassis, 36/-, P. & P. 3/6.

Used metal rectifier, 230 v. 50 mA., 4/6; gang with trimmers, 6/6; M. & L. TRF coils, 5/-; 3 obsolete ex-Govt. valves, 3 v/h and circuit, 6/6; heater trans., 6/-; volume control with switch, 3/6; wave-control kit, 4/-.

change switch, 2/-; 32x32 mfd., 4/6; iron core 465 IFS, 7/6; min. gang, 5/6; volume control with switch, 4/-; wave-change switch, 2/6; heater trans., 7/6; 4 v/h, 1/6; 4 obsolete ex-Govt. valves, metal rectifier and Xtal diode with circuit, 14/6; 25 x 25 mfd., 1/-; 16x16 mfd., 3/3; valve plus kit (17, 7/6; resistor kit (14), 3/6.

USED 4-VALVE PLUS METAL REC. A.C. MAINS 230/250 SUPERHET. Complete in outstanding cabinet, size 22x14x10 1/2 in. Valve line-up: 6K8, 6K7, 6Q7 and 6P8. Medium wave, in mahogany cabinet, size 14 1/2 x 9 x 7 1/2 in. These have been checked and are in first-class working order, and first-class performance. 6 1/2 in. P.M. speaker, 33/10/6. P. & P. 5/-.

USED 5-VALVE A.C. MAINS 200/250 3 WAVEBAND SUPERHET. Complete in outstanding cabinet, size 22x14x10 1/2 in. Valve line-up: 6K8, 6K7, 6B8G, 12G, and U00 rec., 8in. P.M. speaker. In first-class working order. 27/10/6. P. & P. 12/6. We have a few of these in A.C./D.C., price as above, or 22/10/- dep., 6 monthly payments of £11/-.

FULLY SHROUDED MAINS TRANSFORMER. Input 110/250, sec. 350-0-350 175 mils 6.3 v. 7 amp., 5 v. 3 amp. 35/-, P. & P. 3/-.

FULLY SHROUDED PUSH-PULL TRANS. Pri. 6,000 ohms, sec. 15 ohms (2 L66 in push-pull) 21. P. & P. 2/-.

FULLY SHROUDED CHOKE 15 Henry 180 mils, 15/- P. & P. 2/-.

FULLY SHROUDED CHOKE 5 Henry 120 mils, 8/6. P. & P. 2/-.

These last four items by very famous manufacturer.

USED C.R.T. TUBES. Heater cathode short 9in., 45/-, 12in. 75/-, Ion burn 9in., 35/-, 12in., 55/-, P. & P. on each 7/6.




COMPLETELY BUILT SIGNAL GENERATOR. Coverage 110 Kc/s-320 Kc/s., 300 Kc/s-900 Kc/s., 900 Kc/s-2.75 Mc/s., 2.75 Mc/s-8.5 Mc/s., 8.5 Mc/s-25 Mc/s., 17 Mc/s-50 Mc/s., 25 Mc/s-75 Mc/s. Metal case 10x6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in., 2 valves and rectifier. A.C. mains 230/250 v. Internal modulation 400 cps. to a depth of 30 per cent., modulated or unmodulated. R.F. output continuously variable 100 millivolts. Black crackle finished case and white front panel. P. & P. 4/-, 24/5/-, or 34/- deposit and 3 monthly payments of £1.

CONSTRUCTOR'S PARCEL No.1 comprising chassis 12 1/2 x 8 x 2 1/2 in., cad. plated 18 gauge, 7 v/h, 1F and trans. cut-outs, backplate, 2 supporting brackets, 3 waveband scales, new wave-length station names, size of scale 1 1/2 x 4 1/2 in., drive spindle drum, 2 pulleys, pointer, 2 bulb holders, 5 paxolin international octal valve holders, 4 knobs and pair of 465 IFS, 16/6. P. & P. 1/6.

AS ABOVE, but complete with 16-16 mfd. 350 wkg. and semi-shrouded drop thro' 250-0-250 60 mA. 6 v. 3 amp. Pri. 200-250, and twin-gang, 31/6. P. & P. 3/-.

CONSTRUCTOR'S PARCEL No. 2, plus 16 x 16 mfd. 350 wkg. semi-shrouded drop thro' 250-0-250 60 mA., 6.3 v., 3 v., 2 v., twin gang and 6 L.M.S. superhet coils complete with trimmers and tracking condensers with circuit. 22/5/-, plus 3/6 post and pkg.

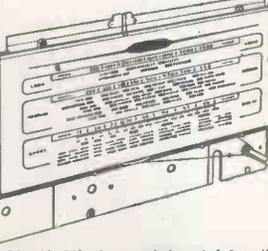BATTERY CHARGER KIT comprising metal case 4 1/2 x 5 1/2 in., transformer 230/250 v., and metal rectifier. Will charge 6 or 12 v. battery 1 1/2 amp. 19/6. P. & P. 2/6.



PERSONAL PORTABLE CABINET. In cream-coloured plastic: size 7 x 4 1/2 x 3 in. Complete 4-valve chassis. Scale and 3 knobs. Takes miniature 90 v. and 7 1/2 v. batteries 9/-, post and pkg. 1/6.

3in. P.M. Speaker to fit above, 10/-. Miniature output transformer, 5/-. Miniature wave-change switch, 1/6. Miniature 1-pole 4-way used as Volume and On, 1/6. 4B7G valve holders, 2/4. Midget twin gang 1in. dia. 1in. long and pair medium and longwave TRF coils 1in. long x 1in. wide; complete with 4-valve all-dry mains and battery circuit 8/6. Condenser Kit, comprising 11 miniature condensers, 3/6. Resistor Kit comprising 18 miniature resistors 4/-. The above receiver (less valve and batteries) could be built for approximately 51/- All valves to suit above available. Point to Point Wiring Diagram 1/-.

R.I. MAINS TRANSFORMERS, chassis mounting, feet and voltage panel Primaries 200/250.

300-0-300 60 mA. 6.3 v. 1 a., tapped at 4 v. 6.3 v. 2 a. tap 4 v., 13/6.

350-0-350 75 mA. 6.3 v. 3 a. tap 4 v. 6.3 v. 1 a., 13/6.

350-0-350 70 mA. 4 v. 5 a. 4 v. 2.5 a. C.T., 18/6. P. & P. on the above transformers, 2/-.

600-0-600 195 mA. 6.3 v. C.T. 4 a. 6.3 v. C.T. 2 a. 5 v. C.T. 2 a., 27/6.

500-0-500 125 mA. 4 v. C.T. 4 a. 4 v. C.T. 4 a. 4 v. C.T. 2.5 a., 27/6.

500-0-500 250 mA. 4 v. C.T. 5 a. 4 v. C.T. 5 a. 4 v. C.T. 4 a., 39/6.

P. & P. on the above transformers 3/-.

Line and E.H.T. transformer 9KVA, using ferrocart core complete with built-in line and width control. Mounted on small all-chassis. Overall size 4 1/2 x 1 1/2 in. EY61 rec. winding. 27/6. P. & P. 2/6.

Valve Holders, moulded octal, Mazda, and local, 7d. each. Paxolin, Mazda and local, 4d. each. Moulded BTG, BSA, and B9A, 7d. each. BTG moulded with screening can, 1/6 each. 32 mfd., 350 wkg. 2/-
 16 x 24 350 wkg. 4/-
 4 mfd., 200 wkg. 1/3
 40 mfd., 450 wkg. 3/6
 16 x 16 mfd., 600 wkg. 4/6
 16 x 16 mfd., 450 wkg. 5/9
 32 x 32 mfd., 350 wkg. 3/9
 32 x 32 mfd., 350 wkg. 4/-
 32 x 32 mfd., 350 wkg. and 25 mfd., 25 wkg. 6/6
 25 mfd., 25 wkg. 11d.
 250 mfd., 12 v. wkg. 1/-
 16 mfd. 600 wkg., wire ends. 2/8
 8 mfd., 500 v. wkg., wire ends. 2/8
 8 mfd., 350 v. wkg., tag ends. 1/6
 80 mfd., 25 v. wkg., wire ends. 1/9
 100 mfd. 350 wkg. 4/-
 100-0-200 mfd., 350 wkg. 9/6
 16-16 mfd. 350 wkg. 3/8
 Ex-Govt. 8 mfd., 600 v. wkg., size 3 1/2 x 1 1/2, 2 for 2/6
 16 x 32 mfd., 250 wkg. 6/-
 60 mfd., 180 wkg. 1/9
 65 mfd., 220 wkg. 1/6
 8 mfd., 150 wkg. 1/6
 60-0-100 mfd., 280 wkg. 7/6
 60 mfd., 12 wkg. 11d.
 32-32 mfd., min., 275 wkg. ... 4/-
 50 mfd., 500 wkg. 1/9
 Miniature wire ends moulded, 100 pf., 500 pf., and .001 ea. ... 7d.

Combined 12in. mask and escutcheon in lightly tinted perspex. New aspect, edged in brown. Fits on front of cabinet, 17/6. P. & P. 2/-.

Frame Oscillator Blocking Trans., 4/6.

Tube Mounting Bracket, size 3 1/2 x 4 1/2 in. 12in. tube clamps, 2/-.

Smoothing Choke, 2 Henry 150 mA., 3/6. 250 mA. 3 Henry, 5/-; 250 mA., 10 Henry, 10/6; 5 Henry 250 mA., 60 ohms, 8/6.

P.M. Focus Unit for any 9 or 12in. tube except Mazda 12in., with Vernier adjustment, 15/-, P. & P. 1/6.

P.M. Focus Unit for Mazda, 12in., with Vernier adjustment 17/6. P. & P. 1/6.

Wide Angle P.M. Focus Units, Vernier adj., shade tube, 25/-, P. & P. 2/-.

Energised Focus Coil, low resistance mounting bracket, 17/6 plus 2/- P. & P. Scan Coils, ion line low impedance frame, complete with O.P. transformer. 17/6. P. & P. 2/-.

Ion Traps for Mullard or English Electric tubes, 5/- post paid.

465 Kc. I.F.s, size 2 1/2 x 1 1/2 in. Q.110 removed from American equipment, 5/- per pair. Standard 465 Kc. Iron-cored I.F.s, 4 x 1 1/2 x 1 1/2 in., per pair 7/6.

Wear-in Standard Iron-cored 465 Kc. I.F.s, 3 1/2 x 1 1/2 x 1 1/2 in., per pair 9/6.

Iron-cored 465 Kc. Whistle filter, 2/6.

OUTPUT TRANSFORMERS. Standard type 5,000 ohms imp., 4/9. 42-1 with extra feed-back windings, 4/3. Miniature 42-1, 3/3. Multi-ratio 3,500, 7,000 and 14,000, 5/6. 10-watt push-pull, 6V6 matching 7/-, 90-1 3 ohm speak coil, 6/6.

PUSH-BACK CONNECTING WIRE. Doz. yds., 1/6, post paid.

STANDARD WAVE-CHANGE SWITCHES. 4-pole 3-way, 1/9; 5-pole 3-way, 1/9; 3-pole 3-way, 1/9; 5-pole 3-w.L.S. Miniature type, 100 spindle 2-pole 4-way, 4-pole 3-way and 4-pole 2-way, 2/6 each. P. & P. 3d.

465 Kc. MIDGET I.F.s. Q.120, size 1 1/2 in. long, 1in. wide, 1in. deep by very famous manufacturer. Pre-wound adjustable iron-dust cores, per pair, 12/6.

APPOINTMENTS

In AC and DC laboratory and electronics laboratory

If you have outstanding ability and would like to share in the unique part this company is playing in aviation progress, our Personnel Department will be pleased to know of your qualifications. Immediate Vacancies are limited, but others occur from time to time due to continued expansion. Only men of high calibre, experience and technical attainment will meet the requirements.

DEVELOPMENT ENGINEERS

Minimum requirements are higher national certificate, but an engineering degree is preferred.

ELECTRONICS ENGINEERS

Should have experience in electronic servo systems and, preferably, experience of magnetic amplifiers.

WRITE, AS FULLY AS POSSIBLE, TO THE DIRECTOR OF ENGINEERING, GROUP D, ROTAX LIMITED, CHANDOS ROAD, WILLESDEN JUNCTION, LONDON.

OUTSTANDING OFFERS

- **TRANSMITTERS**
RCA ET-4336, Hallcrafters BC-610, GO-9, all with accessories.
- **RECEIVERS**
AR-77, AR-88, BC-348
- **TRANSMITTER-RECEIVERS**
W/S Nos. 11, 17, 18, 38, 58, 68. SCR-522, SCR-610.
- **RADAR EQUIPMENT**
APS-3, APS-6, BM-1, BN-1, VF, AN/APA, Mk. 26 and AN/APN Series of Radio and Radar Equipments.
- **TEST EQUIPMENT**
TS-10A/APN, TS-36/AP, TS-51/APG-4, TS-56A/AP, TS-127/U, IE-46, Type 205A, Type LR-1, BC-221, AN/UPM, SE-2, 79-B, W1117, etc.
- **MOTORS**
Accelerating, Aircraft, Generators, Dynamotors, Inverters, Rotary Converters, wide range of U.S. production.
- **SPARES**
(Radio and Radar U.S.A.) Full range of spares for most U.S.A. Aircraft, Naval and Ground Radio and Radar Units. (SCR-187, 188, 193/269, 274-N, 287, 399, 508-10, 17, 536, 566, 593, 608-10 (very large quantities) 694, 695; MRN-3, TRA-1-ABK, BM, BN, SM, SO, SQ, SK, APS-2, 3, 4, 6, 15 etc.), Klystrons 2K33.
- **AIRCRAFT INSTRUMENTS & ACCESSORIES**
British and U.S. (catalogues supplied upon request).

SPECIAL EQUIPMENT (NOT ADVERTISED ABOVE) AVAILABLE FOR N.A.T.O. GOVERNMENTS AND THEIR ACCREDITED CONTRACTORS.

All enquiries to be addressed exclusively to

BRITISH SAROZAL LTD.

(Head Office)

1-3 MARYLEBONE PASSAGE, MARGARET ST., LONDON, W.1

Telephone: LANgham 9351 (3 lines).

Cables: Sarozal, London

ALL EQUIPMENT AS ADVERTISED IS AVAILABLE FOR IMMEDIATE DELIVERY FROM STOCK AND IS FULLY CHECKED AND TESTED—PRIOR TO DESPATCH—IN OUR OWN WORKS AND LABORATORY.

We buy for cash American surplus equipment.



Late ALEC DAVIS SUPPLIES LTD.

RELAYS

D.C. COIL RESISTANCE

3,000 TYPES: 1.9Ω to 80,000Ω
600 TYPES: 0.4Ω to 9,200Ω.

ALSO LARGE STOCKS OF DOUBLE & TRIPLEWOUND AND SLUGGED COILS. SIEMENS TYPE HIGH SPEED


CONTACTS

3,000 TYPES: up to 8 sets.
600 TYPES: up to 4 sets.


3,000 TYPES: Make (M), Break (B), in Twin-silver Twin-platinum, Dome-silver (2 amp.), Tungsten (5 amp.), and Flat-silver (8 amp.). Change-Over (C), in all but Tungsten: Make-Before-Break (K), in Twin-silver and Twin-platinum.

600 TYPES: (M), (B) and (C), in Twin-silver and Twin-platinum.

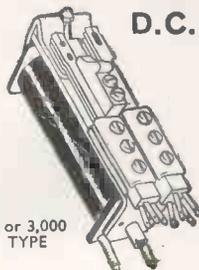KEY SWITCHES.
2 C/O, to 8 C/O. Special types made up to order.



600 or 3,000 TYPE

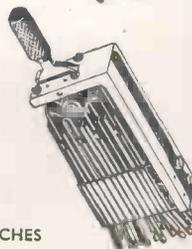

KEY SWITCHES

Wireless World Classified Advertisements

Rate 7/- for 2 lines or less and 3/6 for every additional line or part thereof, average lines 6 words. Box Numbers 2 words plus 1/-. (Address replies: Box 0000 c/o "Wireless World" Dorset House, Stamford St., London S.E.1.) Trade discount details available on application. Press Day: April 1954 issue, Tuesday, March 2nd. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components and valves which may be offered for sale through our columns carry no manufacturers' guarantee: Many of these items will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such items purchased.

NEW RECEIVERS AND AMPLIFIERS
ALL types of audio equipment designed and built to order.—Bernard J. Brown, 33, Goldhawk Rd., London, W.12. [0024]

12-watt high quality amplifiers, bass and treble boost; £12/15; lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [10065]

TRIUMPH AMPLIFIERS offer a new push-pull 10-watt high fidelity amplifier with remote tone control unit, £16/10 complete; illustrated list available.—Triumph Amplifiers, 26, Lower Richmond Rd., London, S.W.15. [2466]

C.J.R. ELECTRICAL & ELECTRONIC DEVELOPMENT, Ltd., Beckford Rd., Witton, Birmingham. (Eas. 0435), the Midlands specialist manufacturers of high fidelity sound reproduction equipment for the world-famous Williamson amplifier and associated accessories, including tone control stages, loudspeaker crossover units, distortionless contrast extenders and radio feeders; send for details and prices. [0105]

NEW TV RECEIVERS AND AMPLIFIERS
A QUANTITY of Ekco Television pre-amps. A new (in packs), model LG4 150 (Sutton Coldfield).—Offers to Crane & Sons, Ltd., Hanover St., Liverpool, 1. [2356]

RECEIVERS, AMPLIFIERS—SURPLUS AND SECONDHAND
SURPLUS amplifiers. [0035]

OFFERS invited for batches of 10 upwards for 1,000 4-valve push-pull speech amplifiers, 100 volt a.c.-d.c. operation approx. 2 watt output. THESE may be seen and tested at the works of Dictaphone Co., Ltd., 28-30, Telford Way, East Acton, W.3. **PHONE** for further details, Shepherds Bush 6141. [2358]

EDDYSTONE 740 receiver, 'phones, speaker, felt-lined box, £35 o.n.o., as new.—Box 3200. [2469]

1355 Sound Receivers, sealed boxes as purchased, R.A.F. 27/6, carr. 7/6.—Smith, Highworth Rd., Faringdon, Berks. [2391]

HERO RX's and coils in 'ock, also AR88, BC348R, CR100, etc.—Requirements please to R. T. & I. Service, 25d, Grove Green Rd., London, E.11. Ley. 4986. [0035]

R.C.A. AR77E complete with speaker and manual, Volt corner horn speaker with twin cone unit and metal rectifier for speaker field.—Offers to Thrift & Co., Penn Fields Terminus, Wolverhampton. [2341]

SOUND SALES DX3 5-waveband tuner, £18; Williamson amp., £10; Goodman's speaker, 12in. in box, baffle, £10; Baker 8in speaker, £4; all n.o.—55, Ranelagh Rd., Southall. [2351]

RECEIVERS, AMPLIFIERS—SURPLUS AND SECONDHAND WANTED
SX28A wanted by enthusiast, London area. Must be in mint condition.—Price and full particulars to Box 2818. [2365]

TV RECEIVERS AND AMPLIFIERS—SURPLUS AND SECONDHAND
PREMIER London TRF vision strip, built and tested; offers?—Box 2711. [2359]

NEW LOUDSPEAKERS
THE superlative Barker Duode reproducer now available at 12gns (post paid), tax free.—Order now or send for full details to Fred Whitehurst, 109, Burnley Rd., Accrington. [2357]

LOUDSPEAKERS—SURPLUS AND SECONDHAND
LARGE R.C.A. H.P. speaker, sectional horn, 100v field, immaculate; offers.—Box 2857. [2377]

NEW DYNAMOS, MOTORS, ETC
BATTERY chargers, 4 models, 2-6-12v, 1-2-4 amp D.C. any mains voltage; also larger types special transformers, chokes, test gear, interior car heaters, etc.—The Banner Electric Co., Ltd., Hoddesdon, Herts. [0112]



*They sought it with thimbles,
they sought it with care,
they pursued it with forks and hope,*

"The Hunting of the Snark." Lewis Carroll.

*The element of blind optimism
has long disappeared from
scientific research and the designer*

*needs no such hit or miss method
today. His brain-child can be
electronically tested and proved from
the earliest stages of conception.*

*The superhuman precision of
electronics demands transformers
of the highest characteristics—*

in fact, Partridge Transformers.



CFE—acknowledged the ultimate in 'C' core technique. Technical data sheet No. 3 on request.



**PARTRIDGE
TRANSFORMERS LTD
TOLWORTH SURREY**

NEW DYNAMOS, MOTORS, ETC.
ALTERNATORS. 230V/150, 400VA, self-energised 3,000rpm, ball bearing, £23/15 del., also special television model same price; voltage regulator 30/- extra. **J.A.P. No. 2A** 1.2hp petrol engine, air-cooled, 4-stroke, starting rope, tools; £17/10 delivered for above alternators. **SPECIAL** rotary converters, guaranteed interference free, fitted radio and television filters. w.t. 60lb; d.c. input 12V 200va, out. 24v, 32v, 50v, 110v, 230v d.c. to 230v, out. 250va, £28/10 del.; also converters for radiogram and general use, inputs, outputs and prices as above; the above also supplied without smoothing, £25 del. immediate despatch; trade supplied. **AT** a purchaser's home 60 mls. S.W. of Sutton Coldfield a 24v. **TELEVISION** converter was tested on Ekco television, 12in tube, stated consumption 135 watts d.c. current from battery only 9½amps, picture and sound were perfect and completely free of interference or flutter. **THE** above are the latest products of British manufacture, and are guaranteed for one year; fullest details of plant, alternators or 400VA alt. or rotary converters, by return post; state which required; terms c.w.o., pro forma invoice c.o.d. (post goods only). **T. W. PEARCE**, 66, Great Percy St., W.C.1 (near Angel). [0013]

ALL types of rotating electrical machinery up to 20kva available, including rotary converters, rotary transformers, motors, petrol and diesel-engined generating plants, alternators and d.c. generators. We are also in a position to quote for power transformers; as actual manufacturers we will be glad to quote for any quantity for home or export. **DIESEL** electric generating plants, 3kva, 230v, with push-button remote control, starting equipment ready for use; £225. **DIESEL** electric plants, special offer.—Diesel electric generating plants, comprising a Petter type AV2 twin cylinder engine, direct coupled to a 6kva 230v, single phase alternator with push-button remote control starting and stopping; limited number only owing to frustrated export order; price £280 each delivered anywhere in United Kingdom. **CHAS. F. WARD**, Lordscroft Works, Haverhill, Suffolk. Tel. 253. [0039]

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND
E.D.C. rotary converter, fitted radio filter, input 110 A.C., output 220 A.C., 1 amp.; guaranteed condition; £20, nearest.—Nicholls, Dolven, Llandawey, Radnorshire. [2447]

ROTARY converter, 230v d.c. to 230v a.c., 2 amps. 1/4hp, 230v d.c. motor and 1hp 230v d.c. motor; £15 the lot, offer or exchange test equipment; buyer collects, Ilford, Essex.—Lanham, 12, Cecil Rd., Harlesden, N.W.10. [2333]

TEST EQUIPMENT—SURPLUS AND SECONDHAND
MURPHY all-wave oscillator type M.1. 200-250v A.C.; £10.—Watson, Radio, Banff. [2477]

A QUANTITY of radio test equipment for sale.—Rellance Radio (Sudbury), 4, Station Rd., Sudbury, Suffolk. [2399]

MEISSNER signal shifter, £20; S.40, £30; Q max. absorption meter, 12/6; Q max. tank unit (150w), £4/10; UM3, £3; two Cydon 100pfd, 10/- each.—Box 2691. [2334]

SIGNAL generators, oscilloscopes, output meters, valve voltmeters, frequency meters, multi-range meters in stock; your enquiries are invited.—Requirements to R.T. & I. Service, 25d, Grove Green Rd., London, E.11. Ley. 4986. [0056]

NEW GRAMOPHONE AND SOUND EQUIPMENT
FERROGRAPH magnetic tape recorder, models 2A and 2B now available, from 76gns.

WEARTE tape decks, and component parts. **DISC** recording machines and blank discs. **MAGNETIC** tape—Ferroglyph. Scotch-boy, etc. **RESLO** ribbon microphones and stands. **EVERYTHING** for the professional recording studio. **SOUND DISCS (SUPPLIES)**, Ltd., 178, Bishopham Rd., Southport, Lancs. Tel. 88153. [2314]

RAESOUND home audio, Hi-Fi amplifier and T/C unit; £24/10; send for details.—R.A.E., 377, High Rd., London, N.2. [0213]

**FOR
SALE AND WANTED
ADVERTISEMENT FORM
TURNS TO
PAGE NO. 147**

INVITATION from

Holley's

TO ATTEND A REPEAT PERFORMANCE OF THE ORIGINAL SOUND

Full Stocks of Leading Lines by:—

LEAK, QUAD, WHARFEDALE, W.B., SOUND SALES, GOODMANS, ROGERS, DECCA, CONNOISSEUR, BARKER, CHAPMAN, TANNON, LOWTHER, ARMSTRONG AND GARRARD.

LIMITED STOCKS of
WHARFEDALE WISCS at £16 each. List price now £17/10/-; also **S.T.C. MICROPHONE HEADS** (as illustrated in last month's "Wireless World") £9/15/- each. These are slightly used but in good working order.

CABINETS TO HOUSE ALL TYPES OF HI-FIDELITY EQUIPMENT. S.A.E. for Photos, sizes and prices.

Hire Purchase terms arranged. **DAILY DEMONSTRATIONS**, Technicians will install our equipment in your home to the best acoustical advantage.

285, CAMBERWELL ROAD, S.E.5
Telephone: **RODney 4988**
Hours: 9-30—6 p.m. Thursday 8-30—1 p.m.
OPEN ALL DAY SATURDAY

SURPLUS

- **TECHNICAL MANUALS.** Official U.S. Army (not photostats) varied stocks include ET4331/2/6, BC-221, BC-342, BC-610, BC-640, AR-88, SCR-522, SCR-508, BC-191, etc., etc.
- **TRYLON LATTICE LADDER TOWERS.** 50ft. and 100ft. high triangle section 12in. sides, highest possible quality complete with all hardware, galvanised and painted. Brand new in original cases.
- **TRIPLE DIVERSITY RECEIVERS.** 1.5 to 30 Mc/s. Built-in loud speaker and power supply. Precision H.F., L.F. and B.F. Oscillators. Variable gain and selectivity. Band pass and tone facilities. Full technical details and photo available.
- **R.C.A. AERODROME AMPLIFIER SYSTEMS.** Include 12-25-watt outside speakers on stands with amplifier and control panels in portable cases. Individual and master control. Built-in warning and all clear sirens. Each speaker audible one mile and reversible as microphone. Brand new.
- **100-WATT BROADCASTING TRANSMITTERS.** British made by Woden. Self-contained in 4ft. 6in. metal cabinet. Input 200/250 v. A.C. Output 250-watt triode. Price £22/10/-.
- **RACKS.** 5ft. 6in. high Channel Iron and shock base or angle iron types, with drilled and tapped sides, also 3' 6" high.
- **TRANSMITTER COMPONENTS,** include all types of transformers, condensers, chokes, relays, etc., etc.
- **INSULATORS.** Large quantities of over 50 different patterns.

Many other items too numerous to mention. Send your requirements. Lists available. All packing and shipping facilities.

H. HARRIS

ORGANFORD DORSET

Telephone: Lychett Minster 212

NEW GRAMOPHONE AND SOUND EQUIPMENT

F.M. hear the ultimate in transmitted quality without background noises, on V.H.F.—Ring Arc. 5078 for demonstration. Bel, Marlborough Yard, N.19. [0185]

A NEW compact tape deck, taking 600ft reels, size only 11inX7in, best quality heads; price £8/18 complete; send stamp for details to—E.W.A., 266, Warbreck Drive, Blackpool. [2140]

C.J.R. ELECTRICAL & ELECTRONIC DEVELOPMENT, Ltd., manufacturers of high quality portable and console magnetic tape recorders for professional and amateur use; full details on application. BICKFORD Rd., Witton, Birmingham, 6. East 0822. [2056]

PRE-AMP/RECORD units for use with Leak, Q.U.A.D., etc., with meter level ind. to suit Bradmatic, Truvox, etc., now £16; to suit Wearite, 17gns; this unit gives you first-class recording with playback via your Hi-Fi amp. AMPS. to suit Wearite 2A (EL24), 5 watts output, 21gns, and £32 for 12 watts P.P. with meter and Partridge out. trans. MOTEK amp. to spec. £11; others for Truvox, etc., 12 watts P.P. £21. **EARDING ELECTRONICS.** 120a, Mora Rd., London. N.W.2. [2385]

CINE-VOX disc recording equipments, type CTJ for high-quality recordings from existing microphone equipment, price from 28gns; also available as a complete channel inclusive of mic., amplifier and playback equipment, at 70gns; type C7, for highest quality professional requirements—recorder mechanism at 48gns, or complete channel at 110gns; demonstrations arranged in London. **PLEASE** write for details to K.T.S., Ltd., 60, Aylward Rd., London, S.W.20 (Liberty 2426). Callers by appointment only. [0209]

GRAMOPHONE AND SOUND EQUIPMENT —SURPLUS AND SECONDHAND

B.B.C. professional dual speed disc cutter, motor scroll, 15ohms, excellent condition; £62.—Box 3180. [2467]

WEARITE 1A tape deck, almost brand new, exceptionally quiet; £27.—Bazire, Vicarage, Lavender Gdns., Battersea 5953. [2455]

TAPE recorders, shop soiled, Emicorda 90gns reduced to 70gns; Sound Mirror, 70gns reduced to 50gns.—Tel. Ley. 1362. [2402]

SOUNDMIRROR portable tape recorder, perfect, Acos mic., 3 reels of tape, £60 o.n.o.—Buckby, Sun Inn, St. Austell, Cornwall. [2409]

C.J.R. tape recorder, D1 with Reslo ribbon mike, 3 tapes, cost £125, little used; nearest £80 secures; owner going abroad.—Box 2997. [2408]

FOR sale, 2 Wirek wire recorders, model B2 with accessories, in excellent condition; will accept reasonable offer.—R. H., 103, Borough Rd., S.E.1. [2476]

FERROGRAPH tape recorder, latest 2A model November, 1953, £69; would exchange for disc recorder, late model and perfect, or would purchase same for cash.—Box 2587, c/o W.W. [2313]

BOOSEY & HAWKES type wire recorder combined with record player, excellent condition; £28.—Burgess Lane & Co., Block J, Sunleigh Wks., Sunleigh Rd., Wembley, Wem. 2378. [2135]

ANY of you tape types building your own? Although we deal primarily in sub-standard cine equipment, it's quite possible that our "Bits and Pieces" list might be useful, s.a.e. please. We also wish to buy tape deck, S. recorder components, etc.—Burgess Lane & Co., Block J, Sunleigh Works, Sunleigh Rd., Wembley. Tel. Wem 2378. [0253]

NEW COMPONENTS

FOR really good results you can do no better than use Osom coils and coilpacks, ask anyone of experience! Send 5d (stamps) today for beautifully-drawn free circuits, our new coil-data leaflets, and latest lists of matched radio components. A speedy mail order department is at your service, and remember, all Osom lines are guaranteed. (Trade enquiries invited.) Dept. C.W.1. **OSMOR RADIO PRODUCTS, Ltd.**, Bridge View Works, Borough Hill, Croydon. Tel. Croydon 5148-9. [046]

70cm television, converter components, as "W.W." January; 8-piece inductance set, 15/-; completed converter with power supply, £15. 3/4in sq canned formers, 2/3 ea.; experimental transistors (callers only); Chanons economy battery set, coil sets, complete 35/- V.H.F. Hi-Fi F.M. receivers, complete parts kit, with valves, wound coils, chassis, £7/5.—Bel Sound Products Co., Marlborough Yard, N.19. [0186]

FLUORESCENT 80 watt 230v complete ballast unit, 39/6; 80w brick choke and starter lamp, 14/6; 40 watt complete ballast 230v, 28/9; complete fluorescent fittings from 45/-; metal reflectors, 12v 4amp 1/2w bridge, 13/9; suitable charger transformer, 16/6; 0-4 ampmeter, 8/6; brand new small radio cabinets, 16/6; multi-ratio output transformers, Goodmans, 7/6; Diamond H switches, 4/6; 4-pole cooker switches, 5/-; charge your dry cell batteries with our special charger from mains, complete unit, 14/9; new C.B.C. 1/2hp electric motors, 230v 8/p, £4/16.—Malden Transformer Supplies, Rear of 5, Coombe Rd., New Malden, Surrey. Mal. 2655 (Longside of Malden S.R. Station). [0038]



Solons save time, reduce costs. Solon soldering is always clean, reliable and simple. Five models, in voltage range 100-250; each with 6 feet Henley flexible. 65 watt; oval tapered or round pencil bits. 125 watt; oval tapered or round pencil bits. 240 watts; oval tapered bit.

Write for Folder Y.10



FULL

CONSTRUCTIONAL DETAILS

for building

9

FIRST-CLASS SUPERHETS

including 3 and 4 valve Feeder Units, 5 and 6 valve Receivers.

also

circuits of TRF Receivers, 10-watt Quality Amplifier, Crystal Set, etc., Soldering, Metal-working, Constructional and Servicing Notes, Coil Pack Constructional Details, Resistance Code, Useful Data, etc., all included in The

"HOME CONSTRUCTOR"

PRICE 2/6 ONLY

Complete with fully illustrated catalogue, Obtainable from Radio Dealers and Stationers, or in case of difficulty send direct to

SUPACOILS, 21, Markhouse Rd., London, E.17.

Hi-G Heads for Acos GP20

All users of this popular pick-up will welcome the improved HGP39 heads. Standard or L.P., 42/3 each.



W. B. STENTORIAN HF1012

No loudspeaker has gained such popularity within so short a time as this new 10in. unit.

The unique cone-construction puts bass resonance as low as 35 c.p.s. and output is well maintained to the higher frequencies. A powerful magnet of 12,000 gauss is employed, and the speaker will handle up to 10W. 3 or 15 ohm. High fidelity speakers have until now been priced considerably higher, and the performance of this speaker at only 73/6 has been a revelation to all who have heard it.

Also 9" 67/-d., 8" 60/8d., 6" 50/8d.

"The Gramophone" AMPLIFIER

Performance vies with the most expensive models, yet inherent simplicity makes it much lower in cost. We offer it either ready built or in kit form.

Amplifier 17 gns. Complete with valves, tested.
Pre-Amplifier for magnetic p.u., 5 gns.
Control Unit for crystal p.u., 45/-.

Extended Payment Terms

Amplifier and Pre-Amp. £7/14/- and 12 monthly payments of £1/8/3.
Amplifier and Control Unit £6/14/- and 12 monthly payments of £1/4/6.

9 w. output, 20 dB. feedback only 0.1 per cent harmonic at 5 w. 20-20,000 o.p.s., latest Mullard valves, 3/15 ohm output, 200-200 v. A.C. mains.
Home Construction details 1/9 post free.

RECORD MAIL SERVICE

Order your L.P. records by post with the assurance of factory fresh, perfect copies. **POST FREE in U.K.** Cash with order or C.O.D. Overseas Tax free at only 4/5ths home prices incl. postage and packing. Monthly RECORD REVIEW annual subscription 11/-.

QUALITY MART

8, Dartmouth Park Avenue, London, N.W.5. GULIVER 1131.

Order by Mail. Demonstrations by Appointment.

NEW COMPONENTS

CRYSTAL microphone inserts (Cosmocord Mic-8), guaranteed brand new: 15/6, post free.—Radio-Aid, Ltd. (Retail Dept.), 29, Market St., Watford. [0036

COMPONENTS—SURPLUS AND SECONDHAND

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188. ELECTROLYTICS, capacity, voltage, size, type of mounting, price post paid: 400. 6v, 1x2in. lug. 1/9; 250+250. 6v, 1x2in. lug. 2/-; 500+250. 6v, 1x3 lug. 2/-; 40+40. 150v. 1x2. clp. 2/9; 40. 150v. 1x2. clp. 2/6; 20+20. 275v. 1x2. lug. 3/3; 16+32. 275v. 1x2. lug. 3/3; 16+16. 275v. 1x2. clp. 3/3; 32+32. 275v+50mfd. 25v. 1x3. lug. 3/6; 60+100. 275v. 1x3x5. lug. 4/6; 100. 275/350v. 1x4x4. clp. 3/6; 32+12. 350v. 1x4x2. clp. 4/-; 16+16+16. 350v. 1x4x2. clp. 1x2. 4/9; 16. 350v. 1x4x2. lug. 1/9; 40+40. 300v. 1x3. lug. 3/6; 10. 450v. 1x2. lug. 1/6; 16. 450. 1x2. tag. 2/9; 20. 450v. 1x2. lug. 2/3; 32. 450/525v. 1x2. clp. 3/9; 30+30. 450v+20mf. 25v. 1x3x3. lug. 5/-; 15+15. 450v+20mf. 25v. 1x3x3. lug. 4/6; 200. 6v. 1x1x1. clp. 1/6; 100. 12v. 1x1x1. clp. 1/9; 8. 450v. 1x2. clp. 2/-; 50. 12v. 1x1x1. tag. 1/6; 150. 25v. 1x1x1. clp. 2/-; 250. 12v. 1x1x1. wire. 2/3; 350. 25v. 1x2in. clp. 2/6; 16+16. 450v. 1x2. clp. 4/-; 40+40. 275v. 1x2. clp. 3/3; 24+24+16. 350/425v. 1x4x2. clp. 4/9. 60+200. 275/350v. 1x4x4. clp. 6/6; 4. 150v. 1x1x1. clp. 1/1; 500. 12v. 1x4x2x2. clp. 2/-; 3. 350v. 1x2. clp. 1/1; 100+175. 275/350v. 1x4x4. clp. 6/6; 32+32. 350/425v. 1x4x2. clp. 5/-; 8+16. 450/525v. 1x2. clp. 4/-; 2. 450/525v. 1x1x1. tag. 1/6; 2. 350v. 1x1x1. tag. 1/3. 1,000. 6v. 1x2. clp. 2/9. 8. 450v. 1x2. clp. 1/9; 6,000. 6v. 1x3x3. clp. 4/9; 32+32. 450/525v. 1x4x2. wire ended. 5/6; all all caps, some with sleeves. W.K.G. surge where marked new stock, guaranteed.

TELEVISION! Set of 3 components, comprising line output trans., with E.H.T. winding to give 7kV using EY51 (heater winding for EY51 also included) and fitted with width control setting coils, low impedance line and frame, focus coil (res. 10,000), current approx. 20 mA); the set of 3 for 42/-, plus 2/- post, diagram of line trans. supplied.

PERSONAL receivers, 3 valve T.R.F. using IT4s, contained in handsome bakelite case with lift up lid, size 7x6x5 1/2in with lid closed, plastic carrying handle, fram. AE in lid, these receivers cover the medium waveband and operate from self-contained dry batts, standard types, W1435 and U2, output to a pair of lightweight 'phones (H.R.), controls, SM tuning and reaction, opening lid switches on supplied brand new, with valves, batteries, 'phones, an ideal set for invalids hos. patients, etc., these receivers are not Govt. surplus and are offered ready to play; carr. paid 24/10.

UNIVERSAL amplifiers, 8-valve 20watt A.C./D.C., black crackle chassis, and black and chrome cover, overall size 15 1/2in x 7 1/2in x 7in. First-class components (Partridge O.P.T. and driver, gardner choke, A.E.E. Mu-Metal input trans. for mike). Valves, 2XEP37, 4XCL33, 2XUR3C. Switched input for high or low imp., top cut and bass cut switches, V.C. mains switch, mains plug and socket, 220-250v, isolated chassis, 150l output. Wired and tested, ready for use, with valves, brand new. £10/19/6, carr. paid.

5 mA meters, moving coil, Bakelite case, 2in square, flush mounting, new, boxed; 8/- post paid.

MAINS trans., 250-0-250v. 80ma. 6.3v. 2.5A. 6.3v. 0.6A. Pri. 0-110-210-240v. 12/- post paid.

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188. 10015

SUPREME RADIO, 746B, Romford Rd., Manor Park, London, E.12. Tel. III. 1260. Est. 17 years.

BARNS for radio and T/V constructors:—METAL rectifiers: R.M.1, 3/11 ea. R.M.2, 4/3. R.M.3, 5/11 ea. R.M.4, 18/- ea. Westinghouse type metal rectifier 14A46, 250v 60m/a. 7/9 ea. SMALL vol./controls, with long spindle and s/p switch, 1meg, 1/2meg, or 1/4meg, 2/6 ea.; with d/p switch, 3/- ea.

FILAMENT trans.: Primary 0-250v. Sec.: 6.3v. 1.5amp. 5/9 ea. or 3amp type, 8/9 ea.

NEW stocks electrolytics: Small metal can types. 16mfd 350v. 1/11 ea. 16+16mfd 350v. 1/11 ea. 16+24mfd 350v. 2/6 ea. 32mfd 350v. 2/6 ea. 32+32+16mfd 350v. 3/6 ea. Special bargain 32+32mfd 450v. 550v surge, 1 1/2in dia., 4/11 ea. 60+150mfd 275v D.C. wkg. 1 1/2in dia., 4/11 ea.

TUB/card w/end types: 4mfd 450v. 1/11 ea. or 500v type, 2/9 ea. 4mfd 150v drylytic type, 10d ea.

STILL, a winner! Mains trans: by "Parmeko" universal fixing. Primary tapped 0-200-220-240v. Sec. 290-0-290v. 80m/a. 6.3v 3amp and 6.3v tapped 4v 2amp, with screen; our price 15/11 ea. inc. pack/post.

POPULAR bargain buy: Mains trans. with vol./panel, tapped primary 0-200-210v, 220-230v, 240-250v, secondary 250-0-2250v 60 m/a with 6.3v tapped at 5v; our price 11/9, inc. p./post. AMAZING value in speakers! All 2-ohm v. coil. 10in P.M. 17/6 ea. 8in P.M. 13/11 ea. 6 1/2in P.M. 12/11, 5in P.M. 12/6. Popular lines: Crystal diodes, with crystal set circuit, 1/6 ea. 28-way tag strip—break it as required, 1/- ea. 2p-2way w/change switches, 1/- ea. or 10/6 pr. doz. Popular value 1/4 and 1/2watt resistors, 4/- doz. Many other super bargain lines in stock.

TERMS, c.w.o., no c.o.d. Send 9d extra for postage orders under £5. 2 1/2d a.s.e. all enquiries and list. [0021

SOUTHERN RADIO SUPPLY, Ltd., 11, Little Newport Street, London, W.C.2. See our displayed advertisement, page 136. 10016

Armstrong

Specialists in the manufacture of the HIGHEST QUALITY CHASSIS for over 20 years



Mode FC.38

MODEL FC.38 An 8 valve Super-heterodyne chassis giving 8 watts push-pull output with negative feedback and separate BASS and TREBLE lift controls, Flywheel tuning and a magic eye. Three wavebands covering 16-50 metres, 190-550 metres and 1,000-2,000 metres. PRICE £23/13/-, including tax.

MODEL RF.41 A 10 valve Super-heterodyne chassis giving 10 watts push-pull output with negative feedback and separate BASS and TREBLE lift controls, also a highly sensitive R.F. stage before the mixer. Flywheel tuning and a magic eye. Four wavebands covering 12-90 metres, 190-550 metres and 800-2,000 metres. PRICE £31/19/8, including tax.

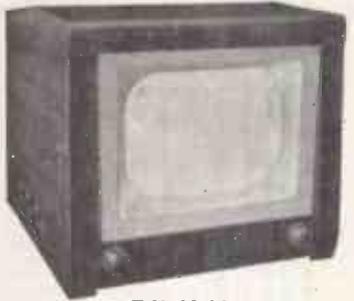


Table Model

TV.5 TELEVISION RANGE

A 19 valve Superheterodyne Circuit with instantaneous 5 channel selector switching and aluminised rectangular flat-faced Cathode Ray Tube with tinted filter. 14in. and 17in. Models available.

THE T.V. THAT HAS THE TRUE BLACK AND WHITE PICTURE


PRICES:

- TV.5 14in. Chassis, £54/0/3 (inc. P.T.).
- TV.5 14in. Table Model, £61/19/- (inc. P.T.).
- TV.5 14in. Console, £72/9/- (inc. P.T.).
- TV.5 17in. Chassis, £64/15/11 (inc. P.T.).
- TV.5 17in. Console, £82/19/- (inc. P.T.).

Our Showroom at the address as below is open daily from 9 a.m. to 6 p.m. (Saturdays 5 p.m.) and we are always delighted to demonstrate any of our Models or supply any information regarding them. If unable to visit us please send for specifications required.

WIRELESS & TELEVISION CO. LTD. WALTERS ROAD, HOLLOWAY, LONDON, N.7 Telephone: NORth 3213/4

TUNERS

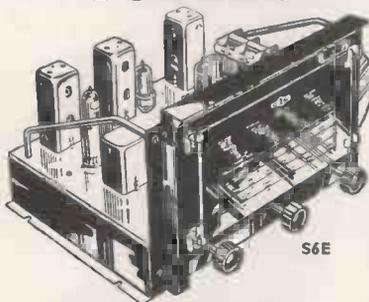

S6E

- S6BS** 9 Band (6 Electrical band spread) with R.F. F.C. 2 I.F. Delayed Amplified A.V.C. Variable Selectivity. Fly Wheel Tuning. Tropicalised. Suitable for use with any High Quality Amplifier. £44. Tax paid.
- S6** A new model similar to the well-known S6BS but only 3 Wave Bands; 16m-50m, 195m-550m, 800m-2,000m. £30. Tax paid
- S6E** As S6 but 4 Wave Bands; 12.5m-37m 35m-100m, 90m-250m, 190m-550m. £30 Tax paid.
- S5** 3 Wave Bands, 16m-2,000m, R.F. pre-Amplifier, variable selectivity I.F. Delayed amplifier A.V.C. £21/6/8. Tax paid.
- S5E** As S5 but 12.5m-550m. £21/6/8. Tax paid.
- S4** The Standard high-quality Feeder Unit. Specification as S5 but without R.F. amplifier. £16. Tax paid.

A modified version of all models is available for use with Leak, Acoustical and other High Quality Amplifiers.

C. T. CHAPMAN (Reproducers) LTD.
RILEY WKS., RILEY ST., CHELSEA, S.W.10
FLAxman 4577/8
Export Enquiries Invited

WANTED. EXCHANGE. ETC.

VHF test equipment.

TS47AP, TS174, TS175/U, TS148 or TSX-45E; analysers; BC221 freq. meters; TS69, and any U.S.A. test gear; Klystrons type 723/AB, 2K33 2K39 2K41; receiver, APR4 and units TN16 17-18-19; RCA AR88D, S27 and SX28s and S27CA; microwave equipment; highest offers given by return.—Ger. 9410. Universal Electronics, 27 Lisle St., Leicester Square, London, W.C.2. [0229]

WANTED, Wilcox Gay V.F.O. units in new or modified condition.
MCLEROY-ADAMS MFG. GROUP, Ltd., 46, Greyhound Rd., London, W.6. Tel. Fulham 1138/9. [0194]

30 amp change-over switches, sliding resistances, 30hm 15amp.—Box 2867. [2352]

WANTED, receivers A.P.R.4, also T.N. 16, 17, 18, 19, etc., and any radio test gear.
LESLIE DIXON & Co., 214, Queenstown Rd., Battersea, S.W.8. Macaulay 2139. [0176]

WANTED, General Electric variable reluctance pick-up.—Box 2867. [2400]

WANTED 240v solenoid, about 1in pull.—Ward, 11, Gover Lane, Newquay, Corn. [2421]

WANTED, R.C.A. transmitters, all types or any R.C.A. components, including chassis and metal work.
MCLEROY-ADAMS MFG. GROUP, Ltd., 46, Greyhound Rd., London, W.6. Tel. Fulham 1138/9 [0196]

A COLLINS 75A receiver wanted.—Parvin, 19, Fellbrook Ave., Acomb, York. Tel. 78283. [2525]

72 in metal projection horns, state price.—Radiovox, Ltd., 5, Oxford Place, Leeds, 1. [2537]

GOOD quality tape desk or recorder, Grundig, Wearite, etc.—45, Rookery Lane, Lincoln. [2464]

WANTED, TCS/6 or TCS/12 transmitters in mint condition; also control boxes for same.
MCLEROY-ADAMS MFG. GROUP, Ltd., 46, Greyhound Rd., London, W.6. Tel. Fulham 1138/9. [0195]

WANTED.—Receiver B.28 coil unit, as recently advertised by Messrs. Cohens.—Pritchard, The Priory, Tebury, Glos. [2446]

WANTED, set manufacturers' or ex-Government radio equipment, large or small quantities of valves, electrolytics, speakers, meters, also components.
LOWE BROS., 5, Fitzroy St., London, W.1. Tel. Museum 4389. [19745]

WANTED, HRO coils, Rxs etc., A.R.88s, BC348s, S27s, etc.—Details to R.T. I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. [0163]

WANTED, three pre-war Wearite Unigen dual-wave coils matched; other matched screened H.F. transformers considered.—Willson, 38, Silver St., Bradford-on-Avon, Wilts. [2380]

NO. 10 headsets or No. 13 microphones, large or small quantities required top prices paid.—Industrial Suppliers (Cambridge) Ltd., 15a-17, Brecknock Rd., London, N.7. Gulliver 5891. [2018]

ALTHAM RADIO Co. pay highest prices in the trade for all American equipment, including test sets, transmitters, receivers, etc.—Jersey House, Jersey St., Manchester, 4. Tel. Central 7834-5-6. [0228]

URGENTLY wanted, manuals or instruction books, data, etc., on American or British Army, Navy or Air Force radio and electrical equipment.—Harris, 93, Wardour St., W.1. Tel. Gerrard 2504. [2369]

WANTED, BC-610 Hallicrafters, RCA-4336 transmitters SX-28, AR-88, S-27, HRO receivers and spare parts for above; best prices.—P.C.A. Radio, Office and Works, Beavor Lane, Hammersmith, W.6. Tel. Riv. 8006. [0080]

WANTED, AN/APR-4 receiver, any units; any other good quality U.S. surplus radio and radar tubes, test sets; laboratory equipment, etc.; give condition and price in first letter.—Engineering Associates, 434, Patterson Rd., Dayton, 9, Ohio, U.S.A. [0234]

WANTED, R.C.A. speech amplifiers, type MI-11220, J or K, and aerial tuning units BC 939A.—Offers, stating quantity and price, to P.C.A. Radio, Office and Works, Beavor Lane, Hammersmith, W.6. Tel. Riv. 8006. [0079]

WANTED, good quality communication rxs.—domestic radios, test equipment, etc.; top prices paid, established since 1937.—Miller's Radio, 38a, Newport Court, 1 min. from Leicester Sq. Tube. Tel. Ger. 4638. Call, write or send. Hours of business 10-6 p.m. Open all day Saturday. [0199]

WANTED, signal generators types 30, 31, 51, 53, 54, 56 and 101, also any American test equipment with prefix TS or BC. American receivers types AR88, APR4 or similar.—Send price and details to Hatfield Instruments, Ltd., 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing 0779/9857. [0037]



THE "FLUXITE QUINS" AT WORK

"You've landed yourself in a fix
Not to mention our set's gone for size!
You'd fixed your wire tight
With FLUXITE all right
But gas pipes and earth wires don't mix!"

See that **FLUXITE SOLDERING PASTE** is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all Ironmongers—in tins from 1/- upwards.

TO CYCLISTS. For stronger wheels that will remain round and true, here's a time tested tip. Tie the spokes where they cross with fine wire **AND SOLDER.** It's simple—with **FLUXITE**—but **IMPORTANT.**

FLUXITE

SOLDERING PASTE

A Staunch Companion to Fluxite Soldering Fluid.

SIMPLIFIES ALL SOLDERING
Write for book on the Art of "SOFT" soldering and for leaflets on **CASE-HARDENING STEEL** and **TEMPERING TOOLS** with FLUXITE.

FLUXITE LTD.
BERMONDSEY STREET, LONDON, S.E.1.

LEWIS RADIO CO.

invite you to send 1/- for our 1954 Catalogue of ALL types of:—

CABINETS
AUTO-CHANGERS
RADIO AND TV CHASSIS
AND LOUDSPEAKERS

CABINETS

made to individual specification.

TAPE RECORDERS

Send for full details of the "ELIZABETHAN" Portable 2-speed Tape Recorder at 48 gns. All "Soundmaster" parts stocked—send for list.

TELEVISION

All "Viewmaster" and "Tele-King" parts stocked. Send for our lists.

AMPLIFIERS

Full details available of our 4½ and 5 watt domestic amplifiers.

Dept. 354; 120, Green Lanes,
Palmer's Green, London, N.13

Tel: BOWes Park 6064

RADIO/RADIOGRAM CHASSIS. The "DULCI" 5-valve S.M.L. chassis, incorporating the most outstanding features of modern design, flywheel tuning, negative feedback over entire audio range, latest type miniature valves, etc., etc., combining to give outstanding clarity of speech, with the most faithful reproduction of music, on gram, or radio, for operation on A.C. mains, 110 to 200/250 volts, at a price offering the finest value for money, £12/12/6; or the Push-Pull 6-valve version, at £15/15/6, complete less speaker, tax paid. Offered under full guarantee, and money back conditions if not fully satisfied. Descriptive literature on request.

T.R.F. RECEIVER. Complete in stylish Bakelite cabinet, ivory finish, 11½in. x 6in. x 7½in., employing four of the latest type valves, incorporated in a highly efficient circuit giving sparkling reproduction, together with high overall sensitivity and selectivity. A.C./D.C. 200/240v. Guaranteed to please, and highly recommended for value at £6/10/6, plus 7/6 carriage and insurance.

SUPERHET TUNER UNIT. A three waveband S.M.L. superhet feeder unit, fitted handsome edgelit multicoloured dial, complete with escutcheon, flywheel tuning, three controls, complete with three valves, and plug and leads for connection to your amplifier. A feeder unit for the discriminate user, at £10/10/6, plus 7/6 carriage and insurance.

A.C. AMPLIFIER. A 3-valve amplifier for A.C. mains, 200/250 volts, employing negative feedback tone control, giving an output of 4 watts for the reproduction of gramophone records with a tonal sparkle, complete less speaker, £4/10/6, plus 7/6 carriage and insurance.

CHASSIS ASSEMBLY. Undrilled aluminium chassis, size 11½in. x 7in. x 2½in., fitted latest type horizontal drive, with multicoloured S.M.L. dial. Flywheel Tuning, complete with escutcheon, at 32/6, plus 2/6 P.P.

O. GREENLICK LTD.

14, Hillside Rd., Tottenham, London, N.15
Tel.: STA. 2991.

WIRE

on $\frac{1}{4}$, $\frac{1}{2}$ & 1 lb. reels
In stock for IMMEDIATE DELIVERY

per $\frac{1}{4}$ lb. reel

ENAMELLED COPPER WIRE

SWG.	price	SWG.	price	SWG.	price
16-18	1/6	26	2/2	34	2/10
20	1/8	28	2/4	36	3/1
22	1/10	30	2/6	38	3/3
24	2/-	32	2/8	40	3/6

Up to 50 swg. available.

DOUBLE COTTON COPPER WIRE

SWG.	price	SWG.	price	SWG.	price
16	1/9	24	2/8	32	3/8
18	2/2	26	2/11	34	4/2
20	2/4	28	3/2	36	4/8
22	2/6	30	3/6	38	6/2

DOUBLE SILK COPPER WIRE

SWG.	price	SWG.	price	SWG.	price
16	1/9	26	3/6	34	5/4
18	2/2	28	3/10	36	6/-
20	2/8	30	4/2	38	6/8
22	3/-	32	4/8	40	7/8
24	3/2				

TINNED COPPER WIRE

SWG.	price	SWG.	price	SWG.	price
14	1/4	20	1/10	24	2/2
16	1/6	22	2/-	26	2/4
18	1/8				

ENAMELLED SINGLE SILK

SWG.	price	SWG.	price	SWG.	price
20-22	2/6	32-34	3/9	38	6/-
24-26	2/9	36	5/-	40	7/6
28-30	3/3				

Intermediate gauges available.

per 1oz. reel

EUREKA ETC.

SWG.	price	SWG.	price	SWG.	price
16-22	1/2	30	1/8	36	2/2
24	1/4	32	1/9	38	2/7
26-28	1/7	34	2/-	40	3/3

NICKEL CHROME

SWG.	price	SWG.	price	SWG.	price
16-22	3/7	30	5/2	36	6/5
24	4/-	32	5/4	38	7/9
26-28	4/9	34	6/-	40	9/7

Orders up to 1lb. Postage 1/0d.
Orders 1lb. to 2lb. Postage 1/4d.
Orders £1 up—Post Free.

HYGRADE

WIRE CO.

Telephone: GERrard 0293
16 Gerrard Street, London, W.1

WANTED. EXCHANGE, ETC.

WILL buy ART/13-T47A or T47 type transmitter; R5/ARN7 radio compass receiver; BC348 receiver; ARC3 radio complete; R77 receiver; FC312 and BC342 receivers; APN9 Loran transceiver; R89B Glidepath; 788C altimeter receiver; IE52C scope; RA20 power units; T17 microphones; TS67 test sets.—Write H. J. Burke Co., 49, Washington Avenue, Little Ferry, N.J. [2310]

VALVES

21 Phillips DCG4/1000(866), 2 RCA866/A, 2 RCA872/A, 7 RCA807, 9 RCA and GE813, 7 RCA845 for sale.—Offers to Thrift & Co., Penn Fields Terminus, Wolverhampton. [2540]

VALVES WANTED

45/- each offered for 813 valves, 60/723A/Bs; any quantity for export.—Write Pype Hayes Radio, 606, Kingsbury Rd., Birmingham, 24, Erdington 4942. [2456]

VALVES urgently wanted for export, types 813, 723A/B, 250TH, 833, any quantity; highest prices paid.—Write Pype-Hayes Radio, 606, Kingsbury Rd., Birmingham, 24 (Erdington 4942.) [2016]

BATTERIES

JUST released by the Ministry.—All-dry H.T./L.T. batteries, 72 volt H.T.+1.5v L.T. Javel type size, 6inx5inx2in; also 60v H.T.+1.5 L.T., ideal for deaf aids, personnel sets, models, etc., size 4inx3inx1in, all tested and guaranteed full voltages before despatch; our special price 4/6 each, post and packing 1/6.—Walters Wireless Stores, 48, Stafford St., Wolverhampton. [1061]

CABINETS

LEWIS RADIO have the best selection and finest finish.—See page 132. [0224]

WALNUT radiogram cabinets; details.—Cabinetware, Ia, Heyes St., Blackburn.

TELEVISION, radio, radiogram and tape-recording cabinets.—157, Bromsgrove St, B'ham, Mid 1054. [2133]

WALNUT radiogram and television cabinets, soundly constructed; stamp for details.—R. Shaw, 69, Fairlop Rd., Leytonstone, E.11. [2462]

CABINETS made to order; send details for quotations; bass reflex cabinets, finished in period or contemporary styles; see display advertisement; open till 5.30 Saturdays.—A. Davies & Co. (Cabinet Makers), Hampstead, Gulliver 5775. [2460]

REPAIRS AND SERVICE

ARMATURE re-winding service to the trade.

VACUUMS, drills, grinders, hood dryers, dental motors, vacuum cleaner armatures replaced from stock; 24-hour service; every job guaranteed; all vacuum cleaner parts, hoses, etc., in stock for any make.

REGAM ELECTRIC, 95, Park Lane, Leeds, 1. [0028]

ELECTRIC blankets and clocks repaired. Efficient service.

ELECTRONIC, 157, Tullibardine Rd., Sheffield. [1994]

MAINS transformers rewound, new transformers to any specification.

MOTOR rewinds and complete overhauls; first-class workmanship; fully guaranteed.

F.M. ELECTRIC Co., Ltd., Potters Bldgs., Warser Gate, Nottingham. Est. 1917. Tel. 47898. [0113]

TRANSFORMER rewind service, mains E.H.T. transformers and chokes, prompt delivery, range of replacement types ex stock or manufactured to your specification.

METROPOLITAN RADIO SERVICE Co., 75, Kilburn Lane, London, W.10. Ladbroke [0230]

MAINS transformers, E.H.T. line outputs, chokes and field coils, etc., promptly and efficiently rewound or manufactured to any specification; 12 months' guarantee.

LADBROKE REWIND SERVICE, Ltd., 820a, Harrow Rd., Kensal Rise, N.W.10. Lad. 0914. [0222]

COILS, stators transformers, any quantity from singles upwards; also F.H.P. motor re-winds.—Coilwinding Services, 26, Lower Richmond Rd., S.W.15. Putney 2667/8930. [2465]

REPAIRS.—Mains, EHT or OP transformers; field coils and chokes; also armatures and motors. New transformers designed to specification. All items fully vacuum impregnated.

TRANSFORMER SERVICE Co., 2a, Frithville Gardens, Shepherd's Bush, W.12. Tel. Shepherd's Bush 5819. [0075]

ELECTRICAL test instruments repaired and standardized, all types British or American, ammeters, voltmeters, ohmmeters DC/AC multi-range meters, etc.; meters converted to specification.

THE ELECTRICAL INSTRUMENT REPAIR SERVICE, 329, Kilburn Lane, London, W.9. Tel. Lad. 4168. [2011]

AUDIO equipment repaired, rebuilt, modified, disk or tape recorders, amplifiers, tone control units, sound projectors; quotations without obligation.—Bernard J. Brown, 33, Goldhawk Rd., London, W.12. [0025]

ALWAYS at your service, high quality transformers made to suit your requirements or rewound to the original specifications. Woodrow Transformers, Ltd., now removed to larger premises, thus enabling the employment of more labour and quicker turn round of orders.—New Address, 7, Dudden Hill Lane, Willesden, N.W.10. All work fully guaranteed. [2243]

Here's how to SAVE MONEY ON INSTRUMENTS!

- ✓ . . how to do faster, better testing with fewer instruments
- ✓ . . how to increase the usefulness of your present instruments
- ✓ . . how to choose the right instrument for each job



✓ . . how to understand instrument operating principles

✓ . . how to evaluate instrument readings and put them to practical use

BASIC ELECTRONIC TEST INSTRUMENTS

By RUFUS P. TURNER
254 pages, 171 illustrations

The instrument book written especially for SERVICEMEN • AMATEURS • EXPERIMENTERS

★ Here, at last, is a book that can save you money on instruments and help you use your present instruments lots more efficiently!

Over 60 instruments—from the most modern TV pattern generators to special-purpose bridges—are carefully described. Their uses are fully explained. Valuable work-saving short cuts are outlined.

Included are complete details on simple meters for current and voltage; ohmmeters and V-O-M's; V-T voltmeters; power meters; impedance meters; capacitor checkers; inductance checkers; special-purpose bridges; oscilloscopes (this material alone is worth the entire price of the book to busy servicemen!); r-f test oscillators and signal generators; audio test oscillators; radio frequency and audio frequency measuring devices; audio-amplifier testing devices; r-f signal tracers and tube testers.

Among other things, BASIC ELECTRONIC TEST INSTRUMENTS is a complete training course in the latest instruments including grid-dip oscillators, TV sweep and marker generators; TV linearity pattern generators, square-wave generators and others.

Price 32/-
plus 1/- postage

THE MODERN BOOK CO.
PRAED STREET,
LONDON, W.2

Tel.: PADdington 4185

PITMAN

Introduction to Ultra-High-Frequency Radio Engineering

By S. A. Knight, F.R.S.A. This new book is intended as a guide to the methods and techniques of modern ultra-high-frequency radio and radar engineering. The author, who has had many years' experience in the practical side of radio engineering, covers such typical aspects as transmission lines and wave-guides, resonant cavities, cathode-ray tubes, disc-sealed valves, Klystrons and magnetrons, measurements, aerial systems and wave propagation. Illustrated. 21/- net.

The Principles of Television Reception

By A. W. Keen, M.I.R.E., M.Brit.I.R.E., A.M.I.E.E. This book provides technicians and service engineers with a qualitative introduction to the theory underlying the design of television receivers and will be useful to students taking any examination (e.g., C. & G., Brit.I.R.E.) of which the syllabus includes television principles. Illustrated. 30/- net.

SIR ISAAC PITMAN & SONS LTD.
PARKER ST., KINGSWAY,
LONDON, W.C.2

BASS REFLEX CABINETS

Walnut, Mahogany or Oak veneered. 30-in. high. For 8 in. Speakers, 10-in. Speakers, 12-in. Speakers.
£9-0-0d. £9-10-0d. £10-0-0d. carriage paid.
Complete Kits in un-veneered acoustic chipboard.
£3-15-0d. £4-7-6d. £4-17-6d. carriage 7/6d.
We will assemble and fix felt for 7/6d. extra.
A. DAVIES and Co. (Cabinet Makers),
3 Parkhill Place, off Parkhill Road, London, N.W.3
(Gulliver 5775)

Introducing the— TYANA TRIPLE THREE



Reg. Design, No. 867884

MAKE SOLDERING A PLEASURE
SMALL SOLDERING IRON

Complete with detachable BENCH STAND 19/6

The smallest high-power soldering iron. Length only 8 1/2 in.; adjustable long bit dia. 3/16; mains voltages 100/110, 200/220, 230/250.

The "STANDARD" Popular Soldering Iron



now reduced to 14/11

Replacement Elements and Bits for both types always available.

KENROY LIMITED

152/297 UPPER ST., ISLINGTON, LONDON, N.1.

Telephone: Canonbury 4905-4663

REPAIRS AND SERVICE

24-HOUR service, 6 months' guarantee, any transformer; rewind, mains outputs and i.f.s., etc.; all types of new trans., etc., supplied on specification, business heading or service card for trade prices.—Majestic Winding Co., 180, Windham Rd. Bournemouth, 16520

AS professional sound recordists and members of the Association of Professional Recording Studios, we are particularly well qualified to give advice and service on all aspects of sound recording and reproduction. Design of tape equipment a speciality. Circuits designed, repairs and modifications carried out quickly. Advice freely given. See also below:—**COMPREHENSIVE** service to trade and amateur; design, manufacture and repair of electronic equipment; carried out by specialists; equal attention given to small or large orders. See also below:—Autochangers, 48-hour service, cleaning and adjusting at fixed price of 45/- plus carriage; also all repairs carried out; trade enquiries invited; callers by appointment only please.—Ariel Sound, 57, Lancaster Mews, London, W.2. Tel. Paddington 5092 (2 lines). [0026]

ARMATURE rewinding service to the trade, dental motors, drills, grinders, hood dryers, dental motors, vacuum cleaners, armatures replaced from stock, 24 hours service; every job guaranteed; we also specialise in complete overhauls and rebuilds of vacuum cleaners; all vacuum cleaner parts, hoses, bearings, fans, brushes for any make in stock.—Regam Electric, 95, Park Lane, Leeds. [2253]

PAINTS, CELLULOSE, ETC. PAINT spraying handbook, 3/6 post free, cellulose and synthetic paints and all spraying requisites supplied; catalogues free.—Leonard Brooks, 53, Harold Wood, Romford. [0207]

BUSINESS AND PROPERTY RADIO, electrical, cycle, modern shop, flat, long lease, situated in quiet Surrey town, no opposition, certified accounts, prospects; £3,500, s.a.v.—Write Box 2817. [2564]

BUSINESS AND PROPERTY WANTED RETAIL radio/television business; any main shopping position within 40 miles London; must have main agencies.—Box 3201. [2473]

BUSINESS OPPORTUNITIES OLD-ESTABLISHED firm of exporters in the electronic field, invite manufacturers seeking overseas sales, to communicate Box 0239.

WORK WANTED ASSEMBLY, wiring of all types of electronic eqpt., control panels, switchboards, etc.—R.A.E., 377, High Rd., London, N.2. [0219]

CAPACITY AVAILABLE CAPACITY available for manufacture assembly and wiring all types electronic equipment sub-contracts, prototypes, etc.—Box 2938. [2411]

CAPACITY available; manufacturer of transformers up to 3000 v. to R.C.S. chokes, solenoids, etc.; have capacity available and invite enquiries from manufacturers; small runs of electronic assembly also undertaken; 1/6th h.p. induction motor in production, good delivery.—A.V. & B. Gals, Ltd., 11, Gosbrook Rd., Caversham, Reading, Tel. 71763. [2076]

MISCELLANEOUS ARE you saving money on your purchases by using our discount facilities?—Write for details: Arcade Recording Circuit, Arcadian Gdns., London, N.22. [2424]

EX-GOVERNMENT steel instrument cases, copper plated and finished grey, size 2 1/2 in. long, 1 1/2 in. high and 7/8 in. deep, 10/- plus 2/6 carriage.—Weatherhead's, Bletchley, Bucks. [2088]

A HIGH vacuum impregnation unit or single or batch of impregnation units to B.I.C. specification 214 or individual requirements.—Blekvac, 505, Lordship Lane, S.E.22. Tel. Forest Hill 7089. [0310]

PLYWOOD—Hardboards. Send s.a.e. for free price lists and samples, including 3/16 in mahogany ply 10d sq ft, sheets 72 in x 36 in; hardboard all sizes, from 6d sq ft, free delivery (100 miles).—N. Gerver, 2-10, Mare St., London, E.8. Amherst 5806. [0027]

ENGRAVING amateurs and trade could take the opportunity of engraving problems in the future by getting in touch with A.G. Engraving, 19a, Windmill Rd., London, S.W.18. Bat. 5793. Brass, bronze, erinoid, Perspex dial; one knob or repetition equally entertained. [0034]

COPPER wires enamelled, tinned, Litz, cotton, silk covered, all gauges; B.A. screws, nuts washers, soldering tags, eyelets, ebonite and laminated bakelite panels, tubes, coil formers; Tufnol rod; headphone boxes, etc.; latest radio publications, full range available; list s.a.e.; trade supplied.—Post Radio Supplies, 33, Bourne Gardens, London, E.4. [10138]

SOUND NEWS PRODUCTIONS, recorders of Commonwealth Youth Service at Westminster Abbey, Midnight Mass from Brompton Oratory, etc.; portable mobile "off the air" and disc from your tape" work at s.a.e.; un-rivalled charges; double-s. 10in records 15/6, 12in ones 18/6, including needles.—3, Clover Mews, London, S.W.3. Flaxman 3706. [2468]

YOUR tapes to disk (78 & L.P. Microgroove, genuine) tape disks, accessories; trade terms on above; E.M.I. & Ferragraph Recorders; 2 BSR disk recorders, condition excellent; reasonable; studio and mobile service, professional standards, "Erolca" Recording Services (Regd. 1949), Peel St., Eccles, Manchester, Eccles 1624, Musical Director Thurlow Smith, A.R.M.C.M. [0121]

BENSON'S BETTER BARGAINS

METERS. New and boxed.

Scale FSD	Size	Type	Fitting	Price
130 v. (1 mA)	2 1/2 in.	MC/Rec	Flush R.	15/6
5 mA	2 in.	MC	Square	7/-
30 mA	2 in.	MC	Proj. E.	7/-
100 mA	2 1/2 in.	MC	Flush R.	8/-
300 mA (100 mA)	2 in.	MC	Square	7/-
500 mA	2 1/2 in.	MC	Flush R.	8/-
1 A	2 1/2 in.	MC	Proj. E.	7/6
3 A	2 in.	TC	Square	6/6
20 A	2 1/2 in.	MI	Flush R.	8/6
30 A	2 1/2 in.	MC	Proj.	8/6
50 A	2 1/2 in.	MI	Proj. Met.	30/6
Freq. 45-55 c/s	7 in.	230 v.	Proj. Met.	75/6
5 mA (500 μA)	2 1/2 in.	MC/TC	Flush R.	17/6
15 v.	2 1/2 in.	MI	Flush R.	10/6
3,500 v. (6 mA)	3 1/2 in.	MC	Proj.	10/6

INDICATORS T233. New, orig. cartons, with VCR57, 3/VR91, 3/VR65, 3/VR54, 2/VR92, 5/6 (carr. 7/6). R1155, B.F.O. box, 4/-; I.F. Filter, 5/6. G.P.O. type magnetto (50 v.), bell and Morse key, in metal case, 12/6 (carr. 2/1). T.V. Pre-amps., with 1/VR136, 7/-; with 2/VR91, 17/6; with 1/VR91, 1/5Z4 and 50c. power pack, 45/- (carr. 5/-). **CONDENSERS,** block, 8 mfd., 440 v., A.C.w., 5/6, 4 mfd., 1kV, v., 3/-; 2.5 mfd., 500 v., A.C.w., 3/6. Trans. Input 110/240 v. Outputs 350-0-350 120 mA., 6.3v. 4 A., 4 v. 2 A., new, 18/6. Special Valve Bargains. VR91, 6C4, 6A05, 6001, 955, ARP12, VR505, NT20, NT37, VR116 at 4/-; VR65, VR60, 7193, VU111, CV54, VU120 at 3/-; VR57, CV181, VT131, VT133, VT501 at 6/6. Metal Rectifiers. HW 270 v. 80 mA., 6/-; 450 v. 80 mA., 600 v. 30 mA., 6/6; FW GT 12 v. 1/2 A., 1/6. **POTENTIOMETERS** 3in. dia., 20k, 10 w., 3/-. **CONDENSERS** 15 kV ceramic, 1 each 500 pF and 750 pF, in sealed case, 5/-. **R.F. UNITS** type 24, 16/-; 25, 20/-; 27, 40/-. **COILS** Eddystone "T" types "P" and "Q" 5-pin horn base each 3/6; **DYNAMOTORS** solenoid cases, D.C. (approx. 250 v. 80 mA. at 6 v.), 8/6. 24 v. to 1230 v. 200 mA. D.C. 17/6; 24 v. to 250 v. 100 mA. (twice), 17/6. **RELAY** 12 v. actuating toothed bakelite wheel, 2/6. **TEST SETS:** Admity.—S.E.2. 160/230 mV, 230 v. 50 c input and m-c, Valves: 2/6A5, 2/EA50, 1/EC52, 1/6X5, 1/6V172, 500 micro Ammeter. New, in metal-lined case, 50/- (carr. 8/6).

List and enquiries, S.A.E. please!
Terms: Cash with order. Postage extra.
Immediate delivery.


Callers and Post
W.A. BENSON (WW),
308 Bathbone Rd.,
Liverpool 13, ST0 1804

Callers only
SUPERADIO (W'ohapel)
LTD., 116 Whitechapel,
Liverpool, 1 ROY 1130

THE POLLOCK M.C. PICKUP

Response 10 c.s. to 20 Kc/s. H.F. resonance 25 Kc/s., L.P. 20 Kc/s. Kit of parts to make pickup complete, including 100:1 transformer and sapphire stylus, 001 or .0025 in., and full building instructions £4. 8s. 6d. Parts sold separately, prices: head and stylus 38/6d.; head for min. thorns 31/-; arm/pivot 26/-; transformer 26/-; all prices post free. S.a.e. for details to:—
A.M. Pollock, 14 Broomfield Lane, Hale, Cheshire

This UNIQUE BENDER

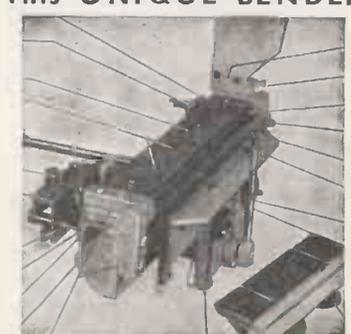

Quickly and Accurately Forms

Angles, Channels, Sections, Boxes, Lids, Trays, Tanks, Chassis Brackets, Clamps, Clips, Shrouds, Chemical, Electronic and Electro Medical apparatus. Used by leading Radio Manufacturers, Invaluable to Specialising Engineers, Hospitals, Universities and Research Workers.

For 6 page Folder write to:—
A. A. TOOLS (W)
197a Whiteacre Rd., Ashton-u-Lyne





NUSOUND SOVEREIGN. The latest super quality Amplifier. All Triode line up. P-Pull PX4 output. Frequency response 20-25 kcs. \pm .6 d.b. and continuing up to 50 kcs. \pm .9 d.b. Sensitivity 120 mv. for max. 10 w. output. Total harmonic distortion .1 per cent. at 1,000 c.p.s. at 6 watts. 20 d.b. neg. feedback. Independent Treble and Bass controls. Chassis size: 14 x 1 x 7 1/2 in. high. A.C. model only, £26.

Any good amplifier can produce the most disappointing results if the input circuit is not correctly matched to the radio or gramophone unit feeding it. Most amplifiers are made without any knowledge of the other equipment to be used with them and the input circuit, therefore, is a compromise which may or may not result in a satisfactory performance. The Nusound 8 1/2 watt is not a mass produced product of this kind. The basic circuitry is identical in all models but the input circuit is designed to individual requirements. The customer tells us which pick up or feeder units are to be used (our own or any other good make) and the amplifier is supplied to ensure the very best results possible from the combination.



Nusound 8 1/2 watt Quality Amplifier = PP 6V6— independent Bass and Treble boost and cut—neg. Feedback—provision for Radio Feeder Unit—Freq. response 25 to 20,000 c.p.s. + 1dB—hum 80 DB down at 6.5 watts—Feedback 14 DB. Available with Remote Control Unit. Price £17/10/-, or as illustrated.

- GARRARD AUTOCHANGERS & PLAYERS**
 R.C.80, less Head..... £15 3 3
 R.C.75A, less Head..... £13 10 0
 T/AC, less Head..... £17 10 9

- HIGH-FIDELITY FEEDERS**
VARIABLE SELECTIVITY, 3-BAND, £16/10/-
SUPERHET, L.M.S., £12/14/-
S/H PRE-SET, 3-STATION, £8/4/-
T.R.F. PRE-SET, 3-STATION, £7/0/9
N.S.P. PRECISION SCRATCH FILTER, 59/6

NUSOUND PRODUCTS LTD.
 (Dept. W3) 136 WARDOUR STREET
 LONDON, W.1. Tel.: GERrard 8845
 Hours of business: 9 a.m.—5.30 p.m.
 Saturdays 9 a.m.—1 p.m.
 Stamp for leaflets on our other products.

COVENTRY RADIO
 189 DUNSTABLE RD., LUTON
 Tele.: Luton 2677.
Component Specialists Since 1925
 All B.V.A. and Tungram Valves
EDDYSTONE COMMUNICATION SETS AND COMPONENTS
 Short Wave Component Catalogue 6d.
 T.C.O., Hunts & Dubilier Condensers, Welwyn and Erie Resistors.
 Lab/Morgaulte, Erie, Dubilier, Colvern and Amplion Potentiometers.
 Denco, Osamor, Wearite and Weymouth Coils and Packs.
 Eddystone, Denco, Wearite and Weymouth I.F.'s. Woden and Elstone Transformers.
 Elsc, Goodman, Plessey, Roia/Delection Speakers. Avo and Taylor Test Meters.
 E.M.I. Scotch Boy and Grundig Recording Tapes. Valradio Vibrator Converters.

These are some of the components we stock. Send for our 60-page Component Catalogue, price 6d.

MISCELLANEOUS

METALWORK, all types cabinets, chassis, racks, etc., to your own specifications; capacity available for small milling and capstan work up to 1 1/2 in. bar.
PHILPOTT'S METAL WORKS, Ltd. (G4B1), Chapman St., Loughborough. [0208]

NOTICES

THE Institution of Electrical Engineers.

SCHOLARSHIPS.
 The Council of The Institution of Electrical Engineers will consider for award this year three Research Scholarships, one Graduate Scholarship and six Student Scholarships as follows:—
RESEARCH Scholarships—Oliver Lodge, value £420 for one year, may be extended for a second year.
I.M.E.A. value £420 for one year, may be extended for a second year; Swan Memorial, value £250 for one year.
GRADUATE Scholarship—for full-time, post-graduate study. Silvanus Thompson, value £200 p.a. for three years.
STUDENT Scholarships—for study at undergraduate level at a University or a Technical College. Silvanus Thompson, value £200 p.a. for three years; Manville, value £150 p.a. for three years; W. B. Esson, value £120 p.a. for two years; Salmons, value £60 for one year; Paul, value £50 p.a. for two years; Thorrowgood value £25 for one year.
 The closing date for the receipt of applications is May 1, 1954, for Student Scholarships and Scholarships—Full particulars of the conditions of award attached to each scholarship and nomination forms may be obtained on application to the Secretary, The Institution of Electrical Engineers, Savoy Place, London, W.C.2. [2457]

PATENTS

THE Office National d'Etudes et de Recherches Aeronautiques, 55, Bd. Malesherbes, Paris (8ème), holder of British Patent 658,341, published on Oct. 10, 1951, "Ultra High Frequency Magnetometer," should like to deal with constructors in Great Britain through licensing. [2429]

PUBLIC ANNOUNCEMENTS

THE UNIVERSITY OF SOUTHAMPTON.

DEPARTMENT of Electronics.
 The Department of Electronics gives an advanced course at honours degree standard in electronics; the course is full-time for one academic year and the university grants a diploma by examination to students who successfully complete the course; entry qualification is a university degree in physics or electrical engineering, or its equivalent; the next course will commence in October, 1954, and application for admission should be made now to the Academic Registrar, from whom further details may be obtained. [2416]

SITUATIONS VACANT

The engagement of persons answering these advertisements is through the local office of the Ministry of Labour and National Service, etc., if the applicant is a man aged 18-64 or a woman aged 18-59 inclusive, unless he or she or the employer is exempted from the provisions of The Notification of Vacancies Order 1952.

RADAR Engineering.

TWO important vacancies exist on the permanent staff of an influential Company concerned with high priority production and systems in Huntingdonshire of radar systems, much of which involves American equipment.

BOTH positions are progressive, pensionable and well salaried.
 THE first is for a Production Controller (Ref. P.E.1) and should attract a candidate with extensive experience of a similar nature and be thoroughly conversant with radar and/or radio engineering production of a high order. He will be a competent executive who knows assembly line production, can handle production layouts. In fact, all aspects of this highly important function.

THE second vacancy concerns a Production Engineer (Ref. P.E.2), who has already established his abilities in an efficient, well-organized production unit, and who has an intimate knowledge of detailed engineering production in the radio/radar field.
 APPLY, quoting above references, in strict confidence, to Box 3166. [2458]

ELECTRICAL engineers.

WAYMOUTH GAUGES & INSTRUMENTS, Ltd., a subsidiary company of Smiths Aircraft Instruments, Ltd. have vacancies in their Aircraft Fuel Gauge Laboratory for Assistant Engineer, required for development of electronic fuel gauging equipment, they should have an engineering degree or Higher National Certificate. Technical Assistants are also required for experimental work in electrical measurements; preference will be given to applicants holding a technical qualification.— Apply in writing to the Chief Development Engineer, Waymouth Gauges & Instruments, Ltd., Station Road, Godalming, Surrey. [2295]


TELEVISION.—Careers for young men.

LIMITED vacancies exist upon work which is an introduction to checking and adjusting of electronic circuits on TV receivers; specialized knowledge not necessary, as suitable applicants will receive training.—Apply in writing to Personnel Manager, Fye, Ltd., St. Andrews Rd., Cambridge. [2273]

MONEY BACK GUARANTEE DUKE & CO
 621 ROMFORD ROAD, LONDON, E.12
 CWO or COD • TEL: GRA 6677

- AMPLIFIERS. 57/6 approx:** 4 watts output. 3 valve A.C. or A.C./D.C., post 2/6.
AMPLIFIERS. 77/6 approx: 7 watts output. 4 valve. Push pull. A.C. or Universal. Post 2/6.
 9/6 Amplifiers. Bargain. Brand new (ex-W.D., unused). Contain EF36, two transformers, 400 ohm relay, volume control, various condensers, resistors etc. Case measures 5 1/2 x 6 1/2 in., or less value, 4/9. Post 1/6. Drawings available free with order.
MIC. & PHONE TRANSFORMERS. Ex-W.D. hand microphone and matching transformer (ratio 400-3) with standard jack plug wired on. BARGAIN 5/6, post 9d.
CAR RADIO TRANSFORMER, 5/9, 6 or 12 v., post 2/-.
PICK-UP TRANSFORMERS. New. Ex-W.D. Unused E.M.I. type. Fully shielded, 3/9, post 1/-.
RECTIFIERS. 8/9. T.V. type. Salvage, guaranteed. 300 volt at 250 mA. Also 250 volt at 80 mA, 5/9, 180 volt at 40 mA, 3/9, post 1/-.

RADIO-GRAM CHASSIS FROM £10. 17s. 6d.

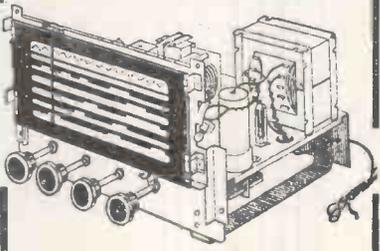

Latest show, hand spread tuning, feed-back, all brand new. 6-waveband (illustrated) 15 guineas, with 6-position tone control. 3-waveband (B3) at 12 guineas. £10/17/6 (X9), similar to above but by another Manufacturer. All models have 5 valves (latest miniatures), flywheel tuning, negative feedback, gain switch, extension speaker and pick-up sockets. Post 3/6.

INDICATOR UNITS. Ex-W.D., but brand new condition. Valves and C.R. tubes only have been removed. Chassis, valve-holders, resistors, condensers, etc., alone are worth more than our price. Units include Design "L" type 6C. BARGAIN at 12/6 each. Carriage 4/6.

POWER SUPPLY UNIT, 17/6. Containing Heavy Duty 330 v. Trans., 6 v. Trans with 12 Tapping, 3 E.H.T. output voltages 3 chokes, various conds. and resistors. Less valvula. Carr. 4/6.

ROTARY CONVERTER, 12/6. Ex-W.D., new. In 24 v., out 200 v., at 50 mA. Post 2/6.

POWER SUPPLY UNIT, 47/6. Ex No. 10 Set, Z.A. No. 5108. New. 12 v., and 24 v., in. Two H.T. output at 275 v., and 500 v. Post 2/6.

EXTENSION SPEAKERS, 37/6. In polished cabinet with 8in. speaker. Post 2/6.

EXTENSION SPEAKERS. Brand new 6 1/2 in. P.M. speaker (low impedance). Mounted on polished and veneered baffle stand or normal box type cabinets, gold fret. 5ft. lead ready connected. ONLY 18/9. Post 1/9.

MICRO-SWITCHES. New American miniatures, 250 volts, 3 a., 1/2 in. x 1/2 in. x 1 1/4 in. BARGAIN OFFER 3/6 each, post 4d.

TELESCOPIC MASTS. Ex-W.D., but unused. Extend to 7ft. 6in. Base diameter 1/2 in., tip 1/4 in. Closed length 16in. Ideal aerial. GIFT PRICE 5/9. Post 1/3.

AERIAL COILS. For portable sets. Brand new. On aluminium frame measuring 4in. x 6in. BARGAIN AT 2/6. Post 6d.

CONDENSERS. Guaranteed. Assorted parcel of fixed and waxed (wire ends). .0003, .001, .0047, .0068, .004 and 1,000 pf. 45 for 10/-, or 100 for £1. Post 1/-.

SPOTLIGHTS. Butlers, ex-W.D., 8/9. New, with reflector and glass. Post 1/3.

SIDE LAMPS. Intra-red glass, ideal tail lamps. New, ex-W.D., 1/9. Post 9d.

CRYSTALS. Germanium. Brand new, made by B.T.H. Give first-class results. SPECIAL OFFER 1/9, post 6d.

FUSE HOLDERS. Porcelain. 15 amp. MEM, Kantark Minor (brand new). Complete with fuse, backing wire type, 250 volts. TO CLEAR AT 9d. Post 4d.

SEND STAMP FOR 1954 CATALOGUE

SOUTHERN RADIO'S WIRELESS BARGAINS

TELESONIC 4-Valve Battery Portable. Complete with HiVac Valves. In Metal Carrying Case. Simply converted to Personal Portable. £2 including conversion sheet.

TRANSMITTER RECEIVERS. Type "38" Mark II. BRAND NEW. Complete with 5 Valves. Headphones. Aerial and Throat Microphones. £4/15/- per set. Less Batteries.

TYPE "18" MARK III. Complete with all Valves but less Batteries and attachments. READY FOR USE. £7/17/6. Carriage Paid.

ONE HUNDRED ONLY—Type "38" Mark II **TRANSRECEIVERS.** Used but complete with all Valves and contained in usual carrying case. Ready for use. LESS ATTACHMENTS. 30/- per set.

CRYSTAL MONITORS TYPE 2. NEW in TRANSIT CASE. Less Crystals. 8/-.

BOMBSIGHT COMPUTERS. Ex-R.A.F. NEW. Contains GYRO, MOTORS, REV. COUNTERS, GEAR WHEELS ETC., ETC. Ideal for MODEL MAKERS, EXPERIMENTERS ETC. £3/5/- each.

LUBBRA HOLE CUTTERS. Adjustable 2 to 3 1/2 in. Improved High Speed Type. For Metal, Plastic, Wood etc., etc. 6/6.

RESISTANCES. 100 Assorted Useful Values. Wire-ended, 12/6 per 100.

CONDENSERS. 100 Assorted Values Mica and Tubular etc. 15/- per 100.

PLASTIC CASES. 1 1/2 in. by 10 1/2 in. Transparent. Ideal for Maps, Photos, Display etc. 5/6.

STAR IDENTIFIERS. Type I A-N. Covers both Hemispheres. In case. 5/6.

WESTECTORS. WX6 and W112. 1/- each.

CONTACTOR TIME SWITCHES. Complete in sound-proof case. 2 impulses per sec. Thermostatic control. 11/6.

REMOTE CONTACTORS for use with above. 7/6.

MORSE TAPPERS. Ex-Government, 3/6. Heavy Duty types, 8/6. Complete Morse Practice Sets with Buzzers, 6/9.

ALL LINES PREVIOUSLY ADVERTISED STILL AVAILABLE.

Full List of RADIO BOOKS, 2 1/2 d.

SOUTHERN RADIO SUPPLY LTD.
11 LITTLE NEWPORT STREET, LONDON, W.C.2
Gerrard 6653

GOODSELL LTD.


for High Fidelity Equipment

40 GARDNER ST.,
BRIGHTON, 1

Tel.: Brighton 26735.

THE HAYES COMPANY

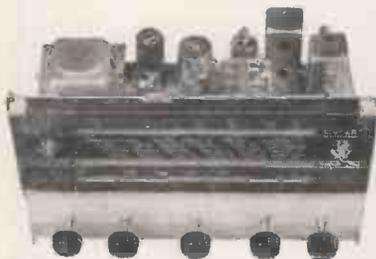INTRODUCING THE RG/115. A 5-valve all-wave chassis, 3.5 watts output. £14/5/-.



RG/250. 10 valve chassis with contrast expansion, variable selectivity. £35.

RG/160. 7 valve chassis, bass and treble controls, push-pull output. £20.

RG/127. 6 valve all-wave chassis with push-pull output. £17/5/-.

TU/100/6. All-wave tuning unit for use with amplifiers. 6.3 heaters. £14/15/-.

TU/100/4. For 4 v. heater supply. £15/5/-.

Full details gladly sent on request.

16 Mare Street, London, E.8. Amh 4400

SITUATIONS VACANT

EXPERIENCED engineers

ARE sought by an established and well-known organisation, to assist in the development of wide band microwave telecommunication systems.

CONSIDERABLE effort will be put into this project and the appointments offer exceptional opportunities for advancement.

AS the successful candidates will be expected to make an immediate contribution it is essential that applicants should have had several years research or development engineering experience in one or more aspects of the above field.

PLEASE apply to Box 2840, quoting ref. HBB. [2371]

RADIO technicians required as

SIGNALS Assistant Inspectors of Police by the GOVERNMENT of Kenya for one tour of two years, extending to three years by mutual consent and with possibility of permanency; commencing salary etc., according to previous experience, in scale £796 rising to £1,134 a year; gratuity (at least £162 after two years' service) payable on satisfactory final completion of service; outfit allowance £30, uniform allowance £10 a year, free passages; liberal leave on full salary; candidates aged 20-35 should be at least 5ft 7in without footwear, have normal vision without glasses and be of good education; they should possess a sound knowledge of the installation and maintenance of modern low and medium powered V.H.F., static and mobile equipment, H.F. transmitters and receivers, petrol generators and diesel electric sets.

APPLY in writing to the Crown Agents, 4, Millbank, London, S.W.1, stating age, name in block letters, whether married or single, full qualifications and experience, and quote M1/35931/WF.

TECHNICAL Specification Writers.

VACANCIES exist in our Design Organization for writers capable of extracting data from engineers' drawings and expressing it in clear and concise English; a methodical approach and thorough knowledge of electrical and/or hydraulic mechanisms are the minimum qualifications for this interesting and progressive post.

WRITE in detail, quoting position sought, to—The Personnel Department (Technical Employment), de Havilland Propellers, Ltd., Hatfield, Herts. [2387]

DE HAVILLAND PROPELLERS, Ltd.

INSTALLATION engineers are urgently required for work on the following projects:—

REF. General propeller development on B.1 Hydraulic and mechanical engineering.

B.2 Scanner development.

B.3 Cold air units—knowledge of thermodynamics required.

APPLICANTS must have had previous experience in engineering but specialised training for these positions will be given to otherwise suitable candidates.

WRITE in detail or send a postcard for Application Form, quoting reference number of position sought, to The Personnel Dept. (Technical Employment), De Havilland Propellers, Ltd., Hatfield, Herts. [2383]

ELECTRONIC engineers are required by

THE ENGLISH ELECTRIC Co., Ltd., Luton, for work on a high priority defence project. Applicants will be required to undertake the engineering of circuitry already developed, which involves close liaison with, and the progressing of work through, the drawing office and production department. Applicants with experience of the engineering of radar and/or aircraft electronics for production will be especially welcome. The posts are permanent and progressive and a staff pension scheme is in operation. Applications to Dept. C.P.S., 356-7, Strand, W.C.2, quoting ref. 1211. [2114]

TECHNICAL Assistants required by the


NIGERIA Government Broadcasting Department for one tour of 12/15 months with option of appointment (a) on agreement with prospect of permanency with salary, etc., according to experience in scale £750 rising to £1,035 a year or (b) on agreement on temporary terms with salary, etc., in scale £807 rising to £1,115 a year plus gratuity of up to £150 a year; outfit allowance £60; free passages for officer and wife; assistance towards cost of children's passages or grant of up to £150 annually for maintenance in U.K.; liberal leave on full salary; candidates should have not less than 10 years' experience in the engineering division of the B.B.C.; those selected will be required to undertake operational duties relating to the control and maintenance of radio equipment at Radio Distribution Studios and to assist in general technical duties.

WRITE to the Crown Agents, 4, Millbank, London, S.W.1; state age, name in block letters, full qualifications and experience and quote M2C/30188/WF. [2335]

RADIO and television engineer required, fully experienced all makes, for benchmark; good salary and opportunities; references.—Marshall, 76, High St., Witham, Essex. Tel. 3117. [2375]

REQUIRED immediately by B.K.S. Engineering, Ltd., Southend Airport, Essex, radio engineers with workshop overhaul and flight maintenance experience. [2469]

Excellence in design..

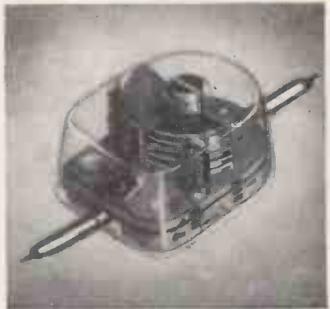

AIR DIELECTRIC TRIMMER
Protected by Acetate Case

Capacities from 4 to 70pfn voltages of 500 and 1,000 D.C. Width 16.5 mm. Length 22 mm. Acetate dust cover optional. Insulation over 10,000 megohms. Power factor less than .001.

Type approved Cat. A. No. 464.

OXLEY

DEVELOPMENTS CO. LTD.
ULVERSTON, NORTH LANCs.
TEL.: ULVERSTON 3306

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE

ROD, BAR, SHEET, TUBE, STRIP, WIRE
3,000 STANDARD STOCK SIZES
No Quantity too Small List on application

H. ROLLET & Co., Ltd.
6 Chesham Place, S.W.1. SLOane 3463
ALSO AT
LIVERPOOL · BIRMINGHAM · MANCHESTER

MAGNEGRAPH

TAPE AND WIRE RECORDERS, second-hand, of all types, bought, sold, exchanged.

NEW RECORDERS

Ferroglyph 2A	76 gns.
Vortexion 2A	80 gns.
Grundig 700L	80 gns.
Magnegraph	59 gns.
B. & H. Reporter, battery operated...	£55 0
B. & H. Reporter, with speaker	£59 0

SECONDHAND RECORDERS

M.S.S. Tape Recorder, with Wearite deck	£85 0
E.M.I. Semi-professional Recorder ...	£60 0
B. & H. Reporter, 7 1/2 i.p.s. battery portable, unused	£45 0
Magnegraphs, complete, from	£45 0
B. & H. Wire Recorder, 50A, excellent condition	£50 0
B. & H. Wire Recorder B2, complete	£30 0

ACCESSORIES

Footswitches	£1 10
Tape Racks, for 12 reels	£2/2/6
Limpet Telephone Pickups	£1 5

All types new and secondhand Tape, Wire, Microphones, Stands, Speakers, etc.

REPAIRS, mechanical and electronic, on all types of recorders carried out by specialists

HIRE SERVICE in Greater London Area only from 2 gns. per week.

S.A.E. for details.

I, HANWAY PLACE, OXFORD ST., LONDON, W.1. Tel.: Lan. 2156

DUODE SOUND UNITS TELL THE TRUTH



We have often said that our units are notable for having no personality of their own. They simply produce in sound what they receive in electrical form from the amplifier, without adding to it. A new friend puts it neatly by writing:—

"I have purchased one of your Units and am completely satisfied. I can best describe it not by saying 'It has something which the others haven't got', but by saying 'It hasn't got a lot of things the others have.'"

Without its context this looks a bit backhanded! But what it really means is that our sound is free from coloration, whisks, boom and other additives: it is just NATURAL.

Duode is without question the best investment anyone can make in good sound.

Write for details to


BARKER

NATURAL REPRODUCERS

3 Newman Yard, London, W.1.

"AUTOMAT" CHARGERS AND KITS S.T.C. and Westalite Selenium Rectifiers

New Goods with Full Guarantee

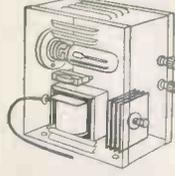

"AUTOMAT" HEAVY DUTY HOME CHARGER self regulating, virtually unreckeable. Damp-proof, selenium rectification, fine workmanship and finish, 12 months guarantee. For A.C. mains, to charge 6 v. or 12 v., 2 amp. model 59/6, p.p. 2/-, 12 v. 3 amp. 69/-, Wt. 8½ lb.

FOOLPROOF CHARGER KITS. Genuinely trouble-free and ultra reliable with components of ample size, standard kit, 12/14 v. 2 amp. rectifier, 46 watt transformer, ballast bulb for 2 v., 6 v., 12 v., 39/6, p.p. 1/10. Ditto, but 12/14 v. 3 amp. Westalite rectifier, 65 watt transformer, ballast bulb for 2 v., 6 v., 12 v., 47/-, p.p. 3/-. Handsome steel case for either above 12/6 extra. "Fully Charged" indicating meter, 13/6. Slider type kit, 12 v. 5 amp. S.T.C. rectifier, 90 watt transformer, slider resistance, ammeter for 6 v./12 v., 24/10/-, p.p. 3/-. Minor kit, 6 v./12 v. 1 amp. rectifier, transformer, ballast bulb, case, 47/-, p.p. 2/-, Wt. 7 lb. Ditto 6 v. 2 amp. only 49/6.

SELENIUM RECTIFIERS. New stock, not surplus. Many 18 mm., 25 mm., 35 mm. bridge, h.w. and c.t. in stock. 12/14 v. 3 amp. to 3.4 amp. Westalite, 15/9, p. 8d.; 6 v. 2 amp. 9/-; 6 v. 4 amp. 16/6; 24 v. 2.5 amp. 27/6; 24 v. 3 amp. 29/6. Large finned type S.T.C. 12/14 v. 6 amp. 33/-; 12 v. 1 amp. train set rect., 4/10, p. 5d.

SMALL SPACE H.T. RECTS. Westalite 250 v. 60 m.a. Brand new. Special offer 7/8; ditto for 260-0-260 v. 100 m.a. 15/-; 250 v. 100 m.a. bridge 15/-; 150 v. 25 m.a. alum. type 6/6; 250 v. 200 m.a. bridge 28/-; 315 v. 200 m.a. bridge 42/-.

"RENEWBAT" battery desulphater and conditioner, works like a charm on elderly batteries, car size, 3/-, p.p. 6d.

ROTARY CONVERTERS for Television from any DC input at 24 v. to 230 v. 250 watts, £25.

CHAMPION PRODUCTS

43 Uplands Way, LONDON, N.21 Phone: LAB. 4457

SITUATIONS VACANT

ADMIRALTY—Royal Greenwich Observatory.

EXPERIMENTAL Officer or Assistant Experimental Officer required in Time Department at Abinger for maintenance and installation of operational equipment of time service. Candidates, British subjects, must possess at least Higher National Certificate or equivalent and have thorough knowledge of basic radio and electronics. Salary, inclusive of pay addition (men) E.O. £649—£800, A.E.O. (according to age) £264—£576. Appointment unestablished, but opportunities occur for establishment through Open Competitions. Application forms from M.L.N.S. Technical and Scientific Register (K), 26, King St., London, S.W.1, quoting D 9/54A. Closing date 9 March, 1954. [2395]

ASSISTANT Signals Officer required by the SIERRA LEONE Government Civil Aviation Department for one tour of 18-24 months with prospect of permanency. Salary (etc.) according to qualifications and experience in scale £742 rising to £1,177 a year. Outfit allowance £60. Liberal leave on full salary. Free passages for officer and wife. Assistance towards cost of children's passage or grant of up to £150 annually for maintenance in U.K. Candidates should be experienced in M.F., H.F., V.H.F. and V.H.F./D.F. and ancillary equipment and should hold the P.M.G. Certificate in Wireless Telegraphy or equivalent. Preference will be given to those holding City and Guild certificates in Radio. Write to the Crown Agents, 4, Millbank London, S.W.1. State age, name in block letters, full qualifications and experience, and quote M2C/30353/WF [2461]

THE STEEL COMPANY OF WALES, Ltd. (Tinplate Division), Trostre Works.

ELECTRONIC technicians required for maintenance of various types of industrial electronic control, consideration will be given to applicants without experience in the above, but with at least five years' experience in the radio industry on maintenance; excellent wages and working conditions in modern cold reduction plant.—Applications, giving details of age, qualifications and experience, should be submitted to: THE Supt. Labour and Wages, The Steel Company of Wales, Ltd. (Tinplate Division), Carmarthen Rd., Swansea. [2225]

An expanding engineering programme has caused vacancies for engineers experienced in one or more of the following fields:

(a) **TUNING** mechanisms and associated V.H.F. circuits.
(b) **SWITCHES** for radio and low-power electrical apparatus.

(c) **VARIABLE** capacitors.
Detailed knowledge of the material problems encountered in this type of development will be advantageous. The salary and future prospects are good, and the laboratory is situated in the London area.—Please reply, giving full details of qualifications and experience, quoting ref. AD/WW, to Box 2712. [2348]

MINISTRY of Supply at Malvern urgently requires skilled:

- INSTRUMENT** Makers.
- TOOLMAKERS.**
- UNIVERSAL** Millers.
- PRECISION** Filtrors.
- CENTRAL** Lathe Turners.
- SHEET** Metal Workers.
- AIRCRAFT** Engine Filtrors.
- AIRFRAME** Filtrors.
- RADAR**/Electronic Instrument Filtrors. To serve as Research and Experimental Mechanics (Special).

RATE of pay for 44-hour 5-day week, on entry as a Research and Experimental Mechanic (Special), is 139/4 plus merit pay of 26/-. There are prospects of advancement to higher rates of merit pay. Hostel accommodation available immediately and housing accommodation may be available within a reasonable period for successful married applicants.

APPLY, giving full particulars of apprenticeship, training (including Forces' training), qualifications and experience to: **DIRECTOR, R.R.E.**, St. Andrew's Rd., Malvern. [2355]

WIRELESS Station Superintendent required by the

GOLD Coast Government Posts and Telecommunications Department for two tours of 18 to 24 months in the first instance. Salary, etc., according to qualifications and experience in consolidated scale £990 rising to £1,230 a year, with gratuity of up to £150 a year. Outfit allowance £60. Liberal leave on full salary. Free passages. Candidates should possess a Higher National Certificate or equivalent, and have had practical experience in two or more of the following fields:—V.H.F. link systems; H.F. communication network; Frequency shift keying and teleprinter maintenance; V.H.F. and E.P. direction finding systems; Aeronautical navigation aids (ground); Manufacture of light engineering instruments. Candidates from the British Post Office should apply through departmental channels.

WRITE to the Crown Agents, 4, Millbank, London, S.W.1. State age, name in block letters, full qualifications and experience and quote M2C/29100/WF. [2355]

TECHNICAL sales engineer required by well-known Group of Companies to specialise in selling, at Home and Overseas, high fidelity sound equipment; give full personal details with application and state salary required, to—Box 3137. [2453]

GEE RADIO

VALVE TESTER TYPE 4A. 230 v. Input. Ex-Govt., in good condition with descriptive book containing circuit diagram of instrument and how to test valves from 1.4 v.-40 v. With Valve-holders for Brit., 4, 5, 7 pin and Octal, U.S. 5, 7 pin. 1/Octal, Side Contact, Large Brit., 4 pin, 9 pin, Acorn and Diode. Housed in substantial wooden case. Price £5/19/6, plus 10/- carriage.

WESTON ALL-PURPOSE A.C./D.C. TEST METER MODEL E.662. New and unused, complete with leads and batteries. A very limited quantity available at £8 each only. Also **WESTON BATTERY OSCILLATOR** MODEL E.692, TYPE 2. Also new and unused. Coverage, 100 Kc/s-26 Mc/s. Audio output approx. 400 c/s. Available at the ridiculously low price of only £5/19/6. If purchased together, these two instruments will be supplied for £12, P. P. 7/6. Booklet of instructions supplied with Oscillator.

42in. METAL EXPONENTIAL HORNS. New and unused. 1½in. fitting. These Horns have a 28in. square flare, weight approx. 25lb., and are 44in. from top to bottom. £2/19/6, carriage 7/6.

150 v. H.T. BATTERIES. (Ex-Govt. ex-38 set). Size 5½in. x 6in. x 1½in. In very good condition, each battery tested before despatch. Also we have in stock again the **90/1½ v. BATTERIES.** Size 8½in. x 4½in. x 3½in. Either battery 4/6 plus 1/6 on each battery for P.P.

TRANSFORMERS. 2,000-0-2,000 @ 450 m.A. Input volts 0-10, 20, 30, 50, 100, 150, 200, 240 volt. £5/10/-, carriage 10/-.

AMERICAN HIGH FREQUENCY SIGNAL GENERATORS. Type 122 A, 110 v. Input 50-230 Mc/s, 8-150 Mc/s. £20, carriage 10/-.

INDICATOR UNITS, TYPE 6C. Complete with 3½in. C.R.T. (VCR 138), mask, base, mu-metal shield. Condensers, resistor, wire wound volume controls, valves J2-VR91's, 2-VR54's). Brand new in original crates, £3/15/-, carriage paid.

ROTARY CONVERTERS. 110 watts output. 230 v. D.C.-230 v. A.C. Complete with variable resistor, in wooden carrying case, £7/10/-, carriage 10/-.

RECTIFIERS. SELENIUM METAL F/B 230 v. A.C./230 v. D.C. @ 1½ amps. £4, P.P. 2/6.

VOLTS AMPS F/BRIDGE PRICE

230 1/2 " " " 30/-

165 4 " " " 160/-

110 1/2 " " " 32/6

50 1/2 " " " 23/6

24 10 " " " 70/-

24 6 " " " 35/-

24 2 1/2 " " " 25/-

24 1 " " " 13/6

12 10 " " " 40/-

12 6 " " " 23/6

12 4 " " " 18/6

12 2 1/2 " " " 16/6

12 2 " " " 12/-

12 1 " " " 7/6

6 " " " " 7/6

P.P. on above recs., 1/-

S.T.C. "K 3" SERIES HALF WAVE RECTIFIERS

K/10-250 v. 1 mA " " " 3/6

K/20-500 v. " " " 5/8

K/25-655 v. " " " 5/8

K/30-755 v. " " " 6/-

K/35-885 v. " " " 6/10

K/40-1 kv. " " " 7/6

K/45-1.140 kv. " " " 8/2

K/50-1.260 kv. " " " 8/8

K/60-1.500 kv. " " " 9/8

K/70-1.780 kv. " " " 11/-

K/80-2.030 kv. " " " 12/4

K/90-2.280 kv. " " " 13/6

K/100-2.550 kv. " " " 14/8

K/120-3.080 kv. " " " 16/8

K/140-3.600 kv. " " " 19/3

K/160-4.100 kv. " " " 21/6

K/180-4.660 kv. " " " 24/3

NB/200-5.150 kv. 5 mA. " " " 26/-

K8/200-500 v. J.50 " " " 5/-

P.P. on the above recs., 6d.


TERMS: C.W.O., C.O.D., or pro-forma invoice.

15 LITTLE NEWPORT ST., LONDON, W.C.2

GERrard 6794/1453

Fidelia

**HAND BUILT
QUALITY
UNITS**

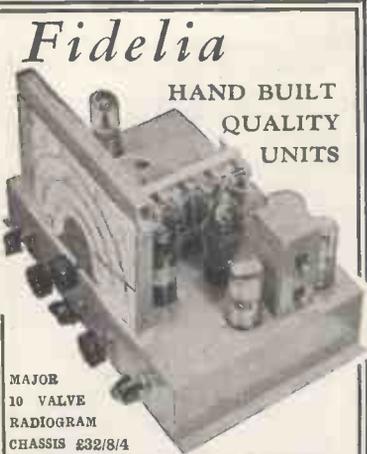

**MAJOR
10 VALVE
RADIOGRAM
CHASSIS £32/8/4**

We have a new amplifier unit particularly for the gramophone enthusiast. The design of this unit has occupied us for many months. In addition to many other features it includes a new continuously variable tone control circuit, the separate controls of which can be operated while playing to give a gradual alteration of tone balance without the sudden jumps and clicks associated with switch circuits. A.F.M. tuner to work with all Fidelia equipment will be available shortly.

Fidelia Standard 7 valve model	£21 12 0
Fidelia Plus 8 valve model	£23 18 4
Fidelia 10 watt amplifier	£27 10 0
Fidelia De Luxe 9 valve model with 7 watt push-pull output stage	£24 6 6

ALL MODELS have triode output stages. Variable Selectivity. Separate Bass and Treble Controls. Cathode follower detector, 20-20,000 cycle audio response.



**ELECTRO
Acoustic
-DEVELOPMENTS-**

2 AMHURST ROAD,
TELSCOMBE CLIFFS,
Nr. Brighton,
SUSSEX
Tel: Peasehagen 3156

-FOR PIONEERS-

400 Mc/s TV. Parts
Experimental Transistors.
Leaflets 1/-

BEL SOUND PRODUCTS CO.,
Marlborough Yard, Archway,
London, N.19. Telephone: ARC 5078.

AUTOMATIC (TIME) SWITCHES

New and reconditioned 15 day clockwork
and electric switches
from **35/-**

Send S.A.E. for illustrated details to —
**DONOHUE (TIMERS) GEORGE STREET
NORTH SHIELDS, NORTHUMBERLAND**

ENGINEERS!

Whatever your age or experience, you must read "ENGINEERING OPPORTUNITIES." Full details of the easiest way to pass A.M.I.Mech.E., A.M.I.C.E. C. & G. (Electrical, etc.), General Cert., etc., on

**144 PAGES
Free!**

Terms and details of Courses in all branches of Engineering—Mechanical, Electrical, Civil, Auto., Aero., Radio, etc., Building etc. If you're earning less than £15 a week, tell us what interests you and write for your copy of "ENGINEERING OPPORTUNITIES" today—FREE

B.I.E.T.

387 College House, 29-31, Wright's Lane, London, W.8.

BRITISH INSTITUTE OF ENGINEERING & TECHNOLOGY

SITUATIONS VACANT
RESIDENT supervising maintenance engineers.
APPOINTMENTS are available in various parts of the British Isles for engineers having sound knowledge of centrimetric radar systems, to take charge of maintenance personnel and to be fully responsible for the serviceability of modern equipment; successful applicants will be given a period of familiarisation with the equipment; the posts are pensionable and, in addition to a good basic salary, generous subsistence allowance will be payable.—Please reply to Box 2841, quoting ref. ABCE. [2372]

ELECTRONIC development engineers.—
Vacancies exist for the following:—
(a) DEVELOPMENT engineer with degree in physics or electrical engineering, preferably with experience of feedback amplifiers or light servo mechanisms.
(b) JUNIOR development engineer with degree or H.N.C.; some experience in industry desirable but not essential.
INTERESTING work on varied development projects in modern laboratories in Surrey; five-day week; pension scheme.—Apply with full details to Box 3066. [2433]

DEVELOPMENT engineer required, design experience of HF and VHF transmitters essential.
GOOD theoretical background and knowledge of production methods desirable.
APPLY with full details to—Personnel Manager, Pyc Telecommunications, Ltd., Ditton Works, Cambridge. [2343]

TELEVISION Radio Engineer, addition to staff; £10 per week.—K & B Radio Services, Ltd., S.E.20. Syd. 8119. [2352]

ELECTRONIC engineers are invited to apply for vacancies in the design and development teams engaged on the following:—
(a) H.F. circuit design.
(b) Domestic and car radio receiver design.
(c) Television receiver designs.
(d) Recording equipment.
(e) Design and development of components associated with above.

APPLICANTS should be of degree or H.N.C. standard and capable of undertaking development work with the minimum of supervision in one of the above fields; the posts carry good salary with opportunity to progress.—Please send full details to Personnel Dept. (ED/154) E.M.I. Eng. Dev., Ltd., Hayes, Middx. [2407]

JUNIOR electronic engineers required for work in the vibration test laboratory on guided weapon projects; vacancies are as follows:—
(REF. 1) For development and constructions of audio-frequency measuring equipment; H.N.C. standard is required.
(REF. 2) For maintenance of audio-frequency test equipment; must be capable of servicing oscillators, power amplifiers, oscilloscopes, stabilised power supplies, etc.; similar experience essential.
GOOD salary, bonus and pension scheme; excellent opportunity for entering the rapidly expanding field of vibration research; 5-day, 36-hour week.—Full details should be sent to the Assistant Manager, The Falrey Aviation Co., Ltd., Dept. W.W. Research and Armament Development Division, Heston Aerodrome, Hounslow, Middx. [2414]

A TELECOMMUNICATIONS firm in the north dealing with multi-channel carrier equipment for use on lines has a number of vacancies in the following fields:

- (1) SPECIALIZED filter designers with experience in conventional type and quartz crystal filters.
 - (2) LABORATORY development engineers of senior grade.
 - (3) EQUIPMENT design engineers.
 - (4) TECHNICAL writer for preparation of handbooks; services experience an advantage; age of secondary importance.
- THE positions are on the established staff of the company, with contributory pension scheme, the usual staff conditions.
APPLICANTS are invited to write, giving full particulars of experience, qualifications and age to—Box 532, Dorland Advertising, Ltd., 18-20, Regent St., London, S.W.1. [2347]

ELECTRONIC Engineers required by The General Electric Co., Ltd., Brown's Lane, Alleyley, Coventry, in their Development Laboratories for work on:
(a) Trials Team in connection with Guided Weapons; 1 Senior Engineer also 3 Engineers.
(b) Servo-mechanisms; 1 Engineer.
(c) Pulse Circuitry; 3 Engineers.
(d) Microwave Circuit; 1 Engineer.
(e) Test Equipment; 2 Engineers.
(f) General Radar Circuit Development; 2 Engineers.
(g) Power units, including electronic stabilizers and rectifier systems; 1 Engineer.
(h) Magnetic Amplifiers; 1 Engineer.

APPLICANTS, preferably with a degree or an equivalent qualification, should have had at least two years' experience in the development and engineering of Service equipment as well as experience in one of the above. Reply, stating age, qualifications and experience, to the Personnel Manager. Ref. E.G. [2463]

ELECTRONIC development engineers (senior and junior) required for electro-medical and industrial electronic equipment development.
APPLICATIONS should be made to the Chief Engineer, General Radiological, Ltd., 15-18, Clipstone St., London, W.1, giving full details of qualifications, experience and salary requirements. [2451]

RECEIVER CHASSIS

TYPE 22

containing a 4 gang and a single gang .0005 condenser, 3 microphone transformers, 3 toggle switches, serial tuning coil former, approximately 2in. diameter by 8in. long, 2 Yaxley switches, 4 potentiometers, complete set of coils, approximately 100 various resistors and condensers, 100 and 500 mfd. capacitors 12 volt. These chassis have been stored in the open with the result that some of the chassis and the front panels are rusty, but the components are available. Offered in 3 grades according to condition, 5/6, 10/-, and 15/-, carriage on each set is 5/6 or 12/6 at a further 5/- per set.

REV. COUNTERS BY SMITHS LTD. 3 1/2in. Dial. Scaled 10 to 5,000 revs. per minute. Luminous pointer. Flexible Metal drive. Approximately 12in. long. Brand new and boxed 25/- Post 1/6.

ROTARY CONVERTERS. Input 6 volts, output 250 volts at 60 mA. Ideal for car radios, electric shavers, etc. Price 17/6. Post 2/6.

ALLERON UNIT—AMERICAN Mk. 4 No. 6H27. Complete in transit case containing pneumatic gear, including air driven gyro. Price 25/-. Carriage 2/6.

ROMEQ VACUUM MPS. These are of course suitable as air compressors size approximately less shaft, 6in. long, 4in. x 4in. dia., fitted 2in. long, 1/4in. dia. splined shaft, pumps are rotary vane type and give a constant pressure or vacuum, develops approximately 40/50 lb. sq. in. New and unused. Price 37/6. Post 2/6.

AMPLIDYNE MOTOR GENERATORS. Ref. 56AMINJ18A. Input 27 volts at 44 amp. Output 60 volts at 8.8 amps, 530 watts. Brand new in Maker's crate. Price 50/-. Carriage 5/-.

POWER UNIT TYPE 46. For 230 volts A.C. Supplies, output 6.3 volts at 13A D.C., and 220 volts at 110 mA. D.C. Contained in ventilated case 19in. x 12in. x 14 1/2in. deep. Weight approximately 1 cwt. For use with 1154 and 1155/T.B. Price 25/10/0. Carriage 15/-.

AMERICAN HEADPHONES. Light-weight type headphones, complete with plug and lead 8/6 per pair. Postage 1/3.

Write for our new List No. 11—ready in March. Price 6d. Postage free inland. Overseas air-mail 2/-.

A. T. SALLIS,

93 NORTH RD., BRIGHTON, SUSSEX
Telephone: Brighton 25806

WE WELCOME YOUR ENQUIRIES S.A.E. PLEASE

VALVES!! TUBES!!

Wholesale and Export Only
First Grade Quality—British & American

S. SZYMANSKI

12a Leighton Grove, London, N.W.5
Tel. GUL 6077/8 Cab. "Shernasske, London"

NEW! Easco HOME BATTERY CHARGER

For 12, 6 or 2 volt batteries
Charging Rate 2 1/2 Amp.
Price Only £5.15s.

EASCO ELECTRICAL LTD. Dept. W.W.
Brighton Terrace, S.W.9
Phone/Grams: BR1xton 4961-2-3.



FIRE!

GENII GALORE IN EVERY NU-SWIFT!

Sealed pressure charges explain the speed, reliability and efficiency of Nu-Swift Fire Extinguishers. Strike the knob—the genii instantly leap out to slay your fire!

NU-SWIFT LTD · ELLAND · YORKS
In Every Ship of the Royal Navy

NEW G.E.C., S.T.C. AND "WESTALITE" SELENIUM RECTIFIERS. Largest L.T. range in Great Britain. Latest Current Products. NOT Surplus.

CURRENT PRICE LIST

ALL S.T.C. & C. RECTS. LESS 15%.
 S.T. & S.E.H.T. K3/15, 4/5; K3/45, 8/2; K3/50, 8/8; K3/100, 14/8.
BRIDGE CONNECTED FULL WAVE.
 17 v. 1.2 a., 16/4; 1.6 a., 26/-; 2.5 a., 29/-; 3 a., 30/-; 4 a., 34/6; 5 a., 37/6, all post free.
 33 v. 0.7 a., 24/3; 1 a., 28/-; 1.5 a., 45/-; 2 a., 51/-; 3 a., 52/-; 4 a., 62/-; 5 a., 67/-; all post 1/-.
 54 v. 1 a., 38/6; 1.5 a., 62/-; 2 a., 69/-; 3 a., 70/-; 5 a., 93/-; 7.2 v. 1 a., 49/-; 1.5 a., 78/-; 2 a., 81/-; 3 a., 92/-; 5 a., 122/-; 100 v. 1 a., 70/-; 1.5 a., 112/-; 2 a., 128/-; 5 a., 174/-; all post 1/2.
BRIDGE CONNECTED HEAVY DUTY 7 1/2 in. SQUARE COOLING FINS. 17 v. 6 a., 49/6; 10 a., 56/-; post 1/6.
BRIDGE CONNECTED HEAVY DUTY Funnel Cooled, also 7 1/2 in. SQUARE COOLING FINS. Revised price, same both types. 17 v. 12 a., 102/-; 20 a., 118/-; 30 a., 164/-; 50 a., 112/15/-; 33 v. 6 a., 91/-; 10 a., 104/-; 12 a., 168/-; 20 a., 188/-; 54 v. 6 a., 120/-; 10 a., 142/-; 7.2 v. 6 a., 154/-; 10 a., 178/-; 100 v. 6 a., 111; 10 a., 112/15/-; all post 1/10.

"WESTALITE" (BRIDGE), 12-15 v. D.C., 1.2 a., 15/10; 2.5 a., 27/8; 5 a., 31/9; 10 a., 54/6; 20 a., 99/6; 30 a., 144/10; 50 a., 257/-; 24 v. 1.2 a., 15/10; 2.5 a., 27/8; 5 a., 51/-; 10 a., 92/7; 20 a., 176/2; 36 v. 1.2 a., 27/8; 2.5 a., 51/7; 5 a., 69/10; 10 a., 130/9; E.H.T. RECTS., 14D, 134, 22/-; 36 E.H.T. 60, 31/10, all post extra.

Wholesale and Retail
 Special Price for Quantity.

T. W. PEARCE

66 GREAT PERCY STREET, LONDON, W.C.1
 Off Pentonville Rd. Between King's Cross and Angel



TAPEMASTER RECORDING COMPONENTS Suitable for use with either Hartley or Culpitts circuits. Retail
JUNIOR MODEL Play/record, imp, 3,000 ohm at 1 Kc. Erase...at each £1 19 6
SENIOR MODEL Play/record, imp, 5,500 ohm at 1 Kc. Erase...at each £2 5 0
 Oscillator Coil in can each 10 6
 Oscillator Unit, incl. coil and 6V6GT valve each £2 5 0

TAPEMASTER MAGNET FEATURES. Electrically balanced to ensure low "hum" level. Play/Record Model with .0005in. gap ensuring max. top response. Beryllium Copper, non-magnetic gappings. Mu-metal cores for Play/Record models. Track width for Play/Record, .082in., Erase .110in. To match for tracking. Bias frequency 45 Kc., exactly matching Tapemaster oscillator units and coils. Output 10 mV. Recording level, 15-20mV. With optimum bias, recording level and suitable correction of Amplifier response in frequency equals tape speed in inches/sec. Full instructions included for oscillator units and amplifier circuits.

AVAILABLE FROM ALL GOOD
 RADIO DEALERS.

WINTER TRADING CO. LTD.

6, HARROW RD., LONDON, W.2.

SITUATIONS VACANT
SENIOR microwave engineers are required by:—
THE ENGLISH ELECTRIC Co., Ltd., at Luton, for work on a high priority defence project. Applicants should have a good theoretical background in degree standard and experience of design or engineering of microwave equipment for development work on aerial and receiving systems. This work includes investigations of new methods of construction with a view to miniaturisation and weight reduction, the design of new components and engineering to the production stage. Successful applicants will be required to take charge of a group and to be responsible for one or more aspects of the system. The posts are permanent and progressive and a staff pension scheme is in operation. Applications to Dept. P.E.S., 336-7, Strand, W.C.2, quoting ref. 1160B. [2115]

RADIO service mechanics required by Smiths (Radomobile) Ltd., for many parts of the country.—Write details of experience and qualifications to Personnel Officer, Goodwood Works, North Circular Rd., London, N.W.2. [0342]

PYE TELECOMMUNICATIONS, Ltd., Ditton Works, Cambridge, will shortly have a limited number of vacancies for junior engineers; experience in VEF design and engineering is essential.

SALARIES according to qualifications and experience; modern factory, sports, social and canteen facilities; single board available. PLEASE apply, stating age, qualifications and experience to the Personnel Manager. [2342]

RADIO and Television. Junior Development Engineers required. Must have had previous experience in this field.—Apply by writing giving full details of experience to Alba Radio, 52-58, Tabernacle St., E.C.2. [2346]

APPLICATIONS are invited for the position as Supervisor of the Test Department of a large established organization engaged in expanding into a new factory on the South Coast; essential qualifications are:—AGE: 35-45 years; good technical background in electronics; considerable factory experience of testing and control of staff, preferably in relation to microwave radar and pulse equipment; the appointment is subject to a probationary period in the existing organization, which will provide every opportunity to prove suitability. WRITE full details of education, experience and expected commencing salary to—Box 2676. [2332]

DRAUGHTSMAN required with experience of light mechanical or electro-mechanical design; good prospects with expanding company in Surrey; five-day week; pension scheme.—Apply with full details to Box 3061. [2454]

EXPERIENCED T.V. and radio engineer required to open service department with old-established firm in Channel Islands; accommodation arranged; good wages; perm. position; interview arranged London.—Box 2816. [2363]

TELEVISION-RADIO service engineer required, fully experienced all makes; help will be given to find accommodation if required. L. Williams, 35, High St., Denbigh, N. Wales. Tel. 305. [2379]

TELEVISION engineer required, must be fully experienced and quick fault finder, progressive position with accommodation if necessary, commencing salary £600 per annum.—Apply giving full particulars to Box 3006. [2423]

RADIO/TELEVISION engineer, qualified, required by West End Murphy dealers, able to drive, permanent situation with top wages to suitable applicant; half-day Saturday.—Larg & Sons Ltd., 77, High Holborn, W.C.1. [2475]

AMPLIFIER equipment manufacturers require testers and service engineers experienced in audio equipment.—Write, giving full details, age and experience, The Trix Electrical Co. Ltd., Maple Place, Tott. Ct. Rd., London, W. [2368]

OXFORD—Vacancies for two experienced television engineers, must be able to drive, £9 weekly plus overtime for demonstrations, large, old established, privately owned music shop.—C. Taphouse & Son, 3, Magdalen St. [2401]

DRAUGHTSMAN required immediately for light electrical engineering factory, Stockport district; must be experienced in electronic instruments and test gear; 5-day week, canteen facilities; write stating salary required and qualifications.—Box 2603. [2326]

I.B.M. United Kingdom requires young engineer or physicist with degree or equivalent qualification and electronic experience; knowledge of digital computer design desirable.—Apply in writing, stating qualifications and salary required, to Box 3102. [2438]

EXPERIENCED radio testers and inspectors required for production of communication and radio apparatus, also instrument makers, wiremen and assemblers, for factory test apparatus.—Apply Personnel Manager, E. K. Cole, Ltd., Ekco Works, Malmesbury, Wilts. [0238]

ELECTRICAL Engineer required for research work on magnetic circuits, B.Sc. essential; exceptional opportunity to work on a new project for a man with initiative and energy; applicant will also act as technical adviser to sales manager; salary commensurate with experience and ability; full details to, Telcon-Magnetic Cores, Ltd., Industrial Estate, Chapelhall, Aldridge. [2386]


SSC Bargains from SHERMAN'S

All Carriage Paid and Money-Back Guarantee!
FLASHER MOTOR UNITS

Containing small 24 v d.c. motor approx. 2 1/2 in. x 1 1/2 in. and Reduction Gear Box, driving cam operated contacts. Ideal for Flashing Indicator, Illuminators, etc. Motor and Gear Box useful for all types of models, 25/-



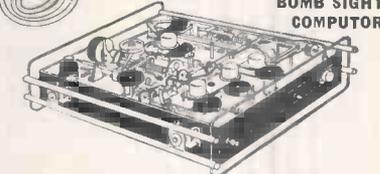SPIRIT BLOW LAMP 7 in. o.a. x 1 1/2 in. diam. Heavy duty brass. Brand new. Ideal for model making. 10/6




BOMB SIGHT COMPUTER

A model maker's paradise, over 65 lbs. of magnificently made gears, driving shafts, bearings, miniature motor, repeater motor, gyroscopes, etc. All supplied in a strong wooden transit case 24 in. x 22 in. x 1 in. high which itself is ideal as a tool box. Only Each 62/6

APOLLO SPRAY GUN

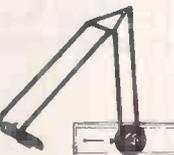Ideal for model maker and handyman. Will spray paints, insecticides etc. Will work from foot pump, spare cartridge, compressor, etc. New and boxed 15/-



PLOTTING ARM Complete with 36 in. long hinged rail for attaching to drawing board. A simple draughting machine without any modifications. Imperial size 25/-

Double elephant size, with rail..... 30/-
Set of TWIST DRILLS 9 drills, 1/8-1/4 in., complete with plastic case and stand. Brand new. 4/6

TOOL BOX

U.S.A. manufacture, size 18 in. x 12 in. x 5 in. Strongly made waterproof ply, all external edges reinforced. Subdivided as illus., leather carrying handle. Outside resprayed green. 17/6



OHMMETER. 4 scales, 2 1/2 in. diameter, reading 0-5,000 ohms, 0-60 mA., 0-1.5 v., 0-3 v., suitable for continuity testing. Will operate from 1.5 v. battery, strong case, with full instructions engraved on back. Brand new, 19/6. Carrying sling, 1/- ex.

TERMS—CASH WITH ORDER. C.O.D. 1/- EXTRA
 Phone Orders Accepted (Dept. W.1.)
 479 HARROW RD., LONDON, W.10.
 LADbroke 1718.

SHERMAN'S SUPPLY COMPANY

SPECIAL OFFERS

INSTRUMENT KNOBS. 2½ inch with 3 inch skirt, Black Bakelite 3/- ea. Post 6d.
RECEIVER R132A. We can offer you this well known 11 valve Superhet covering 100/124 Mc/s together with a standard 200/250 v. A.C. Power Pack No. 3 at the special price of £6/15/-, carr. 10/-. These units are brand new and unused including valves, but as they have been in storage some are slightly marked.

AMPLIFIERS. A high fidelity unit with separate Bass and Treble controls, constant Impedance attenuator for setting volume level. In metal case with handles, 15 watt output, for 200/250 v. A.C. Mains operation. Although intended for use with the Gaumont British Projector, this fine amplifier is ideal for P.A. work, dances, etc.

SPECIAL OFFER. LESS VALVES, £12/10/-. Overcomplete with all valves, £15/12/6. Carriage 10/-.

SPEAKERS P.A. Goodmans P.M. 12in. 15 ohms. Type T.2. A high class speaker at a low price. Ideal for above amplifier, £5/10/-.
SPEAKER CASE, suitable for above. 19 x 17 x 13in. With lock, carrying handle, compartment for cable. £3/10/-. Worth double.

AMMETER. 2½in. Flush 0/25 amps. Moving Iron. D.C. 7/6, post 1/-.

MILLIAMMETERS. Moving Coil. D.C., 2½in. Flush 0/30, 0/200, 0/250, 12/6; 3½in. Flush, reading 150-0-1,500, 22/6, post 1/-.

VOLTMETERS. Electrostatic 2½in. Flush 0/2,000, 40/-; 0-300 Flush D.C. Moving Coil, 10/6; 0-20 2in. Flush Moving Coil, 7/6; 0-40 2in. Flush M.C., 10/6, post 1/-.

RECEIVER R.1355. As specified for "Inexpensive Television." In original packing, as new. Complete with all valves, 38/6, carriage 7/6.

WILCO ELECTRONICS

DEPT. WW

204 LOWER ADDISCOMBE RD., CROYDON

TAPE-DISC

SERVICE

Have your favourite tape-recording made into a gramophone record. 1½d. stamp for free literature to . . .

H. R. McDermott, 10, Duke Street, Darlington, Co. Durham

TANNOY

PRODUCTS

SOUND EQUIPMENT

clearly the best for all occasions


WEST NORWOOD, S.E.27. - Gipsy Hill 1131 (7 lines)



TELETRON SUPER INDUCTOR COILS

Miniature Dust Core Types.

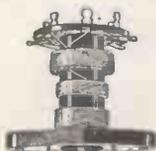Type HAX.R.F. Transformer, Triple wound for Germanium Xtal Diodes. ● Q 100 ● Gain 33 Times ● No overlap. Unique performance. Each 3/-.



DUAL WAVE TRF. COILS

Type TRF.A/HF. or TRF.A/D. Tuned anode with reaction. Ae. Primary windings designed with rising characteristic to balance fall in ckt. Q. Matched pairs. Fr. 7/- 5/6d. range for S., M. and L.W. Fr. 6/-.

I.F. Transformers, Filters, etc. Stamp for circuits and data.
THE TELETRON CO.,
 266, Nightingale Road, London, N.9.
 Trade enquiries to sole distributor: **SAM MOZER,**
 95, Kendal Avenue, N.18. Edm. 7707.

SITUATIONS VACANT

HIGH frequency heating service engineer required; age not over 30; keenness is more important than previous experience; the applicant should be able to drive and have a good knowledge of radio and electricity.—Apply below.

HIGH frequency heating technical representative required; applicants should preferably have had previous experience on the sale of all classes of such equipment.—Apply Managing Director, Radio Heaters, Ltd., Easthewth Ave., Wokingham, Berks.

A.B. METAL PRODUCTS require additional technical representatives; connections with leading radio and electronic equipment manufacturers essential.—Apply in confidence, Sales Manager, A.B. Metal Products, Ltd., 16, Berkeley St., W.1. [2362]

ELECTRICAL test room assistants required with practical experience in assembling and calibrating precision instruments, good prospects for men with the required qualities.—Apply by letter to Cambridge Instrument Co., Ltd., Sydney Rd., London, N.10. [2428]

DRAUGHTSMAN, aged 22-25 years, required for mechanics and electronic work; must be neat and accurate and capable of making production drawings from original sketches and ideas; excellent working conditions, bus services to Kingston, London, Guildford, pass the premises.

CANTEEN, pension scheme, sports and social club, with recreational facilities. **APPLICANTS** must be of British Nationality, full details of experience and salary required should be addressed to: THE Joint Secretary, Cottage Laboratories, Ltd., Portsmouth Rd., Cobham, Surrey. [2360]

QUALIFIED men, with sound mechanical background (fitting, etc.) and preferably some electrical knowledge, wanted for maintenance work in field and factory on intricate mechanical devices used on radar.—Write, giving details of experience, qualifications and age, to Box 2778. [2361]

SENIOR broadcast receiver designer for leading radio manufacturer capable of assuming responsibility for presentation, and mechanical design and with some knowledge of broadcast receiver circuits; extensive experience of tool-room and machine-shop practice essential.

REPLY in confidence with full details of qualifications and experience and salary required.—Box 2894. [2403]

RADIO and television field service and bench service engineers required, with first-class experience; excellent opportunities in new service factory with good working conditions and good salary.—Write or telephone Leytonia Radio, Ltd., 784/786, High Rd., Leyton, E.10. Tel. Leytonstone 3003.

QUALIFIED radio and television engineer required as branch manager for new shop in Bridgwater; permanent pensionable post; assistance given with housing, state wages re-quired; applications to be received by February 1st 1954.—West Somerset Co-operative Society, Ltd., 27-30a, East St., Taunton. [2410]

TRANSFORMER Designer required for development projects involving audio-frequency power transformers, with experience in oil-filled units, etc.—Apply stating age, qualifications and experience, to The Personnel Manager (Ref. R.G.), The General Electric Co., Ltd., Brown's Lane, Allesley, Coventry. [0260]

ASSISTANT Engineer reqd. for valve production dept. in Ruislip area; applicants must have had previous experience of valve manufacture and a sound knowledge of vacuum technique; minimum qualifications Inter B.Sc. or O.N.C.—Apply by letter to Personnel Dept., E.M.I., Ltd., Hayes, Middx. [2426]

ASSISTANT development engineer, experienced in design of C core transformers, chokes, toroidal coils and various couplings for electronic equipment; good salary and a permanent position with first-class working conditions in well-equipped laboratories; good canteen sports ground and social club; 5-day week. The premises are situated on the main bus route from Kingston and Guildford. **APPLICANTS** must be of British nationality and should submit full details of age, qualifications and experience to the Joint Secretary, Cottage Laboratories, Ltd., Fairmile Cottage, Portsmouth Rd., Cobham, Surrey. [2444]

DRAUGHTSMEN required for design and production of light electro-mechanical apparatus, varied and interesting work; previous experience in the radio industry an advantage; please apply, stating age and full details of past experience to—Personnel Manager, Pyc Telecommunications, Ltd., Ditton Works, Cambridge. [2344]

A TECHNICAL Sales Representative with electronic knowledge of the application of electronic components is required by a large radio component manufacturer. The position offers excellent scope and prospects to a man of outstanding personality with the necessary experience and knowledge of the trade.—Reply to Box 2777. [2359]

TEST gear design engineers and maintenance engineers required with practical experience of this class of work based on sound knowledge of electronic principles; these vacancies are permanent and progressive; a company pension scheme in operation; London area.—Please write in confidence, giving full details of qualifications, to Box 2843. [2374]

EUREKA & CONSTANTAN RESISTANCE WIRES

Prices per ounce

SWG	Enam.	DASC.	SWG	Enam.	DASC.
16	1/6	1/6	28	2/1	2/6
17	1/6	1/6	29	2/2	2/6
18	1/6	1/6	30	2/2	2/6
19	1/6	1/6	31	2,3	2,8
20	1/6	1/6	32	2/3	2/9
21	1/6	1/6	33	2/4	3/-
22	1/6	1/8	34	2/6	3/-
23	1/6	1/10	35	2/8	3/3
24	1/8	2/-	36	2/9	3/6
25	1/10	2/2	37	3/-	3/9
26	2/-	2/4	38	3/3	4/3
27	2/-	2/4	40	3/6	4/9

COPPER WIRE

ENAMELLED		TINNED	
SWG	2ozs	4ozs.	4ozs.
16	1/4	2/-	1/4
18	1/4	2/2	1/4
20	1/5	2/4	1/5
22	1/6	2/6	1/6
24	1/7	2/8	1/7
26	1/8	2/10	1/8
28	1/9	3/-	1/9

SEND STAMP FOR LIST. TRADE SUPPLIED

POST RADIO SUPPLIES
 33 Bourne Gardens, London, E.4

WATERLOO RADIO

METAL RECTIFIERS. Bridge, 2 Amp. 11/3, 3 Amp. 12/6, 4 Amp. 15/-, 6 Amp. 23/6, post 1/4.
TRANSFORMERS for use with above rects. Input 200-250V 50~A.C. to charge 6 or 12 Volts at:—1.5 Amps. 13/9, 3 Amps. 22/9, 6 Amps 32/6, post 2/-.
HALF WAVE RECTIFIERS. 125 A.C. input RM1, 60mA 3/9, RM2, 100mA 4/3, RM3, 125mA 5/3, RM4, 250V A.C. in. 276mA, for TV 15/6, post 6d.
Overseas enquiries invited.

35 TENISON WAY, LONDON, S.E.1

THE

CHAFFEY

CABINET COMPANY

50a, CHELTENHAM RD., LONDON, S.E.15
 TEL: NEW CROSS 4766

Chassis, Cases and

all metal fittings made to specification for the Radio and Electronic Industry.

STAR METAL PLATE WORKS

74 CHURCH RD., BARNES, S.W.13
 Tel: RIV 6673/4

U.S. WAR SURPLUS WANTED

APR-4, APR-5, APR-1, ARC-3, etc.; TS-12, 13, 34, 35, 36, 45, 120, 146, 155, 173, 174, 175, 323 and other "TS"-units, etc., particularly for the MICROWAVE REGION; also U.S. commercial laboratory equipment (General Radio, Ferris, etc.); special tubes such as 723A/8, 3C22, etc.; spare parts technical manuals; single units or large quantities.

Sell direct to us, receive the full top price. Describe and price to:

ENGINEERING ASSOCIATES

444 Patterson Road,
 Dayton 9, Ohio, U.S.A.

Free from distortion



cannot introduce hum

E.M.G.

STEEP-CUTTING INFINITELY VARIABLE FILTER

No other filter combines all the advantages of this model which are, briefly, to cut response above any desired level between 4,000 and 8,000 c.p.s. at an average steepness of 30 db. per octave, easy fixing (connects between 15 ohm speaker and amplifier output), robust construction, no distortion or appreciable loss of volume. Recommended for reducing surface noise on '78' records, cutting 'edge' on some L.P. records, and eliminating high-pitched interference on radio. Price £4/10/0. Leaflet on request.

E.M.G. HANDMADE GRAMOPHONES, LTD.
6, Newman St., Oxford St., W.1
Telephone: Museum 9971-2-3

Most types of coil winding undertaken. Very quick delivery, small or large quantities. Transformers, Chokes, Solenoids, Relay Coils, etc., wound on your own bobbins or formers for your own assembly. Impregnating (varnish) on all work done if required. Best quality material used. Single prototypes made to high standards, regulation and cool running, etc.

FOR CATHODE RAY TUBE FAILURES. Special low capacity secondary winding for Heater/Cathode shorts to restore picture after this fault has occurred. All Primaries tapped, framed and tag panelled. 200/250, 2 v. at 2 a., 4 v. at 2 a., 6.3 v. at 2 a., 10.8 v. at 0.3 a., at 29/6 each.

EMISSION REJUVENATORS. 200/250 tapped output tapped in steps. 2 v. to 2½ v. to 2½ v. at 2 a., at 35/6 each. Output 200/250 tapped in steps 6.3 v. to 7 v. to 8 v. up to 9½ v. at 2 a., at 37/6 each.

Both space wound for Heater/Cathode shorts also

T.V. HEATER TRANSFORMERS 200/250 6.3 v. at 7 a., 0.2-6.3 v. at 2 a., at 19/6 net.

T.V. AUTO TRANSFORMERS. 0.190-210-230-240 at 6.3 v. at 7 a., 0.2-6.3 v. at 2 a. at 27/6 net.

T.V. FRAME TRANSFORMER. 60 H. magnetic deflection, suitable for most home constructed sets at 15/6 net.

HALF SHROUDED, 200/250 input, 250/0 250 80 mA, 6.3 v. 3 a. and 5 v. 2 a., 12/9 net plus 1/1 P. & P.

NORTHERN TRANSFORMER CO.
215 BARKEREND ROAD,
BRADFORD, YORKS.

SITUATIONS VACANT
ELECTRONIC Testing: Test Room Foreman required by Hearing Aid manufacturers. Must be familiar with miniature amplifiers. Factory training and organising ability essential.—Apply: Amplivox, Ltd., Abbey Trading Estate, Wembley. Tel. Wembley 5906. [2396]

ENGINEER required for electrical development department of a progressive communications company; national certificate standard required; salary according to ability.—Write Box 444, Sells, Ltd., Brettenham House, Lancaster Place, W.C.1. [2415]

TELECOMMUNICATIONS Sales Engineer, with good experience of V.H.F. communication equipment, wanted by important company in Nairobi, Kenya, who represent well-known British manufacturers throughout East Africa. Free air passages, home leave, pension scheme, annual bonus.—Details in strict confidence, to Box JA/51, c/o 95, Bishopsgate, E.C.2. [2398]

A. C. GOSSOR Ltd., require jun. development engs. for radio communications, television and instruments projects: eng. degree or equiv. prof. quas., expd. in developing equip. to Government and other specifications an advantage.—Write, stating age, quas., exp. and salary reqd., to Personnel Manager, 22, Highbury Grove, N.5. [2440]

MECHANICAL designer for television and radio domestic equipment required, candidates should be at least of H.N.C. or similar educational standard, with a workshop apprenticeship and have 3 years' experience as a mechanical designer; salary according to experience and qualifications but not less than £600 p.a.

APPLY in writing to the Personnel Officer, MITCHAM WORKS, Ltd., New Rd., Mitcham Junction, Surrey, quoting reference R.2A [2420]

MECHANICAL engineer with knowledge of electronics required to take charge of small department (North-West London area) engaged in the measurements of dynamic stresses in aero engines; applicants should have previous experience in this field.—Apply Box 6C 87067, Samson Clark, 57/61, Mortimer St., W.1. [2437]

DEVELOPMENT engineer required for electrical engineering laboratory, engineering degree or equivalent, for work on all types of electrical measuring instruments.—Write, giving full details of education, experience and salary required, to Employment Manager, Sangamo Weston, Ltd., Great Cambridge Rd., Enfield. [2472]

DEVELOPMENT Engineer reqd. for the design and development of equipment for interesting new project on television relay; previous experience of T.V. carrier-type telephone systems, or wide band amplifiers an advantage; applicants with a degree in Engineering or the equivalent preferred.—Apply to Personnel Dept., (SS/2), E.M.I. Ltd., Blyth Rd., Hayes, Middx. [2425]

A WIREMAN is required by the research laboratories of The General Electric Co., Ltd., North Wembley, Middx.; applicants should have a good working knowledge of electronic circuit practice and must be capable of working to schematic diagrams.—Apply in writing to Staff Manager (Ref. RLO/16), giving full details of age, qualifications and experience. [2471]

APPLICATIONS are invited from craftsmen for radio and television service in areas within Herefordshire and Shropshire; applicants must be fully experienced in the repair and maintenance of all types of radio and television receivers; rate of pay at present 3/8 per hour, N.J.C. conditions.—Apply in writing to Sub-Area Manager, Midlands Electricity Board, Ditherington, Shrewsbury. [2307]

ELECTRONIC engineers to become section leaders of small teams responsible for the preparation, testing in the field, and further laboratory development of guided weapons, applicants should have at least H.N.C. and 5 years' experience in the micro-wave, pulse or communication field; equivalent training and experience in H.M. Forces will also qualify for these positions.

ASSISTANT engineers to form such teams, either (a) with a similar background to the above or (b) having considerable experience of developing and testing small prototype electro-mechanical instruments.

THE vacancies which offer exceptional scope for advancement are at Heston Aerodrome, Middlesex, periods of work at outstations in the U.K. are covered by adequate allowances and week-end leave privileges; there are likely to be opportunities for continuing some of this work in Australia at a later date; good salary with bonus, pension scheme.—Details of experience and qualifications should be sent to the Assistant Manager, Dept. W.W., The Fairley Aviation Co., Ltd. Research and Armament Development Division, Heston Aerodrome, Hounslow, Middx. [2384]

PRODUCTION engineer required in the factory engineering section of a radio and television manufacturer; applicants should have had experience of engineering new designs through the pre-production stages and into full production, and will be required to liaise between production and design departments.—Reply to Fulco, Romford Rd., Chigwell, Essex. Tel. Hainault 4151. [2405]

H. FRANKS

58 NEW OXFORD STREET LONDON, W.C.1
PHONE: MUSEUM 9594

One minute from Tottenham Court Road Stn.

COLD CATHODE RELAY UNITS, fitted two S.T.C. Cold cathode tubes, No. G240/2D, two Siemens High Speed Relays, 1,700/1,700 ohms, size of unit approx. 6in. x 7in. x 4in. £3/2/6 each.

METROPOLITAN VICKERS D.C. RELAYS, Type B.1, 10/24 v. D.C., coil resistance, 425 + 425 ohms, four heavy make carbon contact, two medium break contacts. Housed in metal case, 7½in. x 6in. x 2½in. 37/6 each.

HEAVY DUTY 12/24 V. D.C. HIGH-SPEED RELAYS, pattern 6357, type J6. Made by Plessey & Co. Two heavy make contacts, fitted in glass case, 5½in. x 3½in. x 4in. 27/6 each.

SOLENOID OPERATED D.C. CONTACTORS, 200/250 volts, coil resistance 2,000 ohms, silver contacts to carry 10 amps. 25/- each.

INFINITELY VARIABLE-SPEED GEAR-BOXES. Fitted ½in. diam. shafts, mounted in ball-races, adjustable torque, reversible, overall size 5in. x 5in. x 4in. approx. Precision made. 47/6 each.

Dicto, smaller type, overall size 3in. x 3in. x 3in. approx. 40/- each.

"BULL" 1/10th h.p. INDUCTION MOTORS, 230/250 volts A.C., 50 cycles, capacitor start, 1,425 r.p.m., reversible, overall size 7in. long, 5in. diam., spindle ½in. diam. £3/15/- each.

PORTABLE FIELD TELEPHONE SETS, type D, fitted handset, extra headset, tuned buzzer, Morse tapping key, etc. £5/10/- the pair.

PRECISION DIFFERENTIAL GEAR-BOXES, fitted ½in. diam. spindle, 48 d.p. gears size 2in. diam., ½in. deep. 8/- each.

CONSTANT SPEED MOTORS, 3,000 r.p.m., governor controlled, continuous rating, size 5½in. x 3½in. x 3in., ½in. diam. spindle. 40/- each.

"STANCOR," U.S.A. 2.5 K.V.A. 50/60 cycle auto-transformers. Input, 115/250 v. Output, 110 v. Completely shrouded. £11 each.

WESTINGHOUSE RECTIFIER SETS. Style 228 G.P.O. Input, 200/250 volts A.C., 50 cycles, output 50 volts D.C., 1½ amps. £3/10/- each, carriage 10/-.

VARIABLE RHEOSTATS. Graduated ½ amp. to 2 amps., 45 ohms. Ideal for chargers, voltage control, etc. Ref. 50/728. Fitted in Bakelite case 4in. square 1½in. deep. 12/6 each.

SPERRY'S CONSTANT-SPEED 115 volt 50 cycles motors, 2,400 r.p.m., ¾in. diam., 6in. long, 5/16in. spindle, 1½in. long. Serial No. LB1931. 37/6.

MINIATURE CLOCKWORK TIMERS Variable, 10 seconds to 3 minutes. Ideal for model work, photographic timing, etc. With slight modifications will run 15 mins. full wind, size 1½ x 1½ x 9/16in. 3/6 each.

20-WATT POTENTIOMETERS, 200 k. Fitted slow motion dial with vernier control, 3½in. diam., overall height 4½in. Pattern 8419. Price 37/6 each.

CANADIAN FULLY SMOOTHED ROTARY TRANSFORMERS, housed in metal case 8½ x 6 x 4½in. Input 12 v. 2.5 amps. Output 220 v. D.C. 60 mA. Price 40/- each.

HOOPER BLOWER MOTORS, ref. No. 10K8/115 for 12/24 volts A.C./D.C., ideal for car heaters, cooling, etc. 27/6 each.

STEPDOWN TRANSFORMERS, input 180/230 volts A.C., 50 cycles, output 4.2-4.2 volts, 10 amps., ideal for soil heating, spot welding, etc. 35/- each.

ROTARY RHEOSTATS, 7½ ohms, 6½ amps. 25/- each.

SANGAMO MOTOR UNITS, model 7, final speed one rev. 24 hours. 200/250 v. A.C. 50 cycles. Price 27/6 each.

SANGAMO MOTOR UNITS, model 7, final speed one revolution per seven days, 200/250 v. A.C., 50 cycles. Price 30/- each.

MINIATURE IMPULSE MOTORS, made by "Gents," size 3 x 2 x 1½in. Suitable for operating models, switches, etc. Operates on 4/6 volts A.C./D.C. and is very powerful for its size. Price 8/6 each, Post paid.

10,000 G.P.O. type 3,000 and 600 relays, assorted contacts and coils. Siemens High Speed Relays, Uniselectors, Telephone Keys, Handsets, etc.

Mailing Lists. Price 6d. each.

HIGH - FIDELITY FREQUENCY MODULATION

REALISE THE FULL COMPASS
OF YOUR EQUIPMENT.

OUR "WW" DESIGN FM AM VHF
RECEIVER is available for EX-
STOCK DELIVERY FIELD-
PROVEN RELIABILITY AND
SENSITIVITY.

- 4v (2 ger. diodes) chassis with
power supply £15.0.0
- Less P/S £11.17.6
- Complete kits £7.5.0

Leaflet 1.0

Ring ARC 5078 for a demonstration.
Trade enquiries invited.
BEL SOUND PRODUCTS CO.,
Marlborough Yard, Archway,
London, N.19.

LOCKWOOD

makers of

Fine Cabinets

and woodwork of every descrip-
tion for the Radio and allied trades

LOCKWOOD & COMPANY
Lowlands Rd., Harrow Middlesex. Byron 3704

THE
DESIGN and DEVELOPMENT
of specialised equipment for
Research and Industry.

DUN (electronics) & CO.,
17 Victoria Gardens, London, W.11. Park 6636

TELECRAFT

AERIALS ENSURE THE
BEST TELEVISION

TRY ONE AND SEE FOR
YOURSELF

HIGH GRADE TRANSFORMERS

FOR ALL PURPOSES

SINGLY OR IN QUANTITIES
TO YOUR SPECIFICATION

VARNISH IMPREGNATED

BAKED WINDINGS

WITH OR WITHOUT TAG PANELS

GOOD DELIVERIES

Our rewind dept. will handle your
repairs promptly and efficiently.

P. HOWORTH

(Dept. W.W.)
51 POLLARD LANE · BRADFORD
Tel.: 37030

SITUATIONS VACANT

ENGINEER, aged 26 to 34, required to take charge of engineering department of factory manufacturing quartz crystals; university degree and experience of industrial or serviced electronic equipment essential; rudimentary knowledge of chemistry an advantage; house could be made available to successful applicant.—Write Box W.B. 8475, A.K. Advc., 212a, Shaftesbury Ave., London, W.C.2. [2412]

ELECTRONIC engineer required by Birmingham Company handling wide range of industrial and laboratory instruments; applicants (age 25-35) must possess degree in Electrical Engineering or membership of I.E.E., be capable administrators, experienced in application engineering and able to expand sales. Salary £750-£1,000 according to age and experience; pension scheme.—Box 3134. [2448]

VACANCIES exist for senior executive and 2 salesmen in one of the largest U.K. electronic organizations to take over planning and marketing in this country of high fidelity sound amplifying equipment; excellent opportunities with first-class prospects for right type of men; experience in this field essential; when applying state age and give full particulars of qualifications.—Box 2999. [2419]

ASSISTANT engineer required for laboratory work, including investigation of climatic effects on radio communication equipment; experience of measurements of radio transmitters and receivers essential; qualifications equivalent to Ordinary Nat. Cert. or Inter. B.Sc. standard desirable.—Apply to Employment Manager, Ferguson Radio Corporation, Ltd., Gt. Cambridge Rd., Enfield, Middx. [2451]

INTERESTING work in connection with the development of loudspeakers of conventional and novel types is offered by a large manufacturing company in the London area. A sound basic knowledge of electro-acoustic problems is the primary requirement, and some knowledge of amplifiers and other electronic apparatus will be of value.—Write quoting ref. Y8/WW, giving full personal particulars to Box 2715. [2351]

TELEVISION service engineers required for long established radio and television organization with branches in the main cities of Scotland; applicants must be capable of servicing television receivers in the field and must be able to drive light van; prospects of promotion for successful candidates; superannuation scheme in operation; excellent remuneration to successful candidates.—Apply Box 2544. [2376]

TELEVISION engineer, experienced, required for new workshops in Mdx.; starting salary £10 p.w. plus overtime, making earnings £12-£14 p.w. with scope for rapid advancement to head area maintenance dept. at salary range £750-£1,000 p.a. and higher posts.—Write, giving full details of training, experience in trade, makes specialized in, etc., and copies of references only; Security Bond required, Box 3063. [2436]

A. C. COSSOR require Development Engineers for radar communications, television and instruments projects in development division. Eng. degree or equiv. pro. qual.; exp. in developing to Government and other specifications and directing work of development engineers, sen. positions.—Write, stating age, qualifications, exp. and salary required, to Personnel Manager, 22, Highbury Grove, N.5. [2442]

SENIOR and junior engineers required for responsible work in radio and television laboratories, applicants for senior position should be able to undertake development work with minimum supervision; excellent conditions and salary available for applicants who are accepted.—Apply in first case to Personnel Manager (Dep't. R.D.) McMichael Radio Ltd., Wexham Rd., Slough. Applicants must be of British nationality. [2021]

A FIRST-CLASS man is required for the inspection and test of industrial electronic apparatus; he should preferably have served an apprenticeship in the electrical industry, be in possession of a H.N.C. and be aged about 30 to 35; good prospects are open to the right man.—Write, giving full details of age, experience and salary required, to Phillips Balham Works Ltd., 45, Nightingale Lane, Balham, S.W.12. [2406]

LIVINGSTON LABORATORIES, Ltd.—We have vacancies for competent personnel in our calibration and test department; all types of electronic instruments pass through our hands, and we aim at the highest standards; applicants interested in such work, in a small specialised organisation with ideals, are invited to approach—Mr. Urry, Livingston Laboratories, Ltd., Retcar St., London, N.19. Tel. Archway 6251, for an appointment. [2422]

A FIRST-CLASS opportunity exists in the London area for a development engineer familiar with the design and production of miniature or telephone type relays or similar electro magnetic devices. Excellent laboratory facilities are available and the successful candidate will be required to initiate new development projects and carry them through to production. The initial salary will be in accordance with qualifications, and generous advancement is possible for a man of initiative.—Write quoting ref.: CB/WW, and send details of qualifications and experience to Box 2714. [2350]

QUARTZ CRYSTAL UNITS



Type
B7

The type B7 unit is mounted in the standard B7G valve envelope and is hermetically sealed and fully evacuated.

Available for the frequency ranges from 100 kc/s. to 500 kc/s. and from 3 Mc/s. to 16 Mc/s. Gold electrodes applied by cathodic sputtering give permanence of calibration. Normal adjustment accuracy 0.01% Max. adjustment accuracy 0.003%

Early delivery can be given of most frequencies, and we will be pleased to quote for your specific requirements.

THE QUARTZ CRYSTAL Co. Ltd.
63-71 Kingston Road,
NEW MALDEN, SURREY

Telephone: MALden 0334

Cables, etc.: QUARTZCO NEWMALDEN



**HIGH CLASS
TAPE RECORDING EQUIPMENT**
HEADS, DECKS, TAPE, ETC.
Send for lists
BRADMATIC LTD.
STATION ROAD, ASTON, BIRMINGHAM 6
Telephone: East 2881-2

PLASTIC RECORDING 20'6 TAPE—1,200 ft. SPOOL POST FREE

Surplus to world famous manufacturer's requirements. Empty spools (plastic) 2/6
RONALD WILSON LTD., FAREHAM, HANTS.



Accurate tests
High, Low and Grid
Bias Batteries.
Write for leaflet 30M.



'Radiospares' Quality Parts

The
**Service Engineer's
First Choice**

POTENTIOMETERS



Wire-wound and Composition types. Single, Ganged, Tandem Units. Characteristics: linear, log., semi-log., non-inductive, etc. Full details on request.

RELIANCE

RELIANCE MNFG., CO. (SOUTHWARK), LTD.
SUTHERLAND ROAD, HIGHAM HILL,
WALTHAMSTOW, E. 17.
Telephone: Larkwood 3245

OPPORTUNITIES IN RADIO

Get this FREE Book!

'ENGINEERING OPPORTUNITIES' reveals how you can become technically qualified at home for a highly paid key-appointment in the vast Radio and Television Industry. In 144 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of TELEVISION and RADIO, A.M. Brit. I.R.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency and General Wireless Courses.

We definitely Guarantee

"NO PASS—NO FEE"

If you're earning less than £15 a week this enlightening book is for you. Write for your copy today. It will be sent FREE and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
38B COLLEGE HOUSE,
29-31, WRIGHT'S LANE,
LONDON, W.8.



SITUATIONS VACANT

A. C. COSSOR, Ltd., have vacancy in Development Division for mechanical designer; the requirement is for a professionally qualified man who has had considerable exp. in design of light electrical engineering equip. to Government specifications and who is capable of directing a team of draughtsmen working on such equip., appt. sen. and salary and conditions of work as such.—Write, stating age, quals. and exp. to Personnel Manager, 22, Highbury Grove, N.5. [2441]

BRITISH Relay Wireless and Television Group of Companies have vacancies for television and radio engineers in grades offering wage rates between £7/15 and £10 per week. Applicants should consider their appointment a stepping-stone in a career offering excellent opportunities. Superannuation scheme and active sports and social club. Apply in writing, stating age, experience and qualifications, to British Relay Wireless and Television, Ltd., 397, Albany Rd., S.E.5. [2312]

McMICHAEL RADIO, Ltd., require senior and junior engineers in their equipment division laboratory at Slough; training and experience in the field of applied electronics (including communications) and experience of working with Government Departments are the chief qualifications required.—Write, stating age and full details of training, qualifications and experience, to the Chief Engineer, Equipment Division, McMichael Radio, Ltd., Slough, Bucks [0198]

TEST Engineers required for specification testing and calibration of a wide variety of medium and high frequency communication transmitters (100W to 10KW) receivers and L.F. amplifiers, etc., also for industrial R.F. heaters (250W to 30KW). Permanent posts with salary according to qualifications and experience; 5-day week; canteen facilities; pension scheme.—Write full details to Redifon, Ltd. (Dept. T), Broomhill Rd., Wandsworth, S.W.18. [2354]

TECHNICIANS, Grade I (Radio) required by East African Posts and Telecoms Administration on probation for pensionable employment; salary, etc., in scale £742 rising to £1,134 a year; outfit allowance £30; free passages; liberal leave on full salary; normal four 4 years; candidates should possess a thorough practical knowledge of the working and maintenance of radio transmitting and receiving equipment; G.P.O. staff should apply through departmental channels.

WRITE to the Crown Agents, 4, Millbank, London, S.W.1; state age, name in block letters, full qualifications and experience and quote: M2C/32424/NF. [2356]

TECHNICAL Correspondent to deal with technical and sales letters and follow up enquiries; detailed information on technical matters will be given by Laboratory, but applicants must have wide enough knowledge to understand general radio technical queries; must be able to write good letters; first-class English essential; write full details experience, qualifications, age and salary required.—Goodmans Industries, Limited, Axiom Works, Wembley. [2427]

HIVAC, Ltd., manufacturers of specialised thermionic and electronic devices offer interesting posts for scientists, engineers and technicians in their expanding organization on research and development projects in valves, cold cathode tubes and transistors; previous experience in these fields, although an advantage, is not essential, but sound education and an active and enquiring mind are; encouragement will be given, wherever possible, to the publication of original work.

The Company is a member of a major communications group and the posts, which are available for both senior and junior applicants, are pensionable and offer scope for advancement; there is a 5-day working week.

APPLICATIONS in writing, which will be treated in strict confidence, stating age, education, qualifications and salary expected, should be addressed to—The Engineer-in-Chief, HIVAC, Ltd., Greenhill Crescent, Harrow, Middlesex. [2452]

A JUNIOR engineer is required having a laboratory background and preferably a degree in physics, who should be interested in the application of resins and similar thermal moulding materials for component protection, etc.; the work is of exceptional interest in connection with guided missile projects; good salary and bonus, pension scheme.—Full details should be sent to the Assistant Manager, Dept. WW, The Fairey Aviation Co., Ltd., Research and Armament Development Division, Heston Aerodrome, Hounslow, Middx. [2413]

ELECTRONIC engineers with several years research or development experience are invited to apply for posts with a well-established company engaged primarily on the development of precision electronic laboratory instruments; applicants should preferably possess an honour degree or equivalent qualifications in physics or light electrical engineering, although this is not essential; a considerable practical experience is equally acceptable; the appointments are of a permanent nature for engineers able to undertake the responsibility for the development of new projects to the prototype stage, and they offer scope for the exercise of individual initiative; furthermore, the work covers a wide range of electronic instruments and similar devices; salaries are commensurate with qualifications and experience; applications should be made in writing, stating full details, to—Chief Engineer, Furze Hill Laboratories, Ltd., Boreham Wood, Herts. [0050]

Samson's Surplus Stores

Amazing offer! First time on Surplus Market. **MINIATURE ACCUMULATORS** made by Willard Co., 36 v. 0.2 amp. Size 3 1/2 x 1 1/2 x 1/2. Weight 5 1/2 oz. 5/-, P.P. 6d. 6 v. 1.2 amp. Size 3 3/4 x 1 1/2 x 1/2. Weight 4 1/2 oz. 7/6, P.P. 6d.; or set of three 36 v. and one 6v. in sealed container, £1, P.P. 1/3. Brand new and uncharged. Easily filled with hypodermic syringe.

BRAND NEW EX-ARMY HYPODERMIC SYRINGES. Complete with 1 needle. 4/9, P.P. 6d. Extra needles 6d. ea.

L.T. SUPPLY UNITS. Brand new AM type 8B Ref. 5P/2399 input tapped 200-250 v. A.C. Output 36 v. 50 amp. at 35 deg. C. Built-in metal cabinet size 3ft. 10in. x 1ft. 6in. x 1ft. 9in., complete with starter switch. £25.

L.T. SUPPLY UNITS. S.T.C. Type 13. Input 100-250 v. A.C. Output tapped 12-24 v. D.C., 3 amps. continuous rating. Completely shrouded in metal case with Fuses, Switch and O.P. Sockets. £4/10/-, carr. 5/-.

S.T.C. BATTERY CHARGERS. A.C. input, 200-250 v. Output 60 v. 10 amps. Incorporating selenium rectifier, ammeter, fuses control switching. Built-in grey metal cases measuring 1ft. 10in. x 1ft. 3in. x 10 1/2in. Supplied brand new at a fraction of the maker's price. £22/10/-.

HEAYBERD BATTERY CHARGERS. Input 200-250 v. output 12 v. 30 amps. Complete with fine and coarse switching fuse and 0-40 ammeter. £22/10/-.

LOOK!! CO-AXIAL CABLE. Lowest price ever. Super quality, ex-Govt. 80 ohms. 50 yds. 32/6; 100 yds. £3; 1,000 yds. £18/10/-.

SPECIAL OFFER OF A.M. H.T. BATTERIES. Layer type. Packed in tropical packing, tested before dispatch and guaranteed to be up to standard. 67 1/2 v. (civilian type B101), 60 v. x 1.5 v., 72 v. x 1.5 v. All at 5/- each. P.P. 9d.

R103A 6-VALVE RECEIVERS. With built-in power pack for 100-250 v. A.C. or 6 volts D.C. Freq. range 1.7-7.5 Mc/s. Output is matched for L.R. phones. Complete with instruction manual. £8/17/6.

24 V. HEAVY DUTY RELAY. A.M. type B, mounted on base size 8in. x 6in. with glass top cover. 15/-, P.P. 2/-.

TELEPHONE EQUIPMENT. Admiralty sound powered head and chest set, comprising microphone on swivel base and headphones. 17/6, P.P. 1/6. Microphone separate. 12/6, P.P. 1/6. Field Telephones, type D5, complete with single headphone hand set and batteries built in strong metal containers suitable for farms, building sites, garages, etc. 49/6, carr. 2/6. Telephone Cable. Single D3, 1 mile drums. 55/-, carr. 5/-.

OFFICE INTER-COM SETS. Special offer of manufacturer's surplus includes master and 2 extensions, built in highly polished wood cabinets operates from 200-250 A.C. Valve line up: 1 UF42, 1 UL41 and metal rectifier. Brand new in maker's cartons. £8/19/6. Originally sold at 16 gns.

All the above items are by famous manufacturers and are guaranteed to be in perfect condition.

169/171 Edgware Road

London, W.2. Tel.: PAD 7851

125 Tottenham Court Road, W.1
Tel.: EUS 4982

All orders and enquiries to our Edgware Road branch, please. This is open all day Saturday.

LONDON CENTRAL RADIO STORES

10-WATT AMPLIFIER, fitted P.U. and microphone terminals. A.C. 220/250 v. in metal cabinet, 13" x 6" x 8in. £8/10/- Carr., etc., 10/-.

SELENIUM FULL-WAVE RECTIFIERS. 80 v. 20 a. Approx. 11" x 6" x 6in. Used, but perfect. Weight 14lb. £3/10/-.

UNISELECTOR SWITCHES. Have many applications, including automatic tuning circuit selection, etc. Operates on 250-50 v. Full Wipers, 3-bank, 19/6. Half Wipers, 6-bank, 27/6. Plus 1/6 P. & P.

GROOVE LOCATING UNITS enabling operator to preselect any point on 10, 12 or 16in. discs for playback purposes.

Consists of substantial machined casting with adjustable counterpoise pick-up arm fitted with high-fidelity pick-up and instantaneous calibrated groove selector with micrometer adjustment and "velvet touch" lever for dropping pick-up. £2/10/-, carr. paid.

ELECTRO MAGNETIC COUNTERS. Ex-G.P.O. every one perfect, electro-magnetic, 500 ohm coil, counting to 9,999, operated from 25-v.-50 v. D.C., 4 1/2in. long x 1 1/2 x 1 1/2in., many industrial and domestic uses. 15/-, P. & P. 9d.

2-VOLT ACCUMULATORS, new, 16 AH in ebonite cases, size 7in. x 4in. x 1 1/2in., approx. 4lb. weight. 6/- plus 1/6 carr. and packing.

See previous issues for other bargains.

23 LISLE ST. (GERARD) LONDON, W.C.2

Closed Thursday 1 p.m. Open all day Saturday

ARIEL SOUND

Professional Recording Engineers.

Public Address Equipment.

Electronic Design, Manufacture and Repair.

(Please refer to Repairs and Services Section for details of some of our services.)

57 LANCASTER MEWS, LONDON, W.2
Telephone: Paddington 5092.

RADIO & TELEVISION COMPONENTS

WE OPERATE A PROMPT & EFFICIENT MAIL ORDER SERVICE.


"VIEW MASTER" & "TELE-KING" specialists

Easy terms available.

JAMES H. MARTIN & CO.,
FINSTHWAITE, NEWBY BRIDGE,
ULVERSTON, LANCs.

ODDIE FASTENERS

PAT. 507249

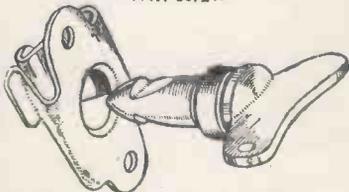

THIS FASTENER WITH ENDLESS APPLICATIONS—SIMPLE—POSITIVE SELF-LOCKING. MADE IN A VARIETY OF TYPES AND SIZES.

SPECIAL FASTENERS TO SUIT CUSTOMERS' REQUIREMENTS.

WIDELY USED IN THE RADIO INDUSTRY.

Illustrated brochures and other information will be gladly sent on request.
DEPT "W.W."

Oddie, Bradbury & Cull Ltd., Southampton
Tel.: 55883. Cables: Fasteners, Southampton

SITUATIONS VACANT

ASSISTANT to chief mechanical engineer. A normal expansion requires appointment in S.E. London of designer (over 32) with creative ideas, considerable experience mass production light engineering, domestic equipment or radio/television range, degree or R.N.C. preferred, but right experience, initiative and ability might well be acceptable substitutes; first-class permanent and progressive opening with equivalent salary prospects.—Write in confidence Box D C.262, A.K. Adv., 212a, Shaftesbury Ave., London, W.C.2. [2432]

ELECTRONIC Engineers are invited to apply for senior posts of exceptional interest and opportunity with Decca Radar, Ltd., to work in their laboratories on an extensive and expanding programme of link and radar development. Applicants must have had responsible development experience in the electronic field. Posts are permanent and pensionable. Good starting salaries and considerable prospects of advancement.—Write, quoting Ref. RLA/6, The Research Director, Decca Radar, Ltd., Research Laboratories, 2, Tolworth Rise, Surbiton, Surrey. [2456]

A. C. COSSOR Ltd., have vacancy for sales engineer for work in the communications field; applicants should have had considerable exp. in and knowledge of the tech. and operational aspects of H.F. and V.H.F.; communications equip. sent with prospectus, and successful applicant will report directly to commercial manager and be expected to be capable of making tech. market appreciations and co-operating with Communications Development engs.—Write, stating age, quals. and exp., to Personnel Manager, 22, Highbury Grove, N.5. [2443]

THE GENERAL ELECTRIC Co., Ltd., Brown's Lane, Coventry, requires senior and junior electronic development engineers for work on guided weapons and like projects, particularly in the field of microwave and pulse applications; mechanical development engineers, designer draughtsmen and draughtsmen, preferably with experience of radar-type equipment, also required for the above projects; salary according to age, qualifications and experience.—Apply by letter, stating age and experience, to the Personnel Manager (ref. R.G.). [0259]

SENIOR Television Development Engineer required by well-known radio and television manufacturer in London area; applicants must have a wide experience in development for mass production of modern commercial radio and television receivers; a good salary will be paid to a person possessing drive and organizing ability and capable of carrying through projects from development to production stages, under the supervision of the chief engineer; kindly state full particulars of technical education and experience to—Box 2675. [2351]

ENGINEERS with radio and radar installation and maintenance experience are required for interesting work which will involve working in various parts of Great Britain; applications will be welcomed particularly from ex-service men and those who possess experience in this field; these positions offer good prospects in a large flourishing company which operates a generous pension scheme.—Applications, which will be treated in confidence, should be addressed to Box WW 873, L. 12, 110, St. Martin's Lane, W.C.2. [2370]

TELEVISION trouble shooters are offered an opportunity to train as maintenance and development engineers of electronic test gear with a large manufacturer in East London; the posts, which are permanent and pensionable, will provide experience on all types of test gear connected with radio, television and radar equipment and there are exceptional prospects of promotion; the company works a 5-day, 40-hour week and has excellent canteen and sports facilities.—Write, giving full particulars of previous experience, to Box 2842. [2373]

JUNIOR engineer required for long-term developments in the communication equipment and general electronics development field; applicants should be between the ages of 21 and 26 and should possess a degree or have had at least three years' laboratory work in the domestic radio or communication fields; these vacancies possess excellent opportunities for keen and ambitious young men; a generous salary will be paid to the selected applicants.—Please reply, giving details of qualifications and experience, to Box 3135. [2449]

A LARGE and well-established electronic engineering company in the eastern suburbs of London invite applications from graduate electronic development engineers, age 28-33, for microwave and electronic development; salary range £700-£1,000 per annum according to experience; the vacancies present attractive opportunities to men with good experience and qualifications; company superannuation and insurance schemes in operation; excellent conditions; please reply, in strictest confidence, stating qualifications and experience to—Box 3250. [2450]

MINISTRY OF TRANSPORT AND CIVIL AVIATION—Radio technicians (men only) required at aerodromes and radio stations in various parts of U.K.; special training courses for keen technicians with basic quals.; interesting work in progress providing electronic aids to navigation; prospect of permanent pensionable posts; rates of pay (London) from £335 p.a. at age 19, to £445 at 25, rising, subject to qualifying test to £540; rates slightly lower for provinces; candidates age 19 or over, with practical experience in maintenance of radio or radar equipment should apply to any Employment Exchange, quoting Order No. Westminster 6627. [2417]

FERGUSON RADIO CORPORATION LTD.

offers exceptional opportunities to DRAUGHTSMEN wishing to make their career in the world of electronics, television and radio. Candidates preferably experienced in the Radio and Television industries, must have knowledge of mass production methods and workshop practice. Familiarity with Ministry requirements an advantage. Good Salaries; Pension scheme. Well equipped Drawing Offices and good working conditions.

Apply: Employment Manager,
Ferguson Radio Corporation
Ltd., Great Cambridge Road,
Enfield, Middx.

MALVYN ENGINEERING WORKS

Precision Engineers

Manufacturers of: Chassis, Small Pressings, Machined Components, Wiring and Mechanical Assemblies to specification.

Single and Production Quantities. Enquiries Invited.

100 PARK ROAD, WARE, HERTS.

Telephone: Ware 465

GRAMPIAN
for
Loudspeakers

GRAMPIAN REPRODUCERS LTD
9 Hanworth Trading Estate, Feltham, Mdx. Tel. Feltham 2657

TR1154/55 RECTIFIERS

Input:—200/250v., 50~S.P. Output:—6.3v., 13A.—220v., 110m.a.—1200v., 200ma.

NEW CONDITION—TESTED—GUARANTEED

£17-10-0 per set. Carriage extra.

A. J. WHITMORE (Aeradio) LTD.
Croydon Airport. Tel: Croydon 5701, 4583, 7744
Surrey. Grams: Aeradio, Croydon.



METERS



FOR WORKSHOP AND LABORATORY

Electrical test instruments repaired and calibrated, all types and makes, ammeters, voltmeters, ohmmeters, DC/AC multirange meters, etc., meters converted and rescaled to specification. Quick service for industry


**THE ELECTRICAL INSTRUMENT
REPAIR SERVICE**

329 Kilburn Lane, London, W.9. Tel. LAD 4168

DIRECT FROM THE MANUFACTURER

Dulci Radio/Radiogram Chassis
A/C 100-120 & 200-250 VOLTS.

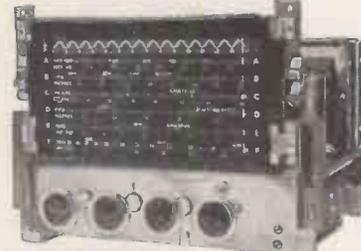All chassis 11 1/2 in. x 7 in. x 8 1/2 in. high. Latest type valves 6BE6, 6BA6, 6AT6, 6BV6, 6X4. Flywheel tuning. Negative feedback over entire audio section. Engraved knobs. 3 Tone position for Radio and Gram.




- FULLY GUARANTEED**
- Model B3, Long, Med., Short (5 Valves) **£12 . 12 . 0**
 - B3 Plus Push Pull Stage (6 Valves) **£15 . 15 . 0**
 - B3 Double Feature P/Pull & RF Stage (7 Valves) **£18 . 18 . 0**
 - Model B6 Six Wavebands Med. L. 4 Short (Bd-Spread) **£15 . 15 . 0**
 - B6 Plus Push Pull Stage (6 Valves) **£18 . 18 . 0**
 - B6 Double Feature P/Pull & RF Stage (7 Valves) **£23 . 2 . 0**

ALL PRICES TAX PAID

Escutcheon for 9 in. x 5 in. dial, 4/9 extra. Matching speakers P.M. type 3 ohms 8 in or 10 in available. Money back guarantee. Free particulars from the Manufacturers.

THE DULCI CO. LTD.

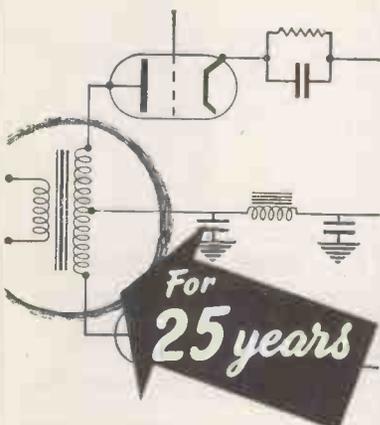97 VILLIERS ROAD, LONDON, N.W.2
Telephone: Willesden 7778



Enthusiastic amateur and experienced research workers send testimonials of Savage accuracy and reliability. Here is one of many.

'A transformer and 2 chokes of your make purchased about 1932 are still doing yeoman service. T. F. MacD., London'



SAVAGE TRANSFORMERS LTD.
Nursted Road, Devizes, Wilts.
Telephone: Devizes 536.

SITUATIONS VACANT
JOSEPH LUCAS (GAS TURBINE EQUIPMENT), Ltd., invite applications for electronic engineers; some knowledge of servo mechanisms would be an advantage; should have university degree; these appointments are desirable and offer good prospects to individuals with initiative and technical ability; salary will be in accordance with experience and qualifications.—Details of experience and qualifications should be sent to Personnel Manager, Joseph Lucas (Gas Turbine Equipment), Ltd., Shaftmoor Lane, Hall Green, Birmingham. [2367]

APLICATIONS are invited from young electronic engineers for a position involving the development of VHF equipment and associated units; prospective applicants should be capable of working from circuit diagrams and specifications with a minimum of supervision and also be capable of original design of the most simple equipment, such as monitors, etc.; previous experience of this type of work or in allied fields would be an advantage; good prospects are open to the right man; write stating age and salary required to—Airtech Ltd., Aylesbury and Thame Airports, Haddenham, Bucks. [2345]

DRAUGHTSMEN required for railway signalling and electrical drawing office in Glasgow, also outdoor work; preference given to applicants holding Ordinary National Certificate in mechanical or electrical engineering; salary range for starting grade up to maximum of £63/15 p. a. £6 years; good prospects for promotion; free and reduced rate travel concessions; staff pension scheme and five-day week; canteen facilities available.—Apply by letter giving details of age, experience, etc., to British Railway Signalling and Telecommunications Engineer's Department, 302, Buchanan St., Glasgow. [2366]

SERVICE engineer required as engineer and manager for a small company in Rugby specializing in the overhaul of domestic television and radio receivers; 44 hours, 5-day week; staff position; the directors wish to engage an engineer with the necessary technical qualifications and experience and capable of controlling a staff of assistant engineers engaged on fault finding, repair and overhaul of radio and television receivers; the applicant must be a hard worker, keen to take full control and expand the business and apply to the position of director which would be available later; salary £750 per annum; replies will be treated in strict confidence.—Box 3062. [2435]

AVACANCY occurs for a Development Engineer in a design group concerned with a wide range of small transformers and inductors of types used in radio equipment and electrical appliances. Preference will be given to applicants having experience of this class of work, but young engineers will be considered, and if successful will have the opportunity of gaining practical knowledge of design problems met in fulfilling commercial and military specifications. An attractive salary is offered together with good future prospects. The company's extensive laboratory and production facilities are situated in the London area.—Please reply, quoting ref.: WG/WV, giving details of qualifications and experience to Box 2713. [2349]

A SENIOR electronic engineer is required who will be directly responsible to head of electronics laboratory for one or more groups of development engineers engaged on guided missile projects; applicants should be over 30 and have considerable experience of at least one aspect of radar, communication, pulse, video or micro-wave work, together with a degree or equivalent qualification; commencing salary will be in the region of £2000 per annum according to experience and qualifications; a pension scheme incorporating life insurance is in operation, and the company is within 15 miles of London. Full details should be sent in strict confidence to Box MB.8142, A.K. Advg., 212a, Shaftesbury Ave, London, W.C.2. [2404]

MINISTRY OF SUPPLY requires senior examiners at or near Birmingham, Bristol, Glasgow, London, Manchester, Sheffield, to supervise inspection at works engaged in (a) aircraft and aero engines, (b) radio and radar, (c) instruments and electrical equipment or (d) materials (metallic and non-metallic); qualifications: British of British parents, recognised engineering apprenticeship or equivalent in radio/radar; appropriate experience, O.M.C. or equivalent desirable; salary: within £592 (age 30) -£733; not established but opportunities to compete for establishment may arise.—Application forms from E.A.994, London Appointments Officer, Ministry of Labour and National Service, 1-6, Tavistock Square, London, W.C.1. [2418]

CABLE AND WIRELESS, LTD., invite applications from telecommunications engineers who are interested in a career in this company's overseas service ashore; applicants must have had practical experience of maintenance and operation of wireless telegraph apparatus and possess C. & G. Radio II Certificate or equivalent; desirable age limit 29; basic commencing salary £324 (age 22) to £456 (age 29) per annum; free accommodation or allowance in lieu; foreign service and expatriate allowances (up to £240 and £550 per annum respectively) additional; tax paid; permanent and pensionable positions for suitable candidates.—Apply in writing, giving experience and qualifications, to Managing Director, Cable and Wireless Ltd., Electra House, Victoria Embankment, London, W.C.2. [0008]

GALPIN'S

ELECTRICAL STORES

408 HIGH STREET, LEWISHAM, S.E.13.

Tel.: Lee Green 0309. Nr. Lewisham Hospital.

TERMS: CASH WITH ORDER. NO C.O.D.

All goods sent on 7 days' approval against cash.

EARLY CLOSING DAY THURSDAY.

D.C. MOTORS, 230 volts, 3 h.p., 3,000 r.p.m., in good condition £3/5/- each; ditto Fan Motors, 230 volts D.C., 20/- each; 110 volts D.C., 17/6 each.

METAL RECTIFIERS, suitable for 6/12/24 volts at 10 amps charging with the correct transformer, complete with TX 97/6 each, or Rectifier only 35/- each.

6 or 12 VOLT RECTIFIERS at 4 amps output, complete with suitable transformer, 200/230 volts input, 45/- each, post 1/6.

12/24 VOLT RECTIFIERS at 4 amps, with suitable Mains Transformer, 200/230 volts input, 55/- each.

MAINS TRANSFORMERS (NEW), input 200/250 volts in steps of 10 volts, output 350/0/350 volts, 180 m/amps, 4 volts 4 amps, 5 volts 3 amps, 6.3 volts 4 amps, 45/- each, post 1/6; another 350/0/350 volts 180 m/amps, 6.3 volts 8 amps, 0/4/5 volts 4 amps, 45/- each, post 1/6; another 500/0/500 volts 150 amps, 4 volts 4 amps C.T., 6.3 volts 4 amps, C.T., 5 volts 3 amps, 47/6 each, post 1/6; another 425/0/425 volts 160 m/amps, 6.3 volts 4 amps, C.T. twice 5 volts 3 amps, 47/6 each, post 1/6.

MAINS TRANSFORMERS (NEW), suitable for spot welding, input 200/250 volts, in steps of 10 volts, output suitably tapped for a combination of either 2/4/6/8/10 or 12 volts 50/70 amps, 95/- each, carr. 7/6.

MAINS TRANSFORMERS, 200/250 volts input, output a combination of 6, 12, 18, 24, 30 and 36 volts at 6 amps, 45/- each, post 1/6.

MAINS TRANSFORMERS, input 180/250 volts, output 435/0/435 volts, 250 m/amps, 6.3 volts 10 amps 6.3 volts 8 amps, 6.3 volts 8 amps, 5 volts 6 amps, 65/- each.

MAINS TRANSFORMERS, 200-250 volts input, output 400/0/400 volts, 280 m/amps, 6.3 v. 8 a., 2 v. 3 a., 5 v. 3 a., 4 v. 2 a., 4 v. 2 a., the last two heaters insulated at 8,000 volts, 85/- each; another 200/230 volts input, output tapped 0, 9, 18 volts at 4 amps, 25/- each, post 1/-.

MAINS TRANSFORMERS, input 200/250 volts, output 45/50 volts, 70 amps, suitable for arc welding, £15 each; another 70 volts, 50 amps, £15 each.

MAINS TRANSFORMERS (NEW), 200/250 volts input in steps of 10 volts, output 0, 6, 12, 24 volts 6 amps, 42/6 each, post 1/6. Another, as above but 10-12 amps, 55/- each, post 1/6; another as above but 25/30 amps, 75/- each, carriage 3/6; another, input as above, output 0/18/30/36 volts 6 amps, 47/6 each, post 1/6.

EX-U.S.A. ROTARY CONVERTERS, 12 volts D.C. input, outputs 500 volts 50 m/a., 275 v. 100 m/a. Complete with smoothing, 22/6 each, carriage 2/6, as new.

EX-NAVAL ROTARY CONVERTERS, 110 v. D.C. input, 230 volts A.C. 50 Cy, 1 ph 250 watts output. Weight approx. 100lbs., £12/10/-, c/forward.

EX-W.D. U.S.A. HAND GENERATORS, less winding handle, output 425 volts at 110 m/a., at 6.3 v., 2 1/2 amps, complete with smoothing, 30/- each, carriage 2/6.

ELECTRIC LIGHT CHECK METERS, useful for subletting, garages, etc., all for 200/250 volts A.C. mains, 5 amp load, 19/- each; 10 amps, 22/6; 20 amps, 27/-; 25 amps, 32/6; 40 amps, 38/6; 50 amps, 46/6; and 100 amps, 57/6 each, all carriage paid.

METERS. Moving Coil, 0 to 14 amps, 18/6 each. Ditto, Moving Iron, suitable for A.C. 0 to 30 amps, 25/- each. Another moving coil, 100 to 250 amps D.C., 35/- each, all 4 in. scale.

1,000 WATT AUTO WOUND VOLTAGE CHANGER TRANSFORMER tapped 0/110/200/230/250 volts, £5/15/- each, carriage 4/6.

3 KILOWATTS DOUBLE-WOUND VOLTAGE CHANGER TRANSFORMERS, 110/130 volts or vice-versa, as new, weight approx. 100lbs., £12/10/- each, carriage forward.

WELDER TRANSFORMER, 200/250 v. input, output 0/60/80 volts, 800 amps. Complete, on trolley, £32/10/-, c/ftwd.

SITUATIONS VACANT

RADIO Maintenance Engineer required for staff post in Edinburgh to take charge of small radio workshop on airfield; in addition to maintaining standard air and ground radio and radar equipments (civil and military) applicant will be required to assist in field trials of new systems; applicants must be in possession of M.C.A. radio licence, minimum "A," preference "A" and "B," good prospects; staff pension scheme; apply, quoting Ref. RME/TID and giving full details of training, qualifications and experience to The Personnel Officer, Ferranti, Ltd., Ferry Rd., Edinburgh, 5. [2389]

ELECTRONIC Engineer to work within our trials division at Edinburgh; the nature of the work involves conducting trials and evaluating the performance of fire control, navigational and landing systems under development; applicants should possess a Physics degree or considerable recent practical experience in this field; good opportunity in expanding department; staff pension scheme; apply, quoting Ref. EE/TID and giving full details of qualifications and experience to The Personnel Officer, Ferranti, Ltd., Ferry Rd., Edinburgh, 5. [2390]

TECHNICIANS required for laboratory and inspection duties in connection with design of quartz and synthetic crystals and associated circuits; applicants should be between 24 and 35 years of age and preferably have had some industrial or services experience in radio techniques; salary £500 to £700 per annum dependent upon qualifications and experience; the position is tenable in South West Lancashire and is on the established staff status with contributory pension fund and usual staff conditions. Applicants are invited to write to Box 530, Dorland Avenue, Ltd., 18-20, Regent St., London, S.W.1, giving full particulars of their qualifications, experience and age. [2338]

FERRANTI, Ltd., Edinburgh, have a vacancy in their Applications Laboratory for an Engineer-Physicist for interesting development work with a control project opening up a new field and involving digital computers, data recording and servo-mechanisms; a degree or equivalent in electrical engineering or physics is essential, and experience in some, or all, of these fields is desirable; the appointment is permanent and offers excellent prospects in an expanding organization; a salary commensurate with the qualifications required for this position will be paid; good conditions; staff pension scheme; apply, giving full details of training, qualifications and experience and quoting Ref. EP/AL, to The Personnel Officer, Ferranti, Ltd., Ferry Rd., Edinburgh, 5. [2388]

AIR MINISTRY requires Experimental Glass Officers at establishment near Marlow, Bucks. Duties concern installation design of static and mobile radar and radio systems used by R.A.F. Work of engineering rather than laboratory type, covering wide range of application of electronic engineering to meet operational needs of R.A.F. with which very close contact is maintained. Membership of Officers' Mess open to accepted candidates offering all forms of recreation in congenial surroundings. Qualifications:—At least Higher School Cert. (Science) or its equivalent although higher qualifications in Physics or Electrical Engineering may be an advantage. Salaries within ranges:—Experimental Officer (min. age 26) £649-£799, or Assistant Experimental Officer £264 (at age 18) to £576. Appointments unrestricted. Application forms from M.L.N.S., Technical and Scientific Register (K), 26, King St., London, S.W.1, quoting D 8/54. Closing date 9 March, 1954. [2394]

We have a large stock of

HIGH STABILITY RESISTORS

Trade enquiries invited: Marris & Cartin Ltd. 42 Brook Street, London, W.1. GRO. 5571

PRE-SET CONTROL LOCK

Designed to lock the spindles of pre-set potentiometers or trimmers without rotational or lateral displacement of shaft.




Will accept wide range of panel thicknesses.

TYPE O (right)

TYPE P (left)

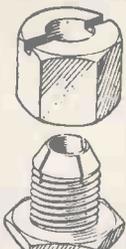Very attractive appearance for panel mounting.



Send for leaflet 12

SUTTON COLDFIELD ELECTRICAL ENGINEERS
6 High Street WALSALL, phone: 2537

SITUATIONS VACANT

DEVELOPMENT Engineer wanted for work on radio and TV. Good working knowledge of electronic circuitry and chassis layout essential. Some experience of mass production an advantage. Permanent and progressive position with good working conditions.—Please write in the first instance to the Personnel Manager, Mains Radio Gramophones, Ltd., 359, Manchester Rd., Bradford. [2397]

TEST assistant with some telecommunication knowledge required, experience of cable test at audio and carrier frequencies desirable but not essential, candidates studying for H.N.C. or O.N.C. Electrical Engineering or City and Guilds Telecommunications Course would be preferred, pension scheme, five-day week and all welfare facilities, commencing salary about £500 upwards in accordance with qualifications and experience.—Write details to Staff Officer, The Telegraph Construction & Maintenance Co., Ltd., Telcon Works, Greenwich, S.E.10. [2474]

MINISTRY of Supply, R.A.E., Farnborough, requires electrical engineers or physicists to work on basic problems of generation and distribution of electric power in aircraft and of electro-technology arising from design and development of equipment; interest in advanced electromagnetic circuit techniques or in physical properties of magnetic materials desirable; aptitude for experimental work essential; minimum qualification Higher School Cert. (science) or equivalent, but further training to degree or H.N.C. standard in physics or elec. eng. may be an advantage; salaries within ranges: experimental officer (min. age 26) £649-£799; assistant experimental officer, £264 (age 18)-£576; women somewhat less; appointments unestablished.—Application forms from M.L.N.S., Technical and Scientific Register (K), 26, King St., London, S.W.1, quoting A31/54A. [2470]

SITUATIONS WANTED

TECHNICAL publicity engineer, A.M.Brit.I.R.E., seeks commissions.—ARB, 13, Gainsford Gdns., Manchester, 10, Fallswood 3711. [2195]

EX-R.A.F. cpl. wireless fitter desires progressive post. From March, preferably London or South; experienced airborne V.H.F. little experience Marconi S.W.B. type transmitters, S.S.B., freq. shift gear.—Box 2856. [2382]

TECHNICAL TRAINING

CITY & GUILDS (Electrical, etc.) on "No Pass-No Fee" terms; over 95% successes; for full details of modern courses in all branches of Electrical Technology, send for our 144-page handbook—free and post free.—B.I.E.T. (Dept. 388A), 29, Wright's Lane, London, W.8. [0117]

TUITION

NOTHING succeeds like success! What we have done a thousand times we can do again for you—see the B.N.R.S. advt, page 42. [0172]

WIRELESS operating; attendance and postal courses.—Stamp for reply to Manager, The Wireless School, Manor Gdns., London, N.7. [5901]

FULL-TIME courses for P.M.G. Certs. C.G.L.I. Telecommunications, Radar Maintenance Cert. and B.Sc. (Eng.); prospectus free.—Technical College, Hull. [0111]

LEARN it as you do it.—We provide practical equipment combined with instruction in radio, television, etc.—Write for full details to E.M.I. Institutes, Dept. WW47, 43, Grove Park Rd., London, W.4. [0179]

SEE the World as a Radio Officer, short training period, low fees, scholarships, etc. available; boarding and day students; see 2d stamp for prospectus.—Wireless College, Colwyn Bay. [0018]

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, etc. on "no pass-no fee" terms; over 95% successes; for details of exams and courses in all branches of engineering, building, etc. write for 144-page handbook—free—B.I.E.T. (Dept. 387B), 29, Wright's Lane, London, W.8. [0118]



A.I.D.

Approved

TRANSFORMERS

of all types up to 25 KVA for Single or Three Phase operation, Phase Conversion, etc.

MAINS

Output, and Special Purpose Transformers for Radio Equipment; Chokes, etc.

COILS

for Contactors, E.M. Brakes, Air Valves, etc., and Coil Windings for all purposes.

SOLENOIDS

for A.C. and D.C. Operation.

W. F. PARSONAGE & Co., Ltd.
INDUCTA Works • Park Rd. Bloxwich • Walsall
Telephone: BLOX. 66464

TUITION

PERSONAL tuition by A.M.Brit.I.R.E., moderate fees.—Write, "ARB," 13, Gainsford Gdns., Manchester, 10. [2378]

T/V & Radio.—A.M.Brit.I.R.E., City & Guilds, R.T.E.B. Cert., etc. on "no pass—no fee" terms. Over 95% successes. Details of Exams, & Home Training Courses in all branches of radio & T.V. write for 144-page handbook—free.—B.I.E.T. (Dept. 387A), 29, Wright's Lane, London, W.8. [0116]

WIRELESS telegraphy: Merchant Navy offers to youths 16 upwards after qualification lucrative positions as Radio Officers.—Apply British School of Telegraphy, 179, Clapham Rd., S.W.9 (Est. 1906). Recognised by Ministry of Education. Moderate fees. Modern equipment. Also postal courses in theory of Wireless Telegraphy for P.M.G. Certs. and Amateur Transmitting Licence. [0124]

THE Institute of Practical Radio Engineers have available home study courses in every phase of radio and television engineering, specialising in the practical training of apprentices in the retail trade; enrolments limited, fees moderate.—The Syllabus of Instructional Text may be obtained post free from the Secretary, I.P.R.E., Fairfield House, 20, Fairfield Rd., Crouch End, London, N.8. [0088]

OPPORTUNITIES in radio and television servicing.—Full-time theoretical and practical 1-year courses at E.M.I. Institutes in London; job assured on successful completion; next course commences April 21st; early enrolment is advised.—Free brochures giving details of these and other courses from E.M.I. Institutes, Dept. WW36, 10, Pembroke Sq., London, W.2. Tel. Bayswater 531/2. [0180]

FREE! Brochure giving details of home study training in radio, television, and all branches of electronics; courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations; train with the college operated by Britain's largest electronic organization; moderate fees.—Write to E.M.I. Institutes, Postal Division, Dept. WW2z, 43, Grove Park Rd., London, W.4. [0001]

WORK WANTED

POLYSTERENE machined, electro-mechanical and miniature work under design; precise toroidal and resistor winding; pulsed power supplies at 20kV, to order.—Bel Sound Products Co., Genl. Electronic Mfrs., A.I.D. approved contractors, Marlborough Yard, London, Archway, N.19. [0183]

BOOKS, INSTRUCTIONS, ETC.

BOOKLETS "How to Use Ex-Govt. Lenses and Prisms," Nos. 1 and 2, price 2/6 each; ex-Govt. optical lists free, for s.a.e.—H. English, Rayleigh Rd., Hutton, Brentwood, Essex. [0181]

I.P.R.E. technical publications, 5,500 Alignment Peaks for Superheterodynes, 5/9, post free; data for constructing TV aerial strength meter, 7/6; sample copy "The Practical Radio Engineer," quarterly publication of the Institute 2/-; membership and examination data, 1/-.—Sec., I.P.R.E., 20, Fairfield Rd., London, N.8. [0089]

BOOKS WANTED

WANTED.—Back copies of "Wireless Engineer" as follows: 1928, July and August; 1929, December; 1930, July; 1935, Jan., March, April, June; 1936, July, Aug. Nov.; 1937, Jan. Feb., April; 1939, June; 1949, March; state price and condition, or will exchange for any of our many spare copies.—College of Technology, Belfast. [2454]

HI-FIDELITY CABINETS

Individual and trade enquiries to

A. A. CRANSTON

(Cabinet Maker)

20, LORRIMORE BLDGS., OLNEY ROAD, WALWORTH, S.E.17. Telephone: RODney 2349

MORSE CODE Training



COURSES for BEGINNERS and OPERATORS, also a **SPECIAL COURSE** for passing the G.P.O. Morse Test for securing an **AMATEUR'S TRANSMITTING LICENCE.**

Send for the Candler **BOOK OF FACTS**

It gives details of all Courses
Fees are reasonable.
Terms: Cash or Monthly Payments.

THE CANDLER SYSTEM CO.
(55W) 52b ABINGDON RD., KENSINGTON LONDON, W.8

Candler System Co., Denver, Colorado, U.S.A.



for High Stability Resistors
by Welwyn, E.M.I., Dubilier

	5%	2%	1%
1/4 watt.	7 1/2 d	10 1/2 d	1/3
1/2 watt.	9 d	1/-	1/6
1 watt.	10 1/2 d	1/3	1/9
2 watt.	1/-	1/6	2/-

Send for List of over 300.

H. L. SMITH & CO. LTD.
287/289 EDGWARE ROAD, LONDON, W.2
Telephone: Paddington 5891
Hours 9 till 6 (Thursday, 1 o'clock)
Near Edgware Road Stations, Metropolitan & Bakerloo

TER *Symons* synonymous with flexibility TER

FLEXIBLE INSULATING SLEEVING

MATERIAL	DESCRIPTION	OUTSTANDING POINTS
*Terylene	"Terylene" is a synthetic fabric which stands up to high temperatures for prolonged periods.	
*Terylene	Varnished "Terylene" is available in straight or bias cut rolls 36" wide, or as a tape of any width.	Suitable for continuous operation at 150 C.
*Terylene	Raw "Terylene" can also be supplied in full width or as a tape.	Heat set or loom state "Terylene" tapes have heat sealed edges.

*The trade mark "Terylene" is the property of I.C.I. Ltd., and is the name given to a particular Polyester fibre.

For flexible insulating materials of consistent dependability — say Symons.

H. D. Symons & Co. Ltd.
PARK WORKS · KINGSTON HILL · SURREY
TELEPHONE KINGSTON 8591 PTE. EX.

MORLEY TRANSFORMERS

QUALITY P.P.O./P. TRANS. 20w., super Silicorlams
Section low leakage windings, prim. ind. 75H.
leakage ind. 075H, Sec. 2 and 15 ohms Prim. to
indiv. requirements. Shrouded and term., wt. 5 lbs.
3 gas. Ditto 15 w., 2 1/2 gns. L.F. CHOKES, 10H, 65
mA. 4/8 15E. 100 mA., 10/6. 20H. 150 mA., 12/6.
OET Htr. Isolation Trans., 25% sec. boost volt, 2 v.,
10/6; 6.3 v., 10/6. MAINS TRANS. 0-200/250 v.
tapped prim. 350-0-350 v. 80 mA. 5 v. 2 a., 6.3 v.
4 a., etc., from 2 1/2-. 6.3 v. 1 1/2 a. Htr. Trans., 7/6.
Quotations for specials and rewinds. Part P. & P. 1/-
2, PAWSONS RD., W. CROYDON, THO 1665

PERSONAL

The opportunity of a life-time is WAITING for a man with a Good Sound Product and real knowledge of electronic engineering principles and practice.

PRACTICAL ELECTRONIC ENGINEER

We are Manufacturers of High Grade electronic equipment interested in expanding our operations in the diversified field of electronic engineering.

IF YOU HAVE AN IDEA AND YOU ARE ABLE TO ORGANISE AND SET UP AN OPERATION WITH MODERN PLANT IN YOUR OWN SPECIALISED FIELD

We will put a separate division at your disposal, staffed and equipped to your specification. YOU will have complete backing and co-operation and will earn and enjoy the highest remuneration possible coupled with a profit sharing arrangement.

If you have a product you think has possibilities and want the chance to make your skill pay dividends, please write giving your background and details of what you have in mind. STRICTEST CONFIDENCE. Box 2398 c/o "Wireless World"

YOUR METER DAMAGED?



Contractors to The Ministry of Supply
Repairs by skilled craftsmen of all makes and types of Voltmeters, Ammeters, Microammeters, Multirange Test meters, Electrical Thermometers, Recording Instruments, etc. Quick deliveries — for speedy estimate send defective instruments by registered post to—

L. GLASER & CO.

Electrical Instrument Repairers
96-100 ALDERSGATE STREET, E.C.1
(Tel.: MONarch 6822)

CLASSIFIED ADVERTISEMENTS

Use this Form for your Sales and Wants

To "Wireless World" Classified Advertisements Dept., Dorset House, Stamford Street, London, S.E.1.

PLEASE INSERT THE ADVERTISEMENT INDICATED ON FORM BELOW

- RATE: 7/- for TWO LINES, 3/6 every Additional Line. Average six words per line.
- Cheques, etc., payable to Iliffe & Sons Ltd., crossed & Co.
- PRESS DAY, MARCH 2nd FOR APRIL
- NAME AND ADDRESS TO BE INCLUDED IN CHARGE IF USED IN ADVERTISEMENT.
- Box No. if required add 2 words plus 1/-.

Please write in BLOCK LETTERS with ball pen or pencil.

NAME ADDRESS

NUMBER OF INSERTIONS REQUIRED..... REMITTANCE VALUE £ : : ENG.




BEADON GARAGE BEADON ROAD LONDON W 6. Telephone: RIVERSIDE 1124 & 7878

INDEX TO ADVERTISERS

	PAGE		PAGE		PAGE
A.A. Tools	134	Furzehill Laboratories, Ltd.	66	Post Radio Supplies	146
Acoustical Mfg. Co., Ltd.	31	Galpins	145	Premier Radio Co.	61, 62, 63, 64
Acola Products, Ltd.	48	Gardners Radio, Ltd.	20	Proops Bros., Ltd.	122
A.D.S. Relays, Ltd.	128	Garland Bros	123	Pye, W. G. & Co., Ltd.	96
Advance Components, Ltd.	45	Garrard Engineering & Mfg. Co., Ltd.	92	Quality Mart	131
Aerialite, Ltd.	32	The	92	Quartz Crystal Co., Ltd.	142
Aero Research, Ltd.	124	Gee Bros. Radio, Ltd.	137	Radio & Electrical Mart, The	124
Aircraft Radio Industries, Inc.	21	General Electric Co., Ltd.	25	Radio Corporation of America	6
Airmec, Ltd.	88	Glaser, L. & Co.	147	Radio Mail	98
Allen Components, Ltd.	88	Goldring Mfg. Co. (Gt. Britain), Ltd.	50	Radio Resistor Co., Ltd., The	20
Alpha Radio Supply Co., The	119	The Goodmans Industries, Ltd.	33, 51, 67	Radiospares, Ltd.	142
Altham Radio Co.	91	Goodsell, Ltd.	136	Radio Supply Co.	116, 117
Amplex Appliances (Kent), Ltd.	60	Gramophone Co., Ltd., The	81	Radio Traders	123
Amplivox, Ltd.	54	Gramplan Reproducers, Ltd.	144	Record Electrical Co., Ltd., The	64
Anders Electronics, Ltd.	36	Gray, Arthur, Ltd.	132	Redifon, Ltd.	60
Anglo-American Vulcanized Fibre Co., Ltd.	80	Greenlick, O., Ltd.	52	Reliance Mfg. Co. (Southwark), Ltd.	143
Antex	27	Grundig (Gt. Britain), Ltd.	99	Reproducers & Amplifiers, Ltd.	15
Antiference, Ltd.	24	Hall Electric, Ltd.	100	Robinson, F. C., & Partners, Ltd.	30
Appointments Vacant	120, 128, 24	Hanney, L. F.	55	Roding Laboratories	46
Arcoelectric Switches, Ltd.	144	Harris, H.	130	Rogers Developments Co.	94
Ariel Sound	144	Halfield Instruments, Ltd.	82	Rola Celestion Ltd.	96
Armstrong Wireless & Television Co., Ltd.	105, 131	Haves Co., The	136	Rollet, H., & Co., Ltd.	136
Ashdown, H.	36	Henley's, W. T., Telegraph Works Co., Ltd.	130	Rudman, Darlington (Electronics), Ltd.	104
Ashworth, H.	103	Henry's	125	Runbaken Electrical Products	142
Associated Cine Equipments, Ltd.	44	Hivac, Ltd.	95	Salford Electrical Instruments, Ltd.	11
Automatic Coil Winder & Electrical Equip. Co., Ltd., The	23	Holley's Radio Household Electrix, Ltd.	130, 142	Sallis, A. T.	138
Automatic Telephone & Electric Co., Ltd.	2	Hunton, Ltd.	142	Samson Surplus Stores	143
A.W.F. Radio Products	46	H.P. Radio Services, Ltd.	38	Sangamo Weston, Ltd.	80
Baird Television, Ltd.	137	Hygrade Wire Co.	36	Savage Transformers, Ltd.	145
Barker Natural Reproducers	115	Imhof, Alfred, Ltd.	133	Service Radio Spares	126
Bartons (Radio)	114, 115	Institute of Radio Engineers	99	Sherman's Supply Co.	139
B.B.C. Publications	22	International Correspondence School, Ltd.	58	Simmonds, L. E., Ltd.	146
Belling & Lee, Ltd.	73	Kenroy, Ltd.	134	Simon Sound Service, Ltd.	40
Bel Sound Products Co.	138, 134	Keyswich Co., The	58	Sky-Masts	148
Benson, W. A.	68	Koskie, B.	60	Smith, G. W. (Radio), Ltd.	122
Birmingham Sound Reproducers, Ltd.	134	Lasky's Radio	111, 112, 113	Smith, H. L., & Co., Ltd.	147
B.K. Partners, Ltd.	28	Leak, H. J., & Co., Ltd.	85	Smith, W. H., & Son, Ltd.	36
Blickvac	42	Leak Products (Gt. Britain), Ltd.	101	Solator Laboratory Instruments, Ltd.	37
Boulton Paul Aircraft, Ltd.	92	Leavers-Rich Equipment, Ltd.	58	Sound Sales, Ltd.	78
Bradmatic, Ltd.	121	Lewis Radio Co.	132	Southern Radio Supply, Ltd.	136
Britain, Chas (Radio), Ltd.	142	Lockwood & Co.	142	Spencer-West	64
British Communications Corp., Ltd.	49	London Central Radio Stores	53	Spicers, Ltd.	38
British Institute of Engineering Technology	138, 143	Lowther Mfg. Co., Ltd.	58	Standard Telephones & Cables, Ltd.	8, 43, 71, 76
British Insulated Callender's Cables, Ltd.	41	L.R. Supply Company, Ltd.	91	Star Metal Plate Works	140
British National Radio School	42	Lyons Radio, Ltd.	126	Seattite & Porcelain Products, Ltd.	17
British Physical Laboratories	50, 102	Magnegraph Recording Co.	136	Stern Radio, Ltd.	107, 108, 109
British Sarazol, Ltd.	128	Magnetic & Electrical Alloys, Ltd.	28	Stewart Transformers, Ltd.	140
Brookes Crystals, Ltd.	48	Magnetic Coatings, Ltd.	34	Stratton & Co., Ltd.	30
Brown, S. G., Ltd.	44	Mail Order Supply Co.	54, 35	Sugden, A. R., & Co. (Engineers), Ltd.	28
Bulgain, A. F., & Co., Ltd.	Edit. 131	Malvyn Engineering Works	144	Supacolls	130
Bull, J., & Sons	59	Marconi Instruments, Ltd.	57	Supersonic Africa (Pty.), Ltd.	88
Bullers, Ltd.	24	Marine Radio Communications Co.	104	Sutton Coldfield Electrical Engineers	146
Candler System Co.	146	Marks, C., & Co.	146	Symons, H. O., Ltd.	147
Chaffey Cabinet Co., The	140	Marris & Carlin, Ltd.	146	Szymanski, S.	138
Champion Products	137	Martin, J. H.	144	Tanno Products, Ltd.	140
Chapman, C. T. (Reproducers), Ltd.	130	McDermott, H. R.	140	Tape Recorders (Electronics), Ltd.	90
Cinema Television, Ltd.	96	McMurdo Instrument Co., Ltd., The	94	Taylor Electrical Instruments, Ltd.	65
City & Rural Radio	10	Measuring Instruments (Pullin), Ltd.	122	Taylor Tunnicliff & Co., Ltd.	12
City Sale & Exchange, Ltd.	90	Midland Instrument Co.	40	Telecraft, Ltd.	142
Classic Electrical Co., Ltd.	93	Miers, N., & Co., Ltd.	103	Telegraph Construction & Maintenance Co., Ltd.	101
Clydesdale Supply Co., Ltd.	106	Modern Book Co.	133	Telemechanics, Ltd.	40
Clyde Radio, Ltd.	127	Modern Electronics, Ltd.	102	Tele-Radio (1943), Ltd.	97
Cohen, D.	126	Modern Techniques	98	Telatron Co., The	147
Cosmocord, Ltd.	72	Morane Plastics, Ltd.	147	Transradio, Ltd.	32, 48
Coventry Radio	135	Morley Transformers, Ltd.	147	Trianon-Electrical, Ltd.	66
Cranston, A. A.	146	M.R. Supplies, Ltd.	56	Trix Electrical Co., Ltd.	149
Davis, A. & Co.	134	Mullard, Ltd.	3, 14, 29, 47, 70	Trusund, Ltd.	16
Davis, Jack (Rays), Ltd.	100	Multicore Solders, Ltd.	Cover iv	Truvox, Ltd.	95
Direct T.V. Replacements	98	Nagard, Ltd.	58	United Insulator Co., Ltd., The	56
Donohoe's (Timers)	138	Northern Radio Services	18	Universal Electrical Instruments Corp., Ltd.	118
Drayton Regulator & Instrument Co., Ltd.	54	Northern Transformer Co.	141	Universal Electronics	124
Dubilier Condenser Co. (1925), Ltd.	4	Nousound Products	135	Valradio, Ltd.	52
Duke & Co.	145	Nu-Swift, Ltd.	138	Venner Accumulators, Ltd.	37
Dulci Co., Ltd.	144	Oddie Bradbury & Cull, Ltd.	144	V.E.S. Wholesale Services, Ltd.	124
Dun (Electronics) & Co.	142	Oryx Electrical Laboratories	36	Vortexion, Ltd.	79
Easco Electrical, Ltd.	138	Osom Radio Products, Ltd.	39	Waterloo Radio	140
Edison Swan Electric Co., Ltd., The	74	Orley Developments Co., Ltd.	136	Wayne Kerr Laboratories, Ltd., The	13
Egen Electric, Ltd.	26	Parfameko, Ltd.	19	Westinghouse Brake & Signal Co., Ltd.	9
Electradix Radios	126	Parsonage, W. F., & Co., Ltd.	146	Weymouth Radio Mfg. Co., Ltd., The	60
Electrical Instrument Repair Service, The	128	Partridge Transformers, Ltd.	129	Wireless Wireless Works	54
Electro Acoustic Developments	138	P.C.A. Radio	120	Whitmore, A. J. (Aeradio), Ltd.	144
Electro Acoustic Industries, Ltd.	53	Pearce, T. W.	139	Wilco Electronics	140
Electro-Winds, Ltd.	64	Pitman, Sir Isaac, & Sons, Ltd.	134	Willenden Transformer Co., Ltd.	42
Electronic Instruments, Ltd.	105	Pollock, A. M.	134	Wilson, Ronald, & Partners	142
Electronic Precision Equipment	84, 85, 86, 87			Winter Trading Co., Ltd.	139
E.M.G. Handmade Gramophones, Ltd.	141			Wright & Weaire, Ltd.	5
E.M.I. Institutes	75, 78, 82				
Engineering Associates	140				
English Electric Co., Ltd., The	89				
Eta Tool Co. (Leicester), Ltd.	40				
Ever Ready Co. (Gt. Britain), Ltd.	44				
Fluxite, Ltd.	132				
Franks, H.	141				

Printed in Great Britain for the Publishers, **CLIFFE & SONS LTD.**, Dorset House, Stamford St., London, S.E.1, by **CORNWALL PRESS LTD.**, Paris Garden, London, S.E.1. *Wireless World* can be obtained abroad from the following: **AUSTRALIA AND NEW ZEALAND:** Gordon & Gotch, Ltd. **INDIA:** A. E. Wheeler & Co. **CANADA:** The Wm. Dawson Subscription Service Ltd.; Gordon & Gotch, Ltd. **SOUTH AFRICA:** Central News Agency, Ltd., William Dawson & Sons (S.A.), Ltd. **UNITED STATES:** The International News Co.

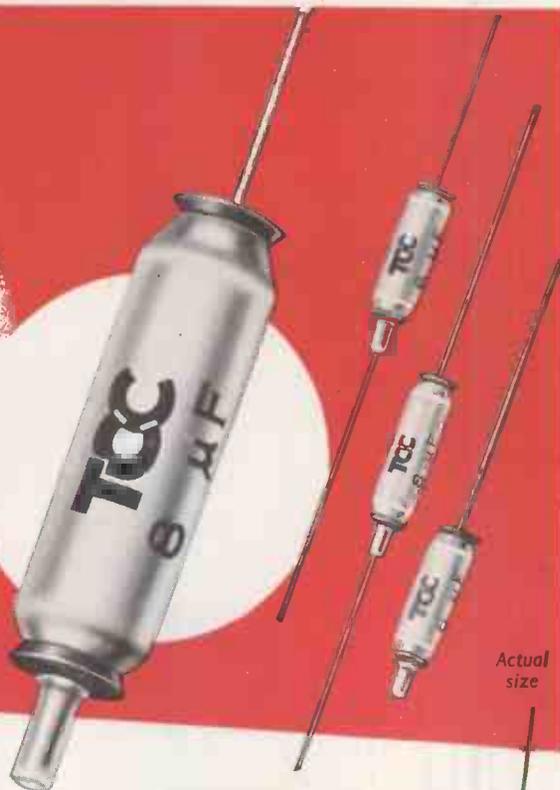FOCUS ON LEADERSHIP SUB-MINIATURE ELECTROLYTICS



Actual size

The recent introduction of transistors has created fresh impetus to the design of ancillary components of comparably small dimensions. For this purpose we have produced a range of Sub-Miniature Electrolytic Condensers, which we believe to be the smallest of their type ever made. These diminutive condensers are equally suitable for use in miniature walkie-talkie equipment, hearing aids, and similar assemblies where every component is scaled down to the absolute minimum physical size.

One feature of their construction is a plug-pin ($\frac{1}{8}$ " long), which forms one of the terminations, thus enabling them to be inserted quickly and easily. On the other hand, these condensers can be supplied with tinned copper wire terminations, $1\frac{1}{2}$ " long, both ends, if required.

The temperature range is $-30^{\circ}\text{C}.$ to $+60^{\circ}\text{C}.$, and the tolerance of capacity -25% to $+50\%$.

Capacity in μF	Peak Working Volts	Dimensions in inches		T.C.C. Type Number
		Length	Diameter	
6	3	.64	.18	CE68AA
8	6	.71	.2	CE69A
2	12	.64	.18	CE68B
4	12	.71	.2	CE69B
*8	15	.75	.26	CE67B
1	25	.64	.18	CE68C
2	25	.71	.2	CE69C
.5	50	.64	.18	CE68D
1	50	.71	.2	CE69D

* This condenser can only be supplied with wire terminations both ends.

T.C.C. Patent Nos. 578 487, 578 509, 587 072.



THE TELEGRAPH CONDENSER CO LTD

RADIO DIVISION


NORTH ACTON · LONDON · W.3 Tel: ACORN 0061

SPECIALISTS IN CONDENSERS SINCE 1906


THE FINEST CORED SOLDER IN THE WORLD

For everything to do with soldering

FROM A HEARING AID
WITH
100 JOINTS

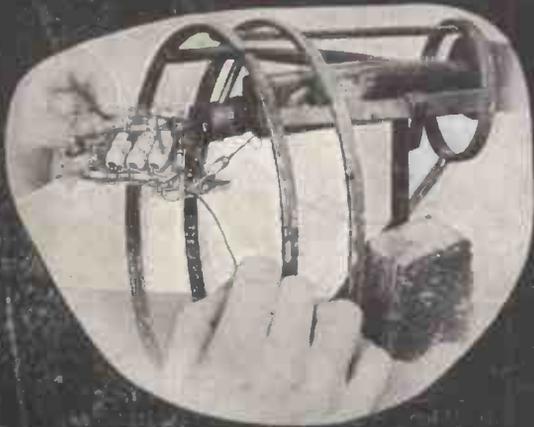

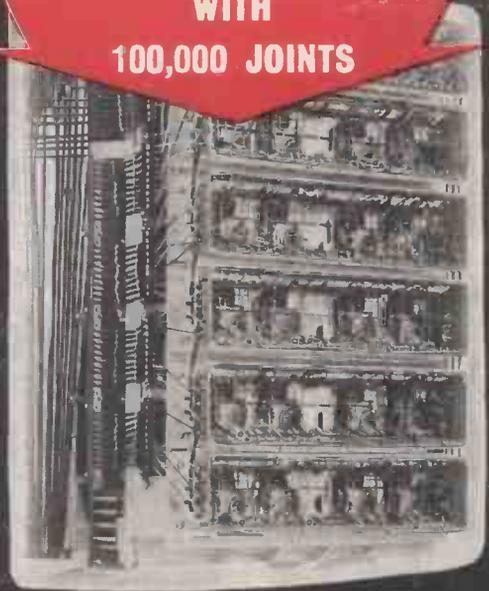TO A DIGITAL COMPUTER
WITH
100,000 JOINTS



ERSIN MULTICORE SOLDER



Reliability of soldering processes is achieved by use of Ersin Multicore Solder which for nearly 15 years has been preferred by leading manufacturers in Europe and the U.S.A. It is supplied as standard containing three cores of non-corrosive Ersin Flux. Ersin Flux is a high-grade resin which has been chemically processed to increase its fluxing action, while still retaining its non-corrosive properties. It makes precision soldering quicker and more economical—not only preventing oxidation during soldering, but actually cleaning the surface to be soldered. Approved by A.I.D., A.R.B. and G.P.O. Fully meets U.S. Federal specifications. Available in 2 flux percentages.

Cat. Ref. No.	Alloy Tin/Lead	S.W.G.	Approx. Length per carton
C 16014	60/40	14	21 feet
C 16018	60/40	18	55 feet
C 14013	40/60	13	19 feet
C 14016	40/60	16	38 feet

*Specially recommended for television work.



SIZE 1 CARTON
5/- (SUBJECT)

Multicore products for specific uses

ALLOYS—made in all the usual Tin/Lead alloys as follows;—60/40, 50/50, 45/55, 40/60, 30/70, 20/80.

SPECIAL HIGH AND LOW MELTING POINT SOLDERS. Ersin Multicore is available in the following special alloys, all containing 3 cores of Ersin Flux:—

Type T.L.C. Melting Point 145°C.

Type L.M.P. Melting Point 179°C. Avoids 'pick-up' of silver when soldering ceramics.

P.T. Melting Point 232°C. When lead-free solder is required.

COMSOL. Melting Point 296°C. Extra high melting point soft solder.

GAUGES. Ersin Multicore Solder is made as standard for factory use in gauges between 10-34 s.w.g. as follows:—10, 12, 13, 14, 16, 18, 19, 20, 22, 24, 26, 28, 30, 32 and 34 s.w.g.

FLUXES. Ersin Multicore Solder is supplied in 2 flux percentages and in the following flux types:—

N. Flux contains Pentacol. Unless otherwise ordered, all Ersin Multicore Solder is supplied with this type of flux.

3E Flux. The original Ersin Flux formulation. Has been supplied for more than 14 years.

R2 & R3 Fluxes. Halide and Chloride free fluxes for modern production soldering process calling for this type.

L Flux. Suitable for high speed machines and particularly Lamp production.

2L Flux. As Type L but with only 2.2% flux content.

Type 362 Flux. Extremely fast A.I.D. approved flux. Latest Multicore development.

RINGS. Butt-jointed solder rings in Ersin Multicore Solder Wire or precision made Solid Solder Wire can be supplied in bulk quantities. Gauges—dependent upon the diameters specified—cover the range from 10 to 22 s.w.g.

TAPE SOLDER. With or without flux cores. Packed on 3½-lb. reels in widths from ¼"-¾" and thicknesses from .005".

SEPARATE FLUXES. For dipping purposes or other processes where it is not convenient to use Ersin Multicore Solder, Ersin non-corrosive Flux is available in liquid form. Approved A.I.D. and D.T.D. 599 specifications. Ersin Jelly Flux with a high viscosity consistency is also available.

ARAX MULTICORE SOLDER. For non-electrical work and particularly for jointing metals. Arax Multicore Solder is supplied with 2 cores of acid-free flux with washable flux residue.

SOLID SOLDER WIRE. For the comparatively few soldering processes where solid wire is required instead of Multicore solders, supplies are available to special order of Multicore Precision Made Solid Wire in all alloys.

FLUID SOLDERS. Araxolder in paint or cream consistency with washable flux residue. A similar product with Ersin non-corrosive flux is also supplied.

MULTICORE SOLDERS LTD., MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3636)