wireless world

JUNE 1976,35p

CD-4 demodulator Wireless across space



Australia \$A1.20 Belgium Fr. 61.50 Canada \$1.50 Denmark Kr. 11.00 Finjland Fmk. 6.20 Germany Om. 4.50 Greece Dr. 45.00 Holland Dil. 4.50 Holgut. 900 Malaysia M83.25 New Zashand \$NS1.20 Norway Kr.10.00 Lincl. mom Portugał Esc. 40.00 South Alrica R. 1.10 Boajn Ptas.80.00 Sweden Kr.6.90 lincl. moms U S.A. 150 

mi's TF 2015 a wider view of signal generation...

The TF 2015 is a versatile 10-520 MHz signal generator with calibrated a.m. and f.m. and an accuracy of output level setting normally found only in instruments costing three times as much. A special system gives very fast tuning across the bands yet provides smooth control within the narrowest of passbands. Leakage radiation is carefully screened out to enable accurate measurements to be made even at levels below 1μ V.

Matched Synchronizer

The clip-on Synchronizer TF 2171 transforms the performance of TF 2015 into the equivalent of a synthesizer at less than half the comparable cost. The frequency is locked to crystal stability and can be dialled in 100 Hz. steps. Tuning is quick and easy – set the decade dials, switch to "lock" and tune the generator to the approximate

frequency and the synchronizer will finish the job for you. Now you can change the frequency by up to 2% using the decade dials **without touching the generator** and all to an accuracy of 2 parts in 10[?]. It stays locked all day and doesn't degrade **any** aspect of the generator performance.

I.F. Probes

These are an invaluable aid to the testing of receivers

with squelch or battery economiser circuits. These circuits are inactivated when the crystalcontrolled signal from the probes is brought into the proximity of the receiver's i.f. strip. This makes it easy to tune the generator to a receiver when its channel frequency is unknown. The probes can also be used to check exact tuning by adjusting for zero beat.



MARCONI INSTRUMENTS LIMITED

Longacres, St. Albans, Hertfordshire, England, AL4 0JN · Telephone: St. Albans 59292. Telex: 23350.

A GEC-Marconi Electronics company.



LEVELL ELECTRONICS LTD. Moxon Street, High Barnet, Herts. EN5 5SD Tel. 01-449 5028/440 8686

Prices include batteries and U.K. delivery. VAT extra. Optional extras are leather cases and mains power units. Send for data covering our range of portable instruments.

WW-051 FOR FURTHER DETAILS

EMI offers the widest choice of options in Cable T.V.

EMI Colorline Cable TV equipment provides long reach, low distortion and high channel capacity. It is based on the RE 1000 range of modular VHF trunk amplifiers offering full two-way facilities. Basic forward bandwidth is 40-300 MHz with optional reverse bandwidths of 5-30 MHz or 5-100 MHz.

2

And now EMI introduces hybrid VHF/UHF systems based on our new RE 1037,* a unique VHF/UHF distribution converter. It enables up to seven VHF trunk channels to be converted into the UHF bands for local distribution together with unconverted VHF channels.

Then there's the ME 670, an ultra wideband distribution amplifier covering the range 40-860 MHz and incorporating its own line or mains power supply. Also covering the same range are the new RE 1022 ultra wideband Subscriber Tap and RE 1032 Splitter.

These are just some of the new developments you can expect from EMI, who cover virtually every requirement for VHF and UHF distribution networks, together with unrivalled technological and design resources and the most comprehensive service facilities in the business.

So when you're planning for cable television contact EMI, the specialists.

*The RE 1037 is manufactured by EMI under licence from the British Post Office.









EMI Sound & Vision Equipment Ltd., 252 Blyth Road, Hayes, Middlesex, England. Tel: 01-573 3888. Telex: 25145. Cables: EMISOUND. A member of the EMI Group of Companies. International leaders in music, electronics and leisure. WW-081 FOR FURTHER DETAILS

www.americanradiohistory.com

We've joined Christopher Wren in the dome business...

... as users of our Dome Tweeters will already know

ISOPHON—are a company who have been manufacturing loudspeakers for over fifty years and are internationally known and respected for quality and reliability. They offer a wide range of tweeters, mid-range and bass units.

Owing to shortage of space we are only able to draw your attention to just two of the models currently being manufactured by Isophon

The KK8

A dome tweeter, well known for its performance and reliability, and chosen by many loudspeaker manufacturers. Two models are available, one up to 50 watts and the other up to 80 watts RMS Power Rating. Frequency range from 800 to over 20,000 Hz.

The PSL 245/60

A new 10" circular loudspeaker, offering up to 60 watts RMS Power Rating.

Our 28 page colour catalogue will give you details of the extremely wide choice of loudspeakers that are available from Isophon.



For your free copy of the catalogue, please post the coupon to . . .

Hayden Laboratories Limited Hayden House, Churchfield Road Chalfont St. Peter, Bucks. SL9 9EW Tel: Gerrards Cross (028 13) 88447

10 to 512 MHz GENERATOR



Model M3A/ADJ is just one item from a range of

communication test equipment from Farnell which may be seen at the Communications '76 Exhibition.

Facilities include:

- amplitude and frequency modulation
- narrowband sweep
- crystal stability and accuracy
- Iow r.f. leakage
- built in r.f. detector and xy outputs
- remote control facilities

Other products on display include:

- Data cartridge recorders
- Computer peripherals
- Video display terminals
- Frequency counters
- Sweepers
- Power supplies Alarms etc.

Telephone us for a ticket to the show or use the publishers reply service for full data on all products.



FARNELL INSTRUMENTS LIMITED SANDBECK WAY, WETHERBY, WEST YORKSHIRE LS22 4DH TELEPHONE: 0937 3541 TELEX 557294 I ONDON OFFICE: 01-864 7433

WW - 070 FOR FURTHER DETAILS

For faster delivery try these sources

мΩ

MEGGER

Our Appointed Distributors have been ordering instruments on your behalf for over a year now. This means they can deliver your order quicker than any other source. They can help you choose the right instrument, too. Here's where to contact them:

LONDON AREA

London

Edmundson Electric Ltd. Tel: 01-891 1331 ERD(South East) Ltd. Tel:01-928 5620 Lugton & Co. Ltd. Tel: 01-348 8247 R.T.&I. Electronics Ltd Tel:01-539 4986 ITT Distributors Ltd. Tel:01-8036522 Harlow **ITT** Instrument Services Tel: 0279 29522 Welwyn Garden City Ellistons (Welwyn) I td Tel:07073 26344 MIDLANDS Coventry

Mercia Electronics Ltd. Tel: 0203 24091 Birmingham ITT Distributors Ltd. Tel:021-236 5030 ERD (Midlands) Ltd. Tel: 021-236 5060 Northampton E.M.F.(Electrical) Ltd. Tel: 0604 21711 Norwich Newey & Eyre Ltd. Tel: 0603 49341 Nottingham Newey & Eyre Ltd. Tel: 0602 866531 NORTHERN IRELAND Belfast Eirco Ltd. Tel: 0232 42911 NORTH EAST Hull Edmundson Electric Ltd. Tel: 0482 20691 Leeds Farnell Electronic Components Ltd. Tel:0532636311 Wetherby: Farnell Instruments Ltd. Tel:09373541 Newcastle upon Tyne

J. Cledson & Co. Ltd. Tel: 0632 860955

NORTH WEST AND N. WALES Salford Hirst Ibbetson & Taylor.Ltd. Tel: 061-832 9711 J. Walton (Electrical) Ltd. Tel: 061-872 4224 SCOTLAND Glasgow ERD(Scotland) Ltd. Tel: 041-647 7141 Elesco-Fraser Ltd. Tel: 041-221 9301 SOUTH WEST AND S. WALES Bristol

THORN

Black Arrow (Electronics) Ltd. Tel: 0454 315824 Cardiff

Newey & Eyre Ltd. Tel: 0222 45831 Bath

ERD (South West) Ltd. Tel: 0225 63281 You will still be able to buy our instruments through your usual wholesaler, although he may not be an Appointed

Distributor.



Avo Limited Evershed & Vignoles Limited MEGGER Instruments Division H. W. Sullivan Limited



Contact Chris Walden on Windsor 51056/7

ALICE (STANCOIL LTD.), 38 ALEXANDRA ROAD, WINDSOR, BERKS, ENGLAND

Also available from Roger Squires, London and Manchester

WW - 018 FOR FURTHER DETAILS



PEP output Transmitter-Receiver covering 2.16 MHz on 4 or 6 channels.

Rugged construction for today's tough environments. Easily accessible for simple maintenance.

Ten plug-in modules give maximum insurance against loss of service.

The advanced technology used in the AEL 3030 provides unmatched efficiency in point to point or mobile communication, minimises size and cost and maximises reliability!

DESIGNED FOR RELIABILITY

For further information and colour brochure write to:



Telex 87116 (Aerocon Horley) Cables: Aerocon: Telex: Horley

WW-056 FOR FURTHER DETAILS



Follow the 'Philips plus' way to prosperity

Make sure that your workshop is the most efficiently equipped and that your service engineer's home visits are the fastest and most effective. Get these Philips instruments now. You won't find better value for money.

NEW



PM5501 PAL TV Pattern Generator Price £149

Extremely light, portable instrument for service in customers' home. 5 different test patterns for colour and black/white installation and service. RF output signal switchable: VHF Band III and UHF Band IV. 1 kHz tone for sound performance checks.

PM5509 PAL TV Pattern Generator Price £350

The ultimate in pattern generators. Full IF coverage; band I, III, IV and V. Electronic tuning with 5 preset channels. 10 test patterns (colour and black/white). Adjustable chroma/burst and HF-amplitude. Special sync, video and VCR outputs.





PM5324 HF Generator

Frequency range 100 kHz – 110 MHz. X-tal calibration. Special band spread ranges. High frequency stability. Electronically stabilised output max. 50 mVrms in 75 Ω . Facilities for internal and external AM and FM modulation.

PM6456 FM Stereo Generator Price £192

Complete stereo signal. L & R signal. Internal L.F. modulation: 1 & 5 kHz. External stereo modulation possibility. X-tal controlled pilot. Adjustable multiplex signal.

Price £297



PM5334 TV Sweep Generator Price £399



8 frequency ranges, 3 MHz – 860 MHz. Sweep width continuously adjustable over selected range. Sweep frequency adjustable, 8 – 50 Hz. One variable and 3 fixed markers. Signal frequency is accurate and thermally stable. Stabilised output into 75 Ω load.

PM2412 General Purpose Multimeter Price £48 DC voltage 300 mV - 1000 V.

AC voltage 300 mV = 1000 V. AC voltage 3 V = 600 V. DC current 10 mA = 6 A. (all values f.s.d.) Resistance 1 Ω + 10 M Ω . Tautband 40,000 Ω/V . suspension-type meter.





2-3°, accuracy on all ranges. Resistance measurements: unique linear scale. No zero adjustment necessary. Automatic polarity

AC/DC voltage ranges 100 mV-1 kV. AC/DC current ranges 1 μ A - 1 A. Resistance ranges 100 Ω - 10 M Ω .

PM2503 Electronic Multimeter

Price £69

indicator.

PHILIPS

PM2513 Low Cost Digital Multimeter

Price £95 DC voltage ranges 0.2 – 1000 V. AC voltage ranges 0.2 – 600 V. AC/DC current ranges 0.2 mA – 2 A. Resistance ranges 200 Ω – 2 M Ω . Full circuit protection. Provision for temperature

measurements, -60 to +200°C.

PM3225 and PM3226 15 MHz oscilloscopes

Comprehensive triggering facilities (Auto, AC, DC and TV) Large 8 x 10 div. screen Sensitivity 2mV/div Ergonomic styling and lightweight construction

Single trace: PM3225. Price £210 Dual trace: PM3226. Price £290

The Philips Plus is the quality of design, specification and appearance – particularly in terms of human engineering – of every instrument. A total test and measuring range capability, which includes 'scopes, meters, counters, pulse generators, power supplies, recorders and generators. The ability to supply all the user's needs from a single source. All prices exclude VAT.

For prompt delivery of any of these instruments, send us your cheque, If you require further information, there is a new t6 page illustrated brochure packed with facts which we would be delighted to send you. Please use the reader reply service, write or telephone to



Pye Unicam Ltd Philips Electronic Instruments Dept.

York Street Cambridge England CB1 2PX. Tel: Cambridge (0223) 58866 Telex: 817331









WW --- 067 FOR FURTHER DETAILS

AMCRON POWER AMPLIFIERS

The AMCRON range of DC-coupled power amplifiers are used by Government, and University Research Departments as well as by Industry for a variety of applications ranging from Shaker, and Vibrator driving, to driving both AC and DC Motors, providing variable frequency power supply, or high voltage material testing. All models are DC-coupled throughout, with Intermodulation, and Harmonic Distortion below 0.05%, damping factor of at least 400 from DC to 1 kHz, and the ability to operate into load impedances from 1 ohm to infinity even into highly reactive loads



M600

RMS power out

8

Power bandwidth Phase response Slew rate Hum & noise Dimensions

750 watts into 8 ohms 1,350 watts into 4 ohms DC to 20 kHz + 1 db - 0 db + 0' - 15' DC - 20 kHz 16 V/ usecond 120 db below 600 Watts 19" std rack, 8¾" H, 16½" Deep



DC 300A

At least 110db below 150 watts 19" Rackmount, 7" High, 934"

DC-20kHz + 1 db - 0 db +0, - 15' DC to 20kHz

8 volts per microsecond



D150A

500 watts rms into 2.5 ohms (1 chan) 200 watts into 2.5 ohms (1 chan) DC-20 kHz + 1 db, - 0 db + 0', - 15' DC to 20 kHz 6 volts per microsecond At least 115 db below 90 watts 19'' Rackmount, 514'' H, 834'' I D

MACINNES FRANCE

45 Rue Fessart

Paris 75019, France Tel: 203-30-01



MACINNES LABORATORIES LTD. Macinnes House, Carlton Park Industrial Estate Saxmundham, Suffolk IP17 2NL. Tel: (0728) 2262 2615

Deep

WW-052 FOR FURTHER DETAILS



THE CINTEC SINUSOIDAL FREQUENCY **VOLTAGE STABILI**

FREGUENCY MO VOLTAGE STABLIZED POWER SUPPL

CINTEC LTD MITOHAM

- ***** SOLID STATE
- HIGH STABILITY
- ***** ROBUST
- *** VERSATILITY**
- ***** RELIABILITY
- ***** SINUSOIDAL

Reliable Frequency & Voltage Stabilization

The efficient operation of sophisticated electrical and electronic equipment is, in many instances, dependent upon an electrical supply which is stable in both frequency and voltage.

In many overseas countries and even in the United Kingdom, during periods of heavy demand, the variation in the frequency and voltage is sufficient to introduce errors and the malfunction of such items as Recording equipment, etc. Likewise, in certain areas, the only source of supply is from a Generator, the output of which can vary considerably when different loads are imposed. This has precluded the use of a wide range of equipment in many countries. Voltage Stabilizers are readily available but these do not stabilize the frequency of the supply which, in many instances, is essential

The CINTEC FREQUENCY & VOLTAGE STABILIZER provides the answer to both these problems.

When the supply frequency is fluctuating wildly, between 40Hz and 60Hz and the voltage by more than 10% the output from the Stabilizer will not vary more than .01% from 50Hz or 1% in voltage, even when different loads are imposed.

It opens up new markets for the manufacturers of a wide range of equipment for use in Recording Studios, Offices, Hospitals, etc., and in particular, when it is required for mobile operation.

C

The CINTEC FREQUENCY & VOLTAGE STABILIZER is also available for supplies of 100-125 volts, 40-60Hz with an alternative output of 50Hz or 60Hz at 115 volts or 230 volts and as a dual frequency model with a switchable output for 50Hz or 60Hz

The Stabilizer may also be used as a frequency converter. For example, the supply to it can be any frequency between 40-60Hz and the output can be switched to either 50Hz or 60Hz. In hotels, overseas visitors frequently bringing with them Audio-Visual arrive. equipment which they wish to use, only to find that the frequency of the supply in the hotel is unsuitable.

Applications for the use of the CINTEC FREQUENCY & VOLTAGE STABILIZER are more numerous than can be listed. Therefore, if you have a supply problem, contact CINTEC LIMITED whose engineers will be only too pleased to assist.

APPLICATIONS SOUND RECORDING EO RECORDING COMPUTERS VIGATIONAL SYSTEMS d

SPECIFICATION

| INPUT: | 100-125 volts or 200-250 |
|-----------------------------------|--|
| OUTPLT: | 115 volts or 230 volts (adjustable within $\pm 5\%$) |
| STABIL TY: Voltage; Frequency: | ± 1% No load to full load ± 0.01% No load to full load |
| FREQUENCY | 50Hz or 60Hz. Single or dual versions |
| WAVEFORM: | SINUSOIDAL |
| DISTORTION: | 2% Max. |
| AMB. TEMP. | -20' to +40' C |
| DUTY: | Continuous |
| DIMENSIONS: | 432 (W) x 196 (H) x |
| | 508mm (D) |
| | (17" x 7 ³ / ₄ " x 20") |
| WEIGHT: | 33Kg. (72 lbs.) |
| CONSTRUCTION: | Cabinet or rack mounting |
| TERMINATION: | Barrier strip connections at rear of case. |

24V DC Inverter

Inverter versions of the Stabilizer are available with output ratings of 500w, 250w and 150w, at 230 volts or 115 volts at 50Hz or 60Hz. The output stability has an accuracy to the same specification as for the A.C. versions and the Unit is housed in a case of similar design and size.

Certificate of Calibration

The Stabilizer has been tested in accordance with National Standards by Bradley Services of London (Certification No. K5149/5832)

| INITEC | Detailed Specification and Brochure - Available Post Coupon or Telephone/Telex |
|---------------|--|
| CINTE | Name |
| | Position |
| HER STAR | Company |
| | Aildress |
| 171 | |
| | |
| i | |
| Wandle Way, M | itcham, Surrey CR4 4NB. England. Telephone: 01-640 2241 Telex: \$46177 |

Type 19

25mm model

RANSPORTS

2 and 4 speed models

section of the section of the

Electric por

Bolestreethore

anstrong the south Straton - and to lea 2E159tworks



WW - 059 FOR FURTHER DETAILS



www.americanradiohistory.com

Take your pick!...

THOMSON-CSF electrostatic CRT's :

for high-performance scopes :

| Tube ref. | Useful screen area cm x cm | Overall length cm | Typical frequency MHz | Capacitance pF | Wilting speed | Deflection factor X1X2 Y1Y2 V. cm ⁻¹ |
|-----------|----------------------------------|-------------------------|-----------------------------|-------------------|------------------|--|
| TH 8203 | 8 x 10 | 37 | 350 | Zc=Z x 150 Ω | 30 | 6.1 1.2 |
| TH 8205 | 8 x 10 | 34 | 200 | 8 | 15 | 5.4 2.2 |
| TH 8206 | 10 x 12 5 | 38 | 100 | 8 | 15 | 6.5 2.8 |
| TH 8207 | 10 x 12 5 | 40.5 | 175 | 8 | 25 | 6.5 2.6 |

for large-screen wideband monitors :

| Tube ref. | Useful screen area cm x cm | Overall length cm | Deflection angle ⊖° | Sersitivity V cm ⁻¹ |
|-----------|----------------------------------|-------------------------|---------------------------|-----------------------------------|
| TH 8000 | 25 x 19 | 44 | 70 | 9 |
| TH 8201 | 18 x 13 | 35 | 85 | 7.5 |

Rugged versions available.



THOMSON-CSF ELECTRONIC TUBES LTD / RINGWAY HOUSE / BELL ROAD / DANESHILL * BASINGSTOKE RG24 OOG TEL. : (0256) 29155 / TELEX : 858865

WW-073 FOR FURTHER DETAILS

£25 extra



12

WW - 023 FOR FURTHER DETAILS

www.americanradiohistory.com





www.americanradiohistory.com

Join the Digital Revolution

Understand the latest developments in calculators,

computers, watches, telephones,

television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures $1134^{\prime\prime}$ x $814^{\prime\prime}$ and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers

Design of Digital Systems



E6.2 plus 80p packing and surface post anywhere in the world. Payments may be made in foreign currencies

Quantity discounts available on request. VAT zero rated.

Also available - a more elementary course assuming no prior knowledge except simple arithmetic Digital Computer Logic and Electronics

In 4 volumes:

- Basic Computer Logic
- Logical Circuit Elements 3
- Designing Circuits to Carry Out Logical Func-
- tions 4. Flipflops and Registers

Offer Order both courses for the bargain price £9.70, plus 80p P. & P

£4.20

plus 80p P. & P

Designer Manager Scientist Engineer Student

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the Enthusiast advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee-no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

| To Cambridge Learning Enterprises, Dept COM FREEPOST, St. Ives, Huntingdon, Cambs, PE17.48R *Please send meset(s) of Design of Digital Systems at £7.00 each, p & p included |
|---|
| forset(s) of Digital Computer Logic and Electronics at £5.00 each, ρ & ρ included |
| for combined set(s) at £10.50 each, p & p included |
| Name |
| Address |
| |
| |
| 'delete as applicable No need to use a stamp — just print FREEPOST on the envelope. |
| WW6 |

COIL WINDING



Manufacturers of all wound components including transformers, chokes, stators and armatures. Prototype and design service available.

Electric Windings' factories are equipped to handle large or small volume production. Vacuum impregnation plants provide varnish impregnation for all temperature requirements.

ELECTRIC WINDINGS (LONDON) LTD. (Dept. WW) Avenue Works, Gallows Corner Romford, ESSEX RM3 0AJ

Ingrebourne 46677

WW-039 FOR FURTHER DETAILS



Wireless World, June 1976



RADFORD

AUDIO HIGH SENSITIVITY **VOLTMETERS & NOISEMETERS**

| HSV1 | Audio Voltmeter. Average reading £125.00 |
|------|---|
| HSV2 | Audio Voltmeter. True r.m.s. reading £175.00 |
| ANM1 | Audio Noisemeter. Average reading £150.00 |
| ANM2 | Audio Noisemeter. True r.m.s. reading £200.00 |

Four instruments are now available for the measurement of audio frequency signals including noise. They are derived from a basic battery operated voltmeter design having 16 measurement ranges from $10 \mu V$ for full scale meter deflection to 300V f.s.d. The Voltmeter has a high input impedance and low inherent noise. It is fitted with a high grade meter having a 5" mirror scale of excellent linearity, calibrated in volts and dBv.

The Audio Voltmeter (HSV1) becomes an Audio Noisemeter (ANM1) by the inclusion of frequency contouring networks having characteristics recommended by international organisations concerned with specifications and measurement standards as being suitable for the quantitative measurement of the subjective effect of noise in audio systems. The HSV1 and ANM1 instruments respond to the average or mean value of the waveform being measured and are calibrated in r.m.s. values on a sine wave

In the HSV2 and ANM2 instruments an r.m.s. to d.c. converter module is incorporated which provides a true r.m.s. reading on waveforms with a crest factor in excess of 10. These instruments are also provided with an additional output socket giving 1.00V d.c. output corresponding to 1.00V at nominal full scale meter deflection to operate a chart recorder or d.c. digital voltmeter.

All the instruments are fitted with a socket to enable an external network of any weighting characteristics to be introduced in the measuring circuit. This extends the use of the instruments to vibration and acoustical measurement as well as to the measurement of gramophone turntable rumble, f.m. receiver noise, etc.

Brief Specification.

| Frequency response as Voltmeter | 4Hz to 500kHZ ± 0.5dB at frequency limits. |
|--|--|
| Input impedance | 1 Mohm shunted by 30pF. |
| Attenuator accuracy | 0.25%. |
| Meter scale linearity | 1%. Typically better than 0.5%. |
| Waveform error in true r.m.s. instruments | 1% for crest factor 10. |
| Noisemeter included weighting characteristics | Wide band (flat response as voltmeter) DIN. 'Audio Band' IEC/DIN. Curve 'A' CCIR |
| Size | 11¼′′′ x 7¼′′′ x 8½′′ deep overall |
| Di ita anabara far dagarir | tive leaflet giving details of the |

Please write design and full performance characteristics of the above instruments, together with a reprint copy of Dolby Laboratories Inc. Engineering Field Bulletin No. 19/2 — 'Noise Measurement on Consumer Equipment'

RADFORD LABORATORY INSTRUMENTS LTD. Ashton Vale Road, Bristol BS3 2HZ Avon Telephone 0272 662301

USA, Roth/Sindell, 540 Kelton Ave., Suite 102 Los Angeles, California 90024. Tel. (213) 473-3687

WW-063 FOR FURTHER DETAILS

WW-037 FOR FURTHER DETAILS

BARR & STROUD **BARR & STROUD BARR &**

The introduction of our EF3 Electronic Filter System was a breakthrough in electronic filtering, a System with options and interchangeability.

Now we introduce two additional modules to extend the scope and versatility of the EF3. To appreciate fully the technical and economic merits of the EF3 System you ought to have our detailed literature which we will be pleased to send. Continuing development of the EF3 System means that we will be announcing yet more modules in the near future.

Send now for full details to



Glasgow and London

Barr & Stroud Limited, 1 Pall Mall East, London SW1Y 5AU. Tel : 01-930 1541 Telex : 261877

EF3 Basic Main Frame

EF3-04 Low Pass

EF3-03 High Pass

EF3-02 Low Pass

EF3-01 High Pass

Cut-off frequency variable from 0-01 Hz to 10kHz

Cut-off frequency variable/from 0-01Hz to 10kHz

WW-041 FOR FURTHER DETAILS



ews of the Decade

11

RESISTANCE CAPACITANCE INDUCTANCE over 60 different models

available, many from stock

CONTACT US IF YOU NEED MORE INFORMATION OR DEMONSTRATION

DECADE BOXES

| | L | ECADE DU/ |
|--------------|----------|------------------|
| "Junior"Seri | es—Resis | tance—1% |
| | Decades | Ohms Range |
| .11 | 5 | 0- 1.111.100 |
| 12 | 5 | 0 111110 |
| 12 | 4 | 0 111 100 |
| 14 | 4 | 0 |
| J4 1E | 4 | 0 11,110 |
| 12 | 3 | 0 |
| 16 . | 3 | 0 1,110 |
| 160 | 6 | 0 - 1111,110 |
| J70 | 7 | 0-11,111,110 |
| "Junior" Ser | ies—Capa | citance—1% |
| | Decades | pF Range |
| JC1 | 3 | 100- 111,000 |
| JC2 | 2 + var | 30- 11,140 |
| "Point One" | Series-F | Resistance-0.1 % |
| | Decades | Ohms Range |
| R3 | 4 | 0- 1,111 |
| R4 ' | 4 | 0 11,110 |
| R5 | 4 | 0- 111 110 |
| R7 | 5 | 0- 1,111,100 |
| R9 | 5 | 0- 111.110 |
| R10 | 5 | 0 11.111 |
| B11 | 5 | 0-11 111 000 |
| B20 | 6 | 0 - 1 111 110 |
| R21 | 6 | 0- 111111 |
| D 2 2 | 6 | 0. 111111 |
| R22 | 7 | 0 11 111 10 |
| D21 | 7 | 0 1 1 1 1 1 1 |
| n 3 1 | 7 | 0 111 111 1 |
| RJZ R41 | 0 | 0 11 111 111 |
| R41 | 8 | |
| R42 | 8 | |
| Hundred | Decador | Ohms Bande |
| D400 | Decades | 0 111 100 |
| R400 | 4 | 0 |
| R401 | 4 | 0 11,110 |
| R402 | 4 | 0 1,111 |
| R403 | 4 | 0- 1111 |
| R600 | 6 | 0 |
| R601 | 6 | 0 = 1 111 110 |
| R602 | 6 | 0- 111.111 |
| R603 | 6 | 0- 111111 |
| R701 | 7 | 011,111,110 |
| R702 | 7 | 0 1.111 111 |
| R703 | 7 | 0- 111,111 1 |
| R802 | 8 | 011,111,111 |
| - | | |

ISTRUMENTS



Ohms Resolution

10

10

10

30.90

30.50 25.10

24.80

20.60

| R803 | 8 | 0- 1, | 111,11 | 1.1 0.01 | | 162.80 |
|--|--|---|--|---|---|---|
| High Dissip | ation—Re | sistance- | 1% | | | |
| HD1 HD1/L | Decades 5 5 | Uhms Rai 0 1, 0 | nge 111,10(111,11(e-5% | 0 0 10 0 0.2 A | Resolution pprox. | £ 104.70 110.30 |
| i onit one | Decador | mH Pao | | m H R | esolution | 6 |
| L1 L2 L3 | 3 2 2 | 0- 0- 0 | 1,11(11(1,10 |) 1) 1 0 10 | esolution | 95.60 67.10 74.50 |
| "Hundred" | Series-I | nductance | -0.3 % | | | |
| L300 L400 | Decades 3 4 | mH Rang 0— 0— | ge 1 110 11.110 | mH Re 0 1 0 1 | esolution | £ 277.00 360.00 |
| | CA | PACIT | ANČ | E BOX | ES | |
| Decades | | | | | | · |
| C3 PC3 C4 PC4 | Decades 3 3 4 4 | pF Rang 100 | e 11.000 11,000 11,000 11,000 | pF Resolution 100 100 100 100 | n Accuracy 1% 5% 1% 5% | £ 48.30 66.70 73.60 103.50 |
| Decade plus | s Variable | 8 | | | | |
| VC4 VC5 PVC5 SVC5 C500 SVC5 specia | Decades 3 4 4 4 4 4 I Details o | pF Rang 50 1 50 1,1 50 1,1 50 1,1 50 1,1 n applica.io | e 11,150 11,150 11,150 11,150 11,150 n | pF Resolution INFINITE | Accuracy 1% 1% 0.5% 0.05% 0.2% | £ 61.00 86.30 128.80 574.20 238.50† |
| Variables | | | | | | |
| PVC1 Mk 2 PVC2 Mk 2 VC2 PVC4 PVC1 'S Switched | | pF Range 5 20 20 0 20 | 200 1,120 1 130 10 120 | | 0 5% 0 5% 1% 1% 0 5% | £ 111.32 101.20 42.60 77.22 67.10 |
| | | uf Bande | | E. Resolution | Accuracy | £ |
| C140 C100 C60 C60P | | 0 0 0 | 140 100 61 61 | 1 0 1 0 0 1 0.1 | 5% 5% 5% 1% | - 156.00 132.00 117.60 239.00 |

DECADE BOXES continued

+ Packing and Handling extra. Prices do not include VAT

J.J. LIOYA Instruments Ltd

Brook Avenue, Warsash, Southampton SO3 6HP Tel: Locks Heath 4221 ww-053 FOR FURTHER DETAILS



17

HATFIELD BAL The FIRST name for WIDEBANDMATCHING TRANSFORMERS

With over 30 year's experience in designing Wideband Matching Transformers Hatfield Instruments design team offer a solution to almost all problems of matching unbalanced to balanced impedances of different values.



INTRODUCTORY PRICES

In addition to National, Mostek and Caltex clock chips, we are now selling a range of General Instrument chips

AY-5-1202 + Futaba 5LT01

AY-5-1202 interfaces directly with 5LTO1 to provide the basis for a very simple electronic clock. The hours and minutes can be in 12 or 24 hour format and 50 or 60 Hz can be used as the timing source. 5LTO1 is a green phosphor diode display. Price £10.56

AY-5-1230 + Futaba 5LT01

This chip similar to 1202. It has an ON / OFF programmable alarm which can be used in 7 segment mode to drive the 5LTO1 or in BCD format to drive logic or TV display chips. Price £11.05

MK50253 + Futaba 5LT01

12 or 24 hour, 6 digit alarm chip. Snooze facility. Price £11.40

MISTRAL CLOCK KIT

Uses AY-5-1202 + Futuba 5LTO1. Complete kit including case. £11.58

CHEVIOT ALARM CLOCK

24-hour 4-digit alarm clock, 0.5" green display, tilt to snooze Finished clock - not kit. £21.85.

Please send S.A.E. for new Catalogue Terms: C.W.O. Access, Barclaycard (simply quote your number and sign) Credit facilities to Accredited account holders ALL PRICES EXCLUDE VAT AT 8%

BYWOOD ELECTRONICS Hemel Hempstead, HP3 9RDF Tel. 0442 62757



can be left permanently in-line in the transmission cable measurements can then be taken without disconnecting the antenna.

MOTOROLA ELECTRONICS LTD., 444 BATH ROAD, SLOUGH, BERKS. TELEPHONE: BURNHAM 62427 TELEX: 847121.

WW - 010 FOR FURTHER DETAILS

68 Ebberns Road

DOLBY NOISE REDUCTION The First Successful Decade: 1966 ~ 1976

Dolby noise reduction has staying power. The A-system has been around for ten years. If you have read our technical papers and otherwise followed our progress, you're probably familiar with the reasons for this success. Here are ten quick reminders.

1

The Dolby system works like a constant-gain amplifier in two critical dynamic regions — low levels and high levels. Error-free signal handling is thus ensured at the dynamic range extremes. Compression and expansion occur only at easy to handle mid-levels.

2

The system employs a simple adding and subtracting scheme which automatically results in mathematically exact complementary compression and expansion. There are no approximations, so the signal must come out the same as it went in (just get the Dolby Level right).

3

Compressor overshoots with high-level transient signals are suppressed without audible distortion, because of the basic system layout (dual signal paths). Since there are no overshoots to be clipped by the recorder, there is no impairment of even the most extreme transient signals.

4

The freedom from overshoot is a result of system philosophy, not an ultra-short attack time, so it is possible to utilize relatively gradual gain changes. This yields a compressor output which is remarkably free from modulation distortion. There is thus no need to depend upon cancellation of modulation products by the expander (which relaxes recorder performance requirements).

5

The reproduced dynamics of low-level signals are essentially immune to rumble in the input signal and head bumps and other frequency response errors in the recorder — the system has a solid low-level 'gain floor'.

6

The system gives a pre-determined amount of noise reduction which is realistically useful (set at 10 dB).

7

The noise that remains has a subjectively constant level. Noise modulation effects are almost non-existent.

8

The principles and parameters used in the Dolby system result in a high margin of safety. The system works well with all types of audio signals – speech, music, effects – and practically all types of noises. High noise levels (from multi-generation copies, for example) do not impair performance.

9

The system functions reliably on a day in, day out basis, with real workaday recorders and other equipment.

10

All of the above have been proved in ten years of dependable service to the industry – 25,000 professional channels in use by well over a thousand studios in more than 50 countries around the world.

The Dolby A-system now looks forward to

The Second Successful Decade: 1976~1986

Dolby Laboratories Inc 'Dolby' and the double-D symbol are trade marks of Dolby Laboratories Inc. 731 Sansome Street San Francisco CA 94111 Telephone (415) 392-0300 Telex 34409 Cable Dolbylabs

WW --- 083 FOR FURTHER DETAILS

346 Clapham Road London SW9 Telephone 01 - 720 1111 Telex 919109 Cable Dolbylabs London



NOW IS THE TIME TO BUY!

Our prices were **reduced** in April. Now VAT has been halved. Will things ever be quite this good again? Make use of your credit card and buy now with confidence.

We give full after-sales service and guarantee with all parts and kits.

If you have already purchased, why not add a

TOUCH-TUNE PRE-SELECT UNIT to your tuner

This is a separate unit, powered from the normal tuner supply, and designed as an alternative to the existing push button unit (K9a). It provides six pre-select channels while maintaining the manual control and frequency meter circuits. The pre-set pots (20 turn cermet types, of course) are accessible from the underside of the tuner without removing the cabinet, being mounted between the chassis and the front panel. The channel selected is indicated by L.E.D. lamps incorporated in the touch buttons, which replace the manual buttons without modification to chassis or front panel.



Send for full details and price list, etc. Or send 50p° for our new booklet fully describing our updated tuner. Refundable on order over £10

Con Desian

33 Restrop View Purton, WILTS. SN5 9DG

ELECTRONIC









Where else will you find for *£125:-

- * Dual trace, full portability
- * 10 MHz bandwidth, 10mV sensitivity
- * Time base 1 µs to 100ms in 16 steps
- * × 5 magnification, Trace Locate button

*UK List ex VAT

- * Trig Level and Polarity by one control
- * Bright, stable trace

For immediate attention write or telephone Scopex Instruments Ltd., Pixmore Industrial Estate, Letchworth, Herts. SG6 1JJ Tel: Letchworth (04626) 72771 An independent British Company

WW-074 FOR FURTHER DETAILS

Wayne Kerr's top-selling bridge



Meets modern requirements. Is accurate to 0.1%.

Is self-balancing. Has 2,3 and 4-terminal connections. Continuous readout of real and quadrature terms. Overall range 10 micro-ohms to 100 gigohms, 0.001pF to 10 farads, 1 nanohenry to 10 megahenrys and 10 picomhos to 100 kilomhos. Built-in source/detector (1592Hz).

Connectors for 200Hz – 20kHz manual operation.

Comparator facilities. Analog outputs. Adjustable sensitivity. Ask for B642 Data Sheet.

Wilmot Breeden Electronics Limited* Durban Road, South Bersted, Bognor Regis, West Sussex, PO22 9RL

Telephone: Bognor Regis (02433) 25811 Telex: 86120 Incorporating FERROGRAPH · RENDAR · WAYNE KERR WW – 016 FOR FURTHER DETAILS



Producing 30 basic types of relay and 15.000 variants with regard to contact stacks, terminals, energizing current and contact material, Zettler is among the largest manufacturers of electro-mechanical components.

Our product range comprises: Low profile (flatform) · Timing Miniature Low contact capacity · Herme-tically sealed · Stepping · Mains switching · Latching · Contact stacks · Solenoids

Flatform Relay AZ 535 for reliable insulation between signal and heavy duty circuits. 1 changeover. Contact material: Silver cadmium oxide, or fine silver.

Printed circuit mounting (32.5 x 20 x 11 mm). Coil voltages: 6 to 110 V DC. Contact rating: 240 V max., 3 A max., 500 VA.

We resolve your switching problems rapidly and expertly. Please contact us for further details.



WW-011 FOR FURTHER DETAILS



WW - 024 FOR FURTHER DETAILS

EQUIPMENT

| N N | • | |
|---|--------------------------------|---|
| FAST RESPONSE STR | P CHART | RECORDERS |
| Type H3020-1 Single pen | Type H3020-: Three-pen | 3 |
| Specification | Recording: | Syphon pen directly attached to moving coil frame, curvilinger on ordinates |
| Basic error. 2.5% Sensitivity 8mA F.S.D. Response 0.2 sec. Width of each channel 80mm Chart sneeds selected by | Equipment: Mar indi etc. | ker pen, Timerpen, Paper footage cator, 10 rolls of paper, connectors, |
| push buttons 0.1–0.2–0.5–1–2.5– –5–12.5–25mm/sec. Chart drive | Dimensions: | H320-1: 285x384x16.5mm H320-3: 475x384x16.5mm PRICE: H320-1 £108.00 H320-3 £160.00 |
| Available for immediat | te delivery | Exclusive of VAT |
| 7 & LAFRO SI | FRVICE | SITD |
| 44A WESTROURNE GR | | W2 5SF |
| Tel. 01-727 5641 | | Telex: 261306 |

WW - 004 FOR FURTHER DETAILS



WW - 013 FOR FURTHER DETAILS

www.americanradiohistory.com



WW - 021 FOR FURTHER DETAILS

www.americanradiohistory.com

WW - 020 FOR FURTHER DETAILS

25



The LR70/71 bulk erasers are currently used in Broadcast Companies, Recording Studios, Government Departments, Educational Establishments and the Computer Industry. *Moderately priced and available from*

LEEVERS-RICH EQUIPMENT LIMITED INCORP. BIAS ELECTRONICS 319 Trinity Road, Wandsworth, London SW18 3SL Telephone 01-874 9054 Cables: Leemag London SW18. Telex 923455 Wembley

WW-069 FOR FURTHER INFORMATION



Our reputation for professional soldering equipment has been built on our precision products, so we have taken extreme care to see that our new ORYX Super 30 iron at, date we repeat it, only £2.95, is going to be the best at its price.

* plus VAT at 8%

Here are some of the features you get as standard:

A neon Safety Light, A long life element, Iron coated screw-on tip, Stainless steel shaft, Styled handle,

A two-minute element change, and a Stainless steel clip-on hook. You can have further technical information, or by ordering one now you will see why we call it the Super 30.

differention actual size.

Greenwood Electronics

Greenwood Electronics Portman Road, Reading RG3 1NE Telephone 0734-595844 Telex 848659

WW - 007 FOR FURTHER DETAILS



D.M.W. ASSOCIATES (ELECTRONICS) 'LIMITED

applications is also available.

A comprehensive range of airborne and ground based Time Code Generators, Translators, and

Tape Search Units. The equipment is used in

conjunction with instrumentation and other types

of magnetic Tape Recorders, for efficient data acquisition and analysis. Manually operated equipment and fully computer controlled systems are available. The computer controlled systems include installation, commissioning and checkout software. A design service for special time code

Time code generators' translators, tape search systems with manual or computer control

High-power wideband linear amplifiers



A comprehensive range of wideband linear amplifier systems covering the frequency range 500 kHz-60 MHz is available. A wide range of power output is available by combination of basic modules. Hybrid couplers for power splitting and combining, sub-octave high power switched filters, and automatic aerial matching units are also available. The company also offers a design and development service for special systems.

HIGH SPEED VIDEO ANALOGUE TO DIGITAL AND DIGITAL TO ANALOGUE CONVERTERS AND SYSTEMS. VIDEO INSERTION UNITS



The third in a series of international expositions METROPOLE CONVENTION CENTRE BRIGHTON, ENGLAND 8 9 10 11 JUNE 1976 Organised by Tony Davie **RESEARCH AND** DEVELOPMENT FACILITIES · **COVERING A WIDE RANGE OF** TECHNOLOGY **DMW Associates (Electronics) Ltd** 6-8 Morris Road Royal Oak Industrial Estate Daventry, Northamptonshire Great Britain, NN11 5PD

Telephone: Daventry (032 72) 71472

STAND 160 COMMUNICATIONS



WW-042 FOR FURTHER DETAILS

26

Now the Alpha costs less than the A***** will the 1567 engineers who are still without one please identify themselves?

1000

1000

Digital Multimeter

Brightness

100

AL A

A ADVANCE

1000-

INSTRUMENT

100

IOMO

DC

It was two years ago that Alpha one was launched by Advance.

As a brand new concept in low cost digital multimeters.

Now, many thousands of instruments later, Alpha I and II are everywhere.

You, too, should claim your Alpha. And to help you, we're listing the advantages engineers of competing firms enjoy:

- ★ Low, low prices. Alpha I now costs only £49 and Alpha II is now only £57 including a mains power supply but excluding VAT.
- Extraordinary battery longevity. One PP9 lasts up to a year in an Alpha I.
- No backache. Alphas are small, light, but in a tough as blazes carrying case.
- ★ No problems reliability is superb with long periods between recalibration.
- ★ No squinting. Our LEDS give bright, clear, unambiguous readouts.

Do get the Gould Advance data on Alpha. You see, it's so much better.

Gould Advance Limited Roebuck Road, Hainault, Essex, England. Telephone: 01-500 1000 Telex: 263785



WW-049 FOR FURTHER DETAILS



28

Wireless World, June 1976

| IN |
|---------------------------------|
| |
| Deine |
| E1.55p E1.75p E1.95p |
| robust rubber in light |
| |
| LE ANO |
| 8.80 10.45 10.06 11.11 |
| |
| |
| ering at |
| at I |
| at I |
| at I |
| at I |
| |

Special Quantity Discounts Available For Radio Clubs, Retail Outlets, Distributors

BOSS INDÚSTRIAL MOULDINGS LTD Higgs Industrial Estate, 2 Herne Hill Road, London, SE24 DAU, England

ephone 01-737 2383 Telex 919693





Iso-Tip Cordless Soldering Iron

Ideal for factory, field servicing, laboratory or home, the Iso-Tip Cordless offers a great advance in soldering. It is completely portable, heats in 5 seconds and recharges automatically in its own stand.

The iso-Tip is powered by long-life nickel cadmium batteries giving tip performance up to 50 watts with a temperature of 370°C. Tips are available in five different sizes ranging from Micro to Heavy Duty to meet all soldering requirements.

Greenwood Electronics

Portman Rd, Reading RG3 1NE, England. Telephone: Reading (0734) 595844. Telex: 848659.

WW - 035 FOR FURTHER DETAILS

WAHE

www.americanradiohistory.com

A





No doubt about it our S22 portable 'scope is beautifully put together, from the compact and elegant case right down to the chassis where its three main circuits fan out giving easy access to the heart of the instrument.

Aesthetics apart, the S22 is a lightweight single-trace 5MHz oscilloscope designed for the travelling service engineer and offering high specification at a competitive price, including all the facilities of trigger selection plus a special TV mode giving auto lock on LINE and FRAME frequencies. Versatile too the S22 can be mains or battery powered, only we don't give you the option—we give you both, complete with internal rechargeable cells and charger. For 10MHz dual-trace requirements the Telequipment D32 is available, with a similar specification.

Interested? Then send today for the full colour leaflet describing both models.

TelequipmenT $\langle || \rangle$

Tektronix U.K. Limited, P.O. Box 69, Beaverton House, Harpenden, Herts. Tel: Harpenden 63141 Telex: 25559

Telequipment S 22 the truly portable portable

WW - 961 FOR FURTHER DETAILS

www.americanradiohistory.com

wireless world

Electronics, Television, Radio, Audio

JUNE 1976 Vol 82

No 1486

Contents

- 33 Myths and maths
- 34 Wireless across space by Tong B. Tang
- 39 News of the month
 New video recording system
 Eye direction recorder in Britain
 New tape format
- 42 Surround-sound decoders 1 by David Heller
- 47 Anti-phase or 180° phase-shift by S. W. Amos
- 48 Sixty years ago
- 49 Communication theory 3 by D. A. Bell
- 52 H.F. predictions. Literature received
- 53 Wireless World Teletext decoder 8 by J. F. Daniels
- 56 World of amateur radio
- 57 APRS preview
- 58 Letters to the editor The consultants Citizens' band in the UK?
 - Microprocessors oversold?
- 62 Low-noise, low-cost cassette deck 2 by J. L. Linsley Hood
- 66 Books received
- 67 Balunamp design nomogram by Andrew M. Stephenson
- 68 Announcements
- 69 Generation of equal-tempered pitches by Robert M. Youngson
- 70 **Circuit ideas** Class A power amplifier
- Wide-band Y amplifier
- 75 Broadcast's biggest by Pat Hawker
- 77 Electronics à Paris
- 79 New products
- 82 Real and imaginary by "Vector"
- 123 APPOINTMENTS VACANT
- 136 INDEX TO ADVERTISERS

Price 35p (Back numbers 50p, from Room 11, Dorset House, Stamford Street, London SEI 9LU.) Editorial & Advertising offices: Dorset House, Stamford Street, London SEI 9LU. Telephones: Editorial 01-261 8620; Advertising 01-261 8339. Telegrams/Telex, Wiworld Bisnespres 25137 London. Cables, "Ethaworld, London SE1." Subscription rates: 1 year: £7.00 UK and overseas (\$18.20 USA and Canada). Student rate: 1 year, £3.50' UK and overseas (\$9.10 USA and Canada) Distribution: 40 Bowling Green Lane, London EC1R 0NE, Telephone 01-837 3636. Subscriptions: Oakfield House, Perrymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Subscribers are requested to notify a change of address.

C IPC Business Press Ltd. 1976



Front cover is a reference to Dr Tang's article "Wireless across space," which examines the feasibility of communication with beings on planets of other stars (photographs by Richard Knox (stars) and AP (earth)).

IN OUR NEXT ISSUE

Video discs. A review of the current state of this area of development, with a look at the latest contender.

Wideband compander. A noise-reducing circuit for tape-recording which uses power law compansion and does not exhibit the

"breathing" effect.

Simple modem for a.p.t. tape recording. Design which overcomes amplitude variation on playback by using the frequency-modulated signal from a phase-locked-loop i.c.

SIXTY-SIXTH YEAR OF PUBLICATION





It makes sense to use the **United-Carr** Supply Service when you require smallerormixed quantities of any of the following:-

CINCH

Barrier terminal strips. Fanning strips. Marker strips. Printed circuit board edge connectors.

D Subminiatures. Multi way plugs and sockets.



Audio sockets. Group boards. Valve holders. Fuse holders. Battery connectors.

Electrical Components. Single and double pole' rocker switches. Mains and low voltage indicator lights. Plunger switches. Mains connector blocks. Automotive lamp holders. Metal and plastic Push on terminations. Fuse holders.

Industrial Fastenings. Tee nuts. DOTLOC single thread lock nuts. Lift the Dot fastenings. Turnbuttons. Plugs and grommets. components. Press studs.



Edge clips. Cable clips. Cover plates. Turnbuckles. Knob clips.

W buttons. Door catches. Cable straps. Metal and plastic components.

Separate catalogues are available for:-Electronic Components. Electrical Components & Industrial Fasteners.

Write or phone for your free copy, stating possible requirements.



32

CONSERVES YOUR CASH. No need to lock up capital in slow moving stocks.

SAVES TIME. Parts usually despatched by return. Orders phoned before midday are often on the way same day.

A PROTOTYPE SERVICE. Invaluable when assorted alternative experimental parts are required.

SOLVES BUFFER STOCK PROBLEMS. Eliminates need for heavy stock holding. Our stocks are at your immediate disposal.

SIMPLIFIES ORDERING. One transaction for a variety of parts saves bookkeeping and paper work.

NO ORDER TOO SMALL. Every enquiry is of equal importance and dealt with expeditiously.

Obviously Single Source Service can solve a lot of your day to day problems. As the first step get the relevant U-C S catalogue, which illustrates and describes hundreds of parts any of which you may want at any moment. Write, or better still phone 0602 328711.

So make United-Carr Supplies your SINGLE SOURCE for:-



United-Carr Supplies Ltd., 112 Station Road, Ilkeston, Derbyshire DE7 5LF Tel: Ilkeston 328711 (STD 0602 328711). Telex 377117 WW - 068 FOR FURTHER DETAILS

)

wireless world

Myths and maths

Why should scientists want to get in contact with possible intelligent beings in other solar systems? The author of "Wireless across space" in this issue does not set out to answer this question – he is writing a technical article. Yet the question is a legitimate one to ask. Much time, money and effort has been expended on this work. One answer could be in the "because it's there" category – the possibility exists, so we must take up the challenge. Another answer could be scientific curiosity. Science is part of university life – which is justified by education and passing on the culture – and science needs problems to work on. The psychologists might suggest that we have an inner wish to find life elsewhere: we are really seeking more evidence to demonstrate purpose and design in the universe, to reasure us that life on this planet is not just an isolated molecular accident.

Practical people will say these are specious answers. But when you try to find the basic motivation behind so much of our science and technology you find yourself among similar, apparently vague and mystical explanations. Technology, in particular, is supposed to serve the needs of man (such as for more communication channels). But the needs of man, beyond those of sheer survival, are largely generated by his visions of himself – in fact by myths. (Here "myths" is not intended to mean things that are not true, but expressions of ideas by which we act and live.)

Behind much of technology is the myth of human progress – that we are on some road that will eventually lead us to perfection if we work away hard enough at our gadgets. And there are also myths of perfection operating in the specialized areas of our progress. Take sound reproduction, for example. Frequency and phase response, harmonic and intermodulation distortion, signal-to-noise ratio and so on are ultimately all measurements – nothing more than meter deflections and points plotted on paper, symbols representing concepts. Yet those of us who feel we cannot rely on our own ears believe that if we make all the measurements absolutely right by sufficient expenditure of money and technical effort, the reproduced sound must necessarily be absolutely right also. This is an example of the myth of objectivity.

Technologists and scientists should always be aware that objectivity is a myth. It is so easy to fall into the trap of imagining that the laws of nature, of logic and mathematics somehow exist independently – that they existed before anyone was around to think them. As the eminent molecular biologist Jacques Monod points out in his book *Chance and Necessity*, the principle that objectivity is necessary for truth is in fact an ethical, and therefore wholly human, decision. Our myths and maths go hand in hand.

Deputy Editor: PHILIP DARRINGTON Phone 01-261 8435

Technical Editor: GEOFFREY SHORTER, B.Sc. Phone 01-261 8443

Assistant Editors: BILL ANDERTON, B.Sc Phone 01-261 8620 MIKE SAGIN Phone 01-261 8429

Production: D. R. BRAY

Advertisements: G. BENTON ROWELL (Manager)

KEVIN BURNAL Phone 01-261 8515

NÎGEL LITTERICK Phone 01-261 8037

O. BAILEY (Classified Advertisements) Phone 01-261 8508 or 01-261 8423

JOHN GIBBON (Make-up and copy) Phone 01-261 8353

IPC Electrical-Electronic Press Ltd Publisher: Gordon Henderson

Wireless across space

Communication with possible intelligent beings on planets of other stars

by Tong B. Tang, M. Tech

St John's College, Cambridge

When the Viking lander-orbiter spaceprobe reaches the planet Mars in July 1976 we may receive the first confirmation that life exists not only on Earth but on extra-terrestrial bodies as well. It is extremely unlikely, however, that we shall find *intelligent* life either there or on other planets in the solar system. On the other hand, it is statistically likely that among the 10¹¹ stars constituting our galaxy (the Milky Way) many have planets which are inhabited by intelligent beings of one form or another and at various levels of social and technological development.

As yet we know of no physical principle which suggests that space travel at speeds faster than light can be implemented. The distances between stars are enormous. The star nearest to the sun is 4.29 light-years away, a distance of a quarter of 1014 miles and nearly ten thousand times our distance from the outermost planet of the solar system. While interplanetary travel could be possible within fifty years, launching interstellar spacecraft, whether manned or unmanned, will at best be grossly inefficient, even after all the technological advances we can have been achieved. foresee

Communication by electromagnetic waves will remain the most convenient and fastest method of making contact between stars. It is also the cheapest, requiring only the expenditure of electrical power, granted that the antennae and associated electronics used for transmission and reception exist already. Using 1970s technology and prices, a ten-word telegram costs less than 10 pence if the antennae are 45 metres in diameter and 10 light-years apart ¹.

Extra-terrestrial civilisations could possess technology much more advanced than ours and make use of telecommunication means which we cannot implement (modulation and

Fig. 1. The radio telescope at Arecibo, Puerto Rico. The paraboloidal reflecting dish, 300m in diameter, is constructed within a natural valley in limestone mountains. The feed is supported 137m above ground by cables attached to three pillars. By moving the feed the telescope is made semi-steerable (at 1.42GHz, to any direction within 20° from the zenith).



demodulation of gravitational waves or neutrino beams, etc.) or cannot imagine. But they would understand that, while some civilisations on other planets could be still more advanced than themselves, some could be behind them. Counting from the dating of the earliest known fossils of living things on Earth, we have been evolving for three thousand million years, and radio technology has been with us for less than a hundred years. Hence, to maximise the chance of achieving contacts, as primitive a communication technique as possible should be used by civilisations; this I shall call the "principle of presumed modesty". That is, every civilisation in attempting communication will try to make things as easy as possible for the other side, irrespective of whether the other side is in fact very advanced, because it does not know beforehand one way or another. Assuming that everywhere technology develops in the same overall sequence², we need therefore consider only radio communication.

Feasibility of interstellar radio communication

Our first television broadcasts took place at Alexandra Palace, London, nearly forty years ago. Within a distance of twenty light-years of our sun there are about a hundred stars and star components. It is not absolutely impossible that they all possess planets, on which there are civilisations who have built radio receivers sensitive enough to pick up those television transmissions. The people who sent out the television programmes, may therefore expect at any time now "replies" from up to a hundred different directions in the sky!

Returning from such speculation, we now show that indeed we already possess radio equipment capable of maintaining point-to-point communication with a planet of another star. Its technological advancement need be no higher than ours. (If it is more advanced the issue does not arise at all.) There is a definite low-noise "window" for the reception of interstellar radio signals, in the microwave region from 1 to 10 GHz (u.h.f. to radar s.h.f.). The window is
determined on the low-frequency side by the onset of intense radio frequency cosmic radiation and on the high-frequency side by that of atmospheric thermal noise. As far as we are concerned, if the interstellar radio station is built on the moon, then the upper frequency limit will be extended to the infra-red, where absorption by dust and debris in the interstellar space begins to be serious. By the "principle of presumed modesty" we should ignore this possibility. Further, the atmospheres of planets where life has evolved to advanced forms must have similar constituents (oxygen and water vapours) and therefore similar noise characteristics.

We now derive an equation for the maximum range of radio communication. If the transmitting antenna radiates a total power P_1 over a bandwidth Δf in all directions with equal intensity, then from a distance *l* away the power received by an antenna of "effective" area A_2 will be

$$P_2 = P_1 A_2 / (4\pi l^2)$$

When l is of the order of interstellar distances, it is obvious that with reasonable values of P_1 and A_2 (reasonable by earthly standards), P_2 will be far too small to be detectable. However, the transmission can be beamed and made highly directional. If then a radio telescope with a parabolic reflector is used, there is a gain over the isotropic radiator of ³

$$G_1 = \pi^2 (d_1 / \lambda)^2$$

where d_1 is the diameter (aperture) of the reflector dish and λ the operating wavelength. (For simplicity it is assumed that it is radiating "uniformly", otherwise a numerical coefficient slightly less than 1 has to be included.)

Likewise, the receiving antenna will be a parabolic type and will have a gain G_2 . If its aperture d_2 is large, as should be the case, its effective area is close to the physical area:

$$A_2 = d_2^2 \pi / 4$$

If now P denotes the minimum detectable signal power at the receiver, and L the maximum range of communication, which we want to find, we can write

$$P = P_1 G_1 A_2 / (4L^2)$$

= $(\pi^2 / 4^2) d_1^2 d_2^2 P_1 / (L^2 \lambda^2)$
so that $L = \frac{\pi d_1 d_2}{4 \lambda} \sqrt{\frac{P_1}{P_1}}$

P will depend on the background and receiver internal noises, characterised as noise temperatures⁴. Without going into the details we can reasonably take *P* as 3.2×10^{-24} watts per hertz. Within the window mentioned earlier the interstellar background noise⁴ is nearly constant at 3.2×10^{-22} watts per hertz (except at a few specific frequencies like 1.42GHz). In addition, since the receiving radio telescope will be pointing towards a star, microwave-frequency radiation of the star will add to this noise. However, if the star is more than ten light-years away it will be quite negligible³⁰. By using masers or parametric amplifiers, and signal processing techniques such as time integration, frequency cross-correlation⁵ and phasor detection⁶, it is possible to dig out signals which are as much as 20dB weaker than this constant noise.

Now, let us assume the receiver passband has been adjusted to be the same as the signal bandwidth Δf so that P in watts is $(3.2 \times 10^{-24} \Delta f)$, with Δf in Hz. Take λ representatively as 10cm, corresponding to a frequency of 3GHz. Further, assume d_1 and d_2 both to be 300m, the same as the aperture of the Arecibo radio telescope (Fig. 1) which is the world's largest in operation at present, so that $G_1 = G_2 \approx 80$ dB. Then if P_1 is 0.25MW, the present limit in our technology, a little arithmetic will show that

 $L = 2 \times 10^4 / \sqrt{\Delta f}$ light-years

The interested reader can draw graphs of L against P_1 for various values of Δf .

at selected values of λ and ds. If one uses log-log scales they will be straight lines of slope -0.5.

It is seen at once that a larger L is obtained with a smaller Δf , though not quite proportionally. This is because f diminishes the background ک noise power. Δf is limited by the frequency stability of the local oscillators of the transmitter and receiver, as it must be larger than the frequency drift. Using state-of-the-art quartz crystal oscillators and phase-locked loop systems for subsequent frequency up-conversion, Δf can now be made as small as 0.1Hz on s.h.f. waves. If this value of Δf is adopted, L is more than sixty thousand light years. In other words, two Arecibo-class radio telescopes, placed almost anywhere in the galaxy, could maintain communication with each other.

Problems and solutions

Interstellar radio communication is not, however, without problems. The first few concern Δf . The maximum amount of information obtainable from a radio transmission lasting a period of time t is, in bits,⁷

 $I = \Delta f \cdot \log_2(1 + \alpha) \cdot t$ $\approx \Delta f \cdot \alpha \cdot t / \log_e 2$ $\approx (3/2) \Delta f \cdot \alpha \cdot t$

where α is the received message signal-to-noise-ratio and is assumed to be small. As an illustration, to send 3 megabits, which is the average amount of information contained in one book⁸, to be received up to points where α is 1, then if Δf is 0.1Hz time t will be nearly 8 months. Unless we merely want to transmit call signals, which are of low I and serve only to advertise our existence and that we send call signals, then the chosen Δf cannot be too small so that the transmission time t will be reasonable. Moreover, signals of low I may be mistaken to be not artifical but of natural origin 9. Here it is interesting to note that when the stellar objects called pulsars were first observed there were speculations that they were radio beacons for interstellar navigation but their emissions pulse with extremely regular periodicity and nothing else. The speculations did not last long.

Also, on the receiver side, the timeconstant of the passband determining filters is set to be $1/\pi \Delta f$. If Δf is very narrow the time τ_i required for a single signal recording (the "integration time") becomes inconveniently long, especially if the signal-to-noise-ratio is low.

More importantly, in the frequency domain, reducing Δf increases the total number of possible channels. Communication is achieved, of course, only if both the transmitter and the receiver are tuned to frequencies within the same channel. The trouble is that each side is ignorant of the other's choice of

Fig. 2. Earth's first message to the stars (from ref. 23). The first bit sent is at the upper right-hand corner. The sequence continues from right to left and down.



frequency before the contact. Within the 1 to 10 GHz window there will be nine thousand channels if Δf is 1MHz, but ninety thousand millions if it is 0.1Hz.

Fortunately, this problem of frequency compatibility seems to be tractable. Within that window there are particular frequencies which have special significance. Although each civilisation does not know beforehand how? the others think, to maximise the chance of contact each should in its planning converge on those points which can be identified by all the others; this has been referred to as the "principle of anti-cryptography".¹⁰ For us, the first such "watch frequency" to be so identified is the 1.42040575GHz spin-flip emission line of neutral hydrogen. As a physical property of matter, its value is universal and known by all other civilisations. Its significance comes from the observation that hydrogen is the most abundant element in the universe, so that it may be regarded as one fundamental constant of nature. However, for the same reason, it is unusually noisy. There has been a suggestion that its second harmonics (2.84GHz) should be chosen instead.¹¹ Also suggested ¹², later, are the 1.667358 GHz radio frequency line of the hydroxyl radical and two "naturally" derived frequencies in the "water hole"13 between it and the hydrogen line. (Water is composed of hydrogen and the hydroxyl radical, and it is most probably the basis of life anywhere in the universe.) All these frequencies lie near the low-frequency end of the window, an additional advantage since $L \propto 1/\lambda$.

There is an analogous problem in the time domain - the synchronisation of the transmitting and the receiving radio telescopes. As mentioned earlier, high gains on the telescopes, and therefore longer L, are obtained by making them highly directional. Hence, they are at one time transmitting or listening to only some small solid angles in the sky - in fact, $(4\pi/G)$ steradians, where G is the gain of the telescope concerned. (The whole sky extends by definition 4π steradians.) For communication to be achieved the two telescopes have to be in the same line of sight and pointing at each other. The probability of this happening by pure chance is $(1/G_1G_2)$. If G_1 and G_2 equal 80dB, it becomes 10^{-16} , an exceedingly small probability. (A field of view of $4\pi/10^8$ steradians is so narrow that generally at most one star lies in it.)

One solution is to reduce G_1 and G_2 , which however decreases L as well. Another solution is the simultaneous use of vast numbers of transmitting and receiving telescopes, pointing in different directions. Practical proposals are not lacking ¹⁴! Even if neither is feasible, the problem may still turn out to be solvable. In the same way that certain frequencies are special and, obviously to all, should be those used for interstellar communication, some astronomical phenomena in the galaxy may be suitably exploited as "time markers" and used for synchronisation purposes. One example is, for binary stars (two suns circling each other), the times when the two stars are nearest and farthest away ¹⁵. Another, I propose, is the occurrence of a supernova¹⁶ (a star "blowing up"; and this is, incidentally, the event responsible for the generation of the heavy chemical elements and the cosmic rays which in turn are requirements for the appearance and evolution of life.)

After the interstellar signals have been located, yet another problem is presented by the demodulation process. Which modulation method has been used by the transmitting civilisation? For reasons of simplicity and obviousness, the information must have been in binary form. According to one analysis¹⁰, the optimum binary modulation process (and by "the principle of presumed modesty" the one to be used) is by sense-switching of the circular polarisation of the radio waves. This means that the waves will be circularly polarised, in the clockwise and anticlockwise directions alternatively to represent 0 and 1. To use amplitude, frequency or phase modulation will be less efficient.

Assuming that we have got the message (as a sequence of 0s and 1s), we have to start decoding it into intelligent information. Much has been discussed about this subject of "interstellar cryptography". The information may be pictorial as was the first interstellar transmission by us (see later: Fig. 2). It may be more sophisticated and high-level, and it will not be so straightforward to interpret and translate into our own concepts. However, the transmitting and the receiving civilisations share quite a few things in common, irrespective of their differing systems of concepts (which in any case all reflect the same objective world). They are the message itself, the "same" understanding of physics (albeit with different "names,,' notations and unit systems), and the (universal) conception of arithmetic (counting one, two, three, etc.). A language of high expressional power can be defined, starting from

anradiohisto

them and nothing else. A long message. can consist of, in the first part, the construction of such a formalised syntactic language, followed then by "books". The reception and deciphering of such a message will have unimaginable effects.

Lastly, there are a few "tactical" problems. The transmitting and the receiving planets will be rotating as well as travelling in space, so that they are moving relative to each other. Hence, there will be a time-varving Doppler shift in the signal frequency, equal to the (varying) relative velocity divided by the speed of light. However, this can be eliminated easily if each side separately compensates for its contribution to the total shift, by using for example a phased frequency-scanned antenna system ¹⁷. Another problem is due to the, fact that interstellar space is not exactly a vacuum, so that dispersion of the radio signal occurs. The lower frequency components of the signal have slightly lower propagation velocities, resulting in distortion. However, with an unusually small Δf , it will not be serious unless the propagated distance. is very large (>10⁴ light-years).¹

The receiving system

Let us now consider the radio telescope receiving system (sometimes referred to as a "radiometer") in some detail. Its basic function is to amplify, within a specified bandwidth at a selected frequency, the signal-carrying electromagnetic waves collected by the telescope. After appropriate demodulation the signal drives an output recorder.

Its front end will consist of a lownoise pre-amplifier - inevitably a parametric amplifier or the more expensive liquid-helium cooled maser 18 - which is usually placed right in the telescope to reduce feeder transmission loss. (A discussion of "noise temperature" and front-end amplifiers can be found in reference 4.) To eliminate misleading outputs due to internal drift in the system characteristics, the input to the pre-amplifier is switched between the telescope feeder and a standard noise source. The pre-amp is followed by several stages of superheterodyning intermediate-frequency amplifier, and

| Investigator | Observatory | Frequencies | Targets |
|----------------------|---|----------------------------------|-----------------------------------|
| Troitsky | Eurasian network, USSR | 0 6, 1 and 1 875 GHz | Entire sky |
| Zuckerman. Palmer | Green Bank, USA | 1.420 GHz | Some 600 nearby sun-like stars |
| Kardashev | Eurasian network, USSR | Several | Entire sky |
| Bridle, Feldman | Algonquin Radio Observatory, Canada | 22.2 GHz | Several nearby stars |
| Drake, Sagan | Arecibo. Puerto Rico | 1.420, 1.653 and 2.380 GHz | \ Several nearby galaxies |

Fig. 3. Project Ozma receiving system schematic (adapted from National Radio Astronomy Observatory diagram).

then by the detector, which is synchronised to the pre-amp switching frequency, so that signals from the feeder which are pulsed at the same frequency will be demodulated but receiver noises etc, which are not will be ignored. An integrator comes after the detector stage. It averages the signal over an interval τ_i equal to its set time-constant, to give successive recordings. The root-mean-square deviation in a single recording is inversely proportional to $\sqrt{\tau_i} \Delta f$, so that a longer τ_i leads to more significant digits in the reading. In the search period, before the signal has been detected, square-law (energy) detectors are used. After the signal has been found, however, a coherent or homodyne detection method is used to retain the phase information. The recordings usually go through analogue-to-digital converters and then are stored on tapes, to be dumped into a computer later. Sometimes, signal processing processes such as frequencycorrelation are performed in real time immediately after the integrator, by a digital correlator¹⁹

The first attempt by mankind to listen for extra-terrestrial radio messages (Project Ozma) was made fifteen years ago.²⁰ In the last five years there were three more publicised searches.^{21, 22} Project Ozma used a telescope of d = 26metres, and searched at frequencies from 1.4202 to 1.4206GHz with Δf from 40 to 100Hz. The other three had dranging from 26 to 50 metres, frequencies at 1.420 and 0.927GHz, and Δf at various values from 13Hz to 2MHz. Results were all negative, which is hardly surprising as these efforts were on very small scale. Using the Arecibo radio telescope (d = 300m) the first radio signalling to other stars was carried out in 1974, just before the first man-made objects to leave the solar system would have left. (These were the Pioneer 10 and 11 space-probes, travelling more than a hundred thousand times slower than the radio signals.), The radio message²³ has 1,679 bits and therefore can be broken down into a two-dimensional picture in only two ways, either as 73×23 , or as 23×73 which is the intended one (Fig. 2). The frequency of transmission was 2.38GHz, Δf was 10Hz and the transmission time lasted 169 seconds. Binary frequency modulation was used, the effective average power was 3×10^{12} W, directed towards the Great Cluster in Hercules, a group of some 300,000 stars 2.4×10⁴ light-years[●] distant. The Doppler shifts in the signal frequencies due to motions on the Earth side had been continuously compensated.





Fig. 4. Multi-channel receiving system

The functional block diagram for the receiving system used in Project Ozma, which will be representative, is shown in Fig. 3. Two horn antennae are connected by waveguides to an electronic switch, and the signals from them are fed alternately to the pre-amplifier. They are placed above the telescope reflector dish, so that one "looks" effectively at the star of interest and the other at a point in the celestial sphere just next to it. The second horn serves as a comparison noise source. The detectors on the right-hand side of Fig. 3 respond only to signal pulses synchronised with the switching frequency. In this way receiver internal drifts, and terrestrial interferences which are collected by both horns, are eliminated, since they are not synchronised.

The quartz crystal oscillator for the first mixing stage is kept at a very stable temperature in an oven-within-oven, and has a frequency drift of less than 1Hz in IGHz. Its output is up-converted, in frequency to 1.39GHz by a phaselocked loop system.

After the fourth i.f. amplifier, two filters pick up one broad (0-200Hz) and one narrow (80-120Hz) band of signals. Their attenuations are in the ratio of 5 to 1, so that if the signals are broad-band their outputs are the same. In this case, the differencing circuit and thus the "interstellar signal channel" will have zero output. (The signal-band filter is shown as passing a Δf of 40Hz, but it can be easily and quickly re-adjusted and in the actual experiment Δf had varied from 40 to 100Hz.) Only when there are signals of bandwidth less than 200Hz will the filters' outputs be different. The other two outputs, shown as "comparison band" and "signal band," serve as checks on system performance.

The other receiving systems used in the search for extra-terrestrial radio messages are similar in construction, except that they are multi-channel so that a number of watch frequencies can be scanned simultaneously. Fig. 4 is a schematic of these systems. There is the radio telescope, and a standard reference source for noise comparison purpose. After going through the switch and the wide-band pre-amplifier, the signals pass several stages of mixers and i.f. amplifiers and are then selectively allowed through a number of pass-band defining filters. After detection and integration they are summed by nonlinear circuit elements and go to an output recorder. Multi-channel one-bit digital correlators²⁴ are also sometimes incorporated. Each channel can be searched individually, and the data from several adjacent channels can be combined to represent a wider channel without any loss of information or sensitivity.

(It may be interesting to compare the

Wireless World, June 1976

receiving systems just described with a home-made one operating at 0.2 and 0.45GHz and for less sophisticated purposes²⁵, which, while being much simpler, contains all the essential ideas.) To be continued

References

1. Drake, F.D., in Interstellar Communication: Scientific Perspective (ed. C. Ponnamperuma and A.G.W. Cameron), Houghton Mifflin (Boston; 1974).

2. Sagan, C., "Life beyond the Solar System" in Exobiology (ed. C. Ponnamperuma), North Holland (1972) p.473.

3. I.T.T. Reference Data for Radio Engineers (5th

ed.), H. W. Sams (New York, 1968) p.26-20. 4. Smith, K. L., "Noise – Confusion in more than one" Parts 3 and 4, Wireless World, vol. 81, pp.235-7 and 326-330 (1975).

5. Drake, F. D., in Current Aspects of Exobiology (ed. G. Mamikunian and M. H. Briggs), Pergamon (1965) p.323.

6. Golay, M. J. E., "Note on the probable character of intelligent radio signals from other planetary system", Proc. IRE, vol. 49, p.959 (1961). 7. ibid Ref. 3, p.38-15.

8. Shkovskii, I. S., and Sagan, C., Intelligent Life in the Universe, Holden-Day (1966) pp.427-8.

9. Slysh, V. L., "Radio astronomic artificiality criteria of radio sources" in Extraterrestrial Civilisations (ed. G. M. Tovmasyan), Israel Programme for Sci. Transl. (1967) pp.38-42.

10. Dixon, R.S., "A search strategy for finding extraterrestrial radio beacons". Icarus, vol. 20, pp.187-199 (1973).

11. von Hoerner, S., "The search for signals from other civilisations" in Interstellar Communication (ed. A. G. W. Cameron), Benjamin (1963) pp.272-286.

12. Drake, F. D., and Sagan, C., "Interstellar radio communication and the frequency selection problem", Nature, vol. 245, pp.257-8 (1973).

13. Oliver, B. M., in Communication with extraterrestrial intelligence (ed. Carl Sagan), M.I.T. Press (1973) pp.284-5.

14. for example, Gindilis, L. M. in Extraterrestrial Civilisations (ed. S. A. Kaplan), Israel Programme for Sci. Transl. (1971) p.68.

15. Pace, G. W., and Walker, J. C. G., "Time markers in interstellar communication", Nature, vol. 254, pp.400-1 (1973).

16. Tang, T. B., "Supernovae as time markers in interstellar communication", J. Br. Interplanet. Soc., 1976 July-Aug.

17. Dixon, R. S., "An isotropic frequency-independent antenna system for simultaneous omnidirec-tional Doppler shift removal", IEEE Trans. Antennas and Propagation, vol. 22, pp.707-9 (1974); Teich, M.C., "Doppler-independent selective heterodyne radiometry for detection of remote species", Rev. Sci. Instrum. vol. 46, pp.1313-1317 (1975)

18. Kollberg, E. L., "A Travelling-wave maser system for radio astronomy", Proc. IEEE, vol. 61, pp.1323-9 (1973).

19. Bowers, F. K., Whyte, D. A., Landecker, T. L., and Klingler, R. J., "A digital correlation spectrometer employing multiple-level quantisation", Proc. IEEE, vol. 61, pp.1339-1343 (1973).

20. Drake, F. D., "How can we detect radio transmissions from distant planetary systems?" in ibid ref. 9, pp.165-175; "Project Ozma", pp.176-7.

21. Troitskii, V. S., Starodubtsev, A. M., Gershtein, L. 1., and Rakhlin, V. L., "Search for monochromatic 927-MHz radio emission from nearby stars", Soviet Astron. - AJ. vol. 15, pp.508-510 (1971).

22. Verschuur, G. L., "A search for narrow band 21-cm wavelength signals from ten nearby stars, ' Icarus, vol. 19, pp.329-340 (1973); Zuckerman, B., "Ozma II", paper presented at US Commission V URSI Meeting, January 1973, Socorro, New Mexico. 23. The Staff at the National Astron. and Ionosphere Centre "The Arecibo message of

November 1974", Icarus, vol. 26 pp.462-6 (1975). 24. Ables, J. G., Cooper, B. F. C. Hunt, A. J. Moorey, G. G., and Brooks, J. W., "A 1024-channel digital correlator", Rev. Sci Instrum., vol. 46, pp.284-295 (1975).

25. Duncan, J. H., "Radio telescope project at Frensham Heights School", Wireless World, vol. 81, pp.289-290 (1975).



New video recording system

When is a video disc not a video disc? The multiplicity of answers to this question seemed to have escaped the organizers of Video Disc 76, a recently held conference in London. For by choosing this title, they automatically excluded at least one system from being presented that has equal, if not more, potential than the best disc systems announced so far. A question and answer period however allowed Mr Sarason Liebler, president of Digital Recording Corporation, to give a brief description which were later expounded to Wireless World (more details next issue).

The system is an optical one that can. store live colour television signals in digital form at a density of 300 million bits per square inch, a density that allows 30 minutes of TV programme to be stored on a 5 \times 7in record. Mr Liebler told Wireless World that for consumer TV playback large-scale production could bring manufacturing cost down to \$120 per unit, as only relatively inexpensive components were required. But a large consumer market was seen to be a long way off, and application is more likely to be in other areas such as archival information storage and retrieval, military situations, and professional areas where high signal-tonoise ratio and a high bit rate or density is desirable.

Material to be stored is converted to a digital code and written as a series of micron-sized dots (or bars) and spaces on a photosensitive plate. For playback, which can use the same unit as for recording, digital tracks are scanned by a light beam. The modulated beam is converted by photodetector and a conventional digital-to-analogue converter to reproduce the original information. Scanning is achieved by a spinning scanning head that has several apertures in its periphery. An optical distributor switches the light beam in such a way that the data at the end of one track are picked up at the start of the next track by the next aperture. It is the scanner that translates, the record remaining fixed.

Eye-direction recorder in Britain

Accurate "eye direction" recording has posed difficult problems for researchers trying to find a system in which the measurement process itself does not interfere with the normal activity of the subject. The "remote oculometer", demonstrated recently in London, is claimed by its designers, Honeywell Radiation Centre, to overcome this problem.

The oculometer, which is the result of 10 years' research at the company's laboratories Lexington. in Massachusetts, uses a beam of infra-red light, aimed at the subject's eye, to operate a special TV camera. This camera locates the position of the eye's corneal reflection, which moves within the pupil area according to the direction of the line of sight. A small computer translates the position of the corneal reflection into a precise "measure" representing the point at which the subject is looking. This measure can be recorded and/or displayed on a TV screen showing the fixation point within the viewed area.

Video tape recording showing a viewer's "eye fixation" on a TV commercial. The fixation point – shown as a white dot on the woman's mouth is superimposed on the screen by an oculometer computer.

There are two basic types of oculometer; one which requires the subject's eyes to stay within one cubic inch of space, and another which, using a two-axis moving mirror and a servo-driven focusing lens automatically controlled by the computer processor, allows movement within one cubic foot of space.

The oculometer, Honeywell says, can provide objective data in many applications such as training and evaluation of aircraft pilot or air-traffic controllers' skills, instrument panel design, driving and road safety research, design of TV commercial and other advertising copy, and reading analysis. The U.S. Air Force are presently using a cubic-foot unit for study into the use of eye control as an alternative to conventional hand control, and oculometers have been purchased by a variety of other research centres, armed forces and universities in both the States and Europe. Honeywell's own Systems and Research Centre uses an oculometer for analysing the viewing pattern of shoppers asked to watch a series of TV commercials, and also for the National Highway Traffic Safety Administration for a night-driving study of headlight effectiveness.

Post Office install electronic director

The first electronic 'director' equipment to be installed in a London telephone exchange is being tested under live traffic conditions. The original director equipment designed for London and other large cities in the 1920s, used Strowger two-motion selectors and





uniselectors to convert the three digits of the exchange code dialled by the subscriber into the necessary routing digits for directing the call across the particular city to the destination exchange. This equipment, which enabled a universal numbering scheme to be employed, has worked efficiently but does not provide some facilities now considered desirable by the Post office. Pye TMC was awarded a contract by the Post Office to design and develop a system which could not only replace the existing electromechanical equipment but would also incorporate additional facilities

The new equipment, designed using m.o.s. l.s.i. techniques, is much more compact and has a translation store of 2,000 individual routing instructions. Any or all of these can be electrically rewritten, providing for the routing of traffic to several hundred local exchanges, to the trunk network or the various information centres as desired. The translators are triplicated for reliability. An added advantage for the maintenance staff will be the reduced noise level in the exchange to improve working conditions.

The first production TXE4 exchange is now carrying public traffic. Between now and March 1980, the Post Office expects to spend about £330M on electronic exchanges at current price levels.

(As pointed out in "Centenary of the Telephone", March issue, the TXE4 is not fully electronic, relying on reed relays. See also "Electronic telephone exchanges", June, July 1974.) Final checking of the Pye TMC electronic director equipment (see news item) before delivery to the Post Office for field trials.

Touch for iron and steel

A touch-sensitive display is taking a role in the investigation of data processing systems and information display techniques being carried out by the British Steel Corporation. Under a contract received by Marconi Radar Systems Ltd, a Digilux touch-sensitive display unit and a television alphanumeric display are being supplied to the Control and Human Factors Department of the BSC's Corporate Engineering Laboratory. The Digilux will be used in conjunction with the laboratory computer; a PDP11/45, to evaluate data processing systems and programmes developed for specific steelworks applications one of which is the operator guidance system for 'basic oxygen' steelmaking control.

The planned experimental programme being carried out by the Corporation also incudes comparative evaluations of equipment and an investigation of the display parameters such as desirable contrast ratios, character size, alphanumeric data format design and techniques of graphical display. Digilux does not rely on physical contact between finger and a bare wire conductor but uses narrow infra-red beams to form an invisible grid over the display screen. At each of the intersection points a small stud is let into the screen and above each stud an item of data to serve as a label is written electronically on the tabular display screen. By touching the appropriate

Wireless World, June 1976

stud, two beams at right angles are intercepted and the data designated by the label is signalled to the computer. This data is then written on the screen and at the same time a new set of labels designating the next stage of information to be fed in, is written above the studs.

Cartridges to Tokyo

Goldring are feeling pleased with themselves as a result of a Japanese order for their new G900 pick-up cartridge. They first sold cartridges in Japan to Sony, with their 850 model, a derivative of the million-selling G800 series. But the 900 cartridge is a completely new design. Though the chemically-etched laminations of the pole shoe assembly, first introduced by Goldring in 1969, improved the mid-range droop of earlier cartridges, it still left a fairly heavy pick-up. The 900 uses the moving magnet technique enabling magnet size and weight to be reduced drastically, resulting in a cartridge weighing only 5gm. The cantilever stylus support has also been reduced in weight - the tube wall measures 0.9 "thou" - and a smaller diamond tip is used. Tip mass is said to be 0.32mg. The coil and pole shoe assembly is also improved with finer laminations and a coil construction technique that avoids the usual bobbin former; inductance of the pick-up is 640mH at 1kHz and 630mH at 10kHz. Droop at 5-10kHz is kept to within -1dB, giving an overall response of 20Hz to 20kHz ± 2 dB.

Local radio for the army

The Ministry of Defence is purchasing a mobile sound broadcasting facility which will enable the British Army deployed anywhere in the world to provide a local radio service of general interest and current news content. Two medium wave sound broadcasting transmitters together with studio equipment, h.f. receivers, antenna arrays, a demountable mast, an aerial tuning unit and a range of associated test equipment are being supplied by Marconi Communication Systems Ltd. All of this equipment is to be mounted in two Army containers so that the resultant station can be transported by air by Support Command to any destination and brought into operation at short notice.

One of the containers will be fitted with two Marconi type B6023 1kW m.f., sound broadcast transmitters with a paralleling unit to provide 2kW of power. This container will also hold the drive units which will provide the choice of either crystal oscillator or synthesizer frequency control and a patching panel. The second container will function as the sound broadcasting studio and will be fitted with a

12-channel sound mixer, microphones, disc reproducers, tape recorders and sound monitoring equipment. A separate compartment within this container will mount h.f. receivers operating in space diversity to enable overseas broadcasts to be received and re-transmitted as required.

I²L in volume

Claimed to be the first European based volume production facility for I²L devices, a facility of ITT Semiconductors at Footscray is approaching a production rate of one million devices per year. At this time, a significant proportion of these devices are for use in digital watch applications where the significant reduction in package size coupled with the capability to directly drive l.e.d. displays give I²L devices advantages over other comparable processes for certain applications. These advantages have potential for other applications and sample products are being evaluated by manufacturers inthe telecommunications, TV, control systems and automotive markets. ITT inform us that development is now well advanced on a new range of consumer time pieces which use new circuit and packaging design techniques.

New tape format

A consortium of Japanese manufacturers consisting of Sony, Matsushita and Teac have announced a new tape format. Called the Elcaset, it consists of a tape cassette containing ¼in tape in a plastics housing of similar appearance to a compact cassette. Designed to run at a speed of 9.5cm/s, the Elcaset is a contender in the professional recording field alongside the BASF Unisette.

The principle difference between this new cassette and its competitor is that the tape is removed in a large loop by the recorder, thus isolating the cassette reel friction from the section of tape passing across the tape heads. Additionally, the track configuration allows for four conventional tracks and two control tracks down the centre of the tape. These control tracks can be used, one in each direction of tape travel, to carry synchronizing pulses for slide projectors, pilot-tone for film projectors, or a numeric code enabling selection of recorded items to be made using a programmable control unit. Automatic selection of bias and equalization is provided for three types of tape, by moulded lugs on the rear edge of the cassette.

Subsequent to the initial announcement, Aiwa and Victor (JVC) also announced agreement to adopt the format. The first machines using this format are expected to appear in the winter of 1976.



Artificially produced showers are among the extreme stress conditions to which Siemens communications equipment is subjected for environmental testing.

Underwater inspection completed

An unmanned undersea inspection vehicle has completed a visual examination of the massive new Brent Spar oil storage and loading buoy for Shell UK Exploration and Production. The vehicle, equipped with colour and black and white television and stereo still cameras, inspected parts of the Spar Buoy in 25 hours of underwater operation. The buoy, whose underwater structures extend 109m below the surface of the sea, is 29m in diameter and can contain 320,000 barrels of oil. A British Aircraft Corporation team operated Consub 1 from a barge tethered alongside the structure. All areas were illuminated by lamps on Consub and real time television pictures were relayed and recorded on videotape at the operator's console on the barge for assessment by engineers.

Broadcasting Convention 1976

The organizers of the biennial International Broadcasting Convention 76 to be held at Grosvenor House, London from September 20 to 24, have announced an excellent response to the call for papers. More than sixty papers by leading experts around the world will be presented during the fourteen sessions of the technical programme. They cover new techniques, systems, developments and trends which will be of interest to engineers concerned with all aspects of broadcasting.

In addition to conventional broadcasting techniques there will be two sessions concerned with new information systems utilising the domestic television receiver for information display. Papers will be presented on Teletext, Viewdata and Text Television. the experimental system of NHK in Japan. A special session will highlight 'Electronic Journalism' using lightweight camera, recording and transmission equipment specially designed for this purpose and now being produced by many manufacturers for increasing use around the world to cover new events for television. The exhibition at IBC 76 at which leading manufacturers will display and demonstrate an extensive range of professional broadcasting equipment will complement the technical sessions and enable delegates to get up-to-date information and firsthand experience of the latest equipment. Over 2000 delegates from 44 countries attended IBC 74.

Marine electronics conference

The Society of Electronic and Radio Technicians, in association with the Institution of Electrical and Electronic Technician Engineers, has organised a three-day symposium on marine electronics at the University of Southampton. The symposium, which is to be held from 5th to 8th July, covers five sessions. The first session will deal with maritime communications and will include papers on ships' aerials, speech processing for high frequency communications and satellite communications. Other sessions will deal with navigation and radar, automation and computers, education, training and future developments of marine electronics, and safety at sea. Eighteen papers are to be presented, the authors being drawn from marine companies, manufacturing companies, government departments and corporations, shipping industries, shipbuilders and colleges. In addition to the papers, technical visits will be arranged and a full social programme is planned. Registration fee is £68 plus 8% v.a.t. (£50 plus v.a.t. for members inclusive of attendance, board and the volume of published papers. Amongst the chairmen are Sir Edward Fennessy, managing director of telecommunications at the Post Office, Air Commodore Alec Morris, Director of Signals (Air), Ministry of Defence, R. M. Billington, Maritime Radio Services at the Post Office, and Col. J. D. Parker, Secretary General, C.I.R.M.

Briefly

Approval for calibration centre. The MSL Calibration Centre of Hunting Gate, Hitchin, Hertfordshire has been approved by the British Calibration Service.

Surround-sound decoders -

System details and circuit description of CD-4 demodulator

by David Heller, B.Sc.(Eng)

42

The Compatible Discrete 4 system (CD-4) was introduced in 1970 by the Victor Company of Japan. As its name implies, it was developed to allow four separate signals to be recorded on a disc record, at the same time having playback capability in stereo and mono when played through existing equipment.

A CD-4 record is cut in the familiar stereo format. Each of the two groove walls are cut at a 45° angle with the disc surface and at a 90° angle with respect to each other. Conventionally, the inner wall closest to the record centre is recorded with the left channel information. Modulation of the walls is perpendicular to their surfaces and, because of their 90° relationship, can be traced by a pickup to produce independent electrical outputs that correspond to the undulations of the wall.

Two signals are recorded on each wall side of the CD-4 disc: a sum signal, L_F + L_B occupying the base band up to 15kHz, and a difference signal, $L_F - L_B$, modulated onto a 30kHz carrier. This last-mentioned signal occupies the 20 to 45 kHz band.

If a CD-4 disc is played on a normal two-channel stereo system, only the sum signal is detected. Information contained in either the left or the right channel is processed and appears in either the left or the right channel as a normal stereo disc. To obtain four audio channels from a CD-4 disc, a high frequency pickup and demodulator are required to recover the f.m. signals and thus obtain the difference signals. By combining these with the sum signals, four independent audio signals are obtained. Although the encode/decode principle used in the CD-4 system is basically simple, certain refinements have to be used in the difference signal processing to ensure that the signalto-noise ratio is not substantially degraded over that obtainable in a normal stereo disc system.

Recording system

Fig. 1 is a block diagram of a CD-4 recording system. Four independent signals are fed into the input matrix amplifiers. The sum signal, delayed by

about $40\mu s$ to compensate for the delay of the difference signal during replay, is passed to the RIAA equalizer.

Before modulating the carrier, the difference signal is compressed and emphasized. To understand why this processing takes place it is necessary to explain two major sources of difficulty encountered in the difference signal path. Noise in the difference signal is caused because the wavelength of the modulated carrier is so short that the ratio of record particle size to wavelength is no longer negligible, and with angle modulation the noise spectrum corresponds with the particular modulation curve used. Angle modulation has a number of unique characteristics. In a frequency modulated signal, the noise density or noise power per unit bandwidth increases as the modulation frequency increases. Carrier deviation caused by the noise at a particular modulating frequency is directly proportional to that frequency. Theory and experimental evidence show that noise from an f.m. signal is greater at the upper frequency end of the sonic spectrum. However, noise from a phase modulated signal is flat throughout the sonic spectrum. Experiments using the best record material available were undertaken by JVC to derive the noise spectrum, and Fig. 2 shows both the theoretical and experimentally-obtained noise spectra; in the frequency range above 2kHz the signal-to-noise ratio and dynamic range are reduced.

Crosstalk occurs between the two modulated signals recorded on the two walls of a 45-45 record groove. It is impossible to entirely eliminate crosstalk between the two channels, but it is possible to minimize it. With modulated carrier systems, crosstalk causes beats between channels on playback and distortion of the sound because of leakage. To minimize this, the fre-quency and phase of the left and right-channel carriers must be the same and to prevent distortion due to leakage, the modulation index should be no greater than 1.9. The choice of the modulation index is, however, a compromise. Fig. 3 shows the frequency spectrum of several modulated signals

www.americanradiohis

for various values of the modulation index (m). For signals in the middle and low frequency ranges, the spectrum is mostly within the range 30 ± 1 kHz. As the frequency increases above 1kHz, the spectrum becomes wider. To ensure that 95% of the energy falls within the frequency limits shown in Fig. 3, it is necessary that the value of m be greater than 1.9 at frequencies lower than 500Hz.

Distortion due to signal leakage depends on the amount of crosstalk and the modulation index. The larger the index and crosstalk, the greater the distortion and, if the signal leakage is the same in both directions, the crosstalk signal leaking from channel A to channel B will be identical in size and spectrum to the signal leaking from channel B to channel A. Distortion becomes significant at frequencies below 500Hz where the modulation index is greater than 1.9. Crosstalk distortion peaks at around '700Hz, as shown in Fig. 4.

A frequency-dependent compression-expansion system reduces interference caused by noise and crosstalk. As distortion caused by crosstalk peaks at about 700Hz, while noise from the f.m. signal starts rising at about 2kHz, the noise reduction system is designed to operate over two frequency bands. In addition, the difference signal is phase modulated over a proportion of its frequency band to minimize noise.

The noise reduction system consists of a compressor in the recording system and a complementary expander in the playback system. To function effectively, it must automatically emphasize low-level signals at about 700Hz and over 2kHz in the recording mode and de-emphasize them by exactly the same amount in the playback mode. Figs 5 and 6 show the compression-expansion level and the frequency versus input level characteristics. The curves are generated by a compressor based on a two-band scheme, with a band-pass filter having 3dB corner frequencies at 200Hz and 2kHz, and a high-pass filter with a 3dB corner frequency at 2kHz.

Response time of the compressor is chosen to make the noise improvement



licant

43

control changes the carrier level accordingly, operating from advance heads on the master tape recorder.

The base-band signal and the carrier signal are then added together in the mixer. At this stage, the shapes of the resultant waveform are predistorted to compensate for the distortion resulting from the tracing of the base band interfering with the tracing of the carrier, which would otherwise degrade the sound quality and channel separation (Neutrex).

Incidentally, because of the restricted frequency range of disc cutting equipment, the composite signal is formed at half frequency to allow half-speed disc cutting.

Circuit description

The demodulator is designed around an integrated circuit, QSI5022. Designed by Quadracast Systems Inc and manufactured by Signetics, it was chosen as it houses all the required functions, including preamplifier. Fig. 8 gives a block diagram of the workings of a complete side of one demodulator. The signal entering via the cartridge is fed to a pre-amplifier and is either RIAA compensated (for a magnetic cartridge) or is amplified at a constant level over the whole frequency range (for a semi-conductor cartridge). In addition, provision is made to use the pre-amp as a buffer/amplifier to accept tuner, tape and auxiliary inputs. The base-band signal is filtered (low pass) and passed to the output matrix. The carrier signal is fed to a bandpass filter and demodulated. The 30kHz carrier is filtered out of the demodulated signal and the resultant signal de-emphasized and then expanded to compensate for the compression which took place during cutting. This difference signal is now added and subtracted from the sum signal in the matrix to produce the resultant back and front signals.



arrangement as inaudible as possible during the automatic gain adjustments. At 630Hz, the rise time is specified at 5 μ s when the level is increased in a jump from -30 to -10dB and the restoration time is 100 μ s for the reverse transition. Above 2kHz, the rise time is decreased to C μ s for a step level change from -40 to -10dB and restoration time is 10 μ s.

Carrier deviation caused by the noise at a particular modulating frequency is directly proportional to that frequency. Consider a signal pre-emphasized with the characteristic of Fig. 7 and then used to angle modulate a carrier. The pre-emphasized signal is kept flat until 800Hz, boosted by 6dB per octave between 800Hz and 6kHz and flattened out thereafter. The total pre-emphasis operates over a range of a little less than three octaves, giving a total boost of 17.5dB.

When this pre-emphasized signal is used to angle modulate the carrier, the carrier is frequency modulated up to 800Hz. Frequency modulation is again resumed from 6kHz upwards. Between 800Hz and 6kHz, frequency modulation is carried out with a linear frequency boost – i.e. phase modulation. In a frequency modulated scheme, phase deviation decreases inversely with modulating frequencies. The same Fig. 7. Static pre-emphasis scheme giving a combination of frequency and phase modulation.

amplitude signal at 2kHz will phase deviate the carrier half as far as a 1kHz signal. If the pre-emphasis counteracts this decrease by a corresponding rise in its amplitude, the phase deviation will be independent of frequency and will only depend on the modulating amplitude. Phase modulation gives excellent signal-to-noise performance at the higher frequencies since any increase in phase deviation is not accompanied by increase in noise.

The difference signal now modulates the carrier, chosen to be 19dB lower than the sum signal reference level to minimize interference between the frequency bands and to ensure cartridge pick-up trackability on replay.

If the high frequency end of the sum signal is large, mistracking of the pickup results, reducing the detected carrier level and raising the susceptibility to interference and noise. To compensate for this, an automatic level

Fig. 8. Block diagram of one channel of CD-4 decoder.



w americanradiohistory co

Preamplifier. The preamplifier, shown within the i.c. in Fig. 10, has antiphase outputs (pins 23 & 24). Its d.c. bias is determined by feedback from the noninverting output through R_4 and R_5 , back to the preamplifier input at pin 25. The ratio of R_4 and R_5 is chosen to ensure that both of the output voltages sit at about 6 volts for a 13-volt supply rail. Components $R_7,\ R_8,\ C_3$ and C_4 determine the RIAA playback characteristic. The demodulated carrier signal is constant for any cartridge as it is a function of carrier deviation and not carrier amplitude. The baseband signal level will, however, vary from cartridge to cartridge. To add and subtract the baseband and demodulated carrier signals correctly, a variable gain is therefore necessary to adjust the gain of the baseband signal, and potentiometer R_9 allows the gain to be changed. Values chosen for R_9 and R_{10} allow the preamplifier to accommodate inputs from 0.7mV r.m.s to about 15mV r.m.s.

A magnetic cartridge can be a.c.coupled to the input of the pre-amplifier by a capacitor but a semiconductor cartridge requires bias current. The Technics 450C or 451C cartridge requires 4mA bias current, and R_{41} and R_{141} supply this current while C_{38} filters out any hum. Components C_{33} and R_{40} form a network to maintain the proper direct voltage across the input capacitor, and R_2 matches the cartridge to the amplifier.

Fig. 9. Right-channel circuitry using QSI i.c. Circuit shown in broken lines is included in one channel only. Bandpass filter circuit, and component values will be given in part 2. Earth input socket at power supply. Point marked X is connected directly to pin 24 in right channel.



The non-inverting output is from a class A stage designed to drive the 15kHz low-pass filter, while the inverting output is a class B output stage, designed to drive the 15kHz low-pass filter and the 30kHz band-pass filter. The band-pass filter is matched by R₁₁. On the left side only, the non-inverting output is used for magnetic cartridge playback. The inverting pin is used for semiconductor cartridge playback. This is required because the left channel of a semiconductor cartridge needs phase inversion to be in proper phase relative to the right channel.

In addition, the preamplifier is used as a buffer amplifier for tape, tuner and auxiliary inputs. In this mode a flat feedback characteristic is applied by switching S_{3a} and S_{3b} to its open-circuit position, making R_9 and R_{109} gain controls ineffective, and by closing switches S_{3c} and S_{3d} thus applying a flat feedback characteristic to the preamplifier. A voltage gain of two occurs in this mode. Output is taken from the non-inverting output at pin 24 via R_{54} and C_{61} .

Limiter. The limiter's function is to provide a constant amplitude carrier to the demodulator and reduce the spike noise and amplitude modulation on the carrier. Components R₁₅, R₁₆ and C₁₄ determine the d.c. bias of the limiter; R_{14} is a matching load for the band-pass filter, coupled via C_{13} and the bias feed. To reduce sum signal interference, C₁₃ is chosen to allow maximum gain for the carrier signal but minimum gain for the sum signal. Components C₅ and R₁₂ determine the overall gain of the limiter. The value of 20 ohms chosen gives a gain of approximately 50dB for this stage.

Phase-locked loop demodulator. Pins 18 and 19 of the phase detector and pins 15, 16 and 17 of the voltage controlled oscillator form the phase-locked loop circuit used for demodulation of the difference signal. The carrier signal from the limiter is fed into the phase detector along with the v.c.o. signal, and the product of these two signals appears at the filter terminals, pins 18 and 19. The filter performs three functions:

- it maintains a large d.c. tracking range for turntable speed variations
- -it controls the a.c. tracking range for optimum audio pass band
- -it reduces carrier feed through to the v.c.o., thus increasing interference rejection.

Resistor R₁₃ determines the a.c. tracking range and, together with C₆ forms a 15kHz low-pass filter for carrier rejection. Varying the carrier input level to the phase detector or altering the value of R₁₃ and C₆ varies audio passband response. Capacitor C₁₅ is the v.c.o. timing capacitor, the value of which changes v.c.o. sensitivity or the audio output level. The only alignment required for the system is the v.c.o. adjustment. This can be done by adjusting the v.c.o. free-running frequency to 30kHz with pin 22 a.c.-shorted to ground.

Carrier level detector. With proper carrier level output of the limiter and the phase-locked loop locked to the carrier, the carrier level detector will unmute the difference sub-channel. Attack and release time is controlled by C₁₉ of the mute. It is advisable in practice to connect pin 14 to the supply rail by a resistor R_{51} . This is not always required and depends on the batch of i.c.s produced. Using a value of $560k\Omega$, the detector should unmute automatically if a 30kHz carrier is present. The four-channel indicator drive is designed to drive an l.e.d. at a maximum of 25mA. Series resistors R₂₆ and R₁₂₆ minimize power dissipation in the i.c. The limiter gain and the preamplifier gain chosen allow the carrier level detector to unmute when the carrier input level is approximately 50µV.

Difference sub-channel mute. This consists of a gated amplifier with the gate control for the difference subchannel mute coming from the carrier level detector. The amplifier serves the additional purpose of level matching between the phase-locked loop demodulator, the expander and de-emphasis. Components C_{21} , R_{25} and R_{27} determine the correction required for de-emphasis. Audio to the mute input arrives from the 15kHz low-pass active filter via filter matching resistor R_{24} and C_{20}

Expander. The expander consists of two a.c.-d.c. convertors, two transductor inversion amplifiers (t.i.a.) and two gain control transconductance amplifiers (t.a.). One of each is used in the mid-band expander and the high-band expander. The system operates over two bands and expands according to the characteristics given in Fig. 5. Values of the external components are chosen for complementing the compressor curves. Parts used here are C27 for the high band with L_5 and C_{28} for the mid-range. The expander characteristics obtained are within $\pm 3dB$ of the standard values stipulated by JVC.

Sum signal mute. Pin 24 of the preamplifier feeds the sum signal into a low-pass filter. This filter has exactly the same amplitude and phase characteristics as the low-pass filter placed in the difference signal channel. A sum channel mute (pins 9 and 10) is incorporated in the i.c. to facilitate the use of semiconductor cartridges. These cartridges when used with automatic turntables are likely to give a large spike into the preamplifier, when lifting off the record. The mute circuit detects this spike before it passes through the sum channel and turns the sum signal off.

radiohis

When the cathode of D_1 or D_{101} is earthed, C_{35} discharges to 0.75 volts, thus muting the sum signal. The difference signal will already be muted by the loss of the carrier. When the cathode potential of D_1 or D_{101} is lifted, C_{35} is charged by approximately 100µA. When C_{35} is at about 1.4 volts, the sum channels unmute and the signals pass normally. The value of C_{35} is chosen for a delay long enough to allow the preamplifier to stabilize again.

Matrix amplifier. The matrix amplifiers recombine the difference signal and the sum signal to form the original front and back signals of a four-channel system. Output level is approximately 300mV r.m.s. for a 0dB (150mV) output from the preamplifier. Amplifier outputs at pins 6 and 7 are then fed into a second pole of a low-pass filter.

Reference supply. Pin 27 is a reference supply output from the i.c. This gives a voltage of around 5.8V which is used throughout the i.c. for reference and power purposes. The supply is filtered by C_{49} Resistors R_1 , R_{29} , R_{31} , R_{33} and R_{35} supply the appropriate circuits.

Filter requirements. The demodulator requires three filters for each i.c. There are two low-pass filters and a band-pass filter. It is essential that the low-pass filters should have a linear-phase response, i.e. a constant delay, and a flat amplitude characteristic to 15kHz. The two low-pass filters should be identical in all respects. The five-pole Butterworth active filter shown in part 2 is used but is split up so that the latter poles appear at the output of the demodulator, thus saving duplication. When a CD-4 disc is cut, the sum signal is delayed with respect to the difference signal. On playback, the difference signal is delayed with respect to the sum signal as it passes through the cartridge system. There are additional delays through the difference channel of the demodulator. In particular, the bandpass filter is designed to have an almost constant delay over its pass band so that the delays during the encoding/decoding process in both the sum channel and the difference channel cancel. The delay of the band-pass filter system shown in the second article is $32\mu s$ for signals between 18 and 45kHz.

Part 2 will give constructional details and performance using various pickup cartridges. A kit of parts for this and other decoder designs to be described subsequently is available from Compcor Electronics Ltd, 9 Dell Way, London W13 8JH. (See advertisement).

Antiphase or 180° phase shift?

A clarification

by S. W. Amos, B.Sc., M.I.E.E.

The 180° phase difference between the signals at the base and the collector of a common-emitter amplifier is well known. Indeed many of us have been aware of it for as long as we can remember; originally, of course, we knew it as the 180° phase difference between the signal voltages at the grid and anode of a valve, but the principle is the same. It is not surprising therefore that an engineer once designed a piece of electronic equipment in which the fundamental mode of operation depended on this phase difference. The equipment did not work and at the ensuing post mortem it was discovered that a common-emitter amplifier does not introduce 180° phase shift: instead it inverts the input signal and this is a fundamentally-different process.

Fig. 1 illustrates the difference. The waveform chosen for this illustration is a sine wave together with some second harmonic. The effect of adding the harmonic is to exaggerate the peak of one half cycle of the sine wave and to flatten the peak of the other so that it is possible to distinguish one half cycle from the other. Fig. 1 shows the effect of phase shifting this signal by 180° and of inverting it. The two results are quite dissimilar waveforms showing that the two processes are fundamentally differ-



Fig. 1. The effect on an assymmetrical waveform (a), of phase-shifting it by 180° (b), and inverting it (c). Note that (b) and (c) are different.



Fig. 2. The effect on a symmetrical waveform (a), of phase-shifting it by 180° (b), and inverting it (c). Note that (b) and (c) are the same.

ent. To facilitate comparison of the waveforms any increase in amplitude due to amplification has been ignored in this diagram and all the waveforms are shown with equal amplitudes. What has caused the confusion between 180° phase shifting and inversion is that, for a waveform which is symmetrical about the time axis, the effects give identical results; this is illustrated in Fig. 2 for a sine wave.

It is surprising that the myth of the 180° phase shift introduced by a transistor or valve should ever have gained credence. The only way of introducing phase shift is by the use of combinations of reactance and resistance e.g. capacitance and resistance or inductance and resistance. An ideal transistor or valve certainly contains resistance but it has no capacitance or inductance and cannot possibly therefore introduce any phase shift. All it can do is to invert the input signal and this has nothing to do with phase shift. In fact the term "antiphase" is a little unfortunate because it suggests that the process of inverting a signal has some

connection with phase. "Signal inversion" might be a better phrase than "antiphase".

To summarise then, for a wave symmetrical about the time axis the effects of 180° phase shift and of signal inversion are indistinguishable; for an asymmetric wave the two processes give quite different results.

These considerations are of importance in the design of an oscillator which can be regarded in general as a combination of a maintaining amplifier and a frequency-determining network as shown in Fig. 3. The requirements to be satisfied for oscillation to occur are: (a) that at the frequency of oscillation the frequency-determining network must introduce signal inversion which, with the inversion in the maintaining amplifier, gives the overall positive feedback which is essential for oscillation and (b) that the gain of the maintaining amplifier must exceed any attenuation in the frequency-determining network at the frequency of oscillation.



Fig. 3. A fundamental block diagram for an oscillator.



Fig. 4. A simple method of obtaining signal inversion using a tapped inductor.





Fig. 5. A Hartley oscillator.



Fig. 6. An astable multivibrator circuit drawn in the conventional manner.



Fig. 7. The circuit of Fig. 6 re-arranged to show that it agrees with the basic form of the oscillator (Fig. 3).



Fig. 8. An oscillator which relies on phase shift in the R-C filter for its operation.

The frequency-determining network must then give signal inversion at the oscillation frequency. One simple way of achieving signal inversion is by the use of a tapped inductor as shown in Fig. 4 and this can be tuned by a parallel-connected capacitor to give operation at a particular wanted frequency. By adding a common-emitter circuit as maintaining amplifier we obtain the familiar circuit of the Hartley oscillator shown in Fig. 5. In a similar way, by tapping the capacitive branch of a resonant circuit to obtain signal inversion, the Colpitts' oscillator circuit can be derived.

Any type of frequency-determining network can be used, and oscillation will result, provided the two conditions set out above are fulfilled. Thus a common-emitter amplifier can be used as a frequency-determining network. It introduces the necessary signal inversion but there is no attenuation. Instead there is usually considerable voltage and current gain at the frequency of operation and this, together with the gain of the maintaining amplifier, means that there is an excess of positive feedback - far more than is necessary just to sustain oscillation. As a result the oscillation amplitude grows rapidly until it is limited on one extreme by collector-current cut off and on the other extreme by the collector voltage falling to base potential and so applying a low-resistance shunt across the circuit. In other words this particular oscillator generates rectangular waves; it is, of course, a multivibrator and because of the symmetry of the circuit either transistor can be regarded as the maintaining amplifier or frequency determining network. The circuit diagram is shown in its familiar form in Fig. 6 but if it is recast as in Fig. 7 it is easier to visualise the circuit as a combination of maintaining amplifier and frequency-determining network. The components R_1C_1 and R_2C_2 are chiefly responsible for determining the free-running frequency which is given approximately by

$$f = \frac{1}{0.7(R_1C_1 + R_2C_2)}$$

So far in this discussion on oscillators it has not been necessary to mention the word "phase" but there is a type of oscillator in which the frequency-determining network operates' by introducing phase shift. This is a workable solution if a symmetrical signal is being generated because, as shown in Fig. 2, for such signals the effect of 180° phase shift and signal inversion are indistinguishable. Thus in one form of phaseshift oscillator the frequency-determining network consists of a three-stage RC filter each section of which introduces 60° phase shift at the required frequency of oscillation. The circuit diagram is given in Fig. 8. If all three frequency-determining resistors have the same value R and all three frequency-determining capacitors have the same value C, the oscillation frequency is given by

$$=\frac{1}{2\pi\sqrt{6RC}}$$

and the current attenuation at this frequency is 29. The current gain of the transistor must hence exceed 29 for oscillation to occur but it should not greatly exceed this value, otherwise the oscillation amplitude will grow as in the multivibrator circuit and, if it is limited by circuit features such as collectorcurrent cut off, the output will no longer be sinusoidal. As shown in Fig. 8 a preset resistor in the emitter circuit can be used to adjust the current gain to the critical value which gives a sinewave output, but a system of a.g.c. which keeps the maintaining transistor operating in class A is perhaps the best method of securing a pure output waveform.



The tremendous transmission distances nonchalantly achieved by Marconi operators and the commonplace use of wireless in military form might tend to obscure the fact that communication was still, in 1916, chiefly telegraphic, using spark-gap oscillation generators. A review article in June 1916 covered the field of such generators and was one of the earliest articles to fully explain the valve oscillator, to be used for the transmission of speech.

"In 1884 Edison showed that an incandescent filament of carbon (such as a lamp filament) possesses the property of ionising the surrounding air, so that it becomes a unilateral conductor.

"This property has been turned to practical utility by Dr Fleming and others, and forms the basis of the well-known Fleming oscillation valves which are now often used as wireless detectors. Some of these values have characteristics (ie volt-ampere curves) which at some point are negative, like an arc characteristic, and hence it is possible to use such valves as generators of oscillations just as the arcs can be so used.

"The mode of operation of this type of apparatus may be briefly summarised as follows: The hot filament has the property of emitting negative electrons, and hence the combination of hot filament and cold plate in an exhausted vessel forms an electrical conductor, which will allow current to flow in one direction only - that is to say, it is a unilateral conductor, and therefore will exert a rectifying action on an alternating P.D. applied to it. Since the current passing through this vacuous space is carried by a stream of moving electrons, and since an electron is merely a negative electric charge, it is evident that the motion of the electrons can be influenced either by an electro-static or by a magnetic field, . . .



COMMUNICATIONS MICROPHONES

9 SHU

COMMUNICATIONS '76 STAND

the vital link when the message must go through.





Shure Safety Communications Microphones are routinely subjected to 2-metre (6 ft.) test drops onto hard floors ... over and over and over again, and even though they've been manhandled and abused

...THEY WORK



Shure Safety Communications Microphones are tested with violent vibrations up-and-down, side-to-side, and back-and-forth simultaneously and even though we tumble 'em around for a while for good measure





SHURE





Shure Safety Communications Microphones are plunged to an appalling -45.6° C for half hour periods during severe temperature tests, and even though they're covered with frost

...THEY WORK

SHURE COMMUNICATIONS MICROPHONES: THE STANDARD OF THE WORLD A definite margin of extra reliability is the reason why, in the United States as well as in many other countries, Shure Mobile Communications Microphones are used with more public safety and professional business communications transceivers than all other brands combined. They are thoroughly field-proved. They perform when the chips are down, as they have been doing for over 20 years. Even after years of constant use and abuse in the most critical situations, often under the most adverse conditions imaginable, *they deliver*... they get intelligible messages through when it counts.



Shure Safety Communications Microphones are tested in super steam baths with humidities of 100% at room temperature, 93% at 38° C and, though they're soaking wet at the end





SHURE

Imagine! Shure Safety Communications Microphones are dragged behind swiftly moving vehicles for miles ... over all sorts of roads, and though scratched-up on the surface

...THEY Work SUBJECTS THEM TO SAND RAIN INFRA-RED ULTRA-VIOLET ACIDS ALCOHOL SALT-SPRAY WIND ELECTROSTATIC FIELDS HIGH ALTITUDE

SHURE

Shure Safety Communications Microphones are carefully quality control checked at every step in manufacture—and random samples from every production run are subjected to the kind of torture testing and abuse that ruins most microphones...





COMMUNICATIONS MICROPHONES

Look for the name Shure moulded into the back of the case of every microphone you buy. It identifies the microphones that have undergone the most rigid and demanding tests in the industry. And, it's your peaceoi-mind assurance of reliability, know-how, quality, quality control, and conscientious fast service!

QUALITY CONTROLLED EVERY STEP OF THE WAY

Mechanically, environmentally, electrically, operationally, acoustically, and visually—Shure Mobile Communications Microphones go through the most comprehensive and extensive quality control procedures. And that's your assurance of getting microphones that have not been simply spot-checked, but thoroughly inspected at <u>every</u> stage in manufacture, from raw materials to finished product.

OUR CASE HISTORY...

Shure Mobile Communications Microphones feature an exclusive, virtually indestructible Armo-Dur® plastic case, which remains comfortable to the touch even if the microphone sits in the hot sun or in freezing temperatures, and is completely corrosion resistant and immune to oil, grease, salt spray, fumes, humidity, and perspiration. Shure's long-life cables and "million-cycle" switches are specially engineered and tested to outlast, by far, these most common failure points of ordinary mobile microphones. They also feature modular construction for easy in-the-field maintenance on those rare occasions when service is required.





THE NEWEST BASE STATION MICROPHONE WITH POWER AND INTELLIGIBILITY!

Strong, Clear Transmission

The new Shure 526T Super Punch Base Station Microphone features a high-articulation dynamic element and a transistorized preamplifier that operates for hundreds of hours on a standard 9-volt battery. The variable output level control allows you to maximize transmitter modulation for increased "talk power," regardless of your speaking distance from the microphone.

Improved Intelligibility

The high quality dynamic transducer guarantees clear voice signals with a response lhat is optimized for maximum intelligibility with AM and sideband transceivers—even with a high background noise level. And the 526T is immune to hum pickup and radio-frequency interference.

All These Extras, Too!

- Includes a two-way NORMAL/VOX switch
- Push-Io-talk switch—locks-in for lengthy transmissions
- · Electronic or Relay switching
- High-impact Armo-Dur* case to withstand the roughest use

SPECIFICATIONS

Model 526T Transistorized Base Station Microphone

Type: Dynamic (with battery powered transistor preamplifier)

Frequency Response: 200 to 6,000 Hz, oplimized for maximum vocal "punch" and intelligibility with AM and sideband units (See Figure C)

Polar Pattern: Omnidirectional

Output Impedance: 5.000 ohms

Load Impedance: 1,000 ohms minimum Output Level: Adjustable from 0.63 to 14 mV for 1 microbar input

Battery Type: 9 Vdc

Battery Drain: 0.9 mA



Switches: Single-bar, locking or non-locking, push-to-talk switch, NORMAL/VOX, single-pole, double-throw slide switch

Cable: Non-detachable, 2.1 m (7 ft.), three-conductor (one conductor shielded), plastic-jacketed cable Case: Black high-impact Armo-Dur

Dimensions: 264 mm x 108 mm x 149 mm deep (10% in. x 41/4 in. x 5% in)

THE MICROPHONE ON THE MOVE ...

The new Shure Ranger 2 Microphone serves double-duty: It combines the quality transmission of a <u>dynamic-element</u> microphone with the Shure reputation for rugged dependability in mobile and fixed-station microphones.

Internally, a silicon transistor amplifier provides a direct replacement for a carbon microphone with reduced sensitivity to hum pickup and susceptibility to interference. The Ranger 2's wide 300 to 5,000 Hz frequency response range and low distortion are specially tailored for unusually smooth, natural voice signals.

Externally, there's the famous Armo-Dur® case that's lighter and stronger than die-cast metal (and comfortable to hold at any temperature). The coil cord is jacketed with long-life neoprene. Constant use and rough handling won't affect the "million-cycle" leaf-type switch—it's engineered to withstand the severest conditions. All this in a compact size for easy handling.

Together, the superior performance and heavy-duty construction offer you the clearest choice in communications microphones today!

SPECIFICATIONS

Model 524C Transistorized Dynamic Hand-Held Microphone

Type: Dynamic (with transistor preamplifier for carbon microphone circuits)

Frequency Response: 300 to 5,000 Hz (See Figure A) Output Level (at 1,000 Hz, 5/16 in.): -44 dB (6.32 mV) with 10 Vdc, 500-ohm load (0 dB = 1 volt per microbar)

Load Impedance Range: 250 to 2,200 ohms Maximum Signal (with 10 Vdc, 500-ohm load): 118 dB SPL at 1,000 Hz produces 0 dBV (1.0V) at 10% THD

DC Supply Voltage Range: 2.5 to 35 Vdc

Switch: Double-pole, single-throw, leaf-type, push-to-talk Cable: Non-detachable, 1.5 m (5 ft.), four-conductor, neoprene-jacketed coil cord

Case: High-impact Armo-Dur®

Dimensions: 52.4 mm x 72.2 mm x 39.7 mm deep (2-1/16 in. x 2-27/32 in. x 1-9/16 in.)



Series 577

Microphones: Break the Sound Barrier!

onob

Be heard, even when ambient noise levels are so high you can hardly hear yourself. The 577 Sonobar Noise-. Cancelling Dynamic Microphones dramatically block unwanted noise and boost close-up voice signals. The 577s' noise-cancelling pickup pattern and "tailored" voice-range frequency response can discriminate against environmental noise so that the transmission sounds loud and clear—even in noisy factories, disaster areas, or airport ramp areas.

The 577 Series features three models: the 577A for high-impedance inputs ... the 577B for longer cable lengths (low impedance) ... and the 577C transistorized carbon replacement model.

All have the tough Armo-Dur[®] cases to repel oil, grease, fumes, salt spray, humidity, and rust! A "lifetime" hang-up button and mounting bracket, Triple-Flex coiled cable, and shock-resistant construction features are all part of the 577s' built-in durability.

SPECIFICATIONS

577 Series Noise-Cancelling Dynamic Microphones Type: Dynamic, Noise-Cancelling

Frequency Response: 100 to 5,000 Hz (See Figure B) Impedance: Model 577A: High impedance for connection to high-impedance inputs

Model 577B: Low impedance for connection to microphone inputs rated at 25 to 200 ohms

Model 577C: Transistorized for carbon microphone type circuits: Load Impedance Range: 250 to 2,200 ohms

Output Level (at 1,000 Hz, 5/16 in.):

Open Circuit Voltage

Model 577A Model 577B

- 63.5 dB (.63 mV) - 84 dB (.062 mV) (0 dB = 1 volt per microbar) *With 10 Vdc, 500-ohm load

Power Level: -61.5 dB (Model 577B) (0 dB = 1 milliwatt with 10 microbars)

DC Supply Voltage Range (Model 577C): 2.5 to 35 Vdc Hum Sensitivity: (Equivalent to)

Model 577C*

47 dB (4.5 mV)

Model 577A: 44 dB SPL in 1 millioersted field Model 577B: 32 dB SPL in 1 millioersted field Model 577C: 27 dB SPL in 1 millioersted field

Switch: Double-pole, single-throw, leaf-type, push-to-talk Cable: Non-detachable, 1.8 m (6 ft.), neoprene-jacketed

Triple Flex coil cord Model 577A: Three-conductor (one conductor shielded) Model 577B: Four-conductor (two conductors shielded) Model 577C: Four-conductor (non-shielded)

Case: Two-tone Grey, high-impact Armo-Dur® **Dimensions:** 66.7 mm x 93.6 mm x 44.9 mm deep (2-5/8 in. x 3-11/16 in. x 1-25/32 in.)





SM10 Unidirectional Head-Worn Microphone

HANDS-FREE TRANSMITTING with built-in noise control!

All new and field-proven! Shure's SM10 Head-Worn Microphone and SM12 Head-Worn Microphone/Monitor have every transmitting convenience you will need built into three ounces of comfort. Both microphones have high-power, clear-signal <u>dynamic</u> elements for maximum intelligibility. Yet, no batteries or cumbersome controls are needed—your hands will be free for note-taking or driving.*

The SM10 and SM12 are specially designed to reduce pickup of annoying background sounds without masking close-up voice signals. Unidirectional pickup pattern means only the sounds of your voice are transmitted. The anti-noise feature is further enhanced by a strong, natural voice frequency response (50 to 15,000 Hz) that minimizes low background rumble. A built-in windscreen filter eliminates other noise distractions.

Headset mouthpiece is designed to pivot and extend to fit any face. Adjustable frame and padded headband assure a pleasant fit for anyone, too

*when used with a footswitch or other relay arrangement (not supplied with microphone)

SPECIFICATIONS

MICROPHONE (applies to both SM10 and SM12): **Type:** Dynamic, Close-Talking

Frequency Response: 50 to 15 000 Hz (See Figure D) Polar Pattern: Cardioid (unidirectional)

response—uniform with frequency, symmetrical about axis (See Figure E)

Impedance: Microphone rating impedance is 150 ohms (200 ohms actual) for connection to microphone inputs rated at 25 to 200 ohms



Output Level (close-talked at 1,000 Hz):

 $(0 \, dB = 1 \, milliwatt with 10 \, microbars)$



Hum Sensitivity: Less than – 62 dBm in 1 millioersted field Phasing: Positive pressure on diaphragm produces positive voltage on pin 2 of microphone connector

Connector: Professional three-pin Male audio connector designed to mate with Cannon XL series, Switchcraft A3 (Q.G.) series or equivalent connector

Cable: Non-detachable 1.5 m (5 ft.), four-conductor, shielded, plastic-jacketed; additional 0.3 m (12 in.), two-conductor receiver cable attached to microphone connector on the SM12

Case: Black thermoplastic microphone and pivot housings. anodized aluminum end caps, stainless steel grille, ear tube and boom

Dimensions: 202 mm $(7^{15}/_{16} \text{ in.}) \text{ long}; 44.5 \text{ mm} (13/_4 \text{ in.}) maximum height (pivot housing).$ Microphone: 15.9 mm (5/₈ in.) diameter; 14 mm (9/16 in.) height

Optional Accessory: A10CH Cough Button

RECEIVER (SM12 Only): **Type:** Dynamic

Frequency Response: 70 to 12,000 Hz

Impedance: 2,000 ohms at 1 kHz (200-ohm cartridge with matching transformer in phone plug)

Output Level: 106 dB SPL with 1.414V at 1 kHz (1.0 mW into 2 cc cavity)

Phasing: Positive voltage on phone plug tip produces positive pressure in ear tube

Connector: Phone Plug (contains matching 2,000:200 ohm transformer)

SHURE

Shure Electronics Limited Eccleston Road, Maidstone ME15 6AU Telephone: Maidstone (0622) 59881

www.americanradiohistory.com



Communication theory

3 — The digital revolution

by D. A. Bell

University of Hull

In speaking of the "digital revolution" I am not thinking of the proliferation of digital computers (though this has its impact on telecommunication through the need for data transmission) nor of the fact that a simple pocket electronic "digital calculator" is now in almost the same price bracket as a good slide rule, its analogue predecessor; I am thinking rather of the impact of digital techniques on television (mostly behind the scenes) and on the use of the Post Office telephone network for the communication of both data and speech, with developments in Viewphone as well. All of these digital developments depend on the flexibility which digital techniques allow in exploiting three key features of Shannon's communication theory, namely redundancy, the possibility of an exchange between signal-to-noise ratio and bandwidth, and a certain symmetry between time and frequency in the calculation of information rate and channel capacity.

The problem of television standards conversion became important in this country as soon as BBC2 was introduced with 625 lines while BBC1 continued to use 405 lines (see Wireless World May 1971.) Then the development of international exchange of television programmes, especially since communication via satellite has been available, has drawn attention to the fact that there are also differences between scanning standards used in different parts of the world: in North America they have 525 lines per picture and 60 (interlaced) fields per second, but in Europe we usually have 625 lines with 50 fields per second. (There are also differences in colour transmission, such as between N.T.S.C., PAL and SECAM.) Conversion between these standards requires storage, and storage of information is simple and reliable only when it is in digital form.¹ Since the development of l.s.i. (large scale integration) both semiconductor memories and shift registérs have become comparatively cheap, so that the digital solution is also an economic solution. In the simplest case each picture element is represented by several bits (as described below for

p.c.m.) and the number of bits is minimised by non-linear quantisation, using small steps for small signals but larger steps at each end of the scale.

There is also a great deal of redundancy in picture signals arising from the fact that neighbouring points are related to each other - they are said to be correlated. This correlation reduces the amount of information in the signal. but it is difficult to use because one must make provision for the occasional picture in which there is not much correlation - e.g. if the camera is panned across a scene. In most pictures, however, the difference between adjacent points in a line is much less than the full swing from black to peak white. It follows that for the same gradation of grey the signal conveying the difference between adjacent points will nearly always require fewer steps than would be needed to convey the absolute value of each point. So this differential p.c.m. (or d.p.c.m.) can use fewer bits per sample than direct p.c.m., which is particularly valuable if the picture has to be transmitted through a limited channel. The addition of vision to an ordinary telephone circuit ("Viewphone" in Britain or "Picturephone" in the Bell System, USA.) is a case where (a) economy of bandwidth is of great importance and (b) occasional momentary degradation of the picture may be tolerable. The addition of vision to an ordinary telephone channel may seem an extravagant luxury, but its supporters claim that it is justified by fuel economy if the addition of vision to the communication channel makes it an acceptable alternative to face-to-face meeting and so reduces travel. Bandwidth economy in television was the subject of a great deal of investigation some years ago² but in those days only analogue devices were considered for providing the storage from line to line or field to field which is needed to take advantage of the correlation in space between adjacent points or the correlation in time between the same points in successive scans ("picture difference" transmission)3. Now Post Office designers of Viewphone suggest digital



Fig. 1. (a) Lumped circuit approximation to an unloaded line. (b) Frequency response of such a network.

storage of a line in shift registers⁴ so that use may be made of correlations between points which are adjacent vertically, in different lines, as well as that between adjacent points in the. same line. A more elaborate system has been proposed for the American Picturephone, utilising correlation between successive scans. This has a buffer store of 67,000 bits (equivalent to about 4,000 words storage for a minicomputer using 16-bit words); and if movement in the picture destroys correlation to such an extent that a scan cannot be compressed into this size, the picture is deliberately degraded in two stages. First the scan is coarsened to use only half as many picture elements per line; and if that does not suffice the second stage is to omit a complete scan and instead re-transmit the previous scan.⁵

Another digital development in television is the transmission in the field blanking interval of alpha-numeric data. The system is called teletext (Oracle by the IBA and Ceefax by the BBC); and any viewer who has the appropriate adjunct for decoding, storage and character generation (as recently described in this journal) can choose at any time to have the picture on his screen replaced by a page of information consisting of latest news or any one of a hundred or so pages which may be available.

But in more mundane telephone communication, digital methods first came in with the use of p.c.m. on junction lines which are usually in the range of 10 to 30 miles long and employ multi-pair paper-insulated cables – the last kind of cable one would think of for the transmission of a wide frequency band or narrow pulses. These cables have very little inductance of their own so that ideally they would behave as CR circuits (Fig. 1a) with a frequency response which falls continuously for all except the very lowest frequency (Fig. 1(b).

The equivalent circuit of Fig. 1(a) with capacitors at intervals is only an approximation, since in fact the capacitance is uniformly distributed along the cable; but Pupin pointed out a long while ago that if one had inductance distributed along the line as well, or an approximation to this in the form of loading coils at intervals (Fig. 2(a), the cable became a lossy low-pass filter which passed all frequencies up to a definite cut-off but very little beyond. So most telephone cables have these loading coils at intervals so as to maintain a uniform pass-band with a signal/noise ratio better than 50dB which is then divided into telephone channels by frequency-division multiplex. Now a binary signal can tolerate a much lower signal/noise ratio and the signal after regeneration is independent of the signal/noise ratio. Therefore a binary signal can use a much wider frequency range in Fig. 1(b), and does not require the attenuation to be uniform within that range.

In p.c.m. we need to sample the analogue signal twice per cycle, but Nyquist says we can transmit two pulses per second per hertz of bandwidth: so there appears to be no change so far. But if we are to reduce the pulses to a binary scale, i.e. p.c.m., we need several pulses per sample; and in fact eight are used, seven to quantize the signal into 128 levels and one for synchronising and signalling. The bandwidth is increased eightfold; but the characteristic of the cable is such that the useable bandwidth increases more than eight times when one drops the signal/noise ratio from that required for a good telephone channel to that required for binary signalling, so there is a net profit on the exchange. In terms of communication theory, this is an example of trading signal/noise ratio against bandwidth.

Pulse code modulation is now in widespread use on junction lines.* It should be recognised that an important factor contributing to this is the availability of solid-state circuits for handling quantized signals which combine complexity of logic circuitry with small size, low power consumption and reliability. In the days of valve amplifiers the repeaters (line amplifiers) were usually housed in telephone exchanges, or occasionally in separate buildings. Such housing was necessary on account of their bulk, the need for a substantial power supply (with means of maintaining power in case of a mains failure) and the need for access for maintenance. Now, a solid-state regenerative repeater is put in whenever a loading coil is taken out. The loading coils were usually inserted at intervals of about a mile, and housed in cable-jointing chambers below manholes. A small solid-state regenerative repeater can be put there instead, and its small power requirement supplied along the telephone cable from the nearest exchange.

The spacing of repeaters is important. The signal must not be attenuated below the permissible signal/noise ratio



Fig. 2. (a) An inductively loaded line. (b) Bandpass frequency response of the loaded line.

before arriving at the next repeater; but the attenuation increases with frequency so that the maximum frequency which can be used depends on the closeness of spacing of repeaters.

For some thirty years engineers have been seeking an all-electronic telephone exchange. Note that I said "all-electronic" because the present generation of what are generally called "electronic exchanges" are really electronically controlled electromechanical exchanges. You must first understand that a telephone exchange has three functions: (a) to provide a switchable path for speech signals from an incoming to an outgoing line; (b) to receive, act upon and generate signals for controlling the speech path and (c) to interpret the signals and other data so as to provide speech paths efficiently. If we think of the old type of manual switchboard, (a) is provided by jack plugs and cords which can connect selected jack sockets, (b) depends on the senses and limbs of the operator (e.g. seeing a calling subscriber's light, switching ringing tone on a called subscriber's line) and (c) depends on the operator's brain.

In the past generations of automatic exchanges, (b) and what could be done towards (c) were implemented by relay logic, and this has been replaced by computer-like electronic circuits in the current generation of electronically controlled exchanges.⁶ But there has been comparatively little success in the search for a solid-state replacement for the metal-to-metal contact in the speech-path switches, though the mechanical form of the contacts has changed from Strowger two-motion switches through cross-bar switches to the sealed reed relays used in the current electronically controlled exchanges.⁷ The metal-to-metal contact has virtually infinite ratio of open to closed resistance, perfect linearity and no noise in normal functioning. Engineers became increasingly convinced that these characteristics could not be approached by any solid-state device and therefore solid-state switches could not be employed in an analogue speech path. But the use of digital signals such as p.c.m. makes the characteristics of the switches far less critical, so that solid-state switches would be useable.

Once an analogue signal has become contaminated with noise, it can never be "cleaned"; and the noise components introduced at successive links in the route are additive. A digital signal, on the other hand, can be regenerated by threshold devices so that it leaves each repeater stage as a perfectly clean on/off signal. The Post Office therefore took the view that a future "System X", which will one day supersede the present generation of electroniccontrol - plus - reed - relay - switching exchanges, will employ digital transmission on the main trunk circuits. Preliminary trials on trunk transmission between Portsmouth and Guildford using high-speed p.c.m. have recently been initiated by the Post Office.8 Again there has been an exchange of bandwidth against signal-to-noise ratio, since p.c.m. at 120Mbit/s is sent over a coaxial cable which could only be used up to 12MHz for f.d.m. The first consequence of this change to digital transmission will be that our familiar frequency-division multiplexing will be replaced by time-division multiplexing. Then instead of picking out a frequency channel with filters we shall pick out a time-slot by strobing. Some of the exchange switching can then be replaced by the matching of time-slots between incoming and outgoing lines, but some switching of circuit connections (known as "space switching") will probably be needed as well. But in view of the greater tolerance of digital signals, "cross-points"** could be solid-state.

^{*} Lines 10 to 30 miles long which give direct connection between local exchanges, without using the trunk system.

[†] See section headed "Electronic exchanges" in "Centenary of the telephone", Wireless World, March 1976, p.92. — Ed.

^{**} See Appendix for explanation of "cross-point".

A few years ago this was unquestioned and there seemed no hope for solid-state cross-points outside digital systems. Recently, however, there has been a revival of interest and a dozen manufacturers in the USA offer private automatic branch exchanges (PABX) using solid-state technology which offers the advantages of small size and little maintenance requirement. Most of them use four-layer devices, analogues to thyristors, as cross-points. But thepoint is that in this case the speech goes through only one solid-state switching system (or at most two if the subscriber at each end of the line has a solid-state PABX). This contrasts with the number of exchanges which may be involved in a long-distance call over a public network, and of course any noise or distortion arising in successive exchanges is additive.

An immediate advantage expected from digital transmission of speech is that data in binary form can immediately replace the p.c.m. signals. There has been much controversy over the question of whether we need a separate data network in addition to the telephone network. At present digital signals are usually fed into the frequency-division multiplexed analogue telephone system through modems (modulator-demodulators) which convert the on/off binary signal into a more or less complicated system of frequency-shift, phase-shift or multi-level amplitude modulation of an audio tone. It is much simpler to send binary digits straight to line, if the line is tailored to handle digital signals. Since the telephone network provides almost universal coverage, it seems uneconomic to set up another network alongside it just to handle data. So making telephoning digital confers a further advantage if it makes telephone traffic and data traffic fully compatible. (But it must be remembered that the telephone system is at times fully loaded, so that extra trunk lines and switching plant would be needed to enable it to carry a significant load of data traffic as well.)

A development in networks intended solely for data is called "packet switching." This arises because transmitting data has some of the characteristics of sending telegrams: there is no need for communication to be instantaneous and simultaneous with the origination of the information, though one would prefer that any delay in data transmission should be measured in seconds rather than hours. Given adequate buffering, data signals which arise at irregular intervals can be sent at a steady rate (most of the time) over the main transmission channel.

The idea is in fact very old since what we shall now call "a node in a packetswitching network" has as antecedent "a torn-tape relay station in a telegraph network." Telegrams are normally transmitted via punched paper tape and if they had to be sent through a relay station they could be received there on a tape perforator. Originally an operator would read the address on an incoming message and at its end tear off the length of tape and transfer it to an appropriate transmitting machine for its particular destination; but later the address was read by machine and the length of tape directed automatically into the appropriate channel for retransmission, where it might join a queue of messages for that destination. The equivalent in modern technology is obviously to have at the relay centre a computer with appropriate buffer stores.

The torn-tape telegraph relay is not of great practical interest now because it is usually easier to switch electrical connections, so why has the principle been revived for data transmission? The first answer is that there is a considerable demand for transmitting small units of data, such as banking transactions of individual customers, which contain no more than a few hundred characters. At the present time it may take 15 seconds to set up a long-distance s.t.d. connection so if the data can then be transmitted in a similar or shorter time the whole process is rather inefficient. Secondly there is the problem of concentration of local traffic into trunk lines, which in telephony is achieved at present by frequency multiplexing. In the transmission of telephony by p.c.m. the sampling pulses are generated within the exchange, so that although there are problems of synchronism between exchanges in the proposed digital telephone network the timing is at least all controlled within the system. (Incidentally, one proposed method of matching time slots between different exchanges is called "pulse stuffing" and consists in inserting extra pulses into the signals from one of the channels. This clearly could not be used in data transmission).

So the idea is that data should be divided into units called "packets" of perhaps 1000 bits, each carrying a destination address. These would originate at sources of various types, ranging from a keyboard to a 48kHz line from a computer centre and would all be sent to a local switching centre or node on the special network. The computer here would take them into store, read the address, sort them into strings according to destination and transmit at high speed (of the order of 100 megabits/second) to other nodes in the network. Precautions have to be taken to see that no packet is lost and to see that the packets in a series constituting one message arrive in the right order. At the present time there is considerable activity in the development of data networks. The first was ARPA, set up by the United States Department of Defense to link a number of computer centres which each contain one or more powerful computers. It has also some

access points in Europe. Part of the

argument for such a network is that a

computer centre may specialise in some

particular type of work for which its computer is particularly suitable on account of features such as the balance between fast-access store, backing store, input and output facilities, etc. It is then economic to send different kinds of work to different computers and a communication network serves this purpose. In Europe the emphasis is more on data collection, as implied in the explanation of packet-switching above. The British Post Office has opened an experimental packetswitched service on the route London-Manchester-Glasgow to assess the commercial value of such a system; the European banks are proposing a network called SWIFT for the rapid transfer of information about international banking transactions; there are plans for a European Information Network (EIN); and a EURONET is proposed to link all major scientific research establishments in Western Europe.

It seems a far cry from Shannon to digital television and packet-switched data networks. But the same principles apply throughout:

(1) All information is finite and can therefore be digitised.

(ii) The maximum capacity of any physical channel can be specified interms of its bandwidth, signal-to-noise ratio and the time for which it is available.

(iii) Within the bounds set by (ii) it is possible to exchange signal-to-noise ratio against the bandwidth-time product.

No doubt we shall see many further applications of these fundamental principles as time goes by.

Appendix: Cross-bar and cross-points

The Strowger system of automatic telephony is based on its two-notion switch. This first moves vertically to one of 10 levels and then horizontally to one of 10 positions in the level so as to select one out of 100 contact pairs. This is a direct mechanisation of the action of the manual exchange operator in



Fig. A. Principle of cross-point switch connecting any of inputs A, B, C, D, E to any of outputs 1, 2, 3, 4, 5.

selecting one out of a square array of jack sockets, but with one important difference. The whole of the Strowger switch remains engaged while the single call is passing through its contact field; but the operator after putting plugs in to make one connection can leave it and attend to other connections until she receives a signal to clear the first connection. The cross-bar switch, which is illustrated in principle in Fig. A comes nearer than Strowger does to simulating the methods of the human operator. The diagram shows input lines A, B, C, D, E crossed by output line's 1, 2, 3, 4, 5. At each point where the lines cross there is a switch, closing of which is indicated by a blob on the diagram. Thus the cross-bar switch can complete more than one circuit at a time: the connections shown are $A \rightarrow 4$, $B \rightarrow 1$, D \rightarrow 2 and E \rightarrow 5. While the numbers of lines in each direction may be varied, the principle is now universal and the only question is what kind of switch or cross point should be used at each crossing. In the original cross-bar switches the contacts were metal-tometal and operated by a mechanical system of solenoids, bars and latches; in the current electronically controlled exchanges they are reed switches; and there is an increasing probability of the future use of solid-state devices as cross-points in some applications.

References

1. J. L. E. Baldwin *et.al.*, "DICE: the first intercontinental digital standards converter," *R.Telev. Soc. Journ.* 1974, vol. 15, pp 140-159.

2. D. A. Bell, "Economy of bandwidth in television," Journ. Brit. Inst. Rad. Engrs., 1953, vol. 13, p.447.

3, R. Barthelemey, "Images Differentielles," Comptes Rendus, 1949, vol. 229, p.61.

 J. E. Thompson and G. A. Gerrard, "A differential p.c.m. encoder for Viewphone signals." Conference on Digital Processing of Signals in Communications, 1972, IERE Conference Proceedings No. 23, pp.329-337.
D. J. Connor, B. G. Hashell and F. W. Mounts, "A frame-to-frame Picturephone coder for pictures containing differential quantizing noise," *Ibidem*, pp. 363-372.

6. M. T. Hills "Electronic telephone exchanges. Conclusion: Computer-controlled Systems," Wireless World, July 1974, p.241.

7. M. T. Hills, "Electronic telephone exchanges. A Review of Techniques," *Wireless World*, June 1974, p.164.

8. "High capacity p.c.m. system," Wireless World, February 1975, p.92.

Literature Received

A guide to the range of thyristors, triacs and trigger devices made by Motorola is now available. Equivalents to other types are suggested and there is information on outlines and leads: application notes are listed. The guide is offered by GDS Data Centre, Michaelmas House, Salt Hill, Bath Road, Slough, Bucks WW401 A price list of over 200 instruments. classified as signal sources, signal conditioners' and analysers and measuring instruments, is produced by Lyons Instruments Ltd, Hoddesdon, Herts EN11 9DX . Measuring instruments for hire are described and classified in the 1976 Livingston Hire Catalogue. Most common electronics laboratory instruments are listed, as well as a range of industrial equipment. The catalogue can be obtained from

Shirley House, 27 Camden Road, London NW1 9NR WW403

"Foundation for a Career" is the title of a pamphlet. produced by the City and Guilds of London Institute, which outlines a scheme of courses to give school leavers vocational preparation. Five courses are described — construction, engineering, science industries, food industries and community care. Copies are available at 50p from the Sales Section of the Institute at 76 Portland Place, London WIN 4AA.

A supplement to the Doram mail-order catalogue has been sent to us. New products include amateur radio modules, a 432MHz-to-28MHz transverter. a 70cm varactor tripler, a 500MHz prescaler and a 50MHz counter. Price reductions on small components are announced. Doram Electronics Ltd, PO Box TR8, Wellington Road Industrial Estate, Wellington Bridge, Leeds LS12 2UF WW407

Hygrometers, dewpoint meters and moisture analysers made by Shaw are the subject of a catalogue recently received. Brief details are given of instruments for the measurement of moisture in a range of materials. Shaw Moisture Meters, Rawson Road, Westgate, Bradford WW409



Predicted disturbed periods are May 21 — June 2 and June 15–21. Seasonal trend and minimum solar activity combine to produce FOTs and LUFs which give a restricted choice of time and frequency for reliable day to day communication. This feature is most evident when both ends of a radio path are in the northern hemisphere mid-latitudes.



Wireless World Teletext decoder

8 - Modifications and lining up

by J. F. Daniels

Most constructors will probably want to use the decoder with a colour television receiver, but for those who use a black-and-white set, a few words on interfacing are needed.

Monochrome receivers

If a black-and-white receiver is to be modified then there are two options open to the constructor. The decoder may be wired in, in a similar manner to that described for the colour receiver, or a separate tuner and i.f. strip may be used, the output of the decoder being fed via a u.h.f. modulator into the receiver's aerial socket. This second method has the advantage that the decoder may be electrically isolated from the TV set. Whichever system is used, the best display will be obtained by mixing the red, green and blue outputs of the decoder together by means of variable resistors, the resistances of which may be varied to give the desired grey levels for different transmitted colours. Mixed syncs must also be added at this point to lock the scan circuits in the TV set. The problem most likely to be encountered with black and white sets, especially the older ones, is lack of bandwidth in the i.f. strip - a good reason for using the extra i.f. and modulator approach.

Character verticals

The following modification to the decoder circuitry has been found advantageous because it reduces the h.f. response requirements of the receiver video amplifier output stages. Fig. 1 shows the circuit, which uses existing "spare" i.c. gates. The extra gates are wired in series with the output of gate (57, 6). Gates (75, 8) and (75, 3) pass the signal through unchanged, but gate (75, 6) adds to the original signal a pulse derived from the trailing edge of the display character components. VR₃ can be adjusted to give the best character appearance, and the setting of this control will depend on the frequency response of the receiver video amplifiers. At zero resistance setting, the signal passes through this stage unchanged, but as the resistance is increased the width of the character verticals gradually increases until the appearance of the characters is obviously distorted. A suitable control setting should be found which gives the best character appearance.

Upper and lower-case characters

Texas Instruments have recently announced a new character generator i.c., the X887, which has been developed as part of their Tifax decoder module, and as the i.c. was specifically designed for Teletext decoders, it has a number of advantages over the 2513.

Firstly, it contains a complete set of upper and lower-case characters, which includes all those characters defined in the latest Teletext code table. Secondly it has provision for a four-bit row-select input code which means that all ten rows of the characters may be addressed independently, and no shifting of address codes is required for characters with "tails". Thirdly, it only requires a +5V supply, which means that the decoder power supply may be simplified as the -12V rail is now unnecessary.

Fig. 1. This modification reduces the degrading effect of poor video frequency / amplitude response in the television receiver. The effect is to broaden vertical components of characters.

The circuit arrangement using the new i.c. is shown in Fig. 2 and is almost identical to the original circuit using the upper-case 2513. The differences are that all seven bits are now fed to the character-select inputs and the four-bit row-select inputs are fed from the Q_A , $Q_{B^*}Q_C$ and Q_D outputs of IC_5 directly. The Y_1 - Y_5 outputs feed, as before, into the five open-collector gates, although the timing of the strobe pulses from IC_{42} has been changed slightly to allow for the faster access time of the X887.

The cost of the X887 is around £20, which makes it rather expensive compared with the 2513, but if a decoder with the lower-case facility is required, then the X887 is the obvious choice.

Line-up procedure

The following line-up procedure has been devised after lining up six decoders, but it does assume that the decoder has no faults and is being fed with a suitable video signal as described earlier. It would also be advisable to check that data is actually being transmitted on the selected TV channel, since the system is still in its experimental period and transmissions may be interrupted occasionally. To check the transmissions are present, reduce the height of the TV picture, or offset the vertical-hold control and look for lines of constantly-changing white dots and



dashes across the full width of the TV line in the field blanking interval.

The line-up procedure requires no test gear, but the power supply rails should be checked with a multimeter prior to following these instructions.

- Set the six preset potentiometers (three on the analogue board, two on digital board 1 and one on digital board 2) to mid-position. A screen full of random characters will probably be obtained, because the flip-flops in the r.a.m.s take up random states at switch-on. Do not, however, push the clear-page button at this stage.
- Adjust VR_3 on the analogue board (set sync separator) to give a display that is free from vertical jitter. Turning the potentiometer too far in one direction will cause the display to jitter vertically and move down the screen. Turning it too far the other way will make the display disappear altogether.
- Adjust VR_1 on the upper digital board (horizontal shift), and VR_1 on the analogue board (display width) to give a correctly-centred and suitably proportioned display.
- Connect a link between pins 13 and 14 of IC₉. This disables the "framingcode allow" monostable, and this is essential during the first part of the setting up procedure.
- Switch the decoder to the "roll" mode and adjust L_1 to give the maximum amount of "movement" of the display. The characters should start changing at random and this may appear to be happening on consecutive rows from top to bottom of the screen, giving a "rolling-through" appearance. If so, adjust the

coil for the most consistent rolling-through action. If the coil former being used is not the specified one, then the oscillation frequency can be checked as follows: - disconnect the uppermost wire link to the analogue board, (lines 11-21) and adjust L₁ to give a display of approximately the correct width. (Disconnecting this link inhibits the display oscillator and makes the data oscillator operate the whole time, so the characters will appear rather ragged). If this is outside the range of adjustment of L_1 , adjust the value of C_2 until the width of the display is approximately correct. Reconnect the link to the analogue board.

Adjust VR₂ on the analogue board (slice level) to improve the rolling through action and some correct pages may now be observed changing very rapidly. Continue adjusting L_1 and VR_2 alternately to give the best rolling action. (N.b., when the roll mode is selected the decoder reads out each data row as it is transmitted, and this enables the effect of each adjustment to be observed, instantaneously, rather than having to wait for up to 15 seconds, which would be the case if pages were selected in the normal way.

Remove the link from IC₉, pins 13 and

Fig. 2. The revised character generator, which uses the Texas X887 to display both upper and lower-case characters, as well as the complete Teletext symbol set. 14. The rolling-through action will probably cease. Adjust VR_2 on digital board 1 carefully, until the rolling-through action begins again. This control has an "on-off" action, unlike those previously adjusted, and is necessarily quite critical in its setting. The adjustment should be checked on different TV channels, since there may be slight differences in the position of the framing code between different channels.

Switch off the roll mode and select a clock-cracker page (at the time of writing page 899 on Oracle or page 140 on Ceefax). This page is used to accurately check the frequency of the data oscillator, and consists of 14 consecutive 1s followed by two 0s repeatedly across each row of the page. This means that the data oscillator gets the least possible amount of locking information on each line and so must free run at the correct frequency for almost two bytes of data. If L_1 is not quite correctly adjusted, a regular pattern will appear on the left-hand side of the screen which will gradually disappear or turn to "rubbish" on the right-hand side. L₁ should be adjusted a quarter of a turn at a time, until the page readout produces a pattern which is even over the whole screen. The two photographs in Fig. 3 show a correct and incorrect clock-cracker readout. These photographs were taken from the output of a decoder which had a lower-case character generator installed, and the characters displayed when an uppercase-only decoder is used are



Fig. 3. The "clock-cracker" page, with L_1 (April issue, p.66) correctly adjusted is shown at (a), while the result of incorrect tuning is seen in (b).

different to those shown. The principle of adjustment is, of course, the same.

- Finally adjust the slice level control $(VR_2 \text{ on the analogue board})$ to give the most error-free page readouts, selecting pages' in the normal manner. If the contrast control on the TV set alters the amplitude of the signal being fed to the decoder, check that both the sync separater and the data slicer work satisfactorily over the required range of the control.
- Check that the decoder function switches operate correctly and adjust VR_3 on the lower digital board to give the most pleasing character appearance.

Fault finding

Experience with a number of decoders has shown that faults are almost invariably caused by i.c. pins being left unsoldered, especially on the top side of the p.c. boards, or missed connectedthrough holes, so it is best to check the boards very carefully before attempting the line-up procedure.

Faulty or suspect t.t.l. gates can be checked fairly easily by means of d.c. tests (remember that t.t.l. outputs can be shorted to the 0V rail for "in-circuit" testing of following gates, but must not be connected directly to the +5V rail.) If an oscilloscope is not available, suspect counters can only really be checked by substitution. Faulty r.a.ms can easily be detected by spotting an abnormally large number of spelling mistakes on each page and by consulting the code table, the bit which is common to all the incorrect letters can usually be located.

Installation

A few final hints on wiring the decoder into a domestic receiver may be of some use. Coaxial cable must be used for the video input feed to the decoder, and this' should be kept as short as is practical. The other feeds to the decoder will be +5V, -5V, -12V and 0V. From the decoder to the receiver there will be red, green and blue output signals, the video switch control wire, and the clamp pulse feed. These last nine feeds may be combined in a single multicore type of screened cable. Screening is necessary to prevent pick-up of the high frequency display components of the output waveforms in the receiver sound or video stages.

Finally it must be stressed again that great care must be taken when connecting the decoder into the TV





receiver, to ensure that every possible safety precatition is taken. The decoder box must be effectively **earthed**, not connected to the TV chassis, and there must be no exposed connections that are at anything other than earth potential. An isolating transformer (which allows the receiver chassis to be earthed) must be used while lining up the decoder, but if the above precautions are observed, this will not be necessary once the decoder is installed in its box.

Acknowledgments

I would like to thank Mullard Ltd for their help with character generator i.cs and also my colleagues, Dave Beavan. Norman Riggs and Arnie Tidder for their helpful suggestions and help with building the prototype decoders.



56

Is h.f. propagation getting worse?

The many months during which amateurs have struggled with low m.u.fs and early closing of the h.f. bands have underlined the recognised problems of the classic 11-year sunspot cycle. It is not so much that long-distance lowpower signals disappear altogether but rather that activity becomes bunched on low frequencies, stations are heard more spasmodically and the resulting contacts go more and more to the elaborately equipped stations having effective aerials, leaving the less ambitious stations struggling after the occasional better "openings."

Such conditions this past winter came as no surprise to those radio amateurs whose memories stretch over several sunspot minima. But beyond this anticipated and transient deterioration there is another possibility that is attracting some attention: is there evidence to support a view that m.f.-h.f. radio propagation may be gradually changing – for the worse? That "average" propagation conditions today are less good than in the twenties or thirties?

Some people believe that a deterioration of conditions has been disguised by the gradual improvement in receivers and in the higher powers used by broadcasters and amateurs. Such a proposition would be extremely difficult to prove conclusively one way or the other; detailed information on signal path losses over many years is just not available, and it would be difficult to distinguish increased attenuation from the practical consequences of increasing mutual interference between stations.

Yet one does find a persistent belief among some old-timers that radio paths have gradually deteriorated or at least changed. One of the few tangible pointers in support of this view is the virtual disappearance of "long delay echoes" which, as recent correspondence has convinced me, were heard regularly and authentically in the period up to 1939. If, in fact, ionospheric propagation has been subject to long-term changes this might be part of some as yet unidentified solar cycle or it might reflect the increasing effect of the vast increase in total radiated power, affecting electron temperatures in the ionosphere (as indicated for instance in the recent artificial radio aurora experiments in the United States).

On the bands

National Field Day, to be held this year on June 12-13, is to be run under new rules, including the dropping of the "double station" entries and the removal of power 'restrictions other than those imposed by the amateur licence. Instead new "open" and "restricted" sections have been created with those clubs entering the "restricted" section having to limit their amount of equipment and type of aerials that may be used. The original purpose of NFD, established by the RSGB in 1933, was to show that low power portable stations set up at short notice outdoors were capable of maintaining reliable communications with similar stations throughout the UK - a proposition that today would be accepted without question with the result that there has been some flagging of enthusiasm in. recent years. It will be interesting to see if the new rules lead to a revival of interest.

Recent Australian microwave activities have included a 244km contact on 2304MHz between Mount Genini, near Canberra and Mount Canobalis, near Orange, New South Wales. This was made between Des Clift, VK2AHC and Bill Cox, VK2ZAC. These amateurs have also been investigating 6cm and 3cm paths, including super refraction over coastal paths.

A new headquarters station of the Royal Naval Amateur Radio Society has been inaugurated at the HMS Mercury training school.

The Home Office has agreed that amateurs holding slow-scan television permits may now use 256-line transmissions as an alternative to 128-line systems without further notification of the authorities.

To avoid interference from radioteleprinter transmissions the RSGB is proposing to change the frequency of its Sunday morning GB2RS news-bulletin transmissions from 3600kHz to 3650kHz.

J. Michale Gale, G3JMG, a civilian instructional officer at the Fleet Air Arm's Air Engineering School, HMS Daedalus, Lee-on-Solent, Hampshire, has been instrumental in the setting up of a local amateur radio society. The society, using the call G3JMG, will be regularly active on 1.8MHz.

Some tips from a lecture by Lewis McCoy, W1ICP, at a recent amateur convention in the United States: "If you have confidence in your antenna it will work better than if you don't"; "If the antenna stays up it is too small"; and "If the confounded thing works, leave it alone." He is a strong advocate of the quad aerial as providing roughly 2dB more gain than comparable Yagi arrays.

For moonbounce operation, Peter Carey, ZE5JJ, is reported to be constructing a new 32ft dish aerial using some 500 metres of aluminium tubing. He also has a 128-element colinear array which gives 24-25dB gain on 432MHz. A 28ft diameter parabolic dish aerial with circularly polarized feed horn is used for moonbounce work on 1296MHz by Hans Lohmann Rasmussen, OZ9CR in Denmark.

25 years ago

25 years ago, following the imposition of unexpected operational conditions, the RSGB abandoned its original plans to equip and operate an amateur radio station in the Dome of Discovery at the 1951 Festival of Britain. However, special stations were established at Manchester, Leeds, Birmingham and Nottingham as part of the Land Travelling Exhibition, operating under the call GB3FB. A Festival amateur radio convention in London failed to attract anticipated support - and perhaps the most memorable feature from an amateur viewpoint of that Festival year turned out to be the publication of the first of the annual "RSGB Call Books", compiled by John Tyndall, G2QI.

In brief

The New Zealand Association of Radio Transmitters (NZART) celebrates its golden jubilee with a special convention from June 4 to June 7 at the North Shore Teachers' Training College, Auckland ... The 1976 Welsh Amateur Radio Convention will be held on Sunday, September 26 at its usual venue:-Oakdale Community College, Blackwood, Gwent. It is being organised by the Blackwood & District amateur radio society . . . A weekly bulletin of ARRL news is transmitted on 14,095kHz r.t.t.y. at 1730 GMT on Sundays by W2QFR, beamed on Europe and with 170Hz frequency shift. DL8VX transmits an r.t.t.y. information bulletin every 2nd and 4th Sunday of the month, except during contests (0900 GMT, 3585kHz) . . . The British Amateur Radio Teleprinter Group has warned its members that a number of Model 54 teleprinters appearing on the surplus market have non-standard keyboards and codes and that it might be difficult to convert them for amateur r.t.t.y. applications.

PAT HAWKER, G3VA



Exhibitors and details for the Association of Professional Recording Studios exhibition

The ninth international exhibition of professional recording equipment is to be held at The Connaught Rooms, Great Queen Street, London WC2 on Thursday, June 17 (09.00-19.00) and Friday, June 18 (09.00-18.00). Fire on February 5 this year at the Connaught Rooms had made the Grand Hall unusable for the time being so alternative arrangements have been made by the organizers within this venue. The exhibition is for professional users and is not open to the public. Tickets are available from E. L. Masek, 23 Chestnut Avenue, Chorleywood, Herts WD3 4HA.

APRS exhibitors

BASF United Kingdom B & K Laboratories Bauch, F. W. O. Beat Instrumental Beyer Dynamic (GB) Bose (UK) Brennell Engineering

Cadac (London) Calrec Audio Cetec Audio UK

Dolby Laboratories Drake Electronics, Philip

EMI Tape

Feldon Audio ' Ferrograph Professional Recorder Fraser-Peacock Associates

H/H Electronic Hammond, C. E. Hampstead High Fidelity Hayden Laboratories Helios Electronics

Industrial Tape Applications International Musician & Recording World

Jackson Recording Studios

Klark-Teknik

Lee Engineering Leevers-Rich Equipment Lockwood & Co. (Woodworkers) MCI (UK) 3M United Kingdom Macinnes Laboratories Magnetic Tapes Midas Amplification Millbank Electronics Group Music Week NTP Elektronik A/S Neve. Rupert North East Audio Penny & Giles Pyral Magnetics Quad Racal-Zonal Group Services

Lennard Developments

Levy, Jacques

Radford Electronics Raindirk Richardson Electonics Rockwool Rola Celestion Rugby Automation Consultants

Scenic Sounds Equipment Shure Electronics Sonaplan Soundcraft Electronics Studio Republic Studio Sound Surrey Electronics

Tannoy Theatre Projects Trad Sales & Service Trident Audio Developments Turner Electrical Industries Tweed Audio

Uher (UK).

Veale & Associates, Edward Vitavox

Webland Electronics

Zoot-Horn

Principle exhibit by Helios Electronics Ltd will be a music recording and re-mixing console designed and built for Release Records Ltd, Dublin. The console has 28 input channels, 16 main output groups and 24-track monitoring. The specification includes parametric equalization on all input channels and four echo sends with eight returns. Length of the console is less than 2m. New from Helios will be a rack mounting parametric equalizer. The unit has two independent channels, each with a four-section sweep equalizer, by-pass switch and overload indicator.

A range of acoustic screens will be exhibited by Sonaplan Ltd. Model A is designed for separating brass and woodwind from quieter sections of the orchestra. Model O has an observation window designed for vocalists, percussion and string sections where visual communication is desirable and Model S is a half size screen ($1.05 \times 1.00m$) for rhythm sections.

Rupert Neve & Company Ltd who will be exhibiting at the show have released information about a new disc mastering system, the Neve/MSR 2000. This is the result of a joint venture between MSR Electronics Ltd and Rupert Neve to produce and market the mastering system on a worldwide basis. The lathe cuts monophonic and stereophonic production masters and direct replay acetates to the requirements of the recording industry and accommodates all standard record sizes. It has a range of four turntable speeds to facilitate half speed cutting of quadraphonic masters. The system offers such facilities as digital computer control of all functions, digital display readout of cutting suspension, a rumble-free servo-control turntable, turntable speed indication by electronic strobe and automatic groove compensation.



Focal point of the Shure display will be the recently introduced SR line of sound reinforcement equipment. The SR101 mixing console when used with the SR106 electronic crossover, SR105 power amplifier and SR108 two-way horn loaded speaker units forms a complete sound system.



THE CONSULTANTS

As one of those interviewed last year by John Dwyer, I have read and followed with interest his article "The Consultants" published in the November 1975 issue, and the correspondence resulting from it. By and large, I found it a fairly well balanced commentary though, perhaps rightly, a little pointed. Not every conclusion he draws is accurate, and since others of your correspondents seem to have misinterpreted my views, perhaps I may be allowed to clarify them.

First of all, I know of no conscientious professional who is also a "26 hour a week" man. This time, as John Dwyer correctly quoted, is easily spent in the preparation and presentation of lecture and tutorial classes, but undergraduate students of engineering are not trained simply with a stick of chalk. Additional to this is the time necessarily spent on the development of a programme of laboratory experiments, projects and research, their supervision, examination and coursework assessment, the organisation and revision of these and other, new courses of conferences, my own registered research and participation in the Polytechnic's Faculty committees, in forming its long term academic plans. Those not qualified to teach might be forgiven for overlooking many of our responsibilities, but I hope they will at least take note of them.

I would have thought that James Moir and those of his calibre need have no fear of a little competition, whilst others have allowed this age-old reason for resentment to colour their judgment. Thus Gordon King (his letter, April 1976 issue) seems to think that an academically-based professional should not be paid for the work he does on commercial development or sponsored research projects. If that were the case, then some of the criticisms levelled at consultants in these columns recently, might eventually become more justified.

The same lack of judgment is evident in Mr King's interpretation of my comments about consultancy fees; it is because I do not wish the profit motive to dominate my work, as it must not, that I do not request high fees. There are other reasons why I want to see the excellent facilities in the PNL Acoustics Laboratory maintained and developed, which I thought were made clear in the article; not firstly to serve the hi-fi press, but to serve the best interests of my undergraduates. My consultancy work has assisted greatly in this; and it has created good will with certain sections of the engineering industry, and it has benefitted our laboratory facility. Recently, as a result of some such work, an instrument worth ten times the fee we received, was donated, at my request, to the Acoustics Laboratory at PNL. Private consultants are not unique in having professional integrity and responsibility.

Finally, I would like to echo the major point made by \hat{C} . A. Henn-Collins (also April 1976 issue) about the crucial importance of the consultant's impartiality, especially when he must earn a living from both company development and consumer review work. Obviously, the two undertakings have contrasting purposes, one for the manufacturer, the other for the user, and must always be viewed accordingly. My position as an academically based consultant affords me the privilege of being able freely to observe this distinction.

Roger C. Driscoll, The Polytechnic of North London.

CITIZENS' BAND IN THE UK?

The concensus of the various references to Citizens' Band radio in your March issue seems to suggest that if CB ever comes to Britain, it will come at 27MHz. Surely this is not necessary.

If we are to have a Citizens' Band, and I hope we are, we would be far better advised to have one operating at v.h.f. with narrow band f.m. This would have many advantages over 27 MHz a.m., including reduced t.v.i. and b.c.i., less chance of interference during sunspot maxima, and smaller antennas. Such v.h.f. transceivers would be somewhat more expensive than 27MHz ones, but if such firms as Yaesu Musen, Inoue, Standard and Trio can make v.h.f. transceivers (for the 2-metre amateur market) for well under £100, I am sure that they can do even better for the much larger CB market.

I know that there is considerable pressure on the v.h.f spectrum, but surely there must be six to ten channels somewhere between 60 and 300 MHz which could be allocated for this purpose — if e.r.p. is limited even this small number is unlikely to be too congested. A further refinement would be to incorporate a station identifying circuit which causes a tone sequence to be transmitted each time a transmitter is keyed. This could serve the dual purpose of uniquely identifying each transmitter and of acting as a selective call system — more sophisticated receivers could be set to unsquelch only on a call from a particular transmitter.

I feel that there will soon be a strong political demand for CB. I hope that when it comes, the Home Office will have plans ready — perhaps similar to those outlined above and will not have an unsuitable 27 MHz system forced upon it from above for lack of a planned alternative.

James M. Bryant, Cheltenham,

Glos.

Unlike Mr Webber I do feel that the introduction of Citizens' Band radio facilities in the UK would lead to abuse, caused by ignorance on the part of the user and commercial exploitation. If there is a need for a Citizens' Band in the UK then let it be

Wireless World, June 1976

introduced in the u.h.f. bands and not in the 27 MHz band.

I and many thousands share a few hundred kilohertz of the 27 MHz band for model radio control. We already suffer from having several hundred pounds' worth of aeroplane and radio equipment "shot down" by the illegal use of walkie-talkies. If CB radio is introduced we may all be grounded. As a professional engineer and a keen modeller I protest!

L. K. Anderson, Braunton, Devon

MICROPROCESSORS OVERSOLD?

Mr Hill has indeed made a number of valid points. Microprocessor technology is very new and by almost everyone's judgement, it has very great potential in the future. This therefore means that microprocessors have attracted considerable publicity in most of the media.

Mr Hill makes the point that the microprocessor chip cannot operate in isolation. This is, of course, true. The microprocessor only becomes a useful microcomputer when attached to memory devices and input/output interfaces, but already due to large-scale production these devices are very inexpensive for what they are. I think the semiconductor industry has proved that once a product goes into large scale production. costs fall dramatically. An example of this is the electronic calculator which, less than two years ago, would have cost £100 and is now available for less than £10. Significant microcomputer systems can be built now in only moderate volume for less than £40.

Mr Hill mentions the "shock situation" facing engineers wanting to use microprocessors in that they must learn some programming. I am sure that the majority of electronic engineers are well able to cope with learning a new technique and history proves that this is so, for every generation of engineers has had to learn to handle new technologies. In less than two decades, the industry has moved from the valve technology, through discrete semiconductors into the integrated circuit, with an aplomb that must have amazed some of the early experimenters and we are sure that the younger engineers will move into even higher levels of technology in the future without too much difficulty.

So, in answer to Mr Hill, I say yes, the engineers will have to learn programming but it is not that complex. The support hardware to help them to produce and debug programmes is available now and will be available in design centres all round the country in the future. Even if a company decides to buy some programme and system-proving hardware, it is no more expensive than a complex oscilloscope.

As Mr Hill says, the microprocessor is here to stay and indeed we are glad to see that he suggests an intelligent approach to dispel the image that it is the panacea for all iils, because, used intelligently, it can solve many problems of today and will obviously solve many problems in the future. We, as a company, are trying to educate the engineering fraternity and would be prepared to help Mr Hill in any way we can and I am sure this is true of all other semiconductor manufacturers concerned in the development of microprocessors.

Yes, we agree, let us get together so that the learning is made less difficult.

- Vic Yates, Motorola Ltd,
- Wembley, Middlesex

madiesex.

When something important happens, like the introduction of the microcomputer, many claims are likely to be made as to the power and capability of the technology. Sometimes these claims are exaggerated and may, therefore, be misleading. You will sometimes find that such claims are made by individuals who have not yet acquired a full grasp of the subject or by companies who enter the new field late and are trying to establish themselves quickly.

However, I feel that Mr Hill's claim that much of the published material on microprocessors is misleading could also be construed to be an exaggeration in itself, since the bulk of this published information is in the form of technical data sheets and instruction manuals.

Now let us have a look at microcomputer systems to see if Mr Hill's other claims are justified. At the low end of the microcomputer spectrum it is possible to construct a powerful calculator-like system with just four chips: the 4040 c.p.u. the 4201 clock generator, a 4001 r.o.m. to hold the programme and a 4269 interface chip. This system will interface directly to encoded or non-encoded keyboards (up to 128 keys) and will drive a variety of multi-digit display devices. The display registers in the 4269 are used as read/write memory. If more r.a.m. is required, this can be provided by an additional chip. The system can be further expanded by adding a 4265 interface chip which will provide four four-bit ports, any of which can be inputs or outputs. These ports can be synchronous or asynchronous. The 4265 also incorporates all the logic necessary for 'handshaking' with a peripheral. These various options are selected by the software.

The important point here is that two chips provided a full keyboard and display interface, 16 programmable I/O lines and all the logic necessary to control a very wide variety of peripheral devices.

The same principles apply to 8-bit microcomputers. Interface chips are available that approach the c.p.u. in terms of internal complexity and which will provide serial, parallel, synchronous, asynchronous and bidirectional inputs and outputs. These chips also contain a great deal of sophisticated control logic, which relieves the c.p.u. from many of the repetitive and mundane tasks needed to service some peripherals.

A company which is about to use a microcomputer as the processing element in a piece of equipment that is being designed for production, will purchase a development system such as the MDS (see *Wireless World*, February 1976, page 40) which will provide the necessary teletype interface and interfaces for other peripheral equipment that might be needed for the project. In addition, the MDS will provide all the other aids required such as hardware and software development and diagnostic facilities. The cost of the MDS will be amortized over all

the systems that are to be produced in this, and future, microprocessor projects.

The alternative to a microcomputer design is to use t.t.l. logic which, if the system is not a simple one, will involve a considerable amount of design effort. Once designed and in prototype form it is difficult, and expensive, to make changes since, amongst other things, circuit board artwork will have to be changed.

The microcomputer is controlled by a programme of instructions stored in read-only memory (r.o.m.). The more complex the task to be performed, the more r.o.m. will be needed. It can be said, therefore, that the r.o.m. in a microcomputer system is being used to replace the gates in a t.t.l. system. It takes between 8 and 16 bits of r.o.m. to form the equivalent of a gate. Since an average small or large-scale t.t.l. circuit contains an average of 10 gates, between 80 and 160 bits of r.o.m. are needed to replace each package. Memories are available with capacities of up to 16kbits and a r.o.m. of this size will replace between 100 and 200 gates.

It can be shown that a microcomputer replacement for a t.t.l. system requiring between 130 and 140 gates will take two circuit boards less, will consume about 14W less power and will save more than 130 cubic inches of space. This means real savings in production costs.

If we take a microprocessor equivalent of a 75-gate logic system of which 100 a year are going to be produced and include all component and production costs, it can be shown that the t.t.l. system will cost in the region of £56 and the microprocessor about £41.

A company starting on their first microcomputer design project can expect to spend around £5,000 on equipment and will take about six months to get an average system into production. This will add about another £5,000 to the cost of the project. On a second design project, using the same microcomputer family, the company will have zero capital expenditure (since they already have the equipment) and could expect to have a similar sized system in production in three to four months (since they have acquired the necessary expertise).

While writing, 1 would also like to comment on the statement made by J. O. Owen in the February issue, that "PL/M reduces the number of lines of programme by a factor of ten." This is somewhat misleading and, if I may beg a little more space, 1 would like to explain why.

What must be kept in mind is that when a microcomputer system is designed, it is usually intended that a fairly large number of identical systems are going to be produced. We know that a microcomputer is controlled by binary coded instructions stored in a read-only memory. These binary instructions are normally produced by a computer from a source programme which can either be written in the high-level compiler language PL/M or in assembly language. It is a fact of life that a source programme written in PL/M will be much shorter than an equivalent assembly language programme. The assembly language programme will, however, result in less machine code than the equivalent PL/M programme. Usually, therefore, the assembly language programme will make more efficient use of the programme store since fewer bytes will be needed, and the saving in memory capacity per system will be multiplied by the number of systems to be produced. In cash terms, the actual saving in

memory cost will depend on the type of memory being used.

On the other side of the coin, it is much cheaper to write a programme in PL/M because it takes far less time. Therefore, the increased cost of writing an assembly language programme must be set against the likely savings on memory components.

As a general rule of thumb, it is more cost effective to use PL/M for systems which are not going to be produced in large quantities - say, below 1,000 systems if mask-programmed r.o.m. is used or below 100 systems if e.p.r.o.m. is used.

'If the programme is very large or very complex, it is probably better to use PL/M regardless of the size of the envisaged production run since, in these circumstances, inefficiencies can be introduced by the programmer writing in assembly language.

Keith Chapple U.K. Manager Intel Corporation (UK) Ltd Oxford

ELECTRODYNAMICALLY INDUCED E.M.F.

The opinions and proofs relating to this old problem as expressed by "Cathode Ray" and Messrs Smith and Masson all make good sense to me. It is clear that regardless of screening no e.m.f. will be measured. I personally do not need to look for proof as the following facts show.

An important measurement in oilwells is the spontaneous potential generated by telluric currents of various sources between a downhole electrode and a surface electrode. This is made by an insulated conductor screened with two layers of steel cable which is partially spooled on a winch drum. It is a fact that if the winch is mounted on a moving barge, the EMF induced in the coiled drum by the earth's field appears as a "noise" on the signal. It is effectively eliminated by mounting a small coil in series opposition in the same field. This coil need not be screened. Again, I would ask any doubting Thomases "Would electric motors, whose conductors are often totally surrounded by iron, work if the iron was effective in screening them?"

"Cathode Ray" (September 1975 Letters) suggests cutting the dipole and inserting a perfect field-effect device to measure the e.m.f. This raises a very interesting point. When he does this, will the capacitance across any real device destroy the effect? In school physics texts we read that a sphere has a capacitance to infinity, whatever that may mean, equal to its radius. If, then we put spheres on the ends of our dipole the theoretical measurement once again becomes practical, because the capacitance created will overide, the effect of capacitance across the amplifier. As "Cathode Ray' points out, the signal must be made into a.c. by rotating it. This will not change its magnitude. The experiment is not only feasible, it can be made with existing semiconductors as the signals, assuming reasonable dimensions of the apparatus, are well above the noise level. Furthermore I have obtained the necessary field-effect amplifier and would like to invite anyone with the time to spare to make the experiment.

What will we measure? Originally I was



attempting to devise an absolute speedometer for a sailing boat. I fear, though, that what we will actually measure will be the differential component of the changing earth's magnetic field.

I include a sketch of the apparatus as I designed it some years ago. There is no need for slip rings because if it is battery operated the whole thing can rotate. There exist a number of output displays which would be legible even if rotating at high speed. R. Hunt-Grubbe.

University of Reading.

I was interested to read in your December 1975 issue Mr Gray's comments on my letter in the September issue, but I continue to maintain that the electric field perceived from the aircraft is real. Far from contradicting the principle of relativity, it is in fact a direct corollary. If the electric field were in any way unreal then the observer on the aircraft would be able to detect this and determine his state of motion without any external reference.

A correct description of the situation would be something like the following: Knowing the values of electric and magnetic fields measured in the aircraft, the navigator may calculate his velocity relative to the inertial frame in which the electric field is zero. Then, from the information that the electric field measured by a ground-based observer is zero, he is able to identify this calculated velocity with the speed of the aircraft relative to the earth.

I would also like to take issue with the other point raised in Mr Grav's letter. Unfortunately I have not been able to find a copy of his reference so I can only comment on his statement that "relative motion between a conductor and the system within which the conductor e.m.f. is to be detected is a basic requirement for electrodynamic induction of e.m.f. in the conductor". This may be refuted by a simple experiment in which a coil of wire is connected to the terminals of a meter. The insertion of a bar magnet into the coil causes an e.m.f. to be induced and the resulting current is indicated by the meter. Relative motion is, indeed, involved but not between the conductor and detector. Other examples may readily be adduced.

"Cathode Ray's" arrangement should work since, as the conductor is rotated, the electrons within it must be periodically redistributed to maintain an equipotential surface (as seen from the aircraft). The meter in the centre of the conductor will register an alternating current constituted by the flow of these electrons. Colin Masson.

Cambridge.

Assuming that magnetic field uniformity is still conditional, in the continuing correspondence relating to Electrodynamically Induced E.M.F. (Cathode Ray's letter in your February issue), I retain my belief that Einstein's axiom is fundamental to the matter under consideration.

I cannot see that Cathode Ray's reference to "the measurement of relative velocity with reference to a field in another system" has any meaning; though I would agree to a condition of velocity of the field's source, relative to the conductor with which the observer is travelling, which returns one to my original argument. Detection of the field's velocity is another matter, for which I suggest that non-uniformity is a necessity.

Acceptance of the argument for "electrodynamic" detection of absolute conductor motion would require acceptance of induced e.m.fs in a multitude of superficial conductors, moving with the earth and within its magnetic field; and I am not aware that these have become manifest. John Gray,

College of Technology, Belfast.

WAS BAIRD FOOLING THE PUBLIC?

THE letter "Was Baird Fooling The Public?" from Mr H. F. Haynes in the April 76 issue, is, I think, likely to cause confusion among readers trying to follow the various articles about the Baird half-centenary. The original article by Messrs. Waddell, Smith and Sanderson, to which Mr Haynes refers, was purely concerned with the period 1925 to 1928 about which information is sparse and frequently contradictory, thanks partly to Baird's own passion for secrecy, a trait shared by many of his contemporary rivals.

But the 30-line story extends to September 1935 (at least) and about these later years there is no shortage of information, since that august body, the BBC, was itself responsible for the regular programme of news and entertainment until December 1935. The "Televisor" referred to by Mr Haynes, in spite of many subsequent mechanical (and even electronic) rivals, continued to be the most popular type of receiver until the termination of the 30-line service, probably because of its basic simplicity, reliability and relative cheapness.

As for "synchronization over a distance" during these later years, the toothed wheel device, covered by a Baird patent, gave adequate results within the transmitter's reception limits, which were very extensive.

Whether the 30-line service gave acceptable standards for entertainment purposes, is perhaps a matter for debate. The recent practical demonstrations of the mechanical low-definition techniques by Mr E. W. Elliott at the University of Strathclyde and on the BBC programme "Blue Peter", and public shows by the Low Definition Television Association, have given a modern generation the chance to judge this issue in a direct and subjective way instead of by the largely sterile method of literary research.

Certainly, if one judges the techniques by the calibre of the artistes offering their services to the BBC for 30-line entertainments, one cannot fail to be impressed. A glance through the TV programmes of 1934 and 1935 resulted in a list of names that included some of the "top liners" of the period, all by courtesy of various kinds of "trundling mechanical image analyser" which remained supreme at both ends of the television process until the demise of the BBC service in September 35. D. B. Pitt,

D. D. 1 M.,

Chairman, Low Definition Television Association, Nottingham

Mr Haynes in a recent letter to the editor, Wireless World, April 1976, p.52, 'Was Baird fooling the public?' mentions an article written by myself and others, "John Logie Baird and the Falkirk Transmitter", Wireless World, January 1976, pp.43-46.

I feel it is Mr Haynes who is fooling the public, not John Baird. The statement in his letter that Radio Societies were amused is inaccurate. Over 600 people attended Baird's lecture, in November 1943, to the Institute of Radio Engineers in London, the lecture being on all-electronic, 3D colour television, a subject in which Baird could reliably be said to be leading the world. The Hankey Committee produced in 1945 a white paper on the future of British television. Up to 1,000 lines with 3D and colour were amongst the recommendations but, to that date, only Baird had demonstrated all three.

Mention is made of Wireless World remaining silent: this is grossly inaccurate. Following the E.M.I.-Marconi and Baird TV demonstrations at Alexandra Palace (November 1936 – Feb. 1937) Baird resumed cinema colour television, a world first. Wireless World reported this pioneering work and gave it much praise on February 17th, 1938, p.148, and August 17th, 1939.

Mr Haynes comments that Baird tried, in the late 1920's, to sell by pretence. This is inaccurate; newspaper articles by Baird in late 1928 stated that he was not yet prepared to sell television to the public on a production basis – keen amateurs could procure kits and check for reception.

I do not recollect in my article asking for "a serious study of the business and technical aspects of Baird's 30-line TV work." I asked simply for any photographic or written proof of what Baird used for TV equipment from late 1924 until early 1928. Mention is made by Mr Haynes of no synchronization: this is a strange comment, considering Baird's London-to-Glasgow demonstration in May 1927 and his transatlantic demonstration of February 1928!

Mr Haynes says that fibre optics were "well known" and not requiring synchronization. This is again inaccurate: Baird's patent (1927) on multi-fibre tube bundles was a world first, so how it could be well known to him beats me, he had to invent it first! Fibre optics still required synchronization; the fibres only eliminated a rotating lensed disc to dissect the transmitter image, but the receiver still had to be synchronized to the 'ransmitter.

I have in my possession information on

John Baird which will, on publication, do much to redress the comments still being made against Baird. I am not ashamed to admit that 1 admire John Baird's many talents and to state that in my opinion the treatment he received in this country in the lack of scientific awards and credits is little short of a national disgrace.

Dr P. Wassell, University of Strathclyde,

Glasgow

aspon

I feel I cannot let Mr Haynes' letter in your April issue pass without comment because in one respect at least, in his last sentence, it is factually incorrect.

The Wireless World did not remain silent. This may be checked by reference to your issue for 12 March, 1930. On page 277 you said in the first paragraph of an article . . . "At last a Baird television receiver built for sale to the public has arrived. As no commercial product can live that does not fulfil the purpose for which it is created, there is the obvious inference that this new apparatus functions in the way it should and that moving pictures can be received by the broadcast transmission. Without further preamble it can be stated that this receiver does give reception of images with sufficient definition to be readily intelligible." In the final paragraph of the article you said . .

"Such results will interest the enthusiast, and these have become possible since the adoption of the signal controlled toothed wheel method of synchronization first introduced towards the end of last year." The article also refers to an earlier article on p.282 of the issue for 18 September 1929 which reports the start of the 11-11.30 a.m. radio transmission from 2LO and illustrates the toothed wheel synchronizer. About this you said . . . "The aim is to provide for the rotation of a disc with a degree of constancy that after long periods of running must possess no cumulative error. In the Baird apparatus we find that this is accomplished by the phonic wheel method." You ended by saying . . . "a few facts as to the results may help others to appreciate clearly the degree of success at present obtainable. The image is viewed through a magnifier and possesses a slight, yet not tiring, flicker. Good brilliance is obtained, but with an excessive contrast between light and shade. A sitter at the transmitter is at once recognised, and his expressions considerably enhance his words which come from an adjoining loud speaker. With a little concentration one can note the time from a normal watch. Letters running past the transmitter in the manner of an advertising sign are clear and easily followed. These results, it is stated, will be obtainable on home equipment working on the broadcast service.

So, your impressions are clearly set down. But a guite different opinion was expressed in a third article in the issue for 18 December, 1929, on page 669. The author says . . "Knowing that the real difficulty in television is that of synchronizing the revolving mechanism at transmitter and receiver, no inventor can claim success who does not firstput forward a solution to this problem." He continues . . . "We know now that Baird had no important contribution to make in solving the synchronizing problem." The author of this article had applied considerable ingenuity in construction to improving the magnetic circuit of the synchronizer. It was unfortunate that he then coupled the light source and synchronizer to his output valve by a circuit different from that used by the Baird television receiver. He added four expensive and unnecessary components (a choke, two $4\mu F$ capacitors and a variable resistor (roughly the cost of 2 to 3 weeks' lunches for a student at that time) which altered completely the shape of the synchronizing pulses. That the pulses were distorted seriously is shown by his own statement in the article that, from the appearance of the pictures, it seemed that the synchronizing pulses lasted for about half the length of a line. This finding, that a method which was different in a number of significant respects from Baird's did not work, clearly does nothing but show that the author had made a mistake. The mistake was entirely justifiable in the technical milieu of that time, but it remains a mistake. The author's name? I nearly forgot; it was F. H. Haynes!

Some of us who later made the simplest possible equipment (this was dictated by cost, not insight) found that synchronization could be held over sufficiently long periods for the pictures to be interesting. Fading of the radio signal, which was then being received in Manchester from the late night transmissions, was the biggest problem. In the comparison with the cinema at that time I would agree that the results were not commercially viable. Entertainment, in anything like the modern sense, had to wait until high frequency transmission made possible a 300 times increase in the picture information. Even then, some years passed before TV became a serious threat to the cinema.

However, the results that could be obtained were just as fascinating as listening on a one or two valve short wave receiver, to snatches of intelligible messages from all over the world. That was not commercially viable as a method of communication either. If the pictures had not been worthwhile there would have been none of the drive that led to a mirror drum receiver projecting a 7×3 in picture and using a polarizer, analyser and Kerr cell to modulate the light source.

Should we not give Baird full credit for what he did do? True, others might have done it equally well. Professional engineers might have done it better. But none of them, if they tried at all, tried long enough or hard enough. What Baird did do, on a shoestring budget, by prolonged and concentrated effort is made. clear in your reports. This surely seems worth full recognition.

Prof. G. D. Dawson, McSc., Dept. of Physiology, University College, London.

I was very interested to read the letter inyour April issue from F. H. Haynes on the claims made for Baird's contribution to the development of television. Those of your readers whose memories of W.W. go back to the 1920s may recall that Mr Haynes was its assistant editor. In that position he undoubtedly looked very closely into Baird's claims on behalf of W.W. and his conclusions should not therefore be dismissed out of hand.

Leslie Bailey in his "BBC Scrapbooks" (Vol 2: 1918-1939) reproduced the following advertisement which Baird inserted in the personal column of *The Times*. "SEEING by WIRELESS. – Inventor of apparatus wishes to hear from someone who will assist (not financially) in making working.model. – Write' Box" Mr Bailey's comments are: "Baird was not a trained scientist. Indeed, it is astonishing to know that his knowledge of radio techniques at this period was so limited that he went to the staff of *The Wireless World* for help over the design of amplifiers. Mr Hugh S. Pocock, the then editor of that magazine, has written to Scrapbook: "I well remember Baird coming into the office and having a talk about his difficulties and particularly the problem of distortion which arose when he tried to amplify the shadow effects he was obtaining. We designed and built for him a suitable amplifier because at that time he had little knowledge of the correct design of distortionless amplifiers'."

P. P. Eckersley, whose ability to cut down to size anyone who made unjustifiable claims is well known to members of the I.E.E. where he so frequently entered into discussions after reading of papers, wrote in his 1941 book "The Power Behind The Microphone" that Baird possessed "that flair for picking about on the scrap-heap of unrelated discoveries and assembling the bits and pieces to make something work and so revealing possibilities if not finality."

I think it was Baird's obituary in 1948 that . W.W. said he was the catalyst in the development of television.

H. W. Barnard, Leigh-on-Sea, Essex.

PHASE AND SOUND QUALITY

Reading all those contributions on "phase effects in loudspeakers," I cannot escape from the impression that many experts do not dare to be too certain and prefer referring to the opinions of others instead. What is everybody so worried about? Undo the tweeter from your loudspeaker cabinet so that it stands off, an inch or so nearer to the listener's ear. The result is a change in phase relationship between the high- and the low frequencies, right? An inch difference in path length corresponds with something in the order of a full wavelength for a tone of, say, 10 kHz. If this is not enought phase shift, move the tweeter further, a foot or so, so that the phase tumbles several times over and over before it reaches your ear. Better still, ask somebody to move the tweeter for- and backwards for you, so that there is a continuously varying phaseshift between the high- and low-frequency components.

Why not try that on a rainy Sunday afternoon?

I did. With sounds of harpsichords, pianos, plucked strings, whole orchestras, voices, rushing water, white noise, square waves. And I eat my hat if I hear phase effects. Hans Evers,

Lammersdorf,

Germany.

Low-noise, low-cost cassette deck – 2

by J. L. Linsley Hood

Any convenient power supply circuit may be used for a.c. mains operation, provided that it can be set to give a stable, ripple-free output of 13.5-14V at output currents up to 250mA. A suitable design is shown in Fig. 8. The low-value resistor in the record amplifier supply line is to limit the supply line current surge through the changeover microswitch when the large capacitor on this line is connected in parallel with the capacitor on the output of the power supply. To avoid noise originating from the pulsating current demand from the d.c. cassette-drive motor-control circuitry, the recorder supply is taken directly from the power supply reservoir capacitor through a 20 Ω , 10W resistor, with the negative return line being also directly connected to the reservoir capacitor, rather than to a chassis return.

The chassis itself is only connected to the zero-volt line at the input to the replay amplifier.

Recording and bias levels

One of the most obscure areas in the field of tape recording, in the eyes of the layman, is the interaction between tape types and biasing levels. While much information has been published on this subject, it is often discussed in obscure terms which make the argument difficult to comprehend. Since it is possible that the construction of a cassette recorder of this type may be of interest to those with no previous experience in this medium, an attempt has been made to provide a simple introduction to this topic.

In general, it is not practicable to obtain an adequate remanent magnetic flux in a magnetic tape, for the reproduction of signal waveforms of low harmonic distortion and good output level, unless a high frequency "bias" of suitable magnitude is superimposed on the signal at the time of recording. The effect upon the various signal parameters of variations in the bias level is shown in schematic form in Fig. 9. From this it will be seen that there is not a single biasing level which is optimum for all recorded frequencies, and that the optimum level for 1kHz is in excess

Fig. 8. Power supply. The motor is fed with 3.5V by the stabilizer, but the solenoid is provided with the full 12-14V. of that which gives the highest output for, say, 10kHz. Also, the level which gives the lowest recorded noise level is less than that which gives the lowest t.h.d.

It is apparent from this that the setting of this parameter is one which demands some compromise, and the one which is chosen will depend upon the preferences of the user. In general, for cassette recorders, the chosen bias is that which gives the maximum output at 330Hz, or a slight excess of that optimum for 1kHz, and the reduction in output at higher frequencies is compensated by modifications to the record pre-emphasis curve. However, the required bias and compensation characteristics will be different from one make of tape to another, and from one design of record/replay head to another. In this design, the decision had been taken, partly in the interests of running costs, and partly in the interests of minimizing wear in the Permalloy heads, to optimize the design for "ferric" tapes rather than chrome types, and the Philips standard low noise C90 was taken as the reference. It was found, however, that the settings derived for this was also optimum for



"super" tapes of the types exemplified by Memorex MRX_2 , and BASF Super LH, although these gave an improved performance.

In general, there is very little difference in the background "bulk-erased" noise levels of most good-quality commercial cassette tapes, although there will be larger differences between the noise outputs of tapes passed through a recorder set to record at zero signal level. The greater the degree of homogeneity of the tape oxide layer, the lower the zero-recorded-level noise will be, down to a minimum which depends on the fundamental granularity of the oxide medium. The recently introduced "super" series tapes have a more uniform oxide coating, which can give a 1-2dB zero-signal background level improvement.

However, there are also improvements which have been made in the output level and harmonic distortion for a given output level, due to a more careful balance of grain shapes and sizes. The extra 2-3dB in output can lead, in total, to a small though audible improvement in overall signal-to-noise ratio (some typical results are shown in Fig. 11, and Table 1.) Useful though this is, a far greater capacity for improvement in overall performance lies in the hands of the user in a careful choice of the recording level setting. Ideally, one should record at as high a level as possible, so long as few signal peaks significantly exceed the DVU level. A 1-2dB excess is unlikely to be noticed in replay, especially with good tape, provided that the duration of overrun is brief, and the difference in s/n ratio from "correct" to over-cautious choice of record levels can readily exceed the difference between a cheap tape and an expensive one.

Probably the best way of choosing recording levels is to set the mechanism to Record but with the pause button pushed in, and in this condition to experiment with the gain settings until the optimum setting is found. when the recording can be started. In the case of a live performance, assuming one has the co-operation of the performers, it is usually possible to persuade them to execute a known fortissimo and set the record levels appropriately for this.

Noise characteristics of the system

During the development of this circuit, the sources of noise in the system were investigated at some length, since, although it was envisaged that some form of external noise-reduction system would be incorporated for use during replay, it seemed advisable to try to minimize noise in the design before taking additional palliative action. The reduction of noise in the replay circuit has already been described; if the unweighted noise level at this stage, without tape, is taken as the unit, the bulk-erased-tape noise level corresponds to about one and a half or two units, and the zero-record-level noise

(with the circuit parameters arranged in accordance with normal practice) was then equivalent to some five or six units.

Obviously there was little that could be done about the noise level of the tape, as received, but it seemed that quite a lot could or should be done about the 14dB worsening of this during no-signal recording. Indeed, if it were possible to get down to the level of the original tape, the overall performance would have been beyond reproach, in spite of the low tape speed and narrow tape width. An additional piece of evidence which seemed of interest was that the replayed noise was "whiter" than would have been expected from an original white-noise source (i.e., the tape) when replayed through the type of equalizing characteristic employed in the replay amplifier. This seemed to be a common characteristic of commercial cassette recorders, which all sounded "whiter" on the replay noise tone than



Fig. 9. The effects of changes in the h.f. bias level on output, t.h.d. and modulation noise.

Fig. 10. Record/replay frequency/amplitude curves for a variety of tapes, optimized for maximum flatness and for best square-wave reproductior



Table 1.

| Relative output at 660Hz (0VU record level) | ing |
|--|--------------------------------|
| Philips Standard C90 OVU (- Ayral C90 - Memorex MRX2 C90 - BASF Super LH C90 + | +OdB) +2dB +2dB 3.5dB |

Fig. 11. Harmonic distortion (including noise) as a function of recording level for three types of tape.



seemed reasonable to expect. It was also observed that changes in the level, frequency or shape of the bias waveform made no difference to the result. The conclusion began to grow that the problem was due to generally-distributed noise, in the source and record amplifier, being selectively amplified in the 10-15 kHz band and applied to the tape at high levels through excessive signal pre-emphasis.

64

Having become convinced on this point, the attempt was made to determine the optimum compromise between flatness of frequency response and signal-to-noise ratio for a given record level. At this stage it was found that optimization of a recorded 1kHz square wave to reduce the initial overshoot and ringing found when more conventional magnitudes of preemphasis were applied gave also the best performance compromise on bandwidth against s/n ratio. The bias levels found during this exercise were compared to those obtained by more conventional setting-up procedures, and found to be substantially identical. However, the zero-signal-level recorded noise was found to have been reduced by about 10dB by the process of square-wave optimizing, as compared to that given by frequency response optimizing. The two curves are shown in Fig. 10, and it will be seen that the h.f. loss amounts to only 1dB at 10kHz and some 4dB at 14kHz, which can be remedied by the use of amplifier tone controls on replay with very little detriment to performance.

The final conclusion is that in general far more h.f. pre-emphasis is employed



Fig. 12. Class A headphone amplifier, with a gain of 5.

Fig. 13. Low-noise microphone pre-amplifier.



on recording, in the interests of maximum flatness of the published response curves, than is sensible in the light of the overall performance, and that with more prudence exercised in this respect, noticeable improvements could well be made. Interestingly, programme recordings made before and after optimizing of the square-wave performance of the recorder did not show the expected small loss of higher frequencies, with the upper register seeming both cleaner and more extended than before, possibly due to the lessening of the incidence of h.f. tape or head saturation.

One final recommendation in this respect is that for one's own use, even on ferric tapes, the 70μ s characteristic should be used both on record and replay. However, this is a choice which can be assessed readily by individual experiment. Certainly, in the case of the author's prototype, the use of this equalizing time-constant, in association with an optimized square-wave characteristic, has given a system in which the tape noise, on a good quality tape, is sufficiently unobtrusive to render further noise reducing circuitry unnecessary.

Bias and equalization settings

It will be apparent from Fig. 9 that adjustment of the h.f. bias level of the recorder will have the effect of altering the whole response curve, by altering the effective recorded levels of the h.f. and l.f. components relative to one another, and it may therefore appear difficult to optimize either the bias or the equalization. The suggested method is therefore as follows:

• Set VR_2 so that the response curve on record is as curve A on Fig. 5., (approx. 85Ω) when measured at the output of IC_3

• Set the bias level so that there is approximately a 1-2dB drop in output at 1kHz.

• Record a square wave at 660Hz, and make small adjustments to VR_2 until the cleanest leading edge is obtained on the replayed square wave, with only a small single overshoot.

• Finally, leaving VR_2 set at the chosen value, record a 660Hz square-wave at various bias levels and adopt the one which gives the best overall square-wave shape for the tape which it is desired to employ.

The technique of square-wave optimization is well known in the audio field as a means for setting tone-controls and filters to optimum flatness, because of the facility which it offers for a simultaneous examination of a wide range of frequencies. On exactly the same score it would appear to be an excellent method of optimizing bias levels.

While it is hoped that the performance given by the prototype will prove to be fairly typical of the results given by other models built to this design, it is appreciated that in a system in which

١
not only will components vary in types and tolerances, but also the tape transport mechanism and heads (which may be changed during the manufacturer's production run for reasons of commercial availablility) may differ from those used by the author, the scope for variability is considerable. Also, from personal experience, and measurements, there is a considerable variation in performance from one tape type to another, although the consistency of performance of the bettergrade tapes from the better manufacturers appears to be fairly good. On the credit side may be set the fact that one does not have quality control problems in a unit that is one-off, and that one can optimize one's channel balance and h.f. performance for the tapes one prefers and the heads one happens to possess.

Headphone operation

Both the output level and the drive capability of the final 741s of the replay amplifier are adequate to give a satisfactory signal strength and quality into the $2k\Omega$ load impedance of the author's headphones (Sennheiser HD414), so, for simplicity, this was the course adopted. However, for those with lower-impedance or less-sensitive headphones, a suitable circuit is shown in Fig. 12. This operates in class A, and is suitable for load impedances down to 100 ohms.

Direct microphone recording

The sensitivity of the record input is only intended to be sufficient for recording from an existing audio amplifier or radio tuner capable of delivering some 50-100mV output at a fairly low impedance, and it would not be suitable for microphone inputs. For this purpose a pre-amplifier can be used, of which a suitable circuit is shown in Fig. 13. Three preset gain positions are given, of 10, 33 and 100×, which should cope with the bulk of microphones likely to be found in practice. A typical gain suitable for a low-output cardioid capacitor electret microphone is of the order of 33, for a normal recording level `at half-gain setting on the recorder.

Final details of the design will be in the final part, including information on the motor controller - lack of space prevents publication in this issue.

We are informed that components and metalwork for this design will be available from Hart Electronics, Penylan Mill, Oswestry.

Appendix

Derivation of record equalisation characteristics.

The generation of a recording pre-emphasis characteristic of the general form shown in Fig. 5 is normally done by incorporating a damped LC parallel[#] resonant circuit in the feedback loop of an inverting amplifier stage. However,



Fig. 15. Frequency/gain response of filter in Fig. 14.



Fig. 14. Basic second-order active low-pass filter (as Reference 1).

Fig. 16. Common-emitter (a) and common-collector (b) arrangements of basic circuit shown in Fig. 14.

since it was desired, in the interests of simplicity, to avoid the use of inductors, and it was also required to avoid possible trouble due to the intrusion of 38kHz signals from multiplex stereo decoders, the decision was made to use the gain/frequency characteristics of an under-damped second-order active low-pass filter, such as that shown in Fig. 14.

This is one of the classic forms of active element, and was analysed by Girling and Good¹ in the first part of their survey of active filters in *Wireless* World. It has a gain/frequency response of the type shown in equation (1) and

illustrated in Fig. 15 for various values of $Q(1/\alpha)$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1 + j\alpha \frac{\omega}{\omega_{\text{c}}}}{1 + j\alpha \frac{\omega}{\omega_{\text{c}}} - \left(\frac{\omega}{\omega_{\text{c}}}\right)^2}$$
(1)

If this is redrawn, ignoring biasing, in the form in which the amplifying element is a single, common-emitterconnected transistor, as shown in Fig. 16(a), it will clearly be seen that this can be rearranged into the common-collector form of Fig. 16(b) without significant alteration of the expression for the

65





normal gain of the stage with feedback.

$$f_{c} \approx \frac{1}{2\pi \sqrt{[C_{3}C_{4}R_{1}(R_{2}+R_{5})]}}$$
(3)

$$\left|\frac{E_{\text{out}}}{E_{\text{in}}}\right| = M\left(1 + \frac{(R_2 + R_5)}{R_1} - \frac{C_1 C_2}{(C_1 + C_2)^2}\right) (4)$$

While, basically, the Q of the system is determined by the ratios of R_1 : R_2+R_s , in a stage with a shunt network, such as that of VR₂, R_{19} and C_{15} in Fig. 4, the gain will change in the frequency region of the filter attenuation band. The associated phase shift due to this network also modifies the Q and allows adjustment of this by VR₂, which is a feature of some practical convenience.

References

l. Girling. F. E. J., and Good. E. F., Wireless World, vol. 75, No. 1406. pp 348-352.

2. Sallen. R. P., and Key, E. L., Trans. IRE., vol. 2. No. 1., pp. 74-85.

3. Baxandall. P. J., Wireless World, vol. 61., No. 1., pp. 8-14.

4. Linsley Hood. J. L., Hi-Fi News and Record Review, vol. 18, No. 2., pp. 293-294.

5. Hemingway. T. K., Electronic Designers Handbook. pp. 283-288.

Component supplies

Goldring-Lenco CRV cassette mechanisms can be obtained from Goldring Ltd, 10 Bayford St, Hackney, London E8 3SE, or Hart Electronics, Penylan Mill, Oswestry, Salop. VU meters are available from J. E. T. Electronics, 90a Mawney Road, Romford, Essex.



according to its sleeve note Problems and Solutions in Logic Design by Prof. D. Zissos, makes easy and reliable logic design techniques available to those with no specialist knowledge of mathematics or engineering. Even those who are not familiar with Boolean algebra will find an appendix giving sufficient foundation for the rest of the book. The emphasis throughout is on optimal rather than strictly minimal designs which have become less important with the availability of integrated circuits. In the case of sequential circuits, these allow hazard-free designs for the realistic engineering constraint of a maximum variation of 331/3% in gate speed. A feature of the book is the comprehensive set of problems and solutions at the end of each chapter. These have been chosen to appeal to the student and include the design of logic circuits for traffic lights, a panel game, digital clocks and electronic dice. For the practising engineer solutions are given for commonly used circuits such as flat sorters, shaft encoders and counters. After an introduction to the basic concepts of logic design, the chapters deal with unclocked sequential circuits, clocked sequential circuits, counters and combinational circuits. The design pattern used

throughout the book was developed by Prof. Zissos several years ago and is now gaining rapid acceptance. The technique involves the conversion of a design problem into a flow diagram which can be converted directly into the basic logic equations before the circuit is then drawn. The three stages are analogous to flow charting, writing the software statements and executing a computer programme. An important feature is that the documentation is inherent in the design. The use of state diagrams and sequential equations eliminates confusion in verbal statements. Price £1.75. Pp.146. Oxford University Press, 37 Dover Street, London W1X 4AH.

different context, by Hemingway5.

The operation of the filter circuit of

Fig. 16(b), like that of the Sallen and

Key configuration, can be realised by

any active element in which there is

approximately unity gain between

points "a" and "b". This allows the use,

for example, of a voltage-follower

operational amplifier as the active

circuit element, or even a non-inverting

operational amplifier having more than

unity gain, as shown in Fig. 17, provided

that an adequate fed-back gain margin

is available at the frequency of interest.

The gain and frequency of maximum

response of such a circuit is given by

equations (3) and (4) where M is the

High Speed Pulse Techniques by J. A. Coebin describes the nature of pulse signals and the deliberate or inadvertent processing of them. The emphasis is on an appreciation of circuit and system behaviour at very high and ultra high speed. It is assumed that the reader is familiar with a.c. theory, use of the Laplace transform, small-signal transistor response, and the fundamentals of logic. Price £5.00 (£3.50 paperback). Pp. 219. Pergamon Press Ltd, Headington Hill Hall, Oxford, OX3 OBW.

Noise and Fluctuation in Electronic Devices and Circuits by F. Robinson. Noise to the physicist represents a phenomena described by statistical mechanics. To the engineer, noise is an obstacle in the realization of useful devices. This book attempts to interest the physicist and be sufficiently practical for the engineer. The emphasis is entirely on the physical origins of noise in electronic devices, and the way noise behaves in electronic circuits which are used as building blocks. Price £8.50. Pp. 246. Oxford Books, 37 Dover Street, London W1X 4AH.

Japanese Consumer Electronics — Schematic/Servicing Manual. This publication contains details and schematic diagrams for about 90 products manufactured by J.V.C., Lloyds, Midland, Panasonic, Sanyo, Sharp, Sony and Toshiba. Items covered are digital clock radios, a.m.-f.m. radios, monochrome television receivers, cassette recorders, eight-track tape players and receivers. Four chapters deal with radio principles, radio, recorder, and stereo servicing, transistor and i.c. cross references, and typical circuit diagrams. Foulsham-Tab Ltd, Yeovil Road, Slough, Bucks SL1 4JH.

Recent additions to the **Tab Books** range are Radio Astronomy for the Amateur by Dave Heiserman (No. 714, \$5.95 paperback). Transistor Theory for Technicians and Engineers by A. Veronis (No. 717, \$5.95 paperback). Computer Programming Handbook by P. A. Stark (No. 752, \$8.95 paperback). Handbook of Multichannel Recording by A. Everest (No. 781, \$7.95 paperback). Toshiba Colour TV Service Manual Vol. one (from 1970 to 1974, \$5.95). Tab Books, Blue Ridge Summit, Pa.17214, U.S.A.



Fig. 17. Use of the active filter in a stage possessing gain, as in Fig. 4.

frequency response. (It was pointed out by Girling and Good that a similar rearrangement leads to the evolution of the filter circuit due to Sallen and Key² from the type based on a feedback loop containing an integrator and a lag, described earlier by Baxandall³.)

Filters of the type shown in Fig. 14, and 16(b) were used in the authors "Modular preamplifier" design (Wireless World July 1969) and the subsequent postscript to this and the earlier class A amplifier, published in December 1970. The performance of the circuit shown in Fig. 16(b) referred to as a bootstrap or "H" filter, was analysed by the author in another place⁴ and, in a

Balunamp design nomogram

Converting an unbalanced signal into a balanced one at low frequencies

by Andrew M. Stephenson

Plessey Telecommunications Research Ltd.

"Balunamp" is my portmanteau neologism for a device which converts a balanced electrical signal into an unbalanced one while providing a predetermined amount of amplification. That the gain may be less than one is irrelevant; the most important feature is that the input impedance is balanced about earth. In practice a balunamp is a special case of a differential amplifier incorporating an operational amplifier. What has been attempted is the design of a simple nomogram with which even a novice may construct a working balunamp with the minimum of fuss and false starts.

Fine. So what use is a balunamp?

Assuming that the reader is not interested in frequencies much above the audio spectrum, nor in the ultimate of performance, the device may be applied to almost any situation where it is desired to produce an unbalanced signal from a balanced one. Instances are microphone amplifiers and preamplifiers, floating a.c. to grounded d.c. converters, and line receivers.

The basic circuit is shown on page 68. This is a much simplified theoretical one; it has been left to the reader to decide what op-amp he will use and hence what other components are needed. The four resistors, R_1 to R_4 suffice to define the basic performance of the device.

The characteristics desired are

- an input impedance (R_{in}) balanced about earth or zero volts. - an output impedance which is not

balanced about earth.

– a certain voltage gain (G).

Few such amplifiers will be required to have a gain above 100. Thus if a good balance is to be preserved it is necessary to choose the values of R_1 to R_4 with care so as to take advantage of those commonly available, assuming that specials are to be avoided. This problem becomes particularly acute at lower values of G, such as 20 or below, and it is the peculiar virtue of this nomogram that it allows this choice to be made quickly and easily – more easily than by heuristic methods. Sceptics may prove this point to themselves if they wish. As this is a practical article no attempt is made to derive the equations on which it is based; essentially they are straightforward 'derivations of standard amplifier design expressions. They are given next.

Knowing R_{in} and G (defined as the output voltage divided by the differential input voltage), then

$$R_1 = R_{in}/2$$
, $R_2 = R_{in}G/2$, $R_3 = R_{in}/2(1+G)$,
 $R_4 = R_{in}G/2(1+G)$.

Two important assumptions must be pointed out: the op-amp is assumed to have an open-loop gain much greater than G, say, more than 20 times, and to have a negligible phase shift (other than 180° inversion) at the operating frequency.

From these equations one could derive values for R_1 to R_4 directly. In practice, however, some difficulty may be experienced in fitting them to real resistors; therefore their values have been calculated for G varying from 0.1 to 100, normalized to give $R_i = 1.0$, and plotted on log-log graph paper, as in the nomogram.

Next, a substitute for a sliding scale has been drawn to the right of these curves, where three decades of the standard E24 series of resistors, commonly available in 2% tolerance, $ar\epsilon$ marked.

Example 1

A balunamp having a G of 10 is required, the differential input impedance to be 300 ohms.

First draw a vertical line through G=10. This intersects the four resistor

curves at $R_1 = 1.0$ (naturally), $R_2 = 10.0$, $R_3 = 0.0909$, and $R_4 = 0.9091$.

Now these values must be scaled to give R_1 =150 ohms, this being half the desired input impedance. Sometimes it is not possible to perform this scaling and arrive at realistic values for the other resistors, as is the case here. Scaling gives R_1 =150, R_2 =1500, R_3 =13.635, R_4 =136.35. Therefore a compromise is necessary.

Often the impedance is not crucially important and may be altered slightly. Here, by extending the unscaled values of R_1 to R_4 across the E24 grid, we find that another suitable set of values is $R_1 = 180$, $R_2 = 1800$, $R_3 = 16$, $R_4 = 160$. This results in R_{in} being 356 ohms, there being an imbalance of only two ohms, or about 2.2%.

If the balance and the value of R_{in} are important, a modification must be made: an additional resistor across the input will adjust R_{in} to the right value while allowing greater flexibility in the choice of the other resistor values; thus $R_1 = 620$, $R_2 = 6200$, $R_3 = 56$, $R_4 = 560$ with an extra resistor of 390 ohms, as on p.68, gives $R_{in} = 296$ and an imbalance of about 0.65%. Naturally one may argue over the definition of imbalance, but for the applications in which the balunamp is likely to be used it is low by any measure.

Example 2

This simple case serves as an introduction. Consider another: a balanced a.c. to unbalanced d.c. converter such as



Application of nomogram to design of a.c. voltmeter - see Example 2.

might be used in an a.c. voltmeter, as shown on page 67. The desired features are: a G of 0.125 and a very high input impedance, partly to make it a useful voltmeter but also to reduce the size of the various capacitors; assume for the moment that the capacitors are large enough to be ignored in these calculations.

Returning to the nomogram, the standardized values of R_1 to R_4 are $R_1 = 1.0, R_2 = 0.125, R_3 = 0.889, R_4 = 0.111.$ Now, there will be practical limitations such as the stability of high value resistors subjected to large voltages (up to 80V here); therefore set an upper bound on the largest resistor, R1 in this case. Say R_1 to be equal to or less than 220 kohm.

Scaling with the aid of the E24 grid $R_1 = 150 \mathrm{k}\Omega$, vields: $R_2 = 18 \mathrm{k} \Omega$, $R_3 = 130 k\Omega, R_4 = 16 k\Omega, G$ is about 0.1215, and the gain imbalance is only about 0.22dB with these values, while the input impedance is 296k Ω . At 50Hz, 1µF capacitors would be more than adequate.

These two examples should suffice to demonstrate the theory of the nomogram. It is left to the reader to recognize the applications which will help him personally.

One final point: at no time has any allowance been made for offset currents or voltages. It was felt that should this be important the designer should be able to devise some means of providing the necessary balance of resistance to ground while keeping the a.c. impedances at their correct values.

Acknowlegment: Thanks to Plessey Telecommunications Research Limited, for whom the early work leading to the construction of this nomogram was done, for permission to publish this article and the diagrams associated with it.



ΟoV



v.americ

Generation of equal-tempered pitches

Robert M. Youngson

An adequate approximation to the equal-tempered musical scale can be derived from a fixed-frequency waveform by integer division. The realization of this process, by t.t.l. m.s.i. integrated circuits, is easy and reasonably economical.

Table 1 gives the frequencies of the 12 equal-tempered semitones in the octave from middle C upwards, based on the standard pitch A = 440Hz. A set of divisor integers is given with the resultant frequencies, for comparison with the standard pitches. In practice, the master oscillator frequency is selected as a convenient binary multiple of that given, so that the chromatic octave obtained by division by these integers lies above the frequency of the highest pitch required. All the necessary musical tones may then be obtained by successive binary division.

As the largest divisor in the set given is less than 256, the divisions may be implemented using 8-bit counters. Fig. 1 shows how pairs of SN 74193 counters may be connected to achieve division by the decimal number corresponding to any 8-bit binary number applied to the set of eight data inputs A,B,C,D,A',B',C' and D'. Note that the A input is the least significant bit and that logical "1" inputs may be left unconnected.

A suitable crystal oscillator circuit is given in Fig. 2 and the connections for

TABLE 1 Master oscillator frequency = (4,8 or 16 ×) 57,290.5628Hz.

| Pitch | Frequency | Divisor | Resultant Frequency | Percentage Error |
|-------|-----------|---------|------------------------|---------------------|
| в | 493.8833 | 116 | 493,8833 | _ |
| A# | 466.1637 | 123 | 465.7758 | -0.08 |
| A | 440.0000 | 130 | 440.6956 | +0.15 |
| G# | 415.3046 | 138 | 415,1480 | -0.03 |
| G | 391.9954 | 146 | 392.4001 | +0.10 |
| F # | 369.9944 | 155 | 369.6156 | -0.10 |
| F | 349.2282 | 164 | 349.3318 | +0.02 |
| E | 329.6275 | 174 | 329.2553 | -0.11 |
| D# | 311.1270 | 184 | 311.3610 | +0.07 |
| D | 293.6648 | 195 | 293.7970 | +0.04 |
| C# | 277.1826 | 207 | 276.7655 | -0.15 |
| С | 261.6256 | 219 | 261.6001 | -0.01 |

TABLE 2 Master oscillator frequency = (4, 8 or 16 ×) 963.600.00H

| - (-, 0 0 | | JJ,000.00112. | |
|-----------|--------------|--------------------|---------------|
| | - | Resultant | Percentage |
| Pitch | Divisor | Frequency | Error |
| В | 1951 | 493.9004 | +0.0034 |
| A≠ | 2067 | 466.1828 | +0.0040 |
| A | 2191 | 440.0000 | _ |
| G # | 2320 | 415.3448 | +0.0096 |
| G | 2458 | 392.0260 | +0.0078 |
| F# | 2604 | 370.0460 | +0.0139 |
| F | 2759 | 349.2569 | +0.0082 |
| E | 2923 | 329.6613 | +0.0102 |
| D# | 3097 | 311.1398 | +0.0041 |
| D | 3281 | 293.6909 | +0.0088 |
| C# | 3476 | 277.2151 | +0.0117 |
| С | 3683 | 261.6345 | +0.0034 |
| Accuracy | with these d | ivisors can be imr | roved further |

by lowering the oscillator frequency so as to distribute errors about zero. the binary division stages for the descending octaves of the chromatic intervals are shown in Fig. 3.

Variations in the frequency of the master oscillator do not, of course, have any effect on the accuracy of the relative tuning of the pitches, and if absolute accuracy is unimportant, almost any crystal can be used, extra division stages being inserted as required. In this event, a single SN 74193 would offer great flexibility in obtaining a suitable clock frequency for the set of 12 programmable dividers. Alternatively, a variable frequency oscillator, allowing immediate "one knob" tuning of the whole instrument may be preferred.

The set of divisors given offers a good compromise between relative tuning accuracy and economy and provides about the minimum of musically acceptable accuracy. The standard of precision may of course, be indefinitely improved by using even higher master oscíllator frequencies with larger divisors. A sample set using 12-bit. counters. and achieving a maximum inaccuracy of 0.013%, is given in Table 2.

This method of deriving musical tones is well suited to large scale integration, 'and implementation by l.s.i. has already been achieved.





Electronic cut-out

70

The circuit shows a practical design used to protect experimental equipment against transients. Resistor R_1 , D_1 , Tr_2 and C_1 form a rudimentary 5V supply for the t.t.l. gates. Diode D_2 prevents overvoltage at gate b input. Transistors Tr_3 and Tr_4 provide the turn-off control. Note that Tr_4 needs no heat-sink because it is used as a switch. The two spare gates, c and d can be used as an indicator. They form an astable oscillator enabled by a 0 on gate c input. Thus the l.e.d. turns on when the power is applied, and flashes when the cut-out "trips.

A variation of this circuit is a complementary version using 7400 gates and an n-p-n sensing transistor for negative rails. Bypassing R_5 with a capacitor reduces sensitivity to tran-



sients, or all a.c. signals, whereas adding a diode in Tr_1 's collector as a reverse voltage protection allows one half-cycle of an a.c. circuit to be monitored. This arrangement is possible because the latch need not have the sensed line as its power supply. The circuit is instantly reset by S_1 but, inexplicably, the circuit invariably resets when switched on. Any explanations would be welcome. C. Woolf,

Swanland,

Yorks.



Variable phase delay for digital signals

In the diagram shown the monostable circuits generate a very narrow pulse on the leading and trailing edges of the input signal. These spikes are OR-ed together and used to trigger a 9601 monostable with a period dependent on C and R. Gate e NANDS the 9601 \overline{Q} output with the input signal and causes a section of the input signal to be gated out. Gate d NANDS the 9601 Q output with the input signal thus generating a pulse at the trailing edge of S_{in}. These two outputs are effectively OR-ed by gate f to produce S_{out}, a delayed version of S_{in}.

If the signal needs to be advanced and retarded with respect to a second signal, an identical delay unit can be incorporated in the other signal line. Delays between the two signals may then assume any desired phase relationship. W. D. Gunn, Claprethes

Glenrothes, Fife.



Wideband Y amplifier for oscilloscope

71

Transistors Tr₁ to Tr₄ operate as a constant-current tail with Tr₅ added to improve linearity. This draws 6mA down each side of the amplifier and results in a voltage drop of nearly half the 200 volts across each $18k\Omega$ collector resistor. Driven by this voltage, and with a slight forward bias provided by the 100-ohm preset potentiometers and diodes, Tr₆ and Tr₇ act as complementary emitter followers. They have their counterparts in Tr₈ and Tr₉ and both sets have a quiescent current of about 3mA. Bandwidth of this circuit seems independent of output capacitance loads up to 200pF and appears to be only limited by the $18k\Omega$ resistors and the collector-base capacitance of the complementary pairs. Rise time of the circuit is 40ns, which improves to around 30ns with compensation. A bandwidth of 10MHz was easily obtained by driving the amplifier from a 50Ω source. An increase in the speed canprobably be achieved by increasing the tail current and lowering the value of the $18k\Omega$ resistors at the expense of increased dissipation. Any complementary small-signal transistors capable of withstanding above 200V can be used, but a supply current-limited at about 20mA is advisable.

B. J. Frost, Paignton, Devon.

Class A power amplifier

This circuit was designed using easily available components. Its operating conditions are unconditionally stable, unaffected by individual transistor parameters and the transistor types are not critical. Short-circuit protection is provided by the constant-current source D₁, Tr₂, Tr₅ and Tr₄. Transistor Tr₄ may be omitted if short-circuit protection is not required. The amplifier may be altered for a different load, impedance (R) or power output (W) by putting the output-stage current I = 2W/R, and supply voltage equal to $2 + 0.61 + 2\sqrt{2WR}$.

Dissipation in the output transistors is roughly $W \times 4$ watts, so the heat sinks need to be adequate. The amplifier shown will deliver 10W into an eightohm load. Diode D₁ and Tr₂ should be in thermal contact.

A. H. Calvert,

London NW1.



* adjust to make point X half the supply voltage (if necessary)

Voltage-controlled ramp generator

72



By using the 555 timer as an astable multivibrator with the charge current supplied by a transistor, a wide frequency range can be covered. With the values shown, the range is greater than 0.2Hz to 20kHz. Potentiometer R_1 sets the lowest frequency, R_2 sets the

average output to zero volts, and R_3 sets the output level. The voltage/frequency relationship is logarithmic which makes the oscillator suitable for use in sound synthesizers.

J. L. Brice, Fulwood, Preston.

Linear d.c./d.c. opto isolator

The circuit shown was initially designed to provide input isolation for mains related thyristor converters. Diode turn-on voltage is rendered insignificant by the amplifier loop gain, and temperature effects are minimised by close tracking of the isolator characteristics. Linearity is within 2%. The circuit may be re-arranged to achieve alternative input/output polarities and operate with other power rails. Resistor R_L must, however, be chosen to limit diode current to 20mA, and the supply rail which provides the feedback current (positive in the circuit shown) must be at least V_{in} + 2 volts. R. J. Haney, Fletching, Sussex.



L.e.d. display

The low voltage and relatively high current requirement of l.e.ds means that when used in the normal way as digital indicators considerable power is wasted. In battery equipment with reasonably high voltages and where a number of indicators are required, it is advantagous to connect the l.e.ds in groups using a constant-current source for each group. The diagram shows a circuit to display a four-bit binary number from a c.m.o.s. counter. T. R. E. Owen,

University of Cambridge.



Low-frequency triangle wave generator

In this generator circuit (Wireless World, May 1976), R_2 in parallel with R_3 is greater than 10k Ω and not R_2/R_3 as shown. Time t is $C_1R_1R_3/R_2$ and F is $1/T = R_2/4C_1R_1R_3$



Contributors to Circuit Ideas are urgea to say what is new or improved about their circuit early in the item, preferably in the first sentence.

Wireless World, June 1976

A good image gets around.

RG Switzerland SRG Switzerland SRG Switzerland SRG Swit France TDF France TDF France T **DF France TD** V USSR TV USSR TV L SSR TV USS Australia ABC Australia AB 3C Australia tes ABC United States AE C United Sta **BBC Great Britain BBC** C Great Brita BC Canada CBC C Canada CBC Inited States C 3 United States C istralia ITV Au Australia ITV Aus vakia T hoslovakia TV Cze V Gre areat Britain IT V Gre United States NBC New Zealand NZE ustria ORF Austria rian TV Hungarian T TV Polish TV Polish TV Po G Switzerland SRC vitzerland SRG Switzerland

EEVs Leddicon[®] is the consistent colour tube.

The EEV Leddicon[®] is the advanced lead oxide colour tube made with high purity materials to the most precise standards.

Ease and speed of line-up are exceptional. Perfect colour registration can be achieved in seconds. Geometry is precise. Manufacture is consistent. Tube dependability is excellent.

EEV Leddicons are in use with most major colour networks. A good image gets around – and so does EEV service. All EEV camera tubes are available across the world from local representatives.

For your nearest contact, please write to EEV at Chelmsford, Essex, England.

B Leddicon is a Registered Trade Mark of English Electric Valve Co Ltd

| Leddicon Type | Application | Features | Leddicon Type | Application | Features |
|------------------|---|--|------------------|---|---|
| P8000 | Monochrome Luminance + Chrominance channels | Jømm diameter. Integral mesh construction. | P8130 | Monochrome Luminance + Chrominance channels | 30mm diameter. coaxial construction. Separate or integral mesh. Fixed integral light bias. |
| P8001 | Monochrome Luminance + Chrominance channeis | 30mm diameter. Separate mesh construction. | P8131 * | Monochrome Luminance 14 Chrominance channels | Similar to P8130 series but with variable integral light bias. |
| P8003 | Red Channel LuminanCe/green Channels MonoChromè Channel | 30mm diameter. Separate mesh with extended red response, with or without IR faceplate fitter. | P8132 | Red Channel Luminance/green channels Monochrome channel | Similar to P8130 series but with extended red response, with or without IR faceplate filter. |
| P8005 * | Monochrome Luminance + Chrominance channels | 30mm diameter. Siaparate mesh. Improved lag under Icw-light conditions. | P8133 * | Red Channel Luminance/green channels Monochrome channel | Similar to P8131 series but with extended red response, with or without IR faceplate filter. |

* Uses integral light bias but requires socket modification and bias supply.

EEVand M-OV know how.

, ENGLISH ELECTRIC VALVE CO LTD, Cheimsford, Essex, England CM1 2QU, Tel: 0245 61777. Telex: 99103. Grams: Enelectico Cheimsford. 🛛 🕫 🕑 🖻



73

WW - 009 FOR FURTHER DETAILS

We've driven germanium out of its last stronghold

Until a short time ago germanium's last stronghold seemed to be the TV tuner.

74

In fact this was the only application left in which the germanium transistor had not yet been replaced by the silicon type.

It wasn't easy for silicon to conquer this field; after all the germanium transistor worked very well, and there did seem to be insurmountable difficulties in the production of equivalent silicon types.

We at SGS-ATES met the challenge when we created the family of PNP silicon transistors which combined the characteristics of germanium and the reliability and stability intrinsic to silicon.

In addition we gained improvement on some important parameters such as noise.

Today these products have become standard for industry, and over 20 million pieces have already been sold.

And now 5 GHz!

An achievement unthinkable during the era of germanium. Today SGS-ATES presents the BFT 95, a 5 GHz PNP silicon transistor with NF = 2 dB at 1 GHz.

Low noise, high gain, minimum intermodulation distortion,

low cost T-plastic package, make it ideal for wide band



amplifiers and converters in the 1 GHz frequency range.



SGS-ATES (UNITED KINGDOM) LTD.



vww.americanradiohistorv.com

Broadcasting's biggest

Highlights of the National Association of Broadcasters 1976 Convention reported by Pat Hawker

The NAB convention and exhibition returned this year to Chicago: by moving into the massive new McCormick Place exhibition centre on the shores of Lake Michigan, the 54th annual convention was able to reach new heights in size and scope. With well over 200 firms participating — including many from Europe — some 6,000 visitors and 4,000 industry representatives it reflected for those more used to Montreux and IBC in London the significant differences in broadcasting outlook and practice in North America and Europe.

At NAB broadcasting is an industry or trade; the attraction of any new equipment tends to be evaluated directly on whether it will increase the appeal of a station to its audience by jumping ahead of the competition or whether it will reduce operating costs or provide better coverage. Higher technical standards, if these are beyond those required to meet FCC regulations, or whose advantages will not accrue for some time to come - such matters are not for NAB unless as a means of securing commercial prestige. Montreux and IBC may give you a better idea of what broadcast engineering will be like in ten years' time - but NAB provides a wonderfully exciting and dynamic panorama of what the stations will be doing in the months ahead, provided that the new products stand up to the hard assessments that constitute the American form of Operational Research.

It is easy to say that the Americans do not have the same engineering dedication as Europeans to high standards of technical quality; that many of their television programmes would never make British screens. But when one considers what is available (for no licence fee) in metropolitan areas such as Chicago - where over many, many hours each day there are three network-affiliated stations (CBS, NBC and ABC); the local independent WGN; a public broadcasting/educational station on a v.h.f. channel (carrying much British and European programme material); a clutch of u.h.f. stations; and separate streams of m.f. and v.h.f. radio

stations — it is difficult not to have at least a sneaking feeling that there is more to American broadcasting, as it is today, than is sometimes conceded over here.

Electronic journalism

News has become a major element in American programming and is still evolving rapidly. This is particularly true in the area known as "electronic news gathering" (e.n.g.). The use of electronic cameras as a replacement for film in news operations has made rapid progress in the past few years (ITN with a compact Range Rover unit have been active in this field). But the emphasis in the States is towards even smaller and lighter equipment, requiring less technical support, and even the complete elimination of news film by some stations.

E.n.g. fulfils the criteria for appeal to American broadcasters: it can provide more national and local news inserts, including 'live' and late news, making newscast more attractive to audiences; potentially it offers (at least debatably) economic advantages if film processing can be eliminated and tape is re-used and not stored for possible archival purposes. But against these must be set the proven reliability, low capital cost and ease of transportation of film, and film cameras.

The past 12 months have seen a number of North American stations convert to all-electronic news, many more to hybrid e.n.g./film working; and many sitting on the fence waiting to see what the competition will do.

All-electronic news became possible with the appearance of light-weight "portable" (though often heavy) backpack cameras and more especially with the improvement in low-cost helical video recorders such as Sony U-matic or JVC units that became possible with digital time-base correctors. Now firms are rushing out new products specially designed for e.n.g. and to eliminate some of the reliability problems that do arise. Cables, cable connectors, head cleaning on recorders, batteries, "instant" interference-free microwave links and general maintenance all give more headaches than the early e.n.g.-advocates anticipated, but these problems are being tackled vigorously in the new designs.

E.n.g. cameras featured at NAB included the Thomson-CSF (CBS Laboratories) "Microcam" which sets a new record for an all-up weight of 13 lbs for a camera based on three 2/3-in. Plumbicons with built-in image enhancement. Camera head including lens weighs 8lb, a shoulder-slung hip pack weighs 3lb, and a typical battery belt weighs 11b. Power consumption is 22 watts, including viewfinder. It is claimed the camera can be fully operational in 4 seconds from switch on. First production units are due to be delivered to CBS this, summer. Size and weight reduction has been achieved largely by the use of l.s.i. circuits.

Other lightweight e.n.g. cameras include the RCA TK76 (shown at Montreux 1975) of about 28lb all-up weight; several Ikegami units including the HL77 with no back pack and weighing 6 kg (plus lens and viewfinder); the NEC MNC-61, again with no back pack, and weighing some 6.7 kg including viewfinder and hand grip; the Hitachi SK80 with a basic weight of 7.5kg. Many other portable cameras including those using 1-in lead oxide vidicons are being offered either for e.n.g. or as portable production or sports cameras, although some call for a strong cameraman rather than camera person. Many use 1-in lead oxide vidicons to give quality comparable with studio cameras.

Another area where considerable development can be seen is in microwave link equipment where it is not only required to set up links quickly and easily but where problems are being encountered in mutual interference between competing teams and those presented in such areas as New York due to high buildings. Trends include "guad polarization" for pick-up, allowing remote selection of right-hand or left-hand circular polarization or vertical or horizontal polarization, often also with remote selection of direction. The mobile units often use circularly polarized aerials.

Nurad have a new 2 GHz "Golden-

Video tape recording

For the past five years or so the "format controversy" of video tape recording has been waging, but most television broadcasts continue to be based on 2-in quadraplex machines — even ENG material is often transferred to 2-in cassettes for transmission. With the issue to RCA, Philips and IVC of licences for the manufacture and marketing of the Fernseh 1-in BCN series of helical scan recorders, and the introduction of a new Sony 1-in unit (BVH-1000), the stage is set for more general acceptance of 1-in tape.

The IVC-Cintel 9000, a 2-in superband helical-scan studio machine, appeared at NAB in a new guise as the IVC 9000-4 half-track machine for archival purposes, where a 3 dB lower signal-to-noise performance (47 dB instead of 50 dB) can be tolerated.

Ampex introduced their new AVR 3. machine aimed at operators seeking modern replacements for the widely used VR2000-series. This uses the super high band plus pilot tone technique which Ampex first demonstrated on 625-line PAL. The pilot tone at 1.5 times colour subcarrier is claimed to provide superior autochroma and time base corrector performance, resulting in reduced head banding and reduced moirè patterning. The AVR3 is the first use of this system as an integral part of the design including automatic switching between normal high band and super high band pilot on playback. Ampex however has for this model abandoned the vacuum-buffered transport system that they introduced with the AVR1 to provide virtually instantaneous lock-up: in the AVR3 lock-up is achieved in 1-2 seconds.

Although the machine was not shown, J. Dierman of Ampex presented a detailed paper on the company's "electronic still store" the first delivery of which is due this summer to CBS. This is designed to replace the large collections of slides and graphics held by most broadcasters (it is suggested that the average broadcaster has a slide library of 3000 to 5000 items) by using computer disc drive techniques to store the material digitally. The system provides instant random access to 1472 stills and can store additional graphics off-line: still sequences can be assembled in advance. The basic storage medium is gamma ferrous oxide coated on to a thin aluminium disc.

A rather similar application was demonstrated by RCA with its optical disc recording system which can store up to 10,000 still pictures on a 12-inch disc. This is based on the original RCA video disc system and is distinct from the firm's later Selectavision technique with capacitance pick-up seen as having consumer applications. Although the optical system was shown working effectively on stills (it could be used for motion) no attempt was being made to indicate the appearance of an early production model, with final development put at 2 to 5 years away. RCA, however, are now offering a half-speed (7.5in/sec) version of their TR600 video tape recorder and also a modification kit including 6mm headwheel tip and use of super high-band f.m. for existing machines.

Other video memory systems include a 3M D8000 system and an Arvin/Echo "video frame-store" handling 400 stills.

As a lower cost arrangement to the massive video cartridge machines, Recortec have introduced a "video spot assembler" which is intended for use with two vacuum-buffered tape machines. The assembler itself is priced under \$9000.

Apart from the IVC 9000-4 and the Fernseh BCN series, a number of new broadcast helical scan recorders have been introduced including a new 1-in Sony BVH-1000 with a tape speed (525-line) of 9.63 in/sec and claimed to be the only machine that eliminates head band flicker by recording in the vertical gap. It is being marketed with built-in time coding, and a 625-line version is expected in 1977.

Transmission

One of the problems which have faced u.h.f. stations using relatively low-efficiency multicavity klystrons has been the rising cost of electricity. This has often meant that with power amplifier efficiency less than 25 per cent the cost of maintaining a high power transmitter on the air has been significant. In recent years a number of klystron manufacturers have shown that efficiency can be increased to just over 40%; at NAB John Bullock of RCA and Robert Schmidt of Varian Associates presented a joint paper on a new approach to klystron operation that could further reduce power consumption by up to about 13%. This pulser or electronic switching system makes use of the fact that maximum output from the klystron is required only during the sync periods, representing on 525-lines just 8% of the total time. At other times the beam current can be significantly reduced, using radar techniques, by reducing the mod. anode voltage from -- 2000 to -4000 volts provided that greater linearity correction is applied. The bi-mode system has been developed for use with Varian "H" type klystrons and it has been estimated that for 16-hour per day operation annual savings of between about \$3500 to \$7000 arepossible with high power u.h.f. transmitters.

Power saving is also seen as one of the attractions of all-solid-state m.f.-a.m. transmitters; Harris, Sparta and RCA

Wireless World, June 1976

were among the firms showing or announcing designs from 1 to 5 kW. RCA were also demonstrating their a.m.-f.m. m.f. stereo system - one of five m.f. stereo systems already proposed to the National AM Stereo Committee of the Electronic Industries Association. This committee is due to report in the Spring of 1977 but it will be some time before FCC is ready to accept a national system. The recent industry report on discrete quadraphonic systems has apparently left the matter up in the air since no direct inter-system comparisons are provided: meanwhile about 100 f.m. stations in the United States are using matrix quad encoders and several hundred are playing matrix encoded records. If a.m. stereo becomes established this could be a serious blow to the f.m. stations who still find it difficult to attract majority audiencesbut undoubtedly would provide a boost for m.f..

Automation of radio stations continues to attract interest although the aim is now often to provide hybrid systems that have the appearance of being "live" stations. A new emergency broadcast system has just been introduced in the United States.

For many years the planning and operation of the m.f. band in the United States has been the envy of European broadcasters, with the effective use of directional aerials and day/night switching. However some U.S. operators are alarmed at the increasing number of extremely high power stations in the Caribbean not under FCC control.

Several firms have developed circularly-polarized v.h.f. and u.h.f. for television transmissions following field trials by RCA (v.h.f.) and Jampro (u.h.f.). To achieve true circular polarization - in terms of good axial and polarization ratios in all azimuth directions for broadband television transmissions - is by no means easy, and if, as seems likely, there is progressive utilization of this technique in North America it is likely to be an expensive undertaking (European use will probably be limited because of the use made of polarization discrimination). Certainly the field trials indicate that considerable reduction of ghosting is experienced by many viewers (especially those using bow-tie aerials). Harris have developed circular polarized v.h.f. aerials using a cavity-backed radiator. So far FCC have authorized only experimental use of circular polarization for television broadcasting.

Digital techniques

A year or two back, NEC introduced a series of large digital framestore synchronizers designed to allow any nonsynchronous colour signal to be locked to the local station sync, and thus to be handled as a local source without special gen-lock techniques. This year Quantel (DFS 3000), and RCA (TFS 121) both show how it is now possible to

t

provide these facilities in a compact unit. The DFS 3000 for instance is packaged complete with power supply and associated analogue circuitry into only 8.75-in of panel space. Prices of framestores are in the region of \$50,000.

Apart from the time-based correctors and frame-store synchronizers, there were few signs that the Americans are thinking as seriously as Europeans of digital video throughout a studio or for transmission networks — although digital control and computer techniques are prominent. The convention papers and discussions on digital video were generally disappointing and undoubtedly the single most-sophisticated digital equipment on display was the first of the Marconi-built DICE (standards converters, to the IBA design.

The recent decision by FCC to permit much wider use of unattended operation of all classes of broadcast transmitters will undoubtedly be reflected in more use in North America of interval test signals and automatic measuring equipment of the type already in use in Europe, and several firms were showing sophisticated systems developed in Europe.

British and European firms were prominent. With the acquisition of CBS Laboratories, CSF-Thomson appear to have moved firmly into North America in a similar manner to Philips. Marconi had their largest display ever at NAB. Rank Cintel featured their new Mark 3 capstan-driven flying-spot colour telecine unit suitable for NTSC operation. Evershed Power-Optics, EEV, Marconi Instruments, Matthey Printed Products, Quantel, Racal, Amplivox, Rupert Neve, W. Vinten and several of the Rank companies were among those present at NAB.

Communications-systems of all types are proliferating, partly as a result of the emphasis on news gathering both television and radio. ABC in New York have been experimenting with extra sub-carriers on their television sound channel — similar to SCA f.m. radio techniques — to provide communications cueing and one-way communication with outside-broadcast units. A related development are more complex multi-channel radio microphone systems (Thomson-CSF are marketing a u.h.f. unit made by RF Technology suitable for up to 15 radio-microphone channels). A recently introduced "Optimod-FM" system by Urban is claimed to raise modulation levels by 2-3 dB with less than 0.25% distortion.

In brief, NAB 1976 was an exciting, rewarding reflection of broadcasting trends in North America; both for broadcast engineering and broadcast management.

Grateful acknowledgement is made to Mr Howard Steele, Director of Engineering, IBA, for permission to publish this report — the views expressed, however, are solely those of the author.

Electronics à Paris

New products at the Paris component show

The air of economic despondency of the previous Paris components show seemed to have disappeared this year although it was difficult to tell if this was a result of enthusiasm on the part of the organizers or of an increase in trade. The number of exhibitors this year (1013) was less than the previous year (more than 1100) mainly due to there being no section for test and measuring equipment. This aspect is to have its own venue in Paris at a later date.

Turnover in the French electronic component industry declined 6% in 1975. The semiconductor and capacitor branches were the hardest hit, their figures being down 24 and 15% respectively. Signs of a recovery appeared in the final quarter of 1975 in the consumer goods field which had been the worst affected early in the crisis along with data processing equipment. The French electronic components industry faces a less gloomy climate in 1976, a marked feature being the upturn in orders for consumer goods. Underlying trends in the international components market are a cause for reasonable optimism between now and 1980 even though competition is likely to be increasingly

tough with new component manufacturers appearing particularly in the developing countries.

A single-chip, 8-bit, 40-pin c.m.o.s. microprocessor, the CDP1802, was launched by RCA. Also introduced by this company were several new memory and timekeeping devices using silicon-

on-sapphire plus numerous additions to the range of c.m.o.s. and linear integrated circuits, power transistors and resistors. The CDP1802 microprocessor family is a development of the existing CDP1801 series, but with the two c.m.o.s. chips in the earlier microprocessor replaced by a single chip using self-aligned silicon-gate fabrication. Although compatible with the CDP1801 series, it is faster and is supplied with a wider range of instruction sets. Typical of the new range of RCA silicon-on-sapphire memories is the MWS 5001, a 1024 \times 1-bit r.a.m. with an access time of 150ns for only 4mW of operating power. Operating



temperature range is -20 to $+85^{\circ}$ C and voltage range is +4.5 to 6V. A colour TV receiver featured by RCA contained several novel circuits. The horizontal deflection system for the 110° precision in-line tube combined a switched-mode power supply with a thyristor deflection circuit. The main point here was that no input inductor is required and the chassis is completely isolated. A similar system was also demonstrated by Videocolor S.A., a joint venture of Thomson and RCA.

An array of new products was exhibited by Plessey. These included two new ranges of circular connectors now in production, together with an interrack wiring connector for telecommunications use. New capacitors exhibited included examples from the recently announced improvements to the 400V a.c. general purpose range which now has a reduction in physical size of up to 25% together with an extension of capacitor values so that values from 0.5 to 20µF are available. The Minican range of aluminium electrolytic capacitors has been extended to much larger capacitance values, up to 360,000 µF. Being shown for the first time were smaller additions to the 1.60 Minibox series of low-cost miniature metallized polyester capacitors. The new values have radial leads at 5mm separation.

A new miniature chip tantalum capacitor to complement the use of ceramic capacitors on thick-film hybrid circuits was announced by Sprague. The type 194D Midget is available in eight chip sizes. Capacitance ratings at the lowest working voltage range up to 100μ F while at the highest working voltage the maximum capacitance is 4.7μ F. The new capacitor can be reflow solder-attached to substrates at temperatures up to 300° C for three minutes without damaging the electrical or mechanical characteristics of the capacitor.

The SGS-Ates BFT95 is a new 5GHz silicon p-n-p transistor with low noise (2dB at 1GHz) intended for high-volume radio-frequency applications such as antenna amplifiers and cable TV. The device is constructed with the Planax silicon nitride technique and is mounted in the SGS-Ates T-plastic package using a copper alloy frame to withstand high currents and thus achieve an improved cross-modulation level. The device has a forward transmission gain of 10dB at IGHz. The BFT95 will shortly be followed by another device able to handle even higher signal levels and designed for ultra-linear output stage applications. SGS-Ates has also developed three high-voltage, high-current Darlington transistor arrays each consisting of seven silicon n-p-n Darlingtons. The L201 array is suitable for d.t.l., t.t.l., p.m.o.s. and c.m.o.s. The L202 is designed for use with 14 to 25V p.m.o.s. elements and the L203 allows operation directly with t.t.l. or c.m.o.s. operating at a supply voltage of 5V. The three devices have an output sink capability



New tantalum miniature capacitor chip, the 194D Midget introduced by Sprague is available in eight sizes.



Pye has introduced a range of foil polystyrene capacitors encased in a newly developed plastic. They are claimed to have high reliability, low self inductance and low series resistance.



Augat's single-in-line terminatingresistor adaptor plug.

maximum of 500mA with a specified level of input current at 50μ A.

One of the most interesting stands was that of Thomson-CSF on which several novel demonstrations took place. The TH7601 flat screen display was operated as part of an alphanumeric storage display terminal. The characters of the display could be generated either from an associated keyboard or read from a punched tape where they had been previously stored. Also demonstrated on the Thomson stand was an experimental system of video transmission by optical fibres and video image delay using a THX1105 charge transfer device. The monitor display consisted of two juxtaposed images one arriving directly, the other having been delayed by the chargecouple device. Each TV line was treated separately, the time lag being constant for each line but being adjustable by modifying the clock frequency of the THX1105 (number of elements: 256,

distortion: 1%, dynamic range: 60dB, delay-bandwith product: 128 and clock frequency: 10kHz to 10MHz).

Siemens are investigating the use of optoelectronics in transistor car ignition units. Ignition units are already in existence in which the mechanical contact breaker points have been replaced by Hall effect generators or inductive type transducers - a light barrier provides an even simpler and longer lasting solution. The high operating temperature of the internal combustion engine to which the optoelectronic elements would be exposed presents difficulties but development work by Siemens has shown there are good prospects of being able to supply suitable light-emitting diodes and phototransistors with an adequate resistance to high temperatures. Siemens has a new m.o.s. device available for manufacturers of multimeters. The device incorporates a four-decade counter and automatically selects one of four possible current or voltage ranges in decade steps. This circuit, S190, has automatic polarity selection and a power dissipation of 50mW.

Several new additions to the Thorn Brimar range of cathode ray tubes were on view including a working demonstration of the smallest monitor tube yet produced by Brimar, the M8.100GX. Designed for avionic applications, the tube is also suitable for other alphanumeric applications where compact, low profile presentation is required. The Brimar TBK3 is a deflection component kit for use on 70°, 90° and 110° cathode ray tubes with 20mm diameter necks. This kit provides a typical final anode voltage of 11kV from an 11.5V d.c. supply and the various auxiliary voltages required by the circuit.

International Electronics S.A., a Greek TV tube manufacturing company were demonstrating a new TV tube whose screen was designed for operation in high incident light conditions. No detailed information is available yet but the tube has a dark raster and is used for both colour and black and white tubes.

News of a new processing technique was released by Isotronics who have begun production of a type of hermetic window which uses a new method of glass-to-metal hermetic sealing permitting high transmission of ultraviolet light for quick erasure of the programme material stored on erasable memory devices. The window can be sealed onto the package with a low leakage level. Windows presently used are made of quartz which also has high transmission of u.v. However, quartz requires time consuming and expensive finishing processes such as mechanical machining and lapping. The new window from Isotronics is claimed to be not only inexpensive to manufacture but easy to seal to the semiconductor packages. The first windows being manufactured are in a form suitable for solder sealing.



Deflection yoke

A colour deflection voke, the type GI 1080-1, has been introduced by General Instrument (UK) Ltd. Intended for use with the Philips 26-inch 110° picture tubes type A66-500X (in for example the Philips 20AX system), it can be used in conjunction with an associated beam, centering device type 1081 or similar assembly. The yoke housing is moulded from self-extinguishing plastic. Saddle coils of the pegged type are used for horizontal and vertical deflection whilst a toroidally-wound quadrapole winding on the ferrite core is used for convergence tolerance corrections. The yoke can be adjusted within the housing after fitting to the TV tube. General Instruments (UK) Ltd, Cock Lane, High Wycombe, Bucks.

WW 301 for further details

Capacitance meter

The ESP 200A linear capacitance meter from Electronic Services and Products Ltd is designed for fast, accurate measurements on a wide range of capacitors. Capacitances ranging from 1pF to 50μ F may be measured simply by selecting the appropriate range and reading the value direct from the meter; no balancing is necessary. The instrument, which is housed in a robust metal case, has a stabilized supply and can be connected directly to a chart recorder for plotting capacitance changes. Short term stability is better than 1% of the meter reading. Electronic Services and Products Ltd, Cross Lane, Braunston, Nr. Daventry, Northants.

WW 302 for further details

Universal breadboard

Up to 36 14-pin d.i.ps can be fitted to a breadboard from GDS. The board, called the "All Circuit Evaluator," is intended for fast, solderless circuit building and testing, and consists of a matrix of 3,648 plug-in tie points. consisting of 512 separate 5-point terminals. 32 vertical distribution buses and 4 horizontal buses. The vertical buses each have five connected 5-point terminals, and the horizontal buses éach have eighteen 4-point types. Any combination of links may be made between buses to provide both unique and common circuit functions. Components are simply plugged into the breadboard terminals and interconnections are made easily using ordinary 22-gauge solid wire. No special patch cords are required. The tie-point material is a non-corrosive nickel-silver with acetal-copolymer dielectric, and the base, which serves as a ground plane, is made from anodized aluminium. Rubber feet are fitted to prevent sliding. The overall size of the breadboard is $10\frac{1}{4} \times 9\frac{1}{4}$ in. GDS Sales Ltd, Michaelmas House, Salt Hill, Bath Road, Slough, Bucks.

WW 303 for further details

Logic troubleshooter

Hewlett-Packard have introduced a probe which can indicate digital states and the presence of pulses in both high-level c.m.o.s. and low-level t.t.l. The logic probe, designated as model 545A, has been designed for simplicity and speedy logic circuit testing. A single lamp display's high, low, unacceptable or open circuit conditions, and it is claimed that this probe enables almost all positive logic up to +18V d.c. to be sensed, including d.t.l., r.t.l., h.t.l., n.m.o.s., m.o.s. and high noise-immunity logic. The probe also features a pulse memory which controls the indicator lamp switching when logic changes occur. A pulse stretching facility allows the operator to see fast pulses - as short as 10ns - pulse trains up to 80MHz being detected in t.t.l. and up to 40MHz in c.m.o.s. logic. The hand-held probe, which requires a supply of up to 15V d.c. on t.t.l., and up to 18V d.c. on c.m.o.s., is protected against voltage overloads. Hewlett-Packard Ltd, King Street Lane, Winnersh, Wokingham, Berkshire RG11 5AR.

WW 304 for further details

Low cost solenoids

N.S.F. have introduced the Ledex "D frame" range of solenoids, designed for simplicity, high performance and low cost. The solenoids, which have a dielectric strength of 1000V r.m.s., may be supplied for operating voltages ranging from 6 to 240V d.c. or 60Hz a.c. Design features include a plunger cavity as an integral part of the nylon/glass bobbin, a dichromate-treated cad-mium-plated frame and multiple tapped mounting holes for easy installation and interchangeability. N.S.F. Ltd, Switches and Controls, Keighley, Yorkshire BD21 5EF.

WW 305 for further details



WW 301 for further details



WW 302 for further details

WW 303 for further details





WW 306 for further details



WW 307 for further details



Wireless World, June 1976

Spectrum shaper

The Kemo type 495 spectrum shaper has 36 channels, the input to each being adjusted by slide attenuators (patch panel optional). The outputs from each channel are summed and applied to an equalized output terminal. Each channel may also be selected by means of a rotary switch and applied to an output terminal. Provision is made within the system to fit two Kemo KA1193, n = 19. pseudo-random Gaussian noise sources which may be switched in at will. Main specifications are: frequency range 1Hz to 100kHz, filter accuracy $\pm 2\%$ of centre frequency, filter level accuracy ± 0.5 dB, maximum equalized output signal $\pm 10V$ peak into $2k\Omega$, output impedance 51Ω. Kemo Ltd, 9-12 Goodwood Parade, Elmers End, Beckenham, Kent BR3 3OZ.

WW 306 for further details

Portable oscilloscope

Small size, light weight and simplicity of controls are the features of the S22 single-beam portable oscilloscope. The Telequipment instrument can be operated from its internal rechargeable batteries, or direct from the mains supply. Although the instrument is small enough to pack into an attache case or tool box, it contains a relatively large screen size of about 6×3.6 cm. Normal bandwidth of the oscilloscope is 5MHz at 10mV sensitivity, but a gain switch enables the sensitivity to be increased to 1mV for a bandwidth of 1MHz. Tektronix UK Ltd, Beaverton House, P.O. Box 69, Harpenden, Herts.

WW 307 for further details

Fast response recorder

The WTR771 portable Miniwriter, made by Environmental Equipments Ltd, is a single-channel fast-response recorder having a 40mm chart width and a frequency response from 0 to 60Hz. This model, which supersedes the WTR711 Miniwriter, features a thermal writing system incorporating an automatic heat control which, it is claimed, improves the record obtained. The WTR771, which has a higher sensitivity and improved chart speed accuracy, has 14 switched input ranges, having a maximum sensitivity of 10mV/cm on the standard version, and 0.5mV/cm on the high-sensitivity version. Chart speeds range from 1 to 50mm/s in 6 switchable steps. The recorder weighs only 5.5kg and can be operated from the mains supply or from a 12V battery. Optional extras include a solenoid-operated event marker, a 1/10 speed gearbox, and a rechargeable battery pack. Environmental Equipments Ltd, Eastheath Avenue, Wokingham, Berkshire, RG11 2PP

WW 308 for further details

Data selecting system

Fenscan 3 is a versatile data scanning and logging system designed for demanding process system applications such as multipoint digital temperature indication, alarm scanning and logging, and intrinsically-safe multiplexing in computer systems. The system, which was launched at the "All Electronics Show" by Fenlow Electronics Ltd, features up to 200 low-level analogue inputs, two 16-segment linearization programmes, manual point selection by a calculator-style keyboard, and a high-accuracy dual-ramp digital voltmeter which uses a strobe-locking technique to reduce series mode mains interference by ensuring that integration is performed over one complete cycle. Optional extras include alarms to aid the automatic point scanning and a trend recording facility. The units are designed to give freedom of location for the scanner, keyboard and display. Fenlow Electronics Ltd, Whittots Eyot, Weybridge, Surrey.

WW 309 for further details

Coaxial attenuators

Fixed 50 Ω 'axial-attenuators, for use from d.c. to 4GHz, are available in six values between 3 and 40dB from Aspen Electronics Ltd. The LDV 5033 series offers an attenuator accuracy of between ± 0.5 dB and ± 1.0 dB, depending on the model, a maximum v.s.w.r. of 1.2, and has a power handling capability of 15W continuous and 13kW peak. Each attenuator unit consists of an internal resistor and black anodized-metal fins on a rugged substrate. The unit has a distributed structure designed for uniform power distribution and low skin temperature. Aspen Electronics Ltd, 18a High Street, Northwood, Middlesex HA6 1BN. WW 310 for further details

Instrumentation amplifier

A compact differential d.c. amplifier has been produced by Fylde Electronic Laboratories Ltd, for instrumentation applications in transducer and recording systems. This modular amplifier, designated as FE-351-UA, has a bandwidth greater than 50kHz and exhibits less than 8µV pk-pk noise. The gain is variable between 0.2 and 10000 from two outputs, one being matched for galvanometers up to 20mA, with less than 0.02% non-linearity and a typical stability of $1\mu V/^{\circ}C$. The amplifier, which can be powered by either an isolated d.c. supply or the integral mains circuit, has both input and output protection, and greater than 100dB common-mode rejection. A wide range of compatible analogue conditioning modules are available and fourteen of the amplifiers can be packed into a 19in two unit high crate. Fylde Electronic Laboratories Ltd, 49 Fylde Road, Preston PR1 2XQ.

WW 311 for further details

Solid State Devices

Names of suppliers of devices in this section are given in abbreviation after each entry and in full at the end of the section.

High frequency transistors

Motorola have added two more n.p.n' silicon transistors to their range of radio frequency products. The transistors, BFR90 and BFR91, are designed primarily for use in high gain, low noise, small signal amplifiers, but are also claimed to be suitable for applications requiring fast switching times. The devices are in Macro-T plastic packages and have radially arranged leads.

Motorola

Amplifier transistors

BCX38 is a family of 60V, 800mA 1W n.p.n Darlington amplifier transistors introduced by Ferranti's Electronic Components Division. The transistors, produced in E-line plastic encapsulations and available in gain bands, offer high gains and input impedances and are claimed to be suitable for use in driver and output stages of audio amplifiers and also for interfacing with integrated circuits. Ferranti

High current transistors

Two high current transistors, designated as 2N4276 and 2N4283, have been introduced by the Germanium Power Devices Corporation. The devices, available in copper TO-3 and TO-41 hermetically sealed packages, have high gain and low voltage saturation and are suitable for inverter and computer power supply applications. GPD

Transistor package

Thirty-four different transistors in the Durawatt 92-Plus package are offered by National Semiconductors. This is a modified TO-92 package containing a small heat sink. The 34 transistor types are n-p-n and p-n-p general purpose devices, n-p-n Darlington pairs and high-voltage transistors (300V V_{CEO}). A square inch of copper p.c. board is required to reach at least 1.2W power dissipation at an ambient temperature of 25°C.

National

Op-amps

The CA301AG, CA307G, and CA748G general-purpose operational amplifiers, CA1458G dual operational amplifiers, CA3401G quad operational amplifier and CA3119 voltage comparator are

additions to the Gold Chip linear i.c. ranges produced by RCA Solid State. All of the circuits are hermetically packaged and are available in industrial and military temperature range options.

RCA

81

High performance r.a.m.

The MK4027 is a 4kbit r.a.m. which has a claimed 200ns access time and a 10% tolerance on all supplies. The 16-pin d.i.p. memory system offers a performance matching the 160ns obtainable from a 22-pin 4-kbit r.a.m. by eliminating the 40ns delay of the 12V clock driver. Features include direct interfacing capability with Schottky-t.t.l., two methods of chip selection, and a cycling operation, called page-mode, which allows an increased access speed of 135ns at decreased power for successive memory operations within the same row address. Mostek

Multipurpose p.m.o.s. dividers

A range of G.I.M. frequency dividers can be driven by both square and sine wave inputs up to 1MHz, and require —13-volt and —27-volt supplies. All outputs are changed on the negativegoing clock edges. In particular, the AY-1-5050 divider, supplied in a 14-lead dual in-line plastic package, can divide by 1, 2, 3, 4, 5, 6 and 7 by appropriate selection of divider elements. **SCS**

Silicon power rectifiers

A series of high current silicon rectifiers, SCSFO5-SCSM6, has been introduced by Semtech specifically for high frequency, high power industrial, military and space applications. The rectifiers, known as "Cupac 150", have fast recovery characteristics and allow heat sinking from both the anode and the cathode. Peak inverse ratings extend from 50 to 600 volts. **Bourns**

Bourns (Trimpot) Ltd, Hodford House, 17/27 High Street, Hounslow, Middlesex TW3 1TE.

Ferranti Ltd, Electronic Components Division, Gem Mill, Chadderton, Oldham, Lancs.

Germanium Power Devices Corp, P.O. Box 65, Shawsheen Village Station, Andover, Ma₄01810, U.S.A.

Motorola Ltd, Semiconductor Products Division, York House, Empire Way, Wembley, Middlesex HA9 0PR.

Mostek UK Ltd, 240 Upper Street, London N.1.

National Semiconductor U.K. Ltd, 19 Goldington Road, Bedford MK40 3LF.

RCA Ltd, Solid State— Europe, Sunbury-on-Thames, Middlesex.

SCS Components, Northfield Industrial Estate, Beresford Avenue, Wembley, Middlesex HAO ISD.



82

"COME IN, REYNARD 51, YOUR TIME IS UP"

I see that the Min of Ag., Fish and Food has been advertising for an electronics engineer. Not any old run-of-the-mill¹ electronics engineer, you understand, but one (and I quote)

"To work in a biological laboratory concerned with control of vertebrate pests. Development of radio-telemetry systems for tracking movements of foxes, badgers, rats, coypu, polecats and other species in a variety of habitats. Considerable scope for research and development."

That first sentence - control of vertebrate pests - is perfectly straightforward and will, I'm sure, meet with the full approval of every thinking electronics engineer. I mean, we could all, at the drop of a microcircuit, provide a long list of vertebrate pests we would like to control; vacillating marketing managers; all group leaders; H.M. Collector of Taxes; that anonymous Scrooge in Accounts Dept who is constantly ringing to reduce our latest expense account presentation by an order of magnitude, et al. By the time this piece gets into print the onerous post at the Ministry will doubtless have been filled and I'm sure the best wishes of all go to the successful candidate. It's a comforting thought to know that one of our fraternity has infiltrated into a Government laboratory and (one earnestly hopes) is actively working on our behalf.

So far, so good, and if only the Ministry man who compiled the advertisement had downed his ball-point at this juncture and gone home to his fish and chips, he would have left me a happy man. But no. I can only suppose that he felt that his story so far didn't constitute a fair week's work and so, after a painful gestation period and a w.p.b. full of rejected copy, he at length gave birth to the foxes, badgers and rats bit and caught the 4.15 back to Pinner, thoroughly exhausted.

I think it's a tribute to the restraint with which affairs in the animal kingdom are conducted that the author of that piece of copy hasn't been torn to pieces by the savage carnivores with which our country is infested. Foxes, in particular, must be feeling grossly ill-used. As is well-known, foxes relish being chased over the terrain by well-bred huntspersons and aristocratic hounds. It is their express reason for being, and, no doubt, as they are being torn to pieces, their last thoughts are of intense satisfaction at having fulfilled their destiny, particularly if the MFH is an Old Etonian. But to be tracked across country by a miscellany of microcircuits is quite another matter. It is devoid of dignity; the babel of binary code will never be an adequate substitute for the resounding "Tally-Ho!" from the throats of the elite and the impetuous "There goes the little brown **!*?!!" from the less erudite followers.

In a Gallup poll taken on the 8.27 a.m. from Woking, commuters were asked whether they considered polecats to be a pest. Of those questioned, 247 thought they were extinct, 123 said "don't know" and one said he preferred the Military Two-Step. It subsequently transpired that his hearing-aid was defective.

But what particularly intrigues me is this; exactly how does one go about selecting a radio-telemetry coypu-tracker? It's worried me to the point where I have a recurring nightmare about it . . The scene is the Ministry office where the Comptroller of Pest Infestation is interviewing a candidate, a gangling six-footer with red hair and a wild look in his eyes. The Comptroller glances down at the application form

"Good morning, Mr Shakespeare –"

"Not Shakespeare, sir – Napoleon." "But it says Shakespeare on your application," says the Comptroller, peering through his gold-rimmed spectacles.

"Ah, yes, sir. That was last week when I sent it in. This week it's Napoleon."

"Good gracious me! Do you change your name every week?"

"No sir, of course not. That would be silly, wouldn't it? No - just every other week."

"H'm. Now, Mr - er - Napoleon; I presume you have had previous experience in a biological laboratory. Which one?

"Broadmoor, sir. It's the invisible ink."

"The what?"

"The invisible ink, sir, why the form is apparently incomplete. I had to do it that way. You see, THEY are after me." "They?"

"No sir. – THEY, in capitals; or, to put it another way, in upper case. THEY. The ones with snow on their boots. They want to know how I do it." "Do what?"

"Why, how I track the movements of foxes, badgers, rats, coypu, polecats and other species in a variety of habitats of course. What else?"

At this the Comptroller leans forward excitedly.

"You mean that you're already doing this? By radio-telemetry?"

"Well, not exactly, sir. It's more what you might call audio than radio."

"Audio? I don't follow."

"Well, sir, I'm not supposed to tell you this – Official Secrets Act, and all that rubbish. But this is how I do it. First, I concrete over their variety of habitats, and then I fit the animal pests with littble hobnailed boots. They make such a noise coming and going that I can keep track of them over quite long distances. Bang, bang, bang they go, all night long; sometimes it makes me go quite funny in the head. But that's the price of science, I always say. What do you always say, sir?"

"But –"

"Funny you should say that sir, because it reminds me of my latest development. I don't need concrete or hobnails any more. It works a treat with my experimental goat. I call him 'Nearly'."

" 'Nearly'? That's an odd name for a goat. Why do you call him 'Nearly?"

"I was hoping you'd ask that, sir. I call him 'Nearly' because he's all but. D'you get it, sir? All butt - see? Why aren't you laughing, sir? I wish you would. I get funny pains in the head and things swim around in a red mist when people don't laugh at my little jokes."

"I do not wish to know that! Now, Mr Napoleon – let us stick to the matter in hand. You say you have dispensed with your earlier – er – apparatus and you can still track this goat of yours?"

"Yes, sir, and foxes, and polecats in a variety of habitats."

"Ah. Now we are getting somewhere. Radio-telemetry this time, I presume?"

"No sir. I sniff them out. Did you ever smell a polecat, sir?"

"Most certainly not. Now, Mr - er - Napoleon; you seem to be under a certain misapprehension as to our modus operandi. Our approach is to catch the pests, implant a miniscule telemetry transmitter in each and then turn the animals loose again."

"Why, sir?"

"Perfectly odvious, I would have thought. By applying modified minedetector techniques we can then track down these pests and destroy them. Ingenious – what?"

"But – sir! If that's what you wanted, why didn't you kill them in the first place? Why bother with implants?"

At this the Comptroller sits bolt upright, his face a mixture of incredulity and joy.

"By jove! A lateral thinker at last! Mr Napoleon — my congratulations, my boy. You've provided us with the breakthrough we've been looking for! When can you start?"

Soundcraft-Series II

revised specification.

Illustrated: Series II original format

The Series II range of recording consoles are now available with many more facilities as standard, enabling the engineer to record four and eight-track with the four-group output mixers, eight & sixteen-track with the eight group mixers. Input modules are available in groups of four channels. All connections between the channels are by multipin connectors and a mother board system. Two types of equalisation:- the standard module features the Soundcraft four-band E/Q with the addition of a high pass filter (bass cut), 12dB/octave below cut-off frequency, continuously

variable between 20Hz and 350Hz. The special module features sweepable frequency of the two mid-frequency peaking and dipping equalisers, addition of a low pass filter to the HF shelving equaliser, and the same 50Hz shelving equaliser and high pass filter as supplied on the standard module. There are four cue sends from each input and monitor channel.

Write for complete details direct to Soundcraft Electronics Ltd., or to the local agent or distributor if listed below.

SOUNDCRAFT - Mixing Consoles to the World of Music

| U.S.A. | Systems & Technology in Music, Inc., 2025 Factory Street, Kalamazoo, Michigan 49001. Tel: (616) 382 6300. (Mr. Verne Wandell) | | | | | | |
|---------------|--|--|--|--|--|--|--|
| CANADA. | Franchised dealer network – write for your local dealer. | | | | | | |
| NETHERLANDS. | selectronic B.V., Sluisplein 3-4, Ouderkerk aan de Amstel. Tel: (02963) 3838/3966. | | | | | | |
| SWEDEN. | Ing. Jan Setterberg, Forstavsgatari 1, S-431 36 Molndal. Tel: (031) 13 02 16 87 58 93. | | | | | | |
| GERMANY. | Franchised dealer network – write for your local dealer. | | | | | | |
| BELGIUM. | Delta Equipment, Rue de Calevoet 112, 1180 Bruxelles. (02) 376 60 34. Calevoet Straat 112, 1180 Brussel. (02) 376 60 34. | | | | | | |
| SWITZERLAND. | Professional Audio Systems, 4132 Muttenz, Kappeliweg 41. Tel: 061/41 51 56. | | | | | | |
| AUSTRALIA. | Klarion Enterprises (Pty) Ltd., P.O. Box 379, South Melbourne, Victoria 3205. Tel: 61 3801. Cables: Klarionmelb. | | | | | | |
| SOUTH AFRICA. | Tru-Fi Electronics S.A. (Pty) Ltd.; P.O. Box 31801, Braamfontein, TVL 2017. Tel: Johannesburg 838 4930. | | | | | | |
| JAPAN. | C.M.C. Inc., Kasumi Building No. 503, 21-20 Nishi-Azabu, 3-Chome, Minato-ku, Tokyo 104. | | | | | | |



5-8 Gt Sutton Street London EC1V 0BX Tel: 01-251 3631/2/3 Telegrams: Soundcraft LDN EC1

For all who want to know about electronic circuits

Here's a book of very special appeal to all concerned with designing, using or understanding electronic circuits. It comprises information previously included in the first ten sets of Wireless World's highly successful Circards – regularly published cards giving *selected* and *tested* circuits, descriptions of circuit operation, component values and ranges, circuit limitations, modifications, performance data and graphs. Each of the ten sets – including additional circuits – in this magazine size hard cover book has been updated where necessary, and is preceded by an explanatory introduction. Circuit designs (1) is the first collection of its kind.

Circuits covered are: Basic active filters Switching circuits Waveform generators AC measurements Audio circuits Constant-current circuits Power amplifiers Astable circuits Optoelectronics Micropower circuits



A new book from Wireless World

ORDER FORM

To: General Sales Department, IPC Business Press Limited, Room II, Dorset House, Stamford Street, London SEI 9LU.

Please send me copy/copies of Circuit Designs – Number I at £10.40 each inclusive. I enclose remittance . value £: (cheques payable to IPC Business Press Ltd.)

| NAME (please print) | | | | | • | | | | | | | | ÷ | |
|---------------------|--|--|---|--|---|--|---|---|--|--|---|--|---|--|
| ADDRESS | | | • | | | | | | | | • | | | |
| | | | | | • | | • | • | | | • | | | |

Company registered in England and a subsidiary of Reed International Limited Registered No 677128 Regd. office Dorset House, Stamford Street, London SET9LU.





ELECTRONIC - SCIENTIFIC - / INSTRUMENTS

Sales Office: 57 High Street, Saffron Walden, Essex. Tel: Saffron Walden (0799) 22876 Factory: 62 Largo Road, St. Andrews, Fife, Scotland. Tel: St. Andrews 2641.

S—DEC Solderless Breadboard for only £1.00



The world proved S-DEC can now be yours at half price.

- S-DEC just plug components directly in, no soldering, use components over and over again
- With your S-DEC you receive FREE a booklet which gives a range of circuits which can be quickly assembled on the S-DEC including Radio-Receiver, VHF Radio-Microphone, 3 Stage Amplifier and many others, also FREE control panel for mounting switches, lamps, etc.

S-DEC normally £1.98 with this advertisement only £1.00

(When ordering direct send £1.20 to cover Post & VAT) T-DEC normally £3.63, with this advertisement £3.38

(When ordering direct send £3.87 to cover Post & VAT) U-DEC-A for discrete and use with I.C. send £4.31.

ALL FULLY **GUARANTEED**

N.B. These half-price S-DECS are seconds and may be chipped or wrong colour

Expo Reliant Drills and Kits



Powerful, miniature, low-voltage drills capable of sawing, grinding, burring, brushing and polishing - as well as drilling holes up to 3mm diameter through virtually any material.

The Expo drill operates from a power supply of 12V d.c. or, using the Titan transformer / rectifier unit (0220), from a.c. mains supplies at 200-250V a.c., 50Hz.

The Expo Reliant Mini Kit, consists of the Reliant Standard Drill (0510) and a set of 20 assorted tools (0305), providing a powerful, versatile kit for use both by the professional and the hobbyist. Prices: **£9.40** including postage and packing, and VAT.

Special offer Fibre Glass Circuit Board

| Offcuts of perfect Fibre Glass material (includes 3 pieces 1.2 x 1.2) | 10 sq. ft. | ONLY £3.00 |
|---|---------------|-------------------|
| 1/32in, thick Fibre Glass Circuit Board, size 12 x 12 | 10 sq. ft. | ONLY £4.00 |
| Resist coated Circuit Board, size 12 x 12 | . 5 sq. ft. ' | ONLY £5.00 |
| All Double sided Circuit Board | 10 sq. ft. | ONLY £4.00 |
| DI LLCO CO L Allaha a Cal Davi R MAT N. D. Na amallas amayota ayan bird | | |

Please add £0.60 to all above for Post & VAT. N.B. No smaller amounts supplied

Make Your Own Circuit Boards

Teach Yourself Electronics Book with Free S—DEC

Zippy Cabinets. Ideal for All Assembly Cabinets



Robust ABS plastic assembly boxes, front panel designed to be cut and drilled, slots inside for mounting circuit boards, attractive colouring and styling. £0.72 1 OFF TP1

80 x 50 x 30mm TP2 115 x 65 x 40mm TP3 155 x 90 x 50mm TP4 210 x 125 x 70mm

£1.27 1 OFF £1.62 1 OFF £2.27 1 OFF

Special low price offer TP4 only £1.75 inc. Post & VAT

Discount for quantity prices include Post & VAT.

PB Electronics (Scotland) Ltd. 57 High Street, Saffron Walden, Essex CB10 1AA Tel: 0799 22876

All stockists of DEC Breadboards Please note PB are the manufacturers and suppliers, please send all orders, communications direct,

WW - 079 FOR FURTHER DETAILS

ELECTRONIC DIGITAL CLOCK with alarm and mooze features



FEATURES: © 0.7-inch high digits © Variable intensity © 24-hour alarm © 5-minute repeating, snooze alarm ● Alarm set indicator ● Snoozeindicator ● Pulsing second indicator ● Power interrupt indicator ● Alarm cancel features -- tilt operation ● Alarm tone output ● AM. PM.Indicator.Size130mm x 90mm xManufactured to high standards by a major American electronics corporation this superbly styled

Size Weight

95mm 10oz

solid-state timepiece is made available to all readers fully guaranteed.



FREE TRIAL IN YOUR HOME. Try out the clock in your home. If digital time is not for you return it in original condition within ten days and we'll refund your money without question. Allow 21 days for delivery.

Mail Order only. Please enclose 55 pence for postage and packing

TIME MICROELECTRONICS BRIGHTON HILL PARADE, BASINGSTOKE HANTS RG22 4EH

Please send _ electronic clocks as illustrated. I enclose cheque _ postal order _ money order _

Name

Address

.

Signature

NEW FROM COMPUTER APPRECIATION!

- ★ VDU KIT. The CT 1024 is the first TV compatible terminal everyone can afford. Featuring: 1024 character memory (2 pages of 16 x 32), serial interface 110 to 1200 baud, video output (RF modulator available). Kit includes all components and fibreglass plated-through cards, TTY compatible ASCII keyboard, and PSU. Price £215 (excl. VAT).
- ★ MOTOROLA M6800 4K MICROPROCESSOR KIT. Includes 4K static RAM, serial interface, PSU, cabinet, and manuals. Manufactured to the same high standards as the CT 1024. Price £375 (excl. VAT).
- ★ Available very soon! A range of interfaces for the M60800, including a cassette recorder interface. We shall also be offering both kits assembled and tested at around £100 extra per kit.

Trade enquiries welcomed

Computer Appreciation, Castle St., Bletchingley, Surrey RH1 4NX, Godstone (088 384) 3106.

WW-076 FOR FURTHER DETAILS



rofessional Tape Recorders ni-Studio Use



REVOX 2-TRACK

REW carry the largest stocks of Revox in the country. All models available for immediate delivery at very low prices to professional and educational users. High speed models of the A77 and A700 ranges off the shelf.





DOKORDER 1140 4-TRACK

Now available for immediate delivery. The 1140 offers the ultimate quality and facilities for a 1/4" 4-channel recorder. Motion sensing logic transport, automatic sync switching, front panel bias adjustment, auto. rewind-replay facility, console format, built-in pink noise generator

For details of our complete range of Professional Audio and Studio Sound Equipment please send for our new catalogue and price list.

REW Professional Audio, 146 Charing Cross Rd. London, WC2. Tel. 01-240 3064/5

WW-078 FOR FURTHER DETAILS



V offer the

TEAC TASCAM 8-TRACK

New Teac Tascam 80-8 8-track 1/2" recorder available in May- 15 ips, modular electronics, perfect sync response. Studio quality, under £2,000 + VAT.

Also in stock the Teac A3340S 4-track 1/411 recorder, 15 jps, 101/211 reels, and also A2340 4-track recorder, 71/2 ips, 7" reels

Winn





Each Price (p)

BF185

BE194

BF195

BF196

BF197

BF198

BF200 BF218

BF224

BF258

BF336

BF337

BF355

BFX86

BFY50

BFY52

BSY52

Qty Type BA115

BA145

BA148

BY126

BY127

BY199

Qty Type

BA154/201

INTEGRATED

Each Type Price (p) ETTR6016 <u>£2.00</u> <u>MC1351P 70</u> SN76003N <u>52.25</u>

SN76013N £1.43

SN76023N £1.43

SN76227N £1.45

SN76532N £1.45

SN76660N 60

SN76666N 90 TAA550 32

TAA700 £3.80

£2.15

SN76013ND £1.25

SN76023ND £1:20

SN76033N

Each

| L | | 20 | | | 1 mar 1 |
|------|-----------|------------|-----------|----------|---------|
| 1 - | Price (p) | Qty Type F | Price (p) | Qty Type | |
| - | 48.0 | PCF802 | 37.0 | DY87 | |
| l: - | 54.0 | PCL82 | 37.0 | DY802 | 1 |
| ° - | 46.0 | PCL84 | 37.0 | ECC82 | |
| - I | 52.0 | PCL85 | 34.0 | EF80 | |
| h - | 50.0 | , PCL86 | 39.0 | EF183 | |
| - | 65.0 | PFL200 | 39.0 | EF184 | |
| - | 63.0 | PL36 | 40.0 | EH90 | |
| 1 - | 30.0 | PL84 | 58.0 | PC 86 | |
| - | 75.0 | PL504 | 58.0 | PC 88 | |
| - | 78.0 | PL508 | 46.0 | PCC89 | |
| - | £1.35 | PL509 | 47.0 | PCC189 | |
| - | 43.0 | PY88 | 38.0 | PCF80 | |
| 1.44 | £1.00 | PY500A | 44.0 | PCF86 | |
| - | 42.0 | PY800 | 46.0 | PCF801 | |
| - | | | | | |

SENI CONDUCTO

| SEI | | NDUCTURS | |
|----------|-----------|----------|-----------|
| Qty Type | Price (p) | Qty Type | Price (p) |
| AC127 | 20 | BC135 | 15 |
| AC128 | 15 | BC137 | 20 |
| AC141 | K 25 | BC138 | 30 |
| AC142 | K 25 | BC142 | 20 |
| AC151 | 20 | BC143 | 25 |
| AC154 | 18 | BC147 | 8 |
| AC155 | 18 | BC147A | 11 |
| AC156 | 20 | BC148 | 9 |
| AC176 | 22 | BC149 | 10 |
| AC187 | 20 | BC153 | 20 |
| AC187 | K 30 | BC154 | 20 |
| AC188 | 18 | BC157 | 11 |
| AC188 | K 30 | BC158 | 10 |
| AD142 | 62 | BC159 | 11 |
| AD149 | 45 | BC173 | 15 |
| AD161 | 38 | BC178B | 20 |
| AD162 | 38 | BC182L | 12 |
| AF114 | 25 | BC183L | 12 |
| AF115 | 22 | BC187 | 25 |
| AF116 | 22 | BC214L | 15 |
| AF117 | 20 | BC328 | 28 |
| . AF118 | 45 | BC337 | 19 |
| AF139 | 35 | BD124 | 75 |
| AF178 | 45 | BD131 | 35 |
| AF180 | 40 | BD132 | 39 |
| AF181 | 40 | BD160 | £1.65 |
| AF239 | 45 | BD235 | 50 |
| AF240 | 20 | BD237 | 60 |
| BC107 | 10 | BDX32 | £2.40 |
| BC108 | 10 | BF115 | 24 |
| BC109 | 12 | BF160 | 35 |
| BC1090 | <u>14</u> | BF167 | 24 |
| BC113 | 15 | BF173 | 25 |
| BC1164 | A 25 | BF178 | 33 |
| BC117 | 14 | BF179 | 38 |
| DC1255 | 10 | DE400 | 24 |



| 29 | BT106 £1.20 | EHT MULTIPLIERS MONOCHRO | ME B.R.C |
|-----------------|--------------------|---------------------------|------------------------------|
| 30 | BU105/02 | | |
| 8 | £1.60 | | 2 |
| 8 | BU108 £1.80 | Qty Type | Price (p) |
| 10 | BU208 £2.20 | 2TQ 950MK2 1400 | £2.05 |
| 11 | E1222 38 | 2DAK 1500 (17" x 19") | £1.85 |
| 23 | MJE340 45 | 2TAK 1500 (23" x 24") | £2.05 |
| 25 | 0C71 18 | | 22.00 |
| 40 | OC72 18 | ENT MULTIOUEDO OO | |
| 20 | R2008B £1.90 | EHI MULTIPLIERS CO | LOUK |
| 26 | R2010B £1.90 | Qty Type | Price each |
| 27 | RCA16334 80 | 11 TAQ ITT CVC 1, 2 & 3 | £5.10 |
| 35 | RCA16335 80 | ITN GEC Sobell | £4.50 |
| 50 | | IITAZ GEC 2110 | £4.50 |
| 28 | TIP32A 62 | IITAM Philips G8 | £4.50 |
| 19 | TIP41A 60 | IITBD Philips 550 | £4.65 |
| 20 | TIP42A 75 | 2TC\M/ Pug 691/693 | 67.49 |
| 30 | 2N3055 55 | 1TH Deese 20 Series | £4.60 |
| - | | TH Decca 30 Series | £4.00 |
| DIOI | DES | 3100 Thorn 3000/3500 | 15.00 |
| I | E.u.b. | 11HAA Thorn 8000 | £1.99 |
| Each ica (n) | Oty Type Price (p) | 11HAB Thorn 8500 | £4.31 |
| 7 | BY206 17 | IITCP Bush 823 | £5.50 |
| 16 | BY238 25 | | - |
| 16 | 0,490 6 | BLACK & WHITE | TUBES |
| 1 12 | 0A202 8 | with Full Vear's Gu | arantee |
| 11 | IN60/0A91 7 | With Full Fours Gut | andriteee |
| 10 | IN914 6 | Qty Type | Price each |
| 25 | IN4002 5 | 20" CME 2013 | £13.90 |
| | | 24" CME 2413 | £15.95 |
| ATE | D CIRCUITS | | |
| | | TOSHIBA TU | REC |
| | | TOSHIDA TO | DES |
| ach | Each Each | with 12 months in service | guarantee |
| ce (p) | TBA120AS 60 | | |
| 2.00 | TBA12050 | Qty Type | Price each |
| 70 | £1.00 | 19" A49-191X equivalents | |
| | TBA4800 | A49-192 and A49-120X | £52.00 |
| 2.35 | £1.40 | 20" 510DJB22 equivalent | |
| | TBA520Q | A51-110X | £54.30 |
| 1.43 | £2.40 | 22" A56/120X | £55.40 |
| D | TBA530Q | | and the second second second |
| 1.25 | <u>t1./5</u> | * All goods subject to | |
| 1 43 | 18A5400 £1.25 | He migoods subject to | |
| 1,43 | | settlement discount of | 5% |

* All goods subject to settlement discount of 5% 7 days and 2% monthly. * Prices subject to 12½% VAT wef. April 12 th '76

* No Postal Charges

* C.P.C. - Price · Quality · Service

* No Minimum Orders

C.P.C. supply many large Multiple Organisations in the U.K. Contact our Export Division for special prices NOW. Or send your order with this page. I enclose cheque/PO to the value \poundsp for the goods as specified above. Name_ Position. Company Address_ Tel. No.

Send this coupon NOW to: C.P.C., Dept.w, 194-200 NORTH ROAD, PRESTON, LANCASHIRE, ENGLAND. Phone: Preston (STD 0772) 55034. Telex 677122 New price list 1.4.76

TBA550Q £2.30

TBA560CQ <u>£2.40</u> TBA800 £1.10

TCA270Q £2.90

TBA920Q TBA990Q £2.50 £2.90



www.americanradiohistory.com

89



Wireless World Dolby®noise reducer

Trademark of Dolby Laboratories Inc

We are proud to announce the latest addition to our range of matching high fidelity units.

Featuring:

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

The kit includes:

- --complete set of components for stereo processor
- --regulated power supply components
- ----board-mounted DIN sockets and push-button switches
- ---fibreglass board designed for minimum wiring
- --solid mahogany cabinet, chassis, twin meters, front panel, knobs, mounting screws and nuts

Typical performance

Noise reduction: better than 9dB weighted

- Clipping level: 16.5dB above Dolby level (measured at 1% third harmonic content)
- Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%.
- Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output.
- Dynamic Range > 90dB
- 30mV sensitivity

PRICE: £34.40+VAT

| Calibration tapes are available for open-reel use and for cassette (specify which) | Price £1.80+VAT* |
|--|--|
| Single channel plug-in Dolby PROCESSOR BOARDS (92 x 87mm) with gold plated contacts components | are available with all Price £6.50 +VAT |
| Single channel board with selected fet | Price £2.00+VAT |
| Gold plated edge connector | Price £1.27 +VAT* |
| | |

Selected FET's 54p each + VAT, 96p + VAT for two, £1.76 + VAT for four

Please add VAT at $12\frac{1}{2}\%$ unless marked thus^{*}, when 8% applies We guarantee full after-sales technical and servicing facilities on all our kits



INTEGREX LTD.

Please send SAE for complete lists and specifications Portwood Industrial Estate, Church Gresley, Burton-on-Trent, Staffs DE11 9PT Burton-on-Trent (0283) 215432 Telex 377106

S-2020TA STEREO TUNER/AMPLIFIER KIT

SOLID MAHOGANY CABINET

A high-quality push-button FM Varicap Stereo Tuner combined with a 20W r.m.s. per channel Stereo Amplifier.



Brief Spec. Amplifier: Low field Toroidal transformer, Mag. input, Tape In/Out facility (for noise reduction unit, etc), THD less than 0.1% at 20W into 8 ohms. All sockets, fuses, etc., are PC mounted for ease of assembly. Tuner section: uses Mullard LP1.186 module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88–104MHz. 30dB mono S/N @ 1.8µV.THD typ. 0.4%

PRICE: £48.95+VAT

Mono £26.31 + VAT

INTEGREX

NELSON-JONES STEREO FM TUNER KIT

A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter / dual IC IF amp.

Sens. 30dB S/N mono @ 1.8µV

LED sig. strength and stereo indicator

Tuning range 88-104MHz

THD typically 0.4%



Brief Spec. Tuning range 88–104MHz. 20dB mono quieting @ 0.75 μ V. Image rejection – 70dB. IF rejection–85dB. THD typically 0.4%

IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

Compare this spec. with tuners costing twice the price

| vith | With | Portus-Haywood | Decoder |
|----------|------|----------------|---------|
| 9 | | £32 | .81+VAT |
| | | 9 | |

STEREO MODULE TUNER KIT

A low-cost Stereo Tuner based on the Mullard LP1186 RF module requiring no alignment. The IF comprises a ceramic filter and high-performance IC Variable INTERSTATION MUTE. PLL stereo decoder IC

> PRICE: Mono £25.55+VAT Stereo £28.65+VAT

With ICPL Decoder £30.58+VAT

S-2020A AMPLIFIER KIT

Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring

Typ. Spec. 20+20W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Headphone output. Tape In/Out facility (for noise reduction unit, etc.). Toroidal mains transformer.

PRICE: £30.94+VAT

ALL THE ABOVE KITS ARE SUPPLIED COMPLETE WITH ALL METALWORK, SOCKETS, FUSES, NUTS AND BOLTS, KNOBS, FRONT PANELS, SOLID MAHOGANY CABINETS AND COMPREHENSIVE INSTRUCTIONS

BASIC NELSON-JONES TUNER KIT £13.13+VAT BASIC MODULE TUNER KIT (Mono) £13.25+VAT BASIC MODULE TUNER KIT (stereo) £15.25+VAT PHASE-LOCKED IC DECODER KIT£4.47 + VATPUSH-BUTTON UNIT£3.50 + VAT

PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER KIT

£7.93+VAT

WW - 029 FOR FURTHER LET.MLS







Acid resistant transfers for direct application to P.C. Board. This is a new approach to printed circuit board manufacture, giving a professional finish with all details that an electronics engineer would require, including all drilling positions automatically marked.

Ideal for single unit boards or small quantities. All at a very low cost—for example an average 6" x 4" layout would cost less than 30p, and the time taken under one hour, including etching to complete.

The system is simple, briefly it consists of 10 sheets of self adhesive acid resistant transfers made in required shapes — i.e. edge connectors, lines, pads, dual in line I.C.s, 8-10-12. T.O.5 Cans, 3-4 lead transistors, etc., etc., which only require pressing into the required positions on the printed circuit board before etching.

The printed circuit transfer system is a genuine offer to the public and industry, A full money back guarantee is sent with each order, trade prices on application.

List of Prices

| Complete system including post and VAT | £2.95 |
|--|-------------|
| Individual sheets | 30 p |
| Sample sheet | ЗОр |
| Ex. U.K. Post Extra | £1.00 |

Printed circuit board PCB transfer systems patent applied for

E. R. NICHOLLS, 46 LOWFIELD ROAD, STOCKPORT, CHESHIRE TELEPHONE NUMBER 061-480 2179





We have made it just about as comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I C s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 40p for spending on orders list value £5 or more SEND NOW FOR YOUR COPY OF CATALOGUE 8, ISSUE No. 2 BY RETURN. It's an investment in practical money-saving and reliability!

+E.V. PRICE STABILIZATION POLICY This is one of reviewing prices every 3 months rather than trying to keep up with day by day changes as they occur. We have on the whole held prices better than anticipated in following this plan. Next review period starts July 1st

+ E.V. DISCOUNT PLAN

Applies to all items except the few where prices are shown NETT $5\,\%$ on orders from £5 to £14.99 10% on orders value £15 or more.

+FREE POST & PACKING The pre-paid mail orders over $\pounds 2$. If under there is an additional handling charge of the pre-paid mail orders over $\pounds 2$. 15p

+ QUALITY GUARANTEE

All goods are sold on the understanding that they conform to makers' specifications. No rejects, seconds or sub-standard merchandise.



All communications to Dept. 4 / 6 28 ST, JUDES RDAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB Zo SJ, SUDEO HOLL, ENGLETIKO UNICAN, DANIE JO ALAN, SO MARINE, SUDEO HOLL, SUDEO HOLL,

| | • | | | | | | | | | | | | | | | | | | |
|---|--|---|---|---|---|--|---|--|--|--|---|---|---|--|--|--|--|--|--|
| P P AC125 20 AC126 20 AC127 20 AC128 20 AC124 21 AC142 17 AC153 27 AC162 27 AC164 20 AD161 42 AP116 42 AF115 24 AF116 24 AF116 24 AF117 24 AF118 20 AF125 30 AF126 33 AF139 34 AF139 34 AF126 50 | ASY26 ASY27 ASY29 ASY29 ASY67 BA145 BA154 BA154 BA154 BA154 BA154 BA154 BA154 BA154 BA16 BC107A BC108 BC109 BC109 BC109C BC116 BC117 BC118 BC119 BC119 | p 30 34 70 15 10 12 10 4 6 11 12 10 11 12 10 11 12 13 15 18 10 28 14 | $\begin{array}{c} \text{BC132'} \\ \text{BC135'} \\ \text{BC136'} \\ \text{BC137} \\ \text{BC137} \\ \text{BC138} \\ \text{BC138} \\ \text{BC143} \\ \text{BC1473} \\ \text{BC14478} \\ \text{BC14478} \\ \text{BC14478} \\ \text{BC149C} \\ \text{BC1578} \\ \text{BC1578} \\ \text{BC1578} \\ \text{BC1559A} \\ \text{BC159A} \\ \text{BC159A} \\ \text{BC1678} \\ \text{BC1678} \\ \text{BC171A} \\ \text{BC171A} \\ \text{BC1774} \\ \text{BC17738} \\ \text{BC17738} \\ \text{BC1778} $ | p 11 16 16 15 32 24 9 10 9 10 11 11 18 18 12 12 12 11 14 14 15 16 17 | BC178B BC178B BC182B BC182B BC182L BC183L BC184L BC184L BC205A BC206A BC205A BC205A BC205A BC204A BC205B BC212A BC205B BC212A BC205C BC212A BC212A BC214 BC215 BC2 | P 18 19 10 11 10 12 11 256 16 15 15 15 11 13 13 15 17 16 15 15 | BC BC BC BC BC BC BC BC BC BC BC BC BC B | 261 A 262 A 266 A 268 B 269 287 300 300 1 300 2 303 300 4 307 A 309 B 307 A 309 B 307 A 319 B 327 328 337 328 337 338 337 328 337 328 337 328 337 328 337 328 337 328 337 328 337 328 337 328 337 328 337 338 337 338 337 338 337 338 337 338 337 338 337 338 337 338 337 338 337 338 337 338 337 338 337 337 | p 16 15 18 13 20 27 26 24 30 27 16 12 12 12 12 20 18 18 18 18 18 5 9 9 | BC559' BCY70 BCY72 BD115 BO123 BD124 BD131 BD132 BD135 BD136 BD135 BD136 BD135 BD136 BD135 BD135 BD135 BD135 BD135 BD135 BD145 BD155 BD220 BF115 BF158 BF158 BF158 | p 9 15 18 60 90 90 8 8 65 37 90 8 6 8 65 37 39 44 47 54 47 54 47 54 34 47 54 20 26 20 | BF166 BF167 BF173 BF173 BF178 BF180 BF181 BF183 BF184 BF194 BF195 BF197 BF200 BF257 BF197 BF258 BF271 BF336 BF337 BF338 BFW10 BFW11 BFW12 BFW11 BFW12 | P 38 21 20 24 25 30 30 30 28 10 10 10 12 12 38 50 50 50 28 30 34 68 55 | | | | | | |
| AP 239 3/2 (a) 25 (4) BE177 (7) BE370 BE3 (7) TL D01 SRIDGE REC D1 SGOS D1 D100 D2 D113 33 SILICON RESISTORS (5) TL D01 SRIDGE REC D1 SOCKETS SOCKETS | | | | | | | | | | | | | | | | | | | |
|) C s LINEAR 709 (8 PIN D) 741 (8 PIN D) LM 380 NE 555 SN76013N SN76023N TBA 800 ZN 414 | L).40p* L).33p* 1.29* .60p* 1.57p* 1.57p* 1.35p* 1.35p* | Z B 3 4 5 7 1 1 1 | ENERS (4) 2X83 BZ93 V3 3V6 3 V3 4V7 5 V6 6V2 6 V5 8V2 9 OV 12V 1 5V 18V 3 All at 12 p | 00nm 88 V9 V1 V5 V1 3V 0v i ead | wi h | VC RE (IC 5V 12 15 5V 12 15 5V 12 | UTA GUI 93) 92 A V 92 14 V 92 14 V 17 | GE AIOF A A | 1. 1. 1. 17 17 17 | LE 12 35 12 35 12 35 20 55p 20 55p 20 55p 20 | D (like Sma 5 Re 5 Gri 5 Ye Lar 0 Re 0 An 0 Gil | e TIL 209 II O 125' d een Ilow ge O 2'' d nber een | 20p 27p 27p 27p 20p 27p 29p | | | | | | |
| | SAE for Flint F Tet. Wal | VAT Tull tis N Touse lingf | Reins r of compo Ain Orden e, High \$ ord (049 | inent inent 1 F Stre 1) 3 | ked add s Same da &P 25p C et, Walli I5529, T | ingf elex | ord. | Rus in to f in -Sa Oxc SPW | it at Viail (t inc on, (ALF | 8 %. Drder Cust DX10 00 RD 849 | International International International International International VAT International International <td< th=""></td<> | | | | | | | | |

| ALL EX-STOCK - SAME DAY DESPATCH | | | | | | | |
|---|-------------------------|--------------------------------------|--|---|----------------------------|--|--|
| MAINS ISOLATI PRI 120/240V sec 120/2 | NG VA | т 8% 12 | Primary 2 | 24-VOL | г | | |
| VA | ned P& P | Ref. No. | AMP 12v | 24v £ | P& P p | | |
| 07 20 £3.10 | P 58 70 | 111 213 | 0.5 0.25 | 1.54 | 28 58 | | |
| 149 60 4.69 150 100 5.33 151 200 8.54 | 72 85 1 12 | 71 13 | 2 1 | 2.41 2.97 | 58 72 72 | | |
| 152 250 10.32 153 350 12.47 | 1.41 | 70 103 | 8 4 10 5 | 5.09 5.50 | 85 85 | | |
| 154 500 14.33 155 750 21.94 | 1.61 BRS | 116 | 12 6 16 8 | 5.80 7.48 | 97 97 | | |
| 156 1000 30.51 157 1500 34.89 158 2000 38.03 | BRS | 115 187 | 20 10 30 15 | 10.91 | 1.61 | | |
| 159 <u>3000</u> 61.48 *115 or 240 sec only | BRS | 226 | | PANGE | BNS | | |
| 50 VOLT RANG | E -50V | SEC. Ret. | TAPS 0-1 | 2-15-20-25-3 | 0V | | |
| Ref. Amps. £ No. | Р& Р р | No. 112 | Amps 0.5 | £ 1.90 | p 58 | | |
| 102 0.5 2.71 103 1.0 3.55 | 58 72 | 79 | 1.0 | 2.52 | 72 | | |
| 104 2.0 4.95 105 3.0 6.10 | 85 97 | 20 | 3 U 4.0 5 0 | 4.70 5.56 6.73 | 85 85 97 | | |
| 107 6.0 12.71 118 8.0 13.63 | 1.25 | 117 88 | 6.0 8.0 | 7.52 1. 10.20 1. | 12 25 | | |
| 119 10.0 .17.75 | BRS | 85 | 10.0 | 10.36 1.4 | 41 DC | | |
| SEC. TAPS 0-24-30-40-48-60V | Ref. | | UTO TAPS | SCONNE | P&P | | |
| нет. Amps £ Р&Р No. P 124 0.5 э.49 72 | 113 64 | 20 0-11 75 0-11 | 5-210-240 5-210-240 | √ 1.75 √ 3.05 | 51 72 | | |
| 126 1.0 3.68 72 127 2.0 5.33 85 | 66 3 | 50 (+11 00 | 5-210-220 | 240V 4.33 6.11 | 72 85 | | |
| 125 3.0 7.90 97 123 4.0 9.19 1.41 | 67 50 84 10 | 00 000 500 | | 9.36 14.36 | 1.25 | | |
| 40 5.0 10.24 1.25 120 6.0 12.07 1.41 | 95 19 95 20 73 30 | 000 | | 25.41 36.84 | BRS | | |
| 121 8.0 15.75 BRS 122 10.0 19.40 BRS 189 12.0 20.25 BRS | SC | REENE | D MINI | ATURES | . P&P | | |
| HIGH VOLTAGE | Ref. 238 2 | mA 200 | Volts 3-0-3 | £ 1.6 | 2 39 | | |
| MAINS ISOLATING PRI 200/220 OR 400/440 | 212 13 | IA 1A 100 | 0-6, 0-6 9-0-9 | 1.9 1.5 | 3 46, 6 25 | | |
| SEC 100/120 OR 200/240 | 235 3 | 30.330 500.500 | 0-9.0-9 | 1.6 9 2.0 9 3.0 | 4 25 2 51 7 58 | | |
| VA Ref. E p 60 243 4.37 97 | 236 214 3 | 200, 200 | 0-15, 0-15 | 1.5 2.0 | 6 25 3 58 | | |
| 350 247 10.93 1.41 1000 250 26.31 BRS 2000 253 44.12 BPS | 221 206 | 700 (DC) | 20-12-0-12 0-15-20, 0 | 2-20 2.3 -15-20 3.6 | 8 58 3 72 | | |
| ON-SITE TOOL ISOLATORS | 203 204 | 500, 500 A 1A | 0-15-27.0 | -15-27 3.1 -15-27 .4.1 | 5 72 4 72 | | |
| 240v to 110v (10 BS3535) Ref. VA £ 277 500 26 66 | 5112 5 | | 12, 15, 20. | 24, 30 1.9 | 58. | | |
| 278 750 34.47 279 1000 37.63 | 240v ma | D AUTO | D. TRAN | USA 2-pin d | ERS outlets | | |
| 280 1500 41.55 P&P BRS Send for details | 20VA £3 | .29. P&P : 6.37, F&P 10 97 P | /2p. 85p P €1 25p | Ref. Ref. | 4W | | |
| BRIDGE RECTIFIERS | 1000VA 2000VA | £18.39 BF | RS. RS | Ref | 84W 95W | | |
| 100v 2A 40p 100v 6A 70p | 3 wart RI | HIGH QU | ALITY M | DULES | £2,30 | | |
| 200v 1A 35p 200v 2A 45p | 5 watt Rf 10 watt I | NS Amplifi RMS Amp | er ifier | | £2.65 £2.95 | | |
| 400v 2A 50p 400v 4A 65p 600v 2A 55p | 25 watt / Pre-Amp | IMS Amp i for 3-5-10 | ifier w (new) | | £3.95 £6.50 | | |
| 500v 10A PM7A6 £2.35 | Power Su Power Su | pplies for 2 pplies for 2 | 3-5-10w 25w | £ | £1.20 £3.00 | | |
| P&P 15p VAT 1212% | Transform Transform | ner for 3 w ner for 5-10 |)w | | £1.90 £2.30 | | |
| AV08 £61.09 AV072 £24.07 | P&P Amp | ner for 25w s/Pre-Amp | / s/Power S | uoplies | £2.60 18p | | |
| AVOMM5 £20.94 | 3&P Tran | stormers V | AT 121/2% | | 37p | | |
| STEREO F.M. TUNER | Complete | NEX e chassis, in | w stered | 30 ms amps, pr | e-amp. | | |
| 4 Pre-selected stations Switched AFC | trans.) | uppiy, fror £15.75. 1 cab €3.6 | າເpaniel, k Mains tra 55, ຄ& ຄ.ອ.ອ | nobs (néeds ns. £2.45. n VAT 1214 | mains Teak | | |
| Supply 20-35v 90Ma Max £19.95. P&P 25p VAT 121/2% | | POV | VER UN | ITS | | | |
| MAGNETIC TO CERAMIC CARTRIDGE CONVERTER | 3V, 4 | CC12-05 | Output sv 5V, 9V, 1 | vitched 2V at 500mA | | | |
| ONLY £2.65 P&P 18p | | L4.08. PE | | GIRONS | | | |
| BSR MINI-DECK | 15W | £2.90. 18 Solder | BW £2.75. ng iron kit | 25W £2.45 £3.90 | | | |
| 4-speed autochanger £6.00. BSR P128R 3 speed single or puto | Stan | d for above | E1.13. P | AP 25p VAT | 8% | | |
| chassis £16.25 Garrard \$P25 Mk. IV (Chassis) | EL STOCK: | ECTROSIL | AND SEMI | CONDUCTOR | RGAIN | | |
| £17.20 P&P. 72p VAT 121/2% | PAKS. | CALLERS SEND | WELCOME STAMP FOI | E (MONFRI R LISTS | I.) OR- | | |
| Barrio El | | | | | | | |
| Sanne E | EC | | | 26 | 1. E | | |
| 3,THE MINORI | ES.L | OND | ONE | C3N | 1BJ | | |
| | | 1.49 | 18 22 | 16/0 | | | |
| | | 1-4-6 | 00.00 | 010/0 | | | |

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST WW-040 FOR FURTHER DETAILS

www.americanradiohistory.com

DEMA ELECTRONICS INTERNATIONAL ELECTRONIC COMPONENTS DISTRIBUTOR FOR INDUSTRY AND HOBBYIST

| "ANN | MD! | THLY | SPECIAL - WHIL | S E THEY L | AST | |
|---|-------------------------------------|----------------------------------|----------------------------|--|---|--------------------------|
| TTL 7400 .09 741 7451 09 74 | B3 .! | 59 | LINI LM3 | EARS 80 .69 55 .69 | LM709 | .19 |
| 7453 .11 74 | 165 .8 | 89 | LM5 | 56 .69 | LM3900 | .29 |
| MEMDRIES 1101 256 - Bit Ram I | Mos. | .99 | 5262 | 2048 - Bit F | Ram | 3.95 |
| 1103 1024 - Bit Ram 5260 1024 - Bit Ram | Mos. | 1.45 1.45 | 1702A 5203 | 2048 - Bit F 2048 - Bit U | rom. J/Violet Pron | 9.95 ns. 8.95 |
| 5261 1024 - Bit Ram | L/Power | 1.45 | 2102 | 1024 - Bit S | Status Ram | 2.75 |
| CT5001 12 Digit 4 Fund CT5002 Batt Dper 5001 CT5005 12 Dig 4 Fund | c49 I .59 w/Mem69 | or 3/1.0 or 3/1.3 or 3/1.5 | 00 531 25 531 50 700 | 1 28 Pi 4 24 Pi 1 4 or 0 | n BCD 6 Dig n 6 Dig Mux 6 Digit Alarm | Mux 2.75 3.25 3.50 |
| TTL 7400 SERIES | .3440 6.0 | | 17495 | 6 0.95 | 174155 6.0 | 60 |
| 7400 £ 0.11 7401 0.11 7402 0.11 | 7440 £ 0 7441 0 7442 0 | .60 | 7485 7486 7488 | 0.24 | 74155 £0 74156 0 74157 0 | 69 69 |
| 7403 0.11 7404 0.13 | 7443 0 7444 0 | .55 60 | 7489 | 1 50 0.40 | 74158 0 | 69 89 |
| 7405 013 7406 0.22 7407 0.22 | 7445 0 7446 0 7447 0 | .75 .85 .75 | 7492 | 0.55 0.43 0.43 | 74162 0 74163 0 74164 1 | .89 .05 |
| 7408 0.14 7409 0.14 | 7448 0 7450 0 | 65 | 7494 7495 | 0.49 | 74165 1 74166 1 | 05 |
| 7410 0.11 7411 0.16 | 7451 0 7453 0 7454 0 | 13 | 7496 74100 74107 | 0.55 | 74170 1 74175 0 74180 0 | .90 80 |
| 7413 0.26 7416 0.22 7417 0.22 | 7460 0 7470 0 | 11 | 74121 74122 | 0 27 0.37 | 74181 2. 74182 0 | 50 80 |
| 7420 0 11 7426 0 23 | 7472 0 7473 0 | .21 25 | 74123 | 0.49 | 74192 0. 74193 0 | 90 85 |
| 7430 0 12 7432 0.22 7437 0 25 | 7474 0 7475 0 7476 0 | .25 .37 .25 | 74150 74151 74153 | 0.59 0.59 0.69 | 74194 0. 74195 0. 74198 1 | 80 70 |
| 7437 0 25 7438 0 25 | 7483 0 | 69 | 74154 | 1.05 | 74199 1 | 70 |
| 74S00 .24 74S02 .29 | 74S04 .29 74S08 .35 | | 74520 74522 | 29 29 | 74S74 1 | .35 |
| 74S03 29 LOW POWER SCHOTT | 74S10 29 | | 74532 | .39 | 1741 6100 | |
| 74LS00 .23 74LS02 23 74LS04 25 | 74LS20 .2 74LS32 .2 74LS40 .3 | 7 | 74LS90 74LS93 74LS95 | 1.35 1.35 2.50 | 74LS193 1 | 65 |
| 74LS08 27 74LS10 23 | 74LS42 1.3 74LS74 .3 | 5 | 74LS107 74LS164 | 39 1.80 | | |
| CMOS 4000 SERIES 4000A £ 0 19 | 4014 £ | 10 | 4028 | £ 0 95 | 4071 €0 | 23 |
| 4001 0 19 4002 0 19 | 4015 | 10 0.55 | 4030 | 0.50 | 4072 0 | .25 .25 |
| 4006 0.90 4007 0.19 4008 1.30 | 4020 | 15 | 4043 4044 4049 | 1.20 | 4075 0 | .25 |
| 4009 0 49 4010 0 49 | 4023 0 |) 19) 85 | 4050 4066 | 0.48 | 4082 0 4528 0 | 29 85 |
| 4011 0 19 4013 0.39 | 4025 4027 | 0 19 0.75 | 4068 4069 | 0.23 0.23 | 4585 1 | 25 |
| LINEARS LM300 TO99 £ | 0 45 340U | T092 | £ 1.25 | 739 | A DIP £0 | 1.65 |
| 302 TO99 304 TO100 | 0.45 381 0.50 546 | A DIP V DIP | 1 05 0 51 | 747 748 | A DIP C | 1.44 |
| 305 TO99 307 V DIP | 0 60 550 0 38 555 | A DIP V DIP | 0.55 | 5556 (145 5558 (145 | 6) V DIP (8) V DIP (| 1.65 1.65 |
| TO99 308 A DIP TO99 | 0.45 556 | B DIP B DIP | 2.55 | LM3900 | A DIP C A DIP C |).35).45 |
| 309К ТОЗ 310 Т.ркд | 1 45 562 0 65 565 | B DIP A DIP | 2.55 1.25 | 75451 75452 | V DIP 0 V DIP 0 | .45 |
| 311 V D(P 320K TO 3 NEG | 0 90 566 | V DIP V DIP | 1.20 | 75453 75454 75491 | V DIP C V DIP C |).45).45).65 |
| 324 A DIP 339 A DIP | 1.07 709 1.49 710 | A DIP | 0.22 | 75492 ICL8038 F | A pkg 0 unct Gen 1 |).75 95 |
| 340K TO3 12V 1 AMP | 2.10 711 723 | A DIP A DIP | 0 30 0.38 | Volt Contr 8864 22 P | Oscillator, Sine In pkg. 1 | . Sq .45 |
| V = Mini Dip A = 14L Data sheets supplied on | Dip B = 1 request Add | SL DIP 1 20 ea. e×c | 099 8-P epted as no | in Header T(pted. | 0100-10 Pin Hea | Ider |
| MEMORIES W/DATA | s £ 17 | 9 | CALC 5001 | Cat Chip | CLOCKS w/DA | TA .99 |
| 1103 1024 Bit Ram M 7489 (8225) 64 Bit Ra | los 2.2 m TTL 1.5 | 5 | 5002 5005 5311 | Cal Chip Cal Chip Clock Chip | 1 | . 19 .49 .95 |
| 8223 Programmable Ri 5260 1024 Bit Ram Lo | OM 2.5 ow Power 1.9 | 5 | 5312 5313 | Clock Chip Clock Chip | 2 | .95 95 |
| LEDS | | | 5314 5316 Data only | Clock Chip Clock Chip (for any of a | 3 Jove n | .45 .95 50 |
| MV 5020 Jumbo Red or MAN I Red 7 Seg. 270' | Ctear £ 0.1 | TRANS | Refundat | le Against Pu | rchase. | |
| MAN 3A Red Seg 127 MAN 5 Green 7 Seg 27 | .3 70 1.7 | 5 2N 221 5 2N 222 | 9A TO5 | £ 0.37 20 8 0.15 20 | 4124 TO92 0 4126 TO92 0 |).10-).10- |
| MAN 5 .5 Solid Seg. 9 Digit Array Fairchild with clear magnifying | 2.5 37 J lens 2.9 | 2N 236 2N 290 | 9 TO | 8 0.10 2N | 4401 TO92 0 5225 TO92 0 | 0.10 |
| DISCOUNTS | M | 2N 322 | , 10 | 0.3212M | - J220 TU92 C | |
| 10% on orders over £ 15% on orders over £ | 10 ORU 25 £ 2 | 5 | Guarant | eed By DEMA | ELECTRONIC | s |
| TERMS: PRICES | LISTED | ARE | BRIT | ISH PO | JNDS & | PENCE. |
| | MERICA | RD, E | H OF | LAY CA | RD ACC | EPTED. |
| Card # | and ex | pirati | on d | ate requ | uested). | TERMS |
| IPOSTAL | AND H | AND | LING | CHARG | ES | |
| SHIPME | NT VIA | AIR add | MAIL | £ 10 | and over | |
| 5.00-9.9 | 9 | add . | 35 | Nc | Charge | |
| DEMA | A ELEC | TRC | NICS | S INT | RNATI | ONAL |
| P.O. Box | 407 | | Sar | Ramor | , Ca. 945 | 83 USA |
| | | | | Cab | Ie DEMA | ELINTL |





Tel: 01-261 8000

www.americanradiohistory.com

Get to the Point Quickly with ANTEX Model X25

Point 1

Near-perfect insulation. Breakdown voltage 1500 A.C. Leakage current 3.5 uA.

Point 2

Top-efficiency in heat transfer. Element slides inside the soldering bit. 25 watts but equivalent in heat capacity to 60 watts.

Point 3

High grade phenolic handle (own moulding!) Stainless steel shaft. - 3 core 0.4mm. Flexible lead.

Point 4

Iron-coated bits that do not stick to the shaft but slide on and off easily. 3 tip sizes 2.4, 3.2 and 4.7mm.

Point 5

Price with standard (3.2mm.) bit £3.20 (P+P 0.22) each Spare elements £1.52 each Spare bits £0.50 each

Point 6

A well balanced tool – length 22cm. weight 50gr.

Prices include VAT Postage + Packing extra as shown in brackets.



ANTEX colour catalogué.

(Giro No. 258 1000)

STAND S.T.3

High grade insulation material, chromium plated steel spring. Suitable for all our models. Replaceable sponges, space for spare bits. Complete £1.37 (P+P 0.24)

| from elec | tric | al | , r | ac | dic |) (| ٦C | Ca | ١٢ | ac | CE | ess | or | Y. |
|------------------------------------|------|----|-----|----|-----|-----|----|----|----|----|----|-----|----|----|
| shops or from Antex Ltd., Freepost | | | | | | | | | | | | | | |
| (no stamp | n re | qı | Jir | e | (t | PI | yı | n | bu | th | | | | |
| PL1 1BR Telephone 0752 67377/8. | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | |
| Name . | | | | | | | • | | | | ÷ | | | |
| Address | | | 4 | | | | × | | | - | ę | ÷ | | |
| 51115 | • • | • | * | ÷ | ę | | | • | • | , | 4 | ŝ | • | ł, |



The James Scott range of Microwave equipment now offers industrial users a greater choice of alternative systems in robust, industrial, cast aluminium housings, for a wide variety of applications.

The range is made up of standard sub-assemblies which can be permutated to suit Individual application requirements.

Some Suggested Applications for these Units Level controllers: Proximity alarms; Small object counters; Process control systems; Positioning systems; Door opening systems; Safety barriers; Presence/detectors; Train control systems; Vibration sensing systems; Intruder alarms; Road vehicle systems.

If any of the above are your problems or if you have a particular problem for which we could adapt a system please write or telephone for further information and technical literature to.





97

WW--054 FOR FURTHER DETAILS

Bahrain Singapore Thailand Iceland Brazil Sweden Germany Iran Jamaica St. Kitts Tunisia



- 7. Set of uw more: the set of potentiometers (including mains switch) £2.05 9. Set of potentiometers (including mains switch) £2.05 9. Set of 4 push-button switches: rotary mode £3.70
- Set of resistors. Capacitors. Country. E3.50
 semi-conductors for power supply. E3.50
 Set of miscellaneous parts including DIM skits. mains input skits. mains input skits. Mains e4.25 knobs. E4.25 14. Set of metalwork parts including silk screen printed fascia panel and all brackets. fixing parts. etc. E6.30 E0.30 16. Teak cabinet 18.3" x 12.7" x 3.1" £9.85

Designed in response to demand for a tuner to complement the world-wide acclaimed Linsley Hood 75W Amplifier, this kit provides the perfect match The Wireless World published original circuit has been developed further for inclusion into this outstanding slimiline unit and features a pre-aligned front end module, excellent a minipedition and temperature compensated varicap tuning, which may be controlled either continuously or by push button pre-selection Frequencies are indicated by a frequency meter and sliding LED indicators attached to each channel selector pre-set. The PLL stereo decoder programmer active filters for birth, suppression and nower is supplied via a indicators and active filters for birdy suppression and power is supplied via a toroidal transformer and integrated regulator. For long term stability metal oxide resistors are used throughout.

STOP PRESS! LINSLEY-HOOD CASSETTE DECK

Goldring-Lenco mechanism, as specified £19.10

PCB, Components - Please send for details

Wireless World Amplifier Designs

Wireless World Amplifier Designs Full kits are not available for these projects but component packs and PCBs are stocked for the highly regarded Bailey and 20W class AB Linsley Hood designs. together with an efficient regulated power supply of our own design. Suitable for driving these amplifiers is the Bailey Burrows pre-amplifier and our circuit board. for the stereo version of it features 6 inputs scratch and rumble filters and wide range tone controls which may be either rotary of slider operating. For those intending to get the best out of their speakers we also offer an active filter system described by D C Read which splits the output of each channel from the pre-amplifier into three channels each of which is led to the appropriate speaker by its own power amplifier. The Read/Texas 20W or any of our other kits are suitable for these. For tape systems a set of three PCBs have been prepared for the integrated circuit based high performance stereo Stuart design. Details of component packs are in our free list.

| 30W Bailey Amplifier | |
|---|-------|
| BAIL Pk 1 F/Glass PCB | £1.00 |
| BAIL Pk 2 Resistors, Capacitors Potentiometer set | £2.35 |
| BAIL Pk 3 Semiconductor set | £4.70 |
| 20W Lipsley Hood Class AB | |
| LUAD PL 1 E / Giper PCB | £1.05 |
| LUAD FK 1 77 Oldss FCD | £3.20 |
| LHAD FR 2 Resistor, capacitor i otentionicito sol | £3.35 |
| LHAD FK 5 Setticoloucio set | |
| Regulated Power Supply | £0.8! |
| 60VS Pk TF/Glass PCB | £1 91 |
| 60VS Pk 2 Resistor, Capacitor set | 62.10 |
| 60VS Pk 3 Semiconductor set | £3.10 |
| 60VS Pk 6A Toroidal transformer (for use with Bailey) | 17.9 |
| 60VS Pk 6B Toroidal transformer (for use with 20W LH) | £7.2 |
| Bailey Burrows Stereo Pre-Amp | |
| BBPA Pk 1 F/ Glass PCB | £2.3 |
| BBPA Pk 2 Resistor, capacitor semiconductor set | £6.10 |
| BBPA Pk 38 Rotary Potentionseter set | £2.40 |
| REDA DL 25 Slider Potentiometer set with knobs | £2.7 |
| DBFATK 55 Shoer Foreitheneter set that theory | |
| | |

Further details of above and additional packs given in our FREE LIST

^{1/a}nd Portugal Mozambique Belgium Sumatra

In Hi-Fi News there was published by Mir Linsley-Hood a series of four articles (November, 1972)-February, 1973) and a subsequent follow-up article (April, 1974) on a design for an amplifier of exceptional performance which has as its principal feature an ability to supply from a direct coupled fully protected output stage, power in excess of 75 watts whilst maintaining distortion at less than 0.01% even at very low power reverse to power amplifier is complemented by a pre-amplifier based on a discrete component operational amplifier referred to as the Liniac which is employed in the two most critical points of the system namely the equalization stage and tone control stage, positions where most conventional designs run out of gain at the extremes of the frequency spectrum. Unusual features of the design are the variable transition frequencies of the tone controls and the variable slope of the scratch filter. There is a choice of four inputs, two equalized and two linear, each having independently adjustable signal level. The attractive slimitine unit pictured has been made practical by highly compact PCBs and a specially designed transformer. Toroidal transformer

FREE TEAK CASE WITH FULL KITS KIT PRICE ONLY £62.40

WIRELESS WORLD FM TUNER



- 5. Fibreglass printed circuit board for storeo decoder 6.
- £3.45
- E3.45 Set of components for channel selector switch, module including libreglass printed circuit board, push-button switches, knobs, LEDs, preset adjusters, etc. E8.30 8

One each of packs 1-16 inclusive are required for complete stereo FM tuner. Total cost of individually purchased packs £76.85

erc. 15. Construction notes (free with complete kit) . . 16. Teak cabinet 18.3" x 12.7" x 3.1"

9. Function switch. 10 turn tuning palentiometer. knobs

Set of capacitors. recurrers. security 2.2.95
 To the second sector of the second sector sector of the second sector sector

Price

65.30

FA 25

£9.85



PRICE STABILITY!

Order with confidence¹ Irrespective of any price changes we will honour all prices in this advertisement for two months from issue date provided that this advertisement is quoted with your order. E&OE VAT rate changes excluded All components are brand new first grade full specification devices. All resistors (except where stated) are low noise carbon film types. All printed circuit boards are fibre-glass, drilled, roller tinned and supplied with circuit diagrams and construction layouts

Orders. Subject to 121/2%* Surcharge for VAT. Carriage free MAIL UΚ ORDER ONLY ('or at current rate if changed) Securicor Delivery For this optional service (Mainland only) add £2 50 VAT

inc per kit Overseas Orders No VAT Postage charged at actual cost plus 50p packing and handling

DEPT. WW06 **POWERTRAN ELECTRONICS** PORTWAY INDUSTRIAL ESTATE ANDOVER, HANTS SP10 3NN

Oman Norway United States Guernsey South West Africa Turkey Ghana Zambia Yugos/₄/

Eire Hungary Muscat &

S Angola Cyprus



| Pack | T20 | T30 | Pack | 20 |
|---------------------------------------|--------------|--------------|--|------------|
| 1 Sel af law noise resistars | 0.95 | 1.05 | 8. Toroidal Iransformer — 240V prim. | |
| 2. Set of small capacitors | 1.50 1.40 | 2.10 2.05 | e.s. screen | .95 .50 |
| 4. Set of miscellaneous parts | 1.90 | 1.90 | 10. Set of metalwork, fixing parts 4 11. Set of cables, mains lead | .20 |
| 5. Set of slide, mains, P.B. switches | 1.20 | 1.20 | |).40 |
| 6. Set of pots. selector switch | 2.00 | 2.00 | 12. Handbook (free with complete kit) 0 |).25 |
| 7. Set of semiconductors. ICs. skis | 7.25 | 7.75 | 13 Teak cabinet 15.4" x 6.7" x 2.8" 4 | .50 |

2 NEW TUNERS!

WW SFMT II

Following the success of our Wireless World FM Tuner kit we are now pleased to introduce our new cost reduced model designed to complement the T20 and T30 amplifiers. The frequency meter of the more advanced model has been omitted and the mechanics simplified however the circuitry is identical and this new kit offers most exceptional value for money Facilities included are switchable afc, adjustable, witchable muting channel selection by slider or readily adjustable pre-set push-button controls and LED tuning indication. Individual pack prices in our free list. our free list

POWERTRAN SFMT

This easy to construct tuner using our own circuit design includes a pre-aligned front end module PLL stereo decoder adjustable, switchable end and push-button channel selection. As with all our full kits, all components down to the last nut and bolt are supplied together with full constructional details



SQM1 - 30

SEMICONDUCTORS as used in our range of quality audio equipment.

| 2N699 2N1513 2N1711 2N2926G 2N3055 2N3442 2N3442 2N3406 2N4062 2N4402 2N4402 2N4402 2N45457 2N5457 2N5457 2N5457 2N5451 2N5451 40361 40362 BC108 BC109 | $\begin{array}{c} {\rm f0.20} \\ {\rm f0.20} \\ {\rm f0.25} \\ {\rm f0.10} \\ {\rm f0.45} \\ {\rm f1.20} \\ {\rm f0.09} \\ {\rm f0.11} \\ {\rm f0.60} \\ {\rm f0.42} \\ {\rm f0.45} \\ {\rm f0.40} \\ {\rm f0.41} \\ {\rm f0.10} \\ {\rm f0.10} \\ {\rm f0.10} \end{array}$ | BC212X BC182L BC182L BC217L BC217L BC217L BC217L BC272 BC27 BC27 | 60.12 60.10 60.11 60.12 60.14 60.14 60.85 60.85 61.60 60.40 60.40 60.40 60.25 60.20 60.20 60.20 60.20 60.20 61.50 60.95 61.20 61.30 | MPSA65 MPSU55 SBA750A SU301 SU301 SU304 SU32748P SN72741P SN72748P TH29A TH29A TH29A TH29A TH29A TH29A TH29A TH29A TH29A TH29A TH2418 TH2418 TH2428 TH2418 TH2428 TH2418 TH245 SB05 SB05 | £0.35 £0.40 £0.60 £2.50 £1.30 £0.40 £0.40 £0.40 £0.30 £0.50 £0.71 £0.78 £0.74 £0.74 £0.99 £0.85 £0.74 £0.99 £0.85 £0.74 |
|---|--|---|--|---|--|
| 2N5461 2N5830 40361 40362 BC107 BC108 BC109 | £0.50 £0.35 £0.40 £0.45 £0.10 £0.10 £0.10 | CA3046 LP1186 MC1310 MC1351 MFC4010 MJ481 MJ491 | £0.70 £5.50 £2.90 £1.05 £0.95 £1.20 £1.30 | TIP42A TIP418 TIP428 1N914 1N916 1S920 5B05 | £0.90 £0.82 £0.98 £0.07 £0.07 £0.10 £1.20 |
| BC109C BC125 BC126 BC182 BC212 BC212 BC182K | £0.12 £0.15 £0.15 £0.10 £0.12 £0.10 | MJE521 MPSA05 MPSA12 MPSA14 MPSA55 | £0.60 £0.25 £0.55 £0.35 £0.25 | FILTÉR FM4 SFG107MA | \$ £0.80 £2.80 |
| | | | | | |





CONVERT NOW TO QUADRAPHONICS!

With 100s of titles now available no longer is there any problem over suitable software. No problems with hardware either Our new unit the SQM1-30 simply plugs into the tape monitor socket of your existing amplifier and drives two additional speakers at 30W per channel. A full complement of controls including volume bass, treble and balance are provided as are comprehensive switching facilities enabling the unit to be used for either front or rear channels, by-passing the decoder for stereo-only use and exchanging left and right channels. The SQ matrix decoder is based upon a single integrated circuit and was designed by CBS whilst the power and tone control sections are identical to those used in our T30 + 30 amplifier which the SQM1-30 matches perfectly. Kit proce includes CBS licence fee **Special offer to T20 + 20 and Texan owners!** Owners of T20 + 20 and Texan amplifiers, which have no tape monitor outlet, purchasing an SQM1-30 will be supplied, on request, a free conversion kit to fit a tape monitoring facility to the existing amplifier. This makes simple the connection to the highly adaptable SQM1-30 quadraphonic decoder /rear channel amplifier. With 100s of titles now available no longer is there any problem

SQ QUADRAPHONIC DECODERS





Feed 2 channels (200-1000mV as obtainable from most pre-amplifiers or amplifier tape monitor outlets) into any one of our 3 decoders and take 4 channels out with no overall signal level reduction On the logic enhanced decoders Volume. Front-Back LF-RF balance LB-RB balance and Dimension controls can all be implemented by simple single gang potentiometers. These state-of-the-art circuits used under licence from CBS are offered in kits of superior quality with close tolerance capacitors metal oxide resistors and fibre-glass PCBs designed for edge connector insertion. All kit prices include CBS licence fee

£5 90

CBS Incence fee £5.90 M1 Basic matrix decoder with fixed 10.40 blend. All components, PCB £5.90 L1 Full logic controlled decoder with wave matching and front back logic for enhanced channel separation. Al components PCB £17.20 L2A More advanced full logic decoder with variable blend extended frequency response, increased front back separation. All components, PCB £24.60 £17.20 £24.60



Kenya France St. Martin, Java New Zealand Borneo South Africa Denmark Nigeria Anguilla Finite Kenya France St. Martin, Java New Zealand Borneo South Africa Denmark Nigeria Anguilla

/1cAmps

Price

30p 30p 30p 25p 25p 35p 35p

Bargains in Semi-Conductors, components, modules & equipment. R-P-P Packs

Originated in 1959 by the Company's managing director, his were the first semi-conductor and component packs to be marketed in this country, and indeed, the company's name grew out of "British Industrial Pre-Packed Components". Today, Bi-Pre-Pak continues to occupy a position of pre-eminence in the supply of packs as well as a vestly extended range of products detailed in our latest 24-page A.4 size free catalogue. Send 10p stamped large addressed envelope for your copy by return. IT'S ALL INI OLD EDEE CATALOGUE

Component Packs

| CP1 | 150 | Capacitors mixed bag of paper, silver mica, electrolytics. |
|--------|-----|---|
| | | etc Approx quantity, counted by weight 60p |
| CP 2 | 200 | Resistors, mixed bag of different types, values, wattages, etc. Approx quantity, counted by weight 60p |
| CP3 | 40 | Wirewound resistors, mixed types, values and wattages 60p |
| CP4 | 12 | Potentiometers, pre-sets, w/wound, carbon, etc. Mixed |
| CP5 | 5 | Earphones, single low impedance for transistor radios, cassettes, etc. Less plugs, for suitable plugs see PAKs CP9 and CP10 60p |
| CP6 | 50 | TO-5 mounting pads, fits between transistor and board, for that pro-finish 60p |
| CP8 | 500 | Cable clips for G P O 1/6" dia. cable Nylon with hardened |
| CP9 | 5 | 3 5mm plugs, miniature jack, to fit earphones in PAK CP5 60p |
| CP10 | 5 | 2.5mm sub miniature jack plugsto fit earphones in PAK |
| CP 1 1 | 6 | Screwdrivers, 1 x mains neon tester, 5 x grub screwdrivers 60p* |
| CP12 | 10 | Reed relay inserts. 1" long 1/s" dia. These will operate from an external magnet or coil For magnets see PAK CP13 60p |
| CP13 | 10 | Magnets of various sizes for operating reed switches on PAK CP12 ideal for burglar alarms on doors and 60p* |
| CP14 | 40 | Potentiometers, presets, wirewounds, carbons, dual gangs, with and without switches, etc. Mixed values and wattages £1.20 |
| CP15 | 12 | Standard crocodile clips, screw fixing, good quality 60p* |
| CP16 | 5 | P.C. boards each containing a BF180 UHF amplifier transistor A good basis for building a T.V. aerial pre-amp |
| CP17 | 25 | Electrolytic Capacitors, various values and voltages, many useful types, from T.V. to transistor radio and Hi-Fi |
| CP18 | 1 | Light activated SCR 50 volts 1.6 amps type L9F. Ready mounted on PC board with gate resistor and leads fitted Full data and circuit diagrams for 1.4 projects includes slave photo flash unit, burglar alarm, etc. |
| CP19 | 3 | Micro switches 1 pole change over, standard model 1%" x 60p |
| CP20 | 10 | Relays assorted types. Ex-G P O and others mixed £1.20 |
| CP21 | 200 | Square inches of copper laminate P C board, in approx 8 60n |
| CP22 | 3 | Fibreglass plain printed circuit boards, approx 21/211 x 1411 60n |
| | | 60p |



4 Switches miniature push to make, single pole

CP23



Semi-Conductors

TESTED AND GUARANTEED PACKS

3 SN7490 integrated circuits, 14 pin dual in line TTL type Decade counter. Get one FREE, these are 60p each in singles. £1.20p TP4

ALL THE FOLLOWING ARE AT 60p EACH PACK

- ALL THE FOLLOWING ARE AT 60p FACH PACK TP9: 5 SN7400 integrated circuits. 14 pin dual in line TIT type Quad 2-input NAN0 gate Get one FREE, these are 15p each. 19:0 2 Light dependant resistors. 400 ohms light, 1 megohm dark, ¼' dia Thi 10 Transistors XB102 and XB112 equivalent to AC126. AC156. OCB1/2. OC72 etc P1:2 3 SV127 Silcon rectifiers 1000 piv 1 amp Plastic T V rectifier TP13 5 OCP11 Light sensitive transistors. TP14 20 OC71 germanium PNP audio pre amp transistor. black glass type TP15 20 OC81 Germanium PNP audio output transistor, white glass type

- type 20 OC200/1/2/3 transistors. PNP silicon T0-5, unmarked 20 1 watt zener diodes mixed voltages 6.8 to 43 volts 20 2N3707/8/9/10 transistors. NPN silicon plastic. TP16 TP18

- PTP18 20 2N37077/8/9/10 transistors. NPN silicon plastic-ummarked
 PTP1 100 Duodes mixture of germanium gold bonded silicon, etc. al useful selection of amary types marked and ummarked useful selection of amary types marked and ummarked 20 BFF50/1/2. 2N856/7. 2N1613. etc. NPN silicon 10-5 uncoded COMPLEMENTARY to PAK TP24
 PTP4 20 BFF562/2N2904/5 etc. PNP silicon 10-5 uncoded COMPLEMENTARY to PAK TP23.
 PT0 20 NPN silicon planar transistors. T0-18 similar to BC108. etc. uncoded.
 PTP1 20 20 NPS 5 silicon planar transistors. T0-18 similar to BC178. etc. uncoded.
 PTP2 20 NPS 5 silicon plastic transistors uncoded and ungraded for colours

UNTESTED PACKS — 60p each Specially for keen bargain hunters

- 50 PNP germanium transistors. AF and RF Very good yield 150 Germanium diodes miniature glass type 40 Zener diodes. 250 mW OAZ240 range average 50% UT2 UT5

- UT5 40 Zener diodes. Z50 mvv OAZ240 Joings Children, 2004
 UT6 25 Zener diodes. 1-1½ watt top hat type, mixed voltages.
 UT9 40 NPN slicon palaar transitors, of the ZN3707-11 range.
 Iow noise amp
 UT0 15 Power transitors, PNP germanium and NPN silicon.
 mostly T0-3 but some plastic and some marked.
 UT13 15 Integrated activuits, experimenters pak, dual in line. T0-5.
 TTL. DTL, marked and unmarked. some definitely good but not house.
- but old types

FOR FULL RANGES - SEE CATALOGUE

Singles BRIDGE RECTIFIERS Plastic encapsulated

| | | | - | |
|-----------------|---------------|-----------|------|-----|
| P.I.V | 50v | 100v | 400v | |
| 1 amp | 25p' | 35p | 45p | |
| 2 amp | 35p' | 45p | 55p | |
| 4 amp | 45p | 50p | 80p | |
| 6 amp | 50p | 60p | 90p | |
| BY164 equiv SKB | 2/02 400v 1.5 | amp. 45p. | | |
| FETS | | UNI-JUNC | TION | |
| 2N3919 | 18p | TRANSIST | ORS | |
| 2N4416 | 200 | 2N2160 | | 65p |
| MOS F.E.T.s | | 2N2646 | | 48p |
| 3N141/MEM616 | 50p | TIS43 | | 31p |
| | | PUTs | | |
| | | 2N26027 | | 50p |
| Also Power Dio | des, Thyris- | | | |
| tors, Triacs, D | iacs-Zener | LEOs | | |

Diodes, Opto-Electronics, etc. TIL209-Red TIL211-Green



Unuss nation determation improved version of our famous Mk 2 model: of which thousands are in regular use Size 150 x 75 x 50mm, strong plastic case with handle/stand. 4 push button operation, 4 patterns. Sett-contained line and frame generator and synchro pulse. Pre-set adjust for R F output and line/frame such tilses 4 alkaline throe 1600 batts. synch Uses 4 alkaline type 1600 batts. Blank raster facility. FOR COLOUR AND MONO. (P/P add 35p)



EXCEPT ITEMS MARKED

WHICH CARRY DNLY 8%

VAT ADD 121/2%



POWER TRANSISTORS

Many other types available from 3 to 115 watts

Watts

20

40

Vce

INTEGRATED CIRCUITS

400 40P1 40N2 40P2 90N1 90P1 90N2 90P2

SIGNAL GENERATOR

For MW and IF Covers 550 KHz to 1.6 MHz for MW and 400 to \$50KHz for IF Fully portable Invaluable in AM repair and alignment (bols (p / p 40p) £4.25

MTEGRATED CINCOTTS WM5314 Dual in line clock chip WS380/SL60745 Dual in line 2w audio amp with data...etc 75p Dual in line I.C. sockets 8 pin 14p; 14 pin 15p; 16 pin 16p;.

| POCKET SIGNAL INJECTOR | |
|--|-------------|
| Fountain-pen type. Invaluable for fault tracing in radio sets. | amplifiers. |
| TVs tape recorders, etc. Takes one HP7 battery | €2.00* |

| EX-G.P.O. 5in SIDECUTTERS Not new but in perfect order per pair | 50p |
|--|--------------|
| EX-G.P.O. 6" LONG NOSE PLIERS Not new, but in perfect order, per pair | 6 0 p |

| ALINS TRAN | SFORMERS | | |
|-------------|----------------|--------|--|
| 116 | 6v 0 6v 100mA | £1.22 | |
| 4712 | 12v 0 12v 50mA | £1.22* | |
| ST9/1 | 9v 1amp | £1.67 | |
| ST12/1 | 12v lamp | £2.05 | |
| ST18/1 | 18v lamp | £2.50 | |
| ST25/2 | 25v Zamp | £3.00° | |
| ST30/2 | 30v 2amp | £4.25 | |
| ST35/4 | 35y 4amp | £5.50' | |
| P 50p any o | nel | | |
| C EDGE CO | NECTORS | | |
| l v pe | Sizes | Pitch | |

| уре | 215.62 | Pitch | |
|-----------|----------|-------|------|
| SEC 6-way | 1.1/8/1 | 156'' | 32p |
| SEC 10 | 1.1/4.17 | 156'' | 150p |
| SEC 12 | 2'' | 156'' | 60p |
| SEC 16 | 2 1/2 '' | 156'' | 75p |
| SEC 18 | . 3'' | 156'' | 850 |
| SEC 22 | 31/2" | 156'' | 1.00 |

UHF TUNER UNITS Brand new, by famous manufacturer 625 lines. Channels 21-65, Ideal for use as TV sound receiver. With data £2.50

BOOKS

All free of VAT. We carry very large stocks of technical books by Babani & Bernard Publishers, by Newnes and Butterworth as well as reference books from the Common Market in English/German/Italian. All detailed in our cataloque

MONEY SAVER FOR CAR OWNERS

The SuperSpark Capacity Discharge Ignition Unit developed out of our original model (of which we have sold well over 9 (000) enables you to engy this system at a truly economic price. Facilities include simple adaption to pos or neg early immediate switch back to conventional ignition, anti-burglar immobilisation with all parts in totally enclosed strong metal case. Very easy to fit and install. With full instructions (P/P add 50p)

18p 33p KIT £7.95 READY-BUILT £10.50

| • B-P-P SE • Write your own nam clearly in block capit | CURITY | CHECK POINT MAKE SURE YOU GET OUR NAME AND ADDRESS RIGHT WHEN ORDERING. |
|--|-------------------|--|
| Check that your orde | n is correct for | Cash (cheque, money or postal order) |
| description, quantity as | nd price | with your order please Made out to |
| Don't forget VAT at 25 | 5% of total value | Bi-Pre-Pak Ltd |
| of order unless other | wise marked' or | Mention this journal when ordering if you |

of order unless otherwise marked or
Mention this journal when order
(8%). don't want to cut out the coupor

TERMS OF BUSINESS: VAT rates subject to alteration if decreed by

Government

Government VAT at 12/95 must be added to total value of order except for items marked ' or (8%), when VAT is to be added at 8%. No VAT on overseas orders. POST & PACKING Add 30p for UK rodres except where shown otherwise. Minimum mail order acceptable - c1. Overseas orders add 11 for postage. And difference will be credited or charged. PRICES Subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.



Co Reg No 820919

TELEPHONE: SOUTHEND (0702) 46344.

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

IT'S ALL IN OUR FREE CATALOGUE


WW-082 FOR FURTHER DETAILS

www.americanradiohistory.com

| A1065 1.25 EF36 0.66 GZ34 0.80 ARP3 0.60 EF37A 1.10 GZ37 1.00 ARP3 0.60 EF40 0.70 KT66 2.90 ATP4 0.50 EF41 0.75 KT88 3.85 DAF96 0.60 EF83 1.25 MH4 1.00 DaF96 0.60 EF83 1.25 MH4 0.70 DF96 0.60 EF83 0.40 OA2 0.45 D192 0.50 EF89 0.36 PC88 0.46 D196 0.70 EF91 0.46 PC88 0.46 D192 0.50 EF89 0.46 PC80 0.40 B1202 0.45 EF92 0.60 PC88 0.45 DY86/87 A5 EF92 0.60 PC88 0.45 B202 0.45 EF92 0.60 PC88 0.45 DY86/87 A5 C70 | PLUMBICON PY80 0.60 U25 PY81 0.50 U27 Py82 0.50 U27 Py83 0.50 U801 Py88 0.50 U801 Py801 0.55 U81 QQv03-10 1.50 U870 QQv03-10 1.50 U870 QQv03-10 1.50 U870 QQv03-12 1.60 UC180 SC1/400 3.60 UC42 VIDECON TUB VIDECON TUB TT21 6.00 UC182 VIDECON TUB AF186 AC126 A522 AC126 | TUBES TYPE XO 1071 1.00 UC43 0.70 1A3 1.00 UF41 0.70 1A3 1.00 UF40 0.40 1A4 0.75 UF80 0.40 1A4 0.76 UF80 0.40 1A4 0.76 UF89 0.50 184 0.45 UL41 0.70 1K4 0.50 UP45 0.50 114 0.50 UP45 0.50 12021 0.50 UV85 0.50 2021 0.50 UV85 0.50 2021 0.50 UV85 0.50 2021 0.60 0.45 S4 324 0.76 UL40 55 2021 0.50 0.45 S601 3.50 0.50 28001 3.00 58/2 0.50 28001 3.00 58/2 0.50 28001 3.00 58/2 0.50 28001 | Mullard £150 1.50 SR4GY 1.00 0.55 SU4G 0.55 0.30 SV4G 0.65 0.30 SV4G 0.65 0.30 SV4G 0.65 0.35 SZ4G 0.60 9.00 6AL5 0.50 0.60 6AL5 0.30 0.50 6AN5 0.60 55M 5.00 6AN6 0.60 55M 5.00 6AN6 0.60 55M 5.00 6AN8 0.40 6AN8 0.40 0.60 55M 5.00 6AN8 0.60 55M 5.00 6AN5 1.00 55M 5.00 6AN8 0.60 6AN5 0.00 1.00 6C36 0.020 1.00 <th>0.00 6AQ5 0.55 6AQ5W 0.70 6AS5 0.80 6AS5 0.80 6AS5 0.80 6AS5 0.80 6AS4 0.40 6AV5 0.70 6BA7 0.70 6BA7 0.70 6BA6 0.40 6B66 0.40 6B66 0.40 6B67 0.70 6B46 0.40 6B66 0.40 6B67 0.70 6B47 1.30 6B874 1.30 6B874 1.30 6B874 1.30 6B874 1.30 6B874 1.30 6B74 1.30 0 00 00 00 2N36384 2N4058 2N4058 2N4058 2N4058 3N126 3N154 3N154 3N154 3N154 3N154</th> <th>68W/7 1.00 6C4 0.40 6C6 0.50 6C66 0.50 6C66 0.50 6C66 0.50 6C66 0.75 6C6 0.45 6C7 1.10 6F8G 0.75 6F12 0.45 6F17 1.00 6F17 1.00 6F17 1.00 6F13 3.50 6H4 0.25 6J5 0.45 6J5 0.45 6J5 0.45 6J5 0.45 6J5 0.45 6J7 0.45 6J7 0.45 6J7 0.45 6J7 0.45 6K7 0.45 6K7 0.45 6K7 0.45 6SJ7 0.55 6SJ7 0.40 6SJ7 0.55 6SJ7 0.55 5SJ7 0.55 5S</th> <th>Link Link 12E1 3.75 12K7 GT 0.55 12SA7 GT 0.56 12SA7 GT 0.56 12SA7 GT 1.60 1945 1.60 20P4 1.10 20C15 1.00 30C17 1.10 30L15 1.00 30P113 1.10 30L15 1.00 30P113 1.10 3U15 1.00 3DP114 1.10 3L5GG 0.20 3DP114 1.10 3L5GG 0.20 3DP114 1.10 3L6GGT 0.455</th> <th>VE WITH A 955 0.50 955 0.50 955 0.50 955 0.50 957 0.50 957 0.50 957 0.50 9533 3.00 6057 0.80 6066 0.70 6067 0.80 6067 0.80 6067 0.80 6067 0.80 6067 0.80 60680 2.50 61468 4.00 9002 0.55 9003 0.70 9004 0.40 9002 0.56 9003 0.70 9004 0.40 9005 15.00 061322 15.00 061323 15.00 058P7 7.00 881 9.00 VCR 139A 8.00 CV 526 8.00</th> | 0.00 6AQ5 0.55 6AQ5W 0.70 6AS5 0.80 6AS5 0.80 6AS5 0.80 6AS5 0.80 6AS4 0.40 6AV5 0.70 6BA7 0.70 6BA7 0.70 6BA6 0.40 6B66 0.40 6B66 0.40 6B67 0.70 6B46 0.40 6B66 0.40 6B67 0.70 6B47 1.30 6B874 1.30 6B874 1.30 6B874 1.30 6B874 1.30 6B874 1.30 6B74 1.30 0 00 00 00 2N36384 2N4058 2N4058 2N4058 2N4058 3N126 3N154 3N154 3N154 3N154 3N154 | 68W/7 1.00 6C4 0.40 6C6 0.50 6C66 0.50 6C66 0.50 6C66 0.50 6C66 0.75 6C6 0.45 6C7 1.10 6F8G 0.75 6F12 0.45 6F17 1.00 6F17 1.00 6F17 1.00 6F13 3.50 6H4 0.25 6J5 0.45 6J5 0.45 6J5 0.45 6J5 0.45 6J5 0.45 6J7 0.45 6J7 0.45 6J7 0.45 6J7 0.45 6K7 0.45 6K7 0.45 6K7 0.45 6SJ7 0.55 6SJ7 0.40 6SJ7 0.55 6SJ7 0.55 5SJ7 0.55 5S | Link Link 12E1 3.75 12K7 GT 0.55 12SA7 GT 0.56 12SA7 GT 0.56 12SA7 GT 1.60 1945 1.60 20P4 1.10 20C15 1.00 30C17 1.10 30L15 1.00 30P113 1.10 30L15 1.00 30P113 1.10 3U15 1.00 3DP114 1.10 3L5GG 0.20 3DP114 1.10 3L5GG 0.20 3DP114 1.10 3L6GGT 0.455 | VE WITH A 955 0.50 955 0.50 955 0.50 955 0.50 957 0.50 957 0.50 957 0.50 9533 3.00 6057 0.80 6066 0.70 6067 0.80 6067 0.80 6067 0.80 6067 0.80 6067 0.80 60680 2.50 61468 4.00 9002 0.55 9003 0.70 9004 0.40 9002 0.56 9003 0.70 9004 0.40 9005 15.00 061322 15.00 061323 15.00 058P7 7.00 881 9.00 VCR 139A 8.00 CV 526 8.00 |
|---|---|--|--|---|--|---|---|
| ECC88 0.165 EM84 0.40 PCL805/85 ECF80 0.46 EV51 0.45 PFL200 0.70 ECF80 0.46 EV51 0.45 PFL200 0.70 ECF80 0.46 EV51 0.45 PFL200 0.70 ECF80 0.46 EV51 0.45 PL30 0.70 EC7804 2.50 EV86/87 0.45 PL81 0.55 EC4804 2.50 EZ40 0.70 PL83 0.50 ECH42 0.45 EZ40 0.70 PL83 0.50 ECH84 0.40 EZ81 0.36 PL504 0.35 ECL82 0.40 EZ81 0.36 PL506 0.85 ECL82 0.40 EZ81 0.36 PL506 0.85 | ACY20 BC113 ACY39 BC116 ACY30 BC116 ACY40 BC136 AD161 BC137 AD161 BC137 AD162 BC148A AD211 BC172 AC172 BC172A AF114 BC212A AF115 BCY31 AF116 BCY33 | 85Y95A 0A73 8Y100 0A79 8Y216 CA91 CR51/20 CA200 CR51/30 CA202 CR53/10 CA202 CR53/20 CC25 CR53/40 CC26 CR53/40 CC28 GET115 0C29 | OC780 2N918 OC81 2N1305 OC82 2N1307 OC820 2N1307 OC820 2N1307 OC83 2N2062 OC83 2N2411 OC139 2N2989 OC140 2N3053 OC170 2N3055 OC200 2N3391 | 3N128 3N154 3N159 2S303 112082 40235 40250 40251 1N23A IN25 IN38A | 6X5G 0.40 6X5G 0.55 6Y6G 0.95 624 0.65 6-30L2 0.90 7R7 0.80 7Y4 0.80 9D2 0.60 9D6 0.50 11E2 6.00 12A76 0.45 | 30PL14 1.10 35L6GT 0.80 35W4 0.56 35Z4GT 0.70 50C5 0.65 50CD6G 1.20 75 1.00 75C1 0.75 78 0.76 80 0.75 85A2 0.75 | VCR139A 8.00 38P1 7.00 5FP7 8.00 88J 9.00 88L 9.00 CV 526 8.00 SPECIAL VALVES CV2339 45.00 M503-214L |
| ECL83 0.75 GYSUI 0.80 PL802 1.85 ECL86 0.60 GZ32 0.66 PY32 0.66 A tot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable | AF118 AF124 AF125 AF125 AF126 AF127 Telephone enqu AF139 AF139 | AND TRANSISTORS unles for valves transistors, etc 4 trade and export 743 0899 | OTHERS IN STOCK inc integrated circuits, CRT & special valves Min Mail Order E1 UK POSTAGE E1-E2 20p E2-E3 30p E3-E5 40p Over E5 free Casual callers welcome | IN43 IN70 IN677 IN4148 IN4785 | 12A17, 0.45 12AU7 0.35 12AX7 0.35 12BA6 0.50 12BE6 0.55 12BH7 0.55 12C8 0.60 | 803 6.00 805 18.00 807 0.75 813 6.50 866A 1.80 931A 6.00 954 0.50 | 80.00 K301 7.00 KRN2A 6.00 725A 25.00 TY4-500 30.00 2J/192140.00 2J/52A 75.00 |





OSCILLOSCOPES 175A with 1750A dual trace vertically plug-in and 1781B delay time base plug-in, 50MHz mini-meter band switch at 50 W/CM Modes of operation Single, mixed, delaying Full spec and price on application

MARCONI TF 867 SIGNAL GENERATOR

DIVERSITY SWITCH TYPE MA168B. Solid state £45.00. REDIFON SSB TRANSMITTER/RECEIVER TYPE GR410. Full particulars and price on request

RACAL RECEIVERS MODELS. RA17 in f Prices on working and tuned condition Pr application RA98A ADAPTOR £85.00.

RACAL FREQUENCY COUNTER SA 550. Measures freq. up to 100MHz, also period and time £135.00 carriage £4.00

524B FREQUENCY COUNTER. Measures besically to 10MHz, Display on neon lamp 8 decibels P.D.A.

PHILIPS AUDIO GENERATOR TYPE GM 2308. 0-16kc/s Attenuator 0 0001. 0 0003, 0 001 to 1 with output asym & sum and matching impedance 5, 250, 600 & 1 000 ohms Price £75.00 carriage 250.

FERRANTI SWEEP GENERATOR LF Mk 2. 0-2 to 20 c p s Band sweep 1 5 10 15MHz Carrier freq 10-220MHz £55.00 carriage £5 00

BOONTON AM/FM SIGNAL GENERATOR TYPE 202E & 202H. 54-216MHz in 2 ranges **£275.00**. SIGNAL GENERATOR TS. 497/URS 2-5Mz, 13MHz, 30MHz, 78MHz, 180MHz. 400MHz. 0 1v-1 uv £150 carriage

£3.00

Open Monday to Friday 9-12.30, 1.30-5.30 p.m. BRUEL & KJOER RANDOM NOISE GENERATOR TYPE 1402. Freq resp 20-20 000 c/s time constant 0 5, 1 5, 5 15 sec. Matching imped 6 60 600 6.000 ohms and attenuator 0 40 012, 0 41 2 4 4.000 output level 1 to 10 Price E55.00 carriage £3 00

TRIGGERED VACUUM SPARK GAP TYPE ZR 7512. Capable of switching 15 000 joules at 45KV £50.00 carriage ±2 00

LOW RESISTANCE HEADPHONES TYPE CLR £2.50. 40p postage, VAT 25%

SOLOTRON CD 1220 OSCILLOSCOPE beam or 20MHz double 40MHz units up to 40MHz single beam of beam £175.00 plus £6 00 carriage

CINTEL TYPE 1873 SQUARE WAVE & PULSE GENERATOR. Freq 5c/s to 250KHz Pulse 0.5 usec 0.3 u3. Output to 50v for 1000Ω & to 5v for 100Ω & to 5v for 100Ω

RADIOMETER TYPE MS111 SIGNAL GENERA-TOR. High quality Danish production 10KHz-110MHz £200 carriage £5 00

CT480 SIGNAL GENERATOR. 7 KMC/S to 1 KMC/S mod C W . F M Pulse £160 carriage £5 00

AVO NOISE GENERATOR CT 410 E30 carriage L2 00

BRIDGE IMPEDENCE No 5. 0 1()-10M() 1pF-1...F 1...H-iH £85 carriage £4 00

EDISWAN STABILIZED POWER UNITS. To 100v 50MA Type R1280 to 300v-150MA and 300v-75mA

TEKTRONIX OSCILLOSCOPES 535, 545 & 545A. With plug in units CA (33MHz double beam) G(20MHz differential 50mV 20v) and D (high gain differential 1MV-50v) Price on application

TECHNICAL MATERIAL CORP EXCITER/ TRANSMITTER MODE SELECTOR. Freq 2-32MHz MD and 10 crystal positions Vernier tuning US8. LSB var carrier insertion etc. **£200** carrage £10.00. Luning USo. LSD ver cerrier induction of the carriage t10 00 FSK EXCITER. Freq 1-65MHz 0 100Hz continued frequency shift up to 600Hz switched freq correction Modes FAX FS MSC CVU E50.00 carriage t5:00 AMPLIFIER UNIT TYPE 1430. Dynairon Production Pulse amplifier with control Differential and Integration time constant 0.08 us to 8 us Attenuation to 200b PO A PULSE ANALIZER. Made by Dynatron with discriminator, all meter reads channel with threshold level PO A

discriminator, all me threshold level POA

RHODE & SCHWARZ. Z-g DIAGRAPH TYPE ZDU 30-420MHz. 501) Directly measures multiterminal net-works, phrase shift, phrase angle with complimentary POWER SIGNAL GENERATOR TYPE SMLM high freq resolution, netrail atternal mod up to 3v out £750. FREQUENCY SYNTHESIZER TYPE XUA. 30Hz-30MHz with FREQUENCY INDICATOR TYPE FKM 15-30MHz. 30-100MHz £1.000.

SIGNAL GENERATOR NO 16. 8cm 11cm £85 carriage 4 00

SIGNAL GENERATOR NO 13, 20MHz-80MHz AM FM, CW 1uv-1v £65 carriage £4 00

KAHN SSB ADAPTOR TYPE RSSB — 62 — 18, Designed for receivers with 455-500KHz IF at 100mV (max) input Features electronic AFC carrier treq diversity to combat fading 20 sce RC memory to maintain turing during severe fading individual carrier meters, nuvishers, 100V distortion production demodulator **£65** carriage ±5 00

BEST PRICES PAID FOR TEST AND COMMUNICATION EQUIPMENT. Single items or quantities. Private or Industrial.



TF 8018/2. Spec as for 801D but minor circuit differences. Few only left £120 carriage ±5.00

TF 8010/1/S SIGNAL GENERATOR. Range 10-805MHz in 5 ranges R F output $0.1uV\cdot1V$ Source C M Dial calibrated in voits decibels and power relative to thermal noise Piston type attenuator 500 output impedance internal modulation at KHz at power relative to tris-real modulation at modulation at modulation at modulation by to 90% depth also external sine and pulse modulation Built in SMHz crystal calibrator Separate modulation Built in SMHz crystal calibrator Separate

TF 1066 SIGNAL GENERATOR. Freq. 10-470MHz with attenuator EMF from 50Ω square -6dB Price on application

TF 1060 SIGNAL GENERATOR 450MHz to 1200MHz with attenuator. Output for 0.1 \downarrow V to 4V CW Int A.M.& Ext. Pulse £200.00 carriage £5.00

TF 1041 B VALVE MULTIMETER. General purpose measuring OC voltage from 300mV to 1 000V AC voltage from 300mV to 300V at up to 1 000MHz and resistance up to 500Mohms. Price £65 carriage ±3 00

TF 1370 R.C. OSCILLATOR FOR SQUARE & SINE WAVE. Freq. \sim 31 6V rms. 10Hz-1MHz square wave. 0.73 2pp. 10Hz-100KHz. Attenuator range. \sim 50db to + 10db. impedance 75. 100, 600t): £145 carriage \pm 5.00

EMI OSCILLOSCOPE WM8 AC/DC to 15 mc/s Time base 0 15Msec-15Msec £40 carriage £5 00

HR 23 TRIPLE DIVERSITY SSB RECEIVERS. Freq 3-275MHz VFO at 6 Xial positions Reception of independent single or double side band transceivers Full spec on application £350 carriage £35.00

TF 885A/1 VIOEO OSCILLATOR. 0 30KHz 5MHz 1Mv-31 6v £85 carriage ±4 00

TF 934 DEVIATION METER. 250MHz £55 carriage 13 00

TF 1400S DOUBLE PULSE GENERATOR WITH TM 6600 SECONDARY PULSE UNIT for testing radad nucleonics scopes, counters hitters etc. $\pounds 175$ carriage 1.5 00

500/250 MEDIUM WAVE BROADCAST TRANSMITTERS. Export only Price and details

PLEASE SEND STAMP WITH ENQUIRIES



TF 995A/1 or A/2 or A/2M or A5 SIGNAL GENERATORS. GENERATORS. Very high class AM/FM 1 5MHz to 220MHz De-tailed spec and price on applica-lion

TF 958 VALVE VOLTMETER. AC voltage 1 5-150v at up to 100MHz OC voltage 1 5-150v £25 carriage ±1 00



SOLARTRON OSCILLOSCOPE **DIGITAL VOLTMETERS** LM 14202 2.2 Sux 1000v in 6 ranges Accuracy 0.05% of range i.e ± 1 digit sensitivity 2.5 vv per digit £320. LM 1426 25mV-1000v in 6 ranges Acc range 1 in 0.029 st70. in 0 02% £170

Also available CD 1420 £170. CD 1440.2 £220.

AR88 D & LF SPARES. We hold the largest stock in

RF METERS. 0.8 amp 2%" (USA) brand new £1.50 iP&P 25p

TELEPHONE TYPE "J" tropicalised 10 LINE MAGNETO SWITCHBOAROS 50 LINE AUTOMATIC PRIVATE TELEPHONE SWITCHBOARDS

CABLE LAYING APPARATUS No. 11. New Production P.O.A

FOR EXPORT ONLY **RCA ET 4336** TRANSMITTERS Also modified version of increased output to

Also modified version of increased output to 700W COLUNS TYPE 231D 4/5KW TRANSMITTER 10 channel Autotone and manual turing C13 TRANSMITTERS 38.62 TRANSCEIVERS NO 53 TRANSMITTERS. REDIFON 100W SSB TRANSCEIVERS. MULLARD C11 HIGH POWER INSTALLATION (1.000W)

VAT FOR TEST EQUIPMENT 8% PLEASE ADD 8%

COLOMOR (ELECTRONICS) 170 Goldhawk Rd., London, W.12 Tel. 01 - 743 0899

Get a great deal from Marshall's

A Marshall (London) Ltd Dept:WW 42 Cricklewood Broadway London NW2 3ET Tet: 01-452 0161/2 Telex: 21492 & 85 West Regent St Glasgow G2 2QD Tet: 041-332 4133 & 1 Straits Parade Fishponds Bristol BS16 2LX Tet: 0272-654201/2 & 27 Rue Danton Issy Les Moulineaux Paris 92 Call in and see us 9-5:30 Mon-Fri 9-5:00 Sat Trade and export enquiries welcome Catalogue price 25p

| OUR RANGE COVERS OVER 7,000 ITEMS SELECTION IN BRITAIN TOP 200 IC'S, T CA30264 0.79 CA30264 0.79 CA3035 137 CA4037 0.87 CA3035 137 CA4037 0.87 CA3035 137 CA4037 0.87 CA3035 137 CA4037 0.87 CA3035 137 CA4041 0.78 CA4041 0.78 CA4041 0.78 CA4041 0.78 CA4041 0.78 CA4042 0.11 CA4042 0.11 CA4044 0.11 | SN7486 0.29 SN74190 1.86 SN7490 0.42 SN74191 1.86 SN7491 0.12 SN74191 1.86 SN7491 0.42 SN74191 1.86 SN7492 0.45 SN74193 1.15 SN7493 0.45 SN74193 1.55 SN7493 0.45 SN74193 1.55 SN7494 0.75 SN74193 1.55 SN7495 0.86 SN74193 1.80 SN74100 1.01 SN76033N.292 SN74170 1.86 SN74119 1.75 SN76033N.292 SN76033N.292 SN76033N.292 SN74119 1.75 SN76033N.292 SN74120 1.20 SN74120 1.20 TAA6511 2.12 SN74135 C.85 TAA66116 1.20 SN74145 1.20 TAA6511 1.23 SN74150 C.20 TA66116 1.63 SN74150 C.20 TA66116 1.63 SN74150 | POPULAR SEMICON 2N686 0.22 2N687 16 2N686 0.22 2N716 1.80 2N699 0.59 2N708 0.14 2N8376 1.280 2N708 0.17 2N916 2.8320 2N918 0.22 2N9306 0.13 2N1302 0.185 2N1302 0.185 2N1302 0.0185 2N1302 0.0185 2N1302 0.0185 2N2148 0.47 2N22158 0.47 2N22164 0.44 2N22184 0.47 2N2245 0.428 2N2245 0.428 2N22194 0.42 2N22219 0.52 2N2245 0.448 2N2246 0.55 2N2266 0.57 2N2266 0.57 2N2266 0.57 2N2266 0.57 2N2260 | AC153 0.35 BC239C 0.15 BFX30 0.34 TP35A 2.00 AC176 0.35 BC239C 0.15 BFX30 0.34 TP36A 2.00 AC188K 0.35 BC259B 0.17 BFK85 0.30 TP41A 0.79 AC188K 0.35 BC259B 0.17 BFK85 0.30 TP2355 0.88 AD141 0.68 BC307C 0.23 BFY51 0.30 TP3955 0.88 AD161 0.68 BC308C 0.22 BFY51 0.32 TP3055 0.88 AD161 0.68 BC338 0.22 MEM0402 2.03 ZTX300 0.13 AF106 0.40 BC337 0.17 MEM042 0.21 ZTX500 0.13 AF117 0.35 BCY71 0.22 ME402 1.17 ME402 0.21 TX500 0.13 AF113 0.35 BC121 0.67 M.440 0.35 IN4400 0.57 |
|---|---|--|---|
| <text><text><image/><text><text></text></text></text></text> | REVOX A-7 REVOX | ACO SERIES CO SERIES CO SERIES CO SERIES CO SERIES CO SERIES CO SERIES CO CO CO CO CO CO CO CO CO SERIES CO C | <section-header><section-header><section-header><text><text><text><text><text></text></text></text></text></text></section-header></section-header></section-header> |



Z & I AERO SERVICES LTD. Head Office: 44A WESTBOURNE GROVE, LONDON W2 5SF Tel.: 727 5641 Telex: 261306

Retail Branch: 85 Tottenham Court Road London W1. Tel: 580 8403

WW-005 FOR FURTHER DETAILS

HART ELECTRONICS

Audio Kit Specialists since 1961

J. L. Linsley-Hood **High Quality Cassette Recorder**

Full kits of parts for this outstanding design, including metalwork, cabinet, low humfield mains transformer and all other parts. Please send SAE for full data

Cassette Mechanism only complete with Erase and Record/Playback head, £19.10 + 121/2% VAT. Post 40p

FM Tuner. Several useful modifications have been made to our compact tuner. The mechanical layout with all its advantages is retained and four important electrical extras are now offered. 1. Multi-turn preset pots for easier tuning. 2. MPX filter for trouble free taping. 3. Extra thermal stabilisation for tuning line to eliminate drift. 4. Provision for remote control tuning of as many stations as you require



STEREO BAILEY 30 WATT TUNER AMP.

This complete tuner/amp unit is of the very highest quality and is the amalgam of our Compact FM Tuner. Bailey 30watt power amps and the Bailey/Burrows/Quilter pre amp. The wooden sleeve is available in either teak or sapele finish to blend with existing equipment or furnishings.

The combination of our excellently designed printed circuits and the high quality components used makes this unit unequalled on the kit market and approached in quality of performance and durability by few made up tuner amps. Full details are in our free lists.

STUART TAPE CIRCUITS. Our printed circuits and components offer the easy way to convert any suitable quality deck into a very high quality Stereo Tape unit. Input and output levels suit Bailey pre amp. Total cost varies but around £35 is all you need. We can offer tape heads as well if you want new ones. All above kits have fibreglass PCB's. Prices exclude VAT but P&P is included.

FURTHER INFORMATION ON ALL KITS FREE if you send us a 9 in. × 4 in. S.A.E

REPRINTS Post free. no. VAT

Bailey 30W 18p.

STUART TAPE RECORDER, All 3 articles under one cover 30p.

BAILEY/BURROWS/QUILTER Preamp circuits. layouts and assembly notes 15p.

All prices exclude VAT @ 12½ per cent except for reprints which are exempt

Penylan Mill, Oswestry, Salop

Personal callers are always welcome, but please note we are closed all day Saturday

104

www.americanradiohistory.com





NICKLE CADMIUM BATTERY

Type VO22 1.2V 22AH height 210mm width 55mm depth 25mm weight 1050 gms. £2.50, post 50p + 25p extra for each additional cell.

GEARED MOTORS



type SD48.15 r.p.m. 80 lb. ns. input 100/120 volt A.C. Length incl. cearbox 270mm, Height 135mm, Width 150mm, Shaft drive 16mm Weight 85 Kitos BRAND NEW Price 610.00, carr (1.00) Suitable transformer for use on 220/240 volt A.C. **£3.85**. Post 50p.

60 R.P.M. REVERSIBLE

otor Milg indle dia





two

20 r.p.m. GEARED MOTOR

General Electric. 230v A.C. 1.600 r.p.m. 0.25 amp. Complete with anti-vibration mounbing bracket and capacitor. O. A size 110mm x 95mm Spinkle 5/16" dia 20mm long. Ex-equipment tested **£3.00**. Post 50p





ROTARY VACUUM AIR COMPRESSOR AND PUMP





LITTLE NEWPORT STREET, LONDON, WC2H 7JJ. Tel.: 01-437 0576

AMPLE PARKING



Displays from major manufacturers backed by our no-quibble guarantee

DISPLAYS



Outstanding Value: Only £1.02 each for this high quality display.

| Part No FND500 TIL322 TIL321 XAN654 XAN652 MAN3M 5LT01 | Manufacturer Fairchild Texas Instr Texas Instr Xeiton Xeiton Monsanto Futaba | Colour Red Red Green Green Red Green | Type Common Cathode LEO Common Cathode LEO Common Anode LED Common Anode LED Common Anode LED Common Cathode LED 4 dig. Phos. Diode | Size 0.5'' 13mm. 13mm. 0.6'' 0.6'' 0.13'' 0.5'' | Price £1.02 £1.20 £1.30 £1.75 £1.75 £1.75 48p £5.80 | |
|---|---|--|--|--|---|--|
|---|---|--|--|--|---|--|

Note TIL322's the Texas Instrument pin-for-pin equivalent of the FN0500, may be supplied instep of FN0500's — please state if you would not want this substitution, e.g. if you want FN0500's match a previous purchase.

DISPLAY PCB's (wired for multiplexed output — each PCB fits neatly into Verocase J) For FND500 or TiL322 or TiL321 D500.6 (6 digit clock) £1.35; D500-4 (4 digit clock) 90p; D500.8 (yot 08 digits counter; etc) £1.35; For DL704 D704-6K (6 digit clock) £1.35; D704-8C (up to 8 digit, counter) £1.35.

ADD VAT at standard rate (now 8%). — 25p p&p on all orders. Price List sent with orders or on request Data available on request Export no VAT 50p (Europe), £1 (Overseas) for Air Mail p&p (no Export outside Europe for databooks and transformers).

SINTEL 53c ASTON STREET, OXFORD TEL. 0865 49791



 Motorola MCMOS Databook (Vol 5 Senes A)
 £2.77 (No VAT)

 IC SOCKET PINS: Lowest Cast Sockets for CMOS. TTL. IC's. Displays Strip of 100 pins for 50p.
 400 for £2.1000 for £4.3000 for £10.50.

 400 for £2.1000 for £4.3000 for £10.50.
 Sockets for CMOS. TTL. IC's. Displays Strip of 100 pins for 50p.

 400 for £2.1000 for £4.3000 for £10.50.
 Sockets for CMOS. TTL. IC's. Displays Strip of 100 pins for 50p.

 400 for £2.1000 for £4.3000 for £10.50.
 Sockets for CMOS. TTL. IC's. Displays Strip of 100 pins for 50p.

 Sway BOSS Switch (for programming. BCD. etc.) & ultramin toggle switches in 16 pin DIL
 E2.60

 DI704E 0 3'' Common Cathode Red LED
 Now only 75p

 ADVANCED CLOCK KIT. Complete kt including attractive sim case for 6 digit alarm clock with optional touch switch controls and crystal control/battery back-up (both exita) using MK50253 and Jumb 0 5''. LED displays kt also includes PCBs. active and passive components. IC socket: minature cool transformer switches. flat cable, loudspeaker perspex panel, and full instructions £26.80

 CRYSTAL TIMEBASE KIT. All components including PCB (47 x 59mm) to provide 50 cps for rook. IC's contex to a final resonation to his includes PCB. 3276B HJ minature in the provide 50 cps for rook. IC's contex to a final resonation and passible and market in a fill descrade and the fill includes PCB. 3276B HJ minature in the provide 50 cps for rook. IC's contex to a fill minature in a fill metable in a fill motion by includes PCB. 3276B HJ minature in a fill metable in a fill motion by includes PCB. 3276B HJ minature in a fill metable in a fill motion by includes PCB. 3276B HJ minatu

The clock will be set of the set components Easy to Build EE DIGITAL CLOCK (Jan. 76). Kit of all components including case. PCB, min transformer, etc., to build this attractive 4 digit clock with 0.511 green display £15.70.



Official Orders Welcomed. Terms 30 days, for writte phoned orders from Companies. Govt. Depts Industries, Univs., Polys, etc. Fast delivery for R&D. Nat

| | INTERPLIS | 58-60 GROVE RD. WINDSOR, BERKS, SL4 HS. ADD 8% VAT TO PRICES MARKED * ADD 12% VAT TO ALL OTHER PRICES. SEND CWO (EXCEPT GOVT. DEPTS.) POST & PACKING 20p FOR THE UK. | NEW FAST SERVICE.LOW PRICES. MONEY BACK IF NOT SATISFIED. ALL BRAND NEW TOP GRADE FULL SPEC DEVICES, CALLERS WELCOME NEW CATALOGUE LIST FREE SAZ. HARCLAYCARD & ACCESS HY POST. OR TELEPHONE ON 15 MINIMUM |
|--|---|--|---|
| FART REDWIRE | IC's LOW PRICES | TRANSISTORS | TELEPHONE 54525 |
| ALL FULL SPEC, DL707 COM, ANODE & DL707 COM, ANODE & DL707 COM, ANODE & DL707 COM, ANODE & DL707 COM, ANODE & DL704 COM, CATHODE DL704 COM, CATHODE DL704 COM, CATHODE AND SP.ea. 747 JUMBO 0.6" CA LED DISPLAY CI.75. 3015F 0-9DP (1.25. DISCO etc STROHE ZENON TUBE C5 ea. COS STYLE OR 0.2" NO CLIP 11P* TIL209 or 0.2"RED & CLIP 13P* GREEN LARGE/SMALL & CLIP 22P* ORANCE CLOCKS MM5311 C5* MM5314 C3.39* MM5311 C5* AY51224 C3.49* PCB C1* CAPACITORS CERAMIC 22pf-0.1uf 50V 5P. ELECTROLYTIC: 10/50/100 uf 10 or 25V 7P, 50V 9P, 2uf/10V 6P. 1000uf 25V 18P.200/500uf 9P. POTENTIOWETERS LIV/LOG 16P ea | $\begin{array}{cccccccccccccccccccccccccccccccccccc$ | $\begin{array}{c c c c c c c c c c c c c c c c c c c $ | DIODES OA81 & OA91 GERMANIUM 5p. IN4001 IA507 & IN4002 5p* IN4004 6p* IN4007 9p* IN4148 & IN914 SILICON 4p. ZENERS HZY88 400mW 9p. ZENERS HZY88 400mW 45p. ZENERS |
| PRESETS 6p. RESISTORS 1 P ea | | CMOS LOGIC | pen uur |
| NEW AUDIBLE WARNING BLEEPER 11 RAMPUS FULL SPEC PAKS 4LL SPEC PAK 5LL SPEC PAK 4LL SPEC PAK 5LL SPEC PAK 4LL SPEC PAK 4LL SPEC PAK 4LL SPEC PAK 4LL SPEC PAK 5LL SPEC PAK 4LL SPEC PAK 4LL SPEC PAK 5LL SPEC | The Full SPEC. 5% off 100MIX 7400 9p* 7474 27p* 7401 10p* 7476 27p* 7401 10p* 7476 27p* 7401 10p* 7476 27p* 7402/3 11p* 7490 60p* 7404 13p* 7491 60p* 7408/9/10 9p* 7496 68p* 7413 26p* 7496 68p* 7420/30 12p* 7412 26p* 7440 12p* 7412 26p* 7440 64p* 74223 58p* | NEw '90TOROLA CD14533 £2.35* CD4000 15p* CD4028 73p* CD4001 16p* CD4046 L1* CD4002 16p* CD4047 73p* CD4003 16p* CD4047 73p* CD4004 45p* CD4049 45p* CD4011 17b* CD4055 61* CD4013 45p* CD4055 61* CD4016 45p* CD4055 61* CD4017 82p* CD4071 17p* CD4018 82p* CD40510 61* CD4017 82p* CD40510 61* | DALO ETCH RESIST PEN 69p* FEC ETCH PAK 500gm 89p* 6x4" COPPER BOARD 50p PCB KIT 3 ITEMS 52* CASSETTE MECHANISM 59 & AS512 TGS GAS DETECTORS 308etcf2* |

WW-012 FOR FURTHER DETAILS

www.americanradiohistory.com

С

M

0

S

PLUSPLAYS

| 108 | | | Wireless World, June 197 |
|---|---|--|--|
| VALVES ECH35 L50 EZ30 0.00 PI.N45DD 0.01 0.01 0.01 0.01 0.01 0.01 0.01 0.01 | VALV 159 Falls Tel: 01 | E MAIL OF brook Rd, Streath -677 2424 Telex | RDER CO. am, London, SW16 6EI c: 946 708. |
| | UF41 0.75 9C/16 2.20 30C/17 10 UF80 0.50 6FSGT 1.50 30C/18 0.9 UL41 0.85 6FSGT 1.50 30C/18 0.9 UL41 0.85 6F2GT 1.55 30/F5 1.0 UL41 0.85 6/F2GT 0.55 30/F1.1 1.0 UY85 0.45 6/F3GT 0.55 30/F1.1 1.0 UY85 0.45 6/F3GT 0.55 30/F1.15 0.9 VP18 1.25 6/F3GT 0.53 30/F1.2 1.0 VP35 0.45 6/F3GT 0.53 30/F1.2 1.0 VP105/30 6/F2G 0.30 30/F1.1 0.0 30/F1.1 0.0 VP105/30 6/F2G 0.30 30/F1.1 0.0 30/F1.1 0.0 VP105/30 6/F3GT 0.55 30/70 30/F1.1 0.0 30/F1.1 0.0 T103 6/F3G 0.00 | $\begin{array}{c c c c c c c c c c c c c c c c c c c $ | $\begin{array}{cccccccccccccccccccccccccccccccccccc$ |
| TRANSISTORS & ICS 20097 AA19 0.07 BF179 0.33 0.X-42 0.40 2N7067 AA213 0.07 BF179 0.35 0.X-42 0.40 2N7067 AA213 0.107 BF179 0.35 0.X-42 0.40 2N7067 AA213 0.10 BF181 0.35 0.C44 0.20 2N1132 AC167 0.15 BF199 0.13 0.C77 0.23 2N1302 AC124 0.25 BF195 0.13 0.C76 0.30 2N1303 AC125 0.25 BF580 0.25 0.C61 0.22 2N1303 AC126 0.25 BF380 0.25 0.C61 0.22 2N1304 AC176 0.21 BF380 0.25 0.C61 0.22 2N1304 AC186 0.55 BF390 0.20 0.C77 0.30 2N1614 AD190 0.55 BF390 0.21 0.C710 0.30 2N1 | 0.15 2.84/289 0.30 SN7476 0.43 0.15 2.84/289 0.30 SN7476 0.45 0.16 3.01141 0.81 SN7480 0.66 0.12 40380 0.44 SN7482 0.87 0.12 40380 0.44 SN7482 0.87 0.12 40361 0.45 SN7482 0.87 0.24 40430 0.65 SN7494 1.00 0.24 40430 0.65 SN7494 0.16 0.22 SN7401 0.16 SN7499 0.35 0.28 SN7403 0.16 SN7493 0.70 0.28 SN7403 0.16 SN7493 0.70 0.28 SN7405 0.22 SN7496 0.86 0.20 SN7406 0.25 SN7497 0.26 0.28 SN7406 0.25 SN7497 0.26 0.20 SN7406 0.28 SN7410 1.89 0.21 SN7407 | $\begin{array}{cccccccccccccccccccccccccccccccccccc$ | $\begin{array}{c ccccccccccccccccccccccccccccccccccc$ |
| C'33 0.38 OA10 0.40 IN4403 0.68 2N3711 C'34 0.45 OA79 0.10 IN4404 0.68 2N3711 C'74 0.48 OA79 0.10 IN4404 0.68 2N3711 C'70 0.18 OA81 0.18 IN4005 0.10 2N3821 C'70 0.18 OA81 0.18 IN4005 0.12 2N3824 C'71 0.22 OA91 0.06 IN4407 0.12 2N3824 C'72 0.15 OA200 0.06 IN4407 0.06 2N3944 D121 1.00 C(1.6 1.00 IN4407 0.06 2N3944 D124 0.65 C/2.0 0.131 0.13 2.13 2N4956 D13 0.42 C(2.23 1.25 IS921 0.01 2N4465 D13 0.42 C(2.3 0.15 IN4203 0.20 2N4666 D13 0.20 C(2.5 0.15 <td>0.11 SN7453 0.16 SN74193 1.30 0.38 SN7454 0.16 SN74195 1.00 0.50 SN7460 0.16 SN74195 1.00 0.50 SN7460 0.16 SN74195 1.20 0.51 SN7470 0.36 SN74195 1.20 0.15 SN7470 0.38 SN74195 2.27 0.20 SN7473 0.41 SN71495 2.27 0.25 SN7474 0.42 SN71495 2.52 0.25 SN7474 0.42 0.59 6.15 0.10 D1L 1.4 p.10 1.5p 0.10 D1L 1.4 p.10 1.5p 0.11 D1L 1.4 p.10 1.5p 0.13 SOCKETS 1.6 p.10 1.7p</td> <td>VAT VALVES & PLASTIC TRANSISTORS 12½% INTEGRATED CIRCUITS 8% AND MATAL CAN TRANSISTORS 0%</td> <td>● OSCILLOSCOPE TUBES TYPE DG 7-5, VCR 139A, CV 1526 Price £8.00 P&P 50p add VAT 8%</td> | 0.11 SN7453 0.16 SN74193 1.30 0.38 SN7454 0.16 SN74195 1.00 0.50 SN7460 0.16 SN74195 1.00 0.50 SN7460 0.16 SN74195 1.20 0.51 SN7470 0.36 SN74195 1.20 0.15 SN7470 0.38 SN74195 2.27 0.20 SN7473 0.41 SN71495 2.27 0.25 SN7474 0.42 SN71495 2.52 0.25 SN7474 0.42 0.59 6.15 0.10 D1L 1.4 p.10 1.5p 0.10 D1L 1.4 p.10 1.5p 0.11 D1L 1.4 p.10 1.5p 0.13 SOCKETS 1.6 p.10 1.7p | VAT VALVES & PLASTIC TRANSISTORS 12½% INTEGRATED CIRCUITS 8% AND MATAL CAN TRANSISTORS 0% | ● OSCILLOSCOPE TUBES TYPE DG 7-5, VCR 139A, CV 1526 Price £8.00 P&P 50p add VAT 8% |
| Terms of Business: Mon. to Fri. Open for cal for transistors. Prices on application for any | Lia SUCKEIS 16 pin 1/p | TRANSISTURS 8% | additional valve. Express postage: 12p per order |
| STEREO IC D | ECODER | AC/DC MULTIMETER | * STAR OFFER BC 207 |
| MOTOROLA MC1310 MOTOROLA MC1310 DELIVER | P EX STOCK | TYPE U4324* With faul band suspension movement High sensitivity movement and full coverage of AC | 50 for £2.50 + 25° VAT Plastic BC 107 * STAR OFFER 2N 3055A |

| DELIV | |
|---|--|
| Separation: 40d8 50Hz-15kHz | Distortion 0.3% |
| L P level 560mV rms | O/Plevel 485mV rms per chappet |
| Input impedance: 5ok() | Power requirements 9 14V at 16mA |
| Will drive up to 75mA st | ereo ioni lamp or LED |
| KIT COMPRISES FIBREGLASS PCB (Roller tinned) Resistors I C Capacitor Preset Potm & Comprehensive InStructi LIGHT EMITTING DIODE Suitable as stereo on indicator for abov MC1310P only £2 | s ONLY WHY PAY ons £3.98 MORE? post free RED 29p gREEN 59p .15 plus p.p. 10p |
| NOTE As the supplier of the first MC1310P dec thousands, our customers can benefit from o V.A. Please add V.A. FI-COMP ELE PORTWOOD INDUSTRIAL ES? | order kit, of which we have sold literally of wide experience T. T. to all prices CTRONICS CATE, CHURCH GRESIEY |

ŧ



RETURN OF POST MAIL ORDER SERVICE







| I VNV | ELECTE | | ОМПОМ | Î TN | |
|-------------------------|-------------|-------------------------------|--------------|----------|-------------------|
| LINA | LLUIT | iunius (r | ONDON | | • |
| AC126 0.15 | BC301 0.32 | BY 206 | 0.15 | 1N4003 | 0.06 |
| AC127 0.16 | BC323 0.60 | BY207 | 0.20 | 1N4004 | 0.07 |
| AC128 0.13 | BC327 0.18 | BYX36-300 | 0.12 | 1N4005 | 0.08 |
| AC128K 0.25 | BC328 0.16 | BYX36-600 | 0.15 | 1N4006 | 0.09' |
| AC141 0.18 | BC337 0.17 | · BYX36-900 | 0.18 | 1N4007 | 0,10 |
| AC141K 0.28 | BC338 0.17 | BTX30-120 | 00.21 | 20696 | 0.14 |
| AC142 0.18 | BCY71 0.14 | DTX30-300 | 0.50 | 20697 | 0.12 |
| AC142K 0.20 | PCV72 0.12 | BYX38-000 | 0.55 | 211/00 | 0.10 |
| AC176K 0.26 | BD115 059 | 87838120 | 0.00 | 211929 | 0.14 |
| AC187 0 18 | BD131 0.36 | BZX61 Ser | 95 | 2N1131 | 0.15 |
| AC187K 0.25 | BD132 0.40 | Zeners | 0.20 | 2N1132 | 0.16 |
| AC188 0.18 | BD135 0.36 | BZX83 or B | ZX88 | 2N1304 | 0.20 |
| AC188K 0.25 | BD136 0.39 | Series | | 2N1305 | 0.20 |
| AD140 0.50 | BD137 0.40 | Zeners | 0.11 | 2N1711 | 0.18 |
| AD142 0.50 | B0138 0.48 | C106A | 0.40 | 2N2102 | 0.44 |
| AD143 0.46 | BD139 | C106B | 0.45 | 2N2369 | 0.14 |
| AD149 0.45 | BD181 0.86 | C106D | 0.50 | 2N2369A | 0.14 |
| AD161 0.35 | BD182 0.92 | C106F | 0.35 | 2N2484 | 0.16 |
| AD162 0.35 | BD183 0.97 | CRS1 05 | 0.25 | 2N2646 | 0.50 |
| AL102 0.95 | BD232 U.BL | CR51/10 | 0.25 | 2N2905 | 0.18 |
| AL103 0.93 | BD233 0.48 | CRS1 20 | 0.35 | 2N2905A | 0.22 |
| AF114 0.20 | BD237 0.55 | CRS1 40 | 0.40 | 2N2926R | 0.10 |
| AF115 0.20 | BD194 1 20 | CRS1/00 | 0.05 | 2N29260 | 0.09 |
| AF115 0.20 | 80220 0.80 | CR53.10 | 0.34 | 21129207 | 0.09 |
| AF117 0.20 | BDY38 0.60 | CB53.20 | 0.50 | 21429200 | 0.10 |
| AF110 0.30 | BDY60 0.60 | CR53.40 | 0.60 | 2N3054 | 0.15 |
| AF239 0.37 | BDY61 0.65 | CRS3-60 | 0.85 | 2N3055 | 0.50 |
| BC107 0.14 | BDY62 0.55 | MJ480 | 0.80 | 2N3440 | 0.56 |
| BC107B 0.16 | BF178 0.28 | MJ481 | 1.05 | 2N3442 | 1.20 |
| BC108 0.13 | BF179 0.30 | MJ490 | 0.90 | 2N3525 | 0.75 |
| BC109 0.14 | BF194 0.10 | • MJ491 | 1.15 | 2N3570 | 0.80 |
| BC109C 0.16 | BF195 0.10 | • • MJE340 | 0.40 | 2N3702 | 0.10 ⁻ |
| BC117 0.19* | BF196 0.12 | MJE371 | 0.60 | 2N3703 | 0.10 |
| BC125 0.18 | 8F197 U.12 | MJE520 | 0.45 | 2N3704 | 0.10 |
| BC126 0.20 | BF224J 0.11 | MJE521 | 0.55 | 2N3705 | 0.10 |
| BC141 0.28 | DF244 0.11 | 0A5 | 0.50 | 2N3706 | 0.10 |
| 90142 0.23 | 85258 0.30 | 0491 | 0.08 | 2113707 | 1.05 |
| BC143 0.23 | BE337 0.3 | 0041 | 0.15 | 2113714 | 1.05 |
| BC147 0.09 | BEW60 0.1 | 0C42 | 0.15 | 2N3716 | 1 25 |
| BC148 0.09* | BFx29 0.21 | 0C44 | 0.12 | 2N3771 | 1.60 |
| BC149 0.09 | BFX30 0.30 | OC45 | 0.10 | 2N3772 | 1.60 |
| BC152 0.25 | BFX84 0.23 | OC 70 | 0.10 | 2N3773 | 2.10 |
| BC153 0.18 | BFx85 0.2 | i 0C71 | 0.10 | 2N3819 | 0.28 |
| BC157 0.09 | BFX88 0.20 | 0C72 | 0.22 | 2N3904 | 0.16 |
| BC158 0.09 ⁻ | BFY50 0.2 | 0C84 | 0.14 | 2N3906 | 0.16 |
| BC159 0.09 | BFY51 0.11 | SC40A | 0.73 | 2N4124 | 0.14 |
| BC160 0.32 | BEY52 0.11 | SC40B | 0.81 | 2N4290 | 0.12 |
| BC161 0.38 | DET04 0.3 | SC40D | 0.98 | ZN4348 | 1.20 |
| BC188B 0.09 | 88100 0.0 | > 5040F | 0.65 | 2N4870 | 0.35 |
| BC182 0.11 | BRY30 0.20 | > 5041A | 0.65 | 2N4871 | 0.35 |
| 001021 0.10 | BSX19 0.1 | SCAID | 0.85 | 2144313 | 0.50 |
| BC1931 0 10 | 85x20 01 | SC415 | 0.60 | 2114320 | 0.50 |
| BC184 011 | BSX21 0.2 |) ST2 | 0.20 | 2N4923 | 0.64 |
| BC1841 0.11 | BSY95A 0.1 | TIP29A | 0.44 | 2N5060 | 0.20 |
| BC207B 0.12 | BT106 1.04 | TIP30A | 0.52 | 2N5061 | 0.25 |
| BC212 0.11* | BT107 1.6 | TIP31A | 0.54 | 2N5062 | 0.27 |
| BC212L 0.11 | BT108 1.6 | TIP32A | 0.64 | 2N5064 | 0.30 |
| BC213 0.12 | B1109 1.04 | TIP34 | 1.05 | 2N5496 | 0.65 |
| BC213L 0.12 | BF116 1.04 | TIP41A | 0.68 | | (|
| BC214 0.14 | 80105 1.8 | / TIP42A | 0.72 | | |
| BC214L U.14 | 02 10 | 1N2069 | 0.14 | | |
| PC237 0.16 | BU126 1.6 | 1N4001 | 0.04 | | |
| BC238 0.10 | 00120 1.0 | 1N4007 | 0.05 | | |
| 00300 0.34 | | | | | |

| DL704 DL707 | 99p 99p | DL 74 7 DL 750 | £1.75 £1.75 | 5 I | 2 RED LE GREEN C | D ONLY | | 13 15 |
|---|---|---|--|---|--|--|---|--|
| THYRIST | ORS | | | | | | | |
| | 84 | 1A | 3A | 6A | 10. | 8A | | 10/ |
| 50 | (1092) | (105) | (C 100 type) 35 | 41 | 20) | 42 | | a 7 |
| 100 | 25 | 25 | 40 | 47 | | 48 | | 54 |
| 200 | 27 | 35 | 45 | 58 | | 60 | | 68 |
| 400 | 30 | 40 | 50 | 87 | | 88 | | 98 |
| 600 | | 65 | 70 | 1.09 | | 1.19 | | 1.2 |
| TRIACS (| PLASTIC TO- | 220 PKG | E. ISOLA | | 3) | | | |
| , , | 4A | 6 5A | | 8 5A | 10 | A | 1 | 5A |
| 100V | (d) (b) 080 080 | (a) | (b) (ð) | (D) 8 078 | (a) 0.83 | (0) | (a) | (0 |
| 200V | 0.64 0.64 | 0.75 0 | 0.75 0.8 | 7 0.87 | 0.87 | 0.87 | 1.17 | 1.1 |
| 400V | 0.77 0.78 | 0.80 0 | 0.83 0.9 | 7 1.01 | 1.13 | 1.19 | 1.70 | 1. |
| 600V | 0.96 0.99 | 0.87 1 | 1.01 1.2 | 1 1.26 | 1.42 | 1.50 | 2.11 | 2. |
| 74 TTL mi | xed prices | When ordering | 1 24 25 99 | 100 - | | 1.24 | 25.00 | |
| 74 TTLL mi 1 24 7400 14p 7400 14p 7402 14p 7402 14p 7403 15p 7404 16p 7408 16p | d under column (b) xed prices 25.99 100+ 12p 10p 12p 10p 12p 10p 12y 10p 13p 11p 13p 11p 13p 11p | 7445 7445 7447 7448 7447A 7470 7470 | 1 24 25 99 85p 71p 81p 75p 75p 62p 95p 83p 30p 25p 25p 21p | 100 + 57p 65p 50p 67p 20p 17p | 7493 7495 74100 74107 74121 74122 | 1 24 45p 67p £1.08 35p 34p 47p | 25-99 40p 55p 89p 28p 28p 39p | 100 32 45 72 23 31 |
| 74 TTL mi 1 24 7400 14p 7402 14p 7402 14p 7403 15p 7404 16p 7408 16p 7409 16p | d under column (b) xed prices 25.99 100 + 12p 10p 12p 10p 12p 10p 12 y 10p 13p 11p 13p 11p 13p 11p 13p 11p | 7445 7447 7447 7448 7447A 7470 7472 7473 7473 | 1 24 25 99 85p 71p 81p 75p 95p 83p 30p 25p 21p 30p 25p 21p 30p 25p 27p | 100 + 57p 55p 50p 67p 20p 17p 20p | 7493 7495 74100 74107 74121 74122 74141 | 1 24 45p 67p £1.08 35p 34p 47p 78p | 25-99 40p 55p 28p 28p 28p 39p 63p | 100 34 45 72 23 31 |
| 74 TTLL mi 1 24 7400 14p 7400 14p 7401 14p 7402 14p 7403 15p 7408 16p 7409 16p 7409 16p 7403 15p 7408 16p 7409 16p 7409 16p 7413 29p | d under column (b) xed prices 25.99 100+ 12p 10p 12p 10p 12p 10p 12p 10p 13p 11p 13p 11p 13p 11p 13p 11p 13p 11p 13p 11p 13p 11p | 7445 7447 7447 7447 7448 7447A 7470 7472 7473 7474 7474 7475 | 1 24 25 99 85p 71p 81p 75p 95p 83p 30p 25p 30p 25p 30p 25p 30p 25p 32p 26p 47p 39p | 100 + 57p 55p 50p 67p 20p 17p 20p 21p 31p | 7493 7495 74100 74107 74121 74122 74141 74145 | 1 24 45p 67p £1.08 35p 34p 47p 78p 68p £1.62 | 25-99 40p 55p 28p 28p 39p 63p 58p 58p | 100 34 72 23 31 53 |
| 74 TTL min 1 24 149 7400 149 7401 149 7402 149 7403 159 7404 169 7409 169 7401 169 7403 159 7404 169 7409 169 7413 299 7412 270 | d under column (b) xed prices 25.99 100+ 12p 10p 12p 10p 12p 10p 13p 11p 13p 11p 13p 11p 13p 11p 24p 20p 22.25p 20p | 7445 7447 7447 7448 7447A 7470 7472 7473 7474 7475 7474 7475 7476 | 1 24 25 99 85p 71p 81p 75p 95p 83p 30p 25p 30p 25p 30p 25p 30p 25p 32p 26p 47p 39p 32p 26p | 100+ 57p 55p 50p 67p 20p 21p 31p 21p | 7493 7495 74100 74107 74121 74122 74141 74145 74154 74174 | 1 24 45p 67p 21.08 35p 47p 78p 6162 £1.62 £1.00 | 25.99 40p 55p 89p 28p 28p 39p 63p 58p £1.48 83p | 100 32 45 72 31 53 48 67 |
| dac are price dac are price 74 TTL mi 1 24 7400 14p 7401 14p 7402 14p 7403 15p 7404 16p 7408 16p 7410 16p 7410 16p 7410 27p 742 27p | d under column (b) xed prices 25.99 100+ 12p 10p 12p 10p 12p 10p 13p 11p 13p 11p 13p 11p 24p 20p 13p 11p 24 20p 13p 13p 11p 24 20p 13p 13p 11p 24 20p 13p 13p 11p 24 20p 13p | 7445 7447 7447 7448 7470 7470 7472 7473 7474 7474 7475 7476 7482 | 1 24 25 99 85p 71p 85p 71p 75p 62p 95p 83p 30p 25p 25p 21p 30p 25p 32p 25p 47p 32p 32p 26p 75p 62p | 100 + 57p 55p 50p 67p 20p 17p 21p 31p 21p 50p | 7493 7495 74100 74107 74122 74141 74122 74144 74145 74154 74174 74180 | 1 24 45p 67p £1.08 35p 47p 78p 68p £1.62 £1.00 £1.00 | 25.99 40p 55p 89p 28p 28p 39p 63p 63p 63p 63p 63p 88p 88p | 100 32 49 72 23 31 53 48 67 71 |
| Addition Addition dac are price 124 74 TTLL min 124 7400 14p 7402 14p 7403 15p 7404 16p 7409 16p 7403 16p 7403 16p 7410 16p 7413 29p 7417 27p 7420 16p 7427 27p 7430 16p | d under column (b) xed prices 25 99 100+ 12p 10p 12p 10p 12p 10p 12p 10p 13p 11p 13p 11p 13p 11p 13p 11p 24p 20p 22 ½p 20p 13p 11p 13p 11p 13p 11p 13p 11p 13p 11p 13p 11p 13p 11p 13p 11p 13p 11p | 7445 7447 7447 7448 7447 7470 7472 7473 7474 7474 7475 7476 7482 7486 | 1 24 25 99 85p 71p 85p 71p 81p 75p 75p 62p 95p 83p 30p 25p 32p 25p 25p 32p 25p 32p 25p 32p 25p 32p 25p 32p 25p 32p 26p 55p 62p 55p 62p 25p 320 260 | 100+ 57p 65p 60p 67p 20p 21p 31p 21p 80p 87p 21 | 7493 7495 74100 74107 74121 74122 74141 74154 74174 74174 74174 74174 74174 | 1 24 45p 67p £1.08 35p 47p 78p 68p £1.62 £1.00 £1.06 £3.20 £1.35 | 25.99 40p 55p 89p 28p 39p 63p 58p £1.48 88p £2.50 | 100 32 45 72 23 31 53 48 67 71 €1.9 |
| Adac are price dac are price 124 74 TTL mi 124 7400 149 7401 7402 7403 7409 7404 7409 7409 7409 7409 7409 7409 7409 7409 7413 29p 7413 7427 7432 7432 7432 | d under column (b) xed prices 25 99 100+ 12p 10p 12p 10p 12p 10p 13p 11p 13p 11p 13p 11p 13p 11p 24y 20p 22'yp 20p 13p 11p 24'y 20p 13p 11p 24'y 20p 13p 11p 22'y 18p 13p 11p 22'y 18p | 7445 7447 7447 7448 7470 7472 7472 7472 7473 7474 7475 7476 7482 7486 7489 | 1 24 25 99 85p 71p 81p 75p 62p 95p 83p 30p 25p 25p 30p 25p 21p 30p 25p 32p 26p 47p 32p 32p 26p 75p 62p 32p 26p 32p 26p 75p 62p 32p 26p 75p 62p | 100 + 57p 65p 65p 67p 20p 21p 21p 31p 21p 50p 87p 21 221 21 | 7493 7495 74100 74107 74122 74141 74125 74154 74155 74154 74181 74192 74192 74193 | 1 24 45p 67p 34p 33p 68p £1.62 £1.00 £1.06 £1.06 £1.20 £1.35 £1.35 | 25.99 40p 55p 89p 28p 28p 58p £1.48 83p £2.50 £1.14 £1.14 | 100 33 41 72 22 33 55 41 80 67 711 £1.9 90 90 |
| Tracs Tracs dac are price 142 74 TTL mi 124 7400 14p 7401 14p 7402 14p 7403 15p 7404 16p 7409 16p 7408 16p 7410 27p 7420 16p 7427 27p 7432 27p 7432 27p 7431 25p 7432 27p 7441 75p | d under column (b) 25-99 100+ 20 100+ 20 100+ 20 100+ 20 100+ 120 100+ 130 110+ 130 10+ 130 110+ 130 110+ | 7445 7447 7447 7447 7447 7470 7472 7474 7474 | 1 24 25 99 85p 71p 81p 75p 62p 95p 83p 25p 25p 21p 30p 25p 32p 25p 32p 25p 32p 25p 32p 25p 32p 26p 32p 26p 22g 2280 | 100+ 57p 55p 50p 67p 20p 17p 20p 21p 21p 21p 21p 21p 21p 21p 50p 87p 21 221 232p | 7493 7495 74100 74100 74107 74121 74122 74144 74174 74174 74174 74181 74192 74196 | 1 24 45p 67p 21.08 35p 47p 78p 68p 21.62 £1.00 £1.06 £1.25 £1.35 £1.35 £1.64 | 25.99 40p 55p 28p 28p 39p 53p 53p 53p 53p 53p 53p 53p 53p 53p 53 | 100 33 44 72 22 33 55 55 41 86 77 71 €1.9 90 90 90 |
| THAS THAS dac are price 124 dac are price 124 74 TTL mi 124 149 7400 149 7402 149 7403 159 7404 169 7409 169 7413 299 7430 169 7432 276 7432 279 7443 257 7442 656 | d under column (b) xed prices 25 99 100+ 12p 10p 12p 10p 12p 10p 12p 10p 13p 11p 13p 11p 13p 11p 13p 11p 24p 20p 22 ½ p 20p 13p 11p 24p 20p 22 ½ p 18p 62p 50p 55n 43p | 7445 7447 7447 7446 7447 7470 7472 7473 7474 7475 7475 7475 7476 7482 7482 7489 7490 7491 7492 | 1 24 25 99 85p 71p 81p 75p 62p 95p 83p 95p 83p 95p 25p 21p 30p 25p 32p 25p 32p 26p 75p 62p 95p 62p 25p 21p 95p 62p 25p 26p 65p 55p 55p 46p | 100 + 57p 65p 50p 70p 20p 21p 21p 21p 21p 21p 21p 21p 22p 45p 221 62.10 32p 45p 26 | 7493 7495 74100 74121 74121 74121 74145 74154 74154 74154 74180 74192 74193 74196 | 1 24 45p 67p £1.08 35p 34p 78p 68p £1.62 £1.00 £1.06 £3.20 £1.35 £1.64 | 25.99 40p 55p 28p 28p 28p 63p 63p 63p 63p 63p 63p 63p 61.44 £1.44 £1.14 £1.34 | 100 32 41 72 22 33 53 54 86 77 71 £1.9 90 90 |
| 74 TTLL 124 124 74 TTLL 124 149 7400 149 7402 149 7403 159 7404 169 7403 159 7413 299 7430 169 7432 279 7432 279 7432 259 7432 259 7432 259 7432 259 7432 259 7432 279 7434 259 7432 279 7432 279 7432 279 7434 259 7442 659 LINEAR LINEAR | d under column (b) xed prices 25 99 100+ 12p 10p 12p 10p 12p 10p 12p 10p 13p 11p 13p 11p 13p 11p 13p 11p 24p 20p 22 ½ 12p 13p 11p 22 ½ 18p 13p 11p 22 ½ 18p 62p 50p 55p 43p C'S | 7445 7447 7447 7448 74470 7472 7473 7474 7475 7475 7476 7482 7482 7489 7490 7491 7492 | 1 24 25 99 85p 71p 81p 75p 62p 95p 83p 95p 83p 95p 25p 21p 30p 25p 32p 25p 32p 25p 32p 25p 32p 26p (1.30 £1.09 32p 26p £2.92 £2.80 49p 40p 65p 55p 57p 46p | 100 + 57p 65p 50p 20p 20p 21p 31p 21p 32p 21p 32p 21p 33p 22p 33p 23p 23p 23p 23p 23p 23p 23 | 7493 7495 74100 74107 74122 74141 74122 74141 74154 74154 74154 74154 74192 74193 74196 | 1 24 45p 67p 81.08 35p 334p 47p 78p 68p £1.62 £1.25 £1.35 £1.35 £1.64 | 25.99 40p 55p 28p 28p 39p 63p 58p £1.48 83p £2.50 £1.14 £1.34 | 100 32 45 72 23 31 5 5 48 67 71 90 90 90 |
| 74 TTLL 124 124 74 TTL 124 149 7400 149 7400 149 7402 149 7403 159 7404 169 7409 169 7400 169 7403 159 7413 299 7432 279 7432 279 7432 279 7441 759 7442 659 LINEAR I 3014 3014 8 pm Dio | d under column (b) xeed prices 25 99 100+ 12p 10p 12p 10p 12p 10p 12p 10p 13p 11p 13p 11p 13p 11p 24p 20p 22'yp 12p 13p 11p 24'yp 20p 13p 11p 22'yp 18p 13p 11p 22'yp 18p 55p 43p C'S L 35p | When ordering 7445 7447 7447 7447 7470 7472 7474 7474 7474 | 1 24 25 99 85p 71p 81p 75p 75p 62p 95p 83p 30p 25p 21p 30p 25p 21p 30p 25p 21p 30p 25p 21p 30p 25p 21p 32p 26p 75p 62p 57p 62p 57p 46p 57p 46p | 100 + 57p 565p 50p 20p 20p 21p 31p 21p 32p 21p 32p 21p 33p 21p 33p 21p 33p 21p 33p 20p | 7493 7495 74100 74107 74122 74141 74122 74141 74154 74154 74154 74192 74193 74196 | 1 24 45p 67p 67p 33p 33p 47p 78p 68p £1.62 £1.25 £1.35 £1.35 £1.64 | 25.99 40p 55p 89p 28p 39p 63p 58p 63p 58p 61.48 88p £1.48 £1.14 £1.14 £1.34 | 100 32 45 72 22 23 31 53 48 € 67 71 €1.9 90 90 99 |
| dac are price dac are price | d under column (b) xed prices 25.99 100+ 12p 10p 12p 10p 12p 10p 12p 10p 13p 11p 13p 11p 13p 11p 24p 20p 13p 11p 24y 20p 13p 11p 22 V/p 18p 22 V/p 18p 22 V/p 18p 62p 50p 55p 43p C'S L 35p 55p | When ordering 7445 7447 7447 7447 7470 7472 7473 7474 7474 7475 7475 7476 7475 7482 7486 7482 7486 7482 7489 7491 7491 7492 7492 7492 7492 | 1 24 25 99 85p 71p 81p 75p 75p 83p 75p 83p 30p 25p 30p 25p 32p 25p 21p 32p 25p 47p 82p 32p 25p 47p 62p 52p 26p 52p 26p 52p 26p 52p 26p 52p 26p 52p 26p 52p 26p 52p 26p 52p 46p 14 pm DIL 14 pm DIL | 100 + 57p 67p 50p 67p 20p 21p 31p 21p 21p 21p 21p 21p 33p 23p 23p 23p 23p 23p 23p 23p 23p 23 | 7493 7495 74100 74107 74121 74122 74141 74174 74174 74192 74193 74196 74196 74196 74196 566 566 | 1 24 45p 67p £1.08 35p 34p 78p 68p £1.62 £1.06 £1.35 £1.64 5 14 pm 5 14 pm | 25.99 40p 55p 89p 28p 39p 63p 58p 88p £1.14 £1.14 £1.14 £1.34 | 100 32 45 72 22 23 31 53 48 67 71 \$1.9 90 99 99 |
| 74 TTLL 124 140 74 TTL 124 140 7400 14p 7401 14p 7402 14p 7403 15p 7404 16p 7403 15p 7413 25p 7430 16p 7432 27p 7432 25p 7442 65p 2132 27p 7442 65p 2133 25p 7442 65p 2130 16p 7432 27p 7442 65p 2131 301A 8 pin Di 307 309K 380 14 pin Di | d under column (b) 25 99 100+ 12p 10p 12p 10p 12p 10p 12p 10p 13p 11p 13p 11p 13p 11p 13p 11p 13p 11p 13p 11p 24p 20p 22 Vyp 18p 62p 50p 55p 43p C'S L 35p 55p 61.60 | 7445 7447 7447 7448 7447A 7472 7472 7472 7475 7475 7475 7475 7476 7482 7482 7489 7490 7491 7492 7492 7492 7492 7492 7492 | 1 24 25 99 85p 71p 81p 75p 62p 95p 83p 95p 83p 30p 25p 25p 21p 30p 25p 32p 25p 32p 25p 32p 25p 32p 25p 32p 26p 57p 62p 57p 46p 57p 46p 14 pm DiL 14 pm DiL 5 pm DiL 4 pm DiL | 100 + 57p 65p 50p 20p 20p 21p 31p 21p 32p 21p 32p 22p 23p 33p 33p 35p 28p | 7493 7495 74100 74107 74121 74121 74123 74121 74124 74174 74174 74174 74174 74192 74193 74196 566 566 566 566 | 1 24 45p 67p 51.08 34p 34p 47p 78p 68p 51.62 £1.62 £1.06 £1.25 £1.35 £1.64 | 25.99 40p 55p 28p 28p 39p £1.48 83p £2.50 £1.14 £1.14 £1.34 | 100 32 45 72 22 23 31 53 31 53 48 67 71 15 390 90 90 99 |
| Adac are price dac are price dac are price 124 7401 14p 7401 14p 7401 14p 7403 14p 7404 16p 7403 16p 7404 16p 7403 7404 16p 7403 7409 7400 16p 7410 7400 7410 7410 7427 7432 7432 7441 75 7442 301A 8 pin Di 301A 8 pin Di 309K 380 14 pin Di | d under column (b) 25 99 100+ 12p 10p 12p 10p 12p 10p 12p 10p 13p 11p 13p 11p 13p 11p 24p 20p 22 ½p 10p 13p 11p 24 20p 22 ½p 18p 13p 11p 22 ½p 18p 55p 43p 55p 43p 55p 61.60 L 90p L 61.60 | When ordering 7445 7447 7447 7447 7470 7472 7473 7474 7474 7475 7475 7475 7482 7482 7482 7482 7482 7482 7489 7490 7490 7492 73900 709 £ 7411 7492 | 1 24 25 99 85p 71p 81p 75p 75p 62p 95p 83p 30p 25p 21p 30p 25p 21p 30p 25p 25p 21p 30p 25p 25p 25p 32p 26p 47p 32p 26p 47p 32p 26p 57p 62p 57p 62p 57p 46p 14 pm DIL 14 pm DIL 14 pm DIL 4 pm DIL | 100 + 57p 565p 50p 20p 20p 21p 31p 21p 31p 21p 32p 21p 32p 21p 33p 22p 23p 23p 23p 23p 24p 33p 23p 24p 33p 24p 33p 25p 36p 36p 36p 36p 36p 36p 36p 36 | 7493 7495 74100 74100 74121 74122 74141 74122 74193 74193 74193 74196 566 566 566 566 566 566 566 | 1 24 45p 67p £1.08 35p 34p 778p 68p £1.62 £1.00 £1.35 £1.64 5 14 pm 6 8 pm 5 14 pm 7 8 pm | 25.99 40p 55p 89p 28p 28p 28p 63p 58p 83p 8250 £1.14 £1.34 £1.34 | 100 32 45 72 23 31 53 48 86 67 71 £1.9 90 99 99 |

HIGHAM MEED, CHESHAM, BUCKS, Tel. (02405) 75151

VAT - Please add 8% except items marked ' which are 121/2%

omputer Spe SALES Peripherals and Systems for Data Processing Systems, Equipment and Components

Mini~Computer Excharige

ERVICES

JUST RECEIVED - PDP8E 8K Processor

PDP11/20 24K Processor with BF11/RS11 Disk Drive and Control and Remex High Speed Reader / Punch & Control Tektronix Graphics Display & Control (for PDP11 series) PDP81 16K Processor, rack-mounted, with Teletype Control

PDP81 Tok Processor, rack-mounted, with reletype Control PC81 High Speed Reader Punch RK05 Disk Drive (no controller) DF32 Disk Drive and Control (for PDP8E series) TU60 DUAL Cassette Drive and Control (for PDP8E series) RT02 Single-line Alphanumeric Display and Control (for

PDP8E series) DEC 6ft Cabinets

OMPUTER AND

S

110

IMMEDIATE EX STOCK DELIVERY OF ASR33 TELETYPES ALSO ASR35 and KSR33 NOVA 2/10 32K Processor with Hardware Multiply / Divide, Floating Point, Real Time Clock and Paper Tape

Reader NOVA 1200 16K Processor with Real Time Clock Twin

NOVA 1200 16K Processor with Real Time Clock. Twin Cassette Unit and Matrix Printer Also available. Nova 4K Memory Module 8103, a few only 8K 8115. From **£250.** NOVA 2/10 16K Processor with Teletype Control – BRAND NEW IN ORIGINAL PACKING!

IBM PUNCHED CARD EQUIPMENT

EX STOCK DELIVERY OF IBM 024 056, 026, 077

Add 8% VAT to all prices shown, Carriage extra — details on request.



EE/

TELETYPE BRPE 110 cps Synchronous Punch 5 7 8 channel Self contained mains operated unit consisting of punch unit base motor and tape supply spool Price £145.00 Sound Helluring chanet available at £25.00

Comment with the LECLOV FACIT 4060 rack mounting heavy duty punch 5 8 channel maximum operating speed 150 cps Complete with supply and take up spools tape low out sensor and large built in chad box £555.00 Control unit also available

TALLY P.120 panel mounted pertorator. Asynchronous operation un 120 cps integral taps supply and take up spots. Price £150.00 TALLY 420 Rack-mounting pertorator. Asynchronous operation up to 60 cps linegral supply and take up spots. Complete with Model 5088 mansstorised drive package £495.00 WELMEC LOW SPEED PUNCH. Magnet cally driven up to 17 cps Ideal for data logging. Large chart box. £45.00. FACIT 4001 Rack mounting high speed reader. A very high quality uni with detertic reading and capstan drive. Read ing speed up to 500 conseculve characters. £650.00. TALLY R150A READER. 150 cps. Fast rewind. Suitable for tack mounting Complete with supply and take up spools £200.00 TALLY 424 rack mounting stawheet reader. Bidrectional operation up to 600 cps. Complete with supply and take up spools. Price £125.00 WELMEC R82 soleroid operated mechanical reader. Tox cost low speed reader for speeds up to 17 cps. Compact three standing unit (45.00 math of NAMICS Punched Card-to Paper Tape Converter Paper

Paper Tape Punches and Readers

Ind5.60 reade for speed op 30 r (p) compare the samining dim DATA_DTNAMICS_Punched Cardio Paper Tape Konverter, Paper tape hand editing units £12.50 (P&P 50p) Paper tape hand splicers £18.50 (P&P 50p) JBM 1130 SYSTEM SK Processor Paper tape reader and punch. Card read punch Automatic typewriter console IBM 1/0 WRITERS Model 73 Golfball Input Output typewriters 8CD Coded £259.500. IBM 7330 TAPE DECKS. Stroped down units (if e no electronics) consisting of complete deck with 74 reak read/write haad drive and vacuum motors and control panel. Read/write speed 36"/ sec 556 bpi low and high speed rewind bpi low and high speed rewind MDS KEY-TO-TAPE ENCODERS. 9-track encoders IBM coded Proc 6450.00.



important

from £69.50



 </r> Keyboards

panese Keyboord. BRAND NEW SURPLUSI MagneticnWy operated read relay nounted on PCB 9 while keys 4 black 2 yellow i red. Dimensions $3^\circ; \times 3$ ice $13\,50$ (P&P 30p)

A BANK HONEYWELL ALPHANUMERIC KEYBOARD - BRAND NEW

4 BANK HUNELTWILL ALTHANUMENTLY ALTONAND — DRAND NEW Mounted on printed circuit bacid (non coded) 53 cheracter keys + 10 instruction keys and 2 space bars Layout can be re-arranged as required ideal for prototypes and special applications Hall-effect switches Power requirement + 5V 420 mA Price £20.00 (P&P_L) switches Power requirement + 5V 420 mA Price £20.00 (PSP ±1) REED-SWITCH 4-BANK ALPHANUMERIC KEYBOARD mounted on printed rout brard with ASOII conde output 43 character keys + 2 shift keys and 12 instructional keys Ideal for data displays computer programming etc. (a) Ex equipment housed in metal case £30.00 + ± 1300 P&P (b) Brand new mounted on PC board only £30.00 + ±100 P&P.

1:100 P&P MINIATURE MATRIX PROGRAMME BOARDS, X-Y matrix board with 3mm grating. BRAND NEW by Ghielmetti of Switzerland. 20x30 positions (4¹/4¹, 3.4¹/1; 15:00: 12x10 (2¹x⁺ x⁺) (6:00; 3x10 (1¹x⁺¹) = 1¹¹/1; 64:00. P&P. 40p. Diode pins available to special order

In the second se

1

COMPUTER SALES & SERVICES (EQUIPMENT) LIMITED Carrs welcome Mi day n.Fr. ay 9 a.m. I 49/53 Pancras Road, London NW1 2QB. Tel. 01-278 5571

ww - 087 FOR FURTHER DETAILS

www.americagradiobistory.com

Completely redesigned with many

new features -- send for brochure



| BENTL CORPC 7A GLOUCESTER ROA ALL PRICES SH 052 054 055 058 | EY ACOUS DRATION L AD, LITTLEHAMPTON, SU HOWN INCLUDE V.A.T. AT HOWN | STIC EL36 0.90 PCC805 0.80 QS75/20 1.00 U50 0.55 2N3968 0.56 BCY12 0.55 GET887 0.26 OC810 TDD. EL36 0.50 PCC806 0.50 QS35/10 1.00 U76 0.77 22323 0.58 BCY12 0.55 GET887 0.26 OC810 OC810 TDD. EL36 1.40 PCF82 0.40 QS15/15 1.00 U153 4.41 A119 0.18 BCY33 0.25 GET886 0.28 OC810 L506 1.40 PCF82 0.40 QS15/20 1.05 U153 4.44 A129 0.18 BCY33 0.25 GET886 0.28 OC810 SSEX. Tel. 674.3 T PCF86 0.60 R11 1.00 U1912 4.40 A213 0.18 BC137 0.14 GET886 0.26 OC81 OC81 OC81 OC81 OC81 OC81 OC81 OC81 | 0.13) 0.13 0.13) 0.13) 0.13) 0.13 0.23 0.28 0.26 1.11 0.26 0.41 0.55 0.53 0.50 0.50 0.50 |
|--|---|--|--|
| 1AGG 1 0.35 6BEG 6 0.40 6LIK 1AGG 7 0.35 6BH6 0.57 6LD12 0.51 1C2 1.00 6BJ6 0.66 6BG 60.56 0.52 0.51 1G6 1.09 6BJ6 0.65 6LD22 0.55 6BH7.4 0.65 6LD22 1G6 1.09 6BK7.4 0.85 6BQ7.4 0.08 6F15 1LM5 0.70 6BK7.4 0.05 6F15 0.10 6U7.6 1LM5 0.73 6BK7.4 0.06 6F15 0.66 6HW2 0.96 6H7.7 1K5CT 0.73 6BK7.4 0.06 6HW7 0.65 6K7.7 1K5C 0.50 6BW6 1.00 6K7.6 0.55 6K7.4 1S4 0.35 6BK7.4 0.36 6BK7.4 0.36 6SA7 1S4 0.30 6BK7.6 0.36 6BK7.4 0.36 6SA7 1S4 0.30 6BK7.4 0.46 6SA7 0.4 | 0.00 125A.6 0.36 30PL12 0.45 2.00 125E6 0.35 30PL13 1.26 2.04.6 125H7 0.85 30PL14 1.26 0.04.0 125H7 0.85 30PL14 1.26 0.04.0 125H7 0.85 30PL15 0.80 17 0.70 125L7 0.46 35A.3 0.80 2 0.40 125L7 0.40 35C.5 0.85 2 0.40 125C7 0.40 35C.5 0.85 2 0.40 125C7 0.40 35C.5 0.85 2 0.40 125C7 0.40 35C.5 0.85 3 0.276T.6 0.50 35C.6 0.80 1.26 0.24 12K7.6 0.50 35K.4 0.76 9.0 0.276T.6 0.53 35Z.4 0.70 35Z.5 1.70 9.0 1.25C7 0.55 4.2 1.50 1.25C.7 0.50 <td>CV6 0.60 EC.88 0.39 EY83 0.60 PCF808 Le0 TT/TAB Li00 U33 0.53 AC156 0.23 BF163 0.23 MAT101 0.56 OC206 CV63 L00 EC92 0.55 EY84 1.20 PCF808 L00 L00 H123 1.00 U33 0.53 BF173 0.44 MAT120 0.45 OC206 CV968 0.25 ECC32 L00 EK97.6 0.40 1.00 L00 H1233 1.00 U340 0.75 AC165 0.39 BF173 0.44 MAT120 0.45 OC206 CV1C L00 ECC32 L00 EV84 0.53 DL204 0.75 AC166 0.39 BF183 0.41 OC206 CC81 0.40 0.75 AC166 0.39 BF185 0.47 OA10 0.50 OC204 D240 0.75 AC166 0.36 BAT23 0.40 0.25 OC204 D240 0.75</td> <td>0.35 0.50 1.05 0.47 0.61 7 0.50 6 0.58 0.21 0.30 0.30 0.21 0.21</td> | CV6 0.60 EC.88 0.39 EY83 0.60 PCF808 Le0 TT/TAB Li00 U33 0.53 AC156 0.23 BF163 0.23 MAT101 0.56 OC206 CV63 L00 EC92 0.55 EY84 1.20 PCF808 L00 L00 H123 1.00 U33 0.53 BF173 0.44 MAT120 0.45 OC206 CV968 0.25 ECC32 L00 EK97.6 0.40 1.00 L00 H1233 1.00 U340 0.75 AC165 0.39 BF173 0.44 MAT120 0.45 OC206 CV1C L00 ECC32 L00 EV84 0.53 DL204 0.75 AC166 0.39 BF183 0.41 OC206 CC81 0.40 0.75 AC166 0.39 BF185 0.47 OA10 0.50 OC204 D240 0.75 AC166 0.36 BAT23 0.40 0.25 OC204 D240 0.75 | 0.35 0.50 1.05 0.47 0.61 7 0.50 6 0.58 0.21 0.30 0.30 0.21 0.21 |
| 10% 0.45 682/50 0.000 053/1 105 0.625 6624 466517 2D21 0.555 66537 66537 6266 6456 65377 2D21 0.555 6756 6626 6.45 65577 2222 0.70 6629 2.00 6507 3A4 0.555 66716 0.80 614/57 0.20 6507 0.30 60763 3D6 0.40 66712 0.235 6466 0.45 6474 354 0.35 6466 6475 324 0.35 6466 0.40 6412 0.35 6466 0.56 6476 324 0.40 6412 0.40 6412 0.40 6412 0.40 6414 6417 334 0.43 641 644 6517 6456 6456 6456 6456 6456 6456 6456 6456 6456 6456 6456 6456 64575 6445 6456 6456 6456 | U-30 12517 0.00 50C-36 9.00 0.45 125.17 0.00 50C-BGI_20 0.00 0.45 125.17 0.00 50C-BGI_20 0.85 0.45 125.17 0.00 50C-BGI_20 0.85 0.45 125.17 0.00 50C-BGI_20 0.85 0.40 125.07 0.80 72 0.70 0.40 125.07 0.80 77 0.45 0.30 14147 0.75 85.42 0.75 0.35 1457 1.10 90.46 3.00 0.45 18 1.25 90.45 3.00 0.45 18 1.25 90.45 1.90 1.90 1.05 1.986 1.906 9.00 2.80 1.90 1.90 1.00 1.906 6.50 1.5082 1.955 1.00 1.955 1.90 | DF30 0.00 ECC607 0.05 FEN46 0.00 UCC85 0.50 VUI33 1.00 ACY22 0.16 0.30 0.21 0.220 0.11 DH763 0.50 ECC607 1.44 GZ30 0.55 FEN456 0.80 W76 0.50 ACY22 0.18 N126 0.21 0.220 0.12 DH77 0.36 ECF870 0.55 GZ33 0.65 FEN456 0.80 W76 0.50 ACY32 0.21 N202 0.12 0.200 0.55 DH77 0.36 ECF80 0.80 GZ34 0.75 FEN464 0.00 N211 0.77 AD149 0.42 BYY23 1.16 0.30 0.211 0.79 DH31 0.00 ECF84 .206 GZ34 .77 FPNDD/ UCH81 0.50 W717 1.30 0.50 C41 0.50 N2711 0.30 0.22 0.44 DK40 0.70 ECH81 0.50 <td></td> | |
| SR4GY 1.00 6C/W4 1.17 786 ST4 1.00 6D3 0.75 787 SU4G 0.60 6D3 0.75 787 SU4G 0.60 6D76 0.80 7D6 SY4G 0.60 6D76 0.85 7H7 S23 1.00 6E5 1.00 7K7 S24GT 0.55 6F6G 0.85 7H7 S24GT 0.55 6F6G 0.80 7V7 S24GT 0.55 6F6G 0.60 7V7 S24GT 0.55 6F6G 0.80 7Z4 6A8G 1.44 6F13 0.90 8D8 6AC7 0.55 6F14 0.90 93W6 6AG5 0.35 6F15 0.50 75 6AG7 0.00 6F18 0.80 10C2 6AH6 0.00 6F18 0.80 10C1 | 0.00 2011 0.70 *301 1.20 0.00 2011 2.50 302 1.20 0.00 2012 2.50 303 1.20 0.00 2012 0.85 303 1.20 0.00 2011 1.00 805 1.30 0.00 2019 1.00 805 1.20 0.00 2019 1.00 805 1.20 0.00 2019 1.00 805 1.20 0.00 2019 1.00 805 2.50 0.00 2014 1.00 1625 2.50 0.80 2054 51.50 1.82 1.00 0.80 2055 1.50 1.82 1.00 0.50 25.56 0.80 2057 5763 1.65 0.50 25.54 0.80 6057 1.00 0.70 25.25 0.75 606 1.00 0.70 25.25 0.75 1.05 | DW71 1.75 ECL83 0.80 H/W22 1.00 PLA4 0.30 ULA4 0.30 A/0/m 6.73 A/12.5 0.21 CD2 0.33 0.73 DW4/350 L15 ECL84 0.70 H/W22 1.00 PL304/200 URIC 1.00 A/16/m 6.73 A/12.5 0.23 CC22 0.73 A/17 A/17 <td>L CES UDE .T. HING RA O</td> | L CES UDE .T. HING RA O |
| 6AJ5 0.75 6F24 0.89 10DE7 6AJ8 0.35 6F25 1.00 10F1 6AK5 0.445 6F26 0.49 10F3 6AK6 0.70 6F28 0.49 10F3 6AK6 0.70 6F28 0.40 10F3 6AL5 0.25 6G6G 0.60 10L14 6AM64 0.50 6G6G 0.60 10L14 6AM64 0.70 6GK5 0.75 10F91 6AM54 0.40 6G32 0.70 10H3 6AL5 0.25 6G6G 0.60 10L14 6AM64 0.70 6GK5 0.75 10P11 6AQ5 6G0 6G14 0.29 10P13 6AQ5 6J6G 0.23 10P14 6AQ6 6AQ5 6J6G 0.23 10P14 6AQ6 6AG5 10P18 6AQ5 6J6G 0.23 12AP1 10P18 6AB5 10P18 6A | 0.80 28D7 2.00 7475 1.20 0.75 30A5 0.75 9002 0.55 1.17 30C1 0.40 9002 0.55 0.655 30C15 1.00 A2134 3.00 0.655 30C17 1.00 A2134 3.00 11 0.75 30F5 0.77 A22PEN L00 12 0.45 30FL1 1.10 A2134 3.00 12 0.45 30FL1 1.01 A242E 1.00 12 0.45 30FL1 1.11 A24PEN L00 1.01 1.02 2.50 30FL12 1.05 AC6/PEN 4.00 1.50 0.60 0.55 0.57 1.50 0.80 30FL2 1.05 AC6/PEN 4.00 1.50 0.50 0.50 0.50 0.57 1.50 0.50 0.50 0.50 0.50 0.50 0.50 0.77 AC/PEN (1.50 0.50 0.50 0.50 0.50 0.50 0.50 | E280F 5.00 EFS1 0.50 MHL4 1.00 py8s 0.50 25175 0.58 25175 0.58 Dit TS2 0.53 Dit TS2 0.59 Dit TS2 Dit TS2 | iv. |
| 01/5 01/5 02/5 02/5 6AS7 1.00 6/7 6.85 12ADE 6AT6 0.50 6/10 6.85 12ADE 6AU6 0.45 6/16 0.35 12ATE 6AV6 0.50 6KSG 0.50 12ATE 6AW6 0.90 6KSG 0.50 12AUE 6AX4 0.75 6L1 2.50 12AUE | 0.01 0.02 <th0.02< th=""> 0.02 0.02 <th0< td=""><td>EBC91 0.02 0.10 PC300 0.00 PC300 PC3000 PC3000 PC300</td><td>add day. e on ies.</td></th0<></th0.02<> | EBC91 0.02 0.10 PC300 0.00 PC300 PC3000 PC3000 PC300 | add day. e on ies. |

MEGGER (Record): 500 volts £20.00 £1.00 post

MEGGER (Evershed Vignoles): 250 volts £17.50 £1.00 post

PRECISION METER: 0-18.5Kv 6" scale. Electrostatic movement in fine wood mahogany box. £7.50 £1.00 post

R216 Receiver MANUAL (photostat copy): £1.50 inc. post

AIRMEC FREQUENCY METER TYPE 265: 0-6000 rpm and 0-100Kc/s £35. Carr.

RACAL I.S.B. ADAPTOR RA-95A: £65. Carr. £2.

MUIRHEAD ATTENUATORS: 75 ohms 0-8 Mc/s 3V MAK 3 ranges 0-5, 0-25. 0-50 DB £3.00 + 75p post.

CREED MODEL 54 TELEPRINTER: £37.50 each. Carr. £4.

CREED MODEL 75 TELEPRINTER: Receiver only £30.00. Carr. £3.

MULLARD VALVE VOLTMETER: E/7555/3 A.C./D.C. 2 ranges 0-5 and 0-500v. £35. Carr £2

EDDYSTONE TELEPRINTER ADAPTOR TYPE 937: £45. Carr. £1.

WAVEMETER CLASS 'D' NO. 2: 1.2 to 20Mc/s 12 volts d.c. input or 240v a.c. £12.50. Carr. £3.

WILD BARFIELD ELECTRIC FURNACE MODEL CCI.22X: With ether indicating temperature controllers Model 990. 0-1400° C. £250. Carr. £5. METROVAC IONIZATION GAUGE MODEL V.C.3: £55. Carr. £3.

AVO VALVE TESTER CT.160: (Portable) similar to Avo Mk. 3 Characteristic

meter. Good condition, £45.00. Carr. £2.00.

ANTENNA MAST: 30ft. consisting of 10 x 3ft tubular screw sections (%" dia.) with base, guyropes and stays, etc. **£7.50** each. Carr. £2.00. **REDIFON TELEPRINTER RELAY UNIT No. 12: ZA-41196 and power supply**

200-250V a.c. Polarised relay type 3SEITR. 80-0V 25mA. Two stabilised valves CV 286. Centre Zero Meter 10-0-10, Size 8in, x 8in, x 8in, New condition, £10? Carr. 75p

SOLARTRON PULSE GENERATOR TYPE G1101-2: £75.00 each. Carr. £2.00. TELEPRINTER TYPE 7B: Pageprinter 24V d.c. power supply, speed 50 bauds per min. second hand cond. (excellent order) no parts broken. £20 each. Carriage £3. AUTO TRANSFORMER: 230V 50c/s, 1000 watts. Mounted in strong steel case 5" x 6½" x 7". Bitumen impregnated. £12.00. Carr. £1.50.

CRYSTAL TEST SET TYPE 193: used for checking crystals in freq. range 3000-10,000KHz. Mains 230V 50Hz. Measures crystal current under oscillatory conditions and the equivalent resistance. C conjunction with a freq. meter. £25. Carr. £1.50 Crystal freq. can be tested in

SOLARTRON VARIABLE POWER UNIT S.R.S. 1535: 0-500 volts at 100 mA and 6.3 volts C.T. 3 amps d.c. 110/250 volts a.c. input. £18.50. Carr. £1.50.

ALL U.K. ORDERS SUBJECT TO VALUE ADDED TAX.

If wishing to call at stores, please telephone for appointment

CLASS 'D' WAVEMETER NO. I: Crystal controlled heterodyne frequency meter covering 2-8 MHz. Power supply 6V d.c. Good secondhand condition. £8.50 Carr £1.50

111

PRECISION PHASE DETECTOR TYPE 205: Freq. 0.1-15MHz in 5 ranges. Variable time delay microseconds 0-0.1c, 115V input. £55 each. Carr. £1. MURHEAD PHASEMETER D-729: A.M. £85. Carr. £3.

ALL CARRIAGE QUOTES GIVEN ARE FOR 50-MILE RADIUS OF LONDON ONLY

RACAL RA17 Front Panels: £5. £1 post.

Q METER: 30MHz-200MHz. £55. Carr. £1.

MUIRHEAD PHASEMETER TYPE D729: A.M. £95.00. Carr. £3.00. CT.420 SIGNAL GENERATOR: 200-8000c/s Variable tuning. Two fixed

requencies 9000 and 10,000. Internal calibrator 100 & 500 c/s. **£75** each carr. **£2**. **NOISE GENERATOR TF-1106:** Frequency 1 to 200 Mc/s Direct noise factor calibration. Output impedance 70 ohms **£65** each. Carr. **£1**.50.

MW-59 UNIVERSAL KLYSTRON POWER SUPPLY: £85. Carr. £3.

IF-1278/I TRAVELLING TUBE WAVE AMPLIFIEK: £125. Carr. 12.

BPL A.C. MILLIVOLTMETER TYPE VM.348-D Mk. 3: 2 millivolts-2 volts, 6 ranges. £30. Carr. £1. CAWKELL REMSCOPE TYPE 741 : Memory scope, 'as new cond. £150.00. MANSON SYNTHESISER Q115-URC: 2-30 mc/s. £175.00. FIREPROOF TELEPHONES: £25.00 each, carr. £1.50.

POWER UNIT: 110/230 volts a.c. input. 28 volts d.c. at 40 amps output. £30.00 each. carr. £3.00.

SMOOTHING UNIT (for the above): £10.00 each, carr. £2.00.

X-BAND MODULATOR CALIBRATOR TYPE MC-4420-X: Mnfr. James Scott. £125 each.Carr. £1.

BACKWARD WAVE OSCILLATOR TYPE SE-125: 6.3 heater, 105V Anode, 7.9mA. Mnfr. Watkins & Johnson. £85 each. Carr. £1. TEKTRONIX TIME MARK GENERATOR TYPE 180-SI: 5, 10, 50 MHz. £65.

Carr. 12, ROTARY INVERTERS: TYPE PE.2181. — input 24-28V d.c., 80 Anips. 4,800 rpm. Output 115V a.c. 13 Amp 400 c/s. 1Ph. P.F.9. **£20.00** each. Carr. **£2.5**0.

FREQUENCY METER BC-221: 125-20.000 Kc/s complete with original calibration charts. Checked out, working order **£20** + £1.50 carr.

SORENSEN VOLTAGE REGULATOR: Input 190/260 volts a.c. Output 220/240 volts a.c. 1000 watts. £40.00, carr. £3.00.

EVERSHED SAFETY OHM. METER: Max 10Ma. Test pressure 30v. Complete in leather case. £25.00 each. post £1.00.

AVO SIGNAL GENERATOR: 200/250 volts a.c. Frequency range 6 bands 50Hz to 80MHz. £25.00, carriage £2.00.

FYLDE AMPLIFIERS TYPE 154 BDM: Rack mounted 3v d.c. and power supply FE.500.TP. £65.00, carr. £2.00. AUTOMATIC VOLTAGE STABILIZERS: Input 207-242v a.c. Output 230v a.c.

at 2.80 amps. £17.50, carriage £1.50.

diobiston

L1. TRANSFORMERS BY PAMOUS MAKERS Open types No. 1 Pil 240. Sec. 26 v 10A and 12 v 01A. 65.60. No. 2 Pin 220:240. Sec Tapped 51.61.65.67.69. 10A. 610.00. car 11.50. No. 3 Pin 220:240. Sec Tapped 51.61.65.60. No. 210.20.20. 10.02.00.20.00. Sec. 20.146.25.00. PP 10.02.00.20.240. Sec 14v 5A. 14v 2.5A. 10.02.00.20.240. Sec 14v 5A. 14v 2.5A. 140.200.220.240. Sec 14v 5A. 14v 2.5A. 140.200.220.240. Sec 14v 5A. 14v 2.5A. 140.200.250.240.50. PP 75p. No. 6 Pin 10.02.00.250.240.50. Sec 4v 5A. 140.200.250.240.50. PP 75p. No. 6 Pin 11.02.00.255. Sec 12.4v 2.2A and 12.v 1A and 200v 35M.7A. 62.60. PP 75p. No. 8 Pin. 11.02.00.255. Sec 12.4v 2.2A and 12.v 1A and 200v 35M.7A. 62.60. PP 75p. No. 8 Pin. 10.220.240.50. Sec 31v.5A. 240.55A. 10.220.240.55. Sec 12.2v 2.2A and 12.v 1A and 200v 35M.7A. 62.60. PP 75p. No. 8 Pin. 10.220.240.00. No. 11. C Core types. Pin 200.200.20.240.00. Sec 31v.5A. 240.55A. 160 VA. Separate windings. 68.60. Carr 6.200. No. 11. C Core types. Pin 200.240.00. Sec 1.12.00.12.00.00. P. 500. No. 13. Potted types. Pin 10.220.240. Sec 13v.5A. 48.200. P. 500. No. 13. Potted types. Pin 10.220.240. Sec 10.12.00.12.00. P. 500. No. 13. Potted types. Pin 10.220.240. Sec. 10.50.14. and 30.v 1A. 13.60. carr 11. No. 14. Pin. 115.220.240.v Sec 430.00. 55A. and 430.05. San d6.3v.1A. 13.60. carr 11. No. 14. Pin. 115.220.240.v Sec 430.00. Sec. 12.5v.1A. And 30.v 1A. 13.60. carr 11. No. 14. Pin. 115.20.20.40.v P. 500. No. 13. Potted types. Pin 10.200.20.40. Sec. 50.240.v Sec. 12.9v.1A. and 30.00. Sec. 50.24.00. Sec. 12.9v.1A. and 50. 15A. 46.400. Carr 11.50. No. 17. Pin.20.20.20.00. Sec. 50.20.240.v. Sec. 12.9v.1A. and 50. 15A. 14.64.00. Carr 11.50.00. 17. 200.220.240.v. Sec. 50.20.240.v. Sec. 12.9v.1A. and 50.00. Pin. 120.220.240.v. Sec. 12.9v.1A. and 50.00. Pin. 120.220.240.v. Sec. 12.9v.1A. and 50.00. Pin. 100.220.240.v. Sec. 12.9v.1A. and 50.00. Pin.

GRESHAM L.T. TRANSFORMERS

GRESHAM L.T. TRANSFORMERS All pumarias tapped 10:0-200-220:240v open type tropicalised. Terminal block connections fraction of naker 3 price No. 2 4-7:13:13:2:33:34v 20A **EB.50.** No. 3 4-7:11:32:33:34v 20A **EB.50.** No. 3 4-7:11:32:33:34v 20A **EB.50.** No: 6:13:20:54:55:85:95 45:66:50. Carr. on all types £1. °C. core types, all primares 200:220:240V. No. 1, 4 separate secs. 1v. 3v, 9v. 27v. All at 15A, £12:00. No. 2, 3 separate sacs. 29:30:31:5A, 23:24:25v 5A, 14:15:17v 5A £12:00, carr. £2

HIGH VOLTAGE TRANSFORMERS Gresham Pri 240v Sec. 2300v 10 M/A 6.34 15A. Open type. Table top connections. **63**:50, P.P. 50p. Woden Pri 230v. Sec. 890-710-0-710-890v, 120 M/A. Open type T. connections, **63**:75, P.P. 75p. Parmeto potted type, Pri 110v 220-240v Sec. 1875v 0 M/A, 6.4v 6A 5v 3A, **55**:50, ctarr. 11

WW - 006 FOR FURTHER DETAILS

www.americanradiohistory.com

Le 2004. CU m/B 0 JV 14 E1, p.p. 40p. ISOLATION TRANSFORMERS Pri 200-220-240v Scr sec 240v 13 amps condervalively rated Open type. terminal block connections C38.00. Carr 1 £4 Pri 200-220-240v Scr sec 240v 100 watts Open type Cable tead Connections E6.80, carr c2 Pri 115 200-220-240v Scr sec connections. conservatively rated 621.50, carr c3 Pri 200-220-240v Scr tepped 90-100-110-120v 75 amps Conservatively field Should type Table top Connections E19.60, carr c3 GARDBERS HEAVY OUTY LT TRANSFORMER Pr. 240v Sec. 50v 20A Very conservati rated (AER Standard) size 9x9x7 in Terminal block connections £28, carr. £3.

LT TRANSFORMERS BY FAMOUS MAKERS. ALL PRIMARIES 2400 Sec. 6-129. 20 amps. open type table top connections. 68.50, carr. £2. 209, 20 amps E10, carr. £2. 129. 30 amps twice E17.50, carr. £2. 129. 30 amps twice E17.50,

Carr 13 GARDNERS LT TRANSFORMERS 'C' CORE Pr: 110-220-230V Sec. 5.6v CT. 28 amps. 24v 3A 6.3v 3A. 5v 2A. 250-0:250v 60 m/a. Table top connections 66.50, carr 15.0 Pri: 110-220-230V, Sec. 2.5v 10A. 2.5v 5A 2.5v 5A. £3.00, carr 11

 HOWELLS "C"

 CORE TRANSFORMERS

 Pri 200-220v, screen Sec 70-0.70v. 10

 amp table top connections. size 7x7x7 inchs.

 E15.00, carr 12.00 Pri 220-240v Sec

 18-0-18v, 12.5 amps, conservaively rated

 Table top connections. £10.00, carr 12.00
 10

AUTO TRANSFORMERS FOR AMERI-CAN EQUIPMENT A.E.I. 240v AC CONTACTORS 20AMP CONTACTS CAN EQUIPMENT 240-110-980-3000-wsits, fitted with 2-3 pm sockets, and 3 core mains lead. Send see for price list. We have England's largest selection of American electrical accessorias 2-3 pin plugs receased and surface type 2-3 sockets multi-way adaptors 2-3 pin grounding adaptors Cable type sockets Extension cords 240V-Edison screw type light builds industrial plugs and sockets. Let us know your requirements Type 0656 0659 0658 Contacts 6M 2B 3M 1B 2M 2B AC 110v Types 0651 0654 0653 3M 1B 2M 2B 4M R nHored e PP all types 250 's n HT TRANSFORMERS BY FAMOUS MAKER. ALL PRIMARIES 2400 OPEN TYPE TAG CONNECTIONS Sec 350.0-350v 120 m/a. 6 3v CT 4A. 5v 2A 6 3CT 4A. 5v-53 v 2A 63.75, p.p. 85p, 3000.-300v 100 m/a 6 3v 3 5A 5v 2A 6 3.00, p.g. 85p, 250.0-250v 120 m/a 6 3v 3/jA 5v 2A 63.00, p.g. 85p, C core type 250.0-250v 50 m/a 6 3v 1A 6 3v 0 7A 6 3v 0 8A 62.00, p.g. 75p, Shouded types, 500.0-500 200 m/a 64.50, carr £1 250v, 20 m/a 6 3v 1A 61, p.p. 400

MINIATURE RELAYS PLESSEY VARLEY 521) 4 CO **75p**, 521) 2 CO **60p**, 2801) 4 CO **60p**, 4301) 40 CO **60p**, 4301) 2 CO **50p**, 12501) 4 CO **60p**, Postage 10p ea. Open type size 1% x 1% ins. 6v OC 1 CO **35p**, P,P. 10p.

Price £1.50 £1.25 £1.25

£1.25 £1.25 £1.25

at a fr

HEAT SINKS 7%x4% ins. With two OC 28 or 2N 3055 either type £1, P.P. 25p

HIGH CAPACITY ELECTROLYTICS 1600 MF0 350v 0C, 2500 350v DC £1.25, P.P. 25p, 7100 MFD 40v DC, 4500 MFD 64v DC, 75p, P.P. 15p.

ITT LEVER SWITCHES Type 601 AAO 72-42 4CO contacts ov size 11/4x2x1/2 ins. White lever, gold f contacts. 60p. Three for £1.50, P.P. 20p. overali flash

BENSON SOLENOIDS AC 240v 25% duty. Approx. 2 ins. ½ in. pull Size 2x1 ½x1 ins. Res. 35012 75p. P.P. 25p.

COIN OPERATION TV METERS

An ideal component unit, comprising of 1½v battary motor, coin mechanism, 240v 5A micro switch, gear wheels, etc. Housed in bakelite case, 75p, P.P. 25p

COMPUTER VANS AC 230v Size 41/2x41/2x2 ins. 100 CFM Ex-equipment Perfect condition. £3.50, P.P. 50p.

AC WKG BLOCK CAPACITORS Dublicar 15mld 3300 AC Wkg 61.25, PP 25p, 10mld 3500 AC Wkg 61.00, PP 25p 5mld 300v AC Wkg, 75p, PP 25p 4mld 500v AC Wkg, 75p, PP 25p 7T C.4 mld 250v AC Wkg, 50p, PP 20p 25mld 300 AC Wkg 50p, PP 20p 0.15mld 400v AC Wkg 75p, PP 20p PP 20p 0.4mld 440v AC Wkg 75p, PP 20p 20p Bosch 1mld 800v AC £1.00, PP 20p

H.T. SMOOTHING CHOKES Parmeko ported types 10H 180 M/A. £2.00, P.P. 50p 10H 75 M/A £1.00, P.P. 35p 150H 25 M/A £1.00, P.P. 35p 14H 75 M/A £1.00, P.P. 35p 50H 120 M/A. £1.00, P.P. 35p Correct types 10H 20 M/A. £1.25, P.P. 35p 20H 80 M/A. £1.00, P.P. 35p Correct type 10H 350 M/A. £3.50, P.P. £1.00

| BOOKS | | Mullard BD232 E3.10 BRY39 50p 8Y128 95p |
|--|---|---|
| MOTOROLA | SPECIAL OFFERS | -12 1/2 % VAT BD233 68p BKY50 52p 9Y164 59p |
| Diodes Transistors, etc., over 3500 Pages £10.50 | IN4148 Diodes 12 for 50p | AC176/128 61p BD235 68p BSX19 32p BY184 41p |
| CMUS over 400 Pages £1.50 Linear Lc. over 800 Pages £2.00 | 1000 for £25.00 | AD161/162 £1.20p BD237 70p BSX20 42p BY206 19p |
| Motorola M6800 Programming Manual £3.50 | 0127" Display (MAN3M) 35p | AC126 32p BU236 50p BS195A 37p 67207 27p |
| Motorola M6800 Applications Manual £7.00 | 5% Discount orders over £5.00 | AC128 190 8F167 27p 8U126 E2.20p 8YX38-180 12p |
| From Minicomputers to Microprocessors E1.00 | Discount not applicable to kit or special offers | AC176 25p BF173 29p BU205 £2.50p BYX36-600 17p |
| SIGNETICS | | AC176/181 25p BF177 63p BU206 13.00p BYX38-600 41p |
| Data/Applications book, over 1600 Pages £4.00 | | - AC188 47p BF179 54p GET103 6p BYX49-600R 43p |
| DMOS: 74LS; Consumer; shift registers: RAM's; PROM's | I.C. SOCKETS | ACY19 43p 6F180 44p GET887 6p OA95 7p |
| 20p each | 14 oin 12n 28 oin 27n | ACY20 23p BF181 42p 0C20 E1.00p 0A200 13p |
| FERRANTI | 16 pm 15p 40 pm 30p | AD140 50p 8F183 48p OC75 6p OAZ223 69p |
| Ed ine Applications | 24 pin 26p | AD149 69p 8F184 25p OC171 5p |
| Complete range of data and applications notes available | | AF114 35p BF194 9p |
| | CAPACITORS | AF116 26p BF194B 14p MULLARD |
| NO VAT THIS SECTION | Electrolytic; paper; Non polar Tant. | AF117 250 BF195 130 DIODES 750585 |
| | Pack of 25 Mixed Our choice 50p | AF121 13p 6F196 12p DIODES 2ENERS |
| LINEAR ICs | Metal Tapt 6v :- 1: 3.3: 4.7: 56: 68: 180: | AF126 30p BF200 30p |
| LM301AV Ext. comp. operational amplifier 36p | 10v :- 150; | AF139 42p BF240 20p AA119 11p BZV10 59p |
| LM307V Int. comp. operational amplifier 45p | 15v :- 4.7 | AF178 60p BF241 27p AA215 13p B2V15CR12 75p |
| NE510A Video amplifier £1.58 | 20v := 0 1; 1; 39; 68 35v := 0 47: 0 55: 0.68: 0.82: 1.2 | BAT10 £1.00 BF263 56p AAZ17 22p BZX61C72 25p |
| 'NE540L Audio power driver £1.17 | 1-8; 2 7; 3 3; 4-7; 10; 15; 33 | BAV10 11p BF336 37p BA102 23p BZX70C11 33p |
| NE555V Timer 44p | 50v :- 3.3; 3.9; 10; 15; 22; 27; 50 | BC107 18p BF337 42p BA154 10p B2X70C30 33p |
| NE516B Phase locked loop with A.M. demode £2.70 | Plastic Tant 6v :- 47 | BC107A 15p BFR90 £3.50 BA156 11p 4.7V-75V 10p |
| NE5628 Phase locked loop with V.C.O. £2.70 | Tubular 20v : 15 | BC108 16p BFR94 £7.00 BA182 23p BZY88C6V8 12p |
| NE566V Phase locked loop function gen. £1.50 | 35v :- 2·2: 3·3: 4 7: 6 8 | BC108A 17p BFX84 41p BAX13 8p 82Y88C13 12p |
| AZ39A Dual low holse stered pre-amp. 95p | All values microfarads | BC108B 13p BFX55 40p 64477 15p 62191015 15.20 BC108C 21p 8FY50 48p 8B105B 33p BZY93C18 74p |
| A747CA Dual op. amp. 90p | Your choice 10p each | BC109B 21p BFY51 48p BB105G 29p B2193C20 74p |
| MC1303L Duel Stereo pre-amp. £1.47 | Pack of 20 mixed our choice £1.00 | BC109C 28p BFY52 36p BR100 33p BZY93C68 74p |
| MC1306P /// W audio amp. 64p MC13048 F M multiplay storeg demodulator 61.12 | Polystyrene - Pack of 25 mixed 50p | BC147 9p BF790 £1.70 BF100-1 39p B2795C15 B8p |
| MC1301P Stereo demodulator £1.92 | RESISTORS | BC148B 12p BR100-1 39p BY126 15p BZY95C24 68p |
| 'MC1312P) £1.94 | 10 for 20p Vatt Carbon. Mullard CR37 10 for 20p | BC149 7p BR101 60p BY127 13p BZY95C68 68p |
| MC1314P) Quadrophonic decoder kit £3.31 MC1315Pi £3.59 | V2 Watt Metal Film Welwyn MR5 10 for 50p | BC158 10p BC159 14p |
| MC1330P Low level video detector 67p | 12 Watt Wirewound Welwyn W23 39p | BC327 27p |
| MC1496G Double Balanced mixer | 20 Watt Wirewound Welwyn W24 41p | BC328 25p AUDIO AND RADIO MODULES |
| MOSICE | CR37 and MR5 min. quantity any one value 10 pcs. | BC 337 Z6p BC V32 24a UP1400 Stereo Decoder Module £8.02 |
| | 27K only. | BD115 31p LP1162 Audio Amp. £5.46 |
| AY-5-1224 12/24 24 nour digital clock circuit £4.25 AY-5-3510.3 ½ digit DVM circuit £6.10 | POTENTIOMETERS | 8D124 80p LP1173 10W Audio Amp. £7.54 |
| AY-1-0212 Master tone generator £5.55 | Moulded Track - Papel Mounting | BD131 50p (P1182/2 Streep pre-amp. £4.46 |
| AY-1-5051 4 stage divider £1.20 | Lin - 1w - 250k; 2M | BD132 68p LP1183/2 Stereo pre-amp. £4.92 |
| AT-1-6/21/5 5 stage divider £1.30 | Log – ½w – 10k; 500k | BD135 42p LP1184/2 Low distortion stereo pre-amp. £8.18 |
| AY-1-5050 7 stage divider £1.75 | Min. Moulded Track Linear – Panel Mitg. | BD136 44p LP1185 FM Tuner Module £7.78 |
| C550 8 digit calculator chip £6.50 | Open Min. Preset 1/4 w Linear | BD138 56p 'LP1194 / 40 Voltage Multiplier (EHT gen) £8 10 |
| C500 8 digit calculator chip £3.25 | 100R: 220R; 250R; 330R; 470R; 500R; 1k; 10k; 25k; 100k; | BD140 68p SPECIAL OFFER |
| | 500k; 500k; 1 M. Sealed Min. Person View Lingse | BD144 £1.80 (1) 10 Watt stereo amplifier comprising - |
| FERRANTI I.C.s | 33R; 100R; 220R; 330R; 500R; 4k7; 5k; 8k; 22k; 25k; 50k; | BD180 E1.00 1 x LP1182/2 and 2 x LP1173 |
| ZN1040E Universal counter/display CCT £12.00 | 100k; 500k. | BD182 £1.00 Normal price £19.08 Offer price £15.00 |
| ZN1034E Precision timer CCT £2.99 | Your Choice 10p each-panel mtg: 5p each - preset | 8D183 £1.00 (2) Five tuber comprising:- |
| Data and Circuits on ZN414 5p | Wirewound helical pots (10 turn) 100R, 5k, 50p each | BD203 £1.30 Normal price £22.08 Offer price £18.00 |
| | | |
| | Dept. WW, Wellington Road | All prices exclusive of VA I which must be added |
| | ondon Colney, St. Albans | PLP LIK 1 00 FFC C |
| COMPONENTS | Add 30p | Callers by arrangement only |

112

| | | | | APRIL 1976 | |
|---|--|--|--|---|---|
| 9 & 01-723 7 ADJAC | 10 CHAPE | (EL L ST., I | SO LECTRONI LONDON, D MET. LINI | M'S CS) LTD. N.W.1 21-262 512 STATION | 5 |
| P | LEASE ADD 8% T | O ALL ORD | TRANSFORM | MERS | |
| Type 1 2 3 4 5 6 | ALL PH Sec. Taps 24-30-40-48-60v 24-30-40-48-60v 24-30-40-48-60v 24-30-40-48-60v 24-30-40-48-60v 24-30-40-48-60v 6-8-10-12-11 CAN BE OBTAIN | Amps 12 10 8 5 3 7 2 6-18-20-24-3 ED FROM TH | Price £20.28 £19.40 £15.78 £10.24 £7.90 £5.53 36-40-48-60v IE ABOVE RANC | Carr £2 00 £1 50 £1 00 75p 75p | |
| 7 8 9 10 | 19-25-33-40-50v 19-25-33-40-50v 19-25-33-40-50v 19-25-33-40-50v 5-7-8-10-13 OR 25-0-2 OBTAINED F | 10 6 2 -15-17-20-2 5v or 20:0-2 ROM THE A | £17.75 £12.00 £6.00 £4.95 5-30-40-50v 20v CAN BE BOVE RANGE | £2.00 £1.25 75p 75p | |
| 11 12 13 | 12-15-20-25-30 12-15-20-25-30 12-15-20-25-30 3-4-5-6-8-9 or 12-0-1 OBTAINED F | 10 5 -10-12-15-1 2v or 15-0-1 ROM THE A | £10.35 £6.70 £3.75 8-20-24-30v 15 CAN BE BOVE RANGE | i1 25 i1 00 75p | |
| 14 15 16 17 18 | 12-24v 12v 60 12-24v 12v 30 12-24v 12v 20 12-24v 12v 10 12-24v 12v 10 12-24v 12v 40 | 0A.24v30A 0A.24v15A 0A.24v10A 0A.24v5A 0A.24v5A 4A.24v2A | £17.50 £14.25 £10.75 £5.50 £2.95 | £200 £150 £125 75p 60p | |
| FL | LLY SHROUDEO | TYPE TERM | INAL CONNER | TIONS | |
| 19 20 21 22 23 24 25 | 4.16-24-32v 4.16-24-32v 12-20-24v 12-20-24v 24-30-36 24-30-36 24-30-36 | 4 10 5 10 5 2 | £6.95 £4.65 £9.50 £6.50 £12.00 £9.50 £4.50 | 75p 65p £1.00 75p £1.25 £1.00 65p | |
| Fully st tapped 36-25- connec 100 m | CENTRE TAPPE prouded terminal blog 1 30-25-0-25-30 0-25-36v 5 amps £ tions Pri 117-220-2 /a 6v 1A £3.75, p.p. | DL.T. TRA ck connection v 2 amps 11.95, p.p. 40v. Sec 28- p. 85p. | NSFORMERS 18. Pri 220-240v 5. £5.95, p.p £1. Open frame 0-28v 3 amps. 3 | Scr. sec 75p. type tag 10-0-30v | |
| 3000 v Open tr case w 240v n | WODEN AU vatts tapped 105-11 ype terminal bock co th twin American 2 nains lead, carrying t | TO TRANSF 5-125-135-2 onnections E /3 pin flush handle. E32. | CORMERS 200-215-230-24 19.50, carr. £2. mounted socket 50, carr. £3. | 15-260v. In metal s. 3 core | |

| TTI & by TEVAS | 74195 750 | | | | TRANSIS | TORS | |
|--|---|---|---|---|--|--|--|
| TILS BY TEXAS 7400 13p 7482 70p 74H00 20p 7483 80p 7401 14p 7484 95p 7402 14p 7485 120p 7403 16p 7486 30p 7404 16p 7489 270p 74H04 22p 7490 40p 7405 16p 7491 75p 7406 38p 7493 40p 7407 36p 7493 40p 7408 16p 7493 40p | 74195100p 74197100p 74197100p 74198198p C-MOSI.Cs CD4000AE16p CD4001AE16p CD4002AE16p CD4002AE16p CD4003AE67p CD4011AE16p CD4011AE16p | UP. AMP'S 1458 - Dual Op. Amp. Int. Comp. 3014 Ext. Comp. 3130 COSMOS/Bi-Polar MosFet. 3900 Quad. Op. Amp. 536T FET Op. Amp. 709 Ext. Comp. 741 Int. Comp. 747 Dual 741 748 Ext. Comp. 776 Programmable Op. Amp. | B pin DIL 70p 8 pin OIL 36p 9 pin DIL 100p 14 pin DIL 70p 70-99 275p 8/14 pin DIL 30p 8/14 pin DIL 22p 14 pin DIL 70p 70-93 215 8/14 pin DIL 70p 8/14 pin DIL 70p 8/14 pin DIL 70p 70-5 140p | AC125 16p AC127 12p AC127 12p AC127 12p AC141 18p AC142 18p AC142 18p AC142 18p AC16 11p AC188 12p AC188 23p AC143 36p AC143 36p AC143 18p AC143 18p AC145 18p AC145 18p | ВFY52 16р ВRY39 34р BSX20 20р #GU105 140р BU108 250р #ML2340 45р ML2355 75р ML2355 65р #MP56534 18р #MP56534 18р #MP565 32р | 2N3442 140p 2N34702 11p 2N3702 11p 2N3703 11p 2N3705 11p 2N3705 11p 2N3705 11p 2N3706 10p 2N3706 9p 2N3709 9p 2N3703 220p 2N3765 90p 2N373 220p 2N3765 90p 2N3765 18p | Dioddes Signal • OA7 9p OA81 8p OA85 10p OA90 7p OA91 7p OA95 7p OA95 7p OA200 8p OA202 10p IN916 9p |
| 7409 20p 7495 65p 7410 13p 7496 78p 7410 13p 7496 78p 7411 22p 74100 108p 7411 22p 74107 30p 7413 32p 74116 40p 7414 60p 74118 84p 7416 33p 74122 46p 7420 14p 74122 46p 7421 40p 74122 70p 7422 18p 74132 70p 7423 34p 74136 70p 7423 30p 74136 65p 7423 30p 741416 65p 7425 30p 741416 65p | CD4013AE 55p CD4017AE 120p CD4017AE 120p CD4017AE 120p CD4020AE 250p CD4022AE 170p CD4022AE 190p CD4022AE 190p CD4022AE 196p CD4022AE 196p CD4022AE 196p CD4022AE 196p CD4022AE 175p CD4028AE 175p CD4023AE 55p | LINEAR I.C.S *CA3028A Diff Cascade Amp (CA3046 5 Transistor Array *CA3053 Diff Cascade Amp *CA3053 Diff Cascade Amp *CA3089E FM IF System *CA3090AQ FM Stereo Multi Dec ICL8038BC VCO Fun Gen ICL8038BC VCO Fun Gen *CA3090AQ FM Stereo Multi Dec ICL8038BC VCO Fun Gen *M380 Stereo Preamp *M381 Stereo Preamp *M252 Rhythm Generator *MC130F FM Stereo Dec MC1495 Bait Multipier *MC1495 Bait Multipier *MC1495 Bait Multipier | TOS 90p 14 pin DiL 50p 16 pin DiL 200p TOS 45p 16 pin DiL 200p 16 pin DiL 200p 16 pin DiL 200p 14 pin DiL 90p 14 pin DiL 275p 14 pin DiL 200p 16 pin DiL 300p 14 pin DiL 150p 16 pin DiL 300p 14 pin DiL 75p 16 pin DiL 300p 14 pin DiL 100p 16 pin DiL 300p 14 pin DiL 70p 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 | Ar1116 18p Ar111 18p Ar113 33p Ar139 33p BC107 9p BC108 9p BC109 10p BC109 10p BC1017 22p #BC147 7p #BC1487 7p #BC1457 11p #BC155 11p #BC155 11p #BC155 11p #BC1657 13p #BC1777 18p | *MPSU06 62p *MPSU05 78p OC28 65p OC35 55p OC35 55p *OC71 20p *TIP29A 40p *TIP30C 60p TIP31C 70p TIP31C 70p TIP31C 70p TIP32A 58p TIP32A 58p TIP32A 90p TIP33A 90p TIP33A 115p | *2N3906 16p *2N4058 15p *2N4059 10p *2N4050 13p *2N4123 18p *2N4124 18p *2N4124 18p *2N4125 18p *2N4299 20p 2N4347 130p 2N4348 160p *2N43401 27p *2N4401 27p *2N401 50p 40360 40p 40360 40p | IN4148 4p RECTIFIER %9Y100 25p %9Y120 12p 12p e6Y125 12p 14002 1N4002 5p 1N4004 6p 1N4005 6p 1N4007 7p 2FV10 33V+ *20mW 9p *1W 18p *1W 18p |
| 7428 36p 74148 160p 7428 36p 74148 160p 7430 14p 74150 125p 7432 25p 74151 72p 7437 25p 74151 72p 7440 14p 74153 85p 7440 14p 74154 150p 7441 65p 74155 76p 7442 60p 74156 76p 7443 140p 74160 99p | CD4042AE 137p CD4043AE 202p CD4043AE 140p CD4047AE 154p CD4047AE 154p CD4054AE 196p CD4055AE 196p CD4055AE 135p CD4056AE 135p | ME555 Timer NE555 Timer NE555 Dual 555 NE561 PLL with AM Demod NE565 PLL NE565 PLL NE565 PLL NE566 PLL NE567 PLL Fun Gen NE567 PLL Fune Dec 2567 Dual 567 SN72710 Dual 567 SN72710 Dual 467 SN72733 Video Amp | 8 pin DiL 40p 14 pin DiL 100p 16 pin DiL 325p 16 pin DiL 325p 14 pin DiL 200p 8 pin DiL 150p 8 pin DiL 150p 16 pin DiL 370p 14 pin DiL 50p 14 pin DiL 120c | BC178 17p BC179 18p #BC182 10p #BC183 10p #BC184 11p BC187 30p #BC213 10p #BC214 14p BC213 10p #BC214 30p #BC214 30p BC478 30p BCY70 18p | TIP34C 160p TIP35A 225p TIP35C 290p TIP36A 270p TIP36A 270p TIP36C 340p TIP41A 65p TIP41A 75p TIP42C 75p TIP42C 82p TIP2955 70p aZTX108 10p | 40362 40p 40364 120p 40409 55p 40410 55p 40411 225p 40594 75p 40595 85p | TUNNEL AEY11 70p VARICAP +8B105 25p NOISE #25J 110p |
| 7444 1400 74161 99p 7445 90p 74162 99p 7446 90p 74163 99p 7447 75p 74164 120p 7448 70p 74164 120p 7450 15p 74174 120p 7451 16p 74174 120p 7451 16p 74176 120p 7453 16p 74176 120p 7454 16p 74176 120p 7450 15p 74180 100p 7450 15p 74180 120p 7450 15p 74180 120p | CD406348 37p CD4071AE 27p CD4071AE 27p CD4072AE 27p CD4082AE 27p CD4510AE 130p CD4511AE 200p CD4518AE 100p CD4528AE 120p TEXAS 75 | SN/5013N Pvr Aud Amp with nit PSN/5023N Pvr Aud Amp with nit PSN/5023N Pvr Aud Amp with nit PTBA561B Audio Amp TBA800 SW Audio Amp TBA810 TW Audio Amp TBA810 TW Audio Amp TBA820 2W Audio Amp TDA2020 20W Audio Amp XR2240 Prog Timer/Counter ZN114 TFF Radio Receiver Basic data sheets on above at 10p cach - | 140p 140p 13 140p 14 120p 11 120p 11 250p 11 90p 11 80p 11 80p 11 80p 11 80p 16 pin Dill 370p 10.18 110p | BCY71 22p BD124 65p BD131 36p BD132 40p #BD135 43p #BD139 63p #BD139 63p #BD140 70p BF115 22p BF176 23p BF177 23p BF177 25p BF177 25p | *27X300 13p *27X502 13p *27X502 18p 2N597 13p 2N598 30p 2N706 16p 2N706 16p 2N708 18p 2N918 40p 2N918 40p 2N918 40p 2N918 18p 2N1131 18p 2N1132 18p 2N1132 18p 2N132 32p | FETs +BF244 25p +MPF102 30p +MPF103 30p +MPF104 30p +MPF105 30p 2N3819 22p 2N3820 57p 2N3823 50p -2N5457 30p +2N5458 30p +2N5459 30p | BRIDGE RECTIFIERS -25A100V 20p +1A 50V 20p +1A 100V 22p +1A 400V 25p +1A 400V 25p +2A 50V 30p +2A 50V 30p |
| 7472 25p 74182 82p 7473 30p 74185 135p 7474 30p 74190 144p 7475 45p 74191 144p 7476 30p 74192 120p 7480 50p 74193 120p 7481 95p 74194 108p | SÉRIÉS 75107 160p 75450 120p 75451 72p 75452 72p 75453 72p 75454 72p | OPTO-ELECTROI Phototransistors OCP70 30p OCP71 120p 2N5777 40p LEDS 0 2' TIL209 Red 14p Red TIL211 Green 30p Green | NICS L.D.Rs. ORP12 50p ORP60 75p ORP61 75p 7 16p en 28p | BF178 28p BF179 33p BF180 33p #BF184 22p #BF194 10p #BF195 9p *BF196 14p #BF197 15p BF200 32p BF257 32p BF258 36p | 2N1305 32p 2N1306 36p 2N1307 36p 2N1308 36p 2N1309 36p 2N1613 20p 2N1613 20p 2N1711 20p 2N2219 20p 2N2222 20p 2N2222 20p 2N22269 14p | MOSFETs 85p 3N128 85p 3N140 85p 3N141 85p 3N187 180p 3N202 120p 40603 58p 40673 58p | • 2A 200V 40p • 2A 400V 45p • 4A 100V 60p 6A 50V 65p 6A 100V 72p 6A 200V 78p 6A 400V 84p TRIACS Amp Volts |
| 2602B 1024 bit RAM 2513(UC) Character Generator 2513(LC) Character Generator | £2.50 £8.50 £8.50 | TIL32 Infrared 75p Yelle SEVEN SEGMENT D | NISPLAYS | *BFR39 30p *BFR40 30p *BFR79 30p *BFR80 30p | 2N2484 30p 2N2904 20p 2N2905 20p 2N2906 20p | UJTs #TIS43 27p | 3 400 120p 6 400 150p 6 500 180p 10 400 185p |
| MULLARD MODULE *LP1186 Varicap FM Tuner | £6.75 | DL704 Com. Cathode 0.3 in DL707 Com. Anode 0.3 in DL707 Com. Anode 0.3 in DL747 Com. Anode 0.6 in. | 140p 140p 140p 225p | ВГХ85 25р ВГХ85 25р ВГХ85 25р | *2N2926E 7p *2N2926E 7p *2N29260 8p *2N29260 8p | 2N2160 80p 2N2646 38p. *2N4871 30p | 10 500 195p 15 400 210p 15 500 250p 40430 99p |
| LOW PROFILE DIL SOCKETS 8 pin 13p. 14 pin 14p. 16 p 40 pin 75p. INSULATORS Mica+2 Bushes | BY TEXAS in 15p, 24 pin 50p. for TO3 & TO66 5p. | OPTO-ISOLATORS Phototransistor TiL 112 (IL 12) Photodarlington. ILCA-55 DRIVERS | 6 pin DIL 140p 6 pin DIL 250p | BFX87 20p BFX88 20p BFX88 24p BFY50 16p BFY51 15p | 2N3053 18p 2N3054 45p 2N3055 50p 2N3439 67p | PUJT *2N6027 48p | 40669 95p DIAC BR100 25p |
| VOLTAGE REGULATORS | | 75491 Quad Segment Driver 75492 Hex Digit Driver | 14 pin DIL 72p 14 pin DE 90p | 3EN 1) T | eletext Decoder | KIIS | |
| 1 Amp Positive 1 A 5V 7805 140p 5 12V 7812 140p 12 | mp Negative ∨ 7905 200p √ 7912 200p | SCR-THYRISTORS | 6 700V Stud 140p 50 (400V Plastic 550 | | U.C. £47.00 inc L.C. £11.00 inc. | VAT and P VAT and P 8 | & P & P |
| 15v 7815 140p 15 18v 7818 140p 18 24v 7824 140p 24 LM309K 1 Amp 5v 103 DUAL VOLTAGE REGULATO 1468 -15v 100mA 16 (Adjustable by resistors from - max i | V 7915 200p V 7918 200p V 7924 200p 140p DR pin DIL 300p. . 8V min. to ± 20V | IA SUV 105 42p *MCI 1A100V 105 42p *MCI 1A400V 105 45p 0.5 1A600V 105 70p 2N3 3A100V Stud 49p 5A/ 3A400V Stud 45p 2.84 7A100V 105+HS 84p 8A/ 7A400V 105+HS 80p *20p 8A 50V Plastic 130p 0.8 | Aloc To-sale Sop A/15v To-sale 25p 525 | 2) T Plea | Time-Code Receiv £26 inc, VAT an (extra £6 include se send S.A.E. fo | ver Clock d P & P s 45 DIL soci on details. | kets |
| VARIABLE VOLTAGE REGU 723 2V to 37V 150mA LM305H 45V to 30V | LATOR 14 pin DIL 45p 20mA TO5 120p | 1 12A400V Plastic 160p ★2N5 16A100V Plastic 160p 0.8/ 16A400V Plastic 180p ★2N5 16A600V Plastic 220p 0.8/ | 5062 A/100V TO-92 37p 5064 A/200V TO-92 40p | VAT RATES: which are at | All items at 8%. 25%. | EXCEPT wh | ere marked * |
| Fully branded devices by Motorola: National, Mull | Texas, RCA | Minimum Order £2 Mail &P 20p Govt | Order Only ., Colleges, etc., o | rders accepted | TECHI 54 SANDHU | NOMAT | IC LTD. |
| | | lease add VAT to total | | | Tel: 01-204 / | 4333 | 14. <u>3. 488</u> - 14. 810 |
| EQUIPMEI | NT designed | l by J. L. | FLECT | RONORG | TECHNICA | Ą | |
| LI AUDIO OSCILLAT Simple design. Very Lov tortion. In kit form £14.00 or READY M £14 | NOLET-MUU OR v Dis- ADE 3.00 | | Car | 'bon | film | RESIS | TORS |
| | FA | MOUS 75 watt | / /o an | 14 VV / | | COL L. I | 2 |

www.americanradiohistory.com

1 8 8 8 8 8

HI FI AMPLIFIER Distortion below normal measurement Price (Kit) **£64** Phase Locked Loop F.M. Stereo Tuner, Full kit Also in component and module form £40 or in pack form See. (Add Tax 12½% (except instruments - 8%)

0 . ALSO AVAILABLE F.M. Sig / Gen-Wobbulator £12. T.H.D. Analyser £18.50.0-60v 1A P.S.U. £17.30 Detailed leaflets gladly sent. Send foolscap S.A.E

TELERADIO ELECTRONICS 325 FORE STREET, EDMONTON, LONDON, N.9. 01-807 3719



113

ELECTRONIC BROKERS

Electronic Brokers Ltd. are one of the leading electronic instrumentation companies in the UK, providing a full range of services to Universities, Industry, Colleges and Governments both at home and overseas.

We have the largest stocks of secondhand test equipment in Europe as well

TELEPHONE **TEST EQUIPMENT**

 IEMENS
 E250

 evel Meter 3D 332 0 3-1200 KHz
 E250

 evel Meter 3D 335 10 KHz-17 MHz
 E300

 evel Oscilator 3W29 0 3-1200 KHz
 E250

 evel Oscilator 3W29 0 3-1200 KHz
 E250

 arrier Frequency Sweep measuring set up Type Rel
 Type Rel

 32 M710 (to 15 MHz) Comprising Level Oscillator
 Feel 3W 518

 Rel 3W 518 Level Meter Rel 3D 35 Sweep
 Arrachment Rel 3W 933 Tracing Receiver Rel 3D

 Ad6 Lised for measurement on carrier telephone
 euidenand radio relay systems (eg V960 V1200 & V2700)

 V2700) and widehand radio relay systems (eg V960 V1200 & V200 & V2700)
 P.O.A.

 MANDEL & GOLTEMAN
 Control 10 KHz-13 MHz
 E375
 £375 £375

10KHz

Level Transmitter TFPS 42 10KHz-14MHz Level Meter TFPM 43 10KHz-14MHz Wandel & Golterman VZM 2 Distortion measu for phase and amplitude mod For multichan Radio Systems up to 12MHz base bands €350

SWEEP GENERATORS

HEWLETT PACKARD Sweep Oscillator 692D 2-4GHz Sweeps from start to stop freq SPECIAL OFFER £300 Sweep Oscillator 693B 4-8GHz SPECIAL OFFER £325

Sweep Oscillator 693D 4-8GHz JERROLD

JERROLD Sweep Signal Generator 900B Central Fr 500KHz-1200MHz Sweep widths narrow as 10KH 400MHz wide 50ohms o pimpediance E £400



as a selected range of new products. These are on display at our London showrooms where customers can examine the equipment of their choice and see it working.



Electronic Brokers Ltd have fully equipped workshops on the premises to test and report on the majority of equipment we sell.

GENERAL RADIO Unit Oscillator 1209C Freq 250-920MHz Accuracy 11 Drift 0.2% O printo 50ohms=150mW supplied with Power Supply Type 1201 - C018 as 6215.00 Unit Oscillator 1218A 900 2000 MHz Power output £140.00

of 200mW across band HEWLETT PACKARD

 HEWLETT PACKARD
 C. W. &

 F.M. A.M. Signal Generator 202H F.M. A.M. C.W. &
 Julie coverage 54 to 216 MH; R.F. o. p. 0.1;V-0.2V
 Sobms Impedance

 V.M.F. Signal Generator 608E 10.480MH; 16 bandis
 Accuracy. = 0.5% o. p. 0.1;V-1V
 Vanable 50ohms

 Int. A.M. 400 & 1000H; Ext. A.M. 20H; 20H; 20H;
 Superb condition
 Superb condition
 SHE Signal Generator 618C 2.8-7.6GHz

£550.00 50ohms U H F Signal Generator 616A 1 8-4 2GHz £475.00

MARCONI INSTS. FM AM Signal Generator TF 995A 3S Ministry type No CT402 15MHz-220MHz R F o p 2/V-200mV Internal & External Mod Facilities V £885
 good condition
 £385

 F M A M Signal Generator TF 995A 51 5-220 MHz
 im 5 bands 0 1µV-200mV F M up to ±120KHz tord

 50Hz-15KHz A.M up to 50% from 100Hz 10KHz
 op (11 2µV-200mV (2) with terminating unit

 1µV 100mV Int mod freqs 400Hz 1KHz & 15KHz
 050% for (2) on internal

 0stortion (1) on internal F M. ±25Hz (2) on internal
 A.M 6% at 30% mod
 A.M. 6% at 30% mod £300 to £450.00 A.M. Signal Generator TF801D 1 Freq range 10-470MHz R.F. output 0 1j-1V Piston attenuator 500hms Impedance Modulation Int A.M. 1KHz Ext A.M. 30 H-20KHz Low spurious F.M. & drift VS.W.R.1.2 or less £400-£800 A.M. Signal Generator TF801D 1S Military Version 10-485MHz £450-£800 10-185MHz £450-£800 RC Oscillator TF1370A 10Hz-10MHz Square Wave un to 100KHz High Outputs up to 31 6V £285 Phase A M Signal Generator TF 2003 04-12MHz £150 A M. Signal Generator I: ovice Jack Telephone (1) ovice Jack Telephone (2) ovice Jack Telephone A.M. Signal Generator TF 801B 3S 12 485MHz 0 10V 1V £195.00
 dance
 E225.00

 FM AM signal Generator 1F937 1
 C1320

 SSKH / 8 SMHZ Asseen condutton
 E80.00

 Portable Receiver Tester TF888 3
 Freq

 70KH-70MHY Xtaicheck 500KHz & SMH/ Output
 Phase A M Signal Generator 1F2003

 Q 41/2MHz
 E150.00

 V H F Mobile Radio Test Set IF10648 5M
 E30000

 Signal Generator IF14H 4
 Late models in superbinding conductor

al Generator TF144H 4 Late models in supero driven £500 to £5500 FM Generator TF995B 5 (Brand new -£750
 NOIMERAD
 LF
 Decarte
 Oscillator
 D880A
 2
 phase

 0.01H,11.2KHz
 £295.00

 Decade
 Oscillator
 D890A
 1Hz-11.2KHz
 £335.00

 RADIOMETER

herator SMG1C Full spec on request £400

Amemberof theEBgroup



AM FM Generator Type MS27G WAYNE KERR £315

ator 0.222 7KHz-8MH £75.00 £150.00 Oscillator 0 22D 10 KHz-10MHz

OSCILLOSCOPES

HEWLETT PACKARD Oscilloscope 140A c w 1415A time domain reflectometer For testing of cables connectors striplines & transmission lines f 750 Sampling Scope 185B DC.3 5 GHz € 395 00 Oscilloscope 175A DC 50MHz Main Frame € 150.00 Plug Ins available from £25-655.00 50MHz single channel 1751A Time Mark Gen 1783 Aus Plug In 1781A Ousplay Scanner 172A Sweep Delay Gen 1781B. Qual Trace Vert Amp 1750A Delay Gen 1781A

HAMEG

Transistorised compact single beam portable scope bandwidth of 8MHz Compensated Y — attenuator 12 ranges 50mV/cm to 30V/cm Timebase sweep range of 10Hz to 500kHz and can be triggered from + Ve or -Ve externally or internally Y input can be AC or DC coupled Display area 6cm X 4cm Rise time 44ns Oimensions 203mm X 160mm X 240mm. Vit 5Kg BRAND NEW Type No HM207 **E85.00**

 Brand New Type no HM207
 LB5.00

 MARCON1
 LB5.00

 TV Scope TF 2200A 1 c w TV Diff plug in TM 6457A DC 30MHz
 L190

 Ponsable Scope TF2203
 15MHz

 Bandwidth DC coupled 50mV cm sensitivity
 E125.00

 SOLARTRON
 DC CMUL Dc ha Dury CC

SUCARTRON Portable Scope DC-6MHz Double Beam GT436 E95 CD 1014 3 DC SMHz Portable Scope D1 400 DC 15MHz Plug ins available CX 1441 1413 Wide Beach CC

CX 1441 14:13 LIGO DC LEMHZ Plug ins available CX 1441 14:13 LIGO DC LEMHZ Plug ins available E180 Wide Band General Purpose Scope CD:1212 (Min spec CT484) Plug ins CX1251 & CX1252 (collection only) E149,50 Portable transistorised CD 1642 Dual trace DC --15MHz 10mV/cm Sensitivity triggering to 25MHz Screen 10 × 6cm E195 HEATHKIT 012 µ Score Scott 2

IO 25MHz E19: 10.12 µ Scope Single Beam 50MV/cm AC coupled 8/W 4.5MHz 5'' Tube Assembled Refurbished 90 Day Warranty Our price ROBAND 25MHz

hed 90 £49.50 ROBAND 25MHz Scope R 050 c/w 5C Plug in 25MHz Scope R 05DA c/w 5C Plug in TEKTRONIX £200 £225

£450 £650

€75

TEKTRONIX Sampling Scope 661 c/w plug ins 453 DC-50MHz Solid state & portable TELEQUIPMENT D31R Dual Beam DC -- 6MHz



Segmented Multiple Cold Cathode Gashiled Indicator Tube Type ZM1500/12 made by Mullard — unused 12 Decades Character height 7 6mm Striking voltage 160. Ideal for Display Applications requiring a large No of digits to be displayed. e.g. Desk Top Catculators Overall width 86.2mm Overall height 26mm 6.3.75+P&P 30p+VAT 8%



SELF SCAN

AN play Model SSD 1000-0030 Direct Visual Panel Display Model SSD 1000-0030 Direct Visual Presentation of Alpha-Numeric Data Each panel is a self-contained package, providing 16 to 18 display positions, each of which may be instructed by a 6-bit coded signal to display one of 64 preprogrammed characters as a 5 x 7 dot-matrix, formed by special gas-discharge units. Each character is 04 inches high providing a bright image, visible over a wide viewing angle. Full applications data is available giving all necessary information.



ADD 8% VAT TO ALL PRICES

WW-85 FOR FURTHER DETAILS

www.americanradiohistory.com

the test equipment people



£32 £40

Type 315-05026540 12V-15A Type 315-0505928G 12V-25A

FLECTRONIC BROKERS EQUIPMENT CATALOGUE

at comprehensive catalogue of its kind The most comprehensive catelogue of its kind sever compiled in the UK. Send 50p towards printing, postage, atc. (Ovarease customers £1) and a catalogue will be sent by return. Electronic Brokers Ltd. will then keep the catalogue updated by 'forwarding revision sheets free of charge.

MULTIMETERS

AVO

meter Test Set No. 1 (Panclimatic Version of Mode vometer Model 8SX (same spec as Model 8) £40 vometer Model 7 £29

Adometer Model J 229 All above relovished calibrated and guaranteed test leads NFW. for above Models 64 RUSSIA AC Clamp Volt-ammeter U 91 Brand New 613.75 Spec Curren 10.25 100-250.500 Amos Voltage 300 600V Accuracy 4% Used for measurements of AC Voltages and currents without breaking the circuits Ranges are selected by means of a Rotary Selector Switch

Switch Megohimmeter Type M410D/3 Brand New £37 Nominal 0/p Voltage (open cct) 500V High measurements Range (at 500V) 500Ms) (Mid Scale

Carriage and packing

charge extra on all items unless otherwise stated. 5M(2) Low measurements Range 1000K(2) Portable (7lbs.) and Hand operated c/w carrying case SEE ALSO INSIDE BACK PAGE.

VOLTMETERS HEWLETT PACKARD

HEWLETT PACKARD DC Vacuum Tube Voltmeter 412A 1MV-1000V 1 Accuracy Can also be used as Ohmeter £75

 tob.co
 tob.co

 3%
 tob.co

 Vacuun: Tube Voltmeter 400H Freq Range 10Hr-4MHz Volts 1 0mV-300V FS (12 ranges) Accuracy ± 1% (50Hz-500KHz) ± 2% (20Hz-1MHz)

 Accuracy ± 1% (50Hz-500KHz) ± 2% (20Hz-1MHz)
 AV Voltmeter 400E Solid state AC volts 1mV-300V FS (12 ranges) Freq 10Hz-10MHz Accuracy 1 P.0.A MARCONI

PHILIPS

PHLIPS LF Millovitmeter GM 6012 12 ranges-1mV-300V dB seale on meter Accuracy 2Hz 5% 5Hz 100KHz 25% 100KHz-1MHz 0.5% Amplifi-cation available 50.70 MF Millovitmeter GM 6014 Measuring Ranges 1mV 300mV in 6 ranges Accuracy et 30KHz 3% of FSD = Amplitude Chail 1KHz 30KHz Hat within 55.00 SIGN ELECTRONICS

N Voltmeter LM1420.2 2.5...V-1Kv in 6

SOLARTRON

On these pages you will find just the briefest selection from the vast range which we hold in stock at any one time

If you are seeking a specific item and it is not listed, it will pay you to ring us first - we believe we offer the best prices and the best service

WORLD WIDE EXPORT. **Enquiries and tenders**

welcome from any part of the world.

HOW TO REACH US We are easy to reach, no matter where you live.

Minutes away from Kings Cross or St. Pancras main-line stations, and a bus ride from Euston; only just over half an hour from Heathrow Airport. Parking is easy too.







Carrying Case £12.50 extra Send for full litera-BRAND NEW

MISCELLANEOUS

P

0

0

ADVANCE Recorder Calibrator HC20 £15.00 AVO Tester CT150. For testing of receiving & low rivalves: Mutual conductance. Emission ode insulation & anode current an tae roeasureal







| 1 | AIR MEC / RACAL E19 Nave Analyser 248A, 5-300 MHz E19 Nave Analyser 853, 30 KHz-30 MHz Sensitivi o 1V up to 20 MHz, 4 uV to 4V up to 30 MHz Nave Analyser 248, Freq, Range | 5-£390 ty. 1 ±V £95.90 5MHz- £110 |
|---------------|---|--|
| | AIRMEC Modulation Meter 210 £75 1 | o £100 |
|) ((| AMPEX FM / Direct Recorder/Reproducer SP 3 Dhannels Speed 1/5, 334, 7/2, 15 ips. Freq. re Instrumentation 50Hz-40Hz at 15 ips. 50Hz-18KHz at 15 ips. Special off | 800. 4 sponse Audio er £850 |
| - | BECKMAN Transfer Oscillator 7580H DC-15GHz with 7 5MHz-15GHz without counter Sensitivity R M S.) SPECIAL OFFE | counter. 100mV R £250 |
| | BELL Saussmeter Type 120, complete with Probes | P.O.A. |
| | Bill K Deviation Bridge 1505 | P.O.A. |
| | Battery Charger 8E370 | £30.00 |
| 1 | Batlery Charger CC 99 | £15.40 |
| | DECCA Power Supply for Noise Source. MW.61 | P.O.A. |
| | FELONIC Band Pass Filter, TBA 140-60-5CC1 5 Section TNC connectors 3411 tubular 60Mhz ba 140Mhz centre freq. Brand new | TNC to ndwidth £20 |
| | Probe type P6006 (with UHF plug fitted) | £12.50 |
| | PYE Thermocouple test set 7556 | £:95 |
| | SENERAL RADIO SENERAL RADIO Wooden Transit Case Unis Null Detector / 212A 20Hz-5MHz Log R with 120dB sacale HEWLETT PACKARD Desention Analyser, 331A | E1090 E1090 esponse P.O.A. |
| | Digital Recorder 560A | £110 |
| | HEWLETT PACKARD Directional detector 787D 1 9-4 1Ghz | 6#0 |
| | Directional detector 788C 3 7-8.3Ghz MARCONI INSTS. | £195 |
| | Attenuator TF 1073A7.25 Our of Limits Indicator TF 2404/2M1, readings from electronic counters and other insta Local and remote visual and electricat in su table for use by unskilled personnel and with Biank & Sync Mixer TF 2908 Quantization Distortion Tester TF 2343 R = Power Meter TF 1152.11 | EB5 Checks r digital dication A T.E P.O.A. E90 P.O.A. |
| | Q Meter TF 329G | £2+0 |
| 1 | Prope kit TM8120/1 X1 for use with valve v TF2600 Brand new | oltmerer E20 |
| | Stereo Coder MSCBN 419272 Polyscop Swob II Attenuator type DPR Z = 60 ohms BN 18042 U H F Millivoltmeter Type URV | P.O.A. £14%0 P.O.A. £125 |
| | Sweep Generator SM 2000 c/w Plug Ins E-3M | 4. S-6-8 |
| 1 | Add 50p Post & Packing p | Jus VAT |
| 1 | *e NSL and these pages | e pricos |
| S. | mutes of | 1 |
| -to | Thege CK ty there | $\left(1 \right)$ |
| in s Iv- u | Anner please 837 7781 | |
| | |) |

WW-084 FOR FURTHER DETAILS

€60

Please note: All instruments offered are

months unless otherwise stated.

secondhand and tested and guaranteed 12

SEMICONDUCTORS



marked *. Remainder add 121/2%. Do NOT add V.A.T. to prices marked †.

| | SOLDERING IRONS |
|--|--|
| | x25. 25 watt |
| - | Model G. 18 watt |
| | SK2.Soldering Kit |
| I covered top | BITS AND ELEMENTS |
| leight Price | Bit No. |
| 2" *£1.25 | 102 for model CN240 3/3 |
| 3" *£1.62 | 104 for model CN240 3/ |
| 11/2" *£0.92 | 1100 for model CCN240 3/3 |
| 2 ¹ / ₂ " *£1.39 | 1101 for model CCN240 3. |
| OXES | 1020 for model G240 3/3 |
| | 1021 for model G240 1 |
| leight Price | 1022 for model G240 3/1 |
| *0.45 | 51 for model X25 1 |
| 2 70.45 | 52 for model X25 3/ |
| 2 *0.54 | ELEARENTE . |
| *0.45 | ELEMENTS* |
| *0.39 | Model ECN Model EC 240 |
| *0.79 | Model ECCN 240 |
| *0.65 | Model EX 25 |
| deep lids & | SOLDERING IRON STAND |
| | ST2 Suitable for all models |
| TAGE AND | Antex heat shunt |
| <u> </u> | PLUCE |
| PAKS | PS I DIN 2 Pin (Speaker) |
| | PS 2 D.I.N. 3 Pin |
| Price | PS 3 D.I.N. 4 Pin |
| values | PS 4 D.I.N. 5 Pin 180° |
| weight .60 | PS 5 D.I.N. 5 Pin 240° |
| d values | PS 7 D.I.N. 7 Pin |
| weight .60 | PS 8 Jack 2.5mm Screened |
| .60 | PS 9 Jack 3.5mm Plastic |
| nixed | PS 10 Jack 3.5mm Screened |
| .60 | PS 12 Jack '4' Screened |
| Trite Rods.60 | PS 13 Jack Stereo Screened |
| .60 | PS 14 Phono |
| es ' | PS 15 Car Aerial |
| *.60 | 13 TO CO-Axial |
| *.60 | INLINE SOCKETS |
| re-Sets 60 | PS 21 D.I.N. 2 Pin (Speaker) |
| 3.5m, 2 | PS 23 DIN 5 Pin 180° |
| Туре .60 | PS 24 D.I.N. 5 Pin 240° |
| pre- | PS 25 Jack 2.5mm Plastic |
| s. types 60 | PS 26 Jack 3.5mm Plastic |
| ardware- | PS 28 Jack 4" Screened |
| nets, etc. *.60 | PS 29 Jack Stereo Plastic |
| hes, | PS 39 Jack Stereo Screened |
| DS Panels .60 | PS 31 Phono Screened |
| Knobs .60 | PS 33 Co-Axial |
| Change | COCKETE |
| .60 .60 | DO RE DI NI A D' (C I) |
| nate | PS 35 D.I.N. 2 Pin (Speaker) |
| *.60 | PS 37 D.I.N. 5 Pin 180° |
| icking on all | PS 38 D.I.N. 5 Pin 240° |
| rther 10p on | PS 39 Jack 2.5mm Switched |
| | PS 41 Jack 4" Switched |
| D | PS 42 Jack Stereo Switched |
| | PS 43 Phono Single |
| TICKY | PS 44 Phono Double |
| | PS 40 CO-Axial Surface PS 47 Co-Axial Flush |
| | |
| | P.C.B. KITS & PEN |
| | |
| ADUCCIVE | PROFESSIONAL D.I.Y. PRINT CIRCUIT KIT |
| ADUCOIAC | Containing 6 chaots of 6" |
| a works in | containing o sneets of b X 4 |

AN

| ITEX EQUIPME | NT * | IT'O MENA IT | |
|--|------------------|--|--|
| ING IRONS | | IIS NEW-II | S POWERFUL! |
| att | *£2.95 | IT'S THE AL | 250 |
| 18 watt | *£3.25 *C2.25 | II SINE AL | .230 |
| ering Kit | *£4.60 | 125 watts R.M.S. | and a stand produce |
| D ELEMENTS' | | The module has a sensitivity | Contraction Providence |
| andal CN240 2 (22 | *490 | of 450mV and frequency | 2 |
| nodel CN240 3/32 | *46p | to 20KHz whilst distortion levels | POWER AMPLIFIER |
| nodel CCN240 3/32 | *46p | are typically below 1% The | Specially designed for use in-Disco Units, P.A. Systems, high nower Hi-Fi |
| nodel CCN240 3/8 | *46p | use of 4, 115w transistors in the | Sound reinforcement systems |
| nodel G240 3/32 | *46p | incorrect or short-circuit loads is preven | rugged while damage resulting from |
| nodel G240 1/8 | *46p | Circuit | ned by a loar nanastor protection |
| 10del G240 3/16 | *46p | The unit is intended for use in many ap | oplications such as disco units sound |
| 10del X25 3/32 | *46p | reinforcement systems background me | usic players etc |
| nodel X25 3/16 | "*46p | SPECIFICATION | Total harmonic distortion |
| TS + | | Output Power: 125 watt RMS | 50 watts into 4 ohms: 01 1 % |
| N | *£1.25 | Operating voltage: 50-80 | 50 watts into 8 ohms: |
| 240 | *£1.60 | Loads: 4-16 ohms | S/N ratio: better than 80dBs |
| CN 240 25 | *£1.60 | Frequency response 25Hz-20kHz Managed - 100 | Damping factor, 8 ohms: 65 |
| 20 | 121.40 | watts | Semiconductor complement: 13 |
| NG IRON STAND | | Sensitivity for 100 watts output | Overall size: Heatsink width |
| ble for all models | *£1.25 | at 1kHz: 450mV | 190mm, length 205mm, height |
| n shum | | | 40mm |
| .N. 2 Pin (Speaker) | 0.10 | UNLY £15.9 | 15 + 8% VAT |
| .N. 3 Pin | 0.11 | | |
| .N. 4 Pin | 0.14 | BIB HI-FI ACCESSORIES | CERAMIC PAKS |
| .N. 5 Pin 180° .N. 5 Pin 240° | 0.15 | REF PRICE | |
| .N. 6 Pin | 0.16 | D' 2 Histi Cable & Flow Tidu | Containing a range of miniat |
| .N. 7 Pin | 0.17 | 'J' Tape Head Cleaning Kit 72n | unrepeatable value. |
| k 2.5mm Screened | 0.17 | 'P' Hi-Fi Cleaner *30p | MC1 24 ceramic capacitors: 22 |
| k 3.5mm Screened | 0.17 | Model 9 Wire Stripper *£1.00 | 27pF, 33pF. 39pF, 47pF, 56pF, 68 |
| k ¼" Plastic | 0.14 | 24 ¹ / ₈ " Cassette Editing Kit *£1.80 | and 82pF |
| k % Screened | 0.20 | 29A Salvage Cassette *44p | MC2 29 ceramic capacitors: 100 120pF 150pF 180pF 220pF 270 |
| ono | 0.09 | 32A Stylus Balance £1.28 | 330pF. and 390pF |
| · Aerial | 0.14 | 36A Record & Stylus Cleaning Kit *32n | MC3 24 ceramic capacitors: 470 |
| Axial | 0.14 | 41 8 Track Cartridge Head Carrier | 1500pF, 680pF, 830pF, 1000 1500pF, 2200pF, and 3300pF |
| OCKETS | | 88p Model 42 Groov-Kleen *c1 e4 | MC4 21 ceramic capacitors: 4700 |
| N. 2 Pin (Speaker) | 0.13 | 42/S Roller & Brush for REF 42 & 2000 | 6800pF, 01μF, .015μF, .022μF, .033 |
| N. 5 Pin 180° | 0.19 | 42 Papard Caus Kis | and .04/µr0 |
| N. 5 Pin 240° | 0.19 | 45 Auto Changer Groov-Kleen 98n | · |
| k 3.5mm Plastic | 0.15 | 46 Spirit level *72p | MAMMOTH I.C. PAK |
| k ¼" Plastic | 0.28 | 48 Record Dust-off *26 p | |
| k ¼" Screened | 0.32 | 53 Hi-Fi Stereo Test Cassette *£2.40 | Approx. 200 FIECES |
| k Stereo Screened | 0.28 | 56 Hi-Fi Hints & Tips Book *48p | including: Logic, 74 series. Line |
| no Screened | 0.17 | Model 60 Groov-Kleen *£1.72 | Audio and D.T.L. Many coded devi |
| Aerial | 0.20 | and Base Sticker for Model 60 *24p | but some unmarked — you to identi |
| AAI81 | 0.20 | 62 Cassette Head Cleaner (Liquid) 48p | OUR SPECIAL PRICE EI |
| N 2 Dim (Secolum) | 0.07 | A Record 'Dust Off' (Displays of ten) | |
| N. 2 Pin (Speaker) N. 3 Pin | 0.07 | 71A Record 'Dust Off' (Bubble Pack) | HANDBOOKS |
| N. 5 Pin 180° | 0.09 | *70p | TRANSISTOR DATA BOOK. DTI |
| N. 5 Pin 240° | 0.10 | 76 Stylus Cleaner *265 | 227 Pages packed with information |
| 3.5mm Switched | 0.11 | 78 Cassette Fast Hand Winder *98p | tion including outlines |
| 4" Switched | 0.19 | 83 Cassette Title & Container Labels | Price † £2.95 es |
| Stereo Switched | 0.28 | (20 & 10) *36p | TRANSISTOR EQUIVALENT BO |
| no Single no Double | 0.07 | AUDIO LEADS | BPE 75 256 Pages of cross referen |
| Axial Surface | 0.09 | S221 5 pin DIN plug to 4 phono plugs | can and Japanese Transistors. This |
| Axial Flush | 0.19 | length 1.5m £1.08 | the most comprehensive equivale |
| B. KITS & PENS | 5 | length 1.5m | introduction in 13 languages. |
| ONAL D.LY PRINTE | | S237 5 pin DIN plug to 5 pin DIN plug | Price † 62.68 ea |
| (IT | | S238 2 pin DIN plug to 2 pin DIN socket | 144 Pages of cross references a |
| 6 sheets of 6" x 4" | single | length 5m .68p S268 5 nin DIN plug to 2 nin DIN plug 1 | and Japanese Diodes Zeners Thu |
| nate, a generous sup | ply of | & 4 and 3 & 5 length 1.5m £1.00 | tors, Triacs, Diacs and L.E.D.'s. |
| tweezers, etch res | istant | S270 2 pin DIN plug to 2 pin DIN socket | Price † £1.98 ea |
| n, high quality pum | p drill | In 10m | MULLARD DATA BOOK |
| s, cutting knite with netal ruler, plus full a | spare asy to | connected to pins 3 & 5 length | popular handbook contains inform |
| uctions. | | 1.5m .70p | tion on Semiconductors. Integrat |
| *£7.80 p | ber kit | connected to pins 3 & 5 length | Valves, Capacitors and Resistor |
| ainer of etchant for a | above, *70n | 23cm .68p | Included in the 161 informative page |
| | | S318 5 pin DIN socket to 2 phono plugs | are 21 pages on Semiconduci Comparables Price + 50m |
| RKING PENS | | 23cm | TTL DATA BOOK DIC 75 N |
| market pens, speci | fically | S404 Coiled stereo headphones exten- | complete Data book of 74 series T |
| or urawing tine et | chant | SION COLD extends to 7m £1.40 | 1/980-/91321 Covering 13 main mar |

- sion cord extends to 7m S217 3 pin DIN plug to 3 pin DIN plug 80p

CERAMIC PAKS

Containing a range of miniature ceramic capacitors in mixed values, unrepeatable value.

MAMMOTH I.C. PAK * **APPROX. 200 PIECES**

Assorted fall-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices but some unmarked — you to identify. OUR SPECIAL PRICE £1.00

HANDBOOKS

TRANSISTOR DATA BOOK. DTE 2 227 Pages packed with information on European Transistors. Full specification including outlines.

Can and Japanese Transistors. This is the most comprehensive equivalents book on the market today and has an introduction in 13 languages. Price † C2.68 each DIODE EQUIVALENT BOOK DE 74 Ida Page of proce professione

Price t 22.68 each DIODE EQUIVALENT BOOK DE 74 144 Pages of cross references and equivalents for European, American and Japanese Diodes, Zeners, Thyris-tors, Triacs, Diacs and L.E.D.'s. Price t £1.98 each, MULARD DATA BOOK MDB 50p. The latest edition of this popular handbook contains informa-tion on Semiconductors. Integrated Circuits. Television Picture Tubes. Valves, Capacitors and Resistors. Included in the 161 informative pages are 21 pages on Semiconductor Comparables Price t 50p each. TTL DATA BOOK DIC 75 Now complete Data book of 74 series TTL (7400-74132). Covering 13 main manu-facturers in U.S.A. and Europe, this book gives full data as well as equivalents Price t £3.74 THE WORLD'S BROADCASTING STATIONS WBS 75 An up-to-the-minute guide for those interested in DX-ing. Contains all the world's broadcasters on SM, MW and LW, as well as European FM/TV stations. Price t £3.56 A full range of technical books available on request.



SLIDER PAK

0.60 0.60 0.60 0.60

0.60

0.60

*33p *441 56r

Containing a range of slider pots. SPI 6 mixed values sliders.... SP2 6 47OR Lin. sliders.... SP3 6 10K Lin. slider SP4 6 22K Lin. sliders... SP5 6 27K Lin. sliders...

47K Log. sliders. 47K Lin. sliders

LOW-NOISE CASSETTES

,6 6 6

SP5

SP6

C60 C90 C120

01

500

COILS CARBON POTENTIOMETERS Log and Lin 4.7K. 1 220K, 470K, 1M, 2M.

| VC. 5 | 100K Log anti-Log | 0.6 |
|-------|--------------------|-----|
| VC 4 | IK Lin Less Switch | 0.2 |
| VC 3 | Tandem Less Switch | 0.6 |
| ¥C 2 | Single D.P. Switch | 0.4 |
| VC I | Single Less Switch | 0.1 |

47K, 100K, 220K, 470K, 1M, 2M, 4.7M.

| 000 50 | | | |
|-----------|----------|---------------|------------|
| MT50/2 | 2 | £5.00 | 0.60 |
| MT50/1 | 1 | £4.00 | 0.48 |
| MT50/1/2 | 1.2 | £3.00 | 0.45 |
| Type | Amps | Price | P&P |
| 8V, 10V, | 40V, 50V | / and 25V-0-; | 25V. |
| available | from sel | ected tappin | gs 4V. 7V, |
| 240V. P | rimary. | Secondary | voltages |

SWITCHES

FUSES

20mm, 100mA, 200mA, 250mA, 500mA

| | 1.021, | 211 | QUICH | DLO W | |
|--|--------|-----|-------|--------|-----|
| | | | | *0.05p | eac |
| | | | | | |

VB 1

containing approx. 50sq. ins. variou: sizes all 0.1 matrix *0.60 VB 2

Etch resistant printed circipen. Full instructions sup pen. Fui each pen

clip and lead



Please add 8% to all prices

.

.

| *0.60p | 6 | | | | | | |
|------------------------------|-----------------------|---|--|--|--|--|--|
| ns. various *0.60p | CYAN The second | IOACRYLATE G2 ADHI wonder bond which wo ds Bonds plastic, rubber, t | | | | | |
| 1.4 | tors. | components, permanently, | | | | | |
| uit marker | diately | /1 | | | | | |
| plied with | 0 | OUR PRICE ONLY 70 | | | | | |
| *0.92p | | for 2 gm phial | | | | | |
| | CABL | ES · Per | | | | | |
| th terminal | CP I | Single lapped screen | | | | | |
| *0.31p each | CP 2 | Twin Common Screen | | | | | |
| | CP 3 | Stereo Screened | | | | | |
| | CP 4 | Four Core Common | | | | | |
| | | Screen | | | | | |
| | CP 5 | Four Core individually screened | | | | | |
| | CP 6 | Microphone Fully | | | | | |
| | | Braided Cable | | | | | |
| | CP 7 | Three Core Mains Cable | | | | | |
| 1 | CP 8 | Twin Oval Mains Cable | | | | | |
| | CP 9 | Speaker Cable | | | | | |
| ' | ČP 10 | Low Loss Co-Axial | | | | | |
| Τ. Ι | | | | | | | |
| | | DED | | | | | |

Postage and Packing add 25p unless otherwise shown. Add extra for airmail. Minimum order £1.00



www.americanradiohistory.com



 Frequency coverage:
 50Hz -- 100kHz for AC 30V and below (* 3%).

 10kHz for other AC voltage ranges
 53kz: 184 x 134 x 88mm

 Size: 184 x 134 x 88mm
 Meter £30.93 (8).

 Weight: 1.34g.
 Meter with Case

118

 Weight: 1.3kg.
 Meter £30.33 (i) old price £40.03

 Meter £37.94 & £49.93
 £12.41. Old price £15.23

To celebrate the transfer of ownership of the Company, its move to new premises, we have decided to offer a selection from the range of **SANWA** meters at **REDUCED PRICES**. We have achieved this by arranging to supply those items marked (C) after the price only direct from **QUALITY ELECTRONICS LTD.**, while those marked (B) are available from selected wholesale/retail outlets only. Instruments marked (A) are widely available through normal wholesale/retail channels. Details of new **QUANTITY DISCOUNTS** are available on application. All prices include VAT at 8%. **Postage and Packing** on this introductory offer is **free.** Full Sanwa catalogue and price list available on receipt of S.A.E.

Sole U.K. Importers:

QUALITY ELECTRONICS LTD. 24 HIGH STREET, LYDD, KENT TN29 9AJ

(FORMERLY OF KINGSTON, SURREY). TELEPHONE: LYDD 20252. TELEX: 965265 (A/B Servolydd)

In association with SERVO & ELECTRONICS SALES LTD, at the same address

Specialist suppliers of Alps Panel Meters, Synchros, Servomotors, Electrical Connectors Test Equipment and Computer Peripherals.

WW-062 FOR FURTHER DETAILS

www.americanradiohistory.com



COMPUTER APPRECIATION Castle Street, Bletchingley, Surrey RH1 4NX. Godstone (088 384) 3106

EKCO M5138 Digital Ratemeter. High precision 6 digit TTL counter-timer, counting freq. to 10MHz and timing with a resolution of 1 microsec. Very extensive range of I/O (incl. analogue output. NEW AND packaged. £48. **EKCO** Field Ratemeter. All solid state multi-range instrument

EKCO Field Ratemeter. All solid state multi-range instrumer with fluid sampling and end-window beta probes. NEW. £45. **RUSTRAK** 2-channel chart recorder. NEW. £30.

HONEYWELL P112 key-to-card printing punches; V126 verifiers. About 40 available. Prices from £85 one-off to around £30 per unit for the consignment. **G.E.** 9-track Data Recorders. £95.

FLEXOWRITER Model 2305 with full ASCII character set. £575 (Other Flexos, from £95).

ITEL Paper Tape Golfball Typewriter, ex-demo. £290. **VIATRON** Data Prep. Units comprising VDU & twin Philips cassettes under microprocessor control. £190. **PDP 8L**, 4k processor with ASR 33. £1,050. 119

ASR 33 Teletypes sometimes available at £325.

BURROUGHS E2100 Computer with typewriter. £79.

HONEYWELL 120 processor with 16k x 8 2 microsec, memory. All manuals.£135 FACIT 4001 Tape Reader, £390, 4015 spooler, £75. PE 1001

Reader, £175. **PRINTEC** 100 C.P.S. ASCII printer. Ex-demo. £450.

VDU Kit and MOTOROLA 4K Computer Kit - see other ad

SUMMER SALE DEDUCT 10% FROM THE PRICES SHOWN HERE. OFFER CLOSES JULY 31st 1976 min. CWO £1.

| LINEAR ICs | 5 | | | DISCRETE | | Modu | les, tuners | |
|---|--|--|---|---|--|--|--|---|
| CA3089E KB4402 TDA1200 HA1137W CA3090AQ MC1310P KB4400 CA3053 CA3088E | 1.94 1.94 2.20 3.75 2.20 2.20 0.40 1.50 | 7805KC 7805UC 78L12 78M12 TDA1412 7812 7815 78M20 78M20 78M24 | 1.75* 1.55* 0.45* 1.20* 0.95* 1.55* 1.55* 1.20* 1.20* | ZTX107n ZTX108n ZTX109n ZTX212p ZTX213p ZTX214p ZTX214p ZTX413n ZTX551p ZTX451n B5224 | 0.14 0.14 0.16 0.16 0.16 0.16 0.18 0.18 0.18 | 5600 EC3302 9001 9002 9007 7700 8011 | Varicap Mosfet with 4 tuned RF ccts. Varicap FET/Bipolar min. tunerhead. Frequency meter, scale $88 - 108$. Strength meter, scale $0 - 10$. Tuning meter, scale $3 - 0 - 3$ 'Off-air' UHF TV sound receiver Varicap tuned, with interstation muting, and sound detection at 38 MHz (Built). inc. P.S.U. 6 station electrnic station selector for any positively tuned varicap tuner system, | 11.00 5.50 2.50 2.50 2.50 2.50 |
| LM1496 MC135OP SN7666ON TBA120AS TBA651 uA720PC uA753 TDA440 LM380 | 1.02 0.70 0.75 1.00 1.81 1.40 0.99 1.75 1.00 | uA723 NE550 LS8038 NE555 NE560 NE561 NE562 NE565 NE566 NE566 | 0.80* BF224n 0.22 0.80* BD515n 0.27 3.10* BD516p 0.30 7252 0.70* BD165n 0.50 7253 2.50 BD535n 0.52 8319 2.50 BD536p 0.53 2020k 2.50 BD609n 0.70 2020HS 2.50* BD377n 0.29 8001k 2.50* BD378p 0.32 Suffix 'k 0.30 1N4001 0.06 NEW M 0.30 1N4004 0.10 NEW M 0.30 1N4148 0.07 5619 0.38 OA91 0.08 7020k 0.50 DL704 0.95* 92310k | 7252 7253 8319 2020k 2020HS 8001k | and scan tuning. Built. Top quality tunerset VHF to audio Varicap tuned with 3 meter outputs. Tunerset with built-in stereo decoder. Varicap tuned. Dual Mosfet tunerhead as used in 7252. TDA2020 stereo amplifier kit. Heatsink for one TDA2020 (only with IC). k 55kHz low pass filter (birdy filter) for stereo radio (between detector and decoder). | 14.99 24.00 24.00 12.00 7.85 0.75 1.75 | | |
| LM381N LM3900 MC3401 uA741 TBA810AS TCA940E TDA2020 | 1.81 0.68* 0.68* 0.40* 1.09 1.80 2.99 | MVAM2 BA102 BA121 MV104 MEM615 MEM616 11C90 | | 50° BD378p 05 1N4001 30 1N4004 30 1N4148 45 OA91 50 DL704 00* SLA1 | 0.32 0.06 0.10 0.07 0.08 0.95* 1.25* | Suffix 'k' NEW MC 5619 7020k 92310k | indicates kit, otherwise supplied built and tested DDULES (EDGE TERMINATED) 6 stage, dual mosfet UHF tunerhead. 10uV FM IF system with muting, agc, main tuning voltage AFC system. Comprehensive 1310 decoder, with notch filters and 5x gain. | f. £12.50 £4.50 £5.35 |
| | | • | | General £7.50. P | Terms: C P for CV | CWO please NO orders | e, official bodies and companies please note 22p per order. (UK and Eire). Overseas custo | min. invoice mers please |

include sufficient for postage. VAT is not included, and must be added at 12%, but where items are marked * only add 8%. In stock orders despatched within 48 hours. INTERNATIONAL include sufficient for postage. VAL is not included, and must be added at 12.27 where items are marked * only add 8%. In stock orders despatched within 48 h 25 High Street, Brentwood, Essex. Tel: (0277) 216029, Telex: 995194.

NOW TELETYPE 35RO ASC11 CODE

HEAVY DUTY CONTINUOUS OPERATION with 240Volt Power Supply and Paper Feed. Circuits, Diagrams, Information supplied with all purchases.

A MUST AT £50 each

To all purchasers of the Teletype 35BO we offer a Re-Buildable Electronic Keyboard. In addition To the conventional keyboard layout there are 21 separate push-button function switches. Circuits of the internal logic and core system are provided. Power requirements obtainable from PU, supplied with 35RO. Price £10 ONLY.

Price £10 ONLY. AND NOW the LOW COST Approach to the IN-OUT problem of the Micro Processor — Means this is a MUST if you can't afford a Teletype 35 Attractive cast alloy front panel, vertical mount, Size 16½ x 15½ x 5½" containing 72 push buttors with manual or electrical reset (28V) with provision for labelling with your code, 65 illuminated symbols or functions (complete with 28V lamps) which again you can change; 15 bit front panel microswitch assembly to enable your coded cards to be read (sample card supplied) and host of other electronic parts Limited quantity — so rush your order £15 each.

| TALLY P/120 Panel mounted perforator | £120 |
|--|------|
| AMPEX TM7 (7211) Nice condition | £350 |
| AMPEX FR600 Recorder (FM) | £250 |
| POLARAD Receiver Model FIM-B2 Complete 1-10GHZ | £750 |
| UNIVAC Buffer Processor 8K Core Store Full info | £100 |
| LOCKHEAD ELECTRONICS 4 Channel Audio Recorder | £65 |
| 12 CHANNEL CHARD RECORDER FSD 5V 20MA per channel | £35 |
| MARCONI ADAPTOR TM6113 for TF2700; TF1313; TF8688 | £45 |
| RHODE & SCHWARZ Gen. BN41022 300-100MHZ | £220 |
| HEWLETT PACKARD Gen. 608D 10-420MHZ | £170 |
| AIRMEC 4 trace scope type 279, Large screen | £150 |
| TELONIC 4 Watt Sweeper PD3, 100-250HMZ | £120 |
| TELONIC Sweeper 2000-1 with LA-1M 20HZ-20KHZ | Ē140 |
| TEKTRONIX 180A Time Mark Generator | £120 |
| TEKTRONIX 181 Time Mark Generator | £60 |
| MARCONI TF1101 Oscillator 20c/s-20kc/s | £95 |
| ROHDE & SCHWARZ Admittance Meter BN3511 As new | £75 |
| CREED Model 92 8 hole reader | £40 |
| CREED 8 hole punch | £65 |
| SOLARTRON VF252 AC Millivoltmeter 1 5mv-150V full scale in 10 ranges. 6" meter : | 1% |

COME AND LOOK ON OUR SHELVES — HUNDREDS OF OTHER ITEMS TO INTEREST YOU, TOO FAR AWAY? THEN SEND FOR LISTS.

SUPPLIES call and see

SUPPLIES — call and see * TELEPHONES. Post Office style 74.5 Black or two-tone grey £6.50 ea. Modern style 706 Black or two-tone grey £4.50 ea. P&P 75p ea. 19" Alloy Blank Rack Panel 84" high 75p ea. P&P 75p MUFFIN FANS. 115V Size 5 x 5 x 1½" Superbly quiet and reliable Ex-eq but tested £1.50 ea. P&P 75p

PHOTOMULTIPLIER type 931A £4 ea. P&P 75p. Other types available also suitable Power

Supplies * POTENTIOMETERS - All 5p ea. P&P extra Metal bodied AB Linear PCB Mount Brand New. 10K; 100K ganged. 250K ganged. 100K ganged concentric shafts * BEEHIVE TRIMMERS 3/30pf Brand New 10 off 40p P&P 15p. 100 off £3.50 P&P 75p. 500 off £15 P&P£1 25, 1.000 off £25 P&P£1 50 LARGE RANGE ELECTROSTATIC VOLTMETERS. From 0.300V 2" £3 to 20KV Max General guide 5KV 3½" £5 Thereafter £1 per KV P&P 75p.

LARGE RANGE ELECTROSTATIC VOLTMETERS. From 0-300V 2" £3 to 20KV Max General guide 5KV 3/3" £5 Thereafter £1 per KV P&P 75p VARIACS 240V input 0-270V output 2A ex-eq £4 ea. P&P ±1 25. BA £18 ea. plus carr 20A £30 ea. plus carr '4.43MHZ CD Crystal 87/Octal base £4 ea. P&P 50p E H T Transformer 26KV AC 10MA 240V 50HZ Crystal 87/Octal base £4 ea. P&P 50p E H T Transformers and EHT capacitors available TRANSFORMERS — All 240V 50HZ inputs. Type A 17-0-17V 250MA 7 50-7.5V 250MA. 0-20V 5A. 0-4V 5A. 0-1-5V 5A. ±2 ea. P&P ±1 25 Type B 17-0-17V 250MA 8-0-8V 250MA. 0-7 5V 5A. 0-1.5-2V 5A. ±1.50 ea. P&P ±1. Type C 19-0-19V 250MA. 0-80V 250MA. 0-7 5V 5A. 0-1.4V 5A. £1.25 ea. P&P ±1 25 Type D 34V 4A, 19V 4A. 17V 4A. £3 ea. P&P ±1 25 Type E 3V 1A 25p ea. P&P 50p Type F 17V 1A 85p ea. P&P 50p Type G 20-0-20V 200MA. 0-6V 100MA 75p ea. P&P 75p

TUBES All Brand New Boxed Electrostatic deflection. Type 408A 1%" dia 7%" TUBES. All Brand New Boxed Electrostatic deflection Type 408A 11%" dia 73%" long Blue Trace £2.50 ea. P&P 75p. Type CV1526 (3EG1) 3" dia £4 ea. P&P £1. Type DG7/36 3" dia (Replacement for Telequipment S31) £15 ea. P&P £1 50 Magnetic Deflection 12DP7 12" round Blue with yellow after glow £1 ea. AND FOR THE VDU BUILDER M38.111GH Rectangular 30x20cm Green trace Superb value £12 or Economy type CME 24 x 18 cm White Trace £9 ea. DON'T FORGET YOUR MANUALS. S A E with requirements 20HZ to 200KHZ SINE & SQUARE WAVE GENERATOR. In four ranges Wien bridge oscillator thermistor stabilised Separate independent sine and square wave amplitude controls 3V max sine 6V max square outputs. Completely assembled PC Board ready to use 9 to 12V supply required. £8.85 ea. P&P 35p. Sine wave only £6.85 ea. WIDE RANCE WOBBULATOR. 5 MHZ to 150MHZ (Useful harmonics up to 15GHZ) up to 15MHZ sweep width Only 3 controls preset RF level Sweep width and frequency Ideal for Iona Blue

15MHZ sweep width Only 3 controls preset RF level sweep width and frequency Ideal for 10 7 or TV IF alignment filters, receivers Can be used with any general purpose scope. Full instructions supplied. Connect 6 3V AC and use within minutes of receiving. All this for only **£6.75** P&P 35p (Not cased, not calibrated).

Minimum Mail Order £2. Excess postage refunded.

Unless stated - please add £2.50 carriage to all units

VALUE ADDED TAX not included in prices - Goods marked with * 121/2 % VAT, otherwise 8% Official Orders Welcomed, Gov./Educational Depts., Authorities, etc., otherwise Cash with Order Open 9 a.m. to 5.30 p.m., Mon. to Sat.







Quality Products Made in America



Blonder-Tongue Field Strength Meter - FSM2 Superb quality and performance. Complete line of MATV and CATV products available.

Astatic - Choose from over 60 different microphones for public address, studio, commercial sound and recording microphones. Quality sound reproduction since 1930. Complete line of Astatic cartridges, needles and arms.

Atlas Loudspeaker - complete line of public address speakers and microphone stands.

Trusonic - speaker systems to meet every indoor and outdoor requirement.

Irish Tape - premium quality tape available in cassette, 8-track, open reel and video.

Gromes Precision - public address amplifiers

Consolidated Wire and Cable

AVA - coaxial connectors

Teleco - telephone answering instruments

Perma Power - portable PA Systems

Utah - complete line of hi-fi speakers and accessories

Automatic Garage Doors, TV Tube Brighteners, Remote Controls

Write for illustrated catalog and specifications for these products.

Morhan Exporting Corp.

270-278 Newtown Road Plainview, N.Y. 11803 Cable Address: Morhanex, N.Y. Telex: 96-7880

WW - 071 FOR FURTHER DETAILS

| 122 | | | |
|--|---|--|--|
| KINNIE COMPONENTS 10, NELMES WAY, HORNCHURCH ESSEX RM11 202 HORNCHURCH 45167 | UNISELECTORS (New) 25 way. 12 Bank (Non brid ohms. £6.50 P.P. 50p. MINIATURE UNISELECTOR (Ex. Equip.) 6 Bank (5 non brid bridging) 100 ohms 24-30 V.D P.P. 500 | | |
| CIRCUIT BOARD P.C.B. 1/16. 1 oz. COPPER FORMICA | 1,000 TYPE KĚY SWITCHES Single 2 x 2 c/o Locking. 50p. Bank of 4-2 x 4 c/o each switch (or £1.20 P.P. 25p. | | |
| Dim. 0.4 x 7.7 in 3 pcs., 90p Dim. 9.4 x 8.1 in 3 pcs., 90p Dim. 10.1 x 7.9 in 3 pcs., £1.00 Dim. 13.1 x 9.4 in 3 pcs., £1.20 Dim. 17.0 x 9.0 in 2 pcs., £1.20 Post & Packing 35p each pack. BARGAIN PACK | MULTICORE CABLE 6-core (6 colours) 14/0076 Scree. 30p per yard; 100 yards at £16.5 a yard, 7-core (7 colours) 7. Screened P.V.C. 30p per yard; £16.50 P.P. 4p per yard. | | |
| To pcs. 10, 1 x 7.9 in. Plus free 7216 etching Xtals £3.10 P.P. 65p. FIBRE GLASS P.C.B. Dim. 6 x 6 in. 50p each Dim. 12 x 6 in. 75p each Dim. 12 x 12 in £1.30 each | RIBBON CABLE (8 colours); 10m. £1.65. P.P. 25 8-core x 14/0.19mm. Bonded sid £11.50 P.P. £1. | | |
| Equals less than 1p sq. in. Post & Packing 15p per sheet. | P.T.F.E. CONNECTING WIRE 1/20 Black or White 100 m. Dr P.P. 30p. | | |
| RESIST COATED P.C.B. FURNINGA 10.1 x 7.9 in. 65p ea. 13.1 x 9.4 in 75p ea. RESIST COATED P.C.B. FIBRE GLASS 6 x 6 in. 65p ea. 12 x 6 in. £1.35 ea. | H.D. ALARM BELLS 6in. Dome. 6/8v, d.c. Heavy car for exterior/interior use. £3.75 Connecting wire (twin/twisted) 2 £3 P.P. 75p. | | |
| 12 x 12 in. £2.00 ea. Post & Packing 10p per sheet. BLUE P.C.B. INK Etch resist use with any pen. Much cheaper than ready loaded pens. 50 c.c. 55p. P.P. 10p. FERRIC CHLORIDE ETCHING XTALS 1 lb - 1 litre pack. 70p P.P. 35p. 5 lb - 5 litre pack. £2.20 P.P. 65p. PRINTED CIRCUIT KIT The no frills all value kit. Containing 4 pcs 8 x 7 Formica laminate 1 pce 6 x 6 Fibre glass | HIGH CAPACITY ELECTROLYT 250mfd/63 volt, 20p P.P. 8p. 1.000mfd/100 volt, 70p P.P. 25 2.200mfd/100 volt, 90p , P.P. 2 4,700mfd/25 volt, 50p , P.P. 20 6,800mfd/16 volt, 50p , P.P. 15 10,000mfd/25 volt, 75p , P.P. 2 25,000mfd/40 volt, £1.25 , P.P. 47,000mfd/40 volt, £1.25 , P.P. 100,000mfd/10 volt, £1.50 , P.F 160,000mfd/10 volt, £2.00 , P.F | | |
| laminate, 1 lb Etching Crystals, 50 c.c. Resist ink, with instructions. £2.40 P.P. 65p. BARGAIN PACK FIBRE GLASS P.C.B. | BULK COMPONENTS OFFER Resistors/capacitors 600 new co £2.75. P.P. 36p. Trial order 100 pcs 75p. P.P. 20p | | |
| 200 sq. in. all usable pieces £1.25 P.P.25p. EDGE CONNECTORS. 54 WAY .1 Vero size etc. Can be cut to any length 55p P.P. 10p. Side Guides to suit above 15p each. OVERLOAD CUT OUTS | SMITHS GEARED MOTORS 24 3 rev. per min. £1.50. P.P. 25p. 4 rev. per min. £1.50. P.P. 25p. 6 rev. per min. £1.50. P.P. 25p. 2 rev. per hour. £1.50. P.P. 25p. 6 rev. per hour. £1.50. P.P. 25p. | | |
| Panel mounting 800 M/A 1.8 amp. 10 amp. 55p ea. | HIGH-SPEED MAGNETIC | | |
| TELEPHONE DIALS (New) £1 P.P. 25p. EXTENSION TELEPHONES (Type 706). Various colours. £3.95 P.P. 75p. 12V MINIATURE | 4 digit (non reset) 24v or 48v (state which) 4 x 1 x 1 in. £1. P.P. 20p. 5 digit (non reset) 24v £1.50. P.F 3 digit 12v (Rotary Reset) 2¼ x £1.40. P.P. 15p. 6 digit (Reset) 220v. a.c. £3.50. | | |
| UNISELECIUK 11 ways. 4 bank (3 non bridging, 1 homing), £2.50 P.P. 35p. | RESET COUNTER (BRAND NEV 6 digit 24v. 25 1.P.S. £5 P.P. 25 | | |
| H.T. TRANSFORMERS. Prim. 110/240v. Sec. 400v. 100 m/a £3. P.P. 65p. L.T. TRANSFORMER. Prim. 240v. Sec. 27-0-27 at 800 m/a. £2.35. P.P. 50p. L.T. TRANSFORMER. Prim. 110/240v. Sec. 50v. at 10 amp. £10. P.P. £1.50. L.T. TRANSFORMER. Prim. 240v. Sec. 18v. at 1.5 amp. & 12v. at 1 amp. £2.25. P.P. 65p. L.T. TRANSFORMER. Prim. 240v. Sec. 18v. 1 amp. £1.10 P.P. 35p. L.T. TRANSFORMER. Prim. 240v. Sec. 12v at 1 amp. £1.8 P. 25c. | TRANSFORMERS L.T. TRANSFORMER. Prim. 1 Sec. 0/24/40v. at 1½. amp. (£1.95. P.P. 50p. L.T. TRANSFORMER. Prim. 2 Sec. 20/40/60v. at 2 amp. (Shrop. 70p. L.T. TRANSFORMER. Prim. 2 Sec. 20/40/60v. at 2 amp. (Shrop. 70p. L.T. TRANSFORMER. (H.D. 200/250v. Sec. 18v. at 27 am 9.8 amp; 40v. at 3.6 amp; 52v. 25v at 3.7 amp. £17.50. P.P. ⊈ L.T. TRANSFORMER Prim. 2.40v. | | |

ifd/63 volt, **20p** P.P. 8p. Omfd/100 volt, **70p** P.P. 25 Omfd/100 volt, **90p.** P.P. 2)mfd/25 volt, **65p.** P.P. 20)mfd/16 volt, **50p.** P.P. 15 Omfd/25 volt, 75p. P.P. 2 Omfd/40 volt, **£1.25.** P.P 00mfd / 40 volt, **£2.00.** P.P. 000mfd / 10 volt, **£1.50.** P.F 00mfd/10 volt, £2.00. P F **COMPONENTS OFFER** ors/capacitors 600 new co . P.P. 36p. rder 100 pcs 75p. P.P. 20p HS GEARED MOTORS 24 per min. £1.50. P.P. 25p. per min. £1.50. P.P. 25p. per min. £1.50. P.P. 25p. per hour. £1.50. P.P. 25p. per hour. £1.50. P.P. 25p. SPEED MAGNETIC TERS (non reset) 24v or 48v which) x 1 in. **£1.** P.P. 20p (non reset) 24v £1.50. P.P 12v (Rotary Reset) 21/4 x P.P. 15p (Reset) 220v. a.c. £3.50. T COUNTER (BRAND NEV 24v. 25 I.P.S. £5 P.P. 25p. TRANSFORMERS TRANSFORMER. Prim. 110/240v. 0/24/40v. at 1½. amp. (Shrouded). 5. P.P. 50p TRANSFORMER. Prim. 200/250v. 20/40/60v. at 2 amp. (Shrouded). £3. '0p. TRANSFORMER. (H.D.) Prim. 250v. Sec. 18v. at 27 amp; 40v. at

imp; 40v. at 3.6'amp; 52v. at 1 amp; at 3.7 amp. **£17.50.** P.P £2.50. L.T. TRANSFORMER. Prim. 240v. Sec. 20v.

at 2.5 amp. £2. P.P. 65p. TRANSFORMER ("C" L.T. CORE).

200/240v. Secs. 1-3-8-9c. All at 1.5 amp. 50v. at 1 amp. **£2.50.** P.P. 50p.

MAIL ORDER ONLY. PERSONAL CALLERS BY APPOINTMENT

| ELECTORS 25 way. 12 Bank (Non bridging), 68 £6.50 P.P. 50p. ATURE UNISELECTOR Equip.) 6 Bank (5 non bridging. 1 ng) 100 ohms 24-30 V.D.C. £1.50 Op. TYPE KEY SWITCHES 2 x 2 c/o Locking. 50p. P.P. 10p of 4-2 x 4 c/o each switch (one biased), P.P. 25p. | SIEMENS MINIATURE RELAYS 6v.4 c/o 65p. 24v.2 c/o 50p. MINIATURE RELAYS (1¾ x 1¼ x ½) 24 v.4 c/o 35p. P.P. 5p. WAINS RELAY 240v.a.c. 3 c/o 10 amp. contacts 80p. with base P.P. 20p 24v a.c. RELAY (PLUG IN) 3 pole c/o 75p. P.P. 15p. 2-pole c/o 55p. P.P. 15p. 2-pole c/o 55p. P.P. 15p. MINIATURE REED RELAY (1 x ¼) 12v. 1 c/o 50p. P.P. 10p. |
|--|--|
| ICORE CABLE (6 colours) 14/0076 Screened P.V.C. er yard; 100 yards at £16.50 P.P. 2p d, 7-core (7 colours) 7/22 mm. ed P.V.C. 30p per yard; 100 yards 0 P.P. 4p per yard. | S-DECS AND T-DECS S-DEC £1.90. U-DEC A £4.20. T-DEC £3.60. U-DEC B £6.90. |
| DN CABLE burs); 10m. £1.65. P.P. 25p. 100m. x 14/0.19mm. Bonded side by side 0 P.P. £1. E. CONNECTING WIRE Black or White 100 m. Drum £2.50 Op. | S.T.C. CRYSTAL FILTERS (10.7Mhz) 445-LQU-901A (50 Khz spac- ing), £3. P.P. 20p. 445-LQU-901B (25 Khz spacing). £4. P.P. 20p. 10.7 Mhz Canned I.Fs. Size 1 x ½ x ½ in. (with data) 65p. P.P. 10p. 3 GANG TUNING CAPACITOR |
| ALARM BELLS borne. 6/8v, d.c. Heavy cast housing sterior/interior use. £3.75 P.P. £1. scting wire (twin/twisted) 220yd. reel P. 75p. | 8.5 PF, to 320 P.F. 80p. P.P. 20p. V.H.F./U.H.F. POWER TRANSISTORS (type BLY 38). 3 watt output at 100-500 Mhz. £2.25. P.P. 10p. |
| CAPACITY ELECTROLYTICS fd/63 volt, 20p P.P. 8p. 0mfd/100 volt, 70p P.P. 25p. 0mfd/100 volt, 90p . P.P. 25p. 0mfd/25 volt, 65p . P.P. 20p. 0mfd/16 volt, 50p . P.P. 15p. 00mfd/25 volt, 75p . P.P. 25p. 10mfd/40 volt, £1.25 . P.P. 30p. 100mfd/40 volt, £2.00 . P.P. 50p. 100mfd/10 volt, £1.50 . P.P. 50p. 100mfd/10 volt, £2.00 . P.P. 50p. | AM/FM TUNING METER 125-0-125 μA Edgewise 1½ x ½, £1.10 SIGNAL STRENGTH METER 250 μA (illum.) Edgewise 1½ x ½, £1.10 OUTPUT METER CLEAR PLASTIC 500 μA 1½ x 1½, £1.30 MINIATURE METERS 500 micro-amp (level stereo beacon, etc) |
| COMPONENTS OFFER ors/capacitors 600 new components 5 P.P. 36p. order 100 pcs 75p. P.P. 20p. | P.P. 15p. PANEL METERS 2% in. x 1% T8 500mA |
| HS GEARED MOTORS 240V AC per min. £1.50. P.P. 25p. per min. £1.50. P.P. 25p. per min. £1.50. P.P. 25p. per hour. £1.50. P.P. 25p. per hour. £1.50. P.P. 25p. | T1 50 μA T9 1Amp T2 100 μA T10 50 ν.a.c. T3 500 μA T11 300 ν.a.c. T4 1mA T12 50/0/50 filA T5 10mA T13 100/0/100 μA T6 50mA T14 500/0/500 μA T7 100mA All at £3.75. P.P. 15p. |
| SPEED MAGNETIC ITERS (non reset) 24v or 48v which) | PANEL METERS 4½ ins. x 3¼ D3 200 µA D1 50 µA D4 500 µA D2 100 µA All at £4.60. P.P. 15p. |
| x i in. £1. F. 20p. t (non reset) 24v £1.50. P.P. 20p. t 12v (Rotary Reset) 2¼ x 1¼ x 1¼ J. P.P. 15p. t (Reset) 220v. a.c. £3.50. P.P. 25p. | S.C.R. ETCH RESIST 1 amp. 400 P.t:V. 35p 5 amp. 400 P.I.V. 40p |
| T COUNTER (BRAND NEW) | MINIATURE "ELAPSED TIME" INDICATORS |

(0.5000 hours) 45 x 8mm 75p. P.P. 15p.

L.T. TRANSFORMER ("C" CORE) Prim. 120v/120v SECS. 1-3-9-20v. 10 amps **£7.50.** P.P. £1.25. L.T. TRANSFORMER ("C" CORE)

200/240v. Secs. 1-3-9-27v. All at 10 amp. **€7.50.** P.P. £1.50 TRANSFORMER ("C" CORE) L.T.

200/240v. Secs. 1-3-9-20v. All at 4 amp. **£5.50.** P.P. 75p.

L.T., TRANSFORMER (''C'' CORE) 120/120v. Secs. 1-3-9-9v. All at 10 amp. **£6.50.** P.P. £1.50.

TRANSFORMER ("C" CORE) L.T. 110/240v. Secs. 1-3-9v. 10 amp. 35v. 1 amp; 50v. 750 M/A. £6.50. P.P. £1.50.

١

L.T. TRANSFORMER. Prim.

Sec. 23/24/25v. at 10 amps **£7.** P.P. £1 L.T. TRANSFORMER. Prim. 110/240v

Sec. 20/21/22v. at 8 amp. £6. P.P. £1.

110/240v.

110/240v



Advertisements accepted up to 12 noon Monday, May 31, for the July issue, subject to space being available. **DISPLAYED APPOINTMENTS VACANT:** £6.50 per single col. centimetre (min. 3cm). **LINE advertisements (run on):** £1 per line, minimum three lines. **BOX NUMBERS:** 45p extra. (Replies should be addressed to the Box Number in the

advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU.) PHONE: Owen Bailey on 01-261 8508 or 01-261 8423.

Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

TESTAND LIAISON ENGINEERS

Ferranti in Edinburgh have a number of Ministry of Defence contracts involving the design and development of advanced avionic equipment for military aircraft in an international market.

We have vacancies for test and liaison engineers who will probably be qualified to HND level in electronic engineering with some years' experience in design, test or support of modern avionic equipment. A knowledge of digital and analogue techniques is essential.

Close liaison with design/development teams currently engaged on inertial navigation and display systems will be necessary and the work will entail factory acceptance testing, fault diagnosis and system commissioning on a variety of sophisticated equipment.

There will be opportunities for some of these engineers after a period of in-house training to be selected for technical liaison duties at locations in the U.K., Europe, Middle and Far East.

The Company offers an attractive employment package which includes 22 days holiday and membership of a life assurance and pension scheme. Incoming personnel will qualify for housing under the Scottish Special Housing Association scheme and realistic assistance will be given with relocation expenses where applicable.

FERRA

Apply in writing giving details of age, experience and qualifications to:

THE STAFF APPOINTMENTS OFFICER FERRANTI LIMITED FERRY ROAD EDINBURGH EH52XS

UNIVERSITY OF STRATHCLYDE AUDIO VISUAL UNIT TELEVISION ENGINEER Grade 6

required with experience in the maintenance of television and sound equipment in addition to supervision of staff, the work includes the running of an electronic workshop and operational duties as a Senior member of the studio crew for television recordings. Candidates should have experience in a television studio, preferably as vision control engineer or sound mixer and should hold an H.N.C. City & Guilds or R T.E.B. Certificate

Salary Scale i 3156 -£3762 per annum Applications in writing. QUOTING REFER-ENCE AV 4. giving details of age and qualifications, should be made to The Personnel Officer. University of Strathclyde. Royal College Building, 204 George Street, Glasgow G1 1XW (5397

SENIOR TEST ENGINEER

To fault find on interesting and varied circuits for a range of equipments. Produced in small batches. Experience of digital and analogue circuits is essential. Above average salary and good promotional prospects. The Company is rapidly expanding with positive management. We have a full order book, mainly for export World Wide.

Please contact in confidence Mr. D. Hemsley DIGITAL ELECTRONICS LTD. Holywell Industrial Estate Watford, Herts Tel: 45991



We have selected from many vacancies those which offer exceptional career prospects and job interest. If you have experience in design, test, sales or service and wish to progress your career, piease telephone. Mike Gernat B.Sc. who is advising on these opportunities.

E.M.A. Management Personnel L'td. Burne House, 88/89 High Holborn London WC1V 6LR 01:242 7773 1360



Radio Officers-now you can enjoy the comforts of home.

Working for the Post Office Maritime Services really makes sense. You still do the work that interests you, but with all the advantages of a shore-based job: more time to enjoy home life, job security and good money. To qualify, you need a United Kingdom Maritime Radiocommunication Operator's General Certificate or First Class Certificate of competence in Radiotelegraphy, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting salaries, at 25 or over, are £2905 rising to £3704 after three years service. Between 19 and 24, the starting salary varies from £2234 to £2627 according to age. You'll also receive an allowance for shift duties which at the maximum of the scale averages £900 a year and there are opportunities to earn overtime. There's a good pension scheme, sick pay benefits and prospects of promotion to senior management.

Right now we have vacancies at some of our coastal radio stations, so if you're 19 or over, write to: ETE Maritime Radio Services Division (L687), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London EC1A 1AR.

Post Office Telecommunications



²⁵ Appointments



SERVICE AND INSTALLATION ENGINEERS

M.E.L., part of the Philips Organisation, has recently achieved outstanding success in gaining new markets for its highly successful range of medical Linear Accelerators – used in the fight against cancer.

This expansion has created new opportunities for skilled engineers to install these highly sophisticated equipments in all parts of the world. As a member of a specialist team, you will be required to carry out installation projects (of up to three months' duration), service equipment and trouble-shoot – wherever your skills are needed.

You must be adaptable and self-reliant, qualified to at least ONC level or equivalent and have a good knowledge of semi-conductor circuitry. Preferably, you will also have worked on such equipment as modern high-power radar systems.

We offer a progressive salary, bonus and pension scheme, generous expenses and twenty three days' holiday. If appropriate, assistance will be given in moving to this attractive part of Sussex, situated mid-way between Brighton and London.

Please write or telephone for an application form to Diana Hill, Personnel Officer, M.E.L. Equipment Company Limited, Manor Royal, Crawley, Sussex. Tel: 0293 28787.



Appointments

TEST GEAR ENGINEERS

Rediffusion, a major British company in television manufacture, is developing a new, state of the art receiver at its Chessington laboratories. To support this project we require additional Test Equipment Design and Development Engineers at senior and intermediate levels to help produce our sophisticated production test equipment. Rediffusion test equipment leads the industry and uses both analogue and digital techniques along with an up-to-date approach to jugging.

Applications are invited from well qualified and experienced test equipment engineers, who will be offered the opportunity to join a young and energetic team. Our work is usually demanding, often under pressure but always stimulating, using new ideas to speed production testing whilst reducing the demands on our test operators.

Salaries, which will depend on experience, are excellent and assistance with relocation will be given where appropriate. Some travelling to our production factories in Co. Durham will be necessary from time to time to assist in the installation and commissioning of new equipment since our design engineers are expected to be responsible for all aspects of their project.

If you are a high calibre engineer and wish to have your ability recognised and rewarded, come and join us.

Write or 'phone to:

A. J. Litteck, Test Equipment Group Leader, Rediffusion Consumer Electronics Ltd., Fullers Way South, Chessington, Surrey. Phone 01-397-5411



REDIFFUSION

(5313)

STROBE EQUIPMENT LTD.

Manufacturers of High Powered Studio Electronic Flash Equipment, which is used all over the world by top photographic companies, require

SERVICE/CONSTRUCTION MECHANICS

To be generally involved in maintaining and building power units, accessories and allied devices. Basic electronic knowledge is sufficient but applicants should be capable of handling bench tools and light machinery and hold a current driving licence.

Phone or write (preferably) Mr. Cecil, Strobe Equipment Ltd. 56 Turnmill Street. London. EC 1 M5QR 01-253 0791 / 3 (5364)

RESEARCH, DESIGN & DEVELOPMENT

We are expanding our Electronics Laboratory and can offer rapid results in all electronic departments. We have 15 years experience working for the Government and industry generally. Give our Technical Director. E. A. Falkner a ring on 01-572 0933. R.C.S. Electronics, National Works, Bath Road, Hounslow, Middlesex

Opportunities for Electronics Engineers

To change to wider fields of electronics - join the EMI Service Team at Hayes.

Vacancies exist on repair and calibration of a wide range of electronic test gear including oscilloscopes, DVMs, pulse generators, power supplies etc.

Also

Servicing and commissioning closed Circuit television equipment including cameras, VTRs, Monitors etc.

Applicants should have at least 5 years practical experience. These positions offer varied and interesting work. Attractive starting salaries, subsidised lunches, 4 weeks holiday and excellent sick pay and pension schemes.

For further details telephone of write to \pm M. Ford, 01-573 3888, Ext. 2167, EMI Service, 254 Blyth Road, Hayes, Middlesex.



The international music, electronics and leisure Group

(5320)

LEICESTER POLYTECHNIC School of Chemistry ELECTRONICS

TECHNICIAN

 (a) the design, development and construction of prototype electronic equipment for chemical applications;

(b) the maintenance of existing equipment. Successful applicant must have a knowledge of analogue and digital electronics and will probably have at least two years' experience subsequent to taking a Full Technological Certificate. HND, or a degree in Electronics.

Salary: £2,922 - £3,702 p.a., plus qualification allowance for certain qualifications.

Apply in writing, giving full details, to Staffing Officer, Leicester Polytechnic, P.O. Box 143, Leicester LE1 9BH (5380)

London Borough of Barking Barking College of Technology LECTURER GRADE I IN MARINE

RADIO/COMMUNICATIONS

required as soon as possible, principally for full-time courses in Marine Radio and for City and Guilds of London Institute Telecommunications Certificate. Applicants should have appropriate qualifications and experience Burnham Scale salary £2,429 to £4,377, plus £351 London Addition. Requests for application forms and further details should be accompanied by a stamped addressed envelope and sent to The Registrar. Barking College of Technology. Dagenham Road, Romford, Essex, RM7 OXU Completed forms to be returned to him within 14 days of the appearance of this notice.

THE UNIVERSITY OF MANCHESTER HESTER ADRIAN RESEARCH CENTRE

Anson House Pre-School Project for Mentally Handicapped Children A vacancy exists for a

(Grade 3)

(Grade 3) in the above project. The successful applicant will work in the pre-school facility which is one mile from the University, but will have access to electronic and mechanical workshops in the University itself. The major requirement will be that the technican will be responsible for the operation of an extensive CCTV system and will undertake the editing of tapes. Experience with CCTV is therefore important Subsidiary functions will involve some electronic and mechanical work. ONC is essential and HNC (Electronics or Physics) (or equivalent qualification)

Salary scale £2.325 - £2.655 p.a. The post is at present vacant a

The post is at present vacant and the successful applicant could start on a date to be arranged.

Applications with full details of age. qualifications and previous experience should be addressed to Dr. J. Hogg. Hester Adrian Research Centre. The University. Manchester M13 9PL (5398)





OMAN

Dhofar Region Television Service

- Very Good Salary
- Free Family Passage
- No Income Tax payable in Oman
- Free furnished Accommodation
- Special End of Contract Bonus
- We pay Local Education Fees
- Comprehensive Free Insurance, Health, Dental, etc.
- Hard work is necessary

We are recruiting on renewable one year contracts and have vacancies for the following and other positions:

PROGRAMME STAFF

- Production Direction
- News
- Film Editing
- Transmission Controller

OPERATIONS STAFF

- Telecine
- V.T.R.
- Sound Dubbing and Mixing
- Film Processing

ENGINEERS

- Studio
- Transmitters
- Microwave
- O/B Van

PLUS

- Aerial Rigger
- Electricians

Let us discuss with you your abilities for these interesting and important positions.

Phone: Tony Towers, 01-573 8333 for more information

PERSONNEL & ELECTRONICS LTD.

Appointments 128

Radio Technology **TELECOMMUNICATIONS OFFICERS**

for a Radio Station in Hertfordshire. The work is mainly concerned with the installation and maintenance of electronic equipment such as radio receivers, spectrum analysers and direction-finding equipment and involves the use of a wide range of test equipment

Candidates (aged at least 23) must have ONC in Engineering (with a pass in Electrical Engineering 'A) or in Applied Physics, or an equivalent qualification. In addition, they should have had experience in the operation of radio receiving equipment and have a knowledge of current operational systems of radio communications.

Salary starting between £3,145 and £3,790 (according to age) and rising to £4,090. A shift system is worked and a shift disturbance allowance is payable Promotion prospects. Non-contributory pension scheme.

For further details and an application form (to be returned by 14 June 1976) write to Civil Service Commission, Alencon Link, Basingstoke, Hants RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours) or London 01-839 1992 (24-hour answering service). Please quote T/9292/3.

HOME OFFICE



Electronics Engineers

VOL is the worlds largest operator of commercial work submersibles. A number of these units are involved in underwater surveying, primarily for the off-shore oil industry.

As a part of our continuing expansion we have vacancies for Electronics Engineers to operate and maintain the computers, data logging and underwater acoustic systems, used in this developing technology;

Past experience should include either underwater navigation, surveying systems or data recording and computer maintenance. Familiarity with DEC PDP11 machines would be particularly useful.

Applicants should be of HNC standard and be able to work on their own initiative in a challenging environment. Off-shore and base training will be provided for suitable applicants. These positions are based at VOL's Leith Base and would involve periods of work at sea, usually not exceeding 3 weeks.

Please write for an application form to the:-

Personnel Officer, Vickers Oceanics Ltd., P.O. Box 215 East Old Dock, Leith Docks, 6PH Edinburgh EH6 Tel: 031/554/0676

International **Broadcast Sales** Engineers

(5495)

RCA Broadcast Division has openings for Sales Engineers to assume responsibility for the marketing and sale of our range of professional television and radio studio and transmitter equipment in areas of Europe, Africa and the Middle East

The positions will be based either in Sunbury on Thames, England, or if appropriate on the continent of Europe, and each salesman/ woman will have direct responsibility for the aggressive promotion and sale of our products.

As a considerable amount of time has to be spent in the countries concerned, applications are invited only from persons willing to spend up to 50% of their time in their sales territory.

Ideally, we seek people with past experience of selling broadcast or associated products, preferably internationally. However, we will also consider for training, candidates with experience in the operation and maintenance of broadcast equipment who are interested and keen to enter commercial and selling activity.

We are looking for people who are interested in overseas travel and who have the initiative, dedication and personality to operate effectively in the challenging environment of international sales. A knowledge of French and/or German would be an asset for some posts.

Salaries are negotiable but will certainly be in keeping with the responsibilities and demands of these posts. Competitive Company fringe benefits etc., exist.

Applications outlining past experience, age etc., should be sent as early as possible to :

Pam Torma, RCA International Ltd., 50 Curzon Street, London, W.1, England.



((5387)

ppointments Wireless World, June 1976 THE BRITISH COUNCIL CCTV SAUDI ARABIA **AUDIO-VISUAL** Engineer **SPECIALISTS** The British Council will require extra staff from July or August. 1976, for established Projects in Communication Skills in English at universities in Saudi Arabia. EMI Service require an experienced CCTV Engineer to supervise a team engaged in the servicing and commissioning of CCTV systems and equipment. For this position, which offers varied and The Projects, which are designed to teach English to students of Engineering, science architecture and medicine, are supported by extensive audio-visual facilities. Vacancies will exist for suitably qualified Specialists in Audio-Visual Techniques and for Electronic Engineers with experience of cctv. interesting work, applicants should have at least 5 years' practical experience in CCTV There's an attractive starting salary, subsidised lunches, 4 weeks Contracts will be for 12 months in the first holiday and excellent sick pay and pension schemes. For further Total empluments will be within nstance details telephone or write to M. Ford on 01-573 3888 ext. 2167 Instance. Total emoluments will be within the range £6.000 · £9.000 p.a. depending on the post and the circumstances of the candidate. They will be free of Saudi income tax. Free furnished accommodation will be EMI Service, 254 Blyth Road, Hayes, Middlesex provided. Further particulars and forms of application are obtainable from Overseas Educational Appointments Department. The British Council. 65 Davies Street. London W1Y 2AA. Please quote reference 76 AU 30-60. The intenational music, electronics and leisure Group. (5379)TWO INSTRUCTORS IN MARINE RADIO LEEDS CITY COUNCIL are required by Department of Education COLLEGE OF I.M.R. COMMUNICATIONS 160-176 CHORLTON ROAD, MANCHESTER M16 7WT Leeds Polytechnic -- Education Technology Unit One will be required to instruct morse sending and receiving to trainee radio officers, and the other will teach the theoretical syllabus for the Home Office **T.V. ENGINEER** General Certificate course. Qualifications and experience will determine the position on a salary scale (Temporary) £2,112 to £3,945 (5524 (Ref. 13/23) T3 £2922 - £3282 The holder of this post works with the media production team in SCOTTISH HOME AND HEALTH DEPARTMENT the operation of the colour television studio and related recording facilities and assists in the maintenance of equipment Application forms (quoting ref. no.) together with further details, WIRELESS should be obtained from the Administration Officer, Leeds Polytechnic, Calverley Street, Leeds LS1 3HE. Please enclose S.A.E. TECHNICIAN Applications are invited for a post of Wireless Technician in Scottish Home and Health Department. Location: Anglian Water Authority Montreathmont Moor (near Montrose) Qualifications: **ELECTRICAL AND** HNC in Electrical or Electronic Engineering or City and Guilds Certificate desirable. **MECHANICAL ASSISTANT** Experience: 3 years' appropriate experience Ref: W1032 Grade 7 £4 650 £5 016 Starting Salary: Applications are invited for the above post based at Milton Keynes $\pounds 2,010$ (age 17) to $\pounds 2,905$ (age 25 or over) scale maximum Office, Old Stratford £3.385. In addition a supplement of £313.20 per annum is The successful candidate will be reponsible for the operation, payable for staff aged 18 or over (£261.00 per annum for staff maintenance and installation of all electrical, electronic and aged 17). Applicants should have sound theoretical and practical knowledge of Radio Engineering and Radio Communications equipment in HF, VHF and UHF bands. The work involves mechanical equipment in the area, including modern processor operated telemetry installation and maintenance of equipment located at considerable Relocation expenses payable in appropriate cases and an essential car users allowance will be attached to the post. NJC for Water Service Staffs Conditions of Service apply distance from headquarters. A clean current driving licence and ability to drive private and commercial vehicles are essential

Appointment is unestablished initially but there is prospect of an established (ie permanent) appointment after 1 year's satisfactory service.

Application forms and further information are obtainable from Scottish Office Personnel Division, Room 105, 22/25 Queen Street, Edinburgh EH2 1LY (quote ref: PM(PTS)2/5/76 (031-556 9222, ext. 727).

Closing date for receipt of completed application forms is $27\,\,\text{May}, 1976.$

(5389)

Further details available from: The Area Manager, Cosgrove Road, Old Stratford, Telephone: Stony Stratford 2481.

Applications in writing to: The Divisional Manager, by May 30th, 1976.

BEDFORD WATER DIVISION Cambridge Road, Harrowden, Bedford, MK42 011

Appointments

Wireless World, June 1976



130

Perhaps we can help!

We have regular contact with hundreds of electronics and electrical companies needing qualified electronics engineers and technicians and TV service engineers. We can, therefore, help you to find an interesting and well paid job. All you need to do is to return the coupon below or give us a ring. Our service is confidential and costs you nothing.

> TJB Electrotechnical Personnel Services 12 Mount Ephraim Tunbridge Wells, Kent

Tunbridge Wells (0892) 39388



TJB Electrotechnical Personnel Services is a division of Technical & Executive Personnel Ltd. and is solely concerned with job placement in the Electronics and Electrical Industries

Please note that this service is available only for engineers who are (or will be) available in the U.K. for interview.

| Please send me an "Application for Registration' | 1 | for | m |
|--|-------|------|---|
| NAME | • • | ••• | • |
| ADDRESS | • • • | | • |
| ••••• | ••• | •••• | • |
| | | (90) |) |



Phillips Petroleum Company, operator for the Phillips Norway Group of companies, is establishing a major crude oil processing; natural gas liquid fractionating and terminalling project at Seal Sands, Cleveland, which will create employment opportunities for high calibre personnel

TECHNICIANS (VVVV/1/76)

An integral and important part of our operations capability at our oil stabilisation and NGL fractionating plant presently under construction will be sophisticated computer and communications controls

Daniels, Kent, AAI computers will be used extensively to optimise plant control functions with the metering and loading of products into sea going tankers.

Communications equipment centres around at Tropospheric scatter shore station and micro wave link with the Ekofisk oil field in the North Sea. In plant radio and telephone systems will also be in operation.

We now wish to establish a small group of technicians to maintain and repair this wide range of equipment and invite applications from candidates who can offer relevant practical experience with preferably a H.N.C qualification

These appointments offer competitive commencing salaries, and conditions of service are those one would expect from a major organisation such as Phillips Petroleum Company

If you are interested in these vacancies, please write for an application form (quoting job reference No.), to: Mr. A. Jackson Personnel Officer

(5395)

(5506)



PHILLIPS PETROLEUM COMPANY esside Operations, Seal Sands, Middle:sbrough, Cleveland TS2 1H0 Tel: 0642 546411

WEST BIRMINGHAM HEALTH DISTRICT

TECHNICIAN

For the Electronics and Bio-Medical Engineering Section

The successful applicant must have sound knowledge and experience of maintenance and development of electro medical respirators, ventilators, laboratory and other electro-mechanical equipment

Salary. Technician III £2931-£3834 (increase pending) Technician II £3558-£4581 (increase pending) Starting salary dependent on qualifications and previous experience

Application form and job description from District Works Officer, Dudley Road Hospital, Birmingham B18 70H Telephone 021-554 3801, Ext. 4838

Please quote ref. 840/WW



INSTRUMENTATION

SECTION LEADER

Michelin seek a graduate or HND engineer (of either sex) to head a small technical group working on vehicle instrumentation systems at Stoke-on-Trent

Applicants must have at least five years instrumentation

experience with road vehicles or aircraft. Knowledge of both digital and analogue data handling is essential, and ability in FORTRAN would be an advantage

As leaders in radial tyre manufacture. Michelio reflect

Please write, with full details of career to date, to

Recruitment Manager (SPS). (M.322/WW)

their favourable world market position in excellent service

MICHELI

THE CONTRACTOR OF SERVICE AND ADDRESS THAT TO ADDRESS THE

conditions including five weeks annual holiday, pension and life assurance schemes, and relocation assistance



An opportunity has occurred in our Pharmacology Department for a Senior Technician to work in the Bioengineering field. There will be some troubleshooting and general maintenance but principally the work concerns the design, construction and servicing of electronic apparatus. The successful candidate, who will join a small and specialised team, must be able to work with both analogue and digital electronic circuits and should be familiar with multichannel equipment used for recording bioelectric signals.

Education is likely to be to H.N.C. level or possibly a technical qualification at a lower level in electronics.

Our Laboratories are situated in pleasant parkland surroundings within easy reach of Bromley and Beckenham, and about 12 miles from Charing Cross. Conditions of employment are attractive and include 4 weeks' holiday, a subsidised canteen and excellent sports and social facilities.

Please write, quoting reference ZH.652, and giving brief details of qualifications and experience to:

N. J. Michell Personnel Officer The Wellcome Research Laboratories Beckenham Kent BR3 3B5



University of Glasgow Department of Music ELECTRONIC MUSIC STUDIO

A TECHNICIAN Grade 5

is required to maintain, modify and build equipment for the Electronic Music Studio in the Department of

Applicants should be interested in digital and audio electronics, be able to maintain analogue and digital audio equipment and have at least an ONC and seven years of relevant experience.

The studio is developing a course as part of the University's B.Mus. degree and provides facilities for professional composers. Equipment includes 16-track recording facilities, based on an Ampex 1000 and including Dolby noise reduction, quadrophonic and stereo playback, a computer-controlled (PDP8/A) Synthi 100 and other synthesizing equipment.

Salary range: £2751-£3207. Further information from, and all applications including a curriculum vitae and the names of two referees, to. The Personnel Officer, The University of Glasgow, Glasgow G12 800, not later than 4th June 1976. (5496)



If you're not earning over £3,500 p a plus a car - then you had better contact us! (5360)

ercy Street, London, W.1 11-636 9659 (day) or 550 0836 (evening)

THERMIONIC VALVE expert specialising in "Rats Nests" re-quired by famous film schood desperate for maintenance assist-ance. Little money, much enthusiasm and satisfaction. Hours 9.30-5 p.m. weekly or by arrange-ment. — Apply to: The Admini-strator. The London International Film School, 24 Shelton Street. London, WC2.

ENGINEER required V.T.R. ENGINEER required by C.C.T.V. Company. Applicants should have at least 5 years ex-perience in the V.T.R. field and bc fully conversant with all helical scan V.T.R.'s. Salary will be negotiable. Applicants should write giving full details of experience, qualifications and give an indica-tion of salary required to Box No. (5530. V.T.R. C.C.T.V. by 5530. (5530)

RADIO TELEPHONE Service Engineer wanted for work-shops in South London. Must be reliable and ex-perienced with Pye, GEC, and other mobile radio equip. Salary Neg. 680-1010. (5329)

Required a TECHNICAL REPRE-SENTATIVE to sell the Electro Voice range of sound reinforce-ment products in the United Kingdom

dom. Ideally the person selected will be a graduate Engineer in Physics, Electronics or Acoustics aged be-tween 25 and 30 years having in-dustrial experience with a company in the electro-acoustial, record-ing or sound reinforcement fields. Selling experience to Recording Studios, National Broadcasting Companies and/or the entertain-ments industry will be a distinct advantage. Remuneration will be on a basic salary plus commission basis and

Remuneration will be on a basic salary plus commission basis and there is ample scope for promotion for the successful applicant, who can successfully demonstrate an ability to build good business for our products in the UK. Please write or telephone Wendy Hunter, Guiton Europe Ltd., The Hyde, Lower Bevendean, Brighton BN2 4JU, Sussex, England. Tel. Brighton (0273) 66271. (5390)

RESEARCH, DESIGN & RESEARCH, DESIGN & DEVELOP. MENT. We are expanding our Electronics Laboratory and can offer rapid results in all electronic department. We have 15 years ex-perience working for the Govern-ment and industry generally. Give our Technical Director, E. A. Falkner a ring on 01-572 0933. R.C.S. Electronics, National Works. Bath Road. Hounslow, Middlesex. (5500) DEVELOP (5500)

c. £4,500

Michelin Tyre Co. Ltd.

Stoke-on-Trent ST4 4EY

UNIVERSITY OF LEEDS TELEVISION SERVICE Applications are invited for the post of SENIOR AUDIO ENGINEER, based at the University Television Service in Leeds, where the faci-lities include two television studios, one film studio an audio-dubbing

dities include two television studios, one film studio an audio-dubbing suite, a mobile television unit and a number of other portable cam-era/VTR units. An active interest and competence in practical sound recording at an appropriate professional level is essential and the duties include the operation and engineering main-tenance of film and television audio recording and dubbing equipment, together with the sup-ervision of, and close working involvement with, other members of staff. of staff

of staff. Evidence of ability will be required and practical tests will be arranged for those interviewed. Salary will be within the range £3,156-£3.762 per annum and the conditions of employment for those applying to full time University technical staff.

technical staff. Details, applications should be sent as soon as possible to The Deputy Director (Technical Services), Uni-versity Television Service, The University of Leeds, Leeds LS2 9JT. (5502)

RADIO TELEPHONE. V.H.F. Both V.H.F. RADIO TELEPHONE, Both bench and field engineers required for maintenance and installation. 5-day week salary, £2.500-£3,500 p.a. depending on experience. Must be capable of using own initiative. 01-573 4541. (5523

RADIO-Telephone Service Engineer/ Manager wanted for workshop in Croydon. Must be experienced in Pye, GEC etc., mobile radio equipment. Enormous potential for the right applicant. Salary accord-ing to ability and experience, 01-680 1010. (5518)

americanradiobis

AUDIO/ COMMUNICATIONS CONSULTANT

(5508)

A leading firm of consultants in the Entertainment Industry are looking for a Specialist to expand their team dealing with theatres, conference halls and studios in the U.K. and abroad. Practical experience in communications systems, sound reproduction and reinforcements, recording and television is appropriate and an ability to define equipment and installation details is required. Based in Central London.

Applications in confidence to Box No 5511.

The Polytechnic of North London

Department of Electronic and Communications Engineering

Two Technicians (Grade 11B)

Applications are invited for the posts of Applications are invited for the posts of two Technicians (Grade 11B) in the Department of Electronic and Communications Engineering. Duties will include provision of general assistance to students as directed and construction, modification and servicing of electronic test equipment, under supervision.

2 to 3 years' similar previous experience is desirable and suitably recognised qualifications.

Salary scale: £2583-£2910 inclusive of London Weighting

Application forms obtainable from the Establishment Officer, The Polytechnic of North London, Holloway Road, London, N7 8DB. (55 (5516) APPOINTMENTS

132

HULL ROYAL INFIRMARY (SUTTON)

Medical Physics Technician (Electronics)

Fixed term vacancy

required by the Medical Physics Department to assist in the development and maintenance of electronic equipment within the health service. The appointment is for one year in the first instance, but may be extended for a further one or two years dependent on the continuance of the funds currently being used for this purpose. Subject to satisfactory performance, the experience gained will improve prospects of a permanent appointment

Candidates (male or female) should have ONC, HNC or a degree in Electronic Engineering and, according to qualifications and experience the salary will be in the range £2346-£3171

Application forms may be obtained from the District Personnel Officer, Victoria House, Park Street, Hull, but applicants are invited to telephone the Chief Technician, Mr. Harrison (701151 Ext. 203) for further information

Hull District Humberside Area Health Authority STER.

SITUATIONS WANTED

PHYSICS TEACHER seeks to broaden his horizons during year from September. Experience in writing. editing, electronics. Full. writing, editing, part, or home Box No, 5507. work considered.

ARTICLES FOR SALE

MICROPROCESSORS This book gives you a general overview of the Technology Design

Ideas and Practical Applications PRICE £9.25 by L. Altman

THE ELECTRONIC MUSICAL INSTRUMENT MANUAL by PRICE £8.00 Douglas AMATEUR'S

RADIO HANDBOOK, 1976 by ARR PRICE £4.80

WORLD RADIO TV HAND-BOOK, 1976 PRICE £4.00 TTL COOKBOOK by D Lancaster PRICE £5.80

ELECTRONIC FUNDAMEN-TALS & APPLICATIONS: FOR ENGINEERS & SCIENTISTS by Millman Halkiss PRICE £9.55

110 COSMOS DIGITAL IC PROJESTS FOR THE HOME CONSTRUCTOR by R M Mar-ston PRICE £3.00

99 WAYS TO KNOW & USE YOUR ELECTRONIC CALCULA TOR by L E Frenzel PRICE £3.80

HANDBOOK OF DATA COM-MUNICATIONS by Post Office PRICE £9.00

ELECTRONICS ENGINEER'S REFERENCE BOOK by L W Turner PRICE £25.60

* PRICES INCLUDE POSTAGE *

THE MODERN BOOK CO SPECIALISTS IN SCIENTIFIC & TECHNICAL BOOKS **19-21 PRAED STREET** LONDON W2 1NP

Phone 723 4185 Closed Sat 1 p m

ARTICLES FOR SALE

(5386)

IBM GOLFBALL 7351/0 TYPEWRITERS

Coding similar to E8CDIC

will accept normal or sprocketed paper Supplied in working order with photo copy of IBM interface manual Each machine serviced and tested $\pounds 100 + 3\xi_k$ VAT As above but modified to take office range of goltballs t118 + 8% VAT (including new golfball) UK delivery by Securicor + packing ± 7.50 Overseas air freight or under all colt

surface at cost

RELAYS HELAYS Varley 2p c o 1851; 65p (12p) Varley 2p c / o 280; 95p (12p) PXB 2p c / o 1500; 40p (12p) BNC Free SKT 8L L1339 J 35p (10p) BNC Chassis SKT SCRND L1339/FS 35p (10p) (10p)

PAPST (or similar) Fans $4\frac{1}{2} \times 4\frac{1}{2} \times 2$ in 100 c f m 50 60 **£3.50** (65p) c/s

 $\begin{array}{l} \textbf{ELECTROLYTICS} \\ 10 \ 000 \ 63\nu \ \textbf{£1} \ (30\rho) \ 2 \ 800 \ \textbf{.} \ 100\nu \ \textbf{70p} \\ (25\rho) \ 2240 \ \textbf{.} \ 100\nu \ \textbf{70p} \ 4000 \ \textbf{.} \\ \textbf{50p} \ (20\rho) \ 2 \ 000 \ \textbf{.} \ \textbf{50p} \ (30\rho) \ \textbf{35p} \ (11\rho) \ \textbf{4} \ 000 \ \textbf{.} \\ \textbf{70v} \ \textbf{80p} \ (25\rho) \ 10.000 \ \textbf{.} \ \textbf{16v} \ \textbf{50p} \ (20\rho) \end{array}$

EX COMPUTER PC PANELS 2 x 4" 50 boards £2.40 (62p) QH bulbs 12v 55w 60p (10p) 250 mixed resistors 60p (18p) 250 mixed Capacitors 60p (18p) Small electrolytics

2 2 2 10v 10u 35v 50u 40v 100u 40v 100u 6v 150u 10v, 64u 10v, 300u 10v 200u 10v 12 for **45p** (12p)

PIHER PRESETS 100mm 10K 47K 100K

220 470 1K 447 1 220K 12 for **50p** (12p) Reed relays 6v coil h/d contacts 5 for £1

Reed inserts h d contacts 10 for £1 (12p) TRANSFORMER 6y 500mA 75p (18p)

TRANSFORMER 31v 330mA 60p (30p) Add 25% VAT to items marked * others 8%

KEYTRONICS Shop open Monday to Saturday 9 30 a m -2 p m 332 Ley Street, liford, Essex

01-553 1863

Wireless World, June 1976

ARTICLES FOR SALE

COLOUR UHF and TV SPARES. Lists available on request "Wireless World" TV tuner project, by D. C. Read. Kits of parts available. New cross hatch kit, Aerial input type. No other connections. Battery operated, portable. Incl. Sync & UHF Moderator units. £11.00 p/p 45p. CRT Reactivator kit for colour and mono £17.48 p/p 70p. Signal strength meter kit £13.00 p/p 60p. 625 TV I.F. Unit, suitable for Hi-Fi amp on tape recording £6.80 p/p 60p. Bush CTV 25 new convergence panels + yoke and blue lateral 53.60 p/p 65p. New Philips single standard convergence panels com-plete incl. 16 controls, coils P.B. switches, leads £3.75 p/p 65p. New colour scan coils, Mullard or Ples-sey, plus convergence yoke and blue lateral £9.20 p/p 70p. Mullard at 1023/05 convergence yoke £2.50 p/p 50p. Mullard or Plessey Blue laterals 75p p/p 25p. BRC 3000 type scan coils £2.00 p/p 60p. Bush CTV25 scan coils, new £2.50 p/p 60p. Delay lines DL20 £3.50, DL40 £1.50, DL1E, DL1 £1.00 p/p 35p. Lum Delay Lines 50 p/p 60p. Bush CTV25 scan coils, new £2.50 p/p 60p. Delay lines bL20 £3.50, DL40 £1.50, DL1E, DL1 £1.00 p/p 35p. Lum Delay Lines 50 p/p 60p. Special offer, colour triplers: 1TT TH25/ TTH £2.00 p/p 40p. GEC 2040 tripler £1.75 p/p 40p. Philips G8 panels, part complete, surplus/salvaged: decoder £2.50, IF, incl. 5 modules £2.25. T-Base £1.00 p/p 50p. CRT base 75p p/p 20p. G.E.C. 2040 panels for sparks. Decoder £3.59. Timebase £1.00 p/p 55p. VARICAP TUNERS UHF ELC 1043 new £4.20. ELC 1043/05. £5.00. VHF ELC 1042. new £5.00. Salvaged VHF and UHF varicap tuners £1.50 p/p 25p. SPECIAL OFFER: RBM 6psn. Vari-cap control units £1.00 p/p 25p. UHF tuners, new, transistorised, incl. slow motion drive, £3.80, 41 position and 6-position push-button transistorised, £4.20 p/p 60p. Philips, Bush, Decca integrated UHF/VHF transd, tuners £4.50 p/p 65p. Thorn 850 dual Standard time base panel 50p p/p 50p. Philips 626 I.F. amp. incl. CT 50p p/p 50p. VHF turets and ard Philips. Stella. Pye, Ekco, Ferranti, Invicta £2.00 p/p 55p. Large selection. LOPTs, FOPTs av



DIGITAL CLOCK CHIP, AY-5-1224. with data and circuit diagram. £3.66 plus VAT. Jumbo' LED digits (16mm high) type economy DL/747 only £2.04 each plus VAT. post free. Greenbank Electronics. 94 New Chester Road. Wirral, Merseyside L62 5AG. (83

C.R.T. REGUNNING PLANT. New and secondhand reconditioned training demonstration, colour or B/W, Barretts, Mayo Road, Croydon, Surrey, CRO 2QP. (36)

| PRECISION POLYCARBONATE CAPACITORS All High Stability – Extremely Low Leakage | |
|--|-----------|
| PARAFOL: DIVIENSIONS VALUE (mm) PRICE SSYRange 1% 2% 3% (1) L () ACR 2007 (2) (2) (2) (2) (2) (2) (2) (2) (2) (2) | |
| $\begin{array}{cccccccccccccccccccccccccccccccccccc$ | |
| $\begin{array}{l} \label{eq:2.1} \begin{array}{l} \mbox{with \mathbf{p}_0}, \mbox{isy}, \mbox$ | |
| st BUINATUR VERTRAT PRESPTSDTW only ALL at 59 each 500 (1000), 2202, 3702, 5001 (kt) 22kil, 47kil, 6 kkil, 10kil, 15kil, 22kil, 47kil, 6 kkil, 1002, 22kil, 47kil, 6 kkil, 10kil, 15kil, 22kil, 47kil, 6 kkil, 1002, 2506, 8 okil, 10kil, 15kil, 22kil, 47kil, 6 kkil, 1002, 2506, 8 kkil, 10kil, 15kil, 22kil, PLASE ADD 50 POST AND PACKING ON ALL ORD RS BELOW 55 ALL EXPORT ORDERS ADD - OST OF SEAAIR MAIL IN 10 POST OF SEAAIR MAIL IN 10 POST OF SEAAIR MAIL IN 10 POST OF SEAAIR MAIL Send SA F. For less is a valiable to bona fide companies MARCO TRADING (Dept. D1) The Old School Edistastion Mr | |
| Tel. Whixail (Shropshire) (STD 094872) 464/5 (Propr. Minicost Trading Ltd.) | |
| From drawings to completed product For quality, service and a keen proce, contact Mr Price-Smith Multiform | |
| CIECTIONICS Limited 22 Portugal Road Woking Surrey GU215. Telephone Woking (04862) 70248 (530 | JE)8' |

PRINTED CIRCUIT BOARDS — Quick deliveries, competitive prices, quotations on request, roller tin-ning, drilling, etc., speciality small batches. larger quantities available Jamiesons Automatics Ltd. 1-5 Westgate, Bridlington, N. Humber-side, for the attention of Mr. J. Harrison, Tel: (0262) 4738/77877. (18 618

CAPACITY available to the Electronic Industry. Precision turned parts, engraving, milling and grinding both in metals and plastics. Limited capacity available on Mathey SP33 jig borer. Write for lists of full plant capacity to C.B. Industrial Engineering Ltd., 1 Mackintosh Lane, E9 6AB. Tel: 01-985 7057. (14 985 7057.

133

Classified

ARTICLES FOR SALE



Classified

VACUUM is our speciality, new and secondhand rotary pumps, dif-fusion outfits, accessories, coaters, etc. Silicone rubber or varnish out-gassing equipment from E40. V. N. Barrett (Sales) Ltd., 1 Mayo Road. Croydon. 01-684 9917. (24

FOR SALE. Heathkit receiver K/SB 303 in perfect order, £300. I. G. Hughes. 01-407 4411 Ext. 240. (5377)

COMPONENT BARGAHS. Full spec. 741 20p, 555 37p, 7447 decoders 58p, BD142 (Motorola 115W 40V) 25p. BC108 6p, Mullard polyesters, 50 mixed 1 & 2.2 microfarads 250V. tested but some cosmetic imperfec-tions so £1. Mixed electrolytics, 500 untested £1. Minimum order £1, s.a.e. for discounts and full list, add 40p p.p. for capacitors or 20p for rest. — R. Wardle 3 Erpingham Road, London SW15 1BE. (5393)

OSCILLOSCOPE. Dynamco D7100 1 x 2 and 1Y2 amplifiers, £185. — Carlisle 20776.

CLTV EQUIPMENT. Aston SPG1 sync pulse generator 170, vision mixer and effects unit. — Phone Carlisle 20776.

QUANTITY OF MARCONI SIGNAL GENERATORS. Type TF 1449, £25 each. Cash with order. Carriage forward. Contact Neil Brady. Ascot 23422. Office hours. (5369)

VALVES RADIO TV TRANSMIT-TING INDUSTRIAL 1936 to 1975, many obsolete types, list 20p s.a.e. for quotation. Postal export ser-vice. We wish to buy all types of valves new and boxed. Whole-salers, Dealers, etc., stocks pur-chased. Cox Radio (Sussex) Ltd., The Parade East Wittering, Sussex, West Wittering 2023. (5392)

QUANTITY OF MARCONI SIGNAL GENERATORS, type TF144G. £25 each. Cash with order. Carriage forward. — Contact Neil Broady. Ascot (Berks) 23422. Office hours. (5369)

100 MHz TWIN BEAM, dual time-base oscilloscope as new £450.00 o.n.o. Ring Bristol 294186 a.m. or Weston super Mare 412178 p.m. (5388)

TELEPRINTERS CREED. Envoy 5-Unit receive only in good working order in CABINETS. Tel Communi-cations Department 01-353 1515. (5408) (5498)

60 KHz MSF RUGBY RECEIVERS. BCD TIME-OF-DAY OUTPUT. High performance phase locked loop radio receiver. 5V operation with LED indication. Kit complete £9.50: assembled and tested unit £11.12 (prices include postage and V.A.T.) Also available low power receiver with signal and audio outputs. Send for details Toolex, Sherborne (4359) Dorset. (21 for deua Dorset.

SIGNAL GENERATOR M.I. TF867A 15 kHZ to 30MhZ. £90.00. — Tel Hedingham 60599. Tel

PRINTED CIRCUIT BOARDS. High quality, fast deliveries. — Photo-techniques, 11 Old Witney Road, Eynsham, Oxford. Tel. Oxford (5595) Eynsham, 03 (0865) 880645 (5525)

INSTRUMENT TURNSCREWS (SCREWDRIVERS). Precision made with hardened tool steel blades and brass bodies. Set of five blade sizes 0.8mm to 2.4mm, packed in strong plastic wallet. To prove BRITISH can still be BEST send only f1.35 (incl. V.A.T., P. & P.) to Dunbar Marketing. Stamford House, Stamford New Road, Altrin-cham, Ches. WAl4 1BL. (5529) TURNSCREWS INSTRUMENT

ARTICLES FOR SALE

134

VARIACS 240v I/P with driving motor. O/P 0 to '240v at 20 amps cont with 1/20v tap by Foster Elec 640. Veeders Counters 5 digit with reset coil 12/24v DC f1.30. Blower Motors small double ended 6 to 27v notor, 0/P 0 to 240v at 20 amps cont with 1120v tap by Foster Elec f40. Veeders Counters 5 digit with reset coil 12/24v DC f1.30. Blower Motors small double ended 6 to 27v DC new £3.60. H.F. Trans Tx type 70w 75 to 600 ohm in case new f3.40. Meter Unit dual aircraft type as 270ft 1 ma & 100-0-100Ua in same case 31 sq. f4.50. Spectrum Filter ,provides 20 channels in range 3 to 20Kc ea with its own o/p. use 20 pot cores, in box 61 sq. f4.30. Crystal Filters 10.7 Mc/s STC size 38 x 16 x 18mm 12Kc bw. f1.60. 30Kc bw. f1.30. New. Tape Decks with amps ex language lab equip. Type A with BSR deck type TD. 2 2 chan. amp with erase osc. mixer & o/p stage provision for rec & playback on both chan. two chan are mixed to give one o/p for phones. Units are complete except for P.U. req 24v DC smoothed for amps. with circ f9.50 also type B similar but valve circs req ext H.T. & L.T. with circ f6.50. Aerial System 8 element Yagi for use on Satellite chan 183.6Mc/s for use with 50 ohm coax N type termination. boom approx 11ft new in cases f21.60. Vidicon Tube standard 1in. type tested f9.60. Ind Unit small sector scan P.P.I. with P7 tube 44in dia with scan and focus coils in case 14in x 6in x 6in, needs ext cht f7.50. Radar Ass with 242 mag. Klystron. TR cells, balanced mixer. 715C. I.F. strip. etc with w.g. for X band f25. Marconi TF942 pulse scope, intended for high speed pulses, trig t.b. int cal marks, mains operated with circ f26, Trans Pria 120v 50c/s sec 34v at 60 amps supplied in pairs for 240v to give 34/120a or 68/70a f30 per pair. Selsyns 230v 50c/s power type f25 per pair. Goods are ex equip unless stated new. prices inc VAT and carr UK. A. H. Sup-plies, 122 Handsworth Road. Shef-field. S9. 4AE. Phone, 444278 (0742) (5501)

2788

LINSLEY-HOOD 75 watt amplifier interference suppression kit — re-duces effects of mains borne/rf interference and parasitic oscilla-tion, virtually eliminates click from filter switch and now contains com-ponents to reduce preamp noise (available separately). Full fitting instructions supplied — f1.35. Headphone socket kit, with instruc-tions, f1.45. Sescosem BDY56 f1.65. Motorola BD529 55p. BD530 55p. BF7879 25p. Inclusive prices. P & P 10p. All components brand new. guaranteed and despatched by re-turn. List SAE. I. G. Bowman (Dept WW), 59 Fowey Avenue. Tor-quay. S. Devon. (5499) LINSLEY-HOOD 75 watt amplifier

LABORATORY SWEEP CT 381 LABORATORY SWEEP GENERATOR SYSTEM for IF/RF alignment, 10KHZ - 33MHz com-prising PSU, generator, and scope, with handbook, spare PSU and scope, £85. Advance 7000 33 digit DPM. new. £15. Sealectroboard programming panels 24 x 32 matrix. with 60 diode pins, new. £15. Ad-ditional pins 10p each. Heathkit ± bildstate voltmeter IM 16 £12. — G3YLQ, Luton 25595. (5365) 381

DEMO DISCS

8958.

www.americapradiobistory.com

DAWE U.L.F. OSCILLATOR 0.01 Hz to 1Khz 90 degrees and ref phase O/P terminals £30. Lapmaster monochromatic light unit £25. Createch Complex ratio bridge to 1Khz 90 degrees and ref phase O/P terminals £30. Lapmaster monochromatic light unit £25. Gretsch Complex ratio bridge CRB B1 mint, 6 decades phase 4 real £300. Wayne Kerr Mod/Demod Unit SA400 £35. Wayne Kerr trans-fer function computer £200. Airmec 853 wave analyser 30khz to 30Mhz £65. Cossor motor driven oscillo-scope camera unit £60. Marconi D.F.M. T.F. 142E £25. Solartron Synchro test unit JM 555.2 £40. B.P.L. megohmeter RM175-LZ Mk 2 £30. Telequipment 33C Amp plug in unit £20. Polaroid oscilloscope camera, mint, £60. P.S.U.s A.P.T. fully stabilised 20V @ 10A Variable+ or -- 10%V £12, 10V @ 10A £10. Terms C.W.O. V.A.T. at 8%. S.A.E. for your electronic com-ponents hists -- ''Q' Services Electronic (Camberley) Ltd., 29 Lawford Crescent, Yateley, Cam-berley, Surrey (0252) 871048. (5366) Wireless World, June 1976

ARTICLES WANTED RACAL SA505 frequency counter, 7 digit DC-40 MHZ with adaptor, handbook, good condition, £20. Uitrasonic cleaner, solid state 60W Generator plus 2 tanks, new £40. Cathodeon BP4706/1 1.4 MHZ SSB filters, unused £5. Amplitude modu-lator TF 1102/1 £5. Wanted Philips LBB5000 pocket radio paging re-ceivers, G3YLQ Luton 25595. (5504). WANTED! all types of scrap and REDUNDANT **ELECTRONIC &** COMPUTER (5504) MATERIALS. with precious metal content **OSCILLOSCOPES** telequipment DC-15 MHz. 2 trace f150. Fairchild DC-25 MHz. 2 Trace 2 time base f270. Both with mianuals Wargrave TRANSISTORS (5503) & PRINTED **CIRCUIT BOARDS** STEREO CASSETTE MECHANISMS. Similar to those used in low-noise cassette deck WW May. Choice of side or top loading. Complete with heads and full technical data. Send S.A.E. Box. No. 5497. **TO COMPLETE** COMPUTERS The COMMERCIAL SMELTING & REFINING Co. Ltd. 171 FARRINGDON ROAD **PYE, GEC, ITT** mobile radio equip-ment for sale. New and second hand mobiles and base stations ex stock. Crystals 2 weeks delivery. Finglas mobile and base station antennas available ex. stock at very competitive prices. While you wait fitting service. Cash waiting for surplus r/t and test equipment. 01-680 1010. (5517) LONDON EC1R 3AL Tel. 01-837 1475. Cables: COMSMELT. EC1 Works: FLECKNEY. nr. LEICESTER (5116) ★ MINICOMPUTERS WE INVITE ENQUIRIES from any-where in the World. We have in stock several million carbon resis-tors ith 1, 1, and 1 watt. I million wire wound resistors 5 and 10 watt - 1 million capacitors - 1 million electrolytic condensers - 1 million transistors and diodes, thousands of potentiometers, and hosts of other components. Write, phone or call at our warehouse - Broadfields & Mayco Disposals Ltd., 21 Lodge Lane, N. Finchley, London. N.12. 01-445 0749, 445 2713. (5097) ★ PERIPHERALS ***** INSTRUMENTATION For fastest, best CASH offer, phone COMPUTER APPRECIATION odstone (088 384) 3106 WANTED, all types of communica-tions receivers and test equipment. Details to R. T. & I. Electronics Ltd., Ashville Rd., London, E.11. Ley 4986. (63 WATTMETERS. Four multirange models covering ranges from 60W to 3KW. Further details from E.M.S. 21 Mount Road, Benfleen, Essex. SS7 1HA. (5362) B-D ELECTRONICS offer prompt settlement for your surplus com-ponents. Our main field of interest is consumer electronics. Please telephone our Miss Hughes. Sandy (0767) 81616. (22 **REQUIRED** from Ministry of Defence and other sources Plessey models P.T.R. 371, also 691, 692 and 693. Please post fullest details to John F. Learney, 16 Pine Walk, Carshalton Beeches, Surrey. (5226) TELEQUIPMENT oscilloscope, dual beam, Model D43, Plug-in high gain y amplifiers. TV line and frame sync: 15 M/Cs bandwidth, Manual. sync: 15 M/CS bandwidth handal. Little used fillo. AVO valve tester Mk. 2, Manual, f70. E.H.T. trans-former, mains input, 15 K.V. centre tapped at 20 mA, Parmeko hermeti-cally sealed, as new. f20. — Tel. Erith (Kent) 30556. (5362) SURPLUS COMPONENTS, Equip-ment and Computer panels wanted for cash. Ring Southampton 772501, (16) WANTED. Agent to purchase Mono and Colour T.V's transistor radios, vacuum cleaners, washing mach-ines, cookers, etc. New and second-hand, Box No. 5328. TAPE RECORDING ETC. AVO VCM163 VALVE TESTER. Wormald 39 Greenside Lane, Cul-lingworth, West Yorkshire BD13 5AP. 0274-33466, Ext. 423 (Day) 053-58-2971 (evenings). (5515) **RECORDS MADE TO** ORDER VINYLITE LICENCE OFFERED MASTERS FOR RECORD COMPANIES PRESSINGS **LIGENCE CIFFERED ACOUSTICALLY ADJUSTABLE LOUDSPEAKERS.** We wish to appoint licensees to manufacture the world's first Monitor Loudspeaker with acoustic adjustabibility: the revolutionary Omal Ambionic TL6. It has no competition and its many unique features include a variable transmission line (patented) giving uncoloured sound reproduction of outstanding quality. For full details (Principals only) write to:---Managing Director, Omal Group Ltd. Omal House. North Circular Road. London, NW10 7UF, England. Single disc. 1 20, Mono or Stereo, delivery single disc. 1 20, Mono or Stereo, delivery 4 days from your tapes Quantity runs 25 to 1,000 records PRESSED IN VINYLITE IN OUR OWN PLANT Delivery 3-4 weeks Sleeves/Labels Finest quality NEUMANN STEREO/Mono Lathes We cut for many studios UK/OVERSEAS SAE list **DEROY RECORDS** PO Box 3, Hawk Street, Carnforth Lancs Tel: 2273 (82) NEW GRAM VALVES WANTED WE BUY new valves, transistors and clean new components, large or small quantities, all details, quotations by return. — Walton's, 55 Worcester St. Wolverhampton, (62) GLASGOW, Hi Fi, Cassette Decks, Tape Recorders, Video Equipment, always available we buy, sell and exchange for Hi Fi sets and photo-graphic equipment. VICTOR MORRIS Audio Visual Ltd., 340 Argyle Street, Glasgow, Gl, 8/10 Glassford Street, Glasgow, Gl, 8/10 Sauchiehall Street. Tele: 041-221 8958. (11 VALVES. Good prices. Types CV2797. CV2798, CV2792, CV2130, CV2131, CV345, CV450. Phone 021-373 4357. (5522



www.americanradiohistory.con



INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 123-135

| ' DACE | PAGE | PAGE. |
|---|---|--|
| FAGE C 24 DC | Cauld Advance I td 27 | De Marsh I als materiae I tel 15 |
| Aero Electronics Ltd 6, 24, 26 | Gould Advance Ltd. | Radford Laboratories Ltd. |
| Alben Engineering Co. Ltd | Grampian Reproducers Ltd 22 | Radio Component Specialists 109 |
| Alice (Stancoil) Ltd | Greenwood Electronics Ltd | Radio Shop, The 94 |
| Ambia International 120 | | Raindirk Ltd |
| Amont International | | Polfe P 106 |
| Antex Products Ltd | Harmsworth Townley & Co. Ltd. Readers Card | Raile, F |
| Arrow-Hart (Europe) Ltd. | Harris Electronics (London) Ltd 15, 20 | Rank Film Equipment |
| ASP | Hart Electronics 104 | R.C.S. Electronics 12 |
| Aspen Electronics I td | Hatfield Instruments Ltd 18 | R.E.W. Audio Visual Ltd 87 |
| Audia Eain 95 | Hatheit Instruments Etd. | Rotex |
| Audio Fall | Hayden Laboratories Ltd. | RST Valves I td 108 |
| Audix Ltd | Heath (Gloucester) Ltd 13 | R.J.T. Valves Etd. |
| Avo Ltd J | Henry's Radio Ltd 106 | |
| 10 | H/H Electronic 16 | |
| Barr & Stroud | | Samsons (Electronics) Ltd |
| Barrie Electronics Ltd | | S.C.S. Components 112 |
| Bentley Acoustic Corp. Ltd 111 | Icon Designs | Scopex Insts. Ltd |
| Rever Dynamics (Gt Britain) I td 23 | 1.P.L. Electronics Ltd 97 | Scott James (Flex Engineers) Ltd |
| B LL Component Eactors Ltd | Imtech Products Ltd 24 | Scott, Sames (Elex: Eligineers) Eta |
| B.H. Component ractors Ltd 116 117 | Industrial Tape Applications Ltd | Semiconductor Supplies Etd |
| BI-Pak Semiconductors Ltd 110, 117 | Integrav I td 90.91 | Service Irading Co. |
| Bi-Pre Pak Ltd 100 | Integrex Ltd | Servo & Electronics Sales Ltd. |
| Boss Industrial Mouldings Ltd 29 | | SGS-Ates (U.K.) Ltd |
| Brenell Eng | Kinnie Components Ltd | Shure Electronics Ltd Bound-in-insert |
| Rywood Electronics | | Sintel 107 |
| Sy wood Electromes to the state of the | | Sounderaft Flectronics I td 83 |
| Cambridge Learning 14 | Lan Electronics Ltd. | Sounderant Electronics Etd |
| Case Systems 28 | Leevers-Rich Equipment Ltd | Special Products Ltd 12 |
| Cateorian 94 | Levell Electronics ltd 1 | Strumech Eng. Ltd 10 |
| Chilteners I I ad | Levor Electronics Ltd | Sugden, J. E. & Co. Ltd |
| Chiltmead Ltd | Lingtond MEG Co. Ltd | Swanley Electronics Ltd |
| Cintec Ltd | Linsteau Mr G Co. Etd. 111111111111111111111111111111111111 | |
| Colomor (Electronics) Ltd 102 | Lloyd J. J. Instruments Etd. | |
| Combined Precision Components Ltd 88 | Lynx (Electronics) London Etd. | |
| Compor Electronics Ltd. | | Technomatic Ltd 113 |
| Computer Appreciation 86, 119 | Provide Table 9 | Tektronix (Equipment) Ltd 30 |
| Computer Appreciation | Macinnes Laboratories Ltd. | Teleprinter Equipment Ltd |
| Computer Sales & Service | Maplin Electronic Supplies | Teleradio Electronics 113 |
| | McLennan Eng. Ltd 14 | Thomson CSE |
| D.M.W. Associates (Electronics) Ltd. | Marconi Instruments Ltd Cover ii | Time Miero & Electronics |
| Dema Electronics International | Marshall A & Sons (London) Ltd | Time Micro & Electronics |
| Dolby Laboratories Inc 19 | Mille W 111 | Trampus Electronics |
| Dolby Noise Unit | Millis, W 122 | Turner Electronic Industries Ltd |
| Drake Philip Electronics Ltd | Modern Book Company 132 | T.O. Supplies (Teonex) 25 |
| Diake, I limp, Electronics Etd. Cover iii | Morhan Exporting | •• |
| Dymar Electronics Ltd. | Motorola Electronics Ltd | |
| D 1. T 4 | Multicore Solders Ltd Cover iv | 11 1 0 0 1 1 1 1 1 0 0 |
| Lagle International Ltd 16 | | United-Carr Supplies Ltd 32 |
| Electronic Brokers Ltd 114, 115, 136 | Nicholls F R 92 | |
| Electronics Weekly Loose insert | Nombrau I td | |
| Electrotime Ltd 101 | Noniblex Etd. | West Hyde Developments Ltd |
| Flectrovalue I td 93 | | Whitelow Electrical Radio Co. Ltd 12 |
| Electronic Windings (I dn) I td | Olean Electronics I td | Winterey Lieutital Radio Co. Edu |
| Electronic windings (Lun) Ltd | Olison Electronics Etd | Wilkinson, L. (Croydon) Ltd |
| EMI Sound & Vision Equipment Ltd | Orchard Electronics | Wilmot Breeden Electronics Ltd 21 |
| English Electric Valve Co. Ltd | | Wilmslow Audio 121 |
| Evershed & Vignoles Ltd 5 | P.B. Electronics I td 85 | Wireless World Circuit Designs 84 |
| | P.D. Lieutonius Liu | ······································ |
| Farnell Instruments Ltd | Powertran Electronics | |
| Fi-Comp Electronics 108 | Precision Petite Ltd 29 | 7 P. J. Anno Services Ltd 23, 104, 113 |
| Future Film Developments Ltd | Pulse Electronics Ltd 13 | Z. of I. Acto Scivices Ltu |
| Fuldo Electronic Labe I td | Pye Unicam 7 | Lettier (U.K.) Division 22 |
| ryide Electronic Labs. Etd | | |
| | | |

Printed in Great Britain by QB Ltd., Sheepen Road, Colchester and Published by the Proprietors IPC ELECTRICAL-ELECTRONIC PRESS LTD., Dorset House, Stamford St., London, SE1 9LU telephone 01-261 8000. Wireless World can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service, Ltd. Gordon & Gotch Ltd. SOUTH AFRICA: Central News Agency Ltd.: William Dawson & Sons (S.A.) Ltd. UNITED STATES: Eastern News Distributors Inc., 155 West 15th Street, New York, N.W.10011.

ww.americanradiobistory
'Phone-in Programme



When you can reach them. And they can reach you. Any time. You've got a Dymar system.

Computer controlled VHF radiotelephone network. Sounds great. The coming thing. At Dymar it's come! And that's the Dymar difference.

Dymar designs systems that take all the local conditions into account. Terrain. Geographical distribution of the labour and the customers available to the user. Emergency situation control. Channel congestion. The lot.

Dymar does it with common frequency coverage using quasisynchronous transmitters. With a CCIR compatible selective calling system. With automatic signal level selection. With computer control of signal routing.

Tomorrow's systems loday. It's what you'd expect from a company 100% devoted to the radiotelephone business ... and nothing else.

Discover the Dymar difference. Make contacting Dymar part of today's programme

DYMAR

the name in radiotelephone systems

Dymar Electronics Limited, Colonial Way, Radlett Road, Watford Herts, WD2 4LA, Tel, Watford 37321 Telex, 923035 Cables, Dymar Watford

WW-002 FOR FURTHER DETAILS

www.americanradiohistory.com

Multicore Solder Creams are oxide free!

Multicore's newest solder creams are designed specifically for hybrid microcircuits P.C.B's and critical component joints. Unlike ordinary creams – which suffer from the problem of oxide around each atomised solder powder particle – they're completely oxide-free. The advantage is faster soldering with clear flux residues and no solder globules.

The new range can be made in any quantity and with a very wide variety of soft solder alloys, fluxes, particle sizes and viscosities. They're suitable for screen printing, stencilling or application by automatic precision dispensers. Add to that the speed, simplicity, reliability and low application cost of solder creams in many operations and you have a product that takes the art of soldering one step further.

Multicore's solder cream can often be used instead of solder preforms. No tool costs are involved and inventories of individual shapes are avoided. The cream can often be applied more quickly and has more uniform flux content than preforms. But for those assemblies where preforms are preferred...

...don't forget Multicore preforms

These precision-made solder preforms come in virtually any size and shape. Rings, washers, discs, pellets and lengths of solder tape in most soft-solder alloys, with or without flux cores, are easily placed between the parts to be soldered.



Whether cream or preforms are used, just raise the temperature of the metal surfaces to around 50°C above the melting temperature of the solder. The solder cream or preform does the rest. Heating techniques can include gas flame, hot plate, oven conveyor, induction coils, resistance/electrode soldering, hot gas and infra-red.



Multicore Solders Limited,

Maylands Avenue, Hemel Hempstead, Herts. HP2 7EP Telephone: Hemel Hempstead 3636. Telex: 82363

Multicore Solders Ltd are Ministry of Defence Registered Contractors and on Qualified Products List QQ-S-571E of U.S. Defense Supply Agency for solder creams and preforms.

Solder