

THE
AUSTRALASIAN

NOVEMBER 10, 1938
VOL. 3 — NO. 7
PRICE, 1/-

Radio World


Registered at the G.P.O.,
Sydney, for transmission
by post as a periodical.



—See Page 8

- ASSEMBLING AND ALIGNING THE "1938 OUTDOOR PORTABLE FOUR": MORE
- ABOUT THE "1938 AMATEUR COMMUNICATIONS EIGHT": NINETEEN-RANGE
- COMBINATION VACUUM TUBE VOLTMETER & MULTI-METER: LATEST S.W. NEWS.

SEALED

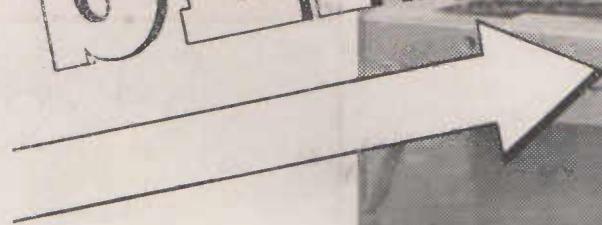

FOR

YOUR

PROTECTION

The Radiotron sealed carton guards every Radiotron from the factory to your set. It cannot be used to disguise a second-hand valve, ensuring that the valve you buy is factory fresh.

For better and brighter radio entertainment . . .

**REVALVE
WITH**

RADIOTRONS

NEW MICRO-SENSITIVE

AUSTRALIAN
GENERAL  ELECTRIC
UNITED

Sydney, Melbourne, Brisbane
Adelaide, Hobart

AMALGAMATED
WIRELESS  (A/SIA) LTD.

47 York Street, Sydney
167-169 Queen St., Melbourne

NATIONAL ELECTRICAL
& ENGINEERING CO. LTD.

Wellington
New Zealand

(Advertisement of Amalgamated Wireless Valve Co. Pty. Ltd.)

MICRO "ALL WAVE AUTOMATIC FIVE"

This is not just another radio receiver—look over its many features! All-wave coverage from 16 to 150 metres and 200 to 550 metres. Automatic tuning of six broadcast stations. Ultra-modern circuit employs an entirely new output tube. Attractive oval four-colour dial (dial shown is for descriptive purposes only). Dial is accurately calibrated, and all main shortwave bands clearly indicated.

Truly an ideal low-priced kit for the "ham," DX enthusiast or for a second set in the home.

Complete with valves and speaker . . . £11/18/6

Complete with speaker less valves . . . £9/17/6
(Freight paid to your nearest railway station)



The kit comes to you with the complete r.f. tuner, dial, gang condenser, and first tube socket ready wired and tested.

THE "MICRO" VIBRATOR POWER UNIT.

Special design allows for entirely hash-free operation on any battery receiver using 2, 4 or 6-volt valves. The new "Electronic" synchronous vibrator ensures long, trouble-free performance. Cut out expensive dry batteries now, and give your radio new life.

Complete Kit of Parts £4/1/6

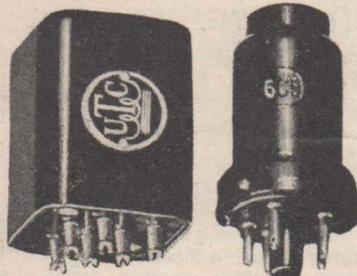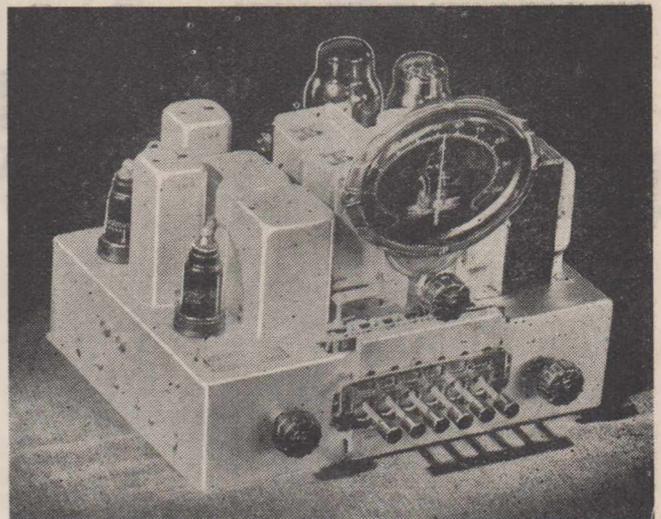Complete Kit, assembled and tested . . . £4/17/6



U.T.C. HIGH FIDELITY AUDIO UNITS.

Designed for broadcast and all quality amplifiers—the frequency range is flat from 30 to 20,000 cycles—series L.S., H.A. and—"A."

WRITE FOR FULL PARTICULARS. HEADPHONES.

FROST, definitely the most popular 'phones in N.Z. . . . 15/-

MICRO, high-grade English 'phones, used extensively in British Government departments, 18/6

British Post Office pattern, heavy brass morse keys. Here's the key you have tried hard to procure 52/6

"MEISSNER ALL-WAVE SEVEN."

Modern in every respect. Band

coverage 7.5 to 550 metres. Four colour dial; tone control, etc.

Complete kit with valves and speaker £19/10/-

HERE'S VALUE !

- Best quality electric jugs, 3 pint 27/6
- Speedee Toasters 18/6
- Speedee Jugs 21/6
- Spiral Indoor Aerial, with two insulators 1/9
- Enamelled Aerial Wire, 100ft. coil 4/9
- "Lektrite" Aerial, 100ft., 4/3
- Push-button Aerial Earth Switches 2/-
- Everything in Radio and Electrical sundries. Make up your order and post it—NOW!

MIKES FOR AMATEURS.

Now—a high-grade dynamic microphone for amateur or P.A. work. Frequency response 50 to 9000 cycles £5/5/-

ASTATIC, acorn model, T-3, crystal mike. Quality reproduction, ideal for dance band or studio work £6/10/-

ASTATIC, model D-104—the "hams" favourite £5/10/-


SHURE, model 70 SW, crystal, with modern desk stand . . . £6/10/-

U.T.C. AGAIN LEADS THE FIELD WITH TWO NEW SERIES TRANSFORMERS.

Series "R" transformers are designed for radio set replacement and manufacture. They are entirely universal and specially treated for long service under adverse humidity conditions. The range includes input, line, microphone, output, and many other types of transformers.

Series "S" transformers consist of a range of very attractive and efficient units for amateur and P.A. service. Varimatch modulation and driver transformers—universal output units to line and voice coil, and also power transformers and chokes.

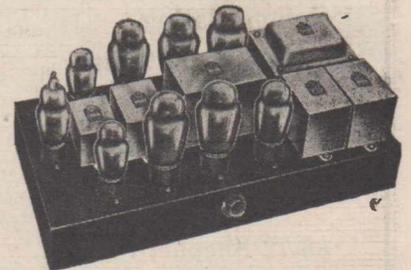U.T.C. manufacture the most complete range of transformers in the world. WRITE FOR DETAILS



COMPLETE AUDIO AMPLIFIERS

Ideally suited for all P.A. or modulator service. Power outputs from 15 to 120 watts. Provided with high and low gain input channels.

F. J. W. FEAR and CO.

31 WILLIS STREET, WELLINGTON, N.Z.

Telegrams "FEAR"

CHASSIS BY ACORN



IS SPECIFIED
EXCLUSIVELY FOR THE
**1938 OUTDOOR
PORTABLE FOUR**

Described in this issue.

Ensure correct specifications for your "1938 Outdoor Portable" chassis by specifying "CHASSIS BY ACORN"—as supplied to the designer's specifications for the original receiver.

★

*If its in Metal
we can make it !*

Our many years of experience guarantee finest workmanship & fastest service.

- Chassis. Valve and coil shields.
- Test equipment cases.
- Rack & panel assemblies
- Metal spinning, stamping, & deep drawn work.
- Die and tool making.
- Chrome, nickel, and cadmium plating.

'Phone or Write
for a Quotation

" ACORN "
PRESSED METAL
Pty. Ltd.
66-72 Shepherd Street,
CHIPPENDALE.

Cable address :
"Acornmetal,"
Sydney.

Tele. :
MJ 4681
(3 lines)

THE AUSTRALASIAN RADIO WORLD

Incorporating the
ALL-WAVE ALL-WORLD DX NEWS.

Managing Editor :
A. EARL READ, B.Sc.

Vol. 3

NOVEMBER, 1938.

No. 7.

CONTENTS :

Nineteen Range Combination Vacuum Tube Voltmeter And Multi-meter	3
17-Watt Amplifier Uses Push-Pull 6L6G's	8
Adding A Pentode Stage To The Atlas All-Waver	10
Aerial Beacon Erected On Ever Ready Building	12
Planning Radio Set Sensitivity	14
New Perth Transmitter Now On Air	16
Assembling And Wiring The 1938 Amateur Communications Eight	17
Assembling And Wiring The 1938 Outdoor Portable Four	21
CFGF Is British Empire's Most Northern Station	29
The "Ultra-Shorts" In Review	30
Coil-Winding Data For Philips EK2G Octode	31
Unique Home Recording Demonstration	32
What's New In Radio	34
Radio Book Reviews	36
All-Wave All-World DX News	37
Shortwave Review	38
Hourly Tuning Guide	43
DX News And Views	45


The "Australasian Radio World" is published monthly by Trade Publications Proprietary, Ltd., Editorial offices, 214 George Street, Sydney, N.S.W. Telephone BW 6577. Cable address: "Repress," Sydney. Advertisers please note that copy should reach office of publication by 14th of month preceding that specified for insertion.

Subscription rates : 1/- per copy, 10/6 per year (12 issues) post free to Australia and New Zealand. Subscribers in New Zealand can remit by Postal Note or Money Order.

desired is one volt, full scale, it was necessary to find a tube whose Eg Ip curve showed a change of 1 m.a. or more for a grid voltage change of one volt. Finally, the 6Q7 was decided upon.

"The fundamental circuit is shown

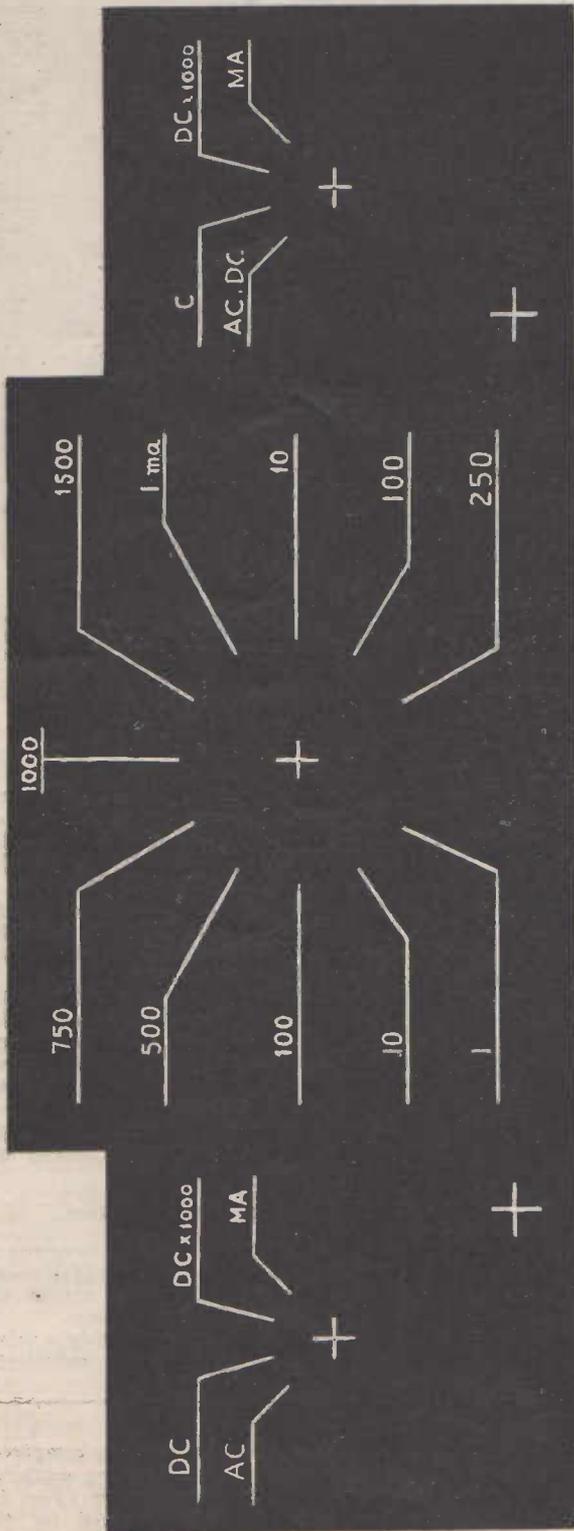in Fig. 1. It is seen that the diodes rectify and filter the a.c. voltage to be measured. The voltage peaks are then applied as extra negative volts on the grid of the triode amplifier. The resultant change in plate current causes an un-balance in the meter



A full-size reproduction of the scale developed specially for the instrument, drilling centres being indicated by crosses. The test prod selector switch "S1" is on the left. In the centre is "S2," meter resistor selector switch, while "S3" on the right is the meter selector switch. For measuring A.C. voltages, turn "S1" to "A.C." and "S3" to "A.C./D.C." For "D.C. x 100,000 ohms," "S1" is placed on "D.C." while "S3" remains on "A.C./D.C." For "D.C. x 1000 ohms," both "S1" and "S3" are placed on "D.C. x 1000." To measure current, "S1" and "S3" are both placed on "M.A." For each of the above measurements "S3" is turned to the appropriate voltage or current range. A block-maker's proof of this scale, taken on heavy art paper, will be supplied on request to readers forwarding 6d. to cover packing and postage. When glued in position, the scale can either be lacquered or a piece of clear celluloid, cut to shape, mounted over it to afford protection.

Nineteen-Range Combination V.T. Voltmeter And Multi-meter.

- 1 0-1 m.a. meter (Palec model 475)
- 2 single-bank switches, 2 pole, 8 position
- 1 three-bank switch, 11 contacts on each
- 1 octal socket
- 2 banana sockets
- 1 1.5v. bias cell
- 3 GR type knobs (1 large, 2 small)
- 1 engraved indicator plate (Palec)
- 1 aluminium chassis, 8½" x 8½" x 2", stamped and drilled to specifications
- 1 crackle-finished steel cabinet, 9" x 9" x 6"
- 1 steel bracket for valve socket, 2" x 2" with ½" flange
- 3 m.a. shunts, 10, 100, 250 m.a. (Palec) R12, 13, 14
- 1 black bakelite handle
- 2 test leads, "+" and "-" (Palec)
- 2 10,000 ohm potentiometers (R18 and R20)
- 1 type 6Q7 valve

FIXED CONDENSERS:

- 1 .02 mfd. fixed condenser
- 1 .25 " " "
- 1 .5 " " "

FIXED RESISTORS:

- 1 5,000 ohm 1-watt carbon (R16)
- 1 10,000 " " " (R17)
- 1 50,000 " " " (R19)
- 1 .5 megohm " " " (R15)
- 1 1 " " " (R1)

FIXED RESISTORS:

- (5% accuracy essential)
- 1 .1 megohm 1-watt carbon (R2)
- 1 .9 " " " (R3)
- 1 9 " " " (R4)
- 1 40 " " " (4-10 megohm) (R5)

(Above are for 100,000 ohms per volt ranges)

- 1 1,000 ohm 1-watt carbon (R6)
- 1 9,000 " " " (R7)
- 1 90,000 " " " (R8)
- 1 .4 megohm " " " (R9)
- 2 .5 " " " (R10, R11)

(Above are for 1,000 ohms per volt range)
Note: Palec multipliers, with an accuracy of 2%, are recommended for the above.)

MISCELLANEOUS:

- Nuts and bolts, hook-up wire, midget grid clip, solder lugs.
- (Power supply used was described in the July, 1938, "Radio World.")

bridge circuit, with a corresponding indication in the meter.

"With the proper choice of bias, the meter will read on the straight portion of the Eg Ip scale.

"With the necessary resistors for voltage dividing, almost any reasonable voltage may be measured, but since high voltages are usually associated with high power, the ordinary low resistance voltmeter section (D.C. x 1000) may be used. Therefore, a maximum scale of 500 volts was decided upon for the a.c./d.c. section.

Fig. 2 shows the circuit finally adopted; it will be seen that the a.c. voltage is rectified by the diodes paralleled in the 6Q7. The voltage peaks are then applied as extra negative bias on the grid of the triode amplifier, the resultant change in plate current causes an unbalance in the meter bridge circuit, with a corresponding indication in the meter.

With the proper choice of initial grid bias so as to insure operation on the straight section of the Eg Ip

Use A PALEC Kit Of Parts for the NINETEEN RANGE COMBINATION VACUUM TUBE VOLTMETER AND MULTI-METER


described this month

SPECIAL PALEC FOUNDATION KIT.

- 1—0.1 m.a. meter (Palec Model 475).
- 2—Single-bank switches, 2 pole, 8 position.
- 1—Three-bank switch, 11 contacts on each.
- 2—Banana sockets.
- 5—GR type knobs (1 large, 4 small).
- 1—Engraved indicator plate.
- 1—Aluminium chassis, 8½" x 8½" x 2", stamped and drilled to specifications.
- 1—Crackle-finished steel cabinet, 9" x 9" x 6".
- 1—Steel bracket for valve socket, 2" x 2" with ½" flange.
- 3—M.a. shunts, 10, 100, 250 m.a.
- 1—Black bakelite handle.
- 2—Test leads, "+" and "-".

PALEC VOLTAGE MULTIPLIERS (2% Accurate).

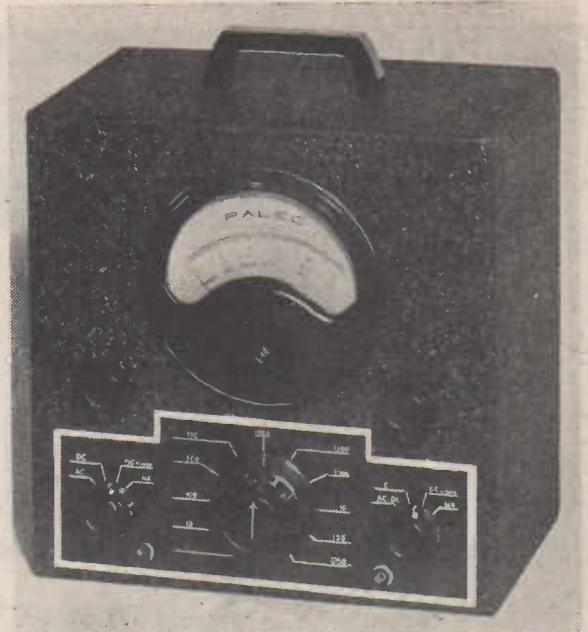- 1—.1 megohm 1-watt carbon.
 - 1—.9 " " "
 - 1—9 " " "
 - 1—40 " " " (4-10 megohm)
- (Above are for 100,000-ohms per volt ranges).
- 1— 1,000 ohm 1-watt carbon



- 1— 9,000 " " "
- 1—90,000 " " "
- 1—.4 megohm " " "
- 2—.5 " " "

(Above are for 1,000 ohms per volt range.)

Write for our special price for the above Foundation Kit, or for the complete kit of parts as listed on page 4 of this issue.


PALEC TEST EQUIPMENT ENSURES FASTEST, SUREST SERVICING ★ USERS REAP RICHEST REWARDS



Palec Model "CM" Multi-tester, which measures D.C., A.C. and output volts, decibels, mills., ohms, and megohms capacity, inductance, impedance and a.c. voltages.



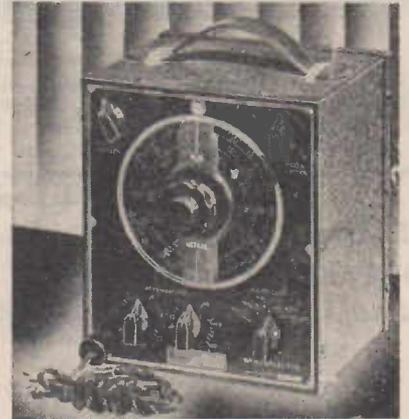Palec Model "VCT" Valve and Circuit Tester, which enables complete valve and circuit analysis. Special country model "VCT" is available, operating either from A.C. mains or six-volt accumulator.



Palec Model "DE" A.C.-Operated Test Oscillator, with vernier direct-reading dial calibrated in k.c. and metres. Has five ranges covering from 150 k.c. to 1600 k.c. Model "DR" is for battery operation.

Terms Available.

Write now for new, sixteen-page PALEC Catalogue—Sent Post Free by return mail.

The PATON ELECTRICAL PROPRIETARY LTD.

90 Victoria Street, Ashfield, Sydney. Phone: UA 1960-1982.


DISTRIBUTORS:

Sydney: Leading Distributors
Melbourne: Lawrence and Hanson Electrical Co. Ltd.
Homecrafts Ltd., 211 Swanston St., Melbourne.



DISTRIBUTORS:

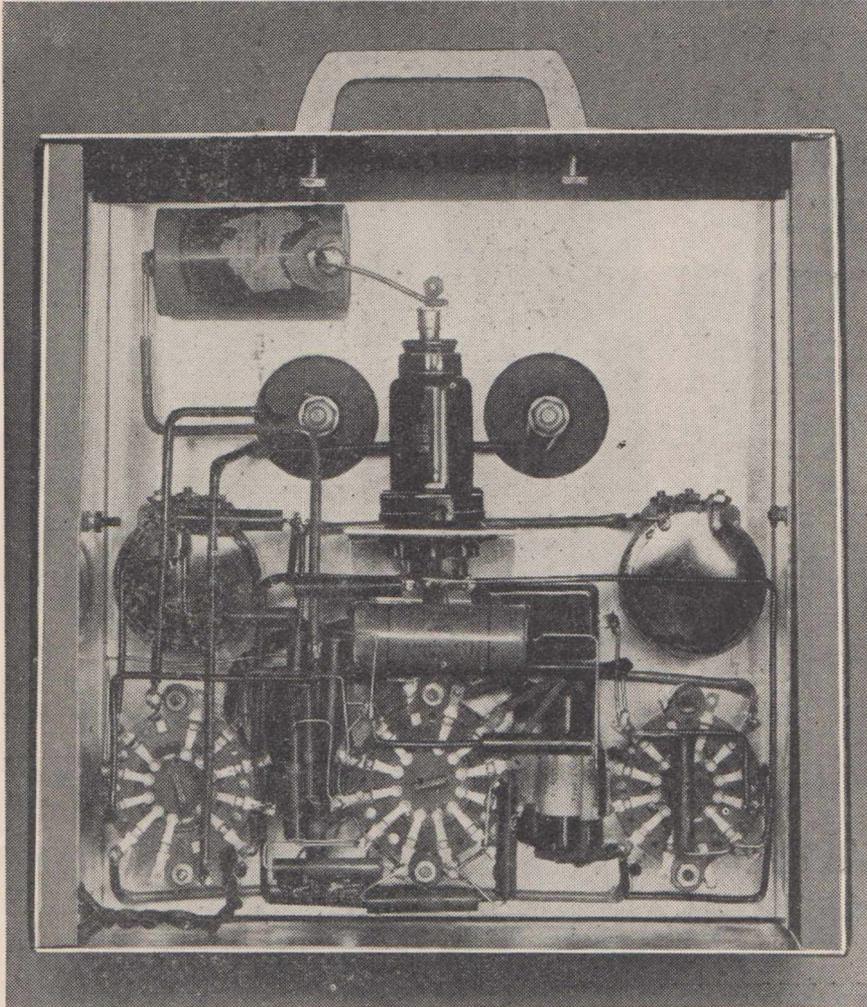Brisbane: Lawrence and Hanson Electrical Co. Ltd.
Adelaide: Newton, McLaren, Ltd.
New Zealand: The Electric Lamp House Ltd., Wellington.
Perth: Carlyle & Co



This rear view of the completed instrument illustrates the method of assembly on the vertical aluminium chassis used. In this view, the test prod selector switch is on the right, meter resistor selector switch in centre, and meter selector switch on the left.

curve, and in selecting the proper value of bridge balance resistors, the meter will indicate exactly 1 m.a. for an applied peak potential of one volt a.c. or d.c.

The writer has always felt that any instrument worth building is worth building well, particularly in the case of a V.T.V.M., which is depended on for its accuracy. So considerable care was taken to insure that all resistors were nearly exact in value, or at the very most having a 5% tolerance.

In the circuit diagram, the test prod selector switch "S1" is on the left, meter resistor selector switch "S2" in centre, and meter selector switch "S3" on the right. These positions are the same for the three lower controls shown in the front view of the instrument. though, of course, they are reversed in the rear view which indicates the location of components.

Low Resistance Wiring Essential.

The layout adopted approximates the ideal, for all vital leads are kept short. A word here in reference to the m.a. selector section might be in order. All leads from "S1" to "S3" and to the meter should be of heavy wire, because on the 1 m.a. scale particularly, any resistance will affect full scale deflection. In the instrument illustrated, 12-gauge tinned copper wire was used.

The bias cell is mounted near the grid cap of the 6Q7, and all resistors for all ranges are grouped round their respective selector switches.

The entire unit is enclosed in a cabinet measuring 9" x 9" x 6". It is intended to standardise with other instruments in this series, and is crackle-lacquered for a fine finish.

Installation of the unit in a metal

Make sure of
maximum efficiency
and longest life—

ADOPT AS YOUR
STANDARD—

Mullard

M A S T E R

RADIOVALVES

MULLARD (AUST.) PTY. LTD., 26-30 CLARENCE STREET, SYDNEY. TELEPHONE B 7446 (3 lines)

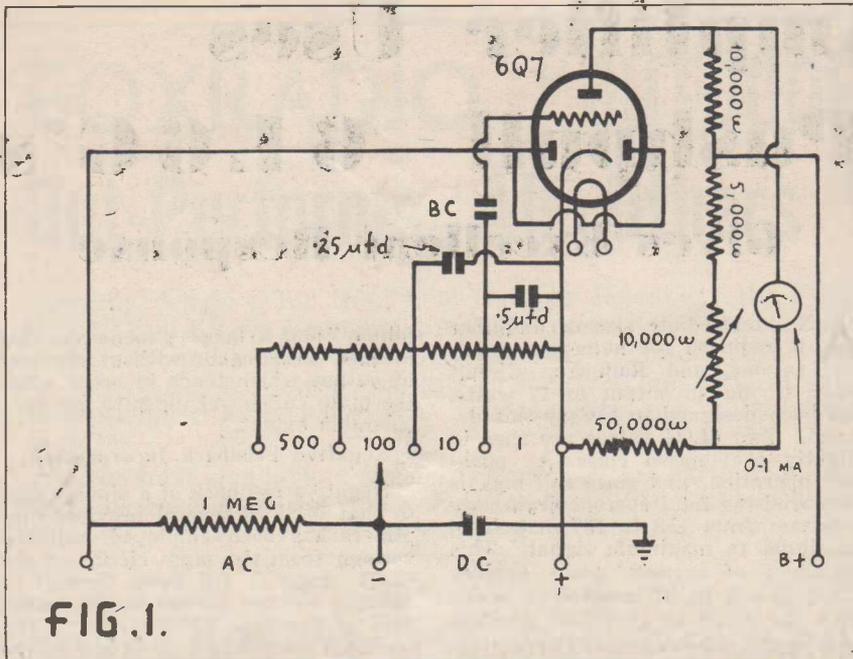


FIG. 1.

Fig. 1.—This diagram (reprinted from the August issue) shows the fundamental circuit used. The diodes rectify the A.C. voltage to be measured, the voltage peaks being then applied as extra negative volts on the grid of the triode amplifier.

cabinet is a desirable feature, and will serve to prevent stray electrical fields upsetting the balance of meter, particularly on the 1-volt a.c. range.

The Three Switches.

The selector banks for the prods and meter (S1 & S3) are 2 pole-8 position single-bank units, a fifth and sixth position being available for any future refinements which may be added. The centre switch is a 1-pole 11-position 3-bank, of which first bank nearest the front panel is for the a.c. d.c. 100,000 ohms per volt range, next bank for m.a. ranges, and third or outer bank for d.c. x 1000 ranges.

The chassis is of the vertical type and is 8½" x 8½" x 2". Positions for all switches and test prods can be punched and drilled through the template supplied for panel mounting. The two rheostats are in line with "S1" and "S3," and are 2½ inches above them.

Calibration Procedure.

Adjustment and calibration of the instrument is extremely easy, and with reasonable care should remain permanent for an indefinite period, although if precise measurements are to be made at any time it is easy to re-calibrate.

To adjust the instrument, throw switch "S3" to calibrate ("C" as indicated on panel) and adjust "R20" until meter reads 250v. or mid scale. Be careful to allow sufficient leeway on "R20" either way for final ad-

justment. By throwing "S3" to "C," it throws "R15" across the power supply, and since the meter requires only .5 mill. in that position, the potential applied to the bridge circuit will be from 4 to 5 volts more when thrown to a.c. d.c. positions on the same switch.

With "S3" on a.c. d.c. and "S1" on d.c. x 100,000, put selector switch "S2" on 1-volt tap and bring meter needle to zero by adjusting R18. Then apply 1 volt d.c. to the input terminals, when the 0.1 milliammeter should read exactly 1 m.a., or full scale. If it does not, juggling both "R19" and "R17" should bring the desired result.

It is not necessary to spend a great deal of time on them, however, because when meter reads within a few per cent. of full scale, juggling "R18" and "R20" will take care of the discrepancy. On the a.c. 1-volt scale, it will probably be found that the meter will give a substantial scale indication when the input terminals are shorted.

This is unavoidable, and may be compensated for when a.c. readings are made.

The a.c. ranges are peak volts, and a scale indicating r.m.s. values should be drawn for quick determination.

The metal case should be grounded, but not to negative return of instrument, as this connects to the positive input terminal and complication might arise if the metal case is made 500 volts positive.

Check THESE POINTS BEFORE YOU BUY MICA CONDENSERS

SAFETY FACTOR

Will they stand up under adverse operating conditions? To ensure complete reliability, every Simplex condenser is tested on 1000 volts A.C. and D.C.

INSULATION

Are they moisture proof? Simplex moulded condensers are designed specially to meet Australian conditions, and are triple-sealed against humidity.

CONTACTS

Will the contacts give a permanent and positive connection? Tinned copper lugs with one-piece electrical contact in Simplex condensers.

ACCURACY

Every Simplex condenser is triple-tested for highest accuracy. Type S/M, capacities from .000005 to .01 mfd. Type P/T (Pigtails) measuring only ½" x ⅝"—capacity range .000005 to .002 mfd.

SIMPLEX CONDENSERS

"FAVoured BY FAMOUS FACTORIES" Manufactured by Simplex Products Pty. Ltd., 716 Parramatta Rd., Petersham, N.S.W.

Phone LM 5615. AGENTS IN ALL STATES.

17-Watt Amplifier Uses Pushpull 6L6G's Gives Excellent Response

The Front Cover.

This month's front cover photograph shows a draughtsman attached to the engineering department of the A.W.A. receiver factory, finalising plans for the manufacture of a Radiola chassis. The outcome of many months of painstaking work in the laboratory is the completion of the "master" chassis, which, together with comprehensive constructional details, is passed on to the production engineers, who carefully plan every phase of construction, and supervise the manufacture of machine tools. Complete plans for the assembly of every Radiola model are drawn up, to ensure that every process of manufacture is carried out with the utmost precision.


AN intermediate size amplifier is required for numerous applications, and Radiotron Circuit A146, giving an output of 17 watts, has been designed to satisfy this demand. Two 6L6G valves are used in slightly over-biased class A, push-pull operation, and since self-bias is employed the total current drain only increases from 158 to 167 m.a. from no signal to maximum signal. This constancy of current drain enables the field coil to be inserted in series with the filter to give the greatest economy in components. Alternatively, if it is desired to operate the am-

plifier from a large genemotor, this is quite practicable without the loss of output which tends to occur when the plate current changes to any considerable extent.

Negative Feedback Incorporated.

Negative feedback of a similar kind to that used in several previous amplifiers has been employed, and the voltage from the plate circuit of the 6L6G stage is fed back through a suitable voltage divider to the screen grid of the first 6J7G stage. The feedback percentage is adjusted so

(Continued on page 48.)

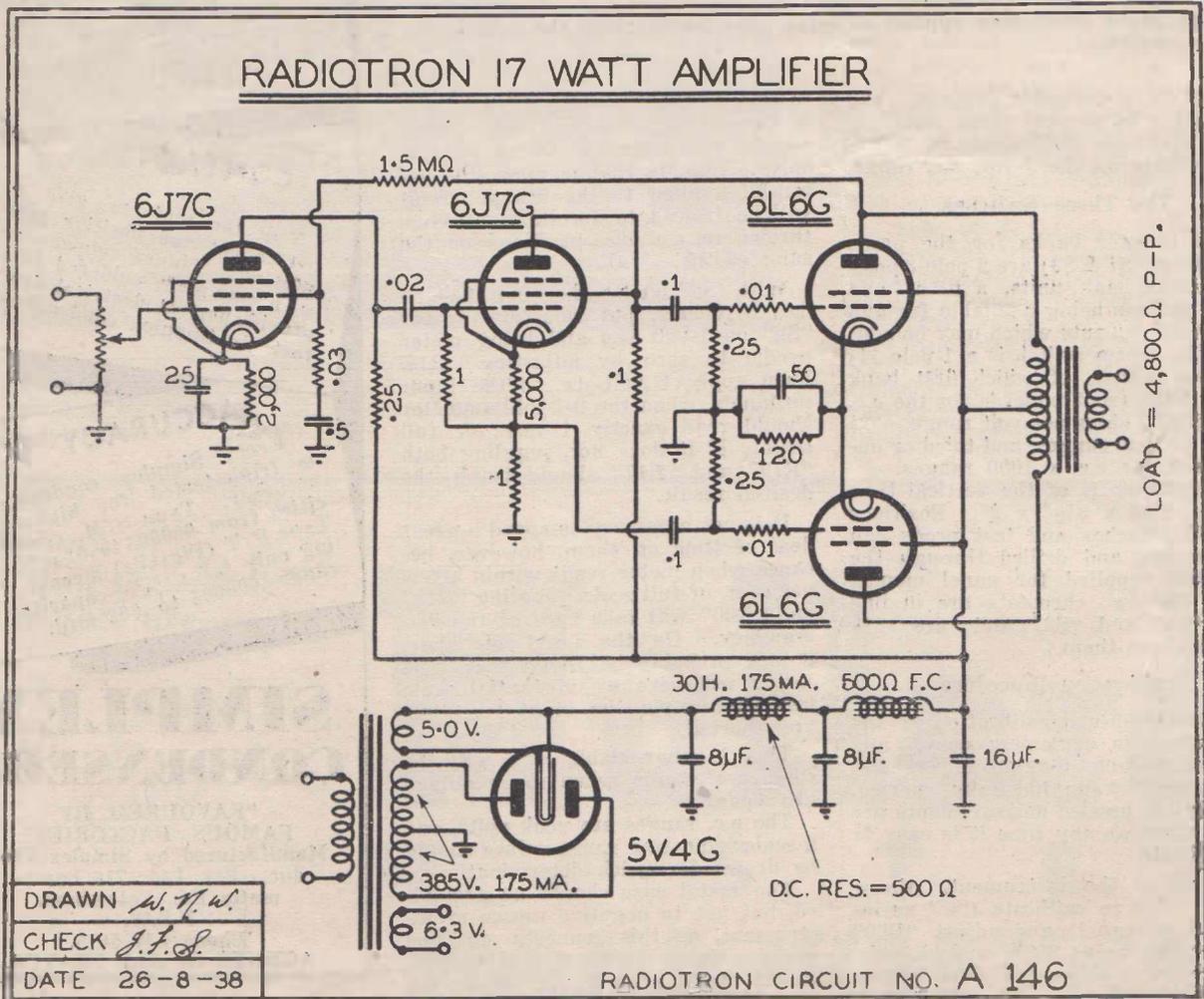


DRAWN	<i>A. F. W.</i>
CHECK	<i>J. F. S.</i>
DATE	26-8-38

FOXRADIO "OUTDOOR PORTABLE" Out-Performs All Others !


Specially designed for the "1938 Outdoor Portable," the FOX-RADIO Coil Kit we recommend for this receiver gives unbeatable sensitivity and perfect tracking. As well, this new coil kit can be substituted for lower gain kits in the 1936 and 1937 models. Exceptionally high gain with full stability are outstanding features.

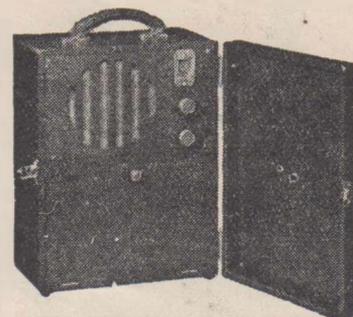We also have available a special complete kit of parts including carrying case, batteries and valves for the "1938 Outdoor Portable Four." Every part guaranteed of highest quality and exactly to the designer's specifications.



Don't buy before writing for our Special Complete Kit Price
—Sent Post Free by return mail

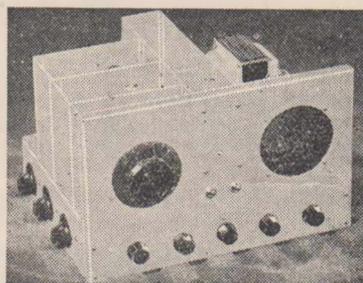FOXRADIO KIT FOR "1938 COMMUNICATIONS EIGHT"



The 1938 version of the most popular amateur communications type receiver ever featured in an Australian magazine, the "1938 Amateur Communications Eight" incorporates many new and exclusive features. Two i.f. stages are used in the latest model, employing three iron-cored i.f. transformers. Other new features include optional a.v.c. and the latest high-gain 6AG-6G output pentode.


WRITE FOR OUR DETAILED PRICE LIST.

Build the "ATLAS ALL-WAVER" with our special FOXRADIO ADD-A-VALVE KIT

Elsewhere in this issue will be found a further constructional article on the "Atlas All-Waver," outlining the method of adding a high-gain economy output pentode.

We have prepared three special kit prices for this receiver—for the single-valve model, and covering the parts required to add the r.f. and output pentode stages. Price of the latter two will apply, even if purchased in a year's time.

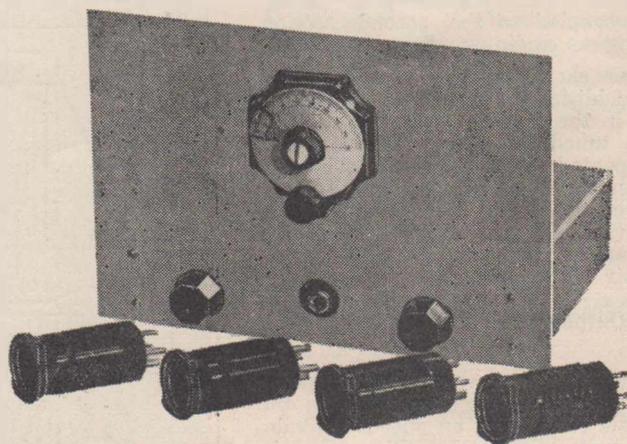- FASTEST SERVICE
- LOWEST PRICES
- HIGHEST QUALITY




Detailed Quotes On Any Of The Above Receivers Sent Free by Return Mail.

FOX & MacGILLYCUDDY Ltd.

MERINO HOUSE, 57 YORK ST., SYDNEY.

Tel.: B 2409.

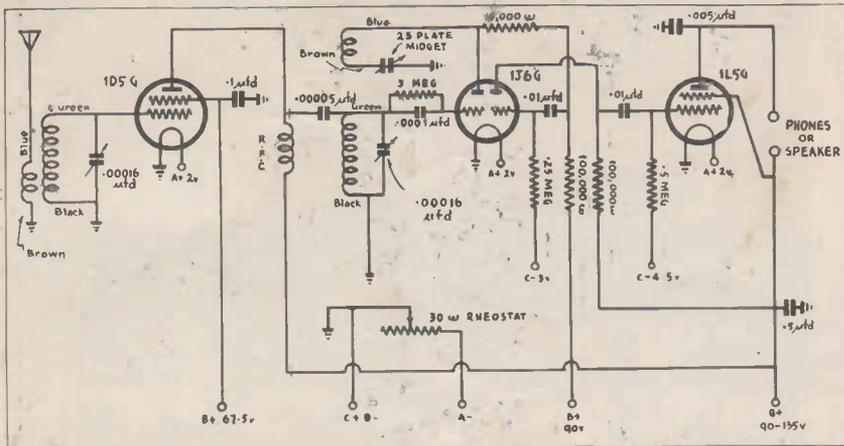

The circuit of the three-valve model, showing the method of adding a resistance-coupled output pentode stage to give speaker operation.


diagrams. The third "C" battery lead is added to the two already present in the set, and passes with them through the rear wall of the chassis via a rubber grommet. This is the "C-4.5v." lead supplying bias to the 1L5G.

World-Wide Reception On Speaker.

In its final three-valve form, the "Atlas All-Waver" will give speaker reception from several dozen broadcast stations, as well as the main shortwave stations throughout the world, provided, of course, that a rea-

sonably efficient aerial and earth system is used.

If desired, the lower right-hand control shown in the front view on the opposite page can be made an audio volume control. To do this, the .5-megohm 1L5G grid resistor should be replaced by a carbon potentiometer of equivalent value. The two outer terminals connect, one to one side of the .01 mfd. audio coupling condenser, and the other to C-4.5 volts. The moving arm is then taken to the 1L5G grid.

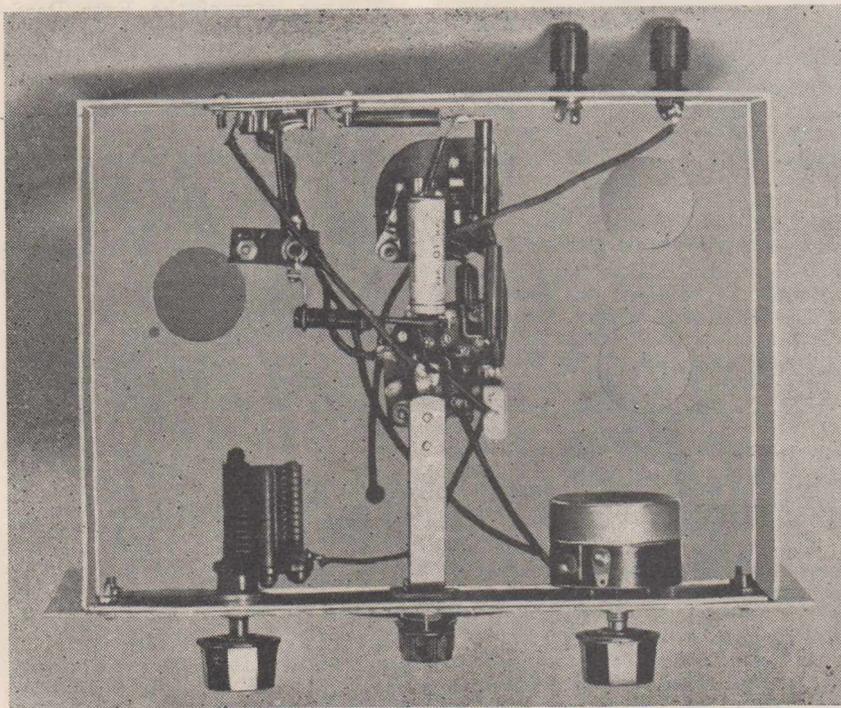

This under-chassis view of the one-valve model shows the extreme simplicity of the wiring. Note the holes already drilled in the chassis to accommodate sockets for the r.f. and output pentode valves, and the coil for the r.f. stage.



TODAY, when most other radio and electrical wholesale houses seem to think more of making you feel at home rather than making you a pleased customer, we still stick to the same sound lines that have made thousands say we are jolly good people with whom to deal. Snappy service . . . the pick of the best products . . . pleasingly reasonable prices . . . a large stock . . . a willing staff . . . and a handy position in the centre of the city!

If you want your money to go a long way, get your next radio and electrical requirements from

Martin de Launay Pty. Ltd.

Cr. Clarence & Drutt Sts., Sydney
M 4268 (4 Lines)


Cr. King & Darby Sts., Newcastle
New. 959 (2 Lines)

86 Keira St., Wollongong
Woll. 681

TELEGRAMS:

"MARTINDEL," SYDNEY & NEWCASTLE

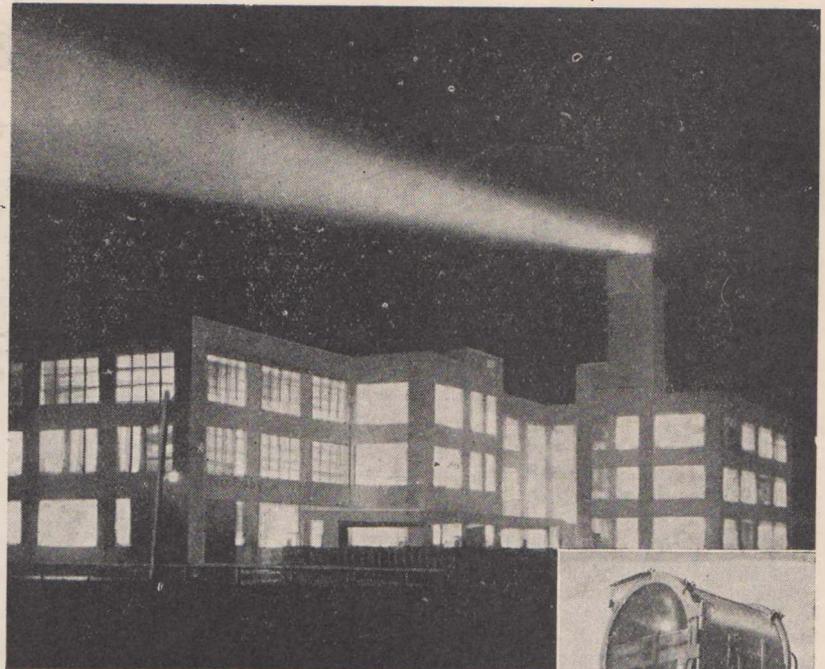Aerial Beacon Erected On Ever Ready Building



Million Candle-Power Rotating Beam Will Guide Pilots To Mascot Aerodrome . . .

THE erection of a new airway light for Sydney has been completed by the Civil Aviation Department, the site chosen being the tower of the Ever Ready Company's factory in Harcourt Parade, Rosebery.

The Civil Aviation Board, after considerable negotiations, accepted the offer of the Ever Ready Company to place at their disposal the large tower which is a feature of the building, and which rises ninety feet from the ground. The new airway light is of the rotating type, and its purpose is to indicate to pilots flying at night a given point on their route. Although at this stage no official tests have been carried out, it is expected that on a clear night the light will be visible roughly eighty miles away. This means that it would be picked up by pilots as far north as Newcastle, and would be used as their direction guide until Sydney is reached, and the flashing light at Mascot aerodrome sighted.

Is Automatic In Operation.

This new airway light is automatic in operation and will function continuously from sunset to sunrise. It will be an invaluable guide to all night flyers, and in particular, to the many commercial services such as Airlines of Australia, Australian National Airways and Ansett Airways.

These companies operate services between Brisbane, Melbourne, Adelaide and Sydney, and their planes are scheduled to reach Mascot Airport at times varying from 5.40 to 6.45 p.m., a period during which, for many months of the year, it is dark, and an airway light is vitally necessary. In addition, there is the air service from New Guinea, overseas services and no doubt many other subsidiary services which will directly benefit as a result of the erection of this airway light.

The light has been erected on 10-foot supports mounted on the summit of the Ever Ready Company's tower, and thus will function precisely 100 feet from the ground level.

It was constructed by the British General Electric Company, and con-

A night view of the Ever Ready factory and tower on which has been erected the million candle-power rotating beacon shown in the inset.

sists of a 1500-watt concentrated filament lamp used with a 24-inch diameter parabolic mirror which produces a beam of 1,000,000 c.p. A deflector mounted on the front glass of the housing directs portion of the beam upwards so that a pilot flying high in the vicinity will not lose its signal. Of the rotating type, the beacon revolves once in 10 seconds, a ¼ h.p. motor mounted in the base supplying the power. The flash of the beam is about ¼ second.

In the event of the failure of the lamp, an automatic changing device comes into operation and swings a new lamp into the correct position. A visual and audible alarm is then operated by the changing device, to warn the maintenance engineer of the failure of the lamp.

The instalment of beacons is but the first step for the equipment of aerodromes for night flying. Ultimately floodlights, wind direction indicators and boundary lights will be brought into use, thus bringing Australian aerodromes into line with the best in the world.

"International Six" Beats 'Em All!

I have built the "1937 International Six" as described in the issue of April 1, 1937, of "Radio World," and have received very fine results as regards tone, sensitivity and selectivity. It is the best receiver I have built and beats any I have heard. I also like your magazine very much.—C. Statham, Market Lane, Ipswich, Queensland.

"...WILL YOU
CALL AND FIX
MY RADIO?"

IS THAT CALL
ON YOUR PHONE ?

DELTA MODEL D 1503

1. COMPLETE VALVE TESTING (American and continental valves). (Emission Method.)
 2. SET ANALYSIS (A.C.-D.C. Voltage, D.C. Milliampers and ohms).
 3. CONDENSER TESTER.
- Final Analysis multimeter:
- Combines in one instrument the equivalent of eight separate units.
 - Complete tests for all valves by the approved emission method.
 - Separate Diode test.
 - Neon Short Test, detects slightest leakages.
 - Electrolytic Condenser Test.
 - Paper Condenser Test (for shorts and opens).
 - D.C. Voltmeter, 10-50-250-1000 Volts at 1000 ohms per volt.
 - A.C. Voltmeter, 10-50-250-1000 Volts.
 - D.C. Milliammeter, 1-10-50-250.
 - Ohmmeter, 0.2-10 megohms in three ranges—0.2-500 ohms, 0-1 megohm, 0-10 megohms.
 - Line Voltage adjustment.
 - Attractive, durable, black, silver and red etched panel.
 - Triplett Model 426 D.C. Instrument, square De Luxe case, 4 1/2 in. x 4 1/2 in.
 - Portable leatherette covered case, 15 in. x 9 in. x 6 1/2 in., sturdily constructed.
 - Test leads, prods, alligator clips, 3 core A.C. supply leads and full instructions.

PRICE £16/10/-



The chances are with you if you are equipped with DELTA INSTRUMENTS

Many radio listeners make an ailing radio receiver do under ordinary circumstances, but the Melbourne Cup and other important events start the 'phone ringing with service calls. Are you ready? Can you service them properly, quickly, AND PROFITABLY?

If you want your 'phone to start and KEEP ringing with service calls, equip and modernise with DELTA Precision Built Instruments. Illustrated catalogue sent FREE on request.

W.G. WATSON & Co. Pty. Ltd.

279 Clarence St., Sydney.
31 Hunter St., Newcastle.

398 Post Office Place, Melb.
91A Currie St., Adelaide.

And at Perth, Hobart and Launceston.



Mr. T. P. Court.

Planning Radio Set Sensitivity

Sensitivity is a major consideration in radio receiver design. In the article below the author explains the meaning of the term, and discusses the factors governing the selection of a suitable sensitivity for a modern receiver.

By T. P. COURT,

M.I.R.E. (AUST.), A.M.I.R.E. (U.S.A.).

Chief Engineer Standard Telephones & Cables (A/sia) Pty. Ltd.

THE term sensitivity would appear to be greatly misunderstood in its full application to a radio receiver.

It may be defined as the measure of ability to receive distant signals while converting them to intelligible sound.

Sensitivity can be regarded as the amplifying ability of the radio frequency amplifier. The "reaching out" qualities of a receiver are completely dependent on amplification before detection. In the case of a super-heterodyne, the intermediate frequency amplifier is considered as part of radio frequency system. The part played by the audio amplifier in overall sensitivity cannot be overlooked, but high audio gain cannot compensate for lack of radio gain.

In the precise measurement of sensitivity certain conditions are always assumed. In fact, the statement of sensitivity in scientific terms merely serves as a basis for comparison.

The term of measurement used is microvolts per metre, and the actual measurement is made with a signal generator which is very carefully shielded so that no radio frequency energy can escape except through the desired outlet. The signal generator employs a potentiometer of elaborate design which permits very close adjustment of voltage. Usually the voltage from the generator can be adjusted from about one volt to about one millionth of a volt, i.e., a micro-

volt. This voltage is led to the aerial terminal of the receiver through a dummy aerial.

A dummy antenna, by the way, is supposed to behave in the same way as an aerial approximately four metres long. It comprises resistance, capacity and inductance so proportioned as to have even characteristics throughout the broadcast wave band. This dummy is not used solely for measurement purposes, as the aerial circuit trimmer adjustment is made with the dummy aerial connected.

Thus, although this aerial circuit adjustment may be made very accurately, it would not hold if the receiver were connected to an aerial proper of very different characteristics. Indeed, many modern receivers are used with indoor aerials whose qualities are far different from the dummy on which initial adjustment was made. The sensitivity of such a receiver suffers through incorrect adjustment.

However, the use of the dummy aerial is justified in the vast majority of cases, and sensitivity measured through it is a fairly reliable index to the performance of a receiver.

Sensitivity Requirements For Modern Receivers.

The actual sensitivity required for effective reception in any location depends largely on the nature of the terrain, but it is fairly safe to say that in the more densely populated States, country receivers of a sensitivity higher than 10 microvolts will be satisfactory. So far as metropoli-

tan areas are concerned, a sensitivity of 50 to 75 microvolts is adequate for interstate reception. In this latter case it is fairly safe to assume that unless a transmitter lays down a signal of at least 50 microvolts it is not worth hearing, owing to parasitic noises which are usually encountered. Daylight reception in suburban areas is not practical owing to absorption effects.

However, it is quite a simple matter to build sets to any requisite degree of sensitivity at broadcast frequencies, so the average set for long distance listening usually has a sensitivity of 5 microvolts or better. This higher sensitivity may be used to great advantage in the country, as there is little or no inductive interference.

It is usually agreed that a sensitivity of about 2 microvolts represents the practical limit, as the inherent noise in a receiver presents a virtually insoluble problem so far as commercial broadcast sets are concerned. Further, if the signals from the broadcast station are so weak as to demand this sensitivity, usually they are almost unintelligible.

Sensitivity Can Be Too High.

The days of the highly sensitive receiver should be numbered. No advantage accrues from high sensitivity where it is not essential, as under certain conditions the operation of the automatic volume control can cause considerable distortion. Further, such

(Continued on page 33.)

Superb Performance! Unbeatable Value!

Are yours with a **Custom-Built**

Precision Radio "1938 Outdoor Portable."

COMPLETELY ASSEMBLED, ALIGNED &
AIR - TESTED, WITH VALVES & BAT-
TERIES, READY TO SWITCH ON


£ 14-14-0

(Including Royalty Plate)

**FINEST VALUE EVER OFFERED ★ SPECIAL
LOW INTRODUCTORY KIT PRICES CANNOT
BE REPEATED**

Our 1938 version of the "Outdoor Portable" is the finest receiver of its kind on the market to-day, regardless of price. Using only the best of components throughout, every receiver is assembled and wired by experts, and must pass the most stringent of performance tests before it is released. Also available is a special complete kit of parts, for those who prefer to do their own assembling.

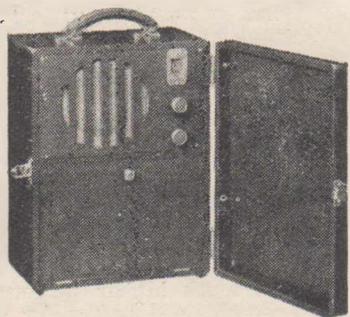WRITE FOR FULL DETAILS, INCLUDING OUR SPECIAL LOW INTRODUCTORY KIT PRICE



NEW PRECISION RADIO COIL KIT OUT-PERFORMS ALL OTHERS

Specially designed to specifications developed in our Laboratory for the "Outdoor Portable," the secret of this receiver's performance lies in the new PRECISION RADIO Coil Kit, which gives unbeatable sensitivity and perfect tracking.

Special introductory kit price (aerial and oscillator coils, three Litz-wound i.f. transformers, and padder) 30/-

We Maintain Hundreds Of Pounds Worth Of Laboratory Test Equipment ★ Special Service To Set-Builders

We maintain hundreds of pounds worth of latest test equipment to ensure rapid and accurate servicing. Receivers of all types thoroughly checked over and aligned for a moderate charge.

Highest quality components are used, sup-

plied at moderate prices. TRY US FOR YOUR NEXT QUOTE. Country readers are invited to take advantage of our special Buying Service, through which we can locate and purchase for you both standard and non-standard parts and equipment.

PRECISION
-- **RADIO** --

L. T. MARTIN, M. Inst. R.E. (Aust.),
20 Carrington Street North,
HOMEBUSH, SYDNEY.
'Phone :: UM 7858.

New Perth Transmitter Now On Air

Technical Details Of 1 K.W. Plant Installed By S. T. C.

THE new unit of the national broadcasting network recently installed in the Telephone Exchange Building in Perth represents the latest developments in broadcast engineering.

The equipment, which was designed and built in Australia by Standard Telephones and Cables Pty. Ltd., Sydney, to the order of the Postmaster-General's Department, incorporates several new features. The full power of the transmitter is 1 kilowatt, capable of 100% linear modulation, but the equipment will be operated initially at reduced power on 500 watts.

Is Air-Cooled Throughout.

The transmitter is exceedingly compact, being housed in two small, totally-enclosed cabinets.

Air cooling is used throughout. The final stage of the transmitter employs one or two S.T.C. type 4279-A valves, according to the power output. These are, incidentally, the largest air-cooled valves of their type manufactured.

Excellent Fidelity: Crystal Control.


The transmitter employs the latest method of grid modulation with stabilised reversed feed-back, which results in exceptional fidelity of reproduction of speech and music and practically eliminates distortion and "background noise." The carrier frequency is maintained constant within 10 parts in a million by means of a low temperature co-efficient quartz crystal in a thermostatically-controlled oven.

Locking Device Protects Operators.

The equipment is made entirely safe to operate by means of a safety isolator switch and key inter-lock system. The keys are normally kept in locks associated with the isolator switch in the front panel.

Before these keys can be removed, the isolator switch must be opened

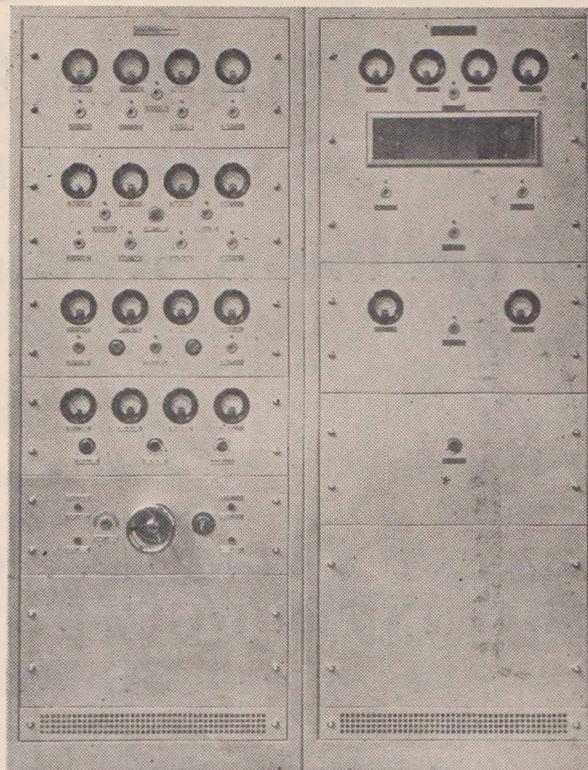A view of the transmitter installed for 6WN, Perth.



and locked open. It is, therefore, impossible to open the transmitter doors until the isolator switch has been opened and all dangerous voltages removed. Conversely, the high voltage cannot again be switched on until the transmitter doors are closed and locked, when the keys can be then removed and replaced in the isolator switch.

Full Automatic Operation.

The transmitter is entirely automatic in operation, and can be switched on or off by push buttons located in a different part of the building. The circuit components are fully protected by means of fuses, overload relays and a system of electrical interlocks.

The transmitter panels are attractively finished in aluminium grey with nickel-plated fittings, and the high class appearance reflects the high quality of workmanship in every part of the apparatus.

World's Largest Shortwave Broadcaster Installed In Rome

On October 31 the Italian Broadcasting Company (Ente Italiano Audizioni Radiofoniche) put into service at Prato Smeraldo, near Rome, a 100 k.w. shortwave broadcaster. This is the highest-powered shortwave broadcaster which has yet been


installed, and the first which will give world-wide radio service.

The station was constructed in the Milan factory of Fabbrica Apparecchiatura per Comunicazioni Elettriche, a company associated with Standard Telephones and Cables Pty. Ltd.

The equipment was designed, manufactured and installed within eighteen months, which is a remarkably short time, considering the development work which had to be undertaken. The new transmitter is undoubtedly the most modern and efficient transmitter in operation to date, as it has new and special circuits for the power amplifiers which give it a much higher performance than ever obtained before for shortwave broadcasting.

The trend in the development of broadcasters is to give higher and higher power as the listening public are taking a great deal more interest in shortwave broadcasting and are comparing the reception with that obtained from medium wave local stations. The quality of this new powerful shortwave station is better than the most up-to-date medium wave station.

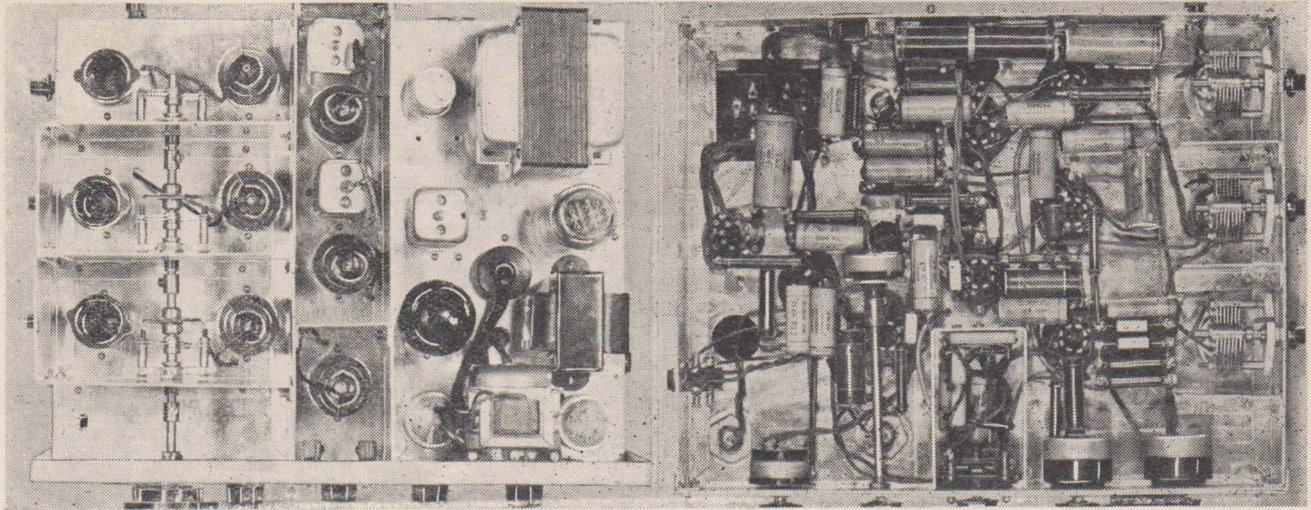The wavelengths need to be changed from time to time to meet changing atmospheric conditions, and facilities are provided to vary the wavelengths in a few minutes. This can be accomplished because the circuits for the high power stages are built on a rotating turntable.



The above chassis view on the left shows the location of the extra i.f. transformer used in this year's model. Immediately in front of it is the new Brimar 6AG6-G high-gain output pentode. The view on the right shows the under-chassis assembly. Note the screening partitions between the band-setting condensers, and the shield around the b.f.o. unit.

Assembling And Wiring The . . . 1938 Amateur Communications 8

Full constructional details of the new 1938 model "Amateur Communications Eight", together with coil-winding data, are given in the accompanying article.

A complete list of the parts required to build the "1938 Amateur Communications Eight" was published in last month's "Radio World." Wherever possible, standard makes of components have been used, though the following points should be noticed.

For the six midget variable condensers used in the aerial, r.f. and oscillator stages of the receiver, the isolantite-insulated variety is strongly recommended. Amphenol steatite sockets should also be used for the coils. The three-plate midget variable condenser used in the b.f.o. to vary the beat note is of the ordinary bakelite-insulated type—in this position the improved insulation is not necessary.

A special RADIOMAC kit of parts for the "1938 Communications Super-het" has been made available by Price's Radio Service, of Sydney, all components supplied being identical with those used in the original model, and detailed in the list of parts last month.

Inclusive price for the Radiomac kit of parts, including valves, speaker and full set of coils, is £19/2/6, while, alternatively, the receiver can be


bought fully assembled and air-tested for £26.

Commercial Coil Kit Available.

While complete turns details are given elsewhere, builders who prefer

not to wind their own are advised that a commercial coil kit is available from Standardised Products. Actually, one of these kits was used in the laboratory model.

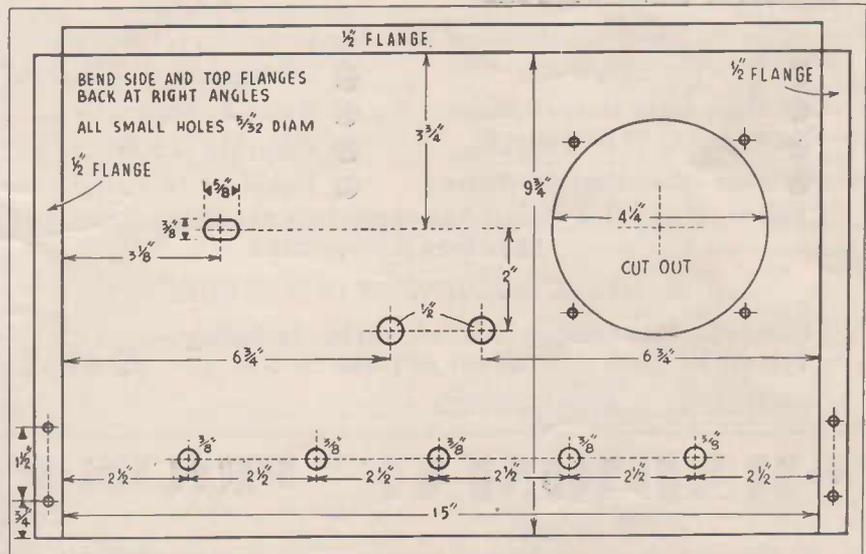The speaker illustrated is a Rola model F-4, a compact 5-inch dynamic that is ideal for the purpose. The total "B" drain is approximately 80 mills., and with a speaker field of 1000 ohms this means a wattage dissipation of approximately 6.4 watts. As this is a little too high for a midget speaker, a 5000 ohm 2-watt resistor



Dimensions for stamping and drilling the front panel are shown above.


has been connected across the field. The 300-ohm 100 m.a. resistor connected in series with the field provides additional smoothing, and as well reduces the smoothed output voltage to 250 volts.

A 30 henry 100 m.a. smoothing choke comprises the second section of the smoothing filter, which has purposely been made elaborate, as a low hum level is essential in this type of set.

The Chassis, Panel, And Partitions.

Sketches of the chassis, front panel and 13 shield partitions required are also included. Nine partitions are needed above the chassis. Three separate the coils, while another two, running from front to rear, isolate the i.f. amplifier, second detector and beat oscillator stages from the r.f. and audio sections. As well, a smaller partition is needed to enclose the 6J7G beat oscillator valve. Another of similar size forms a rear bracing for the long front-to-back partitions, while two more serve the same purpose for the three coil shields, and also eliminate any hand-capacity effects that might otherwise result when the band-setters are being adjusted.

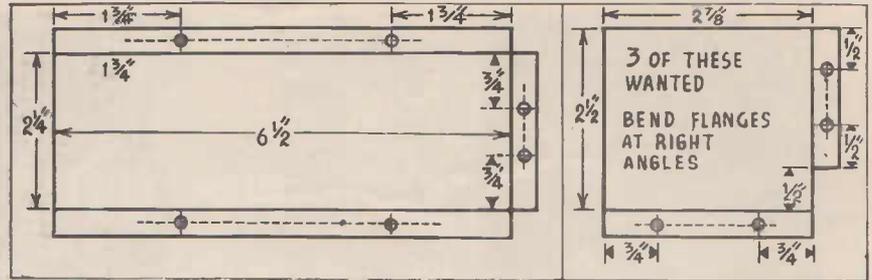The under-chassis view shows the locations of the three shields isolating the band-setters, and also illustrates how the b.f.o. unit is enclosed



The sketches above show dimensions of the partition isolating the b.f.o. from the second detector (left), and of the shields separating the band setters below the chassis (right).

by a three-sided partition, forming a small box.

Eight Front-Panel Controls.


In the front view shown of the receiver, the five lower control knobs are (left to right), mixer regeneration control, i.f. gain control, b.f.o. note adjuster, tone control (combined with switch "S1"), and audio gain control. The two toggle switches are beat frequency oscillator on/off (left) and "B+" on/off. The latter is used when coils are being changed, or minor adjustments made.

Along the left wall of the chassis are the three band-setters (front to rear, oscillator, mixer, r.f.), while the 'phone jack is located on the

right wall. On the rear wall of the chassis are the aerial and earth terminals and power socket, with the a.v.c. switch mounted in the centre.

The first step in the construction is to mount the aluminium steel partitions, commencing with the three that support the bandspread tuning condensers. It is particularly important that the latter should be perfectly aligned, so that there will be no undue drag on the dial movement. The flanges for all three coil shields face the front of the chassis.

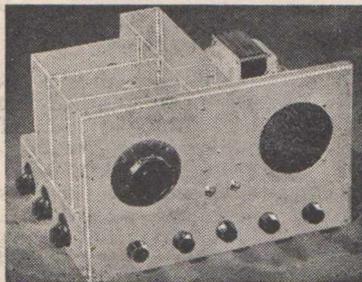Next, mount the two partitions on the left of the coil shields, and then the large partition running from front to back of the chassis, between the r.f. and i.f. sections of the receiver.



Build the New Improved
Amateur Communications Superhet
with a
"Radiomac"
KIT

Some features of this fine receiver are:—

- Effective A.V.C.
- High Gain Output Stage.
- Separate H.F. Oscillator.
- New Multi-Purpose Valves
- Continuous Band-spread.
- Two I.F. Stages.
- Separate B.F.O.
- Equal to 10 Valves.

You must see this receiver to appreciate the improvements that have been incorporated.

IT IS ON VIEW AT OUR STORE.

Complete "Radiomac" Kit of parts, including Valves, Speaker and full set of Coils **£ 19-2-6**

ASSEMBLED AND TESTED **£26**

A Few Bargain Lines That Will Sell Quickly


- So rush your order.
- AERO DIALS . 3/6**
3 3/4" dia. with pearl scale, 12-1 ratio. Fitted with pilot lamp holders. Suitable for 3/8 or 1/4 inch spindles.
- HEADPHONES . 3/11**
Sensitive 4000 ohm type. Suitable for crystal sets, etc.
- HYDRA 3x-5mf . 6d.**
Worth easily 2/-.

American Transmitting **CRYSTAL HOLDERS . . . 10/6**
Ceramtex insulation with monel metal plates. Just arrived.

Readrite Millamp. METERS now available 5/9
20, 50, 100, 150, 250 and 300 m/a.

Write for your copy of our 1938-39 Catalogue—
It is Free!

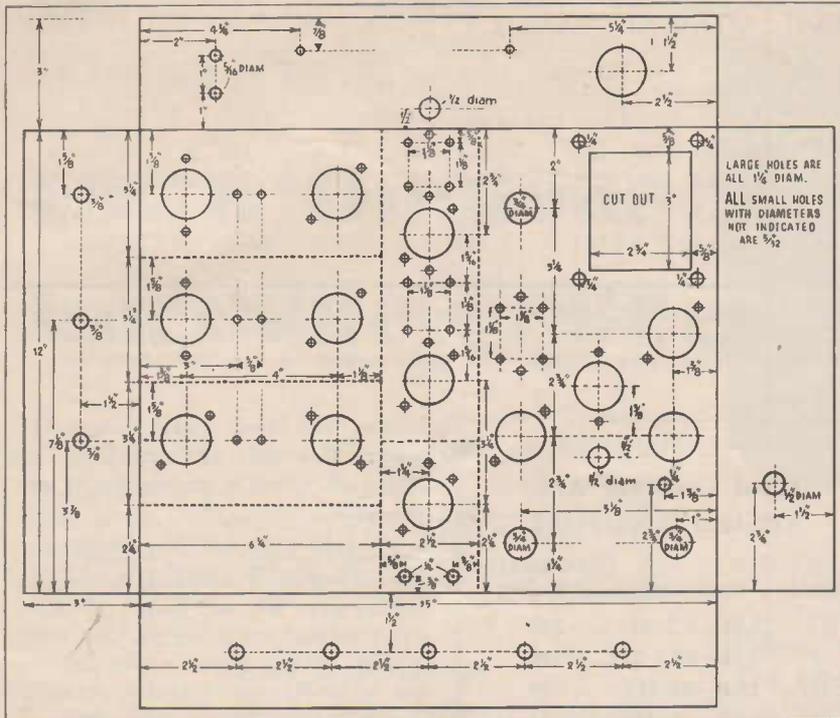"RADIOMAC" PRICES RADIO SERVICE
COMPONENTS
are only obtainable from:—
D. G. McINTYRE
5 & 6 ANGEL PLACE,
SYDNEY.



Dimensions for preparing the aluminium chassis are given in this sketch.

coil sockets, and the three i.f. transformers. The three coil shields with their end partitions and the left-hand front-to-rear partition are next bolted in place. Next, two leads can be soldered to each of the three band-spread condensers, and the latter then mounted loosely in their correct positions on the shields. To eliminate unwanted noise, it is a wise precaution to connect flexible pigtailed to every midget variable that is not provided with them.

Leads are now soldered to each one of the two toggle switches and the latter mounted on the front panel, which is then re-bolted to the chassis. The dial is mounted next, and the couplers put in to link up the three bandspread condensers. The latter can then be lined up so that the dial rotates smoothly over the whole of the scale without any backlash.

Mounting The Speaker.

Next, unsolder one lead of the speaker voice coil, solder two wires as shown in the circuit diagram, and then mount the speaker on the front panel, followed by the five controls. Be careful to insulate the latter where required.

Lastly, mount the three small shields underneath the chassis, and then complete as many coil socket connections as possible before mounting the band-setting condensers.


The main portion of the wiring can now be put in, commencing with the filament and power transformer wiring, followed by that of the smoothing filter, speaker socket, and so on. Next, commencing with the aerial terminal, systematically complete the remainder of the wiring.

Assembling The B.F.O. Unit.

The shielding around the beat frequency oscillator and its associated circuits is intended to isolate this unit from the remainder of the circuit, thus avoiding unwanted coupling. This shielding is indicated by dotted lines on the circuit diagram.

The pigtail components associated with the b.f.o. circuit are next mounted directly on the 6J7G socket. Small "V's" are cut out of the b.f.o. under-chassis shield so that the 6J7G heater and "B+" leads can pass through. The leads to the b.f.o. switch pass upwards through the chassis, while the 5 mmfd. coupling condenser shown is formed by twisting a shielded flex lead from the plate of the 6J7G around the 6U7G grid lead from the first i.f. transformer. A little experimenting will indicate the correct amount of coupling.

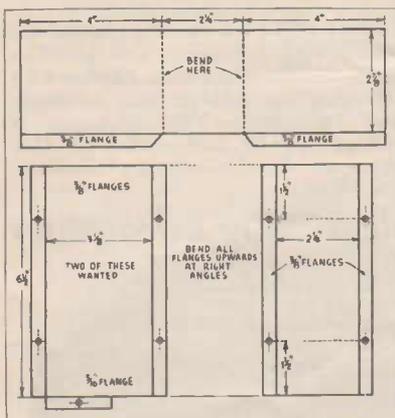The b.f.o. coil is replaced in its can, and the latter mounted horizontally on two pillars bolted to the front of the chassis, one on either side of the 3-plate midget variable.




The shield that isolates the b.f.o. valve from the second detector is mounted next, followed by the second front-to-rear shield, and the small partition enclosing the rear end. The flanges for the two long shields face outwards, and for the two small ones, towards the front of the chassis.

The front panel is next mounted so that its lower edge and the bottom edge of the chassis are level. Lastly, mount three small shields between the band-setters underneath the chassis, together with the three-sided b.f.o. shield partition. When this has been completed, all shields can be removed and a start made on the assembly.

First mount the valve, speaker and

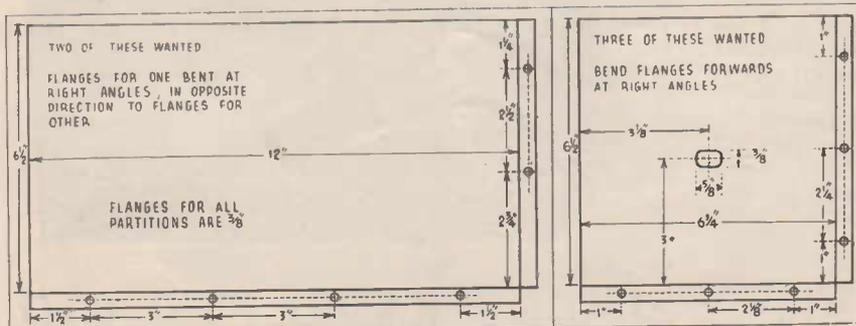The top sketch shows the under-chassis b.f.o. shield, while dimensions of the two end partitions for the coil shields are given in the sketch below (left). The third partition (lower right) is located behind the first i.f. transformer.



Dimensions for the two long front-to-rear partitions are given above (left), together with those for the three coil shields (right).

COIL WINDING TABLE

AERIAL.			R.F.			OSCILLATOR.	
Band	L1	L2	L3	L4	L4 Cathode Tap	L5	Tap
I	9 (a)	33 (b)	25 (a)	33 (b)	1½ (e)	36 (b)	10 (e)
II	5½ (a)	15¼ (c)	11 (a)	15 (c)	1 (e)	15½ (c)	4¼ (e)
III	2½ (a)	5¾ (d)	4½ (a)	5½ (d)	¾ (e)	6 (d)	2½ (e)
IV	1¾ (a)	2⅞ (d)	1¾ (a)	2⅞ (d)	⅝ (e)	3⅞ (d)	1½ (e)

(a) 30g. SWG. DSC. wire interwound in secondary starting from the bottom. (b) 28g. SWG. Enamelled wire wound 32 T.P.I. (c) 20g. SWG. Tinned Copper wire wound 20 T.P.I. (d) 20g. SWG. Tinned Copper wire wound 6 T.P.I. (e) Tap on secondary counted from bottom. All coils wound on 1¼ inch diameter ribbed formers.

Testing The Completed Receiver.

After the wiring is completed, it should be thoroughly checked over. Next, the valves and coils can be plugged in and the set switched on. The three band-setters are adjusted until resonance is obtained, indicated by an increase in the noise level, and then the main tuning dial is brought into operation. The i.f. gain control can be fully advanced, but the mixer regeneration control should be kept

Band Coverage And
Amateur Bandsread

Band	Freq. Range	Amateur B.S. Deg.
I	2.35—5.3 M.C.	280
II	5.15—12.1 M.C.	108
III	10.9—26 M.C.	90
IV	14.2—33 M.C.	84

turned well back until required—when extra gain and selectivity are needed to "lift" a station out of severe QRM.

As this receiver is intended only for experienced builders, a detailed wiring plan will not be given. However, readers requiring further information on any points connected with the assembly are invited to write in, enclosing a stamped, addressed envelope.

CALSTAN

(CALibrated to STANDARD)


TEST EQUIPMENT

A.C. Model 223 will test every valve used in Australia, including American and European P. and V., and in addition to the emission test a Neon leakage indicator is fitted for individual electrode selection. Eleven steps for filament voltage from 1.5 to 30 volts is provided. The Multitester range is:—A.C. and D.C. VOLTS: 5, 10, 50, 250, 1250. MILLIAMPERES: 5 Ranges, 1, 5, 25, 100, 250. OHMS: 5 Ranges, from 1 ohm to 5 megohms. This is also an excellent instrument for lining up sets and as a "Multimeter" operating in conjunction with the Power Supply an electrolytic condenser leakage test is available, and condensers may be checked at 10, 25, 100, 150, and 250 volts, and a "GOOD" — ? — "BAD" meter scale provides the necessary indications.

FREE! For a limited period to purchasers of the AC223 Multitester a new 6-v. Vibrator Unit to convert the Multitester to a General Purpose Instrument for 240-v. A.C. or 6-v. battery operation. This Vibrator, which is separate from the Tester, is a general utility converter, strong, light in weight, and is easily portable. Will run a Mantel Model 5-valve A.C. Set from a 6-volt accumulator, drive an Electric Shaver, and generally act as a universal unit between the battery and the A.C. device. By the use of this New Vibrator Unit, which is plugged into a six-volt battery, the AC223 Multitester now becomes a universal A.C. Tester. The plug on the other end is an A.C. outlet, and the multitester may then be hooked up in the usual manner.

Released by SLADE'S RADIO PTY. for the discriminating Radio Dealer and Serviceman who appreciate and practise the finer points of efficient Radio Service, this is an outstanding instrument for all-round perfection, combining the multiple functions of a Valve Tester and Multitester. This instrument is a boon to the Radio Serviceman and Dealer, and needed by ALL who rely on RADIO SERVICE as an effective means of building up a MODERN RADIO BUSINESS.

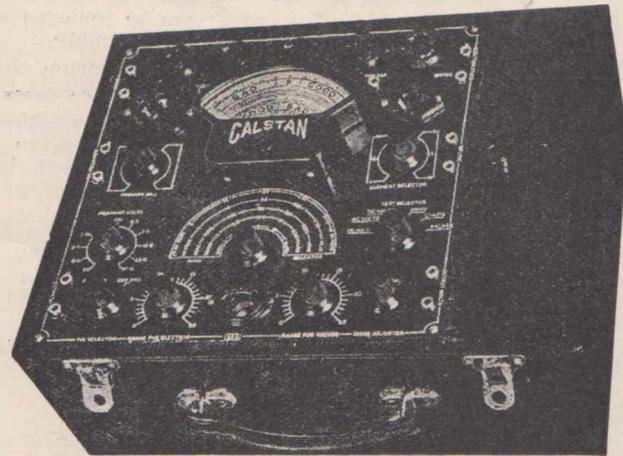the Ideal Portable Testing Laboratory
... the AC223
Calstan Multimeter



MADE BY

SLADE'S RADIO PTY. LTD.

LANG ST., CROYDON, N.S.W. Telephones: UJ5381, UJ5382

Assembling And Wiring The . . .


1938 Outdoor Portable Four

LAST month a review was given of the main design features of the "1938 Outdoor Portable Four," together with an explanation of the operation of the special reflex circuit used. This month further details of this receiver will be given, together with an outline of its assembly and alignment.

Battery Requirements.

Two Ever-Ready type WP60 60-volt light duty "B" batteries are required, together with a Clyde type 2VS7 2-volt 40-amp. hour accumulator.

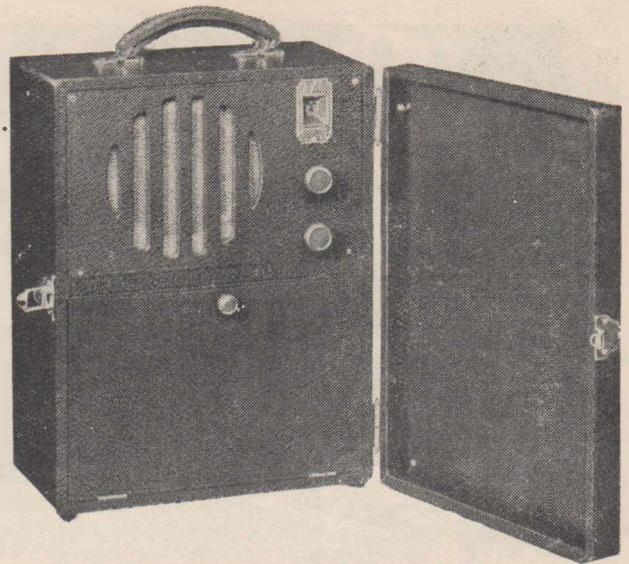The total "B" drain of the set when the batteries are new is approximately eight mills. This drops by several mills. as the voltage drops to 95, but when the economy switch is put over the "B" drain is increased to its original level. As




mentioned previously, increasing the screen voltage on the first two valves in this way restores the performance almost to that obtained when the batteries were new.


The total "A" drain, including a 60 mill. pilot lamp, is .6 ampere, and so, using a 40 ampere hour accumulator, nearly 70 hours of operation can be obtained from a single charge.

There are only four battery leads, two each for "A" and "B." These are taken down through holes in the shelf to their respective battery compartments.

The set is housed in a leatherette-covered carrying case measuring $14\frac{1}{2}$ " high x $11\frac{1}{4}$ " wide x $7\frac{1}{2}$ " deep, specially built for the purpose by the Western Manufacturing Co., of Sydney. A horizontal shelf is provided upon which the chassis rests, with a vertical partition in the lower compartment to separate the "A" and "B" batteries. In this year's cabinet, the hinges of the battery compartment flap have been shifted to one side, which makes it easier to change batteries when needed.

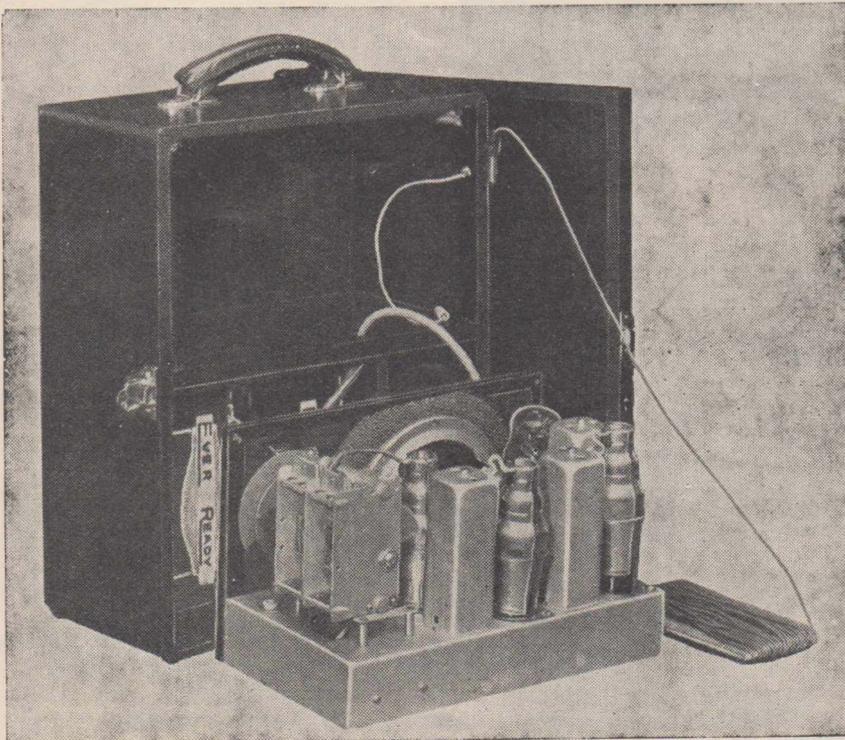

The view above shows the completed receiver ready for operation, while that on the left shows the chassis removed from the cabinet. The lid has been lifted from its hinges to illustrate how the spare aerial carried in the battery compartment is plugged into the socket portion of the top hinge. The four-wire battery cable shown can conveniently be replaced by two pairs of twisted leads running down through two holes in the horizontal shelf to the "A" and "B" battery compartments below.

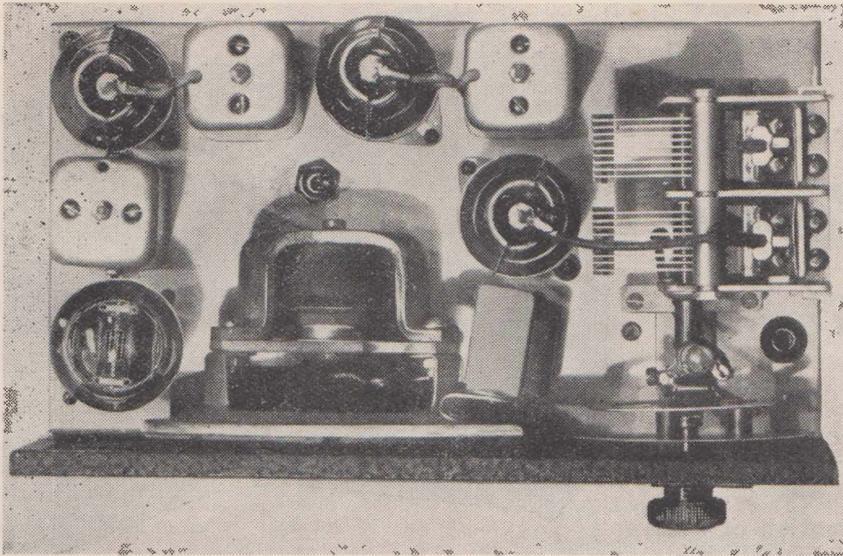

The aerial used for local work consists of a sheet of copper gauze mounted in the lid, connection from the gauze to the set being made via the top metal hinge as shown in the photograph of the dismantled receiver. The top wood screw in each section of this hinge is replaced by a $\frac{5}{8}$ " bolt, a short length of flex being connected from the gauze to one bolt, and a further length of flex from the other bolt inside the cabinet terminates in a banana plug. This fits into the aerial socket mounted in front of the condenser gang, as shown in the plan view of the completed set.

Connecting An External Aerial.


The hinges for the lid are arranged so that the latter can be lifted off at will. In the accumulator compartment is carried an extra aerial, consisting of about eight yards of rubber-covered flex, wound round a piece of three-ply $2\frac{3}{4}$ " wide by 6" long. A hole is bored in the centre of this, one end of the aerial passed through, and a knot tied. A banana plug is mounted on the other end of the aerial. In locations where interstate reception is required, the lid is slipped off and the aerial carried in the case plugged into the top hinge socket.

Chassis Of Frosted Aluminium.

The receiver chassis is of 16-gauge frosted aluminium, and measures $10\frac{1}{4}$ " x $5\frac{1}{2}$ " x $1\frac{3}{4}$ ". The assembly of the components is clearly shown in the above and under-chassis photographs accompanying this article.

The aerial and oscillator coils are mounted horizontally on the rear wall

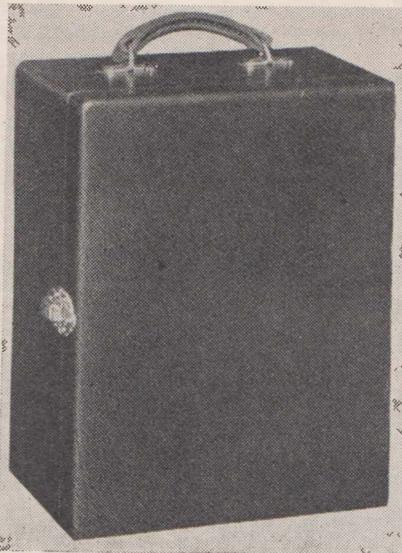This under-chassis view illustrates the method of mounting the aerial and oscillator coils, and also shows the general under-chassis assembly and wiring.



A plan view of the chassis showing the compact layout adopted. The socket in front of the condenser gang is for the aerial connection, while the economy switch can be seen at the rear of the speaker. Below is shown the receiver with the lid closed. It is housed in a carrying case measuring $14\frac{1}{2}$ " high x $11\frac{1}{4}$ " wide x $7\frac{1}{2}$ " deep, and complete with batteries weighs 25lbs.

of the chassis underneath the condenser gang. To the left of the latter (above the chassis) is the 1C7G mixer oscillator. Behind this is the first i.f. transformer, next to it the 1D5G i.f. amplifier, then the second i.f. transformer, and the 1K7G diode detector, a.v.c. voltage generator, and reflexed i.f. and a.f. amplifier. Immediately in front of this valve is the third i.f. transformer, and in front of this again the output pentode. The economy switch is mounted behind the speaker, which is a Rola 5-6 PM.


For so small a speaker this has very high sensitivity, and gives really good tone.

Parts Should Be As Specified.


The parts used should all be exactly as specified; otherwise some difficulty may be encountered in fitting them in place. Dimensions for preparing the chassis are given elsewhere, and should be followed exactly.

The coil kit chosen for the original model of the "1938 Outdoor" is a kit specially made for the receiver by Precision Radio, of Sydney. The kit comprises one type A1B aerial coil and one type O1B oscillator coil, both mounted in small square cans, three type 465LW litz-wound 465 k.c. i.f. transformers, and one type P7 padder. The kit is supplied complete with colour code chart.

Colour coding of the aerial coil is

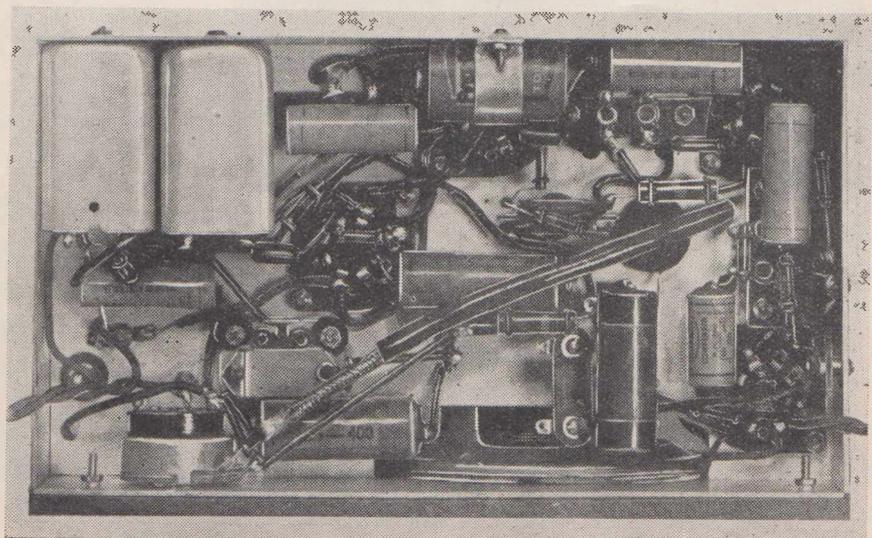

An Amazing Offer on an Amazing Kit

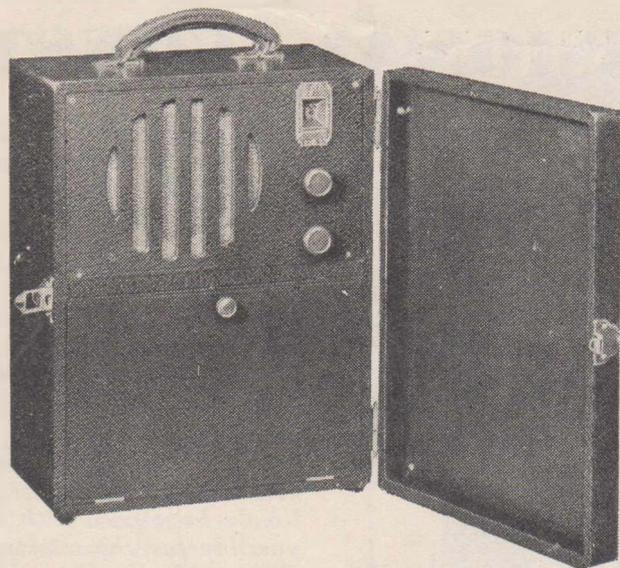

Build the 1938 OUTDOOR PORTABLE 4

During the past three years the "Outdoor Portable Four" has proved to be the outstanding battery receiver of the year. Now the 1938 model with octal-based valves and A.V.C. gives still greater improvement. Read the complete constructional details in this issue . . . see how easily and simply YOU can build this new portable . . . then write to Vealls for details of their special offer, either as a complete kit ready for assembly or as a complete set ready for use.

MONEY CANNOT BUY BIGGER
VALUE ——— WRITE TO-DAY

POSITIVELY THE BEST FOUR VALVER EVER
OFFERED IN EASY TO BUILD KIT FORM

Vealls 1938 Radio Catalogue Now Ready

An essential to every Radio Fan and Listener—Vealls Big 60-page Radio Catalogue covers the entire field of radio, including Amplifiers, Radio Gramo units and Test Equipment. Write for your copy to-day—it's Free! Merely enclose a 2d. stamp to defray cost of postage—your copy will be sent by return mail.

THOUSANDS OF RADIO ITEMS
HUNDREDS OF ILLUSTRATIONS

THE MOST COMPREHENSIVE RADIO
CATALOGUE PUBLISHED IN AUSTRALIA



VEALLS 6 BIG STORES

All letters to Box 2135T., G.P.O., Melbourne, C1.

490 Elizabeth Street, Melbourne. F 3145.
168 Swanston Street, Melbourne. C 10524.
3-5 Riversdale Road, Camberwell. W 1188.

243 Swanston Street, Melbourne. C 3059.
299-301 Chapel Street, Prahran. Wind. 1605.
97-99 Puckle Street, Moonee Ponds. FU 7822.

FIRST CHOICE OF BOTH THE AMATEUR AND PROFESSIONAL CONSTRUCTOR

From the largest commercial manufacturers of Battery operated radio receivers down to the amateur constructor making his first set, the choice of a battery inevitably ends with an Ever Ready.

Made in Australia, in the most up-to-date dry cell factory in the world, and proved by countless tests, they have demonstrated their ability to deliver more power and to give a much longer period of serviceable life, not once but

literally millions of radio sets in use throughout the Commonwealth.

In YOUR set, if you use the most popular "Radio World" battery in this issue, remember that to ensure performance better than competitors, you must use genuine "Ever Ready"



Ever Ready Batteries literally grew up with new circuits, new valves, were designed to keep pace with new and improved radio sets. It is possible for the constructor to-day to select a battery for practically every known Radio need. You can fit a set to almost any type of cabinet.

Newest developments in Ever Ready Air Cell that has superseded it eliminates re-charge attention whatsoever. power capacity that lasts for over 12 months under conditions of use. If you use a battery receiver from a set manufacturer, you are "Ever Ready Operated."

Keep A Torch In Your Trouble Kit

Every set constructor should keep an Ever Ready torch in his kit. Throws a brilliant beam exactly where you want it for delicate wiring jobs or repair work. Inexpensive, too—a few shillings is all any good model costs.

And for best results see that weak or rundown batteries are replaced promptly with "factory fresh" Ever Ready Refills. Made to give you the same superlative service that has made Ever Ready Superdynes the most popular radio batteries in Australia, you will find them 100% dependable under all conditions and capable of truly extraordinary long life. Obtainable everywhere.

EVER READY RADIO

EVER READY CO.


AMATEUR CONSTRUCTOR

of times—in the thousands
in use in the country districts of
wealth to-day.

if you are planning to build the
"Radio World" portable set described
remember that the biggest sell-
in Australia is still the best and
for perfect results you cannot do
connect your circuit to a set of
Ever Ready's."

up with the radio industry. As
designed and perfected, so too Ever
Ready batteries. As a result it is
to secure an Ever Ready Battery
need—and in a size that enables
of cabinet.

development in country radio is the
"Air Cell"—the new type battery
which has succeeded the accumulators because
it requires no re-charging worries and needs no
maintenance whatsoever. Guaranteed maximum
life expectancy the day you buy it, it is good
for months' service under normal con-
ditions. If you are planning to build a
portable set, ever follow the lead of 23 leading
radio constructors and make it "Air Cell

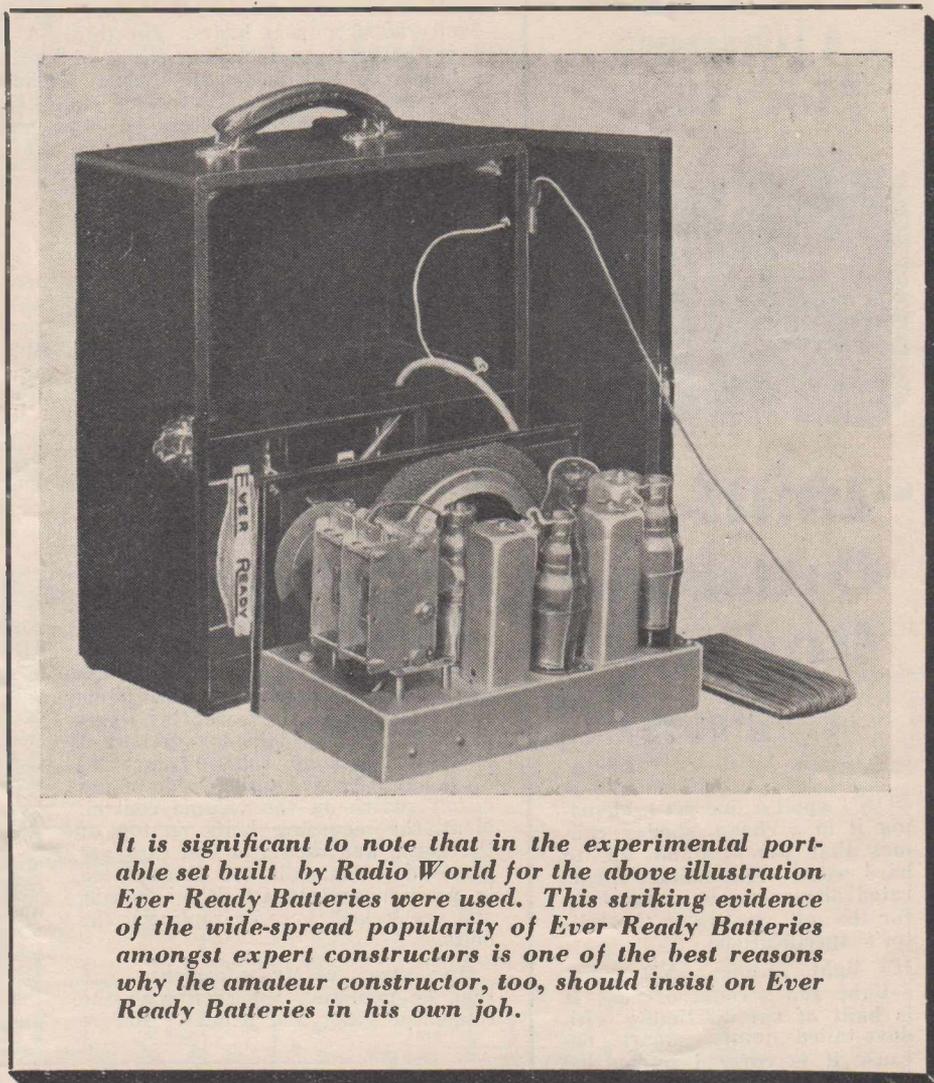

It is significant to note that in the experimental portable set built by Radio World for the above illustration Ever Ready Batteries were used. This striking evidence of the wide-spread popularity of Ever Ready Batteries amongst expert constructors is one of the best reasons why the amateur constructor, too, should insist on Ever Ready Batteries in his own job.


EVER READY

RADIO BATTERIES ★ AIR CELLS ★

Y CO. (AUST.) PTY. LTD.

SYDNEY

Here's Your Cabinet for the

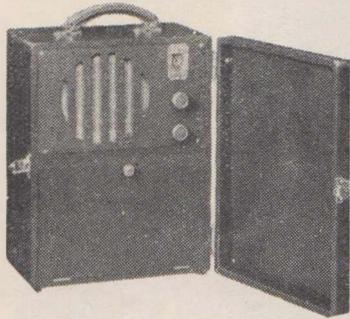

“1938 Outdoor Portable Four”

DON'T spoil a fine set by housing it in a cheap, shoddy cabinet that won't stand up to hard wear. The cabinet illustrated above was built specially for the job, exactly to the Editor's specifications.

It's light, strong, AND smart—light and strong, because it is built of special timber with dove-tailed joints, smart because it is covered in mottled leatherette, obtainable in black, blue, red, brown, and crocodile, and is fitted with plated hinges and catch.

PRICE ON APPLICATION

MANUFACTURERS, DEALERS & SERVICEMEN!

We specialise in making all classes of cases for test equipment, exactly to your specifications. Workmanship and accuracy guaranteed.

WESTERN MANUFACTURING Co.,
18 THIRD AVENUE,
FIVE DOCK, SYDNEY

'Phone U 3444

★
The Clyde type 2VS7 two-volt "A" battery chosen for the "Outdoor Portable" has a capacity of 40 ampere hours. The total "A" drain of the receiver, including the pilot light, is .6 ampere, which means that nearly 70 hours of service can be obtained from a single charge. It is an excellent plan to buy two of these batteries, so that a fully-charged one is always available when required.



★
as follows: black, aerial; red, earth; green, grid; yellow, a.v.c. return. Oscillator coil: black, oscillator plate; red, oscillator "B+"; green, grid; yellow, padder. I.F. colour code: black, plate; red, "B+"; green, grid or diode; yellow, a.v.c. return.

In building the receiver, the four valve sockets should be mounted first of all, followed by the aerial socket. In the case of the four sockets a small solder tag should be slipped under the nut belonging to each mounting bolt. These are used later on as required for earthing the "A-" side of the filaments, and for other earth returns.

The filament wiring can now be put in in the underchassis wiring diagram, all the valve socket terminals marked "X" are joined together, a lead finally being taken from "X" on the 1C7G socket to one side of the on/off switch on the volume control. Next, the mounting bolts on top of the aerial and oscillator coil cans are removed. The coils are then placed in position underneath the chassis, and are locked there by replacing the bolts.


The three i.f. transformers can then be mounted, together with the condenser gang and padder. Before

mounting the gang, solder a six-inch length of push-back to the lug underneath each section. These leads pass through the chassis, and are soldered to the green lugs on the aerial and oscillator coils. Finally, the various small terminal strips indicated on the wiring diagram can be put in; these are mounted clear of the chassis by means of half-inch brass spacers.

Putting In The Wiring.

Now, commencing at the aerial socket, wire the aerial coil, oscillator coil, 1C7G, first i.f. transformer, 1D5G, second i.f. transformer, and so on. At this stage the 1½-volt bias cell can be mounted on the rear wall of the chassis by strapping it in place with a strip of aluminium, and also the single-pole/double-throw economy switch can be mounted.

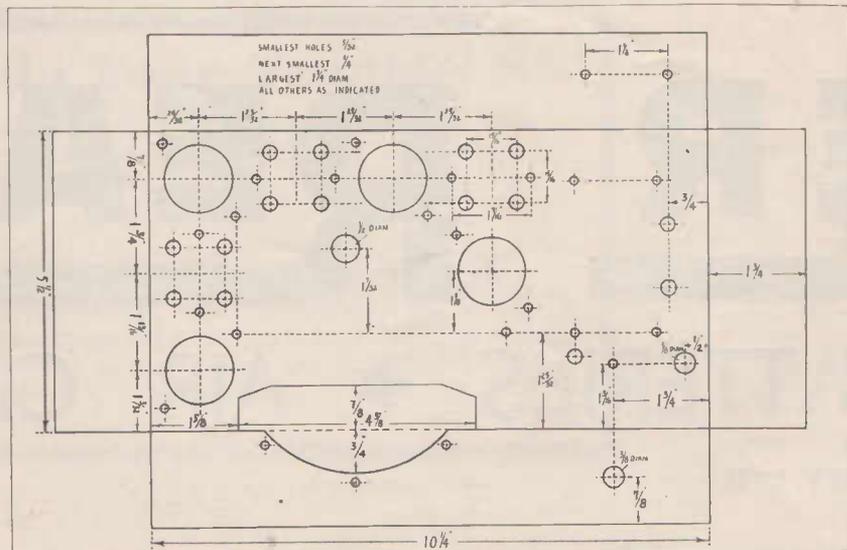In a set of this type it is particularly important that the assembly and wiring be completed slowly and carefully. All leads, particularly grid and plate leads, should be as short, direct and as well-spaced as possible, while all by-pass condensers should be mounted as close as possible to the points they are intended to by-pass. In addition, all earth returns



Dimensions for stamping and drilling the 16-gauge frosted aluminium chassis, measuring 10¼" x 5½" x 1¼", are given in this sketch.



and pass a bolt through both bar and chassis, securing it with a nut and washer. Of the two dial light lugs, one is earthed to the dial frame, while a length of push-back is run from the other through the chassis to the terminal of the volume control connected to "A+".

The speaker can now be bolted to the front of the chassis, and the leads from it connected to the plate and screen lugs on the 1L5G socket.

Four Battery Leads.

Only four battery leads are required—two for "A" and two for "B." Each pair is soldered to the points indicated on the wiring diagram, and twisted together. When the set is placed in position, these leads pass through the holes drilled in the horizontal shelf on which the chassis rests, to connect to the "A" and "B" batteries below.

With the wiring completed and checked, the set can be tested and aligned before it is mounted in the cabinet.

The Alignment Procedure.

With the batteries connected up, and using a few yards of flex plugged into the aerial socket as a make-shift aerial, switch on and check over the valves to make sure all the filaments are alight. Then set the two trimmers on top of the gang and the padder about halfway out. Advance the volume control, and tune in a station operating on about 220 metres.


Adjust the aerial trimmer on top of the gang for best results. If no peak is found, screw in the oscillator trimmer a turn or so and re-tune the station. Then again adjust the aerial trimmer. Next, a station towards the top end of the waveband should be tuned in, and the padder adjusted. While this is being done, rock the dial backwards and forwards across

Two of these Ever-Ready 60-volt type WP60 light-duty "B" batteries are required for "B" supply. As the average "B" current taken by the receiver throughout the life of a set of "B" batteries is only approximately 6 mills., up to six months of normal portable receiver service can be expected before replacement is needed.

the station until a point is found at which volume is greatest. This alignment procedure can then be repeated once again.

Finally, the trimmers on the three i.f. transformers can be given a slight adjustment to ensure peak results, commencing with the third transformer and working towards the first. These trimmers should only be shifted a fraction of a turn, and also the original positions should be marked so that the trimmers can be returned to them if desired.

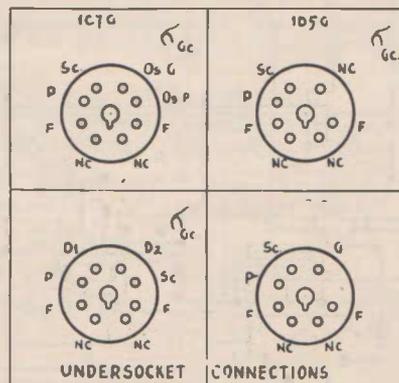If carefully carried out, the above should result in substantially correct alignment that will hold satisfactorily



The under-socket connections of the four octal-based "G" type valves used are given in this sketch. Bottom left sketch shows 1K7G socket, and bottom right, 1L5G socket.

over the entire waveband. However, alignment using a service oscillator will ensure maximum results. With the volume control full on, there should be no instability whatsoever, and it should be easily possible to tune in several dozen stations at good speaker volume.

Fitting The Copper Gauze Aerial.

The set can now be laid aside while

the copper gauze aerial is mounted in the lid.

After taking out the four corner screws, the inside cover of the latter is removed, and the sheet of gauze placed flat in position underneath. The top wood screw attaching the top hinge section to the lid is taken out and is replaced by a $\frac{5}{8}$ " bolt. One end of a 2" length of flexible pushback is now soldered to the copper gauze at a point nearest the bolt, while the other end is wound around the projecting end of the latter and locked in place with a nut. The inside cover of the lid can now be replaced.

Next, the lower of the two wood screws attaching the top section of the hinge to the cabinet is removed and replaced by a $\frac{5}{8}$ " bolt, as with the lid. A 6" length of flex, terminating in a banana plug, is attached to this bolt inside the cabinet.

The leatherette-covered front panel is now placed into position in front of the receiver chassis, and the two bolted together by means of two $\frac{5}{8}$ " bolts and nuts, located one in each bottom corner.

Mounting The Set In The Cabinet.

Next, the two pairs of battery leads are passed through the hole in the horizontal shelf provided for them and the set slipped into the cabinet. The aerial is plugged into its socket while this is being done.

The control knobs and dial escutcheon are then fitted, and the front panel secured in position by means of a wood screw passing through each top corner. The "B" batteries are now connected up and slipped in in an upright position, one at a time. Finally the two "A" battery leads are passed through the shelf and connected to the accumulator, which is then slipped into its compartment.

The Clyde type 2VS7 "A" battery specified for the "1938 Outdoor" will give nearly 70 hours of service from a single charge. An excellent plan is to use two of these batteries, so that a fully-charged one is always instantly available.

The aerial carried in the accumulator compartment consists of about wound around a piece of three-ply. eight yards of rubber-covered flex

The battery compartment flap is next closed and the lid replaced, making the set ready for operation.

With normal use, the two 60-volt light duty Ever-Ready "B" batteries will last from four to six months, depending on the use they are given. After about two months' operation, when the "B" voltage will have dropped to approximately 100 volts, the economy switch can be put over. This will restore the performance so that it becomes more or less equivalent

to that obtained when the batteries were new, and also enables the last ounce of power to be obtained from the "B" units.

An Outstanding Performer.

For sheer "pulling power" on DX work, combined with excellent volume and tone, the "1938 Outdoor" is in a class of its own. Correctly built and aligned, it will easily outperform any other standard four-valve battery superhet taking the same "B" drain.

(Note: The aerial and oscillator coils supplied with the Precision Radio kit can be distinguished by their black and red base centres respectively.)

CFGP Is British Empire's Most Northern Station

Contributed By GORDON YOUNG,
(AW250DX). Queensland.

In Canada, to the north of the State of Alberta, "lies an Empire within an Empire." The great Peace River Country is recognised as being one of the richest areas in agriculture lumber and minerals, spreading over 93,000 square miles with a population of over 80,000 souls.

Nature has isolated this territory from what is colloquially known as "the outside." From Grande Prairie to Edmonton by road is 400 miles, and although a telephone system is in operation in the Peace River Country itself, there is no telephonic communication beyond its own borders.

Radio reception from "the outside" was very poor, so the people set about and established a radio station of their own, with every modern facility.

CFGP is the most northern commercial broadcasting station in the British Empire, transmitting on a frequency of 1200 k.c. with a power of 100 watts. The studios and offices are located in the Donald Hotel, Grande Prairie, with Mr. C. L. Berry as manager and Mr. George Sinclair, VE4UY, as engineer.

No daily newspapers are available in the Peace River, no billboards, in fact, no daily medium of advertising except CFGP. Using an eight-valve Marconi receiver with a two-wave rhombic beam aimed at New York, U.S.A., news is obtained, and four daily newscasts are then sent out by CFGP to its listening audience, estimated to have 10,000 radios.

Transmitter consists of a 59 crystal oscillator followed by a R.C.A. 804 pentode suppressor modulated by a 59 audio. R.C.A. 805's class B with 100 watts output. The antenna is a ¼-wave lattice type guyed mast with an elaborate ground system.

REMEMBER, GIRLS . HE'S HERE TO FIX THE RADIO



Some radio service men get themselves into some awkward predicaments. But there's one way to avoid valve trouble, and that's change to Brimar. By using a really dependable replacement you gain prestige as a radio man who really knows his valves.

Brimar stocks are immediately available in every possible type in any quantity—no waiting—no substituting.

Make "Brimar throughout" your motto.

BRIMAR

VALVES

DISTRIBUTORS:

NEW SOUTH WALES: Standard
Telephones & Cables Pty. Ltd., 258-
274 Botany Road, Alexandria.

QUEENSLAND: Trackson Bros. Pty.
Ltd., 157-9 Elizabeth Street, Bris-
bane.

VICTORIA: Noyes Bros. (Melbourne)
Ltd., 597-603 Lonsdale Street, Mel-
bourne.

SOUTH AUSTRALIA: D. Harris &
Co., 140 Rundle Street, Adelaide.

WESTERN AUSTRALIA: M. J.
Bateman Ltd., Milligan Street,
Perth.

TASMANIA: W. & G. Genders Pty.
Ltd., 69 Liverpool Street, Hobart.

NEW ZEALAND: Standard Tele-
phones and Cables Pty. Ltd., Tro-
jan House, Manners Street, Wel-
lington.

The "Ultra-Shorts" In Review . . . (3)

In this concluding instalment the author continues his review of VK's now experimenting on the "ultra shorts," and appeals to amateurs generally to arrange more organised tests.

By **DON B. KNOCK**

Radio Editor, "The Bulletin."

ONE of the keenest experimenters on five metres in Sydney is W. McGowan (2MQ), who is now just completing a new crystal-controlled five-metre transmitter. 2MQ also has plans for a new five-metre receiver using the recently-released type 1851 television pentodes.

A newcomer to the u.h.f. band is Ross Treharne (VK2IQ), with a splendid transmission from a crystal-controlled 100-watt transmitter, using 800's in the final. For a receiver he has a converter using a 6J7 r.f. stage and a 6K8 mixer, operated in conjunction with his amateur band superhet. A Bruce beam array will shortly be in use at this station.

One new amateur in the Sydney area is worthy of commendation for his interest in breaking into amateur radio by making a start on five metres before the other bands. This is VK2AJH, of Epping, who now has an excellent 'phone signal, and who will be changing to crystal control with 804's in his final very shortly. In the past four years, many other Sydney amateurs have taken part in 5-metre activity, but those referred to are the consistent workers with modern equipment.

In the other States, Victoria has many keen men, but at present South Australia shows most activity, following no doubt on the success of VK5ZU. Stations active there are VK5ZU, VK5HM, VK5CR, VK5OJ and others.

Since I recently visited Brisbane, a burst of activity is reported from the Northern City, and VK4MM, VK4WT, VK4HR, VK4AW, VK4JL and VK4JP are known to be on the job. VK4WT has crystal control and startled the local gang with his powerful signal from an 807 final and a vertical W8JK aerial. VK4JP is expected to be a shining light, having just returned from two years in U.S.A., where he took part in much five-metre communication.

In New Zealand, ZL4DQ, ZL2UD, ZL1IR and others are known to be on the job with modern gear. ZL2UD and ZL1IR have recently been logged

350 miles distant. In the country of N.S.W. there are VK2DN, VK2PN, VK2GU and others who can be counted upon, and recently I have received details of much activity among the VK6's in Western Australia.

With the advent of summer, it is expected this year that there will be some really tangible and satisfying results following on the May and June work in America.


DX Reports.

Although the matter of DX on five metres is an interesting one, the fact should not be lost sight of that the band is primarily a very useful local communication channel. For that reason alone it is well worth population, and the trend of events internationally is such that we may need to make full use of it before many years have passed.

There have been many instances of DX recorded on five metres, and the history of such reports goes back to 1926. DX on five metres is really nothing new, but with advanced apparatus the possibility of turning it to good account is totally different. In Australia, the outstanding long distance reports include the reception of telephony in Nth. Wales, Britain, by Mr. Cecil Mellanby, from my own station over a year ago. This report came as a great surprise, to no one more so than to me. The radio world everywhere was incredulous to the extent of putting it down as a case of "imaginitis."

In England I know that everything was done to attempt to discredit Mellanby, for the reason, I venture to say, that he is a short-wave listener and not a transmitting amateur. However, Mellanby could be no guesser to the extent of guessing what a man would be doing 11,000 miles distant on five metres.

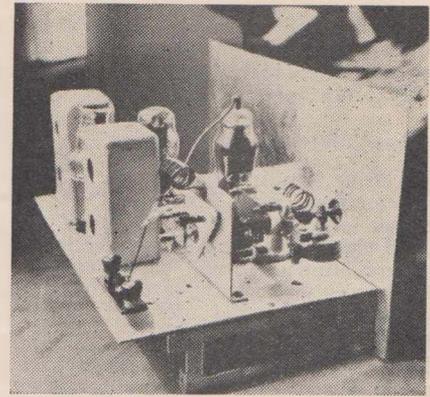Examination of my log showed the transmission time exactly as reported, during a local QSO with VK2HL. Mellanby again reported reception a second time, and also the reception of a



The new 56 m.c. "Super-Gainer" built by Don. B. Knock (VK2NO) is a three-valve superhet with a remarkable performance. It uses a 6J8G as mixer-oscillator, 6D6 i.f. and 6A6 as second detector, combined b.f.o. and audio stage. Special 1600 k.c. i.f. transformers were supplied by Tasma Radio, these giving an unusually high gain for the frequency. The receiver shown is now being used by Ross Weeden (VK2PN), of Tumut, N.S.W.

harmonic from VK2UC, of Lismore. Then later he reported hearing something of VK2HL. Needless to say, five-metre reception over the distance staggered the imagination so much so that some amateur officials in England sent members along to interview Mellanby in his receiving location.

Evidently he gave them no loophole to discredit his reception, for it was reported that he would say little beyond show his verifications from not only VK2NO, but the several Americans he had also heard on the band. They did come away impressed, however, with his location, which is high up in the hills at Pwllheli in North Wales. Mellanby's receiver is a three-valve t.r.f. type with two-volt valves.

Time progressed, and then the U.S. Bureau of Standards went to the trouble to check up on ionosphere conditions at the time, and stated definitely that such reception would have been possible over the path between Australia and Britain. Thus is a lesson learned, not to assume that signals will not unexpectedly cover great distances at 56 m.c. Remember that the same was said by commercial radio engineers in 1928 of 10 metres. Anything below 12 metres was useless. And to-day those commercial people have snagged a lump of 10 metres, and done the same to five metres!

Nothing more has been heard from England about the unreliability of the Mellanby report, and one magazine has published a definite acceptance of the facts.

On June 27, 1937, a five-metre test day was in progress, organised by the N.S.W. Division of the W.I.A. Each Sydney station transmitted at pre-arranged periods. VK2DN, of Deniliquin, suddenly heard the i.c.w. transmission from VK2NO, a matter of 360 miles across country.

More Organised Tests Wanted.

More organised tests of this kind with a number of stations participating are badly needed, and such tests are run off every Sunday by VK2NO and VK2EM. VK2WJ has now come into these tests, which are run from 11 a.m. to noon Sydney time for New Zealand and BERS195, and 3 30 p.m. to 4 p.m. for VK2DN, VK2PN, VK5ZU and the Brisbane men. After 4 p.m. a check is made on 40 metres to note results, if any. These tests will run throughout the summer until around April next.

The reception of VK5ZU in New Zealand has been referred to previously. At the time, ZL4DQ was using a superhet with limited frequency coverage, but by this time is using an acorn t.r.f. receiver.

In 1937 communication was, as most VK's know, effected between VK2ZC of Newcastle, and VK2NO. VK2EM was heard, and succeeded in hearing VK2ZC. The interesting part of VK2EM's work was that he was at this time located right on water level and water edge at Darling Point, Sydney. This substantiates Mr. Conklin (W9FM) in the assertion that a station over a salt marsh or water is likely to reach out on five metres. Distance to Newcastle is around 70 miles, and this cannot be considered as visual range. The gear in use at that time, moreover, was the old-fashioned type with super-regen. receivers, so that under the advanced conditions 100 per cent. results could be expected.

There is yet much to be done in the development of apparatus, and in this respect it behoves those who like amateur radio from an experimental aspect as well as from the DX QSO point of view, to come into the picture and give assistance. It takes two stations to make a contact, and there is more than there is in talking locally on 40 or 20 metres, for the interference problem is not so acute. Many stations put in a lot of time with 'phone QSO's on 20 and 40 metres, exchanging technical ideas while awaiting DX. Why not do it on five metres and help to populate the band?

If everything sits back and adopts the attitude that it is not worthwhile, we shall be a long while getting very far, and it seems certain that in future years the ultra-high-frequencies, and five metres in particular, will be vital amateur territory. But if we let the band pass by relatively unused, then somebody with commercial ideas will want to appropriate it as they are determined to appropriate the other bands.

Coil-Winding Data For Philips EK2G Octode Oscillator Grid Current Values

THE accompanying drawings show coil-winding data for the Octode EK2G (octal base) designed for a 4/5 receiver for dual-wave operation. It must be realised, of course, that these windings are based on a certain experimental receiver, and slight variations may be necessary to compensate for varying factors, such as wiring and stray capacities. The recommended capacity range for the tuning condenser is 9 to 400 mmfd. (Stromberg type "F"—Ed.) and independent trimmers (5-30 mmfd.) are required for circuit alignment.

The operating voltages for the EK2G valve should be adjusted as follows:—

- Plate 250 volts
- Screen 50 volts
- Oscillator plate 200 volts
- Negative grid bias 2 volts

It is also suggested that a non-inductive resistance of 50 ohms be inserted between the oscillator grid and the grid coupling condenser (.0001 mfd.). This serves to reduce the ten-


dency towards excessive oscillation at the high frequency end of the tuning range. The grid leak resistance (50,000 ohms) is taken directly from the oscillator grid to ground, and is not connected in series with the 50-ohm resistance.

Padding Condensers.


For the broadcast band a padder having a maximum capacity of 0.0004 mfd. was used with the original coils. This padder was made up by connecting a fixed capacity of 0.0003 mfd. in parallel with a trimmer condenser of 0.0001 mfd. maximum capacity. A fixed padder of 0.0045 mfd. is used with the short wave coils.

Oscillator Grid Current.

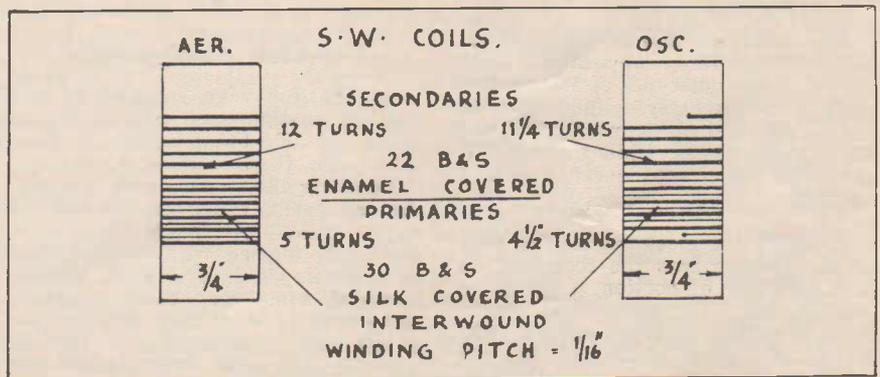A current of 100-200 microamps. should be realised on the broadcast band with the suggested windings and electrode potentials. Under the same operating conditions on short waves the grid current should fall (Continued on page 46.)



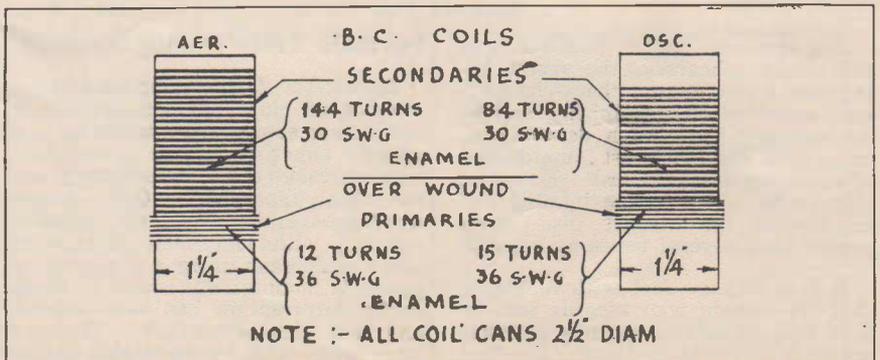These sketches show EK2G coil data for the broadcast and shortwave bands.



Unique Home Recording

Demonstration



A QSO on the outskirts of a country town during field tests.

Lakemba Club Meeting Recorded And Played Back ★ Club Auction Sale ★ Portable Tests

By W.J.P.

AN interesting demonstration of the quality obtainable from home recordings with modest apparatus was given at the Lakemba Clubrooms last month. The lecture was presented in a unique manner, it having been previously recorded, permitting the opening 15 minutes of the discussion to be played through the amplifier.

The lecturers had on display the complete recording apparatus, together with various types of records and discs from the early cylinder type to the latest 15-inch transcription and early talkie types, while an old Edison 1900 model reproducer was also on view.

Probably the most fascinating part of the evening was the recording on a 12-inch disc of portion of the general meeting. The record was played back immediately after cutting, and all present were astounded at the quality and detail recorded thereon, including sound effects, clapping and even noise of passing traffic on the street outside.

The recorded matter had not been previously rehearsed, the result being that a few errors, "back-chatter," etc., appeared on the finished article. At ordinary times such details pass unnoticed, but are most outstanding when taken on a record. However, this really added to the interest and amusement, the finished disc being played back several times by request.

It is a strange fact with recording that the person who records for the first time is seldom entirely satisfied with his own voice, despite the fact

that other listeners claim it to be an exact reproduction.

At the conclusion of the demonstration the lecturers, Messrs. Warren, O'Donnell and Phelps were accorded a hearty vote of thanks for a very entertaining evening.

★

The Club Auction Sale.

At the following meeting of the club an auction sale was conducted under the able baton of Mr. V. Bennett. On these occasions members bring along their spare radio apparatus and parts, which are offered for auction sale. Although these were previously termed "junk" sales, they have developed into a much higher standard, some very good apparatus being sold at very keen prices. As an example, a perfectly good 500-500 volt 150 m.a. power transformer was disposed of at 3/-.

★

Portable Tests During Summer.

During the forthcoming summer, a number of club members anticipate conducting some very interesting and useful experiments in connection with portable radio transmitting and receiving apparatus. Over recent months several have been experimenting with long and ultra-short wave equipment using a minimum of power in mountainous country. Much useful information has been gained, and it is anticipated that in the very near future radio gear of this nature

will be put to really beneficial use.

Those desirous of obtaining information in connection with the club may do so by calling or writing to the Secretary, 14 Park Avenue, Concord, or the Publicity Manager, 14 Watkin Street, Canterbury.

Waverley Radio Club Notes. By 2AHJ.

The club should in the near future make rapid progress, now that the new transmitter and receiver are in operation. Both are working excellently, and as far as design and construction are concerned will take a lot of beating. The 20 and 40-metre bands will be used primarily and the 10-metre band will be used on occasion. Five-metre operation will eventually be attained, and this should be quite unique, insofar as the crystal oscillator used is temperature-controlled and the signal will in all probability be used as a marker signal on that band.

The members recently gave a very interesting demonstration and lecture on "ham" activities before the members of a local social club. Intense interest was displayed by the audience, some of whom did not know previously that "ham" radio existed. The lecture on the subject was very capably handled by Morrie Lusby (2WN) and the working exhibit by Jack Howes (2ABS).

A very interesting "ham" visited the club on October 11 in the person of Mr. Cawood (VS4CS), who has spent the last eight years in North

Borneo. Mr. Cawood gave an interesting discourse on that remote DX land, and is going to become a member of the club. On the same night, Gordon Wells, the president, gave a lecture on the design and construction of the new transmitter, accompanying it with circuits of the coil and crystal switching.

The club welcomes back in its ranks Dud McGowan (2MQ), who recently spent several weeks in hospital. Dud reports being 100 per cent. and fit for lots of DX.

On October 18 Dev. Dunn (2EG) gave an interesting lecture on the composition of music. As a result, members no longer lament the disappearance of their radio licence fee, but instead they more readily appreciate the broadcasts of symphony recitals.

Club meetings are held every Tuesday evening at the rear of 13 MacPherson Street, Waverley, and anyone intending paying us a visit may be sure of finding plenty to interest him.

★

VK2MZ—The Hurstville Amateur Radio Club

(Affiliated With The W.I.A. (N.S.W. Division).

Classes for the A.O.C.P. examination in January have just commenced, these include morse code practice, theory and regulations.

The modulator of the club's transmitter has been re-built. The line-up is now a 57, 56 into a pair of 89's in parallel. Reports show that it is working very well. Another addition to the Club's equipment is an a.c. audio oscillator, and code practice is given every Thursday night from 8.15 to 9 p.m. b- 2VT.

Members were pleased to meet VK2AKP, who visited the club while on vacation in Sydney. His QRA is Moree, and he is at present working on 40 m.

The club entrance is at the rear of 316 Forest Road, Hurstville, and any information regarding the club's activities can be obtained from the secretary, J. Ackerman, 34 Park Road, Carlton, or from Mr. G. Colvert, 4 Jolley's Arcade, Hurstville.

Radio Set Sensitivity.

(Continued from page 14.)

a set is prone to bring in more "squeals," interstation racket, and a host of unpleasant incidental noises.

In America there is a tendency to revert to the "good old days" in the matter of sensitivity. One well-known firm has produced a low sensitivity high quality reproduction receiver

which gives perfect reception over a limited distance—an ideal set for the urban listener, but scarcely suitable for existing rural conditions in Australia. All the same, a receiver should be no more sensitive than is required for good reception.

There is another complication introduced by the use of high sensitivity—the ability to separate the numerous stations brought in. It is usual to see these qualities embodied in equal measure in a well-designed chassis.

The apparent lack of selectivity in a highly sensitive set can only be offset by elaborate design, as if selectivity is achieved by "brute force" methods, bad side band cutting with its consequent distortion will result. All unsatisfactory.

Sensitivity Considerations On The Short Waves.

All the foregoing has reference to the orthodox broadcast wavelengths. What of short waves? The position here is simple. We are struggling to attain sensitivity, especially on the very short waves, while the selectivity problem is confined to avoiding second spot interference.

It is possible to obtain sensitivity on the wave-bands from 25 metres up equal to that of the broadcast band, but from 19 metres down this is considerably more difficult. However, if an overseas short-wave station is laying down a satisfactory signal at the receiving aerial, a sensitivity of about 25-50 microvolts is adequate, and if the short-wave signals are weaker than this the results are usually not worth hearing.

The progress made in the development of more efficient tuning systems and components during the last few years makes the attainment of sensitivity a fairly simple matter, provided correct principles are followed. Measuring instruments have also been improved greatly, and the engineer has almost a cut and dried technique in these matters. One says "almost," because the matter of economics is not to be dismissed lightly. Unfortunately high efficiency in a receiver does not always connote a high sales level.

One looks forward to the extension of the broadcast network to the point where receivers can be designed of low sensitivity, flat tuning and high grade reproduction. The handling of such a receiver would be delightfully easy, while its freedom from noises of various kinds would make it a valuable source of entertainment.

However, it does not seem likely that a set of this kind would find a market in Australia for some time to come.

Get Better DX and more QSL Cards!

Signals jump from R4 to R9+!

Here's a quick, easy, inexpensive way to put power in your radio, and pull in far-away stations at loudspeaker strength—yes, stations that many owners of even the most expensive radios are unable to hear.

The "NOISEMASTER" Engineered All-purpose Aerial Outfit dramatically wipes out noise and local static. At the same time it boosts up signals to incredible strength, so that you get smooth, free-from-noise reception of all stations that can be heard in your locality. No matter how bad the man-made interference, no matter how distant the station, the "NOISEMASTER" Outfit will clear out all noise and boost signals anywhere from R4 to R9+!

Here's the secret of its wonderful performance: The "ANTENNEX" Aerial Energiser. The "NOISEMASTER" Aerial Outfit is the ONLY NOISE-REDUCING, SIGNAL-BOOSTING OUTFIT AUTHORISED TO USE "ANTENNEX" . . . the amazing American invention that cuts out noise and peps up sensitivity. You get in the "Noisemaster" Kit, as well, 200 feet of special aerial wire, 12 specially designed transmission blocks, earth clamp, lead-in strip, screws, lightning arrestors, etc. Easy to follow instructions and drawings with each Kit enable you to set up your aerial in a very short time. No testing. No doubt. No delay. Once "Noisemaster" is fitted, your noise-troubles end! Send this special form for your "Noisemaster" Aerial Kit NOW, and get marvellous DX on broadcast and shortwave bands. If you want yours NOW, send this Coupon!

Antennex (A'sia) Agencies,
Kembala Building,
48-60 Margaret Street,
SYDNEY.

Send me right away your "Noisemaster" Kit. I enclose 52/6 in postal notes, money order, cheque. (Add exchange to country and interstate cheques.)

Name.....

Address.....

A.R.W. 5/38.

What's New In Radio

A monthly review of latest releases
in sets, kit-sets, and components

Vealls Release Radio And Electrical Catalogues.

A new departure has been made this year by Vealls, of Melbourne, with regard to their annual catalogue, in that in place of one volume covering both the radio and electrical fields, two catalogues covering these fields separately have been released.

Radio Catalogue No. 38 comprises 58 pages, and covers what is perhaps the most comprehensive range of radio components, kit-sets and receivers carried by a single firm in Australia. For quick reference, seven pages are devoted to a combined Radio Index and Price List, reference also being made to the pages on which complete details and illustrations can be found. The General Electrical Catalogue (No. 38) is equally comprehensive.

Copies of either or both of these newly-released catalogues can be obtained free of charge from any of Vealls stores, or alternatively by writing to Box 2135T, G.P.O., Melbourne, C1., Victoria. In the latter case a 2d. stamp should be enclosed to defray postage.

★

In "Radiotronics" No. 91.

Amplifier enthusiasts will be interested in the circuit and data on the new 17-watt amplifier using push-pull 6L6G's, described in the latest issue of "Radiotronics" (Technical Bulletin No. 91), issued by Amalgamated Wireless Valve Co. Pty. Ltd.

The fidelity curve published is a guarantee of excellent performance, as the second harmonic distortion is below 2.5 per cent. over the entire useful audio range, while third harmonic distortion is below 3 per cent. at all frequencies.

Other articles comprise R.C.A. application notes on the improved type 906 cathode ray tube and on the gas triode OA4-G.

New Radiotron valve releases listed comprise type 1613 (6F6, specially selected for operation on 350 volts and about 40 megacycles, and intended for use in transmitting circuits); and type 1614 (6L6, specially selected for operation on 375 volts at approxi-

mately 42 megacycles in radio transmitters).

The 6L6G beam tetrode power amplifier, which until recently was limited to 135 volts maximum, has now been approved with plate voltages up to 200 volts, while the type 906 3in. cathode ray tube is now available with a new construction having a graphite coating inside the envelope, enabling it to be used with lower voltages.

Accompanying "Radiotronics" No. 91 is a further supply of data sheets covering types 6AF6-G, 6F8-G, 6J8-G, 6K8-G, 6Y6-G, and 302.

★


P.M.G. Type Microphone From Foxtadio.

Of interest to both set-builders and amateur transmitters is the P.M.G. type carbon microphone illustrated below (obtainable from Messrs. Fox & MacGillycuddy Pty. Ltd., 57 York Street, Sydney).

Manufactured by the Automatic Electric Co., of Chicago, U.S.A., the microphone is supplied complete with stand and built-in matching transformer. Of solid construction, it has a sensitivity that compares very favourably with that of the P.M.G. microphone in use throughout this country,



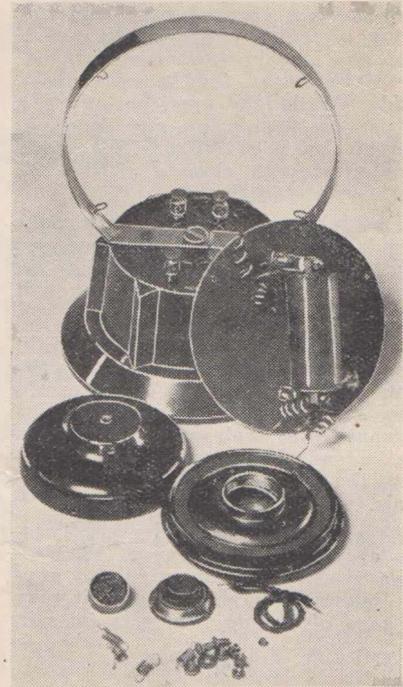The American-made P.M.G. type microphone described in the accompanying review.



The microphone dismantled, showing the solid construction. The transformer is mounted on the base.

and at 12/6 net it represents particularly good value (postage and packing 1/- extra).

★

Vidor "Showboat" Portable Radio From Fear & Co.

Of interest to New Zealand set-builders is the new English Vidor "Showboat" superhet portable radio now being handled by Messrs. F. J. W. Fear & Co., of 31 Willis Street, Wellington, N.Z.

A four-valve battery-operated superhet, the receiver employs an octode frequency changer, pentode i.f. amplifier, duo-diode triode second detector, a.v.c. voltage generator, and first audio amplifier, and a power pentode output valve. Other features include permanent magnet moving coil speaker, full-vision illuminated scale and non-spillable jelly-acid type accumulator. Overall dimensions are 11½ x 10¾ x 7 inches, while weight, complete with batteries, is 20lbs.

Complete details are obtainable free on request from Fear & Co. at the address given above.

★

New N.S.W. Office For Rola Opened In Sydney.

The New South Wales office of Rola Pty. Ltd., Melbourne, which was opened last month, is located on the third floor of Country Traders' House, 116-118 Clarence Street, Sydney (telephone B 5867). In charge is

Mr. G. R. S. Allen, late of George Brown & Co. Pty. Ltd., who has been appointed as resident engineer for the Rola Company in New South Wales.

Full stocks of spare parts are available, and all service work will be carried out at the new headquarters. Stocks of Rola speakers, however, will not be carried, these being available only through the joint distributors, George Brown & Co. Pty. Ltd. and John Martin Pty. Ltd.

To fill the gap created by Mr. Allen's appointment, Mr. Bruce Eaton, formerly of Mullard Pty. Ltd., has joined George Brown & Co. in charge of radio sales and service. Mr. Eaton was associated with Messrs. Fox & MacGillycuddy for ten years as sales manager and secretary, while for the last 2½ years he has been in charge of the valve sales department for Mullard.



Mr. E. Ashworth Rejoins Clyde.

The trade will be interested to learn that Mr. E. Ashworth, well-known battery expert, has rejoined the Clyde Engineering Co. Ltd., to control the production of Clyde bat-

teries at their works at Granville, N.S.W.

Mr. Ashworth has been associated with the manufacture of storage bat-



Mr. E. Ashworth.

teries since the inauguration of Australian manufacture by the U.S.L. Company in 1922. He was production manager at the Clyde battery factory from 1924 to 1926, and in 1927 was retained by the Australian General Electric Company as supervisor of their Melbourne and Newcastle factories.

For a period of two and a half years prior to 1931, Mr. Ashworth was works manager, Century Storage Battery Co. Ltd., Sydney, and for the past seven and a half years was works manager at Vesta Battery Co. (Pty.) Ltd., Leichhardt, and recently visited New Zealand for the purpose of setting up battery production at Wellington.

Mr. Ashworth is a qualified draughtsman and engineer, and is a member of the Electro Chemical Society of America.



Two New Palec Releases.

Two new test equipment releases by Paton Electrical Pty. Ltd., of Ashfield, Sydney, comprise the Pales Model "CJ" oscillograph, using Radiotron type 902 2-inch cathode

He's your best advertisement, Mr. Dealer . . . that every morning shaver who finds such delight in new and electric shaving . . . Packard Lektro Shaving!

List Price
£4-19-6

Inclusive of step-down transformer.

PACKARD

Lektro Shaver

Write or call now to "The Friendly Wholesale House" for full particulars.

JOHN MARTIN PTY LTD  **RADIO & ELECTRICAL SUPPLIES**

"Oh boy, I gotta tell"



TELEPHONE :
BW 3109 (2 lines)

TELEGRAMS :
"JONMAR," SYDNEY

116-118 CLARENCE STREET, SYDNEY.

ray tube, and the Palec Model "RCD" decade box.

The new oscillograph is housed in a black crystalline-lacquered steel case measuring approximately $8\frac{1}{2}$ x 10 x $12\frac{1}{2}$ inches. Included in this case are the cathode ray tube, vertical and horizontal amplifiers, saw tooth oscillator and power supply equipment.

The Model "RCD" decade box has a panel measuring $8\frac{3}{4}$ inches square, overall depth being $5\frac{1}{2}$ inches. The engraved metal panel carries 10 knobs and two pairs of terminals, providing two complete and independent decade systems. One of these is for resistance, and any value between about 2 ohms and one megohm can be obtained in steps of approximately 2 ohms. The remaining decade system is for capacities, and here a complete range of values from about 20 mmfd. to 1 mfd. is available, the steps in this case being about 2 mmfd. on the lower decades.

This new instrument has a wide variety of applications, and should find ready acceptance among servicemen.

Full details of these two Palec releases are obtainable free on request from the Paton Electrical Pty. Ltd. of 90 Victoria Street, Ashfield, N.S.W.



New S.T.C. Four-Valve Electric Mantel Model 410.

This latest release from the S.T.C. factory features the new high slope Brimar output pentode—6AG6-G, and presents what all dealers want, a mantel model with the added appeal of low price.

The cabinet has an attractive crocodile leather finish, and is provided with a large, clearly marked and easily read quasi-edge-lit dial and chromium escutcheon.

This new model has metal-dust core

coils, and is air trimmed. The circuit is a 450 k.c. air trimmed superheterodyne using one stage frequency converter, one stage i.f. amplification, diode detector, resistance-

coupled to a Brimar high slope pentode.

S.T.C. claim that the 410 is a four-valve broadcast radio with five-valve performance.

Radio Book Reviews

"Admiralty Handbook Of Wireless Telegraphy"—1938 Edition.

One of the most popular textbooks used by students of radio engineering is the "Admiralty Handbook of Wireless Telegraphy," which for years has been regarded as a standard work by radio colleges, universities, etc. The 1931 edition has now been superseded by a new 1938 edition, which is divided into two volumes.

The first volume of over 450 pages covers the field of magnetism and electricity. Chapter headings are as follows:—General Introduction; Electricity and Magnetism; Electromagnetism, Inductance and Capacity; Alternators, Generators and Motors; Alternating Currents; The Transformer, Measuring Instruments, R.F. Effects; The Oscillatory Circuit—Damped Oscillations; Three-phase and Polyphase A.C. Systems.

Volume 2 deals entirely with wireless telegraphy theory. It is divided into 11 sections, each section being separately numbered and cross-indexed for ready reference. Section heads are as follows:—The Spark Transmitter; Thermionic Valves, Reception of Electromagnetic Waves; Amplification—Receiver Design; Power Supplies; Valve Transmitters; Radio-Telephony—Sound Reproduction; Propagation of Electromagnetic Waves; Aerials, Feeders, Directional Arrays; Direction Finding; R.F. Measurement—Wavemeters and Oscillators.

At the end of each section is given a selection of typical examination questions, answers being given to mathematical problems.

Each volume contains, in addition to the matter reviewed above, a variety of tables, appendices, and is provided with a comprehensive index.

"Handbook of Wireless Telegraphy" (volumes 1 and 2), 1938 edition. Our copy from Messrs. Angus & Robertson Ltd., 89 Castlereagh St., Sydney. Price 16/6, postage 2/-.
★

"Practical Wireless Service Manual."

Designed to supply the needs of both amateur and professional radio servicemen, "Practical Wireless Service Manual," by F. J. Camm, F.R.S.A., provides an invaluable collection of useful material for all those engaged in the testing and servicing of radio receivers.

Special chapters are devoted to methods of simple testing suitable for amateurs who do not possess elaborate test equipment, while other chapters are designed to appeal to the professional man.

A particularly useful feature of the book is that full constructional details are given of practically all types of test equipment, including an a.c./d.c. multimeter, capacity bridge, vacuum tube voltmeter, audio oscillator, signal generator and valve tester. A particularly useful chapter is devoted to planning a service workshop.

Included among the reference material provided are symbols, abbreviations, wire tables and useful formulae.


"Practical Wireless Service Manual," by F. J. Camm, F.R.S.A., 296 pages, 221 illustrations, first published in 1938. Our copy from Messrs. Angus & Robertson Ltd., 89 Castlereagh St., Sydney, price 7/6, postage 6d.
★

"A.C. Motors Of Fractional Horse Power."

"A.C. Motors of Practical Horse Power," by H. H. Jones is a newly-released manual on the design, construction and maintenance of a.c. motors of all types.

The working principles of a.c. motors—universal, repulsion, induction, synchronous, and eddy current—are explained in detail, and data given for their construction. The treatment of the subject has been kept simple, and no advance mathematical know-

(Continued on page 46.)

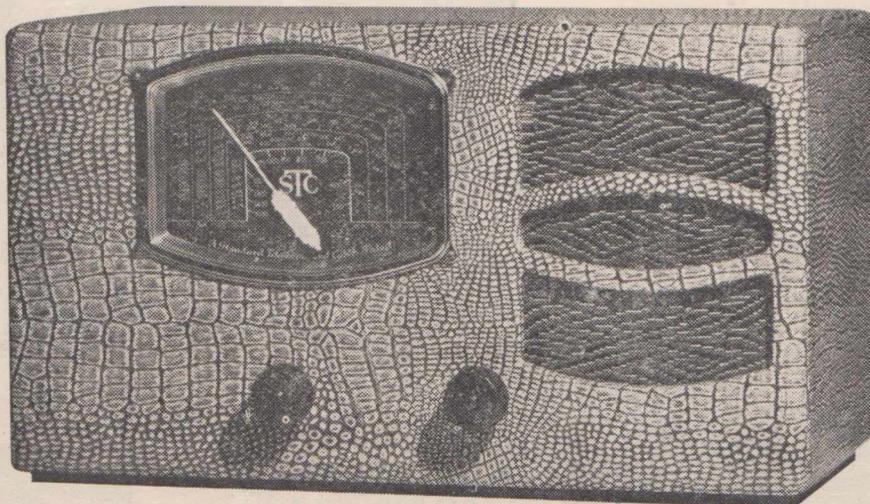

The new S.T.C. Model 410 a.c. four-valve mantel broadcast superhet.

The



All-Wave All-World

Official Organ of the
All-Wave All-World DX Club

DX News



DX Notes And News.

Record For Crystal Set DX?

I noticed in the September issue where a crystal set in Adelaide could get 2FC, 5KA and others. My crystal set here has picked up the following stations:—7LA, 7NT, 5CL, 2FC, 2CO, 5KA, VK5WS, VK5WJ, 3LO and 3AR. The set includes a coil former made from a custard powder carton, .0005 mfd. condenser, crystal detector, .0005 mfd. aerial tuning condenser and 22 D.C.C. wire, built on 3-ply wood base and panel. W. J. Simmons (AW437DX), Port Lincoln, South Australia.

Latest Loggings On "Twenty."

Lately I have been listening quite a lot on the 20-metre band, which has been very active, and my best loggings have been Peru OA4AI, Venezuela YV1AQ, Cuba CO2WM, CO2RA, Japan J5CC, Northern Ireland GI5ZY, Ecuador HC1JW, Burma XZ6DW, Mexico XE1U, Argentine LU4BC, Canal Zone NY2AE, Norway LA1G, PK6XX, and, of course, heaps of KA's, W's, F3's, G's, K6's, PK's, etc.

My latest verifications are from ZBW and VS6AB Hong Kong, 9MI, HBJ Radionations, PK2DF, W7BVL, K6ILW and G2AK. The last-mentioned came to hand just twelve months all but two days after I sent my report.—M. N. Wicks (AW425DX), Balhannah, S.A.

American DX Organisation.

The International Listeners' Association (P.O. Box 745, Dryden, Washington, U.S.A.) is an organisation formed to aid members interested in DX to increase the size of their logs, and to assist them in the collection of QSL and SWL cards. Foreign membership fee in Australian currency is 5/3. President Floyd J. Slosson is interested in exchanging QSL's with readers.

VK-ZL's Logged In Channel Islands.

The following VK2ZL amateurs have been heard here in the Channel Islands recently from September 4 to October 4, on 14 m.c.: VK2's ADE, ADV, AEK, AES, AHG, AIB, AII,

AJF, ANS, CX, DG, EZ, IBK, IG, KZ, LS, NQ, NS, OQ, QZ, RA, SS, TF, TI, TO, VA, VG, WI, YL and YO; VK3's BC, BG, BV, CP, CT, CX, EG, EH, HG, JF, KX, LA, MD, MK, NK, NS, OR, PE, QK, QR, TS, VQ, WA, WL, WX, XP and XU. VK4's BB, DD, GE, JB, JP, KC, PX, SD, UR; VK5's CS, FL, FM, JP, JS, LL, LS, ML, PS, TR and WR; VK6's AF, KO, XI; VK7's AB, LZ, RZ; VK9VG; ZL1's BT, DV, FT, HY, KE, LM, MB; ZL2's BD, CW, FA, GW, LA, NT, QA, SM; ZL3's AJ, AZ, GC, GF, GR, GU, GW, JA; ZL4's AF, AR, BQ, CK, FK, FT, GM, GY; VR4AD and VF6AY.

I am always willing to co-operate with any station by listening for their signals if they will communicate with me direct, giving frequency and times

of operation. In any case, I would be pleased to correspond with any VK-ZL operator. Those requiring to work new countries should listen for G3GS (Channel Islands), 7050, 7190, 14,100, 14,380 k.c., EL2A, ZD2H, ZB2A all on approximately 14,300 k.c.'s, and ZD4AB on approximately 14,320.—M. G. Bourke (G2AOU), "Crediton," Samares, Jersey, Channel Islands, England.

Illness Prevents Dixer Returning QSL's.

Due to illness, A. W. Wilbur has not been able to return numerous S.W.L. cards that have been received from Australia and New Zealand, but will do so when sufficiently recovered in health.

ALL-WAVE ALL-WORLD DX CLUB Application for Membership

The Secretary,
All-Wave All-World DX Club,
214 George Street,
Sydney, N.S.W.

Dear Sir,

I am very interested in dxing, and am keen to join your Club.
The details you require are given below:

Name.....

Address.....

[Please print both plainly.].....

My set is a.....

[Give make or type, number of valves, and state whether battery or mains operated.].....

I enclose herewith the Life Membership fee of 3/6 [Postal Notes or Money Order], for which I will receive, post free, a Club badge and a Membership Certificate showing my Official Club Number.

(Signed).....

[Note: Readers who do not want to mutilate their copies of the "Radio World" by cutting out this form can write out the details required.]



Short-wave Review

CONDUCTED BY

ALAN H. GRAHAM

New Foreign S.W. Stations ★ Change To Summer Conditions ★ Overseas News Broadcasts In English

Angola.

CR6AA is using three new frequencies, as follows: 13,000 k.c., 24.3 m.; 9660 k.c., 31.06 m.; and 7177 k.c., 41.75 m. Schedule is 5.45 to 7.30 a.m. every Thursday and Sunday.

Argentina.

LRA, Buenos Aires, heard recently on 9690 k.c., 30.94 m.

A new station, call unknown, announcing as "Radio Splendid," heard on 17,760 k.c., 16.89 m.

Belgian Congo.

"Radio Leo" is the slogan of a new low-powered transmitter located at Leopoldville. Operates on 6140 k.c., 48.86 m.; power, 25 watts; schedule, 8.35 to 10 p.m. Sundays and holidays, also irregularly at 1 a.m.

Bolivia.

CP-1, Sucre, is new on the air on 9892 k.c., 30.33 m. Operates from 2-3 a.m. daily. Announces as "Radio Chuquisaca."

CP-12, Cochabamba, will soon be on 6150 k.c., 48.78 m. Will use 200 watts and will announce as "Radio Tanari."

British Guiana.

VP3BG, Georgetown, and VP3MR have merged and now use only the former call on 6130 k.c., 48.94 m. Revised schedule is given as midnight-1 a.m. and 5.15-9.30 a.m. daily; Sundays, 8.30 p.m.-2.30 a.m. (Mondays); Mondays, 6-8 a.m.

Chile.

CB-1185, Santiago, is now relaying CB-138. Frequency 11,850, 25.3 m.

Colombia.

Yet another new Colombian, another "Voz de Colombia." This is HJ3ABY, 6120 k.c., 49.0, located in Bogota.

Costa Rica.

Several new stations either on the air or in course of construction.

TIEMC, relaying BCB station

TIEM, on 10,050 k.c., 29.8 m. Announces as "Radio el Mundo." Schedule is 7.20 a.m.-3 p.m. daily. QRA is Apartado 1049, San Jose.

TI2XD, also in San Jose, relays TIXD from 9 a.m.-2 p.m. Announces as "Radio Pilot" on 11,922 k.c., 25.1 m.

TIRA, Cartago, will operate on 6080 and 6090 k.c., 49.34 and 49.26

m., when completed.

Cuba.

From Senor Ricardo F. Rubio, West Indies representative of the "Radio World," comes the very latest re Cuban S/W stations.

COCO relays CMCK. QRA, San Miguel 86, or P.O. Box 98, Habana. Power, 2½ kws.; 6010 k.c., 49.92 m. Schedule, 10.55-2.30 p.m. daily.

COCQ relays CMQ. QRA, Monte 17 esq. a Prado, Habana. Power, 5 kws., 9740 k.c., 30.76 m. Schedule, 9.55-4 p.m. daily. Slogan, "de la crema dental Colgate y el Jabon embelecedor Palmolive."

COBZ relays CMBZ. QRA, San Rafael 14 altos, or Box 866, Habana. Power 250 watts, 9030 k.c., 33.32 m. Schedule, 10.45-4 p.m. daily. Slogan, "Radio Salas."

COBC relays CMBC. QRA, Box 132, Habana. Power, 1½ kws. 9963 k.c., 30.12 m. Schedule 9.55 p.m.-3.15 a.m., except Sundays; Sundays, 9.55-2 p.m. Slogan, "del Progreso Cubano y los Almacenes de Trajes el Gallo."

COCW relays CMW. QRA, Prado 105 altos, or Box 130, Habana. Power, 2½ kws., 6300 k.c., 47.6 m. Schedule, 9.55-3 p.m. daily except Mondays (till 1 p.m.). Slogan, "La Voz del Philco Radio."

COCM relays CMCM. QRA, Box 33, Habana. Power, 1 kw, 9833 k.c., 30.52 m. Schedule, 11-3 p.m. daily except Mondays (till 2 p.m.). Slogan, "Transradio Columbia."

COBX relays CMBX. QRA, San Miguel 194, Habana. Power 500 watts, 9200 k.c., 32.59 m. Schedule, 11-2.30 p.m. daily. Slogan, "de los talleres de Radio Alvarez."

COCA relays CMCA. QRA, Galiano 102, Habana. Power 100 watts. 9100 k.c., 32.97 m. Schedule, 11-3 p.m. daily.

COCB relays CMCB. QRA, Box 2294, Habana. Power, 250 watts, 6130 k.c., 48.94 m. Schedule, 1 a.m.-2.30 p.m. daily except Mondays (till noon). Slogan, "La Voz del Aire."

COCH relays CMCF. QRA, Box 41 Habana. Power, 5 kw., 9437 k.c., 31.8

DX Club Requirements.

All-Wave All-World DX Club members are advised that the following DX requirements are obtainable from Club headquarters, 214 George Street, Sydney.

REPORT FORMS.—Save time and make sure of supplying all the information required by using these official forms, which identify you with an established DX organisation. Price, 1/6 for 50, post free.

NOTEPAPER.—Headed Club notepaper for members' correspondence is also available. Price, 1/6 for 50 sheets, post free.

DX CLUB STICKERS.—Enlarged two-colour replicas of the Club badge, in the form of gummed stickers, designed for attaching to envelopes, QSL cards, etc. Price, 5 dozen for 1/6, post free.

DX CLUB LOG SHEETS.—Designed by the Shortwave Editor, these headed and ruled log sheets are indispensable to dxers who wish to keep a simply-prepared and accurate list of loggings. Price, 3 dozen for 1/6, post free.

m. Schedule, 11-3 p.m. daily. Slogan, "de la General Electric."

COCX relays CMX. QRA, Box 32, Habana. Power 2 kw., 11,740 k.c., 25.55 m. Schedule, 11-4 p.m. daily.

COGF relays CMGF. QRA, General Betancourt 51, La Playa, Matanzas. Power, 250 watts, 11,800 k.c., 25.43 m. Schedule, 11-1 p.m. daily except Mondays (noon-1 p.m.). Slogan "Ecos del Valle del Yumuri."

COHB relays CMHB. QRA, Box 85, Sancti Spiritus. Power, 2 kw., 6280 k.c., 47.77 m. Schedule, midnight-1 a.m., 3.30-4.30 a.m., 7-10 a.m. and noon-2 p.m. daily.

COJK relays CMJK. QRA, Finlay 3 altos, Camaguey. Power 1 kw., 8665 k.c., 34.6 m. Schedule, 1.30-3.30 a.m., 10 a.m.-2 p.m. daily. Slogan, "Radio Zenith."

COKG relays CMKG. QRA, Box 137, Santiago de Cuba. Power 2400 watts, 8935 k.c., 33.81 m. Schedule, 11-3 p.m. daily. Slogan, "Emisoras Grau."

Curacao.

PJC-1, Willemstad, is on 9590 k.c., 31.28 m.; and PJC-2. same location, on 15,220 k.c., 19.71 m.

Ecuador.

HCJB, Quito, has lately been heard testing on a new frequency, namely 12,460 k.c., 24.2 m.

Finland.

The new Finnish station at Lahti has a 19 metre frequency 15,190 k.c., 19.75 m.). Its schedule is: Weekdays, 3-5 p.m.; Mondays, 3-4 p.m.

French Indo-China.

The new S/W transmitter at Hanoi is operating on 11,900 k.c., 25.21 m. Announces as "Ici Radio Hanoi," signing with "La Marseillaise." Programme is partly native and Chinese, and partly French. Closes at midnight.

Iraq.

Baghdad has a new station which is on the air several times a week on an irregular schedule. Frequency is 7110 k.c., 42.2 m. Power is 500 watts.

Irish Free State.

Athlone is the location of the new Eire station soon to be on the air. It will transmit on the following frequencies: 6190 k.c., 48.5 m.; 9595 k.c., 31.27 m.; 11,740 k.c., 25.55 m.; 15,120 k.c., 19.83 m.; 17,840 k.c., 16.8 m.

India.

The latest available information regarding the new Indian stations is as follows:—

9590 k.c., 31.28 m., VUD-2, Delhi; 11.30 a.m.-1.30 p.m., 4.30-6.30 p.m., 10.30 p.m.

4995 k.c., 60.06 m., VUD-2, Delhi; 10.30 p.m.-12.30 a.m.

15,160 k.c., 19.79 m., VUD-3, Delhi; 11.30 a.m.-1.30 p.m.; 4.30-6.30 p.m.

9590 k.c., 31.28 m., VUD-3, Delhi; 10.30 p.m.-12.30 a.m.

9550 k.c., 31.41 m., VUB-2, Bombay; 12.30-1.30 p.m., 4.30-6 p.m.

4905 k.c., 61.16 m., VUB-2, Bombay; 10 p.m.-midnight.

4950 k.c., 60.3 m., VUM-2, Madras; 10 p.m.-midnight.

9530 k.c., 31.48 m., VUC-2, Calcutta; 5.06-7.06 p.m.

4880 k.c., 61.44 m., VUC-2, Calcutta; 9.54 p.m.-12.06 a.m.

In addition to the above stations, which are already on the air, VUD-4, Delhi, will shortly commence operations on 9550 and 15,290 k.c., 31.41 and 19.62 m.

Italy.

Stations IRF, 9830 k.c., 30.52 m., and IQY, 11,676 k.c., 25.67 m., are still carrying relays from 2RO, Rome.

Martinique.

Fort de France, announcing "Ici Radio Martinique," has increased its power from 200 watts to 1½ kws. 9700 k.c., 30.9 m. Call FZF-6 (?).

Netherland Indies.

YDA, Bandoeng, now uses a new frequency, 7410 k.c., 40.46 m.

Nicaragua.

YN3DG, which was heard as an

'amateur, is the call of a new station using the slogan "Estacion Gilfillan," at Leon. On 7130 k.c., 42 m., from 12.15-12.30 p.m. (From Senor Rubio, Cuba.)

Panama.

New schedules for the Panama stations, HP5G and HP5J:

HP5G, 11,780 k.c., 25.47 m., from 9 a.m.-1 p.m.

HP5J, 9604 k.c., 31.24 m., from 3-4.30 a.m., 9:30 a.m.-1.30 p.m., and 4-6.30 p.m.

Paraguay.

ZP-8 is a new station on 9264 k.c., 32.4 m. Heard from 9-11.30 a.m.

Poland.

SPW-SPD are now relayed by SP-19 and SP-25 on 16,120 k.c., 19.83 m., and 11,700 k.c., 25.65 m., respectively.

Portugal.

Several changes are reported in the operation of station CSW. CSW-3 is now on 9670 k.c., 31.03 m. (previously 9737 k.c.). CSW-3 also on 9740 k.c., 30.7 m., operating a new schedule to Mozambique (3-5 a.m.), to Europe (8-9 a.m.), and to North America 9-11 a.m.). CSW-4 has a new frequency, 11,840 k.c., 25.35 m. On the air, 9-11 a.m. Power to be increased to 50 kws.

Have Your "RADIO WORLD" Posted To You Direct

Readers who want to take the "Radio World" on a subscription basis and have their copies posted to them direct each month are invited to complete the coupon below (annual sub. 10/6). New readers are advised that all back numbers in Volumes 1 and 2 are still available, price 9d., post free for copies in Volume 1 (May 1936 to April 1937) and 1/-, post free, for copies in Volume 2 (May 1937 to April 1938).

Enclosed please find remittance for 10/6, in payment for an annual subscription to the "Australasian Radio World," commencing with the..... issue.

Name.....

Street and No.....

City..... State.....


Country.....

Note.—N.Z. Subscribers can remit by Money Order or Postal Note.

THE AUSTRALASIAN RADIO WORLD, 214 George Street, Sydney, N.S.W., Australia.

RAYWAY

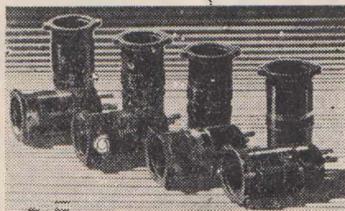COIL KITS ARE
SPECIFIED
EXCLUSIVELY
for the . . .



AMATEUR COMMUNICATIONS EIGHT
.. and the ..



ATLAS ALL-WAVER!

(See descriptions elsewhere in this issue)

Precision-wound on moulded formers of the highest-grade imported bakelite, every RAYWAY coil is scientifically planned to give the last ounce of gain from the lowest to the highest frequency covered.

★

Used for the "Atlas All-Waver," the new RAYWAY 15 to 600-metre Amateur All-Wave Coil Kit gives continuous coverage from 15 to 600 metres.

Each kit is packed in a solidly-built box intended for use as a permanent container. A pamphlet included with each kit shows under-socket connections of coils, together with their colour code.

Rayway 15 to
600-metre
Amateur All-
Wave Coil Kit

25/-

If unobtainable from your local dealer, write direct to:—

Standardised Products

629 PARRAMATTA ROAD,
LEICHHARDT, SYDNEY
N.S.W.

'Phone LM 5957

Salvador.

YSP, San Salvador, 10.400 k.c., 28.8 m., Spanish news at 1.30 p.m. Spain.

A new propaganda station at Victoria is reported on 11,950 k.c., 25.1 m., around 7 a.m. daily.

Sweden.

The latest available schedule for p.m.-midnight; Sunday, 6-7.15 p.m.; m., is 2-5 15 a.m., 4.20-5 p.m., and 9 p.m.-midnight; Sunday, 6-1.15 p.m.; Thursday, 11 a.m.-noon.

Switzerland.

A new station at Berne is testing irregularly on 9535 k.c., 31.46 m. It is usually on the air in the very early a.m.

Turkey.

A powerful new station in the morning hours is "Radio Ankhara." It uses either 9465 or 15.195 k.c., 30.0 or 19.7 m. Closes at 7 a.m.

United States.

A new high-frequency transmitter, W9XTA, Harrisburg, was granted a construction permit with 500 watts power. Will operate on 26,500 k.c., 11.3 m.

W9XA, Kansas City, will be on regular schedules very soon on 26,450 k.c., 11.33 m.

★

Change To Summer Conditions

With the change to summer conditions now becoming noticeable, dxers will find the best overseas reception during the evening hours. The higher frequency bands are now providing good results, and will continue to improve. Now is the time when 13, 16 and 19 metres provide real DX after 8.30 p.m.

Morning reception at present is still fairly good, particularly from the Americans. During the period between 9 a.m. and 2 p.m. those who have both time and opportunity would do well to watch the U.H.F. bands. At present 11 metres is good, W6XKG, W9XJL and W9XUP (the last mentioned a new station not yet listed in any publications to hand) all putting through fairly strong signals. The 9.49-metre B.C. band is definitely disappointing and will continue so until the many transmitters there are assigned new and different frequencies; several reports have been received that the F.C.C. in America were to re-allot frequencies, but as yet no sign is apparent in actual reception.

Police stations are frankly not up to last year's standard as yet. Several loud signals are easily logged, especially Los Angeles, but there is no trace of many stations heard in 1937. By the way, new police stations will no longer use the old experimental calls (i.e., including the letter "X"), but will be given regula-

tion four-letter calls (as W amateurs).

★

Overseas News Broadcasts In English.

Many readers will undoubtedly be interested in the details given below of news broadcasts in English. These should be found of particular interest in view of the troubled conditions in both Europe and Asia.

Japan.

JZK, 19.79 m., 5.35 a.m.

JZJ, 25.42 m.; 5.35 a.m., 11.55 p.m.

JVN, 28.14 m.; 7.55 p.m.

Italy.

2RO-3, 31.13 m.; 10.40 a.m.

Czecho-Slovakia.

OLR4A, 25.34 m.; 7.30 a.m.

Spain.

EAQ, 30.4 m.; 6.45 a.m.

Switzerland.

HBO, 26.31 m.; and HBJ, 20.64 m.; 5.30 and 6 p.m.

France.

TPB-7, 25.24 m.; 2 p.m.

TPA-4, 25.6 m.; 2 p.m.

TPB-11, 31.35 m.; 7.15 p.m.

TPA-2, 19.6 m.; 10 p.m.

Germany.

DJB, 19.74 m.; DJD, 25.49 m.; 1.30 p.m.

DJB, DJN, 31.4 m., DJS, 13.8 m., DJE, 16.89 m., DJQ, 19.6 m.; 10 p.m. and 12 midnight.

★

Reports From Observers.

Mr. C. Anderson (West Australia).

This month I have spent considerable time on the "ham" bands, particularly 20 metres. Conditions on this band have varied considerably from day to day—at times reception was very poor indeed, only a few VK's being audible. 10 metres has also been very disappointing—not many stations there, and those heard are only at very moderate strength.

The U.H.F. broadcast bands have been poor, even allowing for the fact that my receiver is not 100% efficient on these frequencies. JZK has been heard opening at 1.30 p.m. on 9.8 metres—obviously an harmonic of their 19.79-metre frequency—strength is about R5, QSA4-5.

Early this month FZE-8, Djibouti, French Somaliland, was logged on 17.3 metres (R6-7, QSA5). They were calling Paris, and closed at 8.30 p.m.

One morning a Spanish-speaking station was logged on about 42 metres. The conclusion of the announcement was ". . . quartro erray, Espana." I do not think there is much doubt that this was EA4R, on 42.5 metres. Time was 6.30 a.m.

(All times are Perth time.)

Broadcast Stations Logged.

13 metres: GSJ, GSH, PCJ.
 16 metres: W3XAL, GSG, DJE.
 17 metres: FZE-8.
 19 metres: LRU, SP-19 (very weak), OLR5A, RV96, HAS-3, JZK, Daventry and Berlin (various frequencies).
 20-22 metres: KHQ, HPJ, SPW.
 25 metres: W8XK, W1XAL, 2RO, OLR4A, COCX, VLR-3, JZJ, Hankow, Daventry and Berlin (various frequencies).
 31 metres: COBC, JDY, ZHP, CSW, EAQ, COCM, TI4NRH, FZF-6, TGWA, COCQ, LRX, CS2WA, COCH, W3XAU, W1XK, W2XAF, KZRM, ZBW.

32 metres: COBZ, HAT-4.
 41-45 metres: EA4R (42.5), PMH.
 49 metres: ZGE, ZHO, 9M1, VFR, Rangoon, W3XAU, FIU, VQ7LO.
 58-100 metres: PMY, Indians 60-62 m., YDL-2 (62 m.), RV15, and other Java stations around 86-90 m.
 Mr. W. H. Pepin (West Australia):
 During the past month conditions were satisfactory, although varying a good deal from day to day on all bands.

13 metres: GSJ is heard nightly around 7 p.m., reaching a peak at 8 p.m.; usually fades around 9.30 p.m., although occasionally remains audible till 11 p.m. W2XE and PCJ (very strong at times).

16 metres: W3XAL (fair), GSG (erratic), PH1.

19 metres: YDC, RV96, Berlin, W8XK. One morning at 8.30 a.m. a station believed to be VUD-3, Delhi, was logged on 19.79 m. Signals strong.

25 metres: W8XK, 2RO, TPA-4 (mornings), JZJ, Saigon.

27 metres: PMN and PLP (very strong).

28 metres: JVM.

30-31 metres: JDY, YDB, KZRM, ZBW and VUB (nights); COCQ, W2XAD, GSC, GSB and COCH (mornings).

49 metres: ZGE, ZHP and VUC (strong above noise level).

58-100 metres: PMY (strong), YDL-2, Indian station on 62 metres, RV15, YDA (98).

(Times are Perth time.)

All amateur fans are advised to keep a look-out for W4DLH (14,210 k.c.) on January 4 or 5, 1939, on his all continents hook-up with Europe, Africa, Asia, Australia and South America. W4DLH will attempt to break his record of 12 minutes established this year.

Mr. G. O. La Roche (West Australia).

DX has been good this month, and quite a few "not so often logged" sta-

tions were noted. Generally speaking conditions are very good from 7 p.m. to 8 a.m.; with daylight reception falling off. (Perth time.)

16 metres: TPB-3, PH1, W2XE.
 19 metres: W1XAL, TPA-2, OLR5A, W8XK, RV96, JZK, YDC and HVJ.

24 metres: TFJ.

25 metres: RNE, IRF, TPA-3, W8XK, OLR4A, 2RO, JZJ, W1XAL, OLB4B, TPA-4, CR7BH, Hankow (XTJ?).

27-29 metres: PLP, JVN, ORK, PMN.

30-32 metres: CSW, EAQ, COCQ, Saigon (30.7), IRF (30.52), ZHP, JFAK, TI4NRH, CS2WA, 2RO, ZRK,

ROUND THE SHACKS

Amateur operators desirous of having their transmitters and activities featured under this heading are requested to forward details to "Reporter," C/- "Radio World," 214 George St., Sydney. Articles should be similar in style to those already appearing in the series, and should, where possible, be accompanied with photographs of operator and transmitter.

VUB, W3XAU, KZRM, TPB-11, YDB, VPD, W2XAF, ZBW, OZF, XEWW, COCH, COBC, COBX.

44-47 metres: PMH (44), TG-2 (47), COHB (47).

48-50 metres: ZGE, VPB, COCD, YDA, VQ7LO, SBG, COCO, Rangoon.

52 metres: YV2RA.

58-100: PMY, YDL-2, RV15, YDQ-3 (89.95), YDA and VUD-2 (60), and VUB-2 (61).

Mr. A. E. Bruce (South Australia).

Reception during the past month has varied quite considerably. I have had some unusual loggings at times, but often the 20 metre amateur band has been very poor.

The 13 and 16-metre bands have been very good in the evenings, Daventry being very strong. 31-metre reception has been so poor that I am beginning to wonder whether my receiver is functioning properly on this band.

I have done a little listening to the "outback" stations on 56 metres in the evenings, and they come in fairly well, though sometimes marred by static. 8TJ and 8TW are best of these transmitters.

10 metres has been disappointing—only a few W's and ZL's.

Mr. R. S. Coggins (South Australia).

Conditions in Woodville have been very patchy of late, although the 20-

metre amateur band has improved somewhat of recent weeks, and some fair loggings have been made.

London and Berlin come in very well on all bands between 13 and 49 metres.

Mr. J. Ferrier (Victoria).

Conditions below 11 metres have been fairly good. The 10 metre amateur band is very good around 9 a.m., W's, K6's and even a few South Americans.

Occasionally I log a very weak station on 30.3 m.c., relaying KGMB Honolulu. No call has yet been heard.

The Police bands have been rather dull. Only W6XPA, Los Angeles, puts in a strong signal (R9).

The 31.6 m.c. broadcast band is still mainly a strong heterodyne whistle. It is almost impossible to identify any station.

W9XJL, Superior, is the best of the 11-metre stations.

Mr. H. A. Callander (Tasmania).

Reception on almost all bands (13-85 metres) has improved slightly during the past month, and some very interesting DX has been obtained at times.

GSH (13.97) puts in a very good signal around midnight; also DJS (13) DJQ and DJE. KZRM is a strong signal on 31 metres at 11 p.m.

JZJ (25.4) has been heard testing with America at 11.45 p.m. Announcements are made in both English and Japanese, and reports are requested—a verification being guaranteed.

On 31.58 metres PRF-5 has been putting in a strong signal, with occasional announcements in English. After each item three notes are struck on a gong.

Amateur DX on the 20-metre band has been extremely interesting. Some good loggings include XU, PK6, HC, LU, F18, NY, ZS and VP7.

Mr. A. R. Payten (New South Wales).

It certainly pains me to have to forward such a poor report, but reception has been very disappointing, with QRN holding sway.

Morning reception has been especially poor, only VLR-3 (25), and HVJ, Vatican City (50) putting in anything like a good signal; the others are very weak and irregular.

During the day scarcely a signal is audible.

The evenings provide what little DX there is on offer.

19 metres: JZK, Daventry and Berlin.

25 metres: OLR4A, GSD, JZJ, Paris, RNE and Berlin.

27 metres: CSW, ZLT-4, PLP.

28-29 metres: ORK, JVN.

30-31 metres: VPD, KZRM, ZBW, HS8PJ, VUB, ZHP.

39 metres: JVP.

44 metres: JVT and PMH (probably loudest signal).

48-50 metres: 9MI, YDA.

The only amateur loggings of note was HC1JW. Recent verifications from HS8PJ and JVP.

Mr. E. Neill (Queensland).

Conditions here have been rather peculiar during the past two or three weeks. One morning I was up at 5 a.m., and shortly after any number of G's were rolling in on 20 metres, R6-8. Yet on subsequent mornings things were so dead that I began to suspect that my rig was "phut." The last day or two things have been much nearer normal, and all sorts of real DX is rolling in. At present the 20-metre band is FB, with LU's a nice R7.

Recent loggings include XEUZ, 49.03; OAX4J, 32.15; and an Hawaiian station (KU ?) on approximately 20 metres relaying to W2XAF.

The usual English and German stations are as strong as ever all round the clock. Incidentally, I had the pleasure of hearing my name in the letter-box session from DJQ.

RNE is very strong in the early a.m.; also TPB-7, 25.24 m.

Mr. J. C. Linehan (South Australia).

Recent verifications to hand may be of interest. A card from VS2AL, Fed. Malay States, verifies reception of his 5-watt 'phone sigs. FZE-8, Djibouti, French Somaliland, verify by letter; they mention that reports from Australia are very rare. Schedule is given as 4.05-4.30 p.m., their time. (From 11.05-11.30 p.m. Aust. E.S.T.)

Also received recently a letter from XTJ, Hankow, 11,691 k.c., 25.66 m. They gave details as to address, etc., but these are not of much use now.

Generally speaking, DX conditions have not been as good as during the previous month, with the exception of 10 metres, where reception has been good. A number of amateurs have been logged—K6, W, PK1, CO, TI, KA, OA and ZL. W6NWK was using only 20 watts when logged.

The 11-metre broadcast band has been rather poor recently—only W6XKG and W9XJL being audible, and they are weak. On 13 metres GSJ and DJS are good; while the 19-metre band is very good indeed during the early part of the evening.

CR7BH are the outstanding DX on 25 metres, and are very strong from 12.05-1.30 a.m. They also operate on 48.87 m. (CR7AA), and on 189.57 m. On 31 metres things are good in the evenings, ZHP being very consistent. 49 metres has fallen off, al-

though conditions are sometimes fair in the early mornings.

Amateur cards to hand include FA3HC, CO2KY, ON4DM, XZ2DY, VE4ZK, VE4SS, CO2OM, PAOEO, and W6NWK (10 m.).

PK1VY is very anxious to receive reports on his 10-metre 'phone.



Amateur Review.


Loggings On 10 And 20 Metres.

The following list of amateur loggings was compiled from information supplied by Observers La Roche, Pepin, Anderson (West Australia); Linehan, Bruce, Coggins (South Australia); Callander (Tasmania); Ferrier (Victoria); Payten (New South Wales) and Neill (Queensland).

10 METRES.

Europe: SU1RO, Egypt: HB9CE, Switzerland (Ferrier).

South America: PY2AK, PY2MI,

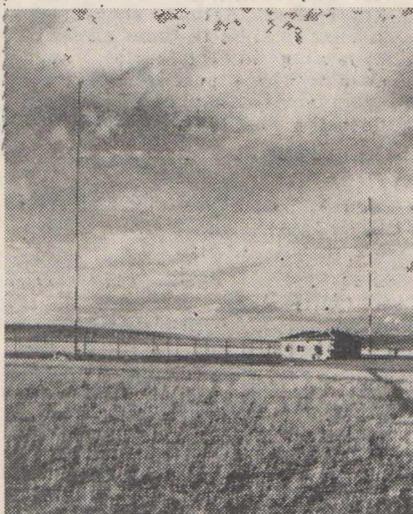

A general view of the aerial masts and station building housing a group of traffic transmitters recently installed by Philips at the Yesilkoy aerodrome, near Stamboul, in Turkey.

Brazil (Ferrier); OA4R, Peru; TI2LR, Costa Rica (Linehan).

West Indies: CO2WM, Cuba (Linehan).

North America: W9CXU, W6NWK, W6ANU, W6LWN, United States (Linehan, Bruce); K7GTP, Aleutian Is. Ferrier).

Philippine Is.: KA1ER (Linehan, Anderson).

Hawaiian Is.: K6LCV, K6OTH (Linehan, Anderson).

Dutch East Indies: PK1VY (Linehan, Anderson); PK6XX (Ferrier).

New Zealand: ZL—1GZ, 1HY, 1JD, 2BE, 2BT, 3BB, 3KZ, 1FY (Bruce, Anderson, Linehan).

20 METRES.

Europe—

France: F3JD, F8QD, F8NT, F8XT, F8KT, F8VP, F8DW (Anderson, Linehan, La Roche, Neill, Coggins).

Great Britain: G6DT, G6WX, G8KT, G5BI, G2HK, G6DL, G5JO, G8NV, G6FS, G8FS, G8TB, G6PC, G6ML, G5ML, G2CV, G2XB (La Roche, Anderson, Neill, Linehan); G16B (La Roche).

Portugal: CT1BW. (La Roche).

Switzerland: HB2KG (Coggins).

Norway: LA6N (Neill), LA1G (Linehan).

Italy: I1MS.

Belgium: ON4AJ, ON4VZ (Anderson).

Africa—

Egypt: SU1MW, SU1JM (Anderson, Linehan).

South Africa: ZS6DW, ZS6AJ, ZS2AH, ZS6EF, ZS2BT, ZS1BL, ZS5BZ, ZS6BG, ZS5AW, ZS6EG, ZS6CZ, ZS5AB, ZS5TL (Anderson, Linehan, Neill, Callander, Pepin, La Roche).

South Rhodesia: ZE1JU (La Roche).

Kenya: VQ4KTB (La Roche).

Mozambique: CR7AU (Neill).

South America—

Chile: CE3AP (La Roche).

Uruguay: CX2AR (La Roche).

Ecuador: HC1FG, HC1JW, HC2HP, HC2AT, HC2CG, HC2CM (La Roche, Payten, Linehan, Neill, Callander).

Argentina: LU4BC, LU1HI (Linehan, Anderson, Coggins, Bruce, Callander).

Venezuela: YV5AK, YV5ABQ (Coggins).

Brazil: PY2JK, PY2JC (Neill, Coggins).

Peru: OA4AI, OA4I (Linehan).

Central America and West Indics.

Cuba: CO2WM, CO7CX, CO2LY, CO6OM (La Roche, Neill, Anderson, Linehan).

Haiti: HH2B (Callander, Linehan).

Honduras: HR5C (Callander, Neill).

Bahamas: VP7NS, VP7NU (Callander, Neill).

Canal Zone: NY2AE (Coggins, Neill, Anderson).

Mexico: XE3AR (Coggins, Anderson).

British Honduras: VP1BA (Anderson).

Costa Rica: TI2FG, TI3AV (Anderson).

Barbados: VP6R, VP6TR (Linehan).

Asia—

Ceylon: VS7GJ, VS7RF, VS7JW (La Roche, Callander, Pepin, Anderson, Bruce, Linehan).

India: VU2BG, VU2CA, VU2DR, (Continued on page 44.)

HOURLY TUNING GUIDE

When and Where To Search

Compiled by ALAN H. GRAHAM.

In order to assist beginners and less experienced dxers, it is intended to publish monthly a special tuning guide, setting out at what times to listen for the more easily logged stations. It should be noted that the guide is not intended to cover all stations audible; for full details as to when and where to look for the best catches are given elsewhere. Moreover, the fact that a station is shown as being on the air at a particular time is no guarantee that reception must follow as a matter of course.

All times are given in Australian Eastern Standard Time.

Key to abbreviations used: S, Sundays only; M, Mondays only; T, Tuesdays only; W, Wednesdays only; Th, Thursdays only; Sat, Saturdays only.

Midnight-1 a.m.	19.74 DJB
13.99 DJS	19.8 YDC
16.89-DJE	19.82 GSF
19.63 DJQ	19.84 HVJ
19.68 TPA-2	19.85 DJL
19.7 OLR5A	25.0 RNE
(exc. M, S)	25.24 TPA-3
19.74 DJB	25.4 2RO-4
19.8 YDC	25.34 OLR4A
19.82 GSF	(exc. S, M)
25.34 OLR4A	25.49 DJD
(exc. M, S)	27.27 PLP
25.4 2RO-4	28.48 JIB
25.42 JZJ	29.24 PMN
27.27 PLP	31.3 VUD
28.48 JIB	31.35 TPB-11
29.24 PMN	48.7 VPB
30.78 COCQ	49.83 DJB
30.96 ZHP	49.9 COCO
31.28 VK2ME	58.3 PMY
(M)	60.0 VUD
31.3 VUD	60.6 VUM
31.38 DJA	61.4 VUC
31.49 ZBW-3	70.2 RV15
31.55 HS8PJ	

2-3 a.m.

31.58 XEWW	16.23 HBH (M)
31.8 COCH	19.71 PCJ (Th)
32.9 COCB	19.74 DJB (M)
33.2 COBZ	19.82 GSF
48.7 VPB	19.85 DJL
49.9 COCO	25.24 TPA-2
49.98 Rangoon	25.4 2RO-4
58.3 PMY	25.49 DJD
60.0 VUD	25.53 GSD
60.6 VUM	31.3 VUD
61.4 VUC	31.35 TPB-11
70.2 RV15	48.7 VPB
98.6 YDA	49.31 VQ7LO

1-2 a.m.

13.99 DJS	60.0 VUD
16.23 HBH (M)	60.6 VUM
16.89 DJE	61.4 VUC
19.63 DJQ	
19.68 TPA-2	19.71 PCJ (Th)
19.7 OLR5A	19.85 DJL
(exc. S, M)	25.24 TPA-3

3-4 a.m.

19.71 PCJ (Th)	19.71 PCJ (Th)
19.85 DJL	19.85 DJL
25.24 TPA-3	25.24 TPA-3

25.49 DJD	(T, Th, Sat.)
25.53 GSD	25.0 RNE
31.13 2RO-3	25.24 TPA-3
31.35 TPB-11	25.34 OLR4A
31.55 GSB	25.42 JZJ
49.31 VQ7LO	25.49 DJD
49.59 GSA	25.53 GSD
49.83 DJC	27.17 CSW
60.0 VUD	30.4 EAQ
60.6 VUM	31.13 2RO-3
61.4 VUC	31.28 PCJ (W)

4-5 a.m.

19.65 W2XE	31.35 W1XK
19.71 PCJ (Th)	31.35 TPB-11
19.85 DJL	31.55 GSB
20.64 HBJ (M)	40.83 DJC
24.52 TFJ	43.1 2ZB

7-8 a.m.

25.24 TPA-3	19.56 W2XAD
25.49 DJD	19.65 W2XE
25.53 GSD	19.72 W8XK
29.04 ORK	19.7 OLR5A
31.13 2RO-3	(W)
31.3 VUD	19.76 GSO
31.35 TPB-11	19.79 JZK
31.55 GSB	19.82 GSF
44.94 HBQ (M)	19.85 DJL
49.31 VQ7LO	25.0 RNE
49.83 DJC	25.24 TPA-3

5-6 a.m.

16.87 W3XAL	25.34 OLR4A
19.56 W2XAD	25.42 JZJ
19.6 GSP	25.45 W1XAL
19.65 W2XE	25.49 DJD
19.67 W1XAL	25.53 GSD
19.72 W8XK	27.17 CSW
19.79 JZK	30.4 EAQ
19.85 DJL	31.09 CS2WA
20.64 HBJ (M)	31.13 2RO-3
22.0 SPW	31.28 W3XAU

(T, Th, Sat)

24.52 TFJ	31.32 GSC
25.24 TPA-3	31.35 TPB
25.34 OLR4A	31.35 KZRM
25.42 JZJ	31.35 W1XK
25.48 DJD	31.41 OLR3A
25.53 GSD	(T)
27.17 CSW	31.48 W2XAF
28.93 EAJ43	31.55 GSB
29.04 ORK	43.1 2GB
31.13 2RO-3	49.83 DJC
31.28 PCJ	49.92 OLR2A

(M, T, W)

31.35 TPB-11	58.31 OK1MPT
31.55 GSB	
39.95 JVP	
44.94 HBQ (M)	
49.59 GSA	
49.83 DJC	

6-7 a.m.

16.87 W3XAL	19.72 W8XK
19.56 W2XAD	19.74 DJB
19.6 GSP	19.76 GSO
19.65 W2XE	19.79 JZK
19.67 W1XAL	19.82 GSF
19.72 W8XK	25.0 RNE
19.79 JZK	25.24 TPA-3
19.85 DJL	25.34 OLR4A
22.0 SPW	(M, S)

8-9 a.m.

19.56 DJR	19.72 W8XK
19.63 DJQ	19.74 DJB
19.65 W2XE	19.76 GSO
19.7 OLR5A	19.79 JZK
(M, S)	19.82 GSF
25.24 TPA-3	25.0 RNE
25.34 OLR4A	25.24 TPA-3
(M, S)	25.34 OLR4A

25.42 JZJ	31.45 DJN
25.45 W1XAL	31.48 W2XAF
25.49 DJD	31.49 LKJ1
25.53 GSD	31.55 GSB
25.60 TPA4	

11 a.m.-noon.

28.9 EAJ43	19.56 DJR
30.04 COBC	19.6 GSP
30.31 CSW	19.63 DJQ
30.4 COCM	19.7 OLR5A
30.43 EAQ	19.74 DJB
30.7 COCQ	19.79 JZK
31.06 LRX	25.26 W2XK
31.09 CS2WA	25.34 OLR4A
31.13 2RO3	25.42 DJZ
31.27 HBL (S)	25.49 DJD
31.28 W3XAU	25.53 GSD
31.32 GSC	25.61 TPA4
31.35 KZRM	31.13 2RO3
31.35 W1XK	31.25 RAN
31.45 DJN	31.28 PCJ
31.48 W2XAF	(M, T, Th, F)
31.49 LKJ1	31.32 GSC
31.55 GSB	31.38 DJA
31.58 XEWW	31.45 DJN
31.8 COCH	31.48 W2XAF
38.48 HBP (S)	31.55 GSB

9-10 a.m.

19.56 DJR	19.56 DJR
19.56 W2XAD	19.56 DJR
19.6 GSP	19.66 GSI
19.63 DJQ	19.71 PCJ (W)
19.7 OLR5A	19.74 DJB
19.72 W8XK	25.26 W8XK
19.74 DJB	25.42 DJZ
19.8 YDC	25.49 DJD
22.0 SPW	25.53 GSD
25.34 OLR4A	25.60 TPA4
25.42 JZJ	31.28 PCJ (F)
25.45 W1XAL	31.32 GSC
25.49 DJD	31.38 DJA
25.51 OLR4B	31.48 W2XAF
25.53 GSD	31.55 GSB
25.61 TPA4	
30.31 CSW	
31.06 LRX	
31.09 CS2WA	
31.13 2RO3	
31.27 HBL (S)	
31.32 GSC	
31.35 W1XK	
31.38 DJA	
31.45 DJN	
31.49 LKJ1	
31.48 W2XAF	
31.55 GSB	
38.48 HBP (S)	
49.1 GSL	

Noon-1 p.m.

19.56 DJR	19.56 DJR
19.66 GSI	19.66 GSI
19.71 PCJ (W)	19.74 DJB
19.74 DJB	25.26 W8XK
25.26 W8XK	25.42 DJZ
25.42 DJZ	25.49 DJD
25.49 DJD	25.53 GSD
25.53 GSD	25.60 TPA4
25.60 TPA4	31.28 PCJ (F)
31.28 PCJ (F)	31.32 GSC
31.38 DJA	31.38 DJA
31.48 W2XAF	31.48 W2XAF
31.55 GSB	31.55 GSB

1-2 p.m.

19.56 DJR	19.56 DJR
19.66 GSI	19.66 GSI
19.74 DJB	19.74 DJB
25.42 DJZ	25.42 DJZ
25.49 DJD	25.49 DJD
25.53 GSD	25.53 GSD
25.61 TPA4	25.61 TPA4
31.28 PCJ (F)	31.28 PCJ (F)
31.32 GSC	31.32 GSC
31.38 DJA	31.38 DJA
31.48 W2XAF	31.48 W2XAF
31.55 GSB	31.55 GSB

10-11 a.m.

19.56 DJR	25.61 TPA4
19.6 GSP	31.48 W2XAF
19.63 DJQ	
19.7 OLR5A	
19.74 DJB	
19.8 YDC	
25.26 W8XK	
25.34 OLR4A	
25.42 DJZ	
25.49 DJD	
25.53 GSD	
25.61 TPA4	
26.31 HBO (M)	
31.13 2RO3	
31.25 RAN	
31.28 PCJ	
(M, T, Th)	
31.32 GSC	
31.38 DJA	

2-3 p.m.

25.61 TPA4	25.61 TPA4
31.48 W2XAF	31.48 W2XAF

3-4 p.m.

13.99 DJS	13.99 DJS
16.89 DJE	16.89 DJE
19.63 DJQ	19.63 DJQ
19.74 DJB	19.74 DJB
19.79 JZK	19.79 JZK
19.85 DJL	19.85 DJL
30.04 COBC	30.04 COBC
31.28 VK2ME	31.28 VK2ME
31.38 DJA	31.38 DJA
32.15 OAX4J	32.15 OAX4J
32.59 COBX	32.59 COBX
33.26 COBZ	33.26 COBZ
49.18 W3XAL	49.18 W3XAL
49.5 W8XAL	49.5 W8XAL

NEWS!

LATEST IN RADIO TEXTBOOKS

NEW EDITION ADMIRALTY HANDBOOK of WIRELESS TELEGRAPHY

Now in two large volumes
(size 9in. x 11in.)

CONTENTS OF VOL. 1

General Introduction —
Electricity and Magnetism —
Electromagnetism, Inductance and Capacity —
Alternators, Generators & Motors—Alternating Currents —
The Transformer, Measuring Instruments, R/F Effects—
The Oscillatory Circuit: Damped Oscillations—
three-phase and Polyphase A.C. Systems.

CONTENTS OF VOL. 2.

The Spark Transmitter—
Thermionic Valves — Reception of Electromagnetic Waves —
Amplification — Receiver Design —
Power Supplies — Valve Transmitters —
Radio-telephony — Sound Reproduction —
Propagation of Electromagnetic Waves—
Aerials, Feeders, Directional Arrays—
Direction Finding—R/F Measurement—
Wave-meters and Oscillators —
Appendices.

Send For Your Copy To-day

ORDER FORM.

Angus & Robertson Ltd.,
89 Castlereagh St., SYDNEY.
Please send me a set of the
"Admiralty Handbook of Wireless Telegraphy 1938" 2 vols.,
for which I enclose 18/6 (16/6 +2/- for postage).

NAME
ADDRESS

4-5 p.m.	31.28	VK2ME (S)	32.09	COBC	29.24	PMN	
13.99	DJS	31.38	DJA	32.59	COBX	30.61	XGOX
16.89	DJE	31.45	VPD2	44.64	PMH	30.78	COCQ
19.63	DJQ	31.49	ZBW3	46.8	TIPG	30.9	ZHP
19.74	DJB	31.55	VK3ME	48.7	VPB	30.96	ZHP
19.79	JZK	34.0	VPD3	49.5	W8XAL	31.28	VK2ME (S)
19.85	DJL	43.1	ZZB	49.96	HPSK		VUD
20.64	HBJ (M)	44.64	PMH	49.98	Rangoon	31.3	VUD
25.24	TPA3	70.2	RV15	58.3	PMY	31.35	W1XK
26.31	HBO (M)			60.0	VUD	31.38	OAX4T
31.28	VK2ME	9-10 p.m.		60.6	VUM	31.38	DJA
31.35	TPB-11	13.99	DJS	61.4	VUC	31.49	ZBW3
31.38	DJA	16.89	DJE	70.2	RV15	31.51	HS8PJ (Th)
49.5	W8XAL	19.58	OLR5B			31.8	COCH
		19.63	DJQ	11 p.m.-midnight.		32.09	COBC
5-6 p.m.		19.68	TPA2	16.88	PHI	32.59	COBX
13.99	DJS	19.7	OLR5A	16.89	DJE	33.2	COBZ
16.86	GSG	19.71	PCJ (W)	19.56	DJR	44.64	PMH
16.89	DJE	19.74	DJB	19.63	DJQ	48.7	VPB
19.63	DJQ	19.8	YDC	19.68	TPA2	49.5	W8XAL
19.74	DJB	19.82	GSF	19.74	DJB	49.9	COCO
19.76	GSO	19.85	DJL (M)	19.79	JZK	49.96	HP5K
19.82	GSF	25.0	RNE (W)	19.8	YDC	49.98	Rangoon
25.23	TPA3	25.4	2RO4	19.82	GSF	58.3	PMY
25.52	GSD	25.57	Saigon	19.85	DJL	60.0	VUD
28.14	JVN	27.27	PLP	25.4	2RO4	60.6	VUM
31.28	VK2ME (S)	28.14	JVN	25.42	JZJ	61.4	VUC
31.35	TPB-11	29.24	PMN	27.27	PLP	70.2	RV15
31.38	DJA	30.23	JDY				
31.55	GSB	30.61	XGOX				
		30.96	ZHP				
		31.28	VK2ME (S)				
6-7 p.m.		31.28	VK6ME				
13.99	DJS	31.38	DJA				
16.86	GSG	31.45	VPD2				
16.89	DJE	31.49	ZBW3				
19.31	PCJ (Th)	31.55	VK3ME				
19.63	DJQ	34.0	VPD3				
19.74	DJB	43.1	ZZB				
19.76	GSO	44.64	PMH				
19.82	GSF	48.7	VPB				
25.23	TPA3	49.5	W8XAL				
25.52	GSD	58.3	PMY				
28.14	JVN	70.2	RV15				
31.28	VK2ME (S)						
31.38	DJA	10-11 p.m.					
31.55	GSB	13.99	DJS				
		16.88	PHI				
		16.89	DJE				
7-8 p.m.		19.58	OLR5B				
13.99	DJS	19.63	DJQ				
16.89	DJE	19.68	TPA2				
19.63	DJQ	19.74	DJB				
19.71	PCJ (Th)	19.8	YDC				
19.74	DJB	19.82	GSF				
25.57	Saigon	19.7	OLR5A				
28.14	JVN	19.85	DJL (M)				
31.38	DJA	25.4	2RO4				
31.49	ZBW3	25.42	JZJ				
31.55	VK3ME (S)	25.57	Saigon				
		25.65	HP5A				
8-9 p.m.		27.27	PLP				
13.99	DJS	28.14	JVN				
16.86	GSG	29.24	PMN				
16.89	DJE	30.23	JDY				
19.63	DJQ	30.61	XGOX				
19.68	TPA2	30.78	COCQ				
19.71	PCJ2 (Sun)	30.96	ZHP				
		31.28	VK6ME				
19.74	DJB	31.28	VK2ME (S)				
19.8	YDC		VUD				
19.82	GSF	31.3	VUD				
25.4	2RO4	25.57	Saigon				
25.57	Saigon	31.35	W1XK				
27.27	PLP	31.38	DJA				
28.14	JVN	31.49	ZBW3				
29.24	PMN	31.8	COCH				
30.96	ZHP						

Amateur Review.

(Continued from page 42.)

VU2FS, VU2FH, VU7FY, VU2JL, VU2LQ (Pepin, Bruce, Linehan, Neill, Anderson).

China: XU8RB, XU8MD, XU6TL, XU8ET (La Roche, Linehan, Neill, Anderson).

Indo-China: FI8AC (La Roché, Callander).

Hong Kong: VS6AG, VS6AO (La Roche, Bruce, Anderson).

Japan: J5CC, J2MI, J2OI (La Roche, Callander, Linehan).

Burma: XZ2DY, ZX2EZ, XZ2JB (Bruce).

Malaya: VS2AE, VS2AB (Bruce). Oceania, etc.—

Philippine Is.: KA—1JM, 1CS, 3KK, 1AP, 1DW, 1FT, 1AF, 7EF, 711B, 1YL, 1AM, 1HS, 1BH, 1ZL, 7ES, 3BW, 1KM (La Roche, Bruce, Callander, Coggins, Linehan, Neill, Anderson, Pepin).

Netherland Indies: PK—1BY, 1GL, 3NM, 2AY, 1RL, 3WI, 2WL, 1VM, 1RI, 1VY, 1ZZ, 1MD, 6ON, 4AY, 1TT (Bruce, Callander, Anderson, La Roche, Pepin).

New Guinea: PK6XX, VK9XX, VK9DK (Callander, Bruce, La Roche, Linehan, Pepin).

Hawaiian Is.: K6—LKN, OJI, MVA, BNR, OQE, ILW, OTH, LEJ, CGK, LKN, OBC, MTE, MXM (Bruce, La Roche, Anderson, Coggins).

Pitcairn Is.: VR6AY (La Roche, Anderson, Callander).

DX News and Views

A page for
letters from
DX readers

Time-Saving DX Forms.

I have been dxing for eighteen months, but the writing of two-page reports for "veries" soon tired me. The Club Report Forms have been a boon, and I started all over again, but I don't worry the "hams" for cards except on B.C. I have reports out to the following:—

B.C. (daylight) VK's 4JN, 4EA, 4XW, 4RJ and 4LW. Shortwave, YDC, KQH, HBJ, PCJ, VPD2, KZRM, HJ6ABH, HI20, ZBW3. Also a new stranger—"This is Singapore calling"—not found in the "R.W."—on about 9.82 megacycles.

QRN has been rather bad on s.w. in the past fortnight, but otherwise stations have been quite good until 2 a.m.—B. R. Ferris, Proston, Q'land.

10-Metre Coil Gives Promising Results.

My dx listening every night covers the band from 10 to 90 metres. I have just wound a 10-metre coil for my receiver, and have obtained promising results from it. I have coupled a 1938 model Mullard super. through an audio transformer to the output terminals of my present receiver; this amplifies my signals considerably. The Mullard super. uses a 42, 6F7, 6A7 and an 80 rectifier.

Conditions on the 20 m. band have not been very good lately, my best loggings being W1AW, W1OM, W5ZS, W6JT, W6CO, W3EOZ, W2JKQ, W2AZ, W4BY, W6BKY, HI7G, K6ILW, K66AD, K6KMP, K6MTE, K64BC, PK1VY, KA1ZM, VU2CQ. GSQ (13 m.) has been coming in at an average strength of R8-9. KZRM (31 m.) and PCJ (19 m.)—D. E. Tolley, Grove Street, Unley Park, Adelaide, S.A.

S.W. Bands In Review.

Lately I have been too busy listen ing to DX to think about writing, but now for some DX news. Starting from B.C. and working down, 2CA Canberra (2000 w.) has now started a midnight-to-dawn programme and is asking for reports from listeners. What is wrong with the boys on the 160 m. band?—there are usually only about four VK's and one ZL on this band. The 80 m. band is usually very lively with VK's and ZL's, but QRN is beginning to creep in, so this band

is losing its popularity. The 40 m. band is good in the afternoons and early evenings, a few W's on c.w. with good strength when not QRM'd by VK 'phones. 20 metres is good in spots, the usual W and VE 'phone stations coming through in the early evening. A few South Americans can be heard in the late evenings, but the band is very dead in the early mornings (2-4 a.m.) and is not worth waiting for.

Moscow has been romping in on 60 m., but it seems as though attempts have been made to interfere with this station on 49 metres. The American and Java station have their usual fight for supremacy until Java closes down about midnight. The 31 m. band has shown signs of improving, and the new station at Singapore comes through on about 30-48 m., closing down at 12.45 a.m. (E.A.S.T.). All the other bands are as usual. My receiver is a 4-tube t.r.f., 1C4 r.f., 32 det., 30 transformer-coupled to 33.—S. E. Molen (AW213DX), Kingaroy, Q'land.

OFFICIAL S.W. OBSERVERS.

N.S.W.: V. D. Kemmis (AW-301DX), "Brampton Hall," 49 Kurraba Road, Neutral Bay, Sydney; A. R. Payten (AW352-DX), High Street, Coff's Harbour.

SOUTH AUSTRALIA: J. C. Linehan (AW323DX), 181 South Terrace, Adelaide; A. E. Bruce (AW171DX), C/- 54 Currie Street, Adelaide; R. S. Cogging, 8 Glen Rowan Road, Woodville.

QUEENSLAND: J. K. Sorensen (AW316DX), "Fairholme," Station Road, Gympie; E. Neill (AW64DX), 26 Canning Street, Nth Ipswich.

WEST AUSTRALIA: G. O. La Roche (AW155DX), 62 Gladstone Avenue, South Perth; W. H. Pepin (AW402DX), Seventh Avenue, Maylands; C. J. Anderson (AW417DX), Dumbleyung.

TASMANIA: H. A. Callander (AW304DX), 1 Franklin Street, West Hobart.

VICTORIA: J. Ferrier (AW-129DX), "Winniburn," Coleraine.

Has 228 Verifications.

It's quite a while since I wrote to the Club, but I have not given up DX. I now have 228 verifications, which include:—79 VK2's, 22 VK3's, 41 VK4's, 6 VK5's, 3 VK6's, 1 VK7 and 1 VK9. Also CN8AM, CR6AA, CSW, CT1AK, CT2AB, EA9AH, F8XT, G5SK, G5VE, G5ZZ, G6AK, G81W, HA8N, HI6F, HA8PJ, J3DE, KZRM, OER2, PK1BX, PK3ST, PK3GD, PY2HM, SPW, SU-1KE, SU1SG, SM5SX, TI5JJ, VS2AK, W3EGG, W3GIF; W5's AD, GDZ, GSJ, OH, SY; W6's AAN, ACL, BCA, BOG, CBK, CQF, CON, FUD, GUU, HAS, LHF, FQK, ICI, IRZ, IZB, JIH, JJB, LGL; W7's AVC, FQK, GKW, GNQ; W8XWT, YV1RH, ZT2G, ZT6AZ, ZT6AL, Z7KG, ZU6P, ZUIT, ZU6E, ZWB. Besides these I have 161 SWL cards.

Overseas reception has not been very good these last few weeks, but seems to be improving a little now. I have been busy building a one-valver using an RK43 (or a 19). The beauty of the RK43 is that it runs off a 1½ volt torch cell, and I have logged dozens of Americans. I am also experimenting with a new antenna system and think it should work O.K. Before concluding I would like to congratulate you on your very fine publication, "A.R.W."—M. W. Eglington (AW268DX), Murwillumbah, N.S.W.

W8XK Verifies Report Sent On Official Club Form.

Regarding W8XK mentioned as a station that will not verify, I have their card—a yellow one with orange-coloured call letters and black print—sent promptly after a report on our official forms. Cards to hand this month are from U.S.A., Italy, New Zealand and Canada. The veri. from 2RO has broken all records, being very prompt indeed. I have sent reports this week to South American, Dutch Guinea, and French Indo-China being outstanding.—Gordon Young (AW245DX), Brisbane, Queensland.

Amateurs Logged On Twenty.

Just a few lines to let you know I am still receiving cards through using the Club's QSL forms, my most recent being from KZRM, 2LF and VK5LW.

The following amateurs have been heard lately on the 20 m. band:—2W1's, 7W2's, 1 W3, 3W4's, 2 W5's, 12 W6's, 1 W7, 3 W8's, 2 W9's,

KA1JM, PK4JP, K4EMG, K6OQE, K6BNR, K6OGR, VE1EH, VE5NK. Commercials: Rangoon 49.94 m., ZBW 31.49 m., COCQ 30.78 m., and KQH 20.11 m.—Wm. Bantow (AW353DX), 237 Point Nepean Road, Edithvale, S.14, Victoria.

Details of Sets And Aerials Wanted.

Regarding the QSL card contest, I would like to suggest that a list be printed of members who have forwarded their cards. I think other club members would appreciate this.

Another suggestion I would like to make is that contributors to the DX news page give particulars of their receiver, antenna system, etc., when writing of their station loggings, not forgetting the direction in which antennas are running. I think this will meet with the approval of every reader and create a certain amount of interest. We are all anxious to get the maximum efficiency from our receiving apparatus, and I think the co-operation of readers on the suggestion just mentioned will help to make it possible.

I have tried a number of antenna systems, and the one that gives me the most satisfaction at my location is a half-wave doublet for 20 metres, running 10 degrees west of north. Dimensions of antenna are 16ft. 6ins. each side of a pyrex insulator, with twisted pair feeders three $\frac{1}{4}$ wavelengths long. Being mostly interested in the 20-metre and 19-metre band, I have found this the most efficient antenna so far. I intend erecting a similar antenna running at right angles to the existing one, thereby probably giving me a 360-degree coverage.

The receiver is an A.G.E. six-valve super with 175 k.c. i.f.'s and a converter is coupled to this using an EK2, and covering from approximately 16 to 50 metres. In conclusion, I would like to add that I am sure members of the club appreciate the action of Mr. J. C. Linehan, of Adelaide, in making the QSL card contest possible.—Charles Jarlett (AW38DX), 26 Edith Street, Hurstville.

333DX Logs "Hot Air Social Club."

Following on a report in the "Mail" re "The Hot Air Social Club," discovered by Dr. Wilson, Flying Doctor, on his recent tour of the north, you may be interested to know that while spinning the dial on Tuesday evening at 9.15 p.m. I tuned in to the "Club."

Two-way conversations are carried on, and there are eight members of the Club, some hundreds of miles apart. The signals came through at R max. on the "Empire."

Stations heard were Wyndham, Angorinchina, 8PJ, Curramoona and Twin Station. Wavelength used is just above the 49.9-metre band. The

signals did not fade, Angorinchina in particular being very strong. Wyndham causes interference at times, working on the same wavelength as the "Club."

The new Flying Doctor base is to be established at Round Hill, about 5 miles from Broken Hill. The Central Wireless Station—installation started this week—will be in direct communication with stations within a 400 miles radius of Broken Hill. The Flying Doctor intends to make regular broadcasts and with the transmitter set, will keep in constant touch with outback stations. Radio advice on minor ailments can thus be given. Some Club members may have heard these two-way conversations; in any case they are very interesting.—H. H. Young (AW333DX), Angaston, South Australia.

Three Enzedders Logged On B.C.

DX conditions here in Western Australia have not been too good, but I managed to log the following stations: 1YA, 2YA and 4YA. HS7PJ Bangkok was logged on the 12th ult. on a wavelength of approximately 750 m. The Japanese are coming in at R4, QSA 3, JOAK1, JOBK1, JOCK1, JOIK and JBCK being the most consistent. I hear the stations better in W.A. than I did while in New South Wales, but so far have failed to log any Americans. I think I will have to change my set to a shortwave model.—G. A. McLennan (AW384DX).

Radio Book Reviews.

(Continued from page 36.)

ledge is required for the solution of the various formulae.

The practical details given of construction, coil winding, testing and repair should prove invaluable for those who have to deal with the care and maintenance of fractional h.p. motors.

"A.C. Motors of Fractional Horse Power", by H. H. Jones, first published in 1938. Our copy from Messrs. Angus & Robertson Ltd., 89 Castlereagh St., Sydney. Price 11/3, postage 6d.

"An Elementary Wireless Course For Beginners."

Written by J. H. Reyner, B.Sc., A.M.I.E.E., and the staff of "Radio Pictorial" and "Television and Shortwave World," "An Elementary Wireless Course For Beginners," now in its third and revised edition, is a book intended for those wanting to gain a working knowledge of how a receiver operates. Written in simple non-technical language, the book treats the entire theory of radio in the simplest and clearest possible way.

To help the reader visualise some of the more difficult principles and theories, the authors have devised many unique analogies, which are not only explained but wherever possible are illustrated as well.

U.H.F. DX Improving Rapidly.

DX on the ultra high frequency bands is coming back to normal in leaps and bounds after the dull period during the winter. The 33.1 meg. band is open again, and to-day I heard the following police stations: W6XHR Monrovia, W5XB Fort Worth, W6XMW Arcadia, W6XM Stockton, W6XEH Longbeach, and W6XWA with W6XWF, which I heard testing but did not get their QRA's.

The 30.1 meg. band has not improved much in the last month, except that W6XPA at times reaches R9+, W2XEM coming a good second. There is no sign of the 9.49-metre broadcast band yet, but within the next month I think these bands should be very good. I have not been doing much on the other bands, but 20 m. is getting better now in the evenings.

I am running my receiver off a genemotor and have been spending most of my spare time trying to filter it.—James Ferrier (AW129DX), Coleraine, Victoria.

Club Forms Bring Good Results.

I have been getting excellent results by using the Club's report forms—they are great time and trouble savers. The stations I have received reports from are as follows:—

2KA, 2MC, 2TM, 2KO, 2HR, 2HD, 2MW, 2LM, 2CR, 2NZ, 2WG, 2KM, 2CA, 2LF, 2DU, 2BE, 2AY, 2GN, 2GF, 2GZ, 2WL, 2NR, 2BL, 2FC, 2CH, 2GB,

The first three chapters are devoted to an explanation of the principle of tuning. Chapters on detection follow, and on the general theory of the thermionic valve. Towards the end of the book a typical three-valve chassis is analysed in detail, the purpose of every component and the principle underlying its design explained.

"An Elementary Wireless Course for Beginners", by J. H. Reyner, B.Sc. (Hons.), A.M.I.E.E., and the staff of "Radio Pictorial" and "Television and Shortwave World". Third revised edition. Our copy from Messrs. Angus & Robertson Ltd., 89 Castlereagh St., Sydney. Price 5/3, postage 6d.

Coils For EK2G Octode

(Continued from page 31.)

within the 50-150 microamp. range. These current values have been quoted as a guide to circuit adjustment and similar values within reasonable limits should ensure satisfactory performance so far as the mixer stage is concerned.

The short wave coils have been designed to cover a wave range of 16-51 metres, and to ensure this coverage, every precaution must be taken to limit stray capacities associated with the tuned circuits.

—Philips Radio Technical Service.

2UW, 2SM and 2RG. Victoria: 3HA, 3SR, 3KZ, 3RO, 3LK, 3DB, 3TR, 3BA, 3WV, 3GI, 3AW, 3UZ, 3XY, 3GL. Queensland: 4BH, 4SB, 4BC, 4AK, 4QG. South Australia: 5RM, 5DN, 5AD, 5PI, 5MU. Western Australia: 6WA. Tasmania: 7LA, 7HT, 7UV, 7EX, 7HO. New Zealand: 1YA, 2YA, 3YA, 4YA, 1ZB and ZJV Suva Fiji.

Shortwave stations logged include VK2ME, VK3ME, VK6ME, VPD2, KZRM, DJB, VLR, W1XK, W2XAF and 2ZB.


All the stations were logged on a 5-valve Radiola. In a few days I am having their 9-valve all-wave model installed.—C. R. Woolsey (AW403-DX), Terrigal, N.S.W.



Tuned Doublet Gives Excellent All-Wave Results.

I have ordered parts for the "Battery Communications Seven" and hope to have the receiver completed next month.

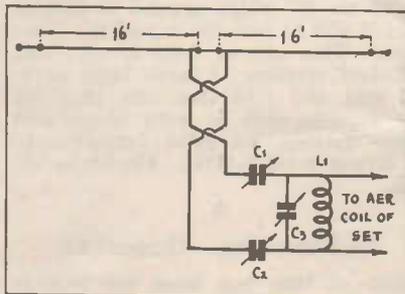At present I am using a 1935 battery five-valve Radiola using a 6A7, 34, 34, 6B7 and 38 output pentode.



This is still serving faithfully, and with several alterations is giving excellent results. I use with it the r.f. amplifier described in your pages some time back, and this results in a tremendous gain, and has been particularly helpful on 14 megs., though noise level has been particularly high lately. I also have a one-tube 2½, 5 and 10-metre job which I built some time back, but have not yet had the time to get down to it and get it going. It uses a 6C5 as a super-regenerative detector.

I now have my receiver and aerial tuners on a rack and panel assembly by my radio table. A small clock is mounted in it, illuminated by a hidden 6.3v. light. I made the panel large with the idea of adding transmitting equipment at a later date. I am using at present a Zepp aerial designed for 14 megs. running N. & S. with optimum reception E. & W. feeders are transposed, and are 60 feet long. These are tuned and I find that this type of aerial works well as an all-wave aerial. The results on 200-550 metres are outstanding. In case anyone would like to try this, then details are shown in the sketch.

C₁, C₂ and C₃ are 250 mfd., and L₁ is 154 turns of 30 enam., tapped at 77, 38, 19, 10, 5 and 2½ turns. Before feeders are brought towards the receiver, they should descend vertically from the antenna for at least ¼ wavelength; in this case, 16 feet.

I am listing below the list of amateurs positively logged on 14 megs. this month, and on consulting my log book find that it represents 16½ hours listening in the morning and late afternoons. I have at the moment about 200 reports out.

Europe: France, F8VP, F8BA; England, G6BO, GM8BD, G5BJ, G5LK, G2TR, G5NI, G8SB, G6BY, G3BM, G2WP, G5BA, G8CH, G5ML, GH3BD, G2DS, G6BW, G2MI, G2AV; Holland, PAOAD, PAOFP, PAOMF; Hungary, HA4A, HA8N.

Asia: India, VU2BG, VU2AC, China, XU8RV; Hawaii, K61LW, K6OQE, K6MIE, K6BNR; West Indies, PK4JD, PK2AY, PK2WI, PK2RK; Phillipines, KA2OV, KA4LH, KA1AP; Burma, XZ2FZ.

North America: U.S.A., 1 W1, 9 W2's, 1 W3, 3 W4's, 5 W5's, 21 W6's, 1 W7, 2 W8's, 4W9's. Central America: Canal Zone NV2AF; Costa Rica, TI2AV, TI2FG and TI3FE. South America: Peru, OA4JN, OA4C; Venezuela, YV1AP, YV5ABQ. Colombia, HK3LC, HJ1EF. West Indies: Porto Rica, K4EMG. Santo Domingo, HI3A, HI5A.

Conditions are up and down, though for the most part the band is very noisy. I sometimes manage to get in a few minutes when home to lunch and have had some success around 1 p.m. our time, such stations as OA4C, G5LK, G2TR, G6BW, TI3FE, G2AV, F8RV, ON4AJ, G2BY, W6AM being heard among others. There are many that cannot be logged owing to bad QRN or QRM—Joseph Bull (AW146-DX), Beria, W.A.




A De Luxe DX Outfit.

My receiver is an eight-valve tri-wave; frequency range:—528-1730 k.c., 1.71-5.8 m.c., 5.75-18.3 m.c. The valves used are 6K7 r.f., first det., and i.f., 6C5 oscillator, 6Q7 first a.f., second detector, a.v.c., 6F6 output, 5Z4 rectifier and 6G5 "magic eye." It has an 8" electro-dynamic with two-speed tuning (automatic) variable i.f.'s and a "movie dial." This dial has an automatic bandsread on "80" of 4ins., "40" 3ins., and on "20" 2ins.; it works on the same system as a movie projector. This "Airline" I have is made in Chicago and is the sample model that came to Wellington.

I am using three antennas, but am still experimenting with them. My location is on a hill top (700ft.) overlooking Wellington Harbour, and apart from QRN, reception is 100 per cent. The earth is a 10ft. iron pipe

sunk in wet ground and filled with salt.

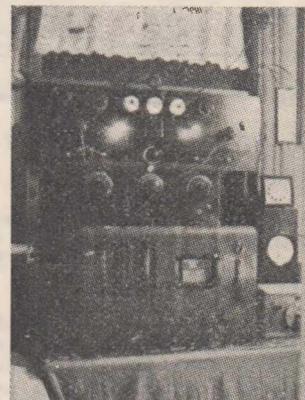In the photo, the switches behind the set operate the antennas, and the three dials operate "pots," shunted across the pickup (a Rothermel brush) and it is possible to have wide-range reproduction. On the right of the set is my antenna tuner, and it works so well that I have enclosed a diagram of it. Behind the antenna tuner is an oblong case inside of




Dxer Raymond Kelly, of Wellington, sent in this view of his listening post. He operates an eight-valve tri-wave American superhet.

which is a globe, so that when the door is opened the light goes out, being a convenient way of knowing someone wants to enter—otherwise difficult with QRN going R max. An electric clock which tells the time in any part of the globe, and the two small lights on the switchboard which automatically light when the pick-up comes to the end of the record, completes the outfit here.

During this year s.w. reception has not been 100 per cent., due no doubt to solar activity, which we are told is taking place this year—a cycle every 11 years. We are in early Spring here, and s.w. during daylight is fast disappearing, but on the other hand, evening s.w. is improving. 20 metres has been poor, and I find that between 8 p.m. and 2 a.m. (N.Z.T.) a few "VK's," "W's," and "PK's" reach R7 on peaks. I have received a veri. from Singapore on 30.49 m., and also have a report out to PK6XS—Archbold 1938 Expedition, New Guinea, on 14 m.c. He was telling a VK that no QSL cards were available until they arrived back in New York—a year hence!

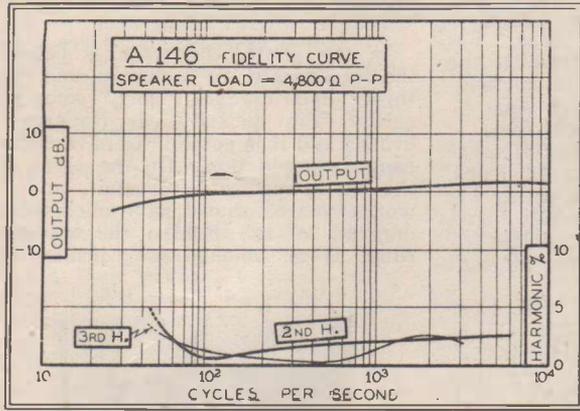The broadcast band so far has been 100 per cent.; noticeable is the numerous American and Japanese stations that "beat" with the carrier waves of most of the Australian stations. Apart from that conditions are very good, with not much QRN.—Raymond Kelly (AW397DX), Wellington, N.Z.



This set of curves reveals the excellent overall response, with low second and third harmonic distortion, obtained from the amplifier.

Push-Pull 6L6G Amplifier.

(Continued from page 8.)

that at full signal output the input voltage to the first stage is 0.24 volt R.M.S., and the gain reduction factor in the 6L6G's is 2.35.

The curve of output versus frequency on a loudspeaker load is shown in the smaller diagram, and it will be seen that the output remains practically constant over a very wide range of frequencies.

The second harmonic distortion is below 2.5 per cent. over the whole of the useful audio range, while the third harmonic distortion is extremely low over the most important part of the frequency range and is below 3 per cent. at all frequencies. This harmonic distortion is as measured over the whole amplifier from the input to the first stage. The amplifier may therefore be claimed to "satisfy" all the requirements of fidelity, while it is also sufficiently robust to be used in any application.

Due to the use of feedback, high voltages are not developed in the 6L6G plate circuit, and there is therefore no likelihood of damage being done to these valves by accidental overload. There is no necessity for the 6L6G valves to be specially matched since they are operating almost under class A₁ conditions.

Power Supply Details.

The power supply incorporates a 385-385 volt 175 m.a. transformer and 5V4G rectifier. A two-stage filter is necessary. The first filter choke is rated at 30 henries 175 m.a. and the second is the field of the loudspeaker. This field will receive energisation to the extent of 12.5 watts at zero sig-

nal, and reaching just under 14 watts with maximum signal. If the first filter choke has a lower resistance than 500 ohms, it will probably be found necessary to add further resistance in series in order to maintain the plate-to-cathode voltage of the 6L6G's at 275 volts on maximum signal. The rise of plate voltage at zero signal is quite permissible, and does not exceed the plate or screen dissipation of the valves.

The characteristics of the amplifier are shown in tabulated form for average valves, but it will be understood that individual valves may show discrepancies from these figures, depending on the individual cathode currents of the valves. However, the variations, which will be found to occur, are comparatively slight, and not sufficient to result in any appreciable change in plate and screen voltage.

Certain variations in the plate currents of power valves are always to be expected, and are no appreciable detriment, particularly when self-bias is used. If fixed bias is used, it may be necessary to take additional precautions such as an individual bias adjustment for each valve.

An Interesting Experiment.

I have taken the "Radio World" since the first issue and look forward to receiving it each month, as it contains some very interesting items and circuits. I am contemplating building the "Air Ace Four."

Just around here where I am living are the Glass House mountains, a group of seven mountains all in an area of roughly five square miles, and ranging from 995 to 1740 feet high. I am going to climb these, taking a

A146 AMPLIFIER CHARACTERISTICS.

	Zero Signal	Max. Signal	
Plate to Cathode 6L6G Voltage	286	275	Volts
Screen to Cathode 6L6G Voltage	286	275	Volts
Total Amplifier Current	158	167	mA.
Grid Bias 6L6G	18.85	19.85	Volts
Field Energisation	12.5	13.95	Watts

portable s.w. job, and will test reception results. The mountains are mainly made up of ironstone, so it should be interesting to see what happens.

My house is situated right at the bottom of Beerburum mountain, and I find that reception on 265 metres and 255 metres is very weak, but others come in o.k.—D. H. Fowler (AW385DX), Beerburum, Q'land.



Cheap Plug-In Coils.

I have built the "1937 Communications Eight" described in "Radio World" and think that while it is a wonderful set, it would be much better if it had a.v.c. in it. The European stations come romping in, but they fade considerably, and I was wondering if you could let me know if it would be best to put in an a.v.c. or use a three-band doublet which was described a few months ago.

The aerial I am using is 40ft. high x 100ft. long, and is situated in a north-east-south-west direction. By the way, here is a little hint which I would like you to publish in the "R. W":

Get some old valve bases and cut the pins out of one or two. Then file about an 1/8" ridge around it just so that it will fit into the top of the other base. This can be held firmly with celluloid cement. I have built several sets and find that this idea for the plug-in coils is very cheap and saves cutting up good formers.—L. F. Evans (AW351DX), Christchurch, N.Z.




Re-Finishing Aluminium

DX of late has been too bad to waste time and power on. However, I heard Daventry in the morning session giving their news in Italian and Portuguese, which made it appear rather confusing at first. The 20-metre band has joined the "Legion of the Lost," I think, because at my location I can hardly hear any DX worth while.

I would like to thank all the DX members who sent their cards in answer to my request.

I have attached to my speaker the baffle that was described in the April "Radio World," and find that it is a wonderful improvement.

The following kink may be useful to readers: There is many a set-builder using aluminium panels for the front of their receivers, etc., who inadvertently get them badly scratched. The appearance can easily be restored by rubbing the panel with a piece of fine emery paper in one direction. Then, using the same emery paper, only attached to a small cork or something similar, make circular motions all over the panel in equal rows. This gives a nice frosted appearance, similar to that of the panel of the "Tom Thumb Portable Two."—W. M. Chapman (AW112DX), Waterloo, Sydney.

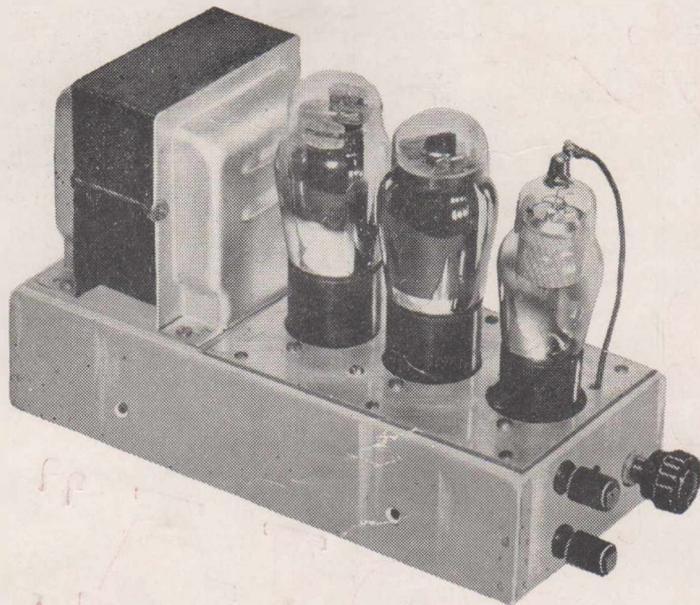

You can build the
**Four-Watt
 Beam
 Amplifier**

FOR ONLY ...

£5-7-6

The Four-Watt Beam Amplifier fully described in the July issue of this magazine is powerful enough for a small hall, and at £5/7/6 for the complete kit represents really wonderful value. The price includes valves and speaker, and—Vealls pay freight to your nearest Railway Station. **ORDER A KIT TO-DAY!**

**Also Available
 VEALLS ELECTRICAL CATALOGUE**

Vealls new 1938 Electrical Catalogue covers all electrical contractors, suppliers' and dealers' requirements, in addition to a complete range of Household Appliances and electrical labour-saving

devices. This catalogue is separate from the Radio Catalogue described elsewhere in this issue. State if you require both. Your name and address on a post card will bring copies to you.

The
VIBRA
DUAL-WAVE FIVE

See the full details elsewhere in this issue . . . a vibrator operated 5-valve dual-wave superhet using the new 6.3 volt .15 amp valves throughout. Ask Vealls to quote you for the supply of the complete kit ready for assembly.

**TEST
 EQUIPMENT**

Vealls can offer a comprehensive range of meters, multimeters and test equipment. Write for full details or see our Big Radio Catalogue, which also fully illustrates and describes Amplifiers, Gramo Motors, Pick-ups, etc.

Remember, Vealls pay freight on all Victorian retail orders excepting radio cabinets and on all Interstate retail orders excepting batteries and cabinets.

VEALLS 6 BIG STORES

All letters to Box 2135T., G.P.O., Melbourne, C1.



490 Elizabeth Street, Melbourne. F 3145.
 168 Swanston Street, Melbourne. C 10524.
 3-5 Riversdale Road, Camberwell. W 1188.

243 Swanston Street, Melbourne. C 3059.
 299-301 Chapel Street, Prahran. Wind. 1605.
 97-99 Puckle Street, Moonee Ponds. FU 7822.

“Speaker

by

ROLA”

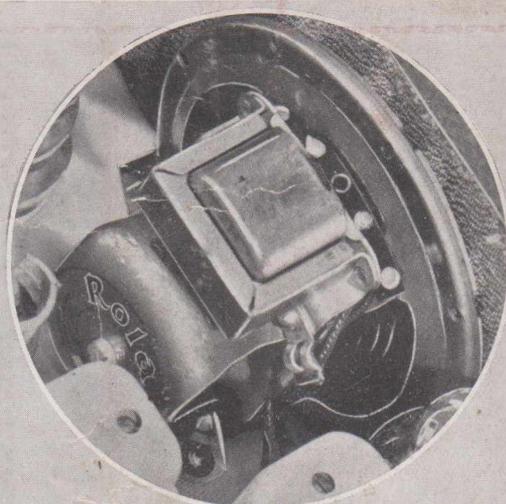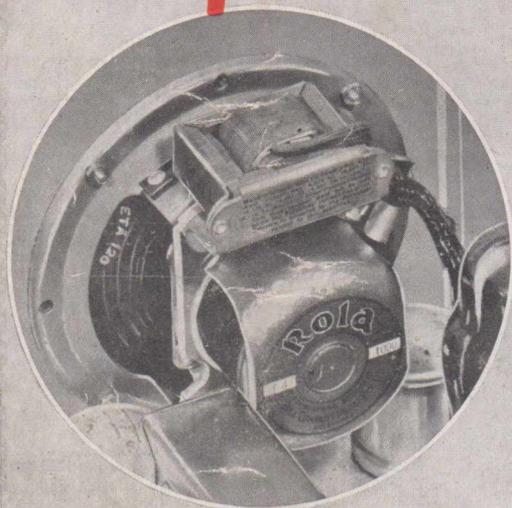

Where unequalled tonal beauty, coupled with highest power-handling ability and finest workmanship are needed, then
“SPEAKER BY ROLA” is the only logical choice.

Vital link between receiver and listener, the speaker used can make or mar the performance of the finest chassis ever designed. That is why leading radio engineers throughout the world insist on Rola. For electro-acoustic efficiency, fidelity of reproduction and sturdy construction, Rola Reproducers give a thrilling realism that is unequalled.

REVOLUTIONARY FEATURES IN LATEST ROLA RANGE: The 1938 range of Rola speakers incorporates the best features of former models and presents new revolutionary improvements, chief of which is the Rola Isocore Transformer, designed to eliminate electrolysis. This new type transformer is fully enclosed and hermetically sealed in a drawn, streamlined case. All vital parts are protected from humidity, ensuring long and trouble-free performance.

Shown above are views of the Rola speakers chosen and specified exclusively by the designer for the “1938 Outdoor Portable Four” and the “1938 Amateur Communications Eight” described this month. To ensure maximum results, follow the designer’s lead and **INSIST ON ROLA.**

Rola Reproducers are standard with the world’s radio and amplifying systems proof positive of Rola Quality !

DISTRIBUTORS AND FACTORY SERVICE FOR N.S.W.

Geo. BROWN AND CO. PTY. LTD.

268 CLARENCE STREET, SYDNEY (Phone M 3437)
 Sole Australian Agents for **ULTIMATE RADIO**



Rola Model 8-20 permanent magnet speaker has remarkable sensitivity; also incorporates Rola dustproof assembly and Isocore Transformer.



Model K-12, a de luxe, full 12-inch unit giving wide-range reproduction. Fitted with Rola Isocore Transformer.