

DYMOCK'S

PRACTICAL WIRELESS CIRCUITS

F. J. CAMM

PRACTICAL WIRELESS CIRCUITS

F. J. CAMM

Registered at the G.P.O., Sydney, for transmission
by post as a Book.

First published (as Twenty-five Tested Wireless Circuits)	December	1931
Revised and expanded (as Fifty Tested Wireless Circuits)	September	1933
Reprinted	May	1935
"	March	1936
"	May	1937
Revised and expanded (as Sixty Tested Wireless Circuits)	May	1938
Reprinted	October	1938
"	December	1939
"	March	1940
"	November	1940
Reprinted (as Practical Wireless Circuits)	February	1941
Reprinted	August	1941
Special Australian Edition	October	1943



Printed and Bound for the Publishers by
New Century Press Pty. Ltd.,
3 North York St.,
Sydney.

PREFACE

In this volume are included typical circuits from crystal sets up to multi-valve sets, superhets, and amplifiers, and which my experience as Editor of *Practical Wireless* indicates are in popular demand. It is not possible within a book of this size to include wiring diagrams of all of the receivers, but full-size blue prints for most of the circuits described in this book are available from the publishers at 1s. each. The circuits which are intended for the beginner are accompanied in most cases by wiring diagrams and pictorial sketches.

The circuits incorporate most of the modern refinements, and they have all been built and tested. As here presented they represent the form in which I found that best results were obtained. None of them presents special difficulty in construction and all can be guaranteed to give excellent results. The Room-to-Room Communicator is an interesting addition to the book.

It is hoped that this general collection of circuits—it is believed to be the only work of its kind—will satisfy most requirements.

F. J. CAMM.

CONTENTS

	PAGE
CRYSTAL CIRCUITS	5
THEORETICAL SYMBOLS	6
ABBREVIATIONS	7
ONE-VALVE SETS	14
TWO-VALVE SETS	24
THREE-VALVE SETS	61
FOUR-VALVE SETS	85
PORTABLE SETS	94
SUPERHET RECEIVERS	106
MAINS SETS	121
UNITS, ADAPTORS, AND AMPLIFIERS	127
ROOM-TO-ROOM COMMUNICATOR	159
CALIBRATING A RECEIVER	164


PRACTICAL WIRELESS CIRCUITS

Abbreviations used in Wireless.—To avoid confusion in subsequent references to components which are usually referred to in an abbreviated form, the contractions applied to wireless parts are given on page 7.

Conventional Signs used in Wireless Circuits.—It will help the reader to be able quickly to follow a wireless diagram if he studies the conventional signs shown in Fig. 2. It will be seen from this that various wireless components have conventional signs, and a wireless circuit is a combination of some of those signs. A circuit, it should be remembered, is a theoretical diagram; a wiring diagram shows the actual components with the wires attached. In some of the sets dealt with in this book wiring diagrams are given; in others the circuits only are included. If any difficulty is experienced in reading the circuits, reference should be made to Fig. 2.

Circuit No. 1.—Fig. 1 shows the very simplest of circuits, employing a crystal detector and an ordinary plug-in coil tuned with a variable condenser. The coil for the normal broadcast band should be a No. 60X, and for the long waves a No. 250X. A short length of flex should be attached to the aerial terminal, and this is connected to the terminal on the X coil which gives the best results. Any

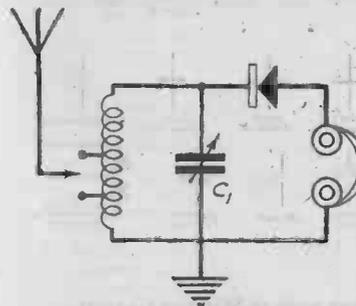type of crystal may be used, but the permanent type is to be preferred as it keeps its contact longer and generally gives better signal strength.



- LIST OF COMPONENTS
FOR CIRCUIT NO. 1**
- .0005 mfd. variable condenser (C1).
 - 1 crystal detector.
 - Plug-in coil-holder.
 - Plug-in coils.
 - Terminals, connecting wire and screws.

FIG. 1.—The very simplest Crystal Circuit.

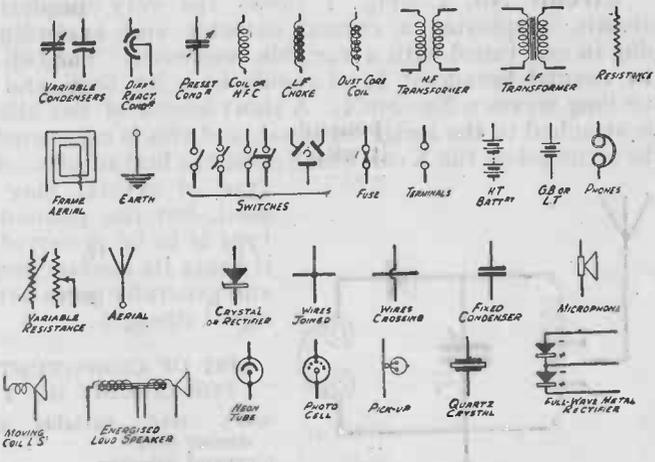
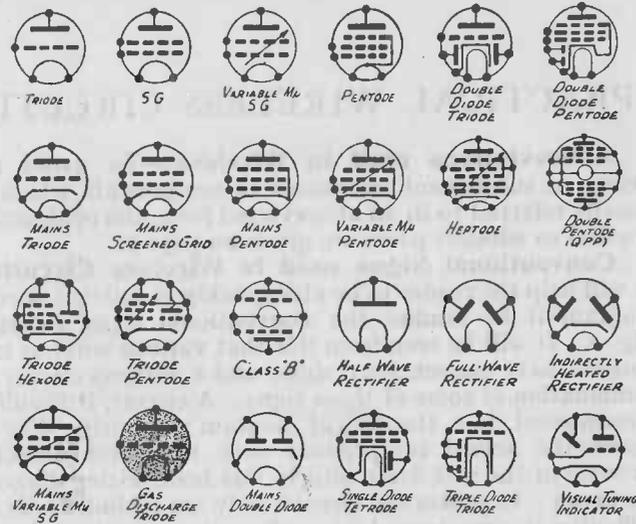


FIG. 2.—Conventional Signs used in Wireless Circuits.

ABBREVIATIONS

- A.—Anode or plate.
- A.A.—Artificial aerial.
- A.C.—Alternating current.
- Æ.—Aerial.
- A.F.—Audio frequency.
- A.F.C.—Automatic frequency control.
- A.G.C.—Automatic gain control.
- A.M.—Amplitude modulation.
- A.T.C.—Aerial tuning condenser.
- A.T.I.—Aerial tuning inductance.
- A.V.C.—Automatic volume control.
- A.V.E.—Automatic volume expansion.
- B.A.—British Association.
- B.C.L.—Broadcast listener.
- B.E.M.F.—Back electromotive force.
- B.F.O.—Beat frequency oscillator.
- B.O.T. Unit—Board of Trade unit = 1000 watt-hours, or 1 kilowatt-hour.
- B.T.U.—British Thermal units.
- B.W.G.—Birmingham wire gauge.
- C.C.C.—Closed circuit or secondary condenser or S.T.C.
- C.C.I.—Closed circuit or secondary tuning inductance or S.T.I.
- C.G.S.—The centimetre gramme-second system of units.
- cm.—centimetre.
- C.P.—Candle power.
- C.W.—Continuous wave.
- D.A.V.C.—Delayed A.V.C.
- db.—decibel.
- D.C.—Direct current.
- D.C.C.—Double cotton covered.
- D.E.—Dull emitter.
- D.F.—Direction finding or finder.
- D.P.—Potential difference.
- D.P.D.T.—Double pole double throw.
- D.P.S.T.—Double pole single throw.
- D.S.C.—Double silk-covered.
- D.X.—Long distance.
- E.—Earth.
- E.M.F.—Electromotive force.
- F.—Filament.
- F.M.—Frequency modulation.
- F.P.S.—Foot-pound second.
- G.—Grid.
- G.B.—Grid battery or grid bias.
- G.C.—Grid condenser.
- G.L.—Grid leak.
- H.F.—High frequency (same as radio frequency).
- H.F.C.—High frequency choke, high frequency coupling, or high frequency current.
- H.P.—Horse-power.
- H.R.—High resistance.
- H.T.—High tension.
- I.C.—Intermittent current.
- I.C.W.—Interrupted continuous waves.
- I.F.—Intermediate frequency.
- I.P.—In primary (of transformer); start of primary.
- I.S.—In secondary (of transformer); start of secondary.
- kw.—Kilowatt.
- L.F.—Low frequency.
- L.F.C.—Low frequency choke, low frequency coupling, or low frequency current.
- L.R.—Low resistance.
- L.S.—Loudspeaker.
- L.T.—Low tension.
- mA.—Milliampere.
- M.C.—Moving coil.
- mfd.—Microfarad.
- mhy.—Microhenry.
- mm.—Millimetre.
- mmfd.—Micro-microfarad.
- O.F.—Outside foil.
- O.L.—Output load.
- O.P.—Out primary (of transformer); end of primary.
- O.S.—Out secondary (of transformer); end of secondary.
- P.—Plate or anode.
- P.A.—Public address.
- P.D.—Potential difference, same as D.P.
- P.M.—Permanent magnet.
- Pot.—Potentiometer.
- P.V.—Power valve.
- Q.A.V.C.—Quiet automatic volume control.
- Q.M.B.—Quick make and break.
- Q.P.P.—Quiescent push-pull.
- R.F.—Radiofrequency (same as high frequency).
- R.M.S. Value.—Root-mean-square value.
- Rx.—Receiver.
- S.C.C.—Single cotton covered.
- S.G.—Screen grid.
- S.H.M.—Single harmonic motion.
- S.I.C.—Specific inductive capacity.
- S.P.—Series parallel.
- S.P.D.T.—Single pole double throw.
- S.P.S.T.—Single pole single throw.
- S.R.—Specific resistance.
- S.S.C.—Single silk covered.
- S.T.C.—Secondary tuning condenser.
- S.T.I.—Secondary tuning inductance.
- S.W.G.—Standard wire gauge.
- S.W.L.—Short-wave listener.
- T.R.F.—Tuned radio frequency.
- T.S.F.—French abbreviation for wireless "Telegraphie sans Fils."
- T.T.—Tonic train.
- Tx.—Transmitter.

Circuit No. 2.—A similar arrangement to Circuit No. 1 is shown in Fig. 3, except that a home-made coil is used. A cardboard tube 3 inches in diameter is required, and round this is wound 60 turns of No. 24 D.C.C. wire. At one end a further length of the same wire is passed through the anchoring hole, and joined to the first winding. This junction is joined to earth. The short length of wire is then wound over six or seven matchsticks which are stuck across the first winding, and tapping loops are made at the 5th, 10th, 15th, and 20th turns. The aerial is then taken to the tapping which gives best results.

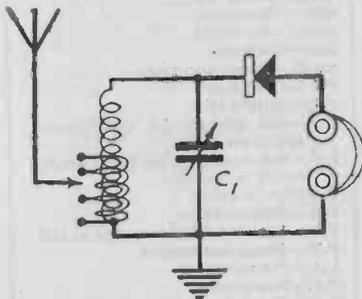


FIG. 3.—Crystal Circuit using a home-made tapped coil.

LIST OF COMPONENTS

.0005 mfd. variable condenser (C1).
 1 crystal detector.
 Coil, as mentioned in above notes.
 Terminals, connecting wire, and screws.

Circuit No. 3.—This receiver has been specially designed so that it can be adapted to suit local conditions. It must be remembered that with a crystal set we cannot use

reaction to compensate for losses or to sharpen up the tuning. It will be noticed in the Circuit Fig. 4 that two of the components are shown in dotted line. The reason for this will be explained later. The set employs a home-made coil, made up of three separate windings. The set is shown in Figs. 5 and 6. The crystal is tapped to a point a short distance from the high-potential end of the coil, and this has the effect of removing the damping exerted in the circuit and gives a slight increase in the sharpness of tuning. The wave-change switch is of the double-pole double-throw type

In the simplest form all that is necessary to change from medium to long waves is to short-circuit part of the tuning coil, but the same degree of selectivity is not required on the long waves as is needed on the medium waves, and thus it is an advantage to be able to modify the aerial connection when changing wavelengths. It will be seen in this circuit that when in the medium-wave position the

aerial is joined direct to the top or high-potential end of the coil (ignoring the dotted condenser), whereas when switched over to long waves, the aerial is transferred to a point much lower down on the coil. It will be noted that a coil is shown in dotted lines joined between the aerial contact for the long-wave position and the tapping on the coil, and this is a

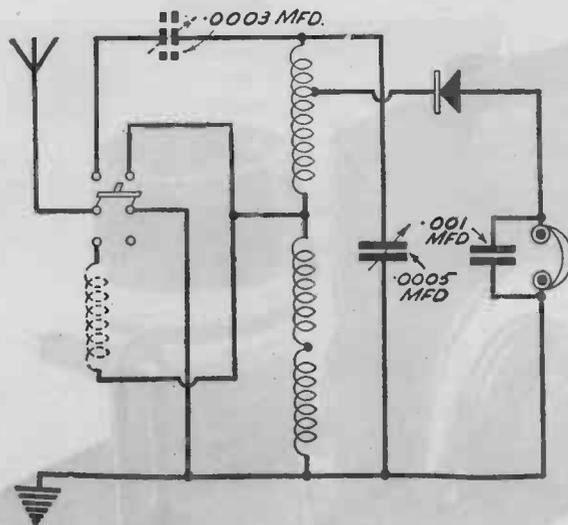


FIG. 4.—Circuit No. 3 for a Modern Crystal Set.

special anti-break-through choke which will be found invaluable to those listeners who are situated close to a medium-wave broadcast station.

The condenser shown in dotted lines is also of value to listeners in a similar position as it may be adjusted to separate the two local stations when a large aerial is employed. Therefore, the receiver should be first made up, ignoring these two components, and if it is found in a particular case that the two locals are heard together, the pre-set condenser should be included between the switch and the top of the coil. Similarly, if when switched over to long waves the medium-wave station can be heard in the background, the special choke should be placed in circuit as shown in the Wiring Diagram.

The panel and baseboard both measure 6 inches by

6 inches, and the former is of paxolin. Ordinary $\frac{1}{8}$ -inch three-ply is used for the baseboard. The panel may be drilled by following the measurements and details given in Fig. 7, and the switch and terminal sockets should be attached. The variable condenser is screwed to the baseboard.

The coil (Fig. 8) is wound on a length of paxolin tubing

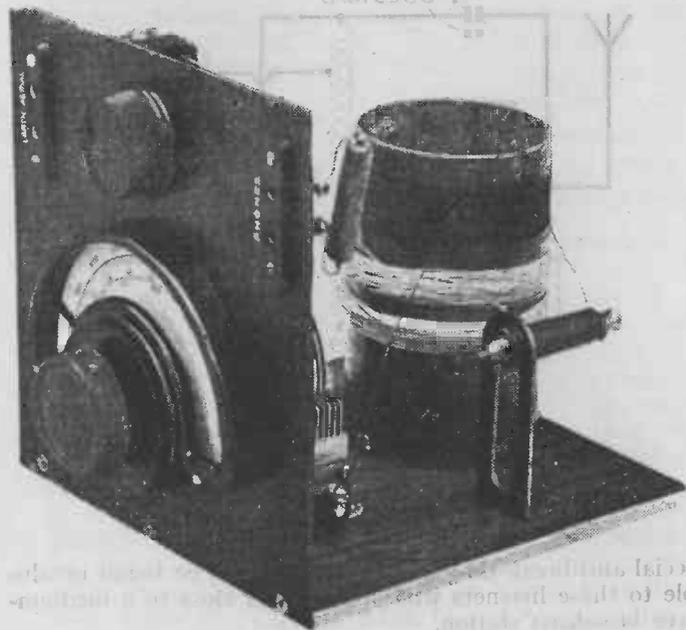


FIG. 5.—Crystal Circuit No. 3 should be built as shown here.

measuring $2\frac{1}{2}$ inches in diameter and 4 inches in length. Two small holes should be pierced at the upper edge and the end of the wire passed through, leaving a length of 5 inches projecting for connection to the variable condenser. Wind on 8 turns and then make a large loop about 2 inches in length, and in the position shown in the diagram of the coil. Continue the winding for another 32 turns and cut the wire so that when passed through a further pair of holes, there will be approximately 5 inches left. About $\frac{1}{4}$ inch from this end of the coil make another pair of holes and pass the

end of the wire through again, leaving a further 5 inches for connection, and then wind on the wire hank fashion for 80 turns, after which let the wire pass across the former for a $\frac{1}{4}$ of an inch or so and wind a similar hank winding of the same number of turns. This will give you a total of 200 turns

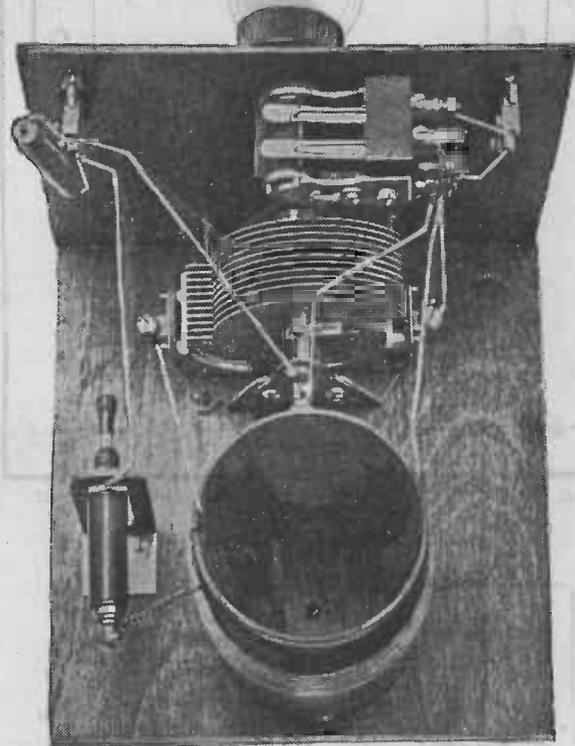


FIG. 6.—A plan view of the Crystal Circuit No. 3.

of wire, the lower two piles forming the long-wave loading coil. The coil is mounted by screwing a strip of wood inside the lower end. Alternatively a disc may be cut from plywood for the purpose.

When the ends of the coils are connected to the respective points (Fig. 9), and if the condenser and choke are to be left out, the end of the first coil and the commencement of

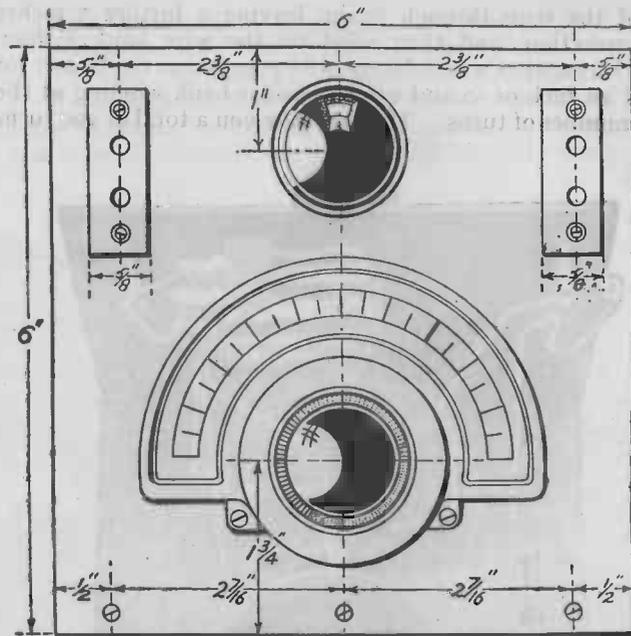


FIG. 7.—Drilling Diagram for the Panel of the Receiver.

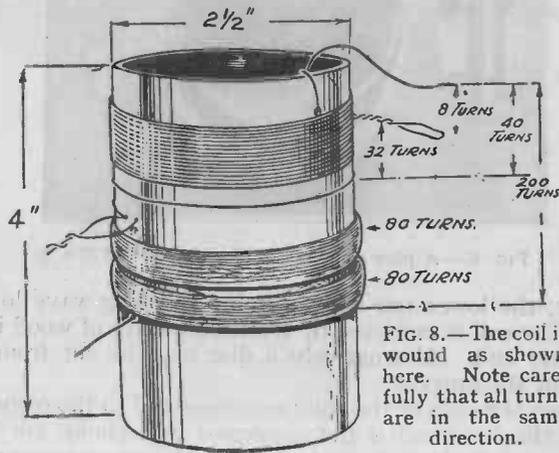


FIG. 8.—The coil is wound as shown here. Note carefully that all turns are in the same direction.

the first of the two-pile windings should be twisted together and taken to the switch. If the choke is to be included it should be joined between the two-switch contacts as shown. Note that the end of the complete coil is joined both to the variable condenser and to the switch and the one length of wire may be used, scraping away the cotton covering for the purpose. The small fixed condenser is joined across the 'phone terminals, and the crystal detector mounted on the component-mounting bracket. The loop of wire in the first part of the coil should be scraped and passed over the end of the detector and locked beneath the terminal nut, whilst the lead from the detector to the 'phone terminals is anchored between the component-mounting bracket and the locking nut on the detector.

The detector should be pulled out, turned and gently released when adjusting the detector. On no account turn this without pulling it out, as by so doing you will spoil the surface of the detector and it will soon need replacing.

If the anti-break-through choke is found necessary it may easily be constructed from the same wire as is used for winding the coil. Cut a disc of plywood about 1/4 inch

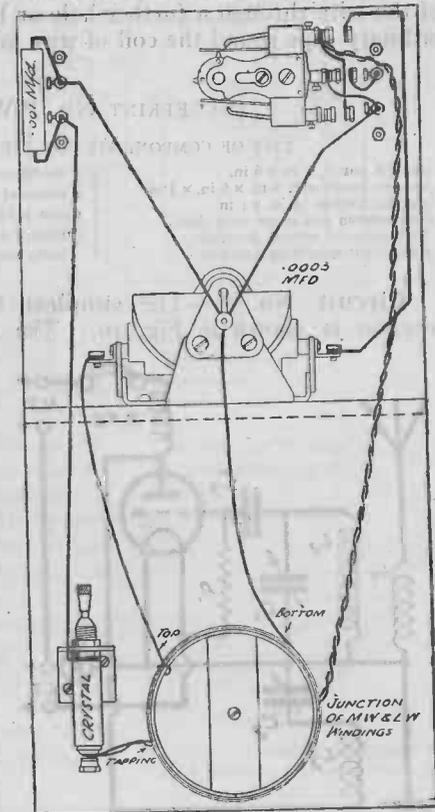


FIG. 9.—Wiring Diagram for Crystal Circuit No. 3.

thick and about 1 inch in diameter, and two discs of similar wood 1½ inches in diameter. Screw these together to form a spool and drill a hole through one disc near the edge of the centre piece. Anchor the wire in this hole and wind 150 turns of wire in the spool, afterwards anchoring the end of the wire through a further hole or by wrapping a piece of ordinary tape round the coil of wire and tying a knot.

(BLUEPRINT NO. P.W.71)

LIST OF COMPONENTS FOR CIRCUIT NO. 3

- 1 paxolin panel, 6 in. x 6 in.
- 1 wooden baseboard, 6 in. x 6 in. x ½ in.
- 1 paxolin former 2½ in. x 4 in.
- 1 slow-motion condenser with dial.
- 1 Red-diamond crystal detector.
- 1 component mounting bracket.
- 1 double-pole change-over switch.
- 2 terminal socket strips.
- 1 .001 mfd. tubular condenser.
- Quantity 22 D.C.C. wire, screws, four 4 B.A. bolts and nuts.

Circuit No. 4.—The simplest form of single-valve receiver is shown in Fig. 10. The tuning arrangements consist of three baseboard mounting coil-holders screwed on to a baseboard side by side, with just sufficient space between them to allow the largest size of coil to be comfortably inserted.

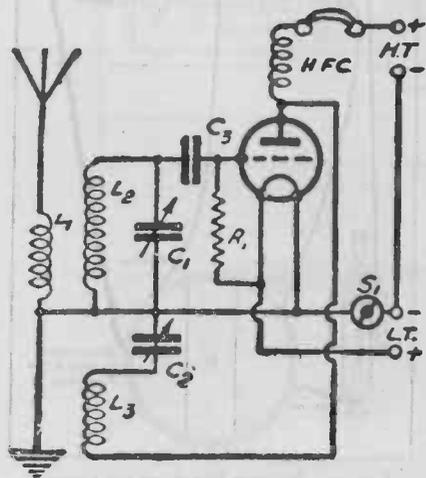


FIG. 10.—A simple One-valve Circuit.

plug-in coils will enable you to listen on any wavelength. For the normal broadcast band the coils should be as follows: L1 a No. 35 coil, L2 a No. 60, and L3 a No. 50 coil. The H.T. should have a value of 60 volts, and the valve should be of the general purpose type.

LIST OF COMPONENTS FOR CIRCUIT NO. 4

- 1 .0005 mfd. variable condenser (C1).
- 1 .0003 mfd. variable condenser (C2).
- 1 .0002 mfd. fixed condenser (C3).
- 1 2-megohm grid leak and holder (R1).
- 1 valve-holder.
- 3 baseboard mounting coil-holders.
- 1 on-and-off switch (S1).
- Set of plug-in coils.
- 1 H.F. choke.
- Terminals, connecting wire, and screws.

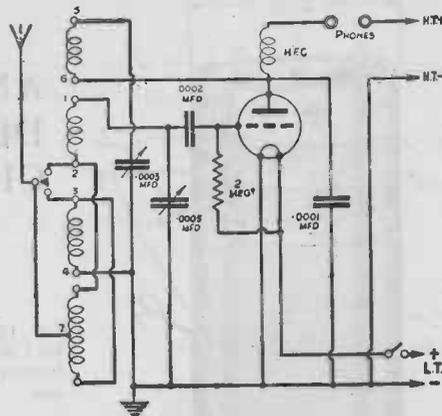


FIG. 11.—Circuit of the single-valve set, Circuit No. 5.

Circuit No. 5.—Circuit No. 5 (Fig. 11), employs a home-made coil the dimensions for which are given in Figs. 13 and 14, and method of mounting the coil in Fig. 12. As the panel is screwed direct to the baseboard the latter should be fairly thick, and measure 10 inches by 6 inches, whilst the panel of 3/8 inch plywood measures 10 inches by 7 inches. For the latter it is better to use a piece of mahogany-faced ply, so that it can be polished when finished.

The sketch (Fig. 15) makes the construction clear.

WOOD OVER WHICH COIL FORMER FITS TIGHTLY.


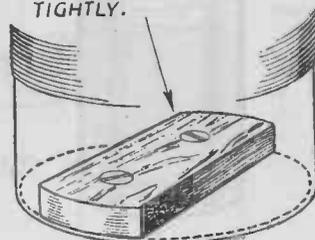


FIG. 12.—A simple and convenient method of mounting the coil for Circuit No. 5 over a piece of wood screwed to the baseboard.

LIST OF COMPONENTS FOR CIRCUIT NO. 5

- 1 tuning coil made as shown in Fig. 11.
- 1 .0005 mfd. panel mounting variable condenser with plain knob and dial.
- 1 .0003 mfd. bakelite dielectric condenser with knob.
- 1 Q.M.B. 2-point on-off switch.
- 1 3-point Q.M.B. on-off switch for wave-changing.
- 1 baseboard mounting 4-pin valveholder.
- 1 .0002 mfd. fixed condenser.
- 1 .0001 mfd. fixed condenser.

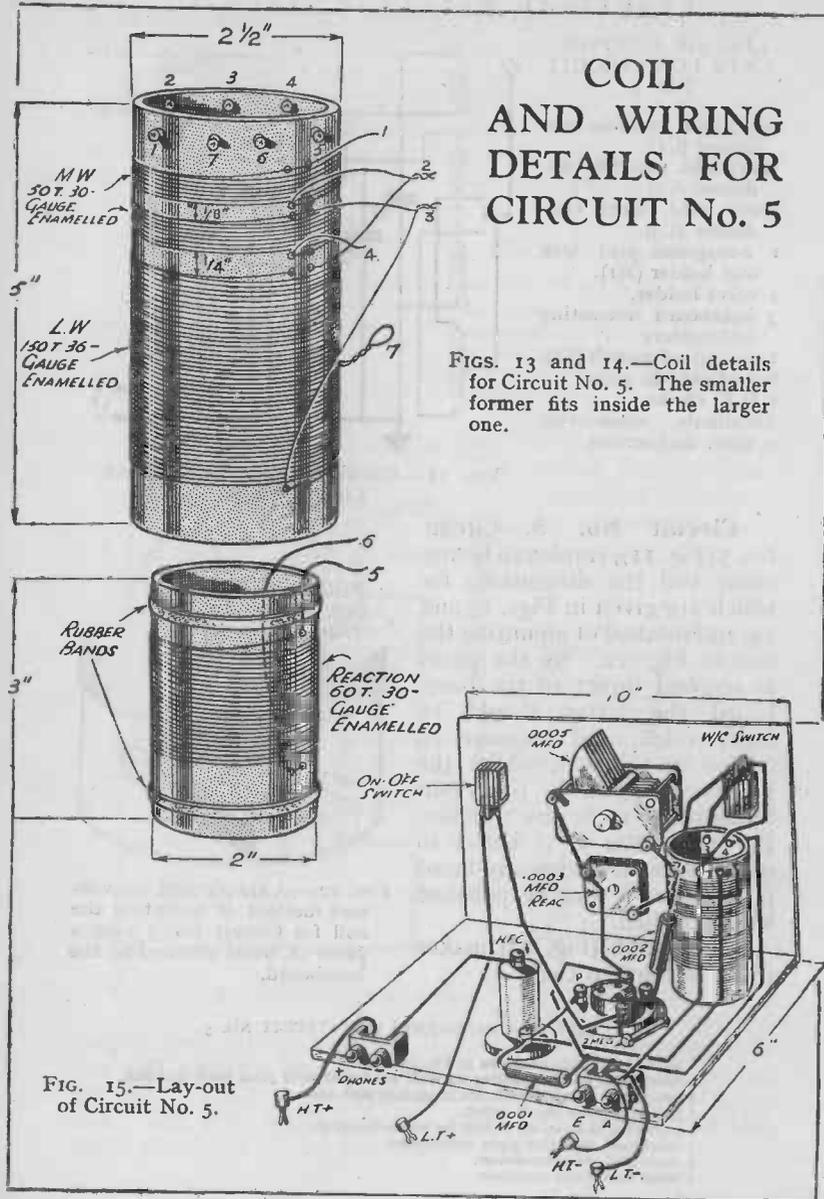COIL AND WIRING DETAILS FOR CIRCUIT No. 5



FIGS. 13 and 14.—Coil details for Circuit No. 5. The smaller former fits inside the larger one.

- 1 2-megohm grid leak.
- 1 high-frequency choke.
- 2 terminal mounts marked A and E and 'phones or L.S.
- 2 spade terminals marked L.T. positive and L.T. negative.
- 2 wander plugs marked H.T. positive and H.T. negative.
- Flex, wood screws, and wire.
- 1 pair of high resistance telephones (2000 or 4000 ohms).
- 1 valve of the detector type.
- 1 2-volt accumulator.
- 1 H.T. battery (100 volt).

Circuit No. 6.—Fig. 16 shows a simple one-valver employing a home-made tuner. The construction of the tuner

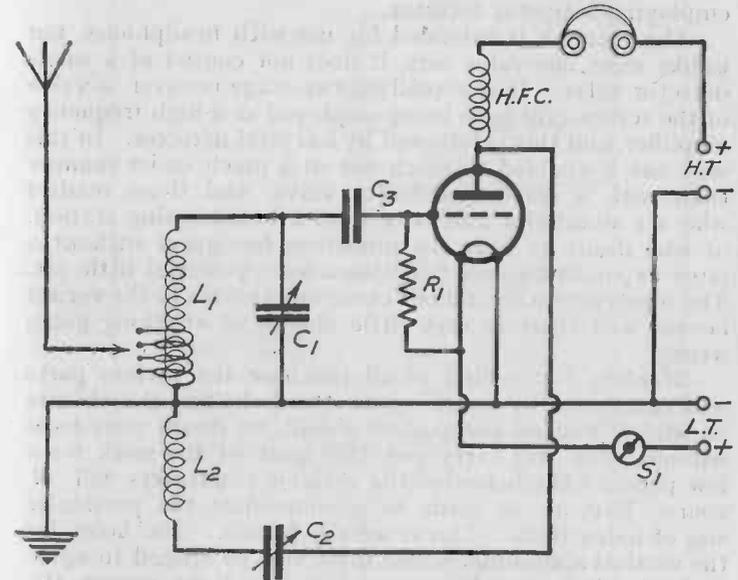


FIG. 16.—Another simple One-Valve Set.

is similar to that of the crystal set, Circuit No. 2, with an additional winding of No. 30 D.C.C. wire wound on about a quarter of an inch below the earthed end of the primary and secondary coils. The end nearest this junction is also earthed. In other respects the arrangement is similar to Circuit No. 4.

LIST OF COMPONENTS FOR CIRCUIT NO. 6

·0005 mfd. variable condenser (C ₁).	Valve-holder.
·0003 mfd. variable condenser (C ₂).	On-and-off switch (S ₁).
·0002 mfd. fixed condenser (C ₃).	Coil, as mentioned in above notes.
1 H.F. choke.	Terminals, connecting wire, and screws.
1 2-megohm grid leak and holder (R ₁).	

Circuit No. 7.—Although included amongst the one-valvers, the set shown by Fig. 17 consists of two stages, but only employs one valve. It is an H.F. and detector set, employing a crystal detector.

The receiver is intended for use with headphones, but unlike most one-valve sets, it does not consist of a single detector valve. It is actually a two-stage receiver, a valve of the screen-grid type being employed as a high-frequency amplifier, and this is followed by a crystal detector. In this way one is enabled to reach out in a much easier manner than with a reacting detector valve, and those readers who are situated a long way from a broadcasting station, or who desire to hear the numerous foreigners without a large expenditure, will find this a very powerful little set. The construction should not cause any trouble to the veriest novice, and there is very little chance of anything going wrong.

Marking Out.—First of all purchase the various parts and commence by marking out and drilling the ebonite panel. If you do not possess a drill, no doubt your local wireless shop will carry out this part of the work for a few pence. The holes for the variable condensers will, of course, have to be made to accommodate the particular size of fixing bush. This is usually $\frac{3}{8}$ inch. The holes for the vertical aluminium screen must also be spaced to agree with the holes in the screen itself. Next mount the condensers and crystal detector, the four terminals and the screen. This part of the work may now be placed on one side.

Arranging the Parts.—Arrange the remainder of the parts on the wooden baseboard, but before screwing them in place arrange the panel in its position and make sure that there is ample clearance for all parts. When you are quite satisfied with the arrangement, drive in the screws, and fix the ebonite strip containing the battery terminals in its place at the rear of the baseboard. The ebonite panel may

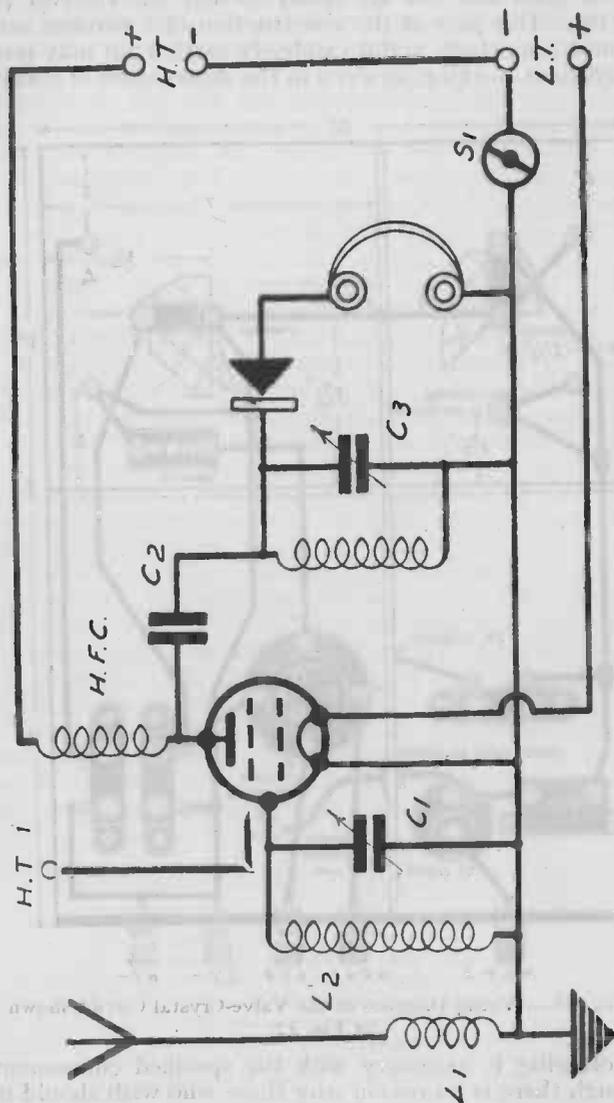


FIG. 17.—A Valve-Crystal Circuit.

now be fixed and you are ready to wire the receiver (see Fig. 18). This part of the construction of a wireless set is the most important, and if carelessly carried out may result in inefficient working, or even in the destruction of a valve.

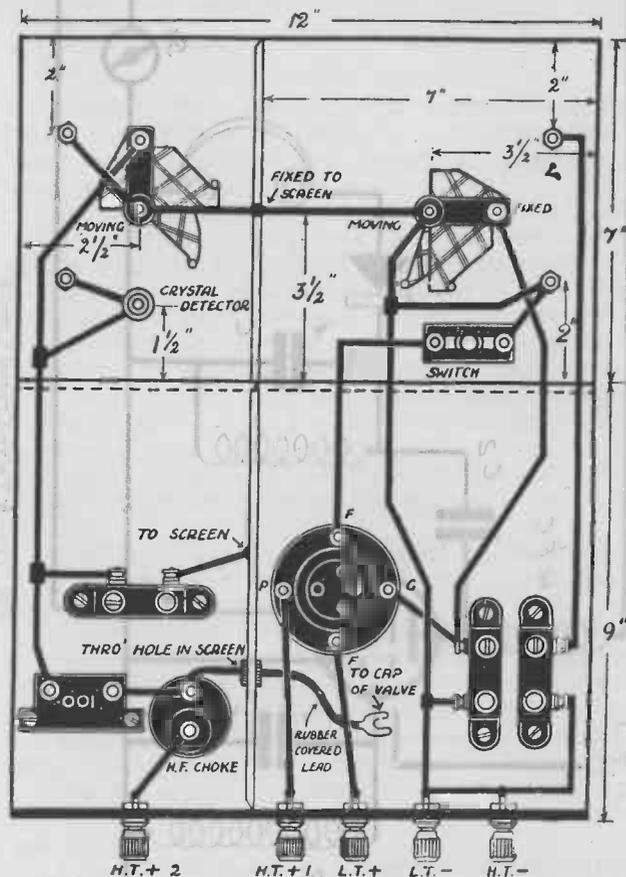


FIG. 18.—Wiring Diagram of the Valve-Crystal Circuit shown by Fig. 17.

No soldering is necessary with the specified components, although there is no reason why those who wish should not use the soldering tags. Keep all wires well spaced, the

closest permissible crossing being $\frac{1}{2}$ inch. As each wire is fixed, cross through the corresponding wire in the wiring diagram to ensure that all wires are put in, and as a check that the correct terminals are connected.

Testing the Set.—In the valve-holder plug a screen-grid valve of the modern 2-volt type, and attach the flexible lead to the terminal on the top of the valve. For the normal broadcast band a No. 25 or 30 coil should be plugged into the left-hand socket and a No. 60 into the socket next to it. In the socket on the right of the vertical screen another No. 60 coil is required. Connect a two-volt accumulator (a 40 ampere-hour type is best) to the L.T. terminals, and the H.T. + 1 terminal should be plugged into a 120-volt battery at the nearest socket to 80 volts. H.T. + 2 goes into the 120-volt socket, and H.T. — into the negative terminal of the battery. Connect the aerial to the upper terminal on the left-hand side of the panel, and the earth to the lower terminal on the same side, whilst a pair of headphones must be connected to the right-hand pair of terminals. Note carefully that the 'phones are connected to the terminals on the right of the panel when viewing from the front.

Tuning In.—Pull out the switch and carefully rotate both dials together. These should tune at roughly the same dial readings, but, especially with weak stations, they must both be in tune, irrespective of the dial numbers, to get maximum signal strength. No difficulty should be experienced in receiving quite a number of stations at good strength, and for those readers who wish to operate a loud-speaker, an ordinary type of amplifier may be connected to the 'phone terminals. Reception on other wave-bands may be carried out by plugging-in the appropriate coils.

LIST OF COMPONENTS FOR CIRCUIT NO. 7

- 1 ebonite panel, 12 in. x 7 in.
- 1 baseboard, 12 in. x 9 in.
- 2 variable condensers, .0005 mfd.
- 1 permanent crystal detector.
- 3 baseboard mounting coil-holders.
- 1 fixed condenser, .001.
- 1 H.F. choke—screened-grid type,
- 1 aluminium screen.
- 1 valve-holder.
- 9 terminals.
- Quantity of Glazite connecting wire.

Circuit No. 8.—Those readers operating crystal sets in districts remote from a broadcasting station and in consequence receiving very weak signals, can add the amplifier shown in Fig. 20 which will increase the strength of the signals considerably. It should be remembered that a crystal set is intended only for local station reception, although instances are on record of the reception of American

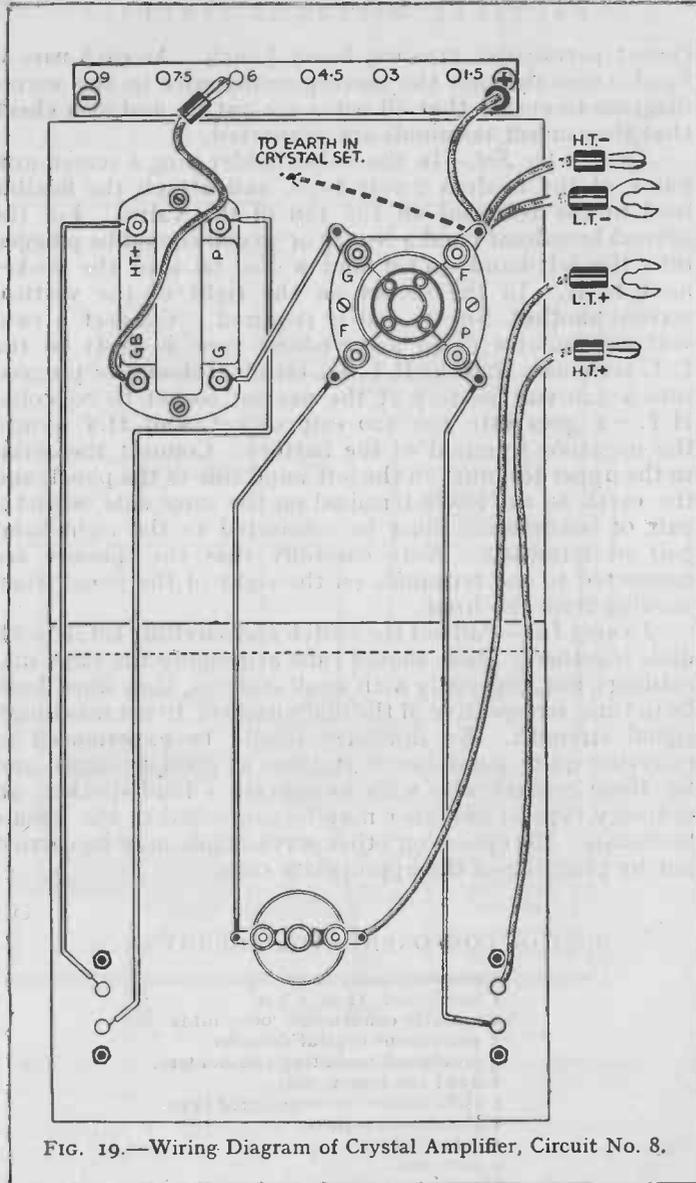


FIG. 19.—Wiring Diagram of Crystal Amplifier, Circuit No. 8.

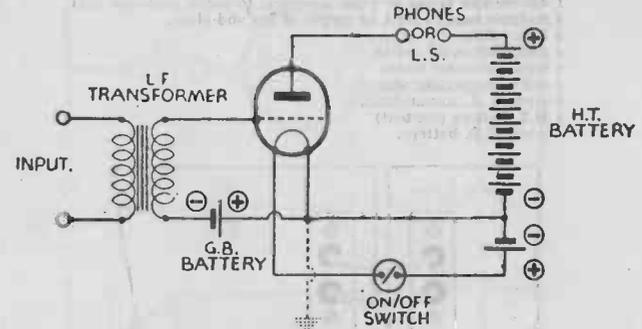


FIG. 20.—Circuit No. 8 for Crystal Amplifier, with the various components clearly identified.

and continental programmes on it when conditions are suitable. It will be seen that a low-frequency transformer is used to feed the signals to a valve, instead of taking them direct to the headphones. The transformer should have a ratio of about 5 to 1. The wiring diagram Fig. 19 is self explanatory. When the wiring is completed the unit should be placed alongside the crystal set, and the two phone sockets on this should be connected across to the two input sockets on the amplifier, Fig. 21, whilst the phones should be plugged into the other socket strip on to the amplifier panel.

In some cases even greater amplification may be desirable, and in that case you can use a pentode valve instead of the L.F. type just mentioned. In this case, you will use a 5-pin valveholder instead of a 4-pin one, and the extra point will be fitted with another battery lead. To the end of this a red plug marked H.T.1 should preferably be fitted, or alternatively a lead of a totally different colour may be used (this will be the case if a 5-way battery cord is purchased). This lead should be inserted into a socket just below the maximum used for the other positive lead, but

later it may be joined direct to the maximum lead with a decoupling scheme. However, this will be dealt with in its place. Again, the G.B. will have to be adjusted according to the makers' instructions for the particular value in use.

LIST OF COMPONENTS FOR CIRCUIT NO. 8

- 1 wooden baseboard 6 in. x 6 in.
- 1 paxolin panel 6 in. x 6 in.
- 1 L.F. transformer (ratio 5 to 1).
- 1 valveholder (4-pin or 5-pin according to valve used—see text).
- 1 multiple battery cord, or supply of flex and plugs.
- 1 L.F. valve.
- 1 push-pull on-off switch.
- 2 terminal socket strips.
- 1 coil of connecting wire.
- 1 2-volt L.T. accumulator.
- 1 H.T. battery (see text)
- 1 9-volt G.B. battery.

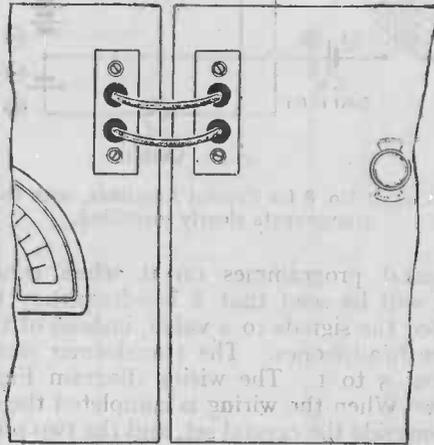


FIG. 21.—How the Crystal Set and the Amplifier (Circuit No. 8) are connected together.

Circuit No. 9.—This is a two-valve set (Fig. 22), designed for purity of reproduction. Plug-in coils are used, and the remarks on Circuit No. 4 relative to this part of the circuit will also apply. The resistance R_2 , the condenser C_4 , and the resistance R_3 are all incorporated in the commercial type of resistance coupling unit, and this may be used instead of the separate components if desired. The second valve should be of the L.F. type, and the H.T. should have a value of 120 volts, with the grid bias adjusted according to the particular instructions of the valve maker.

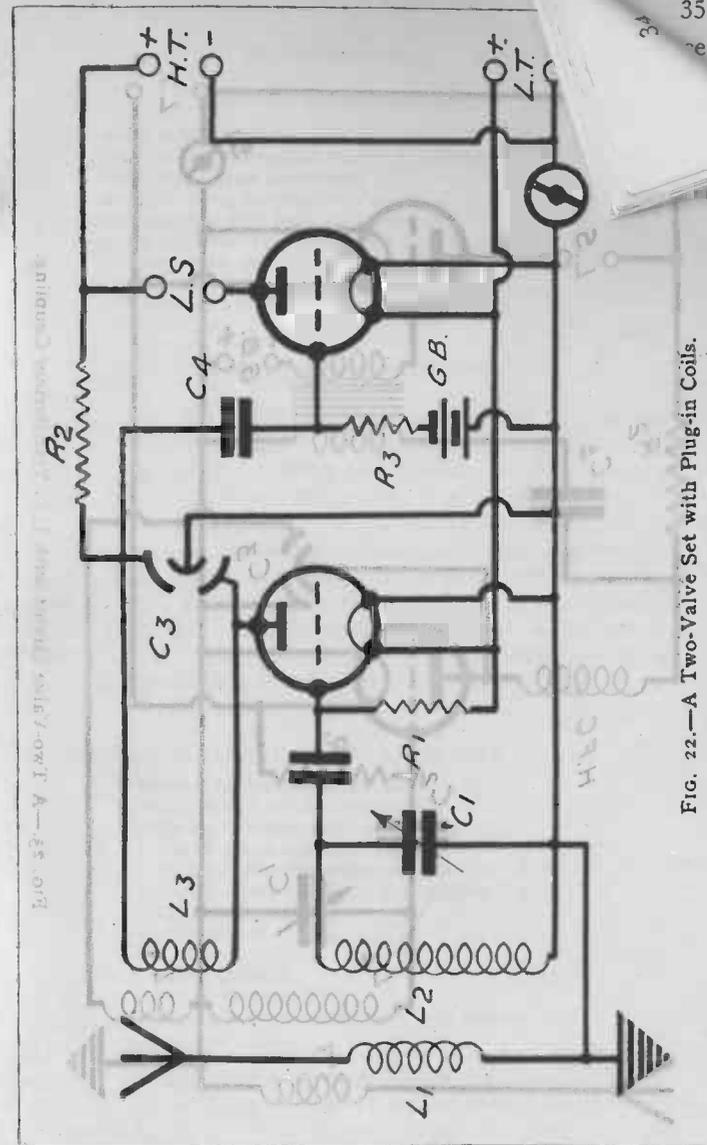


FIG. 22.—A Two-Valve Set with Plug-in Coils.

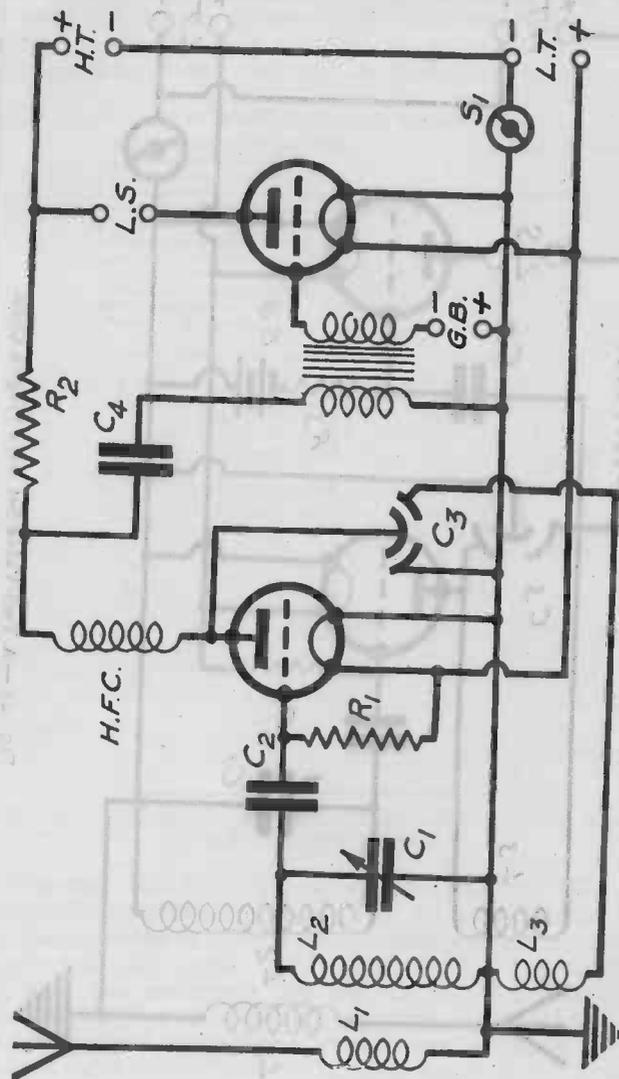


Fig. 23.—A Two-Valve Circuit with L.F. Transformer Coupling.

(BLUEPRINT H9)

LIST OF COMPONENTS

- 0005 mfd. variable condenser (C1).
- 0002 mfd. differential reaction condenser (C3).
- 0002 mfd. fixed condenser (C2).
- 01 mfd. fixed condenser (C4).
- 1 2-megohm grid leak and clips (R1).
- 1 100,000-ohm resistance and holder (R2).
- 1 25,000-ohm resistance and holder (R3).
- 2 valve-holders.
- 1 on-and-off switch (S1).
- 3 coil-holders.
- Set of coils.
- Terminals, connecting wire, and screws.

Circuit No. 10.—Fig. 23 is a similar set to the preceding one, but this time an ordinary L.F. transformer is employed. In order to keep the quality of reproduction on a high standard, this transformer is parallel fed, that is, the primary is not placed direct in the anode circuit of the detector valve, and therefore no current passes through its primary. This keeps its inductance high and preserves the bass notes. Further, the values of the grid condenser and leak have been modified to give what is known as power grid detection. Consequently, provided plenty of H.T. is employed, this receiver will give absolutely tiptop quality.

LIST OF COMPONENTS FOR CIRCUIT NO. 10

- 0005 mfd. variable condenser (C1).
- 0001 mfd. fixed condenser (C2).
- 0002 mfd. differential condenser (C3).
- 1 1-mfd. fixed condenser (C4).
- 1 250,000-ohm resistance and holder (R1).
- 1 30,000-ohm resistance and holder (R2).
- 1 L.F. transformer.
- 3 coil-holders.
- Set of coils.
- 2 valve-holders.
- On-and-off switch (S1).
- Terminals, connecting wire, and screws.

Circuit No. 11.—The two-valver shown by Fig. 24 is designed primarily for long-distance headphone work, and consists of a screen-grid H.F. stage followed by a simple detector valve. The aerial circuit consists of a No. 60X coil, and the coils L2, L3, and L4 are included in a

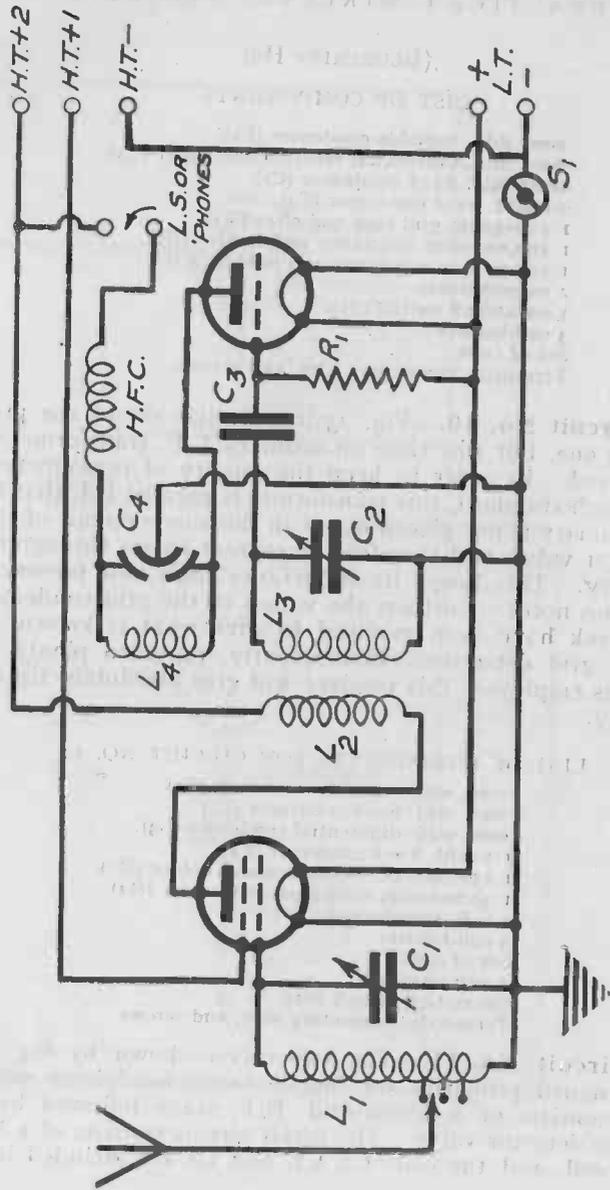


FIG. 24.—Two-Valve Set for Long-Distance Headphone Reception.

commercial six-pin coil unit. Several firms make this H.F. transformer as it is called, and therefore any particular make may be chosen by the constructor. Care should be taken that a transformer for use with S.G. valves is obtained as there is a different type of transformer for the triodes, or ordinary three-electrode valve. Differential reaction control is employed for stability, and the detector valve may be of the H.F. or general purpose type. As there are two tuned circuits in this receiver, care will have to be exercised in tuning in, as, unless both circuits are tuned to the wavelength of the desired station, nothing will be heard, unless, of course, the station is very close to you.

LIST OF COMPONENTS FOR CIRCUIT NO. 11

- 2 ·0005 variable condensers (C1 and C2).
- 1 ·0002 fixed condensers (C3).
- 1 2-megohm grid leak and holder (R1).
- 1 differential reaction condenser (C4).
- 1 H.F. choke.
- 1 6-pin H.F. transformer and base.
- 1 Plug-in 2-pin coil-holder.
- 1 tapped 60 turn coil.
- 2 valve-holders.
- 1 on-and-off switch (S1).
- Terminals, connecting wire, and screws.

Circuit No. 12.—This short-wave adaptor unit (Figs. 25-26) has been designed for attachment to existing sets. Those possessing ordinary receivers, which have been built for the broadcast band, often wish they were able to tune down to the short waves and pick up stations situated as far away as America or on the other side of the globe, Kenya, etc. These short waves seem to come in remarkably well, and the short-wave unit here described may be connected to any ordinary receiver (provided it is not a Mains driven set), and which will enable reception to be carried out on most of the short wavelengths at present in use. The unit is quite cheap and the total expenditure need not exceed £1. No extra valve is needed, as will be explained later.

The list of components should be studied, and practically any make of standard design may be used. The only point which requires careful attention is the method of connection used in the variable condensers. These must be fitted with "pigtail" connections if rustling noises are to be avoided when tuning in on the short waves. Most of the better


makes of variable condenser now employ this method of connection.

The Panel Lay-out.—Having obtained the various parts, proceed to mark out the panel, using as your guide the measurements given on the wiring diagram. The exact size of the holes will depend, of course, on the particular make of component chosen. Mount up the condensers and then proceed to fix the remaining components to the base-board. Pay particular attention to the coil-holders, allowing sufficient space between them to permit the largest of the coils to be safely inserted without touching its neighbour. The only two terminals required in this unit may be mounted on a spare piece of ebonite, or one of the Belling-Lee special terminal blocks may be purchased; they are cheap.

When everything is in its place you may proceed to wire up. This should be carried out with heavy gauge wire, say 16 or 18 bare copper, well spaced, and by the most direct method. Do not try to make this part of the work look neat by taking the leads a long way round with nice right-angle bends. Where short waves are concerned the leads must be as short and direct as possible. Do not let any wire run within $\frac{1}{2}$ inch of another unless it crosses at a dead right angle. Attention to this part of the work will be well repaid in efficient working. Note also that the moving vanes of both condensers are connected together and to earth.

The Connecting Link.—When the unit is wired you will have to make the actual connecting link with your present receiver, and this will have to be made of such a length that it will comfortably reach your present detector socket. Three single lengths of flex are required, and to avoid mistakes these should preferably be of different colours. Alternatively, you may cut three lengths of ordinary flex and bind the ends of each separate strand with a different coloured thread. These three strands are connected up in the following way. One strand to each of the filament terminals of the valve-holder in the unit, and to each filament pin of the valve adapter. The remaining strand from the plate terminal of the valve-holder to the plate pin of the adapter. No connection whatever is made to the grid pin of this adapter.

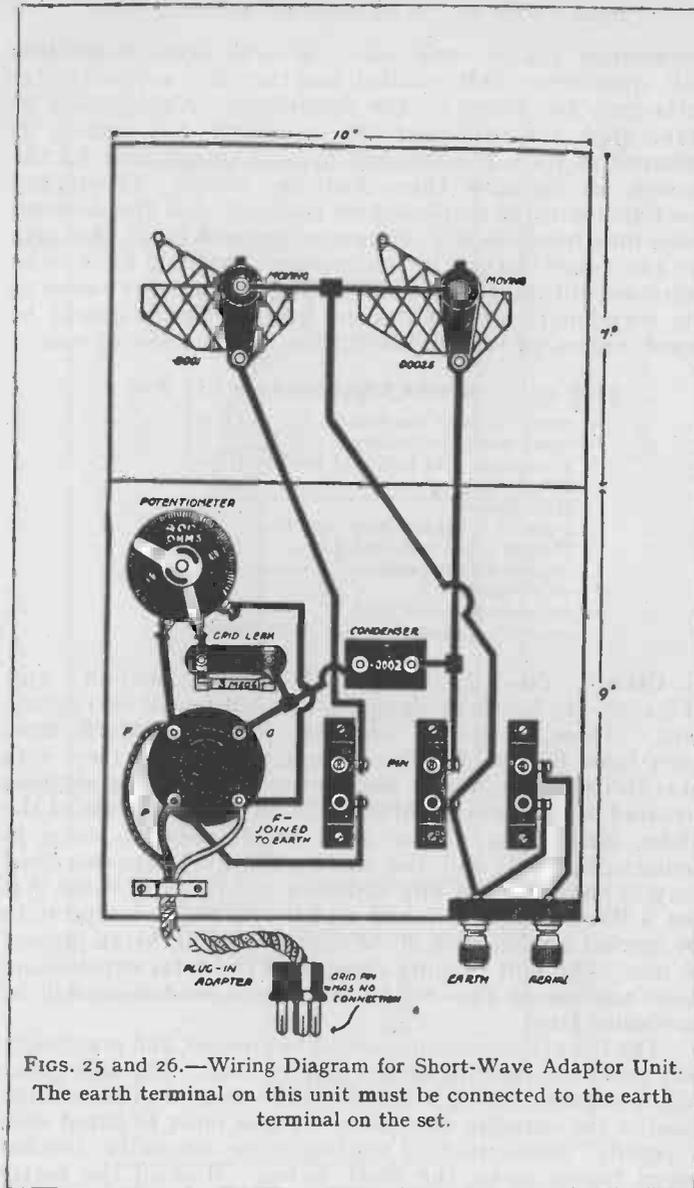Having finished this part of the work, carefully check over all connections, and when you are quite sure no mistakes have



FIGS. 25 and 26.—Wiring Diagram for Short-Wave Adaptor Unit. The earth terminal on this unit must be connected to the earth terminal on the set.

condenser of about .0002 mfd. between the aerial lead and the aerial socket of the set. Fig. 28 shows the cabinet drilling dimensions, Fig. 29 the completed chassis, and Fig. 30 the wiring diagram.

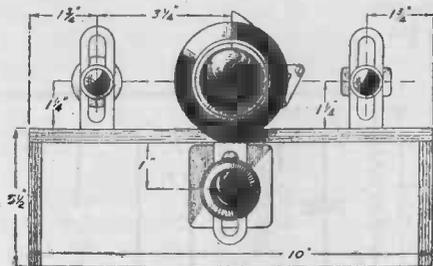


FIG. 28.—Method of mounting the controls for Circuit No. 13.

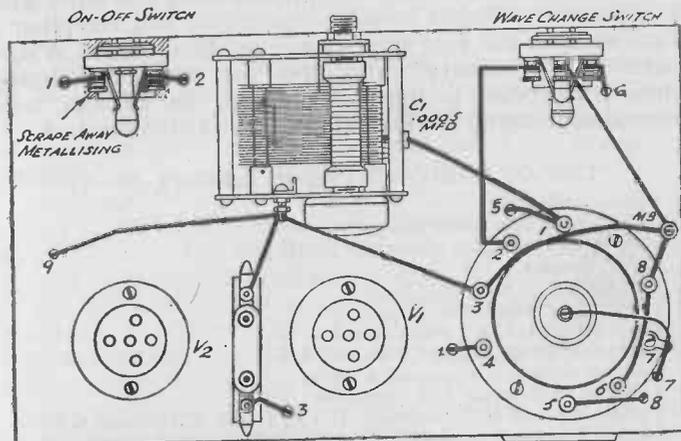


FIG. 29.—Circuit No. 13 as built.

(BLUEPRINT NO. P.W.76)

Reaction is provided by means of a differential reaction condenser, thereby ensuring an effective path to earth for the H.F. component at the anode of the detector valve. A special L.F. coupling unit is used between the detector

and output valves. This incorporates a resistance and a condenser as well as a transformer. Parallel-feed coupling is therefore provided with resultant good bass



MB—METALLISED BASEBOARD.

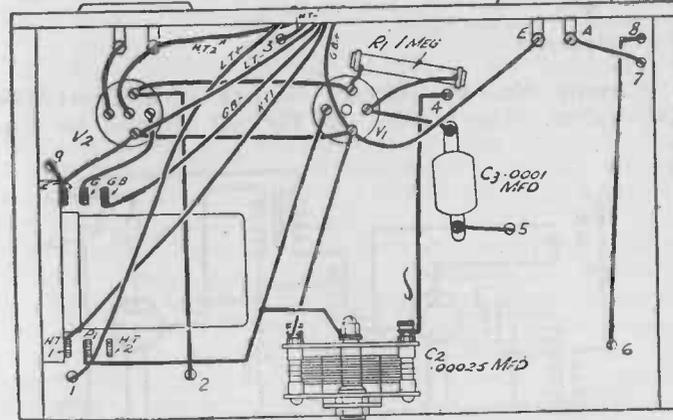


FIG. 30.—Wiring Diagram of Circuit No. 13

response. When a straight transformer coupler is used direct current passes through the primary winding of the transformer and bass response is consequently adversely affected. The transformer section of the coupling unit has a step-up

frequencies than we ever cover on the normal 300–500 metre waves. It is, of course, a fact that there is more "station-room" in the five metres between 30 and 35, for instance, than there is between 200 and 600! Thus, if we try to cover too wide a band with one swing of the tuning condenser, no one but a superman can hold a station, even if he succeeds in finding it at all. With this .0001 condenser three plug-in coils are needed to cover all the interesting wavelengths. The three bands into which the range is split up are roughly 15 to 30 metres, 30 to 60 metres, and 60 to 130 metres. All the long-distance broadcast that can be received at all regularly on the short waves is somewhere in these three bands. This allows comfortable tuning without incessant coil-changing.

The other variable condenser, for control of reaction, is of

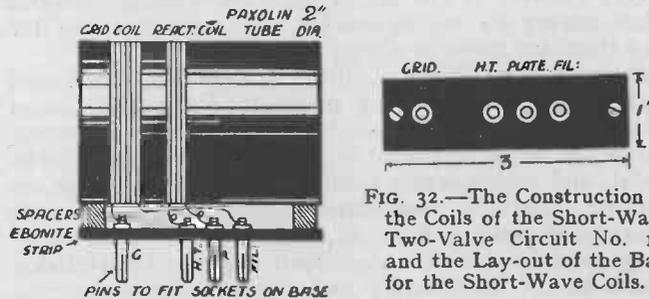


FIG. 32.—The Construction of the Coils of the Short-Wave Two-Valve Circuit No. 14, and the Lay-out of the Base for the Short-Wave Coils.

.0003 mf. capacity, the usual value for this purpose. The method used for this control, incidentally, is probably the best of all the known methods for short-wave work, and when the set is properly adjusted, gives a beautifully fine and smooth control. Swinging-coil reaction is, of course, years out of date, although it can still be seen in use.

Lay out the components and the wire up in accordance with the diagrams given, check over carefully, and insert the valves as follows: for the detector (the right-hand valve-holder from the back), use an "H.F." type—the standard general-purpose and detector valve. The make is unimportant, and the voltage must, of course, be chosen to suit the accumulator with which you propose to use the set. For the L.F. stage use a good power valve of the same rating.

Connect the H.T.— terminal to the negative end of your battery, H.T.+1 to a tapping in the region of 60 volts, and H.T.+2 to the full voltage, which should be 100 or 120. There is little point in using more, particularly if you value your ear-drums, for even a simple two-valver of this kind is capable of producing very loud signals.

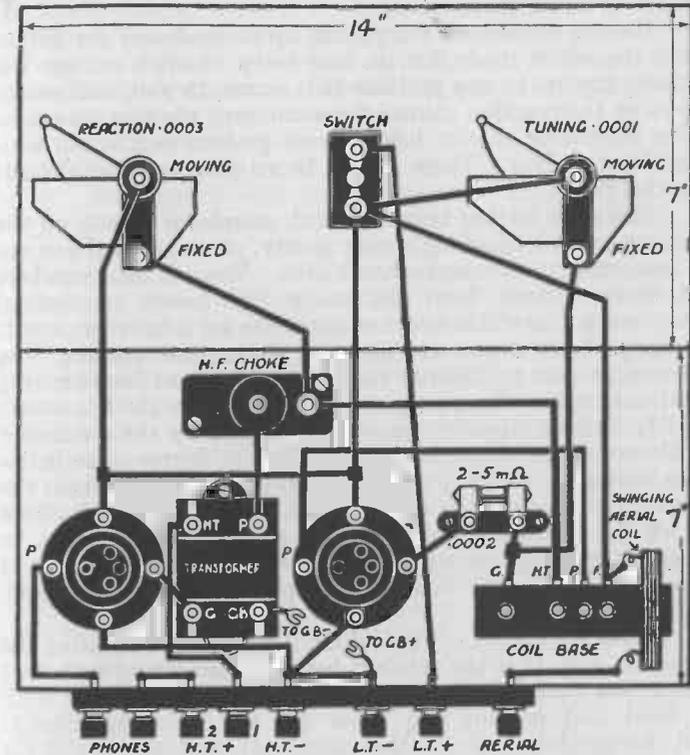


FIG. 33.—Wiring Diagram for the Short-Wave Two-Valve Set.

The Telephones and Accumulator.—These have now to be connected to their respective pairs of terminals, and also the aerial, which has not yet been mentioned. All the terminals, of course, are housed on one ebonite strip at the rear.

There is no particular point in using a very large aerial, since a small indoor affair, run round the picture-rail, or taken straight across the ceiling, will often give equally good signals. Your particular location will almost certainly enter into the question, and it will pay you to experiment with different lengths and heights. No provision has been made for the use of an earth on the set, since it very rarely has any effect at all on these waves.

Having connected everything up in readiness for listening, the set is ready for its first tests. Switch on, set the tuning control to any position that occurs to you, and gently revolve the reaction control from the zero position upwards. You should be able to hear the set go into oscillation, with the faintest hiss. There should be no pop or musical howl at this point.

This state having been achieved, search for signals on the tuning control, handling it very gently, particularly if you are a newcomer to the short-wave bands. You will hear numbers of Morse signals from the many high-power commercial stations, which will indicate whether the set is in order or not. Among these, if you are listening during the evening, you should be able to identify the carrier waves of broadcasting stations, among the most powerful of which are the following: HVJ, Vatican City, on 50.2 metres (high up the condenser scale on coil 2); Moscow, on 50 metres (a degree or so below the Vatican); Madrid (Spain, EAQ 2) on 31.5 metres (near the bottom of the scale on coil 2); W2XAF, Schenectady, New York (just below Madrid, but not audible until 11 p.m. or thereabouts); Rome, on 25.4 metres (at about the centre of the scale on coil 1); GSD, the Empire broadcasting station, a little above Rome.

Adjusting the Set.—First of all, if you find, on rotating the reaction dial, that the set does *not* start oscillating with that faint hiss that I have already mentioned, but does so with a loud and painful pop, look for the following causes: (a) accumulator needs charging; (b) voltage on H.T. too high for the particular detector valve you are using. Reduce gradually until you find the best position.

If, instead of the pop it develops a musical howl or hoot, the following remedies are sure to include one that stops it: (a) reduce high-tension again; (b) connect a small fixed condenser (above .0005) directly across the telephone terminals at the rear of the set; (c) use a resistance of $\frac{1}{2}$ -megohm or even $\frac{1}{4}$ -megohm across the secondary terminals

of the L.F. transformer, in place of the 1-megohm leak already shown there. It will be as well to use a leak of the clip-in type for this purpose in case such an alteration has to be made.

Coils.—All the diagrams of this set show the arrangement that is used for the particular set of short-wave coils that were employed in the original set.

Fig. 32, showing the coil base and a specimen coil, is sufficiently clear to need no extensive description.

Two windings are wound straight on a 2-inch paxolin tube. The wire is No. 22 enamelled, and it is "close-wound." About $\frac{1}{4}$ inch should be left between the two windings, which must, of course, be in the same direction.

Looking at the former with the "grid" pin (the pin separated from the other three) at the left-hand end, the "grid" winding should be commenced there, with its commencement taken to that pin. The end of the winding goes to the "filament" pin, at the other end. The reaction winding is then started. The end nearest to the "grid" winding goes to the terminal marked "H.T." and the far end goes to the remaining terminal, marked "P." or "Plate."

The numbers of turns for the 3 coils are: coil 1—grid 3 turns, reaction 2 turns; coil 2—grid 6 turns, reaction 5 turns; coil 3—grid 18 turns, reaction 12 turns.

In addition to these two windings mount an aerial coil in such a way as to swing towards the other, at the "filament" end. This consists of four turns, also of 2 inches diameter, and remains the same for all three wavelength-bands.

LIST OF COMPONENTS FOR CIRCUIT NO. 14

1 bakelite or ebonite panel, 14 in. x 7 in.	1 L.F. transformer.
1 cabinet for same, with base-board 7 in. deep.	1 3-megohm grid leak with clips.
1 set of short-wave coils, with base ("Air-King," Rothermel Corporation).	1 1-megohm grid leak with clips.
2 valve-holders.	1 .0002 fixed condenser.
1 .0003-mfd. variable condenser.	1 H.F. choke.
1 .0001-mfd. variable condenser.	1 ebonite strip with 8 terminals.
	1 L.T. switch.
	2 slow-motion dials.
	Glazite or tinned copper wire, wood screws, etc.

(BLUEPRINT NO. H.13)

Circuit No. 15.—In Fig. 34 is shown the circuit for a midget short-wave two. Like most short-wave sets it is straightforward. The aerial input signal is taken through a .0001 mfd. fixed condenser C.1 to the top of the aerial

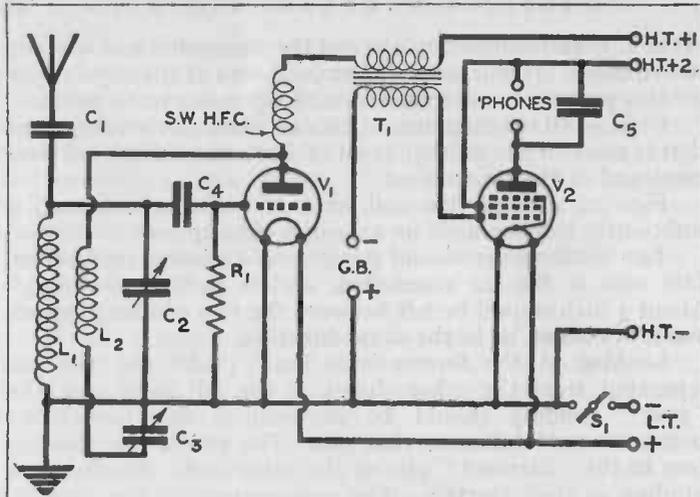


FIG. 34.—Circuit No. 15 for Midget Short-wave Two,

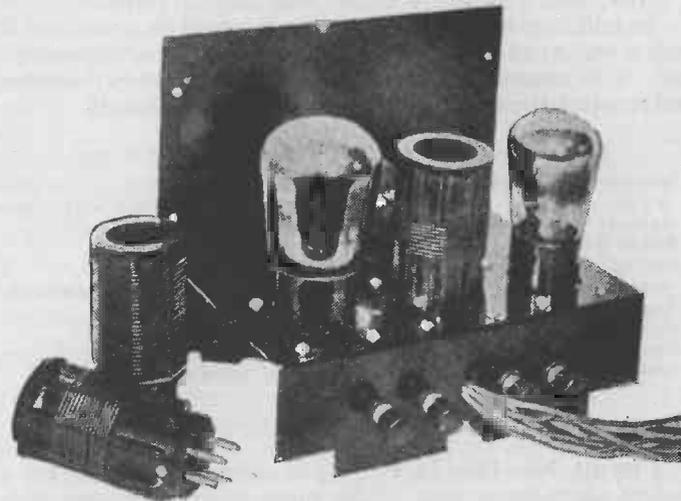


FIG. 35.—The Midget Short-wave Two as built (Circuit No. 15).

tuning coil L.1. This coil together with the reaction coil L.2 is wound on a small diameter ribbed 4-pin former. The turns are spaced and wound with 22-gauge enamelled wire, the ribs being slotted to ensure coil rigidity. The ranges for the coils, if such are purchased, are as follows: 10 to 21 metres, 18 to 37 metres, and 33 to 77 metres. This covers the most important of the short-wave transmissions including those stations which can be readily received under normal conditions. The first valve V.1 is a leaky grid detector and the reaction feed from the anode of this valve is *via*

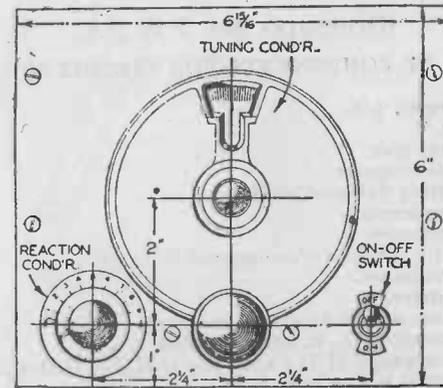


FIG. 36.—Drilling details for the Panel for Circuit No. 15.

coil L.2 and variable condenser C.3. For short-wave reception it is absolutely essential to have a really smooth reaction control, and, apart from the necessity of ascertaining the correct detector anode voltage to ensure this, a fine degree of accuracy is required in the reaction control. Erratic or coarse motion must be avoided, and then it is possible to bring in the weak signals which would otherwise not be possible. By having a calibrated scale and a ten-to-one reduction in its drive, the condenser employed in the actual receiver has proved most reliable.

Another factor which has to be watched in the case of a short-wave set is the high-frequency choke. First of all it must be free from any resonance peaks in the wavelength range covered, and the turns so spaced that they have a very low self-capacity. The component chosen embodies these two points, being wound as four small honey-

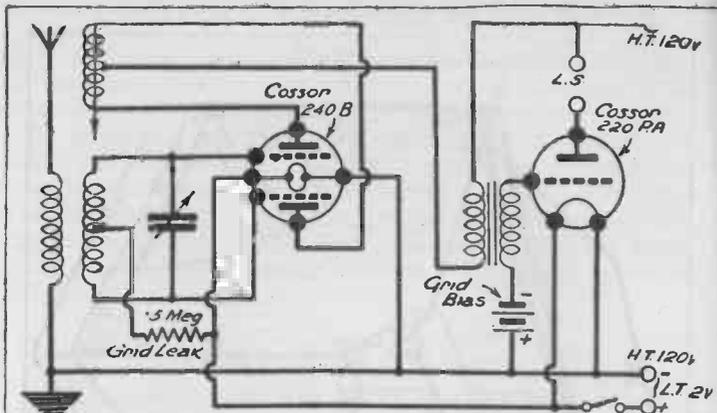


FIG. 39.—Theoretical Circuit of the Class B Detector Two-Valver

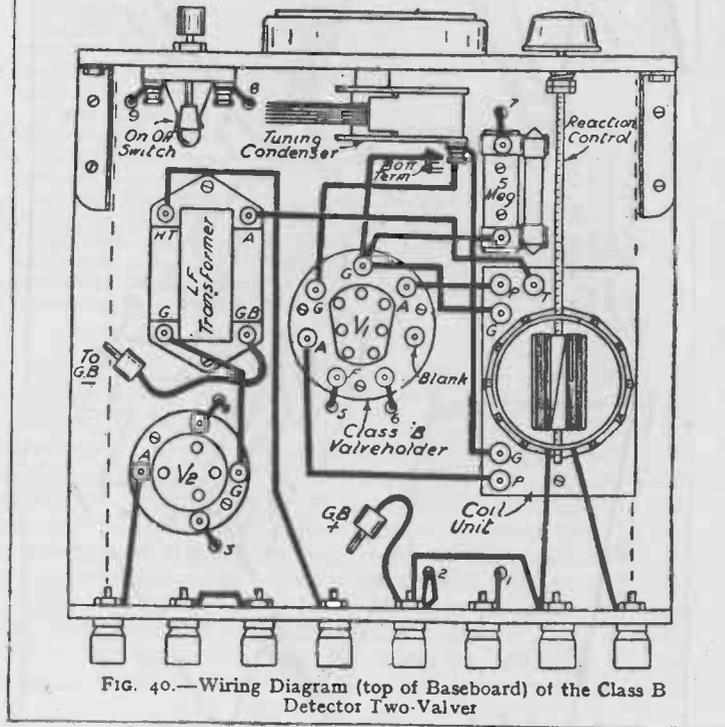


FIG. 40.—Wiring Diagram (top of Baseboard) of the Class B Detector Two-Valver

circuit is connected between the two grids and that this grid circuit is isolated from the rest of the wiring, except for the grid leak; also notice that there are no grid condensers at all. The grid coil is energised by magnetic induction from the aerial coil, so that the oscillating current in the circuit charges one grid negatively at the same instant that the other grid is positively charged. The two grid potentials are therefore always exactly half-a-cycle out of step with each other, consequently the H.F. component of the current from their respective anodes is also half a cycle out of phase. Now the two anodes are connected (after the push-pull reaction coil) to a common output, and in this output the


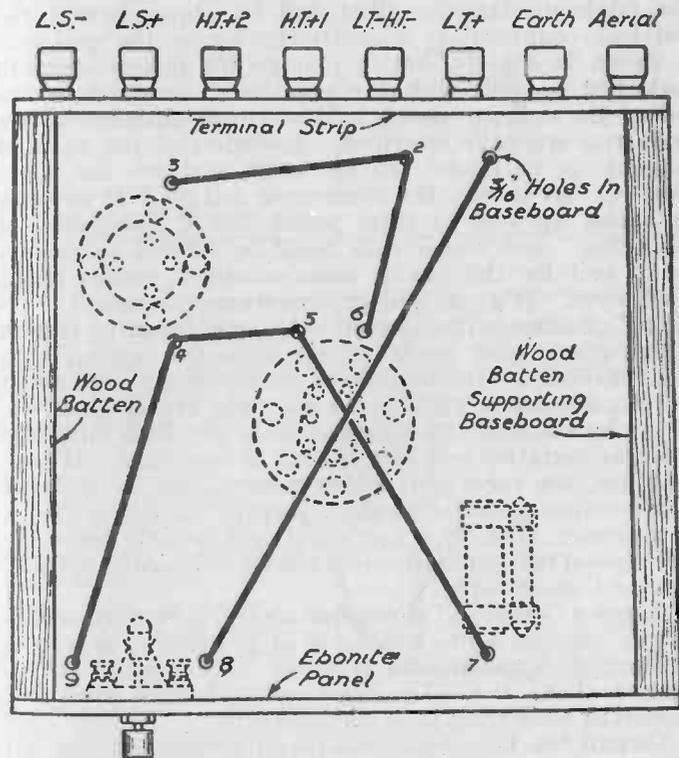


FIG. 41.—Sub-Baseboard Wiring Diagram of the Class B Detector Two-Valver.

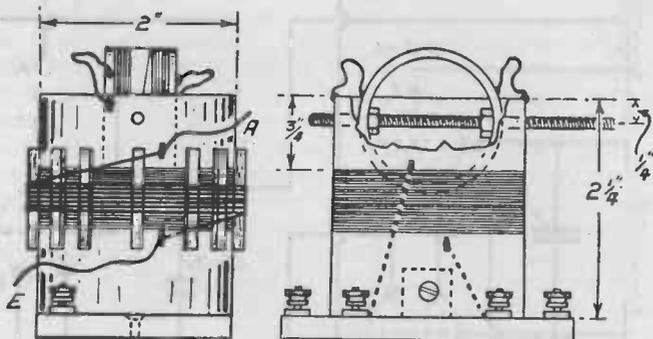It is essential to adhere to the components specified. The transformer, for instance, has a particularly high primary inductance, and gives definitely better results than a cheap transformer.



AERIAL COIL OMITTED TO SHOW GRID COIL

FIG. 44.—Further details of the Coil.

Also, if other valves are used, it may be found that it will be necessary to alter the number of turns on the reaction variometer. Reaction is frequently supposed to be unsatis-

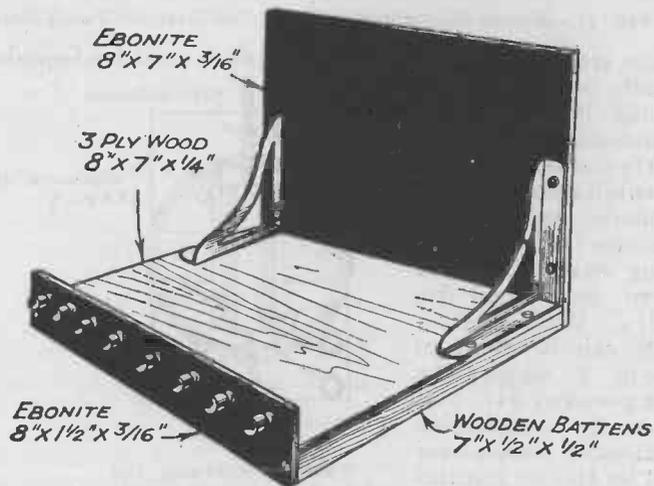


FIG. 45.—The Chassis Construction.

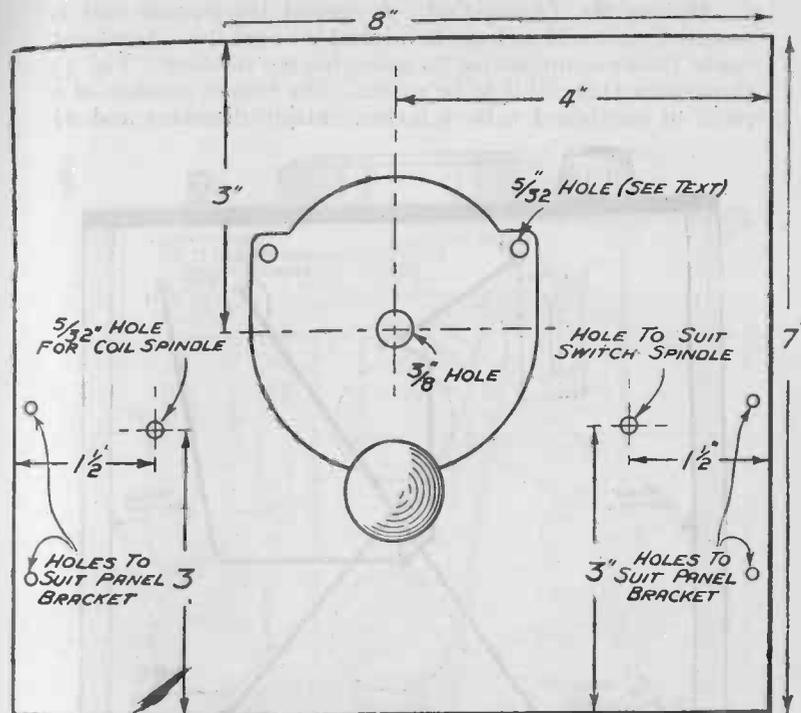


FIG. 46.—How to drill the Panel for the Push-Pull Detector Two-Valver.

factory with push-pull detection, on account of distortion, but in applying the push-pull principle by means of a variometer in the manner described, very satisfactory results can be obtained.

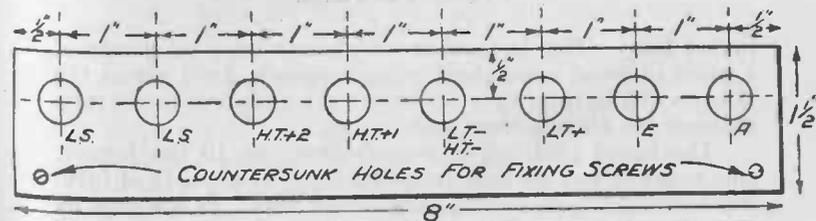


FIG. 47.—The Terminal Strip.

Making the Tuning-Coil.—A special home-made coil is required, so it will perhaps be advisable to get this component made before commencing to assemble the receiver. Fig. 43 shows how this coil is to be made. The former consists of a piece of cardboard tube 2 inches outside diameter and 2½

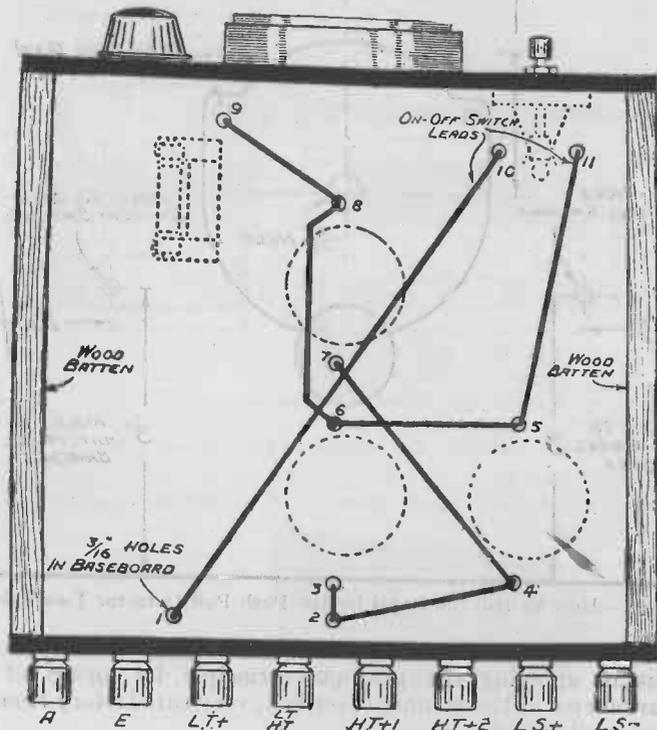


FIG. 48.—Sub-Baseboard Wiring Diagram for the Push-Pull Detector Two-Valver.

inches long. This is fixed to an ebonite base by means of a piece of wood about half an inch square, fixed across the bottom of the tube by a screw at each end, and two screws through the ebonite from underneath.

The tuned grid coil is wound direct on to the former, commencing ¾ of an inch from the top. It consists of fifty-five turns of No. 36 double silk covered wire; fix the ends by threading the wire three or four times through two small

holes about ¼ of an inch apart. Run the ends down the inside of the tube and then out to the two terminals marked "G." Now, cut twelve pieces of wood ¼ of an inch square and 1 inch long (good sound matches will do) and arrange these equidistantly round the former over the grid coil, and

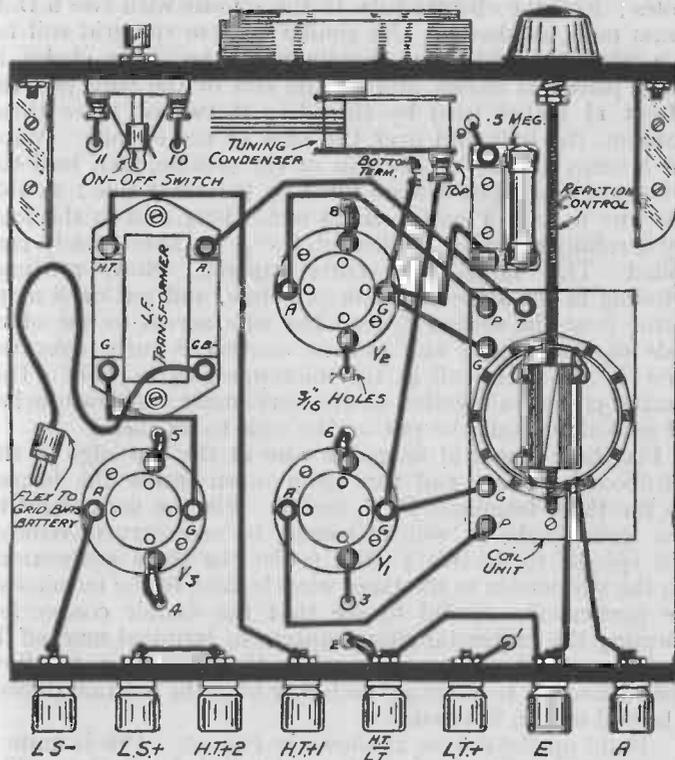


FIG. 49.—Baseboard Wiring Diagram of the Push-Pull Detector Two-Valver.

fix them to the former with a touch of secotone or other adhesive at each end. Wind the aerial coil on top of these pieces, as shown in Fig. 44. Use 28 gauge enamelled wire for this, and put on 12 turns; fix the ends as you did for the grid coil, but do not attach the ends to terminals and leave about 3 inches free and run these ends straight to the aerial and earth terminals of the set.

proved to be equally satisfactory for each wave-band. The grid leak is taken to the slider of a 250-ohm potentiometer, wired across the filament supply, so that exactly the correct grid voltage can be applied under all conditions. The potentiometer can be left in almost any position for more or less local reception, but it is extremely valuable when carrying out long-distance or S.W. reception. The H.F. choke has to deal with all wavelengths, and that chosen is specially designed for this purpose.

Instead of the usual L.F. transformer, a "Transcoupler" is employed which combines a high-efficiency transformer with a parallel resistance-capacity anode-feed circuit. The arrangement makes for "straight-line" amplification of all frequencies, besides giving a greater degree of amplification due to the absence of D.C. current in the primary windings. A decoupling resistance and condenser are used to feed the transcoupler, so preventing motor-boating and L.F. feed-back. A 100,000-ohm non-inductive resistance (actually a metallised one) is inserted in the grid lead of the power valve to prevent the passage of any stray H.F. currents into the amplifier. The power-valve chosen is one of the newer high-efficiency types, which gives a very high degree of magnification on a small anode current.

Practical Details.—A plywood panel is specified in the list of components, but an ebonite one may be used in its place, if desired. The plywood is, of course, cheaper, and is possibly the best material, because it can be finished in such a variety of ways to match cabinets or furniture. The position and diameters of the panel holes are given in Fig. 51. Details of the construction and wiring are most easily obtained from Fig. 52. All wiring is in "Glazite" insulated wire, which can be attached to the terminals after baring the ends by looping and fitting it under the nuts. It might not be quite clear from the wiring plan that two connections are made to the aluminium baseplate of the coil assembly. These are made by looping the wires round the holding-down screws before tightly screwing down the latter. These two connections slightly simplify the wiring and, of course, serve to "earth" the entire screening system. The two leads to the grid-bias wander plugs are made with flex, so that they can be moved more easily. The spaghetti resistance itself is used to connect the "high" terminal of the transcoupler to the 2-mfd. by-pass condenser. Little need be said of the other wiring, since this is perfectly straightforward.

LIST OF COMPONENTS FOR CIRCUIT NO. 18

1 plywood panel, 14 in. by 7 in.	2 '0001 mfd. (max.) pre-set condensers.
1 baseboard, 14 in. by 9 in. by 10 in.	1 3-megohm grid leak.
1 pair panel angle brackets.	1 grid leak holder.
1 ebonite terminal strip, 14 in. by 1 in. by $\frac{1}{4}$ in.	2 '0001 mfd. fixed condensers.
1 ebonite panel, 14 in. by 7 in.	2 low-loss valve holders.
9 terminals, marked A, A1, Earth, L.T.+, L.T.—, H.T.—, H.T.+, L.S.+, L.S.—.	1 universal H.F. choke.
1 '0005 mfd. variable condenser with slow-motion drive.	1 L.F. transcoupler.
1 dial indicator.	1 30,000 ohm spaghetti resistance.
1 '0001 mfd. reaction condenser.	1 2 mfd. fixed condenser.
1 2-spring battery switch.	1 100,000 ohm metallised resistance.
1 3-spring wavechange switch.	1 pair G.B. battery clips.
1 250 ohm potentiometer.	2 wander plugs, marked G.B.+ and G.B.—.
1 set "Four Range" coils; supplied complete with ganged aligned switches and baseplate (Colvern "Four-Range").	2 coils, glazite, odd lengths flex, $\frac{1}{2}$ -in. screws.
	2 valves (Cossor 210 H.L. and 220 P.A.).
	1 cabinet.

Circuit No. 19.—Fig. 53 shows a very simple three-valve set, consisting of a simple detector followed by two transformer coupled L.F. stages. The first transformer should be of low or medium ratio, say 2·7 or 3 to 1, and the second may be of the 5 to 1 type. Plug-in coils are employed for tuning, and the remarks on Circuit No. 4 are also applicable to the detector side of this circuit. The valves required are detector, L.F., and power, the first valve having about 60 volts H.T., the second 100 volts, and the last, or power, valve having the maximum which the makers recommend. As mentioned in regard to previous circuits, pay particular attention to the adjustment of the grid bias, as you will thereby prolong the life of both H.T. battery and valves.

LIST OF COMPONENTS FOR CIRCUIT NO. 19

1 '0005-mfd. variable condenser (C1).
1 '0002-mfd. fixed condenser (C2).
1 '0002 differential reaction condenser (C3).
1 2-megohm grid leak and holder (R1).
1 H.F. choke.
2 L.F. transformers.
3 valve-holders.
3 coil-holders.
1 on-and-off switch (S1).
Set of plug-in coils.
Terminals, connecting wire, and screws.

Circuit No. 20.—In this circuit, the first transformer has

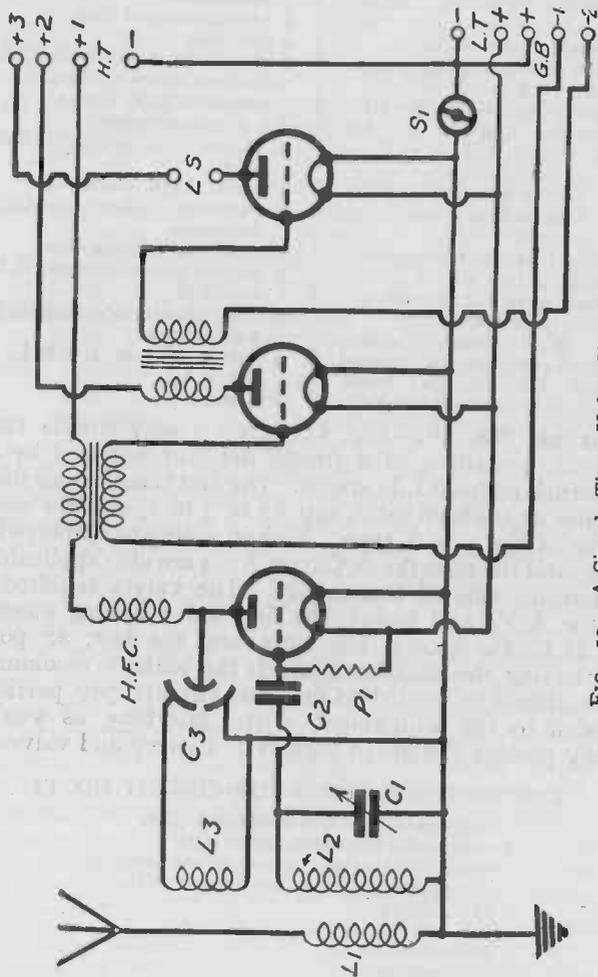


FIG. 53.—A Simple Three-Valve Circuit.

been substituted by a resistance-capacity coupling arrangement (Fig. 54).

Circuit No. 21.— In this arrangement (Fig. 55), a special type of L.F. coupling has been incorporated. This is known as an auto-transformer, and it gives a large step-up in voltage, besides being very good from the purity point of view. In other respects the receiver is similar to the two preceding sets. To make this receiver selective, a special form of band pass tuner is employed, and this is made by the same firm that makes the auto-transformer. The set will be eminently suitable for those who live fairly close to a regional station.

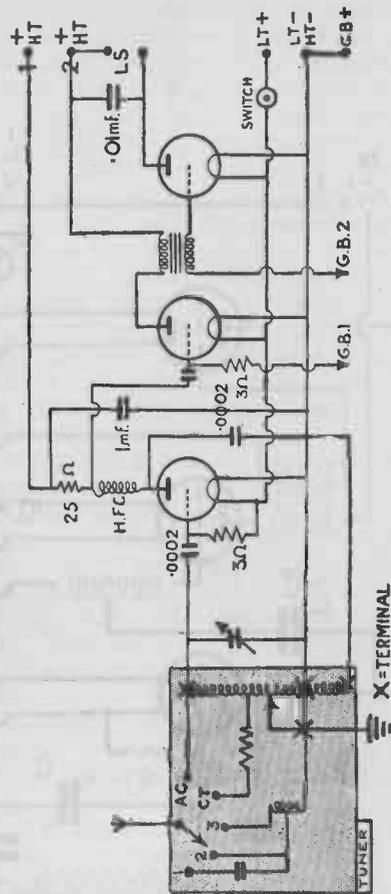


FIG. 54.—A similar Circuit to Fig. 53, except that it employs Resistance Capacity Coupling.

LIST OF COMPONENTS FOR CIRCUIT NO. 21

- | | |
|---|---|
| 2 .0005-mfd. variable condensers (C1 and C2). | 1 .5-mfd. fixed condenser (C5). |
| 1 square peak tuner. | 1 auto-transformer. |
| 1 .04-mfd. non-inductive condenser (C4). | 1 low-ratio L.F. transformer. |
| 1 .0002-mfd. fixed condenser (C3). | 3 valve-holders. |
| 1 2-megohm grid leak and holder (R1). | 1 on-and-off switch (S1). |
| 1 30,000-ohm resistance and holder (R2) | Terminals, connecting wire, and screws. |
| | 1 .0001 reaction condenser (C6). |

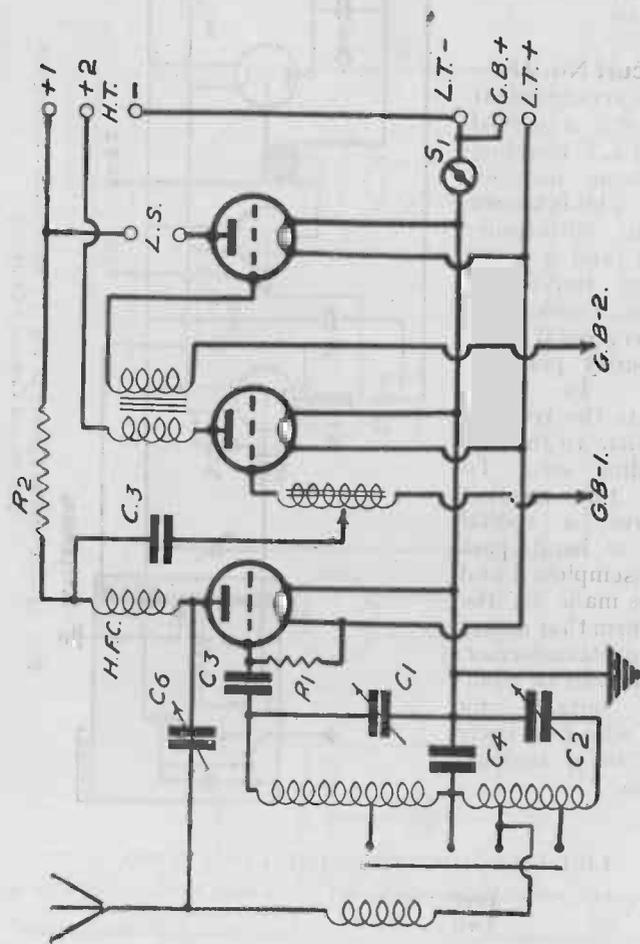


FIG. 55.—Three-Valve Circuit employing Auto-Transformer Coupling.

Circuit No. 22.—With the production of very small components has come the demand for a small and light-weight portable. Previously, receivers which masqueraded under the title of portable were in many cases heavier than a table receiver. You can now obtain midget speakers, valves, accumulators, H.T. batteries, transformers, tuning coils, variable condensers, and so on. Although this receiver is small it will receive a large number of stations at comfortable loud-speaker strength. It is an ideal receiver for cyclists, hikers, motorists, or for use on the river, picnicking, etc. It will be seen from Fig. 56 that there are three valves—a screen grid acting as H.F. amplifier, a triode as detector, and a pentode in the output stage. There are two tuned circuits, the frame aerial winding being tuned by a .0005 mfd. variable condenser, whilst the inter-valve coil is tuned by a second .0005 mfd. variable condenser. The reaction winding is arranged on this inter-valve coil, thereby considerably simplifying the construction of the frame aerial. I have made provision for a throw-out aerial to improve selectivity, although within normal distances of a broadcasting station, this is not necessary. A chassis is employed and the components are mounted on the sub-chassis principle. A wooden panel is attached to the front of the chassis to carry the speaker and to provide the necessary rigidity for the very light cabinet. This wooden panel also carries the frame aerial winding which is pile wound.

Coming now to the actual constructional work, this will be found extremely simple (see Figs. 57 and 58), and at the same time interesting, on account of the slightly novel form taken by this particular receiver. The accompanying illustrations show that the frame aerial is wound on the panel, and the theoretical diagram shows that the coil and the L.F. transformer are provided with colour-coded leads in place of the more usual terminals. This has been done in order to reduce weight and to avoid making extra connections, as the makers have already connected leads to the components and as shown in the diagram (Fig. 59) these are coloured for identification. The chassis is supplied by the makers ready drilled and the only components to be mounted upon it are the L.F. transformer, valve-holders, and the coil. Nuts and bolts should be used for these, and the tuning and reaction condensers which are mounted on the front should not be attached until the panel has been finished. Therefore, the wiring should be commenced as

soon as the three main chassis-mounted components have been fitted in position.

It will be noted that the frame aerial is wound on screws fitted to the front of the wooden panel. An alternative

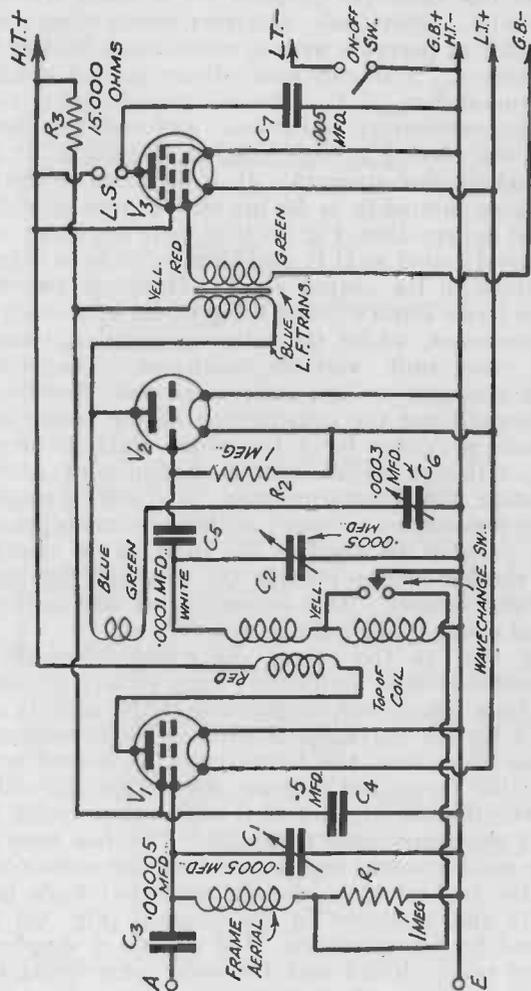


FIG. 56.—Circuit No. 22 for a Small Lightweight Portable.

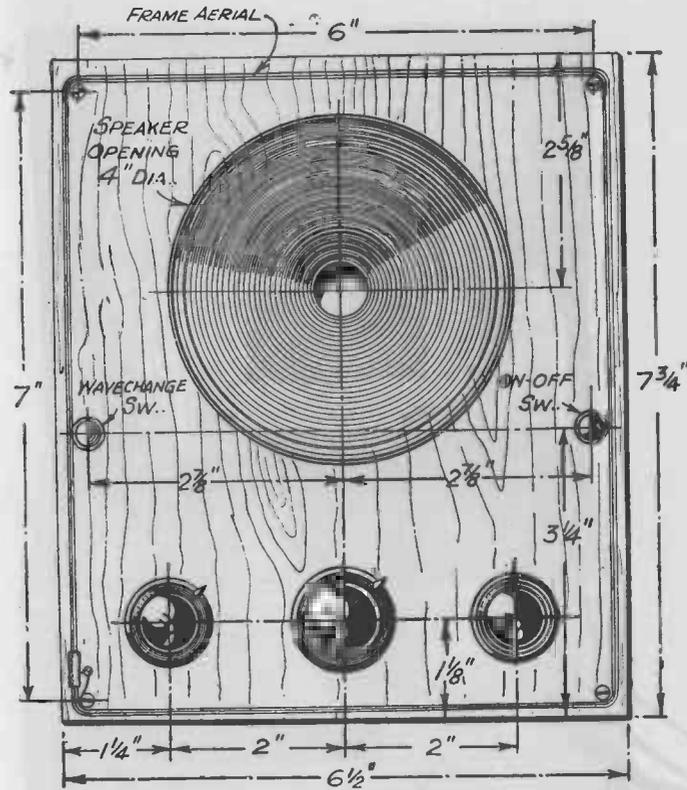


FIG. 57.—Dimensions for drilling Panel and making frame-aerial winding for Circuit No. 22.

scheme may suggest itself to the handyman—for instance, short ebonite rods may be tapped and bolted to the panel, or lengths of ordinary B.A. studding may be cut off and held in position with lock-nuts at front and rear. Whatever course is adopted, the length should be approximately the

same as the control spindles of the condensers. If metal is employed for these supports, some insulating material should be placed over them. Ordinary insulating tape may be placed over them. Ordinary insulating tape may be wrapped round two or three times, or lengths of thin glass-

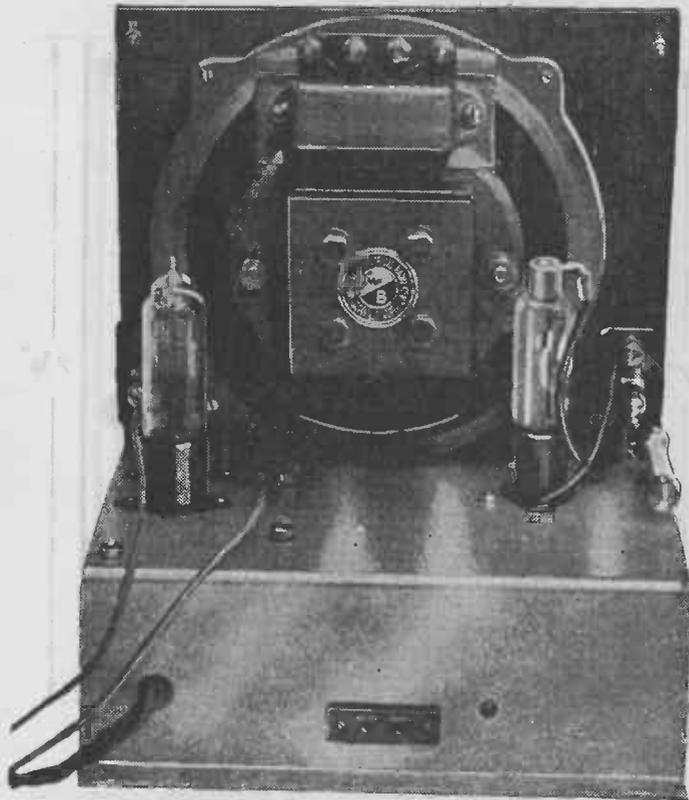


FIG. 58.—The Chassis of Circuit No. 22.

tubing may be slipped over and held in position with sealing wax—Chatterton's Compound or some similar medium. The panel is attached to the front of the metal chassis by means of the frame-aerial supporting bolts, and also by the fixing nuts on the three condensers. The frame aerial

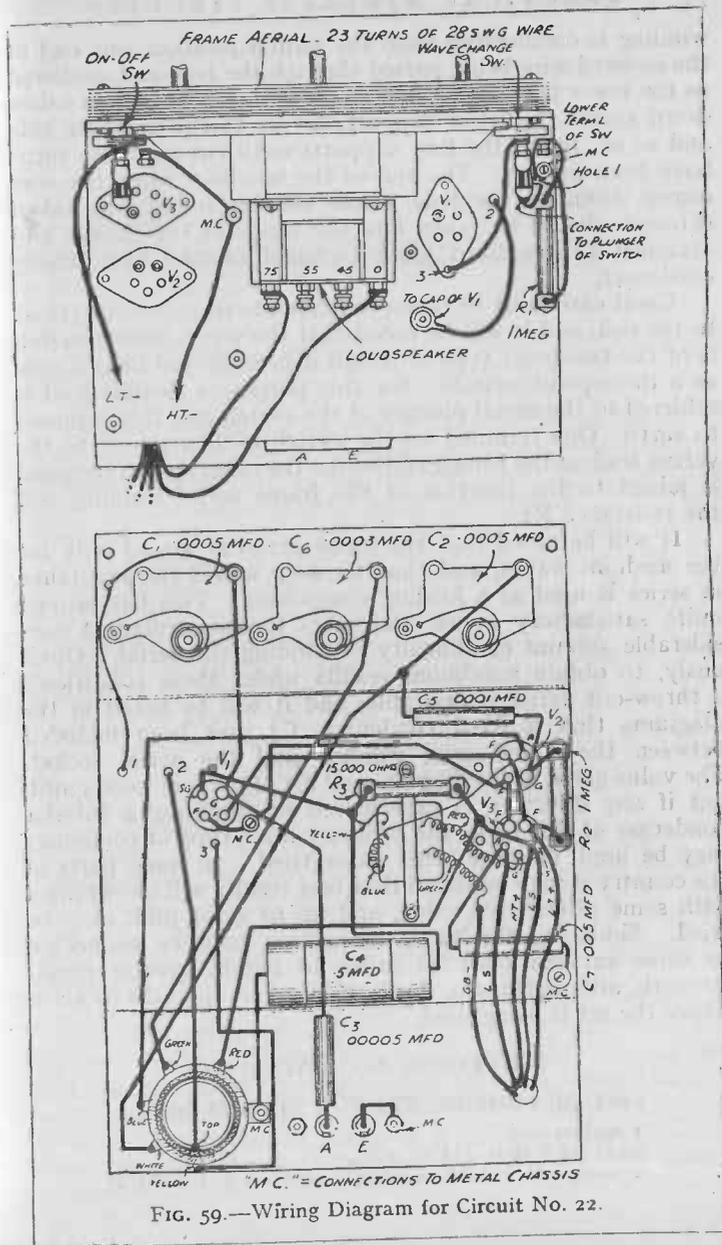


FIG. 59.—Wiring Diagram for Circuit No. 22.

winding is commenced from the switch position, one end of the covered wire being passed through the hole and anchored to the lower terminal on the on-off switch. It is then taken down round the lower support, across to the opposite side and so on, round the four supports until twenty-three turns have been put on. The end of the winding, when the wire comes down to the hole where the beginning was taken through, should be taken into the inside of the chassis and attached to the fixed plate terminal on the first tuning condenser.

Great care must be taken to make the correct connections to the coil, and it will be noted that the wave-change switch is of the two-point type although it is employed in this case as a three-point switch. For this purpose a flexible lead is soldered to the metal plunger of the switch and this is joined to earth. One terminal on the switch is then joined to the yellow lead on the tuning coil whilst the other switch terminal is joined to the junction of the frame aerial winding and the resistance R1.

It will be noted that the frame aerial is wound only for the medium waves, and thus for long waves the resistance in series is used as a loading component. This has proved quite satisfactory in use and saves the constructor a considerable amount of difficulty in winding the aerial. Obviously, to obtain maximum results under these conditions, a throw-out aerial is desirable, and it will be noted in the diagrams that a fixed condenser, C₃, has been included between the frame-aerial winding and the aerial socket. The value given in the diagram and list of parts is .00005 mfd, but if any difficulty is experienced in obtaining a tubular condenser of this type, the ordinary mica type of condenser may be used, or some other value tried. In some parts of the country it may be found that best results will be obtained with some alternative value, and up to .0002 mfd. may be tried. Similarly, the earth connection may be connected to some earthed body in order to obtain greater signal strength, although again, much will depend upon the location where the set is being used.

(BLUEPRINT NO. P.W.77)

LIST OF COMPONENTS FOR CIRCUIT NO. 22

- 1 midget coil.
- 60 ft. 28 S.W.G. D.C.C. wire.
- 2 .0005-mfd. bakelite tuning condensers (C.1 and C.2).

- 1 .0003-mfd. bakelite reaction condenser (C6).
- 4 fixed condensers (tubular type): .00005-mfd. (C3), .0001-mfd. (C5), .005-mfd. (C7), .5-mfd. (C4).
- 3 fixed resistors 1-watt type, 2 1-megohm (R1 and R2), 1 15,000-ohms. (R3).
- 1 L.F. transformer.
- 1 terminal socket strip.
- 3 valveholders, midget type: 2 4-pin, 1 5-pin.
- 2 switches type S.22.
- 3 midget valves, S.G. detector and pentode.
- 1 metal chassis, 6½ in. × 4½ in. × 2½ in., and panel 6½ in. × 7½ in.
- 1 pair of headphones.
- 1 midget loud-speaker type 37M.
- 1 H.T. battery (72-volts).
- 1 3 A.H. accumulator, type PRP3.
- 1 cabinet.

Circuit No. 23.—Figs. 60 to 62 show a circuit for an all-wave receiver employing three valves. It will be seen that although a straight three arrangement is employed the short-wave and normal broadcast units are separated, a complete changeover being effected by the self-contained switch. This arrangement is preferable to the method where all coils are connected in series. A further point is that in the detector grid circuit a small capacity tuning condenser is employed on short-waves and the standard capacity on the broadcast wavebands. This is carried out by using a 3-gang condenser in which two of the sections have a maximum capacity of .00025 mfd. and one of .0005 mfd. The two smaller sections are wired to contacts on the switch element so that on the broadcast bands the two sections are in parallel, but on short-waves only one section is in use and this is connected in parallel in the usual way with the short-wave coil. In the aerial circuit, where the tuning is not critical on short waves, the addition of a .00005 mfd. trimmer attached to the tuning dial enables the tuning to be satisfactorily adjusted, and the inductances of the coils are arranged so that the correct waveband is covered with the .0005 mfd. condenser.

The first valve is a variable-mu H.F. pentode, adjustment of bias by means of a panel-controlled potentiometer providing a control of volume or signal strength. The parallel-tuned anode coupling is employed between the first valve and the detector, and this valve is transformer coupled to the output pentode. Instead of using an H.F. choke for reaction purposes a resistor is employed, and this gives a much smoother control of reaction on the short-waves, and

direct fed, and the H.T. supply for the detector valve, as well as for the screen of the H.F. valve, is arranged with a separate lead so that the optimum working conditions may be found under all circumstances.

Attach lengths of wire to terminals 4, 5, 6, and 7 on the coil unit and place the latter in its position, cutting off the wires so that they will just reach to the respective connecting points as shown on the blueprint. Then cut off lengths of insulating sleeving and slip over each of these wires. Push the end of the short wire on terminal 6 through the grid socket on V.1 and screw down the coil unit, afterwards attaching the wires from terminals 4; 5, and 7 to their respective points. Replace the terminal on the grid condenser when the lead from terminal 4 on the coil unit is in position, and then attach one end of the anode resistance R.3 (15000 ohms), to the detector anode socket, locking this together with the wire from terminal 5 on the coil unit.

(BLUEPRINT NO. P.W.69)

LIST OF COMPONENTS FOR CIRCUIT NO. 23

- 1 all-wave coil unit.
- 1 3-gang condenser (.00025 + .00025 + .0005 mfd.) (C₁, C₃, C₄).
- 1 slow-motion drive including .00005-mfd. trimmer (C₂).
- 1 .0005 mfd. reaction condenser (C₅).
- 6 fixed resistances; 3 1 mfd., 1 .005 mfd., 1 .0001 mfd., 1 .0002 mfd.
- 3 half-watt resistors: 1 15,000-ohms, 1 50,000-ohms., 1 2-megohms.
- 1 volume control potentiometer with switch, 50,000-ohms.
- 1 all-wave H.F. choke.
- 1 L.F. transformer.
- 2 component mounting brackets.
- 3 baseboard mounting short-wave valveholders, 2 4-pin and 1 5-pin.
- 7 bowstring wanderer plugs: H.T.-, H.T.1, H.T.2, H.T.3, G.B.-1, G.B.-2.
- 2 spades L.T.+ and L.T.-.
- 3 valves.
- 1 speaker.
- 1 H.T. battery.
- 1 G.B. battery.
- 1 2-volt L.T. accumulator.
- 1 cabinet.

Circuit No. 24.—This is an ideal three-valver for the very beginner and employs a baseboard so that the wiring presents no difficulty. Fig. 63 shows the circuit, which covers four separate wave-bands, and the circuit is one which has been well tried. The main features are to be found in the initial stage which is a simple detector in the grid circuit of which a pair of coils are fitted. These consist

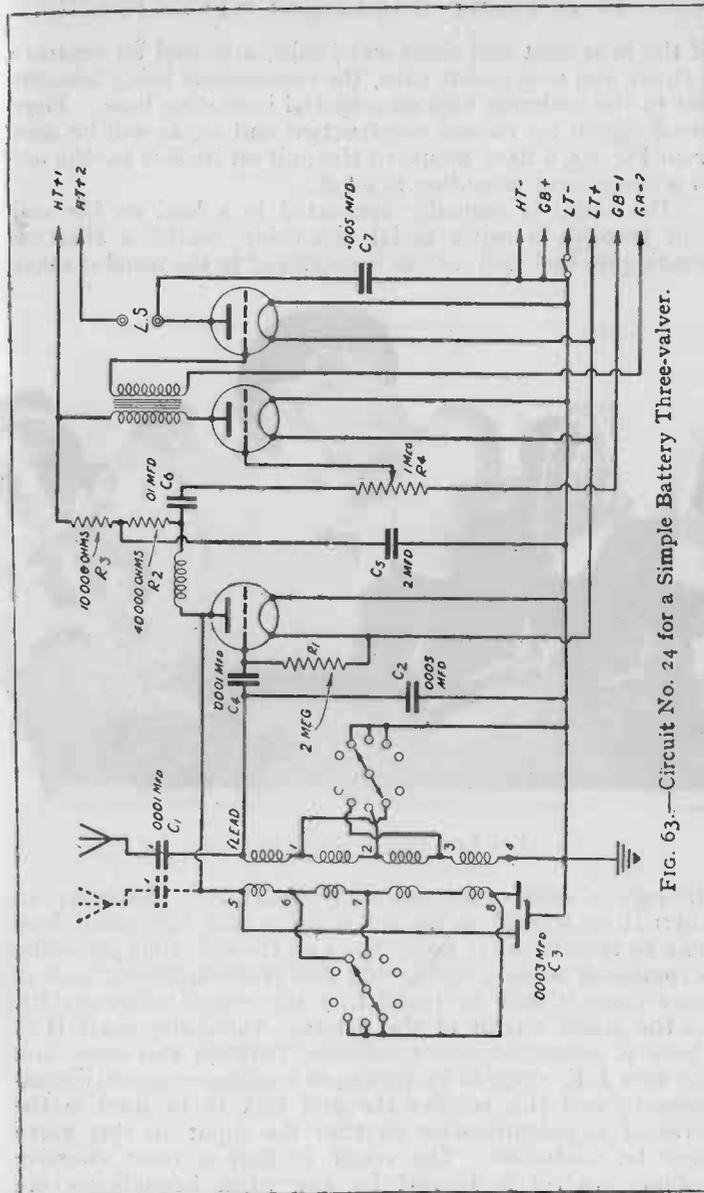


FIG. 63.—Circuit No. 24 for a Simple Battery Three-valver.

of the broadcast and short-wave coils, arranged on separate formers and in separate cans, the connections being brought out to the soldering tags on a special insulating base. They are designed for chassis construction and so, as will be seen from Fig. 64, I have mounted the unit on its side by the aid of a component mounting bracket.

The aerial is normally connected to a lead on the coil unit through a series aerial condenser, whilst a reaction winding on each coil section is employed in the usual manner


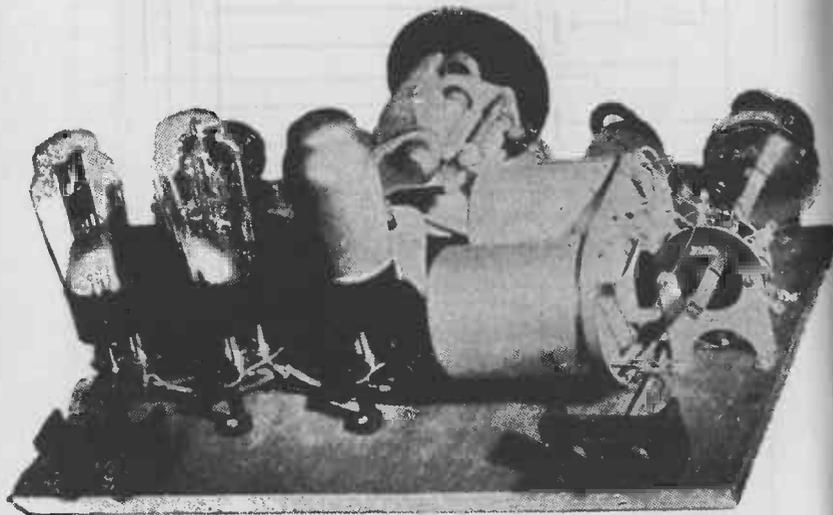


FIG. 64.—Circuit No. 24 as built.

through a differential reaction condenser. However, an alternative scheme is made available and the aerial lead may be transferred to point No. 5 on the coil, thus providing a combined aerial coupling coil and reaction circuit, and in some cases it may be found that this offers better results. In the anode circuit of the detector valve the usual H.F. choke is connected, but connection between this stage and the first L.F. stage is by means of resistance-capacity components, and this enables the grid leak to be used in the form of a potentiometer so that the input to this valve may be controlled. The result is that a most effective volume control is formed for use when headphones are

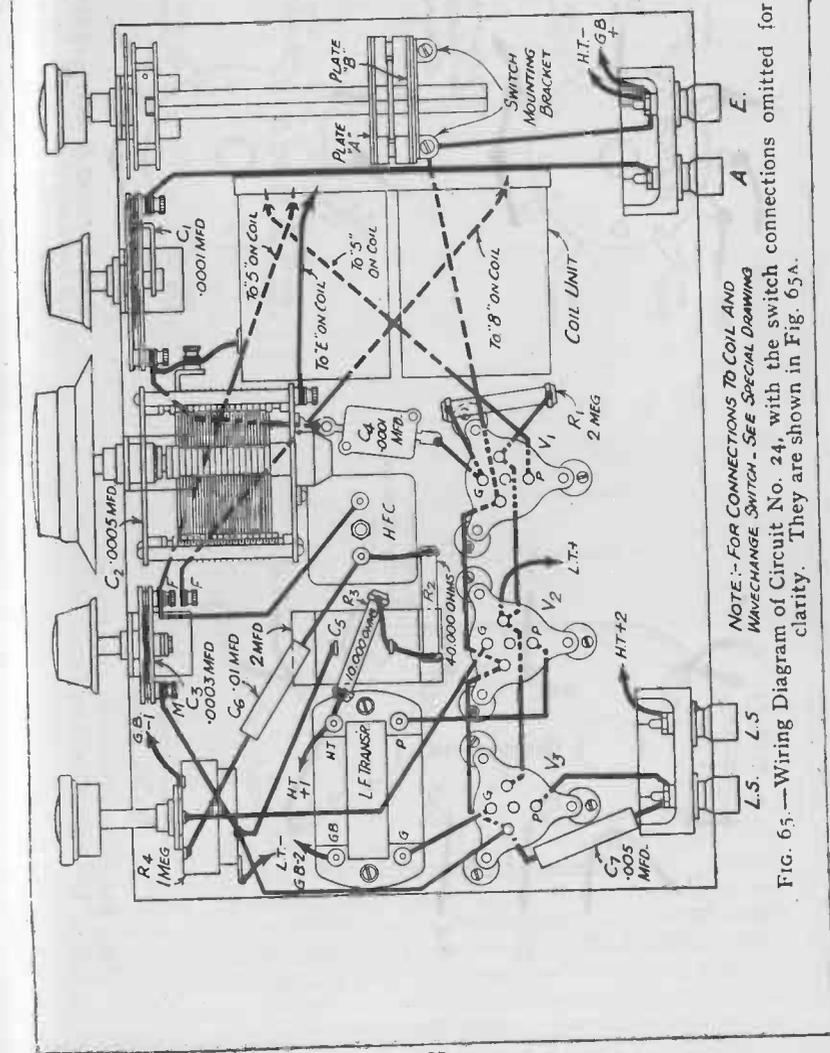

employed for searching, and this avoids the sudden bursts of volume which are liable to be met when no such control is fitted. Ordinary transformer coupling is employed between the L.F. and output stage, and for the latter a Power valve is used in preference to a pentode, both in the interests of economy and simplicity.

All the other usual circuit refinements which may be fitted to this type of receiver are to be found.

The four ranges covered by the receiver are approximately from 15 to 35 metres, 30 to 85 metres, 200 to 550 metres, and 1000 to 2000 metres.

(BLUEPRINT No. P.W.72)

LIST OF COMPONENTS FOR CIRCUIT NO. 24

- 1 4-range coil, No. C56.
- 1 driver-locator unit No. S150.
- 1 5-way contact unit No. S153.
- 1 .0005 mfd. condenser No. 2SM.
- 1 .0003 mfd. differential reaction condenser.
- 1 .0001 mfd. Compax condenser (C1).
- 4 fixed resistors: .0001 mfd. (C4), .005 mfd. (C7), .01 mfd. (C6), 2 mfd. (C5).
- 3 fixed resistors: 2 megohm (R1), 40,000 (R2), 10,000 (R3) (1-watt type).
- 1 potentiometer, 1 megohm with 2-point switch (R4)
- 1 L.F. transformer 3/1 No. LT135.
- 1 all-wave choke No. A.W.C1.
- 3 4-pin S.W. type baseboard mounting valveholders.
- 2 terminal blocks with A.E. and L.S. terminals.
- 6 plugs: H.T.-, H.T.1, H.T.2, G.B.+, G.B.-1, G.B.-2.
- 2 spades L.T.-, L.T.+.
- 1 baseboard 12 in. x 8 in.
- 6 component brackets.
- 3 valves: 1 detector, 1 L.F. and 1 power.
- 1 speaker.
- 1 H.T. battery 120-volts.
- 1 G.B. battery 9-volts.
- 1 L.T. accumulator.

Circuit No. 25*.—This circuit (Fig. 66) employs a Quiescent Push-pull output stage, and although this has now been superseded by the Class B arrangement, it is included in this book for the use of those readers who may possess one or more pentode valves, and prefer the slight lack of efficiency to the additional expense of purchasing Class B components. The tuning is carried out by means of band-pass circuits, and the condenser is of the ordinary two-gang type, having a separate concentric trimming knob. The L.F. transformer

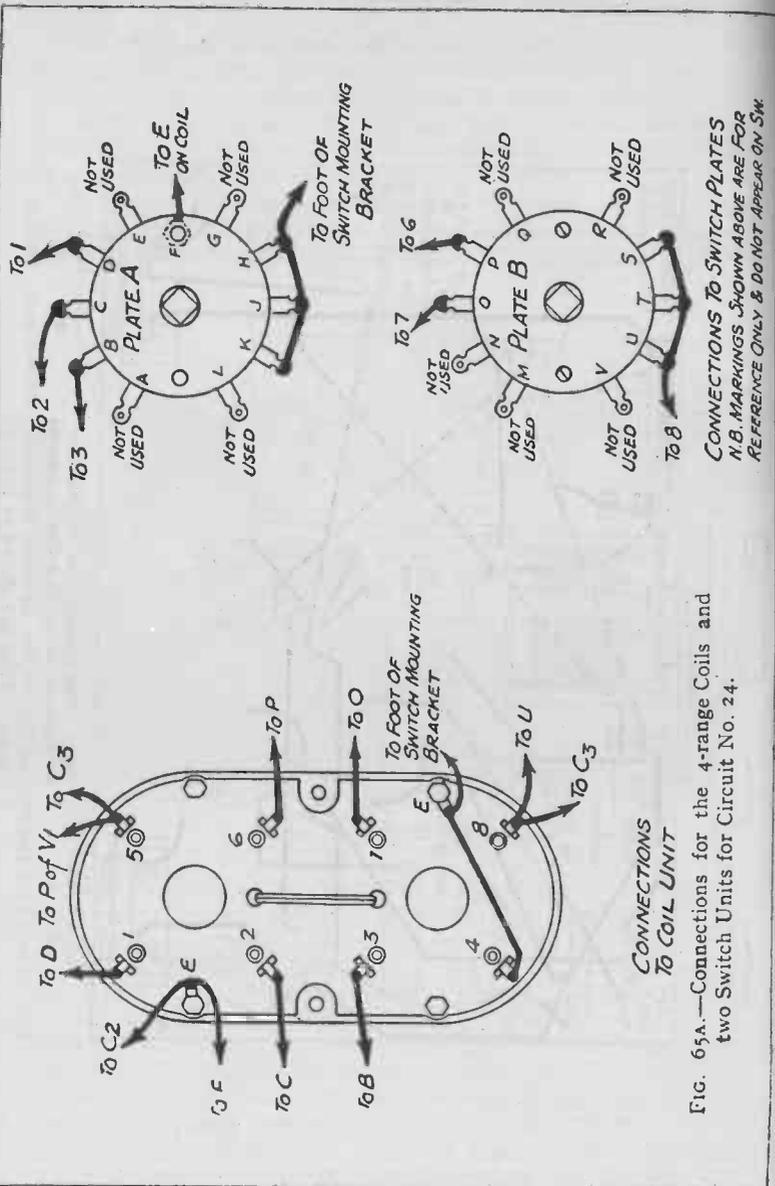


FIG. 65A.—Connections for the 4-range Coils and two Switch Units for Circuit No. 24.

should be of the special high ratio Q.P.P. type, and the grid bias should be carefully adjusted. This gives a very large signal output, and the range of the detector valve (which is of the S.G. type) is quite considerable. It is worth while building this receiver in one of the Consolette types of cabinet, with the speaker housed in the upper portion.

(BLUEPRINT NO. P.W.14)

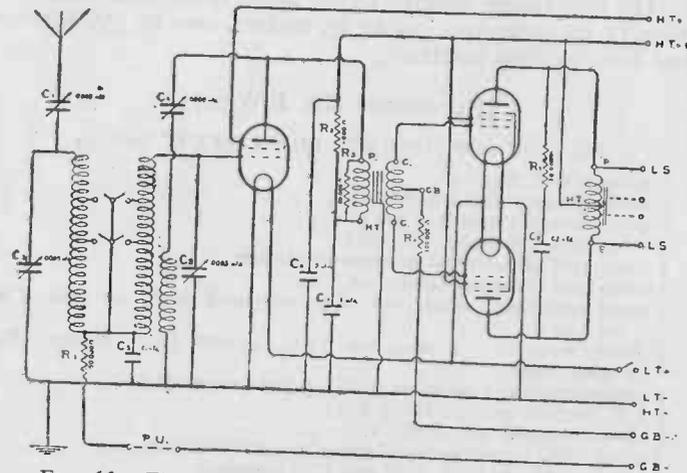


FIG. 66.—The theoretical Circuit of the Q.P.P. Three-valver.

LIST OF COMPONENTS FOR CIRCUIT NO. 25

- | | |
|--|---|
| 1 2-gang .0005-mfd. variable condenser with escutcheon (C2, C3). | 1 4-pin valve-holder |
| 1 .0003-mfd. fixed condensers (C1). | 1 coil unit. |
| 1 .01-mfd. fixed condenser (C5). | 1 On-Off switch. |
| 1 1-mfd. condenser (C7). | 6 terminals, marked E, A, L.S., L.S., Pick-up, Pick-up. |
| 1 2-mfd. condenser (C6). | 6 wander plugs, marked G.B.+, G.B.1, G.B.2, H.T., H.T.+1, H.T.+2. |
| 1 .02-mfd. condenser (C8). | 1 7-way battery cord. |
| 1 .0005-mfd. reaction condenser (C4). | 2 L.T. spade terminals. |
| 1 1000-ohm 1-watt resistance (R2). | 1 grid-bias clip. |
| 1 20,000-ohm 1-watt resistance (R5). | 2 coils Glazite. |
| 1 80,000-ohm 1-watt resistance (R3). | 2 valves Pen. 220A. |
| 1 50,000-ohm 1-watt resistance (R1). | 1 valve 215 S.G. |
| 1 100,000-ohm 1-watt resistance (R4). | 1 P.M. moving coil speaker. |
| 1 Q.P.P. transformer. | 1 panel, 14 in. x 8 in. |
| 1 Q.P.P. output choke. | 1 plywood baseboard, 19 in. x 7 in. |
| 2 5-pin valve-holders. | |

Circuit No. 26*.—This (Fig. 67) is an efficient receiver of simple construction, capable of giving high quality results from a number of stations. Tone control is incorporated, and although no H.F. stages are fitted, the range of the receiver is quite considerable. Switching for gramophone pick-up is incorporated, and therefore the receiver lends itself to the construction of a neat radio-gramophone. The receiver is very economical to run, the total H.T. consumption being only approximately 7 milliamps. The output varies between 110 to 140 milliwatts. The wiring is very straightforward, and no difficulty should be experienced in the construction.

(BLUEPRINT NO. P.W.10)

LIST OF COMPONENTS FOR CIRCUIT NO. 26

- | | |
|--|--------------------------------------|
| 1 plywood panel, 14 in. x 8 in. | 1 standard .0005-mfd. condenser. |
| 1 micro-dial. | 1 .0015-mfd. differential condenser. |
| 1 type "T.D." coil. | 1 3-point wavechange switch. |
| 1 On-Off battery switch. | 1 radio-gram switch. |
| 1 5000-ohm potentiometer. | 1 3-megohm grid leak. |
| 3 valve-holders. | 1 .0002-mfd. fixed condenser. |
| 1 5000-ohm potentiometer. | 1 3-megohm grid leak. |
| 1 .0002-mfd. fixed condenser. | 1 grid-leak holder. |
| 1 3-megohm grid leak. | 1 standard H.F. choke. |
| 1 grid-leak holder. | 1 Transfeeda. |
| 1 standard H.F. choke. | 1 2-mfd. condenser. |
| 1 Transfeeda. | 1 L.F. transformer. |
| 1 2-mfd. condenser. | |
| 1 L.F. transformer. | |
| 1 baseboard fuse-holder with 60 mA. fuse. | |
| 10 terminals—1 each marked A, E, L.T.+, L.T.-, H.T.-, H.T.+, L.S.-, L.S.+, and 2 marked Pick-up. | |
| 6 wander plugs—marked G.B.+, G.B.-, G.B.-1, G.B.-2, H.T.+, H.T.-. | |
| 1 strip ebonite, 14 in. x 1½ in. | |
| 1 G.B. battery clip. | |
| 1 coil Glazite connecting wire. | |
| 1 short length flex. | |
| 1 5-ply baseboard, 14 in. x 8 in. | |
| 2 pieces hardwood, 8 in. x 3½ in. x ½ in. | |
| 1 piece 3-ply, 14 in. x 2 in. | |

(BLUEPRINT NO. P.W.46)

LIST OF COMPONENTS FOR CIRCUIT NO. 27

- 1 metaplex chassis, 10 in. x 8 in. with 3 in. runners.
- 1 2-gang condenser, Baby type with dial.
- 1 2-coil assembly, type T.D.S.
- 1 reaction condenser .0003 mfd. (C3).
- 1 pre-set condenser, .0003 mfd. (C.4).
- 4 fixed condensers, 2 .5-tubular (C7 and C10), 2 .1-tubular type 250 (C5 and C6).
- 4 .0002-fixed condensers, type "M" (C8, C9, C11, C12).
- 1 50,000-ohm. potentiometer (R1).
- 4-ohm. resistances, 1 meg. (R2), 30,000 (R3), 2 10,000 ohms. (R4 and R5).
- 1 input push-pull transformer, type DP36.
- 1 H.F. choke, type H.F.8.
- 3 potentiometer brackets.
- 2 terminal strips, A.E. and L.S. P.U.
- 6 plugs, G.B. -1, G.B. -2, G.B. +, H.T. -, H.T. +1, H.T. +2.
- 2 spade terminals, L.T. + and L.T. -.
- 4 valves: 1 variable mu H.F. pentode, 1 detector valve, and 2 economy triodes.
- Loudspeaker.
- 1 on-off switch (3-point).
- 2 5-pin valve-holders.
- 2 4-pin valve-holders.
- 1 cabinet.
- 1 120-volt H.T. battery.
- 1 9-volt G.B. battery.
- 1 2-volt accumulator.

Circuit No. 28.—Fig. 69 is a simple four-valve arrangement, consisting of a screen-grid valve, detector, and two transformer-coupled low-frequency stages. The H.F. valve is coupled by what is known as the parallel-fed method, a H.F. choke being included in the anode circuit of the screen-grid valve. This choke must be of the special kind designed for use with this type of valve. There will be loss of amplification if the usual type of choke is included here. For the L.F. transformers, a low-ratio one should be used for the first stage, and a high-ratio for the second. The valves required, in their order, are: screen-grid, general-purpose or detector, L.F., and power. This last valve should be of the type which will handle a fairly powerful signal if distortion is to be avoided. Ordinary plug-in coils are used, a No. 60X for the aerial circuit, No. 60 for L2, and No. 50 for L3. These are, of course, for the normal broadcasting band. For the long waves, they will be No. 250, 250, and 100, respectively. The H.T. values should be 80 volts for +1, 100 to 120 volts for +2, and the maximum taken by the particular valve purchased for +3. In the case of battery valves this will be 150 volts.

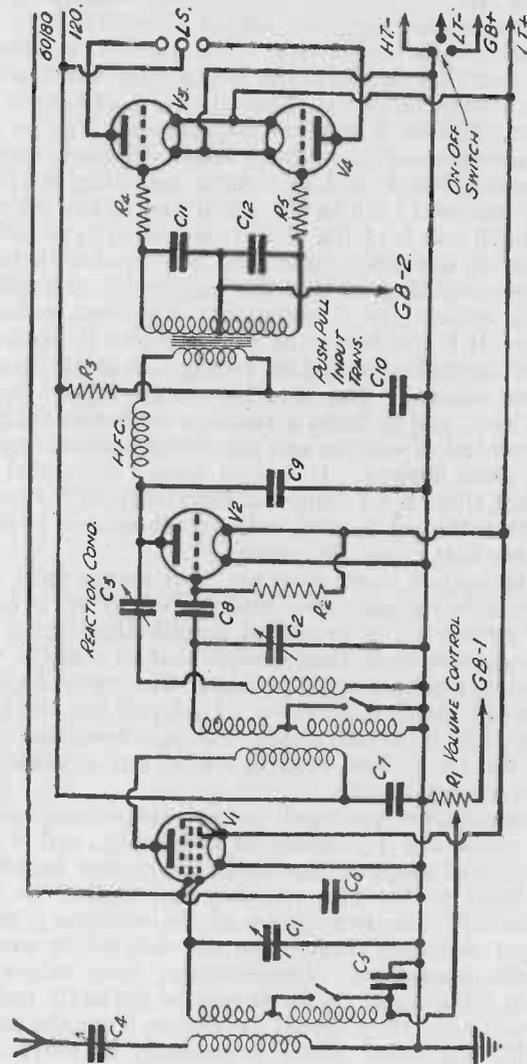


FIG. 68.—Circuit No. 27 for Battery Receiver with Push-pull Output.

LIST OF COMPONENTS FOR CIRCUIT NO. 28

- 2 ·0005-mfd. variable condensers (C1 and C2).
- 1 ·0003-mfd. variable condenser (C3).
- 1 ·0002-mfd. fixed condenser (C5).
- 1 ·001-mfd. fixed condenser (C4).
- 1 H.F. choke—screen-grid type.
- 1 H.F. choke—ordinary type.
- 1 low-ratio L.F. transformer.
- 1 high-ratio L.F. transformer.
- 1 2-megohm grid leak and holder (R1).
- 3 baseboard mounting coil-holders.
- Coils as mentioned in above notes.
- 1 on-and-off switch (S1).
- Terminals, connecting wire, and screws.

Circuit No. 29.—This circuit (Fig. 70), is on the same lines as No. 20 except that the H.F. valve is coupled by the tuned-anode method, which gives greater signal-strength, but requires a little more care in construction. A special type of commercial coil will be required, and this should be wound in what is known as the astatic manner. In addition, a vertical screen of copper or aluminium must be affixed to the baseboard, and a hole in the screen should allow the valve to be mounted with the screening grid in the same plane as the screen. On one side of the screen all the grid circuit components are mounted, whilst on the other the anode components are fixed. The screen is shown in the circuit diagram. The aerial circuit coils L1 and L2 may be ordinary plug-in coils or a commercial six-pin aerial transformer. No H.F. choke is required in the anode circuit of the detector valve, as the anode resistance acts as an efficient H.F. stopper.

LIST OF COMPONENTS FOR CIRCUIT NO. 29

- 2 ·0005-mfd. variable condensers (C1 and C2).
- 1 ·0003-mfd. variable condenser (C3).
- 1 ·001-mfd. fixed condenser (C4).
- 1 ·0002-mfd. fixed condenser (C5).
- 2 2-megohm grid leaks and holders (R1 and R3).
- 1 100,000-ohm anode resistance and holder (R2).
- 1 medium-ratio L.F. transformer.
- 1 astatic tuned anode unit with reaction.
- 1 aerial transformer or coils and holders.
- 4 valve-holders (one of the horizontal screen-grid type).
- 1 on-and-off switch (S1).
- Aluminium screen with hole for valve.
- Terminals, connecting wire, and screws.

Circuit No. 30.—Fig. 71 shows a circuit for a four-valve receiver battery operated covering three wave-bands but having two tuned circuits.

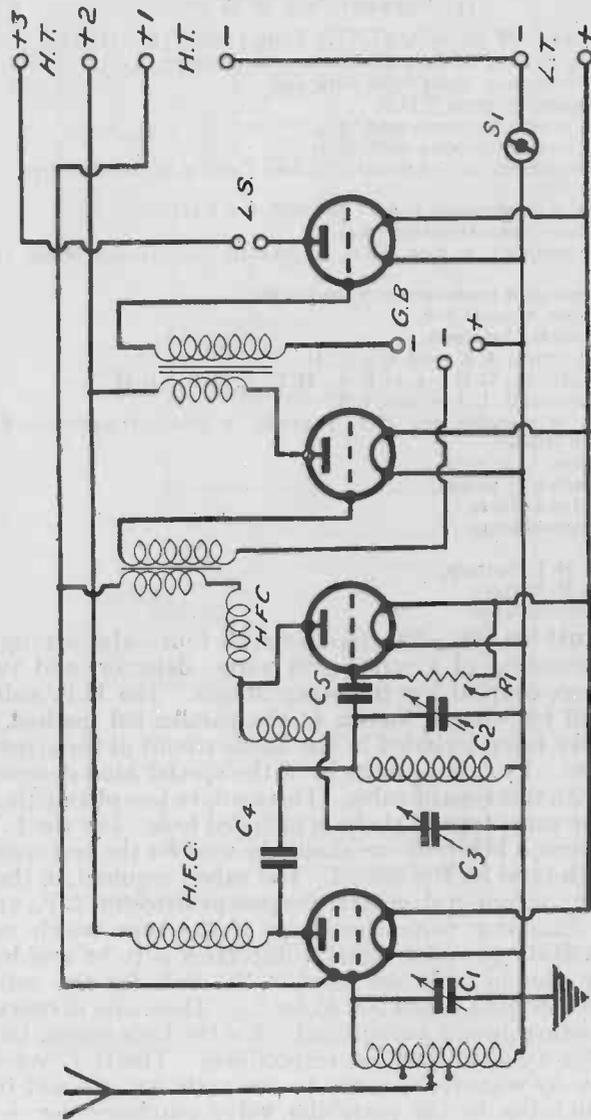


FIG. 69.—Four-valve Circuit No. 28, with Screen-Grid, Detector, and two L.F. Coupled Valves.

enable the chassis easily to be inverted from time to time during wiring, two lengths of wood should be screwed to the side runners, of sufficient length to clear the condenser, and the set will rest on these when inverted and thus stand firm.

The wiring should be carried out with a fairly heavy gauge wire—say 18 or 20 bare-tinned copper. Make certain that all leads are fairly rigid and stretch them from point to point to avoid difficulties on the short-wave band which might be introduced by wires which move when subjected to vibration. Where the leads pass through the chassis it may be advisable to take some precaution to avoid short-circuits and there are two methods of doing this. Firstly, lengths of insulated sleeving may be slipped over the wires of such a diameter that they wedge into the hole and thus prevent the wire from touching the edge of the metal. A simpler plan is to remove the metal round the hole, either with a countersink bit, or by scraping round with a pen-knife. The insulated sleeving is the most business-like method, and lends a finished appearance to the set. The points marked M.C. on the blue-print indicate that the wires at that point are in contact with the metal chassis. The method of doing this is to take a long bolt and two fairly large washers which may then be used to hold in place the wires referred to. On the coil units the two M.C. points will be served by the screws used to hold down the coil screens. Remember in all of these cases, that the ends of the wires should be turned in a clock-wise direction so that when the screws are tightened up the wires will not be pushed out. If the ends are turned in an anti-clockwise direction, as the screws are tightened the ends of the wires will be pushed out from between the washers or screw-head.

In the case of the ganged condenser it is important to note that the two leads which come up through holes 4 and 6 are joined to the tags in contact with the *fixed* sets of plates. There are two contacts on the underside of the condenser chassis for this purpose, and they are in the same electrical relationship as the tags on top of the condenser to which the leads from terminals S on the two coil units are joined. By making use of the lower tags you avoid the necessity of running long leads up from the chassis to the top of the condenser. It is also necessary, if this is your first attempt at receiver construction, to be on your guard when wiring the five leads to the combined volume control and

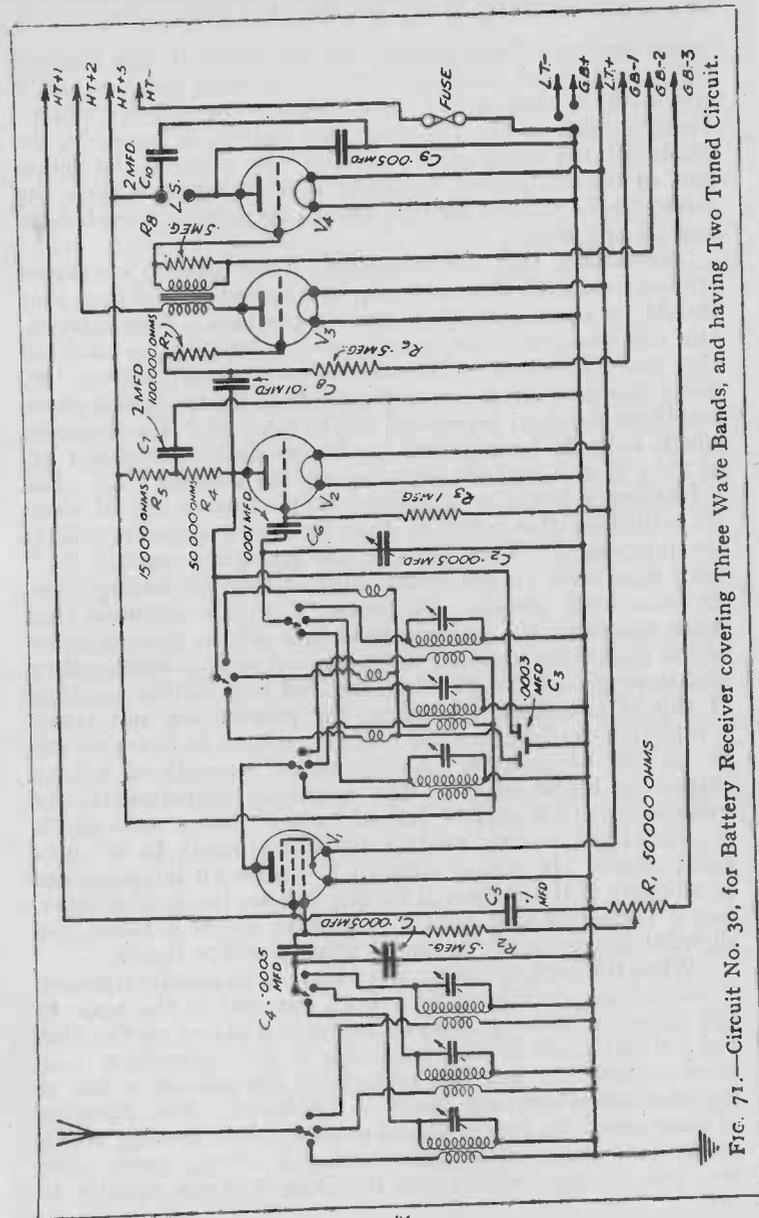


Fig. 71.—Circuit No. 30, for Battery Receiver covering Three Wave Bands, and having Two Tuned Circuit.

on-off switch. Three connections are made to the top and three to a lower part, and the leads from holes 7 and 8 and from the chassis (M.C.) are joined to the switch contacts. These appear on the raised ebonite portion attached to the centre of the component. Round the edge of the larger part of the component are three further lugs and these are joined to the volume control, and to them leads from holes 9 and 10 are joined.

Remember that the trimmers on the ganged condenser are not used with this particular coil assembly, and thus they should be opened to their widest position. Alternatively, you can unscrew them entirely, and open them out so that they have no effect at all on the inter-circuit wiring. By doing this you will make quite sure that the minimum wavelength on the short waveband will be covered. The trimmers which have to be adjusted for the medium-wave band are in the coil unit and are identified by the number "2." Use a thin screwdriver or a pointed or sharpened slip of wood for adjusting this screw so that no undue capacity effects are introduced. Turn each of the trimmers marked "2" until maximum volume is obtained at the dial setting given for your local station. Of course, it will be assumed that when mounting the dial you have first set the moving vanes of the condenser to either the minimum or maximum setting and have placed the point on the dial to a similar position. If this is not done, of course, the pointer will not travel completely across the scale and the station indications will be all out of position. As the signal strength of a local station is increased with the trimming adjustments, the volume control should be turned back so that a weak signal is maintained as this enables the adjustments to be more easily made. It is very difficult to notice an improvement in strength if the station is blaring out on the loud-speaker, but if turned so that only a very weak signal is heard, the slightest improvement or loss of volume will be heard.

When the medium waves have been satisfactorily trimmed it should be possible to turn from one end of the scale to the other and pick-up stations at various places on the dial, the stations heard in your particular locality depending upon local conditions. For this reason, do not publish a list of the stations which are likely to be heard. The direction of your aerial, its height above ground, any screening which might be introduced by surrounding buildings, trees, hills, etc., will all affect results and therefore it is not possible to

say just what you will hear. It should be possible, however, in most parts of the country to pick up quite a number of stations, both English and continental, at good volume. The long-wave band is trimmed by adjusting trimmers numbered "3" and the same procedure is carried out as has been mentioned for the medium-wave band.

For the short-waves the process is slightly more difficult and all adjustments must be made very carefully indeed. This time the trimmers used are numbered "1" and the location of a station upon which to make the adjustments may be found rather difficult if you have never used a short-wave receiver before. In spite of the reduction gearing on the tuning control, the very slowest adjustments should be made, and you will probably find that the reaction condenser may now be used as an aid to trimming. Advance the reaction condenser until the receiver is brought to the verge of oscillation. This will be indicated by a rushing sound in the loud-speaker, and if carried too far, a whistle will be heard. When a station is tuned, a rising whistle will be heard, and this may fall as the condenser is turned still further. Slacken off the reaction control until the whistle ceases and re-adjust the tuning condenser. Then adjust the trimmers and note carefully when any improvement is made in signal strength, without touching the reaction condenser. You will probably find it necessary to trim on stations at both ends of the scale on the short-waves and a slight compromise may have to be effected so that the best results are obtained throughout the scale. The reaction condenser will, of course, slightly modify the effects of the trimmers and thus the trimming on short-waves will have to be carried out carefully in order to obtain maximum results. When once adjusted, however, no further difficulties should arise, and it should then be possible to turn through the scale on either of the three wavebands, and pick up stations at various parts of the dial, augmenting signal strength, where required, by means of the reaction condenser. The type of aerial which you use will prove of importance, and next week we will deal with this part of the equipment.

(BLUEPRINT NO. P.W.79)

LIST OF COMPONENTS FOR CIRCUIT NO. 30

- 1 all-wave coil, type Triogen, with 2-gang spindle.
- 1 2-gang condenser, Bar type 0005 mfd. (C1, C2).

- 1 S.M. drive, with station names.
 1 differential reaction condenser, .0003 mfd. (C₃).
 1 potentiometer, 50,000 ohms. with 3-point switch (R₁).
 1 L.F. transformer, type AF8.
 7 fixed condensers: 2 2 mfd. (C₇, C₁₀), type 65, 1 .0001 mfd. (C₆), 1 .0005 mfd. (C₄), 1 .005 mfd. (C₉), 1 .01 mfd. (C₈), 1 .1 mfd. (C₅).
 7 fixed resistances: 1 1-meg. (R₃), 3 .5-meg. (R₂, R₆, R₈), 1 100,000-ohms. (R₇), 1 50,000-ohms. (R₄), 1 15,000-ohms. (R₅), type F $\frac{1}{2}$.
 4 valveholders: 4-pin chassis mounting.
 2 socket strips, A.E. and L.S.
 2 component brackets.
 1 chassis, 12 in. x 8 in. x 3 in. (ready drilled for valveholders).
 8 plugs: H.T.1, H.T.2, H.T.3, G.B.+ , G.B.-1, G.B.-2, G.B.-3 midget type.
 2 spades, L.T.-, L.T.+.
 4 valves: variable- μ pentode, 2 detector valves, and a small power valve.
 1 fuse and holder, 100 m/A.
 1 speaker.
 1 H.T. battery, 120-volt.
 1 G.B. battery, 9-volt.
 1 accumulator, 2 volt.

Circuit No. 31.—Fig. 72 shows another very lightweight portable battery type of receiver. The circuit is quite orthodox, employing an S.G.H.F. stage, detector, Driver, and Class B valves and thus provides a large output. A diagram is given (Fig. 73) showing the connections to the terminals, and to enable this particular unit to provide maximum results it is suggested that the H.F. coupling condenser be reduced in capacity to .0003 mfd.

The framework of the cabinet is constructed from strip-wood 1-inch wide by $\frac{1}{4}$ -inch thick and this is screwed together by means of short metal strips. The following illustrations show the method of building it and give all dimensions. The opening or speaker grille is 5 $\frac{1}{2}$ inches in diameter, and is covered on the inside with silk or the special fabric obtainable from any good radio dealer. The cabinet is afterwards covered with leatherette glued in position and a carrying handle is attached to the cross strips on the upper surface. The front of the cabinet is attached by hinges to the lower edge so that it may be lowered to insert the batteries and make tests or voltage measurements.

The frame aerial is wound on the inside of the front, spacing strips of ebonite being screwed diagonally in the four corners. These strips are no longer on the market, but may be made by obtaining a piece of $\frac{3}{8}$ inch ebonite and cutting strips half an inch wide and 2 $\frac{1}{4}$ inches in length.

Drill holes at each end so that they may be screwed to the front of the cabinet and then with a hacksaw make eight cross cuts about $\frac{1}{4}$ inch deep, followed by two further slots made by making two cuts and breaking out the intervening piece of ebonite so that these two slots are nearly $\frac{1}{8}$ of an inch in width. All of the slots should be cut at an angle so that when the wire is wound in it will be prevented from falling out. One end of the 24-gauge wire is soldered to the upper right-hand contact of the tuning condenser and the wire is then passed across to the upper slot of the nearest spacer. Run the wire across to the left, through the upper slot on the left-hand spacer and down to the lower spacer, across

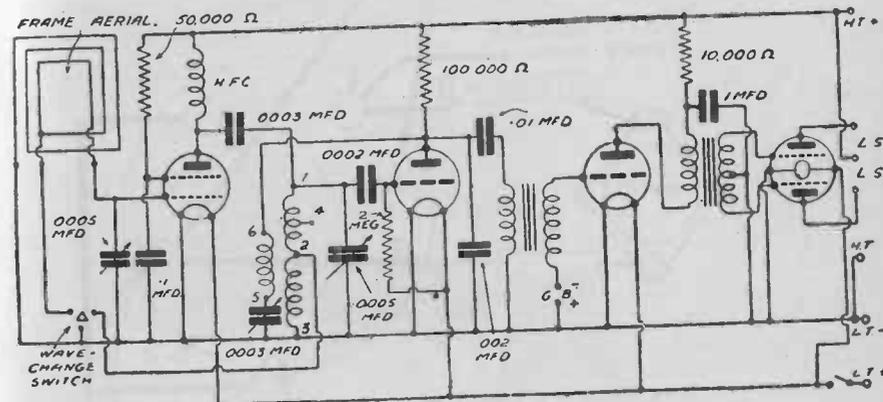


FIG. 72.—Circuit No. 31 for Lightweight Portable Battery Four-valve.

the lower edge, and so continue to the slot where you commenced. Carry the wire through this slot again, and make a further turn, repeating the process so that there are three turns in the first slot. Pass to the second slot, and wind three turns in this, after which two turns only are wound in each remaining slot until eight slots have been used. There now remains the two wide slots. The end of the 24-gauge wire must be cut, and it should be soldered, together with the beginning of the 34-gauge wire to the upper terminal of the 3-point switch. The long-wave winding consists of 23 turns in each slot, and the finish of the winding is joined to the lower terminal of the left-hand tuning condenser. Upon completion of the frame aerial winding the slots may

be sealed with sealing-wax or Chatterton's compound. (See also Figs 74 to 78.)

Normally the receiver should be perfectly stable in operation, but it was originally found that due to the compact form taken by the receiver a few constructors experienced instability. This was due to the fact that they had run many of the wires too close together, and thus the first step to take if this trouble is experienced is to space out the wiring as much as possible. Initially, no screening of leads should be introduced, but if it is found impossible to obtain stable working the lead from the anode of the S.G. valve


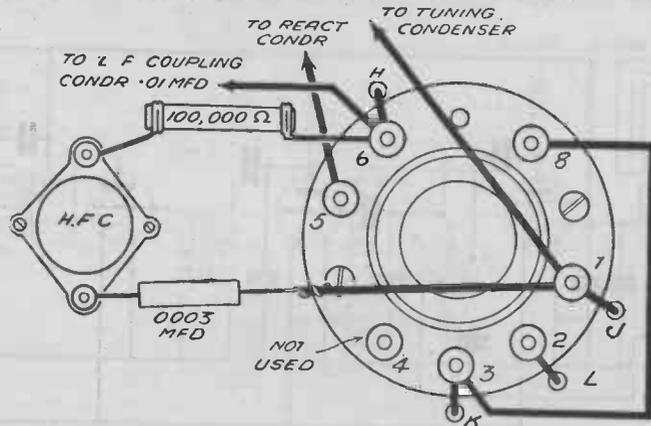


FIG. 73.—Connections for the Bulgin coil, Type C22, which is used in Circuit No. 31.

may be passed through a length of ordinary screened sleeving and the sleeving connected by means of a short length of wire to the nearest earth terminal. The leads to the reaction condenser may also be screened in a similar manner, whilst in a very severe case of instability the two leads to the loud-speaker may also be similarly screened. It must be emphasised, however, that such extreme screening should not be necessary unless the wiring is very badly carried out or some other difficulty arises. The voltages applied to the various parts will occasion no difficulty. The H.T. positive lead is inserted into the maximum voltage socket on the H.T. battery and the two L.T. leads are connected to the appropriate terminals on the accumulator. The Grid Bias positive lead

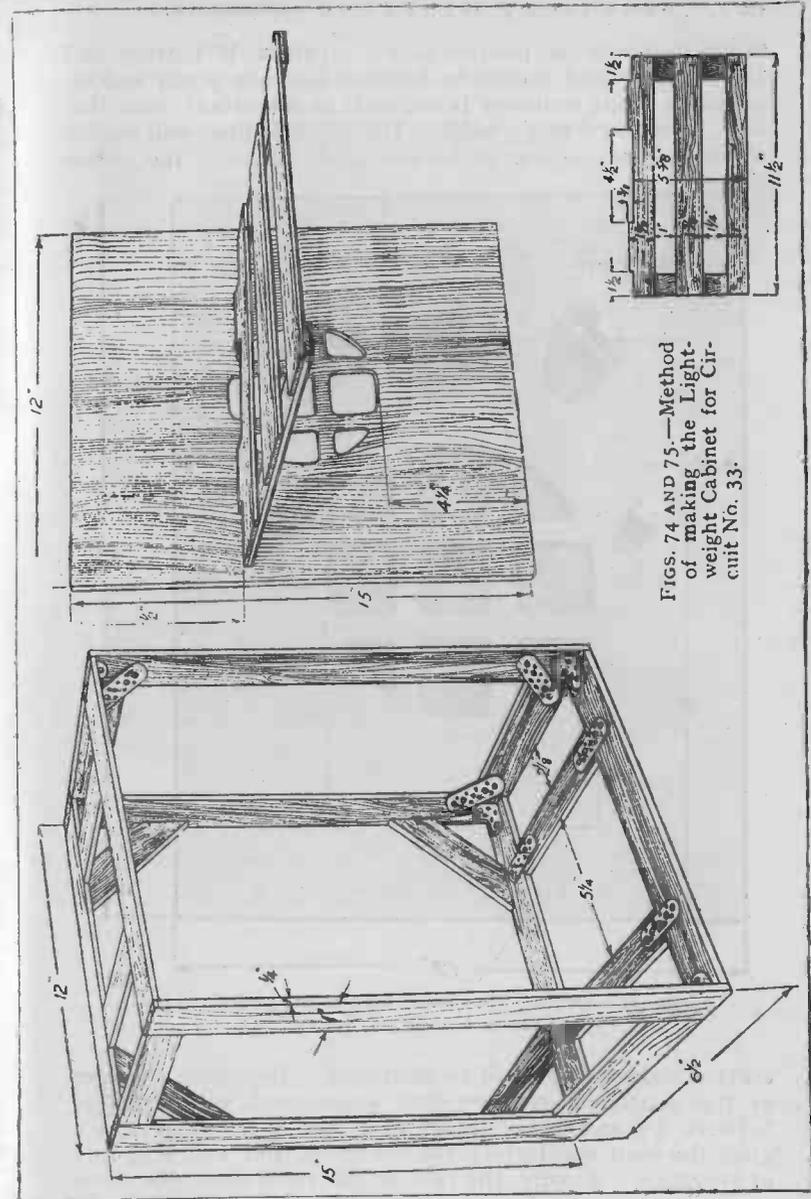

FIGS. 74 AND 75.—Method of making the Light-weight Cabinet for Circuit No. 33.

is inserted into the positive socket on the G.B. battery and the negative lead should be inserted into the 9-volt socket, although where economy is not such an important item, this may be reduced to 7.5 volts. The latter voltage will enable slightly more volume to be obtained, although the anode

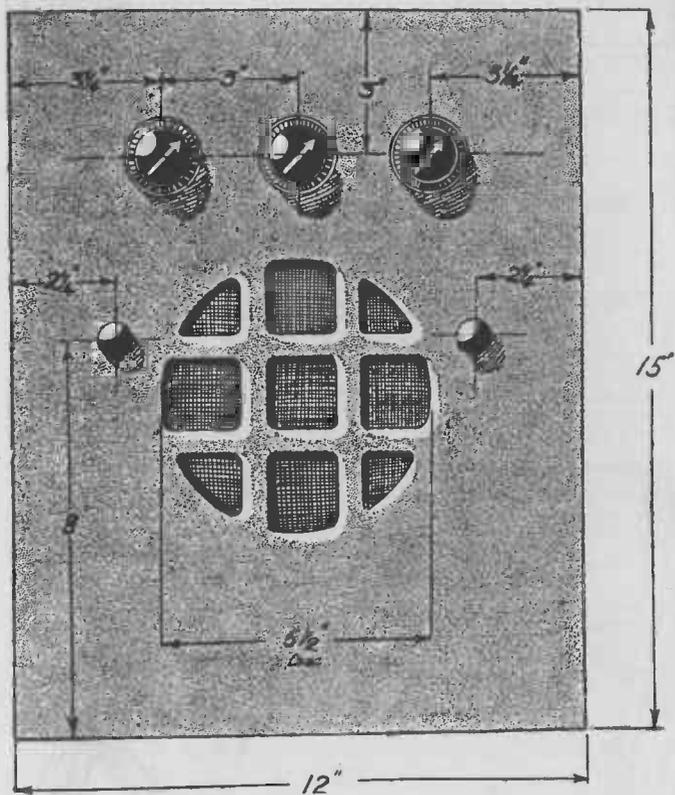


FIG. 76.—Drilling dimensions for the swinging front of Cabinet for Circuit No. 31.

current consumption will be increased. Therefore, the user of this particular receiver may experiment with voltages between 4.5 and 9 volts in order to find the voltage which gives the most satisfactory volume compatible with economy of operation. Finally, the two outside controls on the panel

front are for tuning and must be kept more or less in step, the centre control operating the reaction condenser. Do not

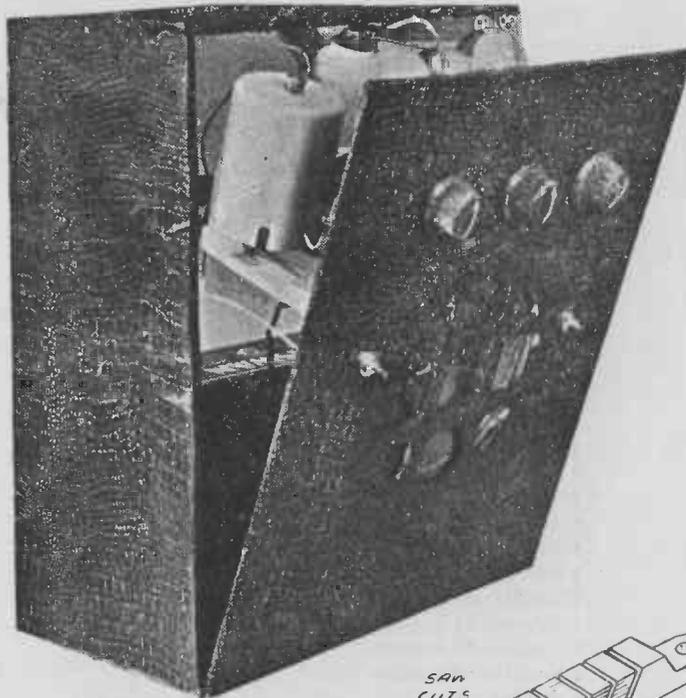


FIG. 77.—Shows the finished Receiver, with the fall front

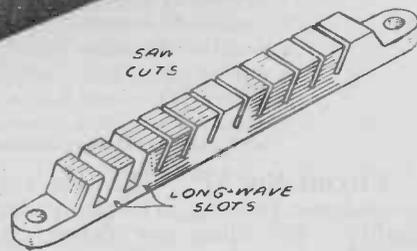


FIG. 78.—Spacers for the Frame Aerial of Circuit No. 31 may be constructed as shown here from strip ebonite.

forget that a portable with a self-contained frame aerial of this type must be orientated so that the directional properties of the frame are utilised. Maximum volume is obtained when the frame is in a line with the station being received.

(BLUEPRINT NO. P.W.12)

LIST OF COMPONENTS FOR CIRCUIT NO. 31

- 1 bakelite condenser, .0005 mfd.
- 1 .0003 condenser.
- 1 H.F. choke.
- 1 Dual Range coil.
- 1 10,000-ohm. wire-end resistor.
- 1 50,000-ohm. wire-end resistor.
- 1 100,000-ohm. wire-end resistor.
- 3 4-pin chassis type valveholder.
- 1 7-pin chassis type valveholder.
- 1 on-off switch.
- 1 Class B. driver transformer.
- 1 2-megohm grid leak with wire ends.
- 1 .01 mfd. fixed condenser.
- 1 .002 mfd. fixed condenser.
- 1 .001 mfd. fixed condenser.
- 1 .002 mfd. fixed condenser.
- 1 .1 mfd. fixed condenser.
- 1 .1 mfd. fixed condenser.
- 1 220 S.G. valve (metallised).
- 1 210 H.F. valve (metallised).
- 1 215 P. valve.
- 1 240 B. valve.
- 1 loud-speaker, Class B.
- Quantity 24 D.C.C. and 34 D.S.C. wire for aerial.
- 1 120-volt H.T. battery.
- 1 9-volt G.B. battery.
- 1 2-volt accumulator.
- 4 wander plugs, H.T.—, H.T.—, G.B.— and G.B.—
- 2 spades, L.T.— and L.T.—.
- Connecting wire, flex, screws, wood for case, leatherette, carrying handle and hinges.

Circuit No. 32*.—This (Fig. 79) is an ambitious 4-valve set designed to bring in as many stations as possible at good quality. The values are critical, and no attempt should be made to alter them. The use of variable- μ H.F. valves is not recommended in this particular instance, but the addition of a Class B output stage could be carried out. The best arrangement of the tuning circuits is carried out by using a two-gang condenser to tune the first two circuits, and a single condenser for the remaining (detector) circuit. A good moving coil loud-speaker is worth while with this set, and the selectivity is regulated by reducing the efficiency

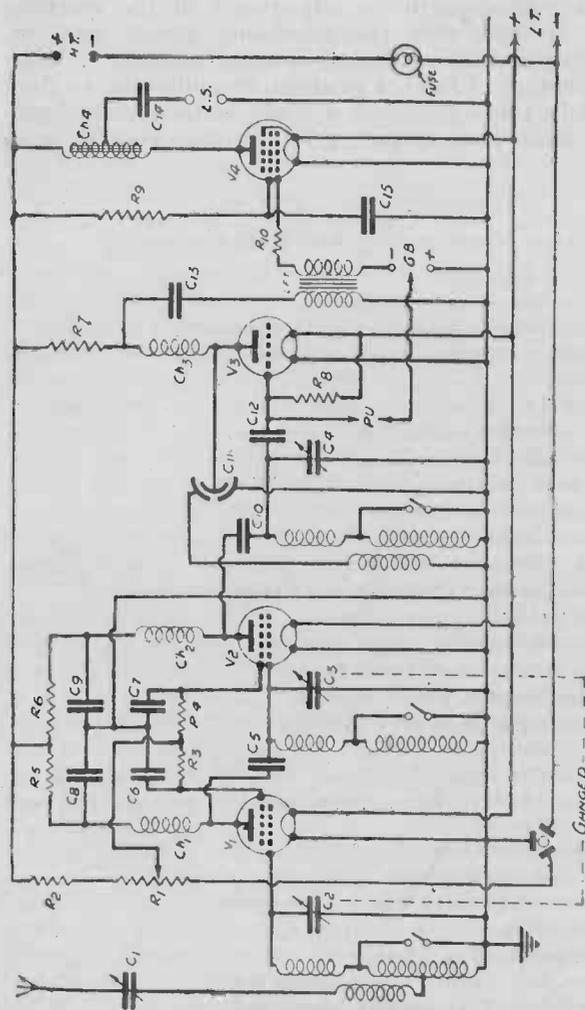


Fig. 79.—Diagram of Circuit No. 32.

C1, C5, C10—.0003 mfd. C2, C3, C4—.0005 mfd. C6, C7, C8, C9—.1 mfd. C11—.0003 Differential. C12—.0002 mfd. C13, C14, C15—.1 mfd. R1—50,000 ohms. Potentiometer. R2, R7—30,000 ohms. R3, R4, R5, R6—1,000 ohms. R8—2 megohms. R9—500 ohms. R10—100,000 ohms. Ch1—Screened S.G. Choke. Ch2—Unscreened S.G. Choke. Ch3—Screened Standard H.F. Choke. V1, V2—Metallised 220 S.C. (Cossor). V3—Metallised 210 H.F. V4—220PT.

of the H.F. valves (by means of the potentiometer R1), and increasing signal strength by adjustment of the reaction condenser. In this way the maximum punch may be obtained when conditions do not demand selectivity. The total consumption of this set is about 20 milliamps, so that care should be taken to obtain a really suitable mains unit when it is desired to operate this from the electric light mains.

(BLUEPRINT NO. P.W.II)

LIST OF COMPONENTS FOR CIRCUIT NO. 32

- 1 3-gang coil assembly.
- 1 2-gang condenser with disc drive.
- 1 .0005-mfd. single condenser with disc drive.
- 1 .0003-mfd. compression type condenser.
- 2 S.G. chokes.
- 1 screened H.F. choke.
- 1 L.F. transformer, ratio 3 to 1.
- 1 pentode output choke.
- 3 1-mfd. fixed condensers.
- 2 .0003-mfd. fixed condensers.
- 1 .0002-mfd. fixed condenser.
- 2 .1 + .1 C.-mfd. fixed condensers.
- 4 chassis-mounting valve-holders, 3 4-pin and 1 5-pin.
- 4 1000-ohm resistors, 1-watt type.
- 2 30,000-ohm resistors, 1-watt type.
- 1 100,000-ohm resistor, 1-watt type.
- 1 5000-ohm resistor, 1-watt type.
- 1 2-megohm grid leak with wire ends.
- 3 terminal blocks.
- 1 4-way battery cord.
- 6 terminals, marked aerial, earth, pick-up, pick-up, L.S. and L.S. (Type B).
- 1 fuse-holder, with fuse.
- 1 50,000-ohm potentiometer.
- 1 .0003-mfd. differential reaction condenser.
- 1 3-point switch.
- 1 ebonite panel, 16 in. x 8 in.
- 3 wander plugs, G.B. +, G.B. 1, and G.B. 2.
- 2 Cossor valves, Type 220 S.G. (metallised).
- 1 Cossor valve, Type 210 H.F. (metallised).
- 1 Cossor valve, Type 220 PT.
- 2 coils of Glazite connecting wire.
- Sundry screws, soldering tags, etc.

Circuit No. 33.—This is a four-valve receiver (Fig. 80) utilising a ganged iron-core tuning coil unit tuned by a 2-ganged condenser. The first valve is of the standard variable- μ H.F. pentode type, and an ordinary triode is used as a leaky grid detector. This feeds an L.F. valve which in turn is coupled to a small power valve, and the coupling employed in the L.F. stages is mixed—one stage using a standard transformer, and the other stage a special component consisting of a combination of resistance-capacity and L.F. transformer. The output from a receiver of this type is large enough for all normal entertainment purposes, and a large number of stations can be received owing to the efficient H.F. stage.

This receiver is ideal for the beginner as all of the components are mounted on a flat baseboard instead of the more usual chassis, and this makes it easier to build and wire the receiver, and at the same time facilitates testing. The baseboard is not covered with foil or otherwise prepared, and an ordinary sheet of thick ply-wood may be used for it. It will be noted that an earth return point is made use of by connecting to the screw used to hold down the 2-gang coil unit. To simplify tuning the condenser should be of a type having a small trimmer mounted on it, operated by means of a knob concentric with the main tuning knob. This enables tuning to be compensated and any slight inaccuracies in the tuning circuit may thus be overcome and at the same time slight mistuning which arises when reaction is employed is also balanced out. The volume control which is specified should be of the type having a switch mounted on it, so that the number of controls are reduced to a minimum. It will be noticed that the grid bias circuit is completed through this switch and thus when the set is switched off the grid bias circuit is also broken. This point is of great importance as if the grid bias circuit is not open when the set is not in use the grid bias battery will discharge itself through the potentiometer. Certain types of volume control of this kind have four points on the switch and two of these should be linked together to act as a single point—the makers usually supply the details for making this connection.

The components may be mounted on brackets screwed to the baseboard, or alternatively may be mounted direct on the cabinet front, and wired direct to the circuit, or preferably a wooden or ebonite panel may be screwed to the front of the baseboard and the components mounted on this.

- 1 ·003-mfd. reaction condenser.
- 3 2-mfd. fixed condensers.
- 1 ·0002-mfd. condenser.
- 1 ·0001-mfd. condenser.
- 1 ·0005-mfd. condenser.
- 1 standard screened H.F. choke.
- 1 H.F. choke.
- 1 L.F. choke.
- 1 3-1 L.F. transformer.
- 1 parallel-fed transformer.
- 1 1,000 ohm., 1-watt resistor.
- 1 10,000-ohm. 1-watt resistor.
- 1 2-megohm grid leak.
- 1 20,000-ohm. volume control with 3-point switch.
- 4 4-pin valveholders baseboard type.
- 1 500,000-ohm. volume control.
- 1 100 m/A. microfuse and holder.
- 3 terminal mounts.
- 6 terminals, A. E. Ls-, Ls+, P.U., and P.U.
- 1 Five-way battery cord.
- 5 wander plugs, G.B.-, G.B.+, G.B.1, G.B.2, G.B.3.
- 2 coils connecting wire.
- 1 120-volt H.T. battery.
- 1 9-volt G.B. battery.
- 1 2-volt L.T. accumulator.
- 1 loud-speaker.
- 4 valves: variable-mu, pentode, 1 general purpose valve, 1 small power valve, and 1 super-power valve.

Circuit No. 34.—This circuit (Fig. 82) is a very popular and satisfactory three-valve superhet giving maximum selectivity, great range of reception, and employing a Westtector as a second detector in place of a valve. This gives economy of operation and enables the receiver to be operated from a small L.T. and H.T. battery. A standard pentagrid frequency changing valve is used and this together with the I.F. valve is of the variable-mu type and enables the volume to be controlled by means of a potentiometer mounted on the panel. A pentode is employed in the output stage and is fed by means of an L.F. transformer connected as a choke giving increased ratio. Unfortunately, owing to the fact that there is only one L.F. stage it is not practical to use their receiver for gramophone record amplification with a pick-up.

The input circuit consists of a pair of band-pass coils and this gives high selectivity and prevents trouble from second channel interference, and these two coils are ganged with a third which acts as the oscillator coil. It is essential when purchasing the three-gang condenser to ask for a superhet type component designed for an intermediate

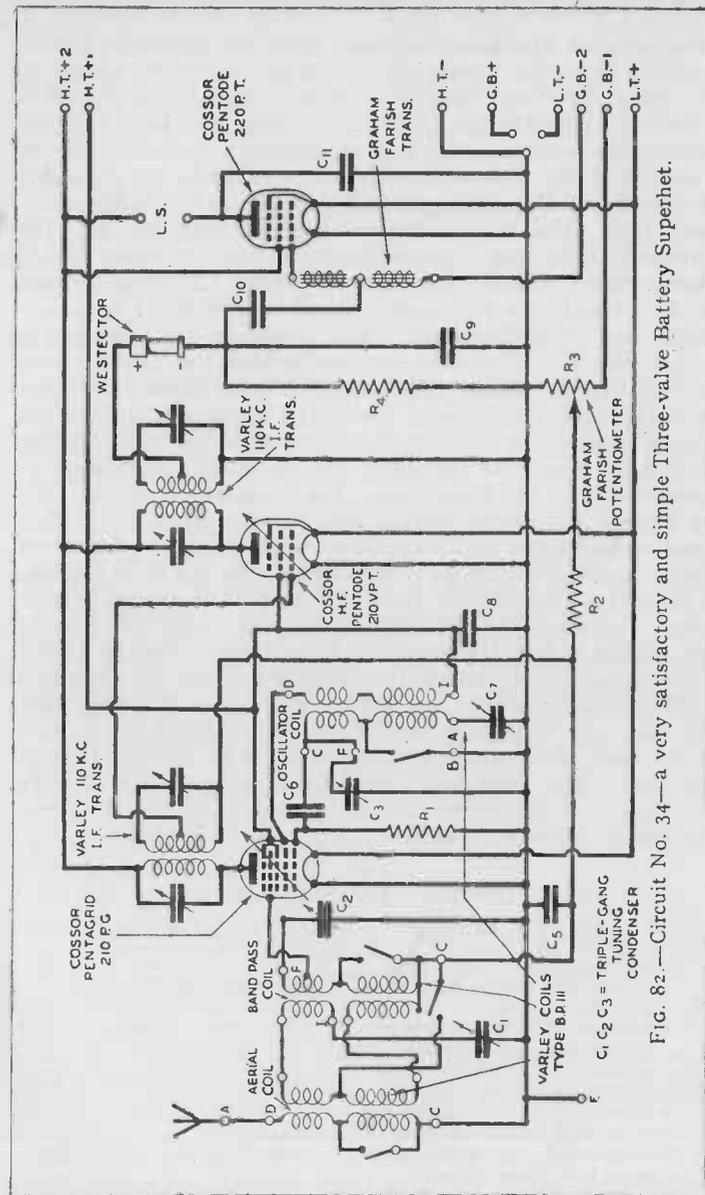


Fig. 82.—Circuit No. 34—a very satisfactory and simple Three-valve Battery Superhet.

frequency of 110 kilocycles and with the oscillator section furthest from the panel. If this is not done the wiring to the gang condenser will be inefficient or if the blueprint is followed explicitly the oscillator section will be connected across the wrong coil. Before maximum results can be obtained from a superhet the circuits must be correctly trimmed, and this is the greatest difficulty in modern receiver operation. The most effective way of carrying out the trimming is to use a properly calibrated oscillator, but if this is not available you should obtain I.F. transformers ready adjusted by the makers when they will not require a great deal of readjustment. The procedure for trimming is as follows: First turn the hexagonal nuts on the I.F. trimmers so that they are nearly tight, in a clockwise direction. Next turn the concentric screws inside the hexagonal nuts in an anti-clockwise direction so that they also are nearly tight. This will bring the primary and secondary windings to approximately 110 kilocycles. The trimmer C₃ should then be turned to approximately half a turn from the full-in position (clockwise rotation), after which C₁ and C₂ trimmers are turned to provide maximum volume on the local station. A distant station should then be located and a final adjustment of the various trimmers made. It should be remembered that unless the correct I.F. is located on the transformers, and the correct frequency-separation is obtained in the oscillator stage, the tuning will not hold throughout the dial, and thus good results will be obtained at one end of the dial, and perhaps no signals at all at another part of the dial. The long-wave padding condenser, C₇ is only adjusted on long waves, and no alteration of the trimmers already mentioned should be carried out on long waves.

(BLUEPRINT NO. P.W.40)

LIST OF COMPONENTS FOR CIRCUIT NO. 34

- 1 set of 3-gang superhet coils.
- 1 3-gang superhet midget variable condenser, and disc drive.
- 2 I.F. transformers.
- 1 .002-mfd. pre-set condenser (C₇).
- 1 50,000-ohm. potentiometer (R₃).
- 1 1-mfd. fixed condenser (C₈).
- 2 .5-mfd. fixed condensers (C₅ and C₁₀).
- 1 .01-mfd. tubular condenser (C₁₁).
- 2 .0001-mfd. fixed condensers (C₆ and C₉).
- 3-ohm. resistances, 150,000 (R₁), 100,000 (R₄), 30,000 (R₂) ohms.
- 1 max. L.F. transformer.

- 1 potentiometer bracket.
- 1 3-point on-off switch.
- 1 7-pin sub-baseboard valveholder.
- 1 5-pin sub-baseboard valveholder.
- 1 4-pin sub-baseboard valveholder.
- 1 Westector.
- 3 wander plugs (H.T. +1, H.T. +2, H.T. -).
- 2 spade terminals (L.T. +, L.T. -).
- 3 G.B. plugs (G.B. +, G.B. -1, G.B. -2).
- 2 terminal strips (A.E. and L.S.).
- 1 Metaplex chassis 11 in. x 10 in., with 2½ in. runners.
- 3 valves: 1 pentagrid, 1 variable-mu H.F. pentode, and 1 economy pentode.
- 1 loud-speaker.
- 1 120-volt H.T. battery.
- 1 G.B. 16½-volt battery.
- 1 L.T. 2-volt accumulator.

Circuit No. 35.—This is a four-valve superhet, the first valve fulfilling two separate functions, thus making the set equivalent to a five-valve receiver. The aerial circuit is a simple H.F. transformer, a simple aperiodic winding serving for both medium and long waves. The circuit is shown in Fig. 83. The component which is used is provided with a tapping point provided for wave-change purposes, but it has been found necessary to use this in the present circuit. The secondary winding is fairly closely coupled which is brought out to a three-point switch mounted beneath the chassis whilst the entire coil is enclosed in a metal screening can. The signal is tuned by the first section of a ganged condenser in the ordinary way, and is applied direct to the grid and filament of the frequency-changer valve. Bias is applied direct to the grid through the volume control potentiometer and resistance R₂, a condenser C₃ being interposed in the grid lead to prevent short circuiting of the bias voltage.

Arranged in the same valve are two further grids, to one of which is joined a tuned circuit coupled to a coil which is included between the other grid and the H.T. battery. This is, of course, a standard reaction arrangement, and the grid in this case functions as an anode. As a result of this arrangement, oscillation takes place and the moving vanes of that section of the gang condenser marked C₂ are cut to a certain shape which causes the tuning in this circuit to be 465 kilocycles above the frequency to which the first coil is tuned. An anode is arranged around the grids which have already been referred to (in addition to a screening grid which functions in the normal manner), and thus a mixed

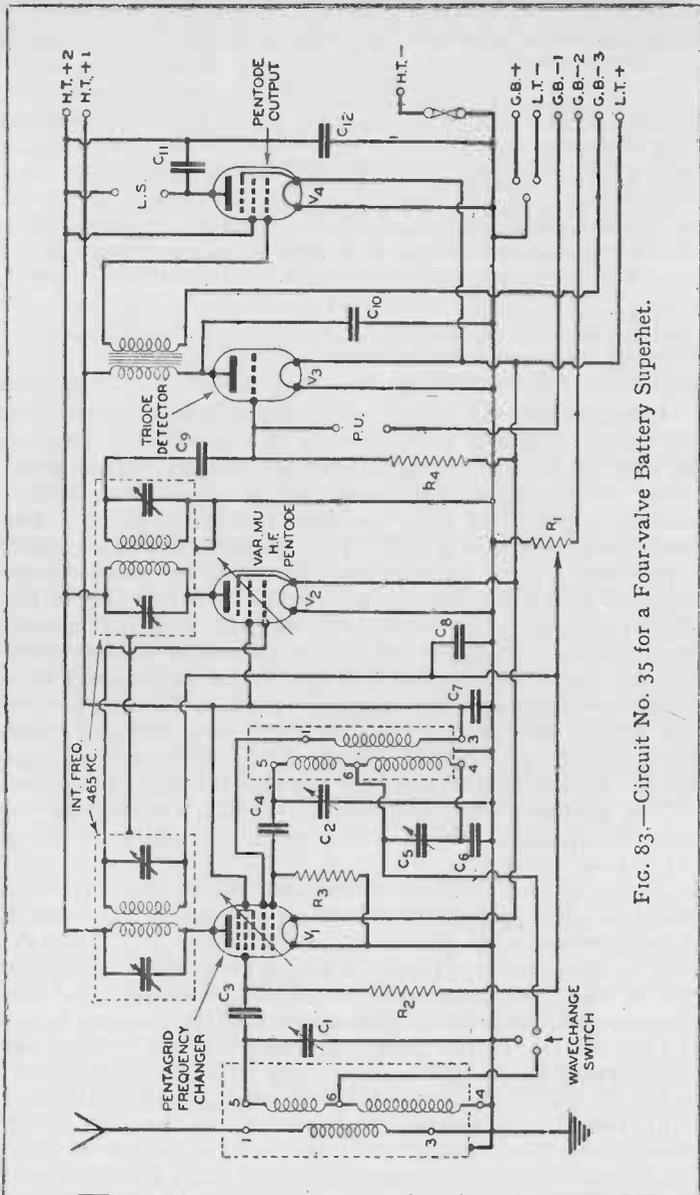


FIG. 83.—Circuit No. 35 for a Four-valve Battery Superhet.

stream of electrons is found passing from the filament to anode. This mixture consists of the original signal tuned by condenser C1 to which are added the oscillations produced in the oscillator coil or section, and so at the anode appears the difference, as a beat note upon which are superimposed the fluctuations of the original signal. The rectification of the original signal impulses have not been referred to, although, in addition to the above mixing, the complication of partial rectification takes place. To enable the condenser C2 to tune the coil over both medium and long-waves, it is necessary to add some additional capacity to the total circuit, and to increase the general "stray" capacity across the coil a pre-set condenser C5 is included, whilst condenser C6 is added in series with the coil. These two condensers are, of course, short-circuited when medium-wave reception is desired, and the same switch as is used for the aerial is employed for this purpose. In the anode circuit of this first valve a transformer is inserted, and this is designed to be tuned to a frequency of 465 kilocycles—small pre-set condensers being included across both primary and secondary to balance out stray capacities. Thus, when each of these windings is correctly adjusted we shall find the original signal impulses present in primary and secondary, but being borne at a frequency of 465 kilocycles instead of the frequency originally received in the aerial circuit. Amplification is next carried out by the variable-mu H.F. pentode in the usual manner, variable bias being applied direct to the grid through the secondary winding of the I.F. transformer, and a similar component is included in the anode circuit of this valve to transfer the signal to the next valve, which is known as the second detector. This is arranged to function on the usual grid-leak rectifier principle, and thus in the anode circuit of this valve we find our signal in the form of an audio or low-frequency impulse which may be employed to operate a loud-speaker or head-phones, or be further amplified at low frequency.

It is obvious from the previous description that great selectivity will be obtained with a circuit of this nature, as apart from the number of tuned circuits employed (there are actually six of these), the production of the beat note in the frequency changing stage adds still further to the selectivity. and thus it becomes possible to obtain such a high degree of selectivity that the musical side-band of the transmitted signal may be cut. Obviously, this is not desirable in the

interests of quality reception, and therefore the general arrangement of the circuit is such that the selectivity reaches just that stage which ensures that a separation equivalent to the band of frequencies which are broadcast is obtained, and provided that a signal is not actually heterodyned due to another station working within the allowed frequency band, it is possible to separate every broadcasting station from its neighbour.

To remove such mush and noises accompanying some of the foreign stations which work rather close in frequency, a simple tone-control device has been incorporated in the anode circuit of the output valve, and this acts very effectively in removing the background noises without spoiling quality. Further tone control is not desirable, if good quality signals are desired, although if it is found that in certain parts of the country a station is required for regular reception but is spoiled by a heterodyne, a high-note cut-off may be introduced. It can only result in a spoiling of the musical quality and I do not recommend such a drastic step.

(BLUEPRINT NO. P.W.58)

LIST OF COMPONENTS FOR CIRCUIT NO. 35

- 1 screened aerial transformer.
- 1 screened oscillator coil.
- 1 2-gang variable condenser with V.P. horizontal drive.
- 1 compression condenser (.0001 mfd.) (variable) (C5).
- 2 .0001-mfd. fixed condensers (C4 and C9).
- 1 .0004-mfd. fixed condensers (C6).
- 1 .0005-mfd. fixed condensers (C3).
- 1 .001-mfd. fixed condensers (C10).
- 1 .003-mfd. fixed condensers (C11).
- 1 .01-mfd. fixed condensers (C8).
- 2 .5-mfd. fixed condensers (C7 and C12).
- 1 100,000-ohm. non-inductive 1-watt fixed resistance (R3).
- 1 .5-megohm non-inductive, 1-watt fixed resistance (R2).
- 1 1-megohm non-inductive 1-watt fixed resistance (R4).
- 1 50,000-ohm. with 3-point switch variable resistance (R1).
- 2 I.F. transformers.
- 1 L.F. transformer (ratio 1-3).
- 1 3-point shorting switch.
- 2 4-pin valveholders (with terminals).
- 1 5-pin valveholder (with terminals).
- 1 7-pin valveholder (with terminals).
- 1 terminal strip marked A.E.
- 1 terminal strip marked P.U. and L.S.
- 7 wander plugs, marked G.B.-1, G.B.-2, G.B.-3, G.B.+ , H.T.+1, H.T.+2, H.T.-.
- 2 spade connectors marked L.T.- and L.T.-.

- 1 100 m/A. and holder.
- 1 pentagrid valve.
- 1 variable- μ H.F. pentode valve.
- 1 triode valve.
- 1 L.F. pentode valve.
- 1 metaplex chassis measuring 10 in. x 8 in. with 3 in. runners
- 2 2½ in. component brackets.
- 1 loud-speaker.
- 1 120-volt H.T. battery.
- 1 16.5-volt G.B. battery.
- 1 2-volt L.T. accumulator.
- Connecting wire, screws, etc.

Circuit No. 36.—This circuit (Fig. 84) is the main version of the battery all-wave three shown in Circuit No. 23. The circuit arrangement is the H.F. detector, L.F. type, using pentode valves in the H.F. and L.F. stages and a triode detector. The aerial circuit is tuned on the medium and long-wave bands, and untuned when switched to the short-wave bands. The primary winding of the medium long-wave-coil acts as an effective H.F. choke when the switch is in the short-wave position. The switch is incorporated in the coil unit, and can be obtained completely wired by the manufacturers. The H.F. valve is of the variable- μ pentode type, having 7-pins, and volume is controlled by means of a 5000 ohms potentiometer connected in series with its cathode resistance. The coupling between the H.F. and detector valves is of the tuned grid type, the H.F. choke being of a modern screened type. It will be noted that the tuning arrangement in this stage is of a novel type. The wavechange switch connects two .00025 mfd. sections of the gang condenser in parallel on the medium and long wavebands thus forming a capacity of .0005 mfd. On the short-wavebands one of these .00025 mfd. sections is disconnected leaving a tuning condenser of .00025 mfd. Resistance capacity coupling is used between the detector and output valve to avoid the possibility of mains hum which might otherwise be caused by interaction between the L.F. amplifier and the mains unit. Resistance coupling also ensures good quality reproduction, and by using a high efficiency pentode in the output stage adequate volume is obtained. The rectifier used in the mains unit is of the Westinghouse metal type. This was chosen owing to its reliability and consequent popularity amongst home-constructors. Style H.T.9 may be used, but style H.T.8 may be employed if one of these is on hand. The H.T.8 has now been discontinued, style H.T.9 taking its place. An

or less standard arrangement there are one or two points of interest in this circuit which require explanation. Firstly, a single tuned circuit is employed for the first stage and also for the detector stage, but this should provide adequate selectivity for all normal requirements. Where excessive interference is experienced, such as when the receiver is

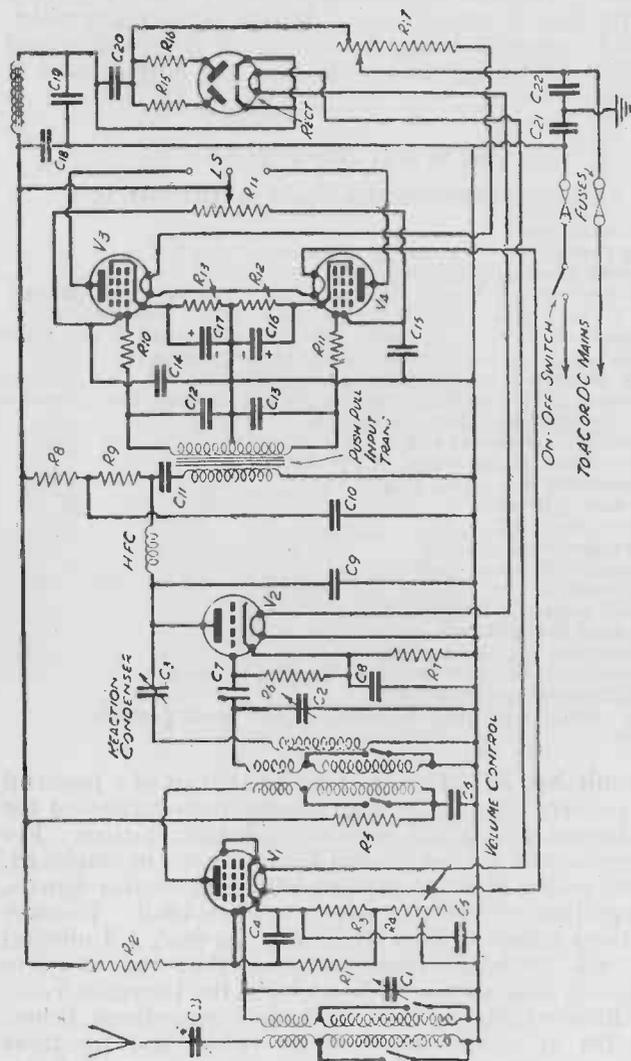


FIG. 85.—Circuit No. 37 for a powerful quality Mains Receiver.

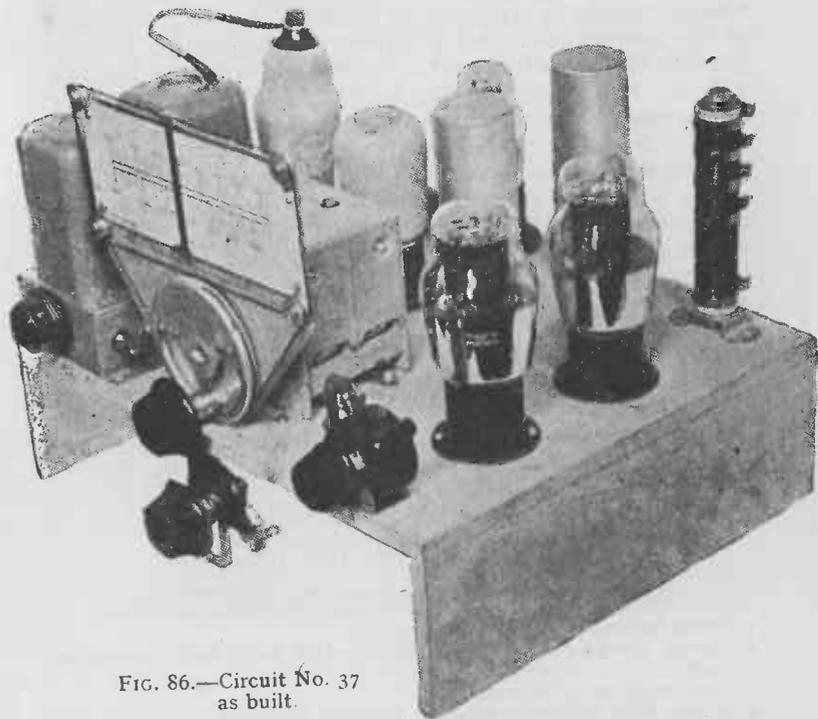


FIG. 86.—Circuit No. 37 as built.

required for use close to a main B.B.C. station, a band-pass tuner could, of course, be employed in the aerial circuit and this would entail the use of a three-gang condenser in place of the two-gang component now specified. The detector stage is quite normal, and it will be noted that a biasing resistor and condenser are included in the cathode circuit of the detector stage.

A pick-up may therefore be used, when required, by connecting it between the grid of this valve and the earth

line (chassis). On the output side several devices have been included in the interests of stability and quality. Firstly, the transformer is parallel-fed to remove the current from the primary and to give an improved low-note response. Secondly, two fixed condensers are connected across the secondary (C12 and C13) and this assists in improving the quality and range of the lower musical frequencies. To ensure stability a resistance is included in series with each of the output grids and a further device for this purpose consists of the inclusion of a potentiometer across the two valves. This potentiometer supplies the voltages to the two screening grids and it will be seen that the arm of the control is joined to H.T. positive. With the aid of this control it is possible to effect a balance between the two valves which will in many cases have the effect not only of improving stability but also of improving quality, especially where the two output valves are not well matched. If, however, when you build this receiver, you find that the adjustment of this control does not have any noticeable effect, it will simply indicate that the two output valves are fairly well matched and it should then be adjusted to a mid-way position and there left. The remaining part of the circuit, supplying the H.T. is orthodox, a full-wave rectifying valve being connected on the half-wave principle and adequate smoothing devices being included to remove possibility of mains hum.

(BLUEPRINT NO. P.W.47)

LIST OF COMPONENTS FOR CIRCUIT NO. 37

- 1 2-gang set coils.
- 1 2-gang .0005-mfd. midget condenser with drive and wavelength scale.
- 1 .00015-mfd. reaction condenser.
- 4 .5-mfd. fixed tubular condensers (C6, C11, C14, C15).
- 2 .1-mfd. fixed tubular condensers (C4 and C5).
- 3 .05-mfd. fixed tubular condensers (C20, C21, C22).
- 1 .0001-mfd. fixed tubular condensers (C7).
- 3 .0002-mfd. fixed tubular condensers (C9, C12, C13).
- 1 2-mfd. fixed condenser (C10).
- 3 25-mfd. electrolytic condensers (C8, C16, C17).
- 2 8-mfd. electrolytic condensers (C18 and C19).
- 1 .0003-mfd. pre-set condenser (C23).
- 14 fixed resistances, 30,000 (R2), 25,000 (R1), 2000 (R5), 500,000 (R6), 20,000 (R8), 30,000 (R9), 10,000 (R7), 250 (R12), 250 (R13), 50 (R15), 50 (R16), 10,000 (R10), 10,000 (R11), 200 (R3).
- 2 potentiometers, 2000 ohms. (R4), and 5000 ohms. (R14).

- 1 mains dropping resistance (R17).
- 1 snap H.F. choke.
- 1 L.F. choke H.T.11.
- 1 in-put push-pull transformer.
- 3 potentiometer brackets.
- 1 mains on-off switch.
- 5-valveholders 4 7-pin, 1 5-pin.
- 2 5-amp. mains fuses.
- 1 mains lead and plug.
- 5 valves: H.F. pen, detector, 2 pentodes, and 1 rectifier.
- 1 loud-speaker.
- 1 Metaplex chassis.
- A.E. strip and plugs.
- 1 cabinet.

Circuit No. 38.—This amplifier is called "Universal," as it is so wired that it may be connected to any existing receiver,

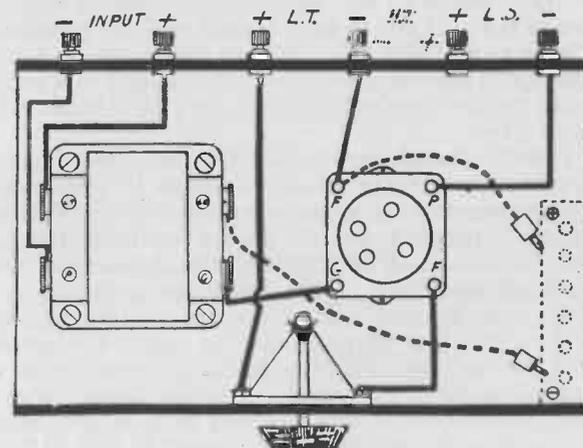


FIG. 87.—A One-valve Amplifier.

whether crystal or valve. A glance at the wiring diagram (Fig. 87) will show that no terminal has been provided for the H.T. negative lead, and also that a grid bias battery is supplied for the amplifier. These two facts are easily explained, however. In any valve receiver the H.T.— wire is connected to one or other of the L.T. terminals, and, therefore, when the two L.T. terminals on this amplifier are joined to the corresponding terminals on the receiver with which the amplifier is used, the H.T.— lead is automatically joined in circuit. The existing receiver may employ a grid battery, but in this case there is not the slightest objection to having

to as the valves are worked at their maximum points. There is very little wiring to be carried out, but in view of the high voltages it should be done carefully. The special band-pass tuner may take any form, but it is essential that this type of tuned circuit is used, otherwise there will be difficulty in separating powerful stations in view of the high efficiency of the first valve stage. This receiver lends itself remarkably well to the design of a self-contained receiver, the mains section and loud-speaker occupying a position in the upper half of the cabinet, and the receiver proper taking up a position in the lower section. Special small Consolette cabinets may be obtained suitable for this type of set. It is not desirable to use a gramophone pick-up with this particular circuit.

(BLUEPRINT NO. P.W.18)

LIST OF COMPONENTS FOR CIRCUIT NO. 39

- 1 band-pass filter.
- 1 2-gang condenser, .0005.
- 1 L.F. transformer.
- 1 .0003 reaction condenser.
- 1 standard H.F. choke.
- 1 Varley 300 henry L.F. choke.
- 1 .0001 fixed condenser.
- 1 .001 fixed condenser.
- 2 .01 fixed condensers.
- 3 1-mfd. fixed condensers.
- 1 2-mfd. fixed condenser.
- 2 4-mfd. fixed condensers.
- 2 5-pin valve-holders.
- 1 4-pin valve-holder.
- 1 $\frac{1}{4}$ -megohm 1-watt type resistance.
- 1 12,500-ohm 1-watt type resistance.
- 1 400-ohm 1-watt type resistance.
- 1 2500-ohm 1-watt type resistance.
- 1 30,000-ohm 1-watt type resistance.
- 1 10,000-ohm 1-watt type resistance.
- 1 15,000-ohm 1-watt type resistance.
- 1 Heayberd mains transformer (Model "A.C. Twin")
- 1 Grampian energised speaker, Type E.L

- 1 mains Toggle switch.
- 1 small mains connector.
- 1 terminal strip.
- 2 wander plugs (1 black and 1 red).
- 1 Cossor 442 B.U. rectifying valve.
- 1 Cossor MS-PEN-A (H.F. pentode valve).
- 1 Cossor MP-PEN (pentode output valve).
- 1 coil Glazite, 3 yards red and black flex, screws, bulb for panel light, etc.

Circuit No. 40.—Although only a two-valver, Fig. 89 will prove a really good little receiver for the listener who does not want every station in the world, and who is satisfied with volume sufficient for domestic use, and does not wish to entertain the neighbours. When built as a complete radiogram, it is possible to reproduce gramophone records at quite a respectable volume—comparable with a good acoustic gramophone. The circuit is extremely straightforward, and there are no points of interest or difficulty. A special gramophone cabinet will be required if the use of the gramophone is desired, and the circuit incorporates tone control for the reduction of needle scratch, etc. The valves are biassed automatically, and the special tuning coil which is used will provide adequate selectivity for normal requirements.

(BLUEPRINT NO. P.W.19)

LIST OF COMPONENTS FOR CIRCUIT NO. 40

- 1 polished plywood panel, 10 in. \times 7 in.
- 1 5-ply baseboard, 15 in. \times 14 $\frac{1}{2}$ in.
- 1 .0005-mfd. condenser with disc drive.
- 1 3-point wavechange switch.
- 1 changeover (radiogram) switch.
- 1 20,000-ohm volume control with combined mains switch.
- 2 5-pin valve-holders.
- 1 coil.
- 2 .0001-mfd. fixed condensers.
- 1 .0005-mfd. fixed condenser.
- 1 1-megohm grid leak.

single circuit and is, in fact, essential for receivers which are situated close to a powerful transmitter. A single circuit tuner may be converted to a band-pass tuner by the addition of the unit illustrated in Fig. 91. It will be seen that very few parts are needed, and the conversion should not take long. In order to prevent interaction between the coil in the additional unit and the coil in the receiver it is worth while to build this adaptor in a metal (or metallised) box. Alternatively, the adaptor may be built in a wooden box, and the side nearest the present receiver may be covered with metal foil, and connected to earth to act as a screen. The differential condenser should be adjusted to give the required degree of selectivity, and this condenser must be adjusted in conjunction with the variable in the present receiver.

LIST OF COMPONENTS FOR CIRCUIT NO. 42.

- 1 plywood panel, 8 in. \times 6 in.
- 1 baseboard, 8 in. \times 6 in. \times $\frac{1}{8}$ in.
- 1 terminal mount (Belling-Lee).
- 2 terminals, marked "A" and "E."
- 2 spade terminals.
- 1 dual range tuner.
- 1 .0005-mfd. variable condenser.
- 1 dial pointer.
- 1 .00013-mfd. differential condenser.
- Short length "Glazite" and a foot of twin flex.

Circuit No. 43.—Fig. 92 shows an adaptor for converting an existing broadcast receiver to Class B working. The input terminals are connected to the loud-speaker terminals on the present receiver, and a small power valve employed in the last socket of that receiver. The loud-speaker is then connected to the output terminals of this adaptor, and the receiver then delivers about 2 watts undistorted. No grid bias adjustments have to be made, and therefore the quality is of a very high order and justifies the use of a good moving-coil speaker. The components should be mounted on a small baseboard, and the whole built into a small cabinet with the valve totally enclosed. Input leads and output leads may be employed instead of terminals, and the unit

then becomes a very neat coupling between the present receiver and the loud-speaker.

LIST OF COMPONENTS FOR CIRCUIT NO. 43

- 1 driver transformer.
- 1 Class B output transformer.
- 1 On-Off switch S.38.
- 1 7-pin valve-holder (baseboard type).
- 1 Cossor 240 B. valve.

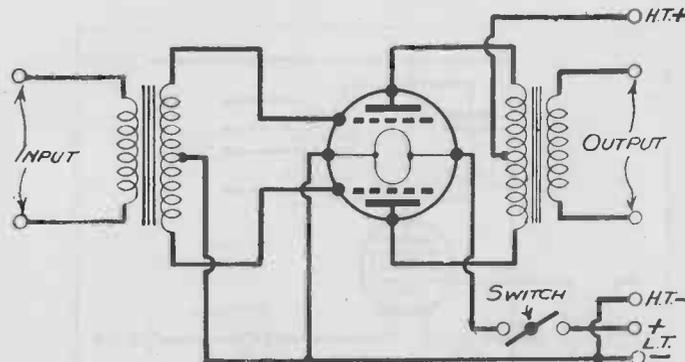


FIG. 92.—Theoretical Circuit of the Class B Unit.

- 4 terminals—Input—, Input +, Output, Output.
- 2 terminal mounts.
- 1 battery cord—H.T. +, H.T. —, L.T. +, L.T.
- 1 baseboard, 9 in. \times 5 in.
- 1 panel, 9 in. \times 5 in.

Circuit No. 44.—This is another amplifier (Fig. 93), for adding to an existing receiver, this time employing a pentode valve. This delivers much greater volume than a triode valve, but has the disadvantage that it will not handle a very great input. Its principal application is, therefore, following a simple detector, or one L.F. receiver. The amplifier is fitted with a tone control which should preferably be mounted on the panel so that the tone may be adjusted to suit the particular musical item which is being received.

The L.F. transformer should preferably be of fairly high ratio, especially when it follows a detector valve.

LIST OF COMPONENTS FOR CIRCUIT NO. 44

- 1 panel, 10 in. × 7 in.
- 1 baseboard, 10 in. × 7 in.
- 1 valve-holder.
- 1 L.F. transformer.
- 1 pentode output transformer.
- 1 2-mfd. fixed condenser.

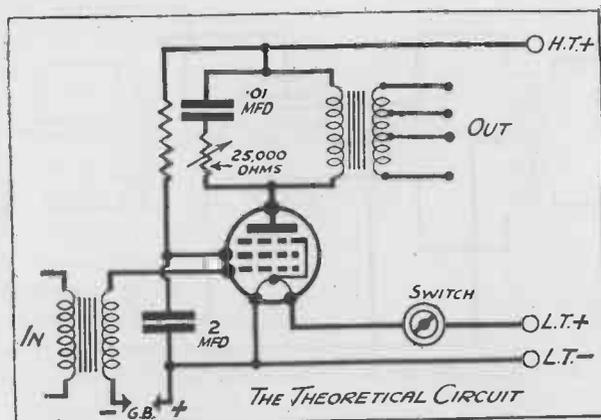


FIG. 93.—The Theoretical Circuit of a Pentode Amplifier Unit.

- 1 .01-mfd. fixed condenser.
- 1 pentode safety decoupling resistance.
- 1 volume control, 25,000 ohms.
- 1 On-and-Off switch.
- 7 terminals—Input, Output, G.B.—, G.B.+, L.T.—, L.T.+, H.T.+.
- 1 strip of ebonite, 10 in. × 1½ in., wire, screws, grid-bias battery, etc.

Circuit No. 45.—The variable-mu valve gives a great increase in range to a receiver of the detector L.F. type, and at the same time enables a very fine variation in volume to be obtained. When situated close to a powerful station

the H.F. valve is overloaded, but the variable-mu valve may be adjusted to suit this condition, by varying the bias applied to the valve. In this way the volume may be controlled from maximum to minimum and no distortion due to overloading takes place. The H.F. unit illustrated in Fig. 94 may be built up for addition to any simple

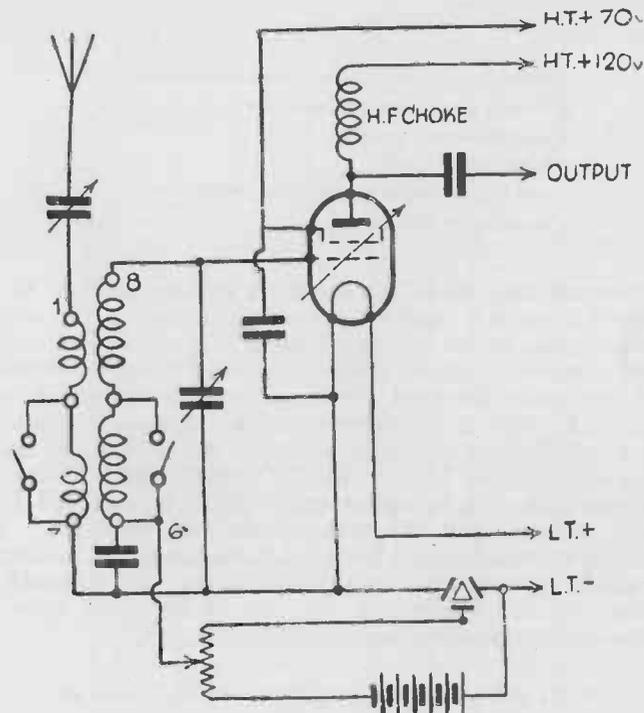


FIG. 94.—Circuit (No. 45) of an H.F. Unit.

set and will enormously improve it, both from the point of view of station-getting and controllability. The coil is rather critical, but the remaining components may be of any suitable type. In order to prevent instability, it is preferable to enclose the unit in a small cabinet of metal, or use a wooden box and line it with foil connected to earth. Of course, great care should be taken to avoid short-circuits.

LIST OF COMPONENTS FOR CIRCUIT NO. 45

- 1 screened coil with switch, Telsen No. 216.
- 1 small friction disc drive.
- 1 wire-wound potentiometer, 50,000 ohms.
 - 1 screened H.F. choke with shielded pigtail.
- 2 1·0-mfd. condensers
- 1 0·0002-mfd. condenser.
- 1 0·0005-mfd. direct drive variable condenser.
- 1 0·0003 (max.) pre-set condenser.
- 1 3-point on-off switch.
- 1 4-pin valve-holder.
- 1 220 V.S.G. valve, Cossor (metallised).
- 1 9-volt grid bias battery.

Circuit No. 46.—This enables a battery receiver to be worked from A.C. mains without alteration to the wiring (4-volt mains valves will be required) (Fig. 95). It provides three separate positive tapings, one of which is variable and especially designed for supplying the screening grid of an H.F. stage or the detector stage. Although only half-wave rectification is employed, the smoothing is quite adequate, and no hum should be experienced. To be on the safe side, the complete unit should be enclosed in a metal cabinet, and the components well insulated. An earthing terminal should be fitted to this case and connected to earth. No shocks can therefore arise. Care should be taken that the condensers, etc., are of the right type, as shown in the undermentioned list of parts.

LIST OF COMPONENTS FOR CIRCUIT NO. 46

- 1 plywood panel, 8 in. × 6 in.
- 1 baseboard, 8 in. × 12 in. × $\frac{3}{8}$ in.
- 1 mains transformer supplying 200 volts at 30 mA. and 4 volts at 4 amps.
- 1 40-henry smoothing choke.
- 1 style H T.7 metal rectifier.
- 2 4-mfd. condensers, for 400-volt working.
- 2 2-mfd. condensers, for 400-volt working.
- 1 baseboard fuse-holder with 60 mA. fuse.

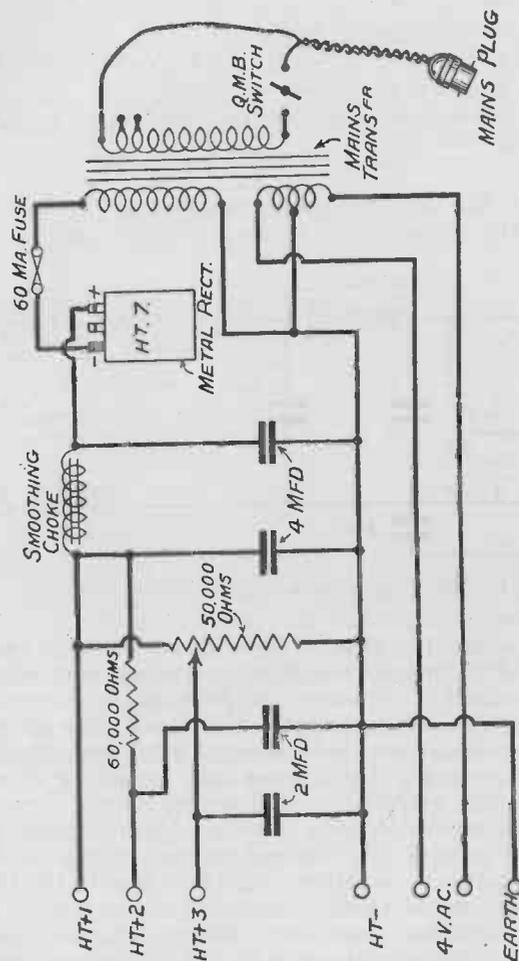


Fig. 95.—The Circuit (No. 46) Diagram of an A.C. Mains Unit.

- 1 60,000-ohm metallised resistance (1 watt).
- 1 50,000-ohm potentiometer.
- 1 Q.M.B. mains switch.
- 3 terminals—2 marked "L.T.A.C." and 1 "Earth."
- 3 terminal insulating washers.
- 4 plugs and sockets, marked H.T.—, H.T.1, H.T.2, and H.T.3.
- 1 mains plug to suit convenient socket.
- 1 coil Glazite, short length Lewcos twin-braided wire, length flex, screws, etc.

Circuit No. 47.—To avoid the expense of continually renewing the high-tension battery a mains unit may be

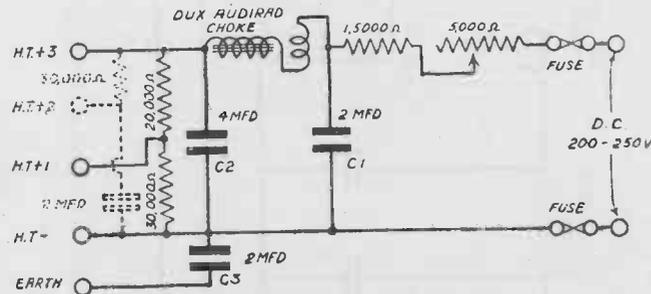


FIG. 96.—The Circuit of a D.C. Mains Unit.

employed where the electric light mains are laid on. In the case of D.C. mains the apparatus is of the very simplest, and the circuit (Fig. 96) shows the parts which are necessary to make up a really neat unit. This should, for safety, be enclosed in a metal box, and the metal fitted with a terminal connected to earth. The utmost care should be exercised to see that the components and wiring do not come into contact with the metal box. The variable resistance should be adjusted to give the required output voltage, and the earth terminal on the receiver should be joined to the H.T.— terminal and *not* to earth. Alternatively, a 2-mfd. fixed condenser should be connected to the earth terminal on the set, and the remaining terminal on the condenser joined to earth. In this way you will reduce the possibility of shocks. A further safeguard consists of including a small condenser in series with the aerial.

LIST OF COMPONENTS FOR CIRCUIT NO. 47

- 1 potentiometer, 5000 ohm.
- 2 1-watt Type resistors, 20,000 and 30,000 ohm.
- 1 2-watt Type resistor, 1,500 ohm.
- 4 plugs and sockets.
- Glazite connecting wire.
- Ebonite panel, $4\frac{1}{2}$ in. \times $3\frac{1}{2}$ in. \times $\frac{1}{4}$ in.
- Baseboard, $8\frac{1}{2}$ in. \times $4\frac{1}{2}$ in. \times $\frac{3}{8}$ in.
- 1 choke (25 henries, 50 mA.).
- 2 4-mfd. condenser, Type 80-81.
- 2 2-mfd. condensers, 750 volt test.

Circuit No. 48.—As all the best gramophone records are electrically recorded, it is only appropriate that the reproduction of sound should also be of an electrical nature.

The Pick-up.—Electrical reproduction is carried out with the help of the gramophone pick-up. In such a pick-up the needle is attached to a small armature which is capable of vibrating between pole pieces of a permanent magnet. Around the armature or the magnet there is a small coil in which electrical impulses are induced owing to the change in the magnetic field caused by the vibrating armature. In this manner each sideways vibration results in an electrical impulse, so that there is a group of such impulses corresponding to each sound. You will realise that the electrical currents generated in the pick-up coil are of a very minute character and have to be amplified. This is done with the help of a low-frequency amplifier such as is described on page 100. The recommended amplifier has two valves, as may be seen from the theoretical diagram shown in Fig. 97. The two wires from the pick-up terminals (the latter are connected to the pick-up coil) are connected across the grid and the filament of the first valve. You will notice that a grid bias is applied to the grid through the pick-up.

The Connections.—The filaments of the two valves are connected in parallel across the L.T. supply, a common filament regulator controlling the voltage across the filaments. The anode of the first valve is connected to one side of the primary of an L.F. transformer, the other side of the primary going to the positive side of the H.T. battery. The secondary

of the transformer is connected to the grid of the second valve on one side, while its other side is given a grid bias in the usual way. The anode of the second valve is connected to the positive side of the H.T. battery through the loud-speaker. You will find that a detector valve in the first stage and a power valve in the second stage will do the trick. Make sure that you use a good quality transformer. A cheap transformer will cause a good deal of distortion. As you will see from the circuit diagram (Fig 97), it is exceedingly simple and can be built up in a couple of hours, including the panel

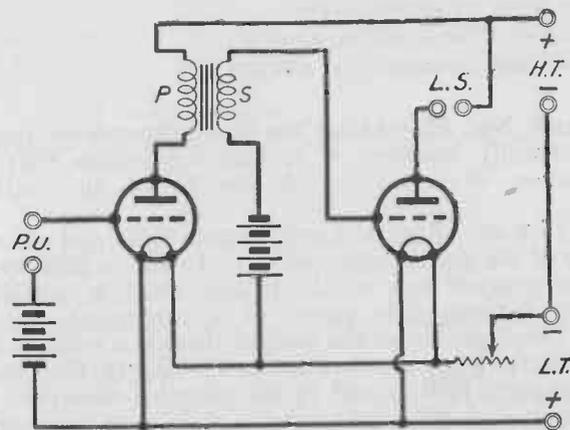


FIG. 97.—Circuit Diagram for a Two-valve Gramophone Amplifier.

drilling and the assembling. Fig. 98 shows how to connect the gramophone amplifier to the set. The following components are required :

LIST OF COMPONENTS FOR CIRCUIT NO. 48

- 1 15-ohm filament regulator.
- 1 detector valve.
- 1 L.F. or power valve.
- 2 9-volt dry grid bias batteries.
- 1 4-volt accumulator.
- 1 150-volt H.T. battery.
- 1 ebonite panel, $9\frac{1}{2}$ in. wide, 4 in. high, and $\frac{3}{8}$ in. thick.
- 1 wooden baseboard, $9\frac{1}{2}$ in. \times $8\frac{1}{2}$ in.

- 1 ebonite terminal strip, $9\frac{1}{2}$ in. \times 1 in. \times $\frac{1}{8}$ in.
- 7 terminals, screws, wood screws, and wire.
- 2 metal brackets.
- 1 gramophone pick-up.
- 2 valve-holders.
- 1 L.F. transformer.

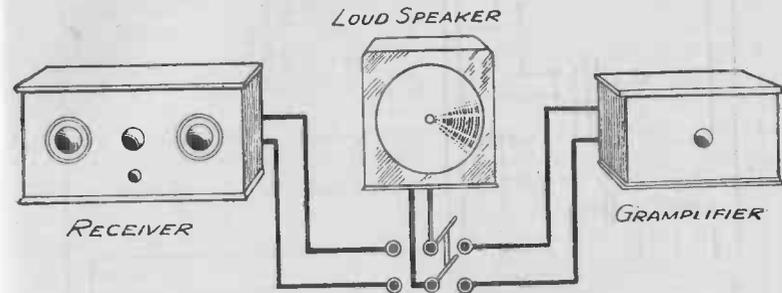


FIG. 98.—How the Gramophone Amplifying Apparatus is connected.

CIRCUITS Nos. 49 to 60

Circuit No. 49.—The simplest type of amplifier for what might be called "universal" use is that shown in Fig. 99. This is battery operated, employs a pentode valve, and can be fed equally well from a small battery receiver, pick-up or microphone unit without alteration. It will be seen that there are very few components required, and that they are mounted on a small wooden baseboard. The parts used are: one baseboard measuring 6 inches by 8 inches; one W.B. 5-pin baseboard-mounting valve holder; four Belling Lee twin-terminal mounts; seven terminals, two-marked input, two marked P.U., two marked L.S., and one marked Earth; one T.C.C. .01 -mfd. fixed condenser (type 40); one .25 megohm Dubilier, 1-watt grid leak; one Varley D.P. 24 low-frequency choke; one pair Bulgin G.B. battery clips; one Bulgin push-pull on-off switch; one Peto-Scott component bracket; one Cossor pentode valve, 220 H.P.T. or 220 P.T. (see later note); flex and wander plugs.

The positions of the few components can clearly be seen in Fig. 99, and no difficulty should be experienced in mounting them and wiring up according to the illustration. It should


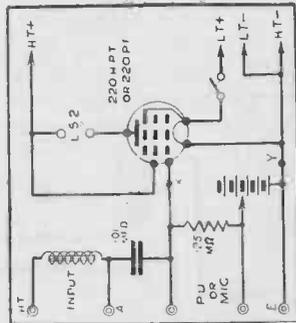


FIG. 99.—The simplest type of Battery Amplifier (Circuit No. 49) without volume control. Tone control can be obtained by connecting a .0003-mid. pre-set condenser to the points marked X and Y.

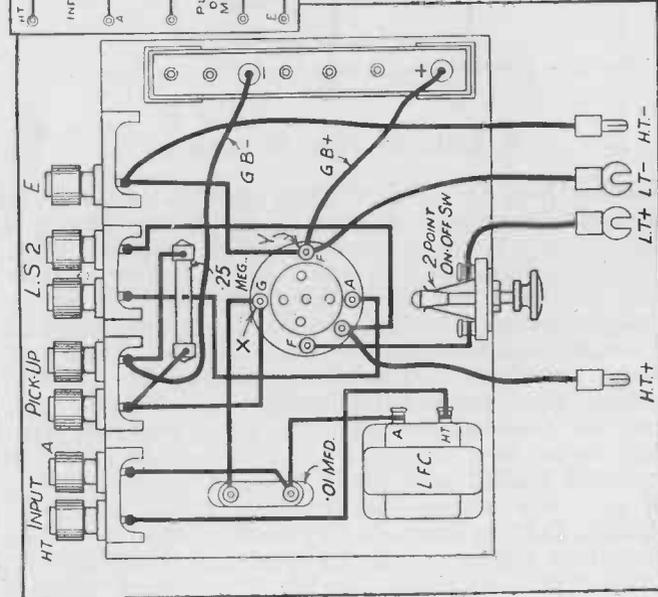

be noticed that only one terminal is fitted to one of the terminal mounts, this being for an earth connection. When the amplifier is required to operate directly from a pick-up or from a microphone—provided with its own input transformer and battery, of course—a 220 H.P.T. valve is to be preferred, because this has a high amplification factor and will permit of fairly good loud-speaker results. The same valve is also suitable when the unit is to be used, after a receiver which is not fitted with an L.F. stage or which gives an output which is insufficient, for the satisfactory operation of a loud-speaker. On the other hand, if the output from the receiver is fairly good, the 200 P.T. valve should be used, because this gives less amplification, but is able to handle a larger input. It should be made quite clear, however, that the amplifier is not suitable for use after a set with a pentode output valve, or which already provides good speaker-strength reception. It could be used in the latter case only by replacing the pentode by a super-power valve such as the Cossor 230 X.P.

The correct grid-bias voltage should, of course, be chosen according to the valve employed, and is -4.5 volts for the H.P.T., -7.5 volts for the P.T., or -15 volts for the P.X., assuming in every case the use of 120 volts high-tension. The latter can be supplied by an H.T. battery, but an eliminator or super-capacity battery is very desirable when using the super-power valve.

In order to use the amplifier with a receiver, the two terminals marked Input should be connected in place of the 'phones or speaker, connecting the terminal marked A in Fig. 99 to that terminal which is joined to the anode of the last valve in the set. If a pick-up or microphone is to be used, this component should be joined to the terminals marked P.U., when the other two terminals previously mentioned should be left disconnected. The terminal marked E should, for preference, be connected to an earth lead in every case when using a pick-up or microphone. The method of connecting the flexible leads is obvious, since they are attached to the battery terminals indicated.

When the amplifier is to be used with a receiver it will be desired to employ the same H.T. and L.T. supplies for both, and this can be done simply by connecting the flexible leads to the same batteries; in this case, however, the earth terminal should be left free, because an earth-return will be obtained automatically through the batteries.

Circuit No. 50.—A rather more advanced type of amplifier of very similar type is shown in Fig. 100, but

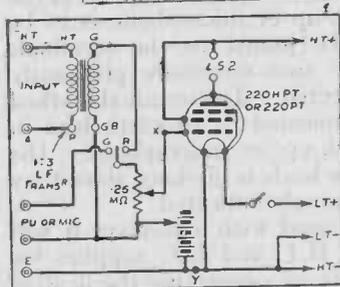
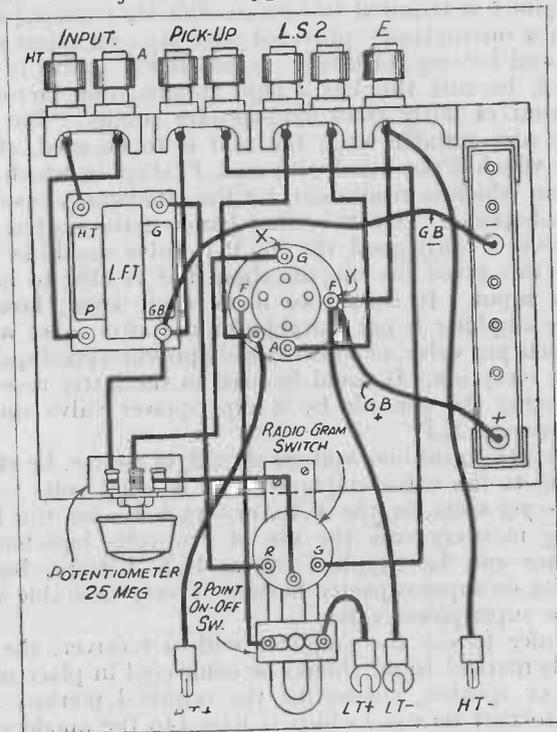


FIG. 100.—A simple Pentode Amplifier with radiogram switch and volume control (Circuit No. 50). Tone control can be effected, if desired, by connecting a .0003-mfd. pre-set condenser between the points marked X and Y.

here the L.F. choke is replaced by a 1:3 or 1:5 low-frequency transformer, such as the Ferranti type A.F., which actually has a ratio of 1:3.5. Additionally, the grid

leak and condenser are replaced by a good quality .25-megohm potentiometer, which is mounted on a second component bracket. There is also a radio-gram change-over switch—the rotary Snap switch is suitable—and this is mounted on the same bracket as the on-off switch.

This amplifier is particularly suitable for use after a short-wave receiver or other set not fitted with a power or pentode output valve, and when the maximum degree of amplification is required. The method of connecting the unit is as described for the previous arrangement, although it will often be found that greater amplification on pick-up and microphone can be obtained by connecting the appropriate component to the terminals marked Input, leaving the actual pick-up terminals disconnected. By doing this the step-up ratio of the transformer is utilised, so that greater volume is obtained. This idea is especially useful when the pick-up or microphone employed is not of a very sensitive pattern.

When using a pentode valve in either of the circuits described, it might be found that reproduction is somewhat high pitched. The tone can be "mellowed," and a fair degree of tone control obtained by connecting a .0003-mfd. pre-set condenser between the points marked X and Y. The tone may then be lowered by increasing the capacity of this condenser.

Circuit No. 51.—Neither of the amplifiers described above will give a very high degree of amplification combined with good quality, and if the amplifier is being built particularly for use with a gramophone pick-up or microphone it will be better to use two valves in the arrangement shown in Fig. 101. This is a combination of the circuits of Figs. 99 and 100 with the addition of a second valve. The input circuit consists of an L.F. choke and .01-mfd. fixed condenser, and these feed into a Cossor 210 L.F. valve, which is in turn coupled to the output valve—Cossor 220 P.—through the Ferranti transformer, or a similar component of another make, used in the second circuit. Again the components are mounted on a flat wooden baseboard, but this time it measures approximately 10 inches by 6 inches. The correct G.B. voltages for the two valves, for 120 volts high-tension, are -3 volts for G.B. -1 and -6 volts for G.B. -2.

It should be noted in mounting the components that

can be used with complete satisfaction with any of the three amplifiers.

Circuit No. 52.—The simplest possible type of mains-operated amplifier is that for use with D.C. mains, and a suitable circuit is given in Fig. 102, along with a wiring plan. The latter shows the use of a flat metallised baseboard, but a chassis could be used if preferred; it was thought, however, that the construction would be simplified by using the baseboard.

The arrangement is similar to one of those given for battery amplifiers, a single pentode valve being used with input arrangements suitable for either radio, microphone, or pick-up. It is for this reason that both choke-capacity, and direct coupling are indicated. One point which should be observed is that a fixed condenser is included in one pick-up lead as a safeguard against shocks. With some types of pick-up, however—piezo-electric types in particular—the condenser must be omitted, because it is necessary that there should be a complete electrical circuit through the pick-up and volume control. In such cases greater care must be taken in handling the apparatus, and the power supply should be switched off when connecting or disconnecting any piece of apparatus. This is a wise precaution even when the condenser is included, but is not absolutely essential.

The valve used is a Cossor 40 P.P.A., which has a heater consumption of .2 ampere at 40 volts, and which requires a total of about 40 m.a. at 150 anode volts, as well as a bias potential of approximately—25 volts. The mains voltage is dropped to the necessary figure for the heater by including in series a 240-volt, 60-watt lamp. This has a resistance of rather less than 1000-ohms, whilst the resistance of the valve heater is 200-ohms, so that the total resistance in circuit is about 1200-ohms. This means that when the voltage of the mains is, say, 240, the current flowing will be 1200 divided by 240, or 1.5 ampere, which is the correct figure. Actually, it is not essential that the current should be precisely this figure, and therefore the amplifier can be used on supply voltages of 230 to 250 volts quite safely. But even if the voltage were only 210, for example, the heater would be only slightly under-fed, and results would not suffer to any serious extent. In order to obtain maximum results with less than 220 volts, however,

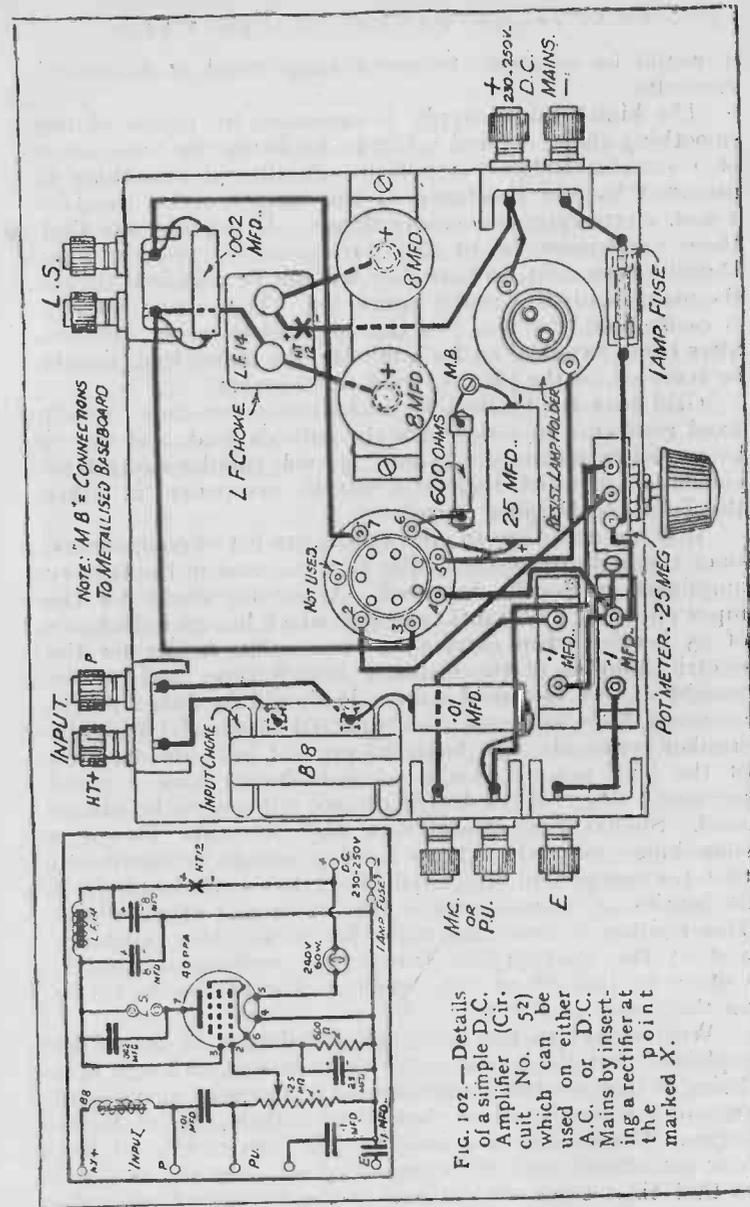


FIG. 102.—Details of a simple D.C. Amplifier (Circuit No. 52) which can be used on either A.C. or D.C. Mains by inserting a rectifier at the point marked X.

it would be desirable to use a lamp rated at 60 watts, 220 volts.

The high-tension supply is smoothed by means of the smoothing choke marked L.F. 14, this being the designation of a suitable Bulgin component. Additional smoothing is provided by the resistance of the lamp and by the two 8-mfd. electrolytic condensers shown. It is preferable that these condensers be of the "reversible" type, such as Dubilier type 0281, so that they will not be damaged should the mains leads be wrongly connected. The correct polarity is easily found by trial; if the amplifier does not function after being switched on for a minute, the mains leads should be reversed, or the plug reversed in its socket.

Grid bias is obtained by including a 600-ohm., 1-watt fixed resistance in series with the cathode lead, and this is by-passed by means of a 25-mfd., 50-volt tubular electrolytic condenser, of which there is a suitable component in either the T.C.C. or Dubilier range.

It is not necessary to give a complete list of components, since the main parts are similar to those used in the battery amplifiers previously described. A suitable choke for the input circuit is a Ferranti type B.8, which has an inductance of 25 henries when carrying 10 m.a. The holder for the electric lamp is of the ordinary batten type, and can be bought at any electrical store. It should be noted that a .002-mfd. fixed condenser is connected in parallel with the speaker terminals, this being to prevent over-accentuation of the high notes. This condenser should have a rated working voltage of not less than 500, but any make can be used. Should any constructors wish to make use of a smoothing choke which is on hand, it should be mentioned that the component suggested above has an inductance of 20 henries at 50 m.a. and a D.C. resistance of 400-ohms. This resistance, combined with that of the bias resistance and of the loud-speaker transformer reduces the anode voltage to just about 150, which is the maximum rating for the Cossor 40 P.P.A.

With regard to the constructional details, it should be explained that the layout is not very critical, although it is desirable that the two chokes should be mounted at opposite ends of the baseboard or chassis, with their axes at right-angles. When using a baseboard, the two 8-mfd. electrolytic condensers have to be mounted on a metal "bridge" so that their cases are earthed to the baseboard and con-

nection to the positive terminals can be made on the underside of the "bridge." If it is not wished to make the mounting bracket, two separate brackets can be bought ready made from many dealers. Other constructional details are obvious from Fig. 102.

The amplifier can be used in conjunction with either a D.C. or battery set, and will provide a maximum output of more than 2 watts. It is recommended that it be fed from mains whose negative lead is earthed, in which case the terminal marked E can be joined either to a separate earth lead or to the earth terminal on the set. Where the positive mains are earthed, it can be used with a D.C. receiver by joining the E terminal to the negative line in the set, and in no circumstance should a direct earth connection be made to the amplifier. Microphone or pick-up can be used by following the general instructions given in the previous article.

It will be understood that the full output of the valve will be obtained only when the input is sufficiently high, for which reason the pick-up or microphone employed should be one of the most sensitive pattern. The amplifier can be used in conjunction with a receiver of which the output is not more than about 300 milliwatts, and of which the last valve does not pass more than a maximum of 15 m.a.

The speaker may be of the permanent-magnet type, but better results will be obtained by using a D.C. energised speaker, the field coil being connected directly to the positive and negative supply terminals.

Should the amplifier be required for either A.C. or D.C. operation at will, this can be provided quite easily by inserting a Westinghouse style H.T.12 metal rectifier at the point marked X, wiring the positive and negative terminals of this as indicated. The rectifier can be left in circuit whether the supply is D.C. or A.C., for it will simply act as a small resistance to D.C.

Circuit No. 53.—Details of an A.C. amplifier capable of providing a greater degree of amplification are given in Fig. 103, where it will be seen that two triode valves are used for amplification, with a full-wave rectifying valve for H.T. supply. The valves recommended are: Osram M.H. 41 for the first stage, Cossor 401 M.P. for the second, and Cossor 506 B.U. for rectifying. The input choke is the same as that used for the D.C. unit, and the L.F. transformer

electrical constituents of the receiver itself. These are the things that we should expect to *hear*, but most of us go on expecting instead of getting them. The first and third hardly require explaining: the second suggests sound radiation, the fourth means character likeness, the fifth a clear definition of all the parts that make up the whole, and the sixth a correct balance between bass, middle, and treble registers. It is well known that the third, fourth and fifth characteristics can be obtained reliably from resistance-capacity coupling, while the first and second can, in my opinion, be best secured from the special form of coupling to be described later. The last feature—proportionality or balance—depends on the shape which the frequency response curve is arranged to take. Since the majority of receivers are used in private houses and the volume level is normally below that of the original, it is essential to raise the response curve at the lower end of the spectrum, while the middle and upper portions should be as free from peaks and troughs as possible, in view of the fact that the loud-speaker characteristic is not innocent of these blemishes. Broadcasting conditions being what they are, there may be a distinct advantage in a slightly drooping response above 8000 cycles provided the droop is gradual, while the reproduction of gramophone records usually demands a gradient in the response curve above 6000 cycles at least.

The response curve of the amplifier is straight between 100 and 8000 cycles. Below 100 cycles the curve begins to rise till it reaches its maximum point at 50 cycles where the gain is eight decibels, and below 50 cycles it starts falling very slightly down to 25 cycles, the drop being of the order of one decibel, so that at 25 cycles the actual gain is seven decibels. Above 8000 cycles the response gradually drops till at 10,000 cycles there is a loss of 3.5 decibels, which is quite inconsiderable. The frequency characteristic, however, gives only a very imperfect idea of the performance of the amplifier, and it is only mentioned in order to satisfy the curiosity of those who are apt to place undue confidence in response curves.

It has already been pointed out that liveliness, fidelity, and clarity of reproduction may be satisfactorily obtained from the employment of resistance-capacity coupling. In accordance with this postulate the first two stages of the amplifier are so treated, and Fig. 104 gives the fundamental

circuit, with (in addition) a special form of high-note control incorporated in the grid circuit of the second valve. This treble control is designed to operate in conjunction with the quarter megohm potentiometer and will be found extremely serviceable in all circumstances. It is well known that as the volume of the receiver is reduced by means of the usual potentiometer control, high-note loss is introduced as the resistance between the coupling condenser and the slider is increased, and in order to compensate for this loss a condenser is shunted across these two points. After careful experiment it has been decided to use a capacity

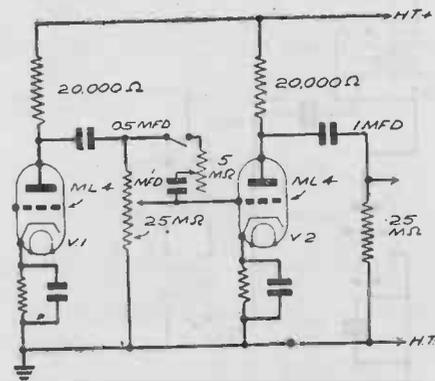


FIG. 104.—The first two stages of the Amplifier (Circuit No. 54) with the special high-note control.

of 0.1-mfd. for this condenser and to graduate the control by means of a half-megohm variable resistor. A switch is also incorporated, since even with half-megohm resistance fully in circuit the condenser still affects the quality to a slight degree.

The complete amplifier consists of four stages, and in order to avoid the overloading of the output valve the stage gain of the two resistance capacity coupled stages is kept down to a low value. Hence the anode resistors are in each case only 20,000 ohms., and the valves employed must be of the power class such as the M.L.4, AC/P., or 104V. If battery valves are used, the P.2 type is recommended.

The third stage introduces the special coupling which places this amplifier very high in the scale of design.

Readers may experience some difficulty in hailing with adequate enthusiasm the appearance in the diagram of Fig. 105 of three transformers. They will, doubtless, remark that this is an expensive arrangement for a single stage coupling; but it must be pointed out that the result amply justifies the extra cost. Besides which, it is hoped that most of my readers already possess at least one of these well-known components. The circuit in Fig. 105 is self-explanatory, all the connections being quite clearly marked. The shorting switch across the secondary wind-

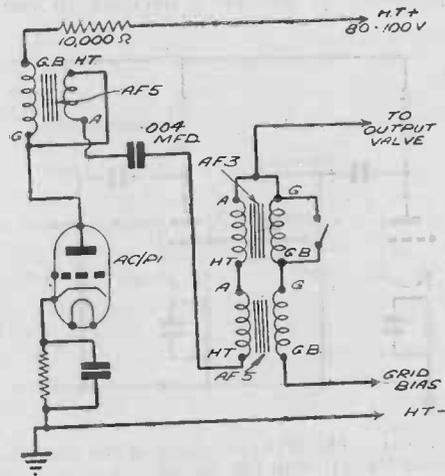


FIG. 105.—The special coupling between the third and last valves of Circuit No. 55.

ing of the A.F.3 transformer should be noticed, since with this winding short-circuited the response curve of the amplifier undergoes a change which should be easily perceptible, even to the average ear. What happens is that the lower frequencies below 500 cycles are gradually increased in strength till at 50 cycles a gain of twelve decibels is attained, while in the upper portion of the curve the response starts falling above 6000 cycles till at 10,000 the decibel loss reaches the figure of ten. Unless a high-range speaker is employed this attenuation in the upper register may be barely noticeable, though if a peak occurs in the speaker or microphone characteristic (or in the pick up, as the case

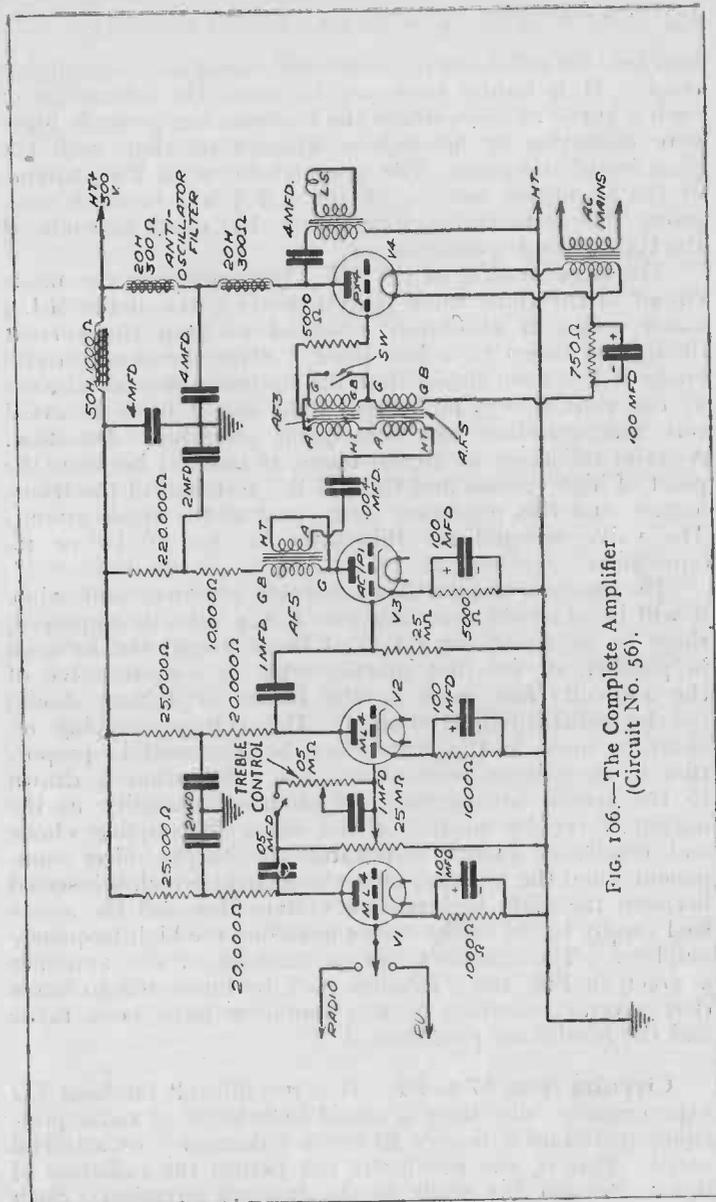


FIG. 106.—The Complete Amplifier (Circuit No. 59).

may be), the fall in the response curve may effect a gratifying result. It is hardly necessary to stress the advantage of such a curve in cases where the transmission presents high-note distortion or heterodyne whistles interfere with the pleasure of reception. For gramophone work the shorting of the secondary winding of the A.F.3 will in most cases prove the more satisfactory course, but much depends on the type of loud-speaker in use.

The large winding of the A.F.5 transformer in the anode circuit of the third valve (also a power valve of the M.L.4 class) makes it absolutely essential to keep the current dissipation down to a low point. After the most careful study it has been found that the optimum flow of current at 100 volts is 0.75 milliampere, the object being to avoid core magnetisation and consequent amplitude distortion. A series resistance of 10,000 ohms is inserted between the point of high tension and the "G.B." terminal of the transformer, and this resistance forms part of the anode circuit. The valve selected for this stage is the AC/PI or its equivalent.

The output stage follows normal practice, and while it will be observed that only one P.X.4 valve is employed, there is no reason why two of these should not be used in parallel, or for that matter, why an output valve of the 400-volt class, such as the DO.26 or P.X.25 should not be substituted, if desired. The voltage-dropping resistances must in this latter case be increased in proportion in accordance with Ohm's law. Attention is drawn to the special arrangement to obviate instability in the output valve by means of the extra de-coupling choke and condenser (which duplicates the output filter components) and the 50-henry smoothing choke which is inserted between the main high-tension voltage line and the anode feed supply to the earlier stages including the high-frequency amplifier. The complete circuit diagram of the amplifier is given in Fig. 106. Readers may be interested to know that several examples of this amplifier have been made and the results are phenomenal.

Circuits Nos. 57 to 59.—It is not difficult for *bona fide* experimenters who have a sound knowledge of radio principles to obtain a licence to use a "dummy" or artificial aerial; that is, one which will not permit the radiation of signals beyond the walls of the holder's premises. Such

people will find a simple transceiver a very convenient initial form of equipment.

A simple transmitter is almost identical in main principles with a simple single-valve receiver. The chief difference is that the receiver, with reaction, is used in a state just short of oscillation, while the principal object of a transmitter is that of providing sustained oscillations. In the case of C.W. or morse transmissions the oscillation is interrupted by means of the tapping key, whilst when telephony is being transmitted, the sound or audio frequencies must be super-imposed on the steady oscillation.

Fig. 107 shows a typical circuit for a single-valve receiver with capacity-controlled reaction. Values given apply chiefly to a short-wave receiver for wavelengths between about 16 and 100 metres, but connections would be the same if it were to be used for medium- and long-wave reception; in that case the tuning and reaction condensers would have higher values.

As you are well aware, this circuit could be caused to oscillate simply by increasing the capacity of the reaction condenser. In that state it would radiate, through the medium of the aerial, a steady oscillation. That oscillation would be the equivalent of the carrier wave of a normal transmitter. Consequently, in order to use the receiver for transmitting it would be necessary only to "inject" into the oscillatory circuit audio frequencies. That could be done by including the microphone and microphone transformer, along with a dry battery to energise the microphone, in one of various positions in the circuit (Fig. 108). Three suitable positions are indicated by means of crosses; one is in the anode circuit, the other is in the earth circuit, and the third is in the grid-return circuit.

Of these, the last mentioned is generally most satisfactory, and a modified circuit—this time of a transmitter with a form of grid modulation—is shown in Fig. 108. The similarity between the two arrangements is very clear. The only important difference is that the H.F. choke is connected directly to H.T. + instead of through the 'phones. In addition to this, it will be seen that the values of grid condenser and leak are different and that the lower end of the grid coil is not joined to the earth line.

For satisfactory working, the valve should be of the small power type and should be fed with not less than 120 volts H.T. If a sensitive microphone were employed

chassis. An alternative switching arrangement consists of employing a three-pole double-throw anti-capacity switch.

Connections for both of the systems mentioned are shown in Fig. 110.

Tuning Difficulties.—One of the great objections to any form of transceiver is that the tuning has to be changed almost every time the switch is turned from the transmit-to-receiver and receiver-to-transmit positions. Consequently, the tuning scale should be clearly marked at the correct

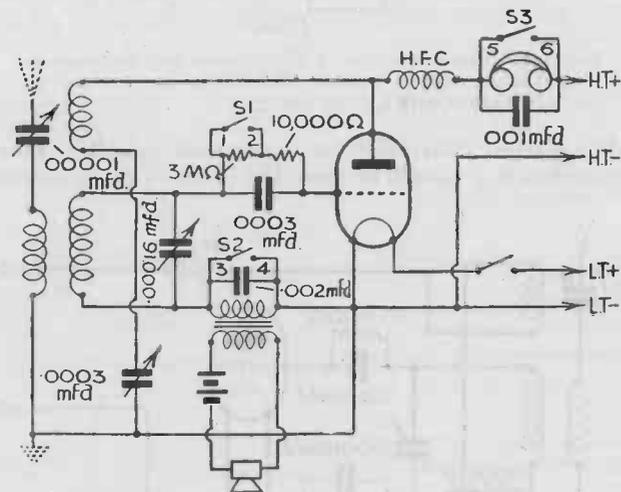


FIG. 110.—How Receiver and Transmitter Circuits can be combined to form a transceiver by means of a simple switching system (Circuit No. 59).

position for the transmitting wavelength. An alternative method would be to have two condensers, one always set to the same wavelength, with a switch to bring either into circuit as required; the switch could be ganged with the other three.

It should be made clear that a simple transmitter of this nature would not be looked upon with favour by the Post Office, due to the fact that there is no system of accurate wavelength control, such as is provided when using a crystal. But, as the set is not in any case intended for use with an "open" aerial, this is not a serious matter. If at any time the set were used by a licenced transmitter on an outside

aerial it would be essential to have an accurately-calibrated wavemeter by means of which the frequency could frequently be checked and adjusted.

On the 5-metre Band.—Transceivers are most frequently used on the 5-metre band (to use, which for transmitting, a special permit is required in connection with the transmitting licence) and on the ultra-short waves they are capable of very satisfactory results. When built in portable form and used in conjunction with a copper-tube aerial only a few feet long, ranges of several miles can often be covered when using an ordinary H.T. battery to supply the power.

Circuit No. 60.—It is possible to use an ordinary moving-

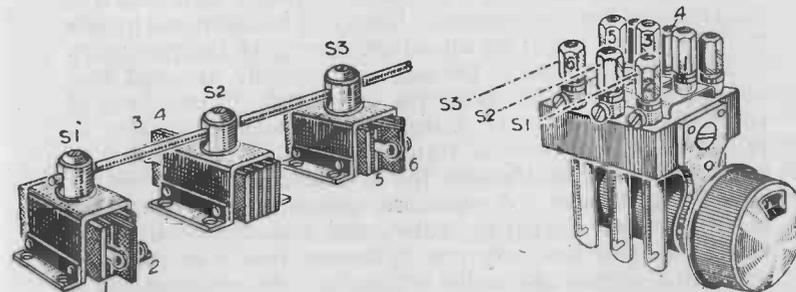


FIG. 111.—Two Transmit-Receive Switch arrangements for Circuit No. 59. The terminal numbers correspond with those in Fig. 110.

coil type of loud-speaker both as a microphone and reproducer and we have also already shown how the speaker may be switched from one position to the other. The unit described in this section utilises this principle and incorporates a two-stage A.C. amplifier with which it is possible to obtain two-way communication over quite considerable distances and with high input sensitivity. Of course, it is possible to arrange that the speaker acts in the dual capacity without the need for a change-over switch for "Talk" and "Listen" positions, but this is a more complicated process and will also be more expensive to construct. It is also to arrange that any pair of sub-stations can call each other and maintain conversation whilst other lines are in action, without interference. The unit here described, however, is of the simplest type and will be found ideal for installation

in the home, so that communication may be established with five different rooms from a central point, and it will also be found of value to a business man who wishes to provide such an installation so that he may be in communication with his various offices or workshops. The illustrations show the general appearance of the finished Master unit from which it will be seen that it is neat and of simple appearance and may take its place on any standard desk without being obtrusive.

The Circuit.—Fig. 112 shows the circuit employed from which it will be seen that an input transformer is provided and fed from a 5-point selector switch *via* a special type of change-over switch. The input valve is coupled to the output pentode through a resistance-capacity unit which is incorporated for two reasons. Firstly, it is cheap and avoids troubles which might be introduced owing to the proximity of other transformers in the set, and secondly, the grid leak may be made variable so that a simple but efficient form of volume control may be utilised. The built-in speaker is provided with an output transformer which is also fed to the selector switch through the special change-over switch already mentioned. A standard mains section consisting of transformer, rectifying valve, and smoothing circuit is fitted and this has only one difference from the standard apparatus as used in radio apparatus. This consists of a split negative H.T. feed, the use of which will be explained at a later stage. The wiring diagrams show how the various parts are arranged and it will be noted that five pairs of terminals are provided for connection to the five sub-stations. It is possible to dispense with five of these terminals by using a common earth return, but there are drawbacks to this arrangement and the saving of expense is very small.

The selector switch is a standard Bulgin 5-point switch and is mounted on the left of the panel, and in the illustrations it will be seen that an indicating panel is provided for this. The component which I used was a Bulgin standard component, but to present a neat appearance this was cut (ordinary scissors will do) to give the shape shown in the illustrations. This change-over switch is a 12-point (four-pole change-over) of the Dewar type supplied by Electradix. One section of this is not used in this particular design, although, if desired, it could be used to operate a calling-up buzzer circuit.

A full list of components is included on page 164, and

it will be seen that the speaker in the Master Unit is a Standard W.B. Midget, but the sub-station speakers should be of the same type, without input transformer. It is possible to use ordinary speakers if you have them handy, but the input transformer should be disconnected and the speech coil winding only used. The input transformer is of the microphone type to give better matching to the input grid circuit and also to provide a better step-up ratio to overcome the losses which are introduced when very long leads are employed between the master and sub-stations. The chassis should be cut as shown in the Wiring Diagram to clear the chassis of the speaker, and holes for the valve-holders and for the passage of connecting leads should then be drilled. On the rear chassis strip ten holes should be drilled for the terminals, and a $\frac{3}{8}$ -inch hole for the Bulgin volume control. A mains connection is shown on the other end of the rear strip, but if desired a mains on-off switch may be placed here instead, and the leads to the nearest mains socket may be permanently attached to the switch and mains transformer. In the design as illustrated the mains must be switched on at the mains plug, but the apparatus may be "disconnected" or rendered inoperative by means of the change-over switch, due to the breaking of the H.T. negative lead previously mentioned.

The panel or cabinet front must be cut to accommodate this change-over switch and two $\frac{3}{8}$ -inch holes drilled for the 5-point selector switch and the small pilot or signal light. This enables the user to see at a glance whether the unit is switched on, and whilst it is kept in a condition ready for use the light behind this small indicator will glow, although, when the switch is in the "up" position it is impossible to talk or listen on the apparatus. This idea avoids the necessity which would otherwise be introduced of waiting for the valves to heat up and thus the apparatus is ready for immediate use at any time. Wiring should be carried out with heavy wire, say 22-tinned copper, and insulated sleeving should be passed over certain of them to avoid possibility of short-circuits. The wiring is very simple and the only point which might introduce difficulty is the change-over switch. The cross connections should be made before the switch is mounted as the contacts will otherwise be found rather inaccessible.

When wiring is completed, the unit should be tested out to make certain that the connections are correct. The

valves should light up (with the signal light) when the mains switch is in the "on" position, and the right-hand lever switch should be pushed into the up, or "off" position. If leads are not connected to the five pairs of terminals, when the right-hand switch is pushed down, the speaker on the Master Unit should hum, showing that the switch is operating correctly. The sub-units or stations consist merely of the small speakers, and these may be mounted in small cabinets, or simply placed in a convenient position in the room. They need not be placed close to where a person sits, and may be tucked away in any convenient position as they will pick up the normal conversation volume of a person in even a very large room although not pointing at the person. Ordinary twin bell-wire may be used for wiring between Master and sub-stations, and if a common earth return is employed the lead to one side of the speech coil on the distant speaker should be connected to the nearest earth point. An earth wire must then be attached to one of the terminals on the rear of the master unit which are shown connected together in the wiring diagram.

In use, the user of the master unit simply pushes the change-over switch down to a horizontal position and turns the 5-point switch to the number corresponding to the distant point to which he wishes to speak. An ordinary conversational tone may be adopted and there is no need to raise the voice. When he has spoken and wishes to hear a reply, the right-hand switch is depressed, and held in position. On this model the switch remains in an "off" or "talk" position only, and thus to hear signals from any of the sub-stations the lever has to be held. If the apparatus is to be used by a business man who is anxious to eavesdrop on his various offices, the inconvenience of holding the switch down to listen may be overcome by changing round the wiring to the two-bridged pair of contacts on the switch in which case the normal central position will be "listen" and it will have to be depressed to talk. If, in the case of any special announcement it is desired to talk to all five sub-stations at once, this may be done by bridging all of the five terminals at the rear by means of a piece of bare wire.

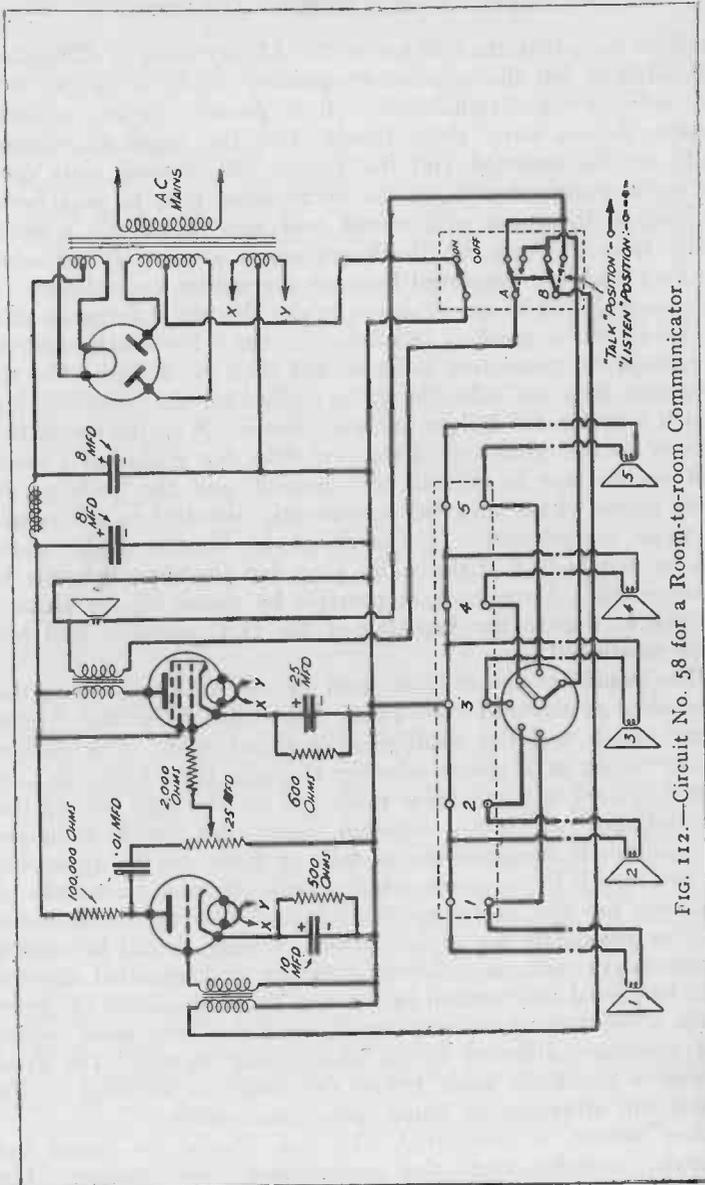


Fig. 112.—Circuit No. 58 for a Room-to-room Communicator.

LIST OF COMPONENTS—ROOM TO ROOM COMMUNICATOR
(5-WAY)

2 8-mfd. electrolytic condensers.	1 600-ohm. 1 watt resistor.	1 microphone transformer.
1 10-mfd. electrolytic condensers.	1 750-ohm. 1 watt resistor.	10 terminal (5 red. 5 black).
1 25-mfd. electrolytic condensers.	1 L.F. smoothing choke	1 4-pole switch.
1 .01 mfd. fixed condenser.	1 volume control, .25 megohms.	1 chassis, 10 in. x 8 in. metallised surface.
1 100,000-ohm. 1 watt resistor.	1 mains connector,	1 cabinet.
1 2000-ohm. 1 watt resistor.	1 5-way rotary switch.	1 41 M.H.L. Valve.
	1 signal light.	1 M.P./pen valve.
	1 mains transformer.	1 506 B.U. valve.
		1 midget Speaker.

SUB-STATIONS

1 midget loud-speaker, type 37M. without transformer. (One for each sub-station.)

Cabinet to suit above, and to harmonise with room furnishings.

CALIBRATING A RECEIVER

Those who are able to receive foreign stations are often mystified by receiving a station, and, being unable to understand the announcements, cannot get any idea whether it is a low-powered station at a great distance, or a high-powered station near by. It is convenient to be able to make a note of the various countries heard on a set, and at the same time being able to know where to set your tuning dials to pick up any station when you see from the newspapers or some other periodical that a certain item is being broadcast which you would like to hear. It is not very difficult to draw up a chart which will make it possible to do all this, and it need only cost a few pence. It will be found a most interesting job drawing the chart, and if it is afterwards fixed inside the lid of the wireless set it will always be handy for reference (see Fig. 113).

Marking out the Paper.—You will want a sheet of squared paper, generally known as graph paper. This is usually obtainable from most good stationers or artists' supply stores. It does not matter whether the squares are in tenths of an inch or millimetres, the actual size chosen depending on the room you wish the chart to occupy when it is finished. Rule along one of the lines near the bottom of the sheet, and mark along this the numbers corresponding to those on your tuning dial. This may be 0 to 100 or 0 to 180, it does not make any difference which it is. Now at the left-hand side of the sheet rule a vertical line running from the line marked

with the 0. Along this line you must mark the metres (or frequencies in kilocycles, just as you desire) corresponding to the tuning range covered by your condenser. If the tuning condenser is of the type known as a "log" scale, then it is preferable to mark the tuning range in kilocycles. For the other types of condenser use the metre scale. Of course, you

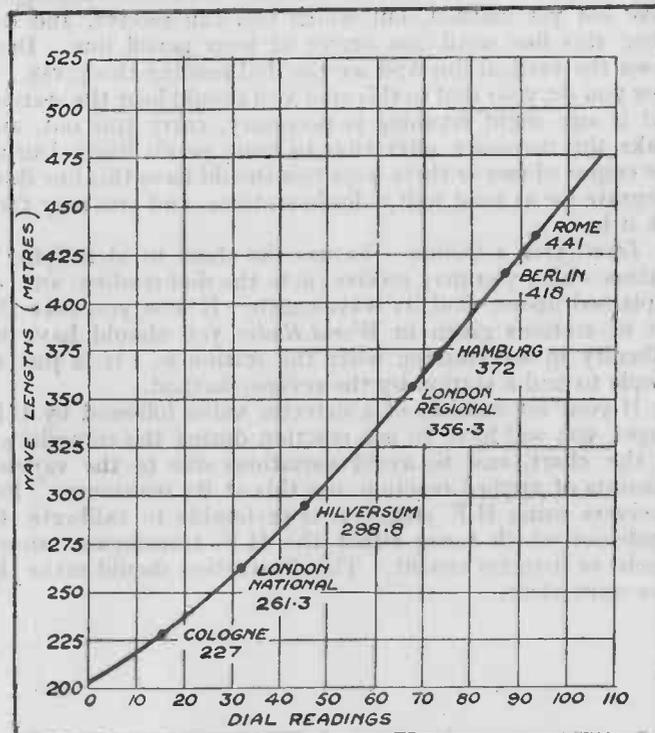


Fig. 113.—The Chart to use for identifying Stations.

may, if you wish, mark this in both the frequency and the wavelength. Having done this, you may settle down to the more interesting job of calibrating your set. First of all tune in to your local station. If possible, avoid the use of reaction when carrying out this calibration. Having tuned-in to the exact spot, make a careful note of the reading on the dial. Now find this spot on the bottom line of your chart, and run

your pencil up the vertical line above this spot until you arrive at the place where the horizontal line corresponding to the wavelength of the station crosses it. Make a small dot at this spot. Now tune in another loud station, and carry out the same process. When you have, say, three or four dots on your chart, carefully join them up with a light pencil line. Now find the wavelength of a station which you have not yet marked, but which you can receive, and run along this line until you arrive at your pencil line. Drop down the vertical line and see the dial reading this gives. If now you set your dial to this spot you should hear the station. but if any slight retuning is necessary, carry this out, and make the necessary alteration to your pencil line. During the course of two or three days you should have this line dead accurate for at least half a dozen stations, and you may then ink it in.

Identifying a Station.—To use the chart in identifying a station which you may receive, note the dial reading, and, as explained above, find its wavelength. If now you take the list of stations given in *World-Radio* you should have no difficulty in ascertaining what the station is. It is just as simple to find a station by the reverse method.

If your set consists of a detector valve followed by L.F. stages, you will have to use reaction during the compilation of the chart, and to avoid variations due to the varying amounts of applied reaction, use this at its maximum. For receivers using H.F. stages, it is preferable to calibrate the condenser which tunes either the H.F. transformer, tuned anode, or detector circuit. The illustration should make the idea quite clear.