

Radio Editors of magazines and newspapers are hereby given permission to reprint in whole or in part, with proper credit to the Aerovox Corporation, the contents of this issue of the Aerovox Research Worker.

The AEROVOX Research Worker

The Aerovox Research Worker is a monthly house organ of the Aerovox Corporation. It is published to bring to the Radio Experimenter and Engineer authoritative, first hand information on condensers and resistances for radio work.

VOL. 9, NO. 7

JULY, 1937

50c per year in U.S.A.
60c per year in Canada

Amplifiers

PART 2

By the Engineering Department, Aerovox Corporation

(Continued from the June 1937 issue)

5. AUDIO AMPLIFIERS: Audio-frequency amplifiers may be divided according to their type of coupling into resistance-coupled amplifiers, impedance-coupled amplifiers, transformer-coupled amplifiers and direct-coupled amplifiers.

The charts of Figures 4, 5, and 6 show the fundamental circuits, their

found in the R. C. A. application Note 67, Jan. 20, 1937.

Resistance coupled amplifiers have the advantage of economy while the frequency response can be made nearly flat. The phase distortion is less than that of other types of coupling except direct coupling. Disadvantages are: lower gain than impedance or transformer coupling with the

the plate voltage higher. The frequency response falls off at the low end as well as at very high frequencies, above the point where parallel resonance occurs. The drop at the low end can be minimized by placing a resistor across the plate choke. If the value of the resistance is 1/3 of the choke reactance at the lowest frequency, or less, the impedance of the combination will not vary more than a few percent over the audio range.

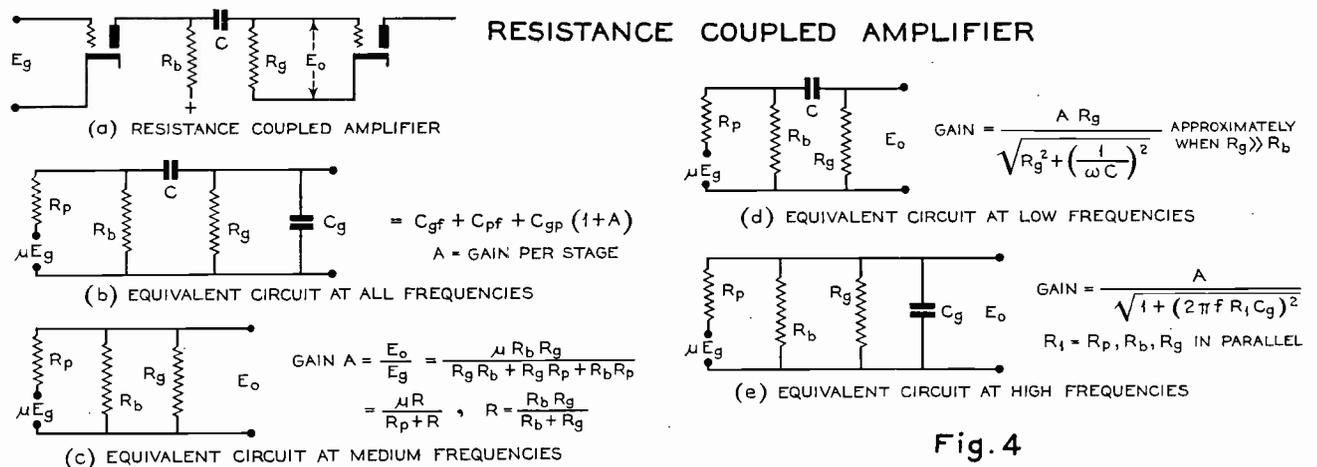


Fig. 4

equivalents and the gain obtainable at low, high and intermediate audio frequencies. Complete information of the constants for Resistance coupled amplifiers and their performance will be


same tubes and power supply and the tendency to "motorboating".

Impedance coupled amplifiers have the advantage that a lower voltage drop occurs across the load, making

At the present state of the art, transformer-coupled amplifiers can be designed to have a frequency characteristic as good as that of a resistance-coupled amplifier. The gain of

AEROVOX PRODUCTS ARE BUILT BETTER

IMPEDANCE COUPLED AMPLIFIER

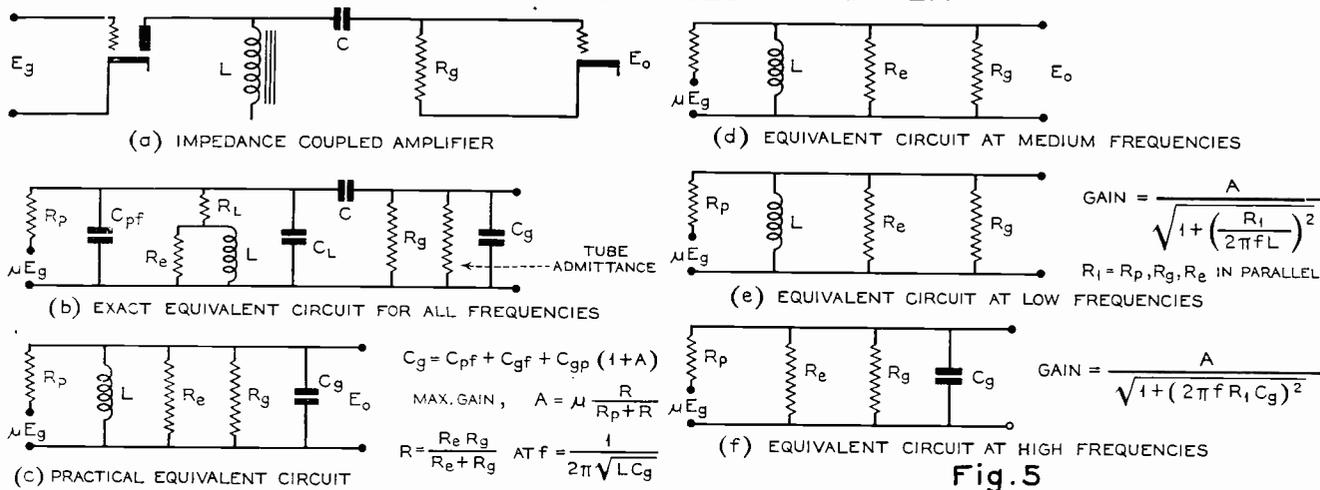


the amplifiers is not as high as that of the resistance-coupled amplifiers using pentode tubes, and the cost of the transformers is very high. When sensitive amplifiers are used and a transformer is at the input, the hum problem is much greater than with r.c. amplifiers. Well shielded transformers are required and even then critical placing is necessary.


Transformer coupling is, however, the only way in amplifiers where the grid circuit takes power, as in class B and C amplifiers.

Direct coupling is really a special case of resistance coupling. In such circuits the plate of the first stage is directly connected to the grid of the next, which requires some juggling with power supplies. Since the load between stages is a resistance and the coupling elements per stage are reduced, this type of amplifier can be made to have a better response than any other type. Response at low frequencies is better and delay distortion is less. The main difficulties are the tendency to drift due to temperature changes and the difficulty in designing amplifiers of many stages. It is, however, possible to make an amplifier employing a drift-corrector which makes the system practical for amplification of a.c. signals but not for d.c. Practical circuits of a single ended amplifier and a push-pull amplifier are shown in Figure 7.

TRANSFORMER COUPLED AMPLIFIER

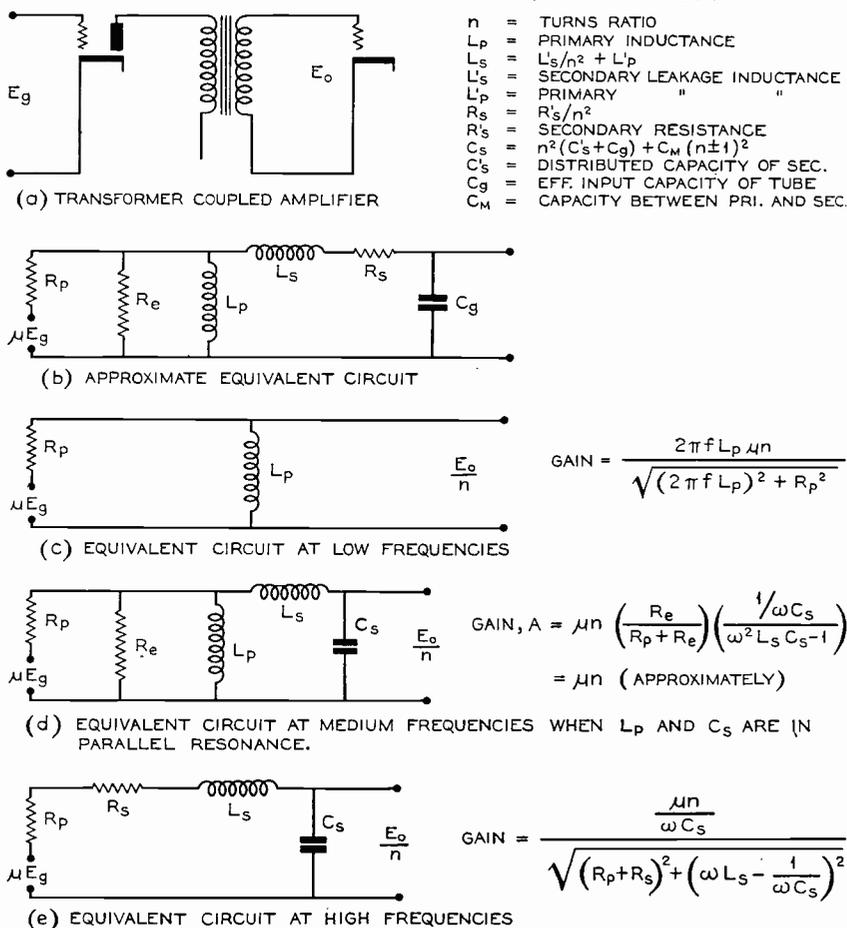

DIRECT COUPLED AMPLIFIERS

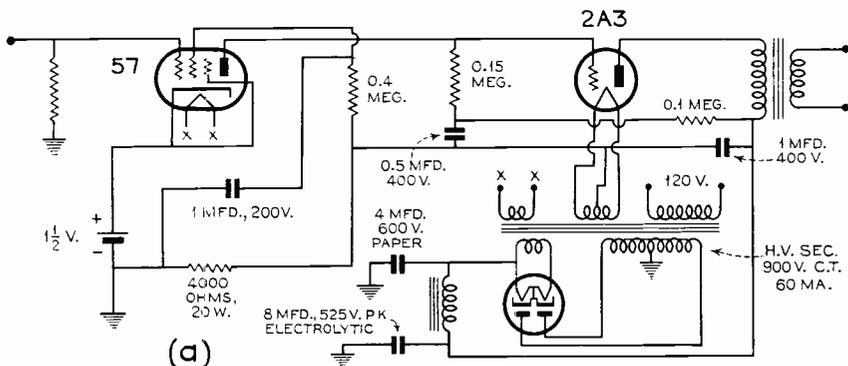

6. FEEDBACK: When a portion, B, of the output of an amplifier having a voltage amplification A, is fed back to the input, the gain becomes:

$$\frac{A}{1 - AB}$$

in this case B is positive for regeneration and negative for degeneration. Non-linear distortion, noise and hum will be multiplied by the factor—

$$\frac{1}{1 - AB}$$

These equations hold when the feedback voltage is in series with the input signal and there are no additional phase shifts due to reactances.

Figure 8 shows several ways of arranging the feedback circuit in transformer-coupled and resistance-coupled circuits. There is a phase shift of 180 degrees in each stage which should be taken into consideration; in addition, there is a phase shift in each stage which varies with frequency but is never more than 90 degrees. This fact limits the number of stages to be bridged by the feedback circuit. When the sum of the shifts amounts to 180 degrees, oscillation starts unless the gain at that point is less than one. For this reason, degeneration is limited as a rule to three stages and to about 30 db.


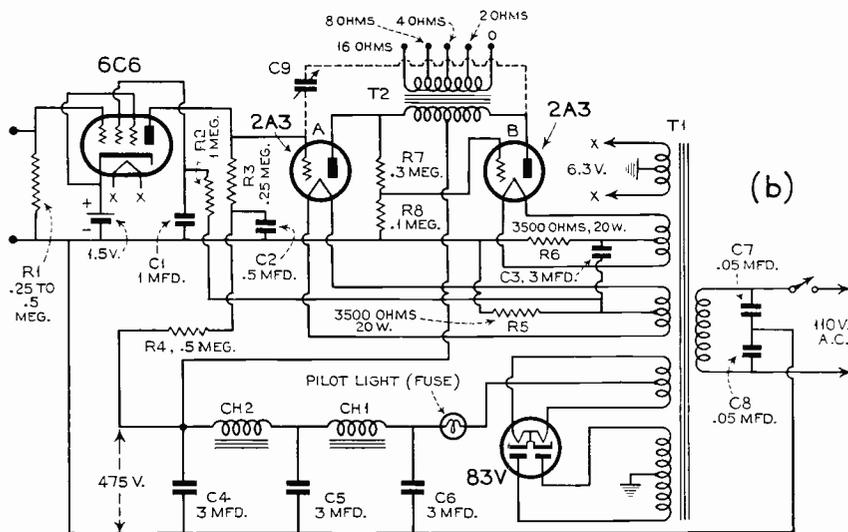
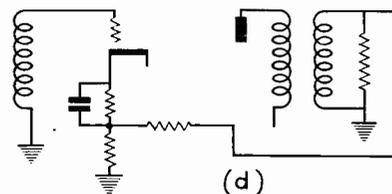
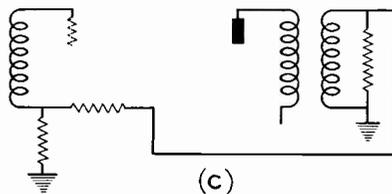
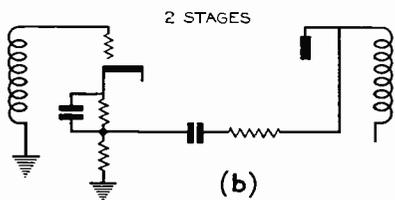


Fig. 7

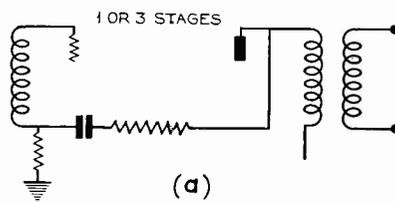COUPLING METHODS FOR RESISTANCE COUPLED AMPLIFIERS



FOR ANY NUMBER OF STAGES, ALL TYPES OF COUPLING



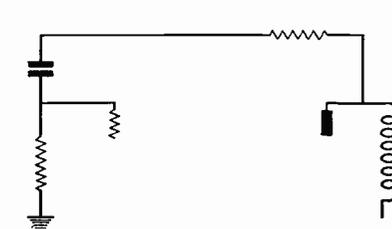


Fig. 8

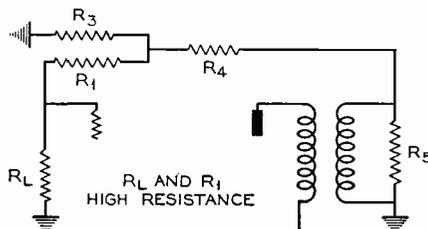

AEROVOX *Interference Filters*

for the Reduction of Man-Made Static

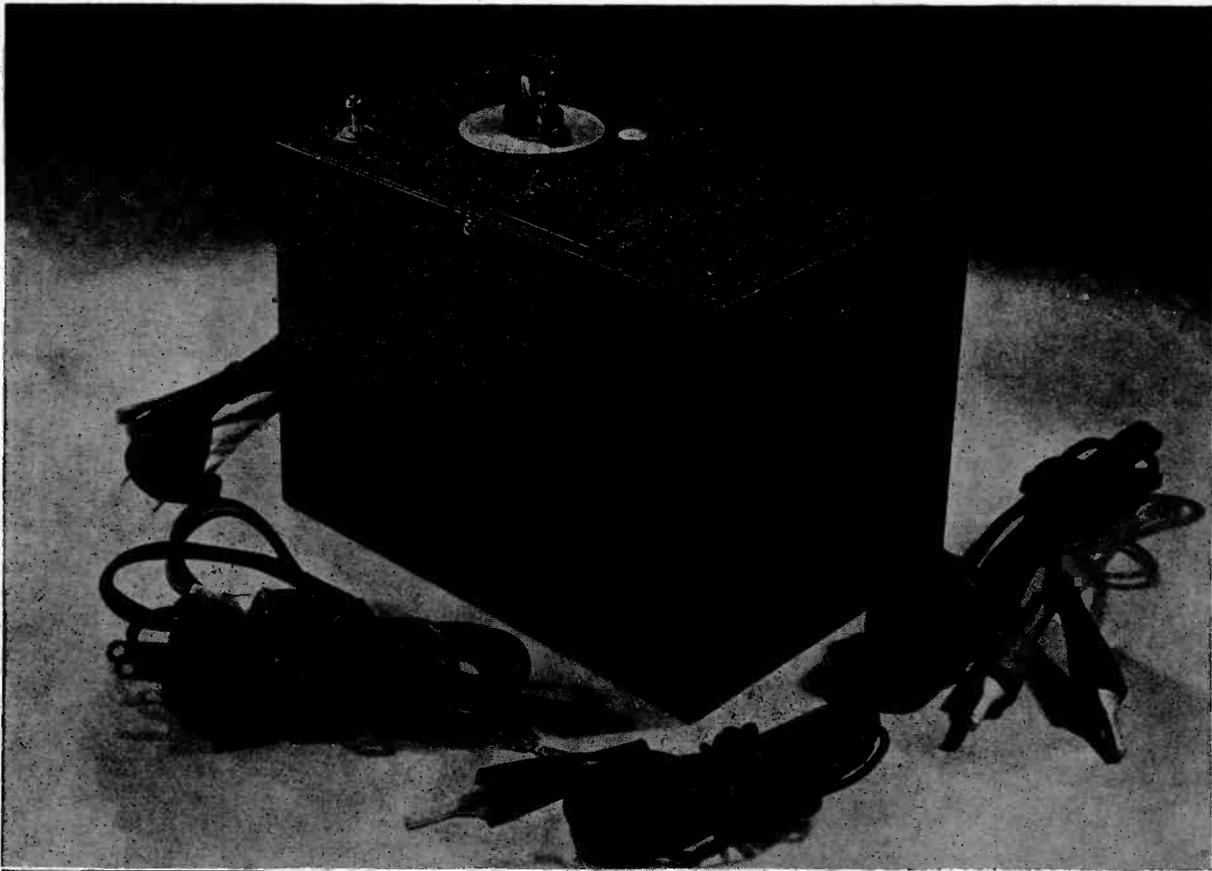

YOU can cure those radio noises. For yourself and for others. In the latter event, there's money in it for you.

the power circuit. Attachment cords permit different connections. When best results are obtained, selector dial indicates the choice of filter, also the proper connection.



AEROVOX has reduced noise suppression to ABC terms. There's the AEROVOX Noise Analyzer (shown above). At the twist of the selector switch, it introduces different types of filters in

Meanwhile, AEROVOX offers a new line of interference filters for practically every noise-producing device. Also for use at the set.



Get the FACTS



New 32-page general catalog has entire section devoted to noise suppression. Also, a new folder, written for the layman, is creating a lively interest among set owners and is paving the way for live-wire dealer and serviceman. Ask your jobber—or write us.



AEROVOX CORPORATION

70 WASHINGTON STREET, BROOKLYN, N. Y.



Sales Offices in All Principal Cities