

TUNGSTEN LAMP (R<sub>2</sub>) AS STABILIZING RESISTOR IN AUDIO OSCILLATOR

are relatively low current devices, as compared with some other non-linear resistors.


Like the Thyrite resistor, the forward-conducting diode is capable of distorting an a. c. current waveform and occasionally is used to accentuate harmonics. The requirement is that the diode current magnitude

be such as to operate the diode in its most non-linear region. Thus, the simple series connection of a diode in the plate or grid lead of an oscillator or amplifier can accentuate harmonic content of the current waveform when this type of operation is required. An example, is the distortion of waveform of a standard-


frequency oscillator to produce high-order harmonics for calibration purposes.

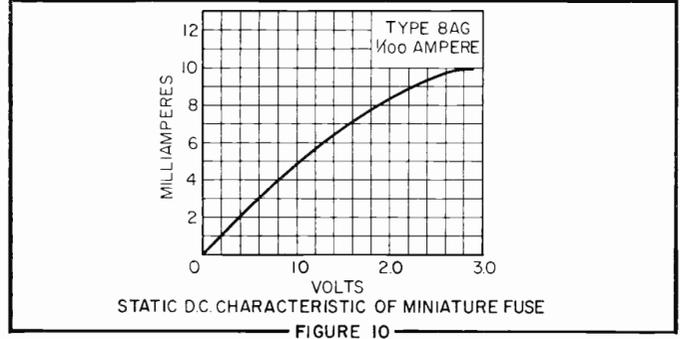**BIBLIOGRAPHY**

- 1—THYRITE. A G. E. RESISTANCE MATERIAL. (Booklet). General Electric Company. Schenectady, N. Y.
- 2—CONDUCTORS WHICH DO NOT OBEY OHM'S LAW. Dunbar. *General Electric Review*, Vol. 24, p. 153.
- 3—THE CALCULATION OF CIRCUITS CONTAINING THYRITE. Brownlee. *General Electric Review*, Vol. 37, p. 175.
- 4—SILICON CARBIDE NON-OHMIC RESISTORS. Ashworth, Needham, and Sillars. *Journal of the Institution of Electrical Engineers*: Vol. 93, No. 69, p. 385.
- 5—APPLICATIONS FOR THYRITE RESISTORS. Rufus P. Turner. *Radio and Television News*, January 1951, p. 50.
- 6—THERMISTORS. (Booklet). Western Electric Company. New York, N. Y.
- 7—PROPERTIES AND USES OF THERMISTORS — THERMALLY SENSITIVE RESISTORS. J. A. Becker, C. B. Green, and G. L. Pearson. *Electrical Engineering*, November 1946.
- 8—THERMISTORS AS COMPONENTS OPEN PRODUCT DESIGN HORIZONS. K. P. Dowell. *Electrical Manufacturing*, August 1948.
- 9—CARBOLOY THERMISTORS. (Booklet). Bulletin No. TH-5 of the Carboloy Department of General Electric Company. Detroit, Michigan.
- 10—GERMANIUM CRYSTAL DIODES. Bulletin EC-36C. Sylvania Electric Products, Inc. New York, N. Y.



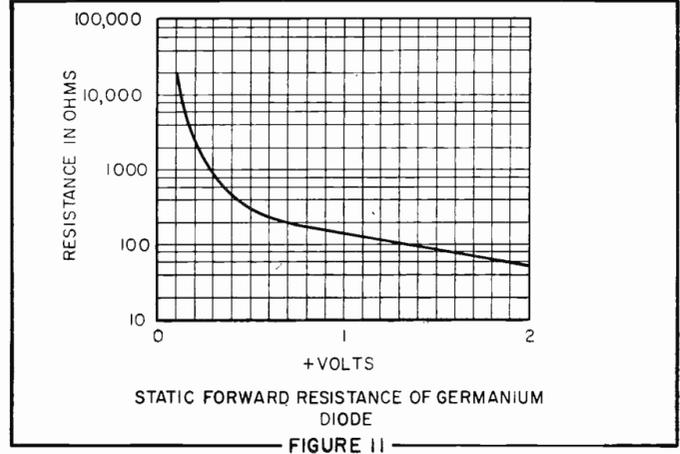STATIC DC CHARACTERISTIC OF MINIATURE FUSE




STATIC FORWARD RESISTANCE OF GERMANIUM DIODE

# Service Plus

FROM THE COMPLETE LINE OF  
**AEROVOX**  
FUNCTION-FITTED

## Components

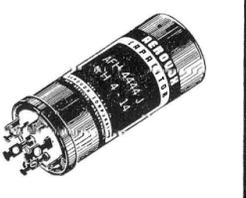

AEROVOX means capacitors of all categories, types, values — electrolytic, paper, plastic tubular, metallized-paper, oil, mica, transmitting, motor-starting, auto-radio, miniature, noise-suppression filters, etc., etc. There's an Aerovox capacitor for every need. Also wire-wound and carbon resistors, and a complete line of filters for all applications.

- LOCAL SALES REPRESENTATIVES at your service...**
- ATLANTA 5, GEORGIA  
1409 Peachtree Street N. E.
  - BOSTON 16, MASSACHUSETTS  
739 Boylston Street
  - CHICAGO 31, ILLINOIS  
6540 Northwest Highway
  - CLEVELAND 14, OHIO  
Room 219 — 2108 Payne Avenue
  - DENVER, COLORADO  
5532 E. Colfax Avenue
  - DETROIT 24, MICHIGAN  
4390 Haverhill Avenue
  - HOBOKEN, NEW JERSEY  
68 Hudson Street
  - HOUSTON 6, TEXAS  
1821 W. Alabama
  - KANSAS CITY, MISSOURI  
406 West 34th Street
  - LOS ANGELES 15, CALIFORNIA  
1169 South Broadway
  - MINNEAPOLIS 16, MINNESOTA  
6110 Excelsior Blvd.
  - NEW HAVEN, CONNECTICUT  
Room 807 — 42 Church Street
  - NEW ORLEANS 22, LOUISIANA  
4108 Clermont Drive
  - NEW YORK CITY, NEW YORK  
from 68 Hudson Street  
Hoboken, New Jersey
  - PITTSBURGH, PENNSYLVANIA  
from 3123 W. 117th Street  
Cleveland, Ohio
  - SAN FRANCISCO 3, CALIFORNIA  
1355 Market Street
  - SEATTLE 1, WASHINGTON  
217 Ninth Avenue North

Need capacitors or resistors? For maintenance work, building special equipment, expediting government orders, as a hobbyist, in industrial activities — regardless?

Then note that Aerovox, through its nation-wide distribution setup, offers you **SERVICE PLUS**, because: You can take Aerovox quality and dependability for granted. No better components are made.


The Aerovox line of capacitors and resistors and filters, is really COMPLETE. You can meet your normal needs every time.

If you are in a big hurry, just remember that your local Aerovox distributor carries a **representative stock virtually at your doorstep**. What's more, he draws on the **outstanding factory stock** for prompt shipment of additional or special items.

Outstanding Aerovox literature — catalogs, folders, bulletins — climaxed by a **free subscription to the Aerovox Research Worker** (ask your distributor about it) — means capacitors and resistors **function-fitted** to latest radio-electronic developments.


So, for **SERVICE PLUS** in obtaining your capacitor and resistor requirements, contact the local Aerovox distributor. Our nearest sales representative is also at your beck and call. Or write us direct.

### WILKOR RESISTORS

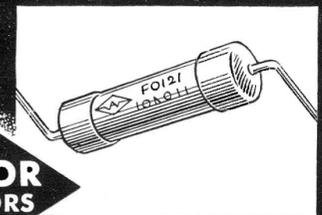

WILKOR means precision-type resistors made with matchless accuracy and intended for circuits calling for the stability of wire-wound resistors with the marked economy of carbon resistors. Widely used in test equipment and laboratory instruments.

### Hi-Q CERAMICS

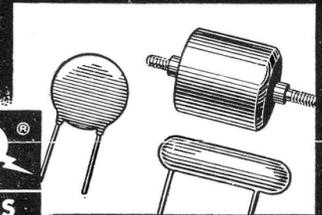

Hi-Q means the outstanding selection of ceramic capacitors and associated components — disks, high-voltage ratings, tubulars, cartwheel or slug, feed-thru, stand-off, etc.



## AEROVOX CORPORATION

NEW BEDFORD, MASS.

Hi-Q DIVISION  
OLEAN, N. Y.

Export: 41 E. 42nd St., New York 17, N. Y. • Cabin: AEROCAP, N. Y. • In Canada: AEROVOX-CANADA LTD., Hamilton, Ont. JOBBER ADDRESS: 720 Belleville Ave., New Bedford, Mass.

Radio Editors of magazines and newspapers will be given permission to reprint in whole or in part, with proper credit to the Aerovox Corporation, the contents of this issue of the Aerovox Research Worker, upon written request.

# The AEROVOX Research Worker

The Aerovox Research Worker is edited and published by the Aerovox Corporation to bring to the Radio Experimenter and Engineer, authoritative, first hand information on capacitors and resistors for electrical and electronic application.

VOL. 23 NO. 10 AND 11

OCT. - NOV., 1953

Subscription By Application Only

## Non-Linear Resistors

By the Engineering Department, Aerovox Corporation

A FEW electrical devices are distinguished by their non-linear current-vs-voltage characteristics of a magnitude sufficiently great to affect performance. Often this phenomenon is a characteristic. For example: non-linearity is observed in the plate characteristic of a vacuum tube under certain operating conditions, the extremity of a diode tube response, iron-cored inductors operated in the region of saturation, and in biased capacitors having special ceramic dielectrics (dielectric amplifiers). These are only a few examples. The non-linearity of certain 2-terminal devices such as resistor also may be employed to modify the operating characteristics of some circuits. These latter *non-linear resistors* do not obey the simple relationship  $R = EI$  of Ohm's Law.

Simple non-linear resistors are used in oscillators, wave shaping networks, voltage regulators, current regulators, constant-output potentiometers and voltage dividers, voltage-selective circuits, amplitude limiters, frequency multipliers, surge suppressors, etc. Their use in electronics is increasing as new requirements for non-linear current-voltage response arise.

This article describes the general characteristics of some common 2-terminal non-linear resistors of several classes. In some instances, as will be seen, these devices have other prime uses and their application as non-linear resistors is secondary. Typical applications will be shown.


### Thyrite

Thyrite resistors were introduced by General Electric Company and were applied in the electric power field some number of years before entering electronics. Thyrite resistors are made of silicon carbide, bound with a filler, then pressed and fired at high temperature. They are fabricated in the form of pigtailed rods (identical to "radio resistors"), discs, washers, and stacks. Small units suitable for electronic applications are supplied up to 10 watts power rating (continuous).

The non-linearity of the Thyrite resistor is expressed by  $I = kE^n$ , where  $I$  is the instantaneous alternating or direct current (amperes),  $E$  the in-

stantaneous applied voltage,  $k$  a constant (amperes at 1 volt), and  $n$  an exponent between 3.5 and 7 governed by the manufacturing process. Figure 1 shows a set of typical Thyrite current-voltage curves for several types of G. E. Thyrite resistors. The curve for a conventional 1-megohm linear resistor is plotted for comparison. From these curves, it may be seen that large current changes result from small applied-voltage changes.

Figure 2 is a plot of resistance vs current for resistor B from Figure 1. Note in Figure 2 that a change of 10,000 to 1 in current flowing through this resistor changes the resistance of the latter approximately 375:1.

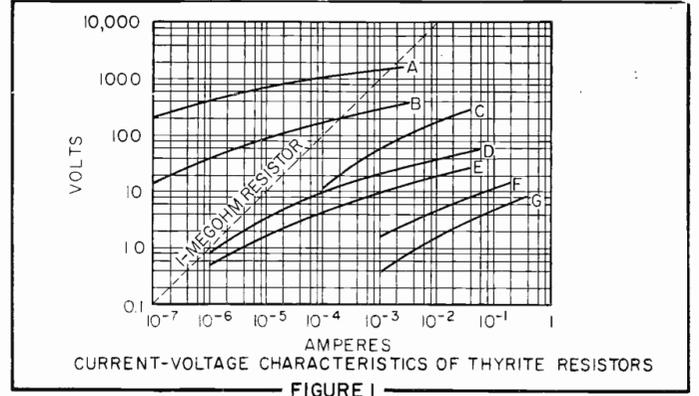

CURRENT-VOLTAGE CHARACTERISTICS OF THYRITE RESISTORS

## AEROVOX - The Sign Of The Complete Capacitor Line

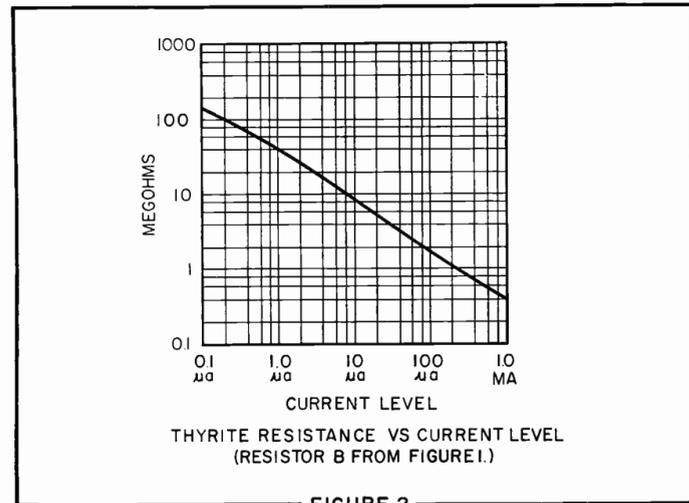


FIGURE 2

Thyrite resistors have the advantage of operating in both a. c. and d. c. circuits. Any rectification effects are negligible. (Figure 3 shows a typical static positive-negative conduction curve). High-frequency a. c. operation of Thyrite is possible, the limiting factor appearing to be capacitance. It should be noted, however, that in a. c. operation the non-linearity of the Thyrite volt-ampere characteristic causes distortion of the

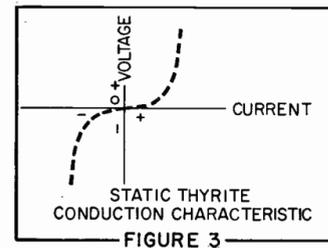


FIGURE 3

current waveform. Figure 4 shows the distorted current wave accompanying a sine wave of applied voltage. Observe that odd-ordered harmonics are prevalent. This phenomenon is utilized in simple frequency multipliers and harmonic accentuators.

The temperature coefficient of Thyrite resistance is negative in sign and varies from  $-0.4$  to  $-0.73$  percent per degree Centigrade in the range  $0$  to  $100^\circ\text{C}$ .

Figure 5 shows several typical circuits utilizing the properties of Thyrite resistors.

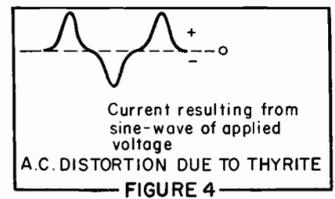


FIGURE 4

Figure 5(D) shows a potentiometer or voltage divider with Thyrite sections. The non-linear E/I characteristic of the Thyrite sections yields a nearly constant output voltage at each tap, although supply and load currents are variable.

For efficient operation of the circuits shown in Figures 5(A) and (D), the Thyrite current must be high with respect to the output load current. In Figures 5(B) and (C), current in resistor R must be high with respect to output load current.


Figure 5(E) shows how a Thyrite resistor can be connected into a circuit to accentuate harmonics and act as a simple frequency multiplier. Alternating current is fed into the circuit and undergoes distortion in passing through the Thyrite. The tuned circuit, LC, is adjusted to the desired multiple frequency. It has been shown already in Figure 4 that odd harmonics are favored by this type of operation. The Thyrite frequency multiplier thus is most practical for tripling, quintupling, etc. The Thyrite resistor is a dissipative element, however, and its insertion into a circuit in the manner shown in Figure 5(E) results in some power loss. In applications where a considerable amount of power is available, the relative simplicity of the Thyrite frequency multiplier can offset its unavoidable power absorption.

**Thermistors**

The thermistor, a product of research by Bell Telephone Laboratories and manufactured by Western Electric Company, is another interesting non-linear resistance device. Its action results from internal heating effects in special materials.

Thermistors basically are thermally-sensitive resistance devices. They are manufactured in the shape of rods, discs, beads, wafers, and flakes and are made of various semiconductor materials. Like Thyrite, the thermistor can be used with either a. c. or d. c.

Figures 6 and 7 show two important response curves describing thermistor action. From Figure 6, it is seen that the voltage drop across the thermistor increases non-linearly and rapidly with current flow up to a point beyond which the rate of increase falls. Finally, a peak is reached and beyond this latter point, the voltage drop decreases with increasing current, displaying negative resistance. An interesting side observation is that this negative-resistance property has been utilized to obtain low-frequency tubeless oscillation and amplification with thermistors.

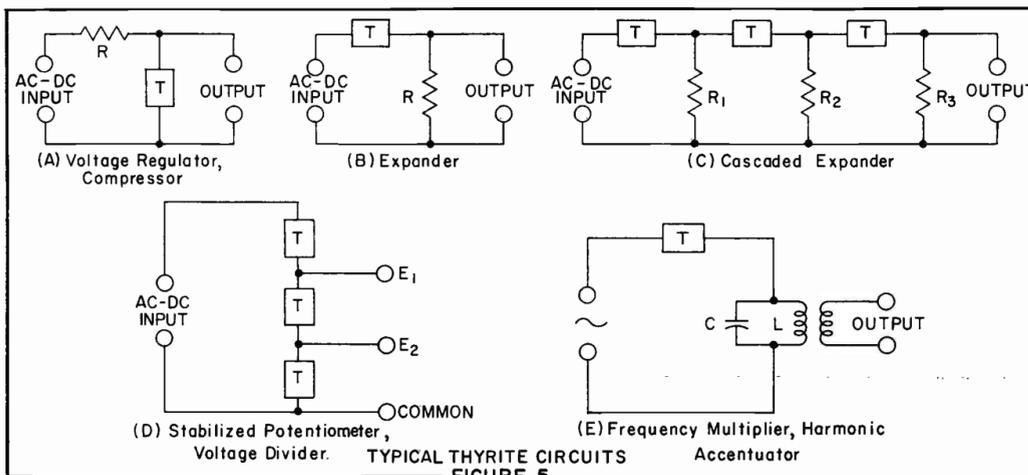

In Figure 7, the plot shows how at a particular applied voltage internal heating causes the magnitude of thermistor current to vary as a function of time. This property has been utilized in various simple time-delay devices.

Figure 8 shows several simple circuits employing thermistors. In all except Figure 8(A), a small current-limiting resistor, r, is indicated. Figure 8(A) is a time-delay d. c. relay based upon the action illustrated by the curve in Figure 7. Some seconds after the switch, S, is closed, the circuit current rises to a value high enough to close the relay. The delay interval depends upon thermistor characteristics and supply voltage level, and can be adjusted to some extent by means of linear series resistance.

Figure 8(B) is the circuit of a regulator for supply-voltage variations and is somewhat similar to the Thyrite voltage regulator. Its operation is based upon the non-linearity of the thermistor which results in small-

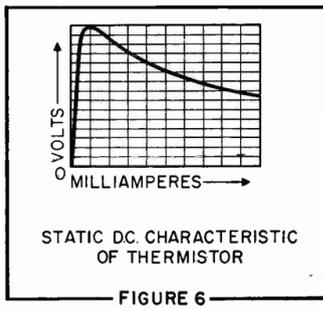


FIGURE 6

er variations in thermistor voltage drop than the fluctuations occurring in supply voltage and current.

Action of the limiter circuit, shown in Figure 8(C), is similar to that of the voltage regulator, amplitude excursions in the input signal being reduced in the output without clipping or slicing action.

Operation of the thermistor expander circuit, Figure 8(D), is the opposite of that of the limiter. The thermistor and load resistor are interchanged in position, output being taken across the resistor. A small signal-voltage change produces a large thermistor current change and a large voltage change across the output resistor.

A voltage division takes place in the circuits shown in Figures 8(B), (C), and (D), as the result of potentiometer action between the thermistor and the linear series resistor. Because of this action, the absolute level of the applied voltage is reduced in the output.

Figure 8(E) shows a lockout-type switching circuit employing thermistors. In each leg of the circuit, r is a load resistor or represents some device, such as a relay, which is to be actuated by current flowing through the associated thermistor. The supply voltage and the value of linear series resistor R are chosen such that this resistor will support the current of only one leg before its voltage drop becomes excessive. When one switch (say, S<sub>1</sub>) is closed, the associated thermistor "breaks down" allowing current to flow through and operate the associated device, r<sub>1</sub>. This lowers the voltage

at the inside of R, so that no other thermistor can "fire." Only after S<sub>1</sub> is opened, can either of the other circuit legs be operated. Operation of any one thermistor leg thus locks out all of the other legs. An arrangement of this type would enable a number of devices having similar volt-ampere characteristics to be connected across a single voltage pair, but with only one device operable at a time.

**Filamentary Devices**

The tungsten-filament incandescent lamp is fairly well known as a non-linear resistor in which current change lags a corresponding change in applied voltage. Up to the point at which heating effects begin to evidence, the filament volt-ampere characteristic is linear, or very nearly so. The non-linear region of lamp-filament resistance has been utilized in voltage-stabilization bridges, simple regulators, and allied devices.

In a common application, the lamp-type resistor is used as an automatic

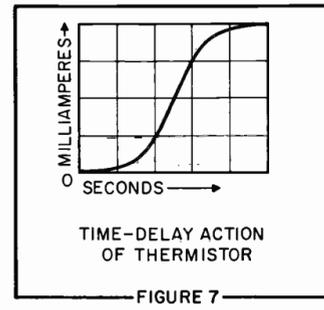


FIGURE 7

regulator of degeneration voltage in low-distortion, RC-tuned oscillators. A typical circuit is shown in Figure 9.

In Figure 9, the lamp (R<sub>2</sub>) is the cathode resistor of the first pentode, V<sub>1</sub>. Feedback current from the output of V<sub>2</sub> flows through capacitor C to the frequency-selective RC network in the grid circuit of V<sub>1</sub>. A portion of this current also flows through resistor R<sub>1</sub> and the lamp, R<sub>2</sub>, establishing a negative feedback voltage across the latter. The lamp resistance is low when the feedback current is small, and is high when this current is large. Thus, strong oscillations result in large amounts of inverse feedback voltage across R<sub>2</sub>, and this degeneration in turn reduces the amplitude. The opposite also is true; at weak oscillation amplitudes; there are lesser amounts of degeneration, and gain through the two-tube circuit automatically rises. The net result is uniform amplitude of oscillation.

Thermistors also are used occasionally in some RC-tuned oscillator circuits to stabilize oscillation amplitude.

Small filamentary, low-current fuses exhibit a type of non-linearity

somewhat similar to that of the tungsten filament. Figure 10 shows the static d. c. volt-ampere characteristic of a sample Type 8AG 10-milliamper Littelfuse. In this instance, response is linear from zero up to the 0.8 v., 4 ma. point. Beyond this, the non-linearity is apparent.

When d. c.-biased to a point within the square-law region of their non-linearity, such fuses often are used as bolometer-type detectors in microwave work. This provides an extremely simple and inexpensive demodulator at frequencies up to many hundreds of megacycles.

**Diode-Type Resistor**

Non-linearity in the forward conduction characteristic of the germanium diode suits this simple component to use as a non-linear resistor in applications within its reverse capabilities. While the reverse-conduction (back-current) characteristic of the diode also is non-linear, it does not in general offer the same possibilities of application that are available with the front conduction.

Figure 11 shows a plot of forward resistance vs applied voltage for a high-conduction-type germanium diode. Here, the polarity of the applied

voltage is such that the anode of the diode is positive. Diodes may be connected in series, parallel, series-parallel, and parallel-series to obtain many attractive non-linear resistance effects.

Various portions of the forward volt-ampere characteristic of the germanium diode exhibit square law, logarithmic, and finally approximately linear relationships between E and I. By operating the diode in a desired one of these regions, the particular corresponding portion of the curve can be utilized to correct or modify the E/I characteristic of another circuit. For example, a linear microammeter may be converted into a square-law instrument by using the forward resistance of the diode as the meter series resistance (multiplier).

Diodes suffer somewhat in comparison with other 2-terminal non-linear resistors because the diode is a rectifier. This limits application in some cases to direct-current use only. However, small a. c. signals may be superimposed upon a d. c. forward bias current applied to the diode, the two currents being so proportioned that the net diode voltage never becomes zero or negative. Diodes also

