

The GENERAL RADIO EXPERIMENTER

VOL. 2 NO. 7

DECEMBER, 1927

The General Radio Experimenter is published each month for the purpose of supplying information of particular interest pertaining to radio apparatus design and application not commonly found in the popular style of radio magazine.



There is no subscription fee connected with the General Radio "Experimenter." To have your name included in our mailing list to receive future copies, simply address a request to the GENERAL RADIO CO., Cambridge, Mass.

DR. HULL JOINS OUR STAFF

An agreement has been made with the Radio Frequency Laboratories of Boonton, New Jersey, whereby on certain problems the facilities of each laboratory will be available to the other. The most important part of the plan, however, is that Dr. Lewis M. Hull will become Director of Research of both organizations, making his headquarters at our laboratories, here at Cambridge.

Dr. Hull is well known in the radio field and particularly for his active participation in the discussion of papers pre-

sented before the New York meetings of the Institute of Radio Engineers. He received his doctor's degree from Harvard University, where he specialized in physics, particularly in radio problems, under the direction of Dr. Pierce. He has taught at the University of Kansas, and was associated for four years with the Bureau of Standards in the capacities of consultant physicist, and then associate physicist. Since the founding of the Radio Frequency Laboratories nearly six years ago, Dr. Hull has been a member of the organization.

Factors Governing the Choice of Power Tubes

By C. T. BURKE, Engineering Department

The proper selection of tubes is of primary importance in the efficient design of an amplifier, that is, in obtaining an amplifier which gives the desired results at least cost, yet the frequent appearance of amplifiers in which a wiser selection would have resulted in a better or more economical amplifier bears testimony to lack of consideration of the factors involved.

Before considering the characteristics of the various tubes it is helpful to review the voltage and power relations in vacuum tubes in general. The following considerations apply to all types of tubes. In Fig. 1 the plate circuit of the tube is shown.

The voltage μE_g appears across the plate circuit as a result of the impressed grid voltage E_g and the amplification factor μ . R_p represents the internal plate impedance of the tube. R_L represents the load in the plate circuit, i. e., the input impedance of a coupling unit or reproducer. R_L is in most cases a reactance rather than a resistance, but it is convenient to consider it as a resistance, and no serious inaccuracies are introduced.

The following relations follow from the laws of electrical circuits.

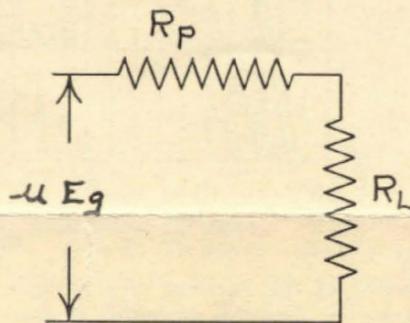


FIG. 1

$$\text{Plate current (alternating) } I_P = \frac{\mu E_g}{R_p + R_L} \quad (1)$$

$$\text{Voltage across } R_L = \mu E_g \frac{R_L}{R_p + R_L} \quad (2)$$

$$\text{Power produced in } R_L = \frac{\mu E_g R_L}{R_p + R_L} \times \frac{\mu E_g}{R_p + R_L} = \frac{\mu^2 E_g^2 R_L}{(R_p + R_L)^2} \quad (3)$$

These equations are fundamental for all vacuum tubes, assuming the tube to be acting on the straight portion of its characteristic, i. e., that plate and grid voltages are properly adjusted.

Since the voltage across R_L is the useful output voltage of the tube, equation (2) summarizes the behavior of the tube as an amplifier. The voltage amplification of the tube and coupling device is seen to depend on three things, the amplification factor of the tube (μ), the plate impedance (R_p) and the load impedance (R_L). Increasing μ or R_L increases the amplification while increasing R_p reduces amplification. The natural conclusion is that a tube with a high μ , low plate impedance and a high load impedance will achieve ideal results. Unfortunately, however, perhaps due to a particularly regrettable oversight on the part of the inventor of the device, amplification factor and plate impedance are not independently variable, but are so tied together in the design of the tube that changes tending to raise the amplification factor also increase the plate impedance. Furthermore, practical considerations limit the impedance of the load. If a resistance coupling device is used, the voltage drop in the resistor limits its value, and cost is a limiting factor when using other forms of coupling devices. The equation does show, however, the desirability of



This may be accomplished with a suitable output coupling device.

We are now in possession of the facts necessary for the proper design of the amplifier, saving excess material and expense as well as preventing bottle necks which limit the capacity of the amplifier at some points.

Three factors are to be considered in designing the amplifier—voltage input at the detector, power output desired, and the power supply available. The importance of the last factor is often overlooked, resulting in the common use of tubes at too low a plate voltage.

Fig. 2 shows the variation of power output with grid voltage (peak) of the standard amplifier tubes. In the vacuum tube data table on page 4 is shown the plate voltage required to maintain emission at the grid voltages specified. It is assumed that a peak signal voltage equal to the grid bias voltage may be used. This is not strictly true, the maximum allowable grid peak voltage being slightly less than the bias voltage. It will be further assumed that the amplification per stage is 0.9μ times the transformer ratio. This relation is approximately correct, provided the coupling device has been properly designed.

It will be seen from the curves of Fig. 2 that when considerable loud-speaker power is required, the power stage cannot operate directly out of the detector. In order to obtain a power output in excess of 10 milliwatts, with any tube, a signal voltage of about 3 is required. The signal voltage in the detector plate circuit is usually 0.1 to 0.5 volts. We will assume 0.3 is an average value in the rest of this discussion. The importance of input voltage is apparent. The importance of the power supply as a limiting factor in the choice of tubes will be demonstrated presently.

Examination of the curves of Fig. 2 shows that at low input voltages the power outputs are bunched closely together. On the basis of the power required for 10 milliwatt output, the tubes range as follows, 112, WD11, 210, 201A, 199, 226, 171 and 120. Up to 10 volts input, the 112 is superior to all other types. In comparing the output of the 210 with that of other tubes, it must be borne in mind that a high plate voltage is required for this tube. The output of the 210 at 180 volts plate is but 145 milliwatts.

The use of the curves can best be demonstrated by discussing a few typical cases.

Case 1.

Receiver—1 stage audio 201A tube 1:2.7 transformer—to add a

power stage—no restrictions on power supply. There is available at the primary of the transformer a signal voltage of $0.3 \times 0.9 \times 8 \times 2.7 = 5.8$

(a) input turns ratio to second stage 1:2.7; $E_g=12$. Inspection of the curves show that a 112 tube will be overloaded at this signal voltage. The 112 tube is so much superior to other types at low input voltages, however, that a greater power output will be obtained if the signal is reduced sufficiently to avoid overloading the 112 than if any other type of tube is substituted.

(b) input turns ratio 1:5.95;
 $E_g=35$

The 210 would be chosen in this case. If the plate supply voltage had been limited, the 171, or perhaps two 171's in parallel or push-pull would be used.

Case 2. Battery operated receiver.

3-volt filament—135 volts plate
1st. stage 1:2.7 transformer

Voltage at primary of second stage

$$0.3 \times 0.9 \times 6 \times 2.7 = 4.4$$

Voltage on tube grid (6:1 transformers) 26 volts.

The battery requirements limits the selection to the 120 tube which would be overloaded, requiring either a reduction in signal voltage or the use of a lower transformer ratio.

Suppose it is desired to operate a separate power stage, with A. C. filament supply permitting the use of a 5-volt tube. If there is no limit to the plate voltage, a 210 would be used. This is another case where the parallel or push-pull connection could be used to advantage, to avoid high plate voltage.

Case 3. Receiver—detector only. It is desired to design an amplifier to supply the full output of a 210 type tube.

The curve shows the grid swing required to be 35 volts.

Assuming 0.3 volts in the detector plate:

$$\text{Required gain} = \frac{35}{.3} = 117$$

(between detector and the grid of the power tube).

Examine the following possibilities.

1. 1:2.7 transformer—201A—
1:2.7 transformer; gain=53
2. 1:2.7 transformer—201A—
1:6 transformer; gain=118
3. Double impedance—201A—
Double impedance—201A—
Double impedance; gain=49

4. Double impedance—201A—
Double impedance—201A—
1:2.7 transformer; gain=147
5. Double impedance—201A—
Double impedance—201A—
6:1 transformer; gain=330

It is apparent that neither the arrangement 1, nor 3 would be satisfactory. Arrangement No. 2 would just "get by," but would not be desirable as it permits no factor of safety. Arrangement No. 4 would be satisfactory, but some might prefer No. 5 which could be worked with lower signal voltages in the detector.

New General Radio Apparatus

TYPE 446 VOLTAGE DIVIDER

The experimenter or home set builder who is building a plate supply unit requires an adjustable resistance, in order to get the correct plate voltages for the several tubes in his receiving set. In the construction of the General Radio Type 445 Plate Supply Unit, a similar requirement existed, and to meet it, a separate wire wound resistance card with four adjustable sliders was developed. There have been so many requests to supply this card separately that we are now prepared to release it under the title of Type 446 Voltage Divider. The list price is \$4.00.

The unit is wound in two sections, the larger section having a resistance of 15,000 ohms, and being provided with three adjustable sliders. This section is used for the plate supply. The second section has a resistance of 1500 ohms, and is provided with a single adjustable slider. This section is used for C biasing. The card, while rugged, is thin so as to keep inductance effects at a minimum. Convenient mounting brackets are provided.

ADJUSTABLE CENTER TAP RESISTANCE

While a resistance to go across the filament of the alternating current tubes usually requires a tap at its exact center, conditions often arise, due to unbalancing, when it is desirable to have the tap slightly off center.

To meet this condition, we have developed a center tap resistance similar to the Type 439, except that the tap is made by means of an adjustable slider. This enables the tap to be placed at the neutral point, thus reducing hum to a minimum.

This new unit, listing for 75c, and designated as Type 437, is now available for distribution.



THE GENERAL RADIO EXPERIMENTER

VACUUM TUBE DATA TABLE

TYPE	FILAMENT		B VOLTS	C VOLTS	PLATE CURRENT MILLS	PLATE IMP. OHMS	MUT. COND. M.MHOS	AMP. FACTOR	PEAK EMISSION MBS.	OUTPUT MILLIWATTS		CAPACITY COLD M.M.F.	MAX. DIA. INCHES	MAX. HEIGHT INCHES
	VOLTS	AMPS								UNDIST.	AS OSC.			
WD 11	1.1	.25	22	0	.4	22000	260	6	25	6				
WD 12			45	-1.5	1.1	18000	345	6.2		30	G-F 6			
CX 11			67	-3	1.8	17000	365	6.2		85	G-P 5.5			
CX 12			90	-4.5	2.6	16000	390	6.2		12	P-F 7.5	1 1/16"	4 1/16"	
\$2.50														
UX 199	3.3	.063	22	0	.4	26000	230	5.9	9	6				
CX 199			45	-1.5	1	19500	320	6.25		30	G-F 3.6			
UV 199			67	-3	1.7	16500	380	6.25		80	G-P 3.5			
CV 199			90	-4.5	2.5	15000	415	6.25		7.5	P-F 4.5	1 1/16"	3 1/2"	
			135							15				
			90	-7.5	1.3	19000	330	6.25		80				
\$2.25														
UX 120	3.3	.130	22	0	1	10000	320	3.2	24	16	G-F 4.5			
CX 120			45	4	2	8500	390	3.3		60	G-P 5.4			
			67	9	3	8000	410	3.3		140	P-F 4.4	1 1/16"	4 1/8"	
			90	16.5	3.2	7700	430	3.3		200				
			135	22.5	7	6600	500	3.3		105				
			135	27	5.5	7500	430	3.2		110				
\$2.50														
UX 201A	5	.25	22	0	.5	26000	325	8.4	45	8	G-F 5.8			
			45	1.5	.9	18500	460	8.4		28	G-P 10.1			
			67	3	1.5	14000	600	8.4		70	P-F 6.1	1 1/16"	4 1/16"	
			90	4.5	2	12000	710	8.5		15				
			135	9	2.5	11000	775	8.5		50				
			180	13	3	9000	940	8.5		230				
\$2.00														
UX 112	5	.5	22	0	1.1	14500	550	8	150	17	G-F 9			
			45								G-P 11	1 1/16"	4 1/16"	
			67								P-F 7.5			
			90	-6	2.4	8800	890	7.9		40				
			135	-9	6	5000	1640	8.2		120				
			157	-10.5	8	4800	1700	8.2		195				
\$4.50														
UX 171	5	.5	22	0	4	3500	850	3	80	60	G-F 6.8			
			45	-5	6						G-P 9.5	1 1/16"	4 1/16"	
			67	-12	7					320	P-F 6.5			
			90	-16.5	11	2500	1200	3		110				
			135	-27	16	2200	1320	2.9		350				
			180	-40.5	20	2100	1380	2.9		700				
\$4.50														
UX 210	6	1.1	90	-4.5	3	9700	775	7.5	500	18	G-F 7			
			135	-9	5	8000	940	7.5		64	G-P 8			
			180	-10	7	7000	1070	7.5		145	P-F 7	2 1/16"	5 1/16"	
	7.5	1.25	250	-18	12	5600	1340	7.5		340				
			350	-25	18	5100	1460	7.6		950				
			425	-35	20	5000	1540	7.7		1500				
\$9.00														
UX 222 (RADIO)	3.3	.132	135	1.5	1.5	850,000	350	300				1 1/16"	5 1/16"	
UX 222 (AUDIO)	3.3	.132	180	1.5	.3	150,000	400	60				1 1/16"	5 1/16"	
UX 200A	5	.25	22		1.2	35000	570	20				1 1/16"	4 1/16"	
			45		1.5	30000	670	20						
\$4.00														
N (215A)	1	.25									G-F 4.4			
			67	-6	1	20000	300	6		8	G-P 4.2	1/16"	2 1/16"	
										40	P-F 3.8			
V (1020)	2	.97										2 1/16"	4 1/16"	
			130	-1.5	.75	60000	500	30		4.2				
L (216A)	5-6	1										2 1/16"	4 1/16"	
			130	-9	8	6000	980	5.9		60				
E (2050)	4.5	1.6										2 1/16"	4 1/16"	
			350	-22.5	33	3500	2000	7		890				
UX 226	1.5	1.05	90	6	3.5	9400	875	8.2		20				
			135	9	6	7400	1100	8.2		70				
			180	13.5	7.5	7000	1170	8.2		160				
UV 227	2.5	1.75	45		2	10,000	800	8				1 1/16"	4 1/16"	
			90		7	8,000	1,000	8						
UX 240	5.0	.25	135	1.5	.2	150,000	200	.30				1 1/16"	4 1/16"	
			180	3	.2	150,000	200	.30						
UX 280	FULL-WAVE RECTIFIER				FIL. TERM. VOLTS 5 V FIL. CURRENT 2 A A.C. PLATE VOLTS 300 V (MAX. PER PLATE)				R.M.S.	MAX. D.C. OUTPUT CURRENT Both Plates 125 M.A.			2 1/16"	5 1/16"
UX 281	HALF-WAVE RECTIFIER				FIL. TERM. VOLTS 7.5 V FIL. CURRENT 1.25 A A.C. PLATE VOLTS 750 V (MAXIMUM)				R.M.S.	D.C. OUTPUT CURRENT RECOMMENDED 65 M.A. MAXIMUM 110 M.A.			2 1/16"	6 1/16"

Note: Except for half ampere filament, UX-112 and UX-171 characteristics are