

SEPTEMBER 1968

73¢ Yet

73

AMATEUR RADIO



JIM
WAGNER

73 MAGAZINE

September 1968
Vol. XLVII No. 9

STAFF

Wayne Green W2NSD/1
Publisher

Kayla Bloom W1EMV
Editor

Jim Ashe W2DXH/1
Tech. Editor

Contents

6	Going VHF in the Mobile	W9HBF
	A veteran VHFer tells all	
14	Communicator Reborn	W6HGX
	Making the most of the Gooney Box	
16	432 MHz Amplifiers	W6AJF
	4 designs for this band	
20	Quick Converters	W9NLT
	Using TV tuner	
27	So You Think You're on Frequency	K6MVH
30	Parallel-T Network	Kyle
	Rejection of unwanted signals	
32	Starting Off On VHF	WA1GEK
	What you need to get off the ground	
34	Learning the Radio Code	W2DXH
	If you are over 30	
38	Sarah Awards for the Amateurs	Staff
	Send your nominations now	
42	I296 - 1968	K2TKN
	Who's doing what on this band	
44	VK3ATN Moonbounce Rhombic	W2NSD
	Australia to N.J. on 2 Meters	
48	K2US: 1968 Ham Expo	WB2DLW
	Public Relations for the amateurs	
52	6 Meter Exciter	W1KNI
	Heterodyne VFO rig	
59	Appliance Ops Turn Page	W1WAI
	A clever bench for the builder	
60	Reviewing the Heath SB 110A	WA2ZSA
	A 6 meter transceiver	
62	6 Meter Transceiver	WA2AJW
	A simple home-brew rig	
70	2 Sidebands on Two	W4KAE
	Converting the Twoer for DSB	
74	Advance Class License Course	Staff
	Part IV—More on transmitters	
86	Care and Feeding of a Ham Club	W5NQQ
	Part III—Have a Party	

Departments

Editorial Liberties	2	Propagation	105
De W2NSD	4	Letters	106
TAG	96	Caveat Emptor	108
WTW Report	100	Ad Index	112

73 Magazine is published by 73, Inc., Peterborough, N.H. 03458. Subscription rate: \$12.00 for Three years, \$6.00 for one year. Second Class Postage paid at Peterborough, New Hampshire, and at additional mailing offices. Printed at Pontiac, Illinois, U.S. Entire contents copyright 1968 by 73, Inc. Postmasters, please send form 3579 to 73 Magazine, Peterborough, New Hampshire 03458.
Stop reading this fine print. Look at page 92 and go out and sell subscriptions.

Editorial Liberties

I would like to take this opportunity to introduce 73's new Technical Editor, Jim Ashe W2DXH. Those of you who are among 73's Fandom will recognize Jim from his many fine articles in the past few years. I consider myself fortunate that Jim agreed to come to work for us, where he will be underpaid, overworked, and rewarded mainly by knowing that he is helping to maintain (would you believe improve?) 73's standards for technical articles. He's only been here two days as of this writing, and he has pitched in like a trooper and is taking much of the load off my shoulders and mind. It's nice to have a man around the shop! Look for great things!

Hardly a day goes by when I don't receive at least one letter from an amateur saying that he has given up CQ and QST and only subscribes to 73. This is flattering, but . . . ! I'm not opposed to your dropping your subscription to CQ, but when you drop your subscription to QST it means you are no longer a member of the *only* organized body devoted to amateur radio and its purposes.

ARRL may not be the best, but, let's face it, ARRL is all we have. If you are unhappy with what the League is doing (or not doing) you won't accomplish anything by resigning any more than you will change the Government by refusing to vote. If you don't like what the League is doing, this is the time to speak. Elections for Division Directors and Vice Directors are taking place in the following Divisions: Central, Hudson, New England, Northwestern, Roanoke, Rocky Mountain, Southwestern and West Gulf. If your director has not done what you feel is to the betterment of ham radio, get out and do something to change it rather than resign.

The rules of the game are roughly as follows. To be a Director or Vice Director you must have been a member of ARRL for five consecutive years without a lapse. You must have a nominating petition signed by 10 League members to HQ by noon on September 20, 1968. You must hold a General Class (or higher) License. And, you should be prepared to work hard to improve the deplorable conditions which now prevail.

If you are not in a position to run for the office, you might take a close look at the

man who is opposing the incumbent in your Division. You might just find that you have a pretty good guy who is willing to work hard to give ham radio the necessary boost.

I certainly don't want to stir up the late AM-SSB quarrel again. I work SSB/CW/AM in that order of preference (when I have time to be on the air at all) and feel each has its place in our hobby. However, there is AM and there is AM with so-called "Super Modulation." The lead article in July CQ on "Modulation Unlimited" seems to me to be a matter of irresponsible editing. That article was in the files at 73 when I came to work here last year. We had paid for it, but the check had never been cashed. I read it and thought what a wonderful article it was for about 15 years ago. It contained nothing new. 73 had already printed a similar article in Feb., 1963. The drafting had been done, the article was already in type and ready for print, but after a close scrutiny of the signal in question on the air, I was convinced that this was definitely not "state of the art" and left it in the file. On the request of W3PHL's attorney, the article was returned to him a couple of months ago. CQ then printed it in their July issue. I'm glad the egg is on Dick Ross' face, not mine. From the information I have been able to gather, the author has had his license suspended for, among other things, excessive broadness of signal. When a signal takes out over 15 kHz on a fairly sharp receiver, it has no justification in my book. Work whatever mode pleases you, but keep it clean and sharp.

A note to prospective authors. We are still eager to read your manuscripts and hope you will write about what you are doing. The August issue contained an article by Ken Sessions K6MVH entitled "Hamwriting" which should act as a guide to good writing. To assist further, pages 94-95 in this issue contain two charts giving all the electronic symbols used on schematics and the abbreviations used both on schematics and in the text. I would like to suggest that you keep these charts handy for reference when writing. You see, I am basically lazy and the fewer corrections I have to make to your manuscript, the better I like it.

. . . Kayla W1EMV

The Model 6000 Modular Frequency Meter will measure frequencies 10 KHz to 600 MHz with .000125% accuracy. Special plug-in modules allow the instrument to be used as an audio frequency meter from 500 Hz to 20 KHz full scale and in addition to be used as a dc voltmeter (10,000 ohms/volt).


The wide variety of plug-in oscillator accessories and range modules makes the Model 6000 adaptable to a number of jobs in the field and in the laboratory. Portable, battery operated with rechargeable batteries.

Model 6000 with 601A charger, less plug-in modules.....\$195.00

INTERNATIONAL MODEL 6000 FREQUENCY METER

measures frequencies 10 khz to 600 mhz with accuracy as close as .000125%

CHARGER

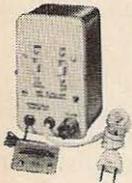


Range Modules (Mixers)
\$25.00 to \$45.00 each

Oscillator Modules
(Crystal Controlled For
Frequency Measurement)
\$30.00 to \$90.00 each


Special Modules
Audio Frequency\$45.00
DC Voltmeter..... 25.00

where
accuracy
counts!

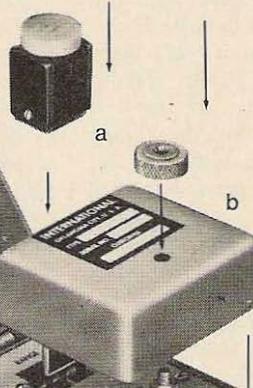

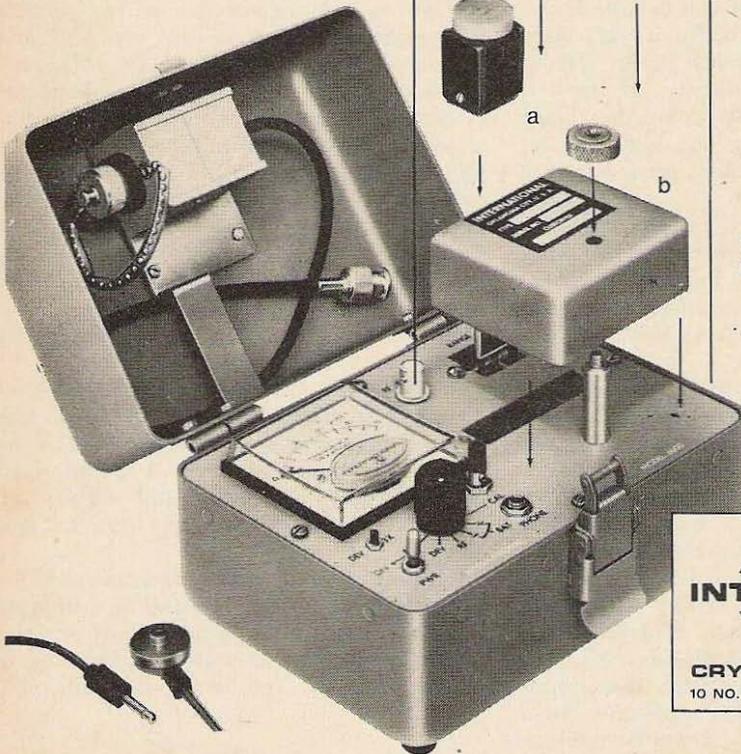- a. Range Modules
- b. Oscillator Modules

... For complete information
write International today.



de W2NSD/1

Miller Confesses!

When word came that Miller had admitted the St. Peter and Paul Rocks hoax expedition I was relieved, but not really surprised. I was aware of a good deal of the evidence that the League had gathered against him in this and about twenty other of his operations. The PYØXA trip was of critical importance though since it was the *only* one where he had a surviving accomplice. I suspect that when Miller found that his accomplice was not about to chance imprisonment by lying under oath that he was trapped into confessing.

Where was he at the time he was claiming to be operating from the Rocks? Well, his license was running out and he didn't have time to get all the way down there to the middle of the Atlantic Ocean off Brazil, so he operated just off the coast of Venezuela, probably near Trinidad on board a ship and a good 1800 miles from St. Peter and Paul.

Miller has withdrawn his suit against the League and Huntoon and I expect that the suit against 73 and myself will be withdrawn shortly. Don't feel too badly if you were taken in by Miller and his stories. He is most convincing and audacious. If there is any rational reason for his doing the things he has done and acting the way he has acted, none of us intimately involved have been able to figure it out.

I understand that Miller's explanations for the other questioned expeditions were vague, contradictory and evasive. Proof of anything? Sorry, but most of the records have been lost or stolen. Passport? Lost that too, just recently.

The League would certainly seem, on the strength of the testimony given, to have adequate grounds for deleting credit for about twenty of Miller's operations. Pressure from DXCC members will probably force them to accept all but the most outrageous.

Where does this hoax confession leave CQ and their seemingly fictional series by Miller. How about the Miller DX book, promised about a year ago? Will CQ bring this out in the face of his disgrace? CQ has backed Miller to the hilt with their reputation . . . where does his confession leave them? Will they give us a public apology

for the libelous attack on me they published for Miller?

If you have any friends who stopped reading 73 because I was writing bad things about their hero, you might pass along the word.

UFO NET SCHEDULE

Wednesdays 0200 GMT 14,300
Thursdays 0200 GMT 3950

Net Controls Needed

The UFO Reporting Net has been growing larger every week and now is much too large to permit all of the interested stations to check in. The net has been meeting on 14.3 MHz every Wednesday night at 0200 GMT.

Jim Sipprell K2HYQ has kindly consented to take on the organization of net controls for nightly operation of the net. The frequency will continue at 14.300 MHz and the time at 0200 GMT. If you are interested in acting as a net control one or two nights a week please drop a note to Jim. You should have a good signal and be dependable. Jim will pick out two for each night that are widely enough separated so they should be able to hear all checkins. We've found that we can get just about everyone with one control up east and one in the south . . . or one in the west and one in the south, etc.

If you can't be sure of being available on any particular night you should call into the net whenever you can make it. The net control stations will keep you informed on how things are going and will be interested in any reports you have to pass along.

To participate in the UFO Reporting Net you should set up communications with your local agencies that might get reports of sightings or would be interested in knowing of nearby sightings. You should talk with your

Turn to page 114

ROHN, as the largest tower manufacturer in the United States, provides outstanding commercial quality equipment for amateurs. We're best known

in this field for our crank-up, fold-over and #25G towers. Like all our big commercial towers, they're hot-dipped galvanized after fabrication according to EIA specifications. We also make commercial hardware and accessories amateurs use, too, and it's all designed with an understanding of your needs, particularly in the area of quality. And don't overlook our constant search for new ideas, processes and products — just for you. Keep an eye out for the ROHN name. It's well worth your while.

ROHN® THE QUALITY PEOPLE

Home Office — Factory
P.O. Box 2000, Peoria, Ill., U.S.A. 61601
Phone 309-637-8416 TWX 309-697-1488


ROHN®

Systems Office —
Box 877, Richardson, Texas 75080
Phone 214-AD1-3481

Western Office
310 Quincy Street, Reno, Nevada 89502
Phone 702-322-9300

Eastern Office
P.O. Box 2101
Hanover, Mass. 02339
Phone 617-826-2511

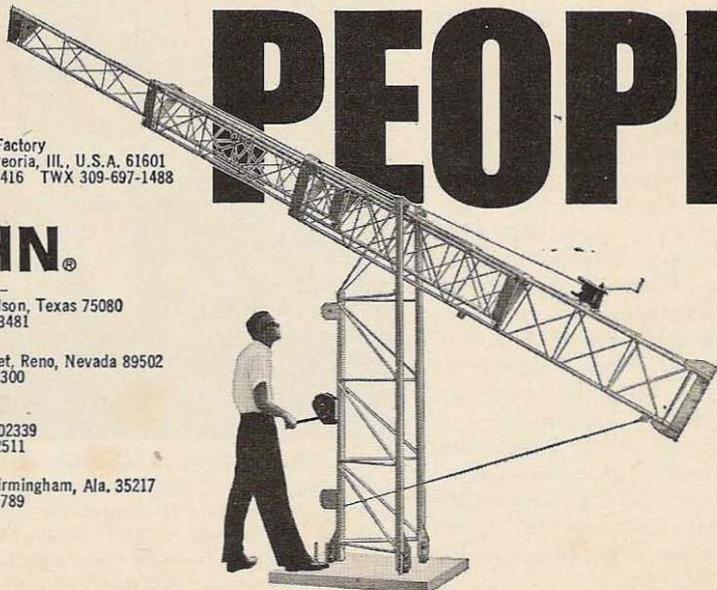Southern Office
P.O. Box 6537, Birmingham, Ala. 35217
Phone 205-841-1789



Going VHF - In The Mobile


Robert M. Brown W9HBF
5611 Middaugh Ave.
Downers Grove, Ill. 60515

VHF mobileers claim it's the greatest — if you know what you're doing. This article outlines mobiling's role on the bands above 50 MHz, what you can expect, and some useful tips from the experts.

To the reader uninitiated in the fine art of exploring VHF from the auto, above 50 MHz mobiling may sound like a total waste of time. Indeed, there are thousands of low-frequency hecklers who'll tell you that (1) ignition noise is too severe, or (2) that there is never anyone on in your area, or (3) you'll be lucky if you can work out of town. The more experienced reader may claim just the opposite, if he answers these charges at all. Actually the truth lies somewhere between these two attitudes, for mobiling at these frequencies is altogether unlike operation in any other region of the amateur spectrum.

Where it all started

When VHF'ing was in its infancy scarcely twenty-five years ago, a few thoughtful tinkers gathered together in various sections of the country to ponder a problem. How could these "experimentalist" frequencies be effectively employed for ham communications? Numerous tests had been conducted on VHF, but they had always been point-to-point affairs, and always prearranged. Results, published periodically in *QST*, substantiated the theory that 5 meters could afford amateurs something truly different, provided enough interest could be aroused. What these ambitious amateurs undertook was the construction of crude mobile rigs, many using single-tube crystal controlled transmitters and super regenerative receivers—others used tuneable converters and modulated oscillators, for operation on this "unexplored" band. Well documented in ham journals is the fact that these famed 5-meter mobiles were directly responsible for VHF coming into its own as an essential yet independent adjunct to the hobby.

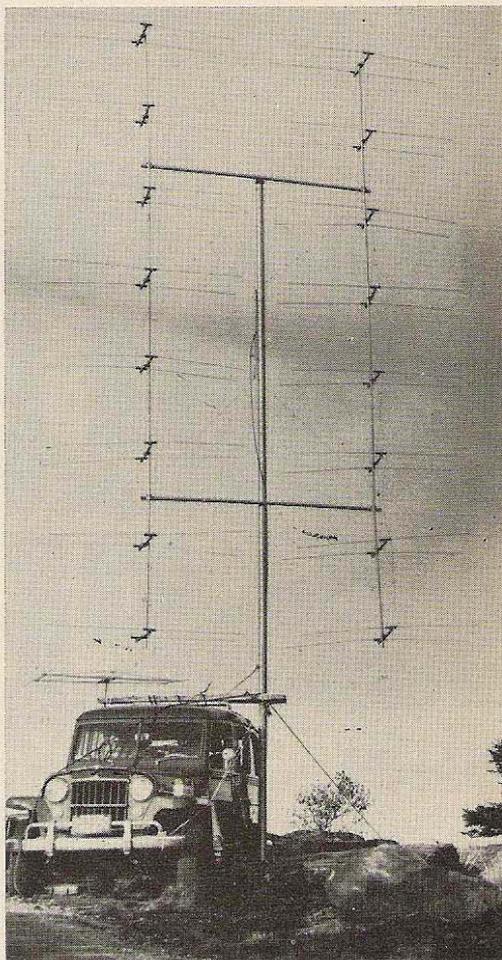

For K2UYH, a frequent extension of mobiling is hilltopping, which is where our camera caught him recently. Antenna is a 32-element 144 MHz collinear, while at left (barely visible) is his 3-element six meter collapsible. Normally halo antennas are employed for in-motion QSO's.



Night time transmitter hunts are a favorite indulgence for anyone equipped for six or two meters during the summer. This photo was snapped during a Portland, Ore., hunt a few years back. (Hidden transmitter is 10 feet to the right of the antenna, well camouflaged in foliage).

Soon more sophisticated equipment began to appear, with superheterodyne receivers and higher-powered transmitters. The magazines encouraged the trend by publishing new circuits as they were developed.

By the early fifties the 6-meter band had emerged as a full-fledged extension of 10 meters, while war surplus gear put operators on 2 inexpensively. Civil Defense, no longer content to see all this going to waste, shifted its entire emphasis from 28 to 144 MHz. Literally thousands of cars sprouted whips, many equipped inside with Conset Communicators purchased by CD. In 1952 the FCC passed an amendment permitting Technician Class ticket holders operation on six. Overnight signals appeared, bringing the 50 MHz band from relative obscurity to a mobileer's holiday. The "Mobile Sixers" was founded in Philadelphia while similar groups organized simultaneously from coast to coast.

What is significant about this recent history is that without mobile participation and pioneering, these two VHF bands could hardly be what they are today. Additionally, the very highs developed in a reverse fash-


ion from the lower frequencies, where base stations were initially what populated the ham bands. Why this extraordinary enthusiasm for six and two meter mobiling?

Perhaps because it is different.

144 MHz techniques

Because VHF mobiling is something unique in our hobby, to enjoy maximum success requires a bit of first-hand investigation. As many know only too well, you can't just put together a set that tunes 145 to 146 MHz, hook into the car radio antenna and expect results. Nor for that matter can you expect to install a vertical radiator on the bumper and start calling CQ on 50.78 MHz. Unless, perhaps, you live in northern Vermont.

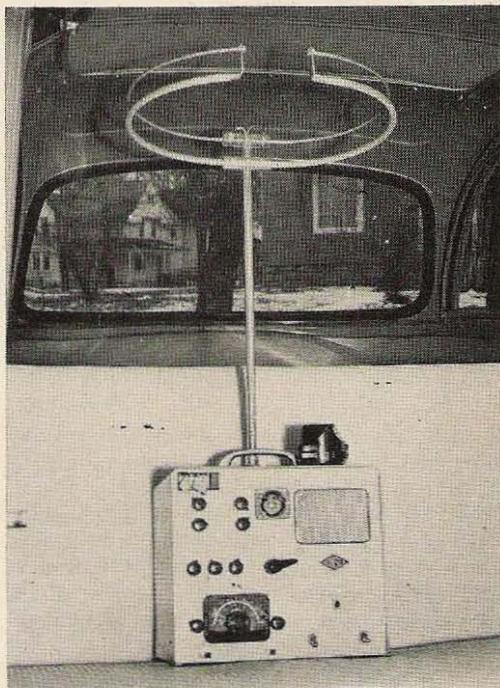At two meters, particularly, it is to your advantage to check local operating habits. The mobiles with the greatest number of QSO's are often those who belong to an on-the-air club or emergency network such as AREC. Why? Because base stations in many sectors are horizontally polarized, while mobile enthusiasts stick to their whips. To reach a happy medium necessitates



Though it might not look it, Arlo Nease, KN9HIH, claims he does quite well with his 144 MHz halo inside the Isetta.



A crowd always gathers around W2FNM's fire-engine-red Model A, "equipped for the works" (160 through 2 meters).

getting together with an active local and finding out his views on the subject.

Mobiling here can afford numerous short-range contacts providing a few basic facts are kept in mind. Most importantly, nearly all two meter stations are still crystal controlled. And they don't tune the entire band after each CQ. For you, it might seem like a small feat, but for a well-equipped base station it can be a physical impossibility to tune 144 to 148 MHz in anything short of ten minutes. For this reason it is a good idea to have several crystals handy if you're at 144.4 and he's tuning only "145 to 146."

Although 95% of two meter stations use AM, certain regions are populated only by hams using converted Motorolas, Links, GE's, etc. (all FM). By the same token the vertical/horizontal observation mentioned above can frequently be reversed! And to add to the confusion is the fact that the most-used frequencies in the band may vary from one state to another.

Dependent on whether you reside in a metropolitan or rural area, you can sometimes do quite well with super regenerative receivers like the still-popular Heath Twoer.

While it may not be a dyed-in-the-wool v.h.f. DX'ers cup of tea, the super regen remains one of the most sensitive designs available, providing excellent reception in low-activity regions.

The "real" 2-meter mobile addict uses three antennas: a 19" whip, a single-element halo, and a collapsible 5-element yagi. Generally the whip and halo are interchangeable at the rig, while the yagi is for hill-topping. The more typical setup, however, is simply either the halo or whip.

At 144 MHz, height is an all-important factor. A good technique to employ when seeking a QSO is to begin the CQ while driving up an incline, such as the side of a hill or bridge ramp. Time your transmission so that your sign-off coincides with the peak of the hill or bridge. In reality this method inflates your signal several "S" units, just enough to catch another station. Once in contact, you'll find you can hold it satisfactorily even though you lose elevation. Since the other station invariably has a directional antenna, *he* does the work.

Another "must", while we're talking about narrow beamwidth antennas, is al-



Here's a shot of the author (about four cars ago) making comparison checks between a Clegg Thor 6 prototype and a 99'er. A 50 MHz linear amplifier in the trunk, remotely controlled from the dash, aided immeasurably in shortening the life-span of this '53 Chevy.

ways to give your location. Nothing is more frustrating than to hear a mobile calling CQ, not know his QTH, and begin turning the antenna only to have him go off while you have him in a null. A good rule-of-



Although mobile-in-motion QSO's are understandably short-lived, WA2VOI really racks up on mountaintops during VHF contests.

thumb here is that one location report with each identification will buy you what it would take three CQ's to secure otherwise.

Obstructions can be severely damaging to a 144 MHz mobile signal, since most *rf* reaches the base receiver by direct ground-wave. Don't call CQ while trapped in downtown traffic between skyscrapers, or under an elevation. Unlike the lower frequencies, your S7 signal can virtually disappear in a matter of seconds. If you find that you'll be losing elevation soon, or that you'll be stuck under an overpass at a light, inform the other operator. He'll be only too happy to either kick in his preamp or stand by until you are in the clear again.

Flutter can be annoying at 2 meters if not approached properly. Rapid QSB can result from cross polarization (a common offender) and/or your fast-moving vehicle. But the most little-known cause that can be remedied easily is simply your car's position. Since wavelengths at two meters can be measured in inches, your proximity to metallic objects and buildings sharply affect your signal. If you are stopped and in QSO, inch the car slowly backwards or forwards while listening to the receiver. Always park exactly where the signal peaks if at all possible. Use this technique at stoplights also by prematurely slowing. When you see the signal begin to rise on the meter, take her forward by the inch. You may find this changes your driving habits considerably, but it is well worth the effort.

In open country two meters is loads of

fun. By closely observing the "S" meter, you'll experience a phenomena seldom found at any other frequency. Buried pipelines, hidden rock formations and underground streams often inflate incoming and outgoing signals by as much as 45 db. The trick is finding the exact spot. When located, you can park, call CQ and wait for the pile-up. This is almost as much fun as mountaintopping, and even more when you inform your captive that you are 40 miles away, running 3 watts and practically at sea level.

The formula is all in keeping the receiver "on" whenever you take a drive. If you are out with the wife and kiddies, keep a watchful eye on the meter even though the volume is turned down. Make a mental note of your location should you see any sharp increase in signal strength that disappears rapidly as you pass. Then, when you are out alone, return to that spot.

Can you get real DX on two without heading for the hills? Certainly, but it takes some doing. By employing the same method outlined above, watch for sudden *and sustained* increases in signal strength in your high-speed driving. For example, a drive on the Pennsylvania Turnpike might net nothing, or the time of your life. It's worth keeping the rig on to find out. Should you get "caught" in a situation where you notice strong signals from an area you know to be unusually far away, pull over to the side and attempt your QSO. Don't continue on your way, for you've accidentally fallen into a VHF phenomena known as the "tropo duct." Like a pipeline, 144 MHz mobile signals can be "ducted" into certain towns up to 200 miles away for periods of time lasting only a few minutes to two hours. The peculiar thing about this condition is that stations five miles away won't hear a peep.

One final tip: If at all possible, install a SWR bridge in the feedline and mount it under the dash with your transmitter. Two meters is the only popular ham band where you'll be making a 2 MHz frequency jumps as a matter of course, and you'd be surprised what that will do to your standing waves! Cut the antenna for the middle of *your* operating range and arrange a tuning device for emergencies. More 2E26's have been blown by two meter mobileers than you'd care to learn about.

50 MHz techniques


On six, the old "there's-something-for-everyone" adage is a fact, if you are prepared for it. Fifty megahertz mobiling has been termed a cross between 10 and 2 meters. Don't you believe a word of it.

In reality six meter monitoring can be compared with no other. It's characteristics resemble no known amateur band; nor do its problems. Perhaps the most pressing annoyance is ignition noise, the cures for which have appeared in all major ham publications. Though not as severe as on the lower frequencies, this problem must nearly always be dealt with before you'll enjoy the true excitement and rewards of six meters in the car. Once this is out of the way, you'll want to spend 20 minutes with a coil of #12 wire and a trimmer capacitor to place a series tuned circuit across your generator. Careful adjustment with an eye on the "S" meter and the engine at full rev will null out your generator whine and you are ready for action.

Unlike two meters, you *will* need more than a few crystals, unless you have a well-regulated 8 MHz VFO handy. Putting yourself on 50.106 can be a tragedy or a blessing in disguise, depending on the weather, time of day and local whims. Most mobileers prefer the 50.200 to 50.500 range, although there seems to be an unwritten philosophy which says that the first operator on 50.250 won't be lonesome. But even this won't help you on a Saturday night or during a band opening, at which time you had better be either on a very high mountain or above 50.750 MHz. Confusing? The best is yet to come.

"Normal groundwave conditions" is a misnomer; one day you will get an S7 report from across the river, the next day an S5. Though your customary working radius is greater than on 144 MHz, it isn't necessarily as dependable. A multitude of variables such as humidity and temperature can drastically alter your average-range picture. To say nothing of Sporadic-E skip, which, depending on whom you consult, either extends or shortens your groundwave coverage.

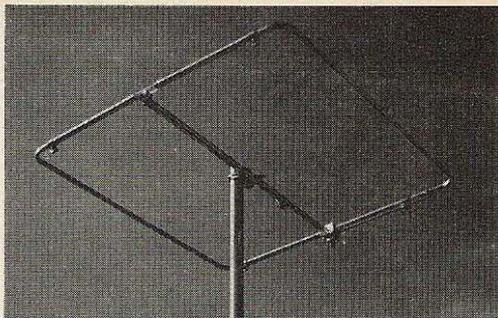The most noticeable difference, though, between mobiling on two and six is your calls-QSO ratio. Since few people really tune on six meters until after they've first checked their frequency, your calls-QSO ra-



A comparatively recent development, the Cush Craft "Squalo" has a loyal mobileer following among many six and two meter operators. The antenna, essentially a "square halo", affords an omnidirectional dipole pattern with compact physical dimensions and is available in models through 432 MHz.

tio is directly proportional to your *proximity to him on the dial*.

But aside from these relatively minor calamities, you can have enough fun to write home about. When you find the neighbors XYL, and junior op's too much with their TVI complaints, you can delight the entire crew by hopping into the auto and stealthily driving off to a new, unsuspecting sector, wreaking havoc as you cruise by. Which, incidentally, might be one of the contributing factors in the tremendous popularity of 6-meter mobiling in this country.


Operationally, it is advantageous on 50 MHz to first check your frequency (a spotting switch is a "must"), and then let loose with a CQ. Due to the concentration of stations in the first 500 kHz on this band, it is seldom necessary to call for more than one minute before tuning. A rapid check of the band thereafter, followed closely by a more careful tune, is also a good habit to get into. Never make a transmission without stating your approximate location unless you are a commercial radio announcer who likes to keep in practice during off-hours.

Unlike two, a good number of 50 MHz stations enjoy working weak-signal mobiles and attempting to hold them until the bitter end. This is important to bear in mind because you can unintentionally offend these long distance runners if your ignition noise overrides their calls, or if you are not in the habit of listening for threshold signals.

Another tip: Since most of your QSO's will be with well-equipped base stations, don't drag out your transmissions. He can

VALUE

ENGINEERED

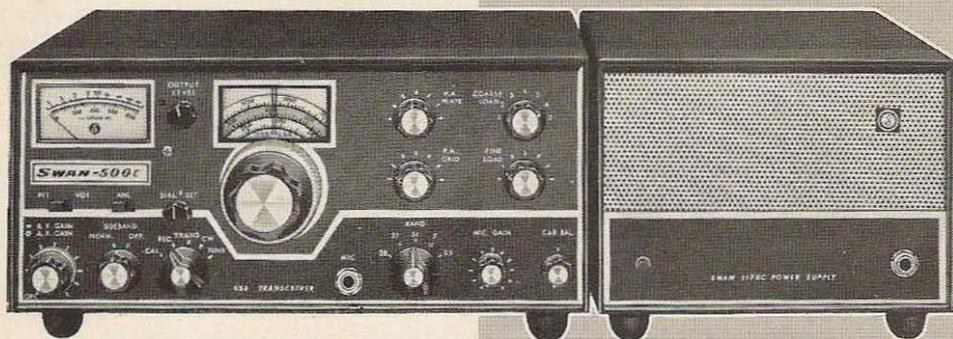

SWAN 500C

There must be some very good reasons why Swan has become the leading manufacturer of transceivers for the amateur radio service. One of the most important reasons is our dedication to the principles of Value Analysis.

Value Analysis is the process of examining a product to find ways of improving its performance, reducing costs, or whatever can be done to make the product a better value to the buyer. It is surprising how often this leads to greater simplicity, improved reliability, and overall consumer satisfaction.

At Swan our engineering depart-

ment is constantly applying these principles in an intensive search for improvements in our products. The 500C transceiver is an outstanding example of the results. It combines all the features you require in a complete SSB-AM-CW transceiver with performance, quality, and reliability second to none. Yet the price is substantially less than competitive gear. There's really no secret or mystery about this. We believe that the 500C is the most completely "Value Engineered" transceiver on the market, and this is why we are in the lead. Visit your Swan dealer soon, and see for yourself.



SWAN

ELECTRONICS
OCEANSIDE, CALIFORNIA

A Subsidiary of Cubic Corporation

SWAN SPEAKS YOUR LANGUAGE

500C Amateur Net \$520
117XC POWER SUPPLY \$105

ASK THE HAM WHO OWNS ONE

hear signals you can't, especially those on your frequency. If you find you have lost contact, standby for instructions. Chances are you'd fare better higher up the band, where QRM is not as prevalent. This technique can also be employed in reverse. To secure your QSO, give a call in the first 100 kHz of the AM band, establish contact, then QSY without waiting for the inevitable heterodynes.

Although only the rank newcomer to six meter motoring will have to be told that 95% of the stations are horizontally polarized, few recognize that installation of a CB-type whip can also be advantageous. Quite often switching to vertical polarization yields unsuspected rewards, particularly if your partner can do likewise when you are stuck on a busy frequency. If you're handy with plumbing, add another loop to a 3-ring halo and listen to the praise roll in. The additional ring, when the antenna is carefully adjusted for best-height-above-ground, frequently eliminates the "typical mobile flutter" that's usually a dead giveaway to operators who don't like mobiles.

If you would really like something different, the next time signals take on that warbly aurora characteristic, head for the highest piece of land around and rotate the auto for a peak reading. Pick out the strongest CQ caller you hear, speak noticeably slower and more distinctly, and give him a shout. The old rule-of-thumb that you must have at least 100 watts into a 5-element array can be proved wrong if you are the persistent type.

The simplest way to pick up DX on six is, of course, through Sporadic-E skip openings. Big antennas and high power mean little. The trick is to get out of the QRM. Make it a practice to always keep a crystal for an odd frequency above 51 MHz handy for emergencies. It is a fact that mobiles invariably cash in first on long-haul skip contacts, probably because a six meter mobileer tunes a receiver with less bandwidth than the base stations employ and therefore is one of the first to hear the higher frequency DX callers. Keep transmissions short, since E-layer openings are unpredictable and can take a turn for the worse in an instant.

The really ardent 50 MHz mobile operator employs both a v.f.o. and a nuvistorized preamplifier. Properly regulated supplies for stability and multiple-wavelength

feedlines for best SWR make for mobile fun you'd never dream possible. By spending 90% of my driving time *listening*, this writer picked up 34 states during a 6-month period not long ago, which, by the way, included five over-200 mile groundwave QSO's. This was accomplished with a 4.5 watts-output transmitter into a 4-ring halo.

Driving through open country, keep an ear out for the weak, out of state signals. If you hear a couple stations in QSO whom you know must be at least 75 miles away, throw your carrier on intermittently to create a "signaling" heterodyne. When they stand by for the breaker, do your stuff. If you've been listening for a while, instruct them *right off* to turn their yagis NNE, or whatever the approximated direction is. They'll never believe you're a mobile.

Be Different

We would be doing you a grave injustice if we did not include in this report the fact that numerous v.h.f. stations simply will not QSO mobiles. Their reasons are worth listening to, if you are seriously contemplating mobile operation: (1) They disappear into the noise before you've had a chance to make a transmission, or (2) They never say anything worth listening to, or (3) Their audio is inferior, or all three. There is much truth in these observations.


We can't stress often enough that you keep your transmissions *short* and to the point, seldom more than two minutes in duration. Let him do the talking; anyway, you have to drive.

Avoid confining your topics of conversation to such earth-shattering developments as a Mack truck has just pulled in front of your vehicle. Keep a scratch pad on your dashboard and *use it* to note what *he* is interested in.

If your audio really delivers, the other station won't care if you are an S1 on the meter. If it doesn't, invest in a CB-type transistorized speech clipper or compressor. They work, you know and are just about the best buys around.

By "being different" you can win over a lot of these soreheads, realize many hours of pleasureable mobiling, and have something you'll remember for a long time as truly worthwhile hamming.

... K2ZSQ

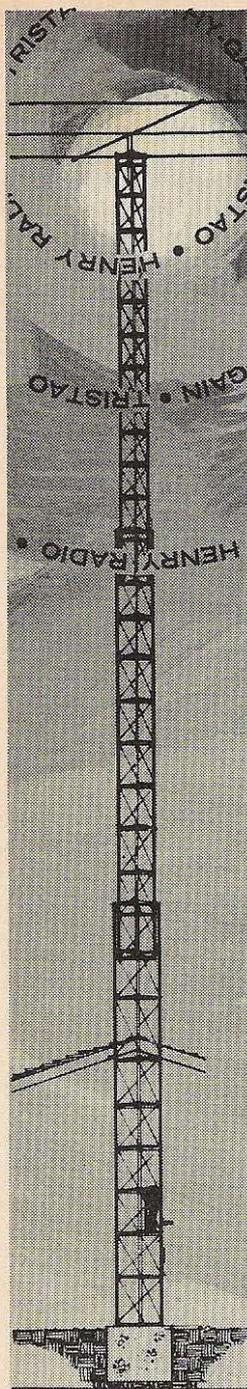

Henry Radio Presents

A NEW CONCEPT IN ITS EXCITING BEAM ANTENNA PROGRAM

Any knowledgeable DX'er will tell you the secret is in the antenna. For over a year Henry Radio has provided an exciting beam antenna package program allowing the average amateur to own an efficient, and unbelievably economical antenna package . . . pre-engineered, pre-matched and pre-packaged to suit his pocketbook and requirements. NOW! This world famous antenna program moves forward. NOW! You can have the antenna of your choice at the same incredible saving.

Basic package No. HR-1

***Tristao CZ-337 New concept 40 ft. crank-up tower w/mast
CDR TR-44 rotator
100 ft. RG-58 A/U Coax
100 ft. Control cable**

Complete with one of the following:

**Hy-Gain TH-3 Jr. antenna \$325.00
Hy-Gain TH-2 Mk 3 antenna \$325.00
Hy-Gain DB 10-15A antenna \$325.00
Hy-Gain 203BA antenna \$330.00
Hy-Gain TH-3 Mk 3 antenna \$375.00**

A savings of approximately \$70.00

Basic package No. HR-2

***Tristao CZ-454 New Concept 60 ft. crank-up tower w/mast
CDR TR-44 rotator
100 ft. RG-58 A/U Coax
100 ft. Control cable**

Complete with one of the following:

**Hy-Gain TH-3 Jr. antenna \$480.00
Hy-Gain TH-2 Mk 3 antenna \$480.00
Hy-Gain DB 10-15A antenna \$480.00
Hy-Gain 203BA antenna \$485.00
Hy-Gain TH-3 Mk 3 antenna \$520.00**

A savings of approximately \$90.00

Basic package No. HR-3

***Tristao CZ-454 New Concept 60 ft. crank-up tower w/mast
CDR Ham-M rotator
100 ft. RG-8/U Coax
100 ft. Control cable**

Complete with one of the following:

**Hy-Gain TH-3 Mk 3 antenna \$560.00
Hy-Gain 204 BA antenna \$565.00
Hy-Gain 402 BA antenna \$575.00
Hy-Gain TH-6 DXX antenna \$590.00
Hy-Gain DB-24B antenna \$620.00**

A savings of approximately \$120.00

***Free standing tower \$10.00 extra**

All complete packages are priced freight prepaid to your door in the continental U.S.A. Substitutions may be made . . . write for prices. And remember, you can buy on time. You can trade your used transmitter or receiver. You can rely on Henry Radio to supply the finest equipment and the best value.

CALL DIRECT . . . USE AREA CODE

Henry Radio Stores

Butler, Missouri, 64730

816 679-3127

11240 W. Olympic, Los Angeles, Calif., 90064

213 477-6701

931 N. Euclid, Anaheim, Calif., 92801

714 772-9200

"World's Largest Distributor of Amateur Radio Equipment"

Communicator Reborn

W. R. Lingenbrink W6HCX
1809 Hill Ave.
Hayward, Calif. 94541

It is impossible to get single-signal-selectivity using a Gonset Communicator (Gooney Bird), but we can sure make some improvements in the selectivity of this "old faithful."

By making the receiver section double conversion, we have been able to eliminate interference from aircraft and repeaters close to the frequency and, in general, have been able to make the Gooney Bird sound like a converter working into a good receiver.


The cost is very moderate (less than ten dollars and about four hours of your time), and in addition no alterations show from the outside so there is nothing to detract from the resale value of the unit.

Looking at the receiver section, either out of the cabinet or at the diagram (if you are lucky enough to have one), we find several stages of six MHz *if*. If we make one of these stages a mixer and change the last two *if* cans to 455 kHz, we have a fine double conversion receiver. By adding crystal controlled local oscillator to our new mixer stage, we are in business. This local oscillator may be added as an outboard stage mounted on a bracket next to the pre-amp on the back apron of the receiver section as shown in Fig. 1.

The choice of oscillator tube may vary. I used the 6AV6 because it was on hand and has shown to work fine.

The bracket should be made and mounted in place before any wiring is done due to the difficulty of getting the mounting screws in place after the wiring is in. The oscillator is then wired as shown in the diagram and test voltages applied. Using a VTVM you should read about -2 to -4 volts at pin one of V11 (6BH6) which is our new mixer stage.

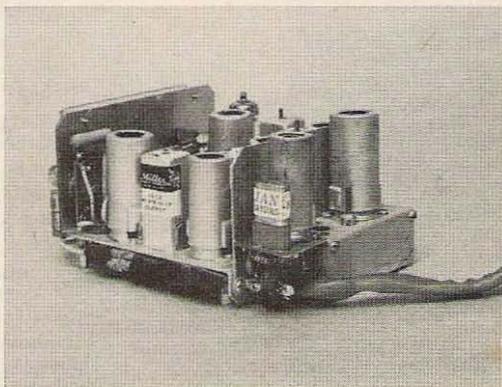Now remove the last two 6 MHz *if* cans (T3 and T4) noting the position of the green dot on the bottom of the existing can so we can place the new ones in the exact position. Remove the wiring from the old *if* cans carefully so as not to shorten the leads any more than absolutely necessary.



This photo shows the oscillator mounted next to the pre-amp on the back apron of the receiver section. One of the new 455 kHz *if* cans can be seen in the center.

These leads will be used on the new 455 kHz *if* cans. I used the Miller "K TRANS" designated 12C1 and 12C2, input and output, since they are of the same size and mounting configuration as the ones being removed.

When the transformers are mounted and reconnected, the cathode resistor (R21) on our new mixer tube should be replaced with a 5 K resistor of the same wattage as the old 150 ohm one. This completes the conversion so check the wiring carefully.

Next, leaving the receiver section out of the case, connect the power plug to the transmitter modulator audio section and begin the line-up of our new *if* section.

When you turn the set on, don't be alarmed at the lack of VHF hiss that you are used to hearing. This will be back when the new *if* transformers are peaked. This can be done either on background noise or by using a noise generator. This process is described in all the handbooks, but it is sufficient to peak to the highest noise level.

When this has been done, you might be


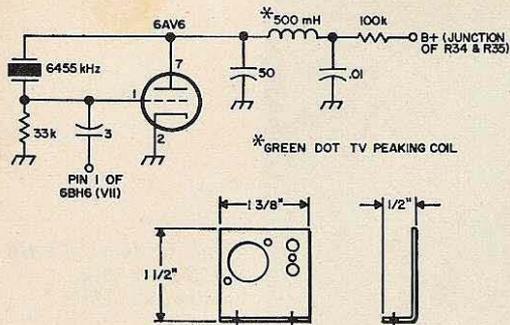


Fig. 1. The oscillator circuit showing the mounting bracket used.

interested in one other modification using low cost rectifier diodes. The replacement of the two 6X4 rectifiers in the power supply with solid state will yield about 25 volts more from the output of the supply and will eliminate a good deal of heat.

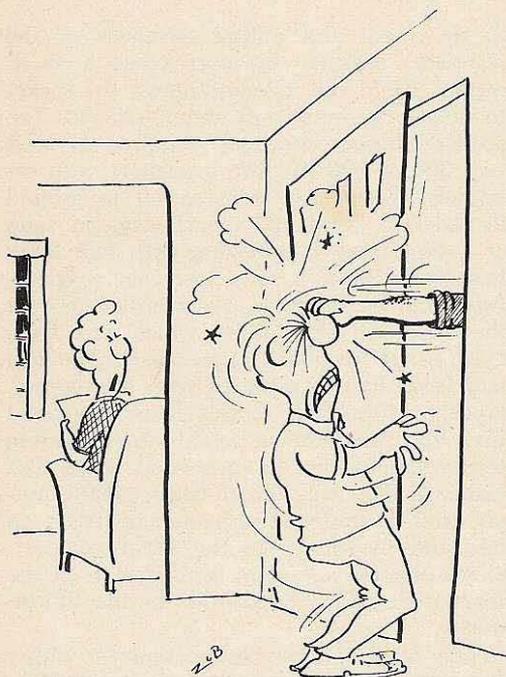All inquiries will be answered if accompanied by a self addressed stamped envelope.
 . . . W6HGX



"IS THAT ANOTHER ONE ABOUT TVI, GEORGE?"




SEPTEMBER CLEARANCE RECONDITIONED HAM GEAR

AMECO	
R5	\$59.00
COLLINS	
75A3 3.1 KC Filter	\$219.00
75A4 (early model)	349.00
75A4 (late Ser. #4500) w/spkr	459.00
75S-1	349.00
DRAKE	
2B Q Multiplier	\$ 29.00
DRAKE 2-A	\$149.00
DRAKE 2-C	\$195
L4 (Brand New) Linear (sealed ctn)	595.00
HALLICRAFTERS	
SX99	\$ 79.00
SX96	129.00
SX110	99.00
S120	49.00
HAMMARLUND	
HQ140X	\$129.00
HO 110C	129.00
HQ170	179.00
HQ170A	219.00
HQ170C	189.00
SP600-JX17	229.00
HEATH	
HR-20	\$ 89.00
MR-1 w/p.s.	49.00
NATIONAL	
NC173	\$ 79.00
HRO 50 R w/Prod Det (4 coils)	109.00
NC270	119.00
NC183D	129.00
CLEGG	
Venus-Xceiver-6M SSB (Like New)	\$319.00
66er	189.00
Zeus 2-6 M 185 watts	329.00
DRAKE	
TR-4 Xceiver (demo)	559.00
GONSET	
Gonset Comm. II 2M	\$119.00
Comm. III 6M	99.00
GSB 100	179.00
G-50 6M Xceiver	\$179.00
HALLICRAFTERS	
HT 37	229.00
HEATH	
HX-11	35.00
DX-60	59.00
HW12 80 Meter XCVR	\$89.00
JOHNSON	
Ranger	\$ 79.00
Valiant	159.00
NATIONAL	
NCX-5	\$385.00
NCL-2000	385.00
SWAN	
SW175 xcvr 75 meters	\$129.00
SW120 xcvr 20 meters	119.00
Swan 500	419.00
400 XCVR	339.00

ALL CASH ORDERS SHIPPED FREE IN THE 48 STATES

MISSION HAM ELECTRONICS

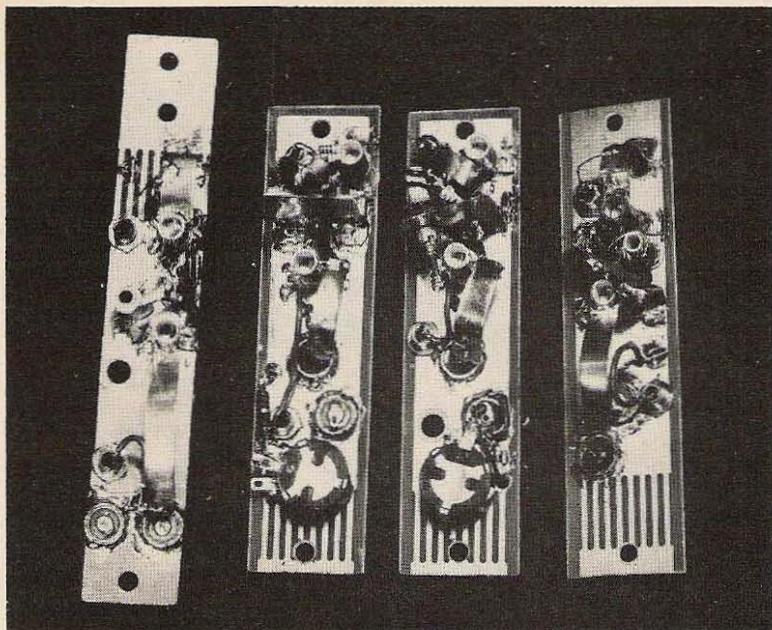3316 Main Street, Riverside 3, California 92501
 Phone 683-0523 (area code 714)



Frank C. Jones W6AJF
850 Donner Ave.
Sonoma, Ca. 95476

432 MHz Amplifiers

The four different 432 MHz amplifiers, shown in the photograph and in the circuit diagrams, were built up on small strips of copper plated plastic board. The purpose was to run a series of tests on different kinds of FET units which might work on 432 MHz. The field effect transistors have come down in price and the three types tested all sold for approximately one dollar each. The three available at the time were the Motorola MPF 102, the Texas Instrument TIS34 and the Union Carbide UC 734. Both grounded-gate and neutralized grounded-source circuits were tried by either making up new strips or rewiring the existing strips. The four amplifiers shown in the photograph from left to right are ground-gate MPF 102, grounded-source TIS34, grounded-gate UC 743 and grounded-source UC 734 (or 2N4416).

The circuits consisted of short pieces of copper sheet from $\frac{1}{4}$ to $\frac{5}{16}$ -inch wide; 1 to $1\frac{1}{2}$ -inches long for the tuned input and output 432 MHz circuits. Low priced plastic piston trimmer capacitors of 1 to 6 pF were used to tune the circuits. These were connected by short leads, usually sheet copper,

to the input and output terminals of the transistor sockets. In most cases a small copper shield was soldered across the socket to isolate the input and output circuits. The grounded-source terminals required at least two 300 or 500 pF disc capacitors with extremely short leads from socket to ground in order to "cool off" the rf stage in spite of a slug-tuned neutralizing coil. The latter had to be from 2 to 4 turns on a white-coded ferrite slug form, $\frac{3}{16}$ -inch diameter for the different FET units which ran from $\frac{1}{2}$ to $1\frac{1}{2}$ pF feedback capacitance. The coil and leads had to resonate with this capacitance to 432 MHz. It was later discovered that the neutralizing coil-form mounting screw should not be grounded since this makes it difficult to obtain correct input, output and neutralizing adjustments. Also, an insulated mounting (in the input compartment) allowed one more turn of wire on the form with wider bandwidth in the adjustments.

The 50-ohm input connection for either grounded-gate or source circuits at 432 MHz always seemed to work out at about the center of the input strap circuit, that is

midway between the tuning capacitor and ground ends of the strap. Apparently both types of circuits functioned at best noise figure with from 200 to 500 ohms impedance into either the gate or emitter terminals. The same circuit showed lower Q (less critical tuning) with emitter input, that is with the grounded-gate connection. This probably meant about 200 ohms input, whereas gate input needed around 500 ohms for best NF.

The output circuit was always adjusted for 432 MHz resonance, maximum gain, together with space variation of the output loop. Too close coupling gave low stage gain. The output loop from coax fitting to ground was made of number 18 wire in order to be able to vary the coupling to the drain tuned circuit, but, at the same time, to keep the coupling constant when in use as a pre-amplifier ahead of the regular 432 MHz converter.

The neutralizing coil in the grounded-source units was adjusted for the value which gave maximum gain without excessive regeneration in all cases. Actual rf oscillation even 2 or 3 MHz away from 432 MHz had to be checked by tuning the *if* receiver across several MHz since this will prevent proper operation of an amplifier. Noise figure and gain measurements were made on all amplifiers using several different transistors of the same FET types. A diode tube noise generator, partially compensated to work reasonably well at 432

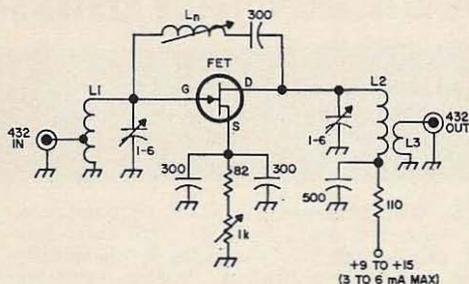



Fig. 1. Grounded source circuit for FET's.

L1 = 1" long x 1/4" wide copper strip, center tapped.

L2 = 1 1/2" long x 1/4" wide copper strip.

L3 = Approx 1" of #18 wire coupled to L2.

Ln = 2-4 turns #22 wire 1/4-3/8" long x 3/16" dia.

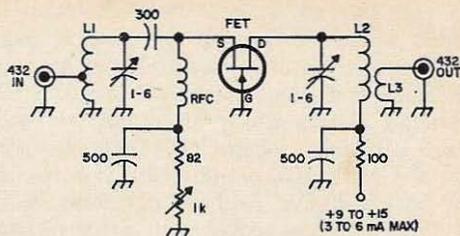

UC734
2N4416



MPF102
MPF104



TIS34

BOTTOM VIEWS

Fig. 2. Grounded gate circuit for FET's.

L1, L2, L3 as in Fig. 1.

RFC = 7" of #22 wire coiled up into solenoid.

MHz, was used for NF measurements. A standard signal generator with a 6 db UHF attenuator between the amplifier and signal generator output connector was needed to insure 50-ohm input impedance, and another similar attenuator was connected in the 50-ohm line between the preamplifier and the 432-MHz converter. The latter helped reduce regeneration in either the amplifier or the converter from spoiling the gain measurements.

The MPF 102 (also some MPF 104s) amplifiers gave very low gain figures ranging from 1 1/2 to 2 times or about 4 to 6 db. The noise figures ranged around 7 or 8 db which wasn't too bad. The converter by itself had a NF of 3 db with a Union Carbide 2N4416 rf stage, a very hot five dollar FET unit. The UC 734 FET units are TO-18 metal-cased units with four leads exactly like the 2N4416's except that they are mass-produced without the many added factory tests made on the 2 N4416's. Therefore, the UC-734 costs about one-fifth as much—\$1.10 in small quantities.

The TIS34 neutralized amplifier showed about 4 to 5 db for the best plastic cased units in the grounded-source circuit and with gain figures ranging from 6 to 8 db for the best units. There wasn't too much variation in units, with over 50% working very well at 432 MHz. The TIS34 grounded-gate amplifier was quite stable, required no neutralization and gave a NF of around 6

db and gain of 4 to 6 db. This type of circuit would be fine for a second rf stage in a converter with a "neutralized" grounded-source first stage, since two "neutralized" rf stages always seems to be full of oscillation problems. These TIS34 plastic units and the MPF 102 plastic units look similar but have different lead arrangements. Both require an in-line socket with three terminals, if a socket is used. A socket increases lead lengths and capacitances but sure saves time in comparing transistors of the same make. Unfortunately, the TIS34 seems to be hard to find at Texas Instrument distributors and outlets.

The UC 734 units, if selected for 432 MHz operation, were by all comparisons far superior to the other FETs. The gain figures ranged from 8 to 12 db in grounded gate, with NF of 4 to 5 db. Twelve db was the highest measured in a run of ten UC 734 units. About 50% were good for 432 MHz with 3 of the 10 being "red hot", fully equivalent to the best of the four 2N4416 units available for these tests.


The neutralized grounded-source UC 734 selected units gave NF of 2½ to 3 db and gain figures of 10 to 18 db. These amplifiers are a marvelous thing for weak signal 432 MHz reception. It takes a very good parametric amplifier with its tricky adjustments and high cost to do any better. Needless to say, these tests were time consuming

since each change of transistors always seemed to require a little readjustment to arrive at best gain and NF. Usually best NF occurred at 3 to 5 mA drain current with a 9-volt battery supply. The source bias voltage should be higher for 12 or 15-volt supplies, but probably at these same current values, since FET units are quite a bit like tetrode tubes.

In conclusion, the Motorola MPF 102 units are not very good at 432 MHz since this is too high a frequency for these general purpose rf and if transistors. They seem to be readily available at the larger Motorola dealer outlets at present for 90¢ to \$1 in small quantities. The Texas Instrument TIS34's are fine at 432 MHz but at the time of these tests, are difficult to find at TI outlets (priced about \$1.10 each). The Union Carbide UC 734 units, if selected, are real fine transistors for 432 MHz. These little gems are replacing all other transistors in my converters since they are far better than the best bipolar transistors that I've been able to obtain. At the time of these tests single UC 734's were \$1.10 and about 75¢ in quantities of 100 and in very good supply. The poor ones at 432 MHz were all less than 2 db NF at 144 MHz, so none were wasted!

... W6AJF

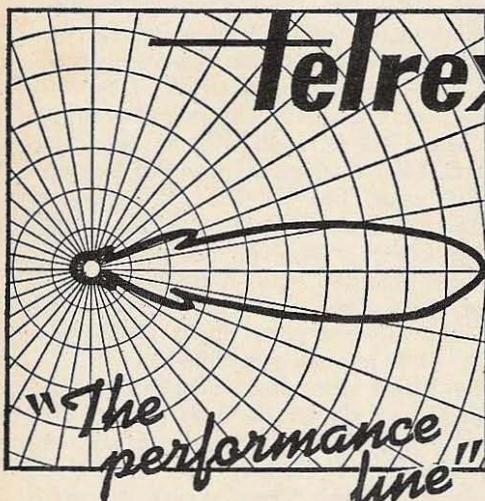**The specifications for I_{ass} , I_{DSS} and g_m are relaxed slightly; capacitance and frequency specs are the same as for the 2N4416. ed.*



— with a MATERIAL DIFFERENCE!

Use, is one of the most dependable testimonials of endorsement, and Telrex products are in use in 139 Lands

“Beamed-Power” ANTENNAS, “BALUNS” I. V. KITS and ROTATOR SYSTEMS!


Most Technically-Perfect, Finest Communication Arrays in the World! Precision-Tuned-Matched and “Balun” Fed for “Balanced-Pattern” to assure “TOP-MAN-ON-THE-FREQUENCY” Results

Enjoy World renown TELREX performance, value and durability! Send for PL68 tech. data and pricing catalog, describing professionally engineered communication antenna systems, rotator-selsyn-indicator systems, “Baluns”, I.V. Kits, Towers, “Mono-Pole”, “Big-Berthas”, accessories, etc. etc.

COMMUNICATION SYSTEMS SINCE 1921 **telrex** Laboratories
Communication Engineering

ASBURY PARK, NEW JERSEY 07712, U.S.A.

\$240!

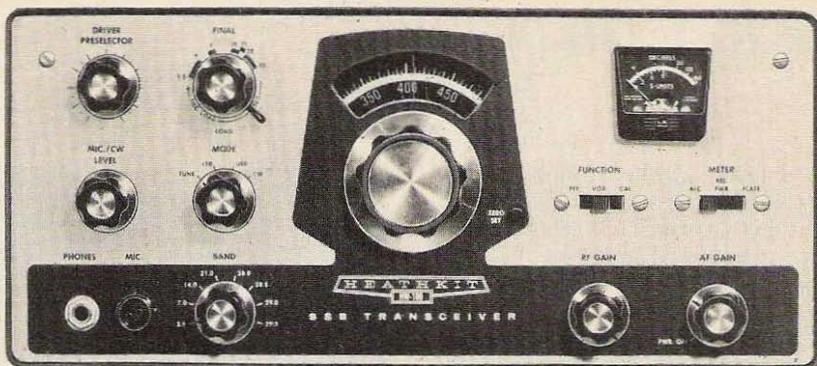

NEW HEATHKIT® HW-100 5-BAND SSB-CW TRANSCEIVER

You asked for it . . . a multi-band version of the Heathkit "single-banders" . . . low-cost SSB operation on 10 or 15 meters . . . an SSB transceiver equal or superior to many assembled rigs, but at *much lower cost*. That's the HW-100.

How did Heath do it? We expanded on the "single-bander" design . . . borrowed from the heritage of the famous SB-101 . . . took a look at the competition . . . and produced the most SSB equipment you can get for the money.

Check the features and the specifications:

- Solid-state (FET) VFO • 80-10 meter coverage • Switch selected upper or lower sideband or CW • 180 watts input PEP SSB — 170 watts input CW • Crystal filter • Full coverage on all bands with 500 kHz per band segment • Smooth vernier control of frequency with patented Harmonic Drive™ dial mechanism • Built-in 100 kHz calibrator • Separate offset CW carrier crystal • TALC • Quiet, enclosed relays • Fixed or mobile operation with HP-23 or HP-13 power supplies • Easy assembly with circuit boards and wiring harness

Kit HW-100, 18 lbs., no money dn., \$22 mo. \$240.00

Kit HP-13, DC power supply, 7 lbs., \$7 mo. \$64.95

Kit HP-23, AC power supply, 19 lbs., \$5 mo. \$49.95

Kit SB-600, 8 ohm speaker, 6 lbs. \$18.95

HW-100 SPECIFICATIONS — RECEIVER. Sensitivity: Less than .5 micro-volt for 10 dB signal-plus-noise to noise ratio for SSB operation. Selectivity: 2.1 kHz minimum at 6 dB down, 7 kHz maximum at 60 dB down (3.395 MHz filter). Input: Low impedance for unbalanced coaxial input. Output impedance: 8 Ω speaker, and high impedance headphone. Power output: 2 watts with less than 10% distortion. Spurious response: Image and IF rejection better than 50 dB.

TRANSMITTER. DC Power input: SSB: 180 watt P.E.P. (normal voice: continuous duty cycle). CW: (A1 emission) 170 watts (50% duty cycle). RF Power output: 100 watts on 80 through 15 meters; 80 watts on 10 meters (50 Ω nonreactive load). Output impedance: 50 Ω to 75 Ω with less than 2:1 SWR. Oscillator feedthrough or mixer products: 55 dB below rated output. Harmonic radiation: 45 dB below rated output. Transmit-receive operation: SSB: PTT or VOX. CW: Provided by operating VOX from a keyed tone, using grid-block keying. CW Sidetone: Internally switched to speaker or headphone, in CW mode. Approximately 1000 Hz tone. Microphone input: High impedance with a rating of —45 to —55 dB. Carrier suppression: 45 dB down from single-tone output. Unwanted sideband suppression: 45 dB down from single-tone output at 1000 Hz reference. Third order distortion: 30 dB down from two-tone output. RF Compression (TALC): 10 dB or greater at .1 ma final grid current. GENERAL. Frequency coverage: 3.5 to 4.0; 7.0 to 7.3; 14.0 to 14.5; 21.0 to 21.5; 28.0 to 28.5; 28.5 to 29.0; 29.0 to 29.5; 29.5 to 30.0 (megahertz). Frequency stability: Less than 100 hertz per hour after 30 minutes warmup from normal ambient conditions. Less than 100 Hz for ±10% line voltage variations. Modes of operation: Selectable upper or lower sideband (suppressed carrier) and CW. Dial calibration: 5 kHz. Calibration: 100 kHz crystal. Audio frequency response: 350 to 2450 Hz. Front panel controls: Main tuning dial. Driver tuning and Presselector. Final tuning. Final loading. Mic and CW Level control. Mode switch. Band switch. Function switch. Meter switch. RF Gain control. Audio Gain control. Side controls: Meter Zero control; Bias; VOX Sensitivity; VOX Delay; ANTI-TRIP. Internal controls: Carrier null; neutralizing. Tube complement: 6A2 Regulator (150 V); 6AU6 RF amplifier; 6AU6 1st receiver mixer; 6AU6 Isolation amplifier; 6AU6 1st IF amplifier; 6AU6 2nd IF amplifier; 6BN8 Product detector and AVC; 6AU6 VFO Amp.; 6CB6 2nd transmitter mixer; 6CL6 Driver; 6EA8 Speech Amplifier and cathode follower; 6EA8 1st transmitter mixer; 6EA8 2nd receiver mixer and relay amplifier; 6EA8 CW sidetone oscillator and amplifier; 6GW8 Audio amplifier and audio output; 12AT7 Heterodyne oscillator and cathode follower; 12AT7 VOX amplifier and calibrator oscillator; 12AU7 Sideband oscillator; 6146 Final amplifiers (2). Diode complement: 6 Germanium Diodes: Balanced modulator, RF sampling, and crystal calibrator harmonic generator; 9 Silicon Diodes: ALC rectifiers, anti-trip rectifiers, and DC blocking; 1 Zener Diode: cathode bias. Transistors: MPS105 FET-VFO; 2N3393 — Voltage regulator. Rear apron connections: CW Key jack; 8 Ω output; ALC input; Power and accessory plug; RF output; Antenna; Spare. Power requirements: 700 to 850 volts at 250 ma with 1% maximum ripple; 300 volts at 150 ma with .05% maximum ripple; —115 volts at 10 ma with .5% maximum ripple; 12 volts AC/DC at 4.76 amps. Cabinet dimensions: 14-13/16" W. x 6-5/16" H. x 13-3/8" D.



FREE '69 CATALOG

Describes these and over 300 other Heathkits. Save up to 50% by building them yourself. Use coupon and send for your FREE copy!

HEATH COMPANY, Dept. 11-9
Benton Harbor, Michigan 49022
In Canada, Daystrom Ltd.

Enclosed is \$ _____, plus shipping.

Please send model (s) _____

Please send FREE Heathkit Catalog. Please send Credit Application.

Name _____

(Please Print)

Address _____

City _____

State _____

Zip _____

Prices & specifications subject to change without notice.

AM-196




Quick Converters

George P. Schleicher W9NLT
1535 Dartmouth Lane
Deerfield, Ill. 60015

Recently I wanted to listen in on two meter activity, preparatory to going mobile. In order to do this I needed a converter to use with one of my station receivers. Naturally, I wanted it in a hurry and at minimum cost. A review of the ham magazines and handbooks disclosed several designs for good looking converters but any of them would have required mail order parts and considerable construction time. My next move, of course, was to open a catalog and price the commercially-made gear. The fine print associated with most of them said, "Specify if Frequency", indicating that they might not be on the dealer's shelf but made to order. So I asked myself, "How can I get one now?"

After thinking about this one for a while I realized that the front end or tuner in every TV set is essentially a converter. I immediately began to disassemble an old TV set that I had been saving for parts salvage and I found a very promising tuner. Incidentally, a few weeks later I made a trip to my friendly TV dealer to see what the "market" might have to offer other hams. I learned that used TV sets, in whole or in part, can sometimes be had for the asking. In fact, I came away with a twin to my first tuner.

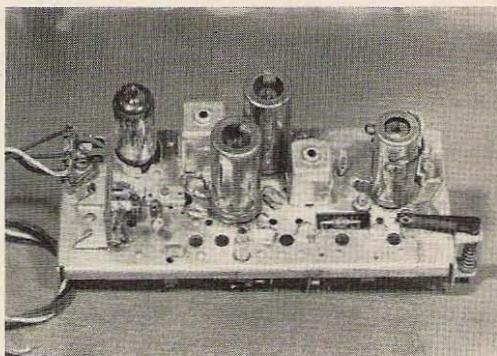As soon as I had scrounged the first tuner I did some research into the industry standards for TV channels and the associated receiver design. I learned that TV broadcast




The circuit deck as it appeared before the removal of the fine tuning assembly, power wires, and the 300 ohm input jack.

channels are assigned in four segments of the radio spectrum that lie between 54 and 890 MHz. Each channel occupies a total bandwidth of 6 MHz. The picture carrier is 1.25 MHz above the lower band edge and the sound carrier is 4.5 MHz above the picture carrier (0.25 MHz below the upper band limit). The current practice in the industry is to arrange the TV set tuner to convert the incoming TV signal to the receiver's nominal i.f. frequency of 41 MHz. (A few tuners may still be found that have an *if* at 21.5 MHz.) This is accomplished by operating the local oscillator 41 MHz above the upper band edge. The following relations exist:

Channel number	Occupied r.f. band	Picture Carrier	Sound Carrier	Tuner Local osc.
2	54- 60 MHz	55.25	59.75	101
3	60- 66 MHz	61.25	65.75	107
4	66- 72 MHz	67.25	71.75	113
5	76- 82 MHz	77.25	81.75	123
6	82- 88 MHz	83.25	87.75	129
7 to 13	174-216 MHz	*	*	221-257#
14 to 83 (UHF)	470-890 MHz	*	*	517-931#

*The carriers have the same relative positions in each of the channels.


#At intervals of 6 MHz.

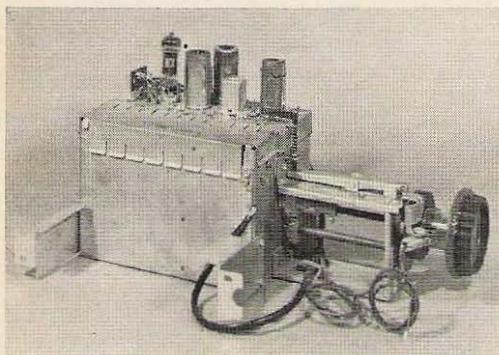

This is the way the tuner looked as it was removed from the TV set. It covered 16 channels, VHF and UHF.

The frequency of a signal at the output of a tuner or converter is equal to the difference between the frequency of that signal and the frequency of the local oscillator. (The sum of the two could be used but that would usually result in an inconveniently high fre-


quency for use in receivers). Note that with the local oscillator *above* the incoming signal, the output of the tuner is inverted. That is, with two signals coming into the tuner, the one at the higher frequency will be translated to the lower of the two frequencies at the tuner output. At the tuner output, each TV channel will occupy a 6 MHz band extending from 41 to 47 MHz; The picture carrier will be at 45.75 MHz and the sound carrier will be at 41.25 MHz. Other signals may also be present as most tuners have a bandwidth of at least 8 MHz; both adjacent-channel and image signals will be present. Two other points are significant: The *if* transformer(s) in tuners are designed as broadband devices and will remain so even though you attempt to peak the primary and secondary windings at the same frequency. Most tuners make no attempt to amplify incoming *rf* signals in the UHF band, utilizing from one to three tuned circuits as a bandpass filter between the antenna and the mixer.

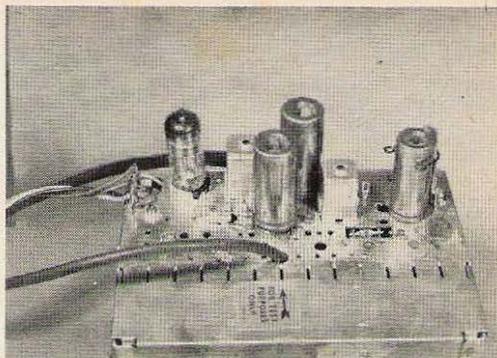

Outwardly the tuner/converter shows only a little change in its interim state.

Amateur Band	Bandwidth	Convenient converter outputs
21.-21.45 MHz	0.45 MHz	X.00-X.45 MHz (X = any whole no.)
28.-29.7 MHz	0.70 MHz	8.0-9.7 MHz, 18.0-19.7 MHz
50.-54. MHz	4.0 MHz	10.0-14.0 MHz, 20.0-24.0 MHz
144-148 MHz	4.0 MHz	4.-8. MHz, 14.-18. MHz, 44-48 MHz*
220-225 MHz	5.0 MHz	10-15 MHz, 20-25 MHz, 40-45 MHz*.
420-450 MHz	30.0 MHz	See text.

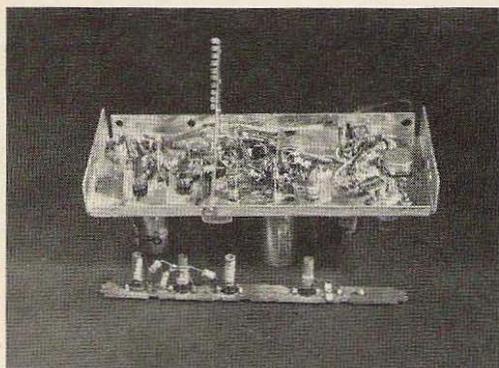*If your receiver will tune over this range you will not have to modify the *i.f.* transformers before use.



The rf coils are shown cemented to the chassis. One of the original channel tuning strips is shown for comparison.

Designing the converter

Two decisions that will have to be made regarding the converter involve the amateur band that you want it to accept and the frequency range that you want that band to have at the converter's output. Operating convenience will be greatest if the output frequency bears some direct relationship to that of the band on which the converter is used, for example:

The converter output frequency should be chosen to fall within the tuning range of your receiver, should be covered without switching bands, and preferably without tuning the receiver across any strong local stations. The outputs listed above assume that you will use a fixed local oscillator in the converter. If a variable local oscillator is used, you might want to consider a conventional *if* frequency such as 10.7 MHz, for which commercially-made transformers are available, or 4.5 MHz, and use the sound *if* transformer from the TV set. If you plan to use the converter between 420 and 450 MHz then you can cover the band in segments by employing a fixed local oscillator and a broadband *if* or you can make the local oscillator tunable across the entire band and use either a broad or a narrow *if* system at any convenient frequency.

As indicated above, you will have a choice of using either a fixed or a variable local oscillator; you may also elect to use either a narrow or a wideband *if system*. Your decision will depend on the band you want to cover, the tuner that you are converting, and your station receiver. Several combinations are possible. I won't attempt to describe them all; it will be more helpful if I show how I made my decisions.


The two meter conversion

My objective was to build a converter to receive the range of frequencies from 144 to 148 MHz. One of my station receivers (an ancient S-36) would tune from 27 to 144 MHz in three bands. I studied the tuner that I wanted to convert. I found that it employed a 6BQ7A cascode *rf* amplifier and a 6S4 local oscillator, both of which fed a 1N82 crystal mixer. The mixer was followed by a second 6BQ7A *if* amplifier which also used a cascode circuit. A 6S4 was used to stabilize the plate voltage supply to the local oscillator. Taken all together it made an excellent line up for use as a converter.

After studying the tuner's construction and its schematic diagram I decided on the following course of action: I would retune the *if* transformers higher in frequency by 2 MHz (from 41-47 MHz to 43-49 MHz) and I would use a fixed local oscillator working at 100 MHz. This would result in the two meter band being converted downward by an even 100 MHz and the frequencies coming into the receiver would be directly related to their position in the band. For example, 144.5 MHz would become 44.5 MHz, 147.3 would become 47.3, etc. It was at this time that I decided to eliminate the existing fine-tuning mechanism, change the input from a 300-ohm balanced to a 50-ohm unbalanced configuration and to use 300-ohm twinlead to connect the converter to the tunable receiver. I noted (for future reference) that this particular tuner provided no amplification on the UHF bands. I also discovered that normally active overtone crystals would oscillate if connected in place of the local oscillator coil.

It was less than an evening's work to disassemble the circuit deck and the coil turret to the extent necessary. My plan was to get filament and plate power from the tunable receiver. This was done by making up a cord and plug to match an octal socket that was provided on the receiver for the connection of external power. I discovered an idle contact on the socket and found that it could be used to make the receiver's *agc* voltage available to the converter. I suggest that if you do not do the same thing, you may want to provide some sort of bias voltage for the converter. Most of them require a bias voltage of from -1 to -3 volts; it is usually supplied by the TV set's *agc* system.

I also removed the assemblies of fingers

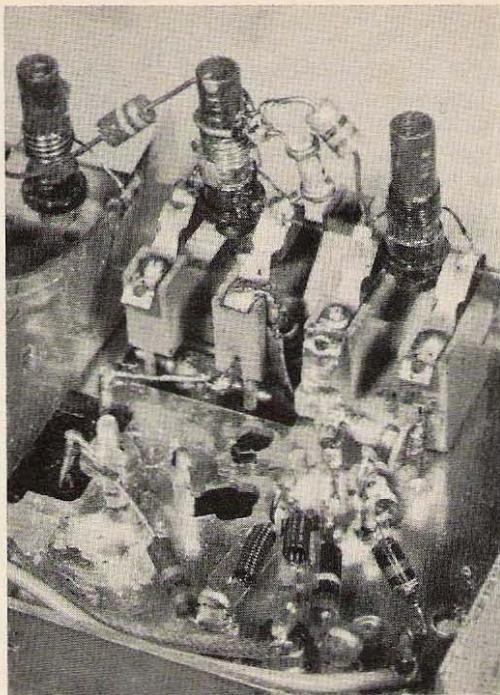

The rf mixer and oscillator coils are shown supported by their leads near the tube socket. The mixer diode is visible through a hole in the chassis.


that made contact with the channel strips in the turret. I found that one of them had to be left in place, however, because the mount for the mixer diode was an integral part of it.

In the second evening I was able to replace the *rf* coils so as to put the converter on two meters. The first operation was to remove the local oscillator coil from the tuning strip for channel #2. It normally works at 101 MHz and so it could be used without change. The tuning slug in the coil will easily change the frequency of the circuit by the required amount. Next I removed the *rf* coils from the tuning strip for channel #7 (174-180 MHz); they were soldered in place and adjusted to resonate in the two meter band. A grid-dipper was a big help in that work. Positioning the coils the way that they are shown permits them to be adjusted with a tuning tool inserted in the normal way from the top of the chassis. The final step was the connection of the input and output leads and the connection of the converter to the receiver. The *rf* coils peaked rather broadly, of course, but I was pleased to find that I had a working con-

verter that had a noise figure in the range of 6 to 7 db and a voltage gain of over 90. During the several weeks of operation that followed, my only criticism of the converter was that the local oscillator frequency was affected by mechanical vibration and that the whole assembly lacked the finished appearance of commercially-made equipment.

Gilding the lily


As indicated above, I originally went into this project with the idea that I was building a temporary piece of apparatus. The initial results convinced me that with a little more work I could have a converter that would be a permanent asset to my station. I considered such improvements as a crystal oscillator and *rf* coils made from commercially-built inductor stock. A crystal at 33.33 or 50.00 MHz could easily be obtained but I was concerned about having to filter out all but the 100 MHz harmonic from the mixer if I was to avoid spurious responses in the receiver. I also decided against high Q inductors as they might result in too narrow a bandwidth to cover the entire two meter band.

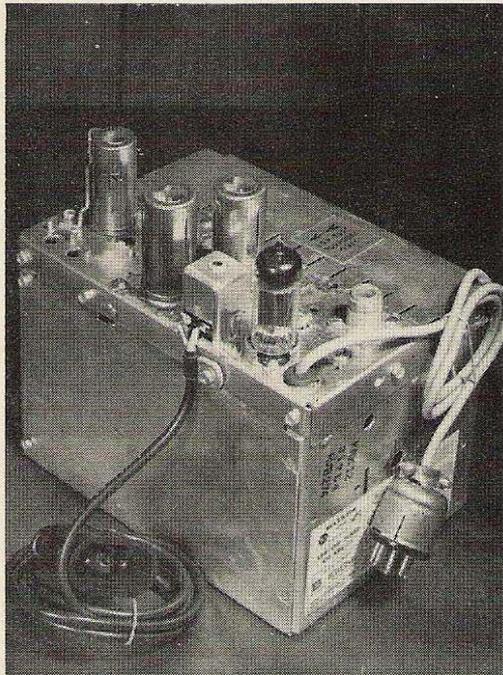

The finished tuner/converter presents a fairly respectable appearance. What was formerly the rear has become the "business end."

CRABTREE'S ELECTRONICS

"The Ham's Heaven"
presents

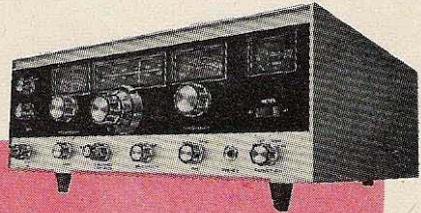

The superb
NEW R-530
by GALAXY

Solid state receiver for the most
exacting performance.

\$695.00

WRITE OR CALL FOR QUOTES
OR TRADE-IN ALLOWANCES

Bob Baker

WA5 BSR/m
Phone 214-748-5361

hy-gain

18HT
HY-TOWER

Multi-band **\$149.50**
vertical antenna

CRABTREE'S ELECTRONICS

2608 Ross Ave., Dallas, Texas 75201

Please ship me the following:

- Galaxy R-530 \$695.00
- Hy-Tower Model 18HT... \$149.50

Shipped pre-paid anywhere in "48"

- Check or Money Order attached

Name _____

Address _____

City _____ Call _____


State _____ Zip _____

American Express - BankAmericard - Diners Club

ANTENNAS


Cush Craft

MONOBEAMS FOR MORE DX PUNCH

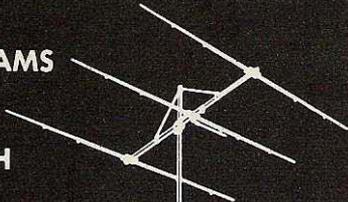

Cush Craft Monobeams combine superior electrical and mechanical features with the best quality materials and workmanship.

A28-3	10 meter, 3 element, boom 10'	\$31.95
A28-4	10 meter, 4 element, boom 18'	42.95
A21-3	15 meter, 3 element, boom 12'	39.95
A21-4	15 meter, 4 element, boom 22'	59.95
A14-2	20 meter, 2 element, boom 10'	49.95
A14-3	20 meter, 3 element, boom 20'	77.50

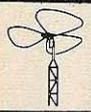


THE BIG WHEEL HORIZONTALLY POLARIZED 360° GAIN ANTENNA

2 Meter #ABW-144	\$11.95
2 Bay Stacking Kit	3.95
4 Bay Stacking Kit	11.75

VHF-UHF COLINEAR ARRAYS

Lightweight High Gain Antenna Systems

CL-116	2 meter, 16 element	\$17.50
CL-216	1 1/2 meter, 16 element	14.50
CL-416	3/4 meter, 16 element	11.50

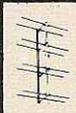


32 & 64 Element Stacking Kits Available

MOBILE/FIXED SQUALO


Squalo is a full half wave, horizontally polarized, omni-directional antenna.

ASQ-2	2 meter, 10" square	\$ 9.95
ASQ-22	2 meter stacked	16.95
ASQ-6	6 meter, 30" square	13.95

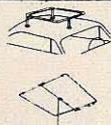

VHF/UHF YAGIS

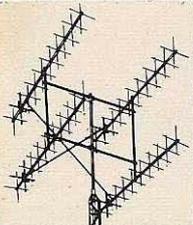Combine all-out performance with optimum size for ease of assembly and mounting at your site. They can be mounted vertically, horizontally, in pairs, or quads.



A144-11	2 meter	11 element	\$14.95
A144-7	2 meter	7 element	11.95
A220-11	1 1/2 meter	11 element	12.95
A430-11	3/4 meter	11 element	10.95
A144-20T	2 meter, Multi polarized		29.50
A 50-3	6 meter	3 element	15.95
A 50-5	6 meter	5 element	21.50
A 50-6	6 meter	6 element	34.95
A 50-10	6 meter	10 element	54.95
A 26-9	6 & 2 meter	10 element	29.95

"HAM STIK"

6 - 10 - 15 - 20 Meter

Adjustable Dipole with

Universal Mount
Ideal For Small Lots,
Apartments, Vacationing

\$23.50 Net

FREE LITERATURE

SEE YOUR DISTRIBUTOR OR WRITE FOR FREE CATALOG

Cush Craft

621 HAYWARD STREET
MANCHESTER, N. H. 03103

My final decision was to use the *rf* coils from a channel tuning strip for channel #6. These coils, together with the local oscillator coil, were cemented directly to the chassis to improve the converters frequency stability. The coils were brought to resonance by removing several turns from each one. I found this to be easier than using the coils for channel #7, as described earlier. The flexible contact fingers were broken off their supports and the coil leads soldered directly to the rivets that had secured the fingers. A type "N" coaxial connector was mounted on the chassis to function as an antenna input jack. One of the FM band rejection filters, previously removed from the 300-ohm antenna input circuit, was connected between the input jack and the antenna winding on the *rf* input coil. I also changed the 43 MHz output lead to coax, terminating it in a plug that would mate with the antenna terminals on my receiver.

The original power leads had been connected to an exposed terminal strip on the top of the chassis. I removed the terminal strip and ran a four conductor cable into the chassis through a rubber grommet. The free end of the cable was terminated in an octal plug that was arranged to mate with the "external power" socket on the back of the receiver, picking up heater, plate and age voltages. I recommend my approach to anyone who wants a converter in a hurry or would like the pleasure of building something worth while out of practically nothing. My cash outlay was exactly zero, since all of the required cables, plugs, etc. that were not a part of the original tuner came out of my junk box.

I find that there is a pretty fair amount of activity on two meters around Chicago right now, but I wonder what the gang are doing up on 420 MHz. Lets see now; I still have that second tuner W9NLT

73 BINDERS

Are your magazines falling down all the time? Our bright red binders will hold them on the bookshelf. Stamped in gold. Specify year. Only \$3 each, but going up before long. Order.

73 PETERBOROUGH NH 03458

73 BOOKS


73 USEFUL TRANSISTOR CIRCUITS

If you've been looking for a transistor circuit to do a special job, chances are there is a circuit in this book that will give you a head start. It covers circuits for audio, receivers, transmitters and test equipment. **\$1**




VHF ANTENNAS

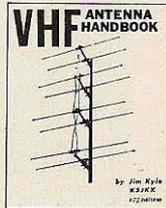This handbook by K5JKX is a complete collection of information about VHF and UHF antennas, with design hints, construction and theory. If you've been wondering what array you need, this book will give you enough background to make the right decision. **\$3**




INDEX TO SURPLUS

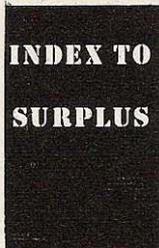Do you have a piece of surplus equipment that you want to convert but can't find an article? If so, this is the book you need. It lists all of the surplus articles and conversions in popular electronic and amateur magazines from 1945 to 1966. **\$1.50**




SIMPLIFIED MATH

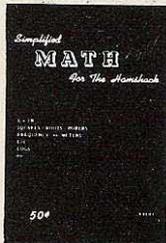Does math scare you? It shouldn't in this easy-to-understand book K8LF1 explains the simple exponential system of arithmetic, simple formulas, logarithms, and their application to the ham shack. **50c**



PARAMETRIC AMPLIFIERS

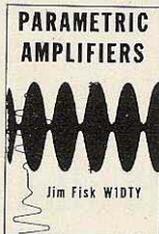For the ham who wants to work DX on the bands above 432 MHz, there is nothing that can beat the gain and noise figure of a paramp. This book shows you how they work and how to build and use them. Lavishly illustrated with photographs and drawings. **\$3**




HAM TELEVISION

The Amateur Television Anthology is a collection of the technical and construction articles from the **ATV Experimenter**, edited by WØKYQ. If you're interested in ATV, this is the book for you. It covers the gamut from the simple to the complex in amateur television equipment. **\$3**



HAM RTTY

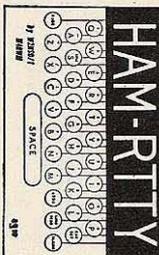More and more hams are joining the RTTY crowd every day. This 112-page book gives you all the basics and tells you what you need to know to get started and get on the air. Written by W2NSD and W4RWM. **\$3**



CW by W6SFM explains code and how to learn it. **50c**

MILITARY SURPLUS TV EQUIPMENT by W4WKM is a necessity to the surplus-scrounging ATV addict. **\$1**

CUMULATIVE INDEX lists all the articles in 73 up through December 1966. **25c**

- Transistor Circuits\$1.00
- Index to Surplus\$1.50
- Parametric Amplifiers\$3.00
- Ham RTTY\$3.00
- VHF Antennas\$3.00
- Simplified Math\$.50
- ATV Anthology\$3.00
- CW\$.50
- Military TV\$1.00
- Cumulative Index\$.25

Please send me the books checked at left:

Name Call

Address

City State Zip

Books shipped prepaid in US and Canada.

73 Magazine

Peterborough, N. H. 03458

So You Think You're on Frequency

Ken W. Sessions, Jr.
4861 Ramona Place
Ontario, California 91762

In at least one area of the United States a quiet war was recently waged by two separate and very active amateur groups. One of these groups is a two-meter RACES net operating on 146.84 MHz AM; the other is an FM channel in 146.82 MHz. The malcontent stemmed from the fact that individuals of both groups had frequently found themselves transmitting simultaneously on a single frequency. Not unnaturally, each person thought the other had drifted off his original frequency.

The AM net operator, just to be on the safe side, double-checks his crystal and verifies that he has the correct one inserted. He wants to lean over backward to be fair. He cursorily checks his transmitter stages to make sure all are properly functioning. Everything checks out. His crystal is plainly marked 146.84 (or some integral multiple thereof). He wonders why those FM operators don't realize their frequency errors. And the wonder eventually turns into a smouldering suspicion that perhaps the FM hams who purport to operate on 146.82 are deliberately interfering with the net. A strong accusation, but still . . .

The FM'er is crystal-controlled on 146.82 MHz. At least once each week he must suffer through the erratic squelching, garbled voices, and foreign carriers that stagger across his sacred channel as the AM hams check into their .84 net. He watches his bobbing, frenzied discriminator from time to time during check-in and cringes when he thinks of how much spectrum those stations consume, taken collectively. With disdain that nearly always turns to hot agitation, he notes that those net check-in stations may transmit anywhere between 146.81 and 146.87 MHz. But from experience, he knows that each check-in station—if challenged—will take an oath to being on 146.84. The FM'er has tried to explain the telling honesty of his discriminator meter to the AM stations in the past, but he's long since given it

up as hopeless. The AM net operator is crystaled on—and everyone knows crystals don't lie!

So this is the biggest point of contention: To the net operator, 146.84 is whatever the signal is when the crystal is cut for .84 operation. To the FM station, 146.82 is wherever the signal is when the discriminator meter reads zero. The very honest fact is that the FM'er knows something the AM net check-in station probably doesn't: A crystal is NOT an absolute frequency-determining device.

The FM'er's crystal probably cost him around seven dollars; it was *specialy ground for the circuit in which it is used*. The crystal manufacturer calculated circuit capacitance and other factors *based on this individual circuit information* to make sure the crystal would put the operator squarely on his "channel." Conversely, the AM station's crystal was probably cut without regard to the peculiar circuit parameters of his individual oscillator. As likely as not, his was originally a military crystal intended for use in an oscillator with a load capacitance of 32 pF. Or perhaps a commercial crystal intended for use in a 20 pF circuit.

Most amateurs aren't even aware of the differences. Most of us don't even know what type of oscillator our transmitters are using, let alone the load capacitance of the crystal circuit.

Whether or not the FM stations were at fault or the RACES net check-in stations were operating off frequency is really immaterial. What *is* important is the fact that a crystal *is not* an absolute frequency-determining device. This may come as something of a shock to bandedge operators who've been thinking they were safely operating all these years because they were crystal-controlled. There are a number of hams who say nasty things about crystal companies after they've been cited for off-frequency operation. But the crystal outfits aren't to blame. If there is

blame to be placed, it must rest at least partially with the amateur himself.

The frequency stability and electrical behavior of a crystal may be considerably altered when the crystal is used in a circuit other than that for which it was intended. So what about all those FT-243's, you ask? What, indeed; they're no exception! It is the responsibility of the amateur to know his own frequency—and that means knowing something about the crystal he's using as well as the oscillator circuit.

Have you ever listened to an active net with a selective receiver? If so, you've probably wondered how so many close-tolerance crystals could be on so many different frequencies. Again, as likely as not, the fault may lie not so much with the crystal as with the circuit. Some oscillator circuits "pull" crystals to such an extent that the actual operating frequency may be as much as 20 kHz off the intended transmitting spot.

The crystal

In many ways a good crystal is like a poor hi-fi speaker. They are both transducers, for instance, that have the capability of converting electrical energy into mechanical energy (and vice versa). Both have resonant frequencies where they will react more freely to the induced energy. A poorly designed speaker will react violently to input signals near the resonant frequency, and will tend to "boom" as the signals approach this resonance. A well-designed crystal yields a reaction that is similar in many respects. As the induced ac voltage across the crystal approaches resonance, the quartz element becomes very stable and will tend to exhibit a high degree of activity.

For communications applications, there are two common types of crystals in general use. One is the plated type, the other is pressure-mounted. In general, the plated type is superior, but both have the ability to maintain a very high degree of accuracy on their established frequencies.

This is not to say that crystals can't be wrong, themselves. They can—and very often are! But a good crystal of the plated type, furnished by a quality-conscious manufacturer (such as Sentry or International) will very likely be *right*. Crystals that go wrong are usually the pressure-mounted types—the FT-243's that depend on stored energy from a mechanical spring to hold them in position.

The surplus FT-243 crystals are very vulnerable to frequency change because of the possibility of positional shift between the crystal blank and the pressure electrodes, and because of gradual—perhaps even imperceptible—pressure changes.

But even if surplus pressure-mounted crystals were perfectly error-free, the problem of off-frequency nets would still exist.

Oscillator parameters

The two prime determinants of actual oscillating frequency are crystal current (drive level) and oscillator load capacitance. If you order a crystal when you're not sure of these factors, you will have no way of knowing how far off frequency you're going to be.

The most universally used value for oscillator load capacitance seems to be 32 pF; most first-rate crystal companies supply crystals to this value when the load capacitance is not specified by the buyer. But the 32 pF value is by no means restrictive; a large number of equipment manufacturers design oscillator circuits with widely varying capacitance requirements.

Most commercial and military two-way radios are designed with a variable capacitor in the crystal circuit so the crystal can be "bent" to frequency once it has been installed in the oscillator circuit. This seemingly important feature, for some unknown reason, is not usually included in amateur transmitters.

The table below shows the actual operating frequencies of a crystal cut for use in a 32 pF circuit of a parallel-resonant oscillator. The first column shows the actual design frequency (which is the end frequency when the crystal is used in the proper circuit). Note how the frequency drops as the load capacitance increases. The last column shows the resultant frequency of the crystal when used in a series-resonant circuit. (Although admittedly not particularly common, series-resonant circuits do appear in amateur transmitters from time to time. The old Black Widow line of VHF transceivers and Robert Dollar units used circuits of this type. At 50 MHz, the Black Widow operator was always about 10 kHz below the rest of the gang.)

It should be noted that series-resonant circuits are not necessarily inferior to parallel-resonant types; the important point is that

their requirements are different. In a series-resonant oscillator, the crystal is in series with a resistance. The crystal appears resistive, and load capacitance is no longer a determining factor with respect to frequency of operation. But unless the crystal is ordered specifically for a series circuit, the user will probably find himself considerably lower in frequency than he'll want to be.

In parallel resonance, the crystal is placed in series with a capacitance, so it appears as an inductive element to the external circuit. Any change in circuit reactance will affect the frequency of oscillation. This mode is of characteristically high impedance and the resulting frequency is higher than that of the series-resonant crystal. The frequency of the crystal may be lowered by increasing the series capacitance or raised by decreasing it.

What can you do?

While I was preparing this article, I wrote to Sentry to obtain permission to use some of the information contained in the technical section of its 1968 catalog. In answering my letter, Mr. George Beyers, president of Sentry Manufacturing Company, said that his company is anxious to supply on-frequency crystals as most amateurs are to receive them. He said his company would be happy to correlate the frequency of a crystal circuit if enough information were made available in each case. So that provides you with at least *one* way to be certain of your frequency: if you want to operate on a specific frequency and you haven't ordered your crystal yet, you're in good shape. Determine the fundamental crystal frequency range, the desired operating frequency, then make a copy (even a sketch will do) of your oscillator schematic. Send the information to Sentry and wait for your crystal to be returned by mail. You can rest assured it will be exactly on frequency.

If you have no frequency-measuring equipment, but a known-to-be accurate signal is available, you can vary your existing crystal capacitance until you zero-beat the known signal. This is a particularly useful

solution for a group of amateurs who participate in net activities. Netting several stations to a given frequency is a project that requires very little time, but one which is particularly rewarding for those who must monitor the net with narrow-bandwidth receivers. Adjacent-frequency stations will also be appreciative, you can be sure. These operators may position themselves far enough away from a net that the two concurrent operations could easily be accomplished. But the off-frequency check-ins always seem to find their mark; and the result is the same as it was in the case of the FM channel versus the RACES group: hard feelings and unnecessary animosity.

Varying the crystal capacitance to a frequency adjustment may be accomplished by replacing the load capacitor (between one side of the crystal and ground) with a trimmer. The original capacitor value should fall approximately in the center of the trimmer's range. In some oscillator circuits, the fixed capacitor that must be replaced is across the crystal itself. The proper capacitor won't be hard to find, in any case. A little experimentation should yield fruitful results.

Measured Crystal Frequency at kHz at:

32 pF Load	15 pF Load	40 pF Load	100 pF Load	Series Resonant
1000	1000.125	999.975	999.915	999.865
3000	3000.625	2999.880	2999.565	2999.315
5000	5001.325	4999.730	4999.020	4998.225
7000	7002.225	6999.525	6998.250	6997.250
9000	9002.835	8999.400	8997.800	8996.500
13500	13503.800	13499.270	13497.250	13495.750

Copyright 1967 by Sentry Manufacturing Co., Reprinted by permission.

An objective observer viewing the cold war that brewed between the two closely spaced net activities on 146.82 and 186.84 MHz might smile with grim amusement. But to those participants, the problem was real and serious. Fortunately, the frequency-netting solution is simple and easy to effect. It's really a wonder someone hasn't thought of it before!


... K6MVH



TELREX (Patd.) "BALUN" FED "INVERTED-V" ANTENNA KITS

EASY-TO-INSTALL, HI-PERFORMANCE LOW-FREQUENCY ANTENNAS

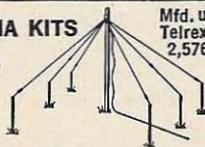"Mono" Bands from \$23.95—Also "Trapped" 2 and 3 Band Kits.
3, 4 or 5 Band "Conical-Inverted-V" Antennas from \$52.95
3, 4 or 5 Band, 5 to 10 DB—"Empirical"—I.V.—Logs"—S.A.S.E.



Mfd. under
Telrex Pat.
2,576,929

WRITE FOR
TELREX PL 68

TELREX COMMUNICATION ENGINEERING LABORATORIES—ASBURY PARK, N. J. 07712

Parallel-T Network Design

Jim Kyle
1236 N. E. 44th
Oklahoma City, Okla. 73111

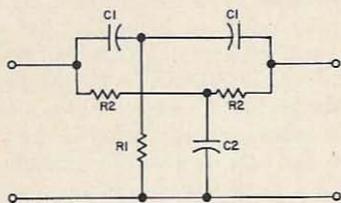


Fig. 1. The Parallel-T Network.

The Parallel-T network (Fig. 1) is a little-known RC circuit which produced infinite rejection of one specific frequency provided that resistance and capacitance values in it are properly chosen. This rejection property makes the network valuable for use as a lightweight low-current power-supply filter, for removing unwanted single-tone signals from amplifiers, and for use in feedback networks to produce oscillators and selective amplifiers.

Values of R_1 , R_2 , C_1 , and C_2 are all inter-related, and will determine both the frequency of infinite rejection (f), and the sharpness of the rejection notch. Most published data on the Parallel-T treats only the case where R_2 is twice the value of R_1 , and C_2 is twice C_1 , but in actuality any set of relationships which will satisfy the following three equations at the same time will function as a Parallel-T:

$$1/wC_1 = KR_2; \quad 2R_1 = K^2R_2; \quad \text{and} \quad 2/C_2w = R_2/K.$$


(In these equations, K is a constant which determines the proportions of R_1 to R_2 and C_1 to C_2 , and w is equal to $2\pi f$. If f is in cps, R_1 must be in megohms if C is to be measured in microfarads).

The algebraically inclined can solve these equations to learn that the most-published version of the Parallel-T is that for a K of 1. However, if $K = \sqrt{2}$, or 1.414, so that R_1 and R_2 are equal, the slope of the sides of the rejection notch will be steeper. Versions published for use as audio notch filters consequently are usually based on a K of 1.414.

The accompanying nomogram can be used to solve the Parallel-T equations for any

desired values of K and f , to an accuracy of better than 2 percent. The result is a product, R_2C_1 , which in turn determines the values of all components. Either R_2 or C_1 may be chosen to be any desired value, and divided into the product to learn the value of the other. The table in the nomogram gives values of R_1 in relation to R_2 , and C_2 in relation to C_1 , for all listed values of K .

For instance, to determine proper component values for a Parallel-T to operate at 1000 Hz, with a K of 1.414, and a value of 10,000 ohms for R_2 , first draw a straight line on the nomogram to pass through 1000 Hz and $K = \sqrt{2}$. Either the 1 or the 10 on the f scale could be used, but the 1 mark (together with the "X 10" K scale) will give greater accuracy. This line passes through 1.10 on the R_2C_1 scale. To locate the decimal point properly, note that the frequency-scale units were "Hz X 100" (the added X10 multiplier was obtained by using the "X 10" K scale). Reference to the

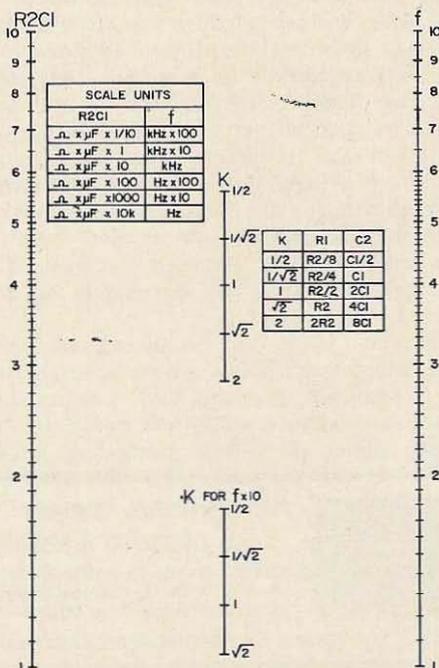

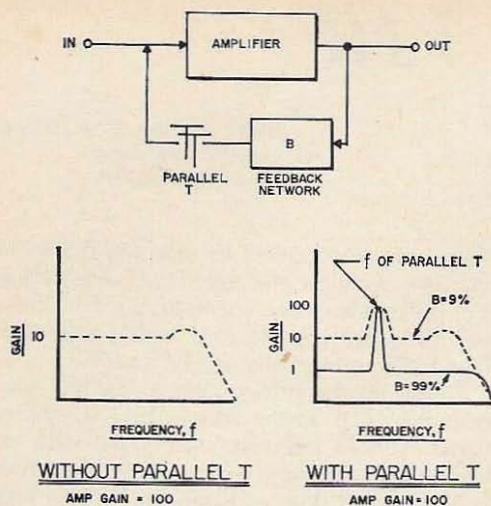


Fig. 2. A parallel-T in series with the feedback network of a degenerative amplifier.

chart shows that in this case, R_2C_1 is in ohms \times microfarads \times 100 so the true value is 110 ohms \times microfarads.

Next, divide the R_2 value of 10,000 ohms into the R_2C_1 product of 110 to determine the value of C_1 . In this case, it is 0.011 mfd (in practice, one 0.01-mfd and one 0.001-mfd unit would be connected in parallel to make up the total value). The table shows that with a K of $\sqrt{2}$, R_1 equals R_2 and would be 10,000 ohms also. C_2 equals four times C_1 , or 0.044 mfd.

The actual choice of K and R_1 is based on several considerations, which vary depending upon the purpose to which the completed network will be put.

For use as a power-supply filter with the rejection notch placed on the predominant ripple frequency, the important considerations are to keep the total series resistance (twice the value of R_2) at a minimum and at the same time to minimize the capacitance requirements. These considerations are contradictory. A K of 1.414 will minimize the value of R_2 , but a value of 1 for K will minimize the total capacitance requirements. In addition, for any specified frequency and K , choice of a low value for R_2 will require high values of capacitance and vice versa. The resulting compromise must be made on the basis of the current to be drawn through the filter, and the space and weight limitations. Typical values used in practice for a ripple frequency of 120 Hz would be $K = 1$, $R_1 = 75$ ohms, $R_2 = 150$ ohms,

$C_1 = 8.75$ mfd (8 mfd actually used in practice), and $C_2 = 17.5$ mfd (16 to 20 mfd actually used). Rejection exceeds 80 db at design frequency.

Placing a Parallel-T in series with the feedback network of a degenerative amplifier (Fig. 2) converts it into a frequency-selective amplifier, by reducing the negative feedback at the Parallel-T's frequency of infinite rejection. Thus the feedback can be arranged to maintain the amplifier's gain at 1 throughout most of the passband, and at the design frequency gain will rise to the no-feedback value.

Adding a minute amount of positive feedback to this selective amplifier will turn it into an oscillator. Positive feedback should be kept to a level which will just permit oscillation, while negative feedback (except at Parallel-T design frequency) should be such that gain without positive feedback is unity. The resulting oscillator produces the lowest distortion of its output of any known; the major reason it is not more widely used is that its frequency is determined by three component values while the popular Weinbridge requires variation of only two elements.

In either the selective-amplifier or oscillator application, the major considerations are to maintain the impedance of the Parallel-T at a level compatible with that of the feedback network. At frequencies far below that of infinite rejection, the Parallel-T becomes effectively $2R_2$ in series with the load. At frequencies far above, it becomes essentially R_1 in parallel with the load. Thus wide impedance variations with frequency are unavoidable.

However, choosing K equal to 2 will make $2R_2$ equal to R_1 , so that if R_1 is then chosen to be equal to the load resistance the total impedance will vary from twice that of the load (at low frequencies) to half the load (at high frequencies). This is the minimum impedance variation with frequency which can be obtained from a Parallel-T.

The impedance variations, though, need not be considered a drawback in many applications. A resonant-circuit trap to produce the same effect has similar variations. And the Parallel-T does offer the advantage of much smaller space and weight requirements when dealing with extremely low frequencies, not to mention being less costly to construct in many cases. ■

Starting Off on VHF

Ralph J. Irace Jr. WA1GEK
4 Fox Ridge Lane,
Avon Conn. 06001

With the advancements of current VHF equipment and the continued pursuit in moonbouncing, experimentation, FM'ing etc., VHF operation nowadays is becoming more and more intriguing and certainly offers many rewarding challenges absent in low band territory, where most green eared general's flock for so called "push the button" operation.

Great strides in VHF achievements have been made over the years on every VHF band that exist (when we refer to VHF, this includes 220 mc and 432 etc.). However there still remain vast segments in the VHF frequencies where there is virtually no activity. Some amateurs and organizations have prognosticated that the FCC won't be long or very reluctant in claiming back portions of the current VHF frequencies, generously allocated to us amateurs. This interpreted into another manner means that if we are to retain current VHF frequencies and the privileges that go along with them, we must all help spark more interest in VHF work and if possible, contemplate VHF setups for ourselves, preferably on 2 or 6 meters and both if possible.

You've probably come across half a dozen or so advertisements highlighting the newest and most recent VHF equipment on the market. And while perhaps not as attractive as a nice low band kilowatt transceiver, you're probably much intrigued as to just what these VHF rigs can do. If you've never been on VHF before, I suggest you start off with a low cost transceiver for say \$50.00 or so. Heath company currently offers the "lunch box series" of either a 2 meter transceiver (HW-30) or the 6 meter version (HW-29A). Both units are identical in physical appearance and structure and each sells for \$44.95 apiece kit price complete with built in ac power supply and a ceramic microphone. Crystals and a dc power supply are optional. Assembling either unit is simplicity in itself and as a rule, can be completed in a few evenings of consistent work. Transmitter power input is 5 watts and the receiver is of regenerative type. The current ham publications occasionally offer modification plans for

these two transceivers in case you'd like to improve upon its performance. I don't think I'm sticking my neck out in saying that these two little rigs are the most widely used low cost VHF transceivers around today.

Going up the price ladder you'll find several 2 and 6 meter transceivers manufactured by both Lafayette and Allied with an average power input of 20 watts. Receiver is of superhet type and built in VFO is also among the features. Other manufacturers include Clegg Laboratories, Gonset, Johnson in addition to several others. A brief letter requesting their catalog of VHF gear should do the trick and is your first step in becoming familiar with what's on the scene.

What about antennas? Among the numerous VHF antennas are yagis, ground planes, Halos dipoles, collinears, verticals in addition to others. VHF antennas in the majority of cases are much smaller than HF antennas, but the dozens of methods you can use in stacking beams, adding reflectors, experimenting with them, building and designing them, etc., makes VHF antennas a field by itself. Some VHF'ers stack up to five beams one on top of another resulting in a directive gain of over 50 db and sometimes more. Others like to homebrew and construct their own antennas sometimes putting up to 50 elements on one boom! Obviously, VHF antennas offer a unique opportunity to build your own skywires and simultaneously learn more about antenna construction and theory. The complexity to which VHF antennas may grow is startling. Some of the more advanced and sophisticated antennas used often for moonbouncing, microwave and several other uses are parabolic dishes, helical antennas, screen reflectors and corner reflectors. Some amateurs may stack half a dozen collinear antennas to form an array of enormous gain while others employ perhaps one screen reflector to equal that of the array of collinears. The amount of gain you want and the purpose for its need most often prescribes what kind of VHF antenna installation would be feasible.

Starting off with a commercially built halo antenna will give you adequate local coverage if you have a fairly good location and when hooked up to a low power 2 or 6 meter transceiver, will often provide reliable coverage and makes a dandy little outfit for rag-chewing and net coverage. Extending your range using the same low power rig can be accomplished by installing a moderate 2 or 6 meter beam. Seven element 2 meter beams can be had for between \$10-\$25 depending upon the type and brand. 6 meter beams with three to four elements sell for \$15-\$30. Installing a yagi beam is no more difficult than installing a good size TV antenna. Attention should be given to the use of a balun however, an item often neglected by many VHF'ers. Use of a rotator is an absolute must if you do intend to use a beam antenna. The many disadvantages of using a beam without a rotator is obvious since the beam will transmit in only one direction and when in net operation with hams in all directions, you'd be lost. Same applies to roundtables with hams in different directions. 50 ohm coax is the feedline used in the vast majority of VHF rigs and its losses through somewhat higher than those of 300 ohm twinlead and open-wire line, are for the time being unimportant.

Range? Normal ground wave transmission on 2 and 6 meters with a power usage of 5-20 watts will as a rule exceed 20 miles and go as far as 45-50 using an omni-directional antenna of appreciable height. Using a beam will extend the range up to 60-70 miles and an occasional 100 mile contact isn't by any means rare. Making use of the ionosphere will of course stretch your signal for a long distance. Tropospheric bending is the most frequently encountered form of DX and 150-200 miles most often prevails in this case, though greater distances have been reached. F2 layer DX occurs at peak years of the 11 year sunspot cycle, and produce ranges nearing 2000 miles. F2 layer DX works well on 50 MHz operation only. Sporadic E layer DX is another frequent ionospheric occurrence and normally will produce 400-700 miles or so on 50 MHz and up to 1400 miles on 144 MHz operation. Meteor scatter and moonbounce, among others, are all effective means of obtaining great distances with relatively low power equipment.

This article merely introduces the basic concept of what to expect on VHF, what's

HUNTER

LINEAR AMPLIFIER

by Hunter



BANDIT 2000C

- 2000 watts PEP ●
- Five bands ●
- Kit form ●

Write for details

HUNTER SALES INC.

Box 1128A

University Station

Des Moines, Iowa 50311

RENEWAL CODE

The two numbers under your call on the address label are the expiration code. We have tried to make it simple. The first number is the month that we send you the last copy on your subscription and the second number is the year. 78 would be July 1968, for example.

YOU WON'T BELIEVE WHAT WE SAY ABOUT THESE FINE NEW UHF BEAMS

—until you get the laboratory reports
WRITE TODAY



NEW! "Multifeed Beams"

J BEAMS

50 MC.—
144 MC.—
220 MC.—
432 MC.—
Arrays,
H Frames,
Towers, etc.

"Continuous reception over 141 mile path on 144 MHz", writes W4ISS/A4ISS

- Multiple driven elements
- Multiple reflectors
- Low SWR
- High front to back Ratio

Distributors invited


Dept. 79, Phone (312) 568-1973, 27 E. 112th Pl., Chicago, Ill. 60628

GAIN, Inc.

needed to begin and why more activity in this region is desperately needed. 220, 432, 1200 mc and higher have to be further explored and pioneered. For additional information on VHF operation, I strongly suggest you obtain a copy of the ARRL "VHF manual" available for \$2.00 directly from League headquarters. If you have any further questions, I'd be glad to hear from you and would like to discuss the matter at length. You might also pen a letter off to 73 Technical Aid Group which is at your service for any assistance you might require. Good luck!

... WA1GEK

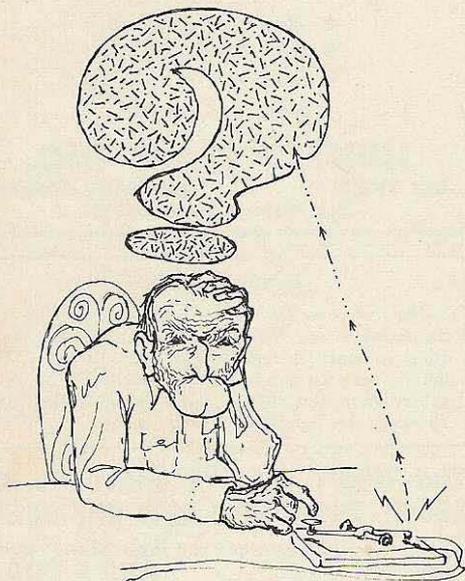Learning the Radio Code if You're over 30



Do you think aging is an obstacle to learning the radio code? If you are over 30 or 40 or so and you have been thinking of getting a ham ticket, learning the radio code probably looks like the hardest requirement. Actually, it seems to be the hardest requirement for people of *any* age. But if you feel your age imposes a specially tough barrier you are only partly correct. Very probably the difficulty looks much worse to you than it actually is.

The age problem

Any man at age 35 knows he could not win a footrace with himself at age 19. Yet he rarely wishes to trade off those years of experience, either, because he knows how much he has gained. And few 19-year-olds, however aggressive they may feel, will challenge a solid relaxed-appearing middle-aged man in a bar. The younger man per-

ceives a certain stability and potential grim determination the older man can summon up if necessary, and he knows his youth might not be such an asset after all.

Yet our society places an almost frantic value upon youth and is so full of divisions between people the older person undertaking a new project almost certainly must feel at a disadvantage. There are stories of loss of learning ability and of mental capacity, and there are other disadvantages too, against taking up something new that is not related to previous experience or to the work at hand.

For instance, the older man very often has very little spare time. Business and family demands may keep him jumping to the time of a drummer he would rather not hear so much, but he cannot escape the beat. There is rarely an adequate place to study anywhere in the house, and code practice work is often very upsetting to others nearby who are not so interested in ham radio. And starting from scratch, while challenging, can also be a tough uphill operation in which hard work seems to generate disturbingly few results of any kind.

And it is perfectly well established there really is a decline with age of learning ability. This may be too obvious in very elderly people, whose memories tend to show a curious porosity for recent events but excellent recall for things that happened many years previously. Concentration span may be reduced, too, so that an older person cannot accumulate long hours of hard study at the same rate as a younger person. This all certainly sounds ominous, at the very least. Now, is it as bad as it sounds?

Something about learning

If we want to maintain a correct perspective on any problem we ought to do some book work. What are the facts? There is so much information available you can become swamped in it or entirely carried

away. This effect appears in medical schools for example, where as new diseases are introduced and studied there is much concern among anxious students who feel they may have developed these illnesses. Tiny things are magnified by too much attention, but when you discover this effect your perspectives can be rearranged to a truer schedule.

The overall picture of aging effects upon learning ability is surprisingly cloudy. The changes are so small up to age 60 or so (on the average) that researchers are still having considerable difficulty in establishing solid results. Natural differences between people are very large compared to differences due to aging.

Test results indicate a fairly definite peak in learning ability somewhere in the third decade, ages 20-30 years, and a rolloff beyond that decade. But researchers are very careful to indicate they do not know what causes the rolloff, and they suspect a large part of the changes they think they observe are caused by psychological and social changes, rather than losses of inherent learning ability.

For example, studies of training older workers for new jobs have indicated the older worker may simply not be as strongly motivated as the young man. Society expects less of him, he expects less return from society, and has probably lost some, or maybe even all, of his youthful enthusiasm through hard knocks and frustrations. You can find this attitude in some conversation without looking very far at all.

Another cause of reduced effectiveness is the very real need for an older person to do better than a younger one. After all, he has been around longer, hasn't he? Should be able to do better. But the younger man has just completed 12 years of school, say, and perhaps four or five years of college. This is a far tougher experience if he worked at it. At age 17 you may have been viewed as a youngster by your parents and others, but you were also a battle-hardened veteran of many learning emergencies. You were

accustomed to everyday hard questions, challenges, tests, book work, writing essays, dodging hard problems. You often succeed, and are not very upset by a prospect of failure. One, two, or three decades later you're so far out of shape for this stress you hardly recall what it's like much less what to do about it. You could panic now, and many older beginners really do.

Research indicates you can achieve practically as well as when you were at your peak, but you've lost the skill. This has been studied closely and one example is that of two professionals aged 35 and 72 years respectively. They did equally well in individual tests but when placed in competition under close observation the older man couldn't take it. He did far poorer work at learning than in previous unforced, non-competitive work.


The anxiety and work-against-pressure and competition effects appear to be the real obstacles in learning the radio code. Tense and worried, you notice the young fellow working like mad in the next seat. Feeling like a relic, candidate for fossil, you probably forget that young as he is he's a veteran, and old as you are you're a beginner. You've been psyched, you're sinking, and your general mood may be as low as panicky despair.

What should you do now?

Learning the code

Well, don't quit. Have a talk with yourself, rearrange your perspectives, and go back at it. You probably were not using the best approach anyway, although this is where your advantage lies. You do have a special strength! The younger man has slightly more learning ability, you have much more experience in life situations. He *can* persist longer than you can but probably you will persist longer than he *will*. He has fewer other things to do but you are more able and inclined to organize your time to best benefit for the job at hand. Now let's look at this code learning problem.

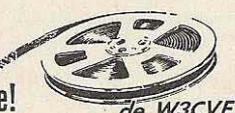LEARN CODE
the right way—with
Code Sound Language!



"The specialized language of sound" brings you a complete study of the International Morse Code. Satisfied users say—"Complete in every detail!"—"Easy to learn!"—"CSL is the best!"—"Increase YOUR receiving speed, master the code now! ★★★★★

CSL NR 1 & NR 2 (1 tape) for the prospective Novice, Technician, General or Amateur Extra First. 3 to 25 wpm.

CSL NR 3 & NR 4 (1 tape) for the advanced operator with a sincere desire to copy code sounds at rapid speeds. How to copy behind, etc. 25 to 55 wpm. Both tapes, plenty of copy—plain and scrambled, numerals and punctuation.

Magnetic tape, 7" reel, dual track, 2 hours. Immediate delivery. Send check or money order. (Specify which tape.) \$6.95 each.

Both tapes on one order, only \$13.50.

Sound History Recording, Dept. 73, Box 16015, Washington, D. C. 20023

SPECIAL TV CAMERA PARTS KIT

ONLY

\$99.95

including vidicon and lens!

To meet the many requests for a low-priced solid state TV camera kit, we have made available from our factory stock the following parts which you can assemble at very little additional expense into a superb TV camera. Included in the kit are the following:

1) **Completely assembled and tested video amplifier plug-in circuit board with a 10-transistor 6 MHz bandwidth amplifier and keyed clamp with adjustable pedestal and sync mixer.**

2) **Completely assembled plug-in sweep circuit board with 8 transistor and 5 diode horizontal and vertical sweep generators and amplifiers featuring excellent linearity and more than enough drive for 1" vidicons.**

3) **Excellent quality deflection yoke and focus coil with beam alignment magnets and raster positioning adjustment. Also included is the vidicon tube clamp and target connector.**

4) **Camera tested vidicon excellent for amateur use and matched to the deflection assembly above.**

5) **Good quality F1.9 or better achromatic lens with matching lens mount.**

Note: All items are brand new except vidicons which we guarantee will work with the parts kit supplied when assembled according to the schematic and adjusted according to normal procedure. Since step-by-step instructions are not available, we recommend this kit only to those who can follow a schematic.

Due to the low price and limited quantity, we cannot sell the above components separately.

When our present stock is exhausted, it will cost at least \$160.00 to repeat this offer. Order now to avoid disappointment.

VANGUARD LABS

Dept. H

196-23 Jamaica Ave., Hollis, NY 11423

There are three basic parts to learning. They are: Registration, Retention, and Recall. The code signal registers, and it registers best if you are not distracted by other problems or sounds. It sticks best if it registers well and there are not too many other recent things on your mind to compete with it. Finally, the meaning is recalled most easily if the previous two requirements are met, and if the recall process is well lubricated by recent practice.

After a decade or three out of school you tend to forget how slow the learning process really is. Over a period of time you have become accustomed to using familiar information and hardly ever finding new facts, to settle matters most usually worked out in minutes or hours at the most. Now, how long does it take to learn the code?

To reach 13 words per minute, 70 hours or more! At the recommended schedule of a half-hour study per day, that works out to 140 days and you'll need more time yet to attain a higher speed or if your practice schedule is not *daily*. In your second decade this gradual progress was a way of life. You forgot about that, didn't you?

Experience and study suggest the best way to get by with least expenditure of time. Firstly, find out what the books say about learning the code. If you just jump in you are passing up the results of other people's useful experience. A good description appears in the Radio Handbook. Unfortunately, the few paragraphs in the Radio Amateur's Handbook are worse than useless because they imply there is nothing more to it than appears there.

Then set up a study/practice schedule, same time and same place every day. Set yourself at it for a half hour, and for a couple of weeks or so do not ever exceed that time. Stick to your schedule. If later you feel you can profit by longer sessions, try it. But do not work into exhaustion.

If you can possibly find or borrow code tapes or records, use them. They are the very best practice, but many hams have learned the code off the air. You can do it too but it will take longer than a well-prepared schedule of exercises.

Next, stay with it. Do you know what a "plateau" is? This is a familiar experience to educators and to persons whose business is study and learning. A "plateau" is a period in which you are working like mad but there seem to be no results. One of the

purposes of your study schedule is to keep you going from habit if nothing else while you are getting through a plateau experience.


Various persons have different difficulties in code learning, but there is one that probably is common to all. This is learning to "copy behind." In the first stages of learning the code, you are simply discovering which letters have which sounds. You will probably experience plateaus in this part of the work. But then you come to a stage at which you need to copy faster but the concentration on writing interferes with attention required to listen to the next letter.

As you continue working at this you are learning to put part of the work into the back of your mind where it goes on without attention. This is a skill that is hard to learn and probably every amateur you can find will give you another story about how he made it over the hump. At this stage in your progress you should think sometimes about how you drive a car, carry on a conversation while watching the other party. There are many things you already know how to do correctly without paying attention to the details. You have the ability but must train your mind in this new application of it.

I did not find anything while I was working up this article to indicate there are some people who are inherently unable to learn the code. Reading this work was a harder job for your mind than reading a code signal, although the code may be a less familiar way of communicating. If you're a beginner get onto the problem and you will learn the code with considerable effort as we all do, and if you have given it up in despair go back and try again. Plan ahead this time, and good luck!

... W2DXH

LEARN RADIO CODE

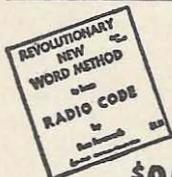

\$9.95

Album contains three 12" LP's 2 1/2 hr. instruction

THE EASY WAY!

- No Books To Read
- No Visual Gimmicks To Distract You
- Just Listen And Learn

Based on modern psychological techniques—This course will take you beyond 13 w.p.m. in **LESS THAN HALF THE TIME!**

Also available on magnetic tape. See your dealer now!

EPSILON RECORDS

206 East Front Street, Florence, Colorado

SPACE AGE KEYS

Only
\$67.50



- Planar epitaxial integrated circuits for reliability. No tubes—No separate transistors.
- Precision feather-touch key built-in.
- Fully digital—Dot-dash ratio always perfect.
- No polarity problems—Floating contacts switch 1-amp.
- Rugged solid construction—will not walk.
- Send QSL or postcard for free brochure.

PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CAL. 92026

FOR THAT

"Extra Class"

YOU NEED THE

BT-LK-2000

LINEAR

AMPLIFIER

For SSB, CW, RTTY

Maximum legal input

Full loading 80-10M

Rugged Eimac 3-1000Z

Dependable operation

Easy to load and tune

No flat topping with ALC

Distinguished console

Instant transmit

High efficiency circuit

Designed for safety

Fast band switching

Real signal impact

Price . . . \$79500

READY TO OPERATE!



Listen for the hundreds of LK-2000 linears now on the air and judge for yourself. Write for free illustrated brochure or send \$1.00 for technical and instruction manual.

BTI AMATEUR DIVISION

Hafstrom Technical Products

4616 Santa Fe, San Diego, Ca. 92109



Oscars . . . Emmies . . . and for the Amateur . . . The Sarah

The next annual SAROC (Sahara Amateur Radio Operators Convention) in Las Vegas will be the scene of the most elaborate and extensive amateur radio "awards" program ever attempted. Sentry Manufacturing Company has just announced the initiation of a continuing annual award presentation program for the ham radio world, to be conducted concurrently by the leading amateur journals.

In a ceremony resembling the Oscar and Emmy affairs of Hollywood, prominent amateur radio operators will be awarded "Sarah" trophies, each of which is inscribed with (1) the winner's name, (2) the category for which the award is presented, and (3) the name of the amateur journal which determined the winner. The name Sarah was chosen because of its similarity to Sahara, the Las Vegas hotel where the presentations will take place, and because it is a natural acronym for Sentry Amateur Radio Award of Honor.

73 will distribute awards for DX, VHF, public service, best technical article of the year, best nontechnical article of the year, and best published solid-state design of the year. 73 will also present one additional Sarah to the individual considered by the staff to be the Outstanding Amateur of the year.

All but the last mentioned category will be determined by 73 readers on the basis of mailed in nominations which will be accepted until 10 October. On this date, three individuals will be selected from the nominations for each category as finalists; their names will be published in the December issue of 73. The names of these candidates will be forwarded in early December to the Sarah Committee, who will objectively evaluate the candidates and select the winner in each category. The Committee's decisions will be final.


Once the Sarah Committee has made its decisions, the winners' names will be forwarded to Mr. Ray Meyers (W6MLZ), a prominent west coast amateur, ham radio columnist for the Los Angeles Herald-Examiner, and radio commentator. Mr. Meyers, as emcee for the SAROC breakfast banquet, will make the actual award presentations.

No photo of the trophy is available yet, because the original design work is still under way. It will have the general character and size of a conventional Oscar award, however, consisting of a male figurine about 15 inches in height. The figure will bear a lightning bolt representing electromagnetic radiation and will be supported on a small pedestal of marble encircled by a metal band for the inscriptions.


Selecting Nominees

Nominations are now open for the six listed categories. Use as much paper as necessary and list the names of your candidates in any format you choose. For each category, try to list the name, call, and address of the individual you have named. (This is not mandatory, but it would be immensely helpful when it comes time to notify the winners.) In as few words as possible, tell your reasons for selecting your candidate. You are entitled to only one nomination per category per journal, so be sure to sign your name and list your own call letters. Here are the particulars on the six 73 Magazine categories:

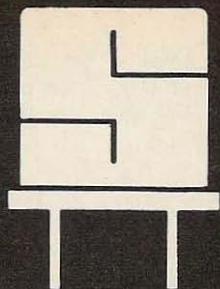Best Technical Article of the Year.—Look through the pages of back issues of 73 to September of last year, and pick out the one technical article that seems outstanding to you for some reason. Perhaps it was a useful circuit that you used; maybe it was an informative piece that did a good job of filling in fuzzy spots in your theoretical understanding of a subject. What-







SPEED


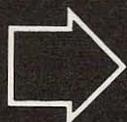


24 HOUR DELIVERY

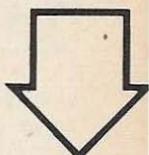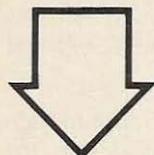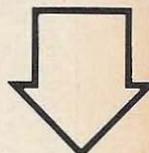
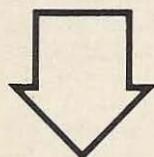
We guarantee that we will ship all orders for 10 crystals or less within 24 hours of receiving the order.



Buy The Best

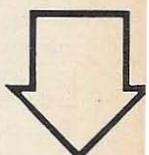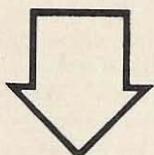

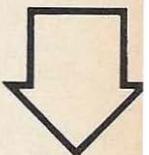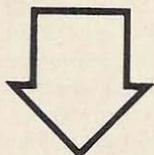SEND FOR OUR 1968 CATALOG OF
PRECISION QUARTZ CRYSTALS AND ELECTRONICS
FOR THE COMMUNICATIONS INDUSTRY



SENTRY MANUFACTURING COMPANY

1634 Linwood Boulevard - Oklahoma City, Oklahoma 73106

PHONE: 405-232-1431



VANGUARD
MODEL 501
Made In U.S.A.

\$279.95

SHIPPING COLLECT
COMPLETE WITH LENS

SUB-MINIATURE SOLID STATE

TV CAMERA

FOR CLOSED CIRCUIT OR AMATEUR TV

THE VANGUARD 501 is a completely automatic closed circuit television camera capable of transmitting sharp, clear, live pictures to one or more TV sets of your choice via a low-cost antenna cable (RG-59U) up to a distance of 1000 ft. without the need for accessories or modifications on the TV sets. The range can be extended indefinitely by using line amplifiers at repeated intervals or by using radio transmitters where regulations permit.

There are hundreds of practical uses in business, home, school, etc. for any purpose that requires you or anyone chosen to observe anything taking place anywhere the camera is placed. Designed for continuous unattended operation, the all-transistor circuitry of the 501 consumes only 7 watts of power.

For complete specifications
send for our illustrated catalog.

VANGUARD LABS

196-23 Jamaica Ave. Dept. H Hollis, N.Y. 11423

ever your reason, write it down. Tell the name of the article, the author, and give your reason for naming it the best technical article of the year.

Best Nontechnical Article of the Year.—73 often carries outstanding nontechnical articles of interest to radio amateurs. As you look through those back copies, select a particularly important nontechnical article that you believe warrants perpetuation in the annals of ham radio. This entry might be any article from the pages of 73 that you found particularly helpful for some reason. All you have to do is give the name of the article and the author, and cite the reason why you feel the article is outstanding.

Best Published Solid-State Design of the Year.—This should be no problem at all. 73's pages are rich with solid-state projects and articles from its knowledgeable readers. Which of these did you build? Maybe a published integrated-circuit article helped you in a miniaturization project. Or maybe there's a design you've been saving to try

later. List the design you think is best and give your own reasons. Remember, you are the one who determines where these coveted awards will go.

73 Public Service Award—Here's an area where back copies probably won't help. Do you know an amateur whom you feel has contributed something "extra" to his community on behalf of amateur radio. Maybe you know of someone who went out of his way to do a service for a fellow human, such as using his radio station to pass traffic in an emergency. Or perhaps you know of someone who has performed some service for the benefit of the public that is undramatic in nature but worthy of commendation. He'll never be commended unless the amateur radio world knows of his actions. Give his name, call, address, and state his praiseworthy act.


VHF Award.—What individual do you feel most deserves a citation of merit for performance in the field of VHF? A two-meter moon-bouncer? A six-meter DX'er? A 432 experimenter? It's up to you. Give his name and call, and state why you feel he is particularly worthy of being awarded the VHF Sarah.

DX.—What amateur radio operator do you feel has contributed most during the year to the field of amateur DXing? There are quite a few to choose from. Who went out of his way to give fellow amateurs a chance to work rare countries? How about a DXer who stayed selflessly for hours at the mike so that more amateurs could add a particular country to their lists? What do you think? Some amateur will be awarded a Sarah for DX, and it's your job to determine that individual.

The most important thing to remember is to get your nominations in before October 10. As a matter of fact, why not do it now—before you forget? Use any kind of paper. Write it longhand or typewrite it—it makes no difference. All nominations are welcomed. At the top of your sheets, place your name, call, and address. Then list the categories, your nominations, and your reasons as indicated above. Then mail your entry to:

73—Sarah Nominations
One Radio Ranch
San Dimas, California 91773

NEW | **Cubical Quads** by *Mosley*

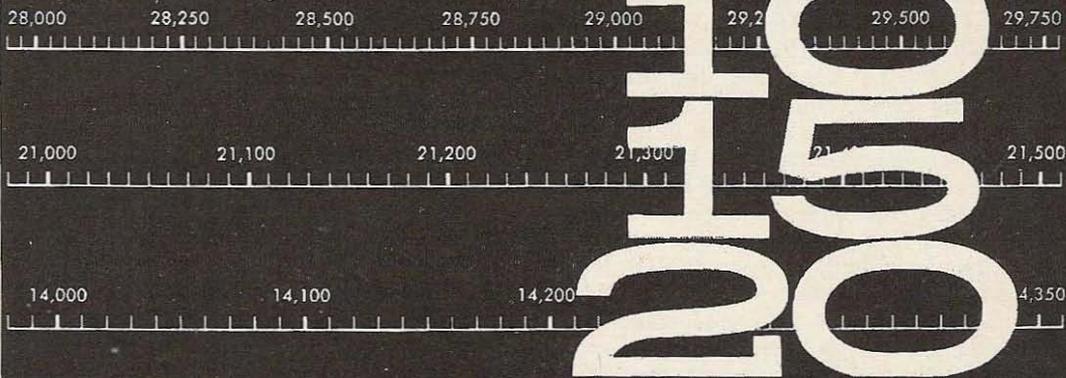

Four NEW Two-Element QUADS

SINGLE BAND QUADS


Model MCQ-10 for 10 meters

Model MCQ-15 for 15 meters

Model MCQ-20 for 20 meters

TRI-BAND QUAD

Model MCQ-3B for 10, 15 & 20 meters

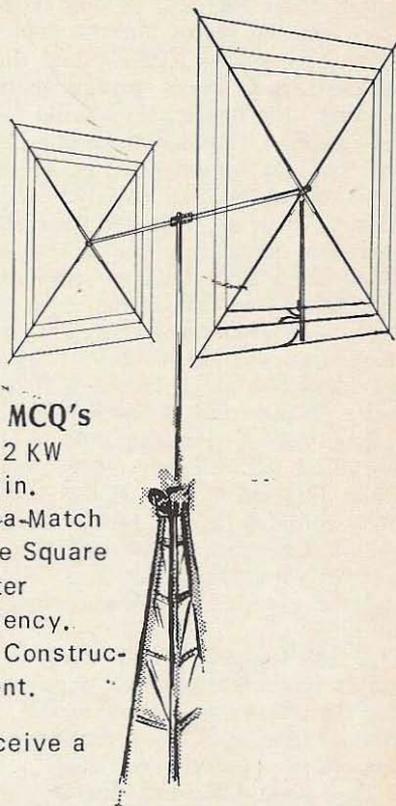

Designed and Engineered for Superior DX, the new **MCQ's** (Mosley Cubical Quads) are rated to 1 KW AM and 2 KW P.E.P. SSB. Maximum Front-to-Back and Forward Gain. A Single 52 ohm Line feeds the Quads via a Gamma-Match resulting in a low SWR over the full bandwidth. The Square Configuration of the **MCQ** Series guarantees better performance by providing optimum electrical efficiency. The Durable, Lightweight, Weatherproof Aluminum Construction yields a lifetime of maintenance-free enjoyment.

For detailed brochure, Write Dept. 169 . . . and receive a **FREE** 1968/69 Mosley Antenna Catalog.

1296 Megacycles-1968

Without doubt, this UHF band of Amateur frequencies has the most promise and with a few outstanding exceptions, provided the least results. Consider the tremendous efforts put forth by Sam Harris and his whole group at W1BU, Hans and the group at HB9RG, the Eimac club on the West Coast, and Tommy, KH6UK, in order to get the first Moon-bounce contacts on 1296. These must be considered as successful experiments that provided all of us with some valuable numbers but lead nowhere at that time, for these groups found it necessary to use equipment unobtainable to even the very serious UHF Amateur. Like mountain-climbing, after getting up there and back, you are not really sure it was worth the effort and certainly not worth repeating—what do you do for an encore! The other side of the coin is the poor soul who reads a glowing report in an old issue of one of the magazines, talks his buddy into this deal, scrounges up a couple of APX-6's, and they spend the next few weeks getting these bombs working, just to find they could have done better with a TWOER and a clip-lead antenna. This can be described as an old experiment, often repeated and not leading anywhere. All in all, a pretty poor piece of *rf* spectrum considering the problems of Antenna, impossible feedline losses, *rf* output and drive headaches, and a 15 db noise-figure with a handbook converter. How many times have you heard, "Boy, 1296 would be the band if you could work Moon-bounce, using 2C39s and a back-yard antenna." *Friend, that is precisely what G3LTF and WB6IOM used to get signals from California to England in June.* If this seems impossible considering the problems mentioned, you are forgetting the availability to all Amateurs of Varactors, Transistors, 3 db couplers, and the experience of those hardy pioneers on 1296.

"3 db Coupler—Whats that?" That is a simple flashing-copper box or piece of strip-line that allows you to use *one* 2C39 amplifier to drive *two* 2C39 amplifiers to drive *four* 2C39 amplifiers, etc. etc.

This same little box provides right-hand circular polarization transmitting and left-hand receiving without switching.

Bill Ashby K2TKN
Box 97, Sunet Lake
Pluchemin, New Jersey

As the memory expert once said "I don't have anything that every four-year old doesn't, but I have spent 30 years developing it" aptly describes the work of the two Peters, G3LTF and WB6IOM. Although each is an extremely competent, state-of-the-art electronics engineer, they have chosen to expend their energies in the direction that many of us more-or-less fortunate Amateurs understand and can participate in.

The best example possible to describe the type of development work Amateurs do best can be summed up in the unit amplifiers being used. Starting with the 2C39 triplers described years ago by W1WID, add the cavity development by WB6IMO (QST Jan 68), Vapor-phase cooling by W2CLL, and a year of hard work on final design of Cliff, W2CCY, and any Amateur anywhere in the world can build a 1296 transmitter of any reasonable power deemed necessary. Of course, the availability of Ceramic 2C39's and 3 db couplers helps, but would be useless with out the efforts of the above Amateurs.

Keep in mind that these signals on 1296 are the weakest signals ever used for communications of any kind, so nothing can be skimped in the receiver. Amateurs have been building par-amps successfully for ten years now and the ready availability of low-noise (5 db) transistor for second stages and mixers (QST Nov. 67) has eased the receiver problem. See info by Al K2UHY on *rf* amplifiers. Replace the collector circuit shown with a two-meter tuned circuit and link. Reduce the bias for 100 microamps of collector current, then inject enough 1152 MHz via a link near the base circuit to drive the collector current back up to one mA. and you have a low-noise 1296 mixer. We have finally seen the last of crystal sets, even on 1296!

Antennas, feed-line and tracking problems are still just as big a problem as ever, but Peter WB6IOM has shown us all that if you get the transmitter and receiver straightened out, a 10 ft dish on a simple back yard mount with a coffee can feed will cut the

buck—it doesn't make it easy, just possible. After finding his echoes with the par-amp, Peter can still hear them with the 5 db second stage, so he sure has the antenna situation well in hand.

During the past year, steady progress has been made here on the east coast by Cliff W2CCY who has managed to interest quite a group into getting on 1296 for nightly local contacts. He has shown that 18 db of antenna and 50 watts of clean signal will do a real job out to 70 or 80 miles without

openings of any kind. Transistor front ends have made a significant improvement in this type of work in the past year.

1296—1968 It should be recorded somewhere that this was the year that Dick W2IMU and the group at W2NFA not only generated a successful series of 1296 tests out of Crawford Hill that resulted in contacts with Europe and California, but of far more long term import, lead to the backyard to backyard signals of WB6IOM to G3LTF with much more to follow.

... K2TKN

VHF Awards

As many of the VHF hams are interested in getting some sort of wall paper to show off to their visitors, I will try to get a few listed just in case you might want to paper the wall and not pay a lot either. Many of the numerous certificates I have were absolutely free of any cost other than the stamp and the envelope. Of course, I think my proudest one is the DXDC #404 from 73 with the 6 meter endorsement. I have the letter from Wayne telling that it was the first for 6. I know many others are qualified but there again, some do not go in for even QSL's.

I have been quite active on the air with both this call and also my 2nd station K8BDT but never had so much fun till I went to SSB over a year ago. I helped form the Florida VHF Sidebanders, of which I am president. Any one working 10 full members of the gang; send the info to me and receive a very nice certificate free and post-paid.

The Golden Triangle Coffee Club has 2 nice ones; one for working the 5 charter members and the other for checking into their morning get together on 50.5 between 6 and 7 AM. Send 3-6 cent stamps to WA4VVW along with the info from log. You also must send QSL's to members worked.

The Floridora Y L's have a very nice one for working 10 of the gals, any mode or band, the info with 35¢ to K4RNS. Endorsements for each extra 10 gals are available from Marg.

The Florida Chapter of the National Awards Hunters Club has a real nice award (along with 4 gold seals) for working 150

of members of NAHC. Many of them count as 2 due to being charter members of their chapter, so get out the old shoe box and start looking for them. Then send list, and 3-6¢ stamps to Al Man-WB4CQU.

The Bayou City VHF club of Houston, Texas also has a real nice one for working 7 member stations and sending the log data to WA5DUJ. A few stamps would be appreciated.

The 6-meter club of Dallas (Texas) has a nice one on parchment for working member stations. Send to Louise-K5ZAM with SASE for correct number to qualify.

The Greater Pittsburgh VHF Society has a nice gold one for issue. Send SASE to W3BWU for more details, other than the fact it's for free.

WBCQU is also custodian for the Michigan Screwballs. Send a few stamps along with the "Screwballs" worked and even get a pin & your certificate.

The Wheat Straw Radio Club in Calumet, Oklahoma has a nice one for working 6 member stations and sending a stamp or so to K5GBN.

Another nice one and free to the XYL, can be had for sending a note to Mabel % W4IYT (editor of Fla. Skip) telling how much she does putting up with you as far as ham radio is concerned.

... K4LLF

CLUB SECRETARIES NOTE

Club members would do well to get their club secretaries to drop a line to 73 and ask for the special club subscription scheme that we have evolved. This plan not only saves each club member money, it also brings badly needed loot into the club treasury, if desired. Write: Club Finagle, 73 Magazine, Peter Boro Ugh, New Ham Shire 03458.

The VK3ATN Moonbounce Rhombic

Wayne Green W2NSD/1

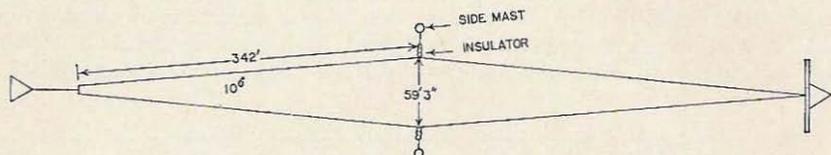


Fig. 1. The Moonbounce Rhombic doesn't require very high towers, the top of it being only 35' in the air. The ends of the antenna are tied to the two end towers and the slack in the wires is taken up by counter weights on pulleys on the side masts. A track on the tower in the forward direction permits the whole rhombic to be swung a few degrees one side or the other to permit aiming it at the moon and thus giving you four or five days a month for bouncing instead of the one or two you would get if it were fixed. The side pulleys permit easy moving of the positions of the side wires to keep the antenna in shape. Ray tried apex angles between 8° and 12° and found that 10° seemed to be optimum.

In January 1966, after being convinced by W1FZJ/KP4 that a long, long rhombic would have the gain necessary for moonbounce on two meters, even with the 150 watt power limit of Australia, Ray Naughton, VK3ATN started researching the published data on these antennas. It was sparse indeed. He wrote to some "authorities" to find out what he might be able to expect from, say, a 50 wavelength long rhombic.

It soon became apparent that he would have to just go ahead and build one and find

out for himself what actual in-practice gain he would get, what lobes would develop, and even more important, what the actual direction of radiation would be. This was, understandably, critical since he intended to point the gigantic antenna at a spot in the sky where the moon would pass on about two days a month. Even a few degrees error and no moon.

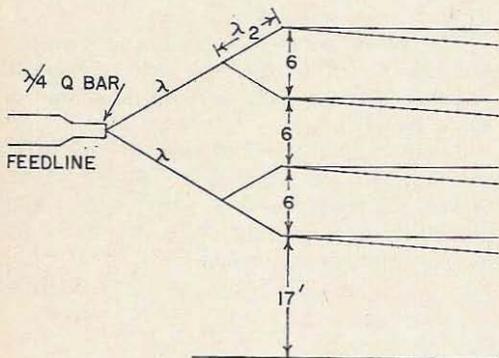


Fig. 2. The bottom rhombic is 17' off the ground. The other three are one wavelength each above that, 6'. They are fed by half wave sections which are in turn connected by two full sections of feedline. The match is made with a quarter wave Q-bar. The half wave, full wave and feedlines are all made with #12 AWG hard drawn copper wire spaced 1/2".

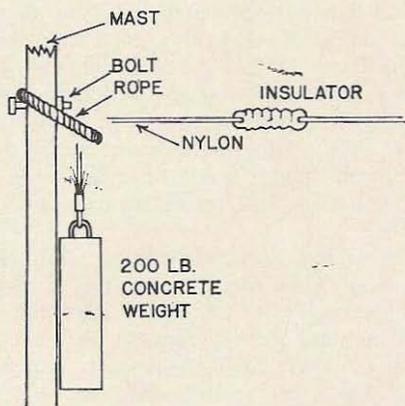


Fig. 3. The 200# concrete weights hold the wires of the rhombics so that there is only about 2' sag in the 342' stretches of wire. You'll need four of the weights for each side, one for each rhombic. Arrange to have them hang down close enough to the ground so you can reach them without a ladder as you have to adjust them now and then, particularly when you want to swing the antenna a few degrees one way or the other.

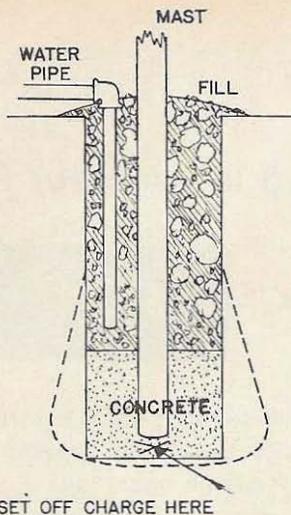


Fig. 4. Ray has towers and masts all over the place and has some good words for planting these things. If you want to plant a tower or mast so it will stay planted through anything dig your hole down as diagrammed. Put a couple of pieces on the bottom of the tower to keep it from pulling up vertically. Put a small dynamite charge in the bottom of the hole. Fill up the hole a little less than half way with concrete. Then put a water pipe down into the hole, almost down to the concrete layer. The end of the pipe should be perforated. Fill the hole with dirt and stones to a mound above the top. Set off the charge. This will expand the bottom of the hole and fill it with the wet concrete. Then run water into the pipe until it runs out the top. Pull out the pipe and when it all dries out you will have a tower or mast that will confound your great-great grandchildren.

Rhombic theory was fairly well established, but Ray wanted to stack them and little had been done on this. Collins had used stacked rhombics during some of their tests during the 50's on 49 MHz, but their published data was of little help.

During February 1966 Ray erected a 50 wavelengths long two-stacked rhombic. He missed the February moon pass, but was all set for the March pass and, sure enough, back came his echoes. They were weak so he got to work and added two more rhombics to the stack. The result was definitely readable and at times strong. By June he was getting good readable signals through from K6MYC on scheds, but Mike was having troubles in receiving and not yet able to hear his own echoes, much less Ray's.

The first two way for Ray turned out to

be with K2MWA. The boys in New Jersey got a chance to use the big dish there during the December 1966 moon pass and K6MYC, who had just installed a receiving filter and was finally set to work Ray, had to sit there, biting his fingernails, hearing both K2MWA and VK3ATN, but missing out on the first U.S./Australia two meter moonbounce contact. This was in November 1966. In December it was Mike's turn and he made it through to Ray.

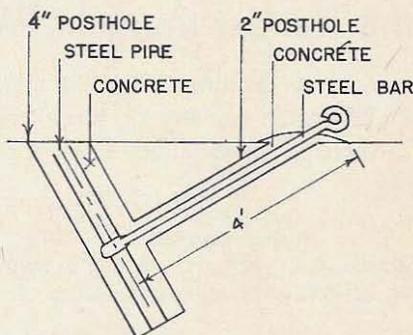



Fig. 5. Most of us just screw our guywire dead-ends into the ground and let it go at that. Not Ray. He makes a permanent job of it per the diagram. Use a 4" posthole digger and cut into the earth at about a 45° angle away from the guy wire direction. This hole should be about 6' deep. Then with a 2" posthole digger run a hole in from 45° in the other direction so it comes out in the 4" hole. Put your 4' long guy shackles into the 2" hole. The ring on one end should just stick above the ground and be verticle with the ground. The other end of the shackle has a ring at 90° from the top one and a steel pipe should be passed through this ring and driven into the ground until it is below the ground level on top. Do not use galvanized pipe as this will rust. Fill in both holes with concrete. Let the concrete come up around the loop on the end of the shackle to half cover it for maximum strength. This is a little more work, but it is not likely to come up in a wind. . .

The bounce club had regular get togethers on 15 meters to coordinate their work and schedules. They decided on a code for bounce contacts to save time. "1" meant they were hearing occasional signals, but that they were not identifiable. "2" indicated identifiable letters. "3" meant complete call sign and report received during two minute call period. "4" indicated almost 100% copy. "5" 100%. After using this system for a while they found that the dots of the numbers tended to get lost in the fading. Next they



ROMEY says FM is the hottest thing in Amateur Radio and

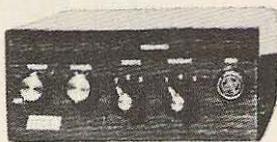
the NEW ICE 2 meter transceiver is the hottest thing in FM



An exciting all solid state transceiver featuring crystal controlled operation on any of three channels. Includes a built in speaker and internal power supplies for 12 volt dc or 117 volt ac operation.

write today to
DEPARTMENT M

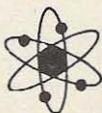10 GRAHAM ROAD WEST · ITHACA, N. Y. 14850
TELEPHONE AREA CODE 607 273-9333



stellar industries
DIV. OF STELLAR I, Inc.
SALES AND SERVICE

Your central New York headquarters for not only the ICE 2 meter FM transceiver, but also for all new and used ham gear — sales and service. Mail orders welcomed.

**Hours: 9:00 A.M. to 5:30 P.M. Monday through Friday 9:00 A.M. to 5:00 P.M. Saturday
July and August Only 9:00 A.M. to 1:00 P.M. Saturday**

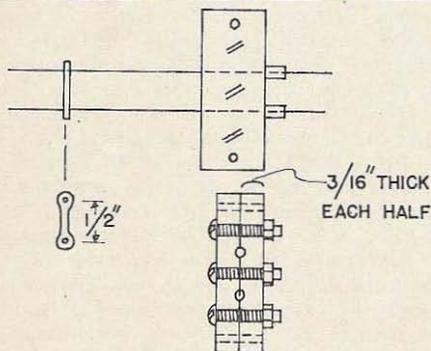


Fig. 6. Ray uses these little half inch spacers for his feedline. They are spaced out every 8' along the line to keep any discontinuity to a minimum. On curves he puts them above every 6". He keeps about 200 pounds tension on his feedlines to keep them in shape, taking up the strain with blocks per the diagram. These polystyrene blocks are used to hold the half and full wave sections, the Q-bar and the feedline taut. The loss of the system is kept very low this way. The half inch spacers are a commercially made item, the blocks are home made.


tried sending "T"s for 1, "A"s for 2, "E"s for 3, "I"s for 4, etc. Still not so good . . . los-

ing those dots. The present system is to use a series of "T"s for 1, "M"s for 2, "O"s for 3, "MT"s for 4, and plain SSB for 5.

The frequency used is around 144.09 MHz. The stability must be good, staying within a few cycles. You have enough problems on moonbounce without having to tune around the band chasing signals.

Ray experimented with various aperture angles for the ends of the rhombic. He tried from 8° to 12° and settled on 10° as being the optimum. It is rough making empirical tests like this for those two days a month go by rapidly and take a long time to come again. On April 24th he got back about 8 minutes of echoes. Nothing on the 25th, the 26th, 27th or 28th, then 12 minutes of echoes on the 29th! More changes and then in May nothing on the 20th, 21st, 22nd, 23rd, and 24th. At last, on the 25th some echoes! And nothing more for the month. It is slow frustrating work this way.

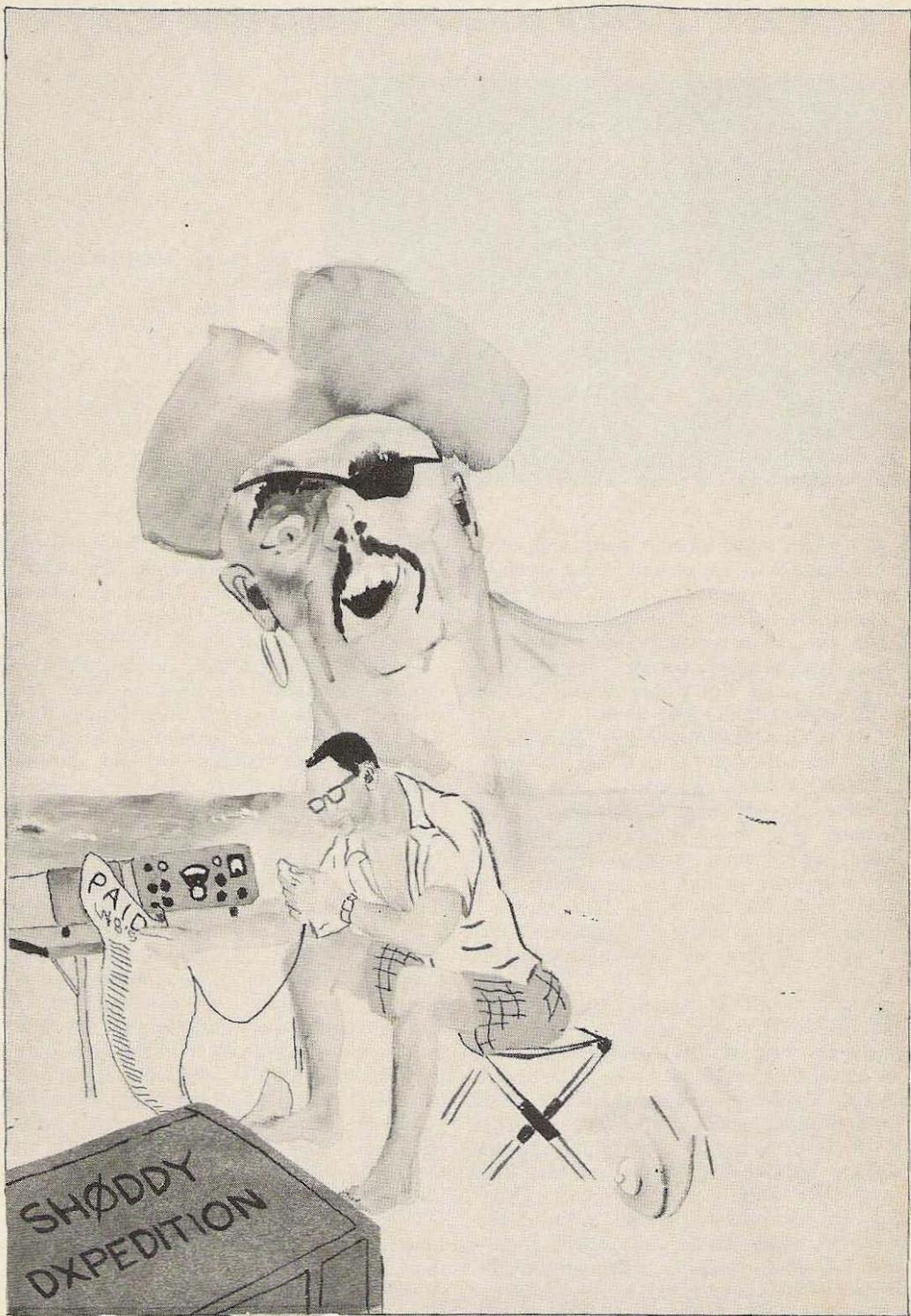Would tilting the rhombic elevate the lobe? No way to know until you try it and see what happens. The answer, to save you a few months of finding out for yourself, is no. . . . W2NSD/1



K2US: 1968 Ham Radio Expo



Mel Snyder WB2DLW/K3AFW
Box 15
River Edge, N.J.

In an era when citizens band and commercial gear have supposedly stolen much of amateur radio's glamor, 15 ham clubs from northern New Jersey believed that all the hobby needed to recapture the public awe was a little overdue exposure. They got their chance to prove this theory at the Garden State Amateur Radio Exposition.

Like most great ventures, this "Ham Radio Expo" started with a lucky break—Steve Flehinger, assistant advertising and public relations manager of the Garden State Plaza, Paramus, N.J., saw a story about Vietnam phone patches in a local newspaper. The story suggested to him the possibility of a major public display at the Plaza, world's biggest shopping center. He contacted first the FCC and then the Newington gang for advice.

Several months later, north Jersey's hard-working SCM Louis Amoroso, W2LQP, finally got wind of Steve's inquiry, and put out a call to area clubs for an organization meeting. Twelve clubs, associations and emergency groups, including such august names as the North Jersey DX Association, Quarter Century Wireless Association and the East Coast VHF Society, sent members. Other clubs present or soon to join included the Bergen Amateur Radio Association; Englewood Amateur Radio Association; Knight Raiders VHF Club; Land Rovers Amateur Radio Club; NASTAR; New England .FM


Repeater Association; North Jersey Radio Club; Stevens Institute of Technology Radio Club; Tri-County Radio Club; Watchung Hills H.S. Radio Club; Oakland 550 Club; Army, Navy and Air Force MARS.

Harry Dannals, ARRL Hudson Division director, attended the meeting and was stunned by the response; the League had withheld official endorsement of the Expo, fearing it might "conflict with the division convention in Tarrytown later in the year." Dannals noted that no division convention ever began so enthusiastically.

As committees formed and the work began, the club representatives made clear the reason for this enthusiasm—the Garden State Amateur Radio Expo was to be no ordinary hamfest, where hams merely talk to hams. "Expo" was to be a unique opportunity to open lines of communication to area non-ham publics, ranging from prospective amateurs to influential community leaders who often decide anti-tower ordinances and what to do about serious TVI cases. Given the chance to change some of the "bad ham" image, north Jersey amateurs attacked the opportunity like a smoking Field Day rig.

For Steve Flehinger and his supervisor, George Chirogene, the planning was awesome.

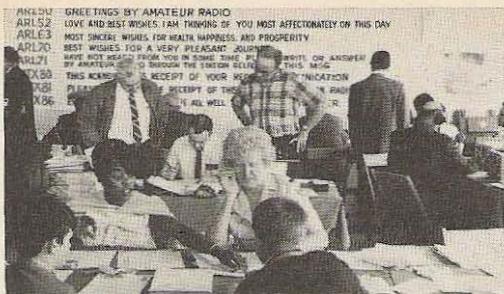"This hobby dissolved into a tangle of ominous words and phrases like "high volt-



Two Red Cross volunteers help young visitors fill out message forms at traffic setup at Expo.

age,” “250-foot coax feedlines” and “just how many amps is this place wired for?” Steve recalls.

“This place” was an empty store in the giant Plaza—7000 square feet of highly prized space, with big plate-glass windows on three sides. And the Expo dates couldn’t be more attractive—May 2 through May 4, anniversary sale days at the Plaza, when perhaps 75,000 of the area’s bargain-happy shoppers would flock to the center.

Despite possible incidence of Murphy’s Law, Expo rolled along from its January beginning. Qantas obligingly flew in Ray Naughton, VK3ATN, of “Moonbounce” fame. Ray captured the interest of hams attending the VHF Conference, which also starred Ralph Thomas, KH6UK; Hans Lauber, HB9RB, who contacted Raf’s friends at Crawford Hill Amateur Radio Club via 1296 mc moonbounce less than a month earlier; Ray Conkel, W6DNG, and many others. The public was charmed by Ray’s great Aussie accent and his fine color slides of “down under.”

With a few days to go, the FCC approved K2US for use at the Expo. And NASA sent



Three well-known DX’ers: Ed Hopper, W2GT; “Musty” Mustermann, W2TP; and Vic “the Digger” WA2DIG discuss the ragged shape this recent pack of DX QSLs arrived in (note: all were salvaged and forwarded!)

a “Surveyor” satellite display, and prepared for two theater shows on outer space for Saturday crowds.

Bergen Amateur Radio Association presented “Gateway to Amateur Radio,” an exhibit showing how to obtain an amateur license. The thousands of Expo visitors watched BARA member Paul Irvine, WA2ANI, and his dad, John, K2GXX, assemble a Heathkit receiver at the booth. Hundreds of youngsters received “Certificates of Communication” marking their first contact via amateur radio, over a 2-meter station in the display. Another section of the BARA



A moving moment at Expo: blind non-amateur at left is shown how to tune receiver by unidentified Mount Carmel Guild ham who is also blind.

display handled visitor questions about TVI, and how it can be cured. A key part of this section was an operating portable TV set with only a rabbit-ear antenna, operating only a few feet from the SR-2000 station loaned by Hallicrafters for K2US contacts—the screen never once betrayed a hint of interference. Hallicrafters donated 12 of its amateur license course kits for a drawing at the BARA display, and hundreds of youngsters flocked in hopes of winning the combos of code record, ARRL manuals and CPO.

East Coast VHF Society members demonstrated the latest in VHF gear and communications techniques. An amateur TV two-way station set up by Alan Katz, K2UYH, drew large crowds, as did a 16-foot-long OSCAR tracking station exhibit set up by NASTAR’s Nick Marshall, W6OLO/2. Nick, who was technical director of OSCARs I and II, used big display boards to show visitors the contents and functions of all OSCARs to date, and exhibited a model of OSCAR I in the booth. Nick also displayed plans for Project Moonray, and demonstrated a sub-laser communications system over which visitors could speak. The modulated laser beam was de-



CW aficionados Steve Petrucelli, WB2WPIX, and Al Bianci, WA2BCN, dazzle Expo visitors with dits and dahs at the outdoor information booth.

tected and used to modulate a 432 MHz transmitter, similar to the way Project Moonray may operate.

Land Rovers Amateur Radio Club showed the public the wide range of RTTY activities possible, from traffic handling to general QSO and "picture" transmission. Prepared tapes on Expo fed a network of teletype printers around the exhibit hall, telling visitors about Expo activities and amateur radio. The New England FM Repeater Association, organizers of an FM Conference held in conjunction with Expo, presented an impressive display on the equipment and communications networks possible with this mode.

Englewood Amateur Radio Association and Tri-County Radio Club combined to present "This is Field Day," an exhibition of a tent-based station and panels of photos and newspaper clippings of past FD activities. An exhibit showing the performance and preparedness of the Amateur Radio Emergency Corps was sponsored by the Knight Raiders VHF Club.



Contrary to his Aussie comrades' jest, VK3ATN is not the longeared type at center! He's at right, displaying the friendly little kangaroo the Garden State Plaza brought to welcome Ray to Expo. Dick Turrin, of the Crawford Hill (NJ) Radio Club group that first QSO'd Ray via 144 moon-bounce, joins in the fun.

Traffic-handling at Expo was directed by Doug Rue, WA2ASM, Tri-County Radio Club, and Knight Raiders president Jack Wilk, K2KDQ, net control of the Passaic Valley Traffic & Emergency Net. Their club members manned VHF and low-band rigs operating AM, SSB and RTTY in routing traffic to the National Traffic System and MARS on 75, 6 and 2 meters. Outside the Expo hall, in their mobile trailer crammed with gear that left public and hams a little awed, personnel from First Army MARS alternated between handling Vietnam traffic to Hawaii and showing visitors the equipment.

North Jersey DX Association was prominent with a display prepared by Herman ("Musty") Mustermann, W2TP. The display showed the wide range of awards and trophies for which amateurs compete using



In a typical moment at K2US, BARA vice president Marv Tischler, WB2TEA, takes a break from contacting to explain station to visitors.

QSL cards, as well as the methods the association uses to handle their QSL bureau responsibilities for the second call area—22,000 cards per month, on the average!

Proof of the hobby's unique rewards for the handicapped were displayed by Alex Alexi, WA2AJE, and other hams from the Mount Carmel Guild, Newark. In a display assembled by Stevens Institute Amateur Radio Club, Alex and others showed blind and sighted non-ham visitors how one tunes a rig when deprived of vision.

Ed Raser, W2ZI, proprietor of one of the nation's top antique radio museums, displayed and demonstrated amateur transmitting and receiving equipment from the early days of the hobby. Ed, who splits his time between SCM duties for southern New Jersey and representing the Delaware Valley Chapter of QCWA, highlighted the display with a crashing half-KW rotary spark trans-



K2US-TV, set up by Alan Katz, K2UYH, gives visitors a look at a homebrew ATV station.

mitter, and a commercial 10 KW hand key as big as a billy-club.

Watchung Hills High School Radio Club prepared a display on radio astronomy for the Expo. The Watchung Hills students showed equipment and antennas they have built for studying signals from deep space and solar and moon-reflected noise. Photo displays illustrated how amateur radio operators began this field in the mid-30's. The students also ran a rear-projection movie on the history of radio that drew 15-40 viewers at every continuous showing during the three-day exhibition.

The recently-formed Oakland 550 Club showed equipment built for hidden transmitter hunting—transceivers, portable loops, etc. An impressive scrapbook of photos and newspaper clippings confirmed the club's expertise with their gear.

Out on the mall area of the Plaza, WB2DLW and other BARA members manned a 40 CW station that attracted hundreds of shoppers to the Expo information booth, and then into the main exhibit hall. Posters explained the reasons for CW, code



First Army MARS operators show visitors inside of van packed with military equipment. MARS maintained link to Hawaii throughout Expo to handle Vietnam-bound traffic.

requirements for various license classes, and the QRP International Amateur Radio Club rules under which the station operated.

And there were many others— 73, *Ham Radio*, International Mission Radio Association, and even a small ARRL booth that contributed to the overall view of amateur radio seen by the crowds. Local newspapers carried Expo news on Monday, Tuesday, Wednesday and Friday of the action-packed week, helping to swell the crowds.

To those who called K2US and were not answered, we offer only the apology of heavy local QRN and our primary responsibility of



Jim Joyce, WB2MEE, holds ticket-stub box for IMRA's Brother Carman in drawing for Hallcrafters code sets at BARA booth.

telling the public about ham radio; to those who were answered, we ask that you QSL via the Bergen Amateur Radio Association, Box 15, River Edge, N.J.; BARA will route cards to those stations you QSO'd at Expo.

Now that the Expo has ended, planning for the next Expo seems imminent. The event did a great deal for the image of amateur radio in north Jersey, and should be a model for others elsewhere.

... WB2DLW/K3AFW

SUBSCRIBERS

We want to make absolutely sure that no one is using our 73 mailing list. We do not rent this list out as do other magazines. If your address label from 73 is distinctive and you find that you are getting any mail addressed in the same distinctive way please let us know immediately and send us the envelope or wrapper that you received so we can take appropriate action. Your help in this will be very much appreciated.

6 Meter Exciter

Kenneth W. Robbins W1KNI
Sperry Rand Research Center
Sudbury, Mass. 01776

During 1965 "73" magazine published a series of articles by Bill Hoisington K1CLL describing heterodyne transmitters for 6 meters.¹ They are fine rigs, the writer having verified performance by breadboard models. Cold start frequency drift averaged about 1 kHz and this only during a short warm-up period, thereafter holding steady within 100 Hz or so. During the summer of 1966 a modified version of his Slippery Six² was constructed using a 3A5-1R5-1L4 tube line-up with solid state regulated power supply. After a few minutes, frequency drift would level off to about 50 Hz per hour even with line voltage excursions of 20 volts. Spurious output signals were 36 db below a 75 mw carrier which drove a 5763/829B transmitter.

Like some vacuum tube receivers, oscillator power may be left on to eliminate warm-up drift. In early 1967 an "always-on" experimental VFO was built using two 2N706 bipolar transistors in an oscillator/buffer configuration on 14MHz. Ambient temperature variations were smoothed by a 3/4 inch soft pine enclosure lined with aluminum foil.

After stabilizing for 24 hours it was operated as a carrier-reinsertion signal on 20 meter SSB stations with receiver in its AM mode. No drift or instabilities were detected. Assuming the SSB station is drift-free, this test requires 50 Hz or less frequency change to keep a voice sounding natural. For home stations use, continuously powering frequency generating circuits is OK but is not too practical for portable or mobile use.

Experience with bipolar transistors has shown they are not easy to "tame" for VFO use³ but most certainly the new FET's are a natural. One of the first to appear was W2YM's unit with eye-bugging performance figures.⁴ Recently W1DITY described his version using JFET's.⁵ These new unipolar devices when used in a modified Solid State Slippery Six⁶ enable the construction of a hybrid 1 watt output 6 meter exciter having excellent frequency stability, small warm-up drift, low spurious output and 12 volt dc operation (dc/dc converter for tube b+). How this may be done and

resolving of various problems that arose is recounted in the following paragraphs.

Little difficulty with the VHF crystal oscillator was expected so its design came first. As is well known, power dissipation in these crystals *must* be kept small to minimize drift due to heating and accelerated aging. For CR23/U and similar units, maximum power specification is 2 mw. How to stay within this limit without some kind of automatic leveling feed-back? Since class C oscillators are amplitude-limiting why not reduce B+ to a low value and thus power in the entire circuit. Many transistor spec sheet curves show good gains with a volt or less and Ft extending into UHF frequencies. A silicon transistor made for TV luner local oscillator use is the GE 2N3662 having an Ft of 1.2 GHz and priced at 75 cents. It appeared to be a likely candidate so breadboarding commenced with B+ supplied by a single flashlight cell. Of various circuits tried, we liked K1CLL's the best since it does not require "tuning out" crystal capacity and impedance levels around the quartz loop are low and easily optimized. Overtone crystals between 45/46 MHz were tried and CB transmit crystals running on their fifth overtone worked just as well; this rig uses a channel 23-T unit marked. 27.255 whose 5th O.T. is about 45.425 MHz.

Low B+ seems to be one easily applied technique in getting crystal power down because warm-up time averaged 5 minutes with a drift of 15 Hz then holding steady within 10 Hz, when checked on a frequency counter. Temperature has a large effect on frequency, warming the metal can with finger heat will produce a few hundred Hz change. It was decided to power the VFO continuously during operation, switching the crystal oscillator off during receive.

Using a resistor as a coupling element, buffer base drive was adjusted for best mixer performance with minimum 45 MHz signal. Other things being equal, frequency insensitive resistance coupling reduces pulling as compared to reactive devices.

VFO circuitry evolved into a configuration using W2YM's oscillator with a source fol-

ing, without a zener, B+ was varied from 9 to 15 volts while the exciter supplied a carrier-reinsertion signal on a SSB station at 50.107, receiver mode being AM. There was no discernable change in voice pitch! A more critical test can be made by beating the fundamental VFO carrier around 5 MHz against a thoroughly stabilized 100 kHz marker in the receiver and adjusting for a low beat of about 1 Hz as indicated by the S meter. This resolution of a few parts in 10^7 shows up effects of B+, loading, temperature, etc. in a hurry.

Mixer performance was poor until collector tapping on its tank enabled a compromise between high Q, impedance matching and sufficient power gain. There was concern about VFO harmonics being amplified to a level where spurious emission would be unacceptable and in initial circuits tried this proved to be only too true. Also, a worse case condition occurs when a VFO harmonic coincides with a desired mixed frequency. A power ratio of only 13 db was obtained in one test; .5 watt carrier, 25 mw of 11th harmonic. Excessive mixer drive level was one reason but wave-form distortion in the VFO/buffer section was really at fault. Worse case spurious outputs in this finalized version are 50 db below a 1 watt carrier. This includes 45 MHz crystal feed-thru, the link trap having been set as described later on.

The straight-thru transistor buffer was impossible to stabilize by neutralization as first constructed and for some time a 330 ohm partial load on the sampler pick-up link was used to prevent self-oscillation. Shielding of low level stages to obtain final amplifier stability refocused attention on the "hot" buffer, where its instability might have been due to insufficient shielding also. Sure enough, bridge neutralization worked right off and energy lost in a swamping resistor now provides a well saturated grid drive.

Tubes tested for final amplifier use included 6EJ7, S686, 12BY7, 5763 and 6CL6 with the latter winning first place. Although its plate area is similar to a 5763, internal shielding is much better and gain at 50 MHz is good. Early tests indicated neutralization was in order because of persistent self-oscillation. However, after considerable electronic detective work, it was found that plate tank energy was radiating back into the sensitive low-level 45 MHz circuits, thus setting up a feedback loop required for os-

cillation. A simple metal shield completely enclosing these stages licked that problem for good and tuning thru plate tank resonance yields not the slightest trace of grid current variation. I suspect operation is in its self-neutralized frequency range which is a welcome bonus. No low frequency or VHF parasitics are in evidence either.

A Darlington transistor gate in series with the cathode performs like a screen grid clamper. 1 volt or more of dc applied to the 10 K resistor causes output transistor saturation and tube current is normal. When *rf* drive is zero (key up, mode switch on receive, spot, crystal out, etc.), sampler output is also zero and there is no forward bias. Transistor impedance becomes high causing tube current to fall, around 5 mils or less. This circuit also has an odd effect on tube current when mixer/driver tuning is varied. Plate mils start to climb with detuning until at 60 mils, sampler voltage is down to a volt and further detuning causes the current to drop rapidly towards zero. No *rf* drive and a dc cathode ground will cause tube dissipation to soar to 14 watts; 70 mils at 200 volts. Therefore this simple circuit should help to extend tube life under no-drive conditions. Perhaps it has possibilities as a cathode modulator if the exciter is run as a QRP rig.

For those who would like to duplicate this exciter, some construction hints are passed on. For L2, close wind 10 turns of insulated wire on a $\frac{5}{16}$ form, remove and secure the turns with Duco or Ambroid cement. When set, unwind the ragged end turns and adjust according to coil data. Add a little cement where it tends to peel off. To tap L1, bare $\frac{1}{2}$ inch of wire and bend it like a tiny inch worm. Sweat solder the loop closed then proceed like L2, winding in such a way that crystal socket connection and coil tap will be adjacent, with $2\frac{1}{4}$ turns between it and B+. For other coils, close wind tinned bus wire on a $\frac{1}{32}$ form, adding extra turns. Remove from the form, stretch, then fully compress. It will spring open naturally after which it is slipped onto a $\frac{3}{8}$ form by a slight unwinding process like a wrap-spring one way clutch. Self-tensioning will hold it in place while trimming to size and cementing. A few extra turns on the toroid will permit frequency adjustment later.

Locate the 2N3662 mixer buffer so that its collector lead can connect directly onto L4, insulated base lead projecting thru a

No, we're not lazy! It's just that "Popular Electronics" (Dec. 1967) tells the DX-150 story so well.

Reprinted Without Editing


"What may be the first really noteworthy advancement in communications receivers is wrapped up in the new Radio Shack imported DX-150. Featuring continuous coverage from the top of the AM broadcast band (535 kHz) to the bottom of the 10-meter band (30 MHz), the DX-150 is a single-conversion superhet with a tuned r.f. stage, two i.f. stages, full-wave product detector for SSB/CW reception — and it's 100% solid state. Selling at \$119.95, the DX-150 has the flexibility of a communications receiver that a ham or SWL is used to buying for \$175-plus. To rattle off a few more "features": there is a front panel antenna trimmer, fast or slow a.v.c. attack, a cleverly concealed built-in monitor speaker, plenty of calibrated bandspread, and noise limiting in both the i.f. and audio stages. Because of the solid state circuitry, the usual warm-up drift expected with a tube-type receiver is virtually absent here. And, although the DX-150 is primarily a base station receiver with a 117-volt a.c. power connection, it can be operated from an outboard d.c. power supply consisting of only 8 D-cells. Radio Shack claims that the receiver will operate for 100 hours — continuously — using only the d.c. supply. Ideal for Field Day and emergency work! The proof of the pudding so far as any communications receiver is concerned is how well it works "on the air".

At POPULAR ELECTRONICS, the DX-150 was hooked up to a 125-foot long-wire antenna and tuned across the AM broadcast band. Needless to say, the S-meter was pinned on just about every single channel, and the audio quality with Radio Shack's voice-selective speaker (extra, \$7.95) was crystal-clear. Tuning the band between 1.55 and 4.5 MHz, your reviewer got a chance to appreciate the comfortable handling on SSB reception. Going a little higher (4.5-13.0 MHz), the 25- and 31-meter bands were "alive" and signals appeared to leap out of the air — possibly due to the very quiet background of the DX-150. While quietness is usually regarded as a lack of sensitivity, that wasn't the case with the DX-150. On the top band (13-30 MHz), the sensitivity still seemed high; and on the CB frequencies, the DX-150 could hold its own against a dual-conversion receiver built just for CB work. **Summary:** Radio Shack has the Model DX-150 in most of its 160 retail outlets. Take a look at it, and get the "feel" of this unusual receiver."


CUSTOM ACCESSORIES



12 VDC Power Set

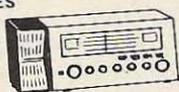

Matching Speaker

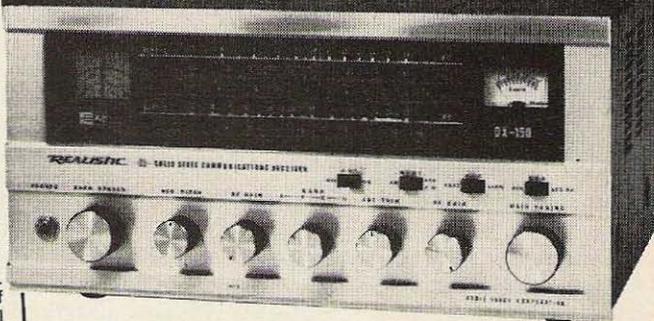

And only Radio Shack has this 119.95 receiver!

Thousands of hams and swl's have discovered that Radio Shack's Realistic DX-150 is truly the "break-through" full coverage receiver of 1968. It's the 100% solid state receiver that *banishes forever* tube failure, tube heat, tube drift, and — thanks to its built-in 117V/12V supply — your dependence upon AC current when power fails or on field day. The brilliant DX-150 is NOW IN STOCK in every one of Radio Shack's over 200 stores.

CAVEAT EMPTOR

Since DX-150 is certain to be the world's most imitated communications product, we advise our readers that "solid state" on a receiver is not necessarily indicative of selectivity, sensitivity and "feel." The DX-150 is built to \$200-\$300 performance specifications; its modest \$119.95 price tag simply designates the extent to which we have sacrificed traditional markup to establish REALISTIC as a quality line! P.S. — DX-150 is a hefty 14 lbs., with a 12 $\frac{1}{4}$ " dial, extruded 11-control front panel, and 14 $\frac{1}{4}$ x8 $\frac{1}{4}$ x6 $\frac{1}{2}$ " in size. It's just the picture that's little! Our no money down policy makes the pain little, too!

FILL IN AND MAIL ORDER TODAY!

RADIO SHACK { EAST: 730 Commonwealth Ave., Boston, Mass. 02215
WEST: 2615 West 7th St., Fort Worth, Texas 76107

Please rush me the item I've checked below. Dept. XO
I enclose \$ _____, plus 50¢ for postage and handling:

- FREE 1968 Catalog Matching Speaker, 20-1500, \$7.95
 Receiver, 20-150, 12 VDC Power Set, 20-1501, \$7.95
\$119.95

Name (print) _____

Street _____

City _____ State _____ Zip _____

small hole for wiring to L3 drive link and emitter lead trimmed to $\frac{1}{32}$ inch and grounded. Another small hole is required for the neutralization connection. Resistor leads running to +12 volts pass thru drilled holes whose ground foil side is chamfered back for insulating clearance. VFO and tube socket sub-assemblies are pre-wired before attachment to the main board.

Copper-clad printed circuit stock is just great for small rig construction; it provides wiring, insulated tie points, chassis, shielding and easy solder-ability all rolled into one! Finalized circuit board is number 4 of a series to be tried in the development of this exciter. Most leads are short and direct. Coil terminals are positioned for minimum lead length to concentrate inductance about the tuning slug. Double clad boards make it easy to apply B+ and ground for distribution of power about the "chassis." Insulated connections are made by cutting narrow channels thru the copper with a Moto-tool and small burr. Ceramic trimmer capacitors and crystal socket are epoxy-bonded in place.

One gallon anti-freeze or oil cans are a convenient source of metal for shielding. Paint remover such as TM-4 quickly removes labeling, leaving a bright tin-plated surface that solders readily. This was used for all metal work required in the exciter. A heat conducting tube shield is highly recommended. Tube socket chassis temperature is fairly high but it is just about ambient near the crystal and VFO area using either horizontal or vertical mounting (tube uppermost).

Initial tune-up and check out should adhere to the following schedule. Connect a jumper wire between pin 1 of the tube socket and ground. For ease of removal during test and trouble shooting, just tack solder the low level circuit shield to ground at each corner. Install a 6CL6 and its shield but do not energize. "Kill" the VFO by shorting its tuning capacitor plates with a bare wire and do not install a crystal. Connect a low current voltmeter such as a Simpson 260 to the drive sampler test point. Apply $+1\frac{2}{3}$ volts at about 40 mils to "Lo B+" and vary all tuning adjustments in a random manner in an attempt to start parasitic oscillations. Zero meter reading indicates all is well and this must prevail before proceeding. A change of neutralizing capacitor value might be required; its value is fairly non-critical however.

Install a crystal and tune the crystal oscillator, buffer, mixer and mixer buffer to its frequency around 45 MHz as indicated by a reading of 2 to 3 volts dc. Operate the mode switch and optimize oscillator tuning for positive starting with best output. Now, enable the VFO. Notice little or no change of meter reading. Mixer and mixer buffer slugs are then backed out a few turns, peaking up on a similar meter reading with output now at 50 MHz. VFO low limit and frequency range may now be set by appropriate adjustment of toroid inductance and the series padding capacitor. This particular rig tunes 50.15 to 51.4 MHz.

50 db of signal/spurious ratio demands nearly ideal mixer operation but it is easily checked. With tuning adjusted as described, zero VFO output should result in a reading of about .1 volt which is crystal feed-thru. With crystal out and VFO running, try peaking up on an in-band harmonic using the station receiver and its S meter. There will be some transistor "white" noise along with a small signal (about S7) but no dc volts on the meter. Variation of the FET buffer gate resistor gave results as shown.

R	DC Meter	S Meter
4.7k	70 mv	+40
6.8k	20 mv	+20
8.2k	trace	S9
10k	none	S7
VFO plus crystal		(crystal out)
8.2k	3.2v	S9
10k	2.8v	S7
18k	1.7v	S6
33k	1.0v	S3
open	.4v	S3

Just a few minutes is required to run a test like this and it enables a best choice of resistor R, in this case 10K. Only if transistors are changed need it be repeated, being a set-and-forget adjustment.

With the solid state circuits squared away, final amplifier tune-up is next. Connect a 50 ohm dummy load to the output BNC. Disable the VFO and retune all slugs to crystal frequency. Move meter, 10 volt scale, to the output sampler and energize the tube. Peak all tanks, about $\frac{1}{10}$ volts indicated then carefully resonate the trap for best null, around a volt or so. Do not alter its tuning unless a different crystal is used. It provides a 22 db reduction in spurious feed-

Now... Tune your Antenna for Optimum Performance

with this new antenna
noise bridge from
omega-t... only *\$24.95!



Test antenna system for both resonant frequency and operating impedance.
Replaces VSWR bridges or other antenna test equipment.
Tests beams — whips — dipoles — quads or complete antenna tuner systems.
For use over entire range — 1 to 100 MHz.

*Freight included in U.S.A.

Complete applications data and operating instructions included. If no distributor near you, order direct. Dealership inquiries invited. For descriptive literature, write:



omega-t systems incorporated

516 w belt line road • richardson, texas 75080 • (214) ad 5-5286

thru. Back out tuning slugs a few turns, enable the VFO and tune up on 50 MHz for a meter reading of about 10 volts (B+ at 160 volts.) Verify the signal as being in-band with a wavemeter, receiver, etc.

Leave all power on and stop the VFO. There should be zero volts at the final sampler, again .1 volt of drive sampler output. Crystal removal drops this to zero also. Check for parasitic oscillations by random tuning of all slugs; sampler outputs must remain at zero, tube current steady at 70 mls. With VFO running, once again try to peak up on an in-band harmonic. Results should be similar to the previous test, no sampler outputs, noise and signal somewhat higher due to tube amplification. Its a bit rough on the "bottle" but generates lots of confidence in exciter stability and insures a clean signal.

Finally, retune for proper operation on 6, remove the cathode ground wire and check out gate performance. For tripling to 2 meters, output at 48 MHz may be obtained by using a 43 MHz rock, remembering to retune the trap. Always keep in mind that *correct* tuning means: "No VFO output — no final output." Tube output will stay

high if the VFO is stopped and incorrect tune-up was made on crystal frequency. Pulling the crystal is *not* a valid test; output will be zero in either case.

The exciter with +160 volts on the plate will drive an 829B to 12 grid mls thru a 5.6K grid bias resistor. The previous battery tube version with its fancy regulated power supply for filaments and plates driving a 5763 buffer produced 8 mls. At maximum tube dissipation, +200 volts will yield a 1 watt output.


From a cold start, drift is about 300 Hz in 15 minutes settling down to something like 35 Hz per hour thereafter. This would seem to be acceptable performance for portable or mobile use. For home station use, warm-up drift may be eliminated entirely by continuously powering the transistor section; a novel power supply is suggested. It will maintain B+ within a .2 volt for line voltage excursions of 85 to 135 volts, is short-circuit proof and draws less power than an electric clock in the standby mode. The VFO may be enclosed in rigid foam plastic for ambient temperature smoothing as the coil and capacitor have non-zero temperature coefficients. Its output may then

35th ANNIVERSARY OPEN HOUSE

for
RADIO
AMATEURS . . .

- ★ Personalized Service
- ★ Trade-ins
- ★ Time Payments
- ★ Engineering Dept.
- ★ Top Brand Lines

REFRESHMENTS & PRIZES!

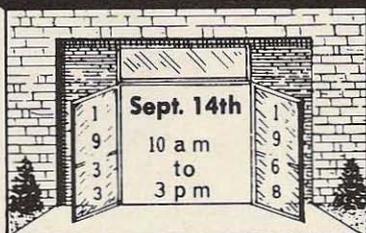

SERVING
as well . . .

- ★ Electrical Contractors
- ★ Industry & Gov't.
- ★ Dealers
- ★ Servicemen
- ★ Citizens Band
- ★ Business Radio
- ★ Audiophiles

EVANS RADIO, INC.
ELECTRICAL SUPPLY CO.

"Your Friendly Supplier"

ROUTES 3A, 89, & 93 • BOW JUNCTION • CONCORD NH 03301

COME PREPARED—MANY CASH SPECIALS

be applied to the mixer emitter thru a length of shielded wire.

It is hoped that this little heterodyne VFO rig will appeal to many of the 6 meter gang. Since its absolute stability is good, operation on hf bands via a power mixer could be used to heterodyne down. For 10 meters, 50.5 MHz beating with 21.5 MHz to get 29.0 MHz, as an example. Low budget hams can shop around for bargains from Meshna, Poly-Paks, etc. and build it for about 20 dollars. Surplus scroungers with fat junk boxes could cut that figure in half. Its quite possible other high frequency transistors would perform as well or better than 2N3662's. A couple of 2N918's tried worked fine. Rag chewers will appreciate its stable operation, running for hours on end without distress. Frequency hoppers can adjust the tuning for flat output over a few hundred kHz or full spread with slight touch-ups of slugs, mostly the sharply tuned mixer. In-veterate tinkerers will note a polarity reversal protection diode, current limiting resistors to prevent sudden death of a transistor should a test prod slip and an odd-ball regulated power supply which keeps its cool when shorted, trying only to improve

117 volt line power factor. And if you're "hooked" on frequency stability like me the exciter comes close to state of the art for LC oscillators!

The "do-it-yourself" adjustment and tune-up technique was cross checked on a spectrum analyzer in the lab. Using a 1 watt carrier for 0 db, crystal feed thru measured -51 db worse case VFO harmonic -53 db and circuit noise -60 db. A couple of CB crystals could be made to "twin", a double mode oscillation heard as an audio tone on the carrier; a slight retuning of the crystal tank stopped it.

In conclusion, a tipe of the ole fedora to K1CLL, W1DTY, W2YM and others whose previously published accounts got this project off to a flying start and to Mrs. Bob Trefry for yeoman effort with her typewriter.


... W1KNI

References:

- | | | |
|---|------------------------------------|---------------|
| 1 | 6 Meter Heterodyne VFO Transmitter | 73 April 1965 |
| 2 | Slippery Six | 73 Nov. 1965 |
| 3 | VFO Stability, Part II | 73 Jan. 1966 |
| 4 | The MOSFET as a Stable VFO Element | QST Jan. 1967 |
| 5 | AN FET VFO for 80 Meters | 73 May 1967 |
| 6 | The Solid State Slippery Six | 73 Dec. 1965 |

Appliance Operators— Please Turn Page

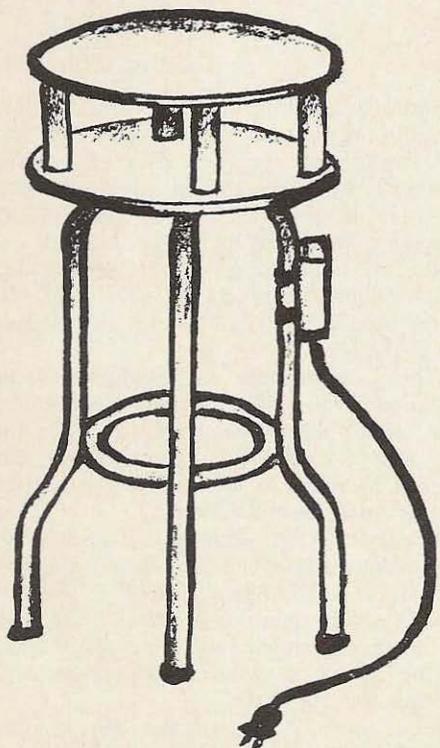Lee Lansing Jr. W4WAI
P.O. Box 236
Triangle, Va. 22172



How many times have you wanted to monitor for a band opening on VHF; waited your turn on the net or just wanted to rag-chew and at the same time be able to catch up on a favorite home brew project?

Normally the average shack does not have bench space at the operating location to permit such a situation.

This project provides for a simple, inexpensive bench, which is portable, and provides for rotation of the bench top to simplify turning of a chassis as well as providing for parts and tool space close at hand.

If you are an avid home-brew fan, read on.

Keep a weather-eye out for a bar or counter stool of the chrome tubing type with swivel top. These normally have a ball bearing base to the seat which is approximately

six to eight inches in diameter and permits 360° rotation of the seat. Remove the wood screws which secure the seat to the bearing plate and your project is well on the way to completion.

Cut two eighteen inch diameter pieces of one-half inch plywood (or other size as desired) and finish with paint, varnish or shellac. Cut four pieces of one-and-one-quarter inch closet pole (soft pine) or square stock, six to eight inches in length and finish in same manner as plywood. Secure the closet pole pieces to the plywood with wood screws about one-half inch from the outer edge at the quarter points in such a manner as to provide two round shelves spaced six or eight inches apart. Place the completed shelf assembly on the floor and invert the stool on the shelf assembly; locate on the center lines and secure the stool to the shelves with appropriate wood screws. The completed "bench" can be provided with an electric outlet, mounted on one leg, for soldering gun or iron, with "patch-cord" to the nearest convenient outlet. A small vise can be mounted on the lower shelf to assist in holding these small parts "too hot to handle" when soldering. The lower shelf affords storage for tools and parts while the top shelf becomes a rotatable bench for the chassis, rig or what have you. Procure a three quarter inch pad of foam rubber or plastic to use as protection when working on panels or components which may be scratched by a hard surface.

Note: This project is not compatible with a reclining type lounge chair.

Mexican Licenses

Mexico seems to have relaxed a bit on amateur radio licenses and you may be able to get one if you are planning a trip down that way. The open door border has been strained by an influx of hippies and weirdos from our country and now it is necessary to get a Tourist Card from a Mexican Consulate before crossing the border.

A Review of the Heathkit SB-110A



Matthew T. Lewis DS2
U.S.S. Biddle (DLG34)
FPO New York,
New York 09501

Want a really great transceiver for six meter SSB? Then this is the one! Assembly takes about thirty to thirty-five hours, and the most difficult step is stringing the dial cord for the final loading. This took me about fifteen minutes of trial and error, mostly error.

A look at the instruction manual will show that all printed circuit boards (six in all) are assembled first. All parts for these are packed in a separate box, so one box is all that should be opened at the start. Assembly of the PC boards, which appear to be of high quality, takes about five or six hours for all of them, including counting and sorting parts prior to starting.

All instructions are very specific, and easy to follow. The boards are also marked on the component side with parts values, so it is very difficult to make any errors, except by carelessness. When all boards are completed (one resistor is left off the receiver RF board for later installation) they are set aside for later use.


Next comes the installation of parts onto the chassis. For this, the chassis is divided into twelve sections, six on the top and six more on the bottom. After a good portion of the parts are installed, including the PC boards, the final stage wiring is begun. Next comes the wiring harness, which is made by Heath, thankfully. A few wires must be

trimmed to provide hook-up wire for later use, but all others are precut to the correct length and stripped. After the wiring harness is in, and partially wired, the coax harness is installed (also precut and stripped). Wires are soldered to the foil side of the PC boards, and the remaining parts are installed. All of this is very easy, due to the excellent drawings and detailed insets in the book.

When construction is complete, before alignment, you will have two resistors left over. *Don't worry about it.* The 47 ohm half watt is used for alignment only, and the 33k two watt is installed in the receiver *rf* stage, after neutralization.

Next comes the alignment. The only test equipment required is an eleven megohm VTVM (or solid state voltmeter, I used the IM-17), a fifty ohm dummy load (light bulbs are no good), and a receiver capable of receiving WWV or a broadcast station on a multiple of 100 kHz.

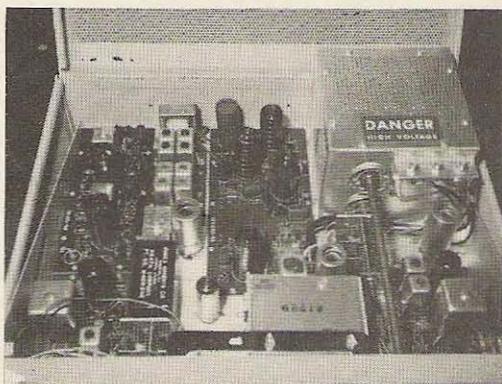Some nice features of the SB-110A are its ability to use crystal control for transmit or transceive, with front panel selection, the crystal socket is inside and it takes a crystal in the 4.975-5.525 MHz; the built in



A Peek Inside The SB-110A

100 kHz calibrator; two antenna connectors on the rear apron, one for the transmitter and one for the receiver, or use the internal relay; phone patch input; ALC input; a spare phono jack for whatever you want (if out for a monitor scope, etc.); and a spare hole which will take a phone jack, this is used for a brass bushing when used with the mobile mount. There is also a set of relay contacts which close on transmit, brought out to the power plug. A CW side-tone generator is included which provides about an 800 Hz. tone and has its own level control (internal). In the CW mode, the receiver is in the USB mode, and the transmitter uses an offset crystal for carrier generation, which bypasses the balanced modulator, so when you tune a CW signal for an 800 Hz. note, you will be close to zero beat with him. The SB-110A also has an excellent noise limiter which is turned on by pulling out the audio gain control. The AGC is normally fast, but pulling out the rf gain control adds .2 mfd, which slows it down considerably.

Unfortunately, Heath included no provision for AM operation. However, if AM is really desired, the carrier null adjust pot inside could be adjusted for about 50-75 watts carrier input, and the microphone level cut down to prevent "overmodulation". This will give you carrier and one sideband, but there is no way to turn off the receiver BFO.

The crystal control feature is quite nice, as it allows split frequency operation for DX chasing, or crystal controlled tranceive for net operation. There is an internal trimmer to "rubber" the crystal slightly and

get exactly on the desired frequency. It appears that minor rewiring is all that would be required to use the SB-640 external LMO which was designed for use with the SB-101, but Heath has no comment in their ads. However, page 99 of the instruction book shows an external VFO connected to the spare phono jack.

When the SB-110A is completed, all that is needed to get on the air is a power supply, a speaker or phones, an antenna, and a key or microphone (Amphenol 80MC2M connector furnished with kit). The recommended power supplies are the HP-13 for mobile (12 VDC) and the HP-23 (117 VAC) which fits quite nicely into the back of the matching SB-600 speaker.

As far as performance goes, the SB-110A far exceeds the Heath spec sheet. I measured 10 db S+N/N at .05 microvolts using an AN/URM-26G and a Simpson 260, and the CW output is slightly over 100 watts measured with a Bird thru-line wattmeter into a fifty ohm load.

In summing up, although I found the SB-110A easy to build, I don't recommend it for anyone who has never built a kit before. Start off with something a little easier, like a Twoer or the power supply you plan to use. Or try the IM-17 solid state multimeter if you don't have a VTVM; for twenty bucks, you can't go wrong. All in all an outstanding rig for the serious six meter SSB man, who wants an easy to operate, well performing rig with a very pleasing appearance, and a reasonable price tag. See you on six.

... WA2ZSA

PICKERING RADIO CO.
Post Office Box 29-A
Portsmouth R.I. 02871



YOUR TAPE RECORDER IS READY TO TEACH CODE!



That's right! Your tape recorder is ready to help your code study. The CODEMASTER tapes give you professional instruction via your own tape machine. Now generated by digital computer, the CODEMASTER tapes are unsurpassed for timing accuracy. Whether you're just starting, going for your Amateur Extra, or somewhere in between, the CODEMASTER tapes are your best code-learning buy! Find your CODEMASTER tape below!



CM-1: For the beginner. A complete course of instruction is on the tape. Practice material at 5, 7, 9 WPM. Prepares you for Novice exam. Includes code groups and punctuation.



CM-1½: An intermediate tape, especially for General Class exam study. No instruction; just practice. ½ hr at 11 WPM; 1 hr at 14 WPM; ½ hr at 17 WPM. Includes coded groups and straight text.



CM-2: For Extra-Class license study. Mostly straight text; some code groups. 1 hour at 20 WPM; ½ hour each at 25 and 30 WPM. For real QRQ, play this tape at twice speed!

CODEMASTER tapes are 2-track monaural; available in two sizes: 7-inch reel (3¾ IPS) and 3¼-inch reel (1½ IPS). Will play on any but full-track machine. SPECIFY both type and size of tape you want. Any tape, \$5.95 postpaid USA 4th class. Any two tapes, \$11.00; all three, \$15.00 PPD. Immediate delivery. CODEMASTER tapes are made only by Pickering Radio Company, P. O. Box 29A, Portsmouth, R. I. 02871. Satisfaction guaranteed. Dealers: inquire.

The power selection switch and socket for external power are mounted on the rear cover.

The antenna socket is mounted on the top right end of the front box. Two holes near the antenna socket allow access to the transmitter amplifier tuning and loading controls.

The only luxury in the transceiver is the meter that is used to measure either battery voltage or rf output depending on the setting of S2. Actually the meter is well worth the investment considering the speed it allows in determining battery condition and ease of transmitter adjustment with different antennas.

S1 switches the transceiver between transmit and receive mode. S1A switches the antenna and S1B switches the dc voltage. S5 turns on the transmitter oscillator for frequency spotting.

Chassis layouts are shown in Fig. 2 for the converter and transmitter exactly as I built them. They are the only units that may be critical in the transceiver and are therefore the only layouts shown. The arrangement of all units as to their position in the transceiver was not found to be critical so a detail layout of the entire transceiver was not prepared. The final locations will probably be determined by ease of operation and by best utilization of space. In any case the two Bud cabinets specified have plenty of room in them.

The receiver

The receiver is made up of two basic parts; a commercial transistor receiver (Japanese variety \$5 to \$8) and a one transistor, Q4, combination oscillator/mixer/converter. The converter operates on the autodyn principle, L6 setting the oscillator frequency at one half the operating frequency. In this case the oscillator tunes 24.195 MHz to 25.195 MHz to cover the receiver range of 50 to 52 MHz. The output of the converter is approximately 1610 kHz. The transistor receiver is used as the *if* amplifier, detector and audio output amplifier and is tuned to the converter output frequency of 1610 kHz. Coupling between the converter and receiver is accomplished by a six turn link wound over the center of the bc set ferrite loop antenna. This link is connected to the 3 turn link over the center of L5 by a 150 pF capacitor. The 150 pF capacitor prevents any chance of too tight a coupling and subse-








Six Meter Transceiver—Controls, bottom left to right; microphone, on/off volume, spot: center left to right; meter switch (DC-RF), receiver tuning, send/receive switch. Antenna shown is a collapsible "CB" replacement type and is mounted with a PL-259 to Phono adapter. Note crystal mounting thru lower right side. Speaker opening cut in top right rear compartment.

quent pulling of the bc set oscillator frequency. Do not use shielded wire for the connecting twisted pair.

L5 is constructed by winding one full length (about 45 turns) of #26 wire on the form, applying a layer of plastic electrical tape, then winding the second layer of 30 turns. L5 resonates to the converter output frequency of 1610 kHz.

Because the bc set is mounted in the rear compartment it is necessary to install an external volume control. The new volume control and switch is connected as follows:

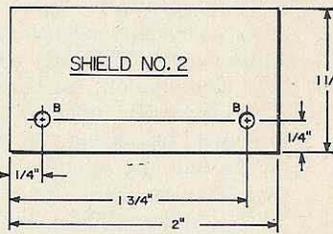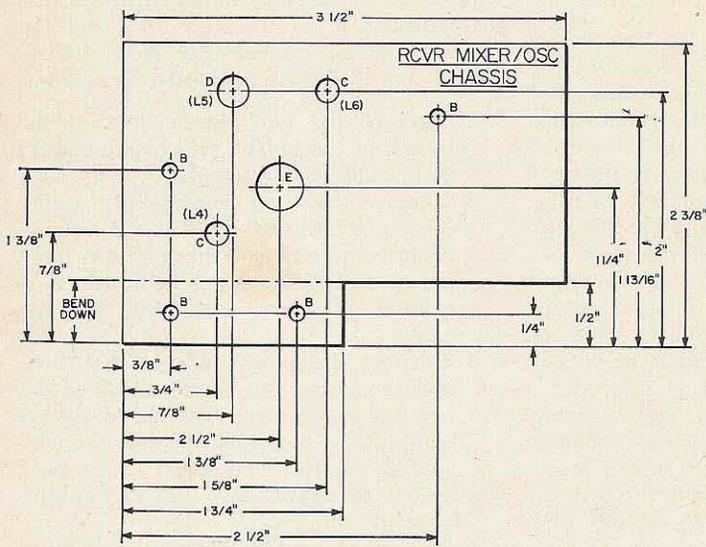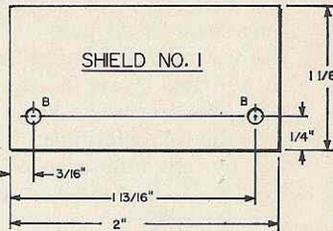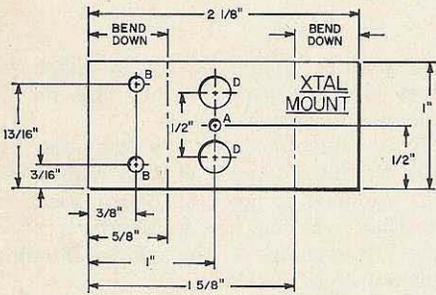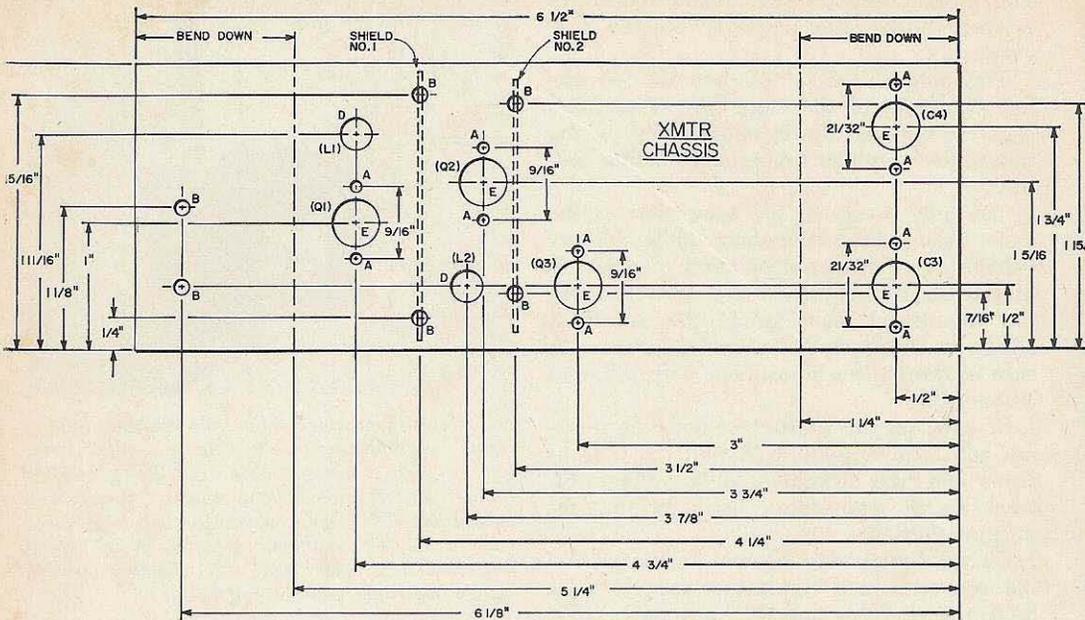1. Remove the two wires going to the switch of the old bc set volume control and solder them together.
2. Remove the three wires going to the resistance element of the old volume control and connect them to the three inner conductors of a length (about 8 inches) of three conductor shielded cable.
3. Connect the other ends of the three inner conductors to like terminals of the new volume control. The shield should be grounded to the chassis near the new volume control. The shield is not connected to anything at the end in the bc set.
4. The on/off switch on the new volume control should be wired as per Fig. 1.



HOLE	DIAMETER
A	3/32"
B	1/8"
C	3/16"
D	1/4"
E	3/8"

Fig. 2. Chassis Layout

Receiver adjustment

Use a grid dip meter to adjust L4 to 41 MHz, L6 to 25 MHz and L5 to 1.6 MHz for a starter. Tune the bc set to a dead spot between bc stations near 1.6 MHz. Because of the lack of shielding in this type of bc set harmonics of the bc set oscillator will be coupled into the 50 MHz converter thru the twisted pair connecting link. With a converter tuning range of 50 to 52 MHz you are bound to get one of those harmonics. By keeping the bc set tuned between 1.6 and 1.62 that harmonic should show up near the 52 MHz end and won't be a problem.


The next step is to couple a signal into L4 and adjust alternately L6 and C1 trimmer until the range of 50 to 52 MHz can be covered by tuning C2.

If you intend to use the entire range of 50 to 52 MHz set the signal source to 51 MHz and adjust L4 and L5 for maximum output from the bc set. If most of your operation will be in the first 1 MHz of the six meter band set the signal source to 50.5 MHz and tune L4 and L5 for maximum output.

The transmitter

The transmitter is constructed on a 4 x 2¼ inch piece of .04 inch thick aluminum with two 1¼ inch lips folded down a both ends. The shields are held in place with spade lugs and have a ⅜ inch hole drilled through them for signal feed through to the next stage.

The oscillator, Q1, uses overtone crystals, feeds Q2 which is a straight thru driver for the final, Q3. Either 2N706's or HEP-50's can be used for the oscillator and driver. The prices aren't bad, \$.99 for the 2N706 and \$.79 for the HEP-50. The final uses a 2N3553 which costs about \$4.75. The 2N3553 has a Collector to Emitter Voltage rating of 65 volts which is required for amplitude modulation of the final (with a 12 volt supply the collector voltage on modulation peaks can reach 48 volts). The 180 ohm resistor in the collector lead of the driver Q2 limits the peak voltage to that stage on modulation peaks. With the arrangement shown 80-90% modulation can be achieved. If 100% modulation is required the 180 ohm collector lead resistor to Q2 can be eliminated, however, Q2 will have to be replaced with a transistor that will handle the 48 volt modulation peaks. On

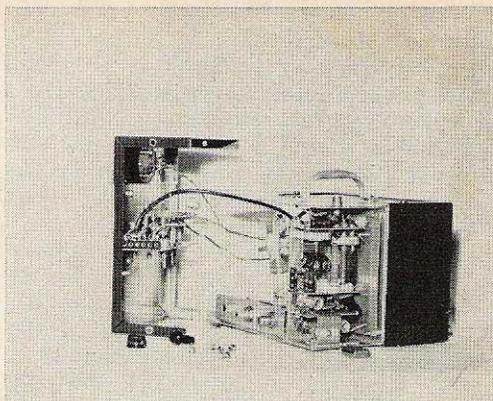

Front compartment with "U" cover removed showing; 1. In lower center the bracket used to mount the microphone jack, on/off volume control and spot switch, 2, on right the transmitter mounting and crystal mounting bracket. Note the modulator printed circuit board mounted on compartment back just behind the transmitter, 3. center left the converter sub chassis.

the air checks with other stations indicate that the modulation, as set up in Fig. 1, was adequate. Both Q2 and Q3 require heat sinks.

The transmitter was mounted in the front compartment with the bottom or wiring side facing to the right. This allows access to the circuitry for checking and possible trouble shooting after the chassis is mounted. The coil slugs are accessible thru the bottom of the forms. An insulated tool should be used for tuning. A bracket is formed for the crystal socket. This bracket mounts on the bottom of the transmitter chassis over the oscillator wiring and makes it possible to change crystals thru a hole cut in the right side of the cabinet.

L3 is a self-supporting coil made of #18 wire. The two turn link is made of #22 solid insulated wire. The link can be best made by taking two turns around the shank of a ⅜ inch drill then twisting the ends of the wire a couple of times next to the turns. The link is inserted between the 1st and 2nd turns of L3 from ground end and is held in place with a couple of drops of glue.

Transmitter Adjustment

L1, L2 and L3 should be grid dipped to 50 MHz. If you can't get a good dip on L2, temporarily remove Q3 from it's socket. If possible do the initial tune up with a 10


volt supply. There is less chance of damaging the transistors at that voltage. Apply power to the oscillator by depressing the spot switch S5 and check with a grid dip meter to make sure Q1 is oscillating. If Q1 does not oscillate adjust L1 until it does. At this point you should be able to tune in the oscillator signal with the converter whenever S5 is held depressed.

Connect a dummy load to the antenna jack. This can be a 51 or 75 ohm 2 watt resistor. Turn S1 to transmit and tune L2, C3 and C4 for maximum reading on the output meter M1. Then go back and adjust L1 for maximum output on M1. Turn S1 back and forth between transmit and receive several times to make sure L1 is adjusted properly for easy oscillation.

The modulator

The modulator is an Eicocraft EC-300 2 watt audio amplifier kit and sells for \$4.95. At that price it is hardly worthwhile to design and build your own. The input impedance is 2k ohms and is matched to a high impedance crystal mike by T1. T1 isolates the amplifier common, which is at a plus voltage, from the transceiver ground system. No form of gain control was needed as the amplifier output was just right with it running wide open. The microphone used with the transceiver is a lapel mike (Lafayette 99H4510) and does a pretty good job for \$1.95.

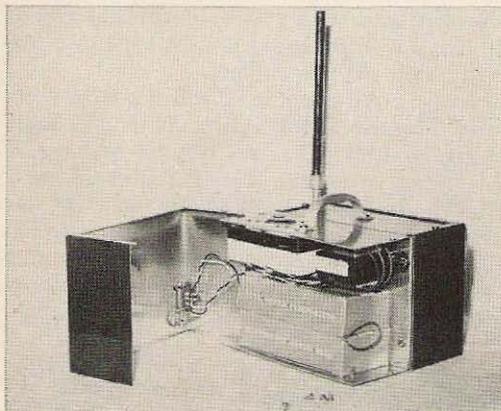The output of the amplifier is 8 ohms and is matched to the approximately 50 ohm input of the final by reverse connecting a



Rear compartment with "U" cover (holding power select switch and external power receptical) removed showing location of BC set, modulation transformer and battery pack.

Knight 54B4149. The common and 8 ohm tap connect to the amplifier output and one side of the secondary, and center tap are used to obtain 50 ohms for feeding the transmitter.

The Eicocraft comes with mounting screws and spacers. This hardware is used to mount the circuit board to the rear of the front compartment behind the transmitter chassis. The spacers provided are not very long so care should be used to make sure all leads on the bottom of the circuit board are trimmed closely.

Conclusion

The converter tuning capacitor is fitted with a Jackson Bros. #4511 vernier drive for smooth operation (available from Arrow Electronics Inc.). The dial plate is a piece of .04 inch thick aluminum 2 x 3 inches that was painted and numbered by using Datak instant lettering.

The transceiver has a built in power supply of 8 series wired Size "D" flashlight cells. A switch and socket is mounted on the rear cover so that an external power supply can be used. This could either be a car battery (plug in cigarette lighter) or a 115Vac supply. If continued portable use is anticipated it would be worthwhile to invest in Nickel Cadmium batteries and build a charger.

Power consumption under three different voltage inputs are:

Voltage	Total input	Final input
10	.35 amp	.18 amp
11	.40 amp	.22 amp
12	.45 amp	.24 amp

In receive mode the transceiver draws between .04 and .05 amp.

The transmitter output circuit is designed for 52 to 72 ohms and can be operated with either a whip for portable use or a beam. A whip should only be used when necessary because of the limited coverage. If a portable beam is not available when operating portable, say from a mountain top, a long wire with a simple tuner will work out much better than a whip.

So there you are—if you want to get your "feet wet" on transistors and also get together with the gang on the local six meter net go to it. I'm sure you will get as much fun and accomplishment out of it as I did.

. . . W2AJW



NEW FROM



HEAVY DUTY SSB POWER TRIODE TYPE 572B/T160L

- Ideally suited for grounded grid linear amplifier service.
- Rugged graphite anode. • Compact Envelope.
- Durable bonded thoriated tungsten filament.
- Relatively low operating voltage minimizes power supply cost.
- Zero bias—no bulky auxiliary power supplies.
- May be used in instant-on, no warmup amplifiers, for home brew linears. In most instances the 572B/T160L directly replaces the 811A providing greater peak power capability and longer life.

MAXIMUM ICAS RATINGS PER TUBE

DC plate voltage	2750 volts
DC plate current	275 Ma.
Plate dissipation	160 watts
Filament power	6.3V @ 4.0 Amps

AMECO DIVISION OF AEROTRON, INC.

U. S. HIGHWAY 1, NORTH • P.O. BOX 6527 • RALEIGH, N. C. 27608

Rejuvenating Old RTTY Ribbons

Is your typewriter or teleprinter ribbon getting old and run down? Does it print dimly and sometimes not at all? Here is a simple remedy.

The first step is to wind all of the ribbon onto one of the spools in the machine. Then remove the ribbon and both spools from the machine and rewind it by hand, feeding it a few drops of oil (ordinary machine oil or SAE-10 motor oil). Put a good sized drop or several drops about every inch or half inch of ribbon as you rewind. The amount of oil needed will depend upon how dried-out the ribbon is to start with.

After oiling, rewind onto the first spool without adding any more oil. Keep the ribbon fairly tight on the spool as you wind. This tends to force the oil into all parts of the ribbon and distributes it evenly.

Now replace the ribbon in the machine and test it by typing with it. If you have too much oil on the ribbon it will type rather messily, but if not enough oil it will print dimly.

Another tip: ribbons which are used in adding machines, posting machines and other

office machines other than typewriters seem to be of better quality and last longer than regular typewriter ribbons. Most users of these machines will give you their discarded ribbons. Since adding machines and such use only one half of the ribbon anyway, a discarded ribbon still has half of its useful life ahead of it. When purchasing a new ribbon it would be good economy to buy one designed for adding or posting machine service.

Joe Wright W5AQN

VACUUM VARIABLE CAPACITOR —JENNINGS type UCS-500. 25-500 pf @ 10KV. Includes panel mounting bracket. BRAND NEW. Factory boxed. (5 lbs.)	\$56.00
AIR VARIABLE CAPACITOR —HAMMARLUND type TCD-240-J. Dual section air variable transmitting type. 31-250 pf per section. (10 lbs)	\$9.95
POWER SUPPLY CHOKE —STANCOR type C-100L. 10.5 Henries @110 ma. BRAND NEW. Factory boxed. (3 lbs)	\$1.00
POWER TRANSISTOR HEAT SINK —MOTOROLA type MS-15. Holes drilled for TO-36 transistor. (1 lb)	\$.125
TUBES —5Y2/GAL5W (GE & RCA)		\$.95
0A4G (RCA)		1.15
5844 (GE)		1.00
5R4WGY .. (GE)		\$1.15
TRANSISTORS —2N44A		.60
2N301		.60
2N314		.60
DIODES —1N540 (GE)		\$.35
1N1202 (BENDIX)		1.20

All items are **BRAND NEW**. Quantities limited. Include sufficient for postage and insurance—any excess will be refunded with your order.

KAPTAINS COMPONENTS

2225 Albion Street • Denver, Colorado 80207
(303) 355-3680




TEN-IN-ONE MINI-LAB

Here is a complete test laboratory all in one package! A modern miracle of electronics. This one unit contains an AC-DC Voltmeter: 50, 150, 500 volts; 0-500 mA; 10K, 100K, 1M ohms; resistance and capacitance substitution; 9 vdc battery supply; RF Signal generator 455 kHz (and up to 700 kHz); plus an audio generator at 400 Hz. You can service just about anything with this lab. You can signal trace and align receivers and trace audio systems, speech equipment, hi-fi and tape recorders. This is probably the single most useful piece of test equipment ever to come along.

SPECIAL \$24.95 pp


**20,000
OHMS
per
VOLT
V-O-M**

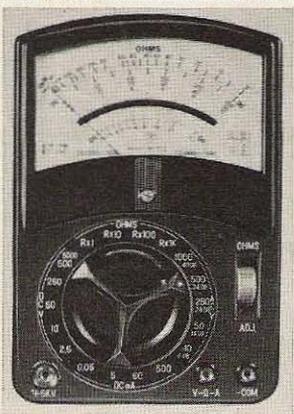

DC Volts:
2.5, 50, 250,
500, 5000.
AC Volts:
10, 50, 250,
500, 1000.
OHMS: 1K,
10K, 100K, 1M.

DC mA: .05, 50, 500. Decibels -20 to +62 db. Few small VOM's read up to 5000 volts, yet this is just what you need for testing your rig. 3" meter with mirror for high accuracy of readings. This meter has both the low scales and sensitivity for checking transistor circuits as well as the high ranges for transmitters. Buy one for the shack and one for the car. Light and rugged for traveling.

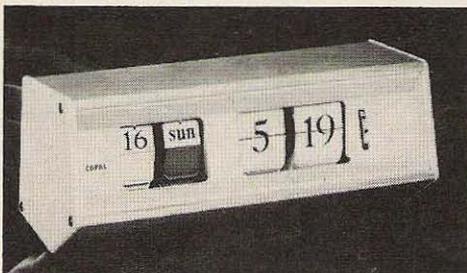**SPECIAL \$9.95
plus 75¢ postage & handling**



24 HOUR CALENDAR CLOCK



DESK NAME PLATE

Your name and call on a beautiful desk plate might normally cost you around \$10. These plates are walnut grained and are available with up to 20 letters and spaces. You can have your full name or your first name and call. Immediate delivery on all orders. 10" long by about 1" high. Identify your station with one of these plates. Sorry, no zero available!

SPECIAL \$2 pp

TRANSISTOR DC SUPPLY

This power supply will operate transistor radios and other devices under repair or where batteries are a drag to replace. Voltage range: 0-20 vdc continuously variable. Meter ranges: 0-20 vdc, 0-20 mA, 0-200 mA. Maximum current capacity: 150 mA/20 v or 200 mA/10 v. Pilot lamp. AC ripple: less than .25 mv rms. Fused. Has built in power transformer and 30 watt power transistor. Built for continuous duty.



ONLY \$14.50 pp

SIGNAL TRACER

Here is an exceptional value. This solid state signal tracer will make servicing of your receiver, AM/FM and TV very easy. Comes complete with shielded prod and clip cord. Self-powered. Six transistors, four diodes and one thermistor. Built in speaker and 200 uA meter. Attenuator 20-40-60 dB. Gain over 70 dB. Outputs for 8 and 600 ohms. You can track down the trouble in a receiver in minutes with this little unit.



ONLY \$17.95 pp

This clock reads out the day, date and time in large, easy to read numbers. None of that little tiny number business for your shack. Set this up on GMT and never make a mistake again on logging time and date. 8"x3 1/2"x3 1/2", brushed aluminum case. Synchronous self-starting movement, 110 v 60 cycles. Make your operating desk look outstanding with this new type of clock.

SPECIAL \$49.50 pp

REDLINE SPECIALS



AM-FM DIGITAL CLOCK RADIO

Here is something entirely new in clock radios - a digital clock plus a very sensitive AM-FM with AFC radio. This is the first digital clock radio ever imported into the U.S. The radio is all solid state, of course. This makes a wonderful radio for the bedroom. Price clock AM-FM radios, even in the bargain fliers, and notice the amazing low price for this one.

SPECIAL ONLY \$49.50 pp



TRAVEL-CLOCK RADIO

Eight transistor clock radio, complete with clock, radio alarm, and slumber setting! Weighs less than 1 1/2 pounds. Great gift for a traveling friend or relative. Or yourself. Ear-phone for private listening, if you like. Batteries included.

SPECIAL ONLY \$17.95 pp



CASSETT TAPE RECORDER

After testing a dozen different makes of cassette tape recorders we found that the Valiant was by far the easiest to use. The fidelity is good and the push button system outstanding. Has battery level meter, recording level meter, jack for feeding hi-fi or tv, operates from switch on mike. Great for recording DX contacts, friends, at the movies, parties, unusual accents and things like that. Once you try it you will be using it like a camera. Check this price anywhere, it is a lulu!

SPECIAL, ONLY \$44.50 ppd

Order today from

REDLINE COMPANY, JAFFREY, N.H. 03452

No COD's—USA and APO only—no taxes—postpaid unless otherwise specified.

Name _____ Call _____


Address _____

City _____ State _____ Zip _____

Amount enclosed \$ _____


tor with more than 5 watts dc input to the preceding stage. And, probably a higher-valued zener, such as the HEP-103 will be necessary. Here we use an International Rectifier 1 watt 3.9 volt job. Incidentally, the correct class A bias for the 6C9 is about minus one volt, so for DSB driving the tube with rf at an average value of -4 volts is quite acceptable. Peak-to-peak swing is about 9 volts, with no more than a small fraction of a peak in the positive grid region. Power in excess of 3 watts will be dissipated chiefly by the control grid (when driven positive), so watch it when using anything larger than a Two'er for drive.

An interesting point is that there is negative current feedback, or degeneration, through the zener for negative audio peaks and this tends to improve the audio fidelity; rf having been safely bypassed to ground through junction capacity. On AM mode screen modulation, using a Cesco Reflectometer in the output line as a tuning/SWR device; we see upward modulation when flat-topping the audio in class AB₂. Simply reduce the audio gain to a point where only when shouting into the mike at 2 inches will produce this symptom (use a dummy load): then relax and talk normally, and no one will know that it is zener offset positive peaked AM!! Of course a scope will come in handy here for setting it properly!

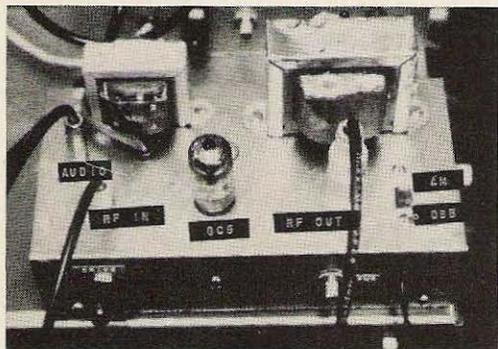

Construction

The first photo shows parts placement on the bright nickel plated steel chassis, with the screen voltage or drive control on the left. Just behind this pot on top of the chassis is an rf coax termination, using approximately 1 yard of RG-58/U coax cable attached to the phono connector output of the Two'er. The Two'er was previously wired for driver plate current to flow through the 350 ohm dc coil desistance of the Dow-Key

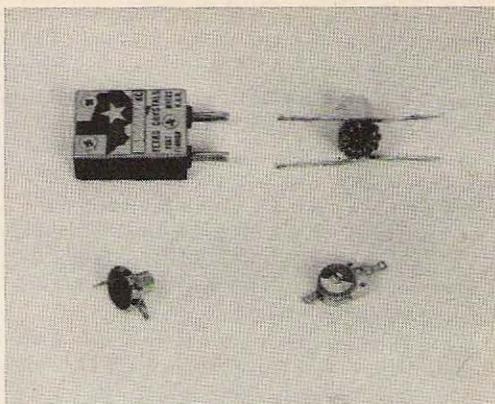

DK-60 send/receive relay, with the 1000 ohm internal dropping resistor removed. This way, the switch on Two'er panel serves as *the* control for all circuits and external contacts on the DK-60 relay open the speaker return on transmit: of the *if* strip used.

Getting back to the modulator. Just behind the termination is an audio input connector patching the KT-92 amp into the VC to 10K CT 5 watt Stancor A-3831 audio transformer. With the tap on the transformer set to a nominal 8 ohms will give good quality audio (almost broadcast quality) if you don't overdrive it! Also, for improved fidelity it is desirable to feed 4 ohm output (or 3.2) from the amp into 8 ohms, but not vice versa, with a power loss. Please note also that if you're using a KT-92: this is an ac-dc type amp with floating ground and plug phasing is important to avoid electrical shock when used with other grounded equipment. Remove the Two'er audio section, after experimenting, to prevent weird results using the balanced modulator in DSB with AM on what is left of the phased-out carrier. Yanking the tubes out (carefully) will do this. Next we see the 6C9 tube in the center with the power transformer behind and a type 60P UHF panel receptacle.


The next photo shows the miniature toroidal tank circuits before they were mounted to the chassis underside with epoxy cement. An FT-243 crystal holder is used to reference the size of the components involved. The left (L1) tank is a bifilar 6 to 2 of #26 Beldsol wired toroid, with an Erie 15-60 PF N1500 trimmer capacitor; and is tuned only by the 2 turn series input capacitor just mentioned, which makes the left (grid) winding into a form of autotransformer for rf. Later on the Q dropped in this circuit

with mechanical tuning adjustments: so we went to an 822EN CRL trimmer. The righthand (L2) tuned circuit uses another toroidal rf tank, wound on an Ami-Tron T-37-10 core, push-pull balanced to single turn output coupling. Both tanks are bifilar wound. Do not use wire any heavier than #24 Beldsol or you *will* break the core! And, it is academic if you'll raise the Q much higher with bigger wire, because circulating current losses may defeat any gain over skin effect at these frequencies.

An important thing here is that we used material type #12* (Carbonyl SF) cores purposely to "keep the field within the core," at a reasonable Q, compared with air-winding, so that shielding would be unnecessary in this unit; and the leads to and from the toroids are much shorter than would be the case with an enclosed trough with removable cover for tuning. It also serves (the cores) to make visible the small Erie 1.5-8.0 pF trimmer for easy tuning with a metal tipped plastic "tuning wand," plus the fact that the size of the miniature components reduces imbalance because of proximity to the chassis lid or front apron, from the inside.

By keeping the "field within the core," we save space, reduce radiation loss (high specific inductivity of 7.43), make the trimmers accessible for tuning without a cover removed, and have shorter leads to the tube. There are no fancy balance controls nor do you see half your power output drop off by removing lid of the Bud CU-482 convertabox! Perfectionists will find that increased balance for a sharper carrier null (more than 20 dB, as observed), can use a JAN type "place-over" shield base over the 6C9 tube socket; and with the unit operating DSB mode, move same eccentrically around-and-about the tube looking for decrease in output, on the reflectometer in forward position with maximum setting on level pot.

The last photo shows the underside of the unit, the neon NE-2's and the fullwave voltage charging electrolytics and the output filter capacitor. The NE-2's were later replaced with higher current NE-83's for longer life (the 83's are pre-aged) and the same component protection. The purpose of the neon's is two fold: First, the highest dc voltage on the plates is limited to the top firing voltage drop of the two in series (about

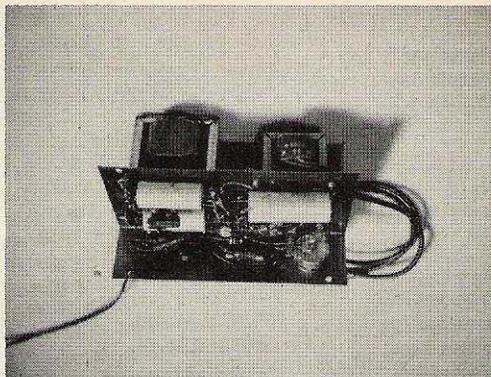

220 volts) plus the drop through the 4.7 k 2 W resistor. Second, the operating point is established for the screen by having a voltage limit of only one neon drop at the lower end of the 20 k pot: this gives rather precise control of the modulated AM output in AB₂. Without the neon's, cathode bombardment may result from the excessively high plate and screen voltages when *not* transmitting or driving with some rf signal, but leaving the mode switch on DSB.

Use

We had trouble, at first, with the Two'er apparently going "spurious;" where the 72 MHz multiplier stage began leaking through the low-Q of the output tank; radiating a 1.5 microvolt signal around town on channel 5. Meck Brazelton, W4JSH, phoned me about it (since he is our local TVI expert), and we thought that this was an image on his new Amphenol Field Strength Meter. But it wasn't! The Two'er output was the cause (ceramic trimmer loosened-up). After this was corrected, we were much cleaner than a nearby Ameco TX-62; and had more 2 meter output.

Stability

The Two'er is crystal controlled and has an output frequency 18 times the fundamental of 8 MHz. Coincidental with the multiplier leak-through mentioned above, we had severe drifting (3 kHz in 10 MIN) which was cleared up with the new trimmer. Art, WB4ENO, helped check this with his new Interceptor receiver. There was some drift over a long period of time; but after a long warm-up this was minimized. We tried W4JKL's idea for "A Low Cost ac Regulator," described in January 1967 73, which improved things. With the Two'er, audio tubes must be removed to lighten the load,

*Available from Permacor, 9540 S. Tulley Ave., Oak Lawn, Ill.

and a 10 watt bulb worked better than 60. Incidentally a similar series current regulator for a dual 30 watt draftsman fluorescent lamp has been in use here for 3 years, with no lamp replacements yet!

Using the KT-92 amp at the full five watts was not necessary. Only about 3 watts were needed to fully modulate 2 watts of rf. Negative peak degeneration allowed this to be; as it is possible in certain cases to use as much audio as rf, power-wise, if you use positive peaks of audio and dissipate maybe ½ watt in the zener impedance of 10 ohms: not overlooking the ½ watt audio dissipated on the screen, itself.

In designing the 6C9 balanced modulator, we chose the rf quiescent point to be fixed at about 2 volts negative (3.9 volt zener) average value; and the dynamic audio screen impedance was figured to be 15 K ohms, when viewed by the secondary winding, of a 10 K CT audio transformer at four watts. It takes a monstrous amount of speech to make the unit flat-top; however, it will do this, even though theory says not! Not at least with screen-fed AM. The best way to set your amp level (and/or preamp) is to use an oscilloscope. Don't worry about DSB and AM being non-compatible! You can initiate QSO's on AM and then just flick a switch to go to DSB.

Traces

Using the 6C9 on-the-air has been a pleasure. Most local hams have not tuned DSB before, and several thought we were flat-topping AM or splattering, until it was explained that they should use their BFO. Oscilloscope traces were made of both screen modulated AM output and DSB, at the same setting of the KT-92 amp gain. It was interesting to see that regular AM had a zero reference line which could be interpolated by visual averaging, in the center; whereas DSB demodulated was like the speech waveform was "all positive or all negative" going; all good quality carrier-less random audio waves, because no carrier was injected in the demodulating probe used. To listen to it on a "james dandy mixer, improved," was to hear the usual, muffled FM type sound on a Brush Clevite brand hi-z crystal earphone. There was a huge increase in level when switching to DSB, as theory would say = 8 dB.


For the engineers in our midst, I'd like to say that the method used here to create a

DSB signal is pretty sound, we think, since the control grids of the 6C9 comprise most of the input capacity for the whole tube; neglecting Miller Effect, so that there is a small imbalance on these inphase electrodes, that very difference compared with the absolute value of the total input capacity is a very small percentage.

Conclusion

In this article we've seen the possibility of low-cost sideband for amateur use in the VHF bands, where it doesn't matter about which sideband is in use! This design can be adapted for 220-225 MHz and maybe 432 MHz with 787 Nuvistor tetrodes! There's really nothing to it, as they say, but start with equipment that doesn't cost too much . . . And start experimenting. If you can get "on," at all with home-brew, this unit should remove some of the hazy ideas you may have had about sideband on VHF. Note that the Two'er output is convenient for driving a varactor for extrapolated UHF design. Finally, the 51J4 set of listeners will have something new to tune, when you get on!
... W4KAE

THE BEST 3/4 METER CONVERTER

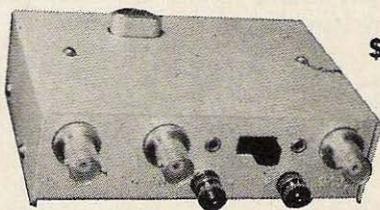

\$49.95

430-432 MHz in. 28-30 MHz out
or up to 440 MHz with additional crystals.

A full description of this fantastic converter would fill this page, but you can take our word for it (or those of hundreds of satisfied users) that it's the best. The reason is simple—we use three RCA dual gate MOSFETs, one bipolar, and 3 diodes in the best circuit ever. Still not convinced? Then send for our free catalog and get the full description, plus photos and even the schematic.

Can't wait? Then send us a postal money order for \$34.95 and we'll rush the 407 out to you. NOTE: The Model 407 is also available in any frequency combination up to 450 MHz (some at lower prices) as listed in our catalog. New York City and State residents add local sales tax.

Closed for Vacation
from Aug. 26 to Sept. 2

VANGUARD LABS

Dept. H, 196-23 Jamaica Ave., Hollis, N.Y. 11423

Getting Your Higher Class License

Part VI — More on Transmitters

Last month we observed that operation of a ham station involves three major items—a transmitter, an antenna, and a receiver.

In this section of the study course for the new Advanced Class license examinations, we're going to take up the second of three groups of questions dealing with transmitters.

The questions from the FCC study list which we'll be dealing with this month are as follows (the numbers are those assigned in the FCC study list, in case you're checking them off as we go):

19. When is an amplifier operating Class A? Class B? Class C?
20. What happens to even-order products in rf linear amplifiers?
23. How are bypass capacitors used? How should their impedance compare to the elements they shunt?
24. How can TVI caused by cross-modulation be remedied?
27. What circuit factors affect the peak envelope power to a transmitter?

Since it's our aim to provide you more than just a list of answers to memorize, we'll follow our normal procedure of paraphrasing all these questions into broader, more general questions covering the same material. If you can answer the more general questions, you should have no trouble at all with the study-list questions—or with those on the actual exam.

The first question of this month's group deals with the classification of amplifiers. Let's rephrase it into the general inquiry, "How are amplifiers classified?"

The second deals with the action of even-order products in rf linear amplifiers. The more general view is, "What are 'products' in amplifiers, and what happens to them?"

The third deals with bypass capacitors and their impedance. Let's make it a little more general by asking, "How can signals on the same wire be separated?"

Number four asks specifically about TVI caused by cross-modulation. Let's generalize

it by asking, "What is cross-modulation and how can it be prevented?"

Finally, instead of the detailed discussion of circuit factors affecting peak envelope power, let's find out "What determines the power output of a transmitter under any conditions?"

Ready? Let's go!

How Are Amplifiers Classified? Maybe this question should begin by asking, "What is an amplifier", because many different kinds of devices can amplify—and an amplifier is anything that amplifies.

For our purposes, though, we can limit the definition of "amplifier" to "a circuit using either vacuum tubes or transistors which accepts as input an electrical signal, and produces as output a second electrical signal which is at every instant proportional to the input signal."

You might say that's not much of a limit, since the output signal can be either greater or less than the input signal—but some "amplifiers" produce voltage loss rather than gain, and a definition must be broad to encompass these too.

One way of classifying the things fenced in by this definition would be as "vacuum-tube" or "transistor" amplifiers, and you will frequently find these classifications used.

Another way would be by the kind of signals handled; this would include such classifications as "audio", "rf", "dc", "if", and "ac" amplifiers. This method of classification, also, is popular.

As it happens, though, a system of classification based upon the amplifier's operating conditions can cut across all other classification systems. This system, which parcels all amplifiers into either Class A, Class B, or Class C, has a unique advantage in that the A, B, or C classification tells you quite a bit about the amplifier's signal-handling characteristics.

If only one such system were in general

use we would have little to discuss here. Unfortunately, a number of systems—all differing in at least one detail from all the rest—use the same A, B, C classifications. If you have learned only one of these, you may find that you're not talking about the same thing as the other guy even though you're using the same words.

For instance, a Class A amplifier is sometimes defined as an amplifier in which current flow in the output circuit remains constant during the operating cycle. This definition cannot be correct—if current flow remained constant at all times, no signal could be developed! If this definition is modified to read "average current flow", then it's okay.

But other authorities define a Class A amplifier as one in which current in the output circuit is never cut off during the operating cycle.

This definition, too, is okay—but it isn't consistent with the first. That's natural, since we're dealing with two different classifications systems that just happen to use the same names.

Still another definition frequently used for a Class A amplifier is "one in which gain remains constant"; a fourth requires that the amplifier be distortion-free.

Before we get completely confused, let's turn and look at definitions for Class B. The system which defines Class A operation as "constant average current" defines Class B as "average current varying". That which calls Class A "current never cut off" class Class B "current cut off for less than half the operating cycle". That which calls Class A "constant gain" calls Class B "varying gain", and that which calls Class A "distortion-free" calls Class B "low-distortion".

How about Class C? In order, it may be defined as "extreme current variation", "cutoff for more than half the cycle", "all-or-none gain", or "highly distorted".

With all these different sets of definitions running around, how are we ever going to come up with an answer which we can consider to be the *the* right answer—or can we?

The answer is yes, we can, because all of these various systems of classification are attempting to describe the same general concepts, and the apparent differences are more in the words chosen to describe the concepts than in the concepts themselves.

Before we get into our attempt to bridge


this particular communications gap—and it is a major gap—let's take note of a couple of facts. All of the four systems we've sketched out use the A, B, or C letters to indicate "pure" cases, and in practice most amplifiers fall somewhere in between. This is particularly true of the boundaries between class A and Class B, and as a result most amplifiers we meet in real life are known as Class AB amplifiers. These are a little of both, and so are exclusively neither!

The concept of a Class A amplifier is that of an "ideal" amplifier in which any input signal is faithfully reproduced at the output, without distortion. In a perfect amplifier, this normally would require that current keep flowing throughout the entire operating cycle (since all devices are imperfect at the extreme limits of their operating ranges, and to be perfect we would have to avoid the imperfect regions), and that the average current flow be constant (if the input signal is symmetrical). Gain would also be constant. Thus all the definitions merge into one—for a perfect amplifier.

The concept of Class B operation is again based upon a perfect circuit, in which non-linearity would be impossible. If the current is biased precisely to the point at which output-circuit flow ceases, then any positive-going input signal would permit current flow in the output circuit. Since we defined the circuit as "perfect" and without any non-linearities, as soon as current flow is permitted the amplifier is producing its normal gain. This in turn makes the output signal a replica of the input signal—but only for the half-cycle of input signal which permits current flow.

Current flow in this arrangement is for exactly one-half of the operating cycle. As a result, average current flow would fluctuate with the signal level—stronger signals would draw more current, on average, than weaker ones. Gain would vary from zero when the amplifier is cut off to normal when it is turned on. And distortion would be 50%; none when the amplifier was on, but total when it was cut off.

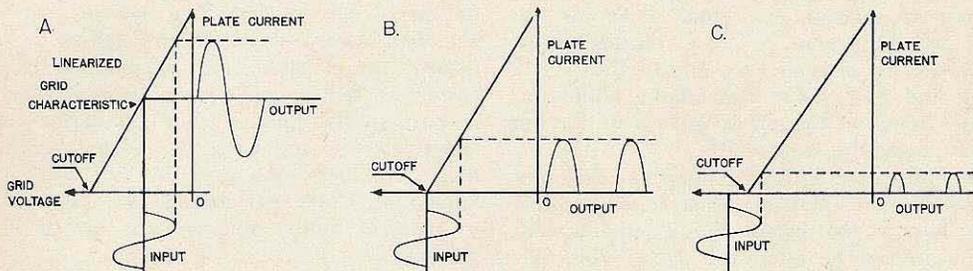In practice, of course, it's almost impossible to keep the bias at the exact point to permit current flow for precisely one-half cycle. Even were it easy, tubes and transistors have such high distortion at low current that proper operation would be difficult. For this reason, in "Class B" designs



Class A—Output is replica of input current flows throughout cycle

Class B—Output is only half of input current flows for only half cycle

Class C—Output is like input only in timing current flows for less than 1/2 cycle

Fig. 1—Transfer curves (with idealized transfer characteristic) illustrate differences between Classes A, B, and C. Actual amplifiers never have sharp break at cutoff, so ideal operation shown here can never be realized. Practical amplifiers do come close to this, however. For illustration, all input signals are same amplitude. Class C circuits are normally overdriven to achieve full efficiency.

bias is set so that current flows for more than half a cycle, but less than a full cycle. In some designs it always flows, but varies widely over a cycle; both these variations are, technically, Class AB operation.

Finally we have the concept of Class C operation. One authority has described this, very accurately, as "switching" operation. The tube or transistor is completely cut off most of the time, and is "switched" on by the most positive peaks of the input signal. When "on", it acts like a closed switch and conducts as heavily as it can. The output is a series of current pulses, each corresponding with the tip of an input signal.

Current flow in this circuit is appreciably less than half an operating cycle, and is either all or nothing at all. Gain, similarly, is "infinite" when the amplifier is "on", and zero when it is "off". Distortion is almost total; those input signals which are strong enough to turn it "on" turn it all the way "on", and those which aren't, leave it "off".

You may notice that in the description of these three concepts we haven't mentioned "grid current", although quite a few persons tend to believe that the flow of grid current is connected directly with the A, B, or C classifications of an amplifier. They use the condition of "no grid current" to define "Class A", and "grid current" to define "Class C", then defining "Class B" as the region between A and C.

However, it is quite possible to design a Class A amplifier in which grid current is permitted to flow, and quite a few Class C circuits without grid current have been built since the high-perveance TV horizontal-output tubes became popular. Presence or absence of grid current is normally indicated by a subscript on the classification, such as AB₁ or C₂; the "1" indicates no grid current, while "2" shows that grid current flows.

In actual fact, though, the grid-current condition has nothing to do with the operating classification. Class A amplifiers may be A₁ or A₂, and Class C circuits may be either C₁ or C₂. The effective classification criterion is the duration of current flow in the output circuit.

Class A amplifiers are used almost exclusively when low-distortion amplification is needed, as in audio circuits or low-level SSB generation. Most receiver circuits are Class A.

Class AB or B amplifiers are widely used to deliver moderate amounts of power, with limited distortion. The audio output stages of many PA amplifiers and almost all hi-fi installations operate in Class AB. Similarly, almost all SSB final liners are either AB or B. In audio, use of class AB or B requires a balanced (push-pull) circuit in order to cancel out the inherent distortion. When rf is being amplified, distortion of individual cycles is not important so long

as the *envelope* of the signal is faithfully reproduced. A properly adjusted amplifier will do this, and so an unbalanced circuit may be used.

Class C amplifiers are limited to rf power amplification in which envelope distortion is not important. This, in turn, prohibits their use for SSB or AM amplifiers, although if high-level modulation is employed all the rf stages of an AM transmitter may operate Class C since modulation is applied only at the output of the final stage. The major advantage of the Class C amplifier is its relative efficiency; Class A amplifiers normally produce about 1 watt out for every 4 watts dc input. Class B circuits may produce as much as 2 watts out for the same 4 watts dc input, but Class C circuits usually produce at least 3 watts and sometimes even more for every 4 watts in.

What Are "Products" in Amplifiers, and What Happens to Them? The word "Product" has become a "magic word" in ham radio. We have "product detectors" and "distortion products", as well as many others. But what are these "products" we keep talking about?

In an earlier instalment of this series we noted that application of two signals to any non-linear element resulted in the production of, not only the original signals, but new signals made up of the sum and difference frequencies of the originals. This "mixing" action is the basis of all kinds of modulation, as well as of the superhet receiver and all common SSB generators.

A "product" is any output signal from such a mixing action. The original signals are "first-order" products, since each represents "one" times itself plus or minus "zero" times the other. The coefficients "one" and "zero" by which the input signals are multiplied produce a sum or difference of "one" whether they are added or subtracted, and this sum or difference represents the "order" of the product.

Similarly, the output signal representing the sum of the two original frequencies is a "second-order" product, since it is "one" times signal F1, plus "one" times signal F2, and one and one make two. The difference signal, on the other hand, is a "zero-order" product, since one minus one is zero.

Keep in mind that the same non-linear

What this means, then, is that in *any* mixing circuit you will never have just two frequencies with which to deal. In addition to the two frequencies you put in yourself, you have many harmonics of each which are generated by mixing action inside the circuit.

Each of these harmonics can mix with each and every other signal present in the circuit, to produce a near-infinite number of "products".

This is *not* just a hypothetical fiction; it actually happens in all non-linear circuits—and virtually all circuits are non-linear to at least some degree.

In a "linear" amplifier we take great pains to reduce the mixing action—in this case we call it "intermodulation"—to the smallest possible degree, but we can never eliminate it completely.

Since it cannot be eliminated, the output could be expected to contain at least small portions of all the possible products from any pair of frequencies present in the input at any time.

In practice, though, only the odd-order products can be found. The even-order products appear to vanish. Why?

F2	F1 x 1	2	3	4	5	6	7	8	9	10	11	12	13
x1	F ₀ x 0	1	2	3	4	5	6	7	8	9	10	11	15
2	-1	0	1	2	3	4	5	6	7	8	9	10	14
3	-2	-1	0	1	2	3	4	5	6	7	8	9	13
4	-3	-2	-1	0	1	2	3	4	5	6	7	8	12
5	-4	-3	-2	-1	0	1	2	3	4	5	6	7	11
6	-5	-4	-3	-2	-1	0	1	2	3	4	5	6	10
7	-6	-5	-4	-3	-2	-1	0	1	2	3	4	5	9
8	-7	-6	-5	-4	-3	-2	-1	0	1	2	3	4	8
9	-8	-7	-6	-5	-4	-3	-2	-1	0	1	2	3	7
10	-9	-8	-7	-6	-5	-4	-3	-2	-1	0	1	2	6
11	-10	-9	-8	-7	-6	-5	-4	-3	-2	-1	0	1	5
12	-11	-10	-9	-8	-7	-6	-5	-4	-3	-2	-1	0	4

Fig. 2—Difference products for first 12 harmonics of two tones are shown here. Those products near the original frequency (indicated by 1 and -1 in the table) cannot be rejected by output tank circuit and so appear in amplifier output. All other products disappear in the output circuit, but may still act as additional tones to create new families of products.

element which permits mixing of two input signals also permits just one signal to mix with itself to produce a second-order product which is the second harmonic of the single input signal. This second-order product can then mix with the original signal to produce a third-order product (the third

harmonic), and this process can continue in an infinite loop so long as the new harmonics which are generated by each step are strong enough to be detected.

Fig. 2 shows the reason. In this chart, we're not interested in exact frequencies. We are, however, interested in the *order* of the products produced by two close but not identical frequencies such as those typically present in a voice sideband. We call these two frequencies F1 and F2. In Fig. 2, each column represents the products of one harmonic of F1, from the first (fundamental) to the 12th, and each row represents the products of one harmonic of F2 over the same range. The column-row intersections contain the number which results when we subtract the harmonic order of F2 from that of F1. As we have already seen, this number (ignoring its sign) represents the order of the corresponding product.

For example, the product formed by the 6th harmonic of F1 and the 4th harmonic of F2, as shown on Fig. 2, is of order 2. The "sum" products formed by F1+F2 are not shown.

The diagonal lines in Fig. 2 represent the selectivity of the output circuit of our amplifier. This tuned circuit can pass most frequencies which are approximately the same as those of F1 and F2, but rejects frequencies which are as much as twice F1 or F2, or as low as half.

Note that all the even-order products are either 0, 2, 4, or higher even numbers. None of these products fall within the passband of the output circuit.

The odd-order products, however, all include at least two products which are of approximately the same frequency as the original signals, and so get through the output circuits. The 5th-order product of either $3F1-2F2$ or $2F1-3F2$ has an order of 1. The highest-order products shown in this illustration are the 23rd order, and two of these still fall within the passband.

Fig. 3 shows this in more detail for the first nine orders of products. In this chart, all differences greater than the nominal original frequency (FO) are omitted. You can see readily that the even-order harmonics fail to fall within the passband, but all the odd-order groupings have two separate difference frequencies which do come inside the limits and get out to cause trouble.

ORDER	COMPONENTS	DIFFERENCE
2	F1, F2	DC
3	F1, 2F2	FO
	2F1, F2	FO
4	2F1, 2F2	DC
5	2F1, 3F2	FO
	3F1, 2F2	FO
6	3F1, 3F2	DC
7	3F1, 4F2	FO
	4F1, 3F2	FO
8	4F1, 4F2	DC
9	4F1, 5F2	FO
	5F1, 4F2	FO

Fig. 3—This table shows only the difference products near the input frequencies and near DC level for the first 5 harmonics of two input tones, and illustrates how the product "order" is identified.

It's especially important to realize that these distortion products cannot be filtered, since they survive in the first place only because they are in the same frequency range as the desired signals. The only way to minimize them is to adjust and operate the amplifier circuit in such a manner as to make it as linear as possible. In such a case, mixing action will be small compared to the amplification, and the unwanted products will be much weaker than the desired signal. Ratios of as much as 50 db between distortion and signal are not uncommon—but overload of the amplifier in an effort to get another watt out to the antenna can make the distortion as strong as the signal.

How Can Signals On The Same Wire Be Separated? Within almost any of our amplifier circuits, we have both dc power for the circuit and ac signal being processed by the circuit present on the same wires. Outside the limits of the circuit, however, we want to keep the ac and dc signals separate. That's the meaning of this question—how can we do it?

The secret of accomplishing this feat of signal separation lies in the fact that ac can be transferred through certain circuit elements which block dc, while dc can go through others which tend to block ac from passing.

For instance, ac will flow through a capacitor while dc will not; on the other hand, dc flows through an inductor while ac is impeded. This is the whole basis of filtering.

Any practical circuit element, of course, has resistance, inductance, and capacitance, all at the same time. This is true even for such a simple element as an inch-long

piece of hookup wire! For a length of straight wire all three are very small values—but they are not always negligible. The inductance present in a fraction of an inch of wire, for instance, can be used to tune a bypass capacitor to form a series-resonant circuit, and thus increase its bypassing efficiency.

To separate an ac signal from a dc signal or power flow on the same wire, then, we must separate the wire to form two paths and then place capacitance in one path to limit it to ac flow while placing inductance in the other path to restrict it for dc only.

We frequently use this principle in untuned rf amplifiers, where an rf choke provides the inductance and a coupling capacitor provides the ac path for the output signal.

When we're dealing with an amplifier circuit, both the ac and the dc output-circuit paths must be complete, from amplifier-tube cathode (or emitter) through the tube or transistor to the plate (or collector), and back to the cathode. The desired output signal is coupled to the next stage by either capacitance or inductive (transformer) coupling in most cases, but this doesn't completely satisfy the requirement for a complete path. Some parts of the circuit, for example, must be at ground potential for ac voltages while remaining at high potential for dc—one example is the screen grid of a tetrode or pentode.

The function of a bypass capacitor is to complete such an ac current path by routing the ac directly to ground, yet keeping the dc voltage isolated. Another function for which bypass capacitors are frequently used is that of maintaining ac ground points throughout the power-supply wiring of a unit, in order to prevent undesired coupling between successive stages. And still another function of some bypass capacitors is that of assuring that all rf circuits contain minimum-length current paths, to prevent "ground loops" which can cause undesired coupling between portions of the same circuit.

In order to perform all these functions, the bypass capacitor must appear to be a very low impedance for the particular ac current expected. However, any specific value of capacitance which might be a "very low" impedance for current of one frequency might be a very high impedance for current of much lower frequency.

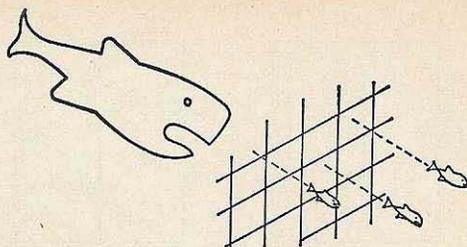


Fig. 4—The problem of separating two signals on one wire is very much like that met by fish-breeders who need to keep the little fish away from the hungry big ones in the same tank. Fish-breeders use a mesh "filter" which the little ones can get through but the big ones cannot. We use impedances to filter signals in much the same manner.

And even if the rated capacitance value represents a low impedance, the physical construction of the capacitor might be such that non-rated inductance could reduce (or even cancel out) its actual capacitance within the circuit.

This is the reason that flat or disc ceramic capacitors are so frequently favored for rf bypass use; their construction minimizes inductance. For most rf applications; capacitance values from 0.01 to 0.001 μf are suitable. In critical positions, capacitance values should be calculated—and this requires a knowledge of the dc impedances to be expected in the circuit.

The rule of thumb most often used when calculating the required value of a bypass capacitor's is that the capacitor's impedance should be at least 10 times less than the impedance of the rest of the circuit.

That is, for instance, in a screen-grid circuit supplied its dc through a 1000-ohm resistor, the bypass capacitor's impedance could be any value up to 100 ohms.

This rule is based upon the fact that in a network containing parallel impedances, current flow through each is determined by the ratio of each impedance to the others. The most current will flow through the smallest impedance. If one is at least 10 times less than any other, that one will carry at least 90 percent of the current.

The figure "10" is not sacred in this rule, but represents the experience of some 40 years of engineers. The ratio certainly should not be less than 10-to-1; an even greater ratio offers better bypassing, up to the point at which a capacitor which is so

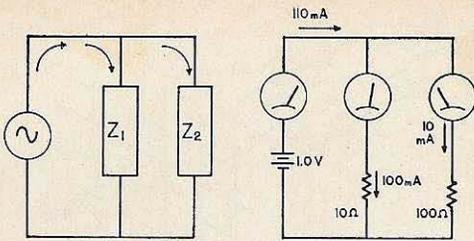


Fig. 5—Principle upon which bypass capacitors work is shown here with generalized impedances (top) and with resistors (bottom). If 10-ohm and 100-ohm resistors are connected in parallel, 10 times as much current flows through the smaller resistor. Similarly, if a low impedance is in parallel with a high one, the low impedance takes most of the current. Bypasses are deliberately-introduced very-low impedances, to “bypass” most of the current away from the rest of the circuit (represented by the higher impedance).

large physically that it begins to lose its effectiveness becomes required.

The filtering or “decoupling” uses of bypass capacitors are not limited to power circuits. They are also widely used in CW keying circuits, for instance, and also (by proper and somewhat critical choice of capacitor values) to bypass rf from audio signal lines and prevent rf feedback into modulators. In every case, the bypass capacitor should offer an impedance to the signal being bypassed which is much lower than that of the element which the capacitor shunts.

What Is Cross-Modulation and How Can It Be Prevented? The term “cross-modulation” is most often heard with reference to TVI, unless you happen to be a VHF addict. In the VHF world, it more often is used with regard to creation of spurious signals in the front ends of sensitive receivers.

No matter which context the term conveys to you, “cross-modulation” is nothing more complicated than our old friend, the mixing action which results when two signals reach a non-linear circuit element.

When the mixing is intentional, as in a superhet receiver, a SSB generator, or a detector, we’re happy and then we call it by its proper name, “mixing”.

When it’s unintentional—as in a distortion-producing amplifier, a case of TVI, or a blocked VHF receiver—we use such

names as “intermodulation”, “distortion products”, and “cross-modulation”, as well as many others which won’t bear repeating in a publication circulated through the U.S. mails!

But whether intentional or unintentional, the process remains the same. Two signals applied to a non-linear circuit element produce not only the original signals, but a whole host of products as well.

If mixing is intentional, it’s usually done within a circuit designed for that purpose—but there’s no physical law which requires that the non-linear element be a part of any designed circuit. For instance, a corroded gutterpipe or a leaky insulator on a power-pole guywire may form a sort of happenstance electrolytic capacitor or chemical rectifier, and there’s nothing much less linear than a device which changes ac to dc.

That’s one of the major causes of “cross-modulation”. Two relatively strong signals reach some completely unexpected (and frequently impossible-to-locate) object which happens to be, in addition to its intended use, a non-linear element. There they mix, and all the products are radiated back into space along with the original signals. In the case of TVI, one of the signals may be your own transmitter and the other may be any other transmitter. Neither need be

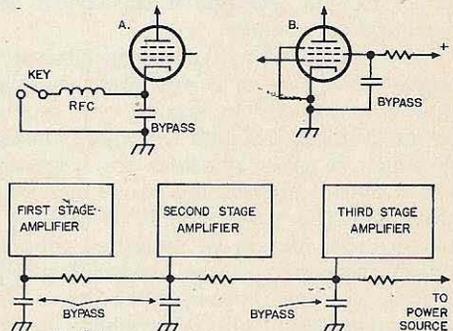


Fig. 6—Several typical applications of bypass capacitors for separation of ac and dc signals are shown here. At A, the long leads necessary to reach the key contacts in a cathode-keyed CW transmitter are isolated from the rf circuit by a choke, and the rf circuit completed by the bypass. At B, the bypass acts to keep the screen grid at the same rf voltage as the cathode by providing an ac short-circuit, while leaving dc voltage at its normal higher potential. At C, bypasses at each stage decouple the various stages by keeping ac signals off of the common power-supply leads.

	F_1	$2F_1$	$3F_1$	$4F_1$	$5F_1$
F_2	$F_1 + F_2$	$2F_1 + F_2$	$3F_1 + F_2$	$4F_1 + F_2$	$5F_1 + F_2$
	$F_1 - F_2$	$2F_1 - F_2$	$3F_1 - F_2$	$4F_1 - F_2$	$5F_1 - F_2$
$2F_2$	$F_1 + 2F_2$	$2F_1 + 2F_2$	$3F_1 + 2F_2$	$4F_1 + 2F_2$	$5F_1 + 2F_2$
	$F_1 - 2F_2$	$2F_1 - 2F_2$	$3F_1 - 2F_2$	$4F_1 - 2F_2$	$5F_1 - 2F_2$
$3F_2$	$F_1 + 3F_2$	$2F_1 + 3F_2$	$3F_1 + 3F_2$	$4F_1 + 3F_2$	$5F_1 + 3F_2$
	$F_1 - 3F_2$	$2F_1 - 3F_2$	$3F_1 - 3F_2$	$4F_1 - 3F_2$	$5F_1 - 3F_2$
$4F_2$	$F_1 + 4F_2$	$2F_1 + 4F_2$	$3F_1 + 4F_2$	$4F_1 + 4F_2$	$5F_1 + 4F_2$
	$F_1 - 4F_2$	$2F_1 - 4F_2$	$3F_1 - 4F_2$	$4F_1 - 4F_2$	$5F_1 - 4F_2$
$5F_2$	$F_1 + 5F_2$	$2F_1 + 5F_2$	$3F_1 + 5F_2$	$4F_1 + 5F_2$	$5F_1 + 5F_2$
	$F_1 - 5F_2$	$2F_1 - 5F_2$	$3F_1 - 5F_2$	$4F_1 - 5F_2$	$5F_1 - 5F_2$

- $F_{1M} = MF_1$
- $F_{2N} = NF_2$
- $P_{MN} = F_{1M} \pm F_{2N}$
- RANGE OF M AND N IS FROM 1 TO INFINITY; PRACTICAL RANGE IS FROM 1 TO 10.

Fig. 7—This table shows the formation of mixing products by two input frequencies F_1 and F_2 and the first 5 harmonics of each. Note that 50 separate products are formed here alone, 25 by the sums and 25 by the differences, although not all of these products are of different frequencies. The equations numbered 1, 2, and 3 define the table for all harmonics; m and n in these equations indicate the harmonics, while P_{mn} is the product pair for any specific harmonics. Whenever P_{mn} has the same frequency as some transmission of interest to someone else, that transmission suffers cross-modulation interference.

operating at anywhere near the frequency of the TV channel—the only requirement is that one of the products of the mixing come out on or near the TV station's frequency, and presto, instant TVI.

This form of TVI is quite difficult to isolate because it will go away whenever either of the two original signals goes off the air. You don't have to do a thing. If the other transmitter goes dead, the TVI ceases.

If the interfering product is formed by your fundamental, any modulation on your signal will be present on the product as well, making it quite easy for the TV viewer to obtain your call and work from there to lodge his complaints.

And the biggest problem about it is that you can do almost nothing to cure it. No malfunction of your transmitter is involved. No filtering, either at the transmitter or at the TV receiver, can stop it, since the interference is an actual radiated signal at the frequency of the desired channel and any filter which would remove it would remove the TV station as well.

The one sure cure is to change your operating frequency enough to move the offending product away from any TV channels. This doesn't actually cure the mixing,

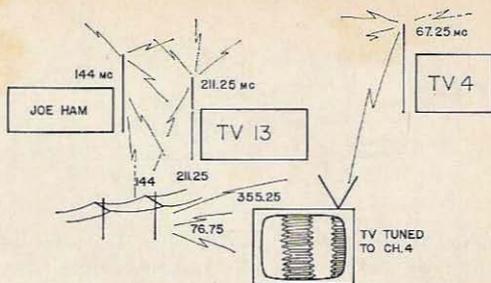


Fig. 8—How cross-modulation causes interference. Joe Ham, operating a completely clean transmitter at 144.0 MHz, and TV Channel 13, also completely clean at 211.25 MHz (video carrier frequency) are on the air at the same time. Somewhere in the neighborhood, a corroded connection on a power-pole guy wire is acting as a non-linear element. Meanwhile, a TV viewer is trying to watch Channel 4 at 67.25 MHz. The 144 and 211.25 MHz signals mix to produce products all over the rf spectrum (only a few are shown). One of these is at 67.25 and interferes with the Channel 4 signal. If, however, Joe moves his frequency up to 144.1, the interfering product will move down to 67.15 MHz and may no longer cause trouble.

but it eliminates any interference to TV reception. Often a change of only a few kilocycles is adequate.

When cross-modulation is interfering with your own operation the picture is different. A classic case of this type of cross-modulation can be observed by any 2-meter operator who lives in an area served by television channels 4 and 13. The frequency separation between these two channels is exactly 144 MHz. When both stations are broadcasting, the DX portion of the band, from the bottom edge up to at least 144.05 MHz, becomes a howling mass of cross-modulated video, FM audio, and carriers.

The only cure for this problem is to avoid that part of the band, which is rather difficult if the stations you want to work stay there most of the time. Unlike ham stations, TV broadcasters are not free to change frequencies.

A cure which is sometimes effective is to locate and eliminate the offending non-linear element. If you're lucky you may find it within a month or two—but keep in mind that a 1-watt signal can be heard for many miles. The re-radiated products are considerably weaker than one watt, but the cause of the crossmodulation may be anywhere within a two-to-three mile

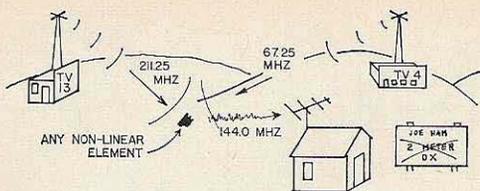


Fig. 9—It's not just the TV audience who get hurt by the problem of cross-modulation. Any two signals can do it, and one of the prime examples is that occurring when TV channels 4 and 13 operate in the same locality. 2-meter DX around 144.0 MHz is completely wiped out by the interference which results. Since any type of non-linear element can cause the mixing action, it's not normally practical to eliminate this problem; most of us just learn to live with it.

radius of your location. One such cause is all it takes, but there may be many. The odds are against you.

Cross-modulation is not limited to the "natural cause" case. It can also occur in the front end of your receiver, and frequently does. This type of cross-modulation can be cured readily by filtering out the offending signal. If the unwanted strong signals are too close to your desired signal (which is possible if you are getting a third-order product) for this to be practical, you may have to introduce an attenuator between antenna and receiver to cut back all signal strengths to the point that no overloading and resulting cross-modulation occurs. This cure is frequently used.

What Determines the Power Output of a Transmitter? Some amateur transmitters boast a power output of more than 2000 watts, legally. Others find favor with do-it-the-hard-way enthusiasts and radiate only a few milliwatts or even microwatts. Each type, as well as the wide spectrum between these limits, has its place.

But what determines the power output? No single answer to this question is possible, because power output is determined by many things. One of the most important factors is that of *what* power output we're talking about, since transmitters are rated by such various standards as average input power, average output power, peak input power, peak output power, peak envelope power (both input and output), and even indicated average input power!

Any attempt to compare various methods

of transmission almost invariably comes a cropper over these differing types of rating power, and the FCC regulations themselves have a sort of built-in discrimination—which is, of all things, in favor of voice transmission and against CW!

The regulations, you see, limit the indicated input power to the stage or stages of the transmitter which supply rf power to the antenna. On the face of it this appears to be consistent for all modes of transmission.

Yet with FM, the indicated input power and the peak envelope input power are identical. The same is true with CW. High-level AM indicates only the carrier power; the additional power present in the sidebands which contributes to peak envelope power is not indicated. This means that with AM, a PEP input of 1500 watts is permitted if audio power is included. When SSB or DSB, with suppressed carrier, are employed, the indicators swing at a syllabic rate. In this case, the regulations state that the 1000-watt limit must never be exceeded by the indicators. They do recognize that the indicators cannot keep up with instantaneous peak levels, by specifying response times for the indicators of $\frac{1}{4}$ second maximum. This means that with SSB or DSB, PEP inputs of 2000 to 2500 watts are permissible just so long as the meters never read more than 1000 watts.

The same flickering effect is present when CW is transmitted, but the CW operator is denied the privilege of taking advantage of it. He must make his power measurements with key down; if he sets up for 1000 watts in this condition, his indicators won't exceed 750 watts in most cases. If he has a particularly choppy first, they may not exceed 600 watts.

In all these cases, "indicated average input power" is 1000 watts. The peak envelope powers, though, vary from 1000 watts up through something over 2000 watts depending upon the type of transmissions being generated. Transmission type, then, must be one of the factors determining peak envelope power's relation to indicated average input power.

It does not, however, affect the peak-power capability of an amplifier. The peak-power capabilities are determined by the characteristics of the tubes or transistors employed in the final stage or stages, by the supply voltage and the amount of cur-

rent available rapidly (size of capacitors in power supply filter), and by the other design characteristics of the amplifier circuit.

Characteristics of the tubes or transistors in the final stage which determine a transmitter's peak-power capabilities are (1) the maximum current-handling ability of the cathode or emitter and (2) the permissible power dissipation or the plate or collector.

The maximum current-handling ability is not directly related to the rated maximum current. A cathode surface may be able to handle a full ampere for a sufficiently brief period of time, yet be rated for only 50 to 100 mA maximum current. This comes about because the *rated* maximum current is a dc value and the tube is supposedly able to handle this amount of current for any period of time. The absolute maximum though, is set by point at which the cathode begins to physically disintegrate and is far greater. Tubes such as the 6C4, for instance, can deliver peak powers in the kilowatt range when operated under pulse conditions with sufficiently long time allowed for recovery between the extremely brief periods of active operation—but are hard put to deliver more than a watt or so in continuous operation.

The influence of the maximum current-handling ability is to set an upper limit on peak power. The tube cannot handle more current than it can; when you have all it can handle, you can't have any more.

The permissible power-dissipation for the tube determines peak-power capability by limiting the amount of *heat* which can be tolerated. This, in turn, is influenced by the type of amplifier involved. A Class A amplifier may turn $\frac{1}{2}$ of its dc input power into heat, while a Class C amplifier (using the same tube) might make heat from only $\frac{1}{3}$ of its input.

Thus a tube capable of dissipating 10 watts would be able to run at an average power input of only 13 $\frac{1}{2}$ watts if operated Class A; 3 $\frac{1}{2}$ watts power output would be produced, and the remaining 10 watts would be dissipated by the tube. The same tube, in Class C, could run at an average power input of 50 watts. Of these 50 watts, 40 would appear as output and the other 10 would heat up the transmitter.

Note that the power-dissipation limit applies to *average* power, not to peak. Heating and cooling take time, and anything that requires an appreciable period of time

must involve only the *average* values over that period of time.

Note also that the effect of the power-dissipation factor is strongly dependent upon the operating conditions chosen for the amplifier—and these are included in those "other" design factors for the amplifier circuit.

The supply voltage and the amount of current rapidly available determine power capabilities, because power is simply the result of multiplying voltage times current. Voltage can be stepped up or down by means of transformers, but in any practical transmitter the voltage applied to the final amplifier stage at any instant rarely exceeds twice the voltage of the power supply, so this supply voltage is still a major factor.

Rapid availability of current is a factor not so widely recognized. In a power supply, though, whenever any current is taken out to produce rf power to be transmitted, that

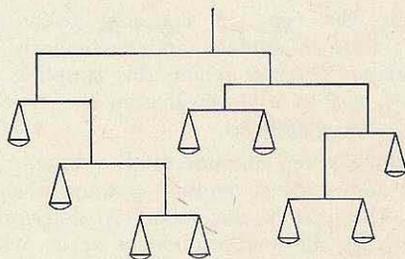


Fig. 10—Circuit factors affecting transmitter power are somewhat like the complicated set of scales shown here. Any change in any one factor will affect the balance of all other factors as well, but almost any combination of the various factors can be made to balance out with sufficient care.

current must be restored through the rectifiers. The current taken out on an instantaneous power *peak* may be much greater than that which the rectifiers can supply, if there will be enough time before the next peak (while less current is being taken out) to make up the difference. The current ratings of the rectifiers, then, are not nearly so critical in determining transmitter power limits as is the amount of current *storage* within the supply. This means that filter capacitors on the output side of the supply should be as large in value as possible. It's difficult to have too much.

Some of the other design factors which influence power capability include the choice to operate Class A, B, or C, discussed

Now, IT'S HERE...THE VEEFO!

Clegg's NEW ALL SOLID STATE VFO FOR VHF

Designed to function with Clegg's 22'er and 66'er, the VEEFO also offers the following superb features for use with any of the popular 2 and 6 meter transceivers, transmitters or exciters.

- FET oscillator and isolation amplifier for rock solid stability
- Crystal holder plug with torroidal matching transformer and CO-AX cable furnished
- Self-contained, regulated power supply
- SPOT switch
- 12 to 13 MHz tuning range — covers 50-52, 144-148 and 220-225 MHz
- VELVET SMOOTH Vernier tuning dial — 10 kHz readability
- Rugged, compact, attractive construction



AMATEUR NET PRICE
\$49.50 complete

Orders accompanied with full payment shipped prepaid. Please include \$10.00 deposit with COD orders.

e.t. *Clegg associates inc.* 7 LITTELL ROAD, EAST HANOVER, N. J. 07936
(212) 887-4940

earlier; the type of coupling from amplifier tube to antenna and particularly the impedance level at which this coupling operates; and to a lesser degree the type of modulation employed.

With a given amount of dc voltage supplied and a given amount of current available, the power developed is determined directly by the load impedance across which the output signal is developed. The "Q" of the final tank circuit gets into the act since it determines the load impedance "seen" by the tube. For any useful power to be produced, the Q must be relatively low. A high-Q circuit may permit as much power to be developed at the tube as does a low-Q one, but the power cannot get out of the circuit if Q is high (by the definition of Q as the ratio of power stored during a cycle to power released during a cycle) and thus is of no use to you. At the same time, Q must be moderately high or the output circuit won't provide the desired tuning action. Choice of Q is always a compromise; the choice is normally made by the "loading" control of the transmitter. When loading is light, the Q is high; when loading is increased, the Q decreases.

Type of modulation to be used affects power in a number of subtle ways. Some of them were mentioned in the discussion of the various legal power limits. The "on-off" effect brought out there for SSB, DSB, and CW signals permits the factor of power dissipation to be modified by intelligent

choice. For example, SSB and DSB signals have a very low *average* power in comparison to their peak-envelope-power levels. For this reason, when only such signals are to be transmitted tubes with very low power-dissipation ratings but very high peak-current capabilities may be chosen, and relatively great amounts of output power be developed. This is the reasoning behind the popularity of TV-output tubes as final amplifiers in the 100-400 watt range. The voltage and peak-current ratings of these tubes permit peak powers of 400 watts or more; power dissipation is low, but in DSB or SSB service the average power to be dissipated is also low and this factor becomes only a small restriction.

For FM service, or for CW, such tubes are pushing their limits at 100 watts or so. The only way in which even these power levels can be realized is to use the most efficient points available in Class C operation, to keep power dissipation within limits. Even so, it's not uncommon to literally melt down parts of the glass envelopes of such tubes in this application!

Next Month. One of the most important practical aspects of radio theory, though, is the making of measurements. Without measurements, you cannot operate. The importance of measurements can be judged by the fact that most of the FCC regulations require measurements of some type—and a major part of the examination deals with measurement techniques. That's our subject, next time. ■

License Plate Holder

One of the nicest little low cost items to turn up recently is a license plate holder which is being marketed by Ken Walkey WB6RSP. Most of the call letter license plates are the standard 6" x 12" and they really stand out when mounted in the Walkey holders. Across the bottom in blue letters on white background it tells the world that you are a radio amateur. The holders are triple chromium plated so they will not rust. They are \$3.95 a pair from Ken Walkey, Box 3446, Granada Hills, California 91344.

Help Wanted

Amateurs looking for a change of job would do well to run an ad in our classified section. A 25 word ad is only \$2 plus \$1 extra for a box number if you wish to remain anonymous. Almost one third of our readers are in a position to either hire men or influence the hiring of men. And you know that all of the ham manufacturers are reading the magazine.

There is an impossible demand for good technicians and engineers now. Try 73 and see what happens.

Employers could do a lot worse than to run help wanted ads in 73. A ham will usually be a better engineer or technician than a straight school man . . . it is the difference between it just being a job and being a dedication. Commercial ads in the classified are \$10 for 25 words plus the dollar for a box service if confidential replies are wanted.


In my talking with ham manufacturers I am constantly being asked if I know where they can find good men. The need is great. Are you working below your level of earnings and opportunity?

MOVING?

Every day we get a handful of wrappers back from the post office with either a change of address on them or a note that the subscriber has moved and left no address. The magazines are thrown out and just the wrapper returned. Please don't expect us to send you another copy if you forget to let us know about your new address. And remember that in this day of the extra rapid computer it takes six weeks to make an address change instead of the few days it used to when we worked slowly and by hand.

THE BEST 2 METER CONVERTER

Model 407
\$34.95
ppd.

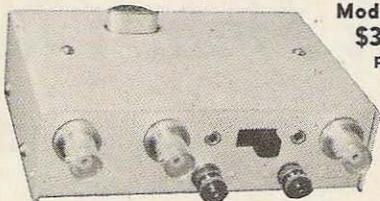

144-146 MHz in. 28-30 MHz out
or 146-148 MHz with a second crystal

A full description of this fantastic converter would fill this page, but you can take our word for it (or those of hundreds of satisfied users) that it's the best. The reason is simple—we use three RCA dual gate MOSFETs, one bipolar, and 3 diodes in the best circuit ever. Still not convinced? Then send for our free catalog and get the full description, plus photos and even the schematic.

Can't wait? Then send us a postal money order for \$34.95 and we'll rush the 407 out to you. NOTE: The Model 407 is also available in any frequency combination up to 450 MHz (some at higher prices) as listed in our catalog. New York City and State residents add local sales tax.

Closed for Vacation
from Aug. 26 to Sept. 2

VANGUARD LABS

Dept. H, 196-23 Jamaica Ave., Hollis, N.Y. 11423

LEGER LABORATORIES announces a new Teletype Repair Facility!

*Cleaning — alignment — repairs
— at realistic prices.*

We want to thank the hundreds that have written to us (from as far away as Hawaii) and let them know that we appreciate their patience. We are in the process of moving into our new facility and ask you to bear with us as we get settled in. We were sorry to miss those that looked for us at the 73 hamfest, but our move tied us down.

We repair, align, calibrate or check out any piece of equipment, commercial or amateur. Write us or call us for an estimate.

We also sell Rohn towers . . . AR speakers . . . Cushcraft antennas and have a wide variety of test equipment available for lease or sale. If you are in the vicinity you might stop in for a visit and see our new plant.

LEGER LABORATORIES

Groton Street, East Pepperell, Mass. 01437
Phone 617-433-6771

Care and Feeding of a Ham Club—III

Carole Allen W5NQQ
308 Karen Drive
Lafayette, La. 70501

How About A Party?

Who needs help with a party, you ask? Sure, anybody can have one, but it takes planning if everyone is going to have fun, be it a ball, banquet, or barbecue.

The social side of radio clubbing means anything from coffee and cake after the business session to a full scale affair at a ritzy restaurant. Most hams like food, and there's no doubt that a bubbling percolator and sack of doughnuts adds to any evening. But these magic ingredients just don't appear out of the air—a committee will have to see that they do.

If meetings are held in members' homes, kitchens are handy, and many public meeting places also have facilities; however, yours may be a club that has to buy a hot-plate or carry in goodies. Stag clubs are sometimes lucky enough to have Ladies' Auxiliaries who function with the purpose of planning refreshments for the fellows. A very satisfactory arrangement for many groups is taking turn-about at providing snacks. To prevent a last minute discovery that nobody is bringing the sugar bowl, it's a good idea to plan a social calendar in advance. If hosts and hostesses volunteer for meetings early in the year, a sheet can be printed and distributed showing who's going to serve and at what meeting.

In addition to regular get-togethers, most clubs sprinkle the year with picnics, barbecues, dances, card parties, and formal banquets. These events, and especially the last one, demand lots more work. Your choice of clambake will depend on your locale; for instance, the Pensacola (Florida) Amateur Radio Club gets a bang out of shrimp boils and fish fries, but a barbecue would probably be first choice in Southern California and a pot-luck buffet in Indiana.

Some wise soul once said that variety is the spice of life, and hams around the country prove it. The secret is not to be afraid



Hams like to laugh, and a party program is more successful with a few jokes. Bill, K9AKF, receives a mobile antenna complete with oil can and other awards from Program Chairman K9AMD.

to try anything once; if the card party is a flop, you won't repeat it; likewise, the party plan you had doubts about may really make a hit with the gang.

Since all types of shin-digs require similar ground-work, let's see how one comparatively small group plans a whale of an annual spring whing-ding. The sponsoring club consists of about thirty active members and twenty not so active. Regular meetings are held monthly with both OMs and XYLs attending. Every April, members and their families hold a "Ham Scramble" at a com-

munity center where there is plenty of room and also kitchen facilities. Although the event is not designed on hamfest proportions, area hams are invited.

The Ham Scramble is held on Sunday and kicks off about 3 p.m. The afternoon is spent ragchewing and working on contests and paper games planned by special committees. QSL cards are displayed as well as surplus gear hauled in for swapping. Everybody mills around contentedly talking and "contesting" while the ladies prepare food and set tables. Each family brings its own table service and covered dishes for "scrambling." Coffee for hams and milk for harmonics is furnished.

"Chow time" is called about 5:30, and no one has to tell a ham what the word "smorgasbord" means. A program following the meal begins with group singing and continues on the same informal note including the awarding of both serious and humorous prizes. This is a good time to award 100% attendance plaques or pins to deserving members as well as a "booby-type" prize to a ham who can take a joke. Ideas that have audiences rolling in the aisles include presenting a can of cleanser to someone who needs to clean up TVI, a megaphone for the fellow who has transmitter trouble or says he can't "get out," an ax or hatchet to cut QRM, a make-shift trophy for a new General Class operator, and other rib-tickling awards for hams who enjoy a good laugh.

The main event of the evening is planned to interest unlicensed wives and children also. An after-dinner speaker with stories for the kids, a colorful travelogue or entertaining film hits the spot with many groups.



If the winter-weather has been rough on the club's generator, a committee will need to step in and get it going before Field Day. Shown left to right: Al, K9OHJ; Burrell, K9JBZ; Dan, W9VEY; Dick, W9VWJ; and winding is Boyd, K9JFF.



A small club holding an annual "Ham Scramble" features contests for YLes and XYLs as well as the jellows. Trying to guess how many red-hot candies and buttons are in the jars are two "contesters." Watching are the chairman of the ladies game committee—(Right—Janean, W9BYQ; and second from right—Mary, K9WUA.)

One year an amateur magician kept everyone on the edges of their chairs.

After door prizes and awards for contest winners have been given, the party breaks up early enough that families will be home before the little people get too tired.

If a "Ham Scramble" appeals to your club, you'll be interested in the following list of committee chairmen who work together:

- General Chairman and/or Co-Chairman
- Registration
- Publicity
- Program
- Dining Room and Decorations
- Entertainment for Children
- Contests
- Exhibits
- Prizes
- Food
- Kitchen and General Clean-Up

Some of these chairmen will also be needed if your club reserves a local restaurant once or twice a year for a banquet. A Reservations Chairman can handle ticket sales and deal with the Maitre D. Since parents usually hire babysitters for a banquet evening, the group will probably be adults and a dance or other entertainment can be planned to last into the late hours.

If you think you've got to have a reason for a party, don't overlook the Fourth of July, Halloween, Christmas, Valentine's Day and all of the wonderful holidays which offer lots of decoration and theme possibilities. A party during December will liven up the winter months when transmitter hunts



An annual dinner or party is a good chance to award amusing prizes or special honors for 100 per cent attendance during the year. The award recipients should, of course, know how to take a joke.

and outdoor activities are at a minimum. A family Christmas gathering may include a gift exchange set up with fun in mind. Hams can wrap radio components and keep them separated from toys brought by children for one another. Wives and girl friends should bring feminine type presents and put them in still another stack. With expenses at an all-year high at Christmas, perhaps a limit of \$1.00 or less can be set on the exchange.

College campus clubs have problems of their own in party-planning such as time, location, money, and fresh ideas. The Michigan Tech Club of Houghton, Michigan, has a real gripe with 2200 fellows on campus, only 39 girls, and not a licensed YL among 'em. Unless the boys can find some girls for dances, record parties, or jazz fests, it looks like they'll have to be satisfied with something less. But an energetic gang of male hams should be able to organize some terrific transmitter hunts or spur-of-the-moment camping trips with portable gear. And if things get too gruesome, see what hams are doing in neighboring towns and pay up a school-term membership.

Admittedly, parties of all kinds require enthusiastic leadership, and when it spreads to the membership, any lack-of-interest problem will soon disappear. Chances are you'll find that your regular meetings as well as social gatherings will be lots more lively.

In the Good Old Summertime!

Shakespeare wrote about rare days in June, and hams talk about two in particular from one year to the next. The words "Field Day" mean alot of things to alot of people: Hams themselves regard this special week-

end as not only a perfectly legitimate reason to skip lawn mowing and house-painting but a chance to see how emergency power and portable rigs work out under less than ideal conditions. A non-radio minded wife may look at Field Day as a pretty poor excuse for the OM to escape visiting her relatives; and Joe Brown, the dedicated television watcher on the other side of town, may sound off about "that bunch of clowns who stay up all night running the noisiest generator they can find!"

But aside from these different views, Field Day is, of course, the June weekend when hams answer the "call-of-the-wild" and set up stations in gullies and hills everywhere.

Field Day is for fun and also to test what your club can do when the chips are down. How quickly can a portable station be set up? Are the generators capable of carrying the load? Can operators endure wind, weather, and long hours behind the mike? All these questions should have some kind of answer when time runs out on Field Day and everyone collapses in a heap.

Your club may feel that lack of preparation adds to the reality of the Field Day operation, but, let's face it, if somebody doesn't do some "getting ready," it may be a lost weekend. For instance, if the commutator of the generator has developed a case of dirt and grime, it will take some pre-Field Day cleaning; and who can claim that an efficient antenna system can be set-up, tested, and put on the air in only a couple hours.

In other words, it's the old "Be Prepared" motto again. Committees appointed in the spring can have Field Day equipment



Club parties will depend on the locale. For instance, the Midwest group shown above really go for spring and fall wienie roasts: Left to right: Rosi, K9ESY; Naoma, K9MSY; Jane, mother of K9RHL; Carole, K9AMD, and Claire, K9TST.



The Fixed Station Committee will supervise the assembling of complete Field Day stations and that may mean a lot of elbow grease. Left—Dan, W9EZA, and Dick, W9VWJ, move a rig into place.

ship-shape before the end of June. That doesn't mean that operators aren't going to be tested on how well they perform over a long haul or that the equipment itself isn't going to face a work-out; it just means that drastic repairs and replacements won't have to be made when the beginning Count-Down is on.

The extent to which your club goes "all-out" will determine what committees will need to pitch in. If you're planning a caravan to a weedy lot, you'll want someone with a mower to visit it first, and maybe one of the members who like to camp out can move in with a large tent and facilities.

Big clubs with lots of mobile stations, portable rigs, generators and lots of operators can and do work out elaborate plans using everything and everybody available. But, big or small, clubs depend on committees and here's a list to stimulate your thinking:

- General Field Day Chairman and/or Co-Chairman
- Antenna Systems
- Portable power plans (Preparation and Fuel)
- Fixed Stations
- Mobile Stations
- Operators (The Personnel Man)

Rig Repairs The Big Count-Up.

Although several of the above titles speak for themselves, let's elaborate on a couple. The Fixed Station Committee will direct the assembling of complete stations on the various bands and also coordinate a pattern of operation. If, for instance, the gang on 40 meters in the pup-tent decides to switch bands, they should know that the fellows in the tent next door are working on 20 phone and don't care for local QRM in addition to what's on the band. Tempers will stay cool if everyone knows who's operating where.

The Mobile Chairman's job is to know whose car will be available and at what times. Since most drivers have only two hands, a log keeper with sharp pencils should be sent with each car.

The Operators' Chairman will serve as the Personnel Man to compile a list of available members. First, who wants to do the actual operating? Do they prefer phone or key? What class licenses do these folks have? It isn't too good to assign a novice to run a kilowatt rig on 14.250. Not only names but times are vital statistics, for you've got to remember that Field Day is a 24 hour affair. Let the fellows and gals pick their own hours, and by looking over the list you'll be able to separate the night owls from the early birds. Next, prepare a 24 hour schedule using every licensed ham to the best advantage and assigning non-licensed enthusiasts to log-keeping posts. Better have some alternates in case of emergencies.

Most clubs have at least one ham who'd rather work on equipment than operate it, and he can save the day (or night) if he's around when a rig goes sour. If stand-by stations can be thrown into use while repairs are being made, all the better; if not, just hope your man Friday will make himself available during the whole weekend.

Hot, cold, or lukewarm coffee is a "must" for Field Day; and it's safe to say that some kind of a pot, percolator, or pan is on the fire at 99 per cent of Field Day locations from start to finish: OMEs are noted for their ability to make coffee in any kind of container but they'll admit that the XYLes do a good job, too. And they'll also note that it's pretty nice to have the wife and kids show up to see what "Daddy's been doing all weekend." If the ladies want to pitch



Bobbi, K9GOL, at the right pours hot coffee on Field Day night for a group of tired operators. The gals who keep the coffee flowing are popular around any operating site.

in and really make Field Day a family event, pot-luck meals and picnics can be planned. An extra popular gal is the one who fries eggs and bacon at 6 a.m. Sunday morning when eyes are red and beards are bushy. Keeping the coffee coming from dusk 'til dawn puts the ladies at the top of the Hams' Hit Parade.

When time runs out along with energy, a big chore remains—the tremendous task of log checking and scoring. If someone skilled in deciphering Egyptian hieroglyphics

doesn't volunteer, a committee will be needed to sort, count, correct, total, and cull out errors. After this gigantic job has been done, the lists are bundled up and sent to the American Radio Relay League, 38 La Salle Road, West Hartford, Connecticut. There's nothing left to do then but wait for the nationwide totals to be released in their magazine, *QST*, and try to think how next year's Field Day in the good old summertime can be made a little better.

Other Contests

Field Day is by no means the one and only contest that your club can enter. Many clubs make an entire career out of the VHF contests. Some specialize in the VHF Sweepstakes in February, while others prefer to shoot for the September VHF Test. They sometimes go to rather great lengths in pursuing these contests.

Up Boston way hardly a VHF contest goes by without the Waltham, King Philip, or Rhododendron Swamp VHF Societies mustering of top of Pack Monadnock in New Hampshire or Mt. Greylock in northern Massachusetts for a king sized go. These fellows set up, even in mid-winter, with enormous beams on every VHF band, high power, and usually win the contest. Any group that hauls a 128 element two meter beam to the top of a mountain and sets it up on a tower deserves to win.

The Philmont Club leans more toward the DX Contests and just about every member is on there, hot a heavy, building up the club score. They use two meter intercoms, and the works. This contest runs in February and March every year.


In November we have the Sweepstakes Contest, another popular club effort. In October many clubs participate in the World Wide DX Contest.

All of these contests are good club projects. The members can work to help each other have their stations set up and also cooperate during the contests for the maximum number of contacts.

More next month.

... W5NQQ

THE BEST 6 METER CONVERTER

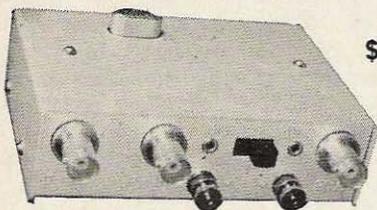

\$34.95
ppd.

50-52 MHz in. 28-30 MHz out
or 52-54 MHz with a second crystal.

A full description of this fantastic converter would fill this page, but you can take our word for it (or those of hundreds of satisfied users) that it's the best. The reason is simple—we use three RCA dual gate MOSFETs, one bipolar, and 3 diodes in the best circuit ever. Still not convinced? Then send for our free catalog and get the full description, plus photos and even the schematic.

Can't wait? Then send us a postal money order for \$34.95 and we'll rush the 407 out to you. NOTE: The Model 407 is also available in any frequency combination up to 450 MHz (some at higher prices) as listed in our catalog. New York City and State residents add local sales tax.

**Closed for Vacation
from Aug. 26 to Sept. 2**

VANGUARD LABS

Dept. H, 196-23 Jamaica Ave., Hollis, N.Y. 11423

**Please Use Your
Zip Code When
Writing 73**

2 Great New Ham Books!

VHF HAM RADIO HANDBOOK



By Edward G. MacKinnon
Amateur Radio Operators! Be the 1st in your area to make use of the many VHF-UHF techniques revealed in this new book.

Even if you've already taken steps to escape the crowded lower frequency bands, you'll find much helpful information and many exciting projects which will whet your appetite to go further. Explains the differences between VHF and lower frequency gear propagation phenomena, including tropospheric of the aurora, sporadic E-layer skip, and 6-meter moon-bounce communications; transmitting equipment for 6 and 2 meters, a 432-MHz tripler, and several modulators. Includes several antenna systems for 6 meters, including a cylindrical parabola and a base-loaded whip. For those who want to use existing equipment, detailed instructions show how to modify the HI Bander, Gonsel II, Heath-Seneca and Heath Sixor. — Equipment Modifications—includes are circuits for medium and low-power transmitters, receivers, preamps, filters, RF amplifiers, a field strength meter, noise generator, and oscillators for 50, 144, 220, 432, and 1296 MHz. Truly a book every ham will want to own. 176 pps., over 100 illus., Scores of construction projects.

CONTENTS: VHF Propagation—VHF Hints and Kinks—VHF Transmitters—VHF Antennas—Power Supply Considerations—Equipment Modifications—VFO Projects—Receiver and Modulator Circuits—Station Listings—Construction Projects.

Order No. 460, only \$3.95 paperbound or \$6.95 hardbound

IC PROJECT HANDBOOK



By Bob Brown & Tom Kneitel

This new book describes 50 different projects, all based on using popular IC's which are inexpensive and available at all parts stores. Some of the devices—such as the personal code practice oscillator and IC power supply—can be built in an evening. More sophisticated projects—like the 11 thru 6 meter receiver—offer a greater challenge. You can build practical devices like the 20-Meter DX Preamp, or the 50-watt amplifier, or some "just for fun" gadgets like the wireless mike or the memory tester. Regardless of your specific interests in electronics, you're sure to find a number of items you'll want to build. Other ham projects include a wide variety of transmitters, receivers, code keyers, mike preamps, etc. For CB's there is a signal booster, crystal calibrator, voice-controlled switch, etc. Technicians can make good use of such items as the IC tester, square-wave generator, and color TV convergence generator. This is the first book of its kind—anywhere—and the projects are among the most fascinating you've ever seen. 160 pages. 50 projects; 100 illus.

Order No. 464, only \$3.95 paperbound or \$6.95 hardbound

Order either or both of these new books at our risk for 10-days FREE examination. Simply fill in and mail NO-RISK coupon below for these helpful volumes.

PUBLISHER'S GUARANTEE: Put the information in these books to work for you for 10 days. If they don't prove to be worth several times their cost, return it and we'll cancel invoice.

NO RISK COUPON — MAIL TODAY

TAB BOOKS, Blue Ridge Summit, Pa. 17214

Please send me _____ copies of "VHF HAM RADIO HANDBOOK" paper hardbound. Also send me _____ copies of "IC PROJECT HANDBOOK" paper hardbound

Payment of _____ herewith (Postage Prepaid)

Please Invoice on 10-day FREE Trial.

Name _____

Address _____

City _____ State _____ Zip _____

Save postage by remitting with order 73-98

MORE JOHNSON VARIABLES

# 152-516	Dual 470 pf/sec. 4500v. 5 1/2" w, 5 3/4" h, 15" l + 1 1/2" for 3/4" shafts. (8 LBS.) NEW.....	4/\$31.00	\$8.50 ea.
# 160-110	2.7 to 19.6 pf, miniature. 3/16" slotted shaft	4/\$3.25	79c ea.

BEST SELLERS, VERY LUCKY FINDS. LIMITED SUPPLY

RF Switch.	2 deck, 5 position, 2 pole double break, 1 deck shorting, 1 deck non-shorting. 4" dia. 6" long + 1" for 3/4" shaft. 1 KW+. (5 LBS.) NEW..	4/\$9.50	\$2.50 ea.
85 KC IF	Late type HI-Q, ceramic form. For R11A. NEW..	4/\$4.75	\$1.25 ea.
85 KC IF	Older type, bakelite form, for BC-453. NEW	4/\$3.75	\$1.00 ea.

More METERS.

0-5v DC	0-1 DC MA, basic movement, with internal 5000 ohm resistor. Black background, white figures. All clear, wide view plastic. Scales—0-10 ma; 0-500 ma; output 0-10. American made, for KNIGHT T-150. NEW	4/\$10.00	\$2.75 ea.
100 Ua DC.	1" square, Level meter, Basic 100 ua DC. JAP. Clear plastic. NEW	4/\$5.50	\$1.50 ea.
1 ma DC	2800 ohm internal resistance, 2" edgewise. JAP.	5/\$9.75	\$2.00 ea.

Hamfest Schedule—Findlay, Ohio, Sept. 8; Peoria, Ill., Sept. 15; Cincinnati, Ohio, Sept. 22.

All orders, except in emergency, or I'm at a hamfest, shipped same day received. For free "GOODIE" sheet, send self-addressed, stamped envelope—PLEASE, PLEASE include sufficient for postage, any excess returned with order. I carry private (Travelers) parcel post insurance, for domestic parcel post. For items too heavy, or too large for parcel post, I suggest bus parcel express. Please advise name of bus line, and city where you can pick up the shipment. Canadian customers—PLEASE add sufficient for postage—\$1.00 first two pounds, 30c each additional pound or fraction.

B C Electronics

Telephone 312 CAUMet 5-2235
2333 S. Michigan Avenue Chicago, Illinois 60616

COMPUTER GRADE CAPS

4,000 mfd at 50 volt\$1.00 each, 12 for \$10.00
6,500 mfd at 18 volt\$1.00 each, 12 for \$10.00

60 WATT TRANSISTORS 80 VOLTS

From computer assemblies, board with 4 each power transistors 2N1137B, 60 watt, 80 volt PNP power\$1.25 per board

SUPER VALUE \$2.50

Computer boards with 8 each 2N1137B power transistors & mounting hardware, also include on the board, 4 each 10 volt zeners, 4 silicon diodes 1 amp 800 volt PIV, computer grade cap 2000 mfd 65 volt Bourns trimpots, precision resistors, etc. Complete assembly like newShip wgt. 3 lb. \$2.50

RF FILTER

From HAWK MISSILE termination contract. Good for 5 amps, 600 volt, 10 cycles to 500 mc, insertion loss 60 DB-plus, low pass pi-network type, excellent as feed-thru filter in converters, transmitters. Hermetically sealed inside are 2 toroidal chokes & 4 low induct. caps. #41102\$1.00 each, 6 for \$5.00

PISTON CAPS

Corning glass, direct traverse type, min. Q at max. C—500 at 50MC. 500 volt breakdown. Capacitance range 1-8 ufd. Brand new military surplus3 for \$1.00 or \$3.00 per dozen

We have a catalog . . . if you send 25c for it, you'll get it someday.

All material FOB Lynn, Mass.
Which means, send postage.

JOHN MESHNA, JR.

PO Box 62 E. Lynn Mass. 01904

IS THIS BRIBERY?



\$5 PARTS BIN

← **FREE**


With 1 New \$6 Subscription!

This three-tiered parts holder is just the thing for the workshop. The three shelves revolve to put parts right at your hand. Stop searching for things.

FREE →


With 2 New \$6 Subscriptions!

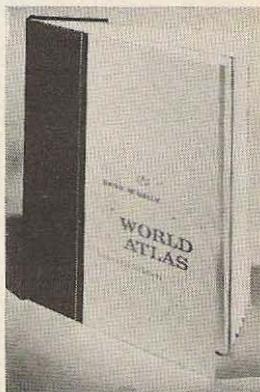The famous Rand-McNally Imperial world atlas. Over 300 pages, handsomely bound. For the ham shack, for the family, for the student. Maps, people, political information, historical gazetteer, facts. Makes working DX twice the fun.



\$13 WORLD ATLAS

HOW COME? We added up the cost of soliciting new subscribers through the mail: mailing lists, brochures (paper, artwork, typesetting, printing, folding, delivery), envelopes (plus printing and shipping) for the brochures, return envelopes, putting brochures together, addressing, bundling by zip, plus postage. Multiply that by ten to account for the one in ten response and add the return postage. We decided to put all that money into premiums and give them to readers that sell new subscriptions to their friends and fellow club members. It seemed worth a try.

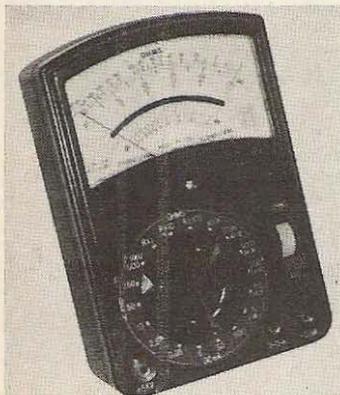

\$10 V-O-M

← **FREE**


With 3 New \$6 Subscriptions

20,000 ohms per volt V-O-M. Ohms: 1K, 10K, 100, 1M; Volts dc: 2.5, 10, 50, 250, 500, 5000; volts ac: 10, 50, 250, 500, 1000; dc mA: .05, .5, 5, 50, 500; db: 0, 14, 28, 34, 40. Invaluable around any hamshack or workshop.

FREE →

With 4 New \$6 Subscriptions!

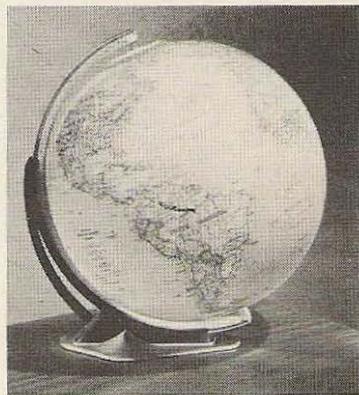Hammond 18" International World Globe. This not only makes DXing more fun, it is of value to the whole family. No child should grow up in a household without a good world globe. You can use charts if you like for swinging your beam, but a globe is better.



\$17 HAMMOND GLOBE

HERE'S THE DEAL. These premiums are for getting new subscribers for 73, not renewals. You, knowing 73 as you do, can sell it a lot better than one of our mailing pieces. You won't get lost in the daily deluge of mail solicitations and the credibility gap that they have wrought. You know what's good about 73 and what's bad. You know that you will be doing your friends a favor if you get them to subscribe because you will be making ham radio a lot more fun for them. Our hobby is much better when you keep up to date on technical and political developments. Send in the subscriptions with \$6 for each new one year sub, each on a separate 3 x 5 card with name, call, address and zip code, and add one card with your name and address and the prize you desire. Not bad for doing a few friends a favor! This offer is good in the USA and APO only. Offer expires Aug. 31, 1968. All subs will start with the October issue.

THEY WOULDN'T DARE!

PRIZES FOR SUBSCRIPTIONS


\$25 TEN-IN-ONE

MINILAB

FREE WITH 5

NEW \$6 SUBSCRIPTIONS

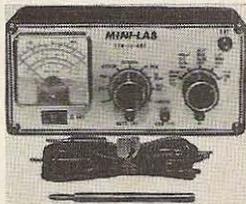Volts ac & dc: 15, 50, 150, 500; Ohms: 10K, 100K, 1M; mA: 500; resistance substitution: 100, 1K, 10K, 100K, 1M; Capacitance substitution: .002, .005, .02, .1, 10uF; RF field strength; 9V battery supply; RF signal generator at 455 kHz to 700 kHz; AF generator at 400 Hz. Comes with test leads, antenna and battery. Invaluable for mobile servicing or around the shack.



\$25 NEW BIG SWINGER

FREE WITH 7 NEW \$6 SUBSCRIPTIONS

The New Big Swinger Polaroid camera uses the regular black and white film packs, making the large 3 1/4 x 4 1/4" pictures. Drop flashbulb into camera. Built in photometer. No focusing two feet to infinity. Why miss out on Polaroid fun any longer?




\$12 BLANKET

FREE WITH 2

NEW \$6 SUBSCRIPTIONS

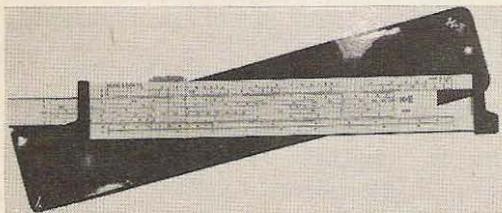
This 50" x 60" sport blanket comes from Spain and is made of virgin wool, cotton and rayon. Machine washable. Beautiful yellow red and black design. Comes in zipper vinyl case with handle. Fine for the car, picnics, etc.



\$3 K & E SLIDE RULE

FREE WITH 1 NEW \$6 SUBSCRIPTION!

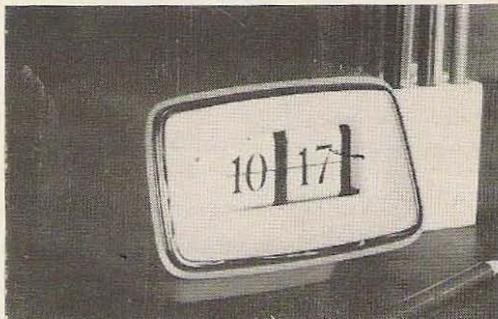A slide rule is indispensable around the ham shack or the office. This one has everything you need, but is inexpensive enough so you can get two or three. Has C, D, A, B, S, T, C1, L, and K scales. Comes complete with case. 10" long with indented green ruling.



24 HOUR OPERATING DESK CLOCK

FREE WITH 5 NEW \$6 SUBSCRIPTIONS!

This beautiful clock has numbers you can really see. Keep it right in front of the rig and set up with GMT time so you can keep the log correctly. The numbers go up to 24 hours. This desk clock normally sells for \$25.

These premiums are offered for groups of new subscriptions to 73. USA or APO only. Send each new subscribers name, call, address and zip on a separate 3 x 5 sheet of paper. Subscriptions take about six weeks to process. On a separate sheet give your name, call, address and zip and the premium you want. Please allow eight weeks for delivery just in case the demand is heavy and we have to wait for factory delivery. We'll try to make immediate delivery when possible. This offer expires July 31st and all subs must be post-marked before that date. Send \$5 for each new sub.

73 MAGAZINE

PETERBOROUGH, N.H. 03458

ELECTRONIC SYMBOLS

ANTENNA	
	NORMALLY USED IN BLOCK DIAGRAMS, BUT MAY BE USED IN ANY SCHEMATIC WHERE ANTENNA IS CONNECTED DIRECTLY TO CIRCUIT WITHOUT BENEFIT OF RF CONNECTOR

GROUND CONNECTIONS	
	
CHASSIS GROUND SYMBOL IS NORMALLY THE ONLY TYPE USED IN SCHEMATICS. EACH GROUNDED CIRCUIT COMPONENT WILL BE SHOWN CONNECTED TO AN INDIVIDUAL CHASSIS GROUND, UNLESS A COMMON GROUND BUS IS ESSENTIAL TO PROPER CIRCUIT OPERATION.	EARTH

BATTERY	
	
SINGLE CELL	MORE THAN ONE CELL
DO NOT FORGET TO INDICATE VOLTAGE AND POLARITY	

HEADSET	
	NORMALLY USED IN BLOCK DIAGRAMS, BUT MAY BE USED IN ANY SCHEMATIC WHERE CONNECTED DIRECTLY TO CIRCUIT WITHOUT PHONE PLUG. INDICATE IMPEDANCE IF VALUE IS CRITICAL.

CAPACITORS		
		
BASIC	* ELECTROLYTIC	VARIABLE
		
FEEDTHRU	SPLIT-STATOR	GANGED
		
DIFFERENTIAL	VACUUM	VAC. VAR.
NOTE THAT CURVED PORTION OF SYMBOL ALWAYS DESIGNATES OUTSIDE FOIL OF FIXED CAPACITORS (EXCEPT ELECTROLYTICS, WHERE IT INDICATES THE NEGATIVE TERMINAL). THE CURVED PORTION IN THE CASE OF A VARIABLE WILL INDICATE THE MOVABLE PART. * INDICATE POLARITY, AND VALUE IN μF . WHEN OTHER THAN ELECTROLYTIC VALUES ARE ASSUMED TO BE μF WHEN 1 OR GREATER, AND nF WHEN LESS THAN 1.		

INDUCTORS		
		
BASIC	TAPPED	ADJ. TAP
		
ADJ. SLUG *	FILTER CHOKE	RF CHOKE
INCLUDE ALL NECESSARY DATA INCLUDING ANY OF FOLLOWING INFORMATION WHICH IS APPLICABLE: WIRE SIZE & TYPE COIL OR FORM O.D. OR I.D. NUMBER OF TURNS AND/OR LENGTH MANUFACTURER'S PART NUMBER TAP POSITION ABOVE COLD END * FERRITE CORE WILL BE ASSUMED UNLESS BRASS IS SPECIFIED. INDICATE TYPE OF FERRITE, IF CRITICAL.		

CONDUCTORS		
		
BASIC	CONNECTED	CROSSED

KEYS	
	
STANDARD	* AUTOMATIC
* BE SURE TO DESIGNATE "DIT" & "DAH" CONTACTS	

CONNECTORS			
			
MALE AC LINE	FEMALE AC LINE	FIXED MULTIPLE *	MOVABLE MULTIPLE *
			
MALE TERMINALS	FEMALE TERMINALS	BASIC TERMINALS	PHONE PLUG
		SHOULD NONE OF THE SYMBOLS DESCRIBED HERE SEEM TO MATCH YOUR SITUATION, DESCRIBE THE CONNECTOR AND/OR LIST THE MANUFACTURER'S PART NUMBER. *FOR ANY COAXIAL-TYPE CONNECTOR, SUCH AS RF, MICROPHONE, PHONO, ETC. * NUMBER THE BLOCKS TO CORRESPOND TO TERMINAL MARKINGS, WHEN APPROPRIATE.	
PHONE JACK	COAXIAL *		

LAMPS	
	
INCANDESCENT	NEON
INDICATE MANUFACTURER'S PART NUMBER AND/OR VOLTAGE & CURRENT RATING	

LOUDSPEAKER	
	INDICATE VOICE COIL IMPEDANCE & POWER RATING, ETC., WHEN CRITICAL.

METERS	
	* INDICATE TYPE OF METER HERE (μA , mA , V , ETC.) * INDICATE SCALE RANGE HERE (0-1, 0-50, ETC.) DON'T FORGET TO INDICATE PROPER POLARITY.

MICROPHONE	
	NORMALLY USED IN BLOCK DIAGRAMS BUT MAY BE USED IN SCHEMATIC WHEN WIRED DIRECTLY INTO CIRCUIT WITHOUT CONNECTOR. INDICATE TYPE (CARBON, XTAL, ETC.)

MOTOR	
	LABEL AS MOTOR, FAN MOTOR, ETC. INDICATE OPERATING VOLTAGE & CURRENT AND/OR MANUFACTURER'S PART NUMBER.

CRYSTAL	
	ALWAYS INDICATE CRYSTAL FREQUENCY (IN kHz , MHz , ETC.)

RELAYS			
			
RELAY COIL	SPST CONTACT CONFIGURATIONS	DPST CONTACT CONFIGURATIONS	SPDT CONTACT CONFIGURATIONS
SPECIFY COIL VOLTAGE, RESISTANCE, ETC., AND/OR MANUFACTURER'S PART NUMBER. CONTACT CONFIGURATIONS SHOWN ARE BASIC AND MAY BE EXPANDED.			





ELECTRON TUBES			
			
DIODE	TRIODE	TETRODE	PENTODE
			
PENTAGRID	VOLTAGE REGULATOR	EXAMPLE OF MULTIPLE SECTION TUBE	
			
CATHODE RAY	PLATE	GRID	DEFLECTION PLATE
			
* HEATER (FILAMENT)	GAS FILLED	COLD CATHODE	
ALWAYS LABEL ELEMENTS WITH TUBE PIN NUMBERS. REFER TO TUBE MANUAL FOR DATA ON INDIVIDUAL TUBE TYPES. * FILAMENTS OR HEATERS (WITH THE EXCEPTION OF DIRECTLY-HEATED CATHODES) SHOULD BE SHOWN EXTERNAL TO TUBE CIRCLE, AND PREFERABLY IN THE POWER SUPPLY.			

RESISTORS			
			
FIXED	TAPPED	ADJUSTABLE	TEMP. COMP.
INDICATE VALUE IN OHMS (Ω), KILOHMS (K), OR MEGOHMS (M), AND/OR MANUFACTURER'S PART NUMBER. 1/2W 10% IS ASSUMED UNLESS OTHERWISE NOTED.			

SEMICONDUCTOR DIODES				
				
BASIC	ZENER	VARACTOR	SYMMETRICAL ZENER	P-I-N
				
TUNNEL	CONTROLLED			
INDICATE MANUFACTURER'S PART NUMBER AND/OR APPROPRIATE RATINGS. REFER TO MANUALS FOR SYMBOLS NOT SHOWN.				

FUSE	
	INDICATE CURRENT, VOLTAGE RATINGS, AND SLO-BLO, ETC., AS APPROPRIATE.

ELECTRONIC SYMBOLS

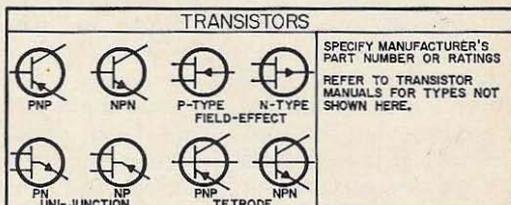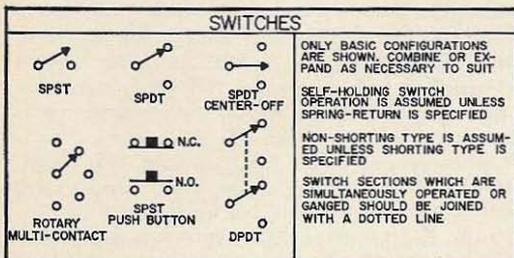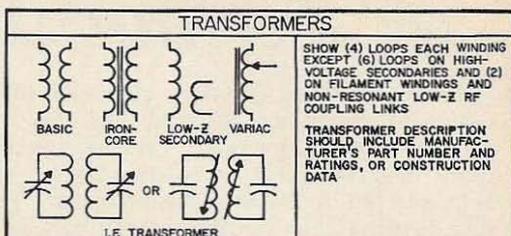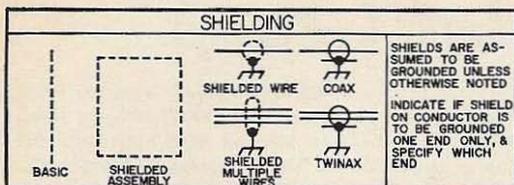

ELECTRONIC ABBREVIATIONS (AS USED ON DRAWINGS AND SCHEMATICS)

NOMENCLATURE	ABBREVIATION(S)
ALTERNATING CURRENT	AC
AMPERE	A
AMPLIFIER	AMP
AMPLITUDE MODULATION	AM
ANTENNA	ANT
AUDIO FREQUENCY	AF
AUTOMATIC FREQUENCY CONTROL	AFC
AUTOMATIC GAIN CONTROL	AGC
AUTOMATIC VOLUME CONTROL	AVC
BATTERY	B
BEAT FREQUENCY OSCILLATOR	BFO
BROADCAST	BC
CAPACITANCE, CAPACITOR	C
CONTINUOUS WAVE	CW
CRYSTAL	X, XTAL
CURRENT	I
DECIBEL	dB
DIODE, SEMICONDUCTOR (ALL TYPES)	D
DIRECT CURRENT	DC
DOUBLE COTTON COVERED	D.C.C.
DOUBLE POLE DOUBLE THROW	DPDT
DOUBLE POLE SINGLE THROW	DPST
DOUBLE SILK COVERED	D.S.C.
ELECTRON TUBE (ALL TYPES)	V
ENAMEL COVERED	ENAM
FILAMENT	FIL
FREQUENCY	FREQ, f
FREQUENCY MODULATION	FM
FUSE	F
GROUND	GND
HENRY	H
HERTZ (CYCLES PER SECOND)	Hz
IMPEDANCE	Z
INDUCTANCE, INDUCTOR	L
INSIDE DIAMETER	I.D.
INTERMEDIATE FREQUENCY	I.F.
JACK	J
KILOHERTZ (KILOCYCLES PER SECOND)	kHz
KILOHM	k, k.A.
KILOVOLT	kV
KILOWATT	kW
LAMP	I
LOUDSPEAKER	SPKR
MEGAHERTZ (MEGACYCLES PER SECOND)	MHz
MEGOHM	M, M.A.
METER	M
MICROAMPERE	μA
MICROFARAD	μF
MICROHENRY	μH

NOMENCLATURE	ABBREVIATION(S)
MICROPHONE	MIC
MICROVOLT	μV
MICROWATT	μW
MILLIAMPERE	mA
MILLIHENRY	mH
MILLIVOLT	mV
MILLIWATT	mW
NEGATIVE (POLARITY)	-, NEG
NORMALLY CLOSED	NC
NORMALLY OPEN	NO
OHM	Ω
OSCILLATOR	OSC
OUTSIDE DIAMETER	O.D.
PICOFARAD	pF
PLUS	P
POSITIVE (POLARITY)	+, POS
POWER AMPLIFIER	PA
PRIMARY	PRI
PUSHBUTTON	PB
RADIO FREQUENCY	RF
RADIO FREQUENCY CHOKE	RFC
RECEIVE	REC
RECEIVER	RCVR
RELAY	K
RESISTANCE, RESISTOR (ALL TYPES)	R
ROOT MEAN SQUARE	RMS
SECONDARY	SEC
SHORTWAVE	SW
SINGLE COTTON COVERED	S.C.C.
SINGLE POLE DOUBLE THROW	SPDT
SINGLE POLE SINGLE THROW	SPST
SINGLE SILK COVERED	S.S.C.
SWITCH	S
TIME	t
TRANSFORMER	XFMR, T
TRANSISTOR (ALL TYPES)	Q
TRANSMIT	XMIT
TRANSMITTER	XMITR
ULTRA HIGH FREQUENCY	UHF
VACUUM TUBE VOLTMETER	VTVM
VERY HIGH FREQUENCY	VHF
VOLT OHM METER	VOM
VOLT, VOLTS	V
VOLTAGE	E
WATT	W
WAVELENGTH	λ

Technical Aid Group

Please refer any questions of a technical nature to one of the following members of 73's Technical Aid Group. These are dedicated amateurs who really want to be of help and do so without compensation. Be sure to state your problem clearly and enclose a S.A.S.E. for a reply. I recently got a request from a reader asking me what to do about mobile noise. What kind of noise? He didn't specify any details. I gave him a general answer and made some suggestions, but it would have been helpful if he had described the kind of noise, under what circumstances it occurred, and what he had already done to try to eliminate the problem. Be specific about what you want. We are not mind readers.

John Allen, K1FWF, high school student, 51 Pine Plain Road, Wellesley, Mass. 02181. HF and VHF antennas, VHF transmitters and converters, AM, SSB, product data, and surplus.

Bert Littlehale, WA1FXS, 47 Cranston Drive, Groton, Conn. 06340. Novice transceivers, test equipment and homebrew projects gone wrong.

Bob Groh WA2CKY, BSEE, 123 Anthony Street, Rochester, New York 14619. Specializes in VHF/UHF solid-state power amplifiers, but will be glad to make comments on any subject.

G. H. Krauss, WA2GFP, BSEE, MSEE, 70-15 175 Street, Flushing, New York 11365. Will answer any questions, dc to microwave, state-of-the-art in all areas of communications circuit design, analysis and use. Offers help in TV, AM, SSB, novice transmitter and receivers, VHF antennas and converters, receivers, semiconductors, test equipment, digital techniques and product data.

Charles Marvin W8WEM, 3112 Lastmer Road, RFD #1, Rock Creek, Ohio 44084. Will help with any general amateur problems.

Stix Borok WB2PFY, high school student, 209-25 18 Avenue, Bayside, New York 11360. Novice help.

Clyde Washburn K2SZC, 1170 Genesee Street, Building 3, Rochester, New York 14611, TV, AM, SSB, receivers, VHF converters semiconductors, test, general, product data.

Richard Tashner WB2TCC, high school student, 163-34 21 Road, Whitestone, New York 11357. General.

J. J. Marold WB2TTZK, OI Division, USS Mansfield DD278, FPO San Francisco, California 96601. General.

Ira Kavalier, WA2ZIR, BSEE, 671 East 78 Street, Brooklyn, New York 11236. SSB transmitting, color TV, computer programming and systems, digital, radio and remote control, rf transmission lines, dipole design, audio amplifiers, linear and class C rf amplifiers.

Fred Moore, W3WZU, broadcast engineer, 4357 Buckfield Terrace, Treviso, Pa. 19047. Novice transmitters and receivers, HF and VHF antennas, VHF converters, receivers, AM, SSB, semiconductors, mobile test equipment, general, product data, pulse techniques, radio astronomy, bio-medical electronics.

Walter Simciak, W4HXP, BSEE, 1307 Baltimore Drive, Orlando, Florida 32810. AM, SSB, Novice transmitters and receivers, VHF converters, receivers, semiconductors, mobile, test-equipment, general.

James Venable K4YZE MS, LLB, LLM, 119 Yancey Drive, Marietta, Georgia. AM, SSB, novice gear, VHF, semiconductors, and test equipment.

J. Bradley K6HPR/4, BSEE, 3011 Fairmont Street, Falls Church, Virginia 22042 General.

Wayne Malone W4SRR BSEE, 8624 Sylvan Drive, Melbourne, Florida 32901. General.

Bruce Creighton WA5JVL, 8704 Belfast Street, New Orleans, Louisiana 70118. Novice help and general questions.

Douglas Jensen, W5OG/K4DAD, BA/BS, 706 Hwy 3 South, League City, Texas 77573. Digital techniques, digital and linear IC's and their applications.

Louis Frenzel W5TOM, BAS, 4822 Woodmont, Houston, Texas 77045. Electronic keyers, digital electronics, IC's commercial equipment and modifications, novice problems, filters and selectivity, audio.

George Daughters WB6AIG, BS, MS, 1613 Notre Dame Drive, Mountain View, California. Semiconductors, VHF converters, test equipment, general.

Glen H. Chapin, W6GBL, 3701 Trieste Drive, Carlsbad, Calif. 92008. HF and VHF antennas, novice transmitters and receivers, VHF converters, semiconductors, receivers AM, SSB, general, surplus.

Tom O'Hara W6ORG, 10253 East Nadine Temple City, California 91780. ATV, VHF converters, semiconductors, general questions.

Steve Diamond WB6UOV, college student, Post Office Box 1684, Oakland, California 94604. Repeaters and problems regarding legality of control methods. Also TV, novice transmitters and receivers, VHF antennas and converters, receivers, semiconductors, and product data.

Orris Grefsheim WA6UYD, 1427 West Park, Lodi, California 95240. TV, HF antennas, SSB, VHF antennas and converters receivers, semiconductors, and general questions.

Hugh Wells, W6WTU, BA, MA 1411 18th Street, Manhattan Beach, Calif. 90266. AM FM receivers, mobile test equipment, surplus, amateur repeaters, general.

Carl Miller WA6ZHT, 621 St. Francis Drive, Petaluma, Calif. 94952. Double sideband.

Howard Pyle W7OE, 3434—7th Avenue, S.E., Mercer Island, Washington 98040. Novice help.

PFC Grady Sexton Jr. RA11461755, WAIGTT/DL4, Hedmstedt Spt. Detachment, APO New York 09742. Help with current military gear, information from government Technical Manuals.

Sgt. Michael Hoff WA8TLX, Box 571, 6937th Comm. Gp., APO New York 09665. Help with all types of RTTY both commercial and military. Also data techniques. Covers conversion of military RTTY equipment.

Eduardo Noguera M. HK1NL, EE. RE, Post Office Box Aereo 774, Barranquilla, Columbia, South America, Antennas, transmission lines, past experience in tropical radio communications and maintenance, HF antennas, AM, transmitters and receivers, VHF antennas, test equipment and general amateur problems. Can answer questions in Spanish or English.

D. E. Hausman, VE3BUE, 54 Walter Street, Kitchener, Ontario, Canada. Would like primarily to help Canadians get their licenses. Would be able to help with Novice transmitters and receivers.

Frank M. Dick WA9JWL, 409 Chester St., Anderson, Indiana 46012. Will answer queries on RTTY, HF antennas, VHF antennas, VHF converters, semiconductors, mobile, general, and microwave.

Gary De Palma, WA2GCY/9, P.O. Box 1205, Evanston, Ill., 60204. Help with AM, Novice transmitters and receivers, VHF converters, semiconductors, test equipment, digital techniques and all general ham questions.

Arthur J. Prutzman K3DTL, 31 Maplewood, Dallas, Pennsylvania 18612. All phases of ham radio. Can assist with procurement of parts, diagrams, etc.

William G. Welsh W6DDB, 2814 Empire Ave., Burbank, Calif. 91504. Club licensing classes and Novice problems.

Ralph J. Irace, Jr., WA1GEK, 4 Fox Ridge Lane, Avon, Conn. 06001. Help with Novice transmitters and receivers and novice theory.

Iota Tau Kappa Radio Fraternity W7YG, Multnomah College, 1022 S.W. Salmon St., Portland, Oregon 97205. This group of radio amateurs will answer any technical questions in the field of electronics.

Ted Cohen W4UMF, BS, MS, PhD. 6631 Wakefield Drive, Apt. 708, Alexandria, Va. 22307. Amateur TV, both conventional and slow scan.

Roger Taylor K9ALD, BSEE, 2811 West Williams, Champaign, Illinois 61820. Antennas, transistors, general.

Michael Burns Jr. K9KOI, 700 East Virginia Avenue, Peoria, Illinois 61603. AM, SSB, receivers, transmitters, digital techniques, novice help, general.

Jim Jindrick WA9QYC, 801 Florence Avenue, Racine, Wisconsin 53402. Novice transmitters and receivers, general.

John Perhay WAØDGW/WAØRVE, RR #4 Owatonna, Minnesota 55060. AM, SSB, novice transmitters and receivers, HF receivers, VHF converters, semiconductors, mobile, product data, general. Has access to full specifications on almost all standard components presently catalogued by American manufacturers.

Ronald King K8OEY, Box 227, APO New York, New York 09240. AM, SSB, novice transmitters and receivers, HF receivers, RTTY, TV, test equipment, general.

Charlie Marnin W8WEM, 3112 Latimer Road, RFD 1, Rock Creek, Ohio 44084. General technical questions.

Michael Winter DJ4GA/W8, MSEE, 718 Plum Street, Miamisburg, Ohio 45342. HF antennas, AM, SSB, novice gear, semiconductors.

David D. Felt, WAØEYE, television engineer, 4406 Center Street, Omaha, Nebraska 68105. Integrated circuits, transistors. SCR's, audio and rf amplifiers, test equipment, television, AM, SSB, digital techniques, product data, surplus, general.

Tom Goetz KØGFM, Hq Co USAMAC, Avionics Division, APO New York, New York 09028. HF antennas, mobile, airborne communications equipment, particularly Collins and Bendix gear, AM, FM, or SSB—HF, VHF, UHF, general.


Robert Scott, 3147 East Road, Grand Junction, Colorado 81501. Basic electronics, measurements.

Does Math scare you?
"Simplified Math for the Ham Shack"
One of 73's books will make it easy.
Order today, only 50c.

BEAM HEADINGS

computed to every call sign area in the world

- Great circle bearing to over 500 locations.
- Distance in miles or kilometers (advise which).
- Return bearings — advise your QSO's of their best beam setting for working you.
- Callsign prefix & time difference for each location.
- On 8 x 11 computer paper mountable in plastic.
- Surface postage paid. Airmail include cost 3 oz.
- If latitude & longitude not given, describe QTH fully and add \$.50 for location service.

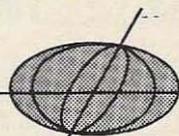

- Send \$3.95 with your name and exact location to:

**MONTGOMERY
GEODETIC
SERVICES**

Box 5707
Bethesda, Md. 20014

**POLICE • FIRE • MARINE
AIRCRAFT • AMATEUR CALLS**

X LINE TUNAVERTERS

**CRYSTAL & TUNABLE = VERSATILITY
USABILITY**



Tunable plus Crystal controlled (selectable with switch) solid state converters to change your auto and home radios into excellent, sensitive, selective, calibrated VHF receivers!

**THE BEST—CALIBRATED —T TUNING—
PLUS —DRIFT FREE CRYSTAL CONTROL—
—COMPLETE INTERCHANGEABLE
CRYSTALS WITHIN BAND!!!**

- 9 volt battery powered.
- Includes coax, mount & screws.
- New FET transistor oscillator & circuit.
- 1 year guarantee on parts & labor.
- Size—2½ x 3½ x 4¼ inches.
- American Made with American Parts.

BAND	MODEL	Tunable & Crystal! COVERS	OUTPUT	PRICE
CB & 10 M	273 X	26.9-30 mc	1500 kc	
6 meters	504 X	50-54 mc	1500 kc	
2 meters	1450 X	144-148 mc	1500 kc	\$32.95 ppd.
Police, fire, } Marine } Aircraft }	348 X 1564 X 1828 X	33-48 mc 150-164 mc 118-128 mc	1500 kc 1500 kc 1500 kc	Each Less Crystal
Models for AM & FM		Tunable only		
Marine	Marine	2.0-2.35 mc	550 kc	\$19.95 ppd.
SW & WWV	SWL	9.5-16 mc	1500 kc	\$19.95 ppd.

Coupling Loop & Ext. Antenna for use with home and Transistor Radios\$3.95 ppd.
Mobile Battery Eliminator, 12V to 9V\$4.95 ppd.
Crystals—State Exact Listening Freq.\$5.10 ppd.

Order from: **Fast AIR MAIL add \$.85 ea.**

HERBERT SALCH & CO. Marketing Division of
Woodsboro 79, Texas 78393 *Tompkins Radio Products*

LIGHTS! ACTION! CAMERA!



SMILE . . . You're on TV

Just think! Televising your family and relatives on the living room TV set with **YOUR OWN TV CAMERA.** Interested?? No matter whether you're considering a camera built primarily from junkbox parts or from a complete kit, **ATV RESEARCH** has just what you need. Over 8 different tube and transistor models to select from. **STARTER KITS \$18.95 up . . . MAJOR COMPONENTS KITS \$58.25 up . . . COMPLETE KITS (transistorized & printed circuit) \$149.50 up.**

Get started in this **FASCINATING HOBBY** today by writing for a copy of our **NEW 1968** catalog. It contains a comprehensive listing of kits, lenses, vidicon tubes, tripods, focus/deflection coils (both regular and slow scan); plus plans, automatic light kits, charts, etc. Please include 10% to cover cost of mailing.

Established dealer inquires invited.

P.O. BOX 453-S **ATV RESEARCH** Dakota City, Nebr. 68731

local and state police. Talk with your local newspaper and radio or television station. Put the word out through the CB group. It is a good idea to canvas all other users of mobile radio in your area too so that if anything is reported by any of them the word will be passed along immediately to you. This could be any doctors with mobile radio, power company trucks, road crews, delivery trucks, taxis, the telephone company, etc.

Our net is tied in with NICAP, the most energetic organization in the country investigating the UFO reports. Net members and net controls will be expected to get in touch with their local NICAP investigating groups so they can coordinate with our net. Your local NICAP man may have an interesting UFO slide show that can be put on for your club. You might drop a line to NICAP, 1536 Connecticut Ave., Washington DC 20036. Membership is \$5 and well worth while.

Even without any on the air alerts, the mere establishing of our net will provide both a useful service for any types of emergencies and a medium for excellent public relations for amateur radio . . . which we can definitely use. Try and get your local paper to do an article about your participation in the net. Perhaps you can get interviewed on the radio station. Talk about amateur radio.

NICAP reports that sightings have been way down for the last few months. Perhaps the UFO people are boycotting us in protest over the University debacle? Or are they worried over our UFO reporting net? Come on out, UFO's, let's see you! I do hope I am sitting by with a tape recorder when the net gets its first UFO report. That will be a historic bit of pandemonium to have on tape. I keep one of those little cassette recorders by the rig now at all times . . . never know when something interesting might happen.

I would particularly like to thank Chuck, W5GDQ (Dallas) for his net control work with the UFO net, right from the beginning. Chuck has only missed one net control so far, and that was when he was out of town.

Auto-Call Wanted

As our net grows more and more operators will be wanting to be able to be alerted whenever something is reported anywhere in the country. Few of us are going to just leave the receiver tuned into the frequency waiting for that call. What we need is a fairly fool-proof calling system. I should think that some sort of tone system . . . or perhaps

two tones might work. There are some fairly sophisticated filters available these days. We are open for articles along this line.

Slow Scan Television

The FCC apparently has finally come through with the slow scan tv permission. We'll have the exact frequency allocations by and by. This rule change has been hanging fire for about seven years now. Opponents to the proposal grumble that the slow scan signals are horribly wide and make a mess in the phone bands. Proponents point out all the things we can do with slow scan. We shall see more of both sides.

We have a couple of slow scan articles in the works here and will publish them as soon as we can. We are interested in more. Andre of Vanguard Labs has an idea that you might like to play around with . . . he is working on a system that will use a regular tv camera and monitor. Then you would record the signal on a drum and slow down the drum for radio transmission. The signals would record on another drum at the other end and this would speed up and the picture could be seen on the monitor. Instead of using a slow phosphor viewing tube you would just repeat the same picture over and over.


At any rate, slow scan is here so let's see what we can do with it. Let's try to cause as little QRM with the signals as we can and see what kind of interesting systems we can work out. It wasn't very many years ago that there were a lot of laughs when I proposed a WAS certificate for RTTY. Now it is time for one for television!

Your Advanced Class License

Our series on the Advanced License Study Course is winding up this fall. If you've followed the series you should have no trouble at all in getting your ticket and keeping most of your allocations. We will continue on with a study guide for the Extra Class and, I suspect, eventually go back and provide you with a course for the General Ticket.

Many of our readers write to tell us that the course is being used with great effectiveness by their clubs, with an hour or so devoted to questions and answers at the beginning of each club meeting based upon the current text. When the series is done we will bring the whole thing out in a separate book which can be kept at hand for future club courses. . . . Wayne

radio amateur callbook

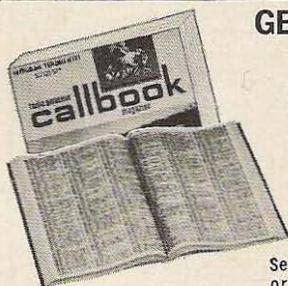

GET YOUR NEW ISSUE NOW!

Over 283,000 QTHs
in the U.S. edition
\$6.95

Over 135,000 QTHs
in the DX edition
\$4.95

See your favorite dealer or order direct (add 25¢ for mailing in U.S., Possessions & Canada. Elsewhere add 50¢).

These valuable EXTRA features included in both editions!

- QSL Managers Around the World!
- Census of Radio Amateurs throughout the world!
- Radio Amateurs' License Class!
- World Prefix Map!
- International Radio Amateur Prefixes
- Radio Amateurs' Prefixes by Countries!
- A.R.R.L. Phonetic Alphabet!
- Where To Buy!
- Great Circle Bearings!
- International Postal Information!
- Plus much more!

WRITE FOR
FREE
BROCHURE!

RADIO AMATEUR
callbook INC.
Dept. B, 4844 W. Fullerton Ave.
Chicago, Ill. 60639

Reader comments on the DX Hand- book . . .

- "Extraordinarily complete" . . . W3BNW
- "The wall map is fabulous" . . . K5MVF
- "Absolutely delighted" . . . W1MRS
- "I use it every day . . . invaluable" . . . W9CEL
- "Particularly appreciate the 80M info" . . . W9YBD
- "Must reading for every DXer" . . . W2API

Order your copy now. \$3 from 73,
Peterborough, NH 03458

NOISE BLANKER



Removes interference generated by auto ignitions, appliances, radars, and other sources of high energy pulse noise. Specifically designed for VHF operators requiring maximum noise suppression for reception of weak DX and scatter signals. Connects in the coax between converter and receiver. All solid-state design features silicon

Field Effect Transistors for reliability and best cross-modulation characteristics. Specify converter output frequency. Choice of 12-18, 100-140, 125-170 VDC; phono or BNC connectors. SWAN 250. Add noise blanking capability to this popular transceiver with the WESTCOM TNB-250 Noise Blinder. Mounts on rear of cabinet without drilling; easy to install. Price: \$29.95 postpaid. Calif. residents add sales tax. All products are warranted for one year and offered on a satisfaction or return basis.

WESTCOM ENGINEERING COMPANY

P.O. Box 1504

San Diego, Cal. 92112

GET IT from GOODHEART!

EVERYTHING UNCONDITIONALLY GUARANTEED

SILIC. RECTIF. 8000 PIV 400 MA. Large user's termin. invent., not rejects! Slater SLA88-2. Max: reverse, 2 uA; fwd drop, 8.2 v. Cost \$8 ea. PAIR Postpaid **\$5.30**

ELDICO SSB Adapter SBA-1 with book, converts any receiver with 455 kc IP to SSB; select either upper or lower side band; also adds CW oscillator if you have none. Many features and a very expensive unit in neat cabinet **\$127.50**

R-23/ARC-5 Command revr 190-550 kc. Shpg. wt. 9# 14.95

A.R.C. 12 #22 Command revr 540-1600 kc. 9# 17.95

LM-14 freq. meter, .01% 125 kc-20 mc, 15# 57.50

TS-323/UR freq. meter 20-480 mc. .001% 169.50

BC-221's OK \$57.50 TS-175 OK 125.00

CLOSING OUT Radio Receivers 38-4000 mc at **CRAZY LOW PRICES!** Ask for APR-4Y/CV-253 sheet.

SP-600-JL Revr. 0.54-54 mc, aligned, grtd. 250.00

R-392/URR grtd OK, w/AC sply & book 525.00

WANTED: GOOD LAB TEST EQPMT & MIL COMMUNIC.

TIME PAY PLAN: Any purchase totaling

\$160.00 or more, down payment only **10%**

WE PROBABLY HAVE THE BEST INVENTORY OF GOOD LAB TEST EQUIPMENT IN THE COUNTRY. BUT PLEASE DO NOT ASK FOR CATALOG! ASK FOR SPECIFIC ITEMS OR KINDS OF ITEMS YOU NEED! WE ALSO BUY! WHAT DO YOU HAVE?

R. E. GOODHEART CO. INC.

Box 1220-GC, Beverly Hills, Calif. 90213

Phones: Area 213, office 272-5707, messages 275-5342

**PLEASE INCLUDE YOUR ZIP CODE
WHEN YOU WRITE 73.**

\$\$\$ More Dollars \$\$\$ FOR YOUR EQUIPMENT

We at Bel-Air pay more. Specializing in police and marine monitoring and transmitting equipment. All HF, FM, business units. Also ham gear and tower equipment. Below wholesale prices on many items with new factory warranties.

Terms available

Write, phone—We pay freight on all purchases

**The Big One
Bel-Air Electronics**

5403 Grand Ave.
Omaha, Nebr. 68104
402 451-6477

WTW Report

Since the last report, conventions and hamfests have caused QRM and we missed the last issue of the magazine. We now have a good system lined up, so my service to all of you will be speedier and more efficient. Remember . . . send all reports directly to me. Don't send anything to 73 Magazine. I have all the certificates here and am sending them directly.

We still need a good club in W/K1, W/K2, and W/KØ, as well as Africa for WTW card check points.

There seems to be some confusion about phone certificates. SSB and AM are both phone, and count toward the award for either mode.

Regarding Don Miller's cards . . . we are only accepting the ones that ARRL accepts toward DXCC, thus no one can say we make our rules as we go along. We accept as a country any spot recognized by any national radio society. If ARRL accepts, we do too. If RSGB accepts it we do too. Send 25¢ to get a copy of the country list/tally sheet. This will relieve any doubts you might have.

There are strong rumors that a number of fellows are getting close to WTW-300 on 20 now. I wonder who will be first to qualify? Check your cards very carefully as we look them over with a critical eye and will disqualify any which show they have been tampered with.

To make the task of anyone checking your cards for the awards easier, I strongly suggest, when possible, to have all QSO information on one side of the card, along with your call sign in fairly large letters. Next time you have QSLs printed, how about keeping this in mind? The business of flipping cards over and over when checking them can become a chore and requires twice the time.

Remember, to qualify for WTW, all contacts must have taken place after May 1, 1966.

The following stations have qualified for WTW since the last listing:
WTW-200, 14 MHz Phone:

Certificate #11, K8YBU
12, PY3BXW
13, W6MEM

WTW-100, 14 MHz Phone:

- 54, K5TGJ
- 55, K4VKW
- 56, SVØWL

WTW-100 21 MHz Phone:

- 13, W6MEM
- 14, K4VKW
- 15, WA1EUV

WTW-100, 21 MHz CW:

- 5, WØRRS

WTW-100, 14 MHz CW:

- 15, K4CEB

21 MHz Phone still has only W4OPM with #1, and 28 MHz both Phone and CW still await someone to pick up #1.

As soon as enough scores are received, I will start a running list of the number of countries various fellows have worked.

... W4BPD

Tell Our Advertisers

You Saw It In 73

USED MODEL 501 TV CAMERAS



MADE IN U.S.A.

\$160.00 FOB Hollis

Each month we have a limited number of used TV cameras which we make available to hams at greatly reduced prices. These cameras were rented out for temporary surveillance jobs on construction sites, county fairs, conventions, etc. All have been checked out and are guaranteed for 90 days. Complete with vidicon and lens.

Used Model 501 sale priced \$160.00 FOB Hollis

Don't delay. Only a few used cameras are available each month. For specifications send for our illustrated catalog.

VANGUARD LABS

Dept. H, 196-23 Jamaica Ave., Hollis, N.Y. 11423

A NOTICE OF HIGH IMPORT

While we have had to reluctantly inch our subscription rates up just a hair, we have managed a real coup for you, the dedicated reader! We have nailed down, for the time being, our three year subscription rate. Take advantage of this obvious oversight. Sock it to us. Gold is up, silver is up, the pound is down. . . . we warned you. This is a good deal. We shall say no more.

Name Call

Address

City State Zip

New subscription — renewal — extension? —



\$12 THREE YEARS!


One year \$6

HAM RTTY \$3

DX Handbook \$3

VHF Antennas \$3

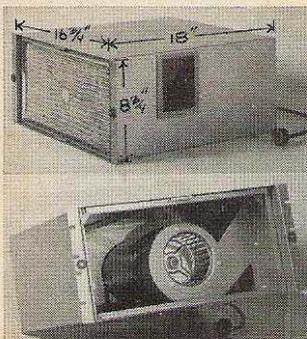While you are at it you might as well order some of our nice books listed above. Also it wouldn't hurt to get a \$3 binder or two. *And remember*, 73 now costs a lousy \$26.28 for three years on the newsstand. Appalling.



BLOWERS

standard 19" rack cabinet size; 110v 60 cyc General Electric 1/2 HP 3750 RPM motor with 5" squirrel cage blower. Mfg. McLean Engineering Lab. with dust filter, 55 lb. shipping wt. **MOTOR ALONE WORTH MUCH MORE THAN THIS PRICE**

NEW \$17.95

COMPUTER GRADE ELECTROLYTICS

40,006 MFD	10 VDC	5,000 MFD	36 VDC
20,000	25	3,500	75
16,000	12	2,500	80
10,000	15	1,500	100
8,000	55		

(If out of stock we will send next highest value)

CHOICE \$1.35 each 10/\$12.25

INTEGRATED CIRCUITS



UL 914 open gate Fairchild with 30 different projects to use this I.C. in. **NEW** from manufacturer \$1.00 ea.

3 DIGIT COUNTERS type used in tape recorders 50c ea., 10/\$4.50

TELETYPE PAPER ROLLS 8 1/2" wide 75c ea., 12 rolls \$7.50

TELETYPE PAPER TAPE 11/16" wide 25c ea., case of 40/\$7.50



CRYSTAL OSCILLATOR KITS USING I.C. UL 914

Stable, Harmonic-rich output crystal osc. range 100 KC to 10 MC—Kit includes Fairchild I.C. UL 914, crystal sockets, resistors, capacitor, & PRINTED CIRCUIT BOARD, with instructions for assembly \$2.00 per kit

12V 5 AMP filament transformer with over load fuse. **NEW** \$3.00 ea.


1000 PIV—1 AMP DIODES 40c ca. 10/\$3.75

IBM Regulated Transistor Power Supplies—heavily filtered and regulated. Extremely low ripple—with plug-in regulator card—with schematics

12 V Output at 20 amp	40 lbs	\$29.95
12 V Output at 16 amp	35 lbs.	\$24.95
12 V Output at 12 amp	30 lbs.	\$19.95
12 V Output at 4 amp	15 lbs.	\$14.95
12 V Output at 2 amp	10 lbs.	\$ 9.95

(ship. wt.)

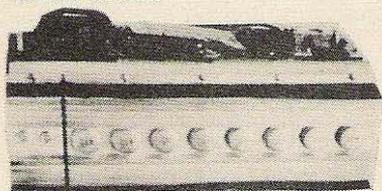Circuit breakers for both AC input and DC output. Voltage variable from 11 to 13 volts with pot. 115 VAC 60 cyc input. Excellent condition.



**Visit our 2nd Store Opening Sept. 1st.
247 So. Meridian, Indianapolis, Ind.
638-7213**



R & R ELECTRONICS
1953 S. YELLOWSPRINGS ST.
SPRINGFIELD, OHIO
Dept. 7F

\$2.00 minimum order FOB Springfield, Ohio COD order 25% deposit. Please add sufficient postage, we refund all unused amount. Ohio customers add 4% sales tax.

**SATISFACTION GUARANTEED
ON ALL ITEMS**


CROSSWORD

by

Michael Kresila

Box 57

Marion, Ohio 43302

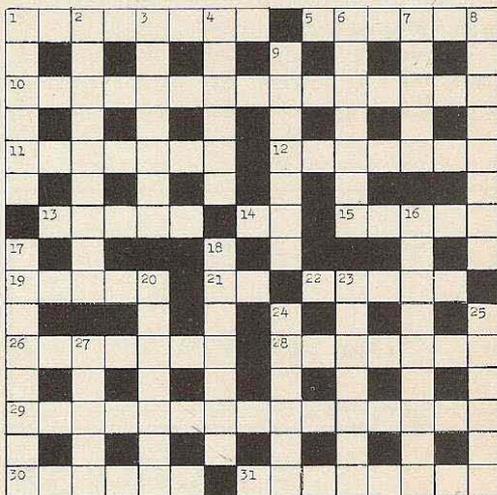

Across

- An amplifying station used to boost the volume on long telephone lines.
- Noise heard in a receiver due to atmospheric disturbances.
- The lack of dilution of a hue by white.
- Flyback.
- An electrode used to initiate conduction at the desired points in each cycle.
- Undesired sound.
- Aluminum. (Abbr.)
- To make merry.
- A series of names, numbers and words.
- A world-governing body. (Abbr.)
- The centimeter-gram-second electromagnetic unit of a magnetic induction.
- Also called piggy-back control.
- Trade name for a phenolic compound having good insulating qualities.
- Use of radio signals for course-plotting.
- To push with sudden force.
- An electrode whose primary function is to reverse the direction of an electron stream.

SCR-SILICON-CONTROL RECTIFIERS!

PRV	16A	25A	PRV	16A	25A
50	.50	.75	400	1.60	1.90
100	.95	1.20	600	1.95	2.75
200	1.15	1.30	800	2.85	3.60
300	1.40	1.65	1000	3.70	4.50

5U4 Silicon Tube ..\$1.50@, 6 for \$5
 5R4 Silicon Tube\$4@, 3 for \$9
 866A Silicon Tube ..\$10@, 2 for \$18

MICA MTG KIT T036, T03, T010, 4/\$1
 ANODIZED T036 INSULATOR5/\$1
 ZENERS 1 Watt 6 to 200V ..80@, 3/\$2
 ZENERS 10 Watt 6 to 150V \$1@, 6 for \$5
 STABISTOR up to Ten Watt, 20 to \$1

Wanted Test Sets (TS) & Equip.

*** TRANSISTORS * SCR'S * ZENERS!!!**

Full Leads Factory Tested & GTD!
 PNP 150 Watt/15 Amp HIFwr T036 Case!
 2N441, 442, 277, 278, D8501 Up To
 50V/VCOB\$1@, 7 for \$5
 2N278, 443, 174, Up to 80V \$2@, 4 for \$5
 PNP150 W/2N1980, 1970 &
 2N2075, 2079\$2@, 3/\$5
 PNP 30 Watt/3A, 2N115, 156, 235, 242
 254, 255, 256, 257, 301 40e@ 3 for \$1
 PNP 2N670/300MW 35e@ 5 for \$1
 2N671/1 Watt 50e@ 4 for \$1
 PNP 25W/TO 2N538, 539, 540 ..2 for \$1
 2N1038 6/\$1, 2N10394 for \$1
 PNP/T05 Signal 350MW 25e@, 5 for \$1
 NPN/T05 Signal IF, RF, OSC 5 for \$1
 Finned Heat Sink 180 SQ., \$1@, 3/\$2
 Finned Sink Equip. 500 SQ. \$3@, 2/\$5
SILICON PNP/T05 & T018 PCKG
 2N327A, 332 to 8, 474 to 9, 541 to 3,
 935 to 7 & 1276 to 9, 35e@4/\$1

866 C.T./2.5V/10A FILAMENT
 XFMR 10 Ky Instld \$2@,8/\$5

Bandwith Ceramic 500W 2P/6Pos, \$2@
 5Hy-400Ma Choke \$4@2/\$5
 250Mfd @ 450 Wv Lectlytic \$3@, 5/\$10

Send 25c for New Catalog

"TAB"

"That's A Buy"

"TAB" * SILICON ONE AMP DIODES

Factory Tested & Guaranteed

Piv/Rms	Piv/Rms	Piv/Rms	Piv/Rms
50/35	100/70	200/140	300/210
.05	.07	.10	.12
400/280	600/420	800/560	900/630
.14	.21	.30	.40
1000/700	1100/770	1700/1200	2400/168
.50	.70	1.20	2.00

** All Tests AC & DC & Fwd & Load!*

1700 Piv/1200 Rms @ 750 Ma. 10 for \$10
 2400 Piv/1680 Rms @ 750 Ma. 6 for \$11

Silicon Power Diodes, Studs & P.F. **

D. C.	50Piv	100Piv	200Piv	300Piv
Amps	35Rms	70Rms	140Rms	210Rms
** 12	.25	.50	.75	.90
** 18	.20	.30	.75	1.00
	.45	1.20	1.40	1.90
	1.85	2.90	3.50	4.60
	240	3.75	4.75	7.75
D. C.	400Piv	600Piv	700Piv	900Piv
Amps	280Rms	420Rms	490Rms	630Rms
12	1.20	1.50	1.75	2.50
** 18	1.50	Query	Query	Query
	45	2.25	2.70	3.15
	160	5.75	7.50	Query
	240	14.40	19.80	Query

We Buy, Sell & Trade As Well!

"TAB"

TERMS: Money Back Guarantee! Our 24th Year. \$5 Min. Order F.O.B. N. Y. C. Add Shipping Charges.

56 DX PEARL ST., BKLYN, 11201 N.Y.

PHONE 212-522-7300

Send 25c For Catalog

DC 3/2" Meter/RD/800Ma \$3@, 2/\$5
 Socket Ceramic 866 Tube5/\$1
 Socket Ceramic 4X150/Loktal4/\$1
 W.E. Polar Relay#255A \$4@,3/\$10
 Toroids 88Mhy New Pkg 75e@,4/\$2
 200 KC Freq Std Xtals4/\$2
 2 Side/ou Printed Ckt Bd New 9x12" \$1
 Finished Piezo Xtals Blanks50/\$1
 Line Filter 4.5A @115VAC 6 for \$1
 Line Filter 5A @125VAC 3 for \$1
 Choke 4Hy/0.5A/27Q \$3@4/\$10
 H'sld Stevens Precision Choppers \$1
 PL259A & SO239 CO-AX M&F Pairs 3/\$2
 Phone Patch Xfmrs Assd 4 for \$1
 FT243 Xtal & Holder, surplus .. 5 for \$1
 Insld Binding Posts "EBY" 25/\$1
 Sun-Cells Selenium Assd10/\$1
 Band Pass Filters 60, 90, 150 cys. 3/\$3
 2.5MH Piwound 500MA Choke3/\$1
 Beam Indicator Selsyns 24VAC2/\$5
 Fuse 250MA/3AG50/\$1, 300/\$2
 Oil Cndsr Strobe, Photoflash 25MFD
 2000V G.E./Pyranol, \$7@2/\$10
 Resistor Bleeder 50K/100W 3 for \$1

Send 25c for Catalog

Discaps .001@1000WVDC 10e@ ..20/\$1
 Discaps, 2x .004@1000WVDC 15e@, 10/\$1
 Discaps .03@1000WVDC 15e@10/\$1
 Discaps .01 @2000WVDC 18e@6/\$1
 Discaps .001 @5KVWDC 20e@6/\$1
 Discaps .005@5KVWDC 25e@5/\$1
 Discaps 130mmG/6KV 20e6/\$1
 .02@50WVDC25 for \$1
 6 or 12VAC Minifan & Blade\$1

X-Formers All 115V-60Cy Primary—

2500V @1CMA & Fil \$2@4/\$5
 1100VCT @ 300Ma, 6v @ 8A, 5v @ 3A &
 125V Bias, abt 1200 VDC \$4@3/\$12
 480 Vet @ 40Ma & 6.3 @ 1.5A CSD \$1.50
 10 Vet @ 5A & 7.5 Vet @ 5A\$5
 6.3 Vet 15.5A & 6.3 Vet @ 2A\$4
 7.5 Vet @ 12A \$3@ 2/\$5

Down

- To preserve for later reproduction.
- A high-vacuum thermionic tube used to control the magnitude of current flow. (PI.)
- Also called antennas.
- An ionized layer in the atmosphere, about 55 to 85 miles above the earth's surface.
- Representation of an operating system by computers and its associated equipment and personnel.
- The rotation of a cross-section of a waveguide about the longitudinal axis.
- The parts of a digital computer which carry out instructions in proper sequence.
- Capable of being heard.
- The transmitted portion of the suppressed side-band.
- A dielectric that retains a charge after the charging field is removed.
- A metallic alloy having special magnetic properties.
- Fixed set of plates in a variable capacitor.
- Slang expression for radio broadcasting.
- A position of authority or trust.
- A refinement added to an impedance bridge to avoid the effects of capacitance to ground.
- A device, also known as acoustic radar.

Solution Pg. 106

\$100,000 IN PRIZES



\$45 OPERATING DESK FREE WITH 10 SUBSCRIPTIONS

Walnut Pervaneer finish 18" x 40" x 29" high with 4 drawers, great for transceivers. Easy to assemble. FOB Mo. 48 lbs. Send 10 new \$6 subscriptions. USA only.

73, PETERBOROUGH, NH 03458

**MORE RANGE . . .
with NO NOISE**

**FOR ALL
MOBILE UNITS**



ELECTRO-SHIELD


**CUSTOM SYSTEMS
KITS • ACCESSORIES**

**ELIMINATE IGNITION NOISE
ELECTRO-SHIELD®
YOUR ENGINE**

FROM \$44.95

ESTES ENGINEERING CO.

543 W. 184th St., Gardena, Calif. 90247

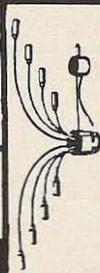

Solution To Puzzle on Pg. 118

1	R	E	P	E	A	T	E	R		5	S	T	A	T	I	S					
	E		L	E		L			9	A		R		W		O					
10	C		O	L	O	R	S	A	T	U	R	A	T	I	O	N					
	O		O		I		Y		D		I		S		T						
11	R		E	T	R	A	C	E		12	I	G	N	I	T	O					
	D		R		L		R		B		W					O					
		13	N	O	I	S	E		14	A	L		15	R	E	16	V	E	L		
17	E		N						18	M		E				E		S			
19	L		I	S	T	20	S		21	U	N		22	G		23	A	U	S	S	
	E												24	O					25	N	
26	C	A		27	S	C	A	D	E		28	F	O	R	M	I	S	A			
	T		C																		
29	R	A	D	I	C	H	A	V	I	G	A	T	I	O	N						
	E		A			R		L		C		V		A		E					
30	T	H	R	U	S	T			31	R	E	P	E	L	L	E	R				

YOUR CALL

Please check your address label and make sure that it is correct. In cases where no call letters has been furnished we have had to make one up. If you find that your label has an EE3* on it that means we don't know your call and would appreciate having it.



Interested in what European hams are accomplishing at the higher frequencies?

Read UKW - BERICHTE, the authoritative German quarterly, now with English summaries! Applications of the latest VHF and UHF techniques; equipment and antenna construction details. Each sixty-page issue packed with practical articles written by the most outstanding amateurs in Europe.


Annual subscription U.S.A. \$3.00, Canada \$3.25
H. Ingwersen, PA6AFN Box 87, Topsfield, Mass. 01983

CQ de W2KUW
All tubes bought
Electronic items wanted
Topping all offers

TED DAMES CO.
308 Hickory St., Arlington, N.J. 07032

**Tell Our Advertisers
You Saw It In 73**

\$100,000 IN PRIZES

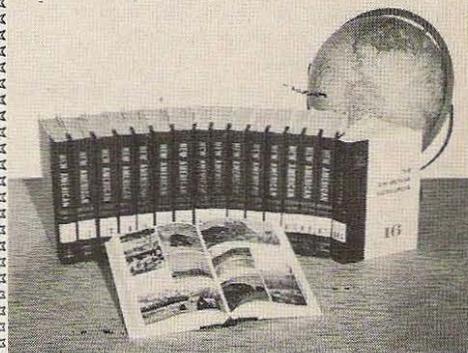

**\$160 ENCYCLOPEDIA
FREE WITH 20 SUBSCRIPTIONS**

New American Encyclopedia in 16 volumes, over 6000 pages, over 1100 full color pictures! Completely up to date, latest edition. FOB. If you have children you should have an encyclopedia. Just send us 20 new \$6 subscriptions to 73. USA.

73, PETERBOROUGH, NH 03458

Propagation Chart

September 1968

ISSUED JUNE 1

J. H. Nelson

EASTERN UNITED STATES TO:

GMT -	00	02	04	06	08	10	12	14	16	18	20	22
ALASKA	14A	14	14	7	7	7	7	14B	14	14	14	14
ARGENTINA	21	14A	14	14	7A	14	21A	21A	21A	21A	21A	21
AUSTRALIA	21	14	14	7A	7A	7	7B	14	14	14	21	21A
CANAL ZONE	21	14	14	14	7A	7	14A	21	21	21A	21A	21A
ENGLAND	7A	7	7	7	7	14	21A	21	21	21	14A	14
HAWAII	21	14	14	7A	7	7	7A	7B	14A	21	21	14A
INDIA	14B	7B	7B	7B	7B	14	14	14A	14A	14A	14	14B
JAPAN	14	14	7B	7B	7B	7	14B	14B	7B	14	14A	14A
MEXICO	21	14	14	7A	7A	7	14	21	21	21	21A	21A
PHILIPPINES	14	14	7B	7B	7B	7B	14B	14	14	14	14	14
PUERTO RICO	14	7A	7A	7	7	7	14	21	21	21	21	21
SOUTH AFRICA	14	14	7B	14	14	14A	21A	21A	21A	21A	21A	21
U. S. S. R.	7	7	7	7	7	14	14A	14A	14A	14	14	7B
WEST COAST	21	14A	14	7A	7	7	7A	14A	21	21	21A	21A

CENTRAL UNITED STATES TO:

ALASKA	14A	14	14	7	7	7	7	7	14	14	14	14A
ARGENTINA	21	14A	14	14	14	7	21	21	21A	21A	21A	21
AUSTRALIA	21A	21	14	14	14	7A	7B	14	14	14	21	21A
CANAL ZONE	21A	14A	14	14	14	7A	14	21A	21A	21A	21A	21A
ENGLAND	7A	7	7	7	7	7	14	21A	14A	21	14A	14
HAWAII	21A	21	14	14	7A	7	7	7B	14A	21	21A	14A
INDIA	14	14	14	7B	7B	7B	7B	14	14	14A	14	14B
JAPAN	14A	14	14	7B	7B	7B	7	7	14B	7B	14	14A
MEXICO	14A	14	7	7	7	7	7	14	14A	14A	21	21
PHILIPPINES	14A	14	14	7B	7B	7B	7B	7A	14	14	14	14
PUERTO RICO	21	14	14	7A	7A	7	14	21	21	21	21	21A
SOUTH AFRICA	14	14	7B	7B	7B	7B	14A	21	21A	21A	21	21
U. S. S. R.	7B	7	7	7	7B	7B	14	14	14A	14	14	7B

WESTERN UNITED STATES TO:

ALASKA	14	14	14	7	7	7	7	7	7	14	14	14
ARGENTINA	21	21	14	14	14	14	14	21	21A	21A	21A	21
AUSTRALIA	21A	21A	21	14	14	14	14	14	14	14	21	21A
CANAL ZONE	21A	21	14	14	14	7A	14	21	21A	21A	21A	21A
ENGLAND	7A	7	7	7	7	7	7B	14	14	14A	14A	14
HAWAII	21A	21A	21	14A	14	14	14	7	14A	21	21A	21A
INDIA	14	14A	14	7B	7B	7B	7B	14B	14B	14	14B	14B
JAPAN	21	21	14	14	7	7	7	7	14	14	14	14A
MEXICO	21	14A	14	7	7	7	7	14	21	21	21A	21A
PHILIPPINES	21	21	14	14	7	7	7	7	14	14	14	14A
PUERTO RICO	21A	14	14	14	7A	7	14	21	21A	21A	21A	21A
SOUTH AFRICA	14	14	7B	7B	7B	7B	14A	21	21	21	21	21
U. S. S. R.	7B	7B	7	7	7B	7B	7B	14	14	14	14	14
EAST COAST	21	14A	14	7A	7	7	7A	14A	21	21	21A	21A

A. Next higher frequency may be useful at this hour.

B. Very difficult circuit at this hour.


Good: 1, 2, 8-13, 16, 17, 19-27

Fair: 3, 4, 6, 7, 14, 18, 28-31

Poor: 5, 14

Note: VHF forecasts have been discontinued due to lack of reliable information.

DUAL GATE MOSFET PRE-AMPS

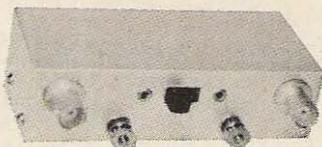

to 175 Mhz. **\$19.95** ppd.
to 300 Mhz. **\$23.95** ppd.
to 400 Mhz. **\$27.95** ppd.
to 450 Mhz. **\$31.95** ppd.

- Available from 5 MHz. to 450 MHz. Bandwidth is approximately 5% of frequency.
- Two Dual Gate MOSFET amplifier stages with each having a tuned input and tuned output. Each Dual Gate MOSFET is actually an integrated cascode circuit thus giving you 2 cascode circuits equivalent to 4 triodes.
- Exceptionally low noise (2.5 DB at 175MHz.), greatly reduced cross modulation and 10 times the dynamic range (signal handling capability) of the best bi-polar transistors. Also superior to preamps using junction FETs and Single Gate MOSFETs.
- Internal connections for high impedance AGC or manual gain control if needed.
- Type BNC input and output receptacles for minimum loss at UHF. Standard impedance is 50-75 ohms.
- Carefully tuned at our laboratory with sweep generator and oscilloscope for the best bandpass characteristic.
- Full wave UHF diodes protect input transistor.
- Operates on 6 to 16 volts DC, 5 to 15 Ma.

VANGUARD LABS

Dept. H

196-23 Jamaica Ave., Hollis, NY 11423

Wouldn't
your ad
Look good
here?

LOOKING FOR THE WEAK ONES?

The TEKRAD Mark V antenna has an enormous capture area compared to quads and yagi antennas . . . really pulls in the weak ones, and you work what you hear!

Missing DX off the side of the beam? The Mark V is omnidirectional so you know where the band is open at any time.

Windstorms worry you? The Mark V is impervious to wind and will stay up while the quad is going through the neighbor's roof.

Like to work all bands? Sure you do, and the Mark V will instantly put you on any band from 80M to 10M, horizontally polarized, with high efficiency and low VSWR. Make your transceiver act like a 2KWPEP rig, loudest on the band.

The Mark V antenna comes to you complete, ready to use, cut to length with 70 feet of feedline for only \$32.50 postpaid. All you have to furnish is a mast or tower about 50-60' tall.

Order today while the bands are hot.

TEKRAD, INC
P.O. BOX 57 VALPARAISO, FLORIDA 32580

W4JM/Ray W4SIW/Bill

DXERS and DXERS-TO-BE

Want to keep up to the minute of what's happening DXwise? Subscribe to Gus Browning W4BPD's new weekly DXERS MAGAZINE. 24 pages of DX events, coming up DXpeditions, QSL info, pix, etc. Rates, US surface \$11.00. US air mail \$12.90, West Indies \$18.50, S. America and Europe \$23.00, rest of world \$30.00.

New rates due to postal increase

The DXERS MAGAZINE
c/o W4 BPD

Route 1, Box 161-A,
Cordova, S.C., U.S.A.



ALUMINUM TOWERS

Send postcard for Literature

Dear 73,

After reading some tower construction articles in the July issue of 73, I had a horrible thought; does the average ham realize what the common termite might do to a wooden tower, if given the chance?

Anyone constructing a wooden tower should take all precautions to prevent damage by termites or other pests or decay. Consult your local lumber or hardware dealer for the necessary materials to treat the wood and nearby ground to prevent any such damage.

George S. Stevens WB2ZFA
Mays Landing, N.J.

Dear 73,

I want to take this opportunity to comment on the incentive license study sections in your magazine. I think they are the best. Really, I'm learning more by your type of presentation than I ever could out of the Handbook. I believe that basically the Handbook is designed for a person who has a basic knowledge of electricity and a little experience of the same. Coming in cold with absolutely no knowledge, the Handbook is very confusing to me. Most of the other hams in the club here think the same. In other words, fine business.

G. Gerald Burger WAØKUA
Secy. Huron Amateur Radio Club

Dear Kayla,

Decidedly like what you are doing. The humor is splendid and your Advance Class course is excellent. Keep laughing and the temptation to wring your hands is not so great. 88 to you too.

Jim Kaufman WAØRD
Boulder, Colorado 80302

Dear Kayla,

The big "40 meter push" which you presented in 73 depicts the beginnings of an excellent campaign. I'm all for, and would like to see 73 Magazine present and lead a year long marathon designed to eliminate the interference caused by commercial stations on 40 meters. If 73 would follow through with such an "elimination marathon", I promise to urge most of the hams with whom I come in contact to support the campaign.

Possibly 73 can print up some pre-written complaint letters to be signed and mailed by US hams to Radio Moscow, VOA, BBC, etc. I bet we can lick the interference problem in one year with cooperation. How about it 73?

Marty Hartstein WB6NWW
Long Beach, Calif.

OK, fellows, what say? I'll print up some form letters to be used as petitions. Let's give it a try. It can only cost postage and the work in getting signatures. Any other ideas from readers as to how to better make use of 40 will be appreciated and put to use.

Dear Wayne, Kayla, and Lin,

After a one year trial subscription I decided that 73 was great. I must say your editorials are right on the beam, so to speak. They are my thoughts entirely on almost every subject.

Keep up the good work and put in more humorous articles like Dilemma in Surplus (June '68). Keep putting in lots of ads, I read them word for word. And . . . best of all, put in more pictures with the articles, especially ones about decibels! HI HI.

Brent Christensen WAØSTS

Dear 73,

Thought that I would let you know that as lousy as the mail service is over here, I finally received my February issue of your most welcome bit of ham news from the States. My subscription was mailed to you in November at the same time that I mailed subs to the other two. I am getting 73 quite regularly even though late. I must say that I am a bit disappointed with the other two magazines as I have yet to receive my first copy. As you well know, there is no operation here and our only contact with the ham world in the states is through your magazines for which we are very appreciative. There are five hams in our group and by the time the magazine gets around, it is well dog-eared and equally as well read and appreciated. Keep up the good work. Just thought I would toss the roses where they are justly due. We do make good use of it and it does get passed around and then filed in the operating room.

Herb Wright WB6IHE
Saigon, So. Vietnam

Dear 73,

With great interest I read W2NSD's editorial on UFO's. I have been interested for several years in this subject. My views parallel those of the editorial and I hope in the near future I can assist in this proposed program. I do not know if there are any amateurs on this side of the pond that are interested but will do my best to find out. I think it would be of great value to have an arm of the network in Europe. I will keep my ears on 14250 and in the meantime try to scare up some interested parties on this end.

Richard J. Malby
APO New York 09176

Dear 73,

All US hams and relations visiting Spain are all times welcomed at the home of very old OM, V. S. Alexandersen, well known in the Amateur World between 1927-1936 as ET2X, ET3CS and ES3CX. I'm not active anymore, but I'm still a ham. Address Camino Son Toells 37, St. Augustin, Palma De Mallorca, Baleares, Spain.

V. S. Alexandersen

Dear 73,

Please pass along the word that I still have a bulk (300+) of National Zip Code Directory flyers to pass out free to anyone sending a request.

Earle and Marilyn McIvor
Box 8151, Rochester, N.Y. 14617

DIODE CIRCUITS HANDBOOK

An invaluable reference book. Covers rectifiers, meter circuits, mixers, detectors, modulators, products, FM detectors, noise limiters, squelch, AGC, BFO/Q-multiplier, xstr protection, AFC, Varicap tuning, audio clippers, FM modulator, balanced mods, Varactor multipliers, field-strength meters, wavemeters, RF probes, dummy loads, SWR bridge, tachometer, noise generator, square-wave gen, zeners, control circuits, voltage control, etc. 111 different circuits.

Andersen
WALCZ



An absolute steal at \$1.
73 MAGAZINE
Peterborough, N.H. 03458

TOROID CORES

Red "E" Cores-500 kHz
to 30 MHz- $\mu = 10$

#	OD	ID	H	EACH
T-200-2	2.00"	1.25"	.55"	\$3.00
T-94-2	.94	.56	.31	.75
T-80-2	.80	.50	.25	.60
T-68-2	.68	.37	.19	.50
T-50-2	.50	.30	.19	.45
T-37-2	.37	.21	.12	.40
T-25-2	.25	.12	.09	.30
T-12-2	.125	.06	.05	.25

Yellow "SF" Cores-10 MHz
to 90 MHz- $\mu = 8$

T-94-6	.94	.56	.31	.95
T-80-6	.80	.50	.25	.80
T-68-6	.68	.37	.19	.65
T-50-6	.50	.30	.19	.50
T-25-6	.25	.12	.09	.35
T-12-6	.125	.06	.05	.25

Black "W" Cores-30 MHz
to 200 MHz- $\mu = 7$

T-50-10	.50	.30	.19	.60
T-37-10	.37	.21	.12	.45
T-25-10	.25	.12	.09	.40
T-12-10	.125	.06	.05	.25

FERRITE BEADS: .125" x .125", $\mu = 900$. With Spec Sheet & Application Notes Pkg of 12, \$2.00

KILOWATT TOROID BALUN KIT: Still only \$5.00

EXPERIMENTER'S 2 CORE TOROID KIT—This famous kit contains cores, wire, and charts so that you can make your own high Q modern inductors for hundreds of practical applications.: \$1.50

MINIMUM ORDER: \$1.00

Please Add 25¢ per order

for Packing & Shipping

AMIDON ASSOCIATES

12033 Otsego Street

North Hollywood, Calif. 91607

"ARCTURUS" SALE

- Tube cartons 6AU6 etc. size, \$2.15 per 100. 6SN7 etc. size, \$2.55 per 100. 5U4GB size, \$2.95 per 100. 5U4G size, .03c each.
- 7" 90° TV bench test picture tube with adapter. No ion trap needed. Cat. #7BP7, \$7.99.
- Silicon rectifier, octal-based replacement for 5U4, 5Y3, 5AS4, 5AW4, 5Y4, 5V4, 5Z4. With diagram. Cat. # Rect 1, 99c each.
- 5 transistor circuit boards containing up to 6 transistors, plus diodes, resistors, capacitors, etc. Cat. # TB10, 99c.
- Kit of 30 tested germanium diodes. Cat. #100, 99c.
- RCA-110° flyback transformer, latest type, includes schematic diagram, applicable to any TV. Cat. # BR-1, \$2.99.
- Color yokes, 70° for all round color CRT's. Cat. # XRC70, \$12.95. 90° for all rectangular 19" to 25" color CRT's. Cat. # XRC90, \$12.95.
- Transistorized U.H.F. tuners used in 1965 to 1967 TV sets made by Admiral, RCA, Motorola, etc. Removable gearing may vary from one make to another. Need only 12 volts d.c. to function. No filament voltage needed. Easy replacement units. Cat. # U.H.F.507, \$4.95.
- U.H.F. Tuner—original units as used in TV sets such as RCA, Admiral, etc. covering channels 14 through 82, as part of #94D173-2. Complete with tube. Drive gearing is removable. Can be used in most sets. Cat. # U.H.F. 3, \$4.95.
- F.M. tuner—HI/FI amplifier tuning unit. Tunes from 88 to 108 mc. Contains two 10.7 Mc. I.F. transformers, one 10.7 sound discriminator, R.F. oscillator and mixer stages and 12DR8 tube. I.F.'s are standard "K" type. Circuit diagram for building F.M. radio included. Also plan for building F.M. tuner. Sam's photofac #620 shows 2 applications, 1 for radio, 1 for Hi-Fidelity tuner and amplifier. Cat. #FM-20, \$4.95. Send for our free catalog listing thousands of similar best buys in tubes, parts, kits, transistors, rectifiers, etc. Orders under \$5.00, add 50¢ handling charge. Include 4% of dollar value of order for postage. Canadian postage \$1.00 extra.

ARCTURUS ELECTRONICS CORP.

502-22nd St., Union City, N.J. 07087 Dept. 73
Phone: 201-UN 4-5568

GATEWAY ELECTRONICS

6150 Delmar Blvd., St. Louis, Mo. 63112

12 Volt Transistor Power Supply for
GE 25 Watt Progress Line Radio \$24.00

GE 4 Fre. Oscillator Deck for GE
Progress Line 150mc units. Pro-
vides osc. sig. for xmtr and re-
ceiver \$14.50

40-0-40 micro-amps Z ero Center
Meter \$ 2.95

12 Volt DC -117V AC Inverter
Parts Kit 200 Watt with diagram
and instructions, less case \$14.95

Jennings Vac. Var. Cap. (UCS-300)
with motor drive 10-300 Pf \$35.00

Telephone op. headset (Western
Electric) \$ 8.50

Minimum order \$5.00. Sorry, no catalog
at this time. Write for specific items.
Watch for our future ads in 73. Stop in
and see us when you're in St. Louis.

U. S. CRYSTALS

Surplus Crystals — Amateur

FT243, DC34, CRIA/AR, FT241,
HC6/U and other misc. crystals

Write for Free Catalog
U. S. CRYSTALS

Los Angeles, Calif.
P. O. Box 78397



Reflectometer SWR Bridge w/Meter, 30-1000mc. ...EX 8.50
BC733F 108-110mc Converts to Satellite Recvr.EX 8.75
TS1019/APM72A 9 Meters SUP1-CRT Tests APG30 EX 37.50
T485/ALT7 200W Xmitter 168-352mc w/2 6161's ...EX 19.50
T485 Schematic pp. 1.00. ... Complete Manual pp. 6.50
TCS12 Xmitter/Recvr Control Box with SpeakerEX 6.75
R443/ARN5D 430mc Recvr 11 Tubes 3 CavitiesEX 4.75
Jones No. 574.23 Micromatch Doubler CouplerEX 12.50
C3186/APS38B Control Box with MeterEX 4.50
C18 A.R.C. Type 12 Equipment Control BoxNEW 1.50
C1457 Control Box for R550/ARR40 ReceiverLN 1.75
C780B/A Control Box for ARN14B&C ReceiversLN 4.50
C45 Control Box for ARCL 4 & 12 EquipmentEX 1.35
6161 Tube w/Connectors. 100 Watts to 1200mc.EX 6.25
R101A/ARN6 100-1750kc Receiver. Four BandsEX 27.50
ID91B/ARN6 4" Navigators Bearing IndicatorEX 7.50
AS313B/ARN6 Station Seeking Loop. 100-1750kc.EX 6.25
RT316/APN12 160-234mc Transceiver w/TubesEX 12.50
ID169C/APN12 3JF1 CRT Scope. Coax SwitchNEW 12.50
AM300 Interfone Amp w/4 Tubes and DynamotorEX 3.25
FP336 Main Power Supply for APR9 ReceiverEX 16.50
PP337/APR9 Klystron Supply for TN130, TN131EX 10.50
ID226 Panoramic Indicator for APR9 ReceiverEX 14.50
R316A/ARR26 14-Tube 162-174mc AM/FM Recvr. LN 22.75
PP468 Power Supply for R316A Receivers 400cy.LN 4.75
C610 Control Box w/4 Tubes for R316A Recvrs.EX 4.50
Scope Xformer 1950V @3ma 5 Fil Windings 60cy.UN 4.75
SA325/U Coaxial Switch SP4T 48VDC MotorEX 6.50
Adaptor Cabr PL239 to BNC Panel SocketLN 3/1.75
OHMITE Z-50 Radio Frequency ChokeEX 6/1.00
Rt. Angle Drive w. Gears, Universal, 1/4" ShaftsEX 2/2.50
Feed-thru Capacitors 15 on Panel.Three Panels .../1.00
BNC (UG290/U Coaxial Panel SocketsEX 8/1.00
Coax 6" long w/BNC (UG260A/U) Plug each end EX 5/1.00
Coax 8" w/1 BNC Plug & 1 BNC Panel SocketEX 4/1.00

E. C. HAYDEN Box 294, Bay Saint Louis,
Mississippi 39520.
Prices: FOB Bay Saint Louis. Terms: Net, Cash.

Caveat Emptor?

★ Price—\$2 per 25 words for non-commercial ads; \$10 per 25 words for business ventures. No display ads or agency discount. Include your check with order.

★ Type copy. Phrase and punctuate exactly as you wish it to appear. No all-capital ads.

★ We will be the judge of suitability of ads. Our responsibility for errors extends only to printing a correct ad in a later issue.

★ For \$1 extra we can maintain a reply box for you.

★ We cannot check into each advertiser, so Caveat Emptor . . .

DAVCO DR30 WANTED. State price and condition. J. A. Tyson, W9JXD. 5345 University Ave., Chicago, Ill. 60615.

WRL's USED GEAR has trial—terms—guarantee! SR46—\$94.50; SR500—\$199.95; HW12—\$89.95; HW22—\$89.95; Galaxy V—\$289.95; Galaxy 300—\$159.95; TX62—\$99.95; 75A3—\$229.00; 51J3—\$395.00; NC-300—\$149.95; RME6900—\$149.95. Hundreds more—low prices—free Blue-Book list. Write WRL, Box 919, Council Bluffs, Iowa 51501.

VERY GOOD LATE MODEL NCX 3. Several modifications, outboard 10 kc receiver tune, ALC, and speaker. \$150. AC power supply, \$35. W7QBT, 890 W. 21 Street, Eugene, Oregon 97405.

WANTED, ANY CONDITION; VOM, VTOM, Weststone Bridge. Resistance Decade Box, meter monuments. Gil Barber, 4155 E. Carey, Las Vegas, Nevada 89110.

NCX-5 MARK II and NCXA in excellent condition. \$450 cash. Write K5TSR, 102 W. Rampart Dr., Apt. Q203, San Antonio, Texas 78216.

HALLICRAFTERS HT 32, like new, \$250. Globe King 500A 160 through 10. CW. AM. with your exciter will run 700 watts SSB. ALC, extra final, VFO. \$195, like new. 3-5 KVA generator, \$200. Ship. John Smith, 1924 Dolphin Blvd., St. Petersburg, Florida 33707.

FOR SALE: HEATH SB-301 rec. with CW filter factory aligned, \$260.00. Knight P2 SWR bridge, \$10.00. Heath Kit H D-10 electronic keyer, \$35.00. Instrograph code practice keyer with full set of tapes, \$25.00. Ameco code practice oscillator and CW monitor, \$5.00. Value of all equipment new, \$390.00. Will sell individually or as package for \$325.00. D. Willson; 7803 Dawn Rd., Cincinnati, Ohio 45237.

MODEL #28 KSR, \$295.00. Write for list of 10 years' surplus, RTTY, FAX, etc. G. White, 5716 N. King's Highway, Alexandria, Virginia 22303.

WANTED: Issues of 73. Oct. '60 to Dec. '62, Jan. '66 to Dec. '67. Kirt Fanning, 6021 Edgewood, LaFrange, Ill. 60525.

FOR SALE: Motorola 80-D, 12v, complete and a Link 50ufs, 110v base complete, both on 52.525HZ. \$120 for the pair. WA9GVE, 7424 Illinois Rd., Fort Wayne, Indiana.

FOR SALE: Clegg Apollo Six Linear Amplifier. Brand new! Below cost! Contact Jack Batts, Five Old Tavern Road, Wayland, Mass. 01778. Phone 653-6891.

NORELCO VIDEO TAPE RECORDER in perfect condition, tape and all additional parts included; CCTV camera—\$115.00, Vidicon—\$10.00, Vidicon Yoke—\$10.00, Elgeet 4" Telephoto lens—f2.7; Reverb—\$15.00; Simpson 260 VOM—\$35.00; Heath RF Signal Generator IG-102, \$15.00; EICO R-C Bridge & RLC Comparator—\$18.00; Tachometer—\$10.00. Wanted: 6M SSB Transceiver. WB2GKF, 506 Mount Prospect Avenue, Clifton, N.J. 07012.

FOR SALE: Complete Hallicrafters station in excellent condition. HT-37, and SX-100 with R-66B speaker. \$300. James Winter, RR 2, Huron, S.D. 57350.

THE HAM-DINGER: Warren (Ohio) A.R.A. 11th Annual Hamfest, Sunday, August 25, Newton Falls, rain or shine. Follow arrows from Rt. 534 or Turnpike Exit 14. Talk-in stations, 10-6-2-. Prizes, swapshop, homebrew-code contests, XYL-YL program, ragchews galore. Food sold or bring picnic. For Hamfest bulletin write W.A.R.A., Box 809, Warren, Ohio 44481.

TWO METER FET PREAMPLIFIER. Typical specifications: 12 DB or better gain with less than 2DB noise figure. \$10.95 postpaid. Communications Associates, P.O.B. 13275, St. Petersburg, Fla. 33731.

HALLICRAFTERS HT32B; \$275; NC-300, \$125; matching pr 813's GG linear with pwr supply, \$50; TR-4 with ac pwr supply and speaker, \$500. Beautiful. K6SUQ, 5 Rydal Court, Orinda, Calif. 94563.

WANTED: Heath-VX-1. Also G-76 AC power supply, must be in fine condition. Cash. G. Gysan, 53 Lothrop St., Beverly, Mass. 01915. Phone 922-3850.

FOR SALE: VHF EQUIPMENT: 6 meter SSB, HX-30 and HA-20 linear, factory wired, mint condition with manuals, \$245.00. Gonset communicator II-B, 6 meters, 12/117v in mint condition with manual, \$115. Gonset #3350, G-76 DC power supply (all transistor), \$50.00. W1VYB-J. Gysan, 53 Lothrop Street, Beverly, Mass. 01915. Phone: 922-3850.

TOROIDs, uncased 44 or 88mH, also individually epoxy encased 88mH for standards, any 5, \$1.50. 255A relay \$2.10, 18B socket 70¢ all PP USA. E. W. Evans, K4OEN, 220 Mimosa Ln., Paducah, Ky. 42001.

"SAROC" FOURTH ANNUAL fun convention scheduled January 8-12, 1969, in Hotel Sahara's new space convention center, Las Vegas, Nevada. Advance registration closes January 1, 1969. Ladies program in Don the Beachcomber. Technical seminars, FM, MARS, RTTY, QCWA, WCARS-7255. Registration \$12.00 per person entitles "SAROC" participants to special room rate \$10.00 plus room tax per night single or double occupancy, admittance to cocktail parties, technical seminars, exhibit area, Hotel Sahara's late show, Sunday breakfast equal to any banquet dinner, ask any "SAROC" veteran. Brochure planned November mailing for details QSP QSL card with ZIP Southern Nevada ARC, Box 73, Boulder City, Nevada 89005.

ARC-1 Transceiver 100-156 Mc, 25 Watts AM, with tubes, schematic, conversion info for 2-meters. Used, good. 50 lbs. \$20.00

ARC-1 only, less tubes, \$12.00
BC-221-AK with AC Power, Calib. Book & Xtal. \$95.00

TS-174, 20-250 Mc. Freq. Meter, on rack panel with AC Power, Calib. Book & Xtal. \$95.00.

Brush BL-202 2-channel oscillograph, Used, Exc. \$90.00

Sorensen 3000S AC Line Voltage Regulator, 3000 V.A. Used, Exc. \$125.00

Non-Linear-Systems 451 Digital Voltmeter. P.U.R. Send 10c for flyer listing surplus equipment, test equipment, new and used ham gear.

JEFF-TRONICS

4252 Pearl Rd. Cleveland, Ohio 44109

GO VHF

Go VHF the easy VHF Associates way. Send for descriptive Technical Bulletins describing our complete line of TRANSMITTER RECEIVING CONVERTERS and VARACTOR FREQUENCY MULTIPLIERS for 50, 144, 220, 432 and 1296 MHz.

VHF ASSOCIATES, INC.

P.O. Box 22135, DENVER, COLORADO 80222

**LARGEST SELECTION in United States
AT LOWEST PRICES—48 hr. delivery**

**JAN
CRYSTALS**

Thousands of frequencies in stock. Types include HC6/U, HC18/U, FT-241, FT-243, FT-171, etc.

SEND 10¢ for catalog with oscillator circuits. Refunded on first order.

2400B Crystal Dr., Ft. Myers, Fla. 33901

EASY CONSTRUCTION

MEANS
UNIT CHASSIS

WRITE
DEVICES

BOX 136, BRONX, N.Y.—10463

Get more watts per dollar

Send for free list—

NC200, AC200, both \$349.00; HRO500, Demo., \$1495.00; Swan 500, Demo., \$420.00; 350 for \$349.00; Markll Lin., Demo., \$530.00; Collins, 32S3, \$650.00; Hallicrafters SR2000 & P2000, both \$1250.00; Used for \$995.00.

FRECK RADIO & SUPPLY CO., INC.

38 Biltmore Avenue • Asheville, N.C. 28801

T. T. Freck W4WL 704-254-9551 Doug Jones WB4IHO

**"THE COMPLETE HAM STORE"
WHERE YOUR DOLLAR BUYS THE MOST**

All leading lines of amateur gear:
We give best trade-in allowance
for your gear on new equipment:
Call us for the best deal:

**WE PAY CASH FOR HAM & CB RADIOS
CALL OR WRITE**


BOB'S AMATEUR ELECTRONICS

927 N.W. 1st. St., OKLA. CITY, OKLA. 73106
Phone 405-CE-5-6387

WE PAY CASH FOR TUBES

Lewispaul Electronics, Inc.
303 West Crescent Avenue
Allandale, New Jersey 07401

VIBROPLEX

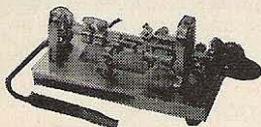

ENJOY EASY,
RESTFUL KEYING
\$21.95 to \$43.95
THE VIBROPLEX
CO., INC.
833 Broadway,
N. Y. 3, N.Y.

TRADE YOUR SURPLUS FOR BRAND NEW GEAR!

Your surplus can easily make a good down payment on brand new ham equipment. Send me your list of surplus and tell me what you want.
Bill Slep, W4FHY

Write-Wire-Phone (813) 722-1843

SLEP ELECTRONICS COMPANY

2412 Highway 301 N, Ellenton, FL 33532

YOUR SURPLUS WANTED BY THE FASTEST GUN IN THE EAST



No horsing around, we pay fast . . . in 24 hours . . . and we pay more. We'll swap or trade new equipment too . . . We quote fast too. We also pay for shipping, insurance, etc. You call fast, now, collect, for fast quote.

SPACE ELECTRONICS

div. of MILITARY ELECTRONICS CORP.

11 Summit Ave., East Paterson, N.J. 07407, (201) 791-5050

ETCHED CIRCUIT BOARDS

Novice Trans.2.75	Novice rec.2.75
RTTY Encoder2.50	RTTY Decoder4.00
UHF Dippers2.25	SWR Bridge1.25
Lab Supply3.50	144 Converter5.75
Keyer4.95	CP Osc. Mon.1.25

Send order or Catalog request to . . .

HARRIS CO.

BOX 985, TORRINGTON, CONN. 06790.
Conn. Res. add sales tax.

SURPLUS SALE

We have to move a quantity of material out of one of our storage areas, and need room. Many parts, assemblies and assorted material will be sold at cost (or below) on a first come first served basis. Our special sale flyer is available by sending 3 unused 6c postage stamps to cover postage & handling.

BIGELOW ELECTRONICS

P.O. Box 17

Bluffton, Ohio 45817

RTTY GEAR FOR SALE. List issued monthly, 88 or 44 MHY torroids 5 for \$1.50 postpaid. Elliott Buchanan & Associates, Inc., 1067 Mandana Blvd., Oakland, California 94610.

3000 V @ 3µF brand new GE Pyronal oil capacitors \$3 each. Can mail 3-lbs each shipping wt., FOB. P. Wandelt, RD # 1, Unadilla, New York 13849.

WANTED: Military, commercial, surplus Airborne, ground, transmitters, receiver, testsets accessories. Especially Collins. We pay freight and cash. Ritco Electronics, Box 156, Annandale, Va. Phone 703-560-5480 collect.

CLEGG VENUS 6 M SSB serial 100 33 w/ac ps and APOLLO LINEAR 1200 265. Both units recently factory checked. Included SS Booster 708 308. Everything \$450.00. Eastern Penna. Write Box 968, c/o 73 Magazine.

SELL. Excellent CE100V, \$495. Kent Markel, Box 144A RR 1, Lexington Park, Maryland 20653. 301-863-5967.

FOR SALE: SX101—\$100; Knight R100A—\$70; Ranger II—\$150; DX60—\$40; HW32—\$75. Don Ahonen, Rt. 1, Bx 291A, Lisle Road, Owego, New York 13827.

WANTED: HA-10 LF/MF tuner, new or used. F. Rafalowski, 525 Home Ave., Trenton, New Jersey 08611.

SELL/TRADE: Collins mechanical filters, F455N-20 (2kc), F455N-30 (3kc), F455N-40 (4kc), on partially cannibalized Collins sub-chassis 5407577006. Will remove filters or send sub-assembly. Trade for or buy 500kc filters for 51J4 receiver: F500B-31, F500B-14, F500B-08, or what have you that fits? W. A. Kernaghan, 1752 Kilohi St., Honolulu, Hawaii 96819.

FOR SALE: Thunderbolt. Complete with spare tubes. Will ship. \$225. K6HLO, 511 Oak St., Roseville, California 95678.

THE CENTRAL NEW YORK CHAPTER OF QCWA will hold its annual banquet and meeting on September 28, 1968, at Hanson's Hotel, Oquaga Lake, Deposit, New York. Cocktail QSOs from 5 to 7 p.m. Buffet dinner at 7 p.m. and business meeting and election of officers at 8:30 p.m. All QCWA members are invited to attend and enjoy this program. Use exit 83 from the East, exist 82 from the West, on route 17. Tickets \$5. For further information contact Clark Galbreath W2AXX, 111 Keeler St., Endicott, N.Y. 13760.

FOUR CORNERS FIELD DAY! September 21, 22. Club station K5WXI will operate 15, 20, 40 and 80 meters SSB and CW day and night. "5 Ø 7" award for working this station.

THE FOUNDATION FOR AMATEUR RADIO will hold its annual Hamfest on Sunday, September 22 from 1000 until 1700 hours at the Gaithersburg Fairgrounds in Gaithersburg, Md.

THE IOSCO RADIO CLUB presents its 4th annual Northeastern Michigan Hamfest on October 4, 5, 6 at East Tawas, Mich. 60 miles north of Bay City on US 23. Programs will begin Friday, October 4, at 6 p.m. ending Sunday afternoon at 3 p.m. For additional information contact Jerry Mertz W8DET or Glenn A. Pohl K8IYZ.



"FLAT PAK" INTEGRATED CIRCUITS!!

BRAND NEW!
\$1.49 **DUAL 914***

We include
 30 Basic IC Projects
RADIO-ELECTRONICS
 January & JULY 68



RTL Logic
 -55° C to +125° C
 Electronics World:

★ First time anywhere two identical IC's in one, package.

EPOXY SILICON TRANSISTORS

- 3-FK-4046, 1W, 0.5A, npn, 250MC \$1.00
- 3-2N3568, 350MW, 200MC, 200BVC, NPN \$1.00
- 4-2N3563, NPN, 600MC, 200MW \$1.00
- 3-2N3683, NPN, 1000MC, 5MA, 200MW .. \$1.00
- 3-14 WATT, B-5000, npn, 3A \$1.00
- 4-2N4313, PNP, 600MC, 200MW \$1.00
- 4-2N3565, 500HFE, npn, 200MC \$1.00

FAIRCHILD INTEGRATED IN-LINE CIRCUITS



Tested, with data sheets

- 930 DUAL 4 INPUT GATE & EXPANDER \$1.00
- 933 DUAL INPUT EXPANDER \$1.00
- 944 DUAL POWER GATE \$1.00
- 946 QUAD 2 INPUT NAND/NOR GATE \$1.00
- 952 DUAL 2 INPUT INVERTER GATE \$1.00
- 953 2-2-3 INPUT AND GATE \$1.00
- 954 DUAL 4 INPUT AND GATE \$1.00
- 955 8 INPUT AND GATE W/2 INPUTS \$1.00
- 956 DUAL INPUT BUFFER \$1.00

100's of other IC's including: Flip-Flops, Registers, Adders, etc. Write for listing.

FAIRCHILD ** BRAND NEW! "FLAT PAK" INTEGRATED CIRCUITS Sale

- 900 Buffer \$1.49
- 903-903* 3 Input Gate \$1.69
- 904-904* Half Adder \$1.69
- 914-914* Dual 2 Input Gate \$1.49
- 923 JK Flip Flop \$1.69
- 923-923* JK Flip Flop \$1.98
- 927 Quad Inverter \$1.69

*First time anywhere two identical IC's in one package, example 923-923 contains two separate JK flip-flops in one package. 914's and 923. We include 50 uses. ** Licensed. 1/4" x 1/4"

LINEAR AMPLIFIERS with circuits & data

- 702C WIDE BAND DC \$3.98
- 703H RF-IF-FM \$1.49
- 709C HI-GAIN OPERATIONAL \$3.98
- 710C HI-SPEED DIFF. COMP. \$3.98
- 711C DUAL COMPARATOR \$4.98

400 mc
5 for \$1 NPN



2N706
 Watts | V_{cb} | H_{fe} | ma
 .5 | 30 | TO-300 | 150

SILICON

\$10 ORDERS
 CHOOSE
 ANY
\$1 ITEM **Free**

100 MICROAMP PANEL METER



SILICON POWER STUD RECTIFIERS

PIV	3A	6A	12A	55A
50	<input type="checkbox"/> .06	<input type="checkbox"/> .16	<input type="checkbox"/> .20	<input type="checkbox"/> .50
100	<input type="checkbox"/> .07	<input type="checkbox"/> .22	<input type="checkbox"/> .25	<input type="checkbox"/> .75
200	<input type="checkbox"/> .09	<input type="checkbox"/> .30	<input type="checkbox"/> .39	<input type="checkbox"/> 1.25
400	<input type="checkbox"/> .16	<input type="checkbox"/> .40	<input type="checkbox"/> .50	<input type="checkbox"/> 1.50
600	<input type="checkbox"/> .20	<input type="checkbox"/> .55	<input type="checkbox"/> .75	<input type="checkbox"/> 1.80
800	<input type="checkbox"/> .30	<input type="checkbox"/> .75	<input type="checkbox"/> .90	<input type="checkbox"/> 2.30
1000	<input type="checkbox"/> .40	<input type="checkbox"/> .90	<input type="checkbox"/> 1.15	<input type="checkbox"/> 2.70



1 AMP TOP HAT AND EPOXIES

PIV	SALE	PIV	SALE	PIV	SALE
50	<input type="checkbox"/> .05	800	<input type="checkbox"/> .19	1800	<input type="checkbox"/> .87
100	<input type="checkbox"/> .07	1000	<input type="checkbox"/> .31	2000	<input type="checkbox"/> 1.05
200	<input type="checkbox"/> .08	1200	<input type="checkbox"/> .44	3000	<input type="checkbox"/> 1.60
400	<input type="checkbox"/> .11	1400	<input type="checkbox"/> .62	4000	<input type="checkbox"/> 1.90
600	<input type="checkbox"/> .16	1600	<input type="checkbox"/> .72	10000	<input type="checkbox"/> 4.80

MICROMINIATURE SILICON RECTIFIERS

Actual Size →

PIV	SALE	PIV	SALE
50	<input type="checkbox"/> 5¢	600	<input type="checkbox"/> 20¢
100	<input type="checkbox"/> 7¢	800	<input type="checkbox"/> 25¢
200	<input type="checkbox"/> 9¢	1000	<input type="checkbox"/> 31¢
400	<input type="checkbox"/> 12¢		



1. AMP

★ Handles 2 Amps
2 AMP
800 PIV for
TOP HAT **\$1**
RECTIFIERS

TUNNEL DIODE
 DIODE
 1N3716/TD3
 Actual Size
 Used in many oscillator and amplifier circuits
\$1

10¢ for bargain catalog on 100's of \$1 Poly Pak assortments, transistors, rectifiers, zeners, ICs, Triacs, SCRs, etc., parts & equipment. "It's the hottest bargain parts catalog in the industry."

Terms: add postage. **Rated:** net 30, cod's 25%
 Phone Orders: Wakefield, Mass. (617) 245-3829
 Retail: 211 Albion, St., Wakefield, Mass.

POLY PAKS

P.O. BOX 942 A
 Lynnfield, Mass. 01940


LIBERTY PAYS MORE!!

WILL BUY FOR CASH ALL TYPES

- ELECTRON TUBES
- SEMICONDUCTORS
- Military Electronic Equipment
- Test Equipment

PRESTEL FIELD STRENGTH METER

(Model 6T4G)

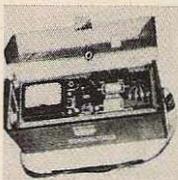

Frequency Range: 40 to 230 and 470 to 860 Megahertz. Calibrated outward from 10 to 50,000 Microvolts. Nothing makes it easier to properly and speedily find the correct place to install TV, FM and Communication Antennas. You can measure and hear the signals with this 4 1/2 volt battery economically powered unit. There is nothing else like it!

Only \$120.00

WIRE, WRITE, PHONE COLLECT! WE PAY FREIGHT ON ALL PURCHASES

Liberty Electronics, Inc.

548 Broadway, New York, New York 10012, Phone 212-925-6000

BIG CATALOG

World's "BEST BUYS" in GOV'T. SURPLUS Electronic Equipment

RECEIVERS:

RCAF GR-10—195-410 KC & 1.4-31 MC, Used, Checked: \$99.95
 BC-603—20-27.9 MC FM Receiver with sensitivity and squelch: Used, Not Checked: \$22.95 Used, Checked for op.: \$32.95
 BC-348 Receiver—200-500 KC and 1.5-18 MC w/Crystal Phasing BFO, and Vernier Tuning, AVC, MVC. Prices: Used, less Dynamotor: \$69.50—Used, less Dynamotor, operation checked: \$79.50

Power Supply for BC-348—115 VAC New: \$18.95

COMMAND RECEIVERS — TRANSMITTERS:

BC-453—190-550 KC, with Dynamotor Used: \$16.95
 BC-454—3.0-6.0 MC, with Dynamotor Re-New: 19.95
 BC-455—6.0-9.1 MC, with Dynamotor Re-New: 14.95
 R-25/ARC-5—1.5-3.0 MC, less Dynamotor New: 19.95
 R-28/ARC-5—100-156 MC, less Dynamotor Used: 22.95
 T-18/ARC—2.1-3.0 MC Used: \$9.95 New: 12.95
 T-20/ARC—4.0-5.3 MC Used: \$6.95 New: 9.95
 T-21/ARC—5.3-7.1 MC Used: \$6.95 New: 9.95
 T-22/ARC—5.3-7.1 MC Used: 18.95 Unused: 9.95
 T-23/ARC—100-156 MC New: 24.95
 BC-969—3.0-4.0 MC Gov't. Reconditioned: 12.95
 BC-456 Modulator—Use with Command Transmitters 3.95
 MD-7/ARC-5 Modulator—ARC-5 and Comm. Trans. 9.95

RECEIVER — TRANSMITTERS:

BC-620 FM TRANSCIEVER—20-27.9 MC Crystal Control, and PE-97 Power Supply—6/12 VDC Re-New: \$19.95
 BC-659 FM TRANSCIEVER—27-38.9 MC Crystal Control, and PE-117 Power Supply—6/12 VDC Re-New: 19.95
 SCR-522 RECEIVER-TRANSMITTER—AM Four Channel Crystal Control—100-156 MC Used: 29.95
 ARC-3—100-156 MC 8 Channel Crystal Control AM—Aircraft Equip. Electric Band Change. R-77/ARC-2 Receiver—Used: 24.95
 T-67/ARC-3 Transmitter Re-New: 29.50

Prices F.O.B. Lima, O.—25% Deposit on COD's.

BIG FREE CATALOG—New edition just off the press! Send for your FREE copy today. Address Dept. 73.

FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

INDEX TO ADVERTISERS

Adirondack, 103	Kapitan's Komponents, 67
Aerotron (Ameo), 67	Leger Labs, 85
Amber Ind., 103	Lewispaal, 110
Amidon, 107	Liberty, 112
Arcturus, 107	Mesna, 91
Arrow Sales, 103	Mission, 15
ATV, 98	Montgomery Geodetic Services, 97
B.C. Electronics, 91	Mosley, 41
Bel Air, 100	
Bigelow, 110	Nat'l ARRL Convention, 104
Bob's Amateur Electronics, 109	Omega-T, 57
BTI (Hafstrom), 37	Palomar, 37
	Pickering, 61
Clegg, 84	Poly Paks, 111
Crabtree's, 23	
Cushcraft, 24	Radio Amateur Callbook, 99
Dames, Ted, 104	Radio Shack, 55
Devices, 109	R&R, 102
Drake, Cover IV	Redline, Cover II, 68, 69
DXer Magazine, 106	Rohn, 5
	Saleh, 98
Epsilon, 37	Scnry, 39
Estes, 104	Slep, 110
Evans, 58	Sound History, 35
Fair Radio, 112	Space/Military, 110
FM Magazine, 26	Stellar, 46
Freek, 109	Swan, 11
Gain, Inc., 33	TAB, 103
Galaxy, Cover III	TAB Books, 91
Gateway Electronics, 108	Tex Rad, 106
Gateway Towers, 106	Tefrex, 18, 29
Goodheart, 100	
Harris, 110	UKW, 104
Hayden, 108	US Crystals, 108
Heath, 19	
Henry Radio, 13	Vanguard, 36, 40, 73, 85, 90,
Hi Par, 97	101, 105
Hunter, 33	Vibroplex, 110
	VHF, 109
International Crystal, 3	Westcom, 99
JAN Crystal, 109	
JeffTronics, 109	73 Magazine, 25, 92, 93, 101,
	103