

60 cents

*hr*<sub>m</sub>

focus  
on  
communications  
technology . . .

# ham radio

JUNE 1968

reactance


3.5mhz

7mhz

14mhz

21mhz

28mhz

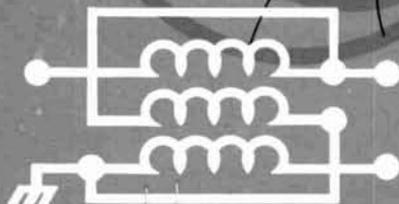


● broadband  
antenna  
baluns 6

## this month

- stable transistor vfo's 14
- six-meter mosfet converter 22
- amateur vhf fm operation 36
- electronic bugging 70
- sporadic-E propagation predictions 84

# Solid-State Projects for the shack

## Build this high stability VFO

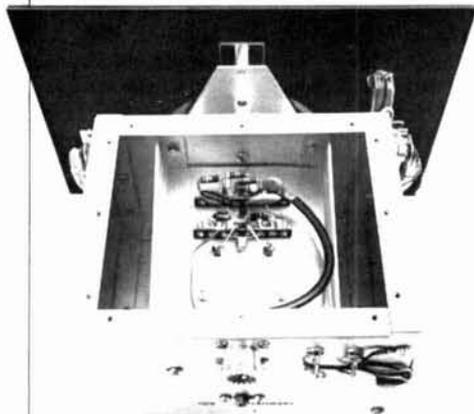


Here's an almost drift-free VFO built around the RCA-3N128 MOS/FET for flexible operation. After just 30 seconds warm-up, it tests out at less than 30 cycles drift in a two hour period.

Look in *The Radio Amateur's Handbook*, 1968 edition or write to RCA, Commercial Engineering, Sec. F175SD, Harrison, N.J. 07029 for full design details, including parts list, schematic, and building tips.

*All listed RCA devices are available from your  
RCA Industrial Semiconductor Distributor*

## Build this VFO calibrator

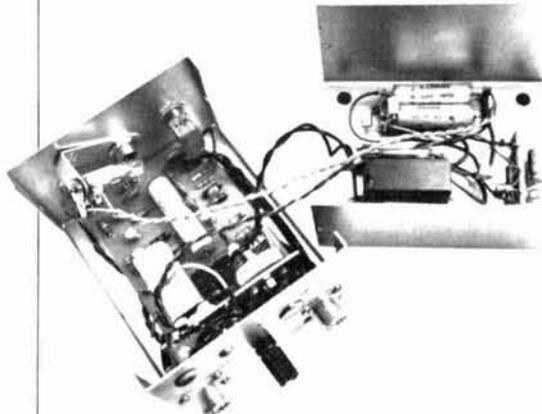


If you're interested in MARS and have just a "ham-bands-only" receiver, this may be your answer to VFO calibration outside normal bands. It uses two RCA-1N3193 rectifiers; two 1N34A signal diodes; one RCA-2N2614 and seven RCA-2N3241A transistors—provides calibrating beats at 100 kHz points as well as 50, 33, 25 and 20 kHz. Handy, too, for calibrating test equipment.

Look in August 1967 QST or write RCA, Commercial Engineering, Sec. F175SD, Harrison, New Jersey 07029 for August 1967 "Ham Tips." RCA Electronic Components, Harrison, New Jersey.

# RCA

the  
**2K-3**  
 ...a true  
 masterpiece

*by Henry Radio*

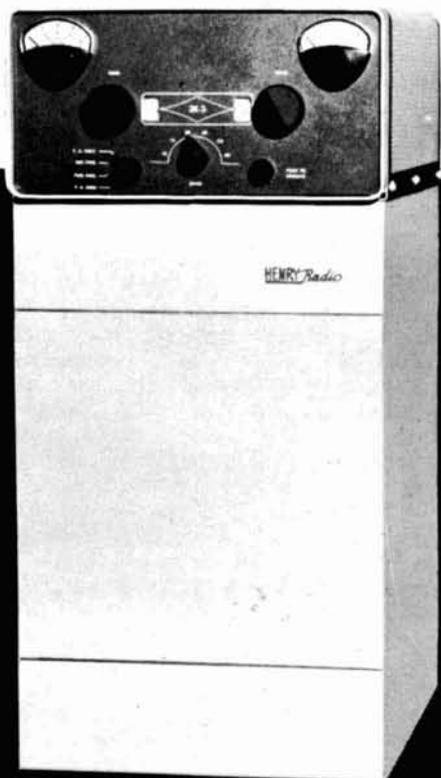

The 2K-2 was good . . . in fact, it was the best linear amplifier for the amateur on the market. But now, thanks to a pair of new and improved Eimac 3-500Z tubes, providing 1000 watts of plate dissipation, the 2K-3 operates with even greater power output and less drive. (Its so much better we're going to call it the 2K-3 now.) Still endowed with the same rugged and reliable mechanical construction, inspired design and using only the very best components, the 2K-3 is unquestionably the finest. You have heard the strong clear signals of the 2K-2 by now. Why not go on the air with an even better signal? You can NOW with the new 2K-3. Console or desk model \$745.00. Let us send you a descriptive brochure.

**EASY FINANCING • 10% DOWN OR TRADE-IN DOWN • NO FINANCE CHARGE IF PAID IN 90 DAYS • GOOD RECONDITIONED APPARATUS • Nearly all makes & models.**

Our reconditioned equipment carries a 15 day trial, 90 day warranty and may be traded back within 90 days for full credit toward the purchase of NEW equipment. Write for bulletin.

**TED HENRY (W6UOU)**

**BOB HENRY (WØARA)**

**WALT HENRY (W6NRV)**

CALL DIRECT . . . USE AREA CODE

Butler, Missouri, 64730	816 679-3127
11240 W. Olympic, Los Angeles, Calif., 90064	213 477-6701
931 N. Euclid, Anaheim, Calif., 92801	714 772-9200


East Coast Rep.: Howard Laughrey, 2 Elizabeth St.,  
 Chappaqua, N.Y. 10514. (914) CE 8-3683

**Henry Radio Stores**

*"World's Largest Distributor of Amateur Radio Equipment"*

**AT LAST!**

## **2 METER FM TRANSCEIVERS**

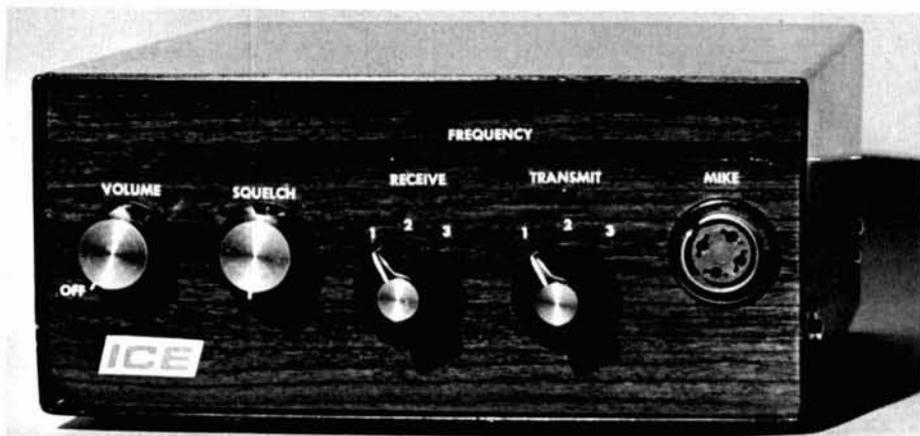

**SPECIALLY FOR HAMS**

### **FULLY TRANSISTORIZED — NO TUBES**

Operates on — 117 VAC — 12 Volts DC — Or Optional Internal Batteries — Separate receiver and transmitter 3 channel operation — Self-contained 3 x 5 speaker — Strong fiberglass Epoxy printed circuit boards — Power supply even regulates and filters on 12 VDC operation — cannot be damaged by Reverse Polarity — 21 transistors — 14 diodes — Double conversion crystal controlled receiver with 3 full watts of audio output and better than .3 $\mu$ V sensitivity (12 DB SINAD) — Transmitter and receiver may be ordered in either wide or narrow band at no extra charge (wide band supplied unless specified) — Small size 8" w x 3 1/2" h x 9 1/2" d — Light Weight - Less than 4 1/2 lbs — True FM receiver not a slope detector — High impedance dynamic microphone input with push to talk — Built in 117 VAC power supply — Simply plug in proper power cable for either 117 VAC or 12 VDC operation — Transmitter power output 4 watts minimum.

Complete with one set of crystals on 146.94, 117 VAC and 12 VDC power cables, less microphone and antenna . . . . . \$285.00

Extra crystals (transmit or receive) \$7.00      Mobile Mounting kit . . . . . \$7.00

# **ICE**

**INTERNATIONAL COMMUNICATIONS AND ELECTRONICS, INC.**  
1917 NW MILITARY HIGHWAY/SAN ANTONIO, TEXAS 78213      512 341-1311

See us at ARRL National Convention and HemisFair '68



**ham  
radio**

**staff**

**editor**

James R. Fisk,  
W1DTY

**roving editor**

Forest H. Belt

**vhf editor**

Robert M. Brown,  
K2ZSQ/W9HBF

**associate editors**

A. Norman Into, Jr.,  
W1CCZ/K2IEO  
Nicholas D. Skeer,  
K1PSR  
James A. Harvey  
W6BIAK

**art director**

Jean Frey

**publisher**

T. H. Tenney, Jr.,  
W1NLB

**offices**


Greenville, New Hampshire 03048  
Telephone: 603-878-1441

ham radio is published monthly by Communications Technology, Inc., Greenville, New Hampshire 03048. Subscription rates: U.S.A. and Canada, one year, \$5.00, three years, \$10.00. Copyright 1968 © by Communications Technology, Inc. Title registered at U.S. Patent Office. Printed in Montpelier, Vermont 05602, U.S.A.

Postmaster: Please send form 3579 to ham radio, Greenville, New Hampshire 03048.

**contents**

Broadband Antenna Baluns	William I. Orr, W6SAI	6
Stable Transistor VFO's	James R. Fisk, W1DTY	14
Six-Meter MOSFET Converter	Donald W. Nelson, WB2EGZ	22
Oscillators for SSB Equipment	Forest H. Belt	26
Amateur VHF FM Operation	John F. Connors, W6AYZ	36
Solid-State Transmitter Switching	John J. Schultz, W2EEY	44
Rack and Panel Construction	Howard S. Pyle, W7OE	48
An Amateur Anemometer	Henry D. Olson, W6GXN	52
Speech Processing in Amateur Equipment	James R. Fisk, W1DTY	60
Receiver Alignment	Lawrence Allen	64
Electronic Bugging	Robert M. Brown, K2ZSQ	70
Sporadic-E Propagation Predictions	Victor R. Frank, WB8KAP	84
<b>departments</b>		
A Second Look	4	Next Month 25
Advertisers Index	96	Propagation 84
Ham Notebook	56	Repair Bench 64
New Products	86	

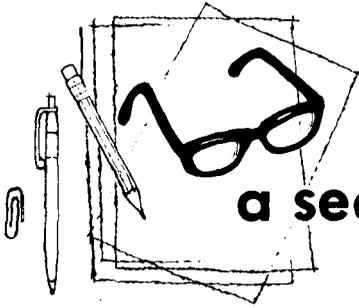

## a second look

by **Jim  
fisk**

**Did you ever wonder** why we are called hams? I suppose we all have at one time or another. We'll probably never know where the term really started, but there have been a lot of stories down through the years.

The first story I heard about "hams" related how the British amateurs referred to themselves as "am's." Because of the British pronunciation of the word, the Americans immediately picked it up as "ham." Since there were no other conflicting stories regarding the derivation of the word, I accepted it at face value.

However, in looking back over the story, this would mean that "ham" did not appear until radiotelephony became popular. Although old timers can't definitely remember the use of the word before the advent of radiotelephone, they're not sure exactly when it came into general use.

A story which was pretty widely circulated a couple of years ago indicated that H.A.M. was derived from the first letter of the last names of three prominent hams in the Boston area around 1910. This story seems to be concocted and apparently has no basis in fact.

The latest story I've heard tells of the derivation of the word ham as used in the theatre and how it was applied to the amateur radio operator. It seems that in the late 1880's there was a popular minstrel show on Broadway put on by one of the greatest blackface

teams of all time, Heath and McIntyre. Their show was called "The Ham Tree." This show ran for a long time and eventually the word ham was applied to all minstrel players. Later on, any person who was not in the professional theatre was called a ham.

As many of you may remember, broadcasting on the ham bands was perfectly legitimate in the early days of amateur radio telephone. In fact, many of our famous radio personalities got their start by broadcasting on the amateur bands. They put on news shows, sports shows, music shows, and general-interest entertainment. These people were called hams, probably quite properly, and through usage, all amateur radio operators became hams.

Of all the stories I've heard, this one seems the most probable. I'm sure that there are a lot of other stories relating how the word came into use. If you have any stories along these lines, I'd be very glad to hear about them. They are just as much a part of ham lore as the story of the "wouf hong," the "retty snitch" or the "old man." These stories are a lot like the lumberjacks' Paul Bunyon. Some of them are pretty far-fetched, but they are always good for a few laughs. Hams we are, and hams we'll stay, but we'll probably never know the true story of the word.

**Jim Fisk, W1DTY**  
**Editor**

# EIMAC

zeroed in on some grid problems so you can get higher power gain.

Want up to 20 times power gain in a cathode driven circuit? Try one of the tubes in our complete zero-bias power triode line. While you're solving problems, throw out the bias power supply. Forget some of the associated circuitry. And don't worry about destroying the tubes if you lose grid voltage. They don't need any.

These triodes are designed for use as Class B or C amplifiers in audio or radio-frequency applications. We've got zero-bias triodes ranging from 400 watts to 10,000 watts—the most complete range of zero-bias triodes available.


For more information on EIMAC's line of zero-bias power triodes, write Amateur Services Department, or contact your nearest EIMAC distributor.

	TYPICAL OPERATION					
	CLASS B RF LINEAR POWER AMPLIFIER, GROUNDED GRID					
	GLASS			CERAMIC		
	3-400Z	3-500Z	3-1000Z	3CX1000A7	3CX3000A7	3CX10000A7
Plate Voltage, Vdc	3000	3000	3500	2500	5000	7000
Max Signal Plate Current, A	0.333	0.333	0.75	0.800	1.56	5.0
Drive Power, W	32	35	85	60	215	1540
Output Power, W	655	644	1770	1170	5500	24,200
Filament Voltage, V	5.0	5.0	5	5.0	7.5	7.5
Filament Current, A	14.5	14.5	21.5	28/33	51	94/104
			73.0			

EIMAC  
Division of Varian  
San Carlos, California 94070

*Eimac*



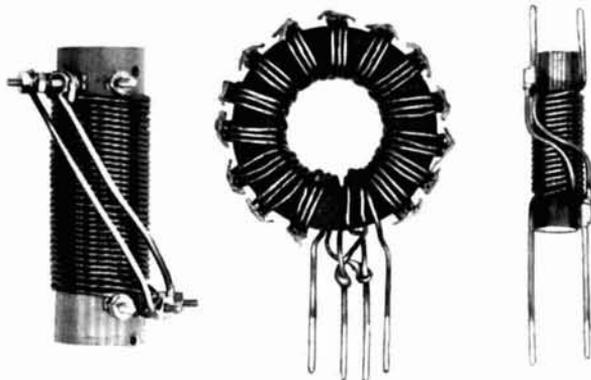

Three wideband baluns which are suitable for use in the hf spectrum. To the left is a simple air-core balun wound on a plastic form; in the middle is a toroid-core balun; to the right is a ferrite-slug balun.

## broadband antenna baluns

A comparison of the impedance characteristics and power-handling capability of three popular types of broadband 1:1 baluns

William I. Orr, W6SAI, 48 Campbell Lane, Menlo Park, California

A balun is an electrical transformer for converting a balanced system to an unbalanced system or vice versa. They come in all shapes and sizes from the midget "ladder transformers" for television receivers to giant ferrite transformers for multi-kilowatt broadcast stations. The baluns that interest the radio amateur are used to match unbalanced coaxial transmission lines to balanced antenna systems.

An inexpensive narrow-band balun may be made with a quarter- or half-wavelength of coaxial line as shown in fig. 1. These baluns will cover a single amateur band, but they are of little practical interest if you're using a three-band beam antenna or multi-band dipole.

Various forms of ferrite toroid baluns that promise broadband operation have appeared recently,<sup>1</sup> as well as a simple broadband coaxial-wound balun.<sup>2</sup> This article discusses some of the more common ferrite balun transformer designs and describes a simple and inexpensive **air-core balun** that works well over the 7- to 30-MHz range.

### the 1:1 balun transformer

The 1:1 balun is well suited to the problem of feeding a split-dipole radiator with an unbalanced coaxial line. If this important balancing function is left out, it may cause


transmission-line radiation and can result in confusing SWR readings when attempts are made to measure the characteristics of the antenna system. For the greatest benefit, a balun should cover the range of 3.5- to 30-MHz so that it can be used with three-band beams as well as "trapped" 80- and 40-meter doublets. Useful, too, are baluns which cover the "tribander" antenna range of 14 to 30 MHz.

Sophisticated ferrite toroid baluns have been built which span the range of 50 kHz to 500 MHz,<sup>3</sup> and simple linear-coil versions of these exotic devices may easily cover the 80-through 10-meter bands. A well-built 1:1 balun is a noncritical device that provides near-unity transformation; it may be used with either 50- or 70-ohm coaxial transmission lines and most common antennas.

winding) inductor, and may be compared to a two-wire transmission line wound in a coil with an extra balancing winding provided to complete the magnetizing-current path. In effect, the balun is comparable to a transmission line transformer having a 1:1 ratio over the higher-frequency region of operation and to a 1:1 coupled transformer at the lower frequencies.

High-frequency response of the coil balun is largely limited by the distributed (shunt) capacitance and coupling between the windings (both of which are quite critical). The low-frequency response is determined by the primary inductance of the coupled transformer.<sup>4</sup> The most difficult part of the balun transformer to adjust is the distributed capacitance of the windings. Much effort must be expended to reduce this to a minimum value

**fig. 1. Narrow-band balancing transformers may be made of lengths of coaxial cable. The upper design provides a 1 to 1 balanced transformation and the lower design, a 4 to 1 transformation. Baluns provide good balance over approximately 0.05% of the operating frequency.**

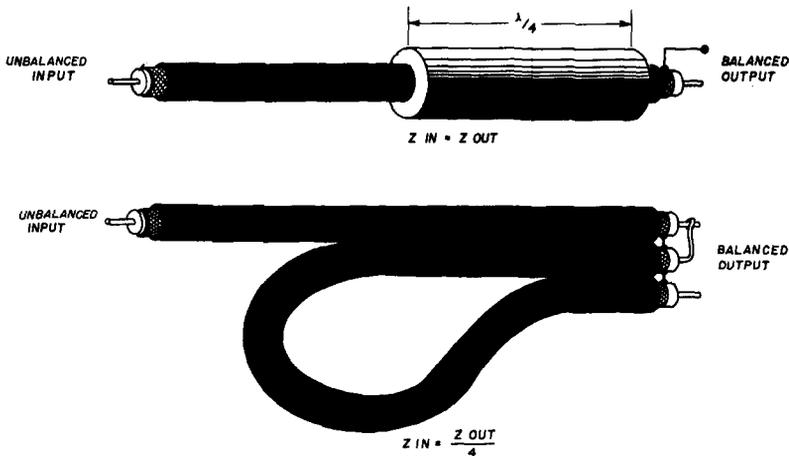

There's more to the balun than meets the eye however, and practical construction information is sorely lacking for these interesting devices. Some simple designs are shown in this article which work well over the h-f range and can be built easily and inexpensively in the home workshop.

The schematic of a 1:1 coil balun is shown in fig. 2. The balun consists of a trifilar (three-

without destroying the interturn magnetic coupling.<sup>5</sup>

A coil balun may be constructed with an air core, and designs of this type work well. However, the number of turns required for good low-frequency response are large, and sufficient distributed capacitance exists in a simple balun of this type to limit the range of proper operation to a frequency span of

3 or 4 to 1. If a high-permeability ferrite core is used in the balun, fewer turns are required on the trifilar winding for a given low-frequency response. This reduces the overall distributed capacitance of the winding and improves high-frequency response. A frequency range of 10 or 20 to 1 is common with a balun of this type. The ferrite core, however, is power limited, especially at the high-frequency end of the operating range.\*

### the ferrite-core toroid balun


Toroid baluns have been described several times, and variations of the basic design shown in **fig. 2** are available in kit form. Several experimental toroidal baluns were built using available information. An expanded Smith-Chart plot\*\* of one of the best designs is shown in **fig. 3**. The chart illustrates the reactive and resistive components of the balun when terminated in a 50-ohm load and examined with an rf impedance bridge. To plot the chart, a frequency run was made with a signal generator driving the balun through an rf impedance bridge; the bridge readings are transferred to the Smith-Chart. A typical test set-up is shown in **fig. 4**.

The curve for the toroid balun shows that it is not a perfect 1:1 transformer. It presents a termination of 49 ohms at 3.5 MHz and gradually rises to 55 ohms at 14 MHz. Thereafter, the impedance drops to about 44.5 ohms at 29.7 MHz. This balun presents considerable reactance at the lower frequencies,

\* According to Sosin,<sup>4</sup> the bandwidth is limited at the low-frequency end by the low value of shunt inductance, and at the high-frequency end by a low-pass pi network formed by spurious shunt capacitance and leakage reactance. In order to keep the leakage reactance small, the winding must have a minimum number of turns. Consequently, the ferrite core is very heavily loaded. The power rating of the core depends on the cooling effectiveness, and the temperature rise of the core might become quite high. As the working temperature is increased, a runaway temperature is reached where operation is impractical because of unbalance; ultimately, the balun will be destroyed.

\*\* The Smith Chart used for this series of tests is an expanded type normalized at 50 ohms. The resistive component of the measured impedance falls along the X-axis and the reactive component falls along the Y-axis in the normal manner. (General Radio #5301-7561-NE).


**fig. 2.** A three-winding transformer provides a balanced 1-to-1 transformation (A). Note that the center winding acts as the balancing coil, completing the magnetizing current path. Connection of balancing winding to transformer winding at the input end must be taken as ground (point A) to preserve optimum balance. The three-winding balun may be used with a toroid core (B).

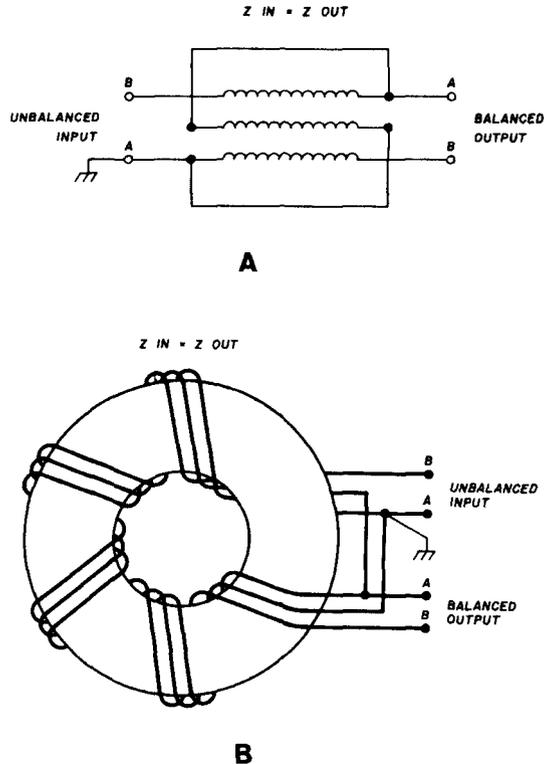

resulting in an SWR greater than 1.1 at frequencies below about 19 MHz. Above 19 MHz, balun reactance is slight. This chart shows that, when terminated in a "perfect" 50-ohm load, the balun will introduce a slight SWR (greater than 1.1 but less than 1.35) on a transmission line at frequencies below 19 MHz. Not indicated on the chart is the fact that the balance of the device begins to deteriorate above 30 MHz or so.

In summary, then, a ferrite toroid balun of this design is a good performer above 19 MHz and a fair performer down to above 3.5 MHz. The quality, or excellence of the balun, of course, is a subjective thing and an arbitrary SWR figure of 1.2 was chosen as a practical limit defining balun excellence. A **really good** balun, however, can plot a curve falling with-

fig. 3. Expanded Smith Chart shows response of ferrite-toroid balun plotted with respect to 1.2:1 and a 1.1:1 SWR circles super-imposed on the chart. Balun consisted of 15 turns number 14 wire bifilar wound on 2.4" diameter, Q-1 toroid. Balun was optimized at h-f end of its range by squeezing and adjusting the spacing between adjacent turns and lacing the windings in place.

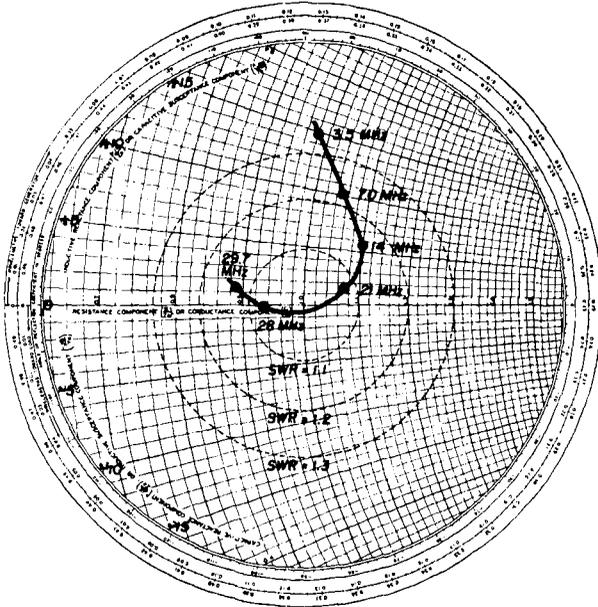

in the 1.2 SWR circle on the expanded Smith Chart.

Not shown on the chart is the difficulty I encountered in constructing a toroid ferrite balun capable of this degree of performance. Neatness of construction is a virtue, and the coupling, or spacing, between each turn and between the trifilar groups of turns is very critical. In the photograph you can see that each trifilar group of wires is tied in place with a length of lacing twine. Unhappily, if the trifilar groupings are too loose on the core, the high-frequency performance of the balun suffers. If, on the other hand, the lacings are too tight and the turns too tightly compressed together, the high-frequency performance suffers equally as before.

I spent a considerable amount of time adjusting the balun windings while it was connected in the measuring circuit. Only by juggling the windings while watching the rf bridge readings was I able to achieve a satisfactory transformation ratio and acceptable


bandwidth. The experience was exasperating in the extreme, and I reached the conclusion that it was virtually impossible to construct a toroid ferrite balun of this type with acceptable characteristics without the assistance of an rf bridge.

The coupling between trifilar windings was very critical and had to be hand-adjusted to a fine degree to make the balun perform above 20 MHz or so. Regretfully, the toroidal construction was cast aside in favor of other designs that could be easily built in the home workshop.

### the ferrite-slug balun

I next turned my attention to the ferrite slug balun, a number of which are available commercially in inexpensive versions. A simple trifilar balun was wound on a one-half-inch diameter ferrite core;\* measurements were taken and plotted on an expanded Smith Chart as shown in fig. 5. The slug balun performed well over the 7- to 50-MHz range (within the 1.2 SWR circle on the chart), and

fig. 4. Balun tests were conducted with an r-f bridge and balanced load. The r-f bridge was compensated for h-f response to 50 MHz. Resistance and reactance measurements were made directly from the bridge and compensated for system errors.

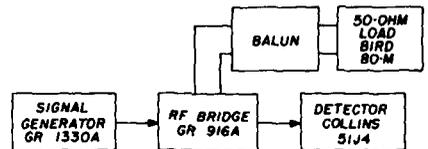

seemed acceptable at 3.5 MHz where the plot fell just outside the 1.3 circle.


Wire spacing on the slug core did not seem to be nearly as critical as on the toroid form, and a neat, closewound coil performed very well. Anchoring the winding proved to be a problem; coating the wires with coil dope, Krylon or nail polish increased the distributed capacitance of the balun and disturbed the

\* The Newark Electronics Corporation Industrial Catalog number 68 carries a partial listing of Indiana General Corporation Ferrites. A suitable 1/2-inch diameter rod is the Indiana General CF-503 which is 7-1/2" long. (Newark part number 59F-1521). The ferrite may be nicked with a file around the circumference at the desired length and broken with a sharp blow.

transformation above 20 MHz. The solution was to coat the end turns and leads of the assembly and to leave the winding free of adhesive material.

After I had built a few ferrite slug baluns and measured them on the rf bridge, they were tested with a transmitter and a dummy load. The balun with an Indiana General CF-503 slug core readily accepted 700 watts of power up to 14 MHz—the core became only slightly warm after three minutes of operation. Above 20 meters, however, core losses went up, and it was necessary to derate the

fig. 5. Chart shows plot of ferrite-slug balun with respect to 1.2 and 1.1 SWR circles. This simple, compact balun performed well over the 3.5- to 50-MHz range and the plot fell within the 1.2 SWR circle over the range from 7 to 50 MHz. The balun consisted of 6 turns of number 14 wire on a Q-1 slug and was patterned after a design by W8FYR. This balun provided the widest frequency response of all the baluns tested but was power limited at the h-f end of the range.

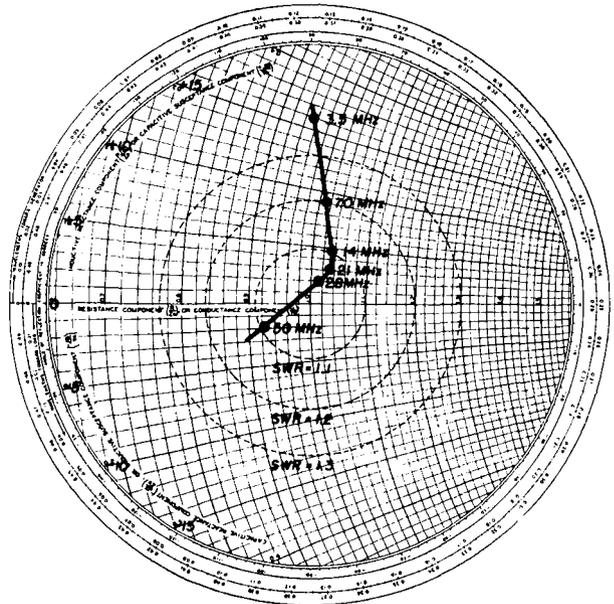

balun to 500 watts at 21 MHz and 400 watts at 28 MHz. I didn't run any power tests at 50 MHz, but I estimate that the balun is good for 100 watts or so at this frequency. With intermittent voice ssb operation, the power capability could probably be doubled with safety.

### the air-core balun

Because of the power limitation and core cost of the ferrite baluns, I decided to explore the capabilities of a simple air-core balun. A suitable design evolved after several failures, and the characteristics of a prototype balun were plotted on an expanded Smith

Chart (fig. 6). The balun plot fell within the 1.2 SWR circle over a range of 9 to 29.7 MHz and was just inside the 1.3 SWR circle over the 40-meter band. The power capability of the balun was better than 1000 watts at all frequencies within the range of operation. Ease of construction, low cost and simple adjustment plus the improved power capability emphasize the fact that this type of balun is well adapted to home construction.

### practical balun construction

A practical air-core balun for the h-f range


is shown in the photograph. It consists of three coils of number 14 Formvar\* coated wire, ten turns to each coil. The windings are placed on a 4-inch long piece of 1-1/16-inch outside diameter polyvinyl-chloride (PVC) plastic tubing. This gray, plastic material is commonly used in most areas of the United

\* *Formvar* (polyvinyl formal-phenolic resin) coating is superior to plain enamel because of its greater dielectric breakdown strength. *Nyclad* (polyvinyl formal with nylon overcoat) wire has even greater dielectric breakdown strength. It is manufactured by Belden Manufacturing Company. *Nyform* is another trade name for this coating (Anaconda Wire & Cable Company).

States for water pipe, and a small chunk of it can be obtained from your local plumber at little or no cost. The trifilar winding is simple to construct after you get the hang of it, and expertise is readily gained after an experimental winding is made.

Three pieces of wire about 4-feet long are

**fig. 6.** Chart shows plot of inexpensive air-core balun shown in the photograph. While the frequency response is not as great as that of the ferrite-slug balun, the less expensive air-core balun works well over the range of 3.5 to 29.7 MHz. Response falls within the 1.2 SWR circle over the range of 9 to 29.7 MHz. Balun consisted of ten turns of number 14 Formvar insulated wire on a piece of 1-1/16" piece of plastic pipe, connected as shown in fig. 2A.

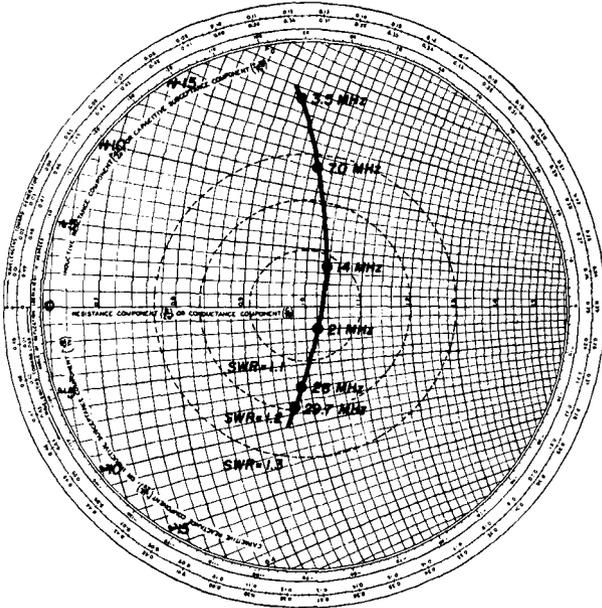

cut and smoothed to eliminate bumps and kinks. The wires are placed parallel to one another and the far ends held in a vise. The near ends are scraped clean of insulation and wrapped around 4-40 bolts placed in the PVC form as anchor points. The three wires are then wound side by side on the form as one, until ten trifilar turns are on the form. If you wind carefully and keep reasonable tension, the coil will adhere closely to the form. The other ends of the windings are scraped clean and attached to the proper bolts as shown in the illustration.

The last step is to interconnect the center, or balancing winding. As you can see in the

photograph, the center coil cross-connects the outer coils. The terminal connections are reversed in physical position from one end of the coil to the other, and the proper balancing connection may be made by connecting the ends of the center winding to the outer coil winding at each end of the bifilar assembly. Neatness is important, and an evenly wound coil with the turns just touching each other will provide greater operational bandwidth than a haywire winding with uneven spots or lumps in the wires. Once the cross connections have been made, the assembly may be held in place by a few drops of epoxy cement, Krylon, or coil dope placed at the ends of the windings.

Note that the input terminals of the balun are non-symmetrical from an electrical point of view. That is, point A at the input end is taken as ground. The free winding, point B, is hot. At the output end, of course, the terminals are balanced with respect to ground. Transposition of the input connections will degrade balancing action. Either end of the unit may be used as the input, of course, provided point A is taken as ground.

### encapsulating the balun

Air-core baluns of the types discussed here are sensitive to nearby capacitance, and some thought must be given to the problem of protecting the windings from sun, rain and weather without upsetting their electrical characteristics. I tried to encapsulate the baluns in epoxy resin, but the resulting increase in distributed capacitance degraded balun performance to a serious degree at the higher frequencies. A simple solution I finally arrived at was to place the balun in a cylindrical case made from a 2-1/2-inch diameter polyethylene "squeeze bottle" that once held hair shampoo. I cut the ends from the bottle and put in plywood discs with small wood screws. The balun was suspended inside the bottle by the wire leads which were connected to 10-32 bolts placed in the plywood discs. When the unit was completed, it was coated with epoxy resin to waterproof the joints.

A subsequent visit to the local plumber disclosed that there was a "welding" torch available which "welded" PVC pipe with a blast of hot air, using a strip of PVC material

as plastic solder. Accordingly, a length of 2-1/4-inch outside diameter PVC pipe was cut to form an outer jacket for the balun. Two end discs were cut from a sheet of the same material. Terminals were placed in the discs, and the balun was wired in place between the terminals. The assembly was then slipped within the larger PVC pipe and "welded" by the plumber with his unique hot-air torch. The result was a neat, compact, waterproof balun assembly ready to mount at the feed point of a beam antenna or hung from the center point of a dipole!

### using the balun with your antenna

The air-core balun makes a fine balancing device for use between the coaxial line and the split dipole element of a three-band beam antenna. While nominally designed for a nonreactive 50-ohm load, the balun will happily accept the degree of mismatch presented by the typical amateur antenna. Most three-band beams using trapped elements present a different picture to the transmission line on each of the amateur bands, and rarely is this a "pure" 50-ohm termination.

Typically, such an antenna represents a frequency-sensitive, reactive load whose resistive component falls to about 25 ohms on 14 MHz, 35 ohms on 21 MHz and 45 ohms on 28 MHz. Because of the complex interaction of traps and elements, the chance of achieving a nonreactive 50-ohm load at more than one frequency in one of the three amateur bands is rather remote.

No matter; the operation of the antenna is not dependent to any great degree upon feed-line match provided the SWR at the transmitter end of the line is not too great to prevent proper transmitter loading. It is permissible, therefore, to use the balun directly with a multi-band beam without additional matching devices other than those normally associated with proper antenna operation. Therefore, the balun may be used with varying beam terminations, possibly over the range of 15 to 100 ohms or so, while still providing worthwhile balancing and feedline isolation.

### low-frequency air-core baluns

During the investigation of air-core baluns, two low-frequency units were built that may

be of interest to experimenters. The first covered the range of 2.5 to 15 MHz and consisted of seven trifilar turns of number 14 Formex wire (21 total turns) wound to a length of 1-3/4-inches on a piece of 2-3/8-inch diameter PVC pipe. The design center of this balun was 8 MHz, and the impedance plot fell within a 1.2 SWR circle on the expanded Smith Chart over the range of 3.4 to 15 MHz.

A second balun covered the range of 0.54 to 2.5 MHz. This balun was composed of eighteen trifilar turns of number 14 Formex wire (54 total turns) wound to a length of 3-5/8 inches on a length of 3-1/2-inch diameter PVC pipe. Design center was 1.2 MHz, and the impedance plot fell within a 1.2 SWR circle on the Smith Chart over the range of 0.7 to 2.1 MHz. This balun is well suited for 160-meter work, while the previously mentioned unit is designed for 80- and 40-meter operation. As it turned out, the smaller unit worked well on the 20-meter band as well and was subsequently used on a two-band 40- and 20-meter beam.

### conclusion

The simple air-core balun is the easiest to make and adjust and the least expensive of the three balun types discussed in this article. It is capable of working at the full amateur power limit over its design range and greatly simplifies the operation and adjustment of any antenna system. Try one and see; you'll like it!

I'd like to thank Willie Sayer, WA6BAN, for his help in the preparation of this article and for his contribution of the hundreds of feet of copper wire that went into various unsuccessful designs along the way!

### references

1. Turrin, "Broadband Balun Transformers," *QST*, August, 1964, p. 33.
2. Orr, "A Broadband Balun for a Buck," *CQ*, February, 1966, p. 42.
3. Ruthroff, "Some Broadband Transformers," *Proceedings of the IRE*, Volume 47, August, 1959.
4. Sosin, "Wideband Technique Applied to HF Transmitter Station Equipment," *Proceedings of the IEE* (England), August, 1963.
5. Maurice, "Very Wide-Band Radio-Frequency Transformers," *Wireless Engineer* (England), June, 1947.

**ham radio**

# TRAP MASTER

Select Quality....  
...Specify **Mosley**

## Classic 10-15

A new beam for 10 and 15 meters. Revolutionary broad band capacitive matching.\* Full power rated. Weatherproof metal encased traps. Lightweight: 27.5 lbs. assembled. May be stacked with 20 and/or 40 meter beams.

\*(Pat. Pend.)

## Classic 33

Hard working for extra gain on 10, 15 and 20 meters. Wider element spacing and improved clamping. Broad band capacitive match.\* Full power rating. Weatherproof traps for constant frequency stability. \*(Pat. Pend.)

## TA-33


Excellent results for full ham bandwidth. Full power rated for 10, 15, and 20 meters. Strengthened center sections of the 28' maximum length elements. Weatherproof traps for constant frequency stability. May be converted to 40 meters.

## TA-33 Jr.

A low power beam with "authority." Rated at 300 watts AM/CW, and 1000 watts P.E.P. on SSB. May be converted to MP-33 for higher power rating. Max. element length is 26' 8"

For more information on these, or any of Mosley antennas see your nearest authorized Mosley dealer, or write.

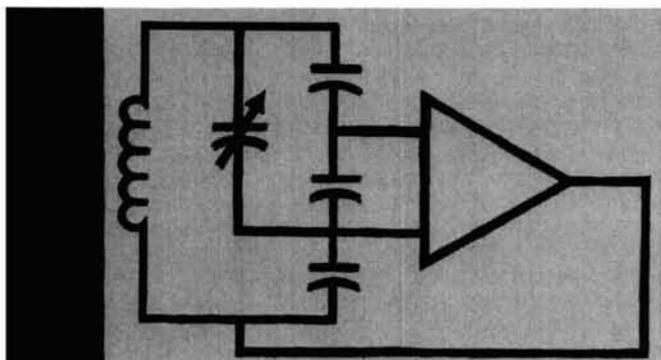Dept. 150  
**Mosley Electronics, Inc.** 4610 North Lindbergh Blvd. Bridgeton, Mo. 63042



## stable transistor vfo's

A discussion of  
the Vackar  
and Seiler  
oscillator circuits

Jim Fisk, W1DTY, RFD 1, Box 138, Rindge, New Hampshire 03461

There has been a lot of interest in the Vackar oscillator lately because of a recent article<sup>1</sup> describing its many merits. Although there hasn't been too much information on this circuit in the American magazines, a wealth of information has been published in the **RSGB Bulletin**. In addition, there have been a number of amateur articles which have used a somewhat similar circuit—the Seiler oscillator.

Actually, both the Vackar and Seiler circuits are closely related to the Colpitts oscillator. The Vackar, named after its inventor, Jiri Vackar, a Czechoslovakian, was originally described in 1949.<sup>2</sup> The Seiler circuit, although almost forgotten, was described in **QST**<sup>3</sup> in 1941. Both of these circuits were designed to minimize loading on the tuned circuit, thereby increasing stability.

Most VFO's in use today use the series-tuned Colpitts or Clapp circuit; interestingly enough, Clapp based his design on the work of Vackar.<sup>5</sup> You can see from **fig. 1** that the Colpitts, Clapp, Vackar and Seiler circuits are very closely related. The Colpitts circuit, of

course, is the father of them all. Seiler added a third capacitor in the divider to lessen the load on the tuned circuit. Vackar did much the same thing, but put a variable capacitor across a portion of the tank circuit to increase the tuning range. Clapp went on to simplify the basic Vackar circuit.

Since the Colpitts and Clapp circuits have been covered quite well in the amateur literature,<sup>17-24</sup> the discussion here will be limited to the Seiler and Vackar circuits.


### the Seiler oscillator

Until Seiler's article in 1941, most VFO's used the Hartley or high-C Colpitts circuit. The Seiler design permitted the amateur to


voltage regulation, and by 1941 standards, the stability was very good.

One of the big advantages of the Seiler circuit is the large capacitors which are placed across the active device—in this case a transistor. These large capacitors tend to swamp out any reactive changes in the transistor and limit the harmonic output, thereby increasing frequency stability. Since capacitors C2 and C3 are usually much larger than C1 or the variable capacitor (Cv) in the Seiler oscillator, the frequency of oscillation may be simplified to:

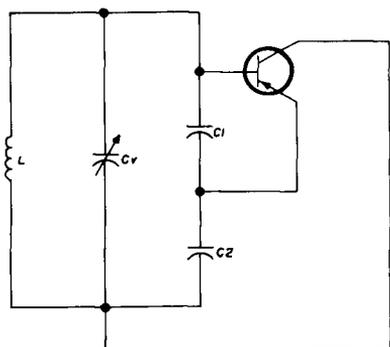
$$f_{osc} = \frac{1}{2\pi \sqrt{L(C1 + Cv)}}$$




COLPITTS

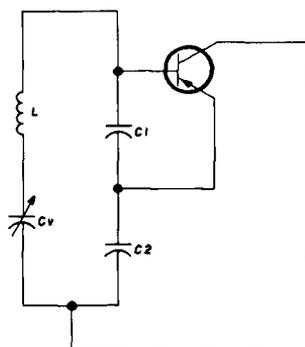

CLAPP

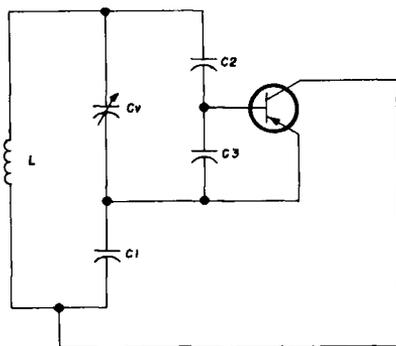

VACKAR

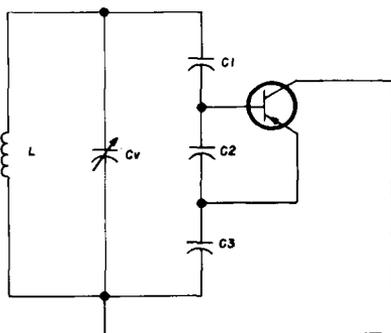

SEILER

fig. 1. Circuit configurations of the Colpitts, Clapp, Seiler and Vackar oscillators. The Clapp, Seiler and Vackar circuits are derivations of the basic Colpitts circuit.

use a relatively low-C circuit that provided high stability and a tuning range of 1.8:1. A 6F6 was used in the original article, without

Several vacuum-tube versions of the Seiler oscillator have appeared in the amateur-radio magazines, but in most cases the designers


weren't aware that their circuit was an extension of W8PK's original design. In at least one case, the author called his circuit a, "ground-plate Colpitts type."<sup>6</sup>

To my knowledge, the first transistorized version of the Seiler oscillator was W3JHR's "synthetic rock" which was published in *CQ* in 1963.<sup>7</sup> This circuit was extremely popular and subsequently appeared in amateur magazines in England, Germany and South America. W3JHR used an old ARC-5 transmitter as the basis for his VFO; he cut the unit down and used the original variable capacitor and tuning coil to cover the frequency range from 4.9 to 6.1 MHz. Although only the oscillator stage is shown in **fig. 2**, he included a 2N384 emitter-follower buffer for isolation from the next stage.

K9ALD described another transistorized Seiler oscillator for ssb in 1964<sup>8</sup> and claimed exceptionally stable results. His oscillator, designed to cover the range from 4.95 to 5.6 MHz, is shown in **fig. 3**. Because of the relatively low-capacitance characteristics of the 2N2219, the feedback capacitors from base to emitter and from emitter to ground are smaller than those which are usually used in the Seiler oscillator. However, drift was negligible—about 25 Hz after warmup, and that was measured with a digital counter!

Don't let that 200-pF capacitor in series with the variable capacitor confuse you. It


**fig. 2.** W3JHR's "synthetic rock"—a Seiler oscillator—tunes from 4.9 to 6.1 MHz with tank components from an old ARC-5 transmitter.

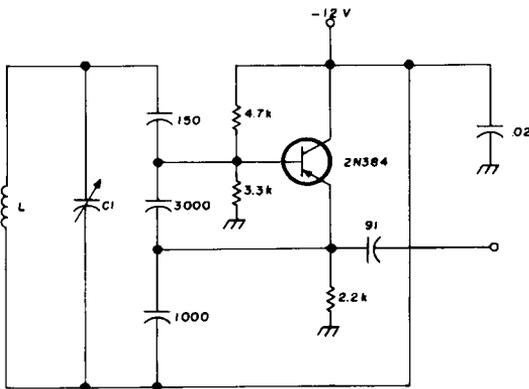

was used to set up the bandspread range of the variable capacitor.

Another transistorized Seiler oscillator was described by G3BIK,<sup>9</sup> although he mistakenly identified it as a Vackar. This oscillator used a 2N706 and covered the range from 1.8 to 2 MHz (**fig. 4**). G3BIK reported exceptional stability with this circuit—a change in voltage from 12 to 6 volts results in a 100-Hz change in frequency. He did experience some diffi-

**fig. 3.** This Seiler oscillator, designed by K9ALD, tunes from 4.95 to 5.6 MHz. Total drift is reported to be 25 Hz. L1 is 2-1/2 turns number 16 on a 1-1/4" ceramic form. Variable capacitor C<sub>V</sub> is a 100-pF variable in parallel with an 82-pF silver mica.

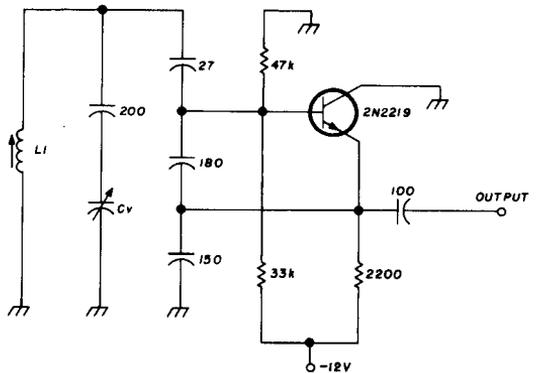


culty with temperature drift, but cured it by using a high-Q coil and silver-mica capacitors and by putting the complete circuit in an enclosed metal box. This doesn't reflect on the Seiler oscillator though—it's good construction practice with **any** VFO!

Since all the amateurs who have built transistorized Seiler VFO's have claimed such extraordinary results, I thought that an FET would make a good thing better. I was right; the results with the circuit shown in **fig. 5** were nothing short of remarkable! When the circuit was breadboarded on a piece of Vector board, drift was unmeasurable, even with a fresh spring breeze blowing through the window. When the supply voltage was varied from 22 to 9 volts, total drift was less than 1 kHz. This could be cured quite easily by putting a zener diode in the circuit.

The total current drain of this circuit is a little over 4 mA, so a couple of 9-volt tran-

sistor-radio batteries would power it for many months of operation. The output is constant within 2 dB over the complete tuning range, 3.49 to 4.01 MHz, so it makes an ideal if driving source. When it's keyed, there is no chirp or drift; it sounds like it's crystal controlled. It far surpasses any VFO circuit I've

fig. 4. G3BIK's Seiler oscillator covers the frequency range from 1.8 to 2.0 MHz. L1 is 65 turns of number 30 on a 5/8" diameter form.

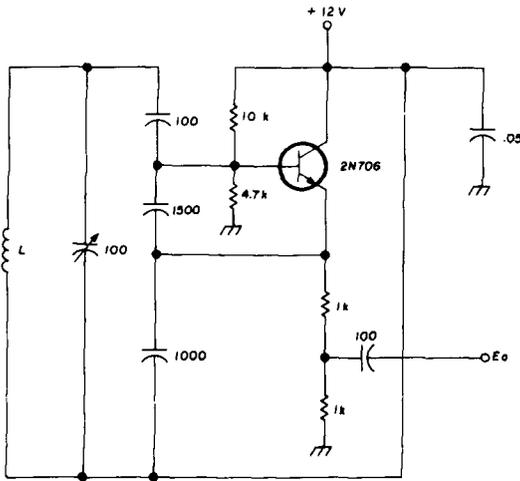

ever built, transistor or vacuum tube.

### Seiler design

The design of the Seiler circuit closely parallels the design procedure used for the basic Colpitts oscillator.<sup>10</sup> First of all, choose a transistor that has an  $f_T$  several times great-

er than the frequency you're interested in. Then design a bias network which will put the transistor in the linear operating range. Choose a value of tank tuning capacitance ( $C_T$ ) from the following formula:

$$C_T = Q/6.28fZ$$

Where  $C_T$  is the sum of  $C_v$  and  $C1$  (fig. 1);  $f$  is the center of the desired frequency range;  $Z$  is the impedance of the tank circuit at resonance; and  $Q$  is the tuned-circuit  $Q$ .

For maximum power transfer from the transistor, the tuned-circuit impedance should equal the transistor output impedance and may be approximated from:

$$Z = V_{CE}/I_C$$

Where  $V_{CE}$  is the voltage between the collector and emitter of the transistor and  $I_C$  is the collector current.


Choose a value of  $Q$  as high as possible, because oscillator stability is very closely related to tank-circuit  $Q$ . For all practical purposes, the  $Q$  of the tank will be determined by the inductance you select, so use the best coil you can. If you have lots of room, air-wound coils are very good; if you're interested in miniaturization, try a ferrite toroid. In any event, when you're calculating for tuned-circuit capacitance, use a value of  $Q$  that is attainable in practice.

After you've calculated the total equivalent tank-circuit capacitance that you need, you can choose the coil to resonate in the center of the desired tuning range.

The values of the two large capacitors in the capacitor divider network,  $C2$  and  $C3$  (fig. 1), are not critical. However, they should be

fig. 5. Stable Seiler oscillator using an FET. The tuning range of this circuit is 3.49 to 4.01 MHz. L1 consists of 44 turns number 30 on a 1/2" ferrite core (Amidon T-50-2\*).

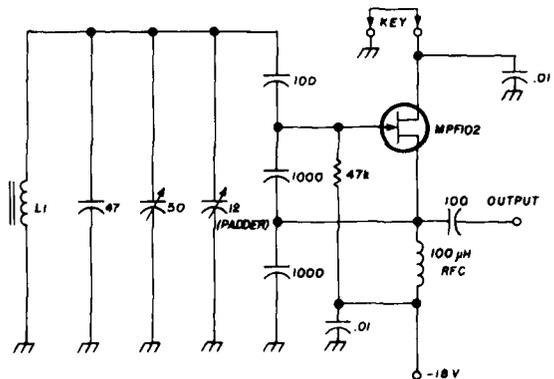\* Amidon Associates, 12033 Otsego Street, North Hollywood, California 91607 (formerly Ami-Tron Associates). T-50-2 ferrite cores are 45c each; minimum order, \$1.00. Add 25c for packing and shipping.




quite a bit larger than C1 or the variable capacitor. Typical values range from 150 pF up to several thousand picofarads, depending on the frequency of interest and the gain of the transistor. The rule of thumb to follow here is to use the largest capacitors that will

bench, you'll have a stable VFO that tunes just where you want it to.

### the Vackar oscillator

The Vackar circuit was another solution to the same problem—to reduce the load on the

fig. 6. Transistorized Vackar oscillator designed by L. Williams, a British SWL. C1 is a 30-pF trimmer in parallel with a 75-pF air variable.

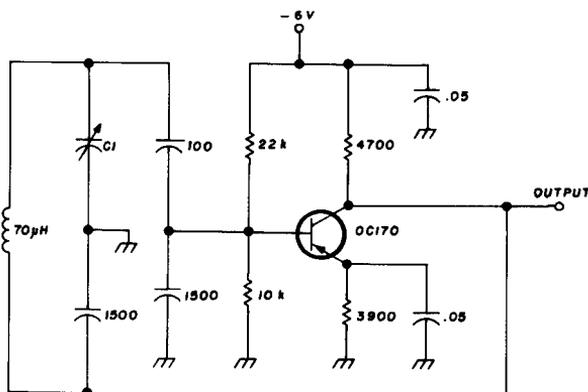


still result in oscillation. If a high-gain transistor is used, these two capacitors are usually equal. If a relatively low-gain device is used, it may be necessary to set the ratio of C3 to C2 less than the current gain of the transistor.

The variable capacitor,  $C_v$ , usually consists of a variable in parallel with a padder. The padder can be adjusted so that the variable will cover the desired frequency range. Capacitor C1 determines the amount of drive to the transistor and is relatively small. The best approach here is to start off with about 100 pF at C1 and reduce it until the oscillator ceases to function. Add about 50% to this value as a safety factor for the final value of C1.

This design method will put you in the right ball park with a working oscillator. All that is left is to set the tuning range of the variable capacitor. This is best accomplished on the bench. First, put in a variable that you think will do the job and measure the frequency with your grid dipper. If the circuit covers the frequency range you want, but the tuning range is too broad, reduce the size of the variable and put in some padding capacitors. If the range is about right, but the center frequency is off, change the size of the inductor. With a few minutes work on the

tuned circuit. In the Vackar, the transistor is again connected across a relatively low impedance and is very loosely coupled to the tuned circuit. This oscillator will tune over a frequency range of at least 2.5:1; the output can be made absolutely constant, and, according to Jordan,<sup>1</sup> it has the greatest inherent stability of any known oscillator configuration except for a design with independent

fig. 7. Vackar oscillator design by G5BB for use on 21 MHz. L1 is 19 turns number 22 on a 1/4" form. C1 is a 35-pF air variable in parallel with a 30-pF trimmer.

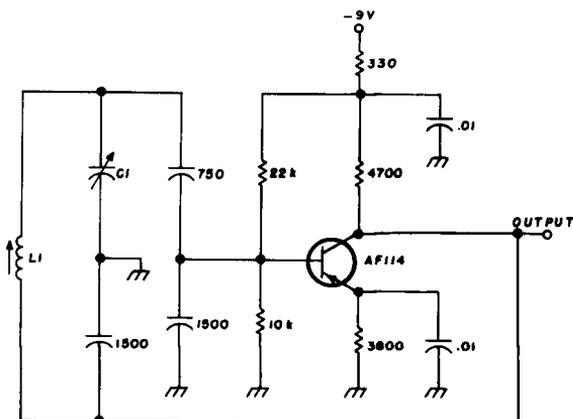

external load feedback. Those are pretty strong words!

Although the Vackar circuit was originally described in 1949, and publicized, at least in this country, by Clapp in 1954,<sup>4</sup> it has remained virtually unused. W9IK described a vacuum-tube Vackar oscillator built by W9TO<sup>11</sup>, and a design appeared in **Radio and TV News**,<sup>12</sup> but that was over ten years ago.

The Vackar oscillator was resurrected when the first transistorized version was published in the **RSGB Bulletin** in July, 1966.<sup>13</sup> This circuit, shown in **fig. 6**, tunes over the frequency range of 2 to 2.5 MHz. The designer reported the prototype "will stay zero beat with a crystal frequency standard for hours."

This article aroused considerable interest in the Vackar oscillator. G3RAE reported<sup>14</sup> that he modified the circuit shown in **fig. 6** for use as a 465-kHz BFO. He increased the inductance to 460 microhenries and changed the tuning capacitor to 100-pF in parallel with a 270-pF fixed capacitor. All other values were the same as shown in **fig. 6**.

Shortly thereafter, G5BB described another transistorized Vackar, this one designed for 21 MHz<sup>15</sup> (**fig. 7**). He experienced some difficulties with temperature drift, but felt they could be cured by putting the circuit in a die-cast box. I suspect that replacing the slug-tuned coil with an air-wound inductor would also help.

The latest transistorized Vackar oscillator was described by G. B. Jordan in the February, 1968 issue of **The Electronic Engineer**.<sup>1</sup> He has done a lot of experimental work with

the Vackar oscillator and found it to be an extremely stable circuit.


Jordan's circuit, shown in **fig. 8**, is particularly interesting since it was designed to tune from 26.9 to 34.7 MHz, both the CB and 10-meter bands. The output amplitude varied 1.5 dB over the frequency range, and the temperature drift was linear from +20 to +100°F. When he compensated the circuit with N750 capacitors at C1 and C3, temperature drift dropped to 10 Hz per degree F. Further compensation would reduce drift to negligible amounts.

Since I had such good luck with the FET version of the Seiler oscillator, I tried the same thing with the Vackar (**fig. 9**)—again, the results were fantastic. Stability was at least as good as the Seiler; drift was negligible, and the keyed note was crystal clear. I went on to add an FET buffer stage, a 2N706 driver and 1-watt 2N697 final. Still no chirps or drift.

Although this circuit was designed to cover the range from 3.5 to 4.0 MHz, by reducing the number of turns on L1, the same basic design could be used as a remote 5-MHz ssb VFO or 8-MHz VFO for vhf use.

Except for output amplitude stability, could detect **no** difference between the Seiler and Vackar circuits. Perhaps with a counter and a controlled temperature environment, different drift characteristics would be apparent, but in the typical amateur environment, there doesn't seem to be any detectable difference. As far as amplitude stability goes, with the Vackar circuit, the output level

**fig. 8.** This Vackar oscillator designed by G. B. Jordan tunes from 26.9 to 34.7 MHz. C1 is a 12-pF air variable in parallel with a 6.2-pF silver mica.

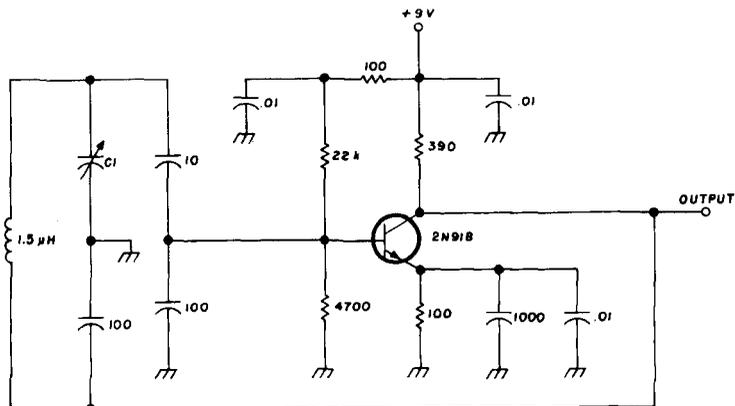


changed less than 1 dB over the range from 3.5 to 4 MHz; the Seiler output varied slightly less than 2 dB. This is a pretty small difference.

### Vackar oscillator design

As with the Seiler circuit, design of the Vackar is very closely akin to Colpitts design. Since the frequency of oscillation is determined essentially by the value of the variable capacitor and C2, these variable capacitors may be taken as the total tank-tuning capacitance. With this in mind, the tank-tuning capacitance and inductor are chosen by the

fig. 9. FET version of the Vackar oscillator is extremely stable. L1 is 48 turns number 30 on a 1/2" ferrite core (Amidon T-50-2)

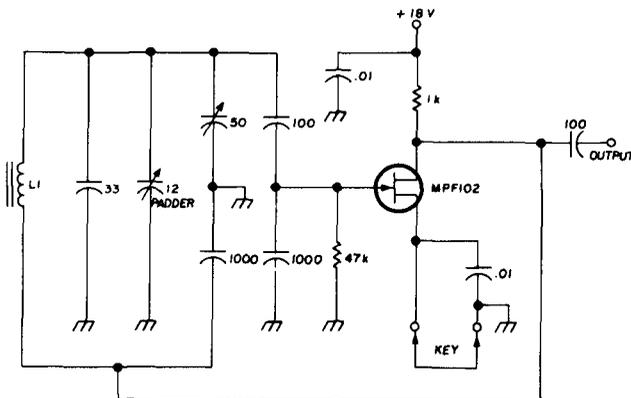

same method we used for the Seiler circuit. Capacitors C2 and C3 are found from the following formula:

$$C2 = C3 = 3000/f \text{ (MHz)}$$

According to Jordan, this formula yields about optimum oscillator stability compatible with other requirements. Capacitor C1 is adjusted so that the transistor operates essentially class A and is not driven into cutoff or saturation. In the circuit in fig. 8, with 10 pF at C1, the peak-to-peak voltage at the junction of the variable capacitor and the inductor was 1-1/2 times the B+ supply. This is a good rule of thumb to go by when you're designing an oscillator of this type.

Most of the authors who have described transistorized Vackar and Seiler VFO's have noticed a tendency for these circuits to oscillate at audio frequencies. Since the feedback loop from the collector to the base of the transistor is through the power supply, the base-bias resistors should be decoupled

from the collector resistor by a bypassed resistor as shown in fig. 8. Another precaution used by Jordan was to bypass the emitter for both audio and rf, although this may not be necessary.

### summary

Both the Seiler and Vackar circuits are similar in design and, from my experiences with the FET versions, similar in stability and output. The original tube-type Vackar circuit used high-C tuning whereas Seiler designed for low-C tuning; the high-C was provided

by a large trimmer across the main tuning capacitor. There **may** be some advantages to the Vackar circuit for very wide tuning ranges and some advantages to the Seiler when the low-C approach is used, but for amateur VFO's I doubt if there is any significant advantage with either circuit. With both of these circuits, stability is independent of the LC ratio, and not very dependent upon the transistor used.

All of the designers of the circuits shown here have indicated exceptional performance and stability with them. If you have done any experimenting along these lines, I would certainly like to hear about it—both of these circuits have been buried in the literature long enough. They seem ideal for transistor work, easy to design and a good choice the next time you're thinking about a new VFO.

### references

1. G. B. Jordan, "The Vackar VFO, a design to try," *The Electronic Engineer*, February, 1968, p. 56.

2. J. Vackar, "L-C Oscillators and their Frequency Stability," *Tesla Tech Reports*, (Czechoslovakia), December, 1949.
3. E. O. Seiler, W8PK, "Low-C Electron-Coupled Oscillator," *QST*, November, 1941.
4. J. K. Clapp, "An Inductance-Capacity Oscillator of Universal Frequency Stability," *Proceedings of the IRE*, March, 1948, p. 356.
5. J. K. Clapp, "Frequency-Stable LC Oscillators," *Proceedings of the IRE*, August, 1954, p. 1259.
6. M. Bernstein, W2PAT, "Amplitude Limiting for the VFO," *QST*, February, 1954, p. 24. (Seiler)
7. P. H. Lee, W3JHR, "A Stable Transistorized VFO," *CQ*, September, 1963, p. 25.
8. R. Taylor, K9ALD, "A Stable VFO for SSB," *73*, November, 1964, p. 10.
9. E. Chicken, G3BIK, "The Transistorized Vackar Oscillator," Technical Correspondence, *RSCG Bulletin*, September, 1966, p. 600.
10. J. R. Fisk, W1DTY, "Designing Transistor Oscillators," *73*, August, 1967, p. 66.
11. H. Woods, W9IK, "Vackar VFO Circuit," *QST*, November, 1955, p. 120.
12. R. J. Ropes, "A High-Stability Oscillator," *Radio and TV News*, June, 1957, p. 142.
13. L. Williams, "Transistorized Vackar Oscillator," Technical Topics, *RSCG Bulletin*, July, 1966, p. 453.
14. "Technical Topics," *RSCG Bulletin*, September, 1966, p. 586.
15. A. H. Bruce, G5BB, "21-MHz Vackar," Technical Topics, *RSCG Bulletin*, November, 1966, p. 718.
16. G. Bird, G3KOV, "Some Thoughts on Transistor Oscillators," *RSCG Bulletin*, January, 1967, p. 42.
17. W. B. Bernard, W4ELZ, "Let's Increase VFO Stability," *QST*, October, 1957, p. 40.
18. R. Cassey, ZL2IQ, "The Clapp Oscillator—and How!," *QST*, February, 1953, p. 19.
19. D. Crowell, K6RIL, "Stable VFO for HF or VHF," *73*, November, 1966, p. 46.
20. J. R. Fisk, W1DTY, "An FET VFO for 80 Meters," *73*, May, 1967, p. 56.
21. L. Howson, W2YKY, "Designing the VFO," *QST*, December, 1955, p. 35.
22. E. L. Klein, W4BR5, "A Toroidal VFO," *73*, April, 1967, p. 10.
23. J. Kyle, K5JKX, "VFO Circuits," *73*, October, 1961, p. 46.
24. O. J. Russell, G3BHJ, "Bandspreading the Clapp VFO," *QST*, October, 1954, p. 37.

**ham radio**

## some interesting aspects of increased solar activity

The present upswing in the sunspot number is expected to reach its peak in the very near future, probably at the end of 1968. It is commonly known that an increase in the number of sunspots will result in a marked over-all improvement of short-wave radio communications. However, during periods of increased solar activity, a prolonged deterioration of propagation conditions is very often experienced. This frequent disruption in radio communications is produced by gigantic flares that originate within the sun. Since the number of sunspots and the probability of solar flares are directly related, poor short-wave communications may be often expected during periods of high sunspot numbers.

A solar flare releases electromagnetic radiation, delayed by 8.3 minutes; cosmic-ray particles, delayed from 15 minutes to several hours; and magnetic-storm particles, delayed between 20 and 40 hours. The electromagnetic radiation is in the form of visible light, radio waves, ultraviolet rays, and x-rays; some of the immediate effects are occasional F-layer increase, frequent E-layer increase, and D-layer increase. Cosmic-ray and magnetic-

storm particles cause delayed effects, such as magnetic storms, ionospheric storms, auroras and a general increase in cosmic-ray radiation.

Besides the well-known "radio blackouts," solar storms produce an increase in earth currents which may cause drastic power-line voltage variations and over-heating of conductors. Power-line voltage fluctuations as much as 108 to 117 volts have been recorded. Corrosion and conductor vibration in areas of high ionization have also been correlated to magnetic storms. With the increase in system voltages and the increasing importance of system reliability, the nature of space plasmas and their associated phenomena on utility systems present a most important study for future utility system design.

As far as amateur radio is concerned, it must be borne in mind that a high sunspot period means "good DX conditions," but at the same time, you should anticipate severe and frequent short-term communications disruptions. The probability of an actual power-line failure is highly unlikely.

**Joe Mikuckis, K3CHP**



## the WB2EGZ six-meter mosfet converter

Construction details  
for a low-noise,  
high-gain converter  
for six meters  
that out-performs designs  
using vacuum tubes  
or bipolar transistors

Don Nelson, WB2EGZ, 9 Green Ridge Road, Ashland, New Jersey 08034

What's this we hear about MOSFET'S? Are they just a laboratory phenomenon? Do they burn-out with the flick of a finger? Are they priced for the idle-rich? Is their frequency response a limiting factor?

Never have I, as an experimenter, been so excited about a device as I am about the MOSFET (metal oxide semi-conductor, field-effect transistor). Immediate success with a simple six-meter converter has prompted my sharing a design which is almost certain to work for anyone with some talent for tinkering.





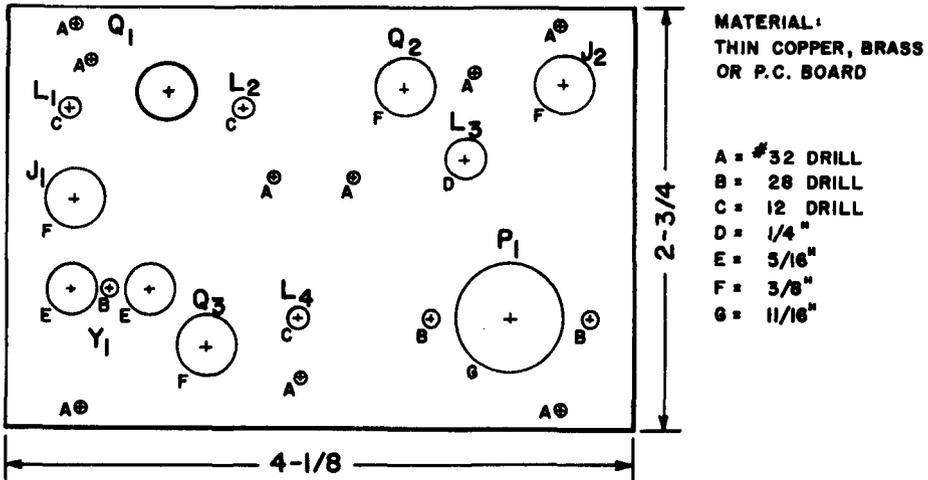


fig. 2. Chassis layout for the 50-MHz MOSFET converter. A full-size drill template is available from ham radio magazine for 25c and a self-addressed, stamped envelope.

but most hams will pay less.

The first stage, an rf amplifier, uses a 3N128 which is an N-channel triode (fig. 1). Both the input and output are tuned, but no neutralizing link is needed. The internal feedback capacitance is low enough so that the stage is stable as long as the source (antenna) and load (mixer stage) are properly matched. A trap may be needed to reject interference from Channel 2 if there is a station near you; the 58-MHz trap used in the **ARRL Handbook** Nuvistor converter would be suitable.

A typical noise figure for the 3N128 is 3.5 dB—this is in line with most good transistors, and superior to the Nuvistor. Evidently, the 3N128's I tried are even lower than the advertised figure. Because of the high gain of the 3N128 at 50 MHz, we can get away with only one rf stage. According to reports, the MOSFET is about ten times better than the bipolar transistor with respect to cross modulation and has 25 times the dynamic range. These characteristics compare favorably with tubes.

The mixer is an N-channel tetrode MOSFET, type 3N141. This is the most expensive transistor in the converter and costs \$1.55. While tetrodes were originally developed to improve the cross-modulation characteristic of the MOSFET in front-end circuits, the mixer application is equally rewarding.

The construction of the device is similar

to two MOSFET triodes in series. That is to say, the drain of one channel is internally connected to the source of the second channel. The gate of the second channel must be biased positive for proper operation by the resistor divider connected to pin 2. That gate also receives the output from the local oscillator, so a choke is necessary in the ground link of the dc divider to prevent rf attenuation.

Gate 1 (pin 3) accepts the output of the rf amplifier which is mixed with the local oscillator to provide the 14-MHz output. This mixer circuit is superior to any transistor circuit, either JFET or bipolar, that I have tried. The noise figure, conversion gain, and cross-modulation characteristics are excellent, challenging the best features of tubes and transistors.

There is nothing sacred about the oscillator circuit. The transistor shown in the photograph is actually a 2N2708, but the RCA40237 is less expensive and an equal performer.

### construction

A simplified chassis hole-center layout (fig. 2) may be used to reduce construction time. Sockets were used and are recommended. In as much as the MOSFET is a high-impedance device, tanks may be dipped with the transistors in their sockets. Only slight touch-up will be required when the receiver is turned on.

Peaking the oscillator coil may cause hard starting. Should this happen, apply power, detune  $L_4$  until the oscillator starts, and secure the slug at that setting.

### testing performance

As you may have guessed by now, I have been impressed by the tube impersonator called a MOSFET. Test equipment was not available for sophisticated measurements of gain and noise figure on the converter, but a few observations were made:

1. The converter is noticeably quieter than the **ARRL Handbook** converter which uses a

neutralized 6CW4 Nuvistor.

2. With the noise level set to S1, signals are about 6-dB greater (one S-unit) using the WB2EGZ converter.

3. No overloading or cross modulation has been detected at signal levels where bipolar transistors have failed miserably.

From the experience gained with MOSFET's on six-meters, I'm ready to try some experiments on my favorite band—two meters. If successful, I shall share the results with you.

ham radio

---

## transistor-tube talk

If you're used to tube-terminology, you're probably often confused by transistor terms. Here is a little play on words that can be used to keep them straight. For those of you who are studying for the advanced or extra-class exam, this is a big help if you don't feel at home with transistors.

Let's review some tube terms first. A triode has three parts or elements: cathode, grid and plate. A transistor also has three parts—the emitter, base and collector. If you'll remember the function of each element, the comparison is simple.

The cathode of a tube **emits** electrons and the **emitter** of a transistor is the corresponding element. The key word is "emits." Carrying this a bit further, electrons are **collected** by the plate of a vacuum tube, so the transistor **collector** corresponds to the plate. The key word here is "collects."

This leaves the grid. As you all know, bias

controls the action of the tube. The key word is "bias." Sounds like **base** doesn't it? So, that's it—the base is equivalent to the grid.

From these simple word similarities, it should be easy to remember that:

1. A grounded-cathode tube circuit is the same as a grounded-emitter transistor circuit.

2. A grounded-plate or cathode-follower circuit is the same as a grounded-collector or emitter-follower transistor circuit.

3. A grounded-grid tube circuit is the same as a grounded-base transistor circuit.

Just remember that the function of a vacuum-tube element is the key to its transistor equivalent. Score one for the advanced test.

George Haymans, W4NED

---

## next month in ham radio magazine:

Bandswitching FET Converter

Solid-State Conversions

One Transistor Transmitter for 40

High-Frequency Transverter

VFO Transmitter for Ten Meters

Troubleshooting Transistor Equipment

1.5-dB Noise Figure on Two Meters

Phase-Shift SSB Generators

Plus many more . . . .

# ssb oscillators

Oscillators are not peculiar to single-sideband. They exist in all ham-radio equipment. Nor does single-sideband use oscillators that are any different, except that they should be extremely stable; the sideband relationships (to one another) have to be maintained consistently throughout a transmitter or receiver. Likewise, when the carrier is re-inserted by the bfo, that oscillator must be steady as a rock and right on frequency, or the recovered voice modulation won't sound much like the original.

There is another reason why you should understand oscillators in single-sideband. There are simply more of them. One fairly elaborate ssb receiver has five oscillators. In a typical exciter there may be that many, too, depending on how many frequency translations there are. At the very least, there will be two or three in a transmitter, and the same in a receiver.

The block diagram in **fig. 1** illustrates a transmitter that uses four different oscillators. Another, of similar design, also has an audio oscillator for A2 transmission and for testing. In **fig. 2** you see a receiver design that uses five different oscillators. In a transceiver, you may find some of the oscillators shown in **figs. 1** and **2** are combined, so that the overall transceiver may have only six or seven oscillators—maybe even fewer.

Somehow, oscillators have gained a reputation for being hard to understand. They are not, provided you are aware of certain principles. When you're trying to make one work that won't, you can simplify your troubleshooting by understanding what makes an oscillator tick.

**Fig. 3** shows the four things it takes to make an oscillator. They are: amplification, dc power, feedback, and tuning. The differences among all the many oscillators that exist are in how each of these four jobs is accomplished. You can learn to classify the oscillator type by noticing how each function takes place. For example, a Colpitts oscillator, even though crystal controlled, derives feedback from a capacitive divider network—two capacitors in series, with a feedback tap-off between them. A Pierce crystal oscillator, on the other hand, has the crystal connected between plate (or screen grid) and control grid, providing feedback and tuning simultaneously. The Hartley uses a tapped coil for feedback.

**Amplification** is handled by a tube or a transistor. The **dc power** is merely to keep the transistor (or tube) working. The method by which these operating voltages are applied is usually the chief consideration whenever you think about or describe an oscillator.

The most important factor, so far as oscillation is concerned, is the **feedback**. Without

Forest H. Belt, 119 Baker Avenue, South Plainfield, New Jersey 07080

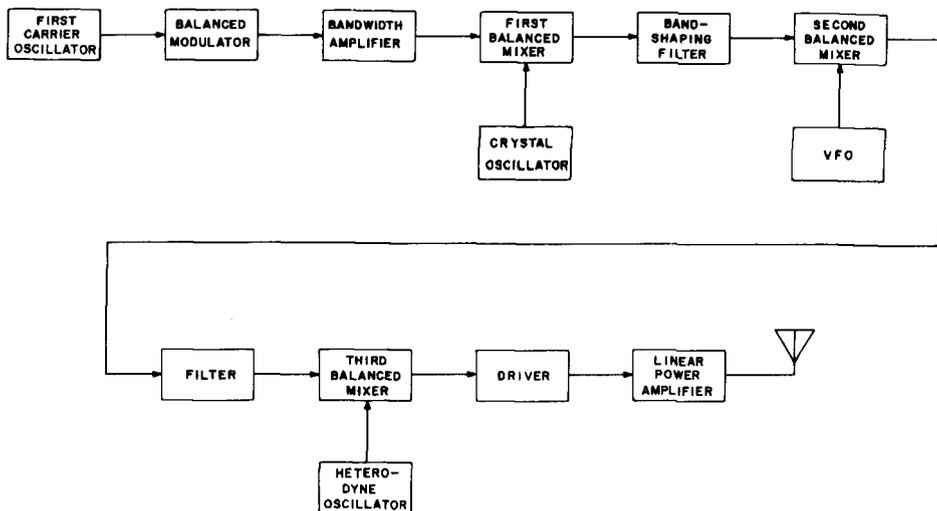


fig. 1. Block diagram of a ssb transmitter with four separate oscillator stages.

it, the tube and its dc operating voltages would form nothing more than another amplifier. The feedback takes some of the output signal voltage of the amplifier stage and feeds it back to the input in such phase that it is re-amplified. The signal is thus self-sustaining. You wouldn't want this action in a normal amplifier tube, but it is the essence of oscillator action.


Finally, the matter of **tuning**. It is of little value to have a circuit oscillate unless it is at some frequency you can use. The form of tuning in the oscillator often determines what kind of oscillator it is—what name it goes by.

Tuning also affects how efficient or stable the oscillator is.

Keep in mind, then, that you can learn to recognize any oscillator by its characteristics in each of these four factors: the type of amplification, the method of applying dc operating voltages, the way feedback is developed and applied, and how the oscillator is tuned.

Rather than go into all the different possible combinations of these four requisites, it's more practical to examine typical circuits that use them. We'll begin with the most popular oscillator in all of single-sideband equipment—the Colpitts.

fig. 2. This communications receiver uses five different oscillators.

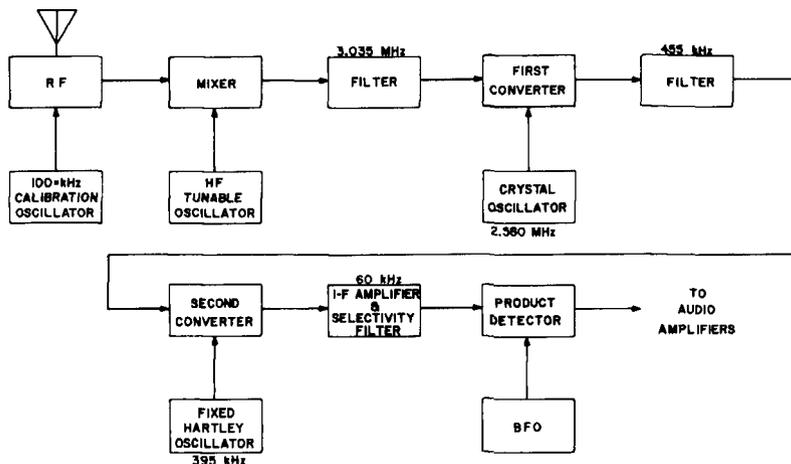

## Colpitts—crystal and variable

The uses for this versatile oscillator are many. In different brands, you'll find it in one form or another as a vfo, as the carrier generator in a transmitter, and as a linear master oscillator (LMO) for transceivers. You'll find it both crystal-controlled and variable in frequency.

There are several reasons why the Colpitts oscillator is so popular. Mainly, it is stable over a wide range of frequencies. Because a capacitive divider is used, the ratio of feedback voltage remains approximately constant, since the reactance *ratio* between the two capacitors stays the same regardless of frequency change.


Fig. 4 shows the common crystal-controlled version. A triode tube is the amplifying device, although a pentode tube or a transistor could be used just as well. Feedback is developed in capacitive divider C2-C3, and fed to the cathode. The dc connection is typical. Voltage is applied to the plate through R2; the plate is grounded for rf by capacitor C4. If the tube is a pentode, a dc screen supply is provided.

The tube is grid-driven, and output is taken from the cathode. This offers lower output impedance than a plate-output arrangement. In a few models, particularly if a pentode is used, which offers better isolation between input and output circuits, you'll find conventional tuned-tank output arrangements. In the Heathkit linear master oscillator, for ex-

ample, output is taken from a broadly tuned rf transformer. B+ is fed to the tube through the primary winding of the transformer.

As in all crystal-controlled oscillators, the tuning is accomplished by the crystal itself. The feedback arrangement can easily be designed to force the crystal into operation on an overtone (harmonic), which is desirable in some transmitters and receivers. Sometimes, where cathode bias isn't needed, an rf choke is used in place of the cathode resistor R1. This offers a high impedance to rf, and yet almost no resistance to dc plate

fig. 4. Crystal-controlled Colpitts oscillator.

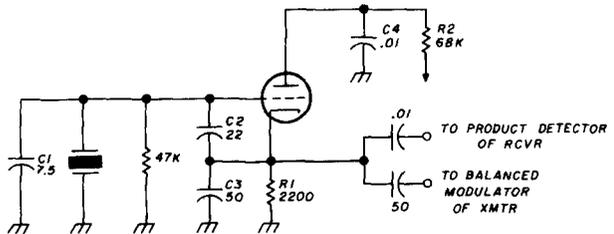


current.

In some transmitters, the frequency of the crystal is "warped" onto precise frequency by a capacitor—C1 in fig. 4. This is done only where frequency is critical, since the "raw" accuracy of a crystal is usually enough for ham work. The capacitor may even be adjustable.

Colpitts oscillators of the tunable variety

fig. 3. The four requirements for an oscillator: amplification, dc power, feedback and tuning.

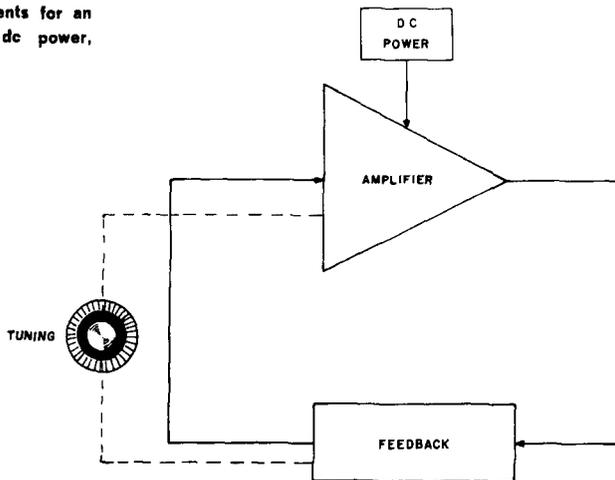

generally use pentode tubes, which offer better input-output isolation. Fig. 5 shows one of the most elaborate. Besides the basic tunable Colpitts oscillator, special innovations make this circuit doubly interesting. The exceptional stability and linear operation of this particular circuit over a range of frequencies makes it particularly attractive for linear master oscillator (LMO) service in transceivers.


The pentode is generally a high- $\mu$  type with remote cutoff characteristics—the kind used frequently in television-set i-f strips. The 6CB6 and 6BZ6 are popular for this. In one version, the tube is operated as a tetrode, with positive voltage applied to both screen and suppressor grids.

Despite all the elaborate devices for tun-

ing, retuning, coupling, and decoupling, the basic Colpitts configuration is easy to recognize. Capacitors C6 and C7 between grid and ground develop the feedback voltage. The tap to the cathode is the giveaway. An rf choke keeps the cathode well above rf ground, so the feedback can be applied.

Output from this version is through a band-pass transformer in the plate circuit. Others use cathode-follower output, and one (in Collins equipment) uses a tapped plate coil and a coupling capacitor.

fig. 5. Variable-frequency oscillator using the Colpitts circuit.

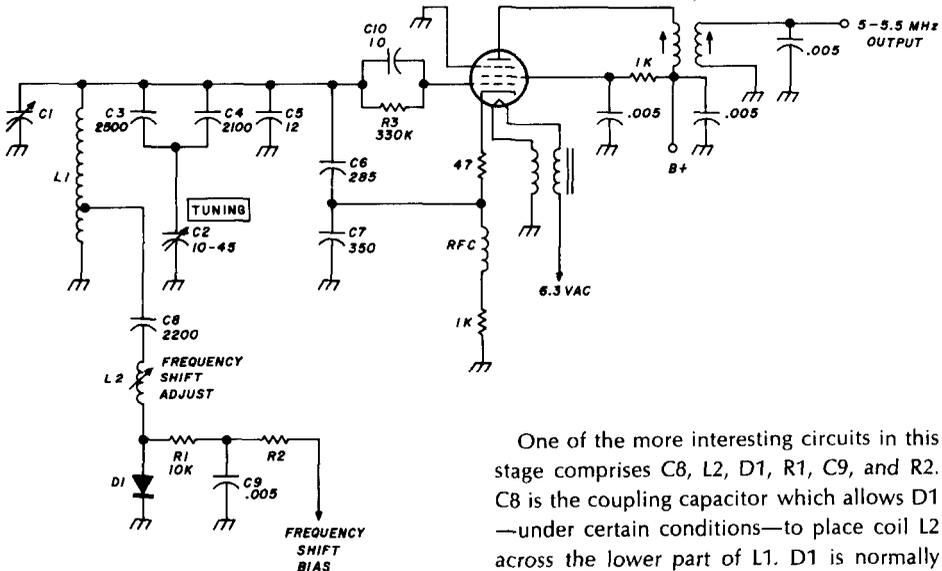

ing, retuning, coupling, and decoupling, the basic Colpitts configuration is easy to recognize. Capacitors C6 and C7 between grid and ground develop the feedback voltage. The tap to the cathode is the giveaway. An rf choke keeps the cathode well above rf ground, so the feedback can be applied.

An unusual form of grid bias is used in this example, although not in most similar Colpitts circuits. Grid-leak bias is developed in RC network C10-R3.

Capacitor C2 is the main tuning capacitor,

and C1 is the trimmer. C3, C4, and C5 are temperature-compensating capacitors; they make sure the oscillator stays at whatever frequency it's set for. To make sure the oscillator does not interact with other rf stages, elaborate decoupling is included. Besides the usual screen-grid and plate-supply decoupling, the filament lead has a bifilar-wound choke. Even when one side of all filaments is grounded, a choke is placed in series with the hot filament lead, with a capacitor to ground.

Output from this version is through a band-pass transformer in the plate circuit. Others use cathode-follower output, and one (in Collins equipment) uses a tapped plate coil and a coupling capacitor.

One of the more interesting circuits in this stage comprises C8, L2, D1, R1, C9, and R2. C8 is the coupling capacitor which allows D1 —under certain conditions—to place coil L2 across the lower part of L1. D1 is normally reverse biased and therefore offers a high impedance. When frequency-shift bias is applied at the end of R2, however, the positive voltage makes D1 conduct. While it is conducting, it effectually grounds the lower end of coil L2, thus placing it across L1. This change in inductance shifts the oscillator frequency just enough to switch the receiver or transmitter to the other sideband. Normally, the oscillator runs at a frequency that produces upper-sideband operation. When the frequency-shift voltage is applied, oscillator frequency is lowered and operation switches to

the lower sideband.



In practically all versions of the tunable Colpitts oscillator, frequency determination is in the grid circuit. The output is broadbanded. In most cases you'll find the frequency range covered by the oscillator is limited, particularly in ssb equipment. The way output frequencies are developed in single-sideband transmitters (by translation) makes it unnecessary for the carrier-generator oscillator to cover a very wide range.

Summarizing, then, you can see that factor No. 1, amplification, is provided by a triode tube in most crystal-controlled Colpitts oscillators and by a pentode tube in most variable-tuned Colpitts circuits. Factor No. 2, dc power, is generally applied to the plate through a resistor or a transformer winding, even in

pentode, connected normally, with a crystal providing both feedback and tuning. The crystal is connected from plate to grid with a triode, and from screen grid to control grid with a pentode. Because of the accuracy and resonant efficiency of a crystal, a Pierce oscillator holds its frequency well over wide variations of dc input voltage. It isn't likely to drop out of oscillation unless plate or screen voltage becomes **extremely** low.

You'll find the Pierce in both transmitters and receivers; it's often used as a heterodyne oscillator for raising frequency in transmitters, and as a frequency-conversion oscillator in receivers. The simplest version, a triode, is shown in **fig. 6A**. The only elaboration is a frequency-warping capacitor connected between the grid end of the crystal and ground.

**fig. 6. Two versions of the Pierce crystal oscillator.**

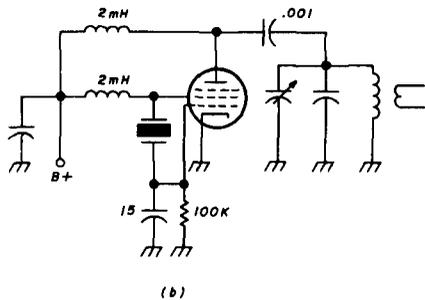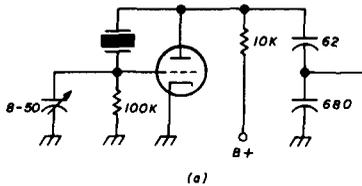

stages that use cathode-follower outputs. Grid bias may be either by a cathode resistor or by grid-leak bias; in a few it is developed by natural grid current in a high grid resistance. Factor No. 3, feedback, is invariably developed in a Colpitts by a capacitive divider from grid to ground, with the cathode tapped in between the two capacitors. The cathode is kept above rf ground by a resistor or an rf choke. Factor No. 4, tuning, is either by a crystal or a tuned circuit from grid to ground. In the latter case, always keep in mind that the feedback capacitors are in parallel with, and form part of, the tuned circuit. The value of any replacement capacitor in the grid circuit of a Colpitts is quite critical.

### second most popular—the Pierce

This oscillator is popular because of its simplicity and stability. It uses a triode or a

It permits fine adjustments of the crystal's resonating frequency.

The output of a Pierce oscillator is usually rather strong. This is the reason for the capacitive-divider output network, which gives a ten-to-one reduction in rf voltage fed from this particular oscillator. This version is used in some receivers as a frequency-control oscillator, with output fed to the second mixer, and in at least one transmitter as a heterodyning (frequency-translation) oscillator.


**Fig. 6B** shows a pentode version of the Pierce oscillator. The dc supply is conventional; some versions use cathode bias while others have the cathode grounded. In either case, the cathode is always kept grounded for rf.

Output is from the plate. Since the tube is a pentode, the plate is isolated from the frequency-control network. The output arrangement shown is a little off-beat; it is

called impedance coupling. The choke from plate to B+ is the untuned plate load. A coupling capacitor feeds the rf voltage to the tuned circuit, part of a transformer. Coupling to the next stage is inductive. Another version uses simple RC coupling—a resistor supplies dc plate voltage and acts as output load, with a capacitor coupling the rf signal to the next stage.

Both plate and screen in this stage are fed through rf chokes, which offer some load for rf developed in the plate-current stream of the tube. The screen grid may sometimes have a capacitor tying it to ground, but is

**fig. 7. Although this Hartley oscillator is part of a pentagrid converter, the same circuit may be used with an electron-coupled oscillator.**

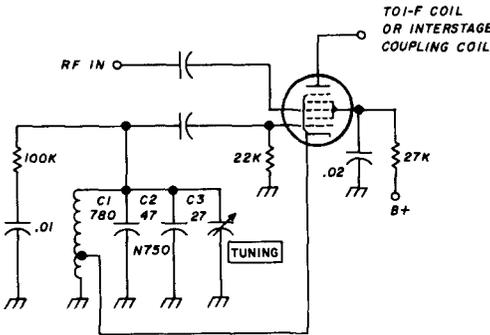

very seldom completely grounded for rf; if it were, feedback couldn't take place from the screen grid to the control grid through the crystal. In the version shown, the screen is not bypassed at all; only a small stabilizing capacitor is connected between the control grid and ground.

There is one version that operates as a cathode follower, with the output tuned circuit in the cathode circuit. Output arrangements have no bearing on the "type" of oscillator. The Pierce gets its identification from the fact that it is controlled by a crystal between the plate and grid. In pentode versions, the screen grid is operating as a plate, not as a screen grid in the usual sense. (That's why it's not thoroughly bypassed for rf.)

### the tapped-coil Hartley

This oscillator is distinctly recognizable

because the tube's cathode always goes to ground through a tap on a coil (see fig. 7). The other end of the coil almost invariably is connected through a capacitor to the grid. The Hartley oscillator is uncomplicated and stable and is used extensively for tunable applications. There is a crystal-controlled version, but it is rarely used in modern ssb equipment.

The version in fig. 7 is part of a pentagrid converter; the same circuit can be used as an electron-coupled oscillator. The Hartley is found in both receivers and transmitters. In one transmitter, it is the first carrier generator, operating at 60 kHz; in another, the second conversion oscillator, operating at 395 kHz.

The oscillator plate in the tube of fig. 7 is the double grid, grids 2 and 4. This oscillator plate doesn't have to be left ungrounded for rf, since the control grid modulates the entire electron stream. The rf from the previous stages—from a station or a transmitter stage—is fed in at grid 3. Grid 4 (part of the double grid) acts as a shield for the rf input grid, very much like the screen grid in an ordinary pentode.

The tapped coil that sets up the feedback is always a part of the tuning circuit. The tank capacitors include tuning capacitor C3, temperature-compensating capacitor C2, and main frequency-determining capacitor C1. All affect frequency. In some circuits, C1 may be a trimmer, and occasionally the temperature-compensating capacitor is omitted.

### the rest of them

Another simple oscillator used in single-sideband equipment is the tuned-plate-crystal-grid oscillator, sometimes called simply **tpxg**. This one commonly appears as the first receiver oscillator in double- or triple-conversion receivers—named, in that application, the heterodyne oscillator.

Triodes are always used, because tpxg oscillators depend on interelectrode capacitance for feedback. The screen grid in a pentode would shield out this Miller effect and keep the tube from oscillating. The crystal is connected from grid to ground. A frequency-warping capacitor or coil can be used with the crystal, although it seldom is.

The dc voltages for the tube are conventional. The cathode may be either grounded or above ground (for cathode bias). In most tpxg oscillators, bias is in the form of grid-leak or "contact" bias across a fairly large-value grid resistor.

Output circuits vary just as much as with any other oscillator. Sometimes a broadband coil is used as the load, with a small capacitor coupling the oscillator output. Occasionally, inductive coupling is used, again with a broadband transformer.

This kind of oscillator is especially suitable for overtone operation—running the crystal at (usually) three times its normal frequency.


tain oscillation at 800 Hz. Capacitors C1 and C2 and the rf choke complete the job. The result is extremely stable audio oscillation. The output is RC-coupled to a buffer amplifier via a volume control that determines how much modulation will be developed.

### what to look for next month

That's the story of oscillators in single-sideband equipment. There are other circuits just as interesting, and often more difficult to understand. We plan to cover most of them in this series on single-sideband.

The method of single-sideband generation in most of today's ssb transmitters is the

fig. 8. An 800-Hz audio phase-shift oscillator.

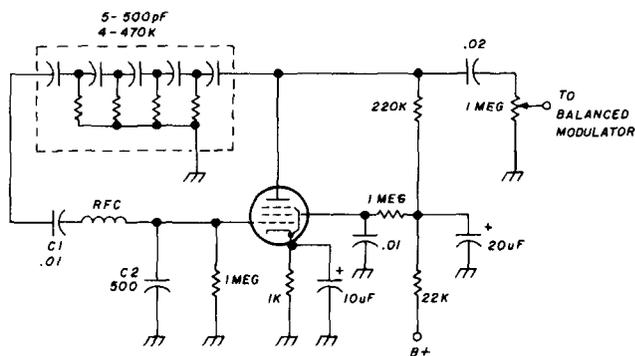

This kind of operation may be necessary in the front end of a ham receiver, and that's why this circuit is not at all uncommon as the up-front heterodyne oscillator. Sometimes, particularly when cathode bias is used, the crystal is separated from the grid by a blocking capacitor. If grid-leak bias is used, there is no need for this.

Occasionally, there is reason to use a tone in a single-sideband transmitter—for testing or for A2 code transmission. Fig. 8 shows an 800-Hz phase-shift oscillator. There are any number of other audio oscillators that can be used, but this one is exceptionally stable and its frequency is independent of output load. This latter characteristic makes it excellent for tone keying.

Feedback is via a printed component circuit (PEC) consisting of five capacitors and four resistors. As they are arranged, they give a phase shift that is almost adequate to sus-

tain oscillation at 800 Hz. Capacitors C1 and C2 and the rf choke complete the job. The result is extremely stable audio oscillation. The output is RC-coupled to a buffer amplifier via a volume control that determines how much modulation will be developed.

Although the phase-shift method is almost never used in commercial ham gear, many readers have wondered about the principles behind it. It is sometimes less expensive than the filter method—particularly at high frequencies, because there is no need for stages of frequency translation. If the suppression ratios were improved, and the circuits made easier to adjust, phase-shift ssb might catch on. Next month, we'll explain how the method works, and give some pointers on making adjustments to this type of ssb generator.

ham radio

# NEW!



TYPE PERFECT CODE

will complete it and, indeed, let you depress the next key without disturbing it. The AC-1 has provision to make AR, SK etc. without gaps.

## The Autovolt Alphacoder Model AC-1

The new Autovolt Alphacoder, AC-1, makes any letter or digit with one stroke of your finger. You can produce perfectly uniform code, including preset letter-to-letter spacing using the standard electric typewriter keyboard of the AC-1.

It is only necessary to start a letter, an automatic electronic latch

\$395.00

also

## The Autovolt Memokey, Mk-2

A self-completing  
automatic keyer featuring

- Instant letter start
- Both dot and dash memories
- lambatic output



The instant letter start frees you from the frustration of synchronizing yourself with a pulse stream when starting a new letter. The AC-2 starts immediately when you hit the first contact.

The memories allow you to "read in" one dot or dash ahead and still produce perfect code. In practice, it's best to aim a little ahead, but less than the full amount possible. Then the memories will absorb timing errors in either direction.

The lambatic output (.,—., etc.) is generated when you close both contacts of a dual paddle key. This enables you to make many letters by a single educated squeeze of the paddles.

If you use a single lever key the Memokey will function perfectly in that mode. The motions that operate a non-memory keyer will also operate a Memokey. Similarly with the instant start. Later on, you may want to get a dual paddle key and try squeeze keying. The price of the Memokey has been made competitive by using the more efficient circuitry that made the Alphacoder, AC-1, practical. The ability of the Memokey to cover all bases makes it a best buy.

The MK-2 has a built in sidetone with loudspeaker output and a built in power supply to operate it from the 117 V. 60 Hz. line.

If you already have a sidetone system, you can obtain identical results from the MK-1, which omits the sidetone and runs from 8 penlite cells. This is practical because the novel circuitry of the MK-1 uses only 7 ma. key "up" and 40 ma. keyed. It's in the same attractive enclosure as the MK-2.

**Memokey, Mk-1 \$65.00      Mk-2 \$85.00**

All of the units described are of solid state design. They include a 100 VA reed-type relay with "floating contacts" for greatest flexibility in transmitter control.

All prices FOB Boston, Mass. 25% with COD orders, please  
To order or for further amplification of details write



# AUTOVOLT, INC.

68 RICHMOND RD., BELMONT, MASS. 02178 • 484-4954

# RELIABILITY

# QUALITY

# VALUE



## SWAN 410C FULL COVERAGE EXTERNAL VFO

The Model 410C Frequency Control Unit is designed for full coverage of 80, 40, 20, 15 and 10 meters. It is intended for fixed station operation and plugs directly into Model 500C. It may also be used with Model 350C. Eight ranges, 500 kc each, 5 kc calibration.

**\$115**

## DUAL VFO ADAPTOR

Provides for the addition of second VFO for separate control of transmit and receive frequencies. Plugs directly into Model 500C and may also be used with Model 350C and other Swan transceivers.

**MODEL 22 . . . . . \$25**



## MARS OSCILLATOR

Five crystal controlled channels with vernier frequency control. Plugs directly into Model 500C and may also be used with Model 350C and other Swan transceivers.

**MODEL 405X  
(less crystals) . . \$45**

## SWAN 500C SSB-AM-CW TRANSCEIVER

**Five band, 520 watts for home station, mobile and portable operation.**

The new model 500C is the latest evolutionary development of a basic well proven design philosophy. It offers greater power and additional features for even more operator enjoyment. Using a pair of the new heavy duty RCA 6LQ6 tetrodes, the final amplifier operates with increased efficiency and power output on all bands. PEP input rating of the 500C is conservatively 520 watts. Actually an average pair of 6LQ6's reach a peak input of over 570 watts before flattopping!

The 500C retains the same superior selectivity for which Swan transceivers are noted. The filter is made especially for us by C-F Networks, and with a shape factor of 1.7 and ultimate rejection of more than 100 db, it is the finest filter being offered in any transceiver today.

For the CW operator the 500C includes a built-in sidetone monitor, and by installing the Swan VOX Accessory (VX-2) you will have break in CW operation.


Voice quality, performance and reliability are in the Swan tradition of being second to none.

**\$520**

## SWAN 117XC MATCHING AC POWER SUPPLY

Complete A.C. supply for 117 volts 50-60 cycles, in a matching cabinet with speaker, phone jack, and indicator light. Includes power cable with plug for transceiver, and A.C. line cord. Ready to plug in and operate.

**\$105**

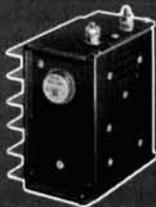

## SWAN 14C DC CONVERTER

Converts the above 117XC A.C. power supply to 12 volt D.C. input for mobile, portable, or emergency operation.

**\$65**

**SWAN SPEAKS YOUR LANGUAGE . . . ASK THE HAM WHO OWNS ONE**

# POWER

# VERSATILITY



## SWAN MARK II LINEAR AMPLIFIER

Two Eimac 3-400Z Triodes provide the legal power input: 2000 Watts P.E.P. in SSB mode or 1000 Watts AM or CW input. Planetary vernier drives on both plate and loading controls provide precise and velvet smooth tuning of the amplifier. Greatly reduced blower noise is provided by a low RPM, high volume fan. Provides full frequency coverage of the amateur bands from 10 through 30 meters and may be driven by any transceiver or exciter having between 100 and 300 watts output.

**\$395**

## PLUG-IN VOX UNIT

Plugs directly into Model 500C, and may also be used with Model 350C and other Swan transceivers.

**MODEL VX-2 . . . . \$35**

## SWAN 350C SSB-AM-CW TRANSCEIVER


Our improved standard 5 band model, now in production and still only . . .

**\$420**

## MARK II POWER SUPPLY

May be placed beside the Mark II, or with its 4½ foot connecting cable, may be placed on the floor. Silicon rectifiers deliver 2500 volts D.C. in excess of 1 ampere. Computer grade electrolytic filters provide 40 mfd capacity for excellent dynamic regulation. A quiet cooling fan allows continuous operating with minimum temperature rise, thus extending the life and reliability of all components. Input voltage may be either 117 or 230 volts A.C.

**\$235**

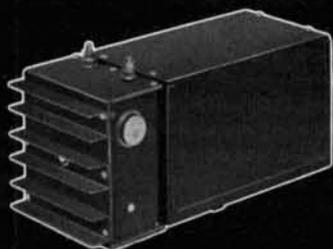

## SWAN 14-117 12 VOLT DC SUPPLY

Complete D.C. supply for 12 volt mobile or portable operation. Includes cables, plugs, and fuses. Will also operate from 117 volt A.C. by detaching the D.C. module & plugging in 117 volt line cord. Negative ground standard. Positive ground available on special order.

**\$130**

Illustrated on these pages is a complete Swan amateur radio station, one of the finest money can buy. Starting with the powerful 500C and an AC power supply, you are immediately on the air with a big, high-quality signal. Thanks to the excellence of the high-frequency crystal lattice filter, made especially for Swan by CF networks, you will have one of the cleanest and most readable signals on the air, as well as outstanding receiver selectivity and sensitivity. The various accessories from the Swan line may be added at any time, providing greater operating pleasure and performance. The tremendous acceptance of Swan products by radio amateurs throughout the world is most gratifying to all of the people at Swan. It is our continuing policy to offer the finest communications equipment we know how to design and manufacture, with quality control, craftsmanship, and service that is second to none.

73

Be Sure to Visit Your Swan Dealer Soon




**SWAN**

ELECTRONICS

OCEANSIDE, CALIFORNIA

A Subsidiary of Cubic Corporation

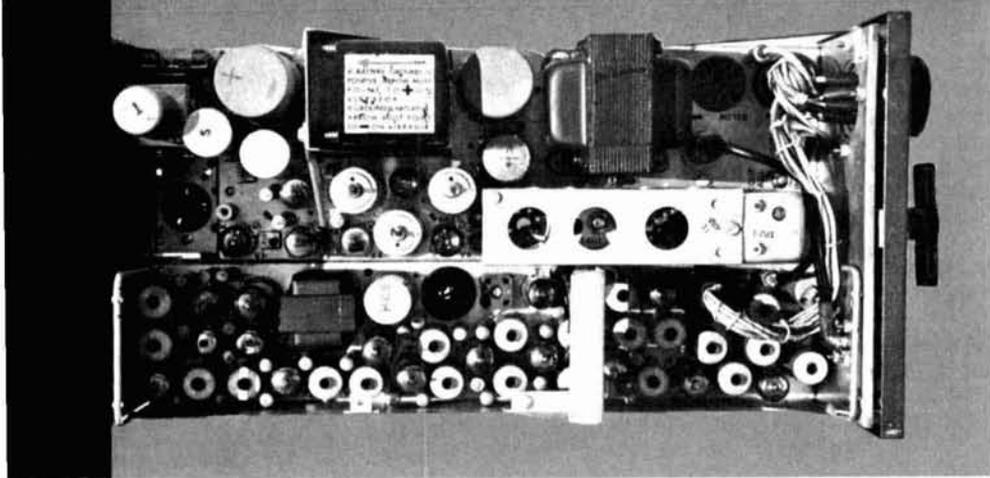

## amateur vhf fm operation

An introduction  
to amateur fm operation  
on 144 and 432 MHz,  
including base stations,  
repeaters  
and accessories

John Connors, W6AYZ, 920 Sir Francis Ave., Capitola, California 94720

This article was written to introduce you to the wonderful world of amateur vhf fm communications. There are a number of books on the market which will explain all the technical aspects of the subject to you; the purpose of this article is to consider fm seriously as a dependable, local communications mode with many advantages over a-m. You will meet some of the various types of equipment in common use and some of the fascinating mutations developed by commercial and amateur users in their quest for reliability and convenience.

Amateur fm owes its very existence to the commercial fm two-way radio used by the mobile services such as police, fire and taxi. The first equipment that the commercial users used on a large scale was designed for wide-band fm. The transmitter was deviated plus or minus 15 kHz from the center frequency. Most of this early equipment was also designed for a six-volt supply.

Commercial two-way radio caught on big however, and the FCC was forced to alter their requirements to what is now called narrow-band fm; the transmitter is only deviated plus or minus 5 kHz from the center frequency. This rules change provided more channels through closer spacing and made all the old equipment obsolete. To help matters further, the automobile manufacturers decided that twelve-volt ignition systems

were more practical than six-volt systems. Result: more obsolete commercial fm equipment. Now, vacuum-tube equipment is being phased out by solid-state units. The result is a lot of low-cost fm equipment for the interested amateur.

### why use fm?

As you may have guessed, the first big advantage of fm for the ham is availability. Commercial users couldn't use much of the older equipment, and no one was willing to buy it. As a result, many equipment owners and manufacturers turned to the amateur market as a way of saving some of their original investment. The second advantage is price. For the price of a good a-m transceiver, you can buy four or five fm transceivers with

**The Link decoder.** Although these units are stubborn at times, they are often used as a command decoder and work quite well as a selective-call decoder.



high-quality receivers and transmitters.

For mobile operation, fm units mount in the trunk and are remotely controlled from the front seat. For weak signals, fm is always more understandable than a-m. Receivers won't drift off frequency since since they are crystal controlled. Positive noise-sensing squelch circuits surpass anything found in a-m gear and completely silence the speaker until a signal is received.

Ignition and other forms of interference

which cause a lot of trouble with a-m operation don't affect fm; a typical mobile installation rarely needs any noise suppression. Another big advantage is reliability. Commercial equipment is built to run continuously and take a lot of abuse while doing it. Mobile units can bounce around in a trunk for years with no failures, and base stations require little maintenance.

### how to get started

You can begin your search for fm equipment and information by writing to the Lynchburg Amateur Radio Club\* for a list of active fm nets or groups in your area. The California Amateur Relay Council\*\* will provide legal and technical advice on repeater operation. There are also a couple of books<sup>1,2</sup> and a magazine<sup>3</sup> which are helpful. After you're armed with this information, contact the people in your local area who use the equipment (both amateur and commercial) to find out what is available and where.

Speak to the man who runs the local fm two-way shop. Many times he has a customer who wants to sell obsolete fm equipment; as a favor to his customer he will get you together. Talk to commercial users directly and leave your name and address around, especially at non-governmental businesses. They are not as involved in red tape as the police, fire and county facilities. You may even find someone willing to sell a group of five or ten units at one time. In this case, it's best to have a group of people go together and split the cost. Prices are generally better and this guarantees that you won't be the only fm station in the area. In any case, don't give up. Acquiring the first few units is the hardest part. Once the ball is rolling, and your group expands, you'll find availability is good.

### equipment

Before discussing the establishment of your fm operation, a brief rundown on equipment is in order. Two-way fm equipment falls in three major categories: low band (30-50 MHz), high band (150-170 MHz) and uhf (450

\* Lynchburg Amateur Radio Club, 1306 Grove Street, Lynchburg, Virginia.

\*\* California Amateur Relay Council, 51 Norwood Avenue, Kensington, California 94707.

MHz). Low-band and high-band equipment is similar in design and appearance. Equipment for uhf is harder to come by and is generally used for repeater control and backbone links.

High-band equipment is the most popular for a number of reasons. First of all, antennas are less cumbersome and objectionable at the shorter wavelengths. Secondly, television interference has always plagued six-meter activity and two meters is relatively free of those problems. Thirdly, in most cases, two-meter equipment is ready to run as is; equipment that does require modification is taken care of with padding capacitors. Low-band equipment must be moved up beyond the 52.5-MHz band edge for wide-band operation. This is generally no big problem, but it can be quite involved.

In all fairness to six meters, it does provide greater range capabilities and less objectionable mobile flutter than two. This could be a major consideration for simplex operation. In addition, some low-band equipment can be converted to ten meters. This is becoming increasingly interesting for fm with the improved band conditions, and 29.6 MHz is a very active fm channel.

Motorola equipment is quite representative of the trends manufacturers followed over the years. It is also quite popular among hams, so it makes it a good example for discussion. Motorola started out with the **Deluxe** line, a separate transmitter and receiver housed in big, blue containers. They are old, bulky, inexpensive and ever so reliable. Some of these units were made with 110-volt supplies for base station use.


Next came the **Dispatcher** series, commonly called the 5V. These were small, single-case units which had six-volt supplies. Sometimes you'll find one which was converted to 12 volts; the transformers are still available for the 12-volt modification. The receivers in the **Deluxe** and **Dispatcher** lines are not well-suited to multiple-channel work since the same oscillator is used for both high and low i-f injection.

After the **Dispatcher** series, Motorola started its **Research** line which is still being expanded. The 41V became the most popular in this line with its six- or twelve-volt supply and multiple-frequency receiver and trans-

mitter. Some units even had 110-volt supplies for base-station use. The basic unit is slightly larger than the 5V. Besides the 41V, the **Research** line contains a wide variety of transmitters, receivers and power supplies mounted on strip-type chassis. They can be rack mounted or put together in various combinations in a mobile housing. The best way to become familiar with these units is through the **FM Schematic Digest**.<sup>2</sup>

When transistors came into service, Motorola's line of equipment was expanded with solid-state units of all kinds. Hybrid handie-talkies like the one shown in the photograph were partially transistorized at first. Many used rechargeable Nikad battery packs; this makes them very economical for amateur use. Pocket-sized transmitters and receivers fol-

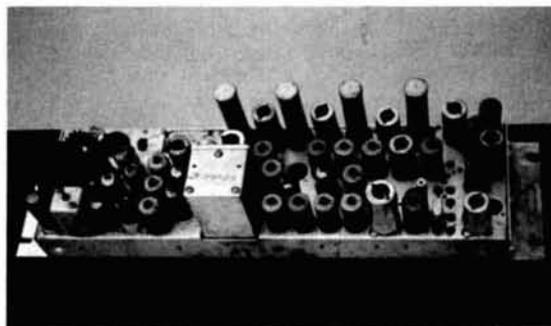**A T-44 receiver strip. Excellent for the 450-MHz primary receiver of a repeater.**



lowed, but they are still pretty scarce. Motorola's main line of mobile equipment went miniature with the advent of the **Motrac**. This is a hybrid unit with various transmitter powers, multiple-frequency kits and extra gadgets.

The other manufacturers have gone the same route over the years. General Electric had their **Preprogress**, **Progress** and **Master** lines. Link is also used quite a bit by amateurs as is RCA, Comco, Karr, and others. Generally speaking, most manufacturers produced models for both low- and high-band operation in a particular line, but this isn't always true.

### **establishing an fm operation**

There are several very important consid-

erations you and your group must make before becoming deeply involved in fm. First is the problem of choosing a frequency. Before you start buying crystals, stop and consider these points:

Do any other amateur activities frequent the channel you intend to use?

Would it be advantageous for the group to use a frequency in the general-class portion of the band to minimize possible interference? This is especially important for repeater

**A homemade test aid for servicing almost any Motorola fm equipment. Adapters for the remaining units are easy to build.**



users since the repeater hears a lot more than a ground station.

Should you make use of some of the present national fm frequencies as your channels for emergency operation?

It should also be kept in mind that once a number of fm stations are set up on a particular channel, it is nearly impossible to change it. Consult the Lynchburg group regarding the channels being used in your area; you may want to join one of them. Monitor your choice of possibilities first and be sure nothing happens which could make you select another channel.

Once the frequency has been chosen, there is the problem of accurately measuring it. Al-

though the transmitters are crystal controlled, they are adjustable over a few kHz and as Aagaard points out<sup>2</sup>, disagreements are sure to arise. Transmitters can be set to the receiver frequency by zeroing the discriminator in the receiver. All discriminators should be zeroed to a common rf carrier. When aligning the reference receiver, use the most accurate signal source available. An accurate frequency meter or counter is a big help in this area.

Point-to-point operation is called local channel or simplex operation and works quite well. For larger coverage, amateurs have gone to repeaters.<sup>4</sup> Repeaters require two methods of control which must be entirely independent. By using dialed tones transmitted to the repeater on the communications channel, secondary or member control is maintained. This is the method used by club members to turn the repeater on and off.

The trustee of the repeater must be able to turn the repeater completely off by using a remote-control system on 220 MHz or higher. His system is only used in emergencies such as equipment malfunctions. This is called primary control. Generally, a 450-MHz fm system is used for primary control because the equipment is more readily available than 220-MHz equipment and takes much less effort to convert.

450-MHz equipment may also be used as a backbone link between two repeaters. This is a two-way relay system in which the audio from one repeater is fed to the other via a 450-MHz link where it is retransmitted on vhf. This allows mobiles or base stations to communicate dependably over great distances. The 450-MHz receivers continuously monitor the channel, and the transmitters are turned on by command from the ground stations. This eliminates any need to monitor the other repeater continuously.

### accessories and ideas

The following are some of the more popular accessories and ideas being used by fm amateurs around the country. This list is by no means complete in scope or content and is offered only as a stimulus to thought.


**Tone oscillator.** A tone oscillator can be the right arm of an fm amateur. By placing a

telephone dial in series with the audio output, it can be used to control a repeater or selective-call system. Generally, provision is made for selecting a number of different preset frequencies with a rotary switch. Special oscillators are used for generating AFSK Teletype and facsimile signals as well as transpond and telemetry signals.

**Selective-call decoder.** For continuous channel monitoring with the speaker off, a de-

**Private Line** is a good example. This is somewhat similar to selective call except that it isn't as selective. To open the speaker on your receiver, two conditions must occur simultaneously. First, there must be a carrier present, and second, a short tone burst of a predetermined frequency must occur. The receiver speaker will then enable until the carrier disappears. A small encoder is used at the transmitter and a decoder at the receiver.

fig. 1. Schematic diagram of a homemade test aid for Motorola fm equipment.

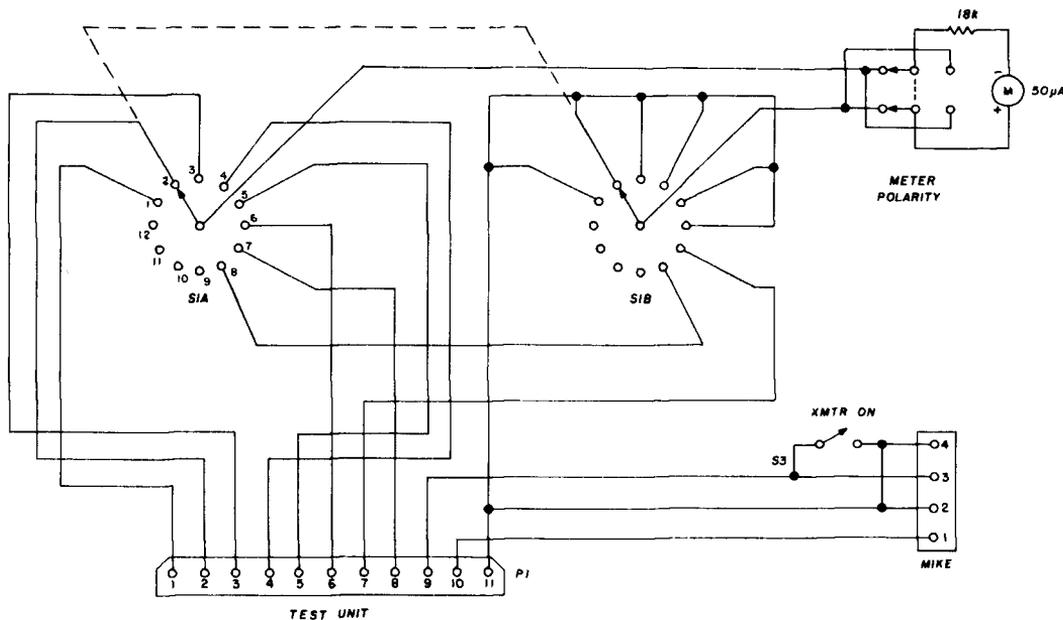

coder is wired into the base station. The call is placed by dialing a series of digits which add up to ten. This completes a circuit which rings a bell and turns on an indicator lamp. Each channel user with this capability should choose a different four-digit number that adds up to ten such as 1-2-3-4, 1-1-7-1 or 3-4-2-1. Some amateurs transmit a short burst of tone back to the caller to tell him that the alarm did go off. This is called transpond and can even be used to indicate whether or not the party being called is home by transponding with different audio frequencies.

**Tone access.** Commercial manufacturers make tone-operated squelch systems. Motorola's

**Autostart Teletype.** For general information bulletins, passing large volumes of information and leaving messages for people not listening, autostart Teletype is very useful. This scheme was discussed in a recent magazine article<sup>5</sup> along with circuits for a complete transistorized system. The most popular machines in amateur service are the Teletype models 26 and 15. The model 26 is a small, quiet unit while the model 15 is a rugged, dependable machine. There are many sources for RTTY gear, and the prices vary, so shop around.

**Facsimile.** Repeater users soon discover that they are doing a lot of running back and

forth exchanging manuals, schematics and so on. Because of the large coverage area of a repeater, one trip to get a schematic can cost a full day. By using facsimile equipment, pictorial information can be passed hundreds of miles in a matter of minutes. While facsimile equipment is less abundant than Teletype machines, these units can be obtained quite readily on the surplus market.

**Telephone and desk remotes.** Remote control of a base station from another room of the building is quite popular with commercial users. Many manufacturers make a desk-top base station, but it is senseless to run two stations at once. By rewiring an old telephone, a versatile remote can be made for practically nothing. A miniature push-button switch installed in the handset converts it to push to talk; coil cords with five conductors sell for under two dollars. The volume control can be hidden behind the handset cradle and other controls similarly placed. An alternative solution is to mount a speaker and

**Typical of equipment available to the ham is this Motorola 5V. They are compact and inexpensive.**



microphone in a small box which can be bolted to the wall in some convenient location. Most amateurs who use remote keep the base station in the shack or garage and use as many remotes as they want in the house. Don't forget to bring in a selective-call wire for the alarm so you will hear it when it goes off.

**Receiving.** Most active fm amateurs leave their receivers running continuously day and night. While this does consume some electricity, it makes operation much more pleasant and convenient.

When operating through a repeater, the receiver can be left running while transmitting. This lets you hear yourself coming back through the repeater. If another operator wishes to interrupt or inject a thought, he merely pushes his mike button and the beat note is heard in your receiver. This type of duplex operation makes communications just like talking on the telephone.

### repeaters

Besides the normal repeat functions, the following additional features are quite popular with amateur repeaters of all kinds:

**Frequency set.** By dialing a command, a highly stable crystal-controlled oscillator is enabled. Any station placing a carrier on the input and duplexing can hear the beat note. He can place his transmitter on frequency by zero beating to the reference signal.

**Signal-strength monitor.** This device may be left on all the time or turned on by command. It delivers an audio beep sequence which indicates proportional signal strength of the carrier present at the repeater's receiver.

**Secondary-control cycling timer.** This is simply a timer which requires setting within a certain period of time or the repeater is automatically shut off. This is handy for mobiles that inadvertently drive out of range.

**CW identifier.** Elimination of repetitious voice identification of the repeater is accomplished through automatic CW identification. The usual procedure is to cycle the identifier once when the repeater comes on and once when it goes off as well as every ten minutes in between. Either mechanical or electronic means is employed to generate the MCW tones.

**Directional antenna rotation.** Some repeaters incorporate facilities for remotely directing antennas to assist in copying weak stations in distant locations. A simpler method is to use separate antennas pointed in the desired

direction; they are selected by command.

**Emergency repeater or portable power.** Some groups will prefer to install an automatic generator at the repeater site for ac power during commercial power failures. Others choose to install a battery-operated repeater which comes on during power failures. The generator has the advantage that normal repeater operation is not affected. However, it requires continuous service as well as maintenance and fuel. The battery-operated repeater gets away from all that, but power capability is limited, and only skeleton operation is possible.

**Multifunction decoder.** The ability to perform many different remote-control functions upon command is a must for some repeater groups. Some have only two commands, repeater on and off, while others have facilities which can handle up to 1000 different commands. Diodes, relays, transistors and tubes all play an important part in units such as these, and each group must assess its own

**A Motorola 41-V. Slightly larger than the 5V and with better features which make it worth owning. Many of these units are coming out of commercial service now.**



needs and potentials. For the group just getting started, a simple command decoder is a modified Link or Secode. These can provide enough commands for any club's beginning needs, but you'll soon discover you're only getting by and are actually quite limited.

**Alternate receivers and transmitters.** Endless combinations of frequencies and modes can be used to avoid conflict with local amateurs who unknowingly fall on the main input

channel or for other special purposes. Most popular is a second-channel monitor which listens to another fm channel and "pipes" the audio out over the repeater at reduced level. Many repeater groups are installing facilities for monitoring and transmitting on one or more of the national fm calling frequencies such as 52.525 or 146.94 MHz. These frequencies can be used for traveling mobiles or local co-ordination activities such as interstate traffic handling.

**A 450-MHz transmitter from the T-44. Power plug is on left and finals and drivers are under the covers.**



**Telemetry.** When many commands are available for use, it's difficult to remember which ones are on and which are off. Remote metering via telemetry overcomes this, and there are a number of different approaches. Slow, repeating "beeps" of three different audio frequencies can be read by ear and decoded by counting their position with respect to a sync pulse of a different frequency. Another method generates a dot pattern on an oscilloscope, and intensity modulates the dots for those commands which are on. Amateurs who are interested in television might consider transmitting a television picture of a lamp panel at the repeater site down to the base station.


**Tape logging.** Repeater logging can be eliminated through the use of recording tapes. A short burst can be made to start the recorder for a predetermined interval of time, or the recorder can run continuously. The advan-

tages and disadvantages of each system are obvious.

**Tape-message secretary.** A tape recorder will record anything on the repeater input for a predetermined time on command. When another command is given, the message can be played back.

I have deliberately ignored the details of

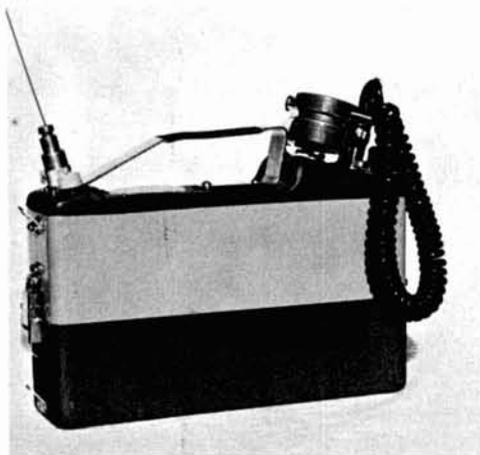**A battery-operated Handie-Talkie.**  
One watt transmit with rechargeable battery, speaker and microphone.



these ideas since most fm groups will have their own ideas and will want a system engineered to their own needs. This is the best part of fm radio. Transmitters and receivers, the major concern of the low-band ham, become only secondary to the vhf fm operator. His major interest lies in the development of a sophisticated communications system, and fm radio is merely a stepping stone to that goal.

#### references


1. J. S. Aagaard, "Wide-Band FM for the Amateur," Evanston, Illinois, 1962 (out of print).
2. S. H. Wolf, Editor, "FM Schematic Digest," Two Way Radio Engineers, Inc., Dept. H, 1100 Tremont Street, Boston, Massachusetts 02120.
3. *FM Magazine*, 2005 Hollywood Avenue, Grosse Point, Michigan 48236.
4. D. Baxter, W5KPZ, and J. Douglas, W5OBV, "Two-Meter Repeater," *73 Magazine*, September 1966, p. 58.
5. J. Connors, W6AYZ, "Autostart Teletype Encoder and Decoder," *73 Magazine*, January 1967, p. 34.

ham radio

# NOW!
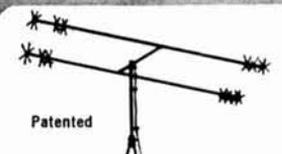
## IN THE WEST

**Now... 2000 Watts P.E.P.**  
Full Power/Minimum Size  
FOR APARTMENTS • SUBURBAN HOMES  
Marine and Portable Operation  
Packaged for APO and FPO Shipping



Bands	6-10-15-20 Meters
Power Rating	2000 Watts P.E.P.
El. Length	11'
Turn. Radius	7'
Total Weight	11 lbs.
Single Feed Line	52 ohm
SWR at Resonance	1.5 to 1.0 max.

### 6-10-15-20 METERS

The time proven B-24 4-Band antenna combines maximum efficiency and compact design to provide an excellent antenna where space is a factor. New end loading for maximum radiation efficiency. No center loading.

**Model B-24**  
Net \$59.95

### MULTIBAND COAXIAL ANTENNA for 6 - 10 - 15 - 20 METERS

Needs no ground plane radials. Full electrical  $\frac{1}{2}$  wave on each band. Excellent quality construction. Mount with inexpensive TV hardware. Patented.

Power Rating	2000 Watts P.E.P.
Total Weight	5 lbs.
Height	11'
Single Feed Line	52 ohm
SWR at Resonance	1.5 to 1.0 max.

**Model C4 Net \$34.95**



Free Delivery On  
"MINI BEAMS"  
From

## QUEMENT ELECTRONICS

1000 SOUTH BASCOM AVE.  
SAN JOSE, CALIFORNIA

95128

PHONE 294-0464 SINCE 1933

# solid-state transmitter switching


If you're tired of holding that PTT switch down, try one of these push-to-talk, push-to-listen circuits described by W2EEY

Sometimes the simplest gadgets contribute the most to your operating convenience. For example, if you replace the push-to-talk (PTT) mode of operation with a push-to-talk and push-to-listen (PTT/L) circuit, you don't have to continually push the mike button during transmit periods.

Amateur operators used to have a simple toggle switch for send-receive switching; push-to-talk was confined to mobile installations. Today, however, transceivers are in the vogue, and push-to-talk operation is used by many stations. The only disadvantage of PTT is that you have to depress the PTT button continuously during transmissions. Your hand can get pretty tired during long operating periods. VOX operation is very convenient, but not all transceivers have VOX built in.

In this article I'll describe some simple ways to convert your rig to push-to-talk and push-to-listen. With this setup, the mike button is pushed momentarily to transmit and then released. When it's depressed again, the rig is switched to receive. The advantages

fig. 1. A tunnel-diode circuit which is the solid-state equivalent of a latching relay.

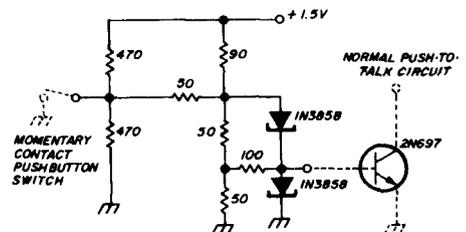

John J. Schultz, W2EEY, 40 Rossie Street, Mystic, Connecticut 06355

may not appear very great, but try to imagine how much easier many QSO's would be if you didn't have to use a death-grip on the mike continuously!

Although you can use relays or special switches to obtain push-to-talk/-listen (PTT/L) operation,<sup>1</sup> the solid-state circuits described here are a lot more reliable. The use of integrated circuits to replace a relay should interest you even if you don't want a PTT/L circuit in your rig. These switching functions can also be adapted to other uses, such as switching filters or crystals.

### solid-state switching conversions

For PTT/L, you have to have a solid-state circuit which will duplicate the action of a "double-push" switch or a latching relay. This can be done electronically with a triggered


multivibrator, but the added components result in some rather complicated circuitry for the simple switching function you need.

### tunnel-diode latching circuit

The two tunnel diodes shown in the circuit of **fig. 1** provide the equivalent circuit in a relatively simple form. Each time the input terminal is grounded, the output terminal alternates between a positive 1.5-volt output and a zero-volt output. The output of this circuit cannot be loaded appreciably if it is to function properly. It is better to drive a switching transistor which activates the actual PTT circuit in the transmitter. It can also be used to pickup a SPST relay which then controls PTT action.

There is nothing complicated about the

**fig. 2.** Internal circuit of an integrated-circuit J-K flip-flop—this circuit can be used in place of a mechanical latching relay as described in the text.

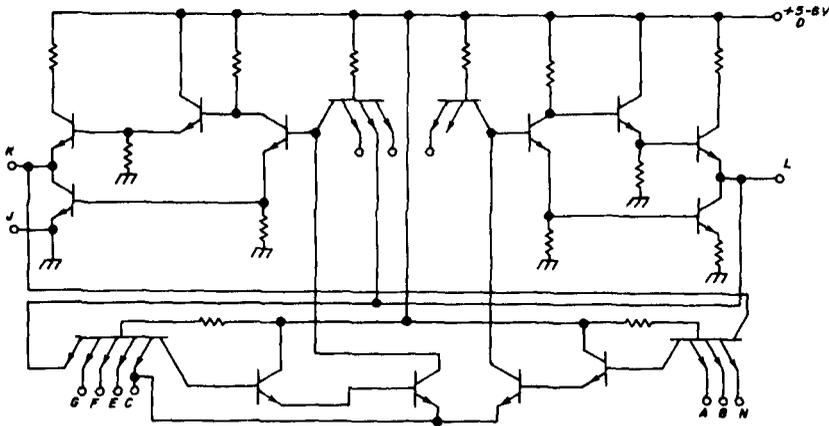

bistable multivibrator. This term may be confusing, but the basic multivibrator circuit has been used by many amateurs as a CW monitor. The triggered circuit will change "states" (that is, have an output or no output) only after a triggering pulse has been momentarily applied to the input. Each successive triggering pulse changes the state of the multivibrator.

It is fairly easy to convert a free-running multivibrator into a triggered multivibrator. However, succeeding pulse inputs to trigger the circuit have to be opposite in polarity. You can add circuitry so that successive pulse

operation or construction of this circuit. If you can buy the diodes reasonably, this circuit is about the simplest electronic latching circuit you can use. For more information on tunnel-diode switching circuits, consult references 2 and 3.

### integrated-circuit switch


Another approach to inexpensive solid-state switching involves the use of an integrated-circuit J-K flip flop. The internal circuitry of the IC is shown in **fig. 2**. With this device, negative-going input pulses of the same polarity will produce alternate "on" or

"off" states at the output. The integrated circuit I used was a surplus unit available from Solid-State Sales\* for \$1.20.

Rather than becoming too concerned with the internal circuitry of the IC, let's examine the switching condition that will provide PTT/L operation. If a positive 3 volts is present at all six terminals **EFG** and **ABN**, every time the input voltage at **C** goes from 3 volts to 0 volts (but **not** from 0 to 3 volts), the voltage at **K** and **L** will reverse. For example, if **K** is at 3 volts and **L** is at zero, momentarily grounding **C** will change **K** to zero and **L** to 3 volts.

**Fig. 3** shows the J-K flip flop in a PTT/L circuit. The integrated circuit cannot be loaded down too much, so a switching transistor

**fig. 3. Connecting an IC and 2N697 relay driver to provide push-to-talk and push-to-listen operation.**

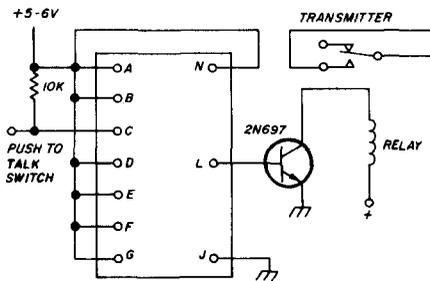

is used to control the relay circuit. An NPN transistor is shown here because a positive control voltage is usually used to activate the send-receive relay. If your transmitter happens to use a negative control voltage (very unusual), simply reverse the emitter and collector terminals of the switching transistor. For added flexibility, you can add a bypass switch so that either PTT/L or conventional PTT operation is possible.

There are only two precautions when using this circuit: don't exceed the recommended supply voltage, and make sure the PTT switch provides a good, clean contact. The IC re-

\* Solid-State Sales, P. O. Box 74, Somerville, Massachusetts 02143; order FF-1 J-K flip-flop integrated circuit.

sponds extremely fast, and a dirty switch will cause it to change states unexpectedly. Otherwise, its switching action is far more reliable than any mechanical mechanism.

## switch replacement

If you feel you have to use a mechanical PTT/L circuit, sometimes the mike switch can be replaced with a so-called "push-push" or "double-push" action switch. These switches will alternately open or close a circuit with alternate depressions of the switch. A double-push switch that will fit in the base of home station microphones is the Cutler-Hammar model 7208-K4. Arrow-Hart and other manufacturers produce similar types. A miniature double-push switch which lends itself to hand-held microphones is the Alco-switch MSP-105D. It is less than 1/2-inch square and costs under \$2.00.

For those situations where a momentary action switch can be replaced with a double-push switch, this may be the easiest conversion scheme. However, in most cases, solid-state methods of switching are usually preferable. Not only do they result in push-to-talk and push-to-listen operation with any PTT microphone, with a simple bypass circuit you can have simple push-to-talk operation too.

## summary

Push-to-talk and push-to-listen operation is certainly not a major technical innovation. However, it has proved to me to be one of those small operating conveniences that becomes invaluable after it has been used for awhile. Try using push-to-talk and push-to-listen operation for an hour or two, and then go back to plain push-to-talk; the inconvenience you've been putting up with will be quite apparent.

## references

1. D. Collins, VE3GLX, "Push to Talk or Speak to Talk," 73, October, 1967, p. 98.
2. RCA, Technical Manual TD-30, "Tunnel Diodes," 1963, pp. 33-54.
3. "GE Transistor Manual," Seventh Edition, 1964, pp. 366-371.

**ham radio**

# Introducing



a **new** monthly  
for amateurs

that's **different** \*

- the latest in technical ideas and home construction . . .
- featuring **Jim Fisk**, W1D7Y, the well known amateur radio editor . . .
- and including articles by your favorite authors.

how different? — \*


It looks different — it is different! It's easier to find information . . . easier to read . . . easier to understand . . . easier to build from . . . it's a magazine you'll find it easy to like.

Write for **FREE** copy . . . or

One year for **\$5.00** . . . or

Get **ONE YEAR FREE** — 3 years for **\$10.00**

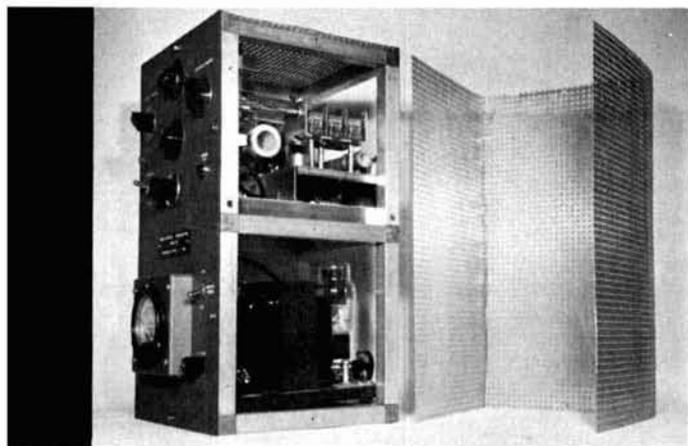to Ham Radio Magazine, Greenville, New Hampshire 03048. Be sure to include your name, address, call and Zip code.



A three-band 80-watt transmitter using modern rack and panel construction.

## return to rack-and-panel construction

Here's  
a construction technique  
that has all  
the advantages  
of the old rack and panel  
but results in neat,  
compact designs

Howard S. Pyle, W7OE, 3434 74th Avenue, S. E., Mercer Island, Washington 98040

Grizzled old timers will nostalgically recall the pioneer days of amateur radio when a station was a scattered collection of motley components arranged as fancy dictated. A tuning coil or loose coupler, a crystal detector, perhaps a variable capacitor of sliding metal plates in a grooved wooden frame arranged on a table top constituted the receiver. A massive helix of copper tubing, a huge capacitor of discarded tin-foil-coated, photo plates, a heavy transformer and an awesome rotary gap somehow found space on the floor, the table or a shelf—wherever they would fit—made up the transmitter. Odds and ends of bell wire, lamp cord and copper tubing tied the scattered pieces together electrically and you were on-the-air!

Because of the inconvenience and space-hogging of such arrangements, the receiving elements were soon combined in a more compact group. Generally this took the form of a breadboard, with all the components screwed down. Sometimes a wooden cabinet was used. The tuning coil or loose-coupler was mounted on the cabinet top, rotary variable capacitors were mounted in the box with their shafts sticking out and fitted with homemade scales and typewriter knobs.


Transmitters were another story. A box the size of a coffin was too small to house the massive items making up the more ambitious

spark transmitters. Commercial companies began to group their components for ship-board transmitters on slate or hard-rubber panels—one manufacturer even used marble! These panels were mounted on a vertical metal framework of angle iron.

The dawn of the vacuum-tube era ushered in a new day. Receivers rapidly progressed to cabinet-style housings with controls on the front panel. Panels progressed from wood through hard rubber to bakelite, often backed with a metal sheet or tin foil to eliminate body-capacity effects, and finally to all-metal panels. Cabinets weren't far behind, and metal cabinets with matching panels began to appear on the market.

How about transmitters? In the 200-meter

fig. 1. The basic rack framework is built from snap-together aluminum extrusions and castings.

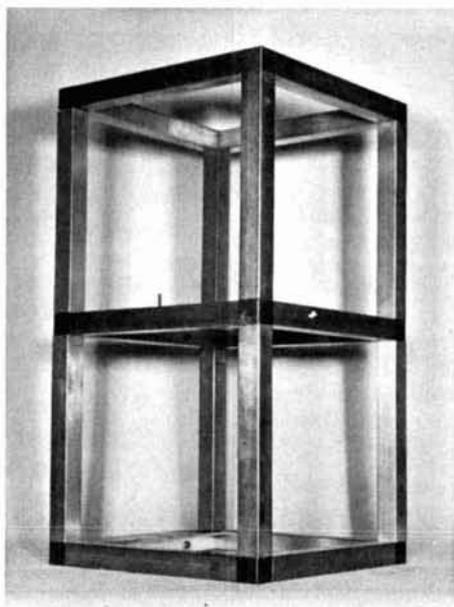

days, the components were rather massive because of the necessity for large spacing to avoid the possibility of flash-over with the high voltages involved. A single cabinet was simply impractical. Vacuum-tube transmission significantly reduced the size of transformers, inductors and capacitors. Again the rack-and-panel scheme looked good. Except for the kilowatt stations, the average low-powered

ham gear no longer required a floor-mounted rack and panel the size of a small closet.

A simple, easily constructed wooden or metal frame occupying about a square foot of table space and standing only a couple of feet high could be used. The idea rapidly caught on; manufacturers started offering metal racks of various heights, drilled for matching panels. Commercial companies adopted a standard panel width of 19 inches and these were available in heights ranging from 1-3/4 to 24 inches in increments of 1-3/4 inch. Later, cabinet racks became available in various heights up to six feet or so.

People have a strong tendency to follow the leader; if an electronics manufacturer encloses his equipment in an attractive metal cabinet and the design catches on, other designers follow the same general pattern. As a result, today's receivers, transmitters and transceivers are almost invariably housed in handsome, compact metal enclosures. This is fine for the ham who is content to place a nice-looking piece of gear on his hand-rubbed, hardwood operating desk in tasteful surroundings, plug it in, twirl a few dials and get on the air. Most of this equipment is pretty reliable; it will sit there and perform for a long time with a minimum of maintenance. But what about the ham who doesn't want to be a push-button operator? There are a **lot** of them and they like to experiment—try this and that, change a switch, a coil—maybe increase power. They hesitate to butcher a piece of factory gear; modifications generally destroy its resale or trade-in value.

The answer? Homebrew of course! But why stick to convention? Hams have always been known to be ingenious, resourceful and quick to come up with new circuits, new ideas. Then why develop a novel electrical design only to become a conformist in the final stage—the housing? Almost invariably, homebrew equipment winds up with the components buried in the bowels of a shallow metal chassis or mounted on a permanently attached panel.

You have to be a contortionist to wire such an arrangement. Poking a hot soldering iron down in the recesses of a crowded chassis generally produces burned insulation, scorched fingers and a string of cuss words!

Changes and modifications which occur from time to time are worse. Can't things be made so that they present a pleasing appearance, are convenient to assemble, wire and modify? Of course they can.

## modern rack-and-panel construction

Let's turn back the hands of the clock a bit—back to the rack-and-panel days of ham radio! However, we are going to do it in the modern mode so that we retain the neat, compact appearance of present-day equipment along with accessibility.

While I was developing a three-band 80-watt transmitter recently, I decided to dip into the past and produce a rack-and-panel job that would compare favorably with the current conception of how ham gear should appear. The result is shown in the accompanying photos.

Your basic unit is the mounting rack. This should be metal. Don't get a sinking feeling envisioning a lot of mitering, hack-sawing, filing, drilling and other strenuous, time-consuming and temper-shortening operations. We've come a long way since we had to be metalsmiths to produce a neat-appearing, substantial job of ham construction.

Take the basic frame shown in **fig. 1**; "Would you believe..." (to paraphrase Maxwell Smart) that cutting the members and assembling this framework consumed just eighteen minutes from the time the raw material was placed in the vise? That's just what it took by the clock! Cutting the aluminum extrusions was like slicing bread; another minute and a few strokes with a file removed the burrs, and the frame members were ready for assembly. With small aluminum castings made especially for use with the extrusions and supplied with springy, toothed locking devices, assembling the final rigid framework was like fastening the snaps down the back of your wife's dress—it was that simple!

Where do you get this kind of material? A good question. There may be others making these aluminum extrusions and castings, but to date I've relied solely on the Ameco Engineering Company.\* Their catalog of small aluminum extrusions and castings is available

\* Ameco Engineering Company, 7333 W. Ainslie Street, Chicago, Illinois 60656.

on postcard request. If you're interested in this type of construction, by all means get the catalog. You'll be surprised at the wide variety of assemblies which you can make up; the catalog shows you how as well. For my project, I used 3/4-inch extrusion for the frame with the castings at the corners and mid-sections.

## construction

The frame was made 8-3/4 inches wide by 16-inches high. For the front panel, I cut the notched ends off a standard 8-3/4-inch high rack panel to reduce the height to 16 inches. These panels should be available at your electronic supplier. If not, most of the mail-order electronics houses catalog them. With the exception of toggle switches, a key jack, an indicator light and a fuse holder, **nothing** was permanently attached to the front panel. The variable capacitors, crystal selector and band switches were mounted on a subpanel on the rf baseboard. This arrangement permits removal of either the power supply or the rf deck **without** unsoldering a single wire. By removing a few knobs and mounting nuts, either of the two decks can be taken out of the frame from the back.

What about the rf and power-supply sub-assemblies themselves? These are also a throw-back—breadboards. I used pieces of 1/2-inch plywood cut to fit inside the frame members as shown in the photographs. The tops were covered with thin sheet aluminum and the exposed plywood edges painted black. Two screws through the boards and tapped into the extrusions hold them in position on the horizontal side members of the frame. Before putting them in the frame, the components were wired and mounted on the breadboards—on the workbench where everything was in plain sight and readily accessible. Terminal strips are used for inter-connection between decks with a small wiring harness.

After all the assembly and wiring is completed, the decks are put in position with the control shafts through the front panel, fastened in place, knobs installed, and, after connecting the wiring harness, the rig is ready to go on the air. If there are any changes, adjustments, or modifications required, you

# HEY! HOW ABOUT THAT

## S.W.R. BRIDGE

- MODEL SWB-2
- READS FORWARD AND REFLECTED POWER SIMULTANEOUSLY
- "EASY READ" METERS
- USE FOR REFERENCE POWER METER
- DUAL 100-MICROAMP METER MOVEMENTS
- LOW INSERTION LOSS
- SIZE-5"X2"X2"



# \$15.95

ALLOW \$1.00 FOR  
PACKING & SHIPPING  
CALIFORNIA RESIDENTS  
INCLUDE SALES TAX

THE BEST  
VALUE WE  
HAVE  
EVER  
OFFERED!

MAY BE LEFT  
IN LINE, UP  
TO 2000 WATTS.

GOOD THROUGH  
2 METERS

SINCE 1933

FAST SERVICE

Phone CY 4-0464

# QUEMENT ELECTRONICS

1000 SOUTH BASCOM AVENUE

SAN JOSE, CALIFORNIA

"Northern California's Most Complete Ham Store"

95128

slide the rack out of the frame, put it on the bench, and go to work on it in comfort.

While the rf deck may require frequent removal as your ideas change, the power supply deck will ordinarily remain pretty much in place. If you want to completely rebuild the rf deck, simply slide it out, remove the components, throw away the breadboard and make up a new one—what could be simpler?

This was not intended to be a construction article. If the return to rack-and-panel construction appeals to you, work out your own design to accommodate the components you intend to use. Slightly different dimensions and proportions would be used to accommodate an additional deck for a modulator unit; my transmitter was designed for CW only.


Devise as you plan; for example, the only milliammeter I had available had a long body and required more space behind the main panel than I wanted to spare from the power-supply deck. I simply cut a 4 x 4 x 2-inch utility cabinet in two; this gave me an extension ring one-inch deep which moved the meter forward.

The subpanel on the rf deck is a 6-inch square of 16-gauge aluminum, mounted vertically on the front edge of the breadboard. The tuning capacitors, band switch and crystal selector are mounted to this subpanel and permanently wired into the circuits. When the rf deck is placed in position in the rack, the subpanel fits up against the back of the main panel with all shafts protruding through matching holes in the main panel.

As a final step, to suppress TVI and for safety, I enclosed the open areas of the frame in a piece of perforated sheet aluminum. It is available at local hardware and building-supply stores. It is easily cut with small tin snips and easily bent by hand to fit the frame. A few strategically placed 6-32 machine screws tapped into the frame members hold the ventilated shield in place.

Frankly, I'm rather proud of this little piece of rack-and-panel fabrication dug from the distant past. I have a nice-appearing rig, well ventilated, handy to work on and it adds a distinctly professional flavor to my shack—give you any ideas?

ham radio

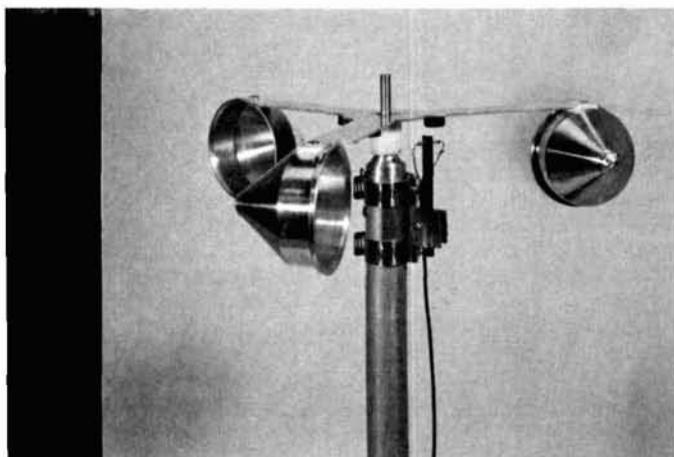

The anemometer wind head. This unit features a teflon bearing and magnetic pickup for long life.

## an amateur anemometer

Here's  
a simple gadget  
that will tell you  
when to  
crank your tower down

Hank Olson, W6GXN, P. O. Box 339, Menlo Park, California 94025

Say, beam owner, when the winds are abroad, and you're warmly tucked in the sack, does sleep come easily? The haunting question, "Will I find my antenna farm in a big pile in the back yard?" gnaws at your brain, and sleep is elusive.

The question of just what to do about protecting your antennas against winds has as many answers as there are antenna types and weather variations. One thing is sure, however; if you are to batten-down for a wind storm, you must know that it's coming. The weather bureau furnishes storm warnings, and by heeding them you won't be caught with your beam down. However, if the antenna is hauled down every time the small craft come in, you can look forward to a busy year of battening down.


Having your own anemometer is another way of determining, for yourself and in your own exact location, whether the wind warrants the work. By keeping an eye on wind velocity, and adopting some criterion of unsafe levels, you're all set.

You can buy a simple, remote-reading anemometer for as little as \$25.00, but the types that are most commonly found in ham shacks cost about \$100.00. The anemometers I have had experience with have worked



The funnels originally had handles; the hole left after removing the handle was used for mounting to the spider tip. A dab of General Electric RTV (Silastic), widely sold for bath-


**fig. 2. Pole structure of the miniature bulletin-board magnets used in the anemometer.**

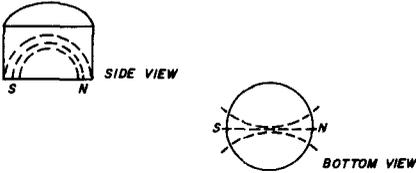

tub and shower caulking, was used to secure the funnel-spider union. The stem of each funnel was also removed and some of the excess metal bent in to close the cone; RTV was used to finish the sealing job.

Three magnets are attached to the spider arms, 1-1/4 inches from the center. RTV is used to cement the magnets to the arms. The magnets must be oriented so that their north-south pole line is tangent to the circle in which they turn. The magnets I used were inexpensive ceramic types (3 for 25c) made for bulletin boards. Their pole structure is shown in **fig. 2**. You can determine the N-S pole line with a small bar magnet. The mount-

**fig. 3. Layout of the wind-head "spider" and location of the magnets. The length of each of the arms is 10-1/2 inches, measured from the center.**

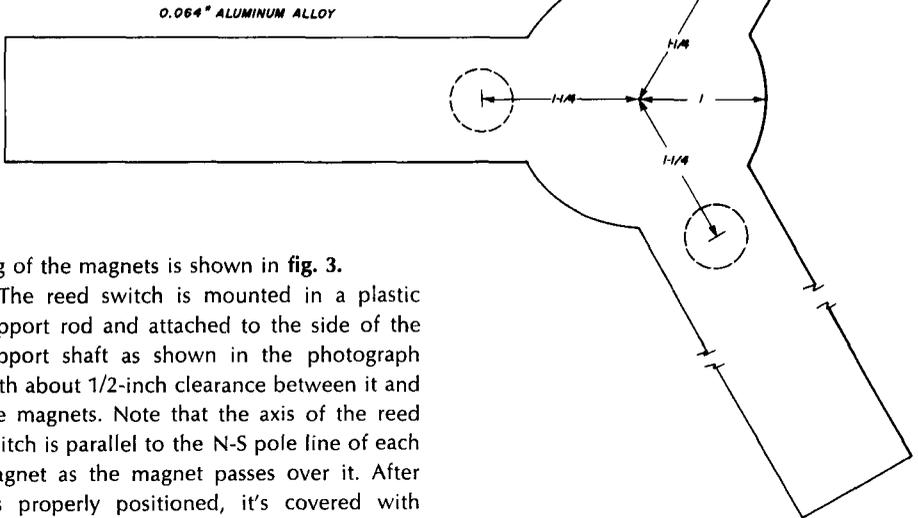

ing of the magnets is shown in **fig. 3**.

The reed switch is mounted in a plastic support rod and attached to the side of the support shaft as shown in the photograph with about 1/2-inch clearance between it and the magnets. Note that the axis of the reed switch is parallel to the N-S pole line of each magnet as the magnet passes over it. After it's properly positioned, it's covered with bathtub caulk.

The main bearing was made of Teflon because it is self-lubricating and should stand up in the weather. I felt that a brass sleeve or ball bearing would lose its lubricant in a driving rain. Probably nylon would do as well as Teflon here, but I didn't try it.

The reed switch is connected to the electronics package through a suitable length of coax—RG-58/U or RG-174/U. The shielded cable was used to keep stray local rf out of the electronics.


The circuit of the indicator is shown in **fig. 1**. It was built in an LMB-WO1A cabinet with self-contained batteries. The pulse length is set by the resistor R, producing a pulse length of about two milliseconds.

### calibration

The anemometer system may be calibrated fairly accurately by mounting it on your car and making various runs up and down a

straight road on a still day. Early Sunday morning seems best for these tests in my area. For best accuracy, your speedometer

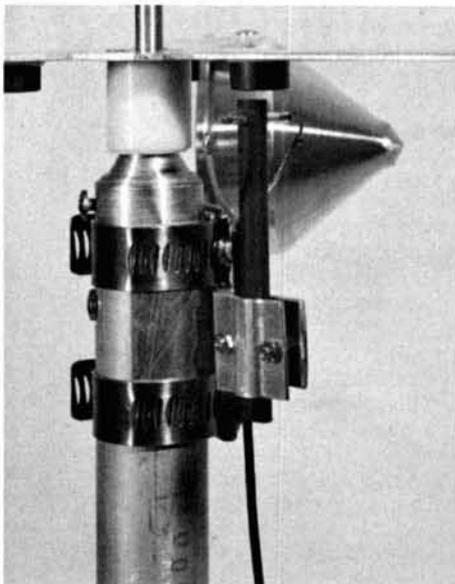Closeup of the wind head showing the reed switch support and teflon bearing.



should be checked at the AAA or similar facility and the wind head mounted on a 2 x 4 that puts it out ahead of the automobile.

ham radio



"Now do you understand what a squelch circuit is, dear?"



## JUNE CLEARANCE!

### RECONDITIONED HAM GEAR RECEIVERS

<b>COLLINS</b>	
75A3 3.1 KC Filter	\$219.00
75S-1	349.00
75A4	349.00
516F2 AC Power supply	110.00
<b>DRAKE</b>	
2CQ QMultiplier	\$ 29.00
L4 (Brand New) Linear (sealed cartons)	595.00
<b>HALLICRAFTERS</b>	
SX99	\$ 79.00
SX100	130.00
SX101-Mk-III	169.00
<b>HAMMARLUND</b>	
HQ140X	\$119.00
HQ160	159.00
HQ170	179.00
HQ170C	189.00
SP600-JX17	249.00
<b>HEATH</b>	
HR-20	\$ 89.00
GR-64	49.00
<b>NATIONAL</b>	
NC173	\$ 79.00
HRO 50 R w/Prod Det (4 Coils)	109.00
NC 270	119.00


### TRANSMITTERS

<b>COLLINS</b>	
32S-3	\$575.00
<b>CLEGG</b>	
Venus-Xceiver-6M SSB (Like New)	\$319.00
<b>DRAKE</b>	
T-4 Reciter to transceiver w/R4A	\$239.00
<b>GONSET</b>	
G-50 6M XCVR	\$189.00
G-77 w P/S	39.00
<b>HALLICRAFTERS</b>	
HT 32	\$219.00
HT 37	229.00
HT 41 LINEAR	159.00
SR 46 A 6 meter xcvr	149.00
<b>HEATH</b>	
HW12 80 Meter XCVR	\$ 89.00
HW32 40 Meter XCVR	99.00
<b>NATIONAL</b>	
NCL-2000 Linear	\$389.00
<b>P &amp; H</b>	
6-150-6M converter-mixer SSB	\$189.00
<b>SWAN</b>	
SW175 xcvr 75 meters	\$129.00
SW120 xcvr 20 meters	119.00
SWAN 250 6 meter Transc.	229.00
<b>RTTY</b>	
Mod. 15 teletype machine	\$ 89.00
Mod. 14TD-units	45.00
Mod. 14 Reperms w/keyboard	49.00

ALL CASH ORDERS SHIPPED FREE  
IN THE 48 STATES
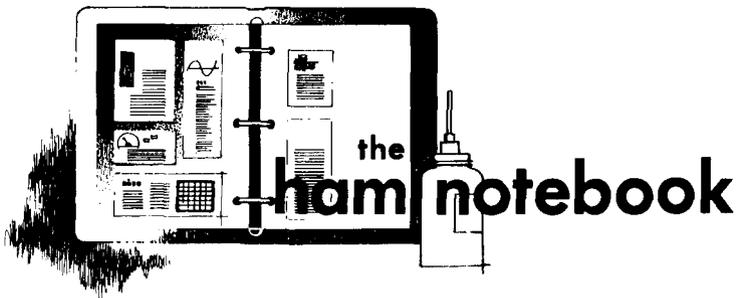
# MISSION HAM ELECTRONICS

3316 Main Street, Riverside 3, California 92501  
Phone 682-0523 (area code 714)



## converting wavelength to inches

It is always exasperating when you have to convert free-space wavelength from meters to inches when you're building an antenna or making a balun. With the help of a simple jingle and a little long division, three-place accuracy is easy:

*"Eleven point eight-o-three inches per k-M-z."*

Here's how it works for 432 MHz (3/4 meters):

$$\frac{11.803 \text{ in/kMz}}{.432 \text{ kMz}} = 27.321 \text{ inch}$$

For coax it's:

$$\frac{11.803 \text{ (in/kMz)}}{\text{Velocity constant x frequency (kMz)}} = \text{coax (inches)}$$

**WA6SXC**

## Motorola MPS transistors

Plastic transistors carrying MPS numbers below MPS6500 are made by Motorola and are similar to 2N transistors carrying the same number. MPS stands for Motorola Plastic Silicon, and numbers over 6500 are special transistor types.

**W2DXH**

## coaxial cable supports

The opener flaps on the new aluminum beer and soft-drink cans make very strong supports for coax cable. Bore a small hole in the flap for a screw or a nail.

**Don Farrell, W2GA**

## s-meter readings


If you have ever wondered what the S-meter readings actually indicate, the following chart may be of some help. This chart is based on an input signal of 50 microvolts at S-9 and 6-dB steps between each S-unit.

s-meter reading	signal strength ( $\mu\text{V}$ )
1	0.18
2	0.37
3	0.75
4	1.5
5	3.1
6	6.25
7	12.5
8	25.0
9	50.0
9 + 10 dB	158
9 + 20 dB	500
9 + 40 dB	5,000
9 + 60 dB	50,000
9 + 80 dB	500,000

That 80 over S9 report you just got means that you have a half-volt signal into the other fellow's receiver.

**Jim Fisk, W1DTY**
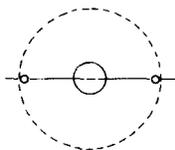
## punching aluminum panels     soldering fluxes




After breaking my share of Greenlee chassis punches, I have found a way of using them on 1/8" aluminum panels. First, drill your starting hole; insert the drive screw; screw on the cutter; and rotate the cutter by hand to scribe a circle. Then scribe a line through the circle; drill two small holes just **inside** the circle where the points of the cutter touch the panel. These two holes allow the cutter to shear the metal rather than punching through it with "brute force."

**Joe Kofron, W7DIM**

There may be some confusion regarding the use of "soldering paste" mentioned by VE3GFN in his article on page 74 of the March 1968 issue of **ham radio**. Although Mike used the term "soldering paste" once modified with the term acid-free, I'm sure he doesn't refer to No-Korode and similar fluxes. These paste fluxes are suspensions of zinc-chloride and ammonium chloride, aqueous solutions in grease. They are excellent fluxing agents for most common metals other than stainless steel, but the residue that is left after soldering is highly hygroscopic. Reaction of water with the residue produces hydrochloric acid. Obviously, this is no material to use with electronics equipment. The inorganic residue is not affected by low heat and requires about 1300°F to be boiled off. It is difficult to remove by washing.

**Dave Heller, K3HNP**

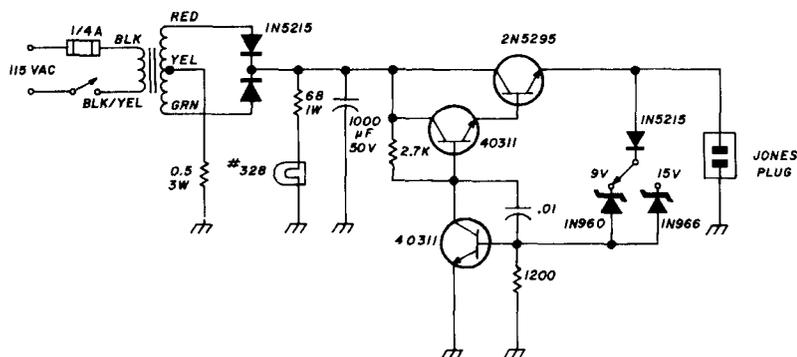

**WB2EGZ's low-voltage power supply. The transformer is a Triad 91X or equivalent.**

## a low-voltage supply

It doesn't take a big power supply with meters, fancy panels and a big transformer for most of the work around the shack. The relatively simple unit shown here is compact, *inexpensive*, and *handles many of my needs*, including the broad category of a second supply.

On the premise that one of two voltages will operate most solid-state amateur converters, receivers and transmitters, a two-voltage supply was devised. Either 9 or 15

volts is available and regulated at any current up to 1 ampere. The series pass transistor is a 2N5295—a low-cost RCA plastic unit, but a TO-66 type, such as the RCA 40310 or 2N3054 is suitable if you can't find a 2N5295.

Any small chassis may be used, but my unit was mounted in a 4 x 2-1/4 x 2-1/4-inch Minibox. The power transistor is heat-sunk with insulating washers and thermal compound to the minibox. Wiring is not critical. You can obtain other fixed voltages by using a 400-mW zener diode of the desired voltage.

**Don Nelson, WB2EGZ**

## LOW PRICE, QUALITY, COAXIAL SWITCHES ...



Don't pay for the 5th and 6th position. The average HAM rarely uses more than 4!

**SPECIFICATIONS:** Silvered Contacts. Write-on ERASABLE escutcheon plate. AVAILABLE EITHER 4 PST (COAX-4) OR LINEAR (COAX-LINEAR) IN-OUT VERSION. Handles 1000 W AM or 2000 W SSB. Insertion loss negligible to 160 Mc. VSWR: Less than 1.2 at 160 Mc. Size: 3/8" dia. x 1 1/8" overall. Single hole mount. SPECIFY MODEL. \$7.65 ea.

## COAXIAL LIGHTNING ARRESTORS

Zero power loss. No increase in SWR at 150 Mc. Does not attenuate signals. Model 210 for 1000 W (AM) or 2000 W (SSB). Model 211 Electronic static arrester for 50 W (AM) or 100 W (SSB). SO-239 UHF type fittings. Other fittings available. Size approx. 3/2" x 1/4" dia. #210 \$3.15 ea. #211 \$4.65 ea. SPECIFY MODEL #.



PRICES above are amateur net. Shipped ppd. in U.S.A. Send Check or M.O. (N.J. ADD 3% Sales Tax)

OTHER PRODUCTS: Feed thru capacitors. Tuned noise filters. Alternator, generator, low-pass and field filters. SEND FOR CATALOG.

**"COMMUNICATION ENGINEERED"**  
By "HAMMIE" RICHARDT—W2WIY

ELECTRONIC APPLICATIONS CO.  
ROUTE 46, Pine Brook, N. J. 07058

# FM

Primary FM BULLETIN

## THE national FMers' journal

A MONTHLY HAM MAGAZINE  
FOR THE AMATEUR WHO IS  
INTERESTED IN:

SIMPLEX FM, REMOTE OPERATION, SIGNALING & TONES, CONTROL TECHNIQUES, CONSTRUCTION, DECODING, FREQUENCY LISTINGS, MOBILE FM, MOBILE RELAYS, AUTOMATIC PHONES, DESIGN DATA, REPEATER INFO, TRENDS, OPERATION, NEWS, VIEWS, HUMOR, SATIRE, CLUBS, ACTIVITIES, DIRECTORIES, EVENTS,.....

....SPECIAL OFFER AT JUST \$2.00 PER YEAR UNTIL  
MAY 31, 1968....REGULAR RATES WILL THEN BE ...

\$3.00 per year or 2 years for \$5.00

SAMPLE COPY 35¢

FM MAGAZINE

2005 HOLLYWOOD AVENUE  
GROSSE POINTE MICHIGAN 48236

## tilt your rig

Modern operating practice for receivers, transmitters and transceivers calls for the cabinets to be slightly tilted. However, most equipment is shipped with four equal-length legs.

To tilt your gear slightly, measure the diameter of the legs at the front of the rig. Then buy some rubber crutch tips from the dime store or your hardware dealer. These will raise the front of the rig sufficiently to allow easier operation. If they're properly fitted to diameter, they slip on and off easily and provide a modern appearance for your operating desk. Cost? 30¢!


George Haymans, WA4NED

## small parts trays

The flat aluminum trays used for TV dinners and make excellent trays for holding small parts and screws while you're building or repairing ham gear.

Don Farrell, W2GA

## transistor storage

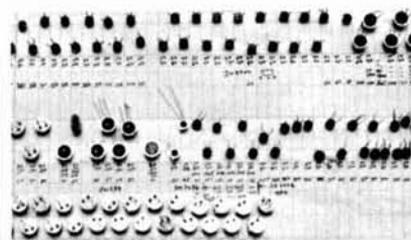

Finding a place to store transistors that have measured characteristics can sometimes be a problem. Try this: lay several pieces of double-backed masking tape across a piece of cardboard as shown in the photograph. Then, stick the transistors to the tape and write their characteristics just below. You can remove and replace the transistors many times if you use this method.

Tom Lamb, K8ERV

NATIONAL  
NCX-200  
complete 80  
thru 10 meter  
coverage for  
SSB, CW, and AM



**SAVE  
\$60.65**

National NCX-200 Transceiver .....	\$359.00
National AC-200 AC Power Supply .....	75.00
National XCU-27 100kc Calibrator .....	26.60
REGULAR PRICE .....	\$460.60

**SPECIAL PACKAGE PRICE  
\$399.95**

- ★ **NO DOWN PAYMENT** WITH APPROVED CREDIT      PAYMENTS AS LOW AS \$13 MONTHLY
- TIME PAYMENT ANYWHERE IN U.S.A.
- ★ **NO INTEREST OR CARRYING CHARGE** IF PAID WITHIN 45 DAYS
- ★ **IMMEDIATE DELIVERY**
- ★ **BIG TRADES** WRITE FOR QUOTE ON YOUR PRESENT GEAR

**EDWARDS  
ELECTRONICS**

TELEPHONE PO 2-8759 / 1316 19TH ST. / LUBBOCK, TEXAS 79401



## some considerations about speech processing in amateur equipment

Since the inception of voice-modulated radio communications, engineers have recognized that speech processing was absolutely essential so you could get optimum use of the system without exceeding its peak-power limitations. The schemes that have been used to accomplish this restriction of peak excursions have fallen into two general categories: agc or alc control, or clipping. The agc system uses feedback to control the gain of one or more amplifier stages, thereby keeping them within their linear operating range.

Rather complicated agc systems are used by every broadcast station in the United States to maintain the average modulation level within prescribed limits. In addition, most modern amplifiers which are designed for amateur use incorporate a feedback system to prevent overmodulation, and keep the modulation level up.

Unfortunately, the "clipping" system of speech processing has earned a poor reputation because of misuse and a general misunderstanding of its advantages and limitations. The important differences between the two approaches is time. The agc system uses

feedback with its associated time constants; the clipping method has no time constants other than the attack time of the device that does the actual clipping.

Each system has definite advantages and disadvantages. In general, with a properly adjusted and operating agc-alc system, you can never overmodulate your transmitter. In addition, the modulation level will be maintained within the range of the agc circuit. Essentially then, the agc circuit generally keeps the system operating within its linear range and acts as an emergency brake in case of overmodulation.

### audio clipping

Clipping systems have advantages and disadvantages not inherent in the agc system. Due to the absence of time constants or long attack times, the amplitude clipper can effectively change the peak-to-average power content in the speech waveform. This is the primary benefit we're all trying to achieve. A linear system modulated with a speech waveform whose average power content has been improved will show the same improve-

J. R. Fisk, W1DTY, RFD 1, Box 138, Rindge, New Hampshire 03461

ment in average output power. However, there are definite disadvantages to the simple clipper technique.

Clipped audio frequencies generate a host of harmonic products which fall within the audio band. In normal a-m transmission, 4 to 6 dB of straight audio clipping is generally considered the most you can use before the disadvantages of high distortion outweigh the improvement in averaged radiated power. Under poor operating conditions, however, this can be a very acceptable technique.


Another disadvantage of audio clipping is that audio processed in this way should not be used to modulate a ssb transmitter. Neither phasing nor filter-type exciters provide the phase linearity required to prevent the audio harmonics from recombining with the fundamental signals. This results in amplitudes that are higher than those present before clipping. A good ssb transmitter with properly operating *alc* will decrease its average power output in order to accommodate the abnormal peaks generated in the exciter by harmonic-rich audio. The system not only suffers from increased distortion due to clipping, it does not provide any benefits of an improved average-to-peak modulation ratio.

Elaborate filter techniques and clipping at rf (which eases the filter problem) have been used to improve this situation, but these systems are clipping three signals at once: the lower sideband, the upper sideband and the carrier. These signals are spaced only by the value of the audio frequency at any given instant; hence their intermodulation products still generate unwanted signals within the up-converted audio band.


With these considerations in mind the next step should be obvious; a speech-processing technique that provides the benefits of instantaneous clipping without the disadvantages of harmonic distortion.
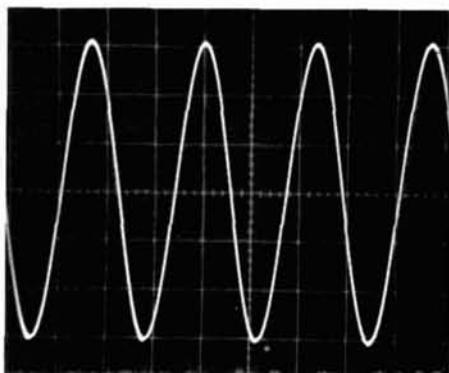
### rf clipping


One answer is rf clipping. This is essentially nothing more than clipping the rf or i-f ssb signal, not the audio. If the single sideband signal is clipped, harmonic products are generated as with audio, but the closest



Pure sine wave at 700 Hz.

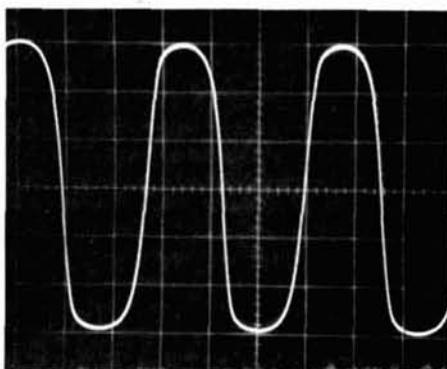

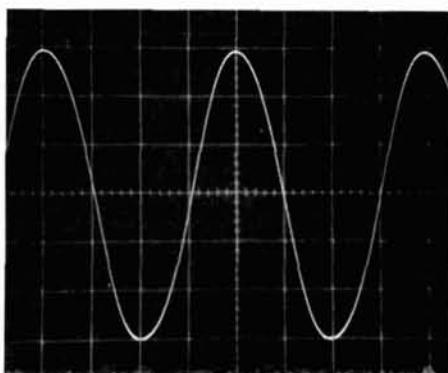Output from a commercial speech clipper with 15 dB of clipping. Note the flattening of the audio peaks.



Output from the Comdel CSP-11 with 15-dB clipping. Note that the output of this speech processor closely resembles the input waveform.

fig. 1. Input and output audio waveforms using a commercial speech clipper and the Comdel CSP-11.


one is removed by at least the value of the i-f frequency. With this approach, the harmonics fall outside the audio band and are easily removed by filtering. The presence of intermodulation products tends to broaden the bandwidth of the signal, so an additional ssb filter is required.

The output signal contains all the original audio information and has an improved average-to-peak power content as much as 15 dB (30 times). This obviously changes the quality of the transmission, but very little distortion is noticed. There is no loss of intelligibility "in the clear" as with a straight audio-clipping circuit, so the rf-clipping circuit may be left in the system permanently.

Modifying existing equipment to incorporate rf clipping is a little bit tricky. For one thing, the additional filter has to track the existing ssb filter very closely, and in practice, this is difficult to achieve. Also, additional gain has to be provided in the right place, since just turning up the audio gain control will cause overloading somewhere—usually in the first balanced modulator.

The Comdel CSP-11, illustrated in block form in fig. 1, is effectively a closed-circuit ssb system incorporating i-f clipping and avoids these difficulties. You can see that there is no frequency error because the same oscillator is used for both generation and demodulation of the ssb signal. The audio out-

fig. 2. Block diagram of the Comdel CSP-11 speech processor.

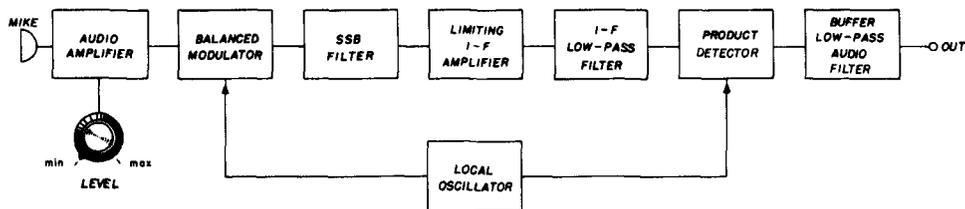

### Comdel CSP-11 Specifications

Frequency response:	500-2500 Hz
Signal-to-noise ratio:	36 dB minimum
Input impedance:	0.5 megohms
Output load:	not less than 6000 ohms
Input level at limiting point:	10 mV peak
Output level at limiting point:	40 mV peak
Power requirements:	9 volts at 18 mA
Battery life:	300-500 hours
Size and weight:	5-1/2 x 3-1/4 x 7-1/2 inches; 32 ounces
Price:	\$120.00 postpaid

\* Comdel, Inc., Beverly Airport, Beverly, Massachusetts 01915.

put of the system is instantaneously peak limited, yet free from harmonic distortion. For best operation, 15- to 20-dB clipping is recommended. The apparent power gain, as confirmed in numerous tests, is often as high as 10 dB at the receiving end.

The circuitry required to accomplish this type of speech processing is quite complex. But power ratio, lack of harmonic content, a fixed known peak audio-input level, and a specifically tailored 3-kHz audio response are well worth the effort.

### references

1. K. Kryter, J. Licklider, S. Stevens, "Premodulation Clipping in AM Voice Communications," *Journal of the Acoustical Society of America*, January, 1947, p. 125.
2. S. E. Stuntz, W1RXX, "Premodulation Clipping and Filtering," *QST*, November, 1950, p. 22.
3. W. K. Squires, W2PUL, E. T. Clegg, W2LOY, "Speech Clipping for Single Sideband," *QST*, July, 1964, p. 11.

ham radio

*New*

*140 dB  
dynamic  
range  
RF  
amplifiers*



PLUG-IN  
MODEL HDR-101ac



IN LINE  
MODEL HDR-102




STRIP LINE  
MODEL HDR-101

**Improve  
system  
sensitivity** RF amplifiers in three package choices from stripline mounting to coaxial "In Line". Constant 9 dB power gain from 0.5 to 50.0 MHz - 140 dB dynamic range. Noise figure negligible; under 3 dB. Unit price range \$75 to \$97 with 10 day delivery. For data or a test sample call or write.

**COMDEL**  
inc.

**COMMUNICATIONS  
EQUIPMENT**

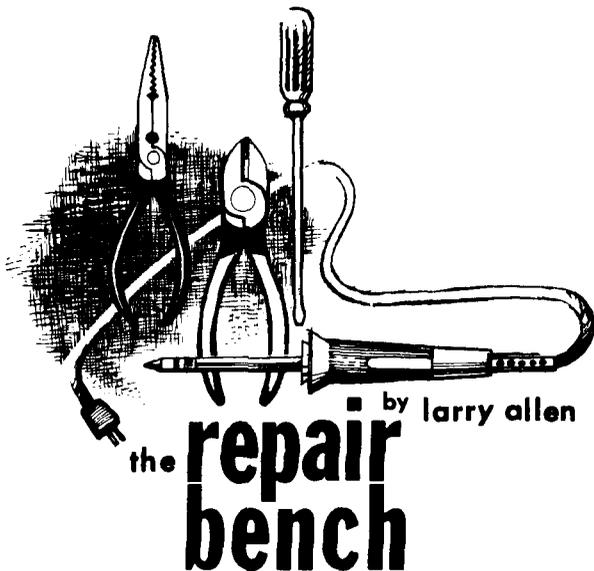beverly airport, beverly, massachusetts 01915  
tel. (617) 927-3144



## ham receiver alignment

**Just about a month ago**, a young college student from down the block telephoned to ask if I could help him. It seems Jeff had built an inexpensive shortwave receiver kit and couldn't get much out of it. Oh, he got some noise, but it was a far cry from the listening he was planning to do.

He brought it over, and we put it on my bench and turned it on. It was a general-coverage receiver, and we could get a few stations in the broadcast band, but very little anywhere else. The top band, which went on up to 30 MHz, was completely dead, even with a beam I have.

I ran through it real quick with the signal tracer and found the *i-f* gain poor. Usually these kits come with *i-f* cans prealigned, so I asked him if he had messed with the alignment screws. He had. The instruction book gave some adjustment instructions, and he had tried to go through them. There wasn't a screw in the *i-f* or *rf* section he hadn't turned. I could see I had my work cut out for me.

My young friend, who aspires to become a novice, had committed a sin that is often committed by adults who should know better. He had attempted to align a sensitive, selective receiver without either knowing how or having the equipment to do it with.

In the first place, you need a small screwdriver and an alignment tool that will fit the *i-f* slug, an *rf/af* signal generator, similar to the one I talked about in this column last

month, and a meter. For good alignment, that generator needs to be fairly accurate. Even better, a heterodyne frequency meter can be used as a source of highly accurate signals. A lot of hams have the old surplus BC-221—I still have mine sitting around. A meter like the Lampkin MFM freq meter is okay for this, too. Anyway, make sure your signal source is accurate. If you have to, check its dial calibration at each of the several WWV or WWVH frequencies, using any receiver that is working. Later, I'll tell you how.

The signal generator output cable is usually terminated in its characteristic output impedance. If not, you can add a resistor of that value across the output leads. In case you don't know the output impedance of your generator, use a 50-ohm resistor. Use a .001- $\mu$ F blocking capacitor, in series with the output lead between the resistor and the set, to make sure no dc reaches the resistor. The sketch shows how.

For an indicating meter, I prefer a vtvm, which I connect to the avc line of the receiver. A few hams and service technicians prefer to use a VOM, set to its "output" function, which puts a capacitor in series with the test lead. They use this as an indicator by hooking it across the speaker or headphone output to monitor the audio developed. The effects of alignment tuning are much broader visualized on this kind of indicator, but the system works.

Alignment has two purposes. One is to adjust all the *rf* and *i-f* tuned circuits so that they pass the correct frequencies as efficiently as possible. In elaborate ham receivers, alignment may even involve some traps to make sure that certain frequencies—such as an upper or lower sideband—are rejected; trap circuits also help steepen the skirts of a band-pass response curve.

The second purpose of alignment is to make sure all the oscillators are operating at the correct frequency, to assure correct calibration of the receiver's dial. Dial calibration is pretty important for both shortwave listening and ham reception. In a simple receiver like the one young Jeff brought by, this part of the alignment can become quite difficult. However, there are ways to overcome the problems, and I'll mention them later.

## lining up the back section

Before you start aligning any shortwave receiver, let it and your test instruments warm up at least a half-hour to stabilize—an hour is better. Stability is important.

The first step is to "calibrate" the detector and the final i-f transformer. The accuracy of the signal used for this step is critical; the effectiveness of succeeding steps depends on this adjustment being made correctly. If the receiver is a multiple-function rig, set the switch for a-m reception. The whole set will be easier to align in this mode. You can clip the vtvm dc—probe to the output of the a-m detector—common lead to chassis, of course.

Connect the signal source at the input (grid or base) of the very first stage of the last or low i-f. Set its frequency very precisely. If the receiver uses a nontunable selectivity filter in conjunction with the low i-f, getting the right frequency will be simplified if you feed the signal in before the filter. Feed in

**Popular kit-type signal generator suitable for receiver alignment.**



only enough of the signal to cause an indication on the meter. Too much will make the tuning so broad you can't really tell when you have peaked a tuned circuit.

Start with the transformer winding nearest the detector. Work your way back toward the input of the i-f section. When you get back to the input transformer of the section, peak it as best you can. It may be a little broad, because of the connection from the signal source. Later, when you have the signal source connected further toward the front

of the receiver, be sure to come back and repeat this one adjustment; you'll usually find the true peak slightly different.

Go through the i-f strip twice. You want to be very sure it's aligned correctly. If this is the last i-f of a double- or triple-conversion receiver, the frequency may be as low as 50 or 60 kHz; on the other hand, it could be as high as 2 or 3 MHz. In Jeff's receiver, it was 455 kHz. Transformers for that frequency are inexpensive and plentiful.

## the middle i-f

This part of the receiver differs considerably from model to model. If the receiver is double-conversion, it may be called the high i-f, being the only one other than the low i-f. It may be a broad-banded stage, if the tuning is done **after** it. (Examples are the Heathkit SB301 and the Collins 75S-1. Both use a crystal-controlled heterodyne oscillator for first conversion and a tunable **linear master oscillator** (LMO) for the second.) In expensive receivers, a bandwidth filter may be used for this i-f instead of tuned circuits; it is not adjustable.

Generally speaking, the **best** place to feed in the test signal is at the grid of the mixer preceding the i-f strip you're about to align. This isolates the output cable of the signal generator, and eliminates the need to re-peak the first input slug.

## the low-cost front end


One problem with an inexpensive receiver is poor image rejection. An image, as you may know, is a signal on the other side of the local oscillator frequency from the desired signal, exactly as far from the local oscillator as the desired signal is. In other words, it is a signal that, when mixed with the local oscillator, also produces the i-f of the receiver. The image response is always separated from the desired signal on the dial by exactly **twice** the i-f frequency. With a 455-kHz i-f, for example, the image is 910 kHz away from the desired signal. When you are receiving rf frequencies in the neighborhood of 20 and 25 MHz, an image is comparatively close, percentagewise—less than 1 MHz away. It is not easy for the preselector tuned circuit to block out the unwanted image. In fact, unless the Q of the

preselector circuit is unusually high, good image rejection in a low-cost receiver is virtually impossible.

This means, then, that the oscillator in such a receiver is hard to get calibrated correctly, because you can't tell if you're picking up the signal at the image or at the fundamental on the receiver dial. If you work very carefully, however, you can surmount this obstacle and do a really good alignment job.

Start with a long warmup—both generator and receiver. You want as much stability as is possible. The vtvm is the best indicator for this step; the VOM across the speaker isn't really sensitive enough. You are going to depend on the meter to help you separate fundamental reception from image reception. As

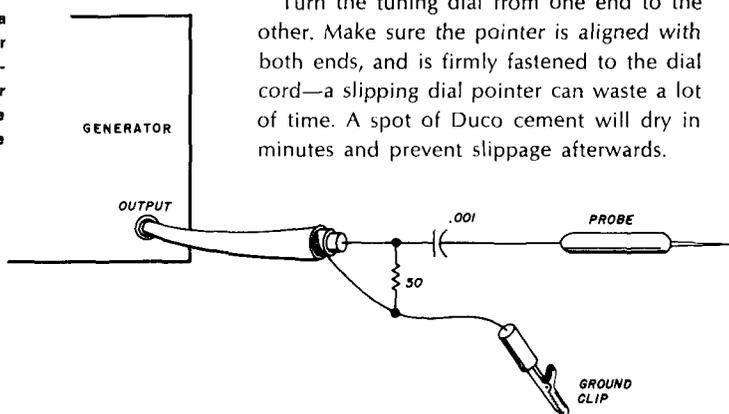**This is how you connect a probe to the output of your signal generator. The resistor terminates the generator cable in a 50-ohm load; the capacitor isolates it from the dc supply in the receiver.**



a general rule, use only enough signal—fed to the antenna terminal of the receiver—to cause an indication on the meter. Any more will distort the avc action of the set, and make accurate alignment difficult.

Make it a rule always to start with the high-end band. In some receivers, adjusting the high bands affects low-band adjustments. In any case, it's a good idea to start with the high band—get the tough part done first.

There are three steps to each phase of front-end alignment, once you have all the i-f's precisely adjusted. The first step is calibrating the high-end dial frequency, with the oscillator trimmer capacitor. The second is adjusting the low-end dial frequency, usually by adjusting a slug in the oscillator coil. There is interaction between these two adjustments;

you have to go back and forth several times. It is very important that you make sure you do not align either end with an **image** signal. The third step is alignment of the rf tuned circuits. There may be more than one rf adjustment. The instruction manual that comes with your receiver will tell.

In preparation for the actual adjustments, make yourself a chart of their locations. Figure them all out **before** you start sticking a screwdriver into them. During the alignment your attention should be on the frequencies and on peaking the adjustments; you have no time to be figuring out where each one is. Label them with a pencil if you can. Do anything to avoid touching the wrong trimmer, because you might then have to begin all over.

Turn the tuning dial from one end to the other. Make sure the pointer is aligned with both ends, and is firmly fastened to the dial cord—a slipping dial pointer can waste a lot of time. A spot of Duco cement will dry in minutes and prevent slippage afterwards.

Now for the first adjustment: the high-end oscillator adjustment for the top-most band. Set the rf generator, modulated, to 30 MHz. Your first job is to identify the image so not to confuse it with the main signal. Tune back and forth in the neighborhood of the high end of the band, and you will hear signals at two points. Tune in one with the receiver dial, very cautiously and carefully, tuning for a maximum meter indication. Then do the same for the other. Notice which dial position produces the higher meter reading. That one is the fundamental.

See where the dial pointer is. If it is not indicating 30 MHz exactly, you'll have to readjust the oscillator trimmer capacitor for that band. Be sure you have the right one. If the dial is off very far, there is only one way

to bring the dial reading into proper position without confusion: Turn the dial just the tiniest bit in the direction to correct its reading, but not so far you lose the sound or the meter indication. Then adjust the trimmer to make the reading strong again. Next, move the dial a little closer to the correct setting, until you almost lose signal again. Then again peak the trimmer. In this manner, you can slowly “walk” the trimmer and dial right onto the correct frequency setting without losing the proper signal and inadvertently zeroing in on the image frequency.

Next, you have the same job to do at the low end of the same band. This might be around 15 kHz, for example. Set the generator to precisely that frequency. Tune the receiver *around the low end until you find the fundamental frequency*; again, use your meter indications to make sure you don’t have the image tuned in. Then, adjusting the slug in the oscillator coil for that band, slowly “walk” the signal onto the correct 15-MHz spot on the dial.

When you tune back to the high end of the dial, you’ll find the frequency has shifted slightly, especially if you had to do much adjusting at the low end. Again, tune in the fundamental 30-MHz generator frequency, being sure it’s not the image, and “walk” the trimmer setting until the dial is accurate. Repeat at the low end and repeat at the high end. Final adjustment should be at the high end, because the oscillator slug has less effect on the over-all frequency.

Before you move to the oscillator adjustment for the next band, make the rf adjustments for this one. There may be a high-end and a low-end adjustment in the rf section, in the more elaborate receivers. Otherwise, there will only be a high-end trimmer or two to adjust. Again, be sure the signal you’re feeding in and tuned to is the fundamental one. You don’t have to “walk” the adjustments in the rf section. Just tune the dial for maximum indication on the meter. Then tune the trimmers—and slugs, if there are any for low-end adjustment—for maximum.

Next, go to the band next below in frequency. Go through the same procedure: First, the high-end oscillator adjustment, “walking” the dial setting into proper posi-

tion. Then the same for the low-end—and then back and forth between the two until both ends are accurate. Finally, peak the rf adjustments. You’ll find that separating the fundamental from the image becomes much easier as you get down in the lower bands, because the 910-kHz (or whatever it is) signal has a wider spread on the dial. In the lowest band, usually the broadcast band, you will have no trouble at all; the image is half the dial length away.

Finish by aligning each band all the way down to the lowest, repeating the procedure already outlined. When you are finished, if you really care about calibration, accuracy, and sensitivity, start with the high band and double-check the high- and low-end frequency settings.

You may want to check the **true** calibration of the receiver, to overcome any inaccuracies the signal generator may have, especially in this highest band. A good test is to tune in the National Bureau of Standards station, WWV, at 15 MHz. You’ll have to do this at a time of day when the band is open. If you can, tune also at 20 MHz and 25 MHz. You may not be in the right locality for best reception at those frequencies, but you can check them whenever propagation permits. See if the receiver dial is correct. If you find the dial is not accurate, make the correction only with the oscillator **trimmer**.

Make the same WWV test in the lower bands, using the 10-MHz and 5-MHz WWV signals. Remember to make corrections only with the oscillator trimmer; **do not** change the oscillator slug. Some night, you can also check at 2.5 MHz, using WWV or WWVH.

The broadcast band is easy to check out, because broadcast stations must be very close to correct frequency. Tune one at the high end and correct the dial calibration with the oscillator trimmer. Pick one at the low end and correct it with the oscillator slug. As you did with the generator, go back and forth to get each precise.

### **verifying generator accuracy**

Probably the handiest way to do this is with a freq meter. The simplest way is just to feed the outputs of the generator and the freq meter into a receiver. It doesn’t really matter

whether the receiver is in alignment or not, since all you are actually doing is using the receiver as a detector to detect the beat between the two.

Set the frequency meter precisely for whatever frequency you want to check—say, 20 MHz. Set the generator there, too. Tune the receiver until you can hear the signals beating together. Don't use an antenna. Swing the generator dial until you hear the whistle caused by the beat between the generator and the frequency meter signal. Swing it slowly back and forth until you find the exact zero

beat between the two. See whether the generator dial actually rests at 20 MHz. You can plot any inaccuracies at intervals of about 5 MHz, and use the graph as a correction factor when you're calibrating a receiver dial.

Another way to check accuracy of the generator is with the receiver and WWV (or WWVH). Just tune in at the 2.5-, 5-, 10-, 15-, 20-, and 25-MHz signals. Then check to see if those corresponding signals from the generator are accurate on the generator dial. A zero beat is your guide to precise tuning.

**ham radio**

## simple untuned crystal mount

Many times in amateur UHF and microwave work you need an untuned crystal mount for detection of small levels of rf energy. Usually a small diode and bypass capacitor are simply haywired into the circuit, but this method usually causes some problems. First of all, if the frequency of operation is high enough and the lead lengths are too long, a lot of the available energy will be radiated. Furthermore, the parasitic reactances, as a result of the lead lengths associated with the capacitor and diode, can cause some rather mysterious results.


This crystal mount is based upon the use of two standard coaxial cable fittings, a type-N jack, the UG-23D/U, and a type-BNC jack, the UG-89B/U. Both of these fittings are available at reasonable prices. To build the mount, discard the braid-clamping washer and rubber gasket from the type-N connector. Then take the female pin and carefully squeeze the large end so that it is a snug fit around the pin of a 1N23-type diode.

Ream out the type-N cable-retaining nut so that a 1000-pF button capacitor may be force fit into the opening. Bend one of the tabs on the capacitor over so it will provide a spring contact to the diode when the nut is screwed into the connector. Bend the other tab so it comes straight up from the surface of the capacitor.

Remove the cable-retaining nut from the BNC connector, and place it on top of the type-N nut. Now, solder the whole works to-

gether, the N and BNC nuts and the feed-through capacitor. Make sure that the N nut has been reamed out sufficiently so the BNC nut sits flush and level. The easiest way to solder the parts together is on an electric stove or hot plate.

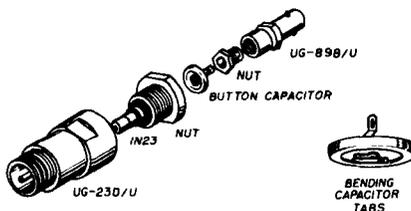After this assembly has cooled down, solder a short piece of wire about  $\frac{5}{8}$  of an inch long to the upright tab on the button capacitor. Place the female pin from the BNC connector



over the end of the wire and put the BNC connector on to test for proper wire length. The wire should be trimmed so that the end of the female pin is flush with the center insulator in the connector. When you find the right length, solder the female pin to the wire.

To use the completed mount, connect a sensitive dc microammeter across the BNC connector, apply some rf energy to the type-N connector, and you're in business. In most UHF and microwave work, the type-N connector will fit right in with existing equipment.

**Jim Fisk W1DTY**



## Radio Society of Great Britain Publications

The various handbooks and publications of the RSGB have been well known in amateur circles for many years and have an excellent world-wide reputation.

The RSGB is currently revising most of these books and two titles are already available. Communications Technology, Inc. is privileged to be able to bring them to you in the United States.

### **RADIO DATA REFERENCE BOOK**

Second Edition

**By G. K. Jessop G6JP**

Here in a 148 page book is one of the most complete compilations of radio and electronic charts, nomographs, formulas and design data available. Sections are included which permit you to design everything from rf power amplifiers to TVI filters. Also included is much related information such as world-wide frequency allocations and commonly used mathematical tables. *Whether you design, build or operate, this is a book you should have.*

Only \$2.50 postpaid in the U.S.A.

### **WORLD AT THEIR FINGER TIPS**

**John Clarricoats G6CL**

This book is a very thorough history of the RSGB and of amateur radio in Great Britain. It gives a great insight into the development of our hobby in England and Europe and the effects these events have had on amateurs here in the United States.

Paper back edition \$2.50 postpaid in the U.S.A.

Deluxe edition \$8.00 postpaid in the U.S.A.

### **Book Division**

**COMMUNICATIONS TECHNOLOGY, INC.**

**Box 592**

**Amherst, N.H. 03031**

One of the more highly publicized bugs is this "007" sugar-cube mike. It is completely self-contained and will transmit up to several hundred feet.



## electronic bugging and the ham

The true  
story behind the  
"electronic  
bugging"  
headlines

Robert M. Brown, K2ZSQ/W9HBF, 5611 Middaugh  
Avenue, Downers Grove, Illinois 60515

Surprising though it may seem, very few surveillance devices are more complex than those shown in this article. For the most part, these simple devices reflect the vast majority of gadgets employed today. Exceptions are custom-built designs used by the CIA and a few other federal branches who have the funds available to develop more advanced (and generally higher-powered) bugs for specific applications. If you can ignore the mass-media spy syndrome ("Get Smart," "U.N.C.L.E.," etc.), you are well on your way.

Basically, the bugs break down into two major types: the audio-microphone group using connecting wires, and self-contained rf transmitters. Countless variations exist, yet these are the exception rather than the rule. Quite naturally, the microphone-types are the least expensive since they aren't nearly as complex as the transmitters and require a bit more installation time. One company that specializes in low-cost mike configurations is Consolidated Acoustics of Hoboken, New Jersey. Perhaps the largest direct-mail solicitor, Consolidated offers mike kits to put together everything from wall-listening devices to parabolic-dish long-range snoopers and also offers inexpensive telephone induction

systems. These normally make use of a Philmore-type pickup coil placed near the phone sidetone coil. Output is coupled into a nearby audio amplifier, recorder, or rf transmitter tuned to the fm music band. While a big outfit in terms of sales, Consolidated's offering is pretty simple in concept. Audio amplifiers, crystal mikes, cabling, and recorders comprise the bulk of equipment sold, and this is fairly illustrative of their competitors, too.

The more recent outpouring of tunable fm band transmitters, however, poses a more serious threat to the potential victim. While pretty much short in range capability (few travel more than 300 yards at 100 MHz), countless forms are taken, since the tiny one-

**Common bugs.** To the left is the model 003; a parallel-connected fm phone bug with a 1/4-mile range. In the middle is a model 001 series-connected phone bug with a 1/2-mile range powered by the telephone. To the right is a model 003A, a room transmitter similar to the 003 with a built-in microphone.

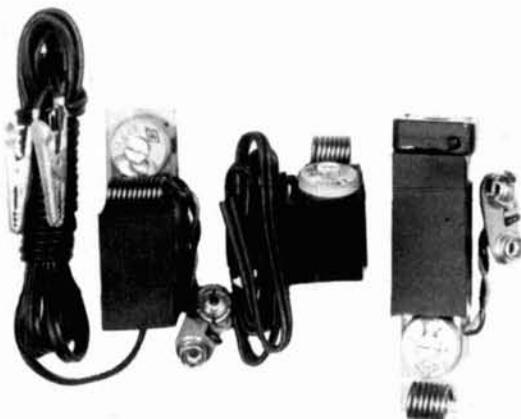


Photo courtesy L. N. Schneider

way devices can be hidden practically anywhere. Although phone bugging is very big right now, these transmitters have turned up behind pictures, inside ashtrays, disguised as diaries, in pen desk sets, and in table lamps. While not elaborate in design circuitry, they're assuredly strong in imaginative application.

Feeding from both sides (microphone-wire, and transmitting) the electronic tailing business emerges. The assortment of car bugs and bumper beepers now saturating the market-

place seems to be a combination of several techniques, with heavy emphasis on rf transmission. Interestingly, these devices are found as voice-bugs, strategically located under the dash and powered by the ignition system with an antenna coupled to the car radio whip, and as pulsed-tone beepers, emitting a constant a-m or fm signal interspersed with a 400-Hz note, antenna trailing just above the road surface. Regardless of method, the tracker assumes the identity of a ham or CB'er, using a vehicle well-equipped with a directional loop antenna, or phased whips coupled to a receiver under the dash. Complex triangulating systems are frequently employed with the aid of other vehicular operatives linked together with a CB set and zeroing in on the target. Yet, even the single agent can approximate distance and direction by looking for a null between the two phased antennas and noting S-meter readings.


While it has been said that telephone bugs have been the biggest boon to the surveillance industry, it is the tailing devices which have had the greatest application to the largest number of U.S. private investigative firms, since they cut required manpower enormously and enable safer tails (ones in which the target car does not have to be in direct sight of the operative).

Even this grouping is not exotic in terms of equipment function or design. From an amateur standpoint, in fact, the majority of devices now in use are rather behind the times. Very few employ IC's, and even fewer make use of tunnel diodes or FET's, although basic solid state long ago replaced vacuum-tube types. The exception to this is the 117L7GT a-m room bug made in Florida and designed to be permanently installed in the wall of a freshly-built apartment or home. This type is constantly on, drawing power from the household currents and transmitting on a frequency just above the tuning range of conventional a-m radios. It is good for the life of the tube, normally several years, since plate current is resistively dropped below the amateur norm. Most of the circuits employed in transmitting devices are straight from an old **Popular Electronics** or **Radio-TV Experimenter**, with certain improvements and changes made in the tanks and power supplies.

## transmitting eavesdrop "plants"

I think we can safely assume that the experienced ham already has a good deal of working knowledge on audio amplification, types of miniature microphones, etc., normally used in direct-line taps and other forms of wired bugs, so for this reason we can skip into the more interesting field of rf transmitting types. As can be seen in some of the circuits shown here, these mini-transmitters are far from complex. The vast majority transmit with outputs ranging from 50 to about 250 milliwatts and seldom contain more than

fig. 1. This a-m room bug can be concealed in a hi-fi, tv or radio cabinet with the speaker as the mike and the line cord as the antenna. Signal is tuned in between 500 and 700 kHz on a standard broadcast receiver.

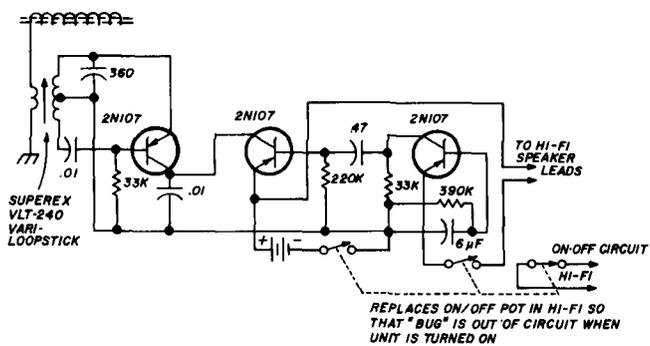

three semiconductors. Yet, determinate upon frequency of operation, the range expectancy can vary significantly.

Most room bugs and a good number of wired-in phone transmitters are powered by Mallory Duracells and the like, require little maintenance, are relatively drift-free, and offer a life expectancy of two to three weeks of constant operation. Often, tiny hearing-aid variety mercury cells will be used too, although the power input to the final transistor (and resultant DX) is proportionately less. Few circuits employ more than 12 Vdc, with most in the 6- to 9-volt area.

Frequency of operation is the key to the questionable success of the modern eavesdropper. Obviously, if he uses standard a-m or fm frequencies, he runs the risk of accidental interception by the very party he's trying to overhear. A great number of private individuals though, dabble in snooping with inexpensive mail-order devices use the 88- to 108-MHz band, centering their transmitters

at 89 MHz. For the most part, however, these are small-time operators, and, judging by the places the ads appear, curious youngsters. Although a professional may begin with such a device, i.e. invariably turns later to a rig capable of transmitting either just outside one of these bands, or on a different frequency range altogether. Consequently, anyone even slightly interested in this aspect of electronic eavesdropping must be prepared for just about anything.

A group of nine operative bands are used in 99% of the transmitting bugs, breaking down pretty much like this:


1. Just below the a-m broadcast band,
2. Just above the a-m broadcast band but below 160 meters,
3. An unused channel on the 27-MHz Citizens' Band,
4. 30 to 36 MHz fm,
5. 42 to 49 MHz fm,
6. 70 to 74 MHz fm,
7. Just below the fm music band (below 88 MHz),
8. Just above the fm music band (above 110 MHz),
9. 150 to 174 MHz fm.

By and large, the most popular range of frequencies falls in category 7, about 1.5 MHz below the bottom of the fm broadcast band. The reason for this is twofold: one, any transistor portable FM radio can be detuned to capture 86.5-MHz signals and, two, the antenna-length requirement is quite minimal (usually on the order of 3 inches and in the form of #28 wire). Additionally, fm operation

at these frequencies is generally interference-free and not troubled appreciably by ignition pulses. It has been estimated that 50% of the professional (law-enforcement, detective agencies, etc.) market for such equipment falls into this band, and more than 80% of the gear sold over the counter or by direct mail to the general public.

To a somewhat lesser extent, category 8 can also be grouped with these bugs, because the same equipment is generally tunable over a 25-35 MHz range (easily hitting above 108 MHz), although it is not as frequently employed. One of the reasons for this is that commercial-aircraft frequencies have been twice "hit" unintentionally by eavesdroppers and monitored by the FAA. Subsequently, vague warning letters arrived from the FCC, and many of the surveillance houses promptly dropped all references to above-the-fm-band operation in their promotional literature. One company, Jones Equipment, of southern California, discontinued their product entirely.

fig. 2. This circuit is the backbone of the commercial spy equipment industry. With a tunable output, this set is generally pocket-sized and will transmit well over 50 feet with a whip antenna cut to the 88- to 100-MHz fm band. L1 is 3-1/2 turns number 26 enameled on a 0.3" diameter ferrite core, 1/4" long.

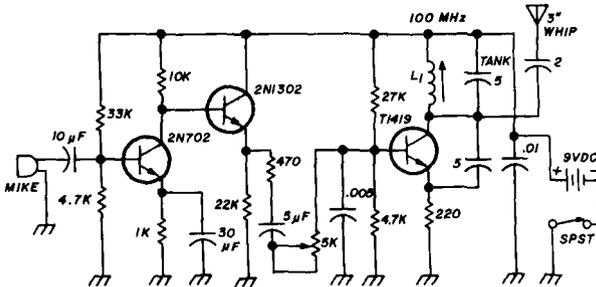

The result has been a recent trend away from anything above 89 MHz.

While a-m broadcasters have been around for years, and new transistor circuits are popping up at an average of one every three months in electronics publications, they are nowhere near as popular as you might expect. Except for permanent-type installations in furniture, such as hi-fi's, TV's, and the like and rugged designs built into the home during construction, the tendency is to pass this one up altogether in favor of hf and vhf. In spite

of this, however, it would be foolhardy to rule this possibility out during a debugging investigation, since you can never be sure. Generally, though, the transmitter is capacitively coupled to the household wiring or to the telephone lines to achieve the required antenna length, and can be rapidly located with this in mind.

Professional "kits," as they are called by federal purchasers (such as the Bureau of Narcotics, Internal Revenue, Customs Bureau, FBI, etc.), more often than not consist of larger transmitters in the 1/2- to 6-watt category which are crystal-controlled in the 30- to 50- and 150- to 174-MHz bands. These bugs often take the form of the "left-behind" attaché case, although at least one is known to have been secreted into a picture frame.

Another band popular with law-enforcement and professional security people is the 70-MHz area, although custom-built fm receivers required for monitoring are available from only three suppliers. Generally, this equipment has a greater transmit range (frequently to 15 miles) and is retrieved as insurance against ultimate detection and for re-use at a later date.

The great proportion of bumper beepers and other tailing aids also falls into this three-band frequency range, although an increasing number are cropping up on the 27-MHz CB band due to the inexpensive availability of pre-wired transmitter printed-circuit boards from such sources as Radio Shack, Round Hill Associates, Lafayette Radio, etc. These transmitters, of course, range anywhere from 100 milliwatts to 5 watts input, although the greatest majority are in the 250 mW area.

Although it has been known to happen (a 1965 case in Los Angeles), the likelihood of an eavesdropper using a ham radio band is nearly nil. The reason is the poor availability of commercial flea-power oscillators for the amateur vhf bands, at least when contrasted with the burgeoning CB marketplace. Additionally, the chances of accidental interception by a monitoring operator might trigger an unofficial investigation, particularly since eavesdropping transmitters are usually at work over extended periods of time.

Stability is another factor that varies considerably from one device to another. For the most part, L/C tanks control output frequency


with very few crystal-controlled bugs. For this reason, the eavesdropper selects a spot on the receiver with ample room both sides of the carrier to allow for drift, however slight. Over extended periods of time, battery drain will cause frequency "jumps" in addition to gradual drift which must be contended with. This can work, though, to the benefit of the countermeasure people, since accidental jarring of the unearthed bug (jogging frequency at the same time) will probably be read at the other end as a normal transmitter characteristic. Too frequent occurrences like this, however, are dead giveaways. It should be noted that diode rectifying fm oscillators

resonant frequency sufficiently to create an fm signal in step with voice frequencies. Best of all, it takes only 10 tiny components in addition to the L/C circuit to do it.

Another TD application not yet beyond the drawing boards is the "free-power" transmitting bug, which uses the tunnel to rectify rf derived from a local high-power broadcast station. In operation, the tunnel follows a tuned circuit and is in turn followed by a hefty storage capacitor. In practice, however, not enough power has been generated in this fashion to power most fm transmitter circuits used by the eavesdroppers.

The advent of transistorized VOX, however,

fig. 3. The much-publicized spike mike can look like this, or have the mike element and audio amplifier separated by a short cord. Since this bug works on a conductance basis, it can be driven into a door or a plaster wall. Transformer is a standard miniature output type, 500 ohms center tapped to 8 ohms; only one-half of the primary winding is used.

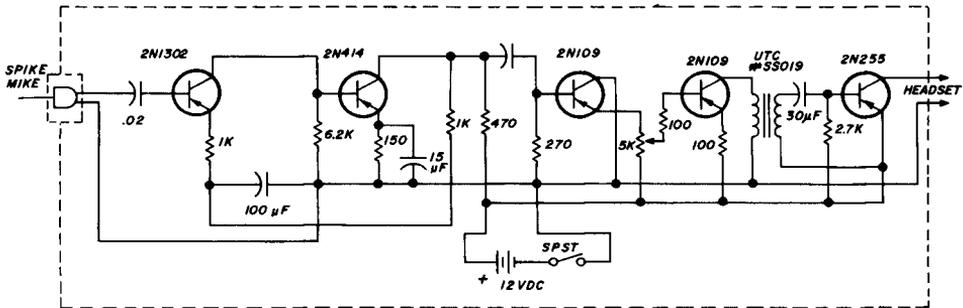

powered by phone-line currents seldom follow this trend, and, therefore, should be treated with care. Aside from minor frequency shifting, these configurations are relatively stable.

### more exotic bugging devices

While it is true that the following devices have received more publicity than those previously described, it should also be noted that their use is nowhere near as extensive in the field. One such animal is the tunnel-diode transmitter, discussed at length in a recent issue of *Electronics World*.<sup>2</sup> This configuration has been developed by R&D shops filling in during slack periods with "custom-engineered" bugs for law-enforcement customers concerned with microminiaturization and increased range. One type produces fm modulation by using the audio signal to change the anode bias of the tunnel. This affects the

has been a boon to the private detective agencies plagued with high manpower costs and low-budget clients. NYC's Manny Mittleman has designed a device which is preset to respond to only normal room sounds such as footsteps, doorknob turning, voices, etc. In the presence of such sounds, the VOX completes the mercury cell circuits and actuates the transmitter. This item is just the ticket for motel-type plants, since it can be placed in the room days ahead of schedule, "in advance of whatever action he is interested in," according to Mittleman.

Carrying this further, some agencies make use of a "double-VOX" system that extends the concept to the monitoring post. Using a broad, constantly running receiver (in case the remote transmitter shifts a bit in frequency), the VOX mechanism is placed between the receiver output (usually squelched by preset) and a Concord-variety tape recorder



Photo courtesy C. H. Stoelting Co.

This transmitter has a range up to two miles and may be completely concealed in the eavesdropper's clothing. The cuff-link mike is in the upper right.


with long recording-time capability. When the receiver "hears" the room noise, it starts the recorder. In addition to permitting a system unattended by agents, it furnishes the client with an unedited, near-continuous tape of what's been happening.

Perhaps the most widely publicized, however, has been the "harmonica bug," a unique circuit that doesn't use rf transmission at all. Designed to be planted in the telephone

table 1. This milliampere-hour chart can be extremely helpful in determining the life of an unearthed "bug". To ascertain maximum power life, divide "mA hours" by the current drain of the bug. Example: a 2-mA bug powered by a 9-volt #146 battery would have 175 hours bug life.

mercury cell life chart		
battery type	mA hours	at drain of (mA)
1	1000	35
3R	2200	42
4R	3400	63
9	2400	50
12	3600	62
42R	14000	250
133	1000	35
146	350	3
163	500	10
164	500	10
165	500	10
177	160	5
233	2200	42
312	36	2
400	75	2
401	800	25
450R	350	3
502R	2400	50
520	130	5
601R	1800	30
625R	250	5
630	350	3
640	500	10
675R	160	5

fig. 4. Here's a popular tracking device which is often used with a second operative at a different location for triangulation purposes. It's a screeching fm bumper beeper which emits a shrill audio tone near the top of the 88- to 100-MHz fm band. Antenna is a 3" whip. Transmitter is attached inside the bumper or under the gas tank with magnets. L1 is 5 turns number 14, spaced 3/4" on a 3/8" diameter form.

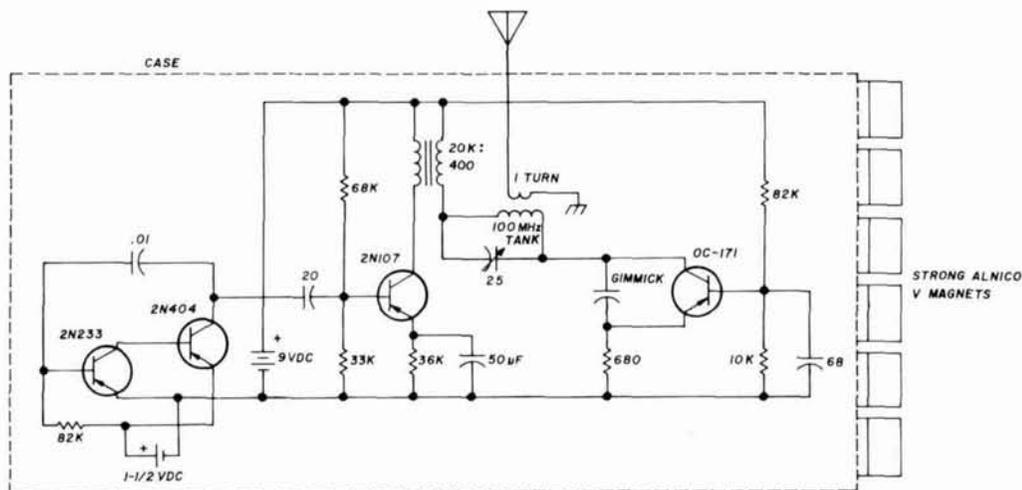

where room conversation is to be overheard, the eavesdropper merely dials the number of the bugged phone from any telephone in the Direct Dialing System, blows a 500-hertz harmonica note into the phone just before the bell at the other end rings, and presto! Instant eavesdrop.

Consisting of a subminiaturized Bramco-Controls-type resonant-reed decoder relay and a miniature single-stage audio amplifier,

Generally installed in the base of the phone itself, this eavesdrop "ultimate" sells anywhere from \$699 to \$1000, depending upon supplier.

Although microminiaturization has given us the sugar-cube mike, fountain-pen transmitter, etc., it is well to remember that these tiny transmitters are limited in terms of range capability. The famed martini-olive, disclosed in a Senate Judiciary Subcommittee on Ad-

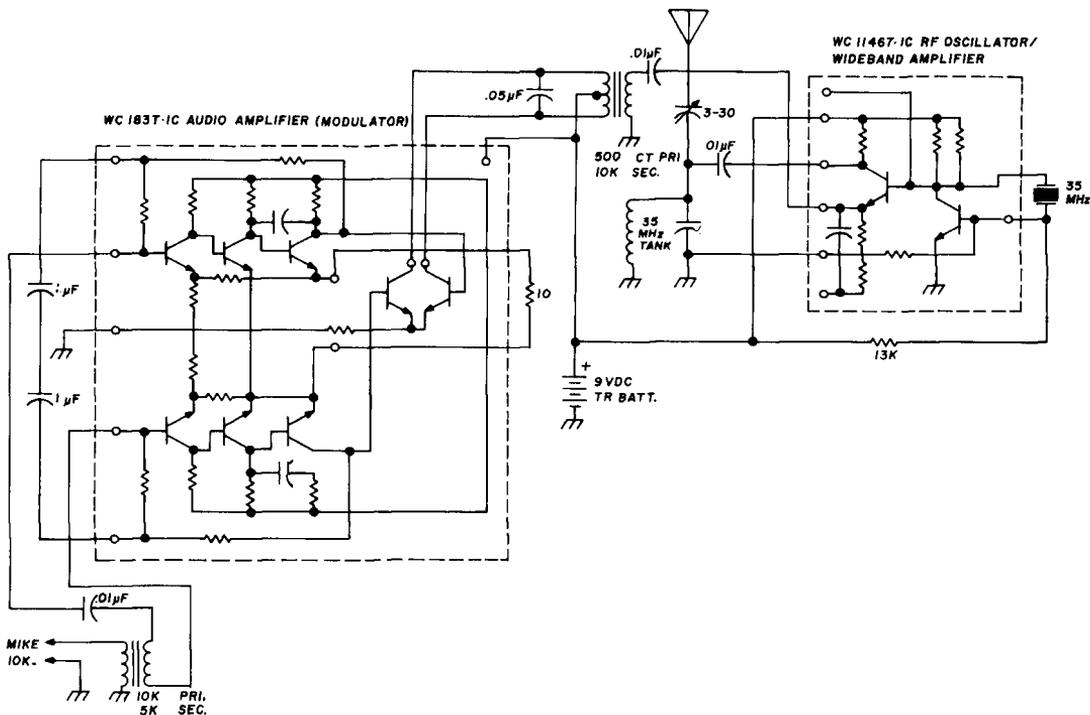


fig. 5. Professional eavesdroppers pay upwards of \$200 for this bug which uses IC's for ultra-compactness. With an output of 50 milliwatts at 35 MHz, the listener only needs a 30- to 50-MHz fm monitor receiver and a dipole.


this sophisticated bug is permanently wired across the phone lines. When the decoder picks up the 500-hertz trigger note, the relay is actuated, simultaneously deactivating the bell-ringing circuit and transferring the mike line to the audio amplifier, which in turns feeds information back to the eavesdropper.

Should someone else dial the number during this period, he merely gets a busy signal. Should the victim desire to use the telephone himself, the eavesdropper simply hangs up just before the victim picks up the phone receiver. If timing is good, no one is the wiser.

ministrative Procedures and Practice session under the chairmanship of Senator Edward V. Long, turned out to have a range of only 20 feet. In spite of the sensation it created in the press, the bug was a custom job not suitable for actual use since submersion in a dry martini would quickly put it out of commission. Other microminiature designs are similarly referred to by professionals as "toys" geared for sale to the general public on their gimmick value. The smallest, known as the "007," measures 1 x 3/4 x 1/4 inches.

From this point on, discussions of exotic

fig. 6. Known as the drop-in transmitter, this item is one of the hottest circuits around. It's built onto the back of a standard telephone carbon mouthpiece with subminiature components. The eavesdropper merely unscrews the existing carbon button and replaces it with this baby. Hot wax is poured over the circuitry to hold it in place.

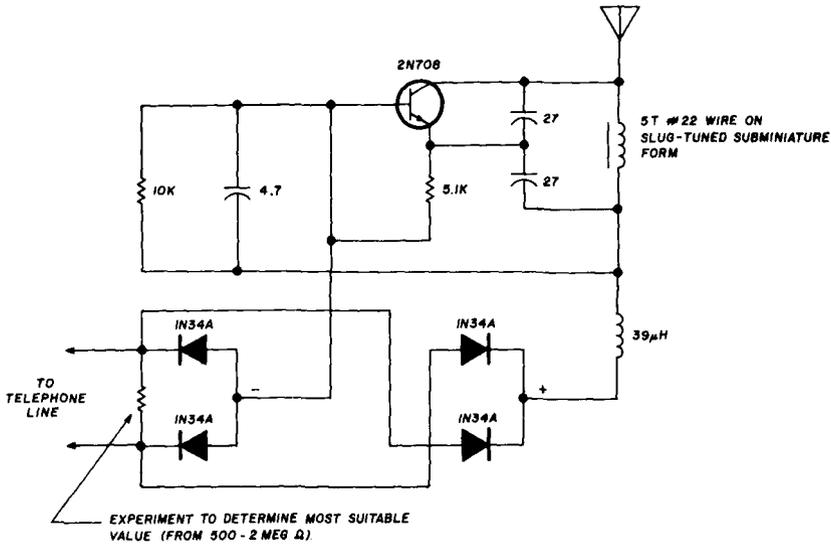


bugs take on an air of the future. Long-range parabolic microphones, while effective in certain circumstances, are unwieldy and easily spotted. The Electro-Voice tubular shotgun mikes (not à la Les Crane) are similar monstrosities not well suited to practical snooping. Additionally, audio-filtering systems are not fully developed to the extent necessary to extract passing automobile noises, etc., from the resultant pickup.

This brings us to the much-discussed laser beam eavesdropping, perhaps the furthest of

all from reality at this point. Experts in laser research feel that it will take a minimum of 20 years before any tangible results are realized, although such media as the TV spy shows and *Esquire* magazine would lead you to believe quite the opposite. While it is true that micro-reflectors consisting of optically invisible Angstrom-thick reflective paint have been developed, its use as a window reflector for laser snooping is pure conjecture right now. And as indicated earlier, audio filtering techniques are far from the ultimate,

fig. 7. Telephone tapping is popular because it's simple. This diagram shows three ways a bug can be hooked up.

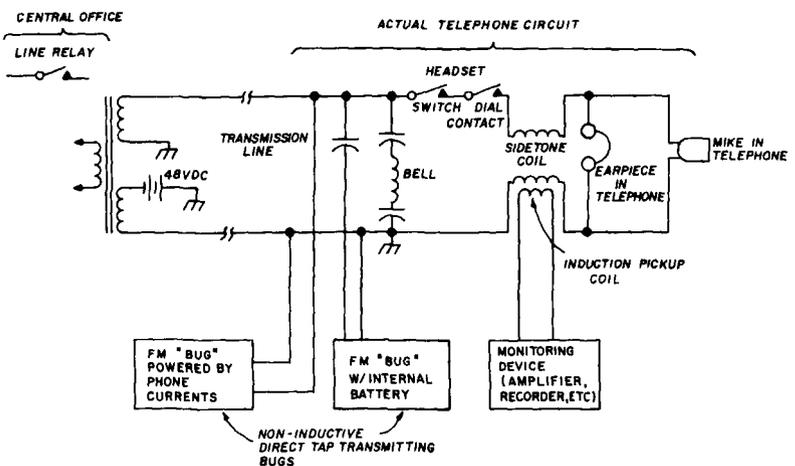


although Miles Wireless Intercom, Ltd., of NYC is said to have perfected a system (primarily for plastic "Sonaband" recording purposes) guaranteed to separate voices from typewriter clatter, cars, air conditioners and overhead airplanes.

### electronic debugging equipment

In addition to having a working knowledge of what he's up against, an amateur reader concerned with detecting and/or defeating electronic bug plants should know something about the so-called professional bug locators often selling for prices many times their component cost.

By and large, the biggest selling countermeasure item is a variation on the tried-and-true field-strength meter. Often going for prices up to \$250, bandswitching FSM's offer the debugging man a means of observing the signal on a meter. They also permit

fig. 8. Cheap and dirty jamming device induces battery-powered buzzer hash into the telephone through induction, although many users prefer direct capacitive coupling to the line.

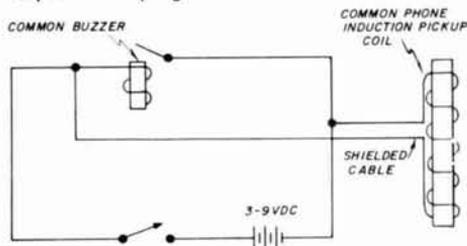


earphone monitoring to insure that the tuned-in "blip" is indeed a bug. Most FSM's are sold as "bug locators" (R.B. Clifton's \$98 model is called the "Hound Dog") and contain at least one stage of amplification. Unfortunately, however, this procedure is frequently beyond the scope of the typical non-electronics type and few manufacturers, who often simply re-label Lafayette instruments, offer clear instructions for the user.

Another instrument uses a TD as a broadband rf detector that operates as an audio oscillator when triggered into operation by the presence of a low-level rf signal. The user only has to adjust the potentiometer until the device is just on the verge of breaking into oscillation; it can also be used as a sensitivity control to insure against triggering

from strong local broadcast stations. Similar in appearance to the Radar Sentry gadgets that clip to your auto visor, these signallers also come in a beep-light configuration for mounting over doors or on desks to catch the

fig. 9. Simple vhf noise generator is an effective bug-defeater if placed close enough to an unearthened fm bug. Simply wrapping the antenna wires creates enough hash to disrupt the bug's oscillator.

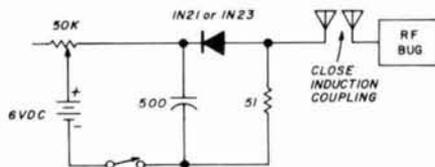

attaché-case types. A specialty of the Dee Company, about \$250 will buy one.

The CPO/keying monitor selling in ham circles for under \$15 is frequently sold to countermeasure people at prices up to 10 times that much. Essentially operating on the same triggering-concept as the TD instrument, this one uses a telescoping whip antenna for pickup and rectifies the signal with a conventional diode, filtered, and fed to an audio oscillator, amplifier, and loudspeaker.

By far the most effective device now employed in countermeasures, however, is the

**With one stage of transistor amplification and a sensitivity to 600 MHz, this field-strength meter is guaranteed to "get the goods."**


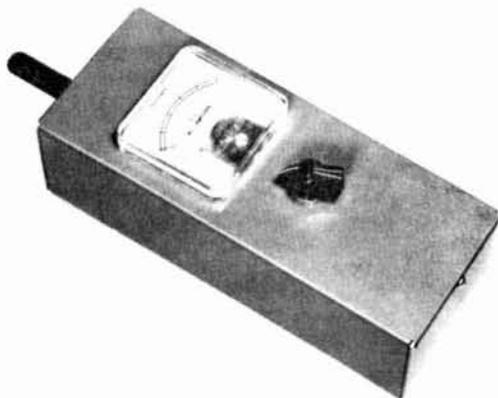


Photo courtesy R. B. Clifton

feedback detector. Although it isn't available through many commercial outlets, it appears to be a "specialty" of Security Electronics and R&S Research, both leaders in good lines of

position to close in on the instrument and pinpoint its location. Good feedback detectors run about \$150 and come with an rf gain control, earphone jack and meter switch.

fig. 10. Block diagram of an effective defeater/jammer. A 2-MHz sweep generator circuit sweeps 1 MHz each side of center. This is amplified to drive a harmonic generator, thereby sweeping through the spectrum from 1 MHz to beyond 400 MHz. Result is complete blanketing over so wide a frequency range that few bugs escape obliteration.

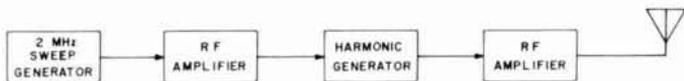


debugging kits. While new to the eavesdropping marketplace, the feedback detector is old hat to hams. Basically, it is a broadband (nearly untuned) super regenerative circuit that functions somewhat like a Heath Sixer or Twoer receiver section. The debugging man only has to tune slowly across the band—which may run 35 to 120 MHz—and listen for the bug's signal.

While such a device will also pick up TV, commercial fm broadcasts and the like, in the presence of a nearby transmitting bug it will screech in the true feedback tradition. Once the bug is revealed, the operator can simply switch from the loud-speaker to an S-meter

It is claimed that the Antibug Mark III "effectively jams all commonly-used electronic eavesdropping transmitters—including the telephone tap." It is basically a souped-up white-noise generator.

fig. 11. This portable broadband superregen is ideal for defeating hidden fm bugs since the regeneration is generally much more intense than the bug's own signal. In addition to wiping out the center carrier frequency, it will obliterate several MHz on each side.

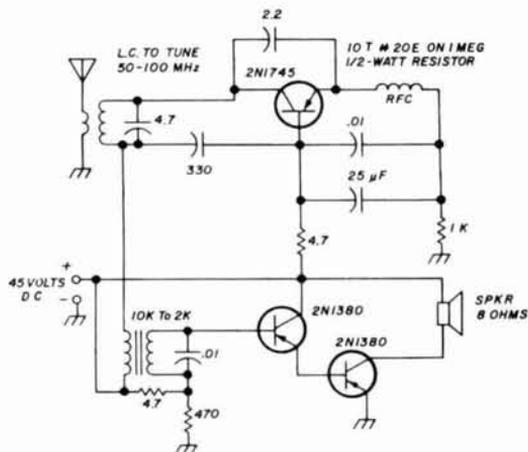

### illegal antibug jammers

While it's ethical to hire a countermeasure man to unearth the suspected bug, it is frequently much less expensive to simply buy a single jamming device guaranteed to render "all kinds of electronic surveillance devices virtually harmless." While illegal from an FCC point of view, these instruments can be turned on and off at will and do wonders for the paranoid corporate executive.

Known as "wiretap traps" and "antibugs," these gadgets are generally souped-up white noise generators that wreak havoc on bugging equipment, to say nothing of nearby radios and TV sets. Since they eliminate the need for



Photo courtesy Dectron Industries, Inc.

Once a bug has been found, the victim should consider the pros and cons before deciding to take one of the following moves:

Feed the bug wrong information purposely designed to make the eavesdropper show his hand.

Defeat its effectiveness by jamming; this often also forces the eavesdropper's hand.

Conduct a search to locate the monitoring post and/or eavesdropper.

Turn the matter over to a private detective agency (and lawyer) before tampering with the device.

Call the local police department now that evidence is at hand.

Carefully drain batteries without affecting bug's operation to accelerate the "death" of the device and move up the replacement time.

Defeat effectiveness by turning on running water (shower) or placing a radio in front of bug.

Notify FCC local office to reveal monitoring post without bringing in local police. FCC may take initiative in contacting authorities, but is discreet.

Remove device entirely.


visual and electronic detection techniques, however, they command good prices, usually from \$225 to \$350.

Other types include ac-powered versions of the super-regenerative feed-back detector. A single tube variety I experimented with used a single tube with about 100 Vdc on the plate. This little gadget put forth sufficient regeneration on the 88- to 108-MHz fm band to completely knock out a commercial 20,000-watt broadcast station at a distance of only

1/2 mile from the jammer. And this was accomplished using only a 3-inch link of hook-up wire as an antenna. Similar designs employed as bug-killers could totally wipe out a low-powered fm listening device at the listening end.

Crude spark-gap transmitters, the ultimate in hash generation, are occasionally em-

fig. 12. The basic field-strength meter is the backbone of the bug-detection industry, although it is frequently souped up for added sensitivity.

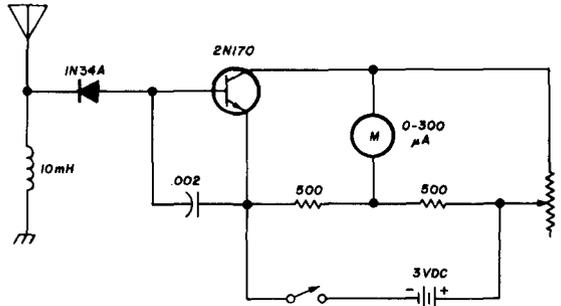


ployed today, but they are not mass-marketed for obvious reasons. In use, the spark-gap is placed fairly close to a source of high-level corporate conferences and powered by dry-cell batteries. By remote-control switching from any convenient point in the building, the spark-gap is actuated during periods of sensitive speech.

### what the law says about transmitting bugs

On September 19, 1966, Congressmen Moss and Gallagher introduced legislation aimed at the ultimate destruction of the surveillance

fig. 13. Circuit used most often in \$100 bug detectors. An amateur with a well-stocked junk box can put one together for less than five dollars.

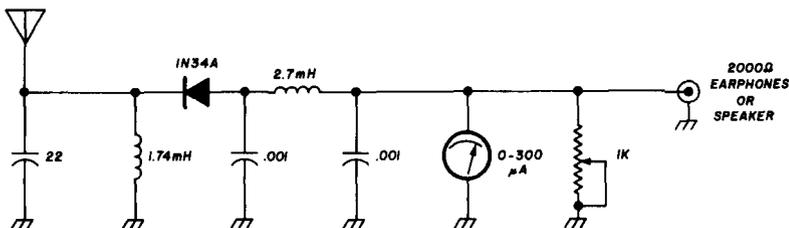


equipment industry (H.R. 17826 and 17827):

"A bill to prohibit the shipment in commerce of electronic eavesdropping and wiretapping devices."

The legislation, if enacted, would give exception to "any department, agency, or in-

**fig. 14. This simple two-stage field-strength meter is about as sophisticated as you'd care to go, since further amplification is unnecessary. In fact, with the circuit you may pick up local radio and tv broadcasts unless the gain is reduced**

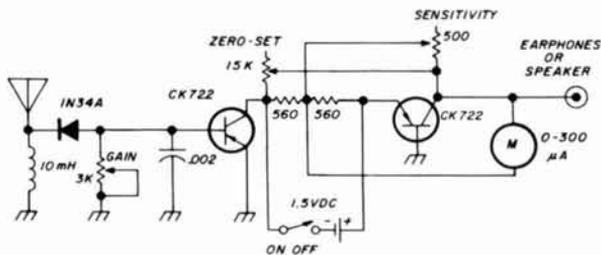

strumentality . . . authorized to use such devices by Federal statute." This would take effect 180 days after passage of the bill. These bills were referred to the Committee on Interstate and Foreign Commerce, where they remained as the 89th Congress closed.

Earlier, the FCC adopted certain amendments to its Rules on April 8, 1966, designed to prohibit eavesdropping. Though entered as a specific regulation (Part 2, Subpart H, Section 2.701), the FCC spelled out the same ruling in Part 15:

"No person shall use, either directly or indirectly, a device required to be licensed . . . for the purpose of overhearing or recording the private conversations of others unless such use is authorized by all persons or parties engaged in the conversations."

Further, this exception was noted:

"... This section shall not apply to operations of any law-enforcement officers conducted under lawful authority."

In Commission Chairman Rosel H. Hyde's 1966 year-end wrap-up statement, it was noted that since this rule change was adopted, the FCC investigated eight cases of al-

leged electronic invasions of privacy. A query I made to Commission Secretary Ben F. Waple, however, succeeded only in learning that such matters are "internal" FCC affairs and regarded "as confidential and not for release." Obviously, however, the FCC cannot apprehend all violators since the vast majority of bugging equipment is used only for short periods of time and is of an extremely low-power nature.

## what the law says about telephone devices

Although no legislation is currently pending, it is hoped by proponents of anti-bugging that Senate investigations may permit some proposal to be worked up in 1968. The only agency that can now become involved is the FCC, which holds as a rule violation of Section 605 the "unauthorized interception" of phone conversations by direct wiretaps, or induction-coupling. Yet, for the Commission to take action, it must have evidence on hand that the

**This bandswitching field-strength meter tunes from 25 to 250 MHz but reaches up to 450 MHz un-tuned. It will function over 400 hours with the internal mercury cell.**



Photo courtesy W. J. S. Electronics

gleaned information has been clearly divulged or in some way "beneficial."

As phone-patch enthusiasts are well aware, many telephone companies have policies prohibiting attachment of any foreign device to its property. An illustration can be provided by this Wisconsin Telephone Company policy:

"No equipment, apparatus, circuits, or device not furnished by the telephone company shall be connected with the facilities furnished by the telephone company, whether physically, by induction, or otherwise, except as provided in this tariff."

The tariff permits connection only of radio equipment of the Armed Forces, mobile telephone systems, and the major U.S. railroads.

### on your own

Since hams are generally more interested in circuit technology of new breeds of devices, I have attempted to emphasize this aspect of eavesdropping rather than illustrative

**Master bugger Fred Gluckman of Security Electronics demonstrates how an fm phone bug can be detuned to confuse the counter-measures investigator.**



The following list covers all known major and minor manufacturers and distributors of eavesdropping equipment. Complete details on equipment types, prices, and street addresses can be found in "The Electronic Invasion" published by John F. Rider Publisher, Inc., New York.

**Baker Electronics Co.**, Greencastle, Indiana  
**Britton Enterprises, Don**, California and Hawaii

**George F. Cake Co.**, Berkeley, California  
**R. B. Clifton Co.**, Miami, Florida

**Consolidated Acoustics**, Hoboken, New Jersey  
**Continental Telephone Co., Inc.**, New York, New York

**Criminal Research Products, Inc.**, Conshohocken, Pennsylvania

**Dectron Industries, Inc.**, Van Nuys, California  
**Dee Co.**, Houston, Texas

**Dehart Electronics**, Sarasota, Florida  
**Ekkotronics Co.**, Milwaukee, Wisconsin

**Fargo Co.**, San Francisco, California  
**Fudalia & Associates Electronic Surveillance Devices**, Toronto

**Kel Corporation**, Belmont, Massachusetts  
**Martel Electronics Sales, Inc.**, New York, New York

**Micro Communications Corp.**, Los Angeles, California

**Miles Wireless Intercom, Ltd.**, New York, New York

**Mittleman, Manny**, New York, New York  
**Mosler Research Products, Inc.**, Danbury, Connecticut

**R & S Research, Inc.**, Houston, Texas  
**S.A.C. Electronics**, Los Angeles, California  
**Saber Laboratories**, San Francisco, California

**Security Electronics**, New York, New York  
**Sierra-Tronics**, Nevada

**Silmar Electronics, Inc.**, Miami, Florida  
**Spindel, Bernard B.**, Holmes, New York  
**Steckler Sales Co.**, New York, New York

**Telephone Dynamics Corp.**, North Bellmore, New York

**Telmar**, New York, New York  
**Tri-Tron, Inc.**, Dallas, Texas

**Tron-X Publications**, Hollywood, California  
**Wireless Guitar Co.**, New York, New York  
**W.J.S. Electronics**, Hollywood, California

As the author has not had the opportunity to visit the places of business or purchase equipment from all the companies represented he cannot vouch for authenticity of product claims or equipment reliability.

This feedback detector sweeps over the frequency range from 6 kHz to 10,000 MHz with a broadband fm receiver configuration.

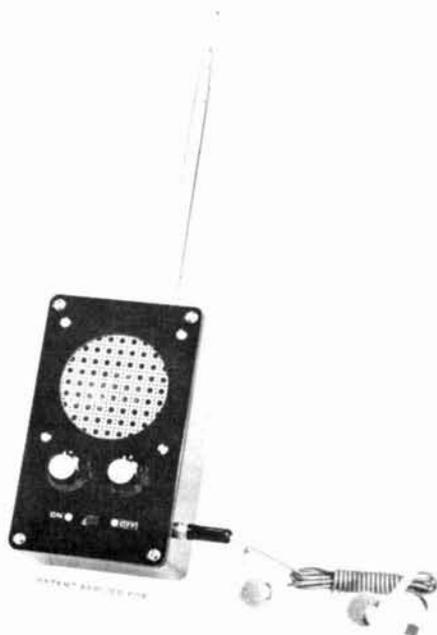


Photo courtesy R&S Research, Inc.

case histories showing where bugs have been unearthed, who has been indicted, and what corporations are involved. For much the same reason, this report has taken on an objective, factual approach and not one interjected with moral overtones.


Electronic invasions of privacy will continue to be part of the American way of life in the years to come, despite federal, state, and local efforts to suppress its growth. It is too well-entrenched now in U.S. business to do much more than go underground.

ham radio

#### references

1. "Electronic Bugging and the Ham," *CQ*, December 1966, page 34.
2. "Electronic Eavesdropping," *Electronics World*, April 1967, page 23.
3. "The Electronic Invasion," John F. Rider Publishers, Inc., 1967.
4. "The Intruders," published by Frederick A. Praeger, 1967.
5. "The Eavesdroppers: Fallout from R&D," *Electronic Design*, June 21, 1966.
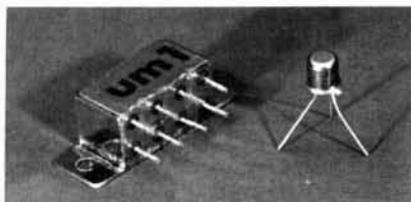
## SOLID STATE—BROADBAND DOUBLE BALANCED MIXER



U.S.L. MODEL UM 1

Frequency Range ..... 200 kHz to 200 MHz  
 When Used in a 50 ohm System  
 Conversion Loss ..... 6 db Nominal; 7 db Maximum  
 Local Oscillator ..... 45 db 200 kHz to 30 MHz  
 Rejection ..... 35 db to 200 MHz  
 Replaces expensive and obsolete vacuum tube circuitry in a miniature R.F.I. package occupying less than 0.5 cubic inch.

P.C. card or chassis mount (indicate preference)

Applications Include:

- Balanced Modulator—ideally suited for use in filter or phasing type S.S.B. generators.
- Receiver Mixer
- Product Detector
- Phase Detector
- Voltage Variable R.F. Signal Attenuator

State-of-the-Art performance and convenience offered by this broadband mixer are yours for only . . . \$15.00 (California residents add 5% Sales Tax)

SEND CHECK OR MONEY ORDER TO:

### ULTRAMATIC SYSTEMS LABORATORY

Post Office Box 2143  
 Sunnyvale, California, 94087

**SOLID STATE REGULATED FILTERED** power supplies, made for 19" panel mount although not all have panels affixed. 115 volt 60 cycle input. A SURPLUS SPECIAL.

#68-3 OUTPUT 10VDC 10 Amp	\$20.00
#68-4 OUTPUT 135 VDC 2.3 amp 15 VDC 7 amp	25.00



#### TRANSISTOR HEAT SINK

w/2N174A ..... \$2.50

#### IBM WIRED MEMORY FRAMES.

Removed from high priced computers. ExInt condition.

160 core	\$ 4.00
1,000 core	10.00
4,096 core	12.50
8,192 core	15.00
16,384 core	35.00

1968 CATALOG NOW READY ..... 25c

## MESHNA

21 ALLERTON ST., LYNN, MASS.  
 All Material F.O.B. Lynn, Mass.



# sporadic-E propagation predictions

Some of the best  
vhf propagation conditions  
of the year  
occur in early summer.  
Here are some forecasts  
of sporadic-E openings  
in June

Vic Frank, WB6KAP, 12450 Skyline Boulevard, Woodside, California 94062

Although high-frequency propagation over paths greater than 2500 miles will be the primary emphasis in the months ahead, I am kicking off the propagation column with sporadic-E predictions for June, 1968. The curve in **fig. 1** shows the percentage occurrence of sporadic-E measured at Point Arguello, California, during the first half of June, 1967, and is indicative of the sporadic-E propagation you can expect this year.

These curves show critical-frequency sporadic-E propagation versus time of day. The critical frequency is the highest frequency at which sporadic-E reflections were obtained with a **vertical** sounder.

Four critical-frequency contours are shown: 7, 9, 11 and 13 MHz. The critical frequency contour of 7 MHz corresponds to a range of 625 miles on 28 MHz; the 9-MHz critical frequency indicates a range of 470 miles on 28 MHz or 1400 miles on 50 MHz. The critical frequency contour of 11 MHz corresponds to a range of 800 miles on six meters; and a 13-MHz critical frequency corresponds to 625 miles on 50 MHz. For a sporadic-E opening

on two meters, the critical frequency must go up to 24 MHz. The corresponding range on six meters would be 250 miles.

In summary, six meters will probably be open to distances between 1000 and 1400 miles more than half the days of the month, but you shouldn't miss many openings by sleeping between 0200 and 0600.

Two meters should open up to distances of 1250 to 1350 miles at least once during the month. The reflection point will probably be south of 38° north latitude between 0900 and 1500 local time at the path midpoint. Unfortunately, two-meter openings may not be noticed because of lack of activity at the proper places. More beacon transmissions and noon-time schedules over distances between 1200 and 1500 miles would help.

### summary of high-frequency propagation

**80 and 40 meters.** On these two bands, summer-time noise levels and absorption will

limit propagation to darkness paths. Since the north pole is in continuous daylight, no propagation is expected over the pole. This is not without merit—foreign broadcast stations will cause less interference than they do during fall and winter.


**20 meters.** Twenty will be primarily a night-time band. The maximum usable frequency should be above 14 MHz for all but polar paths during the pre-dawn hours.

**15 meters.** Fifteen should be open during day-light and evening hours to directions south of east and west. Short skip may be prevalent because of sporadic-E.

**10 meters.** Ten should be open up from the southern half of the United States toward the south. Short skip sporadic-E propagation will be prevalent. Double-hop sporadic-E will permit occasional communications up to 2500 miles.


ham radio

fig. 1. Percentage occurrence of sporadic-E measured with a vertical sounder at Point Arguello, California during the first half of June, 1967.

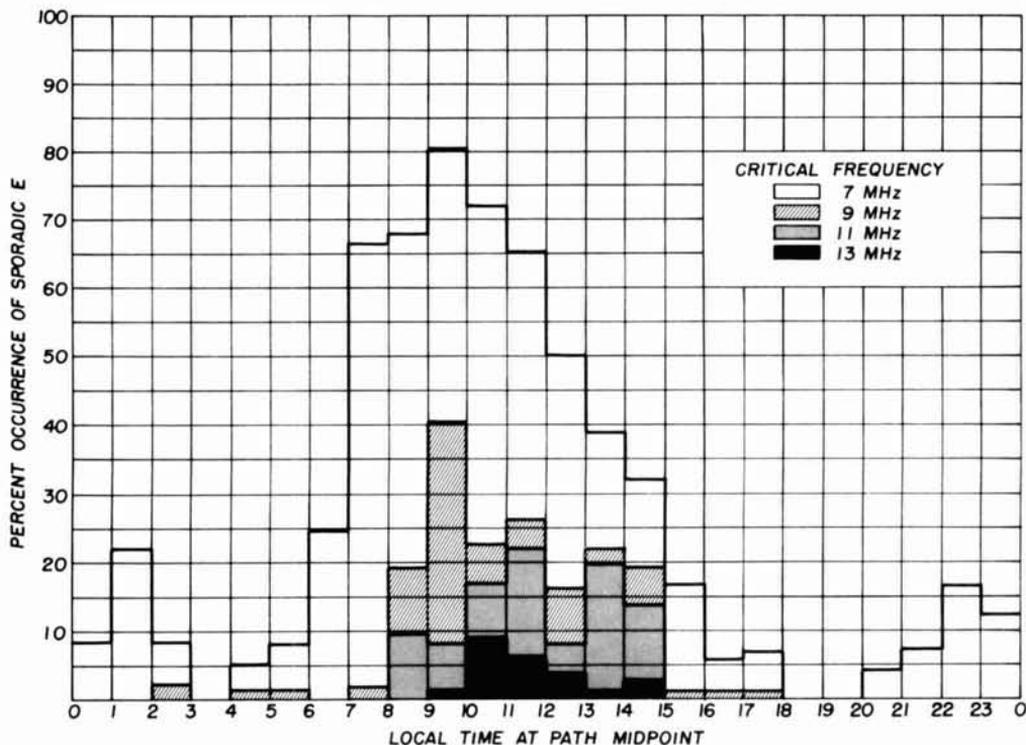

# new products

## Main cw audio filter

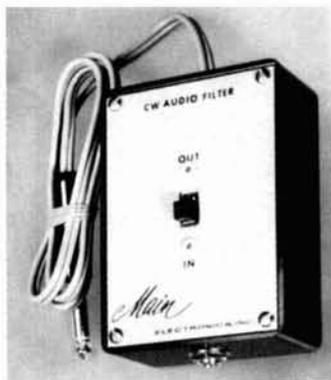

If you are irritated by the QRM level on the CW bands these days, this new device will be of interest to you—the new Main Electronics high-selectivity CW audio filter. This unit offers very high selectivity for CW reception on all transceivers and receivers. To use the CWF-1, you merely plug into the 2- to 4-ohm audio output of your receiver and plug your headphones into the CWF-1. A switch is provided for taking the filter in or out of the circuit as interference dictates.

The passband of the filter is 120 Hz wide at the 6-dB points and 200 Hz wide at the 10 dB points. This is achieved by the use of high-Q toroidal inductors in a four-pole filter circuit. The output is designed to match 2000-ohm headphones. The filter not only separates the wanted signals out of the QRM, it also improves the signal-to-noise ratio when receiving weak CW signals which are close to the noise level such as in vhf DX work.


The CWF-1 Audio Filter is 2-7/8-inches wide, 1-5/8-inches high and 4-inches deep. A descriptive brochure is available upon request; \$19.95 from Main Electronics, Inc., 353 Pattie, Wichita, Kansas 67211.

## Raytrack 50-MHz Converter

Raytrack Company has introduced a new six-meter converter using FET's in both the rf and mixer stages. These transistors give high immunity to cross modulation and a 3-dB typical noise figure. A 15-dB nominal gain is claimed. Features of the *Horizon VI* include a trap for TV Channel 2 and a built-in power supply. Crystal switching from the front panel permits a choice of expanded coverage to operating band segments. An output jack is also provided in the crystal oscillator circuit to permit transceive operation with your transmitter.

This converter has both a 150-ohm input and output impedance. It is designed to operate over the frequency range from 50 to 54 MHz with an output from 14 to 18 MHz. It is built on a fiberglass chassis and weighs only 18 ounces. The *Horizon VI* is priced at \$59.95 by the Raytrack Company, 211 Springhill Drive, Columbus, Ohio 43221.

## electronic components encyclopedia

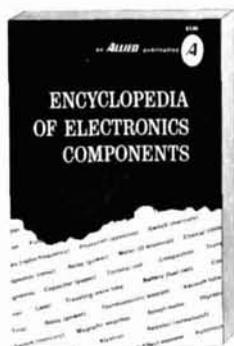

A new encyclopedia of electronic components recently put out by Allied Radio alphabetically lists, describes and illustrates the basic electronic components currently in use. This book is virtually an electronics text that provides an understanding of individual units used in electronic devices and systems in one reading. Descriptions are completely non-technical. Each component is identified, and its use is carefully explained. In addition, any special handling or installation requirements are covered.

This is a handy reference book for anyone in electronics and is an interesting and useful aid to amateur radio operators, experimenters and students. One dollar postpaid in the USA. For more information, write to Allied Radio Corporation, 100 North Western Avenue, Chicago, Illinois 60680.

## new Lafayette catalog

Lafayette has just announced its new 1968 Summer Catalog #684. This catalog is available free upon request and has the latest electronics and home entertainment equipment. It includes Lafayette's equipment plus many other major manufacturers, plus values in power tools for the home workshop, marine accessories and a complete line of amateur radio equipment, test equipment and citizens band two-way radio. It may be obtained free by writing to Lafayette Radio Electronics Corporation, P. O. Box 10, Department HR, Syosset, Long Island, New York 11791.

# Genuine **TEXAS** "BUG-KETCHER"<sup>®</sup> KILOWATT 80 THRU 10 MOBILE ANTENNA

You've heard them on the air . . . Now . . . Available for the first time!!!

The Texas "Bug Ketcher" has been one of the best radiating antennas on the air for years . . . and yes, low power rigs can increase effective radiated power with this high "Q" coil.

"Bug Ketchers" are custom made of top quality materials, engineered to withstand abuse where other antennas fail . . . **Send For Yours Now** . . . Be ready for a full season of mobile fun!

BUG-KETCHER  
COIL ONLY ..... **\$21<sup>95</sup>**

### POSTPAID SPECIFICATIONS

- COIL SIZE: 2 1/2"
- WIRE SIZE: #14
- COIL LENGTH: 12"
- COIL REPLACEMENT: AIR DUX = 2008
- LENGTH OF BASE EXTENSION: 36" preferred
- LENGTH OF WHIP: 96" preferred
- COIL FORM CONSTRUCTION: Phenolic with machined brass fittings. All fittings are standard 3/8" throughout

"The Southwest's Leading Ham Store . . . All Popular Lines In Stock . . ."



**electronics center, inc.**

2929 N. HASKELL 214-LA6-2023 DALLAS, TEXAS 75204



**\$12.95**  
AMAT. NET

**AMERICA'S MOST ADVANCED QUALITY-CONTROLLED BALUN**  
**W2AU BROAD BAND BALUN 2.8 TO 40 MC**  
**WITH BUILT-IN LIGHTNING ARRESTER**  
**HANDLES FULL LEGAL POWER LIMIT**

**\$12.95**  
AMAT. NET

4 PURPOSE BALUN

4 PURPOSE BALUN

THE BALUN THAT HAS BEEN PROVEN AND ACCEPTED. NOW BEING USED BY THE U.S. NAVY, COAST GUARD, AIR FORCE, ARMY, FCC, CIA, RCA, NBC, FAA AND CANADIAN DEFENSE DEPT. AND BY THOUSANDS OF HAMS IN THE USA AND THROUGHOUT THE WORLD.

**—ANOTHER FIRST—**

Our exclusive sealed type lightning arrester helps prevent lightning damage to your valuable equipment, balun and coax. Don't wait until lightning strikes. Protect your investment now. **DON'T BE MISLED!** Our one style balun is adaptable to all antennas, Yagis, quads, inverted Vees and multi-bands.




Backed by 50 years of electronic knowhow

Proven over the years.

Available at all leading dealers. If not, order direct.  
IT'S WHAT'S INSIDE THAT COUNTS

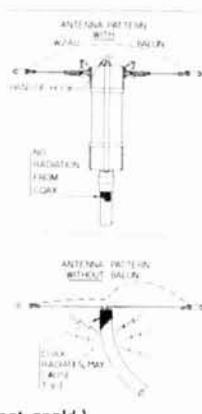**W2AU BALUN LETS ENTIRE ANTENNA RADIATE!**



STOP WASTING YOUR SIGNAL! REMEMBER, YOUR ANTENNA IS THE MOST IMPORTANT PIECE OF GEAR YOU OWN.

- No Radiation from Coax
- No Center Insulator Needed
- Perfect for Inverted Vees (Use Hang-up Hook)
- Built-in Lightning arrester
- Broad-Band 2.8 to 40 Mc.
- Takes Legal Power Limit
- Two Models:
  - 1:1 50 ohm coax to 50 ohm balanced
  - 4:1 75 ohm coax to 300 ohm balanced
- A must for Inverted Vees, Doublets, Quads, Yagis etc.
- Weighs 6 1/2 oz. 5 1/2" long

(pat. appl.)

\$ for \$

Your best balun buy.

**HELPS TVI PROBLEMS IMPROVES F/B RATIO**  
BY REDUCING LINE PICKUP

UNADILLA RADIATION PRODUCTS, Mfrs. of Baluns & Quads, Unadilla, New York 13849

one year  
**FREE**  
three-year subscription to

**ham radio**


only \$10.00

regular one year rate \$5.00

ham radio magazine, greenville, new hampshire 03048

# IMPORTANT ANNOUNCEMENT
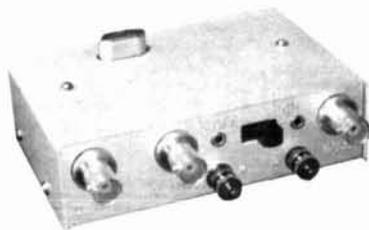
## ALL VANGUARD CONVERTERS NOW USE R C A DUAL GATE MOSFETS FOR BOTH THE RF AND MIXER STAGES



**prices start at \$19.95**

The performance and features of our new converters are so spectacular that they can only be fully described in our new illustrated catalog which is available **FREE**. Send for it today and see our entire line of converters, pre-amps and other communications equipment.

**VANGUARD** now makes the best converters. Buy one and be convinced.

# VANGUARD LABS

196-23 Jamaica Ave. Dept. R  
Hollis, N.Y. 11423

### GET ACQUAINTED OFFER


We would like to get your name on our mailing list for our 64-page pictured catalog of Government Surplus bargains. To attract the attention of the readers of "Ham Radio", we are presenting some very special values. Your order will automatically place your name on our mailing list, or send 25 cents.

#### ADJUST-A-VOLT TRANSFORMER



Adjust-A-Volt Transformer sometimes called a Vari-arc a very rugged unit made to Government specifications. Used to adjust output voltage between 0-130 volts with a rated load of 22.5 Amps. New in original cartons with dial and knob. Ideal for slowing motors, dimming lights, and any other variable voltage application — If you have a linear you shall find it useful. Wt. 35 lb.

AA-V x \$22.50

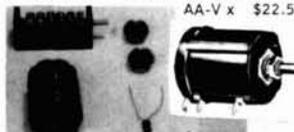

Would you believe a Digital Voltmeter for \$15.00? Would you believe \$25.00?

We supply a large 6 digit numeral precision counter, a In429 precision reference zener diode, a 10 turn 0.25% linearity potentiometer, and a D.C. motor. For \$15.00. You must beg, buy, borrow or steal a \$10.00 operational amplifier (Analog Devices Nexus or equivalent) and your ready to roll. Schematic included list price of components we supply is over \$175.00.

Digital Voltmeter Kit DVM \$15.00

**TRANSFORMERS:** These are all rugged military units rated for continuous duty. On intermittent or commercial service the current ratings may easily be increased 40% (we have operated the 18 amp filament transformer continuously at 30 amps with no discernible temperature rise. Allow for postage.

No.	Primary	Secondary	Price
T1	115, 120, 126, 123 volts	6.6 volts @ 1.2 amps center tapped	\$1.75
T2	60 Hz Single Phase	6.6 volts @ 1.2A, c.t.s.	\$2.50
T3	"	6.6 V @ 5 amp, 6.6 V @ 1 amp, c.t.	\$3.00
T4	"	6.6 V @ 10 amps, c.t.	\$3.00
T5	"	6.6 V @ 10 amps, c.t., 6.6 V @ 1.0 amps c.t.	\$3.50
T6	"	6.6 V @ 18 amps, c.t.	\$4.75
T7	115 V, 60 Hz	44, 22 or 11 V c.t. @ 2.0 amps	\$4.00
T8	Audio, 20-20 Hz, 7000 $\mu$ c.t.	265 $\mu$ c.t. or 80 $\mu$ c.t.	\$3.75
T9	Audio 500-10 Hz, 15,000 $\mu$ A ma.	95,000 $\mu$ split 11 dbm	50c
L1	Choke .05 to 0.25 Henry	@ 0.8 amperes d.c.	\$1.50
L2	Choke 0.5 to 0.25 Henry	@ 0.2 to 0.6 amps d.c.	\$2.50
T10	208 V, 3 phase, 60 Hz	275, 290 V @ 0.25 amps	\$2.50
T11	"	460, 490 V @ 0.25 amps	\$5.00
T12	"	202, 212 V @ 0.25 amps	\$2.50
T13	"	103, 109 V @ 0.408 amps	\$3.00
T14	"	180, 195 V @ 0.49 amps	\$3.50
T15	"	280, 325 V @ 0.75 amps	\$4.50
T16	"	24, 27 V @ 11.4 amps	\$4.75

#### TELETYPE SPECIAL — GOV'T SURPLUS

101 New packaged spare parts for models 14, 15 and 19 teletypes. Over 40 different items include cams, balls, reels, covers, springs, type, key caps, etc. Government cost over \$900.00. The first part used will cover the cost of the kit, and you will have the added advantage of being back in operation immediately. This is one of our most popular items. Price: \$5.90 plus postage (include \$1.00 east of Miss., \$2.00 west).

#### TRANSISTOR TONE OSCILLATOR



Do not confuse this well-made military unit with low price commercial "ice cube packs." This unit operates from 1.5 to 6.0 volts, and has transformer isolated output. Frequency is 1000 Hz, may be varied with external pot. New package, and complete with spare set of transistors.

Applications: Continuity, component, and semiconductor tester, code practice oscillator, keying monitors, alarms, RTTY SHIFT Oscillators, etc.

TTC \$2.00 P.P.

**B & F ENTERPRISES**  
GOV'T SURPLUS · ELECTRONIC · OPTICAL · HOROLOGICAL · MECHANICAL

P. O. BOX 44, HATHORNE, MASS. 01937

"CHOICE OF THE DX KINGS"



2 ELEMENT-3 BAND KIT SPECIAL

CONTENTS

- 8 Fiberglass Arms-skyblue color
- 2 End Spiders (1 pc. castings)
- 1 Boom/Mast Coupler-h.d. aluminum
- 16 Wraplock Spreader Arm Clamps
- 1 CUBEX QUAD Instruction Manual

ONLY  
**\$59.95**

Add \$3.50 for PPD  
Frt. Cont. U.S.

2-3-4 or more element Quads available  
Write for FREE BROCHURE 'H' & Price List

**CUBEX COMPANY**

P.O. Box 131, Altadena, California 91001  
Phone: (213) 798-8106

YOU CAN'T SAY "QUAD" BETTER THAN "CUBEX"

FOR THAT  
*"Extra Class"*  
YOU NEED THE

**BTI LK-2000  
LINEAR  
AMPLIFIER**  
For SSB, CW, RTTY  
Maximum legal input  
Full loading 80-10M  
Rugged Eimac 3-1000Z  
Dependable operation  
Easy to load and tune  
No flat topping with ALC  
Distinguished console  
Instant transmit  
High efficiency circuit  
Designed for safety  
Fast band switching  
Real signal impact  
**Price . . . \$795.00**  
READY TO OPERATE!

Listen for the hundreds of LK-2000 linears now on the air and judge for yourself. Write for free illustrated brochure or send \$1.00 for technical and instruction manual.

BTI AMATEUR DIVISION  
**Hafstrom Technical Products**  
4616 Santa Fe, San Diego, Ca. 92109

HAMS!! DON'T BUY TUBES UNTIL YOU GET  
OUR LOW PRICES ON BRAND NEW TUBES  
NOT PULLS OR REBRANDS

6J6 .45	OB2 .60	807 1.95	6360 2.50	4-400A 37.50
6TR .75	2X2 .50	6146 2.50	8632 12.95	4PR60B 55.00
6U8 .69	10Y .50	6360 3.00	2C39 10.00	4-250A 35.50
OA3 .80	7025 .55	12AU7 .52	4-65A 9.00	4X150A 10.50
OC3 .60	6AQ5 .50	832A 6.00	4-125A 25.00	4CX250B 19.00
OD3 .60	6BQ7 .88	2E26 2.50	UX200 1.50	4-1000A 80.00
OA2 .70	6CG7 .54	811A 3.75	1AX2 .39	6 FOR 2.00

3CX100A5 9.95 .5725/6AS6 50..5842/417A 2.25 .5874/404A 2.25..

Silicon Repl. For OZ4, 5U4, 5Y3, 5AS4, 5Z4 98..  
50 Diodes-IN34A, etc. \$1.00.. 8 Top Hat 450 Piv. 500 MA-1.00..

10 Sil. Epox. Diodes-400-750-Piv-1 Amp-\$1.00.  
4 Power (20W) Transistors-\$1.00.. WE 701A-1000W Tetrode-\$5.95

Sale on brand new CH & H & H Toggle Switches never used-Removed from new equipment

SPST 6 Amp-\$1.50 DZ. SPDT 6 Amp-\$1.69 DZ.  
DPST 6 Amp-1.69 DZ. DPDT 6 Amp-1.85

DPDT 15 Amp-2.95 DZ. SPST Slide SW. 8 for \$1.00  
AC DC Elect. Cond. 50X30 MFD at 150 V. 25.. 3X15 MFD at 450V. 49..

1625 Beam Power Amplifier 95. 841 Power Triode for 6-30MC 50. 6.3V Fil. Transf. PRT 115VAC 60 Cy. Sec. 6.3V at 1.5A Open Type .39.. 25 Ft. 2-3 Wire #14 Rubber Shielded Cable \$1.25. 12 Spkr. Plug \$1. 6 Audio Outp. Trans. \$1.. 75

Asst. 1W Resistors \$1.. 40 Asst. 2 W Resistors \$1.. 60 Precision Resistors \$1. 6 1/2 Meg. Vol. Controls \$1.. 25 Asst. Pilot Lights \$1.. 60 Asst. TV Pkg. Coils \$1.. 12 Asst. Dual Controls \$1.. 12 Spkr. Cords W/Plug \$1.. 12 Asst. RF Coils-SW \$1.. 100 Asst. AB-IRC1/2-1-2W Res. \$1.. 50 Asst. Crystal Diodes IN34, etc. \$1.. 50 Asst. Mica Cond. \$1.. 12 Vol. Controls \$1.. 25 Asst. Trimmer Cond. \$1.. 50 Asst. Paper Tubular Cond. \$1.. 12 Asst. Elec. Cond. Kit \$1.. 20 Asst. Wire Wound 5-25 W \$1

Canadians Must Remit in U.S. Funds. No C.O.D. Orders.

The above is only a sample of over 5,000 bargains we have. Min. order 5.00 not including postage (extra). Send Stamp for bargain tube and parts catalog.

**UNITED RADIO CO.**

56 Ferry St. Newark, N.J. 07105

Estab. 1920

**DIODES**

EVERY DIODE WE SELL IS CURVE TRACED ON A SPECIAL TESTER THIS TESTER DRIVES 2 AMPS AVERAGE CURRENT THROUGH THE UNIT IN THE FORWARD DIRECTION WHILE THE REVERSE LEAKAGE IS MEASURED (25 MICROAMPS). THE OPERATOR EXAMINES THE CURRENT VOLTAGE PLOT OF EACH DIODE ON AN OSCILLOSCOPE SCREEN WE FULLY GUARANTEE EVERY UNIT SOLD OR YOUR MONEY REFUNDED.

PIV	TOP-HAT 1.5 AMP	EPOXY 1.5 AMP	EPOXY 3 AMP	STUD-MOUNT 6 AMP
50	.04	.06	.12	.20
100	.06	.08	.16	.25
200	.08	.10	.20	.35
400	.12	.14	.28	.50
600	.14	.16	.32	.58
800	.17	.20	.40	.65
1000	.20	.24	.48	.75

**ZENERS**

ALL UNITS TESTED AND GUARANTEED  
ALL 1 WATT

5% 3 for \$1.00 10% 4 for \$1.00

11	12	13	15	16	18	20	22	24	27	30	33	36	39	43	47	51	56	62
68	75	82	91	100	110	120	130	150	160	180	200							

VOLTS

**3 YEARS OF SERVICE  
TO THE AMATEUR FRATERNITY  
HAMS SERVING HAMS**

PLACE YOUR ORDER WITH ONE OF THE FOLLOWING HAMS

M. Weinschenker K3DPJ PO Box 353 Irwin, Pa. 15642	Pete Fragale W8AEN PO Box 585 Clarksburg, W. Va. 26301
---	--

PA Residents Please Add 6% PA Sales Tax Minimum Order \$3.00 All Orders Ppdt in USA



GALAXY V MARK 3  
**—THE NEW 500 WATT MASTERPIECE**

Changes aren't accidental at Galaxy . . . we make them on purpose. It takes a lot of guts (and know-how) to improve an already great product and still sell it for the same price . . . **\$420.00** . . . but we've done it!

We use two of the specially designed GE 6LB6's — the most efficient tube of this type. That means a 30% increase in plate dissipation . . . less heat . . . more reliability, and longer life!

New "horsepower"! The all-new power capability is greater. We're rating the new Mark 3 with a conservative **500 Watt PEP** input. Any questions?

**WANTED:  
 WE BUY USED AMATEUR AND CB EQUIPMENT FOR CASH!**

**RECONDITIONED USED GEAR: FULLY GUARANTEED**

**DRAKE**

R4A	\$290.00
T4X	\$290.00
L4	\$550.00
MS4 & AC3/PS	\$50.00

**\$1180.00**

**Package Deal All Above . . . \$1050.00, Cash**

**JOHNSON**

2000 Complete	Very Good	\$525.00
500 Complete	Very Good Cond.	\$325.00

**SWAN**

240 & AC/PS	\$250.00
350 SSB Kit	\$345.00

**CLEGG**

Apollo Six Lin	\$165.00
----------------	----------

**GONSET**

Comm 111 2Mtr.	\$150.00
----------------	----------

**SBE**

SBE-34	\$325.00
SB2-LA	\$180.00

LOTS OF GOOD CHOICE GEAR FOR SALE OR TRADE — WRITE FOR LATEST LIST.

IN STOCK FOR IMMEDIATE DELIVERY, GALAXY, SWAN, SBE AND DRAKE

*Bob's* **AMATEUR**  
**ELECTRONICS**

"THE COMPLETE HAM STORE"

**Phone CE 5-6387**

927 N.W. 1st Oklahoma City, Oklahoma 73106

"WE TAKE TRADE-INS ON ALL LINES OF NEW EQUIPMENT"  
 TWO-WAY RADIOS — SALES • SERVICE • INSTALLATIONS

# QUADS SKYLANE QUADS

6 meter  
up to 8 elements  
from \$23.95

10 meter  
up to 6 elements  
from \$39.95

11 meter  
up to 6 elements  
from \$39.95

10 - 15 - 20 meters tri-banders  
of 2, 3, or 4 elements  
from \$39.95

Quad Kits — or complete quads

Aluminum Centerplate  
10" x 10" x 3/16"



Aluminum Casting  
2-piece  
for any boom from  
1" to 2" in diameter



Fiberglass Spreaders  
12' 7" long  
1 3/8" butt - 1/2" tip  
\$7.00 each



Bamboo Spreaders  
12' 7" long  
1 3/8" butt - 1/2" tip  
\$2.25 each




Reflector Coils



Extra Special Offer to the purchaser of any E-Z Way Tower and any Quad, we offer 5% off the amateur net price and ship prepaid to your door in any of the 48 states.

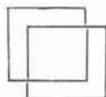Florida Authorized Distributor for E-Z WAY TOWERS



SKYLANE PRODUCTS • Amateur Antenna Kits

406 BON AIR AVENUE, TEMPLE TERRACE, FLA. 33617 • PHONE 813-988-4213

radio amateur

# callbook

GET YOUR NEW  
ISSUE NOW!

Over 283,000 QTHs  
in the U.S. edition  
\$6.95

Over 135,000 QTHs  
in the DX edition  
\$4.95



These valuable EXTRA features included in both editions!

- QSL Managers Around the World!
- Census of Radio Amateurs throughout the world!
- Radio Amateurs' License Class!
- World Prefix Map!
- International Radio Amateur Prefixes
- Radio Amateurs' Prefixes by Countries!
- A.R.R.L. Phonetic Alphabet!
- Where To Buy!
- Great Circle Bearings!
- International Postal Information!
- Plus much more!

See your favorite dealer or order direct (add 25¢ for mailing in U.S., Possessions & Canada. Elsewhere add 50¢).

WRITE FOR  
FREE  
BROCHURE!



RADIO AMATEUR  
callbook INC

Dept. Q 4844 W. Fullerton Ave.  
Chicago, Ill. 60639

## ATTENTION ALL ACTIVE AMATEUR RADIO OPERATORS

The **HAM PHONE DIRECTORY**, which heretofore concentrated on the South Florida area, with profits going to a local charity, will now accept listings from any active Amateur in the U. S. for the next edition (8th). Amateurs who may care to participate will kindly submit the following information. Call, name, full address, zip, area code and phone numbers. Please include a self-addressed, stamped #10 size envelope for further info regarding dates of availability, low advance subscription price et cetera. Thank you.

Mail to:

*Ham Phone Directory*

1136 S. W. 74th CT.  
MIAMI, FLORIDA 33144

## SLEP ELECTRONICS COMPANY WANTS YOUR MILITARY SURPLUS EQUIPMENT

BUY • SELL • TRADE

**AIRBORNE EQUIPMENT:** ARC-34, ARC-38, ARC-44, ARC-45, ARC-51, ARC-52, ARC-54, ARC-55, ARC-59, ARC-60, ARC-73, ARC-95, ARC-102, ARC-111, ARC-115, ARC-131, ARC-134, ARN-14, ARN-18, ARN-21, ARN-30D, ARN-31, ARN-32, ARN-52, ARN-59, ARN-67, ARN-68, ARN-82, ARN-83, ART-34, APN-9, APN-22, APN-70, APN-117, APN-122, APN-129, APN-133, APN-134, APN-141, APN-158, RT-279A/APX-25, APX-44, APX-68, APX-72, ARA-25, ARA-31, ARA-41, ARA-48, ARA-50, ARA-54, ARA-56. **COUPLERS,** CU-527/AR, CU-942, CU-991/AR, CU-1658. **ASQ-3, ASQ-18, ASQ-19, SCR-695A IFF, APA-69, APA-89, ASA-13, ARR-36, VHF-101, 102. COLLINS 17L-6, 17L-7, 51X-2, 18S-4A, 618S-1, 618T, 618F, 618M, 51RV-1, 51Y-4.**

**GROUND EQUIPMENT:** RT-66, 67, 68, 70, 77, PP-112/GR, PRC-8A, 9A, 10A, PRC-25, PRC-41, TRC-24, VRC-24, GRC-9, GRC-19, GRC-27, GRC-46, T-217A, R-278B/GR, MD-129A, UPX-1, UPX-5, UPX-7, UPX-12, TMQ-5, TED, TDE, SPA, URA, SRA, SRT.

**RECEIVERS:** R-220/URR, R-388/URR, R-389/URR, R-390A/URR, R-391, R-392/URR, R-836/ARN, R-1051, R-1125, R-1297/AR, R-1388/ARN, R-1391/ARN, R-1433/U, COLLINS 51J-3, 51J-4, 51S-1, URR-13, URR-27, URR-29, URR-35, APR-5A, 13, 14, 17, RDO, RAL, SP-600JX, ARN-41.

**TEST EQUIPMENT:** SG-1A/ARN, SG-2/ARN, SG-3/ARN, SG-12A/U, SG-13/ARN, SG-24/TRM-3, SG-66A/ARM-5, SG-92/U, ARM-5, ARM-8, ARM-11, ARM-22, ARM-25, ARM-31, ARM-45, ARM-47, ARM-63, ARM-66, ARM-68, ARM-69, ARM-92, UPM-98, UPM-99, URM-25, URM-26, URM-32, URM-43, URM-47, URM-48, URM-52, URM-76, URM-78, URM-80, URM-81, URM-103, URM-105, URM-120, URM-127, BC-376, ARC H-14, H-16, H-23, HEWLETT PACKARD 606A, 608D, 612A, 616B, 618A, 620A, 626A, etc. BOONTON "Q" and RX METERS. HLI-103 TACAN TESTER. 479S-3, 479T-2. TS-505D/U, TRM-1, TRM-3, TS-183/U, TS-330/U, TS-510A/U, TS-683/U, TS-710, TS-723/U, etc. MD-1, MD-2, MD-83A/ARN. ALSO OTHER SURPLUS EQUIPMENT WITH PRM, PSM, UPM, USM, URM, GPM, SG, APA, ASA, APR, ASG, ASM, ASN, GRR, PRC, GRC, URC, VRC PREFIXES.

**COMMERCIAL TEST EQUIPMENT BY:** BIRD, BOONTON, MEASUREMENTS, H-P, NARDA, GR, SPERRY, ARC, GERTSCH, EMPIRE DEVICES, STODDART, LEEDS & NORTHRUP, BENDIX, NORTH ATLANTIC, ESTERLINE ANGUS, CMC, FAIRCHILD.

**AIRCRAFT INVERTERS:** 400 Cycle Type by BENDIX, LELAND, JACK & HEINTZ.

**TECHNICAL MANUALS:** Buy and Sell, Military and Commercial Books.

**TUBES:** Transmitter Type by EIMAC, RCA, AMPEREX, VARIAN, RAYTHEON, WESTINGHOUSE, etc.

**WANTED:** SURPLUS SCOUTS IN EVERYTOWN, WORLDWIDE. TELL US WHAT EQUIPMENT IS AVAILABLE AND WE WILL ADVISE YOU WHAT IT IS WORTH IN "CASH". EARN GOOD MONEY SPARE TIME. REFER TO THIS AD FOR TYPE EQUIPMENT NEEDED.

**TRADE YOUR SURPLUS FOR NEW HAM GEAR:** WE STOCK: AMECO, BTL, DRAKE, EIMAC, E-Z WAY, GONSET, GALAXY, HAMMARLUND, HAM-M, HY-GAIN, MOSLEY, NATIONAL, SWAN, SBE, SHURE, SONAR, WEBSTER, TRI-EX. WE PAY SHIPPING ON TRADE-INS. CASH DEALS PAID AT ONCE UPON RECEIPT. TRADES SHIPPED FROM STOCK. COMPLETE PACKING FACILITIES, EXPORT ORDERS SHIPPED F.O.B. SEAPORT, TAMPA, FLORIDA.

WRITE - WIRE - PHONE (813) 722-1843 BILL SLEP, W4FHY

## SLEP ELECTRONICS COMPANY

2412 HIGHWAY 301 N. ELLENTON, FLORIDA 33532



PHONE (813) 722-1843


### ATV'ERS

For the largest US ATV magazine; Technical reports & ATV directory SEND \$2 for a 1 year subscription TO:

**A5 MAGAZINE**

150 DeLong Ave.,  
Dumont, NJ 07628

### ALL-BAND ANTENNA CONNECTOR

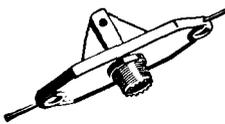

**HYE-QUE 1** molded connector has eyelets for securing antenna elements, heavy copper leads, coax PL259 connector for feedline, and tie-point for antenna support. Drip-cap protects connector. Reinforced. At your dealer's, or \$2.95 postpd. Companion insulators. 2 for 99¢ ppd. Instructions included.

**BUDWIG MFG. CO.,** P.O. Box 97H, Ramona, Calif. 92065

**NOW**

EXCLUSIVE 66 FOOT **MOR-GAIN** 75 THRU 10 METER DIPOLE

**NO TRAPS — NO COILS — NO STUBS — NO CAPACITORS**

Fully Air Tested — Thousands Already in Use

**NEW BEAM**

**MULTIBAND SECTIONS** FULLY GUARANTEED US PAT #3,229,298

40% Copper Clad wire—Under three lbs. Air Weight—Rated for full legal power—AM/CW or SSB—Coaxial or Balanced 50-75 ohm feed—VSWR under 1.5 to 1 at most heights—Rust resistant hardware—Drop-proof insulators. Completely assembled, ready to put up. Model 75/40 Amateur Net \$26.00. Terrific Performance—No coils or traps to break down or change under weather conditions—Fully Guaranteed. MODEL SB20 "SHORTY" 10 & 20 METER TRAP BEAM—\$59.95.

**NEW SUPER HEAVY DUTY DIPOLES 66' LONG. RATED 4KW PEP-2000 POUND BREAKING STRENGTH—DELTRIN CENTER & CERAMIC END INSULATORS—OUT PERFORM FULL SIZE DIPOLES;**

75/40 SHD \$33.00; 75-20 SHD \$38.00; 75-10 SHD \$48.00

MODEL 75-15 NOVICE.....\$30.00 • 66 FEET LONG  
MODEL 40/20.....\$20.00 • 36 FEET LONG  
MODEL 80/40CW.....\$28.00 • 69 FEET LONG  
MODEL 75-10.....\$37.00 • 66 FEET LONG  
MODEL 75-20.....\$33.00 • 66 FEET LONG

ORDER DIRECT OR WRITE FOR FULL INFORMATION

**MOR-GAIN**

P.O. Box 6006  
Alexandria, Virginia 22306

OR THRU YOUR FAVORITE DISTRIBUTOR

Phone: 703-768-7766; Nights and Holidays 703-780-2171

## oscillator/monitor

- a sensitive broadband RF detector gives audible tone signal in the presence of any RF field from 10mc to 1 kw and 100kc to 1000mc
- a CW monitor with positive "RF" switch uses only 8" pickup antenna and NO connection to rig or key
- a code practice oscillator with adjustable tone & built in speaker
- high gain 4 transistor circuit powered by long life AA pencil
- 16 gauge aluminum cabinet in white & black epoxy finish, 3 1/2" by 2 3/8" by 1 1/4", weight 8 ounces
- 100% US made and guaranteed



1295 (batt incl)  
ppd usa & can  
send cert ck or m.o.  
ny res add 5% tax

the James research company  
11 schermerhorn st., brooklyn n.y. 11201

### ETCHED CIRCUIT BOARDS

Novice Trans.	2.75	Novice Recvr.	2.75
RTTY Encoder	2.50	RTTY Decoder	4.00
UHF Dippers	2.25	SWR Bridge	1.25
Lab Supply	3.50	144 Conv.	5.75
Keyer	4.95	CP Osc. Mon.	1.25

Conn. Residents add Sales Tax.  
Send order or Catalog request to . . .

HARRIS CO., BOX 985,  
TORRINGTON, CONN. 06790

### WE PAY CASH FOR TUBES

LEWISPAUL ELECTRONICS INC.  
303 W. Crescent Avenue  
Allendale, New Jersey 07401

### CQ de W2KUW BEST OFFER!!

Paid . . . . . for any piece of aircraft or ground radio units, also test equipment. All types of tubes. Particularly looking for 4-250 • 4-400 • 833A • 304TL • 4CX1000A • 4CX5000A et al. 17L • 51X • 390A • ARM • GRM • GRC • UPM • URM • USM units.  
TED DAMES CO., 310 Hickory St., Arlington, N.J. 07032

## NOISE BLANKER

Removes interference generated by auto ignitions, appliances, radars, and other sources of high energy pulse noise.



Provides the noise suppression required for reception of weak VHF DX and scatter signals. Connects between converter and receiver; for 50-93 ohm coax. Solid-state design features silicon Field Effect Transistors for reliability and minimum cross-modulation. Adjustable output coupling for optimizing system gain.

Send for technical brochure TNB

WESTCOM ENGINEERING COMPANY  
P.O. Box 1504 San Diego, Cal 92112



KEEP UP TO  
DATE ON  
YOUR DXING

A weekly magazine (16 to 24 pages each week.

Current DX that's on the air, and info about what's planned for the immediate future. What's being heard by the boys. Etc.

FULL DX INFO EVERY WEEK.

Per year—Surface mail (they say most 1st class mail actually goes via air) \$11.00

The DXERS Magazine, (W4BPD)  
Route 1, Box 161-A,  
Cordova, S.C. 29039

### HIGHEST \$ \$ PAID FOR TUBES



120 WEST 18th STREET

NEW YORK 10011 • 212-242-7400

Free Tube List

### RADIO COMMUNICATION CO.

• THE COMPLETE HAM STORE  
SERVING COLORADO and ADJACENT STATES  
W. 100 Avenue and Alkire Street  
Arvada, Colorado 80002  
303-466-3000



### NOW

RAZOR SHARP CW  
RECEPTION WITH  
YOUR TRANSCEIVER!

WITH A *Main* CWF-1  
Between Your Headphones  
And Your Rig

REQUEST BROCHURE \$19.95  
Money Back  
Guarantee

- ★ No Power Required
- ★ Plugs Into Phone Jack
- ★ Low Insertion Loss
- ★ 120 Cycles Narrow
- ★ 2 to 4 Ohms In. 2K Out



ELECTRONICS, INC.

Dept. H-6  
353 Pattie  
Wichita, Kans. 67211  
(316) 267-3581



**Radio Amateurs  
Reference Library  
of Maps and Atlas**

**WORLD PREFIX MAP** — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables . . . postpaid **\$1.00**

**RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD** — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities; Boston, Washington, D.C., Miami, Seattle, San Francisco & Los Angeles. . . . postpaid **\$1.00**

**RADIO AMATEURS MAP OF NORTH AMERICA!** Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus informative information on each of the 50 United States and other Countries . . . postpaid **\$1.00**

**WORLD ATLAS** — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages, size 8 1/4" x 12" . . . . . postpaid **\$2.00**

**Complete reference library of maps — set of 4 as listed above** . . . . . postpaid **\$3.00**  
See your favorite dealer or order direct.

**WRITE FOR  
FREE  
BROCHURE!**

RADIO AMATEUR



**callbook INC.**  
Dept. Q 4844 W. Fullerton Ave.  
Chicago, Ill. 60639

**DON'T QRT!**

**LT-5**



When you leave your QTH put your LT-5 portable 40-80 meter CW transmitter in your pocket.

**\$24.00 KIT**  
**\$35.00 WIRED**

**SEND FOR FREE  
DATA SHEET**

**OMEGA ELECTRONICS COMPANY**  
10463 Roselle St. • San Diego, Calif. 92121

**SURPLUS EQUIPMENT WANTED TO BUY BY  
THE FASTEST GUN IN THE EAST**



No horsing around, we pay fast . . . in 24 hours . . . and we pay more. We'll swap or trade new equipment too . . . We quote fast too. We also pay for shipping, insurance, etc. You call fast, now, collect, for fast quote.

**SPACE ELECTRONICS**  
div. of **MILITARY ELECTRONICS CORP.**

4178 Park Avenue, Bronx, New York 10457, (212) CY 9-0300

**LET W3KT  
FORWARD YOUR  
DX QSLs**

Join the thousands of satisfied hams who have been using this service for the past seven years. During 1967 alone, over 200,000 QSLs were forwarded to DX stations. This is a DELUXE service, insuring prompt and continuous mailings, and involving a minimum of effort on your part.

Just fill in your QSLs and send them to W3KT. You don't have to address the cards, or indicate the QSL manager, or send any SASEs. Where a DX station uses a stateside QSL manager, your card will be sent to him with an SASE, and the reply will come back to W3KT, who will send it to your call area QSL bureau. Other QSLs will be sent to the proper QSL Bureau, or, if necessary, direct.

Remember, your QSL is a personal message. Therefore W3KT sends it by FIRST CLASS MAIL only.

The charge: Four cents per QSL, 30 cards per dollar. **NO MEMBERSHIP FEE.**

**SAVE TIME! SAVE MONEY!**

**W3KT QSL SERVICE**

RD 1, Valley Hill Road Malvern, Penna. 19355

**GET IT from GOODHEART!**

**EVERYTHING UNCONDITIONALLY GUARANTEED**

**SILIC. RECTIF.** 8000 PIV 400 MA. Large user's termin. Invent. not rejects! Slater SLA08-2. Max: reverse, 2 uA; fwd drop, 8.2 v. Cost \$8 ea. Bakel. encapsul. 3x1/2x1" **\$5.30**  
ht. ea. PAIR postpaid

**MARCONI FM DEVIATION METER TF-934**, regularly \$890. Reads dev. w/ranges 5, 25, 75 kc. Has audio monitor. Made for MIL. 2 1/2-100 mc. easily reaches 1000 mc on harmonics; we include all instructions. **\$249.50**  
Checked out, ready to use.

**Brand New VHF revrs** look like BC-453 Command but are 9-tube 108-135 mc. 2 uv sens., 2 rf's, 3 IF's; noise lmtr; ave W/schem. instruct., spline knob & graph to set freq. by counting turns. A.R.C. Type 13B, 28v htr **\$22.50**  
wiring: 7# shpg. wt.

**R32** is same but w/squelch; 14v htr wiring **\$27.50**  
**R-23/ARC-5** Command revr 190-550 kc. **14.95**  
**A.R.C. 12 #22** Command revr 540-1600 kc. **17.95**  
**LM-14** freq. meter, .01% 125 kc-20 mc **\$7.50**  
**TS-323/UR** freq. meter 20-480 mc., .001% **\$69.50**  
**BC-221's OK** **\$67.50** **TS-175 OK** **\$27.50**  
**CLOSING OUT Radio Receivers 38-4000 mc at CRAZY LOW PRICES!** Ask for APR-4/YCV-253 sheet.

**ALL-BAND SSB RCVR BARGAIN:** Hallicrafters R-45/ARR-7, 550 kc to 43 mc continuous. Voice, CW, MCW, aligned, grtd, w/book; 2-RF, 2-IF's, S-meter; noise lmtr; 3 xtl, 9 non-xtl selectivity **\$149.50**  
choices. Less pwr sply: **\$120**  
60 cy pwr sply: **\$30**. SSB product detector: **\$20**

**SP-600-JX** Revr 54-54 mc, Exc. Cond., w/book **\$25.00**

**TIME PAY PLAN:** Any purchase totaling \$160.00 or more, down payment only **10%**

**DO NOT ASK FOR CATALOG! ASK FOR TYPES OR SPECIFIC ITEMS. FAST REPLY GUARANTEED. WE ALSO BUY! WHAT DO YOU HAVE?**

**R. E. GOODHEART CO. INC.**  
Box 1220-HR, Beverly Hills, Calif. 90213  
Tel: Area 213, office 272-5707, messages 275-5342



TRI-EX'S

NEW

IMPROVED

THD

GUYED TOWERS

shown with internal  
rotator, 2" mast,  
Tri-Band Beam

Choose from 8 models, 4 with 20 ft. sections, 4 with 10 ft. sections — all hot-dipped galvanized, inside and out, *after* fabrication.

GET THESE  
FEATURES

- Tower Heights to 88 ft.
- Easy to Erect
- Cranks up & down
- Geared winch
- Aircraft raising cable
- Ball-bearing pulleys
- Precision formed guides
- Hinged base plate

PRICES START AT

\$138<sup>25</sup>

FREE BROCHURE



**Tri-Ex TOWER CORPORATION**

7182 RASMUSSEN AVE., VISALIA, CALIF.

# Advertisers iNdex

A-5 Magazine .....	93
AMECO Equipment Corp. ....	Back cover
Autovolt, Inc. ....	33
B & F Enterprises .....	89
Bob's Amateur Electronics .....	91
Budwig Mfg. Co. ....	93
Ceco .....	94
Comdel, Inc. ....	63
Comtec, Inc., Book Division .....	69
Cubex Company .....	90
Dames Co., Theodore E. ....	94
DXERS Magazine, The .....	94
Edwards Electronics .....	59
EIMAC a division of Varian .....	5
Electronic Applications Co. ....	58
Electronics Center, Inc. ....	87
FM Magazine .....	58
Goodheart, Co., Inc., R. E. ....	95
Gordon Co., H. W. ....	Cover III
Hafstrom Technical Products .....	90
Ham Radio Magazine .....	47, 88
Harris Co., The .....	94
Henry Radio Stores .....	1
International Communications and Electronics Corp. ....	2
James Research Co., The .....	94
Lewispaul Electronics Inc. ....	94
Main Electronics, Inc. ....	94
Meshna, John Jr. ....	83
Military Electronics Corp. ....	95
Mission Ham Electronics .....	55
Mor-Gain .....	93
Mosley Electronics, Inc. ....	13
Omega Electronics Co. ....	95
Phone Direct .....	92
Quement Electronics .....	43, 51
Radio Amateur Callbook, Inc. ....	92, 95
Radio Communication Co. ....	94
RCA Electronics Components & Devices .....	Cover II
Skylane Products .....	92
Slep Electronics Co. ....	93
Swan Electronics Corp. ....	34, 35
Tri-Ex Tower Corp. ....	96
Ultramatic Systems Lab. ....	83
Unadilla Radiation Products .....	88
United Radio Co. ....	90
Vanguard Labs. ....	89
W3KT QSL Service .....	95
Weinschenker, M. ....	90
Westcom Engineering Co. ....	94

The Yaesu FTdx400, imported exclusively into this country by Spectronics, has demonstrated appeal to most American hams. It seems to have been designed around our requirements and is indeed the first of a new breed of high value transceivers offered by the Japanese. The FTdx400 provides for 500 watts of PEP input, using 6KD6 tubes, which have approximately 30% greater surface area in their anode structure than is provided by the 6LQ6 or the 6HF5. Thus, a more conservative approach is indicated in the linear portion of this product.

Containing its own built-in power supply with a transformer weighing 21 pounds, the FTdx400 will operate cool and with better regulation than most of its American counterparts.

Pleasing appearance and the inclusion of features not found elsewhere make the FTdx a delight to operate. For example, the FCC has modified our regulations so that certain classes of licenses can only work to 25 KHz points. This transceiver provides for both 100 KHz and 25 KHz markers. The VOX is built in, as is incremental tuning for both receiver and transmitter. The FTdx400 covers all of 80, 40, 20, 15, and 10 meters, but in addition, provides for three 500 KHz



### A SUPERIOR TRANSCEIVER

#### BOX SCORE

- Frequency Range:**  
3.5-4 Mc, 7-7.5 Mc, 14-14.5 Mc, 21-21.5 Mc, 28-30 Mc (3 more 500 KC receiver bands can be added).
- Frequency Stability:**  
Less than 100 c/s drift in any 30 minute period after warm up.
- Antenna Impedance:**  
50 to 120 ohm unbalanced.
- Maximum Input:**  
500W PEP SSB, 440W CW, 125W AM.
- Carrier Suppression:**  
-40 db
- Sideband Suppression:**  
-50 db (at 1,000 c/s)
- Distortion Products:**  
Down at least 25 db
- Audio Bandwidth:**  
300-2, 700 c/s  $\pm$  3 db
- Receiving Sensitivity:**  
0.5  $\mu$ V, S/N 20 db (14 Mc SSB)
- Selectivity:**  
2.3 Kc (-6 db), 3.7 Kc (-55 db)
- IF and Image Ratio:**  
More than 50 db down
- Audio Output:**  
1 watt @ 5% distortion
- Output Impedance:**  
8 ohm, 600 ohm
- Tubes and Semiconductors:**  
18 tubes, 9 transistors and 33 diodes
- Power Source:**  
AC 117 or 220 volts, 50/60 c/s
- Dimensions:**  
15 $\frac{1}{4}$  wide, 6 $\frac{1}{4}$  high, 13 $\frac{3}{4}$  deep
- Weight:** 50 pounds

segments outside of these amateur bands. A separate oscillator is available for those wishing to operate with split frequencies. This device sells for \$75.00.

Up to four crystal controlled receiving positions may be accommodated, without the use of the external oscillator. Exceptionally good resolution for read out is provided. You can, for example, read to 500 cycles easily. The self-contained meter reads plate current and acts simultaneously as an S meter and RF output indicator. A 1.6 shape factor crystal lattice filter provides 2.3 kc selectivity at -6 db points, and operates at a center frequency of 3180 KHz. Unexcelled stability and suppression are provided in this rig. Study the box score and see for yourself.


Best of all, the price of this Yaesu with self-contained power supply and external speaker in a matching cabinet is but \$615.00. Service is not a problem, for standardized parts are used and are stocked in California as well as here at this firm.

If you want the best value, the most flexibility and one of the highest ratios of power to dollars, choose the Yaesu FTdx400. It's really a smoothy. Send for your brochure today.

## HERBERT W. GORDON COMPANY

Harvard, Massachusetts 01451 • Telephone 617 - 456 - 3548

*"Helping Hams to Help Themselves"*

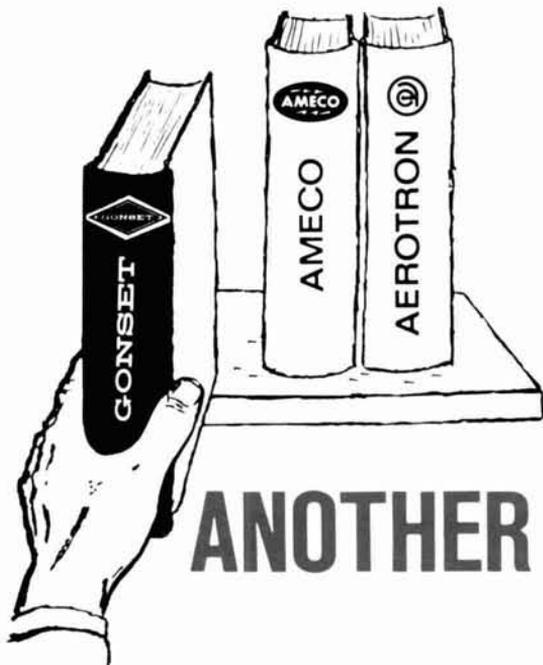

## ANOTHER ADDITION

**AEROTRON** is proud to announce the acquisition of the famous Gonset line of quality amateur radio equipment. This acquisition appreciably broadens the line of equipment and components which we have to offer to the amateur and related markets. We are now shipping directly from our award-winning plant in Raleigh, the Gonset Communicators, Single Sideband VHF transceivers, HF and VHF linear amplifiers and other items bearing the Gonset name. In the coming months we will have even more.

**AEROTRON**, with more than twenty years in the two-way radio manufacturing business, has also acquired the AMECO Equipment Corporation during the past year. Ameco, formerly of Mineola, New York has been completely moved to our Raleigh plant and we are constantly adding to this popular line of economically priced equipment which is sold by more than a thousand radio supply outlets throughout the country.

The **GONSET** name has been a familiar and respected one by hams the world over for many years. It is with a great deal of pride that we now have it as a division of Aerotron, Inc.



DIVISION OF AEROTRON



DIVISION OF AEROTRON

### AEROTRON

U. S. HIGHWAY 1, NORTH RALEIGH, NORTH CAROLINA 27608

CU at the A·R·R·L New England Division  
Convention in Swampscott, Mass., June 1 & 2



Stuart F. Meyer, W2GHK/4.