

HAM

AN ARGUS SPECIALIST PUBLICATION

SEPTEMBER '84

RADIO

Margem

99p

TODAY

The ALPHA

a single band top quality
SSB/CW transceiver
design for HF

Plus

Belcom LS202E 2m
FM/SSB Handheld –
a realistic proposition?



A Fresh Look at the Yaesu FT200 with G3LLL

VHF CONTESTING – from hardened practitioner, John Ridd, G8BQX.



PARTNERSHIP MICROSYSTEMS ... Things for the VHF man.

The G3WZT 2m GaAsFET mast head pre-amp.

PCB 41601 £14; S3030 £8.65; BF256A 55p

N-type connector (rear cable entry) £4

Misc. parts; comprising

- 2 off 100n ceramic monobloc C7, 18
- 2 off 1n5 chip C9, 11; 2 off 15n chip C10, 12
- 4 off 5082-2835 D1-4; 36" 18 swg silver plated wire
- Copper foil for cable termination and input screen £3.25

Control units

PCB 41602 £9; PCB 41603 £6.50; 100n ceramic monobloc 10p

Relay DR 12V (Good for 50W at 144 MHz) £4

Chip capacitors 1n5 100V or 15n 50V 10 for £1

All the above components are EXACTLY as used by G3WZT to build prototypes.

Complete pre-amp built, tested and aligned £88.25

Logbooks for the VHF man, with VHF countries and countries list — includes space for QTH/WAB locator £2

All prices include VAT. Post & packing 50p per order.



**PARNERSHIP MICROSYSTEMS LTD, TARDIS HOUSE, COWFOLD,
WEST SUSSEX RH13 8DR Telephone: 040386 227**

Bredhurst
electronics



ANTENNA BITS	£	C&P
Hi-Q Balun 1:1 5kW PEP	9.95	(0.75)
W2AU Unadilla 4:1 Balun	19.90	(1.20)
7.1/14/21/28 MHz Unadilla traps — pair	19.90	(1.20)
7.1 MHz Rat-traps — white epoxy — pair	8.95	(1.50)
Self amalgamating Tape 10m x 25mm	3.95	(0.75)
T-piece Polyprop. Dipole centre	1.50	(0.40)
Polyprop Strain insulators	0.50	(0.10)
Small ceramic egg insulators	0.50	(0.10)
Large ceramic egg insulators	0.75	(0.10)
75ohm Twin Feeder — Light duty per metre	0.16	(0.04)
300 ohm Twin Feeder — per metre	0.14	(0.04)
UR67 Low loss coax 50 ohm per metre	0.65	(0.20)
UR76 50 ohm coax per metre	0.25	(0.05)
UR70 70 ohm coax per metre	0.30	(0.05)
4mm Polyester Guy Rope(400kg) permetre	0.18	(0.04)

H.F. RECEIVERS

Icom IC-R71 Gen. cov receiver	649.00	(—)
Icom IC-R70 Gen. cov. receiver	565.00	(—)
Trio R2000 Gen. cov. receiver	436.00	(—)
Trio VC-10 VHF converter for R2000	117.00	(—)
Yaesu FRG 7700M with memory	455.00	(—)
Yaesu FRG 7700 without memory	385.00	(—)
Yaesu FRT 7700 antenna tuner	48.25	(1.50)
Trio R600 Gen. cov. receiver	272.00	(—)

UHF/VHF RECEIVERS

A.O.R. AR2001 25-500MHz	345.00	(—)
J.I.L. SX200N	299.00	(—)
F.D.K. ATC720 Airband handheld	169.00	(—)
F.D.K. RX40 handheld 141-179 MHz	142.00	(—)

HEADPHONES

Trio HS5 deluxe	24.48	(1.50)
Trio HS6 Ultra lightweight	17.49	(1.50)
Yaesu YH55 padded	12.50	(1.50)
Yaesu YH77 lightweight	12.50	(1.20)

TEST EQUIPMENT

V.H.F. Wavemeter (130-450 MHz)	27.50	(—)
DM 81 Trio Dip Meter	75.00	(0.75)
Black Star Frequency Counter(600MHz)	134.00	(1.50)

H.F. TRANSCEIVER

Trio TS 930S	1195.00	(—)
Trio TS 430S Gen. Cov. Receiver	779.00	(—)
Trio TS 830S	758.00	(—)
Yaesu FT 757GX Gen. Cov. Receiver	719.00	(—)
Trio TS 530 SP	669.00	(—)
Trio TS 130S	576.00	(—)
Yaesu FT77	479.00	(—)

VHF/UHF TRANSCEIVERS

Trio TS 780 2M/70cm multimode	850.00	(—)
Yaesu FT726R (2M fitted) multimode	775.00	(—)
Trio TW4000A 2M/70cm FM mobile	488.00	(—)
Trio TM401A 70cm FM mobile	310.00	(—)
Trio TM201A 2M FM mobile	279.00	(—)
Yaesu FT290R2M multimode portable	279.00	(—)
Trio TR3500 70cm handheld	265.00	(—)
Yaesu FT790R 70cm multimode portable	259.00	(—)
Trio TR2500 2M handheld	246.00	(—)
Icom IC02E 2M handheld	239.00	(—)
Icom IC4E 70cm handheld	229.00	(—)
Yaesu FT 208R 2M handheld	209.00	(—)
Yaesu FT708R 70cm handheld	189.00	(—)
Icom IC2E 2M handheld	179.00	(—)

BREDHURST ELECTRONICS — HIGH ST — HANDCROSS — W. SUSSEX — 0444 400786

QUARTZ CRYSTALS

CRYSTALS FOR 2 METRES

STOCK CRYSTALS	PRICE
HC25 £2.15 FOR ONE CRYSTAL	£1.96 WHEN 2 OR MORE PURCHASED
HC6 £2.15 FOR ONE CRYSTAL	£2.05 WHEN 2 OR MORE PURCHASED
TX CRYSTALS	RS CRYSTALS
HC6/U 8MHZ 30PF	44 MHZ SERIES RES
HC25/U 12MHZ 30 & 40PF	44 MHZ SERIES RES
HC25/U 18 MHZ 25 & 20PF	1415 MHZ 20 & 30 PF
HC25	SCANNER XTLS (NOT SR9)
	full list available on request please send SAE
4 METRE CRYSTALS FOR 70.20 IN HC6/U AT £2.40 each	
TX 8.78250	RS 29.78000
70CM CRYSTALS £5.00/pr or £2.50 each	
For Pye PF1 PF2 & PF70 series Wood & Douglas and FDK MULTI U11	
SUB(433.2) SU20 RBO RB2 RB4 RB6 RB10 RB11 RB13 RB14 RB15.	
ALSO for MULTI U11 ONLY SU12 SU16 SU18	
CONVERTER CRYSTALS IN HC18/U AT £2.85 each.	
22,000, 38,666, 70,000, 96,000, 116,000, 101,500, 116,000	
FREQUENCY STANDARDS £2.75 each	
HC6/U 200kHz 1000kHz 3.50 MHz 5.00 MHz 10.000 MHz 10.700 MHz	
HC18/U 10000kHz 7.00 MHz 10.70 MHz 48.00 MHz 100.00 MHz	
Also HC6/U 200 kHz 455 kHz £3.25 each	
TONEBURST, I.F. & MPU CRYSTALS IN HC18 £2.25 EACH	
7.168 MHz (For 1750 Hz Tone), 10.245 (for 10.7 I.F.)	
3.2768 5.0688 14.3180 15.00000	
YAESU CRYSTALS for FT101's FT901 & etc £4.00 each	
Many available ex stock (A list is available on request please send SAE.)	

FUNDAMENTALS

FREQUENCY RANGE	PRICE	3rd OVT	5th OVT	7th OVT	MADE TO ORDER CRYSTALS OVERTONES	FREQUENCY RANGE	PRICE
5 TO 50 KHZ	£21.00				2.0 TO 175.0 MHZ	2 TO 3 weeks	
50 TO 150 KHZ	£11.00				5 TO 999.9 kHz	6 to 8 weeks	
150 TO 500 KHZ	£7.80				1 TO 1.499 MHZ	3 to 4 weeks	
160 TO 999 KHZ	£11.90						
1 TO 1.5 MHZ	£10.75						
1.5 TO 2.0 MHZ	£5.10						
2.0 TO 6.0 MHZ	£4.75						
6 TO 21 MHZ	£4.55						
21 TO 25 MHZ	£6.50						
25 TO 30 MHZ	£8.50						

Unless otherwise requested fundamentals will be supplied for 30pf load capacitance and overtones for series resonant operation

HOLDERS:— PLEASE SPECIFY WHEN ORDERING — else HC25/U supplied for XTLs above 3 MHz HC13/U 6-200 kHz HC6/U & HC33/U 170 KHZ-175 MHz HC18/U & HC25/U 2-175 MHz

DISCOUNTS: Price on application for 10+ units to same frequency/spec. or bulk purchases of mixed frequencies. We supply FREE xtals for use in U.K. repeaters.

COMMERCIAL CRYSTALS: available on fast delivery and at competitive prices. Please send for list stating interests

EMERGENCY SERVICE: for XTALS 1 to 125 MHz. Add the surcharge for each XTAL. Days refer to working days. 4 days +£12, 6 days +£7, 8 days +£5, 13 days +£3.

CRYSTAL SOCKETS HC25 £0.20 ea. HC6 £0.25 ea. MINIMUM ORDER CHARGE £1.50 unless ordered with crystals

TERMS: Cash with order post inc. to U.K. & Ireland. Cheques & P.O.'s to OSL LTD.

A stamped addressed envelope with ALL enquiries please.



QuartSlab
MARKETING LTD

P.O. Box 19
Erith
Kent DA8 1LH

**ALL PRICES ARE
EX VAT PLEASE ADD 15%**

Telephone: 01-318 4419 24Hr Ansafone: Erith(03224)30830
Telex: 8813271 GECOMS-G (Attention QUARTSLAB)

HAM RADIO TODAY

Acting Editor
Steve Ireland, G3ZZD
Consultant Editor
Dave Bradshaw

Advertisement Manager
David Gadsden, G4NXV
Classified Sales Executive
Debbie Miller

Managing Editor
Ron Harris
Chief Executive
T. J. Connell

Published by:
Argus Specialist Publications Ltd.,
1 Golden Square,
London W1R 3AB.
Telephone: 01-437 0626


Distributed by:
SM Distribution Ltd.

Printed by:
The Garden City Press Ltd.

Subscription Rate:
UK £14.00
O/Seas Sur: £14.45
O/Seas Air: £27.00
Ham Radio Today,
Subscriptions Dept,
Infonet Ltd,
Times House,
179 The Marlowes,
Hemel Hempstead,
Herts HP1 1BB
Tel: (0442) 48432

ABC

Ham Radio Today is normally published on the first Friday in the month preceding cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1983 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variation affecting price or availability which may occur after the publication has closed for press.

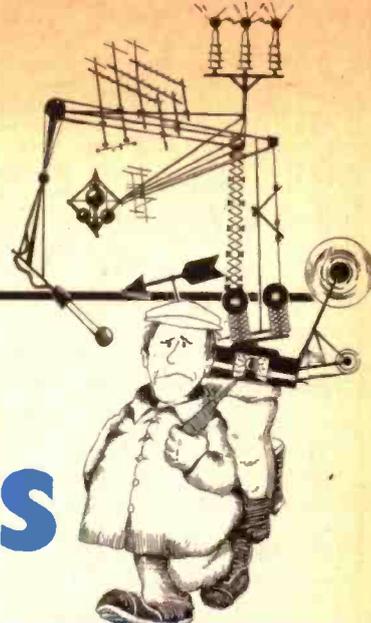

VOLUME TWO NO.9 SEPTEMBER 1984

CONTENTS

REGULAR COLUMNS

LETTERS	4
RADIO TODAY	6
RADIO TOMORROW	46

CONSTRUCTION

THE ALPHA TRANSCEIVER	12
<i>Single band SSB/CW design for HF by G4JST and G3WPO.</i>	
CONTROL UNITS FOR THE 2m GaAsFET PRE-AMPLIFIER	49
<i>Here are two designs by G3WZT to compliment last months project</i>	

FEATURES

RADIO IN THE RISING SUN	21
<i>Tom King, VK2ATJ, visits Japan - land of one million 'hams'</i>	
A FRESH LOOK AT THE FT200.	25
<i>G3LLL profiles and offers servicing advice on this old warhorse</i>	
BASICODE FOR RADIO AMATEURS	31
<i>If you've got a home computer in the shack read this!</i>	
VHF CONTESTING TODAY	40
<i>Veteran John Ridd, G8BQX, gives a pungent personal guide</i>	

REVIEWS

BELCOM LS202E 2m FM/SSB HANDHELD TRANSCEIVER	36
<i>Still hot from the production line An assessment by G3OSS</i>	
NEXT MONTH IN HRT	11
ADDENDUM	24
ADVERTISEMENT INDEX	58
FREE READERS' ADS	59
Emporium Guide.	63
Classified	65

LETTERS

FIFTEEN ALL

Sir, to all those who do *not* support the introduction of a novice licence — I *do*. Two can play at this game.

P. Thompson

AMATEUR RADIO NOVICE LICENCE CAMPAIGN

Sir, A mistaken impression is being given of the proposed UK novice licence and the reasons why it is now necessary. I hope you will allow me to clarify the position of the ARNLC.

Firstly, the idea of a novice licence is not new. I have been pursuing it for 15 years, as has the RSGB for some 37 years, so for people to now say that the aim of the novice licence is to pamper to 'CBers' is a false argument. A novice licence has nothing to do with CB. Its aim is to put back into the hobby of Amateur Radio what was there when I started, an apprenticeship in radio: learning by doing. At the moment the air waves

offer an alternative to CB — which must be a lower class of amateur radio licence. It would be easier but very restricted, but what is wrong with that, given its aim? Let us not have the class A vs class B argument all over again. After all, when the class B licence was introduced the same could have been said that the class B's were being "molly-coddled" etc. Now there are more class B than class A licensees.

The novice licence would put the self-training back into the hobby. How many new G4's have had their first QSOs on CW with the American novice licensees? A novice licence would have no age requirement, 10 watts maximum power, be CW *only* on the CW parts of 28, 21, 7 and 3.5 MHz amateur bands. The licence would be valid for 2 years — if you did not upgrade in that time then the licence would be lost for 1 year.

The novice licence has proven extremely popular in the 28 countries that have already introduced one. It

of the hobby as I have known it is in great doubt.

The novice licence has the full support of the RSGB, the G-QRP Club and other respectable bodies. I have also received hundreds of letters of support.

Ian Abel, G3ZHI, Secretary ARNLC


Ian has also provided HRT with a fairly detailed proposal for the licence. The letter contains most of the main points but misses out on perhaps the most fundamental. To obtain this licence, a morse test at 5wpm and a technical examination must be attempted. The examination would cover radio theory, operational theory and licence conditions — at a lower level than the present RAE. The examination would be set by the City and Guilds and the morse test would be "examined by appointed amateurs, such appointments being made by the RSGB or local Radio Interference Officer." The latter sounds OK in theory but the "appointed amateurs" could hardly be expected to provide this service voluntarily...

So, what ARNLC are proposing is basically an additional lower grade of licence, certainly not quite a charter for free-loaders. As far as the Editor is concerned, and he has said this before, the present RAE can be passed by anyone with sufficient interest and application. On the basis that a novice licence should be introduced because the RAE is too difficult, definitely no dice.

However, there is another way of approaching this. Although many of the HF bands are overcrowded, the 28MHz band is very quiet. And who has heard anyone on 18 and 24MHz lately...

How about this ARNLC? — a class 'C' licence offering CW operation at 10W maximum on a 25 KHz of 3.5MHz (the CW end of this band can be pretty quiet) and 50kHz of 28 MHz — and perhaps with equal rights to the present Class A licence on 18 and 24 MHz. The CW test to be administered by the Post Office on a similar basis to the present Class 'A' test and a C&G examination with the emphasis on operational procedure and the prevention of interference.

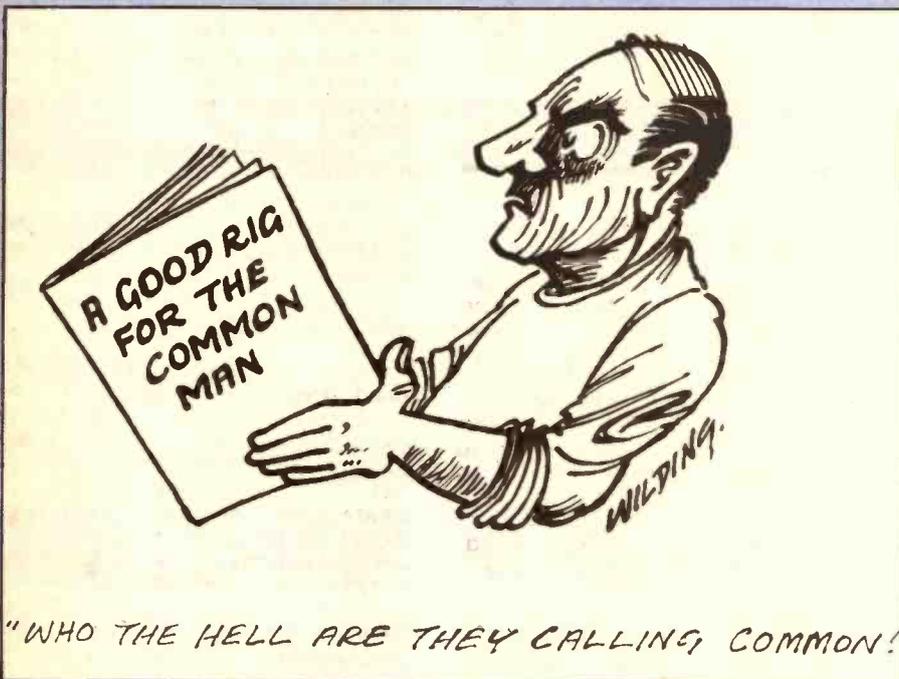I don't think a licence of this kind will decrease "black box" operation much, but it will fill up some underused segments of our allocation and introduce quite a few more people to the delights of



are full of Black Box operators, a lot of whom do not stay, because they have never gotten a true 'feel' for the hobby.

The present route into the hobby from the chaos of CB is unacceptable. Those who think that this route will not in time damage our hobby are not being realistic. The fact is that to attract people into our hobby we must

has brought a lot of people into the hobby who would otherwise not have found it; some of these people have gone on into the field of radio/electronics to become very highly qualified. Can we afford not to give such people an opportunity to discover the hobby? Whilst there are those in amateur radio who show false prejudice then I predict that the future

CW operation. What say you, readers?

PRACTICAL JACK

While it might appal the purist, the choice of MOSFET in Jack Hum's 6m converter seems to me almost ideal.

Having used this MOSFET recently, both in 70MHz IF amplifier design and broadband video, I have interpreted the data sheet into a practically orientated form. Some of this information is here summarised for the interest of constructors.

Transfer admittance 10mA/V
Drain/Source voltage (MAX) 20V
Drain Current (Max) 20mA

A noise figure of typically 0.7dB can be obtained at 100MHz with a source resistance of about 1k Ω in parallel with about 2pF and a gate 2 bias (Vg25) of 4V. (In order to achieve a reasonable gain a high impedance tuned drain load is needed).

Andrew Armstrong, G3YZW

MISCARRIAGE OF JUSTICE

Sir, Warning to all Amateur Radio Operators!!; one believes that this is a pleasant harmless hobby?? but may I suggest that they change to Stamp, Butterfly collecting. It has been said in the past that the easiest way to become a law breaker was just to own a car but, according to the Argus, Thursday, 21 June 84, this isn't so! One ham, of 11 years operating, didn't give out his call sign and forgot

Radio ham fined £100

A radio ham, who 11 years ago was the youngest person to hold an amateur licence, transmitted without using a call-sign or making a log. Brighton magistrates heard today.

Computer consultant, Paul Thomas Russell, 26, of Montpelier Road, Brighton, admitted failing to log a call, failing to notify a change of address, to the licensing authorities, and two offences of not using a proper call-sign, all in breach of conditions of holding a licence.

He was fined £100 with £50 costs. The prosecution was brought by the Home Office, under the 1949 Wireless Telegraphy Act.



"...SO KEEPING IT SHORT, I'LL TURN IT BACK..."

to enter in his Logbook! Bingo, £100 fine and £50 costs. Also in the same paper, clubbing another person with an iron bar (which could have killed?) £75 compensation to the innocent victim (I wonder if he ever gets it?) and the culprit told not to do it again? Sell your rigs, tear up your log books — iron bars are cheaper to buy and use??

Reg Moores, G3GZT/VS6 CD

ABUSE OF RAYNET

Sir, May we, through your letters section, bring to the attention of your readership an issue of vital importance to all Radio Amateurs, and also to the future of Amateur Radio in general.

The issue is the use of Amateur Radio frequencies by the RAYNET organisation for exercises on behalf of County emergency planning officers to do with 'Home Defence'. These exercises, using the two meter and seventy cms bands, seem to be becoming more and more regular, and during these exercises many licence conditions are being broken, and complete disregard for normal Amateur conventions is the rule.

The RSGB refuses to enter into discussion of this matter, many letters have been written to the RSGB council without the courtesy of a reply, and letters to RADCOM have been refused publication. Because of this reaction, this society has been formed, the membership of which includes amateurs of all shades of opinion throughout the British Isles and also in other countries, but united on this issue. The main aim of this Society is:-

to maintain the impartial use of the frequencies allocated to Amateur Radio, by ensuring that they are not used for propaganda purposes, nor for any military, quasi-military, or for any sectarian purposes.

This society is non-political, and is not anti-RAYNET, having many members of RAYNET in its membership. Our main worry is that this use of Amateur Radio frequencies will put in doubt the future of Amateur Radio.

I am enclosing a copy of a leaflet that our members distributed at the RSGB national convention recently. If you or any of your readers would like more information, please contact me at the address below.

Sid Frisby, G4NFF

Sid may be reached at 42 Holsworthy Road, Bowthorpe, NORWICH, Norfolk. Whilst I agree with much in the letter, I was disturbed by a paragraph in the SPARS manifesto, distributed at the NEC, which read "To monitor the amateur radio frequencies so as to detect any further abuse, and to advise operators of their obligations as to their conduct whilst using amateur radio frequencies, in order to establish behaviour which is acceptable to all other amateur radio operators on a legal, social, and moral basis."

This rather smacks of Mary Whitehouse and Big Brother — in direct contradiction to the concerned liberalism of much of the manifesto.

Please address correspondence to:
Ham Radio Today,
1, Golden Square,
LONDON W1R 3AB

RADIO TODAY

Ham Radio Today — The Movie!

The last time Amateur Radio was dramatised for TV was Tony Hancock's hilarious but rather quaint 'The Radio Ham'. News recently reached the HRT office of a new and promising play about our hobby. 'CQ', a new play by 'Driving Ambition' author Paula Milne, has just completed shooting at Limehouse Studios. This has been produced for Limehouse Productions and Channel 4 by Susi Hush and directed by Moira Armstrong.

The play is the story of Norman, an amateur radio enthusiast who becomes the 'voice' of a round-the-world yachtsman and wins local fame on radio and TV with his daily bulletins of the lone sailor's progress — until a sudden loss of radio contact with the yachtsman threatens his new-found celebrity status.

Meticulous attention has reportedly been paid throughout the production to the modus operandi of the amateur radio world. Equipment for Norman's shack was obtained from Amcomm Services Ltd of Harrow and the various books and wall charts from the RSGB. Peter would like to thank both of these for their great helpfulness.

All the individual call-signs featured during the play are genuine, although currently unused. The production had a technical advisor, Peter Marcham, G3YXZ, who ensured authenticity in the radio conversations, and also advised on the correct equipment for Norman's radio shack. This includes a transmitting aerial attached to the roof of Norman's house which, in exterior shots, is shown nestling among the chimney pots and television aeriels. HRT readers, particularly those who dwell in cities, may cast envious and even disbelieving eyes on the possibility of a 5 element yagi from a semi-detached suburban. Well, this is actually part of the plot...

That being said, the street, Norman's house and the aerial-filled skyline are actually miniatures specially built for the production by Richard Henry, a former BBC senior designer who now concentrates on his hobby of model making.

'CQ' stars Michael Elphick as Norman, the insurance loss adjuster by day, whose prowess across the airwaves earns him the renewed respect and admiration of family and friends, and Michael Graham-Cox is Alec, the nautical wayfarer whose erratic exploits make such a profound difference to Norman's life. The cast also includes Marjorie Yates as Norman's wife, June and newscaster Gordon Honeycombe



Michael Elphick in the radio shack, specially built at Limehouse Studios for the production of Paula Milne's 'CQ'

as a television presenter.

Full details of the screening date are not presently available but it is hoped that the play will be shown around mid-October in a fairly 'prime' evening slot. Watch this space for more information...

Scottish Amateur Radio Convention

This year's Scottish Amateur Radio Convention, to be held in Glasgow on Saturday, 8 September, should be an even bigger event than last year's 'record-breaker' at the same venue according to the organisers.

More traders have been attracted to exhibit this time than have appeared at any previous show north of the Border, a larger amount of various aspects of the hobby has been arranged and new record attendances are expected.

The RSGB will have an information stand with books and there will be the traditional large bring-and-buy sale.

The organisers, from the West of Scotland Amateur Radio Society, have arranged a programme of lectures including: "Amateur radio — an alternative approach" by Rev. George Dobbs, G3RJV, of QRP fame, "Modern Developments in Electronics" by Chris Bartram, G4DGU, of Mutek Ltd., and "An EME DXpedition to Andorra" by the HADRABS contest group.


The convention takes place in Cardonald College which apparently proved an "ideal location" when it was used for the first time last year. It is situated just a short distance from the M8 which affords easy access from most parts of Scotland and the south. Facilities include extensive car parks within the college grounds, bar, restaurant and facilities for snacks.

A demonstration HF station will be on the air all day and, on VHF and UHF, talk-in will be provided on S22 and the GL repeater on RB14. The convention will be open from 11 am till 5 pm and admission is £1.

Attention Omega Builders!

Doubtless most of you will be aware that there have been some problems raised in the development of the QRO PA module for Omega. We have made some progress towards their solution. This is the latest position.

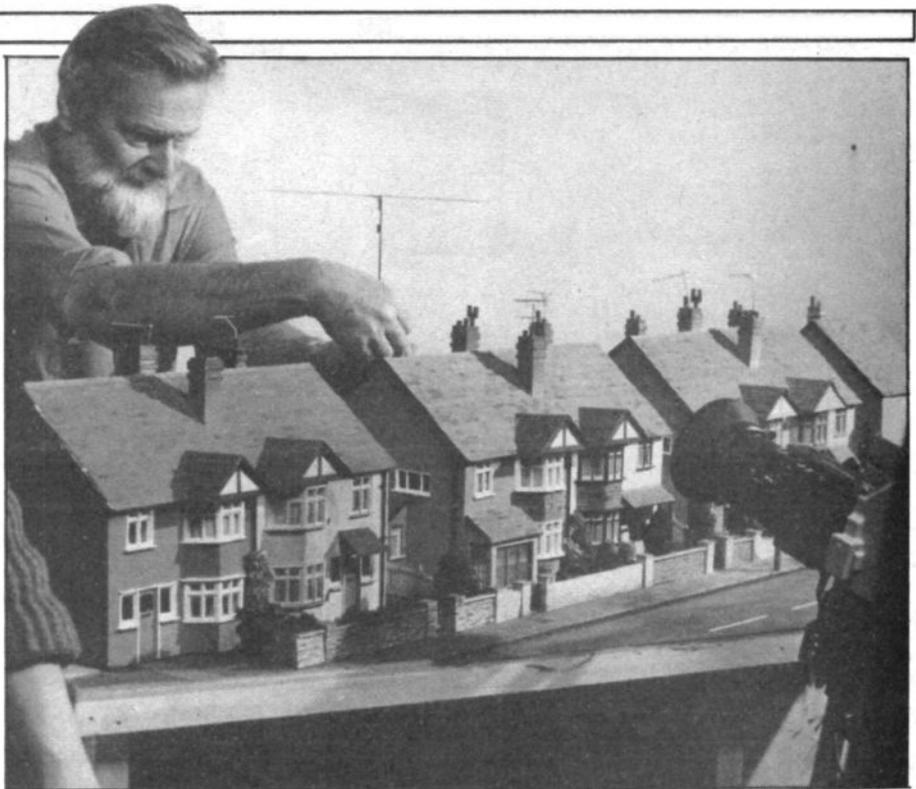We have produced an initial development unit using TRW PT9784 devices. Driven from the existing QRP PA, it delivers around 120W on the lower bands falling to 80W on 10m.



Designer Richard Henry makes the final adjustments to Norman's radio mast (in miniature form — an XYL's dream!)

This indicates a gain of around 12dB, some 4dB below that quoted by TRW, the manufacturer of the output devices.

Although the unit is electrically robust, the gain falls rather short of the 100W+ to be expected from these top quality devices when driven from the 3W PEP available from the QRP PA module. According to data supplied by TRW, the 1.5:1 or better VSWR matching presented by the development module using a circuit originally produced by that company should result in a saturated power output of more than 150W on all bands. The performance which we have recorded in practice runs considerably short of the TRW test circuit.

Having scratched our heads to the point where the hair is falling out, we have given the problem to TRW's R&D labs in Bordeaux, France. They are being exceptionally co-operative and we expect an answer shortly. Be assured that we will pass on the good news just as soon as we have it.

During development tests with the solid state changeover board we have noticed that the BF259 transistor can go outside its voltage rating when run with raw RF at the 120W level. This was not picked up on earlier development because, although it passed its qualifying tests to 250W, we were not using the output of a broadband amplifier with its attendant high harmonic overvoltage. Changing the transistor to type BUX87 should allow an adequate safety margin.


We are doing everything possible to expedite development of the recalcitrant PA and that, when we are

ready to publish the design, it will have the excellent performance characteristics of the rest of the Omega project. G4JST/G3WPO

ATU Kits From TAU

Tau Systems have recently marketed two new types of HF ATU — in kit form. The unique feature of the ATUs are the wide spaced 'transmitting type' capacitors and 'roller coaster' tuning coils used — until Tau came on the scene these had become practically unobtainable as 'new' components. Many is the desperate amateur I have observed, raking over piles of junk at a mobile rally and muttering 'split stator' and 'roller coaster' under his breath! Both the roller coaster, and various of split and single stator wide spaced capacitors are obtainable as individual components from Tau. Tau will also supply non-standard value capacitors to order — although these will naturally cost extra. The power ratings of the capacitors is either 1kW or 5kW PEP.

Coming back to the ATUs, the first of these is their 'Super Transmatch ATU with split-stator capacitor, roller coaster and single stator capacitor which handle impedance transformation ratios of at least 10:1 and is suitable as it stands for un-balanced aërials such as long wires and vertical antennas fed against ground. With the addition of an optional ferrite balun (a number are available for a selection of transformation ratios and rated at a

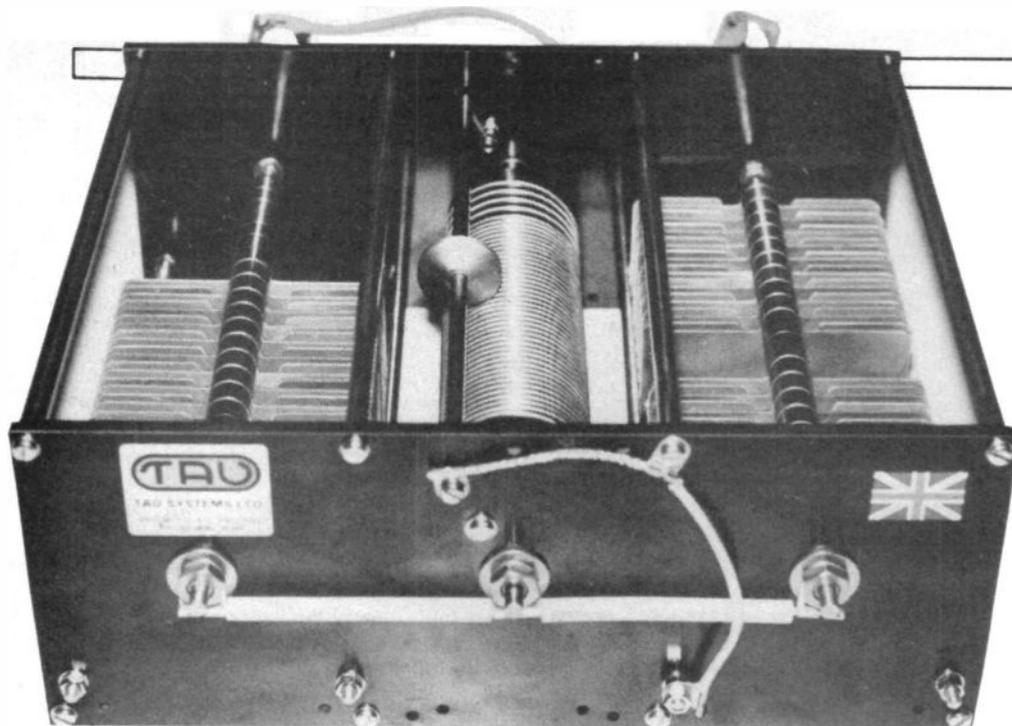

Do-It-Yourself rollercoasters and capacitors included in the Tau System's ATU kit

variety of RF powers) balanced antennas such as dipoles, yagis etc may be used with the ATU. The design is based upon the classic "Super Transmatch" from the American ARRL handbook.

The second is their "L and C match" ATU, a slightly simpler device than the aforesaid but which Tau claim can handle impedances from 5 ohms to 5000 ohms resistive and 2000 ohms capacitive to 2000 ohms inductive. The ATU is based on an old Marconi design and according to ebullient Tony Johnston, G40GP, Tau's Technical Director, should operate at the high impedance levels with no fear of flashover. Having seen the quality of the Tau components, in particular the insulation and wide spacing of the capacitors, at close quarters, the Editor is inclined to agree with him.

Tony, a keen 160m operator with quite a few countries to his credit, recently made a whirlwind visit to the HRT offices to show off the Super Transmatch and Tau components. The



Tony Johnston, G40GP, in the shack

Tau philosophy is very much that British Engineering is the best in the world — amply supported by the gear in Tony's shack which is 80% UK made.

In addition to the ATUs and ATU components, Tau also manufacture a very tough clip-on spacer for open wire feeder. Enough of these for 18m of open wire feeder are included in the Tau "Aerial Kit", along with dipole centre and end insulators, which retails at £12.70.

The Super Transmatch kit is available in two variants — the 1kW version is £160 and the 5kW is £185. These can be ordered direct from Tau (0695 24662) or can be obtained from SMC or Amateur Electronics (UK). According to Tony, distribution is being currently negotiated with other UK and overseas dealers.

So You Want To Study The Radio Amateurs Examination?

Loughborough Technical College are holding a RAE course in the Department of Electrical Engineering and Computing at Radmoor, Loughborough, Leics on Tuesday evenings, commencing on the 11th September for 26 weeks. Morse code is studied from 6-7pm and Radio Theory and Licence Conditions from 7-9pm. The tutor is Doug Doughty, G3FLS, and the fees are £7.30 for the Morse and £15.90 for the theory. For further information, telephone 0509 215831.

Dacorum College at The Marlowes, Hemel Hempstead are holding an RAE course on Wednesday evening from

6.30-9pm (and Mondays 6.30-9pm if there is sufficient demand) commencing 26th September. Enrolment is on 10th September and course tutor is CB Burke BSc., G3VOZ. For further information, please ring 0442 63771.

Bradford and Ilkley Community College are holding a very interesting course in Amateur Radio, commencing in September 1984. The syllabus is 1st year, preparation for the City and Guilds RAE; 2nd year, optional — this is also available for existing Class 'B' licencees who wish to obtain an 'A' licence; 2nd/3rd year, a project based course for holders of the RAE certificate who wish to gain more in-depth knowledge of amateur radio topics. The courses are being run by the Department of Electrical and Electronic Engineering and the tutor is P. Nurse. Enrolment commences on 11th September.

Beckenham Adult Education Centre are holding a Beginners Morse Class commencing in September. Enrolment is either by post during the period 28th-30th August to Bromley Adult Education Service, Aylesbury Road, Bromley, or in person at 28 Beckenham Road, Beckenham, Kent (01-650-4208). The tutor is Fred Henschel and students are encouraged to reach 12wpm by the end of the course in May.

Walsall College of Technology are holding a course leading the RAE. Enrolment is on the 4th, 6th and 10th September. For further details ring Aldridge 52706.

During the session 1984/85 the Langley College of Further Education in Langley, Slough, Bucks, will again be offering classes for the Radio Amateurs' examination. The course follows a modular scheme.

- | | | |
|--------------|-----------|--|
| 1. Thursday | 1730-1900 | Operating Techniques
(on the air operation) |
| 2. Thursday | 1900-2020 | Morse |
| 3. Wednesday | 1900-2100 | Theory |

Students can choose modules to make an individual programme. The College has a fully equipped station (G3XPL). In addition, the College hopes to offer short courses (8 weeks) on such topics as "Use of Test Equipment by Radio Amateurs". Enrolment will be at the college on either of the following dates: Tuesday 11th September 1984 from 12 to 8 pm or Wednesday 12th September from 12.30 to 8 pm.

For any further information please contact Mr. A J Parcell, (G8BIX), the course tutor at the Department of Technology on 0753 49222.

Hendon College in North West London will be offering a course for the Radio Amateurs Exam, starting in September 1984. They have been running the course for the past three years, with excellent results. The tutor will be

Tony Essex, G8WCX, and the course is held in the Williams Building, Hendon College of Further Education, The Burroughs, London NW4 4BI. Classes run from 7-15 to 9-15 on Tuesday evenings. Enrolment is on 12th September from 2-8 pm.

The RAE courses at **Paddington College in West London** are claimed to be something special! Not only do they cover the syllabus for the City & Guilds RAE exam, but also make use of the facilities provided by the Electrical Engineering Department, allowing students to carry out practical experiments in the electronic theory covered by the course. The course is none the less pitched at the student with no previous experience of radio or electronics. Paddington College also has an active club station (G4UWU) operated by the course tutors and past students.

Because of the extended scope of the course, attendance is required twice a week during term time between the end of September and the examination in May (30 weeks). Inevitably, this means the course fees are slightly higher than those charged by some colleges (special rates are available for pensioners, those at school fulltime, and the unemployed, residing within the ILEA area). However, over the past few years they have maintained a pass rate better than 90%.

Enrolments are on the 10th, 11th and 12th September between 1-4 pm and 6-8 pm in the evenings at Paddington College, Paddington Green, London W2 1NB. If these times are inconvenient, just turn up on the night. Course tutors are: David Peace, G4KKN, and David Hunt, G6MFR. For further information contact David Peace on 01-402 6221 Ex. 54.

Arnold College of Further Education in Mapperly, Nottingham are offering a very comprehensive range of classes in Amateur Radio.

For those wishing to take the RAE there are two options: full courses, for the May examination, are on Wednesdays at 7pm and commence on 19th September, whilst there is a 'crash course' on Thursdays at 6.30 p.m., commencing on 20th September, for the December examination. Both these courses are suitable for those with a basic knowledge of electronics.

In addition to the above, the college offers construction classes, a course entitled 'After the RAE', for licenced amateurs who wish to take their technical knowledge a stage further, and a course called 'Introduction to Amateur Radio', commencing June '85, for those who wish to find out what they are letting themselves in for when they take up the hobby.


Further details of the above are

available from R G Wilson in the General Studies department (0602 876503).

HRT will be pleased to accept details from colleges and adult education centres of RAE courses for publication in the next issue of the magazine.

The "Third Hand"

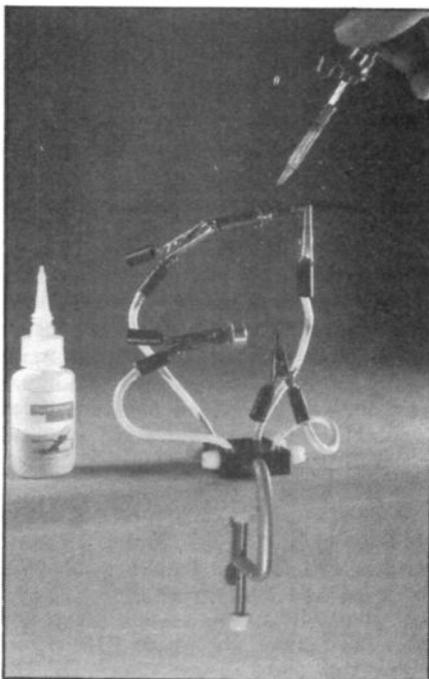Few DIY jobs are more frustrating than the one that needs "three hands" — two to hold the work and a third to apply solder or adhesive. The smaller the component, the more difficult it usually proves to position it accurately and firmly.



Angle of application — no problem with this Gripmate

Gripmate, produced by an innovative Sussex company, is one of those "Why-didn't-somebody-think-of-it-before?" inventions — a tiny clamp that provides not just one extra 'hand' but four, able to grip small electronic components and similar items in an infinite number of positions.

A base block clamped to any bench or table top carries four semi-rigid wires, each fitted with a crocodile clip to hold the work. Alternatively, any of the wires can be replaced with one holding either a magnifying glass for close-up work, or a magnet where this is more appropriate than the clip.

Gripmate is only only rather clever but inexpensive. The four-handed model costs £4.85 (a basic type with two arms sells for £1.00 less), and the magnifier and magnet come for £2.50 and £1.50 respectively — all inclusive of VAT and postage, direct from Kemplant Ltd. Durfold Wood, Plaistow, Billingham, W. Sussex RH14 0PN.

New Club For The Midlands

The inaugural meeting of the Welland Valley Amateur Radio Society took place on Tuesday June 5th at Welland Park College.

18 radio amateurs and future 'hams' met to set up this new radio society which it is hoped will attract more members from both Leicestershire and Northamptonshire. The aim of the society is to encourage and develop amateur radio in an area which up till now has not had a local group. During the evening the club radio station, G4WVR, was in operation the first contact was with VU2AU in Nagpur, India.

The society is to meet in future on Mondays at 7.15 at the college and it is intended to make the first meeting of each month a special meeting with perhaps a guest speaker, a demonstration or visit to a place of technical interest. Alan Faint, G46TZY, (Market Harborough. 62827) was elected chairman and Dave Lunn, G3LSL, (M.H.880746) was elected secretary.

Licensed and prospective amateurs are cordially invited to join the society and should either contact Alan or Dave, or just turn up at a meeting.

9L1FTN — New 28 MHz Beacon

By Roger Frisby, G4OAA of the Cheshunt DARS

Well, we made it — 9L1FTN came on the air on the last day of the Region 1 Conference in Cefalu. It was touch and go to the last. Wally Hood of the Colston Case Co (Goff's Oak) agreed to pack the beacon and waive his freight forwarding charges and it finally arrived at Lungi Airport, Sierra Leone on Monday 9th April. Unfortunately so did Sierra Leone's President Stevens returning from a visit to London. Confusion at the airport meant that Vidal, 9L8K, was not notified until Tuesday and the documentation went somewhat awry. Vidal obviously had some problems in clearing customs as I received the following telex dated Thursday 12th April: "Beacon collected 1700Z yesterday from Lungi. Jumped several guns swinging sledgehammer to collect. Thanks all CDARC members and others for knightly effort. Beacon is really grand. Installation commences now." I sent a message to Cassandra 9L1YL and to Dr. John Allaway G3FKM in Cefalu resulting in an announcement. I have heard since that this went down well as help and co-operation with third world groups was a major talking point at the conference.

Friday the 13th was a lucky date for us. Just after I arrived home from

work at 6.15 pm, Dennis G3TIK phoned to say that 9L1FTN was on the air — the phone didn't stop ringing that evening! Speaking to Vidal on the air I learned that because of a fault, the shack mains supply had been disconnected for the first few days of operation and that he had been taking a fresh car battery up every morning. It's quite a difficult journey up to the shack from the town, and it's all credit to Vidal for his efforts. He also told me that he was only measuring an output of 1.5 watts. Whether a fault exists or this is because of Vidal's unfamiliarity with the equipment's adjustment I don't know, but with 1.5 watts to a dipole, the beacon has been audible here for several hours each day, on most days, since switch on. The earliest I have heard it has been 11.30 GMT and the latest 20.55 GMT. In early May, peak signals are occurring around 18.30 GMT.


For HRTs overseas readers, here are a few technical details of 9L1FTN: Frequency — 28.27250 MHz (keying to 28.273350 MHz)
Location — Kortright, Mount Aureol, Freetown; 08° 30N, 13° 20W
ASL — 400 metres
Antenna — Vertical half wave
Power — 10 watts to antenna
Supplies — 240 volts AC or 12 volts DC with auto-changeover
Keying — FIA "de 9L1FTN" at 12wpm with 20 second interval. When running on standby supply, up to eight dits are sent before the callsign, depending on the state of battery charge. (This item courtesy of the Cheshunt District Amateur Radio Society)



Roger Frisby, G4OAA, with the 9L1FTN 10 metre beacon

New Miniature Low Voltage Soldering Irons

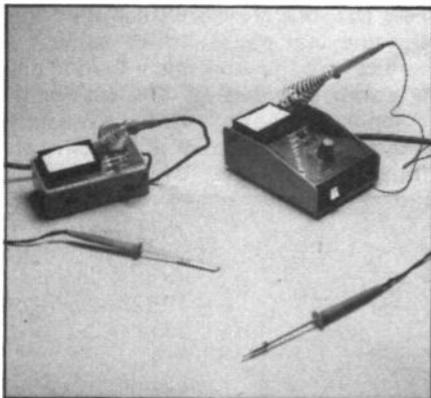A series of miniature low voltage soldering irons, the Oryx Micro Series, has been introduced by Greenwood Electronics, the Reading-based electronics production equipment specialists.



The Oryx 'Micro' soldering irons

These professional irons, the smallest in the Greenwood 'Oryx' range, have been designed for intricate circuit work. They provide maximum heat in a concentrated area and offer typical tip temperatures of around 320°C. Typical unit weight is *only 4 grams*, though.

The Oryx Micro soldering iron range includes, 5,6,9,11,12,18 and 25 watt models and operating voltages include 6,12,24 and 50 volts.

A power supply station stand and cleaning facility, the Micro P66, offers 115/240 VAC mains operating and delivers a safety isolated output for the 6V, 6W Micro iron. A more elaborate version, the Micro PT66 variable temperature unit is also available. With this unit the tip temperature of the iron can be controlled between 120°C and 400°C via control knob on the base stand. Information can be obtained from: Greenwood Electronics, Portman Road, Reading, Berks. RG3 1NE. Tel: 0734 595844.

If Junk Sales Were All Like This...

The second Junk Sale 'Extravaganza' held in early Spring by the Cambridgeshire Repeater Group was an unqualified success with an attendance of over 400. Amidst comfortable seating and pot plants bidding was quick and fast for the 528 lots for sale ranging

from complete HF stations to bags of components. Security patrolled car parking was provided adjacent to the large hall, and tea, coffee, and biscuits were available as well as a licenced bar on site, (which had only six pints left in the barrel at the end of the day!); several radio traders attended to those who wished to buy new equipment, and a vintage wireless stand and GB3PT RTTY demonstration station (both with operational gear) attracted much interest.

The most commonly-asked question on the air after the event was, of course, "when's the next one?". In view of the enormous success, next year the organizer will be extending the event into a 'Mini rally' to provide even more for everyone. See you there? Contact man — Chris, G4HCL.

Circuit Steps Up Business In Toko Components

The renewal today, of an exclusive United Kingdom distribution agreement between Toko Incorporated, who are the world's largest manufacturer of wound components, and Cirket Holdings PLC, marks the beginning of the two companies' second decade of association.

The original agreement, signed in 1974, with Ambit International, one of the principal founding members of the Cirket Holdings group, made them the first franchised Toko distributor in the UK, and since this time the number of products stocked has grown steadily.

In addition to being the sole UK stockist of Toko coils, Cirket holds a comprehensive inventory of their other components including filters of all types, fixed inductors, bi-polar ICs, numerically controlled LSI, Vari-cap diodes and push button switches. Most recent addition to the Cirket range of Toko products is helical filters.

Commenting on the renewal of the Toko franchise, Cirket's chief executive, Christopher Sawyer said, "Perfected over some 30 years of development, Toko's miniature transformers are now produced in quantities of more than 100 million units per month and are used in virtually every radio and television set, hi-fi and communications system produced around the world.

Ken Michaelson, G3RDG, has asked us to convey his apologies to Ian Wade, G3NRW, and Peter Martinez, G3PLX, for the omission of acknowledgements to them for the use of certain subject matter which was used in his article entitled 'A Guide to AMTOR in the June issue of HRT.'

Reg G2BSW **REG WARD & CO LTD** Rodney G6LUJ
 1, Western Parade, Axminster, Devon.
 Tel: (0297) 34918

The South West's largest amateur stockist
 Complete range of Yaesu and Icom equipment available from stock plus
 demonstration facilities.

Now official TRIO agents.

Ancillary equipment by Microwave Modules, Datong, Drae, Mutek, BNOS,
 Welz, Tokyo Hypower, Hansen, Himound, Shure, LAR, Tono and Toyo.

Aerials by Jaybeam, TET, Hygain, G-Whip and Minibeam.

NOW AVAILABLE - FDK AND AZDEN.

Plus connectors, dummy loads, rotators, cable, etc.

ACCESS - Instant Credit - BARCLAYCARD

Open: Mon., Tues., Thurs., Fri. 9-5.30. Wed. 9-1.00. Sat. 9-5.



ICOM



TALK TO THE WHOLE WORLD

Study now for the
**RADIO AMATEUR'S
 EXAMINATION**

We have had 40 years successful experience
 in training men and women for the
 G.P.O. Transmitting licence.



FREE R.A.E. brochure without obligation from:-

British National Radio & Electronics School
 READING, BERKS. RG1 1BR

Name

Address

HRT/9/846

BLOCK CAPS PLEASE

CHOICE OF PROFESSIONALS TOWERS, MASTS, AERIALS AQ6-20 Four Band **Spacesaver** Beam

6M-20M

Also 3 ELE

Not the same
as other lookalikes!!
Spot the differences!!

- * Unique fully sealed coils for max stability
- * Double insulated elements
- * Easy trim alloy spokes with locknuts (spares incl)
- * Only 1.9M turning radius
- * Engineered to BSI Standards

- * Resonant length reflector and driven elements for improved VSWR (1:1 min)
- * Maximized F/B performance by selective detuning (No gimmick "quad" needed)
- * Minimized wind load and weight (only 8lb wt)

**IT'S BRITISH!
 ECONOMICALLY PRICED!**

£114.50 (UK P&P £4.50)

Send SAE (9 x 6) for full details of these and many
 other Altron Products - Callers welcome. Open
 Mon-Fri 9am-5pm. Sat 9am-12.45pm
 WE DESIGN - WE MAKE - WE SUPPLY DIRECT
 YOU GET BEST VALUE AND SERVICE - SAVE £££'s
 Prices include VAT. C.W.O.
 THE ONLY MANUFACTURERS OF ALTRON PRODUCTS
ALLWELD ENGINEERING
 UNIT 6, 232 SELSDON ROAD
 SOUTH CROYDON, SURREY CR2 6PL
 Telephone:
 01-680 2996 (24hr)
 01-681 6734
 Normally despatched within 7 days

HAM RADIO TODAY

NEXT MONTH

TEQUILA AND TRI-BANDERS -
 radio Mexican style!

Introducing **MICRO NET** - the
 bi-monthly forum for radio
 amateurs with a computer
 in the shack.

THE ALPHA TRANSCEIVER -
 Constructional details!!!

PLUS

A synthesised VFO for 2m transceivers.
 By G3WPO and suitable for our
 'Talkbox' design.

WRITE FOR HAM RADIO TODAY!

We are always looking for new contributors to the magazine and we pay a competitive page rate. If you have built a project or you have some experience that you would like to pass on, or if you have a particular point of view that you would like to get across to others, drop us a line and describe what it is you'd like to write about. We'll get back to you to tell you if we're interested and to tell you all the boring details. Don't forget to tell us your address and telephone number (preferably a day-time telephone number too).

The ALPHA Transceiver

Everybody knows about the joys of mobiling on two metres; the ubiquitous black box has added a completely new dimension to our hob-

station equipment tends to be distracting and complicated to use whilst driving. We both saw the answer to all this as a high perfor-

about six feet, they also tend to have a narrow bandwidth. Restricting operation to a single band enables greater radiation efficiency to be obtained — which means more chance of an interesting contact!

Here is a project for an HF SSB/CW transceiver which is capable of operation on any single band from 160-20m and can hold its own against the latest commercial rigs. Design by Frank Ogden, G4JST, and Tony Bailey, G3WPO.

Our Alpha transceiver is essentially a single band design, but the alteration of just a few cheap components will customise the set for operation on any band from 160 to 20 m, including the new 30 m sector (although you can't, of course use SSB on this band). If you get fed up with, say, 160m, simply replace a crystal, six toroids and a few small capacitors and you will be set up for 20 m or whatever. **This article will give details for 160 and 20 m only — requests for the mods to get it on the other bands will be treated sympathetically providing there is a demand!**

by. Regrettably only a few of us so far have discovered the even greater joys of taking an HF black box into the car. Chatting through the local repeater does take the tedium out of a long journey, but holding a QSO with a station in Australia while driving through the middle of London is even better!

Tony and I felt that the greatest drawback to HF mobiling was the complexity and cost of existing equipment. Nobody in their right mind leaves a brand new FT757 invitingly under the dash. Equally it is a real bore to have to pull out gear from the car everytime one wishes to use it in the shack. Also, base


mance, minimum knob-count purpose designed transceiver.

A Single Band

The biggest design decision was to restrict operation to a single band. Band switching is a major hurdle when the object of the exercise is to keep cost and complexity to a minimum. Some people may regard this as a major limitation, but in reality this is not so. Mobile aerials tend to be difficult to manufacture in multiband form while retaining a reasonable degree of performance. Because it is not practical to make them longer than

The Specification

Alpha uses a synthesised VFO, and a high level Schottky ring mixer feeding into a high performance

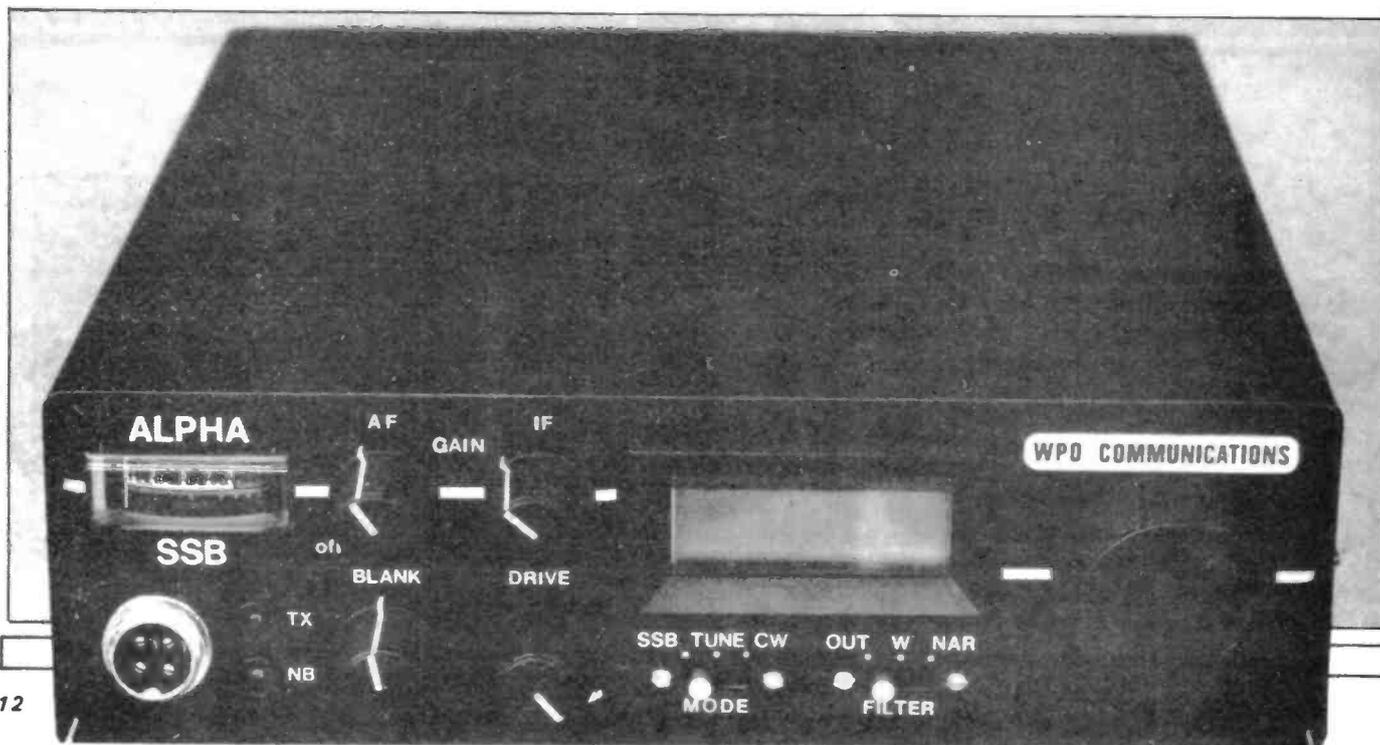

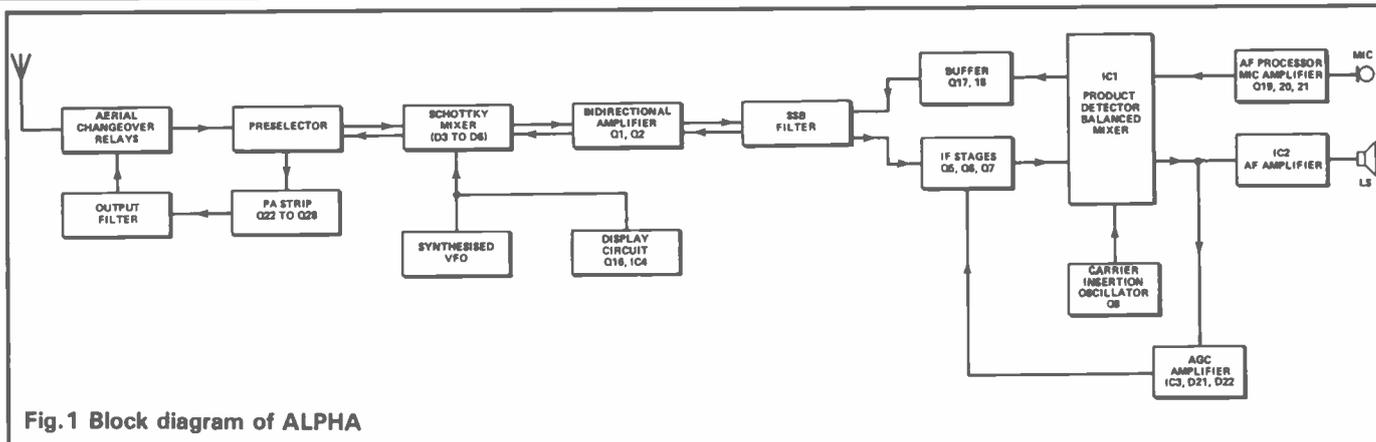


Fig.1 Block diagram of ALPHA

8-pole 10.7 MHz IF to create a receiver system guaranteed to give 90 dB+ of dynamic range (two frequencies spaced 100 kHz apart in-band against the equivalent input for a minimum discernible signal). For a full description of our measurement procedure, please refer to page 113 of the ARRL *Solid State Design For the Radio Amateur*. This performance puts Alpha among some of the best performers available anywhere. We have backed this with a full RF sidechain type noise blanker to reduce the inevitable car ignition noise to acceptable proportions. This same facility also reduces the Woodpecker from, typically, S9 +20 dB to around the S3 level.

In transmit, Alpha puts out a minimum of 50 W PEP from a 13.8 V supply; more than enough power to receive European 5 +9 reports using a centre-loaded bumper mount quarter wave aerial on daytime 20 m working, or to work the World from home. An in-built speech processor (permanently wired into the microphone circuit) effectively boosts talk power by over 12 dB typically. The push-pull transmission line MOSFET output stage is 'unburstable' as Tony and I have proved many times during development. We can honestly (cross our hearts) say that we have not lost a single output transistor in spite of the horrible things which we have unintentionally done to our new little baby.

Reports

I can't really (well, I hope I can!) expect the critical readers of *Ham Radio Today* to believe the outstandingly good reports we have received when using the set both mobile and connected to a quad loop

antenna at home. However every word is true. The transmit audio, even accepting that it is fed through the on-board processor, is as clean as any commercial set on the market, we are told. The ultimate test is when people tell you that "your modulation is very good" without knowing that you built the rig yourself.

The punch of the signal carries well through the QRM. Sunday morning a couple of months ago saw G4JST sitting in his car outside his garage playing about with the new toy. I tuned in idly to an N1 station calling CQ from New York. His signal was only around S3 so I went back to him not expecting a reply. I nearly fell out of the car when he came back to me — the US station was running 1 kW PEP output but we managed a reasonable two-way QSO in spite of European interference.

Circuit Description

Receive

The signal from the aerial socket is routed from the changeover relays (activated by the PTT switch on the microphone) to the preselector bandpass circuit L1, L2. Diodes D1 & 2 offer protection to the easily damaged Schottky mixer diodes in the event of RF leakage from the changeover relays. After filtering, the signal passes via T1 to the Schottky diode ring, D3 to 6, through matching transformer T2 to the dual gate MOSFET bi-directional amplifier Q1, Q2. This circuit uses DC switching to take one of the transistors essentially out of circuit — Q2 in receive and Q1 in the transmit mode. Transistors Q3 and Q4 perform the DC switching. Note that delayed AGC is applied to gate 2

of Q1 during receive. More about the AGC action later.

Please note that those components indicated by an asterisk on the main circuit diagram are chosen according to band. The drawing shows the values for operation on 20 m. Detailed changes are given in the components list and in the constructional details for 160 m.

A PIN diode D8, together with its associated transformers, cuts off the signal path to the crystal filter F1 during heavy interference spikes. Switching action for the diode is provided by JFET Q13. This transistor, normally on, cuts off when the noise blanker sidechain Q15, Q14 amplifies a signal derived before the crystal filter to the point where the rectified DC interference pulse, generated by D25, D26 is sufficiently big to cut off Q13. This same pulse is also applied to Q10 which acts as an audio switch. Note that the impulse blanker will only operate effectively when the interference pulse is substantially greater than the wanted signal. Front panel control VR2 sets the gain of the noise blanker sidechain.

Matching to the crystal filter is controlled by R6, IFT2, T9 and R13. If a unit other than that quoted in the parts list is used, then these components will require modification (as will the PCB). The characteristic impedance of the filter is 600 ohms.

SSB amplified by the three-stage IF amplifier at 10.7 MHz is fed to the product detector/transmit balanced mixer IC1 (KB4412). AGC generated by level detector (D19,20) AGC amplifier IC3 and rectifier D21,22 is applied to the first two IF stages via voltage follower Q11. Q12 is an additional current follower for driving the S

meter. AGC hang characteristics are defined by C46, R48, with preset resistor RV1 setting up the log-law IF gain stage Q6. This should be adjusted so that the voltage drop across R17 is around 0.5 V at no signal.

'S' Meter

The diode chain D10 to D17, together with resistors R19 to R23, give an approximately (very!) log characteristic to the overall receiver AGC. This results in an 'S' meter response which actually means something. A 15 k resistor for R51 (meter series shunt) together with the 100 uA movement gives an S9 reading for approximately 50 uV input at the aerial socket. The voltage double AGC rectifier configuration enables the AGC line to swing negative with respect to ground — this pro-

duces excellent AGC characteristics for signals in excess of 10 mV input.

The audio stages following the product detector are completely conventional. Q10 is a noise gate driven by the impulse blanker circuitry. Q8 provides the carrier insertion signal for the product detector. It is essential to the successful construction of any highly sensitive SSB set such as Alpha that signals do not find their way into the front end of the IF strip. Such unwanted coupling will result in the powerful AGC characteristic creating all manner of unwanted low frequency oscillations and effects on levelling time. *We strongly recommend the use of our PCB for the construction of this project.*


As the set is intended for SSB primarily, no additional IF filtering has been incorporated for CW use,

but CW facilities have been built in. Additional AF filtering for CW reception has been allowed for, and the multipole active filter used in Project OMEGA can be fitted into the design. Details will be given in Part Two.

Transmit

Signals from a low impedance dynamic microphone are fed through the RFI filter, C61, R78 and C62, to voltage amplifier Q19, 20. Negative feedback controlled by RV9 sets the overall gain. This preset is the mic gain control and is used to establish the amount of processing produced by the circuit Q21, D28 and D29. Intermodulation products introduced by the clipping action of the limiter diodes are taken out by the action of the crystal filter. To obtain effective speech processing with a baseband

Fig.2 Mixer, IF and AF stages of ALPHA

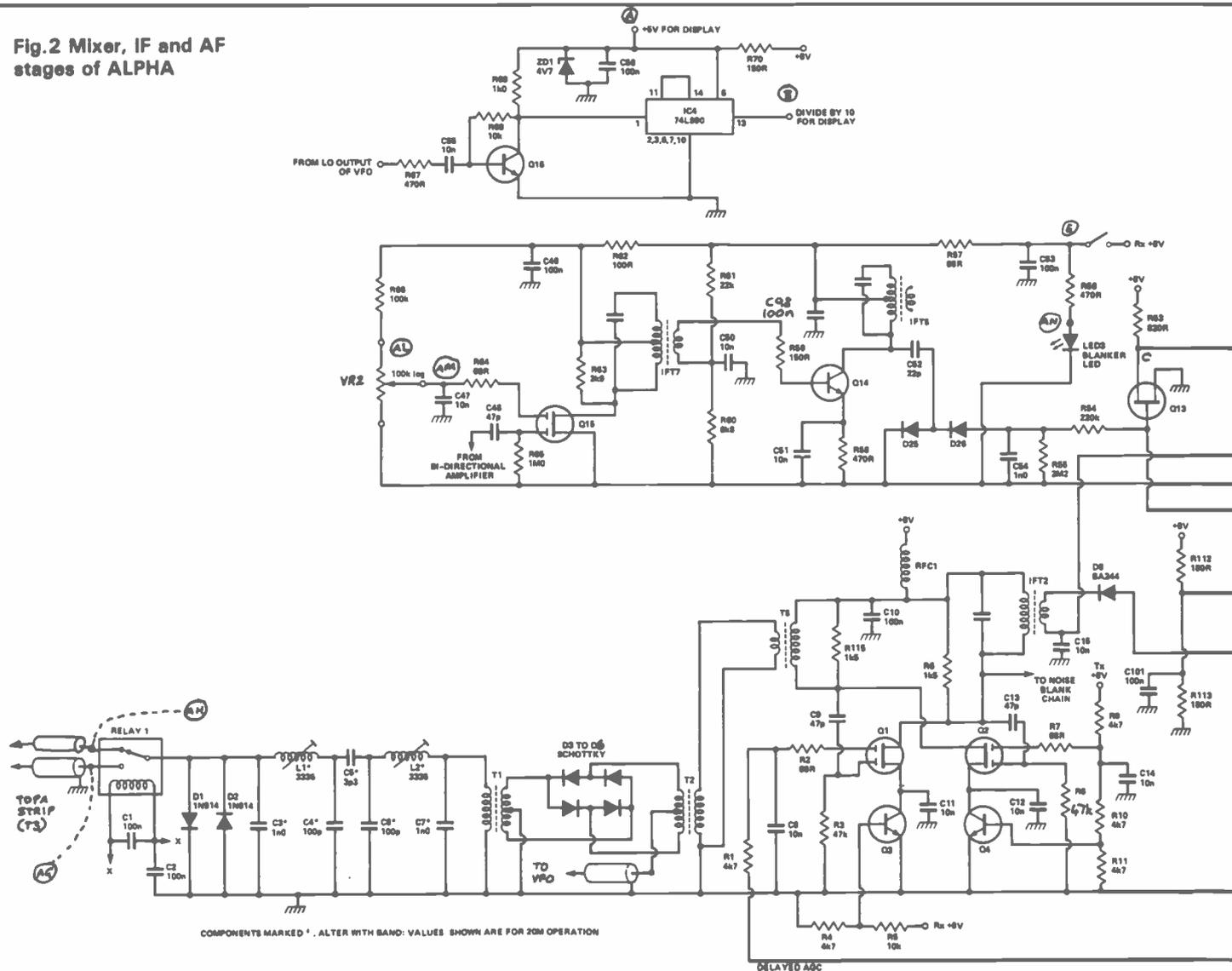

type of circuit, it is essential that frequencies outside the communications speech band are removed before application to the limiter. This filter function is provided by the second order filter ahead of the clipper, Q21. RV3 sets the level of processed audio going to the IC balanced mixer, IC3.


Double sideband taken from the output of this chip is fed through Q17 and Q18 PNP buffer stages to the crystal filter, where the unwanted sideband is stripped off. These transistors provide approximately unity gain in transmit but stop the carrier insertion signal from the sideband oscillator finding its way into the front of the IF strip, as outlined earlier. The resistor network surrounding these two transistors creates reversed biased conditions at their junctions in the receive mode ensuring the highest possible isolation.

From the filter, the SSB signal passes through the bi-directional amplifier picking up gain on the way before entering the power amplifier strip. Relays control this signal routing. MOSFET Q22 has front panel drive control connected to gate 2 to enable variation of transmitter output power anywhere from 2 to 50 W+ (on Top Band you will of course need to set the output power so that it does not exceed the 25 W or so permitted by your Licence!). This control is normally used to back-off the indicated meter output by a division from 'flatout' maximum. When the transmitter is used in this manner no splatter can result — even when shouting into the microphone!

The remaining sectors of the PA strip are all operated in push-pull to reduce the amount of second order harmonic products in the essentially broadband power

stages. Power MOSFET transistors Q25 and Q26 bring the power level up to the 3W level for coupling into the output stage. The value of RFC5 is chosen to resonate with the input capacitance of these devices (about 30 pF gate-to-gate). A balanced output is taken from the bifilar transformer T6 into the power stage matching network.

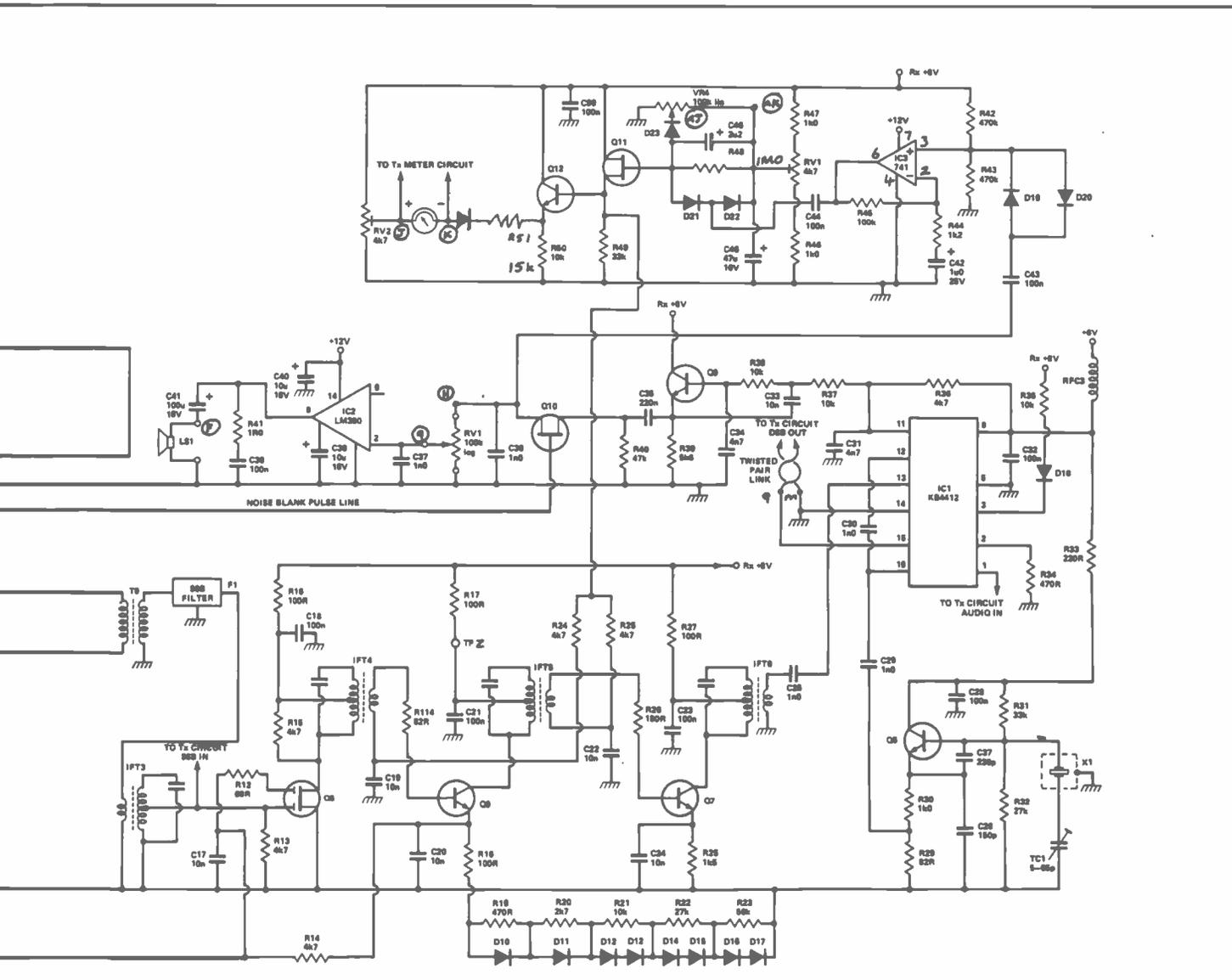Q27 and Q28 are a pair of audio power MOSFETs of the IRF120 variety, matched on both the inputs and outputs by transmission lines. This combination, the subject of a patent application, enables remote fixing of the power transistors (on an aluminium heat-sink integral with the line of the custom case) while eliminating the effect of the package parasitics which make LF packaged MOSFETs unsuitable for use at RF. Essentially modern power



MOSFETs are so fast that the silicon dice which make up the transistor can operate up into the VHF range. However, the long bonding wires and header capacitances 'slugs' the operating speed at full power (or rather slow rate) to the very low MHz region.

Our new matching system gets over the problem. The result is that cheap MOSFETs offer better linearity, robustness and efficiency in RF output stages than any bipolar stage, cost for cost. The only appreciable drawback is that, having a higher input impedance, the broadband characteristics are inferior — about one and a half octaves. In single or dual band operation this is unimportant.

The power gain of the devices shown is around 15 dB at 14 MHz. The input power from the drivers is dissipated in the silicon gate resistance of the output transistor structures.

A simple Pi-section harmonic filter removes the comparatively small amount of rubbish generated by the PA strip. Power output is monitored by a simple diode rectifier arrangement feeding the 100uA meter.

Display

With the availability of the PCIM177 frequency counter at comparatively low prices, it seems futile to go to the considerable mechanical convolutions needed to produce a corded mechanical drive. The display offers a full LCD frequency counter with backlighting in a small package, but in its normal state only allows operation up to 4 MHz maximum. For this application, we want to use it to read the VCO frequency (either 25 or 12.5 MHz depending on band), and subtract the IF frequency of 10.7 MHz to get the actual frequency in use. The PCIM177 allows this internal subtraction (one of a number of preset IF frequencies programmed into it) as well as a programmable decimal point.

By dividing the VCO frequency by 10 in IC4 (after amplification and level shifting in Q16), the VCO frequency is brought into the counters range, and by suitable shifting of the decimal point, will now read the final frequency to a resolution of 1 kHz (ie 1.896 or 14.234 MHz).

The display is mounted directly


on the front panel of the case, and interconnected to the prescaler output via a short length of coaxial cable. The stabilised supply it needs is obtained from the simple zener arrangement of ZD1 on the main PCB.

VFO

The VFO used in ALPHA is nearly identical to that of the MINISYNTH PLL VFO published in the April 1984 issue of *HRT* as a separate design. This has been incorporated onto the same board as the rest of the Transceiver. The only differences are that the CW offset circuit is not used, and an air spaced VFO capacitor has been used to achieve ultimate stability, of the order of 50 Hz per hour when warmed up after a few minutes. The actual VFO drive uses a combination of 6/36:1 and 6:1 drives with the VFO capacitor to provide a very smooth, no backlash tuning action with fast and slow tuning.

The block diagram shows how the VFO works, as some people may be unfamiliar with the PLL design used. A fixed frequency crystal oscillator (Q29, BC239)

Fig.3 Microphone amplifier, driver and PA stages of ALPHA

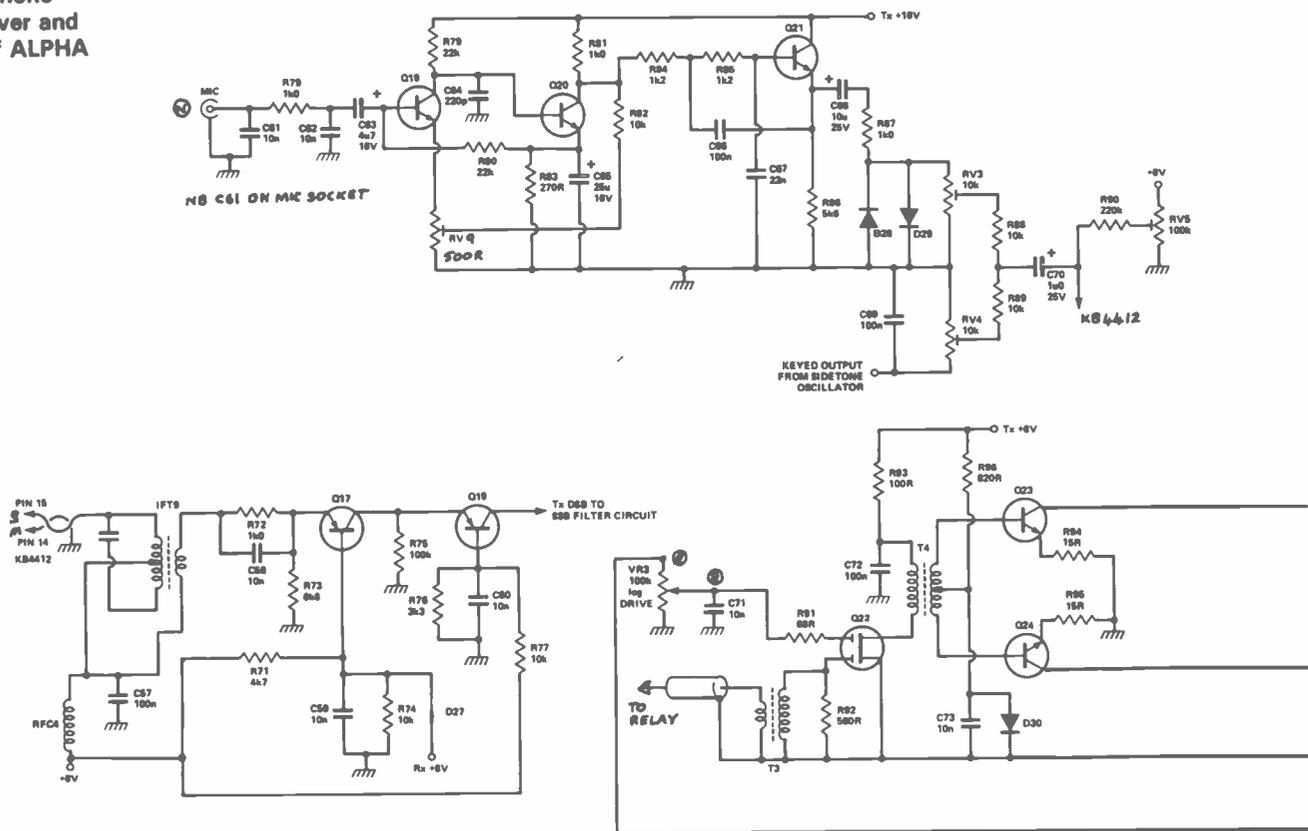

mixes its output with a narrow band VCO (Q32, BC308) tuning only the amateur band required). A buffer transistor Q33 (2SK55) provides a +10 dBm output via T10 suitable for driving the Schottky ring mixer directly. Another portion of the VCO signal, tapped off of L8 mixes in Q31 (BC239) – the loop mixer, to produce a difference frequency between the crystal and the VCO.

This difference signal is filtered out by the low pass circuitry associated with RFC9, amplified by a series of CMOS buffers (IC6a,b & c) configured as an amplifier, and applied to the phase detector (pin 14) of a 4046 phase detector.

This is compared with a reference frequency derived from a free running, but very stable, low frequency LC oscillator configured from a further pair of CMOS buffers (IC6d,e). This output is then fed to the other terminal (pin 3) of the 4046 phase detector.

Any frequency or phase error appears as a DC voltage, after filtering by the loop filter components, at the varicap diode on the input to the VCO. This brings the oscillator back into perfect lock

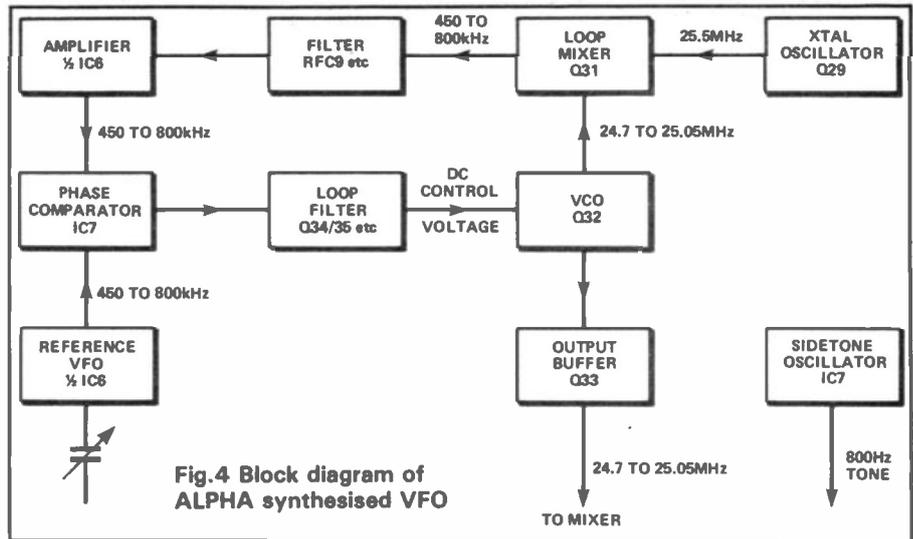


Fig.4 Block diagram of ALPHA synthesised VFO


against the reference VFO. The control loop bandwidth is around 10 kHz, which is quite sufficient to 'clean up' the VCO output spectrum over the few critical kilohertz either side of the output frequency (there are some slight changes to the loop filter values against the original design).

Frequencies

For 160 m, which needs a 12.5-12.7 MHz VCO signal, the

crystal oscillator uses a 13.4 MHz parallel resonant circuit, and a reference VFO running from 0.70-0.90 MHz (yes – we know Top Band is 1.81-2.0, not 1.8-2 MHz, but it makes the explanation easier!).

For 20 m, the VFO injection frequency is 24.7-25.05 MHz. This requires a series resonant 3rd overtone crystal at 25.5 MHz, in conjunction with a reference VFO at 0.45-0.8 MHz. Because of the

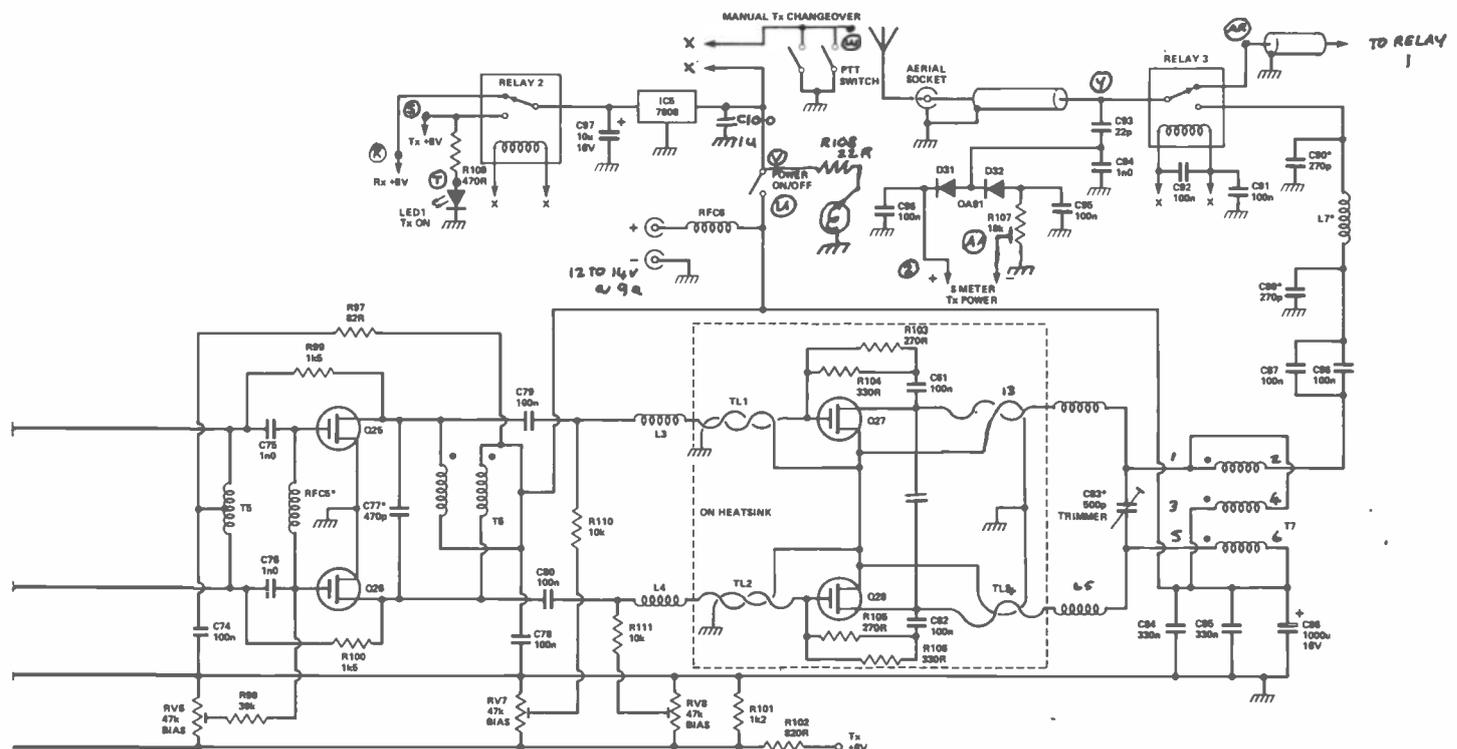

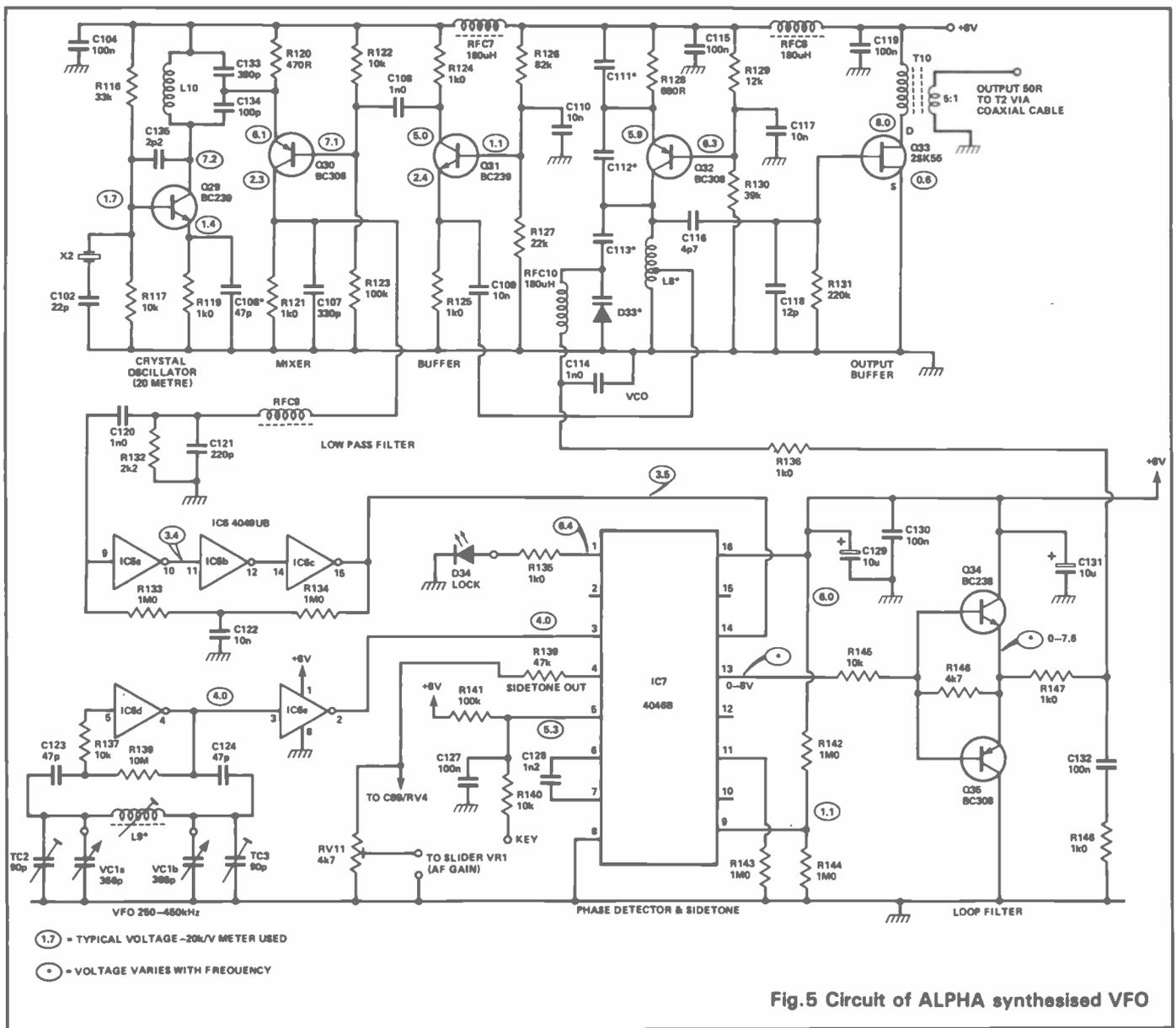


Fig.5 Circuit of ALPHA synthesised VFO

higher frequency crystal, the oscillator circuit for 20 m is different to that of 160 m. This is explained in detail on the circuit diagram, components list, and the assembly instructions.

Sidetone

For CW use, a sidetone circuit has been provided, which uses the voltage controlled oscillator of the 4046, otherwise unused in this application which only requires its phase comparator. R142,144 and C128 set the oscillator frequency, which will be around 800 Hz. Exact adjustment can be made by varying the value of R144. Earthing R140 switches the oscillator on, and the output from pin 5 goes to the slider of the volume control, RV1 via R139, and the level control

RV11 (thus the setting of the main volume control does not affect the sidetone level). On transmit the sidetone signal is routed to the microphone amplifier section.

The ALPHA Case

While we were designing the main PCB, we decided that ALPHA would have a low-profile custom case which would be suitable for either fixed or mobile use. Full drawings will be given for this case, or you will be able to buy it in a completely finished state.

It is constructed from 16 gauge steel, and is therefore extremely rugged. In its commercial form, it comes with welded internal mounting studs for the PCB, speaker and heat sink, and is fully punched, painted and screen printed (much

as in the photographs). The heat-sink for the PA transistors is mounted underneath the lid, and in direct contact with it, giving an efficient solution to the problem of where to put a heatsink when you can't make one as part of an extrusion in the case, like the Japs dol. With the use of the transmission lines to feed the PA devices, this means that just the transistors and a few components are mounted remote from the main PCB.

The front panel offers the following controls and other facilities: S Meter, Frequency Counter, Mic/PTT socket, AF gain/Power On/Off, IF Gain, Drive, Blanker Gain/Blanker On/Off, SSB/TUNE/CW, AF Filter OUT/Narrow/Wide, status LED's for the Blanker and Transmit, and the main VFO tuning control.

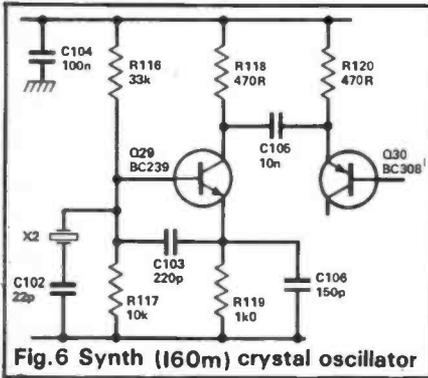


Fig.6 Synth (160m) crystal oscillator

The latter goes to two epicyclic reduction drives, one at 6:1 and another dual type at 6/36:1, connected in series mechanically. We played around a lot with this part of the design, as the VFO 'feel' is very important to most operators. Without resorting to expensive flywheel-type geared reduction drives it is difficult to produce a decent drive system, but we feel this is a very good answer. For several revolutions of the main tuning knob the tuning rate is very slow, with

no trace whatsoever of backlash, then changing to a fast drive for tuning around the band. The transition between the two rates is almost imperceptible, and the torque needed to tune very low. The drives are mounted on two internal brackets in the case, welded as part of the case assembly (or screwed if you make it yourself).

A mobile mounting bracket is part of the design, and is capable of being fixed either over the lid or under the base of the main Transceiver.

Construction

Part Two of this article will describe in full the construction and alignment of ALPHA.

It has to be said now that ALPHA is not a project for the beginner! It involves close soldering work, and if you have not attempted anything like it before, you would be advised to try a few other

simpler projects before tackling this. Despite this, the constructional details will be detailed, allowing almost anyone to tackle ALPHA with a high degree of confidence.

Kits

Kits of parts for this project will be available from WPO COMMUNICATIONS. Options available, for either the 160 m or 20 m version will be a complete PCB KIT, with all board mounted components, PCB, VFO capacitor, pots, wire and drilled heat sink for the PA, priced at £149.50 or a COMPLETE KIT with case (ready punched, painted and screened) plus mobile mounting bracket, and all switches, speaker, hardware etc (leaving only a microphone, key and PSU required) priced at £199.50 (all inclusive of VAT & Post).

Printed circuit boards alone (drilled and tinned) are priced at £22.45 inc.

Component Listing

R1,4,6,9,10,11, 13,14,15,24, 25,36,71,146	4k7	R65,133,134, 142,143,144,48	1M0	C5	160m 1n5 ceramic disc 20m 3p3 ceramic disc 160m 120p ceramic disc
R2,7,12,57, 64,91	68R	R76	3k3	C8,11,12,14, 15,16,17,19, 20,22,24,33, 47,50,51,55, 58,59,60,61, 62,71,73,101, * 105 (* 160m only), 109,110,117, 122	10n ceramic disc
R3,139	47k	R83	270R	C9,13,48,123, 124	47p ceramic disc
R5,21,35,37, 38,50,68,74, 77,82,88,89, 110,111,117, 122,137,140, 145	10k	R92	560R	C25,29,30,36, 37,54,75,76, 94,108,114, 120	1n ceramic disc 150p ceramic disc
R8,40	47k	R94,95	15R	C26,136 C27,64,* 103 (* 160m only), 121	220p ceramic disc 4n7 mylar 0.22uF 16v electro radial
R16,17,18,27, 62,93	100R	R98,130	39k	C31,34 C35	
R19,34,56,67, 109,118,120	470R	R103,105	270R 0.5W	C38,40,68,97, 129,131	10uF 16v radial electro 100uF 16v radial electro
R20	2k7	R104,106	330R 0.5W	C42,70,100 C45	1uF 16v radial electro 47uF 16v sub-min radial electro
R22,32	27k	R112,113	180R	C46	2u2 16v+ tantalum bead
R23	56k	R126	82k	C52,93,102 C63	22p ceramic disc 4u7 16v radial electro
R26,59,70	150R	R128	680R	C65	22uF 16v radial electro
R28,99,100, 115	1k5	R129	12k	C67	22n ceramic disc
R29,97,114	82R	R132	2k2	C77	20m 470p silver mica 160m not used
R30,46,47,69, 72,78,81,87, 119,121,124,125		R138	10M0	C83	20m 500p mica compression
R31,49,116	33k	All resistors 0.25W 5% carbon film unless otherwise stated.			
R33,108	220R	VR1	100k Alps Log pot with rotary switch		
R39,86	5k6	VR2	100k Alps log pot with push/pull switch		
R41	1R0	VR3	100k Alps Log pot		
R42,43	470k	VR4	100k Alps Lin pot with push-pull switch		
R44,84,85,101	1K2	RV1,2,11	4k7 10mm hor preset		
R45,86,75,123, 141	100k	RV3,4	10k 10mm hor preset		
R55,	2M2	RV5	47k 10mm vert preset		
R51	15k	RV6,7,8,10	47k k10mm hor preset		
R53,96,102	820R	RV9	470R 10mm hor preset		
R54,90,131	220k	C1,2,10,18, 21,23,28,32, 39,43,44,49, 53,56,57,66, 69,72,74,78, 79,80,81,82, 87,88,91,92, 95,96,98,99, 104,115,119, 127,130,132	100n ceramic disc 20m 1n ceramic plate 160m 10n ceramic disc 20m 100p ceramic disc		
R60,73	6k8	C3,7			
R61,79,80,127	22k	C4,6			
R63	3k9				



C84,85	160m 4n7 silver micz	D8	BA244	T7	6 Trifilar turns (18t total) 1mm en Cu wire on two cores as RFC6
C86	470n polyester film	D31,32	OA91		2t primary, 8t secondary as T1
C89,90	1000uF 16v radial electro	D33	BB204B	T8	2t primary, 6t secondary as T1
C106	20m 270p silver mica	LED1,2	3mm Red LED	T9	10t primary 2t secondary on core as T1
C107	160m 3n6	ZD1	4v7 400mW Zener	T10	20m TOKO KANK 3335R
C111	20m 47p ceramic disc	IC1	KB4412	L1,2	160m TOKO KANK 3334R
C112	160m 150p ceramic disc	IC2	LM380N	L3,4	20m 5t 1mm en Cu wire on Amidon T68-6 core
C113	33p ceramic disc	IC3	741N	L5,6	160m 10uH axial choke
C116	20m 470p polystyrene	IC4	74LS90	L7	20m not used - link, see text
C118	160m 820p polystyrene	IC5	7808	L8	160m 5t 1mm en Cu wire on Amidon T50-2 core
C128	20m 100p ceramic disc	IC6	4049UB (must be UB)	L9	20m 10t 0.8mm en Cu wire on Amidon T68-6 core
C133(20m only)	160m 220p ceramic disc	IC7	4046B	L10 (20m only)	160m 25t 0.8mm en Cu wire on Amidon T68-2 core (NB: -6 cores are Yellow -2 cores are Red)
C134(20m only)	20m 27p ceramic disc	F1	Uniden SSB Filter	TL1-TL4	20m 7t 0.56mm en Cu wire tapped at 2t from earthy end on Amidon T50-6 core
C135(20m only)	160m 56p ceramic disc	X1	10.7MHz 2.2.kHz type 10M02DS	DISPLAY	160m 12t 0.56mm en Cu wire tapped at 3t from earthy end on Amidon T50-6 core
C136	4p7 ceramic disc	X2	20m 10.6985MHz		20m TOKO RW06A7752EK
CT1	12p ceramic disc	RL1,2,3	160m 10.7015MHz		160m RW06A7752EK
CT2,3	1n2 polystyrene	IFT2,3	20m 25.500MHz 3rd ovt HC18/U.		160m RW06A7752EK
VC1	390p ceramic disc	IFT4-9	160m 13.400MHz		TOKO 301KN 0700 (Violet)
Q1,2,5,15,22	100p ceramic disc	RFC1,3,4	30pF par. res HC18/U		twisted pair transmission lines at 5 t.p.i. using PTFE covered wire - see text for details
Q3,4,8,9,12,19,20,21,29,30,31,34	2p2 ceramic disc	RFC5	Kam Ling KUIT-A or B.		
Q6,7,14,16,23	150p (20m only)	RFC6	12v SPCO Relay		
Q10,11,33	60pF max 10mm trimmer	RFC7,8,9,10	TOKO KACS 3894A		
Q13	90pF max 10mm trimmer	T1	TOKO KALS 4520A		
Q17,18,32,35	Jackson Type 00 air variable. Twin gang	T2	10uH axial choke		
Q25,26	365 + 365pF.	T3	20m 6.8uH axial choke		
Q27,28	3SK45 or 3SK51	T4	160m 3k9 resistor		
D1,2,10-30	2N2369 or BSX20	T5	14t 1mm dia enamelled Cu wire on Fair-Rite Core type		
D3,4,5,6	2SK55	T6	59-61001101		
D7,9	J310		180uH TOKO type 7 BA or BS (marked 181)		
	BC308		6t Primary, 6t CT secondary		
	VN66 AF (Siliconex)		0.2mm en Cu wire on Fair Rite Balun core type 28-43002402		
	IRF120 or IRF123 (ex International Rectifier) or VN64 GA (Siliconex) (see text) with mounting kits		6t CT primary, 6t Secondary as T1		
	1N4148		2t primary, 6t secondary as T1		
	Schottky type		10t primary, 4t CT secondary as T1		
	Not used		8t CT as T1		
			10t Bifilar wound (20t total) 0.56mm en Cu wire on core as RFC6		

Radio in the 'Rising Sun'

The next time 20 metres goes dead, ponder this fact about the most prolific users of the band. If all the radio amateurs in Japan were to stand with outstretched arms touching, the human chain formed would extend for over 1,700 km. (This is roughly the air distance bet-

that the amateur population in Japan will have increased a bit. I'm sure that in the 10 hours it took me to fly from Sydney to Tokyo, the bands greeted a few more DXers and rag chewers. I was pondering the possibilities when I touched down at Narita International Air-

port.)


As we sped towards Tokyo, all the passengers around me must have been contemplating how they would spend their few days of stop-over or their two week holiday in one of the world's largest cities. Most undoubtedly would opt for the initial buzz-around-town city tour to see somber Kasumigaseki where the government offices are located; the massive 400 year old Imperial Palace; the sophisticated and shop-lined Ginza; the 1,350 year old Asakusa Kannon Temple with its god of thunder guarding the entrance and the amusement and shopping area of Old Ueno, concluding with a leisurely cruise down the Sumida River and a traditional tea ceremony. None of these tourist activities for me — or at least not until I've finished my mission — I thought, as I spotted a bay of 44 440MHz yagis stop eight well guyed tower sections.

On the drive to Tokyo I heard exclamations from fellow passengers about "how modern all this is", and "gee, it sure is spread out." I only exclaimed about the number of yagis, quads and dishes I saw... but very quietly, as I didn't want anyone to know that I was planning a more interesting time than they would have!

Down To Business

At last we arrived in the heart of skyscraping Tokyo. I transferred my well travelled luggage to the boot of a spotless taxi and said, "Shinjuku," to the spotless white-gloved taxi driver. We located the Take-No-En Minshuku (a guest house-type lodging charging £13 including two meals) without much difficulty. The quiet surroundings and comfortable bed coupled with flight fatigue beckoned me to rest. The importance of my mission urg-

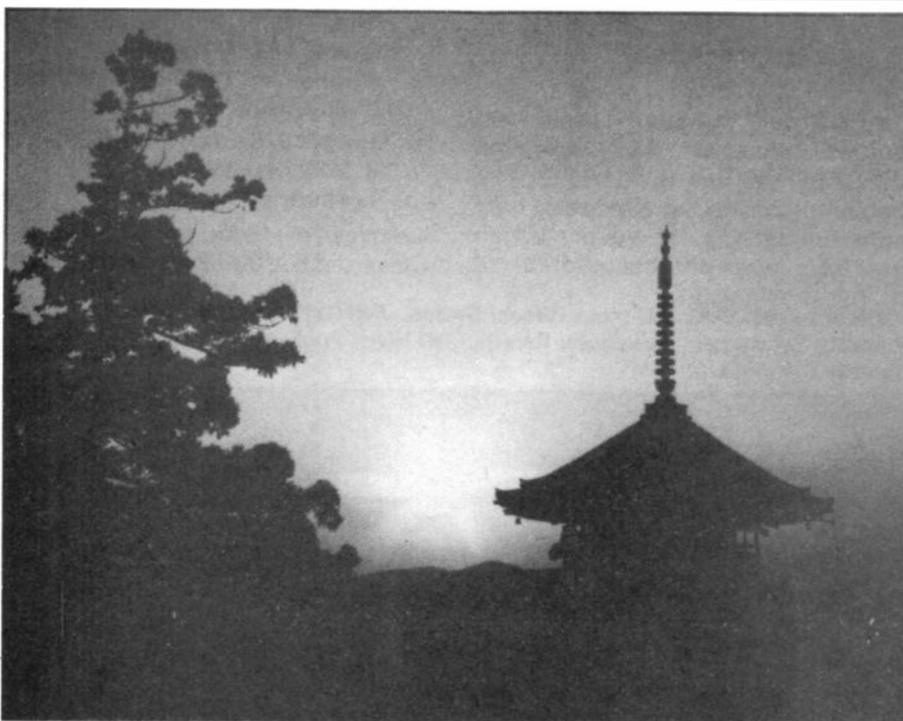Much of today's Amateur Radio equipment comes from Japan, which also has the largest number of licenced amateurs in the world — well over 1 million! Tom King, VK2ATJ, packed his typewriter and went! to investigate.



ween London/Naples, and about half the way from the cool climate of northern Hokkaido to the subtropical warmth of the Southern Okinawa Islands). That's quite a distance, but more importantly it's an astounding number of amateurs.... some 1,020,000.

By the time you've finished reading this, the odds are very good

port; I had arrived in the Land of the Rising Sun.

Ultra modern Narita must have received an award for being so far from Tokyo as it's 60 km between airport and capital, a distance which is covered in a little over an hour. (Fortunately, there are frequent coaches which offer white glove courtesy and a welcoming



The HQ of the Japanese Amateur Radio Relay League (JARL) in Sugamo, Tokyo

ed me on however . . .

The Shinjuku railway station was not far from the minshuku so I walked the distance, hardly noticing the multitude of cinemas and restaurants sprouting from the suburb. I purchased a ticket for Sugamo station (6 stops north of Shinjuku on the Yamanote line), checked for the correct platform and waited for the next train. (All this, I must emphasise, was undertaken during off-peak hours, otherwise the commuter experience becomes a rib-bruising ordeal!)

Since railway stations are labelled in English as well as Japanese, it was easy to get off at my destination. "I've conquered Tokyo," I thought as I headed out of the station, hopefully armed with a tiny slip of paper containing just one address in Japanese.


I showed the address to a street corner policeman and he pointed to the other side of the station. Immediately to the left of the station I found a small circle of grass and a narrow street which ran parallel to the station. I followed the street for one block, then scanned the roof line for any telltale indications. It worked, as a few buildings from me was an assorted array of every imaginable type of antenna. It was on the doorstep of 14-2 Sugamo, 1-chome, Toshimaku, the headquarters of the Japan Amateur Radio League. Fortunately, I had called ahead (03) 947.8221 so Mr. Hiroshi Onoda, Deputy Chief, JARL Publicity Sec-

tion was awaiting my arrival. Mr. Onoda, JM1RYK, like Mr. Takenobu Kaieda, JH1HNN, Publicity Manager for the League, spoke excellent English and provided a fascinating look at JAs and the JARL.

A Bit Of History

'Official' amateur radio activities began in 1927 (although the JARL was set up in 1926). The beginning of the modern era of ham communications, however, began in 1952 with the resumption of

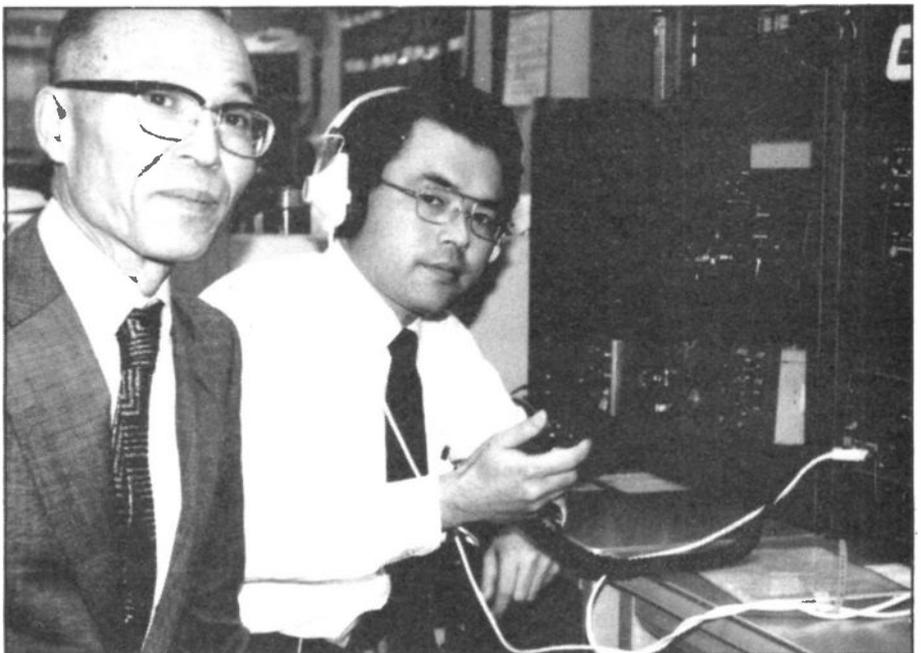Visitors to the JARL will meet Hiroshi Onoda, JM1RYK, Deputy Chief, Publicity Section and Takenobu Kareda, JH1HNN, Publicity Manager and can operate the JARL station



amateur radio operations which had been suspended during World War II. The intervening 32 years has witnessed a virtual explosion of amateur interest and enthusiasm seen nowhere else in the world.

Thanks to the 600 training classes offered throughout the 147,200 square mile island nation of Japan, some 30,000 new amateurs are added to the ham ranks each year. (By the year 2000, according to current projections, Japan will have an estimated 1,500,000 licensed amateurs and somewhere around 750,000 equipped stations!)

The JARL plays a unique role in the procedure to become an amateur as the organisation writes, gives and marks the exam and then sends the results to the Radio Regulatory Bureau for the issue of a call sign. The entire process from exam to call sign takes three to six months.

There are four grades of licence in Japan:

- * 1st Class, all bands and all modes, 500W output.
- * 2nd Class, all bands and all modes, 100W output.
- * Phone, no 14MHz or 10 MHz, 10 W output.
- * Telegraph, no 14 MHz or 10 MHz, 10 W output.

Testing charges for the four licenses are around £10.25, 1st Class; £8.80, 2nd Class and

£5.85 for the two 10 watt licences. Exams are given twice a year for 1st and 2nd Class.

While some aspects of amateur activity and legislation in Japan are absolutely astounding for their progressiveness, other aspects are not as sophisticated as would normally be expected in a country with a million plus amateurs. For instance, third party traffic of any kind is forbidden. A reciprocal licensing agreement is in progress, however. Until 1982 repeaters were illegal, but, now, the "horizon extenders" are so popular that Japan's 70cm band of 430 MHz to 440 MHz is filled to capacity. Another UHF band is receiving overflow, with activity on 1.260-1.300 GHz gaining new operators every day. Commercial gear for this band is selling well in the half-a dozen equipment outlets in Akihabara (six railway stops beyond Sugamo on the Yamanote line).

The JARL, like amateur radio leagues in most other countries, is in constant negotiation with the government to allow increased privileges. This, however, is only a small part of its overall commitment to developing the art of amateur radio in Japan.

Highly Organized

Aside from its active involvement in the amateur exam and licensing process the JARL liaises with its more than 2,000 affiliated radio clubs. It does this by staffing a regional office in each of the 10 JA call areas. (In all, there are 130 staff members of the JARL.). Headquarters lend 16 mm films and video tapes and have staff who can present non-technical and technical lectures to widely diversified audiences. Additionally, HQ co-ordinates a TVI assistance program which involves 700 JARL members and TV and audio equipment manufacturers.

Within the JARL headquarters office in Tokyo is a state-of-the-art station setup (operational from 10am to 5pm) and a publications division which produces a call book (only in Japanese), a QSO manual (in seven languages), the monthly official journal, "JARL News" (which contains news — particularly awards and contests and information on activities of local clubs)



JA1QCQ, Managing Editor of 'CQ Ham Radio', displays the world's largest ham radio magazine

and the International Amateur Radio Union "Region 3 News" magazine (a bi-annual publication). The Sugamo office also has another major task with the processing of 2 million QSL cards a month through the JARL QSL Bureau!

Yearly membership in the JARL is around £14. This is hardly a financial burden to Japanese amateurs who live in Asia's most affluent country, yet JARL members number only about 130,000 or about 12 per cent of the total ham population in the country. Japan's largest selling independent amateur magazine "CQ Ham Radio" doesn't have a much greater share of the market with its 150,000 monthly sales figure.

The offices for "CQ Ham Radio" are conveniently located in the same building as those of JARL. Mr. Oneda of JARL's publicity section can usually arrange for a visit to the magazine for a look at how the world's largest amateur magazine is put together. (While it may not sell the most copies in the

world, "CQ Ham Radio" consistently runs over 500 pages an issue).

Mr. Sumio Miyamoto, JA1QCQ, Editor-in-Chief, heads an editorial team of 20 journalists (*I've just gone green — Ed.*) and 6 advertising personnel. The issue he was involved in during my visit was shaping up to the 532 page mark which is a far cry from the 24 pages for the first issue which appeared in September, 1946. The biggest issue to date was December, 1980, which contained 596 pages of ads and articles. The economic situation in Japan has seen a drop in advertising by equipment manufacturers but *not* a drop in the number of articles "CQ Ham Radio" publishes every month.

Despite the availability of advanced commercial equipment, Mr. Miyamoto noted that Japanese amateurs are still interested in building at least some of their own gear. There's interest in amateur TV, RTTY, antennas, computers and microwave articles with 10,000 MHz now receiving much attention.

Mr. Miyamoto has noted a change in hams' interests since he's been editor-in-chief, with Japanese amateurs preferring more technical articles. "CQ Ham Radio" is now having to work harder to explain techniques, and explain them on different levels, as beginners are just as interested but their relative recent entry into amateur radio may mean their level of experience and understanding is somewhat limited.

Japanese amateurs not only like to work DX and exchange cards but they like to know who's worked what, when it was worked and how. Consequently, "CQ Ham Radio" carries much DX information. In the early days of the recent operation from China, the magazine dispatched staff to China with the result being a massive colour feature eagerly devoured by DX-hungry readers.

"What's the most difficult aspect of editing the world's largest amateur radio magazine," I asked Mr. Miyamoto. His answer was simple. As he handed me a copy of "CQ Ham Radio" he said, "judging what amateurs want to read and meeting those challenges in a country where the sun is just dawning in amateur radio."

Addendum

Iambic Keyer (June 1984)

In the process of publication, a number of errors crept into this project, which we regret.


Circuit diagram, P60: The circuit of the keyer on page 60 is incorrect in that IC4 a and b pins 1 and 15 connect only to C3 and C4 respectively — not to earth as shown. There are a few labelling errors on the circuit which could serve to confuse. These are as follows: IC4a pin 4 should be 'A' not 'B'; IC2b CLK pin 3 and S pin 6 should be pin

numbers 11 and 8 respectively as in IC1b; The arrow between R4 and R5 should be labelled +12V.

Overlay diagram, P61: Alterations are necessary to the PCB in the area of IC4. The corrected overlay diagram shows these in simple diagrammatic form; for clarity, the pin connections of IC4 are given below; Pin 1: remove earth connection, this pin should connect to C3 — only; Pin 2: connects to C3 + and R3; Pin 3: OK; Pin 4: connects to IC3 pin 11;


Pin 5: connects to negative supply; Pins 6 to 14: all OK; Pin 15: remove earth connection, connects to C4 only; Pin 16: OK.

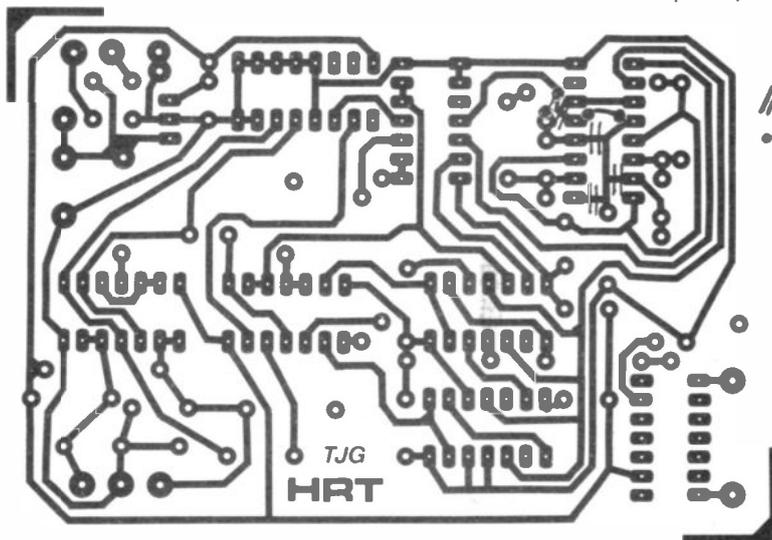A small piece of PCB track is missing between Pin 1 of IC1 and the adjacent wire link which should connect the positive 12 V supply to pin 1 of IC1 to connect the positive 12 V to the IC. On this diagram, the potentiometer should be labelled RV1 not R2; R3 becomes R2; R4 becomes R3; R5 is correct; R6 becomes R4.



// = CUT
 — = LINK

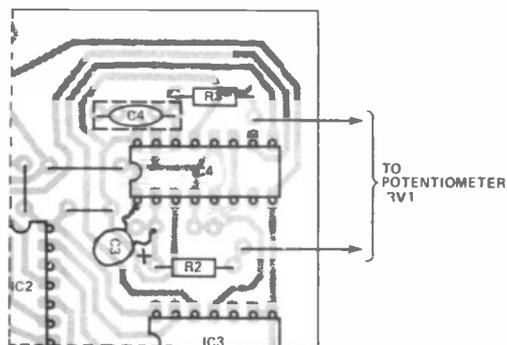Finally, we would like to apologise to the author, David Silvester, for not only getting his project slightly less than perfect — but also for spelling his name wrong. Sorry, it was one of those months.



WPO COMMUNICATIONS

G3WPO 20 FARNHAM AVENUE, HASSOCKS
 G4KEI WEST SUSSEX BN6 8NS (07918) 6149

ITS UNFORGETTABLE . . . IT'S THE UNIVERSAL MORSE MEMORY



The **POWERFUL** CW memory add-on offering up to 2 mins of message storage from **ANY** type of Morse key. Connects between **YOUR** key and **YOUR** rig.

ALL THESE FEATURES: works with iambic keys, Vibraplez keys, paddle keys, hand keys, two pieces of Meccano, your key. Variable speed control can upshift 20 wpm CW to more than 200 wpm for meteorscatter. Repeat feature for beacon mode message storage. Handles any Morse speed from 0 to 400 wpm. Ideal for effortless contest working. Retains character of operator. Good Morse in; good Morse out; bad Morse in, bad Morse out. Excellent teaching aid. Inbuilt Sidetone oscillator. Memory retention when off. All this for just £49.50 ready built inc VAT & P&P.

Telephone in for:

OTHER SUPERBLY ENGINEERED PRODUCTS FROM WPO:

Kits — DSB80 QRP Transceiver £37.45; DSB2 QRP Transceiver £68; 2 metre FM Transceiver £68 (Rx £39.50, Tx £32.90); VFO Kits — single band HF or Multiband — 2 metre VFO £38.50; Project OMEGA — 10 band Transceiver for the enthusiast constructor; ALPHA — Single band SSB 50W Transceiver, 160 or 20 metres, £199.50 with case etc; HF QRP ATU — £28.52; Commercial enquiries welcome. 24 hour Ansaphone for credit cards. Mostly ex-stock but allow 28 days for delivery. Short catalogue 16p stamp — Full 50p stamps.



A Fresh Look at the FT200



Lowe's of Matlock introduced the FT250 by Sommerkamp in 1969. The rig was manufactured in Japan by Yaesu for Sommerkamp; Yaesu directly marketing it themselves as the "Yaesu FT200". In the USA the same rig carried the Henry Radio label and was known as the "Temp One", all three rigs being identical apart from the name

ment. This system with a few alterations was later incorporated in the FT101ZD. The general block diagram of the FT200 is shown in Fig.1, and Fig.2 shows how the pre-mixer system operates when the rig is tuned to the 15m amateur band. Pre-mixing avoids the cross modulation and noise problems caused by the usual need to use

weight transceiver, with a separate and heavier loudspeaker and power supply unit. All bands 80-10 metres are included with the exception of the new WARC bands. Full coverage of 28-30MHz is provided for in the switching, but only the 28.5-29MHz crystal was supplied as standard. Fitting the extra crystals needed to give full 10 metre coverage is simplicity itself, but I know of no simple way of incorporating 1.8MHz or the new 10, 18 and 24MHz bands on the FT200.

If you are considering buying a second hand FT200/250, Bill Lowe's original advert, reproduced here courtesy of Lowe Electronics, tells most of the plus points, and it only remains for me to point out the shortcomings in what, after all, is an economy rig.

The FT200 is full of valves. Nothing wrong with bottles, of course, they do have some advantages over solid state devices, but they don't last as well. Usually transistors have only three possible states: good, bad or 'noisy', and they do not gradually tail off in performance under normal cir-

After Harry Leeming's excellent and highly popular series on up-dating the FT101, HRT received many requests for a similiar article on the FT200. Well, G3LLL got to work and here it is!

plates. The rig's success can be judged by the fact that it remained in production ten years, and during this time went through very few circuit changes, and the only way later production models can be easily identified is that in the last few years' of production the original grey cabinet was replaced by a black one.

The FT200 does not use the common double superhet arrangement as do most other rigs of its era, but it uses a pre-mixer arrange-

ment. This system with a few alterations was later incorporated in the FT101ZD. The general block diagram of the FT200 is shown in Fig.1, and Fig.2 shows how the pre-mixer system operates when the rig is tuned to the 15m amateur band. Pre-mixing avoids the cross modulation and noise problems caused by the usual need to use two mixers in a double superhet and without the complication of synthesisers or phase locked loops to provide the oscillator injection. With the FT200 the VFO operates over a fixed frequency range of 5-5.5MHz, so that frequency stability is not too much of a problem.

Looking at Fig. 1, one sees that apart from the VFO the FT200 is almost entirely non 'solid-state'. Mechanically, the complete Yaesu outfit consists of a fairly light

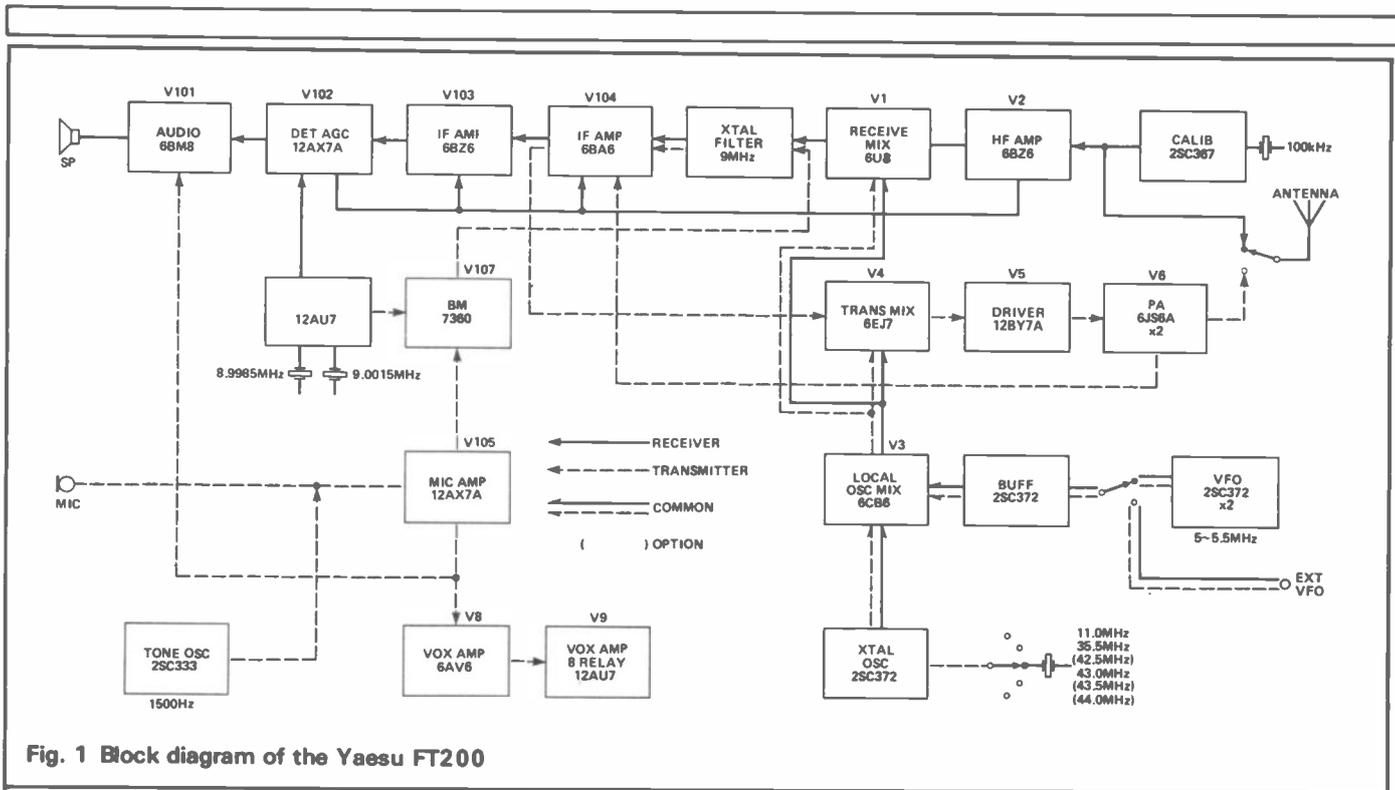


Fig. 1 Block diagram of the Yaesu FT200

cumstances. Valves do occasionally suffer from, "catastrophic failure" but more often than not they just gradually deteriorate. To bring an old and tired FT200 up to scratch can mean the purchase of over £50 worth of valves. Some of the valves are just not made any more by the original makers, and not all equivalents of other manufacturers work; some can even cause extensive damage if fitted — more about this later.

No provision is made for a CW filter on receive. Transmit wise, in particular, the FT200 will give good account of itself in the CW mode, and can be run at near the full legal limit. The best one can do for reception is to back-up the 2.3kHz wide SSB filter with a good active audio filter such as one of those made by Datong. (*The Editor would like to point out that he used an FT200 largely on CW for a number of years with no extra filtering — the SSB filter has very steep 'sides' and the rig is considerably better than, say, an FT101 without a CW filter.*) The FT200 also has no noise blanker. On paper this is a disadvantage when compared with other rigs made at around the same time, but in practice it is just as good to have a rig without a noise blanker, than it is to have one with a noise blanker that doesn't work!! Unfortunately, this is about all most noise blankers

on competitive rigs made at around the same time can offer!

The scale of the FT200 S-meter is marked logarithmically up to S9 plus 60, but the circuit which drives it seems to operate almost linearly. The result is that readings on signals below about S8 are insufficient whilst readings over S9 are too generous. Not too much to worry about once you learn to add a few S points to your DX signal reports, and to subtract 20-40dBs off your locals signals.

A Word Of Advice

An FT200 in good condition

can be an excellent first buy when funds are somewhat tight; untried bargains can, however, prove to be expensive and so as the rig has been around for over fifteen years, condition and value for money can vary enormously. Faulty rigs can usually be repaired, but equipment that has been butchered or which has had unrecorded modifications carried out on it can prove to be a very expensive proposition, so that it is wise to have a good look inside and outside first. As with a car purchase there is little to beat a trial run, and if fed with a reasonable aerial system the rig should work well on all bands, but expect the S


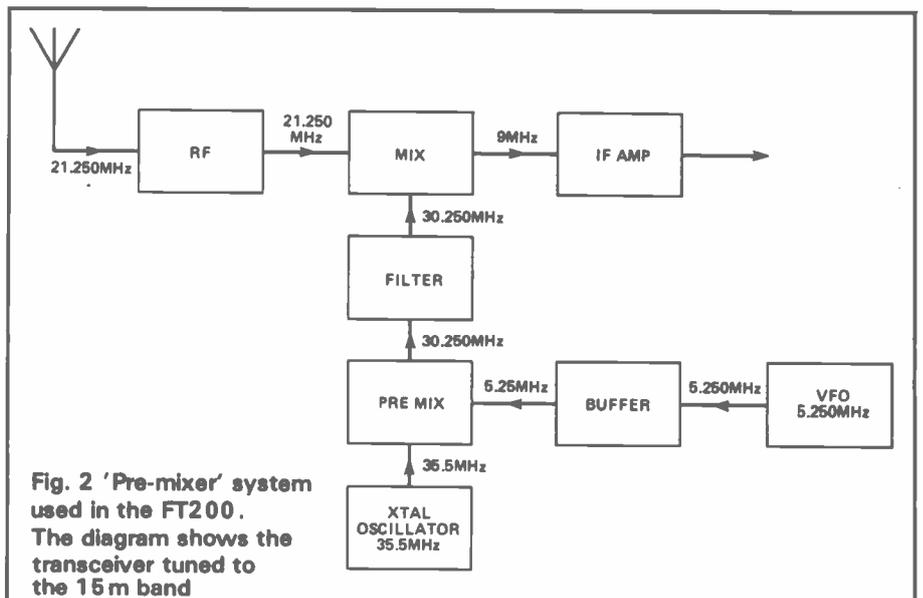


Fig. 2 'Pre-mixer' system used in the FT200. The diagram shows the transceiver tuned to the 15m band

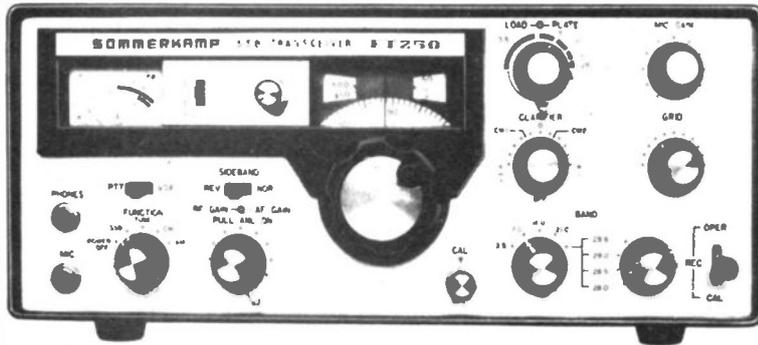LOWE ELECTRONICS 50/52, WELLINGTON STREET,
MATLOCK, DERBS. DE4 3GS
MATLOCK 2817 (2430 evenings)



SOMMERKAMP FT-250 TRANSCEIVER - £160.0.0.

240W p.a.p. 80 to 10 (4 segments of 10 if required with 3 extra crystals) Receiver sensitivity 0.3 microvolts for 10dB S + N/N. Selectivity: 2.1 kHz at 6dB, 3.4 kHz at 8dB. This is an incredible 1-82 shape factor. Stability: plus or minus 100 cycles after warm-up. Meter reads cathode current, relative power out, or ALC on transmit and acts as an "S" meter on receive. Power required: 800-800vdc at 200mA average, 300vdc at 50mA; 150vdc at 150mA; -100vdc at 10mA and 12.6vac at 5A. This 5A may be obtained from two sources (2A and 3A) if preferred as there are two separate heater circuits (just another thoughtful touch!). Size: 13 1/2" w x 5 1/2" h x 12" in overall depth. Weight: 18 lbs. This latest addition to the Sommerkamp range is designed to compete with the lower cost equipment in price while at the same time outperforming it handsomely. It does this by leaving the construction of a power supply to the owner. This is no great hardship to most amateurs who can soon lash up a p.s.u. We can of course, supply a matching p.s.u. if you really want one, for £45.0.0 (but I'd much rather help you build your own!). The high quality and thoughtful engineering associated with Sommerkamp has not been relaxed in the least and examining the FT-250 closely there are a few nice touches not usually found in this price range:—
1—The designer has avoided using the PA tank as the Rx input—he has used proper r.f. coils of optimum design. If you think about it, a Pi net by itself makes a pretty poor Rx input.
2—VFO and heterodyne oscillator are pre-mixed before being injected into the Rx chain. Hence the great sensitivity and low noise performance.
3—Transistors are used where they are best suited, not just for the sake of using them. Where valves are superior, valves are used.
4—A derived band pass filter between the VFO and following mixer. Very nice touch, this.
5—Built in tone oscillator for tune-up and CW sidetone.
6—Amplified agc.
7—"S" meter sensitivity (as well as zero) pot. This will delight the "60db over S9 OM" boys!
8—All crystals have trimmers for extreme accuracy.
9—A very nice robust geared drive plus a ball drive for slow, slow tuning (15 KHz per turn).
The above points, Gentlemen, are niceties the spec. sheet doesn't cover—niceties which are unusual in low priced gear. Also, of course, you have a full complement of operating facilities which are built-in as standard and not optional extras—10 KHz calibrator, VOX, PTT, MOX, switcheable sidebands, monitored ALC, R.I.T., extremely linear VFO with 1KHz calibration and a healthy long-life PA virtually identical with the FL-500 Tx.
All this adds up to a very fine rig at a rock bottom price and I for one, wouldn't blame you one little bit for wanting one! Needless to say, it carries a 12 month guarantee.

73 de Bill, G3UBO/VBSP

Original advertisement for the FT200 which neatly summarises the main advantages of the transceiver

meter to be mean and sensitivity a little down on 10 and 15 metres. RMS power output into a dummy load should be well over 100 watts on all bands below 15 metres, and around this figure on 10 and 15m. Check the grid tuning control; if the correct valves are fitted and alignment is OK the point of maximum sensitivity on receive should coincide near enough with maximum output on transmit. ALC action should be obtained on all bands except, perhaps, on 10 metres and the point of maximum output on the PA tune control should coincide with minimum dip if neutralization is OK and the correct PA valves are fitted.

Servicing The FT200

The original RF and IF valves in the FT200 were made by Toshiba and are difficult, if not impossible, to obtain now. Replacement of several of the receiver valves with less gainy substitutes does not help a receiver which initially was perhaps a little short of gain. One

way of adding extra gain, recommended by the FT200 club in New Zealand, is to remove the 6BZ6 RF amplifier valve and its holder, and wire in a new holder to take an EF183. This is perhaps a move only recommended for the technically adventurous, and Colin Wilson, G4AZM, (often seen surrounded by

hundreds of valves at mobile rallies) recommends the 6DC6 as being a plug in replacement for the 6BZ6 with higher gain; this being an easy way to hot up the FT200. Other mention the 6EW6 as being another suitable substitute for the 6BZ6 when more gain is required.

The FT200 gets hot — very hot — and so despite some effort having been put in by Yaesu to ensure temperature compensation, a little long term frequency drift is inevitable. The same heat can also cook components and reduce their life — adding a fan to suck out the heat from the rear of the PA cage is a very worthwhile move and considerably increases stability and long term reliability.

The AGC System. As on most valve rigs the FT200 AGC line is of very high impedance, and is soon upset by any small 'leakage'. The most common trouble with the AGC system is that as the set warms up, the receive gain tends to drop and the zero on the S meter drifts up for the first hour or so. A couple of S points drift is normal but more than this indicates that one of the AGC control valves is flowing grid current and is gradually biasing off the AGC system. The most common culprit is V104, a 6BA6, and this should be replaced by its heavy duty equivalent the 6BA6W which, in most cases, will very considerably reduce the drift on the S meter.

The RF gain circuit functions by applying a controlled negative voltage to the AGC line. Sometimes, the high valve resistors

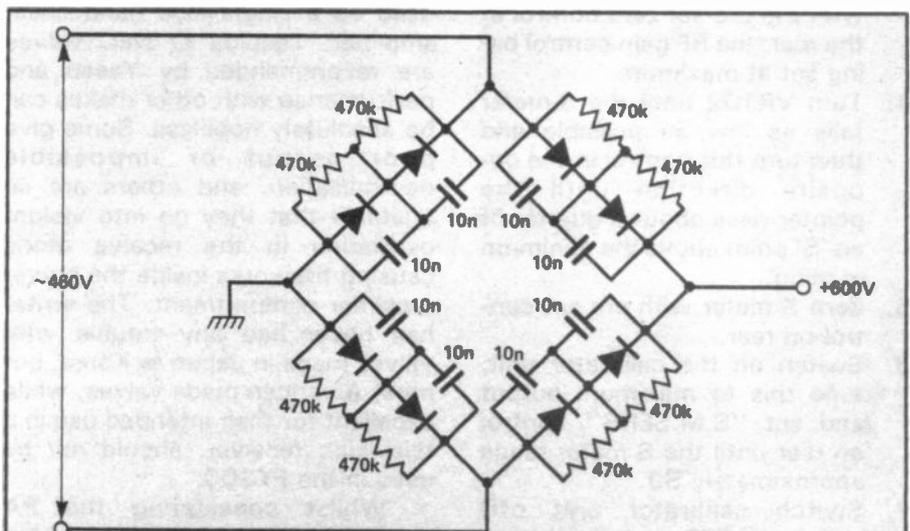


Fig. 3 In the event of trouble with the HT rectifiers, not uncommon with the FT200, they should be replaced by a bridge of 8 BY127 rectifiers as above

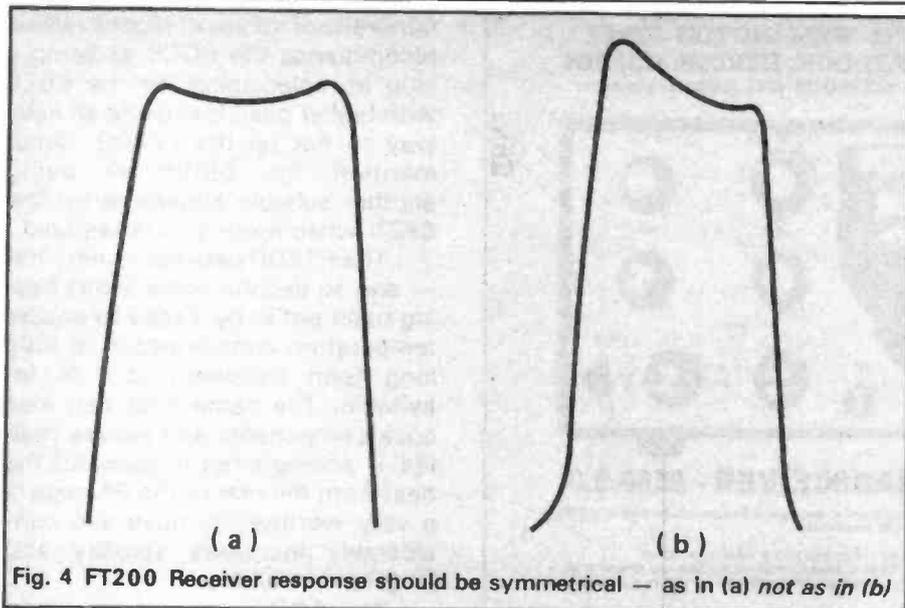


Fig. 4 FT200 Receiver response should be symmetrical — as in (a) not as in (b)

around V102B, and in the grid circuits of the AGC controlled valves, multiply in value or go open circuit. This gives distortion on strong signals, low receive gain, or incorrect operation of the RF gain control.


Setting up the AGC system. Presuming that there is no fault in the AGC circuitry, distortion on strong signals with attendant necessity of excessive backing-off of the RF gain control indicates that the AGC system is out of adjustment. To re-align this, proceed as follows:

1. Remove case of FT200 and leave to warm up for about 20 minutes.
2. Remove aerial and tune to 3.8MHz in the AM receive mode.
3. Set the 'S-meter' to about S2 with the pre-set zero control at the rear; the RF gain control being set at maximum.
4. Turn VR102 until the S-meter falls as low as possible and then turn this control in the opposite direction until the pointer rises about a quarter of an 'S' point above the minimum reading.
5. Zero S meter with pre-set control on rear.
6. Switch on the calibrator unit; tune this to maximum output and set "S.M.SENS" control on rear until the S meter reads approximately S9.
7. Switch calibrator unit off; switch to SSB and check that zero on SSB is the same as on AM.

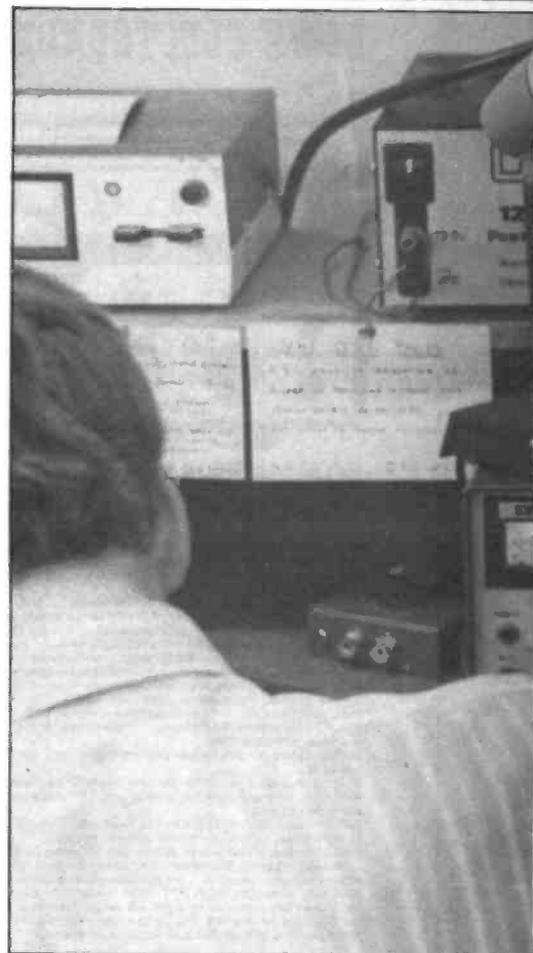8. If zero rises above S1, reset capacitor (twisted wire under V102) until the reading falls.
9. If much adjustment was necessary repeat steps 3 to 8.

The PA Stage. This used originally a pair of 6JS6A valves; these being replaced in later production by the slightly higher rated 6JS6C. These valves, which preferably, should be in matched pairs are plug-in replacements for each other, although it is sometimes recommended that when using the former, the I/C current is set at 50mA, whereas, with the latter, setting the bias for 60mA is advised. It is important to note the 6JS6 is a television line output valve, and that its specification does not guarantee inter-electrode capacity or linearity when used as a single side band linear amplifier. Toshiba or NEC valves are recommended by Yaesu and performance with other makes can be absolutely hopeless. Some give poor output or impossible neutralisation, and others are so unstable that they go into violent oscillation in the receive mode causing fireworks inside the power amplifier compartment. The writer has never had any trouble with valves made in Japan or Korea, but most American made valves, while excellent for their intended use in a television receiver, should *not* be used in the FT200.


Whilst considering the PA stage, do not forget the 11-pin plug which must be inserted into the rear of the FT200. A link in this



Despite its age, the FT200 is still a popular rig for driving VHF/UHF transverters because of the readily accessible very low power output at the rear of the transceiver. The picture shows the 70 cm station at G3AYC where an FT200 drives a Microwave Modules transverter.

plug completes the PA heater circuit for the rig, and whilst it should be removed when driving a transverter, so as to disable the PA, the transceiver will not work in its normal mode without it.

Blown PA Valves. Before replacing faulty 6JS6 valves, it is wise to check that the new ones will not be immediately blown! With the valves removed, a high impedance voltmeter should be used to check the bias voltage on pins 5 of the valve bases. This should read around -50volts with the rig on SSB transmit with the mic gain at minimum, and about -90 when switched to receive. Lack of these negative voltages will result in the very quick destruction of any new valves fitted with, perhaps, damage to other components as well. A common 'bias' fault is the

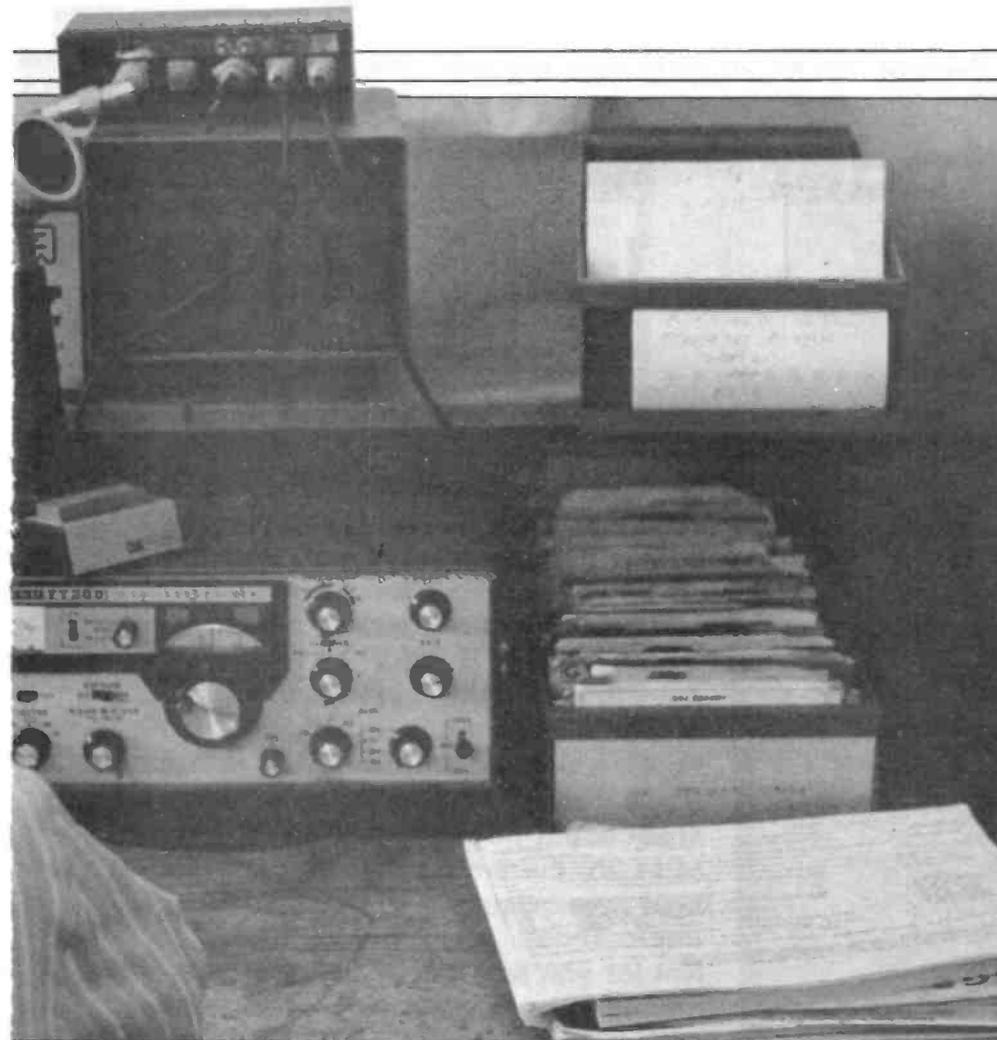

failure of the coupling capacitor which runs from the anode of the driver valve to the grid of the PA (C55), and if the capacitor shows the slightest leakage it should be replaced — as it will couple the +300volt supply on to the bias network!

The Driver Stage. The 12BY7A once again is not a transmitter driver valve, but was developed for video amplifier use and so certain parameters will vary from one maker to another. Yaesu, like other Japanese manufacturers, designed their rig around Japanese valves and Toshiba or NEC valves should be used. The use of other makes usually results in either a shortage of drive, or Tx and Rx peaking at different points on the grid tune control. Whilst discussing the driver stage, note the choke L11. This is in the neutralisation circuit, and shorted turns on this component is a fairly common cause of low drive on the FT200. Its presence can be easily overlooked; if it is suspected it can be temporarily replaced by almost any shortwave RF choke if desired to prove as to whether or not it is the cause of trouble.

Carrier Balance. Listening to FT200s on the air one soon notices that carrier balance can be a problem, and quite a few have inadequate carrier rejection. Rejection of carrier on the FT200 relies on a correct balance in the 7360 balanced modulator valve *and* the correct positioning of the carrier frequency about 20db down the slope of the SSB filter. The latter can be checked by first tuning the receiver in the SSB mode for maximum S-meter reading on a crystal calibrator and then by re-tuning for zero beat. Zero beat should occur at a point of about 3-5 S-points below that obtained at maximum signal, and this test should be repeated on the reverse side-band. If the S-meter does not appear to fall much at zero beat on one side band, switch off the calibrator and compare the background hiss on each sideband. A carrier crystal which is too close into the pass band of the crystal filter will result in a deeper pitch of hiss, and the relevant crystal trimmer TC101 or TC102 should be adjusted until the pitch of hiss becomes higher and then the first test should be carried out again.


Balance in the 7360 stage is adjusted by VR106 and this adjustment will be found to be less critical once the carrier frequency is correctly set. Carrier balance does vary slightly as the 7360 warms up, and can be very erratic as the valve gets older so that eventually replacement becomes essential. Be warned, however, that the 7360 valve is rather expensive and may cost as much as a pair of PA valves.

Blown Fuse. When using the recommended power supply, a common cause of trouble is the HT rectifiers. Yaesu's circuit shows 4 HT rectifiers in a bridge format but, as in the FT101, some power supplies are fitted with 8 as per Fig.3. When any trouble is experienced with HT rectifiers, the final cure is to fit 8 new BY127 TV type rectifiers, adding the necessary resistors and capacitors as shown.

Alignment. Full details for this are given in Yaesu's manual if it is really necessary. Alignment doesn't normally seem to be often needed in the RF driver and front end circuits, but the 9MHz IF transformers do drift a little. L101 and L102 should be peaked on receive whilst L103 and L104 are best first peaked for maximum drive on transmit. After peaking L103 and L104 on Tx, switch to receive and tune through the crystal calibrator on the 40m band, watching the S-meter. The response should be as per Fig.4a and not Fig.4b. Detune 103 and 104 the minimum amount possible so as to get the maximum possible Tx gain with a symmetrical receiver response. Finally, check that the receive response is asymmetrical without any tendency to oscillation on the 3.5 and 14MHz bands. Any problems, here, can be cleaned up by slightly retuning the trap coil L1.

On The Air. The FT200 does not match modern low-Z mics but has a 50Kohm input for the mics of the 1970s. Most of these were of Jap origin and were somewhat short of treble (a lot of Japanese mics still are). The FT200 is much better for working DX if used with a bright mic, and Shure's 444 Hi-Z or 444D dual impedance are recommended. If funds won't run to these, try a crystal insert or a CB high output crystal mic such as the "Pace" hand held — have fun with your FT200.

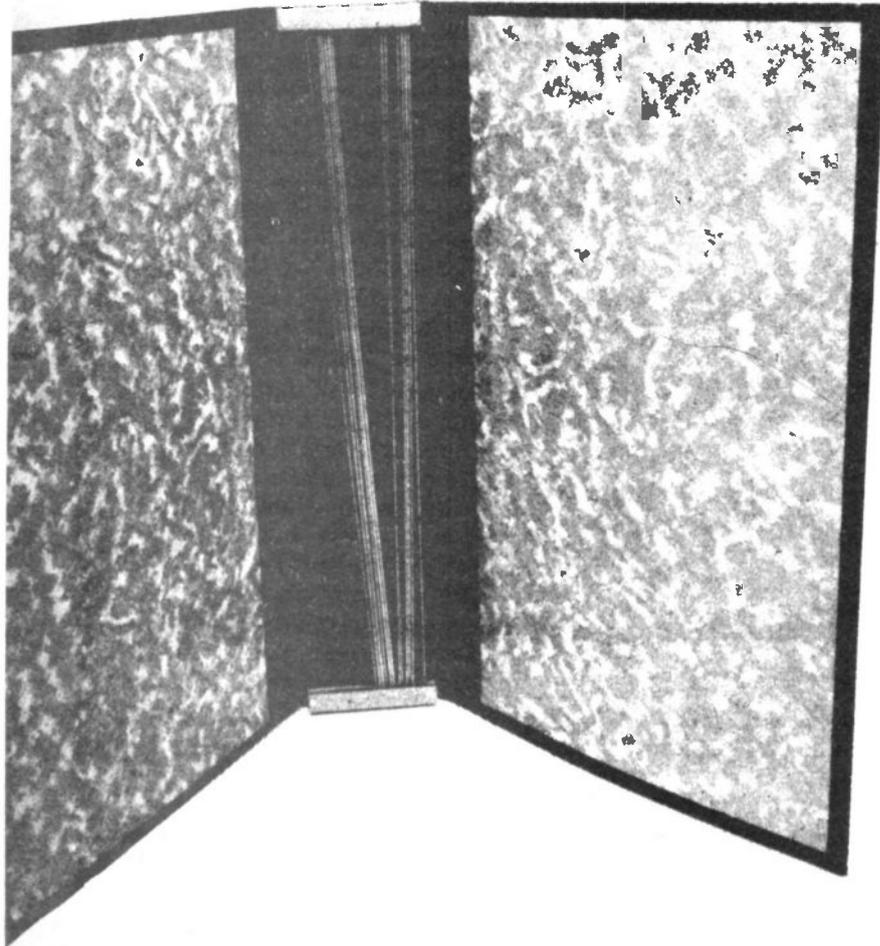SAVE £4.25 by receiving a FREE magazine binder when you subscribe to.....



It's true, by subscribing to *Ham Radio Today* you will not only receive your personal copy direct to your door for a whole year but also have a superb magazine binder in which to keep your copies AND IT'S FREE!
 All you have to do to receive your FREE binder is book a new subscription or renew an existing subscription to *Ham Radio Today*.
 What could be simpler? Normally priced at £4.25, these attractive binders will hold approximately 12 issues of *Ham Radio Today*.
 Not for you any longer the chore of having to track down dogeared copies of your favourite magazine, instead you will merely go to your bookshelf and they will be waiting for you in pristine condition. Don't miss out on this outstanding offer — subscribe today and receive your FREE binder within 14 days of your order being received.

SPECIAL OFFER

SUBSCRIPTION ORDER FORM

Cut out and send to:
 HAM RADIO TODAY,
 INFONET LTD,
 TIMES HOUSE,
 179 THE MARLOWES,
 HEMEL HEMPSTEAD,
 HERTS HP1 1BB

Please send my free binder and commence my personal subscription to HAM RADIO TODAY with the

..... issue

- SUBSCRIPTION RATES** (tick as appropriate)
- £14.00 for 12 issues UK
 - £14.45 for 12 issues Overseas Surface
 - £27.00 for 12 issues Overseas Air Mail

I am enclosing my (delete as necessary)
 Cheque/Postal Order/International Money
 Order for £.....
 (made payable to ASP Ltd)
 OR
 Debit my Access/Barclaycard*
 (*delete as necessary)
 Insert card no.



.....

Please use BLOCK CAPITALS and include post codes.

NAME (Mr/Mrs/Miss)

ADDRESS

.....

.....

..... POSTCODE

Signature

Date

BASICODE

for Radio Amateurs

In the autumn of 1983 the BBC began their first broadcasts of computer programmes to accompany their new 'Chip Shop' series. The unique feature of those transmis-

greater application of computer techniques in amateur radio.

In this article, I will be generally talking about BASICODE with the idea of transmissions taking place

grammes, there were the 'Chip Shop Takeaway' computer programme transmissions, which followed the shipping forecast on each Saturday, Sunday, Tuesday and Wednesday night. However, these nocturnal transmissions (which had an infuriating habit of not being broadcast at one specific time but whenever the shipping forecast had finished!) used the same system as the Dutch domestic service — NOS. They had been using BASICODE with considerable success, since January 1983 in the 'Hobbyscoop' programme, which went out every Sunday at 17:10 GMT (18:10 in the summer) on 747 kHz. This allowed a number of different computers to access the 'universal' program via a BASICODE translation program, which was specific to each machine.

There were three main problems with the 'Chip Shop' which gave BASICODE a somewhat inauspicious start in the UK; firstly, the demand for the translation program cassette was grossly underestimated which led to long delays; secondly, the program transmissions were far too late at night for most people; and thirdly, because the transmission times wandered about, it was impossible to use a timer to record the data if short C15 computer grade cassettes were used. Nevertheless, the series did serve to introduce BASICODE on a large scale and that in itself was worthwhile.

As for the origin of BASICODE itself, many technical advances have had their beginnings in the amateur radio world, and BASICODE is no exception. Its inventor was Klaas Robers, a Dutch radio amateur who was particularly interested in the possibility of exchanging and developing computer programs using a universal language which could be transmitted by radio. He formulated the original version with the help of a

If you've got a micro in the shack and don't know about BASICODE you've been missing out on a computer 'esperanto' which has a unique application for amateur radio. Dave Bobbett, G4IRQ, keys in.

sions was that they were transmitted in BASICODE, a sort of 'computer esperanto' which enabled virtually all machines to make use of the broadcast. Here, I will give an outline of the BASICODE system, and suggest ways in which radio amateurs can make use of it to extend the scope of our hobby.

Amateur Radio And Computing

With the level of computer-ownership being amongst the highest in the world, it is hardly surprising that amateurs in this country are more 'computerate' than most. Satellite prediction, automatic log-keeping, morse sending and decoding, RTTY, antenna steering (and playing space invaders!) are just a few of the many uses for a computer in the shack. However, there has always been one major draw-back with all this technology — one brand of machine couldn't 'talk' to another. For whilst it is true to say that certain computers can be used as RTTY terminals, and there are commercial programs available to get them to do this, such systems are not suitable for the interchange of computer programs on a direct 'load and run' basis. *Up until now it was not possible to transmit a program directly to another station's computer where it could be used straight away, unless it happened to be of the same type.* The use of BASICODE has overcome this problem and should allow much

on the VHF and UHF amateur bands using FM, so as to take advantage of both the inherently quieter nature of these frequencies and the 'capture effect' of FM.

The History Of BASICODE

Whilst in the UK there were one or two experiments with direct program transmission, initially using a Sinclair ZX81 in the BBC's 'Tomorrow's World' programme in 1982 and, more recently, using a BBC Micro in 'The Computer Programme', there was little activity in this area other than one or two computer 'shows' on Independent Local Radio, such as Radio West's in Bristol. These were all machine-specific, however, and of course for the ILR's, local! That was the state of play until the BBC launched its 'Chip Shop' programme in the Autumn of 1983 on Radio 4.

To complement the main pro-



group of computer enthusiasts in 1979, and this early version was later refined when Klaas got together with Jochem Herrman and produced BASICODE-2; this is the version which is currently in use.

What is BASICODE?

Before looking at BASICODE in more detail, it may be useful to briefly outline how computers record information on tape, and why compatibility problems exist. When computers store programs they do so by representing each character with a block of seven or eight 'bits' (we will use eight) — so for example the letter 'A' will be represented by '01000001', the letter 'B' by '01000010' and so on, with each character having its own unique sequence according to 'The American Standard Code for Information Interchange' (ASCII). If you listen to the noise of a computer tape, you will notice that there are two tones present; one of them representing the '0' and the other representing the '1'. It is by this form of AFSK (Audio Frequency Shift Keying) that each character which goes to make up the complete program is recorded. So, if '0' is a low tone and '1' is a high tone the letter 'A', (which is '01000001' in binary) would be recorded as: 'low-HIGH-low-low-low-low-low-HIGH'.

One of the sources of the compatibility problems between micros is that the tones used can be different. There are also various speeds at which the information is stored on tape, and, in order to save time, various command words which are used frequently are often saved in a form of a 'short-hand' which is specific to each computer. In a few instances, the ASCII code is not followed *at all*, and in most cases the codes from '0' to '31' are used for the various special features which each micro offers.

Having dealt with the encoding side of the problem, there is also the question of language compatibility, for, although most micros use BASIC, there are numerous versions or dialects of this language, which are again *machine-specific*. At first sight it would seem to be an impossible task to accommodate all the varia-

tions available, but BASICODE has succeeded in doing just this.

Using A Standard Format

To get over these problems, Klaas Robers and Hochem Herrman decided upon a standard tone and speed format which computers could be programmed to accept — 1200 Hz for the low tone (binary 0) and 2400 Hz for the high tone (binary 1), with data being sent at a speed of 1200 Baud in ASCII — a good bit faster than 50 Baud RTTY! Each character would be sent in the following format; 1 start bit — 8 character bits — 2 stop bits. The start bit (a binary 0) would indicate to the computer that a character was about to follow, the 8 character bits would define the



character, and the two stop bits (both binary 1's) would indicate that the end of the information for that character had been reached. The whole sequence of 11 bits is known as a 'byte', and every character is represented by one 'byte'. In this way, a stream of 'bytes' can be built up to represent one line of text, such as a BASIC program line; and if there is a sequence of such lines then you have a whole program!

So the first task of the BASICODE translation programme is to set up the computer in such a way that it can decode the standardised data format.

Developing A Standard Language

Having persuaded the computer to accept the incoming program in its special format, the next job is to translate the program from

BASICODE BASIC, into each computers version of BASIC — once this has been done, the universal program will be in a form which can be run immediately.

Fortunately, one thing which the vast majority of micro's have in common is that they use BASIC and so a large number of their commands, although executed in varying ways, have the same effect from one micro to another — for example, the command 'PRINT' varies little from one machine to the next. If each command is defined so as to fit the capabilities of the 'least able' micro, then a program using such commands is bound to work on all micro's in the group. Here the major advantage of BASICODE can be seen as also being its major deficiency, in that users are limited by the shortcomings of the less sophisticated machines. Given that computer capabilities are destined to dramatically improve with time, it follows that BASICODE will have to delete the more restricting micros from its repertoire so that the advantages of more advanced machines are not lost. However this is a difficult issue and depends upon exactly what applications are suitable for the 'Esperanto' approach to programming. Certainly, from the point of view of distributing the type of 'universal' programs which would be used in amateur radio, such restrictions are far outweighed by the obvious advantages of BASICODE.

Apart from the features which are common ground, there are also a number of commands which are non-standard but which must be used, such as 'clearing the screen' for example. BASICODE gets over this problem by setting aside all line numbers below 1000 to accommodate a series of sub-routines, which have the same overall effect on all machines. For example, the command to 'clear the screen and return the cursor to the top left-hand corner' (simply CLS on a BBC micro) is achieved by writing 'GOSUB 100' in BASICODE. The sub-routine at line 100 then contains whatever commands are needed by that particular micro to clear the screen and home the cursor. There are twelve of these sub-routines in all and can be used by calling the appropriate

'GOSUB xxx' — further details of these routines can be found in the manual which accompanies the BASICODE cassette. From the users point of view, it is very easy; just remember to use the simpler options with most commands, and to use the GOSUB routines to replace the twelve non-standard commands.

Which Computers Can Use It?

Like all good inventions, BASICODE is a simple idea — the computer is first loaded with the appropriate 'translation program' (so that it is set up ready to convert any incoming program into a format acceptable to the machine), and then the 'universal program' can be received, translated and used. As a result, all that is needed is the right 'translation programme' for your machine and any BASICODE program is accessible. Because this process takes place at high speed, there is very little delay before a program is 'up and running'. Currently, the following machines have translation programs available for them:

Apple I & IIE
Colour Genie
Commodore 3000, 4000, & 8000
Vic 20
Sinclair ZX-81
BBC Models A & B
Commodore 64
Pet 2001
Sharp MZ80A & MZ80K
TRS-80 /Videogenie

In addition to those listed, the Sinclair Spectrum should be supported by now, and I have also heard 'Hobbyscoop' transmitting a translation program for the Newbrain AD. For those machines which are not supported yet, there is an outline of the BASICODE protocol in the manual which should give the more 'computerate' amongst us enough information for them to write their own translation programs.

Why Use BASICODE?

Apart from the sheer fun element of experimenting with something a little different (we are supposed to be indulging in 'self-training' after all!), BASICODE allows radio amateurs to transmit

'live' information in the sense that a program will DO something when it is received, unlike other forms of data transmission which effectivley just 'sit there' on the paper. As well as being of direct interest to the stations involved, there are usually numerous people tuning around who would welcome the chance to experiment with what may almost be called a new mode — and for no outlay at all, assuming that they have a computer and a cassette machine handy.

On an individual basis, it would be quite easy to write a program to generate an animated QSL card with moving messages; not exactly pushing back the frontiers of human knowledge I admit, but at least it is a bit of a change from the inevitable 'you-are-five-and-nine-how's-the-weather' type of QSO! And on a more serious/sensible note, it would be ideal for RSGB newscasts which have to transmit data concerning satellite orbital parameters, special event callsigns and various other complex data. Wouldn't it be nice, for instance, to be able to look up propagation predictions which are clearly written down and only a day or two old? For that matter, it would be a perfectly feasible proposition for club newsletters to be transmitted direct to many members — five minutes of repeater time would reach a lot of people, providing that the powers that be could be persuaded that such transmissions were a good thing, of course! In addition, it would be a new field of interest for a group which I think we tend to forget about, the Short

Wave Listeners; a radio-related on-air computer forum with programs being transmitted to and fro would undoubtedly attract considerable interest, and I can see no reason why programs developed by SWL's could not be transmitted for them.

Get Typing!

As with conventional computing, the diversity of applications for BASICODE is only limited by the ingenuity of the users. Regulations (and propagation) permitting, it occurs to me that 10 Metres FM with its trans-Atlantic capabilities may offer further room for experimentation in the future. Whilst at first sight, SSB operation using data at 1200 Baud may seem out of the question, it could be interesting to see if a data SSB mode was viable. Given the stability of modern equipment this may not be such an impossible task.

As for the software used in BASICODE transmissions, a program's originator should always be acknowledged out of courtesy, unless otherwise requested. BASICODE was produced to encourage program exchange and development and so contributors are usually willing for their work to be used by all.

Although it should hardly need mentioning — amateur bands are (hopefully!) very public parts of the radio spectrum and commercial computer software manufacturers would be extremely 'unchuffed' to find that their latest pride and joy was gracing the airwaves as a 'test-program' from a ham station!

CQ Micro Net?

Next month's issue of HRT will see the launch of a brand new bi-monthly column which will be specifically aimed at those of us who are deviant enough to be interested in both radio and computing! The column, which will be called 'Micro Net', will be unique (as far as we know) in that most programs will be in BASICODE so that they can be used by the vast majority of computer users. In the meantime, if you are already a BASICODE user, we would be very interested in publishing not only details of any regular times

that you are on-the-air if you are licensed, but also any other information which may help others to get started. The column will be *strictly* radio orientated. We think there is considerable interest in a column of this kind — let the Editor have your views. Oh yes, and please *don't deluge him with programs!*

The BASICODE kit, containing a cassette of both translation and demonstration programs with an instruction manual detailing the BASICODE protocols, is available for £3.95p from: Broadcasting Support Services, PO Box 7, London W3 6XJ.



South Midlands

★ FREE FINANCE · 2 YEAR GUARANTEE

BRANCHES AT: SOUTHAMPTON, LEEDS, CHESTERFIELD,

YAESU FOR VHF EQUIPMENT — 'SMC' YOUR SUPPLIER

SUPERVENT SAVERS

FT290R & FT790R MULTIMODE



***432MHz PORTABLE SSB/CW/FM £259!**

FT690	Multimode Transceiver 6m	£259.00
FT290R	Multimode Transceiver	£279.00
FT790R*	Multimode Transceiver 70cm	£259.00
SMC2.2C	2.2Ah Nicads 'C' size	per set £21.80
SMC8C	220mA Charger (13A Style)	£9.20
MMB11	Mobile Mount	£28.19
CSC1A	Carrying case	£4.45
FL6010	6m 10W Amplifier	£49.00
FL2010	2m 10W Amplifier	£66.55



FT726R MULTIMODE UHF, VHF, HF



FT726R	Transceiver main frame only	£619.00
FT726R(2)	Transceiver c/w 2m	£775.00
21/24/28	HF module	£209.00
50/726	6m module	£195.00
430/726	70cms module	£259.00
SAT726	Full duplex module	£99.95
XF455MC	6000Hz CW filter	£41.85

SEVENTY CMS. SUPER SAVER

FT203R & FT703R HANDHELDS



"THUMBWHEEL" TINY HANDHELD

Ultra compact 65W x 34D x 153H mm, synthesised handheld. Computer aided design and component insertion (with chip capacitors and resistors) has produced this modern marvel: 2.5W RF (10.8V) (3.5W RF (12V)). It has VOX (for use with YH-2 lightweight headset, and built in 'S'/PO meter. Supplied with tone burst, helical and appropriate case.

FT203R	c/w FBA5, CSC6 etc.	£155.00
FT203R	c/w FNB3, CSC6 etc	£175.00
FT203R	c/w FB4, CSC7 etc	£185.00
FBA5	7.2/9V Cell case only (6 x AA)	£6.85
FNB3	10.8V NiCad Pack (425mAh)	£33.50
FNB4	12.0V NiCad Pack (500mAh)	£38.25
CSC6	Soft case (FBA5 or FNB3 fitting)	£6.00
CSC7	Soft case (FNB4 fitting)	£6.85
YH2	Headphone/Microphone option	£14.50
MH-12A 2b	Speaker/Microphone option	£17.89
MMB21	Mobile mounting bracket	£8.00
SMC8.9AA	Charger (slow) 13A style	£8.05
NC15	Charger (quick) and Power Unit	£49.95



FT230R & FT730R FM MOBILES



FT230R	2m Transceiver 25w	£269.00
FT730R*	70cm Transceiver 10w	£239.00
MMB15	Mobile mounting bracket	£14.85

S* SEVENTY CMS. SUPER SAVER

SUPER SAVER

FT208R SCANNING HANDHELD



KEYBOARD ENTRY SCANNING = L.C.D.

4 bit CPU provides: — ten memories, up-down manual tuning. Scanning of: memory, band or between limits (busy and clear), autoscan restart, ±600KHz and programmable repeater splits. Standard European Synthesiser steps of 12.5 and 25KHz. The keyboard also offers 16 tone D.T.M.F. tones and the unit is supplied with NiCad pack, helical and soft case.

FT208R	2M Handheld 2.5W	£209.00
SMC8.9AA	Charger (slow) 13A style	£8.05
NC7	Charger (base)	£34.65
NC8	Charger (quick) and Power Unit	£56.75
PA3	DC adaptor and charger	£16.00
FNB2	NiCad Battery Pack	£23.00
FBA2	Battery pack sleeve	£3.65
FLC5	Heavy duty case	£25.30
MMB10	Mobile bracket	£8.45



FM2033 FM MOBILE, 144 MHz



NEW £239

144 MHz 12VDC FM Transceiver. 25W/5W H/Low (both adjustable). Compact 2 2/16" x 6 3/16" x 7 3/16". 12 1/2 KHz steps (100 KHz fast QSY). Amber LCD 'Sunlight View'. Side 88. Display, 100's of Hz + channel number. Sensitivity <0.2µB for 12dB SINAD. Single knob frequency control "Dial". Endless or non endless dial options. RIT; 1 KHz steps V.F.O. + memory. Two 5 slot memories A, B, A+B, Z x B.

11th memory Instant "call" channel. Memory simplex or duplex channels. Band scanning programmable limits. Scan halts squelch + centre zero. Pause on scan halt for 3 seconds. Scan/Tune/RIT from microphone ±600 KHz split, plus cross memory. Repeater input listen — press "dial". Setable; steps, tone, splits, limits. Simple controls for safe mobile. CW mobile mount, mic, handbook.

SMC SERVICE
Free Securicor delivery on major equipment. Access and Barclaycard over the phone. Biggest Branch agent and dealer network. Securicor 'B' Service contract at £5.00. Biggest stockist of amateur equipment. Same day despatch wherever possible.

*** FREE FINANCE**
On many regular priced items SMC offers Free Finance for invoice balance over £120. 20% down and the balance over 6 months or 50% down and the balance over a year. You pay no more than the cash price!! details of eligible items available on request.

GUARANTEE
Importer warranty on Yaesu Musen products. Ably staffed and equipped Service Department. Daily contact with the Yaesu Musen factory. Tens of thousands of spares and test equipment. Twenty-five years of professional experience. 2 Year warranty on regular priced Yaesu products.

SMC STOCK CARRYING AGENTS WITH DEMONSTRATION FACILITIES

Neath John GW4FOI (0639) 52374 Day (0639) 2942 Eve

Bangor John G13KDR (0247) 455162

Stourbridge Andrew G4BJY (0384) 390916

Communications Ltd.

MAIN DISTRIBUTOR FACTORY BACKED

BUCKLEY, STOKE, GRIMSBY, JERSEY, EDINBURGH.



'YAESU' FOR H.F. EQUIPMENT — 'SMC' AT YOUR SERVICE

FT-ONE 'ULTIMATE' TRANSCEIVER



FT ONE	Transceiver HF All Mode.....	£1569.00
KEYT901	Curtis Keyer.....	£28.50
DCT1	DC Power Cable.....	£10.85
RAMT1	Non volatile memory.....	£14.49
FMUT1	FM unit.....	£44.99
XF8.9K*	Filter 300Hz or 600Hz or 6KHz each	£19.35

FT77 THE IDEAL MOBILE

↑100W. PEP
8 BAND HF
SSB/CW/FM
AM

£479!



FT77	8 Band Rx/Tx 100W output.....	£479.00
FT77S	8 Band Rx/Tx 10W output.....	£449.00
FP700	Matching AC PSU.....	£145.00
FC700	Matching antenna tuner.....	£103.85
FV700DM	Digital VFO unit.....	£209.00
MKT77	Marker unit.....	£10.85
FMUT77	FM unit.....	£28.55
AMUT77	AM unit.....	£24.00

SUPERB QUALITY

FT102 THE "WORKHORSE" BASE



FT102*	Transceiver 9 band.....	£719.00
SP102	External speaker.....	£55.00
FC102	Antenna coupler.....	£185.00
AMFMUT102	AM/FM unit option.....	£49.00

S* SUPER VALUE — VALVE FINALS

FT757GX THE BIGGEST SELLER

Every Item normally sold as an extra is provided as standard including AM and FM modes, a 600Hz narrow CW filter, lambdaic keyer with dot-dash memory, 25KHz marker generator, IF shift and width filters, effective noise blanker and AF speech processor... all at no extra charge.



FT757GX	Transceiver General Coverage Rx.....	£719.00
FC757AT	Automatic antenna tuner.....	£245.00
FP757GX	Switch mode PSU (50pc duty).....	£145.00
FP757HD	Heavy duty PSU (100pc duty).....	£179.00
FIF80	Computer interface for PC8001 NEC.....	£105.05
FIF65	Computer interface for Apple II.....	£54.05
FIF232C	Computer interface RS232C.....	£59.00

SUPERB QUALITY

FT980 "COMPUTER COMPATIBLE"



FT980	Transceiver General Coverage RX.....	£1329.00
SP980	Ext. speaker with audio filter.....	£61.55
XF455.8MCN	300Hz CW filter (455KHz 8 pole).....	£49.00
XF8.9HC	600Hz CW filter.....	£29.50
XF8.9GA	6 KHz AM filter.....	£29.50
FIF**	Computer Interface (see FT757GX units)	
D410004	Interconnect lead FT980-FC757AT.....	£26.99
TST980	Technical Supplement FT980.....	£8.50

FRG7700 COMMUNICATIONS RX



FRG7700	Receiver 0.15-30MHz AM/CW/SSB/FM.....	£385.00
FRG7700M	Receiver c/w 12 channel memory.....	£445.00
MEMG7700	Memory option.....	£75.00
FRT7700	Antenna tuner/switch.....	£48.25
FRA7700	Active antenna.....	£43.95
FF5	Low pass filter 500KHz.....	£11.25
FRV7700	VHF Convertors, 6 models.....	From £84.50-£94.25 each

SUPERB QUALITY

LEEDS
SMC (Leeds)
257 Otley Road
Leeds 16, Yorkshire
Leeds (0532) 782328
9-5.30 Mon-Sat

CHESTERFIELD
SMC (Jack Tweedy) Ltd
102 High Street
New Whittingdon, Chesterfield
Chesterfield (0246) 453340
9.5 Tues-Sat

BUCKLEY
SMC (TMP)
Unit 27, Pinfold Lane
Buckley, Clwyd
Buckley (0244) 549583
10-5.00 Tue-Fri
10-4.00 Sat

STOKE
SMC (Stoke)
76 High Street
Talkie Plts, Stoke
Kidsgrove (07816) 72844
9-5.30 Tues-Sat

GRIMSBY
SMC (Grimsby)
247A Freeman Street
Grimsby, Lincs
Grimsby (0472) 59388
9.30-5.30 Mon-Sat

JERSEY
SMC (Jersey)
1 Belmont Gardens
St. Helier, Jersey
Jersey (0534) 77067
9-6 p.m. Mon-Sat

EDINBURGH
SMC Scotcomm,
23 Morton Street
Edinburgh EH15 2HN
Tel: 031-657 2430
10-5 Tues-Fri, 9-4 Sat

HEAD OFFICE | S.M. HOUSE, RUMBRIDGE STREET, TOTTON, SOUTHAMPTON, SO4 4DP, ENGLAND,
& MAIL ORDER Tel: (+44) (0703) 867333, Telex: 477351 SMCOMM G, Telegram: "Aerial" Southampton

Belcom LS202E

2m FM/SSB Handheld – a realistic proposition?

Although many amateurs are quite content with FM only 'handy talkies' such as the Icom IC02E, the Yaesu FT203 and the Trio TR2500, there is undoubtedly a case for having a rig which also incorporates an SSB facility. Up to recent times, only Standard and Yaesu have offered 2m multimode portables with this facility, and

the rig into a stand incorporated into an accessory mobile linear. The right side cheek is blank, whilst on the back is a special clamp for a belt clip. And now I have to come to the first drawback – the most crowded and cramped top panel I have yet encountered on a handle-talkie. A BNC socket is provided for connecting the supplied rubber duck

wheels select MHz, hundreds of kHz and tens of kHz. Across the top, to the right of the BNC socket, is the rather cramped S meter, scaled in odd numbers only, which doubles as a battery indicator on transmit, and two concentrically-mounted pairs of controls. The first pair includes, on the bottom, a centre-indented receiver incremental tuning rotary adjustment which adjusts up to ± 1 kHz. Above this is the VXO control which changes the transmit and receive frequencies by up to ± 5 kHz. These two controls operate on SSB only. At the top right are concentrically mounted 'squelch' and audio gain controls, the squelch working on both FM and SSB, which is useful, and the audio gain incorporating the main on/off switch. Two different rechargeable battery

The Belcom 2m FM/SSB handheld offers facilities previously unavailable in a rig of its size. A brave effort undoubtably, but would the RF performance hold water? Angus McKenzie, G3OSS, took one into his shack...


both these rigs are definitely portables rather than handhelds. The Belcom LS202E would seem to be the first truly handheld multimode available and I was extremely keen to put the rig through its paces to see if it would be a useful asset. Before delving into its performance characteristics which, frankly, are rather depressing, let us have a look at its facilities and ergonomics.

The size, $165 \times 62 \times 40$ mm, and weighing about 500 grams, is typical of its FM only competition. The front panel is completely blank other than the loudspeaker/microphone at its top. The left side cheek includes a PTT lever, which was rather stiff and intermittent unless you held it down very firmly, 1750Hz tone on/off, high/low power switch and repeater shift, which is 600kHz up or down on transmit. There is also a small push button which controls a light inside the S meter so that it can be more easily read. At the bottom of this side cheek is the charging hole for interconnection with the charging adaptor. Underneath the rig are holes for locating and interfacing

antenna or for feeding external aerials. This BNC socket unfortunately does not stand up proud enough from the panel to allow some types of BNC plug to lock in position. We tried a standard BNC to N adaptor and this was incredibly tight on the socket.


In front of this socket are two miniature jacks for interconnecting an external speaker/mic. A little rubber cover is fitted with blobs that can push into these holes for protection from dirt.

Along the front are three deeply recessed thumb wheel switches which I found extremely awkward to use, particularly if you have stubby fingers like me! I found these so awkward that it took a considerable time to change frequency by a reasonable amount, and thus virtually impossible to use them for scanning rapidly across the band because of the deep recessing. To the right are three slide switches including the mode switch; this switch selecting either FM, USB or LSB. The second switch activates a noise blanker, whilst the third gives a 5kHz 'up' shift on both modes. The thumb

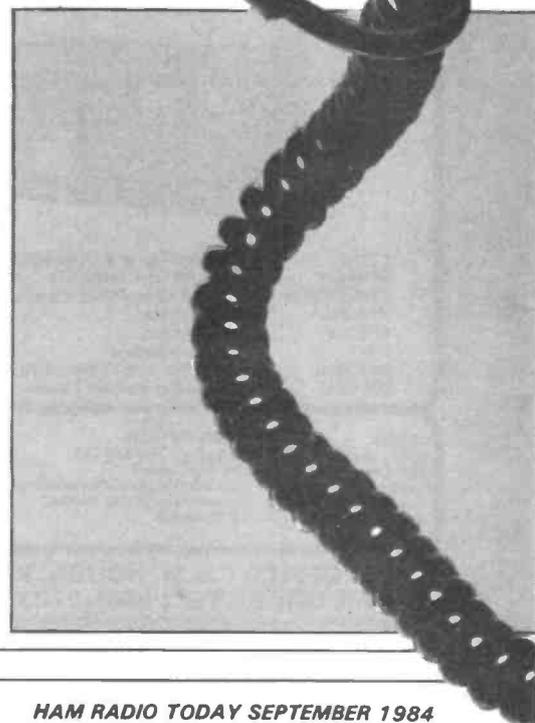

packs are available, the review sample being fitted with the quick-charging 7.2V version type NP6, a 10.8V rechargeable type NP9 also being available, which enable the LS202E to give a higher RF power (3.5W output is claimed with this). Four chargers are available, two types for each different voltage battery pack, allowing batteries to be charged from either mains or car battery. A speaker mic was supplied, type SH1, sensibly having separate sizes of jack for the PTT line and audio, which thus makes it impossible to fit them in the wrong way round. This unit had a belt clip on its back and was found easy to use, the quality being better than that from both the rig's internal speaker and microphone. The PTT lever was also much easier to use, having a longer throw than that on the LS202E itself and requiring only light pressure to engage it.

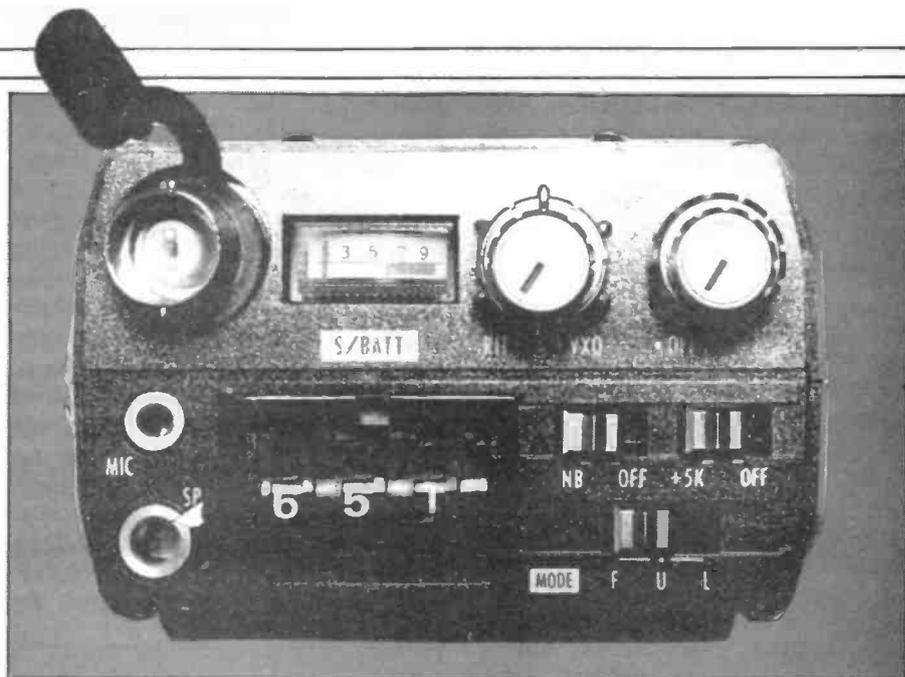Other optional accessories available include a soft case, a headset with



Top panel of the LS202E

built in VOX, a quarter wave whip, a mobile console with front speaker and mobile mount, and a 25W 2m linear amplifier.

The rig is amazingly compact and I consider it a great shame that some of the top panel functions were not positioned on the right side cheek, or the back, in order to facilitate simpler frequency changing. It was easy to hold and seemed fairly well made although perhaps rather 'plasticky'.

The received signal from the antenna passes through a low pass filter and is then amplified at RF before being fed through a band pass filter, a 3SK114Y dual gate FET being the amplifying device. The signal then mixes in a single transistor type 2SC2786L to the

first IF of 10.695MHz, which incorporates a switchable crystal filter. The first IF is mixed down by the crystal controlled second local oscillator in an integrated circuit mixer to the second IF of 455kHz. The signal passes into two filters and then onto a limiter and quadrature detector, incorporating active filtering and the squelch circuit. For SSB, the 10.695 MHz IF is fed through a crystal filter, and, after amplification, is fed to a conventional product detector working at this higher IF frequency. The audio output circuit is a simple IC, giving an audio output power claimed to be more than 400mW into 8 ohms for 10% distortion.

The microphone circuit output is split into two paths: SSB and FM. There appears to be no internal SSB mic gain preset (which explains some of the problems I encountered and which will be explained shortly) whilst, on FM, there only appears to be a deviation preset. This results in the microphone gain being completely fixed which is not a good thing.

The SSB audio signal feeds into an integrated circuit double-balanced modulator followed by a crystal filter which eliminates the unwanted side band. This signal is mixed up to the final frequency fairly conventionally and then amplified by several stages. Frequency modulation is achieved by modulating the VCO. The phase-lock-loop synthesiser is too complex to describe here and includes a 10.24 MHz reference crystal with



division, multiplying up again with phase locking, and mixing in with the VCO, and thence up to final frequency.


Subjective Performance

I first tried out this rig on FM and found the sensitivity to be rather poorer than I might have expected. This was briefly checked in the lab to be -120dBm ($0.22\mu\text{V}$) pd for 13dB sinad. This is around 4dB deafer than most of the competition. I have already had a moan about the poor tuning ergonomics but after sorting this out, the first problem I encountered was the very limited reproduced audio output available on receive. This clipped very severely if it was turned up slightly too much. I cannot see how this rig could, say, be used sensibly in a car where the background noise can be quite high. If used at a rally, or for Raynet exercises, the lack of reproduced volume could be a severe handicap, although in an average quiet shack it might be just about adequate. The selectivity seemed adequate and the squelch worked very well. We found it possible to receive frequencies right across the band from 140 to 150MHz, which was a little surprising. It was a pity that the VXO facility had not been designed to permit adequate tuning in of adjacent 12.5kHz spaced stations.

When I first used the transmitter on FM on the local North London Raynet channel, a station came up saying "QRZ, your modulation is very distorted, please try again!" Somewhat taken aback by this, I retreated away from the rig about 12 inches and tried again, to be told that that was much better but rather thin and poor. At least I had achieved readability 5, but accompanied by the reverberation in my shack which could clearly be heard due to excessive and non-variable gain. Several stations reported that if I went closer than 6 inches or so, the modulation quality deteriorated badly. The quality was thought to be worse than that of any other handie-talkie that I had tried in the last year or so.

Giving up FM, I switched to SSB and tried calling on the calling channel for a considerable time. Eventually a station came back and

stated that whoever it was calling was unreadable, but whose 'voice' bore slight characteristics which might be attributed to G3OSS! I tried again, only to receive a report of readability 3 and strength 9. At this point, I thought it a good idea to read the instruction book, which explained clearly that the recommended speaking distance was around 4 inches. I had been using around 2 inches, so I backed off and QSY'd. Stations then gave me just about readability 5, although everyone said that the modulation was of the type that I am always grumbling about when other stations produce it on the band. By

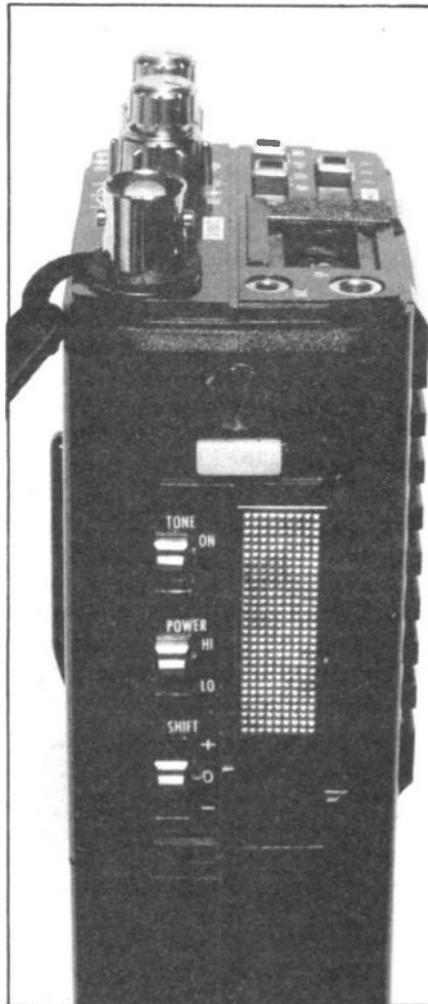

Sideways on

now, I was getting rather embarrassed, so I tried backing off to around 8 inches, which gave considerably improved results. The modulation was then rather thin but fully readable and the distortion was acceptable. The quality, though, was way short of any reasonable SSB rig, and very far short of a model such as the

IC202S, or FT290 (provided the latter was fitted with the PA mod which increases the standing current).

When receiving SSB I was struck by the deafness of the RF input and the lack of IF gain. As the available maximum audio output power was severely limited, I had to bring the audio gain control up and down almost like a yoyo in between different stations' overs in a net — in order to avoid overloading when a strong signal was received, as compared with almost inaudibility for a weak signal. The AGC also appeared to be rather poor, and there seemed to be a complete lack of any punch in the reproduced audio. It was found practically impossible to use the rig for tuning up and down the SSB section, for this took an age. The VXO facility on SSB was useful in getting the voice pitch correct on receive. The rig excludes any CW facility, which is a pity, for this would not have cost much to put in.

We did take just a few lab measurements, although the Editor agreed that extensive ones were not really justified in this particular case as the rig was somewhat disappointing. On FM, the output power was 2W high, and 125mW low power. We had a quick look on the spectrum analyser, and could see no second or third harmonic outputs above the noise floor at -65dB . We did not note any spuri, but did not really have much time to look close in. The FM deviation peaked at just under 5kHz which is about right, but this was reached all too readily, confirming that the microphone was too sensitive. We checked the audio output power for 10% total harmonic distortion, and the rig only achieved 370mW into 8 ohms.

The rig was able to transmit from 144 to 148 MHz and, in passing, thus conflicts unfortunately with the new British Telecomm's Act requirements. To end this section on a high note, the transmitted frequency accuracy was phenomenally good.

Final Thoughts

Belcom's concept in this rig is clearly an excellent one, but what seems to have gone badly wrong is the extra touches in design required



what competition occurs. Otherwise, my advice would be to look again at the FT 290 and the Standard alternatives, and only consider the Belcom if these are too bulky for you.

Finally, I would like to thank Lowe Electronics for supplying the rig for review, and especially for the helpful way in which they listened to my criticisms which were acknowledged fairly and with complete integrity. This rig had so much promise in advance, and it is such a shame that I have been so disappointed with it, but such is life. Maybe some users will get a lot of fun out of it, but I hope they will remember to keep well back when they are talking into it.

Since the writing of this review, Lowe Electronics have informed HRT that at their instigation, the SSB transmit gain of the LS202E has been reduced so that talking into the transceiver from a distance of 1/2 inches produces full audio *without distortion*, thus rectifying one of Angus's main criticisms. Try one if you are interested and see what you think. G3ZZD

for the rig to give good transmitted and receive quality. I have to criticise very severely the lack of any SSB internal mic gain pre-set, but, perhaps the problem could be partly due to a lack of adequate carrier level into the double balanced modulator, which could then cope with a wide variation of audio levels from the mic amp. If the AGC characteristics had been good at IF, then varying speech levels into the microphone could have been accommodated without the severe distortion problem. On FM the same lack of a mic gain control means that the rig will pick up a lot of the noise that may be present in the vicinity of the user. This could

affect readability in noisy environments. Apart from this, the inefficient loudspeaker, (the speaker mic also suffers in this respect), must be criticised, for 370mW should give a louder sound than this rig gives. Perhaps the most awkward feature of the LS202E, however, is the recessed thumb wheel frequency switches. On balance, it is only fair to point out that the rig is very reasonably priced, and if you are attracted to it because of its facilities, I consider it essential for you to try one out first and then make your mind up. Perhaps another manufacturer will bring out a better model soon; I think it is worth waiting to see

RSGB BOOKS



A GUIDE TO AMATEUR RADIO
Written by Pat Hawker G3VA, this book introduces amateur radio to the newcomer. It bridges the gap between elementary principals of radio and electronics and understanding the complex equipment often used on the amateur bands. Buying this book will be your first sound step into the world of amateur radio. Price £3.44

RADIO AMATEURS' EXAMINATION MANUAL

This is the course text book for anyone sitting or intending to sit the radio amateurs examination. It contains all the information necessary for you to pass the RAE. The subject is treated briefly and is based on the 1982-85 syllabus of the RAE. Its an excellent introduction to the theory of radio.

Price £3.42



AMATEUR RADIO OPERATING MANUAL

Covering essential operating techniques, all radio amateurs and shortwave listeners will find something in this book to enhance their enjoyment of the hobby. The book will help improve your operating technique and offers friendly advice on how to avoid bad operating practices. Price £5.22

Price £5.22

OTHER RSGB PUBLICATIONS

Amateur Radio Awards.....	£3.41
HF Antennas for All Locations.....	£6.91
Microwave Newsletter Technical Collection.....	£6.83
Morse Code for the Radio Amateur.....	£1.31
RSGB Amateur Radio Call Book 1984 Edn.....	£7.14
Radio Communication Handbook (Vols 1 & 2).....	£10.91
Teletypewriter Handbook (2nd edn).....	£13.84
Television Interference Manual (2nd edn).....	£2.13
VHF/UHF Manual (4th edn).....	£10.31
Meteor Scatter Data.....	£3.24

Logbooks	
Amateur Radio Logbook.....	£2.77
Mobile Log Book.....	£1.14
Receiving Station Logbook.....	£2.72

Maps	
Great Circle DX Map (wall).....	£2.12
IARU QTH Locator Map of Europe (wall).....	£1.43
QTH Locator Map of Western Europe (wall).....	£1.43
World Prefix Map in full colour (wall).....	£2.17

Other Items	
RSGB morse cassette Stage 1 (up to 5 w.p.m.).....	£3.84
DX Edge (HF propagation prediction aid).....	£13.98

New Non-RSGB books
The Complete DXer by Bob Locher, W9KNI
Many secrets of successful Dxing are explained in this book. Written in story-book style, its sure to become an important accessory in the rising DXer's shack ... £7.77

The RSGB is the national society representing the UK radio amateurs. Membership is open to all interested in the hobby, including listeners. The Society publishes a range of books, log books and maps for the radio amateur. A large selection of other radio and electronics books are also stocked. Contact the membership services section for more information about amateur radio, the RSGB and a full list of publications. All items advertised here include postage and packing and are available at reduced prices for personal callers. All publications are sold to members at discounted prices. Please allow up to 28 days for delivery.



RSGB Publications
Cranborne Road, Potters Bar,
Hertfordshire EN6 3JW

VHF CONTESTING

The Editor has asked me to write an exposition on the running of a VHF contest station. He was kind enough to say that he thought I was well qualified to do this, on the strength of a talk I gave many years ago to the radio club he belonged to.

For my part, I feel the only qualification I have to write such an article is that I have twisted the odd arm, and otherwise conned some of Hastings locals into a VHF contest group, and we have par-

ticular contest. This has been recognised, and the event has been reinstated this year. So, I am saying nothing about how to run a VHF contest, and will concentrate solely on organising an entry.

I would also like to emphasise at this point that the ideas I am putting forward are by no means unique or original, and only represent my way of doing things. I would not presume to dictate how to do it, and will merely suggest a framework that seems to give

in general.

So, for a start, **why contests??**

- a. To test the ability of a group or an individual to make effective communication.
- b. To "improve the breed." Contest operation, in the pouring rain (or sunshine) brings people together under conditions of adversity — variable food supply, a lack of soft beds and a minimum of equipment sorts out the men and women from the boys and girls.
- c. To enable a contestant to measure his effectiveness against the rest.
- d. To demonstrate to Authority that there is an occasional full use of the limited bandspace afforded to the Amateur Radio Movement.
- e. To assist non-contestants in not-so-good locations in contacting stations in some rare locations — which are normally out of their range due to the scarcity of well-placed fixed operation in those locations.
- f. It's fun!
- g. To do well is good for the ego!

What are the necessary qualities required to do well?

- a. Technical ability.
- b. Organising ability.
- c. Operating skill.
- d. Application.
- e. Persistence in maintaining the aim.

So much for that. Now read the rules of the contest you wish to enter. Now read them again. They are, in my view, often unnecessarily complex. However, make sure *exactly* what is meant, then you


John Ridd, G8BQX, a successful participant in VHF contests with the Hastings ERC since the early seventies, looks keenly at the requirements of VHF contesting today.

ticipated, mainly on 2 metres, since 1969. We have had the occasional success, and there are several certificates on the wall of the club shack. We won the RSGB 2m September contest one year when for some inexplicable reason, the conditions favoured us to the exclusion of the rest of the UK.

I did, for my pains, organise a contest, at very short notice, last year, to compensate for the strange omission of a regular 2 metre event, after it had previously been advertised! However, this was the exception that proves the rule that I hold dear, to the effect that the RSGB is the sole body in the UK that has the cause and the authority to run contests (*Hmm — Editor*). The one I organised was to indicate that there was a need for this par-

some chance of an effective contest entry. Apologies in advance are given for any failures or inconsistencies, for this is the first article that I have written for a national periodical. Apologies are also rendered for my (occasional) execrable misuse of the English language. You may find a certain bluntness in my prose, to the point perhaps of being obnoxious, when you come to my particular 'hobby horses', but there are some detrimental things that I feel need to be said about VHF contesting today.

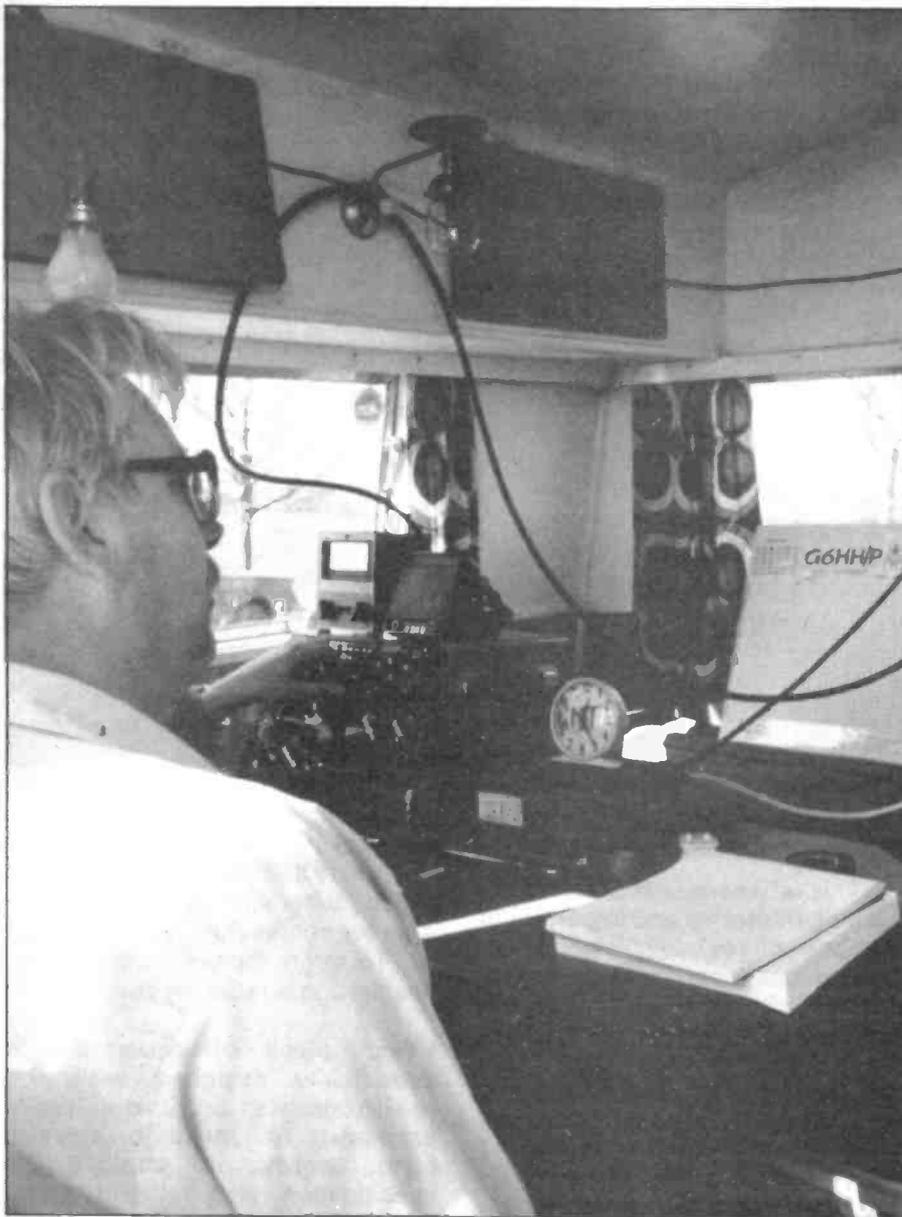Many of the points about "improving the breed" refer equally to non-contest VHF operation, and it is to be hoped that these points will assist in the improvement of technical and operating standards



G8BQX himself, giving the Hastings ERC 2m station a pre-contest checkover

can start planning your effort on a sound basis. Don't forget to write away for the LSVHF log sheets, the 427 forms, and the 4422 forms for RSGB contests.

Technical Ability

Equipment ought to be first class, especially if the contest site is near to a centre of high activity. The transmitter must give as 'clean' a signal as possible, of as high a power as possible, within the permitted level. The only reason for using high power is to keep up with the general contest rat-race. The contest group I'm involved with had just about got it together with 25 watts of AM when the opposition went SSB. That was no problem for us. A VFO

of sufficient stability enabled us to keep up and mix it with the SSB gang, the majority of whom did not cotton on that we were using AM. The average distance of the contacts we made was no worse than now. We finally had to go SSB when the trend was more and more power, when techniques, in the opinion of some, came secondary to brute force. Certainly, we get more contacts now, but the number of participating stations has also increased considerably. As has the level of unwanted rubbish — due to the high power run by people with untameable equipment. It is to be hoped that my effusions here will result in stations like G3 (expletive deleted) and that noncompeep G8(ouch!) getting their equipment sorted out!

Preferably with a 14 lb. hammer (or the metric equivalent.)

Even so, there is every reason for a new station embarking on a contest career to have a go with modest power for a start. Progressive improvement towards the top of the list is the thing to *aim* for.

The receiver used must be able to work efficiently in the presence of many strong signals. Superb rejection of unwanted signals is even more important than absolute maximum sensitivity. As an illustration, try putting half a dozen pre-amplifiers in series in your aerial lead. You will get super sensitivity. You will be able to (metaphorically) hear a chap striking a match a hundred miles away, but, with strong local signals on the band, your receiver will be completely blocked with mixtures of all the signals around — 'wall to wall' as they say on the HF bands.

Strong Signals!

Signal levels as high as 100 millivolts can be present at the aerial socket of your receiver from just one line-of-sight station. Such a signal strength is enough to make an in-line power meter indicate when you are receiving! 100 millivolts in 50 ohms corresponds to an S meter reading of S9 + 63dB. 100 dB down on this is about S2. So, with a receiver with 100 dB spurious rejection, spurious S2 signals will be found *all over the band*. Even more spurii will be found when there are several strong but clean transmissions in progress. With transmissions of this order of strength 'clean' only down to 100 dB there will be a lot more spurii apparent on your receiver. Imagine trying to work a really weak S1 signal in a constant spurious level which can approach S3 to S4 on a busy band.

Ideally, transmitter and receiver spurii should be 120 dB down, practically impossible, but an ideal to be aimed at. The local oscillator of an unmodified FT225 is only 'clean' down to about 90 dB. Changing the mixer to a double balanced passive mixer results in some improvement since the oscillator noise sidebands tend to balance out, and the intercept point is adequate, but, even so, the oscillator cleanliness still really needs improving, especially since

that same oscillator is used for transmission!

A professional spectrum analyser costing about 5 kiloquid is only quoted as having oscillator noise sidebands of -70 dB, so you can see that serious contest gear must be several orders better than professional VHF gear! Especially so, since we use high power and high gain aerials, with signals close together, whereas professionals use relatively low gain aerials, low power, and a wide frequency spacing between adjacent transmissions. Life is difficult! However, we do get some assistance from the (hopefully) good back-to-front ratios and sidelobe nulls of our aerials, but, if there is a high powered station situated in the direction you want to point — you have problems!

'Clean' Gear Is Essential

It behoves us all to get our gear as clean as possible. No wonder most contest reports are S9!

Now, what about the isolated VHFer, living in an isolated valley far from normal centres of high VHF activity. He has naturally specialised in getting very high RF gain so that he can hear the distant stations. Along comes a contest station, on the local hilltop, running the full permitted power, and line-of-sight to our chap. He switches on, hoping to work a few new ones, and finds his receiver absolutely full of funny noise every time the contest station sends. He is aggrieved, naturally. Bang goes his chance of working a few new 'Squares'. But whose fault is it?? Suppose the contest station halves his power. The received level is 3 dB down, but the effect of this on the swamped receiver is minimal. The contest station halves his power again. The received level is now 6 dB down. 1 S point! The contest station now reduces power again — now 25 W p.e.p. — result 2 'S' points down. And the poor old receiver is still swamped, because a transmit power reduction of 12 dB can do nothing much to help a receiver with up to 30 dB of pre-mixer gain. With an active mixer, as found in most bog-standard VHF transceiver front-ends, there is *no* chance of much improvement, due to an unsatisfactory intercept point (see *Radio Communication*, March 1984).



HERC in contest action. From LHS, G4 KNU, G4 KNU, G4 FET, G4 RIT

Could Do Better!

This is where I take issue with the manufacturers and importers of 'bamboo boxes', available at inflated prices (cost as much here in numbers of pounds as they cost in numbers of dollars in the States!) For the last ten years I feel there has been no basic improvement in transceiver front-ends. We still have the very unsound line-up of FET RF amp. into FET active mixer. One rig even has the temerity to include *an extra preamp!* This must be about the potentially worst possible line-up for spurious responses there is. Everytime I see new 'improved' transceivers advertised, I find it funny how the adverts only deal with what are essentially ancillaries, but keep a graveyard hush about the RF things that really matter! More bells and whistles on the front panel (and the back, as well, for some completely anti-ergonomic reason.) Memories, multi VFOs — every possible lily-gilding accessory you can think of. The important part — the communication line-up, there seems essentially no improvement in whatsoever. An active mixer means far too much RF gain is necessary in order to drown the mixer noise.

And now we have the ultimate lunacy. You have an 'improved' im-

ported transceiver, which has to be modified to include a proper front-end (bully for muTek) *at your expense*, before it is any good RF wise for contesting. Words fail me!

To quote from a recent advertisement in a radio magazine.

"Each piece of equipment is specifically designed with the requirements of.....the radio amateur in mind.....always been.....policy.....to improve the specification and reliability.....by listening to the valuable comments of radio amateurs....."

Right, Honourable Sirs, listen to this. If you can produce a transceiver with a proper double balanced passive receive mixer, with an adequate intercept point, an oscillator chain with noise sidebands down below 110 dB, and similarly, transmitter spuri down 110 dB, I will definitely consider acquiring one. You can reduce the number of noise-inducing digital displays, and the various auxiliary bells and whistles, to pay for it, by all means!

Plenty of Iron

The aerial should be the largest attainable. The best and most linear amplifier, both up and down, is the ironwork in the sky. Four big yagis,



in a square, at optimum spacing, will give about 18 dBd. After this, the next step, 8 yagis(!), will give theoretically another 3 dB making 21 dB in total. The law of diminishing returns comes in, because another 3 dB gain will require 16 yagis, which is definitely a bit much! And don't forget the array should have good front-to-back ratio and minimum sidelobes, for the ability to null out the unwanted is probably just as important as the forward gain. The next step the Hasting's Contest Group is contemplating is to have another medium gain aerial, switched by a footswitch controlled relay and set at 90 degrees azimuth to the main array, to cater for the types who will call from middle distances just after we have swung the beam!

Aerial height depends ultimately on the local terrain. Clearance of nearby surrounding objects (including hills!) is the important factor. Heights above 100 ft start showing a diminishing return because of feeder losses (and cost!)

Adequate Power!

The power supply for the station must be adequate. Ideally, there should be enough reserve current capacity to ensure that the voltage available does not 'droop'

under load conditions, for serious variation can lead to distortion in power amplifiers, which will adversely affect signal quality. Illumination may be needed at the generator, for fuel refilling in the dark. A card should be displayed at the operating position, setting out definite times for refuelling — with space for the signature of the person who refills. Woe betide the one who neglects! Re-priming a diesel can be a swine!

A little tip to assist refuelling. An electric petrol pump plus float chamber (ex-Mini, perhaps) with a supply pipe into the bottom of the existing fuel tank, will enable the genny automatically to be topped up from a larger container, jerrican or similar, will obviate the danger of letting the 'genny' run dry — and will also keep the operators dry if the weather is inclement. Don't feed the electric pump straight into the carburettor — the float needle of a gravity feed machine won't cope with the fuel pressure and the machine will flood.

Getting A Contest Site

Local landowners, particularly local authorities, will be found to be most accommodating once you have sold them the idea of harmless VHF Contesting. It isn't necessary to travel miles to a contest site. There are usually quite adequate locations available almost everywhere and a good height above sea level is not everything. It takes a little reconnaissance to find sites but they are there often close at hand. My own group's site is in the adjacent small QTH square to our headquarters and the next best site locally is less than a kilometre from the clubroom. Our usual site is only 174 metres ASL but is superb for VHF propagation.

Equipment Finale

Above all, *all* the equipment must be *reliable*, and capable of going for 24 hours without failure. In saying this, I realise I am asking a lot but this is vital. Strict attention and consideration of correct engineering method, particularly interconnections between equipment, is all important. No twisted wires and tapes joints are to be contemplated. All must be secure,

with proper lockable plugs and sockets between items.

Last, but not least, think on the accommodation for operators. I well remember visiting one 'contest station'. The operators were sitting on the ground inside a tent. A frying pan of congealed bacon was sitting on top of the rig. The torch battery had failed. Blankets and other clutter all over the place. A leaking 12 V battery was on a sleeping bag. The irony was that these lads had organised a £10,000 public liability insurance, at the landowner's behest, and had travelled some sixty miles to their site! The operating techniques were as jaded as the operators looked!

Separate sleeping accommodation, *way out of earshot of the operations*, is the first requirement. Comfort for the duty operators is the next. Then, reliable lighting, and warmth, for resting and duty operators, in the winter. A proper table and chairs. All equipment "to hand." Food (cooked somewhere away from the operating position. Booze — for voice lubrication only. No distraction for the operators. And so on. All this may *seem* obvious but needs thought beforehand.

And a final word, the contest group I mentioned earlier were using a Liner 2 — *unmodified*. They never went out contesting again; the aforementioned facilities to one side, it is easy to understand why. They were giving a nearby high power station some trouble with spurious transmission from their Liner 2. But they were getting it back in spades — 100 dB stronger. The poor fellows didn't need to tune the rig — that same station was everywhere round the dial. Unfortunately, they had neglected to try out their rig with a good aerial near strong activity at their home location.

Forethought. Rigorous testing. Planning. That's what's required. Which leads to the next consideration:

Organising Ability

Any club has the ability to assemble an adequate contest station. HF is probably easier than VHF in this regard, but, even so, it must be rare to find a group who cannot get together a workable VHF station. And the more remote

a group, the less worried they have to be about spurious responses in Rx and Tx; providing their contest venue is not frequented by one of the 'tiger' groups on contest day, gear can be that much more elementary and bog-standard 'off-the-shelf'. Any group *must*, if they put themselves to a little trouble, be able to scrape together a Tx/Rx, a pair of 8 ele yagis plus a combining unit, a 30-40 ft mast and a power source, either 250 V AC generator, or some 12 V accumulators plus a means of floating them with a generator. This latter can consist of an old lawn-mower engine, belt driving a car dynamo plus control box, or else a car alternator. Accommodation requirements are a couple of tents, one for kipping in and one for operating, a table, a couple of chairs, and some reliable lighting. Don't forget a clock — not one relying upon 50 Hz for accuracy!

What is *not* required is a transceiver over-driving a cheap transistor linear amplifier and 'whiskering' up the band in an area well-populated with contest stations. This situation is, to a certain extent, self-limiting, since a bad rig operating in the home location in a well-populated area will soon be sorted out by a self-respecting owner, with the assistance of his concerned(!) locals. There is a wealth of assistance available around, especially at your local club — use it! However, if a chap has no self-respect in this regard, and persists in wallowing in his own self-inflicted electronic grottness there is no way will others assist him — on contests or otherwise!


The organiser should assemble together all the gear to be used at some convenient time a few weeks before the contest, and the whole lot should be rigorously tested under simulated contest conditions for as many hours as possible. Efficiency is not the only fact to be checked: reliability and endurance are of paramount importance. One would expect to choose one source for the Tx/Rx plus linear amplifier (if any), for problems can occur 'marrying up' different combinations, in particular with regard to drive levels between transceivers and amplifiers. Just because the specification in the transceiver handbook says "ten watts out," and the label on the amplifier says

"ten watts in for 100 watts out" does *not* mean they may be connected together with any guarantee of the right output of the right cleanliness. You must test things out and see. Very often you will find that 4 watts in is enough for the amplifier! A linear amplifier should not be 'driven', it is gently led! The assistance of local fixed stations, who can assess the quality of the signal from the station, is very helpful to finally check things out.

The ability of the prime mover power source to supply the station

to nominate a supremo (if I can't be captain, you can't use my football!) If the load is too heavy, put one person in charge of the equipment, and another in charge of the operating rota. People to choose are those who can inspire confidence (or can thump the hardest — the table or anything or someone as required.) They must remember an old military maxim — "delegation is the art of command."

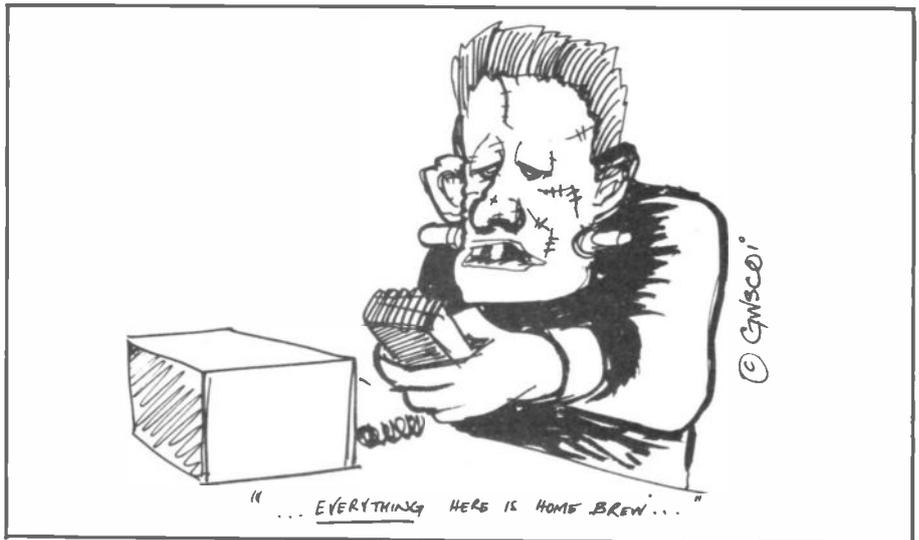Prepare lists: check off each item as it is to hand. Another military maxim: "time spent in reconnaissance is seldom wasted."



reliably requires to be tested. Nothing more frustrating than a 'genny' which packs up after six hours, and will not start when hot! It happens!

The location for the tests need not be the contest site; all that is needed is some small patch of ground which is line-of-sight with the co-operating fixed stations. The aerial installation needs a certain amount of checking to ensure that all the necessary guys are there, that the aerials match the feeder, that the top end preamp is reliable under strong signals, and that all know how to put the thing up, for the aerial arrangements usually take the most time to set up on contest day. As the generator is to be sited as far as possible from the operating and sleeping tents, check that there is no unacceptable voltage drop in the supply leads to the gear. For safety, an earth leakage trip, preferably of the unbalance detector type, should be used with a 250 V AC system of power generation.

The best way of organising is

Similarly time and care in preparation pay dividends in efficacy of the final result.

Operating Skill

What makes a good operator??

- a. The ability to write and talk into a microphone at the same time.
- b. The ability to identify the really valuable weak distant station from among all the importunate middle-distancers.
- c. The ability to instill good order and discipline on a frequency when faced with a multiplicity of callers, some of whom will, either through cussedness or through interference at the wrong moment, insist on calling whilst a contact is in progress.
- d. The knack of reading weak stations *underneath* the noise: I sometimes think this is inborn rather than learnt. In connexion with this, I believe the over-frequent use of the FM mode is the kiss-of-death when it comes to reading weak SSB.

Too many newcomers seem to adhere to the FM channels instead of getting in there with weak SSB contacts and thus training themselves to comprehend low level distorted speech in high noise levels — which is essential for contest operation!

- e. The ability to exude confidence and the feeling that a contact with your station is a good thing towards the often diffident people hearing your calls. (As a local once said, "You *WILL* contact us....it's good for you !!) This is connected with....
- f. The ability to transmit good feeling, fellowship, and good humour towards correspondents, even when the going is tough. In other words, to be *positive* in a contact, and *not* giving the impression it's a bore!
- g. The ability to pronounce and project one's voice properly — none of this diffident muttering so redolent of the FM channels. Proper pronunciation obviates the use of "speech processors" — properly called "speech distorters" — we don't use such foul devices. The old Service mnemonic for speech transmitting RSVP — RHYTHM, SPEED, VOLUME, PITCH, is much better than a processor when applied well.

Which would YOU prefer to work, given equal contact value? The mutterer? The mumblor?? The one who pronounces clearly??? Actually, *all* of them; we want to work the station who is just casually tuning around on the off-chance, as well as all the other testers. And I am sure that the casual tuner would rather work the positive, clear, easily read, forthright, *interesting sounding* station rather than the wishy-washy, diffident, apparently back-of-the-mike, offhand, unconfident type of caller.

- h. The ability to be patient, helpful, kindly, and of assistance to the new operator when in contact. It is most putting-off to the new licensee if his correspondent appears to be contemptuous, down-putting, hurried, and off-hand,

just because the new chap isn't that far away and is obviously new to the game. Any of my operators who behaved in such a fashion would soon get a fat ear'ole! Paul M. Segal's "The Amateurs Code" is required reading for all contest operators for guidance in all the aforementioned aspects.

- i. To have stamina — to be able to press on with the traffic right to the end of one's stay on the mike.

Application

The station which presses on calling — even in the middle of the night when it seems hopeless to raise new contacts — who keeps the pressure on, even when others give up — that is the station who gets the most contacts. Sweat is proportional to success. There are stations of equal excellence and capability in most parts of the country who will win if the propagation favours them. The one who pushes hardest wins!


Maintenance of the Aim

Finally, for this month, another good old military maxim. The contest is not over until the log is in the post to the adjudicator. How easy it is to relax, having worked a good bit of DX. That's no good. One has to keep hammer, hammer, hammer, all time until the job is done. It's all too easily for those all-important post-contest fourteen days to go by. Lots of stations who are heard to do well during the contest don't even appear in the results! It surely is a daunting task to bash out a log with 700-800 contact in it or more, but no more daunting than writing an exposition like this. *Must* be done if the other members of the group are not to be let down. All that effort they put in for nothing? No fear!

Snatching defeat from the jaws of victory???

Next month — the practicalities and actualities

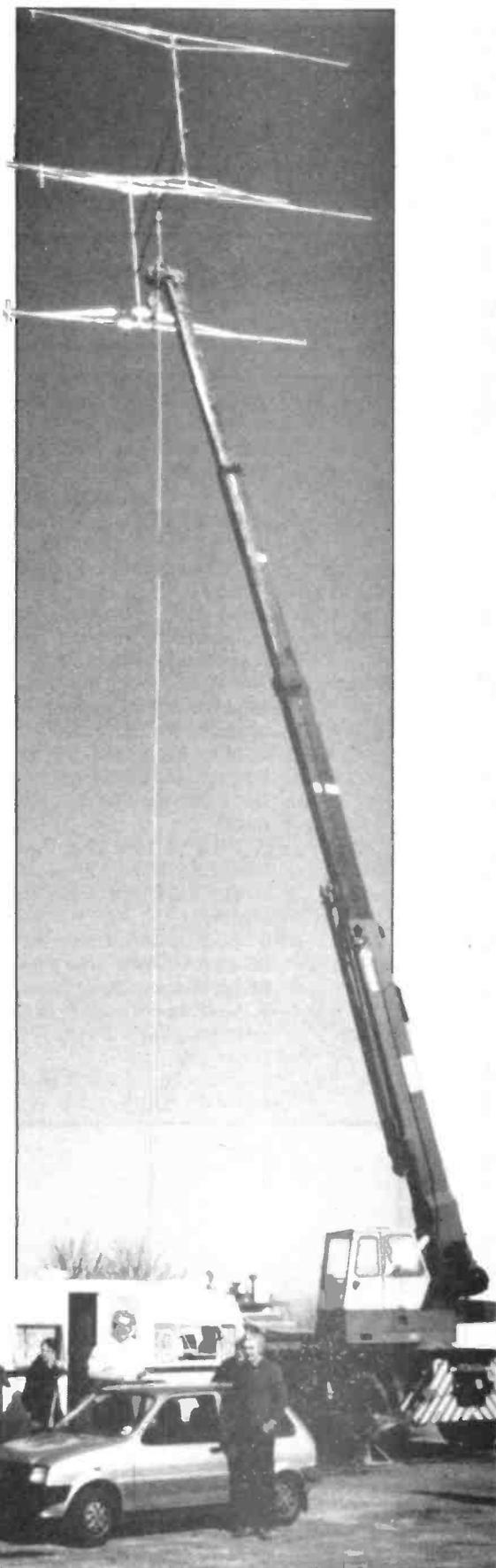Hastings ERC and their Contest set-up — including the 90' jib crane!



RADIO Tomorrow

Your at-a-glance guide to what's happening around the clubs, on the air and in general radio-wise.

- | | |
|---|---|
| <p>1 Aug Wirral DARC: D & W
S. Bristol ARC: Lecture — ring PRO for details
Wirral ARS: ring PRO for details
Lincoln SWC: RAE
Stockton DARG: ring PRO
Worthing ARC have changed their venue to Lancing Parish Hall, South Street, Lancing, W. Sussex. Info Eric Sandaver 0903 766318</p> <p>2 Aug Nene Valley RC: Natter Nite
Horsham ARC: <i>Automated Noise Figure Measurement</i> by G4EJG</p> <p>3 Aug Axe Vale ARC: 2m Foxhunt
Haverhill DARS: <i>Mobile Suppression</i>
Medway ARTS: <i>Satellite Working</i> by G8XLH
S. Manchester RC: 160m DF Contest
Harrow RS: G2UV Memorial Quiz
Dunstable Downs RC: <i>Computers in Amateur Radio</i></p> <p>4 Aug RSGB 432 MHz Low Power and SWL
GB4FES/GB8FES at Festival '84, a Christian Family Festival at the County Showground, Stafford
GB2EGL at the Welsh Eisteddfod</p> <p>5 Aug RSGB 144 MHz Low Power and SWL
RSGB Woburn Rally
S. Manchester RSGB 160m DF Qualifier</p> <p>6 Aug Horndean DRC: <i>Car Ignition Suppression</i> by Lucas Eng.
Leighton Linlade RC: ring PRO
Braintree DARS: 'Live' Operating Evening</p> | <p>7 Aug Southdown ARS: ring PRO
Stowmarket ARS: <i>Metrowave Awards</i> by Jack Hum, G5UM
Thornton Cleveleys ARS: <i>Switch Mode PSUs</i> by G4KPY</p> <p>8 Aug Wakefield DRS now meet at the Ossett Community Centre, Prospect Road, Ossett at 8 pm
S. Lakeland ARS: 2m Foxhunt
Chichester DARC: ring PRO
S. Bristol ARC: Pocket Phone Rally with G4SDR
Farnborough DRS: to be arranged
Lincoln SWC: On-air
Stockton DARS: ring PRO
Nene Valley RC: <i>Solar Data</i> by G8AFN
Cheshunt DARS: Natter Nite</p> <p>9 Aug Southgate ARC: Demonstration of Equipment and Social Evening
Stowmarket ARS: 2nd DF Hunt
S. Manchester RC: <i>QRO Miscellany</i> by G2HW
Harrow RS: Informal and Practical</p> <p>10 Aug Wirral DARC: DF Hunt</p> <p>12 Aug Exeter ARS: Construction Evening</p> <p>13 Aug Sutton and Cheam RS: Inter-Club Quiz with Coulsdon ATS at St Swithins Hall, Purley
Thornton Cleveleys ARS: Brush Up Your Morse with G3ZRZ</p> <p>14 Aug Mid-Warwickshire ARS: Town and Country Festival Planning
Bury RS: Fox Hunt</p> |
|---|---|



- 15 Aug Basingstoke RS: Contact G4OAC for details
Wirral DARC: D & W
S. Bristol ARC: VHF CW Night with G4OPQ
Wirral ARS: ring PRO
Lincoln SWC: RAE/Hamfest meeting
Stockton DARS: ring PRO
Nene Valley RC: *SSTV — in Colour and B/W by G4ENB*
Cheshunt DARS: Equipment Evening
- 16 Aug S. Lakeland ARS: ring PRO
Chichester DARC: ring PRO
- 17 Aug Medway ARTS: Demonstration of Satellite Working by G8XLH
S. Manchester RC: to be arranged
Harrow RS: Informal and Practical
Haverhill DARS: Interference
Dunstable Downs RC: Df Hunt on 160 and 2m
- 19 Aug Glenrothes DARC: Forward Planning Discussion
RSGB 1296 MHz Contest
RAIBC/FRARS Hamfest at Flight Refuelling Social Club, Merley, Wimbourne, Dorset. Parking, Trade Stands, Camping and Caravanning facilities. Fun for all the family, including model railway rides and barbeque refreshment. Bring and Buy. RSGB Stall. Talk-in. Open 1100-1700. Fund raising event for the Radio Amateurs Invalid and Bedfast Club. Info Bob Burrows 0202 762828. East Kent ARS regret that their mobile rally is cancelled. All booking fees will be refunded.
- 20 Aug Braintree DARS: *Computers and Amateur Radio by G8NPF and G6CHJ*
Thornton Cleveleys ARS: contact PRO for details
- 21 Aug Biggin Hill ARC: *Construction Techniques by G4VTD*
Wakefield DRS: Pitch and Putt Competition
Halifax DARS: *Radio Calderdale by David Keitch*
Midland ARS: Discussion Night
Fylde ARS: Natter Nite and Morse Class
- 22 Aug Wirral DARC: Junk Sale
S. Bristol ARC: End of Club VHF Contest
Farnborough RS: to be arranged
Lincoln SWC: Homebrewing with G8ZCD
Stockton DARS: ring PRO
Nene Valley RC: Natter Nite
Cheshunt DARC: Natter Nite
- 23 Aug Edgeware DARS: SSB FD Briefing
- 24 Aug S. Manchester RC: ring PRO
Harrow RS: Informal and Practical
- 26 Aug RSGB ROPOCCO 2
Preston Mobile Rally at Lancaster University. Free Parking. Admission 50p plus free prize draw. Cafe and Bar. Trade stands plus RSGB bookstall and Grand Bring and Buy. Rally starts at 1100. Talk-in S22 and 70cm. Info G3DWQ 0772 53810
British Amateur Teleprinter Group Rally at Sandown Park Racecourse, Esher, Surrey. Trade stands galore, BARTG kits and publications stall, demonstrations, refreshments and a Car Boot Sale. Close to A3, M3 and M4. Open 1030-1700. Talk-in S22. Free parking. Info Ted Batt 01 549 8253
- 27 Aug Southgate ARC: Trent Park DF Hunt and Social Extravaganza.
- 28 Aug Mid-Warwickshire ARS: HF on-air night
- 29 Aug Wirral DARC: D & W
S. Bristol ARC: QRO Activity Night
Lincoln SWC: RAE
Stockton DARG: ring PRO
Nene Valley RC: *The Six Metre Band by G4BAO*
Cheshunt DARC: 2m Portable on Baas Hill Common
- 31 Aug Medway ARTS: Talk and Demonstration by KW Communications Ltd
S. Manchester RC: ring PRO
Harrow RS: Informal and Practical
Haverhill DARS: Lightning Protection
Dunstable Downs RC: *Microwaves by G3BNL*
RSGB 144 MHz Trophy and SWL Contest
RSGB SSB Field Day
Stourbridge ARS: "Your Construction Project" (a forum)
Leighton Linlade RC: AGM
Braintree DARS: Test Gear and Operating Aids
Southdown ARS: ring PRO for details
Stowmarket ARS: A Visit to Suffolk Police HQ
Thornton Cleveleys ARS: *Japanese Morse by G3CSG*
Wakefield DRS: to be arranged
Fylde ARS: Aerial Circus with G6CJ (video)
Vale of White Horse ARS: Talk by G3RZP of Plessey
Chichester DARC: Visit by the Sussex Repeater Group
- 4 Sep Fareham DARC: Satellite Communications
Wirral ARS: Debate on "CW is a dying art?"
S. Bristol ARC: AGM
Wirral DARC: D & W
S. Lincoln SWC: CW/RAE/Hamfest
Stockton DARG: ring PRO
Nene Valley RC: Natter Nite
Cheshunt DARC: Natter Nite
Horsham ARC: Junk Sale
- 5 Sep **World Association of Christian Radio Amateurs and Listeners Conference Weekend at the London Bible College, Northwood, Info G3AGX 0482 822276**
Axe Vale ARC: *The RSGB by G3XC*
Cray Valley RS SWL Contest. 1800-1800 Sun. Up to 18h of logging to be done. Arguably the best SWL contest there is! Log sheets and rules from Owen Cross, 28 Garden Avenue, Bexley Heath, Kent DA7 4LF
- 6 Sep
- 7 Sep
- 8 Sep **Scottish Amateur Radio Convention at Cardonald College, Glasgow (short distance from the M8). Trade Stands, demonstrations, RSGB bookstall and guest lecturers, including George Dobbs of the G-QRP Club and Chris Bartram of muTek. Parking and refreshments readily available. Open 1100-1700. Admission £1. Talk-in on S22.**
Wirral DARC: 5th and Final DF Hunt.
Telford Amateur Radio Rally at Telford Town Centre, (junction 10A off M6) Telford, Shropshire. Displays, over 80 trade stands, Flea Market and the rally is nearby the town park. Talk-in and refreshments (Ansell's Bitter!) Info G8DIR 0743 64273
Chichester DARC: G2NM Commemorative Station at Chalk Pits Radio Museum.
- 8 Sep
- 9 Sep Exeter ARS: to be arranged.
Milton Keynes DARS: ring PRO
Thornton Cleveleys ARS: Morse Class
Mid-Warwickshire ARS: *Metal Bashing*
Bury RS: *Video Vs Photography by G4OAC*
Fareham DARC: On-air/natter night
Wirral DARC: Equipment demonstration by
- 10 Sep
- 11 Sep
- 12 Sep

	Lowe Electronics	20 Sep	Chichester DARC: ring PRO
	Farnborough DRS: Pre-AGM discussion	23 Sep	Lincoln Hamfest. Trade Stands, Bring and Buy, fairground attractions and model aircraft display. Food, picnic area, parking and Talk-in. Located at Lincolnshire Showground (4 m N of Lincoln A15)
	S. Bristol ARC: VHF/UHF Activity Night — <i>all beams west, folks.</i>		Dunstable Downs Car Boot Sale at The Shuttleworth Collection, Old Warden.
	Lincoln SWC: <i>VHF Aerials by G3FDW</i>		Thornton Cleveleys ARS: Club Project and Construction Evening.
13 Sep	Stockton DARG: ring PRO	24 Sep	Mid-Warwickshire ARS: Junk Sale
	Cheshunt DARC: Junk Sale	25 Sep	Fareham DARC: on-air/natter night
14 Sep	Southgate ARC: "Birds Nest" Night	26 Sep	Wirral DARC: Inter Club Quiz Night with Chester at Irby
	Edgeware DARS: Informal		Farnborough (Hants) DRS: Annual Construction Contest
16 Sep	Haverhill DARS: Open Evening		S. Bristol ARC: SWL Activity Night with Ron Gardner
	Dunstable Downs RC: <i>RTTY, AMTOR and Packet Radio by G3NRW</i>		Stockton DARG: ring PRO
17 Sep	RSGB 70MHz Trophy and SWL		Cheshunt DARC: Club Project Discussion with G4OAA
	Vange Amateur Radio Society Mobile Rally at Nicholas School, Basildon 1000-1700. Info Mrs. D. Thompson 0268 552606		Edgeware DARS: Quiz with G3PSP as MC
18 Sep	Stourbridge ARS: ring PRO for details	28 Sep	Haverhill DARS: HF Operating Procedures
	Leighton Linlade RC: ring PRO		Dunstable Downs RC: <i>Colour Offset Printing by G4WYO</i>
	Braintree DARS: <i>Clay Pigeon Shooting</i>	30 Sep	Welsh Convention at Oakdale Community Centre, Blackwood.
	Thornton Cleveleys ARS: to be arranged		
19 Sep	Biggin Hill ARC: <i>Antennas by Louis Varney, G5RV</i>		
	Wakefield DRS: t.b.a.		
	Halifax DARS: AGM		
	Fylde ARS: Informal and Morse Class		
	Fareham DARC: <i>Multi-band HF Antennas</i>		
	Wirral DARC: D & W		
	S. Bristol ARC: ATV Activity Night		
	Wirral ARS: Air Your (radio) Problems Night		
	Midland ARS: Homebrew Evening		
	Lincoln SWC: CW/RAE/Hamfest		
	Stockton DARG: ring PRO		
	Cheshunt DARC: Natter Nite		

Will Club Secretaries please note that the deadline for the November segment of Radio Tomorrow (covering radio activities from 1st October — 1st December '84 is 26th August).

Contacts		
Axe Vale ARC	Roger Jones	Upottery 468
Barking RES	R. Woodberry	01 594 4009
Braintree RS	Alan Moore	0304 822738
Bury RS	Bryan Tydesley	0282 24254
Cheshunt DARC	Roger Frisby	0992 464975
Chichester DARC	C. Bryan	0243 789587
Cambridge DARC	David Wilcock	0954 50597
Dunstable Downs RC	Phill Morris	Dunstable 607623
Exeter ARS	Roger Tipper	0392 68065
East Kent RS	Stuart Alexander	0227 68913
Edgeware DARS	John Cobley	30 64342
Fylde RS	PRO	Lytham 737680
Halifax DARS	DL Moss	0422 202306
Harrow RS	Dave Atkins	0923 779942
Hastings ERC	Dave Shirley	0424 420608
Haverhill DARS	Rob Proctor	0787 281359
Hornsea ARC	Norman Bedford	0262 73635
Horsham ARC	Pete Head	0403 64580
Leighton Linlade RC	Pete Brazier	052 523 270
Maltby ARS	Ian Abel	Rotherham 814911
Medway ARTS	Andy Wallis	0634 363960
Mid Ulster ARC	DF Campbell	0762 42620
Preston ARS	George Earnshaw	0772 718175
S. Bristol ARS	Len Baker	0272 834282
S. Lakeland ARS	Dave Warburton	Ulverston 54982
S. Manchester ARC	Dave Holland	061 973 1837
Stockton DARS	John Walker	0642 582578
Stowmarket DARS	M. Goodrum	0449 676288
Southdown ARS	P. Henly	0323 763123
Vale of White Horse ARS	Ian White	Abingdon 31559
Verulam ARC	H. Clayton Smith	St Albans 59318
West Kent ARS	J. Green	0892 28275
Welland Valley ARS	J. Day	0858 32109
Wirral ARS	Cedric, G4KPY	625 7311
Wirral DARC	Gerry Scott	051 630 1393
Worthing DARC	Jim Hicks	0903 690415
308 ARC (Surbiton)	Dave Davis	01 399 5487

CONTROL UNITS for a 2m GaAsFET pre-amp

My article in last month's *HRT* described a GaAsFET masthead pre-amplifier for the 2m band, and made reference to a suitable control unit which would be published in a later issue.

various installations and user requirements. Hard switched changeover is used and fed to the masthead via the receive signal coaxial cable. Two levels for PTT operation may be internally

amplifier, allowing correct sequencing of the co-axial relay at the masthead. The unit has a built-in mains driven power supply and a user-adjustable PIN diode attenuator in the receive line with a range of 30dB. It is housed in a standard diecast box and all components are mounted on a double-sided PCB with plated-through holes.

Remember our high performance 2m pre-amplifier last month? Here are two remote control units, capable of handling 350W and 40W of RF respectively, to suit a variety of station requirements.
By John Matthews, G3WZT.

The unit described here fulfills the requirements previously mentioned, allowing great flexibility for


selected; either +9/12V or earthed on transmit. A separate PTT output is provided for control of a linear


Circuit Description

PTT INPUT (Fig.1). The PTT line is fed into SK1 from the transceiver. Two levels are catered for, either earthed on transmit or plus 9/12V. These are selected in the control unit by means of a link on the PCB (C to E for earth, C to P for +V). Q5 is a simple DC controlled switch which earths the internal PTT line when the appropriate input is present on SK1.

SEQUENTIAL SWITCHING. (BREAK). IC3 is a dual monostable multi-vibrator. IC3a delays the pre-amp switching when going from transmit to receive; IC3b delays the PTT out to the external PA when going from receive to transmit. IC3a is a positive edge triggered monostable and provides a positive going pulse at the Q output when pin 4 changes from a low to a high level (ie when the PTT is released). The duration of the Q pulse is set by C3,R4 ($T = \text{approx. } 0.5 C3 \times R4$). With the values indicated the pulse duration is around 100 mS.

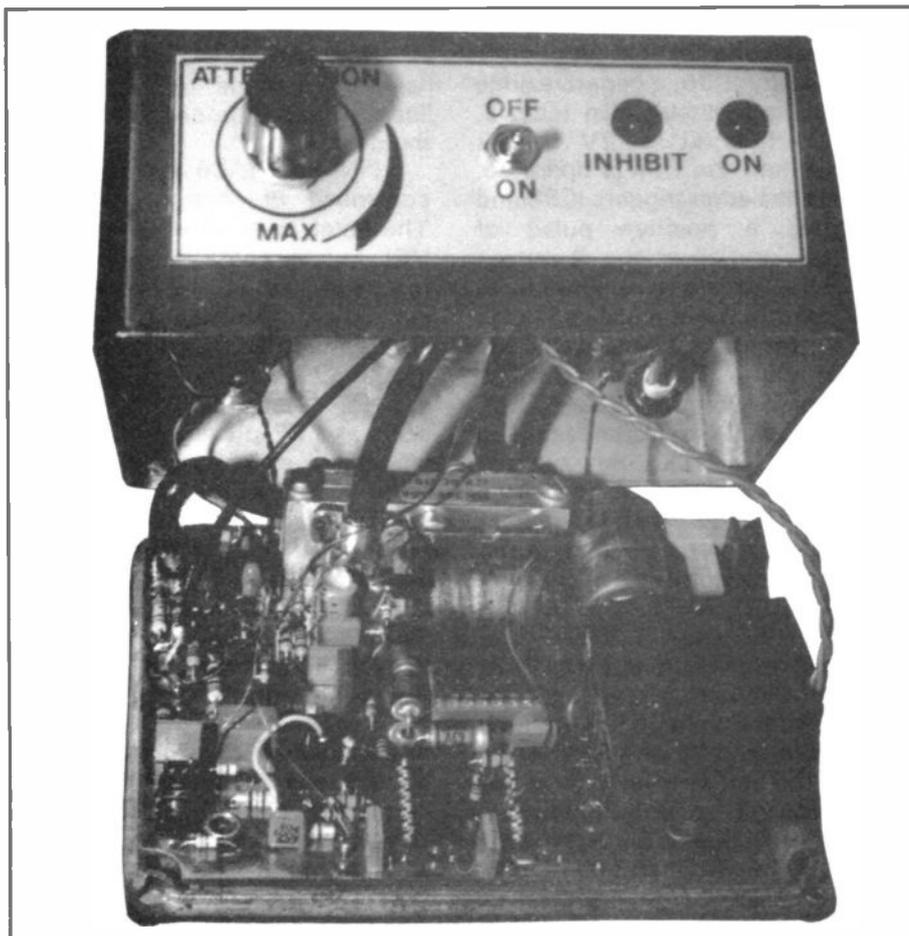IC1a,b are used as buffer/inverter gates with the output (pin 4) driving relay driver transistor Q1. On transmit Q1 is off and RL1 de-energised; when the PTT is released, the negative pulse at Q1 base holds RL1 'off' for a further 100 mS. This allows ample time for the RF to decay before DC is ap-



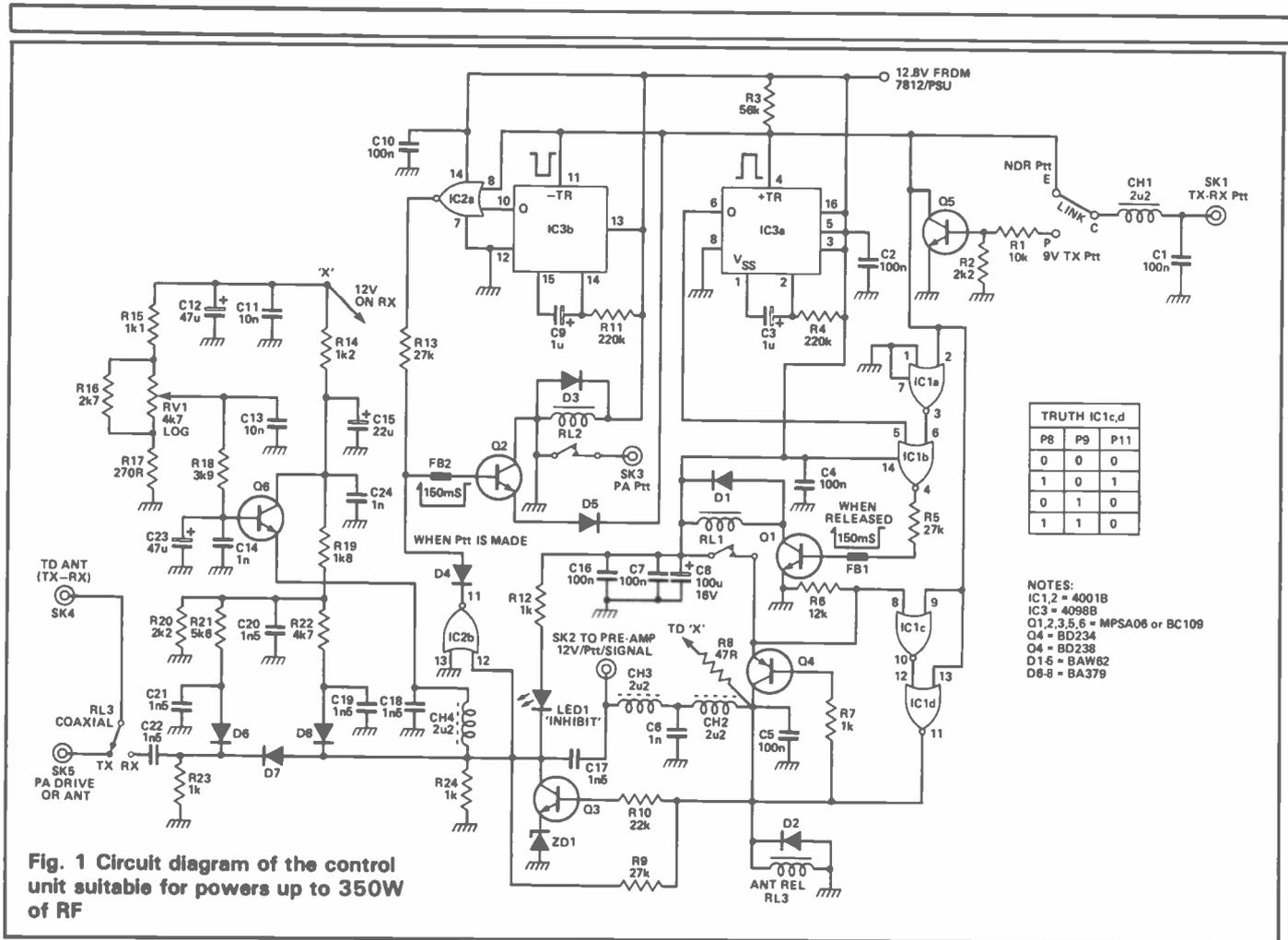

plied to the masthead pre-amp, and to co-ax relay RL3. The contacts of RL1 supply +12V to the series-switching-and-inhibit transistor Q4. IC1c and d perform an IMP-NOT function (Q = pin 8 AND NOT pin 9). Q being true is not a valid combination of PTT functions because it implies that the masthead unit is being supplied with 12V and the transmitter is also being keyed. As this condition must constitute an internal failure, Q4 is turned off, removing the masthead supply at SK2. Under the above conditions, the output of IC2b (pin11) goes low and prevents the power amplifier PTT line from operating by inhibiting Q2. Transistor Q3 is turned on and illuminates a front-panel LED to indicate that an inhibit condition exists.

SEQUENTIAL SWITCHING (MAKE). When the transmitter is keyed, it is most important to ensure that the masthead co-axial relay is in the de-energised position before RF power is applied to it. This is ensured by delaying the power amplifier PTT line at SK3.

The sequencing for this function is controlled by IC3b, a negative edge triggered monostable. On receive, pin11 is held at +12V by R3 (56K). When the PTT is operated, the negative edge triggers IC3b and generates a positive pulse of 100 mS duration at the Q output (pin 10). IC2a is a NOR gate buffer which inverts the Q pulse and holds Q2/RL2 off for 100 mS after the PTT switch has been pressed. The emitter of Q2 is returned to the PTT line as a precautionary measure to ensure that RL2 can only operate when on transmit. D5 prevents reverse V_{BE} of Q2 when in transmit mode. Sequential switching functions are shown in Fig.2.

PIN DIODE ATTENUATOR. On receive the signal from the masthead amplifier is fed into SK2. Isolation between signal and the 12V operating voltage fed via SK2 is provided by C17 and CH2,3. To control the signal level fed to the main receiver, a PIN diode attenuator is included between SK2 and RL3. The attenuator configuration is similar to other published designs, and no originality is claim-

ed. However, some modifications have been made to improve the linearity and gain control range of the device.

PIN diodes, D6,7,8 form a DC controlled PI section attenuator. The level of attenuation is set by VR1, which controls the base current into Q6. Components associated with the output side of Q6 are arranged so that with minimum attenuation set, D6 and D8 present a high impedance path to signal earth and D7 presents a near short circuit in series with the signal path. The reverse is true when maximum attenuation is set by means of VR1. Insertion loss of the attenuator at 145 MHz is 2.5 dB and could be reduced at the cost of passing additional current into the PIN diodes and reducing reliability. However, with the high gain available from the masthead unit, this small loss is insignificant.


Interconnections for installation of the control unit pre-amplifier combination are shown in Fig.3 with separate diagrams to show use with or without a power amplifier. Although some doubt

may be cast on the use of diodes in the receive path from the point of giving rise to unwanted intermodulation products, there is no cause for concern. The third order products are well below those of the pre-amplifier and are suppressed by more than 70 dB with respect to an output level of 0 dBm (each tone) giving a 3rd order intercept point of +35 dBm. (see Fig.4). At these signal levels, pre-amplifier and attenuator performance are of little concern as most receivers will be grossly overloaded when signals of this magnitude are applied to the input. Co-axial relay RL3 switches the common Tx and Rx (aerial input) sockets of a transceiver between the pre-amplifier output on receive, and the aerial or power amplifier input on Tx. If separate units are used for Tx and Rx, the features of this control unit may still be used to full advantage. In order to maintain sequential relay switching when moderate power levels are used (50W) with a separate transmitter, the PTT will need to be modified so that its Tx/Rx switching is controlled from SK3. In its simplest form, the microphone PTT must be separated from the Tx and fed to SK1 on the control unit, with the output PTT at SK3 used to control the Tx/Rx changeover functions. Under these circumstances the Rx is fed from SK4; the Tx output goes to the original aerial feeder, leaving SK5 unused. If separate units are used with a low power transmitter, existing PTT facilities may be used as the problems associated with switching high power levels do not exist.

When using a separate high power amplifier in conjunction with individual transmitter/receivers, the interconnections are as shown in Fig.3 a, except that the receiver is connected to SK4 and the transmitter to the PA drive socket.

Construction

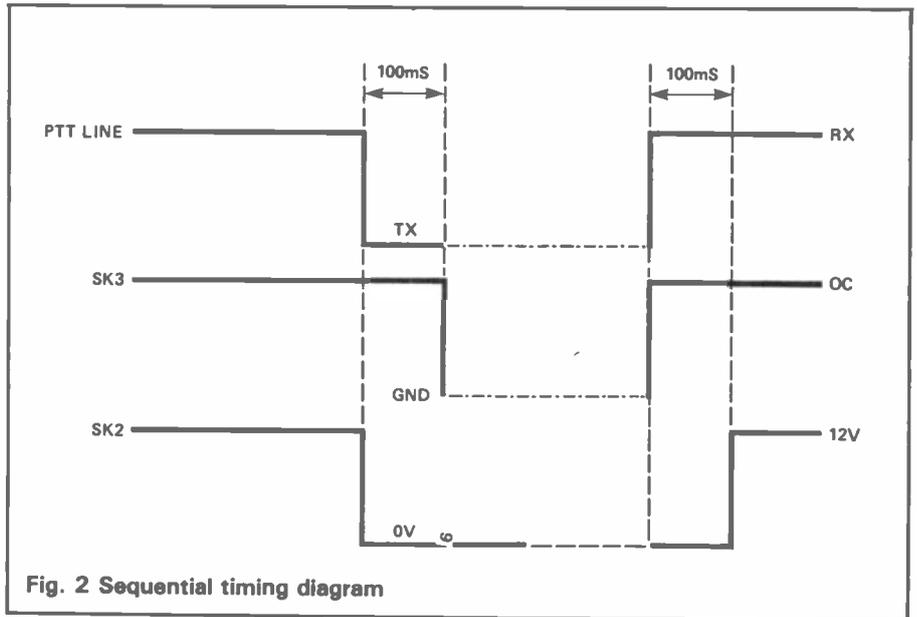Construction of the unit is straightforward, all components are mounted on a double sided PCB with plated through holes. Component layout is shown in Fig.5. The mains driven power supply unit and regulator are integral and mounted on the same PCB as the control cir-



cuitry. The completed unit is housed in a standard diecast box (114 x 89 x 55 mm) with the PCB mounted on the lid. Co-axial sockets and PTT input and output phono-sockets are mounted on the rear of the unit with the attenuator control, power 'ON', 'INHIBIT' LED and mains switch mounted on the front. Mains is fed through the rear of the unit and secured with a nylon strain relief bush.

Begin by soldering the chip capacitors (C17-C22) in position. These are very small, and care should be taken to ensure that a minimum of heat and solder are used consistent with good joints. Holders may be used for IC1,2,3 if preferred, but be sure to use

modern types as reliability will be reduced if old or second-hand types are used. All other components may be fitted in any order, but be sure to observe the polarity of all diodes and electrolytic capacitors. Chokes in the bases of Q1 and Q2 are formed using a wire linked with a ferrite bead passed over the link. Where connections from the board to controls and sockets on the enclosure are required, leads may be soldered directly into the holes on the PCB or to pins previously soldered into those holes.

When all components are soldered to the board, make up and fit 3 six-inch lengths of UR43 to the co-axial relay. The cable braid clamps allow the cables to be

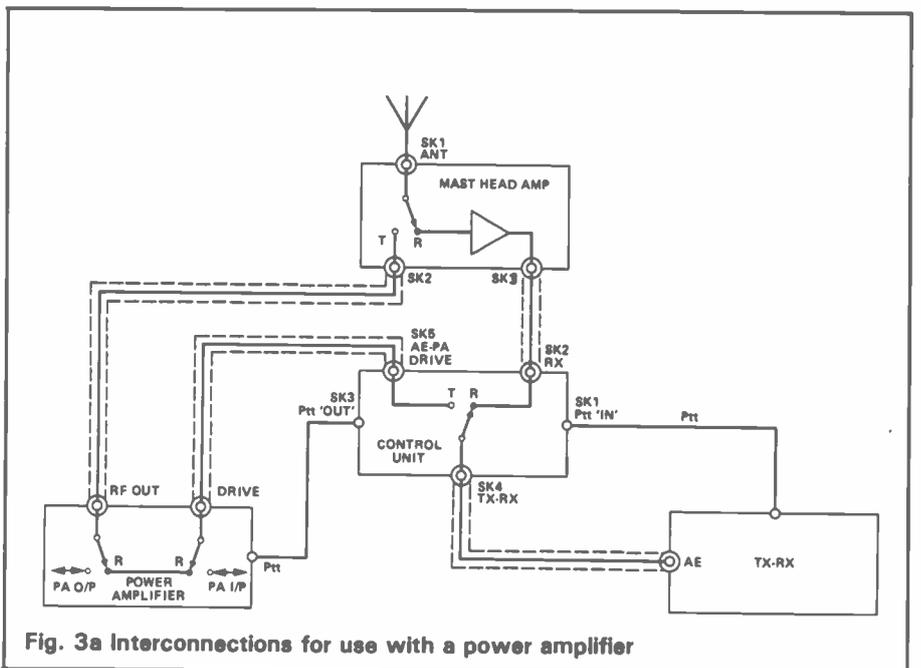


Fig. 3a Interconnections for use with a power amplifier

brought out from the relay in several configurations. To ensure correct fitting, proceed as follows. Place the relay in front of you with the energising coil towards you, and the coil connections on the left-hand side. The co-ax connection on the front of the relay adjacent to the coil should be made up to feed out vertically and at right angles to the body of the relay. This connects to SK5. The rear right co-ax is fed out in exactly the same way, and goes to SK4. The remaining co-ax lead is arranged to feed from the left-hand side along the axis of the relay body. This connects to the pad provided at one end of C22. A short piece of 28 SWG copper wire is used to connect the braid to the earth plane. Mount the relay, using M3 screws, with the coil facing towards the centre of the PCB and the coil terminals adjacent to C8. Solder one side of the coil to the earth plane, and the other side to the two points shown on Fig.5.

The completed circuit board is secured to the lid of the control box by means of 4 x 3 mm clinch nuts fitted to the underside of the PCB. These provide a 6 mm spacing between the underside of the PCB and the base of the unit. The drilling diagram for the front and rear of the enclosure (Fig.6) is correct for the components used on the two prototypes. Changes may be needed to accommodate components used by the individual constructor.

All cables should be earthed to the appropriate sockets using short pigtailed soldered to earth tags. SK2 is connected by a length of 50 ohm co-ax to the point shown in Fig.5. Mains input is fed via a miniature DPDT switch to the pads provided adjacent to the mains transformer.

PTT Selection

As mentioned earlier, 2 levels of PTT are catered for, earthed on transmit or +9V - +12V. Selection is made by a wire link on the PCB. For transceivers giving a +ve voltage on transmit, link C to P; for those giving ground on transmit, link C to E.

Testing

After thoroughly checking component values and orientation, examine the board for solder

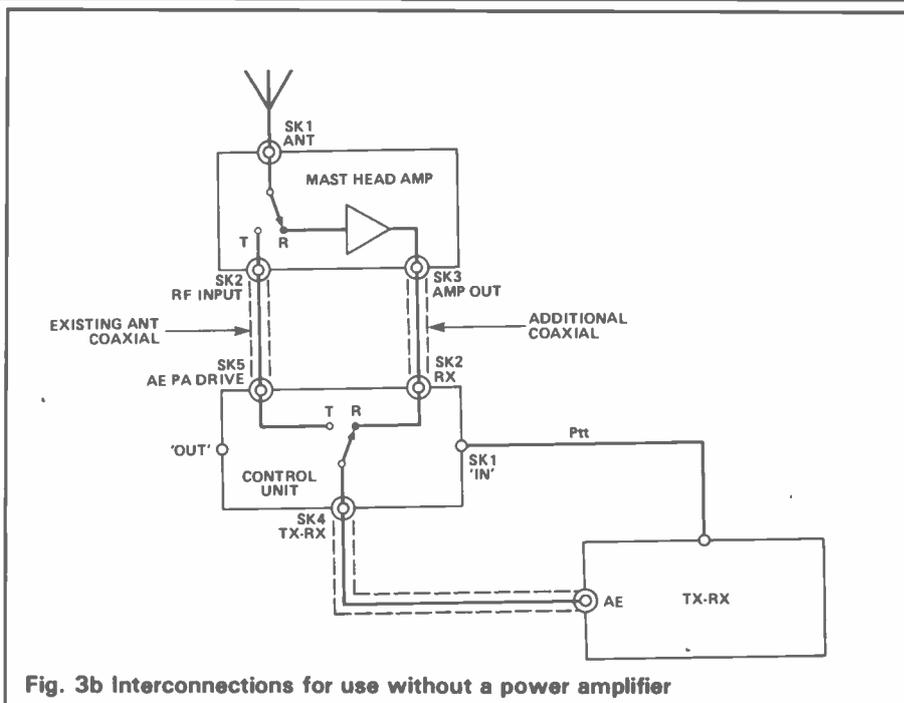


Fig. 3b Interconnections for use without a power amplifier

splashes and poor joints. If plated-through holes are not used on the PCB, make sure that components are soldered on both sides of the board and that vacant holes are pin-

ned through. If all looks well, switch on and check that 11 to 12 volts is present at the Rx/12V co-ax socket (SK2). The 'POWER ON' LED should be illuminated. Monitor

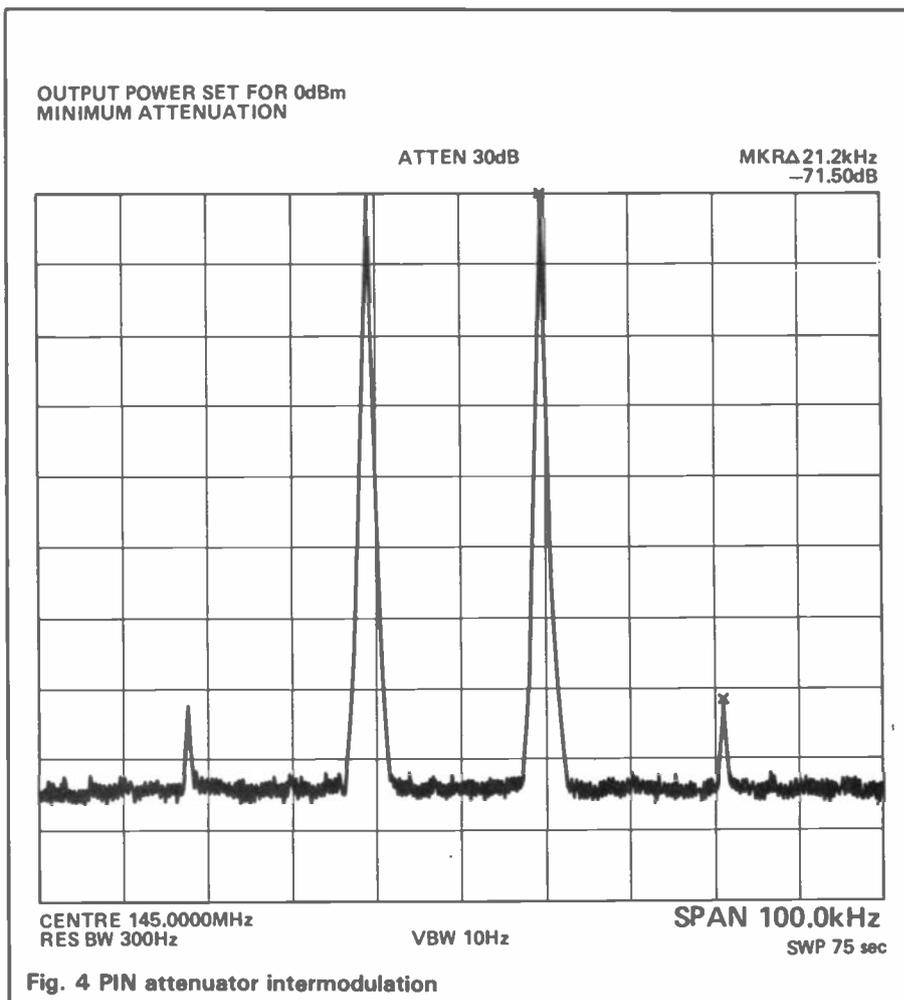


Fig. 4 PIN attenuator intermodulation

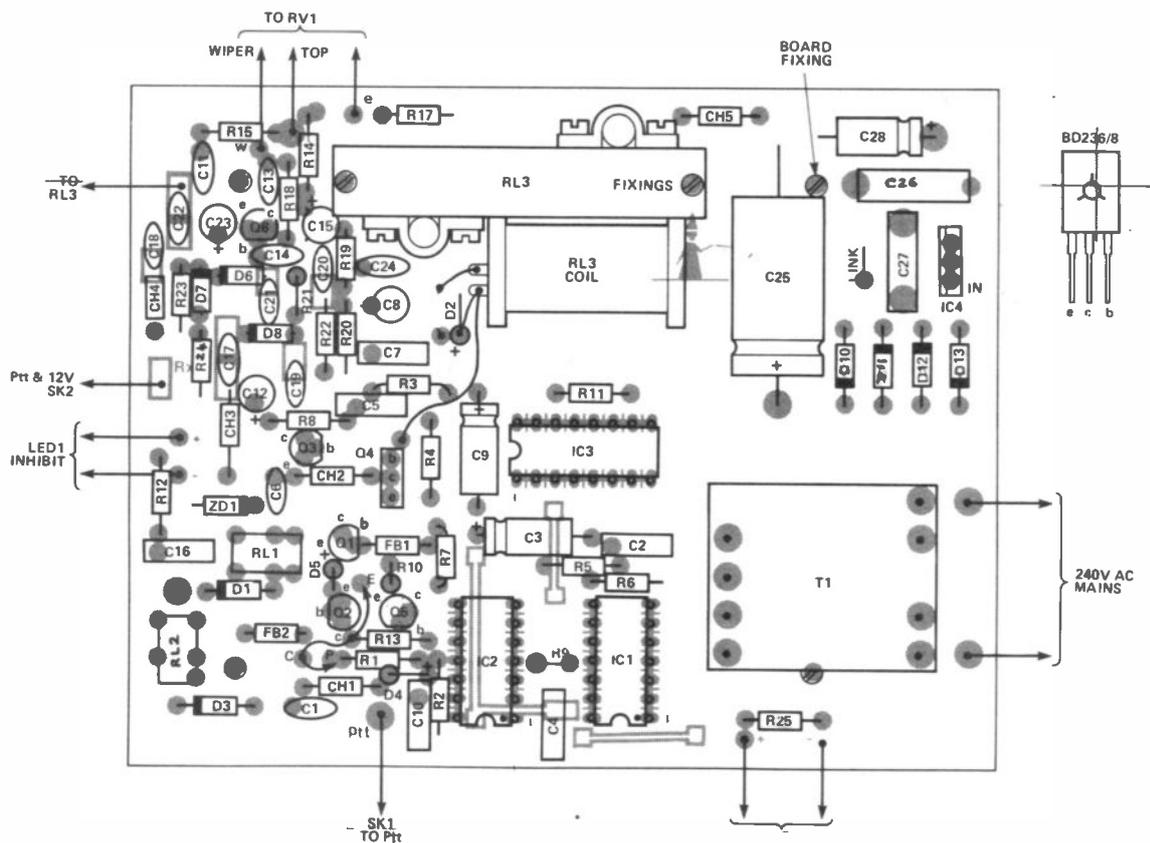


Fig. 5 Overlay diagram for the control unit suitable for 350W

the voltage at SK2 and operate the PTT by applying a ground of +9V - +12V at SK1 (depending on the link selected). The voltage at SK2 should return to zero immediately. Remove the PTT from SK1 and check that the DC level at SK2 returns after a short delay (approx. 100 mS). If this is satisfactory the sequential switching of the pre-amplifier is working.

Place the ohmmeter across SK3 and check that the contacts on RL2 are open. Operate the PTT at SK1 and check that a short delay occurs (approx. 100 mS) before the ohmmeter shows short-circuit. This ensure that the PTT out to a linear amplifier is delayed enough to allow the co-axial relays in the mast head amplifier and control unit to de-energise before RF power is applied to them. To check the inhibit circuit, place a temporary short between pins 8 and 14 of IC1. Switch the control unit on and operate the PTT at SK1. The 'INHIBIT' LED should illuminate and RL2 de-energise, removing the 'PTT out' from SK3.

The variable attenuator is most easily checked in a complete system. Connect the pre-amp and control unit combination as shown in Fig.3. Rotation of the attenuator potentiometer should alter the received signal level by approximately 30 dB.

Use Of Attenuator


The amount of attenuation required will vary according to individual installations and user requirements. Sufficient gain is available from the pre-amplifier to cater for long runs of inexpensive co-ax between the pre-amplifier

output and the control unit. Users with runs of average length will have the ability to adjust the gain at will to suit band occupancy and conditions at the time. The attenuator can sometimes have a dramatic effect. During a contest, for example, the band often contains a number of very strong signals (all of which seem a bit "wide") and the spaces between the strong signals are filled by a 'spitchy' noise. Tune to a space between strong signals and slowly back off the attenuator. Suddenly the noise decreases dramatically! If you now tune the band, you find that the spaces between the strong


Component Listing

Resistors

R1	10K	R6	12K
R2,20	2K2	R7,12,23,24	1K0
R3	56K	R8	47R
R4,11	220K	R10	22K
R5,9,13	27K	R14,25	1K2
		R15	1K1
		R16	2K7
		R17	270R
		R18	3K9


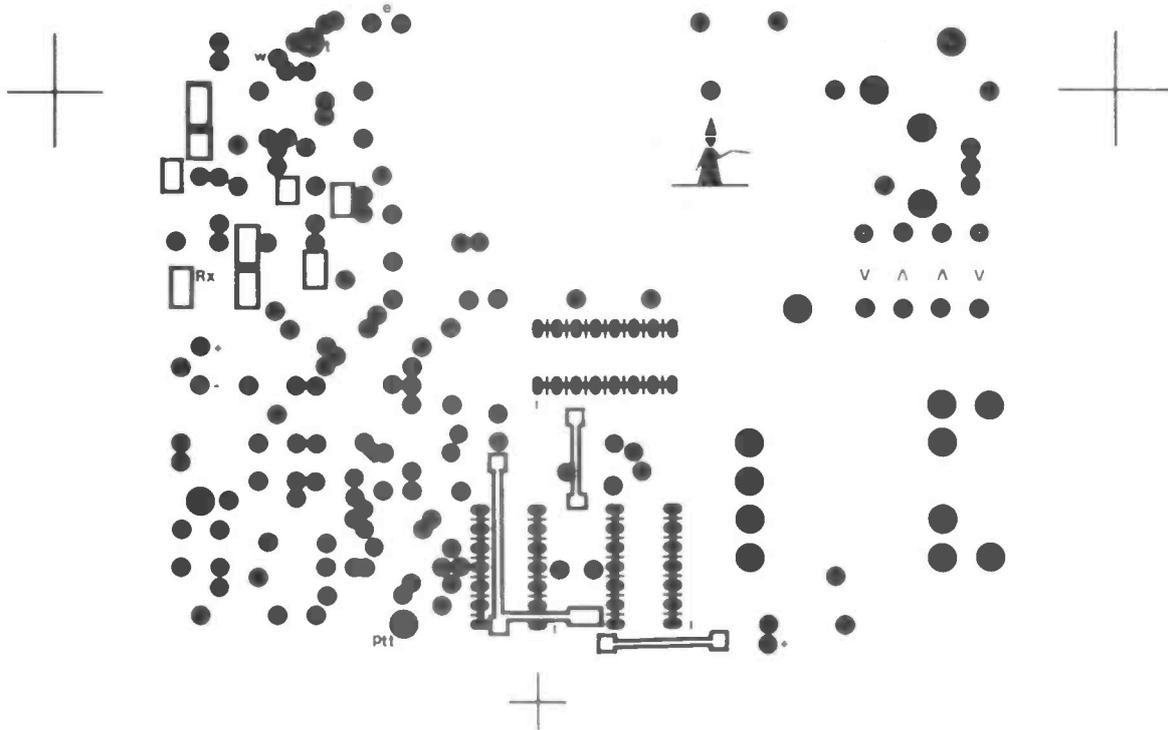


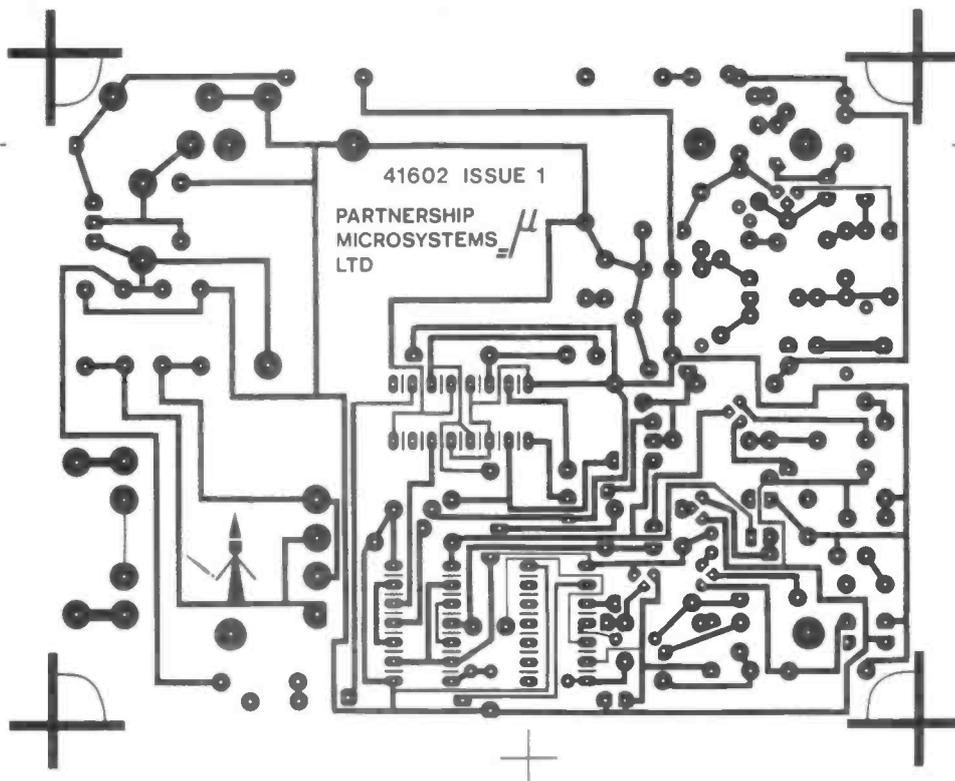Top foil of 350W control unit. WILL CONSTRUCTORS PLEASE NOTE THAT ETCHED AREAS ARE SHOWN IN BLACK



Bottom foil of 350W control unit. In this, the TRACK areas are shown in BLACK!

R19	1K8		05-10810)	dil, 1 x 16 pin dil
R21	5K6	C26	470n polyester RS	RL1,2 12V min dil type
R22	4K7		113-926	OUC (AM
VR1	Min. 4K7 log	C27	220n polyester RS	46-70040)
			113-910	RL3 12V co-axial RS
All resistors are 1/4W, carbon film, Style TR4		C28	2.2uF 63V Electrolytic (axial)	349-686
Capacitors		Semiconductors		
C1,2,4,5,7,10,16	100n ceramic monobloc (PM)	ZD1	3V3 400mW Zener	CH1-4 2.2uH min moulded RF choke
C3,9	1uF 25V tubular electrolytic (axial)	D1-5	BAW62 or 1N4148	CH5 4.7uH min moulded RF choke
C6,14,24	In ceramic monobloc	D6-8	BA379 PIN diode	FB1,2 FX1242 ferite bead
C8	100uF 16V elect. (radial) RS 103-339	D10-13	1N4001	SK2,4,5 BNC skt. single hole fixing with earth tag
C11,13	10n ceramic monobloc	LD1,2	Red LED with panel mounting	RS 455-674 & 456-469
C12,23	47uF 16V sub min radial elect. RS 103-979	Q1,2,3,5,6	MPSA06 or BC108 plastic (AM 58-00238)	SK1,3 Phono skt. single hole fixing RS 478-093
C15	22uF 16V bead tantalum RS 101-838	Q4	BD236 or BD238 Regulator 7812	T1 15-0-15V 3VA RS 207-841
C17-22	1n5 chip (PM)	IC1,2	4001B	SW1 Min DPDT toggle switch 250VAC RS 316-989 or AM 53-00201
C25	1000uF 25V axial elect (AM)	IC3	4098B	Strain relief bush RS 607-774; PCB See text (PM 41602) and die cast box Eddystone 6908P
		Miscellaneous		
		IC Skts (if required) 2 x 14 pin		

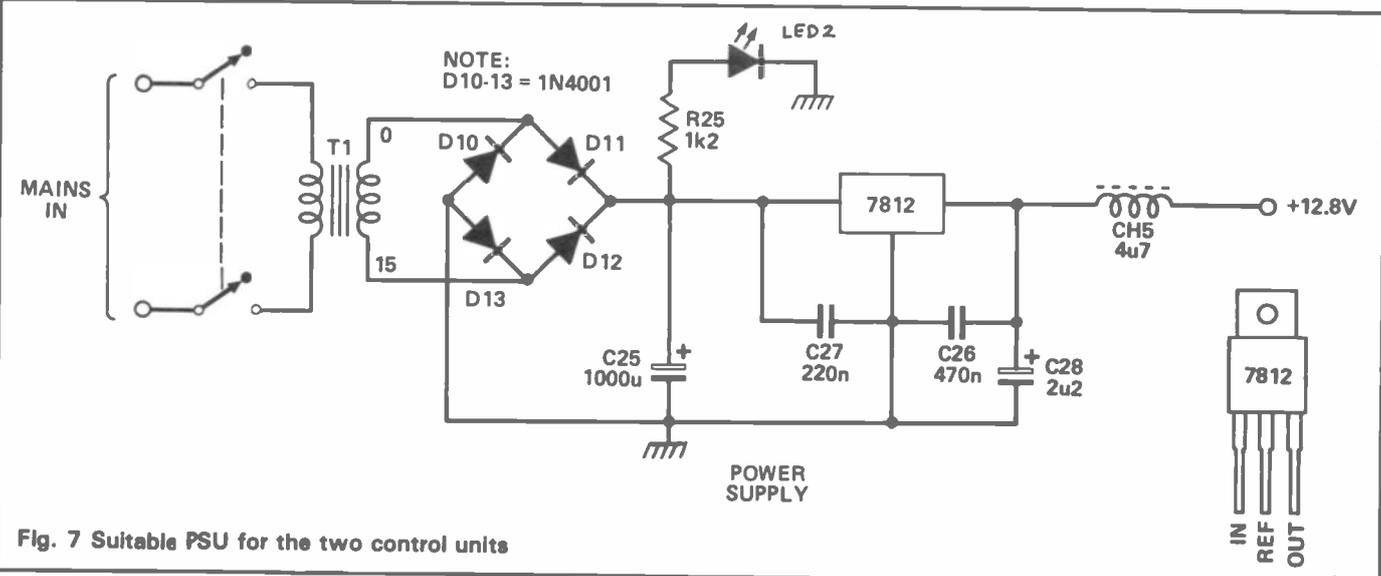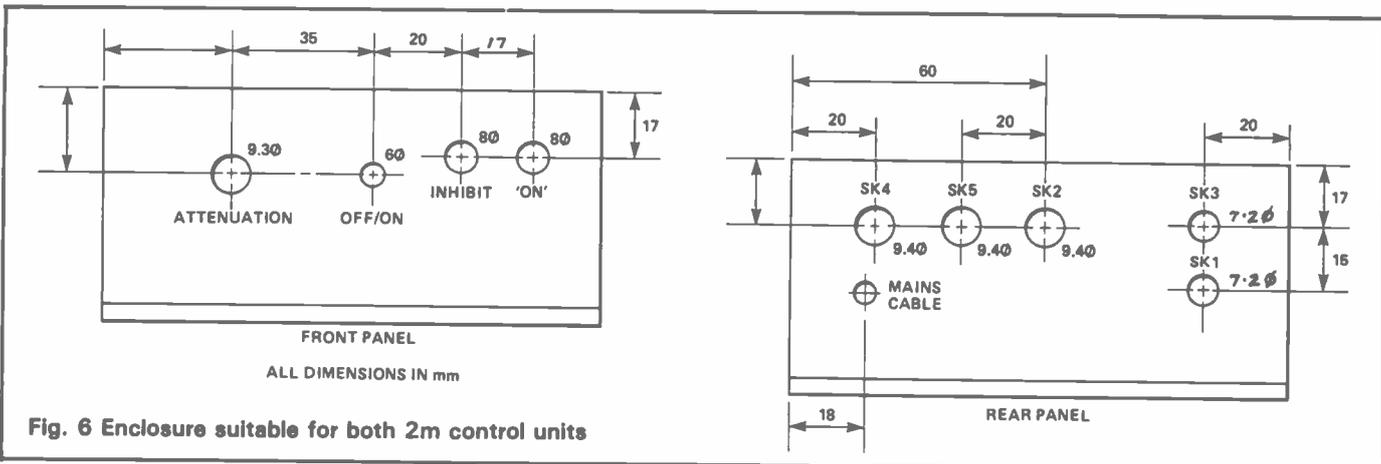

signals contain numerous weak (but readable) signals. You also notice that most of the strong signals no longer spread across the band. The stations that still spread are those that really DO have transmitter intermodulation problems!

Alternative Low Power, Low Cost Control Unit

This is a lower cost design, with a reduced specification. A DIL reed relay is used for RF switching, switching is not sequential, and there is no provision for control of a linear amplifier. Transmit power is limited to 40W maximum. RF sensing is used to switch to transmit mode; hard switching can be used (and is preferable) if the rig has a PTT output. A 6 dB fixed resistive attenuator is included to reduce the pre-amplifier output. The attenuation may be changed to suite individual needs by changing the values of three fixed resistors. The unit is powered from an external 12V DC supply.

Circuit Description

RF power is sampled at SK1 via C1 and detected in the diode voltage doubler D1,D2. Decoupling is provided by C2 and the rectified voltage clamped at this point by ZD2. The hang-time of the RF VOX is set by C3. To maintain a high input impedance (preventing excessive loading of the detector) the rectified RF sample is fed to a NAND Schmitt trigger IC1a. The output at pin 3 goes low when the input threshold has been reached. The threshold level is to some extent dependant upon the supply voltage, and will increase as V_{DD} is increased. At +9V the RF VOX will require around 0.5W to operate

As some form of buffering is required between IC1a and the relay driver transistor Q1, the remaining gates are used to form an RS flip-flop. The output at pin 10 goes low when RF is present at SK1, turning Q1 off and de-energising RL. Hard-switched changeover can be selected by taking the centre pin of SK1 to pin A for ground on transmit or pin B for +9V - +12V on transmit. When hard switching is selected, RF sensing is not disabl-

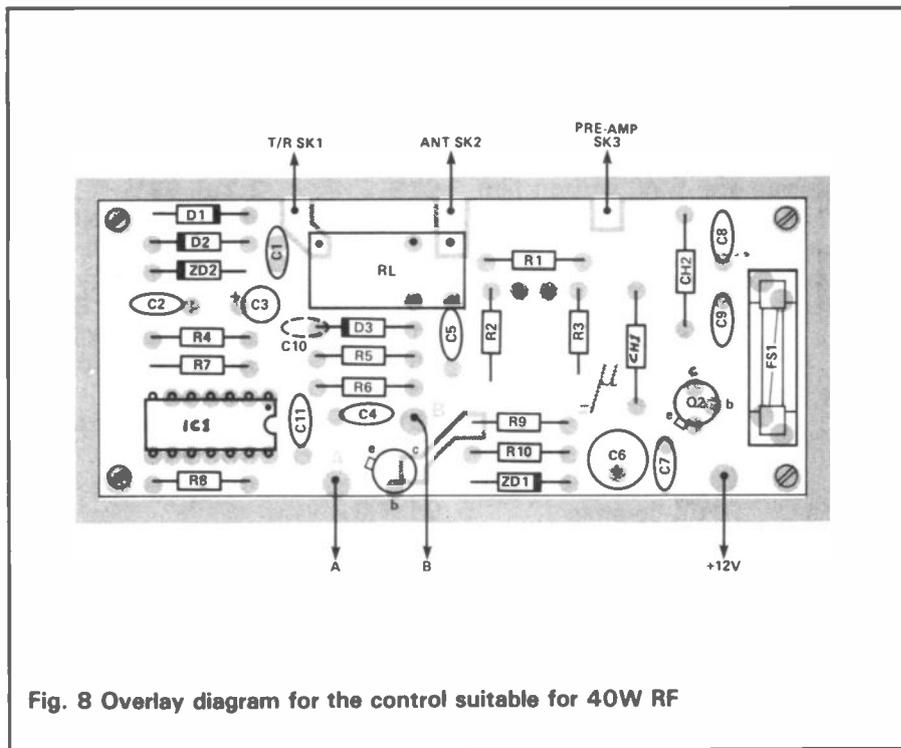


Fig. 8 Overlay diagram for the control suitable for 40W RF

ed. This provides a built in safety function should a failure occur on the PTT line. Q2 is a DC switch which supplies DC via SK3 to the mast head amplifier. When no RF is present at SK1, Q1c is at 0V and Q2 is switched hard on, giving +12V at SK3. CH1,2 and C8,9 provide isolation between DC supply and signal.

Input from the mast head amplifier at SK3 is fed to the attenuator R1,2,3 via isolating capacitor C10. The values of R1,2,3 given in the component list provide 6 dB attenuation. For different levels of attenuation, see Table 1.

ZD1, in conjunction with the input fuse, provides protection



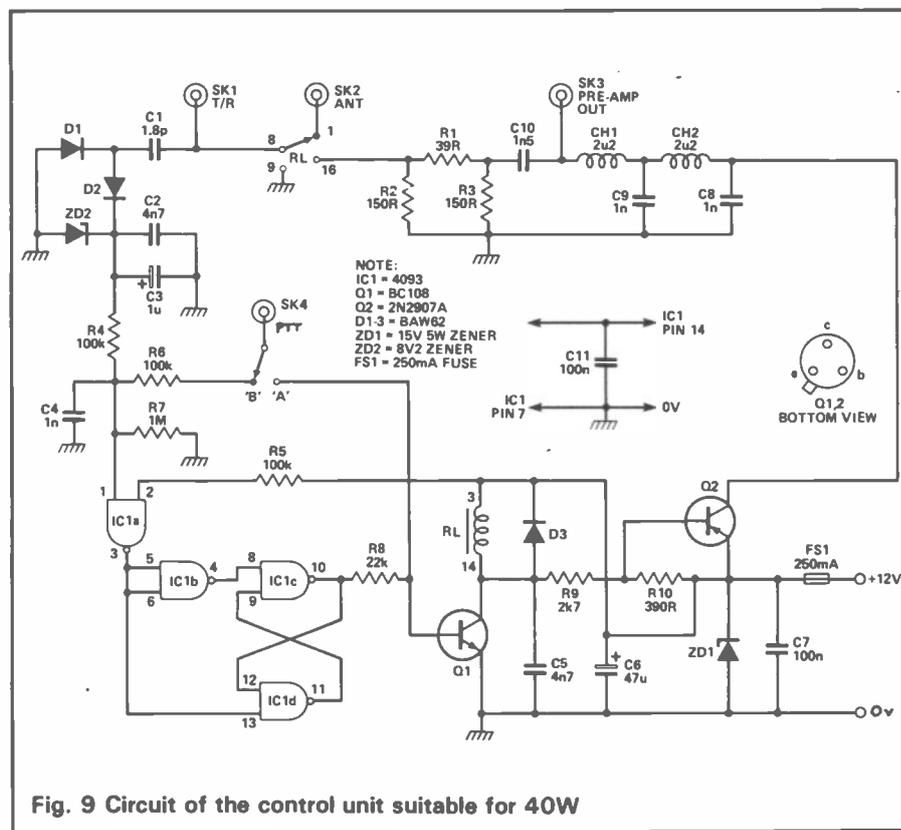


Fig. 9 Circuit of the control unit suitable for 40W

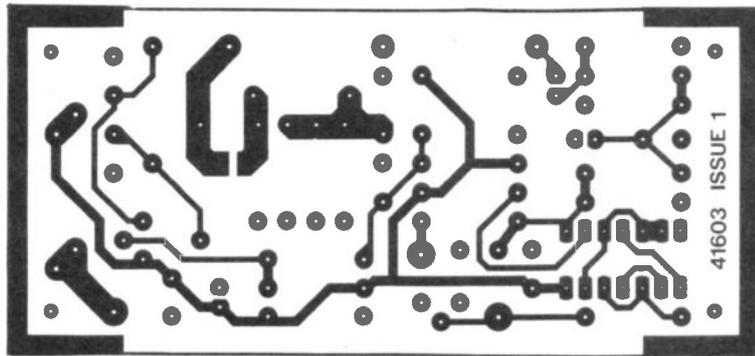

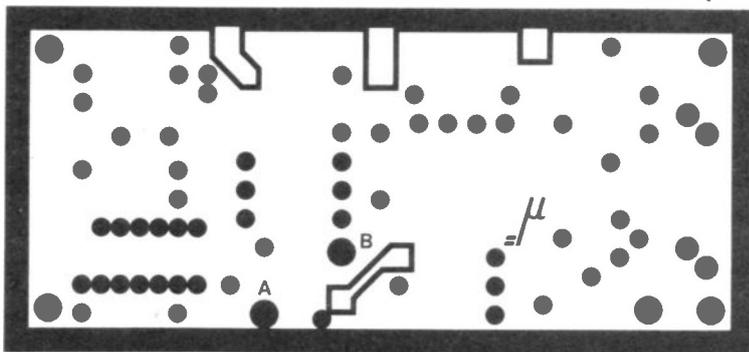Bottom foil of 40W unit. TRACK areas are shown in BLACK



Top foil of 40W unit. ETCHED areas are shown in BLACK

against excessive or reversed supply voltage.

Construction

The unit is constructed on a double-sided PCB with plated through holes and housed in a small standard diecast box. Construction is very straightforward. All components are mounted on the top (earth plane) side of the board except C10. This is a chip capacitor, and is soldered to the underside of the board across the gap in the 50 ohm strip-line leading to SK3. When fitting the fuse-holder clips, take care to stand them off the earth plane. Component layout is shown in Fig. 8. The completed unit is mounted in a 110x6x28 mm die cast box, by means of 4xM3 screws. SK2 is fitted to the exact centre of the rear edge of the box, with SK1,3 spaced 20 mm either side. This allows the inners of the BNC sockets to be soldered directly to the pads provided on the PCB. A phono socket is mounted on the front edge of the box for PTT input. 12V DC enters via two PTFE feed through insulators.

John would like to thank John Cooper, G8NGO, for "translations from the Sussex dialect into English".

ATTN db's	R1	R2/3
3	18	292
4	24	220
5	30	178
6	37	150
7	45	130
8	53	116
9	62	105
10	71	96
12	93	83
14	120	75

Table 1 Values of resistance needed for different values of attenuation

Component Listing

Resistors

R1,2,3 See text and Table1
 R4,5,6 100K
 R7 1M
 R8 22K
 R9 2K7
 R10 390R
 All resistors are 1/4W carbon film
 Style TR4

Capacitors

C1 1.8pF ceramic
 C2,5 4n7 ceramic monobloc
 C3 1uF 35V bead tantalum AM 05-10501
 C4,8,9 1n ceramic monobloc
 C6 47uF 16V radial electrolytic RS 103-979
 C7,11 100n ceramic monobloc (PM)

C10 1n5 chip (RM)

Semiconductors

D1,2 BAW62
 D3 BAW62 or 1N4148
 ZD1 1N5352B (or any 15V, 3W Zener)
 ZD2 8V2, 400mW Zener
 Q1 BC108/B238 plastic
 Q2 2N2907A
 IC1 4093

Miscellaneous

RL SDS DR12V (PM)
 SK1,2,3 BNC single hole fixing (AM 10-01000)
 SK4 Phono socket

Fuse holder clips RS 412-784; PCB (PM 41603); Die cast box Eddy-stone 7134P or RS 509-939 and Feed-through insulators RS 433-882




The Key Element

SSB clarity starts at the microphone...

Hell Sound, the company that pioneered proper audio equalization techniques for major performing groups and communicators, invites you to be part of one of the biggest advancements in Single Sideband transmission since the "Donald Duck" vs. AM days. If you are not satisfied with the "sound of your station" - It's no wonder - most "communications" microphones used today were designed for "public address" use, not for sophisticated SSB techniques.

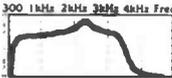No one microphone can be all things to Hams, so this new



... Have not yet heard an FT-101 sound any better than when used with The Key Element... - Paul, G3AWP

... I now have a comfortable feeling that my audio is better than the rig was originally capable of... - Ken, W9UBS

... Thank you for the fine report, all reports to date have been excellent... - Lee, W1SE

For those who desire the ultimate audio into and out of your transmitter/transceiver, consider the ideal combination of the Hell EQ-200 audio equalizer and HM-5 microphone.



HC-3 element and HM-5 mic were developed only for maximum clarity on SSB transmissions. The response of this tiny ceramic element rolls off sharply under 350 Hz and above 3100 Hz with a peak at 2400 Hz for high articulation in the speech range.

Hams who care about maximum results in getting over, around and through DX pile-ups now have another weapon in their arsenal... The Key Element!

You can easily install this small, advanced HC-3 element, with its broad-range impedance-matching characteristics, into virtually any microphone case you own, or purchase the custom HM-5 with HC-3 installed.

All prices include VAT and Carriage. £. + OE.

For further information, or to order the HC-3 cartridge element at £17.99, the HM-5 SSB microphone at £49.95 or the EQ-200 at £45.95 contact our Sole European Distributor, Amcomm Services Ltd., 194 Northolt Road, South Harrow, Middlesex or Telephone 01-422 9585.



Hearing is Believing...

AMTRONICS (TONBRIDGE) G4SYZ Closed Mondays.
THE AMATEUR RADIO SPECIALISTS IN KENT 9-5.30 Tues.-Sat.
Fridays 6pm.

30FT. LATICE TOWER £299

Wall or post mounted on display at shop.
In stock (cash-n-carry) or delivered.
Call in at the shop or send SAE for details.

Yamato Rotor still	£40	NEW from MET Antennas
Alinco EMR400 still	£79	70cms 5 Eli 9.5db 0.7m long
Uniden CR2021 Receiver	£160	Fantastic performance and will fit in a suitcase
Camma Twin	£7.95p	Also coming soon 2m/70cm power splitters.
HB9CV 2m	£6.95p	
We also sell:		CREDIT - Through Shepherd Finance (instant will call sign) Call in or ask for details.
YAESU-FDK-ICOM		
ADONIS-DATONG		
JAYBEAM-MET-BNOS		
WELZ-ADONIS etc.		



8 TOLLGATE BUILDINGS, HADLOW RD., TONBRIDGE. TEL: (0732) 361850

Please mention Ham Radio Today when replying to adverts

HAM RADIO TODAY SEPTEMBER 1984

ADVERTISERS INDEX

Allweld Engineering	11	PNP Communications	65
Amtronics	58	Quartzlab Marketing	IFC
ASP Software	IBC	Radio Society of Great Britain	39
Beta Comm	65	Reg Ward and Co.	11
BNR and ES	11	SAT Electronics	65
Bredhurst	IFC	SM Tatham	65
Commutech	OBC	South Midland Communications	34/5
Dewsbury Electronics	OBC	Tan Systems	68
Paul Sergent	65	Technical Software	65
Partnership Micro-systems	IFC	Weirmead	65
Pinehurst Data Studios	65	WPO Communications	24

Don't forget, when calling an advertiser, mention Ham Radio Today - it helps them and us.

73's Dave Gadsden, G4NXV Advertisement Manager

Free Readers' ADS!

URGENTLY WANTED by 16 year old G6, a TA1062AP and 144.800 CRYSTALS Tx and Rx for trio 2200. G6TMI QTHR phone Telford (0952) 5530 above items needed to join Raynet.

MML144/100-S 2M 100 watt amplifier with preamp VGC £89. H.F DIPOLE 10-80m VGC £18. 4M 4ELE JAYBEAM GC £9. G4NRG Brentwood 810831.

Om-10 SLR Camera 50mm F1.8 Lens. 80-200mm F4.5 Macro Zoom and various extras £210 or will exchange for FT208R and charger G6YCV QTHR. Tel: Calne (0249) 812966 anytime.

BBC Mod 8 fitted with word-wise and exmon roms. plus BBC cassette recorder plus software and books. £399 also available OPUS desk phone John 0744 819453 evenings after 8.00p.m. and weekends will haggle.

WANTED VALVES W81 or equivalents 7H7 W143 W148 to fix BRT400 RX. also wanted manual or any info for GERTSCH FM3 'FREQ. Meter. call Ed G8FAX evenings on Rayleigh (0268) 770716.

STANDARD 2mtr FM Transceiver C8900 very small neat and compact measuring only 5 1/2" x 7" x 1" approx. nice and inconspicuous in the car cheap way to get on two. Phone 691-3939.

GRUNDIG SATELITE professional 3400 £140. Freeman Tel: 0604 47409.

VALVES ex equipment QQVO3/10 QQVO2/6 5763, EL91, KT88, 6L6, 6CH6, 6J6, QY3/65, TT21, 807, all metal 6/12volt series. cheap for clearance lists G8BSK 290 Priory Road, St. Denys, Southampton. SO2 1LS.

EXCHANGE my FT101 mark 2, fully crystaled CW crystal filtered all modes spare valves. Wanted FRG7700 with AT4 and active ANT if possible call or write 214 Horninglow Road Firth Park Sheffield S5 6SG. or phone 389202 10.30a.m. to 4.30p.m.

MMD050/500 500MHZ frequency counter and probe £60. Mk123 SPYSET VGC

£65. Codar AT5 Tx £30. Telford T7 tuneable 10 metre IF SSB/CW/AM/FM £30 VARIAC 240v 15amp £25 RCA AR88 instruction manual £5 ring Dursley (0453) 811454 after 6p.m.

WANTED FT480R in good condition for sale trio R-300 general coverage RX £60 ono. phone (0272) 719163.

RTTY to TV converter model MM2001 for sale or exchange for good quality CB; AM, FM, USB LSB plus usual facilities expected on this type of rig. offers to Claude 01-431-2919 evenings. CB for use abroad.

YAESU FT201 transceiver, base and mobile, just back from amateur electronics after complete service. This includes DATONG ASP PROCESSOR G whip for 20m and 80m coils manual microphone all for £275 plus carriage air test willing G3MLP tel: Peterborough 63851.

KW2000 SSB/CW 50W transceiver incl PSU, speaker, manual recently overhauled. £110 delivery may be arranged or at cost G4NZX 0302 854985 after 6p.m.

YAESU FT980 General broadcast transceiver as new used few times only £900.00

phone daytime 01592 7800 evening 0277 823434.

SHIMIZU SS105S HF all mode transceiver absolutely as new condition. Fitted FM boards and CW filter. £275 might also sell matching state of the Art Homebrew Transverter, 16W output, £60. G4ILO. Colchester 572685.

MICROWAVE MODULES MM4001 KB RTTY ASC11 transceiver and keyboard perfect condition £200 Fincher 27 Albert Street Tring Herts HP23 6AX Tel: Tring 6752 also DATONG mobile doppler radio direction finding equipment £100 ono.

80cm through 70cms station. TS130V transceiver, MMT144/28, MMT432/28, VFO120. DF230, YK885N, R.F. switching module and interconnecting cables. Demonstration available. Prefer not to split. £170 oven carriage at cost can deliver locally. Graeme G6CSY, QTHR, Orpington (0689)29230 evenings.

CAMBRIDGE Amiod working 70.26 AM with Garlex FM board and manual £35 MMC/435/600 ATV converter £20 Starphone UHF mobile £20 OS-15 OSCILLOSCOPE, needs work

£10 all ono can deliver at cost. Mike Denham (0895) 834167 evenings.

RADIO CONTROL have two large models aerobatic pattern model with 10cc engine, tuned pipe, retracts. Big biplane "PUPPETEER". Both flying order sell/swap HF Linear AMP, RF generator etc. 10 Laburnum Road, Wellington, Somerset. Tel: 4109 Mr. Vanaway.

TITAN 500 Linear 500W output at 26/30 Mhz £120 carriage extra. Realistic DX200 £85 carriage extra G1AFQ Harry Penzance 3084.

PYE TX/RX 1.6/3.9 KHZ 50 watts spares manual as new offers. BC221 vgc with charts PSU £40. Dawe test oscillator 0.1 10000 hz dual quadrature output vgc £40. Serviscope and spare valves £45, valves QV08/100 723/AB QF41 11E3 KT66 0502 715419.

SELL OR SWAP YAESU FT101ZD Mk 3 mint condition with boxes and manual £410 or swap IC720A plus PSU with cash settlement might consider why but IC720A wanted. Telephone Clive 0279 28857.

2MTR 5XY plus phasing harness £8 magnum 2mtr transverter £45 or exchange for HF ATV MK products SSTV unit sell or exchange for transverter for four or seventy. Brian G4RHZ QTHR Tel: 0302 770663.

WOOD & DOUGLAS 70cms transceiver 6 channel scanner 3 channels fitted RB2 SU8 RB14 PTT changeover tone burst speaker s.meter etc., built in aluminium box with 12 volt 6 amp hour nicads, good working order £90 ono. Tel. Huddersfield 643124 G4GMT QTHR also MBM 28 70cms antenna £10.

SINCLAIR SPECTRUM 48K WH Smith's matching data recorder both still under guarantee also over £100 worth software £150 ono orexchange for Solid State HF transceiver pair Pye socket phones on SV8 complete with nicads and stand in charger £35 ono also Rotel R.V.C. 220 40 channel CB rig 9 mon-



As reported in this month's *Radio Today*, Cirkit have recently made a new deal with Toko Ltd, the worlds largest supplier of coils and chokes, which should improve the availability of these sometimes hard-to-get components. Richard Sanders, General Manager of Toko UK is pictured here (LHS) with Cirkit's Mike Sandham and Richard Bulgin.

ths guarantee £15 Huddersfield 643124 G4GMT (QTHR)

HEATHKIT SOFTWARE receiver SW717 and general coverage phones and ????? good order £20, Galpin, 23 Upper Highway, Hunton Bridge, Kings Langley, Herts. **TRIO SP230** new/boxed £25. Europa 28-2m transverter with heater transformer £35, G4UDG Tel. Kidsgrove 72100.

KENWOOD WANTED DG5 digital display for TS 520 SW, W Salt, 8 Smallways lane, Chilton Polden, Nr Bridgewater, Somerset. Tel. 0278 722402

GENERAL COVERAGE receiver Century 21 complete coverage 0.50KHz to 29.999MHz Excellent condition £70 ono, 13 element crushcraft 2 metre beam 15dB gain £25. Trio 2400 2 metre hand held c/w charger etc. £125, Texas Inst T199 computer £40 ono or would swap for something useful W.H.Y Tel. Chester (0244) 311496. Wanted HF mobile and trap vertical antennas.

YAESU FT227RB 2m FM Tx/Rx 10 watts mic m/bracket £135. Yaesu FT208R hand-held 2m FM NC9C charger. Mint boxed £160. Trio 7010 2m SSB/CW Tx/Rx mic etc., vgc boxed £95. Yaesu YP150Z dummyload wattmeter mint £70. Telephone Weymouth 786930.

MM2 MORSEMATIC keyer by Advanced Electronic Applications as advertised by ICS swap for TR7010 or similar or WHY. 3 hrs use mint condition might accept computer, ring 049525 6794 ask for Carl.

ROTEL RVC240 Citizens band radio, mint condition and original packing. Also regulated power supply, SWR meter 3 aerials, 2 ground planes, 50ul coax, patch leads, car boot mount. Lot £65. Phone Mark, Sheffield 377504 evenings.

ZENITH R700 £350 mint, exchange 35mm Nikon camera, video recorder, WHY Chas Haynes, 01 850 1543

ZX81, 15K, excellent external keyboard, ICL cassette course with 2 manuals, software, books £69 ono prefer buyer collects, postage extra, Tel: 0253 45431. Wanted rotator in excellent condition to turn 2m beam, Martin Kay 107 St.



Thames Valley ARTS operated in NFD from "a luxury caravan" (!) parked in the lush meadow of G3OGP's farm.

Martins Road, Blackpool, Lancs FY4 2D2

YAESU FRG7 general coverage receiver, one owner, in first class condition, manual, original packing. Can demonstrate. £125 ono. Buyer collects. N. Richardson, 2 Edna Road, Ringlestone, Maidstone, Kent ME14 2QJ

70CM TRANSVERTER MMT 432/144R 10W output. Attenuators for 10W or 3W 2 metre rig. 1.6MHz shift £110 Realistic DX201 general coverage communications receiver with internal crystal calibrator, user manual and box £90 ono. Gary Davey (G6TBT) Telephone 01 995 4701 after 6.30 pm

DRESSLER VV200 GaAS, 2m preamp complete with interface vgc only £40 T.E.T. 8 ele quad 2m beam £35 ring Mike 01 504 4134 evenings.

DRAKE SPR4 comm Rx, Datong ANF auto filter. American military service manuals printers perforators BC610. Books from 1919 onwards. Valves components, S.A.E. lists offers Trowell G2HKU Hamlyn, Saxon Avenue, Minster, Sheerness Kent ME12 2RP. Tel: 0795 873100

WANTED DETAILS on converting Pye bantam from AM to FM. Tel. Cliff Manchester 061

740 9830 after 6 pm will pay expenses.

CREED 7B teleprinter plus power supply unit. Perfect mechanical condition. Baudrate needs adjusting for amateur use. Recently professionally overhauled. Sell for £25 no offers. Buyer collects. Phone Dave on Ramsey (Cams) 831396

WANTED Midland 7001 400CH owners manual. A Evans, 16 Dove House, Close Fowlmere, Royston, Herts. SG8 7SE.

WANTED Yaesu FTV650B 6 metre transverter good price paid for clean unit will fetch or pay carriage also SP101 speaker console please write G3XSI QTHR or phone 0742 51417

YAESU FRG7700 (+FM) 0-30MHz digital G.C.R., FRT7700 ATU, FRU7700 VHF converter 118-130MHz, 140-150MHz, 70-80MHz, all new and unused in boxes with manuals etc., (unwanted Christmas gift). Accept £300 the lot. Burgh Heath (07373) 60460

ICOM IC-255E exc cond two VFOs, band scan etc lcom scanning mic boxed and instruction manual 5XY Yagi beam western 5 way antenna switch £145 QTHR phone 0268 555645 (Mr Butler).

IC2E 2 batts mic/sp £110. HP41C port computer £95. VHF comm mags 1968 to 83 £25. LCD multi/m 16 auto ranges £30. Thandor freq counter 0 to 600 MHz 10mv sen £150. Rotring drawing system A3-rapidboard, many pens templates £50. Ultrasonic alarm £35. ring Peter 04738 5526

TEKTRONIX made tele-quipemnt scope D61. Dual trace 10MHz bandwidth complete with two X10 probes and manual £100. 021 451 3369.

HAM MAJOR all channels offers around £35-40. Wanted Nato 2000 or similar type. 0283 221870.

4E1MAC 4CX250B valves 2 SK610 bases 2 chimneys all new boxed abandoned project or P/exch YQ901P monitor scope cash, Milne, 0635 253019 Hants.

TRIO TR9130 and B09 Base £320. Kenwood TS130S ATU 130, VFO 120, SP120, PS30, MC35, mobile mount £500. Daiwa rotator £75, 13 element portable towna £10. 0229 23348 evenings.

HRO 500 HF. RX. synthesised 500KHz bands from 0.5MHz to 30MHz £300. FT101B MK2 recently overhauled and realigned. 10MHz band and CW filter fitted £295. Airmec



Over 400 people attended the latest 'monster' junk sale organised by the Cambridge Repeater Group. Photo by Chris Lorek, G4HCL

304 100MHz power signal generator £50 buyer collects. G3WZT QTHR tel 0403 710565 (Horsham, Sussex) MIZUHO SB-2X crystallised 144.00-144.600 and 144.800-145.00 excellent condition Nicads £100 ono Trio 2300 Nicads power leads heclical aerial mobile mount good condition £90 ono 144 MHz valve linear 40W output £50 ono. Woods GW8XAN Newtown, Llantwitt 201694 after 6.30 pm

DIGITAL VOLTMETER type DM2022S with i.f.amplifier module A1 and R.M.S. detector module B1 by "Digital Measurements Ltd". Good condition price £250.00 also video oscillator signal generator type 65B "Marconi" price £125.00. Collin Rogers, 64 Armagh Road, Newry, N.Ireland. Phone 67766 anytime.

DYMAR 3 channel portable xtal'ed R2 S20 S16. 4 battery packs Dymar automatic battery charger NOT fully working as lost interest sell £35 or swap for anything interesting radiowise. Tel. Heath Hayes (0543) 75410. Terry G1AMQ.

SONY ICF6700W 1.6-30MHz, med and FM bands just serviced £150 surplus due to purchase TS430S with GC receiver. Has digital readout, dual conversion and is very sensitive. BM Taylor, Hillside, Ebbesborne Wake, Salisbury SP5 5UB. Telephone Broadchalk 396.

TRIO 7010 2M SSB/CW transceiver 144.100 to 14.300MHz. Complete with microphone and mobile mount £80. G4UZG QTHR. Telford (0952) 582903.

SOMMERKAMP FT277B amateur radio transceiver. SSB very good condition £330 ono, Hy-gain five element beam aerial £40, base station power mike £20. Thanet (0843) 43700.

SHINWA CP80 dot matrix printer, centronics interface have to swap for Yaesu FT 290R. Dave Crowborough 63910.

HAVE PENTAX ME super (auto) flash, 200mm tele F3.3 lens (1 year old), Halina super 8 movie camera, Gnome slide projector, big screen 122, slide magazine. Wanted FRG 7700 and ATU. (0375) 72689.

GPV5 2M Colinear 6.5dB £17. 8 ELE 2m jaybeam vgc £10. Wanted 4m to 2m converter circuits or module. Homebrew OK wanted high gain 2m ant eg. 16 ele tonna or 8/B jaybeam. Wanted VHF beam rotator. Telephone Jason, Sapcote 2484.

TRIO TS-780 VHF/UHF multimode base station £625 13V 15amp power supply £60, BBC/Electron morse tutor program £6 Creed 7B £5, PCB's for ST5 TU £5. Contact T. Tugwell, 11 The Dell, Stevenage Herts. Tel. 0438 354689.

RCA AR88 communications RX with full manual and spare

set new valves £55 ono. Tel 0278 423288.

TRIO R600 general coverage receiver two years old hardly used boxed £160 plus FRT 7700 ATU £10 plus ultra loop UL 1000 pre-amp £10 will separate. I Randall, Manchester 061 320 7080.

EXCHANGE YAESU FTDX401 transceiver, matching speaker, Collins hand microphone 160-20 560 watts very nice condition. Plus HF5 vertical and unused radial kit. For Yaesu FLDX400 FRDX400. Must be in good condition and working. Tel. 0446 733907.

YAESU FRG7 general coverage receiver digital readout excellent condition £120. FRT7700 ATU for receivers £30 Mr Jenkins, Sixty-One, Edinburgh St, Swindon, Wilts SN2 6DE Phone Swindon 725914.

ICOM IC2E charger DC1 BP4 CP1 spare BP3 £139, Kenwood 2500 case spkr mic £189, Kenwood 2400 240/12V chargers £110, microwave modules MM2000 RTTY converter £100, wanted FT290 Kenwood AT230 tuner, pse phone 0277 354378 (24 hrs) (Central Essex).

UNIDEN 2021 Tandy DX/400 receiver. Superb portable. Very stable, sensitive, selective. 150kHz to 30MHz. Mains battery 12V-DC new £145. Yaesu FRT7700 ATU New £35 MM converter 156-158MHz (marine) to 28-30MHz £23. Ring Wom-

bourne (Staffs) 896625.

TOTAL SHACK CLEAROUT Eddystone 830X £30 ono plus del. Audioline 40CH FM CB 8 ext sp. Resistance box 1 -1M fully variable £10 ono. 2X 6nf 500VDC TCC capacitors 1 daly 400nf 400V cap plus daly 800nf 250V DC all caps 50p ea. Spares for Pye Vanguard radio telephon POA. Tel 0685 74061.

ICOM IC240 2m Tx/Rx complete with mic, mobile mount, two power leads and manual. All in good condition £100 phone G4ANW 0730 61859. **HEATHKIT SOLID STATE** SB303 receiver 80-10m, matching SB401 Tx with transceiver capability, matching SB610 speaker, HDP-21 microphone, manuals, Professionally built VGC Tx never used on air. £275 ono. Buyer inspects and collects. G6XHR Tel. 07014 55459, QTHR.

YAESU FT221RMutek good condition £300 ono also IC2E boxed 1 year old 1/4 wave, battery pack ICBP4, DC/DC converter, charger, case, boxes all as new £140 telephone Alex on Farnborough (Hants) 520227.

TS120V HR transceiver 80-10m 20 watt input plus DFC 230 digital VFO 4 memories and scanning mike £300 also QR666 communications receiver 170kHz-30MHz AM CW SSB band-spread tuning £75 phone 0670 815587 (Ashington, Northumberland).

TRIO 3200 eleven channels crystallised three SU, eight rb, case, nicads, charger Wood & Douglas pre-amp very sensitive £115 63DSV Tedburn, St Mary 472 (day) 753 (after 6pm).

CODAR AT5 with power supply £25. 20m (new), 15m, 10m, Reyco traps, £25 the set. Collector's surplus Morse keys (over fifty available), list SAE please. Hatfield RF bridge LE300A, £15. G3IRM, 2 Briarwood Avenue, Bury St Edmunds, Tel: (0284) 4318

WANTED: RTTY programs for TRS80 Mod 1 Level II. Telephone Hinckley (0455) 612655 evenings. G8AFY QTHR.

YAESU FRG7700 mint condition £220 ono. Trio TS120V £240 no offers buyers collect please, tel. Welwyn Garden City 28831.

EMPORIUM GUIDE

AVON

Booth Holdings Bath

6 GOLF CLUB LANE,
SALT FORD,
BRISTOL
Tel: 02217 2402
Open Tues-Sat 9am-9pm
Close Mondays

HAMPSHIRE

FARNBOROUGH COMMUNICATIONS
97 Osborne Rd, North Comp,
Farnborough. Tel. 0252-518009
Open: 6 days 10-6
Yaesu, Icom, FDKs, Mosley aerials, Jaybeams,
G Whips

W. MIDLANDS

DEWSBURY ELECTRONICS
176 Lower High St, STOURBRIDGE
Tel: (0384) 390063
Open: 9.30-5.15. Closed Thurs. & Sun.
ACCESS/BARCLAYCARD

Radio Communications
Amateur P.M.R. Marine

UPPINGTON
Tele-Radio and more Ltd
12-14 PENNYWELL ROAD, BRISTOL, BS5 8TJ

KENT

HEWARD'S HOME STORES LTD. (Est. 1963)
822/4 Kingstanding Rd., Birmingham
B44 9RT. Tel. 021-354 2083
G4RJM with 38 years in The Radio Trade
Ham Equipment urgently wanted!
Open: Mon-Sat 9-6

ADVERTISE YOUR
BUSINESS HERE
TEL: 01-437 0699

THANET ELECTRONICS
95 Mortimer St, Herne Bay
Tel: (02273) 89464
Open Mon-Sat 9-5.30pm
except Thursday 9-1pm

Technical enquiries G4STG

NEW IDEA LTD
133 Flaxley Road,
Stechford, Birmingham
Stockists of Yaesu, Trio, Kenwood,
Totsuka, Tonna Antennas, Bantex.
Full servicing repairs on all makes of
amateur radio. Open Mon-Sat, 10am-7pm,
Sundays, 10am-1pm.
Tel: 021-784 3129

SALES G4SOV

BUCKS

Photo Acoustics Ltd. • OF NEWPORT PAGNELL •

See the Professionals

JAYBEAM, WELZ, DAIWA
58 High St, Newport Pagnell
Milton Keynes, Bucks
Tel: 0908 610625

SCARAB SYSTEMS
AMATEUR RADIO SOFTWARE
ICOM STOCKISTS
29 Stafford Street, Gillingham
0634-570441

WARD ELECTRONICS

DIAWA LOWE PRODUCTS COMMODORE COMPUTERS
HOKUSHIN I.C.S AMTOR/RTTY EQUIPMENT R5GB BOOKS
GSLIV PCBs FOR SSTV/RTTY FOR RADIO ENTHUSIASTS

Soho House (1st Floor), 362-4 Soho Road
Handsworth, Birmingham B21 9QL
Tel: 021-554 0708 (Closed Mondays)

CHESHIRE

AMTRONICS (TONBRIDGE) G4 SYZ THE AMATEUR RADIO SPECIALISTS IN KENT

DW ELECTRONICS G3X CF
Amateur Radio Supplies
71 Victoria Rd, Widnes
Tel: 051-420 2559
Open Mon-sat 9-6 (closed Weds) Sun 9.30-12
We supply Yaesu, Trio, Kenwood, Tonna, Jaybeam,
Microwave Modules, Datongs etc

IT'S AMATEUR RADIO
from AMTRONICS

8 Tollgate Buildings
Hadlow Road, Tonbridge, Kent
Tel: (0732) 361850
FDK, AZDEN, YAESU, JAYBEAM,
FORTOP, DATONG, etc.

R. Withers Communications

584 Hegley Road West,
Oldbury, Warrley B68 0BS
Tel: 021-421 8201/2 Tel: 021-550 9324
Opening hours: Mon-Sat 9.30-5.30pm
Late night Thursday 8pm
For all your communication requirements.

ESSEX

LANCASHIRE

ARROW
Electronics Ltd
5 The Street, Hatfield, Peverel
Nr. Chelmsford, Essex CM8 3YL
Tel: 0245 381673/381626

Trio/Kenwood, Tonna, Welz, T.E.T
K.D.K., Daiwa, Tono, Tasco

AMATEUR ELECTRONICS U.K./HOLDINGS



Yaesu, Ten J-Elem, Frequency
Counters, Drea, Datong, FT101
Experts. Repairs 6JS6C, 12BY7A,
8KDG, RF Clipper, Double Balanced
Mixer, Wave Kit etc. S.A.E. 14p, 15
min. Junc. 31 M8. Free parking.
48 Johnston Street
Blackburn B22 1EP.
02541 59595
CLOSED THURSDAYS

AUTRONICS

142 Priory Road, Hall Green
Birmingham B28 0TB Tel: 021-474 4638
10.30am-6pm Tues-Fri. Closed Mon.
Sat 10-5. Closed lunch 2-3
Surplus equipment/components &
P.C.B assembly

HAMPSHIRE

LEICESTERSHIRE

GREATER MANCHESTER

CALBRESO LTD
258 Fratton Road
Portsmouth
Tel. 0705 735003
Open 10.30am-6pm 6 days
Sunday by appointment
COMMUNICATIONS EQUIPMENT
COMPONENTS, BOOKS, ACCESSORIES

ELLIOTT ELECTRONICS
FOR THE RADIO ENTHUSIAST

28-28 BRAUNSTON GATE,
LEICESTER. TEL: 553293
Open: Mon-Sat 9.00am to 5.30pm



BETA COMM

Open 7 days a week
Ham Radio CB & TV. 27 + 934 MG combined rig
Computer software • Aerial fitting service
231 Chorley Road, Swinton, Manchester
Tel: 061-793 1010

EMPORIUM GUIDE

NORFOLK

SPANNER CITY CB CENTRE



Open 6 days
9am-6pm

Parkside Garage
Thursford
Fakenham
Tel: Thursford
402

Grandstand
LA 83
27 to 934 MHz
TRANSVERTER

D.P. HOBBS (Norwich) Ltd

13 St. Benedicts Street, Norwich
Tel: 615786

Open Mon-Sat 9-5.30
Closed Thurs

Stockists of:
YAESU, FDK, ICOM, JAYBEAM
& Electronic Component Specialists

Eastern Communications



31 Cattle Market Street
NORWICH

(0603) 667189

OPEN: 9.30-5.30 Mon-Fri
9.30-5 Sat

MAIL ORDER



NOTTINGHAM

SP ELECTRONICS

48 Limby Rd
Huckhall, Nottingham
Tel: (0602) 640377
open Monday-Saturday
8.30-5.30

**ADVERTISE
YOUR BUSINESS
HERE**
Tel: 01-437 0699

SCOTLAND

JAYCEE ELECTRONICS

JOHN GM30PW

20 Woodside Way, Glenrothes, Fife KY7 5DF
Tel: 0692 756862
Open: Tues-Sat 9-5.
Quality secondhand equipment in stock. Full range of TRIO
goodies. Jaybeam - Microwave Modules - LAR.

SOMERSET

G6HKT **AVCOMM LTD** G8KVG
25 Northoad Street,
Glastonbury
Tel: 0458-33145
Open 9.30-5.30. Closed Wed

SUSSEX

SOUTHDOWN
RADIO
SUPPLIES
40 TERMINUS RD (opp.
EASTBOURNE Railway
Tel: (0323) 638361 Stn.)
Open: Mon-Sat 10-6 (Closed Tues)
Stockists of: Yaesu, Trio, Tonna, FDK etc +
secondhand and ex-Government equipment in
stock

SURREY

GUILDFORD COMMUNICATIONS

34 Aldershot Rd., Guildford

Open Mon-Fri 8am-6.30pm
Sat 8am-5.30pm

Secondhand wanted



ICOM
IFDK
TRIO



0483-574434

TYNE & WEAR

Approved
Dealer

ALYNTRONICS



129 Chillingham Rd, Newcastle-upon-Tyne
Tel: 0632 761002
Open: Tues-Sat 10am-6pm

WILTSHIRE

PACE ELECTRONICS

76 Victoria Road, Swindon
Tel: (0793) 46807

Yaesu equipment, BBC Computers + Software for the
Spectrum, Commodore 64 & Amtror.
Open 9-5 6 days a week
We do everything for the BBC

YORKSHIRE

4 Cross Church St, Huddersfield Tel:
Open: 6 days 9-5.30. 0484 20774

Closed Weds. Thurs 9am-8pm
G4MH Mini Beam



'Always a good selection of new & 2nd hand equipment in stock'

Amateur Radio Shop

DISCOVER THE WORLD WITH AMATEUR RADIO FROM
Sales 27 Cookridge Street Leeds LS2 3AG
LEEDS 452657 OPEN MON-SAT
9am-6pm
the PROFESSIONALS!

TRIO ICOM YAESU
LEEDS: AMATEUR RADIO MAIL ORDER & SERVICE DEPT. OPEN MON-FRI
60 GREEN ROAD MEANWOOD LEEDS LS8 4JP TEL: 782274 9.30am-5pm
BRITISH MADE LAR PRODUCTS

TELECOM

6 New Street, Barnsley
South Yorkshire
Tel (0226) 5031
Specialists in Yaesu, Icom
and So-Kamp

Please include my business details in the
next available issue of Ham Radio Today

Only £17.50 per insertion, call us
for series discounts on 01-437 0699

Business Name:

Address:

Tel. No:

Open Hrs:

Contact (Office Use Only):

Post to: Emporium Guide, Ham Radio Today,
1 Golden Square, London W1.

Lineage:

35p per word (minimum 15 words)

Semi Display: (minimum 2 cms)

£7.00 per single column centimetre

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

Advertisements are accepted subject to the terms and

conditions printed on the advertisement rate card (available on request)

01-437 0699

EXT 332

Send your requirements to:

Debbie Miller

ASP Ltd.,

1 Golden Square,
London W1

EQUIPMENT

ALPHA KEYS

Precision engineered keys for the connoisseur. Twin or single paddle keys individually made to be one of the smoothest and lightest movements ever. For the fast operator.

CAVITY WAVEMETER

One wavemeter to cover 144MHz to over 2500MHz. Can measure RF as low as 50 Milliwatts with suitable meter. Also now short version to cover 430MHz to over 2500MHz.

10GHz WAVEMETER KIT

A pre machined cavity to make a 10GHz wavemeter using your microphone. Can be fixed direct to your wave guide.

COAXIAL RELAY KITS

The cavity block is pre machined to take your BNC or N type sockets.

Send large SAE for full information to:

PAUL BERGENT G4ONF
6 GURNEY CLOSE
COSTESSEY
NORWICH NR5 5HB
Tel: (0603) 747782



ALL AMATEUR AND CB NEEDS
ICOM, TRIO and YAESU, CYBERNET
HARBARD and UNIDEN.
TAGRA, G.WHIP, HOXIN, MICRODOT
RTTY, SWR & power meters.
Receivers & linears. Plus all other
accessories.
Aerial Fitting Service
231 Chorley Rd., Swinton,
Greater Manchester.
Tel: 061-793-1010

BRITISH TELECOM plug sockets & leads etc. Tel: C.W.A.S (0274) 731532. Or visit our showroom opposite Odsal Stadium, Bradford.

SOFTWARE APPLICATIONS

Special prices on surplus equipment

Racal RA17 Receivers High grade communications receivers 500KHz-30MHz in 30 effective bands. From £175. **Eddystone receiver** 730/4 500KHz-30MHz in 5 bands £1.45. All in excellent condition. Can £15.
TANYO-RP8880 9 Bands Portable Communications Receiver £125.00. High Westminster W15 Low band A.M. £30 p&p £2.50. 27 foot telescopic mast with guys, insulator, etc. £25 collected. High impedance headphones with boom mike new £7.50.
Avo valve testers £35 p&p £4. **New 28 range digital multimeters** £40.25
PCR Receivers LW/MW/SW Untested less PSU £20 p&p £5. **12' Whip aeriols** £4 p&p £1.50. **Creed teleprinters** £25. Various single and double beam oscilloscopes, signal generators, valve testers, output meters etc always in stock.
Surplus circuits Book containing circuits and notes on many surplus receivers, transceivers etc. £7.50. **Send 50p for illustrated catalogue** includes £1 voucher. Over 500 sets in stock. **Avo amateur rigs WANTED** for cash.

New shop open at 218 St Albans Road.
Come and see the bargains

WEIRMEAD LIMITED, 129, St Albans Road, Watford Herts

Telephone Watford 49456

Access/Visa cards welcome.

CARDS, STICKERS & BADGES

DX QSL CARDS display your best cards in our clear plastic hanging wallets, holds 20 cards. Pack of 3 £2.20. Viola Plastics, Dept HRT, 36 Croft Road, Hastings, Sussex.

RUBBER STAMPS. Personalise your QSL, Special designs no problems. Discount for quantity. Two day service. S.A.E. for catalogue. Ben Nevis, 42-44 Princes Rd., Hull. (0482) 48134.

QUALITY

Personalized QSL's cards any quantity from £11.00

Nutley Press, 11 Barons Way
Woodhatch, Reigate, Surrey
Tel: Redhill 71023

LISTENER & QSL CARDS. Quality printing on coloured & white Glass Card at competitive prices. S.A.E. for samples: S.M. Tatham, "Woodside", Orchard Way, Fontwell, Arundel, W. Sussex.

PLASTIC BUSINESS AND MEMBERSHIP CARDS



QUALITY RUBBER STAMPS, club emblems from 85p each completely mounted address stamps £2.75. Free catalogue: Jones (HRI) St Ivy, North Rd., Queenborough, Kent. (0795) 665789.

MORSE SOFTWARE

MORSE READING PROGS.

Work on clean signals without hardware interface.

ZXB1 1K UNEXPANDED MEMORY Translated code with word and line spaces for easy reading. Automatic scroll action. £7 Incl.

SPECTRUM 16/48K Scroll action with 10-page scrolling memory, instantly accessible page by page. £8 Incl. All types variable speeds. Feed signal directed into EAR socket.

Pinehurst Data Studios
69 Pinehurst Park, West Moors
Wimbome, Dorset BH22 0BP

CBM 64, VIC20, Spectrum, ZX81-16K MORSE TUTOR Absolute beginner to any test standard. Teaches in easy stages. Letters, figures, words, plain language.
You won't find a better program
QTH LOCATOR Worldwide. Locator or lat & long. Distance, beam heading, VHF contest points and total.
RAE MATHS TUTOR All you need to become perfect. VIC 20 needs expansion.
All programs are menu-driven easy to use and come with full instructions.
Only £6 each, inc. p&p 1st Class by return.
technical software
Fron, Casarea, Caernarfon LL54 7RF
Tel: 0286 881886

RTTY

COMPUTER RTTY

Use your micro to transmit and receive RTTY

PL1 - PLL RTTY Terminal unit
170Hz Shift Transmit & receive
Also handles ASCII TTL in/out
Kit £13.50 Built £17.50
FP1 - Two channel active filter & PSU
for PL1. Requires 15/0/15v AC.
Kit £7.25 Built £10.75

Software for the DRAGON 32
RTTY send-recv program by G4BMK

Split screen receive - Type ahead buffer. QSO review & many other features.

Cassette £12.00
ROM Cartridge £21.00

MORSE transceive program up to 150 wpm!
Cassette £9.75 Cartridge £18.50
Hardware interface also available.

Please add postage to all orders -
U.K. 60p Overseas £1.50
Other hardware available for the DRAGON 32

For further details & full price list please send LARGE S.A.E. to:-

PNP COMMUNICATIONS
62 Lawes Avenue, Newhaven
East Sussex BN9 9SB
P. Simmons G3XUS
Tel: (0273) 514465
Callers by appointment only please.

SURVEILLANCE DEVICES

MICRO-MINI TRANSMITTERS

— all supplied ex-stock, return post delivery, no special equipment required, built, tested, with instructions.
CT10H, 4 mile range, broadcast quality speech pick-up £13.98.
CT10M, prof grade, extra high power, tunable freq 70-120MHz variable microphone sensitivity, £19.48.
CT10MB, as above + unique dual microphones to eliminate echoes, noise etc £21.40.

All specialised requirements catered for.
EVEN RADIO STATIONS — + telephone line recorded device.

Please enquire: 081-905 1040.
S.A.T. ELECTRONICS
164 Washway Rd, Sale, Cheshire M33 1RH

MICRO-TRANSMITTERS. Professional grade. Range 6 miles on VHF/FM (90/110 MHz). Kit £4.50. Built £6.25. D.E.G.A.S. (HR), 15 Windmill Gardens, Whixall, Whitchurch, Shropshire.

AERIALS

AERIAL WIRES & ACCESSORIES
Hard drawn copper wire 140ft 14swg £7.90 50 metres 16swg £6.90 10 metres 12swg soft enamelled copper wire £3.50. 50 metres 1.4mm soft enamelled copper wire £5.75. G5RV Type Aerials. 1/2 size £12.00. Full size £13.95. 4mm Polypropylene Rope 50 metres £3.95. 4mm Nylon Guy Rope 50 metres £6.90. Ceramic Egg Insulators Large 50p. Small 40p. All items postage paid.

S.M. TATHAM, 1, Orchard Way
Fontwell, Arundel, West Sussex

IF YOU
SPECIALISE
IN HAM
EQUIPMENT
AND WANT
TO BUY, SWOP
OR SELL IT,
RING DEBBIE
ON
01-437 0699

HAM

RADIO

TODAY

ONLY
£11.45
INC. P&P!

MORSE COURSE


The most effective route yet to your Class A amateur licence!

Professionally produced for HAM RADIO TODAY by Shirley Hesketh G4HES and Ron Ray G3NCL, this advanced interactive learning system makes use of the stereo cassette format to provide tuition to the 12wpm test standard.

With its carefully designed structure, we think that the HRT MORSE COURSE is more effective than either morse classes or electronic morse generators.

Based on TWO C-60 cassettes, it offers the controlled prompting so necessary for the initial stages of morse tuition, followed by carefully paced test material to bring the student up to speed. Full tuition notes are provided with the cassettes.

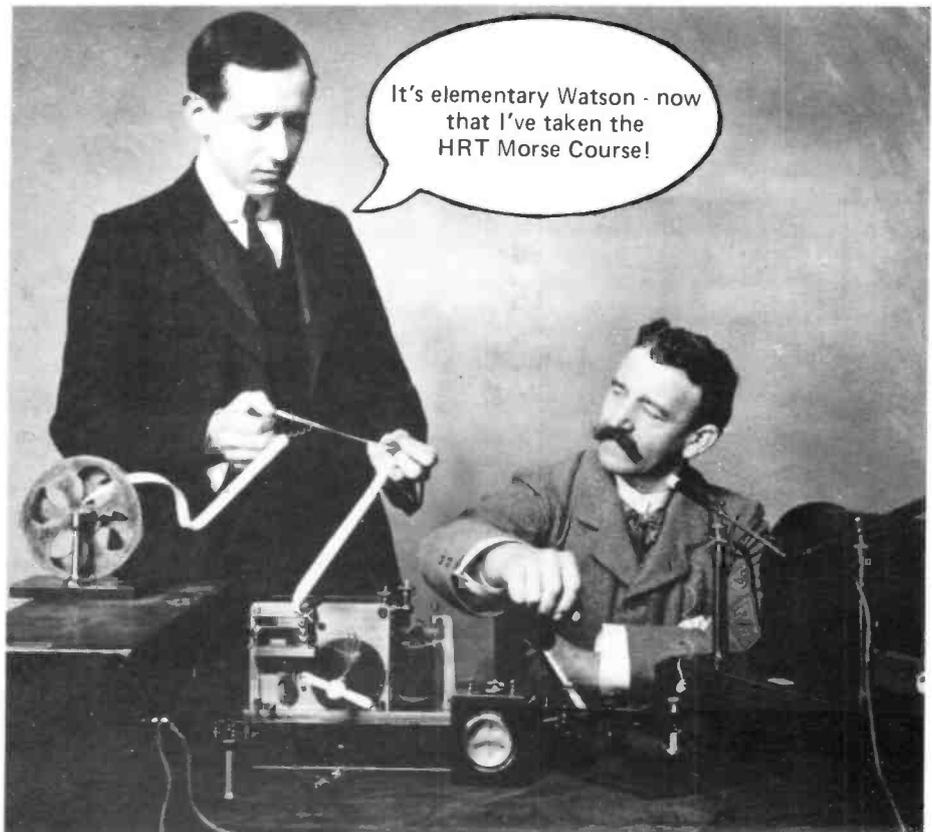To receive your MORSE COURSE simply fill in the coupon below and return it to: 'HRT MORSE COURSE', Argus Press Software, No. 1 Golden Square, London W1R 3AB.



Photograph reproduced by kind permission of Marconi Ltd

Please send me the 'HRT Morse Course' at £11.45 all inclusive of P & P and VAT.
I enclose cheque/PO for £..... (payable to ASP Ltd) OR Debit my Access/Barclaycard (delete as necessary).

Please use BLOCK CAPITALS
Name (Mr/Mrs/Miss)

Address

Postcode

Signature

Date

Please allow 21 days for delivery

GAMMA TWIN

**2 METRE FOLDED
1/2 WAVE ANTENNA**

Copyright Gamma Aerial Products 1982

This antenna is based on the very popular and successful 'SLIM JIM' design.

The GAMMA TWIN has the following unique features:

- ★ VERY LOW ANGLE OF RADIATION
- ★ ADJUSTABLE RADIATOR. (140-150 MHZ)
- ★ COMPLETELY WEATHERPROOF CONNECTING BOX
- ★ VERTICAL FIX DIRECTLY TO MAST

£7.95

incl VAT
- £1.15 p&p

Dewsbury Electronics, 176 Lower High Street,
Stourbridge, West Midlands.

Telephone: Stourbridge (0384) 390063.
Instant finance available subject to status.
Written details on request.

Closed Monday.



TAU

**TAU SYSTEMS LTD,
51 GREENHEY PLACE,
EAST GILLIBRANDS,
SKELMERSDALE,
WN8 92A**

**ATU KITS
CAPACITOR KITS
BALUNS
AERIAL FEEDER
SPREADER KITS**

Phone
0695-24662

Phone
0695-24662

TAU Old Fashioned Radio Engineering enables our Aerial Tuner Units to perform at an unsurpassed High Level, by virtue of being infinitely Variable they will tune almost any Transceiver/Aerial combination to the Optimum.

The best Transceiver In the World is only as good as the Aerial System its obliged to operate through — Realise its Full Potential with a Tau ATU.



THE ULTIMATE SUPER-TRANSMATCH ATU


Send for free colour brochure on full range. ATUs, Roller Coasters, Open wire antennas, split stator capacitors.

The Laws of Physics haven't changed over the years. Get back to Basic Principles and enjoy complete Signal Readability and Full Strength — courtesy of Tau. Trade enquiries from UK & Overseas welcome

TAU SYSTEMS LTD — NOBODY MATCHES UP TO US!

GENERAL COVERAGE RECEIVER KIT FCR 130

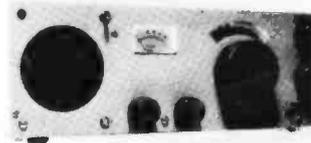Model FCR 130 Receiver kit
ONLY £75.30 inc VAT. Post & Packing £2.40



- ★ 30:1 Geared analogue tuning
- ★ 3 Band switch with spare position
- ★ Tape record socket
- ★ Headphone socket
- ★ Signal Meter
- ★ Internal speaker + On/Off sw.
- ★ A.F. Gain and Tone Control
- ★ C.W. A.M. SSB.

This is a complete kit which allows you to build and learn as you go.

Suitable for anyone who has an interest in radio and can manage a soldering iron. It really is within the scope of most beginners. You don't have to be a 'semi-professional amateur' to understand how it works as we supply very comprehensive and complete instructions, written in plain language. Well spaced components so its OK for fat fingers! The receiver tunes, in 3 bands from 1 to 30 Mhz. Solid aluminium tuning and control knobs and base panel. Black anodised front panel.

Nice to build... nice to look at... nice to own.



COMMUTECH (Devon) LTD
Chapel Street, Holsworthy,
Devon EX22 6AR Tel: (0409) 253504