

Radio Call Book Magazine and Technical Review

VOL 13 #3
MARCH 1932

Established

1921

25¢

March, 1932

In This Issue:

Automobile Radio Receivers
Television on a Light Beam
Television and Sound Films
Television Notes
Photo-electric Cells
Radio Controlled Aeroplane Movements
Wavemeter for Service Men
Linear Amplifiers in Broadcasting
Long Line Frequency Control
Notes on Distortion


Performance Curves and Schematics of:

Crosley 127, General Electric K-62, Gulbrandsen 23,
Howard AVH, Kennedy 56, Sparton 15, Stewart-
Warner R-102A, United American Bosch 31, U. S.
Radio & Television Apex 10B, Zenith 91

*Frequency Assignments of All Broadcast,
Short Wave Relay, Police, and Visual Stations*

SERVICE - ENGINEERING - SALES

A MIGHTY INFLUENCE

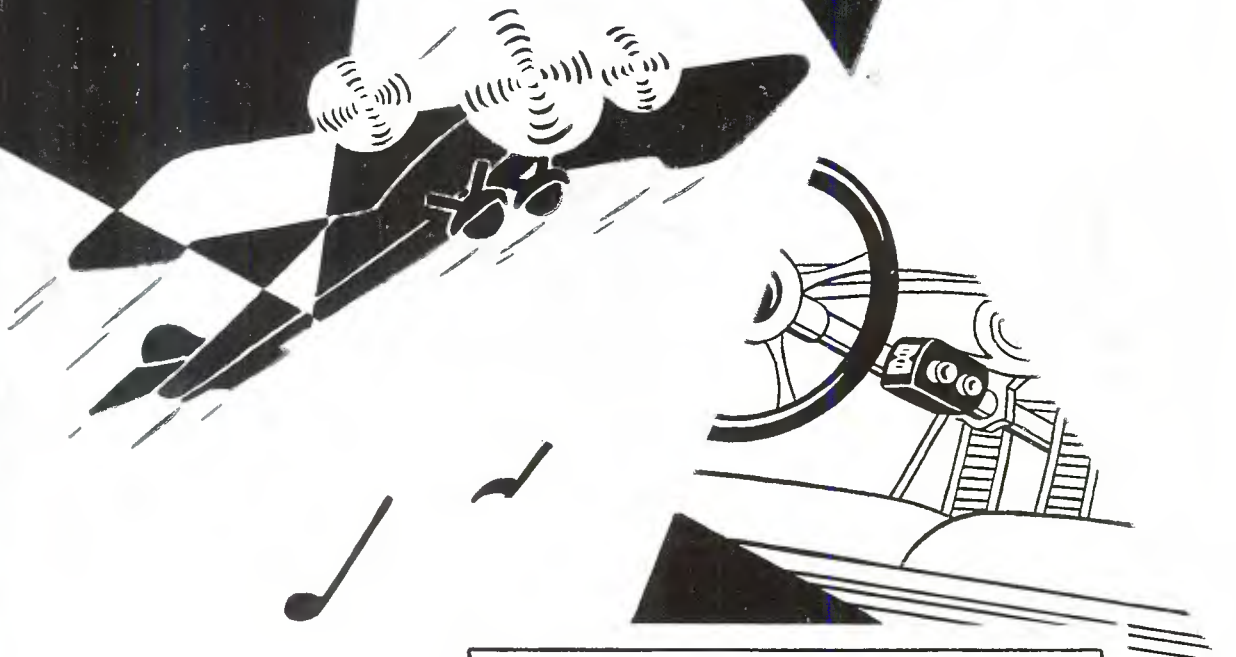

MODERN—modern as the automotive industry itself is the new **MOTOMASTER**, the first super-heterodyne for motor vehicles. After many years of pioneering **MOTOMASTER** takes pride in announcing this new marvel. Endowed with superlative, unflinching performance and superb colorful tone, it is a magnificent achievement. It typifies modern engineering skill and reveals revolutionary characteristics. **MOTOMASTER** is the acclaimed leader.

Accepted as standard it can be installed in all types of motor vehicles within an hour. **MOTOMASTER** is a genuine contribution to the motoring world.

Over 27,000,000 motor vehicles are registered in the United States, scarcely 2 per cent radio equipped. More than one million auto-radio receivers will be sold in 1932.

Through the extensive merchandising program now under way, **MOTOMASTER**, a mighty influence, is opening new markets, winning public acceptance and becoming a definite source of profit to leading distributors and dealers.

HERE IS YOUR OPPORTUNITY TO CASH IN ON THIS VAST MARKET—Some valuable territories still open. Consult the nearest **MOTOMASTER** distributor or wire for liberal franchise plan immediately.

MOTOMASTER
Radio

LICENSED UNDER R.C.A. PATENTS

536 N. MICHIGAN BLVD., CHICAGO


MOTOMASTER Super HETERODYNE
R.C.A. AUTO RADIO

TRADEMARK REGISTERED

GATENBY

This advertisement is one of a series appearing in leading trade and class publications that will reach over two million prospective purchasers

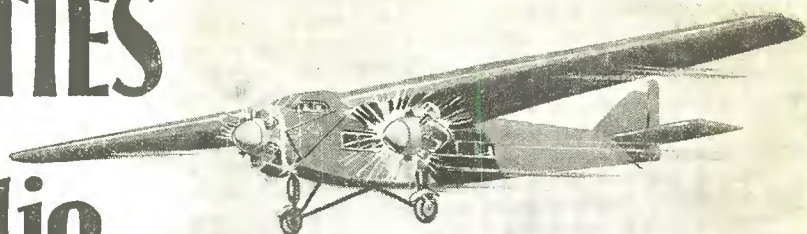OPPORTUNITIES *are many* for the Radio Trained Man



Don't spend your life slaving away in some dull, hopeless job! Don't be satisfied to work for a mere \$20 or \$30 a week. Let me show you how to get your start in Radio—the fastest-growing, biggest money-making game on earth.

Jobs Leading to Salaries of \$50 a Week and Up

Prepare for jobs as Designer, Inspector and Tester—as Radio Salesman and in Service and Installation Work—as Operator or Manager of a Broadcasting Station—as Wireless Operator on a Ship or Airplane, or in Talking Picture or Sound Work—HUNDREDS of OPPORTUNITIES for a real future in Radio!

Ten Weeks of Shop Training

We don't teach by book study. We train you on a great outlay of Radio, Television and Sound equipment—on scores of modern Radio Receivers, huge Broadcasting equipment, the very latest and newest Television apparatus, Talking Picture and Sound Reproduction equipment, Code Practice equipment, etc. You don't need advanced education or previous experience. We give you—RIGHT HERE IN THE COYNE SHOPS—the actual practice and experience you'll need for your start in this great field. And because we cut out all useless theory and only give that which is necessary you get a practical training in 10 weeks.

TELEVISION *and* TALKING PICTURES

And Television is already here! Soon there'll be a demand for THOUSANDS of TELEVISION EXPERTS! The man who learns Television now can have a great future in this great new field. Get in on the ground-floor of this amazing new Radio development! Come to COYNE and learn Television on the very latest, new-

est Television equipment. Talking Picture and Public Address Systems offer opportunities to the Trained Radio Man. Here is a great new Radio field just beginning to grow! Prepare NOW for these wonderful opportunities! Learn Radio Sound Work at COYNE on actual Talking Picture and Sound Reproduction equipment.

All Practical Work At COYNE In Chicago

ALL ACTUAL, PRACTICAL WORK. You build radio sets, install and service them. You actually operate great Broadcasting equipment. You construct Television Receiving Sets and actually transmit your own Television programs over our modern Television equipment. You work on real Talking Picture machines and Sound equipment. You learn Wireless Operating on actual Code Practice apparatus. We don't waste time on useless theory. We give you the practical training you'll need—in 10 short, pleasant weeks.

Mail Coupon Today for All the Facts



Many Earn While Learning

You get Free Employment Service for Life. And don't let lack of money stop you. Many of our students make all or a good part of their living expenses while going to school and if you should need this help just write to me. Coyne is 32 years old! Coyne Training is tested—proven beyond all doubt. You can find out everything absolutely free. Just mail coupon for my big free book!

H. C. Lewis, Pres. RADIO DIVISION Founded 1899
COYNE Electrical School
500 S. Paulina St., Dept. 32-5H, Chicago, Ill.

H. C. LEWIS, President

Radio Division, Coyne Electrical School
500 S. Paulina St., Dept. 32-5H, Chicago, Ill.


Dear Mr. Lewis:— Send me your Big Free Radio Book, and all details of your Special Offer.

Name

Address

City State

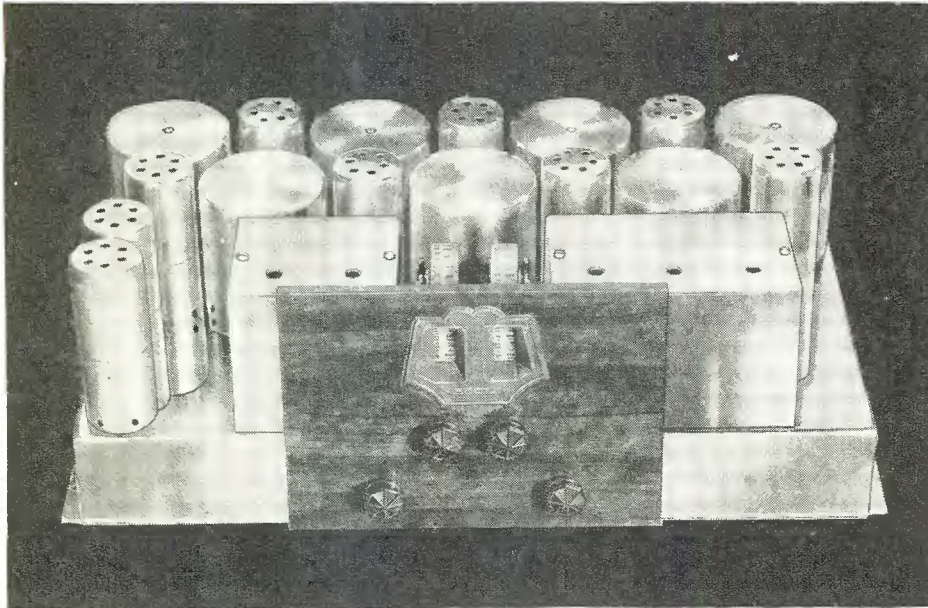The SCOTT 15-550 METER ALL-WAVE *is the only*



living in 63 foreign countries have voluntarily written their testimony of the Scott All-Wave's prowess as a dependable 'round the world receiver. Six big volumes of unsolicited praise from over 600 owners—and there are hundreds more Scott All-Wave users who are too busy listening to the whole world, to write us!




JOAK
JAPAN



ZEESEN
GERMANY

Expect Great
Things

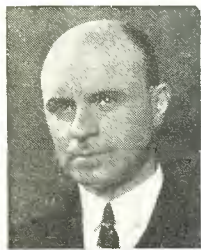SINCE the advent of the Scott All-Wave 15-550 meter superheterodyne, this receiver has become the preference of extremely particular listeners, the world over. It has become the radio of Kings and Presidents—of American Consuls abroad and of Foreign Consuls here—



E. H. SCOTT
Pioneer Builder of
World Record Receivers

of music masters—of broadcasting stations who use it to pick up short wave transmissions for re-broadcast—and it has become the dependable instrument of radio broadcast advertisers who need a receiver with a wide daytime range and with tonal capability by which the quality of advertising broadcasts may be accurately checked. And its owners have written enough praising letters about this receiver to fill six big volumes! Think! Not six volumes of ordinary testimonial letters, expressing mere satisfaction, but rampantly enthusiastic letters that tell of loud, clear, perfect reception from stations 7,000 to 10,000 miles away. They're letters from American owners who tune in Europe and the Orient as fancy dictates. And there are letters from foreign owners, men and women located at all points of the globe, who listen to America and other far-off lands with their Scott All-Wave receivers.

Scott owners living in every state in the Union have written, just to tell us that the Scott All-Wave they purchased, gives them more than the results we promised them—more than we are promising you here. And people

SPECIFICATIONS

Custom built in the laboratory—by laboratory experts and entirely to laboratory standards. Superheterodyne circuit. Covers all wave lengths 15-550 meters. Twelve tubes. Pre-selector R. F. stage. Three I. F. stages. Double push-pull audio. Perfectly matched speaker. All coils treated to withstand climatic extremes. Chassis and amplifier chromium plated.



VK3ME
AUSTRALIA

Order it too, in full belief that you will hear Germany, France, Holland, Australia, Indo-China, South America, Central America, Cuba, and the other strange places you've always wondered about. You'll hear them with your Scott All-Wave—and with perfect clarity and exact tone! Then remember, your Scott All-Wave is guaranteed for five full years against defect in material or workmanship—the broadest, most completely protective guarantee ever placed on radio equipment.

Result of Round-the-World Research

The Scott All-Wave was not designed to be just a good receiver for domestic reception. Instead, it was designed and built especially for foreign reception, by an engineer who has made 3 complete trips around the globe to study radio conditions—and overcomes the difficulties heretofore encountered in such work. Perfected for reception of foreign stations, the Scott All-Wave automatically became the most efficient receiver possible to buy, for domestic work.

The E. H. SCOTT RADIO LABORATORIES, INC.


(Formerly Scott Transformer Co.) • 4450 Ravenswood Avenue • Dept. CB3 • Chicago, Ill.



G3SW ENGLAND



LSX SOUTH AMERICA

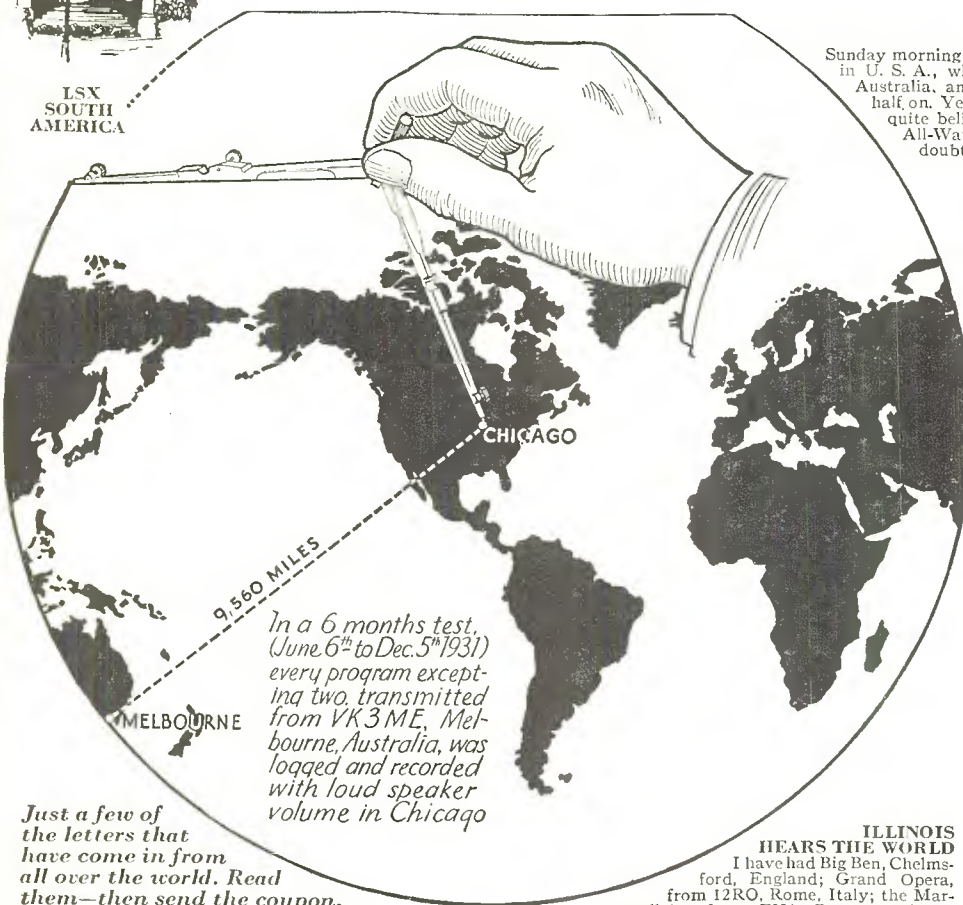

In a 6 months test, (June 6th to Dec. 5th 1931) every program excepting two, transmitted from VK3ME, Melbourne, Australia, was logged and recorded with loud speaker volume in Chicago

Just a few of the letters that have come in from all over the world. Read them—then send the coupon.

NEW ZEALAND REGULARLY

Have had 5 nights consecutive reception of complete program from 2YA, Wellington, New Zealand. One night I had them for nearly 3½ hours, using an aerial only 49 ft. long.

A. R. Miller, Calif.

CONNECTICUT HEARS EGYPT

Reception on short wave nothing short of marvelous. I picked up the Belgenland, in Alexandria Harbor, Egypt. Australia comes in as loud as a local.

J. B. Tracy, Conn.

ILLINOIS HEARS THE WORLD

I have had Big Ben, Chelmsford, England; Grand Opera, from I2RO, Rome, Italy; the Marseillaise, from FYA, France, and the Laughing Jack Ass, from VK2ME, Sydney, Australia. I am writing to express to you my greatest thrill since I began twisting the dials.

G. Bermel, Illinois.

RECORDED AUSTRALIA

Last Saturday night I received VK2ME, Australia, loud enough to make a record of it. It suddenly gave me a thrill to hear the announcer say "The time is 20 minutes to 4, Sunday afternoon," when it was 20 minutes to 12 Saturday night here.

J. R. Cole, Miss.

VK2ME TOO LOUD

Sunday morning I was listening to what I thought was a station in U. S. A., when in comes the call-letters, VK2ME, Sydney, Australia, and I only had the volume control turned about half on. Yet it was too loud for room reception. I could not quite believe all the testimonials I read about the Scott All-Wave, but results this morning have removed all my doubts that the Scott is the King of all radio sets.

B. Firmer, Mich.

EUROPE LIKE LOCAL

I am getting England, Italy and France, good as local stations on just an inside aerial.

B. Leger, Mass.

CUBA HEARS CHICAGO

The Scott Receiver is just what we need here in Cuba. On the long wave we have had over 50 stations in U. S.; on the short waves, I have had Schenectady, Pittsburgh, Boston, Chicago, etc. Also Italy, with as much volume as I get Pittsburgh.

B. Chibas, Cuba.

GREECE HEARS THEM ALL

Performance on the set has been very satisfactory. Have been receiving London, Budapest, Prague, and Belgrade, Poulouse, Barcelona, etc., and a score of unknown stations.

M. D. Cenerales, Greece

HAWAII LIKES SCOTT

Station F31CD, Indo-China, comes in every night as clear as a bell, while W2XAF, I can tune in any time of the day they are on the air.

E. Bernard, Hawaii.

THE PHILIPPINES, TOO

The Scott All-Wave Receiver is far beyond my expectations. So far I have logged London, Romanopoli, Radio Colonial France, Moscow, Russia, Saigon, Indo-China, and Japanese stations on short wave.

R. A. Balanquit, P. I.

ITALY LIKE LOCAL

The performance is simply wonderful. The same day the set arrived I got Italy as clear and strong as though it were a local station.

R. Collazo, Porto Rico.

PORTO RICO GETS ENGLAND

Daylight reception of English, French, and Italian stations is constant with loud speaker volume. They come in with a bang.

J. M. Lieber, Porto Rico.

SIAM HEARS EUROPE

Although in a reputed bad location I have logged Chelmsford, Rome, Holland, Paris, and U. S. A. stations with fine volume.

W. Knox, Siam.

SEND COUPON for full Particulars

Read a few of the letters from the six big volumes of praise. They're reproduced on this page. Then send coupon for the whole story of the Scott All-Wave—for particulars of the advanced design and precision engineering and custom construction which make its sensational performance possible. You'll be surprised, too, at its moderate price. Clip the coupon—mail at once.

THE E. H. SCOTT RADIO LABORATORIES, Inc.
 4450 Ravenswood Ave., Dept. CB3, Chicago, Ill.

Send me full details of the Scott All-Wave

SET BUILDER DXER DEALER

Name.....
 Street.....
 Town..... State.....

Radio Call Book Magazine

AND TECHNICAL REVIEW

Established 1921

Advertising Representatives

Chicago—C. O. STIMPSON, Adv. Mgr.
Phone Wabash 1901, 508 South
Dearborn St.
New York—J. J. LAMSON,
Phone Wisconsin 7-5681,
Room 1125, 154 West 42nd St.
Los Angeles—NED BRYDENE-JACK,
Petroleum Securities Bldg.
San Francisco—THOMAS EMORY, Russ Bldg.

Executive Offices:

508 So. Dearborn St., Chicago, Ill.

Member Audit Bureau of Circulations

GEO. H. SCHEER, JR., *Editor*

E. H. PETERSON, *Service Dept.*

MARCH, 1932

Vol. 13, No. 3

Table of Contents

U. S. Broadcasting Stations . . .	6-9	U. S. Radio and Television, Apex 10B	27
U. S. Broadcasting Stations by Frequencies	10	Zenith 91, 92	28
List of Police Broadcasting Sta- tions	11	Service and Repair Section . . .	29-30
U. S. Visual Broadcasting Sta- tions	11	868 Type Phototube	30
U. S. Relay Broadcasting Sta- tions	11	Automobile Radio Receivers .	31-32
Simple Time Chart	11	Notes on Distortion	33-34
Foreign Broadcasting Stations .	12-13	Photo-electric Cells	34
Foreign Short Wave Phone Stations	14	Radio Engineering Section . . .	35-36
Linear Amplifiers in Broadcast- ing	15-16	Wavemeter for the Service Man	37
Sound Films and Television Broadcast	17	Television Note	38
Receiver Performance Curve Section	18	Radio Control and Aeroplanes	38
Crosley 127	19	Sound on Trucks	38
General Electric K-62	20	Long Line Frequency Control .	39
Gulbransen 23	21	Television on a Beam of Light .	40
Howard AVH	22	Voltage Analyses Charts . . .	41-42
Kennedy 56	23	Set Manufacturers and Brand Names	43
Sparton 15	24	New Products Section	44-46
Stewart-Warner R-102A . . .	25	Brief Items Section	47-52
United American Bosch 31 .	26	RMA Television Notes	53
		Blue Print Page	60
		Index to Advertisers	63

Editorial

In answer to many requests received every day for voltage analyses charts for broadcast receivers, we have incorporated this feature beginning this issue. We plan on running the charts for the receivers published for the month, but occasionally they are not immediately available. Now the receiver reports are complete with curves, schematic wiring diagram, and socket voltage chart, all in one issue. We hope this service will find all of the needs our readers may have. Tell us about it.

The feature article this month is the use of linear amplifiers in broadcasting. This comprehensive treatment should give a clear understanding of the subject. Another deals with all phases of automobile radio receivers from the commercial angle and should be of help to the dealer in mapping out his campaign for the next season.

Three television articles will appeal to the television enthusiast and he will always find the latest information on the subject as it is issued to us. For our friends with a mathematical turn of mind, we recommend the notes on distortion in this issue. The history of the development of loud speakers is treated in a general manner on the pages devoted to radio engineering, and of special interest to the service man is the intermediate-broadcast frequency wavemeter write-up given on page 37.

—Editor.



J. E. Smith, President, National Radio Institute, the man who has directed the Home-Study training of more men for the Radio Industry than any other man in America.


YOU'RE WANTED for a Big Pay Radio Job

I'll Train You at Home in Your Spare Time
for **RADIO · TELEVISION · TALKING MOVIES**



Set Servicing

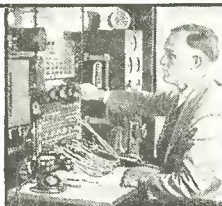Spare-time set servicing is paying N. R. I. men \$200 to \$1,000 a year. Full-time men are making as much as \$65, \$75 and \$100 a week.



Broadcasting Stations

Need trained men continually for jobs paying \$1,200 to \$5,000 a year.



Ship Operating

Radio operators on ships see the world free and get good pay plus expenses.

Aircraft Radio

Aviation is needing more and more trained Radio men. Operators employed through Civil Service Commission earn \$1,620 to \$2,800 a year.



Talking Movies

An invention made possible by Radio. Offers many fine jobs to well-trained Radio men, paying \$75 to \$200 a week.



Television

The coming field of many great opportunities is covered by my course.



IF YOU are earning a penny less than \$50 a week, send for my book of information on the opportunities in Radio. It is free. Clip the coupon NOW. Why be satisfied with \$25, \$30 or \$40 a week for longer than the short time it takes to get ready for Radio?

Radio's Growth Opening Hundreds of \$50, \$75, \$100 a Week Jobs Every Year

In about ten years Radio has grown from a \$2,000,000 to a \$1,000,000,000 industry. Over 800,000 jobs have been created. Hundreds more are being opened every year by its continued growth. Men and young men with the right training—the kind of training I give you—are stepping into Radio at two and three times their former salaries. J. A. Vaughn, 4075 S. Grand Boulevard, St. Louis, Mo., writes: "Before I entered Radio I was making \$35 a week. Last week I earned \$110 selling and servicing sets. I owe my success to N. R. I."

You Have Many Jobs To Choose From

Broadcasting stations use engineers, operators, station managers and pay \$1,200 to \$5,000 a year. Manufacturers continually need testers, inspectors, foremen, engineers, service men, buyers, for jobs paying up to \$7,500 a year. Shipping companies use hundreds of Radio operators, give them world-wide travel with board and lodging free and a salary of \$80 to \$150 a month. Dealers and jobbers employ service men, salesmen, buyers, managers, and pay \$30 to \$100 a week. There are many other opportunities too.

So Many Opportunities Many N. R. I. Men Make \$200 to \$1000 While Learning

The day you enroll with me I'll show you how to do 28 jobs, common in most every neighborhood, for spare-time money. Throughout your course I send you infor-

mation on servicing popular makes of sets; I give you the plans and ideas that are making \$200 to \$1,000 for hundreds of N. R. I. students in their spare time while studying. My course is famous as the one that pays for itself. G. W. Page, 2210 Eighth Ave., S., Nashville, Tenn., writes: "I picked up \$935 in my spare time while taking your course."

Talking Movies, Television and Aircraft Radio are Also Included

Special training in Talking Movies, Television and home Television experiments. Radio's use in Aviation, Servicing and Merchandising Sets, Broadcasting, Commercial and Ship Operating are included. I am so sure that I can train you satisfactorily that I will agree in writing to refund every penny of your tuition if you are not satisfied with my Lessons and Instruction Service upon completing.

64-page Book of Information Free

Get your copy today. It tells you where Radio's good jobs are, what they pay, tells you about my course, what others who have taken it are doing and making. Find out what Radio offers you, without the slightest obligation. ACT NOW!

J. E. SMITH, President
National Radio Institute
Dept. 2CE
Washington, D. C.




THIS COUPON IS GOOD for
One FREE COPY OF MY BOOK *mail it now*

J. E. SMITH, President
National Radio Institute, Dept. 2CE
Washington, D. C.

Dear Mr. Smith:
I want to take advantage to your Special Offer. Send me your two books "Trouble Shooting in D.C., A.C. and Battery Sets" and "Rich Rewards in Radio." I understand this does not obligate me and that no salesman will call.

Name.....
Address.....
City..... State..... "M"

SPECIAL FREE OFFER

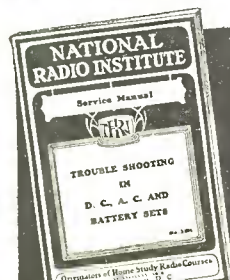

Act now and receive in addition to my big free book "Rich Rewards in Radio," this Service Manual on D.C., A.C., and Battery operated sets. Only my students could have this book in the past. Now readers of this magazine who mail the coupon will receive it free. Overcoming hum, noises of all kinds, fading signals, broad tuning, howls and oscillations, poor distance reception, distorted or muffled signals, poor Audio and Radio Frequency Amplification and other vital information is contained in it. Get a free copy by mailing the coupon.

American Broadcasting Stations

Station assignments shown in the following pages were made by the Federal Radio Commission. This list is revised from issue to issue and is therefore up-to-the-minute. Initials such as E, C, M, and P denote Eastern, Central, Mountain and Pacific time.

- KABC**—1420 kc, San Antonio, Texas, Alamo Broadcasting Co., 100 w, C.
- KARK**—890 kc, Little Rock, Ark., First Church of the Nazarene, 250 w.
- KBPS**—1420 kc, Portland, Ore., Benson Polytechnic School, 100 w, P.
- KBTM**—1200 kc, Paragould, Ark., Beard's Temple of Music, 100 w, C.
- KCRC**—1370 kc, Enid, Okla., Champlin Refining Co., 100 w, C.
- KCRJ**—1310 kc, Jerome, Ariz., C. C. Robinson, 100 w.
- KDBB**—1500 kc, Santa Barbara, Calif., Santa Barbara Broadcasters, Ltd., 100 w, P.
- KDFN**—1210 kc, Casper, Wyo., D. L. Hathaway, 100 w, P.
- KDKA**—980 kc, Pittsburgh, Pa., Westinghouse E. & M. Co., 50,000 w, E.
- KDLR**—1210 kc, Devils Lake, N. D., KDLR, Inc., 100 w.
- KDYI**—1290 kc, Salt Lake City, Utah, Intermountain Broadcasting Corp., 1000 w, M.
- KECA**—1430 kc, Los Angeles, Calif., Earle C. Anthony, Inc., 1000 w, P.
- KELW**—780 kc, Burbank, Calif., Magnolia Park, Ltd., 500 w, P.
- KEX**—1180 kc, Portland, Ore., Western Broadcasting Co., 5000 w, P.
- KFAB**—770 kc, Lincoln, Nebr., KFAB Broadcasting Co., 5000 w, C.
- KFAC**—1300 kc, Los Angeles, Calif., L. A. Bdstg. Co., 1000 w, P.
- KFBB**—1280 kc, Great Falls, Mont., Buttery Broadcast, Inc., 1000 w, M.
- KFBK**—1310 kc, Sacramento, Calif., James McClatchy Co., 100 w, P.
- KFBL**—1370 kc, Everett, Wash., Leese Bros., 50 w, P.
- KFDM**—560 kc, Beaumont, Tex., Magnolia Petroleum Co., 500 w, C.
- KFDY**—550 kc, Brookings, S. D., State College, 500 w, C.
- KFEL**—920 kc, Denver, Colo., Eugene P. O'Fallon, Inc., 500 w, M.
- KFEQ**—680 kc, St. Joseph, Mo., Scroggin & Co., 2500 w, C.
- KFGG**—1310 kc, Boone, Iowa, Boone Biblical College, 100 w, C.
- KFH**—1300 kc, Wichita, Kan., Radio Station KFH Co., 1000 w, C.
- KFI**—640 kc, Los Angeles, Calif., Earl C. Anthony, Inc., 50,000 w, P.
- KFIO**—1120 kc, Spokane, Wash., Spokane Broadcasting Corp., 100 w, P.
- KFII**—1310 kc, Juneau, Alaska, Alaska Elec. Light & Power Co., 10 w.
- KFIZ**—1420 kc, Fond du Lac, Wis., Reporter Printing Co., 100 w, C.
- KFJB**—1200 kc, Marshalltown, Iowa, Marshall Electric Co., 100 w, C.
- KFJE**—1480 kc, Oklahoma City, Okla., National Radio Mfg. Co., 5000 w, C.
- KFJI**—1210 kc, Klamath Falls, Ore., KFJI Broadcasters, Inc., 100 w, P.
- KFJM**—1370 kc, Grand Forks, N. D., University of North Dakota, 100 w, C.
- KFJR**—1300 kc, Portland, Ore., Ashley C. Dixon, KFJR, Inc., 500 w, P.
- KFJY**—1310 kc, Ft. Dodge, Iowa, Cedar Rapids Broadcast Co., w, C.
- KFJZ**—1370 kc, Ft. Worth, Texas, Henry Clay Meacham, 100 w, C.
- KFKA**—880 kc, Greeley, Colo., Mid-Western Radio Corp., 500 w, M.
- KFKB**—1050 kc, Milford, Kan., KFKB Bdstg. Assn., 5000 w, C.
- KFKU**—1220 kc, Lawrence, Kan., University of Kansas, 500 w, C.
- KFKX**—See under KYW.
- KFLV**—1410 kc, Rockford, Ill., Rockford Broadcasters, Inc., 500 w, C.
- KFLX**—1370 kc, Galveston, Texas, Geo. Roy Clough, 100 w, C.
- KFMX**—1250 kc, Northfield, Minn., Carleton College, 1000 w, C.
- KFNF**—890 kc, Shenandoah, Iowa, Henry Field Seed Co., 500 w, C.
- KFOR**—1210 kc, Lincoln, Neb., Howard A. Shuman, 100 w, C.
- KFOX**—1250 kc, Long Beach, Calif., Nichols & Warriner, Inc., 1000 w, P.
- KFPL**—1310 kc, Dublin, Texas, C. C. Baxter, 100 w, C.
- KFPM**—1310 kc, Greenville, Texas, The New Furniture Co., 15 w, C.
- KFPW**—1340 kc, Ft. Smith, Ark., John Brown Schools, 50 w, C.
- KFPY**—1340 kc, Spokane, Wash., Symons Broadcasting Co., 1000 w, P.
- KFQD**—1230 kc, Anchorage, Alaska, Anchorage Radio Club, 100 w.
- KFQU**—1420 kc, Holy City, Calif., W. E. Riker, 100 w, P.
- KFQW**—1420 kc, Seattle, Wash., KFQW, Inc., 100 w, P.
- KFRF**—610 kc, San Francisco, Calif., Don Lee, Inc., 1000 w, P.
- KFRU**—630 kc, Columbia, Mo., Stephens College, 500 w, C.
- KFSO**—800 kc, San Diego, Calif., Airfan Radio Corp., 500 w, P.
- KFSG**—1120 kc, Los Angeles, Calif., Echo Park Eyan. Assn., 500 w, P.
- KFUL**—1290 kc, Galveston, Texas, W. H. Ford, 500 w, C.
- KFUO**—550 kc, St. Louis, Mo., Concordia Theological Seminary, 500 w, C.
- KFUP**—1310 kc, Denver, Colo., Fitzsimmons General Hospital, 100 w, M.
- KFVD**—1000 kc, Culver City, Calif., Los Angeles Broadcasting Co., 250 w, P.
- KFVS**—1210 kc, Cape Girardeau, Mo., Hirsch Battery & Radio Co., 100 w, C.
- KFWB**—950 kc, Hollywood, Calif., Warner Bros. Broadcasting Corp., 1000 w, P.
- KFWF**—1200 kc, St. Louis, Mo., St. Louis Truth Center, Inc., 100 w.
- KFWI**—930 kc, San Francisco, Calif., Radio Entertainment, Inc., 500 w, P.
- KFXD**—1420 kc, Nampa, Idaho, Frank E. Hurt, 100 w, M.
- KFXE**—920 kc, Denver, Colo., Colorado Radio Co., 500 w, M.
- KFXJ**—1310 kc, Edgewater, Colo., Western Slope Broadcasting Co., 50 w, M.
- KFXM**—1210 kc, San Bernardino, Calif., Lee Bros. Broadcasting Co., 100 w, P.
- KFXR**—1310 kc, Oklahoma City, Okla., Exchange Avenue Baptist Church, 100 w, C.
- KFXY**—1420 kc, Flagstaff, Ariz., Mary M. Costigan, 100 w, M.
- KFYO**—1420 kc, Abilene, Texas, Kirksey Bros., 100 w, C.
- KFYR**—550 kc, Bismarck, N. D., Meyer Broadcasting Co., 1000 w, C.
- KGA**—1470 kc, Spokane, Wash., Northwest Broadcasting System, Inc., 5000 w, P.
- KGAR**—1370 kc, Tucson, Ariz., Tucson Motor Service Co., 100 w, M.
- KGB**—1330 kc, San Diego, Calif., Don Lee, Inc., 500 w, P.
- KGBU**—900 kc, Ketchikan, Alaska, Alaska Radio & Service Co., 500 w.
- KGBX**—1310 kc, St. Joseph, Mo., KGBX, Inc., 100 w.
- KGBZ**—930 kc, York, Nebr., Geo. R. Miller, 500 w, C.
- KGCA**—1270 kc, Decorah, Iowa, Chas. W. Greenley, 50 w, C.
- KGCR**—1210 kc, Watertown, S. D., Greater Kampeka Radio Corp., 100 w.
- KGCC**—1200 kc, Mandan, N. D., Mandan Radio Association, 100 w, M.
- KGCC**—1310 kc, Wolf Point, Mont., First State Bank of Vida, 100 w, M.
- KGDA**—1370 kc, Mitchell, S. D., Mitchell Broadcasting Corp., 100 w, M.
- KGDE**—1200 kc, Fergus Falls, Minn., Jaren Drug Co., 100 w, C.
- KGDM**—1100 kc, Stockton, Calif., E. F. Peffer, 250 w.
- KGDY**—1200 kc, Huron, S. D., J. A. Loesch, 15 w, C.
- KGEE**—1300 kc, Los Angeles, Calif., Trinity Methodist Church, 1000 w, P.
- KGEK**—1200 kc, Yuma, Colo., Beehler Elec. Equip. Co., 100 w, M.
- KGER**—1360 kc, Long Beach, Calif., Consolidated Bdstg. Corp., 1000 w, P.
- KGFW**—1200 kc, Ft. Morgan, Colo., City of Ft. Morgan, 100 w, P.
- KGEZ**—1310 kc, Kalispell, Mont., Chamber of Commerce, 100 w, M.
- KGFF**—1420 kc, Shawnee, Okla., KGFF Bdstg. Corp., 100 w, C.
- KGFG**—1370 kc, Oklahoma City, Okla., Oklahoma Broadcasting Co., Inc., 100 w, C.
- KGFI**—1500 kc, Corpus Christi, Texas, Eagle Broadcasting Co., 100 w, C.
- KGFL**—1200 kc, Los Angeles, Calif., Ben S. McGlashan, 100 w, P.
- KGFK**—1500 kc, Moorhead, Minn., Red River Broadcasting Co., Inc., 50 w, C.
- KGFL**—1370 kc, Raton, N. Mex., KGFL, Inc., 50 w, M.
- KGFV**—1310 kc, Kearney, Neb., Central Neb. Bdstg. Co., 100 w.
- KGFX**—580 kc, Pierre, S. D., Dana McNeil, 200 w, C.
- KGGC**—1420 kc, San Francisco, Calif., Golden Gate Broadcasting Co., 100 w, P.
- KGGF**—1010 kc, South Coffeyville, Okla., Powell & Platz, 500 w.
- KGGM**—1230 kc, Albuquerque, N. Mex., New Mexico Broadcasting Co., 250 w.
- KGHF**—1320 kc, Pueblo, Colo., Ritchie & Finch, 250 w, M.
- KGHI**—1200 kc, Little Rock, Ark., O. A. Cook, 100 w.
- KGHL**—950 kc, Billings, Mont., Northwestern Auto Supply Co., 1000 w, M.
- KGIQ**—1320 kc, Twin Falls, Idaho, Radio Broadcasting Corp.
- KGIR**—1360 kc, Butte, Mont., KGIR, Inc., 500 w, M.
- KGIW**—1420 kc, Trinidad, Colo., Leonard E. Wilson, 100 w, M.
- KGIX**—1420 kc, Las Vegas, Nev., J. M. Heaton, 100 w.
- KGIZ**—1500 kc, Grant City, Mo., Grant City Park Corp., 100 w, C.
- KGKB**—1500 kc, Tyler, Tex., Tyler Commercial College, 100 w, C.
- KGKL**—1370 kc, San Angelo, Tex., KGKL, Inc., 100 w, C.
- KGKO**—570 kc, Wichita Falls, Tex., Wichita Falls Broadcasting Co., 250 w, C.
- KGKX**—1420 kc, Sandpoint Idaho, W. W. von Cannon, 100 w, P.
- KGKY**—1500 kc, Scottsbluff, Nebr., Hilliard Co., Inc., 100 w, C.
- KGMB**—1320 kc, Honolulu, Hawaii, Honolulu Broadcasting Co., 250 w, P.
- KGMP**—1210 kc, Elk City, Okla., Bryant Radio & Elec. Co., 100 w, C.
- KGNF**—1430 kc, North Platte, Nebr., H. L. Spencer, 500 w, M.
- KGNO**—1210 kc, Dodge City, Kans., Dodge City Broadcasting Co., Inc., M.
- KGO**—790 kc, San Francisco, Calif., National Broadcasting Co., Inc., 7500 w, P.
- KGRS**—1410 kc, Amarillo, Texas, Gish Radio Service, 1000 w, C.
- KGU**—940 kc, Honolulu, Hawaii, Marion Mulrony, Advertising Publ. Co., 1000 w.
- KGVO**—1420 kc, Missoula, Mont., Mosby's, Inc.
- KGW**—620 kc, Portland, Ore., Oregonian Pub. Co., 1000 w, P.
- KGY**—1200 kc, Lacey, Wash., St. Martins College, 10 w, P.
- KHJ**—900 kc, Los Angeles, Calif., Don Lee, Inc., 1000 w, P.
- KHIQ**—590 kc, Spokane, Wash., Louis Wasmmer, Inc., 1000 w, P.
- KICK**—1420 kc, Red Oak, Iowa, Red Oak Radio Corp., 100 w.
- KID**—1320 kc, Idaho Falls, Ida., KID Broadcasting Co., 250 w, M.
- KIDO**—1350 kc, Boise, Idaho, Boise Broadcasting Station, 1000 w, P.
- KIT**—1310 kc, Yakima, Wash., C. E. Haymond, 100 w, P.
- KJBS**—1070 kc, San Francisco, Calif., Julius Brunton & Sons Co., 100 w, P.
- KJR**—970 kc, Seattle, Wash., Northwest Broadcasting System, Inc., 5000 w, P.
- KLCN**—1290 kc, Blytheville, Ark., C. L. Lintzenich, 50 w, C.
- KLO**—1400 kc, Ogden, Utah, Interstate Bdstg. Corp., 500 w, M.
- KLPM**—1420 kc, Minot, N. D., John B. Cooley, 100 w, C.
- KLRA**—1390 kc, Little Rock, Ark., Arkansas Broadcasting Co., 1000 w.
- KLS**—1440 kc, Oakland, Calif., Warner Bros., 250 w, P.
- KLX**—880 kc, Oakland, Calif., Tribune Pub. Co., 500 w, P.
- KLZ**—560 kc, Denver, Colo., Reynolds Radio Co., Inc., 1000 w, M.
- KMA**—930 kc, Shenandoah, Iowa, May Seed & Nursery Co., 500 w, C.
- KMAC**—1370 kc, San Antonio, Texas, W. W. McAllister, 100 w, C.
- KMBC**—950 kc, Kansas City, Mo., Midland Broadcasting Co., 1000 w, C.
- KMED**—1310 kc, Medford, Ore., Mrs. W. J. Virgin, 100 w, P.
- KMJ**—1210 kc, Fresno, Calif., J. McClatchy Co., 100 w, P.
- KMLB**—1200 kc, Monroe, La., Liner's Bdstg. Station, Inc., 100 w, C.

- KMMJ**—740 kc, Clay Center, Neb., The M. M. Johnson Co., 1000 w, C.
- KMO**—860 kc, Tacoma, Wash., KMO, Inc., 500 w, P.
- KMOX**—1090 kc, St. Louis, Mo., Voice of St. Louis, Inc., 50,000 w, C.
- KMPC**—710 kc, Beverly Hills, Calif., R. S. Macmillan, 500 w, P.
- KMPR**—570 kc, Los Angeles, Calif., KMTR Radio Corp., 500 w, P.
- KNX**—1050 kc, Hollywood, Calif., Western Broadcast Co., 5000 w, P.
- KOA**—830 kc, Denver, Colo., National Broadcasting Co., Inc., 12,500 w, M.
- KOAC**—550 kc, Corvallis, Ore., Oregon State Agricultural College, 1000 w, P.
- KOB**—1180 kc, State College, N. M., N. M. College of Agri. & Mech. Arts, 20,000 w, M.
- KOCW**—1400 kc, Chickasha, Okla., Oklahoma College for Women, 250 w, C.
- KOH**—1370 kc, Reno, Nevada, Jay Peters, Inc., 500 w.
- KOH**—1260 kc, Council Bluffs, Iowa, Mona Motor Oil Co., 1000 w, C.
- KOIN**—910 kc, Portland, Ore., KOIN, Inc., 1000 w, P.
- KOL**—1270 kc, Seattle, Wash., Seattle Broadcasting Co., 1000 w, P.
- KOMO**—920 kc, Seattle, Wash., Fisher's Blend Station, Inc., 1000 w, P.
- KONO**—1370 kc, San Antonio, Tex., Mission Broadcasting Co., 100 w, C.
- KOOS**—1370 kc, Marshfield, Ore., H. H. Hanseth, Inc., 100 w, P.
- KORE**—1420 kc, Eugene, Ore., Eugene Broadcast Station, 100 w, P.
- KOY**—1390 kc, Phoenix, Ariz., Nielsen Radio & Sporting Goods Co., 500 w, M.
- KPCB**—650 kc, Seattle, Wash., Queen City Broadcasting Co., 100 w, P.
- KPJM**—1500 kc, Prescott, Ariz., A. P. Miller, 100 w, M.
- KPO**—680 kc, San Francisco, Calif., Hale Bros. & The Chronicle, 5000 w, P.
- KPOF**—880 kc, Denver, Colo., Pillar of Fire, Inc., 500 w, M.
- KPPC**—1210 kc, Pasadena, Calif., Pasadena, Presbyterian Church, 50 w, P.
- KPQ**—1500 kc, Wenatchee, Wash., Westcoast Broadcasting Co., 50 w, P.
- KPRC**—920 kc, Houston, Texas, Houston Printing Co., 1000 w, C.
- KQV**—1380 kc, Pittsburgh, Pa., KQV Bdstg. Co., 500 w, E.
- KQW**—1010 kc, San Jose, Calif., Pacific Agric. Foundation, 500 w, P.
- KRE**—1370 kc, Berkeley, Calif., First Congregational Church, 100 w, P.
- KREG**—1500 kc, Santa Ana, Calif., Pacific-Western Broadcasting Federation, 100 w, P.
- KRGV**—1260 kc, Harlingen, Texas, KRGV, Inc., 500 w.
- KRLD**—1040 kc, Dallas, Texas, KRLD, Inc., 10,000 w, C.
- KRMD**—1310 kc, Shreveport, La., Robert M. Dean, 50 w, C.
- KROW**—930 kc, Oakland, Calif., Educational Broadcasting Corp., 500 w, M.
- KRSC**—1120 kc, Seattle, Wash., Radio Sales Corp., 50 w, P.
- KSAC**—580 kc, Manhattan, Kan., Kansas State Agricultural College, 500 w, C.
- KSCJ**—1330 kc, Sioux City, Iowa, Perkins Bros. Co., 1000 w, C.
- KSD**—550 kc, St. Louis, Mo., Pulitzer Pub. Co., 500 w, C.
- KSEI**—900 kc, Pocatello, Idaho, Radio Service Corp., 250 w, M.
- KSL**—1130 kc, Salt Lake City, Utah, Radio Service Corp., 5000 w, M.
- KSMR**—1200 kc, Santa Maria, Calif., Santa Maria Radio Co., 100 w, P.
- KSO**—1380 kc, Clarinda, Iowa, Iowa Bdstg. Co., 500 w, C.
- KS00**—1110 kc, Sioux Falls, S. D., Sioux Falls Broadcasting Assn., 2000 w, C.
- KSTP**—1460 kc, St. Paul, Minn., National Battery Broadcasting Co., 10,000 w, C.
- KTAB**—560 kc, San Francisco, Calif., Associated Broadcasters, 1000 w, P.
- KTAR**—620 kc, Phoenix, Ariz., KTAR Broadcasting Co., 500 w, M.
- KTAF**—1240 kc, Ft. Worth, Tex., S. A. T. Broadcasting Co., 1000 w, C.
- KTBR**—1300 kc, Portland, Ore., M. E. Brown, 500 w, P.
- KTBS**—1450 kc, Shreveport, La., Tri-State Broadcasting Co., 1000 w, E.
- KTPI**—1320 kc, Twin Falls, Idaho, Radio Broadcasting Corp., 250 w, M.
- KTSS**—1040 kc, Hot Springs, Ark., Chamber of Commerce, 10,000 w, C.
- KTLC**—1310 kc, Houston, Tex., Houston Broadcasting Co., 100 w, C.
- KTM**—780 kc, Los Angeles, Calif., Pickwick Broadcasting Corp., 500 w, P.
- KTRH**—1120 kc, Houston, Tex., Rice Hotel, 500 w, C.
- KTSA**—1290 kc, San Antonio, Texas, Lone Star Broadcast Co., 1000 w, C.
- KTSL**—1310 kc, Shreveport, La., Houseman Sheet Metal Works, Inc., 100 w, C.
- KTSM**—1310 kc, El Paso, Tex., W. S. Bledsoe and W. T. Blackwell, 100 w, C.
- KTW**—1220 kc, Seattle, Wash., First Presbyterian Church, 1000 w, P.
- KUJ**—1370 kc, Walla Walla, Wash., Paul R. Heitmeier, Inc., 100 w, P.
- KUOA**—1390 kc, Fayetteville, Ark., University of Arkansas, 1000 w, C.
- KUSD**—890 kc, Vermillion, S. Dak., University of South Dakota, 500 w, C.
- KUT**—1500 kc, Austin, Tex., KUT Bdstg. Co., 100 w, C.
- KVI**—760 kc, Tacoma, Wash., Puget Sound Radio Broadcasting Co., 1000 w, P.
- KVL**—1370 kc, Seattle, Wash., KVL, Inc., 100 w, P.
- KVOA**—1260 kc, Tucson, Ariz., R. M. Ricculfi, 500 w.
- KVOO**—1140 kc, Tulsa, Okla., Southwestern Sales Corp., 5000 w, C.
- KVOR**—1270 kc, Colorado Springs, Colo., W. D. Corley, 1000 w, M.
- KVOS**—1200 kc, Bellingham, Wash., KVOS, Inc., 100 w, P.
- KWCR**—1310 kc, Cedar Rapids, Iowa, Cedar Rapids Bdstg. Co., 100 w, C.
- KWEA**—1210 kc, Shreveport, La., Hello World Broadcasting Corp., 100 w, C.
- KWG**—1200 kc, Stockton, Calif., Portable Wireless Tel. Co., 100 w, P.
- KWJJ**—1060 kc, Portland, Ore., KWJJ Broadcasting Co., Inc., 500 w, P.
- KWK**—1350 kc, Kirkwood, Mo., Thos. Patrick, Inc., 1000 w, C.
- KWKC**—1370 kc, Kansas City, Mo., Wilson Duncan Broadcasting Co., 100 w.
- KWKH**—850 kc, Shreveport, La., Hello World Broadcasting Corp., 10,000 w, C.
- KWLC**—1270 kc, Decorah, Iowa, Luther College, 100 w, C.
- KWSC**—1220 kc, Pullman, Wash., State College of Washington, 1000 w, P.
- KWWG**—1260 kc, Brownsville, Texas, Brownsville Herald Publishing Co., 500 w, C.
- KXA**—570 kc, Seattle, Wash., American Radio Tel. Co., 500 w, P.
- KXL**—1420 kc, Portland, Ore., KXL Broadcasters, Inc., 100 w, P.
- KXO**—1500 kc, El Centro, Calif., Irey & Bowles, 100 w, P.
- KXRO**—1310 kc, Aberdeen, Wash., KXRO, Inc., 75 w, P.
- KXYZ**—1420 kc, Houston, Texas, Harris County Broadcasting Co., 100 w, C.
- KYA**—1230 kc, San Francisco, Calif., Pacific Broadcasting Corp., 1000 w, P.
- KYW**—1020 kc, Chicago, Ill., Westinghouse E. & M. Co., 10,000 w, C.
- NAA**—690 kc, United States Navy Department, Washington, D. C., 1000 w, E.
- WAAB**—1410 kc, Quincy, Mass., Bay State Bdstg. Corp.
- WAAF**—920 kc, Chicago, Ill., Drovers Journal Pub. Co., 500 w daytime, C.
- WAAM**—1250 kc, Newark, N. J., WAAM, Inc., 1000 w, E.
- WAAT**—940 kc, Jersey City, N. J., Bremer Broadcasting Corp., 300 w, E.
- WAAW**—660 kc, Omaha, Neb., Omaha Grain Exchange, 500 w daytime, C.
- WABC**—860 kc, New York City, N. Y., Atlantic Broadcasting Corp., 50,000 w, E.
- WABI**—1200 kc, Bangor, Maine, Pine Tree Broadcasting Co., 100 w, E.
- WABO**—See under WHEC.
- WABZ**—1200 kc, New Orleans, La., Coliseum Place Baptist Church, 100 w, C.
- WACO**—1240 kc, Waco, Tex., Central Texas Broadcasting Co., Inc., 1000 w, C.
- WADC**—1320 kc, Tallmadge, Ohio, Allen T. Simmons, 1000 w, E.
- WAGM**—1420 kc, Mars Hill, Me., Aroostook Bdstg. Corp., 100 w.
- WAII**—640 kc, Columbus, Ohio, Associated Radiocasting Corp., 500 w, E.
- WAILR**—1210 kc, Zanesville, O., Roy W. Waller, 100 w, E.
- WAPI**—1140 kc, Birmingham, Ala., Alabama Polytechnic Institute, 5000 w, C.
- WASH**—1270 kc, Grand Rapids, Mich., Kunsky-Trendle Bdstg. Corp., 500 w, C.
- WAWZ**—1350 kc, Zarepath, N. J., Pillar of Fire, 250 w, E.
- WBAA**—1400 kc, Lafayette, Ind., Purdue University, 500 w, C.
- WBAC**—1430 kc, Harrisburg, Pa., Pennsylvania State Police, 500 w, E.
- WBAL**—1060 kc, Baltimore, Md., Consolidated Gas, Elec. Co., 10,000 w, E.
- WBAP**—800 kc, Ft. Worth, Tex., Carter Publications, Inc., 10,000 w, C.
- WBAX**—1210 kc, Wilkes-Barre, Pa., John H. Stenger, Jr., 100 w, E.
- WBBC**—1400 kc, Brooklyn, N. Y., Brooklyn Broadcasting Corp., 500 w.
- WBBI**—1210 kc, Richmond, Va., Grace Covenant Presbyterian Church, 100 w, E.
- WBMM**—770 kc, Chicago, Ill., WBMM Bdstg. Corp., 25,000 w, C.
- WBRR**—1300 kc, Brooklyn, N. Y., People's Pulpit Association, 1000 w, E.
- WBZZ**—1200 kc, Ponca City, Okla., C. L. Carrell, 100 w, C.
- WBZN**—1410 kc, Bay City, Mich., James E. Davidson, 500 w, E.
- WBZN**—See under WENR.
- WBEN**—900 kc, Buffalo, N. Y., WBEN, Inc., 1000 w, E.
- WBEO**—1310 kc, Marquette, Mich., Lake Superior Bdstg. Co.
- WBFG**—1370 kc, Glens Falls, N. Y., W. Parker & N. Metcalf, 50 w, E.
- WBHS**—1200 kc, Huntsville, Ala., Hutchens Co., 50 w.
- WBIG**—1440 kc, Greensboro, N. C., North Carolina Broadcasting Co., 500 w, E.
- WBIS**—See under WNAC.
- WBMS**—1450 kc, Hackensack, N. J., WBMS Broadcasting Corp., 250 w.
- WBNN**—1350 kc, New York, N. Y., Standard Cahill Co., Inc., 250 w, E.
- WBOQ**—See under WABC.
- WBOW**—1310 kc, Terre Haute, Ind., Banks of Wabash Broadcasting Assn., 100 w, C.
- WBRC**—930 kc, Birmingham, Ala., Birmingham Broadcasting Co., 500 w, C.
- WBRE**—1310 kc, Wilkes-Barre, Pa., Louis G. Baltimore, 100 w, E.
- WBSO**—920 kc, Needham, Mass., Bdstg. Service Org., Inc., 250 w, E.
- WBT**—1080 kc, Charlotte, N. C., Station WBT, Inc., 5000 w, E, shared.
- WBTM**—1370 kc, Danville, Va., Piedmont Bdstg. Corp., 100 w, E.
- WBZ**—990 kc, Boston, Mass., Westinghouse E. & M. Co., 15,000 w, E.
- WBZA**—990 kc, Springfield, Mass., Westinghouse E. & M. Co., 1000 w, E.
- WCAC**—600 kc, Storrs, Conn., Connecticut Agricultural College, 250 w, E.
- WCAD**—1220 kc, Canton, N. Y., St. Lawrence University, 500 w, E.
- WCAE**—1220 kc, Pittsburgh, Pa., WCAE, Inc., 1000 w, E.
- WCAH**—1430 kc, Columbus, Ohio, Commercial Radio Service Co., 500 w, E.
- WCAJ**—590 kc, Lincoln, Neb., Nebraska Wesleyan University, 500 w, C.
- WCAL**—1250 kc, Northfield, Minn., St. Olaf College, 1000 w, C.
- WCAM**—1280 kc, Camden, N. J., City of Camden, 500 w, E.
- WCAO**—600 kc, Baltimore, Md., Monumental Radio, Inc., 250 w, E.
- WCAP**—1280 kc, Asbury Park, N. J., Radio Industries Broadcast Co., 500 w, E.
- WCAT**—1200 kc, Rapid City, S. D., South Dakota State School of Mines, 100 w, M.
- WCAU**—1170 kc, Philadelphia, Pa., Universal Broadcasting Co., 10,000 w, E.
- WCAX**—1200 kc, Burlington, Vt., Burlington Daily News, 100 w, E.
- WCAZ**—1070 kc, Carthage, Ill., Superior Broadcasting Co., 50 w.
- WCBA**—1440 kc, Allentown, Pa., B. B. Muselman, 250 w, E.
- WCBD**—1080 kc, Zion, Ill., Wilbur Glen Voliva, 5000 w, C.
- WCBM**—1370 kc, Baltimore, Md., Baltimore Broadcasting Corp., 100 w, E.
- WCBS**—1210 kc, Springfield, Ill., Dewing & Meester, 100 w, C.
- WCCO**—810 kc, Minneapolis, Minn., Northwestern Broadcasting Inc., 5000 w, C.
- WCDA**—1350 kc, New York, N. Y., Italian Educational Broadcasting Co., 250 w, E.
- WCFL**—970 kc, Chicago, Ill., Chicago Federation of Labor, 150 w, C.
- WCGU**—1400 kc, Brooklyn, N. Y., U. S. Broadcasting Corp., 500 w, E.
- WCHI**—1490 kc, Chicago, Ill., People's Pulpit Association, 5000 w, C.
- WCKY**—1490 kc, Covington, Ky., L. B. Wilson, 500 w, E.
- WCLB**—1500 kc, Long Beach, N. Y., Arthur Paske, 100 w, E.
- WCLO**—1200 kc, Janesville, Wis., WCLO Radio Corp., 100 w, C.
- WCLS**—1310 kc, Joliet, Ill., WCLS, Inc., 100 w, C.
- WCMA**—1400 kc, Culver, Ind., General Broadcasting Co., 500 w, C.
- WCOA**—1340 kc, Pensacola, Fla., City of Pensacola, 500 w, E.
- WCOC**—880 kc, Meridian, Miss., Mississippi Broadcasting Co., 500 w, C.
- WCOD**—1200 kc, Harrisburg, Pa., Keystone Broadcasting Corp., 100 w, E.
- WCOD**—1210 kc, Yonkers, N. Y., Westchester Broadcasting Corp., 100 w, E.

- WCRW**—1210 kc, Chicago, Ill., Clinton R. White, 100 w, C.
WCSC—1360 kc, Charleston, S. C., Lewis Burk, 500 w, E.
WCSH—940 kc, Portland, Me., Congress Square Hotel Co., 1000 w, E.
WDAE—1220 kc, Tampa, Fla., Tampa Publishing Co., 1000 w, E.
WDAF—610 kc, Kansas City, Mo., Kansas City Star Co., 1000 w, C.
WDAG—1410 kc, Amarillo, Texas, National Radio & Broadcasting Corp., 250 w, C.
WDAH—1310 kc, El Paso, Texas, W. S. Bledsoe, 100 w, M.
WDAS—1370 kc, Philadelphia, Pa., WDAS Broadcasting Station, Inc., 100 w, E.
WDAY—940 kc, Fargo, N. D., WDAY, Inc., 1000 w, C.
WDBL—930 kc, Roanoke, Va., Times-World Corp., 250 w, E.
WDBO—1120 kc, Orlando, Fla., Orlando Broadcasting Co., 1000 w, E.
WDEL—1120 kc, Wilmington, Del., WDEL, Inc., 250 w, E.
WDEV—1420 kc, Waterbury, Vt., H. C. Whitehill, 50 w.
WDGX—1180 kc, Minneapolis, Minn., Dr. Geo. W. Young, 1000 w, C.
WDIX—1420 kc, Texarkana, Ark., North Mississippi Broadcasting Corp., 100 w, C.
WDOD—1280 kc, Chattanooga, Tenn., WDOD Broadcasting Co., Inc., 1000 w, C.
WDRG—1330 kc, Hartford, Conn., Doolittle Radio Corp., 500 w, E.
WDSU—1250 kc, New Orleans, La., Jos. H. Uhalt, 1000 w, C.
WDZ—1070 kc, Tuscola, Ill., James L. Bush, 100 w.
WEAF—660 kc, New York, N. Y., National Broadcasting Co., Inc., 50,000 w, E.
WEAI—1270 kc, Ithaca, N. Y., Cornell Univ., 1000 w, E.
WEAN—780 kc, Providence, R. I., Shepard Broadcasting Service, 250 w, E.
WEAO—570 kc, Columbus, Ohio, Ohio State University, 750 w, E.
WEBC—1290 kc, Superior, Wis., Head of The Lakes Broadcasting Co., 1000 w, C.
WEHQ—1210 kc, Harrisburg, Ill., First Trust & Savings Bank, 100 w, C.
WEHR—1310 kc, Buffalo, N. Y., Howell Broadcasting Co., 100 w, E.
WEDC—1210 kc, Chicago, Ill., Emil Denmark, Inc., 100 w.
WEDH—1420 kc, Erie, Pa., Erie Dispatch-Herald, 30 w, E.
WEEL—590 kc, Boston, Mass., Edison Elec. Illum. Co., 1000 w, E.
WEPB—830 kc, Reading, Pa., Berks Bdstg. Co., 1000 w.
WEHC—1350 kc, Emory, Va., Emory and Henry College, 500 w, E.
WEHS—1420 kc, Evanston, Ill., WEHS, Inc., 100 w, C.
WELL—1420 kc, Battle Creek, Mich., Enquirer-News Co., 100 w, E.
WENR—870 kc, Chicago, Ill., Great Lakes Radio Broadcasting Co., 50,000 w, C.
WEPS—See under WORC.
WEVD—1300 kc, Brooklyn, N. Y., Debs Memorial Radio Fund, 500 w, E.
WGW—760 kc, St. Louis, Mo., St. Louis University, 1000 w, C.
WEXL—1310 kc, Royal Oak, Mich., Royal Oak Broadcasting Co., 50 w, E.
WFAA—800 kc, Dallas, Texas, Dallas News and Journal, 50,000 w, C.
WFAM—1200 kc, La Porte, Ind., South Bend Tribune, 100 w, C.
WFAN—610 kc, Philadelphia, Pa., Keystone Broadcasting Co., Inc., 500 w, E.
WFBC—1200 kc, Knoxville, Tenn., First Baptist Church, 50 w, E.
WFBE—1200 kc, Cincinnati, Ohio, Post Publ. Co., 100 w, E.
WFBG—1310 kc, Altoona, Pa., William F. Gable Co., 100 w, E.
WFBI—1360 kc, Syracuse, N. Y., The Onondaga Co., Inc., 1000 w, E.
WFBI—1230 kc, Indianapolis, Ind., Indianapolis, Power & Light Co., 1000 w, C.
WFBP—1270 kc, Baltimore, Md., Baltimore Radio Show, Inc., 250 w, E.
WFDF—1310 kc, Flint, Mich., Frank D. Fallain, 100 w, E.
WFDV—1310 kc, Rome, Ga., Dolies Goings, 100 w, E.
WFDW—1420 kc, Talladega, Ala., R. C. Hammett, 100 w, C.
WFEE—1430 kc, Manchester, N. H., Rines Hotel Co., 500 w.
WFEI—560 kc, Philadelphia, Pa., Straw-bridge & Clothier, 500 w, E.
WFIW—940 kc, Hopkinsville, Ky., WFIW, Inc., 1000 w, C.
WFLE—620 kc, Clearwater, Fla., Clearwater Chamber of Commerce and St. Petersburg Chamber of Commerce, 250 w, E.
WFOX—1400 kc, Brooklyn, N. Y., Paramount Broadcasting Corp., 500 w.
WGAL—1310 kc, Lancaster, Pa., WGAL, Inc., 100 w, E.
WGAR—1450 kc, Cleveland, Ohio, WGAR Broadcasting Co., 500 w, E.
WGBB—1210 kc, Freeport, N. Y., Harry H. Carman, 100 w, E.
WGBC—See under WNBK.
WGBF—630 kc, Evansville, Ind., Evansville on the Air, Inc., 500 w, E.
WGBI—880 kc, Scranton, Pa., Scranton Broadcasters, Inc., 250 w, E.
WGBS—1180 kc, New York, N. Y., American Radio News Corp., 500 w, E.
WGCM—1210 kc, Gulfport, Miss., Great Southern Land Co., Inc., 100 w, C.
WGCP—1250 kc, Newark, N. J., May Radio Broadcast Corp., 250 w.
WGES—1360 kc, Chicago, Ill., Oak Leaves Broadcasting Corp., 500 w, C.
WGH—1310 kc, Newport News, Va., Hampton Roads Broadcasting Corp., Inc., 100 w, E.
WGL—1370 kc, Ft. Wayne, Ind., Allen-Wayne Co., 100 w, C.
WGMS—See under WLB.
WGN—720 kc, Chicago, Ill., Tribune Co., 25,000 w, C.
WGR—550 kc, Buffalo, N. Y., Buffalo Broadcasting Corp., 1000 w, E.
WGST—890 kc, Atlanta, Ga., Georgia School of Technology, 250 w, E.
WGY—790 kc, Schenectady, N. Y., General Electric Co., 50,000 w, E.
WHA—940 kc, Madison, Wis., University of Wisconsin, 750 w, C.
WHAD—1120 kc, Milwaukee, Wis., Marquette University, 250 w, C.
WHAM—1150 kc, Rochester, N. Y., Stromberg-Carlson Tel. Mfg. Co., 5000 w, E.
WHAP—1300 kc, New York, N. Y., Defenders of Truth Society, Inc., 1000 w, E.
WHAS—820 kc, Louisville, Ky., The Courier Journal Co. & Louisville Times Co., 10,000 w, C.
WHAT—1310 kc, Philadelphia, Pa., Independence Broadcasting Co., 100 w, E.
WHAZ—1300 kc, Troy, N. Y., Rensselaer Polytechnic Institute, 500 w, E.
WHB—860 kc, Kansas City, Mo., WHB Broadcasting Co., 500 w, C.
WHBC—1200 kc, Canton, Ohio, St. John's Catholic Church, 10 w, E.
WHBD—1370 kc, Mt. Orab, Ohio, F. P. Moler, 100 w, E.
WHBF—1210 kc, Rock Island, Ill., Beardley Specialty Co., 100 w, C.
WHBL—1410 kc, Sheboygan, Wis., Press Pub. Co., 500 w, C.
WHBQ—1370 kc, Memphis, Tenn., Station WHBQ, Inc., 100 w, C.
WHBU—1210 kc, Anderson, Ind., Anderson Bdstg. Corp., 100 w, C.
WHBY—1200 kc, Green Bay, Wis., St. Norbert's College, 100 w, C.
WHDF—1370 kc, Calumet, Mich., Upper Michigan Bdstg. Co., 100 w, C.
WHDH—830 kc, Boston, Mass., Matheson Radio Co., Inc., 1000 w, E.
WHDI—1180 kc, Minneapolis, Minn., Dr. G. W. Young, 500 w, C.
WHDL—1420 kc, Tupper Lake, N. Y., Tupper Lake Broadcasting Corp., 100 w, E.
WHDC—1440 kc, Rochester, N. Y., Hickson Electric Co., Inc., 500 w, E.
WHFC—1420 kc, Cicero, Ill., WHFC, Inc., 100 w, C.
WHIS—1410 kc, Bluefield, W. Va., Daily Telegraph Printing Co., 250 w, E.
WHK—1390 kc, Cleveland, Ohio, Radio Air Service Corp., 1000 w, E.
WHN—1010 kc, New York, N. Y., Marcus Loew Booking Review, 250 w, E.
WHO—1000 kc, Des Moines, Iowa, Central Broadcasting Co., 5000 w, C.
WHOM—1450 kc, Jersey City, N. J., New Jersey Broadcasting Corp., 250 w, E.
WHP—1430 kc, Harrisburg, Pa., WHP, Inc., 500 w, E.
WIAS—1420 kc, Ottumwa, Iowa, Poling Electric Co., 100 w, C.
WIBA—1280 kc, Madison, Wis., Capital Times Co., 500 w, C.
WIBG—930 kc, Elkins Park, Pa., WIBG, Inc., 25 w, E.
WIBM—1370 kc, Jackson, Mich., WIBM, Inc., 100 w.
WIBO—560 kc, Chicago, Ill., Nelson Bros. Bond and Mortgage Co., 1000 w, C.
WIBU—1210 kc, Poynette, Wis., W. C. Forrest, 100 w, C.
WIBW—530 kc, Topeka, Kan., Topeka Broadcasting Assn., Inc., 1000 w, C.
WIBX—1200 kc, Utica, N. Y., WIBX, Inc., 100 w, E.
WICC—600 kc, Bridgeport, Conn., Bridgeport Broadcasting Station, Inc., 500 w, E.
WIL—1200 kc, St. Louis, Mo., Missouri Broadcasting Co., 100 w, C.
WILL—890 kc, Urbana, Ill., University of Illinois, 250 w, C.
WILM—1420 kc, Wilmington, Del., Delaware Broadcasting Co., Inc., 100 w, E.
WIOD—1300 kc, Miami, Fla., Isle of Dreams Broadcasting Co., 1000 w, E.
WIP—610 kc, Philadelphia, Pa., Gimbel Bros., Inc., 500 w, E.
WIS—1010 kc, Columbia, S. C., South Carolina Broadcasting Co., Inc., 500 w, E.
WISJ—See under WIBA.
WISN—1120 kc, Milwaukee, Wis., Evening Wisconsin Co., 250 w, C.
WJAC—1310 kc, Johnstown, Pa., Johnstown Automobile Co., 100 w, E.
WJAG—1060 kc, Norfolk, Neb., Norfolk Daily News, 1000 w, C.
WJAK—1310 kc, Marion, Ind., The Truth Pub. Co., Inc., 50 w.
WJAR—890 kc, Providence, R. I., The Outlet Co., 250 w, E.
WJAS—1290 kc, Pittsburgh, Pa., Pittsburgh Radio Supply House, 1000 w, E.
WJAX—900 kc, Jacksonville, Fla., City of Jacksonville, 1000 w, E.
WJAY—610 kc, Cleveland, Ohio, Cleveland Radio Broadcasting Corp., 500 w, E.
WJBC—1200 kc, LaSalle, Ill., Kaskaskia Broadcasting Co., 100 w, C.
WJBI—1210 kc, Red Bank, N. J., Monmouth Broadcasting Co., 100 w, E.
WJBK—1370 kc, Highland Park, Mich., J. F. Hopkins, 50 w, C.
WJBL—1200 kc, Decatur, Ill., Commodore Broadcasting Co., 100 w, C.
WJBO—1420 kc, New Orleans, La., Valdemar Jensen, 100 w, C.
WJBU—See under WEBB.
WJBU—1210 kc, Lewisburg, Pa., Bucknell University, 100 w, E.
WJBW—1200 kc, New Orleans, La., C. Carlisle, Jr., 30 w, C.
WJBY—1210 kc, Gadsden, Ala., Gadsden Broadcasting Co., 100 w, C.
WJDX—1270 kc, Jackson, Miss., Lamar Life Ins. Co., 1000 w, C.
WJDD—1130 kc, Chicago, Ill., Loyal Order of Moose, 20,000 w, C.
WJKS—1360 kc, Gary, Ind., Johnson-Kennedy Radio Corp., 1000 w, C.
WJMS—1420 kc, Ironwood, Mich., Johnson Music Store, 100 w.
WJR—750 kc, Detroit, Mich., The Goodwill Station, Inc., 10,000 w, E.
WJSV—1460 kc, Alexandria, Va., Independent Publishing Co., 10,000 w.
WJTL—1370 kc, Oglethorpe University, Ga., 100 w, E.
WJW—1210 kc, Mansfield, Ohio, Mansfield Broadcasting Association, 100 w, E.
WJZ—760 kc, New York City, N. Y., National Broadcasting Co., 30,000 w, E.
WKAQ—890 kc, San Juan, Porto Rico, Radio Corp. of Porto Rico, 250 w, E.
WKAR—1040 kc, East Lansing, Mich., Michigan State College, 1000 w, E.
WKAV—1310 kc, Laconia, N. H., Laconia Radio Club, 100 w, E.
WKBB—1310 kc, Joliet, Ill., Sanders Bros., 100 w, C.
WKBC—1310 kc, Birmingham, Ala., R. B. Broyles Furniture Co., 100 w, C.
WKBF—1400 kc, Indianapolis, Ind., Indianapolis Broadcasting Corp., 500 w, C.
WKBH—1380 kc, LaCrosse, Wis., WKBH, Inc., 1000 w, C.
WKBI—1420 kc, Chicago, Ill., WKBI, Inc., 100 w, C.
WKBN—570 kc, Youngstown, Ohio, WKBN Bdstg. Corp., 500 w, E.
WKBO—1450 kc, Jersey City, N. J., Camith Corp., 250 w, E.
WKBS—1310 kc, Galesburg, Ill., Permil N. Nelson, 100 w, C.
WKBY—1500 kc, Connersville, Ind., Knox Battery & Electric Co., 100 w, C.
WKBW—1480 kc, Buffalo, N. Y., WKBW, Inc., 5000 w, E.
WKBZ—1500 kc, Ludington, Mich., K. L. Ashbacher, 50 w.
WKJC—1200 kc, Lancaster, Pa., Lancaster Bdstg. Service, Inc., 100 w, E.
WKRC—550 kc, Cincinnati, Ohio, WKRC, Inc., 1000 w, E.
WKY—900 kc, Oklahoma City, Okla., WKY Radiophone Co., 1000 w, C.
WKZO—590 kc, Kalamazoo, Mich., WKZO, Inc., 1000 w, C.
WLAC—1470 kc, Nashville, Tenn., Life & Casualty Ins. Co., 5000 w, C.

- WLAP**—1010 kc, Louisville, Ky., American Broadcasting Corp. of Kentucky, 1259 w, C.
- WLB**—1250 kc, Minneapolis, Minn., University of Minnesota, 1000 w, C.
- WLBC**—1310 kc, Muncie, Ind., Donald A. Burton, 50 w.
- WLBK**—1420 kc, Kansas City, Kan., WLEB Broadcasting Co., 100 w, C.
- WLBG**—1200 kc, Petersburg, Va., WLBG, Inc., 100 w, E.
- WLBL**—900 kc, Ellis, Wis., Wisconsin Department of Markets, 2000 w, daytime, C.
- WLBW**—1260 kc, Oil City, Pa., Radio-Wire Program Corp., 500 w, E.
- WLBX**—1500 kc, Long Island City, N. Y., John N. Brahy, 100 w.
- WLBZ**—620 kc, Bangor, Me., Maine Broadcasting Co., 500 w, E.
- WLCL**—1210 kc, Ithaca, N. Y., Lutheran Assn. of Ithaca, 50 w, E.
- WLEV**—1370 kc, Lexington, Mass., Lexington Air Station, 100 w, E.
- WLIB**—See under WGN.
- WLIT**—560 kc, Philadelphia, Pa., Lit Brothers, 500 w, E.
- WLOE**—1500 kc, Boston, Mass., Boston Broadcasting Co., 100 w.
- WLS**—870 kc, Chicago, Ill., Agricultural Broadcasting Co., 5000 w, C.
- WLSI**—See under WPRO.
- WLTH**—1400 kc, Brooklyn, N. Y., Voice of Brooklyn, Inc., 500 w, E.
- WLVA**—1370 kc, Lynchburg, Va., Lynchburg Broadcasting Corp., 100 w, E.
- WLW**—700 kc, Cincinnati, Ohio, Crosley Radio Corp., 50,000 w, E.
- WLWL**—1100 kc, New York, N. Y., Missionary Society of St. Paul, 5000 w, E.
- WMAC**—See under WSYR.
- WMAL**—630 kc, Washington, D. C., M. A. Lese Co., 250 w, E.
- WMAQ**—670 kc, Chicago, Ill., National Broadcasting Co., 5000 w, C.
- WMAY**—1180 kc, Macon, Ga., Southeastern Broadcasting Co., 500 w, E.
- WMBA**—1500 kc, Newport, R. I., LeRoy Joseph Beebe, 100 w, E.
- WMBC**—1120 kc, Detroit, Mich., Michigan Broadcasting Co., Inc., 100 w, E.
- WMBD**—1440 kc, Peoria Heights, Ill., Peoria Bdstg. Co., 500 w.
- WMBE**—See under WIOD.
- WMBG**—1210 kc, Richmond, Va., Havens & Martin, Inc., 100 w, E.
- WMBH**—1420 kc, Joplin, Mo., Edwin Dudley Aber, 100 w, C.
- WMBI**—1080 kc, Chicago, Ill., Moody Bible Institute Radio Station, 5000 w, C, shared.
- WMBJ**—1500 kc, Wilkensburg, Pa., Rev. John W. Sproul, 100 w, E.
- WMBO**—1310 kc, Auburn, N. Y., WMBO, Inc., 100 w, E.
- WMBQ**—1500 kc, Brooklyn, N. Y., Paul J. Gollhofer, 100 w.
- WMBR**—1370 kc, Tampa, Fla., F. J. Reynolds, 100 w, E.
- WMC**—780 kc, Memphis, Tenn., Memphis Commercial Appeal, Inc., 500 w, C.
- WMCA**—570 kc, New York, N. Y., Knickerbocker Broadcasting Co., Inc., 500 w, E.
- WMIL**—1500 kc, Brooklyn, N. Y., Arthur Faske, 100 w, E.
- WMMX**—890 kc, Fairmont, W. Va., Holt Rowe Novelty Co., 250 w, E.
- WMPC**—1500 kc, Lapeer, Mich., First Methodist Protestant Church, 100 w, E.
- WMRI**—1210 kc, Jamaica, N. Y., Peter J. Prinz, 10 w, E.
- WMSG**—1350 kc, New York, N. Y., Madison Square Garden Broadcast Co., 250 w, E.
- WMT**—600 kc, Waterloo, Iowa, Waterloo Broadcasting Co., 500 w, C.
- WNAC**—1230 kc, Boston, Mass., The Shepard Broadcasting Service, 1000 w, E.
- WNAD**—1010 kc, Norman, Okla., University of Oklahoma, 500 w, C.
- WNAX**—570 kc, Yankton, S. Dak., Gurney Seed & Nursery Co., 1000 w, C.
- WNBB**—1500 kc, Binghamton, N. Y., Howitt-Wood Radio Co., 100 w, E.
- WNBH**—1310 kc, New Bedford, Mass., New Bedford Broadcasting Co., 100 w, E, shared.
- WNBO**—1200 kc, Silver Haven, Pa., J. B. Spriggs, 100 w, E.
- WNBR**—1430 kc, Memphis, Tenn., Memphis Broadcasting Co., 500 w, C.
- WNHW**—1200 kc, Carbondale, Pa., Home Cut Glass & China Co., 10 w, E.
- WNBN**—1200 kc, Springfield, Vt., First Congregational Church Corp., 10 w, E.
- WNHZ**—1290 kc, Saranac Lake, N. Y., Smith & Mace, 50 w, E.
- WNJ**—1450 kc, Newark, N. J., Radio Investment Co., 250 w, E.
- WNOX**—560 kc, Knoxville, Tenn., WNOX, Inc., 1000 w, C.
- WNYC**—570 kc, New York, N. Y., Department of Plant & Structures, 500 w, E.
- WOAI**—1190 kc, San Antonio, Texas, Southern Equipment Co., 50,000 w, C.
- WOAN**—See WREC.
- WOAX**—1280 kc, Trenton, N. J., WOAX, Inc., 500 w, E.
- WOBU**—580 kc, Charleston, W. Va., WOBU, Inc., 250 w, E.
- WOC**—1000 kc, Davenport, Iowa, Central Broadcasting Co., 5000 w, C.
- WOCL**—1210 kc, Jamestown, N. Y., A. E. Newton, 50 w, E.
- WODA**—1250 kc, Paterson, N. J., Richard E. O'Dea, 1000 w, E.
- WODX**—1410 kc, Mobile, Ala., Mobile Bdstg. Corp., 500 w, C.
- WOI**—640 kc, Ames, Iowa, Iowa State College, 5000 w, C.
- WOKO**—1440 kc, Albany, N. Y., WOKO, Inc., 500 w, E.
- WOL**—1310 kc, Washington, D. C., American Broadcasting Co., 100 w, E.
- WOMT**—1210 kc, Manitowoc, Wis., Francis M. Kadow, 100 w.
- WOOD**—1270 kc, Grand Rapids, Mich., Walter B. Stiles, Inc., 500 w, C.
- WOPI**—1500 kc, Bristol, Tenn., Radiophone Broadcasting Co., 100 w, E.
- WOQ**—1300 kc, Kansas City, Mo., Unity School of Christianity, 1000 w, C.
- WOR**—710 kc, Newark, N. J., J. Hamburger Broadcasting Service, Inc., 5000 w, E.
- WORC**—1200 kc, Worcester, Mass., A. F. Kleindienst, 100 w, E.
- WOS**—630 kc, Jefferson City, Mo., State Marketing Bureau, 500 w, C.
- WOV**—1130 kc, New York, N. Y., International Broadcasting Corp., 1000 w, E.
- WOW**—590 kc, Omaha, Neb., Woodmen of the World, 1000 w, C.
- WOWO**—1160 kc, Ft. Wayne, Ind., Main Auto Supply Co., 10,000 w, C.
- WPAD**—1420 kc, Paducah, Ky., Paducah Broadcasting Co., 100 w, C.
- WPAP**—See under WQAO.
- WPAW**—1210 kc, Pawtucket, R. I., Shattenberg & Robinson, 100 w, E.
- WPCC**—560 kc, Chicago, Ill., North Shore Congregational Church, 500 w, C.
- WPCH**—810 kc, New York, N. Y., Eastern Broadcasters, Inc., 500 w, E.
- WPEN**—1500 kc, Philadelphia, Pa., Wm. Pen Broadcasting Co., 100 w, E.
- WPG**—1100 kc, Atlantic City, N. J., WPG Broadcasting Corp., 5000 w, E.
- WPOE**—1370 kc, Patchogue, N. Y., Nassau Broadcasting Corp., 100 w, E.
- WPOR**—See under WTAR.
- WPRO**—1210 kc, Providence, R. I., Cherry & Webb Bdstg. Co., 100 w, E.
- WPSC**—1230 kc, State College, Pa., Pennsylvania State College, 500 w, day, E.
- WPTF**—680 kc, Raleigh, N. C., Durham Life Insurance Co., 1000 w, E.
- WQAM**—560 kc, Miami, Fla., Miami Broadcasting Co., 1000 w, E.
- WQAN**—880 kc, Scranton, Pa., Scranton Times, 250 w, E.
- WQAO**—1010 kc, New York, N. Y., Calvary Baptist Church, 250 w, E.
- WQBC**—1360 kc, Vicksburg, Miss., Delta Broadcasting Co., 300 w, C.
- WQDM**—1370 kc, St. Albans, Vt., A. J. St. Antoine, 100 w, E.
- WQDX**—1210 kc, Thomasville, Ga., Stevens Luke, 100 w, E.
- WRAC**—1370 kc, Williamsport, Pa., C. R. Cummins, 50 w, E.
- WRAM**—1370 kc, Wilmington, N. C., Wilmington Radio Association, 100 w, E.
- WRAY**—1310 kc, Reading, Pa., Reading Broadcasting Co., 50 w, E.
- WRAX**—1020 kc, Philadelphia, Pa., WRAX Broadcasting Co., 250 w, E.
- WRBJ**—1370 kc, Hattiesburg, Miss., Hattiesburg Bdstg. Co., 10 w, C.
- WRBL**—1200 kc, Columbus, Ga., WRBL Radio Station, Inc., 50 w, E.
- WRBQ**—1210 kc, Greenville, Miss., J. Pat Scully, 250 w, C.
- WRBX**—1410 kc, Roanoke, Va., Richmond Development Corp., 250 w, E.
- WRC**—950 kc, Washington, D. C., National Broadcasting Co., 500 w, E.
- WRDO**—1370 kc, Augusta, Me., Albert S. Woodman, 100 w, E.
- WRDW**—1500 kc, Augusta, Ga., Davenport's Musicove, Inc., 100 w, E.
- WREC**—600 kc, Memphis, Tenn., WREC, Inc., 500 w.
- WREN**—1220 kc, Lawrence, Kan., Jenny Wren Co., 1000 w, C.
- WRHM**—1250 kc, Minneapolis, Minn., Minnesota Broadcasting Corp., 1000 w, C.
- WRJN**—1370 kc, Racine, Wis., Racine Broadcasting Corp., 100 w, C.
- WRNY**—1010 kc, New York, N. Y., Aviation Radio Station, 250 w, E.
- WROL**—1310 kc, Knoxville, Tenn., Stuart Broadcasting Corp., 100 w, C.
- WRR**—1280 kc, Dallas, Texas, City of Dallas, 500 w, C.
- WRUF**—830 kc, Gainesville, Fla., University of Florida, 5000 w, E.
- WRVA**—1110 kc, Richmond, Va., Larus Bros. & Co., Inc., 5000 w, E.
- WSAI**—1330 kc, Mason, Ohio, Crosley Radio Corp., 500 w, E.
- WSAJ**—1310 kc, Grove City, Pa., Grove City College, 100 w, E.
- WSAN**—1440 kc, Allentown, Pa., Allentown Call Pub. Co., 250 w, E.
- WSAR**—1450 kc, Fall River, Mass., Doughty & Welch Electrical Co., Inc., 250 w, E.
- WSAZ**—580 kc, Huntington, W. Va., WSAZ, Inc., 250 w, E.
- WSB**—740 kc, Atlanta, Ga., Atlanta Journal Co., 5000 w, E.
- WSBC**—1210 kc, Chicago, Ill., World Battery Co., 100 w, C.
- WSBT**—1230 kc, South Bend, Ind., South Bend Tribune, 500 w, C.
- WSEN**—1210 kc, Columbus, Ohio, Columbus Broadcasting Corp., 100 w, E.
- WSFA**—1410 kc, Montgomery, Ala., Montgomery Bdstg. Co., 500 w, C.
- WSIX**—1210 kc, Springfield, Tenn., 638 Tire & Vulcanizing Co., 100 w, C.
- WSJS**—1310 kc, Winston-Salem, N. C., The Journal Co., 100 w, E.
- WSM**—650 kc, Nashville, Tenn., National Life & Accident Ins. Co., 5000 w, C.
- WSMB**—1320 kc, New Orleans, La., WSMB, Inc., 500 w, C.
- WSMK**—1380 kc, Dayton, Ohio, Stanley M. Krohn, Jr., 200 w, C.
- WSOC**—1210 kc, Gastonia, N. C., A. J. Kirby Music Co., 100 w, E.
- WSPA**—1420 kc, Spartanburg, S. C., 100 w, E.
- WSPD**—1340 kc, Toledo, Ohio, Toledo Broadcasting Co., 1000 w, E.
- WSUI**—880 kc, Iowa City, Iowa, State Univ. of Iowa, 500 w, C.
- WSUN**—See under WFLA.
- WSVS**—1370 kc, Buffalo, N. Y., Seneca Vocational High School, 50 w, E.
- WSYB**—1500 kc, Rutland, Vt., Weiss Music Co., 100 w, E.
- WSYR**—570 kc, Syracuse, N. Y., Clive B. Meredith, 250 w, E.
- WTAD**—1440 kc, Quincy, Ill., Illinois Broadcasting Corp., 500 w.
- WTAG**—580 kc, Worcester, Mass., Worcester Telegram Pub. Co., Inc., 250 w, E.
- WTAM**—1070 kc, Cleveland, Ohio, National Broadcasting Co., 50,000 w, E.
- WTAQ**—1330 kc, Eau Claire, Wis., Gillette Rubber Co., 1000 w, C.
- WTAR**—780 kc, Norfolk, Va., WTAR Radio Corp., 500 w, E.
- WTAW**—1120 kc, College Station, Texas, Agri. & Mech. College of Texas, 500 w, C.
- WTAX**—1210 kc, Springfield, Ill., WTAX, Inc., 100 w.
- WTBO**—1420 kc, Cumberland, Md., Associated Bdstg. Corp., 100 w, E.
- WTEL**—1310 kc, Philadelphia, Pa., Foulkrod Radio Eng. Co., 50 w, E.
- WTFI**—1450 kc, Athens, Ga., Toccoa Falls Bdstg. Co., 500 w, E.
- WTIC**—1060 kc, Hartford, Conn., Travelers Broadcasting Service Corp., 50,000 w, E.
- WTJS**—1310 kc, Jackson, Tenn., Sun Publishing Co., 100 w, C.
- WTMJ**—620 kc, Milwaukee, Wis., Milwaukee Journal, 1000 w, C.
- WTNT**—1470 kc, Nashville, Tenn., Life and Casualty Ins. Co. of Tenn., 5000 w, C.
- WTOC**—1260 kc, Savannah, Ga., Savannah Broadcasting Corp., 500 w, E.
- WTSL**—Laurel, Miss.
- WWAE**—1200 kc, Hammond, Ind., Hammond-Calumet Broadcasting Corp., 100 w, C.
- WWJ**—920 kc, Detroit, Mich., Evening News Assn., 1000 w, E.
- WWL**—850 kc, New Orleans, La., Loyola University, 10,000 w, C.
- WWNC**—570 kc, Asheville, N. C., Citizens Broadcasting Co., 1000 w, E.
- WWRL**—1500 kc, Woodside, N. Y., Long Island Broadcasting Corp., 100 w.
- WWSW**—1500 kc, Pittsburgh, Pa., Walker & Downing Radio Corp.
- WVVA**—1160 kc, Wheeling, W. Va., West Virginia Broadcasting Corp., 5000 w, E.
- WNYZ**—1240 kc, Detroit, Mich., Kinsky Trendle Broadcasting Co., 1000 w, E.

U.S. Broadcasting Stations by Frequencies

550 Kilocycles, 545.1 Meters:
KOAC, WGR, WKRC, KFUO, KSD, KFDY, KFYR

560 Kilocycles, 535.4 Meters:
WLIT, WFI, KFDL, WNOX, KTAB, KLZ, WIBO, WPCG, WQAM

570 Kilocycles, 526.0 Meters:
WNYC, WMCA, WSYR, WMAC, WKBN, WWNC, KGKO, WNAX, KXA, KMTR, WEAQ

580 Kilocycles, 516.9 Meters—Canadian Shared:

WTAG, WOBU, WSAZ, KGFX, KSAC, WIBW

590 Kilocycles, 508.2 Meters:
WEEL, WCAJ, WOW, KHQ, WKZO

600 Kilocycles, 499.7 Meters—Canadian Shared:

WCAO, WREC, WOAN, KFSO, WCAC, WMT, WICC

610 Kilocycles, 491.5 Meters:
WFAN, WIP, WDAF, KFRC, WJAY

620 Kilocycles, 483.6 Meters:
WLBZ, WTMJ, KGW, WFLA, WSUN, KTAR

630 Kilocycles, 475.9 Meters—Canadian Shared:

WMAL, WOS, KFRU, WGBF

640 Kilocycles, 468.5 Meters:
WAIU, KFI, WOI

650 Kilocycles, 461.3 Meters:
WSM, KPCB

660 Kilocycles, 454.3 Meters:
WEAF, WAAW

670 Kilocycles, 447.5 Meters:
WMAQ

680 Kilocycles, 440.9 Meters:
WPTF, KPO, KFEQ

690 Kilocycles, 434.5 Meters—Canadian Wave:

700 Kilocycles, 428.3 Meters:
WLW

710 Kilocycles, 422.3 Meters:
WOR, KMPC

720 Kilocycles, 416.4 Meters:
WGN, WLIB

730 Kilocycles, 410.7 Meters—Canadian Wave:

740 Kilocycles, 405.2 Meters:
WSB, KMMJ

750 Kilocycles, 399.8 Meters:
WJR

760 Kilocycles, 394.5 Meters:
WJZ, WEW, KVI

770 Kilocycles, 389.4 Meters:
KFAB, WBBM, WJBT

780 Kilocycles, 384.4 Meters—Canadian Shared:

WTAR, WPOR, KELW, KTM, WMC, WEAN

790 Kilocycles, 379.5 Meters:
WGY, KGO

800 Kilocycles, 374.8 Meters:
WBAP, WFAA

810 Kilocycles, 370.2 Meters:
WPCB, WCCO

820 Kilocycles, 365.6 Meters:
WHAS

830 Kilocycles, 361.2 Meters:
KOA, WHDH, WRUF, WEEU

840 Kilocycles, 356.9 Meters—Canadian Wave:

850 Kilocycles, 352.7 Meters:
KWKH, WWL

860 Kilocycles, 348.6 Meters:
WBOQ, WABC, KMO, WHB

870 Kilocycles, 344.6 Meters:
WLS, WENR, WBCN

880 Kilocycles, 340.7 Meters—Canadian Shared:

WQAN, WGBI, WCOC, KLX, KPOF, KFKA, WSUI

890 Kilocycles, 336.9 Meters—Canadian Shared:

WJAR, WMMN, WGST, KARK, WILL, KUSD, KFNF, WKAQ

900 Kilocycles, 331.1 Meters:
WKY, WLBL, KHJ, KSEI, KGBU, WJAX, WBEN

910 Kilocycles, 329.5 Meters—Canadian Wave:

920 Kilocycles, 325.9 Meters:
WWJ, KPRC, WAAF, WBSO, KOMO, KFXF, KFEL

930 Kilocycles, 322.4 Meters—Canadian Shared:

WIBG, WDBJ, WBRC, KGBZ, KMA, KFWI, KROW

940 Kilocycles, 319 Meters:
WCSH, WFIW, KOIN, KGU, WHA, WDAY, WAAT

950 Kilocycles, 315.6 Meters:
WRC, KMBC, KFWB, KGHL

960 Kilocycles, 312.3 Meters—Canadian Wave:

970 Kilocycles, 309.1 Meters:
KJR, WCFL

980 Kilocycles, 305.9 Meters:
KDKA

990 Kilocycles, 302.8 Meters:
WBZ, WBZA

1000 Kilocycles, 299.8 Meters:
WHIO, WOC, KFVD

1010 Kilocycles, 296.9 Meters—Canadian Shared:

WQAO, WPAP, WHN, WRNY, KGGF, WNOAD, KQW, WIS, WLAP

1020 Kilocycles, 293.9 Meters:
KYW, KFKX, WRAX

1030 Kilocycles, 291.1 Meters—Canadian Wave:

1040 Kilocycles, 288.3 Meters:
WKAR, KTHS, KRLD

1050 Kilocycles, 285.5 Meters:
KNX, KFKB

1060 Kilocycles, 282.8 Meters:
WBAL, WJAG, KWJJ, WTIC

1070 Kilocycles, 280.2 Meters:
WTAM, WCAZ, WDJ, KJBS

1080 Kilocycles, 277.6 Meters:
WBT, WCBD, WMBI

1090 Kilocycles, 275.1 Meters:
KMOX

1100 Kilocycles, 272.6 Meters:
WPG, WLWL, KGDM

1110 Kilocycles, 270.1 Meters:
WRVA, KSOO

1120 Kilocycles, 267.7 Meters—Canadian Shared:

WTAW, WISN, WHAD, KFSG, KRSC, WDEL, WDBO, KFIO, KTRH, KMSC, KMBC

1130 Kilocycles, 265.3 Meters:
WVO, KSL, WJJD

1140 Kilocycles, 263.0 Meters:
WAPI, KVOO

1150 Kilocycles, 260.7 Meters:
WHAM

1160 Kilocycles, 258.5 Meters:
WVVA, WOWO

1170 Kilocycles, 256.3 Meters:
WCAU

1180 Kilocycles, 254.1 Meters:
KEX, KOB, WHDI, WDG, WMAZ, WGBS

1190 Kilocycles, 252.0 Meters:
WOAI

1200 Kilocycles, 249.9 Meters—Canadian Shared:

WABI, WNBX, WORC, WIBX, WHBC, WBHS, WLBG, WNBO, WKJC, WNBW, WABZ, WJBW, WBBZ, WFBC, WRBL, KGCU, WJBC, WJBL, WVAE, WFAM, KFJB, WCAT, KGDY, KFWF, KGDE, WCLO, WHBY, KSMR, WIL, KVOS, KGY, KGEK, KGEW, KGH, WCAZ, WCOD, WFBE, KBTM, WEPS, KMLB, KGFJ, KWG

1210 Kilocycles, 247.8 Meters—Canadian Shared:

WIBI, WGBB, WCOH, WOCL, WLCL, WPAW, WPRO, WLSI, WJW, WBAX, WJBU, WMBG, WSIX, WJBY, WRBO, WPCM, KWEA, KDLR, KGCR, KFOR, WHBU, KFVS, WBO, WODX, WCRW, WEDC, WCBZ, WTAX, WHBF, WOMT, WSBC, KDFN, KMI, KFXM, KPPC, WALR, WBLB, WMRJ, KGMP, KGNO, WSEN, WSOC, WIBU, KFJJ

1220 Kilocycles, 245.6 Meters:
WCAD, WCAE, WREN, KFKU, WDAE, KWSC, KTW

1230 Kilocycles, 243.8 Meters:
WNAC, WBIS, WPSG, WSBT, WFEM, KFQD, KYA, KGGM

1240 Kilocycles, 241.8 Meters:
WACO, KTAT, WXYZ

1250 Kilocycles, 239.9 Meters:
WGCP, WODA, WAAM, WLB, WGMS, WRHM, KFMX, WCAL, KFOX, WDSU

1260 Kilocycles, 238.0 Meters:
WLBW, KWWG, KRGV, KOIL, KVOA, WTOC

1270 Kilocycles, 236.1 Meters:
WEAL, WASH, WOOD, KWLC, KGCA, KOL, KVOR, WFBR, WJDX

1280 Kilocycles, 234.2 Meters:
WCAM, WCAP, WOAX, WDDO, WRR, KFBB, WIBA, WISJ

1290 Kilocycles, 232.4 Meters:
WNBZ, WJAS, KTSB, KFUL, KLCN, KDYL, WBCB

1300 Kilocycles, 230.6 Meters:
WBBR, WHAP, WEVD, WHAZ, KFH, KGEF, KFAC, KFJR, KTRB, WIOD, WMBF, WOO

1310 Kilocycles, 228.9 Meters:
WKAV, WEBR, WNBH, WOL, WGH, WHAT, WEBG, WRAW, WGA, WSAJ, WBRB, WKBC, WTJS, KRMD, KFP, WDAH, KPPL, KFXR, WKBS, WCLS, WKBB, KWCR, KFYP, KFGO, WBOV, WJAK, WLBC, KTSB, KFUP, KFXJ, KFBK, KGEZ, KMED, KTSB, KGCC, WJAC, WSJS, KXRO, KGFV, KFIU, KGBX, KIT, WMBO, KCRJ, KTLC, WEXL, WROL, WTEL, WBEO, WFDV

1320 Kilocycles, 227.1 Meters:
WADC, WSMB, KID, KTFI, KGHF, KGMB, KGIQ

1330 Kilocycles, 225.4 Meters:
WDRG, WTAQ, KSCJ, WSAI, KGB

1340 Kilocycles, 223.7 Meters:
KFPW, WCOA, KFPY, WSPD

1350 Kilocycles, 222.1 Meters:
WMSG, WCDA, WBNX, KWK, WAWZ, WEHC, KIDO

1360 Kilocycles, 220.4 Meters:
WOBZ, WGES, KGIR, KGER, WFBL, WCSC, WJKS

1370 Kilocycles, 218.8 Meters:
WSVS, WCBM, WHBD, WJBK, WIBM, WRAK, WDS, WHBO, WRAM, KGGF, KFJZ, KGKL, KFLX, KGDA, KRE, WPOE, KFB, KWKC, WRJN, KGAR, KVL, KGLF, WHDF, KOOS, WGL, KFJM, KCR, WMBR, WRBJ, WLEY, WBGF, WBTM, WLVA, WQDM, WRDO, KONO, KMAC, KUJ, WJTL, KOH

1380 Kilocycles, 217.3 Meters:
KQV, KSO, WKBH, WSMK

1390 Kilocycles, 215.7 Meters:
WHK, KLRA, KUOA, KOY

1400 Kilocycles, 214.2 Meters:
WCGU, WFOX, WLTH, WBBZ, WCMA, WKBF, KOCW, WBA, KLO

1410 Kilocycles, 212.6 Meters:
KGRS, WDAG, KFLV, WHBL, WBCM, WODX, WSFA, WAA, WRBX, WHIS

1420 Kilocycles, 211.1 Meters:
WTBO, WKBI, WEDH, WMBZ, KGGF, KABC, KPYO, KICK, WIAS, KGGC, WLBZ, WMBH, KRIZ, KORE, WILM, KGIW, KGY, KFOV, KLFM, KXL, WHDI, WHFC, WEHS, KFOU, KFXD, KGIX, WBO, WELL, WFDW, WPA, WSPA, KBPS, KFX, KXYZ, WAGM, WDEV, KGO, WJMS, WDX

1430 Kilocycles, 209.7 Meters:
WHP, WCAH, WGBC, WNBR, WBAK, KECA, KGNF, WFEA

1440 Kilocycles, 208.2 Meters:
WHCC, WABO, WOKO, WCBA

1450 Kilocycles, 206.8 Meters:
WBMS, WNJ, WKBO, WSAR, WGAR, WTFI, KTBS, WHOM

1460 Kilocycles, 205.4 Meters:
WJSV, KSTP

1470 Kilocycles, 204.0 Meters:
KGA, WTNT, WLAC

1480 Kilocycles, 202.6 Meters:
KFJF, WKBW

1490 Kilocycles, 201.6 Meters:
WCKY, WCHI

1500 Kilocycles, 199.9 Meters:
WMB, WLOE, WNBZ, WMBQ, WLBX, WWRL, WKBZ, WMPG, WOPI, WPEB, KGB, WKBV, KPJM, KDB, KGFL, WMBJ, KREG, WCLB, WRDW, KGIZ, KGKY, KPO, KUT, KXO, KGF, WSYB, WWSW

LIST OF POLICE BROADCASTING STATIONS

Call	Kilocycles	Meters	Location	Call	Kilocycles	Meters	Location
WPDO	2,458	122.05	Akron, Ohio	KGPE	2,422	123.86	Kansas City, Mo.
WPDY	2,452	122.34	Atlanta, Ga.	WPDL	2,470	121.50	Kokomo, Ind.
KGPS	2,416	124.17	Bakersfield, Calif.	WPDL	2,440	123.00	LaSalle, Mich.
KGPF	1,712	175.23	Beaumont, Tex.	KGPI	1,712	175.23	Los Angeles, Calif.
KSW	2,410	124.50	Berkeley, Calif.	WTDE	2,440	123.00	Louisville, Ky.
WEY	1,596	187.97	Boston, Mass.	WPEC	2,470	121.50	Memphis, Tenn.
WRDQ	1,596	187.97	Brooklyn, N. Y.	WPDK	2,452	122.34	Milwaukee, Wis.
WJW	2,422	123.86	Buffalo, N. Y.	KGPK	2,416	124.17	Minneapolis, Minn.
WBR	257	1,165.00	Butler, Pa.	WPY	458	685.00	New York, N. Y.
KGQZ	2,470	121.50	Cedar Rapids, Iowa	WPY	500	600.00	New York, N. Y.
WDDV	2,458	122.05	Charlotte, N. C.	WCF	1,596	187.97	New York, N. Y.
WPDB	1,712	175.23	Chicago, Ill.	KGPH	2,452	122.34	Oklahoma City, Okla.
WPDC	1,712	175.23	Chicago, Ill.	KGPI	2,470	121.50	Omaha, Neb.
WPDD	1,712	175.23	Chicago, Ill.	KGIX	1,712	175.23	Pasadena, Calif.
WKDU	1,712	175.23	Cincinnati, Ohio	WPDJ	2,440	123.00	Philadelphia, Pa.
WRBH	2,452	122.34	Cleveland, Ohio	WPDJ	1,712	175.23	Pittsburgh, Pa.
WPDI	2,416	124.17	Columbus, Ohio	WPDJ	2,416	124.17	Portland, Ore.
KVI	1,712	175.23	Dallas, Tex.	KGPP	2,416	124.17	Richmond, Ind.
KGPN	2,470	121.50	Davenport, Iowa	WPDH	2,416	124.17	Rochester, N. Y.
WPDM	2,416	124.17	Dayton, Ohio	WFDI	1,712	175.23	St. Louis, Mo.
KGPF	2,506	180.51	Des Moines, Iowa.	WFDI	2,416	124.17	St. Paul, Minn.
WRDP	1,596	187.97	Detroit, Mich.	WFDI	2,470	121.50	Salt Lake City, Utah.
WCK	2,000	150.00	Detroit, Mich.	KGPP	43,000	6.97	San Francisco, Calif.
WPDX	2,410	124.50	Detroit, Mich.	KGPD	1,596	187.97	San Francisco, Calif.
WDF	2,440	123.00	Flint, Mich.	KGPD	2,410	124.50	San Jose, Calif.
KGPR	1,712	175.23	Ft. Worth, Tex.	KGPM	2,470	121.50	Seattle, Wash.
WMP	1,662	180.51	Framingham, Mass.	KGPA	2,416	124.17	Sioux City, Iowa
WPEB	2,440	123.00	Grand Rapids, Mich.	KGPK	2,470	121.50	Toledo, Ohio
WHL	257	1,165.00	Groesbeek, Pa.	WRDQ	2,470	121.50	Tulare, Calif.
WRDR	257	1,165.00	Grosse Pointe Village, Mich.	WQXA	2,416	124.50	Vallejo, Calif.
WBA	257	1,165.00	Harrisburg, Pa.	WQXB	2,410	124.50	Washington, D. C.
WMO	2,410	124.50	Highland Park, Mich.	WMB	257	1,165.00	West Reading, Pa.
KGQZ	2,452	122.35	Honolulu, T. H.	KGPIZ	2,450	122.4	Wichita, Kans.
WMDZ	2,440	123.00	Indianapolis, Ind.	WDX	257	1,165.00	Wyoming, Pa.
WRDS	1,662	180.51	Ingham, Mich.	WFDG	2,458	122.05	Youngstown, Ohio

U. S. VISUAL BROADCASTING STATIONS

Call	Kilocycles	Meters	Owner	Call	Kilocycles	Meters	Owner
W1XAU	1,500	193.6	Short Wave & Television, Boston, Mass.	W3XAD	48,500	6.18	RCA-Victor, Camden, N. J.
L1XV	2,850	106.30	Short Wave & Television, Boston, Mass.	W3XAD	60,000	5.00	RCA-Victor, Camden, N. J.
W2XAB	2,750	109.10	Atlantic Broadcasting, New York, N. Y.	W3XAD	2,100	142.90	RCA-Victor, Camden, N. J.
W2XBC	2,750	109.10	United Research Corp., Long Island City, N. Y.	W3XK	2,000	150.00	Jenkins Laboratories, Wheaton, Md.
W2XBU	2,000	150.00	Harold E. Smith, Beacon, N. Y.	W3XHI	3,000	100.00	Pioneer Mercantile Co., Bakersfield, Calif.
W2XCD	2,000	150.00	DeForest Radio Co., Passaic, N. J.	W3XHO	43,000	6.97	Don Lee, Inc., Los Angeles, Calif.
W2XCR	2,100	142.90	Jenkins Television, Jersey City, N. J.	W3XN	2,100	142.90	Don Lee, Inc., Los Angeles, Calif.
W2XCR	2,000	150.00	Jenkins Television, Jersey City, N. J.	W3XAV	2,100	142.90	Westinghouse, East Pittsburgh, Pa.
W2XCW	2,100	142.90	General Electric, Schenectady, N. Y.	W3XAA	2,750	109.10	Federation of Labor, Chicago, Ill.
W2XDA	1,544	194.30	Athletic Broadcasting, New York, N. Y.	W3XAB	1,564	191.82	Federation of Labor, Chicago, Ill.
W2XDS	43,000	6.98	Jenkins Television, New York, N. Y.	W3XAC	2,000	150.00	Western Television Corp., Chicago, Ill.
W2XDS	48,500	6.18	Jenkins Television, New York, N. Y.	W3XAD	2,100	142.90	Daily News, Chicago, Ill.
W2XDS	60,000	5.00	Jenkins Television, New York, N. Y.	W3XAE	43,000	6.97	Journal Company, Milwaukee, Wis.
W2XDP	43,000	6.97	National Broadcasting, New York, N. Y.	W3XAF	48,500	6.18	Journal Co., Milwaukee, Wis.
W2XDP	48,500	6.18	National Broadcasting, New York, N. Y.	W3XAG	60,000	6.00	Journal Co., Milwaukee, Wis.
W2XDP	60,000	5.00	National Broadcasting, New York, N. Y.	W3XAH	2,750	109.10	Purdue University, W. Lafayette, Ind.
W2XR	2,850	106.30	Radio Pictures, Inc., Long Island City, N. Y.	W3XAI	2,850	105.30	Great Lakes Broadcasting, Chicago, Ill.
W3XAD	43,000	6.97	RCA-Victor, Camden, N. J.	W3XAJ			

U. S. RELAY BROADCASTING STATIONS

Call	Kilocycles	Meters	Owner	Call	Kilocycles	Meters	Owner
W1XAL	6,040	49.67	Short Wave Bdstg. Corp., Boston, Mass.	W6XAF	4,938	112.10	Dept. Agriculture, Sacramento, Calif.
W1XAL	11,800	25.42	Short Wave Bdstg. Corp., Boston, Mass.	W6XAF	5,870	51.11	Dept. Agriculture, Sacramento, Calif.
W1XAL	15,250	19.67	Short Wave Bdstg. Corp., Boston, Mass.	W6XAL	6,050	49.34	Pacific-Western Broadcasting, Westminster, Calif.
W1XAL	21,460	13.97	Short Wave Bdstg. Corp., Boston, Mass.	W6XAL	15,250	19.67	Pacific-Western Broadcasting, Westminster, Calif.
W1XAZ	9,570	31.35	Westinghouse Elec., East Springfield, Mass.	W6XAL	21,500	13.95	Pacific-Western Broadcasting, Westminster, Calif.
W2XAD	15,340	19.56	General Electric, Schenectady, N. Y.	W6XAN	12,850	23.35	General Electric, Oakland, Calif.
W2XAF	9,530	31.43	General Electric, Schenectady, N. Y.	W6XAL	6,060	49.50	Crosley Radio Corp., Cincinnati, Ohio
W2XAG	550	545.00	General Electric, Schenectady, N. Y.	W6XAN	6,130	48.85	Westinghouse, East Pittsburgh, Pa.
W2XAG	860	455.00	General Electric, Schenectady, N. Y.	W6XAN	9,570	31.35	Westinghouse, East Pittsburgh, Pa.
W2XAG	790	380.00	General Electric, Schenectady, N. Y.	W6XAN	11,880	25.25	Westinghouse, East Pittsburgh, Pa.
W2XAG	1,150	260.00	General Electric, Schenectady, N. Y.	W6XAN	15,210	19.72	Westinghouse, East Pittsburgh, Pa.
W2XAG	1,500	200.00	General Electric, Schenectady, N. Y.	W6XAN	17,780	16.87	Westinghouse, East Pittsburgh, Pa.
W2XAP	6,120	49.02	Atlantic Broadcasting, Jamaica, N. Y.	W6XAN	21,540	13.93	Westinghouse, East Pittsburgh, Pa.
W2XAP	11,540	25.34	Atlantic Broadcasting Co., Jamaica, N. Y.	W6XAA	6,050	49.34	Federation of Labor, Chicago, Ill.
W2XAP	15,280	19.63	Atlantic Broadcasting Co., Jamaica, N. Y.	W6XAA	11,840	25.34	Federation of Labor, Chicago, Ill.
W2XAP	610	491.50	National Broadcasting, Bellmore, N. Y.	W6XAA	17,780	16.87	Federation of Labor, Chicago, Ill.
W3XAL	6,100	49.18	National Broadcasting, New York, N. Y.	W6XAP	6,020	49.83	Great Lakes Broadcasting, Chicago, Ill.
W3XAL	6,060	49.50	Universal Broadcasting, Newton Township, Pa.	W6XAP	11,800	25.42	Great Lakes Broadcasting, Chicago, Ill.
W3XAU	9,590	31.23	Universal Broadcasting, Newton Township, Pa.	W6XAP	21,500	13.95	Great Lakes Broadcasting, Chicago, Ill.
W3XAL	6,425	46.70	National Broadcasting, New York, N. Y.	W6XAU	6,060	49.50	Mona Motor Oil Co., Council Bluffs, Iowa

SIMPLE TIME CHART

(Time changes every 15 degrees of Longitude East or West)

PLACES ON, OR NEARLY ON, THE MERIDIAN INDICATED.	LONGITUDE WEST OF GREENWICH												
	180°	165°	150°	135°	120°	105°	90°	75°	60°	45°	30°	15°	0°
	FIJI ISLANDS	UNALASKA	SEWARD	JUNEAU	LOS ANGELES	DENVER	CHICAGO	NEW YORK	BUENOS AIRES	RIO JANEIRO	AZORES	ICELAND	(GREENWICH) LONDON
TIME	Midnight	1 a.m.	2 a.m.	3 a.m.	4 a.m.	5 a.m.	6 a.m.	7 a.m.	8 a.m.	9 a.m.	10 a.m.	11 a.m.	Noon
↑ International date line. When it's Monday East of 180° it is Tuesday West of 180°.													
	LONGITUDE EAST OF GREENWICH												
	0°	15°	30°	45°	60°	75°	90°	105°	120°	135°	150°	165°	180°
	(GREENWICH) LONDON	BERLIN	ODESSA CAIRO	ADEN	MAURITIUS ISL.	LAHORE	CALCUTTA	BATAVIA	MANILA	KOBE	EASTERN AUSTRALIA	NEW CALEDONIA	FIJI ISLANDS
TIME	Noon	1 p.m.	2 p.m.	3 p.m.	4 p.m.	5 p.m.	6 p.m.	7 p.m.	8 p.m.	9 p.m.	10 p.m.	11 p.m.	Midnight

FOREIGN BROADCAST STATIONS

Table listing foreign broadcast stations by country (Algeria, Argentina, Australia, Austria, Belgium, Bolivia, Brazil, Canada, Canal Zone, Canary Islands, Ceylon, Chile, China, Colombia, Costa Rica, Cuba, Czechoslovakia, Danzig, Denmark, Dominican Republic, Dutch East Indies, Egypt, Estonia, Finland, France, Germany, etc.) with columns for Call, Location, Kc., and other details.

FOREIGN SHORT WAVE PHONE STATIONS

Call	Location	Kc.	Call	Location	Kc.	Call	Location	Kc.
ARGENTINA			FINLAND			Mexico City 6.667		
L5X	Buenos Aires	10.352	FRANCE			XFD	Mexico City	9.091
L5G	Buenos Aires	19.900	FYR	Agen	9.760	XFD	Mexico City	11.111
L5N	Buenos Aires	21.200	FYR	Lyons	7.463	XFA	Mexico City	6.977
AUSTRALIA			FYR	Lyons	5.172	XFA	Mexico City	7.143
VK3ME	Melbourne	9.510	F8AV	Nancy	19.350	XFA	Mexico City	21.243
VK6AG	Perth	7.194	FLJ	Paris	3.750	MONACO		
VK2ME	Sydney	10.526	F8LH	Paris	9.230	MOROCCO		
VLK	Sydney	10.526	F8GC	Paris	7.317	CNSMC	Casablanca	6.881
AUSTRIA			F8GC	Paris	4.918	CNSMC	Casablanca	5.832
.....	Vienna	13.514	Pontoise-Seine-et-Oise	11.720	Rabat	12.610
UOR2	Vienna	11.801	Pontoise-Seine-et-Oise	11.995	Rabat	9.300
OU1H	Vienna	8.060	F8BP	Rugles	15.243	Rabat	12.605
UOR2	Vienna	6.072	FTD	St. Assise	19.840	Rabat	9.300
OHK2	Vienna	4.274	FRO	St. Assise	19.417	NEWFOUNDLAND		
BELGIUM			FRE	St. Assise	19.417	V08A	St. Johns	6.800
BOLIVIA			FTM	St. Assise	19.355	NEW ZEALAND		
BRAZIL			FTE	St. Assise	18.248	ZL2XX	Wellington	9.550
PPU	Rio de Janeiro	6.122	FSE	St. Assise	13.441	NORWAY		
PPU	Rio de Janeiro	19.270	FQO	St. Assise	12.161	PERU		
BRITISH COLONIES			FQE	St. Assise	12.161	PHILIPPINE ISLANDS		
VRY	Georgetown, Guiana	6.726	PTN	St. Assise	12.265	K41XR	Manila	12.245
TJW	Hamilton, Bermuda	9.500	PTL	St. Assise	9.950	KZRI	Manila	11.840
.....	Mombas, Kenya	13.895	PTF	St. Assise	7.770	Manila	9.570
.....	Mombas, Kenya	8.230	PTB	St. Assise	7.490	Manila	6.140
VQ7LO	Nairobi, Kenya	6.100	Touraine	7.500	POLAND		
V80WX	Singapore	7.190	Toulouse	6.122	Poznan	11.001
CANAL ZONE			FRENCH COLONIES			Poznan	8.900
CANADA			FMSKR	Constantine	7.009	PORTUGAL		
VE9GW	Rowmanville, Ont.	6.095	FMSKR	Constantine	3.750	PTIAA	Lisbon	7.143
VE9GW	Rowmanville, Ont.	11.810	GERMANY			Oporto	12.000
VE9GW	Rowmanville, Ont.	24.380	D4AUF	Eiberswalde	7.407	ROUMANIA		
VK0G	Calgary, Alta.	6.110	DHA	Kothen	7.042	Y01	Bucharest	13.950
VE9CA	Calgary, Alta.	6.030	DIIC	Nauen	11.760	SALVADOR		
VE9CA	Calgary, Alta.	11.860	DIIC	Nauen	15.200	SHIP PHONE STATIONS		
VE9DR	Drummondville, Que.	11.780	DGW	Nauen	6.020	GMJQ	SS. Belgenland	17.650
VE9CF	Itafax, N. S.	6.050	Nauen	17.760	GMJQ	SS. Belgenland	13.049
VE9CL	Middlechurch, Man.	6.150	Nauen	9.560	GMJQ	SS. Belgenland	8.570
VE9DN	Montreal, Que.	6.005	GREAT BRITAIN			DDDX	SS. Bremen	11.710
VE9DN	Montreal, Que.	9.580	GBK	Bodmin	18.105	DDDX	SS. Bremen	7.560
VE9DN	Montreal, Que.	11.895	GBK	Bodmin	9.260	IBDX	SS. Electra (Marconi's Yacht)	11.240
VE9BA	Montreal, Que.	6.130	G58W	Chelmsford	11.750	SS. Hamburg	13.040
VE9BA	Montreal, Que.	11.705	GBX	Rugby	16.164	GDLI	SS. Homeric	12.380
VE9BA	Montreal, Que.	15.190	G8S	Rugby	18.310	GDLI	SS. Homeric	4.734
VE9AK	Red Deer, Alta.	2.830	GBW	Rugby	18.138	WSBN	SS. Leviathan	8.830
VE9FJ	St. John, N. B.	6.090	GBW	Rugby	14.493	WSBN	SS. Leviathan	6.637
VE9CS	Vancouver, B. C.	6.070	GBU	Rugby	12.290	WSBN	SS. Leviathan	4.392
CURACAO			GBX	Rugby	12.195	WSBN	SS. Leviathan	3.429
PJZ	Curacao	11.718	G8S	Rugby	12.195	GFVW	SS. Majestic	17.590
CZECHOSLOVAKIA			G8S	Rugby	9.020	GFVW	SS. Majestic	13.228
.....	Bratislava	5.000	G8S	Rugby	6.993	GFVW	SS. Majestic	4.390
OK1MPT	Prague	5.119	G21N	Sonning-on-Thames	14.320	GLSQ	SS. Olympic	12.387
OK1MPT	Prague	4.412	HAITI			GLSQ	SS. Olympic	16.456
CHILE			GUATEMALA			GLSQ	SS. Olympic	8.840
CHINA			HOLLAND			SIAM		
XCTE	Shanghai	5.000	PEF5	Hague	6.438	HS2FJ	Bangkok	10.169
COLOMBIA			PCJ	Hilversum	9.590	HSP2	Bangkok	9.500
HKA	Barranquilla	5.837	PHI	Hilversum	15.220	HSP2	Bangkok	7.300
HKD	Barranquilla	6.993	PCK	Kootwijk	17.775	SPAIN		
HKF	Bogota	7.194	ICV	Kootwijk	18.400	EAI1	Barcelona	15.789
HKG	Bogota	6.250	HONDURAS			EAR96	Barcelona	6.522
HKX	Bogota	6.977	HRB	Tegucigalpa	6.170	EAR25	Barcelona	6.000
HKX	Bogota	7.143	HUNGARY			EAR58	Las Palmas, Canary Islands	7.210
COSTA RICA			ICELAND			EAI10	Madrid	7.026
T1H	Heredia	9.734	INDIA			EAI25	Madrid	7.026
T1TR	San Jose	11.790	VUC	Calcutta	11.870	EAI25	Malaya	3.000
CUBA			INDO-CHINA			EAI25	Malaya	6.522
CM2LA	Havana	10.007	F31CD	Chi-hoa	6.122	SWEDEN		
CM2MK	Havana	9.360	FZR	Saigon	16.216	Motala	6.070
CM6XJ	Tuinucu	15.008	FZR	Saigon	12.043	SWITZERLAND		
DANZIG			IRISH FREE STATE			HB9OC	Berne	9.130
EK4ZZZ	Danzig	7.500	ITALY			HB9XD	Zurich	9.380
DENMARK			12RO	Rome	11.811	HB9XD	Zurich	7.229
OXZ	Skamlabæk	9.520	12RO	Rome	3.750	HB9XD	Zurich	3.488
DOMINICAN REPUBLIC			12RO	Rome	3.750	TURKEY		
HIX	Santo Domingo	4.610	Turin	3.750	UNION OF SOVIET SOCIALIST REPUBLICS		
DUTCH EAST INDIES			HVJ	Vatican City	5.968	RW15	Khabarovsk	4.273
PMB	Bandoeng	20.620	HVJ	Vatican City	15.120	KW3KAA	Leningrad	8.333
PLE	Bandoeng	18.830	JAPAN			Leningrad	11.111
PLG	Bandoeng	15.957	J1AA	Kemikawa	17.391	Leningrad	10.526
PMY	Bandoeng, Java	5.172	J1AA	Kemikawa	8.000	RW62	Minsk	6.120
PK2AF	Djocjarta, Java	5.172	JUGOSLAVIA			RW61	Moscow	51.724
PK6KZ	Mekassar	6.000	Belgrade	13.000	RW38	Moscow	5.514
PK2AG	Semerang, Java	2.609	LATVIA			RW59	Moscow	6.000
PK3AN	Surabaya, Java	6.036	LITHUANIA			Moscow	6.611
PK1AA	Surabaya	2.143	MADAGASCAR			RW50	Moscow	11.924
.....	Weltevreden, Java	4.000	Tananarive	6.000	RW65	Peredvika	3.500
ECUADOR			MADEIRA			RW19	Tomsk	8.111
.....	Riobamba	7.540	CT3AG	Funchal	6.383	URUGUAY		
EGYPT			MEXICO			UNION OF SOUTH AFRICA		
ESTONIA			XDA	Mexico City	14.634	ZTJ	Johannesburg	9.380
FIJI			XDA	Mexico City	9.380	VENEZUELA		
VPD	Suva	14.430	XDA	Mexico City	6.818			

Linear Amplifiers in Broadcasting

By H. M. SMITH*

WITH the advent of vacuum tubes and associated circuits in radio communication, the status of radiotelephony was changed from an interesting laboratory possibility to a point where its economic practicability was strongly indicated. Hitherto, investigations of radiotelephony had been confined to arc transmitters, high frequency alternators, etc., as sources of continuous waves, and the difficulties encountered in efficiently modulating the usually high power output of such devices made for low over-all transmitter efficiency and extremely doubtful economics.

By means of vacuum tubes in oscillatory and amplifying circuits the possibilities of voice transmission became increasingly evident. Many and varied schemes of modulation were evolved, ranging from absorption methods to frequency modulation. The Heising, or so-called "constant current" system of amplitude modulation has been adopted more generally in this country, due to its comparative simplicity and efficiency of operation. The general theory of modulation has been treated exhaustively in the technical literature. A practical application of some of the principles involved has apparently become somewhat obscured in the recent trend towards linear amplifiers.


Any system of amplitude modulation is essentially a method of varying the output power of a radio transmitter by an appreciable amount at the modulating frequency. Previous to the introduction of linear amplifiers, this was effected in the oscillator or power amplifier. An audio amplifier of suitable power (usually termed the modulator) is so connected in the power amplifier plate supply that the varying output voltage of the modulator raises and lowers the d.c. plate voltage on the modulated tube at an audio frequency rate. Within the approximate limits of plate saturation and cut-off the radio frequency voltage across the tank circuit of the modulated tube, and consequently the antenna current, are directly proportional to the instantaneous plate voltage applied to the modulated tube.

Until comparatively recently, radio frequency amplifiers having power outputs up to 50 kw and more were modulated in this manner without serious difficulty. As has been pointed out, the so-called modulator is essen-

tially an audio amplifier, and, as such, is subject to the inherent limitations of any class A amplifier, i. e., very low efficiency if distortion is to be kept at a low value. In practice a bank of low impedance tubes is usually required to fulfill the conditions of high percentage modulation with low distortion, with the necessity for a choke of high inductance capable of carrying a large amount of direct current. In

is generally used to lower the plate voltage applied to the modulated tubes. At the higher powers, such a device becomes rather bulky and expensive and the power dissipated in this device becomes appreciable.

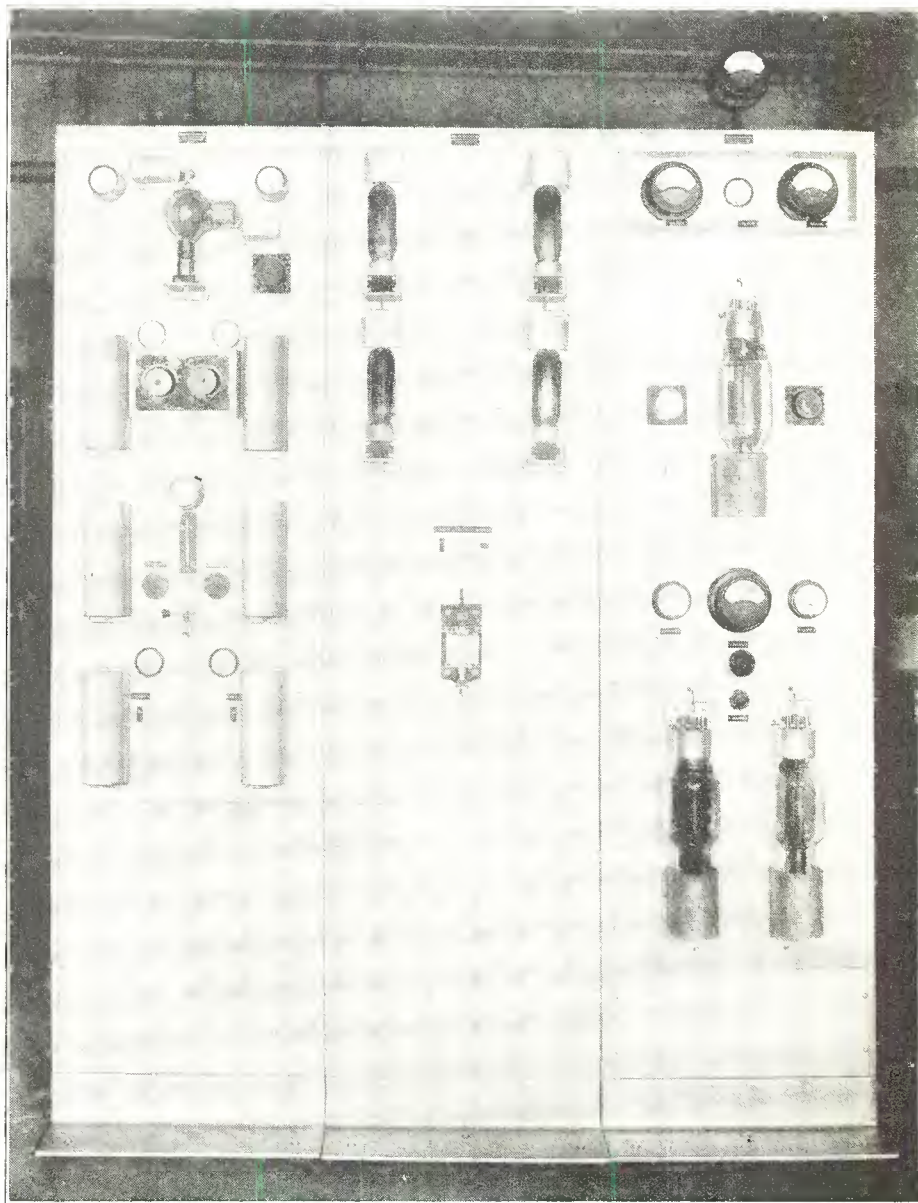Due to the large variety of power outputs and plate impedances of available air-cooled tubes, high level modulation is usually to be preferred in transmitters of power outputs up



the case of high power transmitters using water cooled tubes, this represents a formidable investment, and due to the low efficiency of the modulator, the operating cost is quite high. To obtain 100 per cent modulation, some sort of voltage dropping device

to about 500 watts. A 250 watt, high level, 100 per cent modulated transmitter of recent design is shown. It is of the crystal-controlled, power amplifier type and has a self-contained rectifier using mercury vapor tubes,

(Continued on next page)

* Engineer, Doolittle & Falknor, Inc.

Linear Amplifiers in Broadcasting

(Continued from page 15)

together with a suitable filter.

Above 500 watts output, the factors mentioned in the previous paragraph, plus a consideration of the ratio of fixed cost to annual charges, usually make the use of some form of linear amplifier desirable. Any amplification taking place after modulation has been effected must be of such a nature that the instantaneous voltages across the antenna coupling device will be directly proportional to the voltages across the tank circuit of the modulated amplifier. It might be supposed that such amplifiers would have to be operated class A to fulfill these conditions. This is not the case however, as the tube has an oscillatory circuit as its load. Such a circuit, if properly designed, has quite a flywheel effect, and its tube may be biased practically to cut-off (without excitation) and still provide an output of good wave form under certain conditions.

In a class B amplifier:

$$\text{Power input} = \frac{E_b I_p \text{ av}}{2} = \frac{E_b I_p \text{ max}^2}{2} \dots 1$$

$$\text{Power output} = \frac{.5 E_p \text{ max } I_p \text{ max}}{2} \dots \dots 2$$

$$\text{Efficiency} = \frac{\text{Output}}{\text{Input}} = \frac{E_p \text{ max}}{4 E_b} \dots \dots \dots 3$$

where: E_b d.c. plate voltage
 $E_p \text{ max}$ = maximum a.c. plate voltage
 $I_p \text{ av}$ = average plate current
 $I_p \text{ max}$ = maximum plate current

Equation 3 indicates that the maximum efficiency is obtained in a class B tube when the instantaneous peak plate voltage equals the d.c. supply voltage. Under such conditions the maximum efficiency would be 78.54 per cent. This value is purely theoretical and cannot be attained in practice. A maximum practical value of 66.67 per cent has been arbitrarily established and can usually be obtained on peaks without difficulty.

It may be shown that the input power to a class B tube varies directly with the grid voltage; the power output varies as the square of the grid voltage. It therefore follows that the efficiency, being a quotient, varies as the first power of the grid voltage. Also, 100 per cent modulation requires that the instantaneous grid and

plate voltages be double the unmodulated value. Therefore the maximum unmodulated efficiency of a class B amplifier cannot be greater than 33.3 per cent or one-half of the 100 per cent modulated value. If it is greater, the transmitter output will not be capable of 100 per cent modulation; if less, the output power will be substantially reduced.

Equation 2 shows that the output power, on 100 per cent modulation peaks produced by doubling the instantaneous grid voltage, is four times the unmodulated value. For this reason it is necessary that the tube capacity in the amplifier be four times as large as would be required if the same carrier power were not modulated.

Conditions noted above for a single-sided circuit hold good where tubes are used in push-pull, if the tubes are individually biased so that without r.f. excitation no plate current flows. In this case the amplifier stage may be considered as a gas engine having two opposed cylinders. Such an arrangement will require less flywheel to supply a non-pulsating flow of power to a steady load than will a single cylinder. In application a higher L/C ratio may be used in the tank circuit of push-pull tubes than with a single tube, with a corresponding decrease in the ratio of circulating kva to kw output. Equations 1 and 2, for input and output power, are each multiplied by 2 where used for push-pull, class B tubes, but the efficiency as given in equation 3 is applicable to both single-sided and push-pull circuits.

To obtain maximum efficiency in a class B amplifier, the grid swing must be sufficiently great to carry the plate current almost to saturation. This usually means that the grids must be swung considerably positive with the result that the input impedance of the amplifier decreases. In operation, this impedance will become low enough to represent a substantial load on the exciting stage. If the load impedance on the driving stage varies, the voltage across this load, and consequently the voltage across the grid of the driven tube will vary, with the result that the amplifier is no longer linear, but rather will have a distorted output. To remedy this situation a constant load is provided for the driving tube, sufficiently great so that variations in input impedance of the driven tube will be so small in proportion as to be unable to vary the constant load to an appreciable extent. Such

loading is usually effected by inserting a suitable resistance in the tank circuit of the driving tube or an equivalent shunt resistance from grid to ground in the driven tube. (In the latter case the resistor is for r.f. only and must have a series capacity to keep the rectified grid current out of this branch.) Regardless of its location it is usually necessary that 50 to 80 per cent of the output of the driven tube be dissipated in this load. This reduces the over-all efficiency of the driving stage and is undesirable to that extent. Consideration of the grid current characteristics of available tubes and the use of a proper L/C ratio in the tank circuit of the driven tube will tend to keep this dissipation towards the lower value given above.

It happens occasionally that the function of such resistance loads which have just been discussed is to preclude the cutting of sidebands in the linear amplifier by broadening the resonance curve of the tank circuit. This is decidedly a secondary consideration for there is usually enough unavoidable resistance associated with tank circuits to satisfy the requirements for efficient transmission of the higher modulating frequencies.

Two recent examples in transmitter design are of interest. In one, using a push-pull amplifier (each tube operated class B) as the output stage, the secondary of an audio transformer is connected in series with the common bias supply. This scheme is in effect equivalent to a conventional linear amplifier, but due to the varying load placed on the speech input equipment, the linear amplifier grids cannot be swung very positive. For this reason the peak efficiency is about 45 per cent and the unmodulated efficiency must be held at about 22.5 per cent.

In the other, the designers have taken advantage of the fact that class B tubes used in push-pull result in a class A stage over-all, and apply this to the modulator system. A much greater amount of undistorted audio power can be obtained from such an arrangement than can be obtained from the same tubes used as conventional class A amplifiers. The modulator output is coupled to the modulated amplifier through a transformer of rather involved design. The gain in over-all efficiency is such as to make high level modulation economically practicable at considerably higher powers than heretofore.

Sound Films & Television Broadcast

THE film output of the moving picture studios of Hollywood, the East coast, Europe, features, news reels and shorts, have been made available for broadcasting by television. Though not in the home at the moment, the moving picture theatre is right at the front door, ready to take possession of the living room. The perfecting of apparatus enables television stations to make use of

speed slower than that at which the recording was made.

Armando Conto, research engineer for Western Television Corporation, of Chicago, sensing the difficulties, set about, 18 months ago, to perfect apparatus that would not only broadcast the pictures, so that the figures move with normal speed, but would also permit the sound to be taken from the film, undistorted.


The Western Television Corporation 3 spiral scanning system with which Conto worked divides any area to be broadcast into 45 horizontal parts at a speed of 15 times per second. This leaves a considerable gap between the 15 pictures per second as broadcast by the television station and the 24 pictures per second projected in the motion picture houses.

Conto looked with disfavor upon the method by which the film is kept in motion as a part of the scanning operation, a practice used in previous technique. He decided that better results could be obtained if the film remained stationary, as it does in the projection of moving pictures, moving forward at a predetermined time. Consequently, it was necessary to design a disc that would combine the effects produced by an ordinary scanning device and the shutter on a moving picture projector.

The resulting disc is so constructed that the apertures through which the light penetrates are placed on radii that are four degrees apart instead of eight degrees as in the ordinary 3 spiral 45 aperture disc. Thus, the 45 apertures occupy a 180-degree segment of the disc, leaving the other half blank to act as the shutter.

Conto uses two identical films. Film number 1 is located at the upper diam-

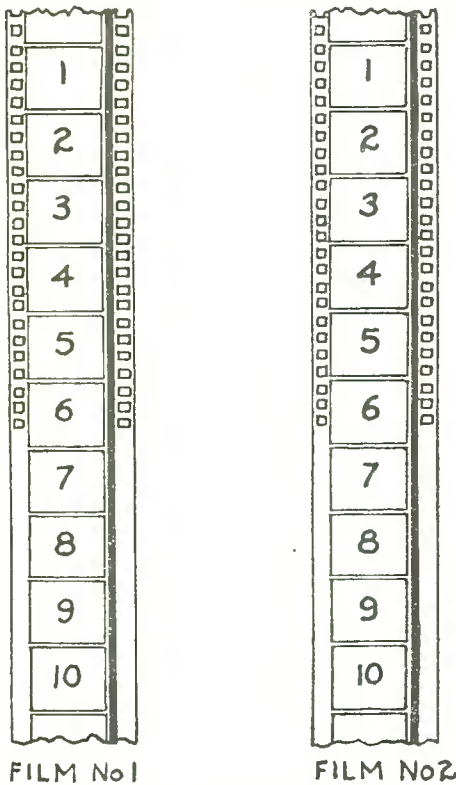
tion in each Geneva movement (the device which moves the films forward). The two Geneva movements and the scanning disc are interconnected mechanically in such a way that when the first aperture of the first spiral is in a position to scan picture No. 1 in film No. 1, film No. 1 remains motionless for the duration of the entire scanning operation.




standard commercial sight-sound films, such as are furnished moving picture houses. These are broadcast without distortion of the sound, the barrier which, until now, was apparently insurmountable.

One of the greatest difficulties encountered in the adaptation of the sight-sound film to television projection was caused by the difference in the rate of speed with which the pictures are taken on the movie lot, and that with which they are scanned in the television studio. The moving picture camera exposes 24 sections of the film each second, whereas television laboratories have experimented with scanning systems that project a maximum of 20 pictures per second.

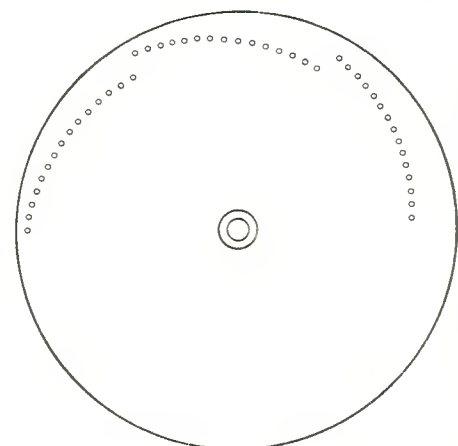The consequent slowing down of the film results in "slow-motion" of the characters in the picture. What is more important, the slower movement of the sound track past the photoelectric cell creates a sound distortion such as that occasioned by rotating the turntable of a phonograph at a



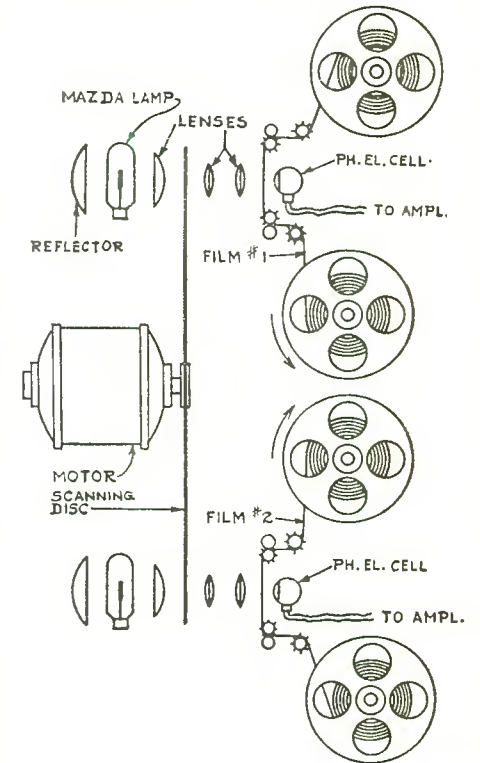eter of the scanning disc and number 2 at the lower. The movement of both films is toward the center of the disc. The films are placed in the same posi-



While picture No. 1 in film No. 1 is being scanned, the blank segment of the disc is passing before film No. 2, shutting off the light. This interval is used to move picture No. 2 in film No. 2 to a stand-still position so that it will be scanned immediately after picture No. 1 of film No. 1 is scanned. So, of the two identical films, the pictures of film No. 1 which will be scanned are Nos. 1-3-5-7-9, etc.; while pictures Nos. 2-4-6-8-10, etc., will be scanned in film No. 2.


Conto's real difficulty came in broadcasting standard sound films taken at a standard rate of 24 picture frames per second without sound distortion and without slowing down the movements of the actors. But he made provision for that, too. He held the opinion that the continuity of the picture would not be broken if part of the pictures in the film were eliminated, for it must be remembered that the movement registered on the two duplicate films is that which takes place in 1/24 of a second, a shorter

(Continued on page 38)

Receiver Performance Curve Section

SERVICE men, dealers and technicians will find on this page our conception of an ideal set of curves. The composite graph may be used to visualize the best possible receiver performance. The more a receiver's curves near parallelism with the ideal, the better the receiver. These curves are not capable of interpretation by a layman. They should be translated only by a service man, dealer, technician or engineer.

Measurements made in our engineering laboratory cover sensitivity, selectivity and electrical fidelity. Standards for these three qualities have been set by the IRE and RMA engineering committees. No standards have yet been adopted for sound pressure measurements. Until a standard is selected, our laboratory will measure only electrical fidelity, which disregards speaker response curves. The fourth measurement appearing with the sensitivity, selectivity and electrical

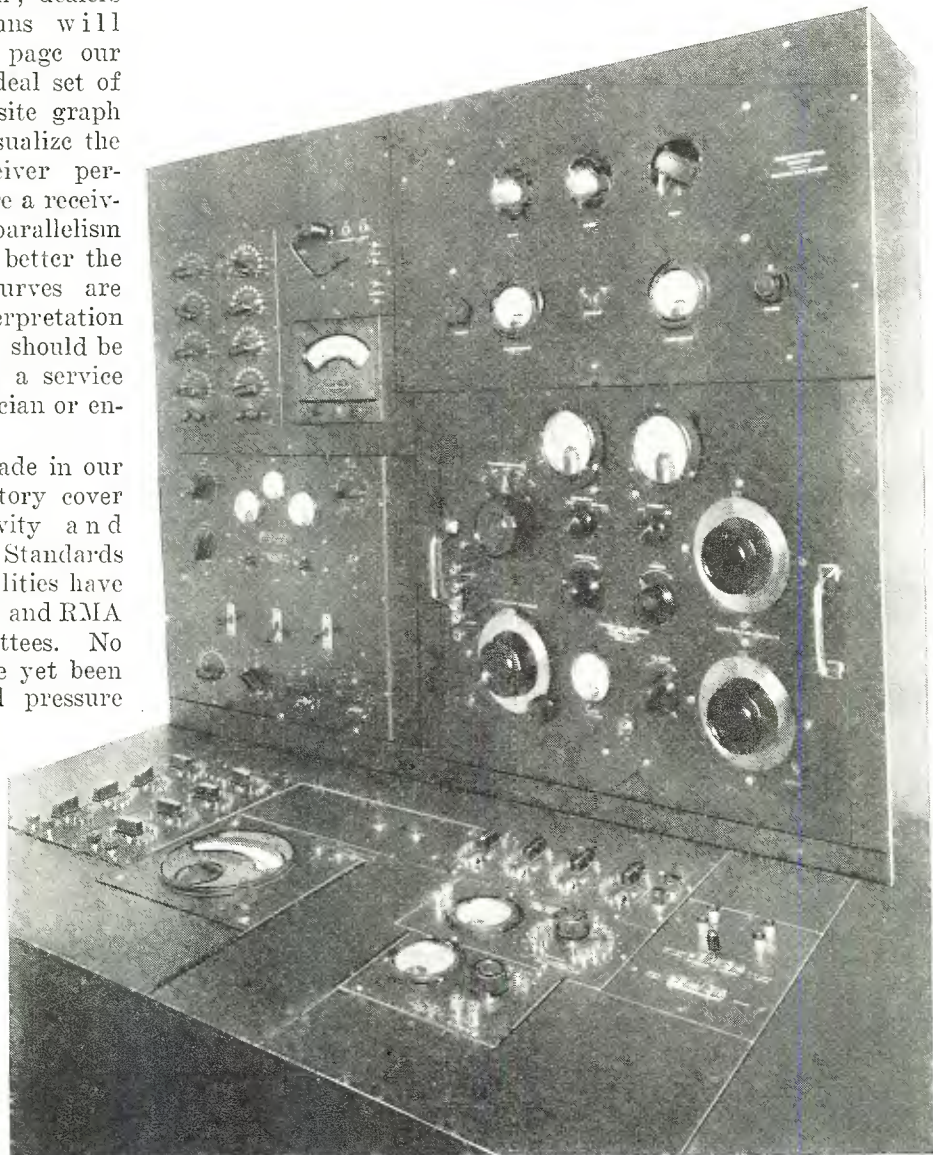


fidelity curves represents power overload curves, or automatic volume control curves, as the case may be.

Definitions of the three major characteristics of a receiver are:

Sensitivity is that characteristic of a receiver which determines to how weak a signal it is capable of responding. It is measured quantitatively in terms of the input voltage required to give standard output. The ideal sensitivity, according to the graph on this page, would fall between the two lines, ranging from 10 to 5 microvolts (absolute) or less. This is an arbitrary value.

Selectivity is the degree to which a receiver is capable of differentiating between the desired signal, and signals of other carrier frequencies. This characteristic is not expressible by a single numerical value, but requires one or more graphs for its expression.

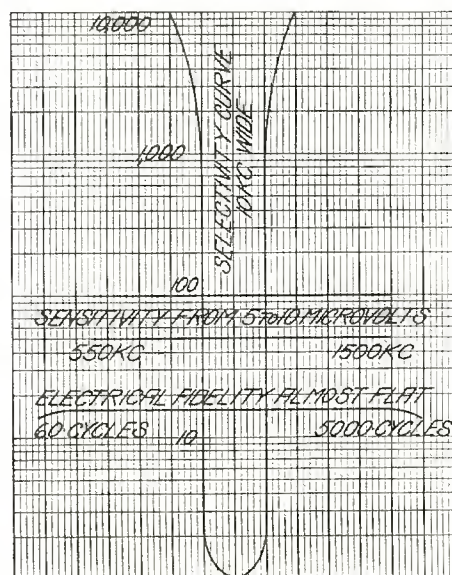Best selectivity possible would be somewhat like a "chimney" whose



Ideal Composite Curve

an arbitrary width.

The photograph illustrates the equipment used in making the measurements. It conforms to the specifications of the IRE and RMA Standardization Committees. All test frequencies are determined by zero beat of a crystal-controlled dynatron oscillator. Voltmeters and microvoltmeters are periodically checked against calibrated standards for accuracy of adjustment. Individual conditions of measurement pertaining to each receiver will be found in the text accompanying each family of curves.

Since curves of all receivers are taken under the same conditions, it may be said that such curves constitute a yardstick by which receivers of the same general class may be compared, as long as this analysis is made by those technically competent to do so.

Crosley Model 127

CROSLEY'S model 127 superheterodyne, when measured in our laboratory, gave the included overall response curves.





Input to the receiver was through the standard dummy antenna of 20 uh, 200 uuf, and 25 ohms, while the output, as measured by the vacuum tube voltmeter, was maintained at a standard level of .05 watts, except for the automatic volume control curve.

drawn by this receiver, with a line voltage of 116 volts. For all tests the volume control was turned for maximum receiver sensitivity, the tubes as furnished by the manufacturer with the receiver were employed, and factory adjustment of trimmers was left undisturbed.

An average sensitivity of 8.8 microvolts was taken from the sensitivity curve of column 1. This is equiva-

lents to the maximum input, i. e., 10,000 microvolts. No consideration is made of the harmonic distortion present in the wave form across the primary of the speaker transformer. Under the selectivity curves of column 3 will be found the band widths taken from them.

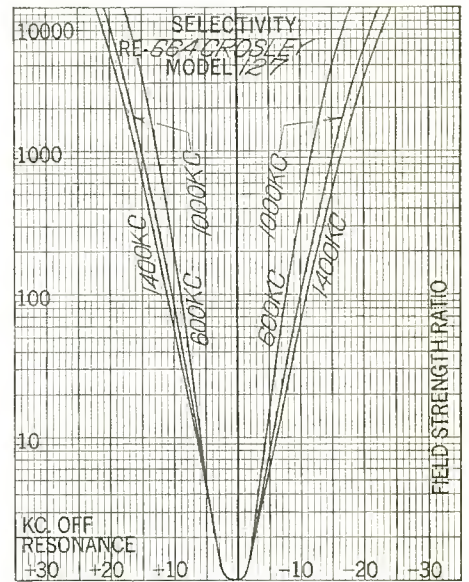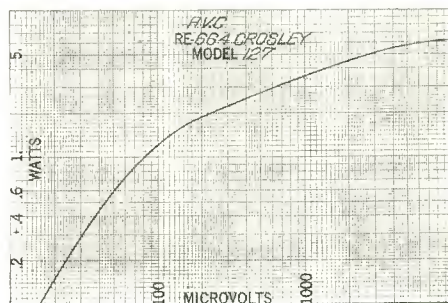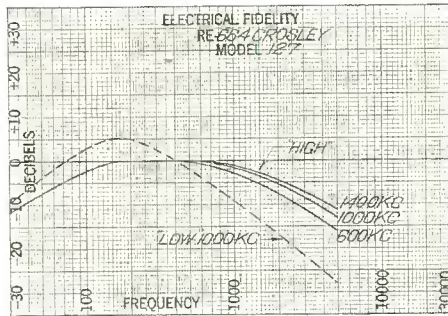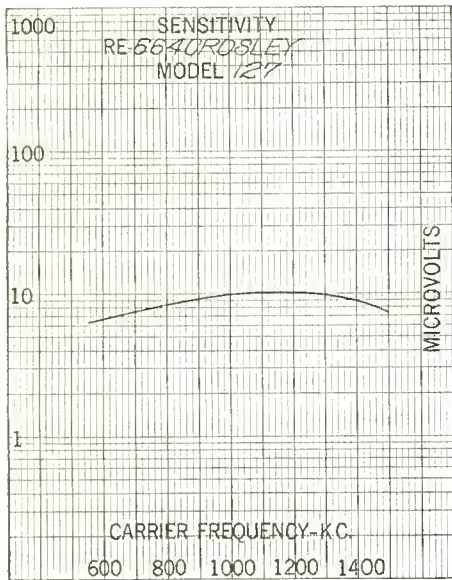A schematic wiring diagram of the model 127 will be found at the bottom of the page. Required tubes are



To match the optimum operating impedance of the push-pull 247 pentodes employed in the last audio stage, a non-inductive load resistance of 14,000 ohms was connected between the plates, and the voice coil circuit was opened to prevent any reflected impedance of the secondary to the primary circuit. The output plates were capacitatively coupled to the output indicating device.


A line current of 1.09 amperes was

lent to 2.2 microvolts per meter when a standard four-meter height antenna is used. A minimum noise level of 4.7 per cent was recorded at 1200 kc and a maximum of 22.1 at 1400 kc. At 1000 kc the measured image ratio was 66,800. In column 2, from the automatic volume control curve, a maximum of 6.2 watts power output

a 235 r-f, 235 first detector, 227 oscilator, 235 second i-f, 235 third i-f, 227 diode detector, 227 a-f, push-pull 247 pentodes, and a 280 rectifier.

Band Widths

Times Field Strength	Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	10	11.5	12.5
100	16.5	20.5	22
1000	24.5	30.5	32.5
10000	35.5	43	46

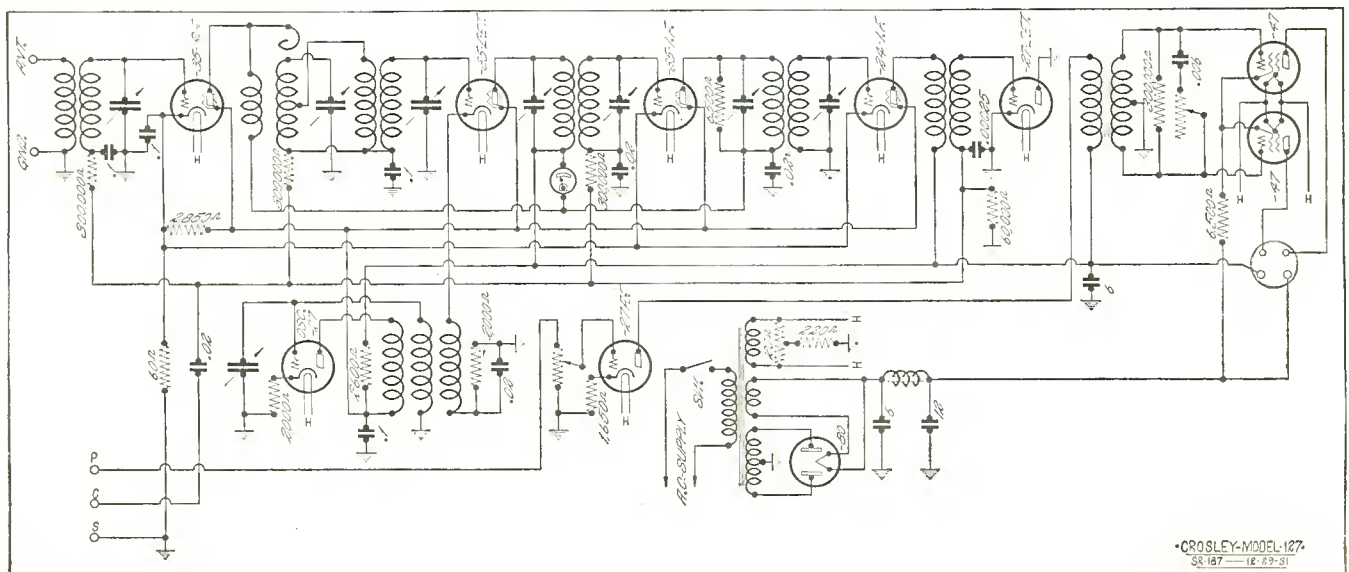

CROSLEY-MODEL-127
SR-187 12-23-31

General Electric Model K-62





CURVES on the performance of the General Electric model K-62 superheterodyne receiver plotted from recent measurements in our laboratory are included on this page.

A dummy antenna standard of 20 uh, 200 uuf and 25 ohms was used to couple the output of the signal gen-

justment, the volume control was set for maximum receiver sensitivity, and the tubes employed in the chassis were furnished with it as standard equipment. With an a-e line voltage of 115 volts, the line drain was .95 amperes.

In column 1 is the sensitivity curve, which gives an average sensitivity value of 7.35 microvolts absolute,

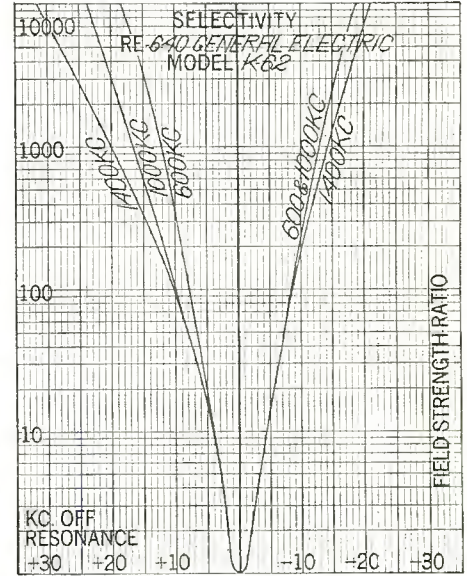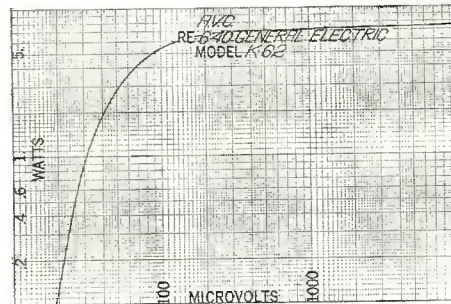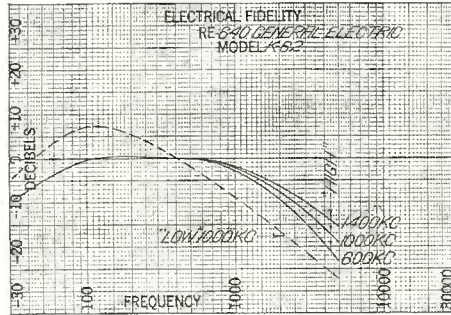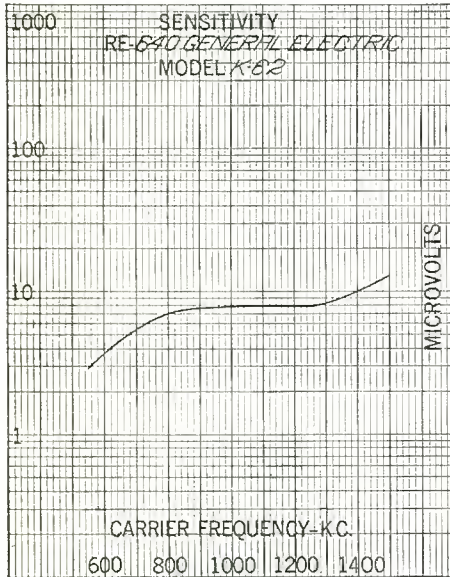ume control curve in column 2, but this figure does not take into account the distortion entered by the harmonics present in the output wave across the primary of the output transformer. From the selectivity curves of column 3 the band widths were taken and they will be found tabulated below the curves.




erator to the input circuit of the chassis. A resistance of 15,000 ohms was coupled across the push-pull pentode plates for optimum plate load, while the voice coil circuit was opened to eliminate the reflected impedance influence on the primary of the output transformer. Output plates were capacitatively coupled to the output tube volt meter, which indicated a standard level of .05 watts in all measurements but the automatic volume control test.

No changes were made in the alignment of the receiver from factory ad-

justment, the volume control was set for maximum receiver sensitivity, and the tubes employed in the chassis were furnished with it as standard equipment. With an a-e line voltage of 115 volts, the line drain was .95 amperes. In column 1 is the sensitivity curve, which gives an average sensitivity value of 7.35 microvolts absolute, which is equivalent to 1.84 microvolts per meter, when the standard four-meter antenna is used. Measured noise levels were 1.4 per cent at 600 k-c and 1.8 per cent at 1400 k-c, the maximum and minimum values respectively. The image ratio measured with the receiver tuned to 1000 k-c was 1450 times against the undesired signal impressed at 1350 k-c. Power output reached a maximum of 7.52 watts at an input of 10,000 microvolts, as seen from the automatic vol-

A schematic wiring diagram of the model K-62 superheterodyne will be found below. The tubes required are a 235 r-f, 227 oscillator, 224 first detector, 235 second i-f, 227 automatic volume control, 227 second detector, 247 push-pull pentodes, and a 280 rectifier. It will be noted that the filter is used on the negative side of the rectifier.

Times Field Strength	Band Widths Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	9	9	9
100	16.5	18.5	19
1000	25.5	29.5	34.5
10000	37	42.5	52

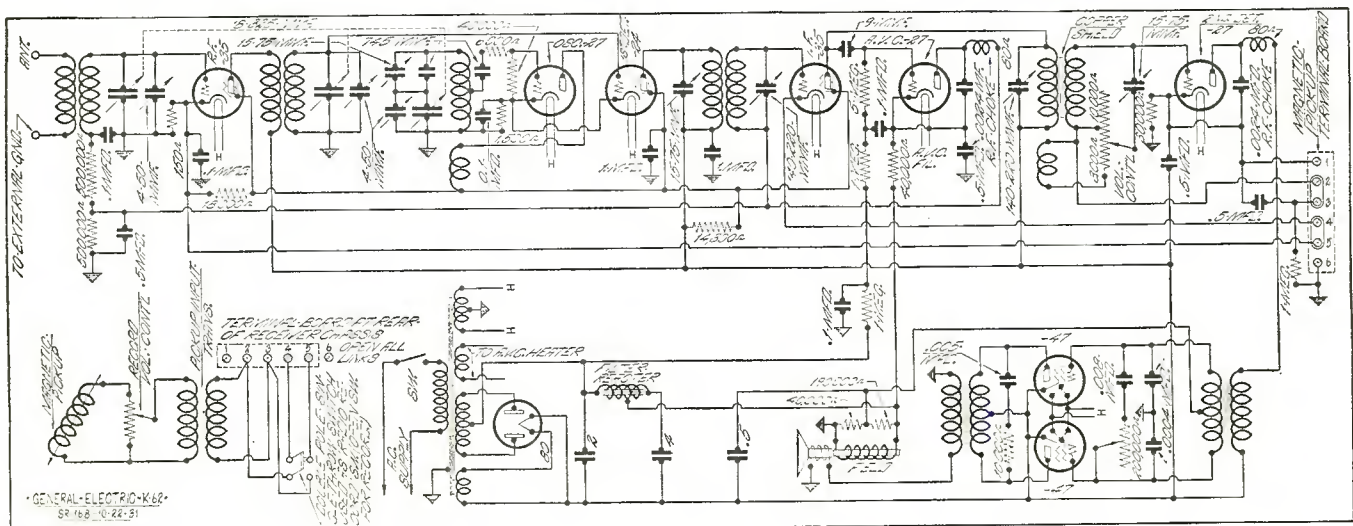

Gulbransen Model 23

ON measurement in our laboratory recently the Gulbransen model 23 superheterodyne produced the included overall performance curves.





Signal generator output was coupled through the standard dummy

sensitivity, the tubes as furnished by the manufacturer were employed in the chassis, and no changes were made in the alignment of tuned circuits from factory adjustment.

From the sensitivity curve of column 1, the average is found to be 1.9

put voltage wave form across the primary of the speaker transformer. Under the selectivity curves of column 3 will be found the tabulated band widths from which they were taken.

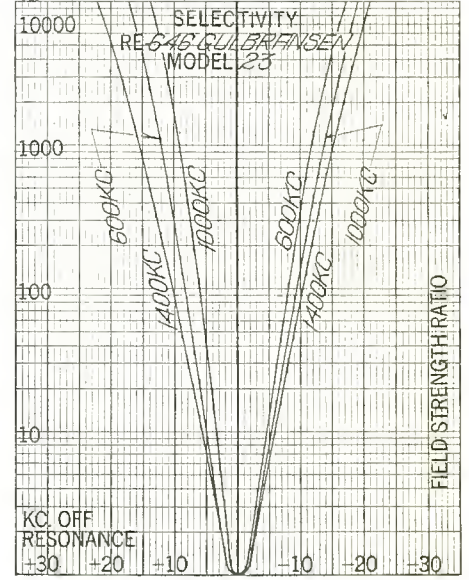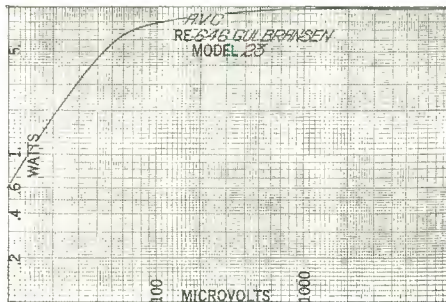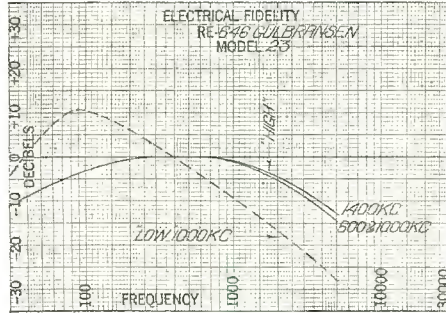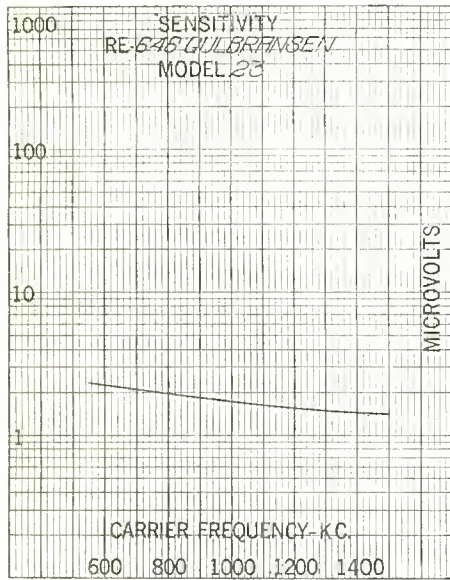Below is a schematic wiring diagram of the receiver. Required tubes



antenna of 20 uh, 200 nuf and 25 ohms to the receiver antenna circuit. A standard output of .05 watts was maintained for all measurements but automatic volume control, and was indicated on the vacuum tube voltmeter coupled capacitatively to the output plates of the push-pull 247 tubes. A non-inductive load resistance of 14,000 ohms was used to match the operating impedance of these tubes. The voice coil circuit was opened to prevent a reflection of undesirable impedance to the primary circuit during measurements.


A line voltage of 112 volts gave the receiver a drain of 1.11 amperes. For all measurements the volume control was adjusted for maximum receiver

microvolts absolute, which value corresponds to .475 microvolts per meter, using a standard four-meter height antenna. Maximum noise level was measured at 1000 ke and had a value of 69 per cent, while the minimum value occurred at 1200 ke and 1400 ke, with a value of 57 per cent. An image ratio of 18.900 was measured on this receiver with the dial adjusted to 1000 ke. From the automatic volume control curve of column 2, the maximum audio output is found to be 10 watts for the highest input value taken, but no consideration was made of the harmonics present in the out-

for operation consist of a 235 r-f, 235 first detector, 235 second i-f, 235 third i-f, 227 diode second detector, 227 audio, push-pull 247 pentodes, 227 oscillator, and a 280 full wave rectifier. It will be noted from the diagram that a resonance indicating meter is used for convenience in tuning the receiver, since there is an apparent broadness in the automatic volume control feature.

Band Widths

Times Field Strength	Kilocycles width		
	600 ke.	1000 ke.	1400 ke.
10	9.5	9	11.5
100	16.5	15.5	21
1000	24	23	31
10000	34	33	43

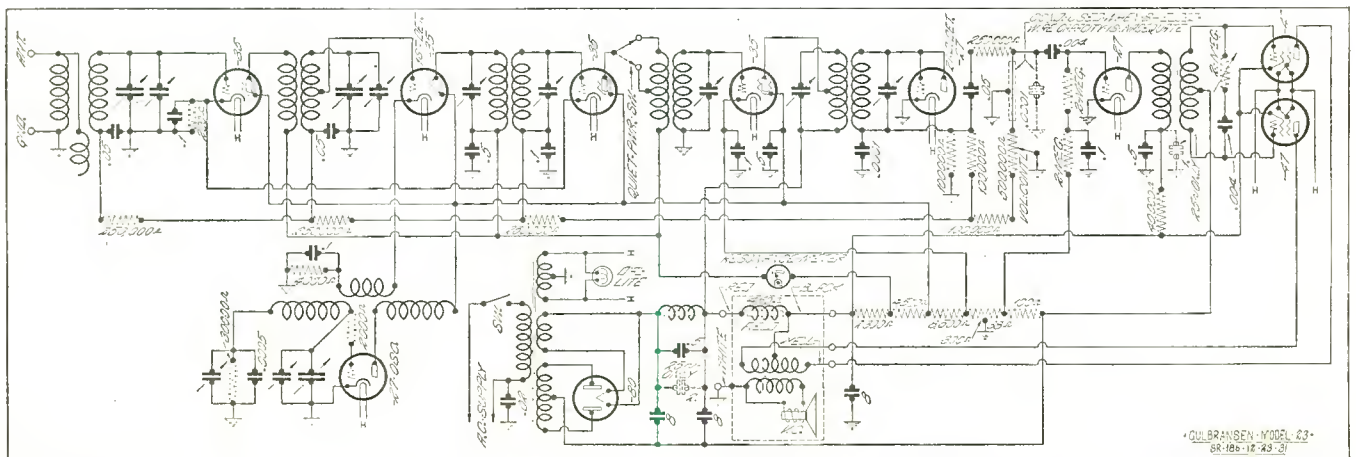

Howard Model AVH





UPON measurement in our laboratory, the Howard model AVH produced the overall performance curves given on this page. Signal generator output was coupled to the receiver input circuit

the tubes as furnished by the manufacturer were employed. The receiver line drain was 1.23 amperes, with a line voltage of 115 volts.

An average sensitivity of 5.60 microvolts absolute was measured, which is the equivalent of 1.40 micro-

present in the output wave form. In column 3 under the selectivity curves are the tabulated band widths.

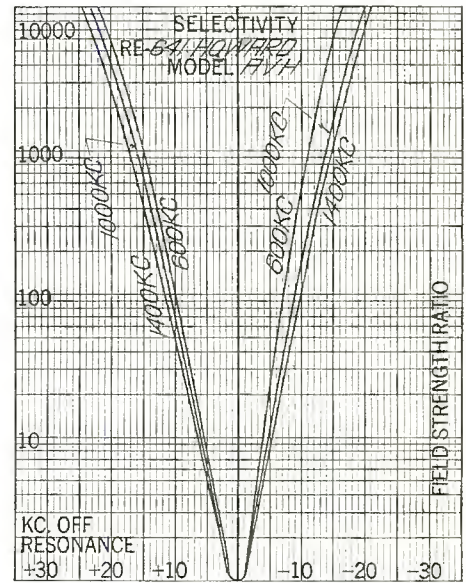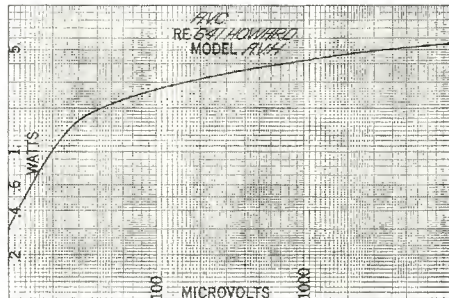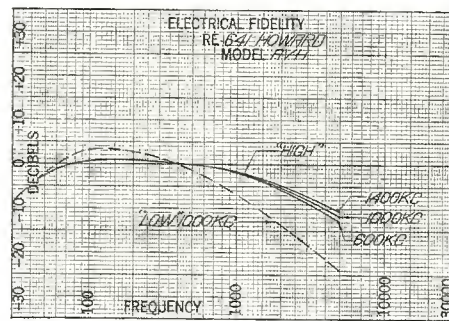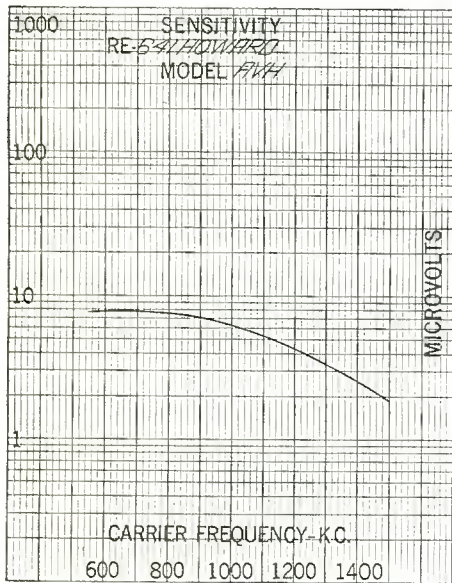At the bottom of the page is the schematic wiring diagram of the model AVH. Tubes required are a 551 r-f, 227 oscillator, 551 first de-




by means of the standard dummy antenna of 20 uh, 200 uuf and 25 ohms, while the output was maintained at a level of .05 watts. The operating impedance of the push-pull 247 tubes was matched with a 14,000 ohm non-inductive load resistance and the plates were capacitatively coupled to the output measuring tube voltmeter. To prevent any reflection of impedance on the primary circuit, the voice coil was opened during all measurements. For all tests the volume control was turned to maximum sensitivity, the alignment of tuned circuits was not varied from factory adjustment, and

volts per meter, using a four-meter antenna. Computed noise levels, maximum and minimum values, were 13.8 per cent at 1400 kc and 5.1 per cent at 600 kc respectively. At 1000 kc the image ratio was measured as 1110 times. At 10,000 microvolts input the maximum measured power output occurred as seen from the automatic volume control curve of column 2, and shows a value of 5.60 watts. This figure does not take into account the produced harmonics

tector, 551 second i-f, 227 automatic volume control tube, 227 second detector, 247 push-pull pentodes, and a 280 rectifier. Oscillator energy is coupled to the secondary coil of the second r-f transformer by means of a pick-up coil. It will be noted that a meter is used for correct resonance indication in timing.

Times Field Strength	Band Widths		
	Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	9.5	10.5	11.5
100	17.5	20.5	21.5
1000	26	30	31.5
10000	38.5	42	45.5

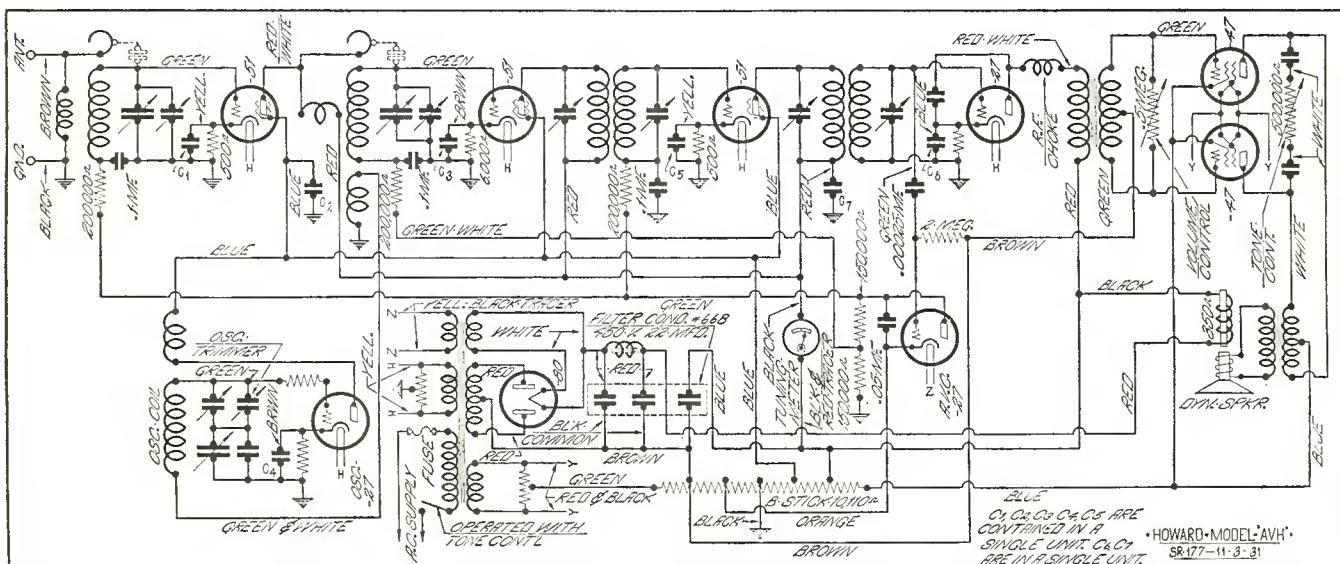

Kennedy Model 56

MEASUREMENTS of the Kennedy model 56 made recently in our laboratory gave the included overall performance curves.





For signal input the standard generator was coupled to the receiver an-

teina circuit by means of a dummy antenna of 20 uh, 200 muf and 25 ohms. Output voltage equivalent to .05 watts of audio power was measured by the vacuum tube voltmeter, capacitatively coupled to the 247 pentodes. The plate load was adjusted to 14,000 ohms to match the optimum operating plate impedance. For all tests the voice coil circuit of the speaker was opened to eliminate any undesirable impedance reflection on the primary side. With a line voltage of 117 volts, the power transformer primary drain was .82 amperes. For all measurements, no changes were made in the factory alignment of the re-

ceiver, the tubes furnished with the receiver as standard equipment were used, and the volume control was turned on full. From the sensitivity curve of column 1, the average sensitivity is taken as 6.32 microvolts absolute,

column 3, from which they were taken.

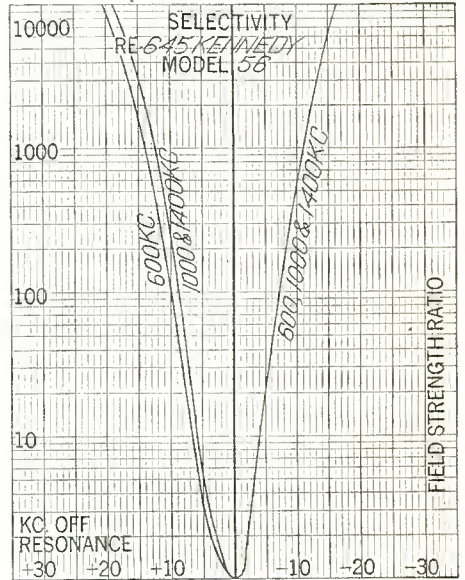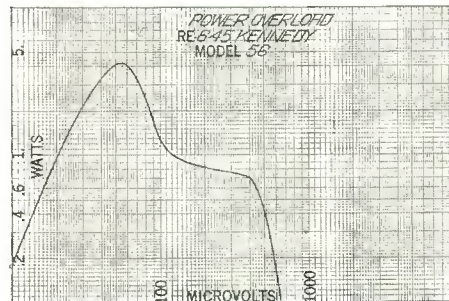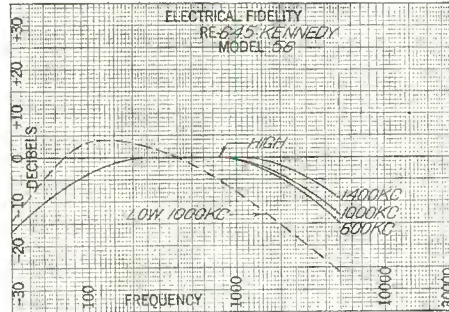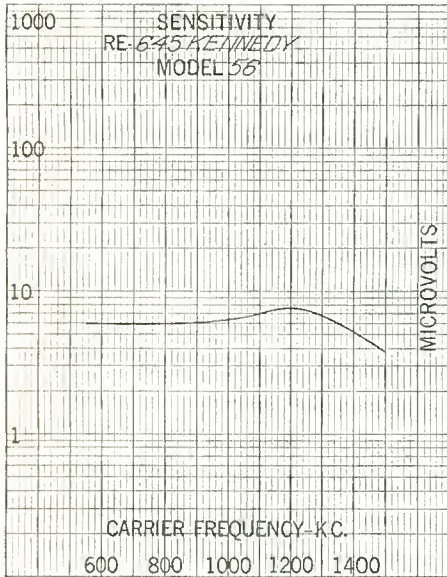Below is a schematic wiring diagram of the model 56 Kennedy superheterodyne. Required tubes are a 551 r-f, 224 first detector, 227 oscillator, 551 second i-f, 227 second de-




which corresponds to 1.58 microvolts per meter, with a standard height antenna. Noise level values were 4 per cent at 600 ke, the minimum, and 53 per cent at 1400 ke, the maximum. An image ratio of 3760 was measured at 1000 kc. From the power overload curve of column 2 a maximum power output of 4.14 watts is found, but this figure disregards the harmonics produced in the wave form across the output transformer primary at this power level. Band widths are tabulated under the selectivity curves of

detector, two 247s in push-pull output, and a 280 full wave rectifier for all B supply voltages. An 8 mfd and 12 mfd condenser are used on each side of the speaker field for hum filtration. Bias for the 247 pentodes is obtained by the drop across a 250 ohm resistor connected from the mid point of the filament winding to ground.

Band Widths

Times Field Strength	Kilocycles width		
	600 ke.	1000 ke.	1400 ke.
10	10.5	10	10
100	17.5	16.5	16.5
1000	25	24	24
10000	36.5	35	35

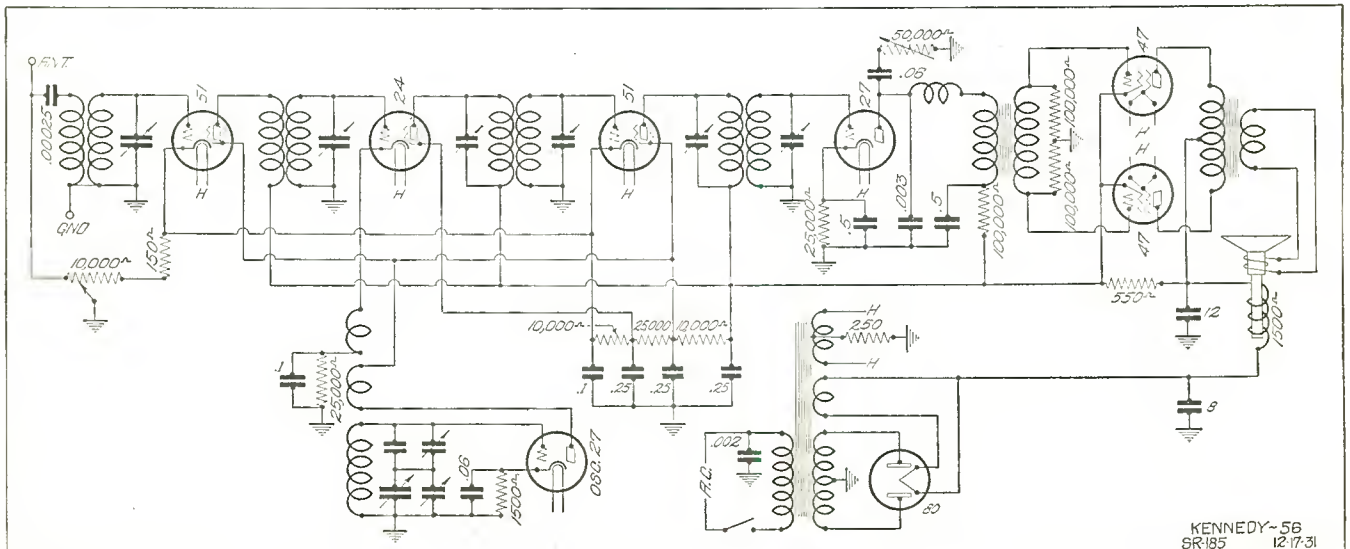

KENNEDY-56
SR-185 12-17-31

Spartan Model 15

SPARTON'S model 15, when measured in our laboratory gave the included curves as indicative of its performance.





A dummy antenna standard of 20 uh, 200 uuf and 25 ohms coupled the

trol was turned on full, and no adjustments were made in the alignment of tuned circuits.

An average of 6.72 microvolts absolute is found from the sensitivity curve of column 1. This value cor-

be 2.56 watts, which value does not take into consideration the harmonic content of the output. Band widths will be found tabulated under the selectivity curves of column 3.

A schematic wiring diagram is

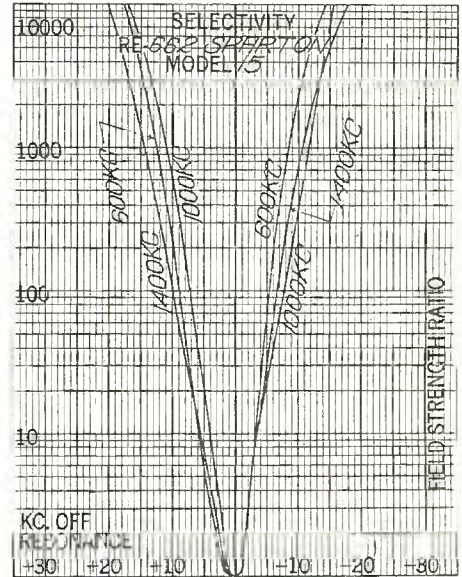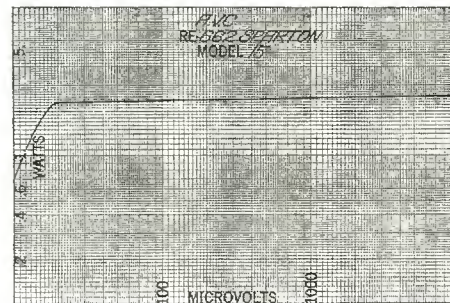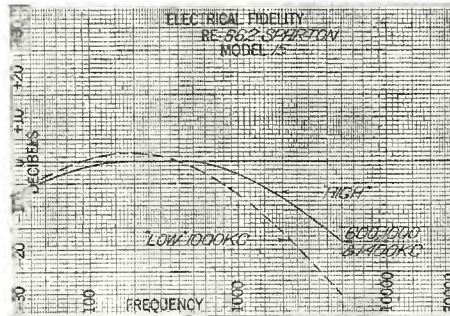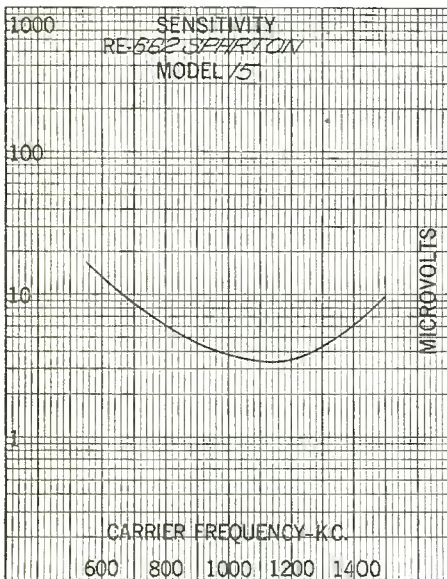


output of the signal generator to the receiver input circuit. A load resistance of 7000 ohms matched the operating impedance of the 247 pentode, which had its plate capacitively coupled to the output indicating device. The voice coil was opened during all measurements.

A line voltage of 116 volts resulted in a current drain of .71 amperes. For all tests, the tubes furnished with the chassis were used, the volume con-

responds to 1.68 microvolts per meter. Maximum noise level occurred at 1000 kc, 1200 kc, and 1400 kc, with a value of 9 per cent, and the minimum of .7 per cent was found at 600 kc. The measured image ratio was 82,000 at a dial setting of 1000 kc. From the automatic volume control curve of column 2, maximum output is found to

shown below, and the required tubes are a 435 r-f, 435 first detector, 427 oscillator, 435 second i-f, 427 automatic volume control tube, 427 second detector, 447 pentode, and a 480 rectifier.

Times Field Strength	Band Widths		
	Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	9	7.5	9
100	14.5	13.5	16.5
1000	21	23	25
10000	32	32.5	37.5

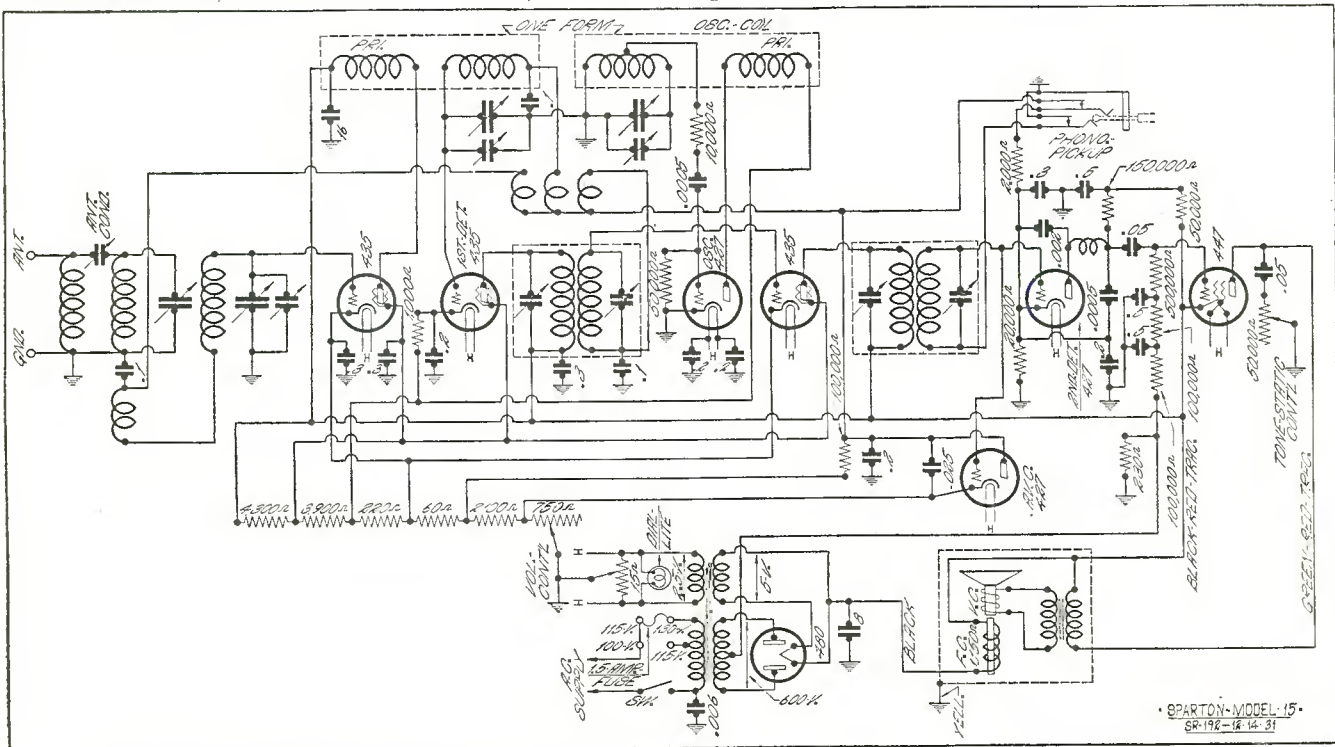

SPARTON-MODEL 15
SR-192-14-31

Stewart Warner Model R-102A

PERFORMANCE curves on the Stewart-Warner R-102A recently made in our laboratory are given on this page.





Receiver input from the standard signal generator was through the standard dummy antenna of 20 uh, 200 uuf, and 25 ohms. To match the

most sensitive position, and the tubes employed were those furnished with the chassis by the manufacturer as standard equipment.

From the sensitivity curve of column 1 the average sensitivity is taken as 4.4 microvolts absolute, which corresponds to 1.1 microvolts per meter

be found under the selectivity curves, from which they were taken, in column 3.

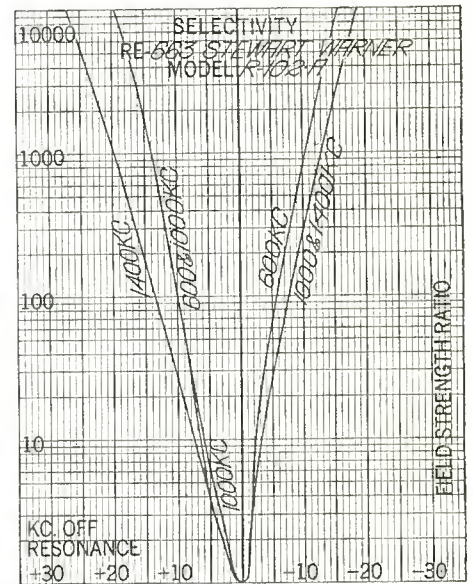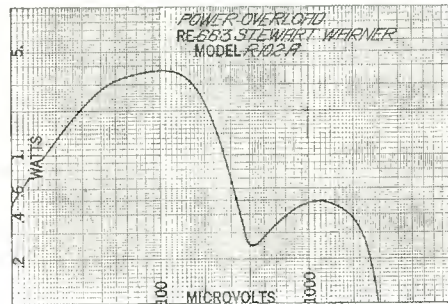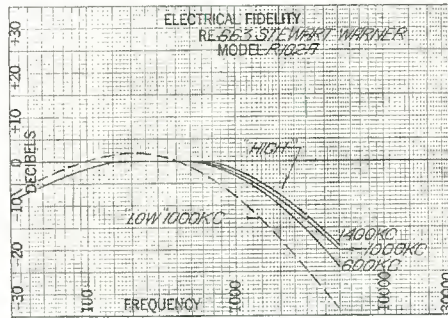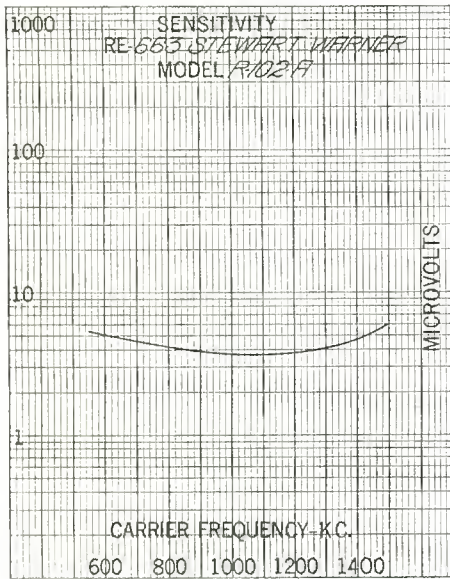At the bottom of the page is a schematic wiring diagram, from which the required tubes are found to be a 224 first detector, 235 second i-f, 224 second detector, 227 oscillator, 247




operating output impedance of the single 247 pentode, a non-inductive load resistance of 7000 ohms was connected across the plate circuit, which in turn was capacitatively coupled to the output indicating voltmeter. A standard level of .05 watts was maintained for all measurements except that of power overload. The voice coil circuit was opened to prevent any impedance error caused by a reflection from the secondary to the primary circuit.

A line voltage of 117 volts gave the receiver a drain of .93 amperes. For all tests no alterations were made in the factory alignment of tuned circuits, the receiver was adjusted to its

when a four-meter antenna is used. At 1000 kc, 1200 kc and 1400 kc the maximum noise level of 22 per cent was measured, and the minimum of 17.6 per cent was found at 600 kc. An image ratio of 3:350 was measured with the receiver tuned to 1000 kc. In column 2 will be found the power overload curve, which gives a maximum audio output of 3.73 watts. However, this figure does not take into consideration the harmonics contained in the wave across the primary of the output transformer at this audio level. Tabulated band widths will

power pentode, and a 280 full wave rectifier for complete receiver B supply. The speaker field is tapped to provide grid bias for the output pentode. Tone control consists of a .05 mfd fixed condenser from the plate of the pentode to ground through a variable resistance of 60,000 ohms. The change in the filter circuit from 60 cycle to 25 cycle operation is noted in dotted lines.

Times Field Strength	Band Widths		
	Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	8.5	9	11
100	15.5	18	21.5
1000	24.5	27	33
10000	35	38	45.5

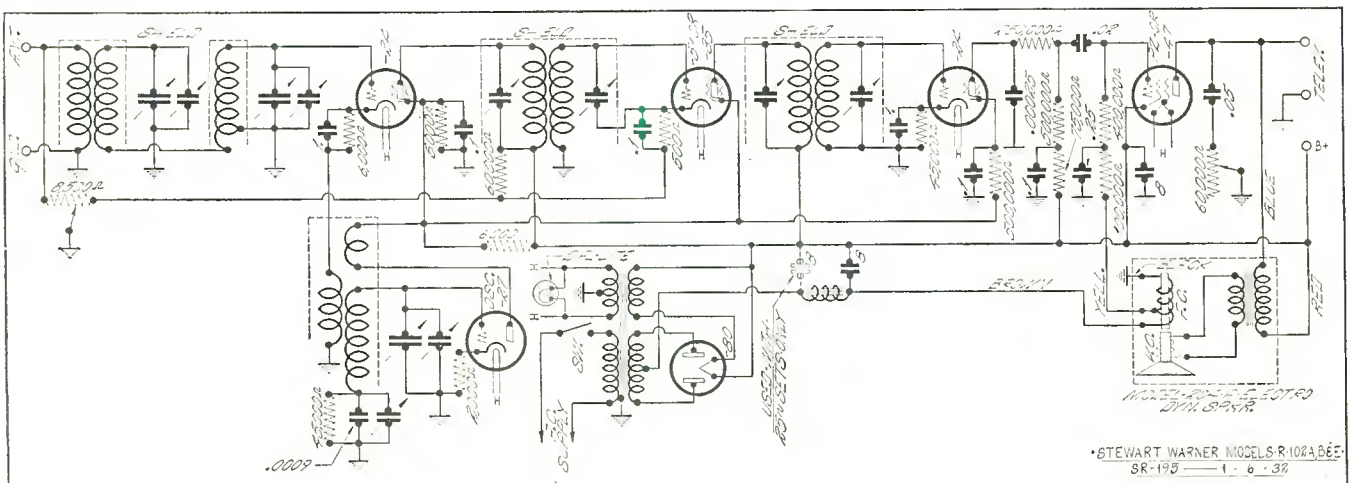

United American Bosch Model 31

UNITED American Bosch models 31 and 32 gave the included performance curves after measurement in our laboratory recently.





A dummy antenna standard of 20 ohms, 200 uuf, and 25 ohms coupled the output of the standard signal generator to the receiver input circuit. To match the operating impedance of the single 247 pentode employed in

voice coil circuit was broken. In all measurements, no changes were made in factory alignment of tuned circuits, the volume control was turned to its maximum position, and the tubes furnished with the receiver as standard equipment were used. An a-c line drain of .64 amperes was recorded, with a line voltage of 117 volts.

An average sensitivity of 12 microvolts absolute corresponding to 3 mi-

gives a maximum output of 2.88 watts of audio power, but this figure does not take into consideration any produced harmonics. At 1000 kc the image ratio was measured as 2510. Below the selectivity curves of column 3 are the band widths taken from them.

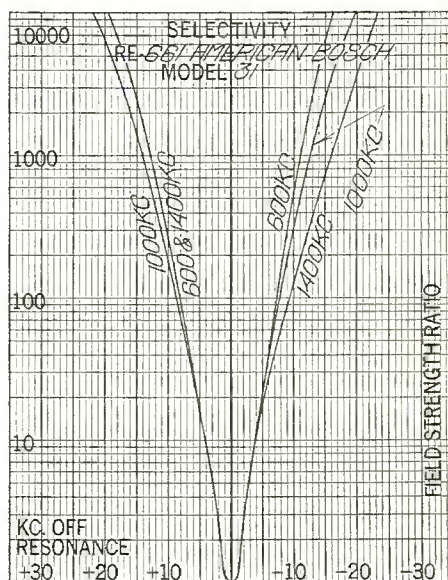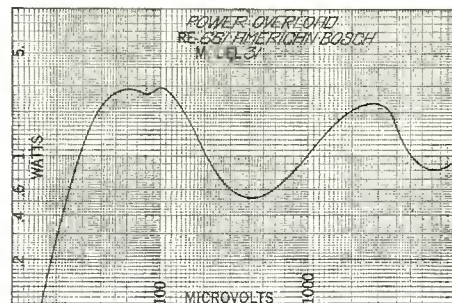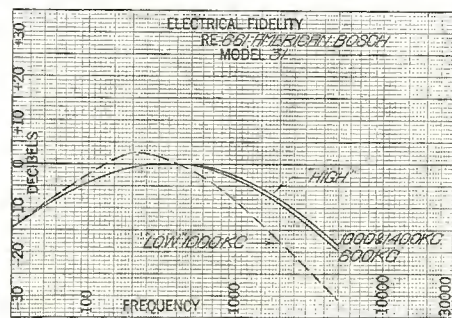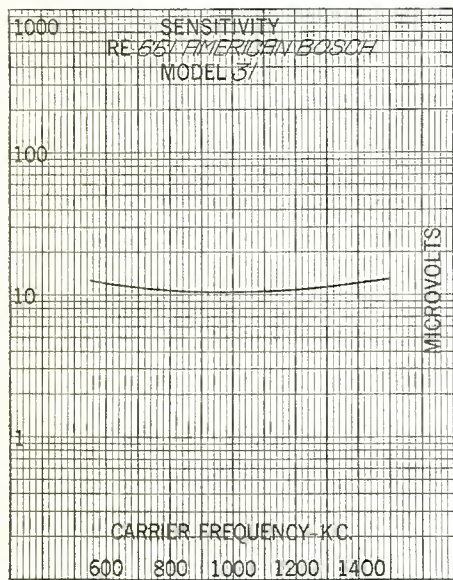At the bottom of the page is a schematic wiring diagram of the model 31 superheterodyne. Required




this superheterodyne, a non-inductive load resistance of 7000 ohms was connected across the plate circuit, which in turn was capacitatively coupled to the output measuring tube voltmeter used to indicate the standard audio output of .05 watts, except for the power overload curve. To eliminate any impedance reflection from the secondary to the primary circuit, the

crovolts per meter with a standard height antenna is taken from the sensitivity curve of column 1. Maximum noise level of 19.4 per cent was measured at 1400 kc, while the minimum of 16 per cent occurred at 1200 kc. In column 2, the power overload curve

tubes for operation are a 551 first detector, 227 oscillator, 551 second i-f, 224 second detector, 247 pentode, and a 280 full wave rectifier.

Band Widths

Times Field Strength	Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	8	8	8
100	15.5	16.5	17.5
1000	23.5	26.5	29
10000	35.5	41	42.5

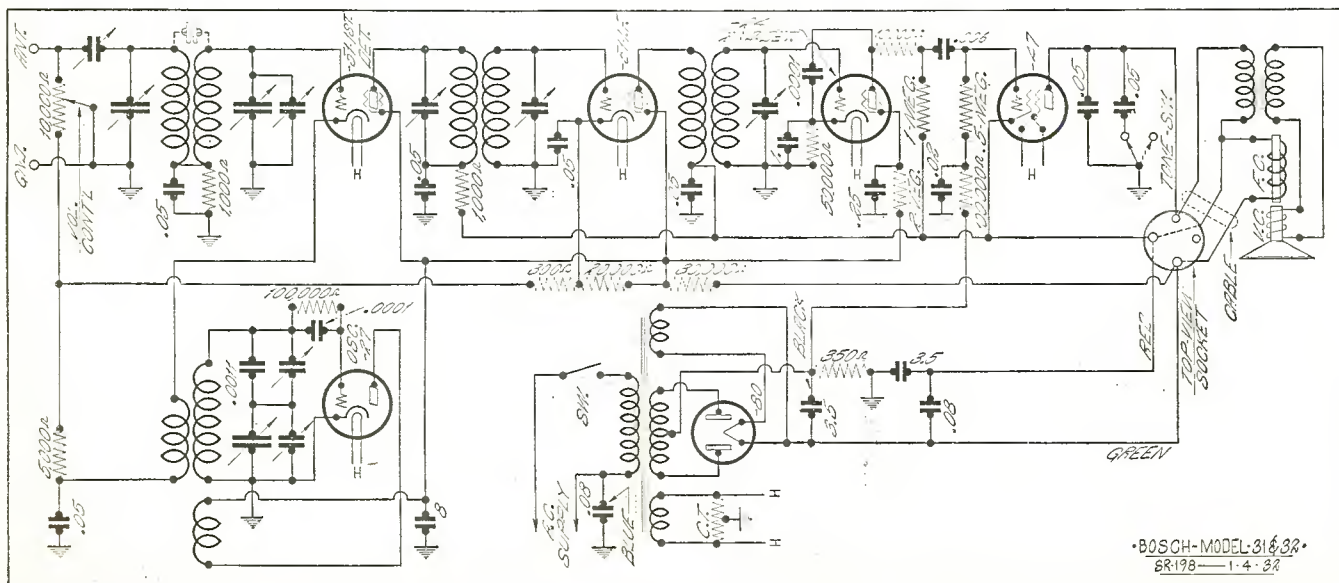

U. S. Radio, Apex Model 10B





U. S. RADIO & TELEVISION CORPORATION'S Apex model 10-B gave the included overall performance curves when measured in our laboratory.

For signal input to the antenna circuit of this superheterodyne the

transformer with an a-c voltage of 116. Tubes employed in the receiver were those furnished with it as standard equipment, the volume control was turned on full, and no adjustments were made on the tuned circuits during measurements. Average

However, this figure does not take into consideration harmonic distortion introduced into the wave form at this high level. Below the selectivity curves in column 3 are the tabulated band widths taken from them.

At the bottom of the page is a

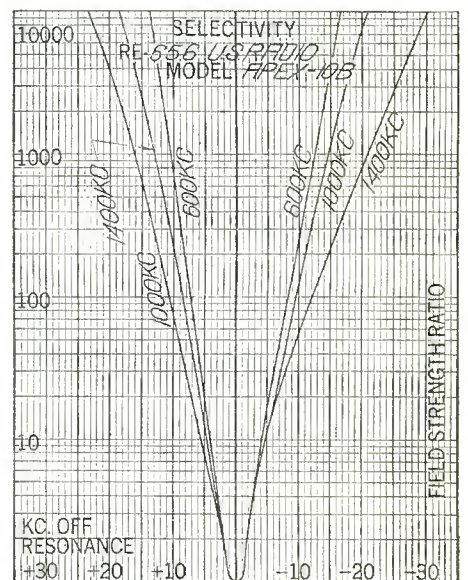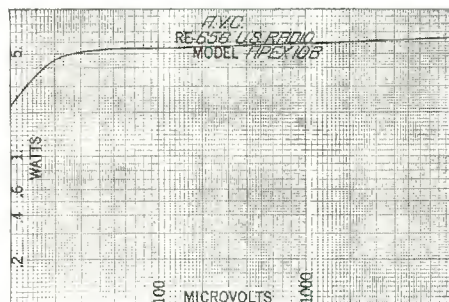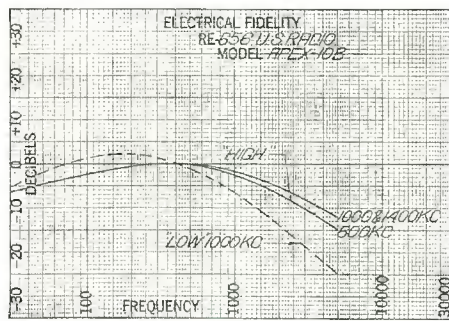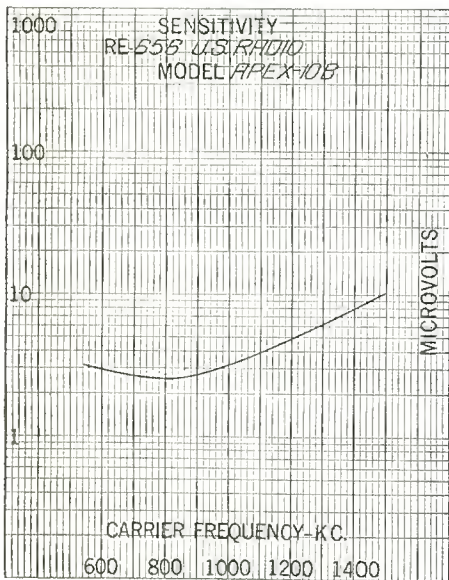


standard signal generator was coupled through a dummy antenna standard of 20 uh, 200 uuf and 25 ohms. A non-inductive load resistance of 14,000 ohms was connected across the plates of the push-pull 247 pentodes to match their optimum operating impedance. The plates were capacitatively coupled to the vacuum tube voltmeter, which indicated the standard audio output level of .05 watts. To prevent any reflection of undesired impedance on the measured circuit, the voice coil was disconnected during all tests.

A line current of .95 amperes was drawn by the primary of the power

sensitivity is computed to be 4.4 microvolts absolute, from the sensitivity curve in column 1. This corresponds to a value of 1.1 microvolts per meter when a standard height antenna is employed. Noise levels, maximum and minimum values, are 37.2 per cent at 800 kc and 9.3 per cent at 1400 kc respectively. At 1000 kc the measured image ratio was greater than 50,000 times. Power output reached a maximum of 6.25 watts at the greatest input used, i. e., 10,000 microvolts.

schematic wiring diagram of the model 10-B. From it the tubes required are found to be a 235 r-f, 235 first detector, 235 second i-f, 227 second detector, 227 oscillator, 227 automatic volume control, 227 audio, push-pull 247 pentodes, and a 280 rectifier. In this receiver a meter is used for resonance indications.

Times Field Strength	Band Widths		
	Kilocycles width		
	600 ke.	1000 ke.	1400 ke.
10	8	9.5	10
100	15.5	18.5	22.5
11000	23	26.5	37
10000	30	39	53

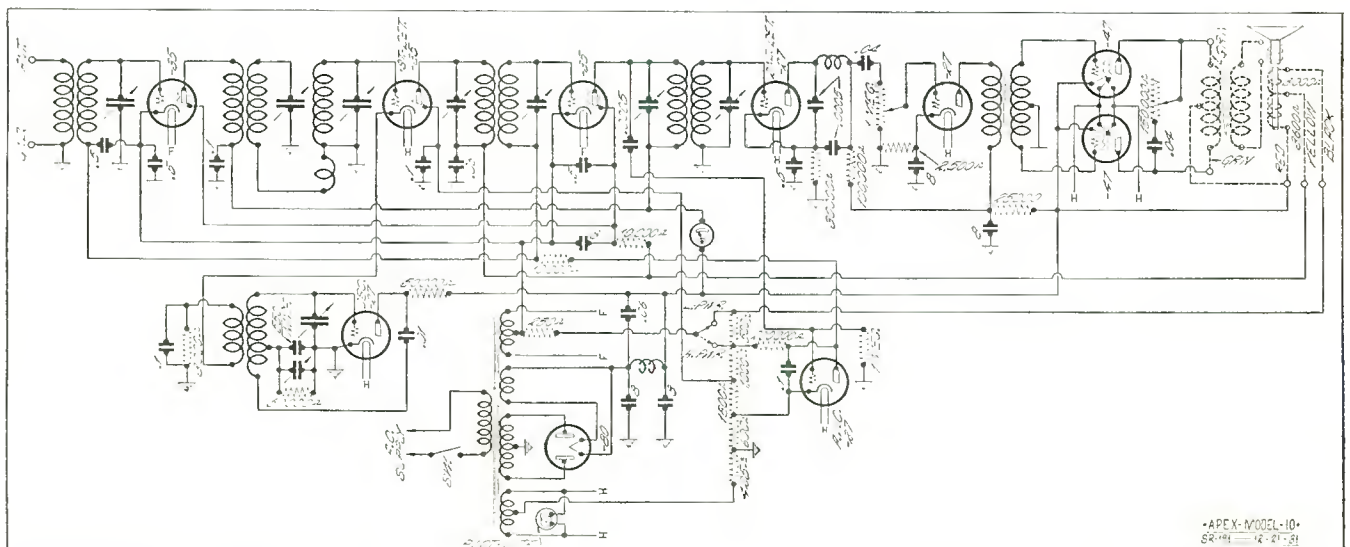

Zenith Models 91, 92

CURVES of the Zenith models 91 and 92 appearing on this page were made from our recent laboratory measurements.





Input to the receiver antenna circuit from the standard signal generator was through the dummy an-

tenna standard of 20 uh, 200 nuf and 25 ohms, while the output was maintained at .05 watts, except for the automatic volume control curve.

On the alignment of the tuned circuits. Average sensitivity as taken from the curve of column 1 is computed to be 4.8 microvolts absolute or 1.2 microvolts per meter, using the standard height antenna. Maximum noise level of 61 per cent occurred at

which they were measured.

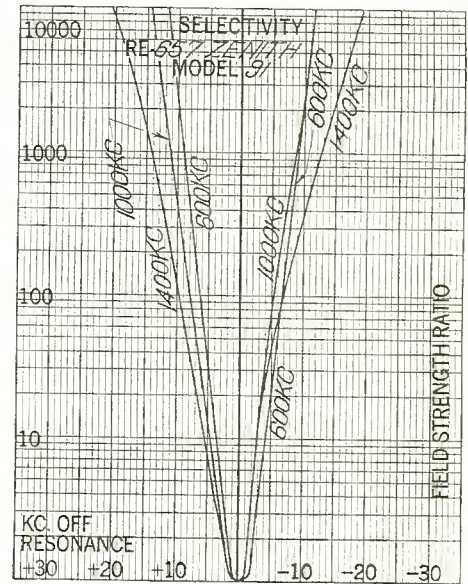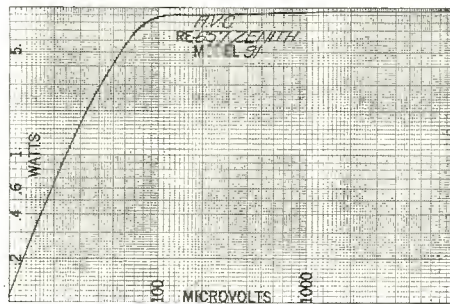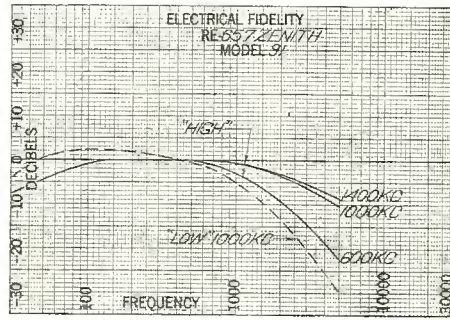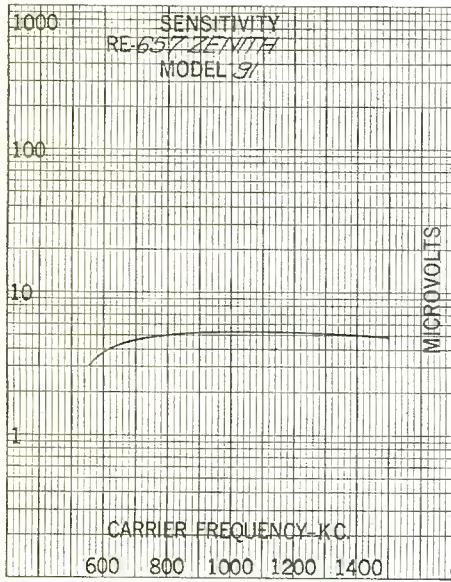A schematic wiring diagram of the Zenith superheterodynes is given below. Tubes required for operation of the receivers are a 551 r-f, 551 first detector, 227 oscillator, 551 second if-, 227 second detector, 224 automatic



tenna standard of 20 uh, 200 nuf and 25 ohms, while the output was maintained at .05 watts, except for the automatic volume control curve. The vacuum tube voltmeter in the output circuit was capacitatively coupled to the plates of the 245 push-pull output tubes, the impedance of which was matched by a non-inductive load resistance of 7800 ohms.


With a line voltage of 116 volts, the receiver current drain was 1.16 amperes. During all measurements the volume control was at maximum, the tubes as furnished by the manufacturer were employed in the receiver, and no adjustments were made

600 kc, while the minimum of 6.24 per cent was measured at 1400 kc. From the automatic volume control curve of column 2 the maximum power output is seen to be 9.46 watts at the point of greatest signal input taken. This figure does not take into consideration the harmonic content of the wave impressed across the primary of the output transformer. At 1000 kc dial setting the image ratio measured 11,900 times. In column 3 are the band widths given in tabular form under the selectivity curves, from

volume control tube, 227 audio, push-pull 245 tubes, and a 280 full wave rectifier. From the diagram it is seen that the first section of the filter employs a tuned unit, while the speaker field makes up the second. Both choke units are in the B return lead and serve to give the proper voltage drop from ground to -B.

Band Widths

Times Field Strength	Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	7.5	7.5	8
100	13	13	16.5
1000	18	20	27
10000	23	26	39.5

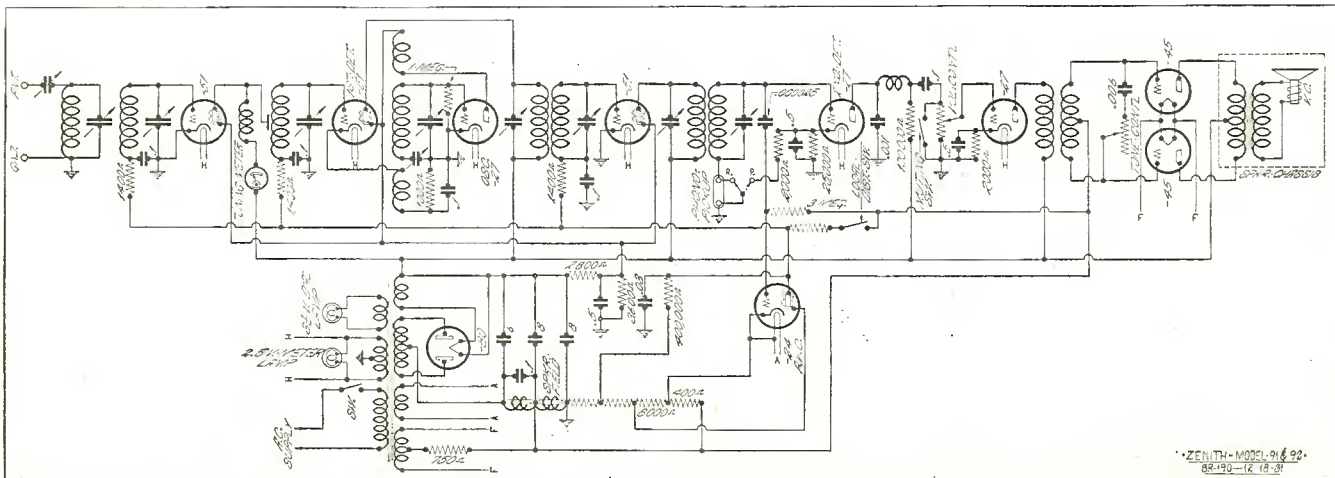

Service and Repair



SCHEMATICS PUBLISHED TO DATE

<i>Model</i>	<i>Published</i>	<i>Drawing No.</i>	<i>Model</i>	<i>Published</i>	<i>Drawing No.</i>	<i>Model</i>	<i>Published</i>	<i>Drawing No.</i>
A. C. Dayton			Brunswick			Freshman		
Navigator	November, 1929	SR24	3KRO	November, 1929	SR23	2-N-12	September, 1929	SR14
Acme Mfg. Co.			15, 22, 32 and 42	November, 1930	SR86	General Electric		
AC7	March, 1929	SR3	S14	November, 1930	SR71	H-32	January, 1932	SR166
AC4	March, 1929	SR4	11, 12, 16	October, 1931	SR148	S-22	January, 1932	SR137
All-American Mohawk			17, 24	December, 1931	SR164	General Motors		
Lyric 90	November, 1930	SR74	E	February, 1932	SR183	A	November, 1930	SR68
Lyric 6	March, 1929	SR1	Colonial			120-A	November, 1931	SR116
Lyric 8	March, 1929	SR2	31AC	January, 1930	SR29	S3A	November, 1931	SR154
Lyric J	October, 1931	SR128	33 and 34 a-c	November, 1930	SR95	S9A	January, 1932	SR173
Lyric B-7	December, 1931	SR165	47-48	December, 1931	SR160	S-10A	February, 1932	SR179
Lyric S-8	January, 1932	SR170	Crosley			Gilfillan Bros.		
Amrad			Roamio	September, 1930	SR67	100	January, 1930	SR32
70	November, 1929	SR22	40S, 41S, 42S, 52S	September, 1930	SR57	Graybar		
81	March, 1930	SR44	608 Gembox	March, 1930	SR41	600	March, 1930	SR42
84	January, 1931	SR106	705 Showbox	March, 1929	SR6	Grebe		
Apex			Jewelbox 704B	March, 1929	SR5	7AC	November, 1929	SR17
48	November, 1930	SR80	77	November, 1930	SR83	AH1	November, 1930	SR96
31 (U. S. Radio)	January, 1931	SR108	53, 54, 57	January, 1931	SR103	Gulbrandsen		
Atwater-Kent			120	October, 1931	SR133	Nine-in-Line	March, 1930	SR40
38	January, 1930	SR28	121-1	November, 1931	SR149	161	March, 1931	SR110
55, 55C (Cap.)	September, 1930	SR51	124	December, 1931	SR150	10, 13	February, 1932	SR175
55, 55C (Ind.)	September, 1930	SR52	125	January, 1932	SR174	Howard		
66	December, 1931	SR114	Dayfan			S. G. A.	September, 1930	SR56
11-2	December, 1931	SR131	5080	September, 1929	SR11	Green Diamond S	September, 1929	SR16
Audiola			Delco			H	October, 1931	SR145
Series 31 (t.r.f.)	November, 1930	SR79	Auto Radio	September, 1930	SR66	SG-B	November, 1931	SR130
Super 31	March, 1931	SR111	Edison			O	December, 1931	SR163
Junior	March, 1931	SR112	R4, R5, C4	November, 1930	SR49	Jesse French, Jr.		
13-S7	February, 1932	SR181	R6, R7	January, 1931	SR99	G	March, 1931	SR118
Balkeit			Erla			Kellogg		
A	September, 1929	SR12	Duo Concerto R-2	January, 1930	SR33	523-528	November, 1930	SR77
Bosch			Eveready			Kennedy		
48	November, 1930	SR73	50	March, 1931	SR50	20	March, 1930	SR48
58	January, 1931	SR109	Fada			26	November, 1930	SR81
60	March, 1931	SR117	7AC	September, 1929	SR13	10	January, 1931	SR38
28-29	November, 1929	SR21	35-35Z	November, 1930	SR70	30-32	November, 1931	SR129
Auto	November, 1930	SR94	KW28-29	December, 1931	SR158	52	February, 1932	SR184
7DC	November, 1931	SR160	Federal			King		
Bremer-Tully			H	November, 1929	SR19	J	January, 1930	SR31
7-70	September, 1929	SR10	Freed-Eisemann					
81-82	November, 1930	SR75	NR80	November, 1929	SR20			
S81-82	October, 1931	SR126						

Model	Published	Drawing No.
Kolster		
K20, K22, K25 and K27	September, 1929	SR8
K21, K23, K24 and K28	March, 1930	SR45
K-43	November, 1930	SR72
K80	November, 1931	SR159
90, 92	February, 1932	SR182
Kylectron		
70	November, 1930	SR65
Majestic		
70	September, 1929	SR7
90B	September, 1930	SR55
130-A	November, 1930	SR84
50	January, 1931	SR98
20	October, 1931	SR124
60	October, 1931	SR138
15	November, 1931	SR157
25	February, 1932	SR178
Philco		
86-82	November, 1929	SR26
95	September, 1930	SR60
90-90A	November, 1931	SR156
112	January, 1932	SR172
Pilot		
148	February, 1932	SR176
Radiette		
F14	January, 1931	SR104
Radiola		
60	January, 1930	SR30
66	September, 1930	SR64
44	January, 1931	SR102
18	October, 1931	SR127
RCA-Victor		
R-7	October, 1931	SR137
R50-55	December, 1931	SR166
R11	January, 1932	SR168
Sentinel		
11, 12, 15, 16	March, 1931	SR115

Model	Published	Drawing No.
106B	March, 1931	SR113
108A	October, 1931	SR146
108	November, 1931	SR123
111	November, 1931	SR155
Silver		
36A	January, 1931	SR105
30B	September, 1930	SR53
30	January, 1930	SR35
35-A	November, 1930	SR82
782	October, 1931	SR120
726SW	October, 1931	SR144
D-E	November, 1931	SR152
F	December, 1931	SR140
G	January, 1932	SR153
A	February, 1932	SR169
Slagle (Continental)		
9	January, 1930	SR27
R-20	March, 1930	SR46
Sonora		
5R	November, 1929	SR25
Sparton		
AC89	September, 1929	SR9
589	September, 1930	SR63
600, 610, 620	March, 1931	SR91
25-26	December, 1931	SR161
10	February, 1932	SR180
Splitdorf		
E175	January, 1930	SR36
Steinite		
261	September, 1929	SR15
70, 80, 95	November, 1930	SR76
600, 605, 630, 635	November, 1931	SR132
Stewart-Warner		
950	September, 1930	SR62
Series 900	January, 1930	SR34
R100	January, 1931	SR85
102A	October, 1931	SR147

Model	Published	Drawing No.
Stromberg-Carlson		
846	September, 1930	SR54
635-636	November, 1929	SR18
12-14	November, 1930	SR93
10-11	November, 1931	SR134
19-20	November, 1931	SR151
Transformer Corp.		
50	November, 1930	SR78
80-81	October, 1931	SR139
Temple		
8-60, 8-80, 8-90	March, 1930	SR37
SG 8-61, 8-81, 8-91	October, 1931	SR125
Transitone		
Auto Radio	November, 1930	SR69
Trav-Ler		
C	March, 1931	SR120
U. S. Radio		
37	March, 1930	SR39
26P	October, 1931	SR143
99A	January, 1932	SR171
Victor		
R32, RE45, R52	September, 1930	SR61
R35, R39, RE57	January, 1931	SR101
Westinghouse		
WR-5	November, 1930	SR92
WR-4	January, 1931	SR107
WR10-12	November, 1931	SR137
WR15	January, 1932	SR168
Zaney-Gill		
54	March, 1931	SR119
Zenith		
52, 53, 54, 522, 532 and 542	March, 1930	SR43
71, 72, 73 and 77	November, 1930	SR97
A, B, C, D	November, 1931	SR141


868 Type Phototube

RCA Radiotron Company, Inc., and E. T. Cunningham, Inc., have recently made available to experimenters a Phototube designated as Radiotron RCA-868 and Cunningham CX-868. This tube is of particular interest because of its use for sound movies in the home and because of its adaptability to many novel experimental uses with light.

is connected across the cathode and anode terminals. The anode or collector, is, of course, connected to the positive terminal of the battery so as to assist the flow of electrons from the cathode to anode. This circuit is not unlike that of the usual vacuum tube except that the electrons are emitted from a light sensitive surface instead of from an incandescent cathode.

The current flowing in the Phototube circuit is dependent on the amount of light received by the sensitized surface. The Phototube, like a vacuum tube, has practically no time lag, so that variations in light intensity instantaneously affect the amount of current passing through the tube. The cathode of the 868 is a semi-

(Continued on page 40)

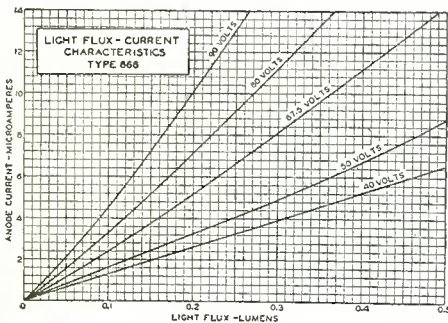

This Phototube is an electronic device and consists of two electrodes enclosed in a glass bulb. One electrode, the cathode, has a sensitized surface which emits electrons when the surface is exposed to light. The other electrode, the anode, acts as a collector for these electrons when a battery

The rating and characteristics of RCA-868 and CX-868 are as follows:

Anode Supply Voltage	90 volts maximum
Anode Current	20 microamperes maximum
Static Sensitivity*	45 microamperes per lumen
Dynamic Sensitivity @ 1000 cycles*	40 microamperes per lumen
Dynamic Sensitivity @ 5000 cycles*	38 microamperes per lumen
Gas Amplification Factor**	Not over 7
Load Circuit Resistance	0.1 to 5 megohms
Maximum Overall Length	4 1/8"
Maximum Diameter	1 3/16"
Window Area of Cathode	0.9 sq. inches
Bulb	T-8
Base	Small Four Prong

* Sensitivity values are given for conditions where a Mazda Projection Lamp operated at a filament color temperature of 2870° Kelvin is used as a light source. A one megohm load resistance is used in the test circuit.

** Gas amplification factor is given as the ratio of sensitivity at rated voltage to the sensitivity at a voltage sufficiently low (approx. 25 volts) to eliminate gas ionization effects.

Automobile Radio Receivers

Twenty-Seven Million Prospects

By L. FREDERICK SINCLAIR*

IN these days of small profits or perhaps losses, and "Old Man Overhead" unescapably with us, a line that will bring new business with a minimum of sales resistance, should receive a hearty "Welcome Stranger" from every dealer who has faith in himself and the future of our country. And when it is learned that the line has a real margin of profit, a real demand, public acceptance, and practically no "grief," the most aggressive dealers are getting themselves lined up with no lost time or lost motion.

There are a few auto-radio receivers which have actually developed to the point where they will give results equal to the best home reception. From every quarter comes the report that auto-radio is here to stay. It is, therefore, apparent that the leading distributors, dealers, and many industrial organizations have recognized the importance, necessity and future of this new marvel of the age. Just a few years ago the auto-radio was looked upon as an experiment, and little or no attention was given to it; but today most of the leading car manufacturers and allied fields realize the importance of this new business stimulant.

There is a vast field for the sale of auto-radios, the surface of which has barely been scratched. Over twenty four million passenger cars are in use in the country, less than 2% being radio equipped, and relatively few being equipped with the modern powerful, efficient, and satisfactory instruments now available. There are also close to three million trucks, busses, motor-boats, aeroplanes, and public motor conveyances to add to the above. Think of it! Twenty-seven million logical prospects! A conservative estimate is that one million auto-radio receivers will be sold in 1932. A year ago auto-radio was practically unknown, yet today there are over half a million sets in use, with the market steadily improving.

A number of manufacturers furnishing parts for radios, are concentrating day and night to produce special tubes, batteries and other equipment for auto receivers. Two of the largest spark plug organizations have perfected a radio spark plug which serves more efficiently than does the ordinary suppressor to eliminate motor noises. Sixteen or more promi-

nent motor car builders are now including a built-in aerial or antenna in their cars as standard equipment. Several of these manufacturers instruct their distributors and dealers to recommend an auto-radio as optional equipment, and distributors are offering these receivers to their dealers as additional sales stimuli.

It is obvious that all this preparation cannot be the result of blind optimism; there are too many big organizations and leading authorities involved. The market and opportunity is so tremendous that many of the interested parties are just realizing the significance of this new product that the motoring public eagerly awaits.

Twelve months ago only a few thousand motor car receivers were in use, but as the public and certain industrial organizations began to realize just what a good auto-radio can do to stimulate sales, a cry went up for better equipment. Today half a million auto-radio receivers are in use. It is true that in this particular industry, like any other new field, much inferior equipment was sold. Many complications had to be overcome and many radio engineering problems had to be solved, to develop a set that would operate under normal as well as adverse conditions, i. e., a receiver that will bring distance with excellent tone quality, plenty of volume, sharp selectivity, and free from extraneous noises. Because of the varying conditions that automobile sets are subjected to, the automatic volume control, available on a few of the finest instruments, is of great benefit in obtaining uniform reception.

Put yourself for a moment in the position of the average motorist, who is also one of the 95% of those who enjoy radio programs. Wouldn't you buy an auto-radio receiver if your dealer gave you a demonstration that proved conclusively that you could enjoy just as good reception on the road in your car, as in your own comfortable home, and (very important) if the price and terms were such that you could pay for it without difficulty? Twenty-five cents a day for a year would pay for an excellent set.

From the dealer's angle it is important to know that the installation of a motor car set is now so standardized and simplified that any mechanic or service man can install one properly in an hour.

For motor conveyances not factory equipped with an aerial, a type of antenna for suspending between the front and rear axles is furnished, out of sight and indestructible. The receiver needs but three holes for mounting and the super dynamic speaker, one hole. The remote control clamps on the steering column. The set may be mounted on either side of the bulk-head, in the engine compartment or inside the body behind the instrument panel, otherwise unused space. B batteries for the battery set or a B automatic eliminator for the all electric set are mounted under the car or any other convenient place. The A current is supplied from the regular car storage battery, and by stepping up the charging rate one or two amperes, an ample current supply is maintained.

The auto-radio line is ideal for the real merchandiser to handle because:

- (1) There is a real demand for it
- (2) The principal sales effort required is to make the demonstration
- (3) There is a wide margin of profit
- (4) The business is clean cut, easy to transact—no "trade-ins"
- (5) It is logically related to your business
- (6) Each sale brings in new prospects
- (7) Small investment and quick turnover

There are many specific sales plans and methods and the dealer is justified in looking to the manufacturer for real merchandising co-operation. Here are some actual instances and suggestions as to the sales possibilities of auto-radio.

An unusual method was employed by a man in Denver, and his plan was disclosed to me after I had a short talk with him. He was in the battery and ignition business. One plan was to rent auto-radios to anyone making trips out of the city. Checking up his records showed that his average sales were 94%. In other words, when the person who rented this equipment returned from the trip and reported at his store, he was so thoroughly enthusiastic about his radio, that it was a simple matter to close the sale on the spot.

During the interim, the plan was to charge the car owners a small fee to cover cost of installation and removal,

* President, Motomaster Radio Corporation.

if not sold when the prospect returned. The charge of fifty cents per day for the use of the set was the only other fee. Wherever the individual had an established credit, no deposit was required on the set. Otherwise an amount representing one half of the sales price was required.

I observed another excellent market in Chicago and St. Louis. Several recognized firms who travel a great many salesmen, were called upon to learn of their interest in auto-radio for their men. In an instance such as this where a quantity purchase was in sight, the distributor was prepared to allow a substantial discount to the firm purchasing the sets, and the firm employing the salesmen installed the sets in any salesman's car employed by them if his sales showed an increase, if he made his quota for three consecutive months, or for any other good reason. In other words, auto-radios were used as a direct stimulant to the salesmen.

A used car dealer found that he had a large stock of cars on hand that were moving slowly. He installed auto-radios in most of the cars and merely added on the cost of the radio to his sales price; so that all in all, the total cost with the auto-radio, was far more attractive to the prospective purchaser than a second hand car alone, or a silent second hand car. He found that after fifteen weeks almost 81% of his cars were sold. This naturally prompted him to make plans for the more extensive use of motor car receivers. He purchased more second hand cars and before they were put on the lot, he had radios put in each one of them. In each instance he received his regular sales price plus the cost of the radio, the purchaser was equally well satisfied, and his profit on the transaction was considerably increased. He found that his sales increased over 300% and that the radio was a very convincing piece of merchandise.

In another instance, a new car dealer handling a well known make decided that he was going to install auto-radios in a few cars on the floor. He also arranged to install this auto-radio in his salesmen's cars and by merely adding the cost of the radio plus anywhere from 10% to 50% as he would any other "extras" he found that the radio acted as a very decided sales stimulant. Sales increased! The salesmen became very enthusiastic and a certain make radio was adopted as standard equipment by this progressive dealer and became optional on all purchases, the same as all other accessories.

In some of the other key cities, a unique plan was used which seemed meritorious if properly executed. It was termed by some as a "European

sales plan," and by others as a "Self-payment plan." The purchaser of an auto-radio was able to acquire this unit and have it installed in his car on the time payment schedule. Usually his car is clear but used as security, and if it carried a first mortgage with enough equity in line with the blue-book requirements, then a second mortgage was taken. The time payments were usually on a ten months basis.

This same customer was permitted to go out demonstrating his radio to other prospects, and for every contract accepted by the dealer from whom he purchased his set, he was allowed a commission equal to one monthly payment. This enabled him to liquidate his obligation to the car dealer or finance company, whichever one held the paper without requiring cash payment. Thousands of auto-radios have been sold by this pyramid-ing method.

State police and a number of other similar organizations have quite an elaborate and efficient plan of operation in effect. They provide all city, county, and state officers with auto receivers. This enables the key personnel of the government to know at a moment's notice when crimes have been committed, when criminals are at large, or to be advised of any other matters of importance immediately. This opened a tremendous market to the officials and other persons who are interested in keeping in touch with activities and plans which will require the purchase of auto-radios.

Recently I learned that several leading motor transportation lines who used trucks in hauling products, both perishable and otherwise, have become interested in auto-radio.

One instance with an organization running one hundred and six trucks, brought out the importance of auto-radio from the safety angle. They were hauling cotton and other freight from the south to some of the northern key markets, when they had a severe accident with one of their truck units en route north. It was later learned that in order to make time the driver kept at the wheel continuously for over fifteen hours. This, of course, prompted the accident. The driver dosing off, ran into a telegraph pole and killed himself, wrecked the truck, and injured others on the road.

This particular transportation company is installing auto-radios in their trucks which will entertain the drivers during these long trips and keep them alert to all road conditions. It will be difficult for them to fall asleep and will enable them to carry on in the face of all travel hazards. Many of the leading passenger bus lines have recognized the importance of installing auto-radios. In the

south the writer was entertained by one of these wonders of the age in a bus going in to Nashville.

Another tremendous field for auto-radios is taxicabs. Usually the taxi fleet owners or the independent owner of a cab, has the remote control of the set placed within an easy reach of the passengers. This adds considerable pleasure to the trip and also is an important factor in keeping the driver alert in dull periods or on long journeys.

One taxicab fleet which installed auto-radios in about 40% of its cars, learned after several months that the cabs so equipped had an income in excess of 35% over others without the same equipment, and also increased their business as a whole because of their reputation for being the most modern cab company in town since putting in the new equipment. Needless to say, they are planning to equip their fleet 100%.

It is obvious that any live distributor or dealer should place auto-radio demonstrators in public garages, battery stations, auto accessory stores, and certain types of gas stations which will automatically create and stimulate a big outlet. Some dealers have raffled off sets in leading theatres in their towns and have secured a great deal of low cost publicity plus thousands of prospective purchasers, many of which have become sales. There are other methods of stimulating sales by giving out a ticket for every purchase or arranging to give special discounts to those who purchase auto-radios from a certain dealer.

The leading "Rent-a-car" systems throughout the nation have recognized the advantages of auto-radio and it has been observed in many of the leading cities that these organizations have capitalized on this business stimulant by installing it in nearly every car made available to the public. The auto-radio in this instance as well as in the case of the taxicab and bus, serves a dual purpose by attracting the attention of the public as well as entertaining it. The auto-radio can also be installed in aeroplanes and motor-boats, or any type of public carrier. This is a new industry which is growing very rapidly and is being quickly recognized by many distributors and dealers as the liveliest field for quick profits.

The foregoing possibilities are but a few and many of the new outlets will be found and created as time goes on. In these times when selling has become scientific merchandising, isn't it worth while to investigate this new "hot" item and get in on it while the going is good? In other words, doesn't this really appeal to you as a "tonic for your business"?

Notes on Distortion

THE two principal sources of distortion in audio frequency amplifiers and reproducers are non-linear response with frequency and the addition of frequencies not originally present.

The first has been fairly well taken care of in modern equipment. The overall response of any audio amplifier can be made flat enough so that no apparent non-uniformity will exist between the amplification of different frequencies. This is not quite the case with loud speakers. The response curve of a good audio amplifier taken with its speaker by means of a calibrated microphone will have a good many peaks and hollows although the average level from 50 to 5000 cycles or higher can be maintained practically constant.

It is interesting to note that the attenuation at different frequencies in any room or auditorium is different for each position in that room. Thus, if one should sit in one seat, there would be certain frequencies which would be much more attenuated than others, and the overall transmission of sound from the source might have even more peaks and hollows than the output curve of the amplifier and speaker. Viewed from this standpoint, the non-uniformity of output of a speaker is not decidedly serious.

It is also a fact that large variations in sound pressure do not cause a correspondingly large difference in the sense of sound. However, it is this ability of the ear which often causes a small amount of discordant distortion to take on more significance than the ratio of its energy to that of the fundamental frequency would signify. Thus, the second cause of distortion, the addition of frequencies not originally present, becomes more serious by virtue of the same trait of the human ear which makes non-uniform response with frequency less objectionable.

To the average radio engineer, the term distortion immediately brings to mind the ratio of the added harmonic voltage to that of a fundamental monotone. As a matter of fact, this is not as important as the attention given it might indicate. True harmonics of any frequency or group of frequencies are, as the term indicates, harmonious with the fundamentals and are fairly well masked by them. It is seldom that anything less than twenty to twenty-five per cent of these can even be detected, to say nothing of causing the annoying discords that often come from the loud speaker even before the actual over-

load level is reached.

However, this harmonic content ratio is in direct proportion to another type of distortion which does produce discords and which has been given less thought than its importance would merit. When two frequencies are applied to an amplifying vacuum tube, non-linearity of its characteristic not only causes the amplifier to produce harmonics in the ratio of whole multiples of the fundamental, but it also causes the addition of sum and difference frequencies, which are often actual discords. It is present-day practice to use but one audio stage following the detector in radio receiver design. For this reason, the r.f. voltages applied to the detector grid must of necessity be large and the detector tube does not depend upon the squared function of its characteristic for its detector action. Thus the average detector tube worked at a sufficient input level so that the negative swing is well below cutoff is not a serious offender when it comes to adding either harmonics or sum and difference frequencies. This is particularly so if the impedance in its plate circuit is well above the plate impedance of the tube, as is the case with a type '27 tube working into a well designed audio transformer. However, the several power tubes and particularly the type '47 pentode will produce sum and difference frequencies which can be detected well before the grid excitation is raised to the overload point. An analysis of the frequencies introduced by the squared and cubed functions of the characteristics of these tubes will indicate the magnitude of this distortion.

Assume that some voltage $A \cos \Theta$ is to be amplified by a '45 power tube. The squared function of the characteristic of this tube would produce a second harmonic of the frequency $\frac{\Theta}{2\pi}$ as follows:

$$A^2 \cos^2 \Theta = \frac{A^2}{2} \cos 2\Theta + \frac{A^2}{2}$$

In the case of the '45, the limit of this second harmonic distortion is taken as 5 per cent. From the above equation we can see that when the coefficient $\frac{A^2}{2}$ is equal to 5 per cent of the peak value of current that there will also be an increase in the d-c. current equal to $\frac{A^2}{2}$. Since the peak current which can pass thru the speaker is equal to the d-c. plate current, the increase in plate current can be taken as a direct measure of the second harmonic dis-

ortion. This, of course, assumes that all of the distortion is due to the squared function of the characteristic only.

If we take this same tube and apply two equal voltages of the same amplitude but of different frequencies, we will have in the plate circuit all of the frequencies caused by the squared function as follows:

$$(A \cos \Theta + A \cos \emptyset)^2$$

This becomes

$$A^2 \cos^2 \Theta + 2A^2 \cos \Theta \cos \emptyset + A^2 \cos^2 \emptyset$$

Upon being still further expanded, this becomes

$$\frac{A^2}{2} \cos 2\Theta + \frac{A^2}{2} A^2 \cos (\Theta + \emptyset) + A^2 \cos (\Theta - \emptyset) + \frac{A^2}{2} \cos 2\emptyset + \frac{A^2}{2}$$

The first and fifth terms are the second harmonics of the frequencies $\frac{\Theta}{2\pi}$ and $\frac{\emptyset}{2\pi}$. The third and fourth terms are the sum and difference frequencies, and the second and sixth terms are increases in the d-c. current. From this expression, it is evident that the magnitudes of the sum and difference frequencies are equal to twice the second harmonic voltages which are produced. Assume that the coefficient $\frac{A^2}{2}$ is equal to 5 per cent of the peak value of the fundamental currents at the frequencies $\frac{\Theta}{2\pi}$ and $\frac{\emptyset}{2\pi}$, then from the coefficients of the sum and difference frequencies we can see that these have an amplitude equal to 10 per cent of the fundamental frequencies.

As stated above, harmonics up to the amount of 20 per cent are not extremely objectionable, but these sum and difference frequencies will produce actual discords. For example let the frequencies $\frac{\Theta}{2\pi}$ and $\frac{\emptyset}{2\pi}$ be middle C and E, the first two notes of a Major Triad, which correspond to 264 and 330 cycles per second. The second harmonic frequencies of 528 and 660 are still harmonious with each other and with the fundamentals. The sum and difference frequencies of 66 and 594 correspond to C two octaves below middle C and to upper D. This latter frequency is a decided discord with the two fundamentals and it is even more objectionable because it delivers twice the voltage or four times the power of the second harmonic frequencies to the speaker.

In the case of the pentode, we have to deal with a large cubed function

in the tube's characteristic. Taking these same two frequencies of equal magnitude and cubing them, we have $\frac{A^3}{4} \cos 3\Theta + \frac{A^3}{4} \cos 3\phi + \frac{9A^3}{4} \cos \Theta + \frac{3A^3}{4} \cos \phi + \frac{3A^3}{4} \cos (2\Theta + \Theta) + \frac{3A^3}{4} \cos (2\Theta - \Theta) + \frac{3A^3}{4} \cos (2\Theta + \phi) + \frac{3A^3}{4} \cos (2\Theta - \phi)$

The first and second terms are the third harmonic frequencies. The third and fourth terms are additions to the fundamental frequencies, and the last four terms are sum and difference frequencies. Here it will be

noticed that the sum and difference frequencies fall on both sides of the second harmonics. In other words, they all include the exponent 2 before either one or the other of the angular velocities of these frequencies. Thus in the case of the fundamentals of 264 and 330, we have additional frequencies of 198, 396, 858 and 924. These correspond to low G, G, upper G sharp and upper A sharp. The first two frequencies are harmonious, and serve to complete the Major Triad, but the last two frequencies cause distinct discords with the fundamentals and their harmonics.

From the expression it is also seen that the coefficients of the sum and

difference terms are all $\frac{3A^3}{4}$ whereas the coefficients of the third harmonic terms are $\frac{A^3}{4}$, or only one third as much. Here again the third harmonic frequencies are not objectionable unless they exceed 20 per cent, but the sum and difference frequencies, which are three times as strong, are at once noticeable because of the discordant results when some of them are combined with the fundamentals and the harmonics. It is for this reason that the '47 pentode must be operated under exactly the proper conditions to keep the cubed function of its characteristic as small as possible.

Photo Electric Cells

THESE photo electric tubes are the culmination of years of experimental research work conducted both in this country and abroad. They represent an attainment that in the past has been but a vision in the minds of physicists.

They have two zones of maximum sensitivity. The first extends into the near ultra-violet, peaking at approximately 3500 Angstroms but falling off rapidly below this point due to glass absorption. The second zone has a much broader peak extending into the red and infra red region and peaking from 7500 to 8500 Angstroms. The great sensitivity at this point taken in conjunction with the fact that radiation from an incandescent lamp source is largely in this region gives great overall sensitivity. The sensitivity of Speed Foto-lectric tubes to radiation from light sources ordinarily employed for talking pictures is of an extremely high order.

Because of the uniformly high sensitivity brought about by a special cathode treatment, it has been found practical to supply Speed Foto-lectric tubes with a somewhat higher ionizing voltage than that generally obtainable. This allows increased latitude in pickup adjustment, in addition to minimizing tube damage from accidental ionization during adjustment, while still retaining gain equivalent to that obtainable from other photo electric tubes at similar operating voltages. Standard Speed Foto-lectric tubes have an ionization voltage of 108 + 8 volts and are designed for operating at 90 volts. However, tubes having other operating voltages are regularly stocked and may be obtained without delay.

No photo electric tube should be operated at voltages above ionization for more than a few seconds, although these tubes will safely handle hun-

dreds of microamperes for short periods without serious damage.

It is recommended that these tubes be protected against intense illumination or excessive heat, to avoid shortening of life. Under light of moderate intensity they will retain their sensitivity for long periods of time.

While the gas-filled photo-lectric



Type B


tube is supplied as standard equipment, vacuum photo-lectric tubes may be obtained to special order in any of the illustrated types. Their sensitivity, however, is only a fraction of that obtained from gas-filled tubes and thus their use is restricted to applications where extreme constancy is of prime importance, such as quantitative measuring, etc. Particular attention has been given in the design of Speed Foto-lectric tubes to a sturdy anchored construction, insuring noiseless non-microphonic operation, free from transient disturbances.

These tubes, without appreciable loss of sensitivity, have an expected life in excess of one year, provided they are not subjected to abuse. They are guaranteed against defects in workmanship or material for a period of six months from date of

purchase.

Type A: small tubular 16 mm bulb supplied with flexible braided leads. (No base.) For use with DeForest Phonofilm, Biophone, Tobis-Klangfilm, Kinoplay. This tube should be mounted in the special cartridge supplied by equipment manufacturer.

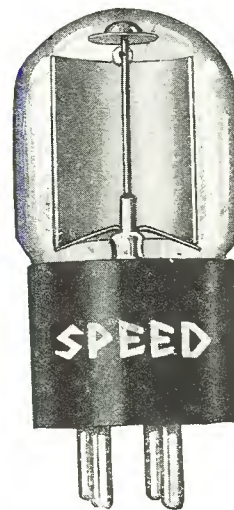
Type B: tubular T8 bulb. Supplied with flexible braided leads. (No base.) For use with Weber Synchrofilm, Platter Phototone (old equipment), Duofone (old equipment), Sonoilm, Brel, Eastern Electric. This tube should be mounted in the special



Type D

cartridge supplied by the equipment manufacturer.

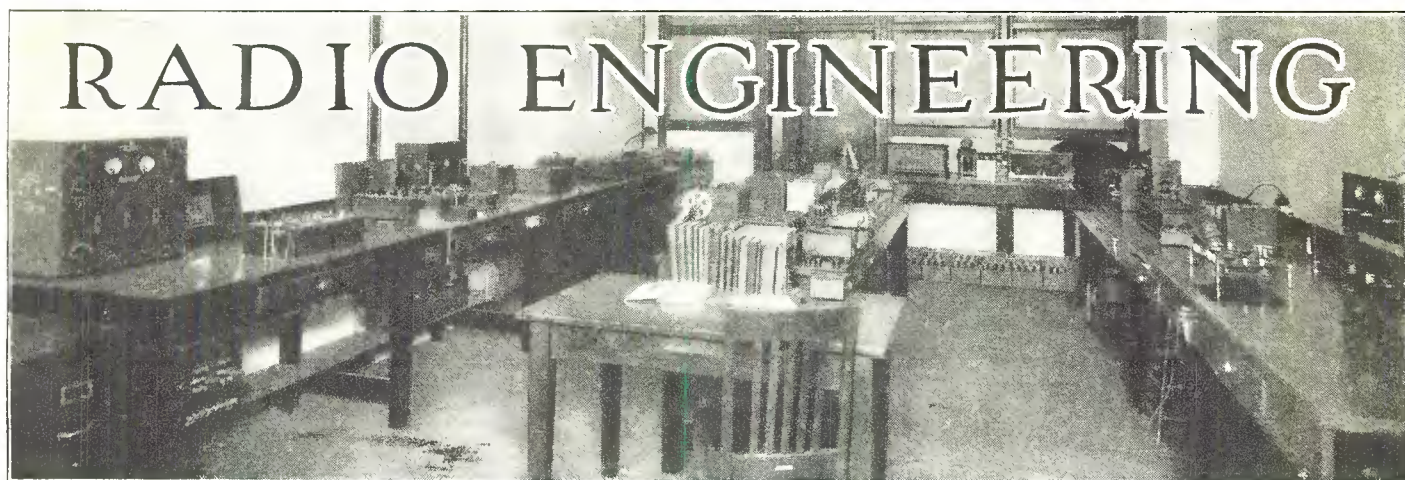Type D: tubular T12 bulb supplied with standard large 4 prong base. Base designation, 2 (D2) for use with Pacent, Powers Cinephone, Motiograph, Tone-o-Graph, Royal Amplitone, Universal, Gries (G. R. C.), Photophone Talkafilm (new equipment), Pulverman Royal, Saf-ray, Bell Portable, Douglas, Lincrophone, National.



Sound Reproducers

SOUND waves may be defined as being more or less regular vibrations in material media. Such waves do not travel through a vacuum but will travel through solids and fluids, the most common of the latter being air, which is practically the universal carrier. In air, sound has a velocity of approximately 1100 feet per second. In other words, it travels a mile in a little less than five seconds. There are many factors which influence the velocity of travel, such as air density, pressure, humidity, etc. An interesting fact for comparing the velocity of sound with light is brought out in the following example. Suppose a symphony orchestra is being broadcast from a hall before an audience and a person 3000 miles away is listening to the program. Let us say that a person is sitting in the audience 100 feet from the orchestra and the former is sitting before his radio receiver, which is 3000 miles away, ten feet from the loudspeaker. Which hears the program first and how much sooner than the other?


First let us take the individual in the audience. As sound travels 1100 feet per second and he is 100 feet from the orchestra, it will take $\frac{100}{1100} = \frac{1}{11}$ or .091 seconds for the sound to reach his ears, almost .1 of a second. Now let us consider the man who is listening to a radio receiver. Radio waves travel with the speed of light, i. e., 186,000 miles per second. It would then require $\frac{3000}{186000} = \frac{3}{186} = .01613$ seconds to travel to the radio receiver. The path between the radio listener's car and the loudspeaker would require a time interval of $\frac{10}{1100} = \frac{1}{110} = .0091$ seconds in addition to the .01613 seconds or a total of .02523 seconds. Thus it

would almost take four times the time for the person sitting before the orchestra to hear the program as it would the radio listener 3000 miles away from the orchestra by virtue of the difference in velocities of sound and electrical waves.

Sounds have three distinct qualities which make them different from each other. These are known as intensity, pitch and timbre. Intensity may be defined as the loudness of sounds which may distinguish one from another; pitch denotes the rate of vibration in cycles per second and hence a low or bass note has fewer vibrations per second than a high or treble note; timbre is probably the most interesting of the three characteristics and determines the quality of the note. It depends upon the harmonic content of the sound wave produced. The so-called overtones are all whole multiples of the fundamental or lowest rate of vibration. Thus a 500 cycle note may have overtones of 1000 cycles, 1500 cycles, 2000 cycles, etc. These overtones of various amplitudes determine the distinction between the note of an organ pipe and that of a violin when the fundamentals are all the same pitch and may have the same intensity. The variation in quality is also caused by the omission of certain of the harmonics, which determines the particular characteristic sound of the instrument.

After demodulation and proper amplification of the audio signal in a radio receiver, some means must be employed to convert the electrical energy into sound energy. Present types require the intermediate stage of a conversion into mechanical energy, which is in turn converted into sound impulses. Very few are the engineers and technicians who did not clamp a pair of head phones over their ears and more or less satis-

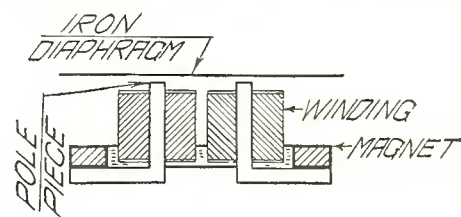factorily catch fleeting phrases from the pioneer station KDKA "way back when." Even before this time head phones were used for continuous wave, interrupted continuous wave, and spark transmissions. In construction and operation the head phone is much like the ordinary telephone receiver. A permanent magnet presents its two poles to a




thin magnetic diaphragm. About the poles are many turns of enameled copper wire, finer than the average human hair. The reaction of variable or pulsating audio currents, first adding and then cancelling the constant flux of the permanent magnet, deflects the diaphragm, which sets up air waves known as sound. Such head phones are limited inherently by the magnet, the diaphragm, etc., which make good quality reproduction impossible as well as limiting the power handling ability. Think of the inconvenience of listening to a program with a constant pressure against the ears and also consider the expense of furnishing enough pairs of phones for a party!

A modification of the phone idea appeared in the horn type speaker, which was more convenient, of course, but which could handle no volume and give no quality. In both of these types the motion is limited by the pole pieces. Reaction of the flux is against the spring tension of the diaphragm, itself, and in these types low frequencies are invariably totally lost in the resulting reproduction. An increase in size of the unit com-

bined with a properly designed exponential horn will make the speaker more satisfactory from the quality standpoint, but the old limitations still hold true for it.

Another variation may be found in the armature type speaker, of which there are at least two distinct styles. In this case a larger permanent magnet is used, and in place of an iron diaphragm, an armature is substituted, which is situated between the poles. Around this armature are found the coils which carry the audio currents, causing the reaction against the field set up by the permanent magnet. The armature is connected

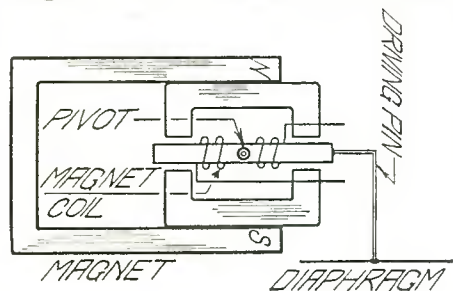


by a rigid member to a non-magnetic diaphragm, which in turn causes motion of the air column. An exponential horn is commonly employed and the quality of reproduction is improved over that of the iron diaphragm type speaker. It is also common practice, in fact, the most common practice in the magnetic speaker, to connect the armature through a lever system to the apex of a fairly heavy, stiff paper cone and thus transmit the magnetic movement to the cone, which in turn would set the air in motion as sound impulses. Better quality results but the output is limited by the motion of the armature which strikes the pole pieces when a definite amplitude is reached.

It might be well to consider the efficiencies of the types of reproducers so far considered. In speaking of efficiency, no account of the energy required to excite the magnetic circuit will be given and only the ratio of audio input to the sound output will be considered. All of the above types fall within the limits of about one-half of one per cent to two per cent, with only exceptional designs showing slight improvement over the latter figure. This immediately explains why power tubes are used in the output stage of radio receivers. Their need is apparent when it is seen that even with present-day speakers only one-twentieth of the audio power is finally transferred to sound energy.

The advent of the dynamic type speaker marked its immediate universal adoption, particularly on receivers operated from house lighting systems. Until very recently a por-

tion of direct current was necessary to excite the field used on all of these reproducers. Instead of an armature or an iron diaphragm to transform the electrical energy to mechanical energy, [this type employs a light weight single layer cylindrical coil, which is placed in a gap in the magnetic circuit, which is set up by a coil of many turns, having a direct current excitation. Such a system for any sensitivity at all must have a very small gap, which means only enough clearance between the coil and the metal to prevent actual rubbing contact. The so-called voice coil, reacts against the flux in the gap and transmits its motion to a paper or composition cone. This cone may be corrugated for stiffness and attached to the frame by means of a flexible strip around the periphery, though on some models it is attached rigidly.

The voice coils range from a single turn to perhaps as high as 200. It is evident, therefore, that some means must be used to make an impedance adjustment with regard to the tube or tubes used in the last audio amplifier. For this purpose a transformer known as the output transformer is commonly employed, having the proper step-down ratio. Ordinarily the types of speakers discussed before give an impedance to the load circuit of the output tube or tubes which is chiefly reactive and, therefore, give very noticeable peaks at various frequencies. Also the actual resonant frequency of the diaphragm or cone itself falls well within the

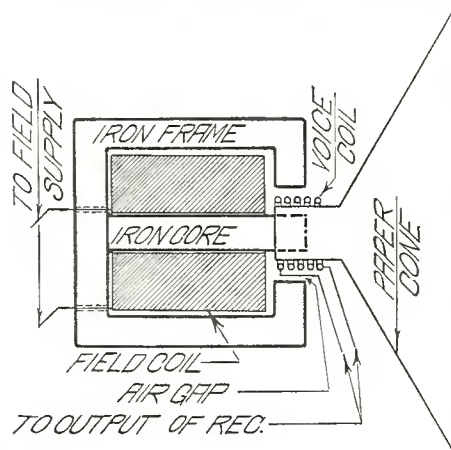

audible range. A dynamic speaker voice coil has only a small reactive component in its impedance, which makes the load practically a resistance, thus affording a nearly flat response for all audio frequencies and a close approach to the ideal. The voice coil's impedance ranges from 5 to 15 ohms for the various common types of dynamic speakers. In a given speaker the change in impedance is usually not more than 2 to 1, from 100 to 5000 cycles, whereas other

type speakers would vary from 1000 to 50,000 ohms for the same audio frequencies picked.

As to efficiency, the very latest types of dynamics have been improved at least 100% during the past year or two, and now a good speaker may run as high as 5%. At resonance, which is usually made to fall above the hum frequency, the efficiency will run as high as 50% or 60%. Thus we now have a reproducer which gives excellent bass note response as well as highs, and we have one of greater sensitivity than was available heretofore. To make use of the low note response, a baffle is essential to the installation of all dynamic speakers to prevent sound waves from cancelling each other from the front of the cone to the back. Without a baffle there is no response below 300 or 400 cycles. The size of the baffle determines the lowest note which may be effectively reproduced, assuming the speaker itself is capable of transmitting this frequency by its inherent design. By the shortest mechanical path a baffle should be at least one-quarter of the wavelength to be reproduced. In other words, if a speaker is installed in a console which has no bottom, the path which governs the low note response is from the front of the speaker to the back via the bottom of the front panel of the console. It is also possible to install more than one speaker in a large baffle, such as for talkie theatre reproducers. Care must be taken that all cones move in the same direction, at the same time, for one being out of phase would prevent good response due to cancellation.


Newest developments in dynamics consist of the addition of a "bucking coil," which is made up of the required number of turns in series with the voice coil and placed in the field winding to "buck" or cancel any hum component introduced into the voice coil by a ripple present in the field coil. This addition in no way affects the response of the speaker itself. The very newest development on the market is a dynamic speaker which has a permanent magnet for the constant flux applied to the gap. This new speaker is in no way a magnetic speaker according to the old terminology, since the response is the same as that for a dynamic. It is entirely possible to duplicate the sensitivity of the separately excited dynamic, but the cost of the magnetic steel required to do this is prohibitive. Hence a metal having good magnetization powers is used so that the reduced response is only two decibels below that of the ordinary good dynamic type. Statements are made that not more than a two decibel loss will occur in five years.

A Service Wavemeter

WE present here a wavemeter which has proved almost indispensable to the author in all types of receiver alignment work. The range of this instrument is from approximately 130 ke to about 2000 ke, so that all intermediate frequencies and the broadcast band are covered, including the so-called long wave bands from 130 ke to 550 ke with only one coil and a single variable tuning condenser.

Cheap to Build

This instrument is very cheap and simple to build and for that reason does not represent the foremost possible design, but the service it renders is well worth the expenditure necessary in building it. The only real item of cost is the Weston model 425 thermogalvanometer used for resonant indications. To cover the frequency bands required, it was found necessary to tap the single inductance in two intermediate points, in addition to the entire coil. Some losses are naturally encountered, therefore, but sufficient indications can be procured under ordinary conditions so this does not merit serious consideration. A coil of No. 24 b. s. enameled wire about 3 inches long, wound on a tube of $2\frac{3}{4}$ inch diameter was used for the inductance. Taps are spaced about 1 inch apart, though the builder may

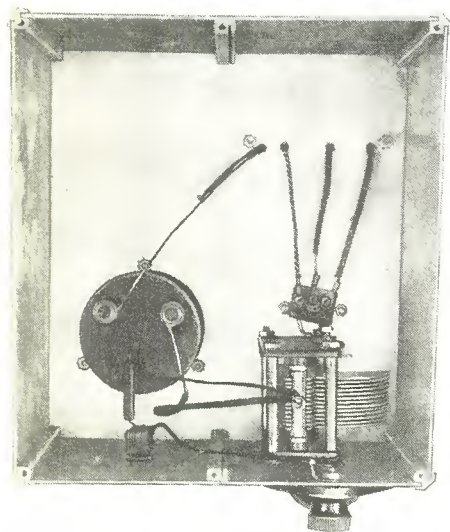


alter the spacing to give the overlap he desires on the frequency bands.

Ranges Covered

For intermediate frequencies a

mica fixed condenser of the necessary capacity is shunted, by means of the switch shown at the right of the front panel, across the .0005 tuning condenser. Only two or three calibration points need be taken for this longest wave range (using the entire tuning inductance), since the dial setting-frequency curve is so nearly a straight line when using an SLF or modified SLF variable air condenser. The next range consists of the variable con-

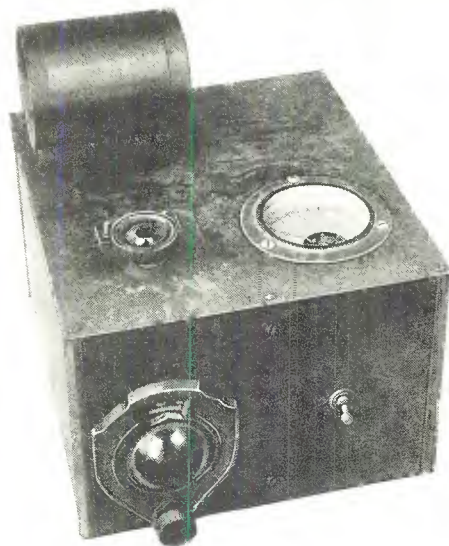

denser only, in series with the whole inductance. This range will probably extend to about 700 ke or 800 ke. Next there is two-thirds of the coil with the variable condenser, and finally one-third of the coil with the variable condenser. As the inductance decreases and the frequency increases, more points must be taken to have an accurate calibration curve. A tap switch mounted on bakelite is used for selecting the proper inductance. In order to maintain a calibration which will hold for any length of time, it is imperative that all leads be of at least No. 16 copper wire and preferably No. 14 tinned copper, since the least movement or vibration will destroy the accuracy of the readings taken.

It is also highly advisable to use a good grade of collodion to fasten the turns of the coil and prevent them from becoming loose, in which case the calibration would be absolutely worthless. A coupling coil may be used to couple the signal to the wavemeter coil, but care must be taken to use only a very small indication to pre-


vent the detuning effects occurring with tight coupling.

An inexpensive aluminum box shield was used as a housing for this wavemeter. Also, any vernier type dial may be used and any good SPST switch. A schematic diagram at the bottom of column 3 shows the simplicity of the circuit layout. The shield is used as the common ground for the switch, tuning condenser, and padding condenser.

Calibration

Probably the best method of calibrating this wavemeter is to use an oscillator which covers the band of intermediate frequencies, in conjunction with a broadcast receiver. For example, the 175 ke calibration point may be quite accurately determined by adjusting the oscillator near the point known to be in the neighborhood of 175 ke and obtain zero beat with a broadcast signal of dependable frequency. The author used WLW on 700 ke, obtaining a beat of the fourth harmonic of 175 ke.

As the frequency becomes higher, the task is simplified. In the broadcast band no trouble will be had in using a broadcast oscillator and zero beating if the fundamental frequencies of the stations employ crystal frequency control. In all cases the coupling to the local oscillator should be very loose. It is recommended in all work, including calibration, that the indication on the 425 galvanometer does not exceed two or three whole scale divisions to prevent any drag effects.

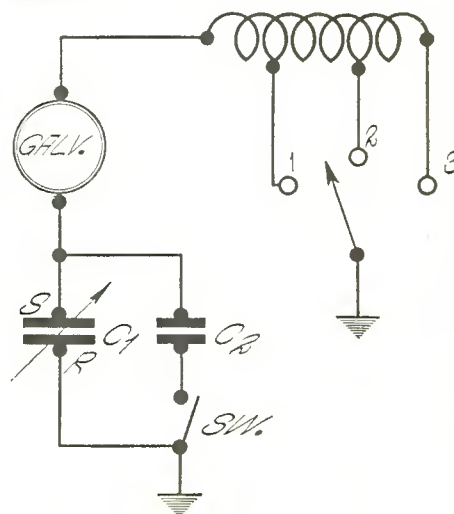

Sound Films and Television Broadcast

(Continued from page 17)

period of time than that required to create an impression on the human visual system. To maintain such unbroken continuity, the inventor controls the operation of the two Geneva movements by means of a cam which automatically selects certain frames out of each unit of 48 consecutive pictures so that the film runs at its normal speed of 24 frames per second.

For example, with "A" designating film No. 1 and "B" designating film No. 2, the following pictures out of a cycle of 48 are scanned successively in this order: 1A - 2B - 5A - 6B - 8A - 9B - 11A - 12B - 14A - 15B - 17A - 18B - 20A - 21B - 23A - 25B - 26A - 29B - 30A - 32B - 33A - 35B - 36A - 38B - 39A - 41B - 42A - 44B - 45A - 47B. Because the film moves forward at the regular rate of speed, 24 frames per second, the sound recorded on the film is reproduced without distortion by using the ordinary photo-cell system.

The perfection of the Western Television apparatus by Conto marks an important step in the development of Television. It is to be looked upon as a means to enable television station operators to present programs that are both interesting and entertaining. At the same time it removes that bugbear of having to develop special moving picture apparatus to produce pictures in the moving picture studios to correspond to the scanning methods employed in the Television stations.

Television Note


TO determine definitely the pulse of the public regarding television, a rather unique idea was carried into effect by A. Pollak, President of the Television Manufacturing Company of America. A temporary store was rented in the Hollywood Theatre Building, 52nd Street and Broadway, New York City for a period of six weeks. Under very capable management free demonstrations of the "SEE-ALL" Television products were conducted daily, day and night, and it is estimated that a half million people obtained their first actual view of television. So vast was the attendance that at times traffic was blocked and it was necessary to lock the doors to keep in check the ever increasing numbers eager to learn about television. Although this store was located in one of the most highly electrically charged zones of New York due to the mass of electrical advertising signs which make up the district, the pictures obtained were exceptionally clear and pleasing.

Two types of "SEE-ALL" models

were demonstrated—one a complete cabinet showing a picture on a screen about 6x9 inches and also a "SEE-ALL" Television assembled from one of the inexpensive kits now being marketed to experimenters by this company. Considerable time was spent by Mr. Pollak personally at this demonstration and much valuable information gathered which will be reflected in the 1932 line of "SEE-ALL" Television Cabinets. The wide range of models and prices of this line to be announced very shortly will place television within the means of everybody.

Radio Control and Aeroplanes

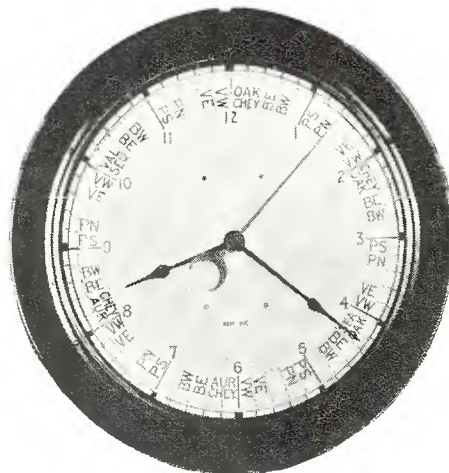SIMPLIFIED radio controlled airplane movements have been developed to the point that the busiest airway radio station in the world,



WUCG, maintained at Chicago Municipal Airport by United Air Lines, can serve twenty-four mail and passenger planes of United Air Lines arriving and departing daily at the Chicago Airport, as well as exchange messages between the other thirty-four stations on United Air Lines' system extending from the Atlantic to the Pacific, from the Great Lakes to the Southwest, from the Rocky Mountain region to the Pacific Northwest and the length of the Pacific Coast. This marks a new step in controlling airplane movements, says a bulletin.

All passengers and mail planes of United Air Lines are equipped with two-way radio telephone, which permits the pilot to talk from his plane to ground stations or to pilots of other planes in flight. However, as United Air Lines never has less than twelve and often as many as eighteen planes in simultaneous flight, some method had to be developed for assigning each pilot a moment when he could phone into the ground station and receive instructions and weather from the dis-

patcher.


So a synchronized clock face was developed. It measures about eighteen inches in diameter; around the rim the minute segments are lettered at one or two-minute intervals with the abbreviation of a division of the airline. The minute hand successively designates the portion of the line over which radio communication is to be permitted, thus eliminating the possibility of garbling messages because of two or three conversations being attempted at the same time.

Thus, in any one hour there are four times when conversation may be held with planes on each section of the entire division, once every fifteen minutes. In addition there is one blank minute in every five-minute period for emergency communication or calls of a non-routine nature, and there is a two-minute period in each ten minutes during which direct station-to-station communication is permitted. Since each airline is assigned but a single frequency upon which to broadcast, it is apparent that, with the great range of the present sending and receiving sets, some such system is essential to successful communication.

One of these stations exchanges direct radio communication with pilots of twenty-four planes arriving and departing from one airport, as well as exchanging messages between the other thirty-four ground stations on United Air Lines' system.

Sound on Trucks

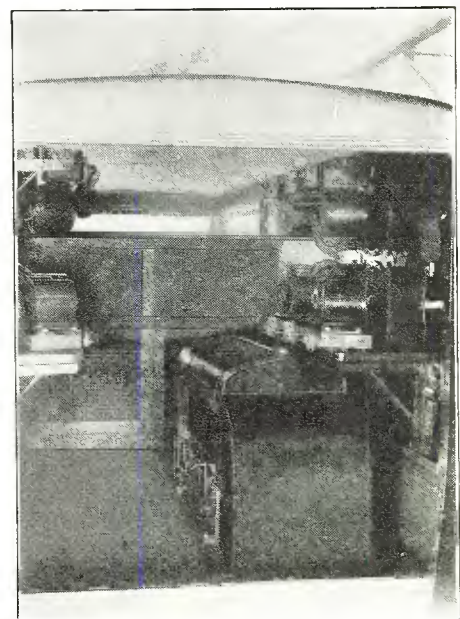IN conjunction with the article in the January issue under the same title, on page 37, the illustration shows



another typical speaker and power plant installation for a portable power amplifier system by the RCA-Victor Company.

Long Line Frequency Control

WHAT constitutes the first practical employment of ultra-short radio waves, which for many years have remained one of the curiosities of radiotelegraph experimental work, has been accomplished with the establishment of the new, inter-island radio telephone system of Hawaii.

The development is regarded as an important milestone of radio, as it taps an altogether new reservoir of wave lengths for commercial utilization. Such an ultra-short wave communications system lends itself to duplication in other archipelago, and particularly in those of the tropical regions. For this and similar short distance communication purposes the ultra-short waves provide definite advantages in reliable, continuous communication, although the efficiency of frequencies now employed for long range communication remains unchallenged.

Attempts to establish inter-island telephone service for Hawaii were begun by the Mutual Telephone Company in 1912, when a survey disclosed that the channels between the islands were too deep to make the use of cables for voice communication practicable. The successful system eventually was established through the cooperation of RCA engineers with the Mutual Company, which called upon R. C. A. Communications, Inc., for assistance following extensive research and experimental work by RCA in the ultra-short wave field.

At the time RCA engineers were brought into consultation, in 1928, experiments had been conducted in Hawaii over a period of years on various frequency bands open for use by the telephone company. However, the spectrum of intermediate and the so-called "normal band" of short waves had been abandoned because of the selective fading and strong atmospheric experiences. It was quickly found that transmission on the ultra-short waves would convey telephone conversation with reliability over the required distances but many problems remained for solution before a practical system could be developed.

Ultra-short waves have many of the properties of light waves, which do not tend to follow the curvature of the earth. In the Hawaiian system they are transmitted from point to point on the same plane, without intervening mountains or other intervening obstacles. This condition was met by locating the Hawaiian stations on top of the mountains and in a direct air line with stations on the mountain

peaks of other islands. Mathematically exact surveys were conducted so as to permit a perfect alignment of sending and receiving antennae at the different stations.

Although ultra-short waves provided, in this instance, the solution to transmission through the ether without static or interference, the apparatus which generated the waves was extremely critical of adjustment. A transmitter on so short a wave length is subject to "frequency drift" or shifting of wavelength, from very slight causes. Even so small a factor as a change in atmospheric temperature would throw it off the appointed wave. This had to be overcome, else the constant attention of trained engineers would be required to keep the stations "in tune" and even then interruptions to the service would be inevitable.

The usual engineering method of maintaining a transmitter on its assigned wave is by means of electric crystal control. But this necessitates much associated apparatus and, in the case of ultra-short waves, so much additional equipment as to place the cost of operation beyond all reasonable limits. RCA engineers solved this difficulty with a new development known as the Long Line Frequency Control. This is an electrical circuit, with no tubes and no moving parts, connected to the five meter transmitting circuit. The action of the Long Line Frequency Control is to correct automatically and entirely by electrical means any tendency of the transmitter to stray from its proper wave length. Through its employment, the apparatus is lifted out of the category of critical, laboratory equipment and made practical for commercial use. The Long Line Frequency Control makes possible installations which need only periodic attention and otherwise maintain telephone communication between islands as dependably as though they were connected by wires. Equipment for the new system was supplied by RCA Victor Company.

The possibilities of ultra-short waves have for some years been a subject of speculation and investigation among radio engineers. Pioneering research in this field has been done by Marconi, both in his independent efforts and in cooperation with the Italian Government. RCA began experiments several years ago. The ultra-short wave band is generally listed in present day parlance as that part of the radio spectrum which extends from five meters downward. There

appears to be little or no difference in the essential properties of these frequencies except that they present more problems in control as the wave length shortens. Research among other frequencies in the realm of ultra-short waves has been and is being conducted at the R. C. A. Communications laboratories at Riverhead and Rocky Point, Long Island. It is believed that the principles of the Long Line Frequency Control will prove of great value in the taming of even the shorter of the ultra-short waves. The Long Line Frequency Control is so named because the electrical circuit which constitutes this device comprises lines having a length many times the length of the wave on which the transmitter operates.

The Hawaiian radiotelephone system is a tribute to the efforts and persistence of J. A. Balch, President of the Mutual Telephone Company, who pushed forward continuous experimental work on the islands. Of its operation, Mr. Balch reported that on the day the new system was opened for commercial traffic a total of 213 calls were handled without a single instance of a call having to be cancelled on account of unsuccessful transmission. During the first week of commercial service the islands were visited by a severe static storm, described by Mr. Balch as one of the worst in his experience, with lightning flashing almost continually for the better part of two days and nights. "No difficulty was experienced, however, in the operation of our ultra-frequency telephone circuits," said Mr. Balch, "and it was a weird experience to be watching the lightning flashing and at the same time talking to Hilo without difficulty, or without any particular annoyance being experienced from the very faint indications of static on the circuit."

The system links the islands of Hawaii, Kauai, Oahu and Maui. A radiotelephone service in which the Mutual Telephone Company is interested between Hawaii and the North American mainland will be opened probably before Christmas this year. For the mainland service, transmitting and receiving stations in Hawaii will be owned and operated by the R. C. A. Communications, Inc., and the transmitting and receiving stations in California will be owned and operated by the American Telephone and Telegraph Company. Connection to the Hawaiian land telephone network as well as to the new, inter-island radiotelephone service will be made through the Mutual Telephone Company.

Television on a Beam of Light

SCHENECTADY, Dec.—Television, transmitted experimentally on a beam of light, utilizing a wave length of but a billionth of a meter, has been successfully demonstrated here in the radio consulting laboratory of the General Electric Company it was announced today by Dr. E. F. W. Alexanderson. This use of the ultra-short waves, Dr. Alexanderson believes, opens the way to a new and valuable era in the art and promises to result in more distinct television pictures.

In the laboratory tests, the pickup device was of the conventional type such as used by Dr. Alexanderson in his previous television experiments. Instead of the electrical impulses being fed into a radio transmitter as heretofore, they were modulated into extremely high frequencies on a light beam from a high intensity arc. This beam was projected the length of the laboratory into a single photoelectric tube, which transposed the modulated light waves back into electrical waves. The electrical impulses reproduced the image by means of an ordinary television receiver.

"The work thus far is highly experimental, yet some day we may see television broadcast from a powerful arc light, mounted atop a single tower high above the city," Dr. Alexanderson said. "These modulated light waves will be picked up in the homes by individual photoelectric tubes or electric eye, instead of the present type wire antennae.

"Light broadcasting may have the same relation to radio broadcasting as the local newspaper has to the national newspapers. These light waves can be received at relative short distances only, perhaps ten miles. Each community could then have its light broadcasting system."

The greatest difficulty in television today, Dr. Alexanderson believes, is in the method of transmission. Radio waves usually follow several paths in travelling from the transmitter to the receiving station. Each ray following a different path produces a different image so that a composite image is apt to be blurred. For this reason television has been tending toward shorter waves.

"The logical progress of this development," said Dr. Alexanderson, "is that in the future we shall explore still shorter waves, until we finally arrive at the light waves which we know travel in straight lines and which can be accurately controlled by such optical means as mirrors and lenses.

"When it was decided to take up experimentation on this subject Dr. Irving Langmuir of the research laboratory was consulted about the probabilities of being able to modulate to a source of light at the required high frequencies of from 100,000 to a million cycles. Dr. Langmuir, who has done much research work with arcs, believed that this could be accomplished by using a high intensity arc. It was concluded that a most desirable light would be a high-intensity arc of the type where the light comes from the arc rather than from the crater. In the 10-ampere arc lamp used for the first test, most of the light comes from the crater, and comparatively little light is in the arc. The lamp was used in such a way that the light from the crater was eliminated, and the arc used was therefore quite a weak source of light. The current from our standard television pickup was superimposed upon this arc, and the light from the arc intercepted by a photoelectric tube at a distance of 130 feet. The photoelectric tube was then used to control our regular television projector. The television image transmitted in this way had the same sharpness of detail as the one ordinarily obtained without the interposition of the light beam.

In 1927 a picture three inches square on the screen was achieved by Dr. Alexanderson; in 1928 the first radio-television drama was broadcast from Schenectady; in the fall of 1929 a picture 14 inches square, not simply black and white like a silhouette but with all the gray shades for depth and detail, was produced; in 1930 Dr. Alexanderson sent television signals to Australia and back, and after traveling 20,000 miles, a rectangle still had four corners; and in the same year television first appeared as part of a regular performance at a theater in Schenectady with an image on a screen seven feet square.

Modulated light has also been used in many previous experiments by the General Electric Company. For instance, there is the talking beam of light that has been used at meetings and convention demonstrations, and the ship-to-shore communication of last summer with a talking light beam.


Similarly, various other radio and pure research findings of other General Electric scientists are reflected in the new experiments with light-transmitted television. For instance, there is the work of Dr. Langmuir and W. F. Westendorp with a fog-penetrating light for aviation, wherein it has been demonstrated that a photoelectric tube is sensitive to modulated light even if the atmosphere is so foggy or hazy that the light source cannot be seen. This had led to the belief, that in event of local broadcasting with modulated

light, haze and fog will not seriously interfere with signal reception.

868 Type Phototube

(Continued from page 30)

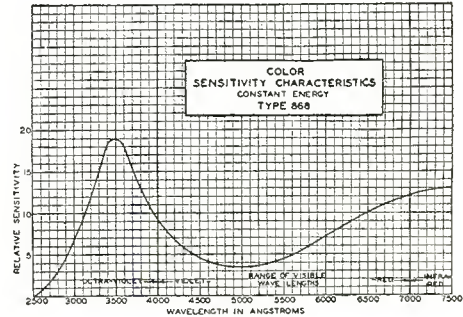cylindrical sheet of metal and is coated with a thin film of caesium. The anode or collector consists of a small wire placed in the axis of the cathode surface. A small amount of gas is used in this tube to produce high sensitivity. The 868 is sensitive to light over the entire visible spectrum and



also to radiation in the near infra red zone. The large response in the red and infra red region makes this tube very well adapted to sound reproduction and television work where incandescent lamps are used for light sources.



Ordinarily, the output of an 868 requires further amplification. This may be accomplished by a suitable tube amplifier resistance coupled to the Phototube circuit.

Plans of the RMA to coordinate its annual convention and trade show next May with the national political campaign have proven successful. In anticipation of the presidential campaign and its probable great stimulus to radio sales, the arrangements for the RMA annual industry gathering and trade show, May 23-26, 1932, in Chicago, now will insure three weeks' time for the radio industry to take advantage of politics to make sales. The Republican national convention will be held June 13th at Chicago, just three weeks after the RMA trade show, and the Democratic national convention is scheduled July 1st.

Receiver Voltage Analyses

Zenith 91, 92

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
51	1st R. F.	2.25	175	.2	0	7.0	100
51	1st Det.	2.25	175	3.5	.4	3.5	90
27	Osc.	2.2	70	0	0	8.5	0
51	I. F.	2.2	200	4.0	0	2.5	115
27	2nd Det.	2.2	115	0	9.	.5	0
27	1st Aud.	2.2	145	0	13.	6.5	0
45	P. P.	2.2	275	54	0	30.	0
45	P. P.	2.2	275	54	0	30.	0
24	A. V. C.	2.2	35	.4	0	0	54
80	Rect.	4.8	355	0	0	76.	0

Silver-Marshall J

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
51	R. F.		220		3		76
24	1st Det.		220		15		76
27	Osc.		76		15		
51	I. F.		220		3		76
51	I. F.		220		3		76
27	2nd Det.		0		3		76
27	Audio		190		18		
47	P. P.		225	16.5			
47	P. P.		225	16.5			
80	Rect.		320				

General Electric K-62

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	R. F.	2.2	205	.1	2	5	75
27	Osc.	2.2	60	0	8	5	
24	1st Det.	2.2	200	7	7	.5	70
35	I. F.	2.2	205	.1	2	5	75
27	A. V. C.	2.2	25	0	0	0	
27	2nd Det.	2.2	180	8	20	.5	
47	P. P.	2.2	205	10		25	210
47	P. P.	2.2	205	10		25	210

Westinghouse WR15

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	R. F.	2.2	205	.1	2	5	75
27	Osc.	2.2	60	0	8	5	
24	1st Det.	2.2	200	7	7	.5	70
35	I. F.	2.2	205	.1	2	5	75
27	A. V. C.	2.2	25	0	0	0	
27	2nd Det.	2.2	180	8	20	.5	
47	P. P.	2.2	205	10		25	210
47	P. P.	2.2	205	10		25	210

Crosley 125

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
24	Osc.-Det.	2.45	175	10			80
35	I. F.	2.45	220	2.3			80
24	2nd Det.	2.45	80	4.5			25
47	Output	2.55	215	16			
80	Rect.	4.95					

Stewart-Warner R-102 A, B, E

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
24	1st Det.	2.45	250	6.5			95
27	Osc.	2.45	95	9			
51	I. F.	2.40	250	3			95
24	2nd Det.	2.45	70	7			30
47	Output	2.45	230	15			250
80	Rect.	4.8	170				

Receiver Voltage Analyses

Crosley 127

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	R. F.	2.4	185	3			85
35	1st Det.	2.4	185	8			85
27	Osc.	2.4	185	10			
35	I. F.	2.4	185	3			85
24	I. F.	2.4	185	3			85
27	2nd Det.	2.4	0	0			
27	Aud.	2.4	185	10			
47	P. P.	2.4	285	16			
47	P. P.	2.4	285	16			
80	Rect.	4.8					

Sparton 15

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	R. F.	2.5	185	3		6	100
35	1st Det.	2.5	180	11		3	100
35	I. F.	2.5	185	3		6	100
27	Osc.	2.5	95				
27	2nd Det.	2.5	135	14		.7	
27	A. V. C.	2.5	40	24			
47	Output	2.5	260	18		36	270
80	Rect.	5	370			55	

T.C.A.-Clarion 80, 81

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
51	R. F.	2.2	233	3	3	5	66
51	1st Det.	2.2	233	7	7	2.3	73
27	Osc.	2.2	80	0	0	4	
51	I. F.	2.2	233	3	3	5	77
24	2nd Det.	2.2	162	6.2	7.2	.5	73
47	Output	2.2	228	15	0	27	233
80	Rect.	4.8				50	

Stromberg-Carlson 19, 20

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	R. F.	2.4	150	3.3	3.3	3.3	80
35	1st Det.	2.4	140	12	12	1.1	66
27	Osc.	2.4	75		7	1.1	
35	I. F.	2.3	140	3.6	4	7.4	71
35	I. F.	2.3	140	3.6	4	7.4	74
27	2nd Det.	2.3	185		26	1.0	
45	P. P.	2.4	245	46		30	
45	P. P.	2.4	245	46		30	
80	Rect.	4.6				58	

Gulbransen 23

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	R. F.		181				90
35	1st Det.		179				84
27	Osc.		92				
35	I. F.		181				90
35	I. F.		303				86
27	1st A. F.		115				
47	Output		240	17			252
80	Rect.		356			118	

Kennedy 56

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
51	R. F.	2.35	208	3-30			98
24	1st Det.	2.35	208	5			30
27	Osc.	2.35	90	10			
51	I. F.	2.35	208	3-30			98
27	2nd Det.	2.35	120	16			
47	P. P.	2.35	220	14			208
47	P. P.	2.35	220	14			
80	Rect.	4.9					

Set Manufacturers and Brand Names

Manufacturer	Address	Brand
All-American Mohawk Corp.	North Tonawanda, N. Y.	Lyric
Andrea, F. A. D., Inc.	Long Island City, N. Y.	Fada
Atwater-Kent Mfg. Co.	4700 Wissahickon Ave., Philadelphia	Atwater-Kent
Audiola Radio Co.	430 S. Green St., Chicago	Audiola
Automatic Radio Mfg. Co.	112 Canal St., Boston, Mass.	Tom-Thumb
Aztec Radio Co.	Atchinson, Kans.	Aztec
Balder Radio Corp.	80—1th Ave., New York City	Balder, Knickerbocker
Balkeitt Radio Co.	North Chicago, Ill.	Balkeitt
Belmont Radio Co.	39th & Ashland Pl., Chicago	Belmont
Brown & Manhart Co.	6219 S. Hoover St., Los Angeles, Calif.	Roamer
Browning-Drake Corp.	West Townsend, Mass.	Browning-Drake
Brunswick Radio Corp.	120 W. 42nd St., New York City	Brunswick
Capchart Corp.	Fort Wayne, Ind.	Capchart
Carteret Radio Laboratories, Inc.	251 W. 18th St., New York City	Carteret, Moto-Radio
Century Radio Products Co.	3007 N. Austin, Chicago	Century
Clago Radio Corp.	2909 Indiana Ave., Chicago	Mayflower
Colonial Radio Corp.	254 Rano St., Buffalo, N. Y.	Colonial
Columbia Phonograph Co.	55—5th Ave., New York City	Columbia
Commonwealth Radio Mfg. Co.	847 W. Harrison, Chicago	Ajax, Commonwealth
Crescent Radio Mfg. Co.	1026—2nd Ave., Minneapolis, Minn.	Crescent
Crosley Radio Corp.	Cincinnati, Ohio	Crosley
Davison-Haynes Mfg. Co.	717 Mateo St., Los Angeles	Angelus
Delco Radio Corp.	Dayton, Ohio	Delco
Dubilier Clock Corp.	40 W. 17th St., New York City	Dubilier
Echophone Radio Mfg. Co.	104 Lake View Ave., Waukegan, Ill.	Echophone
Electrical Research Lab.	1731 W. 22nd St., Chicago	Erla
Elgin Radio & Tel. Corp.	41 W. 14th St., New York City	Elgin
Federal Radio Corp.	717 Mateo St., Los Angeles, Calif.	Federal Orthosonic
Fink Industries	706 Sheridan St., Lansing, Mich.	Imperial
Freed Television & Radio Corp.	Long Island City, N. Y.	Freed, Freed-Eiseman
French, Jesse, & Sons Co.	New Castle, Ind.	Jesse French
Frost-Minton Corp.	12 E. 41st St., New York City	Frost-Minton
Galvin Mfg. Co.	857 Harrison St., Chicago	Motorola
General Electric Co.	Bridgeport, Conn.	General Electric
General Motors Radio Corp.	Dayton, Ohio	General Motors
Gillfillan Bros., Inc.	1815 Venice Blvd., Los Angeles, Calif.	Gillfillan
Grand Rapids Radio Mfg. Co.	Grand Rapids, Mich.	Gypsy
Graybar Elec. Co., Inc.	Graybar Bldg., New York City	Graybar
Grebe, A. H., & Co., Inc.	70 Van Wyck Blvd., Richmond Hill, N. Y.	Grebe
Grigsby-Grunow Co.	5801 Dickens Ave., Chicago	Majestic
Gulbransen Co.	816 N. Kedzie Ave., Chicago	Gulbransen
Halsen Radio Mfg. Corp.	49 Lispenard St., New York City	Halsen
Herbert H. Horn	1629 S. Hill St., Los Angeles, Calif.	Tiffany-Tone
Howard Radio Co.	South Haven, Mich.	Howard
Insuline Corp. of America	27 Park Pl., New York City	Envoy
International All-Wave Corp.	510—6th Ave., New York City	Duo
Jackson-Bell Co.	5600 McKinley Ave., Los Angeles, Calif.	Jackson-Bell
Jackson Research Lab.	Malden, Mass.	Jackson
Kacemper-Barrett Corp.	871 Folsom St., San Francisco, Calif.	Radiette Troubadour
Keller-Fuller Mfg. Co., Ltd.	1573 W. Jefferson, Los Angeles, Calif.	Radiette
Kennedy, Colin B., Corp.	South Bend, Ind.	Kennedy
Kolster Radio Corp.	67 Broad St., New York City	Kolster
Leutz, C. R., Inc.	2700 Industrial Ave., Altoona, Pa.	Leutz
Lincoln Radio Corp.	329 S. Wood St., Chicago	Lincoln
Los Angeles Radio Mfg. Co.	3683 S. San Pedro St., Los Angeles, Calif.	Los Angeles
Midwest Radio Corp.	909 Broadway, Cincinnati, Ohio	Midwest
Minerva Radio Co.	10 N. Clark St., Chicago	Minerva
Mission Bell Radio Co.	1125 Wall St., Los Angeles, Calif.	Mission Bell
National Co., Inc.	Malden, Mass.	National
Ozarka, Inc.	1257 Fullerton Ave., Chicago	Ozarka, Viking
Patent Dev. Co.	South Bend, Ind.	Wren
Patterson Radio Co.	239 S. Los Angeles St., Los Angeles	Patterson
Perry Products, Inc.	150 W. 22nd St., New York City	Perry
Philadelphia Storage Battery Co.	Ontario & C Sts., Philadelphia, Pa.	Philco
Pierce-Airo, Inc.	510—6th Ave., New York City	Dewald
Pilot Radio & Tube Corp.	Lawrence, Mass.	Pilot
Premier Elec. Co.	Grace & Ravenswood Ave., Chicago	Premier
Radio Mfgs. Corp.	3900 N. Claremont Ave., Chicago	
RCA Victor Co., Inc.	570 Lexington Ave., New York City	Radiola
Remler Co., Ltd.	2101 Bryant St., San Francisco, Calif.	Remler
Revere Mfg. Co.	Mansfield, O.	Revere
Royal Radio Mfg. Co.	2482 University Ave., St. Paul, Minn.	Royal
Savil Mfg. Co.	73 Grand St., New York City	Savil
Scott, E. H., Radio Lab.	4150 Ravenswood Ave., Chicago	Scott
Service Elec. Co., Ltd.	Indianapolis, Ind.	Service
Silver-Marshall, Inc.	6401 W. 65th St., Chicago	Silver-Marshall
Simplex Radio Co.	Monroe & King Sts., Sandusky, Ohio	Simplex
Sparks-Withington Co.	Jackson, Mich.	Sparton
Steinite Mfg. Co.	Ft. Wayne, Ind.	Steinite
Sterling Mfg. Co.	2831 Prospect Ave., Cleveland, Ohio	Sterling Concertone
Stewart-Warner Corp.	1824 Diversey Pkwy., Chicago	Stewart-Warner
Story & Clark Radio Corp.	173 N. Michigan Ave., Chicago	Story & Clark
Stromberg-Carlson Tel. Mfg. Co.	Rochester, N. Y.	Stromberg-Carlson
Transformer Corp. of America	Keeler & Ogden Ave., Chicago	Clarion
Trav-Ler Mfg. Co.	1818 Washington Blvd., St. Louis	Trav-Ler
Trojan Factories, Ltd.	5862 S. Hoover St., Los Angeles, Calif.	Trojan
United Air Cleaner Corp.	9705 Cottage Grove Ave., Chicago	Sentinel
United American Bosch Corp.	Springfield, Mass.	Bosch
Universal Auto-Radio Corp.	1223 S. Michigan Ave., Chicago	Universal
U. S. Radio & Television Co.	Marion, Ind.	Apex, Gloritone
Waltham Radio Corp., Ltd.	4228 S. Vermont Ave., Los Angeles	Waltham Utility
Ware Mfg. Co.	480 Lexington Ave., New York City	Ware
Westinghouse Elec. & Mfg.	150 Broadway, New York City	Westinghouse
Zenith Radio Corp.	3620 Iron St., Chicago	Zenette, Zenith

NEW PRODUCTS FOR THE TRADE

Motomaster Superheterodyne

Motomaster announces its 1932 seven tube superheterodyne autoradio, which it states has the efficiency of a nine tube set, built on a shock-proof Eraydo chassis, using a special alloy container to completely protect and shield its parts, eliminating motor interference and insuring continuous perfect performance.

The Motomaster superheterodyne has three multi-mu 235s, two screen grid 224s, one 227, and one 247 pentode. They state for the first time a

automatic volume control to eliminate surging, fading and broadcasting inequalities.

The electro-dynamic speaker, designed for the Motomaster superheterodyne, synchronizes perfectly with the output of the receiver. The mounting is simplicity itself, requiring one hole for center mounting or three holes for side mounting.

The remote control with lock-switch and key is mounted on the steering column to give maximum accessibility. The station selector is electrically illuminated and, with the manual volume control, is encased in a silvery, chromium-plated housing. This affords finger tip control of station selection and volume.

235, or variable mu tube, in the radio frequency circuit. The second detector is a 224 tube with a 247, or pentode tube, in the audio circuit, greatly increasing the performance through its ability to perform the work of practically three tubes. A full wave 280 rectifying tube completes the tube complement.


The manufacturer states ease in tuning is obtained through use of a vernier drive on the tuning dial, which is of the arc type, while complete volume control is obtained through a combination volume control which controls the amplification of the receiver as well as the input to the antenna circuit. By this method, overloading is prevented if the set is used near a powerful station. The off-and-on switch is operated by the volume control knob, a slight turn to the right switching on the current and placing the volume control in position ready for operation. The 6-inch speaker is of the dynamic type and is matched to the receiver and cabinet to give the maximum range of reproduction.

The "Little Corporal" is housed in a walnut-finished cabinet, outlined with an ebonized pattern. The dial is in the center, flanked on either side by the tuning and volume control knobs, and set off with a rosette pattern. With a height of only 15 inches, a width of 11 inches and a depth of 8 inches, the Little Corporal may be moved easily from place to place.

Motor Radio Suppressor Kits

Electrical noises generated by the electrical system of the automobile and interfering with the enjoyment of the automobile radio set may now be eliminated by the installation of a kit of I. R. C. units for installation in the spark plug leads and in the main distributor lead, together with comprehensive and complete directions on the use of filter condensers and the proper adjustment of the electrical compo-

(Continued on next page)

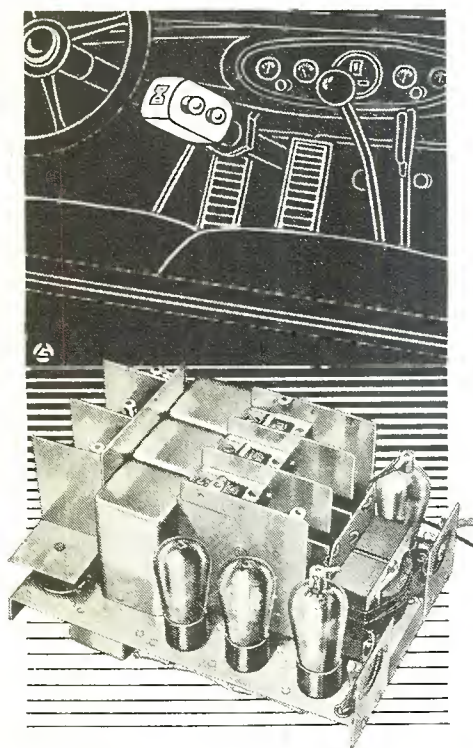


superheterodyne has been developed to perform satisfactorily in automobiles, giving coast to coast reception, with an ample reserve of power, and ten kilocycle selectivity and tone quality to surpass the average home set in performance, including a newly perfected

General Motors Little Corporal

A six-tube superheterodyne receiver, priced at \$39.50, has been announced by the General Motors Radio Corp., Dayton, Ohio. The new receiver is known as the Little Corporal.

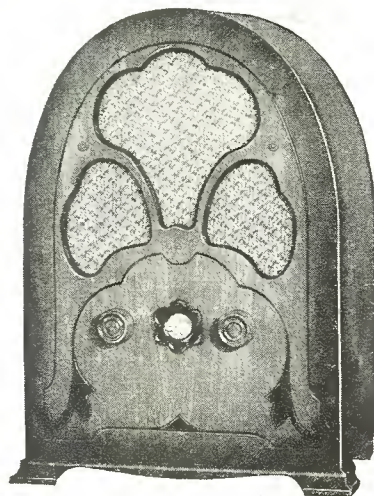Both the new variable mu and the pentode tubes are used in this new set.



A 224 tube is used as the first detector with a 227 as an oscillator and a

nents for complete noise elimination. The directions are complete in folder form for the service man. The kits are available for four, six, and eight cylinder automobiles, with resistors packed in a carton. Individual suppressors are available if desired.



In meeting the requirements of motor radio suppressors, the engineers of the International Resistance Co., Philadelphia, Pa., have developed units to fit most makes of cars. These units are moisture-proof because of impregnation with a special compound. They are shock-proof, with terminals designed to withstand severe vibration. The resistor is imbedded in a high-grade ceramic tubing which is unaffected by heat and non-combustible. The units have an exceptionally low capacity, less than 1/2 mfd, permitting the choking out of ultra short waves and eliminating all spark plug noise. They make positive contact and have a long service life.

Dubilier Dry Type Electrolytic Filter Condensers

A line of Dubilier dry type electrolytic filter condensers is announced by the Dubilier Condenser Corp., New York City. These condensers, in paraffined cardboard containers, are available in the standard capacities, 4, 6, 8, 10 and 12 mfd, and for peak voltages up to 430, according to the conservative Dubilier rating. They will withstand 500 volts without appreciable deterioration. When supplied with wire leads, the red wire is the anode or positive while the black wire is the cathode or negative.


The new Dubilier electrolytic condensers aim at providing high capacity values with ample working voltage for the usual filter function in an a-c radio set. They may be substituted for the usual aluminum can type electrolytic condenser, effecting a saving

in cost while at the same time permitting compact condenser blocks to be assembled with a number of these cardboard container units.



Stromberg-Carlson New Telektor System

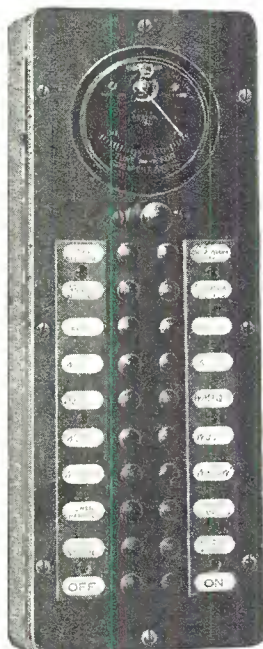The Stromberg-Carlson Tel. Mfg. Co., backed by 37 years in the manufacture of telephone transmitting and receiving apparatus, has presented a new Telektor System (residence type electrical remote control system), which gives complete remote control of both radio and records.



By push buttons in a small control box, one may, from any part of the house, start or stop a radio receiver, start or stop a multi-record phonograph at the same time switching from

radio to phonograph, or vice versa, tune silently and automatically to any eight stations, tune silently and visually to other stations, adjust volume, adjust phonograph volume, switch four loud speakers on or off, switch off radio, loud speakers and phonograph by one button.

The new system is composed of radio, phonograph units in separate console cabinets, or in combination cabinets; or one or both may be concealed from view. With the provision of complete remote control of an entire system, the radio receiver loses its claim to a place in the living room and may be relegated to any dry place in the attic, basement, garage or a convenient closet or cupboard.

The Telektor control boxes are equipped with ten foot or thirty foot flexible cords. The portable type is 10 inches by 3 3/4 inches by 2 1/2 inches in size, made of walnut, with walnut finished formica top, and weighs about a pound. Control boxes for mounting flush in walls can also be had.

A Stromberg-Carlson Telektor installed on Stromberg-Carlson receivers Nos. 12, 22, 27 and the No. 14 multi-record radio, if the No. 14 is equipped with phonograph relay, will operate simultaneously four dynamic speakers, or sixty magnetic (cone) speakers, or two dynamic in combination with 20 magnetic speakers. A power amplifier may be provided when more speakers are required. The system may readily be installed in old houses as well as those under construction, and requires a minimum of conduit wiring. All Telektor circuits operate at approximately 25 volts a-c, which is classed in the same category as door-bell wiring.

New Condenser Microphone

Shure Bros. Co., 337 W. Madison St., Chicago, Ill., announce their model 44 condenser microphone.



The manufacturers state that this instrument is designed to meet the most exacting requirements for high
(Continued on next page)


NEW PRODUCTS ITEMS

Manufacturers who have items that come within the scope of this department will find it of advantage to keep our name on their mailing list for announcements of new products. Half-tones or electros should not exceed 2 1/4 inches in width. Address—New Products Editor, care this magazine.

quality radio broadcasting, sound recording, and sound measurement tests, and its outstanding characteristic is its relatively uniform response to all frequencies from 40 to 10,000 cycles. In the special design of its amplifier are combined the advantages of high output level with extreme wealth of richness in tone quality. Its reproduction is so realistic as to make it difficult for even the trained ear to discern the use of the instrument between the original source of sound and the listening ear.

Balkeitt Model L-7

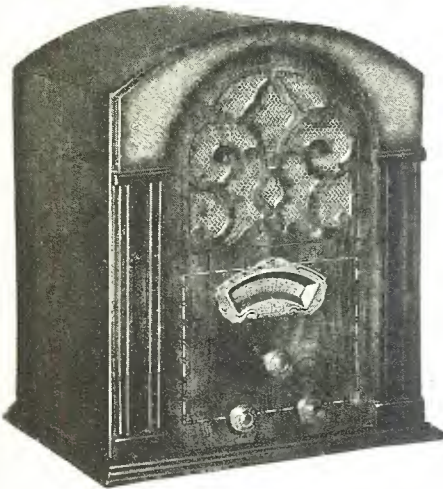
The Balkeitt Radio Co., North Chicago, Ill., announce their model L-7, being licensed by RCA and Hazeltine.



The cabinet is made of walnut with full vision illuminated dial. Height 18 inches, width 15½ inches, depth 10½ inches. This model uses two variable Mu type 235, two 224, one 227, one 247, and one 280 tubes.

The manufacturers state that this receiver uses a full size dynamic speaker, equipped with special hum bucking coil to reduce hum to a minimum. Shipping weight 34 pounds.

RCA-Victor Ten Tube Super

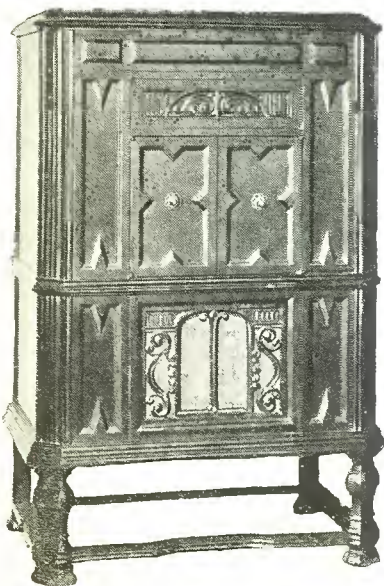

RCA Victor Corp., Inc., announces their model RAE-59, which is a ten tube superheterodyne with radio-phonograph combination. Equipped with totally shielded chassis, automatic volume control, micro tone control, low impedance pickup and inertia-type tone arm. Provided with the device for playing long-playing records, home recording with studio microphone, and automatic record changing. Chassis rubber-floated in beautiful walnut cabinet. Dimensions: height 46 inches; width 29¾ inches; depth 19¼ inches. Uses 2 RCA-247, 1 UX-280, 1 UY-224, 3 UY-227, 3 RCA-235 Radiotrons.

Sentinel Perfects 5 Tube Super

A unique detector-oscillator system which operates equally well over the entire broadcast range, which is trouble-proof and non-critical, and which does not require specially selected tubes, is incorporated in the Sentinel 116 five-tube superheterodyne radio receiving set recently developed and placed on the market by the United Air Cleaner Corp., 9705 Cottage Grove Ave., Chicago, Ill. This detector-oscillator system, together with the fact that there is a total of seven tuned circuits, gives a standard of performance which surpasses that of the ordinary seven tube superheterodyne receiver.



The new Sentinel 116 five-tube superheterodyne is housed in an attractive table model cabinet made of selected walnut with simple design and pleasing lines. The cabinet measures 15¾ inches high, 13¼ inches wide, and 8 inches deep.

Buss Radio Fuses

The Bussmann Mfg. Co. of St. Louis, makers of Buss fuses and Buss lights, announce a new radio fuse assortment, copying a similar step taken by the Bussmann Co. in the automobile fuse field in 1926, when fuses were packed in a metal box on which educational fuse information was printed.

"For years fuses were sold to automobile owners by dealers just to oblige them," an official of the company stated in announcing the new line, until the Bussmann company presented this item in a way to make it a staple




in any garage, hardware or service store. We furnished the dealer and service man with an attractive stand in which to store his stock and packed fuses five in a metal box for the convenience of the car owner. Since that time, spare automobile fuses have become almost as important in the tool kit as the jack and tire tools. The purpose of the radio fuse assortment is to supply the radio dealer and the independent service man with an assortment of fuses which will service various makes of radios as well as to provide a counter display which will increase the sale of fuses to the home mechanic who likes to service his own set."

The announcement sets forth that the radio service man who carries the assortment will always have the correct fuse in his tool kit, and that the individual user may prevent the loss of an evening's entertainment by having a spare box of fuses on hand at his home.

New Jewell Oscillator

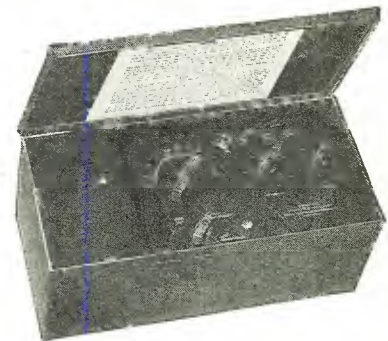A new radio service oscillator, the pattern 563, has just been announced by the Jewell Electrical Instrument Co., 1650 Walnut St., Chicago, Ill.



This instrument employs one '30 type tube operated from self-contained batteries, in a self-modulated circuit. The output is continuously variable over three frequency ranges: 550 to 1500 kc, 125 to 185 kc, and 175 to 450 kc. These ranges provide for the adjustment of radio frequency circuits in all modern radio frequency and superheterodyne receivers.

BRIEF ITEMS OF INTEREST TO MANY

ERRATA—We are sorry that an error occurred in our January, 1932, issue, page 20, on the General Motors S-9A. The sensitivity as given is 50.3 microvolts absolute corresponding to 12.56 microvolts and should read 30.2 absolute, which is equivalent to 7.55 microvolts per meter.

Fred Haddock, Texon, Tex.: Find enclosed check for your magazine and Radio Service Schematics. I am a dealer here in Texon and I like your magazine the best of all the radio publications, as you have the radio tests and schematics which I believe are very instructive for radio men.

Victor McBeth, Spalding, Nebr.: Which is the best form of short wave set: super converter, a-c short wave t-r-f, a-c short wave superheterodyne or d-c? Would like to have a good one. I tried one but did not get very good results. Ans. We believe the best results are obtained in short wave reception, which is exclusively short wave, by the new combination short wave broadcast superheterodyne now on the market and entirely satisfactory. Otherwise we suggest a converter in preference to an adapter. Probably there will be a little less noise and local disturbance if a d-c job is used, but there always remains the inconvenience of batteries.

D. V. Fuller, Butte, Nebr.: I am interested in purchasing some new radio testing equipment and I notice in the last issue of Popular Mechanics a diagram for a vacuum tube voltmeter using a 0-200 microammeter. I wish to buy a Jewell oscillator, and in fact have ordered it without an output meter, pending my decision as to whether I decide on the output meter or a vacuum tube voltmeter. What I wish to know is whether the vacuum tube voltmeter would be as easy to use for the same purposes as the output meter? I would also like to know if it is practical to add automatic volume control to sets that do not have it. Ans. For accuracy we would recommend the vacuum tube voltmeter, but such an instrument is delicate, fragile and requires at least one battery for operation. It is primarily a laboratory instrument and is too sensitive for making a service alignment of a receiver. If you wish to have an instrument which is rugged, reasonably accurate and very good for alignment purposes, there is no question but what the rectifier type voltmeter, which is of very good sensitivity, is the proper instrument to use. You will find in our Brief Items columns of a previous issue that we do not recommend anyone attempting to add automatic volume control to a receiver which is not so equipped, because of the many difficulties which will be experienced and the redesigning necessary.

S. M. Lockwood, Chicago, Ill.: I wish to compliment you on your new monthly, which is just what the service man needs to help him along. The articles on Multi Range Meters certainly came along in good time. I was running around in circles and getting nowhere until you were kind enough to light the way. At the present I am badly in need of a tube tester that will give fairly reliable service every day, but owing to the present prices I have hesitated in buying. Can you supply me with constructional data for a tube tester that will not cost me too much? Any help will be appreciated. Ans. We wish to thank you for your kind words and hope that we may continue to serve our readers with valuable information and service
(Continued on next page)

WHAT IS RCA INSTITUTES?



... and what can it offer you in RADIO?

HERE are a few quick facts about RCA Institutes: It is America's oldest radio training school. It offers complete elementary and advanced instruction in practical radio. It is not a one man school. On the contrary, this organization is composed of a number of well trained men. Each is a specialist in his own field. Added to their knowledge are the benefits of association with the largest research laboratory in the radio industry. Yet tuition costs are moderate.

There are four resident schools, in New York, Boston, Philadelphia and Chicago. In addition, we offer extension courses for home study. Special laboratory equipment is available in many courses.

More than 20,000 men have graduated. Many of them now hold positions of responsibility in radio and its allied fields.

If you like radio, and would like to get into it, it will pay you to find out more about RCA Institutes. So mark and mail the coupon NOW... before you forget.

A Radio Corporation of
America Subsidiary

	RCA INSTITUTES, INC. Dept. RC-3, New York 75 Varick St.
	Please send me your General Catalog. I am checking below the phase of radio in which I am interested.
<input type="checkbox"/> Microphone Technique	<input type="checkbox"/> Talking Pictures
<input type="checkbox"/> Aviation Radio	<input type="checkbox"/> Disc and Film Recording
<input type="checkbox"/> Broadcast Station or Studio	<input type="checkbox"/> Television
<input type="checkbox"/> Servicing Home Entertainment Equipment	
Name.....	
Address.....	
Occupation.....	Age.....



STOP kicking DOLLARS in the FACE ..

WHEN you look on your Service Department as a necessary "nuisance" you are kicking dollars in the face.


Stop fooling yourself!

Service work is the source of substantial PROFIT to organizations that take it *seriously*.

Your Service Department is a BUSINESS WITHIN A BUSINESS—and it is a business which is growing rapidly and profitably for service men who make their replacements with time and money-saving ELECTRAD QUALITY Resistors and Voltage Controls.



ELECTRAD
TRUVOLT
RESISTOR

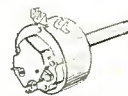

ELECTRAD
VOLUME
CONTROL

Mail Coupon for Literature

175 Varick St., New York, N.Y.
ELECTRAD
INC.

Please send me complete TRUVOLT literature and special replacement volume control slides.
Name.....
Address.....
City.....

CB-3

A new training FOR RADIO MEN!



To make real money in radio requires **KNOWLEDGE!** There is no substitute for it—not even practical experience. Our new advanced training is ideally suited for the experienced radio man who wants to equip himself for more important work.

Endorsed by Leaders

Our institute is highly recommended by Radio Service Managers Assn., Howard Radio, American Radio Relay League, etc. Thousands of students testify to our home study methods of instruction in basic radio engineering. That is because we teach the "WHY" of radio—the fundamental principles of radio theory.


Write for Booklet

Send for the details of our training. Absolutely free of charge or obligation. But don't put it off—do it now—while you have the time. State whether you are interested in Radio or Television. (Don't write if you have not had at least 2 years radio experience.)

CAPITOL RADIO ENGINEERING INSTITUTE

14th St. & Park Road, N. W.
(Dept. C-14)
Washington, D. C.

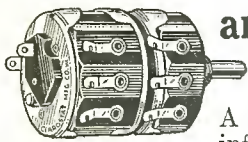
CLAROSTAT CONTROL HANDBOOK and CATALOG for 1932 FREE!



A real handbook of radio and sound information—A handbook for the Manufacturer, Distributor, Dealer, Serviceman and Experimenter. Many circuits explained including Volume Control, Tone Control, Voltage Regulation, Television, etc. Here is a book for constant reference.

Write for the "Clarostat Control Handbook" and mention this magazine—No Charge, of course.

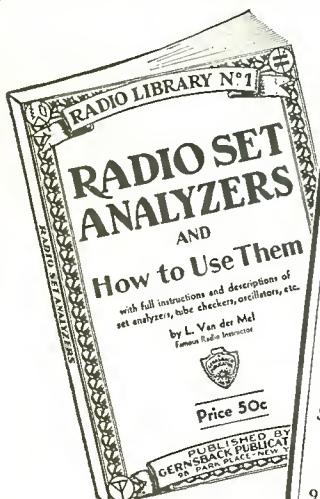CLAROSTAT MFG. CO., Inc.
285 North 6th St. Brooklyn, N. Y.



Makes Radio Set Servicing EASIER!

If you are a Service Man, or intend becoming one, this new book telling how to use radio testing equipment is absolutely invaluable to you. It covers every phase of testing, and gives you the information which you have been looking for. It contains complete descriptions and hookups of every important analyzer on the market. Completely illustrated with photographs, diagrams, hookups, tables and charts.

64 Pages—6 x 9 Inches—Over 50 Illustrations.
Send for your copy today. Price Prepaid 50c.

Gernsback Publications, Inc.
96B Park Place New York, N. Y.

Brief Items Continued

data. You will find what you desire, we believe, on page 30 of the January issue, where ways and means are given for measuring all of the essential characteristics of vacuum tubes.

H. W. Shannon, Soledad, Calif.: In reading over your new monthly addition I notice in Brief Items different comments from interested subscribers. It has long been my contention that four issues of your magazine per year was not enough, more so now in view of the fact that new models and new ideas are being produced on short notice. I have always felt that your Review is the best for these reasons: clear and explicit hook-ups and schematics, accurate and importance values and data are always shown in your testing, your experimental schematics and manufacturers' schematics. We all know these agencies furnish necessary data to their own service men and we find your publication of help to the independents. Your receiver performance and curve section is the most important in your magazine and it should be used by all service men after working over sets before delivering to the customer. You left out one necessary page in your call section and that is stations listed by cities and states. Please put this back. There is also one more important section which should be included in your Review, and that is all available data and schematics pertaining to elimination of interference in antenna and a-c lines. Your schematics, if kept by subscribers, will eliminate the necessity of going to the expense of purchasing large and cumbersome books. If the Call Book magazines are filed properly and an index is kept by the subscriber showing the contents of each of your issues in one separate note-book, by writing down contents of each issue, I find that one automatically seems to remember just where to look up information when he wants it. Your New Products section will become more important now that it is issued monthly. Also because of the fact that you print statements regarding these articles, can be relied upon. This also applies to your paid advertisers, as we have come to look upon your magazine as our reliable purchasing agent. By cutting out unimportant reading you have given us a quicker reference guide with which no other publication can compete. One thing before I close, and that is I wish you would show the correct voltage at the sockets in chart form. Remember that the experimenter comes first, as I stated in the first part of my letter regarding commercial data. Ans. We wish to thank you for your kind words and thoughtful suggestions in your letter. We appreciate a boost now and then from our subscribers. You will find in this issue the inauguration of the receiver voltage charts published in each issue whenever we can get them. Also we shall publish the charts for receivers which are appearing in all of our monthly issues.

V. H. Herndon, Odon, Ind.: You know once in a while you are forced to boil over whether you want to or not, and after reading your Brief Items of Interest to Many in the January issue, I could not stay put any longer. These apple knockers get my goat, so here I go to quote on. "After having reexamined the December issue I find that it does consist of the following: 16 pages of advertising, 9 pages of station calls, 13 pages of performance and 1 page of contents, also 9 pages of reading matter and worth every cent I gave for it, and not even you could improve it if you tried. I know what I am talking about because I received the first number of the General Radio Experimenter in 1924 and still have it, as I do the last number they put out. I also have all the Call Books from Vol. 6, No. 1, to the present, every issue of Radio Craft, 60 issues of Radio, 74 issues of QST, 90 issues of Radio

(Continued on next page)

Brief Items Continued

News, Radio World every week for ten years and the following until they signed off: Radio in the Home, Radio Mechanics, Radio Digest while a weekly, Radio Review, and Radio Listeners' Guide and Call Book, and other manuals. I want to say that I have received a lot of good reading in the Call Book, and also that it has always gone forward and never back and still remains in a class by itself, and in view of the fact that I have taken, read and still possess the above publications, I will leave it to you as to whether or not I have the right to be judge. So just go ahead as you are, for your curves are great and I sold the first super sold in this town through your curves and my explanation."


Roger D. Spencer, Middlefield, Conn.: I have been reading one of the criticisms you received, but we all get that. Some people don't believe that service men read your paper and are not interested in curves, but wanted something to read. I always look forward to getting your magazine and always find good dope in it. I am not particularly interested in curves, as I consider actual reception conditions vary receiver performance a great deal. For instance, we have one location in town where you can get nearly anything you want, while farther down in the country it takes a long aerial to get anywhere near normal volume on reception. Quite often I find a set with a partial short in it, which will reduce the voltage on the output of the 280 tube 50 to 100 volts, making the set weak and causing excess heating. Often the short is insufficient to blow the fuse, if the receiver is equipped with one. Did you ever have one of the Atwater-Kent 55 sets which caused trouble by a reduction in volume? I had this and searched all over and could not find anything which varied until I looked in the first audio bias resistor, which is a flat wire-wound resistor, one end of which is grounded. This resistor had been dipped and never cleaned. Another cause of variation in volume is a dirty local-distance switch on some receivers. Some of the Grebe SK-4 receivers which faded were troubled with a defective local-distance switch.

Carl Roemer, Lakewood, Ohio: I have a set of superheterodyne intermediate transformers which are peaked at 37.3 ke, using a .0075 fixed condenser, and I wish to know if these may be peaked at 175 ke and, if so, what capacity condenser to use. Ans. The calculations show the inductance of these coils to be 2.39 millihenrys. Therefore, the required capacity will be in the neighborhood of .00034.

Harold Mantz, West Bend, Ia.: 1. In charging a 6 volt battery from the a-c line by means of a step-down transformer of 12 volts output and a rectifier, is this too much for a 6 volt battery? 2. I have a 6 to 12 volt dynamic speaker and would like to use this step-down transformer along with a rectifier to furnish field excitation. Would it be satisfactory? 3. With item 2 I should probably need a condenser to filter out hum. What would you suggest? 4. Should the rectifier be rated at 2½ amperes and would one of 3 amperes capacity be better? I am asking you these questions because I know the answers I get will be reliable. Ans. A transformer having 12 volts output on a suitable rectifier is perfectly satisfactory on a 6 volt storage battery. Since your dynamic speaker is rated from 6 to 12 volts, such a rectifier may be used. It is always advisable to use a high capacity low voltage electrolytic condenser for filtration, and we suggest one with a value in the neighborhood of 2500 to 3000 mfd. The best results will be obtained from the rectifier of highest rating because of the prolonged life.


(Continued on next page)

for SUPERHETERODYNE SERVICING

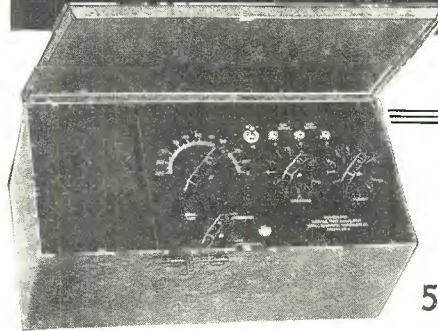

**Jewell
563 Oscillator**

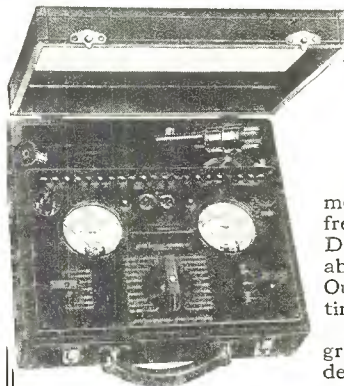1. Output adjustable to any frequency in the three bands by means of fundamental waves: broadcast 550-1,500; low intermediate 125-175; and high intermediate 160-280 K. C.
2. Calibration curve for each range carried in the cover.
3. Entire instrument, including self-contained batteries, is shielded by the metal case.
4. Jewell traditional sturdy construction assures long-lived dependability.
5. Priced remarkably low for a quality instrument.



**Jewell
444 Set Analyzer**

Makes every necessary test on all modern radio receivers—tuned radio frequency and superheterodyne. Direct tests are provided for variable-mu and output pentode circuits. Output measuring and resistance continuity ranges are provided.

Simplicity of operation allows greater speed in servicing. Careful design and sturdy construction assure results that can be depended upon.

Many unusual features are embodied that give greatly increased durability—non-shatterable meter glasses, panel and over fifty other parts of molded bakelite, test cord and plug detachable at analyzer panel, and others. Write for complete description of this remarkable instrument.

**Get This
Catalog**



Jewell Electrical Instrument Company,
1642-G Walnut St., Chicago, Illinois

Please send me the new Jewell Service Instrument Catalog.

Name.....

Address.....

City.....State.....



It's FREE

this story of Centralab Fixed Resistors

THOUSANDS of copies have already been distributed to servicemen, amateurs and engineers. Get your copy now; and this well-illustrated, informative booklet is free for the asking. Use the coupon today.

NOTE: Effective January 1st, 1932, new low price on Centralab Volume Controls now make these REPLACEMENT UNITS more popular than ever.

Centralab

CENTRAL RADIO LABORATORIES

MAIL COUPON TODAY

CENTRAL RADIO LAB.

Keefe Ave. and Humboldt, Milwaukee, Wis.

Please send me your free booklet on Fixed Resistors.

Name

Address

City..... State.....

C. R. C. B.

DO 'T MISS THESE BARGAINS!!!

and many more items not listed

Radio Receptor Portable Amplifier—complete with: single button mike, 1—280, 1—247, 1—227, 1 dry cell, dynamic speaker, A. C. operated—new... Special \$47.50

International 1 watt pig-tail metallized resistors—new.....16c
International 2 watt pig-tail metallized resistors—new.....22c
Condensers 1 mfd. 750 D.C. working voltage, card board cased.....65c
Condensers 1 mfd. 1000 D.C. working voltage, card board cased.....75c
Uncased Condensers, 1000 D.C. working voltages: 1 mfd. 49c; 1 1/4 mfd. 55c; 1 1/2 mfd. 59c; 2 mfd. 65c; 3 mfd. 80c
Metal cased condensers, black Jap. painted—1 mfd. 600 D.C. working voltage.....50c
CeCo 866 Tubes, RCA licensed, 6 months guaranteed.....\$3.65

New National S.W.3 and S.W.5—A.C. or D.C. and any other National product in stock—Lowest Prices!

We also stock: Flechtheim, Cardwell, Siemens & Halske, R.E.L., New DeForest, RCA and Cunningham tubes, Thordarson, Dongan, Weston and other nationally advertised products for Servicemen and Amateurs.

WRITE FOR PRICES. OUR PRICES ARE ALWAYS THE LOWEST!!

All parts Doubly Guaranteed! No order too small for us to ship. We ship to any part of the World. 20% deposit with orders—include postage. Open evenings! (Say you saw it in the Radio Call Book.)

"If It's Radio—We Have It"

**Maurice Schwartz & Son 710-712 Broadway
Schenectady, N. Y.**

AUDIOLA

KNOWN FOR ITS TONE

HIGH GRADE SET BUILDERS SINCE 1921

AUDIOLA RADIO CO. 430 S. Green St.
Chicago, Ill.

Brief Items Continued

Synthane Corp., Oaks, Pa., manufacturers of Synthane laminated bakelite, have prepared a valuable data chart on "Standards of Quality, Properties and Applications of Laminated Phenolic Sheets." Copies may be secured free by addressing Synthane Corp.

H. B. Duncan, Wilmington, Del.: I have noted with great interest your article on page 38 of the January, 1932, issue regarding a special type of aerial installation to mitigate electrical interference. However, the size of the transformer given as a 3 inch diameter tube seems too large. Could a smaller size be used? As a service man I would appreciate as many articles on construction and use of testing equipment as would be consistent with your program. Ans. Constants for the transformer need not be held to very close limits, but we suggest approximately 200 to 300 microhenrys inductance. If you have had the issues of the CALL BOOK beginning with October, at which time it became a monthly publication, you will find a very comprehensive library on equipment for service men.

Theo. P. Long, 210 W. Collins St., Oxford, Ohio, desires to buy either a 1/2 kw or 1 kw transformer and a rotary gap without a motor for his high school radio club.

Steven Grek, Chicago, Ill.: What causes a set to vibrate on certain stations? To make myself a little more clear, the program sounds as if it came over a tightly strung wire that was twanged continually as a harp. Ans. We presume you are having trouble with microphonism. Try changing the detector tube or, if necessary, mount the receiver on soft pads. Microphonism is caused by mechanical vibration of tube elements in the detector or audio stages. Many times it is brought about by the vibration of the plates of the gang condenser, especially if the plates are of thin material.

There seems to be some mistake about the price given in our last issue on letter-size blue print performance curves on any receivers so far run in the monthly issues. The price is 6c each, or 24c per set of four for a receiver.

O. M. Owen, Hastings, W. Va.: I have been a reader of your magazine for about nine years and have always looked forward to the next copy until recently. It does not contain the "thrill" such as was contained in the September, 1930, issue, in which you describe how to modernize a Victoreen superheterodyne. As an experimenter I am interested in such articles. When radio settles down to a cut and dried proposition, such as most magazines are now treating the subject, it will cease to be more than a drab subject. Imagine a magazine treating on pianos and phonographs. However, as a service man I do get some good from your publication, but the big interest factor is gone. A recent letter in your Brief Items columns describes the matter pretty thoroughly.

L. S. Lustie, Chicago, Ill.: Thanks for the past information shown by you. Your schematic wiring diagrams are the best. I have subscribed to all kinds of publications, but they seem to be afraid to show capacity and resistance values on their diagrams. The tube curves and characteristics in the January issue were fine, but please be a little careful because all of us are not mathematicians.

Electrad, Inc., 175 Varick St., New York, N. Y., has prepared a new resistor handbook. This book is 5 by 8 inches and designed to fit into the service man's pocket or kit. Supplements will be issued four times a year.

(Continued on next page)

Brief Items Continued

Electrad states: "The Resistor Replacement Handbook contains circuit diagrams, useful information and resistor values used in practically all models of all popular makes of radio receivers now on the market, as well as many obsolete models still in use, which you may be called on to service.

Single copies, \$1.00; in quantities of 6 or more, 75c each. Each subscription covers one year's service for 1932, consisting of first edition and four 1932 supplements.

D. V. Chambers, New York City: I am very pleased with the new order of things, the monthly issue and thereby more diagrams, since diagrams are the service man's standby. If a condenser or resistor becomes defective, how else would one find the value? If you would put the circuit diagrams on only one side of the page and the articles on the reverse side, it would simplify filing. As it is, it is necessary to compile an index, for I don't save the magazines but I do the diagrams, with some of the articles that I want, or put ads or anything on the reverse side.

R. F. Renuad, Syracuse, N. Y.: Your design of multi-range volt milliammeters and voltmeters is all very interesting and let's hope a future issue of your magazine will carry a design for utilizing the Weston universal a-c and d-c meter. The Brief Items columns are just what you have needed for a long time and I sincerely hope you continue to publish it.

Henry Schroeder, Whitehaven, Tenn.: I notice in your response curves you have a dotted line called "low 1000 kc." Does this curve refer to the fidelity when the tone control is turned to its maximum bass position? Ans. Yes, and 400 cycles is used as a reference point as usual.

Hammond Mathews, Silverton, Colo.: I am obliged to write you after having to use your CALL BOOK for the last three or four months and tell you where you have failed in part of it, with the sincere hope that you will see your way clear to bring out the next issues in 100% manner. Page 10 of the January issue is about useless, in that after one may gaze at any kilocycle number, he has to then spend a number of minutes in finding out where in heck "PONUTELL" is located. If you will do as the old issues did, you will have a better issue and certainly one which will be appreciated by the writer and thousands of others. Ans. There would be no difficulty, of course, in adding the wavelength in meters as was heretofore given, but in keeping with the trend of the times, which is ever for advancement, we have eliminated what we consider antiquated material. We have found that it does not require more than ten seconds to obtain the information you mention for any station. Other comments desired.

W. C. Edens, Magness, Ark.: We have a set which plays perfectly for a couple of hours, when it will suddenly break out with the most outlandish noise, similar to an a-c hum, only amplified a thousand times. Sometimes a sudden jar will start this noise, but usually it starts after an hour or two of operation with the set undisturbed. Ans. Your complaint is one of quite common occurrence and may be due to a defective tube, but more likely it is a condenser with a very bad leakage or a resistor which is not firmly fastened at its ends. Since a time interval is necessary to cause the noise, it is logical to assume that the heating of the chassis by the power transformer and tubes causes sufficient expansion to open some circuit at least partially.

(Continued on next page)

Are You Wondering How a WRIGHT-DeCOSTER Reproducer

Will Increase the Efficiency of Your Short Wave Receiver?

WE are constantly receiving letters from short wave enthusiasts telling of new stations which they have heard and how they are now getting increased volume and clarity on stations which were faint before they installed the Wright-DeCoster Model 217 Junior Chassis.

We can fit it to your present cabinet, or supply it in a beautiful table or console cabinet in A C or D C models.

Write for complete information
and address of nearest sales office.

WRIGHT-DeCOSTER, Inc.

2215 University Avenue


ST. PAUL

MINN.

Export Dept.

M. SIMONS & SON
25 Warren Street, New York

Cable Address:
Simontrice, New York

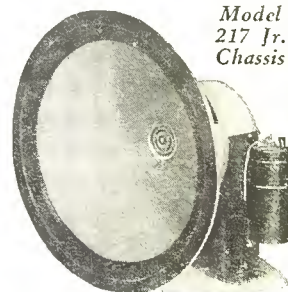

Model
217 Jr.
Chassis

The Speaker of the Year



The 15 TO 550 METER
COMET
SUPER-HETERODYNE

EUROPE, Asia, Africa, Australia, South America—at your fireside. It's the thrill of a lifetime with the new Hammarlund COMET Super-Heterodyne.

No adaptors, no converters, no make-shifts—but a superbly engineered receiver especially designed for all wave lengths between 15 and 550 meters.

A. C. operated, using eight newest type tubes. Super-sensitive — super-selective — super-fine, as Hammarlund Custom Built Radio always is.

The all-purpose receiver — for the home — office — laboratory — newspaper — police — airport — steamship. Write Dept. CB-3 for descriptive folder with list of world short-wave stations.

HAMMARLUND-ROBERTS, Inc.
424 W. 33rd St., New York

CUSTOM
BUILT

by **HAMMARLUND**



Money Making Information Servicing Superheterodynes

By JOHN F. RIDER


is the book the entire radio servicing industry has been awaiting for a long time. . . . This book will give you all of the superheterodyne service information you desire and need in order to service superhets at a profit.

Principles underlying the operation of superheterodynes—Explanation of different types of superhet circuits—Breakdown of the superheterodyne circuit and the function of the individual parts—Troubles and symptoms encountered in supers—short wave converters—Servicing superhets—application of RF and IF oscillators—application of set testers—peculiarities in superhets—Design of RF and IF oscillators—Everything about superhet servicing—Sold with a Money Back Guarantee—Type set—Bound in canvas cover—pocket size.

PRICE
\$1.00
Postpaid

PERPETUAL TROUBLE SHOOTERS MANUAL

By JOHN F. RIDER

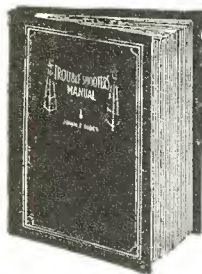


the only reliable and dependable reference manual furnishing wiring diagrams—chassis diagrams—voltage data—electrical values—color coding—etc. . . . 1000 pages of profitable service information—See it at your dealer. . . . If he does not carry it write us his name. . . . Sold with a Money Back Guarantee.

Price \$5.00 Postpaid

Send for descriptive literature covering both of these books

RADIO TREATISE CO., INC.
1440 BROADWAY NEW YORK CITY

ACROCYCLE \$17.50 OSCILLATOR

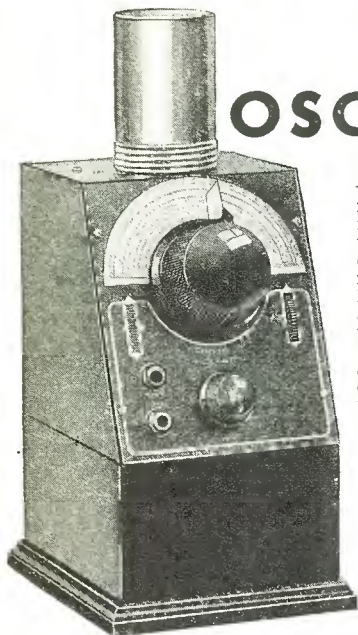

A SELF-CONTAINED, fully shielded oscillator, with full vision scale calibrated directly in Kilocycles—no charts used—micrometer slow motion dial—can be set at exactly any frequency from 115 to 1680 K.C. Uses four flashlight cells and one 22½ volt battery automatically connected when inserted. Uses one 30 tube self-modulated. Can be checked for accuracy when attached to any receiver by the "beat" method to within 20 cycles.

Dealer's Price—Oscillator with test leads \$17.50. Complete set of batteries and tube \$2.25 extra. Leatherette Carrying Case \$2.00 extra. If your jobber does not carry, order direct. Sent express collect or C.O.D. with a deposit of \$1.50. **Free circular.**

[[This instrument is made by the manufacturers of the "Submariner" Short Wave Adapter now priced at \$12.50. The first adapter on the market built since 1926.]]

ORDER TODAY!

J-M-P MANUFACTURING CO. INC.

(Established 1922)

3002—No. 34th St.

Milwaukee, Wisconsin, U. S. A.

Brief Items Continued

Jas. A. Robinson, Methuen, Mass.: Keep up the schematics, but add values of resistors and condensers. Cut response curves smaller and put in voltage charts of tube voltages. Service men appreciate your efforts. Ans. Every schematic we publish has all the values of resistors and condensers which are available from the manufacturers. You will find in this issue the inauguration of the publication of 12 voltage analysis charts, which will be continued from this time on.

Jack Bender, Evansville, Ind.: It is gratifying to note that there is one organization in the field of engineering that can be depended upon for reports on modern radio equipment. Hence, we do not have to depend upon the biased (probably) measurements made by some manufacturers of today. Also many times they are very misleading in their assertions as to the performance of their products. It is too bad that some of these manufacturers cannot see the futility in building such things as signal generators without having them carefully rechecked at such places as the Bureau of Standards or at *Radio Call Book Magazine's* laboratory. The engineers of such plants take for granted that they are equipped with sufficient knowledge and data to build test equipment equal to that of men who have specialized in nothing else for many years. The word "almost" expresses the whole theme of this letter, for one slight mistake in strays or leakage will cause much grief when it comes to a problem of mass production.

Radio Service Laboratories, formerly located at 440 S. Dearborn St., Chicago, Ill., are now at Clinton, Ia., in their own factory.

Jos. Daniel, New York City: I appreciate the monthly publication of your interesting radio magazine. I am glad that you have changed it from a quarterly and I am certainly a satisfied subscriber. In the January issue the article on page 33 is very interesting to read. Ans. We are happy to learn from your letter that you found the article on page 33 of benefit and we hope that each succeeding issue will prove of more value to our readers. With reference to your suggestion on the wave trap, we are always glad to review ideas and write-ups on equipment which are sent in to us.

Harry E. Edsal, Bellefontaine, Ohio: In your *Radio Call Book Magazine and Technical Review* there was an article describing the Scott All-Wave Model 31, a superheterodyne all-wave receiver. In one of the paragraphs you used symbols uh and uuf. These are strange to me and I wish that you would enlighten me since none of my technical books use these representative letters. Ans. The symbol u is the closest approach in Arabic to mu, which stands for one millionth. Therefore, uh represents microhenrys or millionths of a henry, uf represents microfarads or millionths of a farad, and uuf represents micromicrofarads, trillionths of a farad or millionths of microfarads. You have probably seen the latter term abbreviated mmfd.

RMA Television Notes

WORKING toward early and orderly development of television, recommendations of television frequency assignments and engineering standards are being made by the Radio Manufacturers Association to the Federal Radio Commission for consideration at the International Communications Conference next May in Madrid. The engineering proposals were drafted at a recent meeting of the RMA Television Committee of which Mr. D. E. Replogle of Newark, N. J., is chairman, and are being transmitted to the Radio Commission at Washington by Dr. C. E. Brigham, Chief of the RMA Engineering Division.

Chairman Replogle has issued the following summary of the television engineering proposals:

From data secured it is apparent that the present television wave length assignments are inadequate to give satisfactory television broadcasting service;

1st—Because of interference between stations at distant points.

2nd—Because of phantom images and fading sent up by reflections of television signals from the heavy side layer. These reflections arrive at a different time from the ground wave of the transmitting station which causes several images to appear and shift back and forth except in areas close to the broadcasting stations. These are quite annoying and entirely upset the detail of the received pictures when present.

3rd—The narrow channels of 100 kc, while wide in comparison with voice channels, are still too narrow to permit satisfactory picture transmission.

4th—In the spectrum assigned to television there are too few channels to assign to sufficient television stations to adequately supply one city without considering the many cities that will want service. This has become quite apparent and there has been a definite surge for other channels in the ether not now occupied that can be used for television.

“This search for new channels during the past year has brought to light sufficient data to make necessary the calling of a special meeting of the RMA Television Section of the General Standards Committee to consider the request for television bands that can be expected to meet requirements in this art for the next five years. It was necessary to make these requirements at this time because of the start of the International Radio Conference in Madrid, Spain, next spring which will set the various international radio channels for the next five years.”

Here's the New HANDY KIT that gives all the values you want WITH 20 RESISTORS



With this Certified Kit in your pocket, you can take care of any resistor problem in any radio set. For besides the 20 most popular values in the kit, you can obtain thousands of others by using the simple formulas that go with it. Here are the ranges in the kit:—

500 ohms	25,000 ohms	200,000 ohms
1,000 "	50,000 "	1/4 meg.
2,000 "	60,000 "	1/2 "
5,000 "	70,000 "	1 "
10,000 "	75,000 "	1 1/2 "
15,000 "	100,000 "	2 "
20,000 "		3 "

This new Certified Kit, with the *new low prices* of I. R. C. Metallized Resistors, has created a sensation in the radio field. It fills a long-felt want among Servicemen. Has speeded up the work of thousands—and will do the same for you. Be sure the gold seal is unbroken, for this kit is **Factory-Sealed, Factory-Tested, Factory-Guaranteed**

The purchase of the kit entitles you to our famous I. R. C. Resistor Replacement Guide (normally costing \$1) **free**—and also our R. M. A. standard Color Code Chart. See your jobber today—or mail the coupon below.

INTERNATIONAL RESISTANCE COMPANY
PHILADELPHIA TORONTO

I R C
Metallized
RESISTORS

International Resistance Co., 2006 Chestnut St., Phila.	R-3
Gentlemen:	
I enclose <input type="checkbox"/> check (<input type="checkbox"/> money order) for \$3.50, for which please see that I receive your Certified Kit of Metallized Resistors—also your Resistor Guide and Color Code Chart.	
Name	
Address	
City	State.....

The Latest Data on the Construction and Repair of Radio Receivers

[Including Short-wave and Television Receivers]

WRITTEN by two widely known radio engineers these three books cover every phase of building, repairing and "trouble-shooting" on modern receiving sets. They include complete instructions for building short-wave and television receivers.


Radio Construction Library

3 Volumes, 6x9, 993 Pages, 561 Illustrations

This practical Library includes: PRACTICAL RADIO—The fundamental principles of radio, and radio set-building, presented in an understandable manner. Illustrated with working diagrams. RADIO CONSTRUCTION AND REPAIR—Methods of locating trouble and reception faults and making workmanlike repairs. How to construct all types of sets, including television receivers. RADIO RECEIVING TUBES—Principles underlying the operation of all vacuum tubes and their use in reception, remote control and precision measurements. The library is up-to-the-minute in every respect and is based on the latest 1931 developments in the design and manufacture of equipment.

10 Days' FREE Examination!

No Money Down

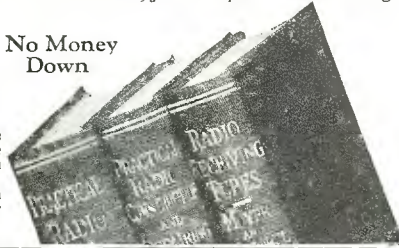

Examine these books free for ten days. You will find them invaluable as a home study course and as a reference in the daily radio problems which you meet in your business. Simply fill in the coupon and the books will be sent to you postage prepaid; there is nothing to pay if they do not prove satisfactory.

FREE EXAMINATION COUPON

McGRAW-HILL BOOK COMPANY, Inc. 330 W. 42nd Street, New York
Send me the new RADIO CONSTRUCTION LIBRARY, three volumes, for 10 days' free examination; if satisfactory I will send \$1.50 in ten days and \$2.00 a month until \$7.50 has been paid. If not wanted I will return the books.

Name

Home Address

City and State

Position

Name of Company

RCB-3-32

Low Range FUSES

INSTRUMENT LITTELFUSES

1/100, 1/32, 1/16, 1/8, 1/4, 3/8, 1/2, 1, 2 amps. for galvanometers, millimeters, etc.



RADIO FUSES
1/8 amp. for "B" circuits; also 1, 1 1/2, 2 and 3 amps. for radio replacement.

WRITE FOR DETAILS

HIGH VOLTAGE LITTELFUSES


1,000, 5,000 and 10,000 volt ranges, in 1/16, 1/8, 1/4, 3/8, 1/2, 3/4, 1, 1 1/2, 2 amps. for transmitters, rectifiers, etc.

LITTELFUSE LABORATORIES 1774 Wilson Ave., Chicago, Ill.

SERVICE MEN AND DEALERS

Get in line for big profits with FILTERMATIC PRODUCTS. Take advantage of FREE newspaper advertising. The Super-Tone control is not an ordinary tone control. It is designed to suit any circuit, and has several distinctively new features. It can be installed in one minute, and allows you a very good profit. Unit installed in an attractive crystallized Gold and Black case. Will bring out the most pleasing tones from any set. List price \$2.50. Send us a check or money order for \$1.25 and we will send you a sample postpaid. Be sure to write your order on your business correspondence to prove you are a Service man or dealer. Write for circulars of other products. Satisfaction guaranteed or money refunded.

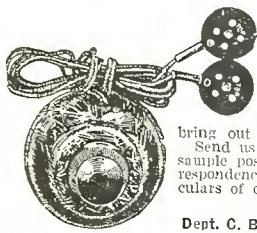FILTERMATIC MFG. CO. 4458 Frankford Ave., Phila., Pa.




JUST OFF THE PRESS!

THE greatest book of its kind ever published. HOW TO BUILD AND OPERATE SHORT WAVE RECEIVERS is the best and most up-to-date book today.

The book has been edited and prepared by the editors of SHORT WAVE CRAFT and contains a wealth of material on the building and operation, not only of typical short wave receivers, but short wave converters as well. Dozens of short wave sets will be found in this book, which contains hundreds of illustrations: actual photographs of sets built, hook-ups and diagrams galore.

WE SAY—AND REPEAT IT—THAT NOTHING LIKE THIS HAS EVER BEEN PUBLISHED BEFORE.

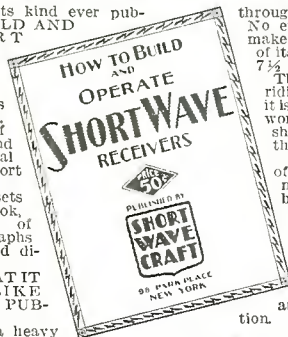The book comes with a heavy colored cover, and is printed



throughout on fine-class paper. No expense has been spared to make this the outstanding volume of its kind. The book measures 7 1/2 x 10 inches.

This book is sold at such a ridiculously low price, because it is our aim to put this valuable work into the hands of 50,000 short wave enthusiasts during the first few months of 1932.

Published by the publishers of SHORT WAVE CRAFT magazine. This alone will be your guarantee that it is a really worthwhile publication.

We know that if you are at all interested in short waves you will not wish to do without this book. It is a most important and timely new radio publication.

This Book Is Not Sold On Newsstands.

Mail fifty cents in stamps, or money order to

SHORT WAVE CRAFT, 95 Park Place, New York, N. Y.

KIT RECEIVER BLUE PRINTS

PRIMARYLY FOR SERVICE WORK

Full sized blueprints are available of any kit circuit ever published in the Call Book. Space permits listing only a few of the more popular ones. Write us if the desired print is not shown here.

COMPLETE ASSEMBLY DRAWINGS

No. 32	Scott "World's Record" Super Eight.....	\$1.00
No. 56	Improved Browning-Drake	1.00
No. 68	Improved Reuter 45 K. C. Super-heterodyne Receiver (5 drawings)....	1.00
No. 73	Magnaformer Super-heterodyne Receiver (5 drawings).....	1.00
No. 99	Magnaformer 9-8 A. C. (5 drawings).....	1.00
No. 123	World's Record Super Ten and Power Pack (6 drawings).....	1.00
No. 167	Scott World's Record SG Nine "Power Pack Operated" (4 drawings)....	1.00
No. 231	Custom-built Model World's Record Shield Grid A. C. 10 (4 drawings) 1.00	
No. 246	Pilot Super-Wasp Short Wave Receiver (3 drawings).....	1.00

GRAPHIC WIRING DIAGRAMS

No. 101	World's Record Economy Super 8.....	\$0.60
No. 174	Sargent-Rayment Seven Receiver.....	.60
No. 202	Silver-Marshall 730 Four Tube Receiver.....	.60
No. 221	Modulated Oscillator60
No. 236	S-M 722 A. C. Screen Grid Receiver.....	.60
No. 244	S-M S. G. A. C. 712 Rec. (to be used with 677 Power Pack).....	.60
No. 245	S-M 677 Power Pack (to be used with 712 Receiver).....	.60

SCHEMATIC WIRING DIAGRAMS


No. 211a	Magnaformer 1929 A. C. Super.....	\$0.50
No. 223a	Silver-Marshall 720 A. C. Shield Grid Six.....	.50
No. 244a	S-M S. G. A. C. 712 Rec. (to be used with 677 Power Pack).....	.50
No. 245a	S-M Power Pack (to be used with 712 Receiver).....	.50
No. 254a	Lincoln DeLuxe Ten A. C. S. G. Receiver.....	.50
No. 254a	Lincoln DeLuxe Ten A. C. S. G. Receiver.....	.50
No. 255a	Silver-Marshall 722 S. G. D. C. Receiver.....	.50
No. 266a	Lincoln DeLuxe 51.....	.50

Any of the above blueprints will be sent postpaid by return mail upon receipt of the proper amount. C. O. D. orders not accepted.

CITIZENS RADIO SERVICE BUREAU
508 South Dearborn Street, 7th Floor, Chicago, Illinois

AMAZING RECEPTION!

"Super Ball" Antenna

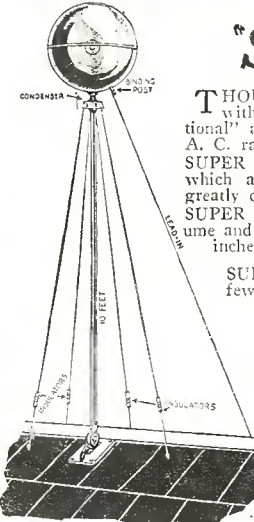

THOUSANDS of users are getting marvelous reception with the SUPER BALL ANTENNA, the "all directional" aerial, which brings out the hidden powers of all A. C. radio sets.

SUPER BALL ANTENNA features a patented condenser which acts as a neutralizer for the entire system and greatly clarifies tone.

SUPER BALL ANTENNA gives greater selectivity, volume and distance due to its conductive surface of 364 sq. inches.

SUPER BALL ANTENNA is easily installed in a few minutes and gives a lifetime of satisfaction.

Over 1,000,000 in Use

Send for prices for Super Ball with Condenser, also complete Kit for Installation and printed matter.

Get one to-day at your radio dealer

YAHR-LANGE
INCORPORATED

142 North Water St.

Milwaukee, Wis.

CANDOHMS


WILL LOWER YOUR COSTS—MAY WE SAMPLE AND QUOTE

The Muter Company

1255 S. Michigan Ave.

CHICAGO, ILL.

A DUAL-RANGE STANDARD-SIGNAL GENERATOR

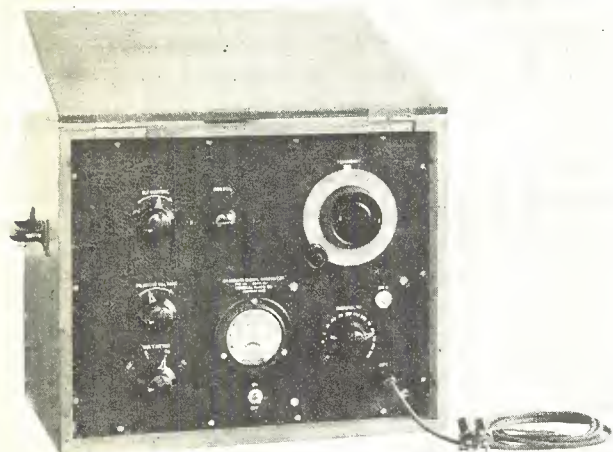

TYPE 601-A STANDARD-SIGNAL GENERATOR

THIS inexpensive standard-signal generator makes standard sensitivity measurements on radio receivers at any frequency between 90 kc. and 6000 kc. by the use of interchangeable inductors. Two inductors are in place in the instrument and either may be selected by means of a switch on the panel. For instance, the broadcast band and the intermediate-frequency superheterodyne band can both be in position, thus facilitating checking on the production line.

Aircraft operating companies also find this instrument useful because it enables them to make thorough sensitivity tests as a part of their rigorous maintenance-inspection schedules. Its low price enables them to keep one at every terminal.

Price \$210.00, without inductors

WRITE FOR LITERATURE

GENERAL RADIO COMPANY

OFFICES LABORATORIES FACTORY

CAMBRIDGE A, MASSACHUSETTS

COME TO SUNNY CALIFORNIA



and Learn RADIO-TELEVISION TALKING PICTURES

Come to California where many of the world's most famous Radio Stars make their homes—where the great Laboratories of the American Television Corporation are located—where hundreds of trained Sound Engineers and Mechanics are employed in the Talking Picture Studios and Theatres of Hollywood.

RAILROAD FARE ALLOWED

Don't worry about the expense of the trip. For a limited time we are allowing the railroad fare to Los Angeles from any point in the United States. This is deducted from your tuition, so the trip costs you nothing extra. Take advantage of this opportunity to visit Los Angeles and Hollywood and prepare for a good job at the same time!

PRACTICAL SHOP TRAINING

At the Oldest Trade School in the West

For over 25 years National has been training men by the practical shop method. Over 20,000 ambitious men from all over America have come to National for their training. You'll find National graduates working in the famous Studios of Hollywood, in Talking Picture Theatres, great Broadcasting Stations; for Radio Manufacturers and Dealers; while many have gone into the Radio business for themselves and are making big money as their own boss. What they have done, you can do!

SCORES OF JOBS WILL BE OPEN

10,000,000 Radio sets to be constantly serviced! 600 Broadcasting Stations employing trained Operators and Mechanics! 10,000 Theatres equipped for sound and the job only half done! Eight stations already sending out regular Television programs! New jobs will be opening up every day—hundreds of golden opportunities for the trained man! And you can prepare for them in 4 months at National.

FREE EMPLOYMENT SERVICE

Spare Time Jobs While at School

When you've finished National Training,—four months of practical work in the great National Television, Talking Picture and Radio Shops—then National's Employment Department will assist you in every possible way to get the job you want. And if you're short of money, National will gladly help you get a spare time job to pay your living expenses while at school.

MAIL COUPON FOR BIG FREE BOOK

Get all the facts! Mail coupon below for Big Free Book telling all about National's famous Shop Training and the many jobs opening up in this fascinating field. No cost or obligation. Just mail the coupon!

National Television, Talking Picture and Radio School,
Dept. 337-E, 4006 So. Figueroa St.,
Los Angeles, Calif.

Please send me your big new Free Book on Television, Talking Pictures and Radio, and all details of your Free Railroad fare offer.

Name

Street No.

City..... State.....



Wet and Dry Electrolytic Condensers

Paper Condensers

Mica Condensers

Resistors

Transformers

Chokes

NEW LOWER PRICES

To SAVE MONEY MAIL THIS

The new 1932 Polymet Radio Parts Catalog contains the widest line of service essentials available from any original manufacturer. Many of these are identical with the units incorporated in leading receivers. Only Polymet Quality permits service-men to confidently give Guaranteed Repairs.

STANDARDIZE ON POLYMET PRODUCTS
Used by Radio's Leaders

MAIL THIS TODAY


Polymet Mfg. Corp.,
829 E. 134th St., New York City

Rush the new 1932 Polymet Parts Catalog to me.
Check below:

SERVICE-MAN *Name*

DEALER

JOBBER *Address*

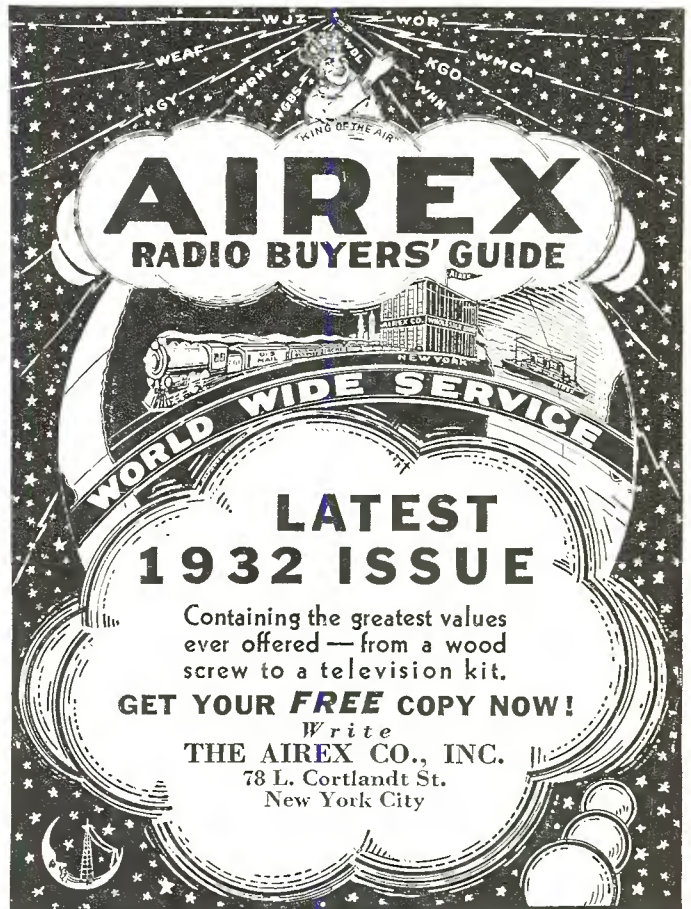

AIREX

RADIO BUYERS' GUIDE

WORLD WIDE SERVICE

LATEST 1932 ISSUE

Containing the greatest values ever offered — from a wood screw to a television kit.

GET YOUR FREE COPY NOW!

Write
THE AIREX CO., INC.
78 L. Cortlandt St.
New York City

R.S.L. SHORT WAVE CONVERTER

UNEQUALLED PERFORMANCE


Send for Descriptive Literature

MODEL 440

Beautiful in Design—

Embodies all the Latest Engineering Developments—

Has self-contained power supply.

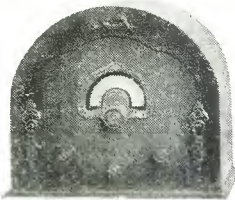

Complete line of SHORT WAVE CONVERTERS and ADAPTERS

With a price range from \$6.95 to \$34.50

R. S. L. Model 440

RADIO SERVICE LABORATORIES

Manufacturers of Short Wave Equipment
CLINTON, IOWA

DOOLITTLE & FALKNOR, Inc.

Radio Engineering and Manufacturing

Field Intensity Curves Allocation Engineering
Station and Studio Installations
Engineering Management

1306-8 W. 74th Street Chicago, Illinois

LEROY M. E. CLAUSING

Consulting and Designing Radio Engineer

5509½ Lincoln Avenue
Ravenswood 9109 CHICAGO, ILL.



RADIO SERVICE TREATISE
AND
RADIO BARGAIN CATALOG
FREE!

GET THIS

Free new No. 23 Edition of our greatly enlarged **RADIO SERVICE TREATISE**. Every radio man must have it. Contains some 75 new hookups, circuit diagrams; over 350 illustrations. **Positively the greatest book ever put out by anyone.** Editorial contents: Vacuum Tube Treatise, with many illustrations; Vacuum Tube Average Characteristics Chart; How to Take Care of Your Tubes.

How to Connect Phonograph Pick-ups; Improving Tone Quality of Old Sets; Connecting Additional Loud Speakers; all fully illustrated with diagrams. Other articles; Modernizing Old Radio Sets; How to Convert Battery to Power Sets; Selection of Tubes; Push-Pull Amplifiers; Replacing Audio Transformers; Phone Attachments; How to Choose Power Transformers; Voltage Dividers; Wattage of Power Transformers; Selecting and Installing Replacement Parts in Radio Sets; Filter Condensers; Repairing Eliminators, etc.

WRITE TODAY. Enclose 2 cents for postage. Treatise sent by return mail.

RADIO TRADING CO., 21 W. Broadway, New York City


BEN J. CHROMY

Attorney at Law

Patents and Patent Causes

National Press Bldg.
WASHINGTON, D. C.

“Radio Patent Service”
Weekly

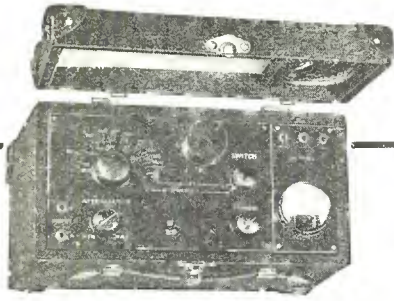

Readrite

No. 550

OSCILLATOR

(Licensed by A. T. & T. Co.)

\$18 Net to Dealer \$30 List **\$21** Net to Dealer With Output Meter

If not at your Jobbers we will ship direct when remittance accompanies order.

A sturdy modulated instrument, carefully made. Completely shielded with separate battery compartment. Furnished with 22½ v. and 3 volt batteries and one '30 tube. Reads directly broadcast band (550-1500 k.c.) and intermediate band (120-185 k.c.). Other i.f.'s obtained by sharp harmonics. Operating instructions attached in case cover with shielded wire leads. Very compact. In leatherette case 6x11½x5½". Weighs but 8 pounds. Built to high standards.

Every serviceman should have the No. 550 Oscillator to align r.f. gang condensers, locate defective r.f. transformers, adjust i.f. transformers, check oscillator stage and determine sensitivity of a receiver. A necessary instrument. Get yours today.

Write for Catalog of Servicing Instruments

READRITE METER WORKS

Established 1904

10 College Avenue BLUFFTON, OHIO



THIS IS A Profitable TUBE for DEALERS and JOBBERS

Every customer of yours who owns or operates any of the following sets, must use Kellogg 401 A.C. tubes for replacements. All these set owners are constant buyers.

KELLOGG Sets—510, 511, 512, 514, 515, 516, 517, 518, 519, 520, 521. McMILLAN Sets—26, 26PT. MOHAWK Sets, SPARTON Sets—62, 63. A-C 7. DAY FAN Sets—5143, 5144, 5145, 5148, 5158. MARTI Sets—TA2, TA10, DC2, DC10, CS2, CS10, 1928 Table, 1928 Console. CLEARSTONE Sets—110. And the first A.C. models of the following: Bell, Walbert, Wurlitzer, Pathe, Shamrock, Bush & Lane, Minerva, Crusader, Liberty, Metro, Supervox and Case.

Get your share of business from this profitable market by stocking and displaying Kellogg tubes now. Write Dept. 59 for name of your nearest jobber.

KELLOGG

SWITCHBOARD AND SUPPLY COMPANY

1070 West Adams Street » » » » CHICAGO, ILLINOIS



Electrolytic Condensers

CONSERVATIVE voltage ratings, fastest reforming, lowest leakage factor, minimum noise, exceptionally low power factor, most effective filtering, longest service life—these features characterize Dubilier Electrolytic Condensers.

Available in upright or inverted aluminum cans, and in cardboard containers with lug or wire lead terminals. In single and multiple section units, and in capacities up to 20 mfd., for high and for low D.C. voltages.

Write for Catalog 121 describing Dubilier electrolytic condensers as well as paper, mica and other dielectric condensers for all purposes.

Dubilier Condenser Corporation
4377 Bronx Blvd. New York City



NEW LOW WHOLESALE PRICES!

VARIO-MU & PENTODE Superheterodynes



Westrad leads again with lowest wholesale prices on modern Varia-Mu, Pentode Superheterodyne Radio Sets! Our Advance Catalog for 1932 is just off the press. Send for it. It contains the most complete line of up-to-the-minute Radio Receivers we have ever offered—and our prices have been further reduced!

WESTERN RADIO MFG. CO.
126 W. LAKE ST. CHICAGO ILL. U.S.A.

Build it Yourself

If you have a home workshop, here's just the magazine you need. Each issue of Popular Homecraft is crammed with plans for making such beautiful and useful things as: Book Cases, China Closets, Bird Houses, Ship Models, Rustic Furniture, Lamps, Children's Playthings, Tea Tables, Antiques, Candle Sticks, etc. Covers wood-working, metal-working, lathe work, leather craft, toys, copper, brass and pewter work. Explains use and care of tools. A real "How-to-do-it" magazine. Scores of large, clear drawings make every step simple as A B C.



SIX MONTHS' TRIAL \$1.00
Send \$1.00 today for trial 6 months' subscription. Money back if not delighted.
POPULAR HOMECRAFT
747 N. Michigan Ave. Chicago, Ill.

Take Advantage of Our
Special Offer
SEE PAGE 64


MIDGET CONE SPEAKER

50c



NEVER before have we been able to offer this Midget Cone Speaker at such a low price—only 50c—and it will pay you to order yours today.

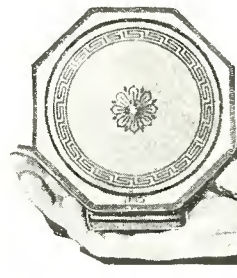This midget speaker has many advantages and its perfect tone has delighted thousands who are using it.



Our Supply Is Limited—So Send Your Order in Today—

CITIZENS RADIO SERVICE BUREAU

508 S. Dearborn Street
CHICAGO, ILL., U. S. A.

Over 25,000 Men have been trained under my supervision for the Better Jobs in RADIO



R. L. DUNCAN, *President*
Radio Training Schools

PROOF



As a graduate and a student under your supervision, I have only the highest praise and satisfaction to offer. Any man of ordinary intelligence wanting to learn Radio could not help but master it by your method of training.
GEORGE A. KRESS,
2937 Montclair Ave., Detroit, Michigan



I am a Projectionist in charge at the Andalus theatre, recently completed. You may quote me at any time or place; refer to me, if you wish, anyone who may be interested in this vast virgin field of all that pertains to Radio and its many allied industries, and I shall be delighted to champion honestly without any reservation, your courses.
A. H. STRENG,
8995 Woodburn Ave., Cincinnati, Ohio.



To study Radio under R. L. Duncan is to learn it properly and in a way that is pleasant and fascinating. Once again thank you for your kind assistance and helpfulness.
E. E. PRICE,
361 Coburn St., W.,
Moose Jaw, Sask., Canada.



Although it has not yet been a year since I enrolled for a course under your excellent supervision, I have opened a Radio Service Shop that is effective, successful and profitable. People come for my services from everywhere.
RUSSELL PEARCE,
926-13th Street, Des Moines, Iowa.

IN hundreds of Broadcasting Stations . . . in Radio Manufacturing Plants throughout the country . . . in Radio Laboratories . . . in Wholesale and Retail Radio Stores . . . in Radio Servicing . . . in Sound Motion Picture activities . . . on hundreds of ships that sail the Seven Seas . . . and even in the latest Television developments—you will find ambitious men who have been trained under my direct supervision.

I have devoted the last twelve years exclusively to the training of men for all branches of Radio. Employers in the Radio field recognize my methods of qualifying men and young men. I have geared my training to the rapid growth and development of the Radio industry. My courses, text books, methods and equipment are based on years of practical experience.

And now, with the organization of my own independent Radio Training Schools, Inc., I am better prepared to help you than ever before, in training for the opportunities which the future of the ever-growing Radio industry will have to offer.

You too can train for Future Success in Radio

The next few years will offer more prospects than ever before. The past several months offer positive proof that the trained man has the best chance. You still can get that training which will qualify you to gain a foothold in Radio. Study at home, in spare time, at minimum expense. Earn while you learn. Capitalize your idle and spare time and reap the benefits of a trained man in a progressive industry—Radio.

Make your Idle and Spare Time Profitable

My courses include everything needed for thorough training. There are no "extras" or "specials" to cost you extra money. The lessons, text books, methods, correcting, grading and returning of examinations, all the extra help and personal consultation you need . . . everything is provided until you complete your training.

RADIO TRAINING SCHOOLS, INC.
326 Broadway New York City

And in addition you are assured *practical* as well as theoretical training.

Pick Your Branch of Radio

I am offering four distinct Radio training courses:

1. Talking Motion Pictures—Sound
2. Radio and Broadcast Operating
3. Practical Radio Engineering
4. Radio Service and Mechanics

Each course is complete. Each starts out with simple principles well within your grasp. Each is right up to date, including latest developments such as Television. Each prepares you for a good paying position. Each leads to a Certificate of Graduation.


Advanced Training for Radio Men

My Practical Radio Engineering Course is an advanced course intended for Radio men who want to go still higher. It provides that necessary engineering background which, combined with practical experience, qualifies the man for the topmost job.

Ask for Facts—Write Now!

Let me sit down with you for an hour or two at your convenience. Let's go over the possibilities in Radio. This we can best do by means of the book I have just prepared. It covers the many branches of Radio and the kind of training required. Be sure to get your copy . . . it is free.

**GET THESE
FACTS
TO-DAY**

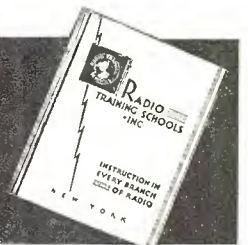

Mr. R. L. DUNCAN, *President*
Radio Training Schools, Inc.
326 Broadway, New York City


3-C.B.

Without incurring the slightest obligation on my part, please send me a copy of your latest book, "Facts About Radio."

Name

Address

City..... State.....

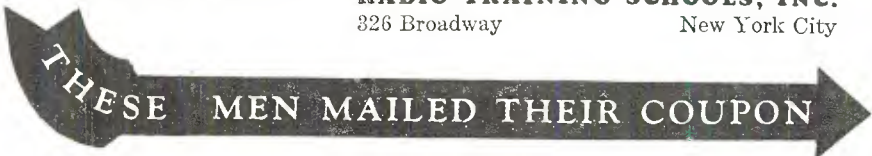

SERVICE BLUE PRINTS

FOR SERVICE MEN, TECHNICIANS AND EXPERIMENTERS

ACCURATE, clear and dependable drawings of nearly every standard circuit. These schematics are drawn to a large scale and so simplified that the whole circuit may be visualized almost instantaneously. This enables the service man to work rapidly and accurately. There is no need for microscopes or clairvoyance in reading our prints.

No. SR24	A. C. Dayton Navigator.....	\$0.75	No. SR130	Howard SG-B.....	\$0.75
No. SR3	Acme AC7.....	.75	No. SR145	Howard II.....	.75
No. SR4	Acme AC4.....	.75	No. SR118	Jesse French Jr. "G".....	.75
No. SR1	All-American Mohawk 6.....	.75	No. SR77	Kellogg 523.....	.75
No. SR2	All-American Mohawk 8.....	.75	No. SR38	Kennedy 10.....	.75
No. SR74	All-American Mohawk 96.....	.75	No. SR49	Kennedy 20.....	.75
No. SR165	All-American Mohawk (Lyric) B-7.....	.75	No. SR81	Kennedy 26.....	.75
No. SR167	All-American Mohawk (Lyric) S-7.....	.75	No. SR129	Kennedy 30 and 32.....	.75
No. SR170	All-American Mohawk (Lyric) S-8.....	.75	No. SR184	Kennedy 52A.....	.75
No. SR128	All-American Mohawk (Lyric) Model J.....	.75	No. SR185	Kennedy 56.....	.75
No. SR22	Amrad 70 A. C.....	.75	No. SR31	King Model J.....	.75
No. SR44	Amrad 81.....	.75	No. SR176	Kolster K20; K22; K25 and K27.....	.75
No. SR106	Amrad 84.....	.75	No. SR45	Kolster K21; K23.....	.75
No. SR191	Apex 10.....	.75	No. SR72	Kolster K43.....	.75
No. SR80	Apex 48 Chassis.....	.75	No. SR159	Kolster 80 and 82.....	.75
No. SR108	Apex Series 31.....	.75	No. SR182	Kolster K-90.....	.75
No. SR23	Atwater-Kent 38.....	.75	No. SR65	Kylectron 70.....	.75
No. SR51	Atwater-Kent 55 and 55C (Cap. Coupled).....	.75	No. SR124	Majestic 20.....	.75
No. SR52	Atwater-Kent 55 and 55C (Inductive Coupled).....	.75	No. SR173	Majestic 25.....	.75
No. SR114	Atwater-Kent 66.....	.75	No. SR157	Majestic Chassis 15.....	.75
No. SR131	Atwater-Kent Super H-2 Chassis.....	.75	No. SR98	Majestic Super Chassis 50.....	.75
No. SR181	Andiola 13-87.....	.75	No. SR138	Majestic Super Chassis 60.....	.75
No. SR179	Andiola 31.....	.75	No. SR7	Majestic 70.....	.75
No. SR111	Andiola Super 1931.....	.75	No. SR55	Majestic 90; 90B; 91; 92 and 93.....	.75
No. SR112	Andiola Junior.....	.75	No. SR184	Majestic 18.....	.75
No. SR12	Balkett A.....	.75	No. SR26	Philco 56-82.....	.75
No. SR162	Bosch 7 (D.C.).....	.75	No. SR156	Philco 90 and 90-A, Series B.....	.75
No. SR193	Bosch 20.....	.75	No. SR60	Philco 95.....	.75
No. SR21	Bosch 23 and 29.....	.75	No. SR172	Philco 112 and 112-A.....	.75
No. SR198	Bosch 31 and 32.....	.75	No. SR176	Pilot 148.....	.75
No. SR73	Bosch 43.....	.75	No. SR194	Radette P-14.....	.75
No. SR94	Bosch Auto Radio 80.....	.75	No. SR127	RCA 44.....	.75
No. SR109	Bosch 58.....	.75	No. SR30	RCA 60.....	.75
No. SR117	Bosch 60.....	.75	No. SR64	RCA 66.....	.75
No. SR10	Bremer-Tully 7-70.....	.75	No. SR92	RCA 80.....	.75
No. SR75	Bremer-Tully 81 and 82.....	.75	No. SR107	RCA 49.....	.75
No. SR126	Bremer-Tully 8-81 and 8-82.....	.75	No. SR108	RCA Victor R-11.....	.75
No. SR23	Brunswick 3KRO.....	.75	No. SR166	RCA Victor R-50 and R-55.....	.75
No. SR148	Brunswick 11, 12, 16.....	.75	No. SR137	RCA-Victor Superette.....	.75
No. SR71	Brunswick S-14.....	.75	No. SR115	Sentinel 11; 15; 16; 12 and 12B.....	.75
No. SR86	Brunswick 15, 22, 32, 42.....	.75	No. SR113	Sentinel 106-B.....	.75
No. SR164	Brunswick 17 and 24.....	.75	No. SR146	Sentinel 108-A.....	.75
No. SR163	Brunswick Chassis E, models 17, 24 and 25.....	.75	No. SR155	Sentinel 111.....	.75
No. SR78	Clarion 50.....	.75	No. SR128	Sentinel Super Midget 108.....	.75
No. SR139	Clarion 80 and 81.....	.75	No. SR169	Silver-Marshall A.....	.75
No. SR29	Colonial 31AC.....	.75	No. SR152	Silver-Marshall D and E.....	.75
No. SR95	Colonial 33 and 34 A. C.....	.75	No. SR140	Silver-Marshall F.....	.75
No. SR160	Colonial 47 and 48.....	.75	No. SR153	Silver-Marshall G.....	.75
No. SR47	Columbia (Chicago) S68.....	.75	No. SR35	Silver-Marshall 30.....	.75
No. SR103	Crosley 43 and 51.....	.75	No. SR53	Silver-Marshall 50-B.....	.75
No. SR174	Crosley 125.....	.75	No. SR33	Silver-Marshall 35-A.....	.75
No. SR5	Crosley 608 Gembox.....	.75	No. SR144	Silver-Marshall 726 SW.....	.75
No. SR16	Crosley 705 Showbox.....	.75	No. SR105	Silver Super 36-A.....	.75
No. SR41	Crosley Jewelbox 704B.....	.75	No. SR120	Silver Midget 7S2-12.....	.75
No. SR57	Crosley 40S, 41S, 42S and 42S.....	.75	No. SR27	Slagle (Continental) 9.....	.75
No. SR67	Crosley "Atomic" (Auto Radio).....	.75	No. SR46	Slagle (Continental) R-20.....	.75
No. SR83	Crosley 77.....	.75	No. SR25	Spanta 5R.....	.75
No. SR133	Crosley 120.....	.75	No. SR192	Sparton 15.....	.75
No. SR149	Crosley 121.....	.75	No. SR161	Sparton 25 and 26.....	.75
No. SR150	Crosley 124.....	.75	No. SR91	Sparton 600; 610 and 620.....	.75
No. SR137	Crosley.....	.75	No. SR19	Sparton AC89.....	.75
No. SR11	Day-Pan 5080.....	.75	No. SR58	Sparton 931.....	.75
No. SR66	Delco Auto Radio.....	.75	No. SR63	Sparton 589.....	.75
No. SR87	Delco Police Short Wave Receiver 3003.....	.75	No. SR3	Spaldorf E-173.....	.75
No. SR99	Edison R6 and R7.....	.75	No. SR15	Steinite 261.....	.75
No. SR49	Edison R4, R5, C4.....	.75	No. SR76	Steinite 70; 80 and 95.....	.75
No. SR33	Erla Duo-Concerto R-2.....	.75	No. SR132	Steinite 600, 605, 630 and 635.....	.75
No. SR90	Eveready Series 50.....	.75	No. SR147	Stewart-Warner 102 A and B.....	.75
No. SR153	Fada KW.....	.75	No. SR34	Stewart-Warner 600.....	.75
No. SR13	Fada 7AC.....	.75	No. SR62	Stewart-Warner 650.....	.75
No. SR70	Fada 35 and 35Z.....	.75	No. SR85	Stewart-Warner R-100A, B and E.....	.75
No. SR19	Federal II.....	.75	No. SR195	Stewart-Warner R-102A, B, E.....	.75
No. SR20	Freud-Eisenmann SR-80.....	.75	No. SR134	Stromberg-Carlson 10 and 11.....	.75
No. SR14	Freudman 2-N-12.....	.75	No. SR93	Stromberg-Carlson 12 and 14.....	.75
No. SR92	General Electric II-31.....	.75	No. SR151	Stromberg-Carlson 19 and 20.....	.75
No. SR166	General Electric H-32.....	.75	No. SR18	Stromberg-Carlson 635 and 636.....	.75
No. SR197	General Electric T-41.....	.75	No. SR54	Stromberg-Carlson 846.....	.75
No. SR137	General Electric S-22.....	.75	No. SR37	Temple S-60; S-80 and S-90.....	.75
No. SR168	General Electric K-62.....	.75	No. SR125	Temple 861; 881 and 891.....	.75
No. SR68	General Motors A.....	.75	No. SR59	Transitone Auto Radio.....	.75
No. SR154	General Motors S-3-A.....	.75	No. SR121	Trav-Ler Model C.....	.75
No. SR173	General Motors S-9-A.....	.75	No. SR43	U. S. Radio & Television (Gloritone) 26P.....	.75
No. SR179	General Motors S-10-A.....	.75	No. SR39	U. S. Radio & Television 37.....	.75
No. SR32	Gillilan 100.....	.75	No. SR171	U. S. Radio & Television 99.....	.75
No. SR42	Graybar 600.....	.75	No. SR119	Vitafone 54 (Zaney-Gill Corp.).....	.75
No. SR92	Graybar 780.....	.75	No. SR101	Victor Micro-Synchronous R-35; R-39 and RE-57.....	.75
No. SR167	Graybar 678.....	.75	No. SR61	Victor R-32; RE45 and R52.....	.75
No. SR96	Grebe Synchrophase AH-1.....	.75	No. SR92	Westinghouse WR-5.....	.75
No. SR17	Grebe 7AC.....	.75	No. SR107	Westinghouse WR-4.....	.75
No. SR59	Grebe SK-4.....	.75	No. SR137	Westinghouse WR-10 and 12.....	.75
No. SR40	Gulbransen Nine-in-Line.....	.75	No. SR163	Westinghouse WR-15.....	.75
No. SR175	Gulbransen 10 and 13.....	.75	No. SR141	Zenith A, B, C and D.....	.75
No. SR186	Gulbransen 23.....	.75	No. SR97	Zenith 71; 72; 73 and 77.....	.75
No. SR110	Gulbransen 161.....	.75	No. SR43	Zenith 52; 53; 54; 522; 532 and 542.....	.75
No. SR177	Howard AVH.....	.75	No. SR190	Zenith 91 and 92.....	.75
No. SR16	Howard Green Diamond 8.....	.75			
No. SR163	Howard 0.....	.75			
No. SR56	Howard SG-A.....	.75			

PUBLIC ADDRESS SYSTEMS

No. SR100	Amer-Tran PA-86.....	\$0.75	No. SR88	Webster (Racine, Wis.) A37-50.....	\$0.75
No. SR90	Silver-Marshall 692.....	.75	No. SR89	Webster (Chicago) D11-250.....	.75
No. SR122	Silver 679-B Amp.....	.75			

The above drawings are intended for service purposes only and are not suitable for the construction of receivers from miscellaneous parts. They will be sent postpaid by return mail upon receipt of the proper amount. C. O. D. orders not accepted.

CITIZENS RADIO SERVICE BUREAU

508 South Dearborn Street, 7th Floor CHICAGO, ILLINOIS

ANNOUNCING

A Personal Course of Instruction in

TELEVISION ENGINEERING

By ARTHUR H. HALLORAN, Television Consultant

for radio men who want to be ready when
CATHODE RAY RECEIVERS
are commercialized. 1932's big promise.

THE course consists of 30 lessons which explain mechanical and electrical scanning, synchronization, generation, transmission and reception of television signals. Each lesson is accompanied by problems to be answered by the student and corrected and graded by the instructor before the next lesson is mailed.

A working knowledge of the fundamental principles of radio and trigonometry is prerequisite to the course. Only a limited number of enrollments can be accepted, preference being given to those who give evidence of a serious interest in the subject. This course is conducted in co-operation with engineers who have developed the cathode ray tube for television purposes. Its purpose is to prepare men for employment in this new industry wherein yesterday's science is today being engineered for tomorrow's sales.

The cost is moderate. A down payment of \$5.00 brings you the first lesson and four more thereafter as the problems are answered. Similar \$5.00 payments bring each succeeding set of 5 lessons, a total of \$30.00 for 30 lessons. Mail the attached enrollment blank with your initial \$5.00 payment. It marks a turning point in your career.

ENROLLMENT BLANK

ARTHUR H. HALLORAN,
430 Pacific Bldg., San Francisco, Calif.

Enclosed is \$5.00 for which enroll me as a student in your course on Television Engineering. I understand simple radio principles and trigonometry and expect to complete the course.

NAME.....
STREET AND NUMBER.....
CITY.....STATE.....

SERVICE-MEN FREE

SEND FOR THIS BOOK YOU NEED IT!

1932 RADIO PRICE GUIDE
TUBES, SETS, REPLACEMENT PARTS,
BATTERIES, ACCESSORIES
Everything for your business from the smallest screw to the finest mike in this book.

Guaranteed Quality Goods
Prices Lowest Ever Quoted
Fresh new dependable Merchandise
at Bargain Prices!
Leading Manufacturers' Lines

RADOLEK Co.
601 W. RANDOLPH ST.
CHICAGO, ILL.

USE THIS CONVENIENT COUPON

Radolek Co.
303 Canal Station, Chicago, Ill.
Please send me without obligation your Service Man's Supply Book.

Name.....
Address.....
City.....State.....

SERVICEMEN DEALERS HAMS

Special Clearance Sale of Hard to Get Items

- R. C. A. Victor Hand Microphones for Public Address Systems and Home Recording \$ 2.95
- POWERTONE Single Button Microphones..... 6.25
- POWERTONE Double Button Microphones..... 11.00
- TUNG SOL 8 Mfg. Electrolytic Condensers (35c each), 3 for..... \$1.00
- CRYSTAL HOLDER, plug-in type, dust proof..... 1.75
- 50 WATT SOCKETS..... 1.45
- MICROPHONE STANDS, Desk Type..... 1.95
- MICROPHONE RINGS..... .95
- REMLER .00035 Condensers..... 1.95
- REMLER .0005 Condensers..... 2.45
- ESICO 85 Watt Irons..... 1.75

COMPLETE LINE of READRITE METERS—40% off list.
COMPLETE LINE of HAMMARLUND and PILOT PARTS at BIG SAVINGS, also complete line of **CARDWELL CONDENSERS.**
COMPLETE LINE of CARTER POWER RHEOSTATS @ 50% off list.

- SANGAMO Audio Transformers @ \$1.50
- SANGAMO input push-pull Transformers @ 1.75
- SANGAMO output push-pull Transformers @ 1.75
- FLECHTHEIM 0-500 volt D.C. Portable Meter..... 1.95
- FLECHTHEIM 0-600 volt A.C. and D.C. Portable Meter..... 2.45
- SIGNAL Key number 112-K..... 1.19
- SIGNAL R. 68 Wireless Practice Set..... 2.05
- UNIVERSAL .0005 Variable Condensers..... .95
- R. C. A. Sockets for 866 or 210 Tubes..... .59
- B. B. L. DeLuxe Pickups 6.95


COMPLETE LINE OF SPEAKERS AT SPECIAL LOW PRICES

- PEERLESS 12-inch A.C. Auditorium "Double Rectifier"..... \$10.95
- R. C. A. Victor A.C. Dynamic Chassis "Tube Rectifier"..... 12.95
- JENSEN Jr. A.C. Auditorium Chassis "Tube Rectifier"..... 10.95
- FARRAND 9-inch Inductor Dynamic used in A.C. & D.C..... 5.95
- OXFORD 14-inch A.C. Auditorium "Tube Rectifier"..... 12.95
- JENSEN D.7—D.C. 2500 Ohm. field..... 7.95
- ROLA MIDGET D.C. 2500 Ohm field for push pull..... 3.45

TRY-MO RADIO CO., Inc. 177 Greenwich St. New York, N. Y.
PROMPT MAIL ORDER SERVICE FREE CATALOG UPON REQUEST

Make a **PROFIT** *from Every Service Call*

Service men make \$90 extra, per month installing **AMPERITE**—the real self-adjusting Line Voltage Control. Saves tubes and power equipment. Improves reception. Easily installed in 5 minutes without chassis changes. A type for every electric radio.




AMPERITE Corporation
561 BROADWAY, NEW YORK

AMPERITE
Self-Adjusting
LINE VOLTAGE CONTROL

TO SERVICE MEN
Send \$1.62 to Dept. CB-3 for demonstrator and sales helps.

WHAT YOU NEED TO SUCCEED IN RADIO

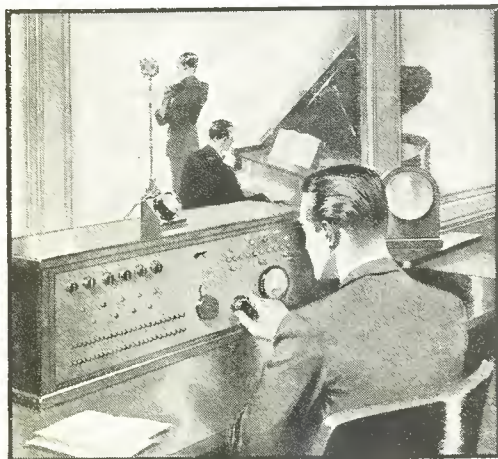

RADIO is a highly specialized business. As it develops it is becoming more exacting in its demands. But radio is the modern field of opportunity for those who keep step with its progress and pioneer in its opportunities!

There is a great demand for *trained* men in the radio industry. There is no place for *untrained* men. Experience must be accompanied by technical knowledge.

A pioneer in radio instruction, the International Correspondence Schools have kept apace of the times and offer courses prepared by authorities, which give practical instruction in fundamentals and latest developments alike. The courses were prepared and are constantly revised by the Who's Who of Radio!

Composed of 24 basic divisions, the Complete Radio Course is designed to give thorough instruction in the whole field of radio. The I. C. S. Radio Servicing Course was prepared specially for men who wish to become service experts. Study of it makes possible leadership over competition. The I. C. S. Radio Operating Course is vital to mastery of operating and transmitting.

We will be pleased to send you details of any or all of these subjects. Just mark and mail the coupon—the information will be forwarded without delay.

INTERNATIONAL CORRESPONDENCE SCHOOLS
Box 8317 F, Scranton, Pa.

Without cost or obligation, please tell me all about the
NEW RADIO COURSE

Name _____ Age _____

Street Address _____

City _____ State _____

*If you reside in Canada, send this coupon to the International Correspondence
Schools Canadian, Ltd., Montreal, Canada*

INDEX TO ADVERTISERS


	Page
A	
Airex Company, The.....	56
Amperite Corporation	61
Audiola Radio Company.....	50
C	
Capitol Radio Engineering Institute, Inc.....	48
Central Radio Laboratories.....	50
Chromy, Ben J.	56
Citizens Radio Service Bureau	
Blue Prints	54-60
Subscription Offer	64
Midget Cone Speaker.....	58
Clarostat Mfg. Co., Inc.....	48
Clausing, Leroy M. E.....	56
Coyne Electrical School.....	1
D	
Doolittle & Falknor, Inc.....	56
Dubilier Condenser Corp.....	58
E	
Electrad, Inc.	47
F	
Filtermatic Mfg. Company.....	54
G	
General Radio Company.....	55
Gernsback Publications, Inc.....	48
Grigsby-Grunow Co.....	Third Cover
H	
Halloran, Arthur H.....	61
Hammarlund-Roberts, Inc.....	51
I	
International Correspondence Schools.....	62
International Resistance Co.....	53
J	
J. M. P. Mfg. Company, Inc.....	52
Jewell Electrical Instrument Co.....	49
K	
Kellogg Switchboard & Supply Co.....	57
L	
Littelfuse Laboratories	54
M	
McGraw-Hill Book Company, Inc.....	54
Motomaster Radio Corp.....	2nd Cover
Muter Co., The.....	54-63
N	
National Radio Institute.....	5
National Television, Talking Picture and Radio School.....	55
P	
Polymet Mfg. Corp.....	56
Popular Homecraft	58
R	
RCA Institutes, Inc.....	47
RCA Victor Co., Inc.....	Fourth Cover
Radio Service Laboratories, Inc.....	56
Radio Trading Co.....	56
Radio Training Schools, Inc.....	59
Radio Treatise Co., Inc.....	52
Radolek Company	61
Readrite Meter Works.....	57
S	
Schwartz & Son, Maurice.....	50
Scott Radio Laboratories, Inc., E. H.....	2-3
Short Wave Craft.....	54
T	
Try-Mo Radio Company, Inc.....	61
W	
Western Radio Mfg. Co.....	58
Wright-DeCoster, Inc.	51
Y	
Yahr-Lange, Inc.	54

**WIRE
WOUND**

CANDOHM

**FIXED
RESISTORS**

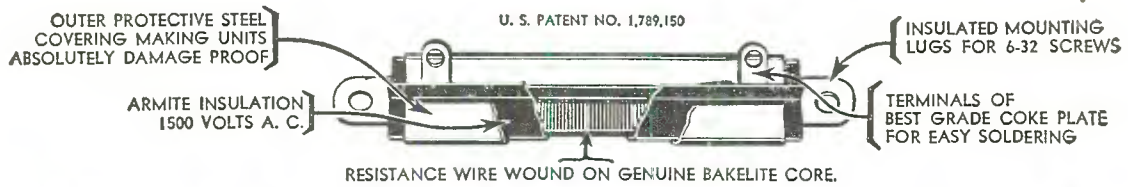**ARMoured REPLACEMENT UNITS
STANDARD EQUIPMENT IN THE LEADING SETS**



SPECIAL INTRODUCTORY MONEY MAKING OFFER

To Readers of Radio Call Book Magazine and Technical Review

**\$ 30
VALUE**

**Complete assortment of 50 Candohms in 24
different values enabling immediate replace-
ment of any service job**

**\$ 00
Prepaid**

Contents of Service Men's Kit



Stock No.	Ohms	Quantity	List	Amt.
702	20	1	\$.20	\$ 0.20
704	40	1	.20	.20
706	60	1	.20	.20
709	50	1	.20	.20
710	100	2	.20	.40
715	150	1	.20	.20
720	200	2	.20	.40
721	250	1	.20	.20
722	300	2	.20	.40
723	400	1	.20	.20
724	500	4	.20	.80
725	600	1	.20	.20
726	750	4	.20	.80
728	1000	5	.20	1.00
730	1250	1	.20	.20
760	1500	3	.40	1.20
762	2000	4	.40	1.60
764	2500	4	.40	1.60
765	3500	2	.40	.80
766	5000	4	.50	2.00
767	6000	1	.50	.50
768	7500	1	.50	.50
770	10000	2	.50	1.00
772	12500	1	.50	.50
Total		50		\$15.30

An actual photograph of the kit you will receive. By far the greatest value ever offered. Order yours today!



THE MUTER COMPANY
1255 South Michigan Ave.
Chicago, Ill., U. S. A.

CLIP—MAIL NOW!

THE MUTER COMPANY
1255 South Michigan Ave., Chicago, Ill., U. S. A.

- Please send Candohm Resistor Kit Prepaid. \$5.00 is enclosed.
- Send c.o.d.

Name

Address

City State

Get this New and Enlarged Edition of

RADIO SERVICE Schematics



with a
Full Year's Subscription
to
Radio Call Book Magazine and Technical Review

For **\$2.50**
Only

(Foreign \$3.00—Canada \$3.50)

You Save \$1.50 by this Combination Rate!

If you purchased RADIO CALL BOOK MAGAZINE and TECHNICAL REVIEW on the newsstand each month, the cost would be \$3.00 for a full year; the regular advertised price of RADIO SERVICE SCHEMATICS is \$1.00, so ordinarily these two would cost \$4.00. *Here's your chance to save \$1.50* and obtain the magazines and schematics you are always in need of. Send your order in today!

The New and Enlarged Edition of Radio Service Schematics Contains:

Over one hundred SCHEMATIC WIRING DIAGRAMS of Popular Factory Built Radio Receivers and Power Supplies, carefully drawn by our own expert drafting force.

Laboratory and workshop formulas in simplified form to aid the Serviceman and Engineer.

RECEIVER RESPONSE CURVES showing sensitivity, selectivity and electrical fidelity characteristics, prepared in our own laboratory as specified by the IRE and RMA are given, showing such popular brands as RCA, MAJESTIC, ATWATER KENT, CROSLLEY, SILVER, SPARTON, STEWART-WARNER, BRUNSWICK and others.

CLIP—MAIL NOW!

CITIZENS RADIO SERVICE BUREAU
508 S. Dearborn Street, Chicago, Ill.

Please find enclosed \$2.50 U. S. A. \$3.00 Foreign. \$3.50 Canada, for which send me the new and enlarged edition of RADIO SERVICE SCHEMATICS and enter my subscription to RADIO CALL BOOK MAGAZINE and TECHNICAL REVIEW for one year, starting with the..... number.

Name.....
Address.....
City..... State.....

Please put a check mark opposite your occupation:

- Dealer
- Serviceman
- Engineer
- Manufacturer
- Distributor
- Salesman
- Technician
- Experimenter


There are 11 Great Models of

Majestic


Superheterodyne

RADIO

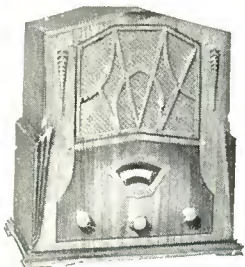Licensed under patents and applications of R. C. A., Hazeltine, La Tour, Lowell & Dumore, and Boonton Research Corporation.



SHEFFIELD \$59.50

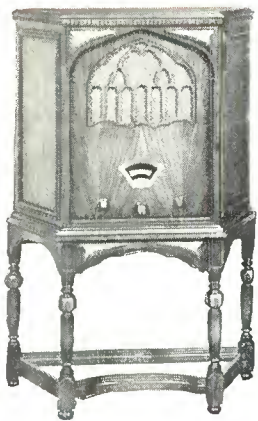

WHITEHALL \$89.50



BERKSHIRE \$59.50

Majestic — world's largest manufacturers of complete radio receivers — offers 11 great new models, each the undisputed value-leader in its class. Each is a superheterodyne, of course, and each is equipped with Multi-Mu, Pentode, Spray-Shield tubes and tone control. The larger models have perfected automatic volume control and the marvelous new development, exclusive with Majestic, the Duo-Diode...push-pull detection in one tube. Cabinets are the work of master craftsmen.

There are two receivers, covering both the 200 to 550 meter range and the 15 to 200 meter bands. Ask to see the new Viking and Explorer models. Prices: \$84.50 and \$94.50. Short Wave Converter, \$38.50.

Over 3,000,000 Majestic sets in use all over the world have made Majestic performance and Majestic value famous. Before you buy any radio set, see and hear these new Majesties.

GRIGSBY-GRUNOW COMPANY, CHICAGO,
and affiliates, with factories at Chicago,
Toronto, London, Bridgeport, Oakland, and Sao Paulo, Brazil
World's Largest Manufacturers of Complete Radio Receivers



ABBEYWOOD
Combination \$290.00



CROYDON \$119.50



FAIRFAX \$69.50

Prices
slightly higher
on West Coast



STRATFORD \$99.50

RADIO DEALERS and SERVICEMEN

Here are two live items that wide-awake Dealers and Servicemen can cash in on.

THE RADIO DEALERS' ANTENAPLEX KIT

This RCA Antenaplex System, when properly installed, due to its superior design and complete shielding, transmits to the Outlet whatever the installed antenna receives. Interference that is not actually picked up at the antenna will be sealed out and not transmitted to the receivers. This system has been found very satisfactory to a great number of Dealers located in crowded and congested districts, where they have been bothered with a great deal of local interference. Many of you dealers who read this well know from sad experience what interference in radio reception will do when demonstrating good sets. It means many a sale lost through no fault of the set or your sales ability. Why not install one of these systems and decrease sales resistance?

The RCA Antenaplex Kit, Model RF-5000, consists of the following parts:


- 1—RCA Antensifier Box—Model RF-5001
- 1—RCA Antensifier—Model RF-5002
- 100 Feet—RCA Cabloy—Model RF-5050
- 100—RCA Cabloy Clamps—Model RF-5055
- 10—RCA Taplets—Model RF-5031
- 10—RCA Radio Outlet Flush Plates—Model RF-5634
- 1—RCA Terminet—Model RF-5091

Special Net Price to Dealers..\$100.00

An attractive proposition awaits Radio Service Organizations or Servicemen doing a fair volume of business who are equipped to handle the RCA Antenaplex System. If you have contacts with Electrical and Building Contractors or are in a position to closely contact apartment house owners, write us for further information.



One of the many uses of the Radio Pillow

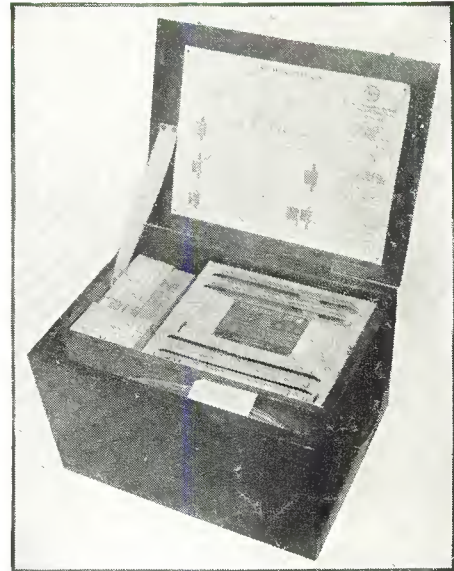

The Radio Dealers' Antenaplex Kit

THE RADIO PILLOW

Feature these Radio Pillows to your trade. Every customer is a prospect. Independent Servicemen and Servicemen connected with Radio Dealers send for literature telling of the many uses and sales appeal of this product. It allows an individual to listen-in to their favorite program without disturbing others. Ideal for use in Guest Rooms, Nurseries, Hospitals, etc.
List Price\$6.95



Centralized Radio System

RCA Victor Co., Inc.

A Radio Corporation of America Subsidiary
Camden, New Jersey
"RADIO HEADQUARTERS"

Centralized Radio Section
RCA Victor Co., Inc.
Camden, N. J.

- Please send me full details on
- The Radio Dealers' Antenaplex System
 - The RCA Antenaplex System
 - The Radio Pillow

Name.....

Address.....