

Radio Call Book Magazine and Technical Review

Established
1921

25¢

May, 1932

In This Issue:

Speech Input Equipment
C Bias Elimination
Majestic 175kc Oscillator
Capacity Decade Box
Set Tester
Signal Generator for Servicemen
841 Class B and Class C Characteristics
New Tube Developments
Photronic Cell Hookups
Filter Design by Graphs
Status of Television

Performance Curves and Schematics of:

All American Mohawk, Lyric S-7, Balkeit L-8,
Crosley 27, Perfectone Auto Radio 7-T-38, Philco
51, RCA-Victor Radiola 43, Silver-Marshall Q,
Stromberg-Carlson 29, United American Bosch 5,
Webster 6043-R Amplifier

*Frequency Assignments of All Broadcast,
Short Wave Relay, Police, and Visual Stations*

SERVICE - ENGINEERING - SALES



WORK FOR YOURSELF • SET YOUR OWN PAY BEGIN NOW • WE'LL HELP

If your pay has been cut—or, if you're slaving away on some hopeless job—here's your chance to get on your feet in a hurry! R. T. A.—one of the oldest, best known radio organizations in the world—offers you the opportunity to go to work for yourself—to name your own pay—and to start making money almost at once. R. T. A. is not just a school that teaches you and then lets you shift for yourself. Instead, R. T. A. makes you a Certified Radiotechnician and provides you with a wonderful service outfit that makes money for you just as soon as you get it. Real money too—up to \$20 a day! With R. T. A. Training and with the R. T. A. Set Analyzer and Trouble Shooter you should be the most popular radio service man in town, and have all the business you want to take care of. No pay cuts—no worry about losing your job—nobody to boss you but yourself.



SEND COUPON for NO-COST MEMBERSHIP PLAN

We have worked out a truly wonderful plan whereby R. T. A. membership, the R. T. A. Course, and the R. T. A. Set Analyzer and Trouble Shooter need not cost you a cent. The coupon will bring you full particulars. Clip—fill in—mail now! Today!

RADIO TRAINING ASSOCIATION OF AMERICA
4513 Ravenswood Ave., Dept. RCB5, Chicago
Send me full particulars of your No-Cost Membership Plan.

Name _____
Street _____
Town _____ State _____

RADIO TRAINING ASSO. OF AMERICA
4513 RAVENSWOOD AVE. Dept. RCB5 CHICAGO, ILLINOIS


815 Logs of 48 foreign stations received in U.S. again Prove

received in U.S. again Prove

SCOTT ALL-WAVE

the One 'Round the World Receiver


JANUARY LOGS From Scott Owners	
Stations Received	Number of Logs
VK2NE	Australia.....100
HKD	Colombia.....85
IKO	Italy.....70
FYA	France.....69
HKM	Colombia.....50
HKA	Colombia.....49
GSSW	England.....43
HKO	Colombia.....37
FRICD	Indo-China.....35
PONTOISE	France.....19
ZEFSEN	Germany.....15
AKN	Argentina.....11
GHW	England.....10
HBE	Colombia.....10
GDF	England.....9
GHS	England.....8
HKC	Colombia.....7
FRADO	Ecuador.....6
BABAT	Morocco.....6
VPT	Bermuda.....6
CNIGI	Cuba.....5
HKF	Colombia.....4
CTIAA	Portugal.....3
PTN	France.....3
KHO	Hawaii.....3
ONY	Denmark.....2
HCIDR	England.....2
JIAA	Japan.....2
PLV	Java.....2
FRY-15	France.....2
VVSBMO	Venezuela.....2
Kongawuster	Hansen.....1
CNK	Cuba.....1
CM2MK	Cuba.....1
DHA	Germany.....1
FAU25	Spain.....1
FAQ	Spain.....1
PTP	Holland.....1
FRAC	France.....1
KRH	Hawaii.....1
SS	Argentina.....1
SNX-LSG	Argentina.....1
T-14-NRH	Costa Rica.....1
VNAV	Venezuela.....1
VEW	France.....1
IZH	New Zealand.....1
ZYA	New Zealand.....1

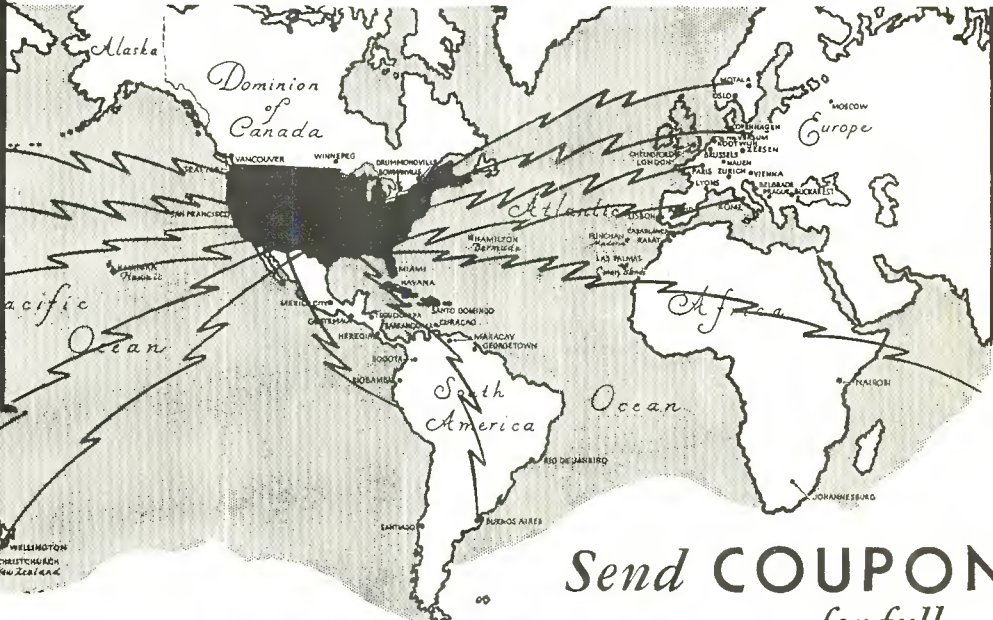

Send **COUPON** for full PARTICULARS

FROM NEW YORK AND SAN FRANCISCO—from Canada and the Gulf Coast—from everywhere in the United States—verified logs of foreign reception have poured in—815 in all—during the month of January. The most distant station was 10,500 miles away from the receiver! And most of the logs that came in were of stations over 6,000 miles distant.

These logs—this reception of foreign stations was accomplished with Scott All-Wave Receivers operating under all possible conditions. The results obtained are, therefore, AVERAGE—and represent the results YOU will get when YOU buy a Scott All-Wave for yourself. They constitute actual PROOF of the SCOTT ALL-WAVE'S ability to give daily 'round the world performance. Not just once in a while—but daily, summer and winter. And by reception, we mean loud, clear, reproduction—ample volume—clear, undistorted tone—thoroughly satisfactory in every way.

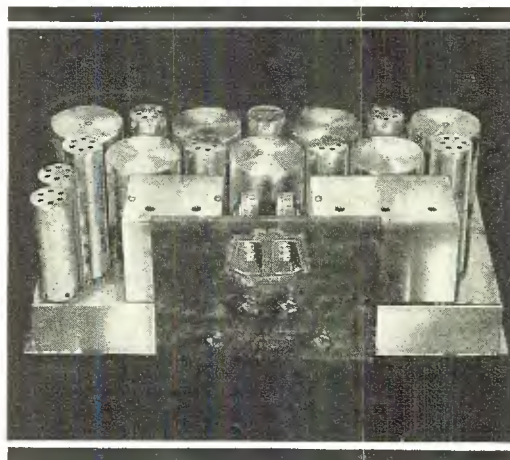

A radio that does not cover a range of 15-550 meters is completely out of date. But you want more than just a set that "dials" 15-550 meters. Even "promises" of foreign reception won't do. The set you want is the one that can PROVE its world-wide prowess BEFORE you buy it. That ONE receiver is the Scott All-Wave 15-550 Meter Superhetrodyne—a custom-built jewel of advanced design and precision engineering. The coupon will bring you full details—and you'll be happily surprised at the modest price. Clip—fill in—mail the coupon now.

The E. H. SCOTT RADIO LABORATORIES, Inc.
(Formerly Scott Transformer Co.)
4450 Ravenswood Avenue
Dept. CB52, Chicago, Illinois

SCOTT ALL-WAVE 15-550 METER Superhetrodyne

The E. H. Scott Radio Laboratories, Inc.
4450 Ravenswood Ave., Dept. CB52, Chicago, Ill.

Send me full particulars of the Scott All-Wave, 15-550 meter Superhetrodyne.


DXER SET BUILDER DEALER

Name

Street

Town.....State.....

Readrite

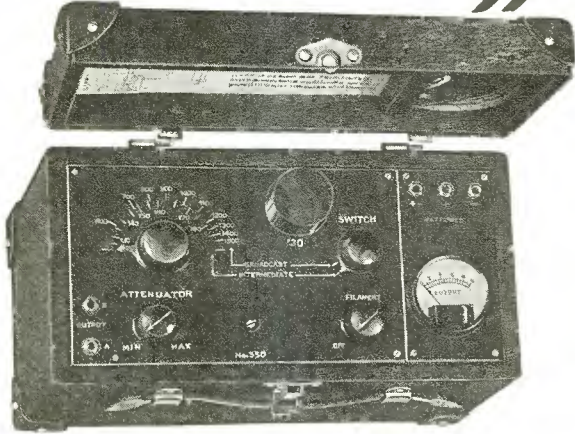

Licensed by A. T. & T. Co.

RADIO SERVICE TEST OSCILLATOR

Indispensable to the Serviceman

**A REMARKABLE INSTRUMENT
AT A POPULAR PRICE**

No. 551

\$18 Net to Dealer
\$30 List

No. 550

\$21 Net to Dealer
With Output Meter

YOU cannot service a present day super-heterodyne without the use of an Oscillator, and this Readrite Test Oscillator will fulfill your every need.

A sturdy modulated instrument, carefully made. Completely shielded with separate battery compartment. Furnished with 22½ v. and 3 volt batteries and one '30 tube. Reads directly broadcast band (550-1500 k. c.) and intermediate band (120-185 k. c.). Other i. f.'s obtained by sharp harmonics. Operating instructions attached in case cover with shielded wire leads.

Very compact, light weight and easy to handle. Comes in strong leatherette case

6 x 11½ x 5½ inches. It is made not only of the best materials throughout and assembled for lasting durability, but its beautiful and trim appearance will be the pride of every serviceman to own and use.

One of the serviceman's most important instruments. Used to align r. f. gang condensers, locate defective r. f. transformers, adjust i. f. transformers, check oscillator stage, compare gain in tubes and determine the sensitivity of a receiver. Furnished with or without output meter built in the panel. A truly remarkable instrument at a remarkable price. Get yours today!

Write for Catalog of Servicing Instruments

READRITE METER WORKS

Established 1904

10 College Avenue

BLUFFTON, OHIO

OPPORTUNITIES *are many* for the Radio Trained Man

Don't spend your life slaving away in some dull, hopeless job! Don't be satisfied to work for a mere \$20 or \$30 a week. Let me show you how to get your start in Radio—the fastest-growing, biggest money-making game on earth.

Jobs Leading to Salaries of \$50 a Week and Up
Prepare for jobs as Designer, Inspector and Tester—as Radio Salesman and in Service and Installation Work—as Operator or Manager of a Broadcasting Station—as Wireless Operator on a Ship or Airplane, or in Talking Picture or Sound Work—HUNDREDS of OPPORTUNITIES for a real future in Radio!

Ten Weeks of Shop Training

We don't teach by book study. We train you on a great outlay of Radio, Television and Sound equipment—on scores of modern Radio Receivers, huge Broadcasting equipment, the very latest and newest Television apparatus, Talking Picture and Sound Reproduction equipment, Code Practice equipment, etc. You don't need advanced education or previous experience. We give you—**RIGHT HERE IN THE COYNE SHOPS**—the actual practice and experience you'll need for your start in this great field. And because we cut out all useless theory and only give that which is necessary you get a practical training in 10 weeks.



TELEVISION *and* TALKING PICTURES

And Television is already here! Soon there'll be a demand for THOUSANDS of TELEVISION EXPERTS! The man who learns Television now can have a great future in this great new field. Get in on the ground-floor of this amazing new Radio development! Come to COYNE and learn Television on the very latest, new-

est Television equipment. Talking Picture and Public Address Systems offer opportunities to the Trained Radio Man. Here is a great new Radio field just beginning to grow! Prepare NOW for these wonderful opportunities! Learn Radio Sound Work at COYNE on actual Talking Picture and Sound Reproduction equipment.



All Practical Work At COYNE In Chicago

ALL ACTUAL, PRACTICAL WORK. You build radio sets, install and service them. You actually operate great Broadcasting equipment. You construct Television Receiving Sets and actually transmit your own Television programs over our modern Television equipment. You work on real Talking Picture machines and Sound equipment. You learn Wireless Operating on actual Code Practice apparatus. We don't waste time on useless theory. We give you the practical training you'll need—in 10 short, pleasant weeks.

Many Earn While Learning

You get Free Employment Service for Life. And don't let lack of money stop you. Many of our students make all or a good part of their living expenses while going to school and if you should need this help just write to me. Coyne is 32 years old! Coyne Training is tested—proven beyond all doubt. You can find out everything absolutely free. Just mail coupon for my big free book!

H. C. Lewis, Pres. **RADIO DIVISION** Founded 1899
COYNE Electrical School
500 S. Paulina St., Dept. 52-5H, Chicago, Ill.

Mail Coupon Today for All the Facts

H. C. LEWIS, President
Radio Division, Coyne Electrical School
500 S. Paulina St., Dept. 52-5H, Chicago, Ill.

Dear Mr. Lewis:— Send me your Big Free Radio Book, and all details of your Special Offer.

Name.....

Address.....

City..... State.....

Radio Call Book Magazine

AND TECHNICAL REVIEW

Established 1921

Advertising Representatives

Chicago—C. O. STIMPSON, Adv. Mgr.
Phone Wabash 1901, 508 South Dearborn St.
New York—J. J. LAMSON,
Phone Wisconsin 7-5681,
Room 1125, 154 West 42nd St.
Los Angeles—NED BRYDONE-JACK,
Petroleum Securities Bldg.
San Francisco—THOMAS EMORY, Russ Bldg.

Executive Offices:

508 So. Dearborn St., Chicago, Ill.
Member Audit Bureau of Circulations

GEO. H. SCHEER, JR., *Editor*
E. H. PETERSON, *Service Dept.*

MAY, 1932

Vol. 13, No. 5

Table of Contents

U. S. Broadcasting Stations . . .	6-9	United American Bosch 5 . .	27
U. S. Broadcasting Stations by Frequencies	10	Webster 6043-R Amplifier .	28
U. S. Broadcasting Stations by States and Cities	11	Service and Repair Section . . .	29-30
List of Police Broadcasting Stations	12	Photronic Cell Experiments . .	30
U. S. Visual Broadcasting Sta- tions	12	C Bias Elimination	31
U. S. Relay Broadcasting Sta- tions	12	Majestic 175kc Oscillator . . .	31
Simple Time Chart	12	Capacity Decade Box	32
Foreign Broadcasting Stations.	13-14	Set Tester	33
Foreign Short Wave Phone Stations	15	Signal Generator for Service Men	34-35
Speech Input Equipment	16-17	Radio Engineering Section . . .	36-37
Receiver Performance Curve Section	18	841 Class B and Class C Char- acteristics	38
All American Mohawk, Lyric S-7	19	Speed Television Lamp	38
Balkeit L-8	20	864 Rating and Characteristics	38
Crosley 27	21	Status of Television	39
Perfectone 7-T-38	22	234 Rating and Characteristics	40
Philco 51	23	Mercury Full-wave Rectifiers .	41
RCA-Victor Radiola 43 . . .	24	Receiver Voltage Analyses . . .	42-44
Silver-Marshall Q	25	New Products Section	45-47
Stromberg-Carlson 29	26	Brief Items Section	48-57
		Blue Print Page	60
		Index to Advertisers	62

Editorial

This issue should appeal very strongly to all classes of our readers because of the varied editorial content. First of all, there appears a list of stations by states and cities, for which we have received many calls, the most interesting of which concerns engineers and the problem of images in congested broadcast areas. Now, at a glance, it will be possible to predetermine the likely difficulties, and provide the necessary selectivity and intermediate frequency to minimize such conditions.

An illuminating article on Speech Input Equipment, fully illustrated, should be of interest to those building or installing sound systems for public address, theaters, recording on films and records, etc. Another Power Amplifier appears on page 28, made by Webster Electric Company.

For the experimenter, we are beginning a series of ten consecutive articles on how to use the Weston Photronic Cell for useful as well as instructive purposes. This cell, described in detail in past issues, is an innovation in the photoelectric cell field, since it requires absolutely no voltage supply itself, and furnishes enough power output to operate a relay directly.

Audio degeneration may be overcome by using a system of separate bias supply for audio amplifier tubes found on page 31. On this same page is a complete oscillator for intermediate frequency alignment purposes. Another set tester, a service man's signal generator, new tube characteristics, real status of television at present, and mercury vapor full wave rectifiers are some additional subjects found in this issue.

May we ask you to give us your candid opinion so that we may better serve you? Perhaps you agree or disagree with some of the letters given in the Brief Items columns. It is your outlet to let the other fellow know what you think yourself or about his ideas. Don't neglect this voice which serves to show the trend of thought of our readers.—EDITOR.

will train you at home

to fill a

BIG PAY Radio Job!



Here's Proof



\$100 a week

"My earnings in Radio are many times greater than I ever expected they would be when I enrolled. They seldom fall under \$100 a week. If your course cost four or five times more I would still consider it a good investment."

E. E. WINBORNE
1267 W. 48th St.,
Norfolk, Va.



Jumped from \$35 to \$100 a week

"Before I entered Radio I was making \$35 a week. Last week I earned \$110 servicing and selling Radios. I owe my success to N. R. I. You started me off on the right foot."

J. A. VAUGHN
Grand Radio & Appliance Co., 3107 S. Grand Blvd.,
St. Louis, Mo.



\$500 extra in 6 months

"In looking over my records I find I made \$500 from January to May in my spare time. My best week brought me \$107. I have only one regret regarding your course—I should have taken it long ago."

HOYT MOORE
R. R. 3, Box 919,
Indianapolis, Ind.

If you are dissatisfied with your present job, if you are struggling along in a rut with little or no prospect of anything better than a skinny pay envelope—clip the coupon NOW. Get my big FREE book on the opportunities in Radio. Read how quickly you can learn at home in your spare time to be a Radio Expert—what good jobs my graduates have been getting—real jobs with real futures.

Many Radio Experts Make \$50 to \$100 a week

In about ten years the Radio Industry has grown from \$2,000,000 to hundreds of millions of dollars. Over 300,000 jobs have been created by this growth, and thousands more will be created by its continued development. Many men and young men with the right training—the kind of training I give you in the N. R. I. course—have stepped into Radio at two and three times their former salaries.

Get Ready now for Jobs Like These

Broadcasting stations use engineers, operators, station managers, and pay up to \$5,000 a year. Manufacturers continually employ testers, inspectors, foremen, engineers, service men, buyers, for jobs paying up to \$6,000 a year. Radio Operators on ships enjoy life, see the world, with board and lodging free, and get good pay besides. Dealers and jobbers employ service men, salesmen, buyers, managers, and pay up to \$100 a week. My book tells you about these and many other kinds of interesting radio jobs.

Many N. R. I. Men Have made \$200 to \$1,000 in spare time while learning

The day you enroll I send you material which you should master quickly for doing 28 jobs, common in most every neighborhood, for spare time money. Throughout your course I send you information on servicing popular makes of sets; I give you the plans and ideas that have made \$200 to \$1,000 for N. R. I. students in their spare time while studying. My course is famous as the course that pays for itself.

Talking Movies, Television, Aircraft Radio included

Special training in Talking Movies, Television and Home Television experiments, Radio's use in Aviation, Servicing and Merchandising Sets, Broadcasting, Commercial and Ship Stations are included. I am so sure that N. R. I. can train you satisfactorily that I will agree in writing to refund every penny of your tuition if you are not satisfied with my Lessons and Instruction Service upon completion.

64-page book of information FREE

Get your copy today. It tells you where Radio's good jobs are, what they pay, tells you about my course, what others who have taken it are doing and making. Find out what Radio offers you without the slightest obligation. ACT NOW!


J. E. SMITH, President
National Radio Institute Dept., 2EE
Washington, D. C.

Our Own Home

Pioneer and World's Largest Home-Study Radio training organization devoted entirely to training men and young men for good jobs in the Radio industry. Our growth has paralleled Radio's growth. We occupy three hundred times as much floor space now as we did when organized in 1914.



Special Free Offer!

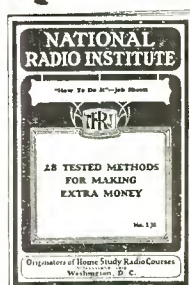


Act Quickly!

In addition to my big free book, "Rich Rewards in Radio," I'll send you my valuable manual "28 Tested Methods for Making Extra Money." Never before available except to students. Now, for a limited time, it is free to readers of this magazine. How to make a good battle for come speakers, how to reduce hum in externally fed dynamic speakers, how to operate 25 cycle apparatus on 60 cycle current, how to operate 110 v. A. C. receivers on D. C., how to shield sets from local interference are five of the subjects covered. There are 23 others. Get this valuable book by mailing the coupon.

.. NEW Radio Equipment for Broad Practical Experience Given Without Extra Charge

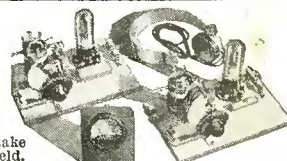With this equipment you work out many of the things you read about in your text books. From it you get the valuable experience that tells an expert from a beginner. In a short time you have learned what would take years to learn in the field. You make experiments illustrating the important principles in the 25 best known receiving sets.



I have doubled and tripled the salaries of many. Find out about this tested way to BIGGER PAY



FILL OUT AND MAIL THIS COUPON TODAY

J. E. SMITH, President
National Radio Institute, Dept. 2EE
Washington, D. C.

Dear Mr. Smith: I want to take advantage of your Special Offer. Send me your two books, "Twenty-Eight Tested Methods for Making Extra Money" and "Rich Rewards in Radio." I understand this does not obligate me and that no salesman will call.

Name.....
Address.....
City..... State..... "J"

Lifetime Employment Service to all Graduates

American Broadcasting Stations

Station assignments shown in the following pages were made by the Federal Radio Commission. This list is revised from issue to issue and is therefore up-to-the-minute. Initials such as E, C, M, and P denote Eastern, Central, Mountain and Pacific time.

- KABC**—1420 kc, San Antonio, Texas, Alamo Broadcasting Co., 100 w, C.
- KARK**—890 kc, Little Rock, Ark., Arkansas Radio & Equip. Co., 250 w.
- KBPS**—1420 kc, Portland, Ore., Benson Polytechnic School, 100 w, P.
- KBTM**—1200 kc, Paragould, Ark., Beard's Temple of Music, 100 w, C.
- KCMC**—1420 kc, Tupelo, Miss., No. Miss. Bdstg. Corp., 100 w, C.
- KCRC**—1370 kc, Enid, Okla., Champlin Refining Co., 100 w, C.
- KCRJ**—1310 kc, Jerome, Ariz., C. C. Robinson, 100 w.
- KDB**—1500 kc, Santa Barbara, Calif., Santa Barbara Broadcasters, Ltd., 100 w, P.
- KDFN**—1440 kc, Casper, Wyo., D. L. Hathaway, 500 w, P.
- KDKA**—980 kc, Pittsburgh, Pa., Westinghouse E. & M. Co., 50,000 w, E.
- KDLR**—1210 kc, Devils Lake, N. D., KDLR, Inc., 100 w.
- KDYL**—1290 kc, Salt Lake City, Utah, Intermountain Broadcasting Corp., 1000 w, M.
- KECA**—1430 kc, Los Angeles, Calif., Earle C. Anthony, Inc., 1000 w, P.
- KELW**—780 kc, Burbank, Calif., Magnolia Park, Ltd., 500 w, P.
- KERN**—1200 kc, Santa Maria, Cal., The Bee Bakersfield Bdstg. Co., 100 w, P.
- KEX**—1180 kc, Portland, Ore., Western Broadcasting Co., 5000 w, P.
- KEAB**—770 kc, Lincoln, Nebr., KFAB Broadcasting Co., 5000 w, C.
- KFAC**—1300 kc, Los Angeles, Calif., L. A. Bdstg. Co., 1000 w, P.
- KFBB**—1280 kc, Great Falls, Mont., Buttre Broadcast, Inc., 1000 w, M.
- KFBK**—1310 kc, Sacramento, Calif., James McClatchy Co., 100 w, P.
- KFBL**—1370 kc, Everett, Wash., Leese Bros., 50 w, P.
- KFDM**—560 kc, Beaumont, Tex., Magnolia Petroleum Co., 500 w, C.
- KFDY**—550 kc, Brookings, S. D., State College, 500 w, C.
- KFEL**—920 kc, Denver, Colo., Eugene P. O'Fallon, Inc., 500 w, M.
- KFEQ**—680 kc, St. Joseph, Mo., Scroggin & Co., 2500 w, C.
- KFGQ**—1310 kc, Boone, Iowa, Boone Biblical College, 100 w, C.
- KFH**—1300 kc, Wichita, Kan., Radio Station KFH Co., 1000 w, C.
- KFI**—640 kc, Los Angeles, Calif., Earl C. Anthony, Inc., 50,000 w, P.
- KFIO**—1120 kc, Spokane, Wash., Spokane Broadcasting Corp., 100 w, P.
- KFNU**—1310 kc, Juneau, Alaska, Alaska Elce. Light & Power Co., 10 w.
- KFIZ**—1420 kc, Fond du Lac, Wis., Reporter Printing Co., 100 w, C.
- KFJB**—1200 kc, Marshalltown, Iowa, Marshall Electric Co., 100 w, C.
- KFJF**—1480 kc, Oklahoma City, Okla., National Radio Mfg. Co., 5000 w, C.
- KFJI**—1210 kc, Klamath Falls, Ore., KFJI Broadcasters, Inc., 100 w, P.
- KFJM**—1370 kc, Grand Forks, N. D., University of North Dakota, 100 w, C.
- KFJR**—1300 kc, Portland, Ore., Ashley C. Dixon, KFJR, Inc., 500 w, P.
- KFJY**—1310 kc, Ft. Dodge, Iowa, Cedar Rapids Broadcast Co., w, C.
- KFJZ**—1370 kc, Ft. Worth, Texas, Ralph S. Bishop, 100 w, C.
- KFKA**—880 kc, Greeley, Colo., Mid-Western Radio Corp., 500 w, M.
- KFKB**—1050 kc, Milford, Kan., KFKB Bdstg. Assn., 5000 w, C.
- KFKU**—1220 kc, Lawrence, Kan., University of Kansas, 500 w, C.
- KFLV**—1410 kc, Rockford, Ill., Rockford Broadcasters, Inc., 500 w, C.
- KFLX**—1370 kc, Galveston, Texas, Geo. Roy Clough, 100 w, C.
- KFMX**—1250 kc, Northfield, Minn., Carleton College, 1000 w, C.
- KFNF**—890 kc, Shenandoah, Iowa, Henry Field Seed Co., 500 w, C.
- KFOR**—1210 kc, Lincoln, Neb., Howard A. Shuman, 100 w, C.
- KFOX**—1250 kc, Long Beach, Calif., Nichols & Warriner, Inc., 1000 w, P.
- KFPL**—1310 kc, Dublin, Texas, C. C. Baxter, 100 w, C.
- KFPM**—1310 kc, Greenville, Texas, The New Furniture Co., 15 w, C.
- KFPW**—1340 kc, Ft. Smith, Ark., John Brown Schools, 50 w, C.
- KFPY**—1340 kc, Spokane, Wash., Symons Broadcasting Co., 1000 w, P.
- KFQD**—1230 kc, Anchorage, Alaska, Anchorage Radio Club, 100 w.
- KFQW**—1420 kc, Seattle, Wash., KFQW, Inc., 100 w, P.
- KFRG**—610 kc, San Francisco, Calif., Don Lee, Inc., 1000 w, P.
- KFRU**—630 kc, Columbia, Mo., Stephens College, 500 w, C.
- KFSD**—600 kc, San Diego, Calif., Airfan Radio Corp., 500 w, P.
- KFSG**—1120 kc, Los Angeles, Calif., Echo Park Eyan, Assn., 500 w, P.
- KFUL**—1290 kc, Galveston, Texas, W. H. Ford, 500 w, C.
- KFUO**—550 kc, St. Louis, Mo., Concordia Theological Seminary, 500 w, C.
- KFUP**—1310 kc, Denver, Colo., Fitzsimmons General Hospital, 100 w, M.
- KFVD**—1000 kc, Culver City, Calif., Los Angeles Broadcasting Co., 250 w, P.
- KFVS**—1210 kc, Cape Girardeau, Mo., Hirsch Battery & Radio Co., 100 w, C.
- KFWB**—950 kc, Hollywood, Calif., Warner Bros. Broadcasting Corp., 1000 w, P.
- KFWF**—1200 kc, St. Louis, Mo., St. Louis Truth Center, Inc., 100 w.
- KFWI**—930 kc, San Francisco, Calif., Radio Entertainments, Inc., 500 w, P.
- KFXD**—1420 kc, Nampa, Idaho, Frank E. Hurt, 100 w, M.
- KFXF**—920 kc, Denver, Colo., Colorado Radio Co., 500 w, M.
- KFXJ**—1310 kc, Edgewater, Colo., Western Slope Broadcasting Co., 50 w, M.
- KFXM**—1210 kc, San Bernardino, Calif., Lee Bros. Broadcasting Co., 100 w, P.
- KFXR**—1310 kc, Oklahoma City, Okla., Exchange Avenue Baptist Church, 100 w, C.
- KFXZ**—1420 kc, Flagstaff, Ariz., Mary M. Costigan, 100 w, M.
- KFYO**—1420 kc, Abilene, Texas, Kirksey Bros., 100 w, C.
- KFYR**—550 kc, Bismarck, N. D., Meyer Broadcasting Co., 1000 w, C.
- KGA**—1470 kc, Spokane, Wash., Northwest Broadcasting System, Inc., 5000 w, P.
- KGAR**—1370 kc, Tucson, Ariz., Tucson Motor Service Co., 100 w, M.
- KGB**—1330 kc, San Diego, Calif., Don Lee, Inc., 500 w, P.
- KGBU**—900 kc, Ketchikan, Alaska, Alaska Radio & Service Co., 500 w.
- KGBX**—1310 kc, St. Joseph, Mo., KGBX, Inc., 100 w.
- KGBZ**—930 kc, York, Nebr., Geo. R. Miller, 500 w, C.
- KGCA**—1270 kc, Decorah, Iowa, Chas. W. Greenley, 50 w, C.
- KGCR**—1210 kc, Watertown, S. D., Greater Kampeka Radio Corp., 100 w.
- KGCU**—1240 kc, Mandan, N. D., Mandan Radio Association, 250 w, M.
- KGDX**—1310 kc, Wolf Point, Mont., First State Bank of Vida, 100 w, M.
- KGDA**—1370 kc, Mitchell, S. D., Mitchell Broadcasting Corp., 100 w, M.
- KGDE**—1200 kc, Fergus Falls, Minn., Jaren Drug Co., 100 w, C.
- KGDM**—1100 kc, Stockton, Calif., E. F. Peffer, 250 w.
- KGDY**—1200 kc, Huron, S. D., J. A. Loesch, 15 w, C.
- KGEF**—1300 kc, Los Angeles, Calif., Trinity Methodist Church, 1000 w, P.
- KGEG**—1200 kc, Yuma, Colo., Beehler Elec. Equip. Co., 100 w, M.
- KGER**—1360 kc, Long Beach, Calif., Consolidated Bdstg. Corp., 1000 w, P.
- KGEW**—1200 kc, Kearney, Nebr., 100 w, P.
- KGEZ**—1310 kc, Kalispell, Mont., Donald C. Treloar, 100 w, M.
- KGFF**—1420 kc, Shawnee, Okla., KGFF Bdstg. Corp., 100 w, C.
- KGFG**—1370 kc, Oklahoma City, Okla., Oklahoma Broadcasting Co., Inc., 100 w, C.
- KGFI**—1500 kc, Corpus Christi, Texas, Eagle Broadcasting Co., 100 w, C.
- KGFL**—1200 kc, Los Angeles, Calif., Ben S. McGlashan, 100 w, P.
- KGFK**—1500 kc, Moorhead, Minn., Red River Broadcasting Co., Inc., 50 w, C.
- KGFL**—1370 kc, Raton, N. Mex., KGFL, Inc., 50 w, M.
- KGFW**—1310 kc, Kearney, Neb., Central Neb. Bdstg. Co., 100 w.
- KGFX**—630 kc, Pierre, S. D., Dana McNeil, 200 w, C.
- KGGC**—1420 kc, San Francisco, Calif., Golden Gate Broadcasting Co., 100 w, P.
- KGGE**—1010 kc, South Coffeyville, Okla., Powell & Platz, 500 w.
- KGGM**—1230 kc, Albuquerque, N. Mex., New Mexico Broadcasting Co., 250 w.
- KGHF**—1320 kc, Pueblo, Colo., Ritchie & Finch, 250 w, M.
- KGHI**—1200 kc, Little Rock, Ark., O. A. Cook, 100 w.
- KGHL**—950 kc, Billings, Mont., Northwestern Auto Supply Co., 1000 w, M.
- KGII**—1320 kc, Twin Falls, Idaho, Radio Broadcasting Corp.
- KGIR**—1360 kc, Butte, Mont., KGIR, Inc., 500 w, M.
- KGIV**—1420 kc, Trinidad, Colo., Leonard E. Wilson, 100 w, M.
- KGIX**—1420 kc, Las Vegas, Nev., J. M. Heaton, 100 w.
- KGIZ**—1500 kc, Grant City, Mo., Grant City Park Corp., 100 w, C.
- KGKB**—1500 kc, Tyler, Tex., Tyler Commercial College, 100 w, C.
- KGKL**—1370 kc, San Angelo, Tex., KGKL, Inc., 100 w, C.
- KGKO**—570 kc, Wichita Falls, Tex., Wichita Falls Broadcasting Co., 250 w, C.
- KGKX**—1420 kc, Sandpoint Idaho, W. W. von Cannon, 100 w, P.
- KGKY**—1500 kc, Scottsbluff, Nebr., Hilliard Co., Inc., 100 w, C.
- KGMB**—1320 kc, Honolulu, Hawaii, Honolulu Broadcasting Co., 250 w, P.
- KGMP**—1210 kc, Elk City, Okla., Bryant Radio & Elec. Co., 100 w, C.
- KGNF**—1430 kc, North Platte, Nebr., H. L. Spencer, 500 w, M.
- KGNO**—1210 kc, Dodge City, Kans., Dodge City Broadcasting Co., Inc., M.
- KGO**—790 kc, San Francisco, Calif., National Broadcasting Co., Inc., 7500 w, P.
- KGRS**—1410 kc, Amarillo, Texas, Gish Radio Service, 1000 w, C.
- KGU**—750 kc, Honolulu, Hawaii, Marion Mulroney, Advertising Publ. Co., 2500 w.
- KGVO**—1420 kc, Missoula, Mont., Mosby's, Inc.
- KGW**—620 kc, Portland, Ore., Oregonian Pub. Co., 1000 w, P.
- KGY**—1200 kc, Lacey, Wash., KGY, Inc., 100 w, P.
- KHJ**—900 kc, Los Angeles, Calif., Don Lee, Inc., 1000 w, P.
- KHQ**—590 kc, Spokane, Wash., Louis Wasmmer, Inc., 1000 w, P.
- KICA**—1370 kc, Clovis, N. M., W. E. Whitmore, 100 P.
- KICK**—1420 kc, Red Oak, Iowa, Red Oak Radio Corp., 100 w.
- KID**—1320 kc, Idaho Falls, Ida., KID Broadcasting Co., 250 w, M.
- KIDO**—1350 kc, Boise, Idaho, Boise Broadcasting Station, 1000 w, P.
- KIP**—1310 kc, Yakima, Wash., C. E. Haymond, 100 w, P.
- KJBS**—1070 kc, San Francisco, Calif., Julius Brunton & Sons Co., 100 w, P.
- KJR**—970 kc, Seattle, Wash., Northwest Broadcasting System, Inc., 5000 w, P.
- KLCN**—1290 kc, Blytheville, Ark., C. L. Lintzenich, 50 w, C.
- KLO**—1400 kc, Ogden, Utah, Interstate Bdstg. Corp., 500 w, M.
- KLPM**—1420 kc, Minot, N. D., John B. Cooley, 100 w, C.
- KLRA**—1390 kc, Little Rock, Ark., Arkansas Broadcasting Co., 1000 w.
- KLS**—1440 kc, Oakland, Calif., Warner Bros., 250 w, P.
- KLX**—880 kc, Oakland, Calif., Tribune Pub. Co., 500 w, P.
- KLZ**—560 kc, Denver, Colo., Reynolds Radio Co., Inc., 1000 w, M.
- KMA**—930 kc, Shenandoah, Iowa, May Seed & Nursery Co., 500 w, C.
- KMAC**—1370 kc, San Antonio, Texas, W. W. McAllister, 100 w, C.
- KMBC**—950 kc, Kansas City, Mo., Midland Broadcasting Co., 1000 w, C.
- KMED**—1310 kc, Medford, Ore., Mrs. W. J. Virgin, 100 w, P.
- KMJ**—1210 kc, Fresno, Calif., J. McClatchy Co., 100 w, P.
- KMLB**—1200 kc, Monroe, La., Liner's Bdstg. Station, Inc., 100 w, C.

- KMMJ**—740 kc, Clay Center, Neb., The M. M. Johnson Co., 1000 w, C.
- KMO**—860 kc, Tacoma, Wash., KMO, Inc., 500 w, P.
- KMOX**—1090 kc, St. Louis, Mo., Voice of St. Louis, Inc., 50,000 w, C.
- KMPCC**—710 kc, Beverly Hills, Calif., R. S. Macmillan, 500 w, P.
- KMTR**—570 kc, Los Angeles, Calif., KMTR Radio Corp., 500 w, P.
- KNOW**—1500 kc, Austin, Tex., KNOW Bdstg. Co., 100 w, C.
- KNX**—1050 kc, Hollywood, Calif., Western Broadcast Co., 5000 w, P.
- KOA**—830 kc, Denver, Colo., National Broadcasting Co., Inc., 12,500 w, M.
- KOAC**—550 kc, Corvallis, Ore., Oregon State Agricultural College, 1000 w, P.
- KOB**—1180 kc, State College, N. M., N. M. College of Agri. & Mech. Arts, 20,000 w, M.
- KOCW**—1400 kc, Chickasha, Okla., Oklahoma College for Women, 250 w, C.
- KOH**—1370 kc, Reno, Nevada, Jay Peters, Inc., 500 w.
- KOIL**—1260 kc, Council Bluffs, Iowa, Mona Motor Oil Co., 1000 w, C.
- KOIN**—940 kc, Portland, Ore., KOIN, Inc., 1000 w, P.
- KOL**—1270 kc, Seattle, Wash., Seattle Broadcasting Co., 1000 w, P.
- KOMO**—920 kc, Seattle, Wash., Fisher's Blend Station, Inc., 1000 w, P.
- KONO**—1370 kc, San Antonio, Tex., Mission Broadcasting Co., 100 w, C.
- KOOS**—1370 kc, Marshfield, Ore., H. H. Hanseth, Inc., 100 w, P.
- KORE**—1420 kc, Eugene, Ore., Eugene Broadcast Station, 100 w, P.
- KOY**—1390 kc, Phoenix, Ariz., Nielsen Radio & Sporting Goods Co., 500 w, M.
- KPCB**—650 kc, Seattle, Wash., Queen City Broadcasting Co., 100 w, P.
- KPJM**—1500 kc, Prescott, Ariz., A. P. Miller, 100 w, M.
- KPO**—680 kc, San Francisco, Calif., Hale Bros. & The Chronicle, 5000 w, P.
- KPOF**—880 kc, Denver, Colo., Pillar of Fire, Inc., 500 w, M.
- KPPC**—1210 kc, Pasadena, Calif., Pasadena, Presbyterian Church, 50 w, P.
- KPQ**—1500 kc, Wenatchee, Wash., West-coast Broadcasting Co., 50 w, P.
- KPRC**—920 kc, Houston, Texas, Houston Printing Co., 1000 w, C.
- KQV**—1380 kc, Pittsburgh, Pa., KQV Bdstg. Co., 500 w, E.
- KQW**—1010 kc, San Jose, Calif., Pacific Agric. Foundation, 500 w, P.
- KRE**—1370 kc, Berkeley, Calif., First Congregational Church, 100 w, P.
- KREG**—1500 kc, Santa Ana, Calif., Pacific-Western Broadcasting Federation, 100 w, P.
- KRGV**—1260 kc, Harlingen, Texas, KRGV, Inc., 500 w.
- KRRD**—1120 kc, Inglewood, Cal., Dalton's, Inc., P.
- KRLD**—1040 kc, Dallas, Texas, KRLD, Inc., 10,000 w, C.
- KRMD**—1310 kc, Shreveport, La., Robert M. Dean, 50 w, C.
- KROW**—930 kc, Oakland Calif., Educational Broadcasting Corp., 500 w, M.
- KRSC**—1120 kc, Seattle, Wash., Radio Sales Corp., 50 w, P.
- KSAC**—580 kc, Manhattan, Kan., Kansas State Agricultural College, 500 w, C.
- KSCJ**—1330 kc, Sioux City, Iowa, Perkins Bros. Co., 1000 w, C.
- KSD**—550 kc, St. Louis, Mo., Pulitzer Pub. Co., 500 w, C.
- KSEI**—900 kc, Pocatello, Idaho, Radio Service Corp., 250 w, M.
- KSL**—1130 kc, Salt Lake City, Utah, Radio Service Corp., 5000 w, M.
- KSO**—1380 kc, Clarinda, Iowa, Iowa Bdstg. Co., 500 w, C.
- KSOO**—1110 kc, Sioux Falls, S. D., Sioux Falls Broadcasting Assn., 2000 w, C.
- KSTP**—1460 kc, St. Paul, Minn., National Battery Broadcasting Co., 10,000 w, C.
- KTAB**—560 kc, San Francisco, Calif., Associated Broadcasters, 1000 w, P.
- KTAR**—620 kc, Phoenix, Ariz., KTAR Broadcasting Co., 500 w, M.
- KTAT**—1240 kc, Ft. Worth, Tex., S. A. T. Broadcasting Co., 1000 w, C.
- KTBR**—1300 kc, Portland, Ore., M. E. Brown, 500 w, P.
- KTBS**—1450 kc, Shreveport, La., Tri-State Broadcasting Co., 1000 w, E.
- KTFI**—1240 kc, Twin Falls, Idaho, Radio Broadcasting Corp., 250 w, M.
- KTIS**—1040 kc, Hot Springs, Ark., Chamber of Commerce, 10,000 w, C.
- KTLC**—1310 kc, Houston, Tex., Houston Broadcasting Co., 100 w, C.
- KTM**—780 kc, Los Angeles, Calif., Pickwick Broadcasting Corp., 500 w, P.
- KTRH**—1120 kc, Houston, Tex., Rice Hotel, 500 w, C.
- KTSA**—1290 kc, San Antonio, Texas, Lone Star Broadcast Co., 1000 w, C.
- KTSL**—1310 kc, Shreveport, La., Houseman Sheet Metal Works, Inc., 100 w, C.
- KTSM**—1310 kc, El Paso, Tex., W. S. Bledsoe and W. T. Blackwell, 100 w, C.
- KTW**—1220 kc, Seattle, Wash., First Presbyterian Church, 1000 w, P.
- KUJ**—1370 kc, Walla Walla, Wash., KUJ, Inc., 100 w, P.
- KUOA**—1390 kc, Fayetteville, Ark., University of Arkansas, 1000 w, C.
- KUSD**—890 kc, Vermilion, S. Dak., University of South Dakota, 500 w, C.
- KVI**—760 kc, Tacoma, Wash., Puget Sound Radio Broadcasting Co., 1000 w, P.
- KVL**—1370 kc, Seattle, Wash., KVL, Inc., 100 w, P.
- KVOA**—1260 kc, Tucson, Ariz., R. M. Ricaldi, 500 w.
- KVOO**—1140 kc, Tulsa, Okla., Southwestern Sales Corp., 5000 w, C.
- KVOR**—1270 kc, Colorado Springs, Colo., W. D. Corley, 1000 w, M.
- KVOS**—1200 kc, Bellingham, Wash., KVOS, Inc., 100 w, P.
- KWCR**—1310 kc, Cedar Rapids, Iowa, Cedar Rapids Bdstg. Co., 100 w, C.
- KWEA**—1210 kc, Shreveport, La., Hello World Broadcasting Corp., 100 w, C.
- KWG**—1200 kc, Stockton, Calif., Portable Wireless Tel. Co., 100 w, P.
- KWJJ**—1060 kc, Portland, Ore., KWJJ Broadcasting Co., Inc., 500 w, P.
- KWK**—1350 kc, Kirkwood, Mo., Thos. Patrick, Inc., 1000 w, C.
- KWKK**—1370 kc, Kansas City, Mo., Wilson Duncan Broadcasting Co., 100 w.
- KWKH**—850 kc, Shreveport, La., Hello World Broadcasting Corp., 10,000 w, C.
- KWLC**—1270 kc, Decorah, Iowa, Luther College, 100 w, C.
- KWSC**—1220 kc, Pullman, Wash., State College of Washington, 1000 w, P.
- KWWW**—1260 kc, Brownsville, Texas, Brownsville Herald Publishing Co., 500 w, C.
- KXA**—570 kc, Seattle, Wash., American Radio Tel. Co., 500 w, P.
- KXL**—1420 kc, Portland, Ore., KXL Broadcasters, Inc., 100 w, P.
- KXO**—1500 kc, El Centro, Calif., Irey & Bowles, 100 w, P.
- KYRO**—1310 kc, Aberdeen, Wash., KXRO, Inc., 100 w, P.
- KXYZ**—1420 kc, Houston, Texas, Harris County Broadcasting Co., 100 w, C.
- KYA**—1230 kc, San Francisco, Calif., Pacific Broadcasting Corp., 1000 w, P.
- KYW**—1020 kc, Chicago, Ill., Westinghouse E. & M. Co., 10,000 w, C.
- NAA**—690 kc, United States Navy Department, Washington, D. C., 1000 w, E.
- WAAB**—1410 kc, Quincy, Mass., Bay State Bdstg. Corp.
- WAAP**—920 kc, Chicago, Ill., Drivers Journal Pub. Co., 500 w daytime, C.
- WAAM**—1250 kc, Newark, N. J., WAAM, Inc., 1000 w, E.
- WAAT**—940 kc, Jersey City, N. J., Bremer Broadcasting Corp., 300 w, E.
- WAAW**—660 kc, Omaha, Neb., Omaha Grain Exchange, 500 w daytime, C.
- WABC**—860 kc, New York City, N. Y., Atlantic Broadcasting Corp., 50,000 w, E.
- WABI**—1200 kc, Bangor, Maine, Pine Tree Broadcasting Co., 100 w, E.
- WABO**—See under WHEC.
- WABZ**—1200 kc, New Orleans, La., Coliseum Place Baptist Church, 100 w, C.
- WACO**—1240 kc, Waco, Tex., Central Texas Broadcasting Co., Inc., 1000 w, C.
- WADC**—1320 kc, Tallmadge, Ohio, Allen T. Simmons, 1000 w, E.
- WAGM**—1420 kc, Presque Isle, Me., Aroostook Bdstg. Corp., 100 w.
- WAU**—640 kc, Columbus, Ohio, Associated Radiocasting Corp., 500 w, E.
- WALR**—1210 kc, Zanesville, O., Roy W. Waller, 100 w, E.
- WAPI**—1140 kc, Birmingham, Ala., Alabama Polytechnic Institute, 5000 w, C.
- WASH**—1270 kc, Grand Rapids, Mich., Kunsky-Trendle Bdstg. Corp., 500 w, C.
- WAWZ**—1350 kc, Zarepath, N. J., Pillar of Fire, 250 w, E.
- WBAA**—1400 kc, Lafayette, Ind., Purdue University, 500 w, C.
- WBAK**—1430 kc, Harrisburg, Pa., Pennsylvania State Police, 500 w, E.
- WBAL**—1060 kc, Baltimore, Md., Consolidated Gas, Elec. Co., 10,000 w, E.
- WBAP**—800 kc, Ft. Worth, Tex., Carter Publications, Inc., 10,000 w, C.
- WBAX**—1210 kc, Wilkes-Barre, Pa., John H. Stenger, Jr., 100 w, E.
- WBBC**—1400 kc, Brooklyn, N. Y., Brooklyn Broadcasting Corp., 500 w.
- WBBL**—1210 kc, Richmond, Va., Grace Covenant Presbyterian Church, 100 w, E.
- WBMM**—770 kc, Chicago, Ill., WBMM Bdstg. Corp., 25,000 w, C.
- WBRR**—1300 kc, Brooklyn, N. Y., People's Pulpit Association, 1000 w, E.
- WBZZ**—1200 kc, Ponca City, Okla., C. L. Carrell, 100 w, C.
- WBCM**—1410 kc, Bay City, Mich., James E. Davidson, 500 w, E.
- WBEN**—900 kc, Buffalo, N. Y., WBEN, Inc., 1000 w, E.
- WBEO**—1310 kc, Marquette, Mich., Lake Superior Bdstg. Co.
- WBGF**—1370 kc, Glens Falls, N. Y., W. Parker & N. Metcalf, 50 w, E.
- WBHS**—1200 kc, Huntsville, Ala., Hutchens Co., 50 w.
- WBIG**—1440 kc, Greensboro, N. C., North Carolina Broadcasting Co., 500 w, E.
- WBIS**—See under WNAC.
- WBMS**—1450 kc, Hackensack, N. J., WBMS Broadcasting Corp., 250 w.
- WBXX**—1350 kc, New York, N. Y., Standard Cahill Co., Inc., 250 w, E.
- WBOQ**—See under WABC.
- WBOW**—1310 kc, Terre Haute, Ind., Banks of Wabash, Inc., 100 w, C.
- WBRC**—930 kc, Birmingham, Ala., Birmingham Broadcasting Co., 500 w, C.
- WBRE**—1310 kc, Wilkes-Barre, Pa., Louis G. Baltimore, 100 w, E.
- WBRO**—920 kc, Needham, Mass., Bdstg. Service Org., Inc., 250 w, E.
- WBT**—1080 kc, Charlotte, N. C., Station WBT, Inc., 5000 w, E, shared.
- WBVM**—1370 kc, Danville, Va., Piedmont Bdstg. Corp., 100 w, E.
- WBZ**—990 kc, Boston, Mass., Westinghouse E. & M. Co., 25,000 w, E.
- WBZA**—990 kc, Springfield, Mass., Westinghouse E. & M. Co., 1000 w, E.
- WCAC**—600 kc, Storrs, Conn., Connecticut Agricultural College, 250 w, E.
- WCAD**—1220 kc, Canton, N. Y., St. Lawrence University, 500 w, E.
- WCAE**—1220 kc, Pittsburgh, Pa., WCAE, Inc., 1000 w, E.
- WCAH**—1430 kc, Columbus, Ohio, Commercial Radio Service Co., 500 w, E.
- WCAJ**—590 kc, Lincoln, Neb., Nebraska Wesleyan University, 500 w, C.
- WCAL**—1250 kc, Northfield, Minn., St. Olaf College, 1000 w, C.
- WCAM**—1280 kc, Camden, N. J., City of Camden, 500 w, E.
- WCAO**—600 kc, Baltimore, Md., Monumental Radio, Inc., 250 w, E.
- WCAP**—1280 kc, Asbury Park, N. J., Radio Industries Broadcast Co., 500 w, E.
- WCAT**—1200 kc, Rapid City, S. D., South Dakota State School of Mines, 100 w, M.
- WCAU**—1170 kc, Philadelphia, Pa., Universal Broadcasting Co., 50,000 w, E.
- WCAX**—1200 kc, Burlington, Vt., Burlington Daily News, 100 w, E.
- WCAZ**—1070 kc, Carthage, Ill., Superior Broadcasting Co., 50 w.
- WCBA**—1440 kc, Allentown, Pa., B. B. Musselman, 250 w, E.
- WCBD**—1080 kc, Zion, Ill., Wilbur Glen Voliva, 5000 w, C.
- WCBM**—1370 kc, Baltimore, Md., Baltimore Broadcasting Corp., 100 w, E.
- WCBS**—1210 kc, Springfield, Ill., Dewing & Meester, 100 w, C.
- WCCO**—810 kc, Minneapolis, Minn., Northwestern Broadcasting Inc., 5000 w, C.
- WCDA**—1350 kc, New York, N. Y., Italian Educational Broadcasting Co., 250 w, E.
- WCFL**—970 kc, Chicago, Ill., Chicago Federation of Labor, 15,000 w, C.
- WCGU**—1400 kc, Brooklyn, N. Y., U. S. Broadcasting Corp., 500 w, E.
- WCHI**—1490 kc, Chicago, Ill., People's Pulpit Association, 5000 w, C.
- WCKY**—1490 kc, Covington, Ky., L. B. Wilson, 500 w, E.
- WCLB**—1500 kc, Long Beach, N. Y., Arthur Faske, 100 w, E.
- WCLO**—1200 kc, Janesville, Wis., WCLO Radio Corp., 100 w, C.
- WCLS**—1310 kc, Joliet, Ill., WCLS, Inc., 100 w, C.
- WCMA**—1400 kc, Culver, Ind., General Broadcasting Co., 500 w, C.
- WCOA**—1340 kc, Pensacola, Fla., Pensacola Bdstg. Co., 500 w, E.
- WCOE**—880 kc, Meridian, Miss., Mississippi Broadcasting Co., 500 w, C.
- WCOD**—1200 kc, Harrisburg, Pa., Keystone Broadcasting Corp., 100 w, E.
- WCOH**—1210 kc, Yonkers, N. Y., Westchester Broadcasting Corp., 100 w, E.

- WCRW**—1210 kc, Chicago, Ill., Clinton R. White, 100 w, C.
- WCSC**—1360 kc, Charleston, S. C., Lewis Burk, 500 w, E.
- WCSH**—940 kc, Portland, Me., Congress Square Hotel Co., 1000 w, E.
- WDAE**—1220 kc, Tampa, Fla., Tampa Publishing Co., 1000 w, E.
- WDAF**—610 kc, Kansas City, Mo., Kansas City Star Co., 1000 w, C.
- WDAG**—1410 kc, Amarillo, Texas, National Radio & Broadcasting Corp., 250 w, C.
- WDAH**—1310 kc, El Paso, Texas, W. S. Bledsoe, 100 w, M.
- WDAS**—1370 kc, Philadelphia, Pa., WDAS Broadcasting Station, Inc., 100 w, E.
- WDAY**—940 kc, Fargo, N. D., WDAY, Inc., 1000 w, C.
- WDBJ**—930 kc, Roanoke, Va., Times-World Corp., 250 w, E.
- WDBO**—1120 kc, Orlando, Fla., Orlando Broadcasting Co., 250 w, E.
- WDEL**—1120 kc, Wilmington, Del., WDEL, Inc., 250 w, E.
- WDEV**—1420 kc, Waterbury, Vt., H. C. Whitehill, 50 w.
- WDGY**—1150 kc, Minneapolis, Minn., Dr. Geo. W. Young, 1000 w, C.
- WDIX**—1420 kc, Texarkana, Ark., North Mississippi Broadcasting Corp., 100 w, C.
- WDDO**—1250 kc, Chattanooga, Tenn., WDDO Broadcasting Co., Inc., 5000 w, C.
- WDBC**—1330 kc, Hartford, Conn., Doolittle Radio Corp., 500 w, E.
- WDSU**—1250 kc, New Orleans, La., Jos. H. Uhalt, 1000 w, C.
- WDZ**—1070 kc, Tuscola, Ill., James L. Bush, 100 w.
- WEAF**—660 kc, New York, N. Y., National Broadcasting Co., Inc., 50,000 w, E.
- WEAL**—1270 kc, Ithaca, N. Y., Cornell Univ., 1000 w, E.
- WEAN**—780 kc, Providence, R. I., Shepard Broadcasting Service, 250 w, E.
- WEAO**—570 kc, Columbus, Ohio, Ohio State University, 750 w, E.
- WEBC**—1290 kc, Superior, Wis., Head of The Lakes Broadcasting Co., 1000 w, C.
- WEBQ**—1210 kc, Harrisburg, Ill., First Trust & Savings Bank, 100 w, C.
- WEBR**—1310 kc, Buffalo, N. Y., Howell Broadcasting Co., 100 w, E.
- WEDC**—1210 kc, Chicago, Ill., Emil Denmark, Inc., 100 w.
- WEEL**—590 kc, Boston, Mass., Edison Elec. Illum. Co., 1000 w, E.
- WEER**—830 kc, Reading, Pa., Berks Bdstg. Co., 1000 w.
- WEHC**—1350 kc, Emory, Va., Emory and Henry College, 500 w, E.
- WEHS**—1420 kc, Evanston, Ill., WEHS, Inc., 100 w, C.
- WELL**—1420 kc, Battle Creek, Mich., Enquirer-News Co., 100 w, E.
- WENR**—870 kc, Chicago, Ill., Great Lakes Radio Broadcasting Co., 50,000 w, C.
- WEPS**—See under WORC.
- WERE**—1420 kc, Erie, Pa., Erie Dispatch-Herald, 30 w, E.
- WEVD**—1300 kc, Brooklyn, N. Y., Debs Memorial Radio Fund, 500 w, E.
- WEW**—760 kc, St. Louis, Mo., St. Louis University, 1000 w, C.
- WEXL**—1310 kc, Royal Oak, Mich., Royal Oak Broadcasting Co., 50 w, E.
- WFAA**—800 kc, Dallas, Texas, Dallas News and Journal, 50,000 w, C.
- WFAM**—1200 kc, La Porte, Ind., South Bend Tribune, 100 w, C.
- WFAN**—610 kc, Philadelphia, Pa., Keystone Broadcasting Co., Inc., 500 w, E.
- WFBC**—1200 kc, Knoxville, Tenn., First Baptist Church, 50 w, E.
- WFBE**—1200 kc, Cincinnati, Ohio, Post Publ. Co., 100 w, E.
- WFBG**—1310 kc, Altoona, Pa., William F. Gable Co., 100 w, E.
- WFBL**—1360 kc, Syracuse, N. Y., The Onondaga Co., Inc., 1000 w, E.
- WFBM**—1230 kc, Indianapolis, Ind., Indianapolis, Power & Light Co., 1000 w, C.
- WFBR**—1270 kc, Baltimore, Md., Baltimore Radio Show, Inc., 1000 w, E.
- WFDF**—1310 kc, Flint, Mich., Frank D. Fallain, 100 w, E.
- WFDV**—1310 kc, Rome, Ga., Dolies Goings, 100 w, E.
- WFDW**—1420 kc, Anniston, Ala., R. C. Hammett, 100 w, C.
- WFEE**—1430 kc, Merrimack, N. H., New Hampshire Bdstg. Co., 500 w, E.
- WFI**—560 kc, Philadelphia, Pa., Strawbridge & Clothier, 500 w, E.
- WFIW**—940 kc, Hopkinsville, Ky., WFIW, Inc., 1000 w, C.
- WFLA**—620 kc, Clearwater, Fla., Clearwater Chamber of Commerce and St. Petersburg Chamber of Commerce, 250 w, E.
- WFOX**—1400 kc, Brooklyn, N. Y., Paramount Broadcasting Corp., 500 w.
- WGAL**—1310 kc, Lancaster, Pa., WGAL, Inc., 100 w, E.
- WGAR**—1450 kc, Cleveland, Ohio, WGAR Broadcasting Co., 500 w, E.
- WGBB**—1210 kc, Freeport, N. Y., Harry H. Carman, 100 w, E.
- WGBC**—See under WNBR.
- WGBF**—630 kc, Evansville, Ind., Evansville on the Air, Inc., 500 w, E.
- WGBI**—880 kc, Scranton, Pa., Scranton Broadcasters, Inc., 250 w, E.
- WGCM**—1210 kc, Gulfport, Miss., Great Southern Land Co., Inc., 100 w, C.
- WGCP**—1250 kc, Newark, N. J., May Radio Broadcast Corp., 250 w, E.
- WGEO**—1000 kc, York, Pa., York Bdstg. Co., 1000 w, E.
- WGES**—1360 kc, Chicago, Ill., Oak Leaves Broadcasting Corp., 500 w, C.
- WGH**—1310 kc, Newport News, Va., Hampton Roads Broadcasting Corp., Inc., 100 w, E.
- WGL**—1370 kc, Ft. Wayne, Ind., Allen-Wayne Co., 100 w, C.
- WGMS**—See under WLB.
- WGN**—720 kc, Chicago, Ill., Tribune Co., 25,000 w, C.
- WGR**—550 kc, Buffalo, N. Y., Buffalo Broadcasting Corp., 1000 w, E.
- WGST**—890 kc, Atlanta, Ga., Georgia School of Technology, 250 w, E.
- WGY**—790 kc, Schenectady, N. Y., General Electric Co., 50,000 w, E.
- WHA**—940 kc, Madison, Wis., University of Wisconsin, 750 w, C.
- WHAD**—1120 kc, Milwaukee, Wis., Marquette University, 250 w, C.
- WHAM**—1150 kc, Rochester, N. Y., Stromberg-Carlson Tel. Mfg. Co., 5000 w, E.
- WHAP**—1300 kc, New York, N. Y., Defenders of Truth Society, Inc., 1000 w, E.
- WHAS**—820 kc, Louisville, Ky., The Courier Journal Co. & Louisville Times Co., 10,000 w, C.
- WHAT**—1310 kc, Philadelphia, Pa., Independence Broadcasting Co., 100 w, E.
- WHAZ**—1300 kc, Troy, N. Y., Rensselaer Polytechnic Institute, 500 w, E.
- WHB**—860 kc, Kansas City, Mo., WHB Broadcasting Co., 500 w, C.
- WHBC**—1200 kc, Canton, Ohio, St. John's Catholic Church, 10 w, E.
- WHBD**—1370 kc, Mt. Orab, Ohio, F. P. Moler, 100 w, E.
- WHBF**—1210 kc, Rock Island, Ill., Beardley Specialty Co., 100 w, C.
- WHBL**—1410 kc, Sheboygan, Wis., Press Pub. Co., 500 w, C.
- WHBQ**—1370 kc, Memphis, Tenn., Station WHBQ, Inc., 100 w, C.
- WHBU**—1210 kc, Anderson, Ind., Anderson Bdstg. Corp., 100 w, C.
- WHBY**—1200 kc, Green Bay, Wis., St. Norbert's College, 100 w, C.
- WHDF**—1370 kc, Calumet, Mich., Upper Michigan Bdstg. Co., 100 w, C.
- WHDH**—830 kc, Boston, Mass., Matheson Radio Co., Inc., 1000 w, E.
- WHDI**—1180 kc, Minneapolis, Minn., Dr. G. W. Young, 500 w, C.
- WHDL**—1420 kc, Tupper Lake, N. Y., Tupper Lake Broadcasting Corp., 100 w, E.
- WHEC**—1440 kc, Rochester, N. Y., WHEC, Inc., 500 w, E.
- WHFC**—1420 kc, Cicero, Ill., WHFC, Inc., 100 w, C.
- WHIS**—1410 kc, Bluefield, W. Va., Daily Telegraph Printing Co., 250 w, E.
- WHK**—1390 kc, Cleveland, Ohio, Radio Air Service Corp., 1000 w, E.
- WHN**—1010 kc, New York, N. Y., Marcus Loew Booking Review, 250 w, E.
- WHO**—1000 kc, Des Moines, Iowa, Central Broadcasting Co., 50,000 w, C.
- WHOM**—1450 kc, Jersey City, N. J., New Jersey Broadcasting Corp., 250 w, E.
- WHP**—1430 kc, Harrisburg, Pa., WHP, Inc., 500 w, E.
- WIAS**—1420 kc, Ottumwa, Iowa, Poling Electric Co., 100 w, C.
- WIBA**—1280 kc, Madison, Wis., Capital Times Co., 500 w, C.
- WIBG**—930 kc, Elkins Park, Pa., WIBG, Inc., 25 w, E.
- WIBM**—1370 kc, Jackson, Mich., WIBM, Inc., 100 w.
- WIBO**—560 kc, Chicago, Ill., Nelson Bros. Bond and Mortgage Co., 1000 w, C.
- WIBU**—1210 kc, Poynette, Wis., W. C. Forrest, 100 w, C.
- WIBW**—580 kc, Topeka, Kan., Topeka Broadcasting Assn., Inc., 1000 w, C.
- WIBX**—1200 kc, Utica, N. Y., WIBX, Inc., 100 w, E.
- WICC**—600 kc, Bridgeport, Conn., Bridgeport Broadcasting Station, Inc., 500 w, E.
- WIL**—1200 kc, St. Louis, Mo., Missouri Broadcasting Co., 100 w, C.
- WILL**—890 kc, Urbana, Ill., University of Illinois, 250 w, C.
- WILM**—1420 kc, Wilmington, Del., Delaware Broadcasting Co., Inc., 100 w, E.
- WINS**—1180 kc, New York, N. Y., American Radio News Corp., 500 w, E.
- WIOD**—1300 kc, Miami, Fla., Isle of Dreams Broadcasting Co., 1000 w, E.
- WIP**—610 kc, Philadelphia, Pa., Gimbel Bros., Inc., 500 w, E.
- WIS**—1010 kc, Columbia, S. C., South Carolina Broadcasting Co., Inc., 500 w, E.
- WISJ**—See under WIBA.
- WISN**—1120 kc, Milwaukee, Wis., Evening Wisconsin Co., 250 w, C.
- WJAC**—1310 kc, Johnstown, Pa., Johnstown Automobile Co., 100 w, E.
- WJAG**—1060 kc, Norfolk, Neb., Norfolk Daily News, 1000 w, C.
- WJAR**—1310 kc, Marion, Ind., The Truth Pub. Co., Inc., 50 w.
- WJAR**—890 kc, Providence, R. I., The Outlet Co., 250 w, E.
- WJAS**—1290 kc, Pittsburgh, Pa., Pittsburgh Radio Supply House, 1000 w, E.
- WJAX**—900 kc, Jacksonville, Fla., City of Jacksonville, 1000 w, E.
- WJAY**—610 kc, Cleveland, Ohio, Cleveland Radio Broadcasting Corp., 500 w, E.
- WJBC**—1200 kc, LaSalle, Ill., Kaskaskia Broadcasting Co., 100 w, C.
- WJBI**—1210 kc, Red Bank, N. J., Monmouth Broadcasting Co., 100 w, E.
- WJBK**—1370 kc, Highland Park, Mich., J. F. Hopkins, 50 w, C.
- WJBL**—1200 kc, Decatur, Ill., Commodore Broadcasting Co., 100 w, C.
- WJBO**—1420 kc, New Orleans, La., Valdemar Jensen, 100 w, C.
- WJBU**—1210 kc, Lewisburg, Pa., Bucknell University, 100 w, E.
- WJBW**—1200 kc, New Orleans, La., C. Carlensen, Jr., 30 w, C.
- WJBY**—1210 kc, Gadsden, Ala., Gadsden Broadcasting Co., 100 w, C.
- WJDX**—1270 kc, Jackson, Miss., Lamar Life Ins. Co., 1000 w, C.
- WJDD**—1130 kc, Chicago, Ill., Loyal Order of Moose, 20,000 w, C.
- WJKS**—1360 kc, Gary, Ind., Johnson-Kennedy Radio Corp., 1000 w, C.
- WJMS**—1420 kc, Ironwood, Mich., Johnson Music Store, 100 w.
- WJR**—750 kc, Detroit, Mich., The Goodwill Station, Inc., 10,000 w, E.
- WJSV**—1460 kc, Alexandria, Va., WJSV, Inc., 10,000 w.
- WJTL**—1370 kc, Oglethorpe University, Ga., 100 w, E.
- WJW**—1210 kc, Mansfield, Ohio, Mansfield Broadcasting Association, 100 w, E.
- WJZ**—760 kc, New York City, N. Y., National Broadcasting Co., 30,000 w, E.
- WKAQ**—890 kc, San Juan, Porto Rico, Radio Corp. of Porto Rico, 250 w, E.
- WKAR**—1040 kc, East Lansing, Mich., Michigan State College, 1000 w, E.
- WKAV**—1310 kc, Laconia, N. H., Laconia Radio Club, 100 w, E.
- WKBB**—1310 kc, Joliet, Ill., Sanders Bros., 100 w, C.
- WKBC**—1310 kc, Birmingham, Ala., R. B. Broyles Furniture Co., 100 w, C.
- WKBF**—1400 kc, Indianapolis, Ind., Indianapolis Broadcasting Corp., 500 w, C.
- WKBH**—1380 kc, LaCrosse, Wis., WKBH, Inc., 1000 w, C.
- WKBI**—1420 kc, Chicago, Ill., WKBI, Inc., 100 w, C.
- WKBN**—570 kc, Youngstown, Ohio, WKEN Bdstg. Corp., 500 w, E.
- WKBO**—1450 kc, Jersey City, N. J., Camith Corp., 250 w, E.
- WKBS**—1310 kc, Galesburg, Ill., Permil N. Nelson, 100 w, C.
- WKBV**—1500 kc, Connersville, Ind., Knox Battery & Electric Co., 100 w, C.
- WKBW**—1480 kc, Buffalo, N. Y., WKBW, Inc., 5000 w, E.
- WKBZ**—1500 kc, Ludington, Mich., K. L. Ashbacher, 50 w.
- WKJC**—1200 kc, Lancaster, Pa., Lancaster Bdstg. Service, Inc., 100 w, E.
- WKRC**—550 kc, Cincinnati, Ohio, WKRC, Inc., 1000 w, E.
- WKY**—900 kc, Oklahoma City, Okla., WKY Radiophone Co., 1000 w, C.
- WKZO**—590 kc, Berrien Springs, Mich., WKZO, Inc., 1000 w, C.
- WLAC**—1470 kc, Nashville, Tenn., Life & Casualty Ins. Co., 5000 w, C.

- WLAP**—1200 kc, Louisville, Ky., American Broadcasting Corp. of Kentucky, 100 w, C.
- WLB**—1250 kc, Minneapolis, Minn., University of Minnesota, 1000 w, C.
- WLBC**—1310 kc, Muncie, Ind., Donald A. Burton, 50 w.
- WLBK**—1420 kc, Kansas City, Kan., WLBK Broadcasting Co., 100 w, C.
- WLBG**—1200 kc, Petersburg, Va., WLEG, Inc., 100 w, E.
- WLBL**—900 kc, Stevens Point, Wis., Wisconsin Department of Agriculture, 2000 w, daytime, C.
- WLBW**—1260 kc, Oil City, Pa., Radio-Wire Program Corp., 500 w, E.
- WLBX**—1500 kc, Long Island City, N. Y., John N. Brahy, 100 w.
- WLBZ**—620 kc, Bangor, Me., Maine Broadcasting Co., 500 w, E.
- WLGI**—1210 kc, Ithaca, N. Y., Lutheran Assn. of Ithaca, 50 w, E.
- WLEY**—1370 kc, Lexington, Mass., Lexington Air Station, 100 w, E.
- WLIT**—560 kc, Philadelphia, Pa., Lit Brothers, 500 w, E.
- WLS**—870 kc, Chicago, Ill., Agricultural Broadcasting Co., 5000 w, C.
- WLSI**—See under WPRO.
- WLTH**—1400 kc, Brooklyn, N. Y., Voice of Brooklyn, Inc., 500 w, E.
- WLVA**—1370 kc, Lynchburg, Va., Lynchburg Broadcasting Corp., 100 w, E.
- WLW**—700 kc, Cincinnati, Ohio, Crosley Radio Corp., 50,000 w, E.
- WLWL**—1100 kc, New York, N. Y., Missionary Society of St. Paul, 5000 w, E.
- WMAC**—See under WSYR.
- WMAL**—630 kc, Washington, D. C., M. A. Leese Co., 250 w, E.
- WMAQ**—670 kc, Chicago, Ill., National Broadcasting Co., 5000 w, C.
- WMAZ**—1180 kc, Macon, Ga., Southeastern Broadcasting Co., 500 w, E.
- WMBA**—1500 kc, Newport, R. I., LeRoy Joseph Beebe, 100 w, E.
- WMBC**—1420 kc, Detroit, Mich., Michigan Broadcasting Co., Inc., 100 w, E.
- WMBD**—1440 kc, Peoria Heights, Ill., Peoria Bdstg. Co., 500 w, C.
- WMBF**—See under WIOD.
- WMBG**—1210 kc, Richmond, Va., Havens & Martin, Inc., 100 w, E.
- WMBH**—1420 kc, Joplin, Mo., Edwin Dudley Aber, 100 w, C.
- WMBI**—1080 kc, Chicago, Ill., Moody Bible Institute Radio Station, 5000 w, C, shared.
- WMBJ**—1500 kc, Wilkesburg, Pa., Rev. John W. Sproul, 100 w, E.
- WMBO**—1310 kc, Auburn, N. Y., WMBO, Inc., 100 w, E.
- WMBR**—1500 kc, Brooklyn, N. Y., Paul J. Golhofer, 100 w.
- WMBR**—1370 kc, Tampa, Fla., F. J. Reynolds, 100 w, E.
- WMC**—780 kc, Memphis, Tenn., Memphis Commercial Appeal, Inc., 500 w, C.
- WMCA**—570 kc, New York, N. Y., Knickerbocker Broadcasting Co., Inc., 500 w, E.
- WMIL**—1500 kc, Brooklyn, N. Y., Arthur Faske, 100 w, E.
- WMIN**—890 kc, Fairmont, W. Va., Holt Rowe Novelty Co., 250 w, E.
- WMPG**—1500 kc, Lapeer, Mich., First Methodist Protestant Church, 100 w, E.
- WMBJ**—1210 kc, Jamaica, N. Y., Peter J. Prinz, 10 w, E.
- WMSG**—1350 kc, New York, N. Y., Madison Square Garden Broadcast Co., 250 w, E.
- WMT**—600 kc, Waterloo, Iowa, Waterloo Broadcasting Co., 500 w, C.
- WMAC**—1230 kc, Boston, Mass., The Shepard Broadcasting Service, 1000 w, E.
- WNAD**—1010 kc, Norman, Okla., University of Oklahoma, 500 w, C.
- WNAX**—570 kc, Yankton, S. Dak., Gurney Seed & Nursery Co., 1000 w, C.
- WNBK**—1500 kc, Binghamton, N. Y., Howitt-Wood Radio Co., 100 w, E.
- WNBH**—1310 kc, New Bedford, Mass., New Bedford Broadcasting Co., 100 w, E, shared.
- WNBO**—1200 kc, Silver Haven, Pa., J. B. Spriggs, 100 w, E.
- WNBK**—1430 kc, Memphis, Tenn., Memphis Broadcasting Co., 500 w, C.
- WNBW**—1200 kc, Carbondale, Pa., Home Cut Glass & China Co., 10 w, E.
- WNBX**—1200 kc, Springfield, Vt., First Congregational Church Corp., 10 w, E.
- WNBZ**—1290 kc, Saranac Lake, N. Y., Smith & Mace, 50 w, E.
- WNJ**—1450 kc, Newark, N. J., Radio Investment Co., 250 w, E.
- WNOX**—560 kc, Knoxville, Tenn., WNOX, Inc., 1000 w, C.
- WNYC**—570 kc, New York, N. Y. Department of Plant & Structures, 500 w, E.
- WOAI**—1190 kc, San Antonio, Texas, Southern Equipment Co., 50,000 w, C.
- WOAN**—See WREC.
- WOAX**—1280 kc, Trenton, N. J., WOAX, Inc., 500 w, E.
- WOBV**—580 kc, Charleston, W. Va., WOBV, Inc., 250 w, E.
- WOC**—1000 kc, Davenport, Iowa, Central Broadcasting Co., 50,000 w, C.
- WOCL**—1210 kc, Jamestown, N. Y., A. E. Newton, 50 w, E.
- WODA**—1250 kc, Paterson, N. J., Richard E. O'Dea, 1000 w, E.
- WODX**—1410 kc, Mobile, Ala., Mobile Bdstg. Corp., 500 w, C.
- WOI**—640 kc, Ames, Iowa, Iowa State College, 5000 w, C.
- WOKO**—1440 kc, Albany, N. Y., WOKO, Inc., 500 w, E.
- WOL**—1310 kc, Washington, D. C., American Broadcasting Co., 100 w, E.
- WOMT**—1210 kc, Manitowoc, Wis., Francis M. Kadow, 100 w.
- WOOD**—1270 kc, Grand Rapids, Mich., Walter B. Stiles, Inc., 500 w, C.
- WOPI**—1500 kc, Bristol, Tenn., Radiophone Broadcasting Co., 100 w, E.
- WOR**—710 kc, Newark, N. J., J. Bamberger Broadcasting Service, Inc., 50,000 w, E.
- WORC**—1200 kc, Worcester, Mass., A. F. Kleindienst, 100 w, E.
- WOS**—630 kc, Jefferson City, Mo., John D. Heiny, 500 w, C.
- WOV**—1130 kc, New York, N. Y., International Broadcasting Corp., 1000 w, E.
- WOW**—590 kc, Omaha, Neb., Woodmen of the World, 1000 w, C.
- WOWO**—1160 kc, Ft. Wayne, Ind., Main Auto Supply Co., 10,000 w, C.
- WPAD**—1420 kc, Paducah, Ky., Paducah Broadcasting Co., 100 w, C.
- WPAP**—See under WQAO.
- WPCC**—560 kc, Chicago, Ill., North Shore Congregational Church, 500 w, C.
- WPCH**—810 kc, New York, N. Y., Eastern Broadcasters, Inc., 500 w, E.
- WPEN**—1500 kc, Philadelphia, Pa., Wm. Pen Broadcasting Co., 250 w, E.
- WPFH**—1370 kc, Hattiesburg, Miss., Hattiesburg Bdstg. Co., 100 w, C.
- WPG**—1100 kc, Atlantic City, N. J., WPG Broadcasting Corp., 5000 w, E.
- WPOR**—See under WTAR.
- WPRO**—1210 kc, Providence, R. I., Cherry & Webb Bdstg. Co., 100 w, E.
- WPSC**—1230 kc, State College, Pa., Pennsylvania State College, 500 w, day, E.
- WPTF**—680 kc, Raleigh, N. C., Durham Life Insurance Co., 1000 w, E.
- WQAM**—560 kc, Miami, Fla., Miami Broadcasting Co., 1000 w, E.
- WQAN**—880 kc, Scranton, Pa., Scranton Times, 250 w, E.
- WQAO**—1010 kc, New York, N. Y., Calvary Baptist Church, 250 w, E.
- WQBC**—1360 kc, Vicksburg, Miss., Delta Broadcasting Co., 300 w, C.
- WQDM**—1370 kc, St. Albans, Vt., A. J. St. Antoine, 100 w, E.
- WQDX**—1210 kc, Thomasville, Ga., Stevens Luke, 100 w, E.
- WRAC**—1370 kc, Williamsport, Pa., C. R. Cummins, 50 w, E.
- WRAM**—1370 kc, Wilmington, N. C., Wilmington Radio Association, 100 w, E.
- WRAW**—1310 kc, Reading, Pa., Reading Broadcasting Co., 50 w, E.
- WRAX**—1020 kc, Philadelphia, Pa., WRAX Broadcasting Co., 250 w, E.
- WRBL**—1200 kc, Columbus, Ga., WRBL Radio Station, Inc., 50 w, E.
- WRBQ**—1210 kc, Greenville, Miss., J. Pat Scully, 250 w, C.
- WRBK**—1410 kc, Roanoke, Va., Richmond Development Corp., 250 w, E.
- WRC**—950 kc, Washington, D. C., National Broadcasting Co., 500 w, E.
- WRDO**—1370 kc, Augusta, Me., Albert S. Woodman, 100 w, E.
- WRDW**—1500 kc, Augusta, Ga., Davenport's Musicove, Inc., 100 w, E.
- WREC**—600 kc, Memphis, Tenn., WREC, Inc., 500 w.
- WREN**—1220 kc, Lawrence, Kan., Jenny Wren Co., 1000 w, C.
- WRIM**—1250 kc, Minneapolis, Minn., Minnesota Broadcasting Corp., 1000 w, C.
- WRJN**—1370 kc, Racine, Wis., Racine Broadcasting Corp., 100 w, C.
- WRNY**—1010 kc, New York, N. Y., Aviation Radio Station, 250 w, E.
- WROL**—1310 kc, Knoxville, Tenn., Stuart Broadcasting Corp., 100 w, C.
- WRR**—1280 kc, Dallas, Texas, City of Dallas, 500 w, C.
- WRUF**—830 kc, Gainesville, Fla., University of Florida, 5000 w, E.
- WRVA**—1110 kc, Richmond, Va., Larus Bros. & Co., Inc., 5000 w, E.
- WSAI**—1330 kc, Cincinnati, Ohio, Crosley Radio Corp., 500 w, E.
- WSAJ**—1310 kc, Grove City, Pa., Grove City College, 100 w, E.
- WSAN**—1440 kc, Allentown, Pa., Allentown Call Pub. Co., 250 w, E.
- WSAR**—1450 kc, Fall River, Mass., Doughty & Welch Electrical Co., Inc., 250 w, E.
- WSAZ**—580 kc, Huntington, W. Va., WSAZ, Inc., 250 w, E.
- WSB**—740 kc, Atlanta, Ga., Atlanta Journal Co., 5000 w, E.
- WSBC**—1210 kc, Chicago, Ill., World Battery Co., 100 w, C.
- WSBT**—1230 kc, South Bend, Ind., South Bend Tribune, 500 w, C.
- WSEN**—1210 kc, Columbus, Ohio, Columbus Broadcasting Corp., 100 w, E.
- WSFA**—1410 kc, Montgomery, Ala., Montgomery Bdstg. Co., 500 w, C.
- WSIX**—1210 kc, Springfield, Tenn., 638 Tire & Vulcanizing Co., 100 w, C.
- WSJS**—1310 kc, Winston-Salem, N. C., The Journal Co., 100 w, E.
- WSM**—650 kc, Nashville, Tenn., National Life & Accident Ins. Co., 5000 w, C.
- WSMB**—1320 kc, New Orleans, La., WSMB, Inc., 500 w, C.
- WSMK**—1380 kc, Dayton, Ohio, Stanley M. Krohn, Jr., 200 w, C.
- WSOC**—1210 kc, Gastonia, N. C., A. J. Kirby Music Co., 100 w, E.
- WSPA**—1420 kc, Spartanburg, S. C., 100 w, E.
- WSPD**—1340 kc, Toledo, Ohio, Toledo Broadcasting Co., 1000 w, E.
- WSUI**—880 kc, Iowa City, Iowa, State Univ. of Iowa, 500 w, C.
- WSUN**—See under WFLA.
- WSVS**—1370 kc, Buffalo, N. Y., Seneca Vocational High School, 50 w, E.
- WSYB**—1500 kc, Rutland, Vt., Weiss Music Co., 100 w, E.
- WSYR**—570 kc, Syracuse, N. Y., Clive B. Meredith, 250 w, E.
- WTAD**—1440 kc, Quincy, Ill., Illinois Broadcasting Corp., 500 w.
- WTAG**—580 kc, Worcester, Mass., Worcester Telegram Pub. Co., Inc., 250 w, E.
- WTAM**—1070 kc, Cleveland, Ohio, National Broadcasting Co., 50,000 w, E.
- WTAQ**—1330 kc, Eau Claire, Wis., Gillette Rubber Co., 1000 w, C.
- WTAR**—780 kc, Norfolk, Va., WTAR Radio Corp., 500 w, E.
- WTAW**—1120 kc, College Station, Texas, Agri. & Mech. College of Texas, 500 w, C.
- WTAX**—1210 kc, Springfield, Ill., WTAX, Inc., 100 w.
- WTBO**—1420 kc, Cumberland, Md., Associated Bdstg. Corp., 100 w, E.
- WTEL**—1310 kc, Philadelphia, Pa., Foulkrod Radio Eng. Co., 50 w, E.
- WTFE**—1450 kc, Athens, Ga., Toccoa Falls Bdstg. Co., 500 w, E.
- WTCI**—1060 kc, Hartford, Conn., Travelers Broadcasting Service Corp., 50,000 w, E.
- WTJS**—1310 kc, Jackson, Tenn., Sun Publishing Co., 100 w, C.
- WTMJ**—620 kc, Milwaukee, Wis., Milwaukee Journal, 1000 w, C.
- WTNT**—1470 kc, Nashville, Tenn., Life and Casualty Ins. Co. of Tenn., 5000 w, C.
- WTOC**—1260 kc, Savannah, Ga., Savannah Broadcasting Corp., 500 w, E.
- WVAE**—1200 kc, Hammond, Ind., Hammond-Calumet Broadcasting Corp., 100 w, C.
- WWJ**—920 kc, Detroit, Mich., Evening News Assn., 1000 w, E.
- WWL**—850 kc, New Orleans, La., Loyola University, 10,000 w, C.
- WWNC**—570 kc, Asheville, N. C., Citizens Broadcasting Co., 1000 w, E.
- WWRL**—1500 kc, Woodside, N. Y., Long Island Broadcasting Corp., 100 w.
- WWSW**—1500 kc, Pittsburgh, Pa., Walker & Downing Radio Corp.
- WWVA**—1160 kc, Wheeling, W. Va., West Virginia Broadcasting Corp., 5000 w, E.
- WXYZ**—1240 kc, Detroit, Mich., Kunsky Trendle Broadcasting Co., 1000 w, E.

U.S. Broadcasting Stations by Frequencies

- 550 Kilocycles, 545.1 Meters:**
KOAC, WGR, WKRC, KFUD, KSD, KFDY, KFYR
- 560 Kilocycles, 535.4 Meters:**
WLIT, WFI, KFDM, WNOX, KTAB, KLZ, WIBO, WPCC, WQAM
- 570 Kilocycles, 526.0 Meters:**
WNYC, WMCA, WSYR, WMAC, WKBN, WWNC, KGKO, WNAX, KXA, KMTR, WEAO
- 580 Kilocycles, 516.9 Meters—Canadian Shared:**
WTAG, WOBV, WSAZ, KSAC, WIBW
- 590 Kilocycles, 508.2 Meters:**
WEEL, WCAJ, WOW, KHQ, WKZO
- 600 Kilocycles, 499.7 Meters—Canadian Shared:**
WCAO, WREC, WOAN, KFSO, WCAC, WMT WICC
- 610 Kilocycles, 491.5 Meters:**
WFAN, WIP, WDAF, KFRC, WJAY
- 620 Kilocycles, 483.6 Meters:**
WLBZ, WTMJ, KGW, WFLA, WSUN, KTAR
- 630 Kilocycles, 475.9 Meters—Canadian Shared:**
WMAL, WOS, KFRU, WGBF, KGFX
- 640 Kilocycles, 468.5 Meters:**
WAIU, KFI, WOI
- 650 Kilocycles, 461.3 Meters:**
WSM, KPCB
- 660 Kilocycles, 454.3 Meters:**
WEAF, WAAW
- 670 Kilocycles, 447.5 Meters:**
WMAQ
- 680 Kilocycles, 440.9 Meters:**
WPTF, KPO, KFEO
- 690 Kilocycles, 434.5 Meters—Canadian Wave:**
- 700 Kilocycles, 428.3 Meters:**
WLW
- 710 Kilocycles, 422.3 Meters:**
WOR, KMPC
- 720 Kilocycles, 416.4 Meters:**
WGN
- 730 Kilocycles, 410.7 Meters—Canadian Wave:**
- 740 Kilocycles, 405.2 Meters:**
WSB, KMMJ
- 750 Kilocycles, 399.8 Meters:**
WJR, KGU
- 760 Kilocycles, 394.5 Meters:**
WJZ, WEW, KVI
- 770 Kilocycles, 389.4 Meters:**
KFAB, WBBM, WJBT
- 780 Kilocycles, 384.4 Meters—Canadian Shared:**
WTAR, WPOR, KELW, KTM, WMC, WEAN
- 790 Kilocycles, 379.5 Meters:**
WGY, KGO
- 800 Kilocycles, 374.8 Meters:**
WBAP, WFAA
- 810 Kilocycles, 370.2 Meters:**
WPCH, WCCO
- 820 Kilocycles, 365.6 Meters:**
WHAS
- 830 Kilocycles, 361.2 Meters:**
KOA, WHDH, WRUF, WEEU
- 840 Kilocycles, 356.9 Meters—Canadian Wave:**
- 850 Kilocycles, 352.7 Meters:**
KWKH, WWL
- 860 Kilocycles, 348.6 Meters:**
WBOQ, WABC, KMO, WHB
- 870 Kilocycles, 344.6 Meters:**
WLS, WENR, WBCN
- 880 Kilocycles, 340.7 Meters—Canadian Shared:**
WQAN, WGBI, WCOC, KLX, KPOF, KFKA, WSUI
- 890 Kilocycles, 336.9 Meters—Canadian Shared:**
WFAR, WMMN, WGST, KARK, WILL, KUSD, KFNF, WKAQ
- 900 Kilocycles, 331.1 Meters:**
WKY, WLBL, KHJ, KSEI, KGBU, WJAX, WBEW
- 910 Kilocycles, 329.5 Meters—Canadian Wave:**
- 920 Kilocycles, 325.9 Meters:**
WWJ, KPRC, WAAF, WBSO, KOMO, KFXF, KFEL
- 930 Kilocycles, 322.4 Meters—Canadian Shared:**
WIBG, WDBJ, WBRC, KGBZ, KMA, KFWL, KROW
- 940 Kilocycles, 319 Meters:**
WCSH, WFIW, KOIN, WHA, WDAY, WAAT
- 950 Kilocycles, 315.6 Meters:**
WRC, KMBC, KFWB, KGHL
- 960 Kilocycles, 312.3 Meters—Canadian Wave:**
- 970 Kilocycles, 309.1 Meters:**
KJR, WCFL
- 980 Kilocycles, 305.9 Meters:**
KDKA
- 990 Kilocycles, 302.8 Meters:**
WBZ, WBZA
- 1000 Kilocycles, 299.8 Meters:**
WHO, WOC, KFVD, WGEO
- 1010 Kilocycles, 296.9 Meters—Canadian Shared:**
WQAO, WPAP, WHN, WRNY, KGGF, WNAD, KQW, WIS
- 1020 Kilocycles, 293.9 Meters:**
KYW, KFKX, WRAX
- 1030 Kilocycles, 291.1 Meters—Canadian Wave:**
- 1040 Kilocycles, 288.3 Meters:**
WKAR, KTHS, KRLD
- 1050 Kilocycles, 285.5 Meters:**
KNX, KFKB
- 1060 Kilocycles, 282.8 Meters:**
WBAL, WJAG, KWJJ, WTIC
- 1070 Kilocycles, 280.2 Meters:**
WTAM, WCAZ, WJZ, KJBS
- 1080 Kilocycles, 277.6 Meters:**
WBT, WCBD, WMBI
- 1090 Kilocycles, 275.1 Meters:**
KMOX
- 1100 Kilocycles, 272.6 Meters:**
WPG, WLWL, KGDM
- 1110 Kilocycles, 270.1 Meters:**
WRVA, KSOO
- 1120 Kilocycles, 267.7 Meters—Canadian Shared:**
WTAW, WISN, WHAD, KFSG, KRSC, WDEL, WDBO, KFIO, KTRH, KMBC, KRKD
- 1130 Kilocycles, 265.3 Meters:**
WOV, KSL, WJJD
- 1140 Kilocycles, 263.0 Meters:**
WAPI, KVOO
- 1150 Kilocycles, 260.7 Meters:**
WHAM
- 1160 Kilocycles, 258.5 Meters:**
WWVA, WOWO
- 1170 Kilocycles, 256.3 Meters:**
WCAU
- 1180 Kilocycles, 254.1 Meters:**
KEX, KOB, WHDI, WJGY, WMAZ, WINS
- 1190 Kilocycles, 252.0 Meters:**
WOAI
- 1200 Kilocycles, 249.9 Meters—Canadian Shared:**
WABI, WNBX, WORC, WIBX, WHBC, WBHS, WLBG, WNBQ, WKJC, WNBW, WABZ, WJBW, WBBZ, WFBC, WRBL, WJBC, WJBL, WVAE, WFAM, KFJB, WCAT, KGDY, KFWE, KGDE, WCLO, WHBY, KERN, WIL, KVOS, KGY, KGEK, KGEW, KGHI, WCAX, WCOD, WFBE, KBTM, WEPS, KMLB, KGFJ, KWG, WLAP
- 1210 Kilocycles, 247.8 Meters—Canadian Shared:**
WBI, WGBB, WCOH, WOCL, WLCI, WPAW, WPRO, WLSI, WJW, VBAX, WJBU, WMBG, WSIX, WJBY, WRBO, WGCN, KWEA, KDLR, KGR, KFOR, WHBU, KFVS, WEBO, WODX, WCRW, WEDC, WCBS, WTAN, WHBF, WQMT, WSBC, KMJ, KF3M, KPCC, WALR, WBBL, WMRJ, KGMP, KGNO, WSEN, WSOC, WJBU, KFJI
- 1220 Kilocycles, 245.6 Meters:**
WCAD, WCAE, WREN, KFKU, WDAE, KWSC, KTW
- 1230 Kilocycles, 243.8 Meters:**
WNAC, WBIS, WPSC, WSBT, WFBM, KFQD, KYA, KGGM
- 1240 Kilocycles, 241.8 Meters:**
WACO, KTAT, WXYZ, KGCU, KTFI
- 1250 Kilocycles, 239.9 Meters:**
WGPC, WODA, WAAM, WLB, WGMS, WRHM, KFMX, WCAL, KFOX, WDSU
- 1260 Kilocycles, 238.0 Meters:**
WLBW, KWWG, KRGV, KOIL, KVOA, WTOC
- 1270 Kilocycles, 236.1 Meters:**
WEAL, WASH, WOOD, KWLC, KGCA, KOL, KVOR, WFBR, WJDX
- 1280 Kilocycles, 234.2 Meters:**
WCAM, WCAP, WOAX, WDOD, WRR, KFBB, WIBA, WISJ
- 1290 Kilocycles, 232.4 Meters:**
WNBZ, WJAS, KTSB, KFUL, KLCN, KDYL, WEEC
- 1300 Kilocycles, 230.6 Meters:**
WBBR, WHAP, WEVD, WHAZ, KFH, KGEF, KFAC, KFJR, KTBR, WIOD, WMBF, WOQ
- 1310 Kilocycles, 228.9 Meters:**
WKAV, WEBR, WNBH, WOL, WGH, WHAT, WFBG, WRAW, WGAL, WSAJ, WBRE, WKBC, WTJS, KRMD, KFPM, WDAH, KFPL, KFJR, WBSB, WCLS, WKBB, KWCR, KFJY, KFGQ, WBOW, WJAK, WLBC, KTSI, KFUP, KFJX, KFBK, KGEZ, KMED, KTSM, KGCN, WJAC, WSJS, KXRO, KGFV, KFJU, KGBX, KIT, WMBO, KCRJ, KTLC, WEXL, WROL, WTEL, WBEQ, WFDV
- 1320 Kilocycles, 227.1 Meters:**
WADC, WSMB, KID, KGHF, KGMB, KGIO
- 1330 Kilocycles, 225.4 Meters:**
WDR, WTAQ, KSCJ, WSAI, KGB
- 1340 Kilocycles, 223.7 Meters:**
KFPW, WCOA, KFPY, WSPD
- 1350 Kilocycles, 222.1 Meters:**
WMSG, WCDA, WBNX, KWK, WAWZ, WEHC, KIDO
- 1360 Kilocycles, 220.4 Meters:**
WOBC, WGES, KGIR, KGER, WFBL, WCSC, WJKS
- 1370 Kilocycles, 218.8 Meters:**
WSVS, WCBM, WBB, WJKB, WIBM, WRAK, WDAS, WBQ, WRAM, KGGF, KFJZ, KKKL, KFLX, KGDA, KRE, WPOE, KFB, KWKC, WRJN, KGAR, KVL, KGFL, WHDF, KOOS, WGL, KFJM, KCR, WMBR, WPF, WLEY, WBGF, WBTM, WLVA, WQDM, WRDO, KONO, KMCA, KUJ, WJTL, KOH
- 1380 Kilocycles, 217.3 Meters:**
KQV, KSO, WKBH, WSMK
- 1390 Kilocycles, 215.7 Meters:**
WHK, KLRA, KUOA, KOY
- 1400 Kilocycles, 214.2 Meters:**
WCGU, WFOX, WLTH, WBBC, WCMA, WKBF, KOCW, WBAA, KLO
- 1410 Kilocycles, 212.6 Meters:**
KGRS, WDAQ, KFLV, WHBL, WBCM, WODX, WSFA, WAAB, WRBX, WHIS
- 1420 Kilocycles, 211.1 Meters:**
WTBO, WKBL, WEDH, WMB, KGF, KABC, KFYO, KICK, WIAS, KGGC, WLBF, WMBH, KFIZ, KORE, WILM, KGIW, KGKX, KFOV, KLPN, KNL, WHDL, WHFC, WEHS, KFOU, KFND, KGI, WJBO, WELL, WFDW, WPAD, WSPA, KBPS, KFX, KXYZ, WAGM, WDEV, KGO, WJMS, WDI, KCMC
- 1430 Kilocycles, 209.7 Meters:**
WHP, WCAH, WGBC, WNB, WBAK, KECA, KGNF, WFEA
- 1440 Kilocycles, 208.2 Meters:**
WHEC, WABO, WOKO, WCBA, WTAD, WMBD, KLS, WSA, WJG, KDFN
- 1450 Kilocycles, 206.8 Meters:**
WBMS, WNJ, WKBO, WSAR, WGAR, WFTI, KTBS, WHOM
- 1460 Kilocycles, 205.4 Meters:**
WJSV, KSTP
- 1470 Kilocycles, 204.0 Meters:**
KGA, WTNT, WLAC
- 1480 Kilocycles, 202.6 Meters:**
KFJF, WKBW
- 1490 Kilocycles, 201.6 Meters:**
WCKY, WCHI
- 1500 Kilocycles, 199.9 Meters:**
WMB, WNB, WMBQ, WLX, WWRL, WKBZ, WMP, WOP, WPEN, KGB, WKBV, KPJM, KDB, KGLF, WMBJ, KREG, WCLB, WRDW, KGZ, KGY, KFO, KXO, KGF, WSY, WWSV, KNW

U. S. Broadcasting Stations Listed by States

ALABAMA

Anniston, WFDW
Birmingham, WBRC, WKBC,
WAPT
Gadsden, WBLY
Huntsville, WBHS
Mobile, WODX
Montgomery, WSFA

ALASKA

Anchorage, KFQD
Juneau, KPIU
Ketchikan, KGBU

ARIZONA

Flagstaff, KPNY
Jerome, KCRJ
Phoenix, KTAJ, KOY
Prescott, KPHM
Tucson, KGAR, KVOA

ARKANSAS

Blytheville, KLCN
Fort Smith, KFPW
Fort Smith, KFPW
Hot Springs, KTHS
Little Rock, KLRK, KGH, KARK
Paragould, KBTM

CALIFORNIA

Bakersfield, KERN
Berkeley, KJLB
Beverly Hills, KMPC
Burbank, KTLA
Culter City, KPVD
El Centro, KXO
Fresno, KAMJ
Hollywood, KNX, KFWE
Long Beach, KFOX, KGER
Los Angeles, KFI, KFSG, KGEF,
KGFL, KILL, KECA, KMTR,
KTM, KFAC
Oakland, KLS, KLX, KROW
Pasadena, KPPC
Sacramento, KFBK
San Bernardino, KFXM
San Diego, KFSD, KGB
San Francisco, KFRC, KPWL,
KBSB, KPLO, KGCC, KYA,
KGO, KPAB
San Jose, KQW
Santa Ana, KREG
Santa Barbara, KDB
Stockton, KGD, KWG

COLORADO

Colorado Springs, KVOR
Denver, KFEL, KFUP, KFNE,
KOA, KPof, KIZ
Edgewater, KFNJ
Greeley, KFLC
Pueblo, KGHF
Trinidad, KGIW
Yuma, KGEK

CONNECTICUT

Bridgeport, WICC
Hartford, WVIC, WDRK
Storrs, WCAC

DELAWARE

Wilmington, WDEL, WILM

DISTRICT OF COLUMBIA

Washington, NAA, WMAL, WRC,
WOL

FLORIDA

Clearwater, WFLA, WSUN
Gainesville, WRUF
Jacksonville, WJAX
Miami, WIOD, WMBF, WQAM
Orlando, WFTS
Pensacola, WCOA
Tampa, WDAE, WMBR

GEORGIA

Athens, WTFT
Atlanta, WGST, WSB
Augusta, WRDW
Columbus, WBIW
Macon, WMAZ
Ocala, WFLC
Rome, WFDV
Savannah, WTOG
Thomasville, WQDX

HAWAII

Honolulu, KGU, KGMB

IDAHO

Boise, KIDO
Idaho Falls, KID
Nampa, KPXD
Pocatello, KSEI

Sandpoint, KGKX
Twin Falls, KTFI, KGIO

ILLINOIS

Carthage, WCAZ
Chicago, KYW, WAAF, WCFL,
WCRW, WFDC, WENR, WGES,
WKBI, WPCD, WGN, WMAQ,
WMBD, WBBM, WSBC, WIDQ,
WLS, WJJD, WCHI
Cicero, WIIFC
Decatur, WJBL
Evanston, WEIS
Galesburg, WKBS
Harrisburg, WBIQ
Joliet, WCLS, WKBB
La Salle, WIBC
Peoria Heights, WMBD
Quincy, WTAD
Rockford, KPLV
Rock Island, WHBP
Springfield, WCBS, WTAX
Tuscola, WJZ
Urbana, WILL
Zion, WCBD

INDIANA

Anderson, WIRE
Connersville, WKBY
Culver, WCMA
Evansville, WGEF
Fort Wayne, WGL, WOWO
Gary, WKLS
Hammond, WWAE
Indianapolis, WFPM, WKBF
Lafayette, WBA
La Porte, WFAA
Marion, WJAK
Muncie, WLBC
South Bend, WSBT
Terre Haute, WBOW

IDAHO

Ames, WOI
Boone, KFGQ
Cedar Rapids, KWCR
Charlinda, KSO
Council Bluffs, KOIL
Davenport, WOC
Decorah, KGCA, KWLC
Des Moines, WHO
Ft. Dodge, KJBY
Iowa City, WSUI
Marshalltown, KFJB
Ottumwa, WIAS
Red Oak, KICK
Shenandoah, KFNF, KMA
Sioux City, KSCJ
Waterloo, WMT

KANSAS

Dodge City, EGNO
Kansas City, WLBF
Lawrence, KFKU, WREN
Manhattan, KSAC
Milford, KFKE
Topeka, WIBW
Wichita, KFII

KENTUCKY

Covington, WCKY
Hopkinsville, WFIW
Louisville, WHAS, WLAP
Paducah, WPAD

LOUISIANA

Monroe, KMLB
New Orleans, WAEB, WJBO,
WJBW, WSM, WWL, WDSU
Shreveport, KTS, KWEA,
KRMD, KTBS, KWKH

MAINE

Augusta, WRDO
Bangor, WAIB, WLBZ
Portland, WOSH
Presque Isle, WAGM

MARYLAND

Baltimore, WCAO, WCBM,
WBAL, WBIR
Cumberland, WTBO

MASSACHUSETTS

Boston, WBZA, WEEL, WNAC,
WBIS, WIDH
Fall River, WSAJ
Lexington, WLEY
Needham, WESO
New Bedford, WNBH
Quincy, WAAB
Springfield, WBEZ
Worcester, WTAG, WORC, WEPS

MICHIGAN

Bay City, WBCM
Berrien Springs, WKZO
Calumet, WHDF
Detroit, WMBC, WWJ, WJR,
WXYZ
East Lansing, WKAR

Flint, WFDF
Grand Rapids, WASH, WOOD
Highland Park, WJBK
Ironwood, WJMS
Jackson, WJBM
Lapeer, WMPK
Ludington, WKBZ
Marquette, WBEQ
Royal Oak, WEXL

MINNESOTA

Fergus Falls, KGDE
Minneapolis, WDDI, WHDI,
WLB, WRIH, WCCO,
WGMS
Moorhead, KGFK
Northfield, KFMY, WCAL
St. Paul, KSTP

MISSISSIPPI

Greenville, KFBR
Gulfport, WGGM
Hattiesburg, WFPB
Jackson, WIDX
Meridian, WCOG
Vicksburg, WQBC

MISSOURI

Cape Girardeau, KFVS
Columbia, KFUR
Grant City, KGIJ
Jefferson City, WOS
Joplin, WMBH
Kansas City, KWKC, WDAF,
WHB, KMBC
Kirkswood, KWK
St. Joseph, KGBX, KFEQ
St. Louis, KFWE, KSD, WEW,
WIL, KMOX, KFUD

MONTANA

Billings, KGHL
Butte, KGR
Great Falls, KFBB
Rapid City, KFBZ
Missoula, KGVO
Wolf Point, KGXC

NEBRASKA

Clay Center, KMMJ
Lincoln, KFAB, KFOR, WCAJ
Norfolk, WAAG
North Platte, KGNF
Omaha, WAAY, WOV
 Kearney, KGBV
Scottsbluff, KGGY
York, KGBZ

NEVADA

Las Vegas, KGIX
 Reno, KOH

NEW HAMPSHIRE

Laconia, WKAJ
Merrimack, WPEA

NEW JERSEY

Asbury Park, WCAP
Atlantic City, WIPG
Camden, WCAJ
Hackensack, WBMS
Jersey City, WAAT, WEDQ,
WLOM
Newark, WAAM, WGCP, WJNJ,
WOR
Paterson, WODA
Red Bank, WJBI
Trenton, WOAAX

NEW MEXICO

Albuquerque, KGGM
Alton, KGFL
State College, KOB

NEW YORK

Albany, WOKO
Auburn, WMBO
Binghamton, WNBZ
Brooklyn, WBBC, WLTH,
WMBQ, WFOJ, WMIL, WBBR,
WCGU, WEYD
Buffalo, WEBR, WGR, WKBW,
WWSV, WREN
Canton, WCAD
Freeport, WGBB
Glens Falls, WBGF
Ithaca, WLCI, WEAT
Jamaica, WMRJ
Jamestown, WOCL
Long Beach, WCLB
Long Island City, WLBX
New York, WHN, WJZ, WBNX,
WJCA, WMSG, WNYC,
WPCU, WRNY, WABC,
WOV, WQAO, WLVL, WBOG,
WCDA, WFAF, WJAP, WPAJ
Rochester, WHAM, WHEC,
WABD
Saranac Lake, WNBZ
Schenectady, WGY

Syracuse, WFBL, WSYR,
WMAC
Tupper Lake, WHDL
Troy, WLAZ
Utica, WIBX
Woodside, WWRL
Yonkers, WCOH
Zarepath, WAWZ

NORTH CAROLINA

Asheville, WUNC
Charlotte, WBT
Gastonia, WSOC
Greensboro, WBIG
Raleigh, WPTF
Wilmington, WRAM
Winston-Salem, WSJS

NORTH DAKOTA

Bismarck, KFYP
Devils Lake, KDLR
Fargo, WDAY
Grand Forks, KFJM
Mandan, KGCU
Minot, KLFM

DHIO

Canton, WHBC
Cincinnati, WKRC, WSAI,
WLW, WFBE
Cleveland, WHK, WJAY,
WTAM, WGAR
Columbus, WAIU, WCAH,
WEO, WSEN
Dayton, WSMK
Mansfield, WJW
Mt. Orab, WHBD
Tallmadge, WADC
Toledo, WSPD
Youngstown, WKBN
Zanesville, WALR

OKLAHOMA

Chickasha, KOCW
Elk City, KGMP
Enid, KCR
Norman, WNAD
Oklahoma City, KFJE, KFNR,
KGFJ, WKY
Ponca City, WBBZ
Shawnee, KGFJ
South Coffeyville, KGGF
Tulsa, KVOO

DRESDEN

Corvallis, KOAC
Eugene, KORE
Klamath Falls, KFJI
Marshallfield, KOOS
Medford, KMED
Portland, KEX, KOIN, KFJR,
KGW, KTRB, RWJJ, KXL,
KBPS

PENNSYLVANIA

Allentown, WCBA, WSAJ
Altoona, WFBG
Carbondale, WNBW
Elkins Park, WIBG
Erie, WERE
Grove City, WSAJ
Harrisburg, WCOD, WBAK,
WHP
Johnstown, WJAC
Lancaster, WGAL, WKJC
Lewisburg, WJBU
Oil City, WLBW
Philadelphia, WCAU, WFL,
WTF, WLT, WRAX, WFXN,
WFAN, WHAT, WTEL, WDAJ
Pittsburgh, KDKA, KQV, WCAE,
WIAS, WWSW
Reading, WRAW, WEEW
Scranton, WGRI, WQAN
Silver Haven, WNBO
State College, WPSC
Wilkes-Barre, WRAX, WBRE
Wilkesburg, WMBJ
Williamsport, WRAP
York, WGEO

PORTO RICO

San Juan, WKAQ

RHODE ISLAND

Newport, WMBR
Providence, WEAN, WPRO,
WJAR

SOUTH CAROLINA

Charleston, WSCC
Columbia, WIS
Spartanburg, WSPA

SOUTH DAKOTA

Brookings, KFDD
Huron, KGZY
Mitchell, KGDA

Pierre, KGFX
Rapid City, WCAT
Sioux Falls, KSOO
Vermillion, KTSD
Watertown, KGCR
Yankton, WNAX

TENNESSEE

Bristol, WOPI
Chattanooga, WDOD
Jackson, WTJS
Knoxville, WFBC, WNOX,
WROL
Memphis, WGBC, WBBQ,
WMC, WNBZ, WOAN,
WREC
Nashville, WLAC, WSM,
WTFN
Springfield, WSIX

TEXAS

Abilene, KFYO
Amarillo, KGRS, WDAG
Austin, KNOW
Beaumont, KFDM
Brownsville, KWWG
College Station, WTAJ
Corpus Christi, KCFI
Dallas, KRLD, WFAA, WRR,
Dublin, KPFL
El Paso, WDAH, KTSM
Fort Worth, KFJZ, WBAP,
KTAT
Galveston, KFLX, KFUL
Greenville, KFPJ
Harlingen, KRGV
Houston, KPRC, KTLG,
KTHH, KXYZ
San Angelo, KGKL
San Antonio, KTSB, KABC,
WQAT, KONO, KMCC
Tyler, KGBZ
Waco, WACO
Wichita Falls, EGKO

UTAH

Ogden, KLO
Salt Lake City, KDYL, KSL

VERMONT

Burlington, WCAX
St. Albans, WQDM
Springfield, WNBX
Rutland, WSYB
Waterbury, WDEV

VIRGINIA

Alexandria, WJSV
Arlington, NAA
Danville, WBTM
Emory, WBHC
Lynchburg, WLVA
Newport News, WGH
Norfolk, WTAR, WPOP
Petersburg, WLBZ
Richmond, WBBJ, WMBG,
WRVA
Roanoke, WDBJ, WRBX

WASHINGTON

Aberdeen, KNRO
Bellingham, KVOS
Everett, KFBL
Lacey, KGY
Pullman, KWSC
Seattle, KOL, KFQW, KJR,
KOMO, KPCC, KRSC, KTV,
KVL, KXA
Spokane, KFIO, KFPY, KGA,
KHQ
Tacoma, KMO, KYI
Walla Walla, KUJ
Wenatchee, KPQ
Yakima, KIT

WEST VIRGINIA

Bluefield, WIDS
Charleston, WOBV
Fairmont, WAMN
Huntington, WSAZ
Wheeling, WWVA

WISCONSIN

Eau Claire, WTAQ
Fond Du Lac, KFJZ
Green Bay, WBLY
Janesville, WCLO
La Crosse, WKBH
Madison, WIA, WIBA
Manitowoc, WQMT
Milwaukee, WIAD, WISN,
WTM
Poyntelle, WIBU
Racine, WRN
Sheboygan, WIBL
South Madison, WISJ
Stevens Point, WLBL
Superior, WEBG

WYOMING

Casper, KDFN

LIST OF POLICE BROADCASTING STATIONS

Call	Kilocycles	Meters	Location	Call	Kilocycles	Meters	Location
WPDO	2,458	122.05	Akron, Ohio	WRDS	1,662	180.51	Ingham, Mich.
WPDY	2,452	122.34	Atlanta, Ga.	KGPE	2,422	123.86	Kansas City, Mo.
WPED	1,712	175.2	Arlington, Mass.	WPDT	2,470	121.50	Kokomo, Ind.
KGPS	2,416	124.17	Bakersfield, Calif.	WPDL	2,440	123.00	Lansing, Mich.
KGPIJ	1,712	175.23	Beaumont, Tex.	KGPL	1,712	175.23	Los Angeles, Calif.
KSW	2,410	124.50	Berkeley, Calif.	WPBE	2,440	123.00	Louisville, Ky.
WBY	1,596	187.97	Boston, Mass.	WPBC	2,470	121.50	Memphis, Tenn.
WFEE	2,450	122.4	Brooklyn, N. Y.	WPDK	2,452	122.34	Milwaukee, Wis.
WRDU	1,596	187.97	Brooklyn, N. Y.	KGPE	2,416	124.17	Minneapolis, Minn.
WVJ	2,422	123.86	Buffalo, N. Y.	WPY	438	685.00	New York, N. Y.
WBR	257	1,165.00	Butler, Pa.	WPY	500	600.00	New York, N. Y.
KGOZ	2,470	121.50	Cedar Rapids, Iowa	WCF	1,596	187.97	New York, N. Y.
WPCD	2,458	122.34	Chicago, Ill.	WPEF	2,450	122.4	New York, N. Y.
WIPB	1,712	175.23	Chicago, Ill.	WPEG	2,450	122.4	New York, N. Y.
WPDG	1,712	175.23	Chicago, Ill.	KGPH	2,452	122.34	Oklahoma City, Okla.
WPDD	1,712	175.23	Chicago, Ill.	KGPI	2,470	121.50	Omaha, Neb.
WKDU	1,712	175.23	Cincinnati, Ohio	KGJX	1,712	175.23	Pasadena, Calif.
WRBH	2,452	122.34	Cleveland, Ohio	WPDP	2,440	123.00	Philadelphia, Pa.
WPD	2,416	124.17	Columbus, Ohio	WPEP	1,712	175.23	Pittsburgh, Pa.
KLP	1,712	175.23	Dallas, Tex.	KGPP	2,416	124.17	Portland, Ore.
KGPN	2,470	121.50	Davenport, Iowa	WPDR	2,416	124.17	Richmond, Ind.
WPDMM	2,416	124.17	Dayton, Ohio	WPDH	1,712	175.23	Rochester, N. Y.
KGPN	2,442	122.8	Denver, Colo.	KGPC	1,712	175.23	St. Louis, Mo.
KGPV	2,506	180.51	Des Moines, Iowa	WPDS	2,416	124.17	St. Paul, Minn.
WKDT	1,596	187.97	Detroit, Mich.	KGPPW	2,470	121.50	Salt Lake City, Utah
WCK	2,410	124.50	Detroit, Mich.	KGPD	1,596	187.97	San Francisco, Calif.
WPDN	2,410	124.50	Detroit, Mich.	KGPD	2,410	124.50	San Francisco, Calif.
WPDF	2,440	123.00	Flint, Mich.	KGPM	2,470	121.50	San Jose, Calif.
KGPR	1,712	175.23	Ft. Worth, Tex.	KGPA	2,416	124.17	Seattle, Wash.
WMP	1,662	180.51	Framingham, Mass.	KGPY	1,574	190.5	Shreveport, La.
KGZA	2,416	124.2	Fresno, Calif.	WPA	2,468	122.4	Syracuse, N. Y.
WPEB	2,440	123.00	Grand Rapids, Mich.	KGPK	2,470	121.50	Sioux City, Iowa
WJL	257	1,165.00	Greensburg, Pa.	WRDQ	2,470	121.50	Toledo, Ohio
WJDR	2,410	124.50	Gross Point Village, Mich.	WPPA	2,416	124.17	Tulare, Calif.
WBA	257	1,165.00	Harrisburg, Pa.	KGPG	2,410	124.50	Vallejo, Calif.
WMO	2,410	124.50	Highland Park, Mich.	WPDW	2,410	124.50	Washington, D. C.
KGPP	2,452	122.35	Honolulu, T. H.	WMB	257	1,165.00	West Reading, Pa.
KGZB	1,712	175.2	Houston, Tex.	KGZ	2,452	122.3	Wichita, Kans.
WJIDZ	2,440	123.00	Indianapolis, Ind.	WDX	257	1,165.00	Wyoming, Pa.
				WPDG	2,458	122.05	Youngstown, Ohio

U. S. VISUAL BROADCASTING STATIONS

Call	Kilocycles	Meters	Owner	Call	Kilocycles	Meters	Owner
W1XAV	1,500	193.6	Short Wave & Television, Boston, Mass.	W3XAD	48,500	6.18	RCA-Victor, Camden, N. J.
W1XAY	2,950	101.8	Short Wave & Television, Boston, Mass.	W3XAD	60,000	5.00	RCA-Victor, Camden, N. J.
W2XAB	2,750	109.10	Atlantic Broadcasting, New York, N. Y.	W3XAD	2,100	142.90	RCA-Victor, Camden, N. J.
W2XAC	2,750	109.10	United Research Corp., Long Island City, N. Y.	W3XK	2,000	150.00	Jenkins Laboratories, Wheaton, Md.
W2XAD	2,000	150.00	Harold E. Smith, Beacon, N. Y.	W3X4H	2,000	150.00	Pioneer Mercantile Co., Bakersfield, Calif.
W2XAE	2,000	150.00	DeForest Radio Co., Passaic, N. J.	W3XAP	2,100	142.90	Don Lee, Inc., Los Angeles, Calif.
W2XAF	2,100	142.90	Jenkins Television, Jersey City, N. J.	W3XAS	2,100	142.90	Don Lee, Inc., Los Angeles, Calif.
W2XAG	2,000	150.00	Jenkins Television, Jersey City, N. J.	W3XAV	2,100	142.90	Westinghouse, East Pittsburgh, Pa.
W2XAH	2,100	142.90	General Electric, Schenectady, N. Y.	W3XAA	2,750	109.10	Federation of Labor, Chicago, Ill.
W2XAI	1,544	194.30	Atlantic Broadcasting, New York, N. Y.	W3XAB	1,564	191.82	Federation of Labor, Chicago, Ill.
W2XAJ	43,000	6.98	Jenkins Television, New York, N. Y.	W3XAC	2,000	150.00	Western Television Corp., Chicago, Ill.
W2XAK	48,500	6.18	Jenkins Television, New York, N. Y.	W3XAD	2,100	142.90	National Broadcasting, Chicago, Ill.
W2XAL	60,000	5.00	Jenkins Television, New York, N. Y.	W3XAE	43,000	6.97	Journal Company, Milwaukee, Wis.
W2XAM	43,000	6.97	National Broadcasting, New York, N. Y.	W3XAF	48,500	6.18	Journal Co., Milwaukee, Wis.
W2XAN	48,500	6.18	National Broadcasting, New York, N. Y.	W3XAG	60,000	6.00	Purdue University, W. Lafayette, Ind.
W2XAO	60,000	5.00	National Broadcasting, New York, N. Y.	W3XAH	2,750	109.10	Iowa City, Iowa.
W2XAP	2,850	105.30	Radio Pictures, Inc., Long Island City, N. Y.	W3XAK	2,000	150	Great Lakes Broadcasting, Chicago, Ill.
W3XAD	43,000	6.97	RCA-Victor, Camden, N. J.	W3XAL	2,850	105.30	Great Lakes Broadcasting, Chicago, Ill.

U. S. RELAY BROADCASTING STATIONS

Call	Kilocycles	Meters	Owner	Call	Kilocycles	Meters	Owner
W1XAL	6,040	49.67	Short Wave Bdstg. Corp., Boston, Mass.	W6XAF	2,938	112.10	Dept. Agriculture, Sacramento, Calif.
W1XAL	11,800	25.42	Short Wave Bdstg. Corp., Boston, Mass.	W6XAF	5,870	51.11	Dept. Agriculture, Sacramento, Calif.
W1XAL	15,250	19.67	Short Wave Bdstg. Corp., Boston, Mass.	W6XAL	6,080	49.34	Pacific-Western Broadcasting, Westminster, Calif.
W1XAL	21,450	13.97	Short Wave Bdstg. Corp., Boston, Mass.	W6XAL	15,250	19.67	Pacific-Western Broadcasting, Westminster, Calif.
W1XAZ	9,570	31.35	Westinghouse Elec., East Springfield, Mass.	W6XAL	21,500	13.95	Pacific-Western Broadcasting, Westminster, Calif.
W2XAD	15,340	19.56	General Electric, Schenectady, N. Y.	W6XN	12,850	23.35	General Electric, Oakland, Calif.
W2XAF	9,530	31.48	General Electric, Schenectady, N. Y.	W8XAL	6,060	49.50	Crosley Radio Corp., Cincinnati, Ohio
W2XAG	550	545.00	General Electric, Schenectady, N. Y.	W8XK	6,140	48.86	Westinghouse, East Pittsburgh, Pa.
W2XAG	660	455.00	General Electric, Schenectady, N. Y.	W8XK	9,570	31.35	Westinghouse, East Pittsburgh, Pa.
W2XAG	790	380.00	General Electric, Schenectady, N. Y.	W8XAP	11,800	25.25	Westinghouse, East Pittsburgh, Pa.
W2XAG	1,150	260.90	General Electric, Schenectady, N. Y.	W8XK	15,210	19.72	Westinghouse, East Pittsburgh, Pa.
W2XAG	1,500	200.00	General Electric, Schenectady, N. Y.	W8XK	17,780	16.87	Westinghouse, East Pittsburgh, Pa.
W2XE	6,120	49.02	Atlantic Broadcasting, Jamaica, N. Y.	W8XK	21,540	13.93	Westinghouse, East Pittsburgh, Pa.
W2XE	11,840	25.34	Atlantic Broadcasting Co., Jamaica, N. Y.	W9XAA	6,080	49.34	Federation of Labor, Chicago, Ill.
W2XE	15,280	19.63	Atlantic Broadcasting Co., Jamaica, N. Y.	W9XAA	11,840	25.34	Federation of Labor, Chicago, Ill.
W2XZ	610	491.50	National Broadcasting, Belmont, N. Y.	W9XAA	17,780	16.87	Federation of Labor, Chicago, Ill.
W3XAL	6,100	49.18	National Broadcasting, New York, N. Y.	W9XF	6,020	49.83	Great Lakes Broadcasting, Chicago, Ill.
W3XL	6,425	46.70	National Broadcasting, New York, N. Y.	W9XF	11,800	25.42	Great Lakes Broadcasting, Chicago, Ill.
W3XAU	6,060	49.50	Universal Broadcasting, Newton Township, Pa.	W9XF	21,500	13.95	Great Lakes Broadcasting, Chicago, Ill.
W3XAU	9,590	31.28	Universal Broadcasting, Newton Township, Pa.	W9XU	6,060	49.50	Mona Motor Oil Co., Council Bluffs, Iowa
W4XA	2,368	126.7	Miami, Fla.				

SIMPLE TIME CHART

(Time changes every 15 degrees of Longitude East or West)

LONGITUDE WEST OF GREENWICH	180°	165°	150°	135°	120°	105°	90°	75°	60°	45°	30°	15°	0°
PLACES ON, OR NEARLY ON, THE MERIDIAN INDICATED.	FIJI ISLANDS	UNALASKA	SEWARD	JUNEAU	LOS ANGELES	DENVER	CHICAGO	NEW YORK	BUENOS AIRES	RIO JANEIRO	AZORES	ICELAND	(GREENWICH) LONDON
TIME	Midnight	1 a.m.	2 a.m.	3 a.m.	4 a.m.	5 a.m.	6 a.m.	7 a.m.	8 a.m.	9 a.m.	10 a.m.	11 a.m.	Noon

↑ International date line. When it's Monday East of 180° it is Tuesday West of 180°.

LONGITUDE EAST OF GREENWICH	0°	15°	30°	45°	60°	75°	90°	105°	120°	135°	150°	165°	180°
PLACES ON, OR NEARLY ON, THE MERIDIAN INDICATED.	(GREENWICH) LONDON	BERLIN	ODESSA CAIRO	ADEN	MAURITIUS ISL.	LAHORE	CALCUTTA	BATAVIA	MANILA	KOBE	EASTERN AUSTRALIA	NEW CALEDONIA	FIJI ISLANDS
TIME	Noon	1 p.m.	2 p.m.	3 p.m.	4 p.m.	5 p.m.	6 p.m.	7 p.m.	8 p.m.	9 p.m.	10 p.m.	11 p.m.	Midnight

FOREIGN SHORT WAVE PHONE STATIONS

Call	Location	Kc.	Call	Location	Kc.	Call	Location	Kc.
AFRICA								
FSKR	Algiers	6,667	PK3CI	Surabaya	2,143	MOROCCO		
			PK3CI	Surabaya	6,662	F5MC	Casablanca	10,710
			PK3CI	Tandjong Priok	6,045	F5MC	Casablanca	6,875
			PK3CI	Tandjong Priok	9,579	Rabat	6,877
			PK3CI	Tandjong Priok	15,336	Rabat	12,830
			PK3CI	Tandjong Priok	15,336	Rabat	9,300
ARGENTINA								
LSOR	Buenos Aires	9,810	ECUADOR			NEWFOUNDLAND		
LSX	Buenos Aires	10,382	El Prado	7,538	VOSZ	St. Johns	6,800
AUSTRALIA								
VK2ME	Melbourne	9,510	EGYPT			NEW ZEALAND		
VK3LO	Melbourne	9,369	SUS	Cairo	9,110	ZL3ZC	Christchurch	6,000
VK3FZ	Melbourne	8,820	FIJI			ZLW	Wellington	10,990
VK2BL	Sydney	9,230	VPD	Suva	14,420	ZL2XX	Wellington	4,776
VK2FC	Sydney	10,520	FRANCE			PHILIPPINE ISLANDS		
VK2ME	Sydney	9,500	YR	Javon	7,463	KAINR	Manila	12,245
VK2ME	Sydney	10,527	PL	Paris (Eiffel Tower)	6,124	KZRM	Manila	11,840
VK2ME	Sydney	10,330	F5GC	Paris	4,262	KZIM	Manila	9,570
			Paris (Pontoise)	15,255	KZRM	Manila	6,140
			Paris (Pontoise)	11,899	POLAND		
			Paris (Pontoise)	11,308	Poznan	9,836
AUSTRIA								
FOR2	Vienna	11,801	FRENCH COLONIES			PORTUGAL		
UOR2	Vienna	6,072	FMSKR	Constantine	7,009	CTIAA	Lisbon	6,995
			FMSKR	Constantine	3,750	CTIBO	Lisbon	10,710
BRAZIL								
PPU	Rio de Janeiro	6,122	GERMANY			ROUMANIA		
PUU	Rio de Janeiro	19,270	DJC	Königs Wusterhausen	6,020	YOI	Bucharest	13,950
			DJA		9,569	SHIP PHONE STATIONS		
			DJD		11,760	GMJO	SS. Belgenland	17,650
			DJE		15,200	GMJQ	SS. Belgeland	13,040
			DJE		17,760	GMJQ	SS. Belgeland	8,570
BRITISH COLONIES								
VRY	Georgetown, Geiana	6,726	GREAT BRITAIN			GMJQ	SS. Belgeland	4,762
V83AB	Johore Baru	7,055	GBK	Bodmin	18,105	DDDX	SS. Bremen	11,710
V81AB	Singapore	7,269	GBK	Bodmin	9,260	EDDX	SS. Bremen	7,560
VQ7LO	Nairobi	6,000	GBX	Chelmsford	11,750	SS. Electra (Marconi's Yacht)	11,240
VQ7LO	Nairobi	6,134	GBX	Rugby	16,164	SS. Homeric	13,040
VQ7LO	Nairobi	9,616	GBS	Rugby	19,310	GDJL	SS. Homeric	12,380
			GBW	Rugby	18,138	WSBN	SS. Leviathan	8,830
			GBW	Rugby	14,493	WSBN	SS. Leviathan	6,637
			GBW	Rugby	12,290	WSBN	SS. Leviathan	4,392
			GBX	Rugby	12,195	WSBN	SS. Leviathan	3,420
			GBS	Rugby	12,195	GWVW	SS. Majestic	17,590
			GBS	Rugby	9,020	GWVW	SS. Majestic	13,223
			GBS	Rugby	6,993	GWVW	SS. Majestic	4,430
			G2MN	Sonning-on-Thames	14,320	GLSQ	SS. Olympic	12,387
CANADA								
VE9GW	Bowmanville, Ont.	6,095	GUATEMALA			GLSQ	SS. Olympic	16,456
CGE	Calgary, Alta.	7,550	TGGA	Guatemala City	10,708	GLSQ	SS. Olympic	8,840
CKS	Calgary, Alta.	7,550	TGGA	Guatemala City	9,370	SIAM		
VE9CG	Calgary, Alta.	6,110	TGW	Guatemala City	6,661	HS2PJ	Bangkok	10,167
VE9CA	Calgary, Alta.	6,030	TGX	Guatemala City	9,516	HS1P2	Bangkok	9,500
CGA	Drummondville, Que.	9,335	HOLLAND			HS1P2	Bangkok	7,300
VE9DR	Drummondville, Que.	11,730	PBF5	Hague	6,438	SPAIN		
VE9CF	Halifax, N. S.	6,050	PCJ	Hilversum	9,590	EAA25	Barcelona	6,000
VE9CL	Middlechurch, Man.	6,148	PHI	Hulzen	17,775	EAB	Barcelona	6,124
VE9DN	Montreal, Que.	6,005	PCK	Kootwijk	18,400	EAM100	Madrid	9,772
VE9DN	Montreal, Que.	5,580	PCV	Kootwijk	17,836	EAR125	Madrid	6,976
VE9DN	Montreal, Que.	11,895	HONDURAS			Madrid	7,025
VE9BA	Montreal, Que.	6,130	HRB	Tegucigalpa	6,170	SWEDEN		
VE9BA	Montreal, Que.	11,705	HRB	Tegucigalpa	6,005	SAS	Karlsborg	11,760
VE9BA	Montreal, Que.	15,190	HUNGARY			SBG	Motala	3,030
VE9OS	Montreal, Que.	2,100	HAT	Szekesfehervar	9,125	SBG	Motala	6,065
VE9AF	Montreal, Que.	2,850	INDIA			SWITZERLAND		
VE9AK	Red Deer, Alta.	2,830	VUC	Calcutta	11,870	HB9OC	Berne	9,130
VE9BJ	St. John, N. B.	6,090	INDO-CHINA			HB9XD	Zurich	9,380
VE9BJ	Saskatoon, Alta.	2,850	F31CD	Chi-hoa	6,119	HB9XD	Zurich	7,220
VE9RM	Toronto, Ont.	2,004	FZG	Saigon	12,010	HB9XD	Zurich	3,488
VE9CS	Vancouver, B. C.	6,148	FZG	Saigon	13,010	TUNISIA		
VE9BZ	Vancouver, B. C.	2,750	ITALY			F8KR	Constantine	7,005
CANARY ISLANDS								
EAR58	Tenerife	7,211	HAJ	Rome	6,667	UNION OF SOVIET SOCIALIST REPUBLICS		
CHINA								
XCTE	Shanghai	5,000	I2RO	Rome	11,810	RW15	Khabarovsk	4,273
COLOMBIA								
HKR	Barranquilla	6,160	I2RO	Rome	3,750	RW3KAA	Leninrad	8,333
HKD	Barranquilla	5,837	THU	Thurin	3,750	Leninrad	11,111
HKD	Barranquilla	6,050	THU	Thurin	3,750	Leninrad	10,526
HKC	Bogota	6,275	THU	Thurin	3,750	RW62	Minsk	6,420
HKF	Bogota	7,616	THU	Thurin	3,750	RW61	Moscow	51,724
HKF	Bogota	8,692	THU	Thurin	3,750	RW38	Moscow	5,515
HKF	Bogota	7,143	THU	Thurin	3,750	RW59	Moscow	6,000
HKF	Bogota	7,139	THU	Thurin	3,750	RW54	Moscow	4,273
HKX	Medellin	11,712	THU	Thurin	3,750	RW50	Moscow	11,924
COSTA RICA								
THNR	San Jose	10,240	THU	Thurin	3,750	RW65	Moscow	3,560
THNR	San Jose	9,734	THU	Thurin	3,750	RW19	Tomsk	8,111
TIRA	Electra Cartago	6,080	THU	Thurin	3,750	UNION OF SOUTH AFRICA		
TIRA	Electra Cartago	9,590	THU	Thurin	3,750	ZTJ	Johannesburg	6,098
CUBA								
CM6DW	Cienfuegos	7,300	INDONESIA			VENEZUELA		
CM2LA	Havana	10,013	PK3CI	Surabaya	2,143	YV2BC	Caracas	6,061
CM2MK	Havana	9,300	PK3CI	Surabaya	6,662	YV4BV	Valencia	11,700
CM2MK	Havana	7,184	PK3CI	Surabaya	9,579	YUGOSLAVIA		
			PK3CI	Surabaya	15,336	Belgrade	10,000
CZECHOSLOVAKIA								
OK1MP1	Prague	5,169	JAPAN			YUGOSLAVIA		
DENMARK								
OXO-0XZ	Copenhagen	6,057	JHBB	Hirasio	7,995	YUGOSLAVIA		
OXO-0XZ	Copenhagen	9,488	J1AA	Kemikawa	8,105	Belgrade	10,000
OXO-0XZ	Copenhagen	15,300	JFAB	Taipei, Taiwan	7,590	YUGOSLAVIA		
DOMINICAN REPUBLIC								
HIX	Santo Domingo	4,610	MADAGASCAR			YUGOSLAVIA		
DUTCH EAST INDIES								
PLB	Bandoeng	9,410	Tananarive	5,552	Belgrade	10,000
PLB	Bandoeng	18,860	MADEIRA			YUGOSLAVIA		
HRB	Bandoeng	5,170	CT3AG	Funchal	6,383	Belgrade	10,000
PK1AA	Batavia	3,998	MEXICO			YUGOSLAVIA		
PK1F	Batavia	17,640	XDA	Mexico City	14,630	Belgrade	10,000
PK1PA	Palembang	59,944	XDA	Mexico City	9,375	Belgrade	10,000
PK2AF	Djocjocarta, Java	5,996	XDA	Mexico City	6,818	Belgrade	10,000
PK6KZ	Makassar	11,993	XDA	Mexico City	5,857	Belgrade	10,000
PK2AG	Semerang, Java	7,890	XDA	Mexico City	11,763	Belgrade	10,000
PK3AN	Surabaya, Java	6,040	XFD	Mexico City	6,667	Belgrade	10,000
			XFD	Mexico City	9,001	Belgrade	10,000
			XFD	Mexico City	11,111	Belgrade	10,000
			X26A	Nuevo Laredo	7,616	Belgrade	10,000

Speech Input Equipment

By Ralph P. Glover *

A DEGREE of satisfaction derived from electrically reproduced entertainment, whether obtained through the home broadcast receiver or the loudspeakers of an extensive sound system, depends on many rather complicated factors. Laying aside the points of purely psychological nature (for they are by no means thoroughly understood as yet), we can briefly tabulate the more basic requirements of satisfactory reproduction which engage the attention of the sound engineer.

1. Each listener of average hearing ability must be furnished an adequate sound intensity. The intensity must be high enough to over-ride local noise but not so high as to become objec-

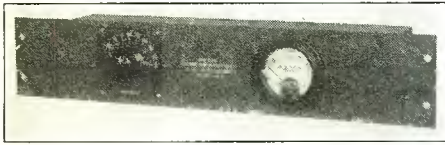


Figure 1

tionable. The matter of proper volume is evidently one for experimentation.

2. Given proper volume, the reproduced sound must also be intelligible and of pleasing quality. This calls for equipment capable of transforming acoustic energy into electrical energy, of properly controlling and amplifying this electrical energy, and then converting back into the acoustic form, with nearly uniform efficiency overall throughout, the useful portion of the audio-frequency spectrum. In the case of broadcasting, the receiver itself is naturally an important link in the chain of complicated equipment which begins at the studio microphone. Probably each individual mechanism in the reproducing channel, including the auditory facilities of the listener, leaves its imprint on the eventual sense impressions, but it is evident that any form of distortion becomes increasingly serious the closer it occurs to the original sound source. Thus the radio receiver can do practically nothing to compensate for deficiencies inherent in the broadcast station itself, nor is it possible within the broadcast station itself, for instance, to correct in subsequent amplifiers for certain forms of distortion arising in the mixer. As still another example, there is nothing that can be done at the loudspeaker end of the public address system which will rem-

edy the effects of an overloaded amplifier.

3. There is still a third characteristic of satisfactory reproduction, not included in the general points mentioned above, which for want of better nomenclature we may term *pleasing and accurate control*. An excellent example can be borrowed from the technique of the motion picture cameraman. Prior to the production of "The Birth of a Nation," by Griffith, the scenes shifted from locale to locale with disconcerting abruptness, and when the last scene reached its invariant culmination the picture simply stopped. Griffith saw the artistic shortcomings of the abrupt transitions and developed the "fadeout" whereby there is a gradual blending or merging of one scene into the next. Every broadcast listener will recognize the acoustic counterpart of this effect in the "fading" from one selection to the next accomplished in the studio control room. Where fading is not possible and it is necessary to switch rapidly from one source to another, preliminary adjustments are always made to insure constant volume. What has been said above also applies generally to all kinds of high quality sound systems such as public address installations, sound recording plants and the like.

A title, "speech input equipment," is loosely applied to all of the audio-frequency apparatus closely associated with the sound source. In the broadcast station this includes the mixing, fading and switching equipment operated by the monitoring control operator, the line and monitoring amplifiers, volume indicators and similar equipment. Only minor differences apply to similar apparatus in sound systems. Practically all control of the outgoing program is centered in the speech input equipment, and its vital nature and position in

the circuit combine to emphasize its importance as outlined above.

Volume Indicator

The volume indicator is a most important accessory of the speech input system, and a typical panel-mounting instrument is shown in Fig. 1. As might be judged from its name, the function of the volume indicator is to measure the "volume," or more strictly, the *power level* of the electrical energy at some point in the cir-

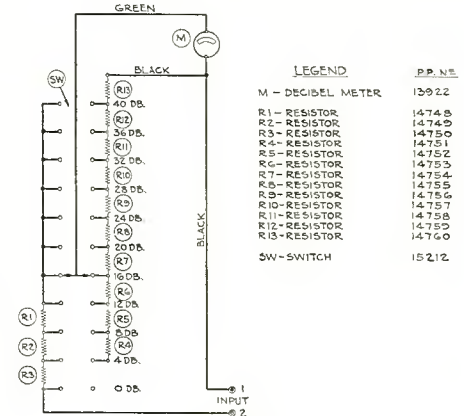


Figure 2

cuit. It is obvious that constant sound volume will obtain if the power level is constant.

Volume indicators occupy a position in the communications field which is closely comparable to that of the wattmeter in commercial-frequency power measurements. When correctly used, it provides an accurate quantitative measure of power just as the wattmeter does. This property enables the control operator to keep the signal well below the overload level of succeeding amplifiers. In broadcasting this is of the utmost importance, for there is a certain peak signal level at which overmodulation of the radio-frequency carrier takes place, resulting in very evident distortion to the listener.

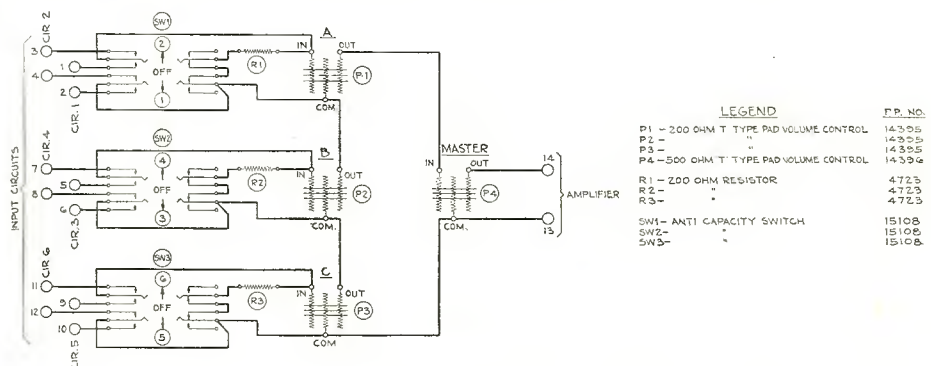


Figure 3

* Sound Engineer, Silver-Marshall, Inc.

It should be remembered that during ordinary speech or music there is no such thing as constant volume from instant to instant. The volume actually varies with the inflection of the speaker's voice from syllable to syllable. Volume changes are also inherently necessary to the proper rendition of any type of music. As a result, the pointer of the volume indicator meter fluctuates back and forth over a considerable range. As mentioned before, the maximum indica-

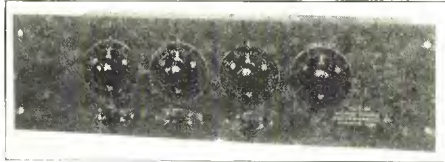


Figure 4

tion of the meter is of importance in broadcast work for overmodulation, as a rule, will only occur during instants of maximum level.

Instead of being calibrated directly in watts as in the case of the wattmeter, the volume indicator is calibrated in decibels. The decibel (DB) is a logarithmic unit long used by the telephone systems for voice-frequency measurements and is based on the common logarithm of the ratio of two powers. One of these powers is arbitrarily selected as a reference power, and any other power can then be stated in terms of decibels above or below the reference value. There are a number of different reference powers in use, the more common ones being .006 watts and .010 watts. If we assume the .006-watt reference power, a power of .06 watts would have a power level of +10 decibels. A power of 0.6 watts would correspond to +20 decibels, and so on. Six milliwatts is evidently at a power level of 0 decibels, and similarly, a power level of 6 microwatts would be -30 decibels in our adopted reference system. The decibel, sometimes known as the transmission unit (TU), is very convenient in all sorts of sound work, for a change in level of 2 decibels is approximately the minimum change in volume readily detected by the human ear, the ear following a logarithmic rather than a linear response law. Thus if the power level fed to a loudspeaker were raised in steps of 2 decibels, the listener would sense a number of volume changes increasing at a constant rate. The usefulness of this relationship is at once evident.

There are two general types of volume indicators. Both types are in reality voltmeters calibrated in terms of decibels for the adopted reference system. It is thus only necessary to connect the volume indicator across the circuit at the point where the

power level is to be measured. A direct indication of power level will be afforded provided the impedance of the circuit is the same as that for which the meter was calibrated. Volume indicators are usually calibrated to read directly on 500-ohm circuits, although a correction factor can be readily applied for other impedances. It is very desirable for obvious reasons that the bridging of the volume indicator across the circuit introduce a negligible volume change due to the shunting effect, which can be compared to the necessity for using a high-resistance voltmeter when checking D.C. plate supply voltages. The early types of volume indicators found in telephone offices and broadcast stations made use of vacuum-tube voltmeter circuits, for no switchboard meters of sufficient sensitivity were



Figure 5

then available. The recent perfection of the rectifier meters simplified the problem greatly by eliminating the expense of vacuum tubes with attendant power supply, and, at the same time, made unnecessary the critical adjustments of grid bias that were formerly required to maintain accuracy. The volume indicator illustrated in Fig. 1 consists of a sensitive low-range rectifier-type meter of high resistance whose scale is calibrated directly in decibels above and below 6 milliwatts. This power is assumed to be dissipated in a 500-ohm circuit. The meter itself covers a range of -8 to +8 decibels, and this is extended, by means of a tapped network, 40 decibels in ten steps of 4 db each.

In the broadcast studio, the volume indicator is usually connected across the telephone line leading to the transmitting station. The peak power level at this point must be limited to 0 decibels to avoid interference by induction in other nearby telephone lines. In public address systems, the volume indicator may be connected across the voice-coil line and thus enables the operator to maintain a constant volume which can be set definitely below the level at which there is danger of damage to the reproducers.

The Mixing Panel

While we have discussed the need for maintaining constant volume, the method of volume or power level measurements and the desirability of

means for producing gradual volume changes without impairing the quality in any way, nothing has been said about the actual method of controlling volume in speech input circuits.

A simple method of controlling volume is obviously that of regulating a potentiometer at the input of the amplifier. Unfortunately this system is never feasible when a variety of input sources, such as microphone or phonograph pickup, are fed to the amplifier, and it is desired to switch from one source to the other without pronounced volume changes. This is evident, for the output level of a high-quality double-button carbon microphone is seldom more than -45 decibels, while that of a phonograph pickup is usually about -20 decibels. It has therefore become common practice to provide separate volume controls for each input source itself, and these volume controls are usually connected together to form a *mixing circuit*. The most rudimentary mixing circuit consists merely of a number of potentiometers connected across the individual sources, the potentiometer outputs being connected in series with the amplifier input terminals. This elementary mixer, however, has a great many drawbacks, and a really satisfactory solution involves a somewhat more complicated arrangement. In the first place, the simple potentiometer mixing control presents an impedance to the source which varies with the position of the potential arm or slider. This does not impair the quality of reproduction when the source is a microphone, but in the case of phonograph input, the quality undergoes marked changes as the control is varied. Moreover, adjustment of any one of the potentiometers will affect the output of other sources not connected directly to the potentiom-

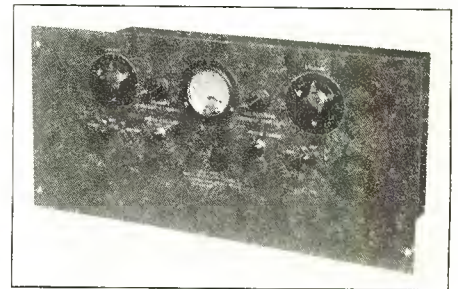


Figure 6

eter in question.

These difficulties are eliminated in the mixing circuit illustrated in Fig. 3. The three mixing controls marked A, B and C, as well as the master control are all of the constant impedance type and are familiarly known as "T" pads. Such volume controls present a constant impedance to both the
(Continued on page 38)

Receiver Performance Curve Section


SERVICE men, dealers and technicians will find on this page our conception of an ideal set of curves. The composite graph may be used to visualize the best possible receiver performance. The more a receiver's curves near parallelism with the ideal, the better the receiver. These curves are not capable of interpretation by a layman. They should be translated only by a service man, dealer, technician or engineer.

Measurements made in our engineering laboratory cover sensitivity, selectivity and electrical fidelity. Standards for these three qualities have been set by the IRE and RMA engineering committees. No standards have yet been adopted for sound pressure measurements. Until a standard is selected, our laboratory will measure only electrical fidelity, which disregards speaker response curves. The fourth measurement appearing with the sensitivity, selectivity and electrical fidelity curves represents power overload curves, or automatic volume control curves, as the case may be.

Definitions of the three major characteristics of a receiver are:

Sensitivity is that characteristic of a receiver which determines to how weak a signal it is capable of responding. It is measured quantitatively in terms of the input voltage required to give standard output. The ideal sensitivity, according to the graph on this page, would fall between the two lines, ranging from 10 to 5 microvolts (absolute) or less. This is an arbitrary value.

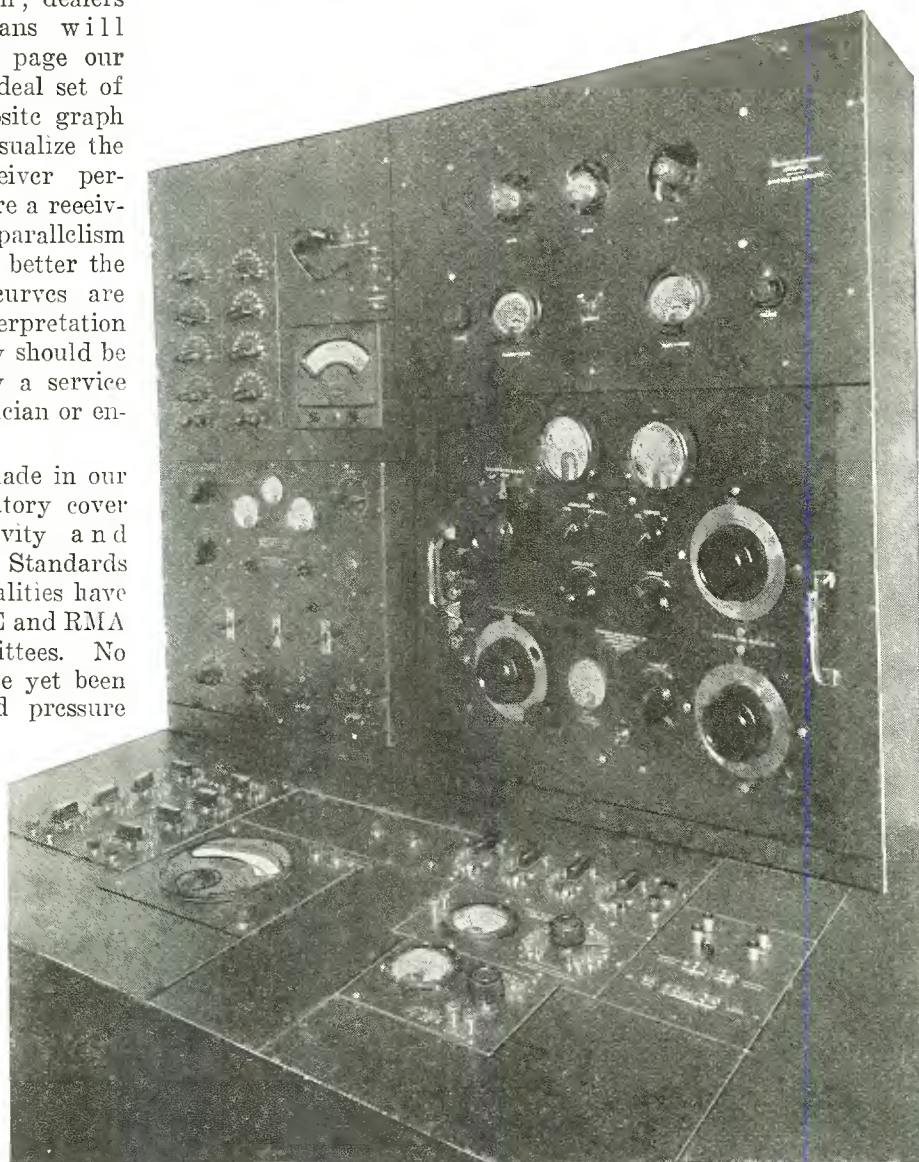Selectivity is the degree to which a receiver is capable of differentiating between the desired signal, and signals of other carrier frequencies. This characteristic is not expressible by a single numerical value, but requires one or more graphs for its expression.



sides would be 10 kilocycles apart nearly all the way up the graph sheet. Selectivity as measured by our laboratory only concerns itself with energy entering the receiver via the input circuit (disregarding shielding effectiveness), since no standard has as yet been adopted to simulate selectivity conditions in the field.


Fidelity is the degree to which the receiver accurately reproduces at its output terminals, the modulated form of the received wave impressed upon it. Ideal electrical fidelity curve would be a horizontal line almost flat over the frequency range from 60 to 5000 cycles. This range is also of

Best selectivity possible would be somewhat like a "chimney" whose

an arbitrary width.

The photograph illustrates the equipment used in making the measurements. It conforms to the specifications of the IRE and RMA Standardization Committees. All test frequencies are determined by zero beat of a crystal-controlled dynatron oscillator. Voltmeters and microvoltmeters are periodically checked against calibrated standards for accuracy of adjustment. Individual conditions of measurement pertaining to each receiver will be found in the text accompanying each family of curves.

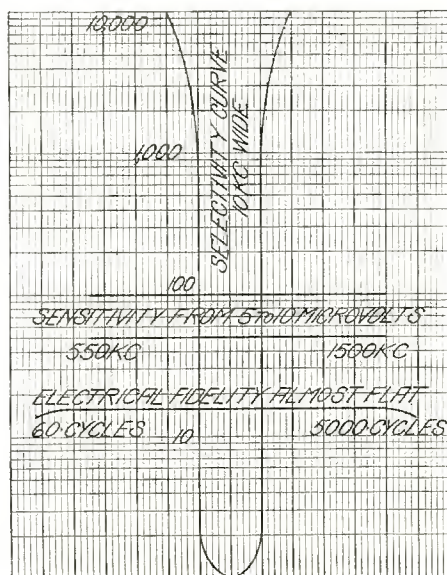Since curves of all receivers are taken under the same conditions, it may be said that such curves constitute a yardstick by which receivers of the same general class may be compared, as long as this analysis is made by those technically competent to do so.



Ideal Composite Curve

All American Mohawk, Lyric S-7





INCLUDED overall performance curves on the All-American Mohawk Lyric model S-7, recently made in our laboratory, are given here as indicative of this superheterodyne's performance.

Input to the receiver antenna circuit was through the standard dummy antenna of 20 uh, 200 uuf and 25 ohms. An output level of .05 watts was maintained for all measurements

the tuned circuits from factory adjustment, and the tubes employed were those furnished as standard equipment with the receiver by the manufacturer.

From the sensitivity curve of column 1, an average value of 11.82 microvolts absolute is taken. This value corresponds to 2.95 microvolts per meter when a standard four-meter antenna is used. At 600 kc the mini-

schematic wiring diagram of the model S-7. The seven required tubes are a 551 r-f, 224 first detector, 227 oscillator, 551 second i-f, 224 second detector, 247 output tube, and a 280 full wave rectifier. The speaker field is used as a choke in the negative return system and has across it the resistance network necessary for properly biasing the output pentode tube. No other filter system is employed in

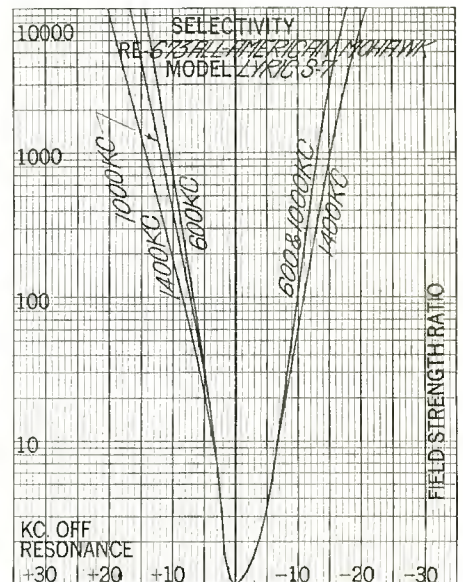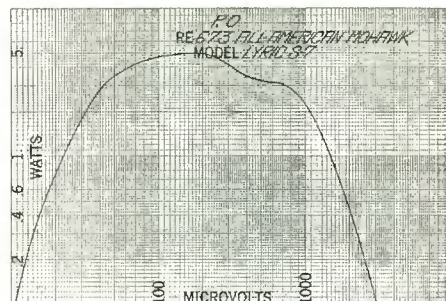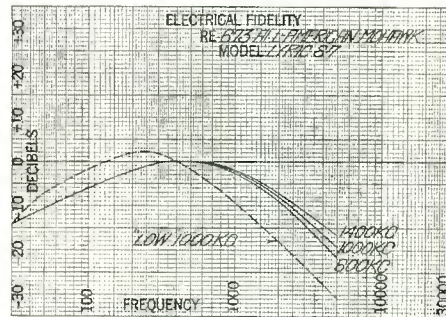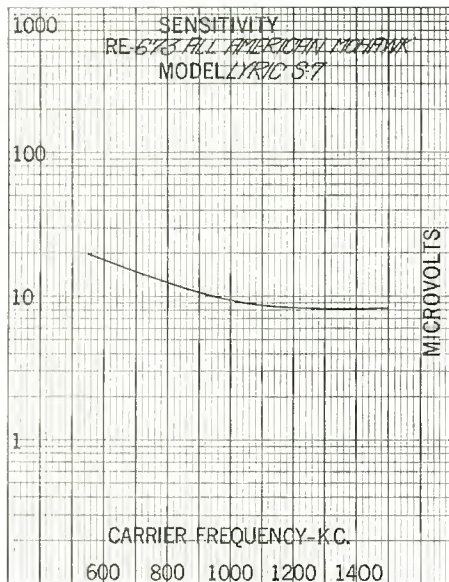

except that of power overload. A non-inductive load resistance of 7000 ohms matched the optimum operating impedance of the single 247 pentode power tube, the plate of which was capacitatively coupled to the output indicating tube voltmeter. To prevent any error in output reading due to secondary load, the voice coil of the speaker was opened.


A line voltage of 119 volts gave the receiver power transformer primary a current drain of .67 amperes. For all tests the volume control was turned to its maximum position, no alterations were made on the alignment of any of

the tuned circuits from factory adjustment, and the tubes employed were those furnished as standard equipment with the receiver by the manufacturer. From the sensitivity curve of column 1, an average value of 11.82 microvolts absolute is taken. This value corresponds to 2.95 microvolts per meter when a standard four-meter antenna is used. At 600 kc the minimum noise level of 7.6 per cent occurred, while the maximum of 36 per cent was found at 1400 kc. At 1000 kc the measured image ratio was found to be 95,300 times. In column 2, the power overload curve gives a maximum output of 4.89 watts. This value does not take into consideration any harmonics introduced into the wave form in the amplifier. Under the selectivity curves given in column 3 are the tabulated band widths.

At the bottom of the page is the

schematic wiring diagram of the model S-7. Oscillator energy is coupled inductively to the grid coil of the first detector tube. Tone control is accomplished with a 30,000 ohm variable resistor in series with a condenser with a capacity of one-tenth microfarad, both connected from the plate of the pentode to plus B.

Times Field Strength	Band Widths		
	600 ke.	1000 ke.	1400 ke.
10	10	10	10.5
100	17	17.5	19.5
1000	24	25.5	29.5
10000	32	34	41

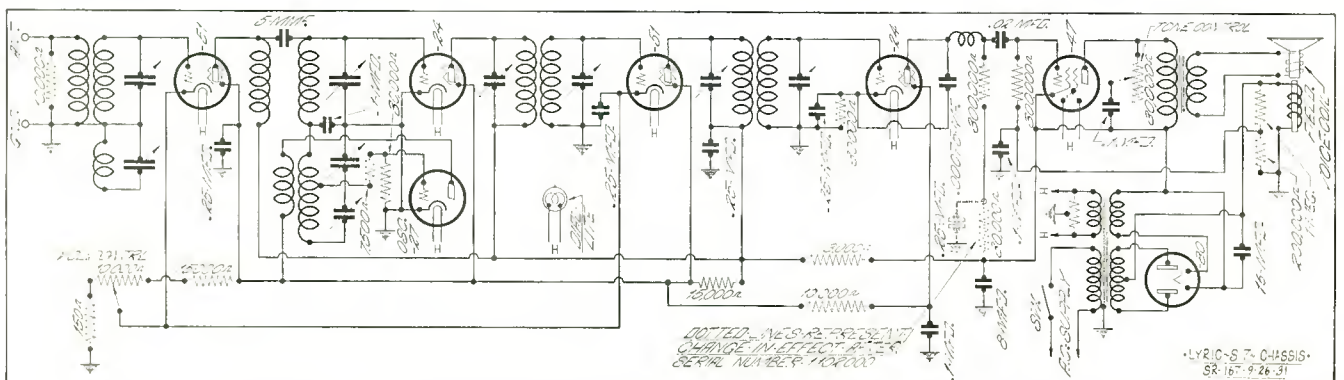

Crosley Battery Model 27

CROSLEY'S model 27 battery operated receiver, when recently measured in our laboratory, gave the performance curves shown on this page.





Output of the signal generator was coupled to the input circuit of the receiver by means of a dummy antenna standard of 20 uh, 200 uuf and 25 ohms. To match the push-pull 231

value. For all measurements the tubes used were those furnished with the receiver by the manufacturer, the volume control was turned for maximum receiver sensitivity, and no changes were made in the alignment of the tuned circuits from factory adjustment.

From the sensitivity curve of column 1, the average is found to be 130

ation is made of the harmonic distortion present at this high level across the plate circuit of the output tubes. Band widths will be found tabulated under the selectivity curves in column 3.

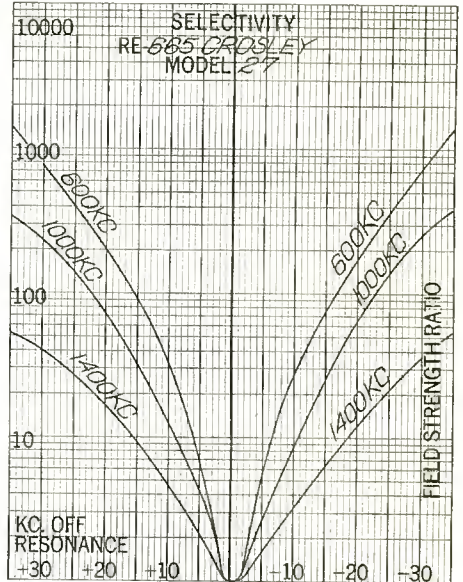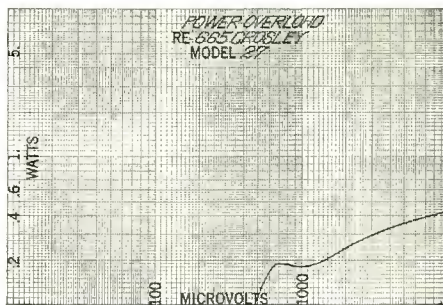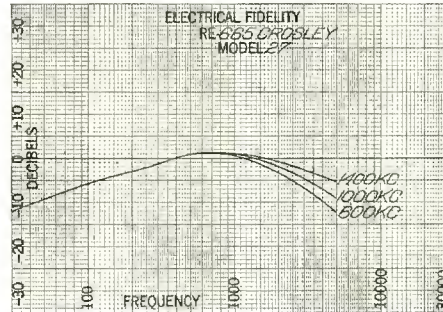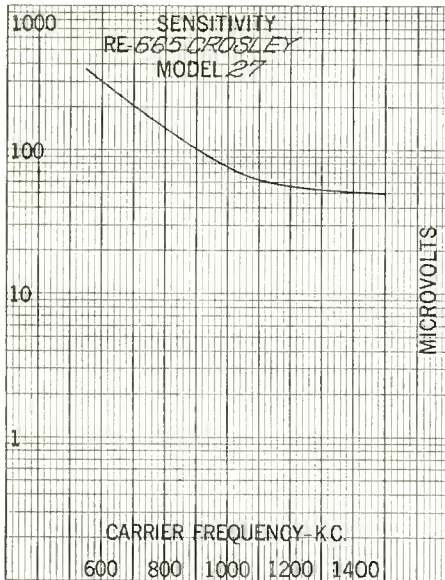Below is the schematic wiring diagram of the model 27. Required tubes are seen to be a 232 first r-f, 232 second r-f, 232 detector, 231 intermedi-




tubes used as the last audio amplifier, a non-inductive load resistance of 9,900 ohms was connected across their plates, the latter being capacitively coupled to the output indicating tube voltmeter, which read the standard output of .05 watts for all measurements except the power overload curve. To prevent any reflection of secondary load impedance on the primary circuit, the speaker transformer was replaced by a choke of suitable

microvolts absolute, which is equivalent to 32.5 microvolts per meter. Noise levels at all points on the dial were less than 1 per cent and hence negligible. From the power overload curve of column 2 the maximum output is found, at 10,000 microvolts input to the receiver, to have a value of .416 watts. However, no consider-

ate audio, and push-pull 231 output power tubes. It will be seen that the antenna is coupled to the antenna coil through two series condensers.

Times Field Strength	Band Widths		
	600 kc.	1000 kc.	1400 kc.
10	12.5	19	34
100	32	45	..
1000	65
10000

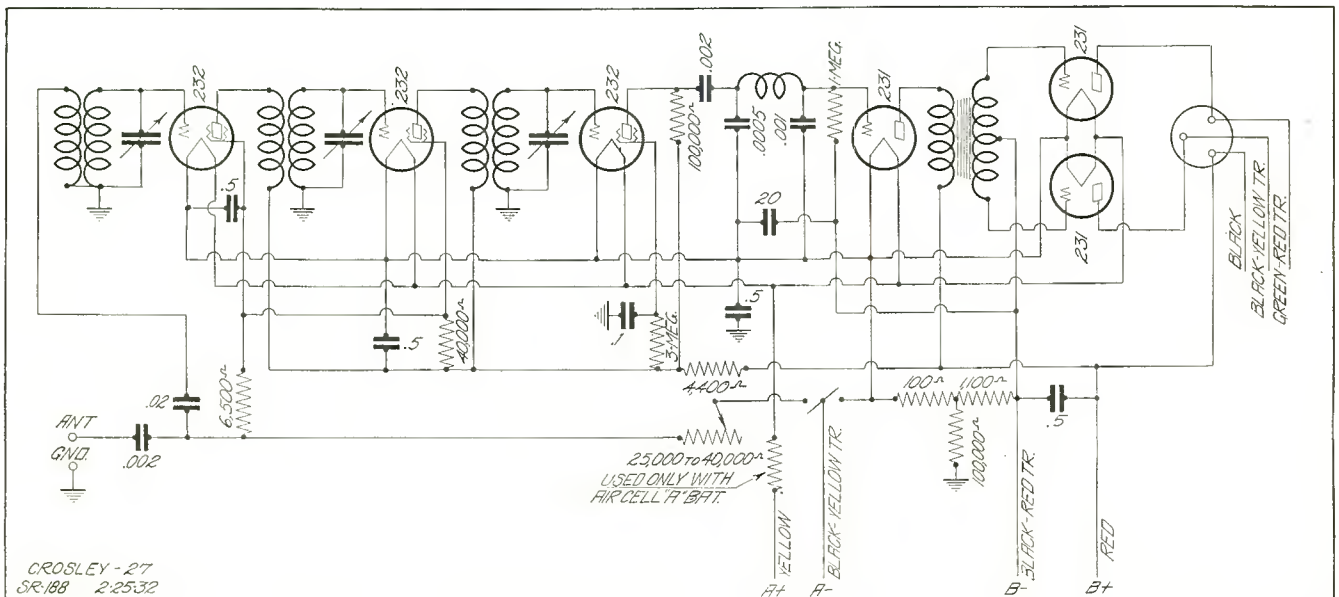

Perfectone Auto Radio Model 7-T-38





PERFORMANCE curves of the Perfectone Auto Radio model 7-T-38 are given on this page.

A dummy antenna standard of 20 uh, 200 uuf and 25 ohms was used to couple the output of the signal generator to the receiver input circuit. To match the push-pull 238 pentodes in the last audio stage, a non-inductive

alignment, the volume control was turned to maximum, and the tubes were furnished with the receiver.

An average sensitivity of 5.64 microvolts absolute was taken from the sensitivity curve, this value corresponding to 1.41 microvolts per meter. At 600 kc the noise level was 8.4%, the maximum, and at 1400 kc, 1.6%,

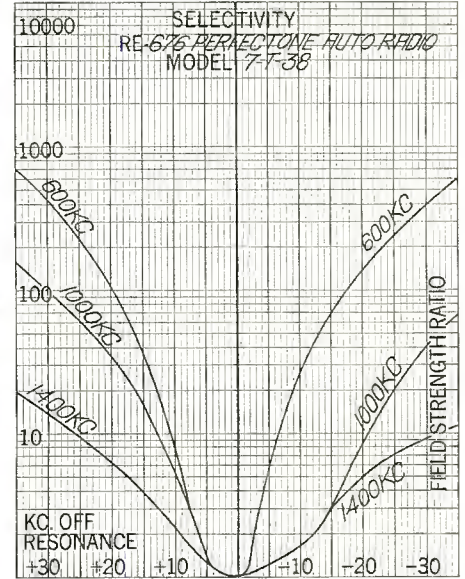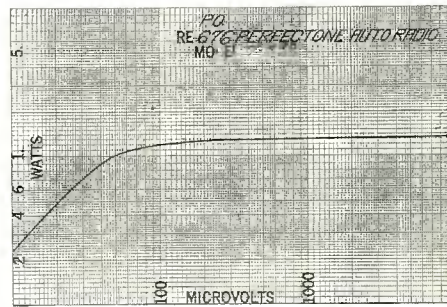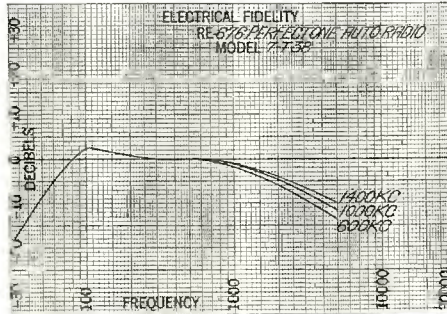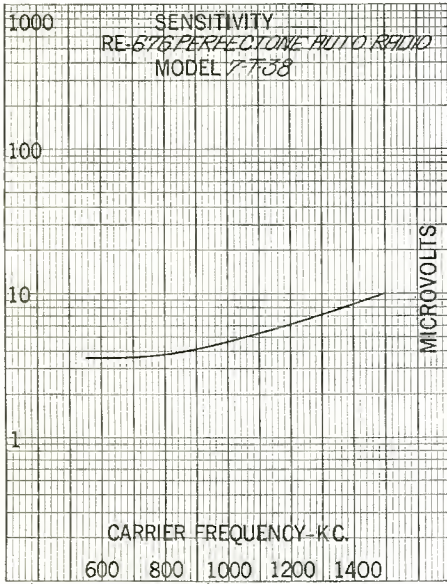At the bottom of the page is a schematic wiring diagram. Tubes necessary for operation are a 224 first r-f, 224 second r-f, 224 detector, 237 automatic volume control, 237 intermediate audio, and push-pull 238 output tubes. Volume control is accomplished by means of a variable resistance from ground to the plate of



load resistance of 30,000 ohms was connected across their plates, which in turn were capacitatively coupled to the output indicating voltmeter. The voice coil of the dynamic speaker was opened to prevent any secondary loading effects.


Measured drain on the 180 volt B battery supply was 44 ma in the —B lead. No changes were made in circuit

the minimum. The automatic volume control curve gives the maximum output as 1.33 watts, no consideration being made of the harmonic content of the output wave form. Band widths are given under the selectivity curves of column 3.

the intermediate audio stage, parallel feed being used on this tube.

Band Widths

Times Field Strength	Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	17.5	33.5	58
100	37	72	...
1000	81
10000

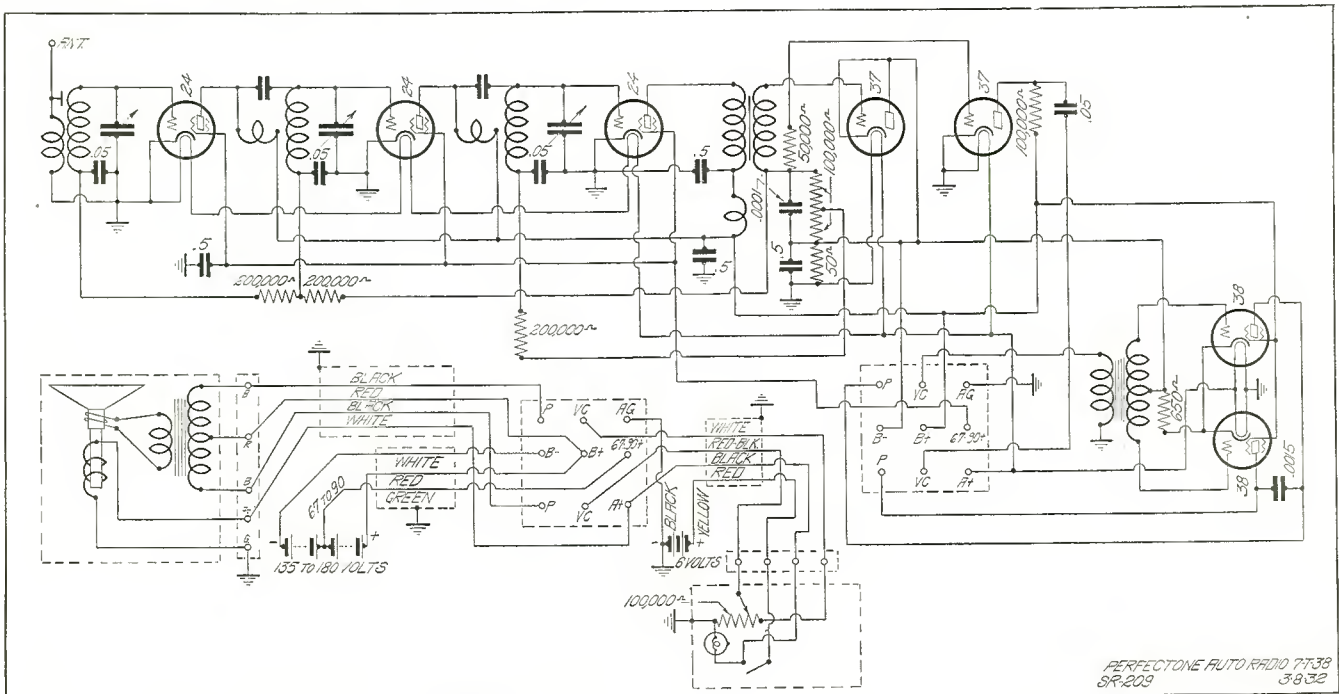

PERFECTONE AUTO RADIO 7-T-38
SR-209 3-9-32

Philco Models 51 & 51-A

RESPONSE curves made on the Philco model 51, given on this page, were recently made in our laboratory.





To couple the signal from the standard signal generator to the receiver, a dummy antenna standard of 20 uh, 200 uuf, and 25 ohms was connected to the antenna circuit. The output indicating tube voltmeter, used to in-

as standard equipment were employed, no changes from factory adjustment of tuned circuits was made, and the volume control was turned to its maximum position.

Column 1 shows the sensitivity average to be 44.4 microvolts absolute, corresponding to 11.1 microvolts per meter when using the standard 4 meter height antenna. Noise level

column 3 from which they were taken.

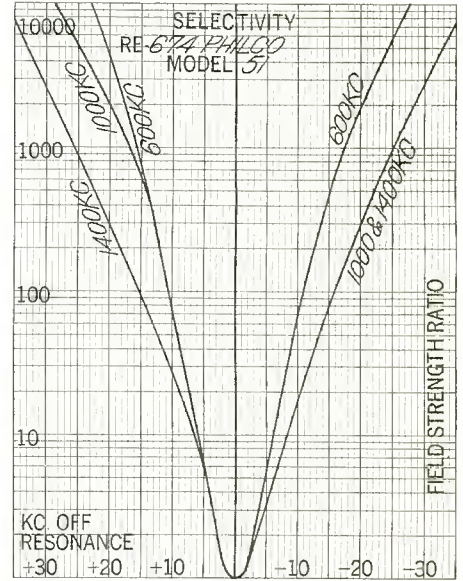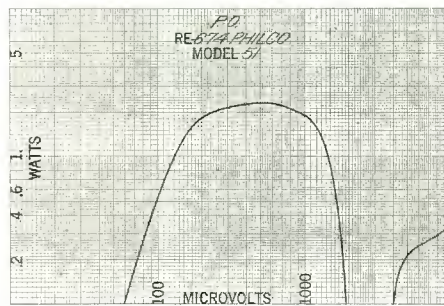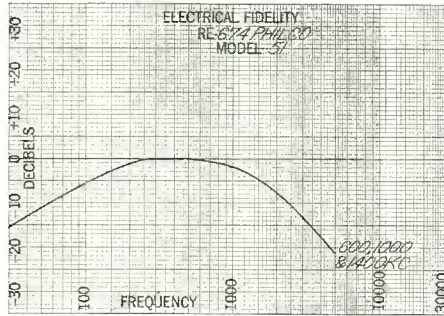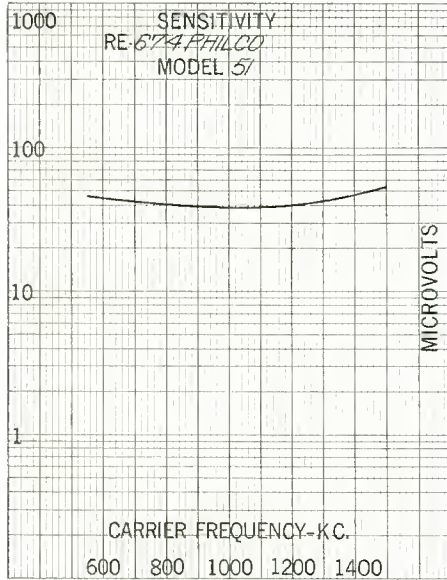A schematic wiring diagram of this Philco superheterodyne is given below in detail. Only five tubes are required, a 224 combination first detector and oscillator, a 235 second i-f, 224 second detector, resistance coupled to the 247 power output pentode, and a 280 type rectifier for power supply to the receiver. The speaker field




dicating watts output, read the standard audio output level of .05 watts except for the power overload curve. To match the single pentode output tube, a non-inductive load resistance of 7000 ohms was connected across the plate circuit. This was in turn capacitatively coupled to the tube voltmeter. The voice coil circuit of the dynamic speaker was opened to prevent any impedance reflection from the secondary circuit to the primary.

A line voltage of 111 gave the receiver a drain of .51 amperes a-e. In all measurements, the tubes furnished

maxima and minima were respectively 2.1% at 800 kc, and 1.2% at 600 kc. At 1000 kc the measured image ratio was found to be 5300 times. Column 2 gives the maximum power output to be 2.27 watts. However, this figure does not take into account the harmonic distortion present in the wave form of the audio voltage across the primary of the output transformer. Tabulated band widths are given under the selectivity curves of

is used in the B return lead to provide bias voltage for the pentode. This bias is taken from a tapped high resistance shunt across the field coil. The volume control operates on the i-f stage, and to provide complete control on locals, on the minimum position it is grounded.

Times Field Strength	Band Widths Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	12	14	15
100	22	27	31
1000	33	42	51
10000	50	66	75

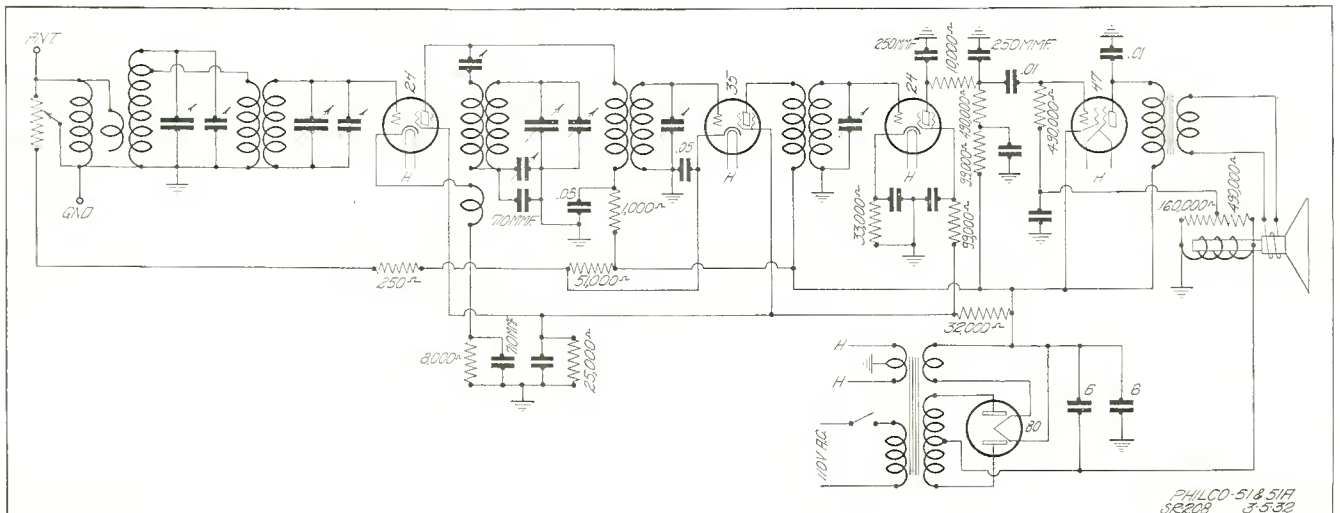

RCA-Victor Model 43





RCA Victor's model 43 gave the included performance curves on measurement in our laboratory recently.

Energy from the signal generator was coupled to the receiver input terminals through a standard dummy of 20 uh, 200 uuf and 25 ohms. The output impedance of the class B 230 push-pull output tubes was matched with

with the receiver as standard equipment, and the factory adjustment of the tuned circuits was not altered.

From the curve of column 1 an average sensitivity of 6.65 microvolts absolute is found, which corresponds to 1.66 microvolts per meter when a standard four-meter antenna is used. A maximum noise level of 30 per cent was measured at 1400 kc, while the

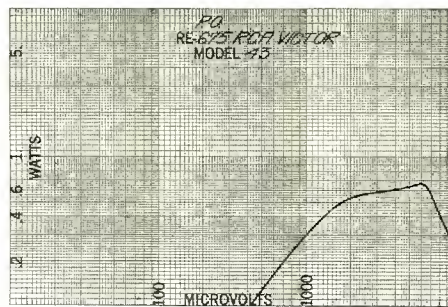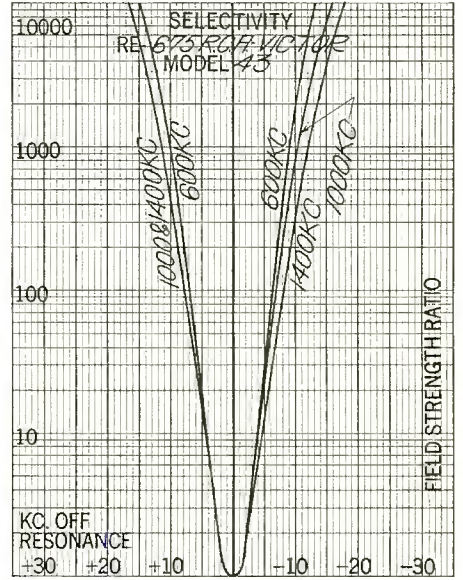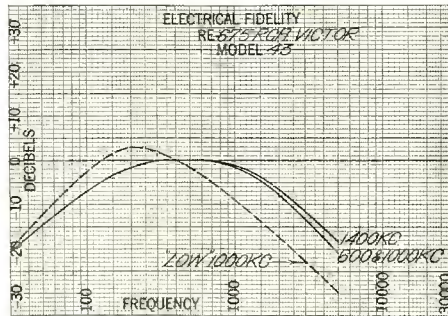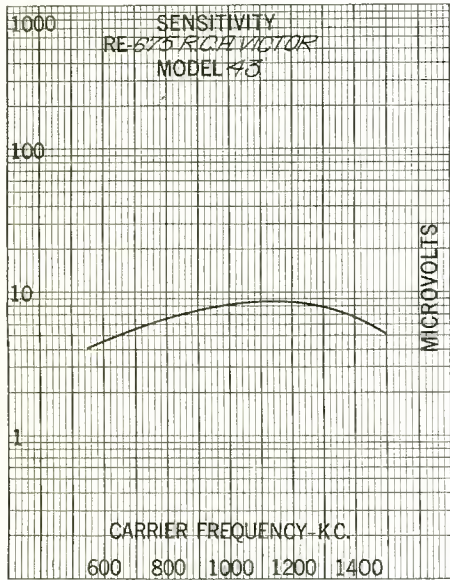given below. From it the tubes necessary for operation are found to be a 232 r-f, 232 first detector, 230 oscillator, 232 i-f, 230 second detector, 230 intermediate audio, and push-pull 230 tubes used in class B amplification. It is interesting to note that the unusual output of more than half a watt of audio power is obtained by using 230 tubes in push-pull by employing



a non-inductive load resistance of 25,000 ohms connected across the plates. These were in turn capacitatively coupled to the output indicating voltmeter, which read the voltage corresponding to an output of .05 watts for all curves except that of power overload. The voice coil of the permanent magnet type dynamic speaker was opened during measurements to prevent any load reflection to cause error in output readings.

A drain of 14 ma was measured in the -B lead of the battery supply. During measurements the volume control was turned to its maximum position, tubes employed were furnished


minimum of 4 per cent is found at 1000 kc. With the dial adjusted to 1000 kc, the image ratio measured 1900 times. A maximum output of .655 watts is taken from the power overload curve of column 2. No account was taken, however, of the produced harmonics present across the output transformer primary. Band widths are tabulated under the selectivity curves from which they were taken in column 3.

A schematic wiring diagram is

class B amplification. Also the B battery drain for this eight-tube superheterodyne is only 14 ma. Most of the saving is due to the output tube circuit which is the first of this system we have measured. A permanent magnet type dynamic speaker gives full dynamic results without requiring external field excitation.

Band Widths

Times Field Strength	Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	8.5	9	9.5
100	13.5	14	16
1000	19	21	23.5
10000	28	32.5	34.5

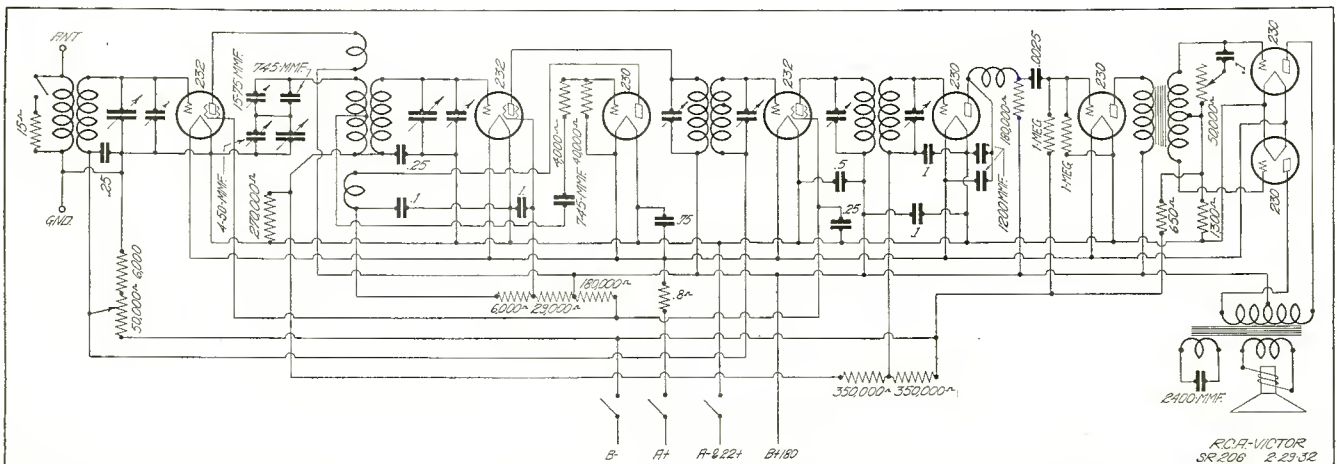

Silver-Marshall Model Q

OVERALL performance curves on the Silver-Marshall model Q are given on this page from data made in the laboratory upon measurement of this combination short wave and broadcast receiver.





Input to the receiver was through the standard dummy antenna of 20 uh, 200 uuf and 25 ohms. The plate

control was turned to maximum, the tubes as furnished with the receiver were employed, and no changes were made in the adjustment of the tuned circuits.

An average sensitivity of 3.31 microvolts absolute is found from the curve of column 1. This value corresponds to .83 microvolts per meter.

sideration of the harmonics produced in the audio system. Under the selectivity curves of column 3 are found the band widths.

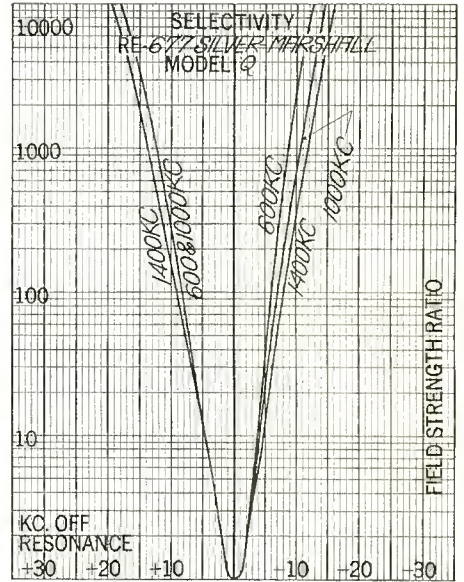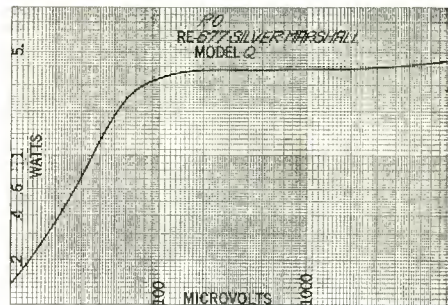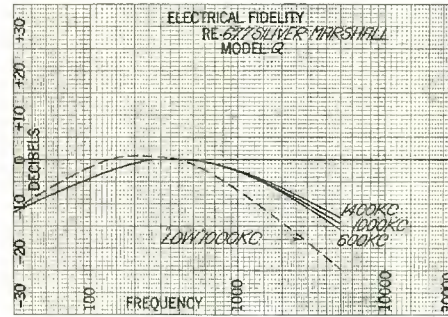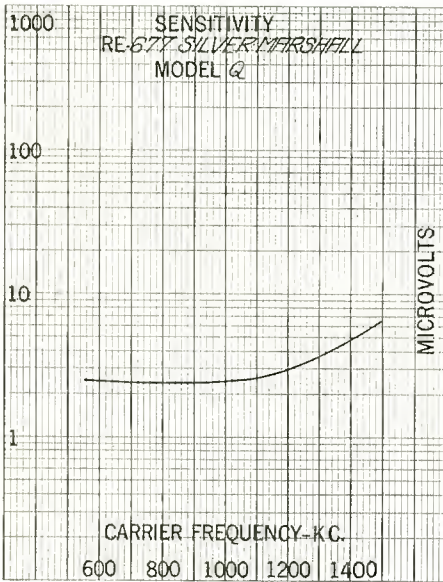At the bottom of the page is a schematic wiring diagram of this superheterodyne. Tubes required for operation are a 224 first detector, 551 second i-f, 551 third i-f, 227 oscillator,




load of the parallel 247 pentodes was matched by a 3500 ohm non-inductive resistance connected across the output circuit. The plates of the output tubes were capacitatively coupled to the output meter, the voice coil being disconnected during measurements.

With a line voltage of 118 volts, the current drain of this receiver was 1.09 amperes. For all tests the volume

At 600 kc, the minimum noise level of 19.2 per cent was measured, while the maximum of 63.5 per cent occurred at 1400 kc. An image ratio of 14,500 was found at 1000 kc. Power output reached a maximum value of 4.45 watts, but this figure makes no con-

227 automatic volume control, 227 harmonic producer, 227 second detector, parallel 247 pentodes, and a 280 full wave rectifier.

Times Field Strength	Band Widths		
	Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	8	8.5	9
100	14.5	15.5	17
1000	21.5	23	25.5
10000	30.5	32.5	34




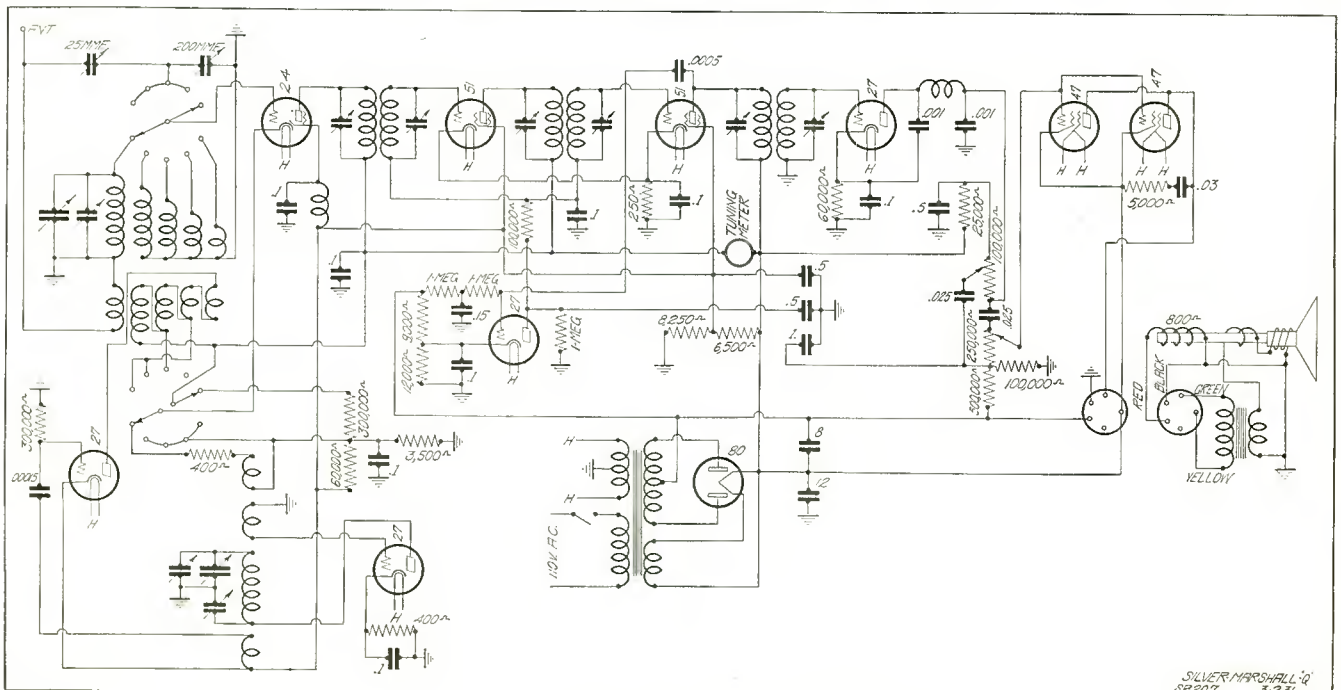


Stromberg-Carlson Model 29

STROMBERG-CARLSON'S model 29 is presented here with curves to indicate its performance. It is supplied with an automatic volume control feature which operates very satisfactorily. A dummy antenna of 20 uh, 200 muf, and 25 ohms served to couple the generator to the input system of the receiver. To properly match the push-

line voltage of 118 volts a-c. In all tests, the volume control was adjusted for maximum receiver sensitivity, no changes were made from factory adjustment of tuned circuits, and the tubes employed were those furnished by the manufacturer with the receiver. A sensitivity average of the curve of column 1 gives a value of 6.94 microvolts absolute, which is equivalent

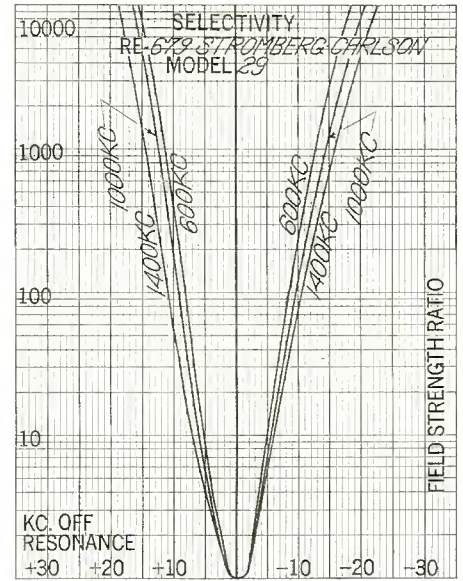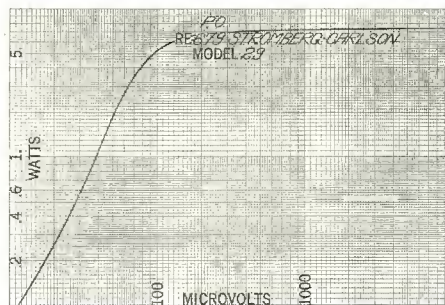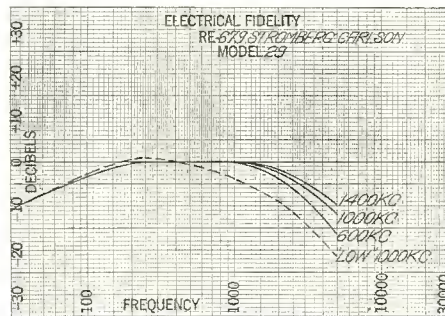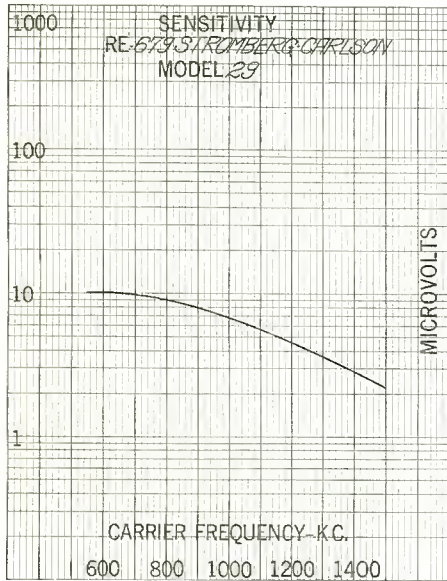No account is made of the harmonic content of the audio wave form at this high level of output. Under the selectivity curves of column 3 are the band widths in tabular form. A schematic wiring diagram of this superheterodyne is shown below. From it the required tubes are seen to be, a 235 r-f, 235 first detector, 235 second i-f, 227 oscillator, 227 second




pull 245 power tubes employed, a non-inductive load resistance of 7800 ohms was connected across their plates which were in turn connected to the output indicating tube voltmeter which read a standard output level of .05 watts for all of the curves with the exception of the power overload. Due to errors which would be introduced otherwise, the voice coil circuit of the dynamic speaker was broken for measurement purposes. Power transformer primary current was .99 amperes with an impressed

to 1.73 microvolts per meter when a standard height antenna is used. At 1400 kc occurred the maximum noise level with a value of 19%, while the minimum value was found at 600 kc, namely 10.6%. With the set tuned to 1000 kc, the image ratio was measured as 137,000 times. The power overload curve in column 2 shows the maximum value to come at an input of 10,000 microvolts. It is 7.4 watts.

detector, 235 audio stage, push-pull 245 power tubes, and a 280 full-wave rectifier. A line filter for the a-c line is made up of two .01 mfd condensers connected across the line with their common point grounded. A tuning meter makes possible exact tuning.

Band Widths

Times Field Strength	Kilocycles width		
	600 ke.	1000 ke.	1400 ke.
10	10	11.5	13
100	17	18.5	21.5
1000	24	28	30.5
10000	34	37	41.5

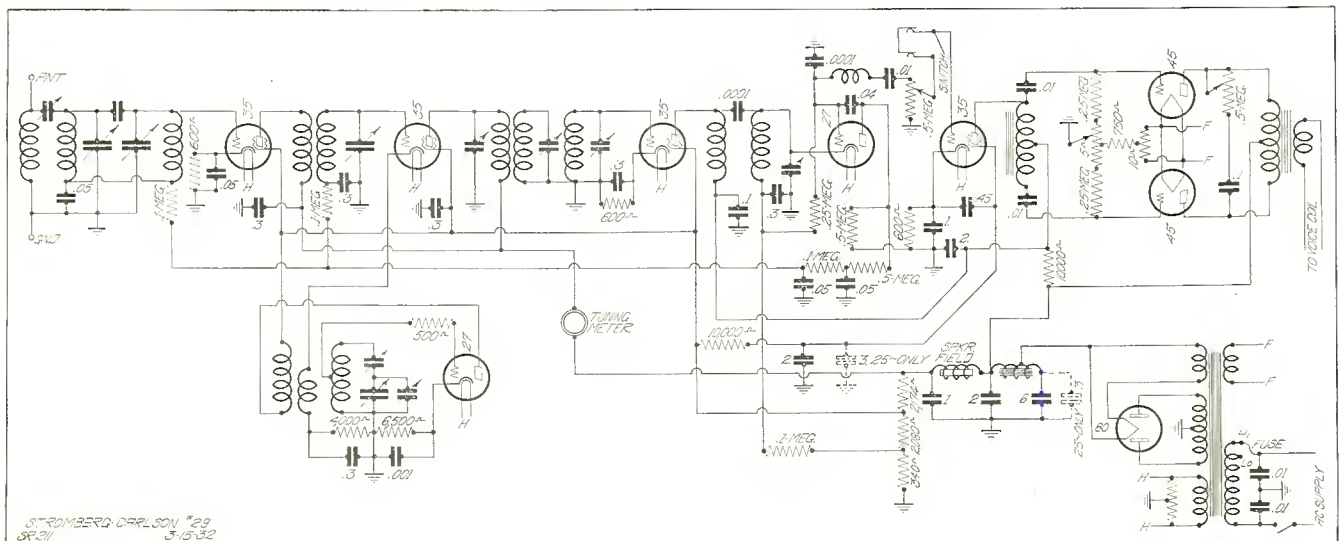

United American Bosch Model 5

RECENT measurements on the United American Bosch model 5 resulted in the included overall performance curves.





For antenna input, the signal generator was coupled by means of a dummy antenna standard of 20 uh, 200 uuf, and 25 ohms. A non-inductive load resistance of 7000 ohms matched the output impedance of the

were made on the adjustment of the circuit trimmers. A line current of .53 amperes was drawn with a line voltage of 115 volts.

An average sensitivity of 44 microvolts absolute is taken from the curve of column 1. The equivalent in microvolts per meter is therefore 11. A maximum noise level of 3.3% is found at 1400 kc, while at all other frequen-

der the selectivity curves in column 3 from which they were taken, are the band widths.

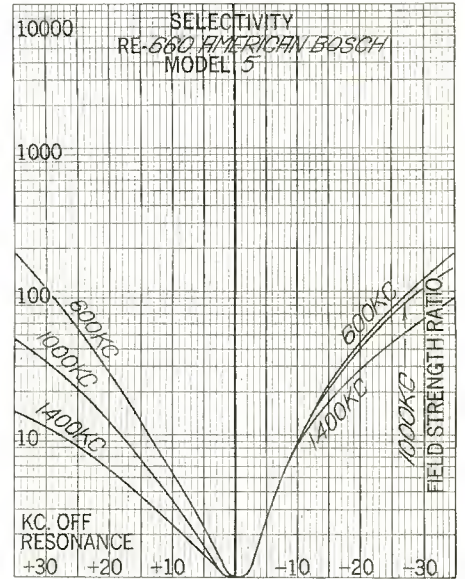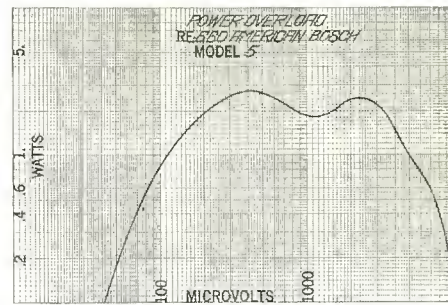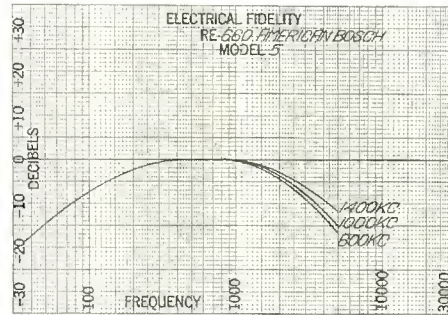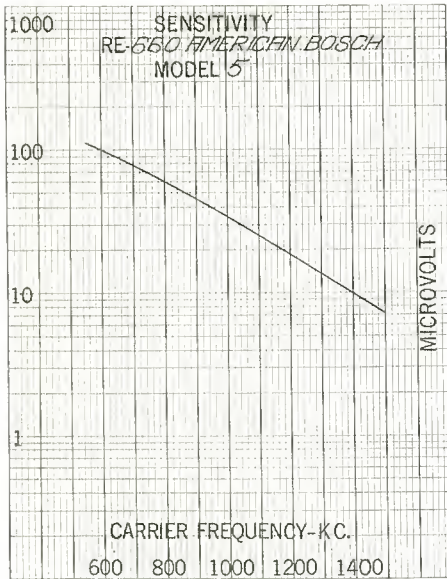Below is a schematic wiring diagram of the Bosch 5. Required tubes for operation are, a 551 first r-f, 551 second r-f, 224 detector, 247 output power pentode, and a 280 rectifier for complete receiver B supply voltages. The only choke employed in the power



single pentode employed in the output stage, while the plate circuit was capacitively coupled to the output measuring tube voltmeter. The voice coil circuit was opened to eliminate any undesirable loading on the primary circuit.


During all tests, the tubes used were those furnished with the chassis, the volume control was turned to its maximum position, and no alterations

cies it is negligible, running about .4%. A power output maximum of 2.3 watts is found from the power overload curve of column 2, but this value does not take into consideration the existing harmonics introduced by the amplifier at this power level. Un-

supply filter is the field of the dynamic speaker which is connected in the high side of the voltage supply.

Band Widths

Times Field Strength	Kilocycles width		
	600 kc.	1000 kc.	1400 kc.
10	24.5	29	39
100	58	79	..
1000
10000

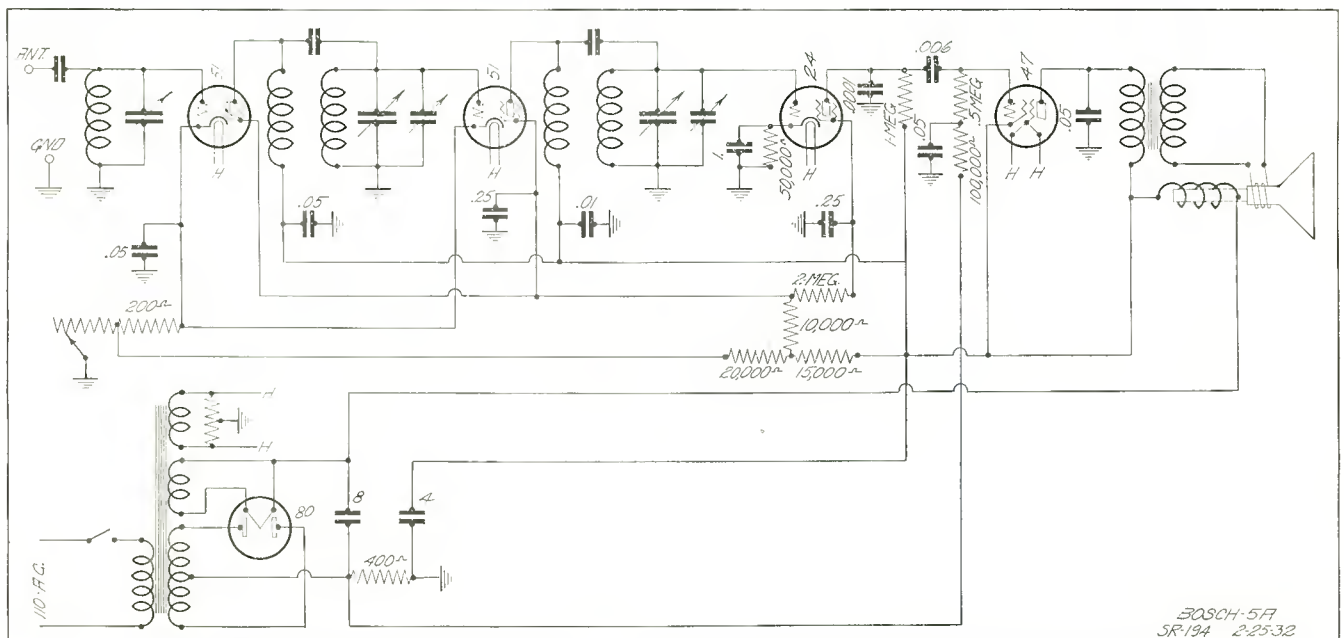

BOSCH-5A
SR-194 2-25-32

Power Amplifier Systems

WEBSTER (RACINE) MODEL 6043-R

At the bottom of this page is the overall response curve of the Webster 6043-R audio power amplifier made by the Webster Electric Company. Measurements were made on it in our laboratory recently.

Overall gain is in the neighborhood of 68 decibels for the amplifier alone, and about 85 decibels when a microphone transformer is used preceding it.

Supplementary features are a B

age supply for a standard two-button carbon type microphone.

An undistorted output of audio power of 15 watts may be had from the output stage of the 250 tubes. Power consumption of the amplifier itself from the a-c line is about 140 watts. Coupling is supplied for 8 ohm and 16 ohm voice coils of dynamic speakers, or any combinations of them to give either or both of these impedance values. The output is sufficient for four or five dynamic speakers or up to twenty-five magnetic speakers, using a suitable matching transformer between them and the amplifier output system.


No volume or tone control is supplied on the amplifier itself, making necessary this auxiliary equipment for proper installation and use. All transformers, chokes and parts mounted on the chassis are covered in two metal cases, the tubes alone being accessible for replacement purposes. A bottom plate prevents any danger from the wiring underneath the chassis. The manufacturer supplies this type of power amplifier for 115 volt, 60 cycle operation, 220 volt, 60 cycle operation, and for 115 volt, 25 cycle operation, the key letters being R, RA, and RZ, respectively.




The upper illustration indicates its small size and compactness, and also that all connections are made on a terminal board at one end of the unit. Two pieces of auxiliary equipment may be had in the CB-713 Control Box and the MC-713 Microphone Coupling Unit. Three stages of amplification are used, a 235 first audio, 227 second audio, push-pull 250 power tubes and two 281 half-wave rectifiers, the latter supplying all high voltages and excitation for one 2500 ohm speaker field. When this is not used, the field is replaced by a suitable resistance-reactance unit described as CR-35 to give the necessary filtration of the B supply voltage.

Since a resistance input system is employed in this power amplifier, the source of input is not required to be of any definite type, and can be either high or low impedance in its characteristics. For maximum output, the signal input is required to be .12 volts of audio voltage, but smaller inputs will satisfactorily operate the unit, though not at maximum output.

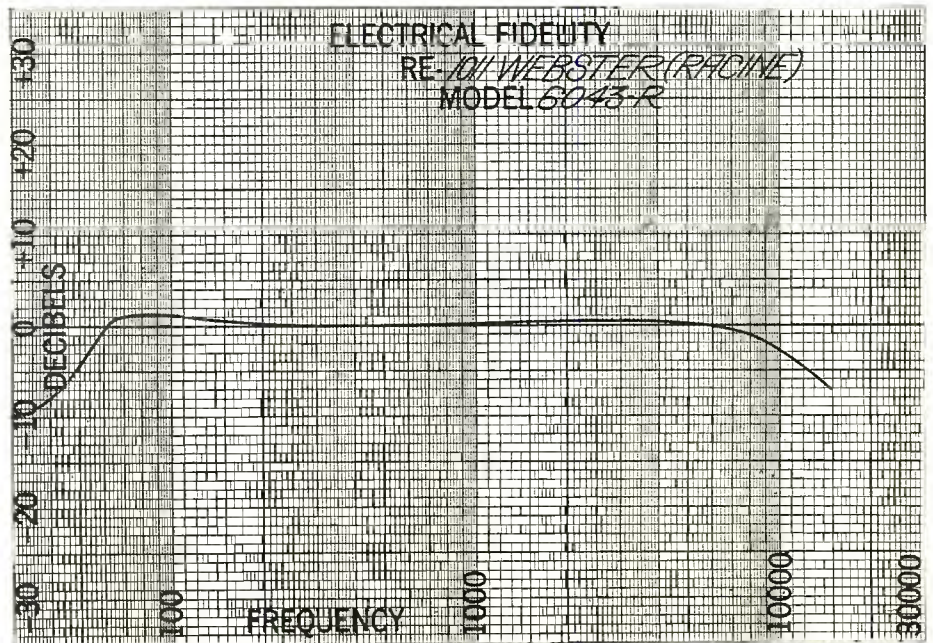voltage supply for a radio tuner and detector unit, but an external filament transformer is necessary since no voltages are supplied for heaters by the amplifier in addition to those for its own tubes. A tap is found on the terminal board for the required volt-



Service and Repair

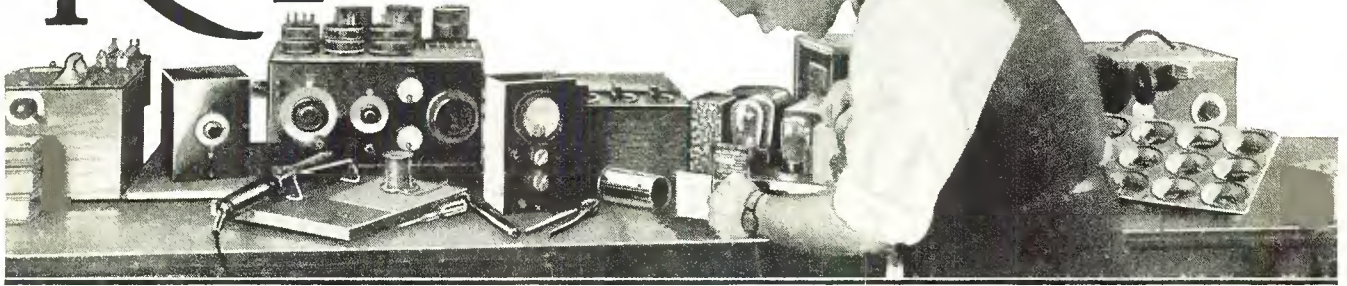

SCHEMATICS PUBLISHED TO DATE

Model	Published	Drawing No.	Model	Published	Drawing No.	Model	Published	Drawing No.
A. C. Dayton			Brunswick			General Electric		
Navigator	November, 1929	SR24	3KRO	November, 1929	SR23	H-32	January, 1932	SR166
Acme Mfg. Co.			15, 22, 32 and 42	November, 1930	SR86	S-22	January, 1932	SR137
AC7	March, 1929	SR3	S14	November, 1930	SR71	K-62	March, 1932	SR168
AC4	March, 1929	SR4	11, 12, 16	October, 1931	SR148	General Motors		
All-American Mohawk			17, 24	December, 1931	SR164	A	November, 1930	SR68
Lyric 90	November, 1930	SR74	E	February, 1932	SR183	120-A	November, 1931	SR116
Lyric 6	March, 1929	SR1	Colonial			S3A	November, 1931	SR154
Lyric 8	March, 1929	SR2	31AC	January, 1930	SR29	S9A	January, 1932	SR173
Lyric J	October, 1931	SR128	33 and 34 a-e	November, 1930	SR95	S-10A	February, 1932	SR179
Lyric B-7	December, 1931	SR165	47-48	December, 1931	SR160	Gilfillan Bros.		
Lyric S-8	January, 1932	SR170	Crosley			100	January, 1930	SR32
Lyric S-6	April, 1932	SR204	Roamio	September, 1930	SR67	Graybar		
Amrad			40S, 41S, 42S, 82S	September, 1930	SR57	600	March, 1930	SR42
70	November, 1929	SR22	608 Gembox	March, 1930	SR41	Grebe		
81	March, 1930	SR44	705 Showbox	March, 1929	SR6	7AC	November, 1929	SR17
84	January, 1931	SR106	Jewelbox 704B	March, 1929	SR5	AH1	November, 1930	SR96
Apex			77	November, 1930	SR83	Gulbransen		
48	November, 1930	SR80	53, 54, 57	January, 1931	SR103	Nine-in-Line	March, 1930	SR40
31 (U. S. Radio)	January, 1931	SR108	120	October, 1931	SR133	161	March, 1931	SR110
10B (U. S. Radio)	March, 1932	SR191	121-1	November, 1931	SR149	10, 13	February, 1932	SR175
7-A (U. S. Radio)	April, 1932	SR189	124	December, 1931	SR150	23	March, 1932	SR186
Atwater-Kent			125	January, 1932	SR174	Hammarlund		
38	January, 1930	SR28	127	March, 1932	SR187	Comet	April, 1932	SR200
55, 55C (Cap.)	September, 1930	SR51	Dayfan			Howard		
55, 55C (Ind.)	September, 1930	SR52	5080	September, 1929	SR11	S. G. A.	September, 1930	SR56
66	March, 1931	SR114	Delco			Green Diamond 8	September, 1929	SR16
H-2	December, 1931	SR131	Auto Radio	September, 1930	SR66	H	October, 1931	SR145
Audiola			Edison			SG-B	November, 1931	SR130
Series 31 (t.r.f.)	November, 1930	SR79	R4, R5, C4	November, 1930	SR49	O	December, 1931	SR163
Super 31	March, 1931	SR111	R6, R7	January, 1931	SR99	AVH	March, 1932	SR177
Junior	March, 1931	SR112	Erla			DL	April, 1932	SR203
13-S7	February, 1932	SR181	Duo Concerto R-2	January, 1930	SR33	Jesse French, Jr.		
Balkeit			Eveready			G	March, 1931	SR118
A	September, 1929	SR12	50	March, 1931	SR50	Kellogg		
Bosch			Fada			523-528	November, 1930	SR77
48	November, 1930	SR73	7AC	September, 1929	SR13	Kennedy		
58	January, 1931	SR109	35-35Z	November, 1930	SR70	20	March, 1930	SR48
60	March, 1931	SR117	KW28-29	December, 1931	SR158	26	November, 1930	SR81
28-29	November, 1929	SR21	Federal			10	January, 1931	SR38
Auto	November, 1930	SR94	H	November, 1929	SR19	30-32	November, 1931	SR129
7DC	November, 1931	SR160	Freed-Eisemann			52	February, 1932	SR184
31	March, 1932	SR198	NR80	November, 1929	SR20	56	March, 1932	SR185
20	April, 1932	SR193	Freshman					
Bremer-Tully			2-N-12	September, 1929	SR14			
7-70	September, 1929	SR10						
81-82	November, 1930	SR75						
881-82	October, 1931	SR126						



Model	Published	Drawing No.	Model	Published	Drawing No.	Model	Published	Drawing No.
King			Silver			Transformer Corp.		
J	January, 1930	SR31	106B	March, 1931	SR113	12-14	November, 1930	SR93
Kolster			108A	October, 1931	SR146	10-11	November, 1931	SR134
K20, K22, K25	September, 1929	SR8	108	November, 1931	SR123	19-20	November, 1931	SR151
and K27	September, 1929	SR8	111	November, 1931	SR155	22	April, 1932	SR201
K21, K23, K24	March, 1930	SR45	Sonora			U. S. Radio		
and K28	March, 1930	SR45	5R	November, 1929	SR25	37	March, 1930	SR39
K-43	November, 1930	SR72	Sparton			26P	October, 1931	SR143
K80	November, 1931	SR159	AC89	September, 1929	SR9	99A	January, 1932	SR171
90, 92	February, 1932	SR182	589	September, 1930	SR63	Universal Auto Radio		
Kylectron			600, 610, 620	March, 1931	SR91	70	April, 1932	SR205
70	November, 1930	SR65	25-26	December, 1931	SR161	Victor		
Majestic			10	February, 1932	SR180	R32, RE45, R52	September, 1930	SR61
70	September, 1929	SR7	15	March, 1932	SR192	R35, R39, RE57	January, 1931	SR101
90B	September, 1930	SR55	Splitdorf			Wells-Gardner		
130-A	November, 1930	SR84	E175	January, 1930	SR36	50 (Areadia)	April, 1932	SR199
50	January, 1931	SR98	Steinitz			Westinghouse		
20	October, 1931	SR124	261	September, 1929	SR15	WR-5	November, 1930	SR92
60	October, 1931	SR138	70, 80, 95	November, 1930	SR76	WR-4	January, 1931	SR107
15	November, 1931	SR157	600, 605, 630, 635	November, 1931	SR132	WR10-12	November, 1931	SR137
25	February, 1932	SR178	Stewart-Warner			WR15	January, 1932	SR168
Philco			950	September, 1930	SR62	Zaney-Gill		
86-82	November, 1929	SR26	Series 900	January, 1930	SR34	54	March, 1931	SR119
95	September, 1930	SR60	R100	January, 1931	SR85	Zenith		
90-90A	November, 1931	SR156	102A	October, 1931	SR147	52, 53, 54, 522,	March, 1930	SR43
112	January, 1932	SR172	R-102A	March, 1932	SR195	532 and 542	March, 1930	SR43
70	April, 1932	SR202	Stromberg-Carlson			71, 72, 73 and 77	November, 1930	SR97
Pilot			846	September, 1930	SR54	A, B, C, D	November, 1931	SR141
148	February, 1932	SR176	635-636	November, 1929	SR18	91, 92	March, 1932	SR190
Radiette								
F14	January, 1931	SR104						
Radiola								
60	January, 1930	SR30						
66	September, 1930	SR64						
44	January, 1931	SR102						
18	October, 1931	SR127						
RCA-Victor								
R-7	October, 1931	SR137						
R50-55	December, 1931	SR166						
R11	January, 1932	SR168						
Scott								
31	December, 1931	A-1						
Sentinel								
11, 12, 15, 16	March, 1931	SR115						

Photronic Cell Experiments

AN alarm which will ring exactly at sunrise on clear days may be easily constructed with the Weston Type 1 Photronic Relay, and provides an interesting and entertaining example of the real usefulness of the Photronic Cell.

Inserted in a UX radio tube socket, the Cell itself should be placed near a window exposed directly to the morning sun unshaded at sunrise by trees or buildings while the relays may be located in any convenient position. The small (plus) prong must be connected to terminal No. 3 of the Miniature Relay and the larger prong goes to terminal No. 1. Studs 2 and 3 should be connected to the coil of the Power Relay in series with a 4½ volt radio "C" battery, as shown in the diagram. All Power Relay terminals can be reached by unscrewing the fiber disc underneath them, and if there is any doubt as to which are

(Continued on page 31)

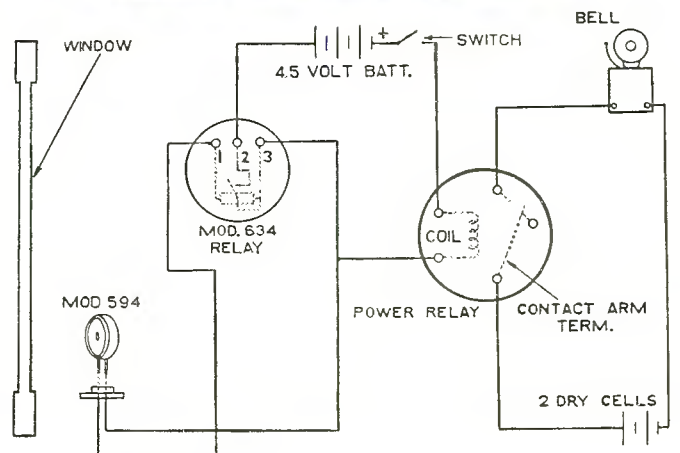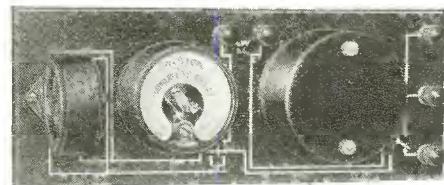

Capacity Decade Box

MANY times, the need for a variable capacity of large value is keenly felt by the experimenter and the service man. With the aim of utmost utility in mind, the author built the instrument described in this article. The effective range is from .05 microfarads to 8.0 microfarads in the steps given in the right-hand column of the schematic layout at the bottom of the page. These steps may be altered by the builder if he feels that other combinations will be of greater value to him in his work.

Uses of Instrument

Need for a capacity decade box, similar to the familiar resistance decade box, is found in any and all power supply filter work, location and elimination of hum, tuning audio chokes, determining the value of bypass and filter capacitors, etc. The usefulness becomes apparent when the builder has such an instrument in his possession. It may also be used for deter-

one condenser is denoted by a single letter, but for clarity in wiring, some are repeated. In designing any piece of apparatus in which a part is used in more than one position, care must be exercised that it is not permanently connected in the circuit through one of the connections. For more combinations, either the number of switch arms or the number of condensers must be increased.

The switch shown in part in figure 2 was built up with four independent arms and nineteen switch points for each arm. Outside of the tediousness of inserting and connecting so many points (some are blank as seen on the diagram), no difficulty should be experienced. They are mounted on a circular piece of bakelite between 4½ and 5 inches in diameter. The contact arms are of spring brass so that the desired electrical contact will always be well made. Stops are mounted at the ends of the arc to limit the revolution of the dial.

Either they may be picked from a quantity and measured, or, at greater expense, they may be purchased with

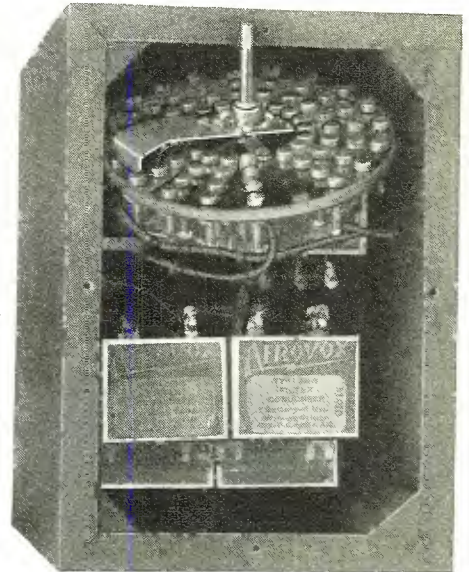


Figure 2

Figure 1 shows the external appearance of the unit, with the two binding posts for circuit connections, and the small dial upon which are the capacity values for each of the nineteen settings. If precision work is to be done with this instrument, the condensers employed must be accurate in value.

tolerances which are far better than the ordinary production runs.

The panel measures approximately 5 x 7 inches and the box is about 6 inches in height.


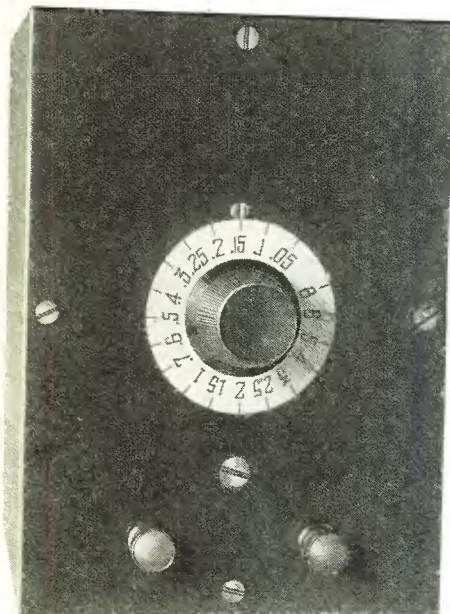


Figure 1

mining open bypass condensers in a receiver, allowing checks with the specified value of condenser without having a dozen different values on hand, scattered all over the work bench.

Constructional Details

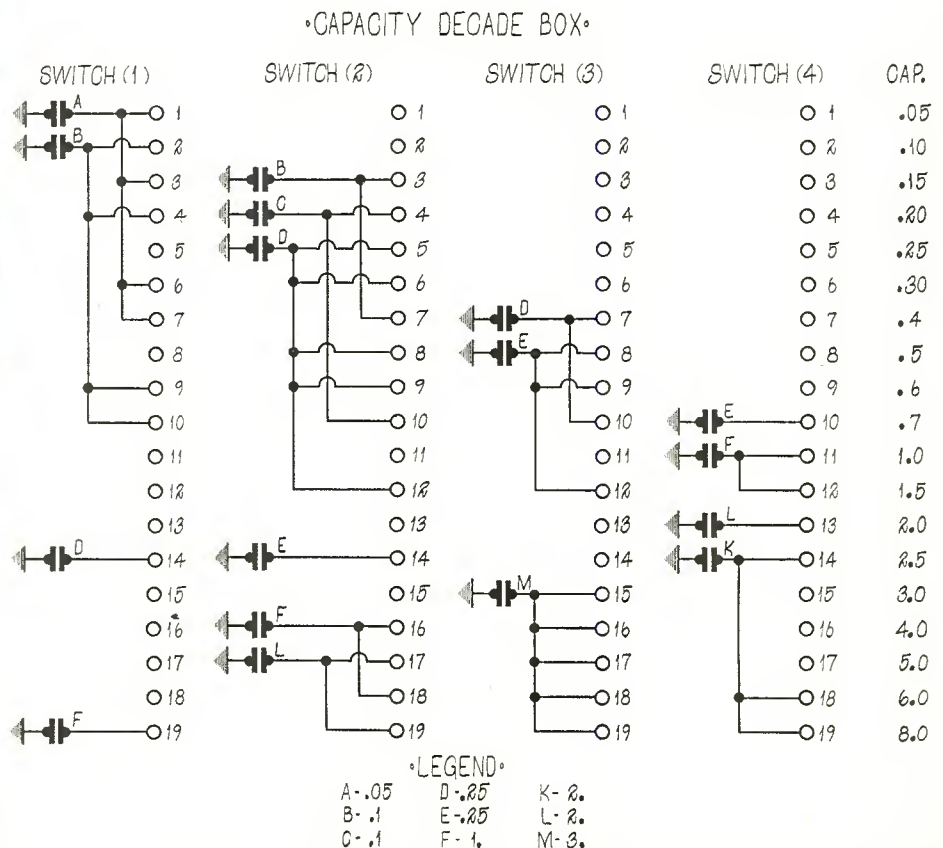
Aerovox condensers of at least 600 volts d-c rating were used in the building. In the legend at the bottom of the diagram are the required capacity values. It will be noted in the circuit layout that some seem to be duplicated, but this is not the case. Only



Set Tester

WE present on this page the set tester which was promised our readers some time ago. Space prevented us from giving it before this issue. The three illustrations give clearly all of the constructional details as well as the schematic wiring diagram. The author submitted the following details as to operation:

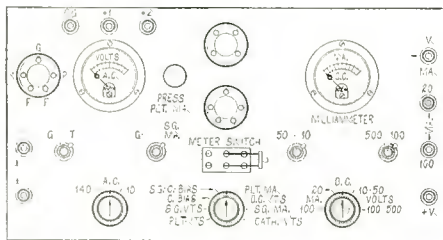Tube, when taken from the receiver is placed in the proper socket of the tester, and the cable plug is inserted in the tester and receiver sockets, using the Control Grid Tip Jack when testing screen-grid tubes.



Read A-C Volts—Adjust sw2 to 10 and read a-e meter. In this test a special plug is useful, made with two leads with phone tips soldered to them for house line voltage tests, using the tip jacks at the left of the meter, putting sw2 to 140.

Read Plate Volts—Set sw1 to plate volts as marked. Also sw6 or sw7 to proper voltage indication. Set sw3 to proper volts and read. In reference to the double scales of the 20-100 milliammeter readings, the voltages are read as follows: all 10 volts or less on 20 scale divided by 2; all 500 volts or less on 100 scale multiplied by 5; all 100 volts or less on 20 scale multiplied by 5.

Read Plate Ma—After plate voltage reading turn sw1 to Plate Ma and sw3 to 20 or 100 Ma as necessary. Press sw8 for direct reading on scale selected.

Emission Test—Swing sw4 to T while pressing sw8 and take Ma reading. In this reference, new tubes can be tested and notes made for comparisons.

Read Screen Volts—Same method as for plate volts except that sw1 is set to SG volts.

Read Screen Current—Same method as for plate ma except that sw8 is not used, and sw5 is turned to SG ma.

Read Bias—Set sw1, sw3, sw6 or sw7 to proper position and read meter.

Read D-C Filament Volts—Set sw1, sw3, and sw6 to proper place and read.

Read SG Control Grid Volts—Lead from cap of tube in tester is inserted in Tip Jack 1. Set sw1, sw3 and sw6 to proper position and read meter.

Emission Test for SG Tubes—After plate ma reading remove lead from Tip Jack 1 and insert this lead in Tip Jack 2 while pressing sw8 and read.



Read Cathode Volts—Set sw1, sw3, sw6 or sw7 to proper position and read.

Test Rectifiers—Separate plates can be tested by applying plate and screen grid voltage methods alternately.

Test Pentodes—By use of the two pentode adapters at the tester, one for the input and the other for the tube, all tests are made similar to those for the screen grid tube. The wire extending from the side of the adapters is inserted in the tip jacks, while that from the input adapter is inserted in the Tip Jack CG. Also the one from the tube adapter is put in Tip Jack 1.

Switch 9 is a double-pole, double-throw type for reversing the meter when such is required. After each reading, all switches should be turned to their off positions.


For cable, about four feet of six wire cable was used. The adapters and plugs were made up from old sockets and old tube bases. The end of the cable to be inserted in the receiver was connected to a plug with five pins, the sixth wire being fastened to the side of the plug to make control grid connection at the receiver while at the tester end of the cable the sixth wire extended from the side of the plug with a phone tip soldered to it for the Tip Jack CG. One 5 to 4 adapter and two pentode adapters will be necessary, the constructional details of which are given in the illustrations.

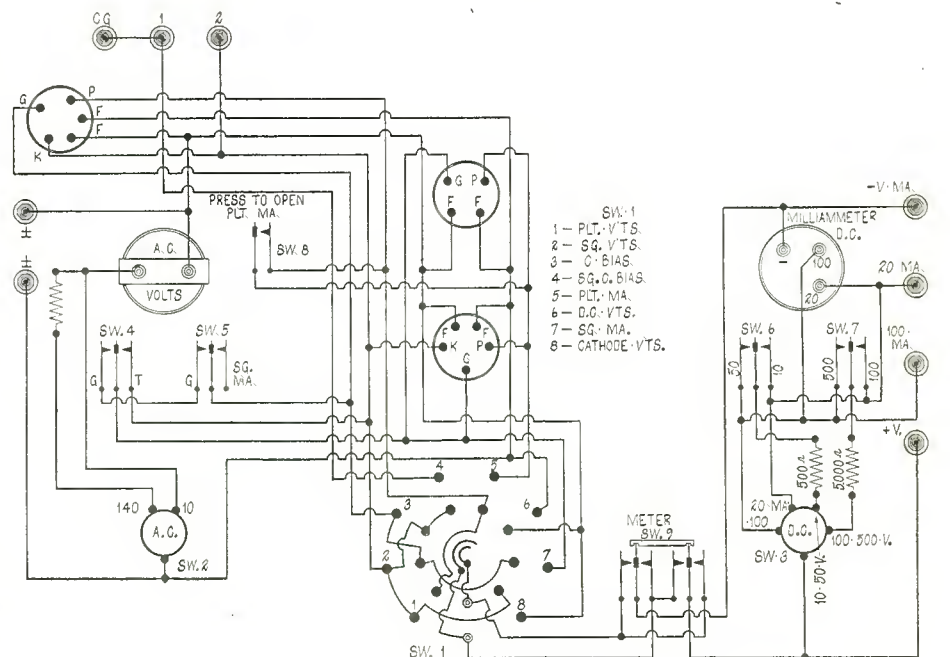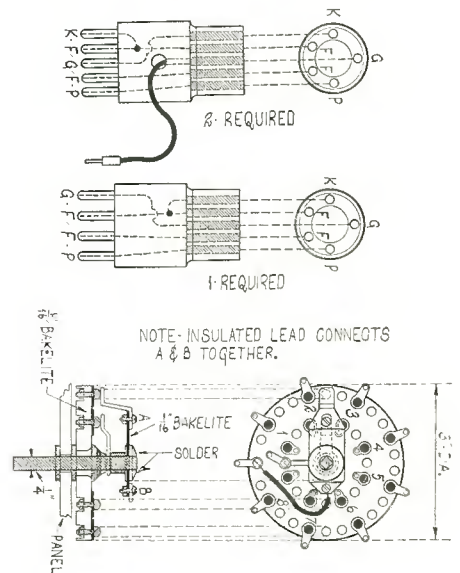

(Continued from page 34)

ing. Mounting supports are fastened to each end of the long coil and a bracket is riveted to the short coil so that it can be slid along the 1 1/4 in. tube by means of a knob which extends through a slot in the front panel.

The output resistor is the most critical part of the circuit. It must be as near non-inductive as possible and its r.f. resistance must be exactly equal to its d.c. resistance. Otherwise, the accuracy of the whole device is spoiled. The resistor is made in two parts (see Fig. 3). The small part has a resistance of 1.41 ohms and the other part 12.73 ohms. The wire is .003 in. Nichrome or Chromel which has a re-

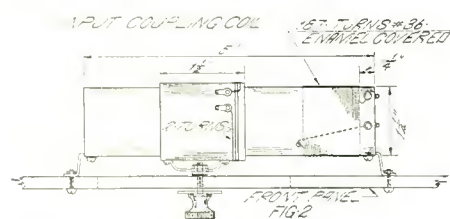

sistance of about 73 ohms per foot. The base is made of 3/8 in. bakelite. The clamps are made of 3/32 in. brass with the corners well smoothed down to prevent cutting the wire.


It is best to use an accurate resistance bridge when setting the clamps but if this is impossible they may be adjusted for the proper resistance by the voltmeter-ammeter method. Pass exactly .3 amperes through the entire wire by placing an eight volt battery, a 0.1 or 0.5 ammeter and a 10 ohm rheostat in series with it. Screw down the clamp which connects to the GND binding post and connect an accurate low reading high resistance voltmeter between the posts marked GND and X7. Adjust the middle clamp until the voltmeter reads .42 volts. Next connect the voltmeter between the GND and X10 posts and adjust the top clamp until the reading is 4.23 volts. Be sure the clamps are secure but not tight enough to damage the wire.

The rest of the circuit is exceedingly simple. The six volt heater battery for the 236 tube also supplies the grid bias. Four dry cells are probably more satisfactory than a storage battery for the ordinary amount of use that such a piece of equipment receives. The "B" battery drain is exceedingly light so the smallest type of batteries is all that will be needed. The 10 ohm and 1000 ohm rheostats are for adjusting the bucking current through the micrometer. The small rheostat acts as a vernier for the larger one. The 1 1/2 volt bucking battery is a single dry cell. The switch in the micrometer circuit is provided so that when the generator is not in

use this circuit can be opened to stop the flow of current backward through the micrometer.

There are two accessories required for use with the signal generator. These are the dummy antenna and the output meter. The output meter should be purchased and must be calibrated in such a manner that it will indicate when 50 milliwatts are being delivered in the output circuit. If it includes a load resistor, this should be variable in order to operate with the different types of output circuits and tubes in different sets.


The dummy antenna can easily be made. It consists of inductance capacity and resistance in series. (See Fig. 4.) The inductance is made by space winding 28 turns of No. 30 wire on a 1 1/4 in. tube so that it covers approximately 1 in. The capacity is a .00025 mfd. fixed mica condenser, and the resistance is 3 1/4 in. of the same resistance wire as used to make the output resistor. In use, the dummy antenna is connected between the aerial binding post of the receiver under test and either of the output terminals of the signal generator. The ground terminal of the output resistor is connected to the ground terminal of the set.

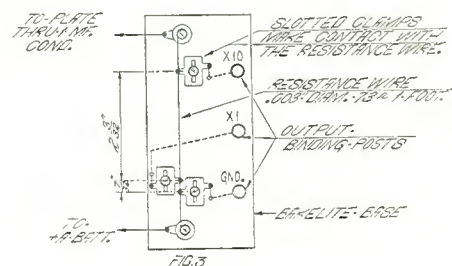

Operation

After the whole assembly has been properly mounted and all connections made, the operation is as follows. Close both the A battery and the micrometer circuit switches and when the tube has come up to heat adjust the bucking battery rheostats until the micrometer reads zero current. It may be necessary to try two or three different tubes in order to find one which holds its zero adjustment well. In case it is impossible to bring the reading to zero, it will be necessary to change the value of the protective resistance either one way or the other. Next turn on the modulated oscillator and adjust it to the proper frequency. This will be just half of whatever frequency is to be delivered by the generator tube. Move the sliding coil to about 3/4 in. from the stationary winding and tune the input of the generator tube until the micrometer shows maximum deflection. Then the sliding coil can be moved until the output meter on the receiver under test indicates fifty milliwatts. If the dummy

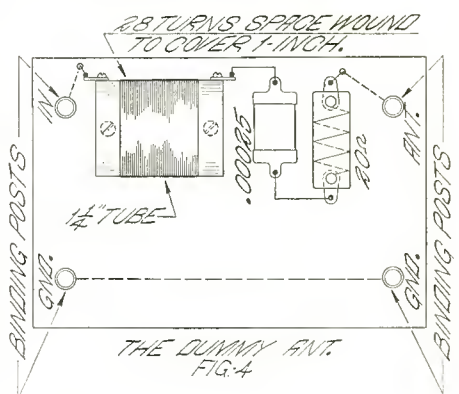antenna is connected across the whole resistance, the reading of the micrometer must be multiplied by 10 to give the output of the generator or the receiver sensitivity, but if it is connected across the 1.41 ohm portion only, the micrometer will indicate microvolts sensitivity directly.




The output range is from 1 to 1000 microvolts, which is sufficient to measure the sensitivity of most any receiver. The only precautions in using this device are to be sure that the receiver under test is tuned to twice the frequency of the modulated oscillator which drives the generator, and that the input circuit of the generator tube is tuned exactly to the oscillator. This last precaution is necessary in order to filter out whatever second harmonic is produced in the oscillator tube itself.

Photronic Cell Experiments

(Continued from page 31)

right until the little arm makes firm contact with the point. If connections have been made correctly the bell will ring. When the hand or some other object is placed in front of the Cell, the contact should open and silence the bell. If the results are not perfect after the first trial, further adjustment should be made until satisfactory operation has been obtained. A distinct click from the Power Relay indicates that all of the connections from the Cell to the coil are correct. If this click is heard and the bell fails to ring, the fault lies somewhere between the Power Relay output and the bell itself. For shutting off the apparatus when not in use a switch may be provided in the "C" battery circuit or else a box or hood may be placed over the Photronic Cell to exclude the light.

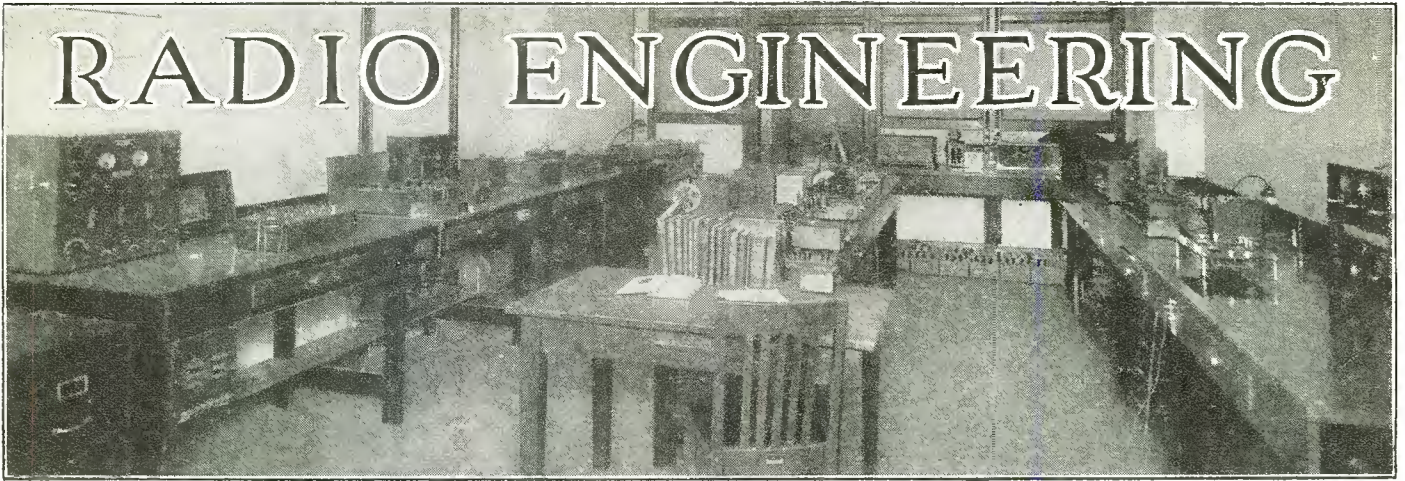After sunset, the device should be placed in readiness with the Cell at the window facing East, and in the morning, when the first rays of the sun appear, the alarm will ring and will continue until it is shut off by hand.



RADIO ENGINEERING

Filter Design by Graphs

PART I'

AS a matter of fact, this situation calls attention to a very important property of the graph. Suppose we have a series inductance capacity combination, and we wish to find its reactance at some frequency other than the frequency of resonance. We follow the line representing the frequency level in which we are interested to the points where it crosses the particular inductance and capacity lines involved, and note the reactance level of each crossing. Then we have only to subtract the lower reactance level from the higher one to obtain the expression for reactance.

Let us assume that we have an inductance of 300 millihenrys in series with a capacity of .04Mfd. and we want to know the total reactance at 2,000 cycles. For one thing, we see immediately that the frequency of resonance of this combination is approximately 1,440 cycles, because it is at this frequency level that the line marked .04Mfd. crosses the 300Mh. line. However, we are at present interested in reactance at 2,000 cycles, so we go to that level and up to where it crosses the .04Mfd. line. This is at a reactance level of nearly 2,000 ohms. If we continue upward to where the 2,000-cycle level crosses the 300Mh. line we are at a point on the reactance level of 3,770 ohms. Subtracting the 2,000 ohms just mentioned from 3,770 ohms, we have 1,770 ohms, the total reactance. The highest reactance (3,770 ohms) was inductive, and thus we say that the 1,770 ohms has an inductive reactance predominance. This is mentioned because the reactance of this same coil-condenser combination at 1,060 cycles is also 3,770 minus 2,000 or 1,700 ohms, the difference

(Continued on next page)

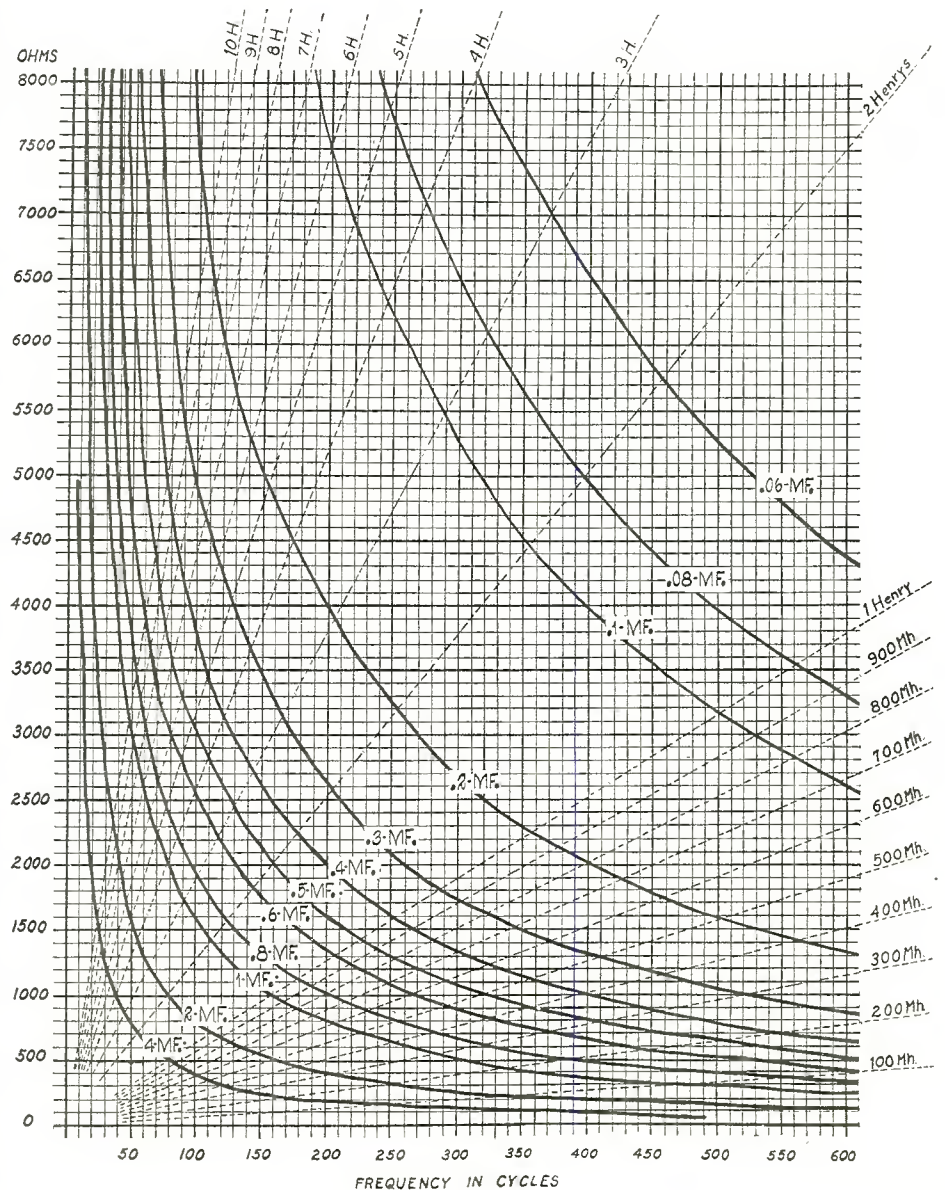


Figure 3.

(Continued from page 36)

being that at 1,060 cycles capacity reactance predominates. For any combination on the graph it is safe to say that reactance differences measured on the left side of the resonance intersection are capacity reactances, while those on the right are predominantly inductive reactances.

So far we have only considered series connections of coil and condenser, and the resonance thereby effected. Had connections been made in parallel as in Figure 2b, the frequency which would have been the resonant frequency in a series connection is now the anti-resonant frequency. Whereas the reactance of a series connection would have been zero at this frequency, it becomes infinity (infinitely large) with a parallel connection. Perhaps we might wish to know what the total reactance (between A and B in Figure 2b) would be, at any given frequency, for the parallel arrangement. Unfortunately the writer is unable to offer any suggestion of how this may be read directly from the graph, but the answer may be obtained quite speedily by using the graph in conjunction with a simple arithmetical operation.

It is first necessary to obtain from the graph the reactance which the combination would have had if the units were connected in series. Then we must note the rating of the inductance in henrys and the value of the capacity in farads. If we denote the inductance by L (as is the common practice) and the capacity by C, and finally refer to the parallel reactance as X_p , and the reactance which the combination would have had at this frequency if it were in series as X_s , then

$$X_p = \frac{L}{C X_s}$$

Of course most of us would much prefer to express the value of the capacity in microfarads. Since there are 1,000,000 microfarads to one farad, we need only to multiply the above formula by 1,000,000 to get


$$X_p = \frac{1,000,000 L}{C X_s}$$

where c is the capacity in microfarads.

In Figure 3 we have a graph which may, at first, seem identical with Figure 1. It has a lower frequency range, however, and is presented for the benefit of those who may be interested in designing low frequency filters for the suppression of "power hum," etc. In principle it is quite the same as Figure 1, and consequently needs very little further description. However,

by way of summary, and also to give additional facility in the use of the graph, let us assume that we need to design a filter for the suppression of power hum from a 60-cycle full wave rectifier.

Figure 4 is a suggestion of the possible arrangement of the reactance units. Since we are dealing with a 60-cycle source of power, we shall probably find that the most serious power ripple is either at 60 cycles or its first harmonic, 120 cycles. Of the two, the latter is frequently the most distressing, since it is a high enough frequency to be distinctly audible, and is present in many rectifiers to a very large degree. If, in Figure 4, we were to choose the units of the series combinations A and C so that their frequency of resonance was 60 cycles, it would produce the desired effect of

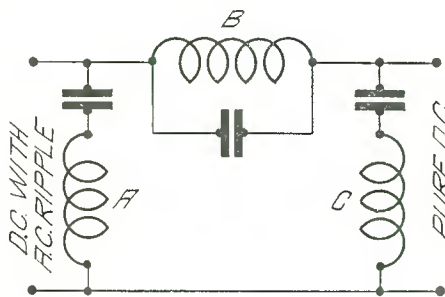

shunting out the 60-cycle ripple before it could reach the pure D.C. terminals. Then, if we made the anti-resonant circuit B anti-resonant at 120 cycles, it would effectively bar the passage of this frequency by reason of its infinitely high reactance.

Turning to Figure 3 and reading upward along the 60-cycle line we find that the 2 Henry line crosses the 4Mfd. at 56 cycles, also that the 7 and 8 Henry lines cross the 1Mfd. and .8Mfd. lines, respectively, at 60 cycles. Of these combinations, it would probably be best to choose the first, in spite of the fact that its resonant frequency is 56 instead of 60 cycles. One reason for this choice is that it is easier to obtain these rated values of inductance and capacity than the others. Another much more important reason is that we should like, as far as possible, to shunt out 120 cycles through A and C, and the graph shows that at 120 cycles the reactance of the first combination is only 1,505 minus 318, or 1,187 ohms, whereas, with the combination of 7 Henrys and 1Mfd., for instance, the reactance at 120 cycles would be 5,300 minus 1,320, or 3,980 ohms.

In constructing the anti-resonant circuit B, we follow the 120-cycle line and find that it marks the crossing of the 2Mfd. line with 900 millihenrys. If this combination were put in series, its reactance at 120 cycles would be zero, but since we put it in parallel,

its reactance is theoretically infinite. It is to be hoped that it also offers a high reactance at 60 cycles. Let us see if it does.

Here we need to recall our little formula for the reactance of an anti-resonant circuit, namely,

$$X_p = \frac{L}{1,000,000 C X_s}$$

First desiring to find X_s , we look at the 60-cycle line and find that the total reactance of the series combination of 900 millihenrys with 2 microfarads is 1,300 minus 340, or 960 ohms. This is the value of X_s . Now, the value of L is 900 millihenrys or .9 Henrys, and the value of c is 2

microfarads, so the ratio $\frac{L}{c}$ is $\frac{.9}{2}$

.45. Forty-five hundredths of one million is 450,000, and, if we divide 450,000 by X_s , that is, 960 (ohms), we obtain the desired reactance figure, 468.7 ohms.

In the light of the figures we have just compiled, we are enabled to estimate the effectiveness of the filter we have designed. In Figure 4, the series combination A and C are now each made up of a 4 microfarad condenser and a 2 Henry choke coil. In the anti-resonant circuit B, we have a 2 microfarad condenser and 900 millihenrys inductance. If a 120-cycle ripple started through the system, it must immediately take the choice of passing through A (which we found had a reactance of 1,187 ohms at 120 cycles), or through B, which has infinite reactance. If we rate the reactance of B more conservatively, say at 1,000,000 ohms, the 120-cycle current still has nearly 900 times the chance of shunting itself out through the much lower reactance A. If we consider a 60-cycle current at the same point, we find that the reactance of A is 90 ohms, while the reactance of B was given 468.7 ohms. Here the 60-cycle current has more than five times as much opportunity to shunt itself out through A as to pass through B. And, finally, if small currents of either frequency do manage to pass through B, we still have the shunt circuit C to operate on them.

If it is possible that this presentation of certain aspects of resonance by graphical means has been valuable, or even interesting, to the reader, he may regret that the limits were not extended to radio frequency. This might very well have been done, howbeit with a certain sacrifice of accuracy, since the very thickness of a line might represent hundreds of cycles, or ohms, as the case may be. Any reader who desires to modify the graph to fit the

(Continued on page 40)

Speech Input Equipment

(Continued from page 17)

source and the load when incorporated in the circuit shown, and this relationship holds regardless of the volume control setting. Each volume control is associated with a cam switch which can be thrown to either of two input circuits or "OFF." The input circuits may lead to a number of microphones which can be operated simultaneously in any desired proportion, or alternative sources can be thrown in and out of circuit with previously determined correct settings on the individual pickup channels. The provision of the master control makes it possible to compensate for unwanted changes in the combined output level without disturbing the adjustments of the individual channel controls. Fading between two channels is easily accomplished by reducing volume on one channel and simultaneously increasing volume on another. Mixing circuits of this type are in use in practically all broadcast control rooms, and in public address and other sound systems as well. Figures 4 and 5 are front and back-of-panel views of such a mixing panel.

Still another type of input control panel is illustrated in Fig. 6. With the mixing panel described above, it is evident that the volume controls must be set to reduce the outputs of all sources to approximately the level of the "weakest." The amount of gain required of the main amplifier (the studio or line amplifier in broadcast work) is thus determined by the "weak" source. The input control panel of Fig. 6 is fundamentally a two-channel mixer without master control in which a self-contained single-stage amplifier has been introduced ahead of the microphone volume control. The other volume control may be switched to either of two other pickup devices, such as a radio detector output or phonograph pickup. "OFF" positions are provided for these switches so that it is possible to cut out any circuit without disturbing the volume control setting. Mixing between channels is accomplished as in the orthodox unit described above.

While the amplifier-mixer unit is not as flexible as the straight mixer, it may be applied in conjunction with main amplifiers having approximately 20 decibels less gain—a feature which adapts the panel to many already existing sound installations with insufficient gain for microphone operation. The meter on the front panel indicates the filament current of the amplifier tube, but can be thrown into the microphone circuit by means of a push-button switch.

841 Operating Characteristics

Operating Conditions—Class B Service

Maximum Operating Plate Voltage.....	450	Volts
Maximum D-C Plate Current (Unmodulated)...	50	Milliamperes
Maximum Plate Dissipation.....	15	Watts
Maximum R-F Grid Current.....	5	Amperes

Typical Operation:

Filament Voltage (D.C.).....	7.5	7.5	Volts
Plate Voltage	350	450	Volts
Grid Voltage (Approx.)¶.....	-5	-8	Volts
D-C Plate Current (Unmodulated).....	43	36	Milliamperes
Peak Power Output.....	12	16	Watts
Carrier Output, Modulation Factor 1.0... 3		4	Watts

Operating Conditions—Class C Service

Maximum Operating Plate Voltage			
Modulated (D.C.)	350	Volts	
Unmodulated (D.C.)	450	Volts	
A-C (R.M.S.)	450	Volts	
Maximum D-C Plate Current.....	60	Milliamperes	
Maximum Plate Dissipation.....	15	Watts	
Maximum D-C Grid Current.....	20	Milliamperes	
Maximum R-F Grid Current.....	5	Amperes	

Typical Operation:

Filament Voltage (D.C.).....	7.5	7.5	7.5	Volts
Plate Voltage	250	350	450	Volts
Grid Voltage (Approx.)¶.....	-20	-25	-30	Volts

Power Output	6	10	13	Watts
--------------------	---	----	----	-------

NOTE: If grid bias is obtained by means of a grid leak, its value should be about 5,000 ohms. This value is not critical and correct circuit adjustment may be obtained with considerably different values.

¶ Grid voltage is given with respect to negative end of d-c operated filament; if the filament is a-c operated, the given values of grid voltage should be increased by 3.75 volts.

SPEED TELEVISION LAMP

This SPEED Television Lamp differs from those formerly available in that it is of the Wall-Electrode type. This construction offers marked advantages including improved efficiency and greatly increased high frequency response.

The Wall-Electrode tube may be operated directly in the plate circuit of a '71A tube. It is not however, recommended for use with the '45 or '47 except where the plate current is limited to 20 m.a. With the '47 Pentode, a series resistance should be used.

Ignition Potential (approx.).....	100	volts
Ignition Current (approx.).....	0.5	m. a.
D.C. Resistance at .020 Amp. of the order of 6000 ohms.		
Recommended Operating Current.....	10	m. a.
Power necessary for complete modulation of light values, 140 milliwatts.		
Optional Operating Current	20	m. a.
Power necessary for complete modulation of light values, 500 milliwatts.		

RCA-864 and CX-864

RATING AND CHARACTERISTICS

Filament Voltage	1.1	Volts D.C.
Filament Current	0.25	Ampere
Plate Voltage	135	Volts Maximum
Grid Voltage	-9	Volts
Typical Operation and Characteristics:		
Filament Voltage	1.1	Volts D.C.
Plate Voltage	90	Volts
Grid Voltage	-4.5	Volts
Plate Current	2.9	Milliamperes
Amplification Factor	8.2	
Plate Resistance	13500	Ohms
Mutual Conductance (Grid-Plate Transconductance)	610	Microhms
Approximate Direct Interelectrode Capacities:		
Plate to Grid	2.3	uuf.
Grid to Filament	5.4	uuf.
Plate to Filament	3.5	uuf.

Status of Television

FOLLOWING its policy to advise the public accurately regarding the progress of experiments in developing television, an authoritative statement was issued today by the Radio Manufacturers Association, the national industry organization. A similar statement was made about a year ago and the new statement, emphasizing that many engineering problems must be overcome before television can be a satisfactory means of home entertainment, was prepared by the Association's Engineering Division which includes all prominent engineers working toward development of television broadcasting and receiving apparatus. The statement follows:

"From such a confused mass of conflicting statements and data regarding Television, only by picking out the pertinent facts from the work that has been done in the past and the facts that are presented in the present situation, is it possible to draw any conclusions regarding the future of Television. These facts have been so many times oversold, at times maligned and altogether misunderstood, not only by the public but by the leaders of the radio industry itself, which must sponsor this new art.

"This statement regarding Television is only intended to array the facts of the past and present to point out some of the future possibilities thus made apparent.

"As far back as 1884 there was recognized by Nipkow, a German experimenter, that to transmit visual images it would be necessary to resolve those images into elements, each element to be faithfully transmitted and re-converted into a corresponding light value at the receiving end. To do this Nipkow employed scanning discs, and later in 1894 Amstutz, an Illinois experimenter, carried on the work in this country even further. In 1913 Jenkins of Washington started his work on the development of Television which culminated in 1925 in the showing of animated motion pictures by Television. In England, John Baird, after several years of work, showed his first pictures in 1926. In 1928 the Bell Telephone Laboratories transmitted a picture from Washington to New York, and since that time several other experimenters have been carrying forward the development of Television. Prominent among these have been the RCA Victor Company in Camden, the Jenkins Television Corporation of Passaic, Philo Farnsworth now with the Philadelphia Storage

Battery Company, General Electric Laboratories in Schenectady, and U. A. Sanabria of Chicago.

"The problems encountered in accomplishing Television transmission and reception have in the past been manifold.

"First—the problem in the method of scanning which started with the ordinary disc, was followed later by a disc with lenses which greatly increased the efficiency. Then came the drums and discs with mirrors. Starting with a Russian named Rosing, twenty years ago, several experimenters have been using electrical principles of scanning which are utilized in the cathode ray oscillograph tube.

"Second—the problem of transmission has proven to be very difficult. The light values of the elements of the transmitted picture must be converted to electrical values and then transmitted faithfully either by wire or by radio. This is only successfully accomplished by employing a frequency side band of several hundred thousand cycles. This becomes of interest when compared with the width of a side band for present day radio voice transmission which is approximately 5000 cycles. Modulation of the high carrier frequencies for these picture transmissions becomes very difficult.

"Third—the reception of Television signals has presented still more complicated problems. The radio Television signals must be received, amplified, de-modulated and again amplified to operate a light source. Demodulation above 30,000 cycles has presented many engineering difficulties. Much work has been done on the light sources, the most common of which have been the neon discharge glow lamp, the Kerr cell and the cathode ray tube.

"Fourth—the great problem has been that of securing finances. Unfortunately, companies have resorted to overstatements, lured prospects with the possibilities of Television in order to sell stock, and often in these statements misrepresentations were made, with the result that the public has been very much confused as to the actual state and present possibilities of the Television art.

"It was early recognized that in this maze of Television work some official organization, representing most of the Television experimenters, should endeavor to crystallize as much as possible the growing embryonic art. Consequently, in 1928 a sub-committee of the Engineering Division of the

R.M.A., known as the Committee on Television, under the direction of D. E. Repogle as Chairman, was appointed. This committee not only embraces members of the R.M.A., but invites as Guest Members every outstanding experimenter. It has helped in encouraging experimenters along every line of development and in securing Federal aid in the wave length assignment of Television, and has been the only official recommended party in this country whose function has been to guide, if possible, this growing art. Due to the work of this committee, much confusion in regard to practices, terms and definitions of Television have been eliminated.

"The present facts of Television which are available are as follows:

"First—for scanning, mechanical features using rotating parts are in wide use and offer a most practical means of securing passable Television pictures.

"Second—a direct pick-up system which has come to the front rapidly this year is that of the camera idea. This system can be used for Television pick-up in a lighted studio, for outdoor pick-up, etc.

"Third—a great deal of successful development has been made with the cathode ray tube system for transmission and reception. This system has proven technically sound and shows the greatest possibility. Its chief difficulties are in the production of large quantities of these systems at a reasonable cost.

"Fourth—the Television broadcast transmission spectrum allows only for five channels, namely 2000-2100 kc, 2100-2200 kc, 2200-2300 kc, 2750-2850 kc, and 2850-2950 kc. This frequency spectrum for Television is not adequate for good picture transmission on account of the very wide side band frequency necessary for picture detail, so in addition to these bands, on the extreme short waves—5-7 meters, frequencies from 35000-80000 kc have been requested for Television service. Most of the present transmitters are operating in the first mentioned bands, but a few operate in the neighborhood of 46000 to 48000 kc.

"Fifth—the reception of Television has been possible by tuning with either a superheterodyne or tuned radio frequency receiver designed for Television reception. Synchronized sound very often accompanies the picture transmission and it is common practice to receive the voice transmission on the standard broadcast receiver.

(Continued on page 40)

Status of Television

(Continued from page 39)

This required two receivers for receiving synchronized sound and picture transmission. In the Television receivers, mechanical scanning and cathode ray electrical scanning have been employed. The cathode ray type of scanning has been capable of excellent results and shows great possibilities for further development.

"Sixth—with the present economics of broadcasting, it has been impossible to secure much data on the entertaining value of the subjects that can be broadcast due to the cost in presenting programs. The Federal Radio Commission has up to the present time considered Television only experimental and will grant no commercial rights. This means that all broadcasting must be done for the experimental value only and no paid programs can be transmitted by Television. This ruling has made impossible the receipt of any money in staging Television programs. With commercial rights granted by the Federal Government, the problem will still be complicated as to whether advertisers will continue to assume the increased costs that Television must impose for its successful operation, or whether the public can satisfactorily be taxed to bear this burden.

"Many problems appear which must be overcome before Television can be a satisfactory means of home entertainment. The most important of these are listed as follows:

- "1. Greater detail should be obtained in received picture.
- "2. Television transmission pick-up equipment should be portable and as easily used as present day sound picture pick-up equipment.
- "3. Transmitting systems must be evolved which will have a satisfactory and reliable service range.
- "4. Receivers as simple in operation as our present radio receivers must be designed and built at a reasonable cost.
- "5. Quiet and satisfactory illuminated picture equipment for the home must be designed and built at a reasonable cost.

"Regardless of the present problems that confront the industry, there has been enough work done to justify some predictions which can be conscientiously made. With the development of the new short wave channels at frequencies higher than 35,000,000 cycles, reliable transmission of Television can be predicted. Ample room for an adequate number of transmitting stations can be visualized in this short wave region. It is perfectly conceivable that a sight and sound service can be worked out to be received on a single receiver with a simplified tuning and control mechanism.

"As never before, the new art of Television is going to require the rigid and sure hand of a governing body to set up the standards for both transmission and reception. Surely no better body is suited for this task than the Radio Manufacturers Association, which embraces both transmitting and

receiving set manufacturers. Because of this situation, Television presents a real challenge to the R.M.A., which if accepted, can and will bring new prosperity to its members but only if this challenge is correctly and courageously met by the entire co-operation of its members."

Filter Design by Graphs

(Continued from page 37)

requirements of a limited radio frequency band will find that this may be done quite satisfactorily in the first graph (Figure 1). Here we have only to multiply the frequency range by 100, and divide both the inductance and capacity values by 100. The scale of ohms reactance is left precisely where it is. Now the graph has a frequency range of zero to 600,000 cycles. In the inductance scale, the broken line now marked 10 millihenrys becomes one-tenth of a millihenry; the 1 Henry line becomes 10 millihenrys, with proportionate changes in the other inductance values. In the heavy capacity lines, the line marked .1 Mfd.

becomes .001 Mfd.; the .02 Mfd. capacity becomes .0002 Mfd., all other capacity values changing in the same proportion. As has been said before, the reactance range still remains between zero and 8,000 ohms.

It is probably true that the subject of resonance by the graph has not, in the past, been exploited very extensively, if at all, and since it is quite improbable that the writer should have discovered all of the possible uses of the graph, the reader is strongly urged to look over the graph with a view to finding its applications to his own particular problems. It is hoped that with this graph, or some subsequent development of it, many routine problems may be brought to a solution quickly and profitably.

RCA RADIOTRON COMPANY, INC., and E. T. Cunningham, Inc., have announced to the trade a new tube designated respectively as RCA-234 and CX-234.

This new tube, a Super-Control R-F Amplifier Pentode, is an addition to the line of 2-volt tubes and is designed primarily for service in receivers operating from dry cells or from a storage battery where economy of filament-current drain is important.

The 234 will not be available through the regular channels of distribution until March 1 or later, when equipment using this type becomes available.

The 234 is recommended for use as a radio-frequency amplifier, intermediate-frequency amplifier, and first de-

tector in battery-operated receivers. Its design is such as to make it especially useful in portable receivers.

It is very effective in reducing cross-modulation and modulation distortion over the usual range of received signals. The design of the 234 is such as to permit easy control of a moderate range of signal voltages without the use of antenna potentiometers or auxiliary volume-control switches. This super-control characteristic makes the tube uniquely adaptable for use in the r-f and i-f stages of receivers incorporating automatic volume control.

The filament employed in the 234 is of the coated type. It is designed to consume as little power as possible consistent with satisfactory operating performance.

TENTATIVE RATING AND CHARACTERISTICS

Filament Voltage				2.0 Volts D.C.
Filament Current				0.060 Ampere
Plate Voltage	67.5**	90	135	180 Volts Max.
Screen Voltage, Maximum*	67.5	67.5	67.5	67.5 Volts
Grid Voltage, Variable	-3	-3	-3	-3 Volts Min.
Plate Current	2.7	2.7	2.8	2.8 Milliampere
Screen Current	1.1	1.1	1.0	1.0 Milliampere
Plate Resistance	400000	500000	600000	1000000 Ohms
Amplification Factor	224	290	360	620
Mutual Conductance	560	580	600	620 Microhms
Mutual Conductance at -22.5 volts grid bias	15	15	15	15 Microhms
Maximum Overall Dimensions:				
Length				4 1/16" - 5 1/4"
Diameter				1 13/16"
Cap				0.346" - 0.369"
Bulb				S-14
Base				Medium 4-Pin
Socket				Standard 4-Contact

* Under conditions of maximum plate current.

** Recommended values for use in portable receivers.

New Electronic Relay

Positively controlling a current of six amperes at 220 volts with a minute flow of one one-millionth (0.000001) of an ampere—that sums up the achievement realized in the latest form of electronic relaying device which we have named the Burgess Micro Relay. Or to put the case in more dramatic yet equally accurate terms, this latest electronic device permits such minute mechanical energy as 1 fly-power, which is more than ample, to control well over 1½ electrical horse-power of energy.

The relay in question transforms normally indistinguishable contacts into readily distinguishable, powerful, useful forces. In this characteristic lies its greatest value for temperature control work, go and no-go, and maximum and minimum control settings on sensitive indicating meters and other apparatus. It fulfills a function heretofore held uncertain because of the lack of a relay mechanism capable of such a wide spread between controlled and controlling energies. This device is particularly recommended wherever it is desired to provide indication or control at some predetermined value as shown by any indicating instrument, such as voltmeter, ammeter, pressure gauge, thermometer, etc., or in industrial equipment wherein positive action must be obtained by the closing of an electrical circuit through a pair of contacts under slightest pressure. The minimum current required eliminates the hazzard of variation or uncertainty of contact due to sparking, arcing, oxidation or contamination of contacts.

The Burgess Micro-Relay consists of an electronic tube in the plate circuit of which is a normally closed mechanical relay, said relay being held open by the residual value of plate current with an unbiased grid. The controlling contacts are so wired that when they come into contact a negative bias is placed on the grid, immediately causing the relay to close. This action occurs even with extremely high contact resistance in the order of twenty megohms; in fact, the relay will function with any contact resistance appreciably less than the insulation between the electrodes of the tube.

The components of this electronic relay are mounted in a stout metal cabinet measuring 7x8½x4¼ inches. A terminal strip inside the cabinet provides for connections with the external circuits. Knockouts permit of permanent wiring using BX or conduit. The relay is arranged to operate with a standard 25-watt lamp wired in series with the filament of the tube. This lamp serves the triple purpose of a resistor, pilot light to indicate that

Mercury Full-Wave Rectifiers


THOUGH rectifiers containing mercury within the bulbs have been in use some time for supplying high voltage and high current requirements of power amplifiers and transmitters, only recently has this type of

tube been brought to the attention of the public in the form of full-wave rectifiers for receiver use. Illustrations are given of two types, the first, a 282 type, and the second, a 986 type. The former has been presented by the Cable Radio Tube Corporation and the Hygrade Sylvania Corporation, while

the latter is developed by the John-sonburg Radio Corporation. Though serving the same purpose, the characteristics vary somewhat, especially as to the filament voltage and current required. One feature of the 280 type tubes has been overcome with the advent of the mercury vapor tubes, namely the high voltage drop across the tube itself which represents loss. A first look at the new tubes immediately impresses the individual because the glass bulb used is that of the familiar 201-A tubes so prevalent in early receivers. This means that the heat produced in rectification must be far less than heretofore. In operation this may be quickly ascertained by touching the bulb. Only one objectionable feature has been noticed in using these tubes, and that is that there is a transfer of noise in the power transformer, probably necessitating a static shield between windings that was not required before. Bypassing from plates to the filament may serve to help reduce the noise.



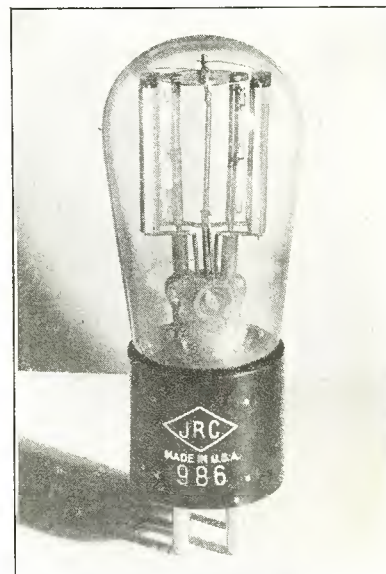Tentative characteristics of these two types of tubes follow:



282 Type

- Filament Voltage2.5 Volts
- Filament Current3.0 Amperes
- Maximum a-c Voltage per Plate500 Volts rms
- Maximum Peak Inverse Voltage1400 Volts
- Maximum d-c Output Current (continuous).....125 Milliamperes
- Maximum Peak Plate Current400 Milliamperes
- Tube Voltage Drop (approximate)15 Volts

986 Type

- Filament Voltage.....5.0 Volts
 - Filament Current.....1.0 Amperes
 - Maximum a-c Voltage per Plate (recommended)....400 Volts
 - Maximum Plate Current (recommended)150 Milliamperes
- This tube may be used to replace the 280 type tube directly with no changes in the circuit since the filament voltage is the same.

the relay is operative, and illuminator for the indicating instrument to which it is attached.

The mechanical relay of the unit is provided with a Burgess Vacuum Contact in place of the usual exposed contact points. This feature permits the handling of currents up to 6 amperes at 220 volts. In addition, the relay may safely be used in explosive atmospheres, since the contact is totally enclosed and no danger of ignition exists. It will be noted that with an infinitesimal operating current for the control end, and a vacuum contact device capable of handling over 1200 watts for the controlled end, this elec-

tronic device produces the greatest span between controlled and controlling functions yet attained in actual practice.

The delicate controlling current required to actuate the micro relay must result in successful applications in equipment which might operate only temporarily without it. The infinitesimal current is reduced to the point where oxidation, arcing and similar undesirable and indeed deleterious phenomena are positively eliminated. As an example of this point, the useful life of a contacting mercury thermometer may be increased indefinitely.

Voltage Analyses Charts

General Electric H-32

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	R. F.	2.5	230	.2*	2	3.5	60
27	Osc.	2.5	50	0	5	4.0	
24	1st Det.	2.5	230	3.5	4	.5	60
35	I. F.	2.5	230	.2*	2	3.5	60
27	A. V. C.	2.5	30	0	0	.1	
35	I. F.	2.5	230	3.5	20	2.5	60
27	2nd Det.	2.5	210	8*		.5	
47	P. P.	2.5	235	10*		25	250
47	P. P.	2.5	235	10*		25	250

Crosley 124

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
235	R. F.	2.38	250		3		90
224	1st Det.	2.38	180		7.5		60
227	Osc.	2.38	90		8		
235	I. F.	2.38	250		3		90
227	2nd Det.	2.38	180		20		
247	P. P.	2.38	250	16.5			250
247	P. P.	2.38	250	16.5			250
280	Rect.	4.80					

Philco 51

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
24	Osc. & Det.	2.2	220	9	9		85
35	I. F.	2.2	210	3	3	6.2	85
24	2nd Det.	2.2	75*	5.2	5.2		54
47	Output	2.2	210	.2*			240
80	Rect.	5.0	240			30-30	

Crosley 121-1

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	1st R. F.	2.3	170		4		90
35	2nd R. F.	2.3	170		4		90
35	1st Det.	2.3	170		7		85
24	Osc.	2.3	35		0		95
24	I. F.	2.3	175		2		95
27	2nd Det.	2.3	0		0		
27	A. F.	2.3	150		10		
47	P. P.	2.3	250	17			255
47	P. P.	2.3	250	17			255
80	Rect.	4.9					

Crosley 120

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
24	R. F.	2.5	160		3		90
24	Osc.	2.5	18		1.5		90
24	1st Det.	2.5	155		7		90
24	I. F.	2.5	160		3		90
27	2nd Det.	2.5	145		15		
45	P. P.	2.4	260	54			
45	P. P.	2.4	260	54			
80	Rect.	4.9					

United American Bosch 5

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
24	1st R. F.	2.3	250	2.5	2.5	4.5	90
24	2nd R. F.	2.3	250	2.5	2.5	4.5	90
24	Det.	2.3	150*	1.5	3.0	.5	20*
47	Output	2.3	250	16*		32	250
80	Rect.	4.8				20-20	

Voltage Analyses Charts

General Motors S-10A

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	1st Det.	2.25	170	5	100	4	87
35	I. F.	2.25	200	1	100	8	95
24	2nd Det.	2.25	120	6	7	.5	77
47	Output	2.25	270	7		35	255
27	Osc.	2.25	90	0	0	8	
27	A. V. C.	2.25	30	2	15	0	
80	Rect.	4.10	360			30-30	

Balkett L-8

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
51	R. F.	2.5	198		3.0		85
51	1st Det.	2.5	198		10.5		85
27	Osc.	2.5	105		17.0		
51	I. F.	2.5	198		3.0		85
27	2nd Det.	2.5	195		16		
47	P. P.	2.5	195		13.5		
47	P. P.	2.5	195		13.5		
80	Rect.	5.0	325				

General Electric S-22

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	R. F.	2.4	240		3.5	5.0	70
27	Osc.	2.4	65		2.5	5.5	
24	1st Det.	2.4	235		5.0	.5	70
35	I. F.	2.4	240		3.5	5.0	70
27	2nd Det.	2.4	220	5*	25	.5	
45	P. P.	2.4	245	30*		25	
45	P. P.	2.4	245	30*		25	

Brunswick E, 17, 24, 25

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
51	R. F.	2.4	250		2.8	4.5	76
24	1st Det.	2.4	250		2	.5	68
51	I. F.	2.3	250		3	3	76
24	2nd Det.	2.3	200		.2	.2	60
24	Osc.	2.3	35		0	1	16
27	A. V. C.	2.3	22		7	0	
47	Parallel	2.5	250	.2*		25	250
47	Parallel	2.5	250	.2*		25	250
80	Rect.	4.8	400			43-43	

RCA-Victor Radiola 43

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
32	R. F.	2.0	155	22			55
30	Osc.	2.0	50			3	
32	1st Det.	2.0	150	.5		.5	65
32	I. F.	2.0	155	22			55
30	2nd Det.	2.0	90*	5			
30	Audio	2.0	150	2		2.5	
30	P. P., "B"	2.0	150	15		.5	
30	P. P., "B"	2.0	150	15		.5	

Kolster K-70

Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	R. F.	2.5	190	.5*	80	.25	60
27	Osc.	2.5	80	2.5	80	5.0	
24	1st Det.	2.5	180	5.0	84	.6	50
35	I. F.	2.5	195	3.0	80	1.0	75
24	A. V. C.	2.5	20	.25	50		25
24	2nd Det.	2.5	100*	4.0	80	.25	24*
47	Output	2.5	235	4.0*		35	260
80	Rect.	5.0				46-46	

Voltage Analyses Charts

Howard DL							
Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	1st R. F.	2.3	180		3.2		89
35	2nd R. F.	2.3	180		4.3		88
35	1st Det.	2.3	175		8		87
27	Osc.	2.3	80		9		
35	I. F.	2.3	180		3		89
35	I. F.	2.3	180		4.4		89
27	2nd Det.	2.3	175		17		
27	A. V. C.	2.4	112*		31*		
27	Phono	2.3	175				
47	Output (4)	2.25	245		8		250
80	Rect. (2)	4.75	408		16		

Silver-Marshall Q							
Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
24	1st Det.		244		14		88
51	I. F.		244		3.4		88
51	I. F.		244		3.4		88
27	2nd Det.		140*		20		
47	Parallel		224	15			244
47	Parallel		224	15			244
27	Freq. Chan'r		244		88		
27	Osc.		88		5		
27	A. V. C.		0	0	46	0	
80	Rect.						

All American Lyric S-7							
Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
51	R. F.	2.5	195		2		70
24	1st Det.	2.5	195				70
27	Osc.	2.5	70		0		
51	I. F.	2.5	195		2		70
24	2nd Det.	2.5	168*		4.5		70
47	Output	2.5	230	17			250
80	Rect.	5.0	350				

Sparton 10							
Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	R. F.	2.5	270	4.0		8.0	100
35	1st Det.	2.5	270	7.5*		3.5*	110
35	I. F.	2.5	270	4.0		8.0	110
27	Osc.	2.5	110				
27	2nd Det.	2.5	135*	14		.7	
47	Output	2.5	260	18		36	260
80	Rect.	5.0	420			55-55	


Kolster K-60							
Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
35	R. F.	2.5	230	.25*	3	6.0	80
27	Osc.	2.5	85	0	0	6.0	
24	1st Det.	2.5	225	6.4	6	1.0	74
35	I. F.	2.5	225	3.5	4	7.0	80
24	2nd Det.	2.5	125*	4.2	6	.2*	22*
47	Output	2.5	225	2*		24	245
80	Rect.	5.0				48-48	

General Motors S-9A							
Tube	Position	Fil. Volts	Plate Volts	Grid Volts	Cath. Volts	Plate Ma.	S. G. Volts
224	1st Det.	2.35	290	6	6	1.5	80
235	I. F.	2.35	290	3	3	6.5	83
224	2nd Det.	2.35	180	7	7	.3	63
247	Output	2.35	270	5*		35	260
227	Osc.	2.35	80	.5		7	
280	Rect.	4.80	370			30-30	

NEW PRODUCTS FOR THE TRADE

ICA Visionette

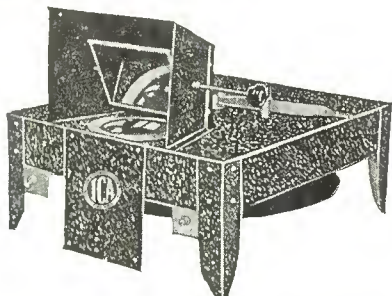Insuline Corp. of America, 23 Park Place, New York City, announce the new Insuline sight reproducer known as the Visionette.



The manufacturers state that the Visionette uses a 5 inch square image having three dimensional depth and permits the whole family to view the television images simultaneously.

The motor utilizes a wound stator for its field and two rotors both on the same vertical shaft. One of the rotors is of the squirrel-eage induction type and is used to bring the scanning disc up to speed, and the other rotor is of the laminated iron-toothed synchronous type.

The Visionette employs a novel magnifying lens system, arranged so as to give maximum enlargement, with accurate correction for spherical aberration.

Lynch Steel Resistor Cabinet Free

To enable jobbers, dealers and service men to keep an accurate check on their resistor stock and to facilitate the filling of orders by being able to find at a glance the resistors wanted. The Lynch Mfg. Co. offers to supply a useful, durable, 50 drawer steel filing cabinet with a special introductory deal on their metallized and precision wire wound resistors. The drawers are 8" x 3" x 2½" wide. The case is 33" x 18½" x 8½". This is just a part of their sales service to the trade, as they also furnish catalog sheets, R. M. A. color code cards, and service men's resistor replacement manuals. For further details, address A. E.

Stevens, Sales Mgr., Lynch Mfg. Co., Inc., Dept. P, 1775 Broadway, New York City.

New Aluminum Solder

The discovery of an all-metal solder that repairs aluminum, pot metal, die castings and steel, promises to be of decided importance to the radio industry. This solder is called Alumaweld and is a development of the Allied Research Laboratories, Glendale, Calif.

As the name Alumaweld implies, the solder actually breaks down the structure of the metal being repaired and fuses or welds with it to form a single, solid piece. It is not to be confused with a surface solder.

Alumaweld is applied to any metal with an ordinary soldering iron or blow torch. It melts at an exceedingly low temperature, but once applied requires a much higher temperature to melt again. The fact that it has a tensile strength of 12,000 lbs., which is over ten times that of ordinary solder, indicates its permanency.


Alumaweld is now being used extensively in radio work for the repair of aluminum cabinets, aluminum housings, and other metal work. Average repairs take from 10 to 12 minutes, and there is no need to tear down the set or remove any parts. Alumaweld is quite ductile, machines easily, and will take a nice polish over which chromium plating or any other plating can be applied.

This solder can be used by anyone regardless of experience. It replaces welding at a fraction of the time and cost, without any danger of cracking during preheating or cooling. Alumaweld cannot possibly rust, inasmuch as there is no electrolytic action between the solder and metal. A free

sample of Alumaweld may be secured by writing the discoverers.

Electrotec-Phototube-Relay

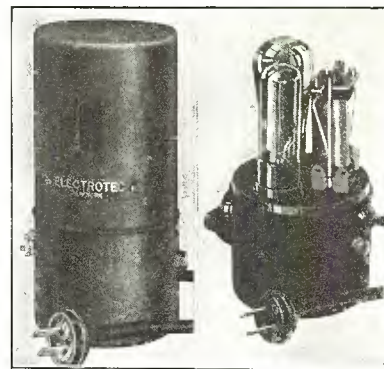Electrotec Engineering Corp., 180 Madison Ave., New York City, announces a universal model phototube relay that covers a wide range of light control applications.



This model has been designed so that it may be set up and operated by anyone with no previous experience. It has an external adjustment that may be set to operate on a change of one-tenth of one foot candle in illumination, from absolute dark to daylight or for impulse operation from a light source.

The Electrotec phototube relay is manufactured in three models that may be purchased from jobbers and dealers, a-c, d-c, and battery types. All models have cord and plugs and terminals for open and closed circuit operation, overall dimensions of all three models are height 7 inches, diameter 3½ inches. Electrotec Engineering Corp. also manufacture a complete line of auxiliary relays for power work and are equipped to furnish engineering services for any specialized application of light control.

NEW PRODUCTS ITEMS

Manufacturers who have items that come within the scope of this department will find it of advantage to keep our name on their mailing list for announcements of new products. Halftones or electros should not exceed 2¼ inches in width.

Address—New Products Editor, care this magazine.

Balkeitt Model DP

Balkeitt Radio Co., North Chicago, Ill., announces their model DP using two pentode tubes, which they state supplies greatly increased volume if the listener desires, or if the receiver is placed in an unusually large room.




This receiver employs a full sized dynamic speaker, with a hum bucking coil, three gang ball-bearing variable condenser, and dry electrolytic condenser, with full vision illuminating dial.

Tubes used consist of three 224s, two 247s and one 280. Shipping weight 27 lbs.

Jackson-Bell "Peter Pan"

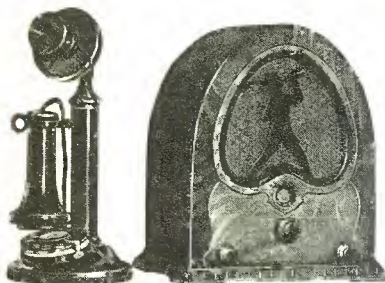Jackson-Bell Co., Ltd., Los Angeles, Calif., announce their model Peter Pan, which sells for \$29.95, complete with tubes.




The manufacturer states that this receiver comprises the smallest modern radio set on the market today and uses the full efficiency of the pentode tube. The Peter Pan weighs just 10 lbs. and is not quite as high as the standard size telephone which is shown in the illustration above. Licensed under RCA, Hazeltine and Latour patents.

Record Playing Attachment for Radio Sets and Address Systems

A new portable and completely self-contained unit for reproducing records through radio sets and power amplifiers has been announced by the Operadio Mfg. Co., St. Charles, Ill.

Housed in the leatherette carrying case are an electric phonograph motor and turntable, and a sensitive electro-

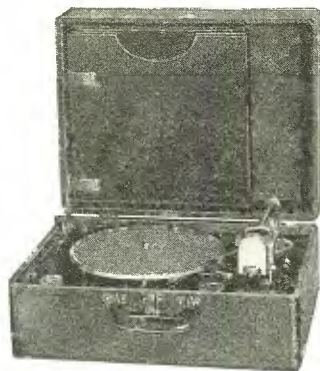magnetic pick-up. A carrying case in the cover provides for storage of




several records without danger of breakage.

This unit is adapted for use with all radio sets and amplifiers having provision for connection to either high or low impedance pick-ups. Adapters are available for connections to most other radio sets.

Available with either high or low impedance pick-up, and with 78 or 33 $\frac{1}{3}$ r.p.m. motors, for 25 or 60 cycle, 110 volt power supplies.

Simplex Model K

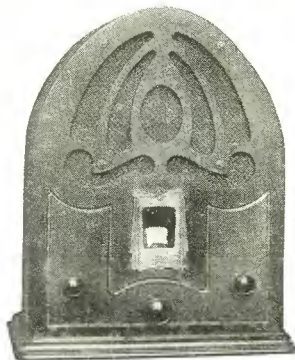The Simplex Radio Co., Sandusky, Ohio, announces their 5 tube model K midget receiver.



This receiver is shown in the illustration above. It is 9 inches wide, 12 inches high, 6 $\frac{1}{2}$ inches deep, and weighs 13 lbs. The tubes used are two 224s, one 235, one 247, and one 280.

Tung-Sol Announces a High Power Output Pentode Tube

Tung-Sol announces the development of a new Tung-Sol tube called a d-c power amplifier, pentode, bearing the designation, TS-257.

This new tube is intended for use in the power output stage of 115 volt direct current operated sets especially designed for it.


TS-257 is designed to operate at a maximum plate and screen voltage of 110 volts and will produce a power output of 800 mw, which is approximately 3 $\frac{1}{2}$ times the power output of the 171-A type and more than twice the output of the TS-233 or TS-238 types when operated at the same plate

voltage.

In receivers designed for operation on direct current power lines, the filaments of two or more of these tubes may be connected in series. Since the filament current rating of the TS-257 is the same as the TS-236, TS-237, TS-238 and TS-239, i. e., 300 amperes, these tubes may be operated in series.

Burgess Micro-Relay

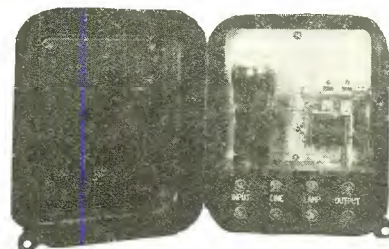C. F. Burgess Laboratories, Inc., 202 E. 44th St., New York City, have taken over the activities of the Burgess Battery Co. in the sale of Burgess Radio-visor Bridges (light-sensitive cells), vacuum contacts, vacuum contact relays, micro relays, light control units and other electronic devices, as well as the acoustimeter line of the Burgess-Parr Co.



The illustration above shows the Burgess micro-relay with electron tube, mechanical relay equipped with vacuum contact, and terminal strip.

New Ohmite Bulletin


Ohmite Mfg. Co., 636 N. Albany Ave., Chicago, announces the publication of a new stock list, bulletin No. 10, which illustrates and describes Carbohm and Wirohm resistors.

The bulletin lists 75 different values of carbon resistors in both 1 watt and $\frac{1}{2}$ watt sizes, as well as 42 different values of wire-wound resistors. These wire-wound resistors, called Wirohms, are of special interest because of their high wattage rating and very small size.

The Ohmite Mfg. Co. will gladly send this bulletin to anyone requesting it.

Mallory-Elkon Announces New Auto B Eliminator

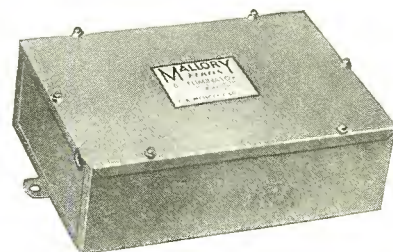P. R. Mallory & Co., Inc., Indianapolis, are manufacturing a B battery eliminator for automobile radio.



This new unit is energized by the 6 volt A battery in the car which is constantly supplied with energy by the automobile generator. It boosts


the 6 volts in the A battery up to 180 volts or the equivalent of four 45 volt B batteries.

The Mallory-Elkon B eliminator can be used for all popular brands of automobile radio sets. It is compact, size 10 inches by 7 inches by 3 1/4 inches, and is easily installed in the car.

The list price of this new unit is \$24.50 complete with nothing else to buy. The installation instructions in full detail are packed with each unit.

New All-Wave Receiver

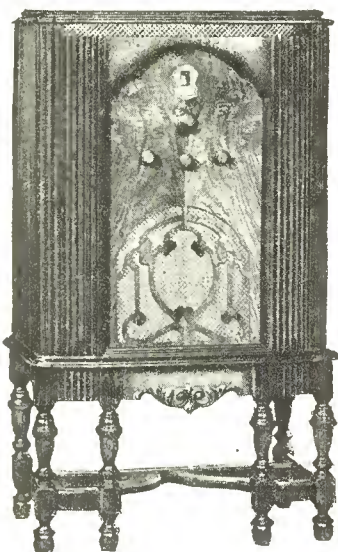United Air-Cleaner Corp., 9705 Cottage Grove Ave., Chicago, announce their new Sentinel No. 125 eight tube all-wave superheterodyne console model.



This receiver covers a range from 13 to 550 meters. Tubes used include one 224 screen grid first detector, one 227 oscillator, two 235 variable mu intermediate frequency amplifiers, one 227 diode detector, which also acts as the automatic volume control tube, one 235 variable mu controlled audio amplifier, one 247 power pentode output tube, and one 280 full-wave rectifier.

Radio Physics Course


The Radio Technical Publishing Co., 80 Fifth Ave., New York City, announces the completion of their Radio Physics Course, including short waves, television and sound pictures. Price \$3.50. Also Radio Servicing Course, which contains a complete course in modern radio servicing, using up-to-date methods. Price \$1.50.

Midget Television Set

The Globe Television & Phone Co., 26th St. and 11th Ave., New York City, announce their midget television receiver in a cabinet no larger than the usual broadcast receiver. The pictures appear on a ground glass screen measuring 4 by 5 1/2 inches. Illuminated scale and control knobs are

placed below the screen.

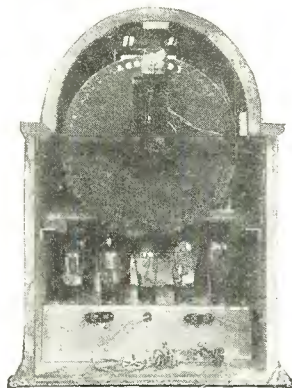
The receiver is mounted on a metal chassis, and uses two screen grid -24 tubes, one -27 detector, one -24 first audio, one -27 second audio and two -45 power tubes for the third audio stage, together with the -80 full wave rectifier. A power pack is included for full a-c operation.



The cabinet measures 16 1/2 inches wide by 14 1/2 inches deep and 24 1/2 inches high. It is finished in walnut.

New Auto Radio

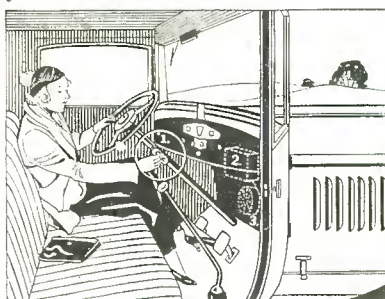Motorphone Radio Corp. of America, 136 Liberty St., New York City, announce their auto radio known as the Bonded Motortone. The manufacturers state that this receiver can be mounted in any automobile in one hour and does not require drills or any other tools.



The 1932 model uses six tubes, which consist of three 236s, one 237 and one 238 in a screen grid push-pull pentode circuit.

The manufacturers state further that this receiver is completely shielded and will withstand all shocks and vibrations. The chassis can be removed from the car by unloosening two hooks, and if repairs are necessary can be repaired in the workshop. The equipment consists of a Utah remote control, Utah 8 inch dynamic speaker mounted in a metal casing, and shielded battery cable.

New Pierce Airo Super

Pierce Airo, Inc., 510 Sixth Ave., New York City, announces to the radio trade a new seven tube pentode superheterodyne, dual wave, single dial receiver, with shadowgraph tuning. It is available in alternating or direct current.

The tubes used are one pentode, two 224s, one 35, one 180, one Amperite L-3, and one 227. It is equipped with phonograph pick-up jacks. The speaker is acoustically correct, with the cabinet design in two-toned walnut veneer.



Anyone interested in ranges from 60 to 600 meters, police calls, short wave and amateur calls will be more than satisfied with the performance and results obtained from this receiver. The price complete is \$49.50.

Literature will be furnished by writing Pierce Airo, Inc., at the above address.

New Show Rooms Feature Free Institute For Radio Service Men

The Wholesale Radio Service Co., formerly at 38 Vesey St., New York City, is now installed in a new location at 100 Sixth Avenue, New York City. The city sales room embraces a spacious lobby, equipped with soundproof booths and a miniature theatre. Special provision is made for the radio service man and his needs. Special testing instruments have been installed and a competent radio engineer is on hand at all times for consulting purposes.

Norden-Hauck Announces New Models

Norden-Hauck engineers, pioneers in the radio field since 1922, have completed several new designs, incorporating the very latest improvements in receiving equipment. These will include a de luxe fifteen tube broadcast receiver, which is also equipped for short wave reception, to be known as the Norden-Hauck Custom Imperial.

A smaller model with single dial feature will be a medium priced combination short and long wave receiver, super DX-10.

A short wave adapter is also included in this group, which is a four tube unit, completely self-contained, and will provide high efficiency on short waves when used in conjunction with other standard receivers.

Further information may be obtained by writing Norden-Hauck Elec. & Mfg. Co., 402 Cherry St., Philadelphia, Pa.


RADIO PHYSICS COURSE

By Alfred A. Ghirardi
You cannot afford to be without these two wonderful new books. Radio's two foremost authorities cover every phase of the subject to the present time. A complete radio education—in your spare time at home!

Author of the Radio Physics Course now running in Radio News.

\$3.50

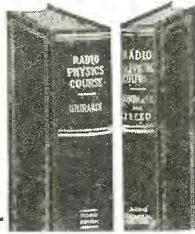Postpaid in the U. S. 992 pages. Over 500 Illustrations.



RADIO TECH. PUB. CO., Dept. RCB-5
Now at 80 Fifth Ave., New York City..
Enclosed find check, cash or money order for copies of Radio Physics Course at \$3.50 each, and copies of the Radio Servicing Course at \$1.50 each. Check here for FREE circular

NAME
ADDRESS

RADIO SERVICING COURSE

By A. A. Ghirardi & B. M. Freed
Bertram M. Freed is contributing Editor of Radio Craft Servicing Department. 192 pages. Over 100 illustrations. Postpaid in U. S.

\$1.50

MAIL THIS COUPON →

Red Seal



Radio Tubes

6 MONTHS' GUARANTEE

Sold on a 6 Months Free Replacement Guarantee. All tubes are carefully receiver and meter-tested before shipping and carefully packed in uniform "Red Seal" boxes. Do not confuse these high quality tubes with any other "low priced" tubes. Invoices stamped with expiration date of guarantee.

WD11	\$.65	210	\$1.00	236	\$.75
WD12	.65	222	1.00	237	.75
112A	.35	224	.30	238	.75
120	.35	226	.30	240	.35
171A	.30	227	.30	245	.30
171AC	.35	230	.60	247	.55
199V	.45	231	.60	250	1.00
199X	.45	232	.75	280	.30
200A	.35	233	.75	281	1.00
201A	.30	235	.55	B. H. Type	1.25



New "Red Seal" Pentode Adapter Gives added Pep to your Set!

Increases volume and clarity. Replaces Old Type 245 Power Amplifier with New Type 247 Pentode Tube.

List Price \$2.50
Your Cost75
In Quantities of 25 or more . . .60 each

TERMS: 20% with order. Balance C. O. D. 5% discount for full remittance. Quick Service.

No orders on Tubes accepted for less than \$3.00

Red Seal Sales Co., 318A Canal St., New York, N. Y.

UNIVERSAL MODEL "BB"

1932 Value—New Design
List Price \$25.00

No other 2-Button microphone can give such superlative value for such a low price. Extra large size. Rugged construction. Built especially for voice pick-up, public address work and amateur broadcasts. 24 Kt. Pure Gold Spot Centers. Duralumin Diaphragm. Frequency range to WELL over 4000 cycles.

Guaranteed Performance at Rock Bottom Price.
UNIVERSAL MICROPHONE CO., Ltd.
424 Warren Lane, Inglewood, Calif., U. S. A.



BEN J. CHROMY

Counsellor in Patent Causes
710 Fourteenth Street
WASHINGTON, D. C.
"Radio Patent Service" Weekly

BRIEF ITEMS OF INTEREST TO MANY

There has been a long felt want in the radio field for a school of recognized standing to give a complete, comprehensive, well balanced course in Radio Communication, to be complete within itself and capable of being finished within a reasonable time. Realizing this need, the University of Wisconsin, Extension Division in Milwaukee, is giving such a course to fit students for advanced places in radio activities. This is a new type of college training of a semi-professional nature with the object of training young men for positions existing in a field between the skilled craftsman and the trained professional engineer.

All trades and professions are now demanding that the men participating in them shall be thoroughly trained in the theory and fundamentals of the trade or profession in question. The ever expanding science of radio is possibly more exacting in this than any other because of the extremely technical nature of the subject and of the enormous responsibilities upon the shoulders of an operator. A few years ago a man could be a fairly good operator or technician without any particular training, but today, if a man expects to succeed in this field he must be thoroughly grounded in the theory and practical applications of the fundamental principles of radio communication. The question has been to the serious-minded person, "Where can I secure such an education without taking a regular degree in engineering?"

The course given in Milwaukee is not an experiment, for it has grown out of auxiliary courses given during the past six years and is planned as a definite preparation for the actual problems met in practice. The work given is substantially of collegiate grade, requiring only a high school education or the equivalent for entrance. The training is very intensive, requiring the entire time of a student for two semesters. The entire day is occupied from eight until four-thirty with lectures, class work and laboratory experiments and special problems and assignments to be completed after class hours. This same course may be taken in evening classes over a period of two years or by correspondence.

The principal course of a complete training in Radio Communication is strengthened by supplementary subjects which assure a thorough understanding of the various phases of the theory and practical applications of receiving and transmitting circuits. These correlated subjects include Elementary Electricity, High Frequency Currents, Thermionic Vacuum Tubes, and laboratory work which is divided into three parts; (1) actual experiments, (2) design of apparatus and circuits and (3) adequate drill in International Morse Code. The entire list of studies is completed more easily because of a study of Technical Mathematics as applied to electricity and Technical English, which pertains to the writing of reports and experiments. The satisfactory completion of the course qualifies a student for the government examination for a Second Class Commercial Operator's License or he may enter many of the allied branches of the radio industry.


Mr. D. T. Siegel, General Manager of the OHMITE MANUFACTURING COMPANY, 636 N. Albany Ave., Chicago, announces that this company has developed a new simple COLOR-CODE CHART for use with R. M. A. coded resistors.

This chart, which may be carried in the pocket or hung upon the wall, consists of a full size drawing of a coded resistor and a reproduction of the actual colors used in the code. This makes it possible to read the value of any coded resistor at a glance without any manipulation or bother.

(Continued on page 50)

only \$37.50 11-TUBE Super-Het!

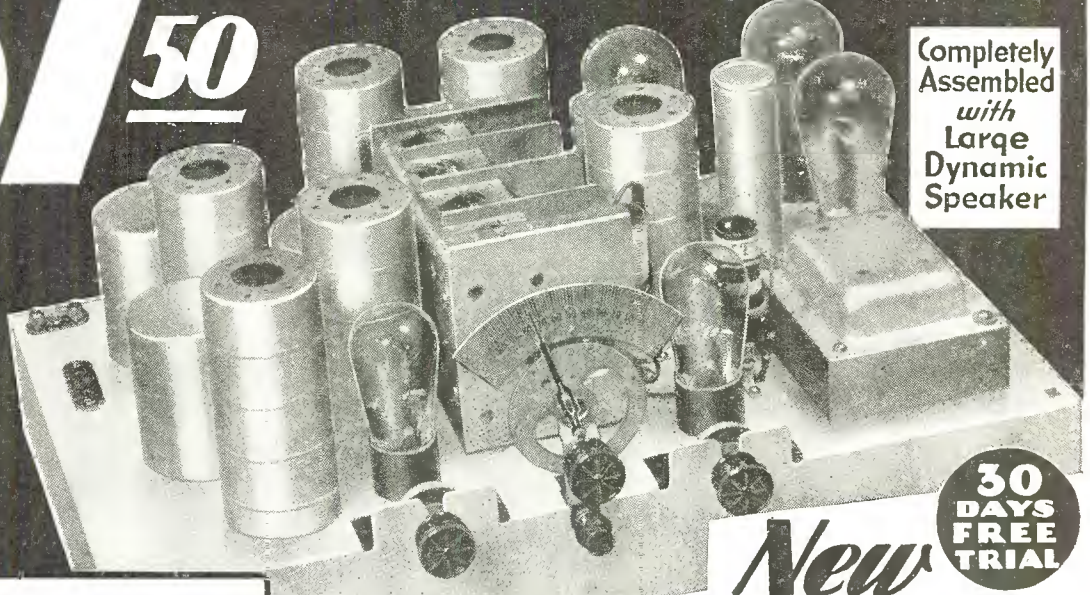Completely Assembled with Large Dynamic Speaker




Pentode Variable-Mu and Real Automatic Volume Control

30 DAYS FREE TRIAL

New

13-Tube and 15-Tube ALL WORLD-ALL WAVE COMBINATIONS!

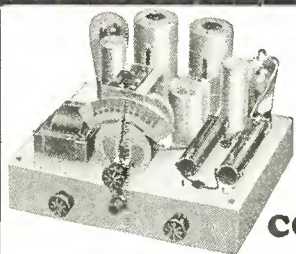

MIDWEST 4-TUBE SHORT-WAVE CONVERTER

World-Wide Short-Wave Reception

Converts any A.C. set of adequate sensitivity into a short-wave receiver for reception of police

calls, airplane conversations, ships at sea, and broadcasts from foreign stations.

This amazing new short-wave converter employs 4 tubes, self-powered. It uses one 280, one 224, and two 227 tubes. In combination with a 9-tube Super-Het, it gives you a 13-tube ALL-WORLD, ALL-WAVE combination. When used with the very latest model Midwest 11-tube super-heterodyne, shown above, it gives you a total of 15 powerful tubes, and ALL-WORLD, ALL-WAVE reception unbeatable even in receivers costing several times as much.

Don't confuse this 4-tube self-powered converter with cheap one- and two-tube converters that are not self-powered. The Midwest Converter actually gives better performance than many converters costing twice as much.

Now you may get SHORT-WAVE broadcasts—airplane calls—police signals—foreign stations—standard long-wave broadcasts—all with one combination set. Hear U. S. stations from coast to coast, and from Canada to Mexico. Hear the Canadian stations, Mexico, Cuba, South America, Europe, Asiatic and other foreign stations and ships at sea. A Midwest 13-tube or 15-tube combination gives you ALL that's desirable in radio. These wonderful new combinations are sold at amazingly low direct-from-factory prices. When you receive our big new catalog and note the low prices, 30-day free trial offer, terms as low as \$5.00 down, you'll be positively amazed. Mail the coupon right now—get the surprise of your life.

Deal Direct with Factory SAVE UP TO 50%

Never have such powerful sets been offered at Midwest's amazing low direct-from-factory prices. You save the middlemen's profits. Your outfit will reach you splendidly packed, rigidly tested, with everything in place ready to plug in. No assembling! Entertain yourself for 30 days absolutely FREE—then decide. And don't forget—every MIDWEST outfit is backed by an absolute guarantee of satisfaction. You take no risk. Mail the coupon now!

TERMS AS LOW AS \$5.00 DOWN

AIR-CELL BATTERY 8-TUBE SETS

For homes without electricity. The amazing new air cell battery does away with all battery troubles. Never needs recharging. Just add a few drops of water occasionally—that's all. It's "Self-charging." No trickle charger—no battery troubles of any kind. Brings the joys of radio to any home, anywhere, any time. 8-tube battery chassis completely assembled (1 c s s tubes) now Only \$19.95.



Complete line of Consoles

The big FREE catalog beautifully illustrates the complete line of gorgeous Midwest Consoles. "De-luxe," "Highboy and Low-boy" models.

Read These Letters from Midwest Owners

Holds VK2ME Two Hours
"I heard VK2ME Australia this morning and held them for over two hours. The volume was ample to hear this station all over the house. Have received amateurs all over the U. S. from Maine to California. I have also picked up GBS and stations in Colombia, S. A., two in Argentina, one in Indo-China and one in Canada. VEADR, which comes in at all hours."
E. APPLEBAUM,
334 Johnson Ave., Newark, N. J.

Gets Germany, Italy, France
"Received converter—am well pleased with it. March 2nd I picked up Germany, France and Italy. On the following day I got Italy again clear and loud. From 2:45 till 6:40 P.M., I heard all of the music from the Royal Opera House."
A. MOSCONI,
7122 Paschall Ave., Philadelphia, Pa.

Bermuda, Philippines, Switzerland, Rome
"I am very well satisfied with my Midwest and have picked up the following: Vancouver, B. C., Hamilton, Bermuda, Geneva, Switzerland; Philippine Islands. Two-way conversation between airports and airplanes. Police radio from every direction. Rome, Italy. It was announced as Italia, Roma, and came in about the position on the dial which would indicate 12-RO Rome."
GEO. E. KUHR,
218 Division St., Bellevue, Ky.


Gets Sydney, Australia
"On February 28th, at 4:30 A.M. Sunday, I picked up VK2ME, Sydney, Australia, which I think is good as I have a poor location for radio."
S. M. BEVENUE,
1815 Dolman St., St. Louis, Mo.

Hears League of Nations Speeches
"I raised Houduras at 78% on middle switch; at 36% a European station at 10 o'clock E.S.T., broadcasting League of Nations speeches. Around 11 A.M. I picked up another European station at 48 broadcasting a fine program of music, the announcing being in German."
A. BAILLARGNON,
6009 Notre Dame East,
Montreal, Canada.

MIDWEST RADIO CORP.
Dept. 77 (Est. 1920) CINCINNATI, O.

Mail this Coupon for Complete Details and Big FREE Catalog!

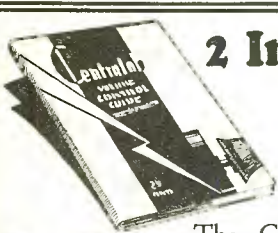MIDWEST RADIO CORP. Send me SPECIAL USER AGENTS' PROPOSITION.
Dept. 77, Cincinnati, Ohio.
Without obligation send me your new 1932 catalog and complete details of 13- and 15-tube All-World, All-Wave Combinations, 4-tube Converter, 9- and 11-tube Superheterodynes, low factory prices, easy terms and liberal 30-day free trial offer. This is NOT an order.
Name.....
Address.....
Town.....
State.....



2 Important Books Send for them today



The **CENTRALAB VOLUME CONTROL GUIDE** tells how to service all old and new sets with but a few Replacement Controls . . . now at new low price. The Guide, 25c.

The **BAPTISM OF FIRE** tells the graphic story of how Centralab Fixed Resistors are made. It is FREE.

Centralab

CENTRAL RADIO LABORATORIES

MAIL COUPON TODAY

CENTRAL RADIO LAB.

Keefe Ave. and Humboldt, Milwaukee, Wis.

Please send me your free booklet on Fixed Resistors.

I enclose 25c for your Volume Control Guide.

Name

Address


City State.....

Radio Call Book

ACROCYCLE

\$17⁵⁰

OSCILLATOR

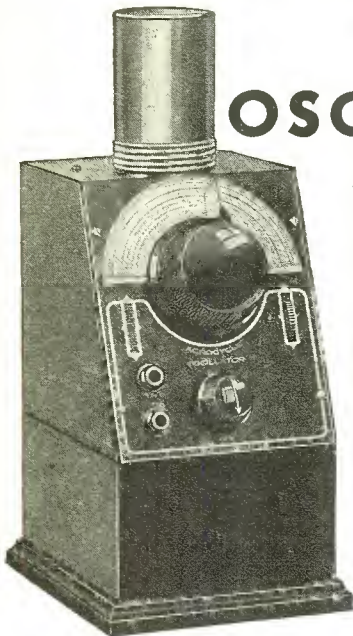

A SELF-CONTAINED, fully shielded oscillator, with full vision scale calibrated directly in Kilocycles—no charts used—micrometer slow motion dial—can be set at exactly any frequency from 115 to 1680 K.C. Uses four flashlight cells and one 22½ volt battery automatically connected when inserted. Uses one 30 tube self-modulated. Can be checked for accuracy when attached to any receiver by the "beat" method to within 20 cycles.

Dealer's Price—Oscillator with test leads \$17.50. Complete set of batteries and tube \$2.25 extra. Leatherette Carrying Case \$2.00 extra. If your jobber does not carry, order direct. Sent express collect or C.O.D. with a deposit of \$1.50. **Free circular.**

[[This instrument is made by the manufacturers of the "Submariner" Short Wave Adapter now priced at \$12.50. The first adapter on the market built since 1926.]]

ORDER TODAY!

J-M-P MANUFACTURING CO. INC.

(Established 1922)

3002—No. 34th St.

Milwaukee, Wisconsin, U. S. A.

Brief Items

(Continued from page 48)

The color-code Chart is offered free to any radio dealer, service man, or manufacturer who writes the OHMITE MANUFACTURING COMPANY on his business stationery.

Wm. A. Schofield, Philadelphia, Pa.: We received your service schematics and reply to my question in regard to sensitivity and noise levels in receivers, in which you state, "if noise levels were the same, then a receiver with a sensitivity of 10 microvolts absolute would not be as desirable as one of 1 microvolt sensitivity. This, however, is never the case, because the noise level increases rapidly as the sensitivity is increased due to normal inherent qualities." I admit that I exaggerated the data I had in mind in order to clarify the question. After obtaining the March issue, I can state my question more definitely: Would not a receiver with a sensitivity of ¼ microvolt absolute with a noise level of 9 per cent to 38 per cent be more desirable than one with a sensitivity of 1.9 microvolts absolute and 57 per cent to 69 per cent noise level? I know your policy has always been to be absolutely impartial and that you have always refused to compare one receiver against another, so I selected two sets of the same manufacture, not because they interested me, but because I wish to clarify the matter in my own mind. In other words, how much consideration should be given sensitivity curves and is there a definite limit beyond which sensitivity does not make much difference? I note that the smaller receiver is more sensitive than the larger and would outperform it if the sensitivity curve is to be taken as the sole method of comparison. Is there any evident reason for this? I have examined the schematic thoroughly and cannot find any radical departure from the expected. Of course, the larger receiver has a greater audio output, i. e., 10 watts against 3.2 watts, but according to authorities, such as G. H. Browning and J. Millen, "an audio output of 50 milliwatts will give about the required volume in a medium sized room provided the loud speaker is of average sensitivity." With the set having a sensitivity as great as ¼ microvolt absolute, the additional audio amplification could not be used on any station this side of China. There is no need of my stating that I think your magazine is just right. Any criticism, constructive or otherwise, would be like looking a gift horse in the mouth. Ans. Noise level in any case determines the utility of the sensitive receiver. The examples you gave showed the most sensitive receiver to have the lowest noise level and, of course, this receiver would be better than that having higher noise level and a lower sensitivity. It would, of course, be a mistake to judge a receiver merely by its sensitivity because of a factor which may, to some people, be more important, and that is selectivity, and, too, tone quality must not be overlooked, and lastly the power overload or automatic volume control. We suggest that the receiver which you mention does contain a considerable amount of regeneration to give such extreme sensitivity. This fact is not desirable in any receiver, especially in a superheterodyne. The above statements should then answer your question as to why one should buy a receiver containing more than seven tubes when a seven tube receiver will give you as much sensitivity as will ever be required.

E. A. Hesing, Harrisonburg, Va.: Every month for some months I have been buying your magazine to keep up to date with the broadcasting stations. Your receiver performance curve section took my eye at once, but as I am just a layman, may I ask you a question? Is there such a thing, and if so, where can I get the same data that a layman can understand? In other words, taking two receivers of about the same price and the same number of tubes, can I get any

(Continued on next page)

Brief Items

(Continued from preceding page)

data as to which should give the best performance without trying both of them out. Ans. After a study of the page entitled Receiver Performance Curve Section, which immediately precedes the ten receiver write-ups, you should be able to understand the points which are necessary for judgment of a receiver. Other than this it is rather difficult to give a further explanation. Our curves are used in many, many cases, not only by service men and dealers, but also by engineers, so you may be sure that they can be relied upon. You cannot be very wrong in assuming that receivers may be compared by means of their curves, since performance in the field will very nearly duplicate these results. This would not be true if receivers were not shielded, but in the present day almost without exception they are. We might point out the following facts to aid you in your selection of a receiver or a comparison between two receivers. First, the lower the average sensitivity, that is, the nearer it approaches the base line, the more sensitive the receiver becomes. The shaping of the curve should not influence the reader's mind to any great degree, but instead, the average sensitivity should be taken. One thing must be considered in connection with ultra-sensitive receivers and that is the attendant noise level. As far as selectivity is concerned, the less spread between the curves, that is, the narrower the band widths, the more selective the receiver becomes. We believe that the fidelity and power overload or automatic volume control curves are self-explanatory.

Sid's Radio Service, Salem, Ore.: I agree with those who wish socket data and voltage charts with the other valuable information you give us. I believe you could make a composite curve to show selectivity and sensitivity and another for fidelity and power overload without crowding. This method would save half the space now devoted to charts or approximately five column inches. Then by explaining on the first page of the performance section that each set was tested under standard conditions you could utilize the space saved by avoiding repetition or about three to three and one-quarter column inches, and you could gain over eight column inches and give no more dope upon which to cogitate except on one page. Let me thank you for making this informative magazine a monthly.

James Wood, WLAYG, Millis, Mass.: I read *Radio Call Book Magazine* and like it very much. I really believe it is the outstanding publication dealing with broadcast problems. Your diagrams contain more complete information than many of the expensive radio manuals which are available. Every resistor and condenser is accurately marked.

Furniture Distributing Corp., Chicago, Ill.: Please explain what is a good power overload curve and why some have so many irregularities. Ans. A good power overload curve is one which rises rapidly with increased input and becomes practically flat after the bend. Irregularities in the curves are due to various overloading phenomena in the detector and audio circuits, especially when automatic volume control is not used.

G. A. Weatherby, Wingo, Ky.: I should like to have information with regard to receiving sets. If a station broadcasts on a frequency, for example 1320 kc with 1000 watts output, how many miles will be its effective range? Ans. There is no rule, absolute or empirical, which will even approximately give a broadcast station's range when the frequency and power are known. Some of the factors which enter into the problem are the height of the antenna system of the broadcast station, its location with regard to the surrounding country, the direction of the antenna, the percentage of modulation, signal absorption by structures and

(Continued on next page)

LEARN NEW BRANCHES OF RADIO AT HOME!

or at resident schools of




THINK of the exciting new branches of radio now opening up! Television and sound, servicing this new equipment, aviation radio, broadcast operating. All of them promise to have a great future. You can become part of radio's future, too, if you are properly trained. RCA Institutes, America's oldest, best known radio school, has home study and resident school courses in every branch of practical radio. All the

latest equipment. Thoroughly experienced instructors. Association with radio industry's largest research laboratories. Tuition costs moderate. Study radio here—thus be ready to grasp your opportunity. Write this very day—before you forget—for new catalog and complete details. RCA Institutes, Dept. RC-5, 75 Varick St., New York City.

A Radio Corporation of America Subsidiary

Radio SERVICE Men . . .

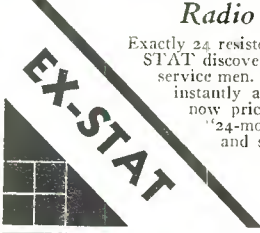Exactly 24 resistor values meet 95% of replacement calls. EX-STAT discovered this and designed the original resistor kit for service men. It puts every value you're ever likely to need . . . instantly at your finger-tips. "Original-equipment" quality—now priced 40% lower than 1931. Do YOU know what the "24-most-used-values" are? Write today for complete details and special introductory offer.



TILTON MANUFACTURING COMPANY
15 East 26th St., New York, Dept. CB
Headquarters for EX-STAT specialties
DESIGNED for radio service men

\$212 Dry Cell Radio Receiver for \$8.50

"Believe it or not" . . . it's true . . . a real give away to clear out the few sets we have left of Model 7 which we made before going into the exclusive manufacture of speakers. Made of finest materials, a wonderful table model. They won't last long at \$8.50. (Less battery and tubes.)

WRIGHT-DeCOSTER, INC., 2215 University Ave. S. E.
Minneapolis, Minn.

"Little Giant" Midget Radio

4 Tubes Pentode
Dynamic Speaker
Beautiful Cabinet
Tone Control

List \$49.50 \$12.95 Complete with Tubes

SERVICEMEN—RMA Resistor Color Code Chart FREE! Write for our Catalogue of Standard Replacement Parts.

STANDARD RADIO CO.
518 So. State St., Chicago, Ill.



AUDIOLA

KNOWN FOR ITS TONE

HIGH GRADE SET BUILDERS SINCE 1921

AUDIOLA RADIO CO. 430 S. Green St. Chicago, Ill.



SAVE SERVICE TIME and MONEY

TRUVOLT RESISTORS, with adjustable clips, mean quicker service and fewer parts to stock. All standard sizes.

175 Varick St., New York, N.Y.
ELECTRAD
INC.

Write Dept. CB-5 for data

NORDEN-HAUCK . . .

ENGINEERS AND PIONEER
RADIO MANUFACTURERS

We are pleased at this time to make a pre-
announcement of new and advanced models:

The CUSTOM IMPERIAL

Admiralty Model-15

SUPER DX-10

Shortwave Receiver

DX-4

Shortwave Converter

For many years Norden-Hauck Radio has been
the acknowledged standard of excellence all
over the world. These new models are the
outstanding NORDEN-HAUCK RADIOS of all
time.

Literature and information will gladly be
sent on request.

NORDEN-HAUCK ELECTRIC & MFG. CO.

Builders of the Highest Class Radio Apparatus in the World

402 CHERRY STREET

PHILADELPHIA, PA.



Moulded Mica Condensers

Dubilier micadons are improved Bakelite moulded
mica condensers. Very compact. Due to special
design and wise selection of materials, electrical
losses are reduced to absolute minimum. All
standard capacities. Tested at 600 volts D.C.

For the Service Man

These units are available in a handy, economical kit con-
taining 36 selected capacities for service work. Regular
prices total \$7.95. In complete kit, the list price is \$6.50.

Write for Catalog 121 describing
Dubilier electrolytic, paper,
mica and other types for all purposes.



DUBILIER Condenser Corporation
4377 Bronx Blvd. New York

LEROY M. E. CLAUSING

Consulting and Designing Radio Engineer

5509½ Lincoln Avenue

Ravenswood 9109

CHICAGO, ILL.

Brief Items

(Continued from preceding page)

ore deposits, the intervening terrain, local interference, nat-
ural interference, seasons, time of day, etc.

II. E. Kline, Buffalo, N. Y.: Please publish in your next
issue in the Brief Items columns the quickest and most effi-
cient way of testing an electrolytic condenser. Ans. To
our knowledge the easiest way to check electrolytic con-
densers would be to apply rated d-c voltage to them and
place in series a d-c milliammeter to read "leakage current."
A shunt should be used on the first check to protect the
meter in case a short circuit exists. Leakage should not be
more than about .2 milliamperes for every 1 mfd capacity.
This is higher than most dry types run.

Henning Laub, Haddon Heights, N. J.: I thought your
list of broadcasting stations and specifications were the
latest. I also find some Canadian and Mexican stations do
not correspond with your data. Also may I suggest that
Radio Call Book Magazine give a page with abbreviations
and symbols used in radio and their explanations. I am en-
joying your magazine very much. Ans. We are sorry that
sometimes our foreign broadcast list is not corrected imme-
diately when changes are made. This is not any fault of
ours, since it is quite difficult to receive the bulletins on
foreign stations as soon as the changes are made. Changes
in the American list are made every month and are a com-
pilation of not less than ten bulletins from several sources.
You will find that the Canadian and Mexican lists have
been entirely revised, and in this issue the entire foreign list
and short wave phone station lists have been thoroughly
checked.

A Canadian reader, Arundel, Quebec, Canada: I agree
with the men who made a few remarks with bricks on page 33
of a recent issue. I agree with one gentleman in regard to
the certain troubles in sets and also the voltage and current
readings. As to the experimenter, I see nothing for him
except to compare curves with some he has drawn himself.
You should have a section named Service Notes for such
letters as the one about the WR-15 set. Then another sec-
tion named "Bricks and Bouquets for This Magazine."
Also why do you not make a schematic on one side of the
paper only and leave the other side for peculiarities of the
radio set? Why not publish a few schematics of the Mar-
coni line of radios, also the Ozarka line? King has made
more radios than the model G, also the Philco battery set
and the Sonora. It would be a good idea to publish a few
old schematics of such receivers as the Radiola 111-A,
RCA portable superheterodyne and Westinghouse super-
heterodyne.

Jerry Davidson, Green Bay, Wis.: In the September
issue of the *Call Book Magazine*, page 31, there was a cir-
cuit drawn pointing out the use of Ohm's law. It so hap-
pens that we have a radio class made up of service men, and
this article was right in step with the subject we were on, so
it was brought in. And there was one point about the draw-
ing about which the class did not seem to agree. That was
the direction of the arrows on the screen grid leads of the
551 tubes. Ans. We can only say that we mention in the
Radio Engineering columns the fact that the arrow direc-
tion is of no consequence in calculations. According to ex-
isting conventions, the arrows are drawn backwards, but if
you consider that the electron flow is opposite to the con-
ventional direction, then they are correct. Either may be
assumed with no effect whatsoever on the results, as long as
the notation is not changed during the course of calculations.

J. W. Schuler, Chicago, Ill.: I should like to know who
(Continued on next page)

Brief Items

(Continued from preceding page)

and where station KDA, Chicago, is located. It gives weather reports for the northwestern parts of the United States and also some kind of time signals. I take your "Call Book" every month and have looked high and low for that call in your magazine and can't seem to find it. Ans. Station KDA broadcasts on a frequency of 350 kc and is located near the Municipal Airport. What you took for time signals was an aircraft beacon signal. In nearby locations the second harmonic is picked up on 700 kc and third harmonic on 1050 kc.

Research engineers of the Westinghouse Electric and Manufacturing Company have perfected an ultra short radio wave, 42 centimeters long, which can be focused into a beam. Since it will penetrate the Heavyside layer, such a beam affords a means of communicating with the Moon, Mars or any other planet.

Electricity has been known since Thales of Miletus rubbed a piece of amber and made it attract light bodies in 600 B. C., according to S. M. Kintner, vice-president of Westinghouse Electric. Theophrastus wrote a treatise on the subject in 300 B. C., and William Gilbert published "De Magnete" in 1600 A. D. "But the past 50 years have produced more knowledge of electricity and its possibilities than all the ages that are gone," according to Kintner.

Dr. Phillips Thomas, Westinghouse research engineer, makes and breaks electric circuits by barking "On" or "Out" into an ordinary telephone mouthpiece after connection has been established by dialing a number. The voice travels over a light beam instead of a wire. Fans and other equipment are operated in the same manner.


J. B. Rostron, Traffic Manager of R. C. A. Communications, Inc., gave out the following statement as a result of published reports that radio communication service between the United States and Shanghai had been disrupted by the fighting in Shanghai:

"Normal service by radio was maintained between Shanghai and the United States continuously. In addition to the main circuit linking Shanghai directly with San Francisco, supplementary transmitters are maintained in the international area of Shanghai giving direct connection with Manila, which has direct connection with San Francisco. This additional safeguard to traffic has not been necessary, as the main circuit has been in operation during the normal traffic hours. The only disruption of the main circuit occurred early one morning, due to a brief interference with the wire line connections between the receiving office in Shanghai and the transmitting station. The wires were repaired quickly and normal traffic via the main circuit was restored before the resumption of business in the United States that morning.

"R. C. A. Communications had handled a greatly increased volume of business between Shanghai and the United States with the beginning of the Shanghai disturbance. Due to the increase in traffic, both the Chinese Government Radio Administration at Shanghai and R. C. A. Communications at San Francisco have placed in service at times second transmitters on the direct circuit, thereby doubling the traffic handling capacity. A large volume of press dispatches has been handled over the main circuit and the American people have been kept advised of happenings from hour to hour by this medium. This is the only direct communications connection between Shanghai and the United States. The circuit, which was placed in operation a little more than a year ago, is one of the longest and most reliable in the world, having installations of the most modern short wave transmitting and receiving apparatus."

(Continued on next page)

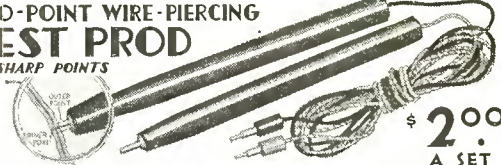NEW! DUO-POINT WIRE-PIERCING TEST PROD
 NO EXPOSED SHARP POINTS



Precision made, using finest materials. Made up to a high standard of quality, not down to a cheap price. 100% meter readings assured. Spade tips available as connector equipment if desired. Specify kind of tips wanted.

\$ 2.00 A SET

Rutherford Electrical Instruments Co.
 SUPERIOR ARIZONA


POLYMET PRODUCTS

Standard of the Industry

Send for the Special Service Men's Catalogue

Polymet Manufacturing Corp.

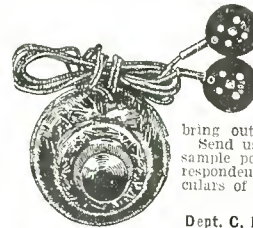World's Largest Manufacturers of Radio Essentials
 839-B East 134th St., New York City




SERVICE MEN AND DEALERS

Get in line for big profits with **FILTERMATIC PRODUCTS**. Take advantage of **FREE** newspaper advertising. The Super-Tone control is not an ordinary tone control, it is designed to suit any circuit, and has several distinctively new features, can be installed in one minute, and allows you a very good profit. Unit installed in an attractive crystalized Gold and Black case. Will bring out the most pleasing tones from any set. List price \$2.50. Send us a check or money order for \$1.25 and we will send you a sample postpaid. Be sure to write your order on your business correspondence to prove you are a Service man or dealer. Write for circulars of other products. Satisfaction guaranteed or money refunded.

FILTERMATIC MFG. CO.

Dept. C. B.

4458 Frankford Ave., Phila., Pa.

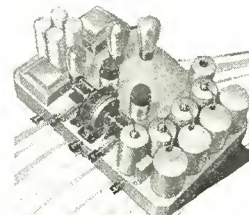

The 15 TO 550 METER
COMET
 SUPER-HETERODYNE


FOR world-wide reception, with quality that will amaze you.

A superbly efficient short-wave receiver, custom-built by Hammarlund. Especially designed to cover also the regular broadcast channels up to 550 meters.

A.C. operated, using eight newest type tubes with Pentode output. Super-sensitive, super-selective, and has remarkably fine tone. Exclusive easy-tuning features.

The perfected receiver for the home, office, laboratory, newspaper, police, airport, steamship.

Write Dept. CB-5 for descriptive folder.

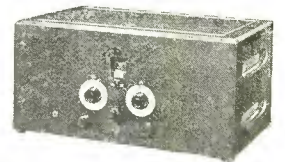

The **COMET**
 14-200 meter "PRO"

Custom-Built High-Frequency Receiver for professional operators. Super-heterodyne circuit. 8 tubes. Efficient band-spread tuning system, with special long-wave oscillator. Phone jack and speaker connections. Connection for external amplifier.

Write for Details

Console for COMET A11-Wave Receiver.



CUSTOM BUILT

HAMMARLUND-ROBERTS, Inc.

424 W. 33rd St., New York

by **HAMMARLUND**

"EXPERIENCE IS A GREAT TEACHER—BUT YOU CAN LEARN MORE FROM BOOKS—QUICKER AND CHEAPER." See below.

WRITTEN by two widely known radio engineers these three books cover every phase of building, repairing and "trouble-shooting" on modern receiving sets. They include complete instructions for building short-wave and television receivers.

Radio Construction Library


[Including Short-wave and Television Receivers]

3 Volumes, 6x9, 993 Pages, 561 Illustrations

This practical Library includes: PRACTICAL RADIO—The fundamental principles of radio, and radio set-building, presented in an understandable manner. Illustrated with working diagrams. RADIO CONSTRUCTION AND REPAIR—Methods of locating trouble and reception faults and making workmanlike repairs. How to construct all types of sets, including television receivers. RADIO RECEIVING TUBES—Principles underlying the operation of all vacuum tubes and their use in reception, remote control and precision measurements. The library is up-to-the-minute in every respect and is based on the latest 1931 developments in the design and manufacture of equipment.

10 Days' FREE Examination!

No Money Down

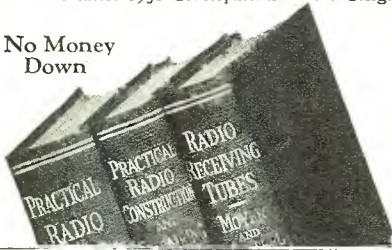

Examine these books free for ten days. You will find them invaluable as a home study course and as a reference in the daily radio problems which you meet in your business. Simply fill in the coupon and the books will be sent to you postage prepaid; there is nothing to pay if they do not prove satisfactory.

FREE EXAMINATION COUPON

McGRAW-HILL BOOK COMPANY, Inc. 330 W. 42nd Street, New York

Send me the new RADIO CONSTRUCTION LIBRARY, three volumes, for 10 days' free examination. If satisfactory I will send \$1.50 in ten days, and \$2.00 a month until \$7.50 has been paid. If not wanted I will return the books.

Name


Home Address

City and State

Position

Name of Company

RCB-5-32

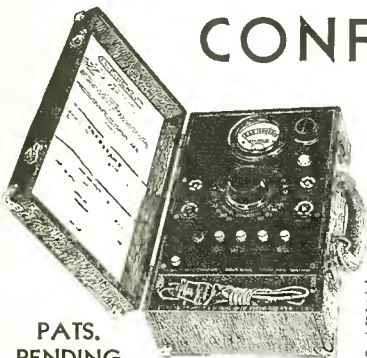

CONFIDENCE

**RADIO TUBE
MERCHANTISING
INTERPRETER
BAD-GOOD-GAS**

The Confidence English Reading Tube Tester is not just a tube tester—it is a selling, merchandising interpreter—it is the most efficient and appealing medium for quick and intensive tube sales. More tubes can be sold by application of the Confidence to sale than by any other known medium. It has appeal. It has "IT". Simple: ABSOLUTELY FOOL PROOF: Every short indicated automatically.

The actual condition of all tubes is told immediately in English to complete satisfaction of all customers.

After 30 minutes use of a Confidence you would not part with it. Try that 30 minute test. In fact we will give you three days' free trial. (See coupon.) We will ship the Confidence to jobbers on two to three weeks' trial. Plan your tube merchandising by using the Confidence which reaches the 75% of public who cannot remove the tubes from their radio to take to a store for test.

Jobbers—take advantage of our trial offer. Compare the Confidence with any other device. See its wonderful internal construction.

Dealers—buy through your jobber or use coupon.

TRIAL OFFER AND DEFERRED PAYMENT PLAN

APPARATUS DESIGN COMPANY, Dept. B, Little Rock, Arkansas.

Gentlemen: Please ship immediately one Confidence Tube Tester for which I will either deposit \$59.50 with the express agent or deposit \$16.50 cash first payment and sign five monthly installment notes of \$10.00 each. If at any time within three days I do not want the Confidence Tester I may return it to the express agent in good condition and receive my money back. I will pay the small transportation charges.

NAME.....
ADDRESS.....

Please attach three trade references 1st and 2nd credit ratings shipped open.
If installment purchase—

\$59.50 Net

Brief Items

(Continued from preceding page)

"Cy Clops" is the name given a new member of the Westinghouse Electric family. Appropriately, Cy has one great eye, right in the middle of his forehead. His head turns and bobs up and down as his scanning orb looks for a fire. When it spots a flame, a stream of extinguisher shoots from Cy's cigar and the fire's out. He's truly a one-man fire department.

Four dozen automobiles can be parked above the ground space occupied by six in the new Westinghouse vertical parking machine. A novel control unit makes parking as simple as pushing a button. As the button is flipped a door to the machine opens. The patron drives on the cradle, moves a small lever that closes the door and gives him a check. Getting the car back is just like retrieving a chapeau from the hat-check girl.

More than 500 engineers visited the Westinghouse works in East Pittsburgh recently to witness a demonstration of the new mercury arc rectifier. Although 3,000,000 times as powerful, this device handled tremendous quantities of electricity as quietly as a small glass tube performs the same service for a radio receiving set.

Engineers of many nations will participate in the International Electrical Congress in Paris, France, in June, 1932, which is a fiftieth anniversary celebration of a similar congress held in 1881, also in Paris.

Recognition of America's important contributions toward engineering and scientific progress is seen in the fact that 22 engineers of the Westinghouse Electric and Manufacturing Company have been invited to prepare technical papers for the Congress.

Plans for the meeting originated with a group of French technical societies in cooperation with the International Electrotechnical Commission, a body organized 20 years ago to handle and direct all technical electrical engineering matters having an international aspect.

Westinghouse men and the subjects they will handle are as follows:

T. D. Yensen, "The Search for Better Ferro-Magnetic Materials."

J. F. Peters, "Measurements of Surges."

F. D. Newbury, "Survey of Progress in Electrical Machinery in the United States."

H. V. Putman, "Transformers."

R. E. Hellmund and L. R. Ludwig, "Commutation and Flashing."

C. L. Fortescue, "Lightning and Its Effects on Transmission Lines."

Joseph Slepian, "The Electric Arc in Circuit Interrupters."

R. D. Evans and C. Wagner, "Stability of Power Systems."

F. H. Shepard, "Railway Electrification."

D. D. Knowles, "The Stroboglow—A New Portable Stroboscope."

E. D. Wilson, "Photoelectric Cells."

W. S. Scott, "Industrial Furnaces."

Frank Thornton, Jr., "Electrical Appliances for the Home."

R. J. Wensley, "Transmission of Signals and Motions." (Supervisory Control.)

D. D. Knowles, "Electric Phenomena in Vacuum Tubes."

A. M. Candy and J. G. Ritter, "Electric Welding."

I. E. Mouroumteff, in conjunction with W. C. White of the General Electric Company, a joint report on "Very Short Waves, Generation and Maintenance by High Frequency Oscillations."

(Continued on next page)

Brief Items

(Continued from preceding page)

C. R. Hanna, "Noise Measuring Instruments."

F. C. Harker, "Electric Power Development in the United States."

While one group of scientists has been perfecting electrical machinery that will run at higher and still higher speeds, another group has been going to the other extreme by perfecting a timing motor that will revolve only twice a day. In fact, according to L. W. Chubb, director of research for Westinghouse Electric & Manufacturing Company, by following the same principles, the speed could be slowed down to once a year or even less, and theoretically there is no limit to the slowness that could be achieved.

Although still in the experimental stage, and not commercially available, the fact that it is practical and workable has been demonstrated in a clock of unique design. The clock has only four moving parts, each of which is necessary to operate one of the hands. The fastest of these revolves only 60 times a minute. If the four points of wear were to be sealed in oil cups and jewels used for bearings as in good watches, the clock should run forever without attention. Such performance, however, would require that electric current never be interrupted. In Chubb's "gearless" clock there are no gear teeth to mesh. The electrical "gears" are held together by magnetism so there is neither wear nor need for lubrication. This prompts the statement that the clock should run forever. The slowest motor in this clock runs but one revolution per minute, and is the speed desired for the second hand.

WGY, the General Electric Company's broadcasting station, is celebrating its tenth birthday with the announcement that it has begun installing at South Schenectady one of the most modern 50-kilowatt broadcasting transmitters in the United States. Approximately three months will be needed to put the transmitter into service, according to the announcement by C. H. Lang, manager of the publicity department of the company, and the work is to be completed by May 8.


This transmitter is designed by General Electric radio engineers for improved operating characteristics, particularly as regards frequency stability, quality of transmission, and continuity of operation. Many of these improvements are being incorporated as a result of the company's experience in operating and maintaining broadcasting transmitters for the past ten years. This experience has continually been used as a basis for continued improvements up to the present time. Throughout the earlier period new design features have been incorporated at WGY for thorough operating tests under actual service conditions before such features were included in transmitters manufactured.

No more than nine other stations on the air today can claim to be as old or to have had as active a part in the development of broadcasting as WGY. In the earliest days of radio experimentation the General Electric Company secured a license to operate a broadcasting station, both to provide a medium for experiments and to promote programs valuable for instruction and entertainment. When the right of WGY to full-time operation and an exclusive channel was threatened, the station's popularity was demonstrated by the thousands of letters from its hearers which poured into the federal radio commission. Through its close association with radio engineering, WGY was able to pioneer in many essential developments—crystal frequency control in the transmitter, the condenser type of microphone, wave propagation tests, and other important adjuncts. From WGY signals of 50,000 watts were heard for the first time—and many listeners feared their receiving sets would be set afire and that their radio tubes would give way under the load.

(Continued on next page)

"I find it Pays to use Jewell Professional Equipment"

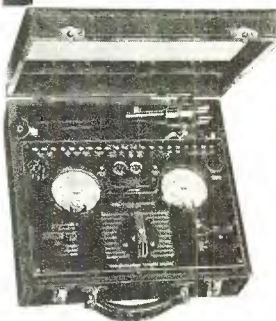
• Experienced radio servicemen find that the high degree of accuracy, convenience, and thoroughly dependable operation of Jewell Service Instruments result in profits that more than offset any saving to be gained by using obsolete or makeshift equipment.



Jewell 444 Set Analyzer

• Socket current and voltage tests on all sets, including those using output and r. f. pentodes. Twenty-four measuring ranges for use with test leads. Triple range output meter. Two range capacity test. Non-shatterable meter glasses. Test cord detachable at analyzer panel. Simplified switching system separates A. C. and D. C. tests. Large, easy-to-read meters with $2\frac{3}{16}$ inch long scales. Panel and over fifty other parts molded of bakelite to assure permanence.

Jewell 563 Test Oscillator

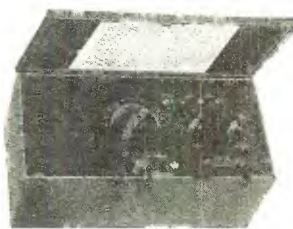

• Three frequency bands: Broadcast, 550 to 1,500 K.C.; low intermediate, 125 to 175 K.C.; and high intermediate, 160 to 280 K.C., covered by fundamental waves. Calibration curves carried in cover. Entire unit, including batteries, shielded by heavy metal carrying case. Separate output for neutralizing. Furnished complete with shielded output lead, batteries, and one '30 type tube. Write for full description of this instrument, the only low priced oscillator that provides frequency coverage for adjusting all popular receivers.

Jewell Electrical Instrument Company,

5 Haynes Avenue, Newark, N. J.

Please send me literature on the Jewell Instruments checked below.

- | | |
|--|--|
| <input type="checkbox"/> Jewell 444 Set Analyzer | <input type="checkbox"/> Jewell 540 Portable Tube-Seller |
| <input type="checkbox"/> Jewell 563 Test Oscillator | <input type="checkbox"/> Jewell 538 Counter Tube-Seller |
| <input type="checkbox"/> Jewell 531 Professional Combination | <input type="checkbox"/> Jewell Panel Instruments |

Name.....

Address.....

Brief Items

(Continued from preceding page)

vertising by radio manufacturers. I note an inquiry in the last issue by R. F. Renaud of Syracuse, N. Y. On a circuit for the new Weston Universal meter. I have designed and am using a circuit that requires only one selector switch and one DPDT switch to get any reading, either a-c or d-c voltages or current. The layout is far cheaper and simpler than any I have ever seen published. How about the set tester you promised the last months? Ans. We are sorry that an error occurred on the diagram concerning the antenna and counterpoise installation about which you ask. The dimension should be in feet and not in inches, which makes it about correct. If you are going to use such an installation for short wave reception, we recommend the inductance as given, but for broadcast it is often found that increasing the turns to give an inductance between 200 and 300 mh gives better results. We cannot give a definite answer because different locations and different receivers react differently. Hence, we suggest a little personal experimentation in these lines will give the required results in addition to some knowledge of the behavior of such a system. The set tester circuit that we had mentioned before appears in the April and May issues.

Stewart Taylor, Memphis, Tenn.: I am sure you will never know what your magazine means to me. I don't believe there is another magazine which can be compared with it. I want to know how to find the correct resistance and condenser capacities in circuits where parts are not marked. Ans. The most convenient way is to use an ohmmeter such as was described on page 28 of the February, 1932, issue, and the capacity meter as described on page 36 of the November, 1931, issue.

Lewis Ceasy Umlauf, Fleetwood Hall, Moon P. O., Mathews County, Va.: I have been subscribing directly for quite some time, but before that, I used to have the magazine sent in by my jobber. In response to queries when renewing previous subscriptions I have indicated interest as that of "experimenter." Now the average experimenter usually uses batteries rather than line current for receiver voltage supply. Of course, I don't know what your reactions are to this class of "bugs," but all with whom I have come in contact are doing as I am, simply not renewing or no longer getting the journal because there is practically nothing in it of any interest to them. For instance, young fellows getting interested in radio ask me for a reference. How can I tell them to be sure to get the *Call Book* when I know there will be nothing in it of any service to them. I am writing bluntly and directly to the point, for it does seem to me that the *Call Book* as now gotten out is a mighty fine piece of work for the regularly employed service man, but not worth a nickel to any other. Battery sets are still built and sold to those who really want results. As a WMAQ man a short time ago said: "Some people think interest is dying out in DX. Well, they should see the volume of inquiries which is sent in with regard to XER." I do not know the WMAQ man, for I never met him that I know of, but just quote him at random, as you may wish to communicate with him. As you probably know, the usual factory set does not satisfy DX demands. Sorrowfully submitted, as like many, many others, I hate to lose the good old *Call Book* of a few years ago. Ans. We should appreciate comments from our interested readers on this letter. Being a DX hound himself, the editor has some of his own ideas on battery sets versus a-c sets, which are quite at variance with those of Mr. Umlauf. Should the demand be great enough for the type of material referred to above, the Editorial Department will include data which will be

ARLAB MIDGET DYNAMIC SPEAKERS
6" AND 8" DIAMETERSR. F. COILS, Shield 1 3/8" diameter x 1 3/8" high.
Smallest and Most Efficient Coil in Years

VOLUME SELECTIVITY DISTANCE

LIST PRICE—50c EACH

Sample set of coils mailed upon receipt of list price and condenser specifications.

ARLAB MFG. CO. 1272 N. Wood St. Chicago, Ill.

MICROPHONES
OF ALL TYPES...

Write for Details

SHURE BROTHERS COMPANY

Manufacturers—Engineers

S. N. SHURE, Pres.

337 WEST MADISON ST. CHICAGO, ILLINOIS

**CANDO HMS**

ARMOURED WIRE WOUND RESISTORS

WILL LOWER YOUR COSTS—MAY WE SAMPLE AND QUOTE

The Muter Company

1255 S. Michigan Ave.

CHICAGO, ILL.

DOOLITTLE & FALKNOR, Inc.

Radio Engineering and Manufacturing

Field Intensity Curves Allocation Engineering

Station and Studio Installations

Engineering Management

1306-8 W. 74th Street

Chicago, Illinois

SPECIAL
INTRODUCTORY OFFER

We need immediately 100,000 users the country over to tell their friends of the improvement of using Pentode tubes in place of 245's, particularly in sets using 245 push-pull.

There is a tremendous improvement in depth of tone and set sensitivity. The improved amplification brings in weak signals.

The Pentode Tube is inserted in Na-ald 954KPC adapter and the adapter put in the socket in the set. No change in wiring.

Money back—Adapters list at \$1.00—But for the first ten people that order from any town we will send two adapters for \$1.00 or—two pentode tubes and two adapters postpaid for \$3.00.

If after trying them in your set, you are not more than pleased with the results, return your purchase anytime within five days and your money will be instantly refunded.


This ad probably will not appear again. Order today.

ALDEN MANUFACTURING CO.
Department C BROCKTON, MASS.**Make a PROFIT**
from Every Service Call

When tubes blow . . . filter equipment fails . . . tone quality suffers . . . install AMPERITE. Automatically regulates line voltage fluctuations, up and down, between 100 and 140 volts to exact requirements.

Easily installed in 5 minutes without chassis changes. Service men make \$90 to \$110 EXTRA per month installing AMPERITE. So can YOU.

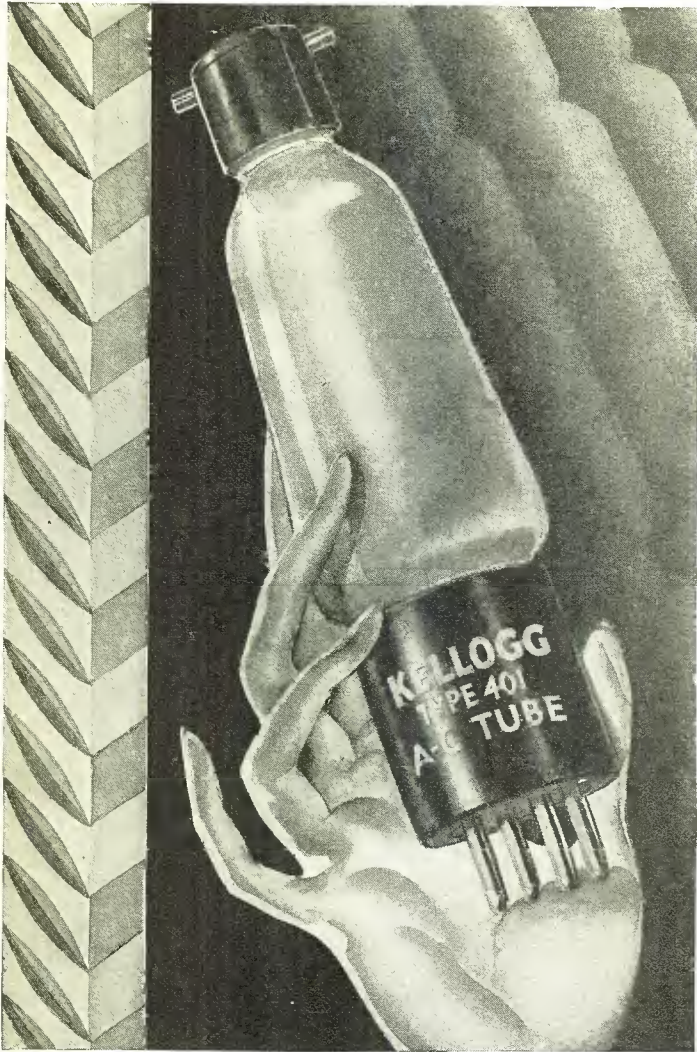**AMPERITE Corporation**
561 BROADWAY NEW YORK**AMPERITE**
Self-Adjusting
LINE VOLTAGE CONTROLWrite Dept. CB-5,
enclosing \$1.62 for
dealer's sample and
sales help



THIS IS A
Profitable TUBE
for DEALERS and JOBBERS

Every customer of yours who owns or operates any of the following sets, must use Kellogg 401 A.C. tubes for replacements. All these set owners are constant buyers.

KELLOGG Sets—510, 511, 512, 514, 515, 516, 517, 518, 519, 520, 521. McMILLAN Sets—26, 26PT. MOHAWK Sets, SPARTON Sets—62, 63, A-C 7. DAY FAN Sets—5143, 5144, 5145, 5148, 5158. MARTI Sets—TA2, TA10, DC2, DC10, CS2, CS10, 1928 Table, 1928 Console. CLEARSTONE Sets—110. And the first A.C. models of the following: Bell, Walbert, Wurlitzer, Pathe, Shamrock, Bush & Lane, Minerva, Crusader, Liberty, Metro, Supervox and Case.

Get your share of business from this profitable market by stocking and displaying Kellogg tubes now. Write Dept. 60 for name of your nearest jobber.

KELLOGG

SWITCHBOARD AND SUPPLY COMPANY

1070 West Adams Street » » » » CHICAGO, ILLINOIS

Brief Items

(Continued from preceding page)

of value to this class of reader, but sentiment along these lines must be definitely proved before material of value is deleted to make room.

Franklin S. Lerch, Schenectady, N. Y.: I bought copies of the December and March issues of RADIO CALL BOOK MAGAZINE. The performance curves of radio receivers published in these issues interested me and I, therefore, am submitting my subscription. With most receivers you give some information about the noise level. However, you omitted this from the Scott All-Wave superheterodyne in your December issue. May I request this information about the minimum and maximum values? My occupation is teaching college mathematics. I feel that your performance curve information on standard receivers is valuable even to the public, as a guide for buying the proper kind of set. I am interested in your magazine for just such a reason. Ans. The noise levels which you request are 79 per cent, the maximum, at 1000 kc, and 46 per cent, the minimum, at 1400 kc. We appreciate your kind words and hope that you will always be a satisfied follower.

Experimental work with the ultra short, 42-centimeter wave, radio beam reveals a new power for such short waves and it is believed the studies will have an important bearing on the commercial development of television.

Electric tubes now sort thousands of cards, bills or checks daily. They simplify the process of taking gold, silver, cement, sulphuric acid, arsenic, coal tar products and other valuables out of smoke and flue gases and they match colors perfectly. Others containing resistances of several billion ohms, make possible the amplification of photo electric currents 10,000 times.

CATHODE RAY TELEVISION

which has finally solved the problems of radio picture transmission

Requires Experienced Men!

A VAST new field is opened wide with the coming of cathode ray television. But only those who KNOW their business will find employment in this new art. A new course of simplified instruction in cathode ray television is ready now. It contains no mathematics . . . nothing that the average radio man cannot understand. It is a personally conducted correspondence course in 10 lessons, prepared by Arthur H. Halloran, Instructor in Television for the Extension Division of the University of California. Cathode Ray television engineers have joined with him in the proper presentation of the heretofore hidden facts. The entire course, by correspondence lessons, costs but ten dollars. \$5.00 brings you the first five lessons, one at a time. Each lesson is corrected by Arthur H. Halloran before the succeeding lesson is mailed to you. Those who desire to enroll in this new non-technical, non-mathematical course should immediately do so. A limited number of enrollments can be accepted now.

ARTHUR H. HALLORAN
430 Pacific Bldg., San Francisco, Calif.

Education by Radio

FORTY authorities on economics, psychology and related fields will speak over a National Broadcasting Company network in its weekly coast-to-coast educational feature for the spring term of 1932.

The speakers will be presented by the National Advisory Council on Radio in Education as a continuation of its "Listen and Learn" lecture series inaugurated last Fall. An economist and psychologist will speak for fifteen minutes each every Saturday over an NBC-WEAF network at 8:30 p. m., E. S. T. The series will continue twenty weeks, closing with a valedictory program the last week in May.

International trade, the tariff and industrial planning will be economic subjects touched upon during the series by James Harvey Rogers of Yale, Ernest M. Patterson of Pennsylvania, F. W. Taussig of Harvard, George Henry Soule, Jr., editor of The New Republic, Walton H. Hamilton of Yale and others.

Changes and growth in personalities, animal behavior and psychology in education will be discussed by Fred A. Moss of George Washington University, Henry W. Nissen of Yale, Frank N. Freeman of Chicago, and others.

Public response to the initial ten lectures broadcast in the Fall has indicated, according to the council, that they reached listening groups in the home, school, special neighborhood gatherings and even remote fishermen of the Nova Scotian coast.

John W. Elwood, NBC vice president who arranged the broadcast series with Levering Tyson, director of the Council, said the series demonstrated what could be accomplished by co-ordinated effort between educators and broadcasters.

"The series has proved that where there is a sincere desire, educators and broadcasters can get along without stepping on each other toes," Elwood said. "It has demonstrated what can come from practical and sensible co-operation and organized effort between the educators and the broadcasters.

"I feel that the broadcasters have learned a good deal about education, and that the educators have learned a good deal about broadcasting technique. It is only the beginning, but it is the first practical research that has been done in radio by educators on a nation-wide scale."

Tyson said the correspondence resulting from the first programs had convinced him that the public welcomes broadcasting that gives authentic information in an interesting way.

Here's the New

HANDY KIT

that gives all the
values you want

WITH 20
RESISTORS



With this Certified Kit in your pocket, you can take care of any resistor problem in any radio set. For besides the 20 most popular values in the kit, you can obtain thousands of others by using the simple formulas that go with it. Here are the ranges in the kit:—

500 ohms	25,000 ohms	200,000 ohms
1,000 "	50,000 "	1/4 meg.
2,000 "	60,000 "	1/2 "
5,000 "	70,000 "	1 "
10,000 "	75,000 "	1 1/2 "
15,000 "	100,000 "	2 "
20,000 "		3 "

This new Certified Kit, with the *new low prices* of I. R. C. Metallized Resistors, has created a sensation in the radio field. It fills a long-felt want among Servicemen. Has speeded up the work of thousands—and will do the same for you. Be sure the gold seal is unbroken, for this kit is **Factory-Sealed, Factory-Tested, Factory-Guaranteed**

The purchase of the kit entitles you to our famous I. R. C. Resistor Replacement Guide (normally costing \$1) **free**—and also our R. M. A. standard Color Code Chart. See your jobber today—or mail the coupon below.

INTERNATIONAL RESISTANCE COMPANY
PHILADELPHIA TORONTO



Metallized
RESISTORS

International Resistance Co.,
2006 Chestnut St., Phila. R-3

Gentlemen:

I enclose check money order for \$3.50, for which please see that I receive your Certified Kit of Metallized Resistors—also your Resistor Guide and Color Code Chart.

Name

Address

City State.....

SERVICE BLUE PRINTS

FOR SERVICE MEN, TECHNICIANS AND EXPERIMENTERS

ACCURATE, clear and dependable drawings of nearly every standard circuit. These schematics are drawn to a large scale and so simplified that the whole circuit may be visualized almost instantaneously. This enables the service man to work rapidly and accurately. There is no need for microscopes or clairvoyance in reading our prints.

No. SR24	A. C. Dayton Navigator	\$.75	No. SR130	Howard SG-B	\$.75
No. SR3	Acme AC7	.75	No. SR145	Howard H	.75
No. SR4	Acme AC4	.75	No. SR118	Jesse French Jr. "G"	.75
No. SR1	All-American Mohawk 6	.75	No. SR77	Kellogg 523	.75
No. SR74	All-American Mohawk 96	.75	No. SR38	Kennedy 10	.75
No. SR165	All-American Mohawk (Lyric) B-7	.75	No. SR48	Kennedy 20	.75
No. SR167	All-American Mohawk (Lyric) S-7	.75	No. SR31	Kennedy 29	.75
No. SR170	All-American Mohawk (Lyric) S-8	.75	No. SR129	Kennedy 30 and 32	.75
No. SR128	All-American Mohawk (Lyric) Model J	.75	No. SR184	Kennedy 52A	.75
No. SR22	Amrad 70 A. C.	.75	No. SR185	Kennedy 56	.75
No. SR44	Amrad 81	.75	No. SR31	King Model J	.75
No. SR106	Amrad 84	.75	No. SR8	Kolster K20; K22; K25 and K27	.75
No. SR191	Apex 10	.75	No. SR45	Kolster K21; K23	.75
No. SR80	Apex 48 Chassis	.75	No. SR72	Kolster K43	.75
No. SR108	Apex Series 31	.75	No. SR159	Kolster 80 and 82	.75
No. SR28	Atwater-Kent 38	.75	No. SR182	Kolster K-90	.75
No. SR51	Atwater-Kent 55 and 55C (Cap. Coupled)	.75	No. SR65	Kyletron 70	.75
No. SR92	Atwater-Kent 55 and 55C (Inductive Coupled)	.75	No. SR124	Majestic 20	.75
No. SR114	Atwater-Kent 66	.75	No. SR178	Majestic 25	.75
No. SR131	Atwater-Kent Super H-2 Chassis	.75	No. SR157	Majestic Chassis 15	.75
No. SR181	Audiola 13-S7	.75	No. SR98	Majestic Super Chassis 50	.75
No. SR79	Audiola 31	.75	No. SR138	Majestic Super Chassis 60	.75
No. SR111	Audiola Super 1931	.75	No. SR7	Majestic 70	.75
No. SR112	Audiola Junior	.75	No. SR55	Majestic 90; 90B; 91; 92 and 93	.75
No. SR12	Bulkeit A	.75	No. SR84	Majestic 130-A	.75
No. SR162	Bosch 7 (D.C.)	.75	No. SR26	Philco 36-82	.75
No. SR193	Bosch 20	.75	No. SR156	Philco 90 and 90-A, Series B	.75
No. SR21	Bosch 28 and 29	.75	No. SR60	Philco 95	.75
No. SR198	Bosch 31 and 32	.75	No. SR172	Philco 112 and 112-A	.75
No. SR73	Bosch 48	.75	No. SR176	Pilot 148	.75
No. SR94	Bosch Auto Radio 80	.75	No. SR104	Radlette F-14	.75
No. SR109	Bosch 83	.75	No. SR127	RCA 18	.75
No. SR117	Bosch 60	.75	No. SR102	RCA 44	.75
No. SR10	Bremer-Tully 7-70	.75	No. SR30	RCA 60	.75
No. SR75	Bremer-Tully 81 and 82	.75	No. SR64	RCA 66	.75
No. SR126	Bremer-Tully S-81 and S-82	.75	No. SR92	RCA 80	.75
No. SR23	Brunswick SKRO	.75	No. SR107	RCA 48	.75
No. SR148	Brunswick 11, 12, 16	.75	No. SR168	RCA Victor R-11	.75
No. SR71	Brunswick S-14	.75	No. SR166	RCA Victor R-50 and R-55	.75
No. SR86	Brunswick 15, 22, 32, 42	.75	No. SR137	RCA-Victor Superette	.75
No. SR164	Brunswick 17 and 24	.75	No. SR115	Sentinel 11; 15; 16; 12 and 12R	.75
No. SR183	Brunswick Chassis E, models 17, 24 and 25	.75	No. SR13	Sentinel 106-B	.75
No. SR78	Clarion 50	.75	No. SR146	Sentinel 108-A	.75
No. SR139	Clarion 80 and 81	.75	No. SR155	Sentinel 111	.75
No. SR29	Colonial 31AC	.75	No. SR123	Sentinel Super Midget 108	.75
No. SR95	Colonial 33 and 34 A. C.	.75	No. SR169	Silver-Marshall A	.75
No. SR160	Colonial 47 and 48	.75	No. SR152	Silver-Marshall D and E	.75
No. SR47	Columba (Chicago) SGS	.75	No. SR148	Silver-Marshall F	.75
No. SR103	Crosley 53 and 54	.75	No. SR153	Silver-Marshall G	.75
No. SR174	Crosley 125	.75	No. SR35	Silver-Marshall 30	.75
No. SR15	Crosley 608	.75	No. SR53	Silver-Marshall 30-B	.75
No. SR16	Crosley 705 Showbox	.75	No. SR82	Silver-Marshall 35-A	.75
No. SR41	Crosley Jewelbox 704B	.75	No. SR144	Silver-Marshall 726 SW	.75
No. SR57	Crosley 40S, 41S, 42S and 82S	.75	No. SR105	Silver Super 36-A	.75
No. SR67	Crosley "Roamio" (Auto Radio)	.75	No. SR140	Silver Midget 78-12	.75
No. SR53	Crosley 77	.75	No. SR27	Slagle (Continental) 9	.75
No. SR133	Crosley 120	.75	No. SR46	Slagle (Continental) R-20	.75
No. SR149	Crosley 121	.75	No. SR25	Sonora Delux 5R	.75
No. SR150	Crosley 124	.75	No. SR180	Spartan 10	.75
No. SR187	Crosley 127	.75	No. SR192	Spartan 15	.75
No. SR11	Daylan 5080	.75	No. SR161	Spartan 25 and 26	.75
No. SR66	Delco Auto Radio	.75	No. SR81	Spartan 600; 610 and 620	.75
No. SR87	Delco Police Short Wave Receiver 3003	.75	No. SR49	Spartan ACS9	.75
No. SR99	Edison R6 and IV	.75	No. SR58	Spartan 931	.75
No. SR49	Edison R4, R5, C4	.75	No. SR63	Spartan 589	.75
No. SR33	Erla DuoConcerto R-2	.75	No. SR36	Splitdorf E-175	.75
No. SR50	Eversady Series 50	.75	No. SR15	Steinite 261	.75
No. SR158	Fada KW	.75	No. SR76	Steinite 70; 80 and 95	.75
No. SR13	Fada 7AC	.75	No. SR132	Steinite 600; 605; 630 and 635	.75
No. SR70	Fada 35 and 35Z	.75	No. SR147	Stewart-Warner 102 A and B	.75
No. SR19	Federal 11	.75	No. SR34	Stewart-Warner 900	.75
No. SR20	Fred-Bisemann NR-80	.75	No. SR62	Stewart-Warner 950	.75
No. SR14	Freshman 2-N-12	.75	No. SR85	Stewart-Warner R-100A, B and E	.75
No. SR92	General Electric II-31	.75	No. SR195	Stewart-Warner R-102A, B, E	.75
No. SR166	General Electric H-32	.75	No. SR134	Stromberg-Carlson 10 and 11	.75
No. SR107	General Electric T-41	.75	No. SR35	Stromberg-Carlson 12 and 14	.75
No. SR137	General Electric S-22	.75	No. SR151	Stromberg-Carlson 19 and 20	.75
No. SR188	General Electric K-62	.75	No. SR18	Stromberg-Carlson 635 and 636	.75
No. SR68	General Motors A	.75	No. SR54	Stromberg-Carlson 846	.75
No. SR154	General Motors S-3-A	.75	No. SR37	Temple 8-60; 8-80 and 8-90	.75
No. SR173	General Motors S-9-A	.75	No. SR125	Temple 861; 881 and 891	.75
No. SR179	General Motors S-10A	.75	No. SR39	Transitone Auto Radio	.75
No. SR32	Gillilan 100	.75	No. SR21	Trav-Ler Model C	.75
No. SR42	Graybar 600	.75	No. SR143	U. S. Radio & Television (Gloritone) 26P	.75
No. SR92	Graybar 700	.75	No. SR39	U. S. Radio & Television 37	.75
No. SR107	Graybar 678	.75	No. SR171	U. S. Radio & Television 99	.75
No. SR96	Grebe Synchronphase All-1	.75	No. SR119	Vitatone 54 (Zaney-Gill Corp.)	.75
No. SR17	Grebe 7AC	.75	No. SR101	Victor Micro-Synchronous R-55; R-39 and RE-37	.75
No. SR59	Grebe SK-1	.75	No. SR81	Victor R-82; RE45 and R52	.75
No. SR40	Gulbransen Nine-in-Line	.75	No. SR92	Westinghouse WR-5	.75
No. SR175	Gulbransen 10 and 13	.75	No. SR107	Westinghouse WR-4	.75
No. SR186	Gulbransen 23	.75	No. SR137	Westinghouse WR-10 and 12	.75
No. SR110	Gulbransen 161	.75	No. SR168	Westinghouse WR-15	.75
No. SR177	Howard AVH	.75	No. SR141	Zenith A, B, C and D	.75
No. SR16	Howard Green Diamond S	.75	No. SR97	Zenith 71; 72; 73 and 77	.75
No. SR163	Howard 0	.75	No. SR43	Zenith 52; 53; 54; 522; 532 and 542	.75
No. SR56	Howard SG-A	.75	No. SR190	Zenith 91 and 92	.75

PUBLIC ADDRESS SYSTEMS

No. SR100	Amer-Tran PA-86	\$.75	No. SR88	Webster (Racine, Wis.) A37-50	\$.75
No. SR90	Silver-Marshall 692	.75	No. SR89	Webster (Chicago) DH-250	.75
No. SR122	Silver 679-B Amp.	.75			

The above drawings are intended for service purposes only and are not suitable for the construction of receivers from miscellaneous parts. They will be sent postpaid by return mail upon receipt of the proper amount. C. O. D. orders not accepted.

CITIZENS RADIO SERVICE BUREAU

508 South Dearborn Street, 7th Floor CHICAGO, ILLINOIS

The story of a service you needed...and how to get it.

HERE'S several million perfectly good receiving sets in operation in these great United States . . . good, if certain vital parts can be replaced quickly, easily and at not too great a cost. Those sets are going to be in operation for a long time to come too, or the folks who own them just aren't going to have any radio.

But, where are those parts to come from? The radio industry has grown up so fast, manufacturers of sets have, necessarily, been vastly more concerned with the production of new models than with service of the old.

And now the time has come when the service men and dealers, on whom the burden of maintenance falls, must have adequate, reliable sources for replacement parts for all those millions of sets . . . many of which are no longer made, by name . . . many more of which are no longer current models.

Replacement Transformers are in the front of these considerations and that's where this organization fits into your scheme of things and begins to help you make money and satisfy your customers.

Since its inception, the transformer units designed and produced by this organization have become the preferred equipment for original installation among radio manufacturers generally. It wasn't long before we



Section of Reserve stock of exact duplicate Replacement Transformers

began to be swamped with requests for this, that and the other transformer for such and such a model of so and so's make. We made 'em and we made so many we decided to *stock exact-duplicate* transformers for a wide range of makes and models of receiving sets so the service man could replace transformers quickly, easily, at a profit to himself and a saving to his customer.

Stancor Replacement Transformers are *exact-duplicates* of the physical and electrical characteristics of the transformers of the sets for which they were primarily designed; properly balanced with other equipment, insure renewal of the original performance of the set. They become an integral part in fact as well as theory.

There is no re-fitting or re-drilling necessary in their installation and there is no unsightly re-wiring to detract from a workmanlike appearance in the completed job.

Dealers and distributors all over the country are prepared to serve you with one, or as many more Stancor Replacement *exact-duplicate* Transformers for practically any model of standard receiving set now in operation, as you may need *from stock*.

Get in touch with your supply house or write direct for the listings and prices of this remarkable new service to the radio industry.



STANDARD TRANSFORMER CORPORATION

Dayton and Blackhawk Sts., CHICAGO, ILL.

GET ONE OF THESE SMOCKS! Made of fine white herringbone weave material, stout and wonderfully made. Fully belted, generous pockets. Embroidered with your name over the upper left hand pocket in two colors on the back. Use the coupon for details.

STANDARD TRANSFORMER CORPORATION
Dayton and Blackhawk Streets, Chicago, Ill.

Let me have listings & prices of Stancor *exact-duplicate* replacement transformers and the details of your smock offer as advertised in Radio Call Book.

Name

Position

Street and No.

City and State

A new training FOR RADIO MEN!



To make real money in radio requires **KNOWLEDGE!** There is no substitute for it—not even practical experience. Our new advanced training is ideally suited for the experienced radio man who wants to equip himself for more important work.

Endorsed by Leaders

Our institute is highly recommended by Radio Service Managers Assn., Howard Radio, American Radio Relay League, etc. Thousands of students testify to our home study methods of instruction in *basic radio engineering*. That is because we teach the "WHY" of radio—the fundamental principles of radio theory.

Write for Booklet

Send for the details of our training. Absolutely free of charge or obligation. But don't put it off—do it now—while you have the time. State whether you are interested in Radio or Television. (Don't write if you have not had at least 2 years radio experience.)

CAPITOL RADIO ENGINEERING INSTITUTE


14th St. & Park Road, N. W.
(Dept. C-14)
Washington, D. C.

INDEX TO ADVERTISERS

	Page
A	
Alden Mfg. Co.....	57
Amperite Corp.....	57
Apparatus Design Co.....	54
Arlab Mfg. Co.....	57
Audiola Radio Company.....	51
C	
Capitol Radio Engineering Inst.....	62
Central Radio Laboratories.....	50
Chromy, Ben J.....	48
Citizens Radio Service Bureau	
Blue Prints.....	60
Subscription Offer.....	64
Clausing, Leroy M. E.....	52
Coyne Electrical School.....	3
D	
Doolittle & Falknor, Inc.....	57
Dubilier Condenser Corp.....	52
E	
Electrad, Inc.....	51
F	
Filtermatic Mfg. Company.....	53
H	
Halloran, Arthur H.....	58
Hammarlund-Roberts, Inc.....	53
I	
International Resistance Co.....	59
J	
J-M-P Mfg. Co., Inc.....	50
Jewell Elec. Instrument Co.....	55
K	
Kellogg Switchboard & Supply Co.....	58
L	
Littelfuse Laboratories.....	56
M	
McGraw-Hill Book Company, Inc.....	54
Midwest Radio Corp.....	49
Muter Co., The.....	57
N	
National Radio Institute.....	5
National Television, Talking Picture and Radio School.....	53
Norden-Hauck Elec. & Mfg. Co.....	52
P	
Pierce-Airo, Inc.....	63
Polymet Mfg. Corp.....	53
R	
RCA Institutes, Inc.....	51
Radio Amateur Call Book, Inc.....	56
Radio Tech. Pub. Co.....	48
Radio Training Assn. of America.....	Second Cover
Radolek Company.....	62
Readrite Meter Works.....	2
Red Seal Sales Co.....	48
Rider Publications, John F.....	Third Cover
Roth Press.....	56
Rutherford Elec. Instrument Co.....	53
S	
Scott Radio Laboratories, Inc., E. H.....	1
Shure Bros. Co.....	57
Silver-Marshall, Inc.....	Fourth Cover
Standard Radio Co.....	51
Standard Transformer Co.....	61
T	
Tilton Mfg. Co.....	51
U	
Universal Microphone Co., Ltd.....	48
W	
Wright-DeCoster, Inc.....	51
Y	
Yahr-Lange, Inc.....	56

RADOLEK

The Radio Serviceman's Supply House

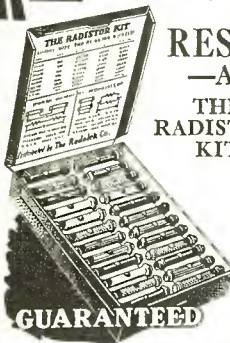

RESISTORS—Every Value You Need! —Always On Hand for Quick Use—

THE RADISTOR KIT Contains 24 of the finest quality, 1 watt carbon resistors that take care of practically every service need.

Kit contains one each of the following resistances: 100; 250; 400; 500; 800; 1,000; 2,000; 3,000; 4,000; 5,000; 6,000; 10,000; 15,000; 20,000; 25,000; 40,000; 50,000; 60,000; 75,000; 100,000; 250,000; 500,000; 1,000,000; 2,000,000 ohms. Can be hooked in series or parallel to provide great range of resistances. Instructions included.

\$2.75 NET

Guaranteed Accurate 10% plus or minus. Most of the resistors are actually within 5% plus or minus. Fine quality insures a first class repair job, and a satisfied customer. Color Code—Each Resistor neatly color coded. No ohm-meter needed to determine value.

COLOR CODE CHART FREE—A Color code chart is furnished FREE with each kit. This chart is a vitally important unit of every well equipped serviceman's kit. Neatly put up in lacquer steel box.

**GREATEST VALUE EVER OFFERED!
ORDER YOURS NOW! GUARANTEED!!**

Send C. O. D. One Radistor Kit at \$2.75 net, plus postage.

Send New FREE, 1932 Service-Man's PARTS CATALOG.



RADOLEK CO.
601 W. RANDOLPH ST.
CHICAGO, ILL.

Name.....
Address.....
City..... State.....

COME TO SUNNY CALIFORNIA



and Learn RADIO-TELEVISION TAKING PICTURES

Come to California where many of the world's most famous Radio Stars make their homes—where the great Laboratories of the American Television Corporation are located—where hundreds of trained Sound Engineers and Mechanics are employed in the Talking Picture Studios and Theatres of Hollywood.

RAILROAD FARE ALLOWED

Don't worry about the expense of the trip. For a limited time we are allowing the railroad fare to Los Angeles from any point in the United States. This is deducted from your tuition, so the trip costs you nothing extra. Take advantage of this opportunity to visit Los Angeles and Hollywood and prepare for a good job at the same time!

PRACTICAL SHOP TRAINING

At the Oldest Trade School in the West

For over 25 years National has been training men by the practical shop method. Over 20,000 ambitious men from all over America have come to National for their training. You'll find National graduates working in the famous Studios of Hollywood, in Talking Picture Theatres, great Broadcasting Stations; for Radio Manufacturers and Dealers; while many have gone into the Radio business for themselves and are making big money as their own boss. What they have done, you can do!

SCORES OF JOBS WILL BE OPEN

10,000,000 Radio sets to be constantly serviced! 600 Broadcasting Stations employing trained Operators and Mechanics! 10,000 Theatres equipped for sound and the job only half done! Eight stations already sending out regular Television programs! New jobs will be opening up every day—hundreds of golden opportunities for the trained man! And you can prepare for them in 4 months at National.

FREE EMPLOYMENT SERVICE

Spare Time Jobs While at School

When you've finished National Training,—four months of practical work in the great National Television, Talking Picture and Radio Shops—then National's Employment Department will assist you in every possible way to get the job you want. And if you're short of money, National will gladly help you get a spare time job to pay your living expenses while at school.

MAIL COUPON FOR BIG FREE BOOK

Get all the facts! Mail coupon below for Big Free Book telling all about National's famous Shop Training and the many jobs opening up in this fascinating field. No cost or obligation. Just mail the coupon!

National Television, Talking Picture and Radio School,
Dept. 437-E, 4006 So. Figueroa St.,
Los Angeles, Calif.

Please send me your big new Free Book on Television, Talking Pictures and Radio, and all details of your Free Railroad fare offer.

Name


Street No.

City..... State.....

ANOTHER DEWALD

"Licensed by RCA"

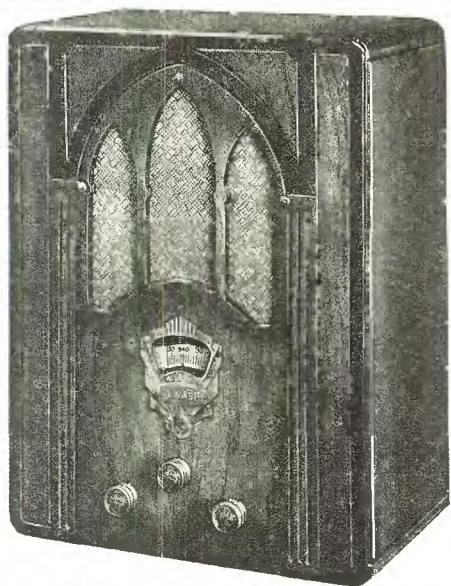ACHIEVEMENT
A DUAL WAVE
SINGLE DIAL
IMPROVED SUPER-HET



A Radio That Will Create New Interest and New Sales

\$49⁵⁰

WITH TUBES

- SINGLE DIAL CONTROL WITH SHADOW-GRAPH TUNING.
- EQUALLY EFFICIENT ON SHORT AS WELL AS LONG WAVES.
- 60 TO 600 METERS WAVE BAND.
- PENTODE VARIABLE-MU.
- AVAILABLE IN EITHER CHASSIS OR CABINET MODEL
- FOR A.C. OR D.C. CURRENT.

Here is real merchandise that will take you out of the "cut throat" class.

There are now available some choice and exclusive territories for factory representatives, distributors and dealers. Send coupon below for full particulars.

PIERCE-AIRO, Inc.

520 Sixth Ave. NEW YORK CITY

Makers of Fine Radios for 11 Years

MAIL THIS COUPON TODAY

Stating whether you are a manufacturer's agent, distributor or dealer. Please send us your proposition.

Firm Name

Street and No.

City State

Get this New and Enlarged Edition of



RADIO SERVICE Schematics

with a

Full Year's Subscription

to

Radio Call Book Magazine and Technical Review

For Only

\$2.50

(Foreign \$3.00—Canada \$3.50)

You Save \$1.50 by this Combination Rate!

If you purchased RADIO CALL BOOK MAGAZINE and TECHNICAL REVIEW on the newsstand each month, the cost would be \$3.00 for a full year; the regular advertised price of RADIO SERVICE SCHEMATICS is \$1.00, so ordinarily these two would cost \$4.00. *Here's your chance to save \$1.50* and obtain the magazines and schematics you are always in need of. Send your order in today!

The New and Enlarged Edition of Radio Service Schematics Contains:

Over one hundred SCHEMATIC WIRING DIAGRAMS of Popular Factory Built Radio Receivers and Power Supplies, carefully drawn by our own expert drafting force.

Laboratory and workshop formulas in simplified form to aid the Serviceman and Engineer.

RECEIVER RESPONSE CURVES showing sensitivity, selectivity and electrical fidelity characteristics, prepared in our own laboratory as specified by the IRE and RMA are given, showing such popular brands as RCA, MAJESTIC, ATWATER KENT, CROSLLEY, SILVER, SPARTON, STEWART-WARNER, BRUNSWICK and others.

CLIP-MAIL NOW!

CITIZENS RADIO SERVICE BUREAU
508 S. Dearborn Street, Chicago, Ill.

Please find enclosed \$2.50 U. S. A. \$3.00 Foreign. \$3.50 Canada, for which send me the new and enlarged edition of RADIO SERVICE SCHEMATICS and enter my subscription to RADIO CALL BOOK MAGAZINE and TECHNICAL REVIEW for one year, starting with the..... number.

Name.....
Address.....
City..... State.....

- Please put a check mark opposite your occupation:
- Dealer
 - Serviceman
 - Engineer
 - Manufacturer
 - Distributor
 - Salesman
 - Technician
 - Experimenter

NOW

KEEP STEP WITH —RADIO SERVICE PROGRESS

Announcing



A NEW MONTHLY MAGAZINE

Dedicated to and Written Expressly for the

RADIO SERVICE MAN

edited by

JOHN F. RIDER

SERVICE, a Monthly Digest of Radio and Associated Maintenance, was born to fill the demand for a magazine devoted solely to radio servicing and intended for distribution among service men only. The service branch of the radio is large and varied and today represents one of the most powerful influences in the entire radio world.

There are many radio magazines—but none written expressly for the Radio Service Technician. This place shall be filled by SERVICE. You—you—and you—earning a livelihood as service technicians do not have time to read long winded, lengthy articles. SERVICE will give you coverage of the entire radio industry and all its branches, broadcast receivers—auto-radio—short wave receivers—refrigeration—public address systems,

etc., in short, brief, but to the point service notes.

In it you will find abstracts of service articles appearing in every radio magazine published in the English language. You will also find an index of articles of interest to Radio Service Men, which have been published in all radio magazines.

The thousands of letters I have received from men who have purchased my various books show that I have given them their money's worth. I assure you, that every subscriber to SERVICE will get his money's worth. You will find this magazine to be of inestimable value in your business and work. You will find it educational—informative—modern—breezy and easy to read.

John F. Rider.

—and the price is LOW! \$1.00 per year in the U. S.

Full size 9x12 inches

Publication date is the 20th of every Month. Sold only by subscription.

COUPON

John F. Rider Publications, Inc.
1440 Broadway
New York City

Here is \$1.00. Enroll me as a subscriber to Rider's NEW magazine SERVICE

Name

Address

City State



YOU

Can Make Money as an Authorized Silver-Marshall Service Station—



SPECIAL DISCOUNTS on 142 Catalog items. Chassis, tuners, amplifiers, all-wave sets, short-wave receivers, converters, speakers, and replacement parts.

SPECIAL RECEIVERS—a line of S-M Bearcat receivers especially for Service Stations.

MERCHANDISING HELP—by the whole Silver-Marshall staff of experts.

INSIGNIA OF AUTHORIZATION—identification card, authorization certificate.

If you have any connection with radio, you ought to have all the details. Send the coupon **NOW**.

If You Are a Radio Dealer » »

and not making the money you should, you ought to know all about the Silver-Marshall line. They are sold **DIRECT TO DEALERS**. The jobber's profit is used in more profit for **YOU** and lower list prices. It is a **COMPLETE** line. Full-size superheterodyne consoles to sell from \$49.95 to \$139.50 complete with Eveready Raytheon 4-Pillar tubes. Silver-Marshall dealers have **EXCLUSIVE** territory. These are some of the reasons why you ought to know about it. Send the coupon for **ALL** the details.



Model C-24. 12 tubes . . . superheterodyne . . . 3-unit construction . . . pentodes in push-pull . . . double tone control . . . built-in tone chamber . . . meter tuning . . . automatic volume control . . . built-in aerial . . . 45-inch door console. The finest receiver made. Complete with Eveready Raytheons . . . \$139.50 list.

SILVER-MARSHALL, Inc.,
6413 W. 65th St.,
Chicago, U. S. A.

Please send me Service Station details.

Please send me Dealer details.

Name.....

Address.....

SILVER-MARSHALL, Inc.

6413 West 65th Street Chicago, Illinois

CANADA
75 Sherbourne Street
TORONTO

EXPORT
41 Water Street
NEW YORK CITY

WEST COAST
S-M Sales Co., 224 E. 16th
Street, LOS ANGELES