

ELECTRONICS ILLUSTRATED

By the Publishers of MECHANIX ILLUSTRATED

NOVEMBER • 35¢

Hi-Fi Special!

ALL ABOUT FM TUNERS


EI LAB REPORTS ON II KITS

Complete specs, performance figures,
construction tips, etc.

PLUS


CIRCUITS FOR MULTIPLEX STEREO FM ADAPTOR

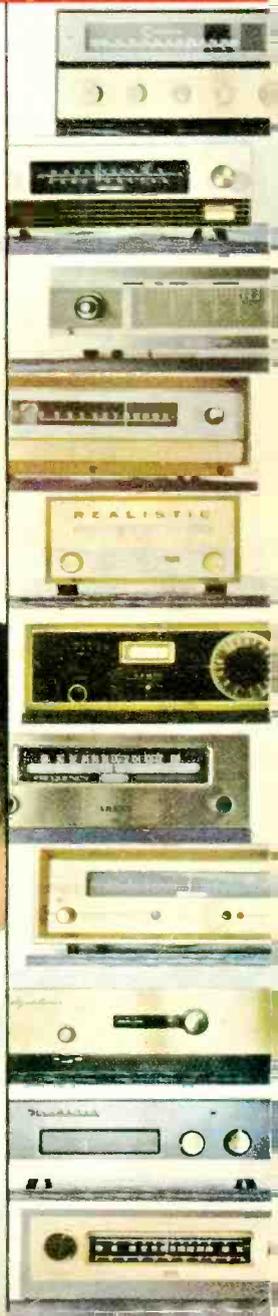Add Automatic Tone Call/Squelch Unit to CB
Build: Frequency Calibrator, Panic Button



al Training Kits tra Charge

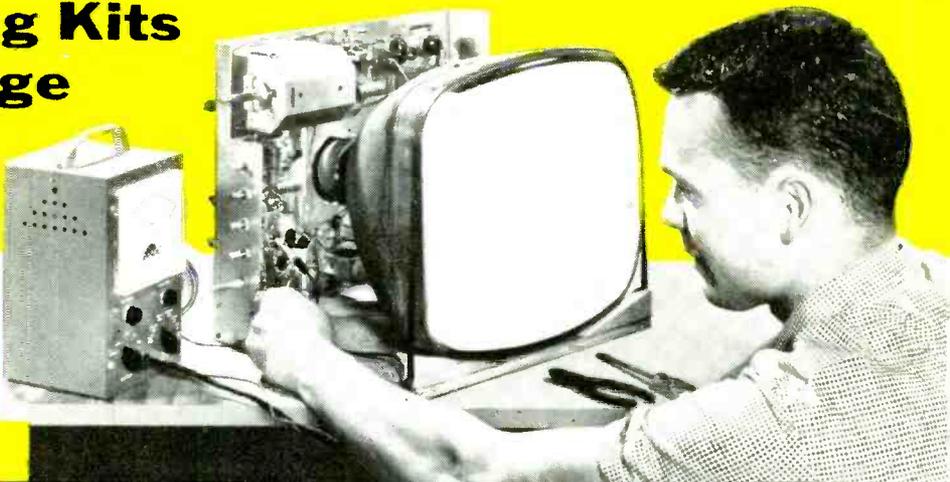practical—based on
ING methods. Be-
ated lessons designed
re—men without pre-
e—you get special
give actual practice,
he things you study.
o keep without extra
le, you get all parts,
icture tube, to build
l vacuum tube volt-
ere. Read course de-
1-PAGE CATALOG.
today.



START AND A BRIGHT FUTURE ONICS Radio Television SPARE TIME

Fast Growing Field of Electronics Needs More Trained Technicians

New developments are creating more and more job opportunities for men with Electronics training, and these are better than average jobs. Take NRI training at home in your spare time. Hold your present job while training. Prepare now for a brighter future.

Added Income in Spare Time Starting Soon

Soon after enrolling we show you how to earn extra money in spare time, repairing sets. Many use this extra money to pay for their NRI course, or buy things they normally couldn't afford. Some have found better paying jobs within a year. Others have started their own businesses.

Train With the Leader—Get Started Fast

NRI is the oldest and largest school of its kind. For 45 years, NRI has featured the best training for beginners—for men without previous experience. Mail postage-free card for 64-page Catalog. Read success stories. See equipment you get. Find out about 60-day trial enrollment offer.

Convenient monthly terms. ACT NOW.

MAIL
CARD
NOW


OLDEST & LARGEST

HOME STUDY

RADIO-TV SCHOOL

National Radio Institute

WASHINGTON 16, D. C. ESTABLISHED 1914

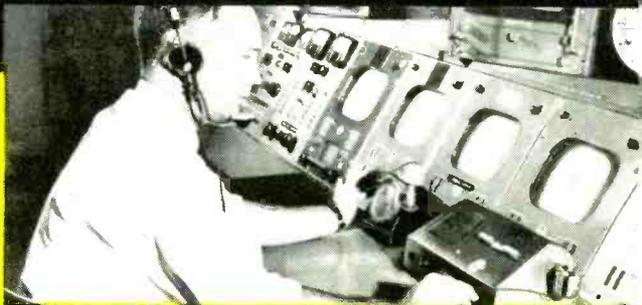

NRI Graduates help build, install, operate and service electronic equipment for the "Space Age" we live in—equipment used in offices, factories, the military. Other are inspectors, laboratory technicians, etc., or work with the Government and Armed Forces.



From Radio-TV Servicing and Broadcasting to missiles NRI graduates share in the gigantic Electronics industry. Interesting jobs await you in studios, on ships and planes in your own Radio-TV business. Mail coupon today.

NRI PREPARES YOU FOR JOBS LIKE THESE.

Electronic Technician • Service Technician • Assistant Engineer
Cameraman • Civil Service Specialist • Computer Technician
Computer Programmer • Designer • Field Technician • Field Maintenance Man • Plant Parts Inspector • Instrument Technician • Laboratory Technician • Radio Operator • Transmitter Engineer • Airlines Technician

NOW - MAKE PEOPLE LISTEN THE MOMENT YOU START TO TALK!

Take This Remarkable "Pocket" Course in Persuasive Speaking for only **10¢** to help cover postage and handling

**AS YOUR INTRODUCTION TO THE NELSON DOUBLEDAY
MONTHLY PROGRAM FOR DEVELOPING YOUR PERSONAL ASSETS**



Learn how to get your ideas across in any business meeting



Learn how to sell yourself, your service, your product



Speak out confidently before club and civic groups

THE ability to speak well is one of the most valuable skills you can own. This compact self-trainer course can make you a more confident, more effective speaker *within the next 30 days!*

In a unique new 64-page book, Dr. David Guy Powers gives you a magical formula for expressing your ideas clearly and convincingly—for standing up and speaking out in any group without hesitation or embarrassment—for using the gift of speech to get more out of life in every way. With this booklet comes one of the most remarkable self-instruction devices of recent years: a set of pocket-size "learn by doing" cards that build speech mastery *right into your daily life*. You actually get the "feel" of being a poised and persuasive speaker in the first ten minutes of use.

Whether you need to speak to one person or a hundred, in private interviews, business conferences, club or civic meetings, the speaking ability you acquire through this course will make every speaking opportunity a stepping-stone to success and popularity. And it is yours for *only 10 cents*, as a demonstration of an extraordinary new development program for men who want to get ahead faster. This plan is remarkable for its low cost, remarkable for its rapid results.

The Nelson Doubleday **PERSONAL SUCCESS PROGRAM**

HERE is the most practical, far reaching plan ever devised to help men increase their earning power and enjoy the good things of life. This brand-new Program shows you how to develop the personal skills and techniques that pave the way to advancement in any field.

Your introductory "Pocket" Course in Persuasive Speaking for 10¢ is a sample of the practical self-improvement package you receive each month. Each "pocket" course — prepared by business and psychological experts — is a short cut to mastery of an essential "success" subject in the Program. There is nothing like it for completeness, authority, practical usefulness.

What Are These Success Skills?

Look at some of the highest paid men in business. They have developed the basic abilities that always pay off . . . the ability to handle people . . . to speak and write effectively . . . to create ideas and "sell" them to others . . . to organize their time efficiently and achieve more. They have learned to understand business procedures . . . how to keep well informed . . . to win important new friends wherever they go. And they are just naturally sought

after whenever a responsible job is to be done.

Now, for the first time, the Personal Success Program offers you a tested, rapid, fascinating plan for making these "success" skills your own—using only a few minutes a day. The cost is amazingly low!

Unique "Live" Practice and Application Material

The Program covers every subject of value to the man who, regardless of his present position or training, wants to get ahead faster. Each subject is brought to you in a monthly package consisting of self-instruction booklet, and "real life" application material that brings results you can see from day to day. These unique cards—a new dimension in self-teaching—will not be found even in courses costing hundreds of dollars!

Mail Coupon with only 10 Cents

Accept this unusual "sample" offer. There is no obligation. If delighted with your first self-training course and wish to continue, you will receive a new package each month, for which you will pay, not the many dollars that most courses on these subjects would cost, but only \$1, plus small shipping cost. No minimum purchase requirement; stop whenever you like. No salesman will call. Personal Success Program, Garden City, N. Y.

**SEND ONLY 10c TODAY
STOP WHEN YOU LIKE**

**Nelson Doubleday Personal Success Program
Dept. I-ET-X, Garden City, New York**

I enclose 10 cents to help cover shipping charges. Send me at once my introductory package containing 1) handbook "How to Say a Few Words Effectively" 2) Practice and Application Cards, plus Pocket Card Holder 3) desk-top File Case.

After trying these materials, I will write within ten days if I do not wish to continue with the Personal Success Program. If I do continue, you will send me a new "Success Course" every month and bill me only \$1 each plus a few cents shipping. I may cancel my membership any time I wish simply by writing to you.

PRINT

NAME

ADDRESS

CITY &

ZONE

STATE

29-PS-30

Same offer in Canada: Personal Success Program, 105 Bond Street, Toronto 2. Offer good in U.S.A. and Canada only.

EXTRA! Self-Scoring APITUDE TEST Included

As part of your introductory package, you receive a complete 32-page self-evaluator that scientifically reveals to you your present aptitudes, vocational interests, "hidden potential."

ELECTRONICS ILLUSTRATED

ROBERT G. BEASON Editor
 Larry Klein Technical Editor

Murray Cooper Art Editor
 Elaine E. Sapoff Editorial Assistant

CONTRIBUTING EDITORS

Robert Hertzberg, W2DJJ Amateur Radio
 Len Buckwalter, 1W5733 Citizens Band
 C. M. Stanbury II SWL-DX
 Harvey Pollack Special Projects

Richard A. Markoff, M.D. Medical Electronics
 Harry Kolbe Audio
 John Milder Audio
 David Muirhead Audio

November, 1961

A Fawcett Publication

Vol. 4, No. 8

In This Issue:

EI's Special Report on FM TUNER KITS	29
---	----

Special Features

Circuits for Stereo Adaptors	Harry Kolbe	44
A High School Student's Radio Telescope	H. Mark Wahl	52
High-Flying Ham	Robert Hertzberg, W2DJJ	56
Phasing Stereo Headphones		63
Should You Go West?	James Joseph	66
New Rules for CB	Len Buckwalter, 1W5733	72
The Incredible Basement of Radio	Tom Kneitel, 2W1965	75
Europe's Top TV DXer		86
Pigskin Electronics	Alan D. Haas	92
The B-70's Invisible Flight		98

EI Projects

Dual Frequency Calibrator	Herbert Friedman, W2ZLF	49
Repair That Microphone	David Herman	64
Panic Button	Fred Maynard	78
CB Tone Call/Squelch	Morris Goodman, 2W1855	82

EI Kit Report

Heath IM-10 Vacuum-Tube Voltmeter	88
---	----

Regular Departments

Feedback from Our Readers	4	
Electronics in the News	6	
Electronic Marketplace	14	
Electronic Brain	46	
CB Corner	Len Buckwalter	47
EI's Electricity Contest		48
The Listener	C. M. Stanbury II	54
Good Reading	John Milder	55
Hi-Fi Doctor: Stereo Straight to Your Ears		70
Hi-Fi Clinic: Souping Up a Lemon		71
Ham Shack	Robert Hertzberg	74
Hi-Fi Record Guide: Basic Library for Beginners II	Warren DeMotte	91

Ralph Daigh Editorial Director
 James Boynton Advertising Director
 Al Allard Art Director
 Ralph Mattison Associate Art Director
 George H. Carl Production Director
 Larry Elsinger Editor-In-Chief
 Phyllis Bendremer Production Editor
 Benita Rockwood Asst. Production Editor
 John F. Webster Advertising Manager

ELECTRONICS ILLUSTRATED is published bi-monthly by Fawcett Publications, Inc., Fawcett Place, Greenwich, Conn. W. H. Fawcett, Jr., President; Gordon Fawcett, Secretary and Treasurer; Roger Fawcett, General Manager; Roscoe K. Fawcett, Circulation Director; Donald P. Hanson, Assistant General Manager.

EDITORIAL AND ADVERTISING OFFICES: 67 West 44th Street, New York 36, N. Y.
 ADDRESS ALL MAIL: Subscriptions, change of address, Form 3579 to Subscription Dept., Fawcett Bldg., Greenwich, Conn.; and all editorial and advertising to Fawcett Publications, Inc., 67 W. 44th St., New York 36, N. Y.

Second-class postage paid at Greenwich, Conn., and at additional mailing offices.
 Subscription price \$4.00 for 12 issues in the U. S. and possessions and Canada. All other countries \$6.00 for 12 issues. Foreign subscriptions and sales should be remitted by International Money Order in U. S. funds payable at Greenwich, Conn.

Printed in U.S.A. Copyright 1961 by Fawcett Publications, Inc.
 Permission hereby granted to quote from this issue of this magazine on radio or television provided a total of not more than 1,000 words is quoted and credit is given to the title of the magazine and issue, as well as the statement, copyright 1961, by Fawcett Publications, Inc.



JOIN THE MEN LIKE YOURSELF WHO ARE NOW ABLE TO SAY—

"Imagine Me Making \$3 to \$5 an Hour in My Spare Time... Fixing Electric Appliances!"

Do you realize that **FOUR HUNDRED MILLION** appliances are in use right now in American homes — and that these are increasing by the millions every year? No wonder that men who know how to service them properly are making \$3 to \$5 an hour — in spare time or full time! **FREE BOOK** tells how you can quickly and easily get into this profitable field.

STOP AND THINK for a minute about your present job and future. Are you making enough money? Are you happy in your work? Can you bank on a steady income — in good times or bad?

Now you can have the answer to these money and job worries, once and for all. Get in "on the ground floor" of a booming industry — servicing electrical appliances. The coming of the auto created a multi-million dollar service industry, the auto repair business. Now it's happening in the electrical appliance field. But with this important difference: anybody with a few simple tools can get started in it!

Why the Boom in Appliances Means Money in Your Pocket

In addition to the 400 MILLION appliances already in use, this year alone will see sales of 76 million new appliances! For example, 4,750,000 coffee makers, 2,000,000 room air conditioners, 1,425,000 clothes dryers. A nice income awaits the man who can service

such appliances. That man can be you! Even if you don't know a volt from an ampere now, you can soon be making \$3 to \$5 an hour in your spare time.

The NRI training in Servicing Electrical Appliances tells you everything you need to know, right from the basic fundamentals about electricity. And your training will cost less than 20¢ a day.

Your Skill Always in Demand — "Set Up Shop" Anywhere

People need their appliances fixed in good times or bad. Once word gets around that you are trained to service them properly, you'll have plenty of work.

You need only the few basic tools that you may already have — and an Appliance Tester which we provide at no extra charge. You can work in a corner of your basement or garage. If you like, you can open up your own shop. And you can save money by fixing your own appliances. Mail coupon for Free Book telling how you can "cash in" on the big opportunities open.



EARN WHILE YOU LEARN with this

APPLIANCE TESTER

Yours—AT NO EXTRA CHARGE

Your NRI Course comes complete with all the parts to assemble a sturdy, portable Appliance Tester that helps you earn while you learn. Easy-to-follow manual tells how to assemble and use the Tester right away. Locate faulty cords, short circuits, poor connections, etc. in a jiffy; find defects in house wiring; measure electricity used by appliance; many other uses.

With this Tester you save time and make money by doing jobs quicker, making sure appliances operate correctly after repairs.

FREE BOOK and SAMPLE LESSON

Our 24-page Free Book tells about America's "Electrical Appliance Boom" — how we train you to "cash in" on it. Free Sample Lesson shows how simple our instruction is — how it can quickly prepare you for a profitable future. Mail coupon to: National Radio Institute, Dept. KM1, Washington 9, D. C. (No obligation — and no salesman will call on you.)



Earns \$510 in One Month's Spare Time

"In one month I took in approximately \$648 of which \$610 was clear. I work only part time. I do a lot of service calls on ranges, dryers, and other major appliances. The NRI course has been priceless to me." — Earl Reid, RFD 1, Thompson, Ohio



His Business a Success

"Since taking your course I have opened up a small repair shop. At present I am operating the shop on a spare time basis — but the way business is growing it will be a very short time before I will devote my full time to the shop." — J. G. Stinson, 1308 Fosssettta St., Long Beach, Cal.



More Than Doubled Cost of Course

"Had practically no knowledge of repair work. Now I am busy almost all the time with more and more work coming in. Have my shop in basement. I have more than doubled amount training cost me." — John D. Pettis, 172 N. Fulton, Bradley, Ill.

NATIONAL RADIO INSTITUTE
Dept. KM1, Washington 9, D.C.

Tell me how I can "cash in" on the "Electrical Appliance Boom." Send me your illustrated FREE BOOK that outlines the whole NRI Course, tells what opportunities are open to me, answers my questions, describes success of other students, and much more. Also send me the FREE SAMPLE LESSON, so I can see how clear and easy your instructions are. I am particularly interested in:

Spare Time Earnings Business of My Own Better Job

I understand there is no obligation on my part; and no salesman will call on me.

Name.....
(PLEASE PRINT PLAINLY)

Address.....

City..... Zone..... State.....

Accredited Member National Home Study Council



Write to: Letters Editor, Electronics Illustrated,

67 West 44th St., New York 36, N. Y.


● New Look

That New Look in your September issue really is something new. I like it. The contents is not bad, either. What are you trying to do, have something for *everybody* interested in electronics?

William Matthews
Tulsa, Okla.

Yes. And thanks for writing, Bill.

● Small Point

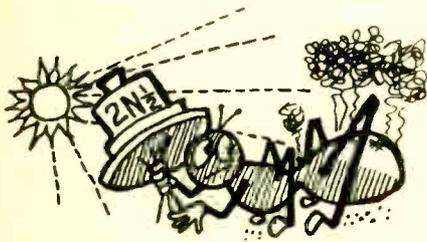

I'm getting sick of all those miniaturization pictures. Every day you see a picture of a transistor dropped through a soda straw, a capacitor sitting on a gnat's wing or a resistor getting lost under its designer's hangnail. My company is doing a promotion on its transistor, 2N $\frac{1}{2}$, that should end all the nonsense. Our lead picture shows an ant using the 2N $\frac{1}{2}$ as a parasol, except the thing is so small that he's getting a sunburn.

Sid Prescott
Houston, Tex.

● Young Fan

I am 12 and I read your magazine every month. I think you have better projects than anybody else in your field. I built your metal detector (April '61 EI) and it works fine.

Marc Finkelstein
Bronx, N. Y.

Congratulations, Marc!


● Swap Shop

It bugs me that other people are looking for old radio parts when that is what I have and wish I had modern equipment. I obtained a whole flock of old tubes (CX-310, SX-200-A, 27, 24, etc.) from a dealer's attic, and also got some pieces of equipment from his shelf. He went out of business in 1929. Anyone want to swap new for old?

Martin Wendell
Burr Oak, Mich.

Do any of EI's readers want antique tubes? Write directly to Mr. Wendell at the address above.

● DC Power Supply

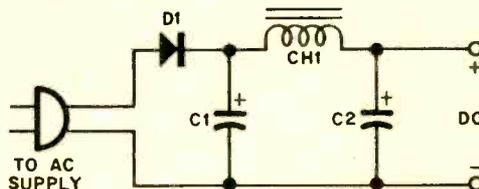

In your January 1961 issue you reported on the Olson T-281 variable AC 500-watt power supply.

In the article you stated that by adding a rectifier and filter network you could convert the T-281 to a DC power supply up to 175 volts.

Can you give me the circuit, plus a list of the parts needed?

Walter F. Lynch
Syracuse, N. Y.

Glad to, Walt. Take a look at the schematic above. Here is the parts list: D1 is a 130 v., 750 ma silicon rectifier; CH1 is a choke of 1 to 10 henries, 200 ma or higher; C1 and C2 are 20 to 40 mf, 250 v. electrolytic capacitors. The rectifier is plugged into either of the unit's two AC outlets. As mentioned in our report, the Olson unit has an AC output adjustable to 140 v. at 500 w. DC output can be run up to about 175 v.

INTERNATIONAL CORRESPONDENCE SCHOOLS



BOX 06057J, SCRANTON 15, PENNA.

In Hawaii reply P.O. Box 418, Honolulu

Without cost or obligation, send me "HOW TO SUCCEED," the opportunity booklet about the field I have indicated below, and a sample lesson.

Name of the course in which you are interested _____

Your Name _____ Age _____ Home Address _____

City _____ Zone _____ State _____ Working Hours _____ A.M. to _____ P.M.

Occupation _____ Canadian residents send coupon to I. C. S. Canadian, Ltd., Montreal, Canada
(Special low monthly rate to members of U. S. Armed Forces)

Cast your ballot for a successful future!

249 I.C.S. COURSES



I. C. S. is the oldest and largest correspondence school. 249 courses. Business, industrial, engineering, academic, high school. One for you. Direct, job-related. Bedrock facts and theory plus practical

application. Complete lesson and answer service. No skimping. Diploma to graduates.

Send for the 3 free booklets offered here and find out how I. C. S. can be your road to success.

ACCOUNTING

Accounting
Auditing
Cost Accounting
General Accounting
Junior Accounting
Practical Accounting
Public Accounting

ADVERTISING

Advertising
Magazine & Newspaper
Advertising

ARCHITECTURE AND BUILDING CONSTRUCTION

Architectural Drawing & Designing
Architectural Interiors
Architecture
Building Contractor
Building Contractor with Drawing
Building Estimator
Building Maintenance
Carpenter-Builder
Carpentry & Millwork
House Planning
Lumber Dealer
Mason
Painting Contractor
Reading Arch. Blueprints
Reading Struct. Blueprints

ART

Advertising Layout & Illustration
Amateur Artist
Commercial Art
Commercial Cartooning
Fashion Illustrating
Figure Drawing & Painting
Magazine Illustrating
Show Card & Sign Prod'n
Show Card Writing
Sign Painting & Designing
Sketching & Painting

AUTOMOTIVE

Auto Engine Tune-up
Automobile
Automobile Body Rebuilding and Refinishing
Automobile Electrical Technician
Automobile Technician
Diesel Engines

Diesel-Gas Motor Vehicle Engines
Gas Engines
Internal Combustion Engines

AVIATION

Aero-Engineering Technology
Aircraft & Engine Mechanic
Aircraft Mechanic
Aviation Engine Mechanic

BUSINESS

Business Administration
Business Correspondence
Business Law
Business Management
Business Management & Marketing
Business Management & Production
Business Psychology
Canadian Business Management
Clerk-Typist
Commercial
Condensed Business Practice
Federal Tax Course
Managing a Small Business
Marketing
Office Administrative Engineering
Office Management
Professional Secretary
Programming for Digital Computers
Purchasing Agent
Retail Business Management
Shorthand
Stenographic
Typewriting

CHEMICAL

Analytical Chemistry
Chemical Engineering
Chemical Engineering Unit Operation
Chemical Laboratory Technician
Elements of Nuclear Energy
General Chemistry
Industrial Analytical Chemistry
Industrial Chemistry
Professional Engineer—Chemical

PULP AND PAPER

Paper Making
Pulp & Paper Engineering

Pulp & Paper Making
Pulp Making

CIVIL ENGINEERING

Bridge & Building Foreman
Civil Engineering
Construction Engineering
Highway Engineering
Mine Surveying & Mapping
Principles of Mapping
Principles of Surveying
Professional Engineer—Civil
Railroad Engineering
Roadmaster
Sanitary Engineering
Section Foreman
Sewage Plant Operator
Structural Engineering
Surveying and Mapping
Water Works Operator

DRAFTING

Aircraft Drafting
Architectural Drafting
Drafting & Machine Design
Electrical Drafting
Electrical Engineer Drafting
Electronic Drafting
Industrial Piping Drafting
Junior Mechanical Drafting
Mechanical Drafting
Sheet Metal Drafting
Structural Drafting

ELECTRICAL

Elec. Appliance Servicing
Electrical Contractor
Electrical Eng'g (Power Plant option—Electric option)
Electrical Engineering Tech.
Electrical Instrument Tech.
Electric Motor Repairman
Illumination Eng'g Tech.
Industrial Electrical Techn.
Power-House Engineering
Power Line Design and Construction
Practical Electrician
Practical Lineman
Professional Engineer—Electrical
Reading Electrical Blueprints

HIGH SCHOOL

Good English
High School Business
High School College Prep (Arts)

High School College Prep (Engineering & Science)
High School General
High School Mathematics
High School Secretarial
Modern Letter Writing
Short Story Writing

LEADERSHIP

Industrial Foremanship
Industrial Supervision
Personnel-Labor Relations
Supervision

MATHEMATICS

Mathematics and Mechanics for Engineers
Mathematics and Physics for Engineers
Mathematics and Physics for Technicians

MECHANICAL

Industrial Engineering
Industrial Instrumentation
Junior Mechanical Engineering
Mechanical Engineering
Professional Engineer—Mechanical
Quality Control
Introductory Technical Writing

PETROLEUM

Natural Gas Production & Transmission
Oil Field Technology
Petroleum Production
Petroleum Prod'n Eng'g
Petroleum Refinery Operator
Petroleum Refining
Petroleum Technology

PLASTICS

Plastics Technician

PLUMBING, HEATING, AIR CONDITIONING

Air Conditioning
Air Conditioning with Draw'g
Air Conditioning Maintenance
Domestic Heating with Oil & Gas
Domestic Refrigeration
Heating
Heating & Air Conditioning with Drawing

Heating, Drawing & Estimat'g
Plumbing
Plumbing, Drawing & Estimating
Plumbing & Heating
Plumbing & Steamfitting
Practical Plumbing
Refrigeration
Refrigeration & Air Conditioning
Steamfitting

RAILROAD

Air Brake Equipment
Car Inspector & Air Brake Diesel Electrician
Diesel Engineer & Fireman
Diesel Locomotive Diesel Machinist
Railroad Administration
Railroad Car Repairer

SALESMANSHIP

Creative Salesmanship
Real Estate Salesmanship
Retail Merchandising
Retail Selling
Sales Management
Salesmanship
Salesmanship & Sales Management

SHOP PRACTICE

Boilermaking
Electric Welding
Foundry Practice
Gas and Electric Welding
Gas Welding
Heat Treatment of Metals
Industrial Metallurgy
Machine Shop Inspection
Machine Shop Practice
Machine Shop Practice & Toolmaking

Metallurgical Engineering
Technology
Physical Quality Control of Metals
Practical Millwrighting
Reading Shop Blueprints
Resistance Welding Technology
Rigging
Safety Engin'g Technology
Sheet Metal Worker
Tool Design
Tool Engineering Technology

Toolmaking
Welding Engineering
Technology

STEAM AND DIESEL POWER

Combustion Engineering
Power Plant Engineering
Stationary Building Eng'g
Stationary Diesel Eng'g
Stationary Diesel-Electric Engineering
Stationary Fireman
Stationary Steam Eng'g
Steam Engine Operation

TEXTILES

Carding and Spinning
Carding
Cotton Manufacturing
Cotton Warping & Weaving
Dyeing & Finishing
Hosiery and Circular Knitting
Loom Fixing
Spinning
Synthetic Fabric Manufacturing
Synthetic Throwing, Warping & Weaving
Textile Designing
Textile Engineering
Textile Mill Supervisor
Woolen Manufacturing
Worsted Manufacturing

TRAFFIC

Motor Traffic Management
Railroad Rate Clerk
Traffic Management


TV-RADIO-ELECTRONICS

Gen'l Electronics Technician
Industrial Electronics
Practical Radio-TV Eng'g
Radio Operating
Radio Servicing
Radio Servicing with Practical Training
Servicing Electr'n Equip't
Servicing Sound Equip't
Practical Telephony
Telephony and Radio Communications
TV Receiver Servicing
TV Technician

For Real Job Security—Get an I. C. S. Diploma! I. C. S., Scranton 15, Penna.

Accredited Member,
National Home Study Council

...electronics in the news

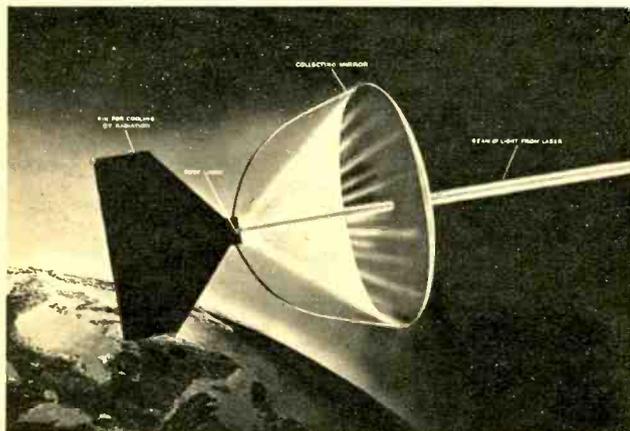

Heliograph, Modern Version . . . Yet another system of jam-proof light-beam communication for outer space is being developed in the laboratories of the American Optical Co., Southbridge, Mass. The unique feature in this system is that it is sun-powered. Its heart is a ruby laser (a term derived from Light Amplification by Stimulated Emission of Radiation), which is to be located at the focal point of a large solar collecting mirror. This system is somewhat like a

searchlight in reverse. The immense energy focused on the ruby rod causes it to emit a thin beam of light which can be modulated for communication. Both satellites and moving space vehicles may make use of the system, which is to have a range in the millions of miles.




Baby Talk . . . Electronics has extended itself further into the field of obstetrics. A team of doctors at Marion County General Hospital and Indiana University Medical Center has perfected a device that picks up the heartbeat of an unborn baby several hours before delivery and instantly reveals any fetal distress that may occur. Electrodes are attached to the patient's body as well as to the fetus. The signals are monitored visually on an oscilloscope and audibly through an amplifier. A tiny radar-like blip keeps popping up on the screen, while a meter indicates the heartbeat rate. But it doesn't tell whether it's a boy or girl.



Moonshine . . . Sunlight is strong enough to actuate even the crudest of photocells, whereas moonlight is too weak to make any impression on the most sensitive. In an effort to make use of the moon's reflection, the Thomas J. Watson Research Center of IBM has developed a new cell sensitive enough to respond appreciably to moonlight, yet rugged enough to withstand direct sun rays. This new Moonlight Photodetector is an unusual combination of a silicon semi-conductor in a liquid electrolyte of sulphuric acid. The process is being developed primarily for the optical sensing systems of satellites, enabling scientists on the ground to keep better track of space flights anywhere in the solar system.

[Continued on page 10]

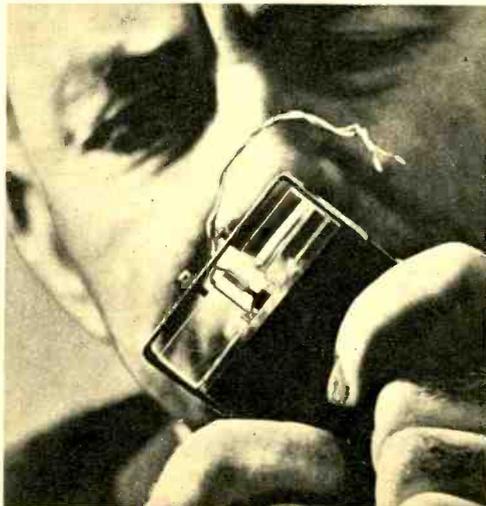

Now! Work Over
300 PRACTICAL
PROJECTS with these
PARTS AT HOME!

to help You learn
ELECTRONICS
RADIO - TELEVISION - RADAR

NOW . . . at home in your spare time you can get the very kind of training and subsequent Employment Service you need to get started toward real earnings in one of today's brightest opportunity fields—TELEVISION-RADIO-ELECTRONICS. Now that Electronics is entering so many new fields, here is a chance of a lifetime to prepare to cash in on its remarkable growth.

DeVry Tech's amazingly practical home method enables you to set up your own HOME LABORATORY. You spend minimum time to get maximum knowledge from over 300 practical projects, using the same type of basic equipment used in our modern Chicago and Toronto Training Centers!

DeVry Tech Provides EVERYTHING YOU NEED . . .

—to help you master TV-ELECTRONICS. In addition to the home laboratory and easy-to-read lessons, you even use HOME MOVIES—an exclusive DeVry Tech series. You watch hidden actions . . . see electrons on the march. Movies help you to learn faster . . . easier . . . better.

EARN WHILE YOU LEARN

DeVry Tech's practical training helps you toward spare time income servicing Radio and Television sets.

LABORATORY TRAINING

Full time day and evening training programs in our modern Chicago and Toronto Laboratories are also available. **MAIL COUPON TODAY** for facts.

**EFFECTIVE
EMPLOYMENT SERVICE**


Get the same Employment Service that has helped so many DeVry Tech graduates get started in this fast-growing field.

"One of North America's Foremost Electronics Training Centers"

Accredited Member
of National Home
Study Council



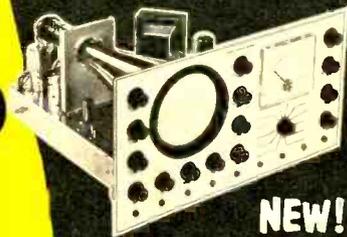**DeVRY TECHNICAL
INSTITUTE**
CHICAGO 41, ILLINOIS



**NEW!
ALL NEW!**

Shown above is the valuable new combination oscilloscope and voltmeter which DeVry Tech men build during their training.



Build and keep this BIG DeVry Engineered TV set—easily converted to U.H.F. (DeVry offers another home training, but without the TV set.)

**✉ CHECK
These Exciting
JOB
Opportunities:**

TV-Radio Broadcast Technician
Color TV Specialist
Radar Operator • Airline Radio Man
Missile Electronic Technician
Laboratory Technician
Computer Specialist
Your Own Sales & Service Shop
... PLUS MANY OTHERS

MAIL COUPON TODAY!

DeVRY TECHNICAL INSTITUTE
4141 Belmont Ave., Chicago 41, Ill., Dept. EI-11-R

Please give me your FREE booklet, "Electronics in Space Travel," and tell me how I may prepare to enter one or more branches of Electronics.

Name _____ Age _____
Street _____ PLEASE PRINT Apt. _____
City _____ Zone _____ State _____

2045 Canadian residents address: DeVry Tech of Canada, Ltd.
970 Lawrence Avenue West, Toronto, Ontario

FIX ANY TV or

These 2 great Ghirardi books bring you **COMPLETE TRAINING** FOR MODERN RADIO-TV SERVICING!

Let these two famous Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved professional methods! Almost 1500 pages and over 800 clear pictures and diagrams explain EVERY troubleshooting and repair operation as clearly as A-B-C. No needless mathematics. No involved theory. You get practical training of the type that teaches you to do the best work in the shortest time. Sold separately—or you save \$2.00 by buying both books. Use coupon or order from Dept. PR-111, Holt, Rinehart & Winston, Inc., Technical Div., 383 Madison Ave., New York 17, N. Y.



A. A. Ghirardi
Electronic's best-known instructor

① RADIO & TV CIRCUITRY AND OPERATION

Complete training in modern circuits and how to service them

You can repair ANY radio, television or other electronic equipment lots easier, faster and better when you really understand circuits and know just how and why each one works. That's exactly the kind of training you get in Ghirardi's 669-page Radio & TV CIRCUITRY AND OPERATION handbook! Gives a complete understanding of modern circuits. Shows what troubles to look for, and how to eliminate useless testing in servicing them. Throughout, it brings you the above-average training that takes the guesswork out of troubleshooting and fits you for the best paid service jobs. 417 illustrations. Price \$9.00 but see money-saving offer! (708214)

Circle No. 1 in coupon to order

② RADIO & TV TROUBLESHOOTING AND REPAIR

Complete training in modern service methods

Ghirardi's Radio & TV TROUBLESHOOTING AND REPAIR is a complete 822-page guide to professional service methods. For beginners, this giant book with its 417 clear illustrations is an easily understood course in locating troubles fast and fixing them right. For experienced men, it is ideal for developing better methods and finding fast answers to puzzling problems. Covers troubleshooting by all methods including both "static" and "dynamic" signal tracing types. Step-by-step charts demonstrate exactly how to proceed. A big television section is a down-to-earth guide to all phases of TV troubleshooting and service. Price \$10.00. See money-saving offer! (708578)

Circle No. 2 in coupon to order

Save \$2.00

Get both of these famous Ghirardi books at a saving of \$2.00 under the regular price. Check MONEY-SAVING OFFER in coupon!

REPAIR ANY ELECTRICAL APPLIANCE!

Save on repair bills! . . . Earn in your Spare Time!



③

This 370-page, profusely illustrated ELECTRICAL APPLIANCE REPAIR MANUAL helps you service practically any electrical appliance in common use—even if you've never fixed an appliance before. Basic principles are first explained—then the book gives you specific how-to-fix-it instructions for both standard and automatic washers, irons, toasters, ranges, cleaners, mixers, razors, clocks, motors, and many more.

Circle No. 3 in coupon to order.

Handy troubleshooting charts quickly help you locate what is wrong. Easy instructions guide you in making repairs, adjustments and parts replacements. Tells how to make your own low-cost test tools. Describes wiring problems. Includes appliance refinishing methods. Throughout, it gives you the practical "know how" to fix your own appliances—or to build a profitable full or part time repair business. Price \$8.25. (708172)



④

REPAIR ANY ELECTRIC MOTOR!

. . . handle any job from minor repairs to complete rewinding

It pays to train for something different! ELECTRICAL MOTOR REPAIR is a complete guide that helps you cash in on this vast, rapidly growing field. Shows how to handle all repair jobs (including complete rewinding) on practically ANY AC or DC motor or generator in common use. Special duo-spiral binding brings text

To order, circle No. 4 in coupon

and related how-to-do-it diagrams side by side so that you learn fast, easily and right. Every job is explained so clearly you can hardly fail to understand it. Over 100,000 copies in use in motor repair shops, schools and for home study. 560 pages. Over 900 how-to-do-it pictures. Price only \$9.25 for the complete training. (708735)



⑤

SHORT CUTS TO TV REPAIRS!

Eliminate Useless Testing—Fix TV Receivers Twice as Fast!

Just turn the dials of these handy, pocket-size Ghirardi & Middleton PIX-O-FIX TV Trouble Finder Guides. When the trouble symptoms shown in the PIX-O-FIX window match those of the screen image on the television set you're repairing presto! . . . you've got your clue. PIX-O-FIX shows the causes of the trouble,

To order, circle No. 5 in coupon

indicates the receiver section where it has probably happened, then gives repair instructions. PIX-O-FIX No. 1 identifies 24 common troubles and gives 192 causes and 253 remedies for them. No. 2 covers 24 more advanced troubles. Together, they are an easy guide to quick "picture analysis" servicing of any TV set. . . . AND THE PRICE IS ONLY \$3.00 for both. (708412)

RADIO EVER MADE!

TRAIN AT HOME FOR TV-RADIO-ELECTRONICS... at rock-bottom cost!

Get your basic training from these easily understood, low cost books!

Here is complete basic electrical-electronic training specifically written for beginners—priced at a fraction of what you might expect. 785 pages and almost 700 pictures, diagrams and charts in these two big books bring you top notch training written so you can understand it. In every respect, the material in these books compares more than favorably with "courses" costing many times as much!

BASIC ELECTRICITY—Fundamental electrical principles are the basis of ALL Electronics—and this 396-page manual gives you a complete working knowledge of them! Covers everything from electromagnetism to phone principles, circuits, wiring, illumination, reactance, impedance, power factor, instruments, controls, measurements, all types of components and equipment, etc. Includes set-up diagrams, practical examples and problem solutions. Price \$6.25 separately. (708859)

BASIC ELECTRONICS—This new 389-page guide takes up where Basic Electricity leaves off. Shows how electrical principles are applied in Electronics and gives you a sound grasp of electronic theory, methods, circuits and equipment. Over 375 illustrations explain details clearly. The ideal basic training for any kind of work in TV, radio, communications, hi-fi, industrial electronics and related fields! Price \$6.25 separately. Specify No. 8 in coupon.

SAVE \$1.50! SEE BASIC TRAINING MONEY-SAVING OFFER IN COUPON! (708974)

DON'T THROW OLD RADIOS AWAY!

Here's the data you need to fix them in a jiffy!

(708297)

Just look up that troublesome old radio you want to fix. Four times out of five, this 3 1/2-pound, 744-page Ghirardi **RADIO TROUBLESHOOTER'S HANDBOOK** tells what is causing the trouble... shows how to fix it. Cuts service time in half. Eliminates useless testing. Even beginners can easily fix old sets which might otherwise be thrown away for lack of service information.

Gives trouble symptoms and their remedies for over

4,800 specific models of old home, auto radios and record changers made between 1925 and 1942... Airline, Apex, Arvin, Atwater Kent, Belmont, Bosch, Brunswick, Clarion, Crosley, Emerson, Fada, G-E, Kolster, Majestic, Motorola, Philco, Pilot, RCA, Silvertone, Sparton, Stromberg and dozens more. Has hundreds of pages of old tube and component data, service short cuts, etc. Price \$10.00.

Circle No. 6 in coupon to order

New! Easy! HANDBOOK OF TV TROUBLES

LOOK, LISTEN—then follow this simplified TV repair guide!

(708453)

This remarkable new 302-page Handbook helps you track down practically any TV trouble from the symptoms it produces in the set itself. Just turn to the Index. Look up the trouble symptoms of the set you want to fix—screen intermittently dark; "blooming"; abnormal contrast in spots; "snow"; poor detail; sync troubles; sound! troubles—or any of the many others. Then **HANDBOOK OF TV**

TROUBLES shows you exactly how to make adjustments or parts replacements. Outlines time-saving short cut... Explains puzzling details. Eliminates guesswork and useless testing. More than 150 television trouble test pattern, wave form and circuit illustrations explain test results, details and procedures so clearly you can hardly fail to understand. Price \$7.50. Circle No. 10 in coupon to order

GET MORE WORK OUT OF YOUR OSCILLOSCOPE!

Learn all about the handiest service instrument of all

Here, in a big, revised 2nd edition, is **THE** book that really shows you how to get more work out of your oscilloscope.

Clearly as **A-B-C MODERN OSCILLOSCOPES AND THEIR USES** gets right down to "brass tactics" in telling you exactly when, where and how. You learn to locate either AM or FM radio or television troubles in a jiffy. Even tough realignment jobs are made easy. Every detail is clearly explained—from

making connections to adjusting circuit components and setting the oscilloscope controls. And you learn to analyze patterns fast and RIGHT!

Includes latest data on quantitative measurements (the alicek method of diagnosing many color TV troubles and aligning sets properly); using 'scopes in industrial electronics, teaching... even in atomic energy work. Over 400 helpful pictures include dozens of pattern photos. Price \$8.00. (708818)

Circle No. 9 in coupon to order

TRY ANY BOOK 10 DAYS FREE!

CUT RADIO-TV TEST TIME IN HALF!

(708933)

In servicing, building or experimenting with any kind of television, radio, hi-fi or other electronics equipment, IT'S WHAT YOU KNOW ABOUT USING INSTRUMENTS THAT COUNTS! This 316-page **BASIC ELECTRONIC TEST PROCEDURES** manual helps you make tests and measurements and locate TV, AM and FM troubles fast and accurately. Tells what instruments to use and exactly how; how to substitute one for another; how to avoid buying unnecessary types; and how to develop time-saving test methods. 190 pictures and dozens of troubleshooting charts make things doubly clear. Covers Current Checks; measurements of Power, Capacitance, Inductance, Resistance, A-F, R-F, Phase Distortion & Modulation; checking Sensitivity, R-F Gain, Fidelity, A-V-C Voltage, Operating Voltages, etc. and includes handy TV Visual Alignment Techniques. Price \$8.00.

Circle No. 11 in coupon to order

Dept. PR-111, Technical Division
HOLT, RINEHART and WINSTON, Inc.
383 Madison Ave., New York 17, N.Y.

623900

Send books indicated for 10-day FREE EXAMINATION. (Circle the numbers of the books you want.) In 10 days, I will remit price indicated plus postage or return books postpaid and owe nothing. (SAVE! Send cash with order and we pay postage. Same 10-day return privilege with money promptly refunded.)

Check here for **SERVICE TRAINING COMBINATION OFFER** (709006)

... on Books Nos. 1 and 2. Send both big books at only \$17 for the two plus postage. Regular price \$18—you save \$2.00!

Check here for **BASIC TRAINING COMBINATION OFFER** (709196)

... on Books Nos. 7 and 8. Send both books at only \$11 for the two plus postage. Regular price \$12.50—you save \$1.50!

CIRCLE NUMBERS OF THE BOOKS YOU WANT TO ORDER!

1	2	3	4
5	6	7	8
9	10	11	

OUTSIDE U.S.A. Name

Add 50¢ to price of each book. Cash with order only. Same 10-day return privilege with money refunded.

Address

City, Zone, State

(Above offers expire July 15, 1962)




Here's the instrument training you need!

things doubly clear. Covers Current Checks; measurements of Power, Capacitance, Inductance, Resistance, A-F, R-F, Phase Distortion & Modulation; checking Sensitivity, R-F Gain, Fidelity, A-V-C Voltage, Operating Voltages, etc. and includes handy TV Visual Alignment Techniques. Price \$8.00.

... News

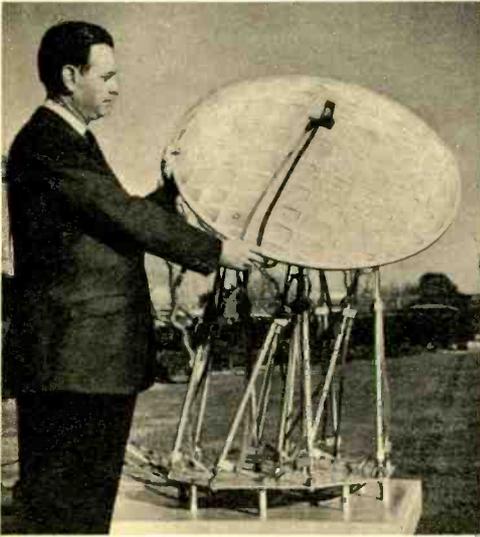Drag Race . . . The dish antennas that are used for radar, satellite spotting and point-to-point communications are highly vulnerable to winds, due to their



large size and mountaintop locations. Sylvania has challenged nature's forces with a rigid new lightweight foam material that reduces the problem of wind drag as much as two-thirds. The weight of a conventional metallic reflector of 60 feet diameter is at least 15 tons, but the Sylvania material brings the antenna's weight down to only three tons.

The 12 legs at the base of the dish structure are long hydraulic cylinders grouped into four tripods. Coordinated changes in the length of the legs, controlled by a servo-mechanism, cause the antenna to move through any desired search or track pattern.

Sound Goes to Work . . . Ultra Sonic Seal, a method of bonding plastic films and synthetic fabrics has been developed by Kleer-Vu Industries, Inc., New York City. The sealer head (see photo), driven by a powerful RF generator, vibrates at the rate of about 20,000 times a second, making contact with the surfaces being joined. The vibration generates just enough molecular heat to

MICRO

ELECTRON TUBE

FABULOUS LOW PRICES!
LARGE, SELECT STOCKS!
DEPENDABLE, FAST SERVICE!

37

¢ ea.

FOR any TUBE LISTED

\$35

PER HUNDRED ASSTD.

All Tubes Sent Postage Paid
Please send 25¢ handling for orders under \$5. Send 25% deposit on C.O.D. orders. Send approximate postage on Canadian and foreign orders.

MICRO

ELECTRON TUBE CO. Dept. EI-11, P. O. Box 55 Park Sta., Paterson 3, N. J.

• Each and every tube is tested in our own laboratory for mutual conduction and life test.


• We guarantee FREE replacement for one year of any tube purchased from us which fails to function efficiently under any or all operating conditions. Prompt refunds are made on any defective merchandise.

• The advertised tubes are not necessarily new, but may be electrically perfect factory seconds or used tubes—each is clearly so marked.

0A2	SX8	6BN6	6SF8	724	19RG6G
024	5Y3GT	6BJ8	6SF7	12A8	19J6
1A7GT	6Y3GT	6BK5	6S17	12A05	19T8
1B3GT	6A7	6BN7	6SK7	12AT5	24A
1N4C	6A8A	6BL7GT	6SL7GT	12AT7	25AV5
1N5GT	6A84	6BN6	6SH7GT	12A06	25B06
1L6	6AC7	6B06GT	6SQ7	12AV6	25D06
1N8GT	6AF4	6BQ7	6S7	12AV7	25L6CT
1Q3GT	6AG3	6BV5G	6T4	12AX4GT	25W4GT
1R8	6AQ7	6BZ6	6T8	12AX7	25Z5
1B8	6AN4GT	6BZ7	6U8	12A7	25Z6
1T6	6AM6	6C4	6V8	12B6	26
1U4	6AK5	6C5	6W4GT	12B6A	35A5
1U8	6AL5	6C6	6W6CT	12B7	35B5
1V2	6AMB	6C88	6X2	12B7A	35C5
1X2	6ANB	6C90	6X4	12B7B	35C8
2A3	6AQ6	6C96	6X5	12B7C	35L6CT
2A74	6AQ6	6C97	6X6	12B7D	35W4
3BC5	6AQ6GT	6C16	6Y6G	12B7E	35V4
3BN6	6AR6	6CM6	7A4/XXL	12B7F	35Z6CT
3C86	6AS8	6CM7	7A6	12B7G	37
3CF6	6AT8	6CS4	7A7	12B7H	39/44
3LFA	6AUC4Y	6CS6	7B4	12B7I	42
3Q4	6AUSGT	6CS8	7B5	12B7J	42
3V4	6AUS	6D06	7B6	12L6	45
40Q7A	6AUSGT	6E6	7B7	12Q7	50A5
4B7	6AV5GT	6H6	7B8	12S47	50B5
5A5	6AV5	6J4	7C4	12S67	50C8
5A5B	6AW8	6J5	7C5	12S7	50L6CT
5A7B	6AXGT	6J7	7C6	12S7A	50X6
5AV8	6AX5GT	6K7	7C7	12S7GT	58
5AW4	6BA	6K7	7C7	12S7GT	58
5BK7	6BC5	6K8	7E6	12S7GT	58
5E8	6BC8	6L7	7E7	12W6GT	71A
5U4G	6BD6	6M7	7F7	12X6	75
5U8	6BE4	6M7	7F7	12X6	75
5V4G	6BF5	6M7	7H7	12Z3	77
5V6GT	6BF6	6S8GT	7H7	12Z3	77
	6BGG	6SA7	7Q7	14A7/12B7	78
		6SC7	7Q7	14B6	80
			7X7/XXFM	14Q7	84/824
			7Y4	18A	1172
				19A4GT	1172A

WRITE DEPT. EI-11 FOR OUR FREE COMPLETE LIST OF TUBES & SPECIAL PURPOSE TUBES

...News

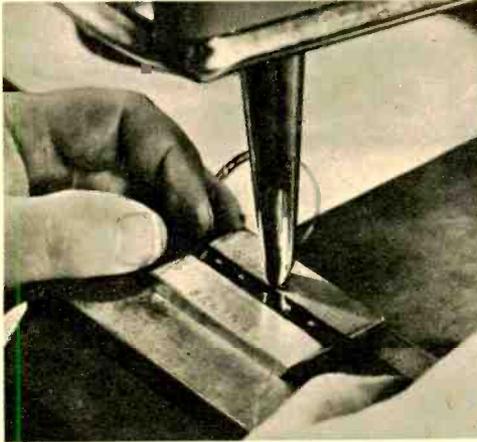

make a firm bond without burning the material.



Thermoelectricity . . . has been put to practical commercial use by Westinghouse in a new water cooler. Completely silent, with no moving parts, it works on a century-old principle that electricity



passing through the junction of certain dissimilar metals causes the temperature either to rise or fall, depending on the direction of flow (see **THERMOELECTRICITY**, September '59 EI).



RADIO SHACK'S 1962 CATALOG NATIONWIDE STANDARD OF EXCELLENCE in Electronics, Music and Communications

RADIO Shack Corporation of Boston, Massachusetts, took its name long ago from the term used for the communications center of a ship. The "radio shack" aboard ship is the vessel's only contact with the outside world—it is the focal point of all news—it is the very center of safety control. Consequently, its equipment is the best and most reliable, its personnel highly trained and skilled in radio, electronic and communication techniques.

Radio Shack Corporation is located in the city called the educational, cultural and scientific "hub" of America. Over the years we have become the communications, music and electronic center for that rapidly expanding group of people—amateurs, professionals or just plain fans—who enjoy the fascination of things electronic.

LAST year, Radio Shack filled over 1,000,000 orders from more than half a million people to become America's fastest growing electronics company. This year we have published the best and most complete catalog in our 38-year history. And we want to send you a **FREE** personal copy. Read about this catalog below and then mail the handy coupon on this page.

RADIO SHACK'S BIGGEST, NEWEST

Electronic Catalog **FREE**

336 pages—Over 100,000 items

IN this new book you'll find the widest line of electronic parts and equipment in the world—Stereo, Hi-Fi, Ham Radio, Test Equipment, Pre-Recorded Tapes, Tape Recorders, Records, Component Parts and Accessories . . . plus 30 pages of New Kits! Every item is easy to own with new No Money Down credit terms. Every item is guaranteed to satisfy or your money back.

When you send for this catalog, you also get a Free subscription to all other Radio Shack books for one full year. So mail the coupon now. You'll get your first free catalog in a few days.


MAIL THIS COUPON TODAY

RADIO SHACK Corp. Dept. 61L8B
730 Commonwealth Ave., Boston 17, Massachusetts
Please send me Radio Shack's new 1962 Electronics Catalog and every new issue for the next 12 months—all **FREE** and **POSTPAID**.

Name _____

Address _____

City & Zone _____ State _____

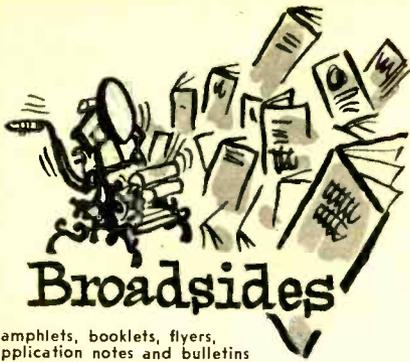

Broadsides

Pamphlets, booklets, flyers, application notes and bulletins available free or at low cost.

A booklet describing **TVI Causes, Effects and Solutions** may be obtained via a request on company letterhead from Television Interference Aids, 1110 Lake Blvd., Annandale, Va. Send a 9x12-inch stamped, self-addressed envelope.

Crystals and other precision-made equipment and their accessories are listed in International Crystal's free 1961 catalog. Technical information, typical circuits and illustrations are included. 18 N. Lee, Oklahoma City, Okla.

A catalog describing 25 electronic courses given by International Corre-

spondence Schools is available from ICS, Scranton 15, Pa. Hi-fi, computers, and communications are among the fields covered.

A Case History in Progress is the title of a Sylvania booklet discussing their new epitaxial germanium and silicon mesa transistors and epitaxial silicon mesa diodes. Free from Sylvania Electric Products, Inc., 1100 Main St., Buffalo 9, N. Y.

Stancor's new **replacement transformer** catalog lists electrical and physical specifications for 870 units. Catalog S-106 is available free from any Stancor distributor or by writing to Stancor, 3501 Addison St., Chicago 18, Ill.

Frequency and time standard systems are described in Hewlett-Packard's Application Note 52. Available free from H-P, 1501 Page Mill Rd., Palo Alto, Calif.

The 1961 **Master Index** to all Supreme Publications' service manuals may be obtained for 25¢. The master index covers Radio Volumes 1-21 and TV manuals 5-18. Supreme Publications, 1760 Balsam Rd., Highland Park, Ill.

TV-RADIO Servicemen or Beginners...

Send for *Coyne's*
7-Volume Job-Training Set
on 7-Day **FREE TRIAL!**



The First
Practical
TV-RADIO-
ELECTRONICS
Shop
Library!

Like Having An Electronics Expert Right At Your Side!

- VOL. 1—EVERYTHING ON TV-RADIO PRINCIPLES!** 300 pages of practical explanations; hundreds of illustrations.
- VOL. 2—EVERYTHING ON TV-RADIO FM RECEIVERS;** 403 pages; fully illustrated.
- VOL. 3—EVERYTHING ON TV-RADIO CIRCUITS!** 336 pages; hundreds of illustrations, circuit diagrams.
- VOL. 4—EVERYTHING ON SERVICING INSTRUMENTS!** How they work, how to use them. 368 pages; illustrated.
- VOL. 5—EVERYTHING ON TV TROUBLESHOOTING!** Covers all types of sets. 437 pages; illustrations, diagrams.
- VOL. 6—TV CYCLOPEDIA!** Quick and concise answers to TV problems in alphabetical order, including UHF, Color TV and Transistors; 868 pages.
- VOL. 7—TRANSISTOR CIRCUIT HANDBOOK!** Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages.

BOOKS HAVE BRIGHT, VINYL CLOTH WASHABLE COVERS

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
1455 W. Congress Parkway, Dept. B1-E1, Chicago 7, Ill.

Yes! Send me COYNE'S 7-Volume Applied Practical TV-RADIO-ELECTRONICS Set for 7-Days FREE TRIAL per offer. Include "Patterns & Diagrams" book FREE!

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Check here if you want Set sent C.O.D. Coyne pays postage on C.O.D. and cash orders. 7-Day Money-Back Guarantee.

**Answers ALL Servicing Problems QUICKLY...
Makes You Worth More On The Job!**

Put money-making, time-saving TV-RADIO-ELECTRONICS know-how at your fingertips—examine Coyne's all-new 7-Volume TV-RADIO-ELECTRONICS Reference Set for 7 days at our expense! Shows you the way to easier TV-Radio repair—time saving, practical working knowledge that helps you get the BIG money! How to install, service and align ALL radio and TV sets, even color-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick." No complicated math or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home. Over 3000 pages; 1200 diagrams; 10,000 facts!

SEND NO MONEY! Just mail coupon for 7-Volume TV-Radio Set on 7-Day FREE TRIAL! We'll include the FREE BOOK below. If you keep the set, pay only \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. Cash price only \$24.95. Or return set at our expense in 7 days and owe nothing. Either way, the FREE BOOK is yours to keep. Offer limited, so act NOW!

"LEARNED MORE FROM THEM THAN FROM 5 YEARS WORK!"

"Learned more from your first two volumes than from 5 years work."

—Guy Bliss, New York

"Sweet set for either the serviceman or the beginner. Every service bench should have one."—Melvin Masbruch, Iowa.

FREE DIAGRAM BOOK!

We'll send you this big book, "150 Radio-Television Picture Patterns and Diagrams Explained" ABSOLUTELY FREE just for examining Coyne's 7-Volume Shop Library on 7-Day FREE TRIAL! Shows how to cut servicing time by reading picture-patterns, plus schematic diagrams for many TV and radio sets. Yours FREE whether you keep the 7-Volume Set or not! Mail coupon TODAY!



Coyne

Educational Book Publishing Division
ELECTRICAL SCHOOL
1455 W. Congress Parkway Dept. B1-E1, Chicago 7, Illinois

BECOME A RADIO TECHNICIAN For Only \$26.95

BUILD YOUR OWN RADIO

Reg. U. S. Pat. Off

CIRCUITS AT HOME OR YOUR MONEY BACK!

PRACTICAL only HOME RADIO COURSE \$26.95

Progressive Radio "Edu-Kit"®

Now Includes

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

SCHOOL INQUIRIES INVITED

Unconditional Money-Back Guarantee

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc. for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.



TRAINING ELECTRONICS TECHNICIANS SINCE 1946

FREE EXTRAS

• SET OF TOOLS

- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRENCH SET
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE • QUIZZES
- TELEVISION BOOK • RADIO TROUBLESHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to make a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Stabilitz, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

FROM OUR MAIL BAG

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

W. Huff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Troubleshooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

YOU DON'T HAVE TO SPEND

HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. This Radio & Electronics Technician course makes use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL.

You will learn how to build radios, using regular schematics, how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 20 Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of \$26.95. The Signal Tracer alone is worth more than the price of the entire Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well-paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio. You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are twenty Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 20 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifiers, volume controls and switches, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electronic soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Oscillator, Progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a device for servicing instruments that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.

ORDER DIRECT FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7

- Send "Edu-Kit" postpaid. I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Rush me FREE descriptive literature concerning "Edu-Kit."

Name _____
Address _____

PROGRESSIVE "EDU-KITS" INC.

1186 Broadway, Dept. 539AE, Hewlett, N. Y.

NEW!

First Miniaturized TWO-WAY RADIO!
\$29.95

each postpaid with batteries. Two for \$59.90

SPACEPHONE—FITS IN SHIRT POCKET! Two-way walkie-talkie sending and receiving set in the smallest case at the lowest price! Absolutely self-contained microphone—loud-speaker, 9-volt transistor radio battery, transistorized transmitting and receiving sets with the latest miniaturized printed circuitry. U. S. designed and made. Volume control and tuning. Range ½ mile up.

Citizen's band—NO LICENSE, NO EXAMINATION—NO AGE LIMIT. For hunting, boating, fishing, hiking, all sporting uses, farms and ranches. Will operate between vehicles.

Electrosolids Corp. products are now in use on such projects as the Explorer VI Satellite. Spacephone replaces and does the same job as equipment costing from \$114 to \$300 per pair.

TO ORDER: Enclose check, cash or M. O. for post-paid shipment. \$5 deposit per unit for C.O.D. 10-day unconditional money-back guar. Dealers inquire. Calif. res add 4% state tax. Electrosolids Corp., 13745 Saticoy Street, Panorama City 37, Calif.




Electronic Marketplace

LOVE THAT IRON . . . Vertical vents in the nylon handle of the new Sidco soldering tool keep it cool even when used continuously. The photo is one of



Sidco's ad illustrations, and the model now is known as Hot Lips McGinty in our bailiwick. Sidco, Box 192, Venice, Calif.



studying antenna system in Tri-State's electronics lab

engineering degree in only 27 months

College graduates enjoy higher income . . . sure advancement. Become a graduate Electronics Engineer. Employers like Tri-State graduates . . . regularly interview seniors here. Qualify faster at Tri-State. Start any quarter. **BACHELOR OF SCIENCE DEGREE IN 27 MONTHS** in Electrical (Electronics or Power major), Mechanical, Aeronautical, Chemical, Civil Engineering. **IN 36 MONTHS** a B.S. in Business Administration (General Business, Accounting, Motor Transport Management majors). For earnest, capable, mature students. Enrollment limited. Small classes. Campus. Modernized buildings. Well-equipped labs. New dorms. Founded 1884. Modest costs. Enter Jan., Mar., June, Sept. Write J. A. McCarthy Admissions, for Catalog and "Your Career in Engineering and Commerce" Book.



TRI-STATE COLLEGE

48111 College Avenue • Angola, Indiana

Coaxial Stereo Earphones . . . are the ultimate for hi-fi buffs who like listening alone. In these Superex Model STM phones, each earpiece contains a separate woofer and tweeter which the manufacturer claims has a frequency response of 20 to 20,000 cps. An adjustable crossover network, in a separate unit, permits the user to regulate the sound in each phone. The phones are relatively light and have foam cushions that, in addition to providing comfort, shut out external noise. The price from Su-

**AT
LAST!**

RADIO-TV and ELECTRONICS TRAINING ... AT A PRICE YOU CAN AFFORD!

***21 INCH**
Receiver Kit included



Yes, this great course costs for less than any training of its kind given by other major schools! Radio-Television Training School will train you for a good job in Television or Industrial Electronics — **AT HOME IN YOUR SPARE TIME.**

Think of it—a complete training program including over 120 lessons, Fourteen Big Radio-Television Kits, Complete Color-TV Instruction, Unlimited Consultation Service . . . **ALL at a really big saving to you.** How can we do this? Write to us today . . . and find out!

And what's more — you can (if you wish)

OPEN YOUR OWN RTS-APPROVED AND FINANCED RADIO-TV SERVICE SHOP
We Want Many More Shops This Year

This 39 year old training organization — called RTS, that's Radio-Television Training School — wants to establish a string of Radio-TV Repair Shops in principal cities throughout the U. S. So far, a great many such shops are **NOW IN BUSINESS AND PROSPERING.** We are helping and training ambitious men to become future owners and operators of these shops in all areas.

FOR UNSKILLED INEXPERIENCED MEN ONLY — WE TRAIN YOU OUR WAY!

We must insist that the men we sign up be trained in Radio-TV Repair, Merchandising and Sales by our training methods—because **WE KNOW** the requirements of the industry. Therefore, we will **TRAIN YOU . . .** we will show you how to earn **EXTRA CASH**, during the first month or two of your training period. **YOU KEEP YOUR PRESENT JOB.** TRAINING TAKES PLACE IN YOUR OWN HOME, IN YOUR SPARE TIME!



Get your free book on the **FAMOUS RTS BUSINESS PLAN** find out how you can open **A REPAIR SHOP OF YOUR OWN**

We supply and finance your equipment

When you are ready and qualified to operate one of our RTS-Approved TV Repair Shops **WE WILL SUPPLY AND FINANCE EVERY BIT OF EQUIPMENT YOU NEED TO GET STARTED** plus an inventory of parts and supplies. In other words we will stake you . . . **AN OFFER NEVER MADE BEFORE BY ANY TRAINING ORGANIZATION.** Under the RTS Business Plan you receive:


1. An electric sign for the shop front.
2. Complete laboratory of test equipment.
3. Letterheads, calling cards, repair tickets, etc.
4. Basic inventory of tubes, parts, supplies.
5. Complete advertising and promotional material.
6. Plans for shop arrangement.
7. Instructions on how to go into business.
8. Continuous consultation and help.
9. The right to use RTS Seal of Approval, and the RTS Credo.
10. The right to use the Famous Trade Mark.

you build these and other units



RADIO-TELEVISION TRAINING SCHOOL
815 EAST ROSECRANS AVENUE
LOS ANGELES 59, CALIFORNIA

Est. 1922

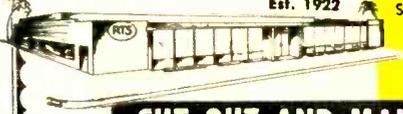

ACT NOW!

CUT OUT AND MAIL — TODAY!

RADIO-TELEVISION TRAINING SCHOOL
815 EAST ROSECRANS AVE Dept. E1-112
LOS ANGELES 59, CALIFORNIA

SEND ME FREE — all of these big opportunity books — "Good Jobs in TV-Electronics," "A Repair Shop of Your Own" and "Sample Lesson." I am interested in:

- Radio-Television Industrial Electronics (Automation)

Name _____ Age _____

Address _____

City & State _____
301

Mail This Coupon Now—No Salesman Will Call



RTS' Membership in The Association of Home Study Schools is your assurance of Reliability, Integrity, and Quality of Training.

ALL THESE FREE!



Now It's Easy and Fun to
**BUILD YOUR OWN
 SUN POWERED RADIO**

with Satellite-Type Solar Cells

24-Page handbook gives you detailed instructions, schematic diagrams, where-to-get-parts information.



25¢

Use solar cells that convert sunlight into electricity to power your own radios, transistorized receivers, Citizens Band 27 mc transmitter... sun powered audio and tunnel diode oscillators, sun relays... clear descriptive text gives you step-by-step directions and explanations for each project. Get these interesting projects in the all new IR "EXPERIMENTER'S HANDBOOK."

Mail 25¢ along with coupon to

IR INTERNATIONAL RECTIFIER CORP.
 222 KANSAS STREET, EL SEGUNDO, CALIFORNIA

Name _____ Age _____
 Address _____
 City _____ Zone _____ State _____

QUICKLY CUT HOLES
 in metal, plastics,
 hard rubber...



GREENLEE CHASSIS PUNCHES

Make smooth, accurate openings in 1½ minutes or less... for sockets, plugs, controls, meters, panel lights, etc.

Easy to use... simply turn with wrench. Many sizes and models. Write for literature.



GREENLEE TOOL CO. 1915 Columbia Ave., Rockford, Illinois


Marketplace



perex Electronics Corp., 4 Radford Pl., Yonkers, N. Y., is \$29.95.




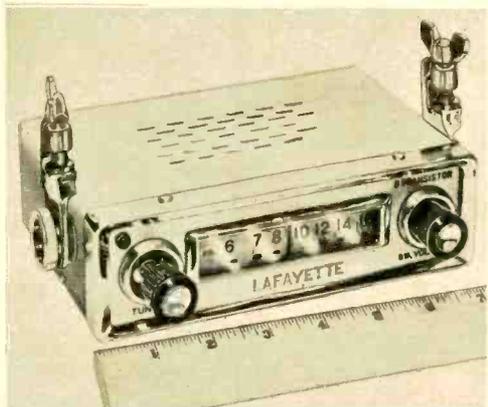Compact Radio for Compact Cars... is Lafayette's newest addition to their auto radio line. This little (7 x 2½ x 4¾ inches) 8-transistor unit has automatic gain control, 3 IF and 1 RF stage and



comes complete with a built-in 4-inch speaker, noise suppressor capacitor and distributor suppressor. For 12-volt operation only. Radio is priced at \$39.95 from Lafayette.

MAKE MORE MONEY

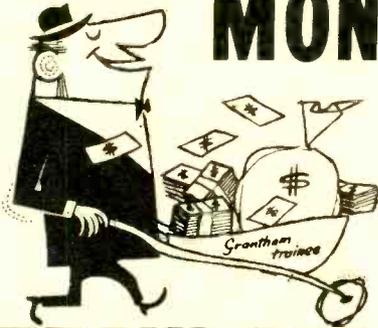

TRAIN FOR ELECTRONICS . . .

In RESIDENT CLASSES

Grantham *resident* schools are located in four major cities—Hollywood, Seattle, Kansas City, and Washington, D. C. Regularly scheduled classes in F. C. C. license preparation are offered at all locations. New *day* classes begin every three months, and new *evening* classes begin four times a year. The day classes meet 5 days a week and prepare you for a first class F. C. C. license in 12 weeks. The evening classes meet 3 nights a week and prepare you for a first class license in 20 weeks. For more information about the Grantham resident schools, indicate in the coupon the city of your choice and then mail the coupon to the School's home office in Hollywood, Calif. Free details will be mailed to you promptly.

Through HOME STUDY

Grantham training is the easy way to learn more quickly—to prepare more thoroughly—for F. C. C. examinations. And your first class license is the quick, easy way to prove to your employer that you are worth more money.

This correspondence course is directed toward two major objectives—(1) to *teach* you a great deal about electronics, and (2) to prepare you to *pass* all of the F. C. C. examinations required for a first class commercial operator's license. We teach you step by step and have you practice with FCC-type tests which you send to the school for grading and comment. You prepare for your F. C. C. examinations under the watchful direction of an instructor who is especially qualified in this field.

GET your first class commercial F. C. C. LICENSE

To get ahead in electronics—first, you need the proper training; then, you need "proof" of your knowledge. Your first class commercial F. C. C. license is a "diploma" in communications electronics, awarded by the U. S. Government when you pass certain examinations. This diploma is recognized by employers. Grantham School of Electronics specializes in preparing you to *earn* this diploma.

Grantham training is offered in resident classes or by correspondence. Our free booklet gives complete details. If you are interested in preparing for your F. C. C. license, mail the coupon below to the School's home office at 1505 N. Western Ave., Hollywood 27, California—the address given in the coupon—and our free booklet will be mailed to you promptly. No charge—no obligation.

Get your First Class Commercial F. C. C. License by training at

GRANTHAM SCHOOL OF ELECTRONICS

HOLLYWOOD


SEATTLE

KANSAS CITY

WASHINGTON

This booklet **FREE!**

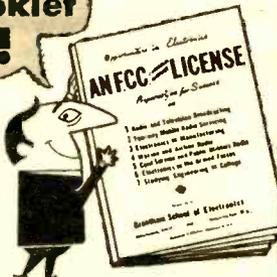This free booklet gives details of our training and explains what an F. C. C. license can do for your future. Send for your copy today.



for **FREE** Booklet **CLIP COUPON** and mail in envelope or paste on postal card.

for **FREE** Booklet **CLIP COUPON** and mail in envelope or paste on postal card.



To: **GRANTHAM SCHOOL OF ELECTRONICS**
1505 N. Western Ave., Hollywood 27, Calif.

Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study, Kansas City classes, 18-S

Hollywood classes, Seattle classes, Washington classes

Marketplace

Beam Antenna Rotor . . . Streamlined, weatherproof and rugged, the "Ham-M" Rotor is designed specifically to support the large, multi-element beams favored by amateurs. It features a positive electro-mechanical brake that locks the antenna against whipping by the wind and a remote-control unit calibrated in increments of 5° for accurate positioning of the antenna. Full information available from Cornell-Dubilier, 50 Paris St., Newark, N. J. \$119.50.



permeability-tuned low-frequency circuits makes for a stable receiver. Complete specs available from Collins Radio Co., Cedar Rapids, Iowa.

For Hams and SWLers . . . Collins has introduced their 51S-1 general coverage high-frequency receiver. An "all-wave brother" to the 75S-1 (which tunes only ham bands), this unit covers everything from 2 to 30 megacycles. The circuit is triple conversion from 2 through 7 mc and double conversion from 7 through 30 mc. The combination of crystal-controlled high-frequency oscillators and

Hi-Fi Hearing Aid . . . Dime-sized and completely self-contained, the Otation Normalizer contains a subminiature acoustic chamber to give the user more normal sound than is furnished by most aids. The effect of the tiny acoustic labyrinth is to improve the clarity of low tones and speech patterns. The device fits flush in the ear and weighs only a fraction of an ounce. It has enough am-

MAKE YOUR INTEREST IN ELECTRONICS *PAY OFF*

Get
Into . . .

The HIGH PAY — PRESTIGE Field of **TECHNICAL WRITING**

HERE'S WHAT YOU GET . . .

- 50 Meaty Lessons
- Over 110 pages of Electronics
- Covers ALL Military Specifications
- Real, practical writing projects
- Full consultation privileges
- Many manuals, charts and diagrams
- Low tuition terms
- Employment Assistance
- State Approved Diploma
- Close personal supervision
- AND MUCH, MUCH MORE

ELECTRONICS WRITERS NEEDED NOW—ATWS will train you at home at low cost for a profitable career in **TECHNICAL WRITING**. Thousands needed in all areas. Get in on the ground floor of this fascinating new field. ATWS offers training specifically designed for the needs of industry. Course includes everything you need to become a top-notch Tech Writer.

YOU ARE JUST A STEP AWAY FROM TOP PAY—Yes, with your present interest in Electronics, you're just a step from the **BIG MONEY**. Technical Writing is one of the highest paying fields **NOT** requiring college training. It's tailor-made for **YOU**—but you must **ACT NOW**.

THIS COUPON CAN BE YOUR PASSPORT TO SUCCESS
Fill in your name and address and rush coupon for full information. We will prove to you that we can train you without interfering with your present income or job.

CAREER BOOK AND SAMPLE LESSON

TRAINING  AMBITIOUS
MEN FOR INDUSTRY

American Technical Writing Schools, Inc.
5504 Hollywood Blvd.
Hollywood 28, Calif.

American Technical Writing Schools, Inc. Dept. EI-111
5504 Hollywood Blvd., Hollywood 28, Calif.

Please RUSH full particulars.

Name _____ Age _____

Street _____

City _____ Zone _____ State _____

**BOTH
FREE**

NO SALESMAN WILL CALL ON YOU



How To Get an

FCC License (Commercial)



An FCC License Or Your Money Back!

Completion of the Master Course (both Sections) will prepare you for a First Class Commercial Radio Telephone License with a Radar Endorsement. Should you fail to pass the FCC examination for this license after successfully completing the Master Course, you will receive a full refund of all tuition payments. This guarantee is valid for the entire period of your enrollment agreement.



Get All 3 Booklets Free . . .




find out how . . .

1. You can get job security. Specialized education is the road to higher salary and important jobs in the growing field of electronics.
2. You can solve the problems that stump other technicians. Problems in electronics are becoming more complex. Your ability to solve problems will help you get ahead in your field.
3. You can handle new electronic devices. Every day, advances are being made in electronics. Only through education can you find out how to keep up with these developments and how to use the new devices.

Get This Handy Pocket Electronics Data Guide Folder

FREE

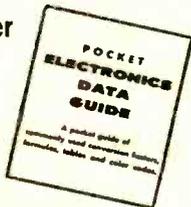Puts all the commonly used conversion factors, formulas, tables and color codes at your fingertips. Yours absolutely free if you mail the coupon today. No further obligation!



Accredited by the National Home Study Council

Cleveland Institute of Electronics

1776 E. 17th Street Desk EI-36 Cleveland 14, Ohio

Sorry—Not For Beginners

Please inquire only if you really want to get ahead and to add to what you have already learned in school, in the service, or on the job. Some previous schooling or experience in electronics, electricity, or related fields is necessary for success in Cleveland Institute programs.

Cleveland Institute of Electronics

1776 E. 17th Street, Desk EI-36, Cleveland 14, Ohio

Please send me Free Career Information Material prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below.

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other |

In what kind of work are you now engaged?

In what branch of Electronics are you interested?

Name Age.....

Address

City Zone..... State

EI-36

ELECTRONICS

Train in the
new shop-labs of
the world famous



COYNE

ELECTRICAL SCHOOL
on a quarter of a million dollars worth
of equipment or learn at home in your
spare time with Coyne's modern tele-
vision training.

Use this coupon to get our FREE BOOK
"GUIDE TO CAREERS"

COYNE ELECTRICAL SCHOOL training training
1501 W. Congress Pkwy. at Coyne at home
Dept. of Electronics 11-W, Chicago 7, Ill.

NAME _____

ADDRESS _____

CITY _____ STATE _____

Unlike most other schools, we do not employ salesmen.

New Electronic Audio Device Trains Your Memory For Immediate Recall *While you sleep!*

NEW YORK, N.Y.—If you have trouble remembering names, dates, facts, languages, here's wonderful news: There's no need to suffer with a poor memory any longer . . . for now you can memorize detailed data, master another language, recall speech material, statistics, math tables, learn bridge rules, music, poetry, or prose. You can actually train your memory—automatically—while asleep!



Here's how: The patented new Dormiphone Memory Trainer, using a dramatic new recording principle, electronically increases memory retention as it speeds the learning process. This amazing teaching tool is used by educators, psychologists, people of all ages and professions. Yet it's so simple, even a child can work its clock-controlled electronic tape system.

While a poor memory may handicap even the most brilliant individual, a good memory opens doors to greater success, added confidence and enjoyment. And now, with the Dormiphone, you can learn not to forget anything you want to remember.

Start right now: *Don't forget* to send for scientific evidence of the Dormiphone's effectiveness. Write for FREE literature TODAY or call for FREE demonstration. There's no obligation. Modernophone, Inc., 367-111 Radio City, New York 20, N. Y. Circle 7-0830.

Marketplace

plification to correct a hearing loss up to about 50 db. Otation Listener Corp., Box 711, Ossining, N. Y.



More Music Power . . . Fisher has announced a new integrated amplifier rated to deliver 110 watts (music power). The Model X-1000 employs two pairs of matched EL34's and offers the



following features: earphone connections to permit personal listening, rear-panel input for remote control, 18 inputs, low and high filters to eliminate turntable rumble and surface hiss, three DC power supplies, etc. Complete specs for the \$329.50 unit may be obtained from Fisher, 21-21 44th Dr., Long Island City 1, N. Y.



Shrinkable Tubing . . . Sure to find many uses in electronic gear of all kinds is the new Alpha Shrinkable Tubing. The product is manufactured in diameters up to one inch. It slips easily over wires, terminals, small parts, etc. and when heat of approximately 135° C is applied it shrinks to a predetermined diameter to form a tight bond. Longitudinal shrinkage, however, is less than 10%. Alpha Wire Corp., 200 Varick St., New York 14, N. Y.



Now... assemble the finest:
A Professional Quality

CUSTOMIZED
TV KIT

ON EASY
"PAY AS YOU WIRE" TERMS*

- ☆ Designed for the perfectionist seeking maximum performance.
- ☆ Easy to assemble; no technical knowledge required.
- ☆ An ideal "Learning" Kit with a complete Course of Study is available.


Professional Quality Features

The Transvision "Professional" Model TV Kit (or Assembled Chassis) is designed to satisfy those video-and-audiophiles who seek the best possible performance of which the art is capable. Nevertheless, the kit builder can assemble this chassis for less than the cost of an ordinary receiver.

Note these unique features:

- Hi-Fi Audio (with 2 EL-84 output tubes, oversize audio output transformer, Woofer-Tweeter Speaker System with heavy magnets and crossover; Extended Range Tone Control).
- Ultra-linear sweep circuits; D.C. restoration; Standard Coil Guided Grid Turret Tuner with provisions for UHF and special low noise tubes; 4 megacycle picture bandwidth; 10 microvolt sensitivity.
- Heavy-duty power supply (power transformer, two low voltage rectifier tubes — no silicon rectifiers).

The TRANSVISION
"Professional"

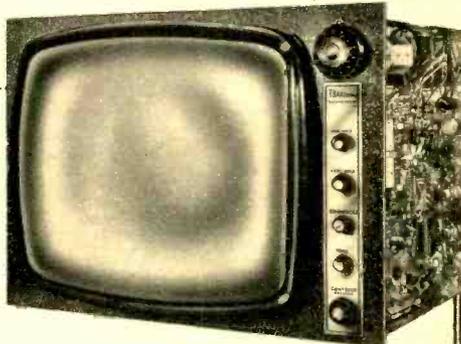

* Only \$15 for the Starting Package!

**ALSO AVAILABLE AS AN
ASSEMBLED CHASSIS**
for custom installations

- Heavy-duty ruggedized construction, no printed circuits; built to give trouble-free performance for many years.
- Includes newest reflection-free 23" tube with bonded face, or the 24" or 27" CRT.
- Selected because of superior performance for use in Educational TV by over 3000 schools and colleges and U.S. Armed Services.

Interested in Electronics?

Learn the basic principles of electronics from the Complete Course of Study which is available with the Kit.



As a preliminary, order the Assembly Instructions for only \$2.00; to be refunded if you purchase kit.

TRANSVISION

Pioneers in Television Kits

NEW ROCHELLE, N. Y.

• NEW Rochelle 6-6000

----- START NOW — MAIL THIS COUPON -----

TRANSVISION, New Rochelle, N. Y.

Dept. PD

- Send Free 8-page Catalog Enclosed is \$2. for Assembly Instructions so that I might see how easy it is to assemble the Transvision Kit. I understand that this will be refunded if I purchase a kit.
- Enclosed is \$15 for the Starting Package. I understand that I can buy packages one at a time as I wire. (Models range from \$119 to \$199.)

Name..... Address.....
City..... Zone..... State.....

2 New easy-to-build KITS from H. H. Scott

Here are kits that make you a professional! Kits you can build that look and perform like factory units.

- Kit-Pak box opens to work-table • All wires pre-cut, pre-stripped • All mechanical parts pre-riveted to chassis
- Parts mounted on special Part-Charts in order you use them, simplifies and speeds assembly • Beautiful gold-finish panel harmonizes with H. H. Scott wired components.



LT-10 FM TUNER KIT

Professional H. H. Scott Wide-Band tuner with pre-aligned, ore-mounted silver-plated front end. Uses Ez-A-Line alignment system . . . no special tools . . . entire alignment takes 15 minutes.

\$89.95*



LK-72 72 WATT STEREO AMPLIFIER KIT

Plenty of power for any speaker systems. Fabulous H. H. Scott features never before available in a kit: Separate bass and treble controls, center channel control, tape recorder monitor, many more.

\$149.95*



H. H. SCOTT

H. H. SCOTT Inc. 111 Powdermill Rd., Maynard, Mass. Dept. 130-11

Send me details on your new kits and stereomaster components for 1961.

Name _____

Address _____

City _____ State _____

*Slightly higher west of Rockies. Accessory case extra.

Export: Telesco International Corp., 36 W. 40th St., N.Y.C.

KUHN

"LEADERS IN SPECIALIZED RECEIVING EQUIPMENT"

MOBILE FIXED CONVERTERS

- POLICE
- FIRE
- COMMERCIAL
- CITIZEN'S BAND

345A Complete \$29.95



A new high gain Crystal Controlled Converter. Excellent sensitivity rugged construction . . . Easy to install. Designed for standard transistor car radios. Requires no high voltage supply. 2-54 MC or 150-162 MC.

KUHN CONVERTERS . . . the most advanced line . . . designed for optimum performance.

348A Complete \$34.95



Transistorized, directly tunable Converter. Powered with self-contained mercury cell. Excellent sensitivity and stability. Designed for car, home or portable receivers. Two types available: Aircraft VHF 115-130 MC or 150-162 MC.

344A Complete \$23.95



A new low cost Crystal Controlled Converter designed for use with standard transistor car radios. Operates directly from 12V DC. Rugged construction. Good sensitivity. Range 2-54 MC.

ORDER TODAY or SEND FOR FREE CATALOG . . . containing complete information on a full line of: CONVERTERS AND RECEIVERS FOR EVERY APPLICATION

315A Complete \$13.95



A low cost Tunable Converter for any 10 MC area of 26-54 MC. Aircraft VHF, or 150-160 MC. Easily installed. For use with home or auto sets. 316A Directly Tunable Converter. Available in four ranges: 26-30 MC, 30-50 MC, 115-130 MC, or 150-160 MC. Complete \$13.95



20 GLENWOOD CINCINNATI 17, OHIO

Marketplace

CB Handi-Talkie(s) . . . Raytheon has brought out a Citizens Band handi-talkie called the Ray-Ette. It comes in two models, the 11-transistor Super and six-transistor Regal, selling for \$99.95 and \$79.95, respectively. The Super has a superhet circuit and the Regal a super-regen circuit.

The Ray-Ette is a nice little handful at 15 ounces and dimensions of 5 1/4 x 2 3/4 x



1 3/16 inches. It has a plastic case and a 46-inch telescopic antenna. Input to the final stage is 50 mw and Raytheon claims ranges of five miles on water, two miles on land and "several blocks" in congested cities. The Ray-Ette operates on a rechargeable dry cell and the charger comes with the handi-talkie.

Raytheon Co., 411 Providence Turnpike, Westwood, Mass.

Smallest Video Tape Recorder . . . is completely transistorized, weighs about 450 pounds and can be readily transported. This console, introduced by the Sony Corp., Tokyo, is designed to operate with the Sony transistorized camera. It will have broad applications in the fields of commercial communication, industry, education, medicine and sports. For example, a hospital can tape an operation for future study, or transmit it over closed-circuit TV for viewing anywhere in the building.

direct road to earning
a successful living in
electronics—here it is!

RIDER'S
**BASIC
RADIO**

by M. Tepper



6-Volume 'pictured-text' course makes it easy for you to master radio communications

**A BACKGROUND IN RADIO COMMUNICATIONS
IS A SPRINGBOARD INTO MANY VITAL
AREAS OF ELECTRONICS**

Radio communications and the areas that comprise this subject—AC and DC electricity, vacuum tubes, receivers, transistors, and transmitters—is the foundation for many important branches of electronics—FM and AM radio, citizens band, amateur radio, mobile and marine communications, telemetry, radar, television, instrumentation, microwave, facsimile, ultrasonics, telephony, remote control, paging, etc. To know the fundamentals of radio communications is to be prepared for all of these important fields, and BASIC RADIO presents these fundamentals more clearly, more accurately than any text, or any group of texts ever published.

**SPECIAL ILLUSTRATIONS MAKE SUBJECT
EASILY UNDERSTANDABLE**

Not only is the content of the course complete, but it is presented in such a manner that anyone regardless of previous education can grasp it quickly and know the subject thoroughly. The reason—carefully selected language, specially prepared illustrations—specially thought out presentation. These illustrations are not the typical ones found in most books on radio. They are specially conceived and selected for their ability to convey an idea, make complex thoughts simple to understand. You can't miss! There is at least one illustration to every page, one to support every idea—more than 650 illustrations in all in this six-volume course.

**COVERS EVERYTHING YOU'LL NEED TO KNOW ABOUT
RADIO COMMUNICATIONS TO GET AHEAD
IN ELECTRONICS**

This 6-volume pictured-text course covers the fundamentals and circuitry of radio communications. While it stresses fundamentals, it does not neglect the practical—it puts these fundamental principles to work. You will be able to read schematics—recognize circuits used in radio equipment. You will understand electricity and magnetism. Following the study of electricity, magnetism, circuit components, vacuum tubes, power supplies, oscillators and amplifiers—the various circuits are put to work in simple and elaborate radio receivers—AM and FM, auto and communications receivers including citizens band, mobile communication equipment, etc.

You are made thoroughly familiar with semi-conductors and transistors their applications; what they are—how they work and how they are used in radio. Transistor circuits and receivers with parts values are shown.

The last volume provides a thorough coverage of transmitters, antennas and transmission lines. You'll understand modulation and transmitter type oscillators, microphones, coupling methods and power supplies and transmitter schematics.

Volume I, DC electricity; Volume II, AC electricity; Volume III, vacuum tubes and vacuum tube circuitry; Volume IV, radio and communication receivers; Volume V, semiconductors, transistors and transistor receivers; Volume VI, transmitters, transmission lines and antennas.

**A LOW COST ELECTRONIC EDUCATION
6-VOLUME COURSE ONLY \$13.85**

This 6-volume course opens the wonderful world of electronics to you. The complete course costs only \$13.85 (soft covers). Or, you can select any volume covering the area of radio communications in which you wish to increase your knowledge. Buy this course today at parts distributors, bookstores or order direct using convenient coupon: FREE: Write for free brochure showing samples of pages demonstrating how special illustrations speed your learning.



10-DAY MONEY-BACK GUARANTEE
JOHN F. RIDER, PUBLISHER INC.
116 W. 14th St., New York 11, New York

I want to save \$1.35 on cost of individual volumes.

Enclosed is \$..... Please send:
....Set of.....Complete 6-vol. course in soft covers, \$13.85.

....Set of.....Complete 6-vol. course in single, cloth binding, \$14.85.
Send me individual volumes:

....Vol. I, \$2.70....Vol. II, \$2.70....Vol. III, \$2.70....Vol. IV, \$2.50....Vol. V, \$1.90....Vol. VI, \$2.70.

....FREE CATALOG....FREE BROCHURE
We guarantee satisfaction or return to us within 10 days for full refund.

NAME.....

ADDRESS.....

CITY.....ZONE.....STATE.....

Free ALLIED

444-PAGE ELECTRONICS CATALOG

WORLD'S BIGGEST • MOST COMPLETE

including the
complete 1962
knight-kit
CATALOG
pages
385-444

best buys
for 1962

EVERYTHING IN
ELECTRONICS
including exclusive
products & special
values available
only from
ALLIED

Send
for it
today!

ALLIED
ELECTRONICS
for everyone

1962

OUR 41st YEAR

CATALOG 210
INDEX: PAGE 204

ALLIED RADIO
100 N. WESTERN AVENUE • CHICAGO 90, ILLINOIS • MAYMORTEL L-8806

NEW Multiplex Stereo FM
All-Transistor Stereo Hi-Fi

exclusive money-saving KNIGHT® products
SAVE MOST on famous KNIGHT Stereo Hi-Fi—comparable
to the best in quality, styling and performance, yet priced far
lower. Select super-value KNIGHT components or complete
systems (including latest Multiplex Stereo and All-Transistor
hi-fi) and save most. KNIGHT products are acclaimed by all
those who recognize integrity in design and manufacture and
who appreciate value.

new

NO MONEY DOWN

on Allied's new Credit Fund Plan
Now—easiest terms ever—see our 1962 Catalog
for the simple details.

SEND FOR 444-PAGE CATALOG TODAY!

SAVE
MOST
ON EVERYTHING IN ELECTRONICS

- New Stereo Hi-Fi Systems—Everything in Hi-Fi Components
- New Multiplex Stereo FM • All-Transistor Stereo Hi-Fi
- Money-Saving Build-Your-Own KNIGHT-KITS® for Every Need
- Best Buys in Tape Recorders, Tape, and Supplies
- Citizens Band 2-Way Radios • Short-Wave Receivers
- Amateur Receivers, Transmitters, and Station Gear
- Latest Public Address Systems, Paging and Intercom Equipment
- TV Tubes, Antennas, Accessories • Batteries, Wire and Cable
- Test and Laboratory Instruments • Tools, Hardware
- Huge Listings of Parts, Tubes, Transistors, Technical Books

Satisfaction Guaranteed or Your Money Back

ALLIED

Electronics Illustrated



BIG PLUS!
In your 1962
ALLIED
CATALOG

includes complete catalog featuring over 70 exciting

knight-kits 
A PRODUCT OF ALLIED RADIO

NEW for '62 and simply great!
available only from **ALLIED**

new



ALL-TRANSISTOR
2-Band AM-Shortwave
DX-er Radio Kit... \$19.95



Amazing 100-In-1 Electronic
Science Lab Kit..... \$29.95

new
MULTIPLEX STEREO



MULTIPLEX
Adapter Kit for
Stereo FM re-
ception... \$19.95



All-In-One FM-AM Tuner-Amplifier Kit
with built-in **MULTIPLEX** Stereo FM...




TRANSISTORIZED
Electronic Tachometer
Kit..... \$24.95



ALL-TRANSISTOR Wireless
Intercom System Kit..... \$45.00



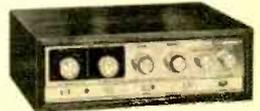Deluxe Stereo FM-AM Tuner
Kit with built-in **MULTIPLEX**
Stereo FM..... \$99.95



ALL-TRANSISTOR
40-Watt Stereo Ampli-
fier Kit, less case \$79.95

**building a Knight-Kit is the
most satisfying do-it-yourself
experience in the world!**

5 BIG REASONS WHY:

- **Convenience Designed**—makes you a kit-building expert—even the very first time!
- **Wonderful to Build**—you'll marvel at the sheer ease of assembly with the exclusive "show-how" manual guiding you like a good instructor.
- **You Own the Best**—you'll enjoy with pride a true custom-built product, professional in its engineering, styling and performance.
- **You Save So Much**—because you buy direct from Allied at our money-saving volume prices—and because you do the easy assembly yourself.
- **Easiest to Buy**—NO MONEY DOWN on Allied's new Credit Fund Plan—easiest terms ever!

MONEY BACK GUARANTEE: Buy any Knight-Kit. Build it! Use it! You must be satisfied or you get your money back!

see more than 60 other **KNIGHT-KITS!**

HI-FI KITS

FM & FM-AM Tuners
70-W Amplifier
40-W Amplifier
32-W Amplifier
20-W Amplifier
Stereo Preamp
Record-Playback Preamp

INSTRUMENT KITS


Lab AC VTVM
VOM's
5" Scopes
Tube Testers
Signal Tracer
Audio Generator
Sweep Generators, etc.

HOBBYIST KITS

"Span Master" Receiver
"Space Spanner" Radio
Transistor Radios
2-Way Intercoms
Electronic Lab Kits
plus many others

AMATEUR KITS

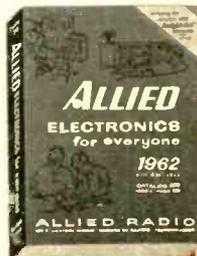R-100 Amateur Receiver
R-55 SW Receiver
Self-Powered VFO
Grid Dip Oscillator
100 kc Crystal Calibrator
Code Practice Oscillator



**Send
for it
today!**



Phone and CW 60-Watt
Ham Transmitter Kit. \$49.95



Mutual Conductance
Tube Tester Kit. \$99.50

KNIGHT-KITS
also available
in Canada

- World's Largest Stocks • Lowest Money-Saving Prices
- Fastest Shipment • Expert Help • Easiest-Pay Terms
- Satisfaction Guaranteed or Your Money Back

send for the world's biggest
electronics catalog!

Free

ALLIED RADIO, Dept. 184-L1
100 N. Western Ave., Chicago 80, Ill.

Send **FREE** 1962 **ALLIED** 444-page Catalog

Name _____
PLEASE PRINT

Address _____

City _____ Zone _____ State _____

RADIO  World's Largest
Electronic
Supply House

November, 1961

BEST BUYS IN STEREO AND MONO HI-FI

New Transistorized Stereo/Mono 4-Track Tape Deck RP100 Semikit (electronics in kit form) **\$299.95** Wired **\$399.95**



New FM-AM Stereo Tuner ST96 Kit **\$89.95** Wired **\$129.95** Incl. FET



New 70-Watt Integrated Stereo Amplifier ST70 Kit **\$94.95** Wired **\$149.95**



New 40-Watt Integrated Stereo Amplifier ST40 Kit **\$79.95** Wired **\$129.95**

FM Tuner HFT90 Kit **\$39.95** Wired **\$65.95** Incl. FET Metal Cover **\$3.95**



28W Integrated Stereo Amplifier HF81 Kit **\$69.95** Wired **\$109.95**



AM Tuner HFT94 Incl. FET Kit **\$39.95** Wired **\$65.95**

Stereo Preamp HF85 Kit **\$39.95** Wired **\$64.95**



Stereo Power Amplifiers

	Kit	Wired
100W HF89:	\$99.50	\$139.50
70W HF87:	\$74.95	\$114.95
28W HF86:	\$43.95	\$74.95



Stereo/Mono Changer/Player 1007 with stereo cartridge and dual sapphire styli **\$49.75**



Bookshelf Speaker System HFS1 Kit **\$39.95** Wired **\$47.95**



BEST BUYS IN CITIZENS TRANSCEIVERS, HAM GEAR, RADIOS

Citizens Band Transceivers from Kit **\$59.95** Wired **\$89.95**



New 60W CW Transmitter = 723 Kit **\$49.95** Wired **\$79.95**



Transistor Portable Radio RA6 Kit **\$29.95** Wired **\$49.95** Incl. FET



BEST BUYS IN TEST EQUIPMENT

New Metered Variable AC Auto-Transformer Bench Supplies Model 1073 (3 amps) Kit **\$35.95** Wired **\$47.95** Model 1078 (7 1/2 amps) Kit **\$42.95** Wired **\$54.95**



Peak-To-Peak VTVM = 232 & Uni-Probe® Pat. = 2,790,051 Kit **\$29.95** Wired **\$49.95**



DC - 5 MC 5" Scope = 460 Kit **\$79.95** Wired **\$129.50**



VTVM = 221 Kit **\$25.95** Wired **\$39.95**

5" Push-Pull Scope = 425 Kit **\$44.95** Wired **\$79.95**

Tube Tester = 625 Kit **\$34.95** Wired **\$49.95**



RF Signal Generator = 324 Kit **\$26.95** Wired **\$39.95**



1000 Ohms/7 Volt V-O-M = 536 Kit **\$12.90** Wired **\$16.90**




6- & 12V Battery Eliminator & Charger #1050 Kit **\$29.95** Wired **\$38.95** Extra-filtered for transistor equip. = 1060 Kit **\$38.95** Wired **\$47.95**



NEW AC Volt-Watt Meter #260 Kit **\$49.95** Wired **\$79.95**



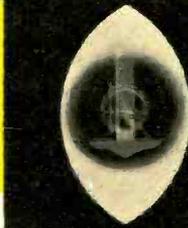Multi-Signal Tracer #145A Kit **\$19.95** Wired **\$28.95**



EICO

EXCELLENCE IN CREATIVE ELECTRONICS

Over 2 MILLION EICO instruments in use throughout the world. Compare, take them home — right "off the shelf" — from 1500 neighborhood dealers, most of whom offer budget terms



EICO, 3300 N. Blvd., L.I.C. 1, N.Y. Et-11
 Send free Catalog describing over 80 top-quality products, free Stereo Hi-Fi Guide, free Short Course for Novice License, name of nearest EICO dealer. Send new 36-page GUIDEBOOK TO HI-FI for which I enclose 25¢ for postage & handling.

Name _____
 Address _____
 City _____ Zone _____ State _____
 Add 5% in the West



EI's SPECIAL REPORT ON FM TUNER KITS

Here are the results of a monumental project in which
EI constructed and tested all major FM tuner kits.
Most comprehensive report of its type ever made!

FM Tuners . . . theory & practice 30

Contributing Editor John Milder discusses FM broadcasting and the general design of FM tuners. Then he points out technical and physical design factors you should consider in the selection of an FM tuner for your system.

Technical Specifications 32

Performance figures on all kits, allowing you to make easy comparisons of price vs. quality. Our specification chart is your best guide when shopping for a tuner kit.

How EI's Tests Were Made 34

A detailed analysis of the construction procedures followed by our builders and the program of rigid tests carried out over a period of several months in our laboratory—plus a listing of the professional equipment used.

Reports on Individual Kits 36

Discussions of the circuitry and special qualities of each FM tuner kit, along with comments by the kit-builders and some tips based on our expert kit analyses. The latter will have great value to the novice kit buyer.

Tech Editor's Test Bench 43

Notes and comments on the reports and their significance by Technical Editor Larry Klein.

FM TUNERS

THEORY & PRACTICE

A discussion of FM broadcasting and tuner design, plus some technical factors a buyer must consider.

By John Milder

BY NOW, even the newest audiophile recognizes FM as *the* medium for high-fidelity broadcasting. The amplitude-limiting circuits built into FM sets effectively clip AM noise riding in with the FM signal. As for wide-range frequency response, the uncrowded FM band allows a station plenty of elbow room to transmit the full range of audio frequencies without disturbing its neighbors on the dial.

FM's only disadvantage for the average audiophile is its fairly short transmission range. This means that only a short distance away from the transmitter we get into the fringe area: hence,



"A short distance away we get into the fringe."


an FM receiver must be sensitive enough to pick up and *use* signals of only a few *microvolts* strength. And now that stereo via FM multiplex is coming over the airwaves, even greater demands are placed on FM receiver sensitivity. Let's look at some of the ground rules for good performance from *any* FM tuner—kit or factory-wired.

FM tuners are necessarily complex, consisting of several sections. The first, usually called the front-end, selects and amplifies the desired station's frequency. In addition to latching onto the

signal, it's important that the front-end produce as little noise as possible, since noise will be amplified right along with the signal. Any tube circuit introduces *some* noise, so manufacturers try for a maximum signal-to-noise ratio by techniques such as the plating of the front-end with silver or gold to increase conductivity, special grounded-grid or cascode circuits and low-noise tubes.

Before the strengthened signal leaves the tuner's front-end, a mixer/oscillator circuit (as in the standard AM super-het) converts it to an *intermediate frequency* (IF). The IF section's job is to get the signal (within the IF bandwidth) as strong as possible before it reaches the tuner's limiter and detector stages.

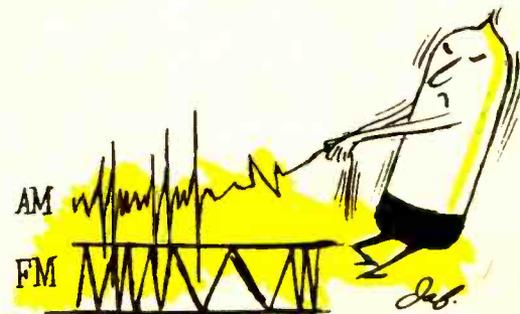The last IF tubes frequently double as limiters—depending upon the strength of the signal reaching them. The limiter's function is to strip off the AM noise. To a great extent, the limiter's ultimate effectiveness depends on the signal-to-noise ratio obtained in earlier stages. Only the right com-




"The limiter's function is to strip off AM noise."

bination of front-end and limiter performance can provide the velvety background that FM is capable of.

Finally, the detector (ratio or discriminator) stage—which nobody has yet dubbed the “rear-end”—separates the audio content of the signal from the RF carrier. The big trend in this area is toward wider detector bandwidth. The wide-band detector generally has an easier time avoiding distortion when a broadcast station overmodulates its signal. In addition, a wide-band detector stage can ignore any slight tendency of a front-end to drift off station—thus eliminating the need for AFC.

Before we go on to look at the standards for good tuner performance, we should point out that the problem of drift—once the bugaboo of FM—has been pretty well licked. If a *narrow-band* detector is used in a tuner, there’s usually an Automatic Frequency Control (AFC) circuit which locks in a station. Some manufacturers even throw in an AFC circuit in a wide-band tuner which theoretically doesn’t need it. There have been arguments pro and con AFC, since some of the circuits tend to cause distortion and a loss of bass response. In any case, if AFC is used in a tuner, make sure that it can be temporarily “defeated” during tuning to prevent it from blocking out the weaker of two close signals.

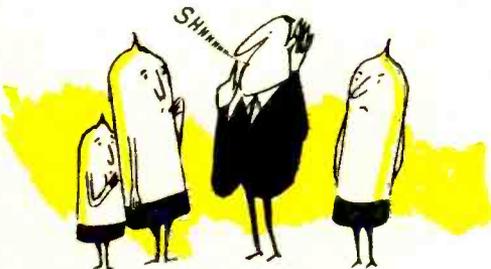A tuner’s primary job obviously is to make the most of whatever FM signal is available. Therefore, the first yardstick for most audiophiles is a tuner’s *sensitivity rating*. Specifications for a tuner’s sensitivity are expressed in the *signal strength* (in microvolts) needed for a *given amount (db) of quieting action* (X microvolts for Y db of quieting).




“30 db of quieting is specified as the standard.”

Until recently, there was no general agreement on techniques for rating sensitivity. But the Institute of High Fidelity Manufacturers now specifies 30 db of quieting as the standard and EI’s ratings in this survey have been measured by this standard.

A tuner also must measure up in the virtues demanded of other hi-fi components. Wide-range audio frequency response is a must, as are low distortion (both harmonic and intermodulation) and a high signal-to-noise level. You’ll find these figures on EI’s spec chart. In addition, there are less obvious factors such as physical size, output, etc., which may be important in your setup.

Capture ratio becomes important if you live in an area that is about halfway between two FM transmitters that operate on—or near—the same frequency. If a tuner has a hard time deciding between the two stations in such a situation, you’ll come up with nothing more than hash when you try to tune either one. Specifications for capture ratio tell you how much stronger one of the two signals must be in order for the tuner to latch onto it and ignore the second sig-

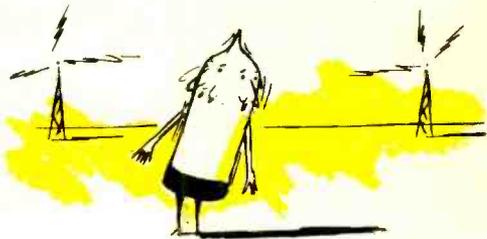

“Capture ratio . . . tuner decides between stations.”

nal. The ratio is stated in db, and the lower the figure the better.

None of the units tested in this survey drifted enough (when correctly tuned to a station and limiting) to make the results worth noting. In all tested units the drift problem seems to be a thing of the past. And frequency response in every case was at least 20 to 20,000 cps, ± 2 db.

Among other general features worth noting, our chart indicates visual tuning aids (if any), the noise level and presence of an [Continued on page 32]

TECHNICAL SPECIFICATIONS

Tuner	Sensitivity		Distortion		Capture Ratio	Signal-to-Noise Ratio	Wiring	Space for Mplx. Adapt.	Fuse
	Home Aligned [Ⓐ]	Instrument Aligned	Harmonic [Ⓑ]	I.M.					
Radio Shack Realistic HK-200	No 4.5 μ v.	4 μ v.	0.78%	1.6%	7.8 db	56 db	pt. to pt.	No	No
Arkay FM-7	No — [Ⓒ]	5 μ v.	1.15%	1.85%	7.5 db	42 db	pt. to pt.	No	No
EICO HFT-90K	No 5 μ v.	3.25 μ v.	1.1%	2.4%	6.25 db	48 db	pt. to pt.	No	No
Heathkit FM-4	No — [Ⓒ]	7.5 μ v.	0.6%	1.35%	9 db	45 db	pt. to pt.	No	Yes
Lafayette KT-650	Yes 8 μ v.	5.4 μ v.	0.15%	0.9%	7.5 db	59 db	printed	No	Yes
PACO ST-35-PA	Yes 4.5 μ v.	4.25 μ v.	0.35%	0.3%	8.5 db	48 db	printed	Yes	No
Grommes 101 GTK	Yes 6 μ v.	4.25 μ v.	1.35%	3.6%	7 db	53 db	pt. to pt.	Yes	Yes
Allied Radio Knight-Kit 83YX732	Yes 2.9 μ v. Ⓓ	2.45 μ v. Ⓓ	0.35% Ⓓ	0.29% Ⓓ	6 db	59.5 db	printed	Yes	Yes
Dynatuner FM-1	Yes 4.75 μ v.	3.25 μ v.	0.25%	0.24%	5.2 db	50 db	printed	Yes	Yes
H. H. Scott LT-10	Yes 1.88 μ v.	1.75 μ v.	0.57%	0.91%	5.8 db	54 db	pt. to pt.	Yes	Yes
Harman-Kardon Citation III	Yes 3 μ v.	1.95 μ v.	0.1%	0.4%	5.4 db	64 db	pt. to pt., term. board	Yes	Yes

FOOTNOTES Ⓐ Yes—aligned according to manufacturer's instructions. No—no home alignment instructions.
 Ⓑ 0.15% subtracted from readings to compensate for residual distortion in test equipment.
 Ⓒ Price includes cabinet unless otherwise noted.
 Ⓓ Pre-wired, pre-aligned RF, IF and detector stages; only power supply and switch require wiring.

output level control and where mounted. "Compatibility" is a term frequently thrown around without much regard for its exact meaning. Were all tuners we tested compatible with any hi-fi setup? We can give a qualified yes. The two points of qualification are the high-frequency loss problem discussed in the Tech Editor's Test Bench and the possible inadequate audio output voltage of some tuners in some setups.

The audio output figures listed in the table were obtained by feeding in 1,000 microvolts of signal modulated 100%. Here again, EI's figures may not match the manufacturers'. Although the various techniques provide differing results, EI's table provides accurate comparisons among the tuners.

If you have an older amplifier with low gain at the tuner input jack you may run into trouble when hooking in one

FROM EI's TEST LABORATORY

Visual Tuning Indicator	Output Level Control	Output Circuit	Pre-Wired Front-End	AFC	Output Level	Size	Price [Ⓢ]
None	None	Direct	Yes [Ⓢ]	Switched (front panel)	1.5 v.	4 3/4" high 9 3/4" wide 6 3/4" deep	\$29.95 \$34.88 wired
Eye Tube (EM 84)	Rear	Modified Cathode Follower [Ⓢ]	Yes	Fixed	0.84 v. 3 v. [Ⓢ]	4 1/4" high 12 1/4" wide 7 3/4" deep	\$39.95 \$4.95 metal case
Eye Tube (DM 70)	Front	Cathode Follower	Yes	No	1.4 v.	3 3/4" high 12" wide 8 3/4" deep	\$39.95 \$65.95 wired \$ 3.95 metal case \$12.50 wood case
None	Front	Cathode Follower	Yes	Switched (front panel) Internal Adjustment	1.25 v.	4 3/4" high 13 3/4" wide 5 1/2" deep	\$39.95 \$62.95 wired
Eye Tube (EM 84)	Front	Feedback Triode	No	Variable (front panel)	1.95v.	5" high 14" wide 11" deep	\$54.50 \$79.95 wired
Eye Tube (EM 84)	Rear	Cathode Follower	Yes [Ⓢ]	Switched (front panel)	2.1 v.	5 3/4" high 15 3/4" wide 11 1/4" deep	\$59.95 \$69.95 semi-kit \$89.95 wired
Eye Tube (EM 81)	None	Direct	Yes	Variable (front panel)	2.45 v.	4 1/2" high 14" wide 9" deep	\$66 (East) \$69.30 (West) \$79.95 wired (\$89.95 with case)
Eye Tube (EM 84)	Rear	Cathode Follower	No	Switched (front panel) Adjustable (rear panel)	6 v.	5 3/4" high 15 1/2" wide 16 1/2" deep	\$67.50
Eye Tube (EM 84)	Front	Feedback Triode	No	No	1.9 v.	4" high 13" wide 7 1/2" deep	\$79.50 \$119.95 wired
Signal Strength Meter	Rear	Feedback Triode	Yes	No	1.35 v.	4 3/4" high 15" wide 10 3/4" deep	\$ 89.50 \$129.50 wired \$ 12.95 metal case \$ 24.95 wood case
Signal Strength Meter and Center Channel Meter	Front	Feedback pair	Yes (plus pre-wired IF strip)	Switched (front panel) Adjustable (rear panel)	1.95 v.	6" high 14 3/4" wide 13" deep	\$149.95 \$229.95 wired \$ 29.95 wood case

- [Ⓢ] Tuner worked before instrument alignment but sensitivity was too poor to permit a valid IHFM test.
[Ⓢ] Choice of high or low impedances gives corresponding voltage readings.
[Ⓢ] Pre-wired front-end is supplied only with partially assembled ST-35-PA.
[Ⓢ] Measurements made with DSR circuit switched in.

of the two or three tuners on the table with the lowest audio output levels. This is particularly true if you are driving a low-efficiency, acoustic-suspension speaker. Note that the *gain* at the tuner input jack of the amplifier bears no relation to the power output capabilities of the amplifier. To be specific, even a 50-watt amplifier driving a low-efficiency speaker, when used with a low-output tuner, may not provide

all the hum-free volume you would like—or need.

Multiplex jacks are present on all the tuners. However, all the facts are not yet in on requirements for reception of stereo. All manufacturers in EI's report say their tuner kits are adaptable to multiplex, but there is no guarantee that they will produce anything to fill the "multiplex adaptor" spaces some have marked out on their chassis. —

How EI's Tests Were Made



ABOUT six months ago, Electronics Illustrated, foreseeing the approaching approval of an FM multiplex system by the FCC, embarked on a testing project which we modestly describe as monumental. It was our aim to construct and test every FM tuner kit available.

Our testing program was planned as follows:

- Each tuner would be constructed according to the manufacturer's manual by a person of limited or average kit experience. He would make notes on difficulties experienced, ambiguities in the instructions, etc.

- The sets were then turned over to the Audio Workshop where they were checked for proper wiring. Any errors made in construction were rectified and the construction manual checked to determine whether the instructions or the builder was to blame. Bad connections were resoldered (this was the major cause of non-operation) and the tuners were then left to heat up.


- We were interested not only in how well the tuners performed under optimum alignment conditions but—more importantly—in how well they would function straight off the constructor's work bench (assuming they were built correctly). The manufacturer's non-instrument alignment instructions (if any) were followed. (Recently, techniques have been worked out for alignment of FM tuners without the usually required RF or sweep signal generator and VTVM. The tuner's built-in tuning eye or meter usually serves as the alignment indicator.)

- After the manufacturer's non-instrument alignment, performance measurements were attempted on each tuner. We say *attempted*, because among the tuners not providing a non-instrument alignment procedure there were several not sufficiently sensitive without instrument alignment for Institute of High Fidelity Manufacturers' figures to be obtained. The sensitivity of each tuner after home alignment or no alignment is listed in the chart (pages 32 and 33).

- The next step was an instrument alignment of each tuner using some of the finest professional equipment available. After alignment, the entire series of measurements was made again and the final results are noted on the chart.

It should be emphasized that our figures are not absolutes. As we state elsewhere, the tuner you build may be somewhat better—or worse—than the unit we constructed and tested. However, be assured that every effort was made to be certain that EI's test units were representative of the average production.

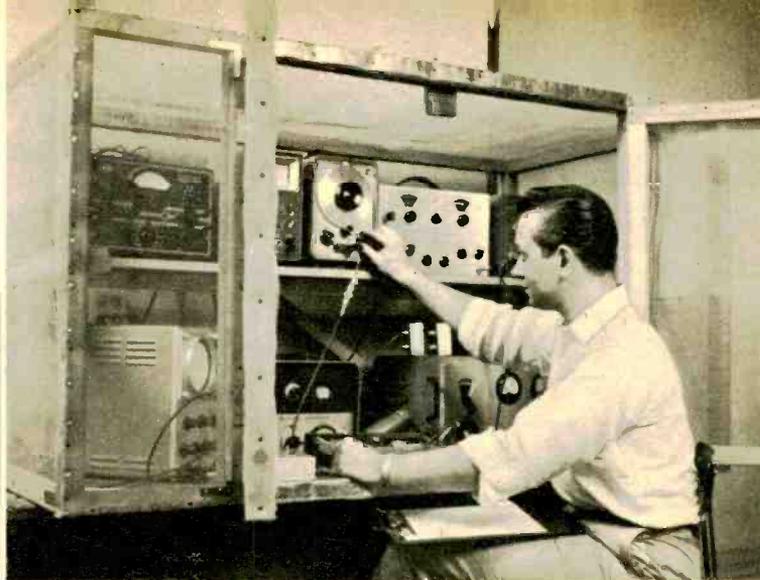Harry Kolbe working on a tuner in the specially constructed shielded cage required by the test procedures.



WHO'S WHO: The bulk of the work represented by this report on FM tuner kits was carried out by EI's three Contributing Editors on Audio: Harry Kolbe, David Muirhead and John Milder. Kolbe and Muirhead are proprietors of the Audio Workshop at 732 Broadway in Manhattan's Greenwich Village. It is a test and development laboratory which EI employs regularly for construction and evaluation work. Milder is a well-known writer on audio and other technical subjects.

LABORATORY TESTS MADE BY EI

USABLE SENSITIVITY was measured for all tuners by the IHFM procedure to make possible direct comparison of all kits. Separate measurements were made after *home* alignment and after *instrument* alignment to indicate whether the inexperienced builder could hope for good performance without special alignment.

FREQUENCY RESPONSE was measured by IHFM standards with full allowance for the high-frequency de-emphasis built into all tuners.

HARMONIC DISTORTION was measured by IHFM standards.

INTERMODULATION DISTORTION was measured by Society of Motion Picture and Television Engineers (SMPTE) standards.

SIGNAL-TO-NOISE-RATIO (internal hum and noise) was measured by IHFM standards.

CAPTURE RATIO was measured by IHFM standards.

OUTPUT LEVEL was measured at 1,000 microvolts input (100% modulation).

INSTRUMENTS used for alignment and measurements included:

Hewlett-Packard: Model 400C AC VTVM; Model 400D/db AC VTVM;
Model 412A DC VTVM; Model 200CD Audio Oscillator

Measurements Corp.: Model 210A Standard FM Signal Generator;
Model 80 Standard Signal Generator

Barker & Williamson: Model 400 Harmonic Distortion Analyzer

Heathkit: Model OP-1 Professional Oscilloscope; Model AA-1 Audio Analyzer (IM Distortion)

EICO: Model 368 TV-FM Sweep Generator

Knight-Kit: AC VTVM

EI's Editors consider the IHFM standards the *best* now available. As presented in our chart, they allow a reader to make direct and valid comparisons between competitive units—which the varying test methods used by manufacturers do *not* allow. If you're interested in having a copy of the IHFM's booklet outlining FM test procedures, write to The Institute of High Fidelity Manufacturers, Inc., 516 Fifth Avenue, New York 36, New York. Ask for publication IHFM-T-100, the cost is \$1.

INDIVIDUAL KITS



The **RADIO SHACK REALISTIC HK-200** is not only the least expensive, but unquestionably the easiest kit in this survey to build. It comes with everything mounted, aligned and pre-wired except the power supply, output and switching.

The front-end uses a 6BS8 as a cascade RF amplifier and a 6AB4 for mixing; a 12AT7 serves as oscillator and AFC tube. Two 6AU6's are used as IF amplifiers and a third serves as a limiter. The discriminator is a 6AL5 tube.

The Realistic instructions are as comprehensive as they need to be. The few construction steps are clear and accurate. It takes about an hour to make the few

electrical and mechanical connections required. No alignment is needed when you've finished building the Realistic—it simply plugs in and plays.

Sensitivity for a unit in this price range is excellent and distortion quite low—under the right conditions. Neither figure could be significantly improved by instrument alignment.

When we first checked out the Realistic we obtained a disappointing harmonic distortion level of almost 4%. In addition, the frequency response test showed about a 3 db rise at 20 kc. Our test lab tried various remedies, and then it turned out that Radio Shack relies upon the capacity of the tuner's output cable (which we did *not* use in our tests) to supply a certain percentage of the required high-frequency de-emphasis. When the tuner was retested with its own output cable, the kc rise disappeared and the distortion figures dropped to those quoted in the chart. There may seem to be little connection between an output cable and HD. However, remember that the high-frequency boost resulting from the too-short cable also boosted the harmonics.

Summing up, the Realistic certainly gives you a lot of tuner for a little money.

The **ARKAY FM-7's** keynote is simplicity, and its design has few frills. The pre-wired front-end is followed by two 6AU6 tubes serving as straight IF amplifiers. A third 6AU6 sees double-duty as an IF amplifier and a single-stage limiter. A wideband ratio detector is used, followed by an audio stage that can be used either as a cathode follower or (for higher gain) a triode amplifier.


Packaging and instructions for the FM-7 are fair. The chief fault of its instruction book is that it is not specific enough. The novice kit-builder wants to know the size of every nut and lock-washer called for. And, since each numbered construction item often includes four or five steps, it would help to make their order clearer.

Some mechanical connections, such as the mounting of the tuning shaft and the stringing of dial cord, may be difficult for the novice, and some soldering points are hard to get at.



The front-end is prealigned, but IF and detector alignment measures are left to the builder, and instruments must be used. Without instrument alignment, reception is only fair. The FM-7's AFC circuit can't be defeated during tuning, which may make for a strong station's overriding a nearby weaker one.

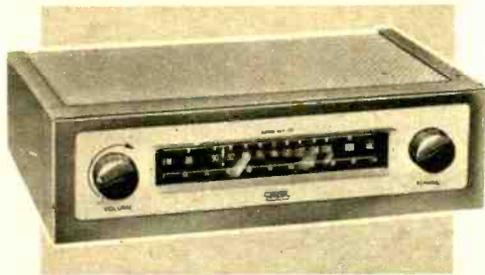The FM-7's performance is adequate if you're not in an FM fringe area.



The **EICO HFT-90's** combination of high performance and simplicity has proved its appeal to kit builders well enough to remain virtually unchanged since its introduction. The sealed, pre-wired front-end (one of the first on the market) uses an ECC 85 grounded-grid RF amplifier and a reflex converter. The tuner has three stages (using 6AU6's) of IF amplification. The last of these also acts as the limiter. A 6AL5 ratio detector feeds the 6C4 cathode-follower output.

One of the first tuner kits to employ a wide-band ratio-detector, the HFT-90 (despite the absence of AFC) shows no evidence of drift.

The HFT-90 instruction book is specific and easy to follow. Like most other EICO

kits, it uses conventional point-to-point wiring, with recommended lead lengths.

Actual construction goes pretty rapidly. The chassis layout is occasionally a little cramping, but there are none of those frustrating instances when the builder wishes he had an extra pair of hands.

The EICO's IF and RF transformers are prealigned at the factory, and you can expect the tuner to play as soon as it is plugged in—without the need of either home or professional alignment. But for extreme fringe areas, instrument alignment will pay important dividends in sensitivity.

A novel and effective "exclamation point" tuning eye also serves as the dial pointer.

The EICO's audio output is fairly low. This means only that the EICO may not adequately drive a low-gain amplifier connected to a low-efficiency speaker. With virtually any modern amplifier, the HFT-90's output level is more than adequate, even with inefficient speakers. To maintain the EICO's good signal-to-noise ratio, the tuner should be operated with its front panel volume control on full at all times. Volume level adjustment should be made at the amplifier.

The **HEATHKIT FM-4** puts a premium on simplicity and value. The new pre-wired and pre-aligned front-end of the FM-4 uses a 6GY8 triple-triode as an RF amplifier, oscillator/mixer and AFC tube. The two IF amplification stages use 6AU6's, and the limiter stage is also a 6AU6. One section of a 6BN8 serves as a ratio detector, and the other as a cathode follower output.

The FM-4 is well packaged and, as expected from Heath, the instruction book is thorough and well illustrated. A novice should be able to assemble the kit with ease. While the veteran kit-builder doesn't need to be told to "make sure that a large blob of solder does not form here," this is exactly what the newcomer has to know.

There are no really tough construction problems with the FM-4, but the small tuner chassis does require an occasional bit of kit-building agility. For the most part, though, construction goes easily and without a hitch. As usual, Heath provides some extra hardware to replace the parts most likely to be lost, and a nice little nut-driver to help out in tight spots.

The Heathkit plays from the moment of plug-in and the pre-aligned front-end helps keep distortion low. Obviously, in-



strument alignment pays dividends in sensitivity. Heath logically suggests that the novice either ignore alignment or turn it over to a qualified serviceman. Detailed instrument procedures are given.

While the FM-4 is certainly not a super-sensitive unit, it's hard to criticize the kind of value it provides for the economy-minded builder—especially the newcomer. Its front-panel volume control allows it to be hooked up directly to a power amplifier. The desired AFC level can be set internally and then switched on and off at the tuner's front panel. Styling is intended to match the older line of Heath units. Heath informs us that the FM-4 will shortly be restyled on the outside, but no circuit changes are contemplated.

The **LAFAYETTE KT-650** is a simple and well-designed kit which uses printed circuit boards and prealigned IF transformers and coils to aid construction. It is designed for good rather than exceptional sensitivity, and actually checks out better than the manufacturer's conservative sensitivity rating indicates.

The front-end uses a 6AQ8 dual triode which doubles as an RF amplifier and mixer. A 6BK7B serves as an oscillator and AFC tube. There are two 6BA6 IF stages and there are two stages of limiting, using 7543's. A 6AL5 is used in the discriminator stage and a 6AV6, with heavy feed-back around it, acts as a "plate follower" output stage.

Lafayette's packaging is good and its instruction book thorough, with numerous pictorials. Parts are supplied in small envelopes with the numbers stamped clearly.


Actual construction is fairly simple, thanks to the well-planned printed circuit boards. Mechanical connections are relatively easy, and there is no need for the brute force approach at any time. The chassis is uncramped, and everything is accessible to the builder without acrobatics.

Although the front-end of the KT-650



is not prewired, Lafayette compensates with good instructions for alignment without instruments. The kit's tuning eye is used for this purpose, along with the ear of the builder. Results are good enough to overcome the lack of a preassembly.

As mentioned earlier, the KT-650 is rated conservatively in respect to sensitivity and actual tests revealed a microvolt more sensitivity than specified. Audio quality is excellent, with both harmonic and intermodulation distortion below 1%. The signal-to-noise ratio also ranked among the best. A front-panel level control permits the KT-650 to be used without a preamp, and audio output is fully adequate for this purpose.

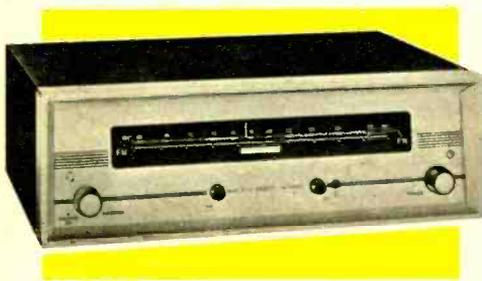

The **PACO ST-35** kit is unusual in that it's available in two forms. As the ST-35, it's a conventional kit with printed circuit boards. As the ST-35PA, the boards are prewired. We tested the PACO ST-35PA kit. In both models all RF and IF coils are prealigned.

Up front, a 6AQ8 serves as a grounded-grid amplifier and mixer. A 6BK7 is used as an oscillator and AFC tube. The first two IF stages, using 6BA6's, provide straight IF amplification. The last two, using 6AU6's, double as limiters. The discriminator section uses a 6AL5, and a 12AU7 serves as audio amplifier and cathode follower output stage.

The packaging of the PACO is good and

the construction book is excellent.

Although we received our unit with the RF and IF circuits prewired, the non-wired version is not likely to be troublesome. The PACO exhibited no really knotty construction problems. There are but few cramped connections, and the chassis is roomy and easy to work on.


PACO's alignment instructions, using only the tuner's tuning eye, are quite good and less than a microvolt sensitivity could be gained with instrument alignment. The harmonic distortion, however, was improved somewhat by the use of instruments. It was brought down from 1.6 to 0.35%. The ST-35's sensitivity should prove adequate for everything short of the most extreme fringe area. The audio quality is good, and the *on-off* AFC push-button on the tuner's front panel is convenient and does not degrade performance in any way.

Available too late for inclusion in this report, PACO has announced a new, less expensive (\$42.95) tuner kit, the ST-25, which has a sealed, prealigned front end. One version (ST-26—\$54.95) includes a small audio amplifier to allow direct connection to a loudspeaker.

The **GROMMES 101GTK** has no fancy trimmings but it's well designed and a good performer. In the pre-aligned front-end, a 6AQ8 serves as an RF amplifier and converter. Two 6AU6 IF stages follow and two more 6AU6's are used in the two limiting stages. Two 1N541 diodes serve as the discriminator and feed directly to the output jack. There is no separate stage of audio amplification. AFC is provided by a "varicap" diode and its level may be set by a front panel control.

Packaging and instructions for the Grommes are fair. The instruction book is not quite specific enough for the novice kit-builder, and there should either be more pictorials or the present ones should be clearer. (One pictorial, for the front-end, did not correspond with the front-end in the kit itself.)

Although the tuner is well laid out and its chassis is uncrowded, there were some problems in construction. The mechanical assembly of the tuner required ingenuity and effort (from an experienced kit-builder). The tuner mounting bracket had to be bent and shims inserted between it and the chassis. The tuning shaft itself required some grease to turn smoothly. The chassis had to be drilled to accommodate

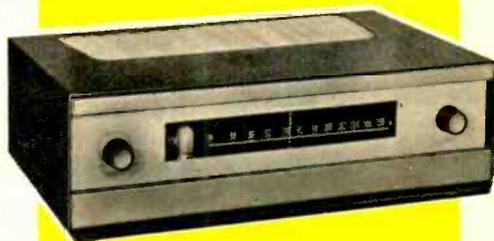

a trimmer capacitor. These problems sound more troublesome than they actually were, but it's nonetheless to be hoped that Grommes will remedy them. As it stands, the kit is not for beginners.

For non-instrument alignment of the Grommes you observe the tuning eye and listen for maximum interstation white noise through an amplifier and speaker.

Overall performance of the Grommes is good. Sensitivity is adequate for all but the toughest of fringe areas. The audio quality and audio output are adequate (2.4 volts) despite the lack of audio amplification stages. Note that this tuner lacks an isolation stage after the detector, and a long output cable should be avoided.



The **KNIGHT-KIT 83 YX 732** is straightforward in design, with the exception of one important feature: there's a special circuit labeled DSR (dynamic sideband regulation) which, when switched in, feeds back part of the discriminator's audio output to the tuner's front-end. Knight says the DSR cuts distortion due to over-modulation by the FM broadcast stations. We suggest it be left switched on at all times because it also substantially improves the sensitivity and distortion rating of the tuner. Both IM and harmonic distortion checked below 0.5%.

The Knight employs two stages of RF amplification using both halves of a 6AQ8. Another 6AQ8 serves as an oscillator mixer. Two 6CB6's serve as IF amplifiers, two 6AU6's as limiters and a 6AL5 is the discriminator.

The kit is well-packaged and the construction book is clear and easily followed. Both the front-end and IF stages use printed circuit boards, and there are few difficult solder connections.

Mechanical assembly, such as stringing the dial cord and mounting the tuning shaft is slightly time-consuming but not difficult.

Thanks to prealigned IF and RF transformers, the Knight performs very well with alignment by the builder. Only for extreme fringe-area reception is instrument alignment at all necessary.

Space is provided on the kit's extra-large chassis for later addition of an AM and/or a multiplex sub-section. All that is required for this purpose are the appropriate boards and a new panel (available from Knight). There's no need to change any of the circuits already built when adding either AM or multiplex. The unit illustrated here, by the way, incorporates an AM section and the new front panel.

As mentioned at the beginning of this report, Knight's novel DSR circuit is effective, and we think that it should be left switched on. In fact, we can't imagine any circumstance in which the user would want to deprive himself of the really exceptional gain in performance that DSR provides.



The **DYNATUNER FM-1** is the latest available of the tuners covered by our report. Third from the top in expense, it need take second place to none in terms of operating qualities.

The FM-1's instruction manual states that it is designed for good (but not top) sensitivity and extremely high audio quality with low distortion. And there's no doubt that the FM-1 fulfills its stated purpose. For example, our tests showed an I.M. distortion figure of less than a quarter of 1 per cent.

Behind the cathode-coupled front-end, (a dual-triode 6AQ8/ECC85), a triode/pentode 6AT8A serves as the oscillator/mixer. Four IF stages follow: the first two using 6BA6's; the second 6AU6's. Each IF stage also functions as a limiter when the signal reaches a high enough level. And there's sufficient gain in the receiver for the last limiter to be effective on input noise. The FM-1 also uses a balanced-bridge discriminator with a wide-band transformer and two matched semiconductor diodes. A 12AX7 serves as an isolating cathode follower (one triode) after the detector and the other triode as a "plate follower" audio output.

Packaging and instructions for the unit are good. And construction is remarkably simple—considering the high level of performance achieved. Printed circuit boards are used for the RF and IF stages. There are a few tight spots for the builder, but most connections are easy and uncramped. Unlike the other Dynakits, the components are not pre-mounted by Dynaco and there are some ambiguously numbered holes on the board. It's a good idea to double-check the component mounting for correctness before soldering. The circuit boards are sturdy, but some care is in order to develop the right soldering technique. Mechanical assembly is easy and fast.

All of the IF transformers, the discriminator transformer, and the slug-tuned coils on the RF board are pre-aligned close to optimum. But, like the other top-rated

kits, final alignment is to be done by the user at home and without test equipment. Dynaco supplies full instructions for alignment procedure, which is accomplished by using the tuner's eye and your ear. Although the procedure takes time, it is well worth it. Note it involves working on a live chassis and in some steps quite close to the high-voltage B-plus. Reasonable care should be exercised to avoid shock.


The results of the recommended home alignment steps are close to what can be obtained with instruments—close enough to make instrument alignment unnecessary. (Our lab obtained only a microvolt and a half more sensitivity and 0.3% less distortion with instruments.)

Our only reservation about the FM-1 concerns its high operating temperature. This is a "hot" tuner in more than one sense. While its heat generation probably won't do any harm to the components inside, adequate ventilation is a must for this unit. Since it's small, the Dynatuner tempts the user to slip it into a convenient cubbyhole in a bookshelf or elsewhere. Don't do it—failure to give it adequate breathing room may shorten the life of components.

Although the Dynatuner's sensitivity is good, its audio quality is unquestionably its real calling card. According to the manufacturer, the balanced-bridge discriminator, the low phase shift IF stages, and the cathode follower between the discriminator and de-emphasis network are the keys to the FM-1 tuner's remarkably low distortion figures. Whatever the reason, the unit's lack of harmonic and I.M. distortion is audible and impressive.

Dynaco will shortly have available a multiplex adaptor and a 10-watt amplifier. Both will sell for under \$35 and either will fit in the space on the tuner chassis.

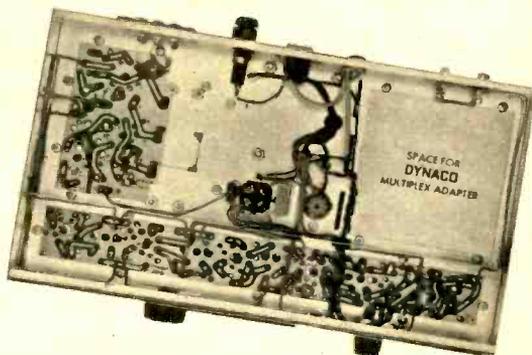Underchassis view shows mounting of the two printed circuit boards. The component parts are soldered in place before the boards are installed.





The **H. H. SCOTT LT-10** is a remarkable combination of simplicity and excellent performance. Although it's the most sensitive tuner (by 0.2 microvolts) tested and rates among the top three in audio quality, it uses only five tubes (plus rectifier) and two diodes. And it's simple enough for the novice to tackle with no qualms.

Like most of the kits in this report, the Scott comes with a pre-wired, pre-aligned front-end. It is unique, however, in that its front-end is silver-plated for high conductivity. A 6BS8 is a cascode front-end and a 6U8 is a mixer-oscillator. Two 6AU6's provide the tuner's two stages of IF amplification, and a single 6U8 serves both as a last IF limiter and audio output stage. The wide-band detector circuit uses diodes.

Scott's packaging and instructions for the LT-10 are outstanding. All parts are mounted and identified in order on separate cards for each construction stage. All insulated lead wires are pre-cut to size and pictorials are big, color-coded, and easy to read. The novice can feel right at home here.

Construction is extremely simple. The kit is broken down into 12 assembly groups of a few steps each, and a separate diagram is provided for each stage. Except for the cases where connections are made from the pre-wired front-end, each stage has its corresponding card of parts. The chassis is extremely roomy and all connections—electrical and mechanical—are easily made. The soldering of the two heat-sensitive diodes is the only critical job.

All sockets, terminal strips, etc., are pre-riveted onto the chassis. This is both a time-saving and trouble-avoiding step. It's little appreciated how much difficulty can arise in high-frequency RF circuits from poor grounding. Scott's attitude is obviously that if they go through the trouble and expense to copper bond the chassis to insure good conductivity, they don't want poor grounding on the part of the kit-builder to lose the advantages realized.

The home alignment specified by Scott

for the LT-10 is simple but effective. The tuning meter and, oddly enough, the pilot lamp, are the only visual aids needed to complete alignment, and the entire procedure takes a little over half an hour. Instrument alignment produced only a marginal gain in sensitivity, but did help cut down distortion slightly. Although a trifle low, the LT-10's output is adequate for any Scott or other modern amplifier.

It's hard to account specifically for the exceptional performance of such a basically simple circuit as the LT-10's, but exceptional it is. Scott has long been a proponent of wide-band design, particularly in the detector stage, and the bandwidth of the ratio detector in the LT-10 is actually 2 megacycles. Scott's combination of a silver-plated front-end and a chassis with copper bonded to aluminum also undoubtedly plays an important role in the LT-10's sensitivity—which checked out *better* than Scott's published figures. The tuner's sensitivity with both home and instrument alignment was the highest, by a slight margin, of any tuner tested. The achievement of 1.88 microvolts sensitivity by a *home alignment procedure without instruments* is an exceptional feat and a fine tribute to Scott's engineering.

The LT-110 kit, identical to the above, but including a built-in multiplex adaptor will be available shortly.

The novel packaging of the Scott kit enables the builder to construct the tuner in its shipping box.





The **HARMAN-KARDON Citation III** tuner, like the Citation preamps and amplifiers, is aimed at the well-heeled and demanding audiophile. It is the most expensive and most ambitious of the units tested for this report, and its overall performance is unquestionably outstanding.

The Citation's front-end uses a 6CW4 Nuvistor for the first stage. A grounded-grid RF amplifier/mixer (ECC85) and an ECF80 triode-pentode, serving both as oscillator and first IF amplifier, are located on the Citation's pre-wired IF strip. The second and third IF amplifiers are 6AU6's and two stages of limiting are supplied by 6BN6 gated-beam limiters. The discriminator employs a pair of semiconductor diodes, and its output is isolated from the de-emphasis network by a cathode follower (one triode of a 12AX7). The audio output uses both sections of another 12AX7 in a "feedback couple" configuration.

Packaging and instructions for the Citation III are up to the standards expected from earlier Citations. They are both excellent—as they must be to tackle a unit of this caliber. All components are grouped separately and in order of their use on special mounting cards. Excellent pictorials for each construction stage and close-ups of important steps are included.

As for construction, the Citation attempts to make it foolproof in every practical way. In addition to the pre-wiring of the Nuvistor RF stage, the Citation III kit also includes a pre-wired and sealed RF/mixer-osc./IF assembly (see photo). And, as with the other Citation units, a terminal board is used (in the cathode-follower and audio sections) for accessibility and uniformity.

Except for a tight corner or two, there is plenty of working space in the chassis and no special demands are made on the constructor for agility in either the mechanical or electrical connections. Despite the pre-assemblies, the complexity of the Citation III insures that you are going to

spend almost 20 hours putting the kit together. Take the kit in slow and easy stages—you'll avoid errors that way.


Harman-Kardon claims an audio frequency response three octaves above and below the audible range. Regardless of whether this kind of response is necessary, there's no denying the fact that the tuner's overall audio quality justifies the pains taken by its designers.


The Citation III incorporates a number of special control facilities not duplicated by any of the other kits covered in our report. In addition to the volume and tuning controls, the tuner's front panel sports an interchannel muting switch (and rear panel control to set the level of muting), an AFC on-off switch and a *local-distant* sensitivity switch to prevent front-end overload on strong stations. Two tuning meters are incorporated; one indicates the strength of the incoming signal, the other indicates channel center for precise tuning.

Home alignment of the Citation III is achieved with the aid of its two front-panel tuning meters. It is exceptionally effective and, as can be seen from our chart, little can be gained by instrument alignment. The tuner is as sensitive as any available and it is interesting to note that some of our tests produced slightly *better* results than Harman-Kardon's already superb specifications. Not that the improvement of 1 db in the signal-to-noise ratio or the 0.05 microvolt higher sensitivity has any real significance in terms of the performance of the tuner. But what our tests *do* demonstrate is that anyone constructing the H-K tuner kit need have no fear that his unit won't be the equal of a factory-assembled tuner.

The Citation III ran first or an extremely close second in every one of our tests. Its many refinements—both in circuitry and control functions—justify its premium price.

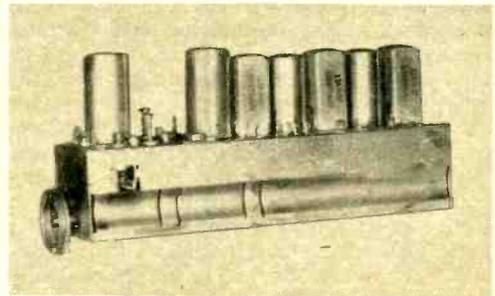H-K's prealigned and sealed RF, osc., and IF strip.



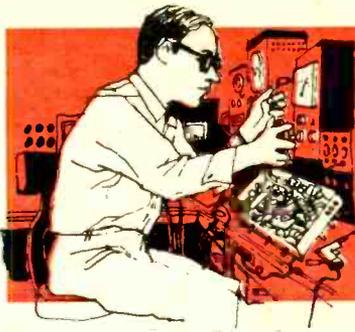

Tech Editor's

Test Bench

by Larry Klein

BESIDES the specific performance figures presented in our report, EI's experiences with the 11 tuner kits led us to some interesting generalizations.

For example, our tests showed that in general, the way to judge a tuner is *not* to count tubes but to look at the performance specs.

The audio output circuits show an interesting variety. There are three general types: the cathode followers, the "anode followers" and the outputs fed directly from the detector stage (see schematics below).

The cathode follower, most familiar to the hi-fi fraternity, provides good isolation between detector and output jack but has a gain of less than 1 and may be noisy.

The anode follower and "feedback pair" employs heavy feedback around one or a pair of triodes to achieve a gain of more than 1 and low distortion.

The third output method, direct coupling from the detector, is the least desirable. True, it does save the manufacturer a tube, but at the risk of high-


frequency loss and distortion (through loading of the detector).

There's a limit to the length of shielded cable that can be used with direct coupling without chopping off the top end of the audio signal. You can get away with cable lengths of three or four feet without running into trouble. If you need greater distance between tuner and preamp, you had best choose a tuner with a cathode or anode follower. If the manufacturer has a recommended cable length or provides a cable—use it. The design of the output stage may require the capacity of the cable to achieve proper de-emphasis of the signal.


Professional alignment of the tuners provided some surprising data. On some kits sensitivity improved, on others distortion dropped. And with a few, the gains on *any* factor were minimal.

This means that it is possible (when the tuner has a wide-band detector, pre-aligned sub-assemblies and a well thought out home-alignment procedure) to achieve close-to-professional alignment without a shop full of test equipment. Note that every tuner did benefit to *some* degree from professional alignment. Whether the improvement is worthwhile or even audible depends on the individual tuner.

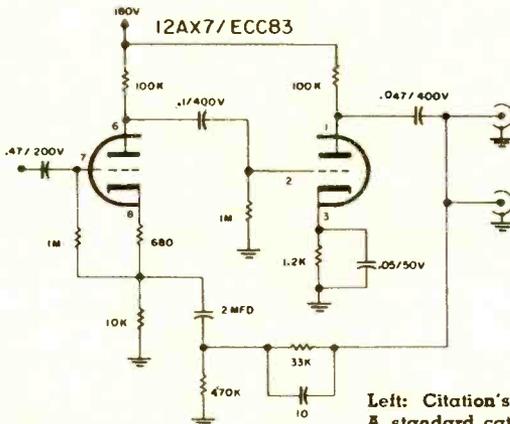A few tuner kits now on the market
[Continued on page 102]



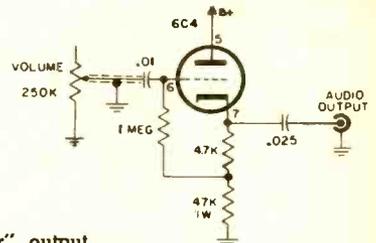Left: Citation's "feedback-pair" output. A standard cathode follower is at right.



CIRCUITS FOR

STEREO FM

ADAPTORS

Two basic multiplex adaptor circuits have appeared. Here's how they operate.

By Harry Kolbe

SINCE the Federal Communication Commission gave its approval to the Zenith-General Electric system of stereo multiplex FM, several circuits have been developed for adaptors which when connected to your present FM tuner makes possible stereo reception. Two basic circuits were designed by GE and Zenith at the beginning, and now there are adaptations of both, plus some new ideas.

The basic concept of stereo FM was taken up in the September '61 EI so we shall confine ourselves here pretty much to a technical discussion of circuitry. Suffice it to say that to receive stereo FM you must have either a multiplex stereo tuner or a standard tuner with a multiplex adaptor (both amount to the same thing) to separate the composite signal into its right and left components. (Multiplex is a method of transmitting two or more channels of information on the same carrier.)

Matrixing and Time Division

The receiving process for stereo FM, can be best understood by looking first at the *transmission* end. One type of stereo transmission originates in a matrixing system. There is a main channel

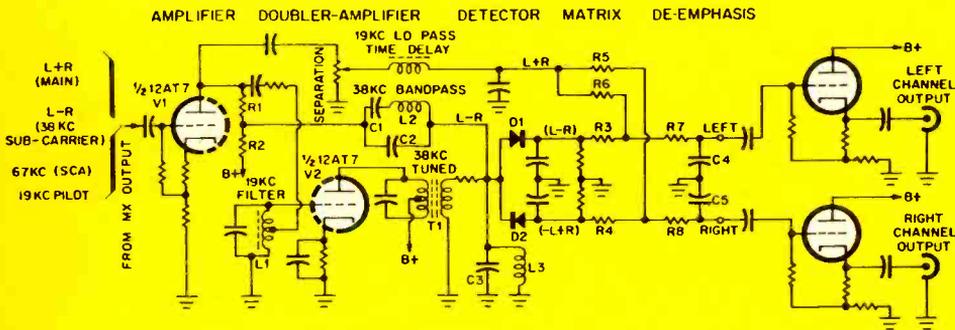


Fig. 2—General Electric stereo FM adaptor circuit.

signal which is the sum of the left plus the right (L+R) channels and also a subchannel or difference (between the left and the right channels—that is) signal (L-R). The difference signal amplitude modulates a 38-kc subcarrier. Sidebands appear as a result of the modulation—and then the carrier is suppressed.

In a second type of transmission, the time division system, the subcarrier modulating signal (L-R) is produced by a switching technique which samples first the whole L signal and then the whole R signal at the rate of 38,000 times a second (38 kc).

Signal Components

Both systems include a 19-kc pilot signal, and also may include a 67-kc SCA (Subsidiary Communication Authorizations) signal (background music for stores, restaurants, etc.).

Although the operation of an FM tuner is the same whether the incoming signal is multiplexed or not, the signal available at the tuner's multiplex jack is quite different. It contains these components (see Fig. 1):

1. The main channel or sum (L+R) signal, which occurs between 50 cps and 15 kc.
2. The stereo subchannel or difference (L-R) suppressed carrier sidebands, which occurs between 23 and 53 kc.

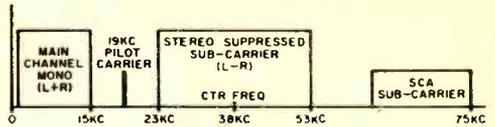


Fig. 1—Components of stereo multiplex signal.

3. A 19-kc pilot signal.

4. An SCA subcarrier, which occurs between 67 and 75 kc (optional).

The L+R signal (No. 1), de-emphasized and amplified, appears at the output jack of a normal tuner as a mono signal. The other components, attenuated by the de-emphasis network, are not audible. To recover the L-R (second channel) modulation you need a multiplex adaptor. As we said, several circuits to do this job have been developed but we will confine our discussion to the GE and Zenith designs.

General Electric Circuit

Let's look first at the GE circuit, which is a matrix type (see Fig. 2). The composite stereo-mono signal appearing at the output of the FM detector is fed via the tuner's multiplex output jack to the stereo adaptor. You will remember that this signal contains the components listed above.

The first stage (V1) of the adaptor amplifies the signal and provides isolation between tuner and adaptor. V1's output is fed [Continued on page 104]


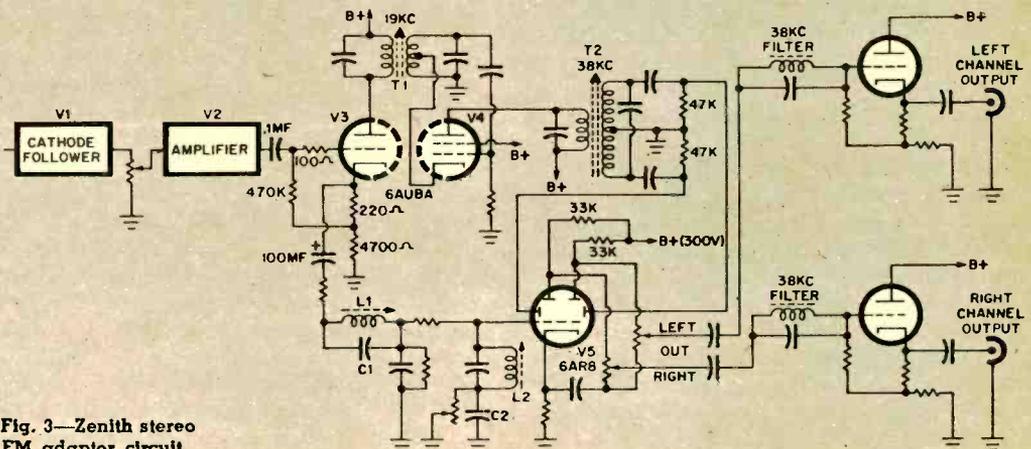


Fig. 3—Zenith stereo FM adaptor circuit.

ELECTRONIC BRAIN

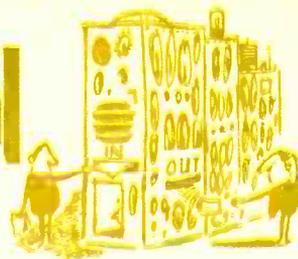


Have a question on electronics? Send it to **Electronic Brain**, *Electronics Illustrated*, 67 West 44th St., New York 36, N. Y. Enclose a stamped, self-addressed envelope for prompt reply.

Resistance Welding

What is a "resistance welder" and how does it operate?

*Richard Klenner
Dubuque, Iowa*

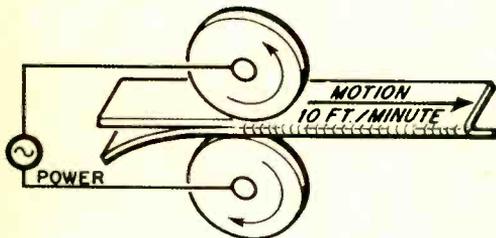Resistance welding is the process of joining two pieces of metal together by passing a heavy current through them so that intense heat is generated at the spot where the desired joint is to be formed. A small portion of each piece melts and the molten portions flow together. When the current is turned off, the metal cools and solidifies and a permanent bond or weld is formed.



All resistance welding systems consist of three general components: a power source, a system of electrodes for applying power to the pieces being welded, and a control system for timing the application of power. The design of these components depends on the materials and the type of weld.

There are three general types of resistance welders. Spot welding, as its name implies, is a method of joining two metals by concentrating welding current on a relatively small area, using small electrodes. Seam welding (shown) involves the use of current carrying wheels that replace the small spot-welder electrodes. The third type is the projection method in which high pressures as well as high electrically-generated temperatures are used.

Iron Heating Time

I have two 30-watt soldering irons, one is a standard 117-volt AC job and the other operates on 12 volts DC. Shouldn't the 12-volt iron heat faster since it draws more current and has a lower resistance?

*Maurice Gilbert
Montreal, Canada*

Since both irons are rated at 30 watts, one will heat as fast as the other provided that the mass of the metal tip and the conductivity rates are the same.

As long as the product of the voltage and current is the same, the time required to produce a certain amount of heat is the same.


The design of the iron determines the heating rate. A 30-watt iron with a massive tip will require more time than a 30-watt iron with a very light tip to reach the same temperature. If conductivity is good, the heating element can transfer heat to the tip quickly.

Resistor Substitution

If a project parts list calls for a 10,000-ohm, $\frac{1}{2}$ watt, 10% resistor, can I substitute a 1 watt, 5% resistor if I have one available?

*Raymond Burke
Jackson, New Jersey*

For all cases of resistor substitution, follow these rules: (1) Resistance value: Always use the resistance value specified; don't substitute larger or smaller values. (2) If you have available space on your chassis, you can always use a larger power rating than called for in the diagram. Never use a resistor with a lower rating. (3) You may always substitute a resistor of closer tolerance (such as 5%) for one of wider tolerance (20%), although this is rather uneconomical. Never substitute a wider tolerance, however.

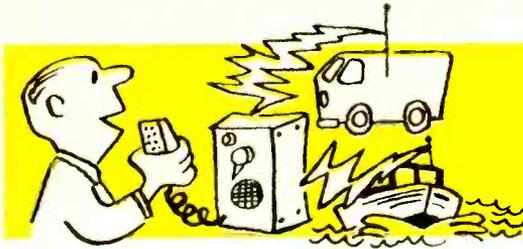

CB CORNER

Citizens Band News and Comments

by Len Buckwalter, 1W5733

WANTED . . . Although a great variety of Citizens Band equipment can be found on the market, we Cbers often have a need for some particular apparatus or design that simply cannot be purchased.

Take the owner of a brand-new mobile rig. He has a lot to be proud of . . . a shiny whip at the rear of his car and an impressive transceiver under his dash to draw the admiration of friends and neighbors. But after so long, the rig becomes important for what it does rather than for its appearance. At this point, the underdash mounting begins to irritate.

The favored mounting point is in the center of the dash, which is fine when you have just a driver and one passenger. But when you pack in three people the guy in the center just may complain while his legs get barked and his kneecaps start forced migrations.

There's another reason to question that center-dash location when the driver has to stretch to reach the transmit-receive switch and other controls. It makes for dangerous driving.

Some manufacturers have taken a step in the right direction with a push-to-talk microphone button and related circuitry. But we'd like to see them go one step further by removing the transceiver from the passenger compartment entirely (see sketch at bottom).


Take a look at a police radio installation and you'll find a mike or handset and tiny control box within easy reach of the driver. The transceiver is stowed in the trunk. This makes sense and leaves the under-dash free for (in private cars) an increasing number of other accessories.

The technical considerations for removing a CB transceiver are not complicated. We could put the important controls (on-off, squelch, channel selector, volume) in a small box mounted on or close to the steering wheel column. A cradle would hold the handset (or mike if you want to use the loudspeaker). We'd mount the transceiver in the forward section of the trunk, close to the whip antenna. This would reduce noise pickup from the ignition system.



Pro Features . . . Don't misunderstand me. Over the past three years we've seen some marvelous advances—improved receivers, multichannel performance, etc.—that have lifted the transceiver out of the wireless mike class and *almost* put it into the same league with commercial communications gear. My point is: why stop at *almost*? As CB becomes increasingly important to the general public, the need for professional features emerges.

[Continued on page 112]

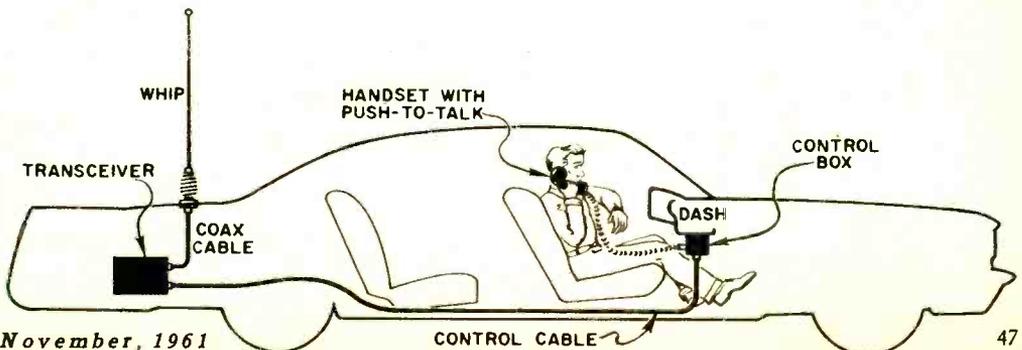

Win \$100 in EI's ELECTRICITY Contest!

HAVE YOU entered EI's Electricity Contest? If not, sit down today and write us your answer to the question, "What is electricity?" If you have entered, try again! It's fun, it's easy . . . and the best answers win their authors \$100. One winning answer is published in each issue.

Remember, you can use any source material desired, but your answer must be in your own words. Just follow the rules at right.

Entries for cash prize No. 4 must be received by November 1, 1961.

Below is our latest winning entry.

Rules: Entries will be judged on aptness of thought, clarity of expression and originality. Entries must be typewritten and double-spaced and may be no longer than two pages of 8½ x 11-inch paper. Ideally, a definition should be short. Print your name and address on your envelope and the first page of your answer. One entry per envelope. EI's Editors are the judges. Entries will not be acknowledged or returned.

Prizes: \$100 will be paid the writer of the best definition. One winning definition will be published in each issue of EI. In case of ties, duplicate prizes will be awarded. Other entries of merit also may be published and will be paid for at the rate of \$10 each.

Mail entries to: EI Electricity Contest, 67 W. 44th St., New York 36, N. Y.

WHAT IS ELECTRICITY?

"The nature of electricity is determined by the particles of the atom which carry a negative charge and are called electrons. These electrons orbit about a positive nucleus, composed mainly of protons (positive particles), in shells or energy levels. Each energy level can hold only a certain number of electrons. In the atoms of electrical conductors the outermost electrons, being farthest from the nucleus, jump easily from atom to atom. During their inter-atom trips they are called free electrons, and they move in a haphazard manner. When we make them move in an orderly manner we have a flow of electric current. To do so, we establish an excess of electrons at one end of a conductor and a deficiency of electrons at the other. The electron-deficient atoms at the positive end attract some of the free electrons in the conductor. Electrons flow in turn from the store of excess electrons at the negative end to replace those attracted by the electron-deficient atoms. This series of actions is due to the fact that an atom in its normal state is electrically neutral and it attempts to maintain this condition."

Dale P. Kingsbury
Mabel, Minn.

for on-the-nose RF accuracy

A Dual-Frequency Crystal Calibrator


By Herb Friedman, W2ZLF

TO MANY, a crystal calibrator is just a means of complying with one of the FCC requirements. But for others, amateurs, experimenters and SWLs, the crystal calibrator is an important tool; useful for calibrating home brew receivers and converters, zeroing bandspread dials on communication receivers and insuring accuracy of test equipment. For the usual cost of a factory-wired single-frequency calibrator (about \$15), you can build a calibrator having *both* a 100 kc and 1 mc output. Each output is independent and can be individually calibrated against WWV. The 1 mc output is of particular advantage on the very high frequencies since there is much commercial and home brew equipment for 6 meters (and some for 10 meters) using superregen receivers. The 1 mc markers will clearly indicate the band edges.

Construction

The major components are mounted on a piece of perforated board as shown in the pictorial. The crystal socket is mounted with a 4-40 screw using a $\frac{1}{4}$ " spacer or stack of washers between the socket and the perforated board.

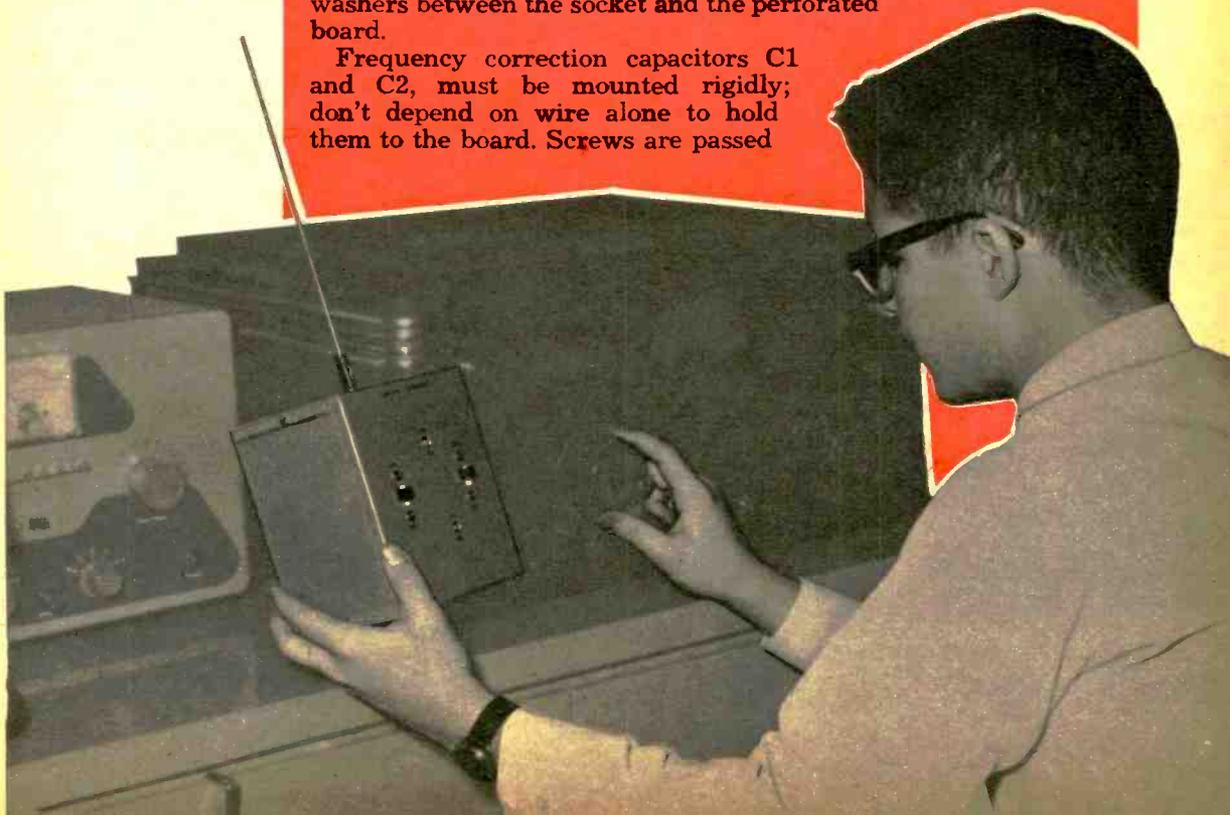Frequency correction capacitors C1 and C2, must be mounted rigidly; don't depend on wire alone to hold them to the board. Screws are passed



through their solder tabs and the board and connection is made to the supporting tab by a solder lug or by wrapping wire around the mounting screw. Use a heat sink such as an alligator clip on the lead when soldering the transistors. Note that transistor Q2 (2N274) has four leads; the center shield lead is unused and should be cut short.

After the board wiring is completed, mount switches SW1 and SW2 and antenna jack J1 on the cabinet. Two $\frac{3}{8}$ " holes should be drilled to permit adjustment access to C1 and C2.

An L-bracket at each end of the board is sufficient for mounting. Take care that the adjustment screws of C1 and C2 do not touch the cabinet and that there is room for the battery. The antenna is made from an 8"-10" length of stiff wire.

Adjustment

Before applying power, adjust coils L1 and L2, aligning the bottom of the slugs with the lower coil winding. Remove the crystals from their sockets and connect up a 10 ma meter in series with the battery. Turn on the unit and if the calibrator is wired correctly the meter will show only a slight indication

(about 150 microamperes). Install the 100 kc crystal and set SW2 to the 100 kc position; the meter will read about 3.5 ma. Adjust L1 for maximum current flow. The tuning is very broad and if after four turns there is no change in current, leave the slug where it is.


Next, plug in the 1 mc crystal and set SW2 to the 1 mc position. Repeat the above, adjusting L2 for maximum current. Disconnect the meter and the calibrator is ready for use.


For precision use, the two outputs can be tuned against WWV. Tune in WWV at a frequency which provides a medium signal level. Turn on the calibrator set to 100 kc and let it warm up for about a minute. Couple the calibrator's signal into the receiver either by radiation or by direct connection. A distinct beat-note will be heard in the receiver. Using an insulated alignment tool, adjust C1 so the beat-note changes to a low growl and disappears. This is the correct setting for C1. Repeat the same procedure for the 1 mc crystal, adjusting with C2.

Checking Mobile Equipment

A mobile receiver or converter can easily be [Continued on page 101]

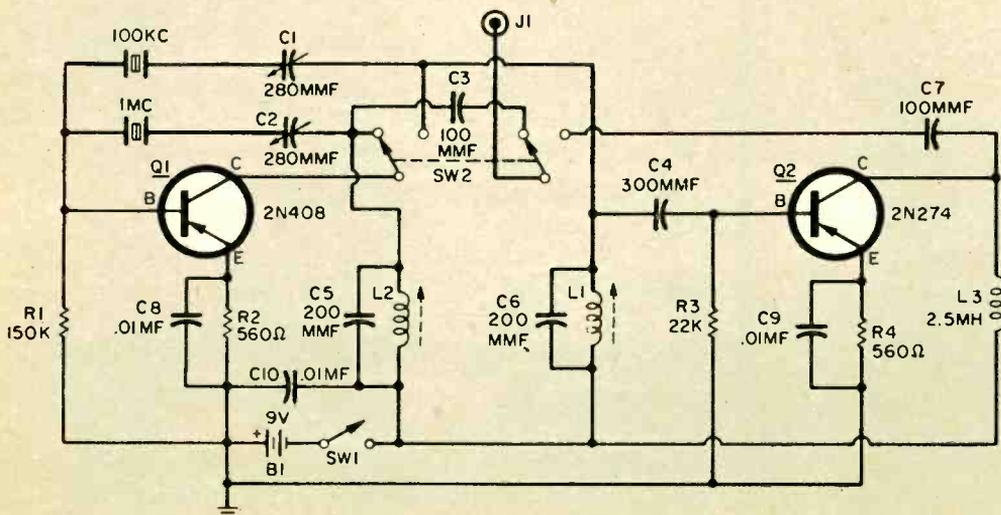Separate crystals and calibration capacitors are used for each of the two fundamental frequencies.



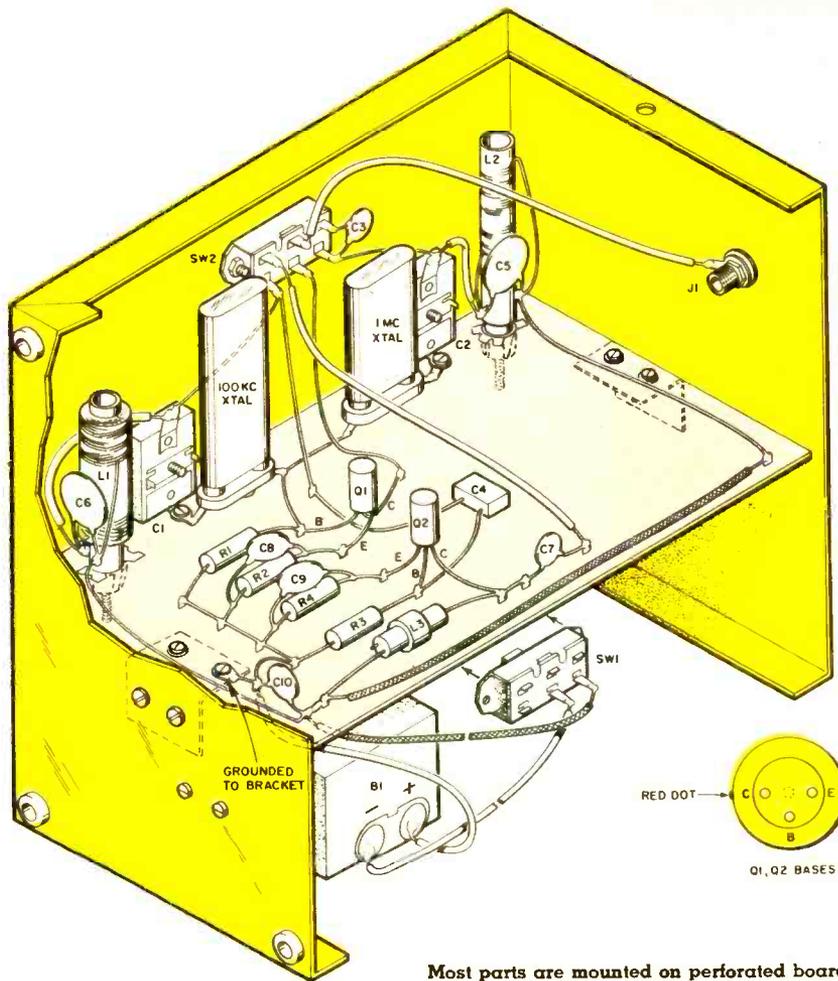

Most parts are mounted on perforated board which is installed in cabinet using small brackets.

PARTS LIST

Resistors; 1/2 watt, 10%

- R1—150,000 ohms
- R2, R4—560 ohms
- R3—22,000 ohms

Capacitors

- C1, C2—25-280 mmf, trimmer capacitor
- C3, C7—100 mmf ceramic disc
- C4—300 mmf mica
- C5, C6—200 mmf ceramic disc or mica
- C8, C9, C10—.01 mf ceramic disc
- S1—SPST slide switch
- S2—DPDT slide switch
- L1—2.18 millihenry slug tuned coil (Miller 6314)
- L2—54-245 microhenry slug tuned coil (Miller 6196)
- L3—RF choke, 2.5 millihenry
- Q1—2N408 transistor
- Q2—2N274 transistor
- B1—9 V battery (largest that will fit cabinet)

Misc.—

- 1 perforated board (Lafayette Radio MS-305);
- 1 cabinet 6"x5"x4"; 1 banana plug to fit J1; 2 packages flea clips (Lafayette Radio MS-263);
- 2 crystals (xtal) 100 kc, 1 mc plus sockets (Use Texas Crystal units as other types may not work properly.)






a high school student's Radio Telescope

Celestial radio signals record themselves on a simple system that uses standard receivers.


By H. Mark Wahl

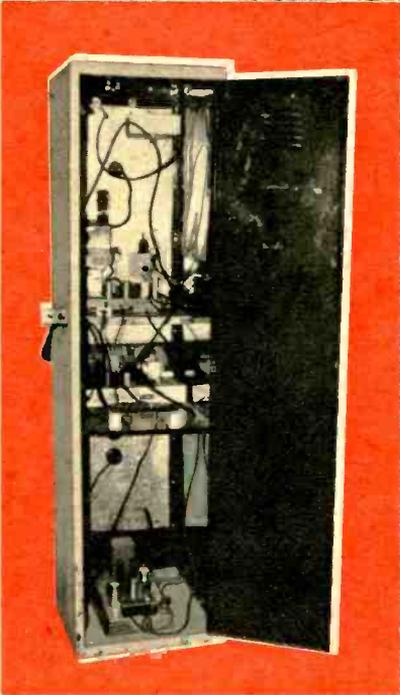


A RADIO telescope is essentially a receiver. It detects and records the emissions of objects whose atoms give off energy in the radio band of the electromagnetic spectrum.

The heart of a simple radio telescope I built as a high school student in Cheyenne, Wyo., is a standard FM receiver converted to AM (celestial static is AM) by eliminating its limiter and discriminator sections. Next, a tuned RF amplifier was placed ahead of it for higher sensitivity and gain. Then I connected a communications receiver to the IF output of the FM radio and tuned it to the FM set's intermediate frequency (10.7 mc). The SW set thus provided detection and audio output to two recorders.

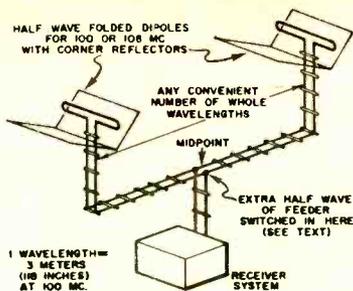
The first recorder employs a pivoted wooden arm which holds a pen against moving graph paper (see diagram) and at its other end is attached to a speaker voice coil. The coil moves in accordance



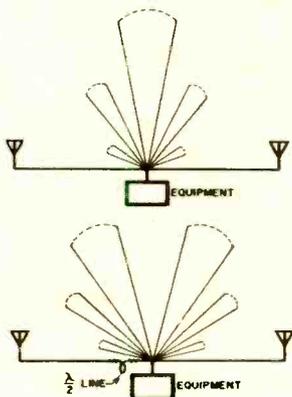
Dipoles are whole wavelengths apart. The extra feeder length is switched in and out on one side.



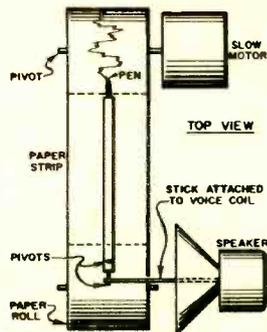Feeder switching above cuts main lobe in and out to make signal stand out from background noise.



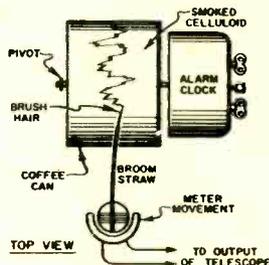Stick holding a pen and attached to voice coil records celestial noise on moving graph paper.



Broom straw controlled by meter movement writes a 12-hour celestial-noise record on celluloid.

with the receiver output and these movements are recorded as a line on the graph paper.

The second recorder uses a meter movement with a broom straw tipped with a brush hair installed in place of a pointer. The brush hair moves back and forth on a piece of smoked celluloid wrapped around a clock-rotated drum, leaving an accurate trace.

All my receiving apparatus was mounted in a school locker (shown on opposite page). The door of the locker became the back of the cabinet. From the bottom, the equipment shown is the power supply, communications receiver, FM set, interferometer equipment (see below) and RF amplifier.


The antenna is all-important in this system, of course. I used two 108-mc folded-dipole antennas with corner reflectors, spaced about 100 feet apart for what is known as an interferometer effect. With this arrangement, the an-

tennas can be made rapidly to receive and then not receive the radio source when a half-wavelength of extra feeder line is switched in and out of the lead-in of one dipole.

This is the way it works: the two dipoles are placed parallel and horizontal any convenient number of whole wavelengths apart to put their energy outputs in phase at the receiver. The feedlines must be of the same length.

With the two dipoles in phase, their pickup pattern has a strong lobe straight up. When an extra half-wavelength of feedline is switched into either feeder, the dipoles are thrown out of phase and the straight-up lobe simply disappears, leaving only the surrounding background noise. When this background noise level is subtracted by the receiver from the straight-up lobe, what you have left is a clear signal from a sky source. The system is relatively simple, but it works!

THE

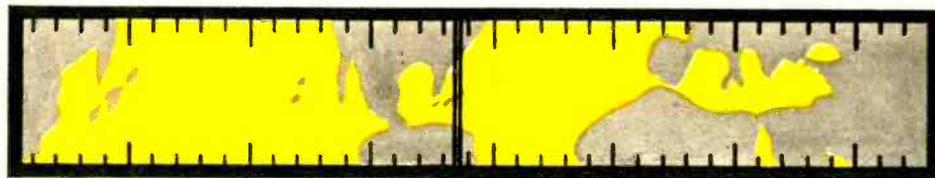

LISTENER

Notes for the short-wave listener and DXer



By C. M. Stanbury II

THE LIARS . . . Regular short-wave broadcasts began in the 1930's but short-wave listening did not come of age as a hobby until the Fifties. Prior to this, most writings on the subject consisted of a sales talk that can be summed up in one line, "listen to short wave and know the world." Just like that.


A lot of people who, one would suppose, wanted to know the world fell for the line. Not a few soon discovered that successful listening involves more than just owning a set, so they simply quit. Those who became serious listeners—who were interested in more than QSL cards and understood something of the potentials of short wave—exerted little influence on the field, unfortunately. Not many people in North America have ever viewed short-wave broadcasts as a medium for the exchange of ideas, of international understanding, of education and all the other worthy goals. Consequently, relatively few (when you consider total population) ever have bothered to listen.


As a matter of fact, when you examine the short-wave picture in detail,

you find few broadcasters anywhere who have even tried for those high goals we mentioned. Such stations as Radio Moscow and, two decades ago, Hitler's radio outlets, have shown how far away from the truth you can get.

A good many SW services are judged merely by their QSL service, with quality and quantity of information being viewed as secondary considerations. And some who *do* seek information in SW broadcasts tend to swallow it whole, even when it's from Moscow or Peiping.


However, most of us are getting craftier about interpreting what we hear or don't hear on the air. We know few things are quite as they seem, or are described, and that rare is the station that sticks strictly to the truth, East or West. Had Raphael Trujillo's assassination occurred ten years ago it is doubtful that many listeners who tuned in Radio Caribe (see QSL card at bottom) on the afternoon of last May 31 would have made much of the fact that nothing but music and commercials were being transmitted and all news programs had been [Continued on page 99]

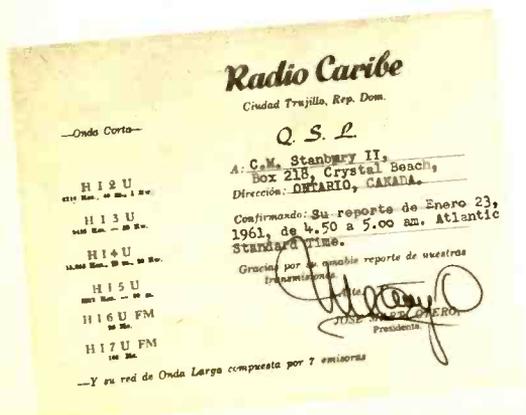

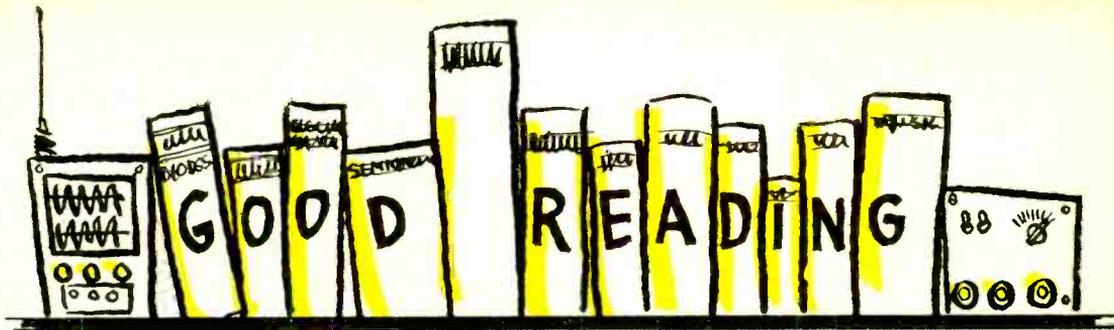

THE INTELLIGENT MAN'S GUIDE TO SCIENCE. *Two Volumes: The Physical Sciences and The Biological Sciences.* By Isaac Asimov. Basic Books, New York. App. 850 pages each. \$15 a set

Here are two valuable volumes for anyone interested in the world and the universe around him. Isaac Asimov, an excellent, fluent writer with several fine science books to his credit, has now made it possible for anyone with the necessary curiosity to learn easily and enjoyably most of the facts now known about man and his universe. Separating the physical and biological sciences into two volumes, he spreads out a vast panoply of knowledge for easy inspection. The illustration below, from the book, shows the smashing of a silver atom by a cosmic ray. The lines are

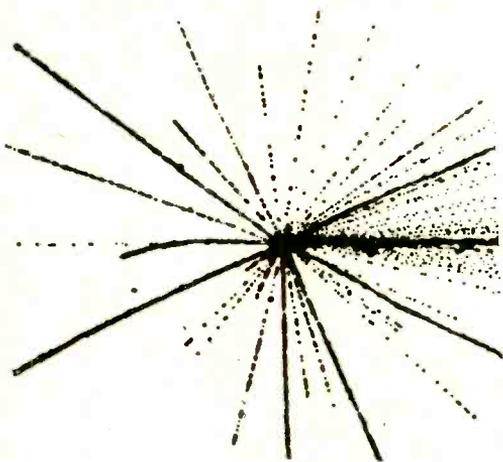

tracks left by the resulting 95 nuclear fragments.

Despite the ambitiousness of Mr. Asimov's project, there is nothing that should be forbidding to the average intelligent reader. The writing itself is crystal-clear and the contents are beau-

tifully organized for the reader with no vast scientific background.

Mr. Asimov begins at the beginning—with the molecule and the atom. And in both volumes he builds his subjects so well that they seem to fall effortlessly into place in your mind, as if they had sneaked in when you weren't looking. What does he cover? Everything from nuclear physics to psychoanalysis; everything from the birth of the solar system to the future of man and his earth in it. If you're interested in filling in the gaps in your knowledge of science, forget the encyclopedia and concentrate on these two volumes. They are far and away the best books of their kind, and they are unlikely to be challenged for a long time to come.

BASICS OF ANALOG COMPUTERS. By Thomas D. Truitt and A. E. Rogers. John F. Rider, New York. 400 pages. \$12.50

For those who feel that computers are trying to be too human these days, analog computers are more fascinating than their digital relatives. The analog computer does more than count, it learns by example and parallel, and can make uncanny predictions based on what it knows. The authors of this book know their subject well and present it clearly. And the book itself is as packed with facts as any computer. But the illustrations are another matter. There are just too many of them at times. They get in the way. There is plenty of useful, important information here, but a picture is not always worth a thousand words.

ABC'S OF RADAR. By Alan Andrews. Howard W. Sams & The Bobbs-Merrill Co., New York & Indianapolis. 112 pages. \$1.95

Now that radar has gone civilian in so
[Continued on page 103]

High-Flying Ham



El's Contributing Editor on Amateur Radio goes on a memorable flight into the blue with KØDWC.

By Robert Hertzberg, W2DJJ

THE altimeter in the cockpit of the C-97 Stratotanker read 15,000 feet as the giant plane droned eastward over Pennsylvania. Back in the passenger compartment, an Air Force officer wearing the three stars of a lieutenant general sat at a small console containing a single sideband transceiver. He adjusted the equipment for the 15-meter ham band, pressed the button on a hand microphone and spoke into it.

"CQ 15, CQ 15. this is K Zero DWC mobile, K Zero DWC mobile."

The transmission lasted hardly five seconds. As he released the button a

babel of voices boomed out of the speaker.


"One at a time, boys," said the officer. "Kurt, did I detect your fine Irish accent in there?"

"Hello, Butch, glad to hear you on again," came the reply, with a marked Swedish inflection. "Yes, this is W2ZXM maritime mobile. Heard you were sick, Butch. How are you feeling?"

"Okay now, Kurt. Where are you?"

"We're in the Pacific about 600 miles northwest of San Francisco."

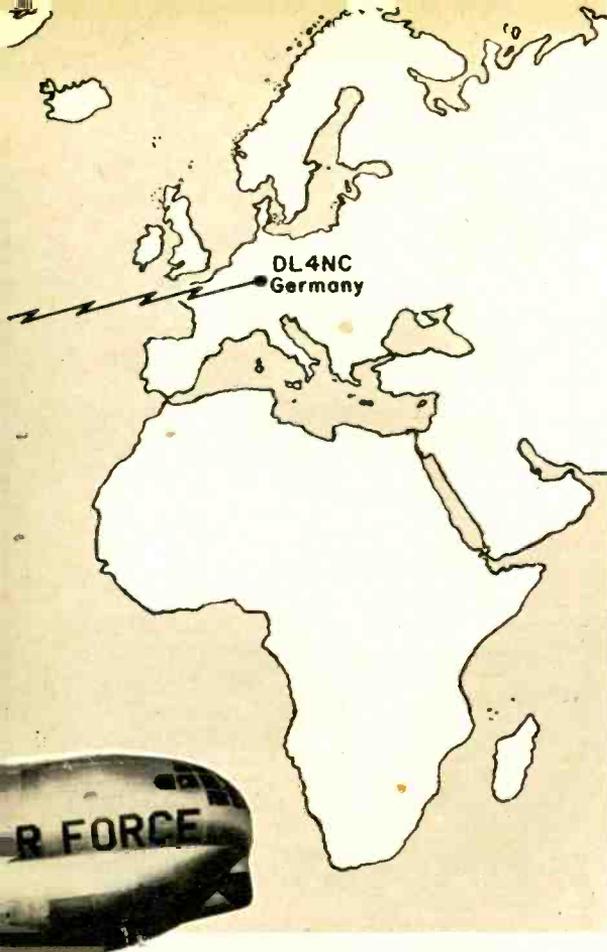The sea-going W2ZXM was Capt. Henrik Carlsen, skipper of a freighter



named Flying Enterprise II. A few years ago he achieved fame when he stayed on his sinking Flying Enterprise I until the last moment.

Other strong signals rattled the speaker.

"K Zero DWC mobile, this is DL4NC. Butch, I thought you'd like to know that you're coming in fine in Germany."

As the general scribbled call letters in his log, two other stations popped in.

"K Zero DWC, this is KZ5AA. There's nothing wrong with your signals in the Canal Zone, either."

"Hey, Butch, add me to the list. This is KL7DKU, Kodiak, Alaska."

And so it went. The officer sat there in his airplane three miles in the sky and talked to friends all around the world.

This high-flying ham, universally known as Butch to fellow amateurs, is Lt. Gen. Francis H. Griswold, 57-year-old Vice-Commander in Chief of the Strategic Air Command. I was interviewing him one day recently at SAC headquarters at Offutt Air Force Base, near Omaha, when he was summoned to a conference with the Chief of Staff in Washington. Since I was there on a two-fold mission—to discuss his ham radio activities, as well as SAC's communication facilities—he offered me an airborne demonstration of his equipment. My official travel authorization was not long in coming, needless to say.

The fun started hours before take-off when Butch took me to the hangar to show me through the C-97 he would use. The C-97 is a transport version of the KC-97 flying tanker. (A typical tanker version of the plane is shown in our lead illustration.) Gen. Griswold's plane is much like a lot of other C-97's, except he has installed a compact ham station, which operates independently of the Air Force communications equipment used by the flight crew.

The day was bitterly cold, so the doors of the hangar were shut tight. Butch flipped on the transceiver just to see if it was hooked up and we nearly flipped ourselves when W2KR roared in with, "Butch, is that you?"

He'd made a Nebraska-to-New York contact from inside a shielded building, and with just an unmodulated signal. As I already knew, and was soon to



Gen. Griswold, the high-flying ham, operates his transceiver on C-97 on Omaha-Washington hop.



Coveted four-color QSL card from "Butch" shows plane flying over mountains and inside shot on back. The author received this card after 1958 contact.

have proved to me again, Butch is a popular guy on the amateur bands. Dozens of hams seemingly lie in wait for him and when they hear any signal near his known haunts they automatically assume (or hope) it's KØDWC.

The four quick contacts on 15 meters which I described earlier (and are indicated on our map at the head of this article) were the most spectacular communications on our flight, but activity on 20 meters was more continuous. From take-off at 10:24 until landing four hours later, with a short break for a sandwich lunch, we took turns

working the scores of hams who were anxious to obtain KØDWC's prized four-color QSL card.

We talked to locals in Nebraska, Iowa, Illinois, Indiana, Ohio and Pennsylvania as the plane passed almost over their antennas, and to others in California, New York, Canada, Florida, Alabama and Massachusetts. Via phone patches by cooperating ground stations, Butch spoke to a friend in Cedar Rapids, Iowa, and to his daughter in Washington. Through W2KR, who seems to be on the air all the time, I got

[Continued on page 100]

KØDWC works a station from shack on the ground at Offutt AFB, Neb. He uses Collins equipment.



El's Bob Hertzberg (lower right) takes a turn at the mike while on flight with Gen. Griswold.



NOW!
at a price
you can afford!



MAKE MORE MONEY in ELECTRONICS TELEVISION-RADIO

**BETTER...MORE COMPLETE...LOWER COST...
WITH NATIONAL SCHOOLS SHOP-METHOD
HOME TRAINING!**

BETTER... Training that is proved and tested in Resident School shops and laboratories, by a School that is the **OLDEST** and **LARGEST** of its kind in the world.

MORE COMPLETE... You learn **ALL PHASES** of *Television-Radio-Electronics*.

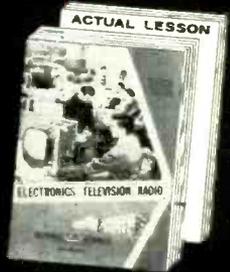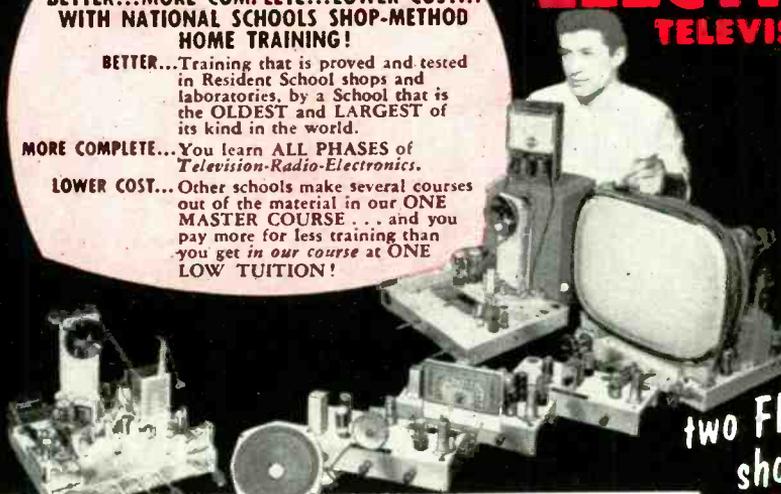LOWER COST... Other schools make several courses out of the material in our **ONE MASTER COURSE**... and you pay more for less training than you get in our course at **ONE LOW TUITION!**



These
two FREE books will
show you how!

TOP PAY... UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry! Trained technicians are in growing demand at excellent pay—in **ALL PHASES**, including Servicing, Manufacturing, Broadcasting and Communications, Automation, Radar, Government Missile Projects.

NATIONAL SCHOOLS SHOP-METHOD HOME TRAINING, with newly added lessons and equipment, trains you in your spare time at home, for these unlimited opportunities, including many technical jobs leading to supervisory positions.

YOU LEARN BY BUILDING EQUIPMENT WITH KITS AND PARTS WE SEND YOU. Your National Schools course includes thorough Practical training—**YOU LEARN BY DOING!** We send you complete standard equipment of professional quality for building various experimental and test units. You advance step by step, perform more than 100 experiments, and you build a complete TV set from the ground up that is yours to keep! A big, new TV picture tube is included at no extra charge.

EARN AS YOU LEARN. We'll show you how. Many students pay for their course—and more while studying.

**GET THE BENEFIT OF OUR
OVER 50 YEARS EXPERIENCE**

APPROVED FOR
GI TRAINING



ACCREDITED
MEMBER



NATIONAL SCHOOLS

World-Wide Training Since 1905

Write to Dept. R4Y-101

4000 So. Figueroa Street
Los Angeles 37, California

YOU GET...

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

**IMPORTANT
SEE OTHER SIDE**

You get all information
by mail... You make
your own decision... at
home! **NO SALESMAN
WILL CALL**

**SEND FOR FREE FULLY-
ILLUSTRATED BOOK AND
ACTUAL LESSON TODAY.**
Your own copy of "Your
Future In Electronics-Tele-
vision-Radio" will be mailed
to you at once. No salesman
will call; there is no obliga-
tion. Cut out card along dot-
ted lines, fill in and rush
air-mail today!
NO POSTAGE NECESSARY.

CUT OUT AND MAIL THIS CARD TODAY

Yes, I want to make more money in Electronics-
TV-Radio. Send me your **FREE Fully-Illustrated
Opportunity Book and Actual Lesson** today.



RUSH AIR MAIL—NO POSTAGE NECESSARY

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Check here if interested only in Resident Training at Los Angeles. R4Y-101
Veterans: Give date of discharge _____

NO SALESMAN WILL CALL; NO OBLIGATION ON YOUR PART

DON'T BE HALF-TRAINED

Be a MASTER TECHNICIAN in ELECTRONICS-TV-RADIO

Only N.T.S. offers you ALL 8 PHASES in
ONE MASTER COURSE



SUCCESS IS THEIRS; IT CAN BE YOURS TOO!



When I enrolled with N.T.S. last November, I was trained as a Seismograph Observer. I was promoted to that job on May 1st of this year. With your school and my practical work in the field, my superiors recognized that I was capable of handling the job of Seismograph Recording. My superiors highly praise your school. The day I enrolled started me off to success.

Edgar Westzke

As field director of Berean Mission Inc., I have complete charge of our radio work.

With the expert advice and training I am receiving from you I can do my own repairs on our recorders and P.A. systems, besides keeping our radios going. My training from N.T.S. helps keep us on the air. I feel privileged to be a member of such a fine institution.

Rev. Enoch P. Sanford



Thanks to N.T.S. I have a business of my own right in my home. I am still in the Air Force but I have paid for all my equipment with money earned servicing TV sets. Yes, N.T.S. gave me my start in television.

Louis A. Tabat

I have a TV-Radio shop in Yorkville, Illinois, about 4 miles from my home, and it has been going real good.

I started part-time but I got so much work that I am doing it full-time. Thanks to National Technical Schools.

Alvin Spera



ALL 8 PHASES IN ONE MASTER COURSE

**PHASE 1
TELEVISION**
INCLUDING COLOR TV
90% of homes have at least one set. Color TV is becoming more popular daily. TV Stations grow in number, need technicians. Maintenance and repair offer big opportunities.

**PHASE 5
FCC LICENSE
PREPARATION**
FCC License holders have a wide range of top jobs open to them. FCC License now a requirement for most Communication jobs.

**PHASE 2
RADIO—AM & FM**
Radios in homes, cars, schools, all need expert upkeep. Stations expand as FM becomes popular. Now transistors boom entire field.

**PHASE 6
RADAR AND
MICROWAVES**
These are the communications systems of the future, already used in tracking and contacting satellites.

**PHASE 3
ELECTRONICS**
Computers, Data-Processing machines, Electronic Controls, Guided Missile Systems are new fields where Electronics play a vital role.

**PHASE 7
AUTOMATION
& COMPUTERS**
Automation and Computer electronics are the new tools of industry and commerce. Skilled Technicians in these fields are in great demand at top pay.

**PHASE 4
SOUND SYSTEMS**
New popularity of Hi-Fi-Stereo, as well as industrial sound systems and business intercoms make this a highly specialized and important field.

**PHASE 8
BROADCASTING &
COMMUNICATIONS**
In the entertainment industry, or in commerce, communications and broadcasting have great importance. Installation and maintenance of equipment requires trained technician know-how.

SEE OTHER SIDE

FIRST CLASS

Permit No. 3087

Los Angeles, Calif.

BUSINESS REPLY MAIL
NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

VIA AIR MAIL

— POSTAGE WILL BE PAID BY —

NATIONAL TECHNICAL SCHOOLS
WORLD-WIDE TRAINING SINCE 1905

4000 So. Figueroa Street
Los Angeles 37, California

RESIDENT TRAINING
AT LOS ANGELES

If you wish to take your training in our famous Resident School in Los Angeles—the oldest and largest school of its kind in the world—check special box in coupon.



Approved for GI Training

NATIONAL TECHNICAL SCHOOLS
WORLD-WIDE TRAINING SINCE 1905

Address correspondence to Dept. R4Y-101
4000 So. Figueroa Street
Los Angeles 37, California

National Technical Schools also offers complete Home Study Training Programs in Auto Mechanics & Diesel and Air Conditioning-Refrigeration-Electrical Appliances. For information and Free Book write the School, Department RDC, stating course desired.

SEE THE ALL-NEW, MOST
COMPLETE ELECTRONICS
CATALOG IN AMERICA!

Send for
**RADIO
SHACK'S**
BIGGER,
BETTER



FREE

Electronics CATALOGS

for one full year!

Get the giant 1962 Buying Guide plus
every other issue for 1961-62.

OVER
100,000
ITEMS!

Stereo, Hi-Fi,
Tapes, Records
Ham Radio
Parts and
Accessories

NEW 30-pg.
LINE OF
KITS

Fascinating
build-it-yourself
kits for
amateurs
and pros!

NO MONEY
DOWN

New easiest credit
terms in our history!
No down payment
on any item . . .
up to 2 yrs. to pay.

FILL IN THIS CARD,
TEAR OFF AND MAIL
TO RECEIVE YOUR

FREE

**year's subscription
to Radio Shack's
Electronics CATALOGS**

FREE 336-page giant catalog for 1962 with more
lines, bigger values than ever before

FREE catalog supplements as issued for one full
year—loaded with exciting values

You'll see more, save more on the best in elec-
tronics for everyone! **SATISFACTION GUARANTEED**

RADIO SHACK CORP.

Dept. 61L8

730 Commonwealth Ave., Boston 17, Mass.

Please send me **FREE** and **POSTPAID**, Radio
Shack's electronics catalogs for one full year.

Name _____
(please print)

Address _____

City & Zone _____

State _____

Don't miss this **FREE** offer

SEND CARD TODAY

PLACE
3¢ STAMP
HERE

RADIO **SHACK** **CORP.**

730 Commonwealth Avenue

Boston 17, Massachusetts

SEND CARD AT LEFT FOR
**RADIO SHACK'S
EXCITING 1962
Electronics CATALOG**

It's all new, it's 2/3 bigger,
better in every way and it's

FREE

- See the most complete line of Electronic Equipment and parts for every purpose
- See money-saving prices made possible by Radio Shack's giant quantity-buying
- See famous makes and our own money-saving "Realistic" brand
- See new 30-page line of hobby kits for beginners or serious amateurs

NO MONEY DOWN
on any item!

Just fill in card and mail. We'll send you our latest big book PLUS all other issues for one full year of super savings!



Phasing Stereo Headphones



JUDGING by the number of hi-fi earphones appearing on the market, private listening to stereo must be gaining in popularity. Here's a quick and simple way to test these phones for optimum phase relationship.

Turn up the volume just enough so

you can hear the music clearly with the phones about 12" away from your ears. Hold the phones as shown above and in Position A with about 2½" or 3" between the phones. Now, while maintaining about the same spacing between the phones, reposition the earpieces as shown in B. If the volume increases at B and fades at A, then the phones are out-of-

phase. The out-of-phase phones fade at A because the sound waves cancel. When both phones are in-phase, there will be little or no change in volume.

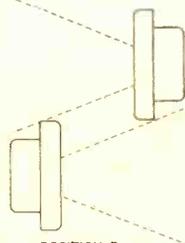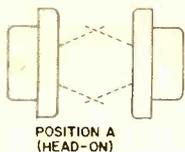If the headphones are out-of-phase, reverse the connections to one of the earpieces.



—Art Trauffer



RADIO SHACK'S 1962 CATALOG NATIONWIDE STANDARD OF EXCELLENCE in Electronics, Music and Communications

RADIO Shack Corporation of Boston, Massachusetts, took its name long ago from the term used for the communications center of a ship. The "radio shack" aboard ship is the vessel's only contact with the outside world—it is the focal point of all news—it is the very center of safety control. Consequently, its equipment is the best and most reliable, its personnel highly trained and skilled in radio, electronic and communication techniques.

Radio Shack Corporation is located in the city called the educational, cultural and scientific "hub" of America. Over the years we have become the communications, music and electronic center for that rapidly expanding group of people—amateurs, professionals or just plain fans—who enjoy the fascination of things electronic.

LAST year, Radio Shack filled over 1,000,000 orders from more than half a million people to become America's fastest growing electronics company. This year we have published the best and most complete catalog in our 38-year history. And we want to send you a FREE personal copy. Read about this catalog below and then mail the card at left of coupon on this page.

RADIO SHACK'S BIGGEST, NEWEST Electronic Catalog **FREE** 336 pages—Over 100,000 items

IN this new book you'll find the widest line of electronic parts and equipment in the world—Stereo, Hi-Fi, Ham Radio, Test Equipment, Pre-Recorded Tapes, Tape Recorders, Records, Component Parts and Accessories . . . plus 30 pages of New Kits! Every item is easy to own with new No Money Down credit terms. Every item is guaranteed to satisfy or your money back.

When you send for this catalog, you also get a Free subscription to all other Radio Shack books for one full year. So mail the card or coupon now. You'll get your first free catalog in a few days.


MAIL CARD OR COUPON TODAY

RADIO SHACK Corp. Dept. 61L8A
730 Commonwealth Ave., Boston 17, Massachusetts
Please send me Radio Shack's new 1962 Electronics Catalog and every new issue for the next 12 months—all FREE and POSTPAID.

Name _____

Address _____

City & Zone _____ State _____

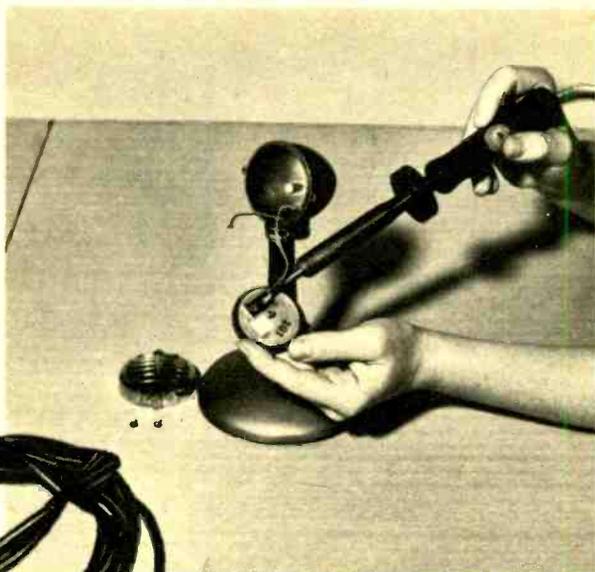

Unsolder the defective cartridge. Be sure to indicate which is ground lead wire.


REPAIR THAT MICROPHONE!

By David Herman


SINCE a substantial part of a microphone's cost is in the case itself, you can save considerable money by rebuilding mikes whose cartridge is defective instead of re-buying the entire unit.

The inexpensive (\$6.47) and rugged Shure R5 controlled magnetic cartridge is particularly suited for replacement service as it has a thick rubber rim which can be trimmed to fit a variety of microphone cases. Practically immune to heat and humidity, the R5 has a smooth frequency response, suitable both for recording and public address use. And by removing the cartridge's plastic damping cover you can cut its bass response to produce a communications microphone with a sharp, crisp quality. The R5 has a *minimum* mounting diameter of 1 $\frac{7}{8}$ " so make sure (before purchase) that it will fit the mike case.

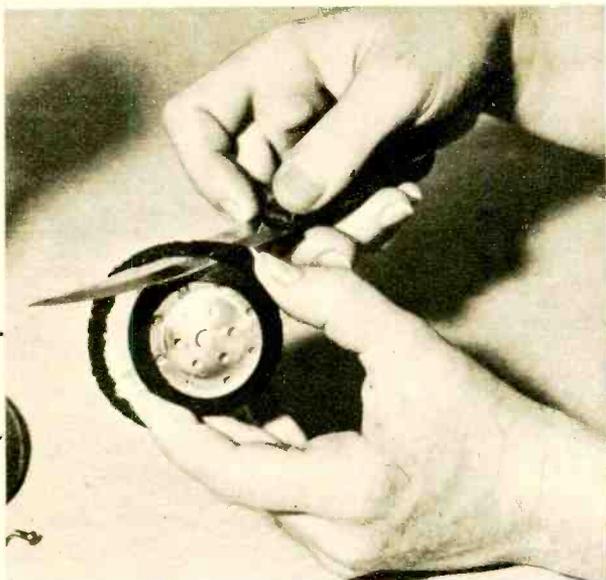The Shure R5 is stocked by most large parts suppliers or it can be ordered through your local Shure microphone dealer. —



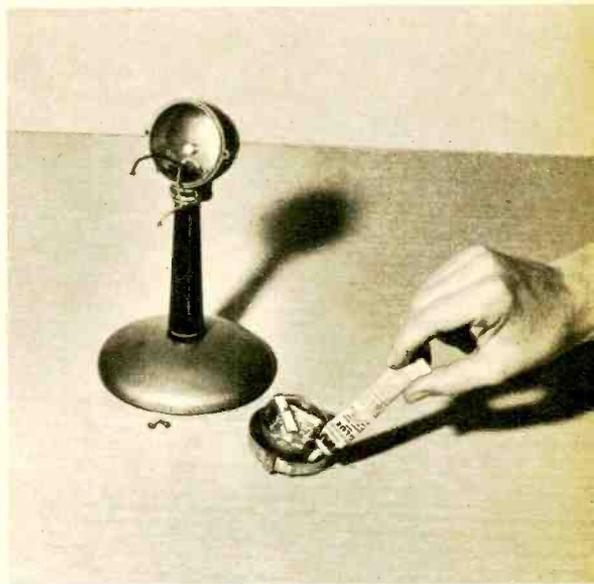
Part of rubber rim is trimmed away with sharp knife. Make certain R5 has snug fit in case.



Position cartridge in case and glue shock mounts in place. New shocks may be made of excess rubber.

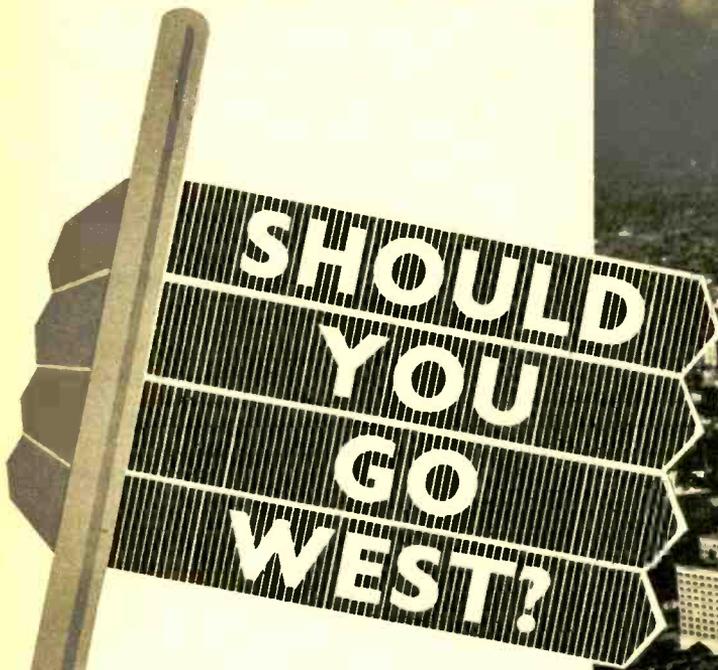Solder both leads to new cartridge making sure that ground lead is connected to correct lug. Although cartridge is not heat-sensitive, it's best to use long-nose pliers to carry off the heat.





**Southern California
could be a true land
of opportunity for you.**

By James Joseph

IF YOU work in electronics or are considering employment in the field, you've probably wondered about the opportunities waiting for you in one of the country's great military-civilian electronic complexes—such as Southern California.

We've all read about the wonderful things that can happen if you throw away your muffler, stock up on sun-tan lotion and head for the "land of electronic opportunity." Southern California boasts more than 500 electronic plants employing 130,000 technicians, engineers and high-level thinkers. Each year the electronic companies do about a billion and a half dollars worth of busi-

ness, some 15% of the nation's electronic total.

But should *you* go west?

EI has conducted a survey in depth in the Southern California electronics industry—from Santa Barbara to the Mexican border—and we've arrived at some important facts for anyone who considers following the trail of the covered wagon. Items:

- Electronics is the brightest spot in the darkening Southern California employment picture.
- Military electronics is growing at a rapid rate in Southern California.
- Service shops and manufacturers of consumer products are feeling the

● LANCASTER

El map points out centers of the electronics industry in Southern California. Below map is photo of Los Angeles.

● PALMDALE



pinch of too much competition.

Although the Department of Labor has classed much of Southern California a labor surplus area (more than 6% unemployment), *electronic* employment jumped 10% in 1960 and an increase of 5% is foreseen for 1961.

Declares one industry expert: "Any technician or engineer worth his salt can find his niche in the Southern California marketplace."

But the area is a paradox. Its electronic industry is expanding and diversified—and also narrowly specialized. Defense work dominates.

Still, in the non-military field, thousands of electronic technicians man TV-


movie consoles in the movie capital, cater to an exploding population that demands intercoms and hi-fi and automatic garage-door openers, and set up all kinds of small shops on a shoestring. Last year, according to the Los Angeles Chamber of Commerce, 650 new businesses (a good many of them electronic) opened their doors every day in their domain.

Defense electronics must be considered the backbone of the business in the land of waving palms and orange groves. Fully 65% of Southern California electronics is military-oriented. Currently more than 16% of the U. S. electronic budget goes to California firms. Only




SANTA BARBARA

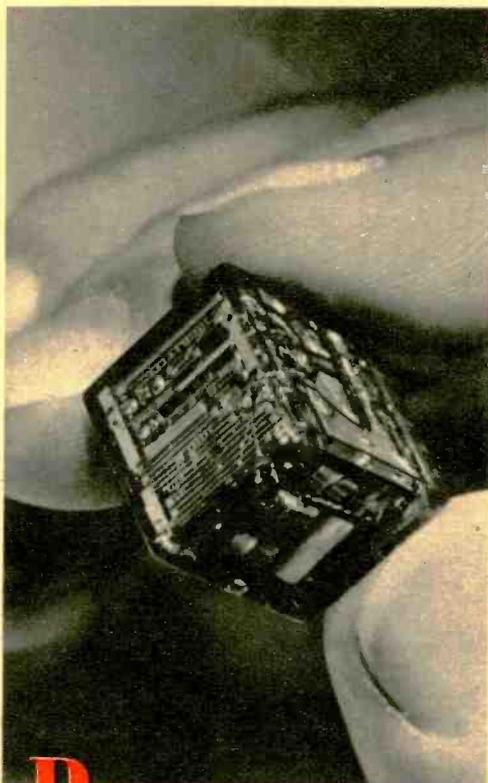Electronic production worker at Hoffman plant assembles part of an airborne navigation system.



POMONA

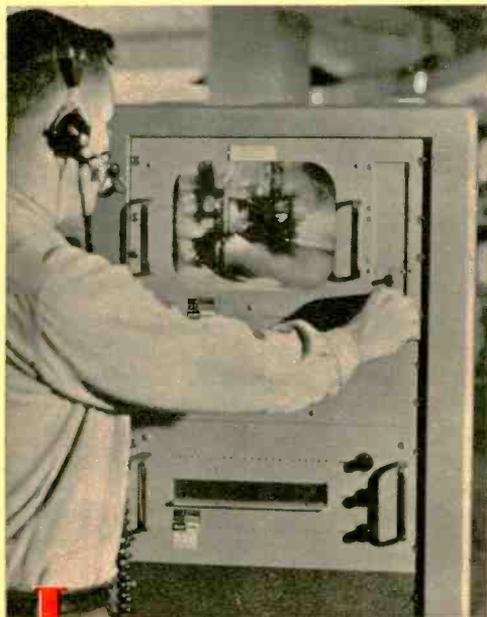Research in Southern California is indicated by solid-state amplifier from the Convair factory.



LOS ANGELES

Technician watches test firing of rocket engine on TV at a Rocketdyne facility near Los Angeles.



CANOGA PARK

Thompson Ramo Wooldridge plant, in San Fernando Valley, typifies beauty of industrial sites.

**". . . any technician or engineer worth his salt
can find his niche in Southern California . . ."**

the New York-Newark complex gets a bigger hunk.

On the other side of the coin, independent TV-radio servicemen find competition fierce and the buck harder and harder to come by. "1960 was pretty sour," says Burbank's Ralph Johonnot, a director of the California State Electronic Association, made up largely of servicemen.

Johonnot figures Southern California's 4,600 independent shops netted an average of only \$5,000-\$7,500 last year. His diagnosis: too many shops in the big metropolitan areas. "Get out of the big towns and you'll do fine," he says. "But in town there's a shop or a guy working from his garage on just about every block."

By contrast, wages are high and opportunity ripe for the job-seeking technician with know-how and experience. Top-flight technicians earn \$250 and more a week, although starting pay for an experienced hand is more apt to be in the \$100-\$150 weekly bracket.

Many research firms (California is a hot-spot for research and development) insist on from five to seven years experience in their specialty. Examples: computer circuitry, semi-conductors, solenoid check-out, telemetering systems installation.

Another facet of the picture shows that hundreds of firms stake promising technicians to a degree via night school at such first-class engineering schools as Cal-Tech, UCLA and the University of Southern California. If you graduate with a C average your company pays the cost.

Take technician John C., who hired on as a components tester with a major electronics firm at \$125 a week. John enrolled at a local university, spent nearly eight years getting a BS in electrical engineering at his employer's expense and was boosted promptly to \$800 a month (engineer's salary) upon graduation. He now earns more than \$12,000 annually. John's is an unusual

case, however. The *average* engineer with ten years of experience earns \$11,716.

Southern California newspapers are fat with ads crying for the electronically skilled technician. Here's a sampling:

"Senior Electronic Technicians . . . R&D test and analysis of high-power amplifier and instrumentation in audio and sub-audio range. Degree not necessary. Top rates, full employee benefits."—Ling Electronics Division, Anaheim, Calif.

"Testing, troubleshooting and repairing such electronic products as small scale digital computers, high speed data printers. Desired: high school grads with additional electronic training."—Clary Corp., San Gabriel, Calif.

Such technician jobs have a wide salary range, partly because of great differences in duties performed. Here are some average hourly wages:

Electronic systems tester—\$2.75-\$3.12.

Electro-mechanical engineering associate—\$3.10-\$3.23.

Electronic production technician—\$2.47-\$2.72.

Precision equipment assembler—\$2.50.

Let's look at the case of a technician in non-military electronics. His name is Harold W., he's 31, married and has four kids. Three years ago Harold and his family piled in their car, bid good-bye to Minneapolis and headed for Los Angeles. After a month of job-hunting he landed a berth as service TV technician for Packard-Bell Electronics in Los Angeles.

With only a trade-school background and almost no previous electronics experience, Harold now finds himself one of two bench technicians in the P-B shop, backstopping the company's field TV repairmen. He is happy and solvent.

Fresh-from-college electronic or electrical engineering grads (with degree) easily latch onto \$500 to \$550 a month to

[Continued on page 102]



Stereo-

STRAIGHT TO YOUR EARS

IF you take a glance through the family snapshot album, you'll probably come across a picture of someone—maybe *you*—sporting a set of old-fashioned earphones as he digs the latest (1920) Paul Whiteman offering on the family crystal set. Thanks to stereo, though, earphones have been making their way out of family albums and ham shacks into the living room.

There are two good reasons for the resurgence of earphones in the stereo era. First, there's the matter of *privacy*. With a headset, you can crank the gain as high as your cranium can take it, without disturbing wives, children, or neighbors. Secondly, there's the undeniable fact that stereo via earphones *sounds* great—sometimes better than it does by way of speakers in a living room.

For the audio purist, stereo via earphones isn't the *real thing*. He contends that phones are meant strictly for listening to *binaural* recordings—made with a pair of mikes spaced as far apart as the average pair of human ears. And he feels that today's stereo recordings, with microphones as much as twenty feet apart, don't yield the proper perspective via earphones. After all, he asserts, *whose ears are twenty feet apart?*

Although this kind of logic is tough to dispute, the fact remains that earphone-stereo is phenomenal—perspective error or no. With stereo phones clamped on your head, you're no longer in your living room; you're right in the studio or hall where a recording was made. The impact is incredible; every subtlety that usually gets lost between the speakers and your ears is *there* to hear!

Most of today's crop of stereo headphones (such as the Koss, Lafayette, and Olson, etc.) actually contain a pair of small loudspeakers, intended for connection to the speaker output terminals of stereo power amplifiers—usually by way of a junction-box that contains resistors to prevent headset overload.

For low-cost, quality stereo, you might refer to an article by Harry Kolbe in the September, 1960 EI. There you'll find an under \$5 build-it-yourself gadget that will match a pair of the new 8-ohm phones to the outputs of stereo *preamps* tuners, or recorders. If you're on a budget, this procedure can temporarily save you the cost of a stereo power amplifier and a second speaker system. And the listening quality of this arrangement is so good that you may put

off buying that stereo power amp for quite a while.

Army surplus stores frequently have a stock of old "bomber-pilot" phones. Some of the latter, with their big, padded ear-



pieces, will give you wide-range stereo with a minimum outlay of cash. But they're not all of the same quality, and there's usually no way to find out *before* you buy them. One remedy for the strident sound of some of these headsets is to unscrew the cap—take out their cardboard or plastic inserts—and substitute pieces of speaker grille-cloth.

Another short-cut is supplied by the older high-impedance headsets. These you can connect to the preamp without a matching box. Companies like S. K. Brown, Permoflux, and AKG still produce them.

If you'd like to follow up the question of stereo *vs* binaural perspective, there's an illuminating article in the Apr. '61 *Journal of the Audio Engineering Society*—"Stereo Earphones and Binaural Loudspeakers." The author discusses the theory of perspective, provides schematics of networks that will convert a stereo recording for binaural listening.

SOUPING UP A LEMON

HI-FI



CLINIC

I have bought a Japanese tape recorder selling for \$29.95 and I think it's a lemon. I want to incorporate a miniature level meter, an AC erase circuit, and tone controls in it. Also, how can I increase its output?

*Charles Hile
Tiffin, Ohio*

The Hi-Fi Clinic would like to ask you a question; why did you buy a \$29.95 tape recorder in the first place? These little jobs are *not* lemons—they're fine, but only for the purpose their manufacturer intended them; that is, voice recording.


Even if the various modifications you inquire about could be made on your machine, this would do nothing about its inherent flutter, wow, noise, distortion and limited frequency response. To attempt redesign of your recorder to bring it up to the standards of a \$200 machine would probably cost you far more than \$200 worth of time and effort.

Intermittent Hum

I am bothered by a very loud hum that occurs whenever I move the shielded cable that connects my tuner and amplifier. I can eliminate the hum by placing the cable in just the right position, but if I move it a fraction of an inch, the hum starts up again. Any ideas?

*Alan Vogel
Huntington, N. Y.*

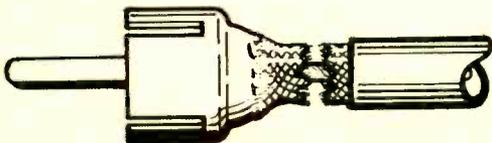There's a break in the shielding of the cable, probably right at the point where the shield braid is soldered to the phono plug. You can tell at which end the break is by close inspection, but the odds are if one end has let go, the other one will follow shortly thereafter.



Rather than attempt to re-solder the plug, I would suggest that you cut the old plugs off, get a new pair of phono plugs and make up a new cable. You can prevent repetition of the problem by wrapping a couple of inches of plastic tape around the shielded leads at the point where they enter the plug.

New Stereo Preamp?

I now have a 20-watt integrated monophonic amplifier and I'd like to go to stereo. Should I purchase a stereo preamp or can I get away with buying only another amplifier?

*Martin Aronstein
Louisville, Kentucky*

I would suggest purchasing a stereo preamp for a number of reasons: first, you will have the additional facilities useful with stereo program sources, such as *stereo reverse*, *balance* and the like. Secondly, the output of some stereo cartridges is low in relation to monophonic cartridges and your mono preamp stage probably lacks sensitivity.

Assuming that you purchase the stereo preamp, you can adapt your integrated amplifier to function as a basic amplifier in one of two ways. One method is to set your tone controls at their flat position; the loudness control, if any, off or at minimum; and the volume control at maximum. Then take one of the leads from your stereo preamp and plug it into the *auxiliary* input. You will then be able to adjust the tone, volume, etc., from your stereo preamp.

If your integrated amp has a *tape output* jack you may be able to use this as an input to the power amplifier section of your unit. The advantage in using the *tape output* jack is that the preamp stage and the tone and volume controls are bypassed. Run a shielded cable from one output channel of the preamp to the *tape output* jack of your amplifier, then check to see if the tone and volume controls are operating.

NEW RULES FOR

CB

What do those changes in FCC regulations really mean to the guy with the mike? Here's the answer.

By Len Buckwalter, 1W5733

THE birth of the Class D Citizens Band in September 1958 stirred up a large amount of enthusiasm . . . and almost as much confusion. Early regulations spelled out only basic features of the band, setting off endless speculation on how far one could go in terms of range and kinds of communication. After a wait-and-see period that lasted about 18 months, the FCC has made clear its answers to those questions in a spate of amendments to Part 19 of the regulations which are found in a group of the agency's Transmittal Sheets. If you are keeping your Part 19 regulations up to date—and you should be if you hold a CB license—it is a good idea to place all the pages in a looseleaf notebook and then add the Transmittal Sheets as they come out, as pictured below.

Most of the new amendments are concerned with improper use of the Citizens Band. Some are strictly technical. All reflect the





New rule limits transmissions to 5 consecutive minutes, to be followed by 2 minutes of silence.

enormous growth of CB and the need to keep the service of value to the greatest number of users.

To bring the limits of operating range into sharper focus, the rules have undergone some substantial rewording. The words "groundwave" and "skywave" are new additions to Part 19. They state clearly that CB is restricted to transmission via groundwave, that part of the signal which travels horizontally between two units. The range on groundwave is upwards of 20 miles, depending on the height and efficiency of your antenna.

Skywaves, which are signals reflected from the ionosphere, can cover hundreds of miles when conditions are right, but their use is illegal for CBers.

It's easy to recognize skywaves. First sign is when you hear stations with call letters outside your area (revealed by the first number in the call letters). These signals can sound like locals but are audible only a few hours a day. They also are subject to fading, growing alternately weak and strong over several seconds. The skywave path is usually a two-way street and contact is possible, but by law can be made only in an emergency or distress situation.


A not-so-obvious change has crept into the section on Permissible Communications. The original law made little distinction between what or what kind

of stations were involved in communications. Now it's more precise, saying that CB is "primarily to communicate with other units of the same station..." This is obviously a crackdown on neighborly, indiscriminate conversation. However, if you have a *definite message* to send to a station bearing different call letters it's still perfectly acceptable.

The commission has taken a firm stand on CQ, the general call used in ham radio. Their opinion is now written into the rules. Although it specifically forbids calling an unknown or random station, it does leave the door open for an important kind of call in CB radio—one that is not addressed to a known station. It might be termed a *limited-general* call. Let's say that you are on vacation in an unfamiliar part of the country, looking for a motel. There is no reason why you can't send out a call to unknown motels in the area for information. This can be extended to include contact with a local CB station for route instructions or other information. In each case you don't know the call of the stations, but there is a valid message to send and CB radio is the ideal medium for it.

New paragraphs have shown up in the rules to limit the time you have for transmitting a message. The original wording left it up to the operator to decide the "minimum practicable transmission time." To prevent excesses, there are now limits which affect two types of transmissions: that of a single station, or the back-and-forth exchange between two units. In neither case may the talking time be more than five consecutive min- [Continued on page 100]

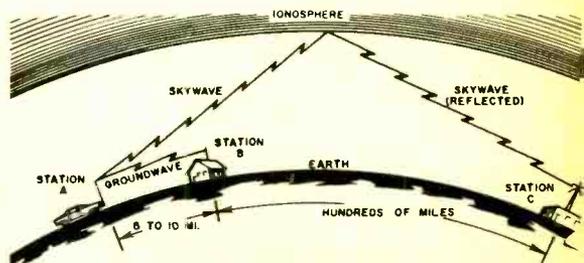The terms "skywave" and "groundwave" have now entered CB rules. Skywave use is illegal.





The Ham Shack

By Robert Hertzberg, W2DJJ



Q CUTIES . . . In the International Q code, QSO means, "I can communicate with . . . direct (or by relay through . . .)." Pronounced "kewso,"



this abbreviation normally pertains to any station-to-station contact on the air. Not so long ago I was puzzled to hear the expression, "eyeball kewso," and it took me five minutes of eavesdropping on a QSO to realize that it meant a meeting in person. But now we can report still further progress, Q-wise—a new Q card. It's a QSL card that confirms an eyeball QSO (see cut).

Patch Traffic . . . It is common to hear a sort of a footnote attached to directional CQ calls that runs, "with phone patch traffic for . . ."

Since telephone companies everywhere are fussy about their instruments and discourage subscribers from attaching things to them, some hams are reluctant to use patches. Actually, there is no need to worry on this score. The patch units now on the market can be connected in about three minutes and do not disturb the normal operation of the phone.


Unofficially, the telephone companies welcome patches for a darned obvious reason: they produce a great deal of extra business in the form of toll calls.

Just as obviously, the phone people must remain officially opposed to patches. To give an okay would be a sure invitation to the destruction of a lot of equipment.

Flying Hoop . . . An odd-looking mobile antenna that resembles a basketball goal (see photo) is seen on the streets and highways with increasing frequency. The rig is for 2- and 6-meter



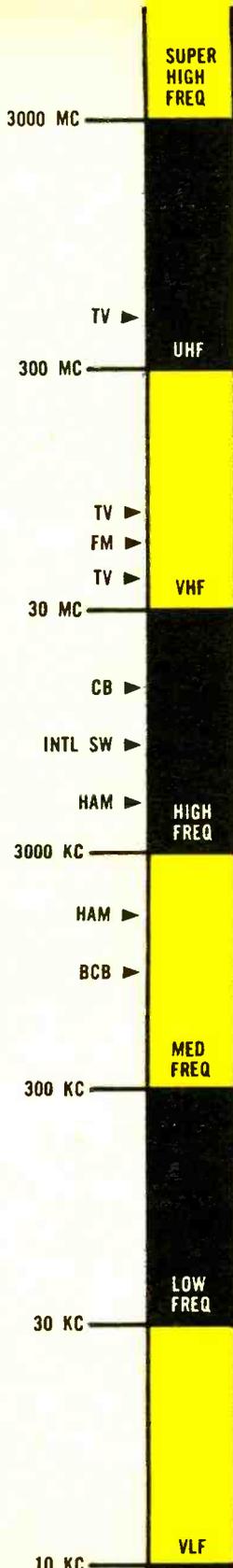mobile operation. It's called the halo and is more effective than a straight whip. Our photo shows a halo sported by K8EGR. [Continued on page 103]



t
h
e
i
n
c
r
e
d
i
b
l
e

Eerie whistles and hisses are companions to CW stations working on the VLF band.

By Tom Kneitel, 2W1965

EERIE . . . weird . . . a jungle . . . wild . . . those are some of the words used to describe the goings-on in radio's fantastic basement—the segment of the electromagnetic spectrum known as Very Low Frequency (VLF). The basement begins at 30 kc and goes down.

The inhabitants of these frequencies are indeed strange. Among them, for instance, is a 2,000,000 watt station of the U.S. Navy which is 40 times more powerful than the biggest commercial station in the country. But even the Navy's behemoth is flea-powered compared to the strangest broadcaster of them all, Mother Nature, who runs about one *thousand million* watts down in the VLF reaches. The old girl puts out some interesting programs, too. You don't get Jack Benny or Elvis Presley, but you do hear some weird whistlers, the dawn chorus, the hiss, echoes, risers, clicks and (in the words of the Naval Research Laboratory) "other unusual emissions." You also can hear "joint-venture" transmissions, those initiated by man and taken over by nature.

To get down to specifics, several stations operate regularly from 30 kc down to about 14.5 kc, and experimental transmissions have gone below that. Obviously, some type of narrow-band, continuous-wave (CW) transmission is required. The 3,000-cycle bandwidth for voice transmissions would leave room for only about five stations between 15 and 30 kc.

However, it is the strange noises which really set the VLF band apart and make it interesting to monitor. These random signals have come under close observation recently and it has been found that they are caused by natural phenomena, some known and some only guessed at.

The most frequently heard signals are eerie descending shrieks called whistlers. They're caused


BASEMENT of radio




A forest of towers occupying a whole peninsula marks Navy's new two-mega-watt station, NAA, at Cutler, Me. Station's huge VLF antenna is supported on 21 towers up to 900 feet tall. Seventeen appear in this picture. Ships as far away as the Mediterranean receive NAA.



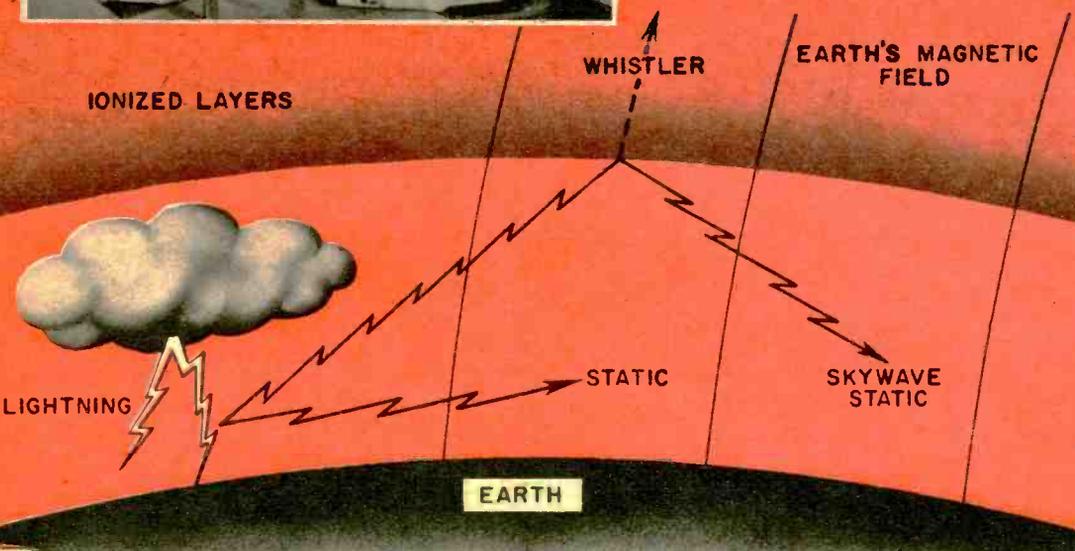The route of the whistlers is shown by looping stick held at left by Harold Dinger of Naval Research Laboratory. Whistlers are generated by lightning (see diagram below) and bound from one hemisphere to the other. Behind Dinger is Navy's whistler monitor equipment.



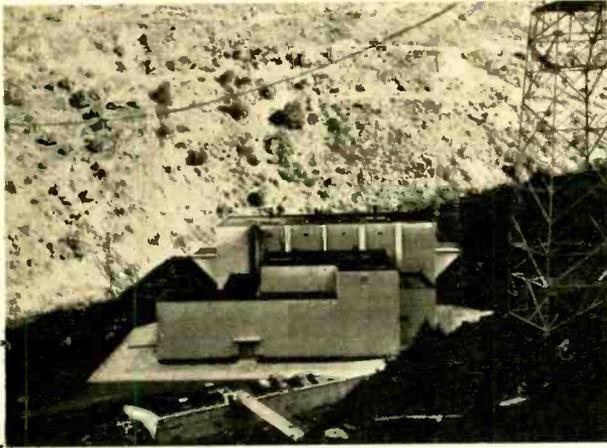

Navy's NLK (Big Jim) is famous VLF station at Jim Creek, Wash.; this is transmitter building.



Control room with quartz-crystal clock (left) at NBA, Navy time station in the Canal Zone.

by the sudden release of about one thousand million watts of peak power into the radio spectrum by a lightning discharge.

To show how whistlers are born we'll start with a burst of lightning. As it flashes it radiates energy in all directions, its groundwave signal causing static on ordinary radios. Some of the lightning's energy bounces off the ionosphere and comes to earth as skywave static. But, most importantly for VLF, some energy penetrates the ionosphere and, being electromagnetic in character, starts traveling upward parallel to the earth's magnetic field (remember the dotted field lines in your physics textbook?). Following these lines, the lightning's signal goes tens of thousands of miles into space and comes to earth at the corresponding latitude in the opposite hemisphere, then bounces back to the point of origin. The trip is made at a speed of 186,000 miles a second.

But what goes out as static comes back as something else—a whistling tone of descending pitch. This is because the original static covered all radio frequencies but during the long trip the high frequencies travel faster than the low ones and return first, followed immediately by the others, causing a descending pitch. Sometimes whistlers bounce back and forth several times along the arc, creating echoes.

As many as 150 whistlers a month

have been recorded, with peak activity in March and October between 11 P.M. and 7 A.M. EST. Whistlers are studied at several sites, among them Stanford University, the National Bureau of Standards Laboratory at Boulder, Colo., and the Naval Research Laboratory in Washington.

Although a good audio amplifier hooked to a large loop antenna can enable even a home experimenter to hear whistlers, the Naval Research Lab employs a long omnidirectional antenna fed into a rig with an amplification factor of 1,000,000. The equipment tunes down to .8 kc (800 cycles), lowest radio frequency yet achieved.

Much remains to be learned about whistlers. Not long ago Professor M. G. Morgan of Dartmouth set sail for Deception Island in Antarctica in a project in which scientists hope to transmit artificial whistlers. [Continued on page 114]

DX GUIDE TO VLF

Call	Kc	Location
NAA	14.8	Cutler, Me.
NLK	15.3	Jim Creek, Wash.
NSS	15.5	Washington, D.C.
GBR	16	Rugby, England
NPM	16.6	Honolulu
NBA	18	Summit, C.Z.
NPG	18	San Francisco
GBZ	19.6	Criggon, Wales



For the man who has everything . . .

and needs help to get rid of it . . .

The Panic Button

By Fred Maynard, Motorola, Inc.

SAY YOU'RE the hard-pressed Madison Avenue type. You worry about everything . . . about the winter house, the summer house, the three cars, the two boats, the wife, the kids, the girl friends. Sweat pops out on your brow, your grey flannels get greyer. What do you do next?

Relax . . . and just press your handy Panic Button. Help is on the way. In fact, everybody in the office will be on the way to your sweatbox to find out what the heck the racket is. So you pass on all your problems to them and stop worrying.

The original version of the Panic Button was an electronic siren hardly as big as a giant-size Miltown box. With an ingenious transistor circuit, a homemade coil and a handful of standard parts, it produces the piercing wail of a true siren. As a novelty, it attracts attention


everywhere—if that's your life's aim.

However, the Panic Button also has a serious side. The fact that its circuit does produce a true siren wail makes it applicable for police, Civil Defense and other emergency duties. On a police car it can be combined with a small PA system to form a dual-purpose unit. Its output is sufficient to drive an efficient PA horn large enough to alert a whole area. And the Panic Button's cost is a fraction of the selling price of an air siren.

Construction

You may build the button in any box large enough to contain the parts. You can see some of the versions in the lead photos. The author's model is built in a $3\frac{1}{4}'' \times 2\frac{1}{8}'' \times 1\frac{5}{8}''$ Minibox.

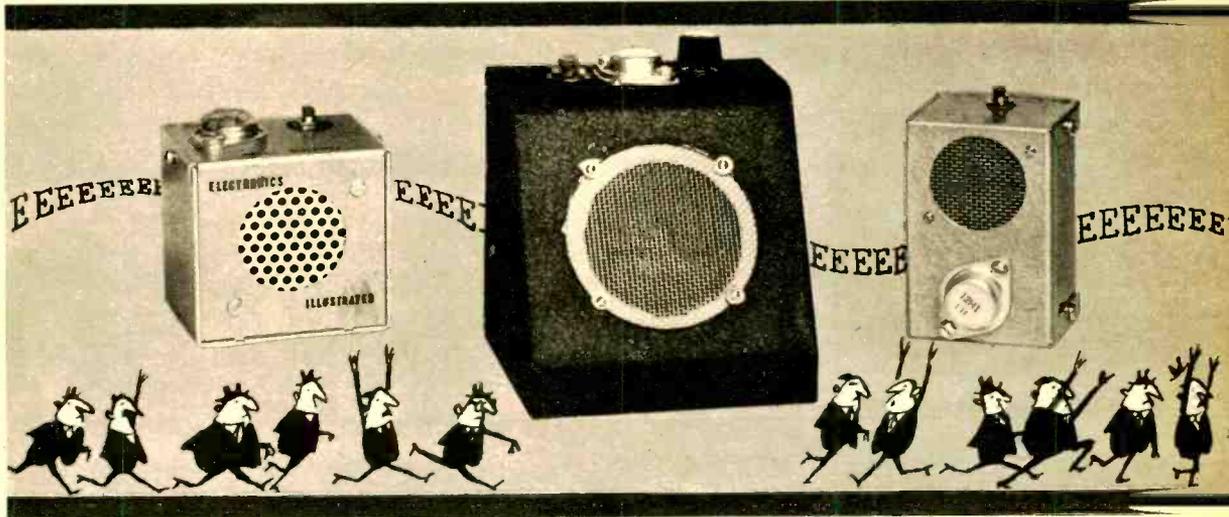Inductor L1 can be wound in a few minutes. The core is a $\frac{1}{4}''$ diameter 2''



long iron stove bolt with two nuts. Screw one nut about 1½" from the head end. Next, cover the bolt with a layer or two of plastic electrical tape to protect the wire from the sharp threads. The coil should be scramble-wound between the nut and the head of the bolt keeping an even distribution of wire over the winding area. The turns should be kept fairly tight since loose turns may result in "ragged" sound.

Start at the nut end of the bolt and wind 150 turns of No. 28 or 30 cotton or nyclad insulated wire. Bring out a 2" loop in the wire (for the center tap) and then continue to wind 150 more turns in the same direction. Wrap the coil with a layer of tape and mount it on a bracket or directly to the cabinet with the spare nut. The 2" loop tap goes to the negative battery terminal.

Circuit Operation


The oscillator comprises C1, Q1, L1, R1, and R2 in a conventional Hartley oscillator with inductive collector to base feedback. The Hartley oscillator alone, however, would produce a sine wave and would sound more like a whistle than a siren. The siren effect is achieved by choosing the proper values of C1, R1, and R2 which establish a quench frequency determined by their time constant. The quenching frequency is highly sensitive to the voltage at the junction of R1 and C2, rising to a high

frequency as the voltage increases.

The charging voltage at the junction of R1 and C2 is dependent on the time constant of R3/C2. In other words, R3 controls the rate at which the frequency of the tone rises. When SW1 is closed, the voltage across C2 starts to rise and continues to do so, as long as SW1 remains closed, causing the sound to rise in frequency. Eventually equilibrium is reached and the pitch remains constant. When SW1 is released, C2 discharges through R1 and R2, the voltage at the junction of R1 and C2 falls, and

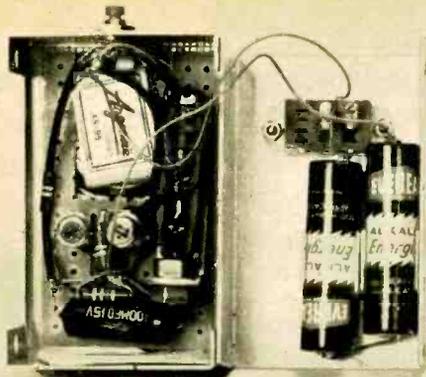For ear-splitting volume an inexpensive PA trumpet such as the Olson Model S-350 may be used.







Inside view of one of the more compact versions of the Panic Button. Components are mounted on a perforated board with a cutout for the loudspeaker. Arrangement not critical.

the frequency of the sound lowers gradually. The rate of rise and decay can be varied by changing the value of R3 or C2. The pitch of the tone can be changed by using a different value for C1. Both the speed at which the sound rises in frequency and the upper limit of its frequency are dependent on the battery voltage. You can experiment with different part values to achieve the most desirable effect with the battery selected.

Almost any audio transistor will produce oscillation in this quenching circuit. However, the dynamic range of the siren tone will be greater if a high-gain transistor such as a 2N1193 is used. An even greater dynamic range can be produced by using two low-gain transistors, such as 2N1191s, in place of Q1, in the Darlington amplifier configuration shown in the schematic. However, this may require further changes in the values of R1, R2, and C1.

The oscillator output is emitter-follower coupled to the base of Q2. For best results, the impedance of the speaker voice coil should be in the range of 45 to 100 ohms. Ten-ohm speakers work well but deliver less audio power, somewhat thinner quality sound, and cause a much higher current drain on battery B1. B1 can be from 3-9 volts; greater volume and a higher pitch is attained with a higher voltage.

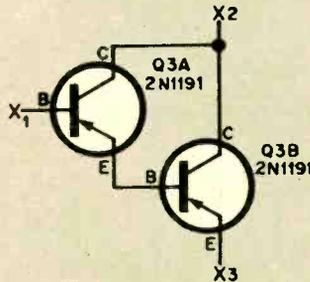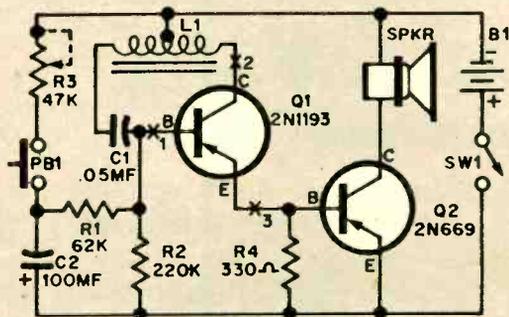If a three-transistor circuit is built and a 10-ohm voice coil speaker is used, it will be necessary to power the Button with at least size D flashlight cells. If only penlight cells can fit in the housing, it is necessary to use Alkaline Energizer cells, such as Eveready E91, to supply



PARTS LIST

- Resistors:** 1/2 watt, 10%
 R1—62,000 ohms
 R2—220,000 ohms
 R3—47,000 ohms (see text)
 R4—330 ohms
- Capacitors**
 C1—.05 mf, 100 volt or higher paper or ceramic
 C2—100 mf, 15 volt electrolytic
 P B1—SPST push button switch
 SW1—SPST slide switch
- Transistors**
 Q1—2N1193 transistor (Motorola)
 Q2—2N669, 2N554 or 2N176 power transistor (Motorola)
 Q3A, Q3B—2N1191 transistors
- Other components**
 L1—Special coil (see text)
 Spkr—100-ohm miniature speaker (Quam 22A06Z100)
 Available from Allied Radio and other distributors
 B1—3 volt to 8 volt (see text)


For greater dynamic range transistors Q3A,B may be used instead of Q1. The two-transistor d.-c. circuit is inserted at the numbered points.

the necessary current. Since the standby current (SW1 closed, PB1 open) of the 3-transistor, 10-ohm voice coil speaker circuit is over 300 ma, SW2 should be turned off when the siren is not in use.

An ideal housing for a king size Panic Button is a \$5.95 intercom substation sold by McGee Radio Co., 1901-07 McGee St., Kansas City 8, Mo. The catalog number is M-45. The sub-station contains a 4" speaker and an output


transformer with a 45-ohm primary. In addition, it includes a small chassis and a spring-loaded DPST switch that can be used for PB1.

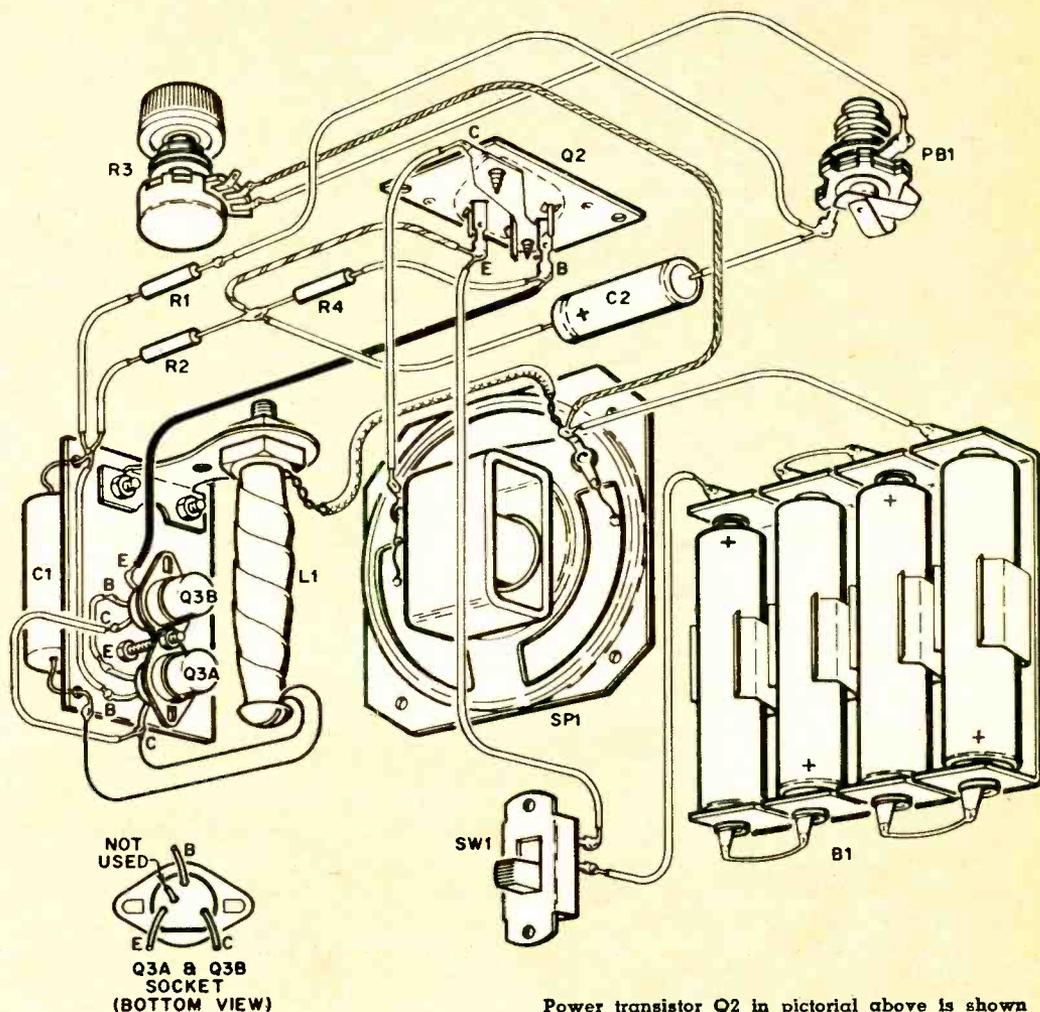When Q2 is connected to the primary of the transformer, its load is 45 ohms instead of 10 ohms; a much better match. Also, the battery drain will be lower. The chassis as supplied will easily accommodate all the Panic Button's components.



Power transistor Q2 in pictorial above is shown mounted in a Motorola power transistor socket. Home wound coil L1 is installed on small bracket.

CB'ers! Build this **TONE CALL/SQUELCH**

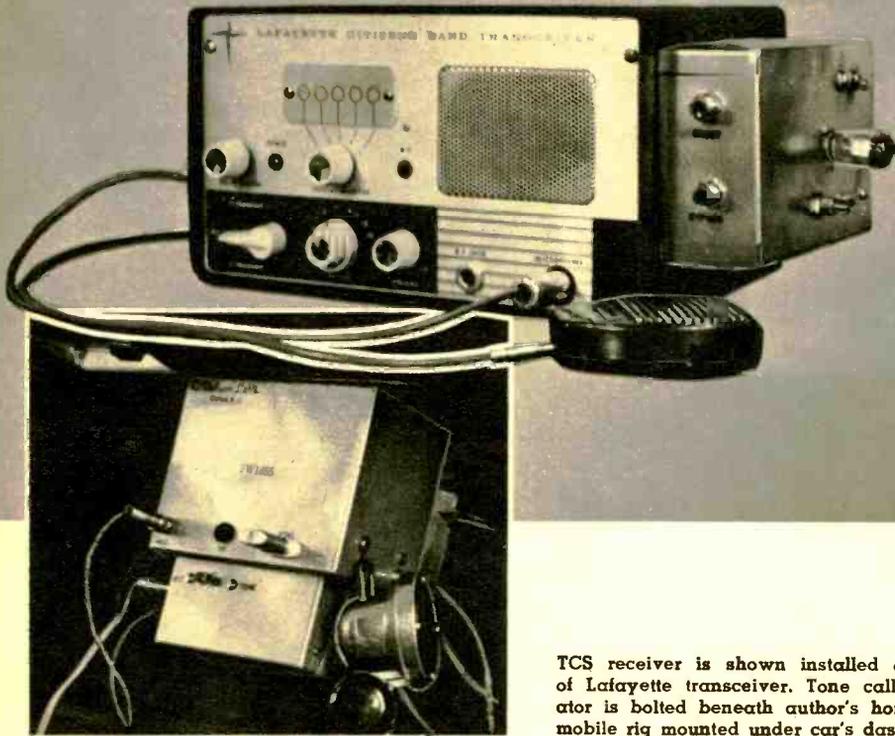

TCS receiver is shown installed on side of Lafayette transceiver. Tone call generator is bolted beneath author's home-built mobile rig mounted under car's dashboard.

By Morris Goodman, 2W1855

MOST CITIZENS Band squelch circuits don't really do what you would like them to. Sure, you can adjust the squelch to kill background hash, but your rig still faithfully delivers every call coming through on your channel. And nothing can be more annoying than to have to listen to the chatter cluttering up the channels when all you want is one short message from your man in the field.

EI's Tone Call Squelch adaptor solves the above problem simply and inexpensively. With our TCS there's absolute silence when your CB unit is switched to standby: another station switches on your set only when its operator wants to call you specifically. And you don't have to mutilate your equipment since the TCS's two units are built on separate chassis and mounted externally.

With the TCS system the base-station receiver is left in the *receive* position with the noise limiter and squelch controls set normally with one exception. One speaker lead is opened and its circuit is completed through a relay in the TCS unit. When the remote station wants to call you he presses (for about five seconds) a button on his TCS call unit. This transmits a tone at a specific

frequency which closes your TCS speaker circuit relay. Once the speaker is activated it is not necessary to transmit the tone again during subsequent transmissions because the circuit is self-locking.

Then you operate your station normally, with the noise limiter and the squelch circuits working as before. After you have cleared your message, you simply press reset button PB1 and the TCS is on standby again. To call from your station, you press bypass button PB2, which closes speaker relay RY2, and then proceed as usual.

The heart of the TCS system is a tone-selective device called a resonant reed relay. This relay uses a thin steel reed as an audio-frequency-sensitive armature which responds to only one frequency: its resonant frequency. A frequency as little as ten cycles away from resonance will not operate the reed.


Receiver operation can be understood by referring to Fig. 1. When the unit is set for *standby*, thyatron tube V1 is held non-conducting by the negative voltage (with respect to the cathode) on grid 1. Relay RY2 in V1's plate circuit, therefore, is open and the speaker disconnected. When the actuating tone is transmitted by a calling station it is picked up by the receiver and is passed on to RY1 by C1 connected to the plate of the CB unit's output tube. The tone voltage causes the reed of RY1 to vi-

brate, which connects a positive voltage to the grid of V1. When the negative cut-off voltage is overcome, RY2 closes and completes the speaker circuit. Since V1 remains conductive even though its grid goes negative again, RY2 remains closed. To reset RY2, V1's plate voltage is momentarily interrupted by depressing PB1.


When the base station wants to initiate a call, PB2 is depressed. This momentarily connects a positive voltage to the thyatron grid and turns on the speaker. Because the reed responds intermittently to speech frequencies, a long time [Continued on page 108]

STONE GENERATOR PARTS LIST

Resistors: 1/2 watt, 10%
 R8—10,000 or 20,000 ohm linear calibration type or miniature potentiometer (tone adjustment)
 R9, R10—15,000 ohms
 R11—820,000 ohms
 R12—10,000 ohms
 R13—500,000 ohm calibration type or miniature potentiometer (output level adjustment)
Capacitors: 50 volts or above
 C3, C4, C5—.01 mf mica* capacitor
 C6—.04 mf paper or disc
 C7—.001 mf paper or disc
 Q1—2N217 transistor or equivalent
 SW1—DPDT slide switch
 PL2—Plug to match mike jack on transceiver
 J1—Jack to match microphone plug
 B1—22.5 volt battery (Burgess U-15 or equiv.) and holder
 3"x5" perforated chassis board
 Aluminum box to house subassembly
 *May be necessary to change these values to reach the resonant frequency of RY1. Increasing the value of the capacitors will lower the frequency of the tone output and vice versa. The values given produce a frequency of about 375 cycles.

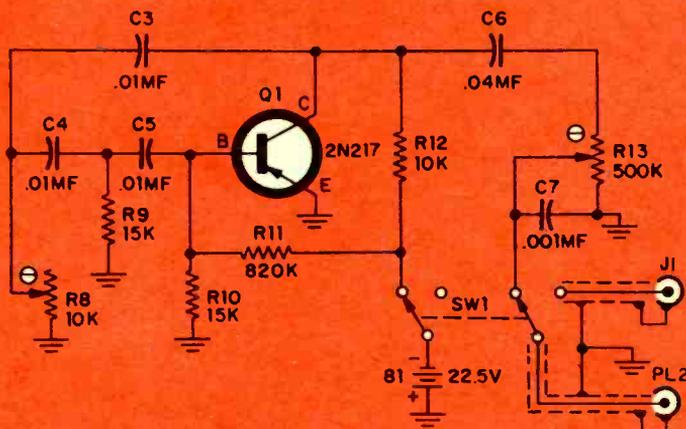


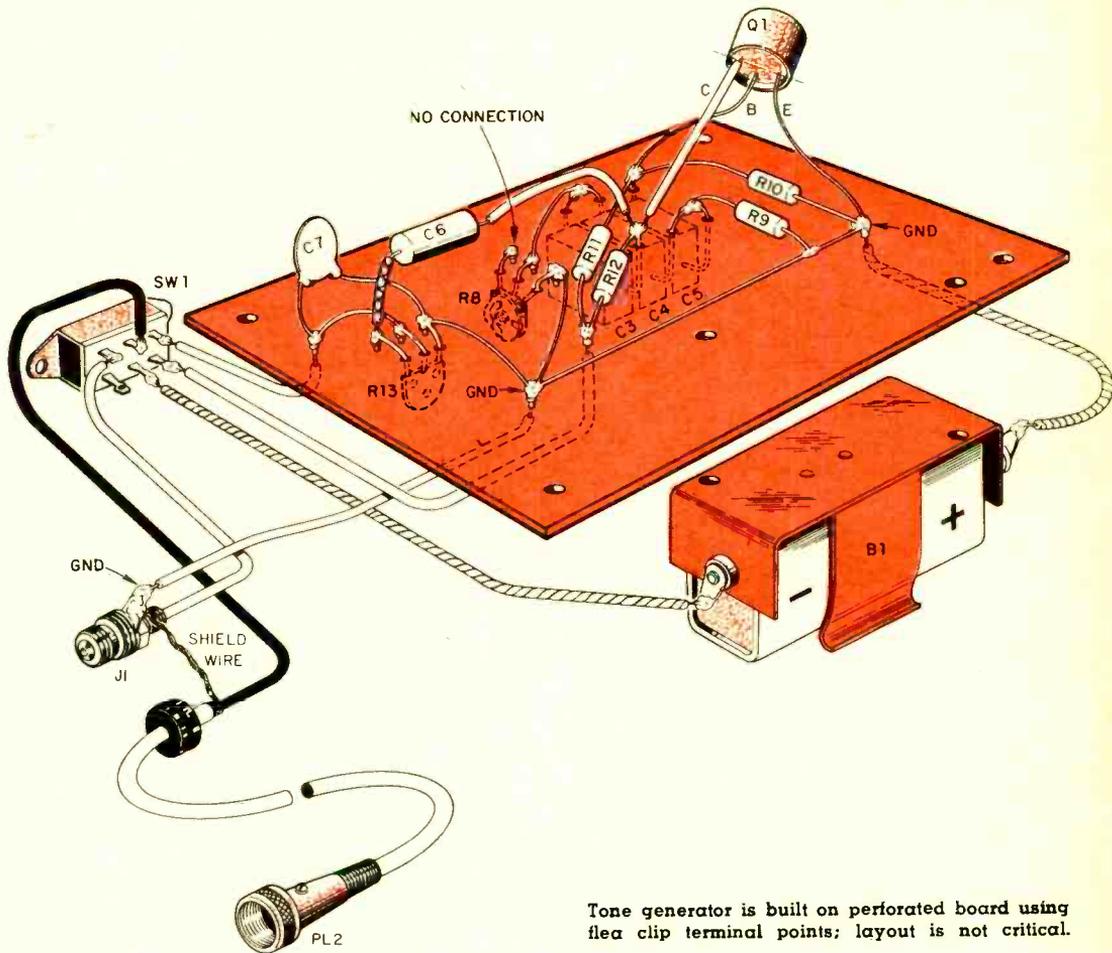
Schematic of transistor tone generator shows simplicity of the design. Phase-shift oscillator provides a stable sine-wave tone signal.



Tone generator is built on perforated board using flea clip terminal points; layout is not critical.


Five-prong socket SO1 is shown installed on the rear apron of a Lafayette Model-15 CB transceiver.

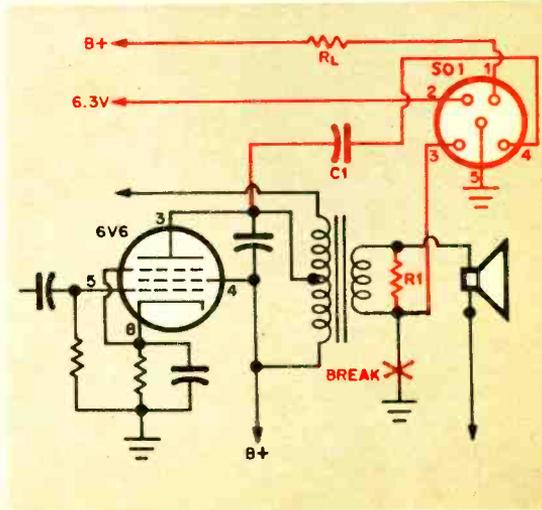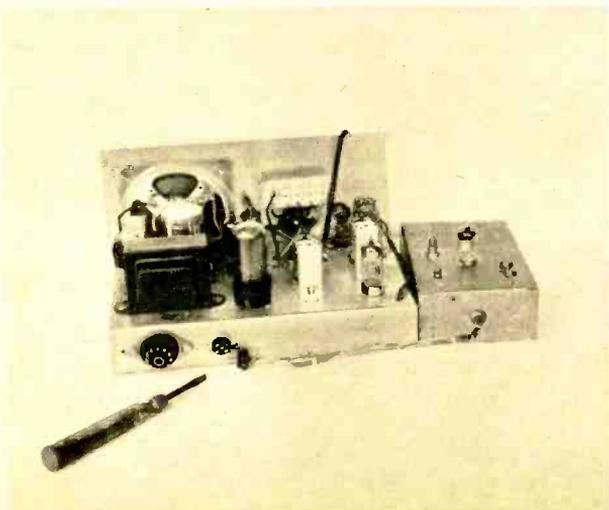Wiring added to CB output stage is in red. Resistor R_L is selected to provide about 135 volts B^+ .




EUROPE'S TOP TV DXer

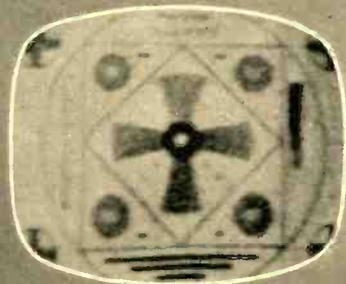TV from Tokyo? From Moscow?
A Belgian hauls in 26
stations with 80-ft. antenna.



BUCHAREST

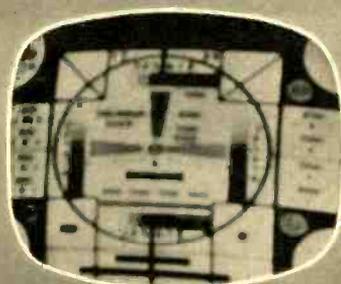

BELGRADE

FEW people have ever heard of Rekkem, a tiny hamlet in the West Flanders section of Belgium hard on the French border, but one Rekkem resident is making a name for himself as a TV DXer.

His name is Jacques Herreman and he is a young dye factory worker, which is why he took up this exciting new hobby. Jacques came down with lead poisoning on his job and had to lay off 18 months. To while away the time, he bought a 21-inch TV set and put a fringe-area antenna on top of the humble Flemish row house where he lives. One night a storm damaged the antenna and, in fixing the trouble, Jacques accidentally souped up the rig.

Where he and his neighbors had once been content with TV from nearby Lille and Brussels, Jacques now began bringing in strange programs with foreign languages he could not understand. It was all Greek to him until one night he picked up the faint image of a young girl on his screen. When she faded, on came a stocky, gesturing man whom Jacques recognized as Nikita Khrushchev. He was receiving Moscow!

Amazed at this accidental success at TV DXing, Jacques Herreman realized his antenna was the secret and put up an 80-foot mast holding eight elements which, by splitting, can become a 13-element layout (shown on preceding page).


Most of the DX images Jacques received with his big antenna were only faint patterns, never good enough to enable him to read station identifications.



Herreman records TV audio on tape and disc and photographs the images on screen in background.

His solution was to purchase both disc and tape recorders to capture the audio and to set up a 2¼ x 2¼ camera to photograph the images on his screen. Armed with photographs and recordings, Jacques began writing to TV stations all over Europe to confirm his reception.

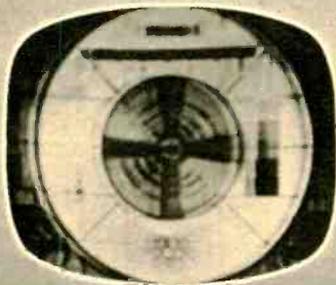
Although troubled by differences in scan systems and weak signals, Jacques in two years of night-and-day DXing was able to receive (and verify) signals from 26 stations in such countries as Portugal, Spain, Hungary, Yugoslavia, Sweden, England, Russia, Rumania and, most amazing of all, Japan (Tokyo). And he has other signals to be traced. A few of his images are shown here. ●



STOCKHOLM



MOSCOW

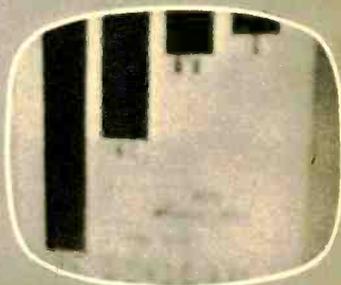

TOKYO




HEATH

VACUUM-TUBE VOLTMETER

AN ELECTRONICS man's best friend is his vacuum-tube voltmeter. It's dependable, versatile, and under some circumstances, far more accurate than the standard volt-ohm-milliammeter. Hams, experimenters, technicians, in fact everybody in the game, sooner or later, end up buying, borrowing or building a vacuum-tube voltmeter.

A VTVM's virtues are derived from the fact that its meter movement is driven by a tube—not by the circuit under test. This means that the VTVM, unlike the VOM, won't act like a shunt resistor and pull current away from the circuit it's measuring. And when you're working in high-frequency, high-impedance circuits only a meter that doesn't load the circuit can guarantee an accurate reading.

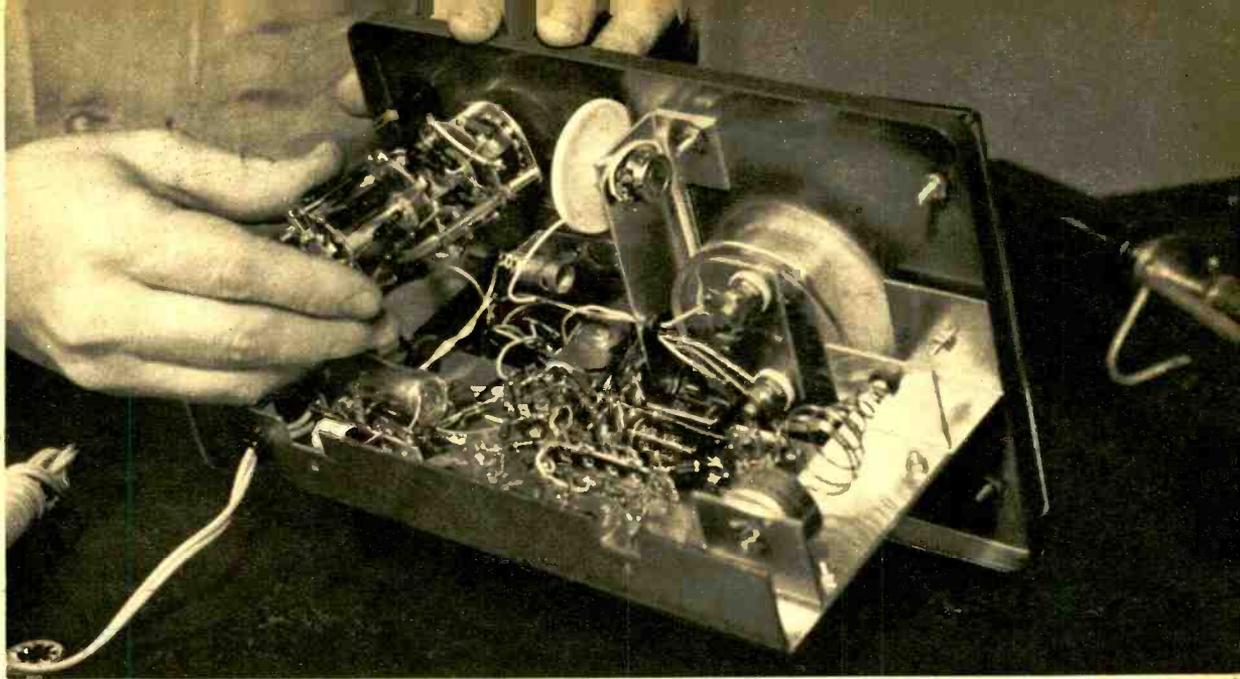A second advantage of the VTVM is that it is burn-out proof. Let's clarify exactly what this means. If you are careless enough



Vertical chassis arrangement makes for open construction and facilitates wiring procedure. Here, range switch is about to be installed in final step.

to apply voltage to the ohmmeter section of your VTVM, there's going to be a small puff of smoke and several of the ohms range precision resistors will bite the dust. How does the burn-out proof claim enter in here? Well, if you were to pull the same stunt with a VOM, you would not only have the resistors to replace, but probably an expensive meter movement as well. In the VTVM, the tube driving the meter movement is biased so that no matter how much voltage is applied to it (via the test probes), the current through the meter can't rise above a certain level. As far as the voltage ranges are concerned, unless the overload is extreme, the voltage divider resistors won't be damaged.

The circuit of the IM-10 is straightforward and conventional. DC voltage to be measured is applied across a series of voltage-dividing resistors (10 megs worth, with another 1 megohm in the probe). A range switch taps off a portion of the voltage and applies it to the grid of one triode of a 12AU7. The two triodes of this tube are arranged in the conventional balanced bridge configuration. The meter—a 200 microamp job—is connected between the cathodes of the two triodes so that a signal applied to the


grid of one upsets the balance and causes current to flow through the meter movement.

The AC rectifier is a 6AL5 in a half-wave doubler configuration. On the high AC ranges, a voltage divider (a tapped sequence of series resistors) holds the voltage within the input ratings of the tube. The DC output of this circuit is proportional to the AC peak-to-peak input voltage, and is fed to the 12AU7 bridge for the actual measurement.

There are no peak-to-peak scales on the meter face (a silly omission in our opinion), but since the circuit *does* respond to P-P voltage you can multiply any AC reading by 2.83 to get its peak-to-peak value.

Several physical innovations in the Heath unit are worth noting. The first thing that hits your eye is the meter movement—it's a big 6" job. And unlike the large movements used by some of Heath's old-time competitors, this meter is well damped. The needle won't oscillate wildly every time you try to take a full-scale reading and it won't beat itself to death if you have it stored in the back of your service vehicle.

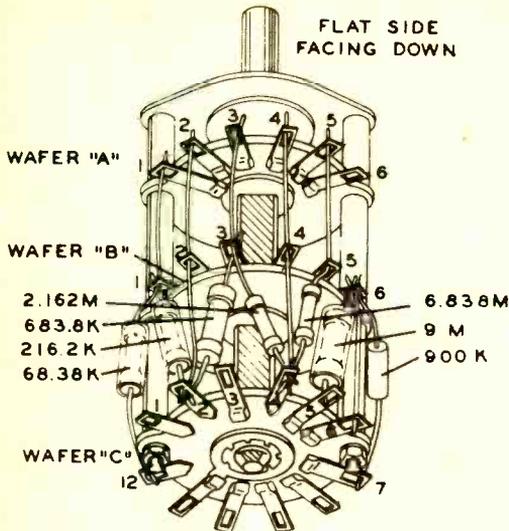The recessed thumb knobs for zero and ohms adjust are an excellent idea,



Heathkit's foldout pictorials of sub-assemblies such as range switch help avoid wiring errors.

not just from the viewpoint of physical appearance but because there's no chance of upsetting your zero adjustment by inadvertently grabbing the wrong knob.

Construction is simple and straightforward, with few pitfalls, none serious. Parts and hardware were all present and easily accounted for. The manual contains drawings of all parts so that even those who don't know a resistor from an orangoutang would have no trouble. All parts and mounting holes matched and the fold-out pictorials and other illustrations are almost exactly where needed in the text. (You can't take either of these two points for granted in the kit world.) Total construction time came to about seven hours.

Subassemblies are used in the IM-10, and you can get at almost everything with ease. No jamming of the soldering iron into remote chassis corners, no scorching parts already mounted. We might warn you that the transformer leads are very brittle—careful. The instructions neglect to warn you to dress transformer leads downward toward the chassis at terminal strip C (p. 13), and this caused a small delay when it was time to install the filter capacitors.

When you get into final assembly and


wiring (p. 16) it might make the next steps easier if you temporarily remove the pilot lamp socket from the front panel and bracket assembly. Don't unsolder anything—just remove the nut and push the lamp socket out of your way.

Another instruction (p. 16) says, "connect the red wire coming from point E on the 8 wire harness to lug 7 . . . If you don't find point E on the Pictorial 6 refer back to Detail 2A.

In the range switch wiring, the instructions sometimes order "S-2" (*solder two wires here*) at switch lugs that have only a single bare wire threaded through them. Don't get confused, Heath is referring to the one wire—coming and going.

Calibration as outlined in the instruction manual is quick and simple. A fresh 1.5-volt battery is used as the calibration standard for DC, and the AC line serves for the AC ranges. The process is simple and a meter calibrated with these two "standards" would be quite accurate enough for general work. For greater accuracy (which the instrument is certainly capable of), leave the unit on for 48 to 72 hours and then take it down to an electronics laboratory or meter repair shop, where high-accuracy standard meters are available. You shouldn't be charged more than a few dollars for calibration and you'll have a meter that's right on the button.

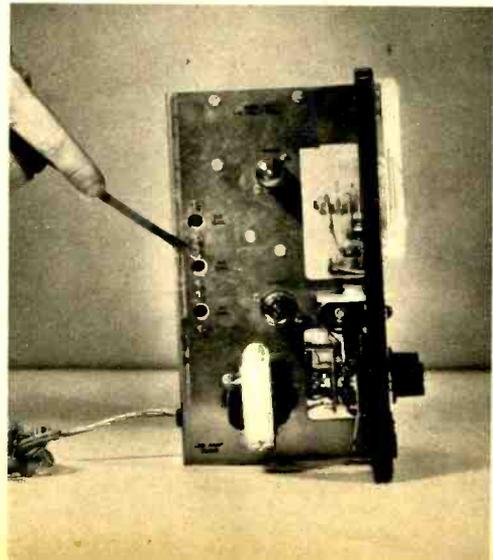Completed VTVM showing the three clearly marked calibration controls along the rear edge.



HI-FI RECORD GUIDE

by Warren DeMotte

BASIC LIBRARY FOR BEGINNERS II

IN this issue we'll wind up our piece on buying a basic record library, the first half of which appeared in the preceding issue.

The sound of a symphony orchestra is so rich, so colorful and stimulating that a basic record library usually is built around symphonic music. The nine symphonies of Ludwig van Beethoven are the heart of the symphonic literature, and the Fifth, in the key of C



Minor, is the most typical and popular. This is the symphony whose four-note opening theme symbolized "Fate knocking at the door" for the composer. As their rhythmic pattern also spells the letter "V" in Morse code, the four notes stood for Victory in World War II, and were sounded often to inspire the Allies in their struggle against the Axis.

Fritz Reiner leads the Chicago Symphony Orchestra in a powerful rendition of this symphony, well recorded, and Josef Krips conducts the London Symphony Orchestra in not quite so powerful a performance, but better recorded.

Offering somewhat more profundity and no less excitement than the Fifth,


Beethoven's Third Symphony, the Eroica, is perhaps an even wiser choice for the basic library. The mightiest performance on records is by Toscanini and the NBC Symphony Orchestra (see cut), but the recorded sound is not particularly faithful to the original. Excellent sound and a worthy performance are available in the recording by the Cleveland Orchestra under George Szell.

Of the fifty-odd symphonies familiar to the experienced concert-goer, probably none is loved more than Franz Schubert's Unfinished Symphony. Its two great movements are poignantly beautiful. Again, Toscanini provides a magnificent reading with less than admirable recording, while Paul Kletzki and the Royal Philharmonic Orchestra perform admirably and are recorded with distinction.

For formal perfection, no symphony surpasses Wolfgang Amadeus Mozart's 40th, in G Minor. It is a miracle of balance, exaltation and passion. Otto Klemperer leads the Philharmonia Orchestra in an inspired performance, well recorded. Less nobly interpreted, but not inconsequential, is the version by Leopold Ludwig and the London Symphony Orchestra, which has the added virtue of being paired with an equally estimable performance of Schubert's Unfinished.

The C Minor Symphony of Johannes Brahms, his First, was hailed on its appearance as the successor of Beethoven's mighty Nine. Its majestic measures are given a vital reading by Toscanini, recorded this time with reasonable fidelity. More vivid sound, though, is accorded the somewhat less compelling utterances of Leonard Bernstein and Antal Dorati.

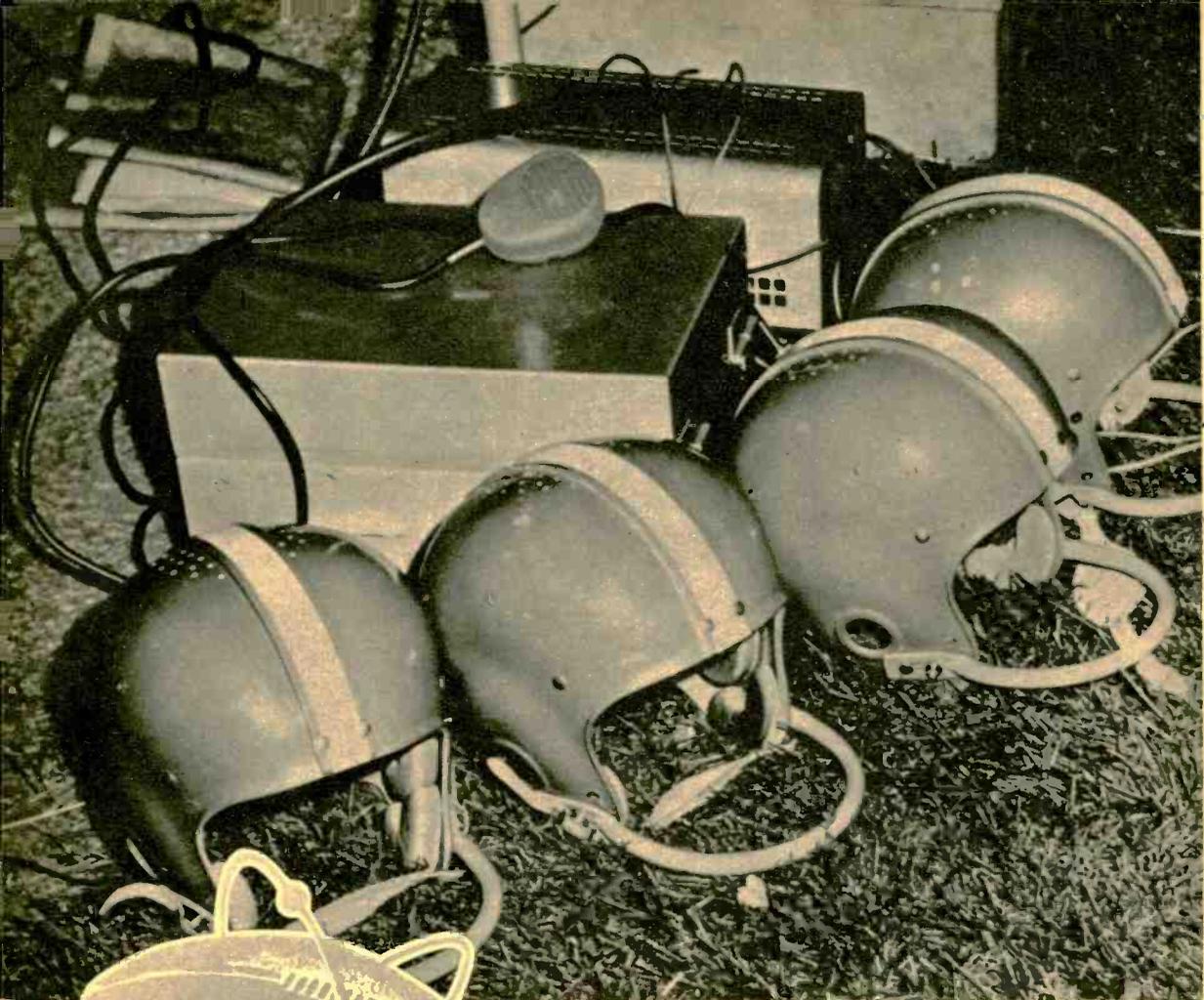The melancholy melody which opens the slow movement of Peter Ilich Tchaikovsky's Fifth [Continued on page 116]



PIGSKIN ELECTRONICS

How well your alma mater does on the gridiron may depend on the number of electronic gadgets it has.

By Alan D. Haas

IN FOOTBALL it's getting so it doesn't matter whether you win or lose, or even how you play the game—just so long as your electronic gear doesn't conk out in the last quarter. For football, like many other fields, has seen a major in-


vasion of electronic gadgets and gimmicks. When your quarterback drops the ball nowadays you can always blame it on a short circuit in his helmet receiver.

Over the past half-dozen years the

A special electrically-driven, fast-developing camera shoots movies at a Rutgers-Columbia U. game. Footage is processed as fast as it is shot, and then . . .



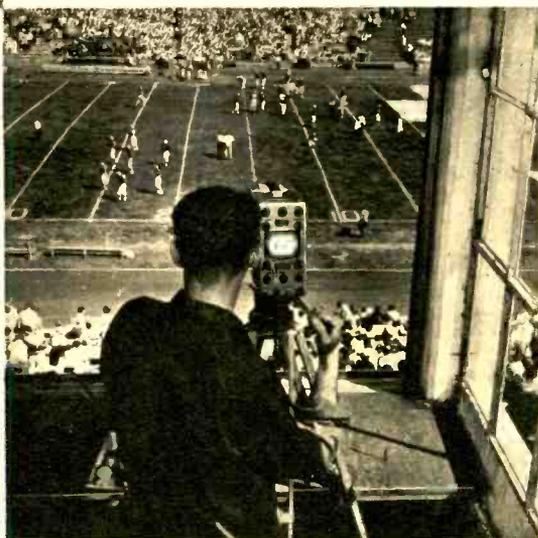. . . between halves the movie is viewed by the players in their locker room. Coach points out mistakes and opportunities. A standard projector is employed.




In a noble Kansas U. experiment a closed-circuit TV camera in press box fed images of game to . . .

. . . a 21-inch receiver being watched by coach on bench. This was first use of CCTV in football.



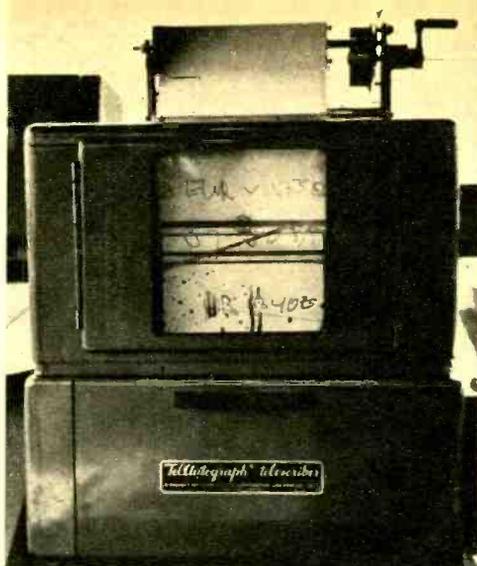Pro player Joe Schmidt lugs mike, amplifier and a radio-equipped helmet as he goes to the field.



L. A. Rams use Telautograph to relay diagrams of plays from spotter in stands to coaching bench.

gridiron has seen the water bucket and the towels joined on the sidelines by two-way radio, closed-circuit TV, video tape, Telautograph machines and instant-developing movie cameras. The coach consults with his electronics engineer before he plans field strategy.

Both the pro teams and college elevens have experimented with electronic gadgetry. A few devices have been declared illegal but others have sprung up to take their places.

As far back as 1954 the University of Kansas installed a closed-circuit TV camera in the press box and a monitoring receiver on the coach's bench. With both ground-level and bird's-eye views of the game, the coach figured he could see exactly what his boys were doing. As it turned out, the Jayhawks didn't have a very good season, TV or not.

Perhaps the most famous user of electronic gimmicks was coach Paul Brown of the professional Cleveland Browns. He set up a four-watt short-wave transmitter on the bench and installed a tiny receiver in the helmet worn by quarterback Otto Graham. With this system Brown could whisper all kinds of orders into Graham's ear. Opponents started screaming about unfair play and all that sort of thing and the commissioner eventually banned the system.

Two other pro teams, the Lions and Cardinals, buried huge induction coils

along the sidelines. Signals pumped into the underground coils were picked up by helmet receivers. Trouble was, opponents could listen in.

Not long afterward, the Los Angeles Rams installed a Telautograph machine, a device in which a pen writing on a roll of paper duplicates the actions of another pen some distance away. The Rams put the writing end of the unit in the stands and the receiving end on the coaching bench. A scout, viewing the game from on high, sent play diagrams down to the coach.

Last season Columbia University used an electrically-driven movie camera which developed the film as it was exposed. The coach sat atop the stands with the camera to review plays seconds after they were run off, and then showed the film to players in the locker room between halves.

Princeton and other Ivy League colleges are known to employ complicated computers to analyze football plays.

Several colleges have arrangements whereby video tapes of televised games are lent to the coach after it's all over. A few schools have gone this one better by getting hold of video tapes showing future opponents in action.

If the trend continues, football players may learn to have more fear of saboteurs with wire-cutters than of opposing teams.

FREE!

340 GIANT-SIZED PAGES
1962 Electronics Catalog
from Lafayette Radio
Electronics Corp.

"America's Hi-Fi & Electronics Shopping Center"



Yours free for the asking — the biggest, best and most comprehensive catalog in the 41-year history of Lafayette Radio. Audiophile, Experimenter, Hobbyist, Technician, Engineer, Student, Serviceman, Dealer — you'll find what you want in this latest Lafayette catalog.

LARGEST STOCK SELECTION. Stereophonic Hi-Fi equipment, Citizens Band, Ham and Amateur equipment, Radio & TV parts, Optics, Industrial Supplies, and much more, including all the favorite name brands.

LAFAYETTE EXCLUSIVES. Featured are the famous Lafayette Kits . . . dollar for dollar the best value for your money today. You'll also see hundreds of Lafayette specials . . . available only from Lafayette. And, as always, **SATISFACTION GUARANTEED OR MONEY REFUNDED.**

LOWEST PRICES. You'll save money too with Lafayette's low, low prices. The lowest prices are always in the Lafayette catalog.

24-HOUR SERVICE. Quick, courteous service is your guarantee at Lafayette. Most orders are fully processed within 24 hours after receipt in the mail Order Division.

NEW EASY-PAY PLAN.
 Now, **NO MONEY DOWN . . .**
 up to 24 months to pay.



**COMPLETELY WIRED,
 FULL SIZE
 TUBE TESTER**
 TE-15 19.95



**10,000
 OHMS-PER-VOLT
 MULTITESTER**
 TE-10 9.95



**TRANSISTORIZED
 PORTABLE TAPE
 RECORDER**
 RK-125 29.95



**9-TRANSISTOR
 CITIZENS BAND
 "WALKIE TALKIE"**
 HE-29A each 39.95
 2-for 78.88



**SUPERHETERODYNE
 COMMUNICATIONS
 RECEIVER**
 KT-200, Kit 64.50
 HE-10, Wired ... 79.95



**FM STEREO
 MULTIPLEX TUNER**
 LT-700 129.50

**LAFAYETTE
 RADIO**

165-08 LIBERTY AVENUE, JAMAICA 33, N. Y.
 OTHER LOCATIONS

NEW YORK, N. Y.
 100 6th Avenue
NEWARK, N. J.
 24 Central Avenue
BRONX, N. Y.
 542 E. Fordham Rd.

BOSTON, MASS.
 110 Federal Street
PARAMUS, N. J.
 182 Route 17
PLAINFIELD, N. J.
 139 W. 2nd Street

Lafayette Radio, Dept. E1K-1 P.O. Box 190 Jamaica 31, New York

- Rush my **FREE Lafayette 1962 Catalog 620**
 Please send me # _____, shipping charges collect.


I am enclosing \$ _____

Name _____

Address _____

City _____ Zone _____ State _____

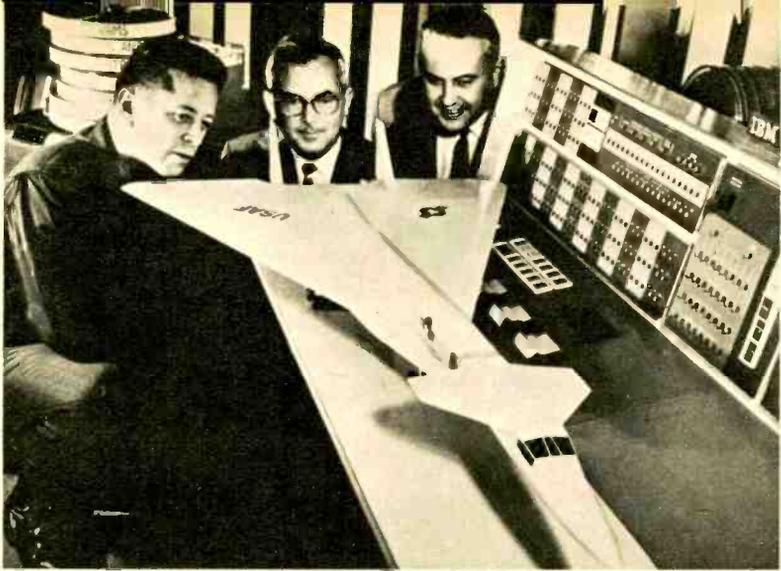Although the triple-sonic B-70 bomber has never left the ground, test pilot Al White (left) and his two associates know pretty much how it will fly because of work by computer on which model sits in this photograph. The computer not only helped design the ship, but has test flown many versions of the rakish plane.



THE B-70's *INVISIBLE FLIGHT*

THE first model of America's newest bomber, the triple-sonic B-70 Valkyrie, has never been built but the futuristic-looking aircraft already has made countless flights and practiced take-offs and landings for hours.


These flights were not of the usual kind, however, and no one could see them. They were all confined to the electronic circuits of computers.

The B-70 is the first aircraft not primarily designed by engineers. Instead, various performance requirements were fed into electronic brains, which then figured out the necessary design.

Computers also worked the other way. They took off, flew and landed a good many test designs worked out by engineers (and cracked up not a few faulty models).

Many computers were used in the B-70 design job, most of them large and incredibly expensive. One exception was a desktop computer employed by Cleveland Pneumatic on the braking system. This brain, designed at the University of Michigan and built by Applied Dynamics, is only about as large as a refrigerator and a stripped-down version costs as little as \$2,000.

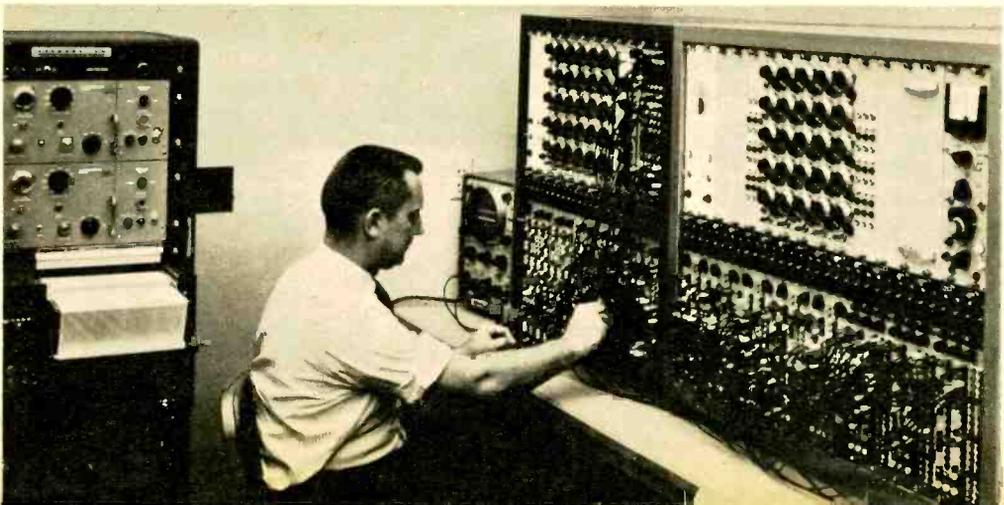This relatively small desktop computer assisted in design of the B-70's complex braking system.



The Listener

Continued from page 54

cut out. But, as it was, we believe many SWLers sensed that something was wrong in the Dominican Republic long before the official announcement came at 4:45 P.M. EST.

—○—
Cuban Catch . . . In addition to fascinating listening, that Cuban invasion produced one DX catch that was pretty wild. At 1932 (7:32 P.M.) EST Radio Caribe (a mortal enemy of Castro) announced that Cordona, a rebel leader, would go on the air at midnight via a transmitter in the Escambray Mountains and proclaim his own provisional Cuban government. This report later was repeated by U.S. news services.

At 2350 (11:50) the station did come on as Radio Cambre, using 7000 kc, right at the bottom of the 40-meter amateur band. One of the American DXers who heard it was Marv Robbins of Omaha. First part of the transmission was instructions for troop movements and the last couple of minutes (which I heard) consisted of anti-government messages.

Then a strange thing happened. Cordona turned up the following morning in New York, making it impossible for him to have broadcast live from the Escambrays at midnight. There seem to be four possibilities: the broadcast was a recording, someone substituted for Cordona, the broadcast came from the Dominican Republic (and Cordona flew out immediately afterward), or some Latin American ham is a practical joker.

—○—
Who's on First? . . . Let's return to the Dominican Republic's Radio Caribe. Officially, Caribe is a private station with plenty of commercials, although all press and radio services there are tightly controlled by the government. In the past, Caribe seems to have carried out some strange jobs, in addition to its usual broadcasting duties.

In the winter of 1959-60 a widely-heard short-wave station was the clandestine Radio Liberacion de Venezuela, operating around 9505 and 6090 kc. Its

campaign against the Venezuelan government was climaxed by an attempted assassination of the President.

After this little cutthroat business failed the plot was laid to none other than the Dominican Republic's El Jefe, the late Raphael Trujillo. The Republic eventually was kicked out of the organization of American States, partly because of this incident. The question immediately arose as to who had been running Radio Liberacion de Venezuela and where its transmitter was located.

Liberacion vanished from the air early in the summer of 1960 and then on the same frequencies appeared HIX Radio Nacional Dominicana. HIX is the traditional call for government stations down there. But HIX also lasted only a few weeks and by mid-summer its frequencies were taken over by Radio Caribe, the Republic's "private" station.

All this seems to boil down to the fact that just one transmitter was involved in these goings-on. HIX and Caribe apparently were just different names for the same station, and it also appears certain that the Venezuelan rebel radio broadcasts came straight from the same place.

After becoming Radio Caribe, the station broadcast in many languages, including English programs for U.S. consumption. Most of these broadcasts attacked the U.S. State Department for trying to cut off windfall sugar profits for the Dominican Republic after the Cuban sugar ban.

After the sugar deals were worked out Caribe stopped most of its foreign language broadcasts and stuck mostly to Spanish.

The station continues to grow technically. It took over Radio Deportive Handicap with operations on 49 meters (6210 kc) and the broadcast band (860 kc), and then its 31-meter transmitter was moved to 9485 kc, just below the 31-meter band, to avoid interference. At last report, new Caribe channels had appeared at 15050 and 3322 kc, and a little later the studios were damaged by fire in a riot.

With such a varied history and the promise of offbeat doings in the future, Radio Caribe bears watching. —○—

New Rules For CB

Continued from page 73

utes. This must be followed by a two-minute silent period to check traffic on the channel. This procedure allows others to dispatch messages. If, after two minutes, the channel is clear, you may occupy it for an additional five minutes, if needed.

Now we come to one of the most welcome revisions in the old CB rules. It opens up a new area of service in the Class D band by permitting the combination of CB radio with commercial telephone-answering services.

According to the old rules in Part 19, a CB station was permitted to provide any person with radio service on a voluntary, no-charge basis. But any shared or cooperative use of the band was prohibited. This last point is the important one. It prevented a telephone-answering service from notifying you of a phone call via CB radio.

To make the combination, you must send a letter to the FCC requesting permission for this proposed use of the band. It must state that you will have access to and control over the equipment. This does not mean you personally have to operate it, but that you hold the license and bear the responsibility for its proper operation. In brief, you can place one of your CB units at the telephone-answering office and instruct someone to contact you when the need arises. All this must be on a non-profit basis, although the cost of the CB facility may be shared.

Changes in the technical part of the rules finally settles the controversy over who may build and tune a CB rig. These changes are found under Operator Requirements. No longer do you have to hold a first- or second-class commercial license to perform some of the superficial adjustments to your set. Part of the burden is placed on the manufacturer. Factory-wired equipment must be designed so that normal transmitter adjustments will not result in improper operation. This would include off-frequency, excessively powerful and false emissions. For kit-built units, the manu-

facturer must provide a sealed crystal oscillator. The rest of the circuit may be constructed in the usual kit fashion.

The changes in regulations accomplish two things. First, they keep the non-technical person out of the critical portion of the circuit, the crystal oscillator. Secondly, they allow the CB licensee to tune a transmitter into an antenna without having to enlist the services of a licensed specialist.

The fact that the FCC has made some ten changes in Part 19 indicates the law is by no means fixed. Its constant state of flux points up the substantial growth and problems of CB radio. Watch for future amendments. They are bound to reflect the FCC's intent to keep the band operating in the "public interest, convenience and necessity."

High-Flying Ham

Continued from page 58

a message to my wife telling her when to expect me.

Butch is a native of Erie, Pa. He attended Columbia University and Ohio State, enlisted in the Air Corps in 1928 and earned his wings in 1929. He spent the next ten years performing normal squadron duties in Michigan, Illinois, Virginia and Hawaii. Fliers of that period were required to know code pretty well, so he had no trouble qualifying for a license when he became interested in the ham game in 1938. His first call was W3IXM, issued when he was at Langley Field, Va. As he transferred from station to station, he acquired W2NRV, W6UFT, KG6AAF, KG6BN and W4OTZ.

When World War II broke out, the then Major Griswold was one of a group of experienced professional airmen whom the Army Air Corps pushed up the ladder almost overnight. In 1942 he went to England to serve with the Eighth Air Force, and before the end of the conflict in Europe he was a brigadier general. By 1952, Butch had become a major general, and then in 1957 a lieutenant general. He has been at SAC since 1954.

Although a high-ranking officer with

Continued from page 51

awesome military responsibilities, KØDWC is without pose or guile. When he contacts a new station his standard introduction is, "My name is Butch." If someone asks him what he does, he replies, "I'm in the Air Force." Many a young airman or soldier, operating at some MARS (Military Affiliate Radio System) station, is flabbergasted later to learn that the friendly Butch he chatted with for five minutes is a three-star general.

Butch has been one of the important proponents of single sideband communications and is given credit for helping make SSB popular on the ham bands. In 1956, while on a routine inspection trip in the Pacific, the general and several cooperating hams demonstrated the effectiveness of SSB as airborne communications equipment by maintaining virtually continuous contact with the United States while his plane was aloft over the Pacific. He used standard ham equipment, such as he has today in his base shack at his quarters at Offutt. During a 15,000-mile flight, the men made more than 1,000 amateur contacts with 26 countries, including Little America, and collected much valuable technical data. That the Air Force was impressed by this feat is indicated by the fact that it has gone all-out for SSB for a variety of air-to-air, air-to-ground, and ground-to-ground communications.

Over the years, Butch has used a good many different planes and pieces of radio gear. His equipment in the C-97 was a standard transceiver which Collins makes for the Air Force. His antenna was merely a single wire running from nose to tail, which is not very classy, but when you get it several miles high, what a reach it has! In his ground shack, the general has a Collins 75A-4 receiver and KWS-1 transmitter, the same equipment he once used in a plane.

As Vice-Commander in Chief of SAC, General Griswold is on what amounts to continuous alert. This wouldn't seem to leave much time for anything other than eating and sleeping. But somehow he does find time, not only for time-consuming amateur activities, but for hot cars and fancy cameras. ⚡

checked for calibration without removal from the car. The calibrator with its antenna is placed several inches from the mobile antenna; a distinct hush will be heard in the receiver at the calibration points. If the mobile receiver is equipped with a BFO so much the better. Up at 6 meters, it may be necessary to connect the two antennas with a clip lead.

A mobile VFO's calibration can be checked by zero-beating the received calibrator marker frequency against the VFO. Tune in a marker (e.g.: 7 mc) and adjust the transmitter's oscillator until zero-beat. The VFO is then set for 7 mc. The same procedure is used for other frequencies.

Using a similar procedure, the calibration of RF signal generators can be checked. The output from a signal generator is fed into a receiver with the output of the calibrator and the generator is calibrated at zero beat. With a broadcast band range generator a standard radio can be used as the receiver.

At very high frequencies where the calibrator's output is reduced, run a wire from the calibrator to an alligator clip on the insulation of the "hot" antenna wire. In some instances, such as calibration of an FM tuner, the calibrator will have to be connected directly to the receiver's antenna terminals. For maximum stability, always ground the case of the calibrator to the equipment under test. Using the 1 mc output, an FM tuner dial can be adjusted or marked "on the button" across the dial.

How It Works

Oscillator transistor Q1 has an anti-resonant feedback path connected between collector and base. At 100 kc, the low-Q coil L1, has low output and requires the use of amplifier Q2. Since the base-emitter conduction of Q2 has a diode action, a signal rich in harmonics is produced. At 1 mc, high-Q coil L2 becomes the oscillator tank coil and the high 1 mc output does not require amplification. This permits the use of low-cost transistors and stock coils. ⚡

Should You Go West?

Continued from page 69

start. Thereafter, they can expect an average \$50 monthly salary boost each year. In ten years they probably will be getting from \$900 to \$1,000 a month.

To get a clearer picture of your chances in Southern California you should know something about the area. In brief, it is swarming with people (6,800,000 in Los Angeles and Orange County alone) and growing like a weed. The electronics complex is a big one, stretching all the way from Vandenberg Air Force Base on the north to the Mexican border 300 miles away, and from the Pacific to Edwards AFB, 100 miles inland. Scattered in this piece of countryside are no less than 17 electronic hubs, each with its own specialties. The map at the head of this article indicates the more important centers. Let's talk about some of them in detail:

The San Fernando Valley is defense-oriented. Here is Lockheed's huge Burbank Division, an aircraft plant with a large electronic payroll. At nearby Canoga Park is Rocketdyne, with 5% of its 11,000 employees in electronics. Rocketdyne's rocket-test facility at Santa Susana employs 1,000—of which 300 are in electronics. There are smaller electronic plants by the hundreds.

In southern Los Angeles the Downey complex includes North American Aviation's Autonetics Division, engaged in design-production of electronic components for the Hound Dog missile, guidance systems for the Minuteman and fire control circuitry for F-104 fighters.

The fastest-growing electronic complex is centered around Anaheim, Fullerton, Buena Park and Santa Ana in Orange County. It runs the gamut from consumer hi-fi (Altec Lansing Corp., Anaheim), instruments (Beckman Industries, Fullerton) to controls (Borg-Warner, Santa Ana).

Around top universities (UCLA in West Los Angeles and Cal-Tech at Pasadena) have grown up modern-day think factories, heavily keyed to electronic research and development.

San Diego is transitioning from air-frame assembly (Convair) to Navy and space electronics (Convair and the Navy's electronic laboratory).

Many hard-hit plane makers are going into electronics. The Autonetics division of North American Aviation is one example. Ryan Electronics in San Diego, a division of Ryan Aeronautical Co., now turns out navigation gear, radar systems and missile guidance controls.

Southern California's defense-heaviness doesn't worry most experts because the area is one of the brain-centers of U. S. missiledom, particularly space electronics. "And," says one expert, "space electronics can go in only one direction . . . straight up."

If you hanker to follow the sun it's a good idea to contact the Western Electronic Manufacturers Association, 1435 South La Cienega Blvd., Los Angeles 35, and obtain their directory (\$2), which has thumbnail sketches on all the major companies.

The Sunday edition of the Los Angeles Times (\$2 a month by mail) has a veritable electronics call-board in its classified section and will give you a good idea of what's going on in the hiring line at any given time.

As the employment agency executive said, it's best *not* to land cold in California. Send out queries by mail first. Besides having a job ready when you get there, many companies will pay your moving expenses . . . and you're in a better bargaining position at a distance.

To sum up, Southern California does offer many opportunities to men in electronics. Whether *you* should become a 1961-style wester is for you to decide. ●

Tech Editor's Test Bench

Continued from page 43

are not covered in our survey. Some are about to be discontinued, according to their manufacturers. Others are not widely distributed. And a few are, in our opinion, not of high enough quality to merit testing.

The tech spec table needs a few extra words, particularly in regard to sensi-

Ham Shack

Continued from page 74

tivity and distortion figures. When dealing with a distortion reading of less than 0.5%, the residual distortion in the test instruments starts to become significant. And, in general, it's extremely doubtful that most audiophiles could hear a difference between two units which check out below the 1% mark.

If you compare EI's test results with manufacturer's specs you'll come across discrepancies. These can be accounted for in several ways. For one, several companies have not yet accepted the Institute of High Fidelity Manufacturers' standards.

On the matter of I.M. (inter-modulation) distortion figures quoted in the chart: for technical reasons we did not use IHFM standards but, since the figures were all derived by the SMPTE (Society of Motion Picture and Television Engineers) technique they can be compared validly.

When you buy a tuner, is its quality going to check out with the figures in our chart? The answer is *maybe*. In electronics, as in other areas, a law of randomness comes into play. The tuner you construct may work slightly better—or slightly worse than the one we built because of a tube with extra high gain, closer coupling in an IF transformer or any of a hundred chance factors.

Occasionally, because of some snafu at the factory, a "pre-aligned" sub-assembly won't be. This, however, is something that can happen even with factory-wired equipment. In short, you run no special risk of getting a lemon when you buy a kit.

The instruction manuals were quite good and would guide the novice step-by-step toward successful assembly of the kit selected. When our reviewers found fault with the instructions, the manufacturer was notified.

When we tested the units built by novices, we found bad solder connections far outnumbered wiring errors as the cause of non-operation. And it seems *printed-circuit boards are no guarantee of good soldering.*

We have not given construction times for the kits, except when unusually high or low. In general, you can figure on about eight hours before plug-in time. ♪

Sideband-ese . . . Virtually identical letters have arrived from several readers reporting the reception of mysterious garbled signals on the upper ends of the 15-, 20-, 40- and 80-meter phone bands.

"I hear lots of other stations loud and clear, so my receiver must be okay," writes Steve Rickman of Columbus, Miss. "Is this stuff some kind of scrambling?"

No, Steve, you have merely made the acquaintance of SSB, which stands for single sideband suppressed carrier. It's a form of voice transmission in which either the upper or the lower sideband resulting from voice modulation and the carrier wave are suppressed in the transmitter, leaving just one sideband—a single sideband—to be transmitted. This signal occupies less than half the space of conventional double sideband (DSB) emissions and is less subject to fading, yet it contains exactly the same voice intelligence.

The trick at the receiving end is to turn on the BFO (beat-frequency oscillator), normally used only for code reception, and to tune carefully.

Most lower-priced all-wave sets and many communication receivers made before 1950 are not satisfactory for SSB because their BFO's are not sufficiently adjustable or stable enough to hold the narrow signal. With a regular SSB receiver the sideband voice loses its monkey-chatter characteristics and booms through with clarity. ♪

Good Reading

Continued from page 55

many ways, for purposes like traffic control and weather forecasting, a new book on the subject is particularly welcome. This slim volume contains a wealth of information, covering everything from basic theory to specific receivers, oscillators, and antenna systems. Clearly written, and well illustrated, it's worth having just for keeping up to date on an interesting part of electronics. ♪

Circuits For Stereo FM Adaptors

Continued from page 45

via a capacitor and resistor to a 19-kc filter (L1), which allows only the 19-kc pilot to pass to the grid of V2. V2 serves as a doubler-amplifier, which amplifies the pilot signal and then doubles its frequency to 38 kc at T1.

Since the 38-kc signal is derived from the 19-kc pilot transmitted by the FM station, it is identical in phase and frequency to the 38-kc subcarrier generated (and then suppressed) at the station's stereo modulator. In fact, the signal developed by V2 is called the recovered subcarrier. The secondary of T1 couples this recovered subcarrier to the detector.

Returning to the first stage, the output of V1 also is fed through a voltage divider (R1 and R2) to a 38-kc bandpass filter (L2, L3, C1, C2, and C3). The bandpass filter allows only the L-R signal (23-to-53 kc) to pass on to the subcarrier detector.

In still another operation, V1's output is also applied via a potentiometer (which functions here as a separation control) and a 19-kc filter network which passes only the L+R signal to the matrix circuit. In addition to filtering the L+R signal, the network provides a time delay to keep the L+R signal in step with the L-R signal, which falls behind because of its longer circuit path.

At the input of the subcarrier detector (D1 and D2) the recovered subcarrier (from T1) is combined with the L-R signal from the 38-kc bandpass filter. The result is a completely reconstituted subcarrier identical to the modulated subcarrier originally formulated at the transmitter.

The sidebands now are detected in the usual way by diodes D1 and D2. Note that the diodes are connected in opposite polarity. Each detects (converts to audio) the L-R signal. However, the output phase of D1 is positive, resulting in $+(L-R) = L-R$, while D2's output is negative, resulting in $-(L-R) = -L+R$, or $R-L$.

The output of the detector (L-R and $-L+R$) is fed to one side of the matrix-

ing bridge composed of R3, 4, 5 and 6. The opposite side of the bridge is fed by the L+R signal from the time delay network. In the matrixing bridge an algebraic addition of the input signals occurs in the following manner: $(L-R) + (L+R) = 2L$ and $(-L+R) + (L+R) = 2R$. It is important to note that the amount of stereo separation depends on how well the bridge is balanced.

One standard de-emphasis network (R7 and C4) is inserted in the left channel output and another (R8 and C5) in the right channel output. The output impedance of the detector is high, so there is a cathode follower at each channel output to prevent excessive loading of the detector.

Zenith Circuit

As shown in Fig. 3, Zenith uses a time division technique. Their adaptor switches alternately between the left and right stereophonic program channels, sampling *each* 19,000 times a second (which adds up to 38,000 cycles—38 kc—per second).

Although the time division technique of stereo transmission is substantially different from the matrix system, the transmitted signal is the same and so is the output signal that appears at the multiplex output jack of the FM tuner.

The input stage of the Zenith adaptor is a cathode follower (V1) whose high input impedance prevents loading of the tuner's detector. The second stage (V2) is a straight amplifier. The third (V3) is a semi-cathode follower with its plate circuit connected to the primary of T1. T1, slug-tuned to 19 kc, appears as a very high impedance to a signal of that frequency. To all other frequencies T1 is a dead short to B+, and V3 is merely a cathode follower.

The secondary of T1 (also tuned to 19 kc) serves as the tank circuit of Hartley oscillator V4. In order to lock in V4 to the desired frequency (19kc), the pilot frequency (which appears at V3's plate because of T1's high primary impedance at 19 kc) locks in V4 and forces it to oscillate at exactly the same phase and frequency as the pilot signal.

The plate of locked oscillator V4 feeds the primary of T2, which is tuned to 38

[Continued on page 108]



"a CREI home study program helped me become an electronics engineer"

—Robert T. Blanks
 Engineer, Research & Study Division
 Vitro Laboratories, Silver Spring, Md.
 Division of Vitro Corporation of America



"THROUGH A CREI HOME STUDY PROGRAM I learned the practical theory and technology I needed to become a fully-qualified engineer—not a 'handbook' engineer, either—and I did it while I was on the job," says Robert T. Blanks. Today thousands of advanced electronics personnel—engineering technicians, engineers, administrators, executives—attribute their present high salaries and positions to their home study of CREI Programs in Electronic Engineering Technology.

DEMAND FOR CREI-PREPARED MEN today far exceeds the supply—has exceeded the supply for many years. Specifically designed to prepare you for responsible positions in electronics, CREI Home Study Programs are the product of 34 years of experience, include the latest advancements in the field. CREI's curricula was among the first accredited by the Engineers' Council for Professional Development. Here Blanks discusses CREI with Director Wayne G. Shaffer of Vitro Labs.



WHEN YOU ENROLL IN A CREI Home Study Program, you join more than 20,500 students working in electronics in all 50 states and most countries of the free world. One CREI Program helped Robert Blanks become an Electronics Engineer. Another helped Robert I. Trunnell become an Electronics Technician. While John H. Scofield—a Mathematician—is enrolled in still a different CREI Program relating mathematics to electronics. All work at Vitro Laboratories.

YOUR LIVING IS BETTER when you prepare for—and get—desired promotions through CREI Home Study. CREI alumnus Blanks is understandably proud of his home in a comfortable neighborhood. The positions of CREI-prepared men in such companies as Pan American Airways, Federal Electric Corporation, The Martin Company, Northwest Telephone Company, Mackay Radio, Florida Power and Light and many others attest to the high calibre of CREI Programs.

YOUR WHOLE FAMILY BENEFITS. Engineer Blanks' growing family pitched in to provide free time for his CREI Home Study. Now they share his success. We invite you to check the thoroughness and completeness of CREI Home Study Programs in Electronic Engineering Technology in the catalog provided on request. For those who can attend day or evening classes in person, CREI maintains a Residence School in Washington, D.C. also offering ECPD Accredited Technical Institute Curricula.

INDUSTRY-RECOGNIZED CREI HOME STUDY PROGRAMS PREPARE YOU FOR INCREASED RESPONSIBILITIES, HIGHER-PAYING POSITIONS IN ELECTRONICS.

REQUIREMENTS FOR ENROLLMENT Pre-requisite is a high school education or equivalent plus basic electronics training and/or practical electronics experience. (Electronics experience and/or training not necessary for Residence School.) If you qualify, send for the latest CREI catalog at no cost. Veterans may apply under the G.I. Bill. If you're doubtful about your qualifications, let us check them for you. Mail coupon or send your qualifications to: The Capitol Radio Engineering Institute, Dept. 1711-H, 3224 Sixteenth St., N.W., Washington 10, D. C.



The Capitol Radio Engineering Institute

ECPD Accredited Technical Institute Curricula • Founded 1927

Dept. 1711-H, 3224 Sixteenth St., N.W., Washington 10, D. C.
 I am interested in the opportunities offered by the CREI Home Study Programs in Electronic Engineering Technology. (Every COMPLETED Inquiry will be acknowledged.)

- I believe my qualifications as listed below meet CREI requirements. Please send me your latest catalog at no cost. Please check my qualifications below and let me know if I am eligible for CREI Home Study Programs.

- CHECK FIELD OF GREATEST INTEREST:**
- Servo and Computer Engineering Technology
 - Automation and Industrial Electronic Engineering Technology
 - Electronic Engineering Technology
 - Nuclear Engineering Technology
 - Aero and Navigational Engineering Technology

My educational and Electronics experience qualifications are: (All information held in confidence) Employed by _____

Type of present work _____

Education: Years High School _____ Other _____

Electronics Experience _____

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Check: Home Study Residence School G.I. Bill

for the Newest Kits, the Finest Quality,
the Greatest Values . . . look to Heathkit,
the world's shopping center for Electronic Kits



NEW STYLING



Deluxe . . . tops in Heathkit stereo/hi-fi styling with luggage-tan vinyl-clad cabinets, plastic fronts, refracted lighting. Choose matching tuner and amplifier. Left: **AA-100** 50 watt stereo amplifier, 31 lbs. **\$84.95**

Everything is

NEW



20 New Stereo Hi-Fi Kits . . . Tuners, Multiplex, Amps., Speakers, from \$16.88 up! Above: **AA-11** Deluxe Stereo Preamp., 19 lbs. . . . **\$84.95**



New "Walkie-Talkies" . . . Deluxe Superhet, 9-Trans. & Economy 4-Trans. Regen. Both in handsome styling. Above: "Deluxe" **GW-21** 3 lbs. **\$44.95**



Short Wave Listeners Radio . . . Circuit board; beige, aqua steel cab.; four bands, 550 kc-30 mc; lighted meter & dial. **GR-91** 9 lbs. **\$42.50**



8 New Test Instruments . . . Capacitor Checker, "Handy-Lab," Transistor Tester, Scope, kit & wired VTVM's. Above: **IM-20** "Handy-Lab," 2 lbs. **\$14.95**

NEW GUARANTEE

We guarantee that you can build any Heathkit!

The Heath Company *unconditionally guarantees* that you can build any Heathkit product and that it will perform in accordance with our published specifications, by simply following and completing our check-by-step instructions, or your purchase price will be cheerfully refunded.

This Heathkit guarantee, unprecedented in the industry, is made possible by our millions of satisfied customers who have proved that building a Heathkit requires no special background, experience, skills or training.

NEW NO-MONEY DOWN TERMS

It's easiest to buy Heathkit! With these new *no-money down* terms you can order the Heathkits of your choice . . . send no down payment . . . and take as long as 18 months to pay! These new, relaxed terms, coupled with our guarantee that you can build any Heathkit, are your assurance of complete satisfaction with your purchase. Any order for \$25.00 to \$600.00 worth of Heathkit equipment is eligible for these new easy time-pay terms; write for details on orders over \$600.00. See the order blank in the new 1962 Heathkit catalog or send for application forms.

NEW is the key word this fall at Heath! NEW KITS . . . in every product line . . . forty new kits, bringing the total to over 250 to choose from . . . the world's largest selection of electronic kits! NEW STYLING . . . three new styling concepts for stereo /hi-fi, completely coordinated . . . new test instrument styling . . . newly styled citizen's band equipment . . . new variations on the Heathkit amateur radio theme. NEW GUARANTEE . . . assures your kit building success, regardless of your background or experience. NEW NO-MONEY DOWN TERMS . . . easier than ever to buy . . . your assurance of complete satisfaction. NEW FREE CATALOG . . . 100 pages . . . the world's biggest kit catalog . . . better, too, with larger photos, complete descriptions and specifications, and now with kit schematics for your complete buying information. Look to Heathkit for the NEW!



Mid-Range . . . styling combines deluxe and popular motifs; tan vinyl-clad cabs., charcoal-grey fronts, for tuner and amps.
Left: **AJ-11** AM/FM Tuner.
19 lbs. . . . **\$69.95**



Popular . . . striking charcoal grey steel cabinets with ivory accents. Choose tuners and amplifiers.
Left: **AA-161** 14 watt monophonic amp-pre-amp.
15 lbs. . . . **\$33.54**

at

HEATH



5 New Amateur Radio Kits
. . . VFO, Tunnel-Diode "Dip" Meter, Basic Receiver, "Q" Multiplier, CW Transmitter. Above: **HG-10** VFO.
2 lbs. . . . **\$34.95**



Another New Educational Kit . . . Two-Part Basic Radio Course (EK-2A & 2B). Each has authoritative textbook and parts for radio receiver.
6 lbs. . . . **\$19.95**



The World's Shopping Center
for Electronic Kits

Send for your FREE copy of the 1962 Heathkit catalog . . . the world's biggest kit catalog . . . 100 pages packed with over 250 kits . . . big new page size, big photos, complete descriptions, specs., schematics . . . we'll be glad to send your friends a copy too!



HEATH COMPANY
Benton Harbor 39, Michigan



Please send Free Heathkit catalog.

NAME

ADDRESS

CITY

ZONE

STATE

Circuits For Stereo FM Adaptors

Continued from page 104

kc and, therefore, picks up the second harmonic of the 19-kc pilot frequency. Considering V4's operation, it might be called a locked-in doubler oscillator whose output in effect is a 38-kc switching signal. And, since V4 is locked in on the 19-kc pilot, the 38-kc harmonic switching signal (to be used in V5) is identical to the original 38-kc switching signal generated at the FM transmitter's stereo time-division modulator.

Returning to the modified cathode follower (V3), the remaining signal components—the L+R signal, the L-R signal and the SCA subcarrier—appear at the cathode. These components feed a 38-kc bandpass filter consisting of L1, L2, C1 and C2. The series arm, L1 and C1 of the filter is the low-pass section which prevents the passage of the 67-kc SCA subcarrier. The shunt arm, L2 and C2, prevents the passage of the 19-kc pilot but allows the passage of the 23-to-53 kc L-R signal and the 15-to-50 kc L+R signal. In addition, the other resistors and capacitors in the network provide the standard 75-microsecond de-emphasis.

Demodulation by Deflection

The fifth stage of the adaptor is the stereo demodulator. V5 is a special type of beam deflection pentode (all grids not shown in Fig. 3). It has a pair of deflection plates placed parallel to the path of the electron beam and a pair of output plates perpendicular to the beam. Normally, the electron beam would travel from the cathode through the grids to the space between the output plates. By energizing the deflection plates, the beam can be deflected to one output plate or the other.

In this circuit, the deflection plates are connected to the secondary of T2. Since the doubler oscillator has developed a 38-kc signal in the primary of T2, the deflection plates reverse in polarity at a 38-kc rate. As a result, the electron beam is switched from one output plate to the other at this rate—38,000 times a second.

The output of the bandpass filter is fed to the control grid of the beam deflection tube. Because the phase relationships between the L and R components of the L+R and the L-R signals, the electron beam coming from V5's output plates looks like the R signal at one moment and the L signal the next. The result is the reproduction of the original L channel signal at one plate and the R channel signal at the other. Each is exactly like the original signal at the transmitter.

Now that we have recovered the original left and right stereophonic program channels, all that remains is to feed these signals through cathode followers to the output of the adaptor. The cathode followers are required for proper operation of the 38-kc rejection filters (traps) inserted between the demodulator and the output. If a large 38-kc component appeared at the output of the demodulator along with the R or L stereo signal it might introduce problems in a hi-fi system. This is particularly true when a tape recorder is connected to the output of the adaptor. The 38-kc component might beat with the bias and erase frequency of the recorder and cause "birdies" and whistles on the tape.

CB Tone Call/Squelch

Continued from page 85

constant (C2, R2) is added to the thyatron grid circuit. This prevents the short speech bursts from overcoming the negative cut-off voltage and makes it necessary for the tone to be transmitted about five seconds before the TCS operates. This time requirement can be adjusted by potentiometer R4, which varies the negative voltage on the grid of V1. The less the voltage difference between the grid and the cathode, the shorter the time required to activate the TCS.


Construction is quite simple. RY1 is insulated from the chassis with rubber grommets because the reed contacts are electrically connected to the relay frame. With the speaker disconnected during

[Continued on page 110]

Universal Replacement Parts Kit

MODEL 31T 3890

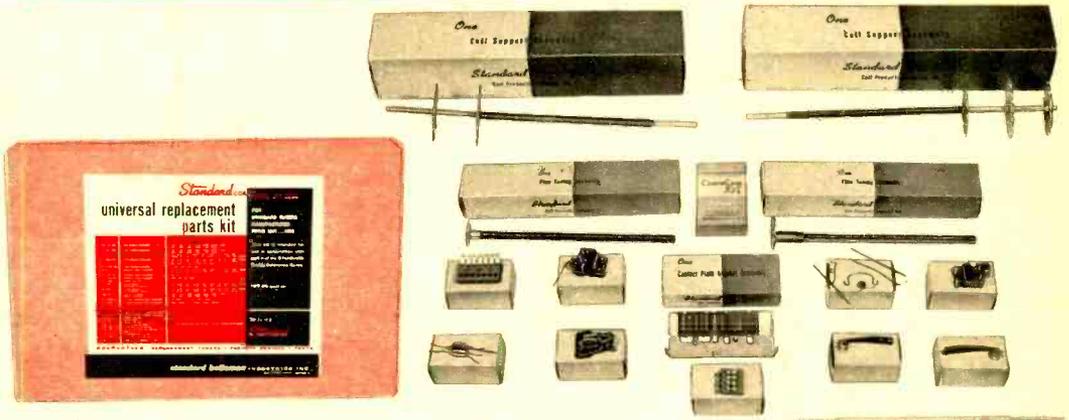Popular Standard Coil field replacement parts used extensively by servicemen for STANDARD tuners manufactured from 1947-1956.



MODEL 31T 3890

A kit of mechanical and electrical parts for shop and field use to be used in conjunction with Section II of the STANDARD Cross Reference Guide. These parts make up 90% of the replacement parts most commonly used in field service.

INCLUDED

FREE

- Special IF alignment tool for late model STANDARD TV and FM tuners.
- Popular special springs, detent springs and roller assembly, detent ball assemblies, etc.

BE PREPARED... GET YOURS TODAY from any authorized

Standard **COIL** distributor

\$27.99 DEALER NET

standard kollman INDUSTRIES INC.

FORMERLY STANDARD COIL PRODUCTS CO., INC., MELROSE PARK, ILLINOIS

Circuits For Stereo FM Adaptors

Continued from page 104

kc and, therefore, picks up the second harmonic of the 19-kc pilot frequency. Considering V4's operation, it might be called a locked-in doubler oscillator whose output in effect is a 38-kc switching signal. And, since V4 is locked in on the 19-kc pilot, the 38-kc harmonic switching signal (to be used in V5) is identical to the original 38-kc switching signal generated at the FM transmitter's stereo time-division modulator.

Returning to the modified cathode follower (V3), the remaining signal components—the L+R signal, the L-R signal and the SCA subcarrier—appear at the cathode. These components feed a 38-kc bandpass filter consisting of L1, L2, C1 and C2. The series arm, L1 and C1 of the filter is the low-pass section which prevents the passage of the 67-kc SCA subcarrier. The shunt arm, L2 and C2, prevents the passage of the 19-kc pilot but allows the passage of the 23-to-53 kc L-R signal and the 15-to-50 kc L+R signal. In addition, the other resistors and capacitors in the network provide the standard 75-microsecond de-emphasis.

Demodulation by Deflection

The fifth stage of the adaptor is the stereo demodulator. V5 is a special type of beam deflection pentode (all grids not shown in Fig. 3). It has a pair of deflection plates placed parallel to the path of the electron beam and a pair of output plates perpendicular to the beam. Normally, the electron beam would travel from the cathode through the grids to the space between the output plates. By energizing the deflection plates, the beam can be deflected to one output plate or the other.

In this circuit, the deflection plates are connected to the secondary of T2. Since the doubler oscillator has developed a 38-kc signal in the primary of T2, the deflection plates reverse in polarity at a 38-kc rate. As a result, the electron beam is switched from one output plate to the other at this rate—38,000 times a second.

The output of the bandpass filter is fed to the control grid of the beam deflection tube. Because the phase relationships between the L and R components of the L+R and the L-R signals, the electron beam coming from V5's output plates looks like the R signal at one moment and the L signal the next. The result is the reproduction of the original L channel signal at one plate and the R channel signal at the other. Each is exactly like the original signal at the transmitter.

Now that we have recovered the original left and right stereophonic program channels, all that remains is to feed these signals through cathode followers to the output of the adaptor. The cathode followers are required for proper operation of the 38-kc rejection filters (traps) inserted between the demodulator and the output. If a large 38-kc component appeared at the output of the demodulator along with the R or L stereo signal it might introduce problems in a hi-fi system. This is particularly true when a tape recorder is connected to the output of the adaptor. The 38-kc component might beat with the bias and erase frequency of the recorder and cause "birdies" and whistles on the tape.

CB Tone Call/Squelch

Continued from page 85

constant (C2, R2) is added to the thyatron grid circuit. This prevents the short speech bursts from overcoming the negative cut-off voltage and makes it necessary for the tone to be transmitted about five seconds before the TCS operates. This time requirement can be adjusted by potentiometer R4, which varies the negative voltage on the grid of V1. The less the voltage difference between the grid and the cathode, the shorter the time required to activate the TCS.

Construction is quite simple. RY1 is insulated from the chassis with rubber grommets because the reed contacts are electrically connected to the relay frame. With the speaker disconnected during

[Continued on page 110]

CB Tone Call / Squelch

Continued from page 108

standby, the output transformer primary of the CB receiver can develop voltage high enough to arc over, so a 47-ohm resistor (R1) is connected across its secondary to prevent this.

The TCS chassis is secured to the base station receiver cabinet with sheet metal screws and is mounted so that its controls are accessible.

The tone generator that supplies the triggering signal for the reed relay must be stable. And because it is self-contained, the tone generator can be incorporated in any CB unit simply by fitting its output cable with a plug to match the mike jack on your transceiver and plugging your mike into the tone generator's input. Mica capacitors are recommended for the circuit because of their better thermal stability. The DPDT microphone/tone switch (SW1), when in the *tone* position, turns on the tone generator and connects it to the transmitter microphone input. In the *microphone* position, SW1 turns off the generator and reconnects the microphone to the transmitter. Since the tone generator is used intermittently, its battery should last for its shelf life.

In order to avoid the tone overmodulating the transmitter, the 500,000-ohm pot (R13) adjusts the output voltage of the tone signal to the same relative value as that of the microphone. There is sufficient signal available from the generator to drive a carbon microphone input circuit also. The tone signal is a fairly pure sine wave, free from sideband splatter.

Another potentiometer, R8, adjusts the tone frequency to the resonant frequency of reed relay RY1. These controls are mounted inside the box because, once set, no further adjustment should be required. Several inexpensive PNP transistors were tried as Q1 in the generator and all gave good results.

The tone generator is installed beneath the mobile transmitter (the author's home-built rig is shown in the photos) so that switch SW1 is easily accessible. A short length of shielded audio cable is run to the original microphone

input plug and a duplicate microphone receptacle is mounted in the tone-generator box and the microphone is connected to it. If your transmitter is a type with the microphone cable wired in, it's a good idea to install jacks and plugs.

Aligning the TCS:

- Connect the squelch unit to the receiver and turn it on. Depress *reset* button PB1. RY2 should open, silencing the receiver. Check the voltages at V1. With the tube non-conducting (RY2 open), the plate voltage (pin 6) should be somewhere near +135 volts. The grid voltage (pin 1) should be adjustable (with R4) from 0-30 volts positive (as measured from grid to ground with a VTVM).

- If RY2 does not remain open, increase the negative voltage on the grid of V1 (as measured to the cathode, pin 2) with control R4 until it does.

- Depress *bypass* button PB2 and RY2 will close, turning on the speaker. Turn up the volume of the receiver about three-quarters and tune in some strong signals. While these noises and signals are coming in, depress *reset* PB1 and the speaker should cut out. Now see whether the strong signals cause V1 to fire. If they do, increase the cut-off voltage with R4 as above.

- Have your partner set up the remote unit within sight and transmit a tone signal to you. Have him adjust the frequency pot (R8) in the tone unit until the resonant frequency of RY1 is found. This is indicated by the widest swing of the reed. R4 usually will not need resetting after these adjustments are made. A tone signal of about five seconds duration for firing the TCS has been found to give the most satisfactory results.

- With the remote station at a distance, have him adjust the tone input level potentiometer R13 so that the transmitted signal does not overmodulate the transmitter.

Be sure to leave the volume of the receiver turned up reasonably high during standby, since the audio amplifier of the receiver supplies the signal to the reed relay. Those of you who question the legality of the system are referred to 19.32 of "Rules and Regulations." 

news from hallicrafters

littlefone

CB-3 TRANSCEIVER

Only Hallicrafters offers 8-channel convenience and all these quality performance features.

The transmitter . . . output circuit matches 50 ohm antenna systems. Standardized CR23/U crystals (3rd overtone, series resonant) readily available. Output amplifier adjustable for max. legal input. 100% modulation on positive peaks. Series-tuned 2nd harmonic trap for excellent TV suppression.

The receiver . . . sensitivity less than 1.0 UV for 10 db. signal-to-noise ratio. Electronic squelch works on less than 6 db. signal strength change. 6 kc. selectivity. Image rej. 40 db. min. Audio output over 2 watts. Auto. noise limiter, series and shunt diodes.

\$14950



citizens band

Before you choose from the countless brands of CB equipment available, consider this fact: Nowhere in the field of communications is a manufacturer's experience, integrity and record of achievement more critical to performance and reliability than in citizen's band. Hallicrafters has produced about 1,000,000 communications units in the past 27 years.

the new ideas in communications are born at . . .

h hallicrafters

CHICAGO 24, ILLINOIS

Export Sales: International Div., Raytheon Mfg. Co., Waltham, Mass.

Canada: Gould Sales Co., Montreal, P.Q.



CITIZEN BAND CLASS "D" CRYSTALS

All 22 Frequencies in Stock

3rd overtone. .005% tolerance—to meet all FCC requirements.

Hermetically sealed HC6/U holders. 1/2" pin spacing—.050 pins. (.093 pins available, add 15¢ per crystal) **\$2.95 EACH**

The following Class "D" Citizen Band frequencies in stock (frequencies listed in megacycles): 26.965, 26.975, 26.985, 27.005, 27.015, 27.025, 27.035, 27.055, 27.065, 27.075, 27.085, 27.105, 27.115, 27.125, 27.135, 27.155, 27.165, 27.175, 27.185, 27.205, 27.215, 27.225.

Matched crystal sets for Globe, Gonsel, Citi-Fone and Hallcrafters Units . . . \$5.90 per set. Specify equipment make.

RADIO CONTROL CRYSTALS IN HC6/U HOLDERS

Specify frequency, 1/2" pin spacing . . . pin diameter .05 (.093 pin diameter, add 15¢) . . . \$2.95 ea.

FUNDAMENTAL FREQ. SEALED CRYSTALS

in HC6/U holders
From 1400 KC to 4000 KC. .005% Tolerance. . . . \$4.95 ea.
From 4000 KC to 15,000 KC any frequency .005% Tolerance \$3.50 ea.

SEALED OVERTONE CRYSTALS

Supplied in metal HC6/U holders
Pin spacing .486, diameter .050
15 to 30 MC .005 Tolerance \$3.85 ea.
30 to 45 MC .005 Tolerance \$4.10 ea.
45 to 60 MC .005 Tolerance \$4.50 ea.



QUARTZ CRYSTALS FOR EVERY SERVICE

All crystals made from Grade "A" imported quartz—ground and etched to exact frequencies. Unconditionally guaranteed! Supplied in:

FT-243 holders Pin spacing 1/2" Pin diameter .093	MC-7 holders Pin spacing 3/4" Pin diameter .125	DC-34 holders Pin spacing 3/4" Pin diameter .156	FT-171 holders Pin spacing 3/4" Banana pins
---	---	--	---

MADE TO ORDER CRYSTALS • SPECIFY HOLDER WANTED

1001 KC to 2600 KC: .01% Tolerance . . . \$2.00 ea.	2601 KC to 9000 KC: .005% Tolerance . . . \$2.75 ea.
.005% Tolerance . . . \$2.50 ea.	9001 KC to 11,000 KC: .005% Tolerance . . . \$3.00 ea.

Amateur, Novice, Technician Band Crystals

.01% Tolerance . . . \$1.50 ea.—80 meters (3701-3749 KC), 40 meters (7152-7198 KC), 15 meters (7034-7082 KC), 6 meters (8335-8650 KC) within 1 KC
FT-241 Lattice Crystals in all frequencies from 370 KC to 540 KC (all except 455 KC and 500 KC) 50¢ ea.
Pin spacing 1/2" Pin diameter .093

Matched pairs ± 15 cycles \$2.50 per pair
200 KC Crystals, \$2.00 ea.; 455 KC Crystals, \$1.50 ea.; 500 KC Crystals, \$1.50 ea.; 100 KC Frequency Standard Crystals in HC6/U holders \$4.50 ea.; Socket for FT-243 crystal 15¢ ea.; Dual socket for FT-243 crystals, 15¢ ea.; Sockets for MC-7 and FT-171 crystals 25¢ ea.; Ceramic socket for HC6/U crystals 20¢ ea.

Write for new free catalog #866 complete with oscillator circuits

ASK YOUR PARTS DEALER FOR TEXAS CRYSTALS

See big red display . . . or order from our Florida plant.

NOW! Engineering samples and small quantities for prototypes now made either at Chicago or at Ft. Myers Plant, 24 Hour Service!

IN CHICAGO, PHONE GLADSTONE 3-3555

RUSH ORDER. Use coupon for 1st Class shipment

TEXAS CRYSTALS

Dept. E-111, 1000 CRYSTAL DRIVE, FORT MYERS, FLORIDA
For extra fast service, Phone WE 6-2100

ATTACH THIS COUPON TO YOUR ORDER FOR SHIPMENT VIA 1ST CLASS MAIL AT NO EXTRA COST

TERMS: All items subject to prior sale and change of price without notice. All crystal orders must be accompanied by check, cash or M.O. with PAYMENT IN FULL. NO COD'S. E-111

CB Corner

Continued from page 47

Selective Call . . . Read the available literature on CB equipment and it conveys a distinct impression that you use it like a telephone. Not really . . . the telephone user only hears calls directed to his number, not all the large volume of traffic flowing within 20 miles of his location. But this is the case with CB.

The squelch on many CB rigs does a fine job of quieting atmospheric noise in the loudspeaker but opens the receiver to any station on the channel. These unnecessary sounds are distracting in the business office and annoying to the housewife who has the transceiver on for many hours a day anticipating a stuck-in-traffic call from her husband.

The FCC provides for tone signaling on the Class D band. Why not make a selective tone-operated squelch available as a commercial accessory to those who need it? (EI, realizing the need, has presented this project on page 82.

When installed on a transceiver, the tone squelch-call circuit is activated only when a signal bearing the correct tone is received. A possible answer to the problem of assigning different tones to a larger number of stations would be the use of two or three tones in combinations.

To avoid chaos in a neighborhood with several radio-controlled garage door openers, manufacturers have resorted to selective tone signaling. How about a system for CB radio?

Increased Cost . . . Remote operation and selective call for transceivers are just two of the features that could improve the effectiveness of CB radio. If the cry of increased cost is raised, we point to the existing demand for high-performance sets by users who lean heavily on the benefits of CB radio. Both these recommendations lend themselves to packaging as optional extras, available to those who require them.

If any CBER wants to sound off on equipment improvements, we'd like to hear from him. Address your comments to the CB Corner in care of EI.

Minivac 601


**Scientific exploration
education
experimentation**

*engineered into an electronic brain that
measures a full 24" wide*

MINIVAC 601 is a fascinating, compact computer that thinks, remembers, plays games. It speaks with authority in the fields of science, mathematics, research. It prepares teenagers and adults for the world of tomorrow.

Created by Dr. Claude Shannon of the Massachusetts Institute of Technology and developed by staff members of Scientific Development Corporation, MINIVAC 601 is built of professional components to professional standards.

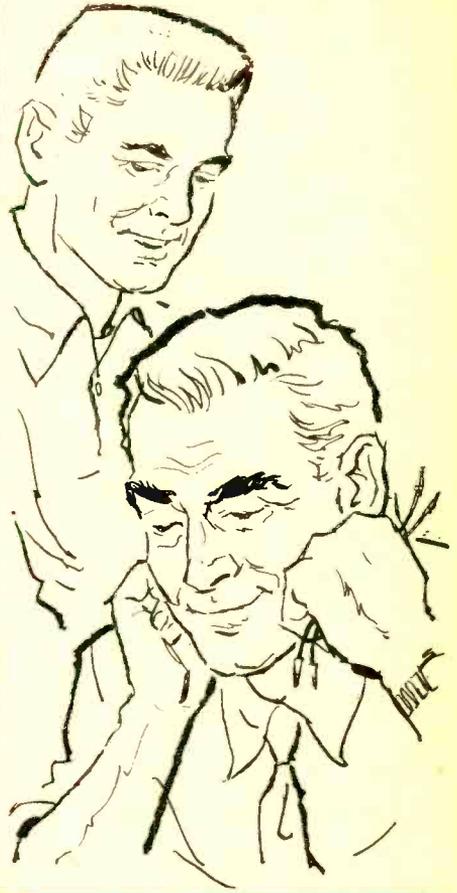It opens the way to exciting experimentation with circuits that solve problems and make decisions. It enables you to duplicate control systems like those used in advanced missiles. You may program it to demonstrate data processing techniques used in business. MINIVAC 601 will even play games with you . . . tic tac toe, and literally dozens of others.



\$85⁰⁰

Complete; computer,
programming patch cords
and set of six manuals.

"Getting Acquainted with
MINIVAC 601", "An

Introduction to Digital Computers", "How
Computers Make Logical Decisions", "How
Computers Do Arithmetic", "How Computers
Work for Man", and "MINIVAC Games".

For complete information on MINIVAC 601
what it is . . . what it does . . . how
it operates . . . write for free brochure today.




SCIENTIFIC DEVELOPMENT CORPORATION

Computer Products Division

372 Main Street Watertown 72, Massachusetts

YOU NEED THIS

FREE GIANT B-A CATALOG

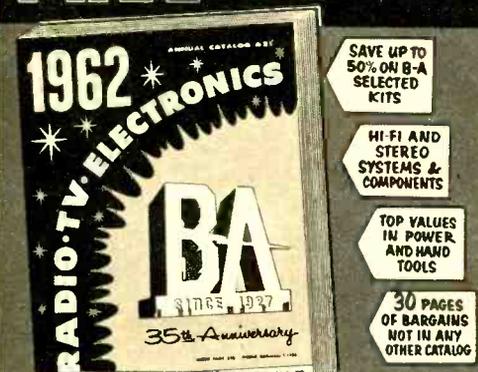

SAVE UP TO 50% ON B-A SELECTED KITS

HI-FI AND STEREO SYSTEMS & COMPONENTS

TOP VALUES IN POWER AND HAND TOOLS

30 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

BURSTEIN-APPLEBEE CO.

Dept. EI, 1012 McGee St., Kansas City 6, Mo.

Rush me New 1962 B-A Catalog No. 621

Name.....

Address.....

City.....

State.....

SEND FOR IT TODAY

EASIEST TO BUILD

LAYER BUILT COLOR GUIDE

Grommes

DE LUXE HI-FIDELITY

KITS

**101GTK
FM TUNER**



Finest tuner kit offered! "Standard Coil" tuning unit is pre-wired, pre-aligned and can be tuned-in as soon as completed, without professional adjustments. Better reception than tuners costing 2 or 3 times as much. Latest circuits, matched crystal diode detector, Foster Seeley Discriminator, AFC, Electronic Tuning Eye. Quiet, drift-free. Simply and successfully assembled by anyone with screwdriver, pliers and soldering iron. Step-by-step instructions. Model 101GTK, only.....\$66.00



20 WATT STEREO AMP.

De Luxe stereo at half the cost! Two 10 watt channels with 2 pre-amps. 40 watts peak. Fre. Res. ± 0.5 DB. 20-20,000 CPS. Complete controls. 20LJK.....\$59.50



10 WATT AMPLIFIER

With built-in pre-amp. 20 watts peak. Fre. Res. ± 1 DB. 20-20,000 CPS. 4 inputs. Output: 4, 8, 16 ohms. Automatic Loudness Control. LJ6K.....\$27.50

Many other kits available—
At dealers or sent prepaid with check or M.O.

FREE!

GROMMES Div. of Precision Electronics, Inc.
9101-T King Ave., Franklin Park, Ill.
Please rush details on Grommes Kit Line.

Name.....

Address.....

City..... State.....

The Incredible Basement of Radio

Continued from page 77

One of Professor Morgan's reasons for going so far for his experiments is that a full-wave antenna for whistler frequencies is more than 30 miles long.

The professor has a plan for stringing five cables across the horseshoe-shaped island and using the sea surrounding the horseshoe as the transmitting antenna. You also get a better quality of whistlers at the poles. The pole-to-pole magnetic field lines are longer than anywhere else and the whistler signals, in traveling so far, become spread out and the highs return relatively far ahead of the lows.

But whistlers are only part of the VLF zoo. Related to whistlers are strange signals called the dawn chorus, a sound like the twittering of birds in the morning. Then there is the hiss, which sounds like air coming from a tire; risers and other assorted clicks, tweeks, and chinks. These sounds are for the most part still unexplained. Scientists speculate that some are caused by streams of minute particles which flow from the sun and spiral down to the earth.

The "joint-venture" VLF signals are generated by such things as nuclear explosions and missile launchings. During a nuclear explosion signals result from the severe motion of atomic particles. In missile launching, the vertical column of ionized gases which follows the bird into the air is both transmitter and antenna, sending signals which are heard over great distances.

On the man-made side of the VLF picture we find what is probably the most unusual transmitting station ever built. It is a Navy installation at Cutler, Me., which went on the air early this year with the historic call letters NAA, first used in 1912 by a high-power Navy rig at Arlington, Va. But the original NAA and all the stations built since then couldn't hold a candle to the Cutler transmitter, which has a power rating in excess of 2,000,000 watts. With an antenna efficiency of more than 50 per cent, the new NAA, operating at 14.8 kc (wavelength: 20,270 meters or 12.6

miles), can transmit to ships in the Atlantic, Arctic or Mediterranean. It even has the ability to get messages to submerged submarines since VLF has a high salt-water penetration factor.

Because of the long wave-lengths, VLF antennas tend to be immense. NAA occupies a whole peninsula of 3,000 acres. Its antenna consists of two arrays shaped like six-pointed stars and mounted on 26 towers ranging in height from 800 to 980 feet. The towers themselves carry no signals. Only the cables between them are parts of the antenna. Each array covers a square mile.

Probably the most famous VLF transmitter is Navy station NLK at Jim Creek, Wash. Dubbed "Big Jim," NLK runs 1,000,000 watts and operates on 15.3 kc 24 hours a day.

A few months ago the Navy started transmitting time signals from another new VLF station, NBA, at Summit in the Canal Zone. Its frequency is 18 kc.

All the Navy's VLF stations have an N prefix on their call letters. The only other regulars on the band are two British stations with G prefixes, although new stations pop up from time to time, usually doing experimental work.

VLF noise is highest in the summer but most CW signals are so strong that it is no problem. Best time for DXing is between 4 and 7 A.M. local time.

As for equipment to monitor VLF, you may have to do some digging. Most rigs are available only on the surplus market. But it is a relatively simple task for most electronic tinkerers to work up a one-tube autodyne or TRF receiver that will pull 'em in.


If you'd rather investigate the surplus market than roll your own, some of the rigs are: U.S. Navy Models RE, RBL, and RAK; RCA's AR-8510; Wireless Specialty Co. IP500, and World War I Navy antiques SE-1420 and SE-143. If you've got a lot of loot and an uncontrollable desire to dig VLF, you can always get yourself a spanking new British Racal RA-17.

For years researchers have been trying to enlarge the usable portion of the radio spectrum at the upper end. Now many realize that through the use of "macrowaves" the spectrum may be expanded at both ends.

EMC

ALL NEW ADVANCES IN TEST EQUIPMENT!

by far the **BEST VALUES**

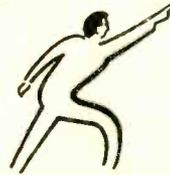


obtainable in
Wired or Kit form.

EMC MODEL 801 RC BRIDGE AND IN-CIRCUIT CAPACITY CHECKER

A new comprehensive resistance and capacity checker. It measures condensers for

actual value, leakage, and power factor. In addition it measures condensers while still connected in their original circuits for opens, shorts or intermittents.

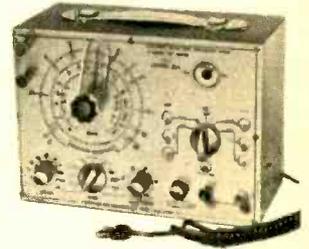MODEL 801 WIRED \$38.95
MODEL 801 KIT 24.95




EMC MODEL 802 SIGNAL TRACER AND GENERATOR

Generates its own audio, IF and RF signal for tracing. Uses both a magic eye tube and a speaker for signal detection. Checks

noisy components. Checks and compares magnetic, ceramic and crystal cartridges. Supplied with two shielded audio probes and RF crystal demodulation probe

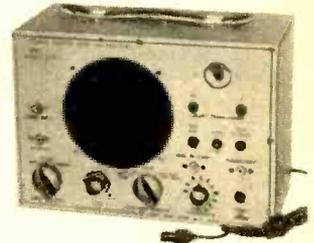MODEL 802 WIRED \$38.95
MODEL 802 KIT 24.95



Yes, tell me more, send me **FREE**—a detailed catalog of the complete EMC line. EL-11

NAME _____

ADDRESS _____

CITY _____

STATE _____

EMC Electronic Measurements Corp.
625 B'way, New York 12, N. Y.

Ex. Dept. Pan-Mar Corp., 1270 B'way., New York 1, N. Y.

Hi-Fi Record Guide

Continued from page 91

Symphony made the same success in Tin Pan Alley that it always makes in the concert hall. The Philadelphia Orchestra's performance of the symphony under the baton of Eugene Ormandy is broadly lyrical and recorded with its sound intact.

Equally compelling is the recording of Dmitri Shostakovich's First Symphony by the Symphony of the Air under Leopold Stokowski. This composition, written in 1925 when the composer was only 19, is an amazingly accurate musical portrait of the temper of modern times.

One of the masterpieces that ushered in the modern age of music was Igor Stravinsky's *Le Sacre du Printemps*, the *Rite of Spring*. This strongly-rhythmed ballet score provoked a riot at its first performance, but it has since become an enticing entry on concert programs and provided an episode in Walt Disney's *Fantasia*. Ernest Ansermet has been associated with *Le Sacre* for many years and his most recent recording of it is lucid and vigorous.

Tchaikovsky's First Piano Concerto, in B Flat Minor, and Rachmaninoff's Second, in C Minor, are among the most immediately appealing in the repertoire, and hence among the most popular. Vladimir Horowitz and Toscanini joined in a tremendously exciting performance of the Tchaikovsky for a War Bond benefit concert in 1943. This was recorded, but the sound, of course, suffers from the circumstances under which it was captured. Better sound, if not nearly as much incandescence, is offered in the recording by Van Cliburn and Kiril Kondrashin, which was made immediately upon the young American's return from his triumphant visit to Russia. Freddy Martin never had it so good!

The violin is the closest rival of the piano as a solo instrument. Mendelssohn and Tchaikovsky composed the two most popular violin concertos, and they are paired on one disc in attractive performances by Isaac Stern, backed by Eugene Ormandy conducting the Philadelphia Orchestra.



*
FREE

*
FREE

*
FREE

*
FREE

*
FREE



Fill in coupon for a FREE One Year Subscription to OLSON'S Fantastic Bargain Packed Catalog — Unheard of LOW, LOW, WHOLESALE PRICES on Brand Name Speakers, Changers, Tubes, Tools, Hi-Fi's, Stereo Amps, Tuners and other Bargains.

10 OLSON STORES
Plus
MAIL ORDER

Visit your local
Olson Stores at...

AKRON, OHIO
69 W. State Street

BUFFALO, N.Y.
711 Main Street

CHICAGO, ILL.
4101 N. Milwaukee Ave.

CHICAGO, ILL.
123 N. Western Ave.

CLEVELAND, OHIO
2020 Euclid Ave.

CLEVELAND, OHIO
6813 Pearl Road

COLUMBUS, OHIO
142 N. High Street

INGLEWOOD, CALIF.
4642 W. Century Blvd.

MILWAUKEE, WISC.
423 W. Michigan

PITTSBURGH, PENN.
5918 Penn Ave.

MAIL TO:
OLSON ELECTRONICS
425 S. Forge Street
Akron 8, Ohio



NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

From Classical to Jazz is not the long step today that it once seemed, particularly when the step is to the reflective, intense music-making of Miles Davis. His *Kind of Blue* offers a satisfying program of imaginative modern jazz conceptions. At the other end of the jazz spectrum, Phil Napoleon's *Memphis Five* treats us to lively revivals of traditional Dixieland favorites.

Vocal stylists are always appealing, though personal preferences are especially strong in this area. However, few collectors will gainsay the eminence of Ella Fitzgerald and Frank Sinatra. In *Get Happy*, she does delightful renditions of a dozen standard songs, and in *Nice 'n' Easy*, he demonstrates why he is still head of the pack.

On Broadway, Bob Merrill's *Carnival* is a big hit, and the *Original Cast* album indicates that he has come up with a potential classic. Anna Maria Alberghetti and Jerry Orbach transmit the same magic atmosphere via disc that they create in the theater. An older show, Leonard Bernstein's *On the Town*, has been reincarnated in a sparkling new production with several members of the original cast and the composer wielding the baton. Both of these albums present musical theater at its best.

Musical theater of another sort is the source of Leontyne Price's album of famous operatic arias by Giuseppe Verdi and Giacomo Puccini. The lovely voice, dramatic insight and emotional expressiveness of the young soprano are effectively displayed by the excellent record.


With Christmas not far in the offing, much seasonal music will be heard under varying circumstances. Not nearly enough of it, though, will be meaningful and worth listening to at any other time of the year. Fortunately, this is not so with the music on *The Holly and the Ivy*. These traditional and medieval carols are done with such exquisite taste that they are always a joy to hear.

So is George Frideric Handel's *Messiah* a joy—in a good performance. The late Sir Thomas Beecham's version is not one for Baroque purists, but it is an overwhelmingly rousing exposition of

the grand old music. If the four-record album seems like too much of a good thing, a single record of excerpts is available and may suffice. And if you want a less aggressive statement of the score, with emphasis on its Christmas associations, Leonard Bernstein provides just that in an attractive disc which will round out your basic record library with a *Merry Christmas* and a *Happy New Year*.

Records discussed in this column, with monaural discs listed first and stereo versions just below:

Beethoven: Fifth Symphony				
<i>Reiner, Chicago Sym. Orch.</i>	RCA Victor	LM-2343	\$4.98	
		LSC-2343	5.98	
<i>Krips, London Sym. Orch.</i>	Everest	6086	4.98	
		3086	5.98	
Beethoven: Eroica Symphony				
<i>Toscanini, NBC Sym. Orch.</i>	RCA Victor	LM-2387	4.98	
<i>Szell, Cleveland Orch.</i>	Epic	LC-3385	4.98	
		BC-1001	5.98	
Schubert: Unfinished Symphony				
<i>Toscanini, NBC Sym. Orch.</i>	RCA Victor	LM-9022	4.98	
<i>Kletzki, Royal Philharmonic</i>	Angel	35779	4.98	
		5-35779	5.98	
Mozart: Symphony No. 40				
<i>Klemperer, Philharmonia Orch.</i>	Angel	35407	4.98	
		5-35407	5.98	
<i>Ludwig, London Sym. Orch.</i>	Everest	6046	4.98	
		3046	5.98	
Brahms: First Symphony				
<i>Toscanini, NBC Sym. Orch.</i>	RCA Victor	LM-1702	4.98	
<i>Bernstein, New York Philharmonic</i>	Columbia	ML-5602	4.98	
		MS-6202	5.98	
<i>Dorati, London Sym. Orch.</i>	Mercury	50268	4.98	
		90268	5.98	
Tchaikovsky: Fifth Symphony				
<i>Ormandy, Philadelphia Orch.</i>	Columbia	ML-5435	4.98	
		MS-6109	5.98	
Shostakovich: First Symphony				
<i>Stokowski, Sym. of the Air</i>	United Artists	7004	4.98	
		8004	5.98	
Sjvrvinsky: <i>Le Sacre du Printemps</i>				
<i>Ansermet, Suisse Romande Orch.</i>	London	CM-9229	4.98	
		CS-6009	5.98	
Tchaikovsky: First Piano Concerto				
<i>Horowitz-Toscanini</i>	RCA Victor	LM-2319	4.98	
<i>Cliburn-Kondrashin</i>	RCA Victor	LM-2252	4.98	
		LSC-2252	5.98	
<i>Entremont-Bernstein</i>	Columbia	ML-5481	4.98	
		MS-6148	5.98	
Mendelssohn: Violin Concerto				
<i>Stern-Ormandy</i>	Columbia	ML-5379	4.98	
		MS-6062	5.98	
<i>Kind of Blue Miles Davis</i>	Columbia	CL-1355	3.98	
		CS-8163	4.98	
<i>Memphis Five Phil Napoleon</i>	Capitol	T-1344	3.98	
		ST-1344	4.98	
<i>Get Happy Ella Fitzgerald</i>	Yerve	V-4036	4.98	
		V-64036	5.98	
<i>Nice 'n' Easy Frank Sinatra</i>	Capitol	W-1417	4.98	
		SW-1417	5.98	
<i>Carnival Original Cast</i>	MGM	E-3946-OC	5.98	
		SE-3946-OC	6.98	
<i>On the Town Original Cast</i>	Columbia	OL-5540	5.98	
		OS-2028	5.98	
<i>Leontyne Price (Arias)</i>	RCA Victor	LM-2506	4.98	
		LSC-2506	5.98	
<i>The Holly and the Ivy Deller Consort</i>	Vanguard	VRS-499	4.98	
		LD-6409	23.92	
<i>Handel: Messiah Beecham</i>	RCA Victor	LDS-6409	27.92	
		LDS-6409	27.92	
<i>Messiah (excerpts) Beecham</i>				
	RCA Victor	LD-2447	5.98	
		LDS-2447	6.98	
<i>Messiah (Christmas Music) Bernstein</i>				
	Columbia	ML-5300	4.98	
		MS-6020	5.98	

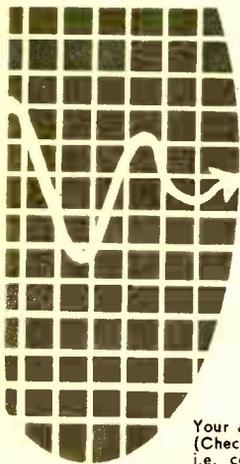

ELECTRONICS ILLUSTRATED

Classified Ads

Your advertisement can reach this mail-buying audience for only 50¢ per word . . . payable in advance (Check or M.O. please) . . . minimum 10 words. Closing dates are the 20th of 4th preceding month i.e. copy for the March issue must be in our office by December 20th. Mail to ELECTRONICS ILLUSTRATED, 67 West 44th St., New York 36, N. Y. Word count: Zone number free. Figure one word: Name of state (New Jersey), name of city (New York); sets of characters as in key (14-D); also abbreviations as 35MM, 8x10, D.C., A.C.

SAVE MONEY • ORDER BY MAIL

• • • FOR SALE

BUY GOVERNMENT Surplus: Electronics; Test Equipment; Oscilloscopes; Transceivers; Radiotelephones; Jeeps; Boats; Aircrafts; Misc.—Individuals can now buy direct from Govt.—Send for: "U. S. Dept Directory & Procedure" \$1.25. To: Brody Surplus, Box 425-EL, Nanuet, New York.

EXCELLENT BUYS on Tubes and equipment all listed in the "Green Sheet." Send .25¢ for your copy today. Cash paid for unused tubes. Write: Barry Electronics Corp., 512 Broadway, Dept. EI, NYC 12, NY.

ELECTRONIC-SCIENTIFIC KITS by Kit-Tronics. Metal Detector, SW Radio, Experimental kits. Catalog and Discount Certificate 10¢. Kit-Tronics Corporation, Dept. B-1, 15208 Stagg Str., Van Nuys, Calif.

RUBBER STAMP with your name and address Free with first order of \$500. Stock stamps at special prices, send for price list. Kays, 172 W. 34 St., Riviera Beach, Florida.

• • • EMPLOYMENT OPPORTUNITIES

PRINTING - ADVERTISING SALESMEN. Excellent moneymaking sideline selling Decalcomania Name Plates. Advertising Specialties. Sign letters, Automobile initials. Free Samples. "Ralco"—EI, Box L, Boston 19, Mass.

• • • BUSINESS OPPORTUNITIES

YENDING MACHINES—No selling. Operate a route of coin machines and earn high profits. 32-page catalog free! Parkway Machine Corp., Dept. 33, 715 Ensor St., Baltimore 2, Md.

GROW MUSHROOMS. Cellar, shed and outdoors. Spare, full time, year round. We pay \$4.50 lb. dried. We have 29,000 customers. Free Book. Mushrooms, Dept. 315, 2954 Admiral Way, Seattle, Wash.

FRANCHISE NEWS. \$5000 income. Fred-A3, 159 Albro Lake Road, Dartmouth, N. S., Canada.

• • • EDUCATION & INSTRUCTION

ENGINEERING EDUCATION for the Space Age. Northrop Institute of Technology is a privately endowed, nonprofit college of engineering offering a complete Bachelor of Science Degree Program and Two-Year accredited technical institute curricula. Students from 50 states, many foreign countries. Outstandingly successful graduates employed in aeronautics, electronics, and space technology. Write today for catalog—no obligation. Northrop Institute of Technology, 1116 West Arbor Vitae Street, Inglewood 1, California.

HIGHLY EFFECTIVE Home-Study Review For FCC Commercial Phone Exams. Free Literature. Wallace Cook, Box 10634, Jackson 9, Miss.

• • • HI-FI

RECORDERS, HI-FI! Free Wholesale Catalogue. CARSTON, 125-G East 88, NYC 28.

• • • RADIO & TV

"TV LIFE-SAVER" eliminates 3 out of 4 TV breakdowns. Saves you money. Just plug in. Pat. #2,914,637. Send only \$1.00, pay postman \$3.95 plus COD postage, or send \$4.95 for postpaid delivery. TV Life-Saver, Box 66, Hallandale, Florida.

16 TESTED TRANSISTOR Plans—25¢, including "Electronics-Science"; 12 issues \$2.50. Laboratories, 1131-K Valota, Redwood City, California.

DIAGRAMS FOR Repairing Radios \$1.00, Television \$2.00. Give make, model. Diagram Service, Box 672EI, Hartford 1, Conn.

GOOD DISCOUNT On TV Tubes. Write Mac's, 425 W. 27th St., Ashtabula, Ohio.

• • • TAPE RECORDERS

LEARN WHILE Asleep with your recorder, phonograph or amazing new "Electronic Educator" endless tape recorder. Details free. Sleep-Learning Research Association, Box 24-EI, Olympia, Washington.

NEW CONCEPT of self-hypnosis teaches you quickly, easily. New tape! New record! Free literature. McKinley-Smith Co., Dept. T-3, Box 3038, San Bernardino, Calif.

TAPE RECORDERS Hi-Fi Components. Sleep Learning Equipment, tapes. Unusual values. Free Catalog. Dressner, 1523J Jericho Tpke., New Hyde Park, N. Y.

RENT STEREO Tapes—over 1500 different—all major labels—free catalog. Stereo-Parti, 811-AY Centinela Ave., Inglewood 3, California.

• • • DETECTIVES

DETECTIVES—EXPERIENCE unnecessary. Detective Opportunities. Write, Wagner, B-125 West 86th, New York 24.

• • • MUSIC

ACCORDIONS, CHORD Organs, Guitars! Buy direct—save to 1/2. Famous makes. Free home trial. Easy terms. Trades. Free catalogs. Mention Instrument. International Music Mart, Dept. EI, 2003 Chicago Avenue, Chicago 22.

• • • PERSONAL

LOANS By Mail. \$50 to \$600 For Any Purpose. Confidential. 2 years to repay. Free loan application. Write: American Loan Plan, Dept. EI-9141, City National Bldg., Omaha 2, Nebraska.

• • • MISCELLANEOUS

ELECTRONIC KITS assembled, wired and tested by Naczas Kit Service, Dept. 1, 18 Wolfe Street, Manchester, New Hampshire. "Where Quality Excels."

BUY DIRECT FROM RAD-TEL!!

UP TO 75% OFF ON

RAD-TEL'S FIRST QUALITY

BRAND NEW TUBES

ONE FULL YEAR GUARANTEE

SERVICEMEN: Now speedy one-day service.

BUY DIRECT FROM RAD-TEL! YOU'LL SAVE PLENTY. YOUR ORDER SHIPPED WITHIN 24 HOURS AFTER RECEIVING AND PROCESSING. RAD-TEL SELLS ONLY BRAND NEW TUBES, NOT USED.

THE SIGN OF RAD-TEL'S RELIABILITY



GUARANTEED RAD-TEL TRANSISTORS SET TESTED

All Transistors Germanium PNP



AF ST* AF Driver. Use as: Driver Low Power Output, Code Osc., DC Amp., Control, Test Instr., Pre-Amp., Timers, Organ, etc. **39c ea.**



RF ST* as Converter in an American set. Use as: Converter Sq. Wave Gen., RF Osc., Amp. Regen. Det., etc. **49c ea.**



IF ST* as 455kc IF in an Amer. set. Use as: IF Amp., Grid Dip Osc., Electronic Computer, RF Osc., Switch, Amp., etc. **49c ea.**



AUTO OUTPUT ST** as Audio Power Output into Speaker, 90% of Auto Radios so Powered. Use as Power Amp., Mobile Power Supply, Voltage Regulator, Osc., DC to DC Converters. **79c ea.**



HI POWER ST** as Hi Power AF Output. Ideal as DC to DC Converter, Multivibrator replaces Vibrator supply. **\$1.39 ea.**

HI CURRENT SILICON RECTIFIERS
15 AMPS
20 ma max
Reverse I at PIV

PIV	Price		Lots of	
	Each	10	50	100
50	2.25	2.00	1.75	1.50
100	2.50	2.25	1.90	1.60
200	2.75	2.50	2.25	1.90
300	3.25	2.95	2.70	2.30
400	3.95	3.50	3.00	2.60

500 MA SILICON RECTIFIER Epoxy construction, size of 1-watt resistor
1 reverse at 450 Volts .3 ma
30c lots of 20 ea. | 35c lots of 10 ea. | 45c ea.
Each rectifier "Performance Tested" on an American TV Set

EACH TUBE INDIVIDUALLY & ATTRACTIVELY BOXED

Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price
	0Z4M	.79		6BA6	.50		12AE6	.43
	1AX2	.62		6BC5	.61		12AF3	.73
	1B3GT	.79		6BC7	.94		12AF6	.49
	1G3	.79		6BC8	.97		12AJ6	.46
	1J3	.79		6B06	.51		12AL5	.45
	1K3	.79		6BE6	.55		12AL8	.95
	1R5	.62		6BF6	.44		12AQ5	.52
	1S5	.51		6BG6	1.66		12AT6	.43
	1T4	.58		6BH6	.65		12AT7	.76
	1U4	.57		6BH8	.87		12AU6	.50
	1U5	.50		6BJ6	.62		12AU7	.61
	1X2	.82		6BK7	.85		12AV5	.97
	2AF4	.96		6BL7	1.00		12AV6	.41
	2CY5	.70		6BN4	.57		12AV7	.75
	2EA5	.71		6BN6	.74		12AX4	.67
	3AL5	.42		6BQ5	.65		12AX7	.63
	3AU6	.51		6RO6GT	1.05		12AZ7	.86
	3AV6	.41		6BQ7	1.00		12B4	.63
	3BA6	.51		6BR8	.78		12BA6	.50
	3BC5	.54		6BU8	.70		12B06	.50
	3BE6	.52		6BY6	.54		12BE6	.53
	3BN6	.76		6BZ6	.55		12BF6	.44
	3BU8	.78		6BZ7	1.01		12BH7	.77
	3BY6	.55		6C4	.43		12BL6	.56
	3BZ6	.55		6CB6	.55		12BQ6	1.06
	3CB6	.54		6C06	1.42		12BY7	.77
	3CF6	.60		6CF6	.64		12BZ7	.75
	3CS6	.52		6CG7	.61		12C5	.56
	3DG4	.85		6CG8	.77		12CN5	.56
	3DK6	.60		6CM7	.66		12CR6	.54
	3DT6	.50		6CN7	.65		12CU5	.58
	3S4	.61		6CR6	.51		12CV6	1.06
	3V4	.58		6CS6	.57		12D8	.75
	4BC8	.96		6CUs	.58		12DL8	.85
	4BQ7	1.01		6CUG	1.08		12D06	1.04
	4BS8	.98		6CUs	.71		12D57	.79
	4BZ6	.58		6CY7	.71		12DW8	.89
	4BZ7	.96		6DA4	.68		12DZ6	.56
	4C86	.56		6DB5	.69		12E05	.62
	4CS6	.61		6DE6	.58		12EL6	.50
	4CY5	.71		6DGG	.59		12EG6	.54
	4DE6	.62		6DQ6	1.10		12E26	.53
	4DT6	.55		6DT5	.76		12F8	.66
	5AM8	.79		6DT6	.53		12FM6	.45
	5AN8	.86		6DT8	.94		12K5	.65
	5AQ5	.52		6EAB	.79		12SK7GT	.74
	5AT8	.80		6EM7	.91		12SN7	.67
	5BK7A	.82		6EUB	.79		12S07M	.78
	5BQ7	.97		6GH8	.79		12U7	.62
	5BR8	.79		6GGT	.58		12V5GT	.53
	5CG8	.76					12W6	.69
	5CL8	.76		6J5GT	.51		12X4	.38
	5EA8	.80		6J6	.67		17AX4	.67
	5EU8	.80		6K6	.63		17B06	1.09
	5J6	.68		6S4	.51		17C5	.58
	5T8	.81		6SA7GT	.76		17CA5	.62
	5U4	.60		6SK7	.74		17D4	.69
	5U8	.81		6SL7	.80		17DQ6	1.06
	5V6	.56		6SN7	.65		17L6	.58
	5X8	.78		6SQ7	.73		17W6	.70
	5Y3	.46		6T4	.99		19AU4	.83
	6AB4	.46		6U8	.83		19B6	1.39
	6AC7	.96		6V6GT	.54		19T8	.80
	6AF3	.73		6W4	.60		21EX6	1.49
	6AF4	.97		6W6	.71		25BQ6	1.11
	6AG5	.68		6X4	.39		25C5	.53
	6AH6	.99		6X5GT	.53		25CA5	.59
	6AK5	.95		6X8	.80		25C06	1.44
	6AL5	.47		7AU7	.61		25CUG	1.11
	6AM8	.78		7A8	.68		25DNG	1.42
	6AQ5	.53		7B6	.69		25EH5	.55
	6AR5	.55		7Y4	.69		25L6	.57
	6AS5	.60		8AU8	.83		25W4	.68
	6AT6	.43		8AW8	.93		25Z6	.66
	6AT8	.79		8BQ5	.60		35C5	.51
	6AU4	.82		8CG7	.62		35L6	.57
	6AU6	.52		8CX8	.93		35W4	.42
	6AU7	.61		8EB8	.94		35Z5GT	.60
	6AU8	.87		11CY7	.75		50B5	.60
	6AV6	.41		12A4	.60		50C5	.53
	6AW8	.90		12AB5	.55		50DC4	.37
	6AX4	.66		12AC6	.49		50EH5	.55
	6AX7	.64		12AD6	.57		50L6	.61
							117Z3	.61

*SET TESTED IN AMER. TRANSISTOR RADIO OF CURRENT MFR.
**SET TESTED IN AMER. AUTO RADIO OF CURRENT MFR. AT 16 VOLT BATTERY SUPPLY.
Rad-Tel eliminates complicated characteristics and numbers with their "SET-TESTED" Transistors. Transistors Tested to Rad-Tel's specifications—available on request. 100% Satisfaction Guaranteed. Substitute or replace with Rad-Tel Transistors on the basis of similar operating characteristics . . . at Low, Low Prices.

● NOT AFFILIATED WITH ANY OTHER MAIL ORDER TUBE COMPANY ●



SEND FOR FREE TROUBLE SHOOTER GUIDE AND NEW TUBE & PARTS CATALOG

RAD-TEL TUBE CO.


DEPT. EI-1161 55 CHAMBERS STREET, NEWARK 5, N. J.

TERMS: 25% deposit must accompany all orders, balance COD. Orders under \$5: add \$1 handling charge plus postage. Orders over \$5: plus postage. Approx. 8 tubes per 1 lb. Subject to prior sale. Prices subject to change. No COD's outside continental USA.

AMERICAN BASIC SCIENCE CLUB

Sensational LOW COST SCIENCE LAB

NOW over 110 fascinating projects with

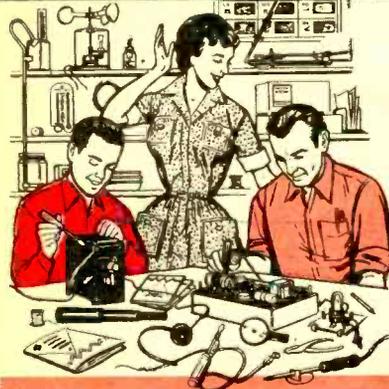

COMPLETE LABORATORY COMES IN 8 KITS, ONE A MONTH... SUPPLIES ALL THE EQUIPMENT FOR ALL THE FOLLOWING:

ELECTRICAL EXPERIMENTS

Educational fun with Electro-Magnets, Transformer, Galvanometer, Rheostat, Relay, Voltmeter, Wheatstone Bridge, and other electric equipment.

RADIO RECEIVER

Three Tube Short Wave (80 Meter) and Standard Broadcast Receiver. Sensitive Regenerative Circuit uses regular 115 volt AC. Complete with Head Set.

DC POWER SUPPLY

Power Transformer, Vacuum Tube Rectifier and 20-20 mfd. Capacitor Filter Circuit. Converts home AC to the DC required for Electronic Circuits.

PHOTOELECTRIC EYE

Photoelectric Cell, Exciter Lamp — and Electronic Relay. Everything you need to control motors, bells, alarms, and do other light beam experiments.

MICROPHONE

A sensitive carbon-button microphone that greatly amplifies unexpected noise. Also adaptable for use with your radio transmitter.

ELECTRONIC EXPERIMENTS

Explore functions of vacuum tubes and other electronic components. Build an Electronic Switch—Amplifier, and other experimental circuits.

CODE PRACTICE SET

Signal Oscillator, Key and Flasher... the complete outfit to learn to receive and transmit the Morse Code... the first step to a Ham License.

STROBE LIGHT

A variable pulse neon lamp. "Freezes" motion of rapidly vibrating or rotating objects for close study and checking frequencies. RPM.

BROADCAST TRANSMITTER

Sends clear transmissions of both code and voice to nearby radios. Can be used with your microphone, record player, or code oscillator.

RADIO SERVICE EQUIPMENT

All the parts to build your own Radio Signal Tracer and a Probe Light Continuity Tester. Both pieces are invaluable in radio servicing.

SOUND EXPERIMENTS

Laboratory demonstration of sound waves, resonance and pitch. Includes Variable Frequency Oscillator, Sonometer and Bippie Tank.

TELESCOPE

A mounted astronomical Telescope. High quality ground lenses enable you to examine details of the moon's surface and distant objects.

PHOTOGRAPHY LAB

Complete dark room equipment: Printer—Enlarger—Electronic Timer—Safe Light—Developing Trays and supply of paper and chemicals.

SLIDE PROJECTOR

Takes 12mm and 35mm slides, sharp focusing, convection cooled. G.E. Projection Lamp included. Also adaptable as a Projection Microscope.

MICROSCOPE

High and low power, precision ground lenses; Substage Light and Polarizer. Adaptable for photomicrography in connection with Photo Lab.

SPECTROSCOPE

Fascinating optical instrument used to identify and analyze substances by observing the spectrum of their flame. Spectrum charts are included.

ATOMIC RADIATION EXPM.

A variety of projects using Spinthariscopes and sensitive Electroscopes. Sample sources of radioactive Uranium Ore and Radium are included.

ATOMIC CLOUD CHAMBER

See illuminated tracks of speeding nuclear particles emanating from radioactive Alpha source and mysterious cosmic rays from outer space.

ULTRAVIOLET LAMP

Produces dazzling color effects with invisible "black light". Used extensively for crime detection, mineralogy and science. Fluorescent Ink, Crayon and Tracer Powder are included.

HEAT EXPERIMENTS

Study the Molecular Theory of heat using 2 Thermometers, Thermostat, 3 foot Gas Thermometer and special Microscope arrangement that shows the effect of Molecular Movement.

WEATHER STATION

Aneroid Barometer, Cup Anemometer that electronically measures wind speed. Sling Psychrometer, Humidity Gauge, Cloud Speed Indicator, Cloud Chart and Weather Map.

A REAL SCIENCE COURSE

Developed with World Famous
SOUTHWEST RESEARCH INSTITUTE

The 8 manuals are expertly written, clearly illustrated, excitingly different.

NO EXPERIENCE NECESSARY

You can complete every project and GAIN A VALUABLE SCIENCE BACKGROUND that will ENRICH YOUR LIFE and could SHAPE YOUR FUTURE!



Analyzing Gaseous Gases with the SPECTROSCOPE

PHOTOMICROGRAPH of a Fly's Wing made with Microscope and Photo Lab (Actual Size 5" diameter)

Trouble Shooting with the SIGNAL TRACER

ALL THE EQUIPMENT FOR ALL THE ABOVE—only \$29⁶⁰

SEND \$200 WITH ONLY COUPON PAY \$345 FOR EACH KIT YOU RECEIVE (ONE A MONTH FOR 8 MONTHS) ONLY

FREE SOLDERING IRON with second Kit

Your Satisfaction or Your Money Back... AND you may cancel at any time without obligation.

These "no risk" assurances because we know you will be...

SURPRISED! AMAZED! DELIGHTED!

A VALUABLE SCIENCE LAB
Containing Parts by
RCA, MALLORY, PYRAMID,
STACKPOLE, TRIM and
other reliable manufacturers.
Retail Value of Parts Alone is
over FIFTY DOLLARS

FOR SAFETY!

Circuits are low voltage supplied by isolation transformer that comes with this kit.



FREE! These 6 Auxiliary Textbooks

AMERICAN BASIC SCIENCE CLUB

501 E. Crockett, San Antonio 6, Texas

Start sending me A.B.S.C.'s "Science Lab" in eight kits, one each month. If not satisfied on inspection of first kit I may return it for immediate refund. (I choose the plan checked.)
 I enclose \$2.00 and will pay \$3.45 plus COD postage on arrival of each kit. I may cancel unshipped kits at any time.
 I enclose \$29.60, full payment, Postage Paid, for all 8 kits. I may cancel any time and get full refund on unshipped kits.

MEMBERS ARE ENTHUSIASTIC!

I wish I could provide each of my Physics students with all of your enjoyable kits. You are doing a wonderful job.

Your course is very enjoyable and educational for all ages. I would not sell mine for twice the price.

Francis Pitcher
13 Friendship Dr.
Tivoli, New York

Allen T. Ayers, Physics Dept.
Jamestown High School
Jamestown, New York

AMERICAN BASIC SCIENCE CLUB, Inc. San Antonio, Texas

NAME _____
STREET _____
CITY _____ STATE _____
MAIL COUPON TODAY

RCA training at home can be the smartest investment you ever made

Look what you get in the Course in Radio and Electronic Fundamentals

40 Fascinating THEORY LESSONS



Containing all the basic principles of radio and electronics in easy-to-understand form.

40 EXPERIMENT LESSONS



Each containing absorbing, practical experiments bound together in 20 books.

40 SERVICE PRACTICES



Full of practical, time-saving and money-saving servicing tips, bound into 20 books.

PLUS ALL THIS AT NO EXTRA COST...

15 KITS

to build a Multimeter, AM Receiver and Signal Generator. Kits contain new parts for experiments, integrated so as to demonstrate what you learn in the lessons and to help you develop technical skills. Each kit is fun to put together!

MULTIMETER




A sensitive precision measuring instrument you *build* and *use* on the job. Big 4 1/2" meter with 50 micro-amp meter movement. 20,000 ohms-per-volt sensitivity d-c, 6,667 a-c.

AM RECEIVER



Have the satisfaction of building your own radio receiver with this high-quality 6-tube superheterodyne set. Big 5" speaker, fine tone!

SIGNAL GENERATOR

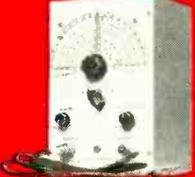

A "must" for aligning and trouble-shooting receivers. Build it for your own use. 170 KC to 50 MC fundamental frequencies for all radio and TV work.

Practical work with the very first lesson! Pay-only-as-you-learn! No long-term contracts to sign! No monthly installment payments. Pay only for one study group at a time if and when you order it!

Stake out your future in electronics now!



SEND FOR OUR FREE HOME STUDY CATALOG TODAY!

Just fill out this card and drop it in the mail—no postage needed.

RCA INSTITUTES, INC.

A Service of Radio Corporation of America • 350 W. 4th St., New York 14, N. Y. • 610 S. Main St., Los Angeles 14, Calif.



The Most Trusted Name in Electronics

RCA INSTITUTES INC. Home Study School, Dept. EI-N1

A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N.Y.

Without obligation, rush me the FREE 64-page illustrated book describing your electronic training program (check one). No salesman will call.

Home Study Los Angeles Resident School New York Resident School

Name (Please Print)

Address

City Zone State

Veterans: Enter discharge date.....

CANADIANS—Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Enclose this card in envelope and mail to: RCA Victor Company, Ltd., 5581 Royalmount Ave., Montreal 9, Quebec.



RCA TRAINING CAN BE THE SMARTEST INVESTMENT YOU EVER MAKE

With RCA Institutes Home Study training you set your own pace in keeping with your own ability, finances and time. You get prime quality equipment as a regular part of the course . . . and you never have to take apart one piece to build another. Perhaps most important, RCA's liberal Pay-As-You-Learn Plan is the most economical home study method *because you pay only for lessons as you order them* . . . one study group at a time! If you drop out at *any* time, for *any* reason, you do not owe RCA one penny! No other obligations! No installment payments required! Licensed by New York State Education Department.

Choose **YOUR FUTURE** from this list of courses:

- Radio and Electronic Fundamentals (see reverse side)
- Television Servicing
- Color Television
- Electronics for Automation
- Transistors

START YOUR CAREER IN ELECTRONICS NOW AT RCA INSTITUTES in Los Angeles-New York City

CHOOSE FROM THIS LIST . . .

	Course	Qualifications	Length of Course
A	Advanced Electronic Technology (T-3)	High School grad, with Algebra, Physics or Science	Day 2¼ yrs. Eve. 6¾ yrs. (N.Y.) 4½ yrs. (L.A.)
B	Television and General Electronics (V-7)	2 yrs. High School, with Algebra, Physics or Science	Day 1½ yrs. Eve. 4½ yrs. (N.Y.) 3 yrs. (L.A.)
C	Radio and Television Servicing (V-3)	2 yrs. High School, with Algebra, Physics or Science	Day 9 mos. Eve. 2¼ yrs. (N.Y.) 1½ yrs. (L.A.)
D	Transistors	Radio background	Eve. 3 mos.
E	Electronic Drafting (V-11 V-12)	2 yrs. High School, with Algebra, Physics or Science	Eve. Basic: 1 yr. Advanced: 2 yrs.
F	Color Television	Television background	Eve. 3 mos.
G	Radio Telegraph Operating (V-5)	2 yrs. High School, with Algebra, Physics or Science	Day 9 mos. Eve. 2¼ yrs. (N.Y.) 1½ yrs. (L.A.)
H	Computer Programming (C-1)	College Graduate or Industry sponsored.	Eve. 24 weeks Sat. 30 weeks
I	Technical Writing (V-10)	High School Graduate	Eve. 2¼ yrs. (N.Y.) 1½ yrs. (L.A.)
J	Automation Electronics (V-14)	Background in Radio Receivers and Transistors	Eve. 9 mos. (N.Y.) Sat. 44 weeks (N.Y.)
K	Digital Computers	Electronics background	Eve. 3 mos. (L.A.)
L	Preparatory Math & Physics (P-0)	1 yr. High School	Day 3 mos.
M	Preparatory Mathematics (P-0A)	1 yr. High School	Eve. 3 mos.

BUSINESS REPLY MAIL

No Postage Stamp Necessary if mailed in U. S.

Postage will be paid by —

RCA INSTITUTES, INC., Dept. EI-N1
350 West Fourth Street
New York 14, N. Y.

FIRST CLASS
PERMIT NO.
10662
NEW YORK, N. Y.

RCA Institutes is one of the largest technical institutes in the United States devoted exclusively to electronics. Co-educational Day and Evening classes. Free Placement Service. Applications now being accepted.

SEND FOR THIS
FREE ILLUSTRATED
BOOK TODAY

Fill in the other side of the postage-free card and check Resident School.



RCA INSTITUTES, INC.

A Service of Radio Corporation of America • 350 W. 4th St., New York 14, N. Y. • 610 S. Main St., Los Angeles 14, Calif.



The Most Trusted
Name in Electronics