

ELECTRONICS ILLUSTRATED®

By the Publishers of MECHANIX ILLUSTRATED

Special Issue: **CITIZENS BAND RADIO**

Complete CB Coverage! **60** Pages of CB Features! **12** CB Projects!

Projects: How to Get Rid of CB TVI • A Novel Modulation Meter
16db Speech Compressor • Perk Up Your Mobile Rig
A "Voice Power" Amplifier • Mapping Your Signal Pattern
CB Signal Booster • Transmission Line Tune-Up Meter
Add a Handset to Your Transceiver • Switch to a Better Mike

- Read the Hilarious "Confidential History of CB"
- What the FCC Thinks of CB • A Survey of CB Kits
- Basic CB Circuit Theory • All About Modulation
- The Truth About CB Skip • The Top Ten CB Clubs



BUILD THIS SPECIAL CITIZENS BAND OSCILLOSCOPE
for precise analysis of your signal

Prepare Now For The Higher Rewards The Electronics Age Offers You

There is an immediate and growing need for trained technicians in Industrial-Military Electronics, Radio-TV Servicing and Communications. Better than average jobs with high pay, interesting work, bright futures await you in the fast growing industry of the 1960's. Join thousands of NRI graduates now benefiting from career opportunities in this Electronic Age.

Training Equipment Included



NRI "learn-by-practice" training is the time-proved way to higher earnings and advancement. Except for FCC License

course, all NRI courses include—at extra cost—special training equipment to give shop and laboratory experience in your own home. Makes NRI training come to life in an easy-to-grasp, interesting manner. Take the advice of job counselors, invest in Electronics if you are dissatisfied with your present job or pay, or you want to prepare for military service.



Oldest and Largest School

For nearly 50 years NRI has featured electronics training at reasonable cost because it is the oldest, largest home-study school of its kind. Take the first step to a new career now. Mail postage-free card. National Radio Institute, Washington 16, D. C.



Industrial ELECTRONICS

The NRI course in Electronics—Principles, Practices, Maintenance prepares you for a career as an Electronic Technician in industry, business, government, the military. Computers, telemetry, automation, missiles, rockets all employ the same basic Electronic principles . . . and that is what this NRI course stresses with illustrated lessons, special training equipment.



Commercial FCC LICENSE

You must have an FCC License if you want to operate or service transmitting equipment used in TV and Radio Broadcasting, aviation, marine, microwave, facsimile or mobile communications. Even a service Technician needs an FCC License today to work on C-Band Radio equipment. From Simple Circuits to Broadcast Operation, this new NRI course trains you quickly to take Government exams.




TV-Radio COMMUNICATIONS

In NRI's Communications course you get actual experience as NRI trains you for your choice of Communications fields. Commercial methods and techniques of Radio-TV Broadcasting; teletype; facsimile; microwave; radar; mobile and marine radio; navigation devices; multiplexing are some of the subjects covered. You work with special training equipment.



Radio and TV SERVICING

NRI's time-tested course in Servicing not only trains you to fix radios, TV sets, hi-fi, etc., but also shows you how to earn spare-time money starting soon after enrolling. Fast growth in number of sets means money-making opportunities for you in your own spare-time or full-time business, or working for someone else. Special training equipment at no extra cost. Mail postcard.

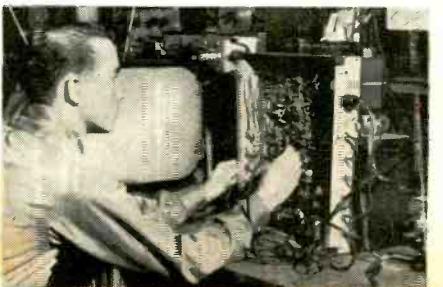



COURIER 1-M

NOW!

QUIETEST

MOST POWERFUL

MOBILE

C.B. UNIT!

HEAR IT TO BELIEVE IT!

Write for Free Brochure \$209.50 list, slightly higher west of Rockies.



electronics communications, inc. 325 no. macquesten pkwy, mt. vernon, n. y.

March, 1963

ELECTRONICS ILLUSTRATED

March 1963

A Fawcett Publication

Vol. 6, No. 2

ROBERT G. BEASON
Editor
Larry Klein, WB2CFJ
Technical Editor
Lou Rubsamen
Art Editor
Linda R. Grossman
Editorial Assistant

Special CB Features

CB Marketplace	8
What the FCC Thinks of CB	29
Basic CB Circuit Theory	40
The Truth About CB Skip	49
CB Corner: More Part 19 Revisions	52
Top 10 CB Clubs	56
Free Movies for CB Club Meetings	64
11 Meters in Canada	75
CB Antennas: Little Things Mean a Lot	78
A Confidential History of CB	81
All About Modulation	84
A Survey of CB Kits	92
How They Make Modular CB Rigs	104

Special CB Projects

CB Signal Booster	Kevin Redmond, K2HTZ	32
How to Get Rid of CB TVI	Bert Mann	37
Switch to a Better Mike	Chet Stephens	39
16db Speech Compressor	Herb Friedman	45
Build a CitizenScope	Herb Friedman	58
A Novel Modulation Meter	Herb Cenani	66
How to Map Your Signal Pattern	Charles O'Neil	68
Add a Handset to Your Transceiver	Gerald Wainwright	74
Transmission Line Tune-Up Meter	Al Toler	76
Direct-Reading Power Output Meter	Herb Cenani	80
Perk Up Your Mobile Rig	Bert Mann	89
Add a "Voice Power" Amplifier	Russ Cogan	101

Radio: CB • Amateur • SWL

The Listener	C. M. Stanbury II	96
Prize Shacks		100
Ham Shack	Robert Hertzberg, W2DJJ	111

Audio & Hi-Fi

Hi-Fi Record Guide	Warren DeMotte	106
--------------------------	----------------	-----

Regular Departments

Feedback from Our Readers		4
Electronics in the News		12
Good Reading	John Milder	88
Beginner's Page: How to Drop a Voltage	H. B. Morris	110

CONTRIBUTING EDITORS

Robert Hertzberg, W2DJJ
Amateur Radio
Len Buckwalter, KBA4480
Citizens Band
C. M. Stanbury II
SWL-OX
Herb Friedman, W2ZLF/2W6045
Special Projects

Richard A. Markoff, M.D.
Medical Electronics
Harry Kolbe
John Milder
David Muirhead
Audio

ADVERTISING

John F. Webster
Advertising Manager

EXECUTIVE STAFF

Ralph Daigh
Editorial Director
James Boynton
Advertising Director
Al Allard
Art Director
Ralph Mattison
Associate Art Director
George H. Carl
Production Director
Larry Eisinger
Editor-in-Chief
Beata Rockwood
Production Editor

ADDRESSES

Editorial and Advertising Offices:
67 West 44th St., New York 36,
N.Y. Subscriptions: Change of
address Form 3579 to Subscription
Dept., Fawcett Bldg., Green-
wich, Conn.

ELECTRONICS ILLUSTRATED is
published bi-monthly by Fawcett
Publications, Inc., Fawcett Place,
Greenwich, Conn. W. H. Fawcett,
Jr., President; Gordon Fawcett,
Secretary and Treasurer; Royer
Fawcett, General Manager; Roscoe
K. Fawcett, Circulation Director;
Donald P. Hanson, Assistant Gen-
eral Manager.

Second-class postage paid at
Greenwich, Conn., and at addi-
tional mailing offices.

Subscription price \$4 for 12
issues in U.S. and possessions and
Canada. All other countries \$6 for
12 issues. Foreign subscriptions
and sales should be remitted by
International Money Order in U.S.
funds payable at Greenwich, Conn.

Printed in U.S.A. Copyright 1963
by Fawcett Publications, Inc.
Permission hereby granted to
quote from this issue of this
magazine on radio or television
provided a total of not more than
1,000 words is quoted and credit
is given to the title of the maga-
zine and issue, as well as the
statement, Copyright 1963 by
Fawcett Publications, Inc.

MEMBERSHIPS

Audit Bureau of Circulations



Magazine Publishers Association, Inc.



COVER—Photograph by
Herb Friedman. Executive
Model 100 Citizens Band
transceiver by International
Crystal Manufacturing Co.,
Inc.



**Has shop in basement — gets
“more and more work all along”**

I HAD PRACTICALLY no knowledge of any kind of repair work. One day I saw the ad of NRI in a magazine and thought it would be a good way to make money in my spare time. Now I am busy almost all my spare time and my day off—and have more and more repair work coming in all along. I have my shop in the basement of my home.”

—JOHN D. PETTIS,
172 N. Fulton, Bradley, Illinois

IF YOU’VE BEEN WANTING TO START “A LITTLE BUSINESS OF YOUR OWN” IN YOUR BASEMENT OR GARAGE

CHECK the advantages of NRI training in Servicing Electrical Appliances

- STEADY DEMAND** for your services. Over 400 million appliances in U.S. — 6 million sold last year alone — mean shortage of trained appliance service men.
- NO ELABORATE EQUIPMENT NEEDED** — just simple hand tools, and Appliance Tester which we provide at no extra charge.
- START SMALL — GROW BIG.** You can start out in your own basement or garage, in spare time. Gradually expand until you open your own shop.
- NO NEED TO RISK YOUR SAVINGS.** Many businesses require a sizable investment. But here you can build up a following of customers *first*, then open a full-time shop if you wish to.
- EARN \$3 TO \$5 PER HOUR.** Fixing appliances is a high-paying skill because the demand for trained men is so great.
- ENJOY SEMI-RETIREMENT ON A GOOD INCOME.** When you’re ready to retire, you can devote a few hours a day to this work. Live and work anywhere you please.
- NO PREVIOUS EXPERIENCE OR TRAINING NEEDED.** We tell you and show you everything you need to know, in plain English and clear pictures.

IF YOU’RE like so many men today, you’ve been “hankering” to start “a little home business of your own.” In spare time at first, then maybe full-time later on. Something you’d enjoy — and that pays well. Something that fills an existing need in your neighborhood or town — that “sells itself,” without any high pressure arguments — that doesn’t take a big investment or elaborate equipment.

This is it—Servicing Electrical Appliances! Now is the perfect time to get into it. Sales of electrical appliances have skyrocketed. Look how **YEARLY SALES** have risen since 1950: Coffee Makers — from 900,000 to 4,750,000. Room Air Conditioners—from 200,000 to 1,800,000. Clothes Dryers—from 318,000 to 1,425,000. Floor Polishers — from 240,000 to 1,090,000. No wonder that men who know how to service appliances properly are making \$3 to \$5 an hour—in spare time or full time!

**Your Skill Always in Demand
— “Set Up Shop” Anywhere**

People need their appliances fixed in good times or bad. Once word gets around that you are trained to service them, you’ll have plenty of work.

Your training costs less than 20¢ a day. And you need only the few basic tools you may already have — and an Appliance

Tester which we provide at no extra charge. You can work anywhere—in a corner of your basement or garage, even on the kitchen table. If you like, you can open up your own shop, have others work for you. And you can save money by fixing your own appliances.

FREE BOOK and Sample Lesson

Our 24-page Free Book tells how you can “cash in” on America’s “Electrical Appliance Boom”—the money our students are making, what they say about us.

Free Sample Lesson shows how simple and clearly illustrated our instruction is—how it can quickly prepare you for a profitable future in this big field. Mail coupon, letter, or postcard to: *National Radio Institute, Dept. KC3, Washington 16, D.C.* (No obligation — and no salesman will call on you.)



EARN WHILE YOU LEARN

with this

APPLIANCE TESTER

—Yours at No Extra Charge



Your NRI Course comes *complete* with all the parts to assemble a sturdy, portable Appliance Tester that helps you earn while you learn. Easy-to-follow manual tells how to assemble and use the Tester *right away*. Locate faulty cords, short circuits, poor connections, etc. in a jiffy; find defects in house wiring; measure electricity used by appliances; many other uses.

With this Tester you save time and make money by doing jobs quicker, making sure appliances operate correctly after repairs.

NATIONAL RADIO INSTITUTE
Dept. KC3, Washington 16, D.C.

Please send me Free Book about your Electrical Appliance Repair Course and a free Sample Lesson. I am particularly interested in:

Spare Time Earnings Business of My Own Better Job

I understand there is no obligation on my part; and no salesman will call.

Name

Address

City Zone State

Accredited Member National Home Study Council

FEEDBACK


from our readers



Write to: Letters Editor, Electronics Illustrated.

67 West 44th St., New York 36, N. Y.

● Last Word?

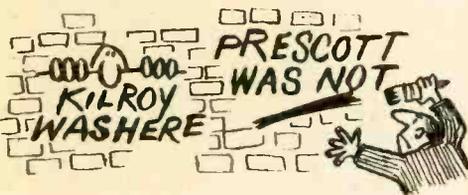

I mailed a letter to Sid Prescott at the Ultra Electronics & Paper Clip Co. in Houston and it was sent back. He was the man who was manufacturing the $2N\frac{1}{2}$ transistor, a sub-miniature resistor and paper clips. You published two of his letters in FEEDBACK. Could you give me a better address?

G.B.
Phoenix, Ariz.

We're not quite sure who is pulling whose leg, G.B. We assumed Sid Prescott was the pen name of somebody who was kidding us and our readers. We suspect you're calling his bluff. If you're serious, forget about old Sid. His paper clips don't work worth a darn.

● Flash!

I am interested in building your MINIATURE SLAVE FLASH (Nov. '62 EI) but I find the CK914 transistor you specify is no longer stocked here. Can you give me a substitute?

Robert J. Binnie
Pittsburgh, Pa.

Any small-signal PNP audio transistor, such as the 2N34, 2N107, CK722, etc., may be substituted for the CK914.

● Mike Mix-Up

Thanks for the thorough-going article on microphones (MICROPHONES!, Jan. '63 EI). It should help clear the air at the buying level, where there is much confusion. I have frequently been critical of attempts in this vein, the usual

results being a watered-down catalog of what is available. I am glad to see a real attempt to provide useful explanations of what to use and when.

A minor note: page 118 says the [Dynaco B&O stereo] mikes are set 3 feet apart. I hope not! It is closer to $8\frac{1}{2}$ inches.

Robert H. Tucker
Dynaco, Inc.
Philadelphia, Pa.


● BFO, SSB, Etc.

I enjoyed your article on TUNING SSB WITH BFO (Sept. '62 EI), but what about us poor guys who don't have BFO? How can we get SSB?

David Cox
Carrollton, Ala.

A Q-multiplier, if you have one, will supply the missing carrier, Dave. Or you could add external BFO or Q-multiplier. As a last resort, just decide you don't care for SSB, anyway.

● In Circles

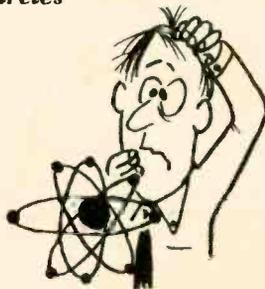

Dr. Millman's expert definition of electricity in the September '62 EI was circular. It is the electron that needs an exact definition. What is it? Your article on transistors in the same issue was wonderfully helpful. You Americans do scientific exposition superbly.

Greg Smelters
Manly, N.S.W.,
Australia

[Continued on page 6]

Let I. C. S. equip you for success in radio-TV-electronics— with professional equipment!



Brand-new "Electronic Laboratory," now being offered for the first time, can help you land in this big money-making field—FAST!

Here's an opportunity for you to turn spare time into cold cash, or begin a whole new career—in a field where the rewards have never been greater. And you *don't* need previous experience to do it!

International Correspondence Schools has just developed a new I. C. S. Electronic Laboratory you can construct in your own home. Includes series of training kits, plus the new I. C. S. VTVM—the professional quality vacuum tube voltmeter shown here. With it comes complete course instruction combining all the fundamentals with practical knowledge you can apply at once. And best of all, you build your own professional test instrument!

**I. C. S. instruction gets you going
with equipment you can really use!**

A famous manufacturer of nationally known electronic testing equipment worked closely with I. C. S. to develop the Electronic Laboratory and the VTVM itself. Everything you get is geared to increase your skill and knowledge step by step. Until finally, you've completed a precision testing

unit you can use for practically any kind of experimentation, design or servicing work.

Here's how I. C. S. instruction works. You begin with basic study lessons. Texts are clearly worded and easy to follow. At the same time, you "act out" what you learn with simple experiments. Then, in 3 easy stages, you assemble your own precision testing unit. Throughout, your instructor gives you expert, professional help. You learn at home, in spare time, as fast as ability permits.

**Coupon brings full details on your
future in this fast-growing field!**

Make up your mind right now to find out how I. C. S. training in Radio-TV-Electronics can pay off for *you*. See how it can help you cash in on the tremendous demand for men skilled in installation, maintenance and servicing of radios, TV sets, hi-fis, computers, automation systems and a host of other space-age devices. Clip and mail the coupon below. You'll receive 3 valuable *free* booklets—including sample lesson. They'll show how you can land in this big money-making field *fast!*

**Coupon brings 3 valuable FREE
booklets. Mail it today!**



INTERNATIONAL CORRESPONDENCE SCHOOLS



BOX K9723A, SCRANTON 15, PENNA. In Hawaii reply P. O. Box 418, Honolulu. In Canada, I.C.S. Canadian, Ltd., Montreal

Please rush me "How to Succeed," sample study lesson and opportunity booklet in the field I've checked below.

RADIO-TV-ELECTRONICS

- Electronic Fundamentals
- Electronic Technician
- F.C.C. License
- General Electronics
- Industrial Electronics
- Instrumentation, Servos, Automation Electronics
- Radio-TV Servicing

ELECTRICAL

- Electrical Drafting
- Electrical Engrg.
- Elec. Engrg. Technician
- Electric Light & Power
- Practical Electrician
- Professional Elec. Engr.

OTHER FIELDS

- Architecture-Building
- Art
- Automotive
- Business
- Engineering
- High School


IF NOT LISTED, PLEASE SPECIFY

Name _____ Age _____ Home Address _____

City _____ Zone _____ State _____ Working hours _____ A.M. to _____ P.M.

Employed by _____ Occupation _____

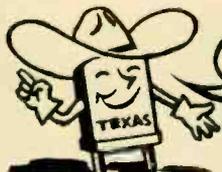Special low rates to members of U. S. Armed Forces



Send for NEW
FREE CATALOG #962
with oscillator
circuits

Citizen Band Class "D" Crystals

CITIZEN BAND CLASS "D" CRYSTALS
3rd overtone — .005% tolerance — to meet all FCC requirements. Hermetically sealed HC6/U holders. 1/2" pin spacing. .050 pins. (Add 15c per crystal for .093 pins) **\$2.95 EACH**

All 23 channels in stock: 26.965, 26.975, 26.985, 27.005, 27.015, 27.025, 27.035, 27.055, 27.065, 27.075, 27.085, 27.105, 27.115, 27.125, 27.135, 27.155, 27.165, 27.175, 27.185, 27.205, 27.215, 27.225, 27.255.

Matched crystal sets for ALL CB units (Specify equipment make and model numbers) **\$5.90 per set**

CRYSTALS IN HC6/U HOLDERS

SEALED OVERTONE .486 pin spacing — .050 diameter — .005% tolerance
15 to 30 MC **\$3.85 ea.**
30 to 45 MC **\$4.10 ea.**
45 to 60 MC **\$4.50 ea.**

FUNDAMENTAL FREQ. SEALED From 1400 KC to 2000 KC .005% tolerance **\$5.00 ea.**
From 2000 KC to 10,000 KC, any frequency, .005% tolerance **\$3.50 ea.**

RADIO CONTROL Specify frequency. .05 pins spaced 1/2" (Add 15c for .093 pins). **\$2.95 ea.**



QUARTZ CRYSTALS FOR EVERY SERVICE

All crystals made from Grade "A" imported quartz—ground and etched to exact frequencies. Unconditionally guaranteed! Supplied in:

FT-243 holders Pin spacing 1/2" Pin diameter .093
MC-7 holders Pin spacing 3/4" Pin diameter .125

CRIA/AR holders Pin spacing 1/2" Pin diameter .125
FT-171 holders Pin spacing 3/4" Banana pins

MADE TO ORDER CRYSTALS . . . Specify holder wanted
1001 KC to 1600 KC: .005% tolerance **\$4.50 ea.**
1601 KC to 2500 KC: .005% tolerance **\$2.75 ea.**
2501 KC to 9000 KC: .005% tolerance **\$2.50 ea.**
9001 KC to 11,000 KC: .005% tolerance **\$3.00 ea.**

Amateur, Novice, Technician Band Crystals

.01% Tolerance . . . \$1.50 ea. — 80 meters (3701-3749 KC) 40 meters (7152-7198 KC), 15 meters (7034-7082 KC), 6 meters (8335-8650 KC) within 1 KC

FT-241 Lattice Crystals in all frequencies from 370 KC to 540 KC (all except 455 KC and 500 KC) **50c ea.**
Pin spacing 1/2" Pin diameter .093

Matched pairs — 15 cycles \$2.50 per pair
200 KC Crystals, \$2.00 ea.; 455 KC Crystals, \$1.25 ea.; 500 KC Crystals, \$1.25 ea.; 100 KC Frequency Standard Crystals in HC6/U holders \$4.50 ea.; Socket for FT-243 Crystal 15c ea.; Dual Socket for FT-243 Crystals, 15c ea.; Sockets for MC-7 and FT-171 Crystals 25c ea.; Ceramic Socket for HC6/U Crystals 20c ea.

ENGINEERING SAMPLES and small quantities for prototypes now made at either Chicago or Fort Myers plants with 24 hour service. IN CHICAGO, PHONE GLadstone 3-3555

IF YOUR PARTS DEALER DOESN'T STOCK Texas Crystals, order direct and send us his name.

TERMS: All items subject to prior sale and change of price without notice. All crystal orders must be accompanied by check, money order or cash with payment in full.

RUSH YOUR ORDER NOW TO

TEXAS CRYSTALS

Div. of Whitehall Electronics Corp., Dept. E-33
1000 Crystal Drive, Fort Myers, Florida Phone WF 6-2100

FOR SHIPMENT VIA FIRST CLASS MAIL AT NO EXTRA COST ATTACH THIS ADVT. TO YOUR ORDER!

FEEDBACK

Continued from page 4

● Dismayed


I was dismayed to read the attack on Russian stations in your November HAM SHACK . . . If you had investigated your facts a little more you'd have found exactly 260 short-wave stations operating on the 40-meter ham band. These represent 60 countries. Included are 16 Voice of America transmitters.

I'm neither pro-American nor pro-Russian . . . just a DXer who believes that both sides are bad at cluttering.

Fred Woodley, Chairman
Canadian DX Club
London, Ont.

We agree with your facts, Fred, but not with your sentiments.

● Crazy Records

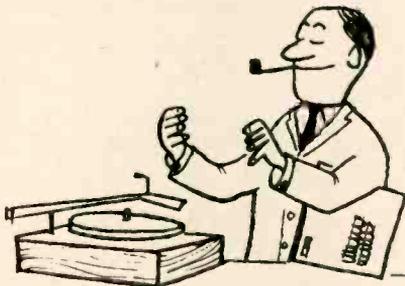

I got a kick out of your article, DIG THAT CRAZY MUSIC!, in the November EI. That music that isn't music is something (I think). Inspired by it, I invented a still newer form of non-music—a record with *nothing* on it. Since then I have improved my invention by eliminating the record. How's that?

J. B. Whittier
San Francisco, Calif.

How's that?

● Clubman

I am interested in forming an electronic experimenters club in my area.

Wayne Bolser
20 Amherst St.
Rosindale 31, Mass.

You Have Aptitude for Electronics

... Why Not Make It Your Career?

Get the Training You Need at COYNE then Step into High Salary Position in the Branch of Electronics You Like Best!

No matter what branch of electronics you prefer, you'll have no trouble landing just the job you want—provided you get the right kind of training.

Without this training you'll not get far. With it most of our graduates start right out with a beginner's salary of \$100 a week or more. Once you've started, you can move ahead fast to more important jobs that pay as much as \$14,000 a year.

AIRLINES NEED MEN

Who pays this kind of money to beginners? You'd be surprised at how many fine openings there are for Coyne trained men—in small towns and big cities everywhere all year 'round. For example, the airlines are always on the lookout for men who can fill jobs as radio mechanics, aircraft electricians and electronic systems technicians, to mention only a few. From a good starting salary, a trained man can quickly boost his income to \$8,000 a year. And that is by no means the limit.



THE MISSILE INDUSTRY

Another field where employers are clamoring for trained men is the missile industry—an industry growing so fast as to be almost unbelievable. Here there is a constantly increasing need for trained men. Every day these companies are hiring electronic technicians, laboratory technicians, electronic assembly inspectors and field service engineers. A field service engineer with minimum experience can easily demand and get \$8,000 a year—plus extra compensation in the form of living expenses and incentive pay.

COMPUTERS—Data Processing

A tremendous field. Men with basic electronic training are welcomed by manufacturers to receive further training—while on salary in—the operation and maintenance of their specialized equipment. Opportunities unlimited. No ceiling on salaries.

TV and RADIO Manufacturers

Perhaps the biggest opportunities of all are to be found with the large electronic manufacturers. With these giants, job opportunities are practically without limit.




And the same thing can be said of salaries. These radio and TV manufacturers are expanding into new fields and are growing at an unheard of rate. Any man with ability and ambition can grow with them, earn promotion after promotion. With these promotions come frequent pay raises as he continues to step from one important job to one still more important.

OR, YOUR OWN BUSINESS

Hundreds of graduates have gone to work for former graduates, servicing TVs and Radios, Air Conditioners, Refrigerators, other household appliances—then, after learning business methods have branched out and started their own shops. Others have started their own shops immediately upon graduating. Profits as independent business men, after taxes and other business expenses, are as high as \$10,000 to \$20,000 a year.

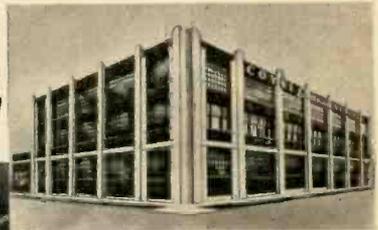These are not dreams. They are realities. But don't try to break into Electronics "on your own." You can save years of struggle and disappointment by first getting the necessary training at the great shop-laboratories of the Coyne School in Chicago.



CHICAGO — THE NATION'S ELECTRONICS CENTER

Don't get the idea that coming to Chicago to learn with Coyne is a costly or complicated undertaking. Nothing could be further from the truth. With modern transportation, Chicago is "close by" no matter where you live. High living costs? Not at all. We find a place for you to live—a place where, in many cases, your room and board cost no more than you would pay at home. And don't forget that you have every opportunity to earn money while you learn. Our employment department helps you get a part time job if you need extra money.

And think of the training you will get! Coyne is the oldest, largest and most completely equipped Resident School of its kind. And it is right in the heart of America's electronics center! Best of all, you can start your training with only a small down payment. They take care of the balance after you graduate!

FREE BOOK You've just read a Coyne offers to men who want to get into electronics. You'll find the complete, fascinating story in our big 48-page book "Your Opportunities in Electronics," we'll be glad to send you free. Read this Book before you make up your mind what you want to do.

We'll mail the book to you free and postage prepaid. You will not be under the slightest obligation. No salesman will call at your home. Mail the coupon now, or send your name on a postcard. When you see this wonderful book, you will be glad you sent for your free copy.

Coyne Electrical School

Chartered as an Educational Institution not for Profit
Dept. 33-A Chicago 7, Illinois



Clip OUT AND MAIL NOW!

COYNE ELECTRICAL SCHOOL, Dept. 33-A
1501 W. Congress Parkway, Chicago 7, Ill.

Send me your big 48 page Book "Your Opportunities in Electronics" and complete information about getting training for a high paying position in electronics. You are to send everything free and postage prepaid and it is understood that no salesman will call at my home.

Name _____
Address _____
City _____ RR No. or Zone _____ State _____

FREE!



Just press
the switch...

you're "on-the-air"

with this powerful transistor CB 2-way radio

New Cadre '510' 5-watt citizens band 2-way radio

Highest Power Allowed • Excellent Selectivity
Completely Transistorized • Maximum Reliability

Press the switch and you're on-the-air with the cleanest 27 Mc "talk" power possible — 5 watts. Reach vehicles and base stations instantly, dependably... up to 20 miles away. Perfect contact assured by 5 crystal-controlled transmit/receive channels.

Release the switch and the sensitive receiver circuit — a dual-conversion superheterodyne — captures weakest signals and reproduces them crisply and clearly.

HIGHEST SELECTIVITY prevents adjacent channel interference; electrical interference is virtually eliminated with an effective automatic noise limiter. Standby reception is noise-free, too, thanks to adjustable squelch.

100% SOLID-STATE DESIGN — Here's the most reliable maintenance-free CB transceiver. Fully transistorized — 26 transistors and diodes — it operates safely all day. No tubes to burn out. Lowest current drain prolongs battery life. Solid-state components absorb road shocks without damage.

EASIEST TO INSTALL — The 3½" height of the smallest, full-power CB radio fits most anywhere, never steals leg room in a vehicle. And it can be used anywhere—mobile, fixed, field, marine craft—with its built-in dual 12VDC/110-220VAC power supply. Add a portable pack accessory (model 500-1) with rechargeable batteries for the lightest, portable 5-watt radio.

Cadre '510' 23-channel manual tuning, dynamic microphone, matched set of crystals, universal mounting bracket, AC & DC cords... \$199.95. Cadre '515' same features as 510 less 23-channel manual tuning... \$187.50

See your Cadre distributor for a demonstration
CADRE INDUSTRIES CORP.

Commercial Products Division, Endicott, N.Y. • Area Code 607, 748-3373

Canada: Tri-Tel Assoc., Ltd., 81 Sheppard Ave. West, Willowdale, Ont.
Export: Morhan Exporting Corp., 458 Broadway, New York 13, New York

CB MARKETPLACE



New Browning transceiver, M-523, has 23-channel operation, measures 8x3x9 inches, comes with DC power supply and TVI filter (harmonic). Accessories: S-meter, rear deck speaker, AC power supply. Browning Labs, Laconia, N. H.



Cadre 510 has 18 transistors, 8 diodes, 5 crystal T-R channels, AC and DC power supplies, squelch, noise limiter and push-to-talk. Meets Canadian DOT specs. \$199.95. Cadre also has on tap the new 515, a stripped-down business model. Cadre Industries, Endicott, N. Y.



DeWald R-1050 has 6 crystal-controlled T-R channels plus manual tuning, S/plate-current meter, PTT with electronic switching. Nuvistor front-end, pi network, squelch, noise limiter. \$119.95. United Scientific Labs. LIC, N. Y.



Kaar TR327B features 2 crystal T-R channels plus three other crystal transmit channels with tunable receiving; squelch and noise limiting. Another model, TR327A, has 4 crystal channels plus 8C band. Kaar Engineering, Palo Alto, Calif.

3 More Big Training Advantages



DeVRY Tech Exclusive!

WITH TRANSISTORIZED METER . . . PLUS NEW "MODULAR CIRCUITS" TO BUILD AT HOME!

Now Prepare for GOOD JOB OPPORTUNITIES IN ELECTRONICS Faster—with

1. **METER** — Transistorized, Portable, AC-DC Multimeter
2. **SCOPE** — 5-inch New Streamlined Commercial-Type Oscilloscope
3. **ELECTRO-LAB*** — For 3-Dimension Circuit Building

To help you get ready F-A-S-T-E-R . . . and THOROUGHLY . . . for good-paying job opportunities in the fast growing Electronics field, DeVry Technical Institute now presents the newest and finest training advantages in its over 30 years of experience. Now . . . AT HOME . . . in your spare time, you prepare with "industry-type" home laboratory equipment. To provide real PRACTICAL EXPERIENCE, you build a quality Transistorized Meter and a 5-inch industrial-type Oscilloscope . . . work with small, 3-dimensional circuits on DeVry's new Design Console . . . use highly instructive home training movies . . . and follow up-to-date lessons with many time-saving fold-out diagram sheets.

Little wonder DeVry men qualify for such fine opportunities in Space-Missile Electronics, Automation, Computer Work, Radio-TV, Industrial Controls, and other fields.

You learn PRACTICAL techniques important in today's Space Age industry, because you build many compact circuits with the streamlined Electro-Lab, using exclusive solderless "modular connectors." You perform over 300 construction and test procedures in all! Your self-built test equipment has function-grouped controls, meter scales color-keyed to the panel markings—much like instruments used on today's jobs. What's so important, the home laboratory and the test equipment are YOURS TO KEEP!

INDUSTRY NEEDS TRAINED MEN

Through this remarkable 3-way method, DeVry Tech has helped thousands of ambitious men prepare for good jobs or their own profitable full-time or part-time service shops. It is the newest in a long series of PRACTICAL training aids that we have pioneered and developed in more than three decades of experience. Sound interesting? Then see how DeVry Tech may help YOU. Mail the coupon today.

From RADIO to SPACE-MISSILE ELECTRONICS

DeVry's training goes all the way from radio repair . . . to space-missile electronics. That's the range of subjects covered in its programs AT HOME or in its well-equipped training centers in Chicago and Toronto. You learn up-to-date techniques, working with new equipment, modern texts, movies—one of today's finest combinations of training equipment . . . geared for RESULTS!

EMPLOYMENT SERVICE

When you complete the program, DeVry's efficient Employment Service is ready to help you get started. There is no extra charge—ever—for this aid.

ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL

DeVRY TECHNICAL INSTITUTE
CHICAGO • TORONTO



OSCILLOSCOPE

DESIGN CONSOLE



METER

* Trademark ©

MAIL COUPON FOR FREE FACTS

DEVRY TECHNICAL INSTITUTE 2082
4141 Belmont Ave., Chicago 41, Ill., Dept. EI-3-T

Please give me your two free booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- | | |
|--|---|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications |
| <input type="checkbox"/> Television and Radio | <input type="checkbox"/> Computers |
| <input type="checkbox"/> Microwaves | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radar | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics | |

Name _____ Age _____

Address _____ Apt. _____

City _____ Zone _____ State _____

Check here if you face military service.
Canadian residents: Write DeVry Tech of Canada, Ltd.
970 Lawrence Avenue West, Toronto 19, Ontario

FREE GIANT NEW 1963 CATALOG

CB MARKETPLACE

1963 ANNUAL CATALOG

BA
SINCE 1927

RADIO-TV ELECTRONICS

BURSTEIN-APPLEBEE CO. 1013-14 McGEE ST. KANSAS CITY, MO.

TOP VALUES IN POWER & HAND TOOLS

HI-FI & STEREO COMPONENTS AND SYSTEMS

TUBES PARTS ETC. AT VERY LOWEST PRICES

30 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

SAVE UP TO 50% ON B-A SELECTED KITS



Globe Master has 11 crystal T-R channels, dual conversion, speech clipping adjustable to 22db, noise limiter, squelch, pi network, S-meter. The set contains 14 tubes, has slide-rule dial. \$229.95. GC Electronics, Rockford, Ill.

BURSTEIN-APPLEBEE CO.

Dept. EI, 1012 McGee St., Kansas City 6, Mo.

Rush me FREE 1963 B-A Catalog.

Name

Address

City..... State

SEND FOR IT TODAY

FREE



Hammarlund CB-23 offers crystal-controlled transmitting and receiving on all 23 channels, has dual conversion with 262-kc IF, squelch, noise limiter, meter. Price of \$229.50 includes all crystals. Hammarlund Mfg., New York 10, N. Y.

WHAT'S HE SO HAPPY ABOUT?

HE JUST HEARD ABOUT THE PEANUTS CARTOON BOOKS IN THE NEW CREST EDITIONS!


ON SALE WHEREVER PAPERBACKS ARE SOLD — only 35¢

CREST BOOKS



Heath GW-42 is a kit which includes 3 circuit boards. It has a 3-way power supply, 5 crystal T-R channels, four-tone selective call, slide-rule dial, meter, noise limiter, squelch. Price is \$119.95. Heath Co., Benton Harbor, Mich.

[Continued on page 14]

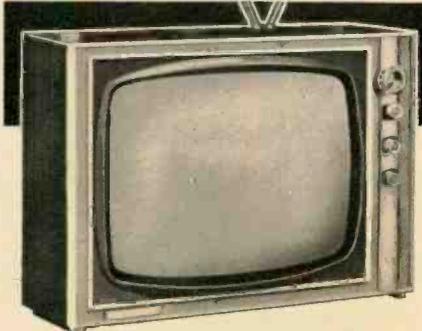

NOW...BUILD YOUR OWN TOP QUALITY TV SET

Save money as you enjoy constructing your own fine table-model TV set. Anyone can build it—no technical knowledge or skill needed. The "Custom 70" is *Performance Guaranteed* by NRI—the top name in Electronics training for nearly 50 years. Picture tube has 206 sq. in. of viewing area. All-American parts. Quality "slim-line" cabinet. Everything included at one low price. Package payment plan. Tear out this ad, write your name and address in margin and mail to CONAR INSTRUMENTS, 3939 Wisconsin Ave., Washington 16, D.C. Conar will rush pictures and facts.

CONAR instruments

A Division of NATIONAL RADIO INSTITUTE

Electronics Illustrated

Learn Electronics

PREPARE FOR YOUR F. C. C. LICENSE—YOUR TICKET TO A BETTER JOB AND HIGHER PAY!

F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. commercial (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire licensed technicians.

WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radiotelephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a **FIRST CLASS F.C.C. license**, and it does this by **TEACHING** you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand. The organization of the subject matter is such that you progress, step-by-step, to your specific objective—a first class F.C.C. license.

CORRESPONDENCE OR RESIDENCE CLASSES

Grantham training is available by correspondence or in resident classes. Either way (residence or correspondence), we train you quickly and well—no previous training required. Even a beginner may qualify for his first class license in a relatively short time.

RESIDENT CLASSES HELD IN FOUR CITIES

To better serve those students who wish to attend resident classes, Grantham School of Electronics offers **DAY** and **EVENING** classes in four different cities—Los Angeles, Seattle, Kansas City, and Washington, D.C. The same rapid course in F.C.C. license preparation is conducted in all four locations. If you are interested in attending a **DAY** or **EVENING** class, indicate the city of your choice in the coupon below, and mail the coupon to Hollywood for *free information*. There is no obligation of any kind.

GRANTHAM SCHOOL OF ELECTRONICS

LOS ANGELES • SEATTLE • KANSAS CITY • WASHINGTON

1505 N. Western Ave., Los Angeles 27, Calif. HO 7-7727
 408 Marion Street, Seattle 4, Washington MA 2-7227
 3123 Gillham Road, Kansas City 9, Mo. JE 1-6320
 821—19th Street, NW, Washington 6, D.C. ST 3-3614

Accredited Member of the National Home Study Council

MAIL COUPON NOW—NO SALESMAN WILL CALL →

This booklet

FREE!



This free booklet gives details of our training and explains what an F.C.C. license can do for your future.

Upgrade Your Income with a First Class F. C. C. LICENSE

HERE'S PROOF...

that Grantham students prepare for F.C.C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
Gary DeLeo, 9219 N.E. 76th St., Vancouver, Wash.	1st	12
Dennis P. Miller, 416 W. Oak St., Alexandria, Va.	1st	12
Cecil C. Hironimus, 113 Berwick Rd., Johnstown, Pa.	1st	12
Max D. Reece, 4222 Fremont Ave. N., Seattle 3, Wash.	1st	20
Robert Bennis, 3802 Military Rd. N.W., Washington, D.C.	1st	12
Jon M. Martin, 7913 Sausalito Ave., Canoga Park, Calif.	1st	24
Kline H. Mengle, 401 Granville Dr., Silver Spring, Md.	1st	24
Gary D. Burnard, Johnson Rd., Kirkwood, RD #1, N. Y.	1st	12

YOUR F. C. C. LICENSE IS U.S. GOVERNMENT EVIDENCE OF YOUR KNOWLEDGE IN ELECTRONICS

(Mail in envelope or paste on postal card)



To: **GRANTHAM SCHOOL OF ELECTRONICS**
 NATIONAL HEADQUARTERS OFFICE
 1505 N. Western Ave., Hollywood 27, Calif.

Gentlemen:

Please send me your free booklet telling how I can get my commercial F.C.C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____


I am interested in: Home Study, Kansas City classes, 38-C

Los Angeles classes, Seattle classes, Washington classes

PASTA, ANYONE? . . . That edible-looking material held by the cute young thing at right fools you into thinking it might be bound for Mother Leone's cooking pot. One nibble and you'd be dribbling teeth on the floor. What the girl holds is an interesting new coaxial cable which has extremely low loss characteristics because the insulation around it is mostly air. A ballooning white plastic sleeve is first slipped over the center conductor. Then it is crimped and sealed at short intervals to form a moisture-proof and gas-tight bond with the metal. The air trapped inside each small cell represents insulation. The coax, called *Ballon*, is a French invention now licensed to Superior and Simplex, U. S. cable firms. Marketing plans haven't yet been announced.



Micro Mike . . . Dwarfed by the O-for-Operator on the telephone dial shown at lower left is the newest thing in microphones. Needless to say, it's also the smallest. Raytheon's Dr. Wilhelm Rindner was studying effects of surface defects on transistors when he accidentally bumped into some phenomena that led to the baby mike. Dr. Rindner noticed that when he probed, scratched and tapped the semiconductor material in a transistor, the current flowing through the device varied in accordance with his puttering. Out of that observation came a mike which consists of a PNP transistor and what looks like a thumbtack, a small one. The point of the tack bears down on the top layer of semiconductor material, while the head represents a tiny diaphragm. The diaphragm, like any normal-size one, responds to vibrations. The resulting pressure is passed on to the semiconductor material and produces variations in the transistor's current flow. Frequency response is a fantastic .01 to 120,000 cps. Raytheon predicts uses in seismology, for weight and pressure tests in labs, as a strain gauge, in space vehicles, in military weapons, in medicine and in hearing aids.

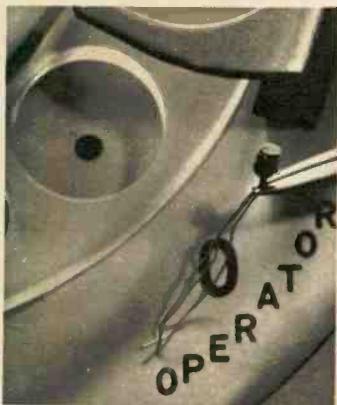

Brain Cell . . . At the heart of the rig at right is a cubic inch of quartz fibers. The action: the chap from Sperry Gyroscope speaks the word *five* into the mike and that number appears on the panel above the apparatus. Sperry calls it a brain cell in that it can listen to, recognize and react to a voice, a single word or any sound. It bears the same Sceptron. By responding selectively to voices or sounds, the cell may make possible dial-less phones, key-less cash registers and secretary-less typewriters. You'd just speak directly to the machine. In the Sceptron thousands of light-carrying fibers react to a sound by vibrating. This pattern is recorded on a light-sensitive plate placed between the fibers and a photo cell. The fibers then react only to the particular stimulus that drew the recorded pattern.





NEW!

build-your-own **knight-kit®**

WALKIE-TALKIE!

ALL-TRANSISTOR 2-WAY TRANSCEIVER KIT



LOWEST PRICE KIT EVER! ONLY... **\$9.95** EACH



- Talk to Neighbors, Family & Friends Up to 1/4 Mile Away
- Works Up to 75 Hours on Just One Battery—Weights 9 Ounces
- No License, Exam, Permit, Age Limit—Anyone Can Use It

Here's the 2-way Knight-Kit everyone wants! In a few fun-packed hours you'll have this 3-transistor beauty assembled and ready for reliable on-the-move communication. The C-100 is great for camping, hunting, boating, picnic outings, or just talking to friends in your neighborhood. Just press the push-to-talk button and you're "on the air" (built-in 2" speaker also serves as mike). Release button to listen. Fits your hand snugly—only 5 1/4" x 2 1/8" x 1 3/4". Operates up to 75 hours on low-cost cell. Has 40" telescoping whip antenna. Includes high-impact Caribbean blue case, all parts, transmitting crystal, wire, solder, easy instructions. Less carrying case and battery. Wt. 9 ozs. **99¢**

83 Y 804DV. C-100 Walkie-Talkie Kit. **Only 99¢**
 83 Y 013. Leatherette Carrying Case. **98¢**
 83 Y 002. 9-Volt Battery. **21¢**

Complete 2-Station System Outfit. Includes 2 Knight-Kit C-100 Walkie-Talkie Kits; 2 Leatherette Carrying Cases; 2 9-Volt Batteries; Wall Soldering Iron; Screwdriver; Miller Wire Stripper/Cutter—everything you need to assemble a complete 2-Station System. Wt., 6 lbs. 83 Y 800DV. \$5 per month. **Only \$24.95**

satisfaction guaranteed or your money back

TYPICAL OF THE QUALITY AND VALUE OF OVER 100 GREAT KNIGHT-KITS

manufactured by **KNIGHT ELECTRONICS CORP.**
A DIVISION OF

ALLIED RADIO

ALLIED RADIO

100 N. Western Ave., Chicago 80, Ill.
Ship me the following:

- C-100 Walkie-Talkie Kit(s) 83 Y 804DV
 - Carrying Case(s) 83 Y 013
 - 9 V. Battery(ies) 83 Y 002
- Complete C-100 2-Station System 83 Y 800DV**
 - \$..... enclosed (check) (money order)
 - Ship No Money Down on Allied's Credit Fund Plan

Name _____
PLEASE PRINT

Address _____

City _____ Zone _____ State _____

ORDER TODAY

New Credit Customers Only: Send name and address present employer, how long employed, position, monthly salary; rent or own home, how long at present address; give age (21 minimum for credit account).



EMC's UNBEATABLE VALUES!!!

You get the most
per measurement dollar!

All New precision instruments . . . satisfaction guaranteed! Best quality! By far the best value obtainable in wired or kit form!



with complete instruction pair of test leads.

EMC NEW MODEL 212 . . . TRANSISTOR ANALYZER . . .
Checks DC current gain in 3 ranges to 200. Tests for leakage. Checks all transistors as oscillators both in and out of circuit. Can be used to signal trace AF, IF or RF circuits. Checks condition of diodes. Tests battery voltage on 0-12 scale. Checks DC current drain on 0-80 ma scale. Supplied manual, transistor listing and Model 212 . . . **\$18.50 Wired**
Model 212 Kit . . . **\$13.50**



Completely modern! Completely flexible! Completely new! Checks all the new 12 prong (Compactron), Nuvisor, Novar, and 10 prong tubes, in addition to octal, loctal, miniature, and 9 prong tubes. Tests each tube for shorts, leakages, intermitents, opens, as well as for quality. Each section of multi-purpose tube is checked separately. Magic eye, Voltage Regulator and HI-FI tubes are also tested. Unique switching arrangement makes the checker obsolescent proof. Supplementary tube listings supplied periodically at no cost to keep instrument up to date. It comes complete with instructions and tube charts in ring bound manual.

Model 213 (In bakelite case with strap) . . . **\$28.90 Wired**
Model 213 Kit . . . **\$18.90**



Model 213P (in wood carrying case) . . . **\$32.25 Wired**
Model 213 P Kit . . . **\$21.90**

EMC NEW MODEL SA SOCKET ADAPTOR . . .
Enables user to check 12 pin Compactron, Nuvisor, Novar and 10 pin tubes with any type tube tester including mutual conductance type.

Model SA . . . **\$9.45 Wired**
Model SA Kit . . . **\$4.95**

Yes, tell me more, send me **FREE** a detailed catalog of the Complete EMC Line. EL-3

NAME
STREET
CITY STATE.....

EMC Electronic Measurements Corp.
625 B'way, New York 12, N. Y.
Ex. Dept., Pan-Mar Corp., 1270 B'way, New York 1, N. Y.

CB MARKETPLACE



Executive Model 10 is stripped rig with 3 crystal transmit channels, manual T-R control, noise limiter. Accessories are power supplies, squelch, PTT, 12-position crystal selector. \$59.50 less power supply. Intl. Crystal, Oklahoma City.



Knight KN-2500 features 6 crystal T-R channels, noise limiter, squelch, pi network, PTT and combination S-meter and RF field-strength meter. Spot switch permits you to locate your own signal. \$99.95. Allied Radio, Chicago 80, Ill.



Lafayette HE-90 gives you 6 crystal T-R channels, a Nuvisor RF amplifier, PTT, noise limiter, squelch, S-and-power meter, spotting switch for locating your signal on tunable receiver. \$94.50. Lafayette Radio, Syosset, N. Y.



EICO 772, for 117-VAC or 12-VDC operation, comes as a kit (\$89.95) or wired (\$119.95). Offers crystal control on 4 transmit, 1 receive channel; PTT, pi network, squelch and noise limiter. EICO, Long Island City, N. Y.


Pick the course for your career...

Electronics Technology



A comprehensive program covering Automation, Communications, Computers, Industrial Controls, Television, Transistors, and preparation for a 1st Class FCC License.

Electronic Communications

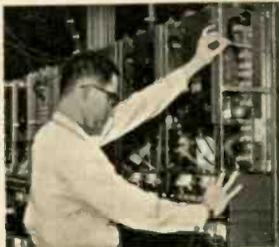

Mobile Radio, Microwave and 2nd Class FCC Preparation are just a few of the topics covered in this "compact" program... Carrier Telephony too, if you so desire.

First Class FCC License



If you want a 1st Class FCC ticket quickly, this streamlined program will do the trick and enable you to maintain and service all types of transmitting equipment.

Broadcast Engineering



Here's an excellent studio engineering program which will get you a 1st Class FCC License and teach you all about Program Transmission and Broadcast Transmitters.

Get A Commercial FCC License ...Or Your Money Back!

A Commercial FCC License is proof of electronics skill and knowledge. Many top jobs require it... every employer understands its significance. In your possession, an FCC Commercial Ticket stamps you as a man who knows and understands electronics theory... a man who's ready for the high-paid, more challenging positions.

Cleveland Institute home study is far and away the quickest, most economical way to prepare for the FCC License examination. And that's why we can make this exclusive statement:

The training programs described above will prepare you for the FCC License specified. Should you fail to pass the FCC examination after completing the course, we will refund *all* tuition payments. You get an FCC License... or your money back!

Before you turn this page, select the program that fits your career objective. Then, mark your selection on the

Cleveland Institute of Electronics

1776 E. 17th Street, Dept. EI-44
Cleveland 14, Ohio



Accredited Member


coupon below and mail it to us today. We'll send you... without obligation... complete details on our effective Cleveland Institute home study. Act NOW... and insure your future in electronics.

Mail Coupon TODAY For FREE Catalog

Cleveland Institute of Electronics

1776 E. 17th St., Dept. EI-44
Cleveland 14, Ohio

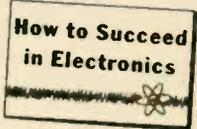Please send FREE Career Information prepared to help me get ahead in Electronics, without further obligation.



CHECK AREA OF MOST INTEREST—

- | | |
|---|--|
| <input type="checkbox"/> Electronics Technology | <input type="checkbox"/> First Class FCC License |
| <input type="checkbox"/> Industrial Electronics | <input type="checkbox"/> Electronic Communications |
| <input type="checkbox"/> Broadcast Engineering | <input type="checkbox"/> _____ other _____ |

Your present occupation _____

Name _____ Age _____
(please print)

Address _____

City _____ Zone _____ State _____


Approved for Veteran's Training under Korean GI Bill. EI-44

Built in Beauty

WITH TRUE PORTABILITY FOR YOUR
TV, FM, HI-FI and STEREO

- Built in Beauty with Wall Plates by MOSLEY
- o Gives you Concealed Wiring!
 - o Improved Signal for better reception!
 - o Enables Multiple Set Use!

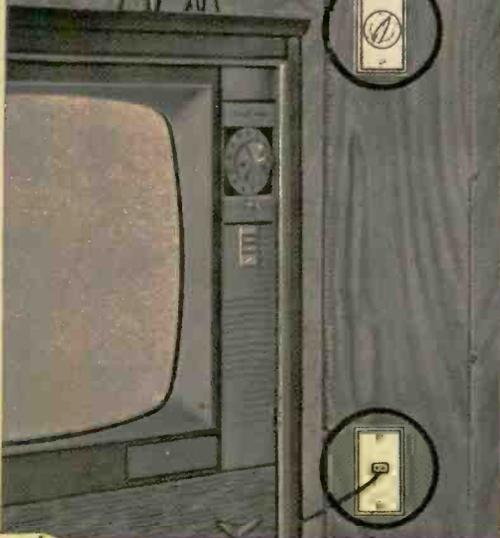CALL PERching 1-3036-TV PLATE DEPT.
or mail Form below for
FREE "DO-IT-YOURSELF" Instructions



Please send me free "Do-It-Yourself" instructions for improving my TV/FM and Hi-Fi Stereo systems.

NAME:
ADDRESS:
CITY/STATE:


Mosley Electronics, Inc.

4610 N. LINDBERGH BLVD. BRIDGETON, MO.

CB MARKETPLACE



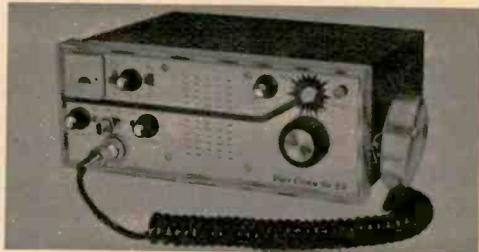Pearce-Simpson Companion features 5 crystal T-R channels, noise limiter, squelch, 3 watts actual RF output. Modulation limited to 95%. Cabinet is 8 3/4 x 12 1/4 x 5 inches. Price is \$189.50. Pearce-Simpson, Miami 35, Fla.



Poly-Comm Senior 23 includes 23-channel, 11-crystal synthesizer, message light, tone call/squelch, S-power meter, PTT, noise limiter, audio output for PA use and tilting bracket. Price: \$349.50. Polytronics Lab, Clifton, N. J.



Falcon Mark V features an RF gain control, 3-way supply, squelch, special noise limiter, double conversion, pi network. S-meter doubles as power meter. \$169.95; twin noise suppressor \$20 extra. Tecraft Sales, S. Hackensack, N. J.



Band Spanner 440 has 10 crystal T-R channels (using one crystal per channel), dual conversion with 250-kc IF, output modulation meter, noise limiter, squelch, simulated wood-grain cabinet. \$209.50. Webster Mfg., S. San Francisco, Cal.

NOW!
at a price
you can afford!

MAKE MORE MONEY in ELECTRONICS TELEVISION-RADIO

**BETTER...MORE COMPLETE...LOWER COST...
WITH NATIONAL SCHOOLS SHOP-METHOD
HOME TRAINING!**

BETTER... Training that is proved and tested in Resident School shops and laboratories, by a School that is the **OLDEST and LARGEST** of its kind in the world.

MORE COMPLETE... You learn **ALL PHASES** of *Television-Radio-Electronics*.

LOWER COST... Other schools make several courses out of the material in our **ONE MASTER COURSE**... and you pay more for less training than you get in our course at **ONE LOW TUITION!**



Prepare
for your
F.C.C. LICENSE

Be prepared for secure future in

- INDUSTRIAL ELECTRONICS
- COMPUTERS
- GUIDED MISSILE SYSTEMS
- ELECTRONIC CONTROLS
- or go into . . .
- COLOR TV REPAIR
- HI-FI AND SOUND SYSTEMS
- BROADCASTING STUDIOS
- INSTALLATION

TOP PAY... UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry! Trained technicians are in growing demand at excellent pay—in **ALL PHASES**, including Servicing, Manufacturing, Broadcasting and Communications, Automation, Radar, Government Missile Projects.

NATIONAL SCHOOLS SHOP-METHOD HOME TRAINING, with newly added lessons and equipment, trains you in your spare time at home, for these unlimited opportunities, including many technical jobs leading to supervisory positions.

YOU LEARN BY BUILDING EQUIPMENT WITH KITS AND PARTS WE SEND YOU. Your National Schools course includes thorough Practical training—**YOU LEARN BY DOING!** We send you complete standard equipment of professional quality for building various experimental and test units. You advance step by step perform more than 100 experiments, and you build a complete TV set from the ground up that is yours to keep! A big, new TV picture tube is included at no extra charge.

EARN AS YOU LEARN. We'll show you how. Many students pay for their course—and more, while studying.

**GET THE BENEFIT OF OUR
OVER 55 YEARS EXPERIENCE**

APPROVED FOR
GI TRAINING



ACCREDITED
MEMBER



NATIONAL SCHOOLS

World-Wide Training Since 1905

Write to Dept. R4Y-23

4000 So. Figueroa Street
Los Angeles 37, California

YOU GET...

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

**IMPORTANT
SEE OTHER SIDE**

THESE TWO FREE BOOKS TELL HOW

SEND FOR FREE FULLY-ILLUSTRATED BOOK AND ACTUAL LESSON TODAY. Your own copy of "Your Future In Electronics-Television-Radio" will be mailed to you at once. No salesman will call; there is no obligation. Cut out card along dotted lines, fill in and mail today!
NO POSTAGE NECESSARY.

CUT OUT AND MAIL THIS CARD TODAY

Yes, I want to make more money in Electronics-TV-Radio. Send me your **FREE Fully-Illustrated Opportunity Book and Actual Lesson** today.

RUSH TODAY—NO POSTAGE NECESSARY



Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Check here if interested only in Resident Training at Los Angeles. R4Y 23
Veterans: Give date of discharge _____


NO SALESMAN WILL CALL; NO OBLIGATION ON YOUR PART

DON'T BE HALF-TRAINED

Be a **MASTER TECHNICIAN** in

ELECTRONICS-TV-RADIO

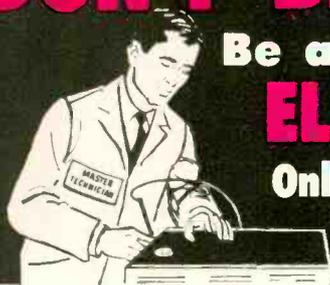Only N.T.S. offers you **ALL 8 PHASES** in **ONE MASTER COURSE**



**SUCCESS IS THEIRS;
IT CAN BE YOURS TOO!**



I cannot praise N.T.S. enough. I've just graduated and already I have started repairing radios and servicing TV's . . . At 53, I'm starting a new life and my diploma from National Technical Schools is my proudest possession.

William E. Eckenrod

As field director of Berean Mission Inc., I have complete charge of our radio work.



With the expert advice and training I am receiving from you I can do my own repairs on our recorders and P.A. systems, besides keeping our radios going. My training from N.T.S. helps keep us on the air. I feel privileged to be a member of such a fine institution.

Rev. Enoch P. Sanford



Thanks to N.T.S. I have a business of my own right in my home. I have paid for all my equipment with money earned servicing TV sets. Yes, N.T.S. gave me my start in television.

Louis A. Tabat

I have a TV-Radio shop in Yorkville, Illinois, about 4 miles from my home, and it has been going real good. I started part-time but I got so much work that I am doing it full-time. Thanks to National Technical Schools.



Alvin Spera

SEE OTHER SIDE

ALL 8 PHASES IN ONE MASTER COURSE

**PHASE 1
TELEVISION
INCLUDING COLOR TV**
90% of homes have at least one set. Color TV is becoming more popular daily. TV Stations grow in number, need technicians. Maintenance and repair offer big opportunities.

**PHASE 2
RADIO—AM & FM**
Radios in homes, cars, schools, all need expert upkeep. Stations expand as FM becomes popular. Now transistors boom entire field.

**PHASE 3
INDUSTRIAL
ELECTRONICS**
Computers, Data-Processing machines, Electronic Controls, Guided Missile Systems are new fields where Electronics play a vital role.

**PHASE 4
SOUND SYSTEMS**
New popularity of Hi-Fi. Stereo, as well as industrial sound systems and business intercoms make this a highly specialized and important field.

**PHASE 5
FCC LICENSE
PREPARATION**
FCC License holders have a wide range of top jobs open to them. FCC License now a requirement for most Communication jobs.

**PHASE 6
RADAR AND
MICROWAVES**
These are the communications systems of the future, already used in tracking and contacting satellites.

**PHASE 7
AUTOMATION
& COMPUTERS**
Automation and Computer electronics are the new tools of industry and commerce. Skilled Technicians in these fields are in great demand at top pay.

**PHASE 8
BROADCASTING &
COMMUNICATIONS**
In the entertainment industry, or in commerce, communications and broadcasting have great importance. Installation and maintenance of equipment requires trained technician know-how.

FIRST CLASS

Permit No. 3087

Los Angeles, Calif.

BUSINESS REPLY MAIL
NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

— POSTAGE WILL BE PAID BY —

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

4000 So. Figueroa Street

Los Angeles 37, California

RESIDENT TRAINING
AT LOS ANGELES

If you wish to take your training in our famous Resident School in Los Angeles—the oldest and largest school of its kind in the world—check special box in coupon.



Approved for GI Training

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905


Address correspondence to Dept. R4Y-23

4000 So. Figueroa Street

Los Angeles 37, California

National Technical Schools also offers Complete Home Study Training Programs in Auto Mechanics & Diesel, Air Conditioning, Refrigeration-Electrical Appliances, and Home Appliances Repair. For information and FREE BOOK write the School, Dept. RDC, stating course desired.

CB MARKETPLACE

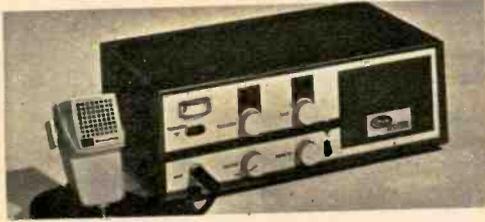

Olson Spotter features 12 crystal transmit channels, dual-conversion receiver, S/modulation meter, squelch, noise limiter, spotting switch. Operates on 117 VAC and either 6 or 12 volts DC. \$119.95. Olson Radio, Akron 8, Ohio.



Ray-Tel 2 is a business rig offering 5 channels without variable tuning. It has adjustable squelch, noise limiting, 10 tubes, 117-VAC or 6/12-VDC operation. Comes with a yoke mount. \$189.95. Raytheon Co., Lexington 73, Mass.



Apelco AR-10 is a 10-channel job with noise limiter, squelch, and combination modulation-output meter. It has 3 IF stages, operates on 117 VAC or 12 VDC. Meets DOT specs for use in Canada, maker claims. Apelco, S. San Francisco, Calif.



Heath GW-30 walkie-talkie is a 90-milliwatt unit which can be operated without a license but requires a ticket when talking to CB stations. Superregen receiver, 1 crystal transmitting channel. Uses 9-volt battery, has 40-inch whip antenna. The kit is \$32.95, wired unit runs \$50.95. Heath Co., Benton Harbor, Mich.

LATEST SAMS BOOKS FOR EVERYONE IN ELECTRONICS



USE THIS HANDY ORDER FORM

- Howard W. Sams International Code Training System.** Amazing new Course, including both text and 33½ rpm recordings, takes you from 3 to 22 words (sending and receiving) in less time, with greater speed and accuracy than any other method known! In just a few hours, you'll be able to receive code at 2-3 words per minute—no need to memorize individual code characters! In a few more hours you'll be receiving in excess of 20 wpm—and sending, too. Includes full text, plus six 7" LP record sides. There's never been anything to equal this System for learning speed! Order CTG-1, only \$4.95
- ABC's of Computer Programming.** Explains principles and applications of digital computer programming, from the simple to the intricate. Also gives you a full understanding of computer functions. An invaluable guide to this most important and least understood aspect of computer use. Order CPL-1, only \$1.95
- North American Radio-TV Station Guide.** Gives protected area, channel number, call letters, assigned power for 1,000 VHF and UHF TV stations; frequency, call letters, location for over 5,000 AM stations and 1,500 FM stations. Includes 14 valuable maps showing station locations. Invaluable for DXers, TV-radio technicians, etc. Order RSG-1, only \$1.95
- Transistor Substitution Handbook.** Shows over 15,000 direct substitutions; includes basing diagrams, polarity indications and manufacturers for over 6,000 transistor types. Explains why substitution is possible; when to substitute and when not; precautions to observe. Order SSH-4, only \$1.50
- Industrial Electronic Circuits Handbook.** A realistic explanation of typical industrial electronics circuitry; includes schematics and text descriptions of circuit operation and functions for over 50 different configurations. Order IEC-1, only \$3.95
- Modern Communications Course, Vol. 3. FM & Multiplex Modulation Systems.** Provides a complete understanding of FM systems and multiplex and pulse modulation systems. Includes projects and experiments, as well as review questions. Order MCN-3, only \$4.95
- Industrial X-Ray Handbook.** Fully explains principles and practices of modern X-ray technology. Covers generation and detection of radiation; basic applications, equipment and techniques; medical, industrial, commercial and lab uses, health physics, etc. A comprehensive treatise. Order IXE-1, only \$7.95



FREE! Ask for the Sams Booklist, describing over 200 important books.

FREE! Index to Photofact, world's finest circuit data on 53,000 TV & radio models.

HOWARD W. SAMS & CO., INC.

Order from any Electronic Parts Distributor, or mail to Howard W. Sams & Co., Inc., Dept. C-123 4300 W. 62nd St., Indianapolis, 6, Ind.

Send books checked above. \$ _____ enclosed.

Send FREE Booklist. Send Photofact Index

Name _____

Address _____

City _____ Zone _____ State _____

IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7

ELECTRONICS

NEW DOUBLE DUTY TOOL SETS

Compact, convertible sets do more jobs with fewer tools, save bench space, lighten the service kit. Remarkable piggyback "torque amplifier" handle slips over pocket too! handles to give the grip, reach, and power of standard drivers. Slim, trim see-thru plastic case fits pocket, has flat base for use as bench stand.




PS-7 SET

2 nutdrivers ($\frac{1}{4}$ " and $\frac{3}{8}$ "),
2 slot tip screwdrivers
($\frac{3}{16}$ " and $\frac{1}{2}$ "), 2 Phillips
screwdrivers (#0 and #1),
all $3\frac{1}{2}$ " pocket size . . .
plus 1" x $3\frac{3}{8}$ " hollow
handle and case.



PS-120 SET

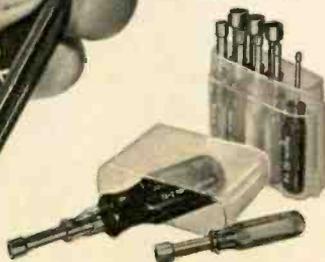10 color coded, $3\frac{1}{4}$ "
pocket size nutdrivers
($\frac{3}{32}$ " thru $\frac{3}{8}$ ") . . .
plus 1" x $3\frac{3}{8}$ " hollow
handle and case.



WRITE FOR LITERATURE

XCELITE

XCELITE, INC. • 16 BANK ST., ORCHARD PARK, N. Y.
Canada: Charles W. Pointon, Ltd., Toronto, Ont.

CB MARKETPLACE

Kaar Hand-D-Phone contains 9 transistors and 3 diodes, has a superhet receiver. Input to final is under 100 mw, making it usable on License-Free Band. Weight is just under 2 lbs. 1 crystal transmit channel. Kaar Engineering, Palo Alto, Calif.



Lafayette HE-66 walkie-talkie has 4 transistors. It features a superhet receiver and 1 crystal T-R channel. Actual RF output claimed is 85 mw. Runs on 6 penlight batteries. \$19.95 each, 2 for \$38.95. Lafayette Radio, Syosset, N. Y.



WRL Spacemate gives you 9 transistors, weighs $2\frac{1}{2}$ lbs. and offers 2 crystal channels (11 or 16). The whip antenna telescopes to 46 inches. World Radio Labs, Council Bluffs, Iowa.



Globe Signal Optimizer is a multi-purpose instrument which gives you actual RF output in watts, percentage of modulation, harmonic readings, SWR, field-strength figures, etc. \$47.50. GC Electronics, Rockford, Ill.

BUILD 10-20 RADIO

Reg. U.S.
Pat. Off.

CIRCUITS AT HOME only
\$14.95 up

with the Deluxe
PROGRESSIVE RADIO "EDU-KIT"®

A Practical Home Radio Course

Now Includes

- ★ RECEIVERS
- ★ TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR
- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ SCHOOL INQUIRIES INVITED
- ★ Sold in 79 Countries



Training Electronics Technicians Since 1946

**YOU DON'T HAVE TO SPEND
HUNDREDS OF DOLLARS FOR A RADIO COURSE**

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and service. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL.

You will learn how to build radios, using regular schematics; how to wire and solder punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice trouble-shooting, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, Square Wave Generator and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 20 Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic background in Electronics and Radio, worth many times the small price you pay. The Signal Tracer alone is worth more than the price of the entire kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby; a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enter the way to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional radio technician.

Included in the "Edu-Kit" course are Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector circuits. There are not only professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build several different radio and electronics circuits guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifiers, volume controls and switches, etc.

In addition you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

FREE EXTRAS

• SET OF TOOLS

- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRNCH SET
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE & QUIZZES
- TELEVISION BOOK & RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB
- CONSULTATION SERVICE & FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

FROM OUR MAIL BAG

J. Statistis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends and made money. The 'Edu-Kit' paid for itself, I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

Sen Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Trouble-shooting Tester that comes with the Kit is really great, and finds the trouble, if there is any to be found."

UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER DIRECT FROM AD—RECEIVE FREE BONUS
RESISTOR AND CONDENSER KITS WORTH \$7

Choose From These Popular

"Edu-Kit" Models

10A: 10 Circuits \$14.95

15A: 15 Circuits \$19.95

16A: 16 Circuits

(Includes Printed Circuitry) \$22.95

#20A: 20 Circuits (Includes Printed Circuitry and 4 Advanced Circuits) \$26.95

MODEL desired..... Price.....

- Send "Edu-Kit" postpaid. I enclose remittance in full.
- Send "Edu-Kit" C.O.D. I will pay postage.
- Send me FREE additional information describing "Edu-Kits."

Name.....

Address.....

PROGRESSIVE "EDU-KITS" INC.

1186 Broadway, Dept. 546AE, Hewlett, N. Y.



* **FREE**

Fill in coupon for a **FREE** One Year Subscription to **OLSON ELECTRONICS' Fantastic Bargain Packed Catalog**—Unheard of **LOW, LOW, WHOLESAL** PRICES on Brand Name Speakers, Changers, Tubes, Tools, Hi-Fi's, Stereo Amps, Tuners, and other Bargains.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

If you have a friend interested in electronics send his name and address for a **FREE** subscription also.

OLSON ELECTRONICS
INCORPORATED

429 S. Forge Street Akron 8, Ohio

GET YOUR FIRST CLASS F.C.C. LICENSE IN EIGHT WEEKS!

Need your 1st class commercial license fast? The proven Grantham F. C. C. license course is now being offered in a special, accelerated eight (8) week course, intact—nothing is deleted. This intensive course has been highly successful, and is especially suited for those who have been employed in the electronics or broadcast industries. However, experience in electronics or broadcasting is not necessary; if you are willing to apply yourself, have above average intelligence and can study at an above average rate, this course is for you! Classes are small and meet for eight hours a day, with maximum personal instruction by our top-notch teacher. At present this accelerated course is being offered only at the Los Angeles Division of Grantham Schools. Write for free details today.

Grantham School Of Electronics
DEPT. C-38

1505 N. Western Avenue, Los Angeles 27, Calif.

CB MARKETPLACE



Seco 510 Transmitter Tester is a portable instrument which gives you a direct reading of percentage of amplitude modulation and actual RF output. High impedance input for handi-talkie checks. \$46.95. Seco, Minneapolis 19, Minn.



Lafayette TM-58 is an SWR bridge and RF power meter which can be inserted permanently in the coax line. It indicates up to 15 watts power, has a built-in dummy load, measures SWR from 1:1 to 4:1. \$7.95. Lafayette Radio, Syosset, N. Y.



Executive Frequency Synthesizer uses 23 crystals to give you frequency control on all CB channels. 24th position is spare. Self-contained power supply. Matches Executive 100 and 50 transceivers. \$159.50. Intl. Crystal, Oklahoma City.



Turner 355C CB microphone has a push-to-talk bar on the side which is gripped by all fingers rather than just one. It has an output level of -50db, response of 80-7,000 cps. \$12.50. Turner Microphone Co., Cedar Rapids, Iowa.

The Same School That Originated The RTS BUSINESS PLAN

...NOW
Proudly
Presents...

A SPECIAL COMPACT COURSE COVERING ALL THREE PHASES OF **ELECTRONICS**

The Entire Course Is Made
Up Of The Following:

- 35 LESSONS COVERING BASIC AND INTERMEDIATE ELECTRONICS
- 9 EQUIPMENT KITS COMPLETE WITH TUBES AND BATTERIES
- SOLDERING IRON
- 25 LESSONS COVERING THESE ADVANCED ELECTRONIC SUBJECTS:
 - Thyratron Tubes • Semiconductors • Electronic Symbols and Drawings • Voltage-Regulators • Electronic-Timers • Control Systems • X-Rays • Photoelectric Devices • Dielectric Heating • Geiger Counters • Pulse Circuitry • Clippers and Limiters • Multivibrators • Electronic Counters • Radar • Magnetic Amplifiers • Analog-Computers • DC Amplifiers • Digital Computers • Storage Systems • Input and Output Devices • Servomechanisms • Telemetering
- 60 EXAMINATIONS
- UNLIMITED CONSULTATION SERVICE
- KIT MANUALS
- DIPLOMA UPON GRADUATION

BASIC • INTERMEDIATE • ADVANCED

DESIGNED FOR THE BUSY MAN OF TODAY

This is MODERN training for the MODERN man. You'll find no "horse and buggy" methods here. Every page of this streamlined course is devoted to important Electronics principles and practical projects. You'll be amazed how fast you grasp Basic Electronics the RTS way. RTS has combined modern THEORY and PRACTICE to make this the finest training program of its kind available!

SATISFIES NOVICE, TECHNICIAN OR HOBBYIST

Whether you're new to Electronics or an old "pro," chances are you'll find this to be the ideal course for you. The novice will appreciate the completeness of the training. It starts with the most basic considerations, covering each important point thoroughly, yet concisely. The technician will enjoy the practical review of fundamentals and profit from the 25 advanced subjects covered.

RTS GIVES YOU "TOP MILEAGE" FOR YOUR TRAINING DOLLAR

The price quoted below buys EVERYTHING — there are no extras to pay for. RTS has gone "all out" to give you the best training value in America. Why pay hundreds of dollars for training such as we offer when it's available for this LOW PRICE? If you can find a better training bargain... BUY IT!

CAN BE COMPLETED IN MONTHS INSTEAD OF YEARS

Some students will complete this course with "Jet-Like" speed but we allow up to two years if your circumstances require it. You study at your own rate. You are ENCOURAGED but not pushed. You'll find the lessons professionally written. LET US SEND YOU ONE OF THESE LESSONS ALONG WITH YOUR CAREER BOOKLET SO YOU CAN SEE FOR YOURSELF. NO OBLIGATION!

AND MUCH MORE...

COMPLETE
COST...
INCLUDES ALL KITS,
TUBES, BATTERIES, ETC.
\$125.00*

* TERMS ALSO AVAILABLE
AS LITTLE AS
\$500 DOWN \$500 PER MONTH
**SAVE TIME — SEND
\$5.00 WITH COUPON**
YOUR FIRST LESSONS AND
KIT WILL BE RUSHED TO YOU
THE SAME DAY THEY ARE RECEIVED!

RTS' Membership In
The Association of
Home Study Schools
is your assurance of
Reliability, Integrity and
Quality of Training.



RTS ELECTRONICS DIVISION
815 E. ROSECRANS AVENUE
LOS ANGELES 59, CALIFORNIA

Est. 1922



**Rush
Coupon**

**NO
SALESMAN
WILL
CALL!**

DON'T LOSE OUT — FIND OUT!

RTS ELECTRONICS DIVISION Dept. E1-33
815 E. ROSECRANS AVENUE LOS ANGELES 59, CALIFORNIA
Rush me full information by return mail. (Please Print)

Name _____ Age _____
Address _____
City _____ Zone _____ State _____

ENROLL ME NOW **SEND MORE FACTS**

BIG MONEY IN THE 4 CORNERS OF THE WORLD!

in TELEVISION, RADIO,
ELECTRONICS, RADAR, SONAR
CHRISTY OFFERS
COMPLETE TRAINING!

Investigate the Christy Complete Course. Why be satisfied with less? CTS Shop Method Home Training makes learning easy. You learn by working with actual equipment. You receive Comprehensive training from the start. Can EARN AS YOU LEARN. You become qualified to open your own Electronics Repair business or to gain high pay as a TV, Radio, Electronics, etc. Technician.

19 TRAINING KITS INCLUDED!

You receive a Multi-Tester, Oscillator, Signal Tracer, Oscilloscope, Signal Generator, Electronic Timer, Regenerative Radio, 27" TV set (optional) and other valuable testing equipment. FREE BOOK and TWO FREE LESSONS yours for the asking! No obligation.

CHRISTY TRADES SCHOOL

Dept. T-2113, 3214 W. Lawrence Ave.
Chicago 25, Ill.

CHRISTY TRADES SCHOOL, Dept. T-2113
3214 W. Lawrence Ave., Chicago 25, Ill.

Please send me the 3 FREE BOOKS and Special Form for
PAYING LATER from EARNINGS MADE WHILE LEARNING.


NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____



Send for 3
FREE
BOOKS

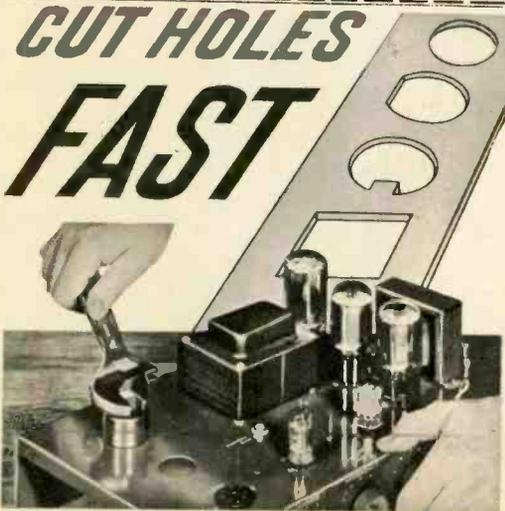

CUT HOLES FAST


GREENLEE CHASSIS PUNCHES

Make accurate, finished holes in 1½ minutes or less in metal, hard rubber and plastics. No tedious sawing or filing — a few turns of the wrench does the job. All standard sizes . . . round, square, key, or "D" shapes for sockets, switches, meters, etc. At your electronic parts dealer. Literature on request.

GREENLEE TOOL CO. 
2028 Columbia Ave., Rockford, Illinois



CB MARKETPLACE

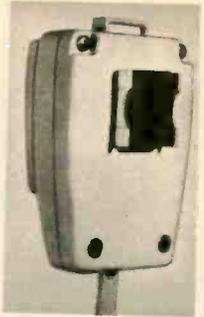Sonotone CM-30M Ceramic has a magnet on the back (shown) which holds it to the dash of your car or any other metal. Sensitivity rating is -49db, response is 60-7,000 cps. PTT button on top. Case is Implex plastic. \$9.70. Sonotone Corp., Elmsford, N. Y.



Big Mike Mark I is a CB microphone with a built-in transistor amplifier. Screwdriver adjustment on the side varies output level and frequency response (tone). The amplifier is operated by a mercury cell. Push-to-talk bar on side; -39db output. \$33.50. Instruments & Communications, Inc., Wilton, Conn.

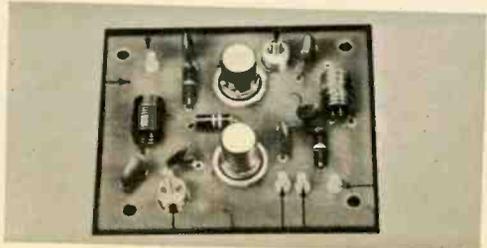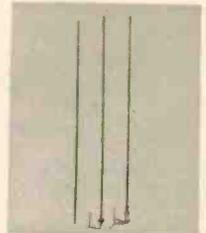Black Beauty Fiberglas mobile antennas (3 shown) have a solid black Fiberglas sleeving for weather protection. They are center-loaded, 48 inches high, can be mounted on cowl, fender or trunk. Antenna Specialists, Cleveland, Ohio.



WRL NA-27 Pre-Amplifier uses two Nuvistors (6CW4's) to give you up to 20db gain in signal strength, can be mounted inside most CB transceivers. Requires 90-125 VDC, 6 or 12 volts for filaments. \$11.95. World Radio Labs, Council Bluffs, Iowa.

Scott Stereo Tuner Kit Wins Rave Reviews from every Leading Hi-Fi Expert!

Just one year ago Scott introduced the LT-110 FM Stereo Tuner Kit. High Fidelity Dealers built this superb kit themselves, examined its many features, and recommended it without reservation. Enthusiastic kit builders deluged us with mail. Now the verdict is in from all the leading technical experts. Never before in the history of the industry has a single kit received such unanimous praise. We reprint a few excerpts below.



from Popular Electronics

A test model of the LT-110 was wired at POPULAR ELECTRONICS in just under five hours. Another 40 minutes was used for careful alignment and the tuner was "on the air." . . . The LT-110 met or exceeded all the manufacturer's detailed specifications on sensitivity, distortion, output level, a.c. hum, and capture ratio. . . . the audio response is excellent, being within ± 1 db, from approximately 20 to 16,000 cycles. . . . Channel-to-channel crosstalk is particularly excellent both in terms of uniformity and the fact that it holds up well above 10,000 cycles. . . . Frequency drift of the LT-110 from a cold start is extraordinarily low — less than 5 kc. The a.c. hum level (referred to 100% modulation) is low and exceeds the manufacturer's rating by 5 db. . . . It's difficult to imagine a kit much simpler to assemble than the LT-110. The full-color instruction book eliminates just about the last possible chance of wiring errors. . . . From a plain and simple operational standpoint, the LT-110 works well and sounds good."

Popular Electronics, Oct. 1962

from ELECTRONICS WORLD

"Construction time for the unit we tested was 6½ hours, without alignment. . . . in listening tests, the tuner showed its high useable sensitivity to good advantage. Using an indoor antenna which produced marginal signal to noise ratios on most other tuners we were able to get noise-free, undistorted stereo reception."

Electronics World, Nov. 1962

from AUDIO

"The LT-110 (is) so simple to build that we unhesitatingly recommend it for even the novice. . . . We found that the useable sensitivity (IHFM) was 2.1 uv. . . . a fine stereo tuner and an unusually easy kit to build."

Audio, April 1962



from RECORD GUIDE

"It seems to me that every time I turn around I am building another of H. H. Scott's kits. And each time I end up praising the unit to the skies.

The Scott instruction books should be a model for the industry. They feature full-color, step-by-step, illustrated directions. Each resistor or other component is shown in the

progressive phases in its color code and in its proper position. . . .

This tuner kit has to be ranked on the same plane as H. H. Scott's factory-wired units. It is an excellent product. . . . very likely to give long, trouble-free service."

American Record Guide, Sept. 1962



Now Sonic Monitor* Added . . .

Scott's unique Sonic Monitor has now been added to the LT-110. This fool-proof stereo signaling device tells you audibly when you are tuned to a stereo station.

- LT-110 FM Stereo Tuner Kit . . . \$159.95
- LK-48 48-Watt Stereo Amplifier Kit . . . \$124.95
- LK-72 80-Watt Stereo Amplifier Kit . . . \$159.95
- LC-21 Stereo Control Center Kit . . . \$99.95
- LK-150 130-Watt Stereo Power Amplifier Kit . . . \$169.95

*Patent Pending. (All prices slightly higher West of Rockies.)



H. H. Scott, Inc. 111 Powdermill Road
Maynard, Massachusetts Dept. 130-3

Rush me complete details on your LT-110 FM Stereo Tuner Kit and other superb Scottkits. Be sure to include your new free Stereo Record, "The Sounds of FM Stereo" showing how new FM stereo sounds, and explaining important technical specifications.

Name _____
Address _____
City _____ State _____

Export: Morhan Exporting Corp., 458 Broadway, N.Y.C.
Canada: Atlas Radio Corp., 50 Winzoid Ave., Toronto

--for a CB system that's got it at both ends!



the **BIG STICK**
at your
base
station

VIP
top loaded
4' whip on your
mobile unit

These handsome all-fiberglass antennas combine inherent protection against precipitation static, corrosion, rust — with professional quality performance in the CB range.

the **BIG STICK**, style 176 — 18' vertical antenna
VIP — style 173 — 4' top loaded whip

COLUMBIA PRODUCTS COMPANY
SHAKESPEARE CO. SUBSIDIARY, COLUMBIA, S. C.



THE GLOBE STAR CITIZENS BAND TRANSCIVER

The pacesetter on today's CB transceiver market. Super circuitry eliminates adjacent channel

interference, gives quieter operation. 16 tube power. Heavy duty chassis built to take it. Send for complete specs now. Use coupon below.



FREE WHEN YOU BUY the STAR

The Globe Citizens Band Book tells you everything you must know to operate CB. What you can and can't do. Installation tips, which antenna, base or mobile, CB language. It's all here. A regular 2.00 value, compiled by experts. Free with every CB transceiver from Globe exclusively.

SEND \$1.00 FOR A COPY NOW...

Like a copy of this great book now? Use the coupon below and enclose 1.00 cash or money order for each copy.

GC ELECTRONICS CO., 400 S. Wyman, Rockford, Illinois

Rush me the Globe Star Spec sheet Name _____

Send me _____ copies of the CB Book. I enclose 1.00 for each copy. Address _____

City _____ State _____



KUHN

"LEADERS IN SPECIALIZED RECEIVING EQUIPMENT"

MOBILE
FIXED
CONVERTERS

- POLICE
- FIRE
- COMMERCIAL
- CITIZEN'S BAND

345A
Complete
\$29.95



A new high gain Crystal Controlled Converter. Excellent sensitivity... Rugged construction... Easy to install. Designed for standard transistor car radios. Requires no high voltage supply. 2-3 MC or 150-162 MC.

KUHN CONVERTERS... the most advanced line... designed for optimum performance.

348A
Complete
\$34.95



Transistorized, directly tunable Converter. Powered with self-contained mercury cell. Excellent sensitivity and stability. Designed for car, home or portable receivers. Two types available: Aircraft VHF, 115-130 MC or 150-162 MC.

344A
Complete
\$23.95



A new low cost Crystal Controlled Converter designed for use with standard transistor car radios. Operates directly from 12V DC. Rugged construction. Good sensitivity. Range 2-3 MC.

ORDER TODAY or SEND FOR FREE CATALOG... containing complete information on a full line of: CONVERTERS AND RECEIVERS FOR EVERY APPLICATION

315A Complete \$14.95



A low cost Tunable Converter for any 10 MC area of: 26-34 MC, Aircraft VHF, or 150-160 MC. Easily installed. For use with home or auto sets. **316A Directly Tunable Converter.** Available in four ranges: 26-30 MC, 30-50 MC, 115-130 MC, or 150-160 MC. Complete **\$21.95**



20 GLENWOOD
CINCINNATI 17,
OHIO

STATEMENT REQUIRED BY THE ACT OF AUGUST 24, 1912, AS AMENDED BY THE ACTS OF MARCH 3, 1933, JULY 2, 1946, AND JUNE 11, 1960 (74 STAT. 208) SHOWING THE OWNERSHIP, MANAGEMENT, AND CIRCULATION OF

ELECTRONICS ILLUSTRATED published bi-monthly at Greenwich, Conn., for October 1, 1962.

1. The names and addresses of the publisher, editor, managing editor, and business managers are: Publisher, Fawcett Publications, Inc., Greenwich, Conn.; Editor, Robert G. Beason, Oradell, N. J.; Managing Editor, Larry Eisinger, Staten Island, N. Y.; Business Manager, Gordon Fawcett, Greenwich, Conn.

2. The owner is: (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual member, must be given.) Fawcett Publications, Inc., Greenwich, Conn.; W. H. Fawcett, Jr., Norwalk, Conn.; Marion Bagg, Kansas City, Mo.; Roger Fawcett, New York, N. Y.; V. D. Fawcett, Greenwich, Conn.; M. B. Fawcett, Norwalk, Conn.; Gordon W. Fawcett, Greenwich, Conn.; Gloria Leary, Santa Monica, Cal.; V. F. Kerr, Bakersfield, Cal.; Allan M. Adams and Jack B. Adams as trustees under the trust agreement with Eva F. Roberts dated July 3, 1959, Greenwich, Conn.; H. A. Fawcett, New York, N. Y.; Roscoe Kent Fawcett, Reno, Nevada, M. F. Fawcett, Greenwich, Conn.

3. The known bondholders, mortgagees, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.) None.

4. Paragraphs 2 and 3 include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, and also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner.

5. The average number of copies of each issue of this publication sold or distributed, through the mails or otherwise, to paid subscribers during the 12 months preceding the date shown above was: (This information is required by the act of June 11, 1960, to be included in all statements regardless of frequency of issue.) 207,089.

GORDON FAWCETT,
Business Manager

Sworn to and subscribed before me this 20th day of September, 1962.

[SEAL] LILLIAN M. KLEIN

(My commission expires April 1, 1963)

TV-RADIO Servicemen or Beginners...

Send for *Coyne's* 7-Volume Job-Training Set on 7-Day **FREE TRIAL!**



The First
Practical
TV-RADIO-
ELECTRONICS
Shop
Library!

Answers ALL Servicing Problems QUICKLY... Makes You Worth More On The Job!

Put money-making, time-saving TV-RADIO-ELECTRONICS know-how at your fingertips—examine Coyne's all-new 7-Volume TV-RADIO-ELECTRONICS Reference Set for 7 days at our expense! Shows you the way to easier TV-Radio repair—time saving, practical working knowledge that helps you get the BIG money! How to install, service and align ALL radio and TV sets, even color-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick." No complicated math or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home. Over 3000 pages; 1200 diagrams; 10,000 facts!

SEND NO MONEY! Just mail coupon for 7-Volume TV-Radio Set on 7-Day **FREE TRIAL!** We'll include the **FREE BOOK** below. If you keep the set, pay only \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. Cash Price only \$24.95. Or return set at our expense in 7 days and owe nothing. Either way, the **FREE BOOK** is yours to keep. Offer limited, so act NOW!

Like Having An Electronics Expert Right At Your Side!

VOL. 1—EVERYTHING ON TV-RADIO PRINCIPLES! 300 pages of practical explanations; hundreds of illustrations.

VOL. 2—EVERYTHING ON TV-RADIO-FM RECEIVERS! 403 pages; fully illustrated.

VOL. 3—EVERYTHING ON TV-RADIO CIRCUITS! 336 pages; hundreds of illustrations, circuit diagrams.

VOL. 4—EVERYTHING ON SERVICING INSTRUMENTS! How they work, how to use them. 368 pages; illustrated.

VOL. 5—TROUBLESHOOTING! Covers all types of sets. 437 pages; illustrations, diagrams.

VOL. 6—TV CYCLOPEDIA! Quick and concise answers to TV problems in alphabetical order, including UHF, Color TV and Transistors; 668 pages.

VOL. 7—TRANSISTOR CIRCUIT HANDBOOK! Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages.

BOOKS HAVE BRIGHT, VINYL CLOTH WASHABLE COVERS

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
1455 W. Congress Parkway, Dept. 33-E1, Chicago 7, Ill.

Yes! Send me COYNE'S 7-Volume Applied Practical TV-RADIO-ELECTRONICS Set for 7-Days **FREE TRIAL** per offer. Include "Patterns & Diagrams" book **FREE!**

Name Age

Address

City Zone State

Check here if you want Set sent C.O.D. Coyne pays postage on C.O.D. and cash orders. 7-Day Money-Back Guarantee.

"LEARNED MORE FROM THEM THAN FROM 5 YEARS WORK!"

"Learned more from your first two volumes than from 5 years work."

—Guy Bliss, New York

"Swell set for either the serviceman or the beginner. Every service bench should have one." —Melvin Masbruch, Iowa.

FREE DIAGRAM BOOK!

We'll send you this big book, "150 Radio-Television Picture Patterns and Diagrams Explained" **ABSOLUTELY FREE** just for examining Coyne's 7-Volume Shop Library on 7-Day **FREE TRIAL!** Shows how to cut servicing time by reading picture-patterns, plus schematic diagrams for many TV and radio sets. Yours **FREE** whether you keep the 7-Volume Set or not! Mail coupon **TODAY!**



Coyne

Educational Book Publishing Division
ELECTRICAL SCHOOL
1455 W. Congress Parkway Dept. 33-E1, Chicago 7, Illinois

A. C. Household Electricity Anywhere ... in your car, boat or plane.

ATR

PRODUCTS FOR MODERN LIVING

ATR PLUG-IN TYPE PORTABLE INVERTERS*

MODELS
6-RMF (6 volts) 60 to 80 watts. Shipping weight 12 lbs. **DEALER NET PRICE** \$33.00
12T-RME (12 volts) 90 to 125 watts. Shipping weight 12 lbs. **DEALER NET PRICE** \$33.00
*Additional Models Available

Operates Standard A.C.
• Record Players
• Dictating Machines
• Small Radios
• Electric Shavers
• Heating Pads, etc.

NO PRINTED CIRCUITRY

Excellent Tone, Volume, and Sensitivity!
Compact, yet powerful. Fits all trucks, station wagons, most cars and boats. Just drill a 3/8 inch hole in roof and suspend the one-piece unit (aerial, chassis and speaker) in minutes. Watertight mounting assembly holds antenna upright. Yoke-type bracket lets you tilt radio to any angle.
Extra-sensitive radio has 6 tubes (2 double-purpose), over-size Alnico 5 PM speaker for full, rich tone. Big, easy-to-read illuminated dial. Fingertip tuning control. Volume and tone controls. 33-in. stainless steel antenna. Neutral gray-tan enameled metal cabinet, 7 x 8 1/2 x 4 in. high over-all. Shipping weight 10 1/2 lbs.

Model TR-1279—12A for 12V Dealer Net Price.....\$41.95
Model TR-1279—6A for 6V Dealer Net Price.....\$41.95

See your Electronic Parts Distributor...
Write Factory for Free Literature...

ATR ELECTRONICS, INC.
Formerly, American Television & Radio Co.
Quality Products Since 1931
ST. PAUL 1, MINNESOTA—U.S.A.



studying antenna system in Tri-State's electronics lab

become electronics engineer in 27 months

College graduates enjoy higher income... advancement. Become a graduate Engineer. Industry likes Tri-State graduates. Major corporations visit us regularly to interview and employ seniors. **BACHELOR OF SCIENCE DEGREE IN 27 MONTHS** in Electrical (Electronics or Power major), Mechanical, Aeronautical, Chemical, Civil Engineering. In 36 MONTHS a B. S. degree in Business Administration. One-Year Drafting-Design Certificate Program. Enrollment limited. Small classes. Campus. Well-equipped labs. Modern dorms. New library. Founded 1884. Moderate costs. Enter June, September, January, March. Write J. A. McCarthy for Catalog and "Your Career in Engineering and Commerce" Book.

TRI-STATE COLLEGE

4833 College Avenue • Angola, Indiana

BEST BUYS IN STEREO AND MONO HI-FI

Transistorized Stereo/Mono 4-Track Tape Deck RP100 Semikit (electronics in kit form) \$299.95 Wired \$399.95



New Stereo FM Multiplex Tuner ST97 Kit \$99.95* Wired \$149.95*



FM-AM Stereo Tuner ST96 Kit \$89.95* Wired \$129.95* *Incl. FET

70-Watt Integrated Stereo Amplifier ST70 Kit \$99.95 Wired \$149.95



40-Watt Integrated Stereo Amplifier ST40 Kit \$79.95 Wired \$129.95

28W Integrated Stereo Amplifier HFB1 Kit \$69.95 Wired \$109.95



FM Tuner HFT90 Kit \$39.95 Wired \$65.95 Incl. FET Metal Cover \$3.95



AM Tuner HFT94 Incl. FET Kit \$39.95 Wired \$65.95



Stereophonic Dual Preamp ST84 Kit \$59.95 Wired \$89.95

Stereo Power Amplifiers Kit Wired
70W HF87A: \$74.95 \$114.95
100W HF89A: \$99.50 \$139.50
28W HF86: \$43.95 \$ 74.95



FM-Multiplex Autodaptor MX99 Kit \$39.95 Wired \$64.95 Cover Optional, \$2.95 (Patents Pending)



Bookshelf Speaker System HFS1 Kit \$39.95 Wired \$47.95

BEST BUYS IN CITIZENS TRANSCEIVERS, HAM GEAR, RADIOS

Citizens Band Transceivers 770 Series from Kit \$79.95 Wired \$109.95



U. S. Pat.



60W CW Transmitter #723 Kit \$49.95 Wired \$79.95

Walkie-Talkie Citizens Band Transceiver #740 Kit \$54.95. Wired \$79.95. Complete with rechargeable battery & charger.



BEST BUYS IN TEST EQUIPMENT

Metered Variable Auto-Transformer AC Bench Supplies Model 1073 (3 amps) Kit \$35.95 Wired \$47.95 Model 1078 (7 1/2 amps) Kit \$42.95 Wired \$54.95



Peak-To-Peak VTVM #232 & Uni-Probe® (U.S. Pat.) Kit \$29.95 Wired \$49.95



VTVM #221 Kit \$25.95 Wired \$39.95

DC-5 MC 5" Scope #460 Kit \$79.95 Wired \$129.50



General Purpose 5" Scope #427 Kit \$69.95 Wired \$109.95

Tube Tester #625 Kit \$34.95 Wired \$49.95



RF Signal Generator #324 Kit \$26.95 Wired \$39.95



1000 Ohms/Volt V-O-M #536 Kit \$12.90 Wired \$16.90




6- & 12V Battery Eliminator & Charger #1050 Kit \$29.95 Wired \$38.95 Extra-filtered for transistor equip. #1060 Kit \$38.95 Wired \$47.95



AC Volt-Watt Meter #261* Kit \$49.95 Wired \$79.95 *Formerly called #260



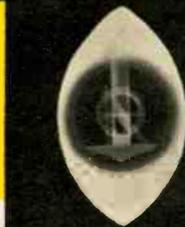Multi-Signal Tracer #145A Kit \$19.95 Wired \$28.95



EICO

EXCELLENCE IN CREATIVE ELECTRONICS

Over 2 MILLION EICO instruments in use throughout the world. Compare, take them home — right "off the shelf" — from 2000 neighborhood dealers, most of whom offer budget terms.



EICO, 3300 N. Blvd., L.I.C. N.Y. E1-3
 Send free Catalog describing over 106 top-quality products, free Stereo Hi-Fi Guide, free Short Course for Novice License, name of nearest EICO dealer. Send new 36-page GUIDEBOOK TO HI-FI for which I enclose 25¢ for postage & handling.

Name _____
 Address _____
 City _____ Zone _____ State _____
 Add 5% in the West

what the **FCC**

thinks of **CB**

IN a little less than five years the Citizens Radio Service has changed from an almost unknown band to one of the liveliest and most talked-about media in the world of communications. A few thousand licensees of 1958 have grown now to almost 400,000. Tens of thousands of small businesses and private citizens derive incalculable benefits from Citizens Band radio, which at once offers a fast, modern means of communication with modestly priced equipment and a simplified licensing procedure. It is truly radio for the average man and the independent merchant. The Federal Communications Commission can congratulate itself for originating a service so useful to so many, but by the same stroke of genius it also created problems in rules-enforcement of a magnitude never before seen. It was not long after the birth of CB that Commissioners and the FCC staff began asking themselves what they could do to regulate the new service without destroying its usefulness. The question did not lend itself to easy solution. It still has not been answered with finality, and probably never will be. But the FCC has definite opinions on the Citizens Radio Service as it now stands and some clear-cut intentions about the near future. Among them:

- Most licensees are using their stations for the purposes intended by the rules.
- The Citizens Band is considered a special "problem band" insofar as Class D stations are concerned.
- Another revision of the rules is under way, though no drastic changes are imminent for CB (see below).
- CB is declining in popularity amongst radio *hobbyists*.
- No new frequency allocations are contemplated and CBers *will be fortunate to hold those they now have*.

The last item may come as a surprise to many CBers—that those who assign and police the radio frequencies would contemplate a squeeze on the band when the number of licensees is expanding so rapidly. Yet it does at this writing appear to be a definite, though vague, threat. The underlying consideration at this point is whether those frequencies now allotted to the Citizens Band are being used properly and are providing the service needed.

(Continued on next page)

what the FCC

The actual make-up of the Federal Communications Commission—who it is and what it does—is the source of no little confusion, even on the part of those who hold radio licenses granted by the agency. The Commission itself is made up of seven men who are given political appointments by the President. One Commissioner serves as chairman, the current one being Newton N. (“Wasteland”) Minow. The Commissioners have the job of formulating policy and doing other such high-level work. Working for the Commission is the FCC staff—such men as Ben F. Waple, Acting Secretary, and Ivan H. Loucks, who now heads up amateur and Citizens Band radio operations. The staff carries out the Commission’s policies, doing the paperwork, making lower-level decisions, running a monitoring program . . . and writing citations.

The Commissioners, as a group, never have made any pronouncement regarding Citizens Band radio—or the Citizens Radio Service, as it is known in official circles. However, last summer one Commissioner, Frederick W. Ford, speaking in Parkersburg, W. Va., at the Annual Tri-State Citizens Band Round-up, aired some of his own views on the band that coincide with those held by members of the FCC staff (they have said). Presumably, other Commissioners also agree, since there has been no postscript from them.

“It seems obvious,” said Mr. Ford, “that if the (CB) service gets so out of hand that the Commission is unable to cope with it; if because of extreme numbers of users and general lack of care for restrictions the service virtually destroys itself, it might become necessary to withdraw the 11-meter frequencies from the service.”

Mr. Ford hastened to tell his listeners, who must have been a little shook up by this time, that such an eventuality seemed drastic and unlikely. But, on the other hand, he continued, “it would be most difficult to justify the extensive and expensive field force which might be required to police the band.”

The speech, which ran to seven close-typed pages, was a transparent attempt to make friends with the CBers at the

roundup, to enlist their help and cooperation in steering CB in the right direction. It was a friendly talk and no doubt had the desired effect, but the carefully gloved hand had to make a momentary appearance.

“Your service has come in for a good deal of attention lately,” Mr. Ford concluded, “and my parting (wish), which I hope will be taken with all the good will with which it is given, is that the future attention which (CB) receives will be all in the nature of commendation and not condemnation.”

Mr. Ford’s journey to Parkersburg was not the first made by the FCC people to Citizens Band gatherings. For more than two years the FCC has been steering on a friendship-and-education tack. Administrators (such as Mr. Loucks) and engineers alike have talked to CBers in groups large and small, telling them where the service had gone wrong and where they hope to see it arrive in the future. The public relations work has not been in vain. Most Citizens Band licensees now view the FCC with friendly feelings, replacing the all-they-do-is-write-citations hostility of the past. The net result has been a vast improvement in operating practices and conditions on the band.

In the words of Messrs. Waple and Loucks, “The Commission believes that by and large most Citizens Radio station licensees are using the stations for the purpose intended by the rules, i.e., short-distance communications necessary to the conduct of business or personal activities.” But then they add: “Unfortunately, however, some licensees operate their Class D stations for purposes other than these, in violation of the rules, and they threaten the utility of the service for the intended purposes.”

The primary violation, they say, and nearly any CBer could guess, is the use

thinks of CB

of the band for hobby-type communications. This is what they call "amateur-radio-type of operation with contacts for the sake of contacts, including discussions regarding carrier frequency, modulation, antennas, signal strength and checking into local nets."

"In some parts of the country," say the two FCC staff members, "stations are used for social conversations that can and should be handled over regular wire-line telephones."

The FCC, pointing to the large number of licensees, resulting from simple eligibility requirements and low-cost equipment, has noted that a small minority of CBers are causing most of the trouble. Less than 10 per cent of the licensees are responsible for 85 per cent of all violations, according to their figures.

As for the hobbyists, Messrs. Loucks and Waple have this to say: "It is expected that after the novelty wears off many of these licensees will settle down, as they already have in some areas, to conservative operation more in line with the rules."

Rules changes or new rules are put together in the form of proposals by the FCC staff and then presented to the Commissioners for adoption or not. The latest proposed rules changes have now been announced. The FCC says there's nothing *radical* about them, but that's *their* term. For a full discussion see CB CORNER in this issue.

At the end of 1962 approximately 380,000 CB licenses had been issued, of which 315,000 were for Class D stations. For the first nine months of the year, an average of 10,564 licenses was granted each month. Figures for the later months are not yet available.

"With no let-up in Class D applications and with some months running one or two thousand over previous months, the popularity of CB appears to be gaining somewhat," Mr. Loucks and

Mr. Waple state. "In the last 12 months the lowest number of applications received for Class D stations was about 10,000 (December 1961) and the highest number was 17,543 (August 1962). The application receipts during each month of 1962 were some 4,000 more than during the same month of 1961."


The mushrooming licensing rate has been accompanied, inevitably, by a jump in citations (also due, to some extent, to stricter enforcement). In one three-month period (April-June) of 1962 the FCC wrote an average of 450 citations every month, compared to about 250 a month a year earlier.

"Apparently applications for licenses solely for hobby-type activity are falling off," the FCC says. "The number of applications appears to be increasing for the combination personal-and-small-business type of activity where the wife takes an active part in her husband's business. Small corporations, associations, volunteer fire departments, auxiliary police, Civil Defense organizations, parcel delivery and taxicab operations now account for many applications."

Ham-type chatter and skip contacts, though major headaches, are not the most serious problems in CB, according to the Commission's view. The worst-offense title goes to totally unlicensed operation of CB equipment and the "lending" of call signs to friends. The FCC's stepped-up monitoring program has hooked more than a few violators on these rules infractions. The new rules changes, the FCC says, will make these and other violations more apparent when they occur (in addition to facilitating the understanding of the rules by licensees).

To help it enforce the rules, the Commission encourages the organization of CB groups interested in self-regulation. "Clubs," says the Commission, "when properly organized and conducted are of help because they discuss the Commission's rules and thus give members a better understanding of how they should operate their stations. They also call each other's attention to faults in their equipment and operating practices."

CB SIGNAL BOOSTER

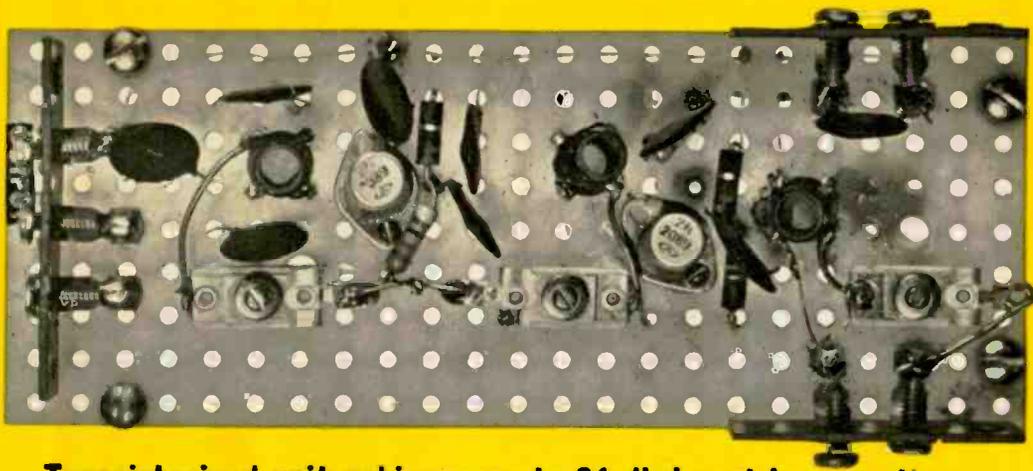

Transistorized unit achieves up to 24 db boost in reception.

By Kevin Redmond, K2HTZ (Head, Semiconductor Applications Laboratory, Amperex Electronics)

YOU can add greater sensitivity, lower cross-modulation, and quieter operation to your rig with the twenty-four db of gain provided by this versatile CB Signal Booster. Low sensitivity receivers use its high gain to improve sensitivity while high sensitivity receivers can use the gain to permit higher squelch settings and therefore quieter reception. Output impedance taps on the booster allow matching to a variety of antennas and receiver input stages. Satisfactory performance is delivered with a DC supply range of six to twelve volts assuring adaptability to various supply systems.


Construction has been simplified by mounting all parts on a perforated board. When completed, the board can be used as a subchassis mounted inside a CB rig or in a Minibox using stand-offs as mounting supports. The three coils are closewound on paper coil forms with the taps at the end of the coil nearest the mounting. Be careful not to bend the lugs too much when mounting the coil as the form may separate from its mounting base. The layout shown in the pictorial should be followed closely, except that the socket of transistor Q1 should actually be installed between L1 and L2 for the shortest possible leads. It's important that the "ground side" of trimmer capacitors C1, C2 and C3 be connected to the bottom end (D) of coils L1, L2 and L3. See photo. If this is not done hand capacitance effects will make tuning difficult.

Coupling capacitors C4 and C5 carry RF and must be kept away from ground leads and RF circuitry or coupling from the capacitor body will reduce gain or cause oscillation.

DC Check. Once the unit has been completed, check the DC operating point first. This can be done by measuring the DC

Photo of author's prototype of Booster differs slightly from pictorial below. Most wires are run on reverse side of perforated board and transistor Q1 is located between L1 and L2. The photo should be followed, particularly in the placement of trimmers C1, C2 and C3.

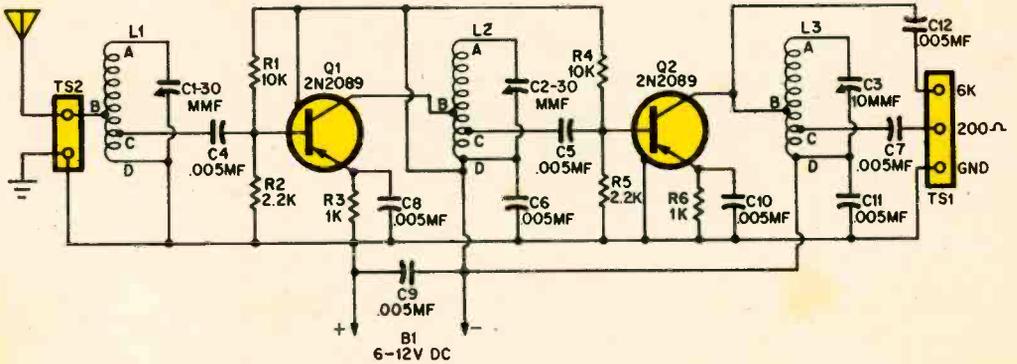In the pictorial below, for the sake of clarity the component and other interconnecting leads are shown longer than required. In this unit, as in all RF devices, leads should be short and run direct as possible. The taps on the coils should be connected to the lettered lugs.




R1, R4—10,000 ohms resistor, 1/2 watt, 10%
 R2, R5—2,200 ohms resistor, 1/2 watt, 10%
 R3, R6—1,000 ohms resistor, 1/2 watt, 10%
 C1, C2, C3—2-30 mmf trimmer capacitor
 C4 to C12—.005 mf low-voltage ceramic discs or .0047 mf tubular types


PARTS LIST

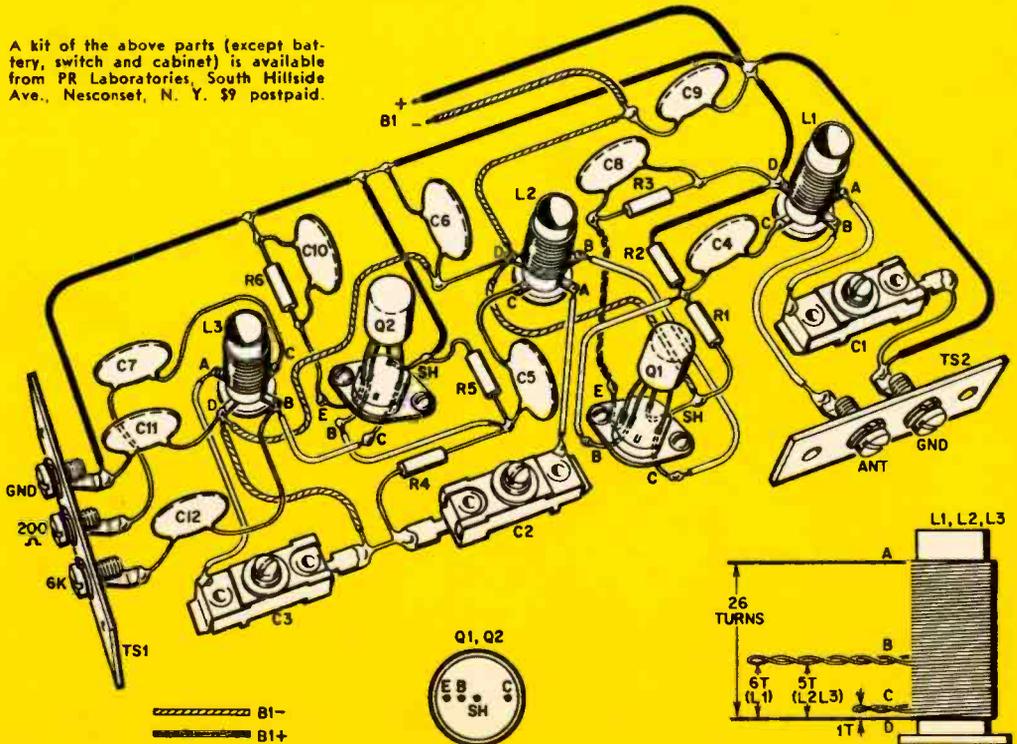Q1, Q2—2N2089 transistor (Amperex)
 L1—285" dia. Cambion coil form, SPC-2J4L, slug removed; 26 turns closewound #28 enam. wire tapped at 1 and 6 turns
 L2, L3—Same form as L1; 26 turns

tapped at 1 and 5 turns
 TS1—3-screw terminal strip
 TS2—2-screw terminal strip
 Misc. — Perforated board (approx. 8 1/2" x 2 1/2"); flea clips; plastic cabinet two 4-lead transistor sockets, hardware, etc.

A kit of the above parts (except battery, switch and cabinet) is available from PR Laboratories, South Hillside Ave., Nesconset, N. Y. \$9 postpaid.



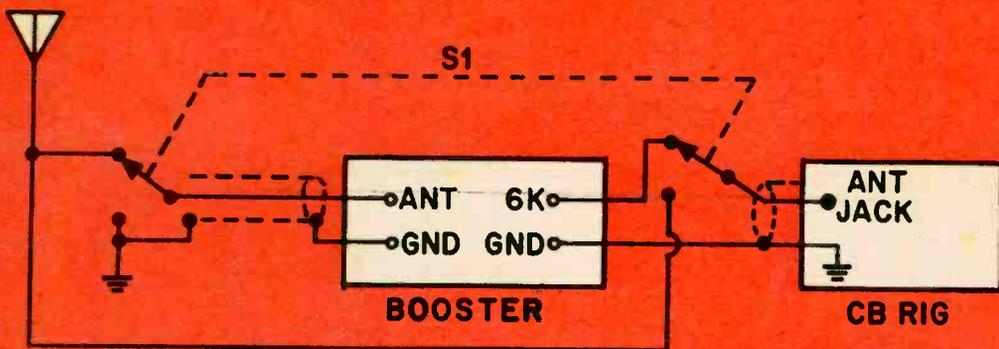

To protect the Booster during transmission periods, a double-pole, double-throw slide switch is required in addition to the transceiver's normal P-T switch. See text for specific details.

voltage across R3 and R6. At a supply voltage of 6 volts, the voltage across each of these resistors should be approximately 1 volt. Or, with a supply voltage of 12 volts, the reading will be about 2 volts. The voltages across R2 and R5 should be .25 volts higher than those across R3 and R6.

Tuning the Booster. To adjust the tuning capacitors (C1, C2, C3) connect the Booster's 6K output and Gnd terminals to a short length of coax cable fitted with a plug to match the antenna input jack of the CB receiver. The receiver should be tuned to a center band channel. A transmitter on the same channel can be used as the signal source if it is kept at least 10 feet away from the Booster. No antenna should be used for the booster at this step. Capacitors C1, C2 and C3 should be now adjusted for maximum signal as determined audibly or read by the receiver's S-meter.

If a signal generator is used as the signal source, an 18,000 ohm resistor should be used between the generator's hot lead and antenna terminal of the Booster. In addition, a 12 mmf capacitor should be installed across the antenna and ground terminal of TS2.

Using the Booster. With transceivers, special precautions must be taken not to damage the booster's transistors when transmitting. The simplest solution is to connect a DPDT switch as shown in the diagram. This switching arrangement will work with practically

all receiving systems. The booster input is shorted during transmission when the DPDT switch is thrown to the *xmit* position. Use a DPDT slide switch or other low capacitance type as both the RF input and output of the booster go through it. S1 is shown set for *receive*.

Standard antennas, including whips, are connected to TS2. An antenna with a loading coil or one which reflects a low impedance because of mismatch or overlong transmission line is connected directly to tap C on L1. Either connection is made via the slide switch mentioned above.


If your rig is transistorized, the 200-ohm output terminal on the Booster can connect directly to the base of the RF input transistor. As an alternative on a handi-talkie type rig, the 6K output of the Booster can be connected directly to the whip antenna. Gnd on the Booster connects to the ground of the CB unit. Super-regen receivers will probably only be able to operate with the direct antenna connection.

There are several inexpensive handi-talkies which use the super-regen receiver stage as their transmitter. Don't expect the Booster to be of much help.

When receiving strong stations, the Booster may provide excessive amplification and cause blocking in the CB rig's input stage. This problem is easily solved by reducing antenna length or by dropping the voltage feeding the Booster.

HOW TO GET RID OF

CB TVI

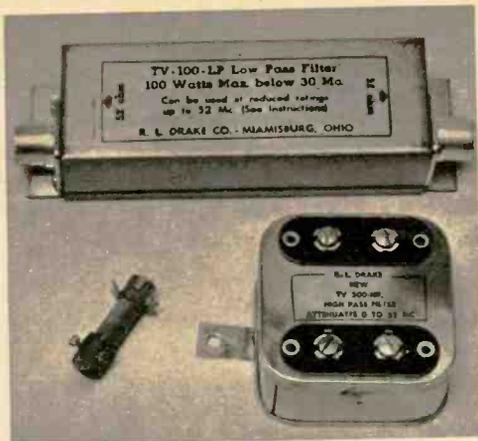

Ten bucks plus a few minutes of work will rid you of that nagging interference problem.

By Bert Mann

WHAT do you do when you get complaints about television interference (TVI)? Many Citizens Banders tremble when they hear the term. Actually, a CB rig's 5-watt input creates only marginal TVI and its elimination is neither difficult nor costly.


CB TVI has two primary causes: second harmonic radiation from the transmitting antenna and TV receiver overload. In addition to a 27-mc signal, your transmitter produces harmonics—multiples of 27 mc. The second harmonic is 54 mc, which falls on TV channel 2. It can cause a herringbone pattern. TV receiver blocking, which produces a herringbone or a negative (reversed) picture, is caused when your 27-mc signal


gets into and overloads the TV's tuner.

To eliminate harmonic output of your transmitter, start with a good ground. Without it, all efforts will be in vain. Use a ground rod or a cold-water pipe and a grounding clamp. Scrape the pipe clean or attach your ground wire (a grounding braid or No. 8 electrical wire) to the bright-metal part of a valve for good contact.

A 54-mc trap installed between the transmitter's final output tank circuit and the coax antenna connector, as close as possible to the connector, will prevent most harmonic power from being fed to the antenna. The best trap is a specific tunable coil (Lafayette Radio HP-59; 49¢) shunted by a 25-mmf, 600-volt (or

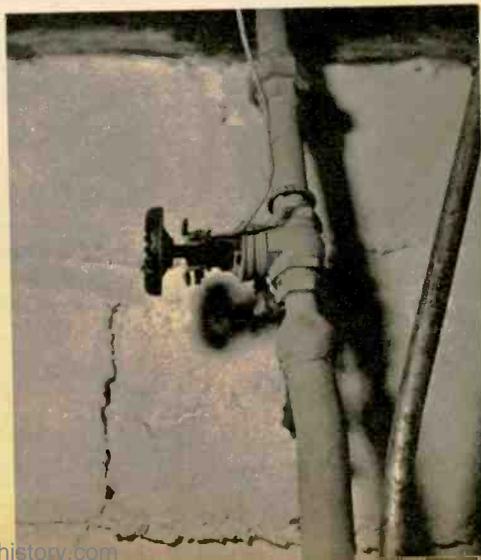Regardless of the transceiver type, the first requirement for elimination of TVI is a heavy ground wire from the set (see photo below) to a cold-water pipe (photo right) or ground rod.



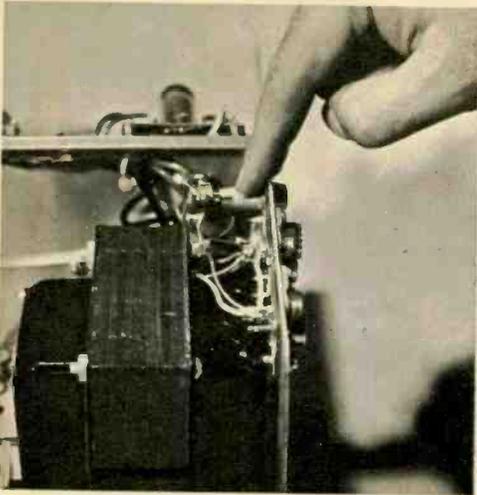

A 54-mc trap (small cylinder just under finger) is installed in the transmitter's output lead as close as possible to the coaxial jack of the rig.

higher) disc capacitor. With the rig grounded, the antenna connected and the transceiver cabinet in place, adjust the trap's slug for minimum TVI on your own TV receiver.

A low-pass filter—a device which passes the CB signal but attenuates its harmonics—will eliminate any remaining harmonic interference. Good low-pass filters are made by several manufacturers (we show R. L. Drake's TV-100-LP; \$5.95) but all must be attached to the transmitter cabinet, permitting a good ground bond between the two. The coax between filter and transmitter should be as short as possible, with the coax shield soldered to the connectors.

Any TVI that remains is caused by TV receiver blocking due to your fundamental 27-mc signal. The answer is a high-pass filter to prevent the signal from entering the TV tuner. This installation is the TV set owner's responsibility, of course, but you can assist his serviceman by seeing that he gets the right filter correctly installed. Our recommendation is R. L. Drake TV-300-HP, which sells for \$3.97 (it is shown in our photos).


An HP filter must be installed *inside* the TV on the tuner (*not* at the antenna terminals) and grounded to the tuner. In an AC/DC receiver, the filter's case is grounded through a .005-mf capacitor.

With just an evening's work and a little care you can banish TVI forever!




A low-pass filter will give you maximum harmonic attenuation if it is installed properly on your transceiver. You must have a firm bond between the cabinet and filter. It may be necessary to scrape paint off the cabinet at mounting spot.

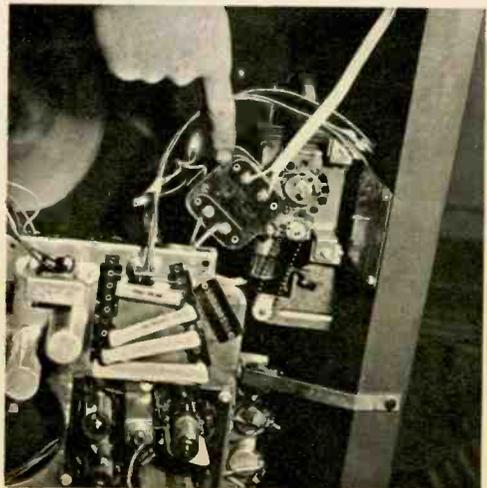The final ingredient of our anti-TV I formula is a high-pass filter (at right) for installation in television sets. It must be mounted as close as possible to the input of the TV tuner; its case is grounded to tuner via a special grounding tab.



Switch to a Better Mike

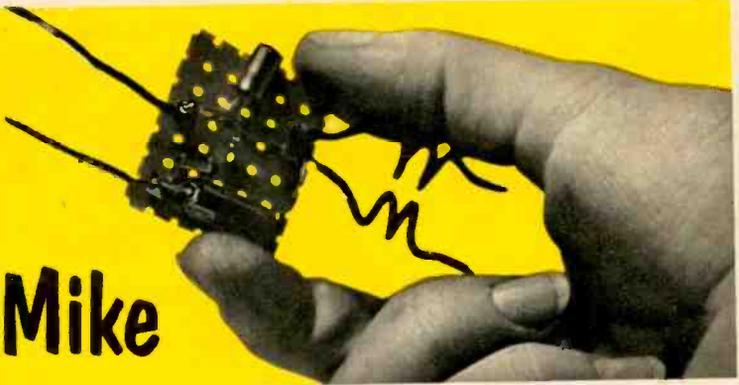


MANY an early CB rig is gathering dust because of the poor audio quality delivered by its carbon microphone. Converting the rig to use a ceramic mike is one answer, but the job may be more trouble than it's worth. However, by replacing the carbon mike element with a controlled-magnetic microphone cartridge and adding a simple one-transistor amplifier you can enjoy the advantage of a rig with lots of clean "talk power." Both the new magnetic element and the amplifier probably can fit inside the old carbon mike case.

No additional battery is needed to

power the amplifier since the transceiver's original carbon microphone voltage supply is used. The amplifier is built on a small section of perforated board, with flea clips as tie points. Layout and wiring is not critical, but protect Q1 from heat damage by placing an alligator clip or similar heat sink on Q1's leads when soldering.


The amplifier has no common ground lead and hence may be connected to the input transformer regardless of the polarity of the DC supply. It is important however, that Q1's collector be connected to a negative voltage.

—Chet Stephens

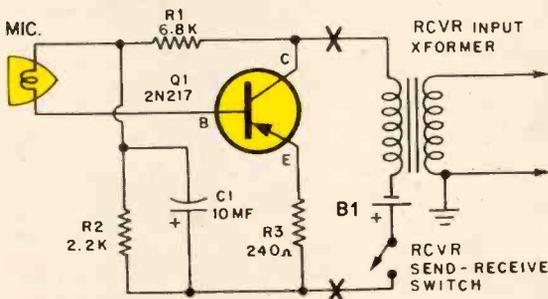

The preamp joins the original input circuit at the points marked X in the schematic. A jack for the original carbon mike, if present, may be used or direct connection to the circuit may be made at these points.

PARTS LIST	
Resistors: 1/2 watt or lower, 10%	
R1	—6,800 ohms
R2	—2,200 ohms
R3	—270 ohms
C1	—10 mf, 6 VDC capacitor
Q1	—Transistor—2N217, 2N109 or equiv.
Mic.	—Magnetic type replacement cartridge (Shure R5 or low-impedance type)
Misc.	—Perforated board; flea clips

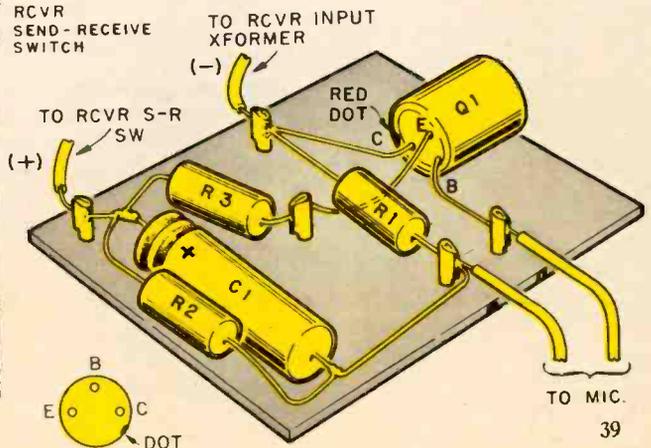

BASIC CB CIRCUIT THEORY

Theory can be downright practical! Here's the inside story of the electronics found in the basic Citizens Band transceiver.... Part 1

By Len Buckwalter, 1W5733

WHY BOTHER with theory when all you have to do is push the mike button and start talking? There are good reasons for theory—for knowing how your station operates is the first step in dealing with the troubles that are bound to arise. Theory gives you the basic know-how when you are buying, modifying, troubleshooting or installing equipment.

Three CB Voltages

In any rig, from a tiny handi-talkie to a \$300-plus unit, you'll find three forms of electrical energy. These may appear singly or in combination.

Audio Frequencies (AF). Any time you speak into a microphone, electrical currents are produced which vary in accordance with the pressure (volume) and frequency of your voice. Microphone signals begin at a level of a few thousandths of a watt and ultimately are boosted to two or three watts at the plate of the modulator tube.

Radio Frequencies (RF). In CB an RF signal of about 27 megacycles provides the carrier which transports the AF signal through space. If an AF voltage were introduced into an antenna it simply would radiate a weak field for a few feet. RF, however, gets out—and goes! There are other RF frequencies in a CB rig, notably in the receiver, which we will investigate later.

Power: AC & DC. No circuit will operate without some source of power. In a CB rig the power may be derived from the AC line or a car battery but, in every case, it must be processed in a form suitable for operating a tube or transistor.

The Transmitter

Illustrated in Fig. 1 is a typical transmitter section. Feeble AF currents developed at the mike are fed to the mike preamp, which gives them a considerable boost and applies them to the modulator. The amplifier-modulator stages are conventional audio amplifiers with an audio output of approximately 2.5 watts. This power is used to impress the AF energy on the RF carrier.

Now let's trace the source of the radio-frequency energy. As any CBer knows, without a crystal you can't transmit. So let's look at the crystal first. A small piece of quartz can be cut to act as an electro-mechanical resonator. When an RF current is passed through such a crystal, it vibrates at a precise frequency determined by its physical characteristics.

This may come as a surprise, but CB crystals are *not* cut for 27 mc. The quartz sliver needed to produce this frequency would be so minute that it could not pass sufficient current without fracturing. Instead, the crystal is cut for one-third the operating frequency, or approximately 9 mc. As the crystal vibrates at the fundamental 9 mc, it also produces several *overtones* or multiple harmonics. The third

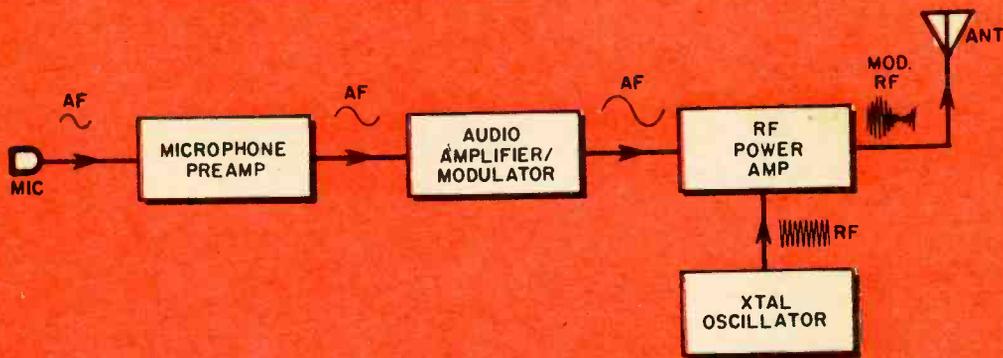


Fig. 1. Block diagram of the transmitter section of a typical transceiver. Switching is not shown.

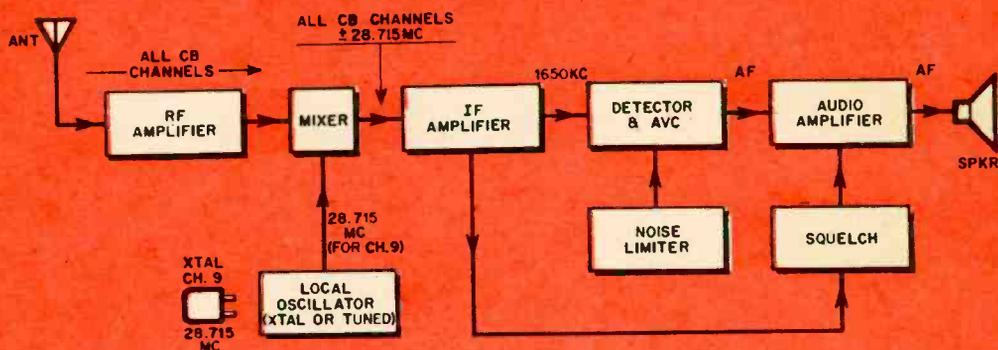


Fig. 2. Typical receiver section. Note the relative complexity in comparison to the transmitter.

such harmonic is at 27 mc ($3 \times 9\text{mc} = 27\text{mc}$). This 27-mc signal is introduced to the RF power output amplifier, where its strength is raised as close as possible to the full 5-watt carrier level permitted in CB. During the final processing, audio is impressed on this RF carrier. The audio signal from the modulator tube aids or opposes the ability of the RF tube to amplify by varying its plate voltage. The result is a shaping of the RF signal's amplitude to make it mirror the audio—called modulation. Note that the RF frequency doesn't change—just its amplitude. Hence the term—amplitude modulation. The audio signal must have a power level about half that of the 5-watt carrier to achieve 100 percent modulation. Fed to the antenna, the modulated carrier is then radiated.

Receiver

The block diagram of Fig. 2 is representative of the superheterodyne circuit found in most modern transceivers.

The signals at the antenna vary from a few microvolts to more than 100 microvolts—enough to pin the S-meter. As shown in Fig. 2, every signal on the band—channel 1 on 26.965 mc to 23 on 27.255 mc—is applied to the RF amplifier. At the output of the RF amplifier tube they are presented in amplified form to the mixer.

Tuning Tricks. Now the problem is how to get rid of 22 undesired channels and leave the desired one. Some inexpensive super-regenerative type receivers use a tuned RF amplifier, but such rigs are prone to co-channel interference due to

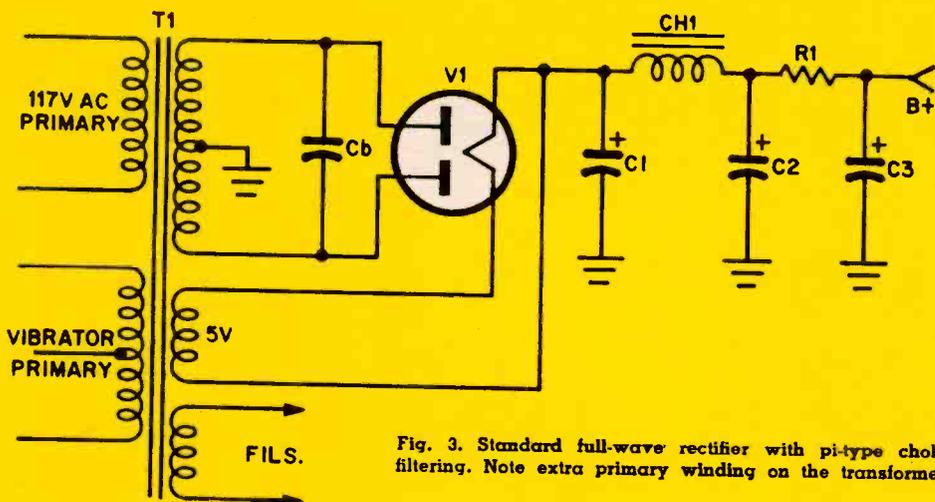


Fig. 3. Standard full-wave rectifier with pi-type choke filtering. Note extra primary winding on the transformer.

inadequate selectivity in the stage.

The problem is this: as the frequency of a tuning circuit increases, its *selectivity*, or ability to separate close-spaced signals decreases. CB's frequency of 27 mc is relatively high. More than 40 years ago Major Edwin H. Armstrong solved this problem by developing a circuit that converted the received signals to a lower frequency, where tuned circuits could be razor sharp. This is the theory behind the superheterodyne receiver.

Assume that 9 is the desired channel. At the output of the RF amplifier (see Fig. 2) all CB frequencies are present. At the output of the mixer, they're all still present, but they've been mixed with an oscillator signal. Among the many signals resulting from the beating of the CB frequencies with the oscillator signal, only one is at 1650 kc—and that is the channel 9 signal. A receiver crystal (cut precisely 1650 kc *higher* than channel 9) switched into the local oscillator did the trick. As we'll see in a moment, only the 1650 kc signal can penetrate further into the receiver.

Other channels are selected by switching other crystals into the local oscillator circuit to generate the appropriate IF (which always is the difference between the original CB signal and the oscillator frequency). For example, channel 2 on 26.975 mc requires a re-

ceive crystal of 28.625 mc—again a 1650 kc difference. In CB rigs with a continuous tuning dial in addition to the crystals, the local oscillator is the tunable element and when tuned across the band produces a signal always 1650 kc higher than that indicated by the channel numbers on the dial. The same theory applies, of course, to CB rigs using 455 kc or other IF frequencies.

Next in the receiver lineup is the IF amplifier. This section is tuned to the IF frequency and rejects everything else. Considerable amplification occurs in the one or more stages of the IF "strip."

Two for the Money. The quality of a CB receiver usually is reflected in the number of IF stages. The more IF's, the greater the selectivity. In the more elaborate systems, double conversion is used. Here the received channel is converted twice, producing two IF frequencies. This insures good image rejection—a problem peculiar to superhet circuits with sensitive IF strips. An image is a station *outside* the CB band which mixes with the local oscillator signal and produces a result at the receiver's IF frequency. For an example, let's say a commercial teletype station is transmitting on 30.365 mc. If some of this energy reaches the mixer it combines with 28.625 mc (receive crystal for channel 9) generating (among others) a 1650-kc

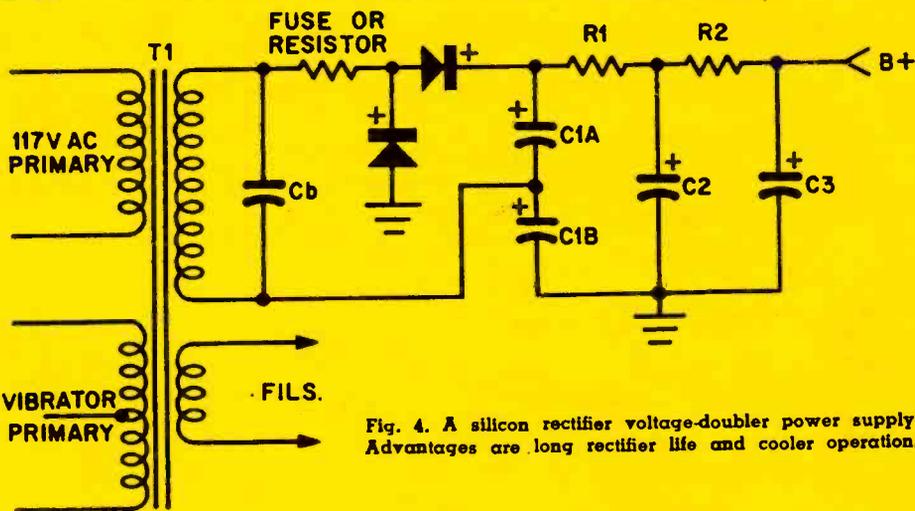


Fig. 4. A silicon rectifier voltage-doubler power supply. Advantages are long rectifier life and cooler operation.

difference signal, which the IF strip accepts and amplifies. In the transceiver's speaker the teletype signal is heard as if it were transmitted on channel 9.

The double-conversion technique meets the problem with *two* IF frequencies. The first is high, to cut out images, and the second low to preserve selectivity. Typical double-conversion IF frequencies are 4 mc followed by 455 kc.

The signal next encounters the detector. It is the detector's job to strip away the RF envelope from the audio. The separation of RF and AF is achieved by the rectifying-filtering action of the detector. The audio signal fed to the audio amplifiers starts out at about .5 volts more or less and is boosted to two or three watts of power at the speaker terminals.

Limiting and Squelching. Two refinements in the block diagram of Fig. 2 deal with problems of noise. The noise limiter, which is tied into the detector, relies on the fact that noise (mostly from auto ignition and other electrical machinery) has peaks higher than the signal itself. The limiter, which effectively clips off anything above a given level, kills these peaks. Although noise still comes through, its audible effect is greatly reduced when both signals are equal.

Atmospheric hiss in the absence of

signal is muted by action of the squelch. Tied into an audio stage, the squelch switches the tube on and off, depending on the absence or presence of a signal. An IF stage supplies the control signal, as explained in Part 2.

The Power Supply

The circuits of the transmitter and receiver sections of the CB rig depend on a power source—a battery or AC power line. In either case, the raw power must be converted into a form the tubes can use. The simplest design (see Figs. 3 and 4) is for operation from the power line.

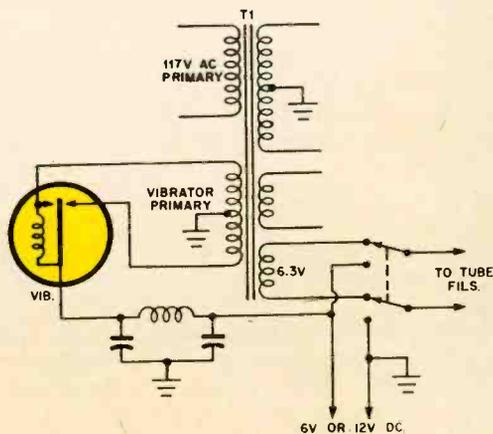


Fig. 5. Vibrator hookup showing filament switch.

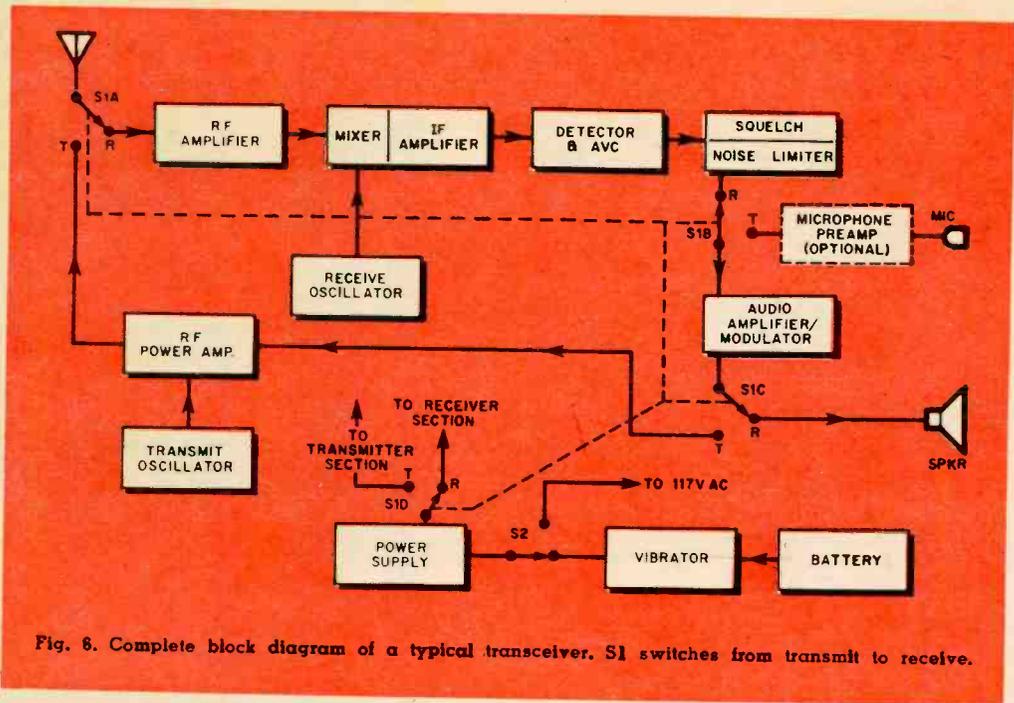


Fig. 6. Complete block diagram of a typical transceiver. S1 switches from transmit to receive.

Starting with the 117-volt AC line, power is applied to a transformer primary. A standard full-wave rectifier (Fig. 3) produces 250 volts DC or higher for the tube plates and screens. One or more filament windings supplies the low-voltage AC required by the tubes. Figure 4 is a voltage-doubler type of supply using silicon rectifiers.

Figure 5 is the same supply now set up to operate on a 6- or 12-volt DC car battery. Since power transformers cannot operate on pure DC, a vibrator's moving contacts chop the battery current into pulsed DC—a form acceptable by a transformer. In some cases, the vibrator is replaced by a transistor oscillator to achieve the same effect. Note that Fig. 5 is quite simplified and that most noise filtering elements have been omitted. The vibrator supply may be separate or built into the transceiver.

Simply plugging in the AC line cord or battery connector (via a cigarette lighter adaptor plug) makes the conversion from AC to DC operation. At the ends of both line cords you'll find an octal socket. When plugged into its male counterpart mounted on the transceiver's rear apron, the jumpers wired into the socket automatically make the correct filament and transformer primary connections.

Switching

How the switching system unifies the transceiver and allows certain sections to be shared is shown in Fig. 6. Switch S1 corresponds to the send-receive relay— or manually operated push-to-talk switch. Each section is shown in the *receive* position.

Beginning at the antenna we note that S1A switches the antenna. On transmit, the antenna picks up the signal from the transmitter's RF power amplifier. (The audio amplifier/modulator is similarly switched by S1, sections B and C.) In the receive position, signals from the receiver detector are fed to the audio amplifier and subsequently passed to the speaker. However, when S1B and C are set to transmit, the audio amplifier is placed at the disposal [Continued on page 118]

16db

SPEECH COMPRESSOR

Novel circuit gives you the biggest 5-watt signal on the air.


By Herb Friedman, 2W6045

WITH MORE AND MORE stations getting on the air, the normal CB problems of short range and interference are compounded. In fact, in metropolitan areas it's frequently difficult to get solid copy even on the shortest-range contact. But now, by adding EI's Speech Compressor you can cut through the interference and considerably extend your solid copy communications range. Speech compression modifies your rig's modulation in such a manner that the effect is equivalent to a large increase in power output.



When you say a CB transmitter's signal is modulated 100%, you refer to the situation when audio power is at its *peak*. The *average* power is another factor—usually about 10db less than peak, producing 30% modulation. Our speech compressor lowers (not clips) the peaks, permitting average modulation to be moved up toward 100%. The effect is a signal that is all audio and one that stands out from others. With the usual CB microphone and EI's compressor, up to 16db compression can be obtained. If you suddenly raise your voice, additional compres-

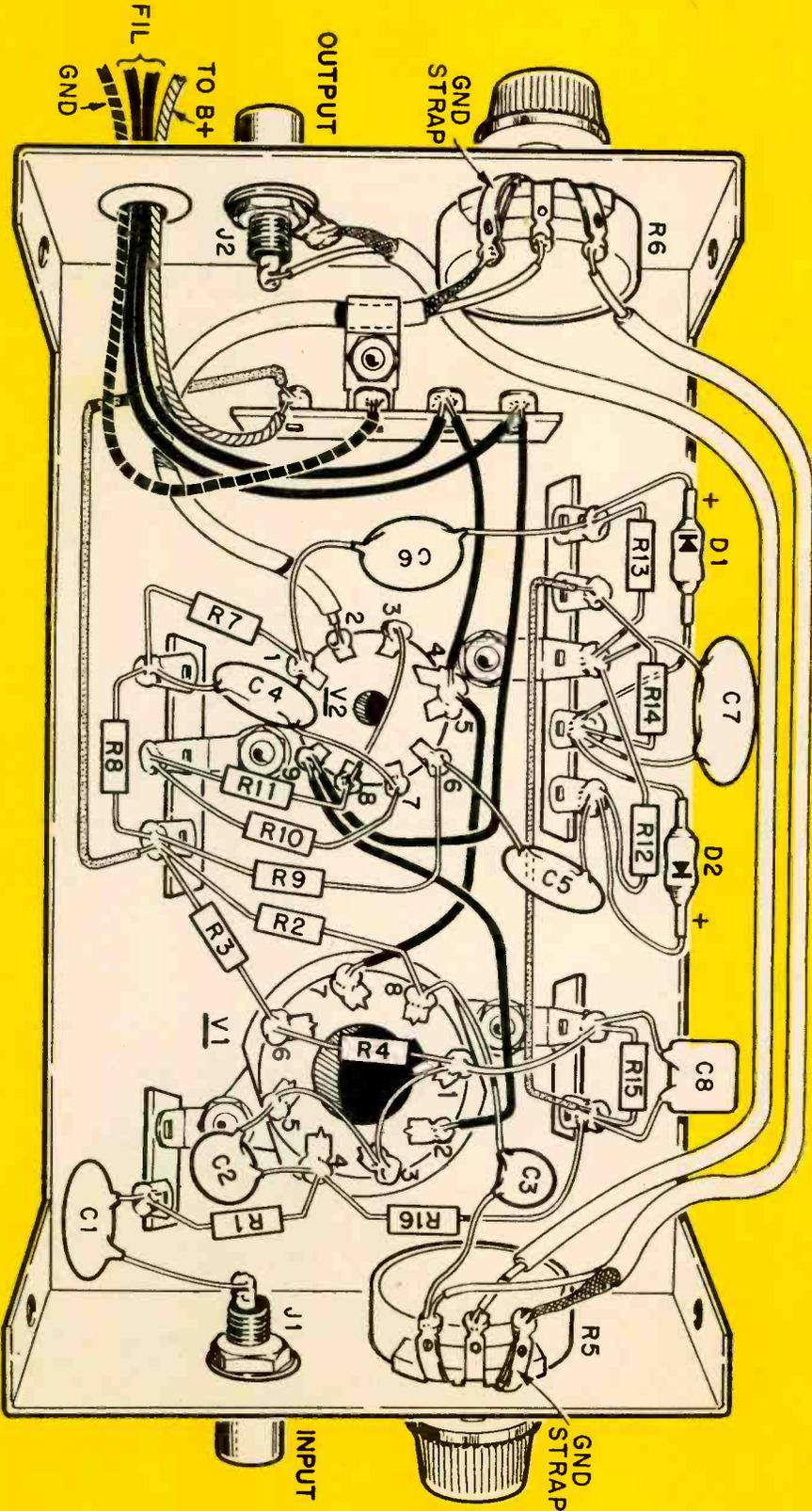Compressor is shown in use with an Olson Electronics transceiver.





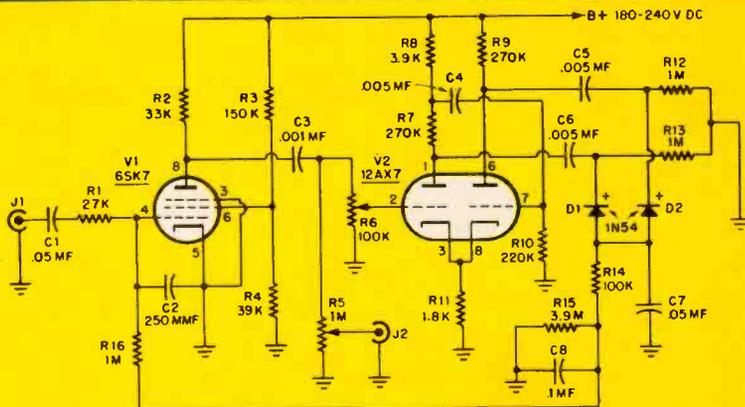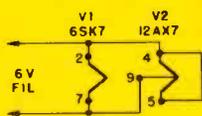Filament leads (shown wired for 6 volts) should be twisted tightly to prevent hum. Note grounding lugs on pins and single grounds on the shields.



PARTS LIST

Resistors: 1/2 watt, 10% unless otherwise indicated
 R1—27,000 ohms R3—150,000 ohms
 R2—33,000 ohms R4—39,000 ohms
 R5—1 megohm potentiometer
 R6—100,000 ohm potentiometer
 R7, R9—270,000 ohms
 R8—3,900 ohms
 R10—220,000 ohms

R11—1,800 ohms
 R12, R13, R16—1 megohm
 R14—100,000 ohms
 R15—3.9 megohms
Capacitors: 1,000 VDC ceramic disc types unless otherwise indicated
 C1, C7—.05 mf
 C2—250 mmf
 C3—.001 mf


C4, C5, C6—.005 mf
 C8—1 mf @ 75 VDC or higher
 V1—6SK7 or 12SK7
 V2—12AX7 or ECC83
 D1, D2—1N54 diodes
 J1, J2—See text
 Misc.—1-octal, 1-9-pin miniature tube socket; terminal strips; Minibox, 2"x3"x5" (approx.) etc.

sion is brought into the act. Not only is there a higher average modulation percentage, but distortion-producing overmodulation is forestalled.

Construction. The speech compressor is built in a Minibox with the tube sockets spaced and oriented so the terminal strips do not interfere with each other. For wiring ease, cut off the center ground post (if present) of V2's socket. Microphone input jack J1 and volume control R5 are mounted side by side, as are compressor output jack J2 and compression control R6. If you intend to use the compressor with a push-to-talk rig, J1 should mate with the microphone plug and J2 should have enough terminals to handle the push-to-talk leads.

Since V1 is an amplifier, care must be taken to avoid hum pickup. Run the filament leads as shown, but twist them together tightly, keeping them away from V1's components and J2. Even if one side of the filament circuit is grounded at the transceiver, do not ground the compressor's filament to the Minibox.

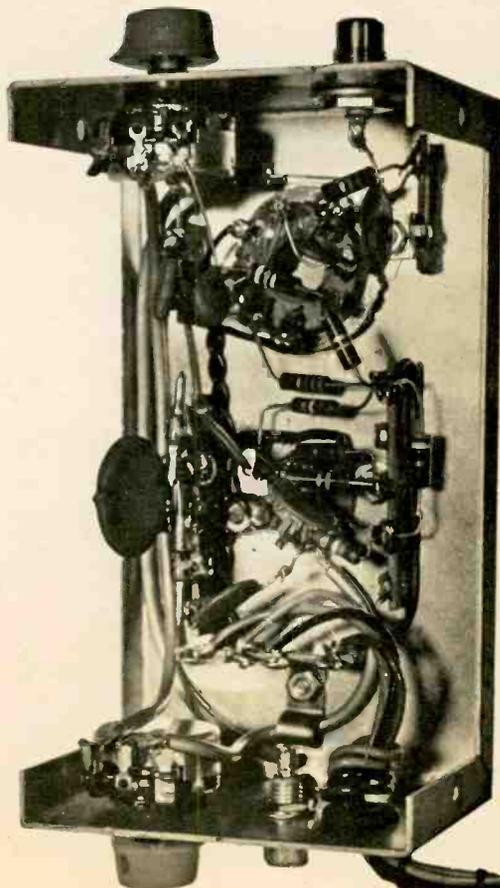Notice that the three shielded leads shown in the pictorial have an insulating outer covering and that the shields are grounded at only one end. To make wiring easy, use thin insulated phono



cable for the shielded leads. When soldering D1 and D2 use a heat sink, such as an alligator clip, on each diode lead.

Tube V2 usually will not require a shield; however, a poorly grounded transceiver or a poor antenna system can cause RF hum. If this occurs shield V2.

Installation and Checkout. Connect the filament leads across the transceiver's filament supply and the ground lead to the transceiver chassis. The compressor's B+ lead is connected to the transceiver's power supply at the point of maximum filtering (this is where the transceiver mike preamp's plate load resistor connects to B+).

Set controls R5 and R6 to full counterclockwise (off). Connect a modulation percentage indicator to the transceiver's output. With the mike in its usual position, speak in a normal voice. Advance R5 until the modulation meter reads 100% on speech peaks. Turn R6 full clockwise and the per cent of modulation will fall considerably. If you are speaking close to the microphone the peak modulation should indicate below 30% (12-16db compression). Advance R5 until the modulation peaks at 85%. At this setting you will have nearly full compression and the 85% setting leaves you a 1.5db safety margin. If you raise your voice, this margin will reduce the chance of overmodulation distortion.

If you do not have access to a monitor

meter, the following adjustment procedure will give satisfactory results. Set your VTVM to the AC function on the highest range, connect the AC probe to the plate of the modulator tube (usually a 6AQ5) and the meter's common lead to the chassis. Connect the microphone directly to the transceiver and, using a dummy load, transmit in the normal manner. Note the peak reading on the VTVM as you speak. This reading will be assumed to equal 100% modulation. Next, connect the compressor and set R6 for maximum compression. Speaking as before, advance R5 until the VTVM indicates the same reading on speech peaks.

If you feel you do not need full compression on short-range contacts, an intermediate setting of R6 reduces compression. Keep in mind that as you reduce compression R5 must also be reduced or the transmitter will overmodulate. (Overmodulation sounds extra loud on short-range contacts but is just a mess of distortion when your signal is weak.)

EI's compressor is designed to operate with microphones supplied with CB transceivers or with such high-output types as the Astatic D-104, the Sonotone CM-30 and the Turner 350C. It will not perform satisfactorily with low-output microphones. Since the compressor provides gain, do not operate with R5 wide open or you will get distortion from overmodulation and overdrive.


THEORY

V1 is a variable-gain preamplifier whose output is fed through volume control R5 to the transmitter via J2. V1's output signal also is fed through compression control R6 to V2, an amplifier phase inverter.


The signal at both plates of V2 is rectified by D1 and D2. The resultant DC is fed back via R14 and R16 to vary V1's grid bias, thereby controlling its gain. With R6 off, no signal is fed to V2 so there is no DC control voltage and V1 operates at full gain.

The use of the phase inverter permits both the positive and negative peaks to be compressed, rather than the negative peaks only, as is the usual case. This system eliminates distortion common to single-peak compression and provides a higher level of control voltage. Further, the frequency response is changed automatically to maintain maximum communications effectiveness. Under full compression the low frequencies are attenuated slightly to give a crisp sound. If the voice signal falls extremely low—below compression level—the low frequencies are attenuated sharply.

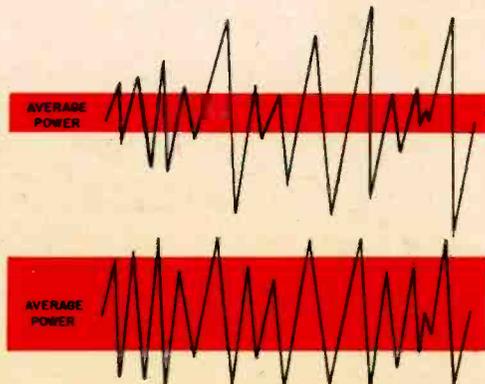The waveforms at right show the difference in effective average power in a non-compressed signal (top) and a compressed signal (bottom).



THE TRUTH ABOUT

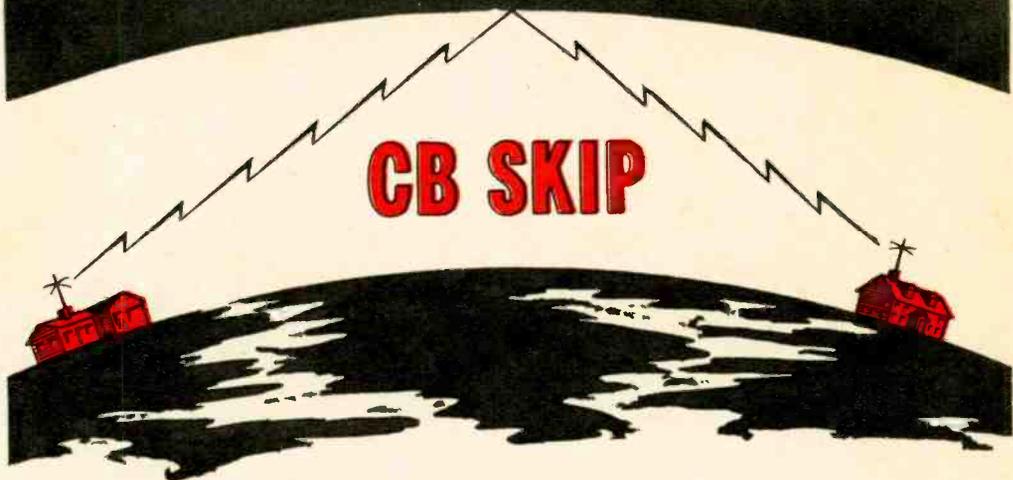

Some straight talk about the headache thousands want to enjoy!

By David Walker

LURKING some 80 to 200 miles above the earth is an invisible battlefield of Citizens Band radio. Scattered here in bits and pieces and layers is the ionosphere, the strange collection of atomic fragments that intercepts radio signals and bounces them back to the ground, producing a phenomenon known as skip.

Skip is one of the biggest controversies in CB radio—always has been and probably always will be. To some licensees it's pure pie-in-the sky; to others it's a confounding source of annoyance. Most CBers simply view skip as a legal enemy and try not to fraternize—at least not so anybody will find out.

It's improbable that there is one active CBER who does not know the Federal Communications Commission's position on working skip. FCC rules say in unmistakable terms that it is illegal. And we all know if you get caught in the act you lose your license. Yet when you monitor the band you find that thousand-mile contacts persist in spite of all rules and threats.

Compiling meaningful facts and

figures on those who work skip is a little like interviewing errant husbands on their follies. What they tell the boys at the bowling alley, what they tell a man with pencil and paper in hand, and the truth of the matter never seem to jibe.

CBers do hear a lot of talk about skip, and once in a while you see something in print on the subject, which might lead you to believe that going after the long contacts is something practically everybody does. I do not share that view. As an educated guess, I would say much less than half of all active CBers have ever made a single skip contact. By active, I mean those who have their own equipment and get on the air frequently—a consideration which eliminates many of the 300,000-plus men and women who hold licenses. I would estimate something like one-fourth of this group has at some time made other than a local contact.

The main reason you hear so much about skip lies with an extremely small minority who get hooked on DXing like junkies take up heroin. For them, days when the band is not open are like



quick-withdrawal at Lexington. But carrying out these nefarious activities is only part of the game for the real addict. He also likes to talk about his little hobby, and talk and talk and talk—except when an FCC monitoring car or a reporter type appears. It's the well-known situation where a minority can sound like an overwhelming majority if they talk long enough and loud enough. Even so, thousands of CBers have worked and are working skip and a good many others would like to try their hand if they knew how and dared.

The irresistible siren call shrilled at the innocent CBER when long-distance signals start pouring in can break even the strongest amongst our law-abiding citizens. Confronted with a chance to stretch his measly five-watt power over 1,000 or 1,500 miles, a poor chap's senses start cart-wheeling. In the old days he was likely to give

a direct call to one of the stations he heard, or perhaps he'd blurt out ingenuously, "Calling CQ!" The FCC's crackdown has pretty much put an end to that procedure. Now there are new techniques designed with an eye toward working skip without losing that prized license.

The enthusiastic tester is a prime exhibit of the new school. He *sounds* like he just wants to make sure his rig is working properly as he calls innocently, "Hello test, hello test, hello test." But if conditions are right a co-conspirator a skip away comes on with, "You're coming in fine in Texas!" Only trouble is, the tester's station may be in Maine.


Then there is the prefix dropper. As he works skip stations he uses only the last four numbers of his call. He not only remains anonymous, but racks up two violations on one contact.

An even more intriguing specimen is the sportsman, the gent who gets a bigger kick out of beating the system than making a successful contact. He begins by calling one of his *own* units in the normal fashion. The only rub is the fact that he doesn't *have* any other units. Meanwhile, across the country a fellow sportsman (they exist everywhere) is engaged in the same activity. It doesn't take long for two DX hounds to find each other. But they're too clever to be caught red-handed. With masterful aplomb they proceed to exchange comments indirectly by addressing messages to their non-existent units. It's like being at a cocktail party and talking to one person while hoping someone else will hear.

There is no doubt that working skip is a challenge from aspects other than the legal. At 27 mc, the Citizens Band is far from being an ideal frequency for skip operations, especially at the present time.

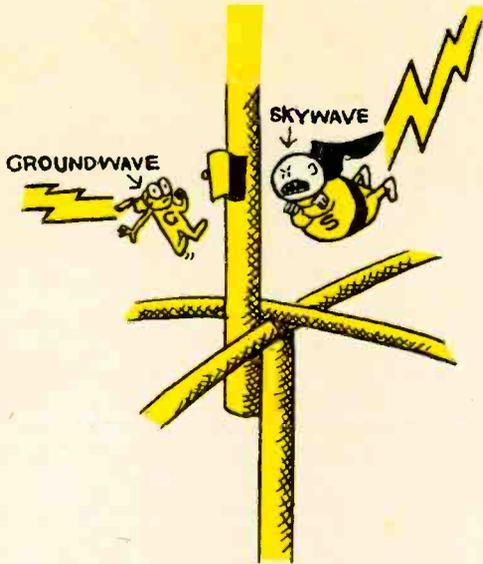As we said earlier, skip signals are a phenomenon caused by the ionosphere, which was first identified by a couple of scientists





named Kennelly and Heaviside. The ionosphere is a region above the earth that reflects radio signals like a mirror reflects light. It is made up of tiny particles of gas which have been ionized by ultraviolet radiation from the sun. In becoming ionized, the particles acquire an electrical charge (a normal atom is balanced, exhibiting no charge) and are conductive. Radio signals of certain wavelengths bounce right off. That's what happens when a CBer hears skip signals. A transmission from a distant station takes off toward the sky, hits the ionosphere and bounces to earth again a few hundred (short hop) or several thousand miles away (long hop). The amount of power in the signal seemingly is a minor consideration. Five-watt CB signals can jump just as far as those from a kilowatt ham rig.


How far do CB signals reach under good skip conditions? We know they've been heard (with readable copy) in several parts of Europe, including the most distant point of Sweden. They also have been picked up in Latin America. California and Hawaiian CBers once communicated almost daily (they theoretically have stopped it now). Here on the East Coast, the Mid-West comes in strong nearly every day, and at times the Southwest and California are heard.

The big variable in skip transmissions is the ionosphere. It keeps changing, sometimes being a good reflector, at other times not reflecting at all. Skip conditions are at their best just after the sun has passed, spraying a big dose of ultraviolet into the atmosphere. This is one reason skip-working is somewhat limited. The best periods are during the day, when most CBers are at work. Nighttime is not usually good for skip.

The ionosphere is a better reflector for signals of certain frequencies than for those at others. Maximum reflection is offered signals between 5 and 17 mc. When you get up to 27 mc you're outside the good-skip spectrum, which is why we say the Citizens Band channels offer a challenge when it comes to DXing.

The ionosphere also is affected by sunspots—the more sunspots, the better are conditions for skip. Sunspots run in 11-year cycles, from maximum to minimum. We're now sliding down a slope. Between 1964 and 1965 we'll hit rock bottom—what scientists call the Year of the Quiet Sun. So CB skip will lessen from now until then, and afterward start improving as the cycle repeats itself.

[Continued on page 121]

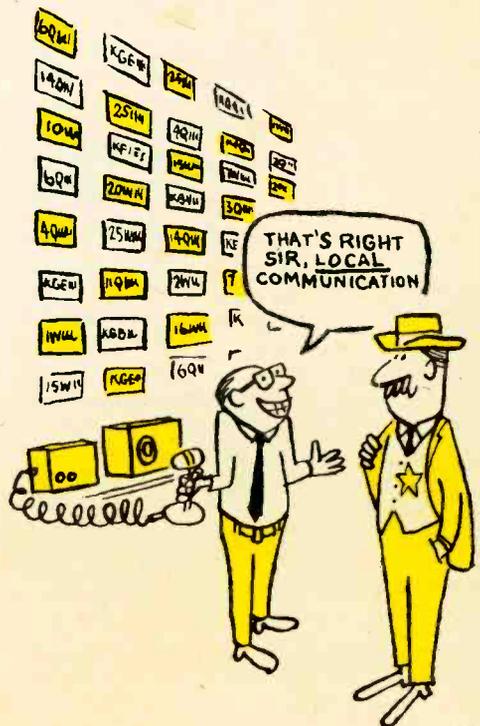



CB CORNER

BY LEN
BUCKWALTER
KBA4480

MORE PART 19 REVISIONS

THOUGH the FCC once said there was nothing radical about the changes being contemplated for Part 19 rules for the Citizens Radio Service, the agency's Docket No. 14843 (Notice of Proposed Rule Making) indicates its idea of what radical means varies a little from the norm. If the changes go through, which seems likely, the Citi-

Before the
FEDERAL COMMUNICATIONS COMMISSION
Washington 25, D. C.

In the Matter of

Amendment of Part 19, Citizens Radio
Service, to revise Subpart D, Station
Operating Requirements, and to make
other changes

zens Band is in for a shake-up.

Copies of Docket No. 14843 (see cut), incorporating the changes, were distributed in a release dated November 16, 1962. With them went an invitation to interested persons to file comments for or against the proposed changes. An original and 14 copies of such statements must be furnished the Commission. Ivan H. Loucks, head of the amateur-CB division, made it a point in a conversation with us to say that the FCC welcomes comments, whether for or against, and considers them seriously. But merely saying you oppose or favor Docket No. 14843 is not enough. The Commission is not trying to obtain a vote before adopting, altering or rejecting the changes. It wants well-thought-out *reasons* why the changes should or should not be made. Deadline for filing comments is January 15.

In an introduction to the proposed changes, FCC Acting Secretary Ben F. Waple says revisions are necessary because of interference on the band, partly due to misuse of operating privileges, which is "so prevalent in some areas as to threaten the continued usefulness of

the service." The FCC's own investigations and complaining letters from licensees brought the condition to light, Mr. Waple says. This abuse of privileges, he goes on, in a service as large as CB is bound to destroy its utility.

Of paramount importance in the proposed changes is one which would limit communications between different stations (e.g., KBA4480 to 2W6045) to five channels (12, 13, 14, 15 and 23). Communications between units of the same station (e.g., KBA4480 to Unit 2) could be transmitted on any channel.

The idea here, of course, is to put a damper on pseudo-hamming, skip contacts and idle chatter by cramming the hobby types into a closet-size speck of the band, where they will kill each other off in one good-DX day. To make things more difficult for the long-distance boys, they'll also have to put up with interference from diathermic machines and other radiation-type industrial, scientific and medical equipment, which operates on 27.12 mc and fills the center channels (12-15) with QRM. On channel 23 they'll have trouble from the high-power (30 watts) modelers and other Class C remote-control transmitters. In addition, a new mileage limit would be imposed. Maximum range would be 150 miles for *any* contact.

Under the proposed changes, the 5-minute rule would give way to a new time system. Any communication between two or more stations would be limited to 3 minutes, and the ensuing period of silence would be 5 minutes long.

Phone patches in any form are outlawed in the changes, and so are speech scramblers and all other non-standard methods of coding (the FCC wants to be able to understand what you are saying). Tone control is still approved but the signal is limited to 5-second dura-

[Continued on page 119]

**Comprehensive courses in
Electronic Fundamentals
TV Servicing – Color TV –
Electronics for
Automation –
Transistors**



LET RCA TRAIN YOU AT HOME

RCA Institutes, one of the leading technical institutes in the United States devoted exclusively to electronics, offers you the finest training-at-home. The very name "RCA" means dependability, integrity, and scientific advance. Practical work with your very first basic lesson. You build and keep prime quality equipment. Pay as you learn. No installment payments necessary. You pay for your next study group only when you order it. And remember, in electronics the more you know the higher you go. Licensed by the University of the State of New York.

Resident school courses in Los Angeles and New York City also offer college-level training in any field of electronics you may choose. Classes begin four times each year. Free Placement Service.

**SEND POSTAGE-PAID CARD TODAY
FOR FREE ILLUSTRATED BOOK!**

Check Home Study or Resident School Box



RCA INSTITUTES, INC. A SERVICE OF RADIO CORPORATION OF AMERICA
350 WEST FOURTH ST., NEW YORK 14, N. Y. • 610 S. MAIN ST., LOS ANGELES 14, CALIF.

The Most Trusted Name in Electronics

Dept. EI-33

TOP 10 CB CLUBS

AFTER SEVERAL YEARS of observing and being associated with Citizens Band clubs, we at EI are asked repeatedly to name the best one in the country. It's a question no one could answer fairly without spending some time with each club—a formidable undertaking.

But amongst the scores of clubs dotting the countryside from Maine to Hawaii are a few truly outstanding groups, if you consider them from the viewpoint of general activities, interest shown by members and success in achieving goals. Without doubt, these are the *better* clubs. We've chosen ten of them as the top CB organizations in the country. They're listed below, along with a paragraph describing the activities of each. The paragraphs also explain our reasons for putting the clubs on our list. The ten are *not* ranked in order. They're arranged *alphabetically* and all are of equal stature. The month or year following the address is the date of founding.

The Top Ten were selected for accomplishments in recent months—deeds which speak well for the clubs—and after careful observation on our part. Why isn't *your* club included? It may be because you do not have a good public relations program, a must for any organization. A PR program lets the rest of the world know what your club is doing. We *do* hear about the activities of what we consider the more outstanding groups. Are



1 **CITIZENS BAND ASSOC. OF CONNECTICUT**, 379 Pine Tree Dr., Orange, Conn. August 1959. Charles Collins, 1W4265, president. 150 members. Club provides frequency checks for members, assists Civil Defense, auxiliary police, marine emergency groups. The organization is expanding, having established three new chapters in recent months. It seeks other local groups wishing to affiliate. Monthly paper, CBAC Journal, runs technical tips and other useful information, some clever and pertinent humor pieces and bright news items. A woman's auxiliary unit is known as the She-BAC.

2 **CITIZENS RADIO LEAGUE**, Box 28, Northlake, Ill. February 1960. Joe Perry, 18W5527, president. 267 members. Club is affiliated with Northlake CD Communications Group, takes part annually in a Boy Scout Canoe Marathon and performs many other public service deeds. Recently club members participated in the rescue of a boat lost on Lake Michigan, devising a method of transmitter clicks to help locate the craft, which was then towed to shore with one member aboard as radio operator. Monthly paper, CB News & Views, is one of the finest in the country, featuring profiles on members, thoughtful editorials, good light pieces, general articles and news about coming events.

3 **DELAWARE VALLEY CITIZENS RADIO LEAGUE**, c/o Allen Miller, Seabrook Farms, Seabrook, N. J. November 1959. Ed Yoos, 3W1343, president. 75 members. Affiliated with RACES. Club is one of the older ones in the country. It has participated in many types of emergency operations and runs a highly interesting series of demonstrations, picnics, banquets, raffles and prize contests, proving that a good club gives its members opportunities for fun while doing public-service work. A monthly paper is published by the group.

4 **DIXIE COMMUNICATIONS CLUB**, Box 2004, Decatur, Ga. July 1960. Larry Peevy, 6W6576, president. 62 members. Club is Georgia's official Civil Defense unit. Members have participated in several emergency operations. They were on hand when a small boat carrying eight persons was rammed on Lake Burton, they found a man who was lost in Lithonia, provided lights for a search on Stone Mountain and were the first rescuers on the scene when a small plane crashed. When the radio in a police car went out, CB units provided communications. Mobile units are used in helping collect toys for underprivileged children at Christmas. Members receive frequent bulletins on rescue and lookout operations; the club keeps three pages of information on each member, including when he is available for emergency work, his home and business telephone numbers, etc. The club's monthly paper, The Dixie Communicator, carries items about club operations, activities of individual members and some humor pieces.

5 **GREATER DALLAS CB CLUB**, 1318 Michigan Ave., Dallas, Tex. November 1959. Dick Johnson, 10W4075, president. 285 members. Associated with Civil Defense, the Dallas Police Department and the Red Cross, the club in recent months has provided mobiles at 62 schools during a mass polio immunization program (sparing police cars for other duties), helped out during a July 4th fireworks display at the city park and was on hand for a Civil Air Patrol air show. Members monitor channel 11 from 10 p.m. to 1 a.m. nightly, listening for emergency calls. Club's paper, The Broadcaster, is filled with safety tips, operating hints and other useful information.

6 **LANCASTER COUNTY CB CLUB**, Box 202, New Holland, Pa. October 1960. Carl Stief, 3Q0333, presi-



you letting others know what *your* club is doing? If you think your club has been unjustly excluded, write us a letter and tell us about your organization and its activities. In a future issue we'll publish a report on clubs which nominate themselves for our Top Ten list.

A good club, to our way of thinking, need not have an extremely large membership. Nor must it be in a large city or possess fancy gear. The interest, enthusiasm and willingness of the individual members alone decide a club's status.

Our files show there are just over 300 established CB clubs in the country. New groups have a way of appearing almost weekly, but others give up the ghost at about the same rate. Our figure approximates the current average total, though it doesn't reflect the hit-or-miss, sometime clubs which never get fully organized. Average number of members amongst the clubs on our books is 52, making a total of something over 15,000 CB clubbers altogether. Local clubs range all the way from 12 to 350 members.

Annual dues run from the \$12 charged by several groups to free membership offered by two clubs. The average is \$5.25 and the most-popular fee is \$6. Independent clubs outnumber those affiliated with regional or larger organizations by six to one, but six out of ten independents express an interest in joining the right kind of national CB association.

Most clubs meet monthly, though one holds a weekly get-together. Favorite activities include working with local Civil Defense organizations (No. 1) and police departments (No. 2). Nearly all involve themselves also in such community activities as July 4th celebrations, town festivals, parades, Christmas drives and so on. The majority have one big annual club event, such as an eyeball QSO, a banquet, a fair or a picnic, and most maintain some kind of emergency program or team.

dent. 145 members. Affiliated with Civil Defense, the State Police and the Pennsylvania CB Association. Organization was founded as a social club but has since developed a useful program of service work, taking part in searches for lost persons, helping out at fires and after water accidents and providing emergency communications wherever needed. Club's emergency channel, 17, is now monitored by the fire and police departments, constables, sheriff, county prison authorities, Red Cross, Civil Defense and Pennsylvania State Medical Department—indicating how well the group is accepted by local authorities. Unit publishes a monthly paper.

7 LYCOMING CB RADIO CLUB, Box 247, Montoursville, Pa. May 1960. Robert Shearer, 20W14E0, president. 80 members. Club works with Red Cross, State Police and West Branch Fire Department, has a frequency meter and members licensed to do frequency adjustments, maintains an emergency communications squad for special assignments, using channel 4. Control station is on a mountain top. Members have taken part in the Montgomery Boat Regatta, Lions Club parades, Civil Air Patrol work (when CAP communications failed), the Montgomery Diamond Jubilee and flood alert work. Club publishes an extensive directory and a monthly paper, Lyco CB News, which carries many news items of interest to members, club programs and some operating information.

8 MOBILE CIVIL EMERGENCY UNIT (MCEU), 1203 Butternut St., Syracuse 8, N. Y. 1960. Chip Cardinali, 20W1803, president. Organization has local chapters in some 20 states and a total of 1,250 members. Chapters carry out their own activities. As examples, the Maumee Valley (Ohio) Chapter got mentioned in

the local newspaper after summoning help quickly to the scene of a grade crossing accident. The Washington-Warren-Saratoga (New York) Chapter has affiliated some members with the Washington County Security Squad, a group of specialists in rescue work, first aid, SCUBA diving and police emergency duties. Many chapters issue individual papers and headquarters publishes a monthly.

9 RACINE CB CLUB, 1019 Crabtree Lane, Racine, Wis. August 1960. Roger Tischendorf, 18A8858, president. 80 members. Affiliated with Civil Defense. Club has given talks on and demonstrations of radio gear for the Racine Junior Deputy Sheriffs, provided communications during Safari Days festivals and July 4th parades, ironed out cases of TYI and during a blizzard in the winter of 1960-61 rescued a couple who had wrecked their car. Members have cleaned up an undesirable situation on channel 11 and persuaded the police to monitor channel 22 on a 24-hour basis.

10 SOUTH JERSEY CITIZENS RADIO CLUB, Box 99, Stratford, N. J. February 1959. Craig Wooster, 3W4964, president. 100 members. One of the oldest—if not the oldest—CB clubs in the country, the organization has proved its strength by having and solving some extremely difficult problems. Affiliated with Civil Defense. The club originated a set of 12 special signals for use in emergency alerts. The signals were approved by the FCC and have been adopted by other CB clubs, CAP units and various communications organizations. The club offers its services in emergencies and in the past has tried to improve CB by emphasizing the need to keep operations within the limits prescribed by the FCC.

BUILD THE EI CITIZENSCOPE

For the first time anywhere! An oscilloscope designed specifically for displaying Citizens Band modulation.

Herb Friedman, 2W6045

SINCE modulation quality is one of the big factors in the get-out ability of a CB transceiver, many CB'ers have rigged up some means of metering the percent modulation of their transmitters. While such metering circuits are useful, they respond to average rather than peak modulation. When an average reading meter indicates 100% modulation, the actual percent modulation may be substantially lower—or higher.


For optimum modulation adjustment, a peak indicating device is necessary. This is particularly true when speech clippers or compressors are employed since their maximum effectiveness is realized when adjusted for 100% modulation with a peak reading indicator.

EI's CitizenScope is a peak indicating unit tailor-made for the CB'er. It displays either a trapezoid (TRAP) or modulation waveform (MW) pattern, can be permanently connected into the transmission line, for monitoring (peak) percent modulation. Properly used, the CitizenScope can give you a transmission effectiveness hitherto unobtainable. EI's CitizenScope is modest in cost—about \$35. The layout is specifically designed to be easy-to-build—even for the novice. Standard components are used, and except for the cathode ray tube, all are readily available.

Construction. The CitizenScope is built in the main section of a 12x7x4-inch Minibox. The first step is to mark all the necessary holes. When drilling the front panel follow the template and allow sufficient clearance around the controls for the cover to be slipped into place. To prevent T1's field from deforming the CRT trace locate T1, as shown, as far as possible from the CRT.

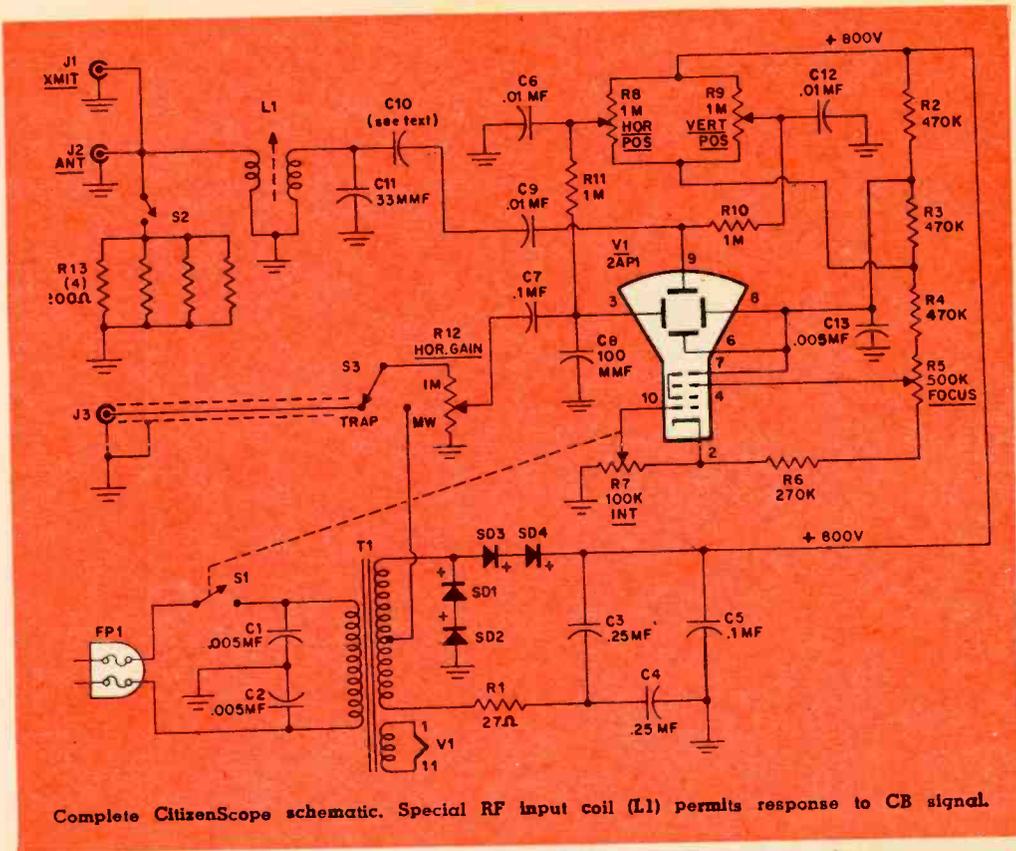RF input components, J1, J2, L1 and S2, should be mounted close to each other toward the cabinet's rear in the





Complete CitizenScope schematic. Special RF input coil (L1) permits response to CB signal.

arrangement shown. Bus bar or doubled wire is used between J1 and J2.

The CRT bezel, which serves as V1's front support is centered on the front panel as shown. V1's base is supported by two 2-inch standoffs, metal or insulated. You can improvise them from metal tubing or use standard standoffs. The standoffs are mounted 6 1/8 inches back from the inside of the front panel.


Wrap six turns of plastic electrical tape around V1's Bakelite base. Using thin scrap metal (as from a tin can) fashion two straps. Bend the straps around the taped CRT base to give a snug (but not tight) fit when assembled.


The green filter in the Millen kit is supplied without a grid. However, grids are included in the Techni-Cal Oscilloscope Decal kit (which also includes the other control labels). It is important that V1's socket be in place before V1 is mounted. For correct trace position, install V1 with pin 1 toward the

bottom of the cabinet. Terminal strip TS4 mounts on one standoff with a solder lug for grounding.

Coil L1 uses a Cambridge Thermionic

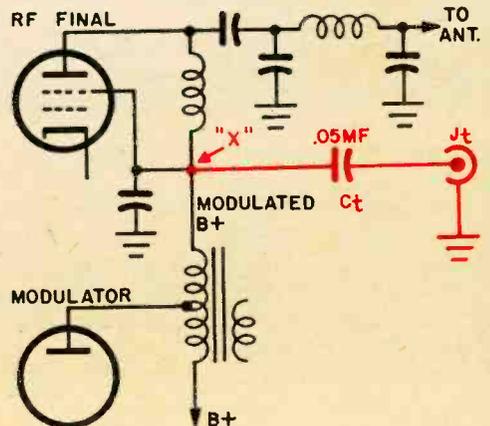J1 and C1 must be added to transmitter output.



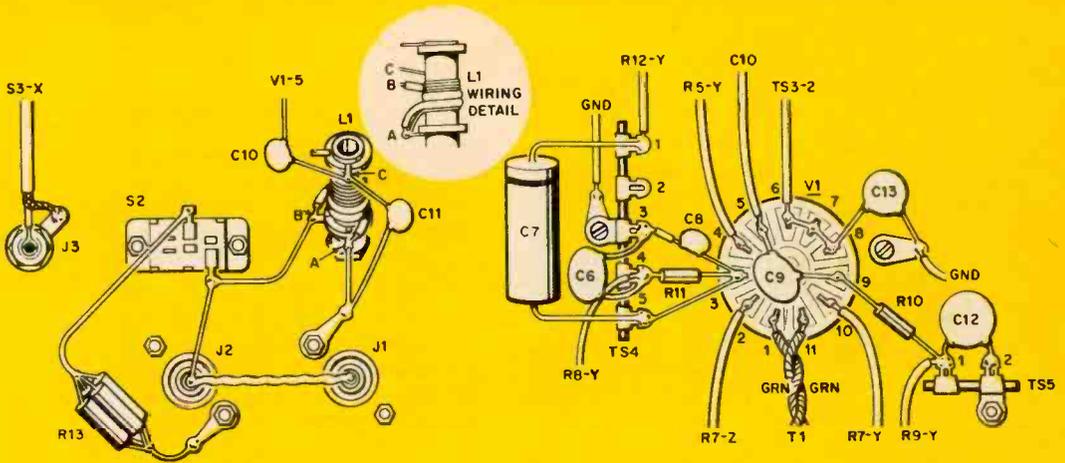

Input circuit and V1 wiring. TS4 and gnd lug mount on V1's neck clamp standoff; TS5 on chassis.

Resistors:

- R1—27 ohms, 2 watts
 - R2,R3,R4—470,000 ohms, 1 watt
 - R5—500,000-ohm linear pot
 - R6—270,000 ohms, 1/2 watt
 - R7/S1—100,000 linear taper pot with SPST switch
 - R8,R9—1 megohm linear taper pot
 - R10,R11—1 megohm, 1/2 watt
 - R12—1 megohm log taper pot
 - R13—4,200 ohms, 1 watt, 5% carbon (not metalized) connected in parallel
- Capacitors:**
 C1,C2,C13—.005 mf, 1,000 VDC ceramic

disc

- C3,C4—.25 mf, 600 VDC
- C5—.1 mf, 1,000 VDC or 2-.05, 1,000 VDC in parallel
- C6,C9,C12—.01 mf, 1 KV or 1.6 KV ceramic disc
- C10—see text, molded mica
- C11—33 mmf, molded mica
- S2—SPST slide switch
- S3—SPDT rotary switch (Centralab 1460)
- T1—Transformer: Secondary—250VCT @ 25 ma; 6.3 V @ 1 a (Allied Radio 62G008)
- J1,J2—SO-239 coaxial jacks


J3,J1—phono jack


- SRI,SR2,SR3,SR4—Silicon diodes, GE 1N696 (500 PRV @ 600 ma or better)
- L1—Wound on CTC-PL55-2C4L/B (Allied Radio 72H446)
- V1—2A1P1 or 2A1P1A (Available for about \$6.00 from surplus dealers such as Barry Electronics, 512 B'way, N.Y.C. and Gyro Electronic Co., 88 Leonard St., N.Y.C.)
- FPI—Fuse plug with 1 A fuses
- Misc.—Millen 80072, 2-inch scope bezel; socket, Amphenol Magnal type 49-SS11L; Minibox (12"x7"x4"); terminal strips

Set S3 to TRAP, turn on the transmitter and speak into the microphone. Adjust R12 until a trapezoid pattern appears. Its shape will vary as you speak. At 100% modulation the trapezoid height


(at the right of the CRT) will exactly double. On the left the trapezoid will come to a point at the baseline. (This is the reverse of the trapezoids shown in the illustration.) If you overmodulate

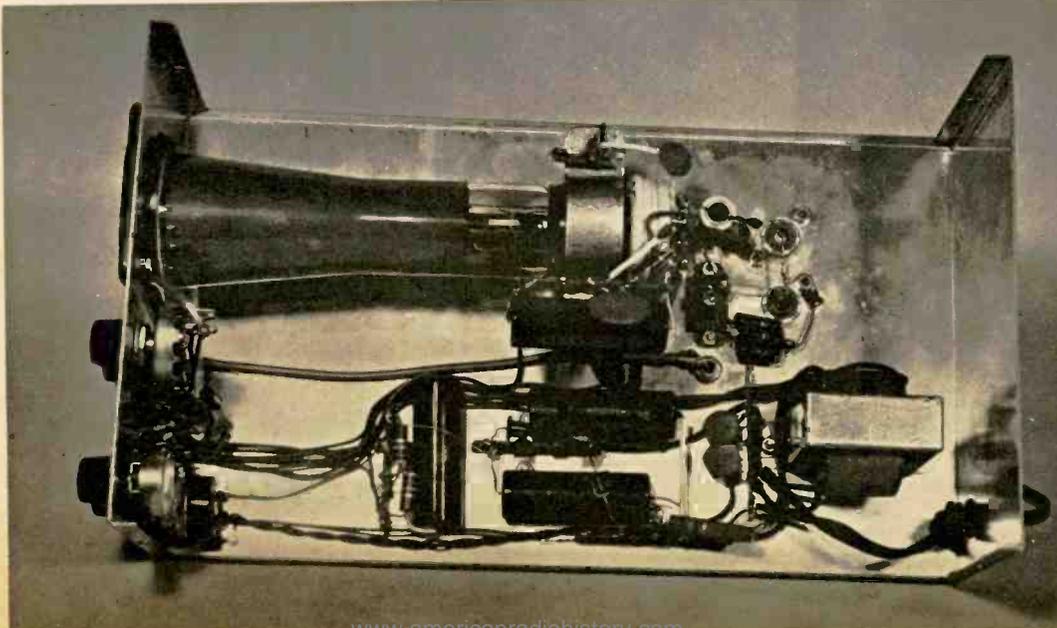Completed CitizenScope with cover removed. Open, logical layout makes wiring this one a cinch.




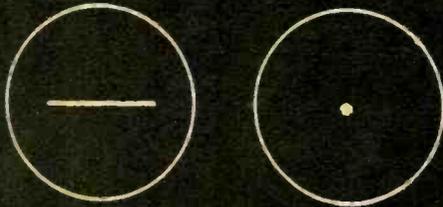


NO CARRIER

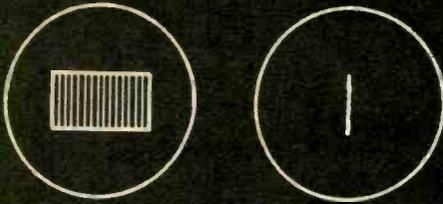


CARRIER ONLY

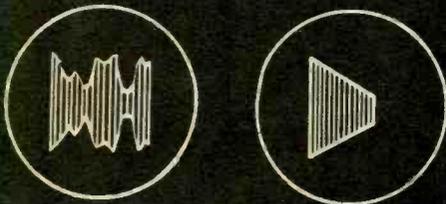

UNDER 100% MODULATION

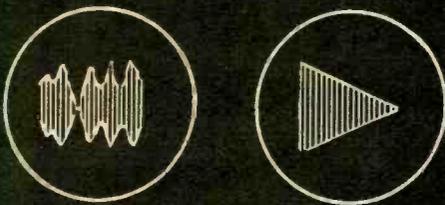

100% MODULATION

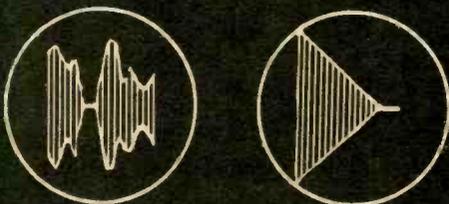

OVER MODULATION

on positive peaks the trapezoid height will be more than double, but this is not important since it is the negative modulation which requires attention. The bright tail line indicates negative overmodulation—the longer the tail, the greater the overmodulation.

Optimum modulation occurs when the modulation peaks just reach 100%. A trapezoid which fails to double its size and doesn't come to a point on the baseline indicates less than 100% modulation. Actually, many CB rigs are designed for 85-100% modulation and this will be indicated on the trapezoid as just missing 100%. We suggest that you don't attempt to improve it.

By setting S3 to MW a modulation waveform will be displayed. Actually, the MW is not as effective as the trapezoid for determining modulation percentage because the MW is a constantly changing jumble of frequencies. (The MW has value for tone tests.) However, a doubling of the carrier height again indicates 100% modulation as does a collapse to the baseline. At 100% negative modulation tiny bright spots appear on the baseline (with the scope on maximum horizontal gain). If short bright lines instead of spots appear on the baseline you are exceeding 100% negative modulation. The lines are equivalent to the trapezoid's tail. The major advantage of the MW function is that it displays noise which may be present. Unmodulated RF appears as a wide pattern with clean edges. Noise, such as caused by a defective mike pre-amp plate resistor, will appear as random spikes on the edges of the pattern. Hum will appear as ripples on the edges, etc.


While the CitizenScope helps you obtain maximum effectiveness in terms of per cent modulation, it also helps tell you what the modulation *quality* is. Other types of modulation indicators cannot do this.

You'll notice that at 100% modulation the sides of the trapezoid are straight and that the positive peak is exactly double the unmodulated carrier height. This condition indicates a distortion-free modulating signal which has adequate power for 100% modulation.


If the negative modulation drives the pattern to 100% but the positive modulation flattens out and then slants downward before the carrier height doubles, the modulator is under-powered. Not only will your output signal then be under-modulated, but the modulating waveform will be distorted. Even though the speech amplifier and modulator may have checked out as distortion-free, the signal is being distorted through the process of modulation. Without a scope you might never detect this condition.

Insufficient RF drive to the final is another cause of distorted modulation. This type of distortion looks similar to the pattern caused by insufficient modulation power. However, instead of flattening out and then slanting down, the trapezoid pattern caused by insufficient RF drive only flattens out. Again you have a picture of distortion which is being added to the signal by the modulation process.

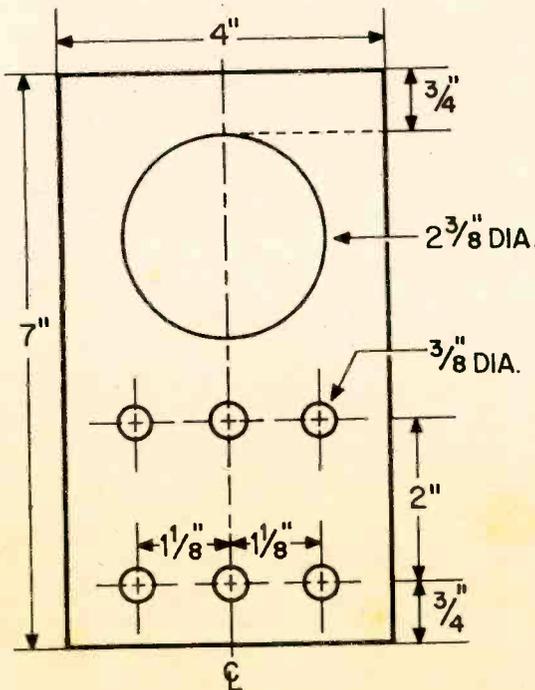Parasitics, which are spurious signals produced by the transmitter, can also



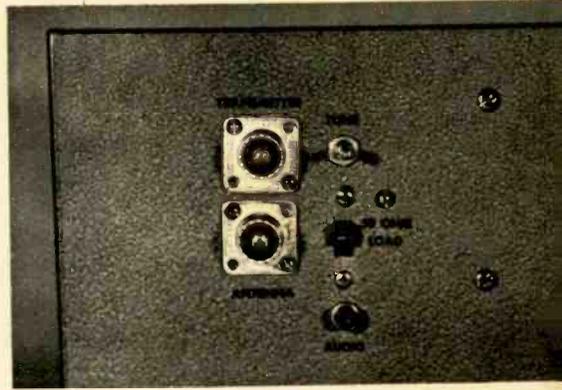Layout of CitizenScope's front panel controls.



Side panel rear showing jacks J1, J2, load switch S2 and input coil L1's slug tuning adjustment.


be indicated by the trapezoid. UHF parasitics which can produce TV interference may be indicated by a fuzzing of the trapezoid. This appears as a halo or fringing of the pattern. Parasitics, at or near the fundamental 27-mc frequency may appear as spikes.

While you might assume that parasitics being spurious frequencies have no effect on modulation, they are part of the trapezoid and that means that at the receiving end your modulation is distorted.

As you can see the modulation process is complex. One cannot connect a low-distortion modulator and then automatically assume there's good audio quality—lots of things can go wrong between the modulator and the final signal. Only a scope can give a visual picture of the complete signal.

Space prohibits detailing all the information which can be obtained from the patterns. A thorough discussion of trapezoid and modulated wave modulation patterns may be found in the Radio Amateurs Handbook.

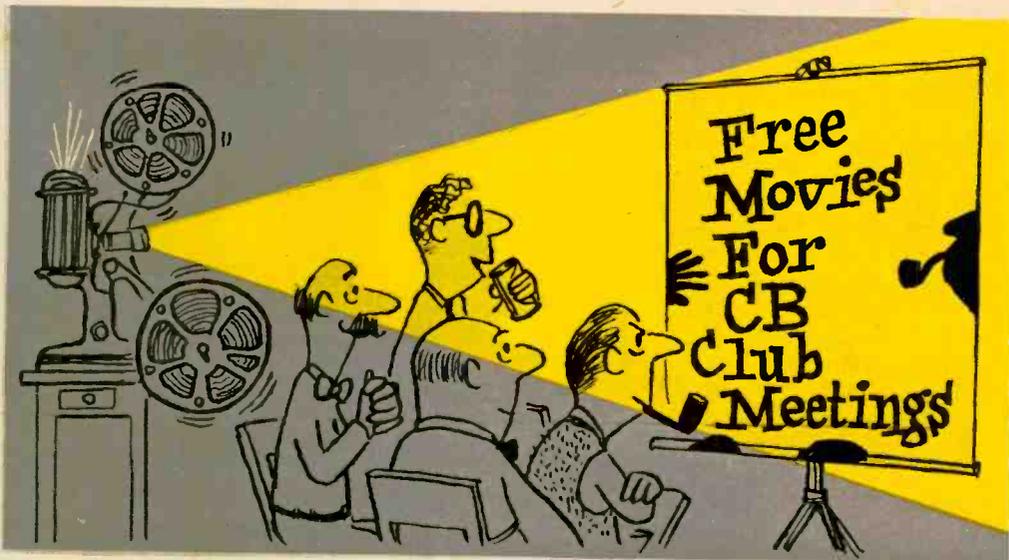The CitizenScope may be left permanently connected in the transmission line, permitting continuous monitoring. Connect the transmitter to J1 and the antenna to J2. Set S2 so the dummy load is out of the circuit. Adjust L1 for minimum SWR (standing wave ratio) or maximum field strength reading from the antenna. When L1 is properly adjusted the CitizenScope will have no adverse effect on SWR.



There's nothing like specialized flickers to heighten interest!

By Vernon Simms

IF YOUR Citizens Band club has ever shown a motion picture, you know there's some truth in the old Hollywood chestnut about there being magic in movies. There *is* magic in them when it comes to arousing enthusiasm on meeting nights.

Just any movie might help bring 'em in, but your films should be selected to cater to your club's special interest in electronics. Fortunately, scores of movies of this type are available to CB clubs, usually free of charge. A few postal cards can bring you complete information.

A veritable bonanza of instructive (and at the same time entertaining) motion pictures is offered by large corporations, public utilities, industrial associations, universities and other organizations. They are delighted to lend films for exhibition at club meetings.

Unlike sleep-provoking home movies, non-commercial films are slick productions created by professionals, often big-name pros. Consider, for example, a two-part epic called *Basic Electricity* and *Basic Electronics* which is offered by Minneapolis-Honeywell. It was produced by Walt Disney and uses the fa-


mous Disney animation to bring theory to life in full-color cartoon style. There's also a minor cartoon extravaganza put together by General Motors. This one shows the proper use of some dozen hand tools.

But the bulk of the movies you can get place less emphasis on entertainment and more on straightforward education. Take the films used by the Navy for training radio technicians. This is a 16-part series that presents electronic fundamentals in lucid fashion—everything from audio oscillators to how to use a volt-ohmmeter. The Navy will send you all 16 reels at no charge. Not to be outdone, the Army makes available its series called *Electricity and Magnetism*. Other films explain tuned circuits, telephony, FM and how radio waves travel.

Whether you secure films from government or industry, the procedure is approximately the same. First step is to send for the catalogues, which describe titles, running time, subject matter and ordering procedure (see list at end of article). Industrial organizations work in a slightly different manner. The Scientific Apparatus Makers Association, for instance, forwards a Loan Film



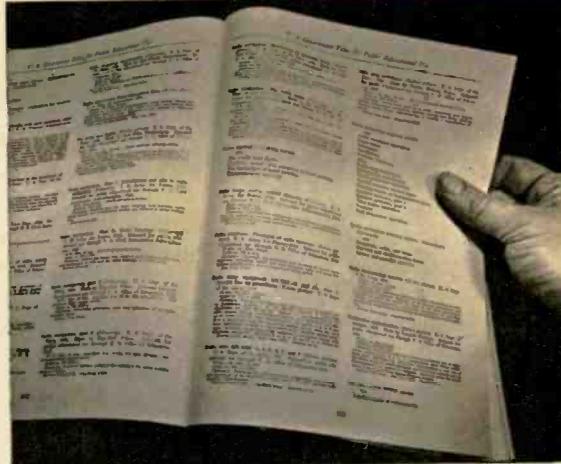Easily obtained film catalogues describe movies in detail, give running time, size, other data.



The biggest listing of pictures available is a government tome with 500 pages and 5,000 films.

Directory that describes the films and gives names and addresses of member firms, which supply the actual reels.

One of the best single lists of non-commercial films is a 500-page catalogue published by the Department of Health, Education and Welfare. It details some 5,000 flickers, telling what they are and where to get them. A copy can be had for \$2.75 from the Government Printing Office (ask for U.S. Government Films for Public Educational Use; No. OE-34006).

Whatever the source, movies usually are sent free of charge on condition that you return them within 48 hours after showing and pay return postage (ask the post office about special low rates for film shipments). The lender often sends along an attendance form for you to fill out. In a few cases a modest fee (usually about \$5) is charged for handling.

When procuring films, remember that other organizations are doing what you're doing. You may not be able to get what you want immediately. The Walt Disney opus, as an example, normally is booked solid for months.

There's one more obvious step between you and a club movie: a projector and screen. By far the most popular non-com movie type is the 16mm color film with sound and a running time of about 30 minutes. If no one in your club has access to a suitable projector, you prob-

ably can rent one at a local photo shop for about \$6 an evening.

A good place to start in your search for interesting movies is your local light & power company, the telephone company, your public library and your state university. Here are some of the organizations which provide catalogues of their films:

Information & Education Dept.
Aetna Life Affiliated Companies
151 Farmington Ave.
Hartford 15, Conn.

Motion Pictures
Advertising Dept.
E. I. DuPont de Nemours & Co.
Wilmington 98, Del.

GM Motion Pictures
General Motors Film Library
GM Building
Detroit 2, Mich.

Superintendent of Documents
U. S. Government Printing Office
Washington 25, D. C.

Institute of Visual Communications
40 East 49th St.
New York, N. Y.

Encyclopedia Britannica Films
1150 Wilmette Ave.
Wilmette, Ill.

Center for Mass Communication
Columbia University Press
1125 Amsterdam Ave.
New York, N. Y.

Scientific Apparatus Makers Assoc.
20 North Wacker Drive
Chicago 6, Ill.

Visual Aids Service
University of Illinois
Champaign, Ill.

Office of Information
Dept. of (Army, Navy, Air Force)
Washington 25, D. C.

Films Incorporated
Wilmette, Ill.



MODULATION METER for CB

By Herb Cenon

DO OTHER operators on the Citizens Band bug you about overmodulation, undermodulation or distorted modulation? You can squelch them once and for all with EI's low-cost modulation meter.

In addition to standard monitoring applications, a modulation meter is almost a necessity for adjusting speech clippers and compressors. Unless monitored, clipper/compressors frequently cause overmodulation because of their built-in microphone preamplification. While a meter is not as accurate as a peak-voltage indicating device (such as an oscilloscope), its rock-bottom cost (\$5 to \$6) and simple construction make it attractive for general CB use.

Construction. The modulation meter is built on the main section of a 5¼x3x2½-inch Minibox. Meter movement M1 is centered on the front panel in a hole cut with a 1½-inch chassis punch. Wiring is not critical but be sure that S1 is hooked up correctly or M1 will blow when the unit is turned on.


The modulation meter is connected to the transceiver's chassis ground and through capacitor C1 to point X, where the modulated B+ feeds the plate and screen of the final RF amplifier (see schematic). Mount a phono jack (J1) on the rear of your transceiver and capacitor C1 between the jack and point X as shown.

Operation. Plug the modulation meter into J1 on the transceiver and set S1 to *calibrate*, which connects M1 across R3. With the transmitter on, use a VOM or VTVM to measure the DC voltage between point X and ground. Next, set the voltmeter to the AC range leaving it connected to point X. If you're employing a VOM it will be necessary either to use the *output* jack of the instrument or to connect a .05 mf, 600 V capacitor between the positive test lead and point X.

Now, feed a 400 or 1,000 cycle tone into the microphone jack. (The tone can be obtained from an audio generator or the AF output of an RF signal generator.) Adjust the tone level so the AC voltage at point X is .707 of the DC voltage. For example, if the B+ voltage is 200 volts, adjust the tone level for an AC voltage of 141 volts (.707x200=141). Next, adjust R4 so M1 reads 100% (same point as 0db on the meter face). The modulation meter is now calibrated.




Set S1 to *modulation* (M1 connected across R2 and R3) and the meter will read voice modulation percentage directly.

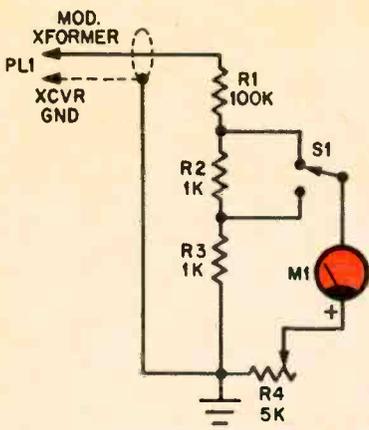Calibration control R4 can adjust for transceivers with B+ voltages between 175 and 250. If your rig uses a B+ lower than 175 volts, drop R1 to about 75,000 ohms. If the B+ is above 250 volts, raise R1 to 125,000 ohms.




PARTS LIST

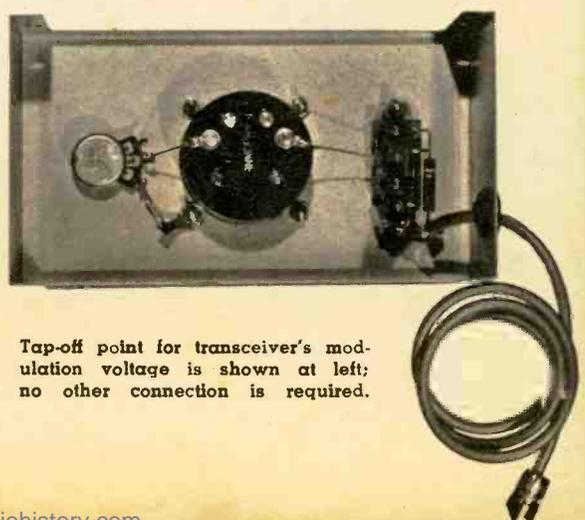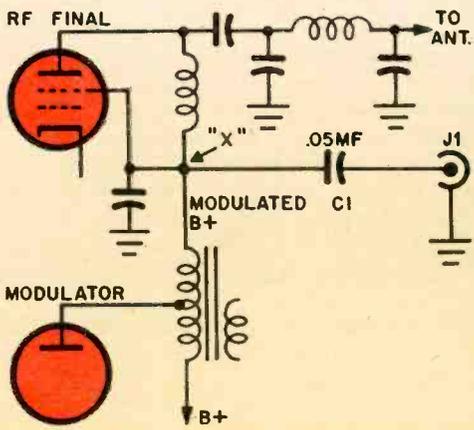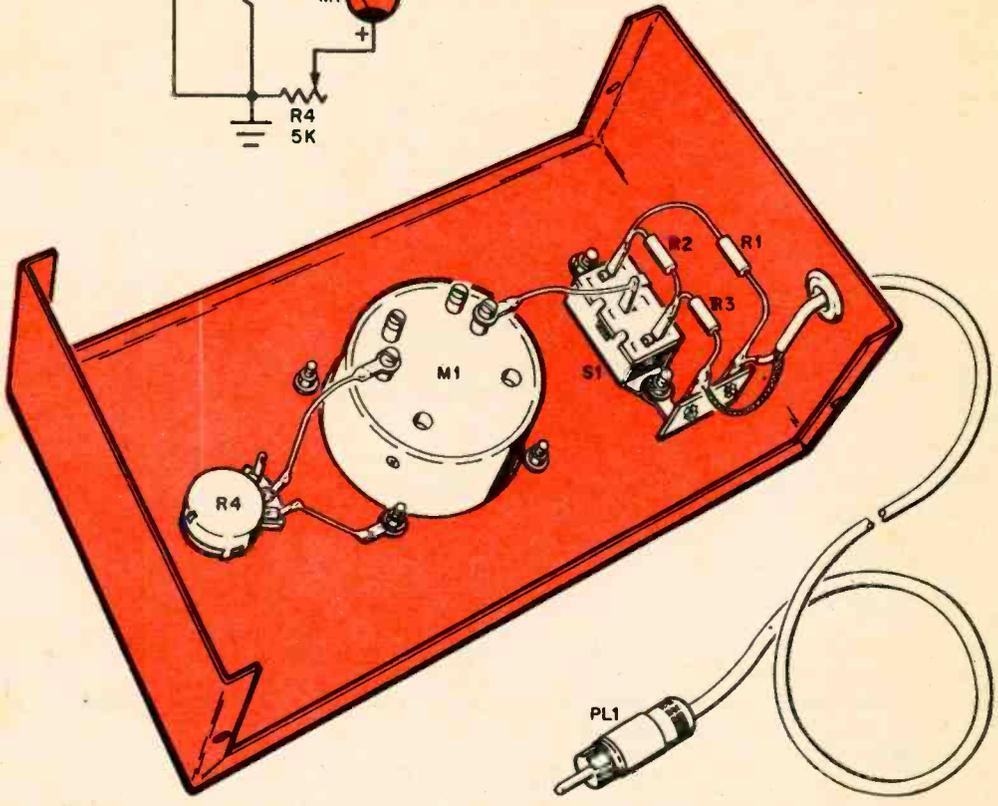R1—100,000 ohm resistor (see text)
 R2,R3—1,000 ohm resistor, 1/2 watt, 5%
 R4—5,000 ohm pot
 C1—.05 mf, 600 VDC capacitor (installed in transceiver, see text)
 M1—VU meter, Lafayette Radio TM-10 (Calibration may not be accurate for any other meter)
 J1—Phono jack installed on transceiver (RCA type)
 PL1—Plug to match J1
 Misc.—Minibox, terminal strips, etc.



Tap-off point for transceiver's modulation voltage is shown at left; no other connection is required.

How to MAP YOUR SIGNAL PATTERN

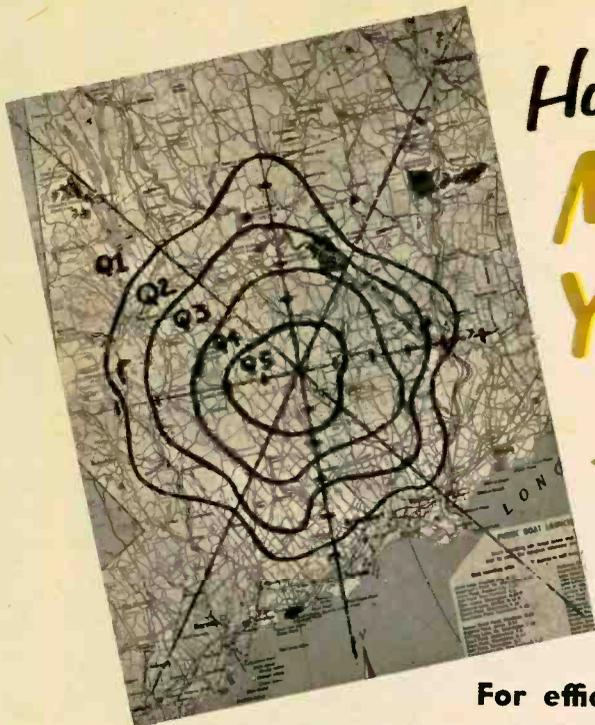

By Charles O'Neil

**For efficient mobile-base operations,
take a leaf from the book used by the broadcast boys.**

YOU can take the guesswork out of your Citizens Band operations with a signal contour map. Pinned on the wall of your shack, the map will tell you at a glance about the effective coverage you can expect in mobile-to-base operations, where your signals are readable and where your fizzling-out points are. It can answer such a specific question as where to locate mobiles for reliable coverage at a parade, Civil Defense drill or other special event.

A signal contour map (see photo above) is by far the best way to display a certain kind of data. It's the type which informs you immediately that a mobile at point A in your groundwave coverage area should give you an S-9 signal-strength reading at your base station, or an S-5 reading if it's at point C.


You can keep this kind of dope in a notebook but finding exactly what you want at the moment it's required is not easy in most communications rooms.

The map is fine for technical purposes, too. You can run comparisons between old and new antennas, transceivers and changes in antenna height. The map shows you differences in clear-cut, before-and-after figures. It also

gives warning of impending trouble. When a tube starts to fail in a mobile rig, for instance, indicated signal strength won't agree with what your map tells you. You know something's wrong.

Preparing a signal contour map is nothing new. Broadcast stations do it regularly to prove to the Federal Communications Commission that their coverage stays within licensed limits. No such requirement is tacked onto CB, of course, and few CBers have ever tried the technique. But it can be extremely useful.

The basic approach is painless. You procure a map of your area and mount it on cardboard (see photo). On a plastic overlay you put a dot at your base station's location, then crisscross it with eight radial lines as shown in our lead photograph. The radials show up like spokes on a wheel whose hub sits on your base station. After signal-strength readings from all areas are gathered, contours are drawn to link up readings of equal strength. The result is a series of irregular circles which picture the signal as it falls off with distance or obstruction.

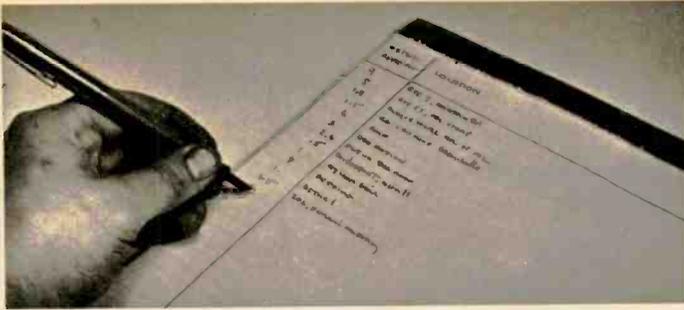

Basic information needed for preparation of a signal contour map is gathered by jotting down signal-strength readings from various geographical points in your coverage area. S-meter numbers, shown in the left column, are transferred later to signal-pattern map. Get readings from as many locations as possible, and in all directions from base.

The broadcast boys hop in a car and drive for days to compile their readings with field-strength meters. It's much easier in CB. You simply record readings over several days or weeks while engaged in normal operations with your mobile units.

After experimenting with charts printed by the U.S. Coast & Geodetic Survey, we found the best map for the job is the everyday road map. It affords the most convenient means for pinpointing the location of a mobile because streets and roads are shown. As a car travels along the driver can report his location in unmistakable terms. For instance, if he says, "I'm at the junction of Route 7 and Mountain Road," you can put your finger on his position instantly.

It's interesting, however, to have on hand the USC&G chart for your area. It contains topographical information, such as terrain height, which helps explain why the signal is blocked in certain locales.

First step in preparing the map is to accumulate dozens of signal-strength readings from your mobiles. If the base rig has an S-meter, you're in business immediately. All readings can be taken in S units.

If you have no S-meter, it is possible to add one with a modest investment of time and money (see ADD AN S-METER, May '62 EI).


As another alternative, you can use a VTVM to take signal-strength readings. To make the instrument work as an S-meter, hook it to the automatic-volume-control (AVC) circuit in the receiver (see schematic on the third page of this article). Switch the VTVM to the DC minus function and use the

lowest range that will provide maximum deflection (this may be the 15-volt range for strong signals and lower ranges for weaker ones).

The VTVM's common probe goes to chassis ground. The other probe is connected to point A or point B. The latter may be easier to find. First, locate the last IF transformer. It usually will be found between the last IF amplifier tube and the detector tube. Point A is the lug on the IF transformer to which are connected a 1-megohm or higher AVC filter resistor (R_f) and several other components.

Point B is located after the AVC filter resistor. Filter capacitor C_f usually is .05 mf.

It is possible to use a 20,000 ohms/volt

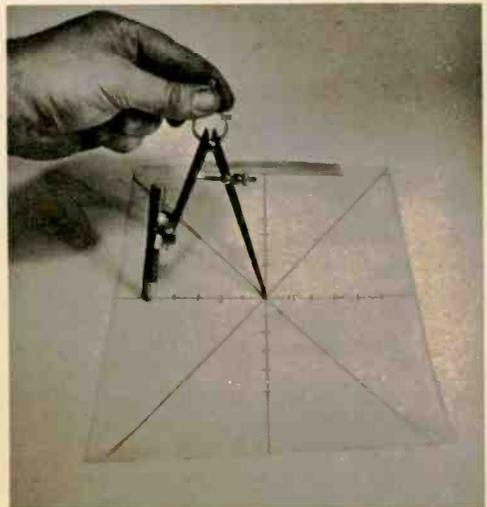


On plastic overlay, shown detached from map for clarity, 8 radials are drawn from location of base; 2-mile range marks are being added here.



A regular road map is best for showing signal pattern; mount it on cardboard and hang on wall.

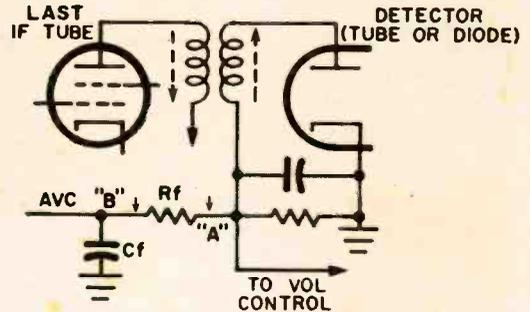Finding AVC for voltmeter connection (see text).



or higher VOM for this job but the instrument creates some loading problems. The level of all readings will be reduced and weak signals may be lost.

With provision for taking readings completed, set aside a sheet of paper in your shack for tabulating readings from mobiles over a period of time. A typical sheet (see photo) lists numerous geographical points in all parts of your coverage area, e.g., NE corner Swope Park, Broadway-Main, Highway 40-Leeds Rd., etc. Beside each you write the meter reading you get when one of your mobiles is in that location. Try to get readings from as many directions as possible. The accuracy of the final map depends on the number of points, so the more the better.

This information can best be transferred to the map by using a transparent plastic overlay, which is mounted right on top of the map with tape. The overlay serves several purposes. If you switch antennas or mounting height, or change some other factor which might alter your reception pattern, it's easy to remove one overlay and put down another.

Our photo shows you how to prepare the overlay, and the lead picture shows the overlay in place on the map. Using a grease pencil or some other instrument capable of writing on plastic, put a dot over your base station's location and crisscross it with eight radial lines. Range points then are marked on each

radial at two-mile intervals.

Mark in the meter readings you have collected, writing the S numbers over the proper locations. When this is completed, a characteristic pattern will be noted. Readings of the same value tend to be located at the same distance from the base station. Now draw lines to link up readings of equal value. The result looks like barometric pressure lines on a weather map—a series of distorted circles around your base station.

Interpreting the map is simply a process of noting signal strength within any area. Each circle represents a contour of RF energy, which drops steadily as distance rises. The warping of the pattern indicates intervening hills, buildings or other high structures. The map we show is for a specific area. Yours will be different. You might, for example, find a completely dead signal pocket quite close to your base station. It should be circled independently of the contour lines. Dead areas will be well defined if enough readings are taken during preparation of the map. A final refinement is the addition of Q signals in each contour.

Q signals represent signal performance in practical terms of readability. The Q code is as follows:

- Q1—Unreadable.
- Q2—Barely readable.
- Q3—Readable with difficulty.
- Q4—Readable with little difficulty.
- Q5—Perfectly readable.

The Electronic Catalog of the Year BY POPULAR DEMAND!


over 1,000,000
new friends—
amateurs, pros,
hi-fi devotees,
hams—
have already
sent for it!

**EASY
TIME
PAYMENT
TERMS**
take up to
2 years
to pay

284 PAGES
OVER 10,000 ITEMS

Partial list of products in our New 1963 Catalog

- | | |
|---|--|
| <ul style="list-style-type: none"> • Amateur Radio • Antennas • Batteries • Books • Capacitors • Controls • Hi Fi • Microphones • Needles • Phonographs | <ul style="list-style-type: none"> • Public Address • Radios • Resistors • Tape Recorders • Test Equipment • Tools • Transformers • Transistors • Tubes • Wire |
|---|--|

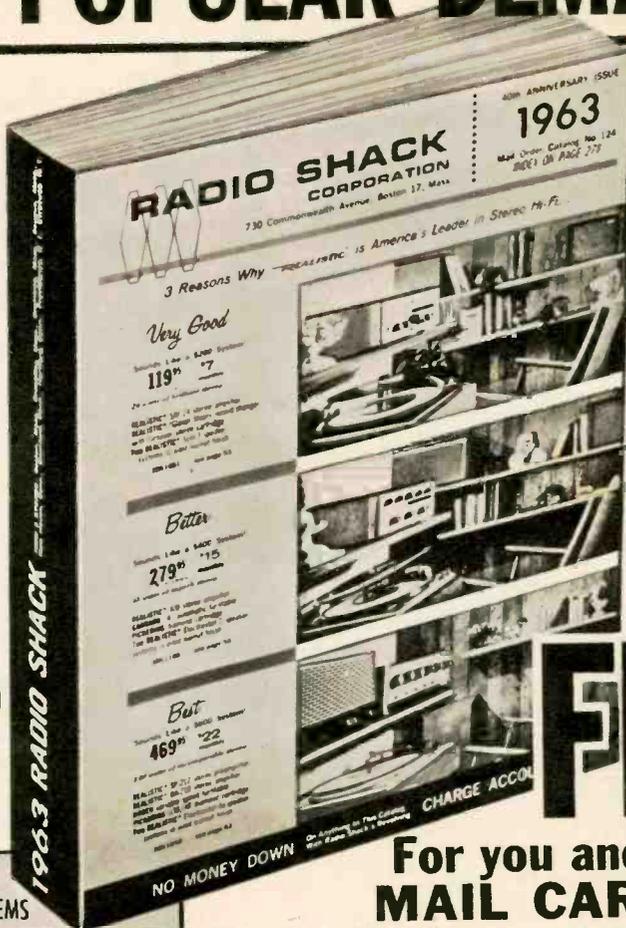

**YOU CAN
STILL GET
RADIO
SHACK'S
GREAT NEW 1963
Electronic
CATALOG**

FREE

**For you and 2 Friends
MAIL CARD TODAY**


Yes, over 1,000,000 brand new friends have been added to the millions who shop regularly from Radio Shack's big catalog but we want everyone interested in electronics to have this great money saving shopping guide so we've printed 500,000 more for you and your friends. Mail the card opposite today and get your share of the newer and better things in electronics in this fine new book.

Whether you are a music devotee, a radio ham, a professional operator, or just interested in the great world of communications as a hobby, you'll be excited and delighted with the vast assortment of precision-built, high-quality, guaranteed products in Radio Shack's famous catalog. And you'll save too as you never saved before. Our easy credit terms make it convenient and simple to buy what you want when you want it and pay later. Mail the card opposite now!

RADIO SHACK CORPORATION 730 Commonwealth Ave.
BOSTON 17, MASS.



ADD A HANDSET to your transceiver

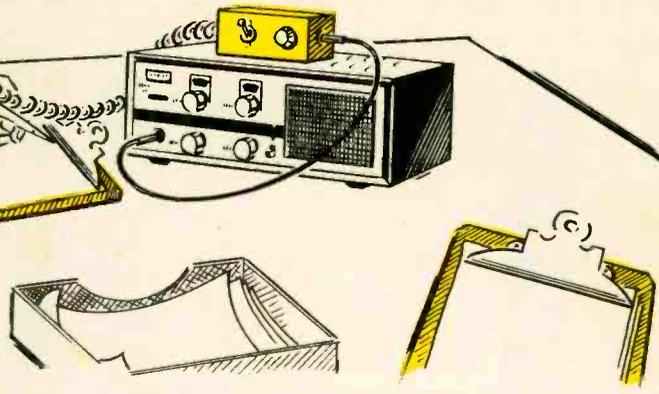

Give your Citizens Band rig the look and convenience of a radiotelephone with this easy and inexpensive modification.
By Gerald Wainwright

To insure privacy or to cut background noise, a handset hooked up to your transceiver is a decided convenience. Handset installation is relatively easy since only minor modifications to your rig are required. It's only necessary to open one speaker lead and to connect the speaker and output transformer leads to a jack or tie point.

The heart of the modification is in a separate control box which permits either normal or handset operation. In one


position S1 connects the speaker to its original wiring. In the other position the speaker is disconnected and the transceiver's output transformer feeds the handset via R1 and R2. R1 supplies the proper transformer load and R2 adjusts the handset earphone to a comfortable volume level.


The handset is a surplus unit avail-

The standard handset must be modified by replacing the mike element and rewiring its output cable.

PARTS LIST

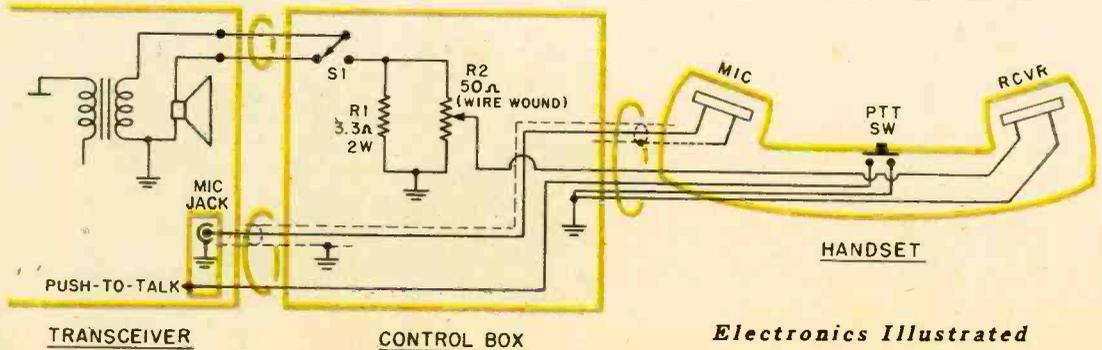- R1—3.3 ohm, 2W, 20% resistor
- R2—50 ohm wirewound potentiometer
- S1—SPDT toggle or slide switch
- Misc.—Handset (see text); microphone element;
- 1 cable—4 conductor plus one shielded conductor; cabinet, any convenient size



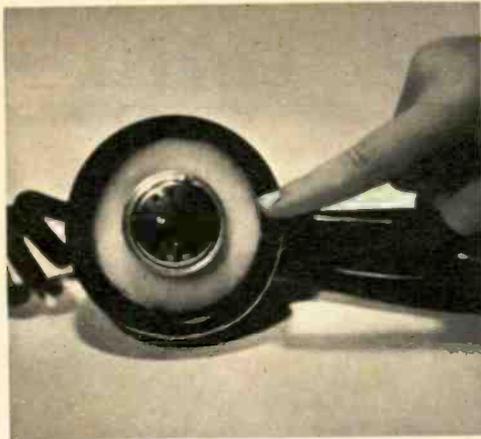

Replacement microphone cartridge is bedded down in foam rubber. This both provides a snug fit and protects the element against impact damage. Connection to element is made via soldering lugs.

able from Radio Shack, Olson Electronics and elsewhere. The handset microphone is a carbon and it must, therefore, be replaced with a ceramic/crystal or dynamic element. Since the new element requires a shielded lead, you can avoid a rat's nest of wires coming out of the handset by using a retractile coil-cord having four conductors plus a shielded lead, such as Alpha type 696/2.

The new cable from the handset can be led through a grommeted hole in the control box. The output cable from the control box includes a shielded mike cable plus the push-to-talk control lead (s). These could terminate in a plug matching the mike jack on your rig. The two other wires from S1 to the transceiver's speaker can be ordinary zipcord.


Cement the new mike element as shown to a piece of foam rubber, install the new handset wiring and then cement the rubber-mounted element into the handset. Make sure that solder doesn't fall into the mike's air relief holes. The earphone element need not be changed.

To hear an incoming signal set S1 to *normal*. When you hear your unit number called, reset S1 to *handset* and you've got telephone convenience. ●

March, 1963

11 METERS IN CANADA

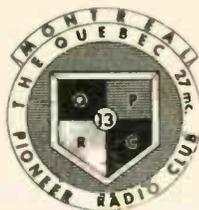To judge by the first few months of operation, the 11-meter General Radio Service in Canada is experiencing many of the problems faced by



the Citizens Radio Service in the United States during its early days. There are other similarities, too. The GRS, a year old next April 1, already has picked up the Citizens Band

nickname from U. S. operators.

In its first six months, Canadian CB saw the issuing of 8,691 licenses, and 30 manufacturers (some of them U.S.) got type approval for their equipment. The Department of Transport, counterpart of the Federal Communications Commission, announces solemnly, "We have received no reports of violations." But, as the FCC learned long ago, the official reports don't always give an accurate picture of what is going on in the world of short-range radio.


CB CLUB DE LA PROVINCE DE QUEBEC

DISTRICT DE MONTREAL
985 AVENUE BISEAU - MONTREAL 40
TEL. 861 1921

As a matter of fact, a goodly number of Canadian CBers have been making like hams by transmitting CQ calls. And they also are working skip stations. These problems, however, do not appear to be as serious as they once were on this side of the border, probably partly because of the relatively small number of licensees. At this point it is not yet clear whether the GRS will become a mostly-business band or a mixture of businesses, personal users and pseudo-hams.

[Continued on page 114]

TRANSMISSION LINE

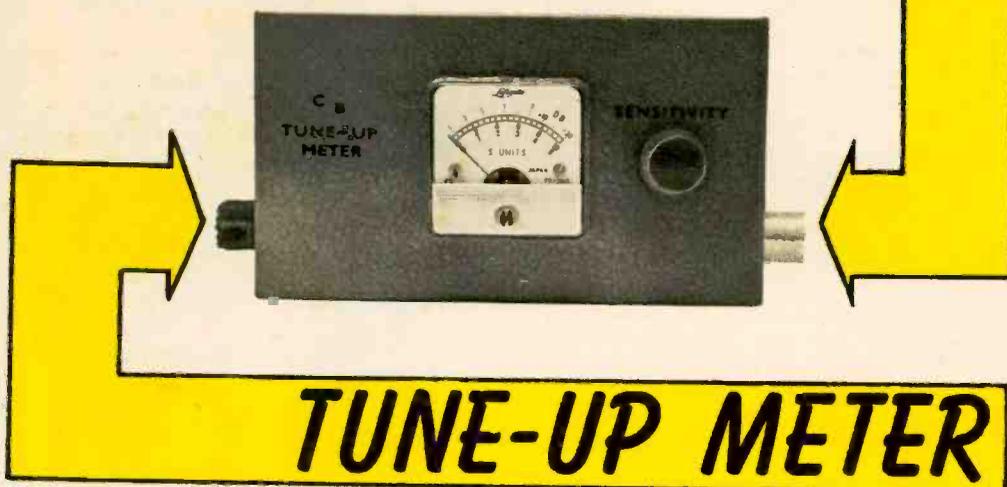

By Al Toler

OF ALL the methods used for tuning a CB transmitter only the SWR meter (which measures relative power into the transmission line) and the field strength meter (which indicates relative power out of the antenna) are accurate indicators. Light bulbs, terminated power meters and plate input meters just can't do an accurate job.

Unfortunately, it's difficult to tune your transmitter while up on the roof with your field strength meter; and, the cost of an SWR meter somewhat limits its availability for CB. But now, EI's \$5 Inline CB Tune-Up Meter brings an accurate tuning indicator within the reach of all CBers.

The Tune-Up Meter samples the power fed into the transmission line. Since maximum power indicates maximum tuning, meter M1 will give the highest reading when the transmitter is tuned on-the-button. The Tune-Up Meter can be left permanently connected in the transmission line.

The Meter is built in the main section of a 5¼x3x2½-inch Minibox. Coaxial jacks J1 and J2 are mounted on the side panels as close as possible to the lower



rear corner. A piece of #16 bus bar (or a section of a coat hanger) connects J1 to J2. Connect it as direct as possible and don't use thin wire.

Connect R1 to sensitivity control R2 in such a manner that the top of R1 is ⅜-inch from the bus bar. Insulate R1's free lead with spaghetti and wrap it three times around the bus bar. Make certain the tip of R1's lead does not extend past the insulation.


Checkout and Use. Connect the transmitter antenna jack via a length of coax cable to either J1 or J2. The transmission line connects to the remaining jack. Energize the transmitter and adjust R2 for a convenient M1 reading. Then, adjust the transmitter tuning for the highest M1 reading. At peak reading the transmitter is tuned for maximum power output.

Note: M1's reading depends on both the power output and the transmission line's SWR. Its exact reading is unimportant since low power output and a high SWR can result in a high reading. Similarly, high power output and high SWR can read low. Only the fact that M1 peaks is important. ⚡

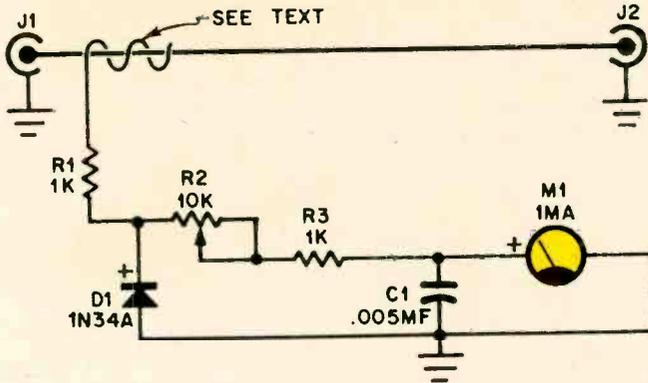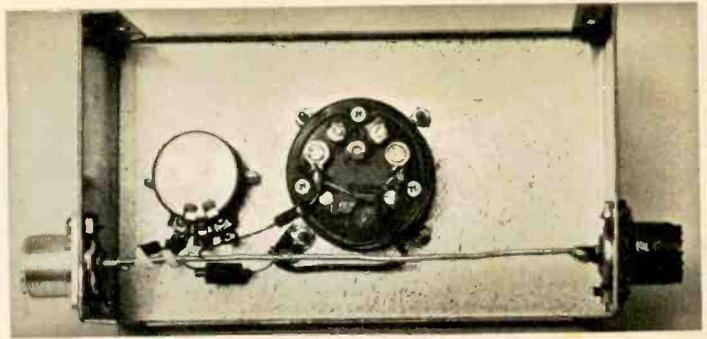
Almost empty Minibox is seen with cover off. Extra terminals on meter connect to its internal lamps which are not used in this application. Any type and size of 1-ma meter will serve.



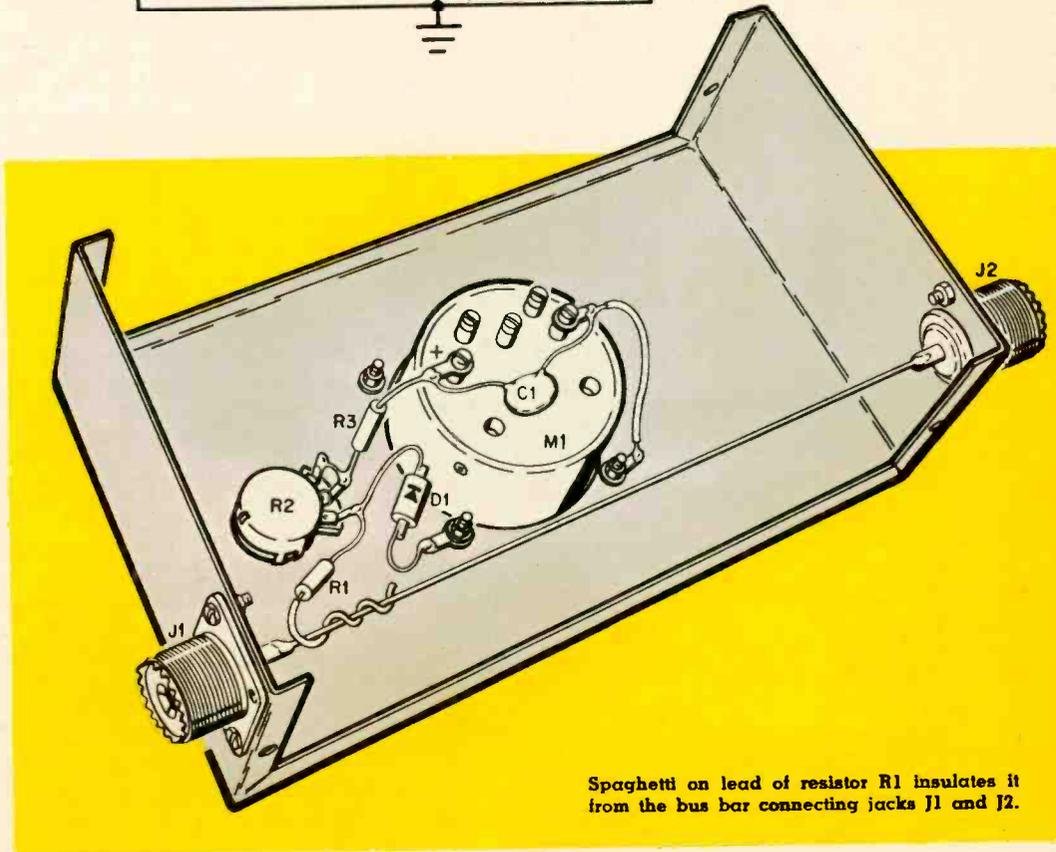PARTS LIST
 R1,R3—1000 ohms, 1/2 watt
 R2—10,000 ohm potentiometer
 C1—.005 mf, 500 VDC ceramic disc capacitor
 M1—1 ma DC meter movement, any type or size
 D1—1N34A crystal diode



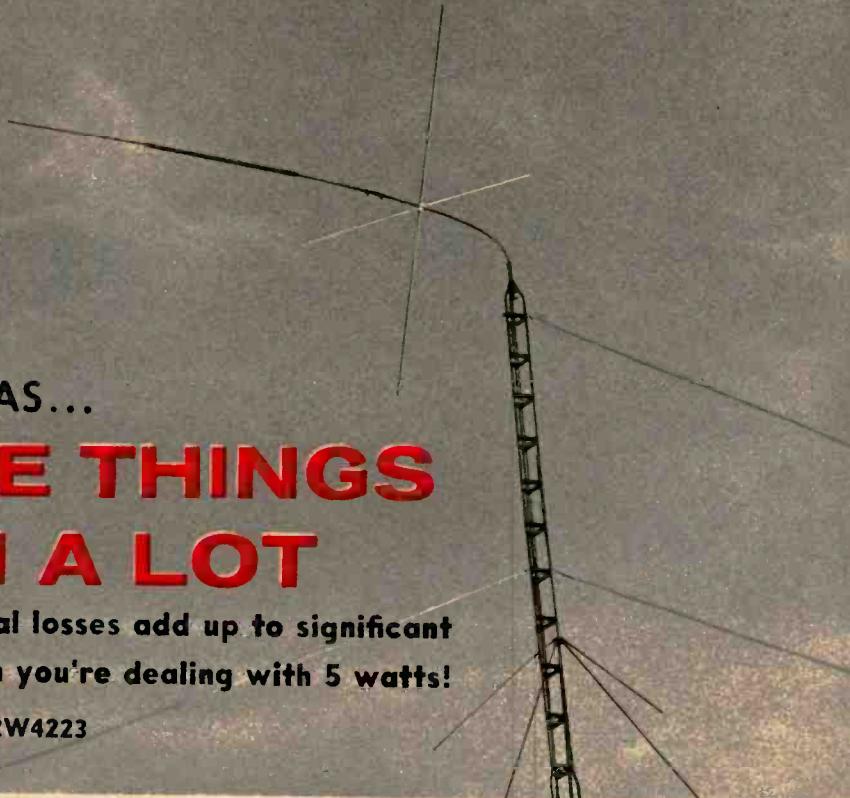Spaghetti on lead of resistor R1 insulates it from the bus bar connecting jacks J1 and J2.



CB ANTENNAS...

LITTLE THINGS MEAN A LOT

Those minor signal losses add up to significant proportions when you're dealing with 5 watts!

By Charles Tepfer, 2W4223

EVERY Citizens Bander knows that 5 watts input to the final of his transmitter doesn't mean 5 watts on the air. He's lucky if he gets something over 3 watts actual RF output. For decent coverage, you have to nurse what little power you have as if it were a rich old aunt making out a will.


The base station antenna is the most important factor but even the best sky-hook is at the mercy of the installation. It can't radiate power it doesn't get. The wrong kind of transmission line or bad connectors can be draining away power.

Most CBers use RG58/U coaxial cable as transmission line. It's cheap, easy to work with and has a characteristic impedance of 53 ohms, matching most base-station antennas. But RG58/U also has relatively high power dissipation due to resistance and radiation losses. It cuts your signal by 2db per 100 feet when dry, more when wet. The average 35-foot coax run to the roof of a one-story house means a loss of some .7db, which doesn't sound like much but converts to a whopping 15 per cent. On a 100-foot run, the loss amounts to a third of your 3-plus watts.


Fortunately, there's a simple remedy. Use RG8/U coax, which costs twice as much (about 12¢ a foot) but has only half the line loss.

Another of those little leaks that add up may lie in your automobile-radio-type connectors. Many transceivers, particularly those designed for car and base-stations use, come with this type socket. You'll find the same connector on your car's broadcast radio, and it works well because of high signal levels. But in CB the connector can be forced out of shape easily, destroying multi-point contact. Or it may separate from the coax braid if the set moves much.

The answer is replacement with threaded coax connectors, which is an easy job. Cut off the auto-type plug, strip off 1¼ inches of insulation, clip off ¾-inch of braid and take off ⅜-inch of inner insulation to expose the center conductor. The outer sleeve of the coax connector (with threads toward the end of the cable) then slides on. Solder the braid to the connector at the four holes provided, solder the conductor to the tip and work the outer sleeve back over the connector.

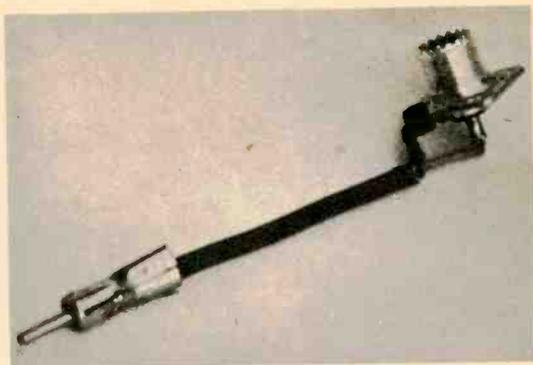

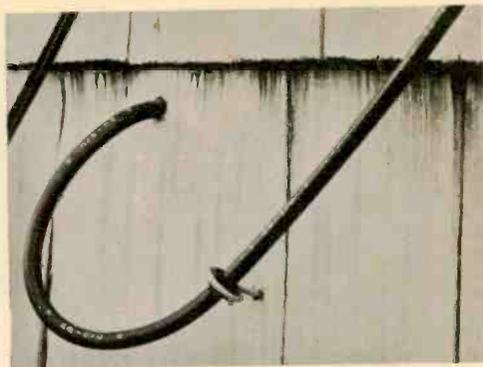A handy adaptor mating an auto antenna plug to coax socket is easy to make; connect with coax.



Drip loop where transmission line enters house drains off rain; note use of stand-off insulator.

Many transceivers have a punched hole for mounting the coax socket. The leads are then merely transferred from the old socket to the new one. Only the conductor need be soldered. If no hole is provided you can make your own ($\frac{1}{2}$ -inch diameter) with an expansion bit or hole punch. Drill four $\frac{1}{8}$ -inch holes for the mounting screws. Mount the new socket as close as possible to the old one.


A useful accessory, if you don't replace the old connector on your mobile, is an adaptor mating an auto-type plug to a coax socket. It permits switching a transceiver from car to base without disturbing the transmission-line coax connector. Use a short length of coax to join the two (see photo).

How the transmission line runs from antenna to transceiver is important for keeping down signal losses. If the line gets close to metal gutters or downspouts some RF energy may be drained away. Keep it a reasonable distance also from TV downloads, telephone wires and the like. TV-type stand-off insulators should be used to hold the line away from the wall. A drip loop where the line enters the house keeps the entrance hole dry by forcing moisture to drop off to the earth.


A lightning arrester, though it won't prevent signal losses, is a worthwhile safety measure. Run a heavy wire from the arrester to your ground rod.

A final safety hint concerns the antenna itself. Our lead photograph shows

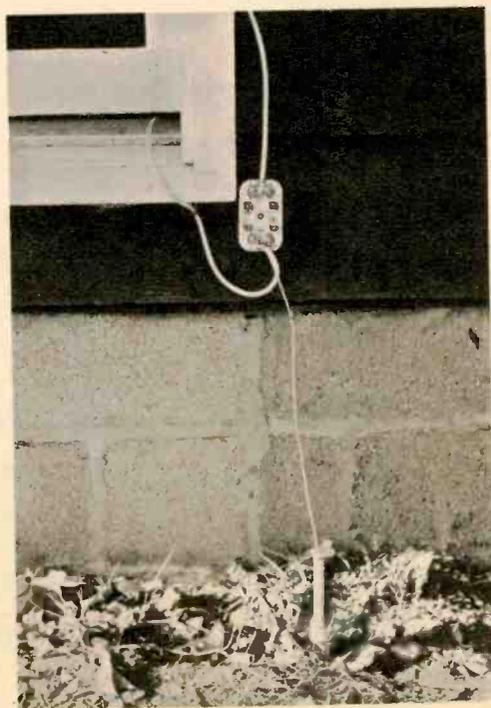what happened to an improperly guyed half-wave antenna in a high wind. Guying the tower wasn't enough here. The rig should have been guyed also right under the radials. The rule of thumb is a set of guys every 10 feet of height—three guy wires 120 degrees apart and all adjusted to equal tension. —



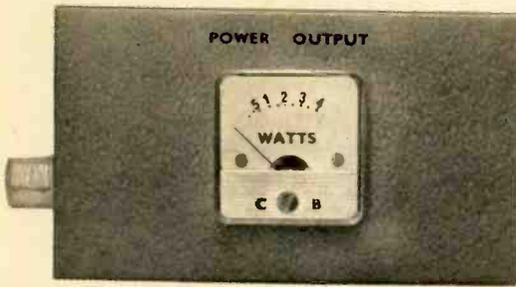Properly mounted lightning arrester with a heavy wire to ground rod. Coax is cut with this type.



DIRECT-READING POWER OUTPUT METER for CB


FOR transmitter tests and repairs, some means of measuring power into a dummy load is required. The EI CB power Output Meter will enable you to check output at a cost—about \$6—well below that of commercial power meters.

To avoid a separate calibration chart, a paste-on meter scale is provided. Note that it is accurate only when the instrument is built with the specified components. All leads should be short, with resistors R1 through R4 mounted as close as possible to J1. Use a heat sink, such as an alligator clip, on D1's leads when soldering.

When the unit is completed with M1


mounted, remove M1's cover by inserting a thin screwdriver blade under the top edge and prying upward. The plastic cover will snap off. Remove the two screws that hold the meter face in place and carefully slide the meter face upward to avoid bending the needle.

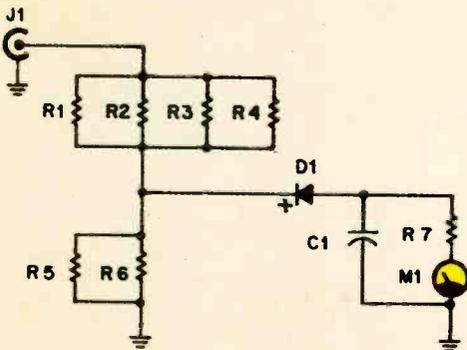Cut out the new meter face and glue it over the old face with a thin coating of slow-drying cement (such as Elmer's). Adjust the new meter scale to exact registration, install the meter face and cover. Assemble a short length of coax cable with plugs to connect the CB antenna jack to J1, and the power meter is all set.—Herb Cenan




Resistors R1-R6 comprise a 50-ohm dummy load for rig in test.

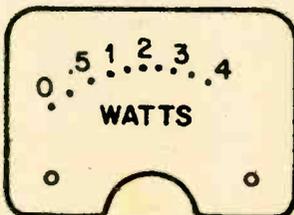
Meter face below should be cut out and cemented directly over the original S-meter dial face.



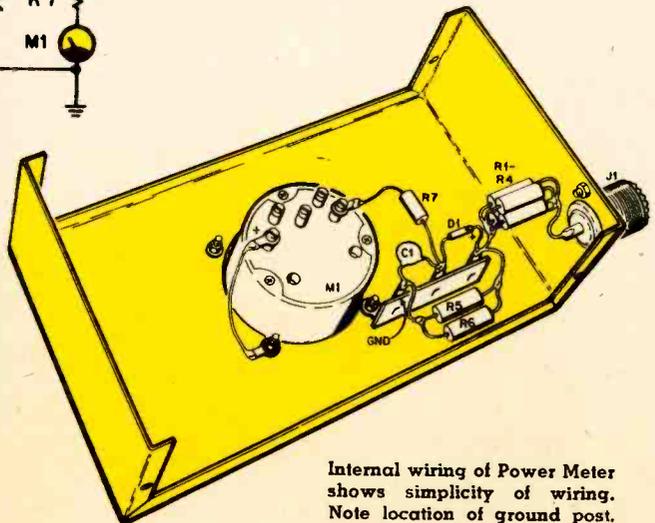- PARTS LIST**
- R1, R2, R3, R4—150 ohms, 1-watt, 5%
 - R5, R6—30 ohms, 1-watt, 5%
 - R7—6,800 ohms, 1/2-watt, 5%
 - C1—250mmf, 500 VDC (or higher) ceramic disc capacitor
 - D1—1N34A crystal diode
 - M1—0-1 ma S-Meter (Lafayette Radio TM-11)
 - J1—Coaxial jack
 - Misc.—Cabinet (5"x3"x2" approx.), terminal strips, etc.



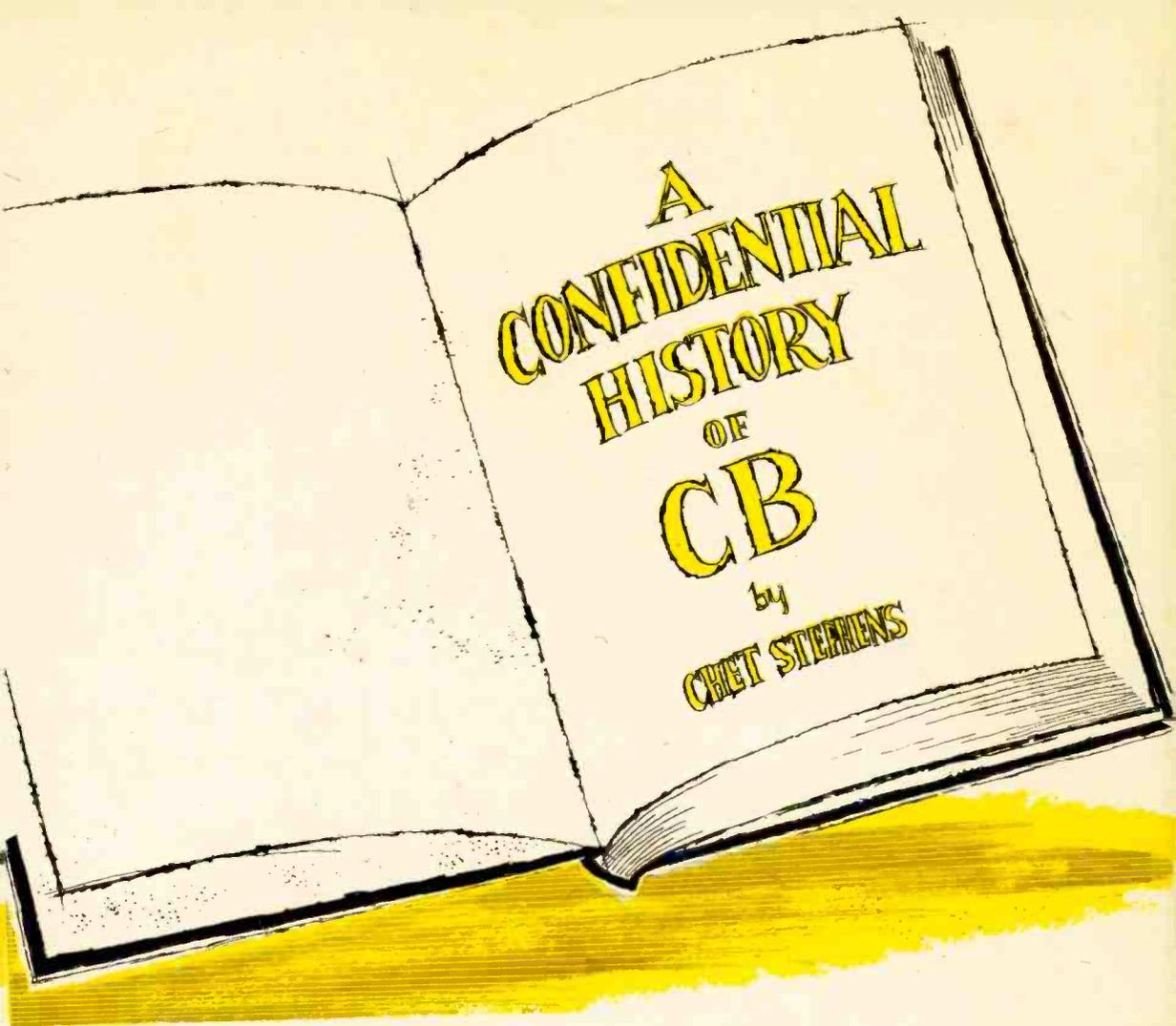Internal wiring of Power Meter shows simplicity of wiring. Note location of ground post.



“I WONDER who will be the first to issue a certificate for ‘WAS’—Citizens Band (WASCB)?”

Amongst all the millions of words written about the Citizens Band you’d be hard put to find any that have been more influential than those 16. They closed an article in the March 1959 Radio-TV News (now Electronics World), a magazine for electronic servicemen and hobbyists with a circulation around 242,000. The piece was by Don Stoner, now a CB equipment manufacturer in addition to being a writer, and it told how to build a low-cost transceiver for the Citizens Radio Service. His parting reference was to a certificate which might be won by a CRS user who contacted other stations in all states—the ham term for this being *Worked All States*.

As of this writing, and so far as we know, no CBer has qualified for or received a WASCB, a failure assuredly not due to lack of heart. Sometimes half the inhabitants of the band in our bailiwick seem to be trying for one. To those of you who have come late into CB (i.e., since Kennedy was elected), this assignment of credits for popularizing CB may seem strange, or we could simply be prejudiced in claiming wide influence for our own medium (magazines). To answer such doubters, let’s take a little tour of CB in its cave-man days. The Citizens Radio Service, to use the formal moniker invented by the FCC, is going on 16


years old. The band, conceived during the last year of the war, opened in 1947. It was assigned to the UHF frequencies between 460 and 470 mc. The event had approximately the same impact on two-way radio as the demise of a cockroach at Ft. Monmouth. The band was as unused as a spittoon at Vassar.

Effective September 11, 1958, the FCC created a new Class D CRS, giving it the chunk of 11 meters then occupied by hams. What happened? Nothing. The Citizens Radio Service dozed on, largely because few people had ever heard of it and even fewer realized its potential. Then came the Stoner article, and the dam burst. Hobbyists by the hundreds for the first time saw CRS as a new form of amateur radio with an examination-free license. Within weeks manufacturers were selling kit versions of the Stoner transceiver and, with the word spreading fast, CB/ham radio was off like a goosed gazelle.

That a couple of hundred thousand people had a concept of CRS which didn't jibe with the official view was not so much the fault of Stoner or the magazine as of Big Daddy in Washington. The FCC, in sweating out Part 19, sat and sat and then hatched a three-footed gooney bird. Never has a set of regulations been so loosely worded, and never has one left so many unasked questions unanswered. A single section, 19.2, has more loopholes than an IOU written on an ice cube. The regs for other services tell you everything but how to unclog the drain, but when it came to Part 19 the rules writers stabbed themselves in the back with their own ballpoints. Like the volunteer faced with his first parachute jump, they've been trying ever since to change that *maybe* to a *no*. The rules have been revised and re-revised, and they're still at it.

Part 19 represented the first time in history that licensees were, in effect, allowed to interpret FCC regulations. Previous regs, as we've said, were so specific that you had answers to questions you never got around to asking. But not Part 19. Here the wording was so loose that even well-intentioned Cbers were left in a daze. We won't attempt to analyze the whole bale, since a look at 19.2 (Definitions) makes the point. Among a few hundred other words, the FCC threw in *personal and business radio-communication* to tell us what CRS was for. The interpretations possible with those four words alone would make up another *Gone With The Wind*. A little later 19.2 says all Class D units are *mobile stations only*. Even base stations were classed as mobile. The idea apparently (to give our own interpretation) was to reserve CRS for use when no other means of communication was available. At home you'd use the telephone, not your CRS transceiver. But the term was not defined soon enough to head off misinterpretation, and still hasn't been fully defined.

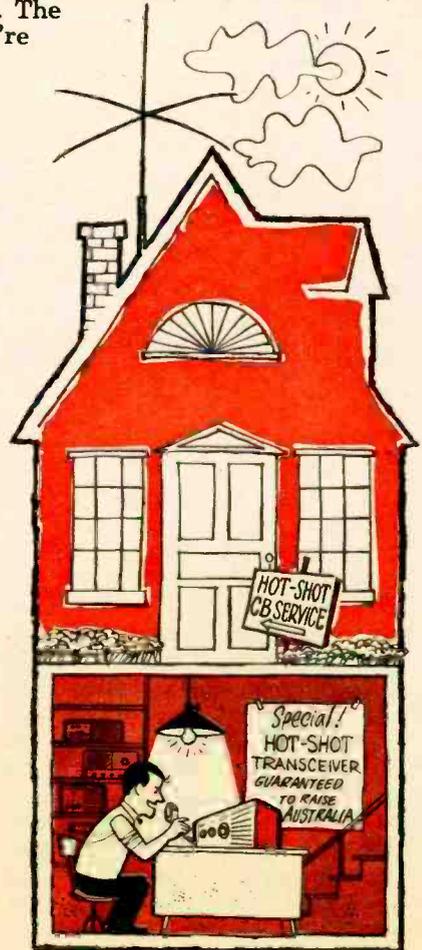After listening carefully to that mound of misinformation from the coaches, CB radio took a healthy swing at the ball and started running—right at third base. The band rang with CQ calls far into the night, and when word finally got around that somebody up there didn't care for that procedure, the hello-test gambit started. With all the testing, you'd



have thought there wasn't a decent piece of equipment on the band. They tested and tested, and talked and talked, even though few had bothered to learn much about this new miracle medium. Never was there so much technical discussion about something so few understood.

Legitimate CRS users found themselves drowned by the CB/hams. There actually were enough channels available but the superregen receivers of the time could be jammed from channel 1 to 23 by just one local talker, who droned on for hours.



The new breed of hams might have choked the band to death if manufacturers hadn't produced receivers with some selectivity. The early transceivers obviously had been designed for business use, having one to three channels crystal controlled. But the CB/hams soon modified them for multi-channel coverage and manufacturers, waking up fast to the fact that the talkers were the major market, started producing multi-

channel jobs with variable tuning (what business needs variable tuning?).

By late 1960 the Citizens Band, as it came to be called after Tom Kneitel gave it that name in *Popular Electronics*, was a disaster in the cities. In the country and a few urban areas, farmers and salesmen and the police had found CB useful. In the big cities the CB/hams had found it entertaining. Among other sad victims was a company set up to make custom installations of CB equipment for businesses in one community. An oil company was the first customer, and the last. The word passed around like a bottle of hooch at a football game. "If you're really in a fix, try smoke signals," the oil-company people advised everybody. "CB will only give you recipes and pseudo-science."

The curtain came down on 1960 with a farce known popularly as the FCC Hi-Fi Show, a rousing production that must have caused Olsen & Johnson to turn green with envy. The FCC suddenly had become fed up with the CB/hams, to the extent that one field office called in the worst offenders and played them tapes of their on-the-air conversations. Before the performance was half over the recipients of this special attention were shouting angrily that the FCC had violated secrecy-of-communications laws by letting the whole group hear the tapes. They skewered the G-men with a few four-letter words and walked out. At home they immediately fired up the old transceiver, broadcast the news of the day to everyone who could hear and then spent several weeks profaning the FCC on the air.

There were about three good reasons why the FCC didn't bash in a few dozen heads. Everyone realized that Part 19 was loosely worded and could be construed to mean nearly anything. Secondly, [Continued on page 116]





ALL ABOUT MODULATION

By Herb Friedman, 2W6045

A few facts to clear up the modulation mystery for CBers.

IF YOU LISTEN to all the talk about modulation in Citizens Band circles you might think most transceivers have difficulty producing signals that are even intelligible. That is far from the truth, of course. Most rigs now on the market are capable of good and efficient performance.

Modulation is something of a bugaboo to many CBers, however; they know it's important but are afraid it is too complicated to understand easily. They're likely also to believe *any* modulation system can be improved.

In reality, the facts you need to know about the system of amplitude modulation used in CB are relatively few in number and not a bit complicated. And, while it is true that some improvement can be made in many transceivers, you can't improve them all.

A CB transmitter consists of two basic sections: (1) a radio-frequency (RF) section, which generates a carrier signal capable of leaving the antenna and traveling through space, and (2) a modulator, which takes an audio (voice) signal and impresses it on the carrier. If the strength of the RF remains fixed, the loudness of the signal at the receiver is determined by the amount of audio impressed on the carrier—the more audio, the louder the signal.

This job of impressing audio on the carrier is performed at the plate of the RF power output amplifier tube (called the final). In most transceivers today this is a 6CX8, 6AQ5, 6AU8 or a 5763. When the audio signal is applied to the

final, it and the RF signal beat together. The result is a modulated carrier—a carrier plus two new signals. These signals appear as sidebands on the carrier.

If a 1,000-cycles-per-second, or 1-kc, sine wave (single frequency) is used as an audio test signal and the RF carrier is on 27 mc, the transmitter's output is the 27-mc carrier plus one sideband equal to the sum of the audio and RF signals (1 kc plus 27 mc = 27.001 mc) and another sideband equal to the difference between the two signals (27 mc minus 1 kc = 26.999 mc).

In the case of speech, we have a complex waveform to produce the sidebands and the audio is at many frequencies, but the addition-subtraction procedure still holds. It is the two sidebands—and only the sidebands—which carry speech intelligence to the receiver. As a matter of fact, only one sideband is detected to reproduce the original audio. The second sideband is a mirror-image of the first. Both it and the carrier just go along to the receiver for the ride, serving no useful purpose. (In single-sideband radio, which even now is starting to be used on the Citizens Band, both the extra sideband and the carrier are suppressed and all power is concentrated in the one sideband.)

We said earlier that the loudness of the signal at the receiver, if the power of the carrier remains constant, depends on how much modulation is applied to the RF signal. This is true—but only up to a point. There is a limit to the amount of *useful* modulation which can be applied. This limit is called 100 per

cent modulation. Actually, as we'll see, it is 100 per cent negative, or downward, modulation which is the limiting factor.

To show how a modulated signal is produced, we'll go back to the basic components. The drawings that follow are graphic representations of electrical waveforms. As in any text dealing with electronics, graphs or charts don't really show what happens. But they're the best visual aids we can produce to put across the ideas.

Figure 1 represents an RF voltage (or current; it does not matter which you

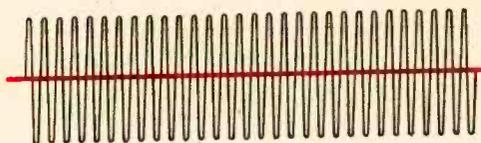


Fig. 1—A 27-mc RF carrier waveform.

consider). It is a sine-wave voltage as generated by a transmitter. In the case of CB, 27 million cycles are generated each second in the RF carrier. Our drawing shows some 30 cycles.

The audio or modulating voltage is represented by the sine wave shown in in



Fig. 2—Sine-wave modulation (audio) signal.

Fig. 2. The frequency here is 1,000 cps. Note that the audio voltage is shown with an axis of its own and has positive and negative peaks (or peaks and valleys) like any normal electrical waveform.

When the RF voltage is modulated by

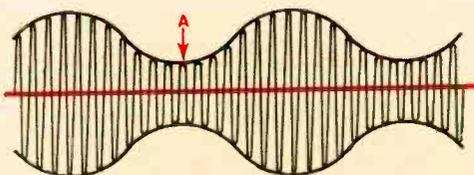


Fig. 3—Modulated carrier.

the audio voltage (when they are mixed together) the result is a modulated car-

rier, as shown in Fig. 3. You'll notice that the amplitude of the normal, unmodulated carrier shown in Fig. 1 has undergone changes in Fig. 3. What happened? The answer lies in the changing polarity of the modulating voltage. When this voltage is above its own axis, or positive, the amplitude of the carrier is boosted above its unmodulated level. When the modulating voltage is below its axis, or negative, it decreases the amplitude of the carrier voltage. The resulting waveform at the top of the carrier diagram is exactly in phase with the modulating voltage and exhibits the same amplitude (all waveforms here are shown in the same relationship). Below the axis of the carrier is an inverted, or mirror-image, modulating-voltage waveform. This image is eliminated at the receiver. The remaining one supplies the information for demodulation of the signal. In the case shown in Fig. 3, the audio voltage's negative swings decreased the carrier about halfway to the carrier's axis (see point A). This represents 50 per cent modulation.

If the amplitude or strength of the

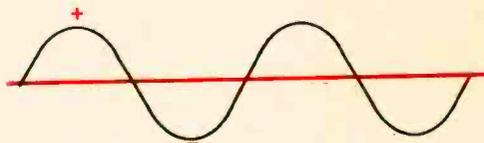


Fig. 4—Audio producing 100% modulation.

modulating voltage is increased, as in Fig. 4, so that at the instant it stands at its maximum negative swing (negative peak) the carrier voltage is col-

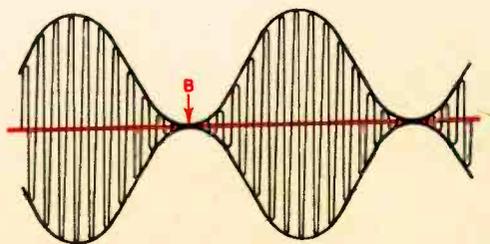


Fig. 5—Carrier showing 100% modulation.

lapsed to zero (its own base line), the carrier is said to be 100 per cent negative

or downward modulated, as shown in Fig. 5 at point B. To achieve 100 per cent positive modulation, the modulating voltage must double the voltage of the unmodulated carrier. A distortion-free transmitter always has a symmetrical waveform, showing the same percentage of both positive and negative modulation.

Modulation of 100 per cent is not only the limit permitted on the Citizens Band, it also gives you the most powerful signal (as represented by the amplitude of the modulating voltage) that you can use efficiently. Modulation of more than 100 per cent produces distortion, besides arousing the ire of the FCC.

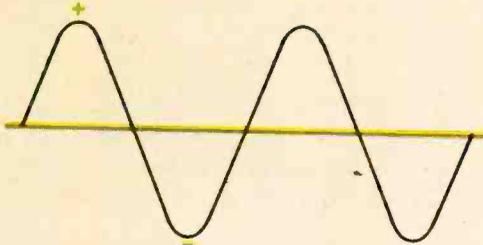


Fig. 6—Excessive modulating voltage.

In Fig. 6 we show a modulating voltage in excess of that required for 100 per cent modulation. Let's see what happens when we apply it to the RF carrier we've been working with.

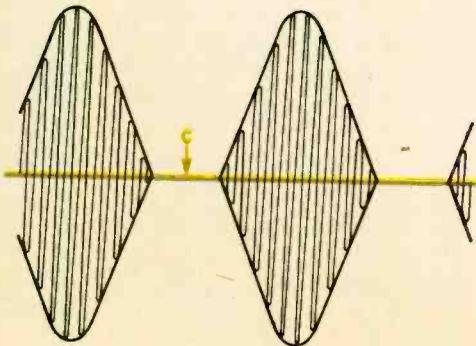


Fig. 7—Carrier modulated over 100%.

The result of this marriage of overly-strong modulating voltage and carrier is shown in Fig. 7. Notice that the carrier is driven to zero (its axis; point C) even before the modulating voltage reaches

its negative peak, which would fall below the carrier's axis. The RF output

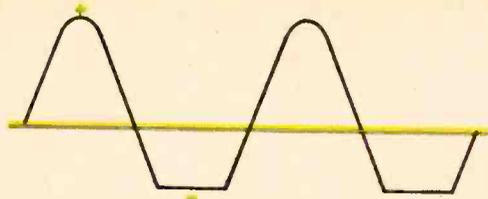


Fig. 8—Distorted signal at receiver.

is cut off completely.

Since the modulation, when recovered at the receiver, will look like the waveform in Fig. 8, the audio will be distorted. A close examination shows that it is the *negative* part of the modulating signal that is distorted. The positive peak does not distort. In practice, you can run 200 or 300 per cent positive modulation and 100 per cent negative modulation and still have no distortion problem. But let your negative modulation go over 100 per cent and all kinds of unpleasant things happen.

A surprising facet of this picture is that distortion of the modulating signal is *in itself* no major headache. Speech clippers cut off the modulating waveform—thus distorting it—but still manage to *improve* communications. Eliminating the higher and/or lower voice frequencies reduces the naturalness of your voice but at the same time increases intelligibility by beefing up the intelligence-carrying midrange frequencies (500-5,000 cps).

The trouble caused by excessive negative modulation has to do with the relationship of the modulating signal to

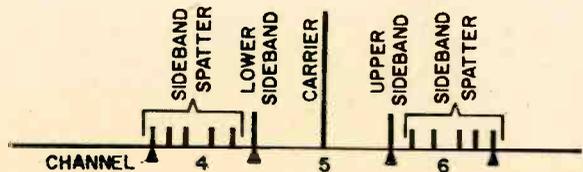


Fig. 9—Sideband spatter in adjacent channels.

the carrier, with distortion of the carrier, and with production of sidebands

ALL ABOUT MODULATION

(see Fig. 9 on opposite page).

When the waveform of the audio voltage becomes distorted it begins to produce harmonics of itself (a 5-kc modulating signal would produce harmonics of 10, 15, 20 kc, etc.). These harmonics then beat with the carrier, with each other and with the new difference frequencies to produce a flock of new sidebands (you will remember that the beating of the modulating signal and carrier produce two basic sidebands). The new sidebands are just like the old ones, although they are less powerful and they're also outside the CB channel you are using. In bad cases they may spread over several adjacent channels, interfering with other stations (which is illegal). The term given to this situation is *sideband spatter*.

Modulation percentages always are given in reference to the *peak* modulating voltage, but you also must consider another factor: *average* modulation. The higher your average modulation runs, the stronger your signal at the receiver. It can be shown mathematically that the *average power* of a complex waveform (such as speech) necessary for 100 per cent modulation is one-fourth the RF input power to the final. In other words, it takes between 1.2 and 1.3 watts, averaged out over many cycles, to achieve 100 per cent modulation when your transmitter is loaded to 5 watts input. An increase above this power results in overmodulation.

On the other hand, a sine waveform must pack one-half the input power to achieve 100 per cent modulation. To insure that the modulator is capable of delivering the peak power necessary for 100 per cent modulation, and to permit the use of sine waves for tests, the modulator in most CB rigs is designed to deliver one-half the RF carrier power.

There's another way to increase your

talk-power—the apparent power of your signal at the receiver. Consider this: if you use a speech clipper to cut off the peaks of the modulation waveform halfway to maximum (6db below the peaks) the new peak audio signal would result in only 50 per cent modulation. So now you can add 6db of modulation power (doubling the voltage) to bring the new peak up to 100 per cent modulation. Since the average level of the signal has been increased 6db, its actual power also has increased that much.

Clipping does distort the modulating waveform but you can clip up to 25 db before intelligibility is lost. In practice about 12db clipping normally is used. Clippers do not produce sideband spatter because it is the modulating waveform, not the carrier, which is distorted.

As a last consideration, the frequency response of your entire audio system can be tailored to make the most of the modulating signal. As shown in Fig. 10, the frequency response of the average voice is about 90 to 10,000 cps, with voice power decreasing as the frequency rises. Most of the voice's intelligence is carried in the range from 500 to 5,000 cps. Your audio system can be arranged—beginning with a selective-frequency microphone—to attenuate the high and low frequencies. This, in effect, boosts the power of the intelligence-carrying midrange to 100 per cent modulation, giving you an increase in talk power of at least 6db.


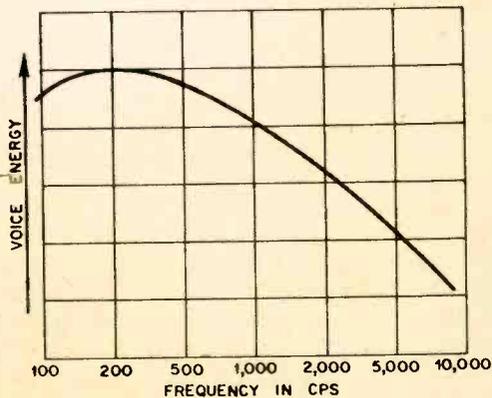


Fig. 10—Voice's power at all its frequencies.

GOOD READING

IT'S EASY TO USE ELECTRONIC TEST EQUIPMENT. By Larry Klein and Ken Gilmore. John F. Rider, New York. 186 pages. \$4

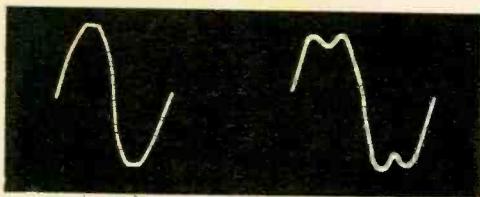Larry Klein, EI's Technical Editor, and Ken Gilmore, a frequent contributor, have collaborated to produce a fine survey of modern test equipment and its uses. The longish title notwithstanding, it is not a book meant for the absolute beginner. It's aimed at hams,



hobbyists and technicians, and its usefulness won't soon be outdated.

The book obviously is meant to be used, and the equipment selected to illustrate each section is just what's likely to be found on your test bench. No words are wasted on superfluous topics and obsolete equipment. The style is informal, readable and to the point without being either overly simple or too professional. If you want to make the most of your own test equipment, this is a book to keep handy.

As a kind of bonus, the authors throw in some welcome words on the testing of hi-fi equipment, a subject that has been given far too scant attention elsewhere. (Our illustration, from the book, shows a sine-wave oscilloscope trace with some clipping at left, more clipping at right.)

THE LP/STEREO RECORD GUIDE AND TAPE REVIEW. By Warren DeMotte. Argyle Publishing Corp., 198 Fifth Ave., New York. 320 pages. 95 cents

If you feel lost in a wilderness at a record store, you have reason. You can find a dozen or more versions of almost

every major piece of music on mono or stereo discs and tapes. That's why a book like the one at hand is long overdue. It helps you make intelligent choices.

The tome is a survey, via convenient capsule reviews, of virtually every available version of major and minor pieces. Mr. DeMotte, who is EI's record reviewer, minces no words when he tells you which version of Beethoven's Fifth or Schubert's Unfinished that he prefers, and he goes on to give enough information about other recordings to help you make a choice of your own. He pays attention to both musical and sonic qualities.

The book's unexpected *lagniappe* is some short but valuable sections on folk music and audio equipment. To my way of thinking, however, the most impressive fact is that Mr. DeMotte has listened to every recording he talks about (EI can vouch for that). There is no cribbing or second-hand evaluation.

SINGLE SIDEBAND FOR THE RADIO AMATEUR. American Radio Relay League, West Hartford, Conn. 223 pages. \$2


Some eight years ago the ARRL published its first volume on single-sideband radio and, since interest is still a-building, we now have a revised edition. It's up-to-date and fact-packed.

CB RADIO ANTENNA GUIDE-BOOK. By David E. Hicks. Howard W. Sams & The Bobbs-Merrill Co., New York & Indianapolis. 136 pages. \$2.50

This is an excellent book on the subject of CB antennas, full of pertinent suggestions for making the most of your rig legally.

And make note of . . .

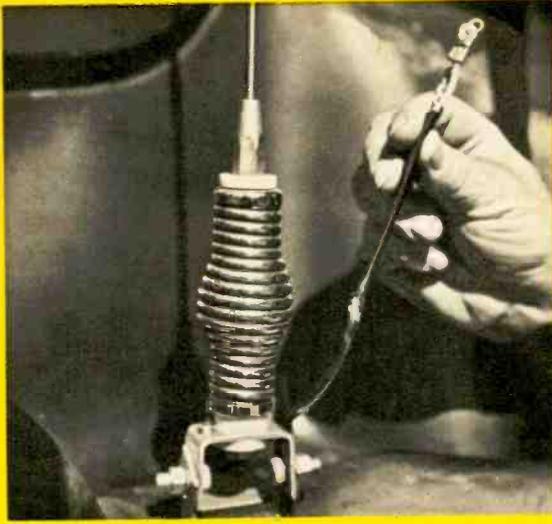HOW TO READ SCHEMATIC DIAGRAMS. By Donald E. Herrington. Sams. 128 pages. \$1.50



PERK UP YOUR MOBILE

Careful inspection and repair can give you like-new performance.

By Bert Mann

TAKE a high-quality Citizens Band transceiver, install it in a car or truck, use it continuously and subject it to vibration and bumps—and what happens? After six months you can't even remember its like-new operation.

To get some of the old zip back you need a perk-up job. A CB rig is just like a car in that respect. For maximum performance a twice-yearly tune-up is called for.

A mobile revamp is considerably different from that given a base station. Dusting, tube-checking and so on may be enough for a home rig but thorough cleaning is required for mobiles.


Start with the tip of your whip and go all the way through your system. That little ball on top of the antenna is more than a decoration. It discharges static electricity built up by air friction, distributing it over a large area. Without it, the discharge is from a sharp point and causes high-intensity noise shots. If the ball is gone get a steel marble, such as those used in toys, and drill a snug-fit hole in it. Then force-fit it on the antenna. A plastic ball also can be used.

Continuously loaded whips usually

have a plastic sheath over their coils. If the sheath cracks the coils can be exposed to damage. If there are breaks or cracks in your sheath wrap it with a single layer of plastic tape and saturate it with poly or coil dope for waterproofing. If insulation is chipped off the coil itself saturate it with Glyptal. When that dries, wrap the exposed coil with tape and then waterproof the job.

The spring at the base has an internal braid running from one end to the other, which prevents the spring from acting as a loading coil (the braid shorts out the would-be coil). To check, bend the coil and look inside to make sure the braid is connected to both ends. If the braid appears corroded jam a pencil or screwdriver into it. Replacement of the spring was past due if the braid breaks.

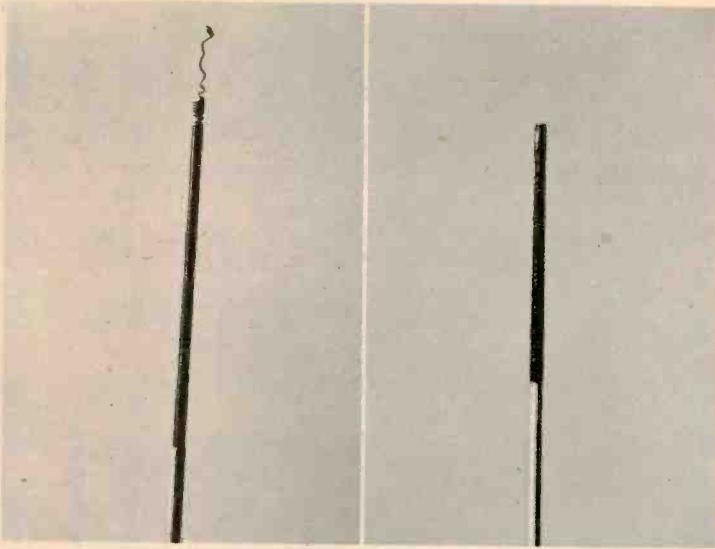In bumper mounts, check the coax at the base (our lead photo shows a cable damaged by bumper vibration). Look carefully for corrosion on the braid (the ground connection). When you find corrosion remove it with a wire brush, trim the end of the coax and form a new ground with the braid. If the coax must run in a tight bend around the bumper,



If a loaded mobile whip's plastic sheath cracks, it can result in damage to the loading coil, as in the picture at far left. To repair, restore coil and wrap exposed section tightly with plastic tape (see photo right, after repair).

cement some rubber grommets to the cable to prevent direct contact.

Body mounts require especially close checking. It is not unusual for the hard Bakelite insulators used on low-cost mounts to develop fine cracks between the ball (the RF hot lead) and the grounded mounting screws. Dirt and grime, accumulated in the cracks, tend to bleed off some of the RF energy. As a temporary measure you can clean the



cracks with carbon tet and cover them with plastic tape. But the only final solution is replacement.


The last check on the antenna is the cable. If it runs under the car, look for rock damage; if under the back seat or floor mats, be on the lookout for a squashed spot. Cable is cheap. Spend a dollar for a new one if you need it.

On front cowl mounts, the mounting nut should be tightened because the

A defective or corroded shorting braid in the whip's spring will break when jabbed with tool.

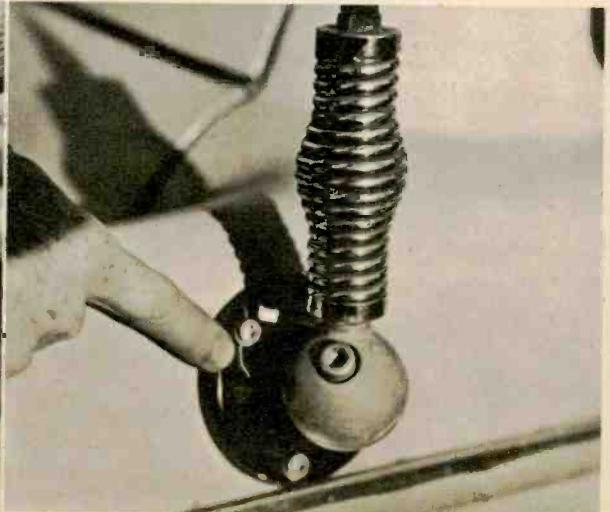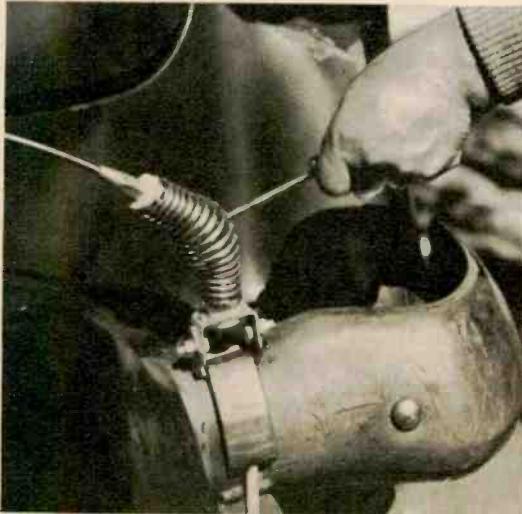Body mounts should be checked for cracks around mounting screws; grime in cracks shorts out RF.



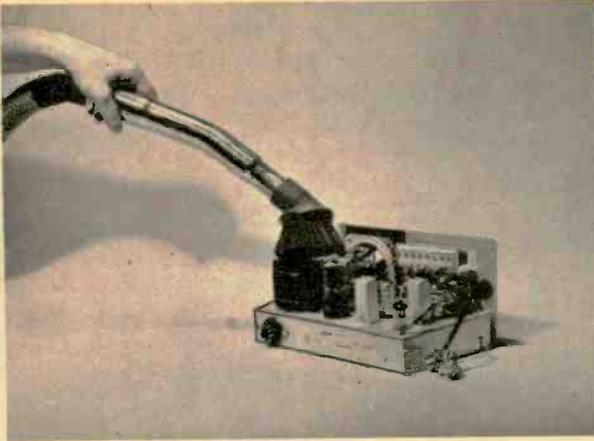

Thorough vacuum-cleaning removes dust and dirt from mobile transceiver. Cleaning can prevent intermittent operation. Do not blow out dust.



Transmit and receive switches require periodic cleaning for trouble-free operation. A liquid cleaner is being used here; never file contacts.

coax ground connection is determined by the tension of the nut.

Turning to the transceiver, take off the cabinet and vacuum the inside thoroughly. If you find dust in the tuning capacitor, dip a piece of washed linen in solvent and pass it through the plates. Rotary switch contacts are cleaned with contact cleaner, while relay contacts can be put in shape with a business card saturated in the same

cleaner (put the card between the contacts and pull it through).

Naturally, you will want to replace any defective tubes. Then check the rig's performance against your base station transceiver. If the set has really had it rough you may have to realign the receiver with a signal generator. After putting the transceiver back in the vehicle, use a standing wave ratio meter to peak the transmitter. 

While usually not required, realignment of a CB rig's receiver may sometimes be necessary after a long period of sustained operation. An RF signal generator is being used below to realign a set.



A SURVEY OF

CB KITS

Do build-it-yourself rigs save you money? Should beginners try them? What about FCC regulations?

By Len Buckwalter, KBA4480

BUILD-IT-YOURSELF kits have become firmly entrenched as part of the Citizens Band equipment market. As in other areas of consumer electronics, kits are a powerful lure to the CBer. They can save you up to 30 per cent, and at the same time you have the pleasure of building a piece of equipment and the later satisfaction of seeing it work. Along the way, you pick up a little knowledge, too, though the educational value of kits often is overestimated, as EI has said.

A wide range of CB equipment comes in kit form today—everything from a stripped-down, under-\$10 handi-talkie to fancy, gingerbread-loaded transceivers. Accessories, too, are starting to appear for the CBer who likes to snip, strip and solder. This survey covers all the major CB kits, though some semi-kits (build-part-of-it-yourself) are not included.

Without doubt, the leading question about CB kits concerns the oscillator section of the transmitter. Part 19, many of us once assumed, would require kit transceivers to come with a wired and sealed oscillator section (the frequency-determining elements). It hasn't worked out quite that way. Virtually all oscillators, apparently with the blessing of the FCC, arrive as bunches of components and are put together by the buyer.

Is CB equipment hard to build? What about alignment? Is it tricky without special instruments? And, in the final analysis, can a pile of coils, resistors and other electronic miscellany be converted by the beginner into a rig that works as well as its factory-built counterpart?

Unlike other electronic kits, those made for CB must not only satisfy the builder, but also some stiff laws laid down by the FCC. There's no relaxation in specs to allow for errors by the hobbyist. Thus, care in construction, especially in the transmitter section, is the rule for CB kits. Some manufacturers have adopted special techniques to help insure legal performance of their completed models.



EICO Model 772 transceiver has 4 transmit channels, a tunable receiver with 1 crystal channel. Squelch, noise limiter. \$89.95.



EICO Model 740 handi-talkie offers 100-mw transmit power, has 1 crystal receive channel. Nine transistors; kit. \$54.95.



Heath GW-12 transceiver is low-cost, 1-channel rig. Superhet receiver, squelch, push-to-talk. Kit for AC operation only is \$39.95.

A typical example is found in the EICO 772 transceiver. Aware that the frequency-determining part of the circuit is critical, EICO supplies a prefab crystal oscillator that is tested and sealed at the factory. During an appropriate point in assembling the kit, the builder bolts the oscillator unit to the main chassis and hooks on a couple of leads. No further adjustments are needed and off-frequency operation is avoided.

Other manufacturers have taken to the printed-circuit board to head off difficulty in the delicate oscillator section. Allied's Knight-Kit C-22 and Radio Shack's TRC-8, for example, overcome the lead-placement problem with copper foil conductors which cannot shift from the position planned by the design engineer. These techniques are by no means universal. If the manu-

facturer provides no pre-engineered assembly, the builder must follow the manual on proper lead placement.

In other phases of CB kit construction, the prospective builder will find the same techniques that have been applied with success over the years to test equipment and hi-fi gear: simple, step-by-step instructions and clear diagrams. There is no sign that the manufacturers have wavered from the golden rule of kit-making—no matter how complex the job, it should be practical for anyone to build. Nevertheless, a certain number of kitchen-table productions fizzle.

The major reason, everyone agrees, is the cold solder joint. It is *not* wiring error, as generally believed by kit builders. (This takes second-place honors.) Nowhere else is it so important to avoid the powdery, dull-gray and

Heath GW-11 has crystal control on 3 transmitting, 1 receiving channel, plus variable tuning. Kit for AC operation is \$69.95.

Heath GW-32: 5 crystal T-R channels, squelch and noise limiter. With selective call. \$64.95; without call, \$59.95.

Heath GW-31 is low-cost 90-mw handi-talkie; 1 crystal control transmit channel and superregen receiver; 4 transistors; \$24.95.





Heath GW-21 is a 9-transistor handi-talkie. It has 1-channel superhet receiver. Transmitter is rated at 100 mw. Kit, \$44.95.



Allied's Knight-Kit C-11 rig features tunable superregen receiver; 1-channel, 5-watt transmitter. Kit price is \$39.95.



Knight-Kit C-22 has 5 crystal T-R channels, squelch, noise limiter. Kit is for 117-VAC or 12-volt DC operation; the list price is \$69.95.

crumbling solder joint as in CB construction. A hi-fi amplifier may work well for years before a poor joint acts up, but a CB rig doesn't always operate under such placid conditions. The rigors of mobile operation soon expose a bad soldering job. This is pointed up lucidly by the experience of one serviceman who specializes in kit repair. He regularly rescues equipment through the simple act of resoldering every joint.

The best way for the beginner to avoid the problem is to stop thinking of a soldering iron as a device to melt solder. Rarely will a cold joint develop if the iron is used only to heat the wire and terminal lug which, in turn, get hot enough to make the solder flow.

With the appearance of the accessory in kit form, the CBER can significantly improve the performance and operating convenience of his station. Two of the

most popular units packaged for home construction are selective call and the audio compressor. The first device is typified by Heath's Tone Squelch (GD-162A). It keeps the transceiver silent unless an incoming call carries proper tone. Other traffic on the channel is muted. To make the kit useful for all makes of CB units, Heath provides step-by-step instructions for wiring it to their own and four other leading transceivers. There's a more general installation procedure for the remaining rigs.

The SpeakEasy by Instruments & Communications, Inc., and the Stoner Audio Ram are audio compressors in kit form for boosting modulation percentage. In most rigs, 100 per cent modulation is achieved only for occasional voice peaks, while average levels tend to remain in the 20 to 30 per cent region. Compressors hook into the mike

Knight-Kit's C-100 3-transistor handi-talkie features superregen receiver and 100-mw transmitter, uses a 9-volt battery. Price: \$9.95.

Knight-Kit KG-4000 has 1-watt transmitting power, 1 crystal channel; basic price, \$59.95; battery charger \$19.95 extra.

Radio Shack's Realistic TRC-8: 8 crystal T-R channels, dual conversion, squelch and noise limiter, S-meter; costs \$109.95.






Stoner Audio-Ram SE-101K is a clipper/compressor accessory for boosting your percentage of modulation. List price of kit is \$14.95.



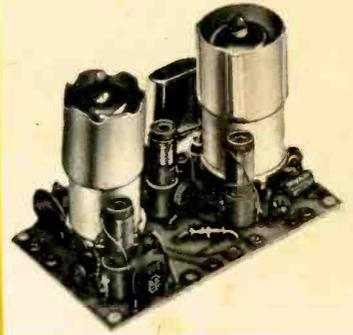SpeakEasy by Instruments and Communications, Inc., is an audio compressor. Meter shows modulation percentage; \$24.95.



International Crystal's FRA-1 converter brings CB calls in on regular broadcast radio. Parts and printed circuit board cost \$14.

lead and raise average talk power as close to the 100 per cent figure as possible without overmodulating. As in other CB kits, complete assembly and installation instructions are included.

The CBER with technical knowhow has not been overlooked by kit makers. International Crystal makes available a series of printed-circuit boards which may be used in equipment of the CBER's own design. Major items of interest are tube and transistor transmitter sections and an RF converter which brings the 27-mc band in on a standard broadcast receiver. Instructions packed with these units have schematics and circuit descriptions but do assume that the user has knowledge of the associated circuits.


The typical CB kit, as opposed to the circuit boards mentioned above, is engineered to eliminate the need for complex test equipment for final alignment and adjustments. However, it is recom-


mended that the builder have access to at least a sensitive (20,000 ohms/volt) VOM. Virtually all manuals give the alignment procedure with and without instruments but stress that best performance results with a meter. Without the milliammeter, for example, it's impossible to determine the power input to the transmitter precisely. The voltmeter allows needle-sharp adjustments to the various coils and transformers in the receive section.

If you're wondering whether the finished product can work as well as a factory-wired model, the answer is yes, when the kit is purchased from a reputable manufacturer. In fact, many rigs and accessories are offered in wired and kit form and contain identical circuits and components. With careful attention to the assembly manual—and by avoiding the cold solder joint—success is easy. ●

International's transistorized transmitter unit has 25-mw output; board and parts \$24.50 (wired).

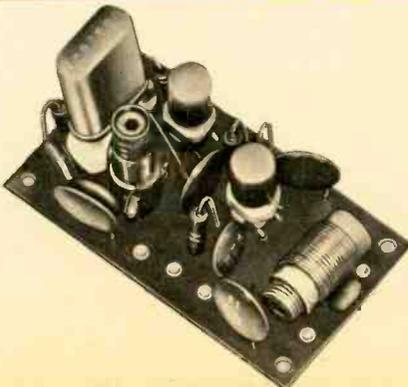Basic 5-watt transmitter is on circuit board. No final tank. crystal. Intl. Crystal. \$9.95 (wired).



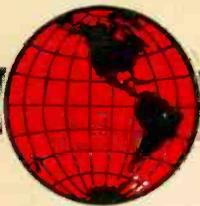

THE LISTENER

SWL-DX NOTES

BY C. M. STANBURY II

LAST CHANCE . . . After May 1 DXers will have one less country to shoot for. Netherlands New Guinea (Irian) on that day becomes part of Indonesia. The territory a few months ago was close to being a battleground between Dutch and Indonesians. The major Irian (*West Irian* is a more popular term) station is RONG, Radio Omroep Nieuw Guinea, on the offshore

pel Hour was taken off the air, and the Mexican station also is having QRM problems with CKLM, Montreal, which operates continuously . . . DXers looking for the Netherlands Antilles should watch 907 kc for PJA6, Radio Victoria, Oranjestad, Aruba. It's a religious station with some commercials.




Long John . . . Every night from 2400 to 0500 EST (0530 on week ends) Long John Nebel holds forth on New York's WOR. The Long John Show is heard regularly in 27 states for, at 710 kc, WOR has QRM trouble only with KMPC, Los Angeles.

Besides being a good DX catch (see QSL card), Long John's show represents some truly unusual listening. He has the most unique guests in radio. For instance, not long ago Long John's listeners were treated to an interview with one Albert Bender, who has some unusual attributes. According to him, when he tuned his radio to a certain spot


island of Biak. It is best heard on 6070 kc between 0530 and 0830 EST. RONG always has been friendly to DXers. Whether it will remain so under Indonesian control, and which way it goes politically, we'll soon find out.

Meanwhile, you might get some clues by listening to Radio Republik Indonesia at Djakarta. RRI's Voice of Indonesia broadcasts in English at 0600-0700 and 0930-1030 EST on 9710 and 9585 kc; also from 1400 to 1500 on 9585, 11795 and 11710 kc. The station in the past has been erratic in the QSL department, preferring to send out decorative program guides (see cut).

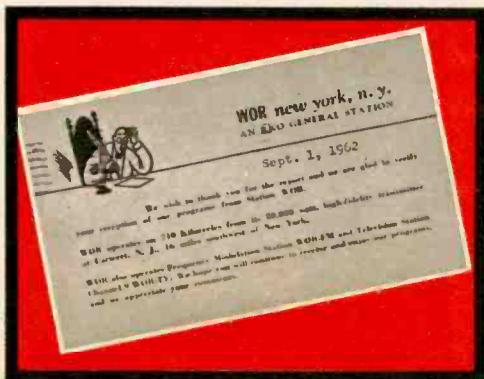Notes . . . R. Australia, favorite target of DXers, has switched its North American transmission to the evening: 2000-2300 EST on 15370 and 17840 kc, its Sunday DX program to 2115 EST . . . Radio preacher V. E. Howard (see March '62 LISTENER) is suing XERF over a refund he says was due him after his Gos-



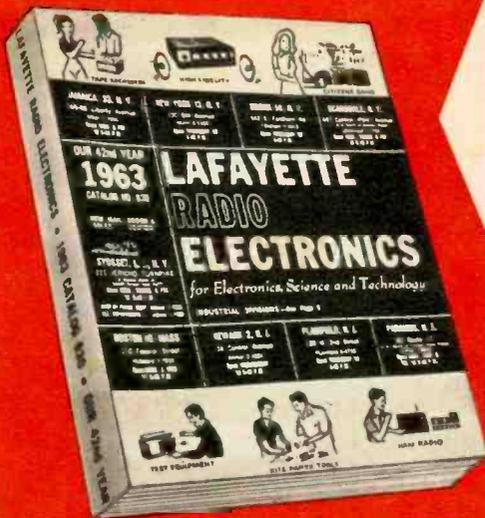on the dial (he couldn't remember just where) he was contacted by beings from the planet Kavik and then transported to Antarctica, where the Kavikites have a flying saucer base. An unusual interview, indeed. But no more odd than many others presented by Long John. You just can't get 'em like that anyplace else.



FREE FOR '63

1963
CATALOG NO. 630

LAFAYETTE RADIO ELECTRONICS

388
GIANT-SIZED Pages
The Largest Catalog
in Our 42-Year History

It's New — It's Big — It's Better Than Ever
It's From the "World's Hi-Fi & Electronics Shopping Center"

The exciting, all-new 1963 Lafayette Catalog features thousands of items for the audiophile, experimenter, technician, hobbyist, serviceman

... Citizens Band, Tape Recorders, Stereo Hi-Fi, Ham and Amateur Equipment, and much more.
No Money Down on Lafayette's Budget Plan

ONLY LAFAYETTE OFFERS THESE OUTSTANDING EXTRAS:

✓ SATISFACTION GUARANTEED OR MONEY REFUNDED ✓ LOWEST PRICES ✓ EXCLUSIVE LAFAYETTE KITS ✓ LARGEST STOCK SELECTION ✓ BUY THE EASY-WAY WITH EASY-PAY ...

LAFAYETTE FM/AM STEREO MPX TUNER

LT-78



89.50

- Tuned RF Stage; Duplex 3 Gang Tuning Condenser
- Automatic Frequency Control and Noise Filter

LAFAYETTE HE-20C C.B. TRANSCEIVER



HE-20C

109.50

- Officially Approved For Use in Canada
- 8 Crystal Controlled Receive and Transmit Positions

LAFAYETTE 10-TRANSISTOR C.B. "WALKIE-TALKIE"



33.95

each,
2-for-62.90

HE-29B

- 50% More Powerful—Extra RF Stage
- Receives and Transmits up to 2 Miles

LAFAYETTE "SQUELCHER"



HE-55

10.95

- Noise Eliminator and Squelcher
- Improves Reception in Most C.B. Transceivers

LAFAYETTE 4-TRACK STEREO TAPE DECK



RK-140

99.50

less case

- Built-in Transistorized Stereo Record/Play Preamps
- Records Sound-on-Sound

MAIL ORDER AND SALES CENTER
111 Jericho Turnpike, Syosset, L. I., N. Y.



OTHER LOCATIONS

Jamaica, N. Y.
New York, N. Y.
Bronx, N. Y.
Scarsdale, N. Y.

Newark, N. J.
Plainfield, N. J.
Paramus, N. J.
Boston, Mass.

OPENING FALL 1962 — NATICK, MASS.

LAFAYETTE RADIO ELECTRONICS, Dept. E1C3-2

P.O. Box 10, Syosset, L. I., N. Y.

\$ _____ enclosed for Stock No. _____, shipping charges collect.

Send me the Free 1963 388-Page Lafayette Catalog

Name _____
Address _____
City _____ Zone _____ State _____



PRIZE SHACKS

WIN \$20! In each issue EI publishes photographs of three Prize Shacks—Citizens Band, short-wave listening and amateur radio rooms or corners that have an attractive and efficient-looking layout. To the owner of each Prize Shack we pay \$20. We invite you to send us a picture of your CB, SWL or ham shack, along with a list of your equipment. We prefer 8x10-inch glossy prints. Pack your picture well to prevent damage in the mail. Unused photos are returned. The address: EI Prize Shacks, 67 W. 44th St., New York 36, N. Y.




SWL

Proprietor of our Prize SWL Shack is Paul B. Silver, Woodbridge, N. J., who's been a radio hobbyist 50 years. He has some 110 countries verified, got all continents in 1935. In his 4,000 QSL's are three from sputniks, 11 from U. S. satellites. He has three receivers and uses two antennas.

Billy K. Hart is the operator at CB station 6W6033. The whole rig is housed in a sliding-door closet in a 10x50-foot mobile home in Augusta, Ga. The panel-mounted transceiver, located below a tape recorder and power panel, is a modified RCA Mark VII, which now has an oversize dial, an S/power meter and a bank of 22 crystals. He really made his trailer space count!

CB

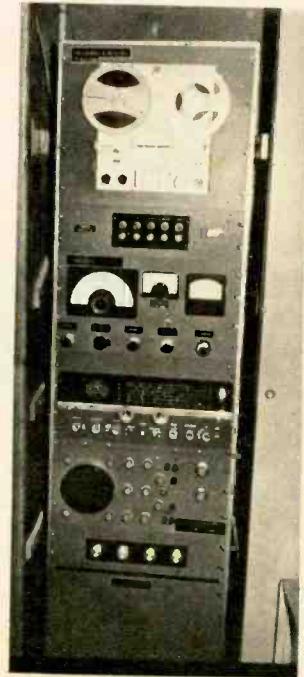

HAM

Most unusual thing about our ham shack is the location—Little America, Antarctica. The operator here is Julian Gudmundson, K4OEE (left). He is a Navy Seabee. The station, a kilowatt Collins SSB rig, is KCAUSA. With Mr. Gudmundson is a visiting U. S. congressman.



VOICE-POWER AMPLIFIER

Microphone preamp with adjustable frequency range tailors mike response to any voice.

By Russ Cogan

A SERIOUS deficiency of most CB rigs is that microphone amplification is established at a value which gives eighty-five to one hundred per cent modulation with an "average" voice. Unfortunately, voices are not average, some are loud, others are soft. Some people tend to swallow the mike—others act as though it had halitosis. All these factors help determine the per cent modulation. Frequently, in order to achieve 100% modulation with a comfortable voice level additional microphone amplification is needed.

EI's CB Preamplifier will provide the additional gain needed to fully modulate the transmitter. Since the preamp is transistorized, it is easily connected to either your base or mobile transceiver without tapping its internal wiring. The low current drain will give a battery life of many months. Level control R1 permits adjustment of the pre-amplification to the exact value required for your voice and mike habits.

As an added feature, the preamp is designed for low-frequency attenuation thereby providing a crisp communications quality. In addition, a variable high-frequency tone-shaping control is provided. By proper adjustment of control R5, audio quality can be varied

from sharply crisp to smoothly mellow.

The preamp is wired on a 2x3 $\frac{3}{4}$ -inch piece of perforated board. Before installing the components drill a hole in each corner of the board for the mounting screws; use a #28 drill for 6-32 screws. Input transformer T1 is held to the board with flea clips. Carefully bend T1's mounting tabs so they are at right angles to T1's frame. Place T1 on the board and insert a flea clip through the tab and board. A small drop of solder applied to the flea clips on the underside of the board will hold T1 firmly in place.

All the other board components are wired to flea clip terminals. The component leads are short so take care not to use excessive soldering heat. Use a heat sink (such as an alligator clip) when soldering transistor Q1.

The battery is held in place by brackets made from cable clamps or a strap can be cut from a tin can.


After the battery is in place mount the perforated board in the cabinet. To avoid short circuiting the flea clips which extend through the board, place a quarter-inch spacer or stack of washers between the cabinet and the board at each of the four mounting holes.

Input jack J1 is selected to mate with


Resistors: 1/2 watt, 10% unless otherwise indicated
 R1/S1—10,000 ohm pot with switch
 R2—100 ohms
 R3—100,000 ohms
 R4—10,000 ohms
 R5—50,000 ohms miniature pot
 Capacitors: All rated at 10 VDC or higher
 C1—.05 mf miniature
 C2—30 mf electrolytic
 C3—8 mf electrolytic
 C4—10 mf electrolytic
 C5—.02 mf miniature

PARTS LIST

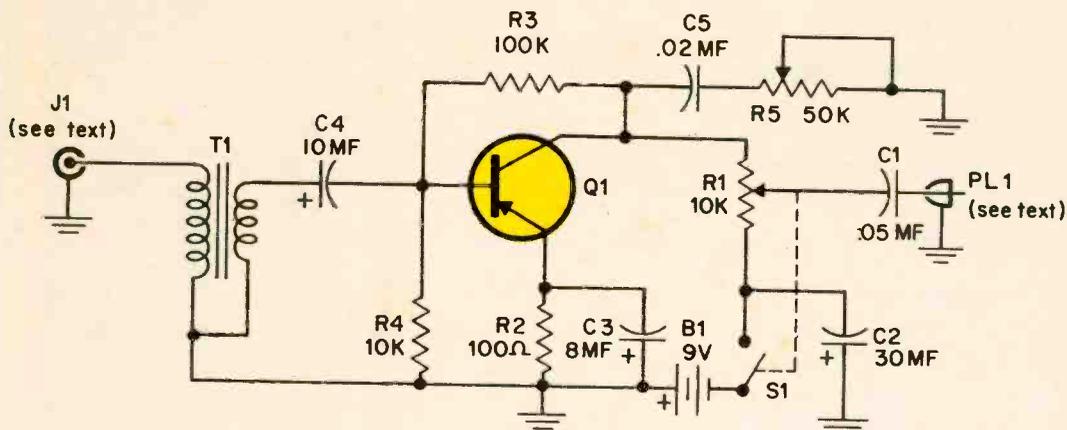C4—10 mf electrolytic
 C5—.02 mf miniature
 B1—9-volt transistor radio battery
 Q1—2N109, 2N217 transistor or equiv.
 T1—Transistor transformer: 200,000 ohms primary; 1,000 ohms secondary (Lafayette Radio TR-120 or equiv.)
 PL1, J1—see text
 Misc.—Perforated board (3 1/2" x 2"); flea clips; Mini-box (5 1/4" x 3" x 2 1/4"); etc.



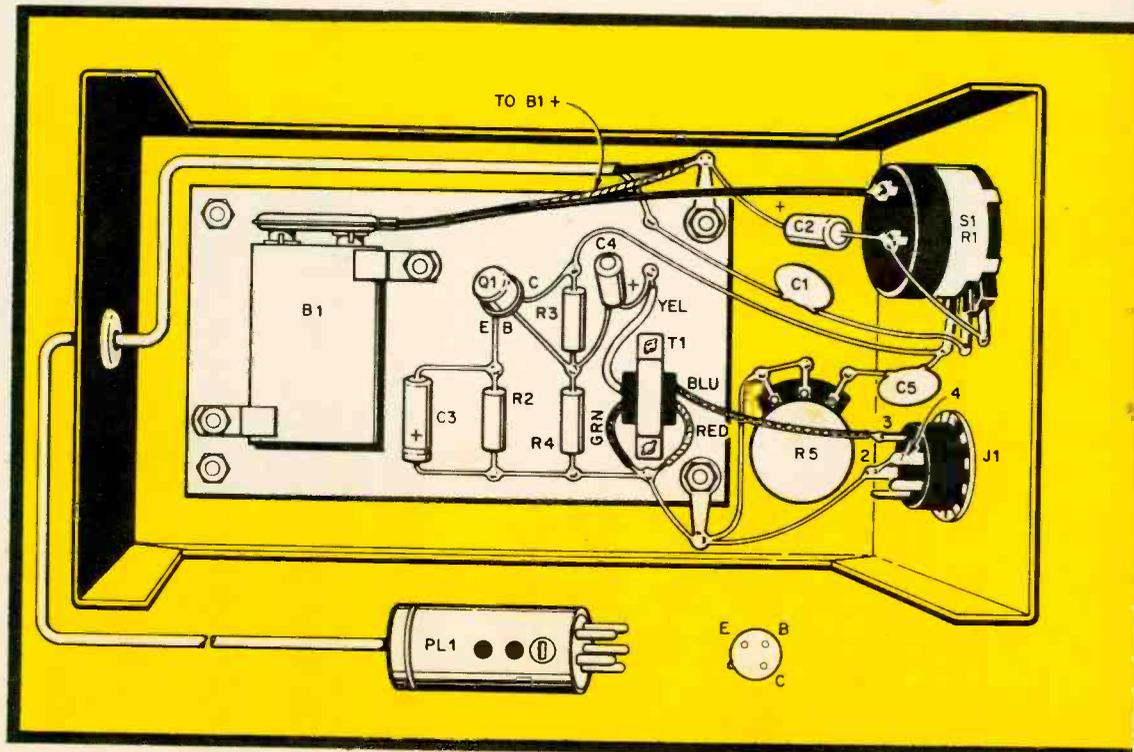
Circuit achieves its frequency characteristic with a fixed bass and a variable treble roll-off.



the plug on the microphone cable. Connect T1's blue lead to the J1 terminal which corresponds to the microphone's hot lead. If your mike has push-to-talk switching, run a pair of control wires from J1 through the output cable to PL1. To avoid hum pickup, the P-T-T leads should be outside the shield used for the microphone's hot lead. Do not use an output cable which has all the wires inside a single shield.


Using the Preamp. Plug the mike into J1 and output plug PL1 into the transceiver. Rotate control R5 full counter-clockwise (off). Then, speaking in a normal voice, adjust R1 until the transmitter is 100% modulated. Some form of modulation meter (EI's Monitor Meter, CitizenScope, or CB Modulation Meter) is necessary when adjusting R1 since the preamp provides more than enough gain to overmodulate the transmitter. After R1 is set, R5 can be adjusted to give the desired frequency response.

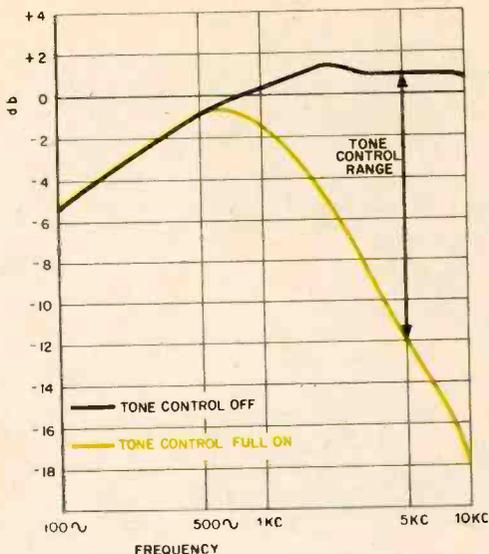
Note that the preamp, is designed for the kind of bass attenuation preferred in communication work. If you desire more bass, use .1 mf for C1.



The graph above illustrates the range of tone control available; the exact curve will depend upon the frequency response characteristics of your mike. The bass attenuation is built in.

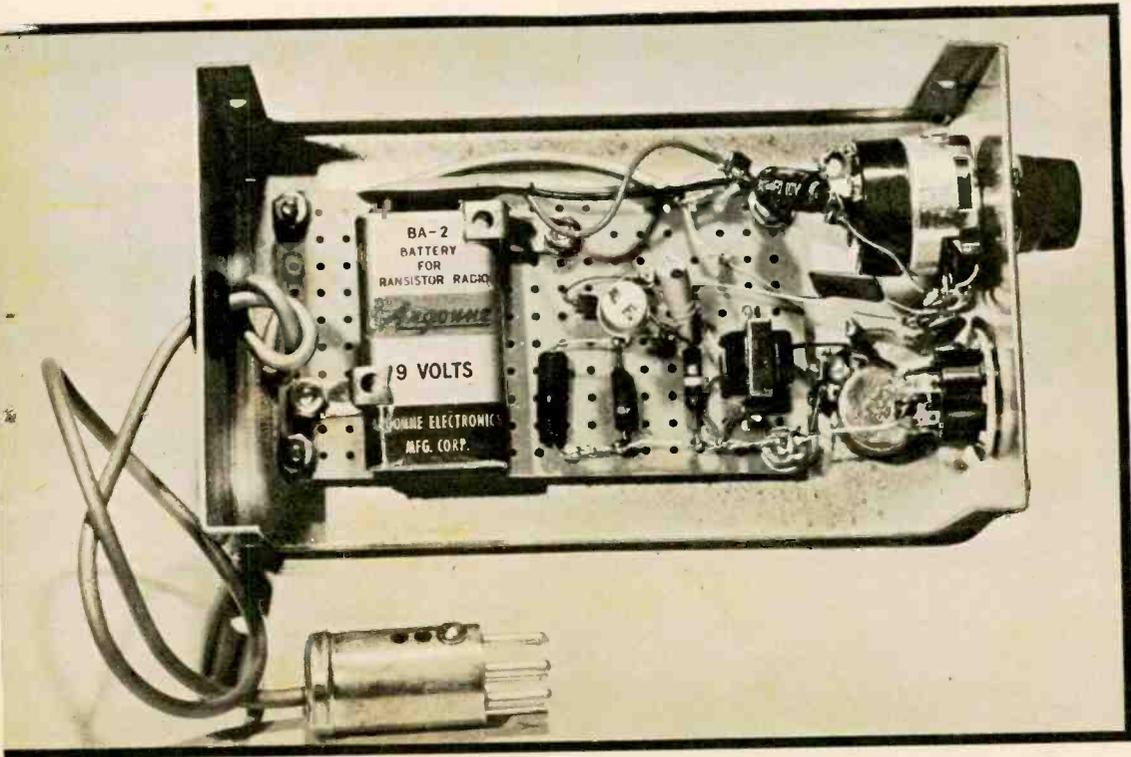Circuit is assembled on perforated board before installation on four 1/4" standoffs in the Minibox.



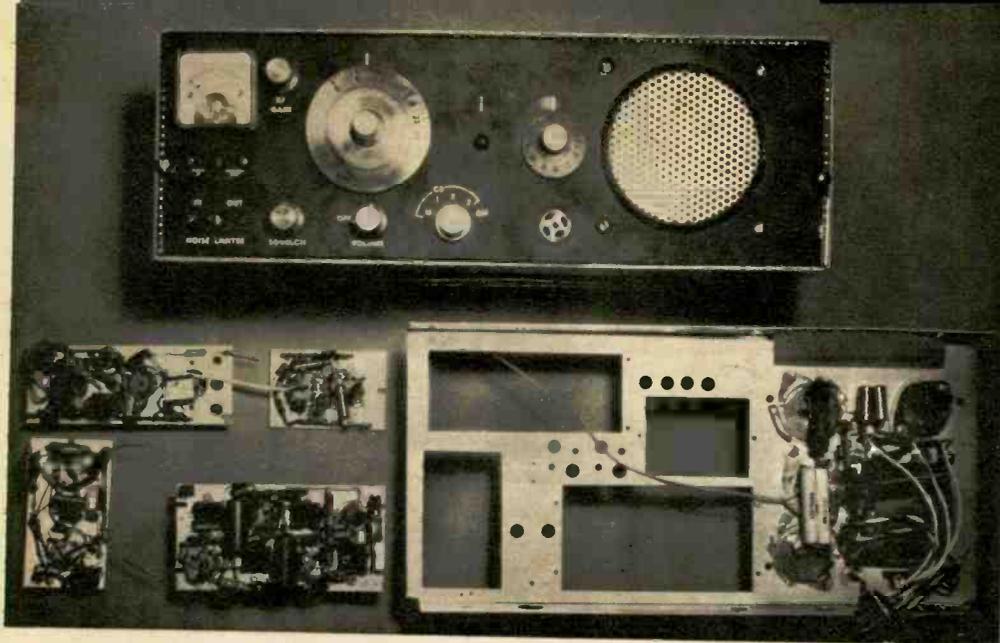


HOW THEY MAKE MODULAR CB RIGS

HOW DO YOU go about manufacturing a Citizens Band transceiver? The usual way is to send a chassis down an assembly line, where workers add one component after another. But ECI, Inc., at its factory in Mount Vernon, N. Y., does it in a different way. Watching production of ECI's Courier I is like seeing a block diagram come to life. Five separate modules are built simultaneously at various spots in the plant. After assembly, they are funneled to a central point and mounted on a main chassis, much as a jig-saw puzzle is put together. In the photo at the top of the page is a completed Courier. Just below it is a chassis with the power-supply module in place, and to the left of that are the four remaining modules: two receiver IF strips (upper left and lower right), the modulator (upper right) and the transmitter (lower left).—Charles O'Neil


1 Assembly-plant worker puts together typical module for ECI's Courier transceiver. He is soldering the leads in the modulator section of the set. Wire placement is by hand. Later, the module will go to an assembly area with chassis.

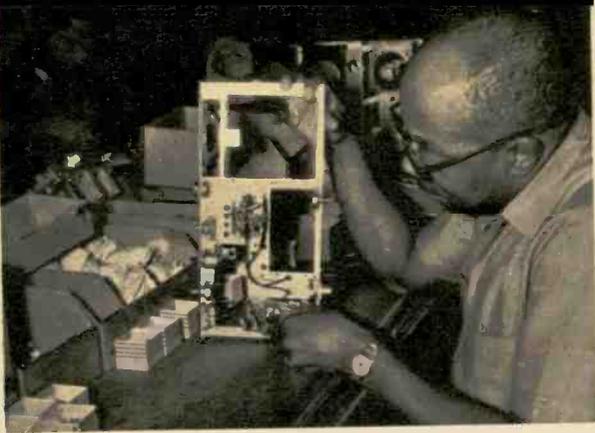2 After the module is assembled, an inspector checks every connection. If the joint makes the grade it is daubed with red marking fluid. Under-chassis eventually has a paint-spattered look. Receiver IF strips get treatment below.





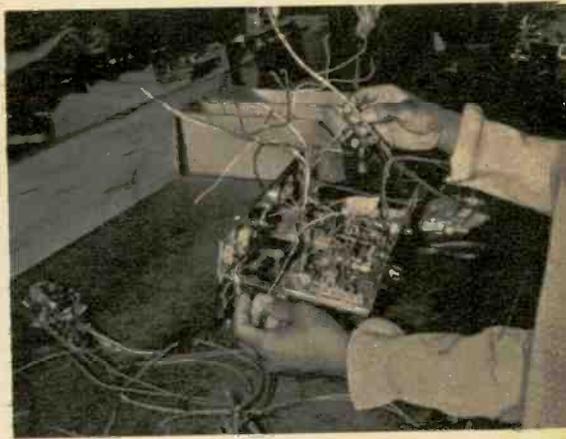3 The five modules that make up a transceiver are mounted on the chassis at this point on the assembly floor. Chassis has been die-cut to outlines of modules, which simply are set in the holes and bolted in place. Nuts and bolts make removal of sections easy at a later date.




4 After the transceiver's modular chassis is put together mechanically (see the preceding step), the various sections—five in all—must be hooked up electrically. The above picture shows a wiring specialist performing this task. This interconnection job is speeded along by a wiring harness which has leads pre-cut to exact length required. The harness is slid into the chassis and the leads are soldered to modules. Worker above is holding part of harness in his right hand.



5 In final stages (see this step and the next) of transceiver assembly, each rig is aligned and tested . . . then touched up and tested again if necessary. In the photograph at left, taken in the ECI laboratory, an inspector is putting a set through its paces after the first job of alignment. Among other things, he checks the actual power output of the transmitter, adjusts the TVI filter and measures the sensitivity of receiver; fixed receive channels are fine-tuned.

6 At this station each transceiver is aligned and realigned until final approval is given. All the tuned circuits on the wired chassis must track correctly, of course. The quality of the audio is checked and the receiver's S-meter is calibrated with care. In the picture below the technician is trimming a capacitor in the receiver.

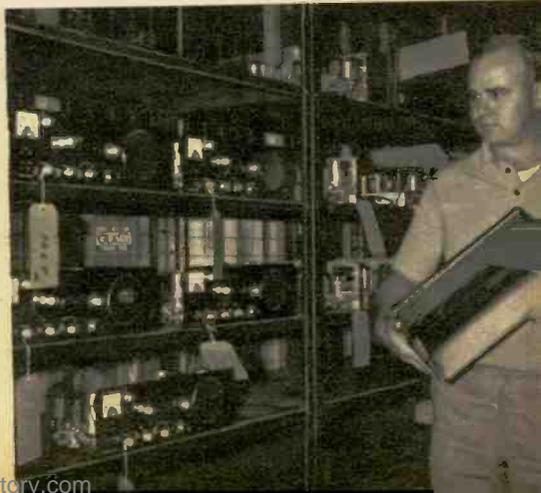7 Last step: completed chassis is slid into cabinet and the transceiver then goes into a shipping carton. An instruction manual is packed in each carton. Any accessories ordered by the buyer, such as extra crystals or power cords, also are put in the box. Cartons are placed on shelves, then go to shipping room; from there to customer.



HI-FI RECORD GUIDE

by Warren DeMotte

CAROUSEL may well be the finest musical written by Rodgers & Hammerstein, though it never achieved the popularity of their *Oklahoma!*, *South Pacific* or *The King and I*. Its characters and situations are more fully developed musically and the words and music are more subtly integrated.

A new recording, with Alfred Drake, Roberta Peters and Claramae Turner heading the cast and Jay Blackton conducting (see cut), is brilliantly performed and engineered. This type of production, done especially for recording, is decidedly worthwhile when done well, as here. It has the spirit of an original-cast performance, plus sound that could not be captured a few (very few) years ago.

Two popular young pianists add little to their reputations with new recordings of standard concertos. Van Cliburn, with Fritz Reiner and the Chicago Symphony, does the Rachmaninoff C Minor, and Philippe Entremont, with Leonard Bernstein and the New York Philharmonic, does the Tchaikovsky. Neither performance gets off the ground—through no fault of either orchestra.

The return of Vladimir Horowitz to recording activity has been brought about by Columbia and the first release is a winner, with magnificent performances of music by Chopin, Rachmaninoff, Schumann and Liszt. The old wizardry is still available in ample supply and the Horowitz tone has never been transcribed so faithfully.

In my recent book, *The LP/Stereo Record Guide & Tape Review*, I compared 16 performances of Chopin's Funeral March Sonata, mono and stereo,

and only Artur Rubinstein's (my choice) is in the same class as this new one by Horowitz. I'll still go along with the Rubinstein, but the margin is mighty slim.


Isaac Stern gains new laurels in Alban Berg's tortured Violin Concerto, which he plays with tremendous conviction and deep involvement. Bernstein and the New York Philharmonic are sensitively cooperative in this work and in the two Bartok Rhapsodies that fill out the disc.

Henryk Szeryng and Antal Dorati, leading the London Symphony, perform the more accessible Brahms Violin Concerto with fervor and rich lyricism. Their reading is accorded excellent engineering assistance.

Erich Leinsdorf is more successful with Wagner's *Die Walkure* than he has been with previous operatic ventures. He has a fine cast and orchestra and he leads a strong, well-knit performance that is dramatically convincing and musically compelling.

Records discussed in this column, with monaural discs listed first and stereo versions just below:

Carousel Drake-Peters	Command RS-843	\$4.98
	RS-843SD	5.98
Rachmaninoff: Piano Concerto in C Minor		
Cliburn-Reiner	Victor LM-2601	4.98
	LSC-2601	5.98
Tchaikovsky: Piano Concerto in B Flat Minor		
Entremont-Bernstein	Columbia ML-5759	4.98
	MS-6359	5.98
Vladimir Horowitz	Columbia KL-5771	5.98
	KS-6371	6.98
Berg: Violin Concerto Stern-Bernstein		
	Columbia ML-5773	4.98
	MS-6373	5.98
Brahms: Violin Concerto Szeryng-Dorati		
	Mercury MG-50308	4.98
	SR-90308	5.98
Wagner: Die Walkure		
Nilsson-Vickers-Leinsdorf	5-Victor LD-6706	29.90
	LSD-6706	34.90

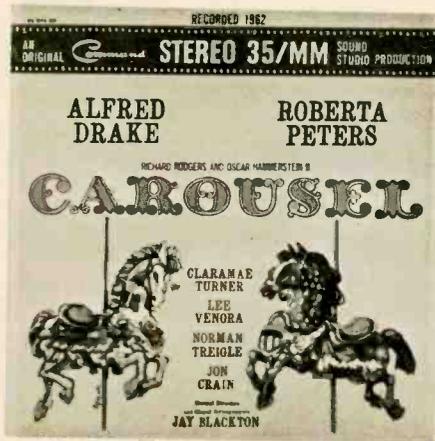

why settle for a routine job in electronics while others move ahead?

Read how CREI Grad Roy S. Reichert has advanced from maintenance work to the design of electronic equipment at one of the world's leading laboratories.



CREI GRAD ROY A. REICHERT makes an adjustment on the prototype of a programmable power supply which he designed and built in his capacity as Senior Technical Aide, Bell Telephone Labs, Murray Hill, N. J.

LET'S LOOK AT THE FACTS. Men with ordinary qualifications may always be accepted for routine, low-paying jobs. But for critical technical assignments in well-paying career positions with engineering status—where electronics is applied to the frontiers of the missile and space programs—only men with advanced technical knowledge will do.

MEN LIKE ROY S. REICHERT enjoy rewarding careers because they have equipped themselves with the practical, up-to-date knowledge of advanced electronic engineering technology which industry demands. Mr. Reichert had a routine job when he enrolled in a CREI Home Study Program. Today he helps design complex test equipment used in the development of Transistors at Bell Telephone Laboratories.

YOU HAVE THE SAME OPPORTUNITY. CREI offers you a complete home study program in electronic engineering technology. We equip you with practical knowledge of electronics required for well-paying positions and put you on the level of specialization where men are in demand and progress most rapid.

FOLLOW THE FOOTSTEPS of thousands of CREI men who hold positions as associate engineers, engineering aides, field engineers, project engineers and technical representatives.

YOU ARE GUIDED and assisted with personal attention from CREI's staff of experienced instructors. You study courses to which a number of leading engineers and scientists have made substantial contributions.

CHOOSE FROM PROGRAMS covering every important field of electronics:

- Servomechanisms • Radar • Instrumentation • Computers • Aeronautical and Navigational • Communications • Aero-Space • Television • Automation and Industrial Engineering Technology • Nuclear Engineering Technology

CREI EDUCATION IS RECOGNIZED by such large corporations as Pan American Airways, Federal Electric Corp., The Martin Co., Canadian Broadcasting Co. and Mackay Radio. They pay all or part of CREI tuition for their employees.

CREI HAS 36 YEARS OF EXPERIENCE in advanced technical education through home study. CREI has developed electronics courses for the Army Signal Corps, special radio technician courses for the Navy and group training programs for leading companies. CREI also maintains a Residence School in Washington, D.C. and invites inquiries from high school graduates.

YOU CAN QUALIFY for a CREI Correspondence Program, if you have basic knowledge of radio or electronics and are a high school graduate or the equivalent. Send for the FREE 1963 edition of our 58-page book describing CREI Programs and career opportunities in electronics. Use coupon below, or write to: The Capitol Radio Engineering Institute, Dept. 1703-A, 3224 Sixteenth St., N.W., Washington 10, D.C.

Mail coupon today for FREE 58-page book
—1963 Edition Now Available

CREI
THE CAPITOL RADIO ENGINEERING INSTITUTE Founded 1927
 Dept. 1703-A, 3224 Sixteenth ST., N.W., Washington 10, D. C.

Please send me details of CREI Home Study Programs and Free Book, "Your Future in Electronics and Nuclear Engineering Technology." My qualifications are noted to obtain immediate service.

CHECK FIELD OF GREATEST INTEREST:


<input type="checkbox"/> Electronic Engineering Technology	<input type="checkbox"/> Nuclear Engineering Technology
<input type="checkbox"/> Servo and Computer Engineering Technology	<input type="checkbox"/> Automation and Industrial Electronic Engineering Technology
<input type="checkbox"/> Aero and Navigational Engineering Technology	<input type="checkbox"/> Communications

Name _____ Age _____
 Address _____
 City _____ Zone _____ State _____
 Employed by _____
 Type of present work _____
 Education: Years High School _____ Other _____
 Electronics Experience _____
 Check: Home Study Residence School G.I. Bill

37

Shop by mail and save more money

Giant savings of up to 50% are yours when you buy Heathkits. First, you save by doing the assembly yourself (and have all the fun that's in the doing). Second, in buying direct from the factory, you save the usual distribution cost. These savings and Heathkits superb engineering enable you to buy far better equipment for far less. Start shopping your Heathkit catalog now—for all the electronic luxuries you've ever dreamed of owning.

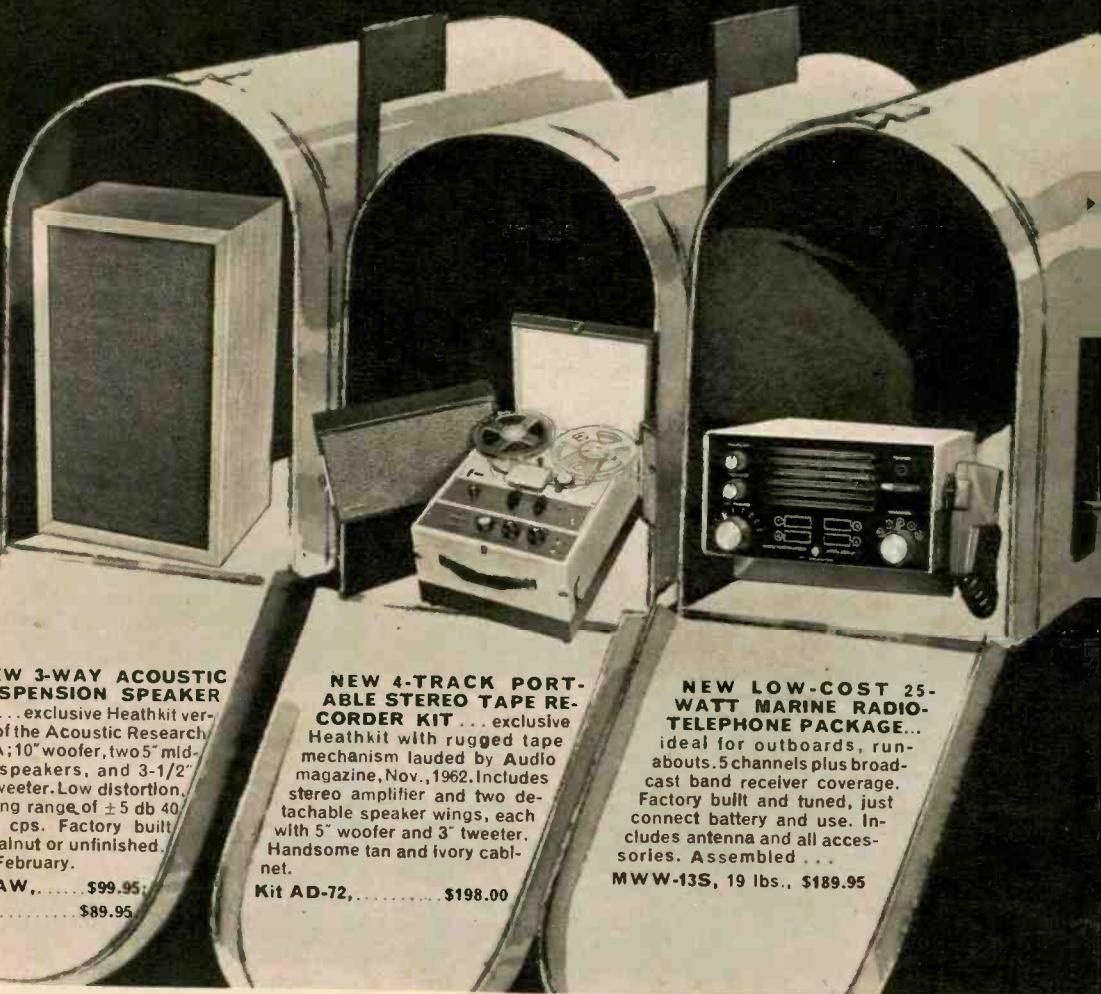

NEW 3-WAY ACOUSTIC SUSPENSION SPEAKER KIT

... exclusive Heathkit version of the Acoustic Research AR-2A; 10" woofer, two 5" mid-range speakers, and 3-1/2" super-tweeter. Low distortion, astounding range of ± 5 db 40 to 20,000 cps. Factory built cabinet, walnut or unfinished. Shipping February.

Kit AS-2AW, \$99.95
AS-2AU, \$89.95

NEW 4-TRACK PORTABLE STEREO TAPE RECORDER KIT

... exclusive Heathkit with rugged tape mechanism lauded by Audio magazine, Nov., 1962. Includes stereo amplifier and two detachable speaker wings, each with 5" woofer and 3" tweeter. Handsome tan and ivory cabinet.

Kit AD-72, \$198.00

NEW LOW-COST 25-WATT MARINE RADIO-TELEPHONE PACKAGE

... ideal for outboards, runabouts. 5 channels plus broadcast band receiver coverage. Factory built and tuned, just connect battery and use. Includes antenna and all accessories. Assembled . . .

MWW-13S, 19 lbs., \$189.95



who is Heathkit?

Heathkit is the pioneer and world's largest manufacturer devoted exclusively to the design and manufacture of do-it-yourself electronic kits. All our efforts are aimed at creating more kits, better kits, easier-to-build kits.



what are Heathkits?


Heathkits are electronic equipment in un-assembled form. All parts are packaged in convenient groups and a complete, easy-to-read, well-illustrated instruction manual tells you how to put them together. Heath offers over 250 kits from simple portable radios to big analog computers.



who builds Heathkits?

Millions build Heathkits. People with absolutely no mechanical ability or knowledge of electronics as well as skilled electronic experts—all find value, economy, fun, relaxation, and pride of accomplishment in Heathkits. You can too.

with Heathkits

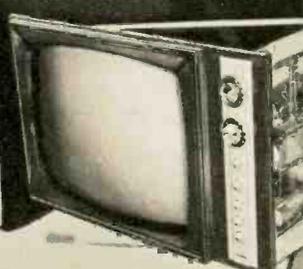

NEW 23" HIGH FIDELITY TV KIT... for finest sound and picture... for custom installations... for sensitive fringe area reception. Prebuilt subassemblies make it easy to complete in 2 evenings. Includes all tubes and parts. Optional UHF, wall mask and cabinet.

Kit GR-22, 70 lbs. . . . \$169.95
less wall mt. accessory.



NEW HEATHKIT VERSION OF THOMAS TRANSISTOR ELECTRONIC ORGAN . . .

Two 37-note keyboards, 10 true organ voices, 13-note bass pedals, variable vibrato, variable bass pedal volume, keyboard balance control, 20-watt peak power amp. and speaker, deluxe walnut cabinet.

Kit GD-232, \$349.95
less bench accessory.

Money Back Guarantee

Heath Company unconditionally guarantees that each Heathkit® product assembled in accordance with our easy-to-understand instruction manual must meet our published specifications for performance or your purchase price will be cheerfully refunded.

The famous Heathkit guarantee

This money back guarantee stands behind every Heathkit. It guarantees that you are getting equipment of the highest quality that will provide years of use and pleasure. Equipment second to none, Heathkit—world pioneer in the exciting hobby of kit building.

HEATHKIT

A Subsidiary of Daystrom, Incorporated

HEATH COMPANY
Benton Harbor 39, Michigan

Please send my free 1963 Heathkit Catalog

NAME _____


ADDRESS _____

CITY _____ ZONE _____ STATE _____

FREE 1963 HEATHKIT CATALOG!



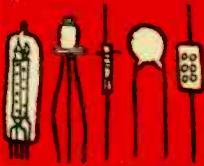largest kit catalog, 100 pages, over 250 easy to built kits. Send today.




BEGINNERS PAGE

HOW TO DROP A VOLTAGE

LET'S TAKE up a question which confuses many beginning experimenters: how do you reduce power-supply or battery voltages? This becomes a practical problem when you need to steal power from a receiver or a CB rig to operate a new accessory; or when you want to power several circuits with a basic supply.

To convert, simply move the decimal point three places to the left. In our example, assume the accessory draws 5 ma. I in the formula is then .005 (amperes).

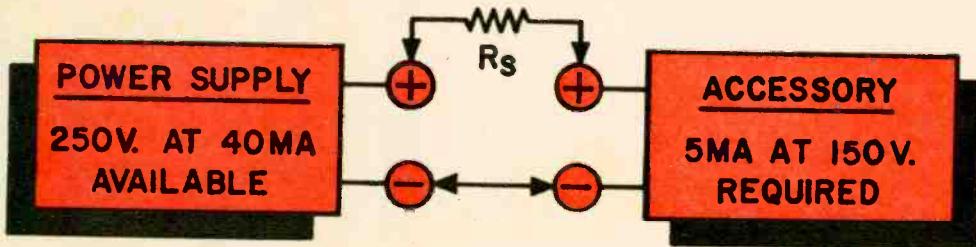(2) Determine how many volts (E) you need to drop with the series resistor. Just subtract the voltage required by the accessory (150 V) from that of the



Say we have a power supply with a 250-volt DC output. The accessory (crystal calibrator, RF preamplifier, etc.) requires 150 VDC. How do we drop the voltage to the required level? A resistor (R_s) in series with the DC supply will do the job (see diagram). We determine its value with the aid of Ohm's Law ($R = E/I$) in this way:

(1) Find the current (I) drawn by the accessory. This is given in the manufacturer's literature or can be determined by totaling the current drawn by the tubes or transistors. A tube or transistor manual will provide this information. An easier technique is to measure the current drawn with a milliammeter if you can operate the device at its normal voltage. For example, if you want to operate a 6-volt device on a 12-volt battery, first run it on 6 volts and measure its normal current with a meter in series with either power lead.

If the current value obtained is in milliamperes, it must be changed to amperes to fit into the Ohm's Law formula.

power supply (250 V). 100 volts becomes the E in the formula.

(3) Then use Ohm's Law to find the value of the resistor (R_s) in ohms.

$$R = 100/.005$$

$$R = 20,000 \text{ ohms}$$

(4) You'll need one more calculation—the wattage (W) of the resistor, determined by the formula $W = EI$.

$$W = 100 \times .005$$

$$W = .5 \text{ watts}$$

The answer calls for a half-watt resistor, but calculated wattage always should be doubled or tripled for long component life.

Although we haven't discussed it, the amount of current available from the power source should be considered also. Usually, an accessory with one or two tubes draws negligible current. If a supply has a 500-ma capability and the device being powered draws only 5 ma there may be a higher than usual voltage available from the supply. In that case, simply calculate R_s for the new higher voltage.—H. B. Morris



A REAL SHACK David L. Marks, W2APF, seems to have a thing about shacks, ham and otherwise. The old timer (he's been on the air since pre-WW I days) is proprietor of Uncle Dave's Radio Shack in Albany, N. Y., one of the first electronic supply stores in the country. When traveling (his second hobby) he always looks up hams he's worked on phone or CW. On a recent South African trip he found a different kind of shack, one with a straw roof. The opportunity was too good to pass up, so he got the occupants outside for a gag shot (see cut). According to him, the two men in the center

are running a two-drumpower transmitter bare-foot.

Flu Fun . . . It's hard to make out a case of flu as an adventure, but during a recent siege I was able, for a change, to get on the air for long periods. Matter of fact, I spent about ten hours a day for almost two weeks doing little but twirling knobs on my SSB rig. Besides the therapeutic effect (it says here), the activity gave me some unusual QSO's. Fr'instance:

Late one afternoon on 15 meters I heard an American voice calling W3TEM, signing OA8I. He was talking about a tape recording he wanted to make for a church at Asbury Park, N. J. When the W3 didn't answer, I tried a quick call: "Break, break . . . this is W2DJJ in New York. Can I help?"

OA8I came right back. Turned out to be a missionary team, Bob and Mary Anderson, at a jungle camp in a remote area of Peru. W3TEM was Mary's fa-

ther, who was to tape a message from Bob and send it to the church supporting him. The message would tell the congregation about his work and how he was doing. I volunteered to try the tape job and, though the band was noisy, I finally got about four minutes of voice from Bob and Mary. It took numerous attempts over about two hours. Next morning, I shot the reel off to Asbury Park, and I don't mind saying that contemplating my good deed made me feel a lot better.

No Gag . . . I should know better, but I keep associating accents with nationalities and countries. In the middle of the crowded 20-meter band one day I heard two British types discussing their experiences in the Royal Navy during World War II. "No question about where those guys are," I told myself while waiting for a chance to cut in. I

almost swallowed my mike when they identified themselves as K5QWZ, Oklahoma City, and VE3CWB/W6, portable somewhere in California.

I finally raised K5QWZ and asked what was going on. Turned out his accent is real, since he hails from Liverpool, but he's

lived here a dozen years now. He chuckled about how his voice baffles Americans (like me), who think they are working England, and English hams, who think they have a local.

He Made It . . . A few issues back I mentioned a friend who bought a complete Collins station even before he learned code, then flunked the exam. Well, he finally made it as WA2WXT. More trouble loomed, however. His landlord said nix to an outside antenna. Undaunted, he simply went out and bought a house and had a four-element beam up before he moved in.





NEW!

INTERNATIONAL


Model 1500 . . . for the Hobbyist . . .

Now . . . you can be on the air, and operate a two-way radio, without a license. The new International Model 1500 Executive transceiver is certified to fill all FCC Part 15 requirements.

Designed primarily for short range radio communication, you can **talk 1 to 10 miles** with the Model 1500 depending on the height of the antenna/transmitter. What's more there are no restrictions on working skip or sky-wave signals 1,000 miles or more when a band opening occurs. You can also use CW (code) transmission for maximum distance communicating.

The International Model 1500 transceiver is designed to put the maximum RF power into the antenna. This is accomplished by combining the transmitter and antenna into one unit for rooftop mounting, thus eliminating loss through a transmission line.

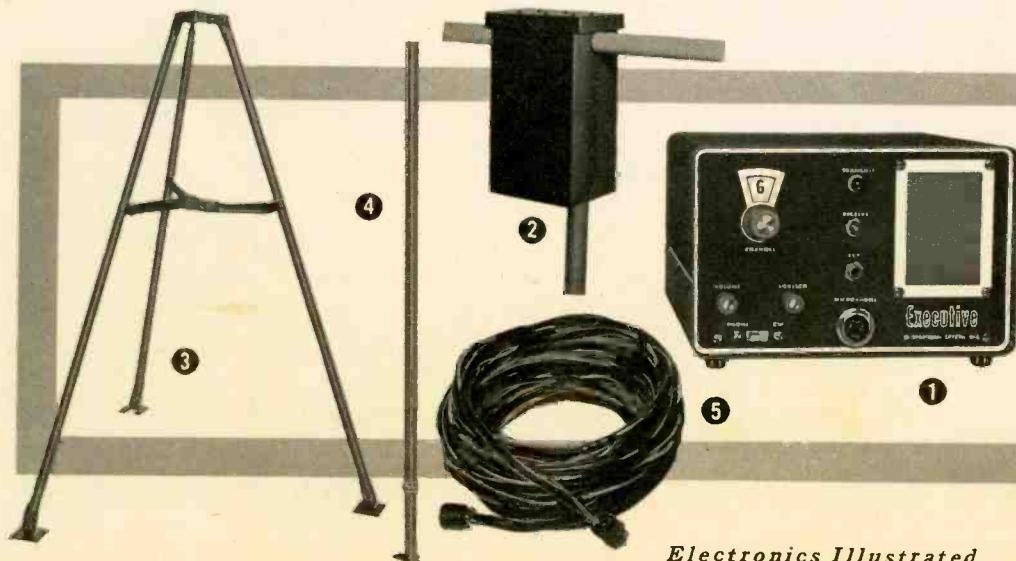The exciter unit remains with the receiver. A receiver preamplifier at the antenna boosts weak signals and helps reception. And in addition, the Model 1500 has a field proven supersensitive receiver with a crystal filter to reduce interference from adjacent channel Class D radio units.



EXECUTIVE TRANSCEIVER

No License Required!

- Certified for FCC Part 15 communication
- 100 milliwatts input / 60 inch antenna
- 27 mc frequency range
- Operates on phone and cw
- Eight channels . . . all crystal controlled
- 115 vac operation
- Quality components and construction

The Model 1500 is a complete package, ready to go on the air. The package includes: ① receiver/driver complete with 8 sets of crystals, ② transmitter/antenna assembly, ③ antenna mount, ④ 5 foot mast, ⑤ 100 feet of control cable, ⑥ microphone, ⑦ key for (CW).

Model 1500 Transceiver complete \$299.50*

See this exciting new transceiver at your International dealer. You can be on the air tomorrow with International's Model 1500.

*other models from \$80.00

Write for International's complete catalog of radio crystals and equipment.



March, 1963

11 Meters In Canada

Continued from page 75

Obtaining a GRS license is not at all like getting a ticket from the FCC. Here you wait several weeks while the wheels turn. In Canada the applications are processed in a matter of minutes while the operator waits. Canadians must pay \$3 for each unit licensed (every transmitter must have a separate license and call letters). Licenses here and there are alike; both are *station* licenses, not operator licenses.

Montreal has something over 1,000 CBers operating on the GRS channels, which correspond to U.S. CB channels 4 through 22. In the Province of Quebec, most populous in Canada, licenses are being issued at the rate of about 300 per month. Licenses are for three years.

All equipment must be tested and approved by the DOT and kits *per se* are banned. However, one U.S. company, Daystrom, has obtained approval for a kit by a clever setup in which the purchaser gets a transceiver that is minus

several important components. After building what he has, the buyer returns the rig to the factory for installation of the missing parts. DOT approval is obtained by the factory and the owner gets back a ready-to-operate unit.

Several CB clubs have been organized. We show letterhead art adopted by two of them (see cuts). Largest are the CB Club de la Province de Quebec (Canada, remember, has many French-speaking citizens) and the Quebec Pioneer 27 Mc Club (Montreal). The former has some 300 members. The president is Roger Trudeau, XM52052. The Pioneer club already has a good reputation for emergency work.

All callsigns begin with XM, but American CBers must pass them by when they crop up on the band. Both the United States and Canada have refused permission for CBers of the two nations to talk with each other. The penalty for this and other rules infractions for Canadians is license suspension for three months to a year.

—Jim Gibson, 2W7610

THE LEADER IN CITIZENS RADIO

EACH MONTH

You can receive a **BIG all-CB** packed issue of \$9 / *the citizens band journal*. Chock full of *simple* CB construction projects, CB features, club news, new product reviews, FCC and DOT news, CB humor, antenna construction, and basic CB-electronics theory! Articles written in easy-to-understand style by *every* top CB author: Tom Kneitel, Don Stoner, Len Buckwalter, Herb Friedman, Ed Noll, and many others. Send only \$5 for 12 great issues, or 50¢ for a sample copy! Send **NOW!**



Rush this to our office **NOW!**

S9

the citizens band journal

\$9 / *the citizens band journal*

300 West 43rd Street
New York 36, N. Y.

Gentlemen:



Enclosed is \$_____ for _____ BIG issues of S9. **RUSH** please, I don't want to miss the next issue!

Name _____, CB Call _____

Address _____

City _____, Zone _____, State _____

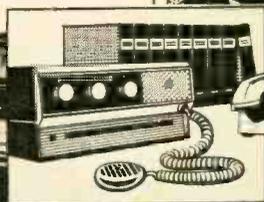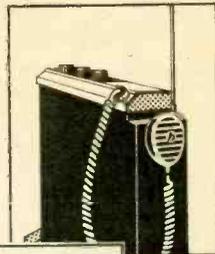Nothing fits all your CB needs like Hallicrafters' versatile new transistorized CB-5



Wherever and however you use citizens band, no transceiver made gets around with the effortless efficiency and consistent high performance of the new CB-5.

A fraction over 3 inches high, 10 inches wide and 8 inches deep, its 18-transistor design solves all normal space problems in mobile or airborne use. It has no vibrator of course, and you can operate it all day with less battery drain than it takes to start your engine once.

A slim, matching pedestal will furnish AC power for base operation. And for carrying between "stations," it weighs just 6¾ pounds.

For occasional portable use, an inexpensive 12-volt battery works out fine; but we've also designed a highly-efficient rechargeable battery pak accessory, in case you're serious about it. (There'll be a tone-coded squelch accessory, too, in the near future.)

Specifications? Here are a few: 5 watts in; 100% modulation capability; 6 crystal-controlled channels; 1 μ v sensitivity for 10 db. S/N ratio; 45 db. adj. channel rej.; PTT ceramic mike; 6 kc. selectivity at 6 db.; 18 transistors, 9 diodes, 3 instant-heat transmit tubes. Price: \$199.95; accessories optional at extra cost. For full details, talk it over with your Hallicrafters dealer or drop us a line.



the new ideas in communications
are born at . . .

hallicrafters

5th & Kostner Aves., Chicago 24, Ill.

Overseas Sales: Contact Export Department, Hallicrafters. Canada: Gould Sales Co., Montreal, P. Q.

A Confidential History of CB

Continued from page 83

the money for enforcement was not forthcoming. Lastly, more than a million dollars worth of equipment had been sold, manufacturers were tooled up for production, a big market was available and the electronics industry needed a shot in the arm. Strict enforcement could have meant enough lawsuits to smother a cloud of locusts.

The basement CB dealer was a phenomenon providing a basic economic insight into the business. With or without the knowledge of the manufacturer, he obtained a dealership or secondary dealership and started selling out of his basement. For advertising, this gent turned on his rig at 8 o'clock in the morning and extolled the virtues of his products far into the night. The only time he shut up was when someone came in to buy. His message always had the implication that only by buying his transceiver, with \$20 or \$30 worth of modifications, could your signal have real punch. His own signal was likely to have enough power to singe the tail feathers of low-flying crows. The real trouble lay in the fact that most of these basement technicians didn't know a tube from a toothpick, damaging many rigs with their modifications. They also encouraged hamming by their incessant yak. If they could do it, why couldn't anyone? In metropolitan areas the QRM was worse than on the 20-meter ham band during an opening to Australia.

A semblance of reason appeared in 1961. Sheer publicity brought CB to the attention of small businesses, garages, druggists, cleaning establishments and so on—people who *had* to stick with Class D radio, once the investment was made, because they couldn't afford a Class A system. This group eventually became the backbone of CB as we know it today. Meanwhile, the more intolerable crew got bored and left, realizing you can't keep saying nothing forever.

But CB had one last fling. This one revolved around the practice of "finking" on fellow licensees. If you didn't conform to what a self-appointed moni-

tor thought was proper CB procedure, he fired off a letter to the FCC, accusing you of everything from cussing to reading the Communist Manifesto. FCC wastebaskets began to look like pregnant hippos. The fact that the beefs were ignored (as gripes from individuals usually are) only infuriated the vigilantes more. One group we know about decided one day that it was illegal for the maintenance crew of a broadcast station to use a channel they claimed for themselves, so they started jamming with carriers powerful enough to fry an egg a block away. On another occasion, the leader of the gang held the air 40 minutes to describe a letter he sent the FCC about a CBER who had violated the rules by talking seven minutes.

Finking seemed to be dying a natural death when CB Horizons jerked it out of the cold, cold ground by organizing its readers in a Voluntary Monitoring Project. Each volunteer was to send "citations" to other CBERs who violated specific rules (usually violated by the volunteer himself). Individuals and clubs jumped in with all four feet. Some home-brew citations looked more official than the FCC's forms. Many victims assumed they had caught a bolt from Uncle Sam himself. Another storm was brewing. But this time the FCC swallowed its bemused smile and let it be known that the citations, because of the style and manner of handling (secrecy of communication was involved), might be in violation of postal regulations. So the let's-play-FCC-inspector game ended in a hurry.

In the last year there has been an increase in CB gear aimed at the ham type, carrying price tags equal to those on true amateur rigs capable of working the world. But another type of equipment also has appeared—the business unit with a single-channel transceiver designed only to provide basic communications at rock-bottom price. CB appears to be approaching a combination of what the FCC intended and "useful" hamming. That term might require some explaining. In the country you can drive for hours and hear only a few signals which are strictly business, coming from service stations, taxi

new and available now!

"MESSENGER TWO" CB TRANSCEIVER



"TONE ALERT"




SELECTIVE
CALLING
SYSTEM

- 10 channels at flip of a switch — illuminated indicator!
- Increased sensitivity, high adjacent channel rejection!
- New . . . high efficiency noise limiter circuit!
- Provision for plug-in selective calling system!

Here's the new "Messenger Two" — with everything you've ever wanted in CB transceiver! Basic circuitry is patterned after the popular "Messenger". Highly efficient circuit design makes full use of maximum legal power . . . delivers a penetrating signal that "outperforms 'em all!" Looking for maximum receiver sensitivity? This unit is hot — pulls in signals you wouldn't know were around with less sensitive equipment . . . and adjacent channel rejection is tops! Tired of noisy receiver? New, noise limiter circuit in the "Messenger Two" lets you know what QUIET really means in a CB rig! Positive acting "squelch" and automatic volume control circuits — 10 channel coverage — push-to-talk microphone. Only 5 $\frac{1}{2}$ " x 7" x 11 $\frac{3}{8}$ ", easy to install anywhere.

Cat. No. 242-162 115 VAC and 6 VDC \$169.95
Cat. No. 242-163 115 VAC and 12 VDC NET

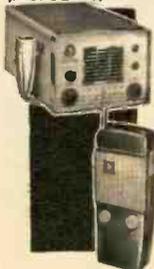5 CHANNEL "MESSENGER" TRANSCEIVER . . . Now at a new lower price, the big seller in the CB field! Excellent sensitivity and selectivity — punches out a power-packed signal! "Squelch" circuitry
Priced from \$129.95 NET



1 WATT AND 100 MILLIWATT "PERSONAL MESSENGERS"—Compact, 11 transistors and 4 diodes. Superhet receiver with exclusive tuned RF amplifier gives twice the sensitivity and 40% more range than similar units with conventional circuitry—more output than similar units with same rated inputs! Priced from \$109.50 NET

SEE YOUR DEALER-DISTRIBUTOR
AND ASK FOR A DEMONSTRATION

BRAND NEW! A complete selective calling system with 37 different available tones!

The ultimate for any CB installation — designed for serious industrial, police and emergency use. Mutes speakers on your units until one calls another — then automatically your stations receive audio note and indicator light flashes "on", remaining lighted until call is answered. Eliminates annoyance of hearing "skip", electrical noise, or transmissions not meant for you!

- Not a kit, ready to go! Plugs into "Messenger Two", fast hook-up to your existing equipment!
- Sharp selectivity guards against random triggering which broad response units can't prevent!
- Wide range of tones permits 37 different systems to operate on the same channel without overlap. Plug-in reed locks unit "on # channel"—no missed calls due to "wrong" position on selector switches!
- Universal mounting bracket for left, right, or remote mounting under dashboard or desk!
- Tone signal heard beyond normal voice communication distance, increasing coverage by miles!

Only 1 $\frac{1}{2}$ " wide x 4" high x 7 $\frac{3}{4}$ " deep — wired with all cables and hardware.

Cat. No. 250-810 115 VAC and 6 VDC \$59.95
Cat. No. 250-811 115 VAC and 12 VDC NET

FREE! 4-COLOR BROCHURE!



E. F. JOHNSON CO

® 7010 10th Ave. S.W. • Waseca, Minnesota

Please rush "Messenger" details to:

NAME _____
ADDRESS _____
CITY _____ STATE _____

firms and farmers. In the cities it's different. During the day there is much business activity and some unused channels. However, these stations do carry on short social conversations interlaced with business messages. In the evening these same CBers use the gear for straight hamming, joined now by night-time businesses, such as all-night garages, which seem to do it for lack of something more interesting. Spread out around the cities are the emergency-service CB clubs which do provide a needed community service by taking part in disaster and rescue work. While they do ham, their conversations usually concern emergency work. This is what we call useful hamming.

However, there is always a hard core of straight CB/hams because as each group of licensees gets bored with saying nothing it is replaced by a fresh new batch. Sometimes you might think the situation is getting worse, but it's getting better. The anything-goes type of operation is all but gone, and the CB/hams don't stay around long.

In the next few years the Citizens

Radio Service is likely to move closer to what was intended, though there always will be a monthly crop of jokers. But the FCC now has an ace in the hole. CBers finally have realized that there is a limit to its patience.

Basic CB Circuit Theory

Continued from page 44

of the transmitter. Now the mike feeds the amplifier (via S1B), which soups up the signal enough for it to serve as a modulation signal. Switch section S1C takes the output of the modulator/amplifier and switches it into the RF amp.

The S1D set of contacts switch the B+ voltage to receiver or transmitter. The modulator, which serves both functions, is powered at all times. In rigs using electronic switching instead of transferring the B+, the transmitter is biased to cutoff in the receive position. In the transmit position, the receiver input circuit is cut off.

Next issue, we'll examine a CB schematic in detail.

ELECTRONICS
ELECTRONICS
ELECTRONICS
ELECTRONICS
ELECTRONICS
ELECTRONICS
ELECTRONICS
ILLUSTRATED

Get the best magazine for all hobby electronics: Citizens Band radio, ham radio, audio & hi-fi, short-wave listening, kits, theory, test equipment... Subscribe now and make sure you get every issue! Special get-acquainted offer:

6 issues for only \$1.98

YES, I want to take advantage of your special get-acquainted offer. Please enter my subscription right away.

- | | |
|---|-----------------------------------|
| <input type="checkbox"/> I enclose \$1.98 | <input type="checkbox"/> Bill me |
| <input type="checkbox"/> New order | <input type="checkbox"/> Re-order |

NAME.....


ADDRESS.....

CITY..... ZONE..... STATE.....

Mail to: Electronics Illustrated
 Circulation Department
 Fawcett Bldg., Greenwich, Conn.

3-63

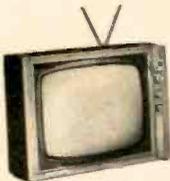VACUUM TUBE VOLT METER KIT (6-INCH METER)—RMS and p. to p. scale. Input impeded. 12.2 mega. Professional performance and appearance. Kit: \$31.95
Assembled: \$44.95



"CUSTOM 70" TV SET KIT—Excellent sensitivity. Transformer power supply; 3 stages of IF. Includes slimline cabinet, 19 inch picture tube—everything. NOT a portable. Kit Price: \$135.00

TRANSISTOR RADIO KIT—Superb tone and sensitivity. No delicate printed circuits. Attractive, durable case. All U.S. made parts. Kit: \$25.50



5-INCH WIDE BAND OSCILLOSCOPE KIT—For black-white, color, AM-FM and electronic applications. High intensity trace. Extremely stable sync. Advanced design. Kit: \$89.50
Assembled: \$139.50

GUARANTEE
Parts and performance guaranteed by NRI—nearly 50 years of pioneering in Electronics.

CONAR
3939 Wisconsin Ave., N.W.
Washington 16, D.C.

CE3C

Send me your new 1963 CONAR KIT CATALOG

Name _____

Address _____

City _____ Zone _____ State _____

Get your FREE 1963 CATALOG from CONAR

It's full of exciting new electronic kits of highest quality. Many items available in both kit or assembled form. Home entertainment items that make perfect family gifts or test instruments for the technician who appreciates quality and high performance. Tools, too, to make your work easier, faster. And you'll like the reasonable prices and convenient payment plans which make CONAR Kits easy to own. Mail coupon for new 1963 Catalog now.



CONAR

division of
NATIONAL RADIO
INSTITUTE

Mail this Coupon

CB Corner

Continued from page 52

tion and, as before, can be used only for selective calling—not for attracting attention or controlling remote objects.

Less far-reaching changes would limit any person to one license (if one is suspended you'd best not apply for a new one), and would require you to give a change of address within 30 days before or after moving your station and prior to operating at the new location.

Any messages relating to the performance, capabilities or testing of equipment, or to signal strength or frequency stability, would be outlawed.


Only substantial change in the antenna-height rules says your skyhook can't be more than 20 feet above a tree (as well as geological formations and man-made structures, as formerly). The FCC previously said trees didn't count, but the new rule would allow you to mount your antenna on top of a tree.

A new power limitation would be im-

posed. In addition to holding the input power to the final to 5 watts, you'd also be required to limit actual RF output to 3.5 watts. Since even the most efficient rig can't do much better than that, the new rule obviously is intended to make it easier for the FCC to check on your power—even from a distance. Input power is difficult to calculate but an RF wattmeter hooked to the output gives the facts in a hurry. One connected to the end of the feedline also would reveal any hidden linear amplifiers.

In the record department, each station would have to keep on file copies of reports on adjustments or alterations of equipment made by commercial licensees (signed by them, with license serial number appended). And, in addition to being familiar with Part 19, each licensee would have to keep an up-to-date copy at the station.

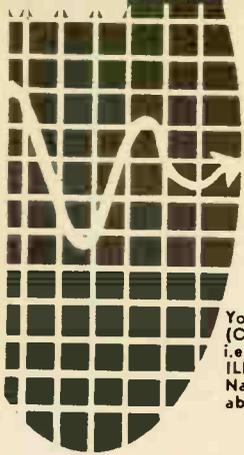Last in our brief of the more important changes is one requiring the complete call sign to be given distinctly, in English, and to be preceded by the words "this is" or "from."



ELECTRONICS ILLUSTRATED

Classified Ads

Your advertisement can reach this mail-buying audience for only 50¢ per word . . . payable in advance (Check or M.O. please) . . . minimum 10 words. Closing dates are the 20th of 4th preceding month i.e. copy for the July issue must be in our office by March 20th. Mail to ELECTRONICS ILLUSTRATED, 67 West 44th St., New York 36, N. Y. Word count: Zone number free. Figure one word: Name of state (New Jersey), name of city (New York); sets of characters as in key (14-D); also abbreviations as 35MM, 8x10, D.C., A.C.

SAVE MONEY • ORDER BY MAIL

• • • FOR SALE

EXCELLENT BUYS on Tubes and equipment all listed in the "Green Sheet." Send .25¢ for your copy today. Cash paid for unused tubes. Write, Barry Electronics Corp., 512 Broadway, Dept. EI, NYC 12, NY.

"LISTEN-IN-COIL" PICKS up any telephone conversation in vicinity. No connection to telephone necessary. Easily concealed. \$2.98 complete. United Acoustics, 512-X East 80, N. Y. 21, N. Y.

CONVERT ANY television to sensitive, big-screen oscilloscope. No electronic experience necessary. Only minor changes required. Illustrated plans, \$2.00. Relco, Box 10543, Houston 18, Texas.

INVESTIGATORS, WRITE for free brochure on latest subminiature electronic listening devices. Dept.-5-X Ace Electronics, 11500 NW 7th Ave., Miami 50, Florida.

GOVERNMENT SURPLUS. How and Where to Buy in Your Area. Send \$1.00. E.I. Surplus Information, Headquarters Bldg., Washington 6, D. C.

SUPERSENSITIVE DIRECTIONAL microphone picks up faint sounds at 300 feet. Detects sound through ordinary walls. Easily built for \$7.00. No electronic experience necessary. Plans \$2.00. Dee Company, Box 7243-C, Houston 8, Texas.

FCC WARNING Decal Against Unauthorized Use 2x3 (mobile) 35¢ 4/1.00, 3x4 (base) 65¢ 2/1.00. CB, Box 457, Encino, Calif.

• • • BUSINESS OPPORTUNITIES

BIG MONEY—Operate your own fix-it shop. Service all household appliances: irons, fans, refrigerators, automatic washer-dryers, etc. Know how they work, what goes wrong, and how to fix them. Learn how to do house wiring, commercial wiring, rewind motors of all sizes, sharpen mowers, skates, saws. How to get business, buy spare parts wholesale. What to charge for your work. FREE BOOK, Christy Trades School, A-413, 3214 W. Lawrence, Chicago 25.

YENDING MACHINES—No selling. Operate a route of coin machines and earn high profits. 32-page catalog free! Parkway Machine Corp., 715E1 Ensor St., Baltimore 2, Md.

\$100 WEEKLY POSSIBLE. Compile mailing lists and address envelopes for advertisers. Home — spare time. Particulars free. National Service, 81 Knickerbocker Station, New York City.

MAKE \$25-\$50 WEEK clipping newspaper items for publishers. Some clippings worth \$5.00 each. Particulars free. National, 81 Knickerbocker Station, New York City.

SECOND INCOME From Oil Can End Your Toil! Free Book And Oilfield Maps! National Petroleum, PanAmerican Building-EI, Miami 32, Florida.

• • • EMPLOYMENT OPPORTUNITIES

PRINTING - ADVERTISING SALESMEN. Excellent moneymaking sideline selling Decalcomania Name Plates. Advertising Specialties. Sign letters, Automobile initials. Free Samples. "Ralco"-EI, Box L, Boston 19, Mass.

ELECTRONICS OPPORTUNITIES. 100 Addresses of Companies Hiring. U. S., Overseas. \$2.00—Box 2061, Springfield, Va.

• • • I. Q. TESTS

I. Q. TESTS. Accurate, inexpensive. Home-administered, professionally interpreted. Research data needed. University Testing Institute, R-25, Box 6744, Stanford, California.

• • • BUILD-IT-YOURSELF

PROFESSIONAL ELECTRONIC Projects—Organs, Timers, Computers, etc.—\$1 each. List free. Parks, Box 1665, Lake City, Seattle 55, Wash.

• • • HI-FI & STEREO

4/TR Stereo Tapes—bought, sold, rented, traded! Bargain closeouts! Catalog/Columbia, 9651 Foxbury, Rivera, California.

• • • TAPE RECORDERS

LEARN WHILE Asleep with your recorder, phonograph or amazing new "Electronic Educator" endless tape recorder. Details free. Sleep-Learning Research Association, Box 24-EI, Olympia, Washington.

RENT STEREO Tapes—over 2500 different—all major labels — free catalog. Stereo-Parli, 811-AV Centinela Ave., Inglewood 3, California.

TAPE RECORDERS Hi-Fi Components. Sleep Learning Equipment, tapes. Unusual values. Free Catalog. Dressner, 1523 Jericho Tpke., New Hyde Park-4, N. Y.

NEW CONCEPT of self-hypnosis teaches you quickly, easily. New tape! New record! Free literature. McKinley-Smith Co., Dept. T-3, Box 3038, San Bernardino, Calif.

SALE ITEMS—Tapes—Recorders—Component Quotations. Bayla, Box 131E, Wantagh, N. Y.

• • • RADIO & TV

DIAGRAMS: RADIO \$.75, Television \$1.50. Baker, 129 Cooper, Santa Ana, California.

BEFORE YOU Buy Receiving Tubes, Test Equipment, Hi-fi Components, Kits, Parts, etc. . . . send for your Giant Free Zalytron Current Catalog, featuring Standard Brand Tubes: RCA, GE, etc.—all Brand New Premium Quality Individually Boxed, One Year Guarantee—all at Biggest Discounts in America! We serve professional servicemen, hobbyists, experimenters, engineers, technicians. Why Pay More? Zalytron Tube Corp., 461 Jericho Turnpike, Mineola, N. Y.

10 DISTANCE CRYSTAL set plans—25¢; 20 different—50¢. Includes Transistor experiments, catalog. Laboratories, 1131-K Valota, Redwood City, California.

DIAGRAMS FOR Repairing Radios \$1.00, Television \$2.00. Give make, model. Diagram Service, Box 672E1, Hartford 1, Conn.

• • • DETECTIVES

DETECTIVE PROFESSION. Easy home study plan. Lapel pin, certificate, future. Free information. Professional Investigators, Box 41197-CC, Los Angeles 41, Calif.

DETECTIVES—EXPERIENCE unnecessary. Detective Opportunities. Write, Wagner, B-125 West 86th, New York 24.

• • • MUSIC

NOVELTY—TURN of the century circus calliope recording 12" L.P. \$3.95—tape 7½" \$3.95. T.V. and radio tubes 40% off list. Discs made from tapes. Ann-Ro Recording Studio, 9211 Grayton, Detroit 24, Michigan.

PLAY LATEST Popular Piano Music at sight, "tricky" rhythm and "wicked harmony" \$2.50. Waiter Kazaks, 234 E. 58th St., New York 22.

• • • PERSONAL

INDEPENDENT THINKERS—investigate Humanism, the scientific personal philosophy! Free literature. American Humanist Association, Dept. EI-2, Yellow Springs, Ohio.

• • • MISCELLANEOUS

ROCKETS: IDEAL for miniature transmitter tests. New illustrated catalog, 25¢. Single and multistage kits, cones, engines, launchers, trackers, technical information, etc. Fast service. Estes Industries, Penrose 13, Colorado.

HYPNOTIZE UNNOTICED, quickly effortlessly or refund! Thousands satisfied! \$2.00. Getro, Box 244, Cedarburg, Wisc.

"HOMEBREWING" . . . BEERS, Wines, Scotchies, Champagnes, Liqueurs, etc. Complete instructions. \$1.00. Harvey's, 1402-EIC, Englewood, Colorado.

CB Skip

Continued from page 51

One of the real troubles caused by skip signals lies in their strength. A direct groundwave, in traveling five miles, is weakened by bumping into hills, buildings, trees and other obstacles, and part of its power is absorbed by the earth. The skip signal follows a path almost clear of obstruction (except for the ionosphere) and arrives a thousand miles away with bulging muscles. If you're trying to call from your car to your house when skip is coming in on your channel, you run into a lot of trouble. The stranger from afar simply clobbers your signal.

What can you do about such interference? Nothing. On the back of your license you'll find a little message wherein you have agreed to accept all interference from CB and other sources. It's a problem you'll have to live with—one that a good many CBers would, unfortunately, like to have.

Working skip on the Citizens Band

was serious enough at one time to be covered when the FCC revised Part 19.

That the Commission meant business was demonstrated by a spate of violation notices sent out to erring CBers.

Before ending our piece we must pass on two of the better skip stories currently going the rounds. In one instance, a couple of practical jokers dreamed up a call with a Hawaiian prefix which they began using while driving in a car. After pulling in a victim, who was thrilled at working a station 6,000 miles away, the two made the whole routine even more convincing by driving in and out of an alley, creating the illusion of atmospheric fading.

The other story concerns an Easterner who was driving along some five miles west of Minneapolis when he heard a station with a call that indicated the West Coast. The two began talking, each believing he had hooked a real long-haul signal. As it turned out, the West Coaster also was in his car—traveling the same road less than five miles ahead of the Easterner.



**NEW...
The World's
most advanced
11 meter
two-way radio...**

General is in command with the new MC 5

3.25 watts minimum output. • New High Power Modulation system for
Zener Diode shunt noise-clamp and series gate

Largest Power supply

ONLY GENERAL MC5 HAS SIDEBAND NOW!

See It At Your General Dealer TODAY!

General Radiotelephone Company, DEPT. E-3

3501 Burbank Boulevard, Burbank, California

RAD-TEL

You Get MORE For Your Money!

RAD-TEL'S QUALITY BRAND NEW TUBES FOR TV, RADIO AND HI-FI 1-YEAR GUARANTEE

UP TO **75% OFF**

1-DAY SERVICE • Over 500 Types in Stock



SERVICEMEN:
RAD-TEL HAS THE LATEST TUBE TYPES.

THE SIGN OF RAD-TEL'S RELIABILITY FOR OVER 15 YEARS

Manufacturers Suggested List Price

EACH TUBE ATTRACTIVELY BOXED & BRANDED RAD-TEL

Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price
—	0Z4	.79	—	6AU8	.87	—	6K6	.63	—	12CU5	.58
—	1AX2	.62	—	8AV6	.41	—	6S4	.52	—	12CU6	1.06
—	1B3	.79	—	6AW8	.90	—	6SA7GT	.99	—	12CX6	.54
—	1DN5	.55	—	6AX4	.66	—	6SH7	1.02	—	12D4	.69
—	1G3	.79	—	6AX5	.74	—	6SJ7	.88	—	12DE8	.83
—	1J3	.78	—	6BA6	.50	—	6SK7GT	.95	—	12DL8	.88
—	1K3	.79	—	6BC5	.61	—	6SL7GT	.84	—	12DQ6	1.04
—	1R5	.77	—	6BC8	1.04	—	6SN7	.65	—	12DS7	.84
—	1S5	.75	—	6BE6	.55	—	6SQ7GT	.94	—	12DT5	.76
—	1T4	.72	—	6BF5	.90	—	6T4	.99	—	12DT7	.79
—	1U5	.65	—	6BF8	.44	—	6T8	.85	—	12DT8	.78
—	1X2B	.82	—	6BG6	1.70	—	6U8	.83	—	12DW8	.89
—	2AF4	.96	—	6BH8	.98	—	6V6GT	.54	—	12DZ6	.52
—	3AL5	.46	—	6BJ6	.65	—	6W4	.61	—	12E05	.52
—	3AU6	.54	—	6BJ7	.79	—	6W6	.71	—	12EG6	.82
—	3AV6	.42	—	6BK7	.85	—	6X4	.41	—	12EK6	.52
—	3BC5	.63	—	6BL7	1.09	—	6X8	.80	—	12EL8	.50
—	3BN6	.75	—	6BN6	.74	—	7A8	.68	—	12EZ6	.57
—	3BU8	.78	—	6BQ6	1.12	—	7AU7	.65	—	12F8	.66
—	3BY6	.58	—	6BQ7	1.00	—	7EY6	.75	—	12FA6	.79
—	3BZ6	.56	—	6BU8	.70	—	7Y4	.69	—	12FM6	.50
—	3CB6	.56	—	6BX7	1.11	—	8AU8	.90	—	12FR8	.97
—	3C56	.58	—	6BZ6	.55	—	8AW8	.93	—	12FX8	.90
—	3DG4	.85	—	6BZ7	1.03	—	8BQ5	.80	—	12GC6	1.06
—	3DK6	.60	—	6C4	.45	—	8CG7	.63	—	12J8	.84
—	3DT6	.54	—	6CB6	.55	—	8CM7	.70	—	12K5	.75
—	3GK5	.99	—	6CD6	1.51	—	8CN7	.97	—	12L6	.73
—	3Q4	.63	—	6CG7	.61	—	8CS7	.74	—	12SF7	.69
—	3S4	.75	—	6C8B	.80	—	8EB8	.94	—	12SK7GT	.95
—	3V4	.63	—	6CL8	.79	—	8FQ7	.56	—	12SL7	.80
—	4BQ7	1.01	—	6CM7	.69	—	9CL8	.79	—	12SN7	.67
—	4C56	.61	—	6CN7	.70	—	11CV7	.75	—	12SQ7GT	.91
—	4DT6	.55	—	6C8C	.92	—	12A4	.60	—	12U7	.62
—	4GM6	.60	—	6CR6	.60	—	12AB5	.60	—	12V6	.83
—	5AM8	.79	—	6CS6	.57	—	12AC6	.55	—	12W6	.71
—	5AN8	.90	—	6CS7	.69	—	12AD6	.57	—	12X4	.47

RAD-TEL TUBE CO. NOT AFFILIATED WITH ANY OTHER MAIL ORDER TUBE COMPANY

—	5AQ5	.54	—	6CU5	.58	—	12AE6	.50	—	17AX4	.67
—	5AT8	.83	—	6CUI6	1.08	—	12AE7	.94	—	17DQ6	1.06
—	5BK7	.86	—	6CV5	.70	—	12AF3	.73	—	18FW6	.49
—	5BQ7	1.01	—	6CY7	.71	—	12AF6	.67	—	18FX6	.53
—	5BR8	.83	—	6DA4	.68	—	12AJ6	.62	—	18FY6	.50
—	5C6B	.81	—	6DE6	.61	—	12AL5	.47	—	19AU4	.87
—	5CL8	.76	—	6DE6	.62	—	12AL8	.59	—	19BG6	1.39
—	5CQ8	.84	—	6DJ8	1.21	—	12AQ5	.60	—	19EA8	.79
—	5EA8	.80	—	6DK6	.59	—	12AT6	.50	—	19T8	.85
—	5EU8	.80	—	6DN6	1.55	—	12AT7	.76	—	21EX6	1.49
—	5J6	.72	—	6DQ6	1.10	—	12AU6	.51	—	25AX4	.70
—	5T8	.86	—	6DT5	.81	—	12AU7	.61	—	25C5	.53
—	5U4	.60	—	6DT6	.53	—	12AV6	.41	—	25CA5	.59
—	5U8	.84	—	6DT8	.94	—	12AV7	.82	—	25CQ6	1.52
—	5V6	.56	—	6EAB	.79	—	12AX4	.67	—	25CUG	1.11
—	5X8	.82	—	6EBS	.73	—	12AX7	.63	—	25DNG	1.42
—	5Y3	.46	—	6EB8	.94	—	12AY7	1.44	—	25EH5	.55
—	6AB4	.46	—	6EM5	.77	—	12AZ7	.86	—	25L6	.57
—	6AC7	.96	—	6EM7	.82	—	12B4	.68	—	25W4	.68
—	6AF4	1.01	—	6EU8	.79	—	12BD6	.50	—	32ET5	.55
—	6AG5	.70	—	6EV5	.75	—	12BE6	.53	—	35C5	.51
—	6AH4	.81	—	6EW6	.57	—	12BF6	.80	—	35L6	.60
—	6AH6	1.10	—	6EY6	.75	—	12BH7	.77	—	35W4	.42
—	6AK5	.95	—	6F67	.69	—	12BK5	1.00	—	35Z5	.60
—	6AL5	.47	—	6FV8	.79	—	12BL6	.56	—	36AM3	.36
—	6AM8	.78	—	6GH8	.80	—	12BQ6	1.16	—	50B5	.69
—	6AQ5	.53	—	6GK5	.61	—	12BR7	.74	—	50C5	.93
—	6AS5	.60	—	6GK6	.79	—	12BV7	.76	—	50EH5	.55
—	6AT8	.49	—	6GN8	.94	—	12BY7	.77	—	50L6	.61
—	6AT8	.86	—	6H6	.58	—	12BZ7	.86	—	70L7	.97
—	6AU4	.85	—	6J5GT	.51	—	12CNS	.56	—	117Z3	.85
—	6AU6	.52	—	6J6	.71	—	12CR6	.67	—	807	.75

ORDER FORM • MAIL TODAY

RAD-TEL Tube Co.
Dept. EI-3
55 Chambers Street
Newark 5, New Jersey

ENCLOSED IS \$ _____

Total Tubes \$ _____
Total Part(s) \$ _____
Postage \$ _____
Grand Total \$ _____

Please rush order.

SEND: _____ (Book(s) Be Your Own TV Repairman @ \$1.00 ea. #170)
Cheater Cord 29c ea. Lots of 3 - 25c ea. #154
Orders under \$5.00 - Add \$1.00 handling charge - plus postage.

FREE! Send FREE Tube and Parts Catalog
 Send FREE Trouble Shooting Guide

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____



Be your own TELEVISION REPAIRMAN
The Original NOW YOU CAN

FIX YOUR OWN TV SET BOOK
You can fix your own TV if you have TV Fixit Book . . . because 80% of troubles are caused by tubes. This book explains, illustrates trouble and what tubes cause this trouble. Pinpoints in over 3000 layouts by model number, position and type tube causing trouble. **\$1.00**



CHEATER CORD Easy to work on set while panel is off.
6 ft., No. 154 **29¢ ea.** Lots of 3 - 25¢ ea.

RAD-TEL TUBE CO.

DEPT. EI-3 55 CHAMBERS STREET, NEWARK 5, NEW JERSEY TV, RADIO AND HI-FI

TERMS 25% deposit must accompany all orders, balance C.O.D. Orders under \$5. add \$1 handling charge plus postage. Orders over \$5. plus postage Approx. 8 tubes per 1 lb. Subject to prior sale. No C.O.D.'s outside continental U.S.A.

The new RCA MARK VIII 27-Mc 2-WAY RADIO



More Features • Improved Performance • AT A LOWER PRICE

Here is THE outstanding bargain today in a 2-way Citizens' Band radio: THE NEW RCA MARK VIII. Compact, dependable, simple to operate, it outperforms and offers more features than even the famous RCA Mark VII.

Look what this remarkable new unit offers you:

- 9 crystal-controlled transmit and receive channels
 - Tunable receiver for reception of 23 C-B channels; dial marked in both channel numbers and frequency
 - Exceptionally good voice reproduction—high intelligibility
 - Maximum allowable transmitter input of 5 watts*—nominal output of 3 watts or more
 - Highly selective superheterodyne receiver with one rf and two if amplifier stages
 - Operates from standard 117-volt AC; separate DC power supply (optional) for mobile installations (you don't pay for unnecessary power supplies)
 - Electronic switching—no relay noise or chatter
 - Illuminated "working channel" feature
 - Light and compact—only 3½ inches high, weighs only 8 pounds with mike; fits easily under the dashboard of even a compact car
 - Improved Automatic Noise Limiter to reduce effects of ignition and similar interference
- plus many more features to increase its usefulness and efficiency.

The new low Mark VIII price **\$149⁵⁰****
puts 2-way radio convenience within reach of everyone

GET THE FULL STORY; FILL OUT AND SEND IN THE COUPON BELOW

RCA Electron Tube Division, Commercial Engineering, Dept. C-134-R
415 South Fifth Street, Harrison, New Jersey

Please! Rush more information on the new RCA Mark VIII 2-way
Citizens' Band Radio.

Name _____

Address _____

City _____ Zone _____ State _____

*Maximum plate input power to final radio-frequency
amplifier stages as defined by FCC regulations

**Optional list price



The Most Trusted Name in Electronics



GET AMERICAN BASIC SCIENCE CLUB'S

New, Revised **ELECTRONICS LAB**

All the Equipment for 65 Exciting Projects

plus a **BASIC RADIO COURSE** for only **\$17.80**

Available in One Complete Shipment or Divided into 4 Monthly Kits as Shown

TROUBLE SHOOTING WITH THE SIGNAL TRACER

YOU GET A VALUABLE **ELECTRONICS LAB**

Containing parts by RCA, MALLORY, PYRAMID, E. CENTRALAB, TACKPOLE, RIM and other reliable manufacturers. Retail value of parts alone is **MORE THAN 25 DOLLARS**

PLUS A COMPLETE **ELECTRONICS COURSE**

You **REALLY LEARN ELECTRONICS**. The progressive "learn by doing" American Basic Science Club system is the **easiest, most thorough and most exciting way** to a solid background in electronics. Basic enough for beginners... rewarding enough for experts. **Nowhere else is a course of this scope available at this LOW PRICE!**

ENTHUSIASTIC MEMBERS WRITE:

"basic principles unforgettably learned" . . .

It is only after having completed the experiments in your kits that I can say I have truly and unforgettably learned the basic principles of electronics. JOHN R. KANIA, 2 Berkeley Ave., Yonkers 5, N.Y.

"your kits are interesting and rewarding" . . .

I am an electronics student in the Air Force and find your kits interesting and rewarding. We have not covered anything in the school that you have not covered in the kits. JOHN G. DILL, Keesler Air Force Base, Biloxi, Miss.

"far ahead of friend taking another course" . . .

A friend of mine is taking a correspondence course in electronics, and I have learned more from your first two kits than he has in twenty lessons. RAY P. BILDEAU, 139 Exchange St., Leominster, Mass.

"the number of concepts presented is amazing" . . .

Your kits offer a range of experiments usually performed only in the better high school and college laboratories. The number of concepts presented, and the clarity and completeness of their development is amazing. R. W. HELM, Professor of Physics, East Carolina College, Greenville, N. C.

KIT 1 — DC AND AC CIRCUITS

Equip. for 26 Projects Including:
 • Electroscopes • Electro Magnet
 • Galvanometer • AC Buzzer • Demagnetizer • Relay • Solenoid
 Coin Tossing • Safety AC Power Supply with Isolation Transformer
FREE with kit 1 — Surprise "Mystery Box"

Subjects Covered Include:
 • Magnetic Fields • Electron Theory • Electric Charge • Direct Current • Electro-Chemistry • Alternating Current • Inductance • Transformer Principles

KIT 2 — RESISTANCE, CAPACITANCE AND RECTIFICATION

Equip. for 18 Projects Including:
 • Strobe Light • Thermocouple • Wheatstone Bridge • Voltmeter • AC Rectifier • DC Power Supply

Subjects Covered Include:
 • Ohm's Law • Power Formulas • Rectification • Resistance • Neon Glow Tubes • Capacitance • Filter Circuits

FREE with kit 2 — Electric Soldering Iron

KIT 3 — AMPLIFIERS AND OSCILLATORS

Equip. for 14 Projects Including:
 • Two Stage Amplifier • Capacitance Burglar Alarm • Proximity Detector • High Speed Strobe Light • Ripple Tank Wave Generator • Code Practice Oscillator

Subjects Covered Include:
 • Vacuum Amplifier Tubes • Voltage Amplification • Oscillator Circuits • Frequency and Wave Length Sound Waves, Pitch and Resonance

FREE with kit 3 — "Steps to a Ham License" Manual

KIT 4 — AUDIO AMPLIFICATION AND RADIO

Equip. for 7 Projects Including:
 • Microphone and Audio Amplifier • Broadcast Radio • Short Wave Radio • Signal Tracer • Continuity Tester • Transmitter

Subjects Covered Include:
 • Audio Amplifiers • Amplitude Modulation • Radio Theory • Regenerative Circuits • Tuning Circuits

FREE with kit 4 — Radio-TV Service Manual

ALL FOUR KITS IN ONE SHIPMENT ONLY \$17.80 POSTPAID

OR—YOU CAN GET THE FOUR KITS, ONE A MONTH

SEND **\$2.00** WITH **PAY \$3.95** PLUS COD POSTAGE ONLY **COUPON** ONLY **ON RECEIPT OF EACH KIT.**

ALL SHIPMENTS ON 10 DAY APPROVAL. YOUR SATISFACTION OR YOUR MONEY BACK. WE KNOW YOU WILL BE AMAZED AND DELIGHTED.

USE THIS "NO RISK" COUPON FOR EITHER PAID IN FULL OR MONTHLY PLAN

—AMERICAN BASIC SCIENCE CLUB, Inc., 501 E. Crockett, San Antonio 6, Texas—

Send me ABSClub's Electronics Lab in four kits — one a month. I enclose \$2.00 and will pay \$3.95 plus COD Postage on arrival of each kit. I understand that all kits will be on 10 day approval with full refund guaranteed and also that I may cancel unshipped kits at any time.

Send me ABSClub's Electronics Lab (all four kits) in one shipment. I enclose \$17.80 full payment, postage paid to me. I understand that this will be on a 10 day approval with full refund guaranteed.

NAME

ADDRESS

CITY and STATE