

Build: VLF Rcvr., Syncopated Metronome, Super-Speed Strobe

ELECTRONICS ILLUSTRATED

By the Publishers of MECHANIX ILLUSTRATED

MARCH 1966 • 354



EXCITING NEW READER-PARTICIPATION
FEATURE BEGINNING IN THIS ISSUE!

UNCLE TOM'S CORNER

Conducted by Uncle Tom Kneitel



Build This **PALM-SIZE**

It weighs just 28½ ounces, and has 2 tubes and

411236 565 777006 3678
THOMAS POULIN 1
5717 RENDLE AVE
DULUTH MINN 55803

Sands Who Gained ough NRI

TRAINING KITS XCITING, FAST

ls of NRI gradu-
, Industrial Electri-
n and Radio
hter futures and
Training men to
ctronics has been
y. NRI pioneered
ome instruction,
g equipment fur-
time-proved way
train. With NRI
tter position with
e on to greater
atter how much
have,
plans



Make \$3 to \$5 An Hour in Spare Time

You don't have to wait until you get an NRI diploma to start earning. As many others have done, you can be making \$3 to \$5 an hour in your spare-time as you train, fixing radios and TV sets for friends and neighbors. You learn how to install, maintain and service stereo hi-fi, radios, TV sets (including color), even how to charge for service and how to set up your own spare-time or full-time business. Many students pay for their NRI training out of spare-time earnings long before they graduate.

Skilled Technicians Are in Demand

There has never been a time when ambitious men with specialized Electronics knowledge were as much in demand as they are today. From television service shops to launching pads, there's a profitable place for you as a skilled technician to help service, operate, install and supervise Electronically-controlled equipment. The NRI diploma is respected and recognized in business and industry. It can be your key to success in America's "glamor" industry.

Achievement Kit Gets You Started Fast

As soon as you enroll with NRI we deliver to your door everything you need to make a fast start in the Electronics training of your choice. This new Achievement Kit is an unparalleled example of the value of NRI home-study training. No other school has anything like it. Find out about the NRI Achievement Kit, about NRI training equipment, about NRI courses, about opportunities for success in Electronics. Send for the NRI catalog. There's no obligation. No salesman will call. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D. C. 20016.

MAIL POSTAGE-FREE CARD NOW

PICK YOUR FIELD FROM NRI'S SPECIALIZED INSTRUCTION PLANS

1 TELEVISION-RADIO SERVICING

Complete training from basic fundamentals of electricity to home entertainment equipment. You learn to fix radios, hi-fi and stereo sets, black-and-white and color TV, etc. A profitable field full or part time.

2 INDUSTRIAL-MILITARY ELECTRONICS

From basic principles to computers. A comprehensive training plan that teaches you the fundamentals, then takes you into such modern-day miracles as servos, telemetry, multiplexing, pulse circuitry, data processing, other important subjects.

3 COMPLETE COMMUNICATIONS*

Designed to teach and provide you with actual practice in operation, service and maintenance of AM, FM and TV broadcasting stations. Also covers marine, aviation, mobile radio, facsimile, microwave, radar.

4 FCC LICENSE*

Specifically designed short course to prepare you for your First Class FCC Radiotelephone License examinations. You begin with a thorough background in fundamental Electronic principles, advance to required subjects covering equipment and procedures.

5 MATH FOR ELECTRONICS

A brief course for engineers and technicians who need a quick review of the essential mathematics used in industry, communications, in government jobs. Basic arithmetic review, shortcut formulas, modern digital number system, much, much more.

6 BASIC ELECTRONICS

A concise course to teach modern Electronics terminology and components. A wealth of practical, useful information to help you better understand the field, to give you some technical knowledge. For anyone who wants basic understanding of Radio-TV Electronics.

7 ELECTRONICS FOR AUTOMATION

This course is not for beginners. Offered for men with some fundamental knowledge of Electronics who want better understanding of Automation in present day use. Covers process control, ultrasonics, telemetering, and remote control, electromechanical measurements, other subjects.

8 AVIATION COMMUNICATIONS*

This course prepares you to install, maintain, service aircraft communications equipment. Covers direction finders, ranges, markers, Loran, Shoran, Radar, landing systems. Earn your First Class FCC License with Radar Endorsement.

9 MARINE COMMUNICATIONS*

Covers transmitters, direction finders, depth indicators, radar, sonar, other equipment used on commercial ships and thousands of pleasure boats. Prepares you for a First Class FCC License with Radar Endorsement.

10 MOBILE COMMUNICATIONS*

Learn to install and maintain mobile equipment and associated base stations. Covers transmitters and receivers used by police and fire departments, public utilities, construction projects, taxis, etc. Prepares you for a First Class FCC License.

*NOTE: You must pass your FCC License exam (any Communications course) or NRI refunds in full the tuition you have paid.

The Oldest and Largest School of its Kind in America



**WHERE YOU TRAIN IS AS IMPORTANT
AS YOUR DECISION TO TRAIN**

At NRI you are backed by 50 Years of leadership in home-study training for Electronics • Automation • TV • Radio



**J. E. Smith,
Founder—1914.**

Fifty years ago, a school teacher named James E. Smith started giving extra instruction to four of his students in the "mysterious" new field of radio. From that small beginning, National Radio Institute has grown to be America's largest home-study school in the many fields of Electronics. Nearly three-quarters of a million students have enrolled over the years. This vast experience is behind NRI's meaningful, interesting, easy-to-understand methods of training; methods that make Electronics a practical subject for almost anyone to learn no matter how much or how little formal education he has.

But experience is only the *base* upon which NRI is built. Today there is a staff of more than 150 dedicated people working with you as a "class" of one, keeping training material up-to-the-minute, providing consultation services as you train, advising you about new developments in Electronics, even helping you with job placement when you're ready. Ask men whose judgment you respect about NRI training. And send for the catalog we offer. Read about opportunities in Electronics, about new developments, about NRI itself and the variety of training plans open to you at reasonable cost. Mail the postage-free card today.

JOIN MEN LIKE THESE— TRAIN FOR SUCCESS WITH NRI

"I went into my own business six months after finishing the NRI Radio-TV Servicing Course. It makes my family of six a good living. We repair any TV or Radio. I would not take anything for my training with NRI. It is the finest."

DON HOUSE, Lubbock, Texas



"Many thanks to NRI for the Electronics training I received. I hold a first class FCC License and am employed as a studio and master control engineer/technician with KXJB-TV."

RONALD L. WOOD, Fargo, N.D.

"I am a Senior Engineering Aide at Litton Systems, in charge of checkout of magnetic recording devices for our computers. Without the help of NRI I would probably still be working in a factory at a lower standard of living."

DAVID F. CONRAD, Reseda, Calif.



"NRI training enabled me to land a very good job as Electronic Technician with the Post Office Dept. I also have a very profitable spare-time business fixing Radios and TV."


**NORMAN RALSTON,
Cincinnati, Ohio**

ELECTRONICS ILLUSTRATED

MARCH, 1966

A Fawcett Publication

Vol. 9, No. 2

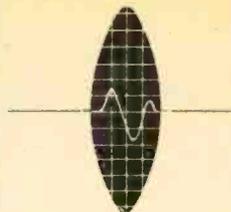

New Feature

Uncle Tom's Corner Tom Kneitel, K2AES/KBG4303 23

General Features

Last Stand For Brass Pounders Elbert Robberson, W2FRQ 49
 EI Picturescope 84

Construction Projects

Super-Speed Strobe Jim Kyle, K5JKX 62
 The Phonocom Lawrence Glenn 68
 The Syncopated Metronome Morris Grossman 75

Radio: CB • Amateur • SWL

The Mini-Mitter Russ Alexander, W6IEL 27
 The Listener: High Seas C. M. Stanbury II 34
 Full-Band VLF RCVR Charles Green, W3IKH 39
 CB Corner: Instant Enforcement Len Buckwalter, KBA4480 56
 Notes From EI's DX Club 61
 Presidential DX Alex Bower 67
 The Ham Shack: Perplexer Robert Hertzberg, W2DJJ 74
 DX à Go Go Don Carter 80

Audio & Hi-Fi

Kit Report: Stereo Tape Deck 32
 Life Goes On & On at 40 Ken Gilmore 45
 Hi-Fi Today: Platters & Promises John Milder 52

Theory & Practice

The ABCs of Radio: Part IV, The Superheterodyne John T. Frye, W9EGV 57
 Six-Bit Meter Saver Chet Stephens 86
 Beginner's Corner: The Case of the Invisible Gate H. B. Morris 87

Regular Departments

Feedback From Our Readers 6
 Electronics in the News 10
 Electronic Swap Shop 14
 Broadides 20
 Subscription Blank 20
 Electronic Marketplace 21
 Good Reading Tim Cartwright 38
 Over and Out Tim Rodrigues 94

Audit Bureau of Circulations



MEMBERSHIPS



Magazine Publishers Association, Inc.



COVER — Ektachrome by
 Grayson Tewksbury, EI
 Studios. Illustration by
 George Janes.

DEVRY TECH NOT ONLY TRAINS
YOU... BUT HELPS YOU GET
STARTED AT NO EXTRA COST IN
THE **BIG-MONEY FIELD** OF

ELECTRONICS!

✓ PREPARE AT HOME

Whether you want to prepare for a good-paying new job or for advancement in Electronics with your present employer, DeVry Tech offers specialized educational programs designed to meet your needs. You set up your own HOME LABORATORY and work over 300 construction and test procedures to develop on-the-job type skills. You build a quality Transistorized Meter, a 5-inch Oscilloscope and a special Design Console. DeVry also includes modern "programmed" texts, Instructive motion pictures, Consultation Service. Effective? Yes!

✓ RESIDENT SCHOOL

If you prefer you may get all of your training in DeVry's U.S. or Canadian resident schools under the close guidance of friendly, experienced instructors. You work with a wide variety of commercial equipment similar to that actually used in industry as you prepare in our laboratories for a technician's job in Communications, Microwaves, Radio-Television, Automation, Radar, Computers, or other branch of Electronics. DeVry even provides part-time job placement service to those who wish to earn extra money while attending day or evening classes.

✓ PLACEMENT SERVICE

Meet W. E. Bartz, who has helped thousands of DeVry men toward exciting, profitable careers in Electronics. When YOU complete your program, he will help you too. As Placement Manager in touch with business and industry across the nation, Bartz knows the employer demand for DeVry-trained men. He has cooperated in placing our graduates with thousands of firms!

Men 18-45, start preparing NOW for this vast opportunity field. Soon you should be ready for DeVry's valuable employment help!

MAIL COUPON TODAY!

**No Advanced
Education or
Previous Technical
Experience Needed
to Get Started**

Your ambition and desire to succeed are more important! DeVry guides you every step of the way toward success.

Free

Send coupon
for these two
factual book-
lets NOW!



DEVRY TECHNICAL INSTITUTE

4141 Belmont Avenue • Chicago, Illinois 60641

Accredited Member of National Home Study Council

HOME LABORATORY EQUIPMENT
— YOURS TO KEEP!



EXPERIENCED
INSTRUCTORS



DEVRY TECHNICAL INSTITUTE
4141 Belmont Avenue, Chicago, Ill., 60641 Dept. EI-3-W

Please give me your two free booklets, "Pocket Guide to Real Earnings," and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- | | |
|--|---|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications |
| <input type="checkbox"/> Television and Radio | <input type="checkbox"/> Computers |
| <input type="checkbox"/> Microwaves | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radar | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics | <input type="checkbox"/> Electronic Control |

Name _____ Age _____


Address _____ Apt. _____

City _____ State _____ Zip _____ Code _____

Check here if you are under 16 years of age.

2103 HOME STUDY AND RESIDENT SCHOOL TRAINING
AVAILABLE IN CANADA

whether you operate
a space
rocket...

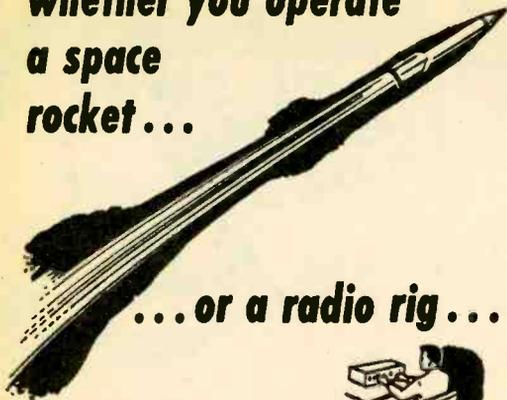

...or a radio rig...



**YOU NEED
TEXAS CRYSTALS
to control frequency!**

Why TEXAS CRYSTALS? Simply because you can be sure of their doing the job perfectly, just as they have in numerous space projects. And, TEXAS CRYSTALS are unconditionally guaranteed! Regardless of your crystal needs—CB, amateur, commercial 2-way, low frequency, marine, aircraft, etc.—see your parts dealer for TEXAS CRYSTALS.

If your dealer can't supply your TEXAS CRYSTALS needs, send his name with your order to our plant nearest you.



- CB • AMATEUR
- COMMERCIAL
- RADIO CONTROL
- MILITARY
- MINIATURE
- LOW FREQUENCY
- AIRCRAFT



**TEXAS
CRYSTALS**

A Division of Whitehall Electronics Corp.

1000 Crystal Drive
Fort Myers, Florida
Phone 813 WE 6-2109

4117 W. Jefferson Blvd.
Los Angeles, California
Phone 213 731-2258

ELECTRONICS ILLUSTRATED

By the Publishers of MECHANIX ILLUSTRATED

editor **ROBERT G. BEASON**
 managing editor **Robert D. Freed**
 feature editor **Richard A. Flanagan**
 art editor **Lou Rubsamen**
 editorial associate **Albert P. Lahndt, Jr.,
K2IAG**
 production editor **Rosanne Walsh**
 advertising mgr. **John F. Webster**
 eastern adv. mgr. **Don Daily, KBI0618**

CONTRIBUTING EDITORS

amateur radio **Robert Hertzberg, W2DJJ**
 citizens band **Len Buckwalter, KBA4480**
 swl-dx **C. M. Stanbury II**
 special projects **Herb Friedman,
W2ZLF/KBI9457**
 audio **Harry Kolbe**
 audio **John Milder**
 audio **David Muirhead**

EXECUTIVE STAFF

president **W. H. Fawcett, Jr.**
 general manager **Roger Fawcett**
 secretary-treasurer **Gordon Fawcett**
 circulation director **Roscoe K. Fawcett**
 vice president **Ralph Daigh**
 asst. general manager **Donald P. Hanson**
 production director **George H. Carl**
 art director **Al Allard**
 associate art director **Ralph Mattison**
 director of advertising **Mortimer Berkowitz, Jr.**

ELECTRONICS ILLUSTRATED is published bi-monthly by Fawcett Publications, Inc., Fawcett Bldg., Greenwich, Conn. 06830. Second-class postage paid at Greenwich, Conn., and at additional mailing offices.

EDITORIAL OFFICES: 67 W. 44th St., New York, N.Y. 10036 (phone 212-661-4000). Contributions must be accompanied by sufficient postage and will be handled with care, though the publishers assume no responsibility for return thereof.

ADVERTISING OFFICES: 67 W. 44th St., New York, N.Y. 10036 (phone 212-661-4000); 612 N. Michigan Ave., Chicago, Ill. 60611 (phone 312-DE 7-4680); 1532 Guardian Bldg., Detroit, Mich. 48226 (phone 313-WO 2-4866); 2978 Wilshire Blvd., Los Angeles, Calif. 90005 (phone 213-DU 7-8258); 681 Market St., San Francisco, Calif. 94105 (phone 415-EX 7-3441); 1430 W. Peachtree St., N.W., Atlanta, Ga. 30309 (phone 404-TR 5-0373); James B. Boynton, 370 Testaqua Dr., Jupiter, Fla. 33458 (phone 305-746-4847); 123 S. Broad St., Philadelphia, Pa. 19109 (phone 215-PE 6-3636).

SUBSCRIPTIONS: \$4 for 12 issues in U.S. and possessions and Canada. All other countries \$6 for 12 issues. All subscription correspondence, including changes of address (Form 3579), should be addressed to ELECTRONICS ILLUSTRATED, Subscription Dept., Fawcett Bldg., Greenwich, Conn. 06830. Foreign subscriptions and sales should be remitted by International Money Order in U.S. funds payable at Greenwich, Conn.

COPYRIGHT © 1966 by Fawcett Publications, Inc. Reproduction in whole or in part is forbidden without written permission of the publishers; however, permission is hereby granted to quote from this issue of this magazine on radio or television, provided a total of not more than 1,000 words is quoted and credit is given to the title of this magazine and issue, as well as the statement, copyright 1966, by Fawcett Publications, Inc.

PRINTED IN U.S.A. BY FAWCETT-HAYNES PRINTING CORP., LOUISVILLE, KY. 40201. Microfilm copies of current and back issues are available from University Microfilms, 313 N. First St., Ann Arbor, Mich. 48103.



If you had started wiring yesterday, today you would own an amplifier as good as a Fisher.



If you didn't start yesterday, why not today or tomorrow? No matter when you start it, you will finish the Fisher KX-200 StrataKit faster than you thought possible. Anyone can build it—even your mother—and end up with a magnificent 80-watt stereo control-amplifier. Once built, it will be fully equal in performance and reliability to its laboratory-wired prototype.

The StrataKit method of kit construction is an exclusive Fisher development that takes the uncertainty and work out of kit building. Large, detailed diagrams and clear, nontechnical language make everybody an expert, regardless of previous experience. Assembly proceeds in simple, error-proof stages (Strata). Each stage corresponds

to a *separate* fold-out page. Each stage has a separate packet of parts (StrataPack). The major components are factory-mounted on the extra-heavy-gauge steel chassis. Most of them are riveted for improved reliability. Wires are *precut* for every stage—which means every page. All work can be checked stage-by-stage and page-by-page before proceeding to the next stage.

The end result is a low-distortion 80-watt amplifier which is powerful enough for *any* music, *any* loudspeaker. The exclusive center-channel output and separate volume control eliminate the need for an additional amplifier with either a center-channel or a remote loudspeaker.

Five minutes of listening to the Fisher KX-200 *you* built will

convince you that it is one of the finest control-amplifiers available, easily worth \$250 or more. Yet the kit costs only \$169.50. (Walnut cabinet, \$24.95; metal cabinet, \$15.95.)

FREE \$1.50 VALUE! Send for The New Kit Builder's Manual, an illustrated guide to high fidelity kit construction, complete with detailed specifications of all Fisher StrataKits.

Fisher Radio Corporation
11-35 45th Road
Long Island City, N. Y. 11101

Name _____

Address _____

City _____ State _____

213

The Fisher

FISHER RADIO CORPORATION, INC., 11-35 45TH ROAD, LONG ISLAND CITY, N. Y. 11101. OVERSEAS AND CANADIAN RESIDENTS PLEASE WRITE TO FISHER RADIO INTERNATIONAL, INC., LONG ISLAND CITY, N. Y. 11101.

FEEDBACK


from our readers



Write to: Letters Editor, Electronics Illustrated, 67 West 44th Street,

New York, N.Y. 10036

● A SWINGER

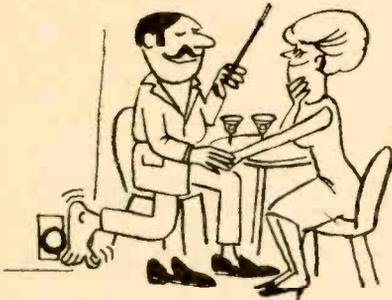

I'm pretty good looking and have a fair amount of charm but that new light-dimming gadget (UNIVERSAL LIGHT DIMMER, Jan. '66 EI) should give me a perfect score. Give most broads a nice romantic setting and a little schmaltz and you have no worries. If you have any more little goodies lying around I sure would like to hear about them.

M. G.
New York, N.Y.

● CASCADER

I seem to be having a problem with a few amplifiers of mine and I regard you as just the people I was looking for. Here's my problem: now I know this sounds silly, but I'm having trouble hooking one amplifier (phono) into another and getting a clean signal, one without hum. The output impedance of the first amplifier is 4 ohms and I don't have any idea how many thousands of ohms the input of the second one is. What I actually want to do is tie four 4-ohm outputs together and feed them into one amplifier (phono type) input.

Stephen C. Keating
Topeka, Kan.

Why?

● SHOPPER


I have been working in order to establish the design and performance characteristics

for a tri-pitched femto waveguide. I am attempting to establish the relationship among the circular cylinders to the left and the quadri-rectangular-prismic resonant cavity. As of this date I have experienced flat response through the upper cylinder with low-pass response in the direction of the lowest cylinder. The mode lattice was impossible to establish in the left central cylinder even though it appears better than the Moreno cross guide coupler. Even and also odd mode impedance in the parallel and the slab line has given me difficulties. Where will I be able to find data that has the potential to establish the necessary susceptance of symmetrical irises?

D. M.
Ann Arbor, Mich.

Have you tried the Yellow Pages?

● A WINNER!

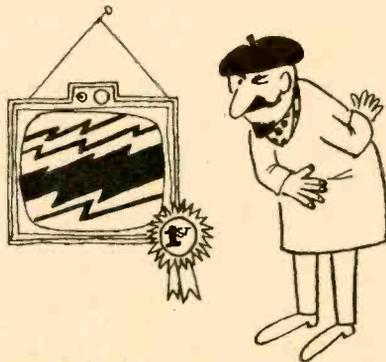

As for Whistler's Ma (AND NOW . . . FLAT TV!!!, Jan. '66 EI), she's been off her rocker for years. And so is anyone who doesn't believe that flat TV will not only be the greatest thing in home entertainment since sex but the biggest inspiration for pop art since the Campbell soup label. Dig those crazy test patterns, man. Who needs Picasso?

C. Z.
San Francisco, Calif.

BUILD YOUR OWN RADIO

CIRCUITS AT HOME

with the New Improved
PROGRESSIVE RADIO "EDU-KIT"®

ONLY
\$20.95



Reg. U. S.
Pat. Off.

A Practical Home Radio Course

Now Includes

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND NEEDED FOR TV
- ★ SCHOOL INQUIRIES INVITED
- ★ Sold in 79 Countries

**YOU DON'T HAVE TO SPEND
HUNDREDS OF DOLLARS FOR A RADIO COURSE**

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL. You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis. You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, Square Wave Generator and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the low price you pay. The Signal Tracer alone is worth more than the price of the Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits and doing work like a Professional Radio Technician.

Included in the "Edu-Kit" course are Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build twenty different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifiers, volume controls and switches, etc.

In addition you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a Professional electric soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to FCC Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation, Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.

UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER FROM AD—RECEIVE FREE BONUS
RADIO & TV PARTS JACKPOT WORTH \$15

- Send "Edu-Kit" Postpaid. I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Rush me FREE descriptive literature concerning "Edu-Kit."

Name _____

Address _____

PROGRESSIVE "EDU-KITS" INC.

1186 Broadway, Dept. 571AE, Hewlett, N. Y. 11557

Training Electronics Technicians Since 1946

FREE EXTRAS

- SET OF TOOLS
- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE & QUIZZES
- TELEVISION BOOK & RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE & F.C.C. AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS


You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

FROM OUR MAIL BAG

J. Stataitis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."


Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Trouble-shooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

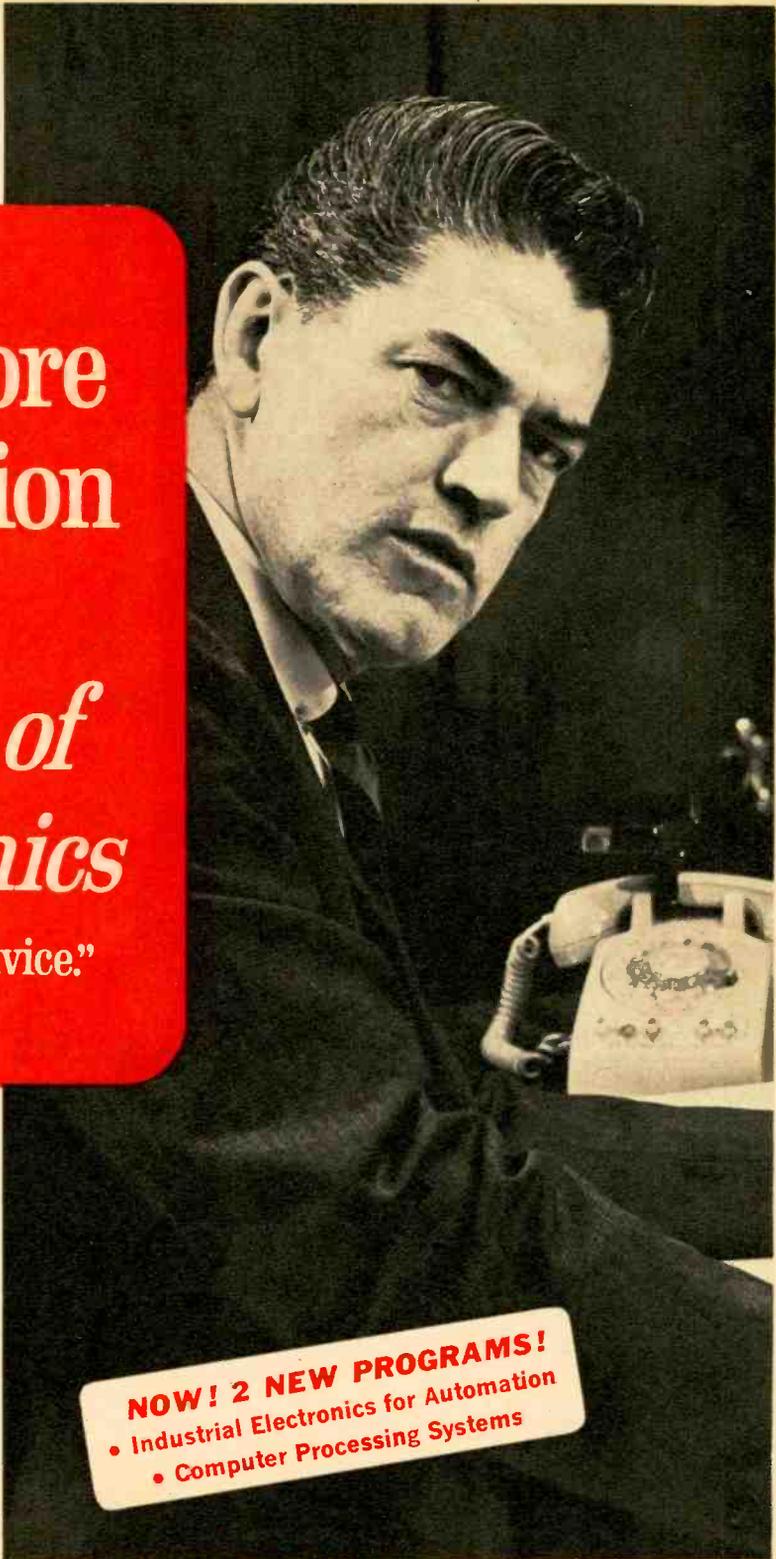

**“Get more
education
or
*get out of
electronics*
...that’s my advice.”**

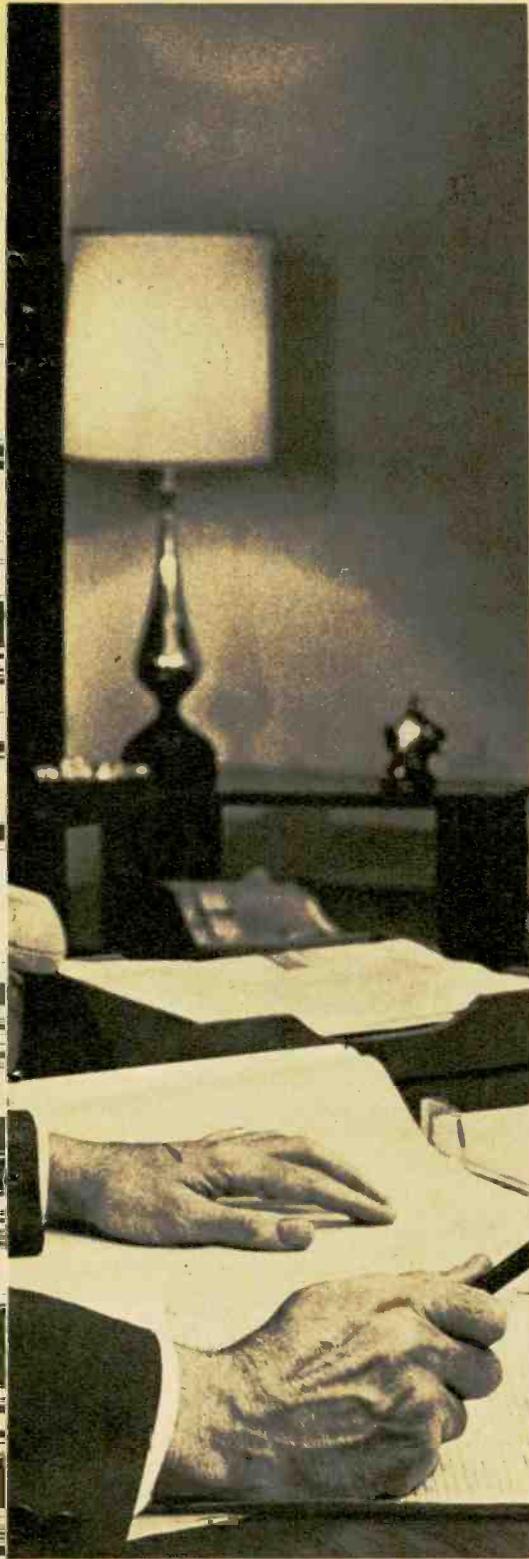- NOW! 2 NEW PROGRAMS!**
- Industrial Electronics for Automation
 - Computer Processing Systems



Ask any man who really knows the electronics industry. Opportunities are few for men without advanced technical education. If you stay on that level, you'll never make much money. And you'll be among the first to go in a layoff.

But, if you supplement your experience with more education in electronics, you can become a specialist. You'll enjoy good income and excellent security. You won't have to worry about automation or advances in technology putting you out of a job.

How can you get the additional education you must have to protect your future—and the future of those who depend on you? Going back to school isn't easy for a man with a job and family obligations.

CREI Home Study Programs offer you a practical way to get more education without going back to school. You study at home, at your own pace, on your own schedule. And you study with the assurance that what you learn can be applied on the job immediately to make you worth more money to your employer.

You're eligible for a CREI Program if you work in electronics and have a high school education. Our FREE book gives complete information. For your copy, mail coupon today or write: CREI, Dept 1703D, 3224 Sixteenth Street, N.W., Washington, D.C. 20010.



SEND FOR FREE BOOK

The Capitol Radio Engineering Institute
 Dept. 1703D, 3224 Sixteenth Street, N.W.
 Washington, D.C. 20010

Please send me FREE book describing CREI Programs. I am employed in electronics and have a high school education.

NAME _____ AGE _____

ADDRESS _____

CITY _____ STATE _____ ZIP CODE _____

EMPLOYED BY _____

TYPE OF PRESENT WORK _____

I am interested in Electronic Engineering Technology
 Space Electronics Nuclear Engineering Technology
 NEW! Industrial Electronics for Automation
 NEW! Computer Processing Systems

FROSTY SILENCE . . . Because booster thrust always is limited, output from transmitters on satellites ordinarily is restricted by considerations of weight and space. Result is, conventional receivers here on earth have trouble picking up satellites' feeble signals. Even low-noise amplifiers fill the bill only to a point, and adding additional stages to boost weak signals coming from greater distances only results in more noise than signal. Promising solution to the problem is a device called a cryogenic stripline circulator being tested by the gal in our photo at the Marconi Research Laboratories, Great Bad-dow, England. Explanation is that even low-noise amplifiers grow more silent the frostier they become. And at the frigid levels of liquid nitrogen (-196°C) and liquid helium (-269°C) the hush is noiseless as pure nothingness. Anxious earthlings now will be able to tune in on signals from distant satellites in a silence that is golden.




...electronics in the news

Round, Man . . . A sphere easily can be seen in the mind's eye, though a perfect sphere (like a perfect anything) seemingly exists more perfectly in the mind than in reality. To be sure, man does pretty well at the sphere business, which explains why it takes sensitive instruments to measure a sphere's irregularities. Such an instrument recorded the amplified imperfections of the 3½-in.-diam. ball in our photo. Currently being used by researchers at the Albuquerque Division of ACF Industries, the device is so sensitive that variations of a mere 3 millionths of an inch appear as minor mountains on the trace.



Junior Juke . . . A record changer sans turntable sounds as believable as smoke without fire, though a trip to Norway's capital city of Oslo soon would reveal that such a changer exists. Developed by Norway's Radionette and known as the Multiplayer, this unique device accepts up to twenty-five, 7-in. 33½- or 45-rpm recordings. All spin simultaneously on a single horizontal spindle. Thing is, pressing one of the 50 buttons juke-box-style causes one of two arms to travel along a guide rail to the desired record side. Total playing time? Over six hours, with hi-fi sound furnished by a built-in, 15-watt, solid-state amplifier and speaker or from optional external speakers that easily may be attached.

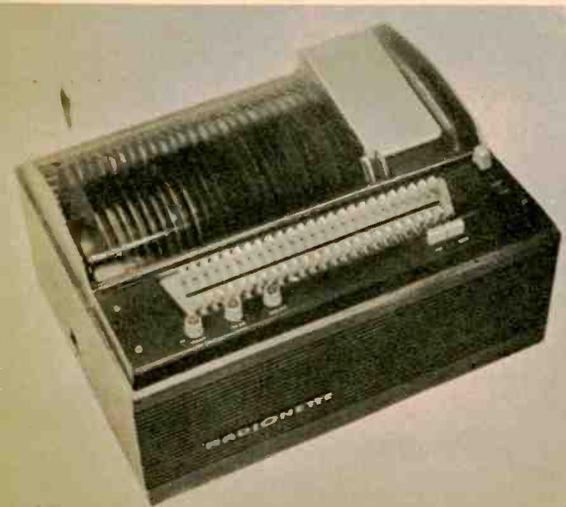

Electronics Illustrated



In this age of extravagance we set out to build the sensible receiver!

Ey We assume your first interest is in the music, not the machine — with no zest for unneeded bulk, excess cost, or useless gewgaws in your equipment.

That's why controls are uncomplicated on the E-V 1178 receiver, despite its versatility.

That's why it is one of the smallest all solid state receivers you can find, despite its 50 watt amplifier power

and full AM/Stereo FM capabilities.

And that's why our performance standards meet the most critical musical taste, not some theoretical ultimate of perfection in printed specifications. The sound is just exceedingly good.

The crisp decorator look of the E-V receiver is your extra bonus.

Just \$315.00 with integral walnut-paneled enclosure.

Guaranteed for two years — the new Model E-V 1178.

We also offer a Stereo FM receiver (E-V 1177) realistically priced at \$280.00. Separate tuners and amplifiers, too. A postcard will bring our color brochure. It makes good sense.

ELECTRO-VOICE, INC.
Dept. 3641, 622 Cecil Street
Buchanan, Michigan 49107



Philippine Powerhouse . . . Though the chap in our photo looks as if he's trying to do something right down at the Rheingold brewhouse, he really is a technician inspecting a motor:



driven tank coil. A vital part in each of ten new transmitters under production at Hughes Aircraft, the coils will be used in the Voice of America's new station in the Philippines. The VOA ordered the 250-kw transmitters with a mind to

bridging the Bamboo Curtain. Reason: each can be tuned to any of 20 preset channels in a mere 20 seconds, thus giving operators an edge in electronic fencing games with Red jammers. The broadcasting complex will be surrounded by some 50 antennas, each capable of radiating a signal as far as 5,000 miles. And should Red jamming ever become too severe, the station still will have an ace in the hole. All ten transmitters tuned to the same frequency would blast a billion watts of effective radiated power.

ITEM . . . The increasing number of pirate stations operating off the British Isles may hammer the government into accepting commercial radio. Official circles, keeping one eye on the popularity ratings of pirate programming and the other on possible fees and taxes, are looking for a face-saving method of issuing licenses. Government recognition of the stations would permit them to move ashore. But, once on land, they would be required to pay income taxes and broadcasting fees. They pay neither now, while enjoying large audiences, large incomes, social acceptance, listings in entertainment columns ("First installment of first pirate radio soap opera, Dr. Paul," notes London Life) and even car-racing gamesmanship. So why should they accept an invitation to come ashore? We don't know—unless they just like to do everything wrong.

Silence is Golden

(in mobile installations)

Only two transceivers can live up to that claim. That's because only two transceivers have the exclusive Squires-Sanders Noise Silencer (patent applied for). There's the famed "23'er", with full 23-channel capability (all crystals supplied). Now, there's an economically priced mate, the "S5S" with 5 crystal-controlled channels. Both have the Noise Silencer—something no other transceiver has.

This unique development utilizes a pre-IF silencer that detects noise before the pulse is broadened by IF selectivity. By detecting before IF selectivity, the noise silencing pulse is as short as possible, so that a minimum of the signal is eliminated. There's no loss in signal level, no introduction of audio distortion—a common drawback of the ordinary noise limiting devices used in other transceivers. The result: crisp, mobile reception of even the weakest signals without annoying background noises. No suppression gadgets are required.

Other features are: an ultra-sensitive (0.5 μ v) receiver featuring sharp 8 kc selectivity accomplished through a crystal bandpass filter; solid-state design (25 silicon transistors, 7 diodes); smooth, adjustable squelch; 3 x 5 front-facing speaker; provision for external speaker and instant conversion to public address via an optional adaptor.



The transmitter utilizes full legal transmitter input (5-watts) with a special high efficiency RF output amplifier, clipped and filtered audio (speech booster) for top talk power (100% modulation). Both units have a built-in power supply for 12VDC (negative ground) mobile operation, mobile mounting bracket, 12VDC connecting cable and quality push-to-talk microphone. Two AC power supplies are available—deluxe Master Model featuring transistor voltage regulation and a built-in "S" meter at \$39.50; Standard model at \$19.50.


THE "23'ER"—23 channels (all crystals furnished) \$235.
NEW "S5S" AM TRANSCEIVER—all the features of the "23'er" (Noise Silencer, ultra-sensitive receiver, etc.) except it is for 5-channel operation. May be used on 27 mc business frequencies. Furnished matched crystal for channel 9 (HELP), only \$185.00.

An exciting new product is the Squires-Sanders FM ALERT, FM emergency receiver with 2 crystals receive channels plus tunable control. Choice of 30 to 50 mc, or 152 to 174 mc, \$89.95. Matching speaker \$9.95. Other products include: Squires-Sanders HF receivers and Clegg VHF transceivers and receivers. See them at your dealer, or write for descriptive brochure. Squires-Sanders, Inc., Martinsville Rd., Millington, N.J. 07946.

Squires Sanders

Only Courier gives you a 23-channel transistor CB rig

for \$169

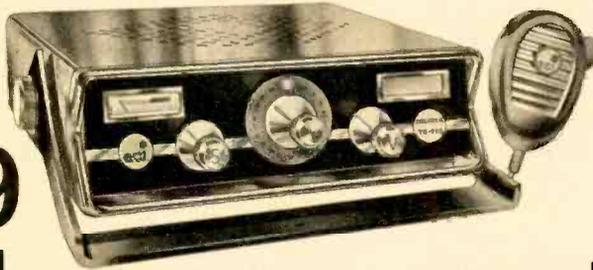

and can guarantee it for 10 years!

What do you do for an encore after introducing the industry's finest 23-channel transistorized CB rig for the unheard price of \$169? Tag it with a 10 year guarantee!

Silicon-transistors throughout bring the size down to 5¾"W x 6¼"D x 1⅞"H. With big-size performance. Complete, with microphone and a long list of features you want. Illuminated S meter. Illuminated channel selector. All crystals supplied for 23 channels. PA system. Auxiliary speaker jack. Single-knob tuning. Modulation indicator. DC cord. Chrome cabinet. Plus exclusive Courier "Safety-Circuit" to protect against mismatched antenna, incorrect polarity, and overload.

You can see the Courier TR-23S at your nearest Courier dealer. Or use the coupon for all the data on the amazing Courier TR-23S—the CB rig with the ten year guarantee.

EI-63

 **e.c.i. electronics communications inc.**
56 Hamilton Avenue, White Plains, N.Y.

Yes! I'd like to know all about the \$169 Courier TR-23S with the 10 year guarantee!

Name _____

Address _____

City _____ County _____ State _____

A "LONG RANGER"

The SHAKESPEARE
fiberglass

WONDERSHAFT

offers:

- protection from weather
a salt water area must
- durable construction
takes high winds with ease
- low background noise
- insulated conductor

The BIG STICK 176 is an excellent CB 18'6" — 27.1 mc fiberglass WONDERSHAFT antenna . . . all direction coverage . . . minimum of dead spots . . . no ground radials . . . independent of mounting location.

See your favorite dealer or write
Columbia Sales Office,

C/P CORPORATION

a subsidiary of the

Shakespeare

COMPANY

RFD 3 • COLUMBIA, S. C.

TELEPHONE 787-8710 area code 803

ELECTRONIC SWAP SHOP

El's Swap Shop provides a way for readers to obtain equipment they want in exchange for items they no longer have use for. Notices must be from individuals; commercial concerns are referred to El's classified advertising columns. Entries must include your name and address as well as a description of what you now have and what you would like in exchange. Address: El's Swap Shop, ELECTRONICS ILLUSTRATED, 67 West 44th Street, New York, New York 10036.

WESTON 301 meter. Make swap offer. L. Cohen, 151-40 13th Ave., Beechhurst, N.Y. 11457.

EICO 368 sweep generator/marker. Want Dynaco 100 or 200 microphones. David J. Raibert, 10 Wilsey Square, Ridgewood, N.J. 07450.

HEATH Apache, Heath DX-40, Hallicrafters SX-99, EICO 723 and Knight Span Master. Will trade for 6- and 2-meter gear. Jim Batka, WA9CUH, 350 18th Ave. S., Wisconsin Rapids, Wis. 54494.

KNIGHT Span Master. Want signal generator or Novice transmitter. Jim Hughes, 412 N. Walnut, Itasca, Ill. 60143.

HOMEBREW signal generator, variable 150-VDC power supply, transistor amplifier and preamp, electric clock, 125-V crank generator. Want coils, crystals, old radios. J. Rodney Clark, 1586 Liveoak Dr., Port Credit, Ont.

TRF BC receiver. Will trade for EICO 211 tube tester. Francis Elmer, Maribel, Wis.

HEATH HX-11 Novice transmitter. Will swap for 2-meter transceiver. Gil Colaianni, 3 Loretta Circle, Little Rock, Ark. 72205.

EICO 955 capacitor checker, Knight Star Roamer. Will trade for CB transceiver. David W. De Wald, 13240 Vassar Dr., Detroit, Mich. 48235.

ATWATER-KENT model 44 receiver, assorted old tubes. Will trade for RCA TV model 9T256. Earle Philhower II, Box 3, Yardville, N.J. 08620.

SPRAYBERRY electronic course. Will swap for automatic code sender. Michael Sutton, 83 Maple St., Rouses Point, N.Y.

AMPLIFIER (6-tube), other items. Want small tape recorder. B. Willmann, 86 Brent St., Port Arthur, Ont.

INVERTER, 6VDC to 120VAC. Need 12VDC inverter or communications equipment. Rich Young, 2-S Laurel Hill Rd., Greenbelt, Md. 20770.

SIMPSON 262 VTVM, model airplane engines. Will exchange for communications equipment or tape recorder. Bob Goldstein, 2620 Ocean Pkwy., Brooklyn, N.Y. 11235.

FISHER-PIERCE 3000-watt lighting control. Want all-band receiver. Norman Spryer, 3659 Ashgrove Dr., Grove City, Ohio 43123.

TRANSMITTING TUBES (5514s), 1200-V plate transformer. Will swap for anything of equal value. D. C. Payne, Pop's Men's Wear, Haw River, N.C.

KNIGHT RF generator, Heath Q-multiplier, BC-453 receiver. Need Knight T-60. Greg Gebele, 421 Second St., Lakewood, N.J. 08701.

HARVEY WELLS Bandmaster with VFO. Will trade for Viking Ranger. Gerald Manning, K4WWL, Rocky Face, Ga.

TESLA COIL TRANSFORMER, 905 CRT, 922 photo-cell, assorted crystals. Will swap for Novice transmitter. Dave Bock, 58780 Romeo Plank Rd., Washington, Mich.

WEBCOR tape recorder. Will exchange for anything of equal value. Joseph Zak, Box 131, Sagamore, Pa. 16250.

HALLICRAFTERS S-38 receiver. Make swap offer. Mike Nazzaro, WA2VBX, Box 85, Rocky Point, N.Y. 11778.


HEATH Twoer transceiver. Need Knight T-60. David Meade, WN2SYR, 91 Elberon Ave., Hawthorne, N.J.

BIG EAR listening device, dynamic mike. Will exchange for any mike listed on p. 215 of Lafayette catalog 650. P. J. Yudell, 425 W. Sierra Madre Blvd., Sierra Madre, Calif.

KNIGHT 100-in-1 electronics lab kit, assorted components. Will swap for transistor radio or hi-fi amplifier. Bob Goettsche, 22439 Park, Dearborn, Mich.

ROYAL typewriter, cameras, other items. Will exchange a tape recorder, Novice transmitter, test

[Continued on page 16]

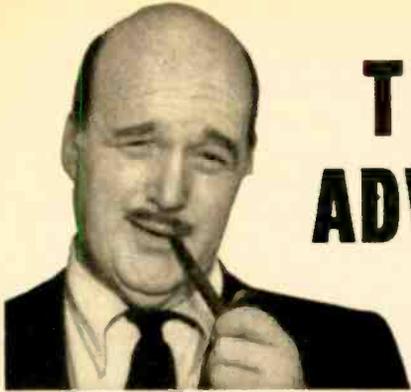

TOM McCAHILL ADVISES SATURDAY MECHANICS

If you're a Saturday mechanic, my guess is you can fix the screen door, build lawn furniture, overhaul the kid's bike, and rotate your own tires.

It's a different story when that fancy electric coffeemaker stops perking or the push-button automatic washer quits halfway through a cycle. You might spend an afternoon admiring the coffee-maker's innards before giving it a permanent vacation on the top kitchen shelf.

As for the automatic washer, after the Little Lady shouts "Do something!" you'll end up phoning an Appliance Serviceman across town. He shows up in 3 days and has the washer going in one-fourth the time it took you to study the coffeemaker. He also presents you with a ticket for 30 bucks. When you consider he could make twice that selling you a new machine, you got off easy.

Maybe you never realized it, friend, but you have more Appliances around your hacienda today than you did five years ago. If you count power tools, your wife's hair dryer, an air conditioner, plus the standard stuff like vacuum cleaner, toaster, refrigerator, freezer and so forth, you probably have well over a dozen.

These electrical gadgets nowadays represent a pretty good chunk of your hard earned dollars. Did you ever stop to think it could pay you in savings and convenience to know how to fix these things? Also, it could be a great source of extra income if you're inclined to tackle the few thousand broken Appliances right in your own neighborhood.

The Appliance Repair business is easier to learn than you imagine. The National Radio Institute's Appliance Division has a downright interesting, low cost course you can take in your spare time. It covers every type of Appliance you can think of plus air conditioning, refrigeration, house wiring, electric motors—even small gas engines. There's a worthwhile section on farm and commercial appliances too.

NRI starts you with the basic principles of electricity to give you a solid background. Using clear-cut picture diagrams, they show you how various types of Appliances work, separating each into groups. Included with the course is a topnotch, professional Appliance Tester for fast troubleshooting.

Easy to read, bite-size lessons are loaded with photos and cutaway drawings so you see how each Appliance comes apart, and more important—goes back together in working order.

Whether or not you agree that knowing Appliance Repair could help you, I recommend you see for yourself. The little coupon below will get you a free book that fully describes this unique home training. It also brings a free sample lesson. No salesman is going to call.

Do yourself a favor and mail the coupon today.

TOM McCAHILL

APPLIANCE DIVISION, NATIONAL RADIO INSTITUTE
3939 Wisconsin Avenue, Washington, D. C. 20016

504-036

OK—I want to see for myself. Send me the free book on Professional Appliance Servicing and a free sample textbook. No salesman.

Name Age

Address

City State Zip Code

Accredited Member National Home Study Council

BIG MONEY

IN THE **4** CORNERS OF THE WORLD!

in TELEVISION, RADIO, ELECTRONICS, RADAR, SONAR

ONLY CHRISTY OFFERS COMPLETE TRAINING!

Investigate the Christy Complete Course. Why be satisfied with less? CTS Shop Method, Home Training makes learning easy. You learn by working with actual equipment. You receive Comprehensive training from the start. Can EARN AS YOU LEARN. You become qualified to open your own Electronics Repair business or to gain high pay as a TV, Radio, Electronics, etc., Technician.

19 TRAINING KITS INCLUDED! You receive a Multi-Tester, Oscillator, Signal Tracer, Oscilloscope, Signal Generator, Electronic Timer, Regenerative Radio, 24" TV set (optional) and other valuable testing equipment. **FREE BOOK** and **TWO FREE LESSONS** yours for the asking! No obligation.

CHRISTY TRADES SCHOOL
Dept. T-3013 3214 W. Lawrence Ave.
Chicago, Illinois 60625



CHRISTY TRADES SCHOOL, Dept. T-3013
3214 W. Lawrence Ave., Chicago, Illinois 60625

Please send me the 3 FREE BOOKS and Special Form for PAYING LATER from EARNINGS MADE WHILE LEARNING.

NAME AGE

ADDRESS

CITY ZONE STATE

Olson

* **FREE**

Fill in coupon for a **FREE** One Year Subscription to **OLSON ELECTRONICS'** Fantastic Value Packed Catalog—Unheard of **LOW, LOW PRICES** on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, and other Values. Credit plan available.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

If you have a friend interested in electronics send his name and address for a **FREE** subscription also.

OLSON ELECTRONICS
INCORPORATED

468 S. Forge Street Akron, Ohio 44308

ELECTRONIC SWAP SHOP

continued from page 14

equipment or SW receiver. Barry Schlosser, 7513 Adventure Ave., Miami Beach, Fla. 33141.

EPSILON Records code course. Will trade for Knight C-100 CB transceiver. Bruce Bennett, 938 Kintyre Way, Sunnyvale, Calif. 94087.

JAPANESE all-band receiver. Will trade for Heath Twoer or other ham or CB gear. Arthur B. Epstein, 3215 Hull Ave., Bronx, N.Y. 10467.

NATIONAL NC-88 receiver, Heath DX-60 transmitter. Want test equipment. William Altenberndt, 258 Harrison St., Chelsea, Mich. 48118.

BC-683 receiver. Need hi-fi tape deck or complete tape recorder. Scott Marovich, 2407 S. Rose St., Kalamazoo, Mich. 49001.

SURPLUS transmitter and WRL TC-6 6-meter transceiver. Want SW receiver. Fred Quandt, 1059 Coronet Dr., Warmminster, Pa. 18974.

HEATH HD-11 Q-multiplier. Will trade for walkie-talkie. Pete Kemp, 25 Prince Pl., Stamford, Conn.

SENTENIAL TV. Want CB walkie-talkies. Lee Freshwater, 2601 Lancaster Dr., Muncie, Ind. 47304.

KNIGHT T-60 transmitter, ARRL books, code course, other items. Will swap for tape recorder or SWL antennas. John Baurhenn, 29-B Robson Pl., Hempstead, N.Y. 11550.

KNIGHT Star Roamer. Will swap for anything of equal value. Greg Virtue, 4580 Fair Oaks Blvd., Sacramento, Calif. 95825.

LAFAYETTE HE-29C walkie-talkie. Want 3- or 4-tube amplifier. T. Cinquini, 6917 Chester Ave., Philadelphia, Pa. 19142.

MAJESTIC AM/FM/SW receiver, tubes, books. Will swap for communications receiver. Dennis Hasler, 1821 N. Routiers, Indianapolis, Ind. 46219.

LIONEL train set with accessories. Want small SW receiver. Stephen Fenn, 441 Chelmsford, Lowell, Mass. 01851.

CDR rotator with control box, Pickett N4-T slide rule. Will exchange for Hallicrafters SX-28, CB rig or what have you. Thomas C. Bennett, Apt. 16, 203 S. Edgefield, Dallas, Tex. 75208.

RECORDING WIRE. Will swap for anything of equal value. Carleton B. Underwood, Mellwood Dr., New Lexington, Ohio 43764.

LAFAYETTE stereo record changer, homebrew AM/FM tuner, 8-watt amplifier, assorted components. Need ham or CB transceiver. John L. Chapin, Jr., 3161 S. Yale St., Wichita, Kan.

COLORORGAN (dancing lights), FM antenna booster, 8-in. hi-fi speaker, other items. Will swap for SW receiver. Rev. Pat Jeffares, Box 38, Campbellville, Ont.

MOBILLETTE 61 converter. Will swap for typewriter or SW receiver. Tommy Baker, Rte. 3, Salem Lane, Gallatin, Tenn. 37066.

HEATH GW-10 CB transceiver, Heath VFO. Want mobile ham antenna or other ham accessories. Bob Battagin, 2541 Hayward Dr., Burlingame, Calif. 94011.

LAFAYETTE Explor-Air receiver, ARC/RU receiver and transmitter, other items. Will exchange for CB walkie-talkie. James Loniak, 31-65 29th St., Astoria, N.Y. 11106.

ELMAC transmitter and receiver, other items. Will swap for anything of equal value. Ronald P. Johnson, Rte. 3, Box 229A, Huntsville, Ala. 35806.

ZENITH Transoceanic, signal generator, Knight C-100 walkie-talkies. Want CB transceiver, SW receiver or tape recorder. Daniel Litteral, Box 17, Eagle Mountain, Calif. 92241.

SHURE telephone transducer. Will swap for 64-in. mike stand. P. J. Yudell II, 425 W. Sierra Madre Blvd., Sierra Madre, Calif. 91024.

RCA Mark II CB transceiver, Wollensak tape recorders. Interested in Collins or Hammarlund communications receiver. Fred Sanborn, Box 667, Eagle River, Wis.

KNIGHT Star Roamer, American Flyer trains. Want Lafayette HE-80. Mark Jenkins, 15103 N.E. 12th St., Bellevue, Wash. 98004.

BC-459. Will swap for Command receiver. M. Sherman, 18891 N.E. 20 Ct., N. Miami Beach, Fla. 33162.

EICO 369 sweep and mark generator, Paco V-70 VTVM. Will exchange for Heath test equipment. William G. Beck, 247 W. Main St., New Holland, Pa. 17557.

Choose Your Tailor-Made Course in N.T.S. "PROJECT METHOD" ELECTRONICS!

Now! N.T.S. — one of America's oldest leading home-study and resident technical schools — offers you GREATER CAREER OPPORTUNITIES IN ELECTRONICS. N.T.S. "Project Method" home training lessons are shop-tested in the Resident School in Los Angeles. The Schools' practical methods, plus more than 60 years of experience, have helped thousands of students all over the world to successful careers. Choose your field and prepare now for a secure future with one of 8 N.T.S. Electronics Courses designed to fit your own particular needs.



SEE OTHER SIDE

1 ELECTRONICS-TV-RADIO-SERVICING & COMMUNICATIONS

A basic course thoroughly covering fundamentals of electronics, radio, TV servicing and communications.

2 MASTER COURSE IN ELECTRONICS-TV-RADIO, PLUS ADVANCED TV & INDUSTRIAL ELECTRONICS

This course covers everything included in Course No. 1 plus Automation and every phase of the Electronics industry.

3 FCC LICENSE

Preparation for this government license essential for interesting jobs in radar, radio, television, communications, guided missiles, many others. Upon completion of this course, if you do not pass the FCC exam for a 1st Class Commercial Radiotelephone License your tuition will be refunded.

4 RADIO SERVICING (AM-FM-Transistors)

Train for radio sales and service with dealer or distributor.

5 TELEVISION SERVICING (Including Color)

Covers installation, adjustment, repair and servicing of black and white and color television . . . prepares you for your own sales and service business.

6 STEREO, HI-FI AND SOUND SYSTEMS

A growing field. Prepares you to build, install and service modern sound equipment for home or industry.

7 BASIC ELECTRONICS

Gives you the fundamentals you must know to build on for a future Electronics career. Also offers an excellent background for Salesmen, Purchasing Agents, and others in Electronics.

8 ELECTRONICS MATH

Simple easy-to-follow instructions in the specialized math you need in many electronics jobs.

HIGH SCHOOL AT HOME

Learn easily. New modern method. National offers accredited high school programs for men and women. Take only subjects you need. Study at your own pace. Latest approved textbooks — yours to keep — everything included at one low tuition. Check High School box in coupon for information.

CLASSROOM TRAINING AT LOS ANGELES

You can take classroom training in our famous Resident School at Los Angeles in Sunny Southern California. N.T.S. is the oldest and largest school of its kind. Associate in Science Degree also offered in our Resident Program. Check Resident School box in coupon for full details.



NATIONAL TECHNICAL SCHOOLS
WORLD-WIDE TRAINING SINCE 1905

Send Postcard for Free Book & Sample Lesson.



CUT OUT & MAIL TODAY. NO POSTAGE NECESSARY.

Please Rush FREE Electronics "Opportunity Book" and sample lesson on course checked below:

- | | |
|---|---|
| <input type="checkbox"/> Electronics-TV-Radio Servicing & Communications | <input type="checkbox"/> Television Servicing (Including Color) |
| <input type="checkbox"/> Master Course in Electronics-TV-Radio Advanced TV & Industrial Electronics | <input type="checkbox"/> Stereo, Hi-Fi and Sound Systems |
| <input type="checkbox"/> FCC License | <input type="checkbox"/> Basic Electronics |
| <input type="checkbox"/> Radio Servicing (AM-FM-Transistors) | <input type="checkbox"/> Electronics Math |
- Dept. 213-26

Name _____ Age _____


Address _____

City _____

State _____ Zip _____

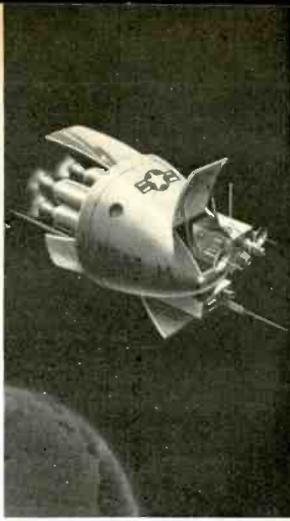- Check here for High School Department Catalog only.
 Check here if interested ONLY in Classroom training at L.A.






You can install and maintain electronic circuitry in missiles and rockets . . . specialize in microwaves, radar, and sonar, or succeed in your own business.

You can succeed in TV-Radio Communications . . . prepare for F.C.C. License, service advanced satellites for industry and defense.

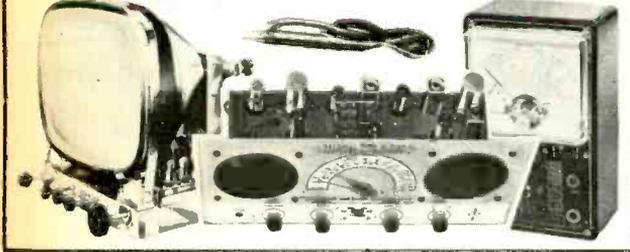Most courses include Equipment Kits. THERE ARE NO KIT DEPOSITS. Everything included in your low tuition.



CLIP & MAIL POSTAGE FREE CARD TODAY FOR FREE BOOK AND SAMPLE LESSON
 in Field of Your Choice. You enroll by mail under N.T.S. "No Obligation" Plan. We have No Salesmen; This means lower tuition for you.

TAKE THE QUICK WAY TO HIGHER PAY, LIFELONG BENEFITS, WITH N.T.S. HOME TRAINING!

N.T.S. "Project Method" Courses can help you get a new and better job — or move up to higher pay in your present one. You work on practical job projects, learn to use shop manuals and schematics. Your N.T.S. training is individual. You proceed at your own pace.

BENEFIT NOW AND ALL YOUR LIFE WITH N.T.S. HOME TRAINING

The personal guidance you receive during your training can be very helpful to your progress. Many N.T.S. students are able to earn more money within a few months. You can pick and choose your career. Work in industry or go into business for yourself. Your services will always be in demand wherever you go — and you can pick your spot!

N.T.S. Graduate Advisory Service can help you answer technical questions in establishing your own business and in countless other ways after you've completed your training.

FIRST CLASS
 Permit No. 3087
 Los Angeles, Calif.

See other side of this card for description of all courses.



Accredited Member
 National Home Study Council



NATIONAL TECHNICAL SCHOOLS
 WORLD WIDE TRAINING SINCE 1905
 4000 So. Figueroa
 Los Angeles, California 90037

BUSINESS REPLY MAIL

No Postage Stamp Necessary If Mailed in the United States

—POSTAGE WILL BE PAID BY—

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

4000 South Figueroa Street
 Los Angeles, California 90037



Hugo Gernsback

Hugo Gernsback Invites You to join his famous Electronics Book Club...

This timely offer comes to you from Hugo Gernsback, the man who coined the word "television", pioneer in radar, space technology and electronics publishing for over 55 years, publisher of Radio-Electronics magazine, founder of the Electronics Book Club.

Build your know-how, boost your income, get more fun out of electronics!

Everyone agrees that KNOW-HOW is the key to getting ahead and staying ahead in electronics. Only the man who keeps pace with fast-changing technology will profit. That's why Hugo Gernsback makes this astonishing offer: See-for-yourself without risk, how the Electronics Book Club keeps you up-to-the-minute on latest developments...increases your know-how and earning power...brings you greater enjoyment if electronics is your hobby!

Learn more, earn more, this practical way!

Every other month the Club's News Bulletin will tell you about a significant new self-teaching book on color TV or radio servicing, test instruments, transistors, hobby projects, stereo, tape recording, industrial electronics, communications, or on some other area of vital interest to you. Each handbook is a working tool designed to help you learn the subject quickly and easily. All are written by experts and illustrated with vivid hands-at-work photos and diagrams. You get clear, practical KNOW-HOW you can put to work at once!

Cash savings to members plus FREE reference service!

As a member, you alone decide whether you want a particular book or not. You get 2 books now for 99¢ and need take only 4 more within a year. And the Club saves you up to 30% off retail prices on the books you take!

What's more, our staff agrees to answer for you personally, any specific electronics questions of your choice. You're entitled to 3 questions for every book purchased — an extraordinary member benefit.

Send No Money Now — Mail Coupon and Enjoy These Advantages at once!

- ★ Get two valuable books immediately for 99¢.
- ★ Free 10-day examination privilege.
- ★ Continuous cash savings to members regardless of higher retail prices.
- ★ Free reference service answers your questions.
- ★ Club books are practical, skill-building tools you can put to work at once!
- ★ Free charts and tables given with many books.
- ★ You alone decide which books you want. Books are always returnable, with no obligation.
- ★ Choose only 4 additional books within a year, from exciting, wide selection to be offered.

Hugo Gernsback, Publisher, Gernsback Library, Inc. Dept. A, 154 West 14th Street, New York, N. Y. 10011.

and get these
2 income-boosting
books for only 99¢

with
membership

Mail Coupon
Now

a \$9.90 value
originally a \$25
home-study course.



Here is a complete self-training course that tells you everything you want to know on HOW TO FIX TRANSISTOR RADIOS AND PRINTED CIRCUITS. Written by servicing expert Leonard C. Lane, it gives you practical guidance you can use at once to spot trouble in the audio section, pinpoint speaker and earphone circuit defects, check distortion in the audio amplifier, locate front-end troubles, eliminate printed-circuit board pitfalls, and work more effectively with signal generator, vtvm, scope and isolation probe. Nothing is left out. Every area is covered, much of it original, unavailable elsewhere in book form. Includes hundreds of illustrations and schematics. So mail coupon now!

Hugo Gernsback, Publisher, Gernsback Library, Inc. Dept. A, 154 West 14th Street, New York, N. Y. 10011.

Enroll me in the Electronics Book Club and send me the TWO-HANDBOOK SET: How To Fix Transistor Radios and Printed Circuits. Bill me only 99¢ plus shipping. If not pleased, I may return both books in 10 days and forget the matter.

As a member, I need accept as few as 4 additional books a year — and may resign any time after purchasing them. All books will be described to me in advance, every other month, in the Club Bulletin, and a convenient form will always be provided for my use if I do not wish to receive a forthcoming book. You will bill me the special Club price for each book I take. This will often be as much as 30% off retail prices, plus a few cents postage.

Name (please print)

Address

City State Zip Code

SAVE POSTAGE COSTS — enclose 99¢ now and we will pay postage. Same return privilege.

YOUR TICKET

... to the very best in hobby electronics is a subscription to EI. If you are a ham, CBER, SWL, audio buff, experimenter or simply have a general interest in electronics, you are sure to find the finest, most up-to-date and the most interesting feature articles and construction projects in EI. To make sure you don't miss a single issue, subscribe now! Fill out the coupon and mail it today!

10 ISSUES

for only

\$2.98

ELECTRONICS ILLUSTRATED
Circulation Department
Fawcett Building
Greenwich, Connecticut 06830

3-66

Here's my ticket. Please cash me in for the next 10 issues of **ELECTRONICS ILLUSTRATED**.

- I enclose \$2.98 Bill me later
 New order Re-order

NAME

ADDRESS

CITY..... STATE..... ZIP.....

BROADSIDES

Pamphlets, booklets, flyers, application notes and bulletins available free or at low cost.

Mobile and base-station **CB antennas and accessories** are illustrated and described in a new brochure from New-Tronics Corp. For your copy of bulletin NT-109, write New-Tronics Corp. 3455 Vega Ave., Cleveland, Ohio 44113.

Canadian electronic hobbyists will be interested in a **24-page catalog** available from an Ontario-based parts distributor. The catalog contains many special introductory offers and all items are shipped postpaid. A copy of Introductory Catalogue No. 1 can be yours by writing Gladstone Electronic Supply Co., 165 Robert St., Toronto 4, Ont.

The more changes a hobbyist makes in a given project, the more the chassis begins to look like aluminum Swiss cheese. But the Seezak people know a way to **breadboard chassis** which requires drilling nary a hole. Their patented 420-line series is designed specifically for breadboarding and a new bulletin explains precisely what the system entails. For your copy, write Seezak Products, Inc., 5057 W. Washington Blvd., Los Angeles, Calif. 90016.

Though **Piezoelectric Technology Data For Designers** may sound like a book for engineers only, the publication can be understood readily by most electronic hobbyists. From the definition of piezoelectricity in the opening to the useful tables, charts and graphs at the close, this 45-page booklet steers the reader toward a comprehensive understanding of crystals and their workings. A copy is free for the asking from Clevite Corp., Piezoelectric Div., 232 Forbes Rd., Bedford, Ohio.


New audio equipment always is of interest to hi-fi buffs who constantly are in search of better sound and better values. Leaflet SAH-96 gives the full rundown on the RM-2—a new low-price **speaker system** by Sonotone. Available free of charge, the publication can be had by writing Sonotone Corp., Electronic Applications Div., Elmsford, N.Y. 10523.

Chances are, you faced a part number rather than a capacitance value last time you replaced a faulty electrolytic capacitor in your TV set, which fact probably forced you to play it leery. Thing is, the **TV Electrolytic Capacitor Replacement Guide** translates these numbers into usable capacitance and voltage ratings and indicates the recommended Aerovox replacements. The booklet is available for 50 cents from Aerovox Corp., 740 Belleville Ave., New Bedford, Mass.

ELECTRONIC MARKETPLACE




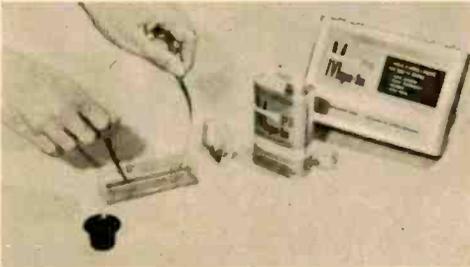INDICATIVE . . . Lacking elaborate instruments, aligning heads on a tape recorder can be a tedious and time-consuming chore. But whether applied to video, instrumentation or



sound recording tape, a substance called Magna-See makes the recorded tracks instantly visible. Result is that head alignment, head wear and track uniformity can be conveniently checked. What's more, tapes can be easily edited with speed and accuracy. \$12. Reeves Soundcraft, Great Pasture Rd., Danbury, Conn.

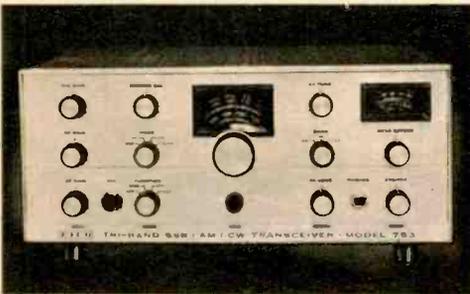
Tri-Banded . . . Available in both kit and factory-wired versions, the three-band 753 ham transceiver sports a 200-watt PEP input on both



SSB and AM as well as a 180-watt CW input on 80, 40 and 20 meters. Thanks to inclusion of an off-set tuning control, the receiver can be tuned over a 10-kc range without disturbing the transmitter frequency. Kit, \$179.95; factory-wired, \$299.95, both less AC power supply/speaker or mobile power supply/speaker (kit, \$79.95; factory-wired, \$109.95). EICO, Inc., 131-01 39th Ave., Flushing, N.Y. 11352.

LEARN

ELECTRONICS

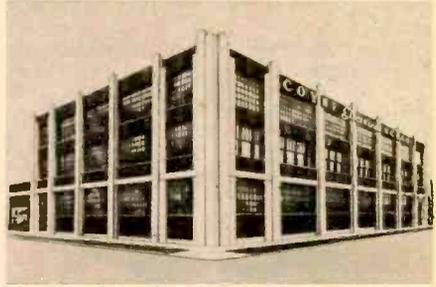

FOUNDED 1899

NOT-FOR-PROFIT

COYNE ELECTRONICS INSTITUTE

Electronics Engineering Technology	—	Degree (2 Yrs.)
Electrical-Electronics Technician	—	Diploma (40 Wks.)
TV-Radio-Electronics Technician	—	Diploma (40 Wks.)
Combined Electronics Technician	—	Diploma (80 Wks.)
Practical Electrical Maintenance	—	Diploma (32 Wks.)
Practical Refrigeration Air Conditioning and Appliance Repair	—	Diploma (24 Wks.)
Specialized Industrial Electronics	—	Diploma (16 Wks.)
Introduction to Electricity-Electronics	—	Certificate (8 Wks.)
FCC First Class Radiotelephone	—	Certificate (100 Hrs.)

Special finance plans. Part time employment service while in school. Also Free graduate employment service.



Use this coupon to get our FREE BOOK "YOUR OPPORTUNITIES IN ELECTRONICS" COYNE ELECTRONICS INSTITUTE, Dept. of Electronics 36-A 1501 W. Congress Parkway, Chicago, Illinois 60607

Name Age

Address Phone


City Zone State

Unlike most other schools, we do not employ salesmen


I only want information on Home Study Courses.

PUT ZIP in your mail

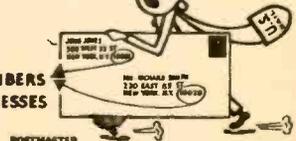Include ZIP CODE NUMBERS IN ALL ADDRESSES



You earn your FCC First Class License

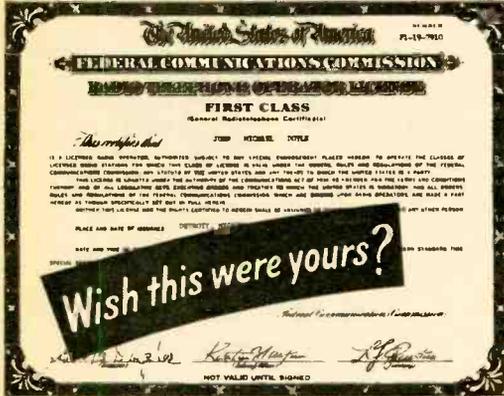

or your money back!

THERE'S A WORLD OF OPPORTUNITY FOR THE MAN WITH AN FCC LICENSE

All it takes is a few spare hours a week and NRI's FCC License Course to open the way to increased opportunities in Communications. With an FCC License, you're ready to operate, service and install transmitting equipment used in aviation, broadcasting, marine, mobile and Citizens-Band communications.

What does it take? Men with absolutely no training or experience in Electronics complete the course in 10 months. A Technician or man with some background can easily cut that time in half. And because NRI has a greater enrollment than any other school of its type, training costs you less than comparable courses offered by other schools. Further, YOU MUST PASS your FCC exams or NRI refunds your tuition in full.

Get full details today about NRI FCC License Course plus 9 other home-study instruction plans offered by NRI, oldest and largest school of its kind. Mail coupon for free catalog. There's no obligation. No salesman will call. NATIONAL RADIO INSTITUTE, Washington, D.C.

MAIL NOW for FREE CATALOG



NATIONAL RADIO INSTITUTE
Electronics Division
Washington, D. C. 20016 20-036

Please send me complete information on FCC License Training and other NRI courses, as checked below. (No salesman will call.)

- | | |
|--|---|
| <input type="checkbox"/> FCC License | <input type="checkbox"/> Radio-TV Servicing |
| <input type="checkbox"/> Complete Communications | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Aviation Communications | <input type="checkbox"/> Electronics for Automation |
| <input type="checkbox"/> Marine Communications | <input type="checkbox"/> Basic Electronics |
| <input type="checkbox"/> Mobile Communications | <input type="checkbox"/> Math for Electronics |

Name _____ Age _____

PLEASE PRINT

Address _____

City _____ State _____ Zip _____

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

MARKETPLACE

Chargeable . . . Though most battery-powered portable tape recorders handle only a given number of tapes before the cells must be replaced, the Charger 760 is equipped to recharge its own.



The 760 will record up to four, hour-long tapes before its nickel-cad battery begins to feel winded. Recharging is an overnight operation. What's more, the 760 can record or play back during the time its battery is undergoing refueling. The book-size, easily totable 5-lb. machine employs a 3 $\frac{3}{4}$ - and 1 $\frac{1}{2}$ -ips capstan drive and can be recharged from any 117-VAC outlet. \$129.95. V-M Corp., Benton Harbor, Mich. 49022.

Color-Coded . . . The KG-625 VTVM likely will interest most any hobbyist, be he novice or



pro. In kit form, the KG-625 provides excellent construction experience for the beginner; factory-wired, it promises to be a welcome addition to the test bench. Multi-range, color-coded scales read AC and DC voltages to 1,500 V, peak-to-peak voltages to 4,200 V and resistance to 1,000 megohms; an optional high-voltage probe boosts the unit's voltage range to 25,000 VDC. \$36.95, kit; \$53.95, factory-wired. Allied Radio Corp., 100 N. Western Ave., Chicago, Ill. 60680.



UNCLE TOM'S CORNER

Uncle Tom answers his most interesting letters in this column. Write him at Electronics Illustrated, 67 West 44th St., New York, N. Y. 10036.

By TOM KNEITEL, K2AES/KBG4303

★ *I do a lot of driving and have considered getting one of those little radar-detector gadgets for my car. What's the story? Do they really work? Thirty dollars is a large investment for a gizmo the size of two packs of smokes.*

*Art Delwynne
Azen, Mo.*

I had one of these things on my car for two years and found that if I went more than a few mph over the limit the detector didn't give me sufficient advance warning of a speed

trap so I could hit the brakes and avoid getting pinched. Your best bet is either to invest in driver-education courses—or do what I did and buy a Jag that can outrun the fuzz.

★ *Like you, I'm a ham radio operator. My problem is my girl friend—she claims that I spend far too much time operating the ham gear. Any advice?*

*B. L. Morrison
Chicago, Ill.*

Explain to her that ham radio is one of the true class hobbies, that the most distinguished and prominent scientists, educators and other citizens choose ham radio to further their intellectual interests. Then whack her good in the slats. She'll get the point.

★ *If I'm not mistaken, didn't you work at a Florida radio station a few years ago? Or was it some other Tom Kneitel?*

*Abner Sherlenn
Kendall, Fla.*

Every now and then my past comes back to haunt me. You're right. That was station WTTT in Coral Gables, a little 250-watter. In 1951-52, while attending the University of Miami, I was a disc jockey and studio engineer. Our antenna tower blew down in a hurricane and we were broadcasting on a long-wire for the last year of the station's life. The studio was five miles from the transmitter on the dead end of the antenna. At night we barely could hear our own signals. If you picked up this bomb in Kendall you must have been a world-champion DXer.

[Continued on page 24]

ABOUT THE AUTHOR

Tom Kneitel has been called an irascible misanthrope, a rabble rouser and the dirty old man of electronics. Whatever he's called, Tom has had a greater influence on hobby electronics in recent years than any other author. As the leading short-wave-listening writer, he once took a major hand in shaping that avocation. He then gave the Citizens Band its name and was instrumental in making it into the world's most dynamic radio service. Tom also has written extensively about ham radio, hi-fi and other areas of electronics. He is noted for his knowledge of his field, his pungent comments and his readiness to state a colorful opinion. He was born in Brooklyn in 1933, started out as a disc jockey, then spent six years with United Artists, selling 16mm films in—of all places—Greenland and Liberia. He is author of four books and scores of articles in a dozen magazines and, along the way, has lived in New York, Florida, California and Oklahoma. Tom now is editor of S9, a special-interest CB magazine, and lives far out on Long Island. His hobbies are fast cars, coins (old or new), hamming and DXing. He drives a Jaguar and leads a bloodhound named Zelda.

FREE GIANT NEW CATALOG



BURSTEIN-APPLEBEE CO.

Dept. E1 1012 McGee, Kansas City, Mo. 64106
 Rush me FREE 1966 B-A Catalog. **SEND FOR IT TODAY**

Name _____

Address _____

City _____ State _____

Please be sure to show your Zip No. _____ **FREE**



LOOK! A NEW ELECTRONICS SLIDE RULE WITH COMPLETE INSTRUCTION COURSE

Professional 10" all-metal Electronics Slide Rule. Designed specifically for technicians, engineers, students, hobbyists. Has special scales not found on any other rule. Enables you to solve electronics problems quickly, accurately. Made to our rigid specs by Pickett, Inc. Slide Rule plus four lesson AUTO-PROGRAMMED Instruction Course with grading service, and top-grain leather carrying case . . . a \$50 value for less than \$20! Send coupon for FREE booklet. Cleveland Institute of Electronics, Dept. EI-109, 1776 E. 17th St., Cleveland, Ohio 44114.

SEND COUPON FOR FREE BOOKLET

Cleveland Institute of Electronics

1776 E. 17th St., Dept. EI-109,
Cleveland, Ohio 44114

Please send FREE Electronics Slide Rule Booklet, SPECIAL BONUS: Mail coupon promptly and get FREE Pocket Electronics Data Guide, too!



GET THIS FREE!

NAME _____ (Please Print)

ADDRESS _____ CITY _____

CITY _____ STATE _____ ZIP _____

A leader in Electronics Training . . . since 1934

Uncle Tom's Corner

Continued from page 23

Ham Beef Dept. Most ham operators, including this one, are bugged by the FCC's proposed new rules which would further force artificial class distinctions upon amateurs. Under the new plan each class of license would have a distinguishing call sign. It's bad enough now with General ops sneering at Technicians and Technicians laughing at Novices. Just think what it's going to be like when the differences are made even clearer. Today ham radio is growing at the slowest rate since the late 1940s. It doesn't need this latest FCC innovation to slow progress even more.

★ *There is a broadcasting station on 1540 kc with a power of 50 kilowatts. They are about five miles from me. Their equipment generates harmonics on 540 and 635 kc. Is there any way I could get rid of the harmonics and also limit the station to about 10 kc (they now occupy most of the frequencies from 1500 to 1580 kc)?*

Kyle Warren
Cooksville, Ont.

Your problem isn't the broadcasting station. It's the dud you are using for a receiver. If you don't want to invest in a new receiver, try disconnecting the antenna from the set you are using. Or take up home movies.

Lost Souls Dept. I don't know the why but short-wave listeners have been the lost souls of electronics for years. They have no licenses and no leadership and they support a dozen or so clubs which (despite a facade of friendliness) hate each other like poison. And the clubs themselves often seem coldly rude to prospective members, businesses and publications—and even to their own members. Worst of all, the SWL has been all but ignored by the electronics industry, which has spent millions to cultivate ham operators and CBers.

Manufacturers of receivers, for instance, produce a variety of general-coverage sets which have a bandspread calibrated for the ham bands. Why don't these manufacturers sell paste-on strips or replacement dial plates calibrated for the short-wave-broadcasting bands? It would be a simple matter to produce this type of accessory, which could be

sold for less than a dollar. Or it could be factory-installed if the set were bought on special order.

That's just one little thing on a long list of injustices being tolerated by SWLs. I can't decide whether SWLs are aware that they are second-class citizens or whether they know it and just don't give a damn.

★ *Can you give me some ideas on obtaining a device which will enable me to see through stone, brick or wooden walls? I know that recent technological developments have placed radar within the budget of home experimenters. How about this?*

Robert Ellis
San Mateo, Calif.

Perhaps you are referring to an amazing invention from Venice. Check your hardware store and ask for window glass.

★ *For years now I've been reading your smart-aleck nonsense in various publications. I think that I know more about electronics than you but I've had dozens of really good manuscripts rejected by leading magazines. If you ask me, something funny is going on somewhere.*


F. B.
Fort Valley, Ga.

Who asked you?

★ *Help! I've been swamped with specifications and statistics on hi-fi gear. Manufacturers must think everyone who buys their equipment is an audio engineer. Where can I obtain a translation of this technical double-talk?*

Vincent Bonelli
Brooklyn, N.Y.

I know purists are going to stick pins in fat little bearded dolls at this answer but, in my opinion, manufacturers go overboard with dazzling arrays of factual but unnecessary statistics on their equipment. I once did an experiment which consisted of interconnecting expensive and moderately priced components and then switching them in and out of a hi-fi system. Most listeners couldn't tell what was playing when! Fact of the matter is that you can't buy hi-fi gear from a poop sheet. The only way to do it is by listening. If an inexpensive component sounds good to you then don't waste your bread on a bushel of statistics and impressive specifications which your ears can't detect.

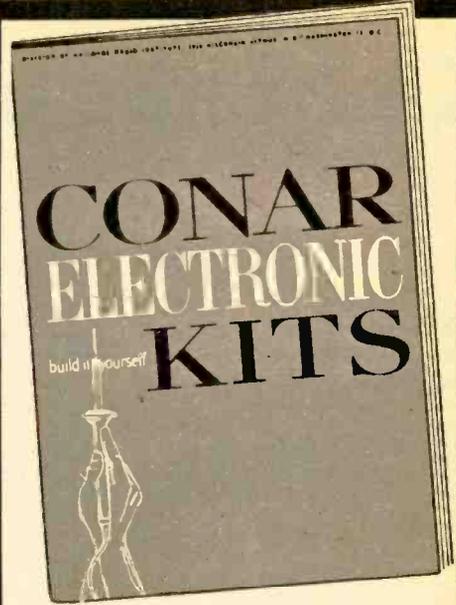

Your copy is waiting
The do-it-yourselfer's
newest catalog

Here's your new catalog of quality electronic kits and assembled equipment . . . your shopping guide for TV set kits, transistor radios, voltmeters, scopes, tube testers, ham gear, PA systems, and a host of other carefully engineered products. Every item in the Conar catalog is backed by a no-loopholes, money-back guarantee. It's not the biggest catalog, but once you shop its pages you'll agree it's among the best. For years of pleasurable performance, for fun and pride in assembly, mail the coupon. Discover why Conar, a division of National Radio Institute, is just about the fastest growing name in the kit and equipment business.

CONAR

MAIL NOW!

CONAR

CE6C

3939 Wisconsin Avenue, Washington, D.C. 20016

Please send me your new catalog.

Name _____

Address _____

City _____ State _____ Z-code _____

Be creative—and thrifty too!

Save up to 50% with EICO Kits and Wired.

EICO supports your sense of achievement with no-compromise engineering, finest parts, dramatic esthetics, simple step-by-step instructions and large pictorial diagrams. You need no technical background—just pliers, screw-driver, soldering iron. Three million

people, ages 8 to 89, have built EICO kits. If you love to create, EICO is for you. And if you want the best buys in ready-to-use factory-assembled equipment, again EICO is for you. Judge critically for yourself. Send for your free catalog. See EICO at your local dealer.

EICO

KITS & WIRED

TEST EQUIPMENT



Model 232 Peak-to-Peak VTVM. A must for color or B&W TV and industrial use. 7-non-skip ranges on all 4 functions. With Uni-Probe. © \$29.95 kit, \$49.95 wired.



Model 460 Wideband Direct-Coupled 5" Oscilloscope. DC-4.5mc for color and B&W TV service and lab use. Push-pull DC vertical amp, bal. or unbal. input. Automatic sync limiter and amp. \$89.95 kit, \$129.50 wired.



Model 324 RF Signal Generator. 150kc to 435mc range. For IF-RF alignment and signal tracing of TV, FM, AM, CB and mobile. Built-in and ext. modulation. \$20.95 kit, \$29.95 wired.

CITIZENS BAND/ HAM RADIO



New Model 779 Sentinel 23 CB Transceiver. 23-channel frequency synthesizer provides crystal-controlled transmit and receive on all 23 channels. No additional crystals to buy ever! Features include dual conversion, illuminated S/R/F meter, adjustable squelch and noise limiter, TVI filter, 117VAC and 12VDC transistorized dual power supply. Also serves as 3.5 watt P.A. system. \$169.95 wired.



New Model 712 Sentinel 12 Dual Conversion 5-watt CB Transceiver. Permits 12-channel crystal-controlled transmit and receive, plus 23-channel tunable receive. Incorporates adjustable squelch & noise limiter, & switches for 3.5 watt P.A. use, spotting, & Part 15 operation. Transistorized 12VDC & 117VAC dual power supply. \$99.95 wired only.



New Model 753 The one and only SSB/AM/CW Tri-Band Transceiver Kit. "The best ham transceiver buy for 1966"—Radio TV Experimenter Magazine. 200 watts PEP on 80, 40 and 20 meters. Receiver offset tuning, built-in VOX, high level dynamic ALC. Unequaled performance, features and appearance. Sationally priced at \$179.95 kit, \$299.95 wired.

STEREO/HI-FI



New Model 3566 All Solid-State Automatic FM MPX Stereo Tuner/Amplifier. "Very satisfactory product, very attractive price"—Audio Magazine. No tubes, not even nuvistors. Delivers 112 watts IHF total to 4 ohms, 75 watts to 8 ohms. Completely pre-wired and pre-aligned RF, IF and MPX circuitry, plus plug-in transistor sockets. \$219.95 kit (optional walnut cabinet \$149.95), \$325.00 wired including walnut cabinet. UL approved.



Model ST70 70-Watt Integrated Stereo Amplifier. Best buy of highest ranked stereo amplifiers according to independent testing. \$99.95 kit, \$149.95 wired. ST40 40-Watt Integrated Stereo Amplifier, \$79.95 kit, \$129.95 wired. ST97 Matching FM MPX Stereo Tuner, \$89.95 kit; \$139.95 wired.

FREE 1966 CATALOG

EICO Electronic Instrument Co., Inc. 81-3
131-01 39th Ave., Flushing, N.Y. 11352

Send me FREE catalog describing the full EICO line of 200 best buys, and name of nearest dealer. I'm interested in:

- test equipment ham radio
 stereo/hi-fi Citizens Band radio

Name _____

Address _____

City _____

State _____ Zip _____

1945-1965: TWENTY YEARS OF LEADERSHIP IN CREATIVE ELECTRONICS

the Mini Mitter



By **RUSS ALEXANDER** IT occupies little more space than a telegraph key, **W6IEL** weighs less than the power transformer it does not have, yet is more powerful than any of the popular lunch-box rigs—that's our Mini-Mitter, a neat 28½-ounce package that can put a clean 15-watt (input power) signal on the 40-meter band.

Secret of the Mini-Mitter's small size, of course, is the missing power transformer. In its absence, power is provided by a solid-state voltage doubler. The two tubes aren't visible because they're mounted on the outside of the back panel to keep everything cool. And because the two tubes have 50-V heaters they are connected in series with a power resistor across the line. This means no filament transformer, either.

The first day we put the Mini-Mitter on the air in California we contacted not only the East Coast but UAØER in *Russia* as well (see log excerpt)!

Unless otherwise indicated in column 6, type of emission is A2, freq. is 7 Mc., input power is 15 watts.
(MINI MITTER)

1. DATE YR.	2. TIME OF QSO START	3. STATION CALLED	4. CALLED BY	5. HIS. SIG. RST	6. OTHER INFORMATION AND CHANGES
3/22	5:30	UAØER	7004	MY R.S.T. *	HANDLE QTH "ED" SAKMALIN ISLES, RUSSIA
3/22	2:29p	40/A1 Q7030	W4Y"1R	56-956-9	"PAV" - AELCROSS, N.C.

Fig. 1—Portion of the author's log shows a contact made with UAØER in Russia with the Mini-Mitter on 40 meters. Input of 15 watts goes to show you that power isn't everything.

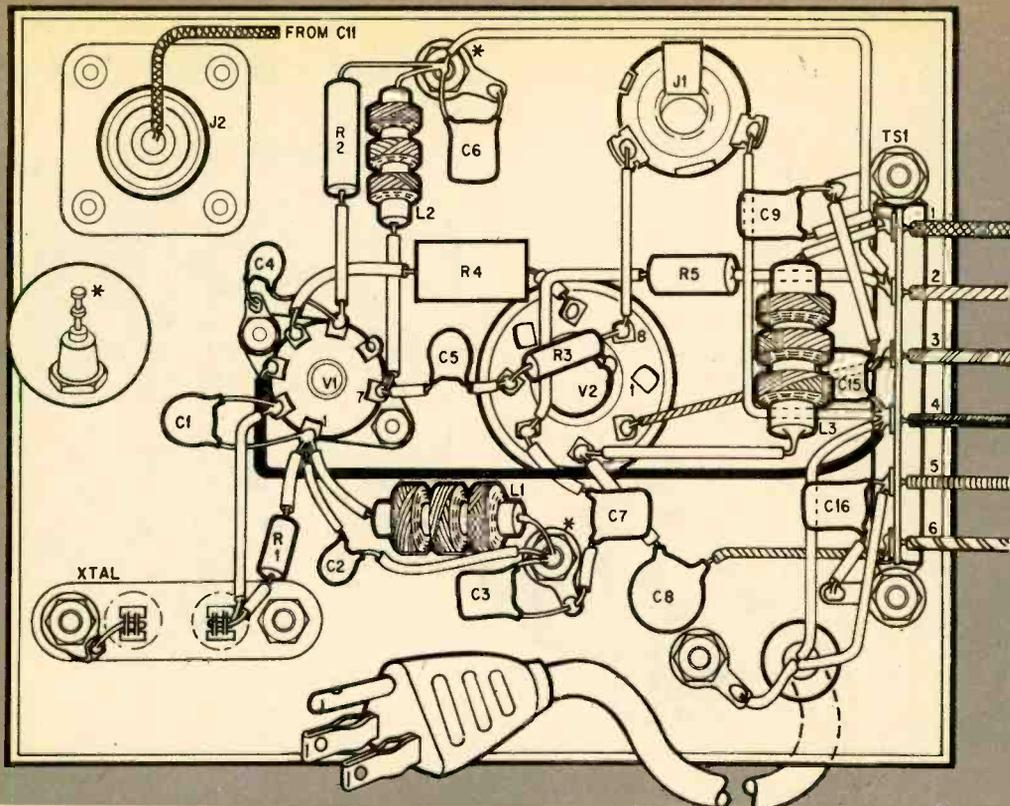


Fig. 2—Rear (above) and front (right) panels. Standoff terminals (circle at extreme left) that hold R9 are sol-

Mini-Mitter


Later we worked Japan, Alaska and many points in the U.S.A.


When our main rig failed, Mini-Mitter kept up our MARS schedules and maintained other schedules up and down the Pacific Coast. Because of its vest-pocket size, Mini-Mitter has been carried along on several field

trips without difficulty. It and a Drake 2-B receiver were powered by a 12 VDC-to-117 VAC converter in the car. On several radio picnics we used all sorts of antennas hung from trees, kites and balloons.

The Mini-Mitter circuit is pretty straightforward but includes several unusual features. As we said, instead of the usual heavy power transformer, there is a solid-state voltage doubler for the plate supply. A neon lamp is used as an RF-resonance indicator.

Fig. 3—Photo of completed panels ready to be installed in cabinet. Only lead from C11 on right panel remains to be connected to J2 in upper corner of left panel. Watch for loose strands on interconnecting wires at terminal strips. These strips are close to panel edges. Mount all of the components near panels.

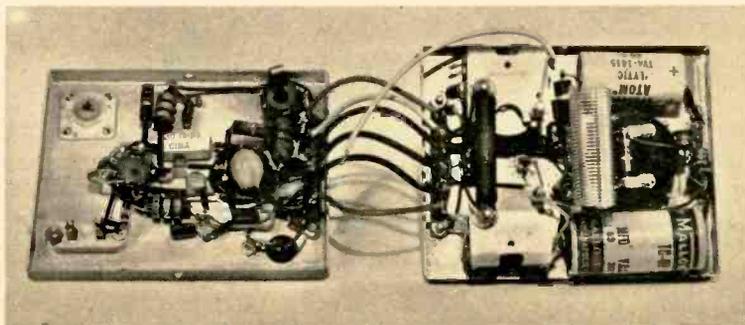

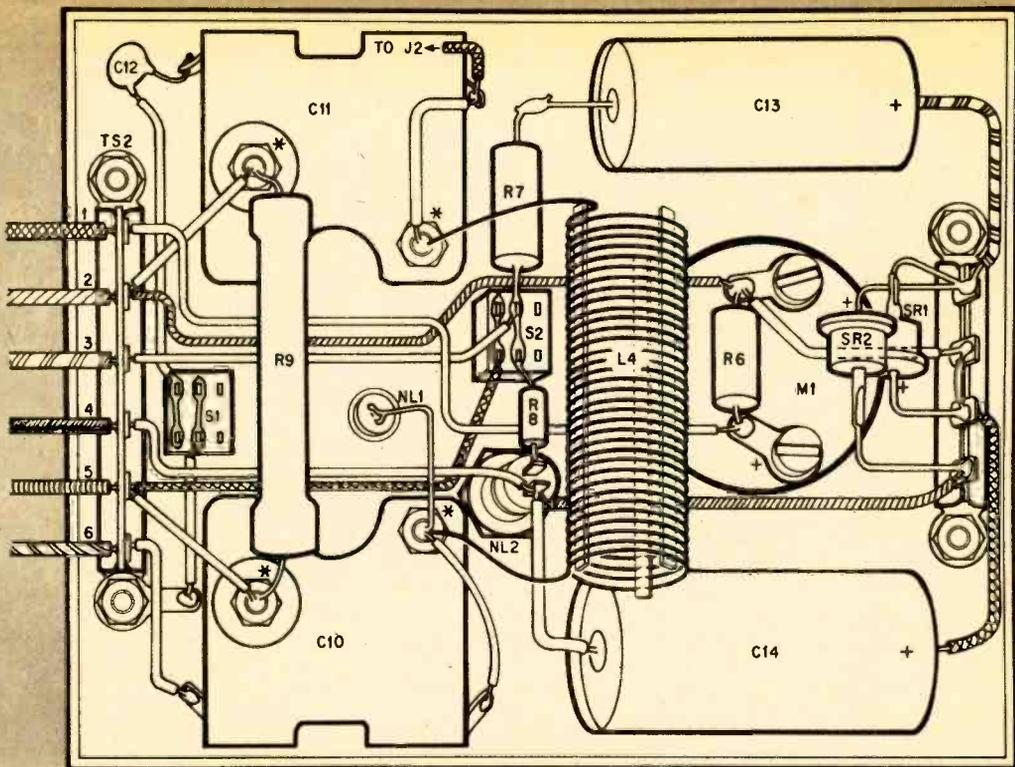

dered to C10, C11. Mount others with screws, seeing that screw heads on L4's don't touch plates of C10, C11.

The rapid response of the lamp to RF voltage provides visual monitoring while you send and is of great help when tuning.

The final has pi-net tuning and there's a switch to add or remove capacity for matching to different impedance antennas. The power supply delivers about 310 V when the key is down. All of this goes to putting out a mighty easy-to-copy signal.

Mechanically, the Mini-Mitter has several features which simplify its construction.

Refer to the pictorial in Fig. 2. Note that the front and back panels are separate parts that are joined electrically by flexible leads. This makes it possible to mark and drill the panels and then mount and wire the components on a flat surface. Layout and handling are thus simplified.

Construction

The first step is to remove the front and back panels from the 3 x 4 x 5-in. case. Holes

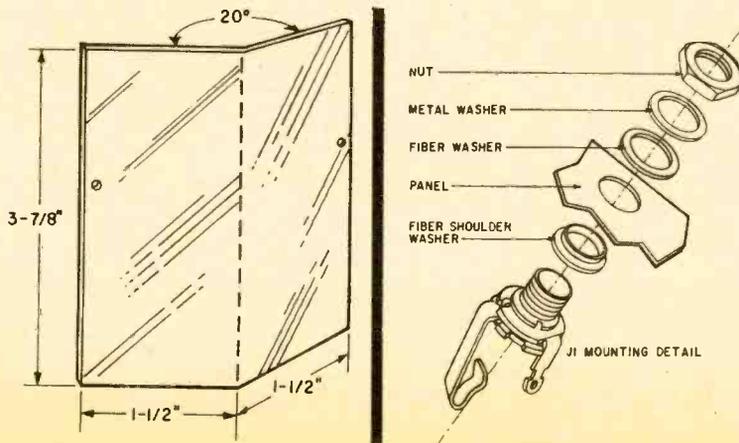


Fig. 4—Sketch at far left is of supporting plate (of 1/16-in. scrap aluminum) that should be used to support and electrically connect front and rear panels so transmitter can be operated out of cabinet. Plate is shown in use in Fig. 6. Sketch at left shows method of mounting key jack J1 so it is insulated electrically from cabinet.

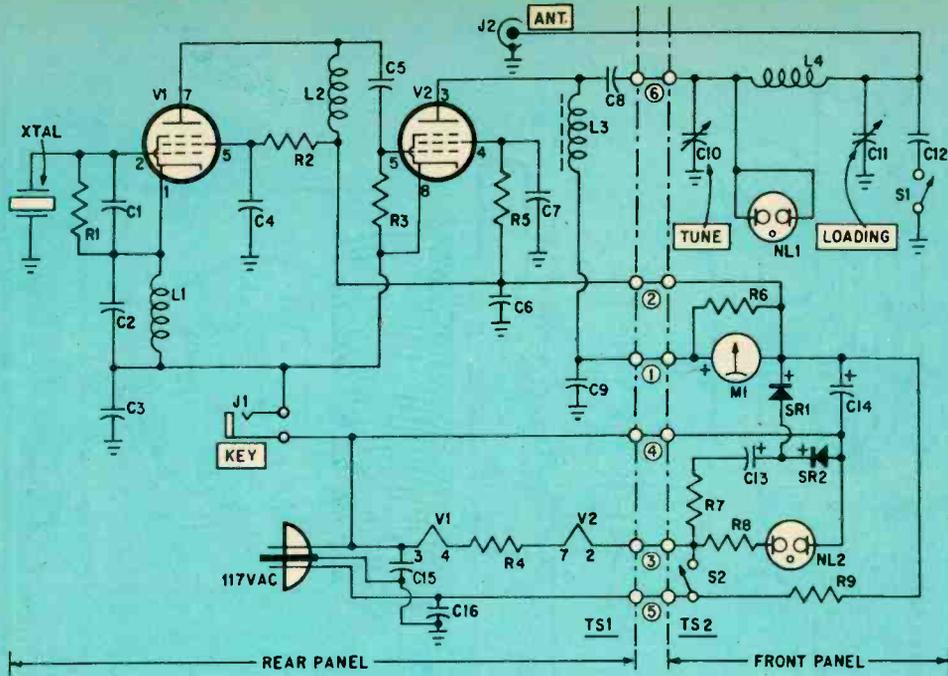


Fig. 5—Schematic of Mini-Mitter. Since J1 is connected directly to one side of line, it must be insulated from cabinet. Make sure the AC plug is wired so that one side of the key will not be hot.

Mini-Mitter

for mounting the components should be drilled next. As an aid to laying out the panels, rubber-cement brown wrapping paper on them. After marking and drilling is completed the paper can be pulled off easily and the rubber cement can be rolled off. This technique prevents the panels from being scratched and permits laying out all holes with easy-to-see pencil markings.

Next, install 6-lug terminal strips (TS1, TS2) on the bottom of each panel. The lugs are the component and wiring terminations (shown as circles on the schematic) and are used to join circuits on front and back panels.

The power-supply filter capacitors (C13 and C14) are mounted by cementing their cardboard jackets directly to the front panel. Cambion (Cambridge Thermionic Corp.) standoff terminals rather than ordinary terminal strips are used to support several components. These lugs are excellent space savers for miniature equipment. One is shown in detail in the circle at the extreme left of the

PARTS LIST

- Capacitors: ceramic disc unless otherwise indicated
 C1—30 μf , 1,000 V, C2—220 μf , 1,000 V
 C3, C6, C9, C15, C16—.02 μf , 500 V
 C4, C5—.001 μf , 500 V, C7, C8—.01 μf , 500 V
 C10, C11—10-365 μf variable capacitor (J. W. Miller No. 2111. Newark Electronics 40F190. \$2.10 plus postage)
 C12—390 μf , 1,000-V
 C13—60 μf , 150 V electrolytic
 C14—60 μf , 350 V electrolytic
 J1—Open-circuit phone jack
 J2—Coax connector, SO-239
 L1—620 mhy RF choke (J. W. Miller No. 4650)
 L2—.15 mh RF choke (J. W. Miller No. 4644)
 L3—2.5 mh RF choke (J. W. Miller No. 6302)
 L4—Barker and Williamson Miniductor No. 3007. 2-in. long, $\frac{1}{2}$ -in. dia., 16 turns per in. (Lafayette 40 R 1616 or equiv.)
 M1—0-100 ma DC milliammeter (Lafayette 99 R 5055 or equiv.)
 NL1, NL2—NE-2 neon lamp
 Resistors: $\frac{1}{2}$ watt, 10% unless otherwise indicated
 R1—47,000 ohms, R2—8,200 ohms, 1 watt
 R3—27,000 ohms, R4—130 ohms, 5 watts
 R5—6,200 ohms, 1 watt, R6, R7—10 ohms, 1 watt
 R8—100,000 ohms, R9—40,000 ohms, 10 watts
 S1, S2—Miniature DPDT toggle switch (Lafayette 99 R 6162 or equiv.)
 SR1, SR2—Silicon rectifier, minimum ratings: 750 ma., 600 PIV
 TS1, TS2—6-lug terminal strip
 V1—50HC6 tube, V2—50L6GT tube
 XTAL—40-meter crystal and socket
 Misc.—Solder terminals (6 reqd. Cambion No. 1947-2. Newark Electronics 40F1842). 7-pin tube socket, octal tube socket, 3 x 4 x 5-in. utility box (LMB No. U-C 971, Newark Electronics 91F1025), 4-lug terminal strip

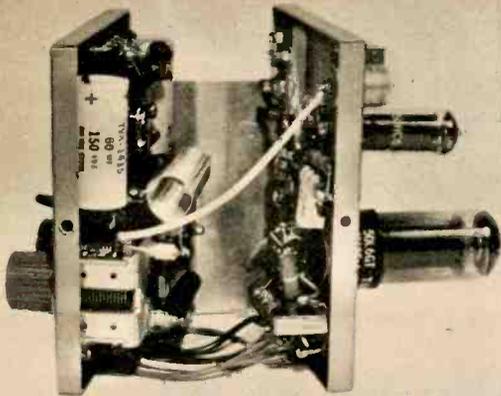


Fig. 6—Photo shows how mounting plate shown in Fig. 4 supports front and rear panels to permit transmitter to be operated out of the cabinet.



Fig. 7—Rear view of Mini-Mitter. If you feel uneasy about building the transmitter in such a small box the answer is obvious. Get a larger cabinet!

pictorial in Fig. 2. Their locations are indicated by asterisks.

Tank coil L4 and bleeder resistor R9 are mounted on two terminals which are soldered to the frames of variable capacitors C10 and C11. Key jack J1 *must* be insulated electrically from the panel with fiber shoulder washers as shown in Fig. 4. To be sure the jack is insulated from the cabinet, check it with an ohmmeter.

Since one side of the line is connected to the key (and J1) be sure you wire the power cord correctly or there will be a dangerous shock hazard. After the unit is wired, connect the front and back panels with the plate shown in Fig. 4. Turn on power and measure the voltage between jack J1 and either panel. If you measure line voltage, interchange the line cord's leads to lugs 4 and 5 on TS1.

Both leads of neon lamp NL1 are soldered together and connected by a single wire to the ungrounded side of *tuning* capacitor C10 at a standoff terminal. The bulb should protrude slightly through a 1/4-in.-dia. hole in the front panel. The lamp's internal elements are coupled capacitively to the panel and RF energy through this capacitance lights the lamp.

After wiring both front and back panels connect the two with flexible insulated leads between the indicated lugs on TS1 and TS2.

Tune Up

The Mini-Mitter is now ready for testing with a 15-watt, 117-V lamp. After inserting the tubes, plug in a 40-meter crystal and the key. Turn on your receiver and tune it to the crystal's frequency. Turn on the receiver's BFO. Turn on the Mini-Mitter's power and note if NL2 and the tubes light up.

After a warmup of about one minute, press the key. If the Mini-Mitter is wired correctly you'll hear its signal on your receiver. Close S1 and adjust C10 (*tune*) to obtain the brightest glow from NL1 and the lowest plate current, as indicated on M1. (From the full counterclockwise position, we used the first dip.) The 15-watt lamp should glow, indicating RF output.

To load the transmitter, gradually decrease the capacity of C11 (open its plate), simultaneously dipping plate current by adjusting C10. At maximum loading the meter should indicate about 80 ma and the neon and 15-watt lamps will glow brilliantly.

The Mini-Mitter is now ready to go on the air. Connect it with RG59/U coax to a dipole or vertical 40-meter antenna and tune it again, using an SWR or field-strength meter, if available. Capacitor C12 may be cut in or out of the circuit, as needed, for different antennas.



Stereo Tape Deck

Knight-Kit KG-415

A DECISION by Allied Radio's Knight-Kit division to put out a stereo tape deck in kit form means the market now is being shared by two companies and that, in any area of electronics, is the rare and absolute low number of competitors possible. More people are fighting over the first ticket to the moon.

Tape decks and tape recorders never have been big sellers as kits. The reason probably has to do with the fact that performance depends so much on mechanical components—the tape transport—which can't be assembled easily by a hobbyist. It's an expensive, exacting job done best by a factory. Thus, manufacturers have little room to maneuver between offering the electronics of a machine in loose-leaf form or wired. And it used to be difficult to create a significant kit/wired price differential. The Knight is a departure from this state of affairs.

The machine, called the Superba KG-415, is a solid-state stereo deck with a pre-assembled transport supplied by Viking, a recognized quality name in the field. The builder's job mainly is one of putting together preamplifiers for recording, playing back and monitoring and other circuitry for switching.

When the job is complete the builder has a deck of unquestioned high quality with all the functions and conveniences of a professional model. A comparable factory-wired deck would cost upwards of \$400.

The KG-415 has a basic price of \$249.95. To that can be added \$19.95 for a walnut


base (\$29.95 for a portable carrying case), \$10.85 each for a pair of matched dynamic microphones and as much as \$8.10 for express charges from Chicago (the \$8.10 is for shipment to San Francisco). The total goes to roughly \$300, representing a substantial savings over a comparably equipped assembled model.

Clearly, for a person in the market for a quality tape deck—and who has had some little experience in kit-building—the KG-415 makes good monetary sense. And that's something that could not be said of most electronic kits—the money-saving possibilities usually are of minor importance.

The KG-415 is a two-speed ($3\frac{3}{4}$ and $7\frac{1}{2}$ inches per second) deck with three heads that is suitable for stereo or mono recording and playing back (one head gives you the valuable ability to monitor the tape just after it has been recorded).

Knight's offering comes off as a machine that once might have been called a *tape recorder*. But tape terminology is getting sticky. A *tape deck*, such as this one, has no speakers. Its preamplifier outputs must be fed into an amplifier to drive one or more speakers. The mechanical part that transports the tape we once called a *tape deck*. Now it is the *tape transport*. A *tape recorder*, on the other hand, is anything with a built-in speaker. But we are going astray.

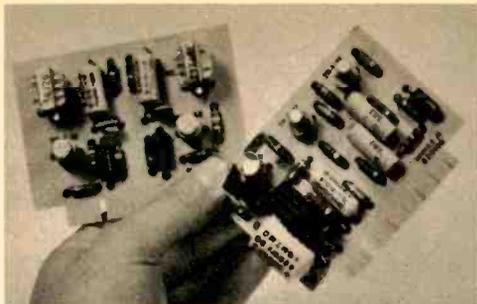Assembling the KG-415 is a relatively straightforward procedure with both easy and difficult spots. Most operating compo-




MAJORITY of KG-415 components are mounted on six printed-circuit modules similar to these two.

nents are mounted on six printed-circuit modules (two record amplifiers, two playback amps, a bias-erase module and a monitor amp), which are easy to assemble. Much of the underchassis work consists of interconnecting leads and, though Knight has done an excellent job of figuring out routing and of locating cable clamps, wiring is intricate and much patience is required. It is for this reason that we say the prospective builder should have a kit or two under his belt before tackling the KG-415. Neophytes often lack the patience and willingness to follow instructions exactly as required here.

The instruction manual is well-done, being logical and easy to follow. Our builder had only one fuss: on page 6, step 13, two sheet-

RIGHT—Chassis is wired and modules are in place at bottom of photo; reverse side of transport is above. Note flywheel at top, fan on the motor. Connecting cables come down at left and right.

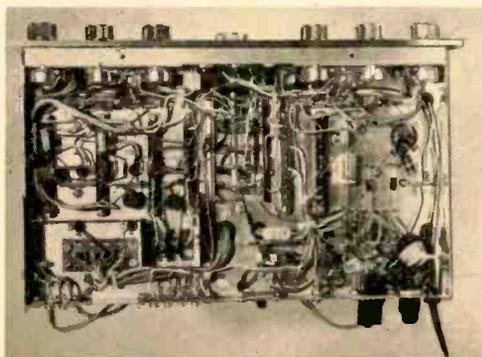BELOW—View of underside of chassis indicates the complexity of the wiring. Our builder found the wiring tedious but instructions were excellent. Front-panel control knobs are at top of photo.




metal screws are threaded into the chassis after mounting other hardware and it is difficult to start them without a screw-holding screwdriver, which should be specified. He also ran short of 4-40 x 1/2-in. machine screws but his kit probably was atypical because such hardware is packaged by weight and most Knight kits include an excess.

Our man got the KG-415 together in 30 hours, 5 minutes. He is an average builder, having put together half a dozen kits, but he is slower and more methodical than average. Even so, he made an error in the underchassis part of the monitor circuit and this required considerable troubleshooting. Oscillation also developed at one point but this was cured easily by moving some of the underchassis leads. Knight's instruction to route all leads directly and keep them close to the chassis must be taken extremely seriously. Failure to keep them close or to route as instructed can produce a multitude of problems.

After the machine was finished and inter-connected with the tape transport our builder tried to slip it into the walnut base—and failed miserably. The manual does not include an in-it-goes instruction, none is packaged with the base and how the two go together is not that obvious. In future production such instructions no doubt will be included somewhere.

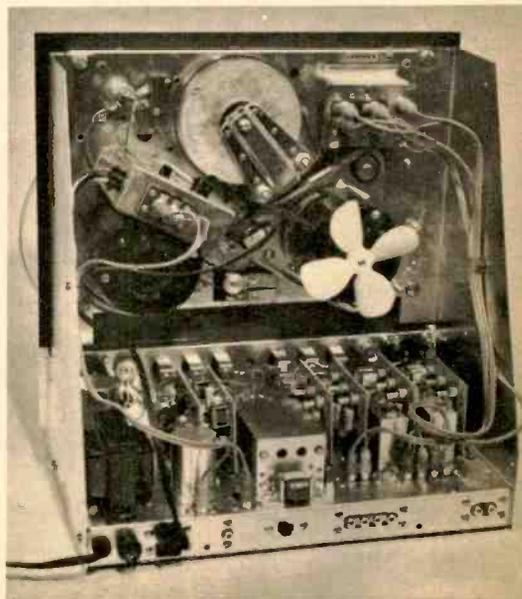We were impressed by several features of
[Continued on page 95]





HIGH SEAS . . .
Weaknesses in the country system of gauging DX prowess are advanced from time to time and we often have said the number of countries logged and

verified was not necessarily the best measure of a DXer (e.g., THE LISTENER, July '65 EI). Currently, a small group of expert DXers is suggesting that cities logged and verified be used as another criterion, an idea obviously not without merit.

But the biggest weakness of the country system has yet to be mentioned. Two thirds of the earth's surface—the water—usually counts for nothing at all. (EI'S DX Club, however, does count International Waters as the equivalent of one country.) Considering the territory involved, this hardly seems fair, especially for utility DXers.

Thing is, if stations on the high seas are to be divided up, exactly how do you go about it? Would the Caribbean be counted as separate from the Atlantic? Would the Gulf of Mexico be credited separately from the Caribbean? And, if so, where exactly would you draw dividing lines?

Without going into these controversies, there would be six divisions no one could quarrel with—well, almost no one, anyway. These are the Atlantic, Pacific and Indian Oceans plus the Mediterranean, Black and Arctic Seas. Paradoxically, easiest way to log any of these isn't via stations aboard ships (with one possible exception). Aircraft passing over these waters afford ample signal sources, assuming you are aware of the various AERO frequencies. (Our map shows

some of the better frequencies for the six divisions mentioned above.)

If you find this new approach to DX gauging worthwhile, let us know. And if enough interest is shown, we'll tackle those controversial areas like the Caribbean and perhaps change the Official Countries List for EI's DX Club.


SW Receiver. A new product recently put on the market by Hallicrafters seems aimed specifically at the DXer. Selling for around \$60, the S-200 is the first U.S.-built receiver in recent years to cover *only* the short-wave broadcast bands—49, 31, 25 and 19 meters—plus the medium-wave BCB. Further (and this is the big thing), a separate 8-in. scale is provided for each band.

This is not to imply that the S-200 doesn't have disadvantages. In addition to virtually no utility coverage (there is a little at each band's edge), there is no RF amplification (so expect images) and only one IF stage. There also is no coverage of tropical bands and, of course, the country names appearing at various points on the dial can be put down as plain decoration. But the fact remains that there is nowhere else, for that price, that the beginner can get such fine tuning and calibration.

Pink-Slip Caper. No one is much surprised that many SWLs are sadly lacking in general reporting know-how. But we recently ran across one DXer who sent out so-called pink slips to stations who did not answer his reports promptly, an approach we think unlikely to win stations or influence chief engineers. (By way of explanation, *pink slip* is another name for an official FCC violation notice—

[Continued on page 103]

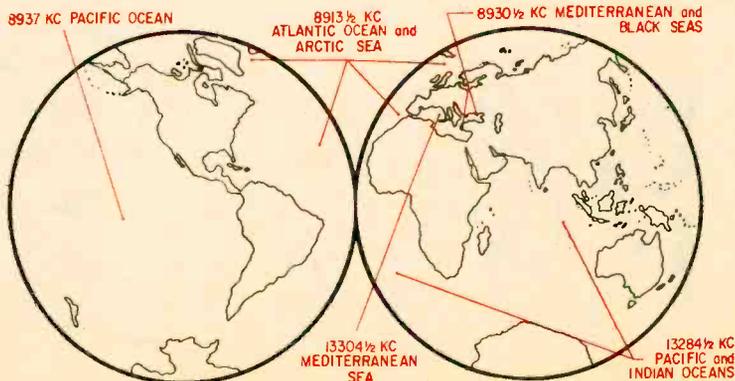Water accounts for the better part of the earth's surface, yet the entire area usually counts as one country—if that—for DX purposes. And though aircraft flying over oceans and seas provide a convenient means of logging these areas on frequencies indicated, problem is how adequately and correctly to delineate such regions.



Cast your ballot for a successful future!

253 I.C.S. COURSES



I.C.S. is the oldest, largest correspondence school. Over 200 courses. Business, industrial, engineering, academic, high school. One for you. Direct, job-related. Bedrock facts and theory plus

practical application. Complete lesson and answer service. No skimping. Diploma to graduates.

Send for the 3 free booklets offered here and find out how I.C.S. can be your road to success.

ACCOUNTING

Accounting for Business
Programmers
Cost Accounting
C.P.A. Review
Estate & Trust Accounting
Executive Accounting
Federal Tax
General Accounting
Industrial Accounting
Legal Accounting
Office Accounting
Personal Income Tax & Social Security
Practical Accounting
Public Accounting
Small Business Accounting
Starting & Managing a Small Bookkeeping Service

ARCHITECTURE AND BUILDING

Architectural Drawing & Designing
Architects
Building Contractor
Building Estimator
Building Inspector
Building Maintenance
Carpenter-Builders
Carpentry & Millwork
House Planning & Interior Design
Mason
Painting Contractor
Reading Arch. Blueprints
Review in Arch. Design & Practice
Review of Mech. Systems in Buildings

ART

Amateur Artist
Commercial Art
Commercial Cartooning
Illustrating
Interior Decorating
Oil Painting for Pleasure
Show Card & Sign Prod.
Show Card Writing
Sign Painting & Designing
Sketching & Painting

AUTOMOTIVE

Automatic Transmission Specialist
Automobile Body Rebuilding & Refinishing
Automobile Electrical Tech.
Automobile Engine Tune-Up
Automobile Technician
Automotive Mechanic

Diesel-Gas Motor Vehicle Engines

BUSINESS

Advertising
Basic Inventory Control
Business Administration
Business Management & Marketing
Business Management & Production
COBOL Programming
Condensed Business Practice
Industrial Psychology
Managing a Small Store
Marketing
Modern Executive Management
Office Management
Programming for Digital Computers
Programming the IBM 1401 Computer
Purchasing Agent
Retail Business Management
Statistics and Finance
Systems and Procedures Analysis

CHEMICAL

Analytical Chemistry
Chemical Engineering
Chemical Engineering Unit Operations
Chemical Laboratory Tech.
Chemical Process Control Technician
Chemical Process Operator
Elements of Nuclear Energy
General Chemistry
Instrumental Laboratory Analysis

CIVIL ENGINEERING

Civil Engineering
Construction Engineering
Highway Engineering
Principles of Surveying
Reading Highway Blueprints
Reading Structural Blueprints
Sanitary Engineering
Sewage Plant Operator
Structural Engineering
Surveying and Mapping
Water Works Operator

DRAFTING

Aircraft Drafting
Architectural Drafting
Electrical Drafting

Electrical Engineering

Drafting
Electronic Drafting
Introductory Mechanical Drafting
Mechanical Drafting
Pressure-Vessel and Tank Print Reading
Sheet Metal Layout for Air Conditioning
Structural Drafting

ELECTRICAL

Electric Motor Repairman
Electrical Appliance Servicing
Electrical Contractor
Electrical Engineering (Power option or Electronic option)
Electrical Engineering Tech.
Electrical Instrument Tech.
Industrial Electrical Tech.
Industrial Telemetering
Power Line Design and Construction
Power Plant Operator (Hydro or Steam Option)

ENGINEERING (Professional)

Chemical Civil
Electrical Mechanical
Industrial Management for Engineers

ENGLISH AND WRITING

Better Business Writing
Introductory Technical Writing
Modern Letter Writing
Practical English
Short Story Writing

HIGH SCHOOL

High School Business
High School College Prep. (Arts)
High School College Prep. (Engineering & Science)
High School General
High School Mathematics
High School Secretarial
High School Vocational

LANGUAGES

(Edited by Berlitz)
French
German

Italian Spanish

LEADERSHIP

Basic Supervision
Industrial Foremanship
Industrial Supervision
Personality Development
Personnel-Labor Relations Supervision

MATHEMATICS

Advanced Mathematics
Mathematics and Mechanics for Engineering
Mathematics and Physics for Engineering
Mathematics & Physics for Technicians
Modern Elementary Statistics

MECHANICAL

Industrial Engineering
Industrial Instrumentation
Machine Design
Mechanical Engineering
Quality Control
Safety Engineering Tech.
Tool Design
Value Analysis

PETROLEUM

Natural Gas Production & Transmission
Oil Field Technology
Petroleum Production
Petroleum Production Engineering
Petroleum Refinery Oper.
Pipeline Engineering

PLASTICS

Plastics Technician

PLUMBING, HEATING, AIR CONDITIONING

Air Conditioning
Air Conditioning Maint.
Domestic Heating with Oil & Gas
Domestic Refrigeration Gas Fitting
Heating
Heating & Air Conditioning with Drawing
Plumbing
Plumbing & Heating
Plumbing & Heating Contractor
Plumbing & Heating Estimator
Practical Plumbing
Refrigeration

Refrigeration & Air Conditioning

Steam Fitting

PULP AND PAPER

Paper Machine Operator
Paper Making
Pulp Making
Pulp & Paper Engineering
Pulp & Paper Making

SALESMANSHIP

Creative Salesmanship
Real Estate Salesmanship
Sales Management
Salesmanship & Sales Management

SECRETARIAL

Clerk-Typist
Commercial
Legal Secretary
Medical Secretary
Professional Secretary
Shorthand
Stenographic
Typewriting

SHOP PRACTICE

Dijl Operator
Foundry Practice
Industrial Metallurgy
Lathe Operator
Machine Shop Inspection
Machine Shop Practice & Toolmaking
Metallurgical Engineering Technology
Milling Machine Operator
Patternmaking
Practical Millwrighting
Reading Shop Prints
Rigging
Tool Engineering Techn'y
Tool Grinder
Toolmaking
Turret Lathe Operator
Welding Engineering Tech.
Welding Processes

STEAM AND DIESEL POWER

Boiler Inspector
Industrial Building Engineer
Power Plant Engineering
Stationary Diesel Engines
Stationary Fireman
Stationary Steam Eng.

TEXTILES

Carding
Carding and Spinning

Cotton Manufacturing

Dyeing & Finishing
Loom Fixing
Spinning
Textile Designing
Textile Technology
Textile Mill Supervisor
Warping and Weaving
Wool Manufacturing

TRAFFIC

Motor Traffic Management
Railway Rate Clerk
Traffic Management

TV-RADIO-ELECTRONICS

Communications Techn'gy
Electronic Fundamentals
Electronic Fundamentals (Programed)
Electronic Fundamentals with Electr. Equip. Trn'g
Electronic Instrumentation & Servo Fundamentals
Electronic Principles for Automation
Electronics and Applied Calculus
Electronic Technician
First Class Radiotelephone License
Fundamentals of Electronic Computers
General Electronics
General Electronics with Electronic Equip. Trn'g
Hi-Fi Stereo and Sound Systems Servicing
Industrial Electronics
Industrial Electronics Engineering
Industrial Electronics Engineering Technician
Practical Radio-TV Eng'g's
Practical Telephony
Principles of Radio-Electronic Telemetry
Principles of Semiconductor Transistor Circuits
Radio Servicing with Radio Equipment Training
Radio & TV Servicing
Radio & TV Servicing with Radio Equip. Trn'g
Second Class Radiotelephone License
Sound Systems Specialist
Telephony, Electronics and Radio Communications
TV Receiver Servicing
TV Technician

Clip coupon — and take your first big step to real success! I.C.S., Scranton, Penna. 18515

Accredited Member, National Home Study Council

INTERNATIONAL CORRESPONDENCE SCHOOLS I.C.S. 75th YEAR

Dept. 1424, Scranton, Penna. 18515

(In Hawaii: P.O. Box 418, Honolulu, In Canada: I.C.S. Canadian, Ltd.)

Without cost or obligation, rush me "HOW to SUCCEED," the opportunity booklet about the field I have indicated below, and a sample lesson. New! Special Package for Women!

Name of the course in which you are interested _____

Mr. _____

Miss _____

Mrs. _____

City _____

Age _____

Address _____

State _____

Zip Code _____

Working Hours _____

A.M. to _____

P.M.

Occupation _____

Employed by _____

Low rates to members of U. S. Armed Forces!
Special training programs for industry




GOOD READING

By Tim Cartwright

ELECTRONIC COMPONENTS HOBBY MANUAL. Edited by R. G. Kempton. General Electric, Owensboro, Ky. 199 pages. \$1.50

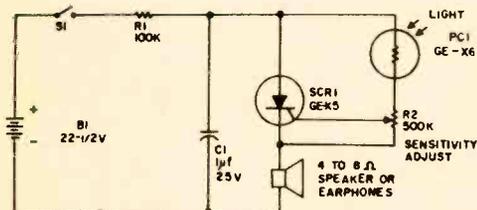General Electric usually is right on target when it aims a book of electronics projects at the hobbyist, and this one is no exception. Well thought-out and well presented (with lots of ultra-clear photos and diagrams), this volume—a second edition—should be a pleasure for anyone to work from.



Taken from the Hobby Manual discussed above, this diagram shows a simple circuit for what GE calls a light-sensitive electronics watch dog.

The projects range in meatiness from a simple warning chime intended to keep you from leaving your car with its headlights on to a dual-voltage power supply that can handle a typical 100-watt ham transmitter. The theory in the book's opening section is presented with just the right tone for a text aimed at hobbyists, and the entire presentation is in marked contrast to other, hastily-thrown-together hobby books. A very nice job, highly recommended.

BASIC ELECTRONICS. Produced by RCA Institutes. Edited by Jack W. Friedman, Harry G. Rice and Gerald McGinty. Prentice-Hall, Englewood Cliffs, N.J. 534 pages. \$12.95

A programmed text for self-instruction, this volume perhaps is the first on the subject of basic electronics. The idea, in case you

haven't been exposed to it, is that you work your way through a series of simple statements (frames), usually supplying a missing part of each statement as you go along. The statements grow weightier in almost imperceptible steps, and you gradually are supposed to find that you painlessly have absorbed an awful lot of information.

Given a few reservations, the approach does work. To be sure, the order of the topics may seem a bit strange and frustrating to someone with but slight acquaintance with the subject, a curious mind may not be able to go in any but one direction at a given moment and there is no real stimulation despite a cleverly programmed text. All in all, though, there's no doubt you *can* learn electronics this way, with a minimum of fuss and feathers. And the cost is pretty low.

HANDBOOK FOR ELECTRONIC ENGINEERS AND TECHNICIANS. By Harry E. Thomas. Prentice-Hall, Englewood Cliffs, N.J. 427 pages. \$15

If the programmed text is very much a product of our era, so is this handbook. More than just a reference for engineers, it also should prove useful to purchasing agents, draftsmen and others on the fringe of today's technology, including anyone concerned with those endless mil spec products for the government.

The book opens with a description of electronics construction and drafting techniques, then proceeds to a discussion of electronics math and a description of testing and measurement procedures for just about every piece of gear under the sun.

INSIDE ELECTRONICS. By Monroe Upton. Signet Books, New York. 222 pages. \$.60

An inexpensive paperback version of the Monroe Upton book reviewed here some time ago, this remains as nicely done and readable an introduction to various electronic subjects as you're likely to find anywhere.



Explore radio's fascinating basement with our 3-tube receiver!

By CHARLES GREEN, W3IKH

TELL someone you have a radio that tunes from 10 kc to 30 kc and he'll figure you spend your time listening to dog whistles and super-duper tweeters.

But way down in this world called VLF (very-low frequency) there's some mighty interesting activity. Imagine hearing a U.S. Navy station transmitting messages to ships at sea and *submerged* submarines! In addition, you'll be able to pick up useful frequency-standard and time transmissions similar to those from WWV.

Why such low frequencies for communications when the trend nowadays is toward higher and higher frequencies in the gigacycle region and beyond? Greater reliability for one thing. Transmissions down in radio's basement are affected little, if at all, by ionospheric disturbances. The other reason is that VLF is about the only way to communicate with submerged subs hundreds of miles from land. Matter of fact, VLF station NAA (17.8 kc) at Cutler, Me., puts out the world's most powerful signal—a 2-million watt—that can be picked up by submerged subs almost anywhere in the world.

You'll find the activity on the VLF band is of two types: frequency-standard and time signals and straight coded CW. The stability of VLF frequency-standard transmissions is much greater than those from WWV since the signals are not affected by ionospheric conditions and magnetic-storm blackouts. The CW often is marine communications, in the form of weather and time reports, and is excellent for code practice.

The output power of most VLF stations is many times greater than that of higher-frequency stations. The power, frequency and type of transmissions of a few stations are listed in our table. But frequencies, power and operating hours change occasionally since experimentation is going on constantly.

Full-Band VLF RCVR

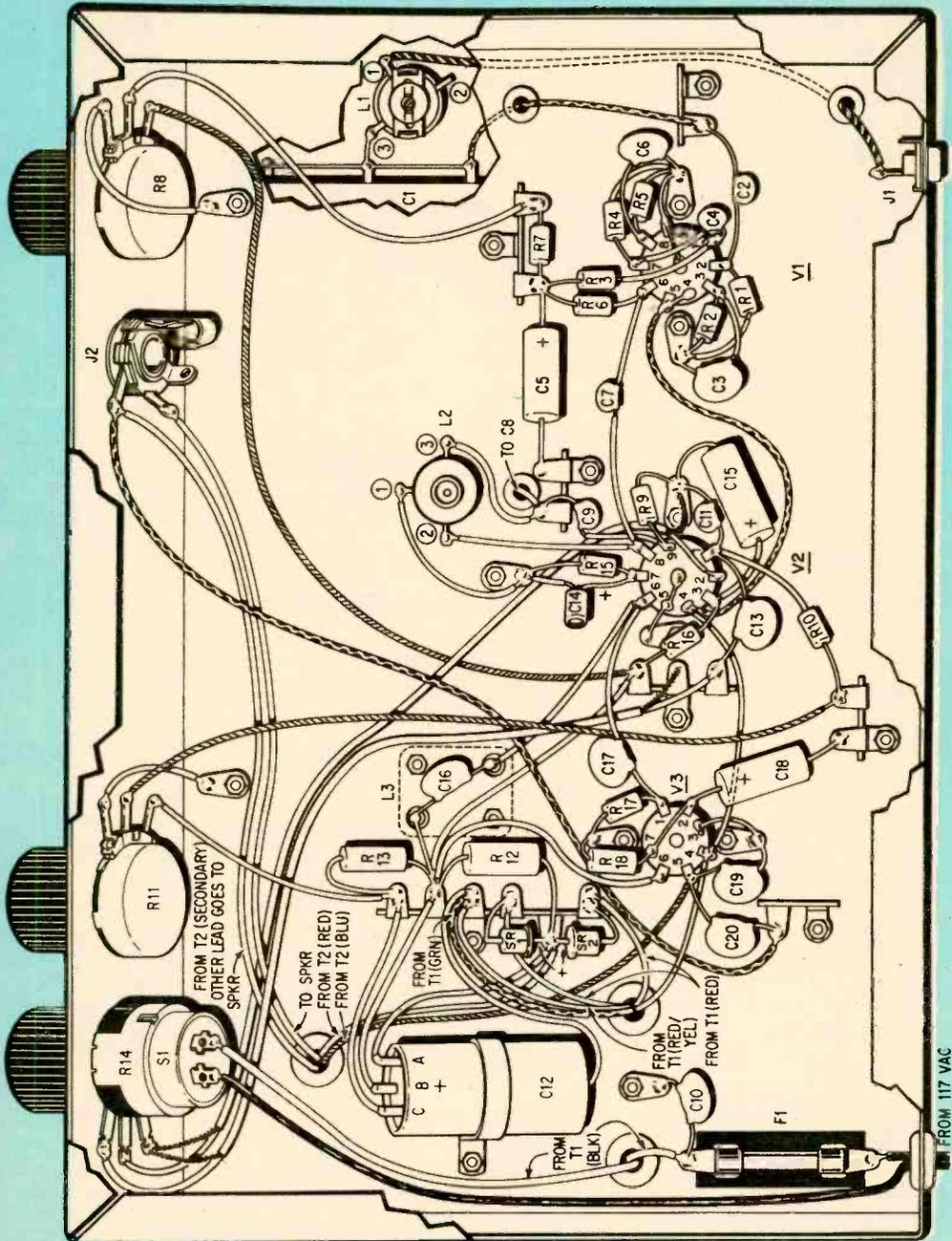


Fig. 1—Underside of receiver. To lay out your chassis, take dimensions from diagram and multiply by 1.7. For best performance duplicate layout as closely as possible. Chassis has been cut away under C1 in diagram to show how three sections of C1 are connected. C8's sections also are tied together.

PARTS LIST

Capacitors: 600 V ceramic disc unless otherwise indicated

C1A, B, C; C8A, B, C—3 gang variable capacitor: 12-367 μmf per gang. (Allied 13 U 522)

C2, C4—1,000 μmf

C3, C6, C19—.01 μf

C5, C15—4 μf , 150 V electrolytic

C7, C9, C11—500 μmf

C10, C13, C17, C20—5,000 μmf

C12A, B, C—20/20/20 μf , 150 V electrolytic

C14—5 μf , 6 V electrolytic

C16—2,000 μmf

C18—10 μf , 25 V electrolytic

F1—1 A fuse and holder

J1, J3—Phono jack

J2—Closed circuit phone jack

L1, L2—65-300 mh tapped adjustable inductor (J. W. Miller No. 9018. Lafayette 34 R 8999)

L3—10 hy variable inductor (UTC No. HVC-9.

Allied 62 G 123, \$9.60 plus postage: not

listed in catalog)

Resistors: $\frac{1}{2}$ watt, 10% unless otherwise indicated

R1, R4—1.2 megohms

R2, R5—4,700 ohms

R3, R6, R10, R16—180,000 ohms

R7—15,000 ohms

R8—200,000 ohm, linear taper potentiometer

R9—2.2 megohms

R11—30,000 ohm, linear taper potentiometer

R12—1,800 ohms, 2 watts

R13—47,000 ohms, 2 watts

R14—1 megohm, linear taper potentiometer with SPST switch

R15—1,000 ohms

R17—1 megohm

R18—560 ohms, 1 watt

S1—SPST switch (on R14)

SPKR—3-4 ohm, 3-in. speaker

SR1, SR2—Silicon rectifier: 500 ma, 400 PIV (Lafayette 19 R 4204 or equiv.)

T1—Power transformer, secondaries: 250 V c.t. @ 25 ma, 6.3 V @ 1 A (Allied 62 U 008 or equiv.)

T2—Output transformer, primary impedance: 10,000 ohms; secondary impedance: 4 ohms (Allied 61 U 448 or equiv.)

V1—12A7 tube

V2—6U8A tube

V3—6AK6 tube (Allied \$1.40 plus postage)

Misc.—2 x 7 x 11-in. aluminum chassis (Premier ACH-405 or equiv.), 7- and 9-pin tube sockets, terminal strips, No. 28 enameled wire, phone plugs, RG174/U Coax.

With this sensitive 3-tube receiver you'll be able to tune in all this activity from 10 to 30 kc. The circuit is a TRF/regen and has both a speaker and a jack for headphones.

Construction

Best way to build the receiver is as we did it—on a 7 x 11 x 2-in. aluminum chassis, mounting the components where shown in the pictorial (Fig. 1) and top-chassis photo (Fig. 5). Since the operating frequency is so low the layout is not terribly critical.

First, drill and punch the chassis. The easy

way to mount variable capacitors C1 and C8 is to make a paper template of the undersides. Then transfer the mounting-hole locations to the chassis. Make sure that C8 is mounted right at the front of the chassis to permit the dial to operate properly. Mount the dial on the chassis with two brackets and extra-long mounting screws.

To mount L1 and L2, first put $\frac{3}{8}$ -in. rubber grommets in the chassis. Next, remove the core and mounting clip from both coils and insert the forms in the grommets as far in as they will go. Then replace the cores and clips. Make sure that you locate L1's mounting hole so C1 doesn't touch the coil.

When wiring the receiver make sure that leads from pin 6 on V2 to L3 and capacitors C2, C4, C7, C9, C13 and C17 are positioned above surrounding wiring. Use rubber grommets when running wires through chassis holes to prevent fraying of insulation.

Antenna Construction

Cut four 22-in.-long x $\frac{3}{4}$ x $\frac{1}{4}$ -in. wood strips and mount them at the corners of a 9 $\frac{1}{2}$ -in.-square piece of perforated Masonite as shown in Fig. 5. Wrap plastic electrical tape on the four screws mounted at the ends of each strip to prevent chafing of the wire.

Wind 38 turns of No. 28 enameled wire

[Article continued on next page,
text continued on page 44.]

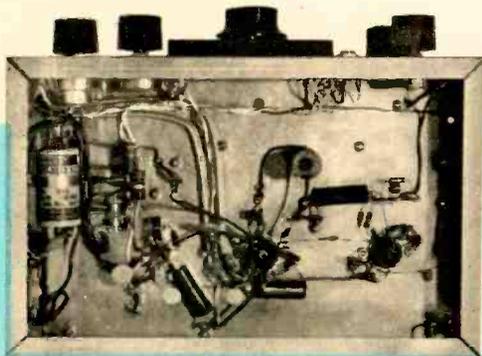


Fig. 2—There's plenty of space so there should be no crowding. Keep long runs of wire at top and center close to chassis in the locations shown.

VLF RCVR

Fig. 3—Schematic of receiver. Signals from the loop antenna enter at J1 and are fed to the L1/C1 tuned circuit. V1A and V1B amplify selected signal and R8 controls the gain of the stages. C7 couples the amplified signal to the regenerative detector V2A via the cathode tap on L2. L2 is tuned by three-gang variable capacitor C8. R11 controls amount of regeneration and C13 feeds the detected signal to volume control R14. Signal then goes to audio amplifier stage V2B. L3 and C16 in V2B's plate circuit constitute a 1-kc peak filter that sharpens receiver selectivity. C17 couples the audio signal to V3 where it is further amplified to drive speaker. T2 and C20 provide output to speaker or phones jack J2. The B+ and heater power is supplied by transformer T1, full-wave rectifier circuit comprising SR1, SR2 and R/C filter which includes R12, R13 and C19A, B, C. Output tube V3, a 6AK6, is capable of delivering up to 1 watt of audio.


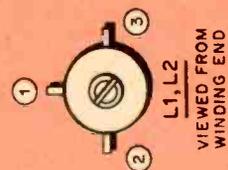
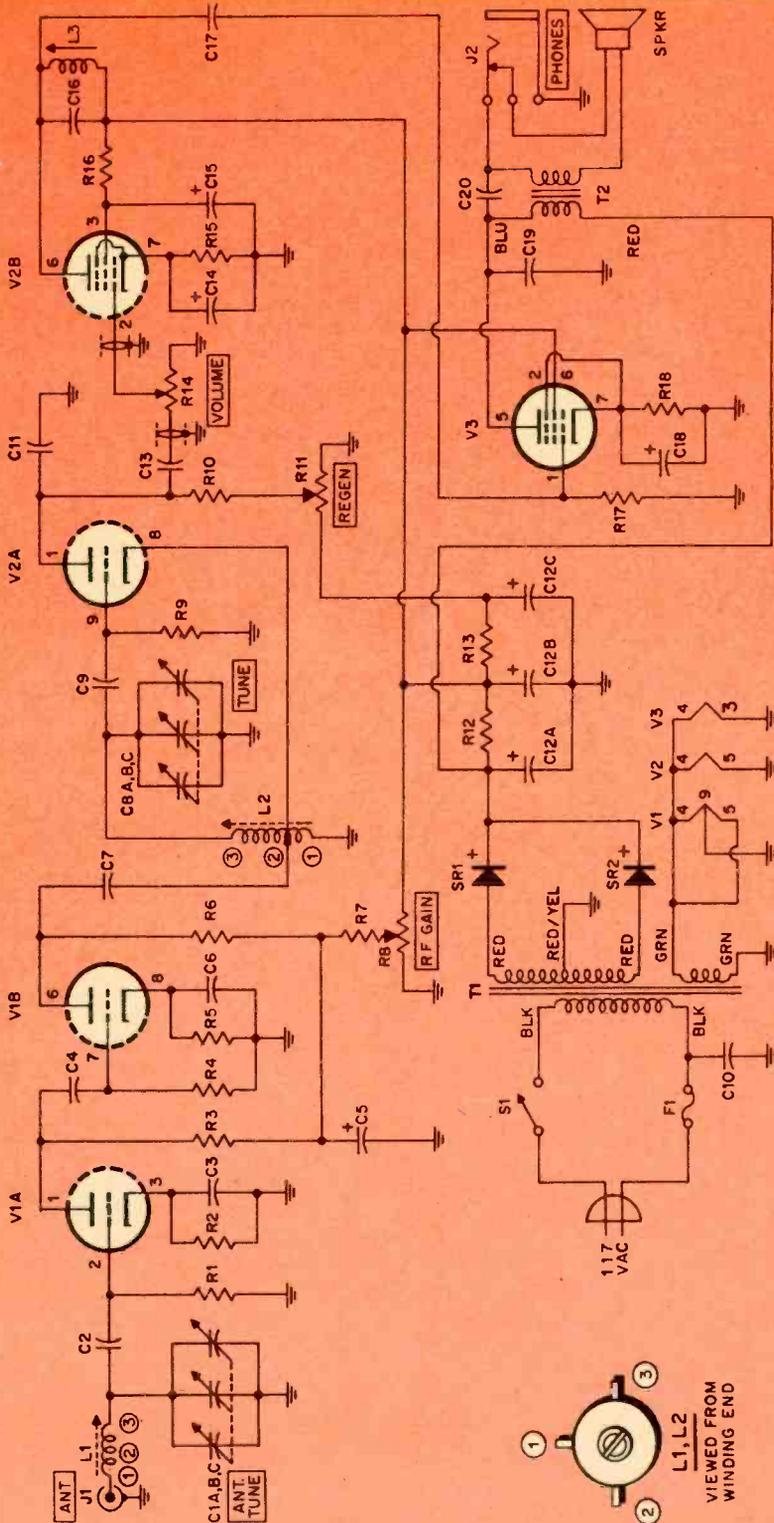


Fig. 4—Loop antenna. Three wooden strips are mounted firmly to Masonite board. Fourth strip should have slots cut for mounting screws so strip can be adjusted to tighten loop. Wind 38 turns of No. 28 enameled wire around screws at ends of wood strips and cover turns with plastic electrical tape. Then wind electrostatic shield over loop. Be sure to space ends of shield as shown in upper left corner. Detail diagram at lower right shows connections of loop and shield. Be sure to connect shield to ground lug on jack J3.

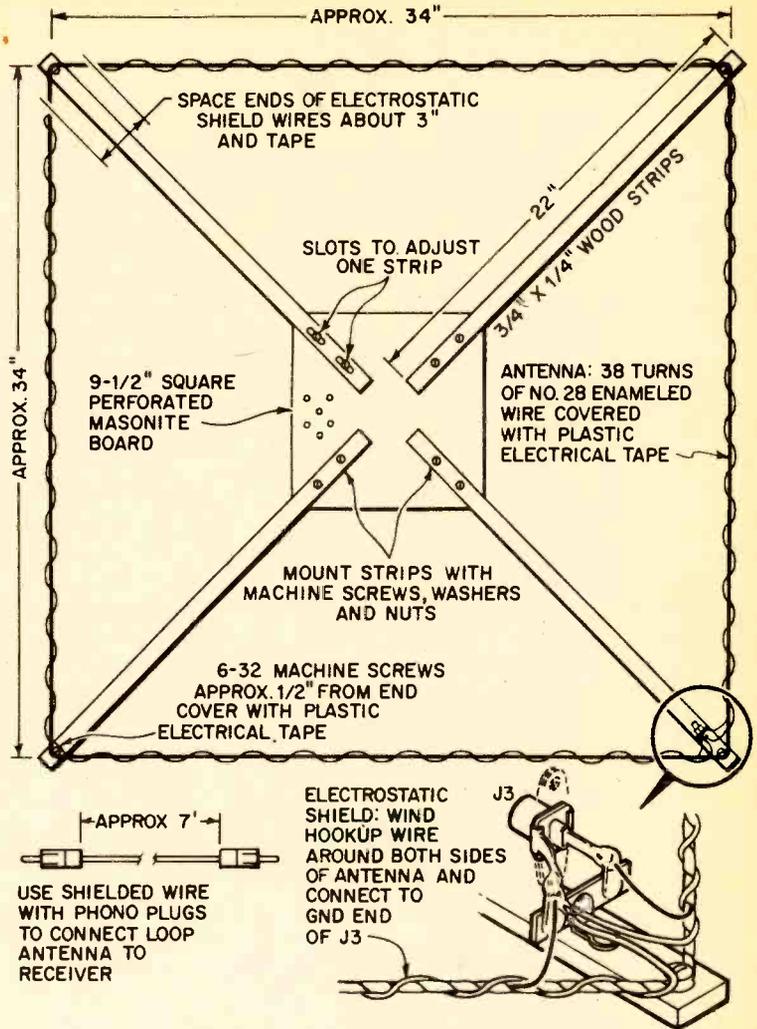

SOME VLF STATIONS

Call	Freq. (kc)	Power (kw)	Location	Transmission
FUB	17.0	—	Paris, France	—
GBR	16.0	300	Rugby, England	—
NAA	17.8	2,000	Cutler, Me.	CW—Navy traffic
NBA	18.0	36	Balboa, C.Z.	Pulses each second. Every fifth pulse omitted.
NPG/NLK	18.6	250	Jim Creek, Wash.	CW—Navy traffic
NPM	19.8	100	Lualualei, Hawaii	CW—Navy traffic
NSS	21.4	100	Annapolis, Md.	CW—Navy traffic
WWVL	20.0	1	Ft. Collins, Colo.	Frequency and time standards. Call sign given every 20 min. and on the hour.

Full-Band VLF RCVR

around the screws and connect the ends to a two-lug terminal strip. Cover the loop carefully with a single layer of plastic tape. To minimize noise pickup, an electrostatic shield made of ordinary hookup wire must be wound around the loop. Connect one end of each electrostatic shield wire to the *ground* side of J3 as shown in Fig. 4 and wind the wire spirally with about 1-in. spacing around the loop. Leave a 3-in. space at the ends of each shield wire as shown. For best performance you can try different loop sizes.

Calibration and Operation

An audio signal generator with a range of 10 kc to 30 kc is a must to calibrate the receiver. If the generator goes only to, say, 20 kc use the second harmonic of a lower frequency.

Allow the receiver to warm up for a few minutes, then connect the output of the audio generator to ground and the high side of *volume* control R14. Set the generator to 1 kc and adjust the screw on L3 for peak volume.

Connect the generator to J1 and set its output to 10 kc. Set R14 to half rotation,

adjust *regen* control R11 until the receiver starts oscillating, then turn *RF gain* control R8 counterclockwise to prevent overload.

Close C8's plates and adjust L2's slug for zero beat. Use the audio generator to calibrate the dial, being careful not to disturb the adjustment of L2. We calibrated our receiver at 1-kc points to 20 kc and every 2.5 kc to 30 kc. Use C1 to peak the signal as required but be sure that you're not tuned to the wrong harmonic.

After the dial is calibrated disconnect the signal generator and connect the loop antenna. When hanging up the loop keep it away from fluorescent lights and large metal objects.

Couple the audio generator loosely to the receiver by connecting a length of hookup wire to the hot side of the generator's output cable and placing it near L1. Set the generator's output to 10 kc and tune the receiver to about 11 kc for a beat note. Set C1 to full capacity (plates closed) and adjust L1's slug for maximum beat-note volume. Disconnect the signal generator and turn it off to eliminate any chance of the receiver's picking up its signal.

Now tune the receiver for signals, keeping C1 in approximately the same position as C8 to minimize reception of station harmonics. Turn the loop around to find stations.


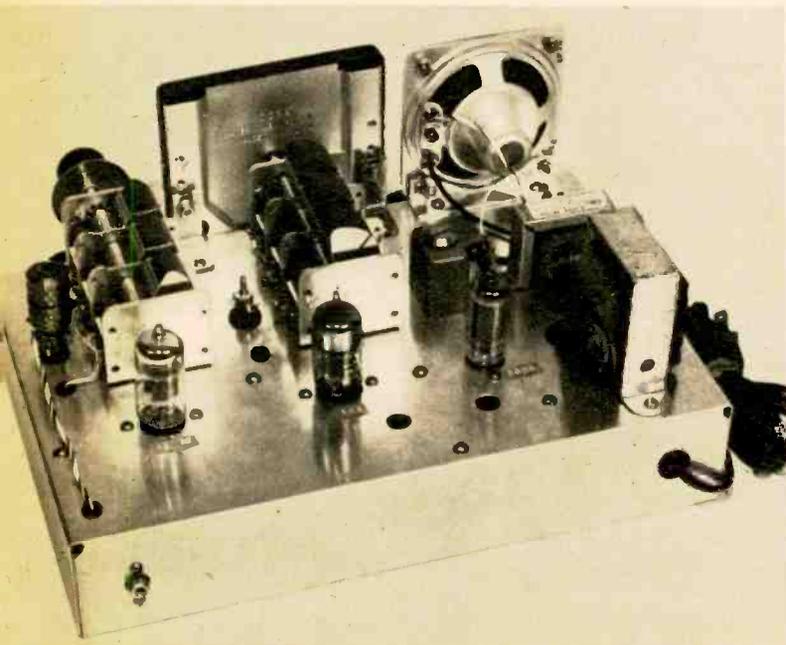


Fig. 5—Top of receiver. Coil L1 is at extreme left and antenna tuning capacitor C1 is right next to it. V1 is behind C1. Main tuning capacitor C8 is located in center of chassis. L1 is located between C1 and C8. Variable inductor L3 is low gray object to the right of C8. Power transformer T1, output transformer T2 and speaker are at right side of chassis.

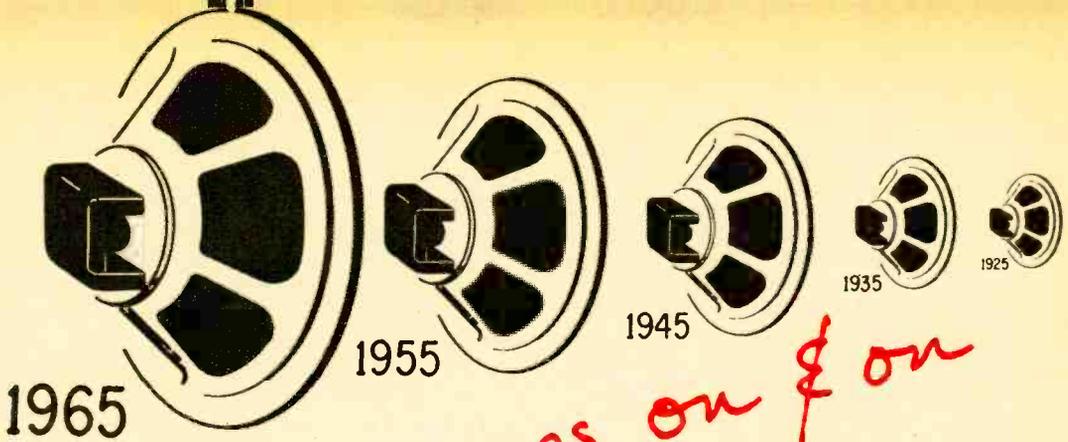

Life ~~begins~~ at 40

BY KEN GILMORE

THE ART (some would have it a science) of sound reproduction has been perfected so markedly in the last decade that it sometimes takes a keen ear to tell real from recorded. And so carefully designed are current stereo sets that few buffs would dare dream—let alone argue—that a 40-year-old component plays a leading role. But it's true.

"A relic in my rig?" you gasp. An antique? A fugitive from the age of crystal set and the wind-up phonograph? Right four times over.

To be sure, most of the home-music machine of the 1920s is dead as a pickled oyster. But one part in the modern audio scene is virtually identical to its 40-year-old ancestor. The basic noisemaker, the loudspeaker in your living room, has remained almost the same since the days of the Stutz Bearcat, the flapper and bathtub gin.

"There have been no real changes in decades," says Karl Kramer, manager of technical services for the Jensen Manufacturing Co., "and there aren't any on the horizon."

"New trends?" asks Saul J. White, chief engineer of Rek-O-Kut's Audax Division. "They don't exist. The dynamic speaker hasn't had any serious competition for years and it will still be around for a long time to come."

The 24-carat wonder is not that it's been around for so long but that it works at all. Take a frame roughly the size and shape of

a hubcap, throw in a magnet, a few turns of fine copper wire and a pie-size slab of cardboard. The resulting contraption is supposed to make noises like the Beatles or bongos, a string quartet or a hundred-man symphony. Funny thing—it does!

This fantastic machine, the direct-radiating dynamic loudspeaker, got its start back in the 1920s. Calvin Coolidge occupied the White House, prohibition was in full swing and the air was full of a strange new sound called radio. Most common sight of the times was an ardent kilocycle-chaser bent over his crystal set far into the night. But radio listeners soon tired of the heavy, uncomfortable headsets. And sometimes several people wanted to listen at once. Needed: a practical loudspeaker.

A lot of people tried to build one. And many speaker makers of the time enjoyed a brief moment of fame. Radio magazines were full of glowing reports.

"The design of this loudspeaker is such that the low notes of the cello, organ, piano, and the brass instruments of the lower register are faithfully reproduced," said one.

The object of this praise was a weird device that looked like a cross between a flying saucer and a reading lamp. The description just quoted appeared in *Scientific American* magazine for December 1924.

And listen to this: "The performance of this new loudspeaker is remarkable for its

goes on & on

Life begins at 40

brilliancy and faithfulness over the whole range of musical notes." That, from the March 1928 Radio News magazine was written in praise of an odd contraption of linen cloth, square wooden frame and adjustable brass rods. It was designed to play music, though it well might have taken off in a high wind.

Competition was intense among the many kinds of speakers on the 1920s market and there was no way of telling which might win out. Then almost without notice two engineers at the General Electric research laboratories in Schenectady began to take a hard look at what device best might make like violin, tenor, marimba band or foghorn.

Chester W. Rice and Edward W. Kellogg built and tested nine basically different speaker designs, from a curious gadget called the Frenophone to an even stranger one known as the gold-leaf thermo phone. Their conclusion, published in the Journal of the American Institute of Electrical Engineers in September 1925: the dynamic moving-coil speaker they had developed was the hands-down winner from every point of view—sound quality, efficiency, cost, ease of con-


struction. Fully forty years later it still is.

The Rice-Kellogg wonder—the dynamic or moving-coil speaker, the one still making the sounds in your stereo set today—works on a simple principle. A small coil of wire known as the voice coil is mounted in a magnetic gap. (Most speakers now use permanent magnets, though electromagnets were commonplace years ago.)

When an electrical current flows through the voice coil it sets up a magnetic field which pushes against the magnetic field in the gap. Shoot current through in one direction and the voice coil moves out. Reverse the current and the voice coil bounces in the other direction. Send an audio-frequency signal through the voice coil and its movements are proportional to the fluctuations of the current. Attach a diaphragm—usually a large paper cone—to the voice coil and the coil's vibrations will move large amounts of air and thus generate sound waves.

Simple? Sure. But it's also unbelievable when you consider that it has withstood all competition for two generations. And there's been plenty. Take one competitor you no doubt are familiar with: the electrostatic speaker.

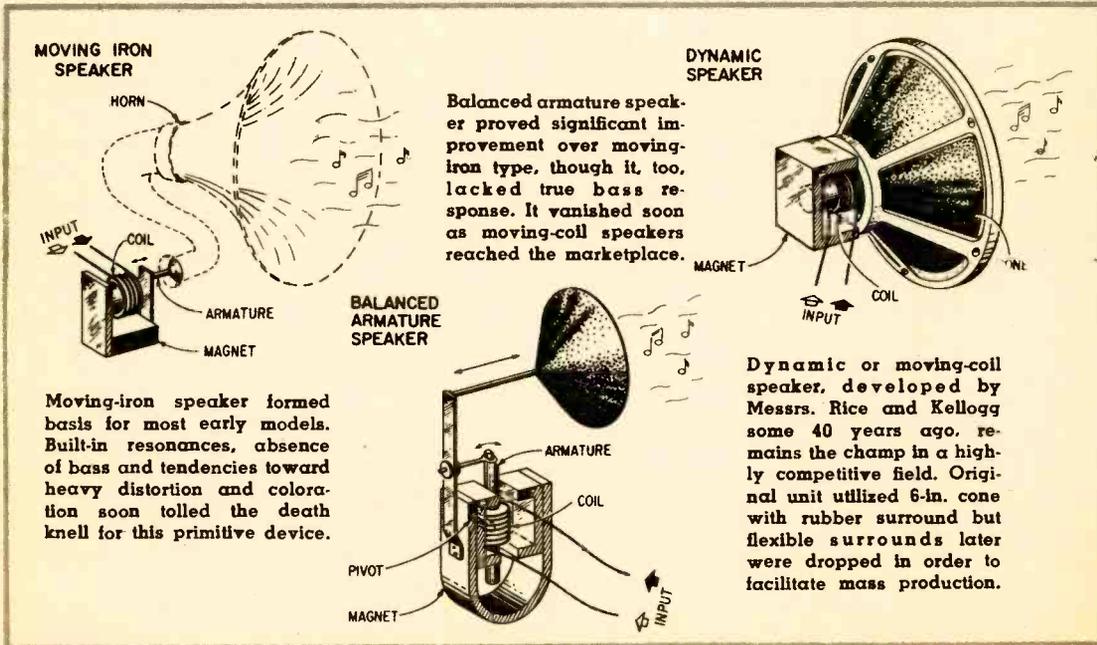This odd sound-maker, which caused a lot of excitement as recently as the 1950s, really is nothing but a big capacitor. Three (some-



times two) large plates are mounted so one is movable, the other rigid. When a varying voltage is placed across the plates, electrostatic attraction and repulsion make the movable plate vibrate.

The electrostatic looks great in theory. Rice and Kellogg thought so, too. It was one of the speakers they tried back in 1925. It couldn't, they found, compete with the dynamic. Electrostatics since have come on the market from time to time and today excellent ones are available. Same old story, though. On the basis of performance, cost, ease of construction and efficiency, they can't beat the dynamic.

Another promising competitor was developed a few years ago by a Paris-born inventor named Siegfried Klein. Klein was trying to overcome one of the speaker designer's greatest problems: the inertia of a diaphragm. Theoretically, the perfect diaphragm would have no mass at all. Such an inertia-less device could wiggle back and forth fast as electrical current could change. It would make a fine high-frequency reproducer.

Klein, for all practical purposes, succeeded in building the mass-less diaphragm. In his speaker, called the Ionovac or Ionophone, air itself is the diaphragm. The air in a pencil-size quartz tube is ionized by radio-frequency current.


An audio signal, representing a modulator, makes the little lavender cloud of glowing air expand and contract. This jiggling gas cloud produces sound, just as does the vibrating diaphragm of a dynamic speaker. (As you might guess, Rice and Kellogg were there first with this one, too. A close relative of the Ionovac was one of the devices mentioned in their landmark paper back in 1925.)

The Ionovac, despite its fine performance, never has made it big for two reasons. First, it's expensive—around \$70. And, second, dynamic tweeters have improved so much in recent years that any differences in performance are marginal.

Another new design that so far has failed to run the dynamic much of anywhere is the French-built Orthophase speaker. A conductor that takes the place of the voice coil is glued in a zig-zag pattern on the back of a flat, grooved plastic panel. The movable panel is mounted so that the wires slither back and forth between rows of small fixed magnets. When current flows through the wires, the magnetic field it generates reacts with the fixed magnets and moves the plastic panel. Surprise: it's a variation of the old ribbon speaker mentioned—naturally—by Rice and Kellogg.

Speakers working on different principles continue to come along from time to time.


IONOVAC SPEAKER

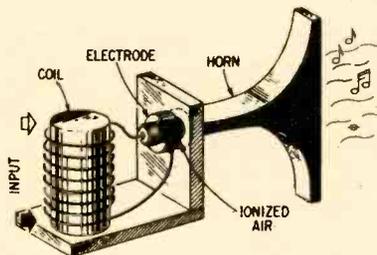

Crystal speaker relies on piezoelectric properties of ceramic or quartz and basically is a crystal microphone in reverse. Though a satisfactory high-frequency reproducer, the device has proven incapable of covering the full audible range.


Electrostatic speaker is modeled on the capacitor and has been produced in both single-side and push-pull versions. Old as the dynamic, it has proven an excellent performer, though the moving-coil remains king of the speaker world.

CRYSTAL SPEAKER

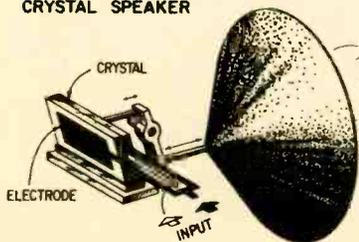

Ionovac or Ionophone speaker employs no moving parts and, therefore, has strong theoretical appeal. Like the crystal speaker, it primarily is a high-frequency reproducer and has yet to unseat the more versatile dynamic or moving coil.

ELECTROSTATIC SPEAKER

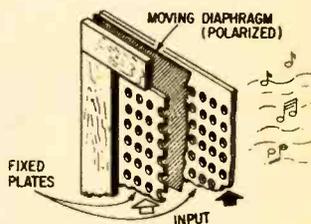

goes on \$ on

Life begins at 40

A few months ago Motorola announced its new solid-state tweeter. Heart of this sound-maker is a thin, 2-in.-long tube of lead zirconate and lead titanate which shortens and lengthens slightly with a varying electrical signal. One end of the tube is anchored rigidly to the speaker frame and the other end attached to a small diaphragm. Feed a signal to the tube and the diaphragm vibrates. In some ways, it's similar to the old crystal speaker that enjoyed a spurt of popularity early in the 1930s.

The fact that no other type of speaker ever successfully has competed with the dynamic doesn't mean that the art of speaker building has stood still four decades. But advances have come largely in improvement and refinements of the dynamic speaker. For though the dynamic has been a remarkably successful machine from its inception, it's been plagued with certain problems, too.

One problem, for example, is what engineers call breakup. At relatively low frequencies the speaker cone moves in and out as a single unit—so-called piston action. As frequency rises, though, the outer edge can't keep up with the faster back-and-forth movement of the voice coil. It begins to vibrate crazily on its own and produces a rough, distorted sound.

The way to minimize breakup, of course, is to make the cone stiffer so it will act as a true piston at all frequencies. But make it stiffer and it also tends to get heavier. Needed is a new speaker material—both stiffer and lighter.

Some speaker designers now feel they finally have found the wonder stuff: plastic foam. Fine speakers have been built using thick but light foam cones.

"Foam construction entirely eliminates breakup over the range in which it is used," says Peter Prichard of Audio Dynamics. "Either the cone moves properly or it doesn't move at all."

Others take a more conservative view. "There are certain advantages in using foam for some applications," observes Larry Le-Kashman of Electro-Voice. "We use it in some of our speakers. But you can do the same thing in other ways."

And some designers fail to see much advantage in the new substance. Victor Brociner of Scott argues: "It is possible to make very good speakers using some of the new materials. But I'm not convinced they're really any better than the old ones."

Other space-age materials and techniques have come along, too. Magnets, for example, now are far stronger, more compact, longer lasting. Famed British speaker authority G.A. Briggs of Wharfedale pioneered the use of flexible material around the cone's outer

[Continued on page 96]

The thoroughness with which Messrs. Rice and Kellogg approached their task of developing a "loud speaker free from the most objectionable of the distortion which characterizes loud speakers in general" is revealed in this old, unretouched photo of their lab at General Electric. Their conclusion: that "it should be possible to make an ideal sound reproducer" utilizing what is known as the moving-coil principle.



LAST STAND FOR



BRASS POUNDERS

BY ELBERT ROBBERSON, W2FRQ

A FEW short years ago, International Morse smeared the spectrum from the bottom step clear up to the then-quiet kilocycles we now call VHF. Pros boasted ears so keen they could read anything sent, even when revved up to machine-age speeds near 100 wpm. In between the tape transmitters, you still could hear real people sending—with artistry only humans can muster and techniques only a book could describe (the Lake Erie Swing and the QLF, two styles familiar to old-timers, perhaps merit mention).

Tune the spectrum now, though, and you'll be hard-pressed to find manual operators anywhere but on commercial ship frequencies and the ham bands. The fluting of teletypes and buzzing of green hornets have taken over. Fact is, commercial brass-pounders look doomed. Wallpaper is about the only thing you can make of telegraph tickets. The brass-pounders truly are making their last stand.

The Beginning. Marconi's first signal spanned the Atlantic in December of 1901. Only seven years and a few days later, on January 23, 1909, the White Star liner Republic was rammed and sunk off Nantucket. Wireless operator Jack Binns summoned help by sending the first pre-SOS distress call (a CQD, presumably meaning CQ distress). Result was that all but six passengers were saved.

In 1911, radiotelegraph became compulsory on U.S. ships. And a ship's radio-distress call again brought help for survivors in 1912, when the Titanic suffered a fatal gash from an iceberg. Jack Phillips, chief operator, lost his life in the disaster and joined the growing ranks of operator-heroes.

On shore, companies formed and folded fast as wildcat oil drillers to capitalize on the miracle of being able to send messages across continents and oceans without wires. Until high-frequency communications were devel-

LAST STAND FOR BRASS POUNDERS

oped, signals were pushed long distances by brute force. To generate the necessary power, great sparks buzzed, molten arcs sizzled and mechanical alternators revved up to as high as 20,000 rpm, their rotors yearning to fly apart with all the urge of 68,000 Gs.

To make these rock-crushers work, an early operator had to be electrician, steeple jack, rigger, mechanic and oiler. To turn on some arc transmitters he also had to be something of an acrobat. The arc was struck by pushing the carbon-holder in by hand until the carbon contacted the other electrode, starting current flow. When forward pressure was removed, the carbon drew back and an arc flamed between the electrodes.

Trouble was, the arc chamber was filled with hydrocarbon gas (which helped the operation). If there also was the right amount of air in the chamber, the gas blew up and the carbon was fired back at the operator. Special starting strokes were developed to avoid broken wrists.

Because receivers had little or no amplification, the operator was forced to develop sensitive hearing. According to the expression, a man would crawl into the headphones in order to copy weak signals. He also had to be able to telegraph. Though some point-to-point circuits used machine transmission and reception, most signals were broken into the dots and dashes of International Morse Code, much of it banged out by hand. Key current was high, contacts had to be heavy and, unless you wanted to burn the contacts

on your Bug (a key operated with a side-to-side movement), you used the old pump handle (an ordinary up-and-down key).

Stations ordinarily were hundreds of miles apart and sending had to be slow. A distant spark signal, for example, sounded like a gnat sighing through a screen and the burbly signal of a far-away arc transmitter might be weaker than the noise, the methodically tapped dihs and dahs audible only through holes in the static. So all-important was an individual's adeptness that every operator struggled to avoid ending up with the trade's own brand of punch-drunkenness—a tin ear and a glass arm.

The Buildup. In the '20s and '30s vacuum tubes took over. Signals became sharper, receivers more sensitive and selective and high frequencies bounced farther with less power than ever was possible with the old ground-slogging lows. It all added up to a boom in radiotelegraphy, scarcely threatened by the novelties of voice transmission and the rattling of a few robot operators.

At high-speed point-to-point stations, tape keyers sent the messages. On the receiving end, inkers squiggled a line of dots and dashes on a tape that was read by the eye. If the tape fluffed in transmitting, the human operator tending the machines either could pull the tape back for a rerun or send the erroneous part by hand.

On circuits where conditions were poor, human operators using the old sending iron (a now-obsolete term for a key, perhaps akin to shooting iron for a gun) and the naked ear would handle traffic through fading, atmospheric noise and interference severe enough to have driven a machine out of its metallic



Lord of the seagoing radio shack and sole contact with a ship's outside world, the radioman aboard a freighter or liner likely will continue to rely primarily on radiotelegraphy for many years to come. For, despite its demise elsewhere, code remains unsurpassed in reliability, the prime requisite for most shipboard communications.

Grace Line

mind. Shipboard operators handled few messages—except on the largest liners, a couple a day was tops. At 21 cents or so a word, people thought twice before putting pencil to paper. Main function of the shipboard sparks was to insure safety. The military, naval and point-to-point circuits, however, handled messages by the stack.

Every service had its distinct ways of handling traffic, as well as its own special procedures and signs. Some circuits were fast, some were slow, some even sloppy. But the operators all pushed traffic fast as their reflexes could function.

On a hot circuit it wasn't uncommon to go on duty and be handed a stack of unsent messages that would take the entire watch to clear. While tapping it out on the key with your right hand, you'd be endorsing the message blank with your left—pencilling time, date, to whom the message was sent and your sine or initials. Then you'd peck out the data on the log sheet, wound around the platen of your mill (typewriter).

When receiving, you'd roll a message blank into the mill, on top of the log, and endorse the blank. By this time, the sender was halfway through the address, so you had to catch up with him. You copied behind, or else turned in your green eyeshade. In your spare time you would log the messages handled.

At one time, Navy operators were doing this by what was called F- or no-answer method. You just didn't miss anything because you got no repeats. It was assumed that you copied everything slammed at you so you even didn't R upon receipt of messages.

It was fairly common to copy press transmissions on a mimeograph stencil. Once you

got the hang of it you could take care of overstrikes with the little glass stylus and correcting fluid, then catch up and go on with your copying. And when you got to be an operator, you could do this and smoke, drink coffee and read a book at the same time.

Plenty of people could copy over 60 words per minute. Champion T. R. McElroy topped 70. And for sending code that would squirt out like water from a hose, speed artists would talcum their fingers.

The Decline. About the time that World War II was brewing, the telegraph key was starting to slip (though automation still was an unthought-of term). As radio-circuit reliability improved and as more effective frequencies were utilized, extensive use of teletype machines became practical. An operator who didn't need to know any more than where the keys were on a typewriter could punch out a message. A thousand or more miles away another machine would print it, at 60 words a minute.

Further, instead of using a radio transmitter for just one message, its carrier could be modulated with several subfrequencies, each of which could be used for a teletype channel. Time-splitting techniques further allowed multiple-circuit use of a radio transmitter. The result sounded like a concerto for buzz saws. But no matter, thousands of words could be transmitted in the time it previously had taken for hundreds.

Whenever the traffic load warranted and sufficiently reliable radio contact could be maintained, machines began to gobble up the traffic. What the machines didn't handle, voice circuits did. Where conversational interchange was necessary, the radiotelephone gave practically the same quick convenience of wire circuits. With the development of single sideband, voices began to relay messages over distances that previously could be spanned only by dots and dashes.


The Twilight. With improved radio circuitry, reliability and automation, it would be easy to conclude that the world is about ready to put a spade in the face of the honorable but old-fashioned order of the commercial brass-pounder. Modern radio schools almost completely have dropped radiotelegraphy courses. And FCC license examiners report that applicants for radiotelegraph licenses virtually are non-existent.

But though on the decline, manual radio-

[Continued on page 101]



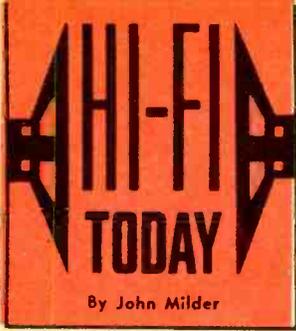Still popular in some ham circles and aboard ships, the familiar telegraph key has become all but a relic in the commercial radio world.



- ✓ *Platters & promises*
- ✓ *Dig that Dynarange*

ONE of hi-fi's more interesting trends over the past three or four years largely is unsung. It's the drift away from the transcription turntable (to which you add the tone arm of your choice) and toward the integrated turntable/arm combination. The past three years, in fact, have seen not one new transcription table marketed in this country, though more than a dozen integrated units—automatic and single-play—have appeared.

What happened? For one thing, manufacturers of automatic turntables have managed to come up with tone arms comparable to transcription designs. The secret is a new breed of changer mechanisms that requires precious little push from a tone arm to trigger the changing cycle and that leaves the arm completely free of restriction during its normal travel across the record. And as things now stand, one would be hard-pressed to find a transcription arm (of the kind that we purists used to shell out \$30-\$70 for in the late '50s and early '60s) of any better overall performance than those now found on automatics like the Dual 1009, Garrard Lab 80 and Miracord 40 (all of which fall in the \$80-\$100 class—with cartridges often thrown in for a penny).

It also pretty well has been demonstrated over these past few years that the integrated designs can offer better performance than the supposedly perfectionist combination of table and arm-of-your-choice. First real hint of this came with introduction of the Stromberg-Carlson PR-500 turntable in '59.

The PR-500 was the first to suspend tone arm and turntable platter on a single sub-assembly sprung from the motorboard. This isolated arm and platter from any vibration that might find its way from motor through baseplate. Additionally, it resulted in an arm and platter that responded in unison to outside disturbances like kids racing across the living-room floor. You presumably would be aware that footsteps were shaking the player

but the unison movement of arm and platter helped keep the stylus in the groove.

Stromberg wasn't in audio long enough to do much with the PR-500 design. But Acoustic Research later took the basic premise, added some important refinements (including a lightweight tone arm and a special belt-drive) and proceeded to show just how quiet a turntable could be. The AR design demonstrated how an integrated suspension of platter and arm could diminish all sorts of problems by eliminating mechanical and acoustic feedback through the turntable assembly. I won't forget easily the shock of substituting the then-\$58, single-speed AR table (now \$78 and two-speed) for my \$250 transcription combination and hearing how much clearer all my stereo discs sounded.

Since the AR's arrival the integrated design has become the almost-universal approach. Others (beside the whole new breed of automatics) include the Empire 488, Rek-O-Kut
[Continued on page 103]



Dynarange 200 by 3M (Scotch) and Formula 15 Low Noise by Audio Devices (Audiotape) are two entries in the low-noise tape field. Ampex's 500 series (not pictured) is a third.

SOMEONE SHOULD DEVELOP AN EASY WAY TO LEARN ELECTRONICS AT HOME

RCA INSTITUTES DID!

RCA introduces new CAREER PROGRAMS—beginning with the student-proved "AUTOTEXT" Programmed Instruction Method—the faster, easier way to learn. You start to learn the field of your choice immediately. No previous training or experience needed.

Pick the career of your choice—and RCA Institutes will do the rest! RCA's new, revolutionary "Career Programs" help you go directly to the career you want! You waste no time learning things you'll never use on your job! Each Career Program is designed to get you into the kind of job you want in the fastest, easiest possible way!

SEPARATE COURSES

In addition, in order to meet specific needs, RCA Institutes offers a wide variety of separate courses which may be taken independently of the above Career Programs, on all subjects from Electronics Fundamentals to Computer Programming. Complete information about these courses will be sent with your other materials.

CHOOSE A CAREER PROGRAM NOW
your first step to the job of your choice!

- Television Servicing
- Telecommunications
- FCC License Preparation
- Automation Electronics
- Automatic Controls
- Digital Techniques
- Industrial Electronics
- Nuclear Instrumentation
- Solid State Electronics
- Electronics Drafting

RCA INSTITUTES BONUS EXTRAS

Only RCA Institutes offers you a Liberal Tuition Plan, one of the most economical ways to learn. Plus, you get top quality equipment in all kits furnished to you with your courses—yours to keep and use on the job. And now, RCA's NEW PROGRAMMED ELECTRONIC BREADBOARD GIVES YOU LIMITLESS EXPERIMENTATION—scientific laboratory procedures

right in your own home! You build a working signal generator, AM Receiver, Multi-meter, Oscilloscope, and other valuable equipment—ALL AS A PART OF YOUR COURSE! Get the facts today!

Classroom Training Also Available. Day and Evening Classes are available to you in New York City at RCA Institutes Resident School. You may be admitted without any previous technical training; prep courses are available if you haven't completed high school. Coeducational classes start four times a year.


SEND ATTACHED POSTCARD TODAY FOR COMPLETE INFORMATION. NO OBLIGATION. NO SALESMAN WILL CALL. FREE BOOK INCLUDED. CHECK HOME STUDY OR CLASSROOM TRAINING.

RCA INSTITUTES, INC. Dept. E1-36

A Service of the Radio Corporation of America
350 West 4th St., New York City 10014



The Most Trusted Name in Electronics

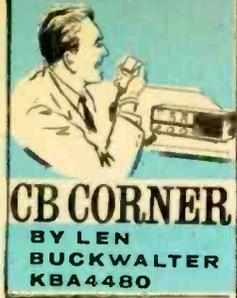

INSTANT ENFORCEMENT

STORY goes that CBers have a flock of dodges for boosting operating range—from screaming into the mike (which doesn't work) to adding outboard amplifiers (good for a \$500 fine). But the best range-busting technique in many a year is part of a tale told by Don Nelson of Sioux Falls, S.D.

Seems the boys up Dakota way were running a giant jamboree. As in most of these affairs, there was a CB-equipped control center to handle communications in the area on the big day. But what an antenna system they cooked up! Transporting component parts for the giant skyhook required a two-wheel trailer.

Came the appointed hour and the trailer unloaded a cargo of long pipe sections. Up went the pipes until they topped out at about 50 ft. above ground. The base was footed firmly in the trailer bed while a series of guy wires kept the slim assembly from toppling. Planted atop this plumber's dream was a Magnum base-station antenna that never had seen such days. Connected to a CB rig down at the car, it transmitted and received signals over a whopping 20 miles.

Meanwhile, down at the jamboree, seeds of the hook's destruction were being sown. Who was star speaker of the day? None other than the local FCC field engineer. Spotting the cool collinear, he applied what might be called instant enforcement in the first case on record of excessive antenna height on a

mobile rig. Take it down, he said, and down it came. The 20-ft. rule seems to apply equally to terrace, tent or Tin Lizzie.

New Kaar Guarantee . . . The auto industry backs it go-carts to the tune of 50,000 miles and TV makers are toying with five-year warranties. Now it is CB's turn. Kaar Engineering, long-time CB maker, is marketing two new transceivers bearing a full two-year guarantee (see our photo). That's an 800 per cent improvement over the usual industry (EIA) 90-day coverage.

"What's the secret?" we asked Frank Genochio of Kaar. Space age, he said, then ticked off components that sound like a bill of materials for Early Bird.

Behind the guarantee lies a canny bit of marketing strategy. Kaar believes its new rigs soon should outdistance the \$99 talk-listen box that provides function but not necessarily long-term reliability.

Big HELP? . . . Unofficially residing on Channel 9, the HELP program really is a sort of old-fashioned CB operation. Public-spirited citizens monitor the frequency for motorists in distress, then dispatch help via 5-watt transmitters. But if a petition now before the FCC reaches fruition, 5 watts could become 30. That petition is the work of the Automobile Manufacturers Association, now

[Continued on page 105]

Pace-setter from Kaar Engineering is a two-year guarantee covering workmanship and materials in its new rigs. Usual guarantee is only 90 days.



Notes

from EI's DX CLUB

ONE of the most interesting BCB DX catches of the year proved to be right here in North America. It was HIFA, the military junta station at San Isidro, Dominican Republic. HIFA opened up on 647 kc as the rebellion began, then moved up to 652, where it stayed until silenced by the provisional government. How many were lucky enough to nab this one?

To answer a question raised by Roger Hallan, WB6BOW, you may use GMT (Greenwich Mean Time) in your EI DX Log if you wish. But if you do so, be sure to indicate that this is the case.

From Fred L. Parsons (Ontario) comes word that R. Ghana now is beaming programs to North America. Times are 2230-2330 EST on 6110 kc and 1500-1600 EST on 9760 and 11800 kc.

As most readers already are aware, Singapore has left the Malaysian Federation and once again counts as a separate country. Easiest spot to log R. Singapore is 11940 kc until 1130 EST sign-off. Incidentally, Perry Brainin (New York City) reports having logged R. Malaysia the hard way. He bagged two of their 49-meter transmitters, 6105 and 6175 kc, between 0600 and 0700 EST.

Reception of R. Malawi on 3380 kc is reported by both Gerry Klinck (Buffalo) and William Sparks (California). Station's 2300 EST sign-on is preceded by the sound of drum beats and a cock crowing. East Coast DXers really have to be sharp on this one, though, since fade-out hits soon after sign-on.

The Burma Broadcasting Service has ventured into the upper SWBC bands and can be heard on approximately 9530 kc until 0200 EST.

The BBC's East Mediterranean relay,

transmitting from strife-torn Cyprus, is reported on 7140 kc at 2300 EST. (Be careful not to mistake 7140 for BBC London on 7150 kc.) Bob LaRose (Binghamton, N.Y.) also has logged this same Cyprus relay on 15420 kc at 1300 EST.

R. Tarawa (Gilbert & Ellice Islands) has moved down to 4912 kc, leaving 49-meter QRM behind. Watch for this one around 0200 EST or a little earlier. Chances for picking this one up on the East Coast should improve as spring approaches; station also may show up on 3218 kc.

Dave Bennett (British Columbia) advises that the CBC's two regional SWBC relays have changed calls. The station at Vancouver, B.C., now is CKZU and the one at St. John's, Nfld., has become CKZN. Both operate on 6160 kc.

A new standard time and frequency station is being heard on 15000 kc late afternoons, identifying as RTA. That's a Soviet call, though no one seems to know much about the station.

Larry Thompson (Cincinnati) recently came up with the Solomon Islands Broadcasting Service on 3995 kc at 0500 EST, clear indication that the East and West coasts have no monopoly on DX. Like R. Tarawa, this station should improve with spring's arrival (as will Down Under hams on 80 meters). Should be interesting to see if amateurs can match these SWL feats on the lower bands.



R. Nacional del Peru's 31-meter outlet has begun to drift up from 9562 kc. Station has been rockbound on that frequency for several years.

Propagation: As days begin to lengthen and static levels in the northern hemisphere
[Continued on page 101]

**SUPER
SPEED
STROBE**

**CAN
STOP
THIS** →

**AND
THIS!**

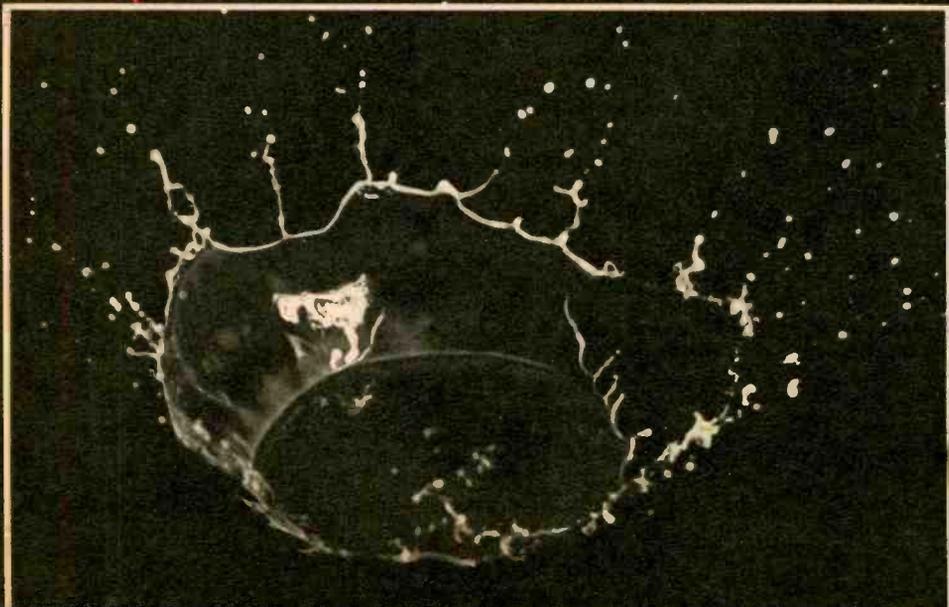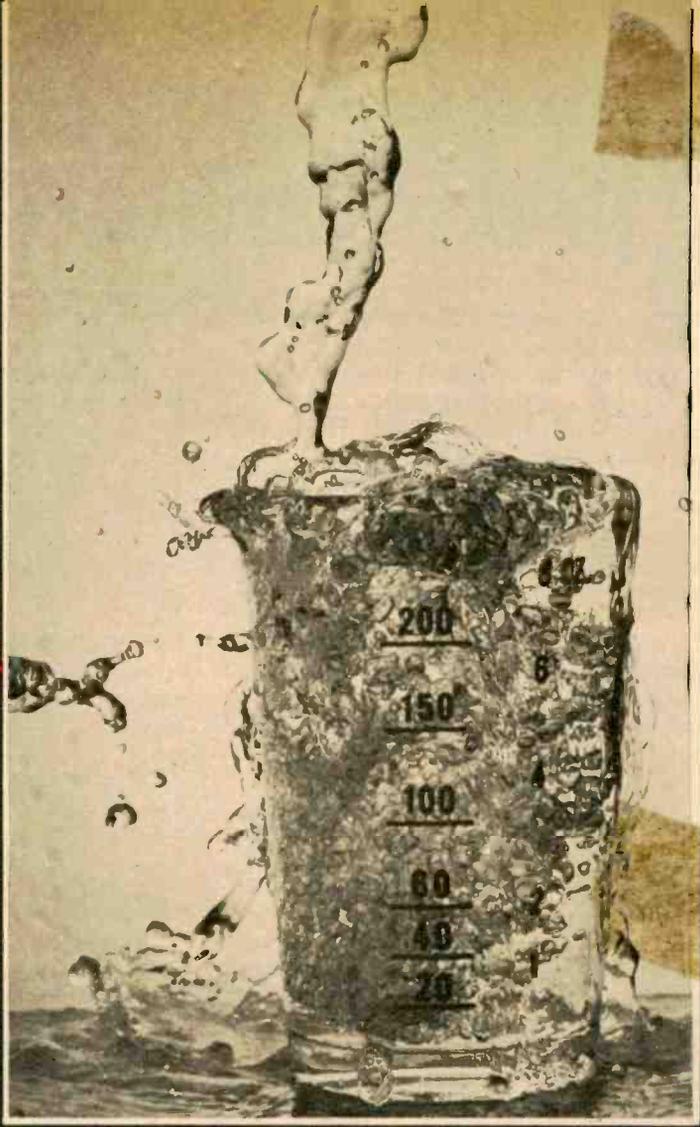

By JIM KYLE, K5JKX A DROP of milk strikes a surface. The eye and an ordinary strobe flash see nothing but a blur. But the 1/10,000-sec. flash of EI's Super-Speed Strobe freezes the action and the milk drop turns into a crown shape in the magnificent photo shown at the bottom of the opposite page. A stream of water falling into a graduate becomes an arresting still-life in the upper photo.

These spectacular photographs could have been taken with a commercial strobe—but only with one manufactured a dozen years ago, not with a modern model. Those early models, though fast, were bulky, had high operating voltages and cost plenty.

As strobes developed over the years, size and cost decreased. But, unfortunately, a price was paid for this—flash speeds decreased. Today, ordinary strobes have speeds that range from about 1/1,000 sec. to 1/2,500 sec.

High-speed photography does not require the expensive bulky strobe equipment of yesteryear. The Super-Speed Strobe proves this. Its power pack is 4 x 5 x 6 in. and it is not much heavier than a dozen or so rolls of film. Best of all, its cost is low. Less than \$50 should put it in your hands.

The Circuit. Before we build it, let's take a quick look at the circuit in Figs. 6 and 7. The power supply is a conventional half-wave voltage doubler that furnishes 450 VDC to storage capacitor C2. To achieve the 1/10,000-sec. flash speed, C2 must be a computer-grade electrolytic capacitor. The type specified in our Parts List is not expensive (\$1.12) and you *must not* substitute an ordinary electrolytic for it.

The charge on C2 is applied to the flash-tube through a connecting cable that should not be longer than 10 ft. After power is turned on, capacitor C3 charges to 225 VDC through R1 and the primary of T2. When the shutter contacts close (SO1's or SO3's contacts are shorted),

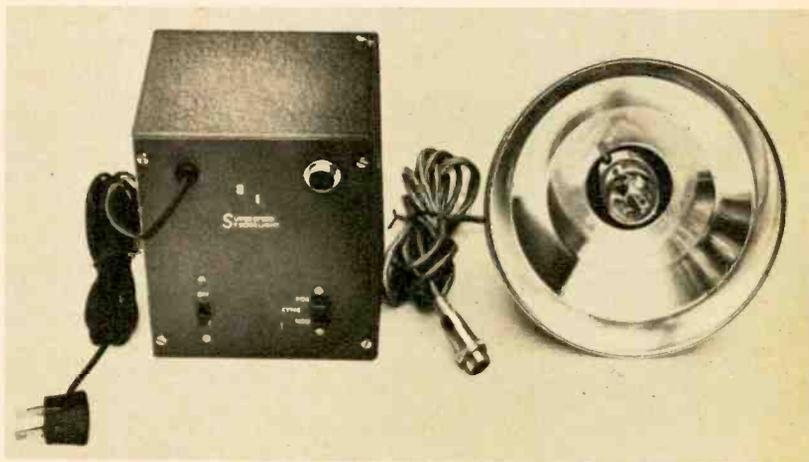


Fig. 1—Strobe consists of 4 x 5 x 6-in. power pack and 6 $\frac{3}{4}$ -in.-dia. flash head. Flash head plugs in socket at top of power pack. Socket below is for sync cable to camera.

SUPER SPEED STROBE

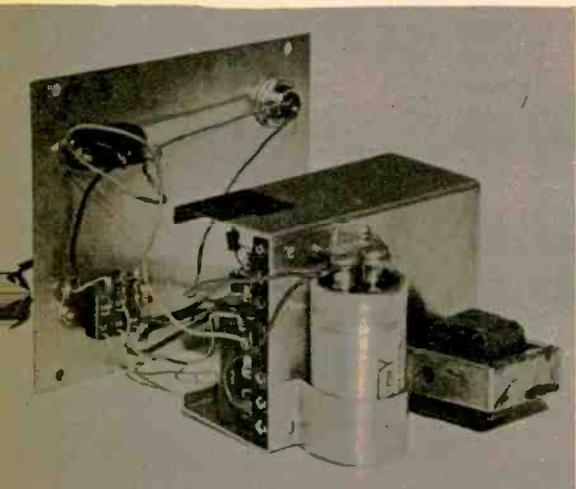


Fig. 2—View of chassis shows how transformer is mounted. Capacitor C2 is held in place with homebrew strap using screws which hold terminal strips. Leads to cover should be at least 6-in. long.

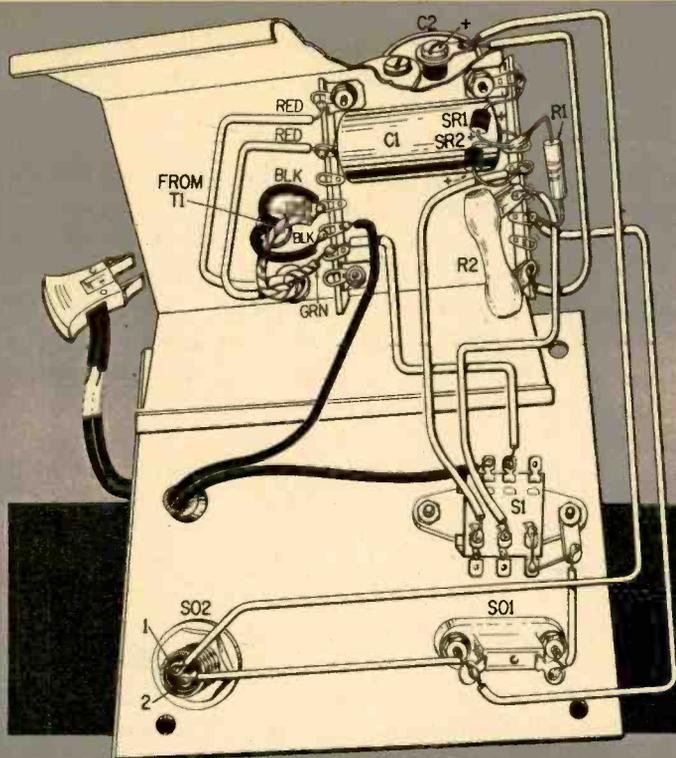


Fig. 3—View of underside of chassis shows wiring to sockets and switch on cabinet cover plate. Negative lug on C2 is connected to chassis with a strap made of scrap aluminum. Before closing cabinet check to make sure lugs on S1 and S01 don't touch edge of chassis.

C3 discharges through T2's primary, causing T2 to produce a 3-kv pulse. This pulse is applied to the flashtube and fires it.

Resistors R3 and R4 (Fig. 6) are a voltage divider for the neon ready-light (NL1). Capacitor C4 causes NL1 to blink, indicating the unit is ready to fire again. The lower C4's capacitance, the faster the blink rate. C2's recharge time and the time it takes NL1 to start blinking after a flash normally are under three seconds.

Construction. Start off with the power supply, which is built on a 2 x 4½ x 3½-in. aluminum chassis as shown in Figs. 2 and 3. Mount transformer T1 and connect its leads but *do not* cut or solder them. Apply 117 V to T1's primary and measure voltage across the red secondary leads. Now interchange the connections of the 6.3-V (green) leads and measure the voltage again. If it's higher, solder the leads in place. If the voltage is lower, *reverse* the connections of the green leads and solder them. Now solder T1's other leads.

Next, install C1, R1 and R2. When connecting SR1 and SR2, hold their leads with

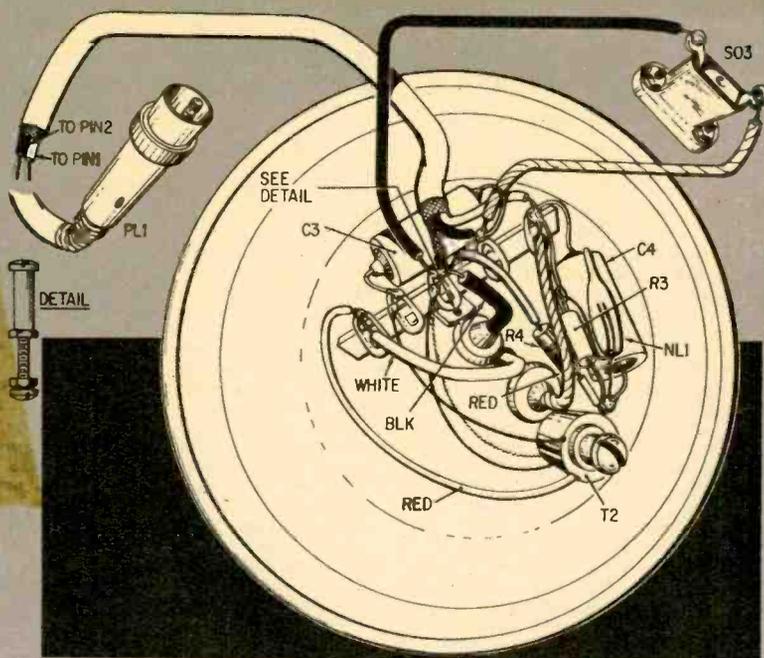


Fig. 4—Back of flash head. Reflector is supplied with holes predrilled for red, white and black leads from flashtube and screws that hold terminal strip and T2. Detail sketch at left shows how a 1/4-in. screw is installed through the reflector to hold the terminal strip and the back cover.

long-nose pliers to prevent heat damage. Mount S1, SO1 and SO2 on one of the box's cover plates and install a grommet for the line cord. Install the line cord then mount C2 (next to T1) on the top of the chassis (Fig. 2) with a homemade clamp. Watch the polarity when connecting C2. After wiring to S1, SO1 and SO2, attach the chassis to the box's other cover plate.

Fit the flashtube's glass lead stems through grommets in the reflector then put two 6-32 x 1-in. long machine screws through the pre-drilled holes (1 3/4-in. centers) in the reflector. Run nuts on both screws then slip T2 on one of the 1-in. screws. Put a terminal strip and nut on the other screw as shown in Fig. 4 and 5. (Use a fiber washer on both sides of T2 so you don't damage its windings.)

When connecting the flashtube's leads to the terminal strip shown in Fig. 4, use care or you'll break its glass stems. Now install R3, R4, C3, C4 and NL1.

Drill holes in the reflector's back cover for the cable and for SO3. Attach PL1 to the cable making sure the 450-V lead goes

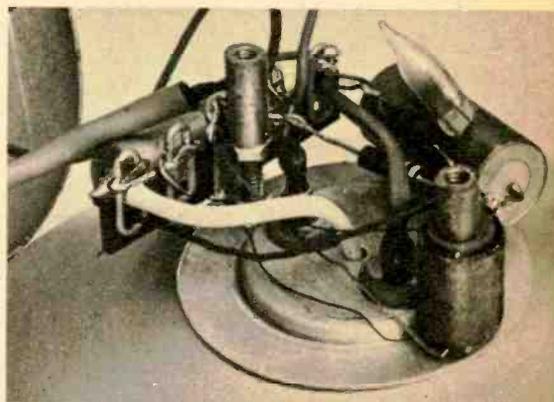


Fig. 5—Back of flash head. Threaded spacer on terminal-strip mounting screw is 3/8 in. long. The threaded spacer that holds T2 is 1/4 in. long.

to pin 1 and the 225-V lead goes to pin 2. Put threaded spacers on the ends of the two 1-in. screws and tighten them so that the rim of cover touches the back of the reflector. Attach the cover with 6-32 x 1/4-in. screws.

Checkout. Plug in the line cord and turn

THE WHITE HOUSE over the years has laid claim to everything from bronco busters (Teddy R.) to waltz wheedlers (Harry T.) but never a dyed-in-the-wool DXer. It doesn't even today, of course, though LBJ does get into the DX act like no previous president. Reason, as most everyone knows, is that Lyndon B. Johnson owns a radio station—or at least Lady Bird does. And with a little effort, DXers in every part of North America should be able to log it.

The station, KTBC at Austin, Texas, actually sports three outlets—AM, FM and TV. Of the three, KTBC-AM probably will be easiest to log. It operates 24 hours a day, seven days a week, on 590 kc. To be sure, there are other 24-hour stations on this same channel, though most go off once a week for maintenance purposes. Thing to do is check early Monday (or possibly Sunday) mornings when such other stations frequently will leave the air for a time. Assuming they do, there's good chance of your picking up KTBC-AM without much trouble.

Unfortunately, KTBC-TV operates on Channel 7 which rules out skip and limits DX reception to the trop mode—in other words, to a maximum of about 500 miles, depending on your equipment. If KTBC does appear on your TV set, you also should give a listen for their potent FM signal on 93.7 mc. This procedure will work in reverse as well, of course (though KTBC-FM occasionally will make it on skip when the TV channel displays nothing but snow).

Nicest thing about the KTBC stations is the fact that all are excellent verifiers. Correct reports are answered on an attractive letterhead that makes a fine addition to any QSL collection. Mailing address for all three stations simply is P.O. Box 1155, Austin, Tex.


—Alex Bower

PRESIDENTIAL DX

Located in the heart of downtown Austin, Tex., stations KTBC-AM/FM/TV commonly are known as the Johnson stations after the name of the family that owns them. The President's family also holds interest in a number of other stations, including KLFY-TV in Lafayette, La.



Wide World

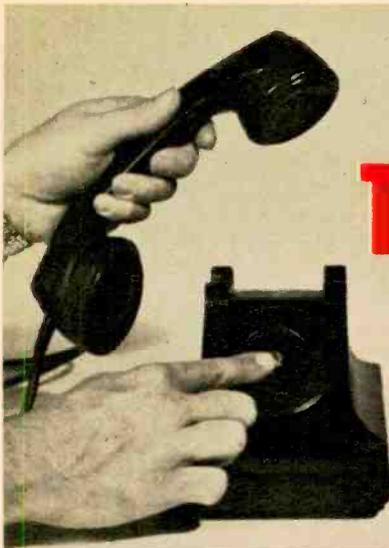

The Phonecom

**An intercom for only \$5 a station?
Right, and every unit is a master
from which you can call all others.**

By LAWRENCE GLENN

LIKE the chap who got a real bargain when he bought a pair of \$1,000 elephants for only \$500, you'd be hard pressed to find a better buy than the no-guts telephones that are now available for around \$8.50 a pair. Only problem is—like the gent with the elephants—what do you do with them after you get them home?

Though they come with handset, cradle and wiring, the phones can do absolutely nothing as they are because they have no bell and no repeat coil, not to mention a few other deficiencies. But for \$1 or so you can make these white elephants into useful telephone intercoms—complete with signals and multi-station convenience (phones are connected in parallel so additional units do not require rewiring the complete system).

The Modification

To convert the basic phone into something useful cut the red wire from the telephone's handset at the terminal strip in the base where it connects to the red output wire. (Virtually all phones in surplus have the same wiring and color-coding.) Then connect a normally-open push-button switch and a 1½-V buzzer across the lugs to which the yellow and green leads connect as shown in the schematic at the right.


S1 is a miniature push-button switch mounted in the center of the dial-hole cover. Don't worry about drilling the case. There is a small knock-out plug in the center of the cover that exposes a pilot hole which

you simply drill larger. If your phone doesn't have the pilot hole, center-punch the cover before drilling or you might crack it.

The buzzer is the sound unit from a one-cell bicycle horn; it can be mounted anywhere on the bottom plate. Both switch and buzzer are connected directly to the screw terminal strip on the phone base. Don't try to cut into the existing phone wires because they are a special cord-wound wire that won't take solder.

The cradle switch shown in our schematic is part of the telephone. Do not remove it and don't disconnect the wiring to it since it is used to disconnect the power supply when the handset is on the hook.

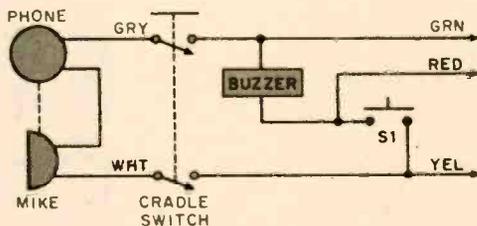
The power supply consists of a 6-V battery in series with the secondary (used as a choke) of a 6.3-V filament transformer (T1). To avoid getting a shock from the kick-back voltage when the buzzer sounds, cut off the black primary leads at T1's case. Do not



Basic telephone modified for intercom. In original unit you must remove red wire from lead connecting phone and mike to the red output wire.



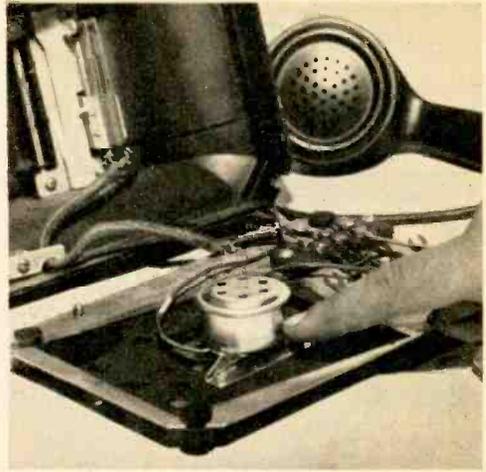Power supply consists of 6-V battery in series with filament transformer's secondary. Mount transformer as shown to change battery easily.




Best place to install the buzzer is inside the telephone on the base. Buzzer is sound unit that is removed from an inexpensive bicycle horn.

eliminate T1 because the system's audio signal is developed across it. If T1 is not used the battery's low internal impedance will short the signal.

Hooking Them Up

The modified phones are connected as shown below. Use a 3-wire cable and connect the matching color-coded wires from one phone to the other. The power supply connects to the yellow and green wires; battery polarity doesn't matter. Additional phones are connected to the system simply by hooking their output cables to the main cable or the nearest phone. Be sure to connect like colors. You can simply keep adding phones until the power supply no longer is able to deliver enough current to sound the buzzers.

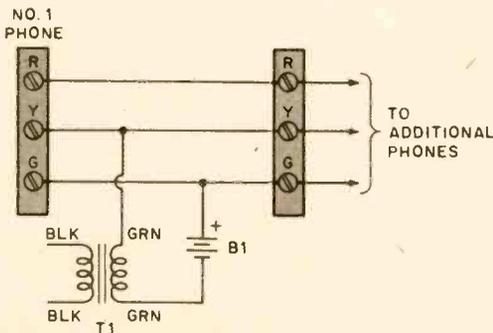

External power supply consists of a battery in series with a choke (secondary of filament transformer). Connect all telephones in parallel.

Operation

The buzzers and the speaking circuit are in parallel. Depressing the button on any phone will cause all buzzers to sound. Anyone can then join the conversation by picking up the nearest handset.

If you use more than two phones, a coded-ringing system can be used for signaling. That is, one ring means the call is for phone No. 1; two rings would mean phone No. 2, etc.

B1 is a heavy-duty battery such as an Eveready 510S. If you don't want to use this type, use four standard D cells wired in series. The batteries and the transformer can be located at any convenient out-of-the-way spot near the connecting cable.

The important thing to remember is that the handset should not be lifted while you press the buzzer. If one of the phones is to be used in an area where there is a lot of noise (such as the basement workshop or garage) install a 6-V pilot lamp in the phone to provide a visual signal. Merely connect the lamp in parallel with the buzzer.

PARTS LIST

- B1—6 V battery (Eveready 510S or equiv.)
- S1—Miniature normally-open push-button switch
- T1—6.3 V filament transformer (Lafayette 33 R 3702)
- Misc.—Telephones (Lafayette 44 R 6501), buzzer from bicycle horn.

You can earn more money if you have an FCC License

FCC Form 700 A

The United States of America

NUMBER
P1-20-6490

FEDERAL COMMUNICATIONS COMMISSION

RADIO TELEPHONE OPERATOR LICENSE

FIRST CLASS
(General Radiotelephone Certificate)

This certifies that TOMMY WILLIS DUFFY

IS A LICENSED RADIO OPERATOR, AUTHORIZED, SUBJECT TO ANY SPECIAL ENDORSEMENT PLACED HEREON, TO OPERATE THE CLASS OF LICENSED RADIO STATIONS FOR WHICH THIS CLASS OF LICENSE IS VALID UNDER THE ORDERS, RULES AND REGULATIONS OF THE FEDERAL COMMUNICATIONS COMMISSION, ANY STATUTE OF THE UNITED STATES AND ANY TREATY TO WHICH THE UNITED STATES IS A PARTY.

THIS LICENSE IS GRANTED UNDER THE AUTHORITY OF THE COMMUNICATIONS ACT OF 1934 AND THE TERMS AND CONDITIONS THEREOF AND OF ALL LEGISLATIVE ACTS, EXECUTIVE ORDERS AND TREATIES TO WHICH THE UNITED STATES IS SIGNATORY, AND ALL ORDERS, RULES AND REGULATIONS OF THE FEDERAL COMMUNICATIONS COMMISSION, WHICH ARE APPLICABLE TO RADIO OPERATORS, ARE MADE A PART HEREOF AS THOUGH SPECIFICALLY SET OUT IN FULL HEREIN.

NEITHER THIS LICENSE NOR THE RIGHTS DERIVED THEREFROM SHALL BE ASSIGNED OR OTHERWISE TRANSFERRED TO ANY OTHER PERSON.

PLACE AND DATE OF ISSUANCE: BUFFALO, NEW YORK SEPTEMBER 11, 1963

DATE AND TIME OF EXPIRATION: SEPTEMBER 11, 1968 AT THREE O'CLOCK A. M., EASTERN STANDARD TIME.

SPECIAL ENDORSEMENT: SHIP RADAR ENDORSEMENT - SEPTEMBER 11, 1963 - BUFFALO, NEW YORK



[Signature]
ISSUING OFFICER

Federal Communications Commission

Tommy Willis Duffy (Licensee) *[Signature]* (Issuing Officer) *Don J. Waples* (Secretary)

NOT VALID UNTIL SIGNED

Employers are paying good money for men holding FCC tickets. Read how to get yours:

When you hold a Commercial License issued by the FCC (Federal Communications Commission) you have written proof that you know and understand basic electronic theory and fundamentals. It's worth plenty . . . particularly to companies on the lookout for qualified electronics technicians. Here's how one of the country's leading office machine manufacturers rates men with FCC Licenses:

"An FCC License is an asset to any man looking to enhance his career in the field of electronics. At our Company, a licensed man is well-rewarded because an FCC License attests to his knowledge of electronics theory . . ."

Thousands of employers will tell you the same thing. Licensed men get the good jobs. They make more money . . . move ahead faster . . . enjoy exciting,

challenging work. What's more, they're needed badly in every field of electronics. Industrial electronics. Radio-TV Broadcasting. Aerospace. Electronics Servicing . . . including mobile and marine radio *plus* CB.

Yes . . . your opportunities are unlimited once you're carrying that FCC Commercial Ticket. AND CLEVELAND INSTITUTE OF ELECTRONICS CAN GET ONE FOR YOU! On the facing page, read how four ambitious men just like you have cashed in on CIE's sure-fire FCC Licensing Program. Read about CIE's exclusive money-back offer. And then send in the postage paid reply card. CIE will quickly send you complete FREE information. You will soon be on *your* way to a Commercial FCC License and the many rewards that go with it!

These CIE men have good jobs (they have Commercial FCC Licenses)



Matt Stuczynski, Senior Transmitter Operator, Radio Station WBOE. "I give Cleveland Institute credit for my First Class Commercial FCC License. Even though I had only 6 weeks of high school algebra, CIE's AUTO-PROGRAMMING teaching method makes electronics theory and fundamentals easy. After completing the CIE course, I took and passed the 1st Class Exam. I now have a good job in studio operation, transmitting, proof of performance, equipment servicing. Believe me, CIE lives up to its promises!"



Ted Barger, Electronic Technician, Smith Electronics Co. "I've been interested in electronics ever since I started operating my own Ham rig (K8ANF). But now I've turned a hobby into a real interesting career. Cleveland Institute of Electronics prepared me for my Commercial FCC License exam . . . and I passed it on the first try. I'm now designing, building and testing all kinds of electronic equipment . . . do a lot of traveling, too. It's a great job . . . and thanks to CIE and my FCC License, I'm on my way up."



Chuck Hawkins, Chief Radio Technician, Division 12, Ohio Dept. of Highways. "Cleveland Institute Training enabled me to pass both the 2nd and 1st Class License Exams on my first attempt . . . even though I'd had no other electronics training. (Many of the others who took the exam with me were trying to pass for the eighth or ninth time!) I'm now in charge of Division Communications and we service 119 mobile units and six base stations. It's an interesting, challenging and extremely rewarding job. And incidentally, I got it through CIE's Job Placement Service . . . a free lifetime service for CIE graduates."



Glenn Horning, Local Equipment Supervisor, Western Reserve Telephone Company (subsidiary of Mid-Continent Telephone Company). "There's no doubt about it. I owe my 2nd Class FCC License to Cleveland Institute. Their FCC License Program really teaches you theory and fundamentals and is particularly strong on transistors, mobile radio, troubleshooting and math. Do I use this knowledge? You bet. We're installing more sophisticated electronic gear all the time and what I learned from CIE sure helps. Our Company has 10 other men enrolled with CIE and take my word for it, it's going to help every one of them just like it helped me."

FCC LICENSE WARRANTY

A CIE FCC License Course will quickly prepare you for a Commercial FCC License. If you don't pass the FCC exam . . . on the first try . . . after completing your course, CIE will refund all your tuition. You get an FCC License . . . or your money back!

Two out three men who took the 1st Class Commercial FCC License exam in 1964, failed.

Nine out of ten CIE-TRAINED men who take this exam, pass . . . the very first try!

And that's why CIE can back their courses with the warranty you see at the left. CIE-trained men know their stuff . . . because CIE AUTO-PROGRAMMED Home Study works!

Get started now. Send postage-paid reply card for free information about a plan that gets you an FCC License *or costs you nothing!*

CIE

Cleveland Institute of Electronics

1776 East 17th Street, Dept EI-62, Cleveland, Ohio 44114



THE HAM SHACK

BY ROBERT
HERTZBERG
W2DJJ

PERPLEXER . . . On a visit to Italy a friend of ours bought an unusual gold-plated microphone with the hope it would make a good conversation piece (no pun intended) for his shack. But when he got it home and hooked it up, the transmitter refused to respond. After much head-scratching

he finally made an interesting discovery.

Having been sold in Milan, the mike naturally had Italian markings. Near the control switch were two small legends, NO and SI. Previously our boy had only glanced at them and unconsciously read NO as ON. Then he remembered that SI in Italian means yes and NO means no and that SI, therefore, must indicate *on* and NO *off*. He flipped the switch and, of course, the rig came to life immediately.

Doing It Right . . . A ham who performs an important public service during an emergency usually is rewarded with a letter of appreciation from the mayor, governor or other official. But not so with Hector Seda, W2BFH, Brooklyn.

In response to an appeal from a doctor/ham in Maracaibo, Venezuela, W2BFH purchased some anti-rabies serum and arranged to have it flown down in a hurry. It arrived in time to save the life of a 9-year-old boy who had been bitten by a rat.

W2BFH's reward from the grateful family? An all-expense-paid trip to South America for himself, his wife and his four children.

Hector learned to pound brass in the Air Corps during World War II and got his ticket soon afterward. Needless to say, the ham fraternity is proud to count him as a member.

Pin-Up, New Style . . . For years we've wrestled with the problem of mounting QSL cards. Thumb tacks, staples, Scotch tape, rubber cement, library paste—each has ruined the walls of several shacks, though none seems ideal. What is? Answer may lie in the Plastic Pockets made by John B. Thomas, K4NMT, Box 198, Gallatin, Tenn. (see our photo).

A single push-pin or thin brad is all that's


needed to hang a pocket of 20 individual but connected transparent sleeves, arranged in two vertical rows. Cards can be inserted or removed in half a second. Better yet, they stay clean and you simply pin up additional pockets as the collection of QSLs grows. (You also can fold them up and take them to club meetings to show how much DX you've worked, all without damage to either pockets or cards.) Three of the pockets, enough for 60 cards, cost a buck.

It's Official . . . As long expected, the FCC has stretched the distance minimum for the Conditional Class license from 75 to 175 miles. Net effect is practically to eliminate the Conditional as a mail-order ticket since the Commission's examining points now cover all but the remotest corners of the 50 states. Still eligible for all the Conditional offers, however, are physically disabled people and members of the armed forces.

Novice Notice . . . Most hams know that the Novice license is good for only one year and cannot be renewed. Thing is, many are not aware that it is unavailable to anyone who ever has held a ham ticket of any kind and let it expire. Obviously, any ham about to give a Novice test should be certain to question the applicant closely on this point.



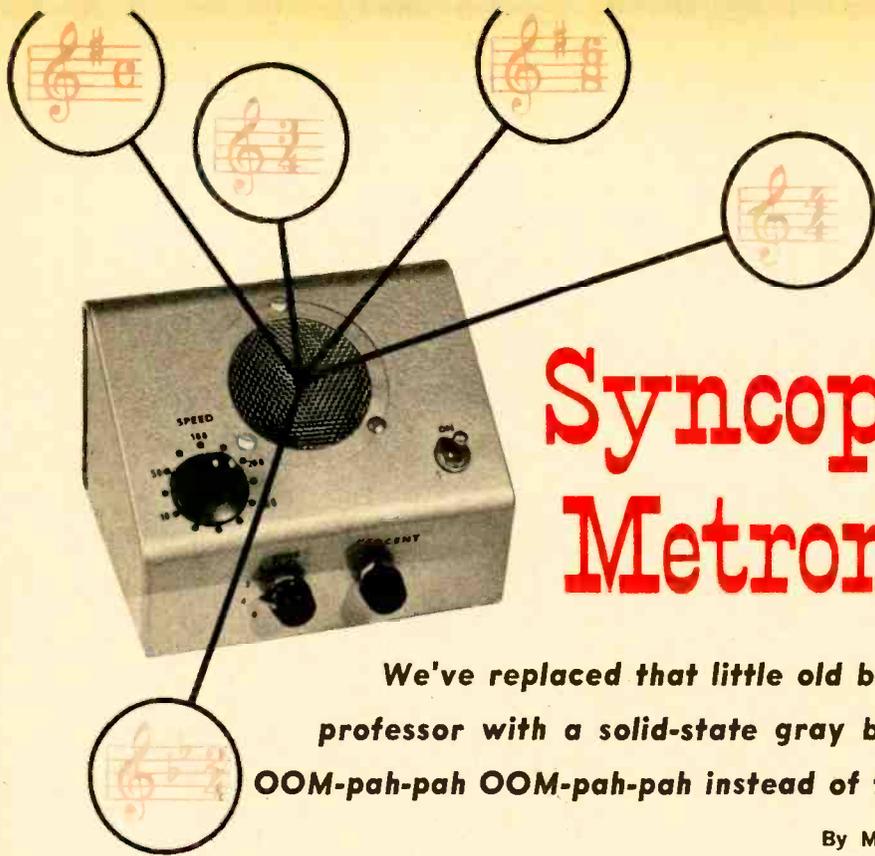QSLs are displayed neatly and conveniently in Plastic Pockets available from K4NMT. Each holds 20 cards, can be supported by a single push-pin.



The Syncopated Metronome

We've replaced that little old bearded music professor with a solid-state gray box that goes **OOM-pah-pah OOM-pah-pah** instead of tick tick tick!

By MORRIS GROSSMAN

FINGERS on the correct keys? What are the sharps or flats? Am I holding my hands properly? What notes come next? When do I hit the pedal? Ready? Now start playing and watch the timing. With all these things on your mind in the early months of music lessons you begin to feel you won't be past chopsticks after a year of practice.

There are no shortcuts to learning to play a musical instrument. It takes plenty of disciplined practice. But one thing—timing—can be developed quickly with a metronome. However, the ordinary kind that just ticks isn't enough. Reason is, this kind merely helps build up speed and gives an evenness to your playing.

In all music, a specific beat in a measure is accentuated. For example, when you think of or play a waltz, you usually count to yourself, **ONE two three, ONE two three**, and so on. Or, the rhythm could be **ONE two three four, ONE two three four**. In both examples you must add a little emphasis to that first beat—**ONE**.

And this is what the Syncopated Metronome does. It relieves you of the chore of counting and accenting. Just set it for the

speed you want (its range is about 10 to 300 beats per minute), set its *time* control for the time of the music (2/4, 3/4, 4/4, 6/8, 9/8) and you're free to concentrate on other things. While you take care of the keys, sharps and fingering, the metronome sits there setting the pace—**ONE two three, ONE two three, ONE two three**. It can almost play a tune itself. Fig. 2. shows the relative amplitude of its output pulses or tick sounds. The vertical bars in color are additional emphasis for 6/8 and 9/8 time.

In fact, it could be used to help dance students keep time. The rhythmic beats and accents also could be helpful in learning typing, doing exercises, lulling you to sleep, keeping you awake, providing inspiration for composing music and acting as an audible timer. Besides all that, it's a mighty interesting electronics project for the experimenter. To the best of our knowledge there is no similar product on the market. All metronomes we have unearthed just go tick tick tick. So if you're fast with the tools you may be the second person in the world to own a Syncopated Metronome (the author modestly claims to be owner No. 1).

Metronome


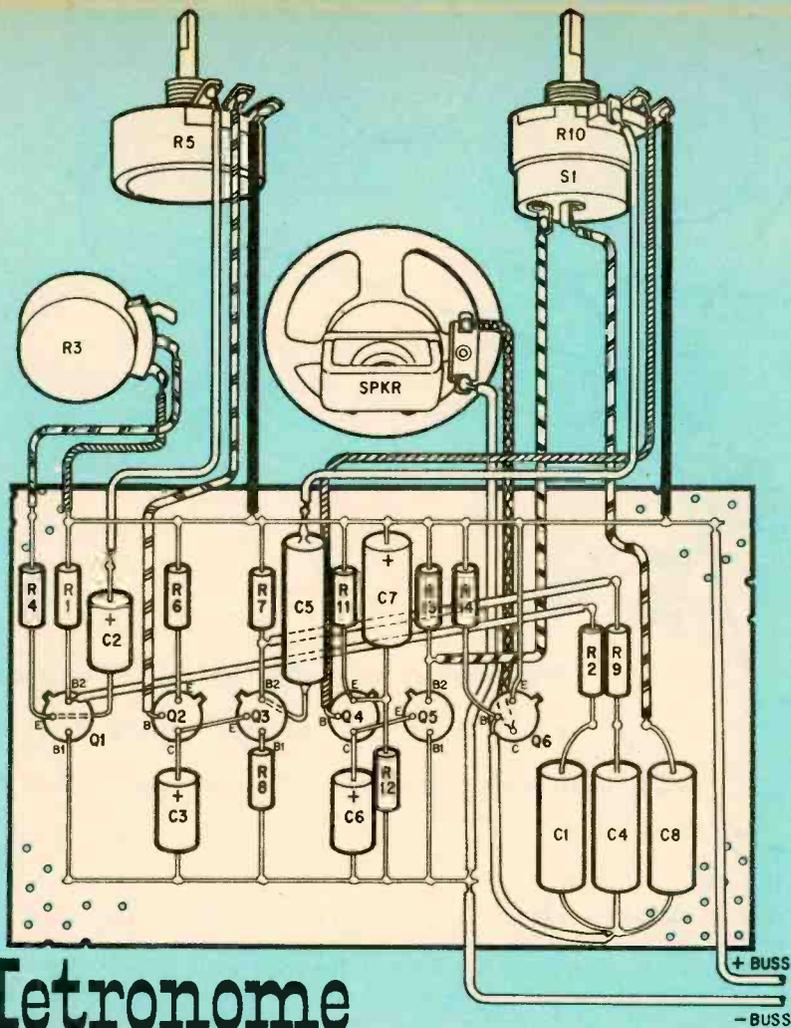


Fig. 1—Mount components on perforated board as shown above and run long leads to R3, R5, Spkr, R10 and S1. Leads to R2, R9 go under board. Mount board in U-section of cabinet as shown below. Toggle switch, upper right of photo, turns unit on.

Construction

The complete unit fits neatly in a $4\frac{1}{4} \times 6 \times 4$ -in. meter case. The circuit is built on a $3\frac{3}{4} \times 5\frac{1}{2}$ -in. piece of perforated board. Most components are installed on the board and can be mounted either with flea clips or by bending their leads on the underside of the board. Interconnecting wires and parts' leads can then be soldered to each other. In most cases the component lead alone is sufficient to connect to its mating part. Very little extra hook-up wire is required. It is important that R3 have a reverse logarithmic taper, as specified in our Parts List, in order to spread out the markings on the *speed* dial.

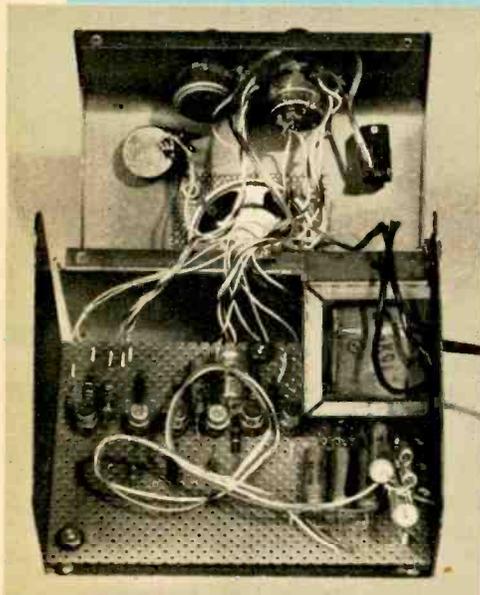

The power supply can be built on the side of the case as shown in Figs. 1 and 3. The opening in the case intended for a meter accommodates the speaker perfectly. Use a piece of copper screen to protect the speaker cone and use three solder lugs to hold it in place. We used a 100-ohm speaker to eliminate an output transformer.

Mount all controls and switches on the front of the cabinet and make sure the leads to them are long. Should repairs be necessary, this will allow the component board to be completely removed from the cabinet without the need to unsolder wires.

Although the dress of the leads and component arrangement is not critical, the layout shown should be followed closely to avoid mechanical problems when the cabinet is finally assembled.

Calibration

The metronome can be calibrated by ear if you have a good sense of time; however, careful calibration of the *speed*, *time* and *accentuate* dials is desirable. The most important ingredients required for calibration are a watch with a sweep-second hand and

Fig. 2—Diagram shows number of beats in a measure for several times. The accentuated beats are determined by setting of R5. Close switch S1 and adjust R10 and you will get additional emphasis (pulses shown in color) for 6/8 and 9/8 time.


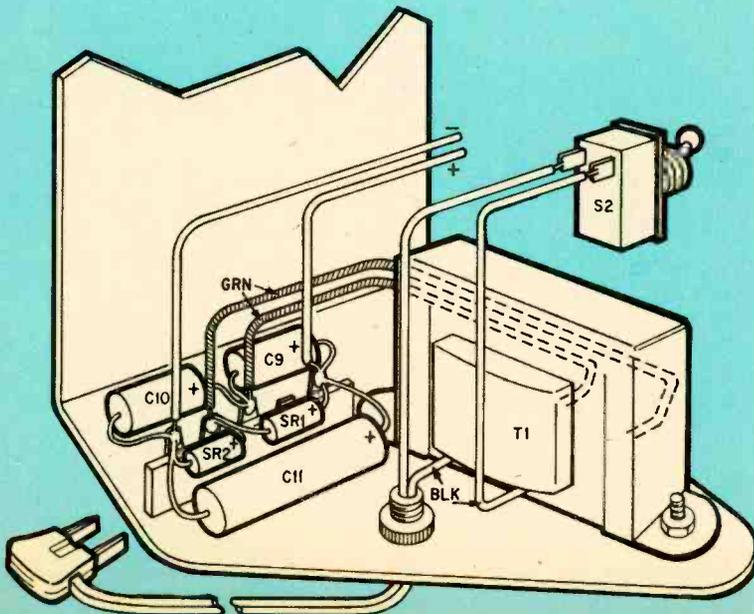
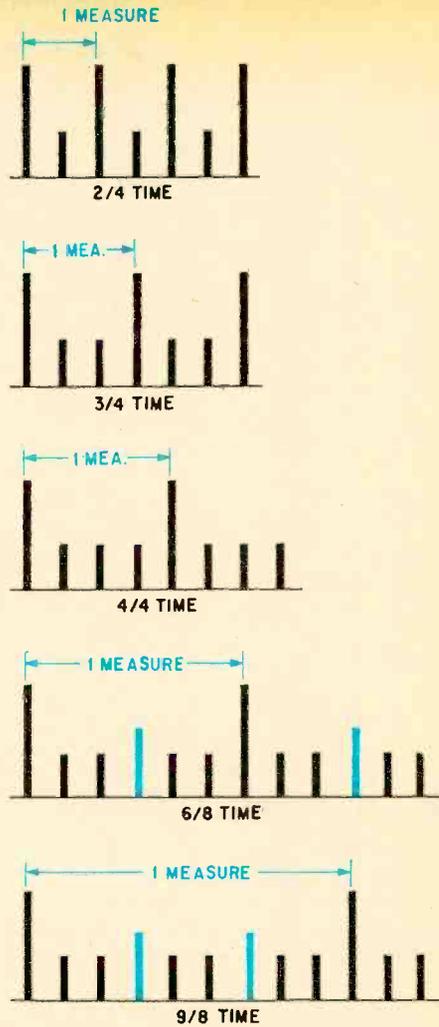


Fig. 3—Power supply is a simple affair that can be built on side of U-section of cabinet. Mount diodes and capacitors on 6-lug terminal strip and make sure ground lug is not used for a tie point. AC power switch S2 gets mounted in the main section of meter cabinet.

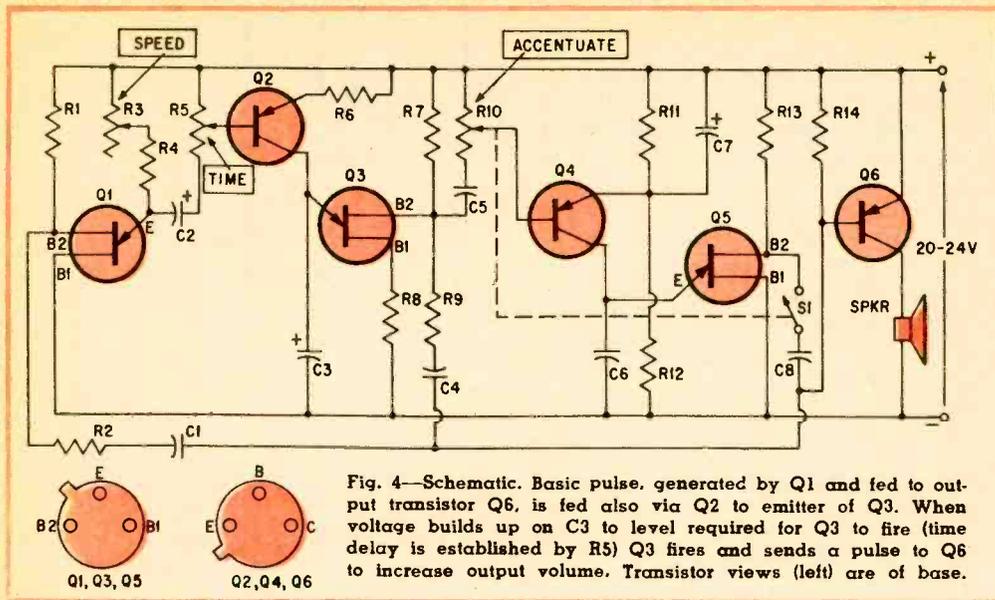

Metronome

a lot of patience.

Set the *speed* pointer anywhere, count the number of beats per minute and mark the dial accordingly. Repeat this for about a dozen places on the dial. Mark these points with a soft marker crayon. Then make the markings permanent with transfer-type numbers and a dab of lacquer.

The *time* dial (R5) is calibrated merely by listening for the emphasized beat. At some point near R5's most clockwise position, every *other* beat will be accentuated (2/4 time). Turning R5 counterclockwise will produce emphasis on every third, fourth, fifth, sixth, and so on, beats. The setting for each of the points is quite broad. The correct spot in each range is where the sound of the accentuated beat is loudest and cleanest. That is, the accentuated beat should not have a crackling sound. A convenient speed of, say, 60 beats-per-minute should be used when calibrating R5's scale.

The dial for *accentuate* control R10 is also calibrated by careful listening. This control and S1 are used to provide a second subordinated accent on, say, the fourth beat of 6/8 or 9/8 time, to visualize this, refer to the two bottom diagrams in Fig. 2. The settings here are somewhat more critical.

PARTS LIST

- C1, C4, C8—.1 μ f, 100 V tubular capacitor
- C2—5 μ f, 25 V electrolytic capacitor
- C3—3 μ f, 50 V electrolytic capacitor (Sprague TE-1302, Lafayette 34 R 8465, or equiv.)
- C5—.47 μ f, 100 V tubular capacitor
- C6—1 μ f, 25 V electrolytic capacitor (Sprague TE-1200, Lafayette 34 R 8506, or equiv.)
- C7—20 μ f, 10 V electrolytic capacitor
- C9, C10—25 μ f, 15 V electrolytic capacitor
- C11—100 μ f, 25 V electrolytic capacitor
- Q1, Q3, Q5—2N2160 unijunction transistor (GE)
- Q2, Q4, Q6—2N404 transistor
- Resistors: 1/2 watt 10% unless otherwise indicated
- R1, R7, R13—330 ohms
- R2—22,000 ohms
- R3—1 megohm, reverse log taper potentiometer (IRC/CTS type Q17-137, Lafayette 33 R 4354)
- R4—33,000 ohms
- R5—50 ohm, wirewound potentiometer (IRC WPK-50 or equiv.)
- R6, R11—100 ohms
- R8—22 ohms
- R9—4,700 ohms
- R10—500 ohm, linear taper potentiometer with SPST switch
- R12—1,000 ohms
- R14—10,000 ohms
- S1—SPST switch on R10
- S2—SPST toggle switch
- SPKR—100 ohm, 2 1/2-in. dia. speaker (Quam 22A06Z100, Allied 59 U 425)
- SR1, SR2—Silicon rectifier; minimum ratings: 100 ma, 50 PIV (RCA 1N3253 or equiv.)
- T1—Filament transformer; secondary: 12.6 V @ 1.5 A (Allied 64 U 136 or equiv.)
- Misc.—4 1/4 x 6 x 4-in. meter cabinet (Bud CMA-1930, Allied 87 Z 583, \$2.40 plus postage. Not listed in catalog), perforated board, knobs, AC line cord.

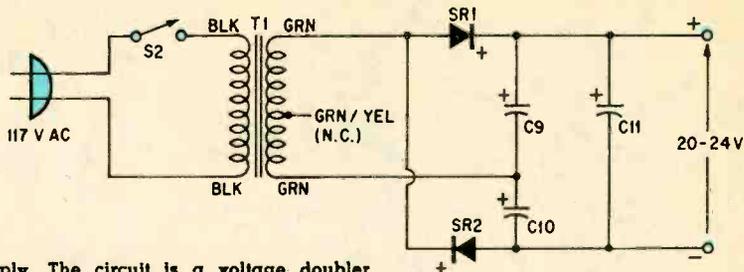


Fig. 5—Power supply. The circuit is a voltage doubler that supplies 20-24 V from a 12.6-V filament transformer.

The exact settings for both the *time* and *accentuate* dials are somewhat dependent upon the setting of the *speed* control and therefore the calibration points are to be considered more as broad guides.

The final setting should always be determined by listening. If R10 is not set properly, the second accentuate pulse may not coincide with the main accent pulse and the sound will be very rough. To correct this merely advance or retard R10 somewhat to pull it into step.

Resistors R2 and R9 affect the relative amplitude of the accentuated and non-accentuated beats. By changing their values you can change the relative amplitudes of the beats.

How it Works

The metronome uses unijunction transistors to provide stable operation. Take a look at the schematic in Fig. 4. Unijunction transistor Q1 is connected as a relaxation oscillator which provides the basic beats. The 1-megohm potentiometer (R3) labeled *speed* provides a speed range of about 10 to 300 beats-per-minute.

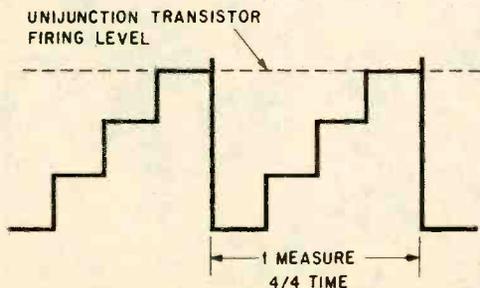


Fig. 6—Q2's collector waveform. When R5 is set for 4/4 time, three pulses charge C3 almost to Q3's firing level. Fourth pulse causes Q3 to fire and produce a pulse that also is fed to Q6.

When the voltage on a unijunction transistor's emitter rises to a particular percentage of the voltage difference between its bases, the transistor conducts, or fires. Until this happens, the impedance between the emitter and base 1 is high.


When power is turned on, Q1 conducts, the impedance between the emitter and base 1 drops to a low value and C2 charges rapidly. As soon as C2 is fully charged, Q1 stops conducting and C2 discharges slowly through resistors R3, R4 and R5. When C2 discharges to the point where Q1's emitter voltage is again at the firing point, Q1 again fires and C2 recharges. This cycle repeats itself continuously at a rate determined by the time constant of C2, and the series combination of R3, R4, and R5.

R4 establishes the maximum speed and R1 determines the lowest speed. Pulses, or spikes, of current, produced by the charging and discharging of C2, are fed via R2 and C1 to output transistor Q6. They produce unaccented ticks.

• **The Time Control.** Pulses of current caused by the charging and discharging of C2 also are fed to *time* potentiometer R5. This control establishes which beat will be accentuated by varying the amount of voltage of a pulse that is fed to the base of Q2 and subsequently the emitter of Q3—a staircase counter.

In other words, R5 determines the amount of charge that will be built up on capacitor C3 for each pulse produced by Q1. Depending on the setting of R5, 2, 3, 4, 5, or 6 pulses from Q1 will be required to charge C3 to Q3's firing level. This is shown in Fig. 6. When the voltage on C3 exceeds the firing point of Q3, Q3 fires and its output pulse together with the output of Q1 are fed to out-

[Continued on page 98]

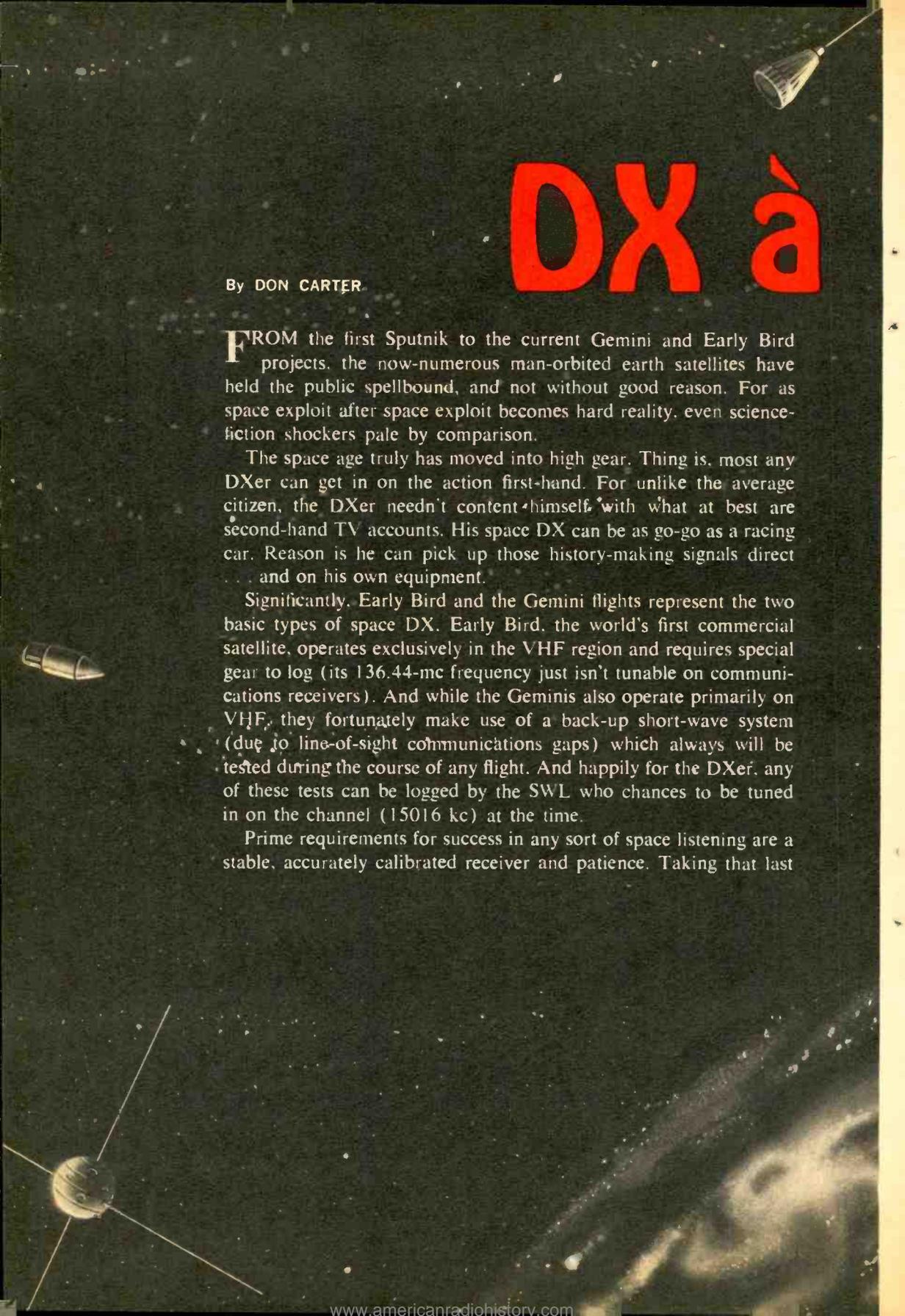

DX à

By DON CARTER

FROM the first Sputnik to the current Gemini and Early Bird projects, the now-numerous man-orbited earth satellites have held the public spellbound, and not without good reason. For as space exploit after space exploit becomes hard reality, even science-fiction shockers pale by comparison.

The space age truly has moved into high gear. Thing is, most any DXer can get in on the action first-hand. For unlike the average citizen, the DXer needn't content himself with what at best are second-hand TV accounts. His space DX can be as go-go as a racing car. Reason is he can pick up those history-making signals direct and on his own equipment.

Significantly, Early Bird and the Gemini flights represent the two basic types of space DX. Early Bird, the world's first commercial satellite, operates exclusively in the VHF region and requires special gear to log (its 136.44-mc frequency just isn't tunable on communications receivers). And while the Geminis also operate primarily on VHF, they fortunately make use of a back-up short-wave system (due to line-of-sight communications gaps) which always will be tested during the course of any flight. And happily for the DXer, any of these tests can be logged by the SWL who chances to be tuned in on the channel (15016 kc) at the time.

Prime requirements for success in any sort of space listening are a stable, accurately calibrated receiver and patience. Taking that last


gO-gO



first, most space DX hunts involve knowing the frequency in advance and simply sitting it out until something happens. Assuming your goal is to log one of the Gemini flights, your only out is to tune to 15016 kc, settle comfortably in your chair and wait. Or, taking another example, most Russian SW space activity takes place within 5 kc of 20000 kc (the actual band in this instance is 19990-20010 kc). If you were looking for Soviet cosmonauts (the so-called Voskhod flights use standard SW frequencies more extensively than their U.S. counterparts), you'd locate the 20000-kc spot, tune ever so slightly below it and keep listening. It all sounds alarmingly simple so far, and it is. Fact is, it's so simple the DXer well may fall asleep! (How's *your* staying power?)

Locating the exact frequency on which to listen understandably requires extra-fine receiver calibration. You, of course, could tune for WWV's 20-mc signal (15 mc for Gemini) and extrapolate from there. But a far better bet is to add a crystal frequency marker—unless your receiver already is blessed with one of these helpful little gadgets. There are several outboard units on the market: the Bud FCC-90B, typical of the lot, runs about \$20, has its own built-in power supply and, once connected to your receiver, provides a marker signal every 100 kc along the dial.

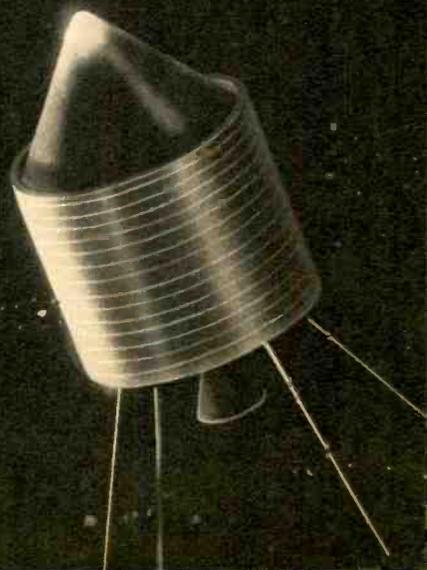Naturally, there is little you can do about stability: your receiver either has it or it doesn't. But regardless of what your set offers in



DX à go-go

this regard, it always should be well warmed up. If it still drifts even after adequate warm-up (say 30 minutes to an hour), you simply will have to tune back to the marker periodically. In this sense, the marker can be said to be partial compensation for a receiver with a liking to creep, though there clearly can be no substitute for stability.


So far we have mentioned only the Gemini and Voskhod flights. But there are numerous other satellites transmitting around 20000 kc. The Russians lay claim to the bulk, though our Explorer 22 and Italy's San Marco also are to be found in this general area. Catch is, the presence of numerous space signals (some coming from secret, unlisted sources) make foolproof identification of a particular signal highly hazardous.

However, a satellite usually will be heard on two or more consecutive orbits. Thus, if Explorer 22 is heard at 1800 after a prolonged monitoring period, it again should be heard 105 minutes later, i.e., at 1945. Reason, of course, is that this particular satellite's orbit period is 105 minutes, as our chart reveals.

On the other hand, if that signal does not appear again until 2049, you could be reasonably certain it is not Explorer 22. Instead, it presumably would be a Soviet vehicle, possibly Elektron 1, which at last report was transmitting on this same general frequency (20005 kc) and had an orbit period of 169 minutes. Or given a different time of reappearance, it might be the San Marco (orbit period: 94 minutes).

Aid in identifying a specific Voskhod flight frequently can be gained from newspapers, TV or radio, since all publicize orbit periods. Needless to say, there's little point in attempting to log a satellite without foreknowledge of its orbit period, since you otherwise would not know when to listen.

Not to be overlooked is the fact that space reception even at 20 mc sometimes can occur via skip. In other words, the signal first reaches the ground at some distant point, then is bounced to the ionosphere, goes around the earth's curvature and comes down to your receiver. Instances of skip at this frequency ordinarily are no more rare than on the 16- or 13-meter SWBC bands. And when skip does occur, signals from the

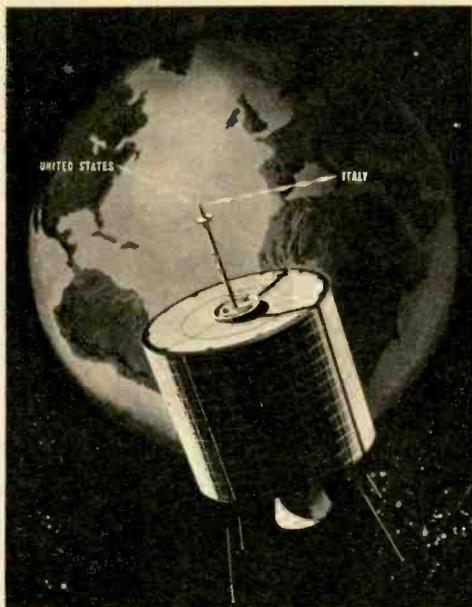

Early Bird, world's first commercial communications satellite, plays prime role in intercontinental TV. It transmits on a frequency of 136.44 mc.

satellites can show up in weird locations (as can signals from most any source). But despite this complication, the orbit period method of identification still is pretty good and certainly is as foolproof as any.

Should reception from what is presumed to be a satellite last more than 14 minutes, chances are that the station concerned is a perfectly ordinary utility broadcaster—radio-teletype, telephone (wonder how many times these have been mistaken for a man in space?) or what have you.

Of course, all satellite signals (except that from the synchronous Early Bird) will show Doppler shift—frequencies will get higher as the vehicles are approaching, lower as they are moving away. Such frequency shifts normally can be detected through use of a BFO, though a receiver that drifts even slightly can fool you.

When it comes to the VHF side of things, DXing the satellites becomes all the more exciting, though all the more difficult. One of the prime requirements for ordinary SW space DX is a stable receiver. But on VHF (where satellites are considerably more plentiful) the prime requirement is any receiver at all! And since rigs tuning 136 to 137 mc (the major U.S. space band) are scarce, a converter ordinarily is called for.

As is the case with crystal frequency markers, there are several suitable converters on the market. One principal manufacturer is the Ameco Equipment Corp. of Mineola, N.Y., which produces a variety of units. Its model CN-144W Nuvistor converter, designed to cover the 2-meter ham band, will be supplied for 136-mc use if this is specified at time of ordering. (It also is necessary to state make and model number of your receiver.) This unit, incidentally, sells for \$49.95 wired, \$34.95 in kit form.

Still another unit is the AOR-C1 converter (\$47) by the International Crystal Manufacturing Co. of Oklahoma City, Okla. Suitable for use with most any communications receiver, it tunes a 200-kc range and provides an output of 10700 kc. Needless to say, the better your basic receiver, the better your AOR-C1 will work.

Reception and identification of VHF space vehicles differ little from the standard SW variety and the same rules pretty well apply. For the most part, there'll be no skip to complicate things. However, satellites again can be distinguished from other broadcasters by the intermittent nature of their transmissions—intermittent in the sense that they will be heard only during a portion of the orbit period.



Of course, famed Early Bird differs from all other satellites in that it's stationary. You'll either hear it or you won't, depending on your location, receiver and antenna. However, the ionosphere has been known to play the tantalizer even at these frequencies, so it's best not to give up at first or second try. Then, too, variations in fringe-area reception of this satellite might make an interesting tale in themselves.

EI'S GUIDE TO OUTER SPACE

FREQ. (mc)	SATELLITE OR SERVICE	ORBIT (min.)	FREQ. (mc)	SATELLITE OR SERVICE	ORBIT (min.)
8.87A	GEMINI recovery network		136.590	ALOUETTE 1 (U.S. & Britain)	104
15.061	GEMINI capsules and ground communications stations		136.62	RELAY 1	185
15.90A	GEMINI capsules and ground communications stations		136.653	1963-38C	107
16.015	Press corps aboard GEMINI recovery ships working RCA NY (WER46)		136.68	EXPLORER 20	104
19.895	POLYOT 2 (U.S.S.R.)	92	136.712	OGO 2	96.5
19.977A	Soviet manned space flights (voice and CW communications)		136.739	EXPLORER 22	108
20.005	EXPLORER 22	105	136.767	GRAVITY GRADIANT 3	70
	EXPLORER 27	108	137.801	SOLAR RADIATION 2	70
	ELEKTRON 1	169	136.803	EGRS 1	104
30.008	ELEKTRON 1	169	136.842	EGRS 3	70
40.01	EXPLORER 22	105	136.857	EXPLORER 23	99
	EXPLORER 27	108	136.86	EXPLORER 25	116
41.01	same as 40.01		136.886	SOLAR RADIATION 1	104
90.023	COSMOS 44(U.S.S.R.)	100	136.89	PEGASUS 1	97
90.225	ELEKTRON 2(U.S.S.R.)	1356		PEGASUS 2	97
136.02	ECHO 2	109	136.919	TIROS 9	119
136.077	ALOUETTE 1 (U.S. & Canada)	106	136.922	TIROS 7	97
136.08	EXPLORER 23	99	136.924	TIROS 8	99
136.125	EXPLORER 28	8559	136.98	EARLY BIRD	
136.14	RELAY 1	185		SYMCOM 2	1438
136.147	EXPLORER 21	2097		SYMCOM 3	1436
136.17	EXPLORER 22	105	145.85	OSCAR telemetry (amateur-radio satellites)	
	ECHO 2	109	145.95	OSCAR beacons	
136.2	OGO 1	3837	145.9A	OSCAR ham relay	
136.232	TIROS 9	119	150	TRANSIT 4A	104
136.233	TIROS 8	99		1963-49B	107
136.234	TIROS 7	97	162	EXPLORER 22	105
136.292	EXPLORER 25	116		ANNA 1B	108
136.326	EXPLORER 20	104		EXPLORER 27	108
136.35	EXPLORER 20	104	324	ANNA 1B	108
136.406	ARIEL 1 (U.S. & Britain)	101		EXPLORER 27	108
136.41	PEGASUS 1	97		EXPLORER 22	105
	PEGASUS 2	97	360.09	EXPLORER 22	105
136.44	EARLY BIRD			EXPLORER 27	108
136.468	SYMCOM 2	1438	400	TRANSIT 4A	104
136.47	SYMCOM 3	1436		1963-49B	100
136.558	ARIEL 2 (U.S. & Britain)	101		1964-26A	107
			400.25	OGO 1	3837
			400.85	OGO 1	3837

NOTES: Frequencies followed by letter A are approximate. All satellites are U.S. unless otherwise specified.


BIRDLESS BIRD CAGES?—If our photo is any indication, Soviet scientists currently have a peculiar preoccupation with what appear to be uninhabited bird cages. Fact is, this rare look at Ivan's secret antics behind the Iron Curtain actually discloses the ears of a Russian-style radio-telescope installation. Dotted the countryside of the northeastern Ukraine, these antennas are the prized possessions of the radio-astronomy observatory at the Radio Physics Institute of Ukrainian Sciences Academy of Chuguev District, Kharkov Region, U.S.S.R. Hope is that these bird-cage-like structures will gather some of the feeble signals that long have been winging their way across millions of light years of space from radiating stars and nebula. And though the Soviets have yet to reveal just how many celestial birdies they've ensnared, their weird antenna array well may provide answers to riddles which have puzzled man for centuries.

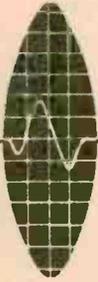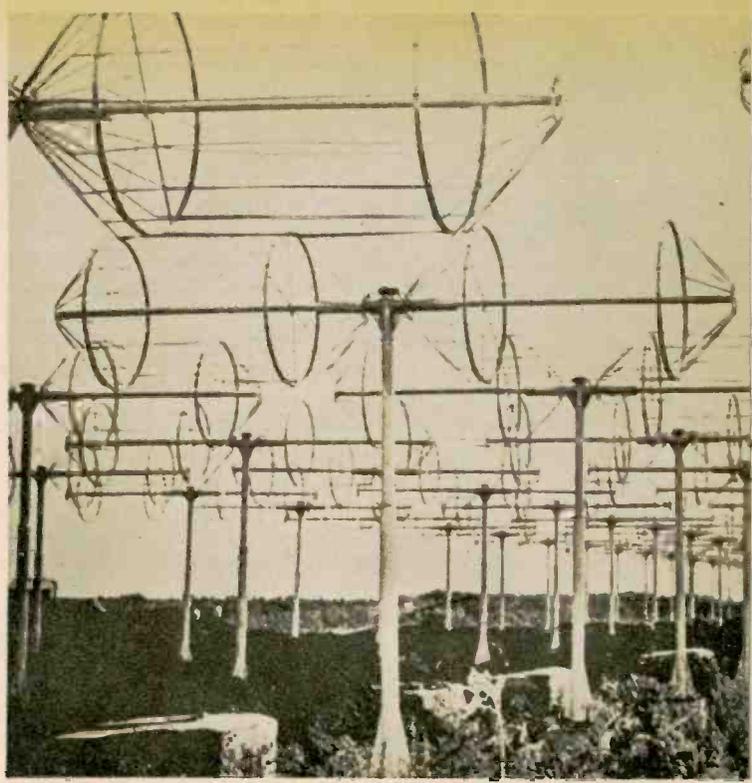


EI Picturescope

LUNAR LANDING SIMULATOR—How do you pick a winner when there are a million horses in the running? Answer is, you don't—unless you take a lesson from scientists and engineers at the Manned Spacecraft Center in Houston, Tex. Reason is the odds in a million-entry horse race are much the same as the ones the people down Houston way are whittling down. Their gigantic task is to reduce the number of sticky wickets a lunar space craft can get itself into at touchdown. Aided by a computer which approximates surface conditions on the moon, the men in our photo simulate lunar landings on a table top while observing and recording the behavior of a scale model of the lunar exploration module's landing gear. Effectively having run their horse race beforehand, scientists will rely on the data collected from these tests to indicate any necessary changes in the landing gear and help compile recommended procedures for the lucky astronaut who pilots the module to the moon.



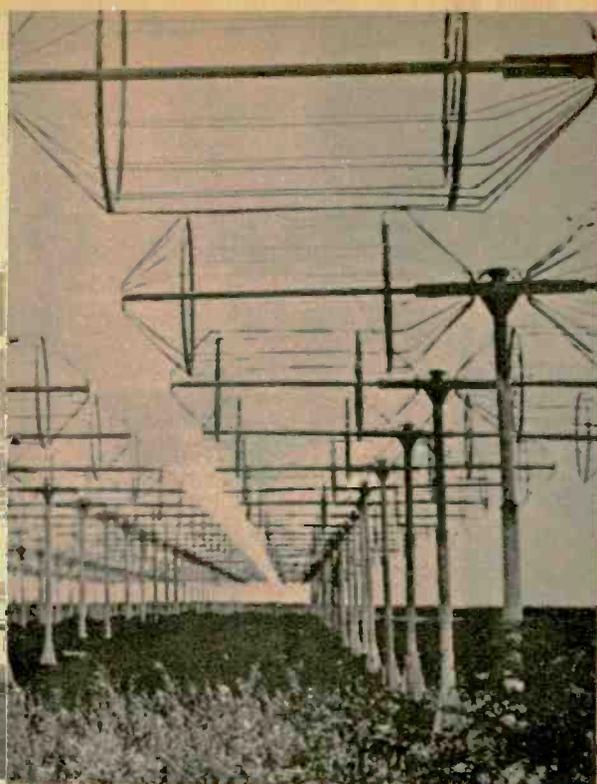


WEATHER WILLING—*Since this is Christmas Eve, I should vote for snow tomorrow; but snow might spoil my hairdo so I'd better vote for a sunny day. What gives? Well, if the people at the Sheaffer Pen Plant, Ft. Madison, Iowa, have their way, willing the weather will be a cinch long about 2065. Plan is to have people cast their ballots on weather-voting machines. Results would be sent to a central computer and then a weatherman, who would oblige the majority.*

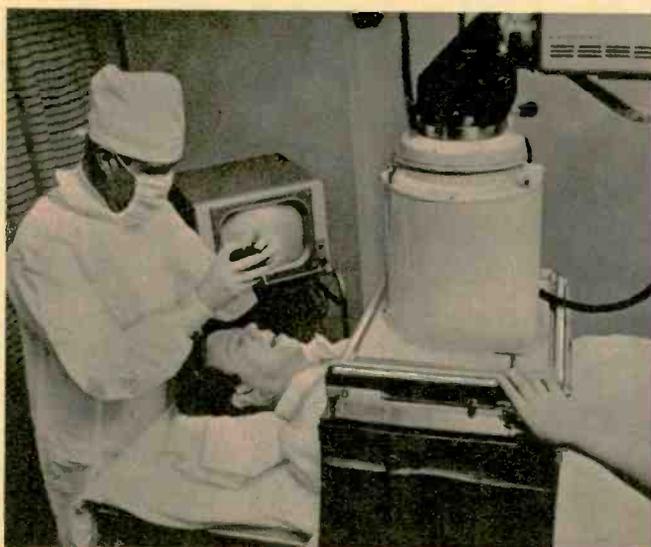

SUPER RAY—*Though the need for color X rays long has existed, none yet has been developed. But a Japanese invention introduced at St. Eriks Hospital in Stockholm, Sweden, will guide doctors to correct diagnoses by providing at least temporary solution to this electronic impasse. Capable of being maneuvered into hard-to-reach locations, the puppet-like device has been found to be particularly useful in identifying causes of stomach ailments. Under the watchful eye of a doctor, the camera, less its hand-held controls, travels down the patient's throat at the tip of a long, flexible tube. When the tip of the tube approaches the vicinity of the stomach, X-ray equipment is called into play to pinpoint the exact locations where pictures are to be taken. All the doctor then need do is shoot his color photograph.*

Six-Bit Meter Saver

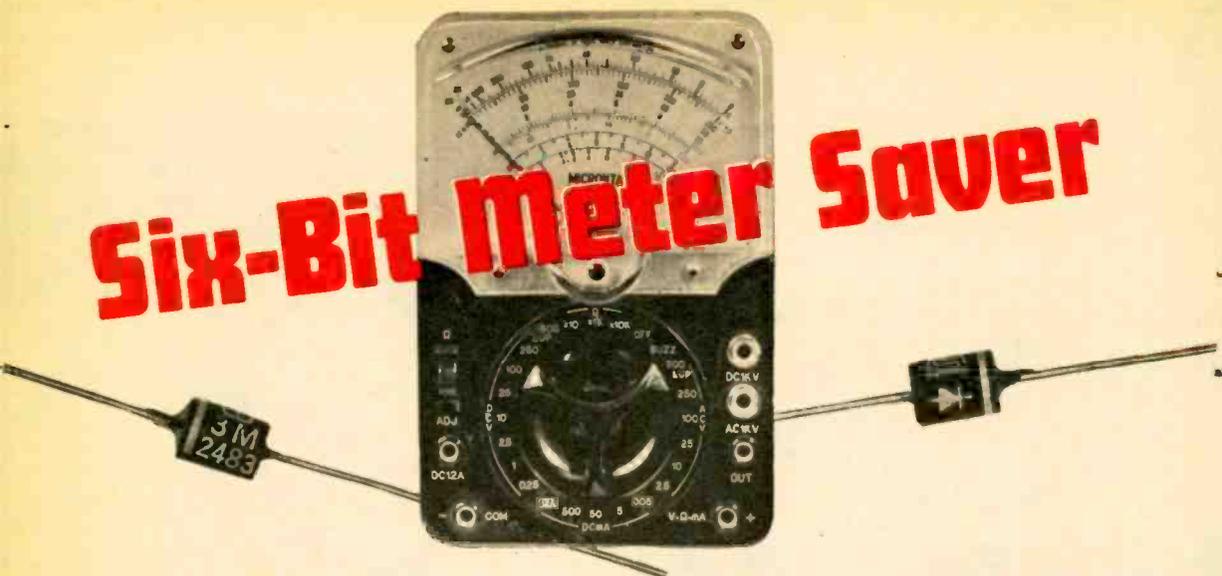

EVEN if it's only a \$10 VOM, nobody likes to see it burned out by a moment of carelessness. And if it's a \$60 instrument you've deep-sixed, the grief and loss of green stuff are horrifyingly real.

Sure, most of us at one time or another by incorrectly setting a switch or by putting a test lead in the wrong place have sent a meter movement to the big shop in the sky. It usually happens fast enough to prevent second chances. All it takes to burn-out proof most any meter is cigarette money and ten minutes work.


The secret is two inexpensive silicon diodes connected back-to-front and paralleled across the meter terminals, as shown below. But you cannot protect a meter that has a series resistor built into it. The terminals must be connected directly to the meter coil.

Silicon diodes require a nominal 0.7 V across them before they conduct. Most me-


ters when deflected fully will have a voltage that is less than 0.7 V across their terminals. The diodes, therefore, will have no effect on the meter. But when the meter is overloaded severely the voltage across its terminals reaches the diode's breakover voltage, the diodes conduct and excess current is bypassed around the meter.


SR1 and SR2 can be any low-cost silicon diodes, such as Lafayette's 19 R 5001. They will protect virtually any 50- μ a to 1-ma DC meter. With some meters the diodes may interfere with accuracy. To check whether they do, try them before they're installed permanently. Measure a voltage and note the quarter-, half-, three-quarter- and full-scale deflections. Connect the diodes temporarily across the meter terminals and repeat the procedure. If the meter readings don't change, connect the diodes permanently in place.

—Chet Stephens

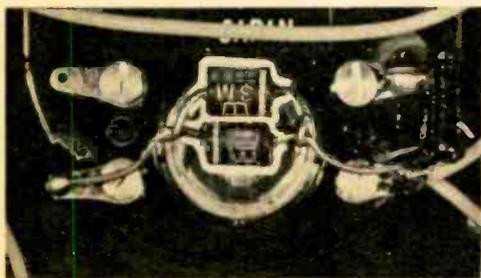

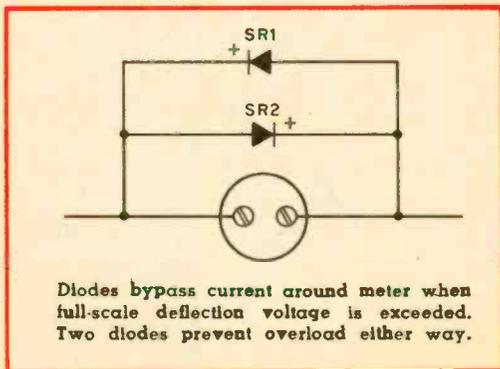Install diodes (shown here outlined in white) directly across meter terminals in VTVM or VOM.



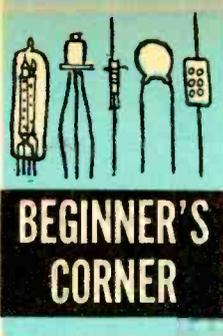

The Case of the INVISIBLE Gate

THERE are no moving parts, yet it switches. The knob you turn to make it dim lights as slow motors is twice its size.

It is the silicon controlled rectifier (SCR)—the up-and-coming little giant in electronics. The steady decline in its price is putting it into more and more light dimmers, battery chargers, motor-speed controls and automobile ignition systems—to mention just a few applications.

The SCR resembles an ordinary solid-state diode rectifier since it passes current in one direction only. But there's an important difference. You can regulate the amount of current the SCR will conduct by means of a third element, called a gate.

Shown in Fig. 1, left, is the schematic symbol of an SCR. Its three elements are anode (positive terminal), cathode (negative terminal) and gate. If this were a conventional diode it would conduct current instantly when connected as shown because its anode is connected to the + battery terminal and its cathode is connected to the - battery terminal.

But since it's an SCR, it will not conduct until a voltage is applied to the gate, which is positive with respect to the cathode. When the voltage on the gate is zero or negative,

the SCR's anode-to-cathode resistance is high. It's like an open switch.

To get the SCR to conduct current all we have to do is adjust the potentiometer (R) so it puts a positive voltage on the gate. When you apply 2 V to the gate of the RCA 2N3228 SCR its internal resistance drops and a heavy current flows from cathode and anode. The SCR now functions like an ordinary diode. That is, current is proportional to the DC voltage applied across anode and cathode.

Now turn R to bring the gate voltage back to zero. Lo and behold, the SCR continues to conduct current! In other words, once current starts to flow the gate cannot stop it—even though it started it. To get the SCR back to its non-conducting, or off, state the voltage must be removed from the anode. But before we go on, let's take a look at how the SCR is constructed to see how it works.

Figure 1, right, shows the four layers of semi-conductor material found in an SCR. These sections (right), however, can be looked at as PNP and NPN transistors which have been joined together. The equivalent of the SCR, a 2-transistor regenerative circuit, is shown in Fig. 2. The gate, then, actually is the base of the lower transistor.

[Continued on page 92]


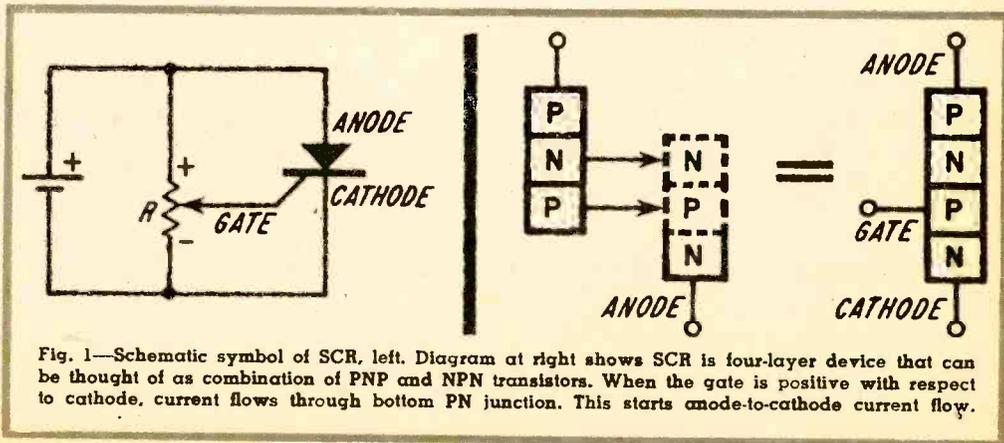


Fig. 1—Schematic symbol of SCR. left. Diagram at right shows SCR is four-layer device that can be thought of as combination of PNP and NPN transistors. When the gate is positive with respect to cathode, current flows through bottom PN junction. This starts anode-to-cathode current flow.

FREE

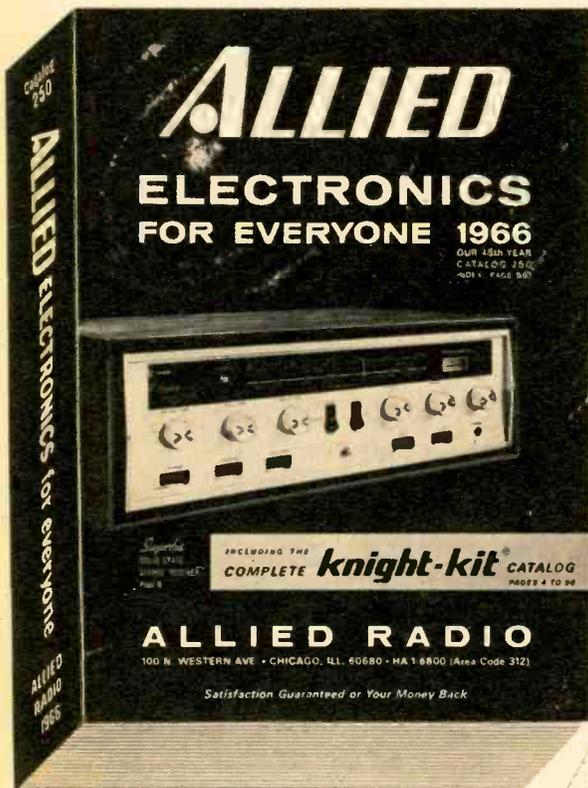

508 VALUE-PACKED PAGES
including exclusive products and
special values available only
from **ALLIED**

send today for your

ALLIED
1966 CATALOG
world's largest selection

SAVE MOST ON:

Stereo Hi-Fi
Tape Recording
CB 2-Way Radio
FM-AM & AM Radios
Short Wave Radios
Portable TV • Phonographs
Amateur Gear
Intercoms & P.A.
Automotive Electronics
Test Instruments
TV Tubes & Antennas
Power Tools, Hardware
Parts, Tubes, Transistors

MORE OF THE BEST IN ELECTRONICS FOR EVERYONE

EASY TERMS
Use the convenient
Allied Credit Fund Plan
—over 24 months to pay

ALLIED RADIO
The World's Largest Electronic Supply House


*satisfaction
guaranteed or
your money back*

SPECIAL in your FREE 1966 ALLIED CATALOG


see what's new in the wonderful world of **knight-kits**®



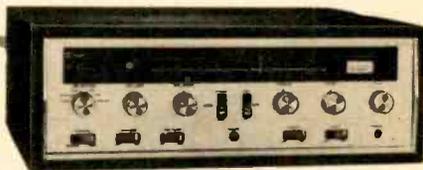KG-895 Superba Series
120-Watt Solid-State
Stereo Amplifier Kit. \$149.95
(less case)



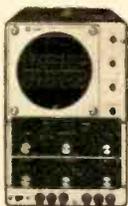KG-964 Superba
Series 64-Watt Solid-
State FM-AM Stereo
Receiver Kit.
\$189.95
(less case)



KG-635 5-Inch DC
to 5.2 Mc Wide-
band Oscilloscope
Kit. \$99.95



KG-371 Solid-State
Auto DC Power
Timing Light Kit.
\$19.95



KG-375 Solid-State
Universal Auto
Analyzer Kit. \$49.95



Safari-1 Deluxe
23-Channel Citizens
Band Transceiver Kit. \$129.95



C-540 Low-Cost
5-Watt Citizens
Band Transceiver
Kit. \$49.95



KG-221 FM Monitor
Receiver Kit
(police, fire, ma-
rine, weather
bands, etc.) \$39.95



KG-201 Solid-State
Motor-Speed/Light
Control Kit. \$9.95

KG-415 Superba
Series Professional
Solid-State Stereo
Tape Deck Kit.
\$249.95
(less case)



Knight-Kit GUARANTEE: Buy any Knight-Kit. Build it. Operate it. You must be satisfied or we refund your money.


THERE IS A knight-kit FOR EVERY NEED!
easiest to build—enjoy big savings

- Stereo Hi-Fi
- CB 2-Way Radio
- Short-Wave
- Hobby Kits
- Test Equipment
- Automotive
- Intercom
- Amateur Gear

send for your 508-page 1966 Allied Catalog

FREE

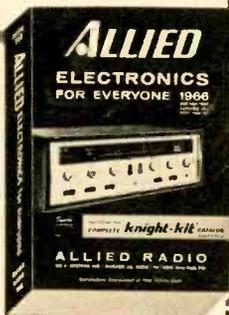Send today for your
508-page Allied 1966
value-packed catalog



Free!

ALLIED RADIO, Dept. 4-C
100 N. Western Ave., Chicago, Ill, 60680

Send FREE 1966 Allied Catalog

Name _____
PLEASE PRINT

Address _____

City _____ State _____ Zip _____

ALLIED RADIO

The Case of the INVISIBLE Gate

We are going to show positive- and negative-going pulses on the elements of the transistors to make it a little easier to visualize what's happening. In a real circuit pulses, generally, do not exist as we show them.

A positive pulse applied to the gate increases current through the bottom transistor (NPN). At the collector the pulse is negative-going. The pulse goes to the base of the upper transistor (PNP) and causes it to conduct. The pulse is inverted again and is positive-going at the collector. However, the top transistor is connected to the lower one in a way that provides positive feedback. The result of this is that the original input signal is amplified and returned to the base of the lower transistor in greater amplitude. It's like positive feedback. Current flow increases rapidly in both transistors and continues after the original input signal to the gate is removed. The only way to stop the current flow is to remove or lower the anode-cathode voltage. We'll get to this later.

The schematic of a lamp dimmer and motor speed control is shown in Fig. 6. Incoming AC is applied to the SCR anode and, through the load, to the cathode. AC is also impressed across a voltage divider consisting of R1 and potentiometer R2. This divider provides the gate-triggering voltage. The purpose of SR1 is to rectify AC since the gate operates only on a positive DC voltage.

At the instant power is applied, we'll assume the sine wave applied to the anode of the SCR starts to go positive (See Fig. 3). When the arm of R2 is at, say, the top of the control, the gate voltage reaches 2 V very quickly. Hence the SCR conducts early in the cycle and power is delivered during most of the positive half of the AC cycle.

But lower R2's wiper arm and the applied AC will have to rise to a higher value before

2N3228 SPECIFICATIONS		
Characteristic	Symbol	Rating
Gate-trigger voltage	VGT	2 V
DC gate-trigger current	IGT	15 ma
Average forward current (rms value)	IFRMS	5 A
Peak reverse voltage (repetitive)	VRM	200 V

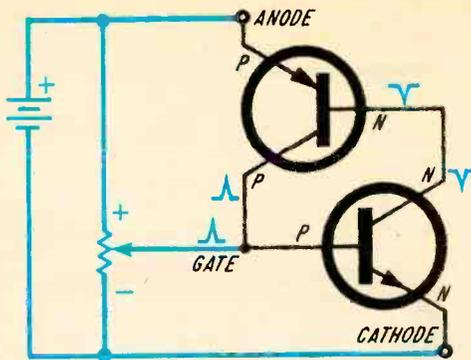


Fig. 2—Positive voltage on gate is amplified and fed from top transistor to lower transistor's base. This keeps the SCR on after the input is removed.

the gate voltage reaches 2 V. This means the SCR will be turned on later in the positive half of the cycle. The result is less power through the load.

Operating the SCR on AC enables the gate to regain control. Here's how. On the second half of the AC cycle the anode is negative and as in any diode, current cannot flow. There is neither a positive voltage on the anode nor the gate. The SCR is reset and awaits just the next positive half cycle.

The circuit just provides half-wave control since the SCR controls only the positive portion of the AC cycle. A lamp connected to the SCR can be adjusted from off to brightness of only about 30 to 40 per cent. More complex SCR circuits, which use additional diode rectifiers, are used for full-wave and consequently full range, control. The circuit shown can also be used to control a soldering iron to reduce heat when working on delicate printed circuits.

Do not use this circuit on transformer-

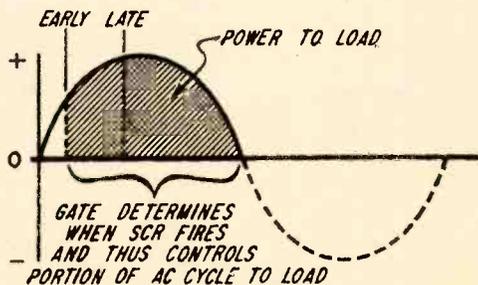


Fig. 3—If R2 in Fig. 6 is set near R1, gate voltage reaches 2 V at beginning of positive half of cycle, causing most of power to go to load.

Fig. 4—Construction of light dimmer/motor speed control in U-section of 3 x 4 x 5-in. Minibox is straightforward. SCR is mounted on vertical aluminum plate which serves as the heat sink. Be certain the SCR is insulated from the heat sink with hardware supplied with it. Because the SCR's case has line voltage on it, it should be kept inside the cabinet to prevent shock hazard.

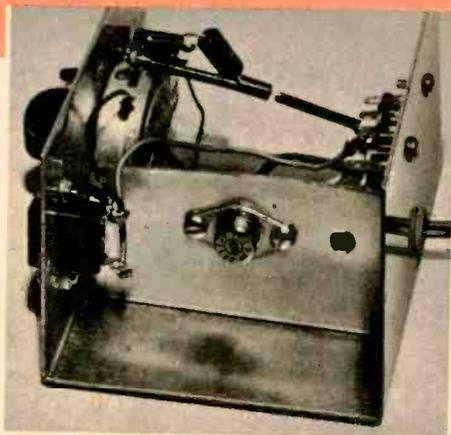
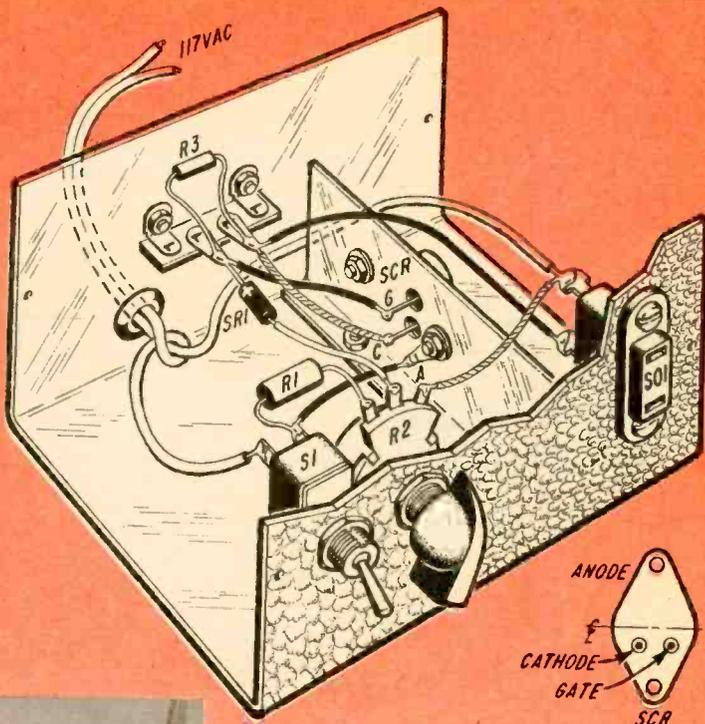


Fig. 5—SCR must be mounted on piece of aluminum to dissipate heat. Use mica and plastic washers supplied to insulate case from plate.

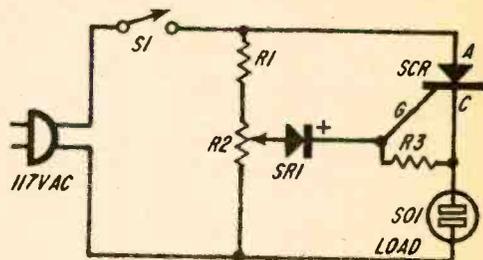


Fig. 6—Schematic of light dimmer/motor speed control. Diode SR1 is necessary in the circuit to rectify AC so only DC will be fed to the gate.

PARTS LIST

- R1—2,200 ohm, 2 watt resistor
- R2—1,000 ohm, wirewound potentiometer
- R3—1,000 ohm, 1/2 watt resistor
- S1—SPST toggle switch (5 A minimum rating)
- SCR—2N3228 silicon controlled-rectifier (RCA)
- SR1—Silicon rectifier; minimum ratings: 400 PIV, 200 ma
- SO1—Chassis mount AC socket
- Misc.—3 x 4 x 5-in. Minibox, knob, terminal strip, AC line cord.

operated devices such as a soldering gun or fluorescent lamp. Incandescent lamps or AC/DC motors may be controlled if their current does not exceed 5 A.

As in any semiconductor device, there are maximum ratings which should not be exceeded. Important characteristics of the 2N3228 are shown in the chart. The forward current (I_{FMS}) determines the amount of power that can be safely handled by the SCR. Since it is 5 A, the 2N3228 can be used with resistive loads to almost 600 watts (at 117 V.)

—H. B. Morris


OVER AND OUT

BY *Rodriguez*




"I'm having quite a time with the FCC. They can't figure out what to call me: mobile, base or base/mobile."

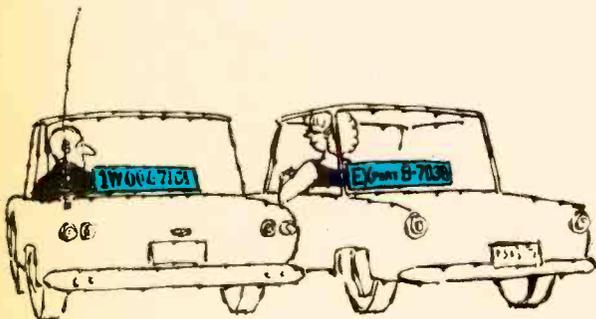"Here's a push-to-talk designed with the ladies in mind. The button needs a 20-pound pressure to keep it open."



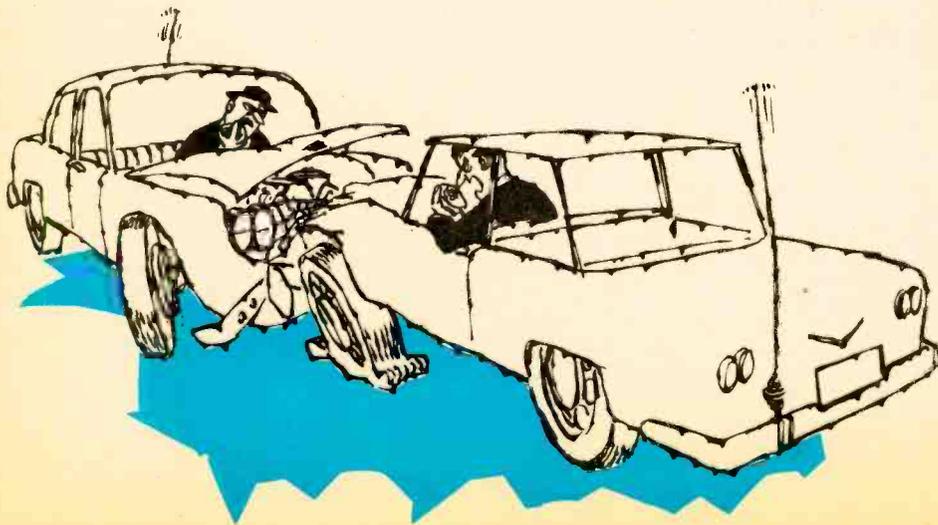"I finally found out why my mobile can work only 65 yards. It's a 12-volt set working off a 6-volt battery."



Stereo Tape Deck

Continued from page 33

the Viking transport. It has two motors—one for capstan drive and another for fast-forward and rewind. There are no pressure pads on the heads themselves—which means less head wear and longer head life—and in their place is a single pad at the left of the erase head. This, in conjunction with the capstan and pinch roller, maintains tape tension across the heads. In the rewind and fast-forward modes, lifters raise the tape from the head surfaces. This, too, increases head life.

Concentric knobs control operations. The inner knob has three positions. At the position marked *cue off* the reels are disengaged from the drive mechanism, yet the tape is held tightly against the heads. This permits the reels to be turned slowly by hand to position the tape for editing.

The middle position of the knob is *neutral*, or off. The right position is for both *play* and *record*. But a safety interlock makes it necessary to push in a button at the same time the knob is turned to the right in order to record. The outer knob has three positions—for *off*, *rewind*, and *fast-forward*.

As for the KG-415's electronics, there are playback, mike and line level controls. (The line level control is for high-level input sources, such as an FM tuner or equalized phono.)

The KG-415 has a professional feature that lets you A-B the input and recorded signals. To balance the recorded signal level and the input signal level for headphone monitoring, there are source-level and playback-level controls. The former varies the level of the input signal and the latter controls the recorded signal level from the playback head.

In addition, there is a 3¾-7½ ips equalization switch and provision for sound-on-sound and echo effects. A master selector switch sets the operating mode of the amplifiers. That is, you set it to record or play stereo or to record or play mono on the left or right tracks. And, of course, there's a digital counter and automatic shut-off.

Our KG-415 met or exceeded all Knight's specs. At 7½ ips the left-channel play response was 3db down at 40 cps and flat within ± 1db from 70 cps to 15 kc. The right-channel play response was 3db down at 55 cps and flat within ± 1db from 80 cps to 15 kc.

As for the record/play response (which is measured by recording a signal and evaluating the output from the monitor head and monitor amplifier), frequency response was 3db down at 45 cps and flat within ± 2db to 18 kc. At 3¾ ips we found the response was the same as that claimed by Knight—flat within ± 2db from 50 cps to 15 kc.

Harmonic distortion (record/play mode) was 1½ per cent and crosstalk (play mode) was 52db down. The signal-to-noise ratio (in record/play mode, erasing a 100 per cent modulated track at 1 kc) was 48db for the left channel and 47db for the right channel—both only a shade under the 50db figure claimed by Knight. (Ours may have been a more severe test.) Flutter was inaudible.

The record bias must be set for the particular tape you are going to use. The setting is critical and affects both high-frequency response and distortion. Switch to another type of tape and the bias must be reset. Adjustment of both the record bias and erase currents is facilitated by a built-in 1-kc oscillator and step-by-step instructions.

Super-Speed Strobe

Continued from page 66

or SO3. Operation is the same as that of any other strobe but exposures are different. In order to achieve such high speed we've sacrificed light output. As a result, the power rating of the strobe is 5 watt-seconds.

The extremely fast flash affects film differently than does the longer flash of conventional strobes or flashbulbs. This means negatives will have less contrast. Thus, film should be developed from one and a half to two times the normal time for comparable contrast.

The photographs on the first page of this article were taken with a Rolleiflex and Tri-X pan film, using an ASA guide number of 20. The shot of the graduate was made with a piece of white translucent screen 6 in. behind the graduate. The strobe light was placed one foot behind the screen and the camera was 12 in. in front of the graduate.

The shot of the drop of milk was taken with the camera and light side by side 12-in. away. In both cases, the diaphragm was set at f.22. The film was developed in Microdol-X for about 22 minutes.

Assemble the finest instrument your money can buy

NEW ALL-TRANSISTOR *Schober*®

ELECTRONIC ORGAN

New Recital Model
compares musically
to instruments
costing 4 times
the price!



meets AGO specifications



PIPE ORGAN VOICING—separate, distinct—32 in Recital Model. LIBRARY OF STOPS™ Kit feature adds extra plug-in voices



ALL TRANSISTOR Models give instant response, easier assembly, full 5 year guarantee



PIPE ORGAN TONE—all four families of pipe tone in all models



REVERBATAPE® Unit—adds "auditorium" depth and power

plus **FULL THEATRE AND CHURCH VOICING, PERCUSSION,** many other quality features!

How is it possible to acquire the skill needed to build a splendid organ—without any previous knowledge of electronics or music?

While the complete organ is a complex instrument, Schober Organ kits are specially designed for do-it-yourselfers. Printed circuitry eliminates a lot of the work and makes errors almost impossible. Many parts come preassembled. You simply follow detailed illustrated instructions for easy assembly, then place in assembled and pre-finished cabinet.

You save costly factory assembly, retail store mark-up—put every penny into fine musical parts. You enjoy the finest instrument your money can buy.

Schober Organ kits cost as little as \$550 in kit form, and you may spread this cost by ordering in sections.

THE *Schober Organ* CORPORATION
NEW YORK, N. Y. 10023

SEND FOR FREE CATALOG WITH FREE "SAMPLER" RECORD

The Schober Organ Corp., Dept. E1-8
43 West 61st Street, New York, N. Y. 10023

Please send me without cost or obligation FREE SCHOBER ORGAN Booklet describing models. FREE 7-inch "sampler" record included.

Enclosed find \$2 for high-quality LP 10" SCHOBER RECORD DEMONSTRATING all three models with different music (\$2 refunded with purchase of first kit).

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP NO. _____

Life Goes On and On at 40

Continued from page 48

edge as well as the lighter, all-aluminum voice coil. Elsewhere, more sophisticated and accurate ways of controlling tolerances during manufacture have been devised, also contributing to better speakers.

The most dramatic change, however, has come not in the speaker itself, but in the box that holds it.

"Not long ago," says Scott's Brociner, "really enormous complicated and expensive horn speakers were considered necessary for reproduction down to 40 cycles. Today we can do better in a 2-cubic-foot cabinet."

One of the pioneers in cutting speakers down to size is Edgar Villchur of Acoustic Research. In 1955 Villchur introduced his now-famous line of AR speakers, in the process launching a controversy still not resolved.

High-quality, low-frequency speakers before the AR were of two types: the horn, a monstrous device of high efficiency dating back to the early days of the dynamic speaker, and the so-called infinite baffle assembly, another sound-maker enclosed in a huge box.

Both the horn and the infinite baffle use speakers in which the cone is supported by a springy mounting around its edge. When a signal pushes the cone away from the center, the springy suspension brings it back. Villchur designed a speaker that instead had a suspension so flabby it hardly could move the cone at all. Then he mounted the speaker in a small, airtight box. The springiness of the air trapped in the box was used to return the speaker to center.

This so-called air-spring or acoustic-suspension speaker not only *could* be housed in a small box, it wouldn't work unless it *was*. You won't be surprised to learn that even the acoustic-suspension idea wasn't new. For though Villchur was the first to build a commercial model, the concept was explained in a book by RCA's famous audio pioneer, Harry F. Olson, in the 1930s.

Villchur, of course, made sacrifices to get big performance from a little box. The price was efficiency. An acoustic-suspension system might take 20 watts to crank out the amount of sound that a high-efficiency horn would produce with a watt or two. And this brings up a crucial point: the real breakthrough in speaker design in recent years

[Continued on page 98]

Some plain talk from Kodak about tape:

The meat of the matter... and some boxing news

Undistorted output from a tape—as from any other link in the chain of audio components—is at the very heart of high fidelity enjoyment. Distortion (or the lack of it) is simple enough to evaluate in theory. You start out with something measurable, and you reproduce it. Everything added (or subtracted or modified) by the reproduction, that can be measured or heard, is distortion. Since most kinds of distortion increase as you push any component of your system closer to its maximum power capability, you have to label your distortion value to tell whether you did this while coasting or at a hard pant.

Cry “uncle”

To make the distortions contributed by the tape itself big enough to measure and control, we simply drive the tape until it hollers “uncle” and use that power reference as our benchmark. Here’s the procedure. Record a 400-cycle signal (37.5-mil wavelength at 15 ips) and increase its level until in a playback, which is itself pristine, you can measure

enough 1200-cycle signal (third harmonic) to represent 2% of the 400-cycle signal level. This spells “uncle!” We use 400 cycles for convenience, but insist upon a reasonably long wavelength because we want to affect the entire oxide depth.


The more output level we can get (holding the reproduce gain constant, of course) before reaching “uncle,” the higher the undistorted output potential of the tape. Simple, what?

“Wadayamean — undistorted output at two percent?”

That’s what makes a Miss America Contest. Two percent third harmonic is a reference point that we like to contemplate for a picture of oxide performance. Since distortion changes the original sound, it becomes a matter of acumen and definition how little a change is recognizable. If you’re listening, two percent is a compromise between a trained and an untrained ear. If you’re measuring, it comes at a convenient point on the meter.

Because undistorted output

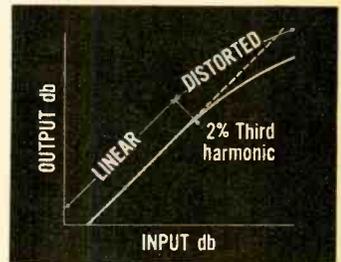helps to define the upper limit realism of the recording, the higher the undistorted output, the easier it is to reproduce the massed timpani and the solo triangle each at its own concert hall level. And this is just another area where Kodak tapes excel... our general-purpose/low-print tape (Type 31A) gives you up to 3 decibels more crisp, clean output range than conventional tapes.



2% third harmonic distortion represents the practical limit to linear recording.

Kodak tapes—in the five- and seven-inch sizes—now look as good as they sound. We’ve put the package identification on a removable sleeve and designed a tape library box with a smart new look. This new box features durable one-piece construction, full index space, plus detailed tape use instructions on the inside. Kodak Sound Recording Tapes are available at most electronic, camera, and department stores.

New 24-page, comprehensive “Plain Talk” booklet covers all the important aspects of tape performance, and is free on request. Write: Department 8, Eastman Kodak Company, Rochester, N. Y. 14650.

The great unveiling — Kodak’s new library box with removable sleeve!



EASTMAN KODAK COMPANY, Rochester, N. Y.



**AS BRITISH AS
BIG BEN**

BALFOUR
Princess 

automatic/manual turntable systems

Only the British could create Big Ben, a marvel of lasting precision. And only Balfour can give you such fine hi-fi quality at low cost!

- Featuring • Built-in Stylus Brush
- Automatic Tone Arm Lock
- Low Wow and Flutter

Priced at \$37.50 & 47.50 See your dealer.



RFS INDUSTRIES, INC.
102 Harbor Road, Port Washington, N.Y. 11050

WANT A JOB? PART TIME— FULL TIME?

No Boss! No Experience!

No Capital! Your Own Hours!

WHAT A JOB ! ! ! !

And yet selling subscriptions to **ELECTRONICS ILLUSTRATED** and other leading publications is just like being in business for yourself.

But no business requires less capital, stock and space. The time you devote and the money you make is up to you. You need no experience to earn steady profits and you keep a cash commission on every sale. You operate in your own community by phone or personal calls. You will be authorized to sell new and renewal subscriptions along with special offers made by the publishers. You'll be amazed at the number of people wanting to take advantage of the convenience, service and savings you can offer them.

To get started immediately—send us your name (on a postal card) requesting *free* supplies and selling materials.

Write to: Subscription Dept. DE
ELECTRONICS ILLUSTRATED
Fawcett Bldg., Greenwich, Conn. 06830

Life Goes On and On at 40

Continued from page 96

didn't come in speakers at all. It came in amplifiers.

Years ago, amplifier power was limited sharply. Engineers, consequently, had to wring as much sound as they could from available audio power. Since horn speakers were the most efficient they were used almost universally.

High-power amplifiers now are commonplace and speaker designers can waste as much power as they like. This makes other important advances possible: Engineers, for example, can design extra-long voice coils that stick out of the magnetic gap on either end. No matter how far the cone moves, the gap still is full of voice coil. This technique wastes power but it also helps produce linear cone movement and a sweet sound.

And so the fight for fidelity reels onward. Though no one has altered the basic design of the dynamic loudspeaker in two generations, it remains undisputed champion. And as audio experts continue to refine and improve its performance, this fantastic sound-making machine, this fugitive from the 1920s, likely will stay on top for the foreseeable future.

The Syncopated Metronome

Continued from page 79

put transistor Q6. The combination of these two pulses provides emphasis upon every second, third, fourth, etc. pulse as shown in Fig. 2.


• **The Accentuate Control.** To achieve compound times such as 6/8 and 9/8, extra emphasis is added to every sixth or ninth pulse, respectively. This is accomplished by closing S1 which adds the output of Q5 to the output of Q1 and Q3. Q5, like Q3, is also a staircase counter, and pulses are accumulated on C6 in the same fashion as they were on C3. Control R10, labeled *accentuate*, is adjusted to provide compound accentuation upon every sixth or ninth, etc. output pulse generated by Q1. Fig. 2 shows the relative pulse amplitudes for 6/8 and 9/8 time. An enterprising musician can achieve many other combinations of emphasis than those shown, for new and off-beat music. Good playing!



99-3027WX

LAFAYETTE SOLID-STATE 5-WATT C.B. TRANSCEIVER
 Model HB-500 Small, Quiet, Powerful . . . only 3" High

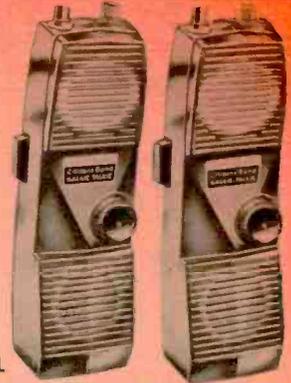- 109⁵⁰**
- Mechanical Filter for Razor Sharp Selectivity
 - 12 Crystal Transmit and Receive Positions
 - 23 Channel Tunable Receiver with Spotting Switch
 - Multi-Stage Automatic Noise Limiting Circuit
 - With Channel 12 Transmit and Receive Crystals, Push-to-Talk Dynamic Mike, Crystal for Dual Conversion, Mobile Mounting Bracket.



99-3046L

LAFAYETTE 12-TRANSISTOR C.B. WALKIE-TALKIE Model HE-100A with Noise Squelch ANL

- 39⁹⁵**
- 2-for-78.88
- Separate Microphone and Speaker for Better Modulation, Increased Range
 - 12 Transistors, 1 Diode and 1 Thermistor
 - Superhet Circuit is Crystal Controlled on Transmit and Receive
 - Variable Squelch Reduces Background Noise
 - Optional Plug-in 117V AC Power Pack
 - Easy to Use and Lightweight
 - With Leather Case, Earphone, Telescoping Antenna, Batteries, Crystals for Channel 10.

THE WIDELY ACCLAIMED LAFAYETTE TAPE RECORDER Model RK-137A

89⁵⁰

- Takes Full 7" Reel of Tape
- 2 Speeds—3¾ and 7½ ips
- Electronic Track Selector Switch
- Features 4-Track Monaural Record/Playback
- Adaptable to 4-Track Stereo Playback
- With Lightweight Carrying Case, Dynamic Mike, Shielded Patch Cords, 7" Take-up Reel.



99-1511WX

LAFAYETTE 70-WATT COMPLETE AM-FM STEREO RECEIVER Model LR-800

179⁵⁰

- Just Add Speakers and Enjoy FM, FM Stereo and High-Quality AM Reception
- FM "Stereo Search" Circuit
- Nuvistor "Front End"
- Powerful 70-watt Amplifier plus Complete Preamp plus AM Tuner plus FM Tuner plus FM Stereo Tuner on One Chassis.



99-0005WX

FREE!

LAFAYETTE Radio ELECTRONICS
1966 Catalog 660
Now BETTER THAN EVER
"World's Hi-Fi & Electronics Center"



512
Pages

LAFAYETTE Radio ELECTRONICS
 Dept. EIC-6, P.O. Box 10
 Syosset, L.I., N.Y. 11791

Send me the Free 1966 Catalog

Name

Address

City

State

Zip

(Please Give Your Zip Code No.)

PRECISION ALL-PURPOSE SIGNAL TRACER



For fast servicing of AM, FM, TV, Audio and Electronic Equipment . . .

Checks all stages from antenna to speaker or picture tube. Tests microphones, appliances, pickups, transformers, speakers, resistors, condensers, etc. Quickly locates intermittents, open circuits, hum, noise, distorted stages. Both visual and aural tracing with super-sensitive indicator eye and built-in 5" speaker. 3 stage preamplifier circuit plus overall feedback. Wide band response, additional voltage gain of 400 for scope or VTVM. 110-120 volts AC at 60 cycles. Wt. 9½ lbs.

Model 202. Signal Tracer with AF Probe. . . . 59.95
Model B Probe. RF Demodulator Amplifier Probe with amplifier-detector tube for high gain and frequency responses to 300 MC. . . . 7.50



See your distributor or write Dept. EI-3
PRECISION ELECTRONICS, INC.
9101 King Street, Franklin Park, Illinois



Ceramic Coil Forms In Stock/In Depth

Ceramic coil forms in .205", .260", .375" and .500" diameters are now stocked in depth for applications in frequency ranges between 50 kc and 300 mc. Bushing mounted forms with fiberglass collars for high "Q"/low loss applications are available in 2-terminal and 4-terminal configurations.

Write for 20-page Coil Form catalog.



J.W. MILLER CO.
5917 So. Main St. Los Angeles, Calif. 90003
NOW GET FACTORY PRICES IN QUANTITIES
TO 750 FROM YOUR LOCAL DISTRIBUTOR


STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION

(Act of October 23, 1962; Section 4369, Title 39,
United States Code)

1. Date of Filing: October 1, 1965.
2. Title of Publication: **ELECTRONICS ILLUSTRATED.**
3. Frequency of Issue: Bi-Monthly.
4. Location of Known Office of Publication: Fawcett Place, Greenwich, Connecticut 06830.
5. Location of the Headquarters or General Business Office of the Publishers: Greenwich, Connecticut 06830.
6. Names and Addresses of Publisher, Editor, and Managing Editor: Publisher, Fawcett Publications, Inc., Greenwich, Conn.; Editor, Robert G. Beason, Oradell, N. J.; Managing Editor, Robert D. Freed, Woodside, N. Y.
7. Owner: Fawcett Publications, Inc., Greenwich, Conn.; W. H. Fawcett, Jr., Norwalk, Conn.; Marion Bagg, Kansas City, Mo.; Roger Fawcett, New York, N. Y.; V. D. Fawcett, Greenwich, Conn.; M. B. Fawcett, Norwalk, Conn.; Gordon W. Fawcett, Greenwich, Conn.; Gloria Leary, Santa Monica, Cal.; V. F. Kerr, Bakersfield, Cal.; Allan Adams & Jack Adams—Trustees, Greenwich, Conn.; John R. Fawcett, Wilton, Conn.; Thomas K. Fawcett, New York, N. Y.; Roscoe Kent Fawcett, Reno, Nevada; M. F. Fawcett, Greenwich, Conn.; H. A. Fawcett, New York, N. Y.
8. Known Bondholders, Mortgagees, and Other Security Holders Owning or Holding 1 Percent or More of Total Amount of Bonds, Mortgages or Other Securities: None.
9. Paragraphs to be included in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of bona fide owner. Names and addresses of individuals who are stockholders of a corporation which itself is a stockholder or holder of bonds, mortgages or other securities of the publishing corporation have been included in paragraphs 7 and 8 when the interests of such individuals are equivalent to 1 percent or more of the total amount of the stock or securities of the publishing corporation.
10. This item must be completed for all publications except those which do not carry advertising other than the publisher's own and which are named in Sections 132.231, 132.232, and 132.233, Postal Manual (Sections 4355a, 4355b, and 4356 of Title 39, United States Code).

Average No. Copies Each Issue During Preceding 12 Months:
A. Total no. copies printed (net press run), 373,330. B. Paid circulation: 1. Sales through dealers and carriers, street vendors and counter sales, 128,479; 2. Mail subscriptions, 167,635. C. Total paid circulation, 296,114. D. Free distribution (including samples) by mail, carrier or other means, 2,244. E. Total distribution (sum of C and D), 298,358. F. Office use, left-over, unaccounted, spoiled after printing, 75,472. G. Total (sum of E and F—should equal net press run shown in A), 373,830.
Single Issue Nearest to Filing Date: A. Total no. copies printed (net press run), 378,009. B. Paid circulation: 1. Sales through dealers and carriers, street vendors and counter sales, 126,500; 2. Mail subscriptions, 178,140. C. Total paid circulation, 304,640. D. Free distribution (including samples) by mail, carrier or other means, 2,145. E. Total distribution (sum of C and D), 306,785. F. Office use, left-over, unaccounted, spoiled after printing, 71,224. G. Total (sum of E and F—should equal net press run shown in A), 378,009.
I certify that the statements made by me above are correct and complete.

(signed) GORDON W. FAWCETT

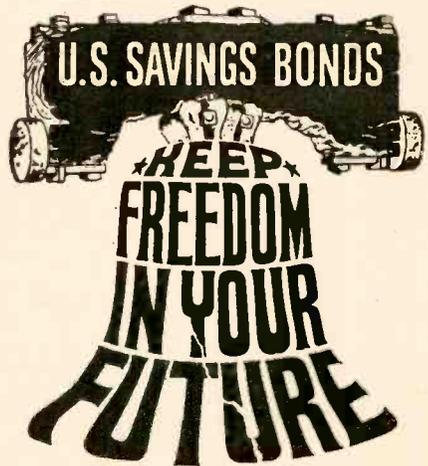

BUY AN EXTRA BOND NOW!

Electronics Illustrated

Last Stand For Brass Pounders

Continued from page 51

telegraphy isn't dead yet. There are places where the best radiocommunication facilities available end up sounding like chowpy chowpy, chow-chowpy chow on the air. Machines clearly can't suffice under such circumstances. It takes warm-blooded people to pound out those chowpies, others to copy them.

For the foreseeable future, ships of all nations will communicate with each other and with shore by code. Reason is that ship radio installations by their nature basically are for safety and reliability. There still is no simple system that beats radiotelegraphy in this field. In the worst calamities, men have been able to lash together some means of getting out dots and dashes—even to the extreme of touching hand-held wires together.

Besides ships and government service, there are berths for licensed radiotelegraphers in communications stations, transmitter-tending and mobile and marine installation and service work. The need for brass pounders may recede but never quite disappear. Even so, we currently are witnessing the twilight of their era—the brass pounders' last stand.

Notes From EI's DX Club

Continued from page 61

increase there will be a drop in the number of broadcast-band DX openings observed during the winter months. And though transatlantic medium-wave DX still will be possible, there will be fewer openings, particularly in April.

April also will witness a seasonal increase in short-skip propagation and this will result in more DX openings in the TV and FM bands than at any time since last summer.

Reception in the SWBC bands generally will be fair to good, except during periods of disturbed ionospheric conditions, which are at a maximum during the spring and fall months.

Best daytime reception will be on the 15-, 17-, and 21-mc bands. At night, reception from Europe and Africa will be best on the 6-, 7-, and 9-mc bands, while Latin American stations will be heard on 11 and 15 mc.

Now you can solder
tuners, planes,
pre-amps and trains
with the finesse
of a production-
line pro



New MARKSMAN PENCIL Soldering Iron

Featherweight precision tool has stainless steel long-reach barrel with replaceable tip. Handle remains cool. Tip runs up to 750°F. Complete with cord. Model SP-23. **\$2.98** list

Also available in kit with two extra soldering tips, handy soldering aid and supply of solder. Model SP-23K. **\$4.44** list

WELLER ELECTRIC CORP., Easton, Pa.
WORLD LEADER IN SOLDERING TECHNOLOGY

TAPE THIS AD TO THE BACK OF YOUR TV SET


ALL TV-RADIO RECEIVING TUBES

\$1

ea.

ALL BRAND NEW!

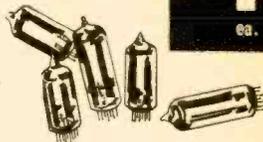All at a flat
discount price
of only \$1.



Stock up now on Top-Quality, Made in U.S.A. tubes from one of America's leading mail-order sources.

Choose from over 800 types of receiving tubes, including the new Nuvistor and Compactrons and tubes for color sets.

All tubes sold on a written 24-month Warranty; all orders shipped 1st Class same day received! *Just send \$1 for each tube (regardless of Mfrs. Suggested List Price) plus 25c postage and handling for your entire order. Why pay more? Write Dept. EI-236,

UNIVERSAL TUBE CO.

Ozone Park, N. Y. 11417


THIS IS A MAGNIFICENTLY-DETAILED 1/24th SCALE MODEL 1896 ENGLISH LIVE-STEAM TRACTOR

COMPLETE TO BRASS BOILER, STEEL FIRE BOX,
COPPER STEAM PIPES



A LIFETIME OF USE

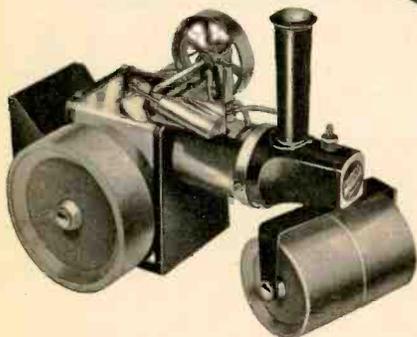These are more than just toys — like the originals they copy, they should still be "in use" 50 years from now. Each is \$35. For those readers who would like both, they are specially priced at \$65.



This is the workhorse companion to the traction engine. In construction and operation it is the same. The polished rollers and rear wheels are aluminum pressure diecastings. Axle caps are spring steel. It also develops 1/15 hp at 3000 rpm, and will also operate other stationary models. It is the forerunner of the present day diesel rollers, and is a real beauty. Made in England, \$35.

**Raises steam in 3 minutes, travels
1/3 mile in a 10-minute run, can be used
to operate other stationary models**

The English traditionally make fine models. This one, beautiful in gleaming brass and copper, has flywheel and other parts in green and red enamel. Everything works as original did in 1896. Brass steam whistle blows, cylinders and pistons are brass, steam pipes are copper, and fire box, scuttle, burner box, front forks, axles and shafts are of steel. You still see the old ones in the English countryside winching timber, hauling hay, and in stationary operations such as driving saws, threshing machines and the like. They were so versatile that specially adapted, they were even used as plowing engines in pairs, one either side of the field, winching the plow to and fro between them; in shipyards, they were fitted with cranes and were in fact the earliest type of mobile crane. It was a brute, and this is some toy! It develops a strong 1/15 hp at 3000 rpm, will haul a good size log, can be used to operate other stationary models. 1 ft. long. Uses alcohol. \$35 and worth it!

MAIL THIS MONEY-BACK GUARANTEE COUPON TODAY!

HAMILTON HOUSE, Dept. 381-3, Cos Cob, Conn. 06807

Enclosed check or m.o. for \$ _____

_____ English Live-Steam Tractor @ \$35

_____ Companion English Live-Steam Roller @ \$35

_____ Both for special price of \$65

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

The Listener

Continued from page 34

which, as a matter of fact, aren't pink at all but white.

Under normal circumstances, one always should wait three months before sending a follow-up inquiry regarding a verification request. After all, large stations have tremendous volumes of mail to contend with; smaller stations often are short on personnel. Further, if your QSL is sent via surface mail, this, too, takes additional time.

Even after a three-month interval, it's advisable to ask yourself whether you really included enough program data to prove reception, though the question actually never should require asking. If the answer is yes and you can't draw up a second report based on fresh, up-to-date reception, only then should you send an intelligently planned follow-up.

Hi-Fi Today

Continued from page 52

R34, Stanton 800B, Thorens TD-150 and Weathers Townsend. Average price tag for the new generation of turntables is roughly \$80, or about half what a top-flight transcription combination would have cost you in 1960.

If turntables are quieter than ever these days, so are tapes. Fact is, Ampex, Audio Devices and 3M recently have marketed new low-noise series of raw tapes; Ampex's is called the 500 Series, Audiotape's is dubbed Formula 15, while 3M labels theirs Dynarange and settles for 200 as a series number. According to 3M, the drop in background noise on their tape is such that you can record at 3¾ ips with the kind of fidelity once obtainable only at 7½ ips.

Audiotape says the intent is to provide a high signal-to-noise ratio under all recording conditions. As for Ampex, the claim of drastically lower noise seems well confirmed by the Ampex-processed prerecorded tapes I've heard over the past few months. Background noise on the best of the new commercial releases has dropped to the point where you can play them at threshold-of-pain volume with hardly a hint of tape hiss.

color coded nutdrivers now in new, handy kits

FOR BENCH, WALL OR TOOL BOX

Sturdy, new pebble-grain plastic cases provide handy means for keeping nutdrivers in good order on the workbench or in tool box for service calls. Lids snap shut, lock tight to protect tools. No. 77 case has hole in lid lock for wall hanging. . . molded compartments keep tools from tumbling out.



No. 77
SOLID SHAFT
NUTDRIVER KIT
7 Hex Openings:
3/16", 7/32", 1/4", 5/32",
3/16", 11/32", 3/8"

No. HS6-18
HOLLOW SHAFT
NUTDRIVER KIT

10 Hex Openings:
3/16", 7/32", 1/4", 5/32", 3/16",
11/32", 3/8", 7/16",
1/2", 3/4"



PROFESSIONAL QUALITY

Precision fit, case-hardened sockets; polished and plated steel shafts; shockproof, breakproof, color coded plastic (UL) handles.

XCELITE

XCELITE INC. • 16 BANK ST., ORCHARD PARK, N. Y.
Send Catalog 162 with information on 77 and HS6-18 sets.

name _____

address _____

city _____

state & zone _____

ELECTRONICS ILLUSTRATED

Classified Ads

Your advertisement can reach this mail-buying audience for only 50¢ per word . . . payable in advance (Check or M.O. please) . . . minimum 10 words. Closing dates are the 20th of 4th preceding month i.e. copy for the July issue must be in our office by March 20th. Mail to ELECTRONICS ILLUSTRATED, 67 West 44th St., New York 36, N. Y. Word count: Zipcode number free. Figure one word: Name of state (New Jersey), name of city (New York); sets of characters as in key (14-D); also abbreviations as 35MM. 8x10, D.C., A.C.

SAVE MONEY • ORDER BY MAIL

• • • FOR SALE

JEeps FROM \$53.90 . . . Trucks from \$78.40 . . . Boats, Typewriters, Airplanes, Electronic Equipment, 100,000 Bargains "as is" Direct From Government in Your Area. Complete Sales Directory and Surplus Catalog \$1.00 (Deductible First \$10.00 Order). Surplus Service, Box 820-T, Holland, Michigan.

JAPAN & HONG Kong Electronics Directory. Products, components, supplies. 50 firms—just \$1.00. Ippano Kaisha Ltd., Box 6266, Spokane, Washington 99207.

GOVERNMENT SURPLUS. How and Where to Buy in Your Area. Send \$1.00. E.I. Surplus Information, Headquarters Bldg., Washington 6, D. C.

CONVERT ANY television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans, \$2.00. Relco-A19, Box 10563, Houston 18, Texas.

GOVERNMENT SURPLUS Jeeps from—\$52.50, Voltmeters from—\$1.05, Transmitters from—\$6.18, Oscilloscopes, Walkie-Talkies, Multimeters. Typical "As Is" Bid Bargains From Uncle Sam. Tremendous Variety. Exciting Free List. Write: Enterprises, Box 402-P4, Jamaica, New York 11430.

INVESTIGATORS, FREE Brochure, latest subminiature electronic surveillance equipment. Ace Electronics, 11500-X NW 7th Ave., Miami, Florida. 33168.

NEW SUPERSENSITIVE transistor locators detect buried gold, silver, coins. Kits, assembled models, \$19.95 up. Free catalog. Relco-A19, Box 10563, Houston 18, Texas.

PRINTED ENVELOPES, gummed labels, business cards. Free samples. G. Skollingsberg, 2737 Lake Street, Salt Lake City, Utah 84106

REMOTE CONTROL Device Small hand held ultrasonic transmitter controls lamps, TV, anything electrical. Full plans and parts information, \$2.00. Electronic Specialists, Box 9339, Rochester, New York 14604

MAGNETS, ALNICO, Ceramic, Flexible, Assemblies. What you need, we have. Maryland Magnet, 5412F Gist, Baltimore, Maryland 21215.

• • • BUSINESS OPPORTUNITIES

GET INTO Custom Upholstery. Turn Old Furniture into big \$\$\$ spare time. Reupholster chairs, divans like new. Make custom slip covers, drapes. No experience required. We supply everything. Write for Big Free Illustrated Book on Easy Home Instruction and how we start you in big \$\$\$ home business. Modern Upholstery Institute, Box 899-SA, Orange, Calif.

BIG MONEY. Learn Electric Appliance Repairing at home in your spare time. How automatic washer-dryers, refrigerators, and all kinds of appliances work, how to find what's wrong, using the Christy Electronic Trouble Tracer, how to fix them. We show you how to get business, what to charge, how to buy parts wholesale. Make \$6-7 per hour by operating your own fix-it shop in your kitchen or basement. No previous experience or training required. Enroll now—pay later from earnings. Send for Free Book. Christy Trades School, 3214 W. Lawrence Ave., Dept. A-1613, Chicago 60625.

INVESTIGATE ACCIDENTS. Earn \$750 to \$1,100 monthly. Men urgently needed. Car furnished. Expenses paid. No selling. No college education necessary. Pick own job location. Investigate full time. Or earn \$8.44 hour spare time. Write for Free Literature. No obligation. Universal, CEE-3, 6801 Hillcrest, Dallas, Texas 75205.

FREE REPORT, "Businesses You Can Launch At Home." Immediate earnings! Wyman Enterprises, B-35, Congers, N. Y. 10920.

VENDING MACHINES—No selling. Operate a route of coin machines and earn high profits. 32-page catalog free! Parkway Machine Corp., 715E1 Ensor St., Baltimore 2, Md.

• • • EMPLOYMENT OPPORTUNITIES

PRINTING - ADVERTISING SALESMEN. Excellent moneymaking sideline selling Decalcomania Name Plates. Advertising Specialties. Sign letters, Automobile initials. Free Samples. "Ralco"-El, Box L, Boston 19, Mass.

• • • EDUCATION & INSTRUCTION

ELECTRONICS CAREER—F.C.C. License Training. Correspondence, or resident classes. Free details. Write: Dept. 8, Grantham Schools, 1505 N. Western, Hollywood, Calif. 90027.

LEARN TECHNICAL Writing at home. Free Brochure. California Educational Enterprises, (D-1), P.O. Drawer XX, Palm Springs, Calif. 92263.

IBM 1401 PROGRAMMING Can be learned by Home Study. For information write SAS, P.O. Box 437, New York 10009

• • • BUILD IT-DO IT YOURSELF

AUTOMATIC WASHER Repair Manuals for: Frigidaire, General Electric, Hamilton, Hotpoint, Kelvinator, Kenmore, Norge, RCA Whirlpool, Speed Queen, Maytag, Westinghouse \$2.50 ea. ppd. Major Appliance, 13106 Caine Ave. (Dept. J), Cleveland 5, Ohio.

MELODY ORGAN, easy to build. Demonstration Record, \$1.00. Construction Manual \$3.00. Free folder. Solotron Company, 29641 Gilchrist, Farmington, Mich.

IT'S SUPERCALIFRAGILISTICEXPIALIDOCIOUS. Free information about Kit-of-the-Month Club, Catalog of Etched Circuit Boards, Radio Books, exclusive items. Leader Enterprises, Box 44718KQ, Los Angeles, 90044.

• • • TAPE RECORDERS

LEARN WHILE Asleep with your recorder, phonograph or amazing new "Electronic Educator" endless tape recorder. Details free. Sleep-Learning Research Association, Box 24-E1, Olympia, Washington.

RENT STEREO Tapes—over 2500 different—all major labels—free brochure. Stereo-Parti, 1616-AY Terrace Way, Santa Rosa, California.

• • • RADIO & TV

BEFORE YOU Buy Receiving Tubes, Transistors, Diodes, Electronic Components & Accessories . . . send for your Giant Free Zalytron Current Catalog, featuring Standard Brand Tubes: RCA, GE, etc.—all Brand New Premium Quality Individually Boxed, One Year Guarantee—all at Biggest Discounts in America! We serve professional servicemen, hobbyists, experimenters, engineers, technicians. Why Pay More? Zalytron Tube Corp., 469-L Jericho Turnpike, Mineola, N. Y.

DIAGRAMS—SENT Airmail—Television \$3.00. Radio 1919-1965 \$2.00. Give model. Diagrams, Box 55E1, Williamsport, Pa. 17704.

FREE! GIANT bargain catalog on transistors, diodes, rectifiers, SCR's, zeners, parts. Poly Paks, P. O. Box 942E1, Lynnhfield, Mass.

15 DISTANCE ONE-TUBE plans—25¢. "One Tube Handbook"—50¢. Includes Transistor experiments, catalog. Laboratories, 993-K, Redwood City, Calif. 94064.

FREE CATALOG. Electronic parts, tubes. Wholesale. Thousands of items. Unbeatable prices. Arturus Electronics EL, 502-22 St., Union City, N. J. 07087

McGEE RADIO Company. Big 1966 Catalog Sent Free. America's Best Values, HiFi—Amplifiers—Speakers—Electronic Parts. Send Name, Address And Zip Code Number To McGee Radio Company, 1901 McGee Street, Dept. E1, Kansas City, Missouri 64108

TV TUNERS rebuilt and aligned per manufacturers specification. Only \$9.50. Any make UHF or VHF. We ship COD. Ninety day written guarantee. Ship complete with tubes or write for free mailing kit and dealer brochure. JW Electronics, Box 51K, Bloomington, Indiana.

FREE ELECTRONICS Catalog. Tremendous bargains. Electrolabs, Department C-572AE, Hewlett, New York 11557.

RADIO & T.V. Tubes—33¢. Free List. Cornell, 4213-15 University, San Diego, Calif. 92105.

• • • MISCELLANEOUS

WINEMAKERS—MAKE Strongest Brews Yourself! Booklet of Formulas, \$2.00. (Supplies, Hydrometers, Equipment Headquarters.) Research Enterprises, 29-B5 Samoset Road, Woburn, Mass.

HYPNOTIZE SECRETLY, cleverly, one glance or money-back. \$2. Elton's, Box 18223-E2, Indianapolis, Indiana, 46218.

HARD-TO-FIND Tools for electronics, instrument makers, clocks. Catalog 10¢. Brookstones, Worthington, Massachusetts 01098.

GADGETEERS—GET your name on our mailing list for free catalog and monthly flyers. Earl's Supply Co., P.O. Box 265, Lawndale, Calif. 90260.

TREASURE, GOLD, Silver, Relics. New 1966 detectors now available. Free information. Rayscope, Dept. 3-L, Box 715, North Hollywood, California.

"WINEMAKING," "BEER, Ale." Strongest methods. Illustrated. \$2.20. Eaton, Box 543-L, Hopland, California.

• • • MUSIC

ACCORDIONS, GUITARS, Band Instruments! Save to 50%. Terms. Trades. Free trial. Free catalog. Mention instrument. Music Mart, 5535-(EL) Belmont, Chicago 60641.

• • • INVENTIONS & INVENTORS

INVENTORS! WE will develop, sell your idea or invention, patented or unpatented. Our national manufacturer-clients are urgently seeking new items for highest outright cash sale or royalties. Financial assistance available. 10 years proven performance. For Free information write Dept. 59, Wall Street Invention Brokerage, 79 Wall Street, New York 5, N. Y.

INVENTORS! HIGHEST cash sale or royalties for your inventions. Patented-Unpatented. Urgent demand from our client manufacturers. Financial Assistance available. Write Dept. 45, United Invention Brokerage, 78 Wall Street, New York 5, N. Y.

• • • ROCKETS

ROCKETS: IDEAL for miniature transmitter tests. New illustrated catalog 25¢. Single and multistage kits, cones, engines, launchers, trackers, technical information, etc. Fast service. Estes Industries, Penrose 13, Colorado.

• • • PERSONAL

KNOW YOUR I.Q. Free Sample. Test Center, Box 139E, Fresh Meadows, New York, 11365.

CB Corner

Continued from page 56

plumping for 30-watt transmitters and the setting aside of two frequencies—27.235 and 27.245 mc—for HELP traffic.

At least one CB manufacturer already has announced a rig to meet the proposed power rating. The company is Squires-Sanders; the rig is Thor Eleven. Actually, the transceiver now can be used in the business band which overlaps the standard 27-mc

channels. But it also indicates the company's confidence that HELP will loom large in highway communications.

Aside from crystal control on business-band frequencies, the receiver is tunable through the conventional Citizens Band. Its transmitter also can be equipped with crystals for the two proposed HELP frequencies.

If predictions are correct, prime users of this high-power equipment would be the nation's garages. The rig would provide them with a strong—30 watt—voice for communicating with the motoring CB public.

INSTANT EMERGENCY COMMUNICATIONS

WITH PEARCE-SIMPSON'S

SENTRY  \$99.90

6 Channel Transistorized CB Two-Way Radio

Ultra-compact and featuring an all transistor power supply and receiver, the Sentry is ideal for mobile operation. It takes no more current to operate than a dashboard clock and transmits a powerful signal even when car battery is so low it will not turn over the engine.



The Sentry, designed for the Highway Emergency Locating Plan (H.E.L.P.) puts the stranded motorist in touch with thousands of H.E.L.P. monitors along the nation's highways

Pearce-Simpson, Inc.
P. O. Box 800—
Biscayne Annex,
Miami, Florida 33152

Please send full information and model specifications.

Name _____

Address _____

City _____ State _____

EI-366



ALL SOLID STATE CB'S



The DIRECTOR
23 Channel CB
\$299.90

The ESCORT II
11 Channel CB
\$239.90

PEARCE-SIMPSON, INC.
MIAMI, FLORIDA

American Basic Science Club's Master Lab... a HOME SCIENCE LAB AND COURSE

You Get ALL the Following Equipment in 9 Monthly Kits

ELECTRICAL LAB

All the equipment for basic electrical experiments with Wheatstone Bridge (measures resistance), Magnetizer and De-magnetizer, Thermocouple, Potentiometer, Continuity Tester, Extinction Voltmeter, Saturated Core Tester, Electromagnetic Battery, Neon Lamp, Galvanometer, Instruction Call, Resistor, Chemicals and Electrodes for Plating and Electrolysis. FOR SAFETY a step-down Isolator Transformer provides required current.

(Available as a Separate Unit for \$8.95 Postpaid)

STROBE LIGHT

A Neon Lamp that flashes at intervals you can synchronize with the speed of rotating or vibrating objects in order to "freeze" their motion to permit close study and checking frequencies and RPM. Flashes are timed by a high speed Oscillator, Operates on the Mains or Lab DC Power Supply. (When bought as a separate unit uses a 90 V Battery that is included in unit price.)

(Available as a Separate Unit for \$7.95 Postpaid)

PHOTOELECTRIC RELAY

Crystal PhotoCell, Electronic Amplifier, Relay, Large Condenser Lens in Cabinet Mount. Features automatic "on-or-off" or holding current operation. Sensitivity Control. Plug-in Outlet for controlled circuit. Use for alarms, counters, etc. Operates on 115V AC. A basic unit for many exciting experiments.

(Available as a Separate Unit for \$8.95 Postpaid)

ANALOG COMPUTER

Electronic Computer multiplies, divides, calculates powers, roots, logarithms. Set up the problem on the scales of two linear potentiometers and find the answer by listening for the null point on the third potentiometer. More accurate, educational, and practical than similar computers that sell for several times the price. Easy to assemble. Complete with Handbooks.

(Available as a Separate Unit for \$4.95 Postpaid)

LIGHT AND OPTICS LAB

Exciting optical projects for the study of light. Equipment includes: Five Fresnel Lenses, Prism, Polarizing Filter, Diffraction Grating, Mirror, Telescoping Tubing, Lens Mounts Tube Holders and Brackets. All the parts and instructions to build a Microscope Camera Obscura, Camera Lucida, Polariscopes, Photometer and many other optical devices.

(Available as a Separate Unit for \$6.95 Postpaid)

PHOTOGRAPHY LAB

A PRECISION 35MM ENLARGER... horizontal type with twin condensing lenses and 3" F11 projection lens. Produces quality enlargements up to 8" x 10". Contact Print Frame takes negatives up to 3 1/2" x 4 1/2". 3 Plastic Developing Trays, Neon SafeLight, Hand Thermometer, Film Clips, Developing Chemicals, Printing and Enlarging Paper and Darkroom Traybook. Makes quality enlargements for 6c. Makes prints for only 2c.

(Available as a Separate Unit for \$9.95 Postpaid)

RADIO LAB AND COURSE

SHORTWAVE AND BROADCAST RADIOS - 3-tube regenerative circuit. Use 115V AC house current. Complete with headset. CARBON MICROPHONE and 2-stage AUDIO AMPLIFIER. RADIO TRANSMITTER for code or voice. RIPPLE TANK WAVE GENERATOR with variable frequency. Produces waves, nodal lines, etc. Invaluable in understanding wave theory. SIGNAL TRACER, SOLDERING IRON and CONTINUITY TESTER. Volume! Troubleshooting tools. Use explained in accompanying manual "Simplified Radio-TV Servicing".

(Available as a Separate Unit for \$17.80 Postpaid)

DC POWER SUPPLY

Changes regulate 110-120V AC to the direct current required for electronic projects and experimenting. Consists of a Power Transformer, Vacuum Tube Rectifier, 20,700MFD Capacitor Filter Circuit, and a Potentiometer Voltage Selector. Dial Control for 0 to 85V. A safe isolated Power Supply that eliminates the need of expensive multi-volt batteries.

(Available as a Separate Unit for \$3.95 Postpaid)

PHOTOMICROGRAPHY LAB

"Projection-Type" Camera takes and prints pictures of subjects mounted on microscope slides. Enlarges up to 100 times. Takes the place of microscope, camera and printer. No other equipment needed. Includes: Developing Trays, Chemicals, Paper, Microscope Slides and Safe Light. Uses standard sizes of regular roll film.

(Available as a Separate Unit for \$7.95 Postpaid)

SLIDE PROJECTOR

Has interchangeable lenses... one for standard 35MM slides, and the other, with greater magnification, for microscope slides. Comes with 140 watt GE Projection Lamp, Large Twin Condensing Lenses for extra brightness, sturdy Steel Housing with view chimney and buff for cool operation.

(Available as a Separate Unit for \$6.95 Postpaid)

LIGHT TRANSMITTER-RECEIVER

TRANSMITTER consists of a Light Source, a Modulating Reflector Diaphragm and an Optical Projection System. THE RECEIVER is a Two-Stage Audio-Amplifier, controlled by a Photo-electric Cell that catches the projected light beam and causes the original sound waves to be reproduced in the headphones. Talking on a Light Beam.

(Available as a Separate Unit for \$14.95 Postpaid)

ATOMIC ENERGY LAB

ATOMIC CHAMBER WITH PROCTOR ILLUMINATOR. See the vapor trails of alpha and beta particles, and of cosmic rays. SPINTHARISCOPES. Shows exploding atoms. ELECTROSCOPES — metal housed with Scales and Magnifying Viewers. Measures back ground radiation and tests sample sources. SAFE RADIOACTIVE MATERIALS. Alpha Source in handy container and Uranium Ore. Full instructions and explanations open up the fascinating field of nuclear physics.

(Available as a Separate Unit for \$6.95 Postpaid)

SPECTROSCOPE

Analyze spectra of glowing gases. See and identify the Fraunhofer Lines. A quality instrument featuring an easy-to-read built-in scale and a powerful condensing system for a bright spectrum. Equipment includes Alcohol Burner and a 2 Watt Neon Spectral Lamp. Full instructions cover theory and use.

(Available as a Separate Unit for \$5.95 Postpaid)

ULTRAVIOLET LAMP

140 watt Filter type UV LAMP. Heavy metal cabinet. 6 Foot Cord, Rotary Switch. Produces dazzling color effects with invisible black light. Has many uses in the fields of Mineralogy, Crime Detection and Science. Accessories include invisible Ink, Tracer Powder, Fluorescent Crayons.

(Available as a Separate Unit for \$6.95 Postpaid)

SURVEYOR'S TRANSIT

A practical Transit 42 and image telescope with Range Rider Reticle for measuring remote distances and heights. Vernier reading for both horizontal and vertical scales. Leveling Head with Thumb Screw Adjustment and Spirit Level. Clamps under hood hold wooden legs of Tripod. (Legs not included.) Instructions cover elementary surveying, range-finding.

(Available as a Separate Unit for \$5.95 Postpaid)

TELESCOPE AND MOUNT

30X erect image. Extends to 20" length. Five ground and polished Lenses. Ramsden Eyepiece. Sturdy Equatorial Mount makes it easy to follow the movement of heavenly bodies. Mount has fittings for wooden legs that complete the tripod (legs not included).

(Available as a Separate Unit for \$4.95 Postpaid)

WEATHER STATION

A REMOTE READING ANEMOMETER AND WIND VANE... Flashing Neon Light on Indoor Indicator board show wind speed and direction. Operates on less than 1 cent per month. Safety Power Cord makes all connections safe. 150 ft. of Lead in Wire. Plus... Air Temp. Barometer with 4 ft. indicator column. Sling Psychrometer measures relative humidity. Rain Gauge measures rainfall to 1/100 inch. ALSO Cloud Chart, Weather Map and Forecasting Manual — a complete set-up for amateur meteorology.

(Available as a Separate Unit for \$7.95 Postpaid)

9 KIT MASTER LAB Includes ALL the Equipment for ALL the Above... only \$37.55

SEND \$200 WITH ONLY COUPON PAY \$395 PLUS POSTAGE FOR EACH OF THE 9 KITS. ONE-A-MONTH CANCEL ANY TIME YOU WISH — MONEY BACK IF NOT DELIGHTED

MULTI-USE DESIGN — A MASTER LAB FEATURE

All the above equipment, as separate units, adds up to \$1400. How can the 9 kit Master Lab have it all for only \$37.55? Multi-use design is the answer. For example: The Slide Projector quickly and easily converts into the Photo-Enlarger, Spectroscopic, Cloud Chamber Illuminator. Similarly, the Transit Head doubles as a Telescope Mount. Such multi-purpose design makes possible an all-science lab of an unheard-of low price. Multi-purpose design is used only where it is advantageous, and not for such applications as the permanently-mounted weather instruments, where it would not be practical.

KIT-A-MONTH — OR ALL AT ONCE Get Master Lab on either plan (see coupon). You may start with the Kit-A-Month plan, and at any time get the balance of the 9 kit series in one shipment by sending \$3.95 for each of the unshipped kits.

SEPARATE UNITS ALL GOOD BUYS You can order any of the individual units and be sure that it is a quality item and the best value in its field. The Master Lab, however, is the "buy of buys" and every science-minded person should try it.

NO EXPERIENCE NECESSARY — IT'S EASY! IT'S FUN!

You will enjoy the easy-to-use equipment and the exciting learn-by-doing course. The 9 instruction manuals and the 6 auxiliary text books are expertly written and clearly illustrated. Over 490 pages. Over 280 illustrations. A real science course for a solid science background.

ACCLAIMED BY EDUCATORS

Everyone interested in science should have your enjoyable kits. You are doing a wonderful job.

Allen T. Ayers, Physics Dept. Jameson High School, Jameson, N. Y.

FREE with first kit!
MYSTERY SHOCK BOX
 Yours to keep even if you return the kit for full refund

KIT-A-MONTH... THE EASY WAY TO A WONDERFUL LAB

* You take only as many kits as you wish — no obligation.
 * You may return any kit and receive full refund.
 These "No Risk" assurances because we know... you'll be amazed and delighted. The first kit will convince you that you want the Master Lab.

Send \$2 today — get your first kit on its way!

All Orders on 10 Day Approval — Your Satisfaction or Your Money Back

- Start sending me the MASTER LAB in 9 monthly kits. I enclose \$2.00 and will pay \$3.95 plus COD postage on receipt of each kit. I may cancel unshipped kits at any time.
- Send me complete MASTER LAB (all 9 kits) in one shipment I enclose \$37.55 Full Payment, Postage Paid.
- Send me only the _____ Unit. I enclose \$ _____, Full Payment, Postage Paid.

Name _____
 Address _____
 City & State _____ (ZIP CODE _____)

AMERICAN BASIC SCIENCE CLUB, INC.
 501 East Crockett St. San Antonio, Texas 78202

FREE

1966 HEATHKIT® CATALOG World's Largest Selection Of "Do-It-Yourself" Electronic Kits



NEW Low Price On Heathkit 21" Color TV Only \$375
Plus New 25" Rectangular-Tube Color TV Kit . . . \$469.95



NEW All-Transistor 30-watt FM/FM Stereo Receiver Only \$99.95



NEW SSB 80-10 Meter Amateur Transceiver . . . Only \$360



NEW 10-Band Transistor Shortwave Portable Only \$159.95



NEW Crystal-Controlled 23-Channel, 5-Watt, All-Transistor CB Transceiver . . . Only \$89.95

- ★ Complete Selection of Portable and Table Model AM, FM and Shortwave Radios.
- ★ Home & Hobby Items . . . Intercoms, Garage Door Opener, Automotive Kits, Tools.
- ★ Famous Heathkit/Thomas Transistor Electronic Organs.
- ★ Heathkit Stereo/Hi-Fi Components . . . Tuners, Amplifiers, Speakers, Turntables, Cartridges, Furniture.
- ★ Citizen's Band Radio . . . Transceivers, Walkie-Talkies, Accessories.
- ★ Heath Educational Kits For Home Or Classroom Study.
- ★ World's Largest Selection Of Amateur Radio Gear.
- ★ Lab & Test Instruments For Home Workshop, Industrial & Educational Use.

Why Millions Choose Heathkit® Electronics

- ★ Biggest Selection . . . Over 250 Kits
- ★ Do-It-Yourself Plus Factory-To-You Savings . . . Up To 50%
- ★ Easiest To Build . . . Famous Heath Step-By-Step Instructions & Large Diagrams Assure Your Success
- ★ No Money Down On Up To \$300
- ★ Free Technical Consultation On Selection & Assembly
- ★ Highest Quality Parts . . . For Long, Dependable Performance

Send For FREE Catalog Today!



39-3



Please Send My FREE 1966 Heathkit Catalog.

Name _____

Address _____

City _____ State _____ Zip _____

CL-230

EXPLORE

The Space-Age World Of Electronic Kits...

With This
FREE
1966
HEATHKIT®
Catalog.



Over 250
Home & Hobby
Kits You
Can Build!

PLACE
5c
STAMP
HERE

HEATH COMPANY
BENTON HARBOR,
MICHIGAN 49023

MAIL TODAY
For Your **FREE**
Copy!

108 pages . . . many in full color . . . contain illustrations, descriptions, specifications and prices of over 250 easy-to-build kits. Illustrates actual assembly manual pages so you can see how fast and easy they are to build. Save up to 50%. Use this card to get your **FREE** copy, or write Heath Company, Benton Harbor, Michigan 49023.