



THE ELECTRONICS, SCIENCE & TECHNOLOGY MONTHLY

SEPTEMBER 1990 £1.60

CROSSOVER NETWORKS
DATA COMMUNICATIONS
VCR AIRWAVE CONTROL

MICROWAVES
SLIDE PROJECTOR
CONTROLLER

MUSIC RELAY SYSTEM
SURFACE MOUNT RECEIVER

ISSN 0142-7229



dmp POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

OMP POWER AMPLIFIER MODULES

Supplied ready built and tested.

OMP POWER AMPLIFIER MODULES Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP100 Mk 11 Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 355 x 115 x 65mm. PRICE £33.99 + £3.00 P&P.

NEW SERIES II MOS-FET MODULES



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor, >300, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm. PRICE £39.99 + £3.00 P&P.



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 155 x 100mm. PRICE £62.99 + £3.50 P&P.



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 175 x 100mm. PRICE £79.99 + £4.50 P&P.

NOTE— MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS, STANDARD — INPUT SENS. 500mV BAND WIDTH 100KHz, PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) — INPUT SENS. 775mV, BAND WIDTH 50KHz, ORDER STANDARD OR PEC



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 + 50p P&P.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE S.A.E. (30p STAMPED) FOR COMPLETE LIST.

McKENZIE— INSTRUMENTS, P.A., DISCO, ETC.

ALL MCKENZIE UNITS 8 OHMS IMPEDENCE

- 8" 100 WATT C8100GPM GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO RES, FREQ. 80Hz, FREQ. RESP. TO 14KHz, SENS. 99dB. PRICE £29.30 + £2.00 P&P
- 10" 100 WATT C10100GP GUITAR, VOICE, ORGAN, KEYBOARD, DISCO, EXCELLENT MID RES, FREQ. 70Hz, FREQ. RESP. TO 6KHz, SENS. 103dB. PRICE £35.58 + £2.50 P&P
- 10" 200 WATT C10200GP GUITAR, KEYBOARD, DISCO, EXCELLENT HIGH POWER MID RES, FREQ. 45Hz, FREQ. RESP. TO 7KHz, SENS. 103dB. PRICE £48.67 + £2.50 P&P
- 12" 100 WATT C12100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO RES, FREQ. 45Hz, FREQ. RESP. TO 7KHz, SENS. 98dB. PRICE £37.59 + £3.50 P&P
- 12" 100 WATT C12100TC TWIN CONE) HIGH POWER WIDE RESPONSE, P.A., VOICE, DISCO RES, FREQ. 45Hz, FREQ. RESP. TO 14KHz, SENS. 100dB. PRICE £38.58 + £3.50 P&P
- 12" 200 WATT C12200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. RES, FREQ. 40Hz, FREQ. RESP. TO 7KHz, SENS. 100dB. PRICE £65.79 + £3.50 P&P
- 12" 300 WATT C12300GP HIGH POWER BASS LEAD GUITAR, KEYBOARDS, DISCO, ETC. RES, FREQ. 45Hz, FREQ. RESP. TO 5KHz, SENS. 100dB. PRICE £87.51 + £3.50 P&P
- 15" 100 WATT C15100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO RES, FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB. PRICE £55.05 + £4.00 P&P
- 15" 200 WATT C15200BS VERY HIGH POWER BASS RES, FREQ. 40Hz, FREQ. RESP. TO 4KHz, SENS. 99dB. PRICE £75.10 + £4.00 P&P
- 15" 250 WATT C15250BS VERY HIGH POWER BASS RES, FREQ. 40Hz, FREQ. RESP. TO 4KHz, SENS. 99dB. PRICE £82.54 + £4.00 P&P
- 15" 400 WATT C15400BS VERY HIGH POWER, LOW FREQUENCY BASS. RES, FREQ. 40Hz, FREQ. RESP. TO 4KHz, SENS. 102dB. PRICE £96.47 + £4.50 P&P
- 18" 400 WATT C18404BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. RES, FREQ. 27Hz, FREQ. RESP. TO 3KHz, SENS. 99dB. PRICE £172.06 + £5.00 P&P

EARBENDERS— HI-FI, STUDIO, IN-CAR, ETC.

- ALL EARBENDER UNITS 8 OHMS** (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED FOAM SURROUND**
- 8" 50 WATT EB8-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR RES, FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 97dB. PRICE £8.90 + £2.00 P&P
- 10" 50 WATT EB10-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR RES, FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB. PRICE £12.00 + £2.50 P&P
- 10" 100 WATT EB10-100 BASS, HI-FI, STUDIO RES, FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS. 96dB. PRICE £27.76 + £3.50 P&P
- 12" 60 WATT EB12-60 BASS, HI-FI, STUDIO RES, FREQ. 28Hz, FREQ. RESP. TO 3KHz, SENS. 92dB. PRICE £21.00 + £3.00 P&P
- 12" 100 WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES, FREQ. 26Hz, FREQ. RESP. TO 3KHz, SENS. 93dB. PRICE £38.75 + £3.50 P&P
- FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
- 5 1/4" 60 WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS. 92dB. PRICE £9.99 + £1.50 P&P
- 6 1/2" 60 WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 30Hz, FREQ. RESP. TO 20KHz, SENS. 94dB. PRICE £10.99 + £1.50 P&P
- 8" 60 WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS. 96dB. PRICE £12.99 + £1.50 P&P
- 10" 60 WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS. 86dB. PRICE £16.49 + £2.00 P&P

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

- 3W FM TRANSMITTER** 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.49 + £1.00 P&P
- FM MICRO TRANSMITTER** (BUG) 100-108MHz, VARICAP TUNED COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATT, PRICE £8.62 + £1.00 P&P

3 watt FM Transmitter




POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS WELCOME FROM SCHOOLS, COLLEGES, GOVT. BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA ACCESS ACCEPTED BY POST, PHONE OR FAX.



* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E., 30p STAMPED FOR CURRENT LIST.

OMP VARISPEED TURNTABLE CHASSIS

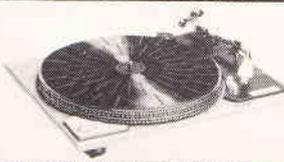

- * MANUAL ARM
- * STEEL CHASSIS
- * ELECTRONIC SPEED CONTROL 33 & 45
- * VARI PITCH CONTROL
- * HIGH TORQUE SERVO DRIVEN DC MOTOR
- * TRANSPARENT SPINDLE
- * 12" DIE CAST PLATTER
- * NEON STROBE
- * CALIBRATED BAL WEIGHT
- * REMOVABLE HEAD SHELL
- * CARTRIDGE FIXINGS
- * GUELEVER
- * POWER 220/240V 50/60Hz
- * 390 x 305mm
- * SUPPLIED WITH MOUNTING CUT-OUT TEMPLATE

PRICE £59.99 + £3.50 P&P.

OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500
PRICE £16.99 + 50p P&P

GOLDRING G850
PRICE £6.99 + 50p P&P

OMP MOS-FET POWER AMPLIFIERS, HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



NEW MXF SERIES OF POWER AMPLIFIERS

THREE MODELS— MXF200 (100w + 100w)

MXF400 (200w + 200w) MXF600 (300w + 300w)

All power ratings R.M.S. into 4 ohms.

FEATURES: * Independent power supplies with two Toroidal Transformers * Twin L.E.D. Illuminators * Rotary indexed level controls * Illuminated on/off switch * KLR connectors * Standard 75mm inputs * Open and short circuit proof * Latest Mos-Fets for stress free power delivery into virtually any load * High slew rate * Very low distortion * Aluminium cases * MXF600 Fan Cooled with D.C. Loudspeaker and Thermo Protection

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

- SIZES— MXF 200 W19" x H3 1/4" (2U) x D11"
- MXF 400 W19" x H5 1/4" (3U) x D12"
- MXF 600 W19" x H5 1/4" (3U) x D13"

MXF200 £171.35

MXF400 £228.65

MXF600 £322.00

SECURICOR DELIVERY £12.00 EACH



OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE



MADE ESPECIALLY TO SUIT TODAY'S NEED FOR COMPACTNESS WITH HIGH OUTPUT SOUND LEVELS. FINISHED IN HARDWEARING BLACK VINYL WITH PROTECTIVE CORNERS, GRILLE AND CARBON FIBRE HANDLE. INCORPORATES 1/2" DRIVER PLUS HIGH FREQ. HORN FOR FULL FREQ. RANGE 40Hz-20KHz BOTH MODELS 8 OHM. SIZE: 116" x 102" x 102".

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100 (100W 100dB) PRICE £159.95 PER PAIR

OMP 12-200 (200W 102dB) PRICE £209.95 PER PAIR

SECURICOR DEL.— £12.00 PER PAIR

IN CAR STEREO BOOSTER AMPLIFIER




TWO SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS

- 150 WATTS (75+75) INTO 4 OHMS
- 200 WATTS (100+100) INTO 4 OHMS
- FEATURES:
 - * HIGH & LOW INPUT IMPEDANCES
 - * HIGH & LOW INPUT SENSITIVITIES
 - * VARIABLE INPUT GAIN CONTROL
 - * SHORT CIRCUIT OUTPUT PROTECTION
 - * POWER REQUIREMENT 12V. D.C.
- PRICES: 150 WATT £43.00
- 200 WATT £26.00 + £3.00 P&P EACH

PIEZO ELECTRIC TWEETERS—MOTOROLA

PIEZO ELECTRIC TWEETERS — MOTOROLA

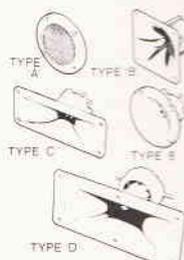
Join the Piezo revolution. The low dynamic mass (no voice coil), of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if you in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.



- TYPE A (KSN2006A)** 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each + 50p P&P.
- TYPE B (KSN1005A)** 3 1/2" super horn. For general purpose installations, stereo and P.A. systems etc. Price £5.99 each + 50p P&P.
- TYPE C (KSN2016A)** 2" x 4" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £5.99 each + 50p P&P.
- TYPE D (KSN1025A)** 2" x 4" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £5.99 each + 50p P&P.
- TYPE E (KSN1008A)** 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each + 50p P&P.
- LEVEL CONTROL** Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85mm. Price £3.99 + 50p P&P.

STEREO DISCO MIXER


STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features 5 inputs with individual faders providing a useful combination of the following— 3 Turntables (Mag), 3 Mics, 4 Line including CD plus Mic with talk over switch Headphone Monitor, Pan Pot L & R, Master Output controls, Output 775mV. Size 360 x 280 x 90mm. Supply 220-240V. Price £134.99 — £4.00 P&P

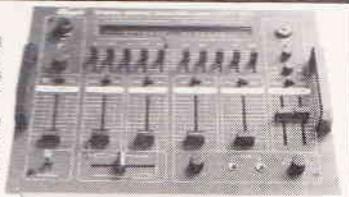

B. K. ELECTRONICS Dept EE
UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR
TEL: 0702-527572 FAX: 0702-420243

Interak 1

Bare Board
£17.50
(plus postage and VAT)

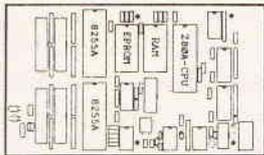

SINGLE BOARD COMPUTER "SBC-1"

A computer doesn't have to look like you'd expect a computer to look. It doesn't have to have a keyboard and a screen and floppy disks and so on.

The SBC-1 has the bare minimum of chips a Z80 computer can have and still be a computer: A 4MHz Z80A-CPU chip, an EPROM chip (up to 32K), a static RAM chip (up to 32K) and a pair of 8255A I/O (input/output) chips giving 48 individual lines to wobble up and down. There are one or two additional "glue" chips included, but these are simple "74LS" or "HC" parts.

A star feature is that no special or custom chips (ie PALs, ULAs, ASICs etc) are used — and thus there are no secrets. The Z80A is the fastest and best established of all the 8-bit microprocessors — possibly the cheapest too!

Although no serial interface is included, it is easy for a Z80A to wobble one bit up or down at the appropriate rate — the cost is a few pence worth of code in the program: why buy hardware when software will do?

Applications already identified include: Magnetic Card reader, mini printer interface, printer buffer, push button keypad, LCD alphanumeric panel interface, 40-zone security system, modem interface for auto sending of security alarms, code converter (eg IBM PC keyboard codes to regular ASCII), real time clock (with plug in module), automatic horticultural irrigation controller.

By disabling the on-board Z80A-CPU this card will plug into our Interak I CP/M Plus disk-based development systems, so if you don't fancy hand-assembling Z80 machine code you don't have to!

The idea is (if you are a manufacturer) you buy just one development system and then turn out the cheap SBC-1 systems by the hundred. If you are really lazy we can write the program for you and assemble the SBC-1 cards so you can get on with manufacturing your product, leaving all your control problems to us.

Greenbank

For more details write or phone us:
Greenbank Electronics, Dept. (T08E), 460 New Chester Road, Rock Ferry, Birkenhead, Merseyside L42 2AE. Tel: 051-645 3391.

Have



delivered to your door FREE!*



That's right, if you take out a year's subscription to ETI we will make sure that it is delivered to your door each month at no extra charge*. Just fill in the coupon below and send it to the address given with a cheque, money order or credit card instructions to cover the cost of the subscription. We'll do the rest.

UK: £19.20; EUROPE: £24.10; MIDDLE EAST: £24.40;
FAR EAST: £26.80; REST OF THE WORLD: £25.85
or USA: \$45.00

Airmail Rates on Request.

*Overseas subscription rates include postage.

Please commence my subscription to ETI with the issue. I enclose my cheque/
money order for £..... made payable to

ARGUS SPECIALIST PUBLICATIONS

Or Debit my Access/Visa

No.

Valid from to

Signature

Name

Address

..... Postcode

Send this form with your remittance to:
SELECT SUBSCRIPTIONS LTD., 5 River Park Estate,
Billet Lane, BERKHAMSTED, Herts. HP4 1HL,
United Kingdom

SURVEILLANCE PROFESSIONAL QUALITY KITS

A range of high quality kits as supplied to leading UK security companies, all in-house designed and produced, not to be confused with cheap imports. All kits come fully documented with concise assembly and setting-up details, fibreglass PCB and all components. All transmitters are fully tuneable and can be monitored on a normal VHF radio or tuned higher for greater security. Build-up service available if required.

MTX Micro-miniature audio transmitter. 17mm x 17mm. 9V operation. 1000m range **£12.95**

VT500 Hi-power audio transmitter. 250mW output. 20mm x 40mm 9-12V operation 2-3000m range **£15.95**

VOX75 Voice activated transmitter. Variable sensitivity. 30mm x 40mm 9V operation. 1000m range **£18.95**

CTX900 Sub-carrier scrambled audio transmitter. Cannot be monitored without decoder fitted to radio. 30mm x 40mm 9V operation. 1000m range **£21.95**

DSX900 Sub-carrier decoder unit for monitoring CTX900. Connects to radio earphone socket. Provides output for headphones. 35mm x 50mm 9-12V operation **£21.95**

HVX400 Mains powered audio transmitter. Connects directly to 240v AC supply. 30mm x 35mm. 500m range **£18.95**

XT89 Crystal controlled audio transmitter. High performance. 100mW output. Supplied with xtal for 108MHz. Others available to 116MHz. 85mm x 26mm. 9V operation. 2-3000m range **£36.95**

TKX900 Tracker/Beeper transmitter. Transmits continuous stream of audio pulses. Variable tone and rate. Powerful 200mW output. 63mm x 25mm 9V operation 2-3000m range **£21.95**

ATR2 Micro size telephone recording interface. Connects between telephone lines (anywhere) and cassette recorder. Tape switches automatically with use of phone. All conversations recorded. Powered from line. 10mm x 35mm **£12.95**

TLX700 Micro miniature telephone transmitter. Connects to line (anywhere) switches on and off with phone use. All conversations transmitted. 20mm x 20mm. Powered from line. 1000m range **£12.95**

XML900 RF bug detector. Variable sensitivity. Triggers LED and beeper when in presence of RF field. Detects MTX 15-20 feet. 55mm x 55mm. 9V operation **£26.95**

XL7000 Professional bug detector/locator. Variable sensitivity. Twin mode ten segment LED readout of signal strength with variable rate beeper. Second mode AUDIO CONFIRM distinguishes between localised bug transmission and normal legitimate signal such as pagers, cellular etc. 70mm x 100mm. 9V operation **£54.95**

UK customers please send cheques. PO's or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft or Eurocheque and add £5.00 per order for shipment. Credit card orders accepted on 0827 714476. Trade enquiries welcome. Send 30p stamp for full 1990 Catalogue.



THE WORKSHOPS
95 MAIN RD. BAXTERLEY
NR. ATHERSTONE
WARCS CV9 2LE



0827 714476


September
1990

VOLUME 19 No 9

Paul Freeman: Editor
Helen Oughton: Deputy Editor
Mark Webb: Group Editor
Ian Houston: Design

Cass Gilroy: Ad Manager
Ben Adewole: Executive Sales
Jerry Fowler: Technical Illustration
Mannie Cefai: Photography

REGULARS

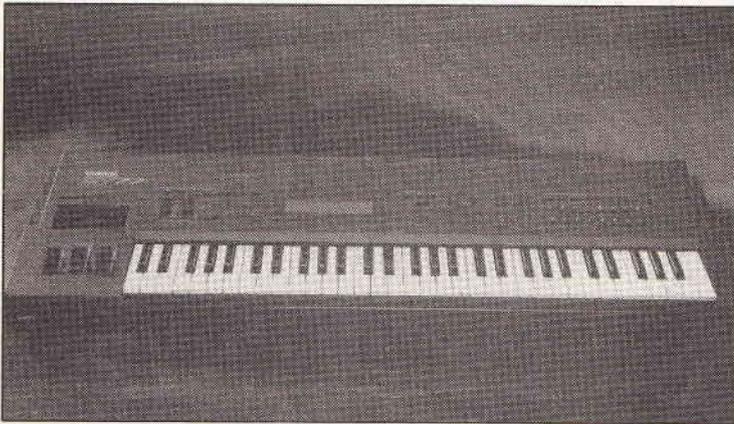

Page 37



Page 16

ISSN 0142-7229

ABC Member of the Audit Bureau of Circulation

ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications and any reproduction requires the prior written consent of the Company © 1990 Argus Specialist Publications. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

• Subscription rates — UK: £19.20. Europe: £24.10. Middle East: £24.40. Far East: £26.80. Rest: £25.85 or US\$45.00.



Argus House, Boundary Way,
Hemel Hempstead HP2 7ST
Tel: (0442) 66551 Fax: (0442) 66998

Read/Write
Your contribution to ETI.

6

Photocopies

8

Subscriptions Direct Debit

8

News

9

Open Channel

13

Blueprint

This month Andrew Armstrong looks at an idea to improve safety in the home.

14


Audio News

Microphones, mini-mixers and digital recorders this month.

42

PCB Service

57

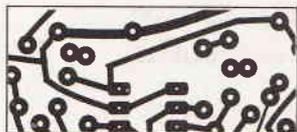

PCB Foil Patterns

62

Oops!

62

Classified Ads

64

Courses

65

ASP Reader Service

66

Ad Index

66

Next Month

66

Last Month

66

Published by Argus Specialist Publications, Argus House, Boundary Way, Hemel Hempstead HP2 7ST. Tel: (0442) 66551. UK newstrade distribution by SM Distribution Ltd., 6 Leigham Court Road, London SW16 2PG. Tel: 01-677 8111. Overseas and non-newstrade sales by Magazine Sales Department, Argus House, Boundary Way, Hemel Hempstead, HP2 7ST. Tel: (0442) 66551. Subscriptions by Select Subscriptions Ltd., 5 River Park Estate, Berkhamsted, Herts HP4 1HL. Tel: (0442) 876661. US subscriptions by Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA90505 USA. Typesetting and origination by Project 3 Filmsetters, Whitstable. Printed by Acorn Web Offset Ltd, Bradford, W Yorks.

FEATURES/PROJECTS

Data Communications

Mike Bedford talks about modems in the first of two articles on communicating between computers.

16



Microwaves

The start of a two part feature looking at the history and the applications of microwaves by Colin White.

34

Tame that Timer

Video Cassette Recorders in Britain may one day be more responsive to remote commands in order to record the whole programme without the guesswork involved in getting that programme taped. James Archer reports.

22



SY77 Music Synthesis

The second part of a modern day synthesis story. Mike Barnes continues his trek through the workings of the SY77 synthesiser.

37

Testing Testing

Mike Barwise uses a signal generator and oscilloscope to measure the bandwidth of an amplifier in this continuing series.

26

Slide Projector Controller

Presenting that audio-visual display with a professional crossfade gives the edge over other slide shows. Professor David Ponting talks us through the construction.

29

Cross-over Networks

Are speaker cross-over networks a necessary evil? Vivian Capel highlights the pros and cons behind using cross-overs for speaker systems.

46

Audio TechTips


Some audio designs taken from our vast archives.

44

Stereo Music Relay System

Ever wanted to listen to your favourite recorded music anywhere around the house? This project will relay the music to your head via your personal stereo. Kenelm Rawlings delivers the goods.

52

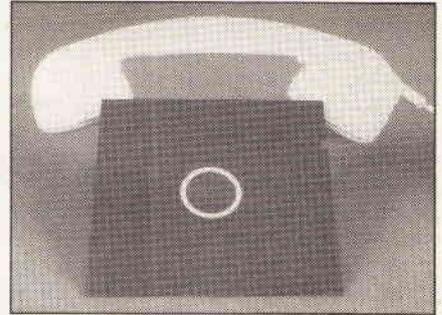

Page 16

The Ultimate Diode Tester


A simple project that will put any diode to the test. Jeremy Siddons construct this handy piece of test equipment.

54


Modern Diode Circuits

In this final part, Ray Marston examines light emitting diodes, photo-diodes and transistors together with the circuits that use them.


58

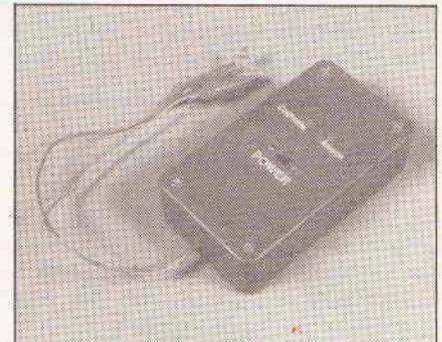

Page 54

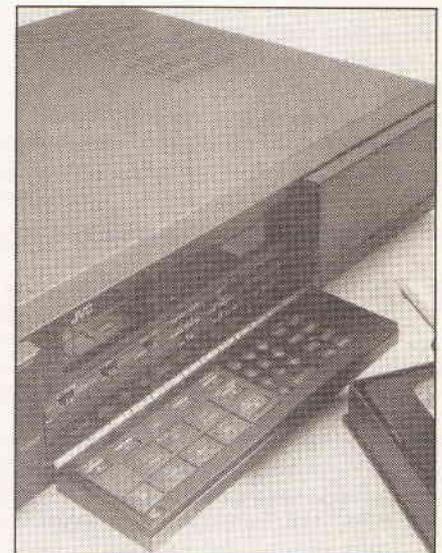

Page 22

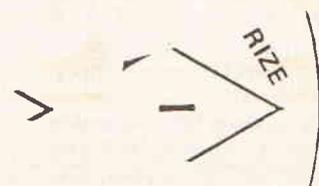

Milling The Earth's Electric Field

The letter from Steve Thackery in the May issue reminded me that I have had for a long time an interest in and a fascination with the Earth's static electric field. I have looked at various ways of measuring the strength of the electric field and have come to the conclusion that the main problem is keeping the measuring equipment weather-proof. The electric field on a fine day is about 100 volts per metre but when thunder clouds appear this figure can change to several thousand volts per metre and reverse its polarity. Clouds however often bring rain and this is where the weather-proofing becomes important.

The Earth's field can be

sampled by using an electrometer or a field mill. Of the two the field mill is probably the best instrument to use as it is sensitive enough to permit the use of low gain low frequency op-amps. A field mill consists of an earthed rotating vane, often with four blades like a cross and an electrode which is alternately exposed to the electric field and then shielded from it by the earthed rotor. The rotating vane chops (or mills) the electric field, producing an AC signal which is easily processed to drive a meter or a chart recorder. As the Earth's field may reverse its polarity near thunder clouds, some means of indicating the the polarity of the electric field

is desirable. The electrode is connected to the electronics which may consist of a voltage follower input stage and a synchronous rectifier giving an output proportional in amplitude and polarity to the electric field.

The field mill I made used a cassette recorder motor to drive a 75mm diameter vane at about 5000 rpm. The electronics consisted of two op-amps of the TL081 type and an opto interruptor driven by a second smaller vane on the same shaft which produced the switching signal for the synchronous rectifier.

I have been unable to continue the project and so it has been put to one side for the time

being.

Here are some references which I found useful in my research into this project:

1. Physics Of Lighting. D. J. Malan, E.U.P.
2. The Design of Simple Instruments for Measurement of Charge on Insulating Surfaces. Dr P. E. Secker, Journal of Electrostatics, 1 (1975) pp 27-36.
3. Apparatus for the Accurate and Continuous Measurement of the Earth's Electric Field. W. W. Mapleson and W. S. Whitlock, Journal of Atmospheric and Terrestrial Physics, Volume 7, 1955 pp 61-72.

**John Noakes
Camberly, Surrey.**

Power Amplifier Parts

Lucas of Glasgow writes in your July issue about his efforts in improving the sound quality of his Audio Design power amplifier by John Linsley Hood.

Audiokits Precision Components have been supplying high performance parts to constructors of the original 1984 design as well as the more recently published version.

For 470nF capacitors, Audiokits offers a choice of parts including the fabulous Wonder Caps from America for those who

can make the space. Or a Bourns conductive plastic volume control which sounds even better than the ALPS.

On the subject of connecting wires, I strongly recommend the use of PTFE insulated cables and have recently introduced a 1 x 0.9mm diameter silver plated copper wire specially for constructors who prefer to use solid cores to stranded cables. In technical terms, PTFE has much lower dielectric loss and dielectric absorption than any other cable

insulator and this factor directly affects sound quality. The disastrous sonic effect of using PVC insulation on wiring in audio circuits can be easily observed simply by removing the insulation from a length of solid core cable and directly comparing it in the circuit with a similar insulated length. Providing that the solid cores are rigid enough not to touch when the insulation is removed, this test can quite easily be carried out.

For the benefit of readers who

are building the latest version of John Linsley Hood's 80W power amplifier, Audiokits has produced a component note ACN22 which describes many more ways in which this amplifier can be further improved in sound quality simply through the use of better quality parts and cables. This is available from Audiokits for £2 post free.

**Graham Nalty,
Audiokits Precision
Components, Derby.**

Labcenter PRO-test

I feel I must point out the following errors and omissions in the write up of our PC-B PRO package in the July issue of ETI.

a) The package allows 20 sizes of circular pads, square pads and track widths (not 6) and the user can configure what these sizes are.

b) Connectivity highlight has always been a feature of PC-B PRO, as has the ability to generate a netlist from the layout for checking purposes.

c) Your reviewer fails to mention that ours is currently the only package with an auto-routing

option.

d) Since October 89, PC-B PRO has been capable of netlist import i.e. the major difference between Boardmaker 1 and 2, so to say it is overpriced against the £295 Boardmaker 2 is debatable.

**John Jameson
Managing Director
Labcenter Electronics**

David Silvester replies:

I must initially apologize for the error that has crept into the review concerning Labcenter's PC-B

PRO. The statement about 6 tracks relates to the low cost PC-B Package only; not to the PRO package which has advanced facilities.

I must however disagree that PC-B PRO AR is the only auto-routing package that is available in this price range; there are also Ranger by Seetrax and EZ-Route by Brigden that are within the price range for autorouters. However it was specifically decided not to include autorouting as it would be impossible to do justice to the autoroute packages in such a short review. I had however

tried out the PC-B PRO AR package and it had failed the test that I had set it. The simplest test that I already knew the answer to was to get the package to draw from a ratsnest a simple bus structure with three 14 pin chips. PC-B PRO AR did not give the output expected with tracks passing between pins but sent tracks all over the board. Ranger incidentally has a special bus algorithm to cope with this problem.

Whilst on the subject of auto-routing, the professional will almost certainly be using a double sided board if he uses normal

components. For the amateur and the professional working with surface mount components a special autoroute algorithm that works on the minimum through board connections is needed. The amateur needs this to allow him to make his own boards which are vastly simpler if single sided with a few wires completing the circuit on the other surface. For the professional, hole drilling costs money.

The test was kept secret to find out how good the company presentation of their product was. In fact they fall into two camps. Easy-PC, Boardmaker and EZ-Route come with large instructional manuals that after working through leave the user in no doubt as to the facilities. PC-B in all its versions and Ranger come only with a few sheets of A4 paper which cannot hope to cover the ground that a booklet

can cover.

Readers of the electronics magazines will be in no doubt that Easy-PC and Boardmaker have undergone substantial price or facility revisions as they both take full and half page adverts in most of the magazines. PC-B is only advertised in small adverts at the back of the magazines that are easy to overlook unless specifically hunting for such adverts with a view to purchase such a

package and as such it is easy to miss revisions. The other packages appear to be rarely advertised in the magazines that I read, Ranger was found by chance whilst attending the British Electronics Week in London earlier this year.

After the review I did in fact purchase one of the packages for personal use based on my experience which formed the basis of the review article.

Feedback On Feed

I was interested in John Linsley Hood's comments regarding Mr Christian's letter (ETI June 1990) and on series and parallel feed. Mr Christian's letter makes it clear that he is referring to the DC feed arrangements. In the Hartley oscillator, this can be via the coil — series feed (ETI April 90, Fig 7 on page 34) — in which case there is a DC component in the coil — or via a choke or resistance (ETI April 90, Fig 8 on page 35) — in which case the choke or resistance is at signal frequency, shunted across (in parallel with) part of the coil.


Each method had its pros and cons. In the early days, when fairly high powered valve oscillators were common, the presence of a high voltage supply in a sizeable coil wound with heavy gauge bare wire — or even thin copper tube — posed a few problems. Even as late as T1154 days, the danger still existed — 1250 volts fed via a 50k resistor and a bare tinned copper wire coil to the master oscillator. The parallel feed system avoids this, but loses out because of the shunting effect of the choke or

resistance across part of the oscillator coil. In particular, efficient RF chokes are not easy to design, especially if a sizeable bandwidth is involved.

In the early days of radio, when battery powered receivers were still common, parallel feed was often used at SF to overcome deficiencies in the intervalve transformers generally used to give some inter-stage voltage step-up. Many of these transformers were very poor performers with DC flowing in the primary windings; parallel feeding was a way round this. "Roll-off" or resonance problems resulting from the value of C and the primary inductance were a small price to pay for the overall improvement.

The obvious next step was to increase the effective transformer ratio by an auto-transformer configuration, using the primary and secondary in series. During the early/middle thirties this circuit used specially designed small transformers with high inductance windings on mu-metal cores.

G W Ashford
Warrington, Cheshire.

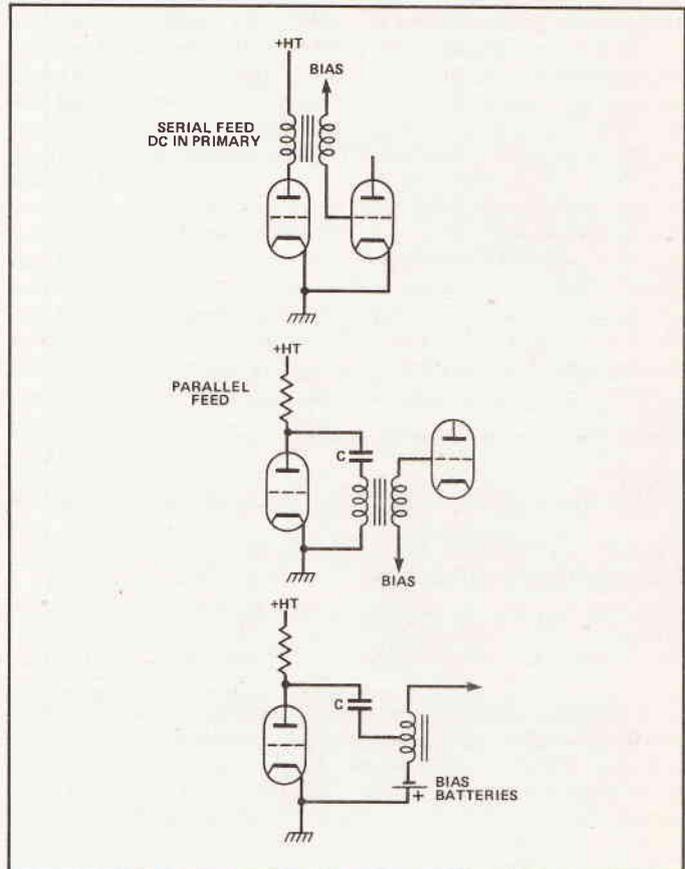

Supplying The Answers

The following is in response to points raised in connection with my article Designing Power Supplies (ETI April 1990). Fortunately none of the mistakes are catastrophic. As you will see, the error on the heatsink calculation serves to make a couple of extra points.

On page 28, the full-wave rectified cycle duration for 60Hz is 0.00833 seconds, not 0.0833 seconds.

On page 30, the expression for calculation of I_{ripple} should be: $1.8 \times 2\pi \times 2 \times 50 \times 0.022$. This does not change the answer

which is correctly given as 14.36A.

The expression for V_{peak} (on-load) should be $(1.414 \times 9.71) - (2 \times 0.7)$. This does not change the answer which is correctly given as 12.33V.

The expression for P_D should be $4 \times (12.33 - (1.8/2) - 5)$. This changes the value of P_D to 25.72W. This value is used in the Equation for θ_{H-A} . Putting in the new value of P_D gives a negative value which is clearly an impossibility. This negative value serves to illustrate a situation not covered in the article. If a negative value

is obtained, this means that even an infinitely large heatsink would not suffice. There are two ways to overcome this problem, and in this example both measures would be required.

Firstly, reduce θ_{J-C} . The 338K, for example, has much better thermal properties than the 78H05, having a θ_{J-C} of 1°C/W .

Secondly, reduce the ambient temperature below 50°C . 50°C is quite high, and the temperature would probably be lower in many enclosures, and could easily be reduced to 20°C by use of a fan. Alternatively, mounting the heat-

sink on the rear of the cabinet on the outside (like power transistors on many amplifiers) would reduce T_A to room temperature.


V_{AC} in equation 3 is used to represent a general AC voltage. $V_{TX MAX}$, on the other hand, is a particular AC voltage, namely the maximum transformer output, either off-load or on-load.

Mike Bedford
Keighley, West Yorks.

Sanyo Electric has announced a significant advance in its amorphous solar cell technology with the introduction of a new flexible light-weight, solar cell film material.

The new Amorton film, which is 0.12mm thick and is flexible enough to be bent into a tube 10mm in diameter, can be shaped to conform to three-dimensional surfaces that would not normally accommodate conventional cells which are fragile or rigid. Because the film is light, it yields a power-to-weight ratio of 200 milliwatts per gram, 10 times that of conventional glass-type cells. The film can be used to apply solar cell technology to a new range of solar-powered products.

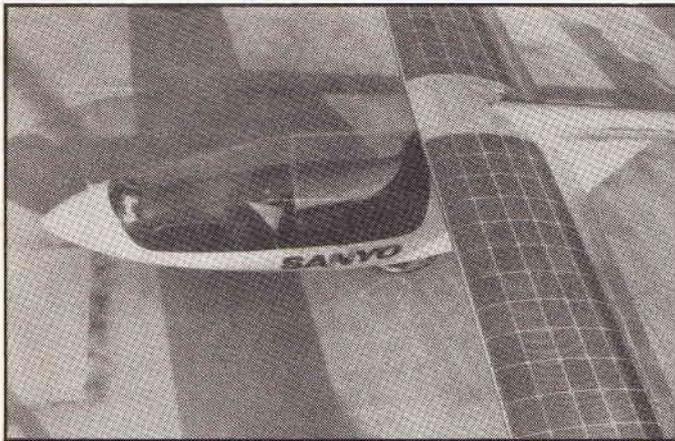To demonstrate the potential for this new technology, the solar film has been used to power the "Sun Seeker" areoplane, the first solar aircraft to attempt a trans-continental flight across the United States.



UPS AND DOWNS

The principle aim of most Uninterruptable Power Supplies (UPS) is to keep a computer system running while the operator completes an orderly shutdown after a power cut. The power needed to do this for a PC is between 90 and 150 watts, and so UPS systems are typically stand-alone boxes with big batteries and big prices.

Emerson Electric have now launched a UPS within the budgets of most PC XT or AT users. Instead of trying to keep the whole system up and running, the ACCUCARD UPS provides just enough power to ensure that every bit of data is saved, and the computer is safely shut down whether the human operator is at the computer or not.

This requires only a small battery, and so may be slotted into the PC. The ACCUCARD hardware is fitted into an expansion slot on the DC side of the PC's internal power supply, and the

Terminate and Stay Resident software is loaded onto the hard disk. Once installed, the system monitors the power being supplied to the PC.

In the event a power loss ACCUCARD is automatically activated. The memory resident program freezes the operating system and then saves to hard disk all data in the RAM as well as the video memory and all mode and status registers. Finally, it parks the disk heads and powers down the mother board.

When power is restored, ACCUCARD commences the restoration of the system software and user files, reloading every bit of data necessary to put the operator back on screen at the exact point reached prior to the power failure, irrespective of the program being used.

The ACCUCARD costs £199. Emerson Electric can be contacted on 0793 512669.

A DOG'S LIFE NO MORE

Betting on the dogs is not always easy. Punters who want to place bets face long queues at the tote — several times per race if they want to place win, forecast and other combination bets. There are long queues again to collect winnings.

However, a Bristol-based company called Data Tote Limited is using computer systems from Control Universal to enable greyhound tracks to economically update their tote facilities. Data Tote systems are installed in many of the countries major tracks, including Wimbledon, Wembley, Bellevue and Bristol.


The systems comprise a central computer linked to a number of ticket issuing machines (TIMs) and video display units. Critical components are duplicated since a system shutdown during a meeting could lose the bigger venues £20,000, as well as the goodwill of racegoers. Systems vary in size from track to track — Bristol has 21 machines, while Wimbledon has 105 and even then has to borrow some for big events like the Greyhound Derby.


Successive developments have been aimed at making the TIMs more portable and easier to operate. The unit houses a

customised keyboard, thermal printer and a large, clear, liquid crystal display. Unlike older manual methods, each operator takes bets in all pools, whether win, place, each way, forecast, trios, jackpots or other novelty combinations. The operator is prompted by the machine to enter pool, dog number and bet, then to press a button to issue the thermal ticket. Each station also has a barcode reader which enables operators to void bets and re-issue tickets if a mistake is discovered. So customers have to queue only once for each race, the queues move much more rapidly, and bets can be changed right up to the off.

During betting, the computer continually reads data from the TIMs, updating the pool and working out the odds for display on the video screens. The off is the signal for automatic shutdown of the TIMs. After the race, results are entered via a keyboard, and the computer calculates returns. Winning tickets are identified by the barcode reader, and the TIM automatically tells the operator the amount of money to be paid out. The payout is virtually immediate, contrasting with manual methods in which, even with high manning levels, customers sometimes had a long wait for their money.

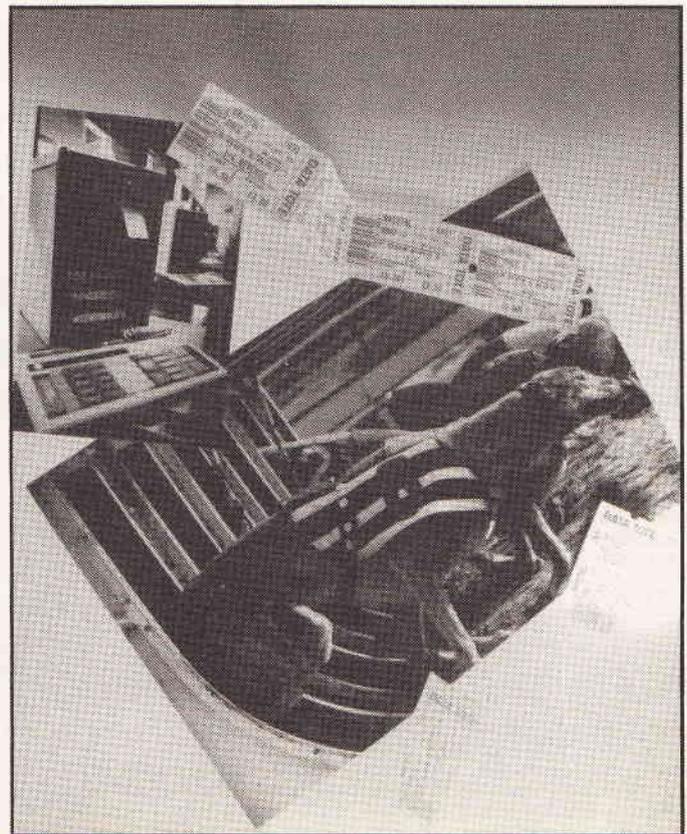For further information contact Edward Keating at Control Universal Limited. Telephone 0223 244447.



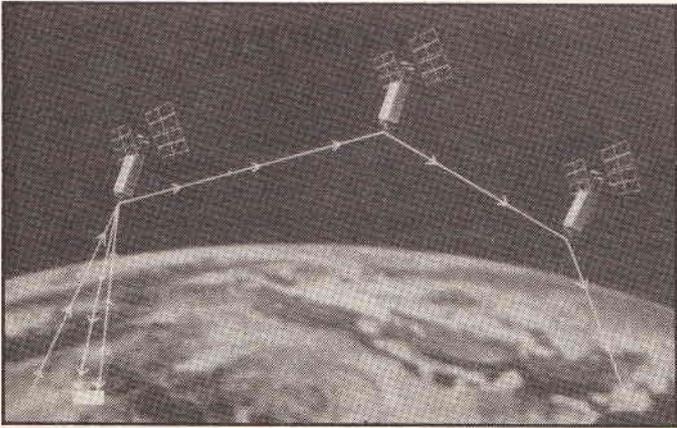

SATELLITE CONSTELLATION

Motorola has announced a new global communications system that will allow people to communicate by telephone anywhere on earth, on land, at sea or in the air — via portable cellular radio telephones operating as part of a satellite-based system. Callers using the new system will not need to know the location of the person being called, and can just dial that person's number. The system will be able to handle both voice and data.

The new system is called Iridium. Its core is a constellation of 77 satellites in low-earth orbit,

working as a digital switched communications network in space. The Iridium system differs from the geosynchronous satellite systems currently used from international communications. The low altitude of the Iridium satellites allows radio links with portable cellular radio telephones on earth, using small antennae rather than satellite dishes. It also supports re-use of radio frequencies, in a similar way to land-based cellular systems.

The system solves the problem of low-orbit satellites disappearing over the horizon by

combining a large number of satellites in a space-based, inter-satellite switching system. The network of satellites will orbit the earth at a height of 413 nautical miles, ensuring that every point on the earth's surface is in continuous line of sight with one of the satellites. The satellites will be deployed in seven circular polar orbits, with 11 satellites per plane.

The satellites are approximately one metre in diameter and two metres tall, and weigh about 315 kilograms. Each satellite antenna pattern will project 37 cells onto the earth's surface. Each cell will provide communications coverage for an area of the earth's surface roughly 350 nautical miles in diameter. People will communicate with the satellites using equipment operating at frequencies of 1.5-1.6 GHz, just above land-based cellular telephones. In addition to voice, the digital system will be able to transmit data at a rate of 2400 baud.

The Iridium satellite can be placed in orbit by a variety of launch vehicles, including the U.S. Delta and Atlas rockets, the European Ariane and the Pegasus air-launched vehicle. Each satellite should have a life span of about five or six years.

A network of gateway surface systems will be able to link Iridium

with the public switched telephone network. The gateways will store details of each user's location and bills.

Although Iridium uses cellular communications principles, it is designed to complement, not compete with, land-based cellular systems. Land-based cellular will remain the most effective way to serve high-density areas, whereas Iridium will bring communications to remote or sparsely populated areas that lack communications.

The Iridium system will be capable of supporting millions of users worldwide. Motorola hope it will be particularly suitable for low population density areas which currently lack cellular communications, and for undeveloped regions, which have no basic telephone service.

Motorola also anticipate that Iridium will be able to provide voice or data links and positioning information for ship and aircraft. It may also be able to play a valuable role in disaster recovery efforts following natural disasters such as earthquakes or hurricanes.

Motorola plan to place two demonstration satellites in orbit in 1992. Implementation of the entire system is planned to begin in 1994, and Motorola hope that the full service will begin in 1996.

DATA DISCMAN

Sony Corporation in Japan have introduced a new portable data retrieval system, the Data Discman, DD-1. This model accesses information from sources such as catalogues or dictionaries on an 8cm CD-ROM disc, and shows it on a liquid crystal display screen. The Data Discman is aimed at computer users who have previously been confined to a desk or laptop computer in order to retrieve information.

Sony Corporation began the portable audio revolution with the Walkman in 1979 and in 1984 introduced the audio Discman, the first portable compact disk player. These machines made music and sound available anywhere, in or out of doors. The Data Discman follows this pattern and allows for data availability anywhere.


The 8cm CD-ROM disc drive and the liquid crystal display allow the unit to be very small, with retrieval software included in the

integrated circuits of the machine. Information access should be as easy as playing a CD.

The screen is able to display text 15 characters horizontally and 10 lines vertically. If additional text is available it will read out in a scroll fashion. As well as displaying data, conventional 8cm audio CDs may be played on the machines.

Software publishers will market information discs of many kinds: travel guides, textbooks, dictionaries, instruction manuals and so on.

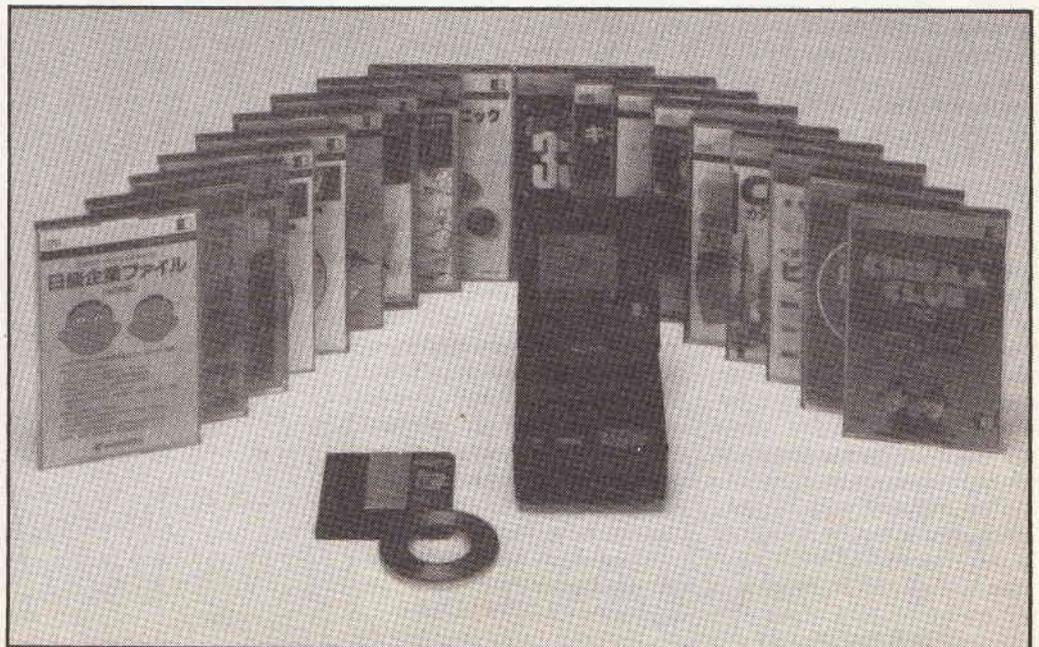For further information, contact Paul Cambell. Telephone 0784 467455.



ELECTROSTRICTIVE MOVEMENT

AVX Limited, who design, develop and manufacture multilayer ceramic capacitors, have used the same technology to produce an electrostrictive actuator for precision displacement monitoring.


Typical applications envisaged for the actuators include mirror angle and focus adjustment in optical and laser systems, micro-movement for tool wear compensation in machine-tools, usage of valves in automotive applications and video tape head adjustment systems.

According to AVX, the advantages of the multilayer ceramic device over its piezo-

electric and magnetostrictive counterparts are repeatability of movement and cost. The multilayer devices suffer very little hysteresis loss, and the absence of rare earth metals makes them cheaper than magnetostrictives.

The mechanical force of 7.5kg per square mm is higher than the piezoelectric product and AVX's devices produce a 90% deflection at 100Hz and 100-150V. In common with piezo electric devices, AVX's electrostrictive parts can be used in reverse to measure loads and forces.

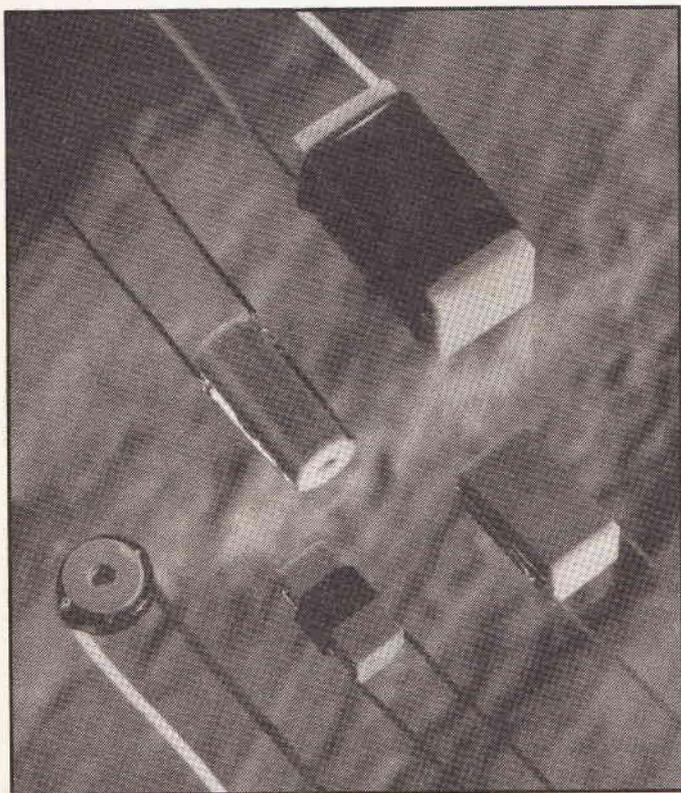For more information, contact Shirley Smart at AVX Ltd., Telephone: 0252 336868.



NEW UK PCB DIRECTORY

A new UK PCB Directory is now available from Technical Reference Publications, which sets out to improve on previous publications by incorporating more detail about the PCB manufacturer's capabilities, by supplying an index of those capabilities for purposes of cross-reference, and by giving manufacturers an opportunity to outline their capabilities and services in their own words.

The desire to present an over-

view of the PCB industry as a whole led to the addition of two further sections, the first listing suppliers of material, equipment, products and processes, and the second sub-contract services.

Priced at £55 plus £2.50 postage and packaging, this publication is available from Technical Reference Publications Limited, Asahi House, 10 Church Road, Port Erin, Isle of Man. Telephone 0624 834888.

MIGHTY MOUSE

Selectech Ltd have announced an easy-to-use remote controller for interactive video systems such as Compact Disk-Interactive, High-Definition Television, Cable TV and video games. The device, called the AirMouse, functions in a similar manner to a conventional computer-type mouse. However, the AirMouse is a hand-held remote, with no connection to the set. It uses patented sensor technology combined with digital

infrared signalling to locate and select on-screen menu functions.

The AirMouse replaces other remote control technologies that either required numerous button functions or use joysticks, track balls and thumb pads. Those controllers are either cumbersome, require considerable hand-eye co-ordination or need two hands to operate.

Selectech are based in Vermont, USA. Telephone: (0101) 802 860 7600.

NEW DMM RANGE FROM QUILLER

Six new multimeters have been introduced by Quiller of Bournemouth. The QI Range comprises "low cost instruments with realistic specifications". From a modest 10A DMM at around £15, the range progresses through analogue units to two high specification DMMs.

The first of three analogue meters is a 500V insulation tester, also offering a 300VAC measure-

ment scale. The remaining two offer large displays, dB ranges, semiconductor test and are suitable for general purpose and desk instrument work.

The range's penultimate DMM is compact, autoranging and features a bargraph display. Top of the range is a powerful and rugged DMM with a comprehensive selection of facilities including temperature, capacitance, frequency ranges and semiconductor test.

All the units are fuse protected except in 10/20A ranges, and are supplied with lead sets, full specifications and operating manuals.

For further information contact Quiller Limited. Telephone: 0202 417744.



COMPUTER NOTEPAD

GRiD Computer Systems has launched a graphics-based computer tablet capable of recognising handwriting.

The computer is called the GRiDPad. All information is entered via a stylus writing on the computer's glass screen. It can be operated while the user is standing up or walking, and is suitable for applications where desktop or laptop computers impose too many restraints. Development of the GRiDPad began three years ago. The algorithm it uses for user-independent handwriting recognition was developed by Jeff Hawkins.


GRiDPad is aimed at the market where the most common medium for data collection, retrieval and storage is the paper form, mounted on a pad or clipboard. GRiDPad replaces these forms and allows

organisation to run a virtually real-time data collection system, bypassing the usual time and effort of having to transfer the data held on the paper forms to its computer.

The GRiDPad runs under the MS-DOS operating system. It weighs 2kg, and has 1Mbyte of random access memory (RAM). A 20Mbyte hard disk unit (of similar size to the main computer) can be clipped onto the back. The unit has built in modem facilities, which allow portable use.

The GRiDPad is already being used in the US. In some states, if someone uses a GRiDPad stylus to sign for a shipment or order, this can be stored and used as a legally binding acceptance.

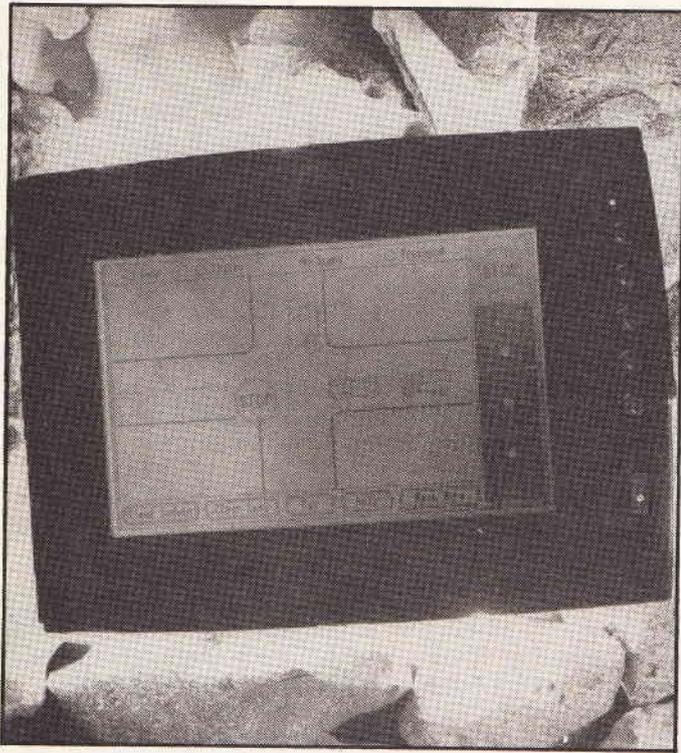For more information, contact Mike Daly at GRiD Computer Systems Ltd. Telephone 0372 60266.



MOTORWAY NETWORK

STC, the communications and information systems group, is to supply the first Digital Networked Managed Transmission system to the Traffic Control and Communications Division of the Department of Transport. This is for the National Motorway Communication System which the Department uses to provide an emergency telephone service and signal system for motorway users every mile along the motorway.

STC's order, worth £1.5 million, is for the supply and installation of improved communication networks for motorways in Manchester, the West Midlands and on the M25. STC will commence installations of the first network in October 1990 and should complete the contract by the end of 1991.

The Department's network, designed for maximum com-

munication integrity and reliability, will be equipped with STC's Network 300 intelligent multiplexers. The intelligent multiplexers incorporate a special management facility enabling the systems manager to automatically reconfigure the network immediately if a rerouting is required.

These multiplexers are designed to be flexible. As the motorways spread during the next decade, the multiplexers should be able to handle the increased volume of telephone and data traffic without impairing the quality and resilience of the network.

During the past two years, there has been continual technical liaison between STC and the Department of Transport; a trial system is already operating successfully between Dartford and Swanley in the M25 area.

million. By 1988, sales had reached \$1.8 billion and by 1995 they are expected to exceed \$9.1 billion. These findings are revealed in a report "World PC LAN Markets" published by Market Intelligence Research Corporation.

Several trends have emerged. These include the replacement of multi-user systems based on mini-

About 35% of the cost of a new office building development goes into the infrastructure necessary for efficient use of IT. And of the cost of refurbishing an existing building, 45% goes on IT. It is cheaper to demolish and rebuild a 1960s speculative office than to refurbish.

These are the findings revealed at Infrastructure 90, a conference organised by Applied Network Research and Commed.

Office buildings of the 1990s will have to accommodate ever increasing layers of communications channels, for voice, data and images, with cabling taking up a correspondingly greater proportion of available space. Communication network cabling is a long term investment, fixed in the building's fabric and expected to last as long as the building itself. A successful "intelligent building" requires co-operation between

architects, contractors, design teams and IT specialists. Poor planning, installation and decisions can lock an occupant into a system which damages business performance.

The conference also discussed the transmission media used in intelligent buildings. Copper cable, particularly in the form of twisted pair cabling (the system used in telephone cables), is expected to have at least five years life left. However, fibre cabling is becoming increasingly popular. While the cost of fibre cabling is likely to fall, the cost of connection is likely to remain high. The blown fibre structured cabling system allows an empty plastic tubing to be inserted at strategic points during construction of the building. These tubes can later be used to blow fibre optic cable into the required operation environment.

computers by PC LANs, and the issue of standard, achieving a common or compatible set of standards, allowing PC LANs to intercommunicate. LANs will be based on network controllers increasingly using 80386 microcomputers.


Manufacturers are likely to try to tap the market potential of PC LANs for customers with specia-

lised needs for communication or file sharing. The efficiency of software must be optimised for use in a LAN environment.

Competition is very strong in the PC LAN market. Manufacturers will be looking to provide the most differentiated systems features combined with optimised systems performance overall, including hardware and software.

In 1985, worldwide sales of personal computer local area network (PC LAN) systems and associated hardware and software products totalled nearly \$600

Since the second world war, worldwide electronics has been largely defence — more precisely, militarily — led. Apart from a monumental glitch when American president John Kennedy committed the USA to a course of manning the moon, first western electronic industries have catered primarily for military purposes. Missiles, rockets, telecommunications, computers, networks and so on are mainly results of this defence-orientated marketplace. A familiar term, the cold war, was coined to represent this electronic race to produce superior weaponry and systems.

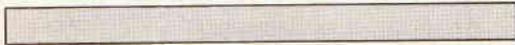

Naturally, as a consequence, we consumers see a benefit (if benefit is the right word) in the off-casts of this race. Off-casts take the form of integrated circuits, without which a spacecraft could never have found its way off the launch pad into orbit, let alone to the moon and back. ICs in adapted forms have since changed most household contents, and continue to do so.

Now Mr Gorbachev comes in from the cold and the race slows to a friendly jog before breakfast. Defence budgets are cut and slashed with considerable ease, even by governments passionately committed to military priority. Many jobs, previously assumed safe, are lost. Worldwide electronic industries are now under considerable pressure to perform and pay their ways.

At home in the UK, we must take note of cold war thaw. It is not too late to make a shift in priorities, and shift we must. There is but one direction to shift, too. Consider Japan, which has not since the second world war had a military presence or requirement. It maintains a strong electronic presence worldwide instead, developed following a consumer-orientated course which has set it at the forefront of a new international electronics race. If our industry (or any country's national electronics base, for that matter) is to be maintained, that is the race now to be run! It would be ironic if we were to find ourselves out in the consumer cold, after being for so many years hot-stuff in defence.



Worldwide, several industries are taking initiatives. Philips, for example, appears to be selecting consumer markets which look as though they will be money spinners. Already, Netherlands-based Philips is forcefully trying to define worldwide opinions in matters like high definition television (HDTV) systems.

It has teamed up with fellow European competitor Thomson of France to develop, make and sell HDTV products by 1995. Indeed, wide-screen receivers are expected before the end of next year.

What Philips and Thomson are hoping to achieve is not just first place in the HDTV race, but to completely define HDTV worldwide on a European basis. Previously, it looked like the Japanese HDTV system would be steamrollered through to being the worldwide standard. However Philips and others hit the Japanese steamroller head on and stopped it.

At a recent plenary meeting of the International Radio Consultative Committee (CCIR), Philips and Thomson presented sufficient evidence to prevent decisions being taken by the committee on number of lines and scanning rate. Thus a worldwide HDTV standard could not be defined. This was despite the fact the Japanese HDTV system is already in use in Japan, while a European system is only in early development. As you might expect, prior to this the Japanese system was expected to be accepted by the committee.

This is an interesting situation. CCIR plenary meetings are held only every four years. Philips and Thomson (and any other companies wishing to ally themselves) therefore have four years to prove their system. And if they can do so before the next plenary, a European HDTV system could just be accepted publicly on a de facto basis.

This, then, is an example of the new electronics race. Not now a cold war, more a hot one, trying to slow down the rising sun — or at least put on a sunhat and sunglasses before high noon.



There are many other areas where British and European manufacturers can team up. Telecommunications is probably the most important now, hence my high definition television example, although computing, networks and software are areas which we must maintain to the best of our ability also. Without excellence in these we will become little more than an offshore European cheap manufacturing base for Japanese companies. I'm not decrying this — after all, such industries employ British people, pay British taxes, and provided good quality products at economic prices — I just prefer to think we are capable of more. Without wishing to sound a zealous patriot, I believe Britain is a nation of innovators. Let us now innovate. We managed to maintain a high priority in the military-orientated market place. We can surely do it in the consumer-orientated complement.

Keith Brindley

OPEN CHANNEL


19" RACK CASES

* Suitable for instruments, high quality amplifiers and many other applications that demand strength and professional finish * New improved construction and finish * Black anodised aluminium front panels * Separate front mounting plate, no fixing screws visible on the front and the side of the enclosure * Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles * With ventilation slits and plastic feet * Rear box manufactured from 1.1mm steel finished in black. Rack mounting or free standing. Comes in quick assembly flat package.

Order Code	Panel Size W H (inch)	Rear Box W H D	Weight kg	Price £
U101	19 x 1.75	17 x 1.5 x 10	2.4kg	26.95
U103	19 x 5.25	17 x 5.0 x 10	3.5kg	29.95
U212	19 x 3.5	17 x 3.0 x 12	3.3kg	29.75
U312	19 x 5.25	17 x 5.0 x 12	4.0kg	31.95
U412	19 x 7.0	17 x 6.5 x 12	4.6kg	34.95

Please add £3.00 P&P for the first item and £1.50 for each additional item.

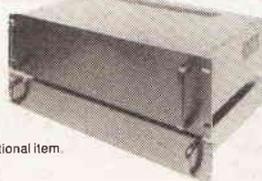Please add VAT to above prices. Overseas orders welcome.



CRICKLEWOOD ELECTRONICS LTD
40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET
 Tel: 081-452 0161 Fax: 081-208 1441

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX • 031 667 2611

New
 catalogue
 available
 NOW

**A COMPREHENSIVE RANGE WITH
 SERVICE SECOND TO NONE**
 OUR MUCH EXPANDED, BETTER ILLUSTRATED
 CATALOGUE WILL COST £1.50 — TO INCLUDE
 VOUCHERS TO USE AGAINST FUTURE
 PURCHASES. TO RECEIVE A COPY, PLEASE
 SEND YOUR REMITTANCE WITH YOUR NAME,
 ADDRESS AND TELEPHONE NUMBER
 REQUESTING A COPY OF THE 1990/91 OMNI
 CATALOGUE.



Open: Monday-Friday 9.00-6.00
 Saturday 9.00-5.00



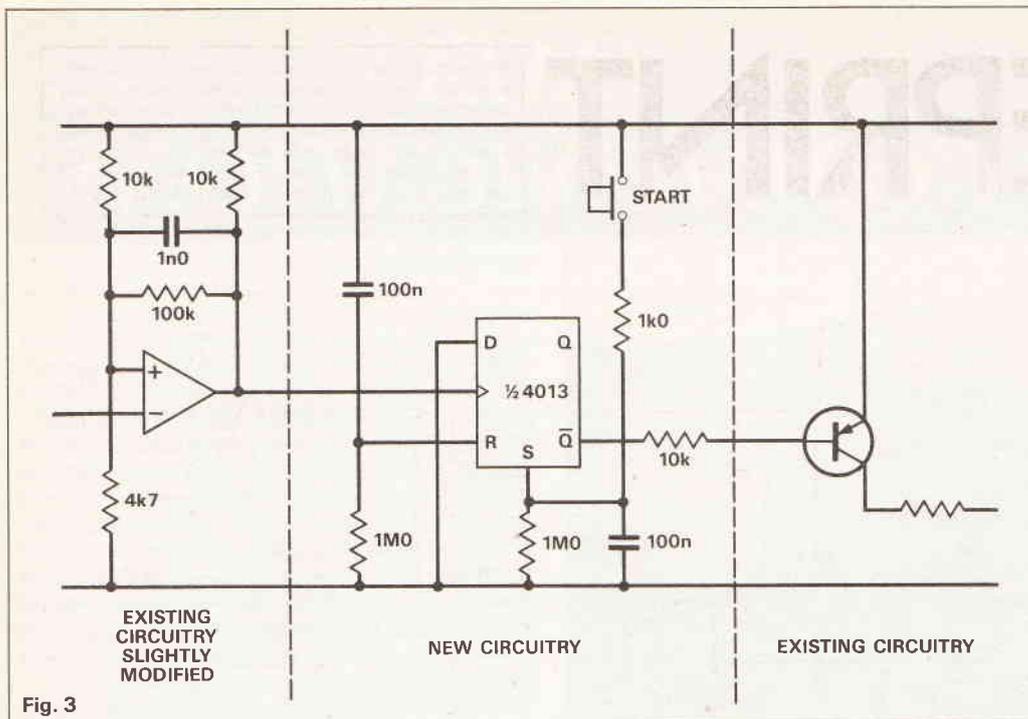


Fig. 3

JG60Q and it needs base part number JG54J. The switch, though it only switches low voltage, is connected to the mains neutral, so it should be a mains insulated type even if the contacts are only rated for less than 240V.

Set/Reset

The final possible elaboration is to add

a flip-flop to the circuit of Fig. 2 to permit the use of the delay timer in the drier. The additional circuitry is shown in Fig 3.

The D-type flip-flop is positive edge triggered, so that when the load current starts to flow nothing will happen. If the current ceases at any stage, the flip-flop will switch over, which will de-energise the relay.

Further clock pulses caused by noise will not switch the relay on again, because the output will simply follow the D input, which is permanently at logic 0.

Capacitors on the set and reset inputs make sure that, if the mains supply is interrupted and then switched back on, the circuit will not power up the drier. Do not forget to ground unused inputs (on the other flip-flop).

Afterthought

It might be worthwhile incorporating an alarm in the system, because a small child is unlikely to fare well in a hot clothes drier even if the heating is off. A means of doing this is shown in Fig. 4. A FET is used to switch the alarm to avoid excessive load on the comparator output.

Andrew Armstrong

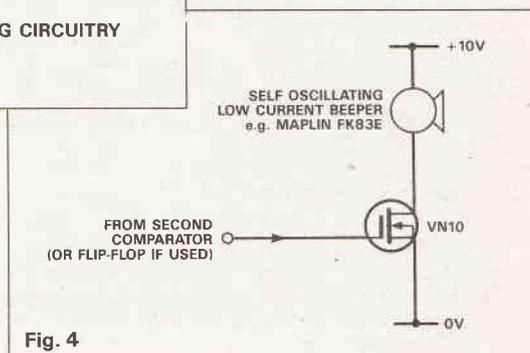


Fig. 4

A HANDY NEW ADDITION TO OUR VERSATILE MULTIMETER RANGE


DIGITAL CAPACITANCE METER

An extremely useful hand-held capacitance meter measuring from 1pF to 20,000µF in nine ranges.

Features include:

- 13mm, 3.5 digit LCD
- Zero adjustment
- Low battery indicator
- One year warranty
- Supplied with battery (PP3), manual and test leads
- Just one of our many low cost Digital Multimeters - send for full details

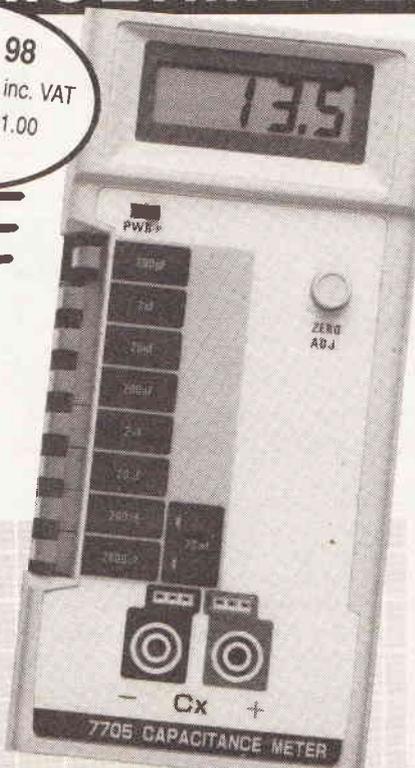£38.98 inc. VAT
please add £1.00 for p + p



Specification

ranges	res.	accuracy
200pF	0.1pF	+ (0.5% + 1 digit + 0.5pF)
2nF	1.0pF	+ (0.5% + 1 digit)
20nF	10pF	+ (0.5% + 1 digit)
200nF	100pF	+ (0.5% + 1 digit)
2µF	1.0nF	+ (0.5% + 1 digit)
20µF	10nF	+ (0.5% + 1 digit)
200µF	100nF	+ (0.5% + 1 digit)
2000µF	1µF	± (1.0% + 1 digit)
20,000µF	10µF	+ (2.0% + 1 digit)

Overload protection	0.25A 250V fuse
Excitation voltage	3.2V, all ranges
Dimensions	180 x 85 x 38mm

OUT NOW!


- The new Cirkit Catalogue
- 184 pages
 - Discount vouchers
 - 1,000's of products

Cirkit

£1.60 inc.

SAME DAY DESPATCH - 0992 444111
Cirkit Distribution Ltd.
Park Lane, Broxbourne, Herts. EN10 7NQ
Tel. Enquiries (0992) 441306 Fax. (0992) 464457

DATA COMMUNICATIONS

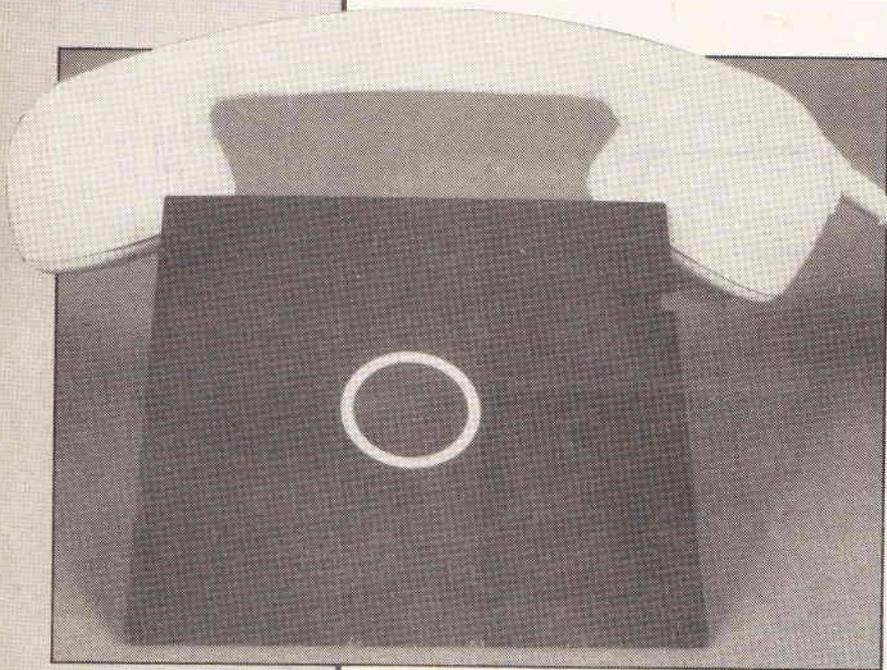

In the first of two articles about how computers communicate with each other, Mike Bedford looks at modems.


In recent years, the use of computers has continued to grow rapidly. One aspect of computing which has grown particularly fast is data communications, the exchange of information between computers. Here we look at the methods and theory of data communications, both wide area and local.

Modems

Most of our experience of interfacing various peripherals to computers is carried out locally. The printer is probably sitting on the desk right next to the PC or

running a dedicated cable is out of the question, even if RS232C or even RS422 would operate over that distance (which they don't). The obvious solution is to make use of standard telephone lines but here we run into a problem. Since telephone equipment was intended to transmit and receive speech, all the circuitry is designed to operate with a bandwidth of 3kHz. Any signals with a frequency of less than 300Hz or greater than 3300Hz will not pass through the system. This means that if RS232C was pumped into the public telephone exchange a steady +12V level and a steady -12V level would both appear the same at the other end — neither would get through and our data stream would be lost. The answer is to convert the binary data into a form which is compatible with the telephone system or in other words to use the data to *modulate* an audio carrier signal.

A piece of equipment to generate a modulated audio signal from a binary signal is called a modulator. The piece of equipment at the other end of the telephone circuit which converts it back to a binary signal is called a demodulator. Normally we require a two way link and as such need to carry out both these functions. The piece of equipment which combines these functions in a single box is our old friend the modem, the name being derived from *modulator* — *demodulator*. The way in which two computers are connected via a telephone system and a pair of modems is shown in Figure 1. The amorphous shaped lump in the centre of this diagram, labelled PSTN (for Public Switched Telephone Network) consists of some combination of telephone lines, repeaters, exchanges and even satellite links. Although we have concentrated on telephone circuits, these techniques apply to any medium designed for speech transmissions. Modems are also used to effect data links via radio communications and, of

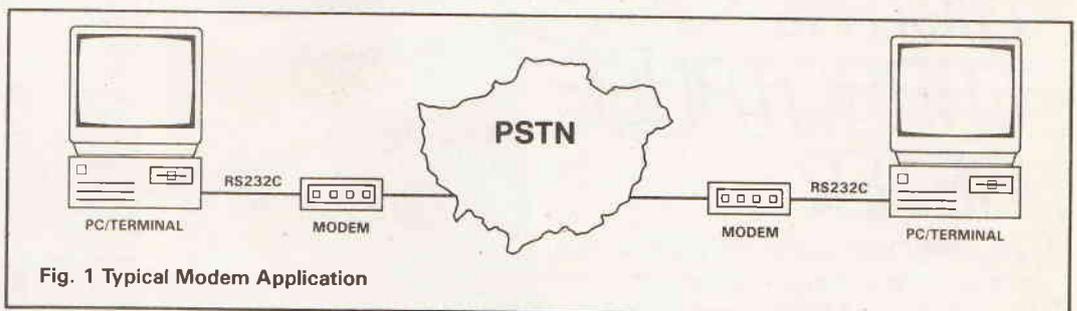

is at most only a few metres away. In this situation the constituent parts of the computer system are interconnected using cables with either a couple of conductors in the case of serial communications or perhaps ten for a parallel interface. As most readers will be aware the binary data which passes along these cables is represented by discrete voltage levels. So, for example, in RS232C, +12V and -12V are used.

Now, what happens if we wish to interface our computer to another which is on the other side of town, or even on the other side of the world? Clearly

course, this is exactly the way data was stored on audio cassette recorders in the early days of home computers.

Those who have dabbled in radio communications will be aware of the modulation methods available and in the most basic terms the options come down to amplitude modulation, frequency modulation and phase modulation. With AM, a frequency in the centre of the passband (say 1500Hz) would be picked and this would be transmitted at different amplitudes for a binary 0 and for a binary 1. The most

obvious such solution would be to have zero amplitude for 0 and maximum amplitude for 1, the resultant signal being somewhat akin to morse code. This is referred to as on/off keying. However the signal-to-noise ratio of this modulation method turns out to be unattractive and this is aggravated by the fact that a constant amplitude signal may vary in amplitude at the other end due to varying conditions of the line or exchange. For these reasons, AM is rarely used, except when it is used in conjunction with phase modulation (as we shall see later).

Neither frequency nor phase modulation suffer from the drawbacks mentioned for amplitude and as such both are used extensively. Most of us will be concerned with general purpose communications, in which frequency modulation (otherwise known as Frequency Shift Keying or FSK) is used, this being relatively simple to demodulate. In phase modulation (Phase Shift Keying or PSK), two phases, 0° and 180° can be used for the two states. However, since detection of absolute phases is quite tricky, the alternative Differential Phase Shift Keying (or DPSK) is more commonly used. In this scheme there is a phase shift at the start of every time interval, $+90^\circ$ for a 0 and $+270^\circ$ for a 1.

Figure 2 shows a binary signal modulated by AM, on/off keying, FSK, PSK and DPSK.

An FSK signal can be considered as two on/off keyed signals of different frequencies, each on/off keyed. As each such signal is keyed, sidebands of a width proportional to the data rate are produced at either side of the mark and space frequencies. The maximum fundamental frequency produced is half the data rate, so the maximum bit rate which can be accommodated within the 3kHz bandwidth of a PSTN is 1200. This is shown diagrammatically in Figure 4(c) which we will cover in further detail later.

PSK is more difficult to understand but in essence very similar constraints apply. In order to provide higher data rates, more advanced modems take data bits in groups of more than 1 at a time in order to reduce the number of transitions and hence the maximum modulation frequency. So, for example, taking bits two at a time (dibits), the possible combinations are 00, 01, 10 and 11, so 4 phase shifts are required and these are typically 0° , 90° , 270° and 180° respectively. This modulation method is often referred to as 4DPSK. Figure 3 shows some phase modulation techniques, and illustrates 4DPSK. We must now use the term bits per second rather than band rate, since the two are no longer interchangeable. The reason for this is explained next month.

For higher speeds still, the next logical step after use of dibits is use of tribits. Now we have to go to 8DPSK, as shown in the phase diagram in Figure 3(d). As a quick explanation of phase diagrams, if a line is drawn from the centre to any point, its angle represents the phase and its length the amplitude.


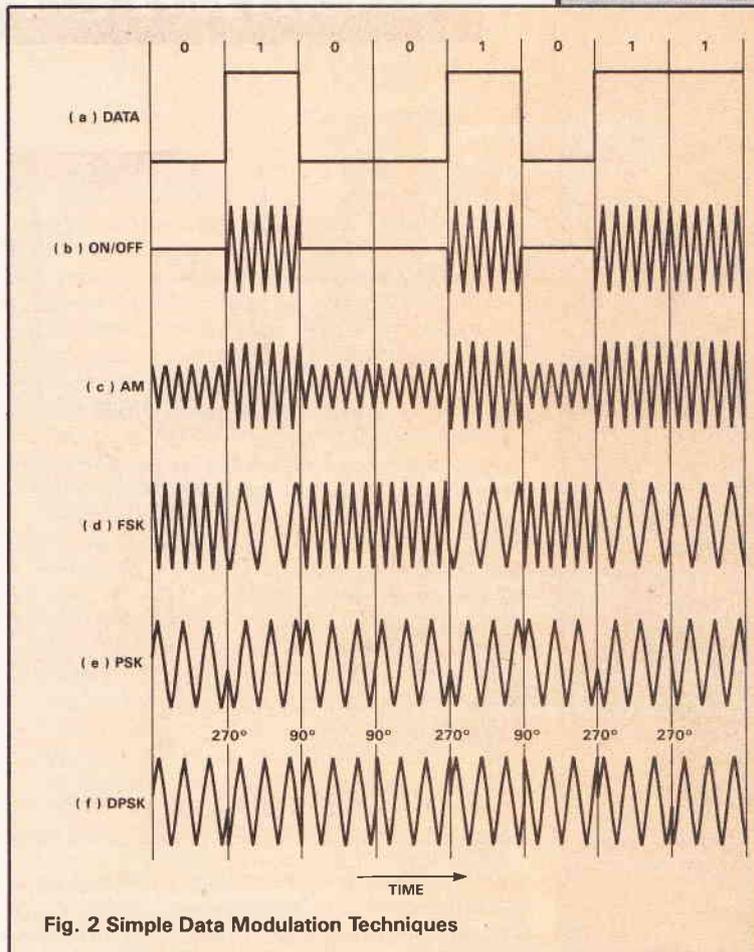


Fig. 2 Simple Data Modulation Techniques

The next logical step for achieving even higher speeds would be to go for 16DPSK but since we are the talking about detecting phase differences of only 22.5° this approach is not usually taken. Instead a modulation method called Quadrature Amplitude Modulation (QAM) is used for the highest specification

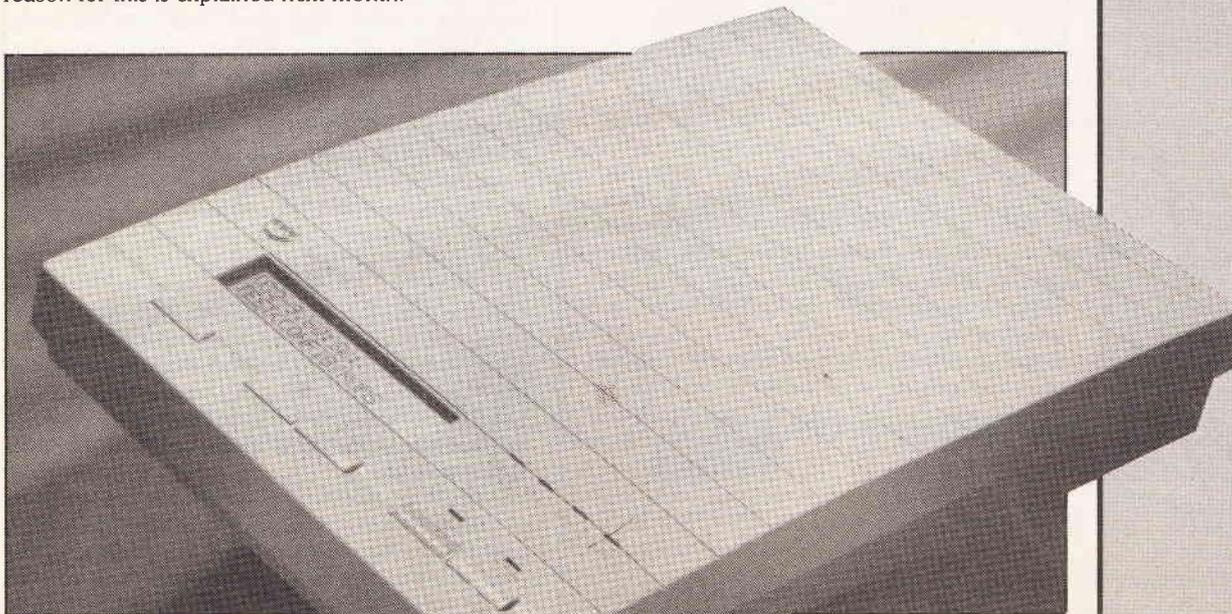

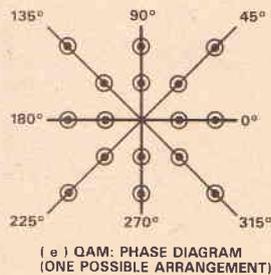
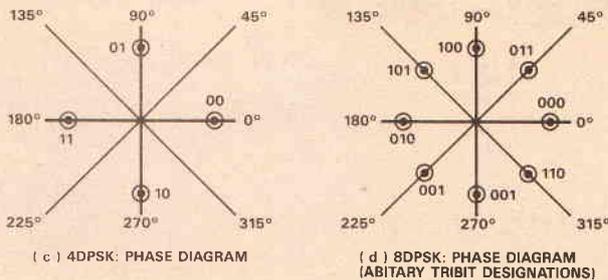
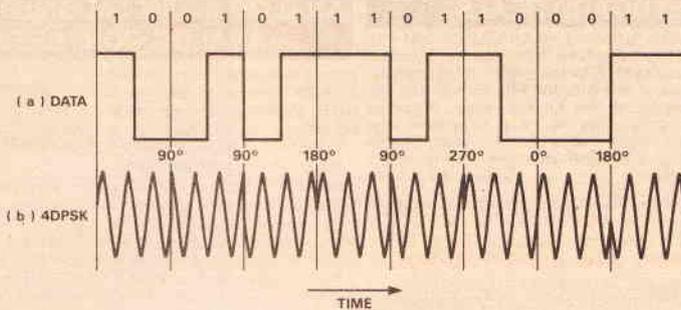


Fig. 3 Advanced Data Modulation Techniques

possible on switched telephone lines. QAM is a hybrid modulation technique in which various combinations of phase and amplitude represent quadbits. Of course, the amplitude modulation must be other than on/off keying, even though we get a poor signal-to-noise ratio, as it is not possible to detect the phase of a signal with zero amplitude! So, for example, four phases each with four amplitudes, or eight phases each with two amplitudes, both give the 16 combinations

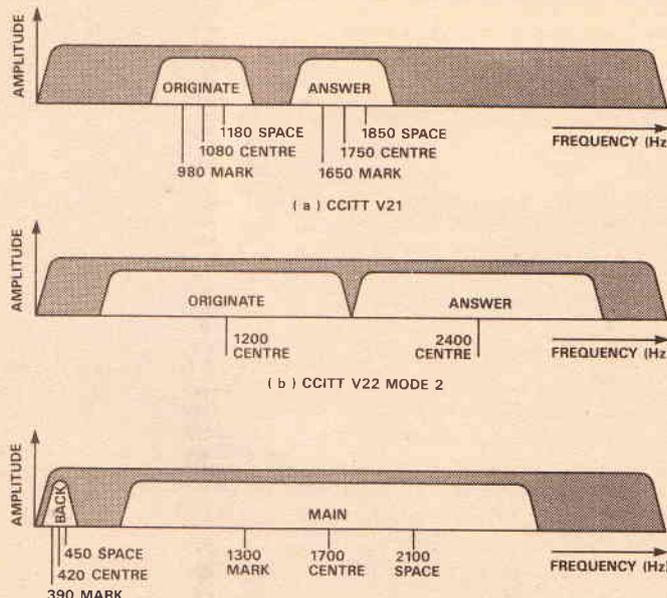


Fig. 4 Modem Frequencies

required for quadbits. The latter alternative is illustrated in Figures 3(e). In fact, there are numerous QAM systems possible.

I ought to point out that this technique of cramming more bits into each time interval cannot go on forever. There is a theoretical limit to the amount of information which can be transmitted on a particular channel, and this depends on the bandwidth and the signal to noise ratio. For those with a mathematical leaning, the formula is as follows:

$$\text{Information rate} = \text{Bandwidth} \times \log_2 \left(1 + \frac{S}{N} \right)$$

This suggests that the absolute maximum for a switched telephone circuit is about 20,000 bits per second (bps). In fact other factors tend to limit this and for all practical purposes, 9600 bps may be considered the limit.

Duplex Communication

Figure 4(c) shows a 1200 bps signal, the highest of the normally encountered transmission rates possible on a PSTN (using FSK). As already mentioned, the mark and space frequencies need a separation of 1200Hz at this data rate and the half-way position between these frequencies if referred to as f_c , the centre frequency of the channel. If the data rate were halved, the mark - space frequency separation also halves to 600kHz and so two such channels could be accommodated. In this case one channel could be used for flow of data in one direction and the other for data in the opposite direction. A communications system in which data can travel in both directions at the same time is called full duplex — FDX, V21 is such a case and is illustrated as Figure 4(a).

To achieve 1200 bps in both directions the channel would have to be half duplex, used alternately for communications in each direction. Actually, a 1200 baud channel does not entirely fill 3kHz and V23 allows a so-called back channel at the reduced speed of 75 baud as shown be seen in Figure 4(c). This is the specification used for the Prestel system. The 1200 baud channel is used for the data passing from Prestel to the terminal whereas the 75 baud channel is used for the limited amount of data passing from the terminal.

The example shown in Figure 4(b) is V22, 1200 bps FDX. It should be noted that since 4DPSK is used here, the baud rate is only 600 and hence FDX becomes possible. This also differs from the other diagrams in not showing mark and space frequencies since we are now dealing with phase rather than frequency shift keying.

Having set the scene, the remainder of this discussion of modems will attempt to guide you through the modem jungle and assist you in selecting one which is suitable for your needs.

Acoustic Modems

It is quite possible to build a modem. Most of the basic functionality can be found in a single chip. These vary from the basic types to sophisticated VLSI designs offering multiple modes which cost in the region of £18.00. The bad news is that having built such a modem it would be illegal to connect it to the British Telecom system.

For this reason most home constructed units are of the acoustic modem variety. Here, instead of plugging directly into a telephone socket, the modem interfaces acoustically to the telephone handset via rubber cups. There is no direct connection to the

telephone system. The modulated signal coming from the modem goes into the mouthpiece of the handset and the return signal to the modem comes from the earpiece. In the days before telephone sockets were as abundant as they are today, acoustic modems were quite popular as they obviated the need to have a modem socket installed at great expense.

Except for the fact that you can build such a modem yourself, the only advantage now is that they can be used in conjunction with a portable computer in hotel rooms, telephone boxes or wherever. The disadvantages, of course, is that acoustic modems can be prone to audible noise pickup.

Integral Modems

The integral modem is another deviation from the conventional modem. It is currently becoming popular, especially in the PC arena. Here, instead of connecting to the computer via an RS232C link, the modem plugs directly into one of the computer's expansion slots. The advantages are that it tends to be a less expensive alternative, it doesn't take up extra desk space and it doesn't tie up one of those valuable RS232C ports.

The disadvantage is that on changing computers, the modem becomes obsolete as it won't migrate to the new machine. This is much less of a problem with PC compatibles, which are stable long-term products with a downward-compatible upgrade oath (PC add-ons will plug into an AT 80286 or 80386 based machine).

Standards

So, now to the V numbers, which refer to any of the categories of modem which we have discussed.

V numbers are CCITT (Comité Consultatif Internationale de Telegraphie et Telephonie) recom-

mendations in connection with data transmission over telephone circuits. Where as these recommendations refer to all sorts of aspects including character encoding, circuit definitions and error control, the ones which are of interest in selecting a modem are those which specify the baud rate and modulation methods which it uses.

Of these, some are only intended for leased lines and even of those intended for ordinary switched telephone lines some are quite obscure. Table 1 shows the more common numbers which define modem operating characteristics for use on general telephone circuits.

Now, if the modem is needed to communicate with one or more bulletin boards then it's simply a matter of ensuring that the modem obtained matches that specified for the services required. For example if you intend to use Prestel (the BT viewdata system) you need a V23 modem.

If, on the other hand, a pair of modems are being obtained to implement a specific link then it makes sense to get a pair which operate at the highest possible baud rate. Remember though, that the higher the speed, the more you can expect to pay. Also, it is possible to get modems which operate on a number of these standards but again these are more expensive.

Sometimes you may encounter modems specified as, say, Bel-103/113 or Bell-202 rather than by a V numbers. The CCITT standards are European, whereas the Bell standards are North American. Some Bell standards are CCITT compatible, others are not. However it is unlikely that many readers in the UK will specifically want Bell compatible modems unless they intend to access American bulletin boards and this practice tends to be prohibitive in terms of telephone call charges. If the modem is being used for say amateur radio data communications, on the other hand, it could be that there is more of a requirement for this compatibility. Modems from North America are unlikely to have the requisite BT certification. It is possible to get multiple standard (CCITT/Bell) modems which are BT certified, but if they are switched to a Bell standard, the certification may no longer apply and the user may be liable to prosecution — you have been warned.

Table 2 shows common Bell standard modems with notes on CCITT compatibility.

A quick word about Hayes compatibility. Simple modems require the telephone number to be dialled on a telephone before connecting the modem. More advanced models have an auto-dialling facility which, when driven by the computer, allows the user to select the name of the required service from a menu after which the computer will look up the number and dial it.

On an integral modem, the auto dialling is carried out by the dedicated software which comes as part of the package. With a conventional modem, auto dialling (and various other functions) are initiated by ASCII commands sent via its RS232C interface. The Hayes protocol is simply an industry standard syntax for these commands, use of which means that the modem will be compatible with most applications software.

Modems are available with either tone dialling or pulse dialling or can be switched between the two. In pulse dialling each digit is represented by a string of pulses varying from 1 to 10 (which represents 0). With

Table 1

Bell Standard	Speed (bits/s)	CCITT compatibility
103/113	300	Uses different mark and space frequencies from V21 hence not compatible.
212A	1200	Compatible with V22.
	300	This Bell 103 compatible mode is not compatible with any CCITT recommendation.
202	1200 (600)	Mark and space frequencies are different to V23 but only by 100Hz. They are interoperable under good conditions.
	1200/75	Some new Bell 202 modems have a 75 baud back channel for viewdata use. This is V23 compatible.

tone dialling, each digit is represented by a different frequency of audio tone.

Obviously it is necessary to ensure compatibility with the local telephone exchange. In the UK, pulse dialling is the most universally accepted and until

System X came into existence was the only method used. The newer System X exchanges will accept both pulse and tone dialling. In other countries it would be necessary to check out the requirements of the local system.

Table 2

Standard /Mode		FDX /HDX	Speed Bits/s	Modulation	Synch/ Asynch	Comments
V21		FDX	0-300	FSK	Asynch	
V22	1	FDX	1200	4DPSK	Synch	300 is FSK
	2	FDX	1200	4DPSK	Asynch	
	3	FDX	600	2DPSK	Synch	
	4	FDX	600	2DPSK	Asynch	
	5	FDX	1200/300	2DPSK	Asynch	
V22 bis	1	FDX	2400	QAM	Synch	V22 compatible V22 compatible
	2	FDX	2400	QAM	Asynch	
	3	FDX	1200	4DPSK	Synch	
	4	FDX	1200	4DPSK	Asynch	
V23	1	HDX	600	FSK	Asynch	Prestel
	2	HDX	1200	FSK	Asynch	
	3	FDX	1200/75	FSK	Asynch	
	4	FDX	75/1200	FSK	Asynch	
V32	1	FDX	9600	QAM	Synch	High price, normally only used for professional applications.
	2	FDX	9600	QAM	Asynch	
	3	FDX	4800	QAM	Synch	
	4	FDX	4800	QAM	Asynch	
	5	FDX	2400	QAM	Synch	
	6	FDX	2400	QAM	Asynch	




The Archer Z80 SBC

The **SDS ARCHER** – The Z80 based single board computer chosen by professionals and OEM users.

- ★ Top quality board with 4 parallel and 2 serial ports, counter-timers, power-fail interrupt, watchdog timer, EPROM & battery backed RAM.
- ★ **OPTIONS:** on board power supply, smart case, ROMable BASIC, Debug Monitor, wide range of I/O & memory extension cards.

CIRCLE NO. 122 ON REPLY CARD

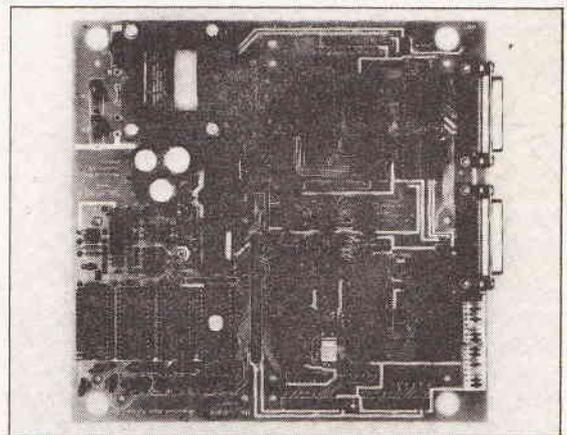


The Bowman 68000 SBC

The **SDS BOWMAN** – The 68000 based single board computer for advanced high speed applications.

- ★ Extended double Eurocard with 2 parallel & 2 serial ports, battery backed CMOS RAM, EPROM, 2 counter-timers, watchdog timer, powerfail interrupt, & an optional zero wait state half megabyte D-RAM.
- ★ Extended width versions with on board power supply and case.

CIRCLE NO. 147 ON REPLY CARD

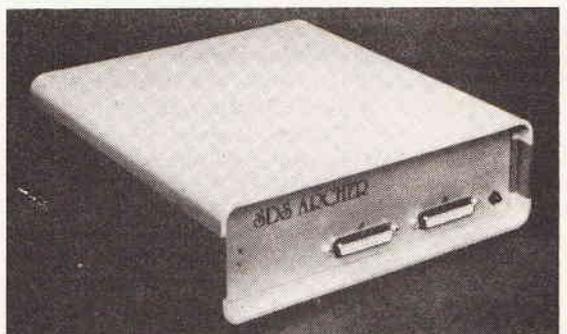

Sherwood Data Systems Ltd

Unit 6, York Way, Cressex Industrial Estate, High Wycombe, Bucks HP12 3PY. Tel: (0494) 464264

TAME THAT TIMER!



James Archer describes how PDC — the Programme Delivery Control System — will take the headache out of setting VCR timers

One of the major successes of the television industry over the past few years, and one that was never predicted by the crystal balls of the 'new technology' pundits, has been the pre-recorded videotape rental market. Who would have foreseen that within a period of about five years the demand for prerecorded tapes would have grown from virtually nothing, until it is now possible to find a video rental

shop in some of the country's smallest and most isolated hamlets, and that it would be worthwhile for shops to stay open late into the night to satisfy the demands of viewers wanting to hire the latest 'movie' to watch whilst eating their takeaway suppers?

Pushing a prerecorded videocassette into the slot and pressing the 'play' button is so simple that anyone can do it, and some video machines are used solely for the playback of these tapes.

The vast majority of video recorders, however, are also widely used to 'time-shift' programmes that are recorded off-air, for playback at a more convenient time. Unfortunately, though, many people find it difficult or even impossible to understand the complex instruction books that come with their recorders, and so are unable to make the best use of their equipment.

Timing Troubles

Modern video recorders offer very sophisticated timed-recording facilities, often allowing the viewer to record many different programmes at different times over a period of up to a fortnight, or to have individual episodes of a favourite soap opera recorded every night for a week.

Since the setting of the recorder timer often appears difficult, most viewers never take the trouble to learn how to make full use of the timer facilities and restrict themselves to being able to record just one programme, finding this sufficient for their everyday purposes. Installation engineers say that the only people who make use of the full range of the timer facilities are teenage children, and they well know that a return call to a customer with a new video recorder can often be avoided if the installer makes sure that the children of the family understand how it all works!

Another problem with recordings being pre-set for some time in the future, is that the broadcasters do not always keep to their published schedules, which can lead to great disappointment when the film doesn't start until later than the published time, and you find that you have recorded all but the last ten minutes of it and that you will never know who the villain was in the murder mystery!

VPS — The German Solution

These problems are not restricted to our own shores, and to help overcome them, the Germans designed a system of controlling timed recording sessions which is much simpler for the viewer to understand and operate. The VPS (Video Programme System) switching system was developed by the West German broadcasting organisations, in conjunction with their equivalent of BREMA, the ZVEI, and has been operational since the autumn of 1985.

Since the early 1970s some of the lines of the vertical blanking interval, the period at the end of a picture during which the scanning spot returns from the bottom right-hand side of the television screen to the top left in order to begin scanning the next picture,


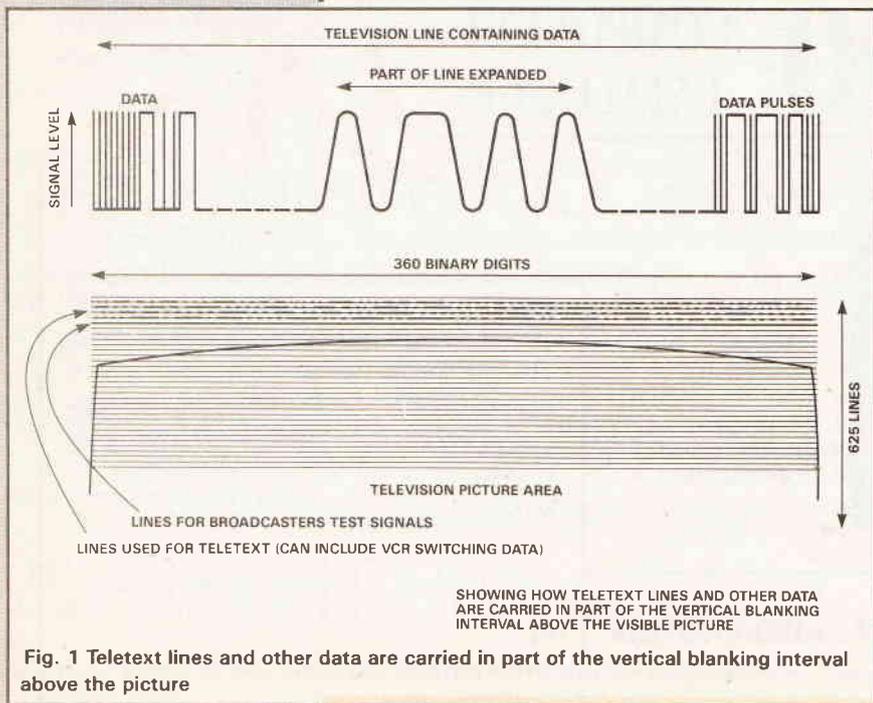


Fig. 1 Teletext lines and other data are carried in part of the vertical blanking interval above the picture

Data bit number	BYTE 11							BYTE 12							BYTE 13							BYTE 14																											
	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31																		
VPS bit number	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31																	
Normal label	ADDRESS REGION							DAY							MONTH							HOUR							MINUTE							COUNTRY							PROGRAMME SOURCE						
System status code	SPECIAL SYSTEM CODES																																																
No label code	A	A	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	N	N	P	P	P	P																	
Interrupt code	A	A	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	N	N	P	P	P	P																		

A = ADDRESS CODE N = COUNTRY CODE P = PROGRAMME CODE

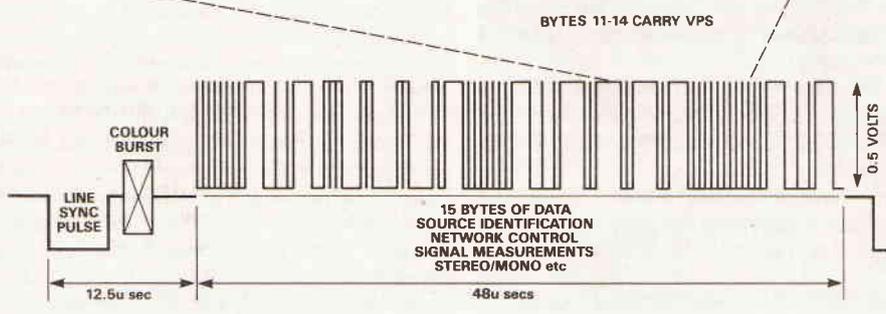Switches to timer when this code is received
Recorder pauses when this code is received



SHOWING HOW LINE 16 OF THE WEST GERMAN TV TRANSMISSIONS IS USED TO CARRY DATA, 4 BYTES OF WHICH ARE USED FOR THE VPS SWITCHING

Fig. 2 Line 16 of the West German TV transmissions is used to carry data, 4 bytes of which are used for the VPS switching

have been used to carry Teletext, an information broadcasting system in which pages of text and graphics are transmitted in digitally coded form. This information is effectively carried on otherwise unused television lines situated above the visible picture.

With the VPS video recorder switching system, each programme is made to carry a teletext-like coded label with each picture, and when the information on the transmitted label matches the information that has been previously put into the recorder, and not before, the programme will be recorded. At the end of the programme the recorder will switch off until it recognises another label for a programme which it has been asked to record. Therefore, the actual time at which the programme is transmitted is unimportant, since the video recorder will not start until it recognises the label at the beginning of the required transmission.

For some years now the West German broadcasters have been carrying coded data on line 16 of each TV picture, one of the data lines in the vertical interval between picture frames. This data is used to provide source identification, remote control of the network, identification of stereophonic sound channels, and for the transmission of test measurement results. The VPS labels for each programme item are carried in four bytes of the data transmitted on line 16. The comparator in the home video recorder continuously checks to see if the label information decoded from bytes 11-14 of line 16 matches the information that has previously been programmed into it by the viewer.

Grundig have actually been making video recorders with VPS for some years now, several German networks are transmitting the labels, and Austria and Switzerland originally announced that they too intended to introduce VPS. Since this system is not in use in the UK, and our line 16 is used to carry ORACLE teletext information, Grundig (UK) have to remove a small VPS circuit board from their video recorders which are sold in the UK. For a long time UK engineers wondered why the Germans did not make use of the standard teletext transmissions for tape recorder switching purposes, since the IBA demonstrated that such a scheme was practicable back in the late 1970s. At that time the IBA's intention

was to use automatic teletext-controlled switching to allow UK schools' broadcasts to be transmitted during the night. The UK teletext standard, on which the German teletext system is based, actually allocates a location in magazine 8, a so-called 'pseudo row address', specifically for this purpose, but the IBA idea was not taken up.

The search for a European standard

The German VPS system showed that it was technically possible to provide a more 'user-friendly' system of programming video recorders, but broadcasting engineers in other European countries were not convinced that this was the best system that could be achieved. It would obviously make sense to have a common system for Europe, in the interests of both manufacturers and viewers, and so for about the last five years members of the EBU have been involved in discussions amongst themselves and with European industry to try to agree on a system which would have all the features of the German VPS system, but with considerable enhancements, and which could encompass all likely future requirements. The Programme Delivery Control System (PDC) is the result of this work.

PDC in practice

The PDC system provides a service, designed for domestic use, which allows suitably equipped video recorders to record automatically programmes which the viewer has previously selected. PDC can essentially be divided into three parts: the labelling of the programmes prior to transmission by the broadcaster, the preselection of the programmes by the viewer, and the automatic control of the video recorder by the label data which is sent as part of the television broadcast signal.

Programme Labelling

Each programme can carry, as an integral part of its accompanying teletext service, various items of

information which exclusively label the programme. Some of the components of the label are essential to the operation of the PDC system, others are optional, to provide extra information, such as the Programme-Type (PTY) byte which identifies the type of programme or the series to which it belongs, and the Conditional Access Flag (CAF flag), a bit of data which indicates whether or not a programme is in scrambled form.

The essential parts of the programme label consist of;

CNI — The Country and Network Identification.

AD — The Announced Date, which gives the scheduled date of start of transmission in terms of years, months, and days.

AT — The originally announced time. This is in two groups, the announced starting time, and the announced finishing time, both being expressed in hours and minutes.

MCP — The Menu Cursor Position. This is used to link the text information on the teletext 'TV-guide' page with the actual programme label information.

It is also desirable, but not essential to the working of the system, for the label to carry;

PTL — The programme title in clear text form.

LTO — The local time offset. All times used in the system are carried as Universal Time, UTC, with an adjustment being made for local time differences, so that the viewer need only ever be concerned with local time.

PD — The expected Programme Duration, in hours, minutes seconds.

A typical programme label therefore consists of a variable number of bits of information, which allow any programme to be uniquely identified, as well as giving further useful information about the programme.

newspapers, or from the appropriate pages on teletext.

Once the viewer has made these decisions, the relevant information must somehow be put into the memory circuitry of the PDC-equipped video recorder. The actual input of instructions, telling the recorder which programmes to record and when, can be achieved in several ways.

We have seen that the digital labels which accompany each programme contain, amongst other things, the month, date, hour and minute of the programme's starting time, plus the code for the programme source, so it is easy to use the remote control handset to insert the required information when prompted by a message on the television screen.

Even easier is to wipe a simple 'light-pen' over the bar-codes that will be printed in the programme journals such as Radio Times and TV Times. Merely passing this pen over the codes printed beside all the programmes you would like to record, sets up the required labels without any further action on the viewer's part, and this is bound to make life much easier for the non-technical. It is interesting to note that Panasonic have recently entered into an agreement with the BBC to carry a list of each week's films accompanied by bar codes in the Radio Times which can be read only by viewers who have bought a particular type of Panasonic recorder, equipped with a light-pen code reader. This must not be confused with PDC, but is an indication that such methods of programming video recorders may well appeal to the public.

A third, and probably the best method of pre-programming the video recorder is to make automatic use of the teletext pages which contain the details of television programmes to be transmitted. There are two recognised methods of utilising teletext for this purpose.

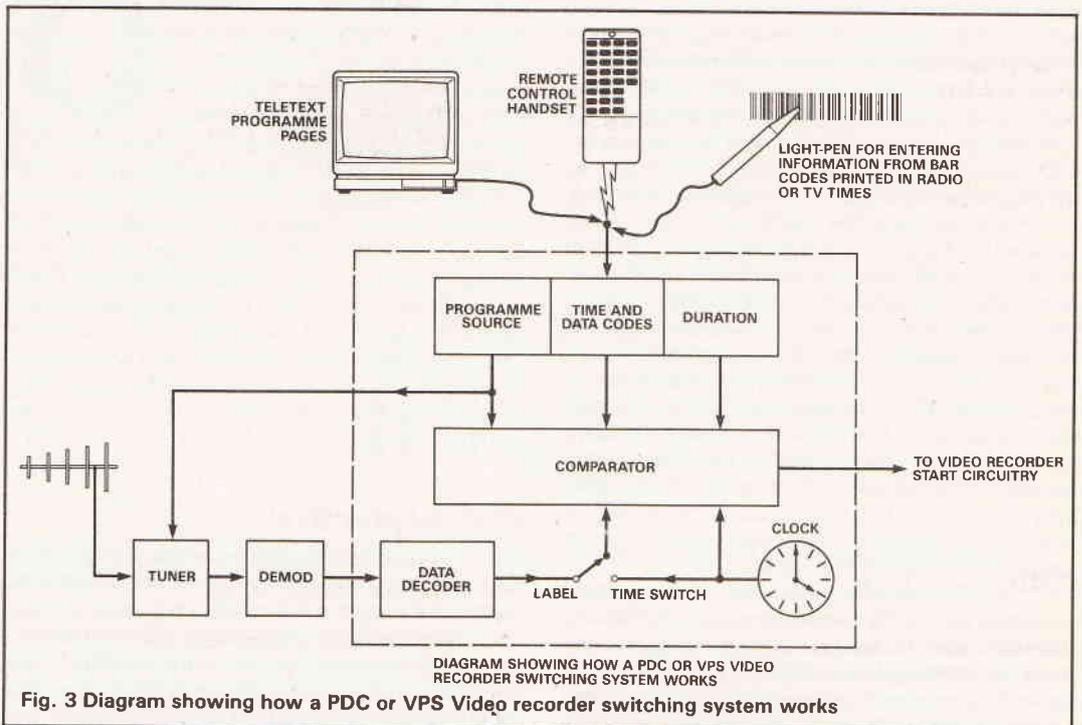


Fig. 3 Diagram showing how a PDC or VPS Video recorder switching system works


Preselecting The Programmes You Wish To Record

The viewer must first of all choose which programmes are to be recorded, and the basic information about which programmes will be transmitted and when, can be obtained from the Radio or TV Times, from the

The first, and simplest, is for the broadcaster to add data to teletext 'TV-guide' pages, which incorporates all the information needed for recording. Some of this information could be visible, such as instructions as to how to proceed, but some of the actual labelling information could be concealed. To preselect a programme to be recorded, the viewer merely moves a cursor up and down the screen until

it is in line with the desired programme, and then presses a button on the teletext handset. The process is repeated for all the other programmes that are to be recorded, and the PDC equipment will then automatically take control.

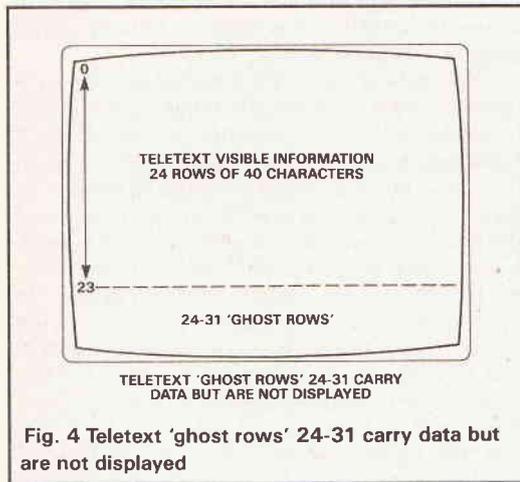A further development of the use of teletext programme pages is for the broadcaster to send information which is additional to the normal teletext TV-guide pages, using the so-called 'ghost rows', rows



of teletext which can carry data, but which are not displayed on an ordinary teletext screen. (A normal teletext page displays only 24 rows of information, but has the technical capability to carry 32 rows.) This additional information can be in the form of a computer programme which can be used to provide a more extensive menu than the normal TV-guide, which can carry more details about the programmes and which can incorporate error-checking to alert the viewer if incorrect entries are made.

Automatic Control Of The Video Recorder

The menu selection process described above first of all causes the labels appropriate to each of the programmes to be inserted into the memory of the PDC-equipped recorder. The recorder then goes into 'stand-by' mode, silently monitoring each of the transmitted programmes until one comes along which is accompanied by a programme label which matches one in the recorder's memory. Once an incoming transmitted label is found to match a label stored in the PDC memory, the recorder switches itself on and records the programme, switching itself off again when it receives a label indicating that the programme has ended. The recorder then continues to look out for a programme containing the next label which has been pre-programmed.

Other Options

Since it is unlikely that all programmes will be labelled with PDC information, especially in the first few years after its introduction, the system allows for the automatic selection of label-controlled or timer-controlled operation of the video recorder, so as to cope with programmes that haven't been labelled. It is possible to envisage that the use of the timer could be arranged to allow the recorder to wait for a label only during a particular time slot, perhaps half an hour before and an hour after the expected transmission time, thus minimising power consumption.

Provision have also been made to allow for the recording of programmes which are unscheduled,

and for programmes which are transmitted at different times from the scheduled time of transmission to be recorded properly.

Interruptions to programmes

If a broadcaster has to interrupt a scheduled programme part way through for any reason, the PDC system allows the broadcaster to send signals to interrupt the recording, and to start it again when the scheduled programme resumes.

Whilst it is true that if the broadcasters would cooperate by putting 'off' and 'on' labels at the start and finish of advertisements, the PDC system could even allow films to be recorded without recording the advertising breaks, it is even more true that in any system supported by advertising there must be sound commercial reasons for preventing this from happening!

Future Applications

PDC has been designed to be compatible with the future MAC satellite transmissions, so that a PDC-equipped recorder will be able to automatically record PDC coded transmissions from satellite as well as from terrestrial sources.

PDC might well turn out to be a good method of enabling teachers to automatically 'download' the schools programmes of their choice. If schools programmes were transferred to night hours, this might free the daytime schedules for more profitable programmes. To do this at present, would require the teacher to learn the intimate workings of the video recorder timer, in order to record some schools broadcasts but ignore others. PDC would make the whole task simple.

Starting Soon – Perhaps!

The PDC system, as defined so far, is a technical transmission specification, which does not yet include any rules for day to day operation of the service. EBU members are to continue their collaboration with industry to ensure the orderly implementation of the service, and the controlled introduction of any new features.

In the UK, Channel Four are likely to take the lead in introducing this exciting new facility, as early as next year, and although this should encourage the video recorder manufacturers to begin to build-in PDC circuitry, there could still be potential problems on the horizon.

Earlier this year the BBC let it be known that it was considering introducing a somewhat different system in which each programme would have its own discrete label, but that these labels would not be in the standard PDC format, and might be exclusive to the BBC and its programme journal Radio Times. The idea was that the BBC's special teletext decoder, which could plug into the back of existing video recorders, would decode the transmitted label, and that the adaptor unit would then emulate the standard infra-red transmission from a remote control unit in order to switch the recorder on and off at the beginning and end of the chosen programme. Novel though the use of this technique would have been, and with the advantage that existing recorders could easily be converted to the new service, the introduction of such a different system could only serve to delay the universal use of the PDC system, and so it was with some relief that manufacturers learned that this idea has now been dropped. Let us hope that all the broadcasters, both satellite and terrestrial, will adopt the PDC system before too long.

TESTING, TESTING

Mike Barwise explains how to test the frequency response of megaphone amplifier

The final test of our megaphone amplifier which is of interest, is a quick look at its *bandwidth* or frequency response. The basic method of testing is obvious; apply constant amplitude input signals over a wide range of frequencies, and record the output amplitude obtained. There are, however, several different practical approaches to this test, and the chosen approach will depend on how much money and/or time you have.

If you are rich and in a hurry, the tool you will use is the *network analyser*. This consists of a spectrum analyser combined with a very accurate and stable oscillator. The oscillator supplies the input signal to your circuit under test (CUT), and the output from the CUT is fed to the spectrum analyser. The oscillator sweeps through a user-determined range of frequencies in an extremely linear manner, and the oscillator signal and output signal from your CUT are compared to provide a display image which is a direct graph of gain against frequency. The network analyser is extremely quick, reliable and accurate, but expect to pay about £3000 for a very basic one.

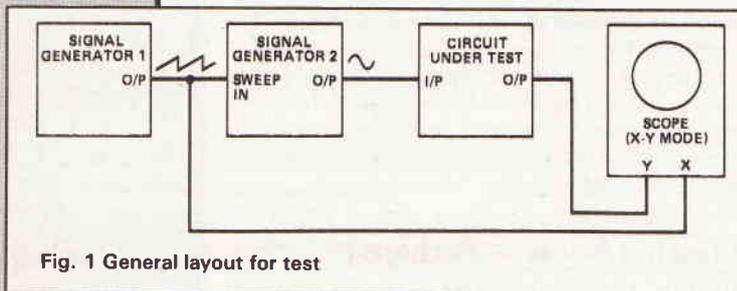


Fig. 1 General layout for test

At the other end of the scale, if you are poor but have lots of time (the position of most amateurs) you can manually switch your signal generator through its frequency range, and, using your 'scope in dual trace mode, take readings of the input and output amplitudes at your CUT by hand and eye. The results from this will be in terms of peak to peak values, whereas the network analyser RMS power values, but for sinusoids the two are directly proportional anyway, so this does not really matter. Just divide your peak to peak values by $2\sqrt{2}$ or about 2.8, and you get the RMS.

There is, however, a very neat third alternative, which is possible if you have a signal generator and 'scope which are a little more than basic instruments. It is effectively to automate the manual method just described. For this, you will need two signal generators; one capable of outputting a reasonably linear sawtooth ramp at low speed, and the other equipped with a sweep input; a voltage control of frequency. You will also need a 'scope either capable of X-Y operation, or equipped with an external trigger socket. The X-Y mode is distinctly preferable.

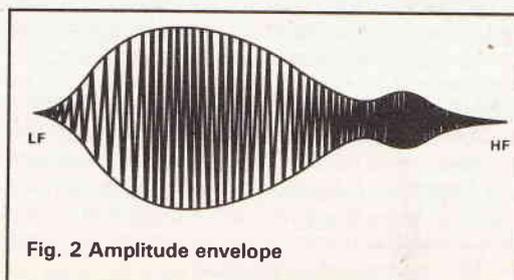


Fig. 2 Amplitude envelope

What we are going to do is drive the CUT with a swept frequency sinusoidal signal from the lowest to the highest frequency of interest and synchronise the 'scope image so that it shows the peak to peak value of the CUT output across the whole frequency range, in a single screen.

The general layout of the test setup is shown in Figure 1. The Y (vertical) axis of the 'scope displays the voltage swing of the waveform as normal. The X (horizontal) axis is driven by the sawtooth ramp which also causes the main signal generator to perform its sweep. The sweep time must be very long compared with the cycle time of the lowest frequency of interest, so that several cycles of each frequency band, from the bottom up, are present on the display. For example, if you are interested in frequencies from 100Hz to 1kHz, there should be about ten cycles at least of even the 100Hz range covering the first division (cm) or so of the display, so the sweep rate should work out to be around 1cm for every $10 \times 1/100 =$ in other words, 1/10 seconds, 10cm/sec. Thus the whole frequency sweep (ten horizontal divisions) will take 1 second. The minimum cycle count per frequency band is the important factor, we are not trying to resolve individual cycles in the display. What we want is the *amplitude envelope* shape across all frequencies (Figure 2). For wider frequency ranges, the sweep time is correspondingly longer, so either a long persistence phosphor (which glows for about twice as long after the electron beam has passed) or an X-Y pen plotter could come in useful, although the latter might fail to resolve the upper frequencies of the sweep adequately. Probably the best all-round alternative is an instant picture camera with the shutter kept open for the whole duration of the sweep. This is a standard technique.

The alternative setup using an external trigger to the 'scope, is shown in Figure 3. In this case, the 'scope timebase must be set so that it takes slightly longer to sweep the whole screen than the ramp time of the controlling sawtooth, and the fast falling edge of the sawtooth is used to trigger the sweep via a high-pass filter, which is often built into the 'scope trigger as an option (HF TRIGGER).

The advantage of the X-Y mode approach is twofold: firstly, the sweep control ramp duration does not have to match a preset sweep time available from the 'scope, and, secondly, any non-linearity in the ramp will not matter. What is essential, however, is a near perfect linearity in the V/F conversion of your signal generator, as any errors here will make interpretation of the display very difficult. There is also another general drawback of both these approaches. The display on the 'scope screen is a broad trace of varying amplitude, and is quite difficult to interpret; not least because the horizontal axis is linear, and we normally want a logarithmic horizontal axis. We normally express rolloff and cutoff in dB per octave.

There is a quite simple gadget you can construct to solve both these problems in one go. A block diagram is given in Figure 4. This gadget replaces the first signal generator (the sweep ramp generator) in the X-Y mode alternative (fig. 1). What it does is to generate a staircase ramp with logarithmic steps instead of a continuous ramp. With steady voltage on the X input to the 'scope, the spot will stop at some point along the horizontal axis, and the Y signal will cause the spot to draw a fine vertical line. The spot only moves horizontally at the transition between

steps, so the resulting trace on the 'scope screen looks like Figure 5a; a bar graph or histogram. The half wave rectifier removes the negative-going half of the signal, producing a horizontal baseline to the graph and simplifying analysis of the data. The EPROM between the counter and the DAC provides the linear to logarithmic conversion, and the excess resolution of the DAC additionally allows compensation of any non-linearity in the sweep function of your signal generator.

In its most basic form, this setup has fixed overall span, resolution and set points, but this should not pose a problem for audio work, where you want nominal half octave points in the range 20Hz to 20kHz. You can, of course, pick any frequencies you choose by putting the right codes in the EPROM. The method of setting up is to monitor the sweep voltage from a stable source using a DVM, measure the associated frequency using your ETI frequency meter, and, when the frequency you want is generated, calculate the DAC input code for programming into the EPROM. The one limitation of this system is that the HF end of the display is crowded together, as the 'scope has a linear sweep. A small refinement is an additional DAC driven direct off the counter outputs. The voltage out of this second DAC feeds the 'scope X axis, and the ramp DAC feeds the signal generator alone. The display then looks like Figure 5b. The diagram of Figure 4 assumes a maximum of 32 lines on the 'scope screen, which is about as many as can be easily read individually. The 8 bit DAC uses five bit input, allowing a user defined 'gap' between the lines.

The beauty of the solution of Figure 4 is that there is no longer any uncertainty in the display. Each line corresponds to a specific spot frequency. Using the methods of Figures 1 and 3, it is much more difficult

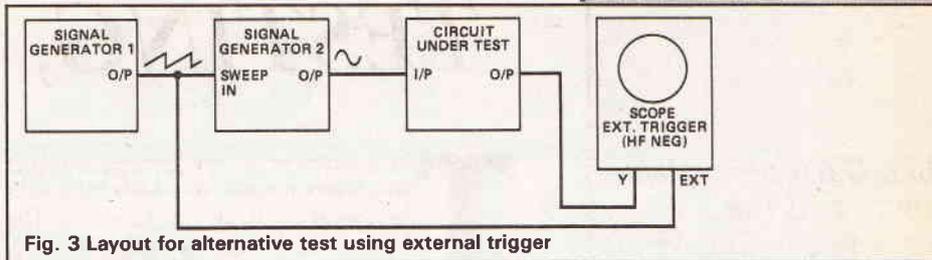


Fig. 3 Layout for alternative test using external trigger

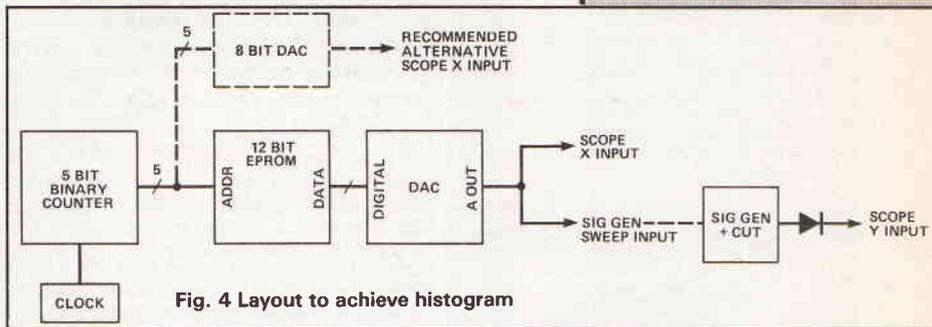


Fig. 4 Layout to achieve histogram

to determine the response at a particular frequency, as there are no on-screen markers.

This type of add-on is a very common requirement in more advanced testing. The ability to come up with such tricks comes with experience, but the need is the most important thing: however much you spend on a given piece of test gear, there will always be a job it cannot do. We will look at a selection of test rig tricks for analogue in the next part of this series, before going on to digital techniques.

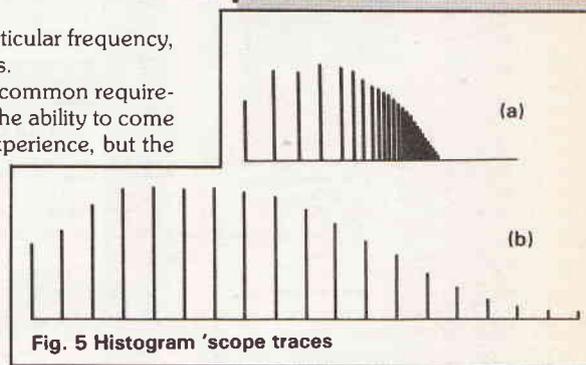


Fig. 5 Histogram 'scope traces

HENRY'S

45th ANNIVERSARY

ELECTRONICS DISTRIBUTORS FOR TRADE/INDUSTRY EXPORT AND HOBBYISTS

BIG DISCOUNTS FOR EDUCATION AND QUANTITY

- Tools/Service Aids
- Test Instruments (UK's largest in-stock Range)
- Public Address/Disco
- Security/CCTV/Doorphones
- TV, Video Distribution
- Components Chassis Speakers, Audio, TV, Computer Accessories

SPECIAL OFFERS

Dmm was (£18.95) **£13.95** (30 models stocked)

1 kw outdoor PIR Lights controller was (£32.95) **£19.95**

VHF/UHF TV/FM Amplifier was (£11.95) **£9.95**

Analogue MM 27 Ranges CAP/Hfe/Temp/10A AC/DC etc. was (£39.95) **£29.95**

ALL PRICES INCLUDE VAT

FREE CAR PARKING

Two Car Parks (Bell and Church Streets). Present your ticket when purchasing and get one hour as discount.

OPEN 6 DAYS A WEEK FOR CALLERS AND TELEPHONED ORDERS

HENRY'S AUDIO ELECTRONICS

404 Edgware Road, London W2 1ED

Instruments/Audio 01-724 3564

Security/Communications/CCTV 01-724 0323

Components 01-723 1008 Fax: 01-724 0322

Trade/Education/Export 01-258 1831

(Please note - from 6 May 1990 the 01 Code changes to 071)

CATALOGUE IN COLOUR


- Instruments
- Security
- Supplements
- Components

Ask Henry's first

£1 for callers: large SAE £2 stamp UK by post. Free to Education with Trade Price List

PUT YOUR AGENT ON THE TRAIL

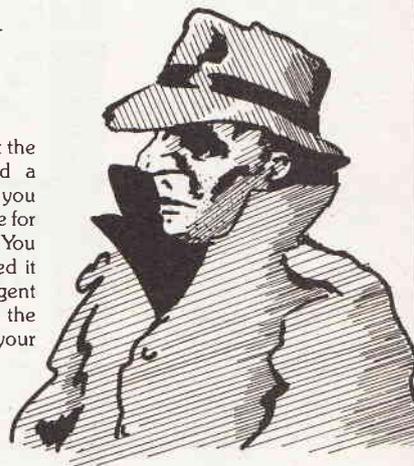You need the facts, just the facts mam. You need a steady source to feed you information. Don't settle for a second-rate squealer. You need ETI and you need it good. Put your newsagent on the trail — clip the coupon and hand it to your neighbourhood shop.



Dear Mr Newsagent
Please order me a copy of ETI and reserve/deliver me a copy every month.



Note this magazine is available to your wholesaler through: SM Distribution, 6 Leigham Court Road, Streatham, London SW16 2PG. Tel: 01-677 8111.

Name _____

Address _____

TK FOR KITS

GUARD DOG KIT




One of the best burglar deterrents is a guard dog and this kit provides the barking without the bite! Can be connected to a doorbell, pressure mat or any other intruder detector and produces random threatening barks. Includes mains supply and horn speaker.

XK125

£21.95

PROGRAMMABLE ELECTRONIC LOCK KIT

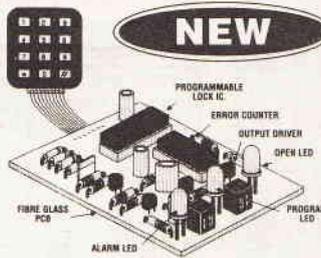


Keys could be a thing of the past with this new high security lock. Secure doors to sheds, garages, even your home or prevent the unauthorised use of computers, burglar alarms or cars. One 4-digit sequence will operate the lock while incorrect entries will sound an alarm. The number of incorrect entries allowed

before the alarm is triggered is selected by you. Further entries will be ignored for a time also set by you. Only the correct sequence will open the lock and switch off the alarm. The sequence may easily be changed by entering a special number and code on the supplied keyboard. Kit includes; keyboard, alarm buzzer, high quality PCB and all electronic components. Supply 5-15V DC. Will drive our Latch Mechanism (701 150 @ £16.50) or relay directly.

XK131

£19.95

SUPER-SENSITIVE MICROBUG

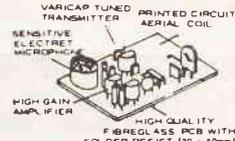

Only 45x25x15mm, including built-in mic. 88-100MHz (standard FM radio). Range approx. 300m depending on terrain. Powered by 9V PP3 (7mA). Ideal for surveillance, baby alarm etc.

£6.35

DISCO LIGHTING KITS



DL8000K 8-way sequencer kit with built-in opto-isolated sound to light input. Only requires a box and control knob to complete ... **£39.95**

DL1000K 4-way chaser features bi-directional sequence and dimming 1kW per channel ... **£23.95**

DLA/1 (for DL & 1000K) Optional op-to input allowing audio 'beat/light response' **95p**

DL3000K 3-channel sound to light kit, zero voltage switching, automatic level control and built-in mic. 1kW per channel **£19.55**

XK139 Unidirectional chaser zero voltage switching and built-in audio input **£12.95**

POWER STROBE KIT

Produces an intense light pulse at a variable frequency of 1 to 15Hz.

Includes high quality PCB, components, connectors, 5Ws strobe tube and assembly instructions. Supply: 240V ac. Size: 80x50x45.

XK124 STROBOSCOPE KIT. £17.25

SIMPLE KITS FOR BEGINNERS

Especially aimed at the beginner. Have fun with your project even after you have built it and also learn a little from building it. These kits include high quality solder resist printed circuit boards, all electronic components (including speaker where used) and full construction instructions with circuit description.



SK1 DOOR CHIME plays a tune when activated by a pushbutton **£4.50**

SK2 WHISTLE SWITCH switches a relay on and off in response to whistle command **£4.50**

SK3 SOUND GENERATOR produces FOUR different sounds, including police/ambulance/fire-engine siren and machine gun **£4.50**

XK118 TEN EXCITING PROJECTS FOR BEGINNERS this kit contains a solderless breadboard, components and a booklet with instructions to enable the absolute novice to build ten fascinating projects including a light operated switch, intercom, burglar alarm and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section component identification and function is included, enabling the beginner to build the circuits with confidence **£17.25**

ELECTRONIC WEIGHING SCALE



Kit contains a single chip microprocessor. PCB, displays and all electronics to produce a digital LED readout of weight in Kgs or Sts/Lbs. A PCB link selects the scale-bathroom/two types of kitchen scales. A low cost digital ruler could also be made.

ES1

£8.25

VOICE RECORD/PLAYBACK KIT


This simple to construct and even simpler to operate kit will record and playback short messages or tunes. It has many uses - seatbelt or light reminder in the car, welcome messages to visitors at home or at work, warning messages in factories and public places. In fact anywhere where a spoken message is announced and which needs to be changed from time to time. Also suitable for toys - why not convert your daughter's £8 doll to an £80 taking doll!!

Size 76 x 60 x 15mm


Message time 1-5 secs normal speed, 2-10 secs slow speed

XK129

£25.95

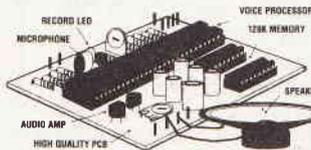

PROPORTIONAL TEMPERATURE CONTROLLER KIT

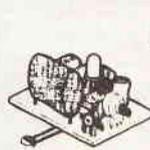

Uses 'burst fire' technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine making, etc.

Maximum load 3kW (240V AC). Temperature range up to 60°C. Size: 7x4x2.5cms. **XK140£8.95**

TK ELECTRONICS

TK ELECTRONICS
13 Boston Road
London W7 3SJ
Tel: 081-579 9794
Fax: 081-566 1916

ORDERING INFORMATION All prices INCLUDE VAT. Free P & P on orders over £60 (UK only), otherwise add £1.15. Overseas Customers divide total order by 1.15 then add P & P: Europe £3.50, elsewhere £10.00. Send cheque/PO/Visa/Access No. with order. Giro No. 529314002. Local Authority and educational institutions orders welcome. Shop Open: Tuesday-Thursday 10 am - 5 pm. Saturday 10 am - 4 pm.




ORDERS: 081-567 8910

24 HOURS

SLIDE PROJECTOR CONTROLLER

PROJECT

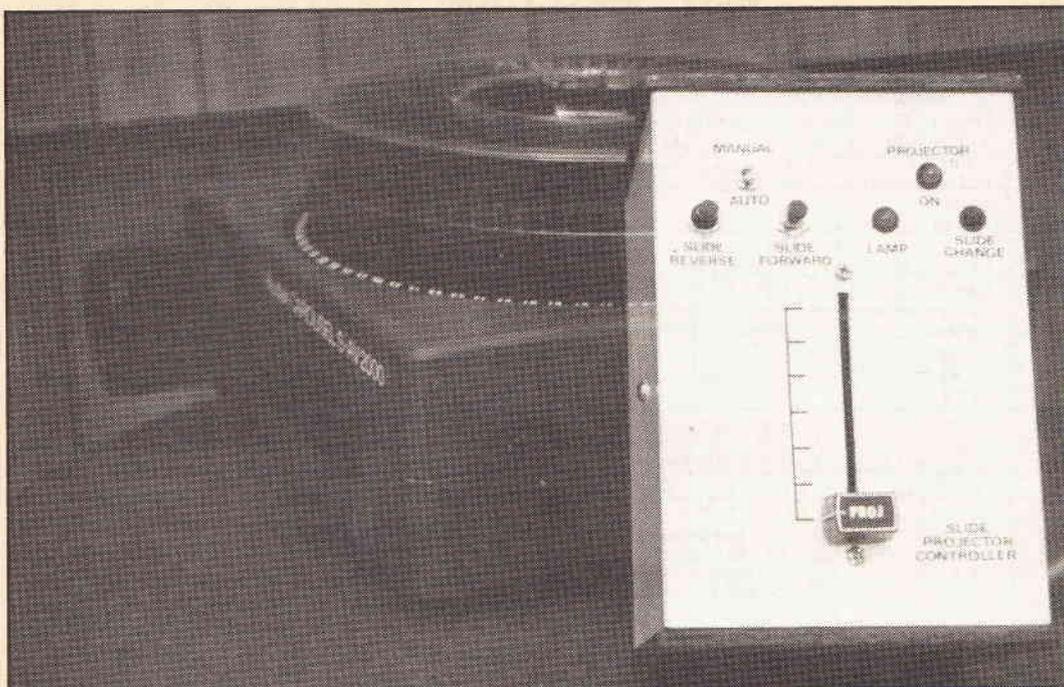

I am just tired of hearing a projector fan whining away whenever I give a talk which needs slides! And I am sure the audience is too. The solution? . . . a small control unit that turns the projector on only when a slide is needed, and changes to the next slide before it switches itself off. As a bonus, it allows each slide to be faded in and faded out for a far smoother presentation. And all this, as they say, with as little inconvenience to the lecturer as possible.

First then, a relatively simple but different phase control circuit which will allow the projector's lamp to be faded in and faded out.

The Dimmer Circuit

Safety has to be a primary feature of this circuit and, as it is controlling mains voltages, it has to be well isolated from them. Secondly, there is a need to control the light output linearly which usually means a highly complex circuit as the light output of a lamp is very far from linear. Another requirement is that it should operate from a single voltage rail and make it simple enough to be built inexpensively from readily available components.

In order to meet some of the above requirements, the circuit was developed around the LM393 dual voltage comparator integrated circuit which is designed to operate from a single voltage rail. Ultimately I came up with the circuit for the dimmer section shown in Figure 1.

Switching The Projector On

It would easily be possible for the lecturer to turn the projector on and then fade the lamp in; but it would be more convenient if starting to move the fader up was, in itself, the way the projector is switched on. This is accomplished by the projector switching circuit shown in Figure 1.

Changing The Slide

Conveniently, the 4538B contains a second and totally independent monostable which can be employed to change the slide before the projector finally switches off. The slide changing circuit can be seen in Figure 1.

The Control Cable: Connecting the projector

Two control cables from the project box to the slide projector are required: One supplies switched mains to the projector and the other, a lightweight 6-core cable (which can be of any reasonable length; 100 yards or more is possible) will control the brightness of the projector's lamp and slide change mechanism. This second cable can terminate at the projector end in a small diecast box which will also accommodate special Kodak twelve-pin plug which fits into the side socket on the Carousel Series projectors. The triac Q5 which controls the lamp's brightness, should, if possible, be mounted inside the projector and bolted to the projector's metal case. This component will get hot when the projector is on and it needs the metal body of the projector as a heat sink.

The connections to the Kodak twelve pin plug and socket are shown in figures 4a and 4b. The 12 pin plug (Kodak Part No. 2 605 4850)

Give that slide show a more professional finish. From the States, David Ponting tells of how its done.

Kodachrome
FILM

comes as a 'lamp-saver' unit. For use in this project, remove the plastic cover and unsolder and discard the shorting connection which joins pins a2 and a3. Cut a 41 by 11mm hole in the lid of the diecast box and mount the 12 pin plug in this hole.

Let me at this point say something about the external triacs. They both carry considerable current. Always use a triac with specifications well beyond the apparent requirements of the circuit. Also bear in mind that the triacs will get hot when the projector is on and their metal tabs must be bolted to heat-sinks. For these reasons I recommend BTA 16 600B triacs, which are 600 volt, 15 amp devices and which have isolated metal tabs making heat-sinking a lot simpler.

In the complete circuit, the timing sequence is shown in Figures 5a and 5b.

Setting Up

I repeat: be careful! The PCB carries mains voltages so extreme care should be exercised when the board is being tested; it must be properly insulated from the box in which it is fitted.

There will be no problem in setting up if you have an oscilloscope and can check the waveforms at the various points; but there will be no major problems if you have not.

Before inserting IC2 and IC3 each into its socket, check that there is a 5 volt supply at pin 3 of IC1, and that there is about 6 volts of (pulsating) DC at the junction of R2 and ZD1. If all is well, set RV3 and RV4 to about halfway, fit IC2 and IC3 into their sockets, plug the projector into its mains socket, join the control

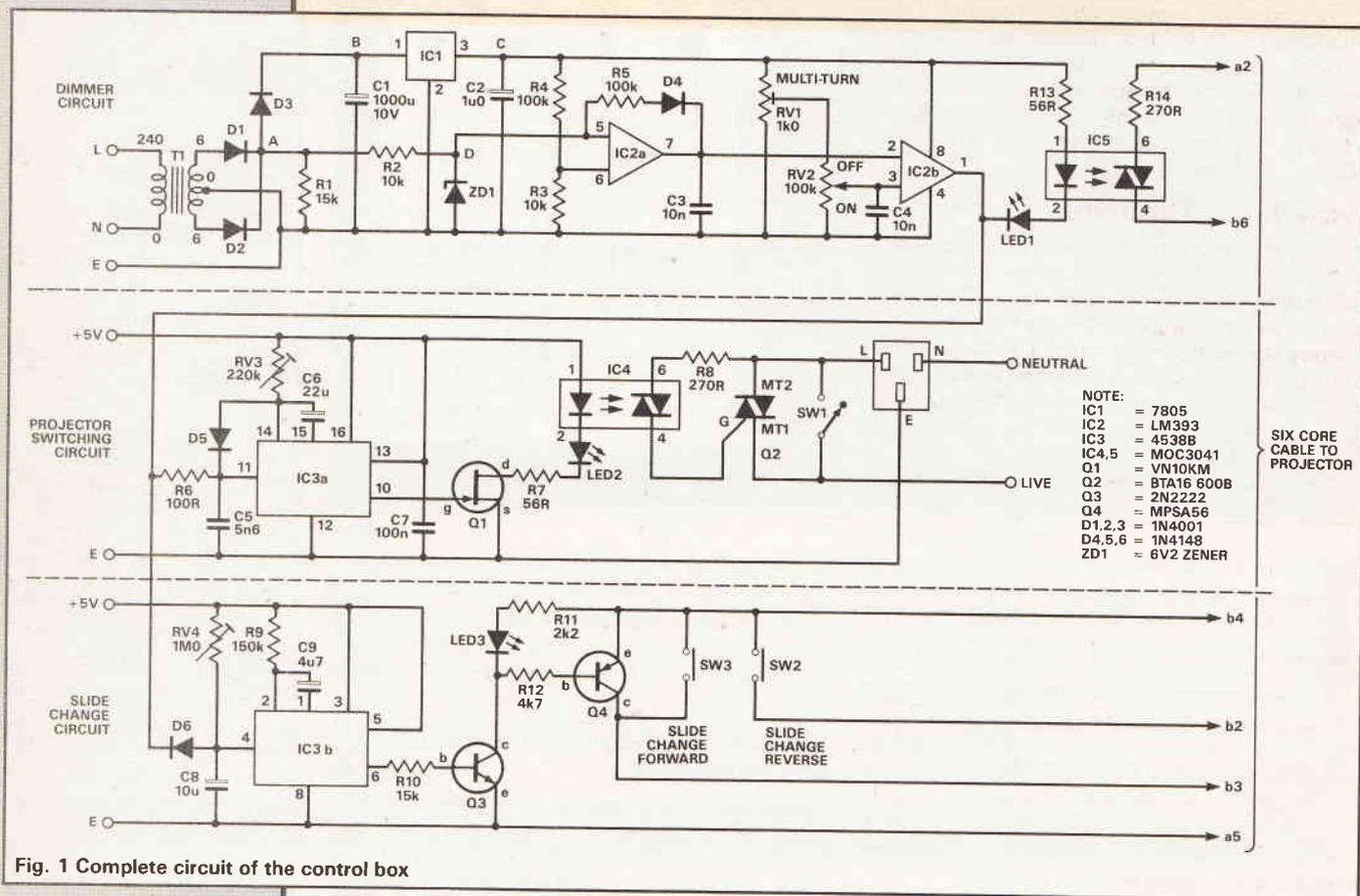



Fig. 1 Complete circuit of the control box

Making The Unit

The whole of this circuit can be built using the printed circuit board outline shown in Figure 6.

Great care should be taken to see that all the polarised components, electrolytic and/or tantalum capacitors, and the diodes are connected the correct way round. The metal tab of the voltage regulator and the triac are shown and these devices should be inserted into the PCB in the way indicated. Make sure that the ICs and the opto-isolators are inserted correctly with pin 1 of each (usually indicated by a dot on the top of the IC) mating with socket pin 1 on the PCB. Incidentally, you probably will not be able to find 6 pin, dual-in-line sockets for the opto-isolators and so carefully cut off two pins at one end of two 8 pin, dual-in-sockets, or, if you prefer, the opto-isolators can be soldered directly into the boards without sockets.

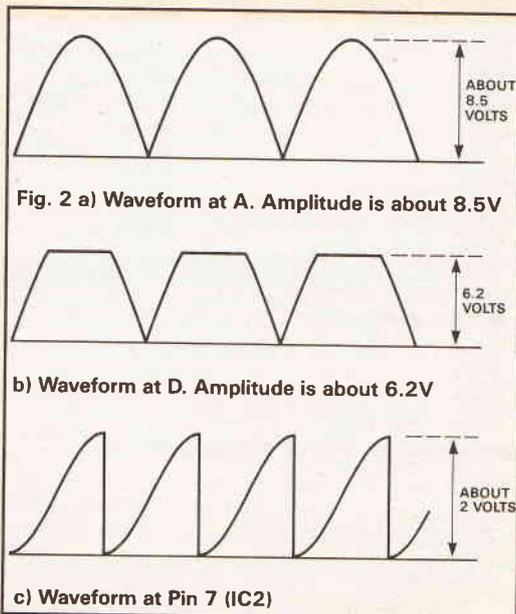There is not a great deal of space to fit all the components, and most of the resistors and diodes will need to be bent into a U shape, inverted and inserted into the board with the component standing vertically.



PROJECT

box to be projector by the 6 core cable, and . . . switch on!

The projector fan may very well start and the lamp be lit, perhaps not fully. Operate RV2 and see if this dims and brightens the lamp. If it allows the lamp to go out completely, the projector should then advance one slide and switch off. Adjust RV3 until the whole slide advancing process is over before the projector switches off. Now leave RV2 in a position so that the lamp is just glowing. Adjust RV1 to brighten the lamp and move P2 until the lamp just glows again. Repeat the process until RV2 is at the 'out' end of its travel, with the lamp just glowing. Now adjust RV1 to fade the lamp out completely, at which time the slide should change and then the projector switch off. This is quite a critical adjustment and so RV1 is a multi-turn potentiometer allowing very fine control. If this potentiometer is set too critically, switching on electrical appliances close to the control unit might trigger the projector on and change a slide. If this happens, back RV1 off a little when the only loss will be that the projector will not switch on at the very bottom of RV2's travel.

Some Final Thoughts

Concern was expressed to me that the projector would not have a chance to cool down if switched on and off in the manner described above. This is not true. In tests on a number of different projectors, no excessive temperature was reached. If the projector is on for a long period, the temperature stabilises after about 4 minutes. If the projector is used intermittently for short periods, it never gets hot enough to reach even this stabilised temperature.

Provided the time period is adequate between

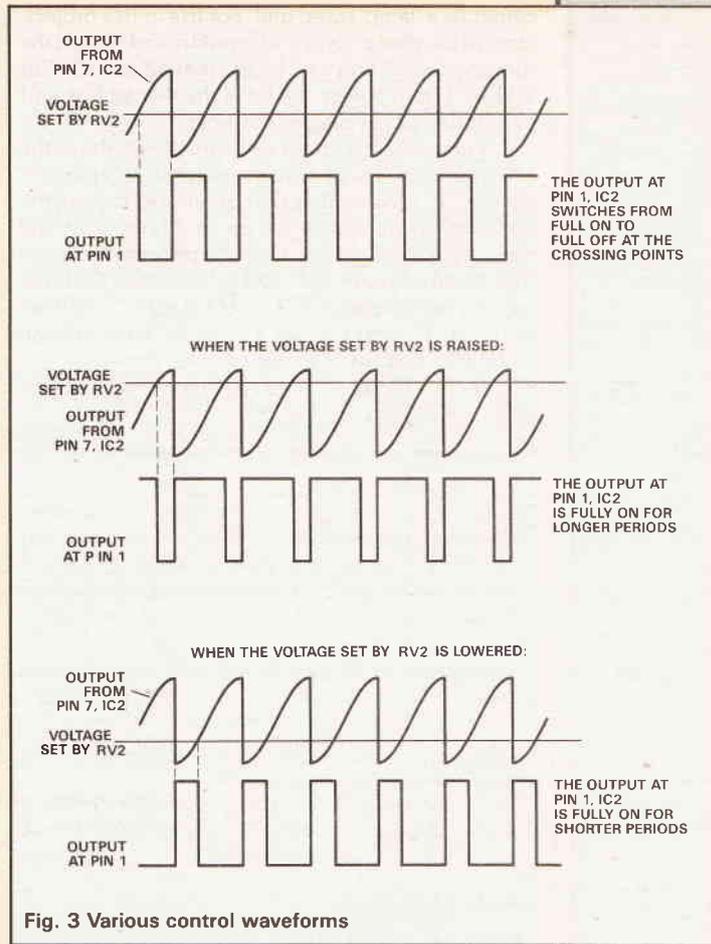


Fig. 3 Various control waveforms

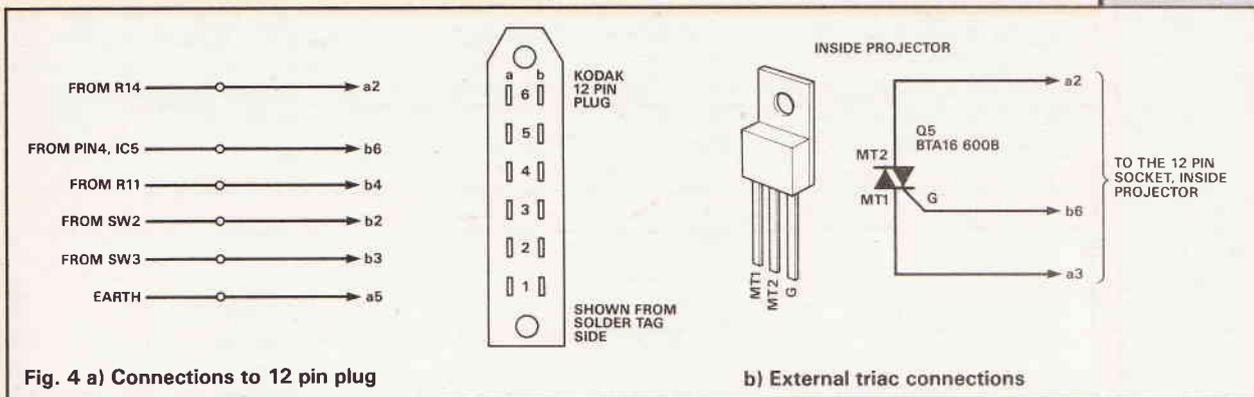


Fig. 4 a) Connections to 12 pin plug

b) External triac connections

the end of time period T2 and the end of time period T1 in the timing sequence (this can be adjusted by RV3), consecutive slides can be shown without the projector turning off after each. If the projector is still running when fader RV2 is opened again, it will continue running without a break and maintain the correct sequence of events.

Although this circuit has been designed with the Kodak Carousel slide projectors in mind, almost any projector can be controlled with this unit. Even a projector using a mains voltage lamp can be dimmed in and out with no change in the component values of the circuit shown above.

Some slide projectors use different ways of changing slides from the Carousels' and another way to forward-change the slide would be to drive a relay directly from the 5 volt supply and the collector of Q3. If you use this method, immediately parallel with the relay's coil, a 1N4002 diode should be connected with its positive end to the 5 volt rail. This will damp potentially harmful transients each time the relay is switched off.

Good viewing!

HOW IT WORKS

DIMMER CIRCUIT

The output from the transformer is half-wave rectified by diodes, D1 and D2; R1 is there just to make certain that enough current flows to switch the diodes fully on (Figure 2a).

D3 isolates point A from the smoothed DC so that the voltage at B should be about 8 volts of pure DC. The IC 7805 ensures that the output at C is a well regulated 5 volts with C2 smoothing out any feedback noise.

R2 and ZD1 regulate the pulsating DC supply and, as far as possible, make this independent of varying mains voltages (Figure 2b).

This waveform appears at pin 5 of the IC LM393, which has an 'open collector' output. This means that until the moment when the inputs at pins 5 and 6 are the same, the output of the IC is effectively an open switch. So, initially, the capacitor C3 is charged by the waveform from point D, via R5 and D4. Clearly this is a very non-linear charging current but it does produce an almost ideal output waveform at pin 7 of IC2. The voltage divider R4/R3 ensures that the input at pin 6 is held just above zero volts. When the pulsating DC at pin 5 returns almost to zero at the end of each half cycle, the inputs to IC2a become equal and the internal transistor at the output of the IC

switches on, discharging C3 each time (Figure 2c).

The vertical sections of this waveform are caused by the output transistor switching on and discharging capacitor C3. The curved sections have this almost ideal shape, which allows the lamp to hurry to start lighting without wasting the low end of the main fader RV2, and to hurry towards full brightness at the high end, while being acceptably linear in the middle. RV1 and RV2 form two other voltage dividers: adjusting RV1 ensures that the lamp is fully off at one end of the main fader RV2. So the two inputs (pins 3 and 2) of the second section of IC LM393 are, respectively, a set voltage which can be varied from about 2 volts to 0 volts by RV2, and a 'sawtooth' voltage of the same amplitude. With RV2 set at halfway, the superimposed inputs are shown in Figure 5.

When the voltage set by RV2 rises just above the sawtooth, the pulses disappear and the output at pin 1 is always high. Conversely, when the voltage set by RV2 is below the sawtooth, the pulses again disappear, but this time leave the output continuously low.

So when the output of IC2 at pin 1 is zero, both LED1 (which is there to give an indication of how bright the lamp is) and the LED inside IC6, the opto-coupler MOC3041, will always be lit. The triac inside the opto-coupler will be fully on, turning the external triac fully on. As RV2 is moved along its travel, pulses synchronised with the 50Hz mains start, and so both LEDs will briefly be switched off each cycle, as will the triacs. The lamp will not now be supplied with the full voltage all the time: it will be dimmed progressively as RV2 is moved towards its other end. IC4 is a bypass capacitor which prevents any noise that might be picked up on the leads from the main fader, RV2, from entering pin 3 of IC2. It should be placed as close as possible to pin 3).

All the above assumes that the mains supply to the projector is on but, at the beginning of the process, the projector is off, waiting for the time when the first slide is needed.

PROJECTOR SWITCHING

The 4538B is a CMOS dual monostable. This IC contains two independent timers each of which, when triggered by an incoming pulse, outputs a pulse timed by the charging of a capacitor through a resistor.

If we now assume that our projector is off, and that the lamp fader RV2 is in the off position, the output from pin 1 of IC2 is high. However, as soon as the fader is moved up, a series of initially thin

pulses will start, the first of which is used to trigger the monostable IC2A. When triggered, the output at pin 10 of IC3a will go high, switching on the VMOSFET VN10KM, and hence the LED in the opto-coupler, IC4. That will turn on both the internal and external triacs as before and power will be supplied to the projector.

At this stage we do not want the timer to time out and switch the projector off until the projection lamp has been faded right up, watched the first slide, the lamp has been faded out, and the slide-change mechanism has advanced to the next slide. So early timing out is prevented in the above circuit simply by adding the diode D5. The first pulse comes in, triggers the start of the output pulse, and capacitor C6 starts to charge through tripot RV3. But each succeeding incoming pulse short circuits C6 via D5 and so discharges it.

Further, when the lamp is fully on, pin 11 of IC2 is low and so the capacitor will not charge at all. C6 will only be allowed to charge fully when RV2 has returned to its fully faded out position and all the incoming pulses have ceased. Only now can the timed output pulse really begin. Provided this pulse length is long enough to allow a third part of the circuit to change the slide (and this time interval can be adjusted by varying RV3), our purpose is achieved.

SLIDE CHANGE CIRCUIT

Initially with the projector off, the output of the 4538B at pin 6 is low, while the input at diode D6 is high. C8 is fully charged via RV4. When the first negative going pulse from pin 1 of IC2 arrives via D6 at pin 4 of the 4538B, C8 immediately discharges through D6. Further pulses keep C8 discharged. As monostable IC3B is configured so that it will only trigger on a rising input, the output at pin 6 remains low and will not be triggered to a high state until C8 is again allowed to recharge fully. This will not occur until the projector lamp fader has been brought back to its fully faded out position. Only now will C8 recharge via RV4 and, as its potential rises through the input threshold of the 4538B, the output pulse start. The slight delay before the output goes high allows the projector lamp to be completely out so that the slide change will not be seen. By using a transistor Q3 to further switch Q4, the "slide forward" connections in the projector can be made without using a relay, and the slide-change mechanism will advance the slide tray by one. LED3 will light briefly to indicate the slide changing.


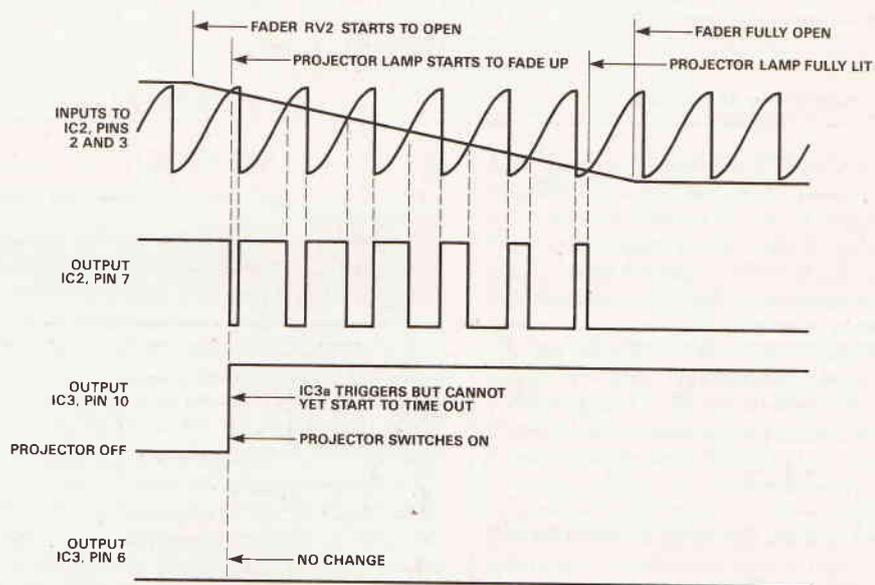


Fig. 5 a) Timing for switching the projector on and fading the lamp up

PROJECT

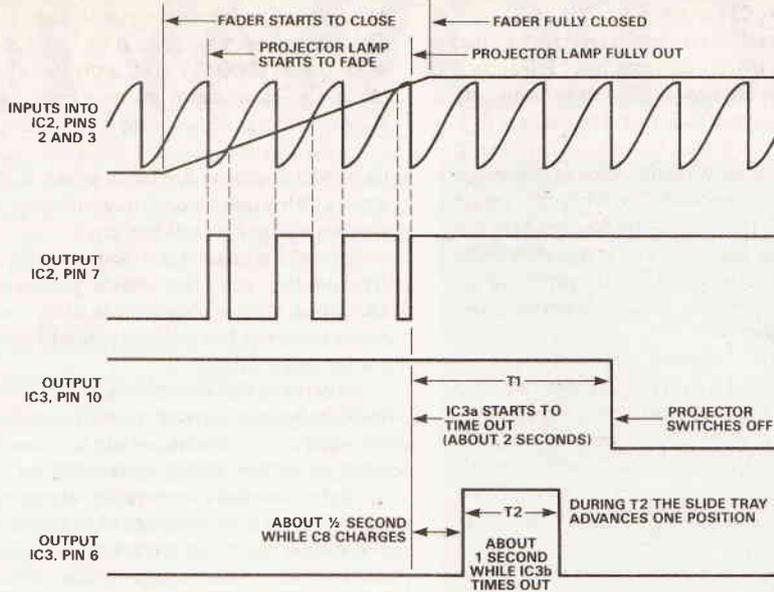

b) Timing for fading the lamp out, changing the slide and switching the projector off

PARTS LIST

RESISTORS (all 1/2 watt or larger)

R1	15k
R2,3	10k
R4,5	100k
R6	100
R7,13	56
R8,14	270
R9	150k
R10	15k
R11	2k2
R12	4k7
RV1	1k multi-turn trim
RV2	100k linear slide pot
RV3	220k trimpot
RV4	1M trimpot

CAPACITORS

C1	1000 μ 10v electrolytic
C2	1 μ 50v elect/tant
C3,7	100n min polyester
C4	10n min polyester
C5	5n6 min polyester
C6	22 μ 10v elect/tant
C8	10 μ 16v elect/tant
C9	4 μ 7 16v elect/tant

SEMICONDUCTORS

D1,2,3	1N4001 (50 piv, 1A7)
D4,5,6	1N4148 (any silicon)

LED1,LED2,LED3	T1 1/4, yellow, green, red
ZD1	6.2v, 0.4watt zener
IC1	7805 volt reg
IC2	LM393 comparator
IC3	4538B (MC14538B) CMOS
IC4,IC5	MOC3041 opto-isolators
Q1	VN10KM (any N power-MOSFET)
Q2,Q5	BTA 16 600B triacs

MISCELLANEOUS

TR1	6-0-6v transformer 0.1A min
SW1	240v, 3A lever switch
SW2,SW3	push-to-make momentary
IC sockets	one, 16 pin DIL two, 8 pin DIL (see text)
6 pin plug	
6 pin socket	
12 pin plug, A12 DIN 41822, Kodak Part No. 2 605 4850.	
LED chassis holders	
3 mains plug and lead	
6 core cable (length as required)	
Knob for slide potentiometer	
Suitable box for control unit	
Suitable box to accommodate the 12 pin plug.	

BUYLINES

There should be no difficulty over the supply of any of the above components. Maplin can supply the BTA 16-600B triacs (Order No. UK55K) and many of the other components.

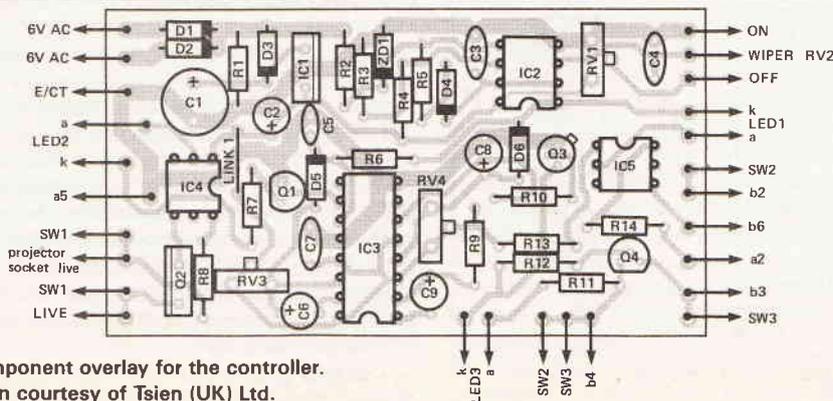


Fig. 6 Component overlay for the controller.
PCB design courtesy of Tsien (UK) Ltd.

1

MICROWAVES

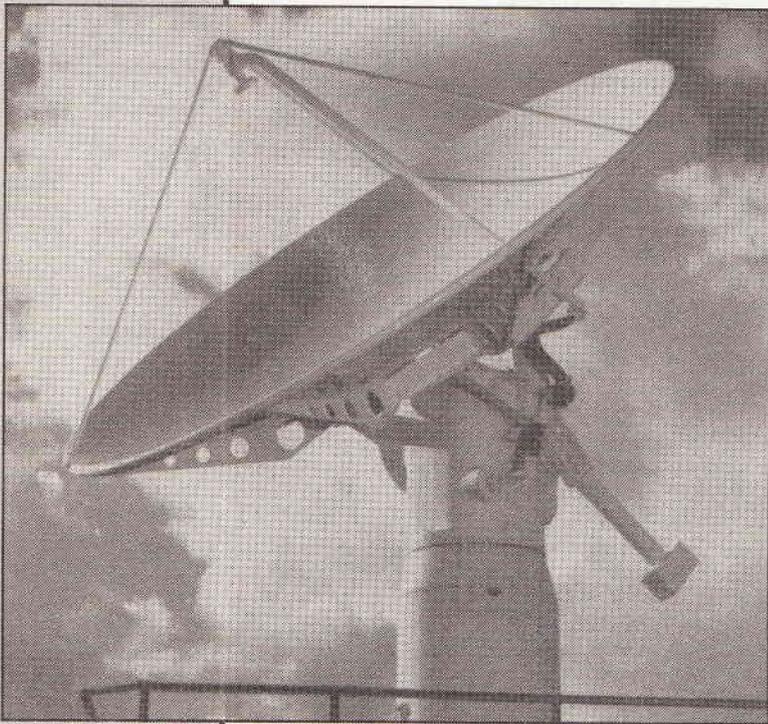


Fig. 2 Satellite Newtonian reflector antenna

Thank you Rupert Murdoch!" Why? ... Because whilst he is losing £200,000 a day on his satellite TV concept, the layperson is not under the misapprehension that microwaves are only useful for cooking the veg! So how can something which casseroles the greens in a tenth of the time of a conventional cooker, be used to beam entertainment from 23,000 miles out in space down to your own haunted fish-tank called a TV.

This article, together with next month's, endeavours to answer this question, as well as to describe the many other applications of microwave technology in use today. It concludes with a prediction of where the microwave industry is heading as we go forward into the 1990s.

So What Are Microwaves, And Why Are They So Useful?

Microwaves lie in the region of the electromagnetic spectrum from 1GHz (10⁹Hz) to 300GHz (3 × 10¹¹Hz). As such, they possess all the properties one expects from electromagnetic waves. They are

reflected and refracted at boundaries. They can also propagate through a vacuum, and they also travel at the speed of light (3 × 10⁸m/s).

Figure 1 shows the complete EM spectrum. (Well, nearly! ... Not much propagates below 100kHz and although some cosmic rays exist beyond gamma-rays, we have yet to succeed in harnessing them for applications).

Note how the microwave band is sandwiched conveniently between two exceedingly useful parts of the spectrum — radio waves and light waves. Therein lies the importance of this region. Microwaves behave as a hybrid of light and radio waves, possessing attributes from both regions. Microwave circuits can for instance, be constructed in a broadly similar manner to radio frequency circuits, although more care must be taken in the design and construction at these higher frequencies. A microwave oscillator may produce a signal which can be modulated with information using AM or FM techniques in the usual manner. However, it can then be transmitted from an antenna which bears a remarkable resemblance to an optical telescope (See Figure 2). Such an antenna can produce a very narrow concentrated beam of energy — an attribute normally associated with light rays by the use of lenses and/or mirrors.

If one considers the radio region of the spectrum in terms of information content, an important trend becomes apparent as the frequency increases. At the low end of the region lie the long wave and medium wave stations — poor quality, hissy, narrow audio bandwidth, monaural reception. Moving up into the VHF region, we then have the capability of low noise, Hi-Fi, stereo reception. At the top of the VHF band black and white TV used to be transmitted on 405 line resolution. To obtain good quality colour TV on 625 line (and by quality here, I refer to quality of the received signal, not program content!) a further increase in frequency is required, taking us now into the UHF region.

Beyond UHF lies the microwave region. We tend not to stop thinking in terms of information quality, but consider quantity of information. We talk in terms of the capability of so many thousand simultaneous telephone conversations on the microwave link, or so many TV channels. Our hero, Rupert, for instance, has the theoretical capability of approximately 150 simultaneous broadcast channels (perish the thought!) He has, in fact, opted for 16 channels using a slightly different frequency for each. This is a reflection of the limitation of the cheap mass-produced receiving equipment, rather than the maximum theoretical channel capacity available.

Let us now consider the effects of diffraction as the frequency is increased. At low frequencies there is no problem picking up radio signals under the shadow of hills and buildings. As the frequency is increased, however, the signal follows a more direct route, skimming over hills with little diffraction. Ultimately, light rays follow a near perfect straight line with diffraction effects only detectable under very special circumstances. Microwaves also follow straight lines with negligible diffraction over hills, buildings, or even the earth's horizon. Microwave communication through free space must, therefore, follow what is known as 'line-of-sight'.

A final property of microwave which may be gleaned from the spectrum of Figure 1 is that of

From cooking to television, microwaves are fast becoming an important part of our lives. Colin White looks at the past, the present and the future of the technology.

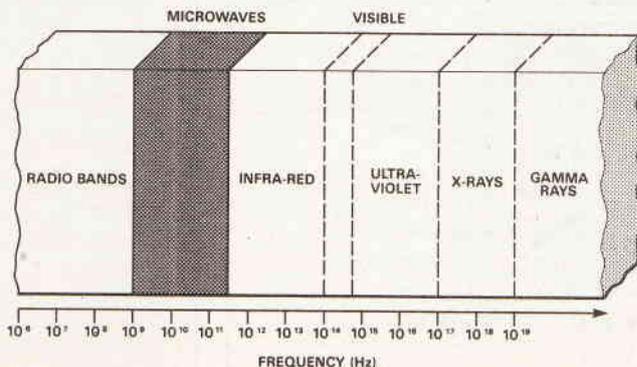


Fig. 1 The electromagnetic spectrum

absorption by, and consequential heating of non-metallic substances by EM radiation (broiling the chicken!) Efficiency of absorption improves as the frequency reduces. Unfortunately RF ovens at frequencies below the microwave region would be too large to be accommodated in the average kitchen.

Having dealt with the properties and attributes of microwave radiation, we are now in a position to consider actual microwave applications. By way of an introduction, and to put things in perspective, I will commence with a short history of microwave technology.

Historical Landmarks In Microwave Technology

The story begins just over a century ago when Hertz proposed the concept of radio propagation and Maxwell first succeeded in generating radio transmissions using spark generators. These produced RF power over a very broad spectrum, including the microwave region. They were of course, unaware of their emission frequencies. They contributed enormously to the theory of RF propagation around this era.

In 1894 Sir Oliver Lodge surrounded a spark generator with a metal tube and noted that this succeeded in guiding the signal into a specific direction. This was in fact, the first waveguide, a component much used to this day.

The 1920s saw much theoretical analysis of the concept of microwave propagation and the advantages of this part of the spectrum were beginning to be appreciated. In particular, George Southworth (of Bell Telephone Laboratories) and Sir Robert Watson-Watt considered applications in communications and Radar, respectively. The first purpose built microwave oscillators were developed during the 30s and more especially, the early 40s. These were obviously thermionic devices although their operation principle was totally different from low frequency valves.

A device known as a magnetron has had a particularly interesting history. It was the first microwave oscillating valve to be developed. It was the most widely used device during the war years, generating high power microwave pulses for radar applications but became obsolete during the early to mid-50s, only to be reborn during the mid-60s as the sole purpose of powering microwave ovens. As such, more magnetrons are presently manufactured than all other microwave oscillators put together.

The war years produced perhaps the greatest number of technological advances in the microwave region, including wide band high power amplifiers (travelling wave tubes) and a variety of new oscillators such as backward-wave oscillators, the klystron, invented by the Varian brothers in 1935 was perfected and became popular during this period. Radar and microwave communication systems were designed, manufactured and successfully implemented supporting the war effort. On the other hand much research went into developing a microwave 'death-ray' at this time. The necessary technology eludes us to this day, much to Mr Reagan's and Mr Bush's dismay.

In 1956 the first non-reciprocal device, the gyrator, was invented by C. Lester Hogan. The gyrator is a two-port device which allows a signal to pass through in one direction with some phase shift θ , but when the signal is sent through the device in the other direction, there is a phase shift of $\theta + 180^\circ$. Although now obsolete, it marked the beginning of a family of non-reciprocal devices which have many applications in switching, protecting, modulating and controlling microwave signals.

Satellite communications were 'launched' in

1962 when Telstar was placed in low earth orbit. The first geostationary satellite Early Bird was launched some three years later. However, the theory of geostationary satellite communication was conceived in 1945 when Arthur C. Clarke (2001 fame) wrote a most prophetic article on the subject, in the journal *Wireless World*, of that year.

Another major advance of the 60s was the development of microwave semiconductor devices, used to replace thermionic valves in some applications. The first such device was the Gunn diode discovered, so it is said, by accident, by J. B. Gunn. This was followed by junction diodes and transit time diodes, which today can produce oscillations beyond 200GHz.

The 70s brought the first microwave transistors, initially bipolar, then MES-FET (Metal Epitaxial Semiconductor Field Effect Transistor) types. Current MESFETS can produce appreciable powers, even at 20GHz. Finally, bringing us up to date, the 80s have seen the development of Microwave Monolithic Integrated Circuits (MMICs); several MESFETS, together with their supporting passive components on a substrate 0.5mm square producing a complete system on a chip.

Microwave Ovens

This is the most popular application of the science by far, with over 15 million ovens installed in the United States to date. The history of these appliances began in 1945, when a manufacturer of magnetrons discovered, supposedly by chance, that microwaves are capable of producing heating effects.

The phenomenon occurs as a consequence of the vibration of atoms within the water molecules of the food, causing frictional warming of the produce. The key to the importance of microwave heating is the fact that the radiation penetrates more deeply than other forms of cooking. When using hot-air, for instance (ie a conventional domestic oven), the heat is generated outside the object and conveyed to the food by conduction and convection. The surface of the object is therefore heated indirectly, and heat then flows towards the inside by conduction only. Infra-red heaters, very popular among the fast-food emporiums, produce heat directly on the surface of the food. The surrounding air is then warmed by convection while the food is heated by conduction

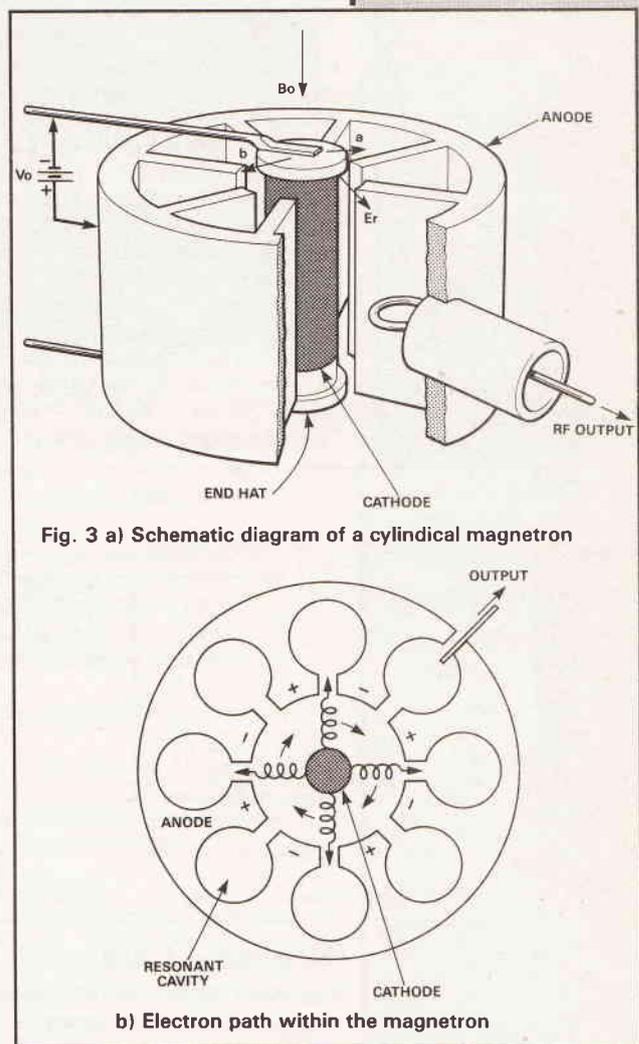


Fig. 3 a) Schematic diagram of a cylindrical magnetron

b) Electron path within the magnetron

from the surface. Microwave heating, however, occurs within the food, and is therefore more energy efficient than the other methods.

Referring to Figure 3, the method of operation of a microwave oven is as follows. A magnetron operating at 2.45GHz generates microwave power at a few kilowatts. A length of waveguide connects the output the magnetron to the main chamber of the oven which acts as a resonant cavity. This means its size is such that it exactly supports the electric and magnetic wavelength inside the cooking volume. This ensures efficient radiation of the food rather than the energy attempting to creep out of the door seals, or back up the magnetron's own output. The mode stirrer, a sort of microwave fan, distributes the energy within the cavity and ensures homogeneous heating.

So what is so special about the choice of 2.45GHz? Not much! Heating efficiency is dependent on radiation at the various resonant frequencies of the molecules, atoms, neutrons, electrons etc, which make up the food substance. In practice it is the resonances within the water molecules which are paramount. These are many and various, particularly within the 1.5GHz to 3.5GHz band.

The choice of 2.45GHz reflects an agreement between the communication channel users, principally military, to minimise communication interference. The implications are that, if your domestic microwave oven radiates into the atmosphere, and if this frequency is detected by the local army base, they will say "Ah-ha, 2.45GHz! — That's no enemy . . . That's the sprouts being cooked."

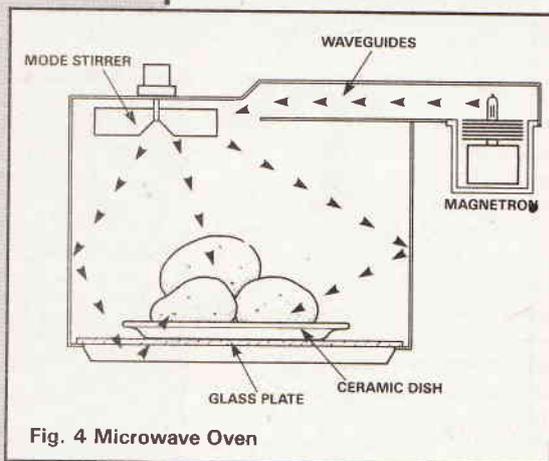


Fig. 4 Microwave Oven

The subject of microwave oven safety is a complex one, and although statistically the chances of permanent health risk from these appliances are minimal, work is still being carried out in an attempt to quantify the dangers.

Microwave Communications

Microwaves are also used extensively in communications either between two ground stations or between satellite and ground station. The advantages of communication at these frequencies are two-fold. Firstly, because antennae at these frequencies are so directional (they send out a narrow pin-point of radiation), a more efficient link can be set up, since much of the energy leaving the transmitting antenna actually arrives at the receiving antenna with minimal spillover. Little diffraction occurs at these frequencies so line-of-sight communication is essential. For military secure communications this is an advantage, since if an enemy attempted to intercept the information, not only would a drop in power be detected at the receiver, but the foe would find it quite difficult to eavesdrop without being seen. Of course, cover of darkness affords little protection, as the modern day soldier is equipped with infra-red night-sight.

The second advantage of using microwave frequencies lies in the broad-bandwidth capabilities. Most microwave links are digitally modulated on either AM or FM (or both) using some form of multiplexing techniques. A typical link would have the capacity of

300 telephone channels, 10 colour TV channels, a few high quality audio channels, facsimile channels and several computer data links; all these transmitted at one carrier frequency.

Microwave propagation over the horizon is not feasible due to negligible diffraction effects, so long distance communications are only possible using cable, repeaters or more importantly, geostationary satellites as a mirror for the communication channel around the earth. A geostationary satellite is one which rotates around the earth above the equator, once every 24 hours, therefore appearing stationary above a fixed point on the equator. The geostationary orbit is 35,800 kilometers above the surface of the earth. At this distance, the gravitational force pulling the satellite towards the centre of the earth is exactly matched by the centripetal force due to the rotation of the satellite attempting to pull it away and out into space. What is more, the velocity of rotation of the satellite exactly matches the velocity of rotation of the earth. The satellite therefore remains in that orbit and above a fixed point on the equatorial line.

The use of a stationary orbit presents very significant advantages for communications:

a) The antenna of the ground station points towards a fixed location in the sky, only small corrections being required to compensate for varying atmospheric diffraction.

b) Since there is no relative movement between transmitter and receiver, Doppler shift of the frequency is non-existent. This can cause major problems with motional satellites.

c) Since the satellite lies well beyond the earth's atmosphere, it is not slowed down by friction due to air molecules. The satellite could remain in orbit for more than a million years theoretically. Its operation is however, limited in time by the fuel required for stabilisation.

On the other hand, the stationary orbit also presents some drawbacks:


a) The time taken for a signal to travel from ground station to ground station, via a geostationary satellite, is twice the geostationary orbit height divided by the velocity of light. This amounts to approximately half a second delay and may be potentially inconvenient.

b) The large distances involved attenuate the signal levels considerably. The signal received from our Rupert's Astra at the first amplifier mounted on the Sky dish is about 1×10^{-13} watt. Only a few years ago it would have been a major research activity to amplify such low levels; today the equipment can be found in the high street stores at 'knock-down' prices — such is progress.

The geostationary orbit is now so densely populated with satellites carrying military, domestic, business, and educational information that the current satellite density of one satellite every 3° of arc is being increased to one satellite every 2° of arc.

A technology closely related to satellite communications is that of space communications to and from deep space probes. Communication is obviously over much larger distances so time delays are longer; 1.28 seconds for a message to the moon, 43 minutes for a message to the Voyager 1 and 2 spacecraft as they orbit Jupiter — still beats first class mail though! The received signal levels are minute, consequently extremely specialised receiving equipment is required.

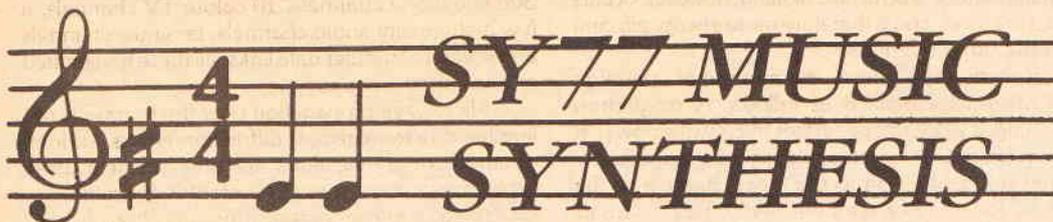Next month, we'll see how microwave technology is applied to the fields of medicine, navigation, target detection and space photography.



SY77 MUSIC SYNTHESIS



The LSI Architecture of SY77

Having looked at the development of RCM and what it actually means, the next step is to dig deeper to the hardware level, before discussing the different operating system modes used by the musician as the final part of this article. The block diagram shown in Figure 7, illustrates the connection of the SY77 system components. The custom Yamaha LSIs shown in the diagram and their function is discussed as follows.

The M3 chip (YM7119)

The M3 is synonymous with the AWMii portion of the tone generator. It is a 16 channel waveform-processing LSI developed in 1988-89. It features a fixed sampling rate using 6th Lagrange Interpolation and time varying Low Pass and High Pass Filters. (LPF/HPF). The LSI reads wave data sampled at 32 or 48kHz in 16 bit format and includes the following key features:

- (1) A 5-segment Amplitude Envelope Generator (AEG).
- (2) Pan Control.
- (3) A Resonant Filter which can be configured as 24, 18, 12, 6 dB/Oct in Low-Pass/High-Pass/Band-Pass modes.
- (4) Wide Cutoff Frequency (10Hz-24kHz for LPF and 10Hz-12kHz for HPF at 48kHz sampling frequency).
- (5) No Microprocessor wait-time allowing continuous data writing and thus user realtime control.
- (6) D/A Converters are Yamaha AFDO and Burr/Brown PCM56 for Individual Outputs.

The OPS3 chip (YM7107)

OPS3 is the heart of the AFM sound generation system. It takes voice data from the CPU into its internal register and receives additional pitch and envelope information from the EGM2 chip. Pitch data from EGM2 and Pitch Bend wheel are converted into Hertz and then into phase data in the phase accumulator and output to the oscillator. OPS3 and EGM2 work together since OPS3 does not implement its

own envelope generator as in M3. OPS3 has the following key features:

- [1] Ability to read a sample as a Carrier/Modulator
- [2] 16 Sine Wave variations available as waveforms for conventional FM
- [3] Operator Fixed Frequency to 0.00Hz
- [4] Operator Phase Control
- [5] 45 Preset Algorithms (and Open Algorithm via MIDI)
- [6] 3 User-definable Feedback Loops per Operator
- [7] 2 LFOs (a main and sub LFO for each FM voice)
- [8] Individual Operator sensitivity to Pitch Envelope Generation

The EGM2 chip (YM7103)

Developed in 1988, this LSI creates envelope and pitch information (eg. pitch envelope and portamento) which is sent to the AFM sound generation chip OPS3 (YM7107). EGM2 permits envelope looping around any one of 4 envelope segments for each operator.

The PAN LSI (YM7102)

The Yamaha PAN chip is designed to integrate with the OPS3 signal channels individually, allowing 16 PAN registers. The PAN chip contains a 6-segment fully user programmable internal Envelope Generator with repeat and delay capabilities which can be controlled for each channel individually. This enables all 16 Voices in a Multi setup to have a completely unique stereo trajectory if required allowing complex spatial movement during the evolution of sounds. SY77 contains 64 Preset panning movements which can easily be applied to any sound that is created. Since an SY77 sound (called a 'Voice') can consist of a number of sound elements, each element can have an independent pan movement.

The LDSP chip (YM3413)

LDSP is responsible for the reverb, delay tone and distortion type of effects in SY77. SY77 implements two LDSPs, one for each stereo output.



Mike Barnes continues his look at the workings of the latest Yamaha synthesizer.

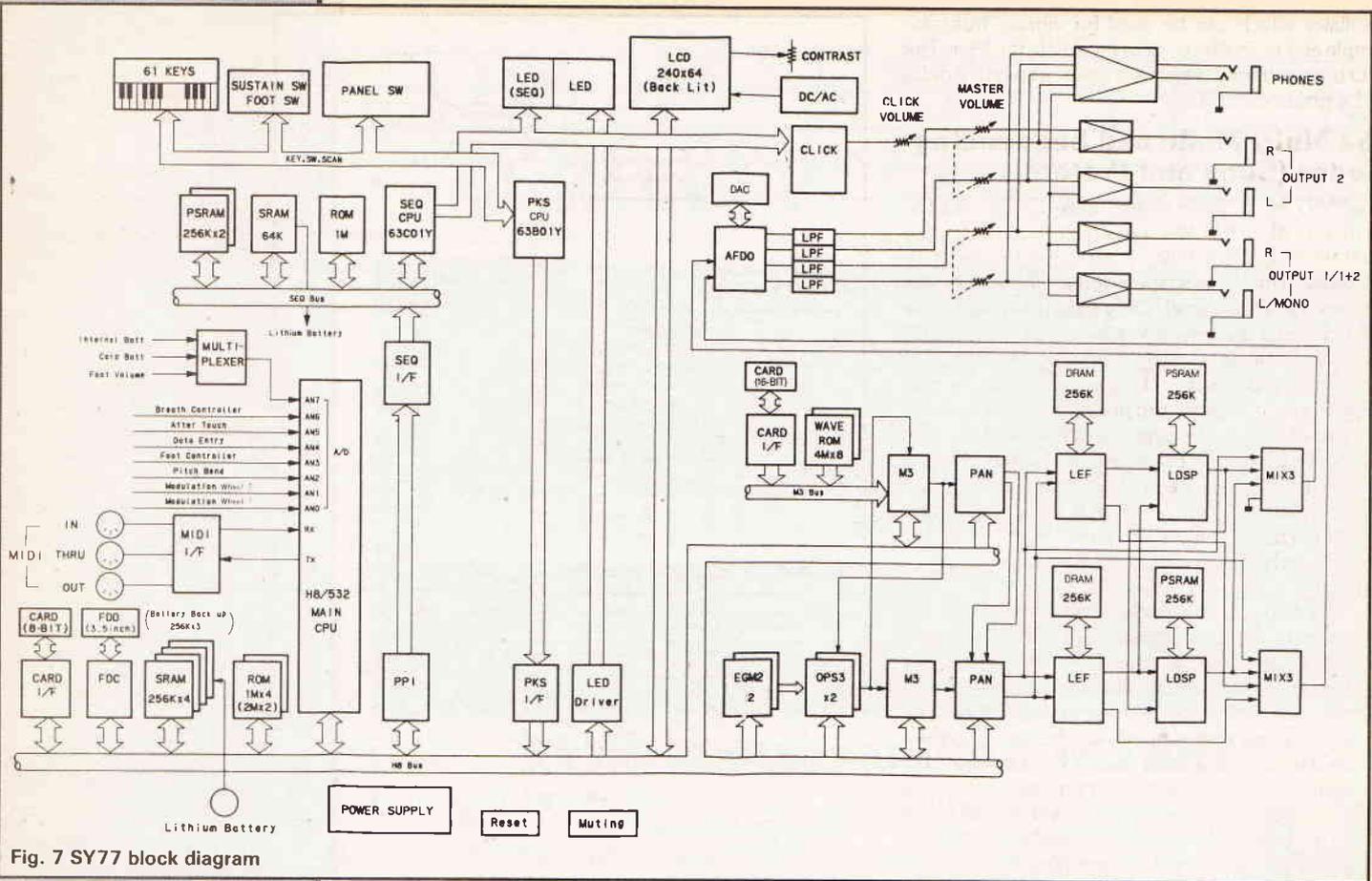


Fig. 7 SY77 block diagram

The LEF chip (YM3415)

LEF is responsible for the modulation effects of SY77 including flange, stereo chorus and symphonic. Again there are two units, one for each stereo output.

The Functional Architecture Of SY77

On top of all the hardware discussed earlier sits the operating system which divides SY77 into five fundamental modes of operation. These are represented to the user as 5 switches on the top-left of the instrument front panel. Each mode is for a specific musical activity. Voice Mode is the most common mode used for simply playing or editing sounds. Multi mode is used to arrange and mix a group of up to 16 sounds/instruments to be played by the sequencer. Song Mode gives access to all the recording and editing functions of the sequencer which is analogous to a 16-track tape machine, and is where all the musical parts are arranged. Pattern mode is really a specialised part of Song Mode where a repeating pattern of music can be made (for example, an 8-bar chorus) and then inserted at all the Chorus points during the song. Utility mode contains all the specialised functions for setting up SY77 to communicate via MIDI and store its internal data to external media.

The Voice Mode Of SY77

On SY77, a Voice is the label used to define all types of sound groupings including single sounds (eg. a solo piano), layered sounds and keyboard split sounds (eg. where a number of sounds occupy predetermined positions on the same keyboard). The Voice is the highest level of sound organisation in the instrument. A Voice consists of parameter settings for one, two or four AFM or AWM 'Elements' (Element Data). These

elements are themselves sub-sounds which can be combined in 11 master configurations:

The AWM Element block structure is shown below:

The waveform block defines which of the 112 preset sampled waveforms to playback, and sets its pitch and fine tuning. The output is fed to the filter block which modifies the tone using a pair of digital

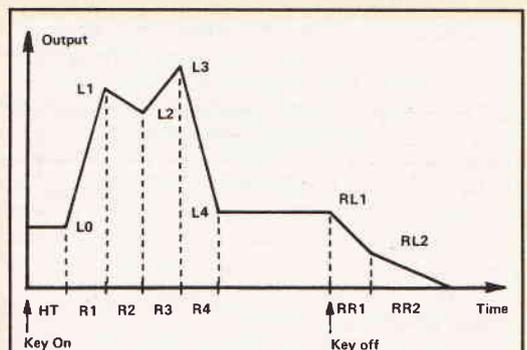


Fig. 8 Typical envelope showing different adjustable rates and levels

filters. These filters can each be configured to both be LPF in which case acting as one 24dB/octave filter or one LPF and one HPF acting as 12dB/octave filters. If the filters are not required, they can be set to THRU position where they have no effect. There is also a resonance control for the filter pair which is the first digital resonance that actually works! (Since each element can use two filters, a 4-element voice can use 8 digital filters simultaneously!) From the filter block, the signal is passed to the Amplifier block and then to the Pan block where the element can be given its own pan table and/or be routed into an AFM element to be used for further sound generation.

The AWM section has one Low Frequency

SYNTHESIS

Oscillator which can be used for vibrato/tremolo/sample and hold effects, or to modulate the filter. This LFO has 6 different waveform types, a speed, a delay and a phase control.

The Multi Mode and Sequencing Modes (Song and Pattern)

The SY77 Multi mode allows up to 16 Voices to be set up and played by the sequencer (ie. it is 16 voice Multi-timbral). Each voice is allocated to one of 16 tracks (like a multi-track tape recorder), and each track is given a MIDI channel. Only data referring to one MIDI channel is allowed to play a voice. The MIDI channel allocation in multi-mode has been fixed to simplify the process of making music so that the user simply chooses a voices and places it on a track (1-16). The track number also represents the MIDI channel number so there is no need to assign a MIDI channel to a particular track. Each Voice in Multi Mode has its own Volume, Tuning, note Shift, PAN, and Output Select Functions. There is also an effects section which is connected to the stereo outputs allowing a degree of mixing.

The Sequencer is really a completely independent part of SY77 and has its own set of control buttons located left of the LCD. This allows the sequencer to be stopped and started even whilst editing a voice enabling changes in sound whilst the sequencer is running. Additionally, the sequencer will not only record data from the SY77's keyboard but also from the MIDI In port, and it can playback on the internal tone generation system or via the MIDI Out port. The tone generator can respond to the internal sequencer or via the MIDI In port. The Sequencer is loosely based around the Yamaha QX3 hardware sequencer, and in fact it will read QX3 sequencer files directly from the SY77 disk drive. It features 16 tracks (15 assignable and 1 drum track), approximately 16000 note recording capability, and a recording resolution of 1/96 of a quarter note. The sequencer has its own dedicated CPU (63CO1Y). The Sequen-

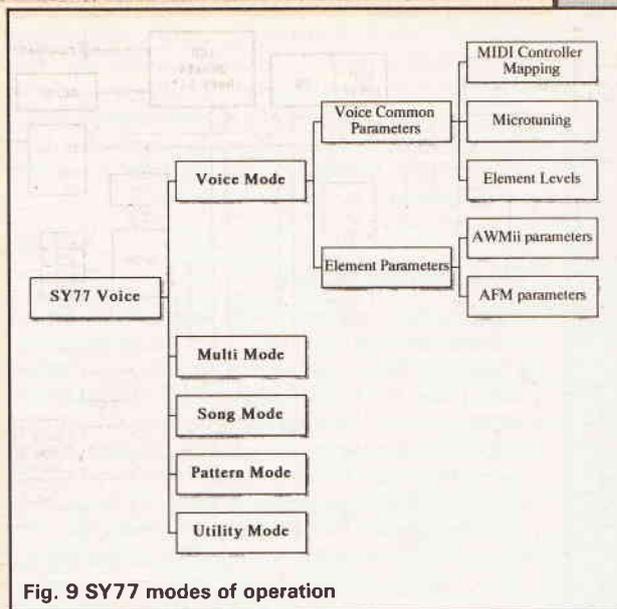


Fig. 9 SY77 modes of operation

Mode	Element	E1	E2	E3	E4
01	1AFM mono	AFM	-	-	-
02	2AFM mono	AFM	AFM	-	-
03	4AFM mono	AFM	AFM	AFM	AFM
04	1 AFM poly	AFM	-	-	-
05	2AFM poly	AFM	AFM	-	-
06	1AWM poly	AWM	-	-	-
07	2AWM poly	AWM	AWM	-	-
08	4AWM poly	AWM	AWM	AWM	AWM
09	1AFM & 1AWM poly	AFM	AWM	-	-
10	2AFM & 2AWM poly	AFM	AFM	AWM	AWM
11	Drum Set	61 AWM waves			

Fig. 10 SY77 element configurations

cer can record in real-time (by playing the keyboard), or step-time (by programming individual notes) and also has the ability to Punch-in and out. It also implements a series of automatic functions which can

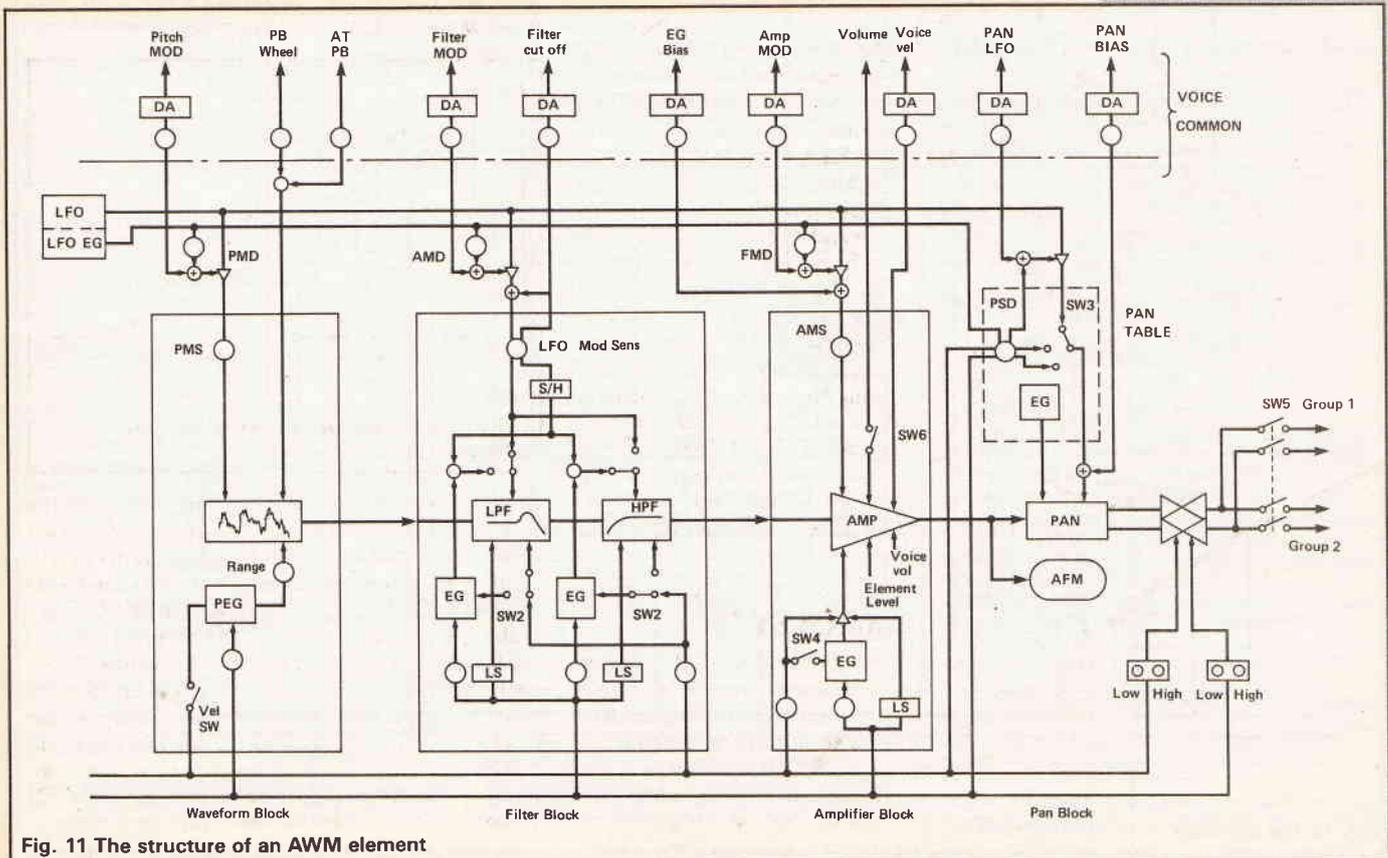


Fig. 11 The structure of an AWM element



quantize (modify the timing) or transpose a specified track or section of the song, make a crescendo, remove bars of music, insert bars of music, etc., etc.

The Sequencer can run in Song or pattern Mode, and the tone generator operates in either Voice (one channel) or Multi Mode (16 Channels). This enables four possible sequencer/tone generator configurations.

The Utility Mode

Utility Mode is concerned with setting up the SY77 to fit a studio with other MIDI products so that it has a unique identity channel for receiving and transmitting data. Master instrument tuning, and keyboard velocity curves (eight different types to weight the keyboard response to your playing style) are under the System menu of Utility mode. It is also the mode used for data storage and retrieval to 3.5" floppy disk (DOS format) and Yamaha data card. To simplify data storage there is an option to store all data types (Multi, Voice, Sequencer, etc.) as one file.

Conclusions

All the technical details focused on here should not overshadow the fact that SY77 is after all a musical instrument. It is well crafted, attractively designed and capable of fantastic expression in the hands of a professional keyboard player. It is always hard to examine something like an instrument from a cold technological standpoint. The experience is in playing and listening to it which is when the impressive technical specifications actually begin to say something relevant. Like a well-designed car, it has to be driven to appreciate it. So giving it a listen at a music shop will put all the details into perspective.

References:

- [1] The SY77 Operating Manual (Yamaha Corporation, 1989)
- [2] The SY77 Service Manual (Second Edition, Yamaha Corporation, 1990)
- [3] J. Chowning: The Synthesis Of Complex Audio Spectra By Means Of Frequency Modulation (Journal Of The Audio Engineering Society 21(7), 1973)
- [4] J. Chowning & D. Bristow: FM Theory & Applications (Yamaha Music Foundation, 1986)
- [5] G. Armbruster (Editor): The Art Of Electronic Music (Quill/GPI, 1984)
- [6] Keyboard Magazine Editor: Synthesizers & Computers (Hal Leonard/GPI, 1985)

NB. The views expressed here are those of the author and are not necessarily the views of Yamaha Corporation.

Mike Barnes is a postgraduate in Music Information Technology, works for the Yamaha Research & Development Centre, London as MIDI Product Specialist and is currently involved in voicing, sampling and demonstration work for the new SY/TG series.

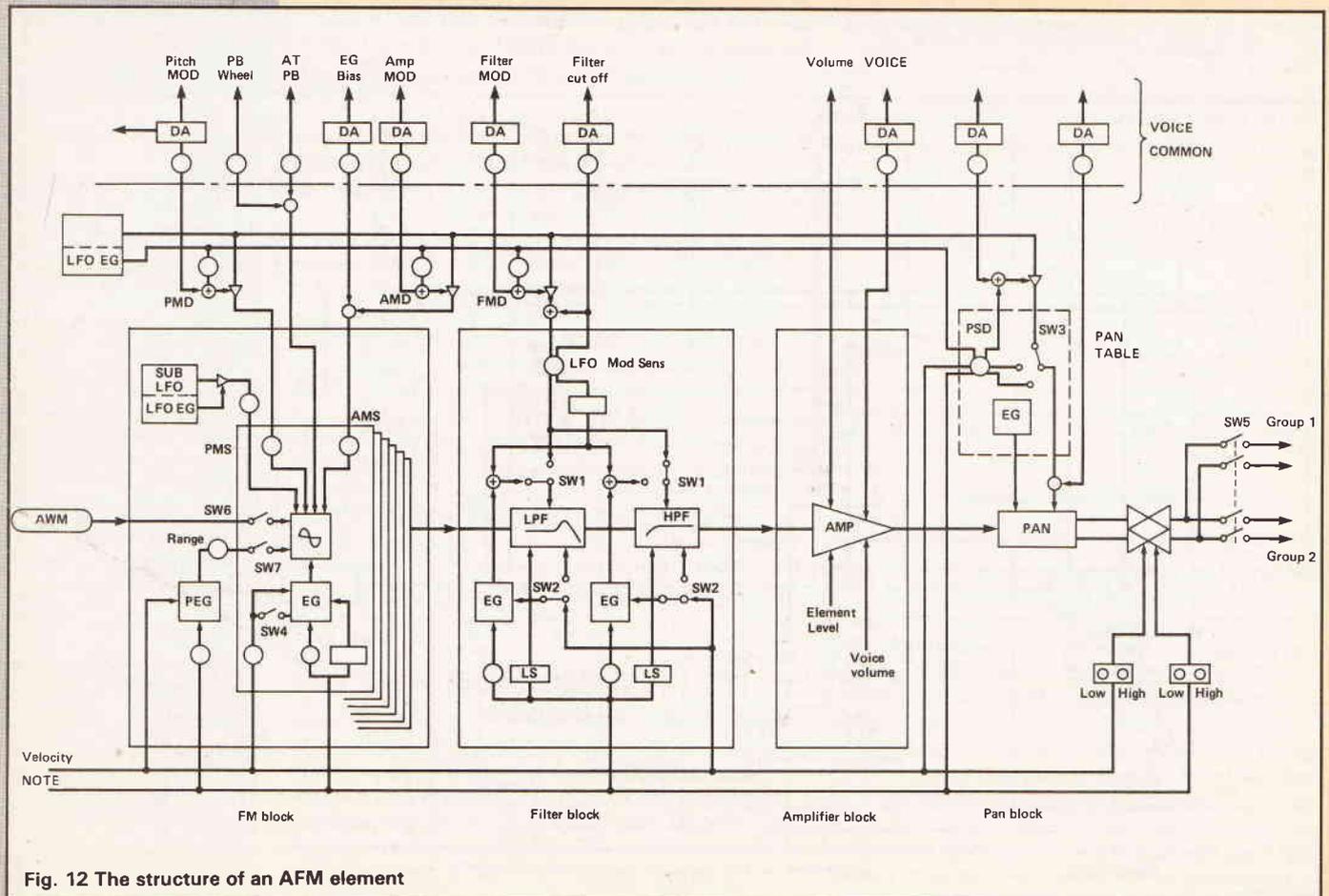


Fig. 12 The structure of an AFM element

ONE POUND BARGAIN PACKS

All packs are £1 each. Note the figure on the extreme left is the pack ref number and the next figures is the quantity of items in the pack, finally a short description.

- BD2 5 13A spurs provide a fused outlet to a ring main where device such as a clock must not be switched off
- BD9 2 6v. 1A mains transformers upright mounting with fixing clamps
- BD11 1 6 1/2" speaker cabinet ideal for extensions, takes your speaker. Ref BD137 + 50p.
- BD13 12 30 watt reed switches, it's surprising what you can make with these — burglar alarms, secret switches, relay etc. etc
- BD22 2 25 watt loud speaker two unit cross-overs
- BD30 2 Nicad constant current charges adapt to charge almost any nicad battery
- BD32 2 Humidity switches, as the air becomes damper the membrane stretches and operates a microswitch
- BD42 5 13A rocker switch three tag so on/off, or change over with centre off
- BD45 1 24hr time switch, ex-Electricity Board, automatically adjust for lengthening and shortening day.
- BD49 5 Neon valves, with series resistors, these make good night lights
- BD56 1 Mini uniselector, one use is for an electric jigsaw puzzle, we give circuit diagram for this. One pulse into motor, moves switch through on pole
- BD67 1 Suck or blow operated pressure switch, or it can be operated by any low pressure variations such as water level in water tanks
- BD103A 1 6v 750mA power supply, nicely cased with input and output leads
- BD120 2 Stripper boards each contains a 400v 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of condensers etc
- BD132 2 Plastic boxes approx. 3" cube with square hole through top so ideal for interrupted beam switch
- BD134 10 Motors for model aeroplanes, spin lo start so needs no switch
- BD139 6 Microphone inserts — magnetic 490 ohm also act as speakers
- BD148 4 Reed relay kits you get 16 reed switches and 4 coil sets with notes on making c/o relays and other gadgets
- BD149 6 Safety cover for 13A sockets — prevent those inquisitive little fingers getting nasty shocks
- BD180 6 Neon indicators in panel mounting holders with lens
- BD193 6 5 amp 3 pin flush mounting sockets makes a low cost disco panel — need cable clips
- BD199 1 Mains solenoid very powerful has 1" pull or could push if modified
- BD201 8 Keyboard switches — made for computers but have many other applications
- BD211 1 Electric clock mains operated put this in a box and you need never be late
- BD221 5 12v alarms make a noise about as loud as a car horn. Slightly solid but OK
- BD252 1 Panostat, controls output of boiling ring from simmer to boil
- BD259 50 Leads with push on 1/4" tags — a must for hook ups — mains connections etc
- BD263 2 Oblong push switches for bell or chimes, these can mains up to 5 amps so could be foot switch if fitted into pattress
- BD268 1 Mini 1 watt amp for record player. Will also change speed of record player motor
- BD305 1 Tubular dynamic mic with optional table rest
- BD653 2 Miniature driver transformers. Ref LT44. 20k to 1k, centre tapped
- BD548 2 3.5v relays, each with two pairs changeover contacts
- BD667 2 4.7uF, non-polarised block capacitors, pcb mounting
- There are over 1,000 items in our catalogue. If you want a complete copy please request this when ordering.

PERSONAL STEREOS Again customer returns but complete and with stereo head phones. A bargain at only £3 each. Our ref 3P83.

MAINS OPERATED MICROWAVE CONTROL PANEL WITH TOUCH SWITCHES This has a 4-digit display with a built-in clock and 2 relay outputs, 1 for power and 1 for pulsed power level. Could be used for all sorts of timer control applications. Only £6. Ref 6P18.

EQUIPMENT WALL MOUNT. Multi-adjustable metal bracket for speak, etc. 2 for £5. Our ref 5P152.

STABILISED POWER SUPPLY KIT. +-+V2.0A. Contains PCB, transformer and all components excluding case, etc. Our price is £20. Ref 20P25.

KEYBOARDS. Brand new uncased with 84 keys plus PCB with several ICs. Only £3. Ref 3P89.

SUB-MIN TOGGLE SWITCH. Body size 8mm x 4mm x 7mm SBDT with chrome dolly fixing nuts. 3 for £1. Order ref BD649.

COPPER CLAD PANEL. For making PCB. Size approx 12in long x 8 1/2in wide. Double-sided on fibreglass middle which is quite thick (about 1/16in) so this would support quite heavy components and could even form a chassis to hold a mains transformer, etc. Price £1 each. Our ref BD633.

POWERFUL IONISER

Generates approx. 10 times more IONS than the ET1 and similar circuits. Will refresh your home, office, workroom etc. Makes you feel better and work harder — a complete mains operated kit, case included. £18. Our ref 18P2.

REAL POWER AMPLIFIER. For your car, it has 150 watts output. Frequency response 20hz to 20Khz and signal to noise ratio better than 60db. Has built in short circuit protection and adjustable input level to suit your existing car stereo, so needs no pre-amp. Works into speakers ref. 30P7 described below. A real bargain at only £57.00. Order ref: 3P71.

REAL POWER CAR SPEAKERS. Stereo pair output 100w each. 4-ohm impedance and consisting of 6 1/2" woofer, 2" mid range and 1" tweeter. Ideal to work with the amplifier described above. Price per pair £30.00. Order ref: 30P7.

TV SOUND DECODER. Nicely cased, mains powered with 8 channels. Will drive a small speaker directly or could be fed into HiFi system etc. £12.00 each. Ref: 12P22.

VIDEO TAPES These are three hour tapes of superior quality, made under licence from the famous JVC Company. Offered at only £3 each. Our ref 3P63. Or 5 for £11. Our ref 11P3. Or for the really big user 10 for £20. Our ref 20P20.



soldering of the components on the pcb. Complete kit £10. Our ref 10P81.

2KV 500 WATT MAINS TRANSFORMERS. Suitable for high voltage experiments or as a spare for a microwave oven etc. £10.00. Ref: 10P93

12" HIGH RESOLUTION MONITOR. Amber screen, beautifully cased for free standing, needs only a 12v 1.5 amp supply. Technical data is on its way but we understand these are TTL input. Brand new in maker's cartons. Price: £22. Order ref 22P2.

STC SWITCHED MODE POWER SUPPLY 220V or 110V operation giving 5V at 2A + 24 at 25A + 12 at 15A and +90V at 4A. £12.00 each. Ref: 12P27.

COMPOSITE VIDEO KITS. These convert composite video into separate h-sync, v-sync and video. Price £8. Our ref 8P39

BUSH RADIO MIDI SPEAKERS. Stereo pair. BASS reflex system, using a full range 4in driver of 4 ohms impedance. Mounted in very nicely made black fronted wainut finish cabinets. Cabinet size approx 8 1/2in wide, 14in high and 3 1/2in deep. Fitted with a good length of speaker flex and terminating with a normal audio plug. Price £5 the pair. Our ref 5P141.

3 1/2in FLOPPY DRIVES. We still have two models in stock: Single sided, 80 track, by Chinon. This is in the manufacturers metal case with leads and IDC connectors. Price £40, reference 40P1. Also a double sided, 80 track, by NEC. This is uncased. Price £60, reference 60P2. Both are brand new.

YUASHA SEALED LEAD ACID BATTERIES 6V only £9.00 each or 2 for £15.00. Ref: 15P37.

SINCLAIR CS WHEELS

Including inner tubes and tyres. 13" and 16" diameter spoked polycarbonate wheels finished in black. Only £6 each. 13" ref 6P20. 16" ref 6P21.

PC STYLE CASES 18" x 18" x 6". Complete with fan and grill illuminated power switch and IEC filtered power input plug. Priced at only £15.00. Ref: 15P38.

VERY POWERFUL 12 VOLT MOTORS. 13rd Horsepower. Made to drive the Sinclair CS electric car but adaptable to power a go-kart, a mower, a rail car, model railway, etc. Brand new. Price £20. Our ref 20P22.

PC POWER SUPPLIES. Brand new with built in fan and power switch on the back +5 -5 +12 -12 150 watt made by AZTEC. £25.00 each. Ref: 25P18

PHILIPS LASER

This is helium-neon and has a power rating of 2mW. Completely safe so long as you do not look directly into the beam when eye damage could result. Brand new, full spec, £35. Mains operated power supply for this tube gives 8kv striking and 1.25kv at 5mA running. Complete kit with case £15.


ORGAN MASTER is a three octave musical keyboard. It is beautifully made, has full size (piano size) keys, has gold plated contacts and is complete with ribbon cable and edge connector. Can be used with many computers, request information sheet. Brand new, only £15 plus £3 P&H.

HIGH RESOLUTION MONITOR. 9in black and white, used Philips tube M24306W. Made up in a lacquered frame and has open side. Made for use with OPD computer but suitable for most others. Brand new, £20. Ref 20P6

12 VOLT BRUSHLESS FAN. Japanese made. The popular square shape 4 1/2in x 4 1/2in x 134in). The electronically run fans not only consume very little current but also they do not cause interference as the brush type motors do. Ideal for cooling computers, etc., or for a caravan. £8 each. Our ref 8P26

MINI MONO AMP on p.c.b. size 4" x 2" (app.)

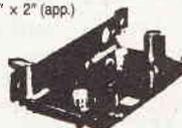Fitted Volume control. The amplifier has three transistors and we estimate the output to be 2W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 13 for £12.



NEW MAINS MOTORS. 25 watt 3000 rpm made by Framco approx 6" x 4" x 3" priced at only £4. Ref 4P54.

SHADED POLE MOTORS. Approx 3" square available in 24V AC or 240V AC, both with threaded output shaft and 2 fixing bolts. Price is £2 each. 24V ref 2P65. 240V ref 2P66.

MICROWAVE TURNTABLE MOTORS. Complete with weight sensing electronics that would have varied the cooking time. Ideal for window displays etc. Only £5. Ref 5P165.

SURFACE MOUNT KIT. Makes a super high gain snoping amplifier on a PCB less than an inch square! £7. Ref 7P15.

INDUCTIVE PROXIMITY SWITCHES. Made by Honeywell these units are brand new and offered at only £12 each which is a fraction of their normal price. 10-36V DC model ref 12P19 or main version 12P20.

1990 CATALOGUE NOW AVAILABLE PLEASE SEND 6" x 9" SAE FOR FREE COPY

BULL ELECTRICAL

Dept. ET1, 250 PORTLAND ROAD, HOVE, BRIGHTON, SUSSEX BN3 5QT.

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Please add £2.50 service charge. Monthly account orders accept from schools and public companies. Access & Barclaycard orders are accepted — minimum £5. Phone (0273) 203500. Fax 23077

POPULAR ITEMS — MANY NEW THIS MONTH

1990 CATALOGUE now available — phone for copy.

YUASHA LEAD ACID RECHARGEABLE BATTERIES. 1.9AH 12v, £6.00 each; 10AH 6v £12.00 each.

JOYSTICKS for BBC, Atari, Dragon, Commodore, etc. All £5 each. All brand new, state which required.

BOSCHERT SWITCHED MODE POWER SUPPLIER. +5 at 15A +12 at 3A -12 at 2A +24 at 2A 220v or 110v input. Brand new and guaranteed. Retail price is £180!! ours £20. Ref: 20P30.

SUB-MIN PUSH SWITCHES Not much bigger than a plastic transistor but double pole, PCB mounting. Three for £1. Our ref BD688

AA CELLS. Probably the most popular of the rechargeable NICAD types 4 for £4. Our ref 4P44.

20 WATT 4OHM SPEAKER With built in tweeter. Really well made unit which has the power and the quality for hi-fi. 6 1/2in dia. Price £5. Our ref 5P155 or 10 for £40 ref 40P7.

MINI RADIO MODULE Only 2in square with ferrite aerial and solid dia tuner with own knob. It is a superhet and operates from a PP3 battery and would drive a crystal headphone. Price £1. Our ref BD716.

BULGIN MAINS PLUG AND SOCKET. The old faithful 3 pin with screw terminals. The plug is panel mounted and the socket is cable mounted. 2 pairs for £1 or 4 plugs or 4 sockets for £1. Our ref BD715, BD715P or BD715S.

MICROPHONE. Low cost hand held microphone with on/off switch in handle, lead terminates in one 3.5 plug and one 2.5 plug. Only £1. Ref BD711.

MOSFETS FOR POWER AMPLIFIERS AND HIGH CURRENT DEVICES 140v 100w pair made by Hitachi. Available in H pack Ref 2SJ99 and 2SK343 £4 a pair. Ref 4P51.

TIME AND TEMPERATURE LCD MODULE. A 12 hour clock, a Celsius and Fahrenheit thermometer, a too hot alarm and a too cold alarm. Approx 50 x 20mm with 12.7mm digits. Requires one AA battery and a few switches. Comes complete with full data and diagram. Price £9. Our ref 9P5.

REMOTE TEMPERATURE PROBE FOR ABOVE. £3. Our ref 3P60

600 WATT AIR OR LIQUID MAINS HEATER. Small coil heater made for heating air or liquids. Will not corrode, lasts for years, coil size 3in x 2in mounted on a metal plate for easy fixing, 4in dia. Price £3. Ref 3P78 or 4 for £10. Our ref 10P76

EX EQUIPMENT SWITCHED MODE POWER SUPPLIES. Various makes and specs but generally ±5, ±12v, ideal bench supply. Only £8. Our ref 8P36.

ACORN DATA RECORDER. Made for Electron or BBC computer but suitable for others. Includes mains adaptor, leads and book. £12. Ref 12P15.

PTFE COATED SILVER PLATED CABLE. 19 strands of 45mm copper, will carry up to 30A and is virtually indestructible. Available in red or black. Regular price is over £120 per reel, our price only £20 for 100m reel. Ref 20P21 or 1 of each for £35. Ref 35P2. Makes absolutely superb speaker cable!

NEW PIR SENSORS. Infra red movement sensors will switch up to 1000W mains. UK made, 12 months manufacturers warranty. 15-20m range with a 0-10min timer, adjustable wall bracket, daylight sensor. Only £24.00. Ref 24P4.

GEIGER COUNTER KIT. Includes tube, PCB and all components to build a 9V operation geiger counter. Only £39. Ref 39P1.

SPECTRUM SOUND BOX. Add sound to your Spectrum with this device; just plug in. Complete with speaker, volume control and nicely boxed. A snip at only £4. Our ref 4P53.

BBC JOYSTICK INTERFACE. Converts a BBC joystick port to an Atari I/O port. Price £2. Our ref 2P261.

TELEPHONE EXTENSION LEAD. 5M phone extension lead with plug on one end and socket on the other. White. Price £3. Our ref 3P70 or 10 leads for only £19! Ref 19P2.

LCD DISPLAY. 4 1/2in digits supplied with connection data £3. Ref 3P77 or 5 for £10 Ref 10P78.

CROSS OVER NETWORK. 8 ohm 3-way for tweeter midrange and woofer. Nicely cased with connections marked. Only £2. Our ref 2P255 or 10 for £15 ref 15P32.

BASE STATION MICROPHONE. Top quality uni-directional electret condenser mic 600r impedance sensitivity 16-18KHz - 88db built in chime, complete with mic stand bracket. £15. Ref 15P28.

MICROPHONE STAND. Very heavy chromed mic stand, magnetic base. 4in high. £3 if ordered with above mic. Our ref 3P80.

SOLAR POWERED NI-CAD CHARGER. 4 Nicad AA battery charger charges 4 batteries in 8 hours. Price £6. Our ref 6P3

MAINS SOLDERING IRON. Price £3. Our ref 3P65

SOLDERING IRON STAND. Price £3. Our ref 3P66

SHARP PLOTTER PRINTER. New 4 colour printer originally intended for Sharp computers but may be adaptable for other machines. Complete with pens, paper, etc. Price £16. Our ref 16P3

KIT to convert the above Printer to Centronics parallel. £4. Ref 4P57.

CAR IONIZER KIT. Improve the air in your car, clears smoke and helps prevent fatigue. Case req. Price £12. Our ref 12P8.

NEW FM BUG KIT. New design with PCB embedded coil 9v operation. Priced at £5. Our ref 5P158.

NEW PANEL METERS. 50UA movement with three different scales that are brought into view with a lever. Price only £3. Ref 3P81.

STROBE LIGHTS. Fit a standard Edison screw light fitting 240v 40/min flash rate, available in yellow, green, complete with socket. Price £10 each. Ref 10P80 (state colour reqd).

ELECTRIC SPEED CONTROL KIT. Suitable for controlling our powerful 12v motors. Price £17. Ref 17P3 (heatsink required)

EXTENSION CABLE WITH A DIFFERENCE. It is flat on one side, making it easy to fix and look tidy. 4 core, suitable for alarms, phones etc. Our price only £5 for 50m reel. Ref 5P153.

METAL PROJECT BOX. Ideal for battery charger, power supply etc., sprayed grey, size 8" x 4" x 4 1/2", louvred for ventilation. Price £3 Ref 3P75.





NEWS

Anyone who is worried about acoustic feedback when performing on stage could try this latest adaption to the C1000S microphone from AKG.

This studio quality microphone is frequently used on stage and if amplifier levels are too high, howlround can result.

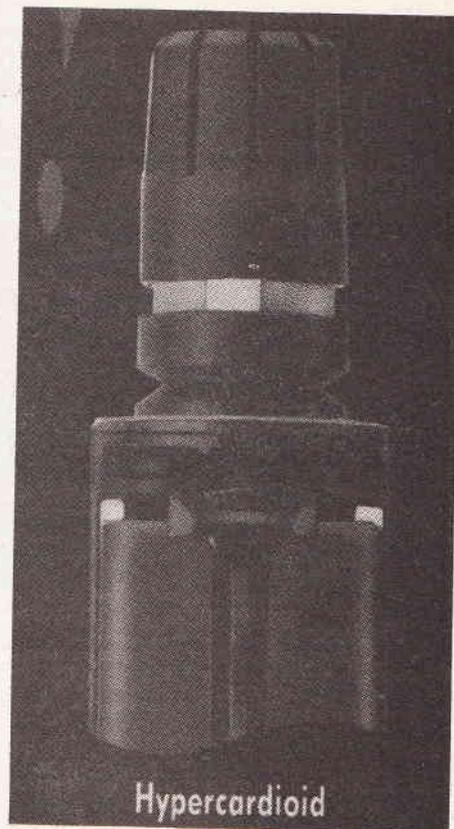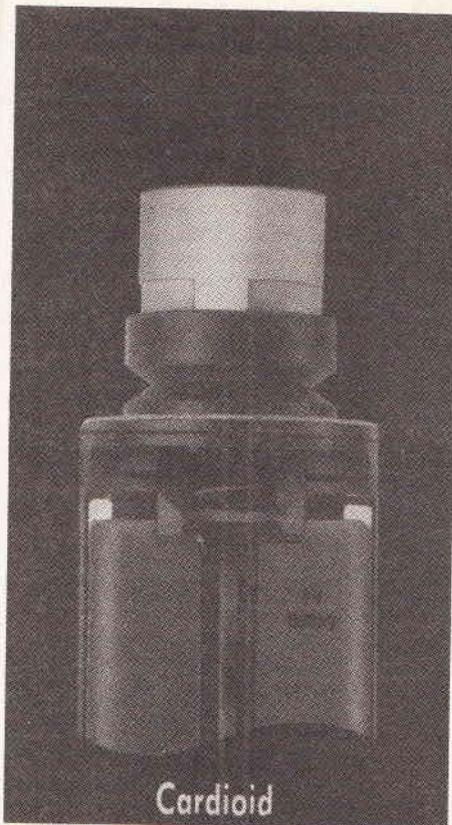The new Polar pattern converter (PPC1000) is a small capsule that fits over the mic insert and will change the familiar heart-shaped response pattern to one of Hypercardioid shape, making it more sensitive and less vulnerable to feedback from the monitors



and giving the vocalist a greater presence on stage.

The pattern converter will not affect the frequency response and is available separately if an existing C1000S is already to

hand. The microphone capsule is a backplate transducer which reduces handling noise to a minimum and is either battery or phantom powered.

The AKG C1000S retails at £149 + VAT.

Wilmslow Audio have now settled in their new premises in Knutsford. They now have 4 single speaker Dem rooms and a large selection of Hifi equipment is now available as well as an extensive range of drive units and kits.

The new catalogue has just been released and contains new kits from KEF, AUDAX, SEAS, PEERLESS and VOLT and is available from Wilmslow Audio at a cost of 1.50.

Wilmslow Audio's new address is Wellington Close, Parkgate Trading Estate, Knutsford, Cheshire, WA16 8DX. Tel No. 0565 50605.

AHifi journal aimed specifically at the DIY constructor is changing format. The magazine Audio Conversions has only been available to people attending Hifi shows, and to associates of the contributors. Up until now, the magazine has been published in black and white and in A5 size.

The magazine now has over a thousand subscribers and from the next issue will be published in colour and in A4 size. Audio Conversions provides information and advice ranging from simple modifications through to kits and full projects and is published quarterly at an annual rate of £8 or £10 for overseas readers and 8 back issues are available at a cost of £1.50 each.

Audio Conversions is available from: Audio Conversions, Coley Lane Farm, Wentworth, Rotherham, S62 7SQ.

Digital audio multi-track recording is fast becoming the normal method of recording and as prices start to tumble with increasing competition, the hardware will eventually find a niche in the home recording market.

Akai has released ADAM, the Akai Digital Multi-track system, which consists of a multi-track recorder, a programmable auto-locator and a meter unit. It gives studios and individuals access to 12 track digital recording using 8mm compact video tapes. The 16 bit linear quantisation recording system uses 48/41.1kHz sampling rates in PCM format via the now familiar rotating helical-scan head. Three record and three playback heads are mounted in the rotating drum with stationary heads for erase and control. Digital


inputs and outputs enable direct transfer of signals from one recorder to another and synchronised control allows up to three 12 channel recorders to be linked.

The retail price of the multi-track recorder (DR1200) is £13950 + VAT, the programmable auto-locator (DL1200) £1050 + VAT and the Meter Unit (DM1200) £695 + VAT.





NEWS CONTINUED

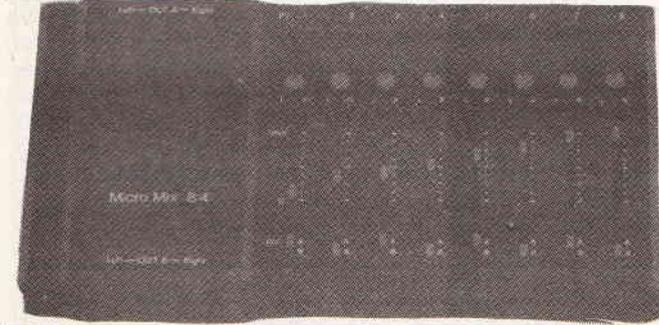

Music mixers are getting smaller and smaller. The AKG Micro-Mix can even be clamped to a drum stand and gives the drummer control over mic mixing of any of his percussion instruments.

The Micro-mix 8 into 4 and 8 into 2 will allow the input of 8 condenser microphones or line inputs. Apart from the normal slide faders, each channel has a switchable output and pan control. Phantom power controlled,

the mixer can boast of a 96dB signal-to-noise ratio, a crosstalk figure of 53dB and a frequency response of 20-20kHz.

The 8 into 4 retails at £189 + VAT and the 8 into 2, £175.50 + VAT.

HHB Communications has landed the contract for the design and installation of audio and video facilities at ITN's impending headquarters in Grays Inn Road.

The main deal is worth more than half a million pounds to the West London-based company. They will install and commission complete audio systems within two separate studios and a sound dubbing suite. The company is also re-locating a further dubbing suite and designing outside broadcast interface facilities for a third studio. HHB has also

been contracted to re-locate and part equip the video presentation suite. This requires meticulous planning, since the suite itself cannot be out of service for more than 72 hours.

The project will include several extensive custom designs and complex hardware configurations and will include the integration and installation of two Solid State Logic 5000 Series consoles. HHB is reporting directly to ITN and most of the work is to be completed by the end of 1990.

Ten years ago the world had its first taste of personal music on the move from Sony. The now legendary Walkman has given pleasure to over 55 million people and earned its place in the Oxford dictionary. Often imitated, the Sony Walkman celebrated its 10th birthday with a dedicated programme of the Design Classics Series on BBC Television, June 19th, 1990.

Now the choice is wider than ever with 25 models to choose from.

The WM2011 is finished in black with new styling and complete with lightweight headphones. Auto shut-off in the play mode and normal/metal tape selector plus belt clip are provided at a price of £19.99. The slim WM2051 fills a new slot in the range with auto reverse tape playback. Battery power can be saved by the use of an optional AC adaptor and this Walkman will sell at around £27.99.

With stereo FM and AM radio the WMF2015 follows the new angled styling of the 2011 model. DC in socket, headphones and belt clip are all supplied for only £29.99.

Finally, for the active user is a new sports model the WMF2078 with water resistant casing and showerproof following headphones. This Walkman is complete with digital FM/AM tuner, 14 presets, clock timer, auto reverse and Dolby B. Finished in bright sports yellow this model completes the line-up at £119.99.

MORE NEXT MONTH

BRIAN PRICE BOHM ORGAN STUDIOS

66 Ashchurch Drive, Wollaton, Nottingham NG8 2RA
Telephone/Fax: 0602-284766

33 years of experience in high quality Organ and Keyboard design behind every BOHM product.

The LATEST from BOHM 900/910 Series Organs

- ★ 400 sounds in NEW BOHM H.D.S. System
- ★ 256 Sampled Rhythms and Accompaniments
- ★ 22 Track Sequencer
- ★ Touch-Sensitive keyboards 49 Notes
- ★ All features fully Programmable by user, Soundcard or Optional Floppy Disc.
- ★ Available in choice of cabinets and Veneers.

520 Expander

- ★ Full Organ features. Stereo Voicing
- ★ Sound Sampled Rhythms
- ★ Fully Programmable from Soundcard

STATION ONE EXPANDER

- ★ All features of 900 Series Organs
- ★ Plus 48 track sequencer
- ★ Unlimited Programming facilities for Sounds, Rhythms and Accompaniments
- ★ Storage on soundcard, Floppy Disc, Hard Disc or very large Internal memory
- ★ Supplied with 400 Sounds and 120 Rhythms.

We are also the UK suppliers for the BOHM IC E510.
Available with full Technical Information.

Supplied in kit form or built by:
THE BOHM SPECIALISTS

Part Exchanges welcome. Please write or phone for NEW English brochures and price list. — Callers by appointment please.

Contact your local agent:

South Wales:
Vernon Pursall
66 Colcot Road
Barry
South Glamorgan
Tel: 0446-733277

Scotland:
Keyboard Services
9 Kingswood Road
Kingswell
Aberdeen
Tel: 0224-744585

North West:
Nick Stammers
Westling, Tenfields
Hetton Le Hole
Tyne and Wear
Tel: 091-526 3589

Peerless CC FORCE




Wilmslow Audio's NEW range of speaker kits from Peerless.

This new range of four kits utilise CC technology drive units for optimum performance.

The kit contains all the cabinet components (accurately machined from smooth MDF for easy assembly).

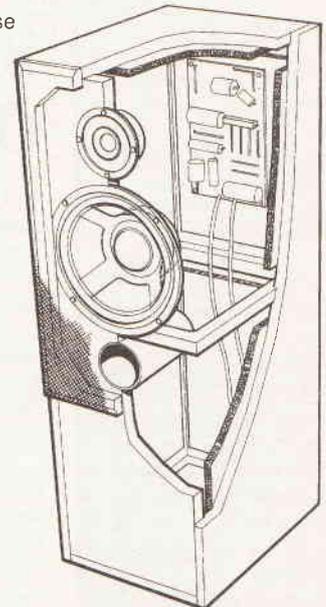Pictured here the Force 6, a large floor standing design.



Dimensions:
800 x 275 x 335 mm
Response:
32 HZ - 20 KHZ
AMP Suitability: 30-120w
Impedance: 8 ohms

Price		carr./ins.
Force 2	£159	£13 pr.
Force 4	£179	£13 pr.
Force 6	£199	£15 pr.
Force 8	£245	£15 pr.

All kits are available in Plus and Basic forms.

Wilmslow Audio

Wellington Close,
Parkgate Trading Estate
Knutsford, Cheshire
WA16 8DX
Tel: (0565) 50605

DIY Speaker catalogue £1.50
post free (export £3.50)



Telephone credit card
orders welcome





AUDIO TIPS

CMOS Mixer


Although this circuit employs only one cheap CMOS IC and two transistors it is capable of high quality results. The IC, a 4011, contains four dual input NAND gates. Two of these are used with their inputs connected together to form inverters and biased into the linear mode by means of the feedback resistors, R2. Inputs are applied through the pots RV1/2 and are mixed by the gate to which they are coupled by C1, R1, R3 and C2. Although only two inputs are shown here, the circuit will mix up to four inputs by duplicating the input circuitry.

For clarity only one mixer gate is shown in the schematic. The other gate, along with all the

components to the left of C3 are duplicated on the other channel. The other two gates are used in a touch operated on-off switch.

The plates, which may consist of a small piece of Veroboard with alternate strips linked together and connected to the input of the gate and line respectively, control the output polarity of the gates.

When the circuit is turned on, by placing a finger on the touch plate, the output of this gate goes high switching Q2 hard on and supplying the circuit with current. To switch off the other touch plate is touched with the finger. The output then goes low removing the operating current from the circuit. The transistor Q2 gives the circuit a low output impedance and the gain with the input pot at maximum is four.

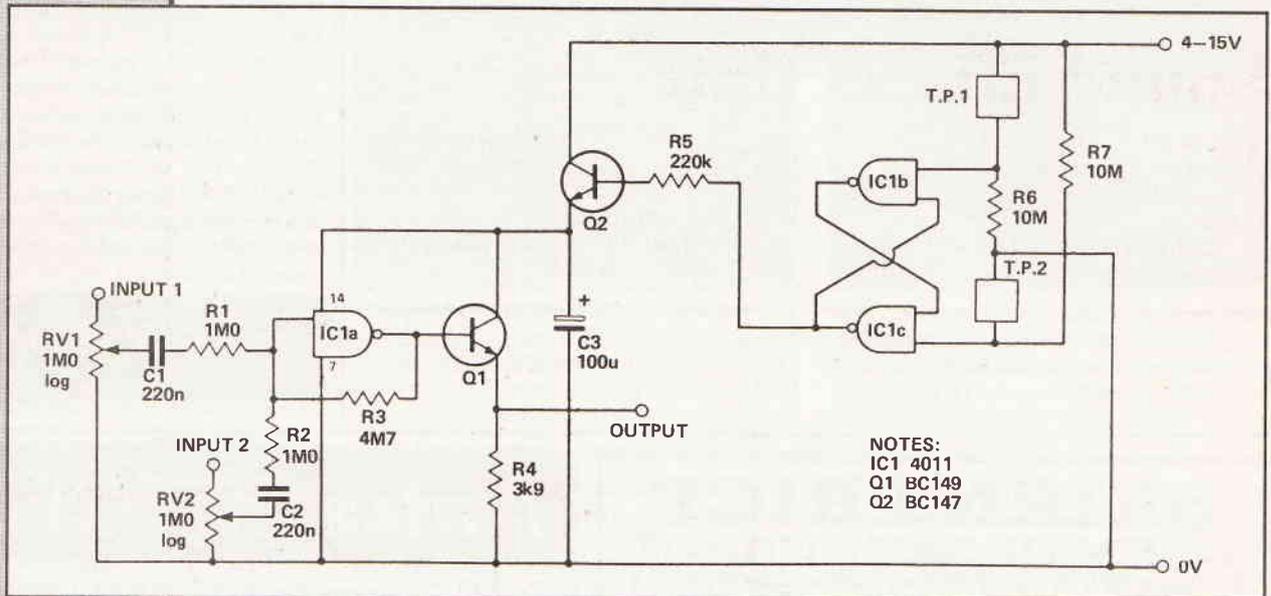

Soft Limiter


One of the fundamental differences between valve and transistor amplifiers is their behaviour when driven into clipping. The valve amps go into so-called soft clipping whilst their transistorised counterparts generate large quantities of harmonic distortion. The circuit shown simulates the soft clipping of valve amplifiers and is intended to be used between the power amplifier's input and the preamplifier's output.

R4 and R5, decoupled by C2 set a half supply reference for the non-inverting input of the op amp. Input signals are fed into the inverting input via the DC blocking capacitor and R1, the latter defining small signal gain and input impedance.


For small signals the amplifier's output is an exact unit gain copy of the input. As the signal level increases, however, the time will come when the voltage across the output and slider of RV1 will be sufficient to bias Q1 or Q2 on. When this occurs the feedback increases due to the shunting effect of R2 and R3.

The net effect is that musical peaks above a certain threshold are reduced in amplitude to prevent the power amplifier going into hard clipping. As a result, distortion is noticeably decreased whilst the subjective loudness appears unaffected.

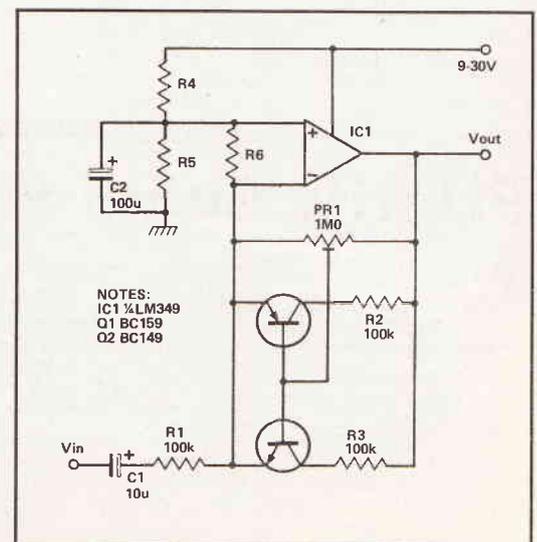The circuit is adjustable in operation between 130mV and 10V rms input sensitivity by means of RV1. To set the circuit up simply set the slider so that it is shorted to the output of the amp. Play some music at high volume through the system and adjust until the harshness just disappears. It's easier to do than describe.



CIRCUITS

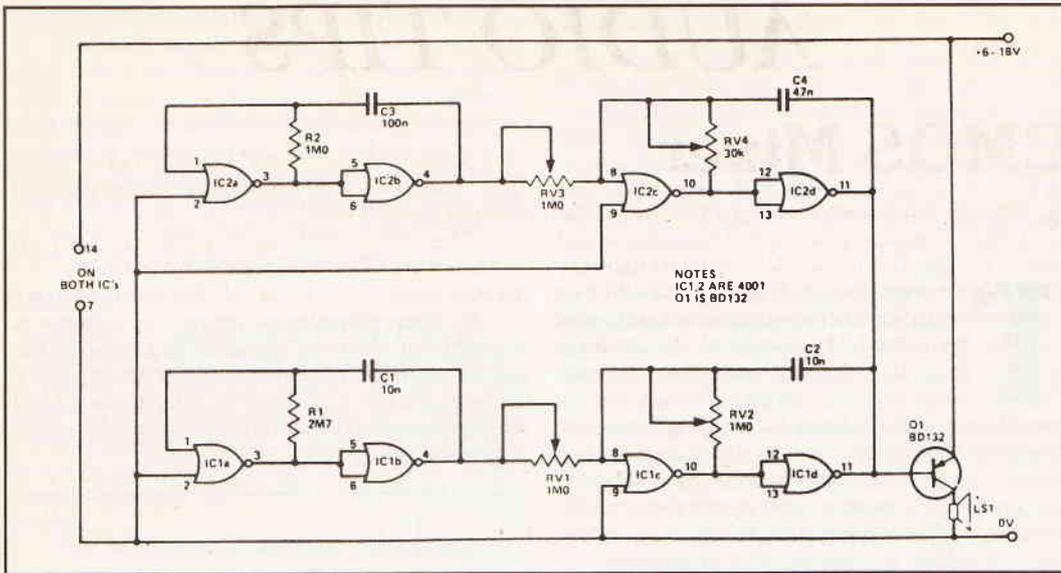


Sound Effects Unit

This circuit consists of four CMOS oscillators gated together in a configuration that will produce a multitude of effects from white noise to a multibanked Triphone.

Each IC is connected as a warble tone generator and mixed together at the base of Q1. LS1 can be from

8 - 100R, but the transistor tends to get a bit hot below 30R, so a small heatsink may be needed.

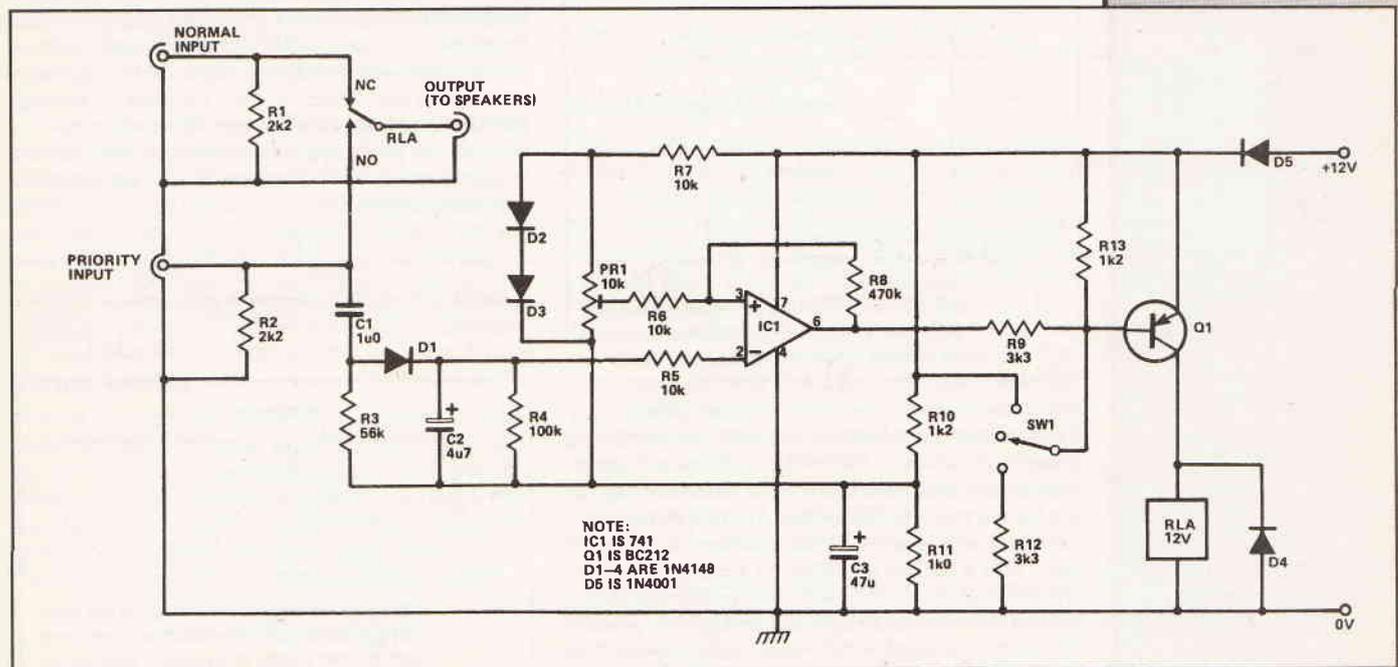None of the component values are critical and if desired, RV1,3 can be replaced by ordinary resistors without affecting the variety of sound effects too much.



Priority Audio Switch

This circuit switches a single loudspeaker from a 'normal' to a 'priority' circuit whenever a signal appears on the priority input. The prototype was used to switch between a cassette player and a two-way radio whenever a call was received. Other uses include priority calls in PA systems, monitoring several infrequently-used radio channels, etc.

Audio from the priority input is rectified and applied to the Schmitt trigger circuit, IC1. If the rectified voltage exceeds the voltage set by RV1, IC1

switches and the relay is operated by Q1. The switching level is set by RV1. The hysteresis is controlled by R8 and the delay before the relay switches back to the normal channel at the end of a priority call depends on C2 (approximately 2s with the value shown).

If stereo outputs from the cassette recorder are to be switched, RLA will require two changeover contacts. Several of these circuits may be cascaded to provide more than one level of priority.

CROSSOVER NETWORKS — A NECESSARY EVIL?


Vivian Capel discusses the effects that crossover units can have on loudspeaker sound.

The majority of hi-fi loudspeakers in use today use two separate drivers to handle the treble and bass frequencies. Often a third is used to reproduce the mid frequencies and occasionally a sub-woofer is used to extend the bass about an octave below that of the bass driver. Super tweeters are sometimes used to extend the response well beyond the content of most programme material and beyond the range of human audibility, though no doubt Nipper, the HMV dog, would have wagged his tail with approval!

Most tweeters would be wrecked if fed with a good bass signal so a crossover network is used to separate the frequency bands and ensure that only

the bass cone.

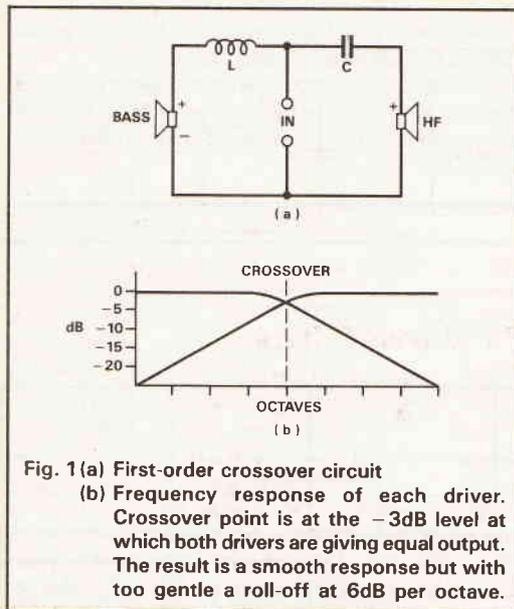To avoid interference effects, an inductor is connected in series with the bass unit to filter out the high frequencies. This single capacitor/inductor circuit is known as a *first-order network*, each leg attenuating the signal outside of its pass range at the rate of 6dB per octave (Figure 1).



the correct ones are fed to the appropriate drivers. Such circuits are therefore regarded as a necessary part of a hi-fi speaker. But because of their side effects they are often described like some medical drugs, as a necessary evil. Is this epithet justified though?

To discover just what those effects are, we will firstly take a look at the different types of crossover and how they work. They are made up from combinations of inductors and capacitors arranged to provide *low-pass*, *high-pass*, or *band-pass* characteristics. The degree of attenuation outside of the pass band depends on the type of circuit which are classified according to order.

First-Order Network

The simplest circuit is of a single capacitor connected in series with the tweeter which prevents low frequencies reaching it. Both low and high frequencies are fed to the bass unit which will reproduce some of the highs due to cone flexure. Having two speakers reproducing high frequencies in close lateral proximity results in interference at certain angles, reinforcement taking place at some frequencies and cancellation at others. Because of this the circuit is used only in cheap radio units, but it can be and is used effectively with co-axial speakers where the tweeter is mounted within

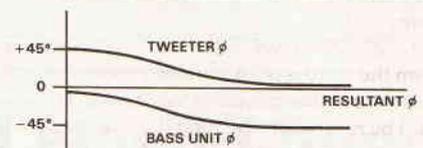


Fig. 2 Phase relationship of tweeter and bass unit. Resultant output is zero phase difference.

The point where they overlap is known as the *crossover frequency* and the values of the components are chosen so that at this point the response of each driver is -3dB or at half power. Now current through a capacitor leads the voltage, whereas it lags through an inductor. In the first-order network, the lead and lag is 45° in each case. These compensate acoustically to produce an in-phase signal from the drivers at the crossover frequency (Figure 2). The two half-power signals thus add to produce full power and so the response through the crossover region is flat. The formula for calculating the theoretical values are:

$$L = \frac{Z \times 10^3}{2\pi f_c} \quad C = \frac{10^6}{2\pi f_c Z}$$

in which L in the inductance in millihenries; C is the capacitance in microfarads; Z is the speaker impedance; and f_c is the crossover frequency.

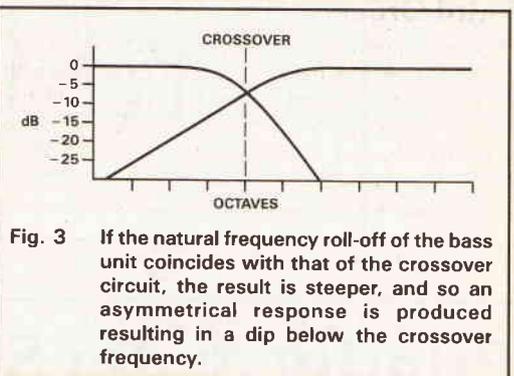


Fig. 3 If the natural frequency roll-off of the bass unit coincides with that of the crossover circuit, the result is steeper, and so an asymmetrical response is produced resulting in a dip below the crossover frequency.

There is a snag here though. The 6dB per octave roll off is too gentle. It means that at two octaves from the crossover point, both drivers are handling a -12dB signal that is outside of their respective bands, while at three octaves there is still a -18dB signal.

The problem arises when the natural frequency roll off of one of the drivers coincides with that of the filter. Then the total roll off for that drive is augmented and made steeper. So the two roll offs for the two drivers are non-symmetrical, one being steeper than the other. This produces a power level of less than -3dB for the affected driver at the crossover

frequency resulting in a dip in the response (Figure 3).

A further snag lies in the fact that the tweeter will be fed with substantial proportions of the bass signal which would not only produce distortion due to overloading it, but could result in damage. Yet another undesirable factor is that the tweeter resonant frequency (which should be kept below the crossover point and so out of the range it is required to handle) can be excited. The result is a peak at that frequency which is general in the mid-frequency range.

Second Order

The solution to these problems is to use filters having a sharper roll off. A 12dB per octave characteristic can be obtained by adding a capacitor across the bass driver and an inductor across the tweeter. This circuit is a *second-order network* (Figure 4), and it is also known as an L-filter because the series and parallel components form an L when drawn in a circuit diagram.

The disadvantage is that the phase difference between the drivers is 180° which produces a dip in the response at the crossover frequency. This can be avoided by reverse connecting the tweeter, but then a hump is produced instead. Also, all the high frequencies are then in an opposite phase relationship to the low, compared to what they were in the original signal.

A musical instrument rich in harmonics such as the cello, may have its fundamental and second harmonic reproduced by the bass driver and the higher harmonics by the tweeter. Having the tweeter reversed thus changes their relationship and so also the signal waveform. While this seems to have little effect on quality, the stereo images could be impaired and it is a departure from the ideal that the reproduced signal should correspond as closely as possible to the original.

Sometimes a resistor is included in series with the tweeter and its series capacitor. This is done to attenuate its output when the tweeter sensitivity is greater than that of the bass driver which is often the case. Sensitivities are thus matched to give a uniform response. A bonus effect of this is to reduce the degree of current lead through the tweeter due to the capacitor, and thus the phase difference between the two drivers.

Third Order

Further components can be added to form a *third-order network*. This has an extra inductor in series with the bass unit and an extra capacitor in series with the tweeter. The circuit for each section looks like a T so it is often called a T-filter (Figure 5). The roll off slope in this case is 18 dB per octave (Figure 6). The formula for calculating theoretical values is:

$$L_1 = 3L_2 = 2L_3 = \frac{3Z \times 10^3}{4\pi f_c}$$

$$\text{and } C_1 = 2C_2 = \frac{2C_3}{3} = \frac{2 \times 10^6}{3\pi f_c Z}$$

Fourth Order

Adding another capacitor across the bass driver and a further inductor across the tweeter forms a fourth-order filter. This looks like the Greek letter π in circuit form, and so is called a π filter (Figure 7). It has a roll off of 24 dB per octave. As with the second-order filter there is a 180° phase reversal so the tweeter can be reverse connected unless other components are included which affect the phasing. Fourth-order filters are rarely used for crossover networks; second and third being the most common.

Optimised Design

The above formulae assume that the driver impedance is constant, which is not the case; it varies with frequency and resonances. They should therefore be considered as a starting point, and the values be modified according to the response of the driver. Sometimes irregularities in the response of one of the drivers can be partly compensated for by extra components, usually resistors across or in series with the main filter components, but additional inductors and capacitors are often used as well (Figure 8). It is thus possible to achieve a very flat response for a particular pair of drivers and enclosure. With so many variable factors the design frequently needs to be carried out by computer.

For any published design therefore, neither the type of drivers nor values of the network should be changed. They have, or should have been, carefully optimised. It follows that choosing a pair of drivers at random, then using an off-the-shelf crossover is very unlikely to give satisfactory results. However, some speaker manufacturers do little more than that, and certain ones have been known to substitute a quite different driver with no modification of the crossover filter at all, for the sole reason of lower cost.

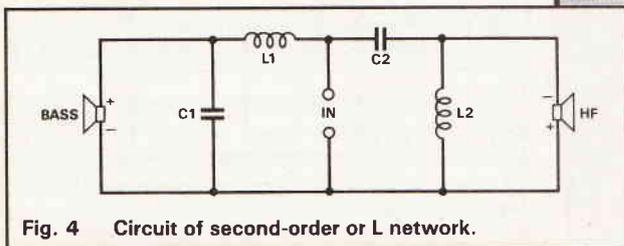


Fig. 4 Circuit of second-order or L network.

Band-pass Filters

When a mid-range driver is added it must be fed via a filter that supplies only the mid frequencies, so it must offer a rising impedance to both high and low frequencies. A first-order bandpass filter consists of a capacitor and inductor in series, while a second-order network has an extra capacitor and inductor, one in parallel across the driver and the other from the junction of the series components (Figure 9). Here too, additional components are often added to compensate for vagaries in the response of the driver.

Compensating components can be in nearly any part of the network circuit, but there are two general rules. No parallel component is ever connected directly across the input as this would be shunting the amplifier output. All attenuating resistors are on the amplifier side of the filter because the crossover

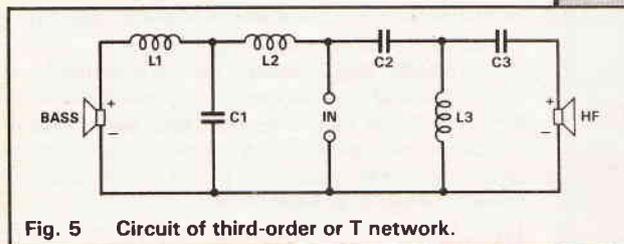


Fig. 5 Circuit of third-order or T network.

frequency would be affected if they were connected on the driver side.

A further convention is that all inputs are in parallel across the amplifier output so that each section may be considered a separate filter circuit. This means that it is not necessary for both, or the three in a three-way system, to be of the same order. Thus a second-order filter may be used for the treble unit to limit the amount of bass it will be fed,



DESIGN

while only a first-order circuit is used for the bass driver, as it may be considered less important to limit the high frequencies it handles. While this may result in some interference effects as we have seen, it reduces the phase difference and the effects of 'ringing'.

Components

The capacitors used are generally in the range of 1 — 10 μ F. Polarised electrolytics with a positive and negative connection are not used as the signal is pure AC. Furthermore, electrolytics have wide tolerances and so a precise value cannot be obtained. So while non-polarised electrolytics can be used, other types are preferable.

The inductors can be either air-cored or ferrite

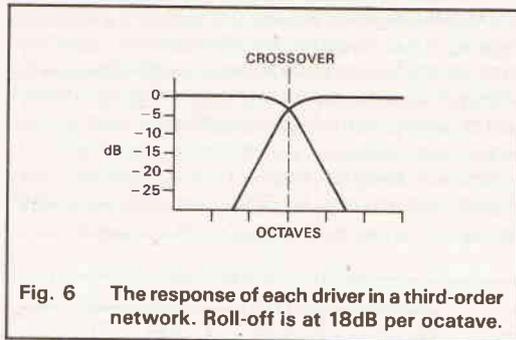


Fig. 6 The response of each driver in a third-order network. Roll-off is at 18dB per octave.

cored. The ferrite components are smaller because they are magnetically more efficient, most of the generated flux being concentrated in the windings by the core. The disadvantage is that it is possible for the core to saturate at high signal levels, thereby varying the inductance, hence also the impedance. The result is harmonic distortion and changing of the crossover characteristics.

Air-cored inductors do not suffer from this possibility, but they are large and heavier. A problem can be the large leakage field which can interact with any other inductor within range and so introduce mutual coupling between them. The effects of this can be strange and unpredictable. All coils, but especially

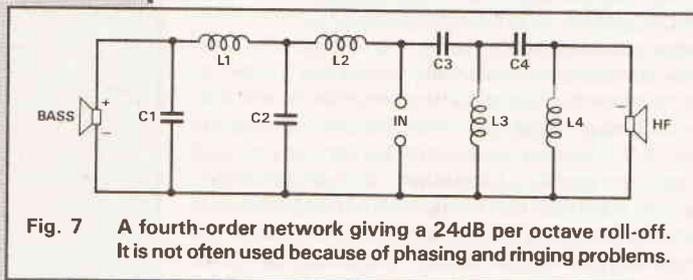


Fig. 7 A fourth-order network giving a 24dB per octave roll-off. It is not often used because of phasing and ringing problems.

air-cored ones, should be mounted well apart, and if possible with their axes at right-angles.

A printed circuit board is the usual method of interconnecting the components, but whichever way the components are connected, they should be fixed securely with no possibility of adjacent ones touching and thereby able to produce buzzes or rattles when subject to high level sound waves.

Ringing

But now the the undesirable side effects. If the signal applied across a capacitor ends abruptly, a charge is left which subsequently discharges through any parallel circuit. In the case of a crossover filter this will almost certainly include the associated driver. Thus terminating transients in the signal are blurred.

A similar effect occurs in the case of an inductor. An abrupt cessation of current flowing through it causes a rapidly collapsing magnetic field which cuts

across its own windings. This generates a voltage that produces a current through any parallel circuit. In the case of a collapsing field, the current so produced is of the same polarity as the original. So the effect is to sustain the current after the signal has ceased. Again a blurring of terminating transients results.

By themselves these overhang effects may not be too bad, but there is worse to follow. The induced current in the inductor recharges the capacitor, which discharges back through the inductor when the current ceases. So another field builds up which produces further current to recharge the capacitor again and so on.

Thus current surges backwards and forwards in oscillatory cycles until the losses in the circuit reduce it to zero. The effect, which is known as *ringing*, is greatest at the crossover frequency and can be clearly seen on tone-burst oscilloscope traces. It is also greater with the higher order filters which have more reactive components. This is one reason why first-order filters are sometimes employed for bass drivers and fourth-order circuits are rarely used at all.

There is another possible effect. Negative feedback from the output of the amplifier is commonly applied to earlier amplifier stages to cancel spurious harmonic distortion. But it can only do this if the feedback signal is truly out of phase at 180°. Any delay causes phase shift and could even turn into positive feedback thereby increasing distortion instead of reducing it.

Now, the oscillatory voltages generated by the crossover filter appear at the amplifier output terminals, and so are fed back to the earlier stage along the feedback path. They thus appear amplified in negative phase back at the output stage. However, the other reactive crossover components cause a phase shift so that they arrive back too late cancel the original oscillation. Instead, they tend to make matters worse by adding to it.

So some amplifiers that have a low distortion specification on paper achieved by heavy negative feedback, can sound worse than those having higher theoretical distortion due to a more modest feedback level. As the precise effect depends both on the amplifier feedback conditions and the nature of the speaker crossover network, this is one reason why some speakers sound better with certain amplifiers than others.

Cone Oscillation Damping

Another reason for many matching anomalies and a further undesirable side effect of the crossover circuit, is its effect on amplifier damping. When the signal ceases the cone tends to oscillate to and fro for several cycles before coming to rest due to the springiness of its suspension. Spurious sounds are thus generated.

These cone oscillations generate currents in the coil, which set up a magnetic field around it that opposes the cone motion. The oscillations are thus self-dampening. The same effect tends to reduce peaks in the speaker frequency response. If the cone motion at one frequency is greater than that of the others for the same input, the induced current is also larger. Thus the opposing force is greater and the excess cone motion is reduced.

Now the only path for the induced current is through the amplifier output stage. As the damping depends on this current, it also depends on the total resistance it has to encounter, the lower the resistance the greater the damping current.

A figure is often quoted in amplifier specifications for *damping factor*. This describes the ability of the amplifier to dampen spurious speaker cone motion

by providing a low resistance shunt path. Output stage internal resistance is much lower than the specified output impedance, and the damping factor is the ratio between the two. Factors of 20 are nowadays considered low, and some go as high as 1,000. Taking a typical damping factor of 100 and the usual 8R load, this gives an internal resistance of $8 \div 100 = 0.08R$. Connected directly across a driver, such a low resistance permits a high damping current and very effective control of spurious cone motion.

However, when a crossover network is in circuit, each driver has at least one reactive component in series, possibly more, and often as we have seen, resistance as well. These may represent a series impedance of several ohms and make nonsense of those very low-resistance high damping factors. The result is that damping is severely impaired.

So, the crossover produces phase anomalies, spurious oscillation, and reduces the control over cone overshoot and minor resonances. To our question as to whether crossover networks are a necessary evil, the answer would thus appear to be positive. But is it? Undoubtedly it is an evil but is it really *necessary*?

Dispensing With The Crossover

Before considering this, we can first make the point that the fewer the drivers, the fewer the crossover components and the fewer the problems. One well known manufacturer gave demonstrations of a range of speakers a few years ago. They all sounded quite good except one which had a distinctly raw sound. This was their top of range model with three drivers; all the others had two.

At one time makers vied with each other as to the number of drivers they fitted. Front covers were made detachable, ostensibly to minimise HF loss, but in reality for the owner to show off to all and sundry, the drivers so exposed. A '*my-speakers-have-more-drivers-than-yours*' syndrome was the order of the day. This practice seems to be dying out, the two-driver systems are the most common at present.

Can the crossover be completely eliminated? There are three possibilities. The first is to divide the audio signal into two bands *before* the power amplifier. This can be easily done and it eliminates all the problems that arise from splitting it at the loudspeaker. The snag is that it requires two amplifiers per channel, and the loudspeaker must provide connections for both drivers separately. Not all speakers do. Different sensitivities for each driver can readily be compensated by adjusting the gain of each amplifier.

The second is to use a piezo tweeter, a range of which is made by Motorola. Being capacitive, they have the characteristic of having a rising impedance as the frequency falls. It is typically 1,000R at 1kHz, and increases exponentially below that. In one model the roll off is at 24dB per octave below 3kHz, which is equivalent to a fourth-order filter. At bass frequencies the impedance is so high that the unit can be connected directly across the amplifier and the bass driver without any crossover, and without damage to it.

Frequency response is up to 40kHz, higher than most super tweeters, and even higher than Nipper would appreciate. More importantly, the harmonic distortion is very low for a transducer, at a mere 0.75%.

If it was required to restrict the HF output of the bass unit to reduce mutual interference, a simple first order crossover, i.e. a series inductor could be included. This would impair its magnetic damping, but would avoid the other vices of the higher order circuits.

Single Driver

Both these solutions suffer from the same drawback, the phasing and interference effects of running two adjacent drivers in the same plane. As it is not possible to arrange a totally sharp cut-off, both reproduce the same frequencies around the crossover point. One answer is the co-axial speaker in which the treble unit is mounted in front of the bass one. The sound produced is coherent, and the phasing does not vary with the off axis angle.

As a result of this, a single capacitor in series with the treble unit is likely to be all that is required by way of a crossover circuit. There can be masking of mid frequencies by the tweeter unit, and sound reflection between the units. These effects can be minimised by careful physical design.

The alternative is to use a single full-range driver. There is an increasing range of these now available. Some have a frequency response from 40Hz-16kHz so there is little lost except at the extreme ends of the spectrum, but many two-unit loudspeakers do no better.

Full-range drivers make use of an effect that has for years been considered a drawback with the moving-coil speaker, that is cone flexure. Ideally, the cone should act like a rigid piston, all parts moving backwards and forwards in unison. Any stroboscopic examination of paper loudspeaker cone will reveal that this does not happen: ripples move out from the

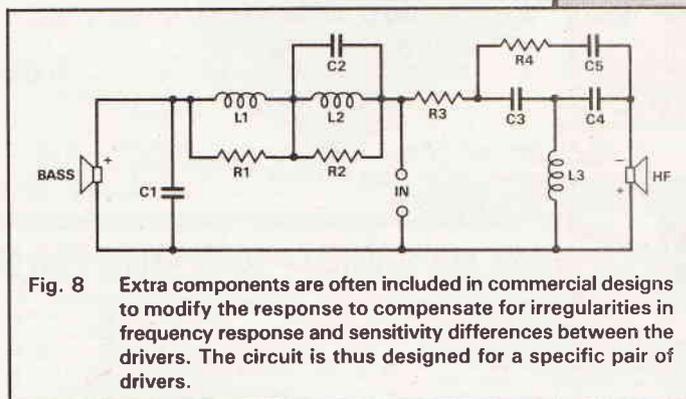


Fig. 8 Extra components are often included in commercial designs to modify the response to compensate for irregularities in frequency response and sensitivity differences between the drivers. The circuit is thus designed for a specific pair of drivers.

centre and back again, some parts flap backwards while others are going forward, in fact it is a wonder that the reproduced sound bears any resemblance to the original at all!

To avoid this, cone have been made from various rigid materials such as metal and polystyrene. These have tended either to be too heavy and so unresponsive to transients and high frequencies, or have added coloration. In spite of all the progress in materials over the years, paper pulp of various types continue to be used for the best subjective uncoloured results.

The full-range speaker has a cone with a curved contour which actually encourages flexure and also controls cone break-up. At high frequencies, the central area moves independently of the rest which has too great an inertia to respond. It thus behaves as a small tweeter. At mid frequencies, a larger area comes into play, while at the bass the whole cone responds. The effect is termed *controlled flexure* and is a prime example of turning a vice into a virtue! In effect there is a separately operating tweeter, mid-range unit and bass driver, without any crossover network, and with true coherent radiation from a single source.

One objection to the full-range driver is that of doppler distortion. The 'tweeter' being the centre of the cone, is moving backwards and forwards at bass frequencies that are being reproduced at the same



DESIGN

time, and so the HF is modulated by them. Critical listening tests suggest though that a bass cone excursion of 20mm is the lower limit below which doppler distortion cannot be detected. This is unlikely to be even approached in domestic hi-fi systems. Using the comparison of the doppler effect heard from a speeding ambulance siren as it

speakers and conditioned into believing that the more the better, cannot accept that a single-unit speaker is anything but a maker's cut-price exercise. In turn manufacturers dare not risk producing speakers that would be so regarded and unlikely to sell.

Of course, single-driver speaker enclosures need to be properly designed and constructed to give first-class results, just as the multi-unit variety. The cheap lo-fi unit using an ordinary speaker in a box as supplied as extension speakers or with low cost players, is no criterion of the results that can be obtained with a good single unit design. For such a design readers are referred to ETI July 1987, which described the Kapellmeister transmission line speaker.

So in answer to our original question, are crossover networks a necessary evil? We can reply no, they are indeed an evil, but they are not necessary!

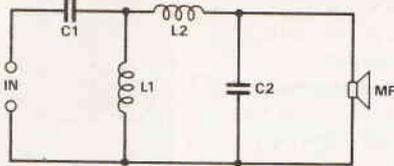


Fig. 9 Circuit of second-order bandpass filter for feeding the mid-range unit.

passes, normal domestic cone excursions are equivalent to an ambulance siren at walking pace.

Doppler effect is thus no real obstacle to the use of single full-range drivers. The biggest obstacle is the public who, having been brought up with multi-driver



19" RACK MOUNTING EQUIPMENT CASES

This range of 19" rack cases features satin black finished 16SWG (1.5mm) steel front panels (no fixing holes visible), with the rear box assembly constructed from 20SWG (9mm) steel. The standard units are 10" (254mm) deep.

NEW FOR 1990 19" project cases only 4" (101mm) deep and are available in the following popular sizes:

PROJECT CASES

Type	Height	Price
PU1	1 3/4" (44mm)	£16.50
PU2	3 1/2" (88mm)	£18.50
PU3	5 1/4" (133mm)	£20.50
PU4	7" (178mm)	£22.50
PU6	10 1/2" (266mm)	£26.50

EQUIPMENT CASES

U1	1 3/4" (44mm)	£20.70
U2	3 1/2" (88mm)	£24.15
U3	5 1/4" (133mm)	£27.60
U4	7" (178mm)	£29.90

Delivery included (UK only).

All prices include VAT.

BLANKING PANELS, RACKING CONSOLES and RACK CABINETS are also available.

Please send SAE for details

Tel: 0275 823983 for Access/Visa Sales or cheque

with order to:

RACKZ PRODUCTS

PO Box 1402 Mangotsfield, Bristol, England, BS17 3RY



Millions of quality components at lowest ever prices.

Mail order only.

Send 30p stamped addressed label for catalogue/clearance lists. All inclusive prices **NO** post, packing, VAT etc to work out and add on.

Brian J Reed Electrical
6 Queensmead Avenue, East Ewell
Epsom, Surrey KT17 3EQ
Tel: 0(7)1 223 5016

HART AUDIO KITS — YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI



HART KITS gives you the opportunity to build the very best engineered hi-fi equipment there is, designed by the leaders in their field, using the best components that are available.

With a HART KIT you have direct access to the friendly HART service, you are not dealing through, or paying for, any middlemen.

Every HART KIT is not just a new equipment acquisition but a valuable investment in knowledge, giving you guided hands-on experience of modern electronic techniques. Telephone or write for your FREE LISTS giving full details of all our Kits, components and special offers. Here are a few selected items:

AUDIO DESIGN 80 WATT POWER AMPLIFIER



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hi-fi system. This kit is your way to get 5x performance for a few tenths of the cost!

Featured on the front cover of 'Electronics Today International' this complete stereo power amplifier offers World Class performance allied to the famous HART quality and ease of construction. John Linsley Hood's comments on seeing a complete unit were enthusiastic: "The external view is that of a thoroughly professional piece of audio gear, neat elegant and functional. This impression is greatly reinforced by the internal appearance, which is redolent of quality, both in components and in layout."


The standard amplifier comes with the option of a stereo LED power meter and a versatile passive front end giving switched inputs, and ALPS precision, low-noise volume and balance controls. A new relay switched front end option also gives a tape input and output facility. This means that for use with tuners, tape and CD players, or indeed any other flat inputs the power amplifier may be used on its own, without the need for any external signal handling stages. Slave and 'monoboc' versions without the passive input stage and power meter are also available. All versions fit within our standard 420x260x75mm case to match our 400 Series Tuner range. ALL six power supply rails are fully stabilised, and the complete power supply, using a toroidal transformer, is contained within a heavy gauge aluminium chassis/hastank fitted with IEC mains input and output sockets. All the circuitry is on a proper printed circuit with low-resistance blade connectors for the six stabilised DC outputs. HART KITS don't leave you to fester a few stabilised DC outputs on the main chassis and wire the power supply the hard way! HART wiring is even pre-terminated, ready for instant use! Remember with a HART KIT you get the performance you want at the price quoted through proper engineering design and the right components. We do not insult your intelligence by offering a kit at what seems a fair price and then tell you that you have to spend three times as much to get an upgraded model!

RLH10 Reprints of latest 'Audio Design Amplifier' articles £2.70
K1100CW HART Construction Manual with full parts lists £4.50

Why not buy the reprints and construction manual to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.

SPECIAL OFFERS FOR THE NEXT MONTH. All orders for complete kits will get the ALPS Precision Pots in the Passive Input Stage included FREE. We can also include the new Relay Switched Input Stage, normally £57.28, for only £30!

ALPS PRECISION LOW-NOISE STEREO POTS

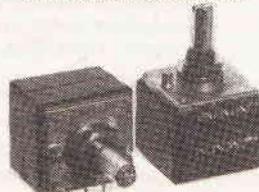

Now back in stock, the last batch sold out months ago! Exciting range of precision audio pots in values to cover most quality amplifier application. All are in 2-gang stereo format, with 20mm long 6mm dia. steel shafts, smooth rotation type with no indentations. Now you can throw out those noisy ill-matched carbon pots and replace with the real hi-fi components only used selectively in the very top flight of World class amplifiers, and HART Kits! The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability. Values available are 10K and 100K. 100K in and 10K Special Balance. (Zero loss in centre position). Our prices are incredibly low for pots of this quality due to large purchases for our quality kits.

2-Gang Lin.	£7.59
2-Gang Log.	£8.67
2-Gang Special Balance, zero crosstalk and zero centre loss	£9.40


LINSELY HOOD 400 SERIES SUPER HIGH QUALITY AM/FM TUNER SYSTEM

This ultra high quality analogue tuner system is the ideal companion to the 80W Audio Design Amplifier in any ultimate hi-fi setup, with case size, front plate layout and even control pitches unified for stacking. Like the 80W Audio Design Amplifier this is your route to ultimate performance at incredibly modest cost! Two designs by John Linsley Hood make up this combination of his ultra high quality FM tuner and stereo decoder and the Synchronyne AM receiver. Novel circuit features in the FM section include a ready built pre-aligned front end, phase locked loop demodulator with a response down to DC and advanced sample and hold stereo decoder together making a tuner which sounds better than the best of the high-priced exotica but, thanks to HART engineering, remains very easy to build and set up. The Synchronyne AM Section with its selectable bandwidth provides the best possible results from Long and Medium wave channels, so necessary in these days of split programming. If you want the very best in real Hi-Fi listening then this is the tuner for you. Since all components are selected by the designer to give the very best sound this tuner is not cheap, but in terms of its sheer sound quality it is incredible value for money. To cater for all needs AM only and FM only versions are available as well as the full AM/FM model, with any unit being upgradable at any time. For further details see our fully illustrated lists.

RLH7 Reprints of articles describing the 'Synchronyne' Section	£2.60
INS450 Construction Manual for 'Synchronyne' AM Section	£2.90
RLH6 Reprints of 3 articles covering the FM Tuner Section	£2.70
INS400 Construction Manual for FM Section	£4.90

Don't forget you can buy the construction manual and reprints to see how easy it is and the cost will be credited IN FULL when you buy your kit.

HIGH QUALITY REPLACEMENT CASSETTE HEADS

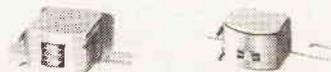

Do your tapes lack trouble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard inductances and mounting make fitting easy on nearly all machines and our TCI Test Cassette helps you set the azimuth spot on. As we are the actual importers you get prime parts at lower prices, compare our prices with other suppliers and see! All our heads are suitable for use with any Dolby system and are normally available ex stock. We also stock a wide range of special heads for home construction and industrial users.

HS16 Sendaat Alloy Stereo Head, high quality head with excellent frequency response and hyperbolic face for good tape to head contact	£17.86
HC40 NEW RANGE High Beta Permalloy Stereo Head, Modern space save design for easy fitting and low cost. Suitable for chrome metal and ferric tapes, truly a universal replacement head for hi-fi decks to car players and at an incredible price too!	£6.65
HX100 Special Offer Stereo Permalloy Head	£2.85
HRP273 Downstream Monitor Stereo Combination Head	£44.39
HQ551 4-Track Record & Play Permalloy Head for auto-reverse car players or quadraphonic recording	£16.79
HSS24 Standard Erase Head	£2.59
SM166 2/2 AC Erase Head, Standard Mount	£12.60
HS9510 2/4 Stereo DC Erase Head	£8.70
HQ751E 4/4 AC Erase Head, tracks compatible with HQ551	£57.06

REEL TO REEL HEADS	
998R 2/4 Record/Play 110mH	£13.34
298E 2/4 Erase Head 1mH	£11.96

TAPE RECORDER CARE PRODUCTS

HART TCI TEST CASSETTE. Our famous triple purpose test cassette. Sets tape azimuth, VU level and tap speed	£5.36
DEM1 Mains Powered Tape Head Demagnetiser, prevents noise on playback due to residual head magnetiser	£4.08
DEM115 Electronic, Cassette Type, demagnetiser	£8.61

Our new SUMMER '90 List is FREE. Send for your copy now. Overseas customers welcome, please send 2 IRCs to cover surface post, or 5 for Airmail.

We now accept inland and overseas orders by post or telephone on all Access/Mastercharge and Visa credit cards.

Please add part cost of carriage and insurance as follows:

INLAND:
Orders up to £20 — £1; Orders over £20 — £2.50; Next day — £9

OVERSEAS:
Please see the ordering information with our lists.

QUALITY AUDIO KITS

24hr SALES LINE
(0691) 652894

ALL PRICES INCLUDE VAT




THE ORIGINAL SURPLUS WONDERLAND!

MONITORS

MONOCHROME MONITORS

THIS MONTH'S SPECIAL!

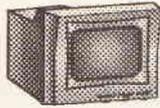

There has never been a deal like this one! Brand spanking new & boxed monitors from NEC, normally selling at about £140! These are over-engineered for ultra reliability. 9" green screen composite input with etched non-glare screen plus switchable high/low impedance input and output for daisy-chaining. 3 front controls and 6 at rear. Standard BNC sockets. Beautiful high contrast screen and attractive case with carrying ledge. Perfect as a main or backup monitor and for quantity users! **£39.95 each (D) or 5 for £185 (G)**

CALL FOR DISCOUNTS ON HIGHER QUANTITIES!

Zenith ZVM-1240-EA brand new & boxed 12" amber flat screen with optional swivel and tilt base. Sunflex filter with dark tint. Standard TTL PC compatible. 18 mhz bandwidth. Very attractive "state of the art" tapered grey case. Standard 9 pin D plug (supplied) on 1 metre cord and mains cord terminated with IEC connector. 240 volts complete with operations manual. An absolute gift at: **£59 (D) 10/£500 (G). Swivel/tilt base £4.95.**

Very high resolution, fully cased 14" green or amber screen monitor with non-glare screen and swivel/tilt base. The very latest technology at the very lowest price! Fully compatible and plug compatible with all IBM PCs and clones fitted with a high res Hercules or equivalent card! Enables superb graphics and resolution, all at a give away price. Has many extra features including aux +5 & 12v DC outputs to power at least 2 disk drives. If your PC power supply is getting hot! Supplied BRAND NEW and boxed. State whether amber or green screen required.

Amber£79 Green£69 (E)

Wang green screen 12" chassis monitor with composite video input. Adjustable for tilt. Requires 12 vdc. Brand new and boxed in perfect condition. **Only £39 each or 2 for £75 (F)**

Motorola M1000-100 5" black & white compact chassis measuring only 11.6h x 12w x 2.2D. Ideal for CCTV or computer applications. Accepts standard composite or individual H & V syncs. Needs 12vdc at only 0.8a. Some units may have minor screen blemishes. Fully tested with 30 day guarantee and full data. **£29.00 (C)**

Fully cased as above in attractive moulded desk standing swivel. Dim 12 x 14.5 x 26cm. **£39.00 (C)**

JVC 751 ultra compact chassis monitor for 12vdc 0.7a. Dim 11 x 14 x 18cm. Simple DIY data included to convert to composite video input. Full data. **BRAND NEW £65.00 (B)**

20" Black & white monitors by Aztek, Cotron & National. All solid state, fully cased monitors ideal for all types of AV or CCTV applications. Standard composite video inputs with integral audio amp and speaker. Sold in good used condition - fully tested with 90 day guarantee. **£85.00 (F)**

COLOUR MONITORS

Decca 16" 80 budget range colour monitor. Features a PIL tube, beautiful leak style case and guaranteed 80 column resolution, features usually seen only on colour monitors costing 3 times our price! Ready to connect to most computers or video outputs. 75Ω composite input with integral audio amp & speaker. Fully tested surplus, sold in little or hardly used condition with 90 day full RTB guarantee. Ideal for use with video recorder or our Telexbox ST, and other audio visual uses. **£99 (E) 3/£275 (G)**

HI-DEFINITION COLOUR MONITORS

Brand new Centronic 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 Mhz bandwidth. A super monitor in attractive style moulded case. Full 90 day guarantee. **Only £149 (E)**

20", 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attractive leak style case. Perfect for Schools, Shops, Disco, Clubs. In EXCELLENT little used condition with full 90 day guarantee.

20"....£155 22"....£170 26"....£185 (F)

COMPUTER SYSTEMS

TATUNG PC2000. Big brother of the famous Elstein. The TPC2000 Professional 3 piece system comprises: Quality high resolution Green 12" monitor. Scriptured 92 key keyboard and plinth unit containing Z80A CPU and all control circuits. PLUS 2 integral TEAC 5.25 80 track double sided disk drives. Generous other features include dual 8" IBM format disk drive support. Serial and parallel outputs, full expansion port, 64K ram and ready to run software. Supplied complete with CPM, Wordstar and Basic. Brand new and covered by our famous 90 day guarantee and backup. Normal price of this unit is over £1400! **Our price only£299 (E)**

V22 1200 BAUD MODEMS

We got a tremendous buy on further stocks of this popular Master Systems 2/12 microprocessor controlled V22 full duplex 1200 baud modem - we can now bring them to you at **half last advertised price!** Fully BT approved unit, provides standard V22 high speed data comm, which at 120 ops, can save your phone bill and connect time by a staggering 75%! Ultra slim 45 mm high. Full featured with LED status indicators and remote error diagnostics. Sync or Async use; speech or data switching; built in 240v mains supply and 2 wire connection to BT. Units are in used but good condition. Fully tested prior despatch, with data and a full 90 day guarantee. What more can you ask for - and at this price! **ONLY £69 (D)**

IBM KEYBOARD DEALS

A replacement or backup keyboard, switchable for IBM PC, PC-XT or PC-AT. LED's for Caps, Scroll & Num Locks. Standard 84 keyboard layout. Made by NCR for the English & US markets. Absolutely standard. Brand new & boxed with manual and key template for user slogans on the function keys. Attractive beige, grey and cream finish, with the usual retractable legs underneath. A generous length of curly cord, terminating in the standard 5 pin DIN plug. A beautiful clean piece of manufacturers surplus. What a deal! **£39 (B) 5/£175 (D)**

Brand new and boxed 84 key PC/XT type keyboards in standard IBM grey with very attractive mottled finish and "clacky" solid feel keys. 10 function keys on side. English layout and £ sign. Green LEDs for Caps, Scroll & Num locks. **£29.95 (B) 5/£135 (D)**

CALL FOR DISCOUNTS ON HIGHER QUANTITIES!

FLOPPY DISK DRIVES BARGAINS GALORE!

NEW 5 1/4 inch from £29.95!

Massive purchases of standard 5 1/4" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from +5 & +12vdc, are of standard size and accept the standard 34 way connector.

SHUGART SA405. BRAND NEW **£29.95 (C)**
TANDON TM100-2A IBM compatible DS **£39.95 (C)**
TANDON TM101-4 80 Track DS **£49.95 (C)**
CANON, TEC etc. DS half height. State 40 or 80T **£75.00 (C)**
TEAC FD-55-F. 40-80 DS half height. BRAND NEW **£99.00 (C)**

3 1/2 INCH BRAND NEW AT £19.95!!

Never before seen price for a 3 1/2" drive. Standard size believed to be by Canon. Brand new and packaged - mint condition! 40 track SS, run from +5 & +12vdc with standard power connector. Only **£19.95 or 2 for £34.50 (B)**

CHOOSE YOUR 8 INCH!

Shugart 800/801 SS refurbished & tested **£150.00 (E)**
Shugart 851 double sided refurbished & tested **£195.00 (E)**
Mitsubishi M2894-63 double sided switchable hard or soft sectors. BRAND NEW **£250.00 (E)**

SPECIAL OFFERS!!

Dual 8" drives with 2 megabyte capacity housed in a smart case with built in power supply! **Only £499.00 (F)**
Ideal as exterior drives!

End of line purchase scoop! Brand new NEC D2246 8" 85 megabyte of hard disk storage! Full CPU control and industry standard SMD interface. Ultra hi speed transfer and access time leaves the good old ST506 interface standing. In mint condition and comes complete with manual. Only **£399 (E)**

MAINS SUPPRESSORS & FILTERS

Roxburgh SDC 021 2 amp mains RFI filter. Has an extra wide frequency range of 150 khz to 30 mhz. Can type, solder lug connection. Quality manufactured to BS 613 standards. Dims 1-1/2"D x 1-3/4"H. **£3.95 or 3 for £10 (A) 10 for £28 (B)**

Roxburgh SDA 013/25. Similar to above rated at 1-1/2 amps. Dims 1-1/2"D x 1-3/4"H. **£3.25 or 3 for £8.50 (A) 10 for £25 (B)**

Suppression Devices SO5 A10. Extra compact general purpose suppressor. Plastic moulded case with single bolt fixing and snap connectors. Rated at 230 vac 5 amps. Dims 1-3/4"L x 1-1/8"W x 5/8"H. **£3.95 or 3 for £10 (A) 10 for £28 (B)**

Belling-Lee type L1217 3 amp mains RFI filters. Has a built in mains cable (English coding), and a three pin miniature non-reversible socket and a mating plug, to go to the equipment. Ideal for those who are bugged by RF interference. Very compact. Dims 3-1/8" x 2.5" x 1.5". **£3.95 each or 3 for £10 (A)**

RECHARGEABLE BATTERIES

LEAD ACID

Maintenance free sealed long life. Type A300.
12 volts 12 volts 3 amp/hours **£13.95 (A)**
6 volts 6 volts 3 amp/hours **£ 9.95 (A)**
12 volts Cente-tapped 1.8 amp hours. RFE. **£ 9.95 (A)**
12 volts 12 volts 24 amp hours. A200. RFE. **£29.00 (B)**

NICKEL CADMIUM

Quality 12v 4ah cell pack. Originally made for the Technicolor video company. Contains 10 GE top quality D nicad cells in a smart robust case with a DC output connector. Ideal for portable equipment. Brand new. **£19.95 (B)**
Ex-equipment NICAD cells by GE. Removed from equipment and in good, used condition: D size 4ah **4 for £5 (B)**
F size 7ah **6 for £8 (B)**

SPECIAL INTEREST

Advance 6120 7 pin A3 plotter HPGL. New **£ 425**
Trio 0-18 vdc bench PSU. 30 amps. New **£ 470**
DEC VAX11/750 Inc. 2 Meg Ram DZ and full documentation, in brand new condition **£3900**
DEC VAX Station 100 **£ 295**
DEC LS/02 CPU board **£ 150**
Calcomp 1036 large drum 3 pen plotter **£ 650**
Thurley LA 160B logic analyser **£ 375**
1.5kw 115v 60hz power source **£ 950**
Tektronics 1140 NTSC TV test signal standard. **£ 875**
Sony KTX 1000 Videotex system - brand new **£ 790**
ADS 2020 VDU terminals - brand new **£ 225**
Sekonic SD 150H 18 channel Hybrid recorder **£2000**
Trend T-9-1 Data transmission test set **£ 525**
Kenwood DA-3501 laser pickup simulator **£ 350**

ANALOG to DIGITAL and DIGITAL to ANALOG CONVERTERS

Brand new and boxed Amdek ADA-200 analog to digital and digital to analog converter packed full of features: Interfaces to most popular PC's; 2 channel input & output by software selection;



Integral input/output filters and address decoder; input pre-amp; over-level detector; trigger signal detector circuit; expansion availability and more. Input level 25mv to 50v p-p. Max. sampling frequency is 44khz and input gain variable to 200 times. Designed for use with almost any personal computer, allowing conversion of analog signals to digital data for processing by the computer plus conversion back to analog signals. The 26 page manual supplied includes data on the correct connection to various CPU's including the 8080, Z-80, 6800, 6502 and 6809 families plus data and schematics for user modification of I/O filter cut-off frequencies. Complete with 50 way ribbon cable and a fraction of the regular price! **£49.95 (C)**

POWER SUPPLIES

All PSUs 220-240vac input and are BRAND NEW unless stated. Many types ranging from 3v to 10kv always in stock.
Fine OP-9619 20 watts switch mode. +5v @ 2a. +12v @ 1a. -12v @ 0.1a. 5" x 3" x 1-1/2". **£19.95 (B)**
Astec AC-8151 40 watts. Switch mode. +5v @ 2.5a. +12v @ 2a. -12v @ 0.1a. 6-1/4" x 4" x 1-3/4". **£19.95 (B)**
Greendale 19AB0E 60 watts switch mode. +5v @ 6a. ±12v @ 1a. ±15v @ 1a. RFE and fully tested. 11 x 20 x 5.5cms. **£24.95 (C)**
Conver AC130. 130 watt hi-grade VDE spec. Switch mode. +5v @ 15a. -5v @ 1a. ±12v @ 6a. 27 x 12.5 x 6.5cms **£49.95 (C)**
Boshert 13090. Switch mode. Ideal for drives & system. +5v @ 6a. +12v @ 2.5a. -12v @ 0.5a. -5v @ 0.5a. **£29.95 (B)**
Farnell G6/40A. Switch mode. 5v @ 40a. Encased **£95.00 (C)**
Farnell G24/5S. As above but 24v @ 5a. **£65.00 (C)**

COOLING FANS

Please specify 110 or 240 volts for AC fans.

3 inch AC 1 1/2" thick **£ 8.50 (B)**
3 1/2 inch AC ETRI slimline. Only 1" thick. **£ 9.95 (B)**
4 inch AC 110/240v 1 1/2" thick. **£10.95 (B)**
4 inch AC 1 1/2" thick **£ 9.95 (B)**
10 inch Round. 3/2 thick. Rotron 110v **£10.95 (B)**
62 mm DC 1" thick. No. 812 for 6/12v. 814 24v. **£15.95 (A)**
92 mm DC 12v. 18 mm thick. **£14.95 (A)**
4 inch DC 12v. 12w 1 1/2" thick **£12.50 (B)**
4 inch DC 24v 8w. 1" thick. **£14.50 (B)**

THE AMAZING TELEBOX!

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER!

Brand new high quality, fully cased, 7 channel UHF PAL TV tuner system. Unit simply connects to your TV aerial socket and colour video monitor turning same into a fabulous colour TV. Don't worry if your monitor doesn't have sound, the TELEBOX even has an integral audio amp for driving a speaker plus an auxiliary output for headphones or Hi Fi system etc. Many other features: LED Status Indicator, Smart moulded case, Mains powered, Built to BS safety specs. Many other uses for TV sound or video etc. Supplied BRAND NEW with full 1 year guarantee.

Telexbox ST for composite video input monitors. **£29.95 (B)**
Telexbox STL as ST but with integral speaker. **£34.95 (B)**
Telexbox RGB for analogue RGB monitors. **£65.95 (B)**
NOT suitable for IBM or Clone type colour monitors.
PAL overseas version please call. SECAM not available.

BRAND NEW PRINTERS

TEC Starwriter Model FP1500-25 daisywheel printer renowned for its reliability. Diablo type print mechanism gives superb registration and quality. On board microprocessor gives full Diablo/Gume command capability. Serial RS-232C with full handshake. Bidirectional 25 cps, switchable 10 or 12 pitch, 136 cpl in Pica, 163 in Elite. Friction or tractor feed. Full ASCII including E sign. Font and ribbon Diablo compatible. **£199 (E)**
DED DPG21 miniature ball point pen printer plotter mechanism with full 40 characters per line. Complete with data sheet which includes circuit diagrams for simple driver electronics. **£49 (B)**
Centronics 150 series. Always known for their reliability in continuous use - real workhorses in any environment. Fast 150 cps with 4 fonts and choice of Interfaces. **£155.00 (E)**
150-SN up to 9.5" paper. **£155.00 (E)**
150-SW up to 14.5" paper. **£199.00 (E)**

Specify whether serial or parallel required.
CALL FOR THE MANY OTHERS IN STOCK.

Visit our Shop - Technical help always on hand plus many un-advertised specials. You can buy a colour television for as little as £29! Come and join the gang at 215 Whitehorse Lane!

LARGE QUANTITIES OF OSCILLOSCOPES AND TEST GEAR ALWAYS AVAILABLE - CALL NOW!

DISPLAY

-Electronics-

MAIL ORDER & OFFICES
Open Mon-Fri 9.00-5.30
Dept ET, 32 Biggin Way,
Upper Norwood,
London SE19 3XF.

LONDON SHOP
100's of bargains!
Open Mon-Sat 9-5.30
215 Whitehorse Lane,
South Norwood,
London, SE25.

DISTEL © The Original
Free dial-up database!
1000's of items info On Line
300 bd 081-679-1888,
1200/75 bd 081-679-6183,
1200/1200 bd 081-679-8765

ALL ENQUIRIES
081-679-4414
Fax- 081-679-1927
Telex- 894502



All prices for UK Mainland. UK customers add 15% VAT to TOTAL order amount. Minimum order £10. PO orders from Government, Universities, Schools & Local Authorities welcome-minimum account order £25. Carriage charges (A)=£2.00. (B)=£4.50. (C)=£8.50. (D)=£10.00. (E)=£12.00 (F)=£17.00 (G)=Call. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guaranteed for 90 days. All guarantees on a return to base basis. We reserve the right to change prices & specifications without prior notice. Orders accepted subject to stock. Quotations willingly given for higher quantities than those listed. Bulk surplus always required for cash.



Listen to your favourite music in FM stereo using a cordless headphone. Kenelm Rawlings shows us how it can be achieved.

THE ENTERTAINER

This project was designed to effectively relay music from your hi-fi system all round the house in stereo at low cost to the builder. It's a miniature FM stereo radio station, and you control the music content of the programmes!

Listening to the Music Relay on a Personal Stereo FM radio, such as a Walkman gives you a high quality cordless headphone system, which is more effective than infra red cordless headphones. So this means you no longer have to be in the same room as your hi-fi system, and can now listen to your favourite music in any room of the house, or even in the garden.

The design of the music relay is based on easy to obtain components. The design uses an ELC1042 TV tuner as an FM VHF low power transmitter. This simplifies the design and eliminates troublesome winding of coils etc. The unit can be hooked up to any audio equipment as long as the auxiliary line outputs are used as the signal source. These can be found on many amplifiers. Sockets marked 'tape output' will also work. The unit should not be connected to the speaker terminals of your amplifier, as this will produce very distorted sound.

your hi-fi equipment. You will need phono leads to do this. They can be made up or bought ready made. All that remains now is to adjust R10 for good stereo separation. The way to do this is to adjust R10 so that the pilot LED goes out, then slowly turn R10 until it just comes on. You should now have good channel separation and a good stereo image.

Finally, the aerial can be a piece of bell cable 15cm to 70cm long. You could also use a telescopic whip aerial. The range of the unit depends on the aerial. If it is a piece of bell cable which is 30cm long the range will be about 10m. In practice the unit can be received all over the average house and even in the garden.

PARTS LIST

RESISTORS (all 1/4W 5%)

R1	18k
R2	2k2
R3,4,11,17,19	10k
R5	5k6
R6	470R
R7,8,9	220k
R10,13	100k
R12	10M
R14,20	150k
R15,21	39k
R16,18	22k
RV1	1k Miniature preset
RV2	220k Miniature preset
RV3	4.7k Miniature preset

CAPACITORS

C1,2,3,7,10	560p Ceramic, polyester
C5	150n Ceramic or polyester
C6,9	100n
C8	1n5
C11,15	5n Ceramic
C12,13,14,16	10µ 16V electrolytic
C17	100p Ceramic
C18	330p
C4,19,20	1n

SEMICONDUCTORS

IC1	LF351 or 741
IC2	4046BE
IC3	4017
IC4	4011BE
IC5	4066BE
Q1,2,3	BC109

MISCELLANEOUS

- 1 ELC1042 TV tuner.
- 1 On/Off switch.
- 2 Phono sockets.
- 8 AA size batteries.
- 2 6V 'AA' battery holders.
- 1 Plastic project case to suit.

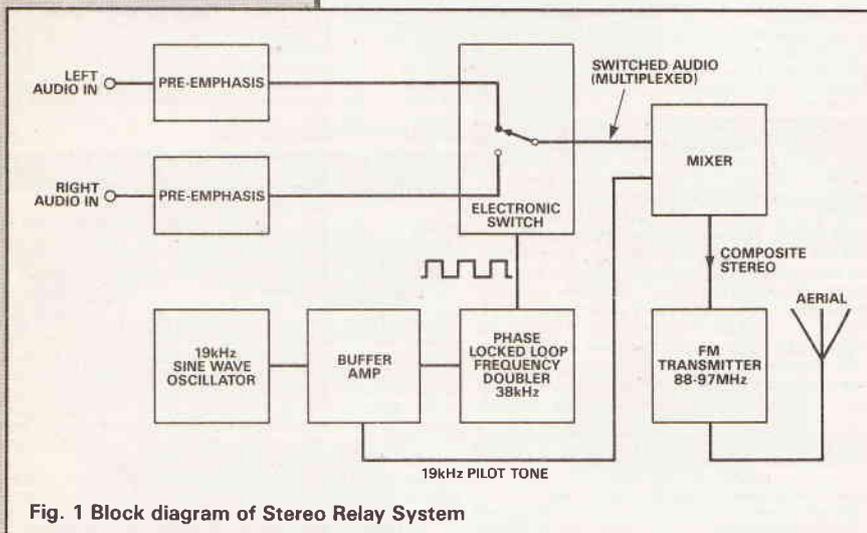


Fig. 1 Block diagram of Stereo Relay System

Testing And Trouble Shooting

When the printed circuit board is assembled and the TV tuner is wired up there are only a few simple adjustments to make. If you don't have a Digital Frequency Counter, don't panic! You can still get the project up and running.

Firstly power the project up with 12V either with batteries (8 'AA' cells) or a regulated 12V mains adaptor.

Then tune your FM stereo receiver (radio etc) anywhere between 88MHz and 97MHz. Choose a frequency that isn't being used by any local radio station. Slowly adjust R23. When a click is heard from the radio, the transmitter and receiver are at the same frequency. Now adjust R7 while having R10 set midway. At some point, the stereo pilot LED on the radio will light. If a Digital Frequency Counter is to hand, connect it to test point 1 and slowly adjust R7 until you get a reading of 19kHz. Then connect the DFM to test point 2, you should get a reading of about 38kHz. Don't worry if its not exactly 38kHz.

It is now time to connect the left and right audio inputs of the project to the auxiliary line outputs of

BUYLINES

All components should be readily available except perhaps the TV tuner. The tuner used in the project was obtained from SENDZ Components, 63 Bishopsteignton, Shoeburyness, Essex SS3 8AF for £6.

PROJECT

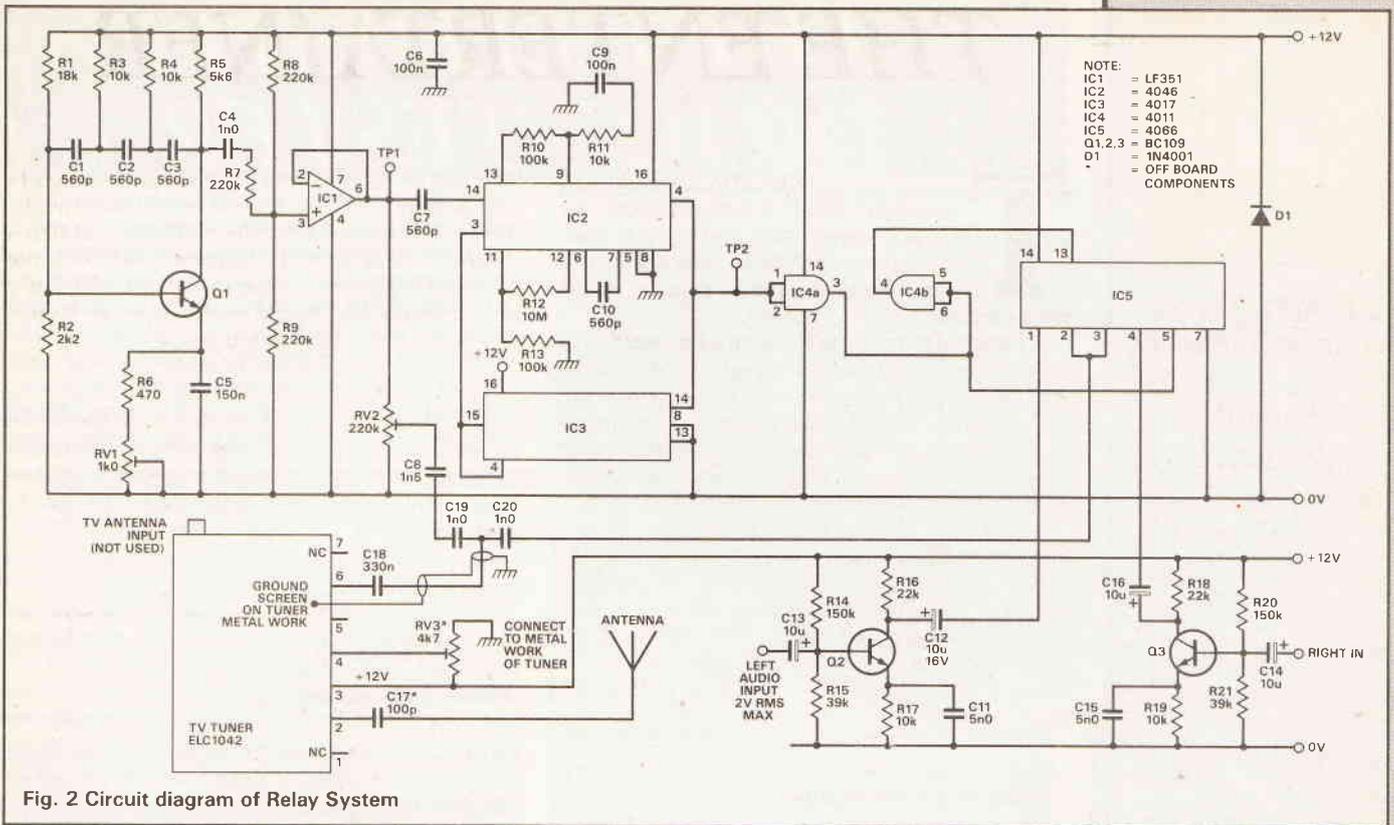


Fig. 2 Circuit diagram of Relay System

HOW IT WORKS

The circuit described is a Switching Encoder. It enables two signals, the left and right audio channels, to be transmitted by one radio carrier.

Q1 and its associated components form a phase shift oscillator, which produces a 19kHz sine wave. IC1 is used as a high impedance buffer. This prevents loading of the oscillator by other parts of the circuit. The next stage generates a 38kHz square wave carried out by IC2 and IC3. IC2 is a phase locked loop and its function is to double the 19kHz sine wave in frequency to 38kHz to provide a switching signal for IC5. IC5 is a 4066 which contains 4 electronic switches.

Only two of these switches are used.

Before the audio is multiplexed by IC5, it is given pre-emphasis (high frequencies are boosted) by Q2, Q3 and associated components. This improves the signal to noise ratio and hence the sound quality. The electronic switches within IC5 (4066) alternate left and right audio channels at a frequency of 38kHz. This produces a multiplexed stereo signal at pins 2, 3 on IC5. The signal is then mixed with the 19kHz sine wave using C8, C19, C20. It FM modulates a VHF carrier generated by the TV tuners local oscillator.


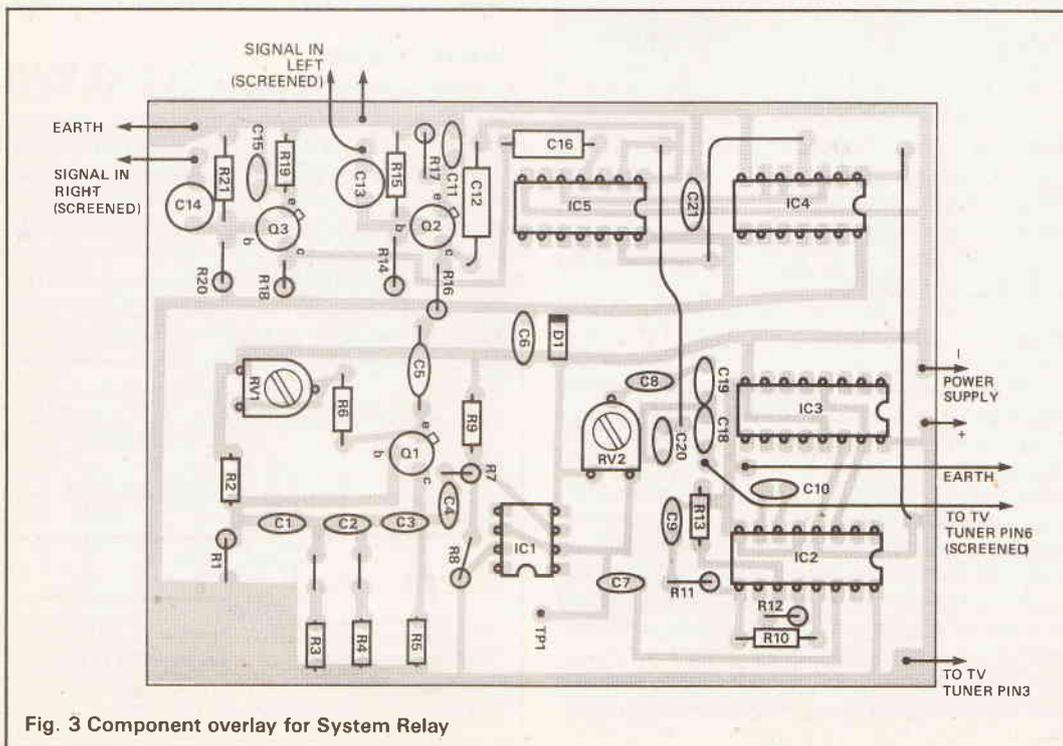


Fig. 3 Component overlay for System Relay

THE ULTIMATE DIODE TESTER

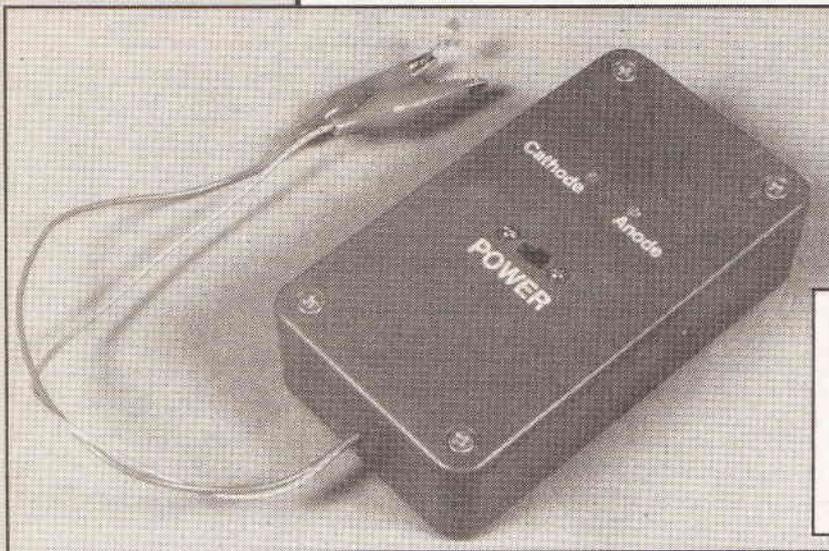

Test all your diodes with a simple and quick visual indication. Jeremy Siddons builds this simple piece of test gear.

Invariably, whilst working on various bits and pieces in the workshop, either a project or just experimenting, the need will arise for testing the odd component or two. Testing is not a means by which a good or bad component can be found, but also a means of finding out more about the component. For instance, one may use the trusty multimeter to test an old diode, by applying the test leads to the diode under test and checking the continuity on the resistance range. The diode is then turned round and the test repeated. This tells you whether the diode works or not, and of course you can then work out which leg is the cathode and which leg is the anode.

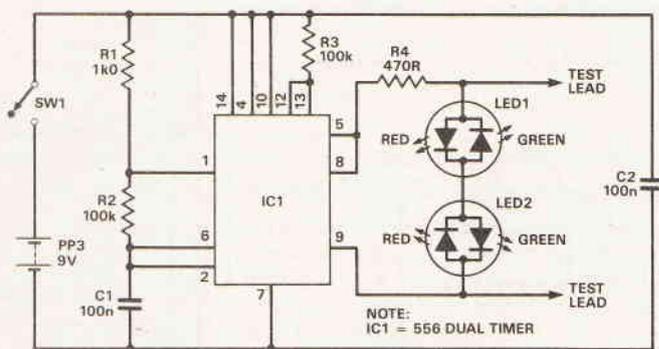


Fig. 1 Circuit diagram of diode tester.

When it comes to testing the contents of your 'bargain pack' of LEDs, the story is different. First of all, few multimeters are capable of testing LEDs. Secondly, testing an LED with a PP3 in one hand, 1k resistor in the other and LED in the other hand is a bit of hassle, especially for those of us with less than three hands. Also the LED has got to be the right way round. By this time, the thought of testing more than one is just a little bit daunting, you could be spending the time doing something much more interesting instead, like reading your favourite mag.

The device described here is simplicity itself and is capable of testing all types of diode, LED (including infra-red types) and even devices such as speakers,

bulbs, fuses and wire. Testing is carried out in one simple operation and no lead swapping is necessary. The tester consists of two bi-colour LEDs and two test leads, one green and one red, labelled 'Anode' and 'Cathode'. When the unit is connected to a diode under test, one of the LEDs will illuminate red and the other green, thus displaying the colour of the lead which is connected to the anode of the diode and the colour of the lead connected to the cathode! If the diode under test is short circuit in both directions, both

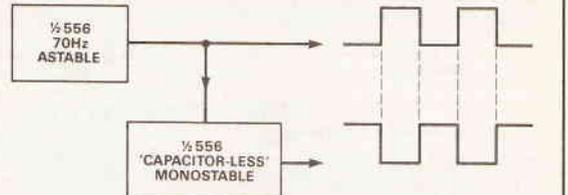


Fig. 2 Dual square wave generator.

LEDs will be extinguished. If the diode is open circuit in both directions, both LEDs will light up yellow. Checking LEDs is just as simple, the unit will illuminate any working LED without the need to know the polarity of the LED beforehand. Indeed, in the same way as above, the tester will display which test lead is connected to the anode and which is connected to the cathode. Current through the device under test will not exceed 18mA peak, 9mA average and the peak voltage across the test leads is limited to about 4V. This ensures that there is no possibility of destroying any component by either too much current or excessive reverse voltages.

The unit can also be used for simple continuity tests too: both LEDs light up yellow for an open circuit, or both LEDs off for short circuit. Furthermore speakers can be tested, a buzz will be heard from any working speaker under test.

Construction

The component overlay is shown in Fig. 3 and is quite straightforward. First insert all the resistors, then the capacitors, ensuring that they are mounted as close to the board as possible. The IC should be inserted next, taking care over correct orientation. It is preferable to mount the IC without a socket to provide a very low profile of the whole circuit, allowing the board to be fixed to the unit's panel directly using the switch mountings. The LEDs can now be mounted, the base of each LED must be 6mm from the board

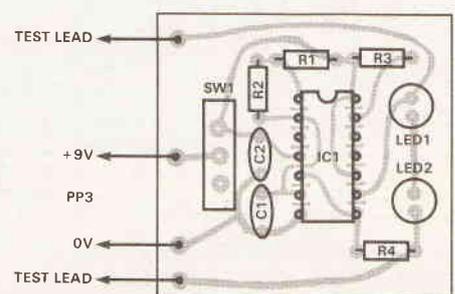


Fig. 3 Component overlay for the tester.

to allow panel mounting. The polarity of these bi-colour LEDs is very important, because their polarity directly affects their output colour under various test conditions, see Fig. 4 for details. Dual-colour LEDs do not have defined anode or cathode terminals and so connection polarity is determined from the lead length. The final component to be soldered onto the PCB is the miniature slide switch. The battery clip can then be connected and the board mounted in the box, fixed using two M2 screws through the front panel onto the switch fixing tags. Once the test leads are connected, the unit can be tested before the box is screwed together.

Testing

Ensure the test leads are not connected to anything, connect the battery and switch on. Both LEDs should light up yellow and you may notice the individual red and green segments in each LED. If the unit is not working at this stage, check the battery and connections. The LEDs will not light if the test leads are connected together and this shows correct operation so far.

Finally, connect a working diode or LED across the test leads and observe the result. One LED should revert to green and the other to red. If they are both the same colour, then reverse one of the bi-colour LEDs. If the test leads are connected to an LED, this should also illuminate regardless of its polarity. Note that the colours of the bi-colour LEDs reverse if the diode under test is reversed. The panel markings can then be applied to finish off your simple yet very useful piece of test equipment.

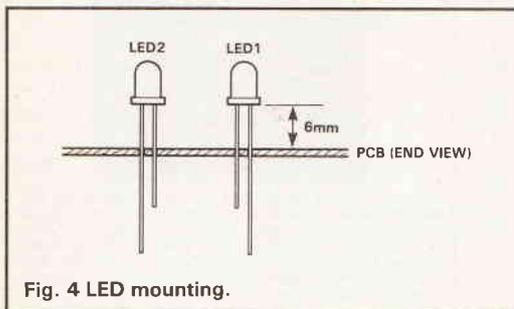


Fig. 4 LED mounting.

PARTS LIST

RESISTORS (all 1/4W 5%)

R1	1k0
R2,3	100k
R4	470R

CAPACITORS

C1,2	100n epoxy case ceramic.
------	--------------------------

SEMICONDUCTORS


LED1,2	3mm bi-colour.
IC1	NE556

MISCELLANEOUS

SW1	Sub-miniature slide switch.
PP3 battery clip,	
box to suit,	
2 x M2 screws,	
2 x croc-clips (one green, one red),	
PCB.	

BUYLINES

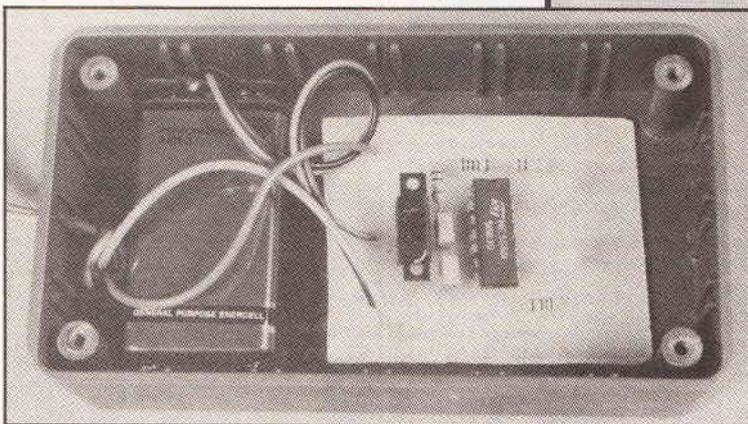All parts should be easily obtainable from your local supplier. The bi-colour LEDs can be ordered from Maplin, part number UF96E. The slide switch must be the correct size to fit the PCB, Maplin supply a suitable switch, part number FF77J.



HOW IT WORKS

The circuit diagram for the Ultimate Diode Tester is shown in Figure 1. The circuit is based around the NE556 chip which is the dual version of the popular NE555 timer IC. One half of the 556 is configured as a standard astable multivibrator working at a frequency of about 70Hz. The output of this half, pin 5, is required to be a square wave and this is ensured by making R1 very much smaller than R2. The second half of this IC is wired as a monostable circuit but with no timing capacitor. This causes the monostable to act as a simple inverter. Thus, if the output of the astable is connected to the input of this capacitor-less monostable, the output of the monostable will be a square wave precisely 180° out of phase with the output of the astable. The arrangement is shown in Fig. 2 and illustrates the action of the capacitor-less monostable. This rather strange configuration is merely a simple way of providing two square wave outputs, one the inverse of the other. In essence, I have produced a pair of outputs that provide an alternating square wave voltage from a DC source, the PP3. Pin 5, the output from the astable is connected to one of the test leads via a current limiting resistor R4. The other output, pin 9, is connected directly to the other test lead. The two bi-colour LEDs are connected in series across the test lead outputs. Because of the alternating voltage set up across these LEDs, they both illuminate as on yellow. This results from each LED oscillating red and green giving the appearance of yellow at about 70Hz.

If a diode is placed across the test leads, then for one half cycle of the square wave, the diode will be forward biased and shunt LED1 and LED2 causing them to extinguish for that half cycle. For the other half cycle, the diode under test will be reverse biased and have no effect on the illumination of LED1 and LED2 during that half cycle. This results in only one segment of each LED being illuminated at some time over the full period of the alternating voltage. If the diode was reversed, the other segment of each LED will light for the same reasons.

The series combination of the two bi-colour LEDs require about 4V in order to conduct. By limiting the voltage across the test leads to less than 4V by the application of an external diode or LED, the bi-colour LEDs will not illuminate during the half cycle in which the external diode or LED is forward biased. A short circuit on the test leads will shut LED1 and LED2 for the entire period of the square wave, resulting in no illumination at all. LED1 and LED2 in this case perform two functions, firstly to display the polarity of any applied diode, and secondly to limit the peak reverse voltage across any device under test to 4V. This is very important in the context of testing LEDs which can be damaged by reverse voltages over about 5V. This is why an LED will illuminate safely regardless of the polarity.

C2 is a supply decoupling capacitor to make sure the 556 behaves itself.

THE RTC MONITOR II

100 WATT SPEAKER KIT £60.00 + £3.50 P&P (pair)

RESPONSE: 55Hz-20kHz

BASS POLYMER CONE D: 22cm

DOME TWEETER: 14mm


OVERALL SIZE

(HWD): 382,252,204mm

RECOMMENDED AMP POWER:
10-100 watts per channel

The performance standard achieved in this compact design is distinctively superior to anything else available at the price. The drive units used are of sophisticated design and have been carefully integrated with a Complex Crossover. Stereo performance is exceptionally good with a well focussed sound stage and sharp resolution of detail. Distortion throughout the frequency range is low even at quite high power input and this gives a great sense of dynamic range and openness especially when used in bi-wired mode.

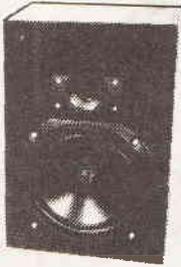Supplied with:— 2 READY CUT BAFFLES, ALL CROSSOVER COMPONENTS, 2 BASS MID-RANGE, 2 DOME TWEETERS, HOOK UP WIRE, GRILLE CLOTH, SCREW TERMINALS AND SCREWS.



ROSS MULTI TESTER

As new condition but have been returned by customers or shops so they may need some attention. Hence the price of £3.50 each plus £1.60 P&P. Order five and get the sixth one free. Postage £5.40.



LCD DIGITAL MULTI TEST METER AC DC Volts resistance and DC Amps. Most of these units are new but have been returned or rejected by the store and sold with all faults at £11.00 each. Postage £1.00. (Made by Ross Electronics).

ROSS PUSH BUTTON RADIO

Mains and battery operated.

High quality VHF/FM, Medium and Long Wave reception.

6 pushbutton selected preset stations. Fully retractable telescopic aerial.

Headphone/earphone jack socket.

Size 230H x 150W x 65D.

Ref RE-5500.

Brand new.

Listed price over £30.00.

Price £14.95 + £2.80 P&P



SHURE HIFI STEREO MAGNETIC CARTRIDGE

Fitted with an elliptical diamond stylus supplied with fitting kit and instructions. A good quality unit made to sell for well over twenty pounds due to scoop purchase, we are able to offer these at a fraction of the manufacturers price. All units are brand new and boxed. £7.20 each. If you order in multiples of five you get one free. Postage £1.30 (Made in U.S.A.)

KOSS STEREO HEADPHONES High quality light weight stereo headphones fitted 3.5mm jack with adaptor to 6.4mm jack. Ideal use HiFi or personal stereos. Made to sell for nine pounds. Our price for this unit £4.25. Postage 60p.

TV SOUND TUNER KIT



In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are quite common and that really is quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact independent TV tuner that connect direct to your Hi-Fi is a must for quality reproduction. The unit is mains operated. This TV SOUND TUNER offers full UHF coverage with 4 pre-selected tuning controls. All parts including Varicap tuner, mains transformer, PCB with IC's, capacitors and coils etc., to build the unit illustrated above; without case and scale.

£11.50 + £2.30 P&P

Case as illustrated £6.90 + £2.00 P&P

MAIL ORDER £1 BARGAIN PACKS BUY 20 GET 1 FREE

Please state pack(s) required

No.	Qty. per pack
BP015B	1 30W dome tweeter. Size 90x66mil JAPAN made
BP016	6 2200µf can type Electrolytic 25V d.c. computer grade made in UK by PHILIPS
BP017	3 33000µf 16V d.c. electrolytic high quality computer grade UK made
BP019	20 20 ceramic trimmers
BP020	4 Tuning capacitors, 2 gang dielectric a.m. type
BP021	10 3 position, 8 tag slide switch 3 amp rated 125V a.c. made in USA
BP022	5 Push-button switches, push on push off, 2 pole change over. PC mount JAPAN made
BP023	6 2 pole 2 way rotary switch
BP024	2 Right angle, PCB mounting rotary switch, 4 pole, 3 way rotary switch UK made by LORLIN
BP025	4 3 pole, 3 way miniature rotary switch with one extra position off (open frame YAXLEY type)
BP026	4 4 pole, 2 way rotary switch UK made by LORLIN
BP027	30 Mixed control knobs
BP029	6 Stereo rotary potentiometers
BP030	2 10k wire wound double precision potentiometers UK made
BP031	6 Single 100k multitune pots, ideal for varicap tuners UK made by PHILIPS
BP032	4 UHF varicap tuner heads, unboxed and untested UK made by PHILIPS
BP033	2 FM stereo decoder modules with diagram UK made by PHILIPS
BP033A	4 6"x3/8" High grade Ferrite rod. UK made
BP034	3 AM IF modules with diagram PHILIPS UK made
BP034A	2 AM-FM tuner head modules. UK made by Mullard
BP034B	1 Hi-Fi stereo pre-amp module inputs for CD, tuner tape, magnetic cartridge with diagram. UK made by MULLARD
BP035	6 All metal co-axial aerial plugs
BP036	6 Fuse holders, panel mounting 20mm type
BP037	6 In line fuse holders 20mm type UK made by BULGIN
BP038	20 5 pin din, 180° chassis socket
BP039	6 Double phono sockets, Paxolin mounted
BP041	3 2.8m lengths of 3 core 5 amp mains flex
BP042	2 Large VU meters JAPAN made
BP043	40 4V miniature bulbs, wire ended, new untested
BP044	2 Sonotone stereo crystal cartridge with 78 and LP stylus JAPAN made
BP045A	2 Mono Cassette Record and play heads
BP046A	2 606 Mains transformers, PCB mounting. Size 42x33x35
BP047	1 24V 0.3VA mains power supply. Brand new boxed UK made by MULLARD
BP047A	1 25V DC 150mA mains adaptor in black plastic case with flying input and output leads new units made for famous sound mixer manufacturer. Size 80x55x47
BP049	10 OC44 transistors. Remove paint from top and it becomes a photo-electric cell (ORP 12) UK made by MULLARD
BP050	30 Low signal transistors n.p.n., p.n.p. types
BP051	6 14 watt output transistors. 3 complimentary pairs in T066 case (Ideal replacement for AD161 and 162s)
BP052A	1 Tape deck pre-amp IC with record/replay switching No LM1818 with diagram
BP053	5 5 watt audio ICs. No TBA800 (ATEZ)
BP054	10 Motor speed control ICs, as used with most cassette and record player motors
BP055	1 Digital DVM meter I.C. made by PLESSEY as used by THANDAR with diagram
BP056	4 7 segment 0.3 LED display (red)
BP057	8 Bridge rectifiers, 1 amp, 24V
BP058	200 Assorted carbon resistors
BP059	1 Power supply PCB with 30V 4VIA transformer. MC7B18CT IC & bridge rectifier. Size 4"x2 1/4"
BP061	5 6.35mm Mono jack plugs
BP063	5 6.35mm stereo switched jack sockets
BP064	12 Coax chassis mount sockets
BP065	1 3mtr Euro-mains lead with chassis socket

MULTIBAND RADIO

VHF 54-176 MHz + AM CB BANDS 1-80
Listen to: AIR TRAFFIC CONTROL, AIRCRAFT, RADAR PUBLIC UTILITIES


RADIO AMATEURS AND MANY MANY MORE

£17.95
POSTAGE
£2.85

SQUELCH CONTROL
"RUBBER DUCK AERIAL"



HAND HELD WALKIE TALKIES

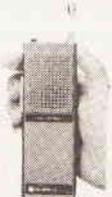

Ideal for sports or any outdoor activities. Built-in call button and separate volume control. Range 1.2km maximum. 49MHz crystal control superhet circuit with built-in condenser mic. and speaker. Unit supplied with vinyl carrying case and personal earphone.


£32.90 a pair
+ £2.60 P&P

RADIO AND TV COMPONENTS ACTON LTD
21 HIGH STREET, ACTON, LONDON W3 6NG

MAIL ORDER TERMS: POSTAL ORDERS and CHEQUES with orders. Orders under £20 add £3.00 service charge. Net monthly accounts to Schools, Colleges and P.L.C. only. ACCESS VISA. Phone orders between 9.30 & 12pm please. Overseas readers write for quote on delivery.

Phone: 071 723 8472 or 081 992 6430
Callers 323 Edgware Road, London W2. Closed Sun.
21 High St. Acton, London W3 closed Sun. Mon & Wed

30+30 WATT AMPLIFIER KIT

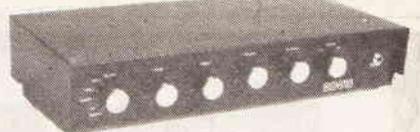

An easy to build amplifier with a good specification. All the components are mounted on the single P.C.B. which is already punched and backprinted.

■ 30W x 2 (DIN 4 ohm)
■ CD/Aux, tape I, tape II, tuner and phono inputs.

■ Separate treble and bass

■ Headphone jack

Size (H.W.D.): 75x400x195mm

Kit enclosed: case, P.C.B., all components, scale and knobs £36.80. post £3.50 (Featured project in *Everyday Electronics* April 1989 issue). Reprint Free with kit.

AMPHONIC 125+125 POWER AMPLIFIER



125 watt per channel stereo power amplifier with independent volume controls, professional 19" rack mount and silent running cooling fan for extra reliability.

Output power 125W RMS max. per channel
Output impedance 4 to 16 ohms (max. power into 4 ohms)

Sensitivity 450V at 22K ohms


Protection Electronic short-circuit and fuses

Power 220-240V a.c. 50Hz

Chassis dim 435 x 125 x 280mm

£142 + £7.00 p&p

STEREO MIXER

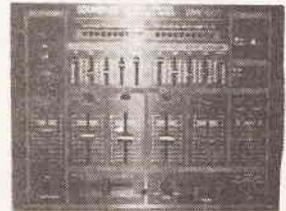

5-channel stereo disco mixer in racking case which can handle up to a total of 10 phono, line and mic inputs, switchable on front panel. Twin 5-band graphic equalizer with insert/bypass switch. Cross fader between channels 1 and 2. Mic channel with low cut filter and talkover switch. Separate L and R master controls. Output for amp, tape and headphones.

Input Mic 0.3mV 600 ohms

Phono 2.5mV 50K ohms

Outputs: Amp & Tape 1.2V

Headphone 50mV @ 75 ohms

Equalizer control frequencies 60, 250, 1k, 3.5k, 12kHz

Equalizer control range ±12dB boost or cut

Size 350 x 280 x 90mm

£118.90 + £5.80 P&P

BELT-DRIVE QUICKSTART VARISPEED DISCO TURNTABLE

- ★ Quick start ideal for scratching
- ★ Pitch control
- ★ Pop-up target lamp
- ★ Strobe lamp
- ★ Counterweighted tubular tone arm with plug-in headshell
- ★ Full manual control
- ★ Remote start/stop
- ★ 7.5kg



£112.00
+ £7.00 P&P

28.0.28V 4 AMP MAINS TRANSFORMERS

With a 5.5V at 0.5A mains input 110-240. Size 90 x 105 x 75 fitted with copper screening band; made for famous HIFI Co. £6.50 each. Postage £2.80. It's weight is 2.7kg! Brand new and unused condition.



PCB

SERVICE

September

TELEPHONE
ORDERS
may be made on
(0442)
66551
ACCESS or VISA

- E9009-1 Slide Projector Controller E
E9009-2 Ultimate Diode Tester D
E9009-3 The Entertainer G

PCBs for the remaining projects are available from the companies listed in Buylines.

Use the form or a photocopy for your order. Please fill out all parts of the form. Make sure you use the board reference numbers. This not only identifies the board but also tells you when the project was published. The first two numbers are the year, the next two are the month.

Terms are strictly payment with order. We cannot accept official orders but we can supply a proforma invoice if required. Such orders will not be processed until payment is received.

Price code	Price (inc. VAT)
C	£1.80
D	£2.50
E	£3.25
F	£4.00
G	£4.75
H	£5.50
J	£6.62
K	£7.20
L	£8.80
M	£10.60
N	£13.10
O	£15.80
P	£17.90
Q	£21.80
R	£23.90
S	£25.90
T	£29.00
U	£32.20
V	£35.80
W	£37.90
X	£40.70

- | | | | | | |
|---------|--------------------------------------|---|---------|-------------------------|---|
| E8908-4 | Digital joystick-to-mouse conversion | H | E9006-5 | Bug Spotter | E |
| E8909-1 | Twin Loop Metal Locator | H | E9007-1 | Guitar Practice Amp | G |
| E8909-2 | Trembler movement detector | D | E9007-2 | Digital Frequency Meter | M |
| E8909-3 | Field power supply (spec 3) | C | E9007-3 | Footstep Alarm | E |
| E8909-4 | Micro monitors active filter | F | E9007-4 | Transistor Tester | C |
| E8909-5 | Chronoscope auto-reset | C | E9007-5 | Decision Maker | J |
| E8910-1 | Multimeter | H | E9008-1 | AC Millivoltmeter | K |
| E8910-2 | MIDI Mapper | M | E9008-2 | Temperature Controller | N |
| E8911-1 | Smoke Alarm main board | F | E9008-3 | FM Generator | L |
| E8911-2 | Smoke Alarm power supply | F | | | |
| E8911-3 | Frequency Meter (3 boards) | O | | | |
| E8911-4 | Serial Logic Scope | L | | | |
| E8912-1 | Mains Failure Alarm | D | | | |
| E8912-2 | Surveillance PCB | D | | | |
| E8912-3 | Slide/Tape Synch | E | | | |
| E8912-4 | Pedal Power | L | | | |
| E8912-5 | Digital Noise Generator | K | | | |
| E9001-1 | 20 metre Receiver | J | | | |
| E9001-2 | Wavemaker FG | L | | | |
| E9001-3 | Motorcycle Intercom | F | | | |
| E9001-4 | Low Voltage Alarm | C | | | |
| E9002-1 | EPRM Emulator | N | | | |
| E9002-2 | Superscope Mother Board | M | | | |
| E9002-3 | Superscope CRT Driver Board | K | | | |
| E9002-4 | Superscope Timebase Board | K | | | |
| E9003-1 | Superscope Y1 input board | J | | | |
| E9003-2 | Superscope Y2 input board | J | | | |
| E9003-3 | Superscope switch generator | E | | | |
| E9003-4 | Business power amp board | L | | | |
| E9003-5 | Business power supply board | J | | | |
| E9003-6 | Business pre-amplifier board | L | | | |
| E9003-7 | Water hole | G | | | |
| E9003-8 | Super Siren | D | | | |
| E9003-9 | Val's badge | F | | | |
| E9004-1 | Bass Amplifier DC Protection | F | | | |
| E9004-2 | Bass Amplifier Graphic Equaliser | L | | | |
| E9004-3 | Bass Amplifier Micro | N | | | |
| E9004-4 | Quad Power Supply | O | | | |
| E9005-1 | Business Display | O | | | |
| E9005-2 | Phone Lock and Logger | F | | | |
| E9006-1 | Dark Room Timer | G | | | |
| E9006-2 | Telephone Extension Bell | C | | | |
| E9006-3 | Telephone External Bell | D | | | |
| E9006-4 | Fecko Box | G | | | |

**TO: ETI PCB SERVICE, READERS' SERVICES,
ARGUS HOUSE, BOUNDARY WAY,
HEMEL HEMPSTEAD HP2 7ST**

Please supply:

Quantity	Ref. no.	Price Code	Price	Total Price
----------	----------	------------	-------	-------------

Post and packing

£0.75

Total enclosed

£

Please send my PCBs to: (BLOCK CAPITALS PLEASE)

Name

Address

..... **Postcode**

CHEQUES SHOULD BE MADE PAYABLE TO ASP Ltd.

4

Ray Marston looks at LED, photodiode, and varicap diode applications in this final part of his mini-series.

MODERN DIODE CIRCUITS

The first three parts of this series looked at the basic characteristics of the junction diode and associated devices (zeners, varicaps, LEDs, etc), and then showed a whole range of practical applications of ordinary diodes, rectifiers, and zeners. This month's concluding episode rounds off the subject by looking at practical applications of LEDs, photodiodes, and varicap diodes, etc.

LED Basic Circuits

A LED (light emitting diode) is a special type of junction diode that emits a fairly narrow bandwidth of visible (usually red, orange, yellow or green) or invisible (infra-red) light, when stimulated by a forward electric current.

LEDs have typical power-to-light energy conversion efficiencies some ten to fifty times greater than a simple tungsten lamp and have very fast response times (about 0.1µs, compared with tens or hundreds of mS for a tungsten lamp), and are thus widely used as 'visual' indicators and as moving-light displays; a variety of basic LED circuits are shown in the present chapter.

COLOUR	RED	ORANGE	YELLOW	GREEN
V _f (TYPICAL)	1V8	2V0	2V1	2V2

Fig. 1 Typical forward voltages of standard LEDs at I_f = 20mA

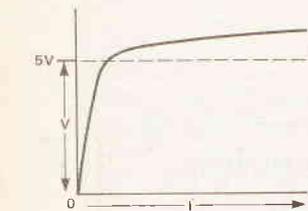


Fig. 2 A reverse biased LED acts like a zener diode

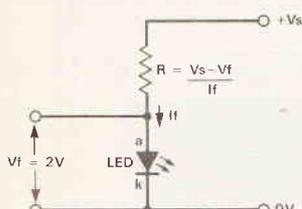


Fig. 3 Method of finding the 'R' value for a given V_s and I_f

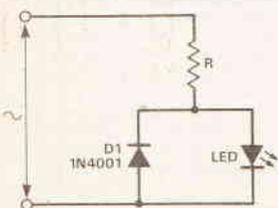


Fig. 4 Using a LED as an indicator in a low-voltage AC circuit

respectively.

The basic Figure 5 circuit can be used as a 'blown fuse' indicator by wiring it as shown in Figure 6. Normally, the circuit is shorted out by the fuse, but becomes enabled when the fuse is 'blown'; under this condition the load current is limited by the C_s value.

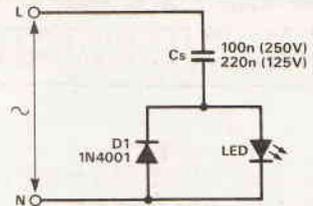


Fig. 5 Using a LED as an indicator in an AC power line circuit

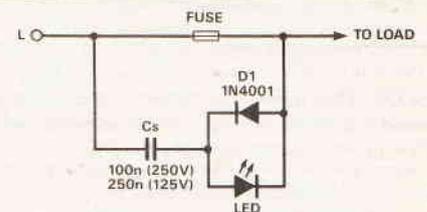


Fig. 6 AC power line 'fuse blown' indicator

Practical Usage Notes

The first practical problem that will be met when using a LED is that of identifying its polarity. Most LEDs have their cathodes identified by a notch or flat on the package, or by a short lead, as indicated in the 'outline' diagram of Figure 7. This practice is not universal, however, so the only sure way to identify a LED is to test it in the basic Figure 3 circuit. Try the LED both ways round, when it glows, the cathode is the most negative of the two terminals; always test a LED before soldering it into a circuit. (Alternatively, the Ultimate Diode Tester project, in this month's ETI!—Ed).

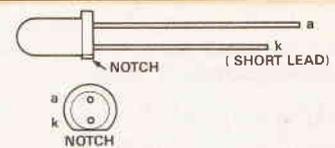


Fig. 7 Typical outline and method of recognising the polarity of a LED

Special mounting kits, comprising a plastic clip and ring, are available for fixing LEDs into PC boards and front panels, etc. Figure 8 illustrates the functioning of such a kit.

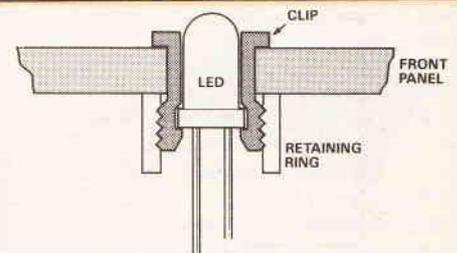


Fig. 8 CLIP and RING kit used to secure a LED to a front panel

A significant voltage (about 2 volts) is developed across a LED when it is passing a forward current, and Figure 1 shows the typical forward voltages of different coloured standard LEDs at forward currents of 20mA. If a LED is reverse biased it avalanches or 'zeners' at a fairly low voltage value, as shown in Figure 2. Most practical LEDs have maximum reverse voltage ratings in the range 3 to 5 volts.

In use, a LED must be wired in series with a current-limiting device such as a resistor. Figure 3 shows how to work out the 'R' value needed to give a particular current from a particular supply voltage. In practice, R can be connected to either the anode or the cathode of the LED. The LED brightness is proportional to the LED current; most LEDs will operate safely up to absolute maximum currents of 30 to 40mA.

A LED can be used as an indicator in an AC circuit by wiring it in inverse parallel with a normal diode, as shown in Figure 4, to prevent the LED being reverse biased; for a given brightness, the 'R' value should be halved relative to that of the DC circuit. Note that if this circuit is used with high-value AC supplies, 'R' may need a fairly high power rating; thus, if used with a 250 volt supply it will need a minimum rating of 2.5 watts at a mean LED current of 10mA. This snag can be overcome by replacing 'R' with a current-limiting series capacitor, as shown in Figure 5. Here, the C_s impedance limits the LED current to the desired value, but C_s dissipates near-zero power, since its current and voltage are ninety degrees out of phase. C_s values of 100nF and 220nF are usually adequate on 250 volt and 125 volt 50-60Hz AC lines

Most LEDs come in the form of a 'single LED' package of the type shown in Figure 7. Multi-LED packages are also available, however. The best known of these are the 7-segment displays, comprising seven (or eight) LEDs packaged in a form suitable for displaying alpha-numeric characters. So-called 'bargraph' displays, comprising 10 to 30 linearly-mounted LEDs in a single package, are also available.

Most LEDs provide only a single output colour. A few specialist devices do, however, provide 'multi-colour' outputs. These are actually 2-LED devices, and Figure 9 shows one such device that comprises a pair of LEDs connected in inverse parallel, so that the colour green is emitted when the device is biased in one direction, and red (or yellow) is emitted when it is biased in the reverse direction. This device is useful for giving polarity indication or null detection.

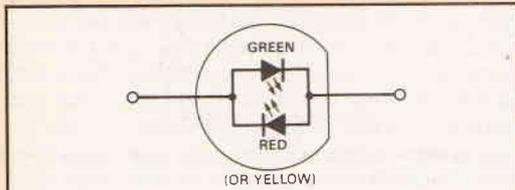


Fig. 9 'Bi-colour' LED actually houses two LEDs connected in inverse parallel

Another type of 'multicolour' LED is shown in Figure 10. This comprises a green and a red LED mounted in a 3-pin common-cathode package. This device can generate green or red colours by turning on only one LED at a time, or can generate orange and yellow ones by turning on the two LEDs in the ratios shown in the table.



Fig. 10 'Multicolour' LED, giving four colours from two junctions

A very important practical point concerns the use of 'second grade' or 'out-of-spec' devices advertised as 'Bargain Packs'. These devices often have forward volt drops in the range 3 to 10 volts, and may thus be quite useless in many practical applications. Always test these devices before use.

Multi-LED Circuits

Several LEDs can be driven from a single power source by wiring the LEDs in series as shown in Figure 11. Note that the supply voltage must be significantly greater than the sum of the individual LED forward voltages. This circuit thus draws minimal total current, but is limited in the number of LEDs that it can drive. A number of these circuits can, however, be wired in

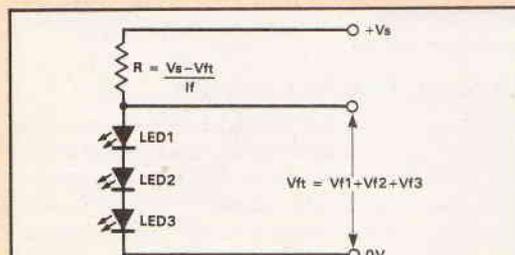


Fig. 11 LEDs wired in series and driven via a single current-limiting resistor

parallel, so that almost any number of LEDs can be driven from a single source.

Another way of powering several LEDs is to simply wire a number of the Figure 3 circuits in parallel, as shown in Figure 12. Note, however, that this is very wasteful of current (which is equal to the sum of the individual LED currents).

Figure 13 shows a 'what NOT to do' circuit. This design will not work correctly because inevitable differences in the forward voltage characteristics of the LEDs will usually cause one LED to 'hog' most of the available current, leaving little or none for the remaining LEDs.

LED-Control Circuits

The three most widely used types of visible-output LED-control circuits are (ignoring the ones used for alpha-numeric LED control) those used for LED 'flashing', for LED 'sequencing', and for LED 'dot' or 'bar' analogue-value indication.

'Flasher' circuits turn a LED repeatedly on and off, to give an eye-catching display action. They may control a single LED or may control two LEDs in such a way that one turns on as the other turns off and vice versa.

'Sequencer' circuits drive a chain of LEDs in such a way that each LED in the chain is switched on and off in a time-controlled sequence, so that a ripple of light seems to run along the chain.

Finally, analogue-value indicator circuits drive a chain of linearly-spaced LEDs, in such a way that the length of chain that is illuminated is proportional to the analogue value of a voltage applied to the input of the driver circuit, eg, so that the circuit acts like an analogue voltmeter.

Simple LED-Flasher Circuits

One of the simplest types of LED display circuit is the LED flasher, in which a single LED repeatedly switches alternately on and off, usually at a rate of one or two flashes per second. A 2-LED flasher is a simple modification of this circuit, but is arranged so that one LED switches on when the other switches off, and vice versa. To complete this look at simple LED

circuits, Figures 14 and 15 show practical examples of 2-LED flasher circuits (readers looking for more complex LED display circuits will find stacks of them in the author's 'Optoelectronics Circuits Manual', available from Heinemann Professional Publishing Ltd).

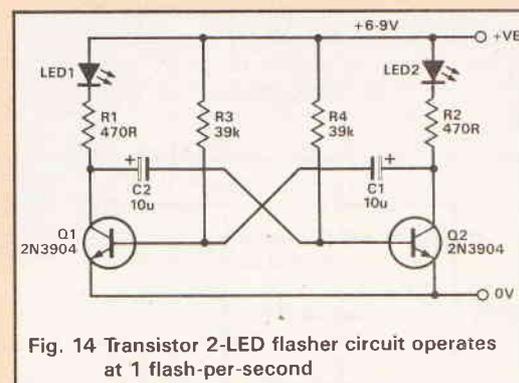


Fig. 14 Transistor 2-LED flasher circuit operates at 1 flash-per-second

Figure 14 shows the practical circuit of a 2-transistor 2-LED flasher, which can be converted to single-LED operation by simply replacing the unwanted LED with a short circuit. Here, Q1 and Q2 are wired as a 1 cycle-per-second astable multi-vibrator, with switching rates controlled via C1-R3 and

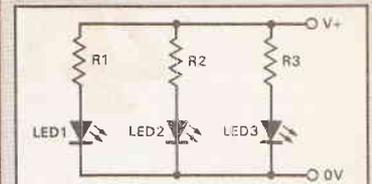


Fig. 12 This circuit can drive a large number of LEDs, but at the expense of high current

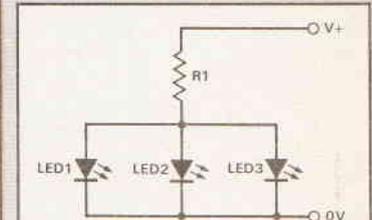


Fig. 13 This LED-driving circuit will NOT work. One LED will hog all the current

C2-R4.

Finally, Figure 15 shows an IC version of the 2-LED flasher. This design is based on the faithful old 555 timer chip or its more modern CMOS counterpart, the 7555. The IC is wired in the astable mode, with its time constant determined by C1 and R4. The action is such that output pin-3 of the IC alternately switches between the ground and the positive supply voltage levels, alternately shorting out or disabling one or other of the two LEDs. The circuit can be converted to single-LED operation by omitting the unwanted LED and its associated current-limiting resistor.

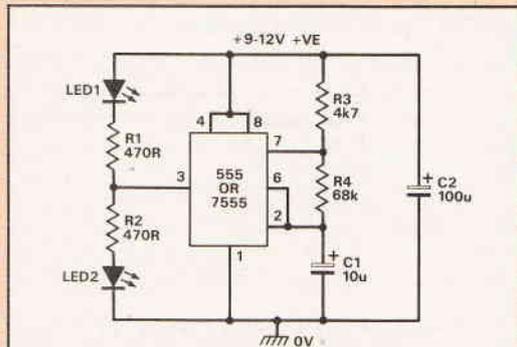


Fig. 15 IC 2-LED flasher circuit operates at about 1 flash-per-second

Photo-Diodes

When p-n silicon junctions are reverse biased their leakage currents and impedances are inherently photo-sensitive, they act as very high impedances under dark conditions and as low impedances under bright ones.

Normal diodes have their junctions shrouded in opaque material to stop this unwanted effect, but photo-diodes are specially manufactured to exploit it, and have their junctions encased in translucent material. Some photo-diodes are designed to respond to visible light, and some to infra-red (IR) light. In use, the photo-diode is simply reverse biased and the output voltage is taken from across a series-connected load resistor, which may be connected between the diode and ground, as in Figure 16a, or between the diode and the positive supply line, as in Figure 16b.

Photo-diodes have a far lower light-sensitivity than cadmium-sulphide LDRs, but give a far quicker response to changes in light level. Generally, LDRs are ideal for use in slow-acting direct-coupled 'light-level' sensing applications, while photo-diodes are ideal for use in fast-acting ac-coupled 'signalling' applications. Typical photo-diode applications include IR remote-control circuits, IR 'beam' switches and alarm circuits, and photographic 'flash' slave circuits, etc.

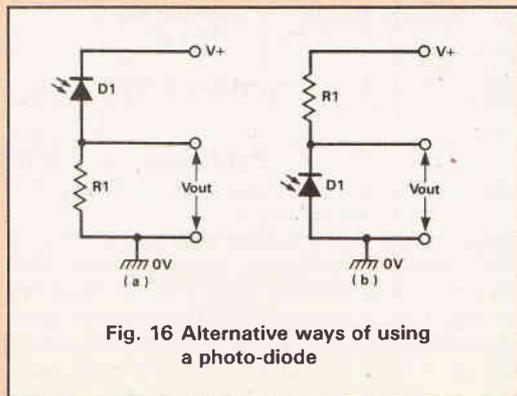


Fig. 16 Alternative ways of using a photo-diode

Photo-Transistors

Ordinary silicon transistors are made from an npn (or pnp) sandwich, and thus inherently contain a pair of photo-sensitive junctions. Not surprisingly, they are also available in photo-transistor form, and use the standard symbol of Figure 17.

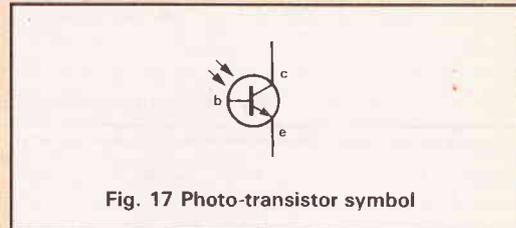


Fig. 17 Photo-transistor symbol

Figure 18 shows three different basic ways of using a photo-transistor. In each case the base-collector junction of the transistor is effectively reverse biased and thus acts as a photo-diode. In Figure 18a the transistor base is grounded, and the device acts as a simple photo-diode. In Figures 18b and 18c the base terminal is open-circuit and the photo-generated currents of the base-collector junction thus feed directly into the base and, by normal transistor action, generate a greatly amplified collector-to-emitter current that produces an output voltage across series resistor R1.

The sensitivity of a photo-transistor is typically one hundred times greater than that of a photo-diode, but its useful maximum operating frequency (a few hundred kHz) is proportionally lower than that of a photo-diode (tens of MHz). The sensitivity (and operating speed) of a photo-transistor can be made variable by wiring a variable resistor between the base and emitter, as shown in Figure 19; with RV1 open circuit, photo-transistor operation is obtained; with RV1 short circuit, photo-diode operation occurs.

Note in the Figures 16 to 19 'opto' circuits that, in practice, the R1 'load' value is usually chosen on a compromise basis, since the circuit voltage gain increases but the useful operating bandwidth decreases as the R1 value is increased. Also, the R1 value must, in many applications, be chosen to bring the photo-sensitive device into its linear operating region.

Opto-Couplers

An opto-coupler is a device housing a LED (usually an IR type) and a matching photo-transistor (or photo-diode); the two devices are closely optically coupled and mounted in a light-excluding housing.

Figure 20 shows a basic opto-coupler 'usage' circuit. The LED is used as the input side of the circuit, and the photo-transistor as the output. Normally, SW1 is open, and the LED and Q1 are thus off. When SW1 is closed a current flows through the LED via R1, and Q1 is turned on optically and generates an output voltage across R2. Note that the output circuit is thus controlled by the input one, but that the two circuits are fully isolated electrically (this is the major benefit of the opto-coupler). In practice, this simple circuit can easily be modified to give coupling of either digital or analogue signals.

Varicap Diode Circuits

Finally, to complete this look at modern diode circuits, Figure 21 shows a basic varicap diode usage circuit. The diode is reverse biased via R1 and a stable external control voltage (usually variable from zero to about 10 volts), and the varicap is coupled to an external circuit via blocking capacitor C1. The varicap capacitance is maximum at zero bias, and decreases as bias is increased.

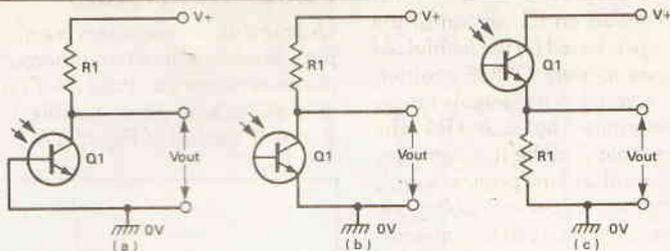


Fig. 18 Alternative ways of using a photo-transistor

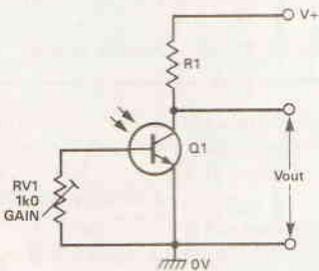


Fig. 19 Variable-sensitivity photo-transistor circuit

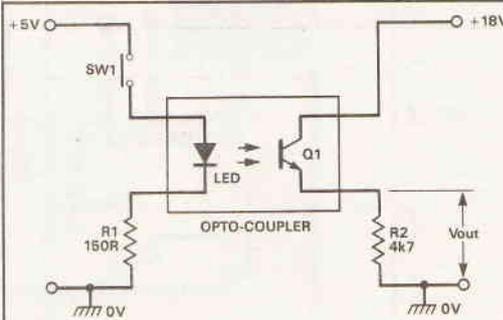


Fig. 21 Basic varicap diode usage circuit

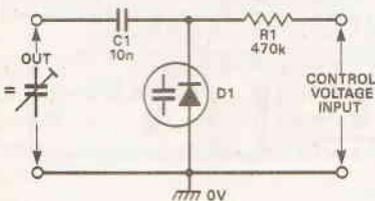


Fig. 20 Basic optocoupling circuit

Ordinary silicon diodes have maximum (zero bias) capacitances of a few pF and have typical maximum-to-minimum capacitance ratios (cap ratios) of about 2:1. Specially manufactured varicap diodes (which are often available as a matched pair) are available with maximum values of about 500pF and cap ratios of 20:1 (ie, the capacitance can be voltage-controlled from 25pF to 500pF). They are widely used in voltage-controlled tuning applications, etc.


HAM RADIO TODAY

HAM RADIO TODAY caters for both the experienced user and newcomer to amateur radio. With generally informative features, the latest news and practical projects this magazine covers all aspects of this growing field; an invaluable complement for any licenced radio amateur worldwide.

Cover Price: £1.50

Published: 1st Friday of each month

Order your copy NOW!

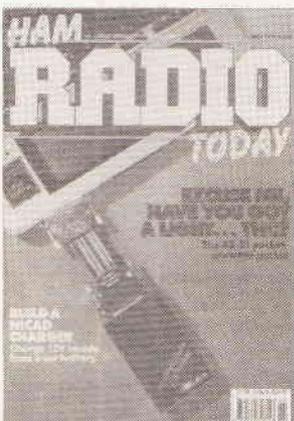

Why not subscribe?
Telephone 0442 66551
Ext 357
for further information



CB CITIZENS' BAND

CITIZEN'S BAND is the only British CB magazine and covers a wide range of topics of interest to the newcomer and the experienced user. In each issue the latest equipment is reviewed, useful practical projects are detailed and all the national and international band news is featured. Of particular interest to overseas readers are the QSL pages, articles on shortwave listening, and reports on UHF CB.

Cover Price £1.50

Published: 3rd Friday of each Month

Order your copy NOW!



Why not subscribe?
Telephone 0442 66551 ext 210
for further information






Some new corrections . . .

Digital Noise Generator (December 1989)
On Fig. 4, C4,5 should be 68n, not 68p. In the Parts List, C6,7 should be 560p, not 560n.

Power Supply Theory (April 1990)
See Read/Write for corrections to the maths.

Flatmate (May 1990)
IC5 and IC6 should be rotated by 180 degrees from the orientation shown in Fig. 4. "Mains In" should read "To Transformer". C12 is missing from the Parts List, and should be 1n0.

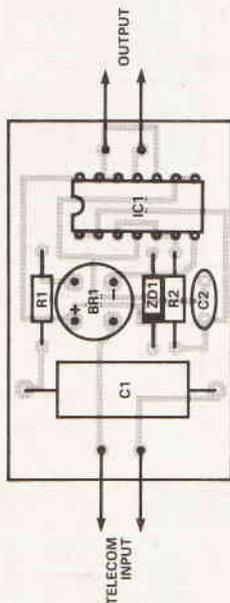
Telephone Extension Bell (June 1990)
The foil was incorrect. A correct foil is printed in this issue. Boards from our PCB service are correct. In Fig. 9, the component overlay was printed wrongly. It should be as shown below.




Testing, Testing (June 1990)
All references to \pm voltages in the section on quiescent current should be + voltages.

Digital Frequency Meter (July 1990)
The resistor connecting IC4 and IC6 should be labelled R13, not R18. The circuit diagram is correct. On the Parts List, PB1 and PB2 should be SW3 and SW4. XTAL1 is not listed; HC-49U 10MHz would be suitable.


PCB FOIL PATTERNS

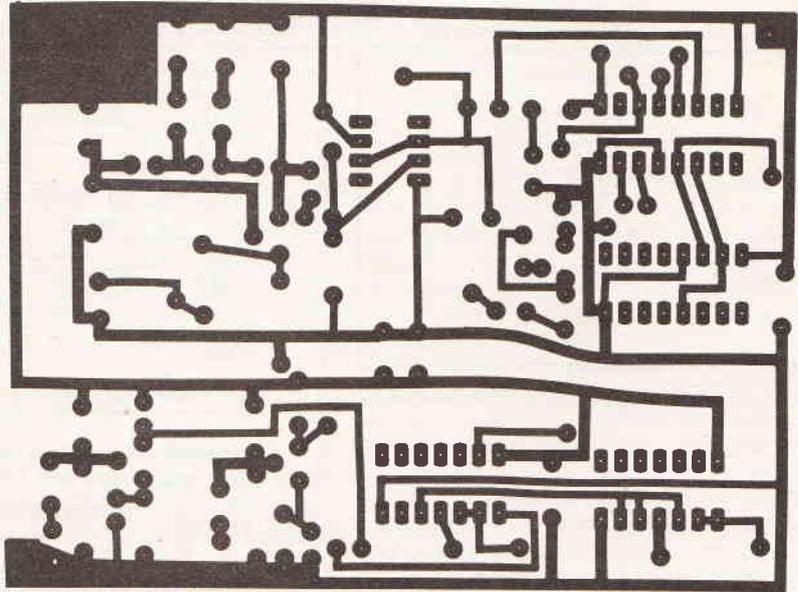


The Entertainer

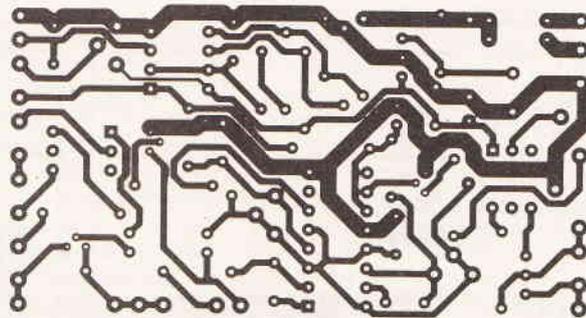

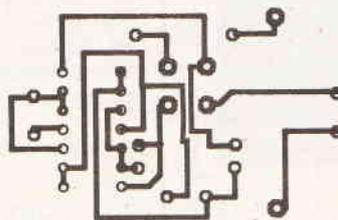Slide Projector Controller
Board designed by Tsien UK using Boardmaker 2



Telephone Extension Bell
(ETI June 90)

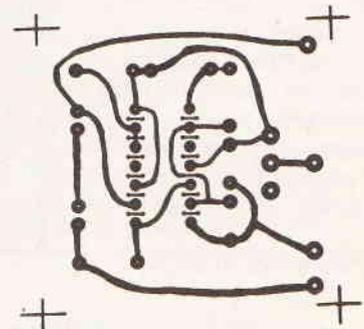

Ultimate Diode
Tester

A complete design workshop in a briefcase



IDEAL FOR:
BUSY DESIGN
ENGINEERS
SCHOOLS/COLLEGES
TRAINING
CENTRES
HOBBYISTS



COMPACT & PORTABLE

Rugged portable Bread-boarding system with its own built-in test equipment and power supplies. Size, when closed, only: 120mm High x 350mm long. Also a complete range of Breadboards is available for both standard and anti-static circuit building needs, along with jumper wire kits. Ask for price list and catalogue.

CIRCUIT MAKER I (ANALOGUE) CIRCUIT MAKER II (DIGITAL)

- * PLUG-IN BREADBOARD - OVER 3,370 TIE POINTS
- * BUILT-IN FIXED & VARIABLE POWER SUPPLIES
- * SIGNAL GENERATOR (SQUARE/SINE/TRIANGLE) 1 Hz TO 1000 Hz.
- * MULTIMETER (AC/DC 10V, 50V & 250V) DCmA, 10mA, 50mA & 250mA) (Res: x1, x10 & x1K)
- * 8 BI-COLOUR LED DRIVERS (Red-High, Green-Low,).
- * 8 LOGIC SWITCHES
- * LOGIC PROBE (Frequency up to 1 MHz - Response <0.8V & >2.0V).
- * LOUDSPEAKER (Circuit Maker I) 0.5W/1W. 8Ω.
- * ADDITIONAL FEATURES ON CIRCUIT MAKER II INCLUDING: PULSE GENERATOR & FREQ. COUNTER



EMS

Euro Market Sales
PO Box 987
STEYNING
West Sussex
BN44 3QH

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX OSCILLOSCOPE 2235 Dual Trace 100MHZ Delay Sweep	£850
PHILIPS OSCILLOSCOPE PM3217 Dual Trace 50MHZ Delay Sweep	£425
GOULD OS300 Oscilloscope Dual Trace 20MHZ	£250
GOULD 1421 Digital Storage Dual Trace 20MHZ	£750
HITACHI Dual Trace 100MHZ Delay Sweep Trig	£400
TELEQUIPMENT D83 Dual Trace 50MHZ Delay Sweep	£300
GOULD OS3000A Dual Trace 40MHZ Delay Sweep TV Trig	£275
TELEQUIPMENT T755 Dual Trace 50MHZ Delay Sweep	£275
S.E. LABS SM111 Dual Trace 10MHZ	£130
GOULD OS255 Dual Trace 15MHZ TV Trig	£180
PHILIPS PM3233 Dual Beam 10MHZ TV Trig	£150
GOULD OS250B Dual Trace 15MHZ TV Trig	£180
TELEQUIPMENT D61A Dual Trace 10MHZ	£120
SCOPEX 4D10 Dual Trace 10MHZ	£90

TEKTRONIX 2215 Dual Trace 60MHz Sweep Delay with manual, probes, front cover, pouch **only £500**

THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE

MARCONI TF2015 AM/FM 10-520MHZ Sig Gen with TF2171	£450
MARCONI TF2015 without Synchroniser TF2171	£250
MARCONI TF2016 AM/FM 10KHz-120MHZ Sig Gen with TF2173	£400
MARCONI TF2016 without Synchroniser TF2173	£175
MARCONI MOD Meters TF2300; TF2300B; TF2303 from	£100
FERRUGRAPH RT32 Record Test Set	from £200
LEADER LM186A Two Channel Millivoltmeter 5HZ-500KHZ 1mV-300V	£100
MARCONI TF2337A Automatic Distortion Meter 400HZ/1	£100
MARCONI TF2700 UNIVERSAL LCR Bridge Battery	from £125

TEKTRONIX 491 Spectrum Analyser 1.5-12.4GHZ	£1,600
SYSTRON DOWNER 1002 Sig Gen 100KHz-1GHZ	£1,250
POLARAD Sig Gen type 1105B 0.8-2.4GHZ	£500
POLARAD Sig Gen type 1106B 1.5-4.6GHZ	£500
POLARAD Sig Gen type 1170A 3.7-6.4GHZ	£500
POLARAD Sig Gen 1209A 8.95-11GH with Freq Doubler 1510 15-21GH	£750
POLARAD 1207A Sig Gen 3.7-8.4GHZ with Freq Doubler 1509 10-15.5GHZ	£750

THANDAR TA2080 Logic Analyser 20MHZ 8 Channel	£375
THURLBY PL320QMD 0-30V 2A Twice Quad Mode Digital Meters	£200
FEEDBACK FSG606 Sweep Function Generator 0.01Hz - 1MHz (P&P £7)	£175
LABGEAR CROSSHATCH GENERATOR Type CM5030.09 Crosshatch Gray Scale Blank Raster, Mains or BATTERY. Unused £18. Used £12 (P&P £3)	
TRIO RF GENERATOR Type SG402 100KHz-30MHz Unused (P&P £7) only £50	
ADVANCE S562B AM 150KHz-220MHz (P&P £7) £45 each	
FARNELL GU500 ISOLATING TRANSFORMER 240V in-240V out 500VA. Cased with lead and 13amp socket. (P&P £7) only £45 each	
VARIACS 2amps from £20 (P&P £5) 8amps from £30 (P&P £7)	
VARIOUS BENCH PSUs - Please Enquire	

TELEPHONES
Yes real dial type telephones that don't slide around the desk. Type no. 746 supplied with standard BT plug (used). Quantity discount

Used equipment - with 30 days guarantee. Manuals supplied if possible. This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for info. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage

STEWARTS OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Tel: 0734 68041. Fax: 0734 351696. Callers welcome 9am-5.30pm Mon-Fri (until 8pm Thurs)

SUMMER SALE

TEKTRONIX 475 Dual Trace 200MHZ Delay Sweep	£550
TEKTRONIX 465 Dual Trace 100MHZ Delay Sweep	£400
GOULD OS100 Dual Trace 30MHZ TV Trig	£180
COSSOR CDU150 Dual Trace 35MHZ Delay Sweep	from £100-£150
TELEQUIPMENT CT71 Curve Tracer	£175
MARCONI TF2603 RF Millivoltmeter 50KHz-1.5GHZ. 1mV-3V FSD	£75
MARCONI TF2430 Digital Freq Counter 10Hz-80MHz	£60
MARCONI AF Power Meter TF893A 20Hz-35KHz; 20mV-10W	£20
MARCONI RF Power Meter TF11521 DC-500MHz 0.5-25W. 50 Ohm	£25
FARNELL Pulse Generator System 1Hz-10MHz Single/Double	£40
KIKUSUI AVM23 AC Voltmeter Dual Chan 10Hz-500KHz. 300V-100V	£75
SOLARTRON 7045 Multimeter 4.5 digit LED 30 ranges Auto/Manual	£95
AVO 8 Multimeters with Batteries & Leads	from £35
AVO CT446 Transistor Analyser Mk2 Sullcase style With Batteries & operation instructions	£20

LABEAR COLOUR BAR GENERATOR - KG1 8 patterns (P&P £4) **only £25**

LEVELL TM3B AC Microvoltmeter 1Hz-3MHz; 5uV-500V	£60
LEVELL TM3B AC Microvoltmeter 1Hz-3MHz; 5uV-500V	£40
LEVELL Oscillator TG152 3Hz-300KHz Sine Sq	from £55
LEVELL Oscillator TG150M 1.5Hz-150KHz Sine Wave	£20
LEVELL Oscillator TG150DM 1.5Hz-150KHz Sine/Square Wave	£25
LEVELL Decade Osc TG66A 0.2Hz-1.22MHz Low Distortion	from £35
FARNELL TM2 RF Millivoltmeter 50KHz-1.5GHz; 1mV-300V	£60
LOGIC PROBE type 3300A TTL CMOS (P&P £3)	£10
MANY MORE ITEMS AT RIDICULOUS PRICES - List available	

NEW EQUIPMENT

HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz Delay Timebase	£792
HAMEG OSCILLOSCOPE HM 604 Dual Trace 60MHz Delay Sweep	£610
HAMEG OSCILLOSCOPE HM2037 Dual Trace 20MHz. Component Tester	£338
HAMEG OSCILLOSCOPE HM205.3 Dual Trace 20MHz Digital Storage	£610
All other models available - all oscilloscopes supplied with 2 probes	
BLACK STAR EQUIPMENT (P&P all units £5)	
APOLLO 10 - 100MHz Counter Timer Ratio/Period/Time Interval etc	£222
APOLLO 100 - 100MHz (As above with more functions)	£295
METECOR 100 FREQUENCY COUNTER 100MHz	£109
METECOR 600 FREQUENCY COUNTER 600MHz	£135
METECOR 1000 FREQUENCY COUNTER 1GHz	£178
JUPITOR 500 FUNCTION GENERATOR 0.1Hz-500KHz Sine/Sq/Tri	£110
ORION COLOUR BAR GENERATOR Pat/VTV/Video	£209
All other Black Star Equipment available	

HUNG CHANG DMM 7030 3 1/2 digit Hand held 28 ranges including 10mV AC/DC 0.1% Acc (P&P £4) £39.50
As above DMM 6010 0.25% Acc £33.50
Carrying Case for above £3



OSCILLOSCOPE PROBES Switchable x1, x10 (P&P £3) £11

EASY-PC, SCHEMATIC and PCB CAD

NEW VERSION! NOW DRAWS EVEN FASTER!

Only
£98.00

BRITISH
DESIGN
AWARD
1989

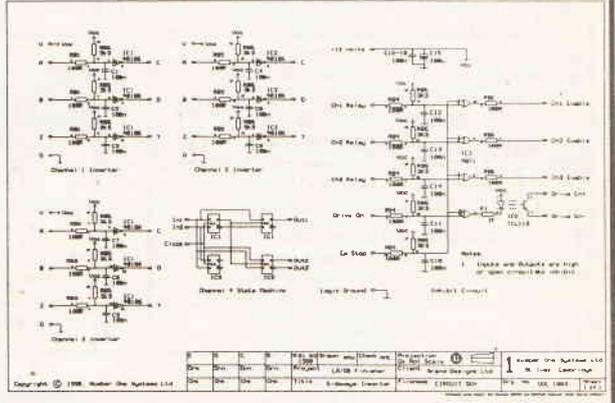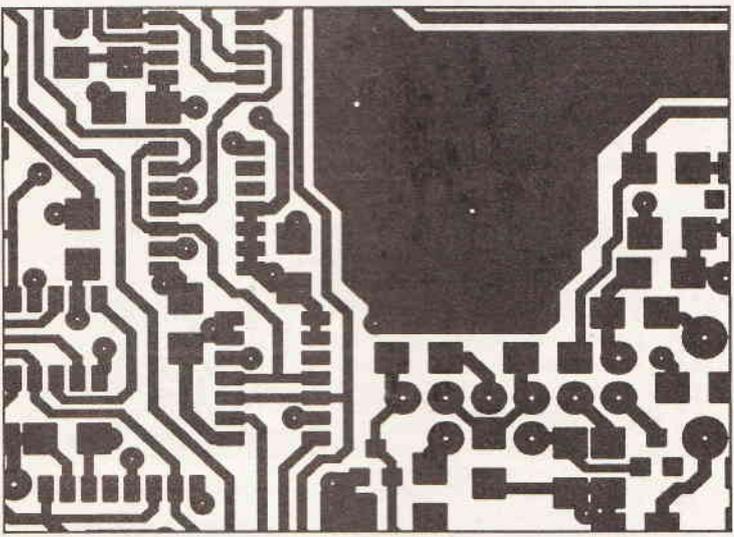

Fast Professional Quality Output at an Affordable Price

Write or 'Phone for full details:-
Number One Systems Ltd.

The CAD Specialists

REF: ETI, HARDING WAY, SOMERSHAM ROAD, ST.IVES, HUNTINGDON, CAMBS, PE17 4WR, ENGLAND.
Telephone: 0480 61778 (6 lines) ACCESS, AMEX, MASTERCARD, VISA Welcome.

Courses



NATIONAL
COLLEGE OF
TECHNOLOGY

PACKAGED SHORT COURSES

The National College of Technology (NCT Ltd) offers a range of packaged short courses in analogue electronics, digital electronics and fibres and optoelectronics for study at home or at work. The advantages are that you may

— commence at any time— work at your own pace — have a tutor (optional) and there is no travelling involved. BTEC certificates are available subject to the conditions of the award. These highly popular packed courses contain workbooks, a cassette tape, circuit board and components necessary to provide both theoretical and practical training.

Whether you are a newcomer to electronics or have some experience and simply need updating, there is probably a packaged short course ready for you. Write or telephone for details, quoting ETI to:

NCT Ltd, Bicester Hall
5 London Road, Bicester, Oxon OX6 7BU
or telephone (0296) 613067 Ext. 202

Start training now for the following courses. Send for our brochure — without obligation or Telephone us on **0626 779398**

(Ref: ETI/9/90)

Name _____

- Telecomms Tech C&G 271**
- Radio Amateur Licence C&G**
- Micro-processor**
- Introduction to Television**

Radio & Telecommunications Correspondence School
12 Moor View Drive, Teignmouth, Devon TQ14 9UN

If you organise a course that may interest ETI readers

Call **0442 66551** TODAY

TEMPERATURE MEASUREMENT

IRREVERSIBLE TEMPERATURE INDICATORS

Miniature labels 11mm x 3mm for the measurement of temperature on small components. Each strip has four temperature points: 40-43-46-49°C, 54-60-65-71°C, 77-82-86-93°C, 99-104-110-116°C, 121-127-132-138°C, 143-149-154-160°C. Supplied in packets of 45 strips priced at £3.00 plus VAT.

These and other types of indicators up to 260°C available from:

Specialised Labels, Block 'D', New Normanton Mills, Stanhope Street, Derby DE3 6QJ, England. Tel (0332) 382421, Fax (0332) 291208.

PLANS

ELECTRONIC PLANS, laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and computer graphics tablet. 150 projects. For catalogue. SAE to Plancentre Publications, Unit 7, Old Wharf Industrial Estate, Dymock Road, Ledbury, Herefordshire, HR8 2HS.

RETAIL OUTLETS

EDINBURGH

OMNI ELECTRONICS

stock a wide range of electronic components at

**174 Dalkeith Road,
Edinburgh EH16 5DX
Tel: 031 667 2611**

Open: Mon-Fri 9am-6pm, Sat 9am-5pm
Send 2x18p stamps for latest catalogue.

LONDON

CRICKLEWOOD ELECTRONICS

One of the largest component retailers in the UK. Fast and efficient, same day personal service on 'IN STOCK ITEMS'. Very competitive prices. No minimum order. Call Cricklewood Electronics now.

40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET
Tel: 081-450 0995/452 0161

SOUTH COAST

ELECTRONIC COMPONENTS are best seen at

FRASER ELECTRONICS
42 ELM GROVE ★ SOUTHSEA ★ HANTS
Telephone (0705) 815584

Barclaycard Access
COME AND BROWSE BEFORE YOU BUY

**FOR MORE INFORMATION
ON SERIES DISCOUNTS
CONTACT
BEN ADEWOLE ON
0442 66551**

LIVERPOOL

PROGRESSIVE RADIO

87/93 Dale Street Tel: 051 236 0154
47 Whitechapel Tel: 051 236 5489

Liverpool 2

'THE ELECTRONICS SPECIALISTS'
Open: Tues-Sat 9.30-5.30

CLASSIFIED ADVERTISING TERMS & CONDITIONS

Our terms for new advertisers (semi-display and lineage) are strictly pro-forma payments until satisfactory reference can be taken up (excluding recognised advertising agencies) Cheques and PO's should be crossed and made payable to ARGUS SPECIALIST PUBLICATIONS and sent together with the advertisements to:

The Classified Dept.,
Argus House, Boundary Way,
Hemel Hempstead HP2 7ST

There are no reimbursements for cancellations. Advertisements arriving too late for a particular issue will be inserted in the following issue unless accompanied by instructions to the contrary. It is the responsibility of the advertiser to ensure that the first insertion of every series is published correctly, and corrections must be notified in time for the second insertion, otherwise the publishers will not accept liability or offer any reduction in charges.

All advertising sales are subject to Government Regulations concerning VAT. Advertisers are responsible for complying with the various legal requirements in force eg. The Trade Description Act, Sex Discrimination Act and the Business Advertisements (Disclosure) Order 1977. Full Terms & Conditions of Advertising available on request.

LONDON

DIRECT ELECTRONICS ELECTRONICS COMPONENT SPECIALISTS

**627 ROMFORD RD,
MANOR PARK
LONDON E12 5AD
Tel: 081-553 1174**

Mon-Sat 10-6 pm/Thurs 10-1pm
We stock a large range of TV & Video spares

LIVERPOOL

ALLPARTS

TV & VIDEO SPARES EMPORIUM
NOW OPEN


Trade and Public Retail Outlet
FERG VIDEO HEADS FROM £10.95 • PANASONIC HEADS FROM £10.95
VIDEO COPY KITS £5.99 OR SCART KIT £9.99
FERG VIDEO LAMP WIRE ENDS 40p • FERG VIDEO LAMP WITH PLUG 60p
20MM A/S FUSES £1 PER PACK OF TEN

ALL YOUR TV & VIDEO NEEDS HERE IN L'POOL

ALL PARTS - 101 ROCKY LANE TUEBROOK
LIVERPOOL 6 4BB • 051 2604825
Mon-Fri 10am-5.30 • Sat 9am-5.30

E
L
E
C
T
R
O
M
A
R
T

E
L
E
C
T
R
O
M
A
R
T

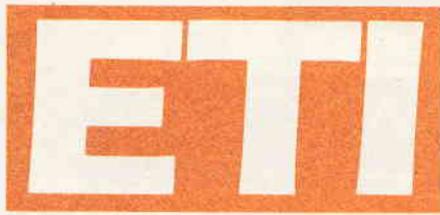

Panel Engraving Service

Now you can give your projects a more professional finish by using the ETI Front panel service. If you have difficulty with drilling clean holes and producing good quality labels for your treasured projects then this service is a must for you. We will supply complete front panels for selected projects featured in ETI in a variety of base colours and coloured type according to your choice. The material used is a tough laminated plastic of extremely durable quality. It can be used as a glue on front-piece to a metal back plate or even as a front panel in its own right, the decision is yours. We believe the prices quoted are extremely good value for money and indeed hard to beat.

All you do is fill in the coupon stating clearly the code number, your name and address and your remittance made payable to: A.S.P. Reader Services.

For the choice of colour you must add two letters to the end of the code. They are these: BW — Black panel, white lettering, RW — Red panel, white lettering, WB — White panel, black lettering, WR — White panel, red lettering.

The ultimate in personal service must be to offer a front panel made to your design requirements and this does not have to be limited to electronic projects. It could be a design for a clockface, a door-panel insignia, even your own logo. Now we can offer that facility too. Send us by letter or Fax, a neat dimensioned millimetre drawing of your panel design and we will be happy to give you a quote for a coloured front panel. On acceptance of the quote just send in the artwork and we'll do the rest. There's a minimum charge of £10.00 + VAT for this custom service but we reckon it's worth it.

Here are some recent popular projects to start this brand new service on its way, the prices are inclusive of VAT and postage and packing:

P9005-1	The Business Bass Amp	£16.95
P9003-1	Superscope CRT Panel	£ 3.95
P9003-2	Superscope X shift Panel	£ 2.95
P9003-3	Superscope T/base	£ 4.95
P9003-4	Superscope Y1 Input	£ 4.00
P9003-5	Superscope Y2 Input	£ 4.00
P9003-6	Superscope All 5 boards	£17.95
P9001-1	Wavemaker FG	£ 5.00
P8910-1	Multimeter	£ 5.95
P9007-1	Decision Maker	£ 8.95

TELEPHONE ORDERS

0442 66551



ETI Reader Services, Argus House, Boundary Way, Hemel Hempstead, Herts, HP2 7ST

Please supply P9005-1	Colour	Qty	@ £16.95
Please supply P9003-1	Colour	Qty	@ £ 3.95
Please supply P9003-2	Colour	Qty	@ £ 2.95
Please supply P9003-3	Colour	Qty	@ £ 4.95
Please supply P9003-4	Colour	Qty	@ £ 4.00
Please supply P9003-5	Colour	Qty	@ £ 4.00
Please supply P9003-6	Colour	Qty	@ £17.95
Please supply P9001-1	Colour	Qty	@ £ 5.00
Please supply P8910-1	Colour	Qty	@ £ 5.95
Please supply P9007-1	Colour	Qty	@ £ 8.95

Cheques/P.O. payable to A.S.P. or debit my Access/Visa

Total £

Signature Expiry

Name

Address

ETI Reader Services, Argus House, Boundary Way,
Hemel Hempstead, Herts, HP2 7ST
Allow 28 days for delivery



NEXT MONTH

In our Audio supplement, we present the first in a series of loudspeaker designs. We start by taking a comprehensive look at electrostatic types with plenty of design considerations in order that you may build one yourself.

In the concluding part of Microwaves, Colin White discusses the uses within the fields of RADAR, astronomy and medicine. Still on the subject, we present a feature on Instrument Landing Systems at airports where microwaves are essential for the safe landing of aircraft.

Will solar power ever become cost effective and establish a place in the energy generating game? The renewable energy series tries to find the answers to this and the different methods of utilising the sun rays.

If you feel like plugging in the soldering iron, we can offer a component tester, a digital countdown timing facility to improve your powers of oratory, be it in lecturing or disco presentation and a guitar pick-up to convert your ageing acoustic music box to perform something rather louder.

Order your copy today and collect the October issue on September 7th.

The above articles are in preparation but circumstances may prevent publication

LAST MONTH

In August we featured the first part on the workings of a modern-day synthesiser. The second in our energy series featured an article on wave and water power and in Electric Eye, we reviewed the latest trials to give blind people easier access to written information.

Projects covered were a Temperature controller, an FM generator, an AC millivoltmeter and an Update on a stereo decoder featured in ETI in 1987. A limited number of back copies are still available from Select Subscriptions (address on contents page).

ADVERTISERS' INDEX

BK ELECTRONICS	IFC	NUMBER ONE SYSTEMS	63
BRIAN PRICE ELECTRONICS	43	OMNI ELECTRONICS	13
CIRKIT HOLDINGS	15	RACKZ PRODUCTS	50
CRICKLEWOOD ELECTRONICS	13,21	RADIO & TV COMPONENTS	56
DISPLAY ELECTRONICS	51	REED ELECTRONICS	50
EUROMARKET SALES	63	SHERWOOD DATASYSTEMS	20
GREENBANK ELECTRONICS	3	STEWARTS OF READING	63
HAPPY MEMORIES	21	SUMA DESIGNS	3
HART ELECTRONICS	50	TK ELECTRONICS	28
HENRYS AUDIO	27	WILMSLOW AUDIO	43
J & N BULL ELECTRICAL	41	YAMAHA KEMBLE (UK)	IBC
MAPLIN ELECTRONICS	0BC		



THE SHOCK IN 3U

The sound of the 90's has been cut down to size.

What promises to be the most popular synth of the decade, the ground breaking SY77, is now available in 19" rack-mount form taking just 3U of precious rack space.

TG77 has all the tone generating wizardry that put the SY77 where it is today. AFM (Advanced Frequency Modulation) and AWM2 (second-generation Advanced Wave Memory). And that means crystal clear samples combined with state-of-the-art FM synthesis.

But there's more. RCM (Realtime Convolution and Modulation) synthesis brings the two different sound sources together to create a third that is greater than the sum of its parts. A whole new world of sound that's unique to Yamaha.

With built-in drums, two stereo and 8 assignable individual outputs, TG77 becomes a powerful production tool. Add the kind of software support that only Yamaha can provide and you can be sure your investment will be one for the future as well as the present.

Come with us and see.



YAMAHA
THE SPIRIT OF MUSIC

For further information on the TG77 and SY77, please complete this coupon and send to: Yamaha-Kemble Music (UK) Ltd., MI & Pro Audio Division, Mount Avenue, Bletchley, Milton Keynes, MK1 1JE.

Name _____

Address _____

_____ Postcode _____

ETI

1991 BUYER'S GUIDE TO ELECTRONIC COMPONENTS

Maplin

FEATURING:
AN ELECTRONICS
CAST OF
THOUSANDS!

POWER-PACKED
WITH OVER
600 PAGES!!

STARRING
HUNDREDS OF
NEW PRODUCTS
AT SUPER
LOW PRICES!

COMING
to your local WHSMITH from
7th SEPT

PERFORMANCES DAILY
At your local branch
of WHSMITH
ONLY £2.45

Order you copy of the New MAPLIN Catalogue on sale September
Pick up a copy from any WHSMITH for just £2.45 or post this coupon now to receive your
copy for just £2.45 + 50p p&p. If you live outside the U.K. send £4.85 or
20 International Reply Coupons. I enclose £2.95.

Name _____
Address _____
Post Code _____
Send to Maplin Electronics,
P.O. Box 3, Royleigh,
Essex SS6 8LR.

ROD BROWN

