


FREQUENCY PLOTTER

Oscilloscope displayed response

CIRCUIT FILE

Constant Current Generators

SIGNALS AT VLF

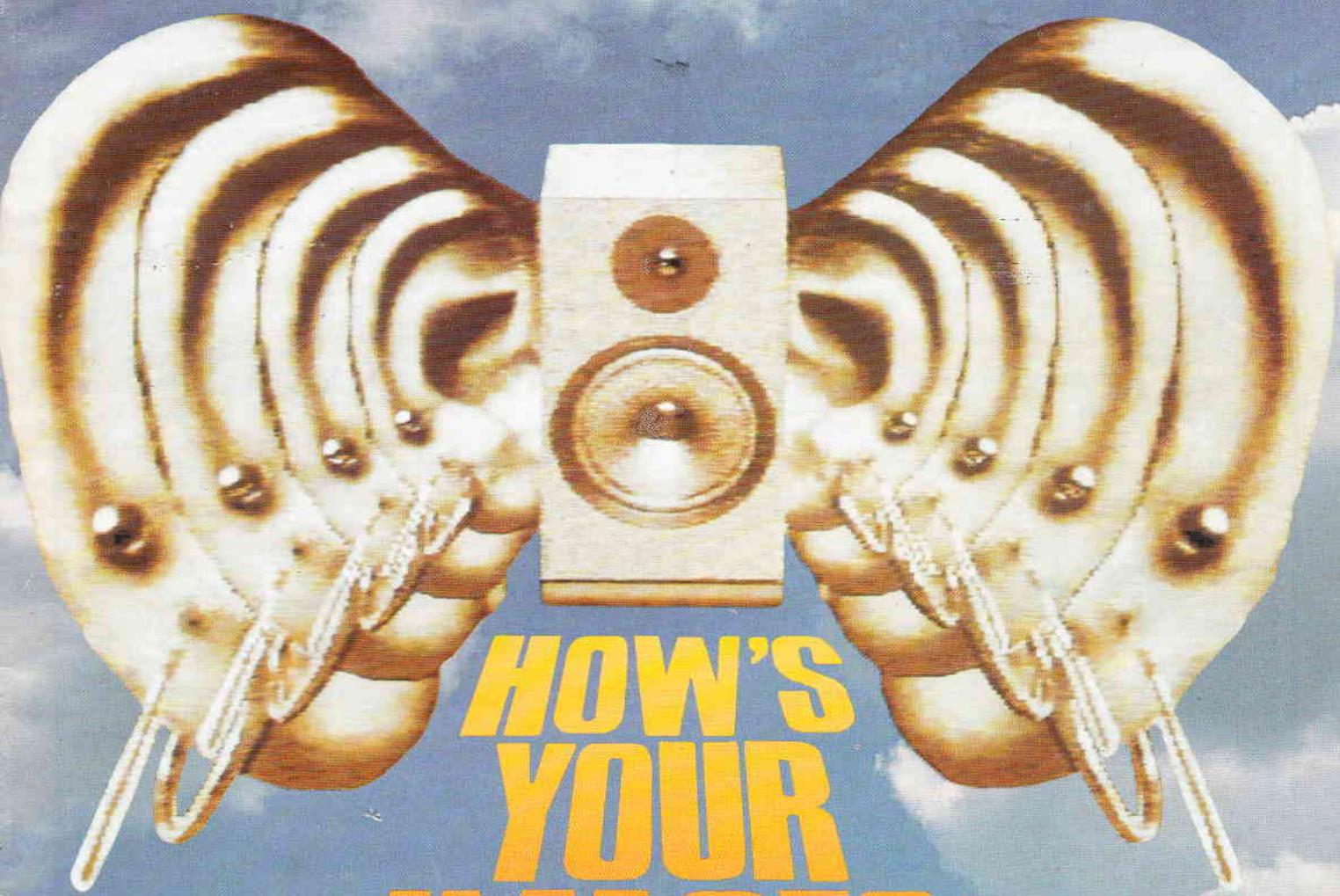

**HOW'S
YOUR
IMAGE?**

The Physics of Stereo Sound

PROJECT LASER

Amplitude Modulating a Laser



POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

OMP POWER AMPLIFIER MODULES

Supplied ready built and tested.

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP100 Mk 11 Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz - 3dB, T.H.D. 0.01%, S.N.R. - 118dB, Sens. for Max. output 500mV at 10K, Size 355 x 115x65mm. **PRICE £33.99 + £3.00 P&P.**

NEW SERIES II MOS-FET MODULES



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor, >300, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. - 125dB. Size 300 x 123 x 60mm. **PRICE £39.99 + £3.00 P&P.**



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. - 130dB. Size 300 x 155 x 100mm. **PRICE £62.99 + £3.50 P&P.**



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. - 130dB. Size 330 x 175 x 100mm. **PRICE £79.99 + £4.50 P&P.**

NOTE— MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS. STANDARD— INPUT SENS. 500mV BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE)— INPUT SENS. 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. **PRICE £8.50 + 50p P&P.**

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE S.A.E. (30p STAMPED) FOR COMPLETE LIST.

McKENZIE— INSTRUMENTS, P.A., DISCO, ETC.

- ALL MCKENZIE UNITS 8 OHMS IMPEDENCE**
- 8" 100 WATT C8100GPM GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID. DISCO. RES, FREQ. 80Hz. FREQ. RESP. TO 14KHz. SENS. 99dB. **PRICE £29.30 + £2.00 P&P**
 - 10" 100 WATT C10100GP GUITAR, VOICE, ORGAN, KEYBOARD, DISCO, EXCELLENT MID. RES, FREQ. 70Hz. FREQ. RESP. TO 6KHz. SENS. 100dB. **PRICE £35.58 + £2.50 P&P**
 - 10" 200 WATT C10200GP GUITAR, KEYBOARD, DISCO, EXCELLENT HIGH POWER MID. RES, FREQ. 45Hz. FREQ. RESP. TO 7KHz. SENS. 103dB. **PRICE £48.67 + £2.50 P&P**
 - 12" 100 WATT C12100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. RES, FREQ. 45Hz. FREQ. RESP. TO 7KHz. SENS. 99dB. **PRICE £37.59 + £3.50 P&P**
 - 12" 100 WATT C12100TC TWIN CONE HIGH POWER WIDE RESPONSE, P.A., VOICE, DISCO. RES, FREQ. 45Hz. FREQ. RESP. TO 14KHz. SENS. 100dB. **PRICE £38.58 + £3.50 P&P**
 - 12" 200 WATT C12200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. RES, FREQ. 40Hz. FREQ. RESP. TO 7KHz. SENS. 100dB. **PRICE £65.79 + £3.50 P&P**
 - 12" 300 WATT C12300GP HIGH POWER BASS LEAD GUITAR, KEYBOARDS, DISCO, ETC. RES, FREQ. 45Hz. FREQ. RESP. TO 5KHz. SENS. 100dB. **PRICE £87.51 + £3.50 P&P**
 - 15" 100 WATT C15100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO. RES, FREQ. 40Hz. FREQ. RESP. TO 5KHz. SENS. 98dB. **PRICE £55.05 + £4.00 P&P**
 - 15" 200 WATT C15200BS VERY HIGH POWER BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 99dB. **PRICE £75.10 + £4.00 P&P**
 - 15" 250 WATT C15250BS VERY HIGH POWER BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 99dB. **PRICE £82.54 + £4.50 P&P**
 - 15" 400 WATT C15400BS VERY HIGH POWER, LOW FREQUENCY BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 102dB. **PRICE £96.47 + £4.50 P&P**
 - 18" 400 WATT C18400BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. RES, FREQ. 27Hz. FREQ. RESP. TO 3KHz. SENS. 99dB. **PRICE £172.06 + £5.00 P&P**


EARBENDERS— HI-FI, STUDIO, IN-CAR, ETC.

- ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohms)**
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED FOAM SURROUND**
- 8" 50 WATT EB8-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES, FREQ. 40Hz. FREQ. RESP. TO 7KHz. SENS. 97dB. **PRICE £8.90 + £2.00 P&P**
 - 10" 50 WATT EB10-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES, FREQ. 40Hz. FREQ. RESP. TO 5KHz. SENS. 99dB. **PRICE £12.00 + £2.50 P&P**
 - 10" 100 WATT EB10-100 BASS, HI-FI, STUDIO. RES, FREQ. 35Hz. FREQ. RESP. TO 3KHz. SENS. 96dB. **PRICE £27.76 + £3.50 P&P**
 - 12" 60 WATT EB12-60 BASS, HI-FI, STUDIO. RES, FREQ. 28Hz. FREQ. RESP. TO 3KHz. SENS. 92dB. **PRICE £21.00 + £3.00 P&P**
 - 12" 100 WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES, FREQ. 26Hz. FREQ. RESP. TO 3KHz. SENS. 93dB. **PRICE £38.75 + £3.50 P&P**
- FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
- 5 1/2" 60 WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 63Hz. FREQ. RESP. TO 20KHz. SENS. 92dB. **PRICE £9.99 + £1.50 P&P**
 - 6 1/2" 60 WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 38Hz. FREQ. RESP. TO 20KHz. SENS. 94dB. **PRICE £10.99 + £1.50 P&P**
 - 8" 60 WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 40Hz. FREQ. RESP. TO 18KHz. SENS. 89dB. **PRICE £12.99 + £1.50 P&P**
 - 10" 60 WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 35Hz. FREQ. RESP. TO 12KHz. SENS. 86dB. **PRICE £16.49 + £2.00 P&P**

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

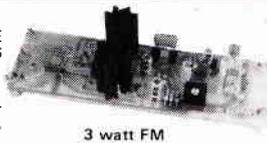3W FM TRANSMITTER 80-108MHz. VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. **PRICE £14.49 + £1.00 P&P**



FM MICRO TRANSMITTER (BUG) 100-108MHz VARICAP TUNED COMPLETE WITH VERY SENS FET MIC. RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATT. **PRICE £8.62 + £1.00 P&P**

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E., 30p STAMPED FOR CURRENT LIST.

OMP VARISPEED TURNTABLE CHASSIS.



★ MANUAL ARM ★ STEEL CHASSIS ★ ELECTRONIC SPEED CONTROL 33 & 45 ★ VARI PITCH CONTROL ★ HIGH TORQUE SERVO DRIVEN DC MOTOR ★ TRANSIT SCREWS ★ 12 DIE CAST PARTS ★ NEON STROBE ★ CALIBRATED BAL WEIGHT ★ REMOVABLE HEAD SHELL ★ 1/4" CARTRIDGE FIXINGS ★ CUE LEVER ★ POWER RESERVE 50.60Hz ★ 390x305mm ★ SUPPLIED WITH MOUNTING CUT-OUT TEMPLATE. **PRICE £59.99 + £3.50 P&P.**


OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500
PRICE £16.99 + 50p P&P

GOLDRING G850
PRICE £6.99 + 50p P&P

OMP MOS-FET POWER AMPLIFIERS, HIGH POWER, TWO CHANNEL 19 INCH RACK

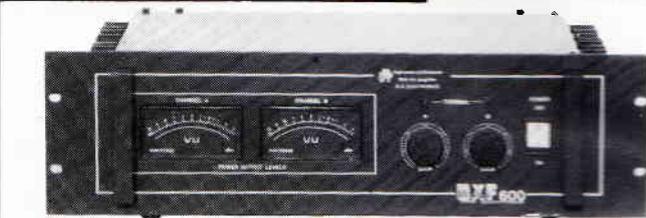THOUSANDS PURCHASED BY PROFESSIONAL USERS



NEW MXF SERIES OF POWER AMPLIFIERS

THREE MODELS:— **MXF200 (100w + 100w)**
MXF400 (200w + 200w) **MXF600 (300w + 300w)**
All power ratings R.M.S. into 4 ohms.

FEATURES: ★ Independent power supplies with two Toroidal Transformers ★ Twin L.E.D. Vu meters ★ Rotary interlocked level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV input ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 Fan Cooled with D.C. Loudspeaker and Thermo Protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:— MXF 200 W19" x H3 1/2" (2U) x D11"
MXF 400 W19" x H5 1/4" (3U) x D12"
MXF 600 W19" x H5 1/4" (3U) x D13"

PRICES: MXF200 £171.35
MXF400 £228.85
MXF600 £322.00

SECURICOR DELIVERY £12.00 EACH

OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE



MADE ESPECIALLY TO SUIT TODAY'S NEED FOR COMPACTNESS WITH HIGH OUTPUT SOUND LEVELS. FINISHED IN HARDWEARING BLACK VINYL WITH PROTECTIVE CORNERS, GRILLE AND CARRYING HANDLE INCORPORATES 12" DRIVER PLUS HIGH FREQ. HORN FOR FULL FREQ. RANGE. 45Hz-20KHz BOTH MODELS 8 OHM. SIZE H18" x W15" x D12".

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100 (100W 100dB) PRICE £159.99 PER PAIR


OMP 12-200 (200W 102dB) PRICE £209.99 PER PAIR

SECURICOR DEL.— £12.00 PER PAIR

PIEZO ELECTRIC TWEETERS—MOTOROLA

PIEZO ELECTRIC TWEETERS — MOTOROLA

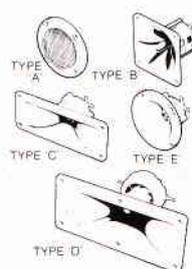
Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. **Price £4.90 each + 50p P&P.**
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. **Price £5.99 each + 50p P&P.**
TYPE 'C' (KSN6016A) 2" x 6" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. **Price £6.99 each + 50p P&P.**
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. **Price £9.99 each + 50p P&P.**
TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. **Price £5.99 each + 50p P&P.**
LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85mm. **Price £3.99 + 50p P&P.**

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. **Many outstanding features:** 5 inputs with individual faders providing a useful combination of the following:—
3 Turntables (Mag), 3 Mics, 4 Line including CD plus Mic with talk over switch Headphone Monitor, Pan Pot L & R, Master Output controls. Output 775mV. Size 360 x 280 x 90mm. Supply 220-240V. **Price £134.99 — £4.00 P&P**

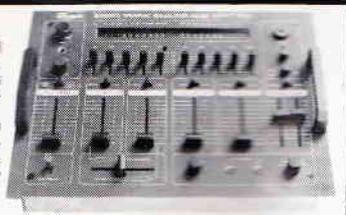


B. K. ELECTRONICS Dept EE
UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX SS2 6TR
TEL: 0702-527572 FAX: 0702-420243

POSTAL CHARGES PER ORDER £1.00 MINIMUM OFFICIAL ORDERS WELCOME FROM SCHOOLS, COLLEGES, GOVT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER. VISA ACCESS ACCEPTED BY POST, PHONE OR FAX.



Cirkit TESTING

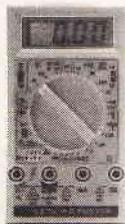


TM SERIES MULTIMETERS D-MM Good Value!

The TM series of low cost meters, with 3½ digit LCDs, full overload protection, strong ABS case and packed with features. Supplied with test leads, battery and manual.


TM 5315	DC current (10A) continuity and diode test	56-05315	£19.99
TM 5365	Capacitance and frequency (200kHz) ranges	56-05365	£37.90
TM 5375	Frequency range (20MHz) and HFE test	56-05375	£36.75
TM 115	AC & DC current (10A), HFE and continuity test	56-00115	£33.67
TM 135	Capacitance and temp. ranges (inc. probe)	56-00135	£45.95
TM 175	Frequency (15MHz) and capacitance ranges and HFE, diode, continuity and LED test.	56-00175	£57.49
7705	Capacitance meter, 1pF to 20,000uF	56-07705	£38.98

BLACK STAR

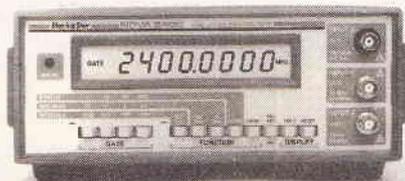Top quality, UK made, frequency counters and generators.



Meteor 100	100MHz counter	56-00100	£125.35
Meteor 600	600MHz counter	56-00600	£155.25
Meteor 1000	1000MHz counter	56-01000	£204.70
Apollo 100	100MHz counter/timer	56-10100	£339.25
Nova 2400	2.4GHz counter	56-02000	£343.85
Jupiter 500	500kHz function generator	56-00500	£126.50
Jupiter 2000	2MHz function generator	56-02001	£171.35

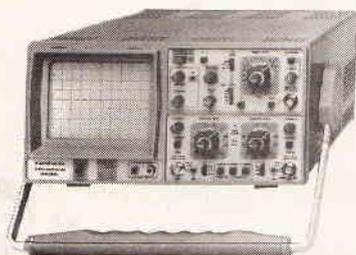

HAMEG 'SCOPES

All Hameg scopes are supplied with two x 10 probes, mains lead, manual and 2 year warranty.

HM203-7	Dual channel, 20MHz	56-52037	£388.70
HM205-3	Digital storage, 20MHz sampling	56-52053	£701.50
HM604	Dual channel, 60MHz	56-56040	£701.50
HM1005	Triple channel, 100MHz	56-01005	£910.85

Full details of all the above are included in our comprehensive catalogue, £1.60 (inc. P&P).

All the above are currently in stock and available for immediate delivery. Standard P&P £1.00, next day delivery £4.50.

All prices include VAT

Cirkit



Cirkit Distribution Ltd.

Park Lane, Broxbourne, Herts EN10 7NQ.
Telephone (0992) 444111.

DID YOU KNOW?

THAT THOUSANDS OF OTHER ETI READERS ALREADY ENSURE THAT THEY REGULARLY RECEIVE A COPY OF THEIR FAVOURITE MAGAZINE BY TAKING OUT A DIRECT SUBSCRIPTION

A SUBSCRIPTION TO ETI ENSURES A COPY IS NEVER MISSED AND WHAT'S MORE IF YOU LIVE IN THE UK, NO EXTRA IS CHARGED FOR POSTAGE*

SIMPLY COMPLETE THE ORDER FORM AND RETURN IT TO THE ADDRESS GIVEN WITH YOUR CHEQUE OR MONEY ORDER TO COVER THE COST OF THE SUBSCRIPTION

Take the stress out of buying ETI, subscribe today!

SUBSCRIPTION RATES

UK: £19.20; EUROPE: £24.10; MIDDLE EAST: £24.40; FAR EAST: £26.80; REST OF WORLD: £25.85; or USA: \$48.00

Airmail Rates on Request.

*OVERSEAS SUBSCRIPTION RATES INCLUDE POSTAGE

Please commence my subscription to ETI with the issue. I enclose my cheque/money order for £..... made payable to ARGUS SPECIALIST PUBLICATIONS

Or Debit my Access/Visa

No.

Valid from to

Signature

Address

..... Postcode

Send this form with your remittance to:
SELECT SUBSCRIPTIONS, 5 River Park Estate, Billet Lane, BERKHAMSTED, Herts. HP4 1HL, United Kingdom



ELECTRONICS
TODAY INTERNATIONAL

EDITORIAL

Editor Paul Freeman

CREATIVE

Art Editor Peter Kirby
Designer Iain Houston
Technical Illustration Jerry Fowler
Photography Manny Cefai


ADVERTISEMENT SALES

Advertisement Manager
Mark Linacre
Advertisement Sales
Michele Donovan
Advertisement Copy Control
Marie Quilter

MANAGEMENT

Managing Director
Terry Patisson
Circulation & Promotions Manager
Debra Stupple
Production Manager
Tony Dowdeswell
Group Editor
Mark Webb

ISSN
0142-7229

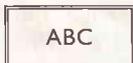

Member of the
Audit Bureau
of Circulation

ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications and any reproduction requires the prior written consent of the Company © 1990 Argus Specialist Publications. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

• Subscription rates — UK: £19.20. Europe: £24.10. Middle East: £24.40. Far East: £26.80. Rest: £25.85 or US\$48.00.



Argus House, Boundary Way,
Hemel Hempstead HP2 7ST
Tel: (0442) 66551 Fax: (0442) 66998

Features & Projects



	Page
Back To Basics 4	16
Paul Coxwell introduces some simple AC theory with resistive circuits.	
How's Your Image	22
Stereo sound images are very important when it comes to serious listening. Ronald Wagner looks at the physics of how we hear and interpret those sounds.	
Lasers 2	30
We now turn our attention to building a modulated He/Ne laser running from 12V. Kevin Kirk continues his theme on Lasers.	
Electronics At The Leading Edge	34
Dr Ken Smith presents the case for taking your studies in Electronics further by taking a course at University.	
VLF And ELF Loop Antennas	37
The second part of our investigation into low frequency Earth signals by George Pickworth.	
Constant Current Generator Circuits	40
Ray Marston wades through another stream of constant current circuits.	
Thyristor Tester	45
As the title suggests, a neat little piece of test-gear for the workshop by Mark Daniels	
HDTV 6a	52
There are many proposed alternative American systems for HDTV and James Archer continues his in-depth look at them.	
Remote Controlled Timeswitch Update	56
Jon Herd presents the problems and challenges when constructing this recent ETI project	
Frequency Plotter	58
Display the frequency response of your electronic circuits on your oscilloscope with this project by Edward Barrow.	

Regulars


Read/Write	6
Open Channel	8
News	10
Blueprint	14
PCB Service	29
PCB Foils	62
Classified Ads	64
Photocopy Service	66

MAY 1991 VOLUME 20 No 5

Published by Argus Specialist Publications, Argus House, Boundary Way, Hemel Hempstead HP2 7ST. Tel: (0442) 66551. UK newstrade distribution by SM Distribution Ltd., 6 Leigham Court Road, London SW16 2PG. Tel: 081-677 8111. Overseas and non-newstrade sales by Magazine Sales Department, Argus House, Boundary Way, Hemel Hempstead, HP2 7ST. Tel: (0442) 66551. Subscriptions by Select Subscriptions Ltd., 5 River Park Estate, Berkhamsted, Herts HP4 1HL. Tel: (0442) 876661. US subscriptions by Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA90505 USA. Tel: (213) 3756258. Typesetting and origination by Project 3 Filmsetters, Whitstable. Printed by Acorn Web Offset Ltd, Bradford, W Yorks.

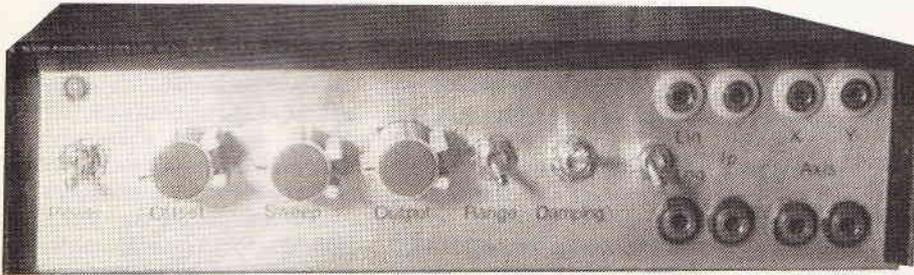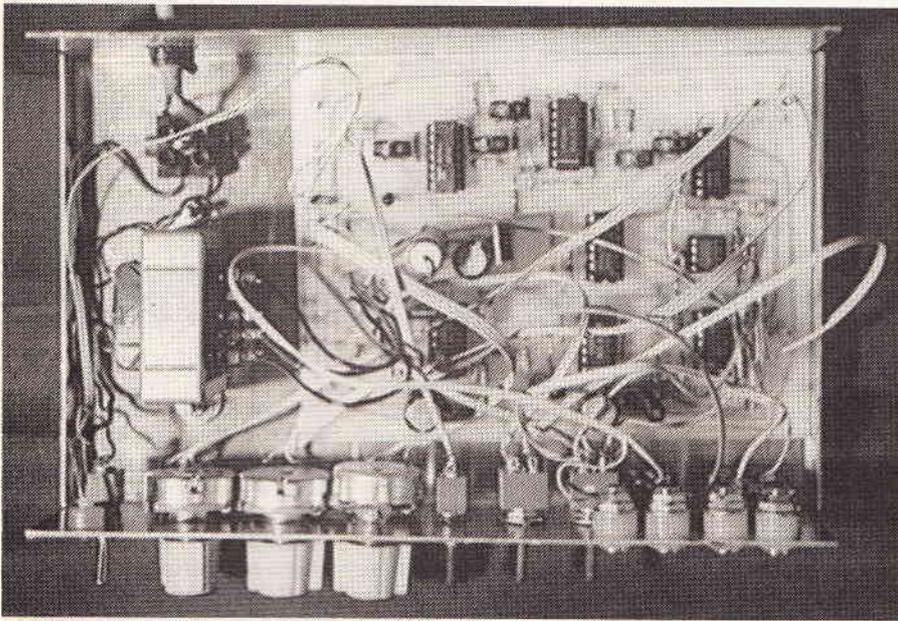

Frequency Plotter Page 58

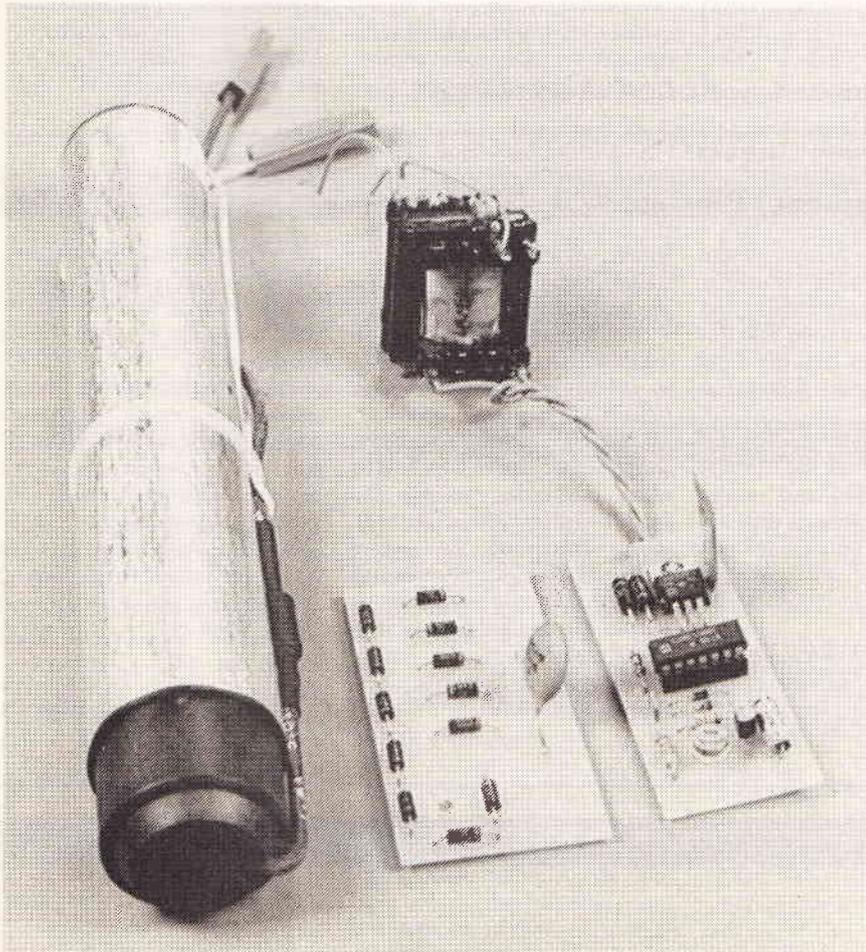

Amplitude Modulated Laser Page 30

Editorial

You have probably noticed ETI has and is undergoing a change in layout. The latest change is as you see within the contents pages including an editorial. Comments on the style and contents are always welcome and you have the chance to express your requirements soon through a readership survey. It has been three years since you last had the opportunity to do so. If pencils are kept sharpened and poised to fill in a form, there may be a prize in store for you if they are returned quickly. More details later.

Mathematics

We must be one of the few newsstand magazines to present mathematics, not 'sums' within our features and projects and 'get away with it'. It is often said that for every mathematical equation that appears in a publication for general release, sales will halve. Professor Stephen Hawking through his very successful book: *A Brief History of Time*, said as much but felt he ought to use one, the famous Einstein equation, $E = mc^2$. Perhaps those in control of publications have misjudged the general public. Could they now be bold enough to take on other similar ventures.

Society says technical subjects including Mathematics are taboo at parties and those that attempt such a bold venture are written off as the 'bore' of the party. Not that I'm advocating such a move as I have known some that could speak of nothing else. It is strange because mathematics is the language of life. If only men and women's cognitive response to numeral and symbolic logic was as straight forward as our verbal language and the written word then mathematics would also be a pleasurable subject. Until then it seems doomed to remain in that allocation of life called work. On this basis, it seems remarkable that magazines like ETI have survived against all the odds.

Paul Freeman.

Cover: Computer Art
by Manny Cefy

Erroneous RIAA

I refer to the article on RIAA equalisation in the March edition which I read with much delight, until I realised the approach the network and what was offered. I realise that anyone may produce a circuit of their own design to produce a particular need but to offer a design and claim it complies with RIAA requirements when it does not, must be misleading to your readers.

Looking at Figure 6(e), when the network response is carefully calculated, the 1kHz gain is found to be 16.5 and not '20' or 21 claimed, whilst the VLF gain is 21.7dB above that at 1kHz (RIAA requirement is 19.9). The response and errors are given below in relation to RIAA.

	VLF	50	100	1k	10k	20k	30k
	+21.7	+17.8	+13.5	0	-11.77	-16.95	-19.6
	+19.9	+16.9	+13.1	0	-13.72	-19.6	-23.1
Error	1.8	0.6	—	—	1.95	2.65	3.5

Some may consider this 'good enough' whilst other will take the view that 'good enough' is not good. The error occurs in considering the break points individually and using a 'rule of thumb' to determine values. To achieve an accurate response, it is essential to consider all three together as they interact. The author is not alone in this as similar designs in ETI March '86 and August '86, both of which were rectified in June 87. Design of RIAA networks is not as easy as it seems, the best step is to use the recognised component ratios which have been known since 1957, but not always remembered.

W Harms,
Bexhill East Sussex

David Silvester replies:

I was aware that there were errors in the calculations that are caused by the availability of components and the tolerances that they are subject to. Taking the 'nearest value to' throws out the calculations at every stage to some extent. The article was not to be a rigorous treatment of the subject with calculation to the n'th degree for that I feel is a fruitless task, and the original request was to answer why it is needed at all. In addition, we must end up with a circuit that we can actually build with components purchased from one of the common suppliers, and those components will only be available with specific values and will also have tolerances.

I would like to see one of Mr Harms designs along with his calculations to find out where in his opinion I have gone wrong. However I would insist that all of

the component values he uses are available in the Maplin catalogue or he names his source. I certainly do not have the money to go out and buy a large number of components just to select the one with the value the circuit needs then throw the rest away. Using mathematics he might then like to work out his circuit using the worst case component tolerances and see what he gets. I shall be most interested in the results. As a final point I have used the circuit shown for a number of years and the reproduction that it gives suits me admirably. It seems strange that having calculated the RIAA equalisation that the 'corrected' output should then be allowed to be distorted by tone controls or graphic equalisers, in the final trial it is the ear that tests the result not the calculator.

David Silvester,
Southampton.

Advantage GN

I was quite disturbed when I found the ETI's letters section which sort of attacked Mr Graham Nalty for his comments suggesting ways to improve some designs sound quality through the upgrading of certain parts, particularly resistors, capacitors and cables.

As I have been following Mr Nalty's articles and notes, in ETI and several other magazines, I do have to say that those letters were at least very unfair. As fairness is supposed to be a British 'invention': lets be fair.

Even so, this seems to be just another subjective/objective discussion continuing to sparkle on

both sides of the Atlantic. "How can you listen to a difference when you cannot measure it? I'd say something is wrong with the instruments then because I do hear the difference. It is slight but it's there.

In ETI, Mr Nalty published a series of articles for his VIRTUOSO Project (pre and power amp) which he shared with us. He also had the courage to back his construction project with a recognised critic's test on that very same project.

He certainly has the right to suggest on ways he believes to be the best to improve the sound of audio projects, his or others part-

icularly when they are on that stage of being built as usually ETI's projects are.

His findings and opinions on 'passive' parts: that he described to us in ETI's VIRTUOSO notes (which I judge as a generous attitude are a quest for a better sound which has been backed by other magazines. People like Martin Colloms: Ben Duncan:, Richard Marsh and Carl Jung are always looking for new measures or tests as sensitive as our hearing system (or should I say our feelings system), to prove to an unbelieving 'Audio Scientific Community' that amplifiers might not sound the same even if they

measure the same, or that amps do not have any sound of its own, as 'they' defend. For 'them', CD is the "perfect" medium, their panacea.

To suggest that Mr Nalty might advise on improving certain parts because he sells them, not considering his background, is like somebody being attacked as an ecologist because he sells flowers. I should say he believes on what he says and invests on it, helping other people secure hard to find parts. Think of it.

Carlos Martinez, Rio de Janeiro

High Lights

Having just read your latest (March '91) edition of ETI, I must say that the project by Kevin

Kirk proved to be most interesting. The idea of a light show is not one which is unique

but his personal interpretation of the idea is most interesting. Please pass on my thanks for an

excellent project to both the ETI editor and to Kevin Kirk.
J P Brister, Somerset.

Advantage JLH

I refer to the correspondence from Graham Nalty, Audiokits, Derby. In an article of approximately 20 years ago (Wireless World) by Mr Linsley Hood, the following appeared — "Unfortunately, it is not possible to simulate under laboratory conditions the complex loads or intricate waveform structures presented to the amplifier when a loudspeaker system is employed to reproduce the everyday sounds of speech and music; so that although the square wave and low-distortion sine wave oscillators, the oscilloscope, and the harmonic distortion analyser are valuable tools in the design of audio circuits, the ultimate test of the final design must be the critical judgement of the listener under the most carefully chosen conditions his facilities and environment allow". Also, Mr Hood referred to in the same article — "listener fatigue". Therefore, I must assume that Mr Nalty failed to 'read between the lines'!

Obviously, one would tend to conduct both 'listening' & laboratory tests subsequent to any component substitution experiment — possibly, the latter would provide some enlightenment on the validity of certain previously held beliefs? ...Further, in the same article (a transistor Class A design); Mr Hood referred to, and I quote "...but they appeared also to give a fuller, 'rounder', quality, the attractiveness of which to the author much outweighs the incidental inconvenience of the need for more substantial power supply equipment and more massive heat sinks.". I wonder, has any

reader a suitable circuit diagram for a 'Roundness' Analyser? Also, Mr Hood referred to 'the time interval between listening tests' (in connection with comparative tests conducted in the absence of 'A/B' switching facilities). Enough said!

Of Hart Electronics, may I simply say that 99,99% of commercial audio equipment is of a considerably lower standard — in terms of layout, printed circuits, components and the like. In fact, I have just got round to building one of Hart's Mk1 Cassette Recorder Kits (bought back in 1976) — a design by Mr Hood. The equipment worked first time — despite using the 14 year old electrolytic capacitors! (although I did connect them across a DC supply via a 18k resistance, and carry out a few basic tests). I can only say

that if Hart Kits (and instructions) have only improved 1% over the last 14 years, their products are beyond reproach!

Of my opinions on the quality of Hart products, I can only say that my one-offs exceed the sort of standards associated with the bulk of commercially available audio equipment (including the 'stuff' praised by 'Golden Ears!'). However, to be fair, I must state that I have not constructed one of Mr Nalty's amplifiers possibly, my obsessionism with internal detail in this respect; would be described by a psychiatrist as some sort of compensation for an imperfect self?!

The internal construction of some of the equipment reviewed by 'Golden Ears' — inc, £1000+ all-American power amplifiers, is typically 'bird's nest' in it's

executions — indeed, some of it would not meet with the approval of the Hook & Crow population!. In fact, I had the opportunity to dismantle a pair of £1000 so-called monitor loudspeakers, but the internal assembly was appalling — particularly the soldering (the plastic enclosure of one of the tweeters displayed much evidence of soldering iron contact, and many joints appeared 'dry'!). Also, sound quality failed to approach that of my own DIY transmission line design (a modified version of A Bailey's 1966 (?) Wireless World design!). Of the associated woodwork I suspect that the corner joints will probably 'move' within five years (moisture absorption in unsuitable particle board — or treatment)

M J Evans, Worcester

Micros With Macro Contribution

Though having taken ETI for about fifteen years this must be the first communication with you, so some reader feedback might be in order.

I have constructed a great number of projects over the years

and learned much from both them and the editorial content of the magazine. The micro-processor and micro-controller projects hold most interest for me at the moment — I feel there is a very secure future for their

application to improve basic electronic equipment used in all areas of life. Your magazine continues to provide excellent value for money.

R Ludlam, Ascot, Berks

Valve Affordability

I was delighted to read, in ETI Feb 91, that Velleman Kits have introduced a high quality valve amplifier that "most of us can afford". Sadly I can't agree that it is affordable.

Would it be possible for ETI to feature a valve amp as a project? I am sure it would be of interest to a lot of readers.

**R White,
Truro,**

Cornwall.

We will do our best to satisfy the needs of a new growing band of constructors who want to return to valve technology — Ed

SBC09 Alternative

You may be interested to know of a simple way to improve the SBC09 (ETI Jan 91) without the use of an add-on card. The 6821 Parallel Interface Adaptor IC (IC4) can be exchanged for the more capable 6522 Versatile interface adaptor. The 6522 has the same 2 × 8bit parallel ports of the 6821 with the added advantage of 2x16Bit timers and an SIPO and PISO shift registers.

To fit the 6522, first remove the 6821 then cut the tracks leading to pins 21, 22, 37 and 38 of IC4. Connect pin 21 of IC4 to

the IRQ pin of IC1 (pin 3 of the 6809), Connect pins 37 and 38 of IC4 to pins 11 and 10 of IC1 respectively, Connect pin 22 of IC4 to pin 32 of IC1 (R/W pin of 6809). Some of these links can be made to tracks running close to IC4.


After carefully soldering the links (I recommend using fine wire-wrapping wire) the 6522 can be fitted to the IC4 socket. The Parallel I/O lines have the same configuration as those of the 6821 and it will require little programming to adjust to the 6522's different register structure.

The Address lines A0 to A3 are not connected in numerical order to pins RSO-RS3 of the 6522 so the registers will appear in a different order to that shown on the 6522 data sheet. For those using a cross assembler this be no problem, the following is a list of 'EQU lines' to use in each program.

.EQU ORB, h'8000
.EQU IRB, h'8000
.EQU ORA, h'8004
.EQU IRA, h'8004
.EQU DDRB, h'8008
.EQU DDRA, h'800C
.EQU TICL, h'8001

.EQU T1CH, h'8005
.EQU T1LL, h'8009
.EQU T1LH, h'800D
.EQU T2CL, h'8002
.EQU T2CH, h'8006
.EQU SR, h'800A
.EQU ACR, h'800E
.EQU PerCR h'8003 ; PCR cannot be used as a label
.EQU IFR, h'8007
.EQU IER, h'800B
.EQU ORA2, h'800F ; Second ORA and IRA
.EQU IRA2, h'800F
I hope this will be of some use.
**A Bardsley,
Fallowfield, Manchester.**

OPEN CHANNEL

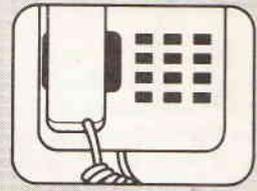

For some reason, all stories I cover in this month's column report possible death knells for systems which have been regularly in the news during recent times. The three systems considered — digital cellular telephones; telepoint telephones; and digital audio tape — have been much vaunted by their proponents and indeed at least one of the three, it has been suggested, we simply cannot do without.

Cells of resistance

In July a new pan-European digital cellular telephone service is due to begin operation. Technically, it is a much superior system to current cellular systems in use here in England and on the Continent. It has the ability to allow inter-country roaming — so 'phones can be used anywhere in Europe and car drivers will be able to drive from country to country without a break in a 'phone link. Being digital it offers much improved communications quality, too; a fact many users, fed up with current speech-link quality may be pleased to hear.

However, there is a distinct possibility the new system won't take to the road for a while. Indeed, its launch in July is being viewed with some scepticism. Some operators of current networks believe it's not a viable alternative to analogue systems, yet. July is looked on as a symbolic start-up date, and it will be around a year before it starts to operate at all successfully. At least one current operator is advising its customers against moving to the new systems, saying 1996 is a more advisable date to consider changing. Significant investment has been put into current systems, they work (albeit with a few hiccups), and a change simply for change's sake isn't going to go down well with anyone.

Is There Any Point

Of course, I've been saying it for a while in *Open Channel*, but it seems even the industry is starting to realise it too — not many people want a Telepoint telephone. Telepoint is, of course, the system where small cordless telephones can be used within sight of a telephone point, to make out-going calls into the public network. Despite significant development investment costs and consequent marketing, sales of these pocket-sized portable telephones are in just thousands, not hundreds of thousands people were hoping. It's not the first time I've said it, but I certainly wouldn't dream getting such a 'phone, considering their operational costs. And I'm a self-confessed gadget-lover, not at all typical of the man-in-the-street.

A report published recently by Communications and Information Technology Research predicts only around 280,000 UK subscribers will be using the telepoint network by the end of the century. With only these numbers involved for four competing operators licensed by the Government are going to find it hard to recoup initial costs, let alone make a profit.

DAT's Enough

There's been a large amount of hype in hi-fi publications

recently, regarding digital audio tape (DAT) systems. It's almost as if the cock-up the hi-fi pundits made over compact disc (remember, there was once a time when no self-respecting enthusiast would dare upgrade a scratchy old analogue transcription deck to a CD player — some even swore blind they could hear the CD's binary digits being reproduced!) was simply too much to take, and so they must throw themselves in wholeheartedly this time to make amends.

Well the latest news from Philips (yes, the company which gave us compact disc in the first place) is of a digital cassette tape system, comparable in performance to DAT, and available from next year. It uses a thin-film playback head, capable of reproduction in both analogue and digital modes. Tapes are identical in size with standard compact cassettes (they were developed by Philips as well, by the way!) and so, yes you've guessed it, existing analogue cassettes are playable, thus beating DAT's inherent incompatibility hands-down. With DAT now on the endangered species list, I give it just two years to become as extinct as a dodo.

Fatal Flaw

These three systems considered this month are examples of a marketing philosophy used in product development which defines a potential customer then makes the product which the customer supposedly wants. Such a market-led design philosophy is, of course, successful when it works. Videocassette recorders form possibly the best example of successful market-led design. Who could have foreseen, ten years ago, nearly all the population of, say, such a conservative nation as ours having one? Yet someone, somewhere in Japan realised it could be possible. And, having seen the possibility, went ahead and designed, developed and produced a product which has sold in its millions worldwide. Although technically quite a complex task, development of videocassette recorders hinged on there being no viable alternatives if a customer wants to record and replay television programmes, or hire films for home use, the customer needs a videocassette.

Where digital cellular, telepoint, and digital audio tape market-led designers may have got their philosophies wrong is in their presumption that customers will want to spend a lot of money buying a product which is either (1) already available in one form or another (2) simply too expensive for the convenience it offers, or (3) bettered by an alternative developed by someone else. Where a market-led product like the videocassette recorder is developed, price is of secondary concern. If customers want to do what a videocassette allows them to do, there is no alternative but to buy a videocassette recorder.

Nobody denies these new products are better than their older counterparts, but the fact must be faced: older counterparts exist. Are the new products sufficiently better — and sufficiently cheap — to win the customer over? Time might prove me wrong, but I think not.



Keith Brindley

STILL CAMERA FROM CANON

Canon has introduced its second ION still video camera. The RC 260 has the ability to capture images electronically on 2" floppy disk, and view them on TV.

Used with the optional film adapter, the RC 260 can also be employed as a device for converting existing collections of slides or negatives to ION images.

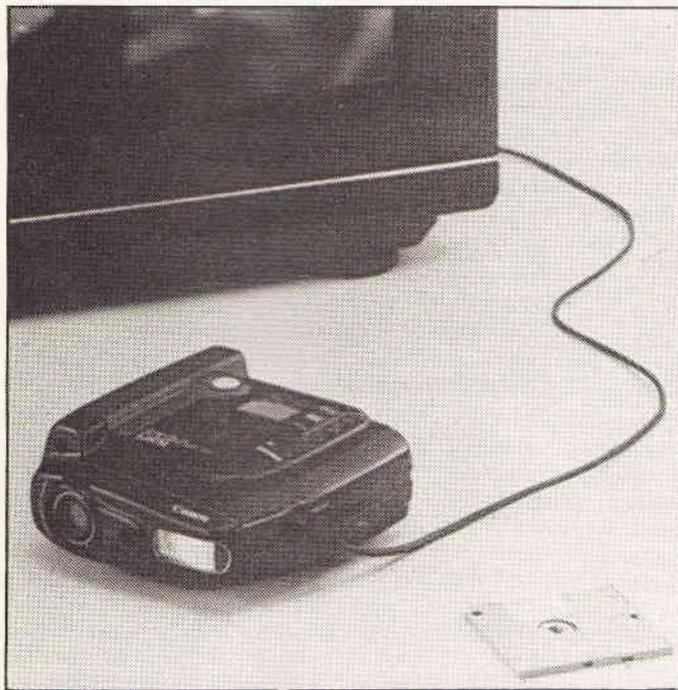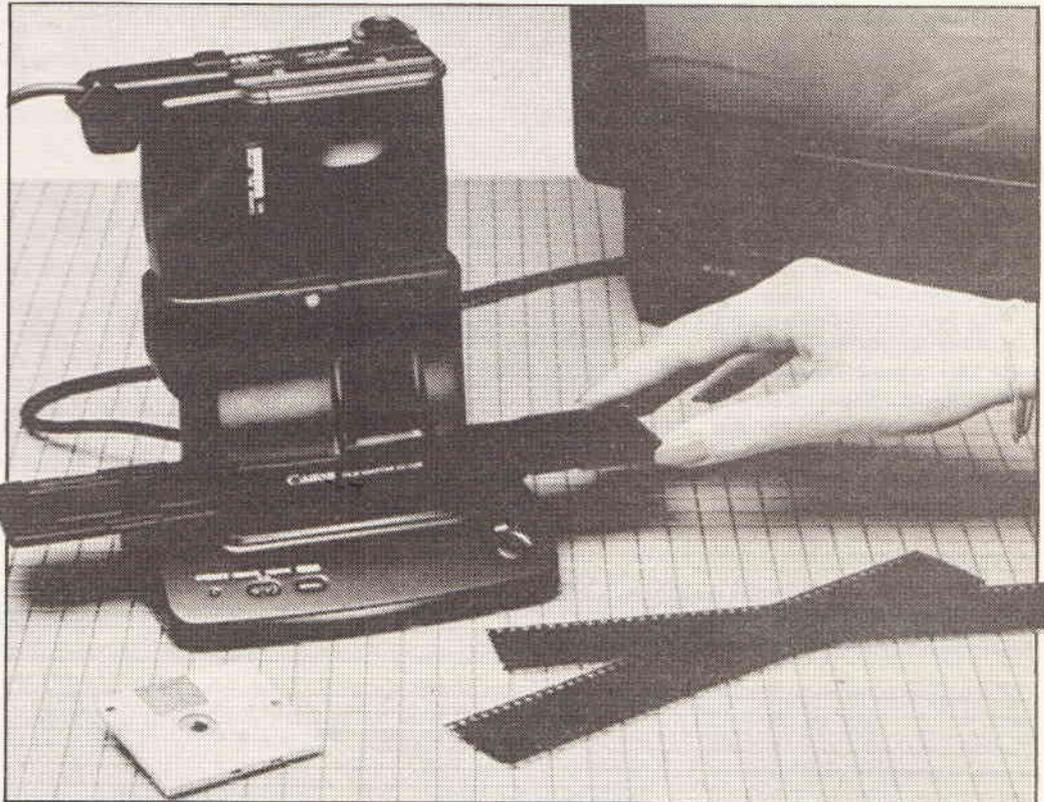Consumer-still video technology was pioneered by Canon with the launch of the RC251 in 1989. Already, the ION has gained substantial interest in both this field and the industrial field. The company has taken this development one step further and has reshaped the new ION using a smaller, more compact design



and relocated key controls, for ease of use.

New features include: Interval shooting for time lapse photography; interval playback; preview facility, enabling pictures to be seen on as they are being taken; infra red remote control; macro facility; backlit compensation feature; a wider angle 9.5mm lens; optional date/time feature on images and individual or all track erase function.

The body shape and size has been re-engineered and is now smaller and lighter than the previous model, weighing only 410g.

The camera is fully automatic with a fixed focus lens, a self-timer, automatic exposure and flash using rechargeable batteries and can take single, continuous (three per second) or interval shots.

It can be set to shoot automatically from 1 to 99 minutes and play back every 3.5 seconds for time lapse photography or for making presentations.

An infrared remote controller allows users to change tracks, control on screen date/time information and control interval playback.

The RC-260 can be used as part of a system according to the application. It links with a VCR (for alternative storage of the image) with portable liquid crystal TVs and a video printer and also with Canon's colour laser copier CLC 500 for hard copies.

As an input device, the RC 260 can be connected via various interfaces to IBM, Macintosh, Amiga, and Atari computers for applications such as desktop publishing. It is available from March at a cost of £499.99.

LANDMARK

Landmark Computer Systems Limited has today launched itself as a distributor of UNIX-based systems, to provide resellers and UNIX software houses with an unrivalled level of technical and marketing expertise.

Based in Worthing, the new company will market a range of UNIX-based systems using the Motorola 88000 RISC processor,

together with products from leading software vendors such as Cincom, Uniplex, Oracle and Informix.

The company has already entered in to an exclusive marketing and distribution agreement with Cincom to port a UNIX version of Cincom Supra onto the Motorola 88000 processor.

Graham Clarke Landmark's marketing and sales manager explains "In the United States, Motorola is the fastest growing manufacturer of UNIX based computer systems and are currently the sixth largest supplier of UNIX systems worldwide.

The 88000 RISC processor is arguably the leading RISC based processor currently available.


Motorola has established itself in international markets as a leader in electronics development.

Other products to be supplied by Landmark will be an extensive selection of terminals, communications and peripheral products from leading manufacturers, to enable the company to provide complete solutions.

MORE POWER FROM BK

To compliment their range of MOSFET amplifier modules, BK Electronics have introduced a 450 Watt RMS version. This features an integral power supply including a toroidal mains transformer, on board DC loudspeaker protection, two second delay anti-thump circuitry and a built in cooling fan.

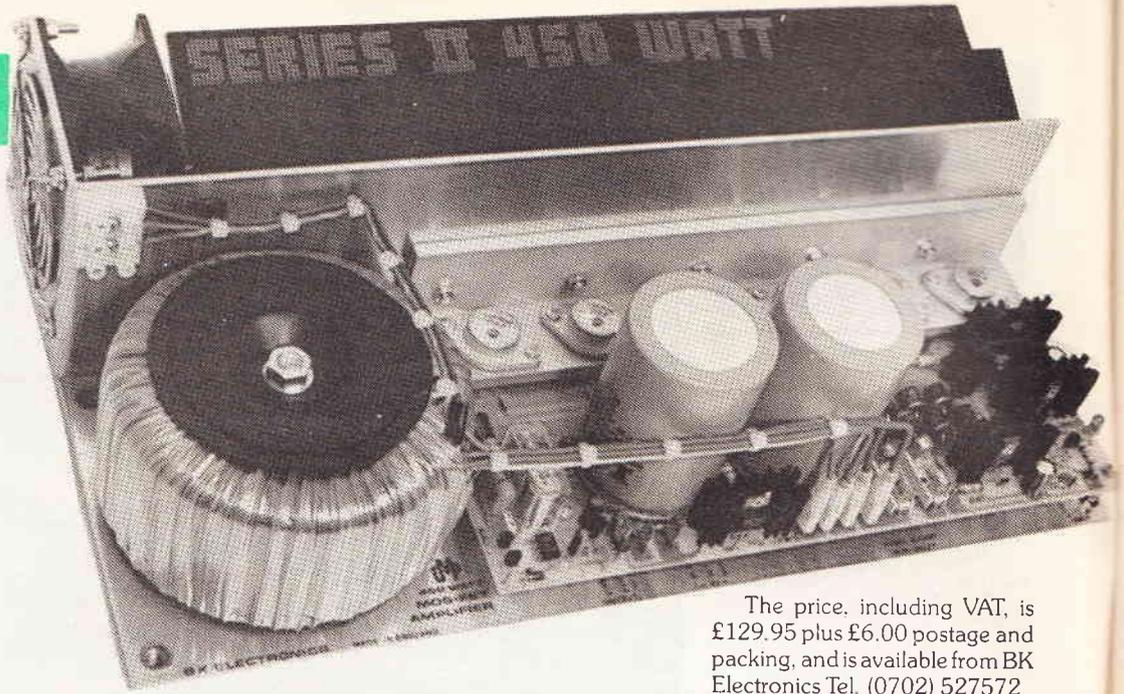The new amplifier delivers 460 Watts RMS into 4R and 315 Watts into 8R. As with their other amplifier modules a choice of input sensitivities is available. The standard version utilises a 500mV input and the professional equipment compatible version features a 775mV input for full power.



The price, including VAT, is £129.95 plus £6.00 postage and packing, and is available from BK Electronics Tel. (0702) 527572

SHARP END OF RESEARCH

The new Sharp Laboratories of Europe Ltd (SLE) research and development establishment is now under construction following the official ground breaking ceremony on the Oxford Science Park on 19 February 1991.

The building, representing an investment of over £3m, will be one of the first on the site sponsored by Magdalen College, Oxford and is due for completion in March 1992.

Already working in temporary accommodation in Abingdon,

SLE has been formed to conduct fundamental research in optoelectronics and information technology.

With an initial capital 75% provided by Sharp Electronics (UK) Ltd and 12.5% each by Sharp Electronics (Europe) GmbH of Germany and Sharp Electronics Espana SA of Spain, SLE is committed to contributing to the European community in an effort to develop basic technology for future products and systems suitable for the European market.

Managing director of SLE, Dr Clive Bradley, was previously head of Secretariat of the Advisory Council of Science and Technology, Cabinet Office. He has extensive electronic research experience, spent six years in Japan at the British Embassy as Counsellor (Science and Technology), and has a wide knowledge of scientific policies in the UK and Europe. Deputy Managing Director is Dr Yoshiharu Nakajima, who had extensive experience of work in Japanese,

German and US universities before joining Sharp Corporation.

SLE will recruit most of the employees from within Europe, particularly the UK and has already been successful in reversing the brain drain by attracting British scientists back to the UK. It will also form partnerships with British and European research organisations including universities.

SOFTWARE THEFT ACTIONS IN LONDON & PARIS

The Business Software Alliance (BSA) and the Federation Against Software Theft (FAST) have announced the filing of legal action against Marconi Instruments Ltd for the alleged unauthorised copying of software. The BSA simultaneously announced in Paris, in conjunction with the French Association Francaise des Editeurs de Logiciels (AFEL), that it had conducted court-ordered inspections concerning the alleged unauthorised copying of software against two French companies — Rhone-Poulenc Films and France Distribution Systems.

The BSA and FAST announced that four software companies — Ashton-Tate, Lotus Development, Microsoft and WordPerfect — obtained authorisation from the High Court in London on 21 November 1990, for an 'Anton Piller' order,

permitting an inspection of the personal computers at two Marconi Instruments Ltd facilities at Stevenage and St Albans. The solicitors for the parties conducted this inspection on 22 November, and following the review of the results, legal proceedings alleging copyright infringement were issued and served on Marconi Instruments Ltd. An application for an interim injunction was heard on December 7th but adjourned until the New Year on certain undertakings given by Marconi Instruments Ltd.

The BSA announced that its actions in the UK and France were the first step in a new wave of legal actions throughout Europe.

"The piracy problem is causing the software industry serious damage, and we have therefore decided to move forward on a pan-European basis with co-ordinated action against software

piracy in corporations." BSA managing director Robert Holleyman said in Paris. "We have several other cases already underway in the UK, France and other European countries, and between now and the Spring of 1991 we will proceed with additional legal actions."

Fox Borgerhoff Mulder, vice-president of BSA and FAST board member, stated: "To our knowledge, this is the first time that the industry has successfully obtained an Anton Piller order in the UK."

An Anton Piller order aims to prevent the destruction of evidence and thus permits a copyright holder to inspect without advance notice the premises of a company suspected of engaging in piracy.

The European Community's Council of Ministers met in Brussels to decide whether to

approve a new directive for the legal protection of computer programs. The BSA, FAST and AFEL have praised the proposed directive's provisions, which will require all EC member states to establish strong remedies against software piracy.

The BSA represents eight software companies for personal computers — Aldus, Ashton-Tate, Autodesk, Digital Research, Lotus Development, Microsoft, WordPerfect and XTree.

Over the past six months FAST has stepped up its efforts to raise corporate awareness of software theft, following a survey conducted by MORI which showed that 55% of those senior managers using PCs at work have copied software illegally. Over £300,000,000 is now known to have been lost in illegal software copying last year, a 100% increase on estimates of four years ago.

MAPLIN SALES

It's good news time for MAPLIN shop customers. But there is not too much time to lose. Until 13th April 1991, 1000's of prices are being discounted - some by up to 50%. The sale covers not only existing goods, but seconds and returned items. A whole range of

electronic products and components will be available at all the local MAPLIN shops.

Discounted components in particular will appeal to the rapidly expanding number of Maplin Professional Supplies customers, who increasingly will find that

Maplin shops are incorporating a special trade counter. Maplin shops can be found in: Birmingham; Brighton; Bristol; Leeds; London — Burnt Oak and Hammersmith; Manchester; Newcastle-upon-Tyne; Nottingham; Reading; Southampton and

Southend-on-Sea. Other MAPLIN shops planned to open in 1991 include: Cardiff, Chatham, Glasgow, Liverpool and Sheffield.

ISDN NEW LINES OF COMMUNICATION

British Telecom have launched ISDN 2 — a new communications service that will revolutionise the way businesses operate. Aimed at the small to medium-sized business and branch offices of larger companies, ISDN 2 (the Integrated Services Digital Network) will open the doors to a

number of new applications as well as enhancing existing services. These include the transmission of an A4 sized page in a couple of seconds by facsimile, faster data communications, low cost video links, and clearer speech for normal telephone use.

BT has made available more than 20,000 ISDN lines to cover


most major cities throughout the UK. It is also intended to cover all high streets and business areas by the end of the year when more than 90,000 lines will be available.

A similar service, called ISDN 30 and aimed at large businesses, has been upgraded and is now available on BT's System Y digital exchange as well as System X.

This means even more large businesses will be able to use the service.

Image transmission could open up several possibilities for estate agents, travel agents, design engineers and many others who need to show images and moving pictures to clients over the phone.

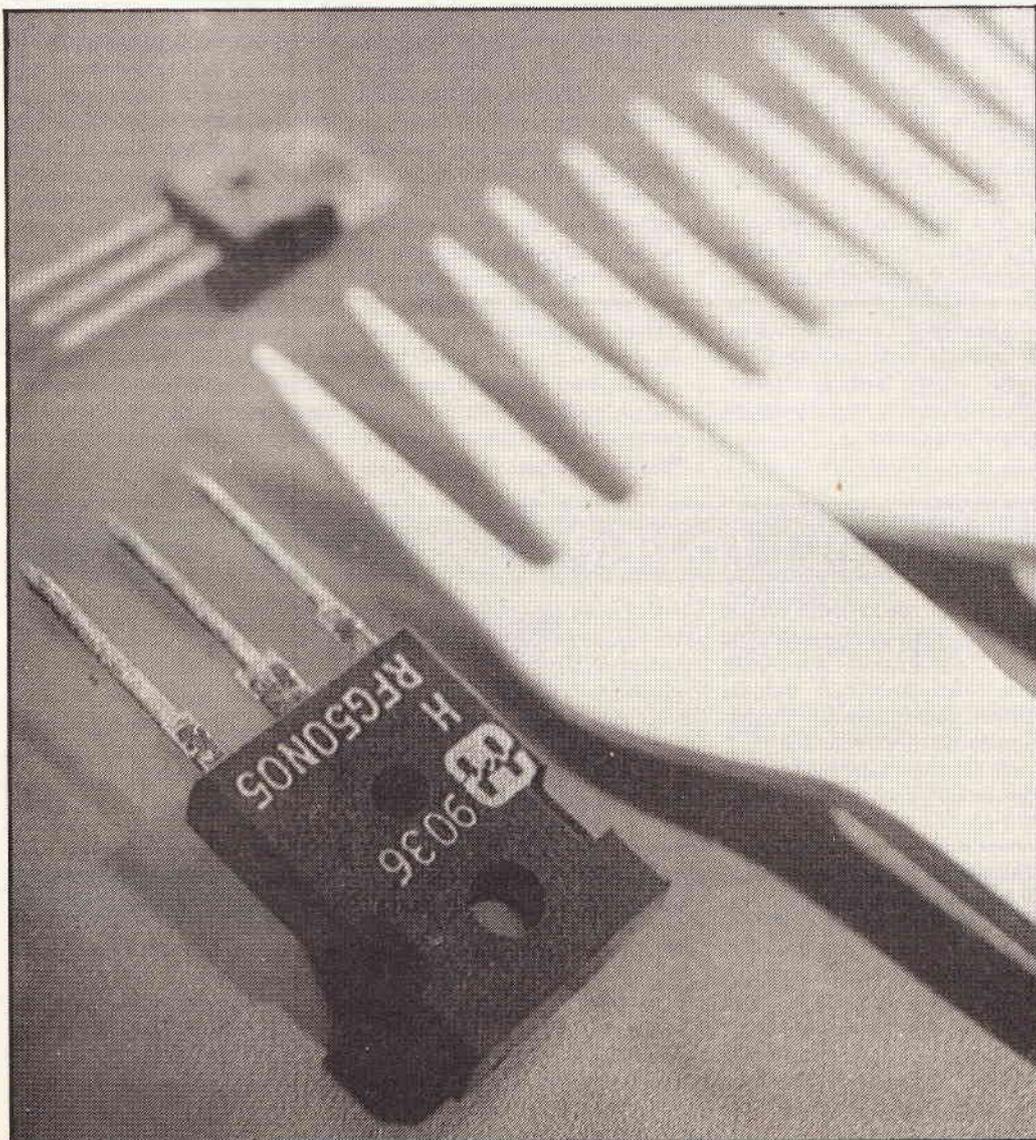JERMYN POWER MOSFET FEATURES LOW ON-RESISTANCE



Now available from Jermyn is a new MegaFET aimed specifically at cost sensitive high power switching applications in automotive, industrial control and power supply circuits.

Known as the Harris Semiconductor RFP/RFG50N05, the device has been electrically ruggedised for use in this type of application. The device has a low resistance when in the on-state with only 22m Ω for the full drain current of 50A. The on-state resistance is one of the lowest for any power MOSFET and has been achieved using MegaFET technology, which uses smaller die sizes to achieve the on-resistance ratings of larger conventional power MOSFETs.

The process employs VLSI ground rules and processing techniques to pack almost 2 million cells per square inch of active silicon area. This is four times greater than conventional power MOSFET processes.

The new RFP/RFG50N05 offers the high switching speeds characteristic of power MOSFETs. Typical turn-on delay and fall times are 15ns and typical turn-off delay and rise times are 50ns typical.

Contact: Jermyn Distribution, Telephone 0732-450144

CIRCUIT DESIGNER MAKES TRACKS

Building small electronic printed circuits has been made easier for schools and colleges with the Quicktrack program for the BBC Master. This computer aided design (CAD) program was refined by trials in schools and colleges and is now sold by the National Council for Educational Technology (NCET) for £25.00. Pupils will often start the design cycle by building a prototype circuit with a systems kit. The development of that prototype into their own printed circuit is where pupils have difficulty. Quicktrack has been shown to help pupils of all abilities overcome that problem.

The young circuit designer uses the computer to assemble pre-designed circuit units on the screen. Components can then be listed from a datafile containing details from the catalogues of well-known suppliers. The final circuit will be small and suitable for fitting into a product design. In one of the trial schools, girls and boys built circuits based on the theme of controlling a premature-baby incubator.

Younger pupils do not need to know a lot about components and circuits, and they can use printed output from the computer to identify the necessary components. Older pupils can do more intensive design work just as easily.

Easier electronic circuit design

is only part of the benefit QuickTrack brings. Unlike the way other programs have been used, this method takes a systems approach and tries to integrate electronics into the design and technology curriculum. Educators should



note the National Curriculum science order prescribes that all pupils should be familiar with electronic control.

The pack includes 80-track ADFS disc, an 84 page teacher-pupil user guide, and data sheets. It is £25.00 including VAT and p&p from NCET sales, Sir William Lyons Road, Science Park, Coventry CV4 7EZ Tel 0203 416994. The datafiles on components can be easily updated.

DESOLDER STATION



The Litesold DSU50 is a British-made de-solder station. The fully earthed metal power unit contains a powerful diaphragm-type vacuum pump remotely controlled from a finger-switch on the de-soldering tool, with an automatic delayed pump shutdown circuit.

The 50 watt, electronically controlled de-soldering tool is connected to the power unit by an anti-static 5mm bore silicone rubber air tube, to a filter mounted in the front of the case, and a multi-way power cord and DIN plug. Power is supplied to the tool at 24V AC.

The de-soldering tool is fitted with a quickly-detachable glass reservoir, to catch removed solder. Special design of the inter-

changeable de-soldering tips ensures that solder removed is kept molten during transfer to the reservoir to prevent blocking. The bores of the tips are lined with stainless steel. Four tips and a set of cleaning tools are provided. An unusual feature of the system is that a vacuum reservoir, closed by a solenoid valve, is pumped down and held until operation of the finger-switch simultaneously opens the solenoid valve and starts the pump. This provides a high vacuum at the nozzle.

Temperature selection of the tool is made from a calibrated scale at the control panel, over the range of 120° to 4200°C. and control is via a closed-loop, fully electronic system.

COMPUTER EXPORT TO VENUS AND JUPITER

An advanced microcomputer called ATAC is helping to guide NASA's Magellan spacecraft on a 15-month, 300 million mile journey to Venus and is now keeping the Mission Galileo probe on course to Jupiter.

The ATAC on-board the

Magellan probe kept the vehicle on course by computing data from the spacecraft's star sighter and then provided vehicle attitude corrections and control outputs that guided the spacecraft on its journey to the planet. The spacecraft was launched by

NASA from the shuttle Atlantis in the spring of 1989 to map the surface of Venus. The Magellan mission was ATAC's first use in outer space.

Mission Galileo is a six-year, 2.4 billion mile journey that took the spacecraft on a looping path

past Venus in February 1990 and back within 620 miles of Earth in December. Two years later the space vehicle will pass Earth again at 200 miles altitude. It will reach Jupiter in December 1995 for a two-year orbit.

BUSINESS WOMEN OF THE YEAR

Awards were presented by Esther Rantzen in February to 13 of Britain's most enterprising women, who have shown outstanding determination and initiative in building successful small businesses, often against great odds.

The overall winner, Pat Meyrick from Plymouth who runs an electronic assembly business received a cheque for £5000 from Barclays Bank to boost her business. Pat set up the contract assembly service in 1988 and now employs 18 people. She now

plans to move into a purpose-built factory.

The national awards scheme, presented by Prima magazine and sponsored by Barclays Bank, was launched last October to highlight the numerous examples of ingenuity and innovation and


encourage Britain's new enterprising women.

Applications were invited from all on-going businesses between one and three years old.

stateside

Pump driven by dual solenoids

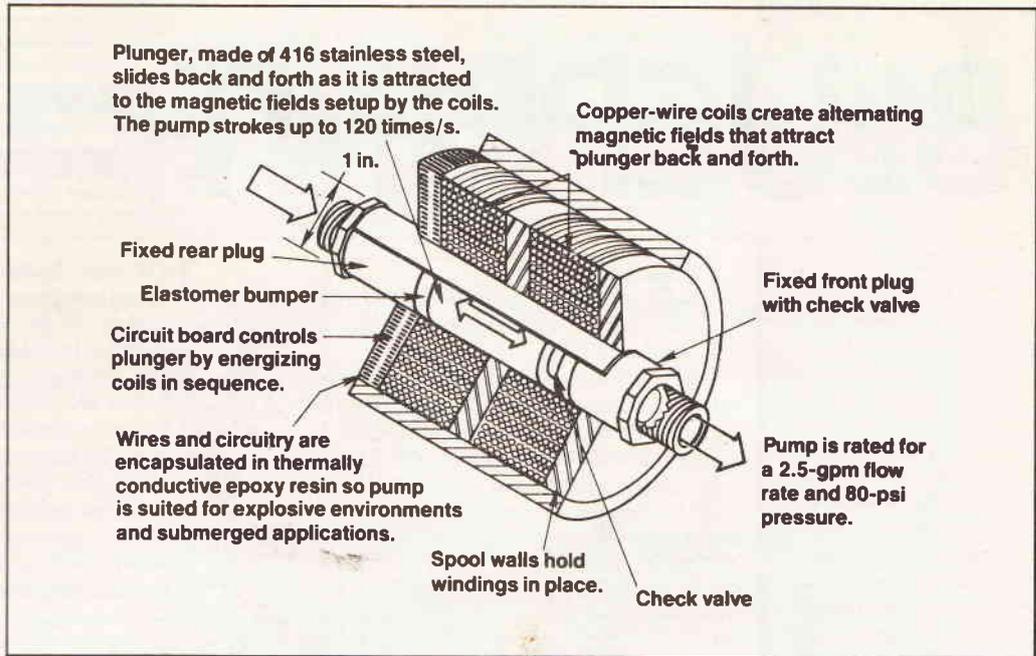Creating opposing magnetic fields that attract a piston back and forth within a cylindrical housing of a new type of pump enables it to be suitable for submerged applications and explosive environments. Electric current, sent at different times through two side-by-side coils



ensures this effect.

The piston, the only moving part in the pump, is driven at up to 120 strokes per second. A circuit board controls the on-and-off sequencing for each coil, so the

pump also functions in variable-flow applications. Fluid direction is maintained with check valves on both the inlet plug and the plunger. No seals are used.

Copper windings and circuit

board are encapsulated in a thermally conductive epoxy resin. The unit can also function as an air compressor

Chip may automate many areas of life

A new chip will help designers to create a new generation of smart products and applications to automate almost every area of life.

The manufacturers say the chip, called Neuron, is not just another embedded micro-controller, but rather the foundation of an embedded operating system of distributed intelligence and control. Like the nervous system of a living organism, a Local Operating Network associated with the chip extends through the entire appliance or component.

The network carries back sensor signals to the Neuron brain, which transmits commands over the LON to actuators and other outputs.

LON technology, in addition to revolutionizing product design, may also bring about changes in personal computers. Less processing power will be needed at the central controller as more intelligence is distributed to peripheral components. Computing power will be redirected to simplify and animate the user


interface, which will likely turn home and office PCs into multimedia control consoles.

The Neuron is described as a communications system on a chip. The IC can sense, count, measure time, and monitor and control switches and relays. These special capabilities stem from a merged CMOS/EEPROM/analog process that packs three CPUs, RAM, ROM, and EEPROM on a 32-pin small-outline package.

Up to 32,000 Neuron-based

applications can be linked by the LON to form intelligent systems within cars, homes, buildings, and factories. Interface transceiver chips that allow Neurons to talk over various media will be available for twisted-pair wire, coax, power line and fibre-optic cable. The Neuron has been developed by Echelon Corp. of Palo Alto, California.

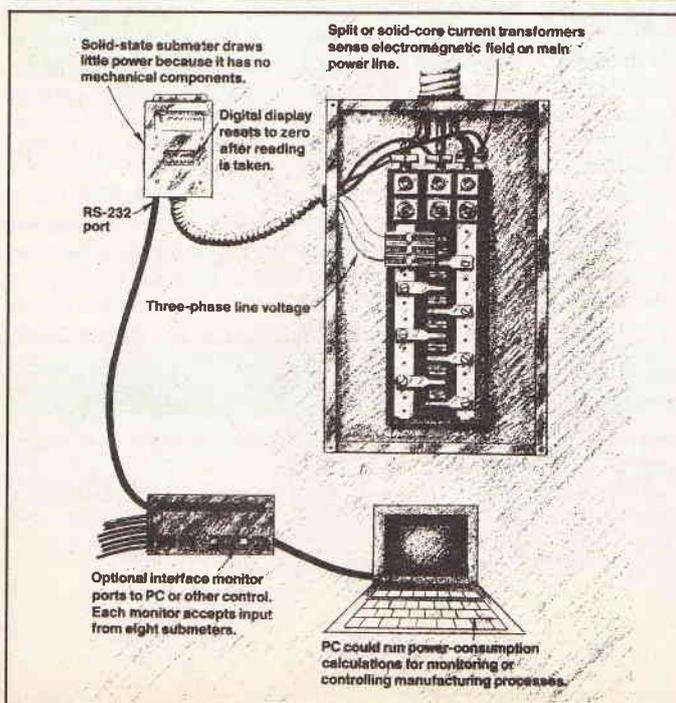ETI will feature an article on the subject of LONs in the near future.



Calculating Power Consumption

A device that has applications for submetering in process control, monitoring consumption, and electrical invoicing, a new electronic submeter with a digital display can fit into a smaller area than conventional electromechanical devices. It uses U-shaped transformers that clip on the outside of power lines to sense the electromagnetic field, and thus occupies a smaller area. Traditional current sensors are much larger than those used in the submeter.

A microprocessor in the unit

calculates power consumption from current power and voltage readings taken from the transformers and directly from the power lines. The integral computer also controls the digital display, which is easier to read than the dials on electromechanical devices.

Called the D-Mon, it operates on single-phase, split-secondary, and three-phase voltage inputs, both grounded and ungrounded. The unit handles up to 600V and 3,200A RMS AC.

E-Mon Corp., Skillman, New Jersey.

EXCLUSIVE READERS OFFER

PORTASOL PROFESSIONAL PLUS FREE SUPER "OCTOPUS"

only £39.95 incl p.&p.

(M.R.P. £49.95)

The Portasol Professional is a completely portable gas operated heat tool providing the professional with a four-in-one precision instrument. The unit is adjustable from 10-60 watts and runs for up to an hour on a single fill from standard lighter refills.

Each Portasol Professional comes complete with four interchangeable tips.

- 1) The Soldering Iron is the ideal static free tool for all soldering needs.
- 2) The Blow Torch operates at a temperature in excess of 1300C which makes it the perfect heat tool for heavy soldering jobs, brazing or silver soldering.
- 3) The Hot Blow is ideal for shrink tubing and is adjustable up to a temperature of 500C.
- 4) The Hot Knife cuts and cauterises synthetic materials and is suitable for cutting and shaping plastics, ropes and is adjustable up to a temperature of 450C.

The Soldering and Hot Knife tips use a unique gauze protected catalytic material to give safe, flameless combustion. New and improved exhaust port design makes for increased heat transfer efficiency.

Don't delay - send now! For your Portasol Professional plus **FREE "Octopus"**

Complete and send your form to: Argus Specialist Publications, Reader Offer, Argus House, Boundary Way, Hemel Hempstead, Herts. HP2 7ST. Or telephone your order stating Access/Barclaycard number on 0442 - 66551. Quoting ROMC/I.




FREE

FREE OCTOPUS WITH EVERY ORDER

RRP £5.95

The extra hands you're always needing.

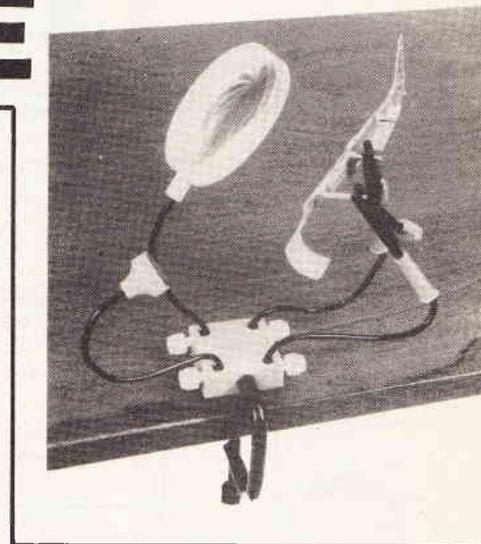

The Octopus has been designed to give the professional or hobbyist a fine, stable working base that won't slip or wobble under pressure. The base block can be fixed in moments with its own simple C-clamp and it features a padded base to protect table surfaces from marking. Use the Octopus for crafts and model-making, holding delicate parts under the magnifier for fine paintwork or tricky assembly jobs, allowing both hands free for intricate soldering and finishing.

Please supply **Portasol Professional + Free Octopus!** at £39.95 incl. p.&p.
ROMC/I

NAME

Or charge my **ACCESS/BARCLAYCARD**

ADDRESS

Account No:

Expiry Date:

Signature:

Paul Coxwell deals with simple AC circuits this month.

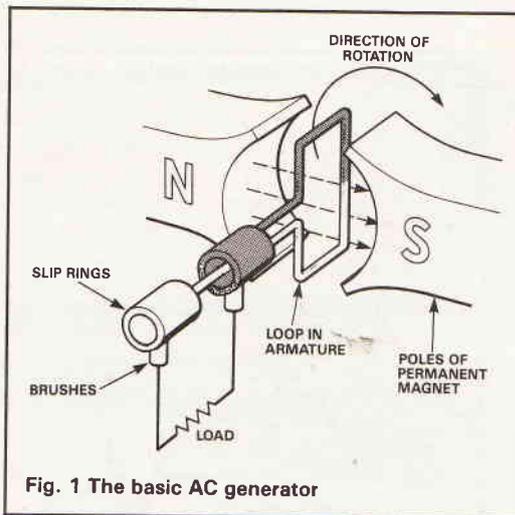


Fig. 1 The basic AC generator

In the first three parts of this series it has been assumed that the power source for a circuit is a battery. In such a circuit the chemical action in the battery ensures that the negative terminal maintains a surplus of electrons and the posi-

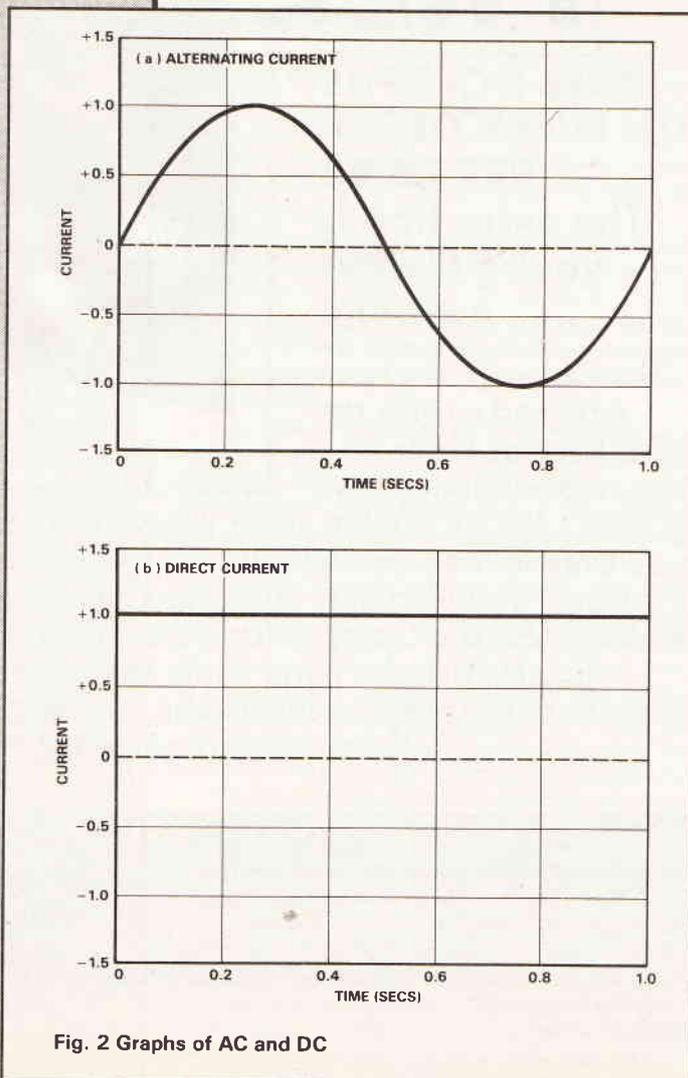


Fig. 2 Graphs of AC and DC

tive terminal always has a deficiency of electrons. Current flow in the circuit consists of electrons flowing from the negative pole of the battery, through the wires and load, and back to the positive pole of the battery. Such a current flow is called direct current, or DC.

Another very important type of electric current, is known as alternating current, or AC.

Figure 1 shows a very simple form of an AC generator. The loop of wire is rotated in the magnetic field, and two slip rings fitted to the shaft allow brushes to connect external wiring to the loop. Recall the right-hand generator rule discussed in part 2 of this series and apply it to the diagram as you follow this explanation. Assume that the loop is rotating in a clockwise direction as viewed from the end of the shaft carrying the slip rings and brushes.

For a current to be induced in a conductor it must cut across magnetic lines of flux. In the position shown, both the top and bottom parts of the loop are moving parallel to the flux lines; the conductor is not cutting through the magnetic field and no current is induced. As the top of the loop (shown shaded) starts to move toward the south pole of the magnet, it will cut across some lines of flux and a small current will be induced in the loop. Application of the right-hand rule shows that the front end of the shaded portion of the loop will be positive.

At the same time, the unshaded portion of the loop is moving toward the north pole of the magnet, and this also causes a current to be induced. This side of the loop is moving up through the magnetic field instead of down, so current will flow in the opposite direction. Because of the way the conductor is looped, it can be seen the two induced currents are actually flowing in the same direction, and aid each other.

By the time the loop has rotated through 90°, each half of the loop is cutting perpendicularly through the magnetic field, and maximum current is induced. As the conductor continues to turn, each side of the loop are moving parallel to the magnetic field once more, and current is zero. Notice the way in which the current starts at zero, gradually increases as the loop turns through 90°, and then decreases to zero again as the loop has completed a half-turn.

In which the current starts at zero, gradually increases as the loop turns through 90°, and then decreases to zero again as the loop has completed a half-turn.

During the second half of the loop's revolution a similar increase and decrease in current will occur, but with one difference: The side of the loop which was previously moving up through the magnetic field will now move down, and vice versa. This causes the direction of current flow to be reversed (confirm this by applying the right-hand rule once again).


One revolution of the generator has resulted in a complete cycle of alternating current: the current flowed one way during the first half-turn and the opposite way during the second half-turn. As the generator continues to turn, this cycle will be repeated indefinitely. It is usual to show alternating current by way of a graph (Figure 2). The horizontal axis represents time and the vertical axis shows either voltage or current flow. The part of the cycle above the zero line represents the current flow during the first half-turn of the generator; that below shows the current

during the second half-turn. The negative values on the graph simply indicate that current is flowing in the opposite direction.

The graph shown assumes that the generator shaft is turning at a rate of one revolution per second. One cycle of alternating current then lasts for one second, as shown on the horizontal axis. If the generator were speeded up to four revolutions per second, the resulting AC output would be at a rate of four cycles per second or 4Hz. The number of cycles

To return to Figure 3, we have seen that the peak value is 1V. The peak-to-peak value, is the difference between the positive peak value and the negative peak value. In a sine wave which has equal positive and negative peak values, the peak-to-peak value will be double the peak value. The AC shown has a peak-to-peak value of 2V.

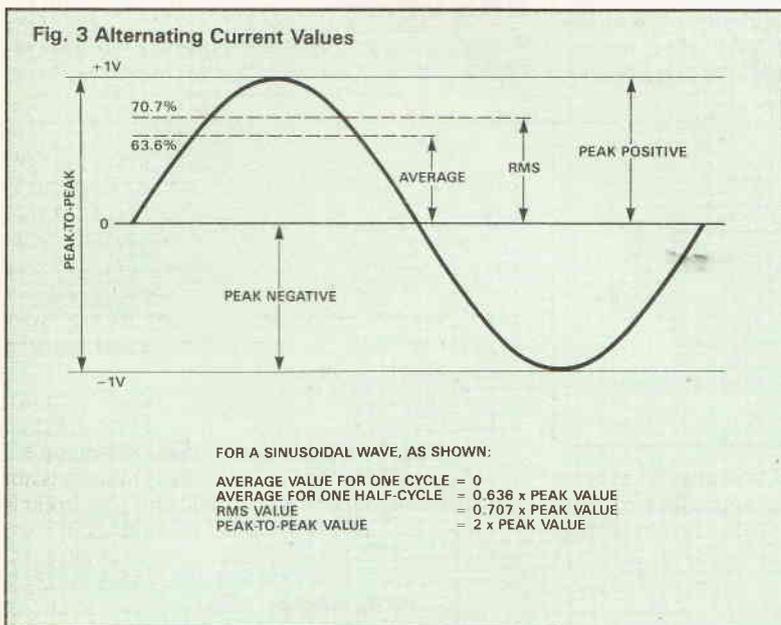The average value of a complete cycle of AC is zero; the positive and negative peak values are equal and therefore cancel each other out. It can be shown mathematically that the average value of one half-cycle of a sine wave is 63.6% of its peak value. A peak value of 1V, therefore, results in an average value of 0.636V. Average



per second produced is called frequency.

Most practical AC generators run at much higher frequencies than those shown here. The power distributed to your home, has a frequency of 50 or 60Hz depending upon the part of the world in which you live (50Hz is the standard in Britain; 60Hz is normal throughout North America).


For comparison, Figure 2 shows how a direct current would appear graphically. Notice how the current never fluctuates, but remains fixed at one level.

AC Values

When examining direct current, we saw four important quantities which may be measured: voltage, current, resistance, and power. If you look at the graph of an AC waveform, it may seem difficult to measure the exact value of voltage or current, because they do not stay at one fixed level.


There are several different measurements that may be made with AC and these are shown in Figure 3. The simplest two to understand are the peak value and the peak-to-peak value. In the example shown, the highest point that the AC cycle reaches is marked as 1V on the graph's vertical scale. The peak positive value is, therefore, 1V. Similarly, the lowest value reached by the cycle of AC is -1V, so the peak negative value is also 1V. In many cases the peak positive value and peak negative value will be equal, but not always. This brings us to an important point.

The cycle of AC shown is sinusoidal; that is, the graph shows a single cycle of a sine wave. This is the shape of AC from a standard generator, and many calculations only work correctly on sinusoidal waveforms. Alternating current may be of different wave shapes; the "alternating" part simply means that the direction of current reverses at some point during the cycle. As this series is only examining electrical basics, we shall not be seeing any non-sinusoidal AC, so the peak positive and negative values will be equal.

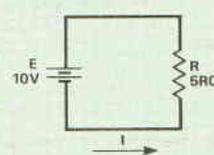

$$I = E/R = 10V/5\Omega = 2A$$

$$P = EI = 10V \times 2A = 20W$$

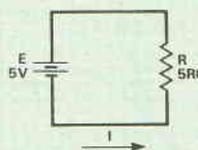

$$I = E/R = 5V/5\Omega = 1A$$

$$P = EI = 5V \times 1A = 5W$$

Fig. 4 DC power calculations

values are not used extensively, because they complicate power calculations.

In last month's article, we saw that power is directly proportional to both current and voltage. Ohm's Law tells us that in a circuit with fixed resistance, current is directly proportional to the applied voltage. The two formulae required are shown in Figure 4; apply them to the first circuit (which is DC, remember), and determine the current flow and power dissipation for the load resistor. (The calculations are shown in Figure 4, but try to perform them by yourself first).

The second diagram shows that the 10V battery has been replaced by a 5V type; the value of resistance has not been altered. Perform the calculations again to determine the new values for current and power.

You should now notice two things: Having the supply voltage has resulted in half the original current, but has caused the power to be reduced to one quarter of its former value. This is to be expected — power is proportional to both voltage and current and both have been halved. We can now state that in a circuit with constant resistance, the power increase varies with the square of the voltage increase (i.e. doubling the voltage increases power by four, multiplying the voltage by three would increase power by a factor of nine, and so on).

The next step is to apply this principle to an AC circuit (Figure 5). Assume that the resistance is the

same as before (5R) and that the peak value of the AC voltage is 10V. Ohm's Law may be applied to AC circuits as well as DC ones, so long as you remember that using peak voltage will give peak current, or average voltage will give average current, and so on. The peak value of the AC is calculated as for the DC circuit in Figure 4, and the result is 2A peak.


Because the value of the AC supply voltage is fluctuating, the current will vary in direct proportion. When the voltage is at 2V, for instance, the current will be 0.4A (confirm this with Ohm's Law). The graph in Figure 3 shows voltage and current plotted on the same axes (the curves are labeled E and I, respectively). Notice how when voltage is at its peak, so is

sine-wave. It differs from the voltage and current curves in that it does not go below the zero line to a negative value. Its minimum value is zero, and its maximum value is 20 watts; so the average power must be 10 watts.

If you compare the first circuit of Figure 4 with that of Figure 5, you should see that 10V peak AC only provides half the power of 10V DC. Clearly, it would be much easier if the figures could be made to correspond.

RMS Values

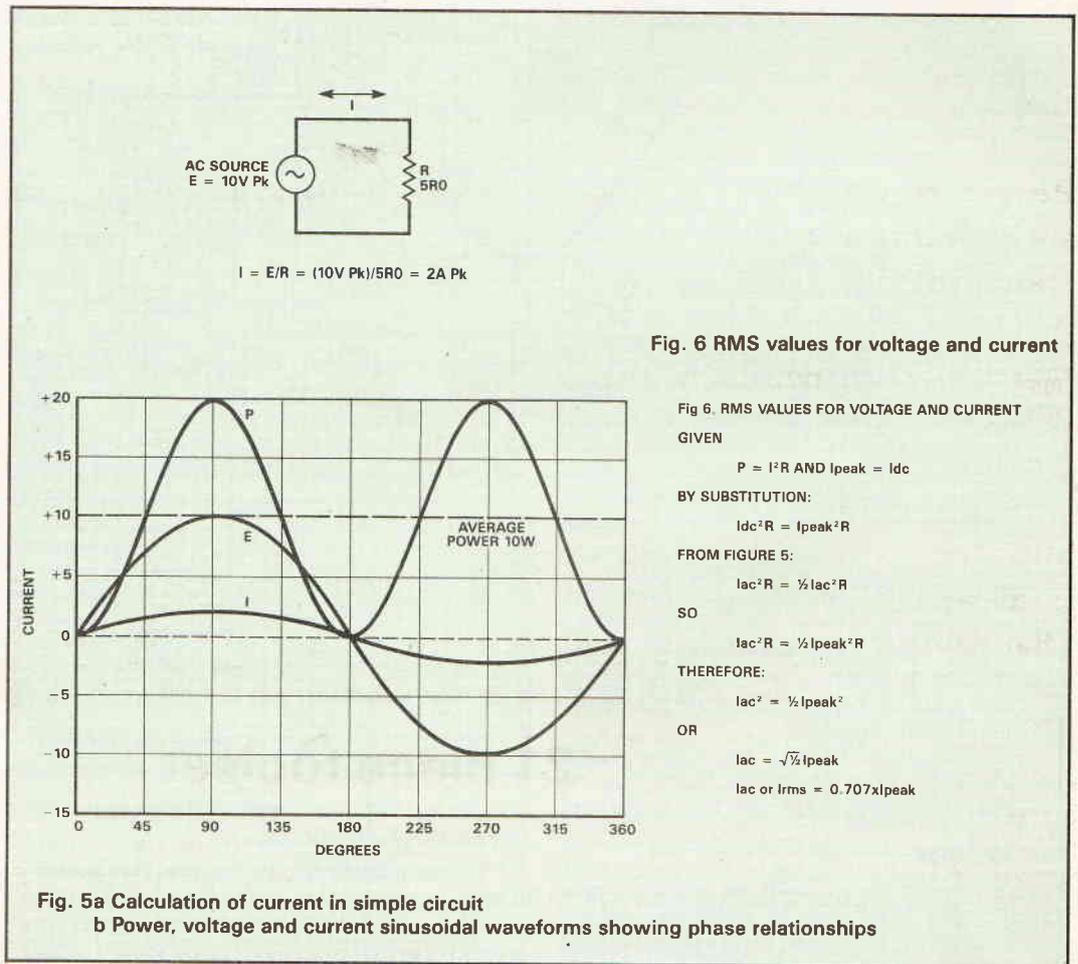At first sight, it may appear the average AC value of 63.6% of its peak value would work. Applying these



current. The two waveforms are said to be 'in-phase', meaning that they both reach their positive peak at the same time, both reach their negative peak at the same time, and both cross the zero line at the same time. The scale for the vertical axis is not marked with any units: the numbers represent volts for the voltage waveform and amperes for the current waveform.

The third waveform on the graph represents power. You have learned that power is equal to the product of voltage and current, so the power curve may be plotted by taking a number of points along the time axis and finding the product of the E and I curves at that point. It should be fairly obvious that the power will be zero when both voltage and current are zero, and that the power will be at its maximum value when voltage and current are also. Look at the second half-cycle carefully, and notice how the product of two negative numbers (i.e. voltage and current) gives a positive value for power. A negative value would imply that the resistor is supplying power rather than using it, which is impossible.

You should see that the power curve is also a

figures to Figure 5 would give an average voltage of 6.36V and an average current of 1.272A. Calculating the average power from these figures gives the incorrect result of a little over 8 watts. The error has come from the fact that both current and voltage have been reduced to 63.6% of their peak value, which when combined has reduced the power to under 41% of its peak value (0.636 squared is 0.405).

The examples above have shown that AC power is half the DC power if the peak AC voltage is equal to the DC voltage. Figure 6 shows a formula which appeared last month — it shows that power is equal to the square of the current multiplied by the resistance. Using this formula and some simple algebra, the effective AC current can be calculated. The last line gives the important point to remember: The effective value of an AC sine-wave is 0.707 times its peak value. This effective value is called the 'root-mean-square', or RMS, value.

In Figure 5 we saw that the average power dissipated by the resistor was 10 watts. Figure 7 shows the same circuit but with the RMS value of the voltage

source shown (7.07V). Ohm's Law shows that the RMS current is, therefore, 1.414A. If these values are now applied to the power formula, the same answer of 10 watts is obtained. More importantly, it should now be clear that in order to get a power of 20 watts (the power in our original DC circuit), the AC voltage must be increased to 10V RMS. An AC source of 10V RMS, therefore, provides the same amount of power as a DC source of 10V. We have now made the values conveniently coincide between AC and DC circuits.

It is RMS values that are most often used when dealing with AC circuits, and it is usual to speak of '100V AC', meaning 100V RMS. If an AC voltage or current is given without any reference to it being a peak, peak-to-peak, or average value, it should be assumed to be a RMS value. The voltage of normal household supplies in Great Britain, for example, may be specified as 240V. The figure of 240V is in terms of RMS, which can be converted to a peak value by multiplying by 1.414 (which is the same as dividing by 0.707). The peak value of the supply is 1.414 times 240, or 340V. The peak-to-peak value is double the peak value: 680V.

Summary

We have covered some important ground in this discussion of alternating current. The following are the key points which should be remembered.

In an AC circuit with resistance, Ohm's Law applies just as it does to DC circuits. Using the basic equation:

$I = E/R$, for instance, gives rise to formulae such as

$$I_{RMS} = E_{RMS}/R \text{ and}$$

$$I_{peak} = E_{peak}/R$$


The average value of a complete cycle of regular

sinusoidal AC is zero. The average value of one half-cycle is 63.6% of its peak value.

The effective, or RMS value of AC is 70.7% of its peak value. The RMS value of AC gives the same amount of power as a DC source of the same voltage, e.g. 10V AC, RMS gives equivalent power to 10V DC.

When dealing with AC, RMS values should be assumed unless stated otherwise.

Fig. 7 Using RMS values

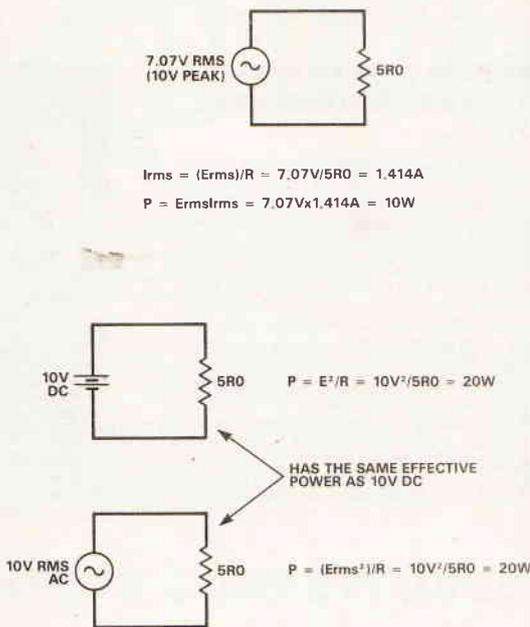

E.T.I. Reader Offer

21 piece toolset

This superb 21 piece toolset offers an invaluable selection of screwdrivers, wrenches and nut drivers in all the useful, smaller 'modelling' sizes and will be in constant use around the workshop.

Here's what you get!


Five crosspoint hex key wrenches/screwdrivers in 4, 4.5, 5, 5.5 and 6mm sizes.

Five precision wrenches in 3, 3.5, 4, 4.5 and 5mm sizes.


Five Hex nut drivers in 1.5, 2, 2.5mm, No. 0 and No. 1 sizes.

Six slot screwdrivers in 1, 1.4, 2, 2.4, 3 and 3.5mm sizes.

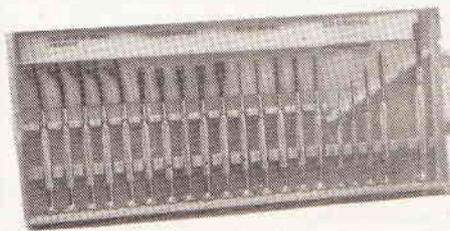And each tool is individually labelled in the handy plastic container for easy access. You'll wonder how you every managed without them!



only
£7.99
inc. p&p

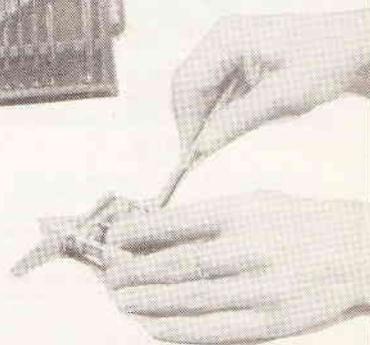

ASP Readers Offer, Argus House,
Boundary Way, Helel Hempstead, Herts HP2 7ST

Please supply RORM/14 @ £7.99

I enclose my cheque/P.O. for £ payable to A.S.P. or

debit my Access/Visa / /

Signature Expiry date


Name

Address

**Telephone orders . . . just call
us on 0442 66551 (24 hours)**

SAVE MONEY ON YOUR RADIO EQUIPMENT

with **ARGUS BOOKS**

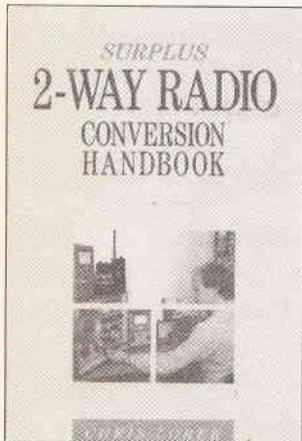

SURPLUS 2-WAY RADIO CONVERSION HANDBOOK

- Chris Lorek

As 2-way radio equipment, used by the police, ambulances, etc is replaced, these sets become available on the surplus market at very economic prices, and they can often outperform purpose designed amateur radio equipment. In this book, Chris Lorek explains how to modify them to amateur frequencies. He describes the equipment suitable for conversion, together with relevant photographs and sources of supply, gives alignment and modification details and covers virtually every variety of surplus Pye equipment suitable for modification. This is the reference and handbook that all amateur radio operators have been waiting for!

ISBN 0 85242 946 0 £10.95



PRACTICAL IDEAS FOR RADIO AMATEURS

- Ian Poole

The author, a regular contributor to *Ham Radio Today*, gives some useful hints and tips for amateur radio enthusiasts in this book. There are six main sections dealing with shack, aerial construction, components, circuits and testing. The book concludes with useful formulae and tables.

ISBN 0 85242 917 7 £6.50




SCANNERS 2 INTERNATIONAL

- Peter Rouse

The companion book to the best selling **Scanners** provides even more information on the use of VHF & UHF communications bands and gives details on how to construct accessories to improve the performance of scanning equipment. The book is international in its scope and contains frequency allocations for all three ITU regions, including country by country variations.

ISBN 0 85242 924 X £9.95

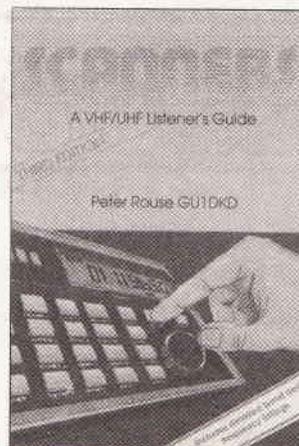

SCANNERS 3RD EDITION

- Peter Rouse

A new and revised edition of the most comprehensive guide ever published in Britain. This book explains in simple terms how the VHF & UHF bands are allocated to different users. It also covers equipment, accessories and aerials and explains basic radio theory, modes, and simplex and duplex transmissions. British bandplans from 26 to 1300 MHz are a major feature of this book, and a review section surveys the equipment currently available in the UK.

ISBN 1 85486 006 2 £8.95

HOW TO ORDER BY POST

- 04045 SURPLUS 2-WAY RADIO CONVERSION HANDBOOK £10.95
 04040 PRACTICAL IDEAS FOR RADIO AMATEURS £6.50
 04088 SCANNERS 2 INTERNATIONAL £9.95
 04188 SCANNERS 3RD EDITION £8.95

Please add 10%, min. 75p for postage and packing.

Please make cheques payable to Eddington Hook Ltd and send to the address below.

I enclose my remittance of £

Please charge my access/mastercard/barclaycard/visa

No.

Expiry Date

HOW TO ORDER BY PHONE

TELEPHONE (0732) 357755 Please ask for the Argus Order Dept. Quote access/mastercard/barclaycard/visa. Allow up to 28 days for delivery

Signature

Name


Address

..... ETE1

Complete details and return form to:

Eddington Hook Ltd, 406 Vale Road, Tonbridge, Kent TN9 1XR

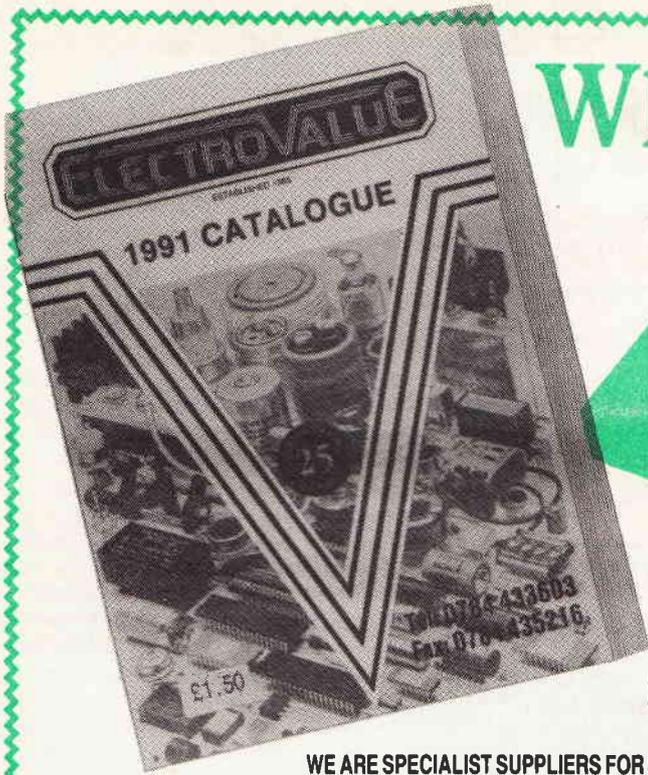Please ensure that all cheques are made payable to Eddington Hook Ltd.



What's so *Special* about

PAGE 37?

and pages 45, 55, 58 among others

Simply that these are some of the pages which show how exceptionally wide and varied are the ranges of COMPONENTS, PRODUCTS and MATERIALS to be found in our 1991 Catalogue. Much practical information is included and it's all well presented, illustrated and easy to look up — and to order from.

IT'S ALL IN THE NEW, LARGER (A.4) ILLUSTRATED 80 PAGE (PLUS COVERS) 1991 ELECTROVALUE CATALOGUE

WE ARE SPECIALIST SUPPLIERS FOR SIEMENS FINE QUALITY COMPONENTS

Please send £1.50 (cash/PO/cheque/stamps) for your 1991 EV catalogue (postage paid in UK) We give you a refund voucher for £1.50 usable towards your next order for £5.00 or more.

ELECTROVALUE

FOR QUALITY COMPONENTS COMPETITIVELY PRICED

Catalogue orders to:—
ELECTROVALUE LTD, 28a ST. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB
Phone: 0784 433 603 Fax: 0784 435 216

MAKE YOURS A FREE COPY

CRICKLEWOOD ELECTRONICS



Now!
Nothing to stop you owning a Cricklewood catalogue


Now free!!

(Whilst stocks last) One of the most comprehensive components catalogues in the business.

Over 13,000 different components from all over the world, the Cricklewood Catalogue is a must for the hobbyist and professional. Simply write, phone, fax or telex for a free copy

90's decade first edition free

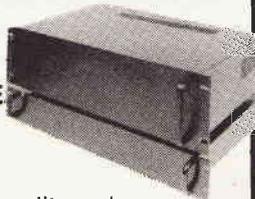- ONE OF THE LARGEST RANGES OF COMPONENTS IN THE UK
- FAST AND EFFICIENT SAME DAY PERSONAL SERVICE
- VERY COMPETITIVE PRICES, QUANTITY DISCOUNTS AVAILABLE
- DISCOUNT VOUCHERS INCLUDED
- NO MINIMUM ORDER



Orders accepted by credit card



19" RACK CASES

* Suitable for instruments, high quality amplifiers and many other applications that demand strength and professional finish * New improved construction and finish * Black anodised aluminium front panels * Separate front mounting plate, no fixing screws visible on the front and the side of the enclosure * Heavy gauge front panels of brushed aluminium finish enhanced with two professional handles * With ventilation slots and plastic feet * Rear box manufactured from 1.1mm steel finished in black. Rack mounting or free standing. Comes in quick assembly flat package.

Order Code	Panel Size W H (inch)	Rear Box W H D	Weight	Price
U112	19x1.75	17x1.5x12	2.5kg	24.95
U212	19x3.5	17x3.0x12	3.3kg	29.75
U312	19x5.25	17x5.0x12	4.0kg	31.95
U412	19x7.0	17x6.5x12	4.6kg	34.95

Please add £3.00 P&P for the first item and £1.50 for each additional item.

Please add VAT to above prices. Overseas orders welcome

CRICKLEWOOD ELECTRONICS LTD, 40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET
TEL: 081-450 0995/452 0161 FAX: 081-208 1441 TELEX 914977



The physics of how we hear stereo images by Ronald Wagner.

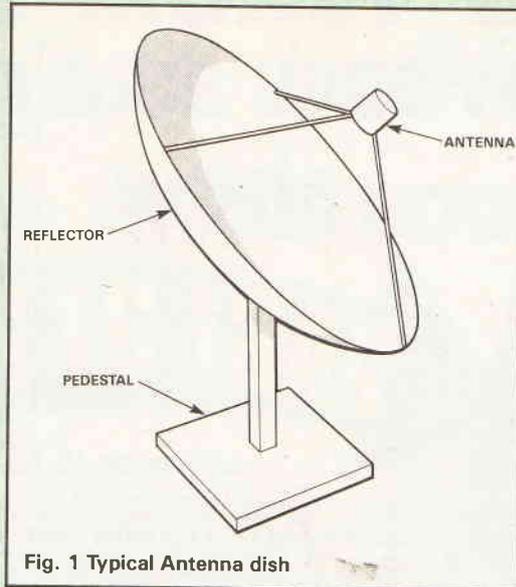


Fig. 1 Typical Antenna dish

The word image has several definitions. It may, for instance, be used to describe how close one object resembles another. In business, many corporations and privately owned companies have an image. In this situation, the word is used to indicate that they are diversified, progressive, technically competent or have the ability to provide products and services of the highest quality. Most of them are extremely conscious of how this projected image affects their customers, creditors and investors. Because it is an important factor in their business operation, they also spend large sums of money to maintain the desired effect.

In addition to the examples already mentioned, individuals can also have a simulcrum. In this case, the picture might be one of wealth, physical fitness or education. The common link between the commercial and the individual image is their creation. Both are manufactured by the mass media.

Stereo Imaging

The word stereo is from the Greek word that means solid observation. People obtain stereo imaging in two ways. In the visual system, our eyes are about 65mm (2½ inches) apart. This physical separation produces a slightly different view of the same thing. Each eye is connected to an optic nerve transferring the image to the brain. Here, sensory signals are combined to produce a visual picture that has three dimensions.

Sonic Imaging

Auditory images are produced by a similar process. Our ears are 150-200mm (6-8 inches) apart and they receive slightly different auditory stimulation. Their separation however, is not the only factor that affects auditory imaging. Others are related to the hearing process, the characteristics of the source and in many instances the environment where the sounds are produced. Before discussing the later two, it helps to understand the physiological concepts that contribute

to our sense of hearing and how it affects this type of stereo imaging.

The Auditory Systems

The human hearing mechanism can be divided into four main sections. These are: the external ear, the ear canal, the middle and the inner ear. Their combined function controls the performance of our auditory system and each of them serves a specific purpose.

External Ear

As a beginning, suppose we start with the most obvious part. In many ways our external ear is similar to a satellite television antenna. The large dish or reflector gathers in the very small satellite signals, and focuses them on to a receiving antenna (Figure 1). The major characteristics that are important to an operating antenna are its frequency response, gain and directivity.

To obtain maximum performance, antennas are built for a specific range of frequencies. For satellite reception this is approximately 3-6GHz. Although these frequencies are very high, their range or bandwidth is limited to approximately one octave.

The gain of an antenna is a number that indicates how its performance compares to a reference antenna. If a certain antenna has a gain of 3 dB, then its output would be twice that of the standard antenna. High gain antennas are often used to improve a systems signal to noise ratio.

Directivity, on the other hand, is an indication of how the gain varies around the antenna's central receiving axis. When the antenna is pointed directly at the source, it obtains the maximum signal. If the antenna is positioned so this axis is at right angles to

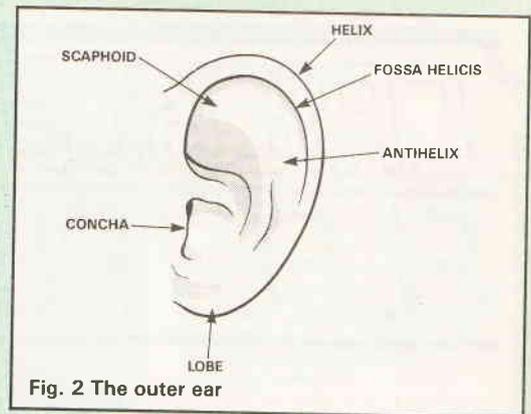


Fig. 2 The outer ear

the satellite signal, its output would be zero. The maximum signal strength is maintained by mounting this type of an antenna on a rotating mechanism and turned for best reception.

Although the external ear, called the auricle or pinna, is smaller and has a different shape to the satellite antenna, it also functions like the reflector. If you look at your ear in a mirror, you will notice that it contains several ridges and valleys (Figure 2). This rolling surface, together with parts of the body, reflects

How's Your

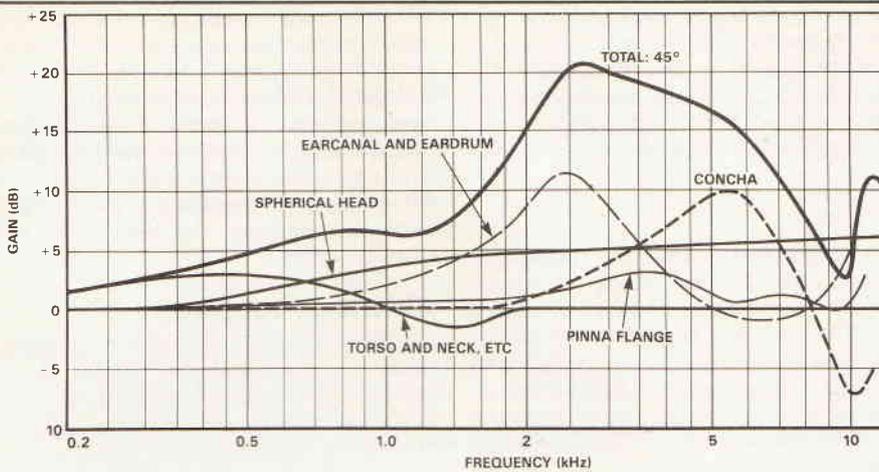


Fig. 3 Response of outer ear

the sound waves toward the ear canal.

The ear drum is at the other end of the canal. Its purpose is similar to the receiving antenna. Reflections from the head and body increase the signal at the ear drum by approximately 15 to 20 dB. The acoustical contribution obtained from some of the significant parts of our anatomy is shown in Figure 3.

The ridges and valleys of the pinna also perform another important purpose. When a sound strikes the ear, the undulating surface creates an acoustic pattern similar to the original sound. These distinct patterns are used by the auditory system to establish the source location^(1&2). As indicated in Figure 4, the maximum auditory gain is obtained when the source is located at an angle of 45° with respect to our ears.

While the size is the most obvious difference between a satellite antenna and the ear, the frequency range and bandwidth of operation are also different. As already stated, the antenna's frequency range is very high, but its bandwidth is low. Just the opposite is true in the auditory system. The frequencies we hear are low, but they cover a bandwidth of 10 octaves.

The directivity of the satellite antenna is determined by the shape of its reflector. The ears directivity is determined by two different mechanisms. When a sound is produced in the lower portion of the audible range, its wavelength is very long. A 100Hz

tone, has a wavelength of 3.41m (134.4 inches). This number is so large in comparison to the ears separation that they both will receive approximately the same amplitude. In this situation, the source location is determined by the difference in the sounds arrival time. If the 100Hz source was directly opposite the left ear, the sound would arrive at the right one about 0.5 ms later.

In the upper frequency range, where the wavelengths are short, (1kHz.) the head acts as a shield. A sound originating from a line opposite one ear will be attenuated before it reaches the other one.

Ear Canal

To be heard, a sound must enter the ear canal (Figure 5). This opening is about 5mm wide and about 28mm long. The ear drum, or tympanic membrane, is located at the inner end of the canal. Due to this location, it acts like a pipe that has been sealed at one end. Maximum sound pressure will occur at the ear drum, when the wavelength of the sound is four times the pipe length. This is approximately 2847Hz., and both Figures 3 and 4 have a peak in this region.

In addition to terminating the ear canal, the ear drum is also part of an impedance matching device. On the side where the canal is located, the impedance of the air is very low. The inner ear, shown as the

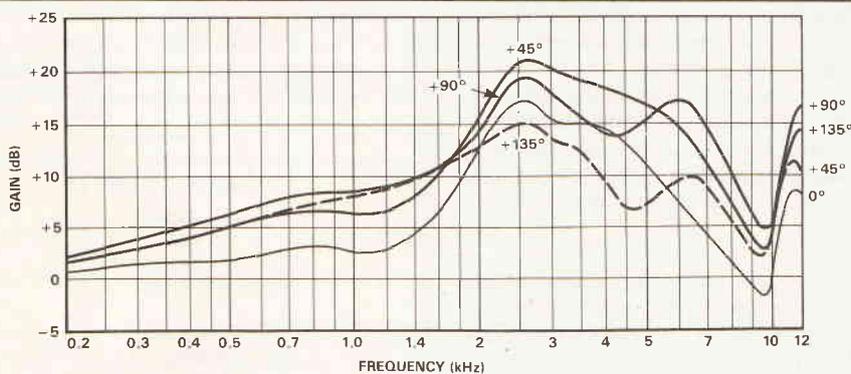


Fig. 4 Response showing gains for different angles

ur Image?



cochlea in Figure 5, contains a fluid having very high impedance. Maximum energy transfer occurs when the source and load have the same impedance. The ear drum and the middle ear must therefore act as an impedance converter. Without it, 99.9% of the acoustic energy that strikes the ear drum would be lost.

Middle Ear

Besides being a contributor in solving the impedance problem, the middle ear also changes acoustical energy into a mechanical force. This is accomplished in two ways. The ear drum is connected to three very small bones called the *ossicles*. The first two are fairly rigid. As the ear drum moves, they transfer the corresponding motion to an inner bone called the stapes. It, in turn, is connected another membrane called the oval window. As shown in Figure 5, this element separates the middle from the inner ear.

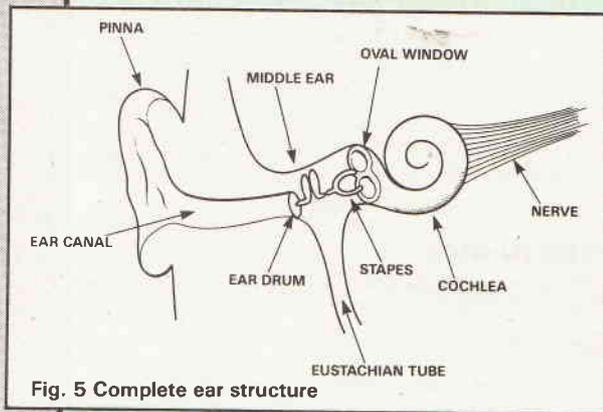


Fig. 5 Complete ear structure

Both the ear drum and oval window perform a similar function. When a sound strikes the ear drum, it produces a force that is equal to the pressure multiplied by the area of the ear drum. This energy is transferred by the ossicles to the oval window. Due to the size difference, the force at the oval window is increased by 17.5. See Figure 6a.

In addition to the increased pressure, the bones which link the oval window to the ear drum create an additional force. As indicated in Figure 6b, the three bones act as a fulcrum. The total force on the oval window is the product of 1.3 (produced by the fulcrum) and the 17.5 from the size difference. This increase is equal to 22.75 or 27dB.

The muscles of the middle ear also have an effect on what we hear. Very loud sounds below 1kHz are attenuated by approximately 12 to 14 db. This provides some protection against loud continuous sounds, but not those that are transient in nature.

Inner Ear

Like the middle ear, the inner ear performs several functions. Its main purpose, is to change the mechanical force that appears at the oval window to neurological impulses. As shown in Figure 5, its shape is similar to that of a snail. For this reason it is called cochlea, being Latin for snail.

The cochlea contains tiny hair cells immersed in a fluid. When the stapes pushes against the oval window it creates a motion in this fluid causing the tiny hair cells to vibrate, each one responding to a different frequency. The overall effect is similar to a third octave filter, and this is one reason why this type of analysis is an important acoustic measurement.

Nerve endings (part of the acoustic nerve) carry the motion of the hair cells to the brain as neurological impulses. Here they are combined, and the encoded information identifies the type and source of the sound.

In essence a sound wave that started as a variation in atmospheric pressure is directed towards the ear canal, increases in value through the middle ear, changed to a mechanical force and passed on to the inner ear. Hair cells encode the resulting force producing a neurological pulse in the brain. The outcome is then identified as being the music of a symphony, the sounds of a baby crying or some other pleasurable or raucous noise that has become part of our every day lives.

Hearing Problems

The preceding explanation has indicated how a normal hearing system functions. When the auditory mechanism has a defect, the result is divided into two categories. Hearing loss before the cochlea is a conductive loss and produces a frequency dependent attenuation. This can quite often be cured by either a hearing aid, antibiotics or surgery.

A hearing loss occurs in the cochlea or auditory nerve is sensorineural and usually develops with advancing age. It, as yet cannot be cured (see Figure 7).

Auditory Images

In a visual system, the three dimensional effect was obtained because each eye received a slightly different view of the same object.

As stated, auditory imaging is related to the difference in a sounds amplitude and arrival time at each ear. The Haas effect, published in 1951⁽³⁾, verified this concept. In his experiment, Haas used two sources. Each one could be independently controlled in both its amplitude and acoustic delay. After trying several locations, the two sources were positioned at an angle of 45° with respect to the listeners position. As shown in Figure 4 this arrangement produces the greatest ear sensitivity.

When two sound sources are arranged so their outputs have equal amplitudes and arrival times, the brain must determine if they are located in front or behind the listener. The solution to this problem is determined by the ridges and valleys of our ears. Those sounds which occur in front of a person will

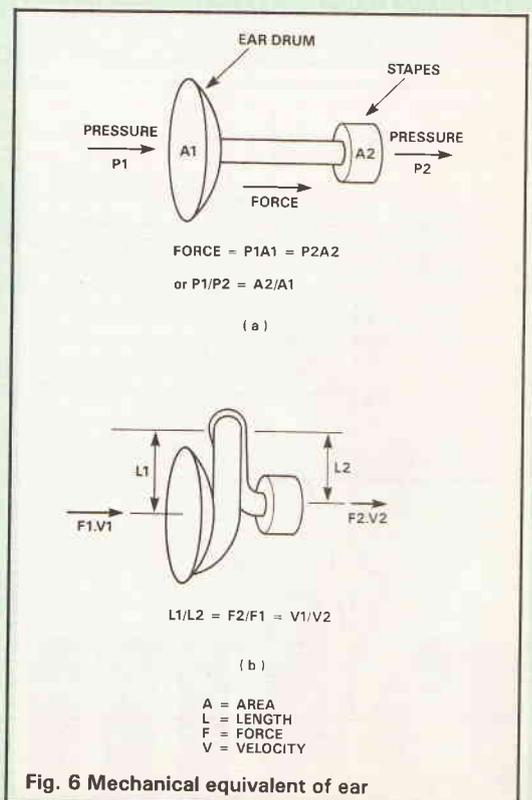


Fig. 6 Mechanical equivalent of ear

have a different neurological pattern from those that originate behind us.

Of course, not all sounds arrive at our ears concurrently. When one ear is stimulated before the other it can be the result of several possible conditions. If the acoustic delay is between zero and approximately one millisecond the brain will conclude that the sound is coming from the side that received the first stimulation. In this time range, the difference in the arrival time also produces an apparent increase in the perceived loudness. In affect it modifies the sound source and this enhances the stereo image.

As the delay between each ear increases toward 10ms, the localization process becomes less apparent. Although both sources may still produce the same acoustic level, our perception of the second source becomes less apparent. Haas concluded that our hearing process locks on to the sound that arrives first. It then ignores those that arrive in the range of 10-30ms (Figure 8). This phenomena was also reported by James Moir⁽⁴⁾.

During this time, the amplitude of the delayed sound does not alter the imaging process. If it is 10dB louder than the sound that arrives first still does not contribute to the imaging effect. It is perceived as another sound source.

When the delayed sound exceeds 30ms, it is heard as an echo. To the average listener this time is of little interest. Most home listening environments cannot produce a delay of this length.

Besides the Haas publication, a similar experiment was described by Wallach⁽⁵⁾. His effect was called precedence. The most interesting aspect of these two experimental procedures is the conclusion. Although each scientist used a different technique, they both arrived at the same result.

The Listening Environment

When a stereoscope is used to view photographs that create a stereo image, the relationship between the pictures, the lens and the eyes are well controlled. Each picture has a separate lens to focus the image on the appropriate eye. Additionally the lenses are aligned so the images are shifted toward each other. This process blends them together, and the viewer obtains the best stereo effect.

Good audible imaging relies on similar techniques. In this situation, the sound is comparable to the pictures of the stereoscope. The speakers function as the lens, and the eyes are replaced by the ears. The major difference between these two methods is the dimensions.

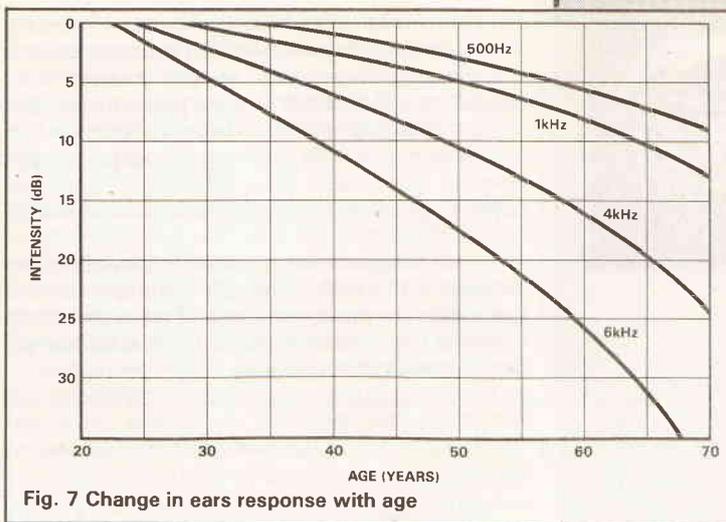


Fig. 7 Change in ears response with age

In a stereoscope, the components are only a few inches apart. Except for some extreme conditions, the result is not usually influenced by the environment. When sounds are produced by a loudspeaker, the dimensions between the different components is in the order of metres or feet. The imaging is now affected by both the characteristics of the speakers and those of the surrounding environment.

The Source

The purpose of a loudspeaker is to change electrical into acoustical energy. In performing this task, there are many factors which contribute to its effectiveness, one being efficiency. This parameter determines the input power required to produce an acceptable listening level.

Another factor is the amount of distortion the speaker produces. If it is too high, the result is a muddy sound that interferes with the imagine effect. A third speaker characteristic is its frequency response. In the previously described Haas and Wallach hearing tests, the positions of the sound source was easily identified. This was due to the transient nature of the test signals. With a continuous sound such as a steady tone, the hearing mechanism has a lot of difficulty in locating the source. A speaker system that does not have an adequate frequency response will not only have poor transient response, but also poor imaging.

Figure 9 indicates how a speakers acoustic output varies as a function of the radiated frequency. Over the 'C' region the cone of the loudspeaker acts as a piston, and the frequency response is flat. For

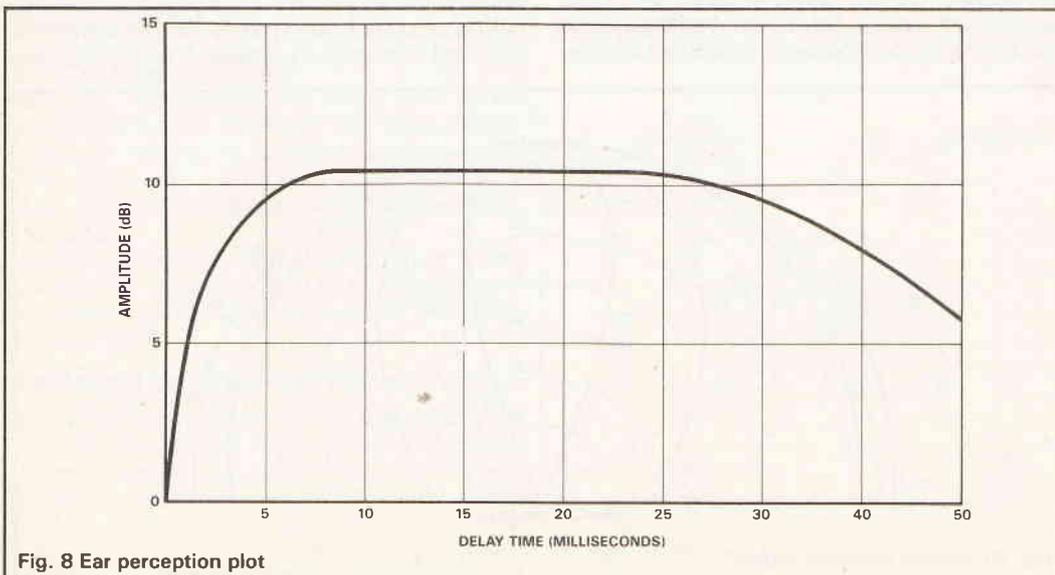


Fig. 8 Ear perception plot



monophonic listening, where the listener is situated on the speakers axis, this is an adequate presentation.

Unfortunately, many people position their speakers so the principle listening position is located off axis. The graph of Figure 9 does not provide any indication of how the acoustic output varies for these listening conditions. This information must be obtained from a graph similar to the one shown in Figure 10.

In this diagram, the zero line corresponds to the speakers axis, and the adjacent numbers indicate a loss in dB. The horizontal line, and those projecting outwards from its intersection with the axial line are the off axis angles in degrees.

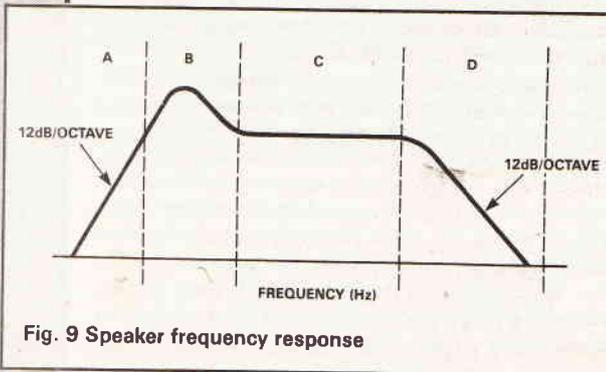


Fig. 9 Speaker frequency response

The 'a' designation of the ka parameter, is the speakers radius in metres. The 'k' in this sequence is a wave number. Its value is equal to $(6.28 \times \text{frequency})/343$. In all speakers, these two factors interact to control the radiation pattern.

If ka is equal to or less than one, the acoustic pattern is hemispherical. As the frequency is increased, and ka becomes greater than one, the cone no longer acts as a piston. When ka equals two, the radiated pattern has decreased in width. Because of this, the acoustic output (60° off the speakers axis) will have a 3dB loss in amplitude. A further increase in the frequency will cause the width of the curves to get even smaller, and the 3dB points will move closer to the speakers main axis. The sound will now be concentrated along this line, and the effect is known as beaming. Table 1 indicates the frequency as a function of the speakers size. (ka = 1). This point could be called the speakers critical frequency.

Environment

To determine how this information is related to stereo imaging, consider the diagram shown in Figure 11. As indicated, the two speakers have been placed against a wall, 8 feet or 2.4m apart. The listeners are seated in the middle of the room, six feet or 1.8m from

a line that is parallel to the front surface of the speakers. Position 'B' is centered between the two speakers, and it is located 34° off of each speakers axis.

This off axis location is approximately the same as the 60° line in Figure 10, and it will have similar characteristics. If the speaker system contained a single eight inch radiator, there would be a 3 dB loss in amplitude at 1000Hz. (ka = 2). When ka equals five, (2690 Hz) the loss will increase to 17 dB. With the width of the radiation pattern decreasing (ka > 3) the off axis listener may not hear the speakers direct sound. Instead, the source may be produced by a reflection from a nearby object or an adjacent wall. This will alter the overall imaging effect.

While some speaker manufacturers have used the reflection principle to increase the width of the sound stage, both speakers must be placed in specific location. The main requirement is to have equal reflection paths.

If the reflection paths are not equal, the sound from one speaker will arrive at the listening position before the other. The brain, must then decide how the two sounds are related. It is unlikely, in the average listening environment, that the delay will be long enough for the brain to conclude there is no relationship. Any delay, will produce a change in the acoustic image.

In Figure 11, listening positions 'A' and 'C' have a different problem. The listener at each of these

TABLE 1
Critical Frequency vs Speaker Size

Speaker Diameter (inches)	Radius (meters)	Critical Frequency (Hz)
15	0.1905	287
12	0.1524	358
10	0.1270	430
8	0.1016	538
6	0.0762	717
4	0.0508	1075
2	0.0254	2150
1	0.0127	4300

locations is approximately 0.6m or 2 feet closer to the axis of the nearest speaker. Not only is the sound from the farthest speaker delayed, but the increased distance will also reduce its amplitude. These two factors, decreased sound pressure and increased time delay will combine, so positions 'A' and 'C' will have

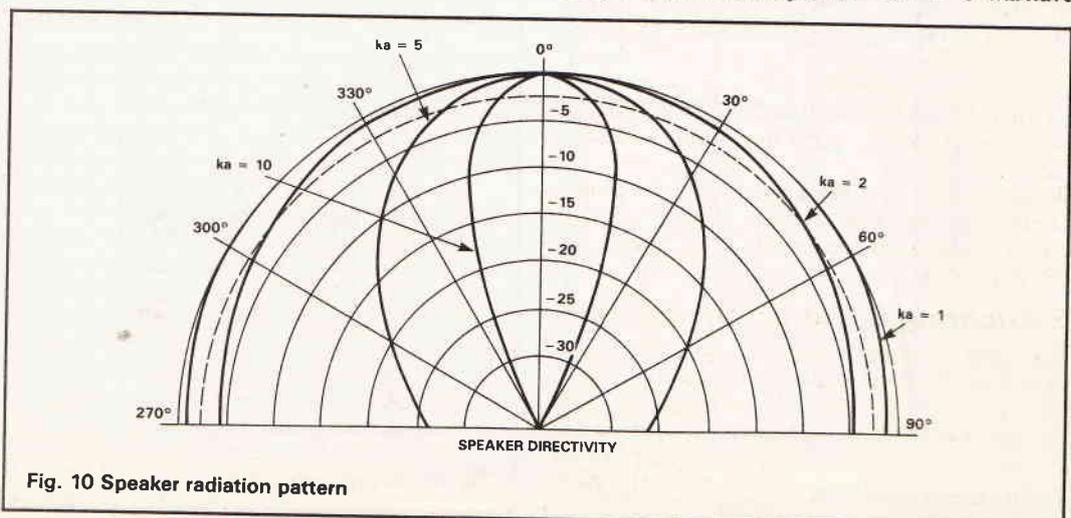


Fig. 10 Speaker radiation pattern

very poor imaging. In fact, for most of the time a listener at either of these two locations will only be aware of the closest speaker.

To overcome some of these problems, the listening position could be moved forward, so position 'B' is at a 45° angle. Another alternative is to move the speakers farther apart. In either case, each speaker should be rotated so that position 'B' is on each of their axis (See Figure 12). In this way the acoustic images are shifted toward each other, and the sound at position 'B' will arrive at an angle of 45°. This ensures that this listener will obtain maximum auditory sensitivity, and will hear the direct sound before any reflections.

Positions 'A' and 'C' will also benefit from the new speaker placement. Each position will now be two feet

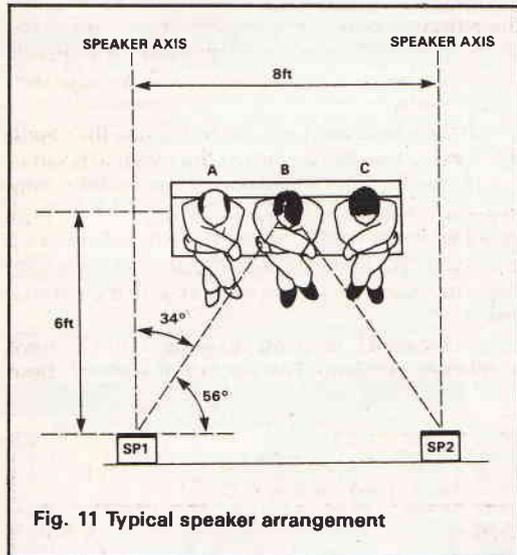


Fig. 11 Typical speaker arrangement

off the speakers central axis. This provides a listening angle of approximately 19°. Both positions are within the sphere of maximum ear sensitivity.

Although 'A' and 'C' will still have a -3dB point, they do not occur until $ka = 5$. Since this is not the top of the audible range, the frequency response is usually extended by using a crossover network and a smaller speaker. If a one inch speaker is used as a tweeter, the -3db point for positions 'A' and 'C' will not occur until the radiated frequency is almost 20kHz.

References

- Gardner, M.B., Gardner, R.S., Problem of localization in the median plane: Effect of Pinna cavity occlusion., *Journal of the ASA*, Vol. 53, No. 2, 1973.
- Batteau, D.W. The Role of the Pinna in Human Localization. *Proceedings of the Royal Society*, B168(1011) pp 158 – 180.
- Haas, H., The influence of a single Echo on the Audibility of Speech, *Acoustica*, Vol1, No.2, 1951 (in German). An English translation appears in the *Journal of the AES* Vol.20, No. 2, March 1972.
- Moir, James, *Stereophonic Reproduction*, Audio, Oct. 1952
- Wallach, Hans, The Precedence Effect in Sound Localization. *American Journal of Psychology*. A reprint appears in the *Journal of the AES*, Vol. 21, No. 10, Dec. 1973

Estimating Speaker Directivity

The most accurate method for determining the directivity of a speaker is by measuring its acoustic output on each side of its central axis. Not only does this take time, but it also requires some equipment that is usually not available to the audiophile or serious listener. It is, possible to estimate the radiation pattern by doing some simple calculations.

Although the result of these calculations can produce a graph like the one shown in Figure 10, this amount of detail is not necessary. If the 3dB points are known, the speakers can be placed for the best stereo imaging and the widest sound stage.

The Ka Factor

The principle factors that determine the directivity of a speaker are its size and the wavelength of the radiated sound. The following example will show how to calculate the 3dB points for an eight inch speaker in an infinite baffle. Because speakers are mounted in a cabinet, this latter parameter is not usually a limitation. Above the point where ka is equal to one, the wavelength of the sound is usually smaller than the baffles dimensions. Therefore, the speaker will appear to be in an infinite baffle.

A speakers off-axis acoustic output will be 3dB down when the value of the following equation is approximately equal to 1.6125.

$$X = ka \times \sin(S)$$

Where $X = 1.6125$ by definition

k = a wave number

a = the speakers radius in metres

S = the off axis angle

Suppose, the off axis location is 45° and the speaker has an eight inch diameter. The radius in metres is 0.1016, and 'S' is 45°. Inserting these numbers into the previous equation and solving for k gives:

$$\begin{aligned} k &= 1.6125 / [(0.1016) \times \sin(45)] \\ &= 1.6125 / [(0.1016) \times (0.707)] \\ &= 22.45 \end{aligned}$$

The associated frequency can be obtained from another equation for k . That is:

$$k = (6.28 \times f) / 343$$

re-arranging and solving for f provides:

$$\begin{aligned} f &= (22.45) \times 343 / 6.28 \\ &= 1.23\text{kHz} \end{aligned}$$

The physical position, on either side of the speakers axis that corresponds to the 3dB points can be determined from the listening position. If, as part of this example, this distance was six feet (1.8m), then:

$$\begin{aligned} \tan(S) &= y/d \\ \text{Where } S &= \text{the off axis angle} \\ d &= \text{the listening distance} \\ y &= \text{the off axis position} \end{aligned}$$

Based on the previous assumption, the 3dB points should be located at:

$$\begin{aligned} y &= 6 \times \tan(45) \\ &= 6 \text{ feet} \end{aligned}$$

Therefore, for an eight inch speaker and a listening distance of six feet, the acoustic output will be 3dB down at 1.23 kHz. The two locations will be six feet on either side of the speakers axis.

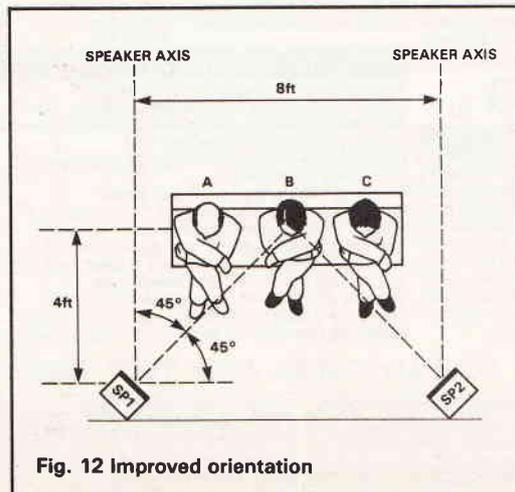


Fig. 12 Improved orientation




THE ORIGINAL SURPLUS WONDERLAND!

MONITORS

MONOCHROME MONITORS

THIS MONTH'S SPECIAL!

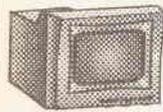

There has never been a deal like this one! Brand spanking new & boxed monitors from NEC, normally selling at about £140! These are over-engineered for ultra reliability, 9" green screen composite input with etched non-glare screen plus switchable high/low impedance input and output for daisy-chaining, 3 front controls and 6 at rear. Standard BNC sockets. Beautiful high contrast screen and attractive case with carrying ledge. Perfect as a main or backup monitor and for quantity users! **£39.95 each (D) or 5 for £185 (G)**

CALL FOR DISCOUNTS ON HIGHER QUANTITIES!

Zenith ZVM-1240-EA brand new & boxed 12" amber flat screen with optional swivel and tilt base. Sunflex filter with dark tint. Standard TTL PC compatible. 18 mhz bandwidth. Very attractive "state of the art" tapered grey case. Standard 9 pin D plug (supplied) on 1 metre cord and mains cord terminated with IEC connector. 240 volts complete with operations manual. Free swivel/tilt base. An absolute gift at: **£59 (D) 10/£500 (G)**

COLOUR MONITORS

Decca 16" 80 budget range colour monitor. Features a PIL tube, beautiful teak style case and guaranteed 80 column resolution, features usually seen only on colour monitors costing 3 times over price! Ready to connect to most computers or video outputs. 75Ω composite input with integral audio amp & speaker. Fully tested surplus, sold in little or hardly used condition with 90 day full RTB guarantee. Ideal for use with video recorder or our Telex ST, and other audio visual uses. **£99 (E) 3/£275 (G)**

20", 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs. In EXCELLENT little used condition with full 90 day guarantee. **20".....£135 22".....£155 26".....£185 (F)**

HI-DEFINITION COLOUR MONITORS

Brand new 12" multiinput high definition colour monitors by Microvitek. Nice tight 0.31" dot pitch for superb clarity and modern metal black box styling. Operates from any 15.625 khz sync RGB video source, with either individual H & V syncs such as CGA IBM PC's or RGB analog with composite sync such as Atari, Commodore Amiga, Acom Archimedes & BBC. Measures only 14" x 12" square. Free data sheet including connection information.



Only **£145 (E)**

Brand new Centronic 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 Mhz bandwidth. A super monitor in attractive style moulded case. Full 90 day guarantee. Only **£129 (E)**

NEC CGA IBM-PC compatible. High quality ex-equipment fully tested with a 90 day guarantee. In an attractive two tone ribbed grey plastic case measuring 15" L x 13" W x 12" H. A terrific purchase enables us to pass these on at only.... **£79 (E)**

SCOOP! 14" Colour Multisync/Multifunction

Never before has such a deal been struck to bring you this quality Japanese manufactured multisync, multifunction professional grade monitor at an unheard of low price! The Electrohome ECM1311 with its host of inputs will connect to most computer systems including: IBM PC/XT/AT/PS2 (CGA, EGA, VGA modes) Atari, Archimedes (up to SVGA), Commodore, BBC and many more. Many other features include: RGB analog & TTL inputs, separate horizontal, vertical, composite and sync on green inputs; auto 15 to 36khz operation; 0.31mm tube dot pitch; tinted non glare etched screen & 30 mhz bandwidth makes this item an absolute snip! Current makers list price over £900! Each supplied with connection data, fully tested in used good condition, some may have screen blemishes. Complete with full 90 day RTB guarantee. Quantity discounts available. Will also function as quality TV with our RGB Telexbox. Full Technical Manual £15.

Only **£149 (E)**

V22 1200 BAUD MODEMS

Master Systems 2/12 microprocessor controlled V22 full duplex 1200 baud modem. Fully BT approved unit, provides standard V22 high speed data comm, which at 120 cps, can save your phone bill and connect time by a staggering 75%! Ultra slim 45 mm high. Full featured with LED status indicators and remote error diagnostics. Sync or Async use; speech or data switching; built in 240v mains supply and 2 wire connection to BT. Units are in used but good condition. Fully tested prior despatch, with data and a full 90 day guarantee. What more can you ask for - and at this price!

ONLY **£69 (D)**

IBM KEYBOARD DEALS

A replacement or backup keyboard, switchable for IBM PC, PC-XT or PC-AT. LED's for Caps, Scroll & Num Locks. Standard 84 keyboard layout. Made by NCR for the English & US markets. Absolutely standard. Brand new & boxed with manual and key template for user slogans on the function keys. Attractive beige, grey and cream finish, with the usual retractable legs underneath. A generous length of curly cord, terminating in the standard 5 pin DIN plug. A beautiful clean piece of manufacturer surplus. What a deal! **£39 (B) 5/£175 (D)**

Brand new and boxed 84 key PC/XT type keyboards in standard IBM grey with very attractive mottled finish and "clicky" solid feel keys. 10 function keys on side. English layout and E sign. Green LEDs for Caps, Scroll & Num locks. **£29.95 (B) 5/£135 (D)**

CALL FOR DISCOUNTS ON HIGHER QUANTITIES!

FLOPPY DISK DRIVES BARGAINS GALORE!

NEW 5 1/4 inch from £29.95!

Massive purchases of standard 5 1/4" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from +5 & +12vdc, are of standard size and accept the standard 34 way connector.

TANDON TM100-2A IBM compatible DS **£39.95 (C)**
CANON, TEC etc. DS half height. State 40 or 80T **£79.00 (C)**
TEAC FD-55-F. 40-80 DS half height. BRAND NEW **£79.00 (C)**

Specials!

TEAC FD-55 half height series in your choice of 40 track double sided 360k or 80 track double sided 720k. Ex-equipment fully tested in excellent condition with 90 day warranty. Order TE-36 for 360k **£29.95 (C)** or TE-72 for 720k **£39.95 (C)**

CHOOSE YOUR 8 INCH!

Shugart 800/801 SS refurbished & tested **£150.00 (E)**
Shugart 851 double sided refurbished & tested **£225.00 (E)**
Mitsubishi M2994-63 double sided switchable hard or soft sectors - BRAND NEW **£250.00 (E)**

SPECIAL OFFERS!!

Dual 8" drives with 2 megabyte capacity housed in a smart case with built in power supply! **Only £499.00 (F)**
Ideal as exterior drives!

End of line purchase scoop! Brand new NEC D2246 8" 85 megabyte of hard disk storage! Full CPU control and industry standard SMD interface. Ultra hi speed transfer and access time leaves the good old ST506 interface standing. In mint condition and comes complete with manual. **Only £399 (E)**

MAINS SUPPRESSORS & FILTERS

Roxburgh SDC 021 2 amp mains RFI filter. Has an extra wide frequency range of 150 khz to 30 mhz. Can type, solder lug connection. Quality manufactured to BS 613 standards. Dims 1-1/2"D x 1-3/4"H..... **£3.95 or 3 for £10 (A) 10 for £28 (B)**

Roxburgh SDA 013/25. Similar to above rated at 1-1/2 amps. Dims 1-1/2"D x 1-3/4"H..... **£3.25 or 3 for £8.50 (A) 10 for £25 (B)**

Suppression Devices SD5 A10. Extra compact general purpose suppressor. Plastic moulded case with single bolt fixing and snap connectors. Rated at 230 vac 5 amps. Dims 1-3/4" L x 1-1/8" W x 5/8" H..... **£3.95 or 3 for £10 (A) 10 for £28 (B)**

Belling-Lee type L2127 3 amp mains RFI filters. Has a built in mains cable (English coding), and a three pin miniature non-reversible socket and a mating plug, to go to the equipment. Ideal for those who are bugged by RF interference. Very compact. Dims 3-1/8" x 2.5" x 1.5"..... **£3.95 each or 3 for £10 (A)**

RECHARGEABLE BATTERIES

LEAD ACID


Maintenance free sealed long life. Type A300.
12 volts 12 volts 3 amp/hours **£13.95 (A)**
6 volts 6 volts 3 amp/hours **£ 9.95 (A)**
12 volts Centre tapped 1.8 amp hours. RFE. **£ 5.95 (A)**
12 volts 12 volts 38 amp hours 7-1/2" L x 6" S. RFE **£35.00 (B)**

NICKEL CADMIUM

Quality 12v 4ah cell pack. Originally made for the Technicolor video company. Contains 10 GE top quality D nicad cells in a smart robust case with a DC output connector. Ideal for portable equipment. Brand new. **£19.95 (B)**
Ex-equipment NICAD cells by GE. Removed from equipment and in good, used condition: D size 4ah **4 for £5 (B)**
F size 7ah **6 for £8 (B)**

SPECIAL INTEREST

Tektronix 1751 Waveform/Vector monitor **£2750**
Trio 0-18 vdc bench PSU. 30 amps. New **£ 470**
DEC VAX11/750 Inc. 2 Meg Ram DZ and full documentation, in brand new condition
Fujitsu M3041 600 LPM band printer **£3900**
DEC LS/02 CPU board **£2950**
Calcomp 1036 large drum 3 pen plotter **£ 150**
Thurby LA 160B logic analyser **£ 650**
1.5kw 115v 60hz power source **£ 375**
Tektronix R140 NTSC TV test signal standard. **£ 950**
Sony KTX 1000 Videotex system - brand new **£ 875**
ADDS 2020 VDU terminals - brand new **£ 790**
Sekonic SD 150H 18 channel Hybrid recorder **£ 225**
Trend 1-9-1 Data transmission test set **£2000**
Kenwood DA-3501 CD tester, laser pickup simulator **£ 525**
£ 350

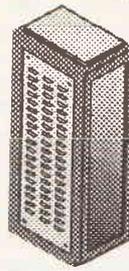

Superb Quality 6 foot 40u

19" Rack Cabinets

Massive Reductions Virtually New, Ultra Smart! Less Than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and removable side panels. Fully adjustable internal fixing struts, ready

punched for any configuration of equipment mounting plus ready mounted Integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels or stand singly. Overall dimensions are 77-1/2"H x 32-1/2"D x 22"W. Order as:

Rack 1 Complete with removable side panels..... **£375.00 (G)**
Rack 2 Less side panels..... **£225.00 (G)**

POWER SUPPLIES

Power One SPL200-5200P 200 watt (250 w peak). Semi open frame giving +5v 35a, -5v 1.5a, +12v 4a (8a peak), -12v 1.5a, +24v 4a (6a peak). All outputs fully regulated with over voltage protection on the +5v output. AC Input selectable for 110/240 vac. Dims 13" x 5" x 2.5". Fully guaranteed RFE. **£85.00 (B)**

Power One SPL130. 130 watts. Selectable for 12v (4A) or 24 v (2A). 5v @ 20A. ±12v @ 1.5A. Switch mode. New. **£59.95 (B)**
Astec AC-8151 40 watts. Switch mode. +5v @ 2.5a. +12v @ 2a. -12v @ 0.1a. 6-1/4" x 4" x 1-3/4". New **£19.95 (B)**
Greendale 19A08E 60 watts switch mode. +5v @ 6a. ±12v @ 1a. RFE and fully tested. 11 x 20 x 5.5cms. **£24.95 (C)**
Conver AC130. 130 watt hi-grade VDE spec. Switch mode. +5v @ 15a. -5v @ 1a. ±12v @ 6a. 27 x 12.5 x 6.5cms. New. **£49.95 (C)**

Bosher 13090. Switch mode. Ideal for drives & system. +5v @ 6a, +12v @ 2.5a, -12v @ 0.5a, -5v @ 0.5a. **£29.95 (B)**
Farnell 66/40A. Switch mode. 5v @ 40a. Encased **£95.00 (C)**

COOLING FANS

Please specify 110 or 240 volts for AC fans.

3 inch AC 112" thick **£ 8.50 (B)**
3 1/2 inch AC ETRI slimline. Only 1" thick. **£ 9.95 (B)**
4 inch AC 110/240v 1 1/2" thick. **£10.95 (B)**
4 inch AC 1 1/2" thick **£ 9.95 (B)**
10 inch AC round. 3 1/2" thick. Rotron 110v **£10.95 (B)**
10 inch As above but 230 volts **£24.95 (B)**
62 mm DC 1" thick. No. 812 for 6/12v. 814 24v. **£15.95 (A)**
80 mm DC 5 v. Papst 8105G 4w. 38mm. RFE. **£19.95 (A)**
92 mm DC 12v. 18mm thick **£14.95 (A)**
4 inch DC 12v. 12w 1 1/2" thick **£12.50 (B)**
4 inch DC 24v 8w. 1" thick. **£14.50 (B)**

THE AMAZING TELEBOX!

Converts your colour monitor into a

QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER!

Brand new high quality, fully cased, 7 channel UHF PAL TV tuner system. Unit simply connects to your TV aerial socket and colour video monitor turning same into a fabulous colour TV. Don't worry if your monitor doesn't have sound, the TELEBOX even has an integral audio amp for driving a speaker plus an auxiliary output for Headphones or Hi Fi system etc. Many other features: LED Status Indicator, Smart moulded case, Mains powered, Built to BS safety specs. Many other uses for TV sound or video etc. Supplied BRAND NEW with full 1 year guarantee. **£29.95 (B)**
Telexbox ST for composite video input monitors..... **£29.95 (B)**
Telexbox STL as ST but with integral speaker..... **£34.95 (B)**
Telexbox RGB for analogue RGB monitors..... **£65.95 (B)**
RGB Telexbox also suitable for IBM multisync monitors with RGB analog and composite sync. Overseas versions VHF & UHF call. SECAM / NTSC not available.

BRAND NEW PRINTERS

TEC Starwriter Model FP1500-25 daisywheel printer renowned for its reliability. Diablo type print mechanism gives superb registration and quality. On board microprocessor gives full Diablo/Qume command capability. Serial RS-232C with full handshake. Bidirectional 25 cps, switchable 10 or 12 pitch, 136 cpl in Pica, 163 in Elite. Friction or tractor feed. Full ASCII including E sign. Font and ribbon Diablo compatible..... **£199 (E)**
DED DPG21 miniature ball point pen printer/plotter mechanism with full 40 characters per line. Complete with data sheet which includes circuit diagrams for simple driver electronics..... **£49 (B)**
Centronics 150 series. Always known for their reliability in continuous use - real workhorses in any environment. Fast 150 cps with 4 fonts and choice of interfaces at a fantastic price! **£159-4** Serial up to 9.5" paper, fan fold tractor..... **£ 99.00 (E)**
£150-4 Serial up to 9.5" paper, tractor, roll or s/sheet..... **£129.00 (E)**
£225 152-2 parallel up to 14.5" paper, tractor or s/sheet..... **£149.00 (E)**

CALL FOR THE MANY OTHERS IN STOCK.

VISIT OUR SHOP FOR BARGAINS

LARGE QUANTITIES OF OSCILLOSCOPES AND TEST GEAR ALWAYS AVAILABLE - CALL NOW!

DISPLAY

MAIL ORDER & OFFICES
Open Mon-Fri 9.00-5.30
Dept ET, 32 Biggin Way,
Upper Norwood,
London SE19 3XF.

LONDON SHOP
100's of bargains!
Open Mon-Sat 9.5-5.30
215 Whitehorse Lane,
South Norwood,
London, SE25.

DISTEL © The Original
Free dial-up database!
1000's of Items-Info On Line
300 bd 081-679-1888,
1200/75 bd 081-679-6183,
1200/1200 bd 081-679-8769

ALL ENQUIRIES
081-679-4414
Fax: 081-679-1927
Telex: 894502



All prices for UK Mainland. UK customers add 15% VAT to TOTAL order amount. Minimum order £10. PO orders from Government, Universities, Schools & Local Authorities welcome-minimum account order £25. Carriage charges (A)=£2.00, (B)=£4.90, (C)=£8.50, (D)=£11.50, (E)=£14.00 (F)=£18.00 (G)=Call. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guaranteed for 90 days. All guarantees on a return to base basis. We reserve the right to change prices & specifications without prior notice. Orders accepted subject to stock. Quotations willingly given for higher quantities than those stated. Bulk surplus always required for cash.



PCB SERVICE

May

**TELEPHONE
ORDERS
may be made on
(0442)
66551
ACCESS or VISA**

E9105-1 Modulated Laser (2 boards)	H
E9105-2 Thyristor Tester	F
E9105-3 Frequency Plotter	K

PCBs for the remaining projects are available from the companies listed in Buylines.

Use the form or a photocopy for your order. Please fill out all parts of the form. Make sure you use the board reference numbers. This not only identifies the board but also tells you when the project was published. The first two numbers are the year, the next two are the month.

Terms are strictly payment with order. We cannot accept official orders but we can supply a proforma invoice if required. Such orders will not be processed until payment is received.

Price code	Price (inc. VAT)
C	£1.80
D	£2.50
E	£3.25
F	£4.00
G	£4.75
H	£5.50
J	£6.62
K	£7.20
L	£8.80
M	£10.60
N	£13.10
O	£15.80
P	£17.90
Q	£21.80
R	£23.90
S	£25.90
T	£29.00
U	£32.20
V	£35.80
W	£37.90
X	£40.70

E9004-3 Bass Amplifier Micro	N	E9103-2 64K EPROM Emulator	N
E9004-4 Quad Power Supply	O	E9103-3 SSB Radio Receiver	G
E9005-1 Business Display	O	E9103-4 Active Loudspeaker board	H
E9005-2 Phone Lock and Logger	F	E9104-1 Testmeter Volts	E
E9006-1 Dark Room Timer	G	E9104-2 Active Direct Injection Box	F
E9006-2 Telephone Extension Bell	C	E9104-3 EPROM Eraser	F
E9006-3 Telephone External Bell	D	E9104-4 Digital Tachometer	F
E9006-4 Fecko Box	G	E9104-5 Radio Calibrator	F
E9006-5 Bug Spotter	E		
E9007-1 Guitar Practice Amp	G		
E9007-2 Digital Frequency Meter	M		
E9007-3 Footstep Alarm	E		
E9007-4 Transistor Tester	C		
E9007-5 Decision Maker	J		
E9008-1 AC Millivoltmeter	K		
E9008-2 Temperature Controller	N		
E9008-3 FM Generator	L		
E9009-2 Slide Projector Controller	E		
E9009-2 Ultimate Diode Tester	D		
E9009-3 The Entertainer	G		
E9010-1 Component Tester	F		
E9010-2 Active Contact Pickup	E		
E9010-3 R4X Longwave Receiver	C		
E9011-1 The Autocue (2 boards, 1 double sided) ...	N		
E9011-2 Infra-lock transmitter (2 boards)	K		
E9011-3 Infra-lock receiver	H		
E9011-4 Four-track cassette recorder (record/playback one channel)	F		
E9011-5 Four-track cassette recorder (Bias/erase oscillator board)	K		
E9012-1 Infra Switch	F		
E9101-1 Remote Control — Main Board	J		
E9101-2 Remote Control — Display Board	H		
E9101-3 Remote Control Timeswitch — Transmit board	E		
E9101-4 SBC Micro-Controller Board	F		
E9101-5 SBC Practice Interface Board	F		
E9101-6 5 in 1 Remote Sensing Switch	E		
E9102-1 Remote Control Timeswitch — receiver board	F		
E9102-2 Anti Theft Alarm (2 bds)	H		
E9103-1 Ariennes Lights	L		

**TO: ETI PCB SERVICE, READERS' SERVICES,
ARGUS HOUSE, BOUNDARY WAY,
HEMEL HEMPSTEAD HP2 7ST**

Please supply:

Quantity	Ref. no.	Price Code	Price	Total Price
----------	----------	------------	-------	-------------

Post and packing £0.75

Total enclosed £


Please send my PCBs to: (BLOCK CAPITALS PLEASE)

Name

Address

..... **Postcode**

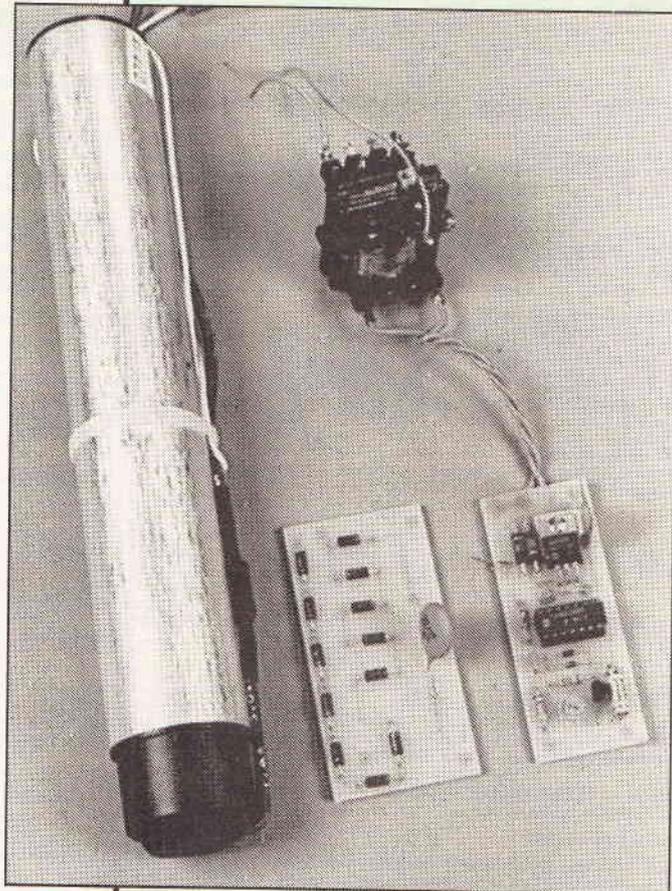CHEQUES SHOULD BE MADE PAYABLE TO ASP Ltd.



This project follows on from last month's article which described how a laser works. Sadly for those of you who want to incinerate the neighbours' cat we will not be describing how to build a 2 kW CO₂ laser but something a little less awesome and with a lot more practical applications.

This laser is a Helium Neon Laser (HeNe for short), it has a power output of about 2mW, which as it requires about 1.500 volts at 5mA to operate gives an overall efficiency of about the same as a pork pie salesman in a kibbutz.

Table 1 gives the details of the laser tube we are using for this project.

Table 1

Number	Phillips LHN-VLP/04
Striking Volts	between 6 and 8 KV
Running Volts	1.2 to 1.5 KV
Running Current	5mA
Output Power	2mW
Wave Length	630nm (strongest) plus others
Beam Diameter	750um
Divergence	1.43 RAD (note 1)
Visible Distance	2 Miles (suppliers data)

Note 1: I am a little sceptical about this figure which came from the suppliers data as this works out at nearly 82 degrees! Supplier J&N Bull Electrical, 250 Portland Road, Hove, Brighton, BN3 5QT Telephone 0273 203500/734648.

The Price is £40.00 plus £3.00 for insured delivery.

Kevin Kirk now turns to the practical aspect of modulating a Laser.

2

Lasers

LASER

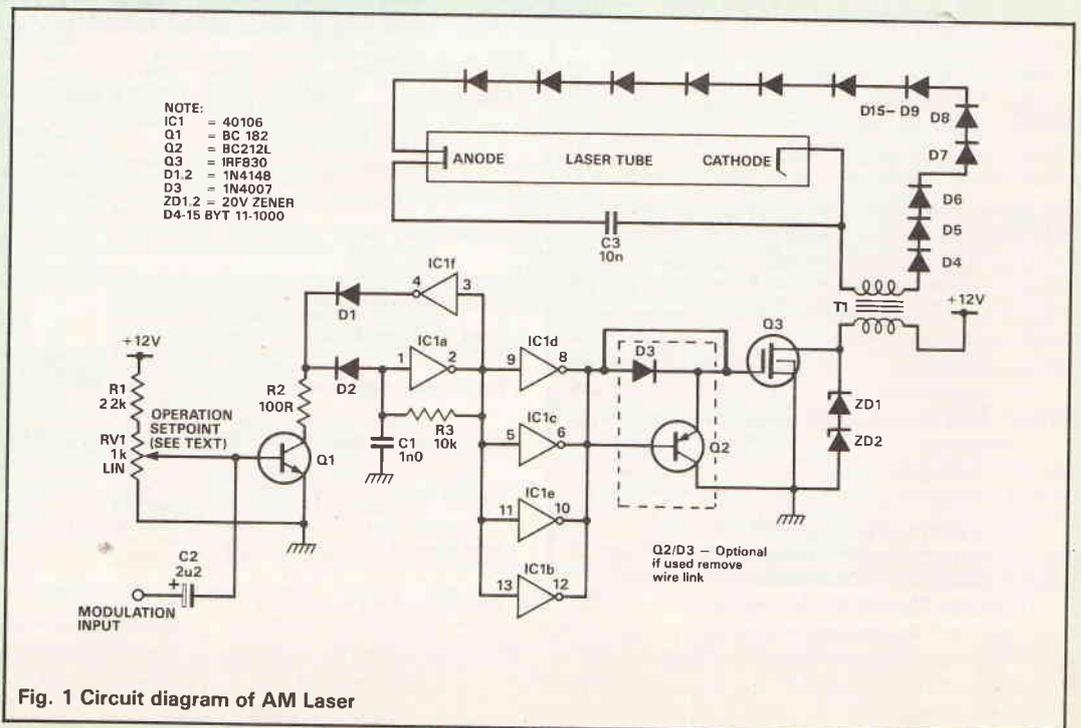


Fig. 1 Circuit diagram of AM Laser

is nasty.

The transformer is wound on a DT2723 bobbin which fits a FX3720 Ferroxcube 'E' core, this set is designed specifically for this job.

The secondary is wound first, 320 turns in 8 layers of 40 turns of 0.2mm diameter wire. Each layer should be separated by paper (not sellotape), the prototype used computer paper. On the prototype a further 2 layers of 30 turns were wound on to provide increased output voltage for different laser tubes.

The primary consists of 4 pieces of 0.4mm wire twisted together and wound 10 turns followed by a further 2 turns to provide a tapping for lower output voltage if required.

The transformer should then be soaked in a good insulating varnish, failing that a polyurethane varnish (with no additives). This should be allowed to dry for 24 hours prior to use. The PCB should also be varnished to prevent arcing.

The rest of the circuit presents no problems as long as the PCB is used, note the leads on the laser are connected to the right positions on the board the white lead goes to the negative (-ve) and the black to the positive (+ve).

Prior to starting, check and recheck and preferably get someone else to check all of the connections. Switch mode supplies, even fairly tame ones like this, tend to be a bit unforgiving especially if the oscillator is not running. If you have access to a 'scope then don't connect the transformer and check that Q3 is getting pulses of around 50% mark/space ratio, if not adjust RV1.

If this is OK, then try turning RV1 up this should alter the mark space ratio. The final setting of RV1 will be determined by the use the laser is put to so an initial setting of 50% mark/space is a good start.

Now connect the transformer and laser tube, the laser should give a red beam shortly after switch on. If not switch off and check all connections.

If it works then directing the beam onto a sheet of paper you should see a red dot. Alternatively blowing smoke across the beam will show it up.

When running the supply don't use it without either the laser tube or some other load connected. If not, the power will be either dissipated in the zeners or the secondaries inside the transformer may arc over.

If the laser is to be run from a power supply which may run other devices then it is recommended that a 100 μ Electrolytic (at >12VDC) and a 100n disc ceramic are put in parallel on the power supply, a

HOW IT WORKS

IC1a is configured as a standard oscillator together with R4/C1. This output at about 70kHz is fed through IC1b-e which act as inverter/drivers for the MOS switching transistor Q3. They will not be able to turn off this transistor quickly enough to give a sharp edge so Q2 is used to achieve this. However, the gates used in the prototype could fire Q3 directly and so Q2/D3 were omitted. The voltage on the primary of T1 will rise rapidly when Q3 switches off and to avoid exceeding the Vds of the transistor Z1 and Z2 (1N5388) will clamp this voltage to 400 Volts. The transformer has a ratio of 32:1 so the output voltage is about 6.4kV which peaks around 9kV so the tube will quickly strike. This supply is designed for use with other laser tubes other than the one specified so they may need up to 9kV to strike. Our tube should be limited to 8kV so there are various tappings to achieve this.

When the tube strikes it will start to draw current which will reduce the voltage on the output of the supply, but to ensure that no diode in the chain (D4-15) hogs more than its fair share, the resistor chain, R4-15 may be inserted.

The modulation is carried out by Q1 which will, when turned on, draw current from C1 which will tend to discharge it faster which will

PARTS LIST

RESISTORS

R1	22k
R2	100R
R3	10k
R4-15	1M (optional - see text)
RV1	1k lin preset

CAPACITORS

C1	1n
C2	2 μ 2
C3	10n/10kV (May have to be made in a series/parallel combination)

SEMICONDUCTORS

IC1	40106
Q1	BC182L
Q2	BC212L (optional)
Q3	IRF830
ZD1,2	1N5388
D1,2	1N4148
D4-15	BYT 11-1000
D3	1N4148 (optional)

MISCELLANEOUS

T1	Ferroxcube 'E' core FX 3720 on DT2723 bobbin
Laser Tube	- HeNe 2mW
Copper Wire	- 0.2mm and 0.4mm dia
PCB	- ETI PCB Service.

BUYLINES

The Laser tube comes from J&N Bull (see text) and ZD1,2 and D4-15 from Farnell Electronic Components. You'll need to shop around for C3 the high voltage capacitor.

couple of ferrite beads on the power leads will reduce any RFI.

It is strongly recommended the supply and laser be built into some form of plastic case before use, but the exact type is left to the constructor but note the laser is longer than 10 inches.

Finally take care with the laser tube, it is packaged inside an aluminium tube, but remember it is glass inside and is fragile.

Try not to drop the tube, because even if the glass envelope survives you may knock the mirrors out of true, which will ruin the final output mode.

reduce the time that Q3 is turned on for thus reducing the energy transferred to the transformer T1. To ensure that this discharge current is only drawn during the Q3 on time, IC1f/D1 will reverse bias D1 ensuring that C1 charge time is not affected by the modulation on Q1.

The actual operating point of the laser may be set with RV1, it may be changed if the laser is drawing too much current, or too little. It also provides a control so that Q1 can be biased into its linear region for analogue/audio modulation and biased non-linearly for digital on/off modulation.

Note that at no point should the laser be turned completely off, it does take a little time to stabilise so turning it on and off quickly is not advisable. So the type of modulation recommended is between two laser brightness levels. This may be readily detected using a straight-forward opto amplifier and the beam being on all the time gives scope for a carrier present signal generation (for communications systems) and laser sighting.

There is one further point to note. The modulation should be limited to less than 20kHz, preferably a lot lower as the oscillator frequency is only 70kHz and the modulation may not be as effective at higher frequencies.



PSST...

Powerful Software Saves Time!

LABCENTER PUTS YOUR PC TO WORK

Why spend hours of your valuable time designing PCBs by hand or with a non-integrated CAD package when your PC can do it for you?

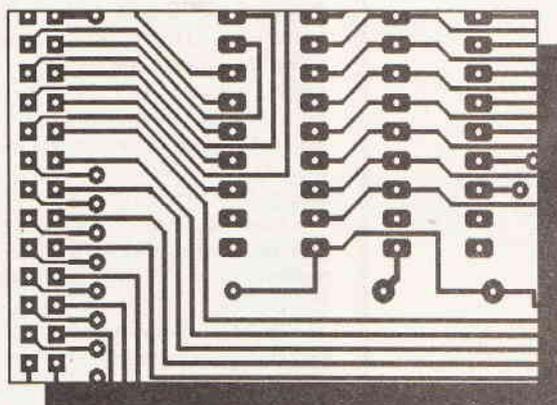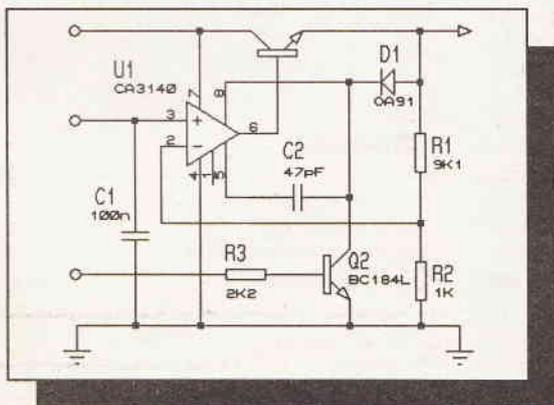ISIS provides the easiest of ways to enter a circuit diagram into your computer and ARES has all the features needed to convert it into an elegant PCB layout. Both packages share the same Graphical User Interface, and the way that they integrate guarantees that your PCB will always match the original circuit.



ISIS - Intelligent Schematics

ISIS DESIGNER.....£275

An easy to use schematic capture package for anyone needing to enter designs prior to further processing with ARES or other EDA software. It features our modern Graphical User Interface and an Intelligent Diagram Editor.

ISIS DESIGNER+£475

A sophisticated design management tool - features such as an automatic annotator/packager, two systems for hierarchical design and ASCII Data Import make DESIGNER+ one of the most powerful schematics packages currently available for the PC.

- Auto wire routing.
- Auto dot placement.
- Auto name generator.
- Powerful editing facilities.
- Object oriented 2D drawing with symbol library.
- Comprehensive device libraries available.
- Output to dot matrix, pen plotters, lasers, POSTSCRIPT.
- Export to DTP packages in IMG or DXF formats.
- Multi-sheet and hierarchical designs handles in single file.
- Netlist output to most popular EDA software.
- Bill of Materials and Electrical Rules Check reports.

ARES - Advanced Routing

ARES.....£275

A netlist based, multi-layer PCB design package that can integrate with ISIS or other schematics software. Includes connectivity checker, design rule checker, power plane generator and auto annotator.

ARES AUTOROUTE£475

Our new autorouter uses an advanced, multi-strategy algorithm to achieve very high completion rates, yet when driven from ISIS, there is remarkably little setting up to do - Package, Router-Strategy and DRC data can all be read from the netlist. As we said at the beginning, Powerful Software Saves Time.

- Topological Route Editor (another Labcenter innovation)
- Unlimited user configurable pad, track and via styles.
- Full surface mount and metric support.
- 10 copper + 2 silk layers.
- 1 thou resolution.
- 30x30 inch max board size.
- Up to 5000 pins, 50000 trace segments using EMS RAM.
- Object oriented 2D drawing for silk screen graphics.
- Drivers for dot matrix, pen plotters, lasers, POSTSCRIPT, Photoplot (Gerber), NC drill (Excellon).
- Graphics export in IMG format.

labcenter
Electronics

COMBINATION PRICES

ISIS DESIGNER & ARES£495
ISIS DESIGNER & ARES AR£675
ISIS DESIGNER+ & ARES£675
ISIS DESIGNER+ & ARES AR£850
Prices inc UK delivery, exc VAT.




Call for a demo pack today - 0274 542868.



14 Murriner's Drive, Bradford. BD9 4JT

Electronics At The Leading Edge

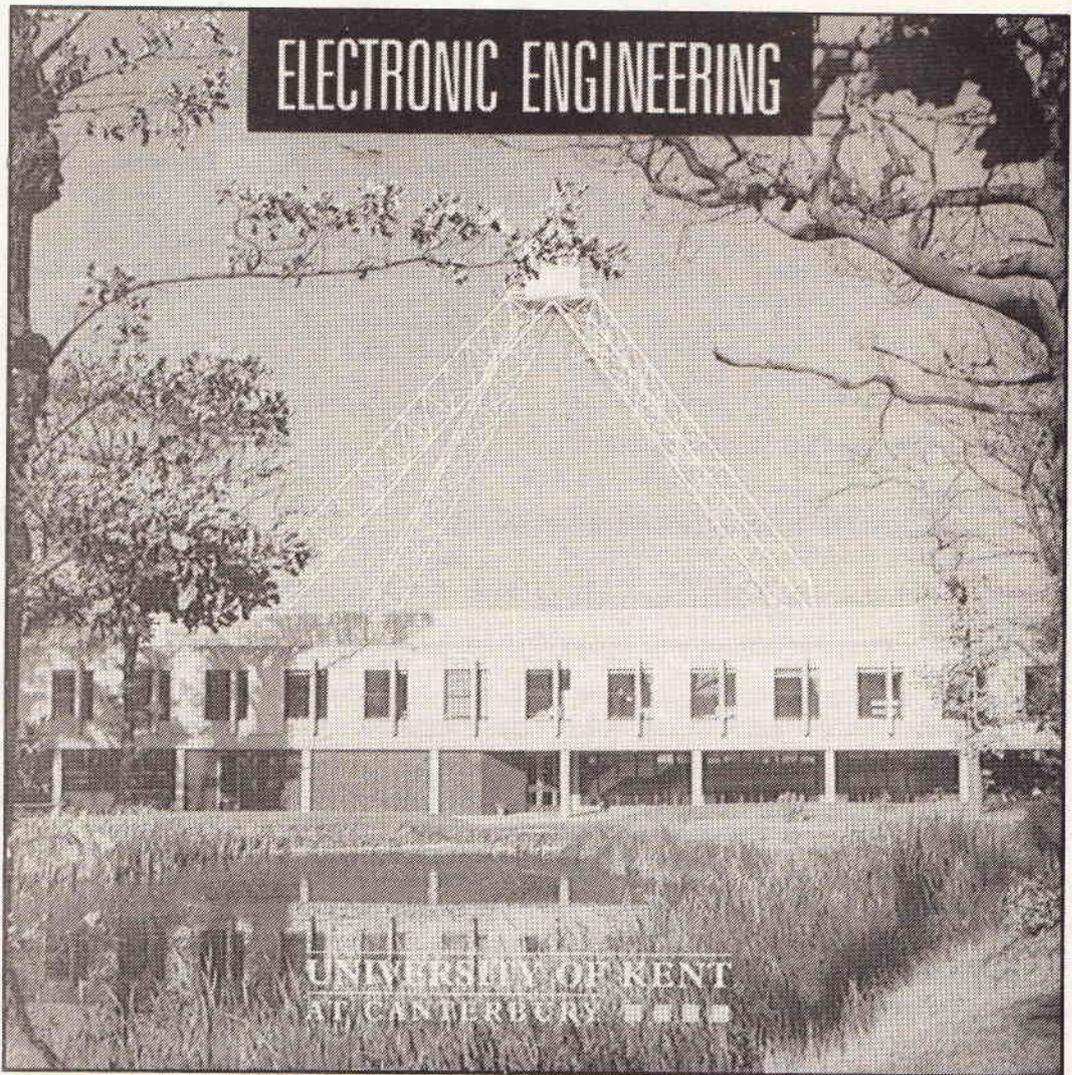

Dr. Ken Smith discusses a new Four-year Degree Course at the University of Kent.

Probably many readers of ETI wonder about how the professional edge of Electronics leaps forward. The news-stand magazines do a very fine job showing some of this — I make the point later that they perform a very low cost educational job, which deserves more recognition. I wonder if the same readers ever give thought to possibilities of studying for an Honours Degree in the subject?

The traditional way into such advanced work involved getting sufficient grades at GCE 'A' Level in science and maths (ugh!) subjects, and this route naturally still applies. But consider all the people who often say (at least to themselves . . .) "If only I'd had the chance — I really would love to go to University." Said not only to themselves, because I have heard many say as much to me at various times.

I said 'ugh!' after mentioning Mathematics just

now. You might have nodded agreement at this point. Perhaps you have been to a party or meeting, and overheard someone boasting that they are 'pretty thick' at Maths, but it has not held them back! (Yet have you come across anyone boasting, "I can't read or write."? No-one admits that, — there's shame in being illiterate, but why not an equal shame at being innumerate. . . ?)

The way Maths has often been portrayed in school becomes so impossible because of bad teaching, that young people turn away pretty quickly. Even in our technical hobby magazines, we end up 'apologising' if a formula slips through. Yet many popular authors in magazines like ETI have done wonders with beginners' articles. So have the Radio Amateurs' Exam Courses. You will find these often introduce ways to simple design calculations which are fun, together with the electronics. The Govern-

ment should be very grateful for this rather widespread area of costless (to them . . .) 'self-help' educational activity in the voluntary sector.

Returning to the arena of public investment, money has become available to some extent (from the Government) to enable many more people to gain access to higher studies in engineering. One or two Universities have begun to develop access type Courses, which should enable more mature, and experienced people to return to studies. Also, (and with apologies to the implicit criticism about teaching at school level earlier) younger people (17 yr olds) than those traditionally entering University can seize the chance to get out of school, if they have found school intolerable for one reason or another and do the Foundation studies in a stimulating one year Course at University.

A Four Year Course


With a course such as this at Kent you would come up to the University for a First year course which lays the foundations in a challenging and stimulating way. You will find these developed in programmes offering Maths, Physics, Electronics and Language Skills, thus enabling you to enter the three year Honours Course for B. Eng Degrees with full Professional credit and qualifications at the end of it.

The First Year I talked about above, has grant assisted status. The Course has plenty of Laboratory practical work on the basics. You would find experiments and measurement techniques, some Electronics projects, even simple Surface Mounting skills and practice. The Course also contains a stimulating Tutor-guided study of the interesting Maths. background required, (here is your chance to start, say, that study of Calculus you've always wanted to do. . .) together with Physical and Electronics Theory, as I indicated.

You might ask, is a such a non-traditional entry to an advanced study likely to succeed? Once in the stuffy old past, the answer would have been "No, because only a few 'special' people possess such ability", (Usually the Middle Class prodigy who went to Public Schools . . .). The Open University has convincingly shown this is a most false assumption — itself no doubt founded on Britain's rather Class conscious Society of some time ago.

Opportunities For The Future

It doesn't need me to state how Electronics has and is revolutionising ways of life. It permeates virtually everything now. Art, including its visual and musical aspects makes mighty use of Electronic techniques, and it has permeated virtually every home and workplace. A glance along the magazines rack in any Bookshop shows many Electronics and Computing hobby magazines on offer. But if you stop to think, it is a most unusual phenomenon — amateurs and hobbyists can vie with professionals, using exactly the

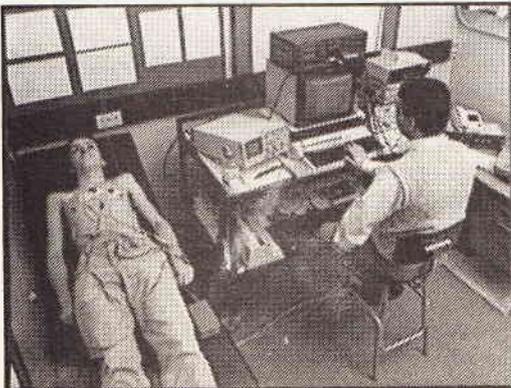


same components/techniques as they do — and make important contributions. The pastime side of the subject is not a 'toy' version as in many other fields.

We are likely to find such applications of advanced techniques, and the research, design and development for the future, continually expanding. More people with skills at all levels will be needed.

What's Next?

Because contemplating a return to full time study may seem perhaps somewhat daunting, or you may know some young person who is unsure about his or her ability and asking you for advice, we have put together a package which explains more detail to help you see what is involved. A second stage when you have read the material in the package, could very well be to take up our offer of help in assessing yourself to see if you would fit in with the scheme on offer. If after that you think you really would profit greatly, and you 'take the plunge', then in a few years time you might be working in projects involving Fourier Methods of Signal Analysis, Cellular and Spread Spectrum Radio Systems, the digital telephone networks and other remarkable developments in Digital Comms. techniques. You name it, you could be doing it. Of course, all the other benefits of University life would widen

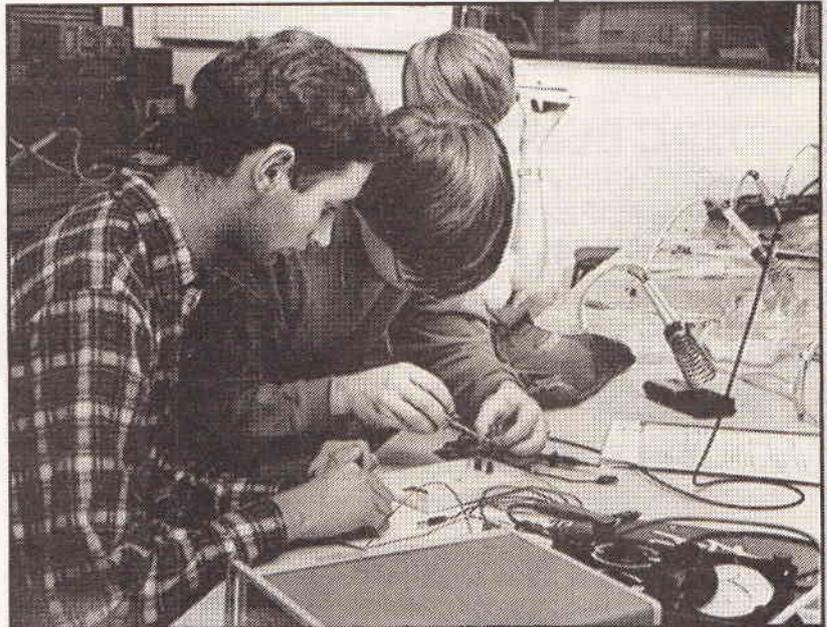


your views. Joining the Clubs and Societies, debating all manner of philosophy and argument — all forms the unique part of the best education we offer — the University.

Do we have a vested interest in the success of this new scheme of study? Well of course we do. As professionals with a commitment in the (Electronic) future of Britain and Europe, we know many keen bright people slip through the educational net year after year. In particular, we wish to show excellent results and success by means of this Course, so that the Government will maintain funding, expand the method to many other Institutions, and generally work to improve our Education system and standards.

If you feel moved with enthusiasm by this possibility, then write to me for more details. And I am sure, the Editor would like to hear from you regarding your views.

Dr K L Smith,
Electronics Engineering Laboratories,
The University,
Canterbury,
Kent CT2 7NT.

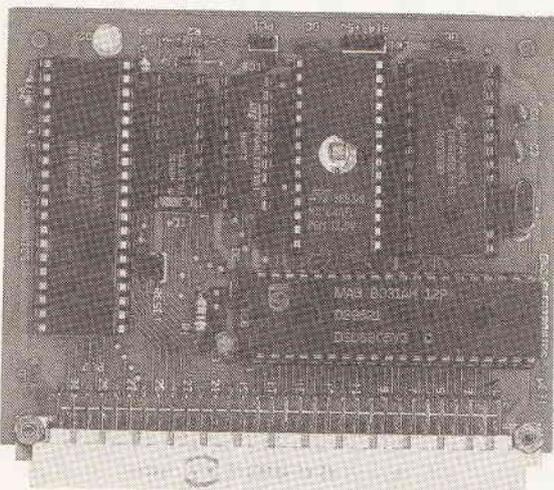★ ★ **8031** ★ ★
LOW COST DEVELOPMENT & TARGET SYSTEM



★ ★ **£99.95** ★ ★ + £5.00 Carriage + VAT

Includes 32k RAM, 8K EPROM, 38 I/D Lines,
 IBM PC/XT/AT Hosted SB51 Cross Assembler,
 Manual and Full Technical Support.

8031 Module only £59.95. 80188 & 64180 modules available

GNC ELECTRONICS

Units 2B-2C Gilray Road
 Diss, Norfolk IP22 3EU
 TEL: 0379 644285



electronize
CAR ALARMS

MICRO-PRESSURE CAR ALARM

This new type of alarm is triggered by a unique pressure sensing system. As any vehicle door is opened air is drawn out, causing a minute drop in air pressure. A sensor detects this sudden pressure change and sets off the alarm. A sophisticated arrangement of electronic filters and timers provide features to match more expensive ultra-sonic systems.

- ★ 1 Micro-pressure intruder detection.
- ★ 2 Operates on all doors and tailgate - no switches needed.
- ★ 3 Automatically armed 1 minute after leaving vehicle.
- ★ 4 10 second entry delay with audible warning.
- ★ 5 Sounds horn intermittently for 1 minute - then re-arms.
- ★ 6 Easy fitting - only 3 wires to connect - no holes to drill.
- ★ 7 Compact design can be hidden below dashboard.
- ★ 8 All solid state Power MOSFET output - no relays.
- ★ 9 Adjustable sensitivity.

MICRO-PRESSURE ALARM £21.75 D.I.Y. PARTS KIT £15.75

MICRO-PRESSURE TRIGGER

This module adds MICRO-PRESSURE sensing to any volt drop operated alarm simply by connecting two wires across the vehicle's 12v supply. Use it to upgrade an existing alarm or combine the benefits of both systems.

MICRO-PRESSURE TRIGGER £14.90 D.I.Y. PARTS KIT £10.85

VOLT DROP CAR ALARM

This alternative alarm uses the popular voltage drop method of triggering. Based on the timers of the micro-pressure alarm it offers features 3 to 9 above but relies on the existing door switch operation for triggering.

VOLT DROP ALARM £20.55 D.I.Y. PARTS KIT £14.55

120dB SIREN

An ear piercing alternative to using the car horn. This high intensity piezo siren can easily be added to attract even more attention.

120dB PIEZO SIREN £12.95

All the above include cable, connectors and clear, easy to follow instructions. All kits include case, PCB, everything down to the last washer, even solder.

All prices now include post, packing and VAT on U.K. orders. Same prices apply to all European countries. For delivery outside Europe please add £3.

Telephone orders accepted with VISA or ACCESS payment.

Order direct (please quote ref. ET15) or send for more details from :-

ELECTRONIZE DESIGN


Tel. 021 308 5877

2 Hillside Road, Four Oaks, Sutton Coldfield, B74 4DQ



BLUE ROSE ELECTRONICS

NEW 1991
CATALOGUE OUT NOW!

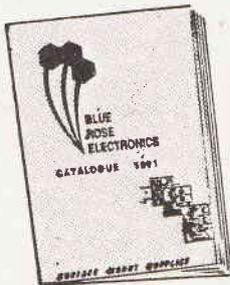

SURFACE MOUNT SUPPLIES

CONTAINS NEW RANGE OF SM KITS
 FULL RANGE OF COMPONENTS
 & SM HARDWARE

SEND £1.50 (inc P&P) FOR
 CATALOGUE & KIT LIST




Mail Order Address: 538 Liverpool Rd, Great Sankey, Warrington, Cheshire WA5 3LU
 Telephone: 0925 72 7848 (Callers by Appointment)

BINDERS

(0442) 66551

TELEPHONE ORDERS (24 HRS)

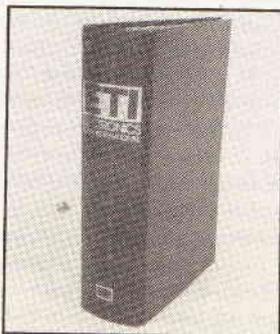Keep your collection of
ELECTRONICS TODAY INTERNATIONAL
 in mind condition with
 these specially
 commissioned binders.
 The price is just £6.90
 which includes postage
 and packing.



How to order

send cheque/p.o. to A.S.P.
 BINDER OFFERS, Argus
 House, Boundary Way, Hemel
 Hempstead, HP2 7ST.

Please supply ETI BINDERS @ £6.90 each inc. p&p

Total £ (Please make cheques/postal orders payable to A.S.P.)

NAME

ADDRESS

.....

.....

Or debit my Expiry

ACCESS/VISA Signature

Please allow 28 days for delivery

A VLF & ELF Earth Loop Antenna

2

For most observations, the author uses the permanent 35m base extending along the garden boundary, but when required, a temporary 135m base is extended into the adjoining farmland where it can be swung over an 180 degree arc. Coaxial cable is used to bring the leads from the earth bases into the garden chalet used as study/laboratory. Almost directly above the 35m earth base is an elevated antenna about 7.0m high and 35m long (Figure 1).

To reduce contact resistance between the earth rods or plates and the soil, they should be as large as practicable, and it was found that 3.0mm mild steel plate to be very suitable; also only a very low level of Galvanic current was produced. For the permanent base, a pair of plates about 300mm wide and 1.5m long, obtained from the local scrap yard, were laid lengthwise in the soil. This gives a DC resistance of about 120R. For the temporary base, a pair of polished spades was an excellent alternative. As far as minimising Galvanic currents is concerned, the ideal earth is a carbon rod of the kind used in search lights, surrounded by crushed charcoal.

Conversion

Antennae convert electromagnetic waves into alternating electric currents which can then be converted into an audible sound, or the waveform displayed by an oscilloscope. Depending upon their design, antennae respond to either the 'total' Hertzian wave, or only its magnetic or electric field. But first let us look at tuners which respond to the electric currents produced by the antenna.

Receivers

Receivers used by the author were generally described in part 1, but now let us look at heart of the receivers — their tuning coils. Tuning 'A' (Figure 2) has an inductor consisting of 500 turns of 0.9mm enamelled copper wire wound on a 15mm diameter ferrite rod 180mm long to give an inductance of approximately 20mH. The coupling coil, located at the end of the tuning coil, has 300 turns tapped at every 50 turns. Tuning as explained in part 1 is by means of a capacity box to give continuous coverage from less than 1.0kHz to more than 15kHz.

'B' also has its coils wound on a ferrite rod, but is 10mm diameter and 180mm long. The tuning inductor is divided into two sections; the original rod with a 'long wave' winding, is retained as one section and the other consists of 250 turns of 0.19mm diam enamelled wire. The original section has inductance of about 4mH but with both sections in series, the total inductance is about 15mH. The coupling coil is located between the two sections and has 500 turns 0.19mm wire tapped every 100 turns. Tuning is by a double gang 500p tuning capacitor (both gangs in parallel). For frequencies between 150-90kHz the original winding is used alone, but for frequencies between 90kHz-40kHz, both sections are connected in series (Figure 3) Tuner 'C' is identical to 'B' except that it has no coupling coil.

The narrow bandwidth of the tuning coil limits frequency response, so when we look at a modulated signal, we see selectivity is reduced by the 500k variable resistor connected across the tuning coil.

Impedance

As already explained, with tuners 'A' and 'B' the tuning

George Pickworth continues to probe the Earth in search of those mystery signals.

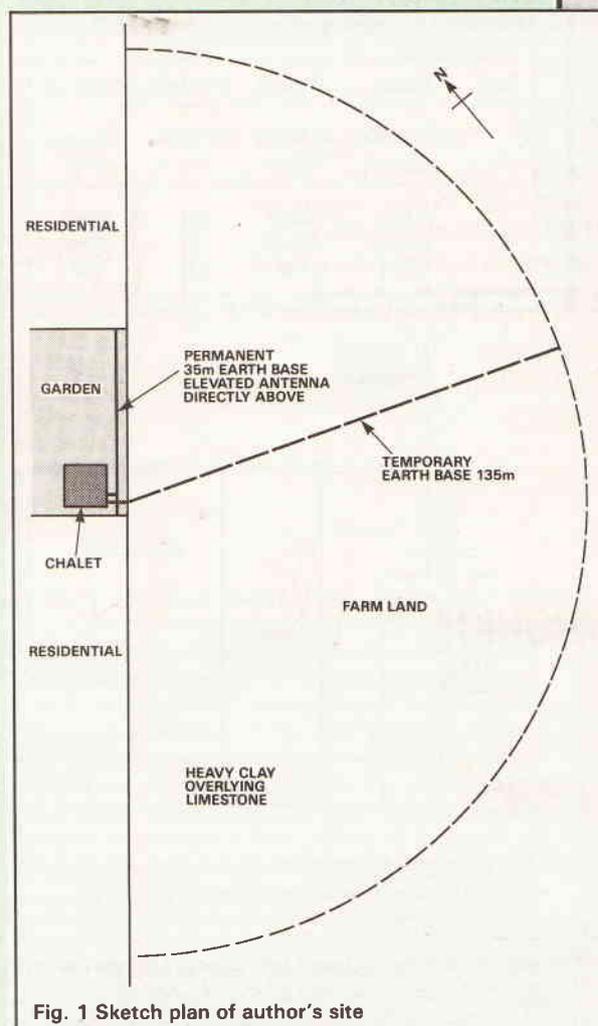


Fig. 1 Sketch plan of author's site

coil is matched to the impedance of the earth loop by means of a tapped coupling coil. With the coupling coil of 'A' tapped to give best signal strength, (DC resistance between 1.0 and 3.0R) the input impedance at frequencies between 1.0-6.0kHz is below 20R. This increases slightly when the tuning coil is brought into resonance with the incoming signal. At about 10kHz, input impedance rises to about 50R with little change when the tuning coil resonates or not. At 16kHz impedance increases to several thousand ohms, but then drops sharply to less than 50R at resonance. The impedance of the coupling coil of 'B', tapped for best signal strength is about 50R at resonance, but rises to a very high impedance when 'off resonance.

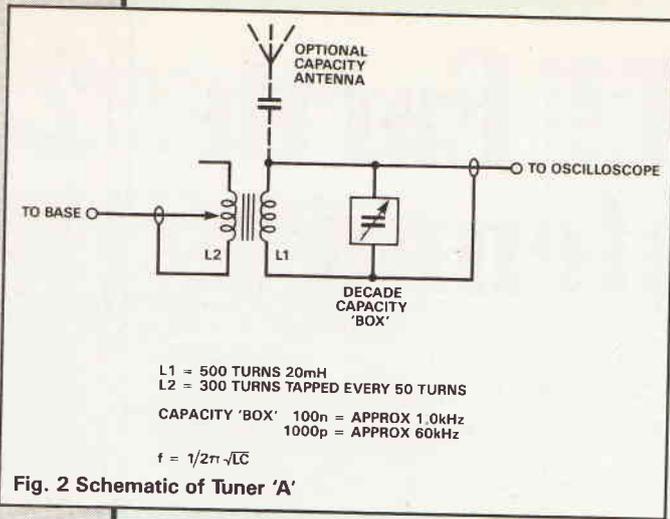


Fig. 2 Schematic of Tuner 'A'

Signal Strength

Signal strength measured across the 2M0 input terminal of the oscilloscope is shown in Table 1 below.

Tuner	Station	35m base	135m base	capacity ant.
'A'	3300Hz-250Hz	10-500mV	100-700mV	No signal
	16kHz	400mV	1.7V	120mV
'B'	60kHz	800mV	2.8V	230mV
	80kHz	475mV	1.5V	110mV
	198kHz	2.0V	6.3V	0.5V

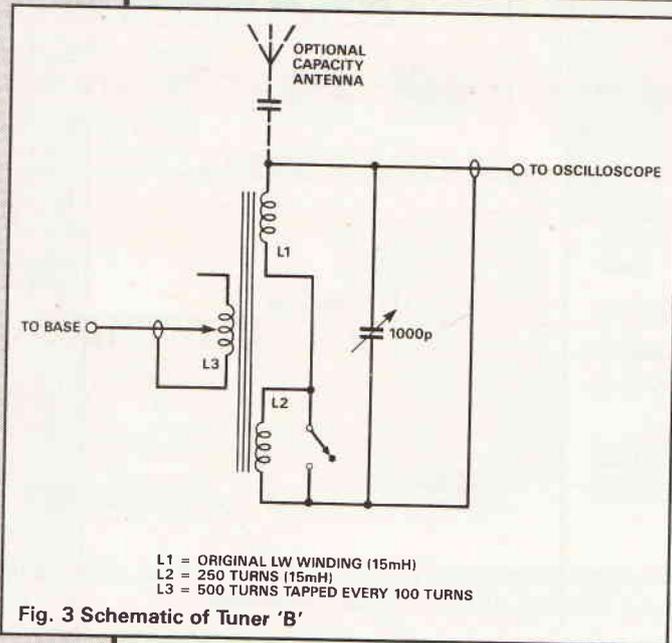


Fig. 3 Schematic of Tuner 'B'

All measurements were made shortly after the top soil became moist following a long dry period but while underlying limestone was still dry. Signal strength dropped by about 15% when the limestone became moist. The DC resistance of the 35m base was 160R, and the 135m temporary base, 210R.

The relative signal strength with a ferrite rod tuner/antenna employed alone and when coupled to the 35m elevated 'capacity' type antenna is shown in Table 2 below:

Station	Ferrite rod alone *	plus 35m capacity ant.
60kHz	8.0mV	225
80kHz	7.5mV	150
198kHz	35.0mV	0.5V

* in open farmland.

Linear Or A Loop

Disconnecting the lead at the distant earth pin and leaving the lead lying on, but insulated from the ground, caused signal strength with all stations to fall virtually to zero. Shorting the two earth pins with an additional lead, so to stimulate the current flowing directly from pin to pin, also gave no signal. However, extending the shorting lead to form a loop 150m in diameter, on the ground, so as to stimulate an earth loop, produced weak signals. The fact that the simulated earth loop gave a signal, albeit weak, and the direct return did not, and also the orientation of the earth base made no significant difference to signal strength, supports the earth loop theory, as a horizontal loop has no lateral orientation.

To gain some insight as to whether a closed loop antenna responds to a 'total' electromagnetic wave or simply its magnetic field, let us first look at a 'linear' resonant Hertzian type antenna, where a current is induced by a wave flowing linearly along the conductor. Being 'open ended' a 'linear' antenna does not significantly respond to a magnetic field. At first sight, therefore, a 'linear' resonant Hertzian antenna may seem to have little in common with an earth loop, but Hertzian antennas can also be in the form of a horizontal closed loop with a circumference equal to a complete wavelength or multiples of a wavelength. The 'Sky loop' is an example of an horizontal loop (Figure 4a and b).

However, the position of the nodes around a resonant horizontal loop antenna is determined by the position of feed point and the direction of the incoming wave, nonetheless the antenna is generally non-directional and its impedance is between 100-200R. Unlike a linear antenna, a loop also resonates when excited by magnetic field.

By inserting a resistor with a value more or less that of the loop's impedance, directly opposite the feed point, to form a so called 'terminated' loop, the loop becomes virtually non-resonant but more significantly, become directive and most responsive to waves flowing either way along an imaginary line connecting the feed point with the resistor. In this mode, one must assume that it now responds to the 'total' wave.

Antennas less than half a wavelength long cannot accommodate a standing wave, so cannot resonate; they intercept the wave's electric field and are known as capacity antennas; typical examples include AM car windscreen antennas where the conductor may also act as a defroster, and short rod type antennas used with earlier medium and low frequency car radios. Capacity type antennas exhibit a high impedance, which imposes minimal damping and are often connected directly to the tuning coil. As resonant long wire antennas are generally impractical at VLF so capacity type antennas are often used instead.

With the authors 35m capacity antenna coupled to tuner 'B' set to receive Radio 4, which has a wavelength of about 1500m. the antenna is only about 1/43rd of a wavelength long. At frequencies around 16kHz where the wavelength is about 19km, the 35m antenna is then only about 1/540th of a wavelength long, a ratio comparable to a typical rod type car antenna connected to a receiver tuned to medium wave station.

Now, as a capacity type antenna is relatively insensitive to a magnetic field, it is reasoned that if a signal was received by both an earth loop and a capacity antenna it most likely arrived as an electromagnetic wave. On the other hand, if no electric field was detected, it could be possible that the signal arrived as an earth current or as a magnetic field. So when required, the capacity antenna was coupled

directly to the 'top end' of the tuner windings of 'B' and 'C' by means of 500p variable capacitor.

Hypothetical Case

Let us, consider the hypothetical case of earth current communication over a range of 10km. WW1 earth current communication had a norm of 5.0km, and 10km is well within the range author's equipment, where the current would theoretically follow a loop having a circumference of about 32km. This is more or less equivalent to one wavelength at 9.0kHz. This assumes that a wave travels at the same speed in the earth as in air. By the same token, for a loop to resonate at 16kHz its circumference need be only about 19km, about 5.0km at 60kHz and only 1.5km at 198kHz. However at 2.2kHz the loops would have to be 136km long! (Figure 5).

Unfortunately, the earth loop theory is complicated by the fact that there is not one single earth loop on either side of the base line, but an infinite number of loops in parallel, each increasing in diameter, and each carrying proportionally less current and therefore the resistance of the soil increases. A resonant earth loop must therefore be compared with a multi-band or broad band antenna and these factors have frustrated the author's attempts to set up standing waves in an earth loop and prove that resonant earth loops can exist.

A study of earth loops is further complicated by the nature of the underlying earth. With overlying limestone, as on the author's site, the stream-lines are confined close to the surface and under these conditions earth current signalling has the greatest range. However, current flow lines are not confined to land; they also develop in water, and as saltwater is a better conductor than earth, stream-lines do not extend as far as on land. In deep water, as Preece demonstrated, stream-lines form a hemispheroid; indeed, the same would theoretically occur on land, but the various strata flatten or distort the hemispheroid.

Nonetheless, as Preece had also shown, the basic principles that govern earth loops on land also apply to water and in 1913, an American named Greenleaf Whittier Pickard patented a system based on current stream-lines for communication between submerged submarines. A magnetic field will extend through water, whereas an electromagnetic wave is

highly attenuated, is it therefore, the magnetic field component of the 16kHz VLF Hertzian wave that allows communication with a submerged submarine?

Conclusion

These experiments show that under the author's conditions, a pair of earth rods form an efficient ELF, VLF and LF antenna, so earth loops presumably occur, but is open minded on whether the loops are resonant, or whether they respond to the 'total' Hertzian wave, or just its magnetic field. As an earth base can theoretically form loops of infinite circumference, resonant earth loops may well exist.

With regard to the origin of ELF signals below 3.3kHz, for which no organisation has admitted responsibility, the author can only speculate. As no complementary electric field has been detected, could these ELF signals originate from latter day replicas of Preece's magnetic communication system, but with

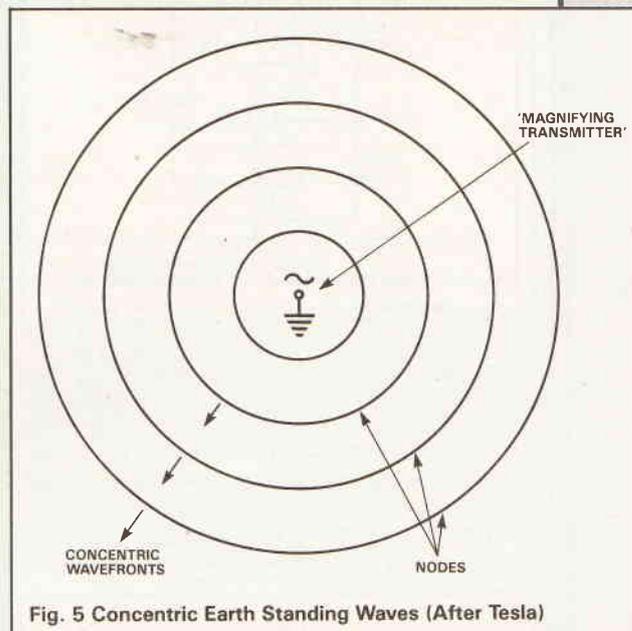


Fig. 5 Concentric Earth Standing Waves (After Tesla)

infinitely more powerful magnetic pulse transmitters? Could they, even result from the resuscitation of Tesla's 'earth standing wave' system? (Figure 5). Indeed the damped waveform of the 2.2kHz signals bears a striking resemblance to what we would expect from Tesla's 'magnifying' transmitters. Or, could they be transmitted as earth currents and, obeying Stanley's theory, travel through the surface of the earth via inductively coupled earth loops?

However, it would seem more likely that the 35m elevated capacity antenna working with an oscilloscope does not have sufficient amplification to detect ELF Hertzian waves, but that they may become apparent with greater gain. Having said that, greater amplifier gain, introduces its own problem.

No matter how the ELF signals arrive, the value of an earth loop antenna for their reception seems beyond doubt, and allows amateur scientists to study these man-made experimental, and naturally generated signals which might otherwise be impossible. Moreover, the cost of an earth loop antenna is minimal and as it can be made invisible, it is environmentally acceptable and does not attract attention.

References:

Tesla Nikola	Colorado Springs Notes	1900
Fahj J J	A History of Wireless Telegraphy	1901
Laughter Victor	Wireless Telegraphy Hand-Book	1909
Signals Service	Technical Instructions (France)	1915-1917
Stanley Rupert	Text Book on Wireless Telegraphy	1919
	Amateur Radio Handbook	1990

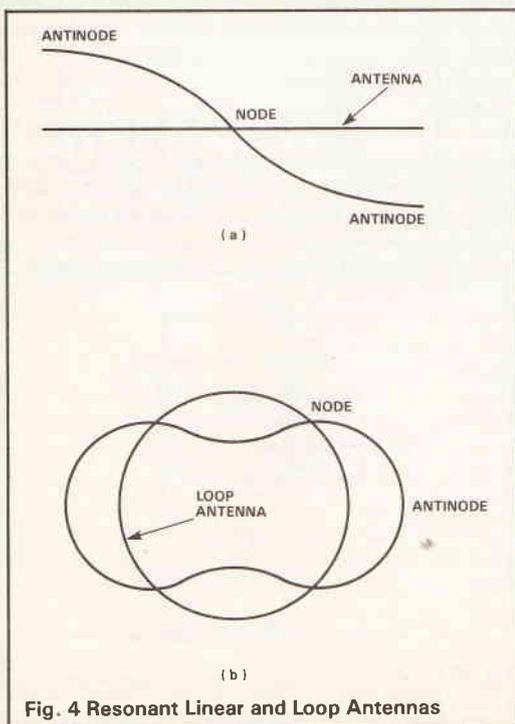


Fig. 4 Resonant Linear and Loop Antennas

Constant Current Generator Circuits

Ray Marston takes an in-depth look at constant current generator principles, applications, and circuits.

Constant current generators (CCGs) are, as the name implies, circuits that generate a constant load current irrespective of wide variations in load resistance or voltage. Figure 1 shows a

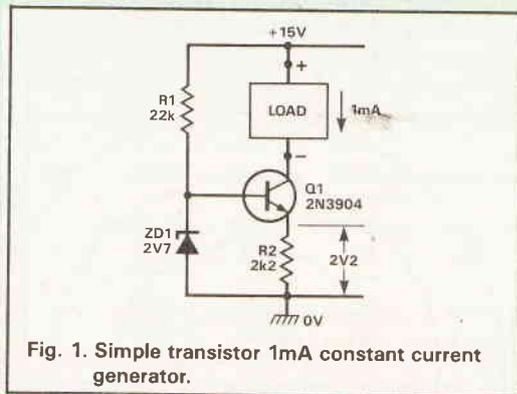


Fig. 1. Simple transistor 1mA constant current generator.

simple example of such a circuit. Here, Q1, is used in the common emitter mode; it has a stable 2.7V set on its base via R1 — ZD1, and thus generates an emitter current of about 1mA via R2; consequently, since the collector and emitter currents of a high gain transistor are almost identical, the collector (load) current remains virtually constant at 1mA in spite of load resistance variations between zero ohms and 12k (at which value the transistor is close to saturation).

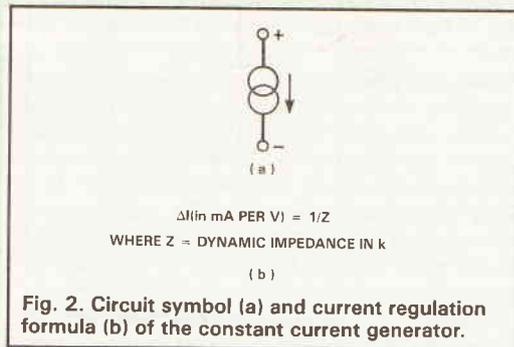


Fig. 2. Circuit symbol (a) and current regulation formula (b) of the constant current generator.

Figure 2a shows the standard symbol used to represent a constant current generator (i.e. the collector-to-ground path of Figure 1); note that the symbol does not indicate the nature of the CCG's circuitry. The most important parameters of a practical CCG are its nominal operating current value and its dynamic impedance (Z). This last parameter represents the current regulation accuracy, as shown by the formula of Figure 2b; thus, if the Figure 1 circuit has a Z value of 1M, its current varies by 1μA per volt change on Q1's collector.

Generator Applications

Constant current generator circuits are sometimes used purely as current generators, as in the four applications shown in Figure 3, and at other times simply as high dynamic impedances, as in the three examples shown in Figure 4.

Figure 3a is the basic circuit of a linear-scale

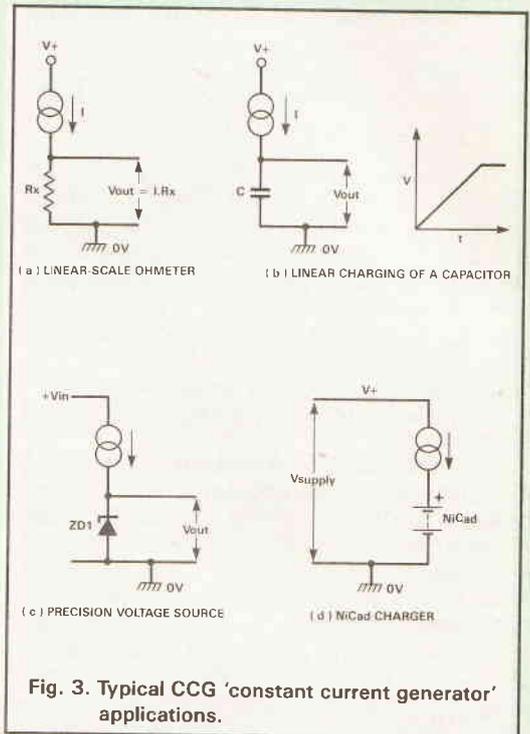


Fig. 3. Typical CCG 'constant current generator' applications.

ohmmeter in which the Rx value is read off on a simple voltmeter; if the CCG's 'I' value is 1mA the output voltage is 1mV per ohm of Rx value, and if 'I' is 10μA the output is 10mV per kΩ, and so on.

In Figure 3b the generator is used to provide

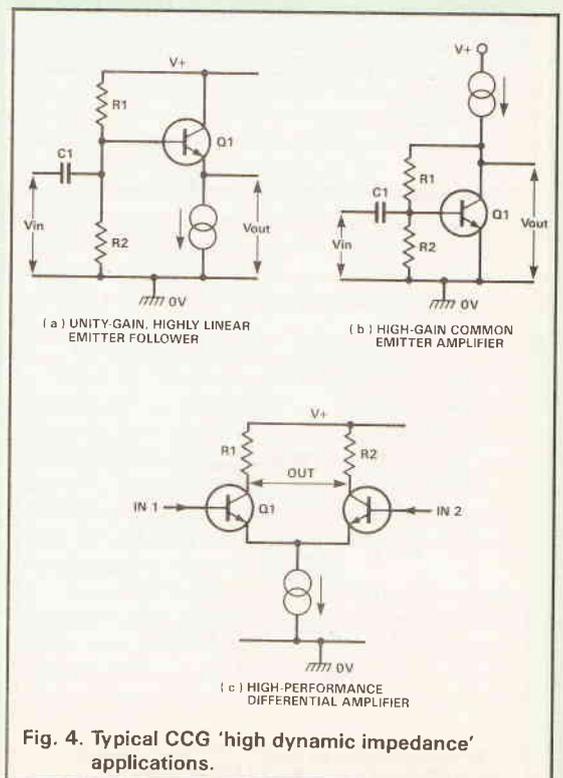


Fig. 4. Typical CCG 'high dynamic impedance' applications.

CIRCUITS

linear charging of a capacitor; this circuit is useful in linear timebase generators and the like.

Figure 3c shows a typical power supply application in which the CCG applies a fixed bias current to the zener diode, irrespective of wide variations of input voltage, and thus enables the zener to generate a very stable output reference voltage.

Figure 3d shows how the generator can be used as a Ni-Cad charger in which the charge current is constant irrespective of the number of cells that are used in the Ni-Cad stack.

Figure 4a shows a CCG used as the emitter load of an emitter follower, where the high dynamic impedance of the generator gives the follower excellent linearity and near-unity gain.

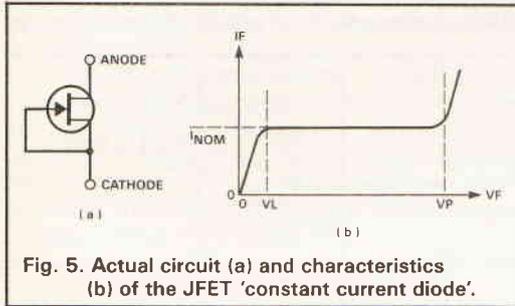


Fig. 5. Actual circuit (a) and characteristics (b) of the JFET 'constant current diode'.

In Figure 4b the CCG is used as the collector load of a common emitter amplifier, where its high dynamic impedance causes the amplifier to operate with very high voltage gain (typically about 70dB).

Finally, Figure 4c shows the CCG used as the emitter load (tail) of a differential amplifier, where its high dynamic impedance causes the amplifier to operate with high gain, excellent linearity, and a high CMR ratio.

Constant Current Diodes

Practical CCGs can be built using a variety of discrete or integrated component, or can be obtained in fully integrated form. The simplest of all CCG devices is the so-called 'constant current diode' which, as shown in Figure 5, is actually an n-channel depletion-mode JFET with its gate and source terminals shorted together so that, when driven by a suitable voltage (typically variable from about 3V to 50V), it passes a constant current with a value pre-set (with a typical tolerance of $\pm 20\%$) during manufacture. These devices are available in a limited range, with typical I/Z values between 0.5mA/3M Ω and 5mA/0.3M Ω .

Transistor CCG Circuits

Bipolar transistors can easily be configured to act as efficient CCGs, as already shown in Figure 1. This basic circuit can readily be altered in a variety of ways to give different characteristics. Figure 6, for example,

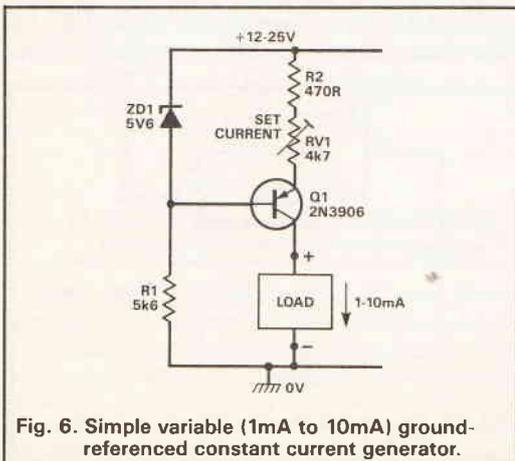


Fig. 6. Simple variable (1mA to 10mA) ground-referenced constant current generator.

shows how it can be 'inverted' to give a ground-referenced constant current output that is variable from about 1 — 10mA via RV1.

In most practical CCG applications the precise magnitude of the constant current is not of great importance, and in such cases the basic circuits of Figures 1 and 6 will satisfy most needs. If greater precision is needed, the characteristics of the reference voltages of these circuits must be improved, to eliminate the effects of supply line and temperature variations. One simple modification is to replace R1 with a CCG, as shown in Figure 7, so that the zener current (and thus the zener voltage) is independent of variations in supply line voltage.

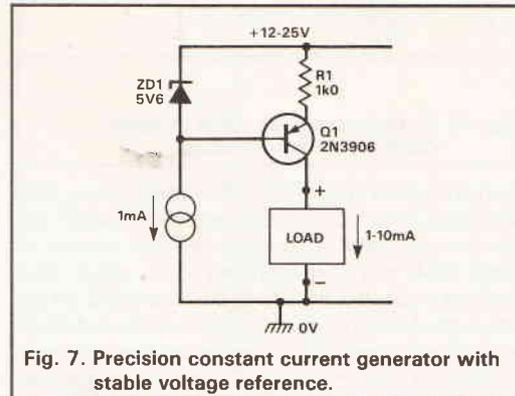


Fig. 7. Precision constant current generator with stable voltage reference.

If high precision is needed the zener reference should have a temperature coefficient of $-2\text{mV}/^\circ\text{C}$, to match the V_{BE} coefficient of Q1. An easy way round this problem is to use a forward biased red LED in place of the zener, as shown in Figure 8; the LED

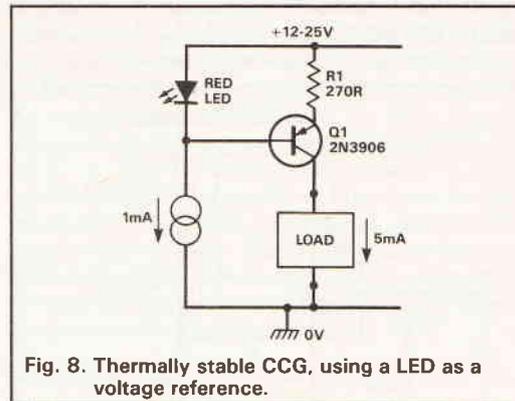


Fig. 8. Thermally stable CCG, using a LED as a voltage reference.

voltage is roughly 2V, so only about 1.4V appears across 270R emitter resistor R1, which sets the constant current output level at about 5mA.

Note that all the transistor CCG circuits shown so far are '3-terminal' designs that need both supply and output connections. Figure 9 shows an example of a 2-terminal CCG that generates a fixed 2mA and

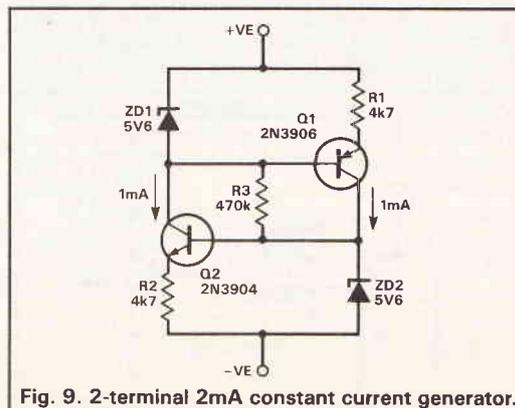


Fig. 9. 2-terminal 2mA constant current generator.

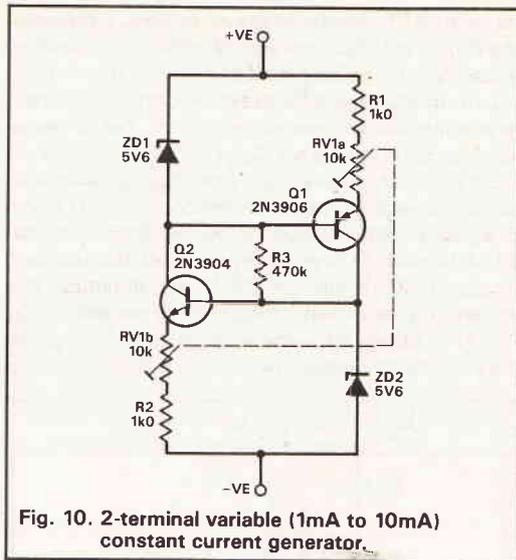


Fig. 10. 2-terminal variable (1mA to 10mA) constant current generator.

can use supplies in the 15V to 40V range. Here, ZD1 develops a fixed 5.6V on the base of Q1, which (via R1) thus generates a constant collector current of about 1mA; this current drives ZD2, which thus develops a very stable 5.6V on the base of Q2, which in turn generates a constant collector current of about 1mA, which drives ZD1. The circuit thus acts as a closed-loop current regulator that generates a total constant current equal to the sum of the two collector currents. R3 acts as a start-up resistor that provides the transistors with initial base current.

Figure 10 shows a variable version of the above 2-terminal CCG; its operating current is variable over the approximate range 1mA to 10mA via RV1. Note that these two circuits need a minimum operating voltage, between their two terminals, of about 12V, but can operate with maximum ones of 40V.

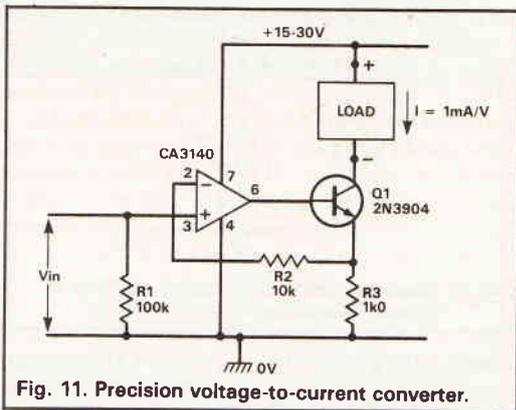


Fig. 11. Precision voltage-to-current converter.

Op-amp CCG Circuits

High-performance constant current generators can easily be built using standard op-amps, either on their own or in conjunction with an external transistor. Figure 11, for example, shows how a precision voltage-to-current converter can be made by wiring a 3140 op-amp and a transistor as a unity-gain voltage

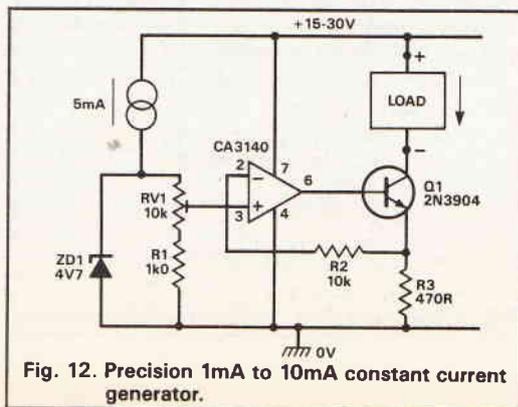


Fig. 12. Precision 1mA to 10mA constant current generator.

follower and taking the output (load) current from Q1's collector; the V-to-I conversion factor is controlled via R1, and is 1mA/V at 1kΩ.

Figure 12 shows how the above circuit can be converted into a precision 1-10mA CCG by supplying the current-setting input voltage via a stable 4.7V zener source and RV1; note that the 4.7V zener has a near-zero temperature coefficient.

All the CCG circuits shown so far are unidirectional current generators, in which the load current can flow in only one direction. A very different type of CCG is the voltage-controlled bilateral circuit, which can be used to convert an AC input voltage into an AC load current that is virtually independent of the value of load resistance. Figure 13 shows a simple example of such a circuit. The op-amp is wired as an inverter, but uses the 'load' as its feedback resistor; the

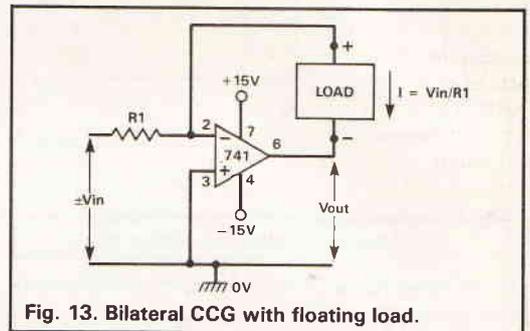


Fig. 13. Bilateral CCG with floating load.

inherent circuit action is such that the feedback (load) current self-adjusts to equal $V_{IN}/R1$, irrespective of the load resistance, so bilateral constant current generation is automatically obtained. Note that the output voltage is directly proportional to the load impedance.

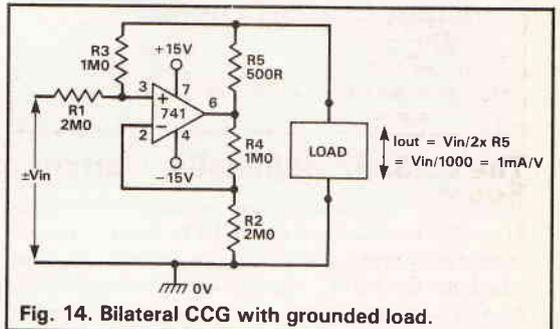


Fig. 14. Bilateral CCG with grounded load.

The above bilateral circuit is useful in applications where the load is fully floating. If the load is not floating but has one end tied to ground the alternative circuit of Figure 14 can be used as a bilateral CCG. Here, when R1 to R4 have the values shown the circuit feedback causes the output load current to be determined entirely by the values of R5 and V_{IN} , irrespective of the value of load impedance. With the R5 value shown the load current equals 1mA/V. Note

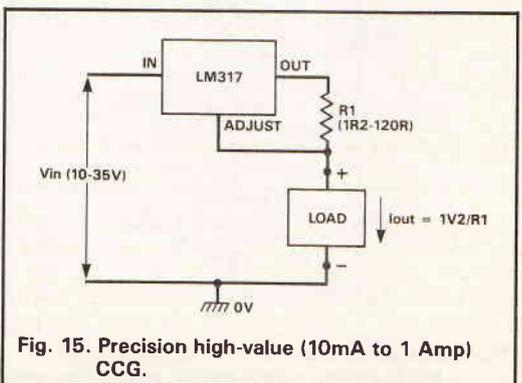


Fig. 15. Precision high-value (10mA to 1 Amp) CCG.

that the circuit's output voltage is directly proportional to the load impedance, and the circuit can thus readily be adapted for use as an impedance-measuring piece of test gear.

A High-current Generator

Most practical CCG circuits are designed to give fairly low outputs currents (usually only a few mA). There are occasions, however (such as when charging Ni-Cads), when fairly large output currents are needed, and one easy way to obtain these is to use an LM317 3-terminal voltage regulator IC in the configuration shown in Figure 15. The basic action of this IC is such that its OUT terminal automatically adjusts to a value 1.2V greater than that set on the ADJUST pin. In the diagram the IC's output current flows to ground via 'sensor' resistor R1, which has its low end taken to the ADJUST pin. Consequently, the output current automatically self-adjusts to a value of $1.2V/R1$, almost irrespective of the load impedance, and the circuit thus acts as a constant current generator. When R1 has a value of 1R2 the circuit acts as a 1 amp generator, and when it has a value of 120R it acts as a 10mA generator. The circuit can be used with any input (supply) voltage in the range 19 — 35V.

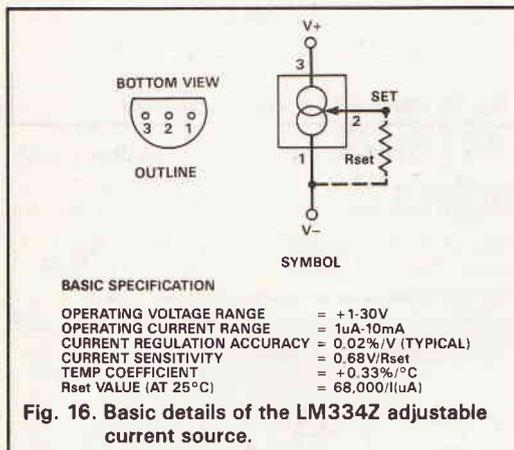


Fig. 16. Basic details of the LM334Z adjustable current source.

The LM334Z Adjustable Current Source

The LM334Z IC is a high-performance 2-terminal constant-current generator that can be used with supplies in the 1-30V range and can have its operating current set to any value between 1A and 10 mA via a single external resistor (R_{SET}). Figure 16 shows basic details of the device, which is housed in a 3-pin package.

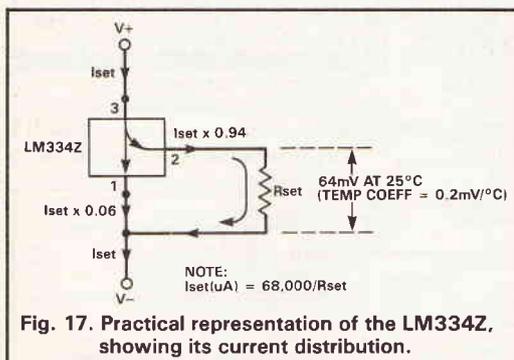


Fig. 17. Practical representation of the LM334Z, showing its current distribution.

Note that the LM334Z symbol of Figure 16 may give a deceptive impression of the device's operation; a more accurate representation of the device action is shown in Figure 17, where the following points should be noted. The I_{SET} current flowing into the LM334Z via pin 3 splits within the device, with only 6% of it flowing to the negative rail via pin 1, and with

the other 94% flowing to the negative rail via pin 2 and R_{SET} : at 25°C a voltage of 64mV is developed across R_{SET} (between pins 2 and 1), and this voltage has a temperature coefficient of +0.2mV/°C. Thus, I_{SET} is temperature-sensitive, and at 25°C has a value (in μA) of $68,000/R_{SET}$.

Figure 18 shows the basic way of using the LM334Z as a 2-terminal current source, and Figure 19 shows how the circuit can be modified, with the aid of R1 and D1 (which must share the thermal environment of the LM334Z), to eliminate the temperature sensitivity of the current source.

The operating current of the LM334Z is inherently temperature sensitive, and is given by the formula:

$$I_{SET} = (227\mu V \times ^\circ K) / R_{SET}$$

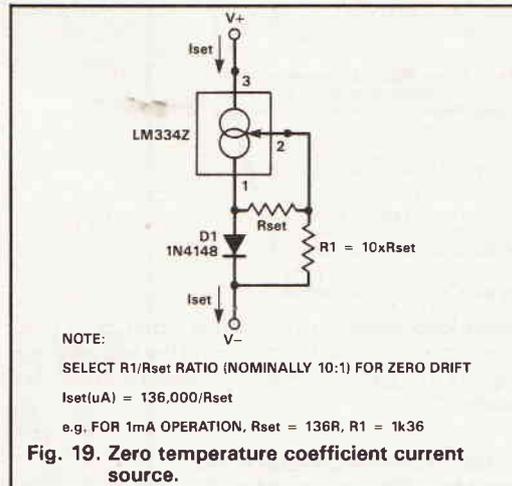


Fig. 19. Zero temperature coefficient current source.

Consequently, although the IC is not specifically designed for this purpose, the LM334Z can be used as a fairly accurate $^\circ K$ temperature-to-voltage converter. Figure 20 shows a version of such a circuit with an output sensitivity of 10mV/ $^\circ K$. Here, R_{SET} is chosen to give an I_{SET} current of (ideally) $293\mu A$ at 20°C (= 2.93 $^\circ K$), so that an output of 2.93 volts is generated under this condition. In practice, the basic circuit (when using 1% resistors) may give an initial error as high as 5% (= 150mV), which translates into a reading error of 15°C; if such an error is important, it can be eliminated by trimming the value of R_{SET} to give an output of precisely 2.93V at 20°C.

The Current Mirror

Before closing this look at constant current generator circuits, mention must be made of one of the most important elements used in modern linear IC design, the so-called 'current mirror', which takes the basic form shown in Figure 21. Here, Q1 and Q2 are a matched pair of transistors (usually integrated) and share a common thermal environment. When an input current (I_{IN}) is fed into diode-connected Q1, it makes Q1 generate a proportionate forward base-emitter junction of Q2 and, since the transistors are closely matched, causes it to sink an almost identical ('mirror') value of collector current (I_{SINK}). Q2 thus acts as a constant current source that is controlled via I_{IN} , but has the outstanding advantage of acting as such even at collector voltages of only a few hundred millivolts.

In practice the I_{SINK} current is (when perfectly matched transistors are used) always 1% to 2% less than I_{IN} , since some of I_{IN} is absorbed as base-drive current. Note that the circuit will still work quite well as a current-controlled constant current generator even if Q1 and Q2 have badly matched characteristics, but in this case may not act as a true current mirror, since its I_{SINK} and I_{IN} values may be very different.

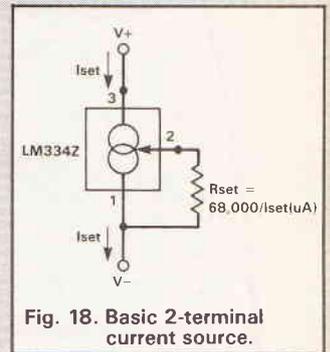


Fig. 18. Basic 2-terminal current source.

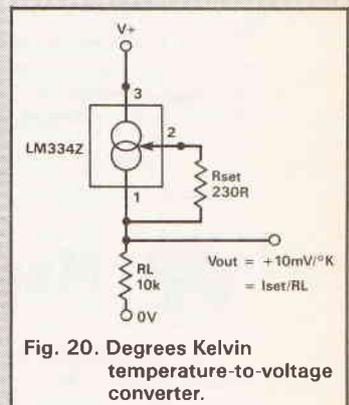


Fig. 20. Degrees Kelvin temperature-to-voltage converter.


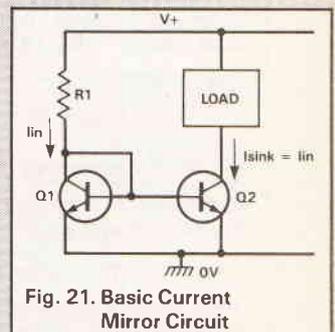


Fig. 21. Basic Current Mirror Circuit

Thyristor Tester

PROJECT

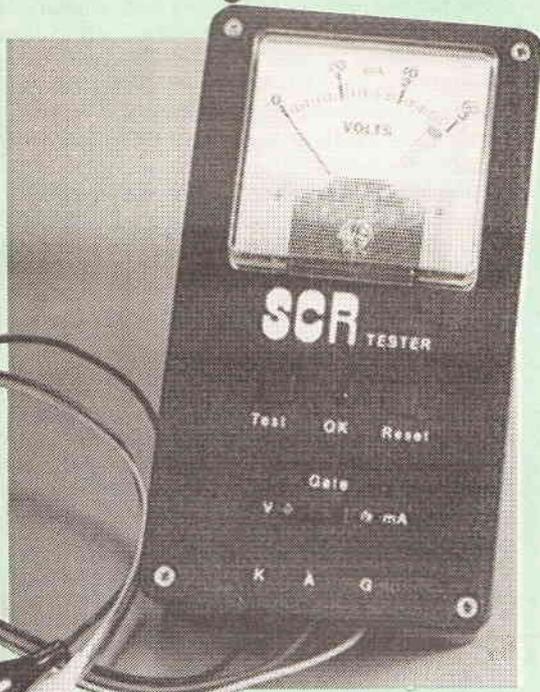

requirements for the device to reliably trigger. It is capable of testing a wide range of these devices, from small T092 encapsulated units to large stud mounting types capable of handling load currents of several hundred amperes!

The Thyristor

The thyristor may be considered as a development of the transistor in which a second emitter layer is added on the collector side. One effect of this is that the device is able to sustain alternative stable states, on and off. It also enables the device to operate in a triggering mode, whereby a small gate current may control the switching of the much larger load current. An indirect effect of the addition of this fourth layer is to enable the device to withstand high reverse voltages (In some devices an excess of 1KV!) and hence function as a rectifier.

With reference to Figure 1 it will be seen that the device has three terminals labeled here as A (anode) C (cathode) and G (gate). If the gate is made sufficiently positive with respect to the cathode a current will flow into the gate and trigger the device into conduction, enabling the load current to flow between the anode and the cathode. Once a sufficiently large anode current is established the gate may be disconnected and, providing that the anode current remains sufficiently high, the device will remain conducting indefinitely.

It may be concluded from the above that some form of variable power supply and current/voltage measurement circuit is required for testing thyristors. The unit, which is the subject of this article provides these functions automatically.

Circuit Description

The full circuit diagram for the thyristor tester is provided in Figure 2. Power for the thyristor tester is provided by a PP3 9V battery, B1 via switch SW3, a push to make-release to break switch. Capacitor C2 is a supply decoupling capacitor and is included to prevent the possibility of any voltage spikes reaching

A large number of modern components, such as resistors, capacitors, rectifier diodes, may often be conveniently checked for operation using a conventional multimeter set to its ohm range. When it comes to testing three terminal devices things become a bit more complicated and dedicated test equipment, such as transistor testers are often employed. The thyristor, in common with the transistor, is a three terminal device and as such requires more than a simple test on the ohms range of a multimeter in order to evaluate its capacity to in fulfil particular application.

The Thyristor Tester described in this article is designed to test thyristors for the correct operation and also to indicate the gate current and gate voltage

Another invaluable test item for the workbench by Mark Daniels.



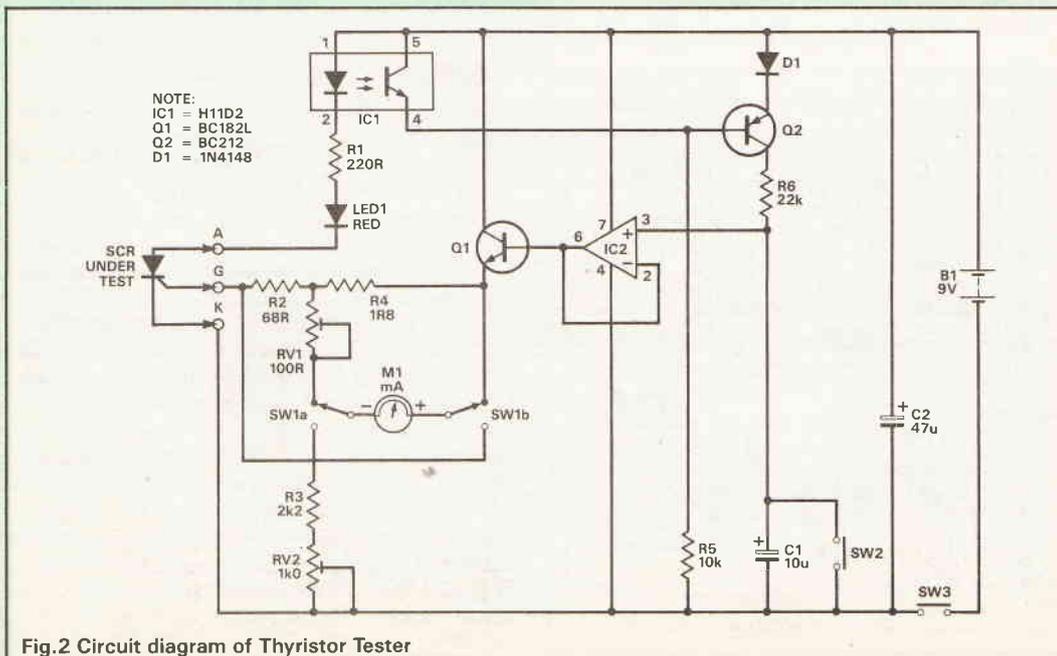


Fig.2 Circuit diagram of Thyristor Tester

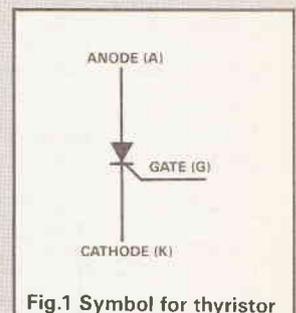

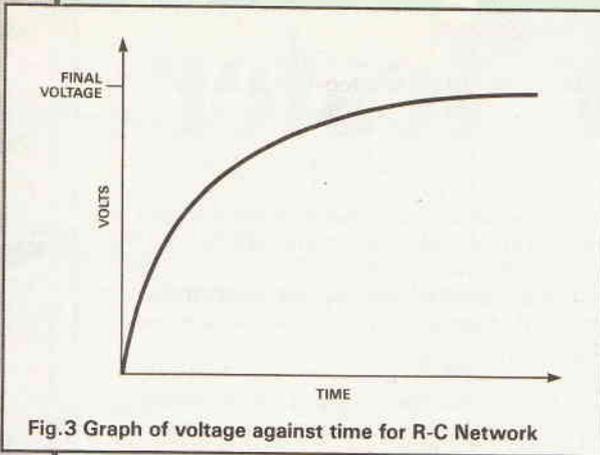


IC1, which could affect this device and cause incorrect readings on the meter, ME1.

When a thyristor is first connected to the tester and switch SW3 is closed, transistor Q2, a PNP device, is forced to conduct by the negative voltage on its base, provided by resistor R5. A small current flows through diode D2, the emitter and collector of Q2 and resistor R6 to charge capacitor C1. The voltage across C1 is initially zero, but as it charges the voltage across this capacitor rises exponentially, as shown in the graph of Figure 3.

The operational amplifier IC2 is connected as a super emitter follower in this application. This provides unity voltage gain but phenomenal current gain. The CA3140E specified for IC2 is slightly unusual in having a CMOS input stage and a bi-polar output stage. This provides it with the extremely predictable performance required in a piece of test equipment, by virtue of its extremely high input impedance (about 1M Ω) and a very low output impedance (negligible in this application). The output from IC2 is buffered by transistor Q1 which is connected as an emitter follower stage to provide the relatively heavy gate currents required by some thyristors under test.

Ignoring the meter circuitry for the present, Q1 emitter provides gate current to the thyristor via resistors R2 and R4. R2 is included to limit this current to a safe maximum under fault conditions. As capacitor C1 charges the voltage on the thyristor gate will rise, as will

the gate current, until a point is reached where the thyristor is conducting between its anode and cathode. A current may now flow through the device from the battery via LED1, resistor R1 and the led across pins 1 and of the opto-isolator IC1. LED1 will light up showing the operator that the thyristor has started to conduct, while the light from the LED in the opto-isolator falls onto the base of the photo-transistor which now conducts. The emitter of this NPN transistor is connected to the base of Q2 and causes Q2 base voltage to fall towards the positive supply rail, switching the transistor off. Diode D2 is included in Q2 emitter circuit to ensure that Q2 base can be made sufficiently positive to guarantee effective turn off of the device. When Q2 is turned off capacitor C1 stops charging and the input voltage to the operational amplifier IC1

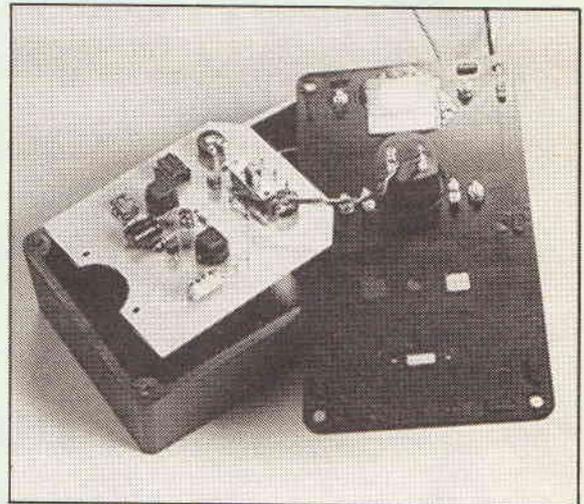

remains fixed at the voltage of C1 positive plate, and hence the thyristor gate current and voltage are stabilised.

The meter ME1, with switch SW1 in the position shown in Figure 2 will read thyristor gate current. Resistor R4 is a current shunt for the meter to enable it to read up to 60mA. Preset RV1 adjusts the current range of the meter. Resistor R3 and preset RV2 set the voltage range of ME1 to 3V, when SW1 is changed over to volts range.


Switch SW2 is included so that capacitor may be discharged completely prior to testing the thyristor. It may also be used to remove the gate signal to the thyristor while it is under test to check that the device remains conducting.

Construction

The majority of the components are mounted on a single sided glass fibre PCB, the foil pattern and component overlay are shown in Figure 4.

The following order of assembly is recommended: fit all resistors, the socket for IC2, then the two presets followed by the capacitors and two push switches. If the recommended switches are used it will be seen that they have a flat on one side. The switches should be mounted with the flat side towards the LED. Switch SW1 may need the holes in the PCB opening into slots before it will fit. It is suggested that double sided terminal pins be used for all external connections to the PCB as some wires need connecting to the underside of the board. The two transistors need to be fitted close to the board in order to clear the case lid. The LED is also fitted close to the board, but should be slightly higher than the transistors in order to protrude slightly through a suitable hole in the case lid. IC1 is soldered directly to the board without the use of a socket. The two meter leads are connected via the top side of the PCB. The rest of the leads are

Fig.4 Component Overlay for Thyristor tester.

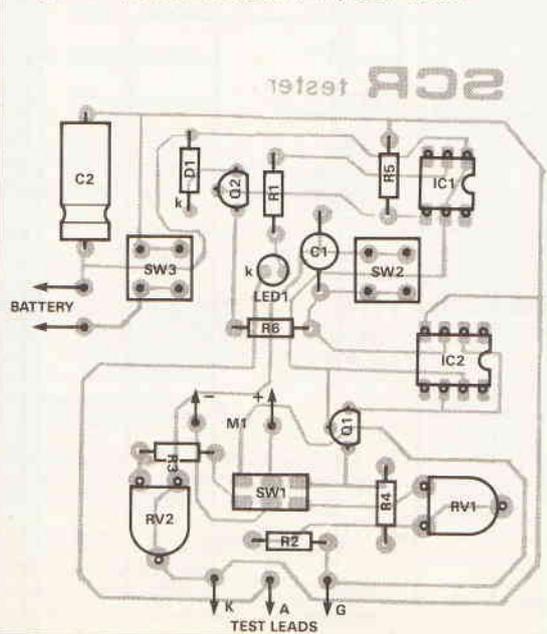

that the meter deflects beyond the end of the scale. The LED should not light. Now connect the anode and the cathode test leads together and again press the test button, checking that the LED illuminates this time. If it does not, check that it is connected with the correct polarity. Next switch to milliamps and with the cathode and gate leads shorted together, press the test button. The meter should once again show deflection greater than full scale, but the LED will not illuminate at all this time.

If all the above tests can be performed satisfactorily by the thyristor tester, the unit may now be calibrated and used to test a thyristor.

Select a thyristor which requires a gate current of 10mA or more using Table 1 or other data as available and connect it correctly to the test leads, referring to Figure 7 if necessary for layout details. Connect a multimeter, set to a low DC voltage range, across the cathode and gate connections (negative to cathode, positive to gate.) and press the test button, with the gate switch set to volts. Adjust preset RV2 such that ME1 reads the same voltage as the multimeter.

Disconnect the multimeter and insert it between

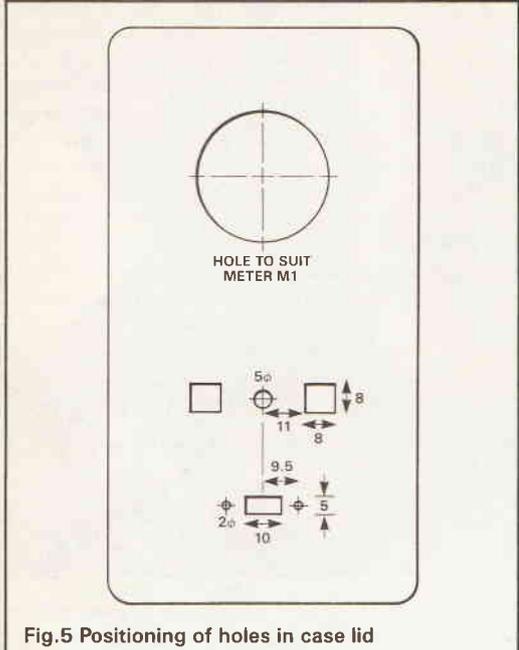


Fig.5 Positioning of holes in case lid

connected to the underside. The op-amp IC2 should be handled with great care while inserting it into its socket: since its CMOS inputs are unprotected and very susceptible to damage from static electricity. All its pins should be kept shorted together until it is inserted into its socket.

The holes should be made in the case lid as in Figure 5 for the three switches and LED. A hole must also be made to suit any meter used for ME1. This is not shown in the figure as it will vary much depend on the meter used. Two holes should be drilled and countersunk to accept M3 x 20mm screws such that the meter will cover the screw heads when fitted. Spaces may then be fitted to these screws to support the top end of the PCB. When it is finally installed the bottom end is held in position by SW1 mounting screws. The test leads are passed through suitable holes in the base of the case before the test clips are fitted. The battery should be fixed securely in place by some means, such that it cannot move around and cause damage to the PCB or wiring. Figure 6 shows a suitable case layout and front panel for the thyristor tester.

Setting Up And Testing

Connect a PP3 battery to the battery clip and set the meter switch to volts. Press the test button and check

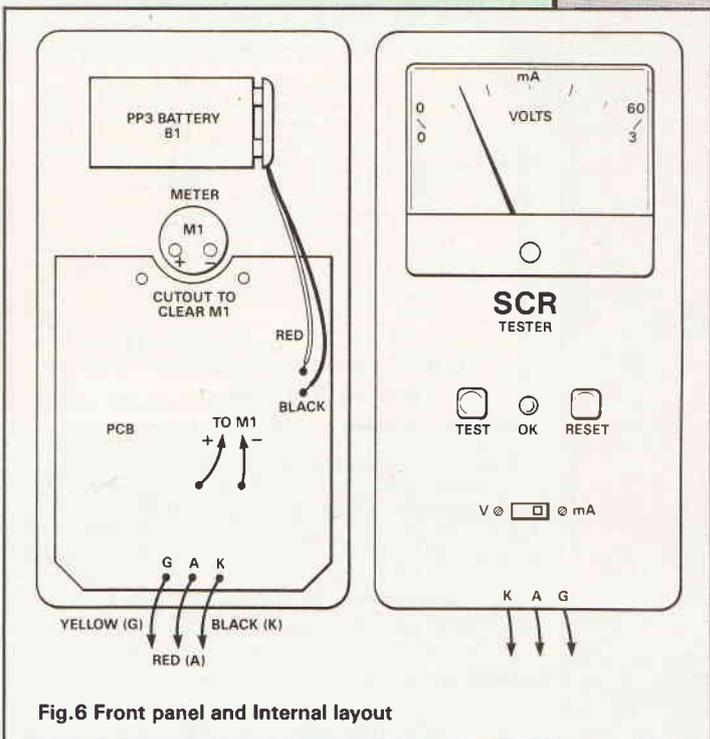


Fig.6 Front panel and Internal layout

the gate lead and the thyristor gate to measure the gate current. Switch the gate switch to 'mA' and the multimeter to a suitable milliamp range for the thyristor under test. Press the reset button before testing. Preset RV1 should be adjusted to obtain a reading on the milliamp scale of ME1 which matches the current measured by the multimeter. The gate current measured will not necessarily be as high as that shown in Figure 1, since this figure is the minimum current guaranteed by the manufacturer to trigger all devices of that type number and most will trigger at much lower currents.

New scales may be applied to the meter, if required, by removing the front glass and using rub down lettering to mark the new numbers on. Typists correction fluid may be used if necessary to cover the original markings.

In Use

The unit should now be fully functional and tested. Its primary design function is testing thyristors, which



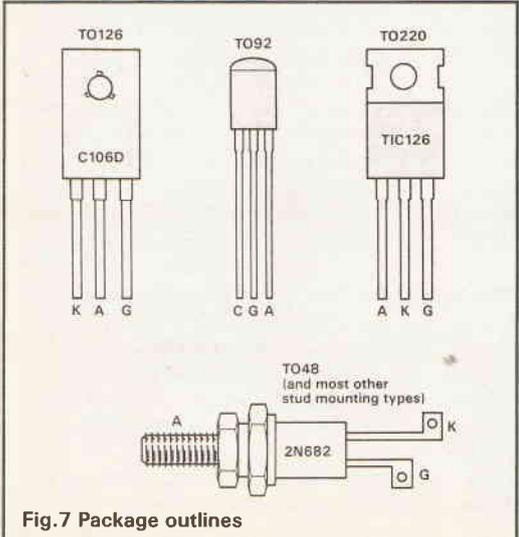


Fig.7 Package outlines

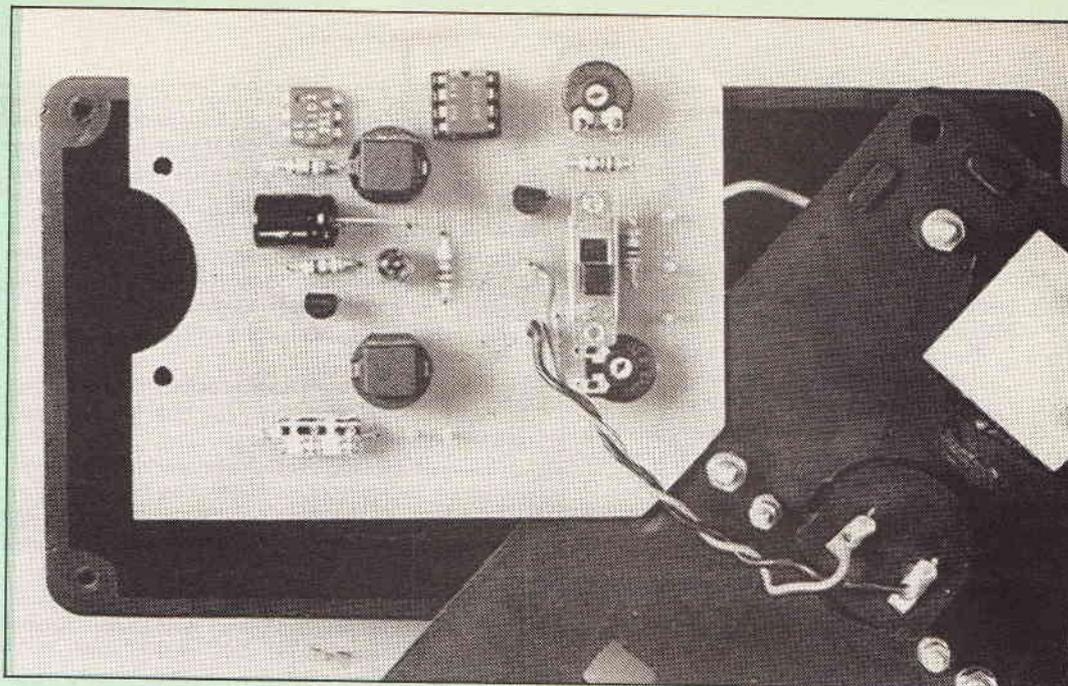

may be tested as follows.

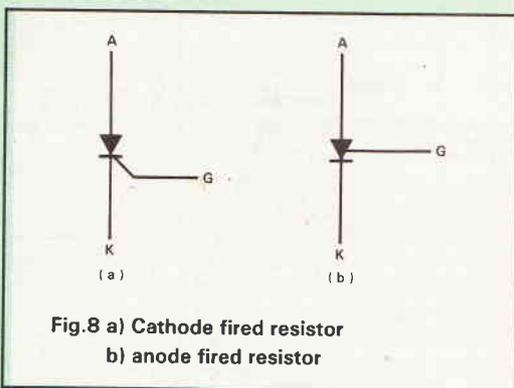Connect the three test leads correctly to the thyristor which has to be tested and press the reset



button to discharge the ramp capacitor C1. Press the test button and check that the LED lights. If it does not make sure that the thyristor is correctly connected (thyristors requiring a large gate current may require a moment for C1 to charge before the LED lights). Set the gate switch to volts and read the gate voltage off the meter volt scale whilst holding the test button depressed. The gate current may be checked in a similar manner with the gate switch set to milliamps. In this case with a very sensitive thyristor with a gate current of less than about 0.5 mA the meter may not register.

SPECIFICATIONS	
Max gate voltage	3V
Max gate current	60mA
Max anode current under test	20mA

DEVICE CODE	V _{GATE} (V)	I _{GATE} (mA)	V _{MAX} (V)	I _{MAX} (A)	I _n (mA)
2N5062	1.2	0.35	100	0.8	5.0
C106D	1.0	0.5	400	2.5	1.7
T1C116D	1.5	20.0	400	8.0	---
T1C126D	1.5	20.0	400	12.0	40.0
2N682	0.75	2.0	75	25.0	15.0
C35D	3.0	40.0	400	35.0	40.0
S8613D	1.5	35.0	400	75.0	---
T70012 3503	1.1	50.0	1200	350.0	250.0

A final test may be made on the latching action of a thyristor by depressing the reset button while holding down the test button. This immediately disconnects the gate of the device, which should remain conducting. Some large devices may appear to fail this test since the anode current provided by the thyristor tester will not be sufficient to latch them even though they may be perfectly sound. See column in table 1. It should be noted that this unit will only test the more common 'cathode fired' thyristors and it is therefore not useable with the rarer 'anode fired' types, usual denoted by the symbol shown in Figure 8b.

Triacs may be part tested with the thyristor tester by connecting the two main terminals to the cathode and anode leads of the tester, and the gate leads to the devices gate. The device will only give a result with its main terminal connected one way around and not the other, so cannot be fully tested.

PARTS LIST

RESISTORS (all 1/4W 5%)

R1	220
R2	68
R3	2k2
R4	1R8
R5	10k
R6	22k
RV1	100R sub-min horizontal preset
RV2	1k sub-min horizontal preset

CAPACITORS

C1	10μ 35V axial electrolytic
C2	47μ 16V axial electrolytic

SEMICONDUCTORS

Q1	BC182L
Q2	BC212
IC1	H11D2
D1	5mm Red led
D2	1N4148

MISCELLANEOUS

S1 D.P.D.T sub-min slide switch.
 S2,S3 P.C.B mounting push to make switches.
 ME1 1mA moving coil meter.
 Plastic box, approx 154 x 84 x 47 or to suit.
 PP3 battery.
 Battery clip for PP3.
 Connecting wire.
 3 minute croc clips.

RTVC HAVE DONE IT AGAIN!

We have secured all stocks of nearly new factory refurbished units with manufacturer approval, at unrepeatable prices. We also offer a 6 month guarantee with all units (this only applies to products marked * on this page.)



Alba digital auto reverse push button AM/FM / LW car stereo with separate bass/treble control APPSS on tape. 25 watts per channel output, with line output for car components use.

★£79.40 + £2.30 pp



Sparkomatic Phoenix Digital auto reverse AM/FM/LW car stereo, with tape volume and balance control. 9 watts output per channel

★£52.40 + £2.80 pp



Sparkomatic Auto reverse AM/FM car stereo with tone, volume and balance control

★£44.20 + £2.80 pp

IN-CAR STEREO BOOSTERS

In-Car Stereo Hi-power booster amplifiers. 400W output. 200W x 2 inputs for low power car stereos and phono inputs short circuit protection

★£110.95 + £2 pp



150W output 75 x 2 inputs as above
★£46.00 + £2.00 pp

IN CAR WOOFERS

6½" 40W Nominal, 60W Max, 4 ohm Goodmans woofer. ★£9.95 + £1.90 pp
8" 60W Nom. 90W Max, 4-5 ohm Richard Allen woofer ★£33.80 + £3.50 pp
10" 100W Nom. 150W Max 4-5 ohm Richard Allen woofer ★£41.50 + £3.50 pp
10" 150W nom, 300W max 4-5 ohm Eminence sub woofer ★£43.50 + £3.50 pp
12" 100W Nom. 250W Max, 4-5 ohm Richard Allen woofer ★£43.50 + £4 pp
12" 150W nom 300W max 4-5 ohm Eminence sub woofer ★£45.00 + £4 pp
15" 200W Nom. 400W Max, 4-5 ohm Richard Allen woofer ★£60.00 + £5 pp

TWEETERS AND MID RANGE FOR IN-CAR USE

4½" 100W 4-5 ohm sealed back mid-range. Goodman ★£5.50 + £1.50 pp
2½" 65W 4-5 ohm Ferro fluid cooled dome tweeter with housing. Audax ★£5.00 + £1.20 pp
3½" 100W 8 ohm Ferro fluid cooled dome tweeter for 4-8 ohm use ★£6.90 + £0.80 pp

FILOFAX

PERSONAL ORGANISER
RADIO/CALCULATOR

Solar Powered Calculator

Eight Digit Display
Imperial, Metric Conversion Tables



Battery Powered AM Radio
High/Low Volume Control

Earphone provided

Listed price £19.95 OUR PRICE £8.95 plus 75p p&p

Genuine FILOFAX. complete

with 91 calendar, A to Z index and address section. ★£5.95 plus 75p p&p

ACOUSTIC REAR PARCEL SHELF

To get the best sound from your car woofers, replace your rear hatchback parcel shelf with one of these 14mm thick fibreboard units, tailor made for your car, supplied with grille cloth and fixings. When ordering please state make, model, and year of Reg. ★£39.80 + £6 pp

AUSTIN ROVER SHELF SPEAKERS

15 watt speaker. Moulded in black plastic housing for vertical or horizontal use, contains 4½" Goodmans drive unit with a good size magnet

SALE OFFER £4.95 pair + £2 pp

HIFI WOOFERS

10" round 100 watt Goodmans Hifi woofer 2" coil, paper cone, foam rubber surround 4½" magnet, frame size 10½" imp 8Ω ★£17.50 + £2.80 pp
8" round 100 watt Audax Hifi woofer, 1" coil with fitted phaseplug, Hiteck TPX polimar core with rubber surround 4½" magnet, die cast chassis, size 9½" 8Ω imp ★£34.90 + £4 pp
8" square 80 watt Audax Hifi woofer, 1½" coil, polypropylene cone, rubber surround, 3¼" magnet, chassis size 8½" square 8Ω imp ★£19.70 + £2.50 pp
8" round 70 watt Peerless Hifi woofer 1" coil, treated paper cone, foam rubber surround, 3¼" magnet, 8Ω imp ★£12.50 + £2.50 pp
5½" 45 watt Audax Hifi woofer 1" coil, Bextrene treated cone, rubber surround, 4" magnet, 8Ω imp ★£9.80 + £3 pp
5½" 35 watt Goodmans Hifi woofer, 1" coil, treated paper cone, rubber surround, 3½" magnet, 8Ω imp ★£7.20 + £2.50 pp
4½" square 35 watt Audax Hifi woofer, 1in coil, paper cone, rolled surround, 2½" magnet, 8Ωimp ★£7.50 + £2.50 pp

HIFI TWEETER AND MID RANGE

4½" square 100 watt Goodmans sealed back mid range, 1" coil, treated paper cone, 2½" magnet, 8Ω imp ★£5.50 + £2.50 pp
4" square 75 watt Audax sealed back mid range ¾" coil treated paper cone, Ferrofluid cooled coil, chassis size 3½" 8Ω imp ★£7.95 + £1 pp
4" round 130 watt Peerless 1" metal dome Hifi tweeter, 1" coil, 2½" magnet, rec crossover freq 3KHz ★£15.90 + £1.60 pp
4½" x 2¼" 75 watt ¾" direct drive dome tweeter, Ferrofluid cooled ¾" voice coil rec crossover, freq 4.5KHz as above but with 3½" face plate ★£6.90 + £1.30 pp

MOTOROLA PIZO CERAMIC TWEETERS

Convert electrical energy into sound without the use of voice coils and magnet assemblies. No moving mass hence excellent transient response and low distortion with high efficiency levels as they cannot reproduce bass sounds. No crossovers are required

SALE OFFER £3.95 + 75 pp

3½" square, 50 watt Pizo super horn tweeter ★£5.75 + 75 pp
2" x 6" wide dispersion 400 watt Pizo horn tweeter ★£11.95 + £1 pp

MULTIBAND RADIO

VHF 54-176MHz + AM CB BANDS 1-80
Listen to: AIR TRAFFIC CONTROL, AIRCRAFT, RADAR, PUBLIC UTILITIES, RADIO AMATEURS AND MANY MANY MORE
★£17.95 POSTAGE £2.85
SQUELCH CONTROL "RUBBER DUCK AERIAL"

ROSS PUSH BUTTON RADIO

Mains and battery operated. High quality VHF/FM, Medium and Long Wave reception, 6 push button selected preset stations. Fully retractable telescopic aerial. Headphone/earphone jack socket. Size 230H x 150W x 65D Ref. RE-5500 Brand new. Listed price over £30.00
★£13.50 + £2.80 pp



4.5" ROSS MONO TV WITH AM/FM RADIO

4.5" Ross mono Television with AM/FM Radio for battery or mains use, supplied with mains adaptor/charger, 12v car plug with lead, earphone, stand and extension aerial socket, battery component holds 8 x UM2 batt, Alkaline or NiCads (batts not included). Control volume, tone and tuning for radio and television.
★£49.95 + £4.10 pp



RADIO AND TV COMPONENTS ACTON LTD

21 HIGH STREET, ACTON, LONDON W3 6NG
MAIL ORDER TERMS. POSTAL ORDERS and/or CHEQUES with orders. Net monthly accounts to Schools, Colleges and P.L.C. only. ACCESS-VISA. Phone orders between 9.30-7.30pm please. Overseas readers write for quote on delivery. Phone 071 723 8432 or 081 992 8430. Callers 323 Edgware Road, London W2. Closed Sun 21 High St. Acton London W3 closed Sun Mon, Tues & Wed

SPECIAL OFFER

DTMF TONE DIALLER

Suitable for remote control of telephone answering machines, videos, appliances etc. requiring DTMF signals over telephone lines.
★£8.95
Please add 75p p&p when ordering



VIDEO SENDER

With this handy unit you can transmit the output of your home video, video camera or satellite equipment over-the-air to a receiving television within a range of 100ft. Simply connect the video and audio output of your equipment into this unit and a 10-13.8V dc power supply extra
★£3.75 size 122 x 70 x 21mm

SALE OFFER £11.50 + 1 55 pp

VHF RADIO TRANSMITTERS

100mW mini bug. Built on a neat little fibre glass pcb with condenser mic. Fully tuneable over the FM band. 9V DC ★£5.75 + £0.90 pp
2 Watt transmitter kit, supplied with fibre glass pcb, all components, diagrams, ready for you to build. 12-24V DC. ★£7.50 + £0.70 pp
25 Watt Transmitter kit. Fully tuneable over the FM band. Kit comprises double sided pcb diagrams and all components, including heat sink. Supply voltage 12-18V DC. ★£67 + £1 pp
Transmitters listed on this page are not licensable in the UK.

30 + 30 WATT AMPLIFIER KIT



An easy to build amplifier with a good specification. All the components are mounted on the single PCB which is already punched and back-printed.

- 30W x 2 (DIN 4 ohm)
 - CD/Aux, tape I, tape II, tuner and phono inputs.
 - Separate treble and bass.
 - Headphone jack.
- Size (H.W.D.) 74 x 400 x 195mm.
Kit enclosed: case, PCB, all components, scale and knobs ★£36.80 + £3.50 pp
(Featured project in *Everyday Electronics*, April 1989 issue). Reprint Free with kit.

QUICK START BELT-DRIVE VARI SPEED DISC TURNTABLE

- ★ Quick start, ideal for scratching
 - ★ Pitch control
 - ★ Target lamp
 - ★ Counter weighted tubular tone arm with plug-in head shell
 - ★ 2-speed full manual control
 - ★ Remote start stop
 - ★ 7.5Kg
- ★£112.90 + £7 pp



AMPHONIC 125 + 125 POWER AMPLIFIER



125 watt per channel stereo power amplifier with independent volume controls, professional 19" rack mount and silent running cooling fan for extra reliability.
Output power.....125W RMS max, per channel
Output impedance.....4 to 16 ohms (max power into 4 ohms)
Sensitivity.....450V at 22K ohms
Protection.....Electronic short-circuit and fuses
Power.....220-240V a.c. 50Hz
Chassis dim.....435 x 125 x 280mm
★£142 + £7.00 pp

GEMINI 2200 DISCO MIXER



This versatile little mixer has a high reputation with DJ's. Its simplicity and quality sound reproduction makes it ideal for bedroom or high power gigs.
Features: Fader control • 2 phono inputs • 1 monitor headphone circuit with high power output • Talk switch • VU meters.
Specification: 5n ratio mic less than 1mv (745dB).
Phono: 0.4mV less than (755dB) • Talkover -12dB • Power AC220-240 at 3 watts • Size 10½" x 8½" x 2½" • Weight 4½ lbs
★£79.95 + £5 pp

EPROM EMULATORS

April 8 — 8 Bit Emulator £65 (inc p&p)
 April 16 — 8/16 Bit Emulator £105 (inc p&p)
 Emulates 2764, 27128, 27256 EPROM's
 via intelligent PC link.

Price includes: PC software, cables and manual.

Please write or call for more information to:
BUSINESS INTEGRATED TEST SYSTEMS
 UNIT 1, HOLMSIDE, HARROW ROAD EAST
 DORKING, SURREY RH4 2AU, ENGLAND
 TELEPHONE: 0306 883309

VELLEMAN KITS

Over 100 Project Kits in stock
 Send 50p for 1991 Catalogue + Price List

RETAILERS WANTED

Why not be one of our many retailers who carry our top
 range of high quality kits (Discounts to be arranged)
 Send Details and Letterhead to:

HIGH-Q-ELECTRONICS
 DEPT ETI, PO BOX 1481 LONDON NW7 4RF

TEL: **0707 263562**

FAX: **081-209 1231**

SCHOOLS AND COLLEGES WELCOME

19" RACK MOUNTING EQUIPMENT CASES

This range of 19" rack cases features satin black finished 16SWG (1.5mm) steel front panels (no fixing holes visible), with the rear box assembly constructed from 20SWG (0.9mm) steel. The standard units are 10" (254mm) deep.

NEW FOR 1990 19" project cases only 4" (101mm) deep and are available in the following popular sizes:

PROJECT CASES		
Type	Height	Price
PU1	1 3/4" (44mm)	£16.50
PU2	3 1/2" (88mm)	£18.50
PU3	5 1/4" (133mm)	£20.50
PU4	7" (178mm)	£22.50
PU6	10 1/2" (266mm)	£26.50
EQUIPMENT CASES		
U1	1 3/4" (44mm)	£20.70
U2	3 1/2" (88mm)	£24.15
U3	5 1/4" (133mm)	£27.60
U4	7" (178mm)	£29.90

Delivery included (UK only).

All prices include VAT.

BLANKING PANELS, RACKING CONSOLES
 and RACK CABINETS are also available.

Please send SAE for details.

Tel: 0275 823983 for Access/Visa Sales or cheque
 with order to:

RACKZ PRODUCTS


PO Box 1402 Mangotsfield, Bristol, England, BS17 3RY



ARGUS BOOKS PUBLISHING FOR THE SPECIALIST

THE FULL RANGE OF ARGUS BOOKS

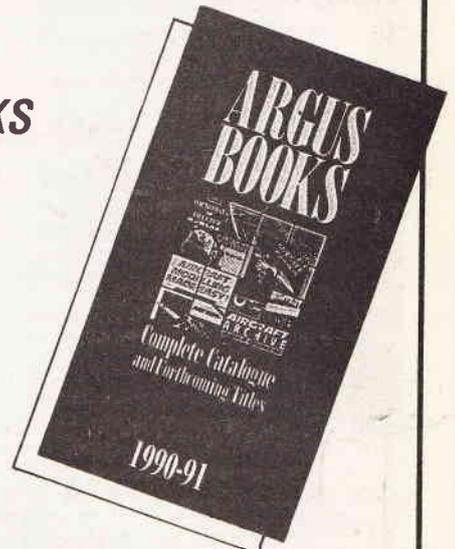is available from
 all good book
 and hobby
 shops or con-
 tact Argus
 Books direct
 for a 1991
 catalogue.



CATALOGUE OFFER, Argus Books,
 Argus House, Boundary Way,
 Hemel Hempstead, Herts.
OR PHONE 0442 66551 EXT. 204

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX · 031 667 2611

New
 catalogue
 available
 NOW

**A COMPREHENSIVE RANGE WITH
 SERVICE SECOND TO NONE**
 OUR MUCH EXPANDED, BETTER ILLUSTRATED
 CATALOGUE WILL COST £1.50 — TO INCLUDE
 VOUCHERS TO USE AGAINST FUTURE
 PURCHASES. TO RECEIVE A COPY, PLEASE
 SEND YOUR REMITTANCE WITH YOUR NAME,
 ADDRESS AND TELEPHONE NUMBER
 REQUESTING A COPY OF THE 1990/91 OMNI
 CATALOGUE.



Open: Monday-Friday 9.00-6.00
 Saturday 9.00-5.00



Millions of quality components
 at lowest ever prices.
 Plus Tools, Watches, Fancy Goods, Toys.
 Mail order only. UK only.

All inclusive prices **NO** post, or
 VAT etc to add on.

Write or phone for catalogue/clearance list at least
 200 offers to amaze you.

Brian J Reed Electrical
 6 Queensmead Avenue, East Ewell
 Epsom, Surrey KT17 3EQ
 Tel: 081-393 9055



SUPPLIERS OF AN EXTENSIVE
 RANGE OF TOP QUALITY
 ELECTRONIC COMPONENTS,
 ACCESSORIES & HARDWARE

BOOKS — PCB PRODUCTION AIDS — TEST EQUIPMENT
 TOOLS — SELF ASSEMBLE ELECTRONIC PROJECTS

ESR Electronic Components
 Station Rd, Cullercoats,
 Tyne & Wear. NE30 4PQ

Tel: 091 251 4363

Fax: 091 252 2296

Schools Colleges and Trade Equities Welcome



OPEN: Mon-Fri 8:30-5:00 Sat 10:00-5:00



NEW 1991
 COLOUR
 CATALOGUE


£1.00

Includes P + P

The Earth needs all the friends it can get. And it needs them now.

For thousands upon thousands of years our planet has sustained a rich diversity of life. Now, one single species - humankind - is putting the Earth at risk.

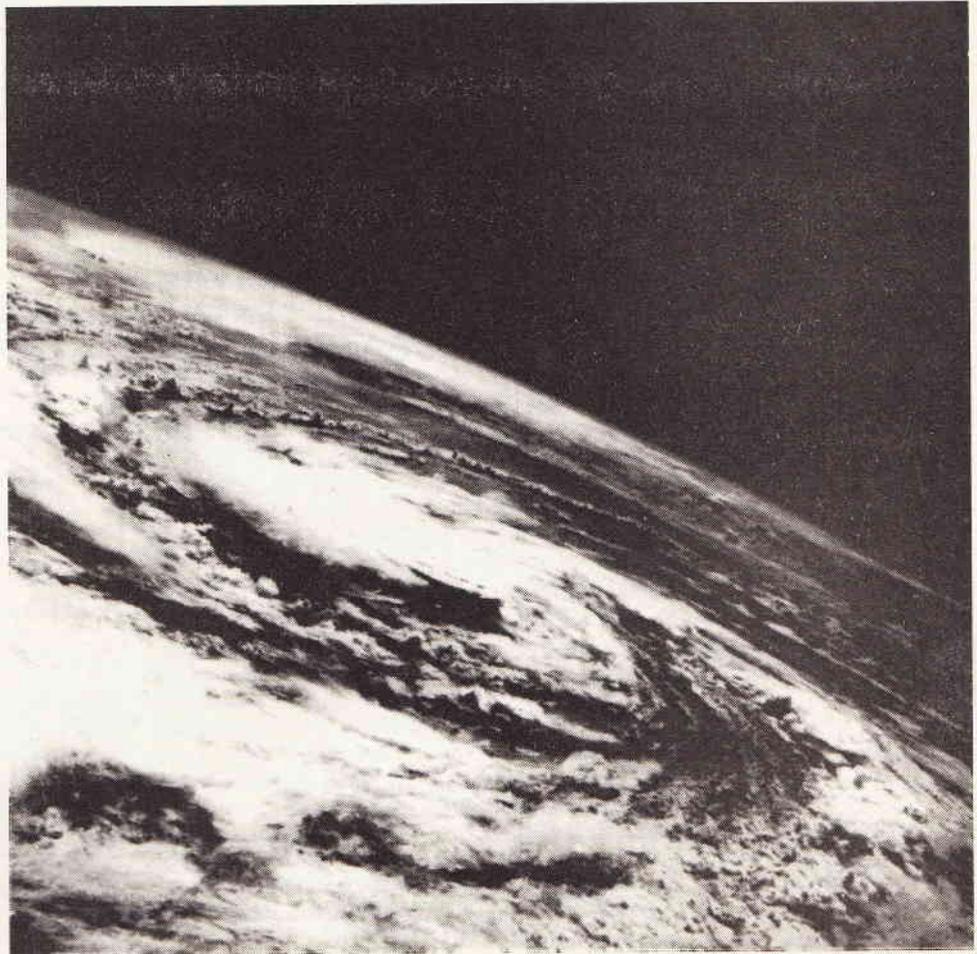People the world over are suffering the effects of pollution, deforestation and radiation. Species are disappearing at a terrifying rate. The warming of the atmosphere threatens us all with devastating changes in climate and food production.



But it needn't be like this - we know enough to reverse the damage, and to manage the Earth's wealth more fairly and sustainably. But the political will to bring about such a transformation is still lacking.

And that's exactly where Friends of the Earth comes in.

IT'S TIME YOU JOINED US

I'd like to join Friends of the Earth. Please send me your quarterly magazine. I enclose:

£12 individual £250 life

I'd like to donate £50 £35 £15 Other £

I enclose a cheque/PO for total of £

payable to **Friends of the Earth** or debit my Access/Visa No:

Card Expiry date:

Signature Date

FULL NAME

ADDRESS

POSTCODE



Send to: Friends of the Earth Membership Department, FREEPOST,
56-58 Alma Street, Luton, Beds LU1 2YZ.

081 200 0200 to join/donate anytime

Friends of the Earth F81 KAFR

High Definition Television

MITVV-RC

James Archer continues his look at the American alternatives for better TV pictures.

This is a more conventional ATV system, which operates in a single 6MHz channel, and which provides improved picture quality for viewers with ATV receivers, whilst enabling viewers with NTSC receivers to obtain relatively normal quality pictures, except for the appearance of a black bar at the top and bottom of the picture when displaying picture signals transmitted from an ATV source.

No video information is carried on the top and bottom 12.5% of the picture, which means that the remaining 75% of the normal 480 active lines are displayed in the form of a picture with a 16:9 aspect ratio. The extended vertical blanking interval, seen as black bars that appear above and below the picture on a standard NTSC receiver, is used to carry luminance enhancement information which can be used to improve the quality of the picture available to the viewer with an ATV receiver. The transmitted luminance resolution is 3MHz over the NTSC area of the picture and 4.2MHz over the enhancement area. Extra chrominance resolution on static portions of the picture is obtained by reducing the chrominance frame rate to half of the normal, (15 fps), at the expense of some reduction in resolution during moving parts of the picture. The transmitted chrominance bandwidth is 0.6MHz, whereas the displayed bandwidth on an ATV receiver is 1.2MHz.

The system described is one of the simplest methods of providing ATV in a compatible manner. On transmission the signal behaves just like NTSC, and it is compatible with all NTSC receivers and video recorders, and can be recorded and played back as usual.

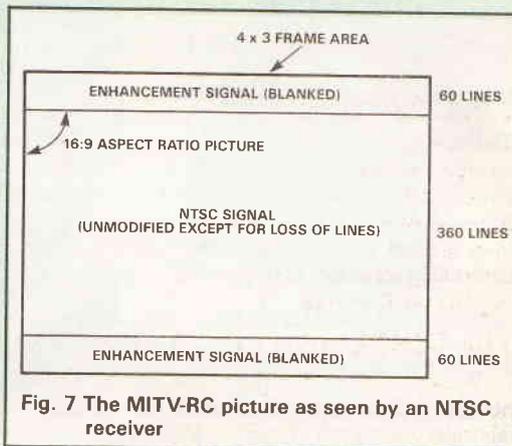


Fig. 7 The MITV-RC picture as seen by an NTSC receiver

The MITV-CC system is in essence simple, in that it makes use of the space freed by reducing the picture height, which provides a great deal of capacity for future improvements.

The MITV-CC system was designed on the assumption that viewers would eventually use 'smart' television receivers, sometimes called 'open architecture' receivers, which allow for a great deal of flexibility and programmability; in essence they can be adapted by using different software to cope with a wide range of ATV systems, and any evolutionary changes which may come about.

One scenario for the introduction of the MITV systems that is being considered is for the receiver-compatible MITV-RC to be introduced first; this would allow viewers with NTSC receivers to continue to use their existing receivers, but manufacturers hope

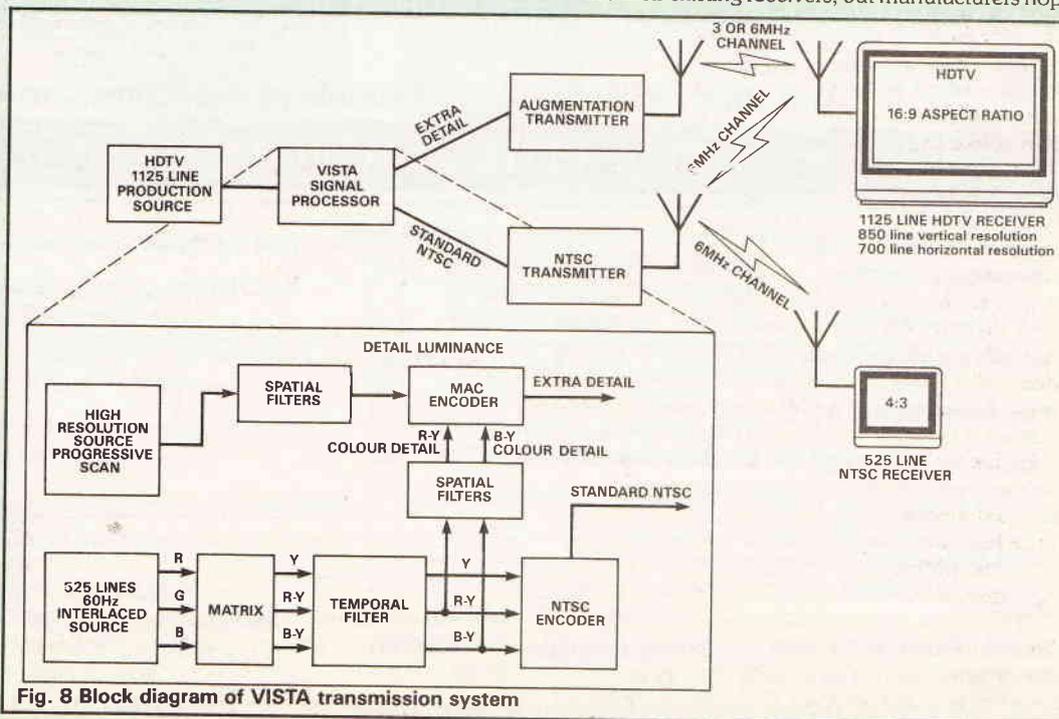


Fig. 8 Block diagram of VISTA transmission system

HDTV

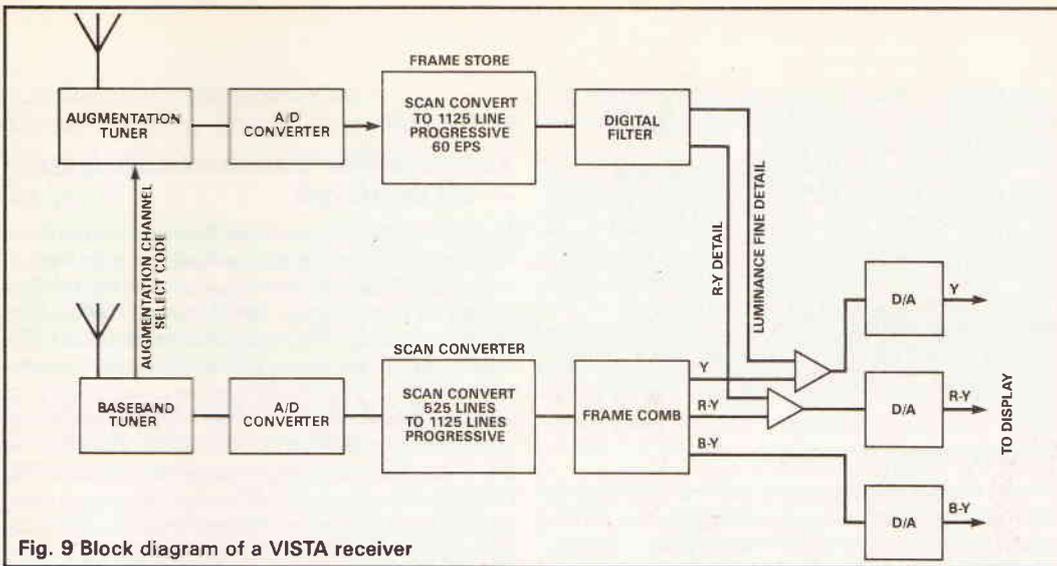


Fig. 9 Block diagram of a VISTA receiver

that many people would then be persuaded to buy an open architecture receiver to provide the wide-screen EDTV quality pictures that MITV-RC makes possible. At a later stage these same receivers could then be used, perhaps with some modification to the controlling software, to display HDTV pictures from the MITV-CC signals.

The VISTA system

Dr William Glen of The New York Institute of Technology NYIT has proposed and demonstrated in the laboratory a system known as VISTA, an acronym obtained from Visual System, Transmission Algorithm. VISTA is a two-channel system, where the first channel carries an NTSC signal and the second channel an augmentation signal. Some of the techniques used are common to other schemes that we have discussed, and it is understood that other systems actually make use of NYIT patents.

VISTA separates the information in the source pictures into components, one set having low spatial resolution and high temporal resolution, corresponding to a standard NTSC signal, and the other having components with high spatial resolution and low temporal resolution, these forming the augmentation signal.

The input signal of the VISTA system is from an 1125 line 16:9 aspect ratio progressively scanned source, chosen because there is already an 1125/525 convertor available from Japan, and the basic NTSC signal for the VISTA system is therefore obtained from the 1125/525 conversion equipment, but very much improved by the application of temporal filtering at the source and corresponding comb filters in the receiver; cross-colour and cross-luminance are much reduced. The information to be transmitted over the augmentation channel consists of the high frequency luminance detail from the source picture and the colour detail, in the form of the higher frequency R-Y information, but this information is sent less frequently i.e. at lower frame rates than the basic picture information. As both 3MHz and 6MHz wide augmentation channels are allowed by the FCC rules, alternative specifications have been provided for the two different cases. Assuming that a 6MHz wide augmentation channel is available, the channel carries information at 15 frames per second, with a maximum video bandwidth of 5.3MHz, and this is carried on a single-sideband suppressed carrier system. Tests have been carried out to confirm that this information can fit into a standard 6MHz wide NTSC channel without causing undue interference, and it has been found that the VISTA augmentation signal produces less adjacent channel interference than NTSC, and can tolerate more interference. If only a 3MHz channel were to be available, perhaps because of problems with 'taboo'

channels, then their augmentation information would be sent at the reduced rate of 7.5 frames per second, with a maximum video bandwidth of 2.7MHz, and code 19 signals in the vertical blanking interval would indicate to the receiver which type of augmentation signal was being used.

Since suppressed carrier modulation is used for the augmentation channel there is no main carrier, no colour subcarrier, and no sound carrier, and its power can be much less than that of the main signal carrier.

When receiving a main signal and an augment-

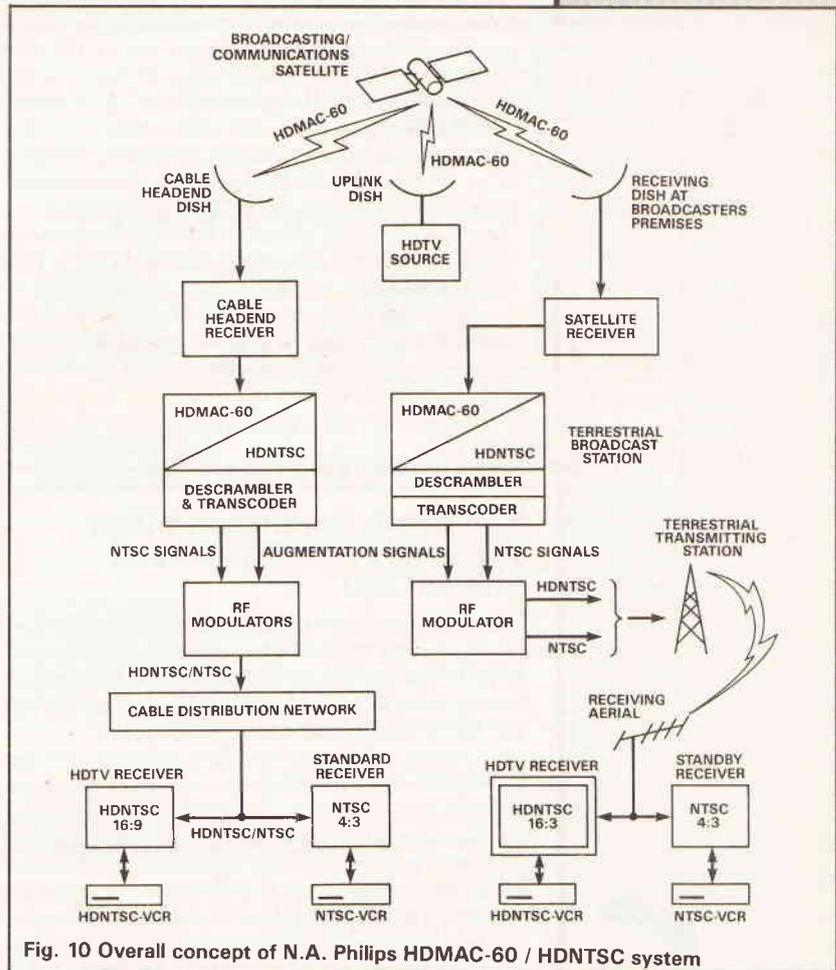


Fig. 10 Overall concept of N.A. Philips HDMAC-60 / HDNTSC system

ation signal care has to be taken to see that the two signals are received at the same time, or else path length variations due to reflections, perhaps from moving aircraft, could cause problems. The augmentation signal therefore has a 3.58MHz burst at the end of each line to phase lock the augmentation signal so that it can be accurately loaded into the frame store

in the receiver. One line of the vertical blanking interval is also used to carry low level digital code signals which identify the individual frames.

Whenever a two channel system is used, some method must be found of telling the receiver where the augmentation information is to be found. To ensure that the receiver always tunes to the correct augmentation channel a digital code is inserted in the vertical blanking period of the NTSC part of the transmission, and this code is used to automatically tune the second tuner in the receiver to the augmentation channel. Figure 9 shows a block diagram of a VISTA receiver.

Wider aspect ratio

In order to obtain pictures with a 16:9 aspect ratio, only 443 of the 448 active lines available in the NTSC system are used in the HDTV receiver; the horizontal blanking interval of the NTSC signal is also reduced by 4µs to help to increase the aspect ratio further. In the receiver the 443 active lines are scan converted to produce 1024 active lines (1125 lines total) for display. The NTSC viewer would see the full 4:3 image, whereas the VISTA viewer would see a vertically cropped image.

The VISTA system can provide an evolutionary path to HDTV which provides existing viewers with NTSC receivers with excellent pictures. VISTA signals are suitable for distribution over cable systems, and could be carried over satellites if two channels were made available.

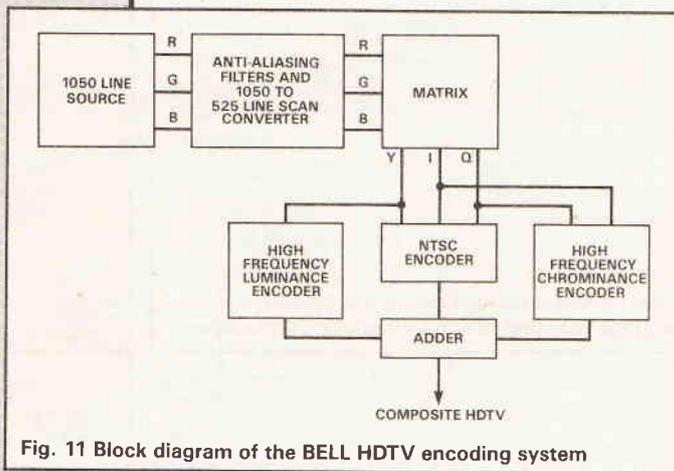


Fig. 11 Block diagram of the BELL HDTV encoding system

The North American Philips proposals – HDNTSC and HDMAC-60

The North American Philips company (NAP) has taken a comprehensive approach to the introduction of HDTV to the United States, and has put forward what is called a 'hierarchical ATV emission system with full NTSC compatibility and HDTV quality'.

This is effectively a system concept offering several options, but essentially containing two related formats for ATV systems, one particularly suited to satellite transmission, the other intended for terrestrial and cable transmission. The signal to be used for satellite transmissions is a widescreen multiplexed analogue components (MAC) signal, whereas the terrestrial version, which can simply be derived from the satellite version, is a two channel system. One of the two channels carries a standard NTSC picture whilst the second channel carries augmentation information which includes side panel information for wide aspect ratio operation, higher resolution detail information about the pictures, and digital audio. One idea put forward by NAP is that the MAC signal could be distributed via satellite, and that these signals could be con-

verted to the terrestrial signal format for distribution by cable or for onward transmission by broadcasters.

The satellite transmission system – HDMAC-60

The basic pictures required by the NAP system are in 525 line, 59.94 frame rate, progressive scan format, with a 16:9 aspect ratio and an active line time of 26µs but, as we have seen previously, these could be derived from an 1125/59.94 studio source if desired. The choice of a 59.94 frame rate simplifies later conversion to NTSC. HDMAC-60 has been carefully designed to provide a balance between spatial and temporal components of the picture signals that matches the characteristics of the human visual system. The HDMAC-60 system uses different compression ratios on different lines, so that different lines are effectively transmitted with different bandwidths. This technique allows high spatial and temporal resolutions to be achieved in vertical and horizontal directions, with low temporal resolution in diagonal directions, a situation that the human visual system is quite content with. Alternate lines are sent as line 22 difference signals at a lower resolution, using a 2:1 time compression ratio; these transmit the vertical/temporal high frequency detail of the luminance component of the signal. One out of every two of the remaining lines, i.e. one line of every four of the picture, is expanded in time by a factor of 16/9 so that it can carry a full resolution signal. The other one of the two remaining lines, again one line in four of the picture, is neither compressed nor expanded, and carries information with medium resolution. The B-Y and R-Y colour difference signals are transmitted on alternate lines, with each signal alternating between 2:1 compression and 4:1 compression. The total bandwidth of the baseband signal, which includes four digital audio channels, is 9.5 MHz, and is suitable for direct transmission over satellite channels.

The terrestrial system – HDNTSC

The HDNTSC system has been designed to carry the same information that is carried in the HDMAC-60 system, whilst remaining fully compatible with NTSC. It provides a standard NTSC signal using a 6MHz channel, whilst the augmentation information needed to provide the extra information for HDTV is carried in a separate radio frequency channel. Although the aim of NAP is to squeeze the augmentation signals into a 3MHz wide channel, at the present time at least 4.6MHz is required. HDNTSC is based upon a 525/59.94/16:9 continuously scanned source, identical to that used for HDMAC-60, and the system has been arranged so that transcoding from HDMAC-60 to HDNTSC can be carried out simply and without introducing any undesirable artifacts, so that it would be practicable for terrestrial HDNTSC transmitters to use HDMAC60 signals from satellites as the source of their programmes.

The information in the baseband HDNTSC signal is separated into two signals, the NTSC signal package, a conventional 525/59.94/2:1/4:3 NTSC signal, and the augmentation signal package (ASP). The NTSC signal to be carried on the first channel is obtained by taking a portion appropriate to a 4:3 aspect ratio of every alternate line of the progressively scanned picture. The portion of the original 16:9 aspect ratio picture which is used to provide a 4:3 aspect ratio picture for the NTSC signal is variable, so that the director of the programme can arrange for the picture to be panned and scanned to provide the most appropriate 4:3 picture. The remaining parts of the 5:3 picture will be in the form of side panels, not necessarily of equal size, and the information representing these

is carried in the augmentation channel. The augmentation channel is thus used to carry the higher resolution horizontal and vertical detail of the image.

Options

The North American Philips company stresses that the basic ideas used in their system could be modified in various ways to provide the 'optimum' NTSC compatible HDTV system, and the company has suggested a number of different options, including the possibility of utilising a digital augmentation signal.

The Bell Laboratories Proposal – The SLSC (Split Luminance/Split Chrominance) system

Bell Laboratories have proposed an HDTV system which requires two 6MHz channels to provide an NTSC compatible system. Figure 11 shows how it works.

The source is a high definition 1050 line picture, which is vertically filtered and then scan converted to provide a 525 line signal which has the same horizontal resolution as a normal NTSC picture. The first radio frequency channel carries this picture signal, which provides standard pictures on standard NTSC receivers. The remainder of the original 1050 line HDTV picture, the higher frequency parts of the luminance and the colour difference signals, are separately encoded and transmitted over the second radio frequency channel. This system is sometimes called the Split Luminance/Split chrominance (SLSC) system, since both luminance and chrominance signals are separated into low and high frequency areas. Figure 12 shows the baseband radio frequency spectrum arrangements used in the Bell system, and although it indicates that adjacent channels are used for the two signals there could be benefits in using quite separate channels.

An HDTV receiver would make use of both the NTSC information coming from the first channel and the augmentation information coming from the second channel. Using the same type of techniques we have seen for other systems, frame stores in the HDTV receiver would be able to provide a 1050 line HDTV picture. Bell claim that the horizontal resolution of their HDTV pictures will be twice that of NTSC, and that there is sufficient capacity available in the second radio frequency channel to carry digital sound as well as augmentation information. Wide aspect ratio pictures could be obtained by using one of the methods utilised by other systems, such as carrying side panel information in the augmentation channel by using suppressed carrier amplitude modulation, but no firm proposal had been made at the time of writing.

of completeness than because of a belief that it will be chosen. HDB-MAC is not generally considered to be a contender for the American ATV crown, because of its basic incompatibility with NTSC receivers; only by using a set-top HDB-MAC/NTSC convertor could an NTSC receiver make use of the signals. The basic principles behind the encoding process are shown in Figure 13.

The 525-line picture with 750 samples per line is diagonally filtered, and the resulting signal is then quincunxially sampled, using a similar method to that used by the European HD-MAC system, and this means that we are effectively discarding every

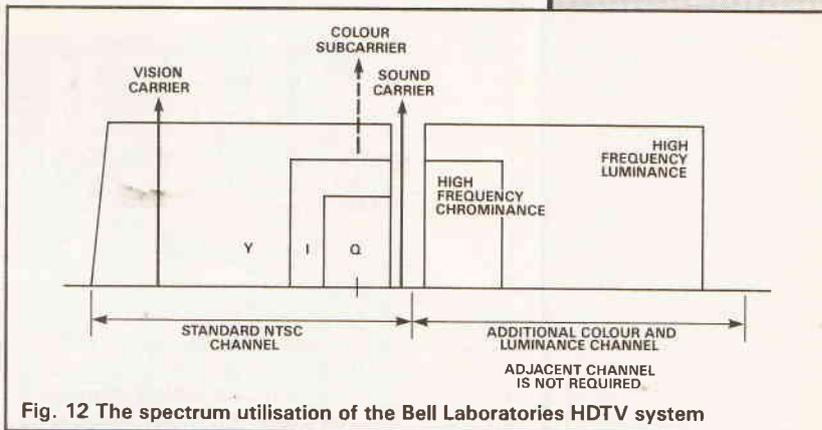


Fig. 12 The spectrum utilisation of the Bell Laboratories HDTV system

alternate sample. The resulting samples from each of the even lines are then moved upwards in the picture to the line above, so that samples from alternate lines are placed side by side, and alternate lines contain no samples at all. The lines without samples are of no use and may therefore be discarded, which effectively produces a 525 line interlaced picture, which can be transmitted via a standard satellite channel.

A standard B-MAC receiver would then display the received signal as a normal 525 line interlaced picture, but an HDB-MAC receiver containing a number of line stores could rebuild a progressive scan picture by looking at the incoming samples and processing them so that missing samples could be inter-

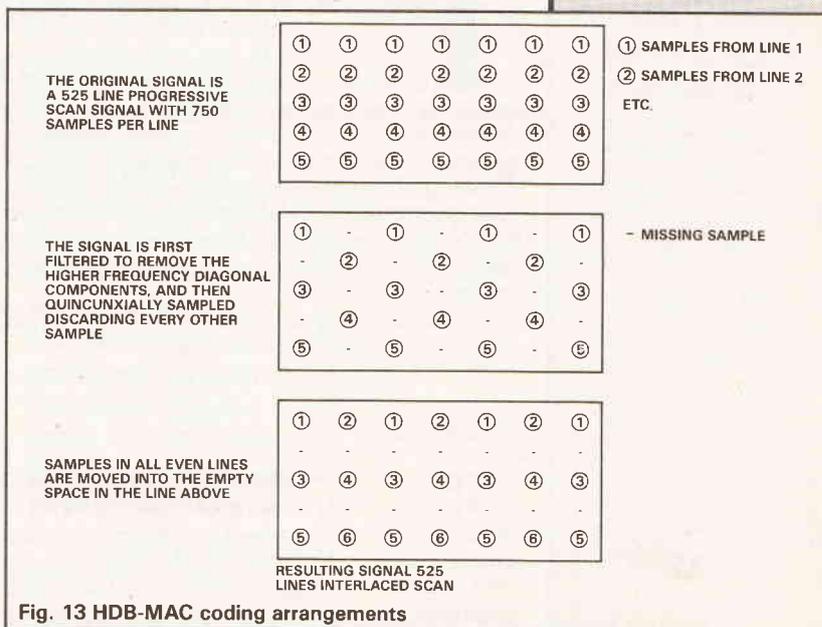


Fig. 13 HDB-MAC coding arrangements

polated from the surrounding samples, and hence the missing lines could be synthesised.

In next month's article we shall look at our fourth batch of ATV proposals, and try to reach some conclusions as to which systems have a realistic chance of coming to fruition, and which are likely to remain pie in the sky.

HDB-MAC – The Scientific Atlanta HDTV proposal

Scientific Atlanta have demonstrated a working wide-screen HDTV system based on their B-MAC transmission system. This allows for the transmission of wide-screen HDTV pictures with up to six high quality audio channels as well as teletext and computer data, and the first major public demonstration in December 1989 showed pictures from a world boxing championship on nine-foot high HDTV projection screens. The source signal can be a 1050 line interlaced-scan HDTV picture or a 525 line progressively scanned picture, but the former must be converted to the latter before the actual signal processing takes place. HDB-MAC is backwards compatible with B-MAC, so that broadcasters using B-MAC could eventually upgrade to HDB-MAC. Although a description of the HDB-MAC system is included in this section about the American approach to HDTV, this is more for the sake

Remote Controlled Timeswitch

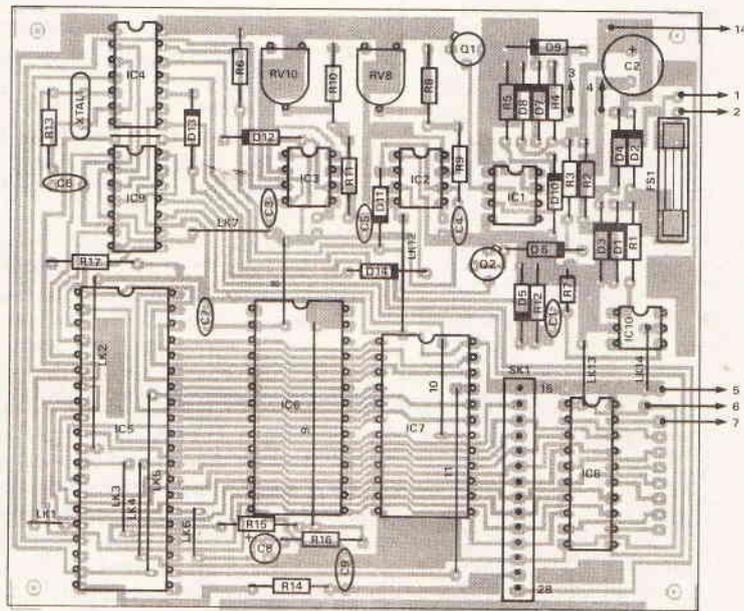


Fig. 13 Update of Main Control Board.

*A Constructors View
by Jon Herd*

Tackling such a large project can be fun if you know what you are doing and the Remote Controlled Timeswitch by Kevin Browne in ETI Dec, Jan, Feb 91 is no exception. Getting a project of this magnitude going is best tackled by testing out the smaller sections with a 'scope as you go. However, a number of problems arose through designer and typographical error and indeed is a problem when a prototype goes through so many hands in getting the information to you the reader. These have been amended and so far things are functioning as they should.

I have set out in table form the adjustments I had to make to the Main Control Unit

Dec 90 Page 29 Fig.4

R12 27k

Fix a 10k preset

Symptom —
Clock too fast
— Cannot
Adjust to zero

This value may not work. I had a lot of trouble trying to adjust to zero. In my circuit with this value the duration of 50Hz pulse was 195µs. This is seen by the CPU as at least 3 times the interrupt pulse and the symptom is the clock runs at 3 times the speed! Eventually, I used a 10k preset in place of R12 and using a 'scope, I adjusted it until a 50Hz pulse of 70µs duration

IC1/Q1

Fix-replace with
7805 +5V
Regulator

Symptom —
No key entry
possible

was received. This is about the best value and gives reliable clock timings. The resistance value of the pre-set was 9.72k for 70µs.

This regulator set-up in my opinion is not very satisfactory. On my project the symptom was that none of the keys would accept an input. Scoping the voltage rail, it was sitting at 5.23V and had a lot of harmonics on it. I replaced with a 7805 regulator and it works OK. To install this, remove IC1 and Q1 Solder regulator into Q1 position and add a link from what was Q1 to the IC2 pin 4 rail.

Opto-isolator

No type or value given in text. I used the cheapest one from Maplin and it worked fine.

Figure 5 Page 29

R8 220k

Fix-replace with
330k

I found that it was not possible to adjust the 50Hz pulses for the correct frequency. They should appear at every 20ms. Replace R8 with 330k. This

Symptom — Clock does not keep correct time in Battery mode and Adjustment is not possible when D11, C1 removed (see set-up in Jan 91)

allows the adjustment to work OK.

R10 22k Replace with 10k

Similar to above. Cannot adjust the pulses to 3.125kHz. Also adjust is not possible in setting up.

Page 38

December 90

Page 40

Fig.6 Main CPU

R15/16

R15/16 are shown transposed. These need to be changed over.

January 91

Fig.13 Page 38 Printing errors

D9 has no polarity shown. Positive, striped end should go to the left (R5/D8 junction) D11 is shown reversed. R13 is shown twice. The one below IC1 should be D6 (Zener) and the positive strip should go to the right (R3

junction) R7 is shown going to the positive rail above IC8. It should go to the negative rail where LK13 is. R18 below IC9 should be R17 and the right hand end should go to the positive rail not the negative rail. The overlay presented on the other page shows the correction.

Section-Calibrating the timing Circuits: The end to the paragraph mentions RV3. This should read RV8.


Parts List R2,11,17 shown as 1k — should be 10k

Main CPU Board Problems

You should inspect the copperside of the PCB closely for any solder bridges. These can occur between the tracks of IC5/6/7 as the tracks are very close together. When I first powered up the project, the display gave a series of blocks. This proved to be shorted tracks on the data address bus lines. I used a 2.5mm soldering iron and 22swg solder and still managed to bridge a few tracks. No damage was done to the display. Check thoroughly your solder work before powering up. I suggest the IC sockets are mounted and soldered first and then before any components are added, use a meter to check all address and data lines for shorts. This avoids problems later.

EASY-PC, SCHEMATIC and PCB CAD

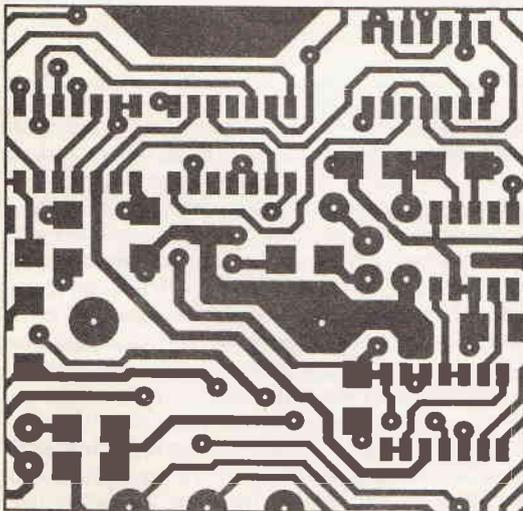
Over 7000 Installations
in 50 Countries Worldwide!



- Runs on:- PC/XT/AT/286/386/486 CGA EGA VGA.
- Design:- Single sided, Double sided and Multilayer boards.
- Provides Surface Mount support.
- Standard output includes Dot Matrix / Laser / Inkjet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Superbly easy to use.
- Not copy protected.

Still Only
£98.00!
Plus P&P + VAT

BRITISH
DESIGN
AWARD
1989

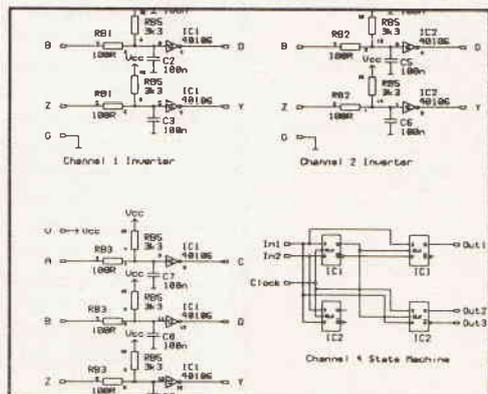

Standard Library includes over 400 Symbols.

For full info' Phone, Fax or Write to:

Number One Systems Ltd.



The CAD Specialists

REF: ETI, HARDING WAY, SOMERSHAM ROAD, ST. IVES, HUNTINGDON, CAMBS, PE17 4WR, ENGLAND.

Telephone: 0480 61778 (7 lines) Fax: 0480 494042

International: +44-480-61778 Fax: +44-480-494042

ACCESS, AMEX, MASTERCARD, VISA Welcome.

Frequency Plotter

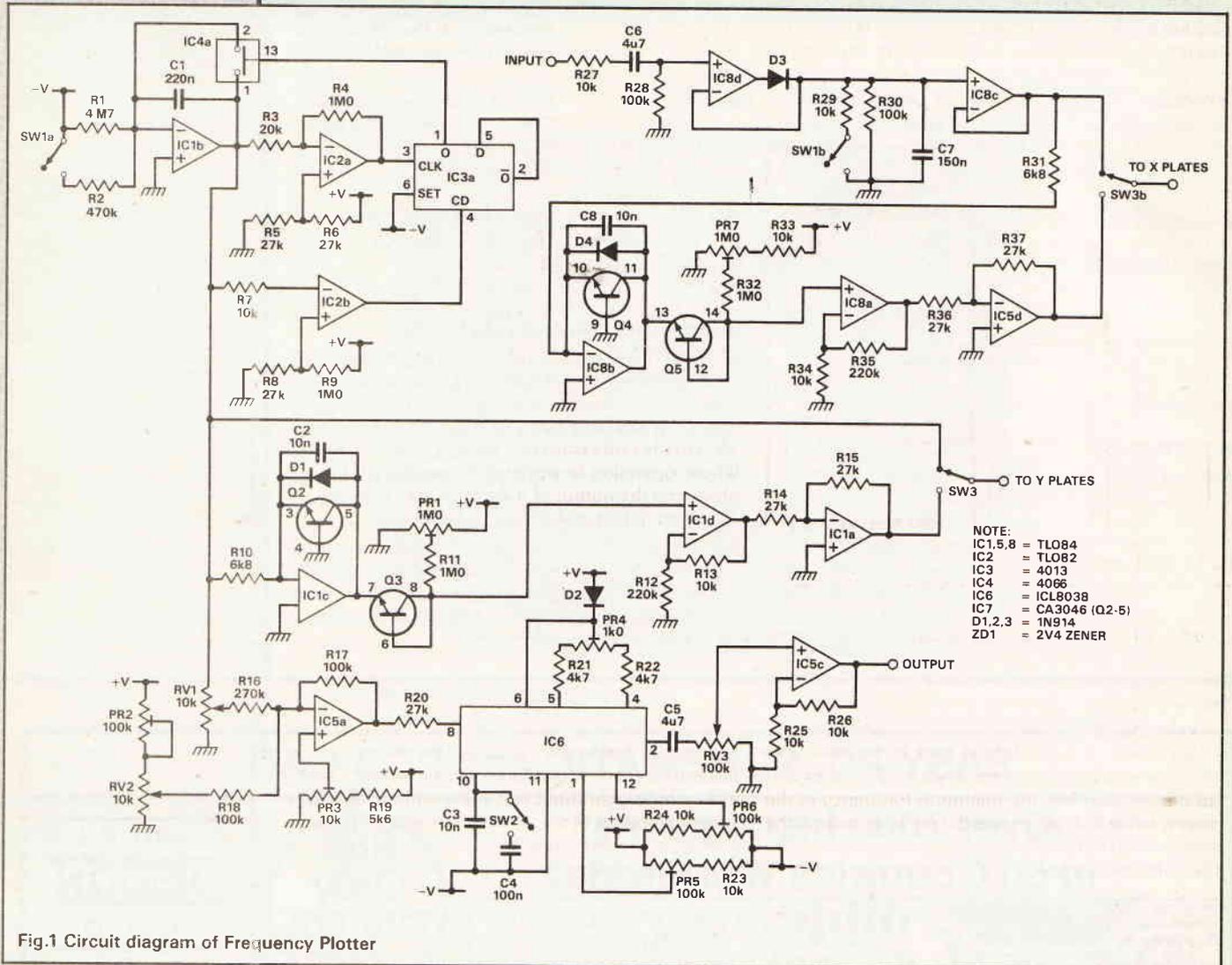


Fig.1 Circuit diagram of Frequency Plotter

Edward Barrow constructs this handy piece of test equipment to use with your oscilloscope.

If you're not confident with the design aspects of passive or active filters or being an audio buff, you want to test the response of your speakers, amplifier or whole system, this project could be for you. You do need an oscilloscope however, to plot the frequency response, of your questionable circuit. By frequency response, we mean the amplitude response (y-axis) versus frequency (x-axis). The usefulness of this project is limited by your own ingenuity.

The unit generates both voltages to drive the x and y plates of the oscilloscope and you have the option of having either logarithmic or linear plots for both amplitude and frequency response — what more could one ask?

Theory

The basic operation can be condensed into a paragraph with the help of a schematic diagram (Figure 1), but to understand its full operation this needs to be expanded.

This project can be broken down into two sections, the first generates a pure audio tone, (a sine wave), which sweeps up the spectrum and so provides

a test signal. After this signal is processed by the circuit under observation it is returned to the second section of the circuit. This signal gives a direct indication of the frequency response but needs the second section to turn this signal into a form palatable to oscilloscopes.

Now we've dispensed with the simplified form lets take a closer look at the workings. The heart of the circuit is the sine wave generator built around IC6. To sweep this, a ramp generator has been built around the integrator IC1 b. By an integrator we mean a circuit which performs the mathematical function of integration. This is done with respect to time and so the result of putting in a DC constant is a linear time function, ie a straight line of increasing voltage. Two comparators and a D-type flip/flop provide the necessary logic to control this integrator. To understand this, its best to do so in conjunction with a timing diagram, Figure 2. When the circuit is first switched on the output of the integrator, originally at zero, starts ramping upwards, when it reaches $+V/2$ the output of comparator 1 (IC2a) changes state to a high one. A slight amount of positive feedback has been added to make this transition a smooth one. This has a knock-on effect as its connected to the clock of the flip/flop

which is configured as a divide by 2. The net result is that the flip/flop's output goes high turning on the bilateral switch thus resetting the integrating capacitor so causing the integrator's output to drop like a lead weight towards zero volts.

If you were to wait for it to reach zero you would be there a long time, because of the exponential nature of the decay it only approaches zero. So we compromise and say when it reaches $+V/50$ then we start the ramping process again. Comparator 2 (IC2b) makes this decision. When this voltage is reached it sends a positive pulse to the flip/flop resetting its output low, turning off the bilateral switch and so stopping the reset cycle. Notice that no positive

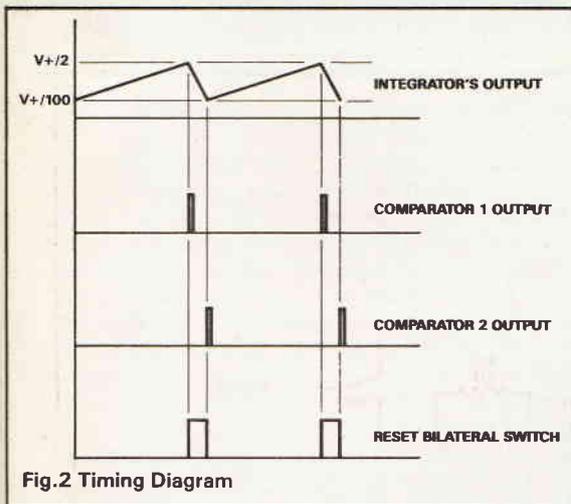


Fig.2 Timing Diagram

feedback has been included as a clean transition is less critical, once the flip/flop has been reset. The result of all this is a linear ramp which we use to sweep both the oscilloscope and the oscillator. To allow the user to tailor the range of sweep and the offset frequency of the oscillator two pots have been included to alter the characteristics of the ramp wave. RV2 provides an offset which sets the minimum frequency of the sweep, while RV1 attenuates the ramp so controls the sweep range. Before the oscillator can be driven the above two quantities have to be summed and inverted as the oscillator has a negative voltage frequency slope, (higher voltages result in lower output frequency).

As mentioned in the introduction, the bottom frequency axis can be made logarithmic as well as linear. An alternative method from the obvious one that is to change the ramp wave sweeping the oscillator from a linear one to a logarithmic one, is used. Instead we change the oscilloscope's sweep voltage from a linear one to a logarithmic one. The bit that does this is, a logarithmic converter. More about its workings in the 'How it works' section.

The returned signal is buffered and simultaneously actively rectified. The DC signal that results has a direct correlation to the attenuation experienced by the generated sine wave. In other words this DC signal represents the frequency response at that particular frequency. So a plot of this would be a plot of amplitude response vs. frequency, exactly the thing we are after.

Again a log converter similar to the previous one allows logarithmic amplitude response to be plotted.

Testing And Setting Up

Since the only people who will build this circuit have access to an oscilloscope this section has been easy to write. The first task is to turn on the power and check

that power is flowing in the right quantity and direction to the right parts of the circuit, namely the supply pins of the IC's. Do this before inserting the IC's in their sockets. Working your way around the circuit with a probe the logical place to start is at the output of the integrator. Check that it is producing a smooth ramp and that by flicking the switch its frequency rises from 2Hz to about 20Hz. If this is not the case then check the states of the comparators and the flip/flop, Figure 2 will give you some help with what to look for. Next check the output of the logarithmic converter and make sure it looks something like the one shown, flat tops and steep sides. To set PR1 use your oscilloscope to adjust it so the output cycle starts at zero volts.

Next on the agenda is the oscillator. Set RV1 and RV2 to zero and adjust PR3 so that the output of IC5a is the same as pin 6 on IC6. This should ensure oscillation at the output (pin 2). Now comes the part where a good eye is required to adjust the symmetry and the distortion. The idea is to monitor pin 2 while firstly adjusting PR4 so that it looks symmetrical, some might find it easier to monitor the triangle or square wave output, pin 3 and 9 respectfully to obtain a 50% duty cycle. After you are satisfied with this then adjust PR5 and PR6 so that the sine wave looks best. Its worth mentioning that the former adjusts the roundness of the top of the wave while the latter adjusts the bottom. If you have access to a distortion meter then life is made more exact and simpler. Lastly check the whole operation is working by turning RV1 while observing the output of IC5c. It should look like the depiction in Figure 4 but more importantly its amplitude should be constant throughout a full sweep. Flipping SW2 will raise the frequency to the next range.

There only remains the rectifier part to check and calibrate. This requires the connection of the unit to both the x and y plates as it would be when in every day use (see In Use section). With no input, the linear and logarithmic outputs should be at zero but logarithmic will require the adjustment of PR7. To test that all is well connect the test output directly to the test input. The result, if all is correct, is a straight line plot above the zero axis on both logarithmic and linear settings. Just to be sure of workings of this project I suggest you test the responses of some simple high and lowpass RC filters. This should yield the well known logarithmic plot of 3db per octave.

In Use

Connecting this project is a pretty straight forward exercise. Before connecting up though, override your oscilloscope's own ramp generator, there is usually a switch to do this marked 'external'. The two sets of plates can now be connected to their respective outputs on the unit.

The sweep frequency has to be selected. Some tips on this: firstly when examining responses in the bottom of the audio range, below 100Hz, it is advisable to use the 2Hz setting to allow the oscillator and the rectifier time to settle. The high range has no such restraint. When setting up the unit for your particular needs set RV1 to zero and adjust RV2 so that the frequency of the oscillator is the minimum frequency you require. Next adjust RV1 so the range of the sweep is adequate for your needs. The other pot, RV3, has been included so that the unit can be used on test circuits which have amplification or can only handle small input signals. So when testing equipment like amplifiers, start with this pot in the zero position and slowly increase it (emphasis on slowly) till you get a reasonable returned signal.

By connecting the unit to your stereo (see above warning) and using a microphone to pick up the returned signal you can test the frequency response of

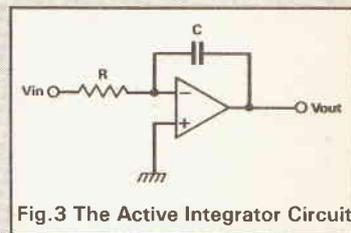


Fig.3 The Active Integrator Circuit

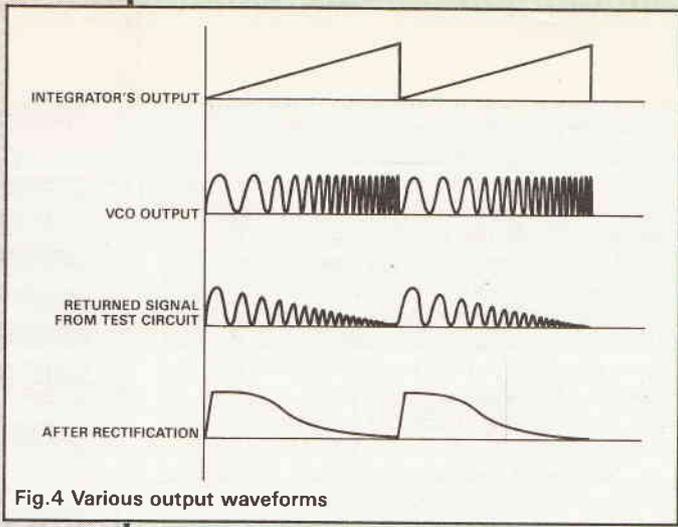


Fig.4 Various output waveforms

HOW IT WORKS

The active integrator is configured in inverting mode so the $-$ input is a virtual ground so for Figure 3 we can postulate
 $V_{in}/R = -C(dV_{out}/dt)$
 or $V_{out} = (-1/RC) \int (V_{in}) dt$
 By making $V_{in} = -V$ supply and choosing values of R and C we can get our desired rate of ramping.

One hurdle in any circuit of this type is the problem of choosing a sweep frequency that will give adequate settling time for the oscillator. It would be ludicrous to sweep an oscillator with a range from 20Hz to 20kHz with a 40Hz ramp as the oscillator will have little or no time to actually generate any audio signals at the lower end of the range. So to get around this hurdle two switchable frequencies are possible, 2Hz and 20Hz. The former frequency obviously will not give a stable trace only a moving dot, but the latter will due to persistence of vision.

Both logarithmic converters are of the same design. The op-amps exploit the logarithmic relationship between the base-emitter voltage and the collector current of a transistor to produce an output proportional to the logarithm of the positive input voltage. The input resistor is necessary to turn this input voltage into a suitable current for the transistors to process. The other transistor is necessary for temperature compensation. The zeroing presets generate a small offset current to set what input voltage gives zero output. The capacitor placed across the transistor is there to stabilise the feedback loop while the diode provides an insurance policy to the transistor if by some fluke the input voltage goes negative. If this is allowed to occur then base emitter breakdown would occur and a bill for a new transistor will follow. The non inverting amplifier provides the gain to bring the output level from hundredths of a volt to volts and a inverting amplifier returns it above the zero volts axis. Before finishing with logarithmic converters it should be noted that its best to use op amps with low offset currents like FET input ones and in the area of transistor selection a monolithic set is preferable as this gives good temperature matching. Here a package of six transistors, LM3046, and common TL084 FET input op-amps are used.

Turning to the oscillator a differential amplifier, IC5a, acts as a both a summer for the DC bias and the attenuated ramp and as an inverter.

your system. Some amplification and buffering may be needed if high impedance microphones are being used. It is possible also to test the frequency response of cassette record/playback mechanisms with different tapes, but the workings has been left to you to figure out, answers on the back of a postcard (only kidding).

Construction

Board construction follows the usual logical pattern, link wires and small components like diodes and resistors first. Secondly IC sockets, presets, and finally the capacitors, regulators and bridge rectifier. Then connect the pots and switches and proceed to test the circuit. After that ordeal, finally solder the connectors in place and fully adjust the presets.

I used a simple U shaped two part aluminium box

preset (PR3) sets the level about which the inversion takes place and so sets the minimum possible frequency. The ICL8038 (IC6) is configured as a voltage controlled oscillator with a 40:1 range. A voltage from about $+V$ supply to $+V$ supply/2 will cover this range. To get around the problem that op amp outputs can only rise to 2V below its positive supply we drop the oscillators positive supply by 2.4V using a zener diode, thus giving some headroom to the op-amps. The timing symmetry of the sine wave can be adjusted by PR4 and the distortion levels of the sine wave can be similarly tweaked by the two presets PR5 and PR6. This chip also produces square and triangle waveforms but these are of no use in this circuit its only the sine wave output that we are interested in. It is not the best of sine waves as it is made from a triangle one by clipping it with a diode ring, but even so distortions of less than 1 are possible. Again two ranges are catered for by switching timing capacitors these are 20Hz-800Hz and 500-20kHz. Amplitude adjustment is made by RV3 before buffering with a little gain by IC5c.

The returned signal is decoupled before being actively rectified, this is done to remove any stray DC components that might have been added by the test circuit. The design of the low pass filter that proceeds the diode (D5) is critical as this determines the speed at which the output can decay and so dictates the steepest measurable falling amplitude response. A balance must be struck between the speed of decay, a high one is preferable, and its other action to smooth the bumps caused by the sine wave, a low one preferred. There is no such problem with the attack time as the diode has negligible resistance when conducting and so the only limiting factor is the output resistance of the op amp IC8d. Two choices of low pass action are available and correspond to the two ranges available on the oscillator. On the high range it is not necessary to have such a heavy low pass action as the minimum possible frequency is 500Hz so the lowpass action is lightened to allow steeper decays. The power supply for this circuit consists of a bridge rectifier generating a DC signal that is smoothed by two large electrolytic capacitors. Two 5V regulators, one positive and one negative, feeds off this and in turn supply the circuit board with power. The only external requirement is a transformer to provide the AC.

PROJECT

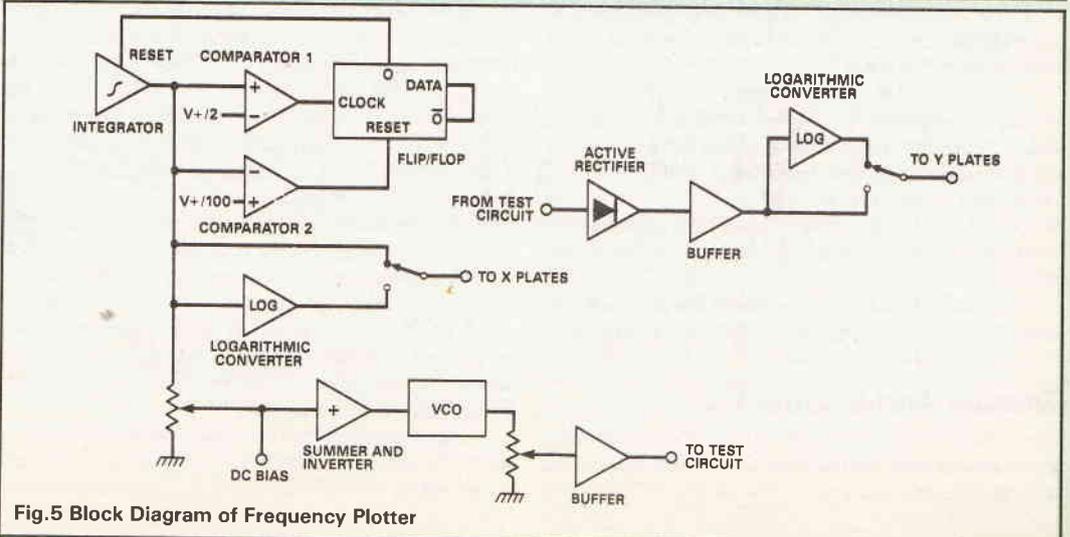


Fig.5 Block Diagram of Frequency Plotter

to mount the unit and power supply. To reduce pickup all high impedance connecting wires were screened. The connectors used on the prototype were 4mm plugs for connection to the test circuit and standard BNC ones for connection to the oscilloscope.

IC sockets were used on the prototype and are as always recommended to you. Take extra care with the ICL8038 as it has a very sensitive disposition to static so apply the usual CMOS precautions. The same is true of the two less expensive and less sensitive CMOS chips.

BUYLINES

No problems in any department as all components are widely available. Only getting hold of a 2.4V zener diode might present problems but a higher value like 2.8 can be substituted.

PARTS LIST

RESISTORS (all 1/4W 5%)

R1	4M7
R2	470k
R3	20k
R4,9,11,32	1M
R5,6,8,14,15,20,	
25,26,36,37	27k
R7,13,23,24,27,	
29,33,34	10k
R10,31	6.8k
R12,35	220k
R16	270k
R17,18,28,30	100k
R19	5k6
R21,22	4k7
R38	1k2
RV1,2	10k
RV3	100k
PR1,7	1M
PR2,5,6	100k
PR3	10k
PR4	1k

CAPACITORS

C1	220n poly
C2,3,8,15	10n Poly

C4,13,14	0.1µ Poly
C5,6	4.7µ Tant
C7	0.15µ Poly
C9,10	4700µ
C11,12	2200µ

SEMICONDUCTORS

IC1,5,8	TL084
IC2	TL082
IC3	4013
IC4	4066
IC6	ICL8038
IC7	CA3046
REG1	7805 +12V 1A
REG2	7905 -12V 1A
D1,3,4	1N914
ZD1	2V4 Zener
LED1	5mm RED

MISCELLANEOUS

SW1,4	SPDT Sub-min toggle
SW2	SPST Sub-min toggle
SW3	DPDT Sub-min toggle
4mm plugs	
6V-0-6V 500mA Transformer	
Case and power lead to suit	

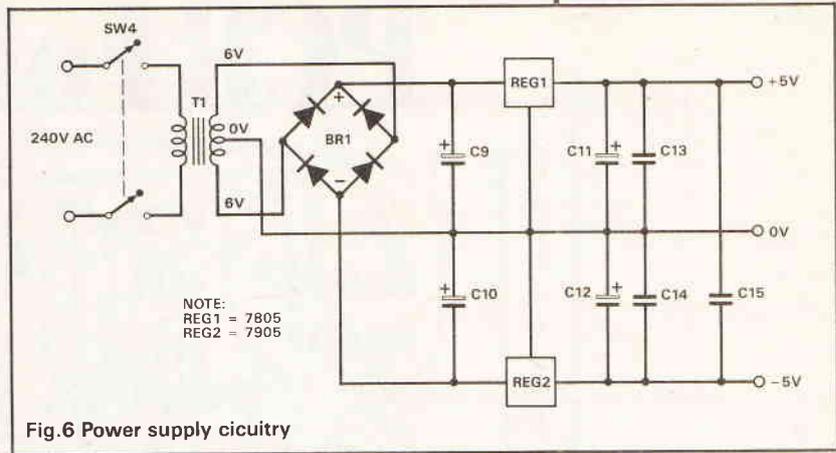


Fig.6 Power supply circuitry


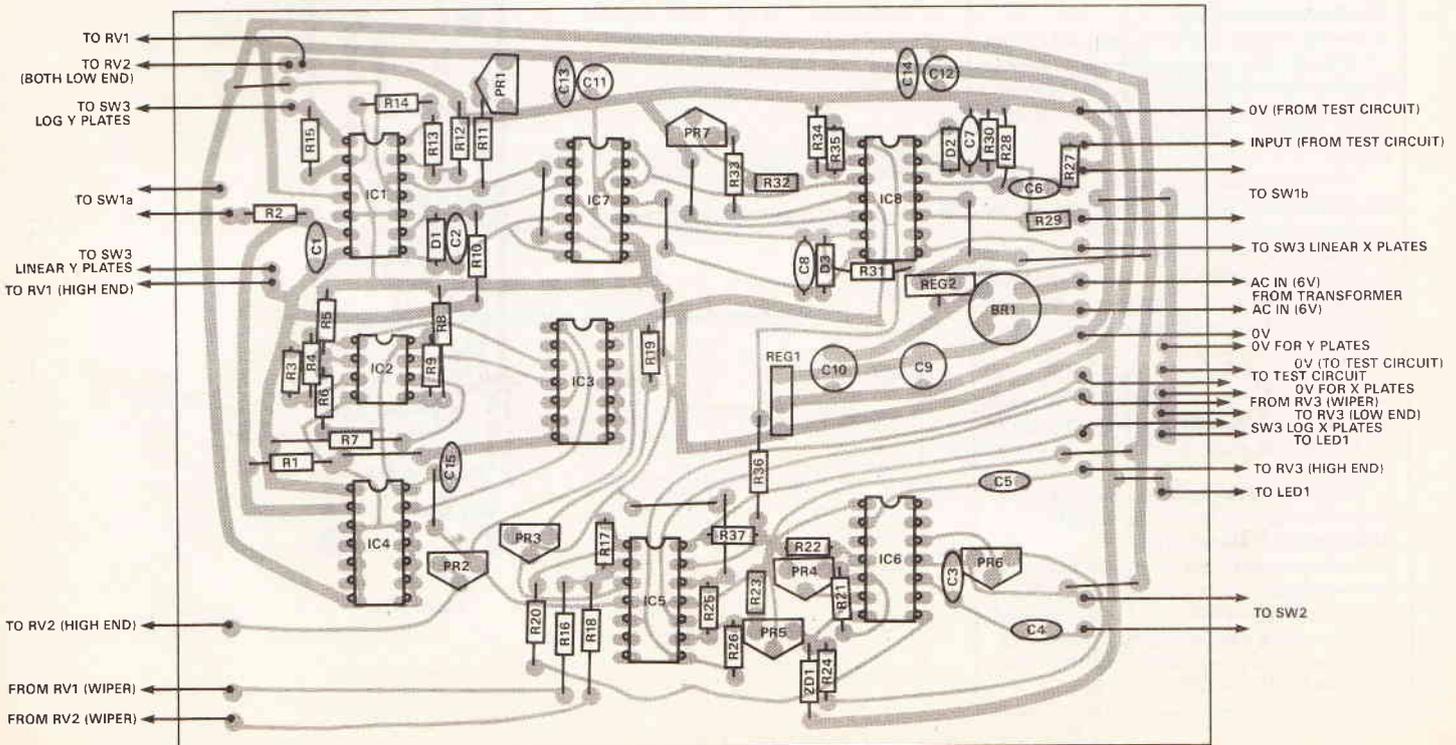


Fig.7 Component Overlay for the plotter

PCB Foils

SCR tester

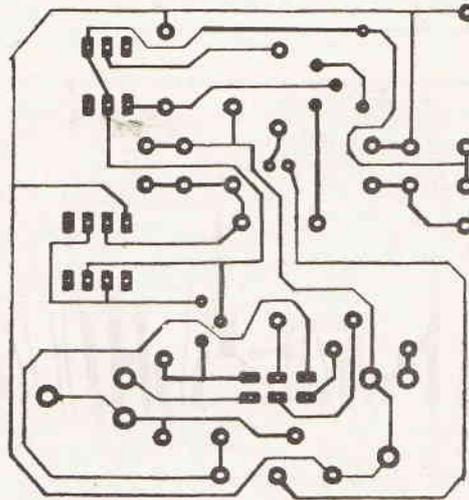

Thyristor Tester Foil



Remote Control Timeswitch Project (Dec, Jan, Feb 91)

The following paragraph is missing from the text.

The Standby Battery

A standby battery should be selected for the control unit. The type must be able to supply 50mA whilst maintaining at least 7V. I used an 8.4V 'PP3' style Ni/Cd battery (Maplin HW31J) which gave a standby capacity of 2hours.


In order to find the correct value of resistor R4 for the type of battery chosen, connect a 10k variable resistor and a meter in place of R4 on the board. Connect the power and adjust the variable resistor until the recommended trickle charging current flows. Replace the 10k pot with a standard resistor of approx the same value resistor.

Any opto-isolator with correct pin layout is suitable for IC10 (Maplin WL35Q). The value of the crystal is 1.8432MHz. In Table 7a on page 32 of February. Note should read 1-link not fitted.


Further modifications to the timeswitch project can be seen in this issue of ETI.

SSB Receiver March 91

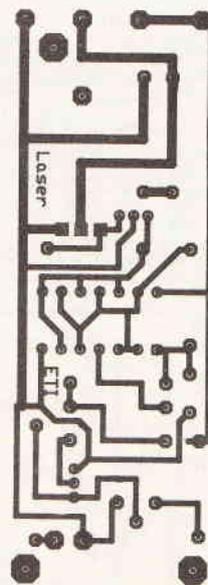
IC3 is shown present on the overlay but not in the circuit diagram or component listing. IC3 is not required and should have been removed from the overlay after development of the circuit. Q1 can be any of a vast selection of PNP transistors like BC557 or BC177 if to hand.



Laser Foil

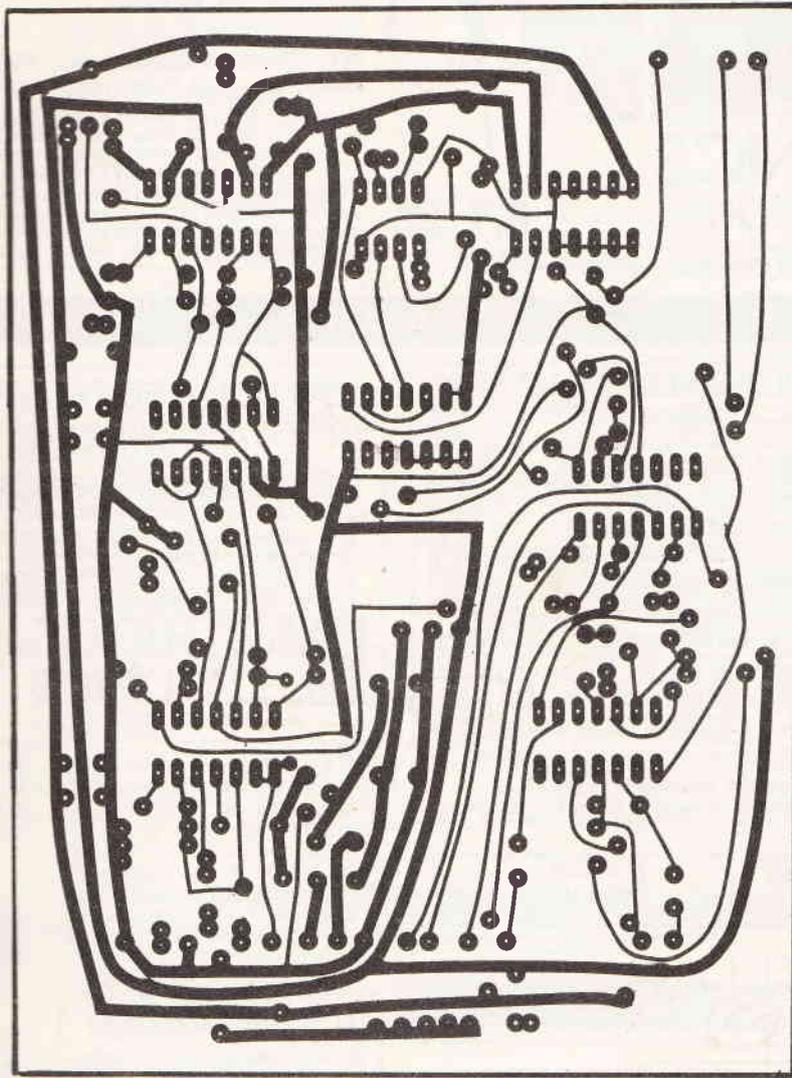

The Frequency Plotter Foil

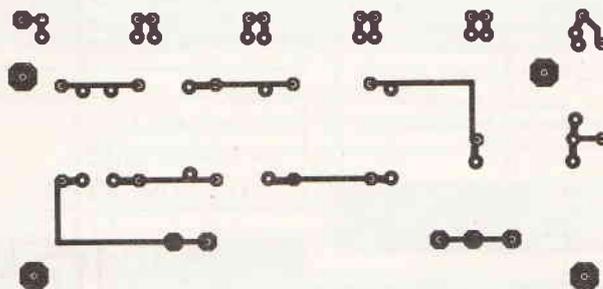

The Laser High Voltage Foil

ETI

ELECTRONICS

TODAY INTERNATIONAL



CLASSIFIED

James Trott
0442 66551 Ext 250

Send your requirements to:
ETI Classified Department, ASP, Argus House,
Boundary Way, Hemel Hempstead, HP2 7ST.

Lineage: 55p per word (+ VAT) (minimum 15 words)
Semi Display: (minimum 2 cms)
£14.00 per single column centimetre (+ VAT)
Electromart £22.00 per insertion (+ VAT)

Ring for information on series bookings/discounts.
All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

FOR SALE

CAMBRIDGE COMPUTER SCIENCE LIMITED

Digital multimeter, 14 ranges with leads, instructions & battery	£16.00 each	164 '165 '174 '191 '193 '240 '253 '257 '260 '298 '353 '365 '373 '390 '399 '570	£1.00 each
LCD Display modules, 40 chars '4 lines with driver board & data	£13.00 each	2764 EPROMS (Ex-equipment)	£1.20 each or £5.00/25
3.5" 720K Diskette Drives	£39.00 each	27128 EPROMS (Ex-equipment)	£2.50 each
10MB, 16 Winchesters, used, 3 months Why	£42.00 each	27C256-25 EPROMS	£3.50 each
5.25" Disk Drives, 80 Tks, DSD	£34.00 each	256K Byte DRAM Modules, removed from equip.	£6.00 each
5.25" drive cases, room for drive PSU & fan	£10.00 each	6116 2K Byte SRAM	£1.10 each
5.25" Disk Drives, 80 Tks, DSD Used, No Why	£15.00 each	6264-12 8K Byte SRAM	£3.80 each
(The £15.00 drives are sold on a strictly 'as is' basis)		62256-10 32K Byte SRAM	£5.00 each
5.25" Disks, DSD, 48kps boxes of 10	£3.00 box	65256 32K Byte rams	£4.00 each
48W PSU 5V 2.5A, 12V 1.5A - 12V 0.4A, cased with on/off switch	£10.00 each	8K Byte NV ram chips £3.00 each	£10.00 four
Bare switch mode PSU 5V 2.5A 12V 2A - 12V 0.1A	£7.00 each	20 pin dll low profile IC sockets £0.50/10	£4.00/100
3V @ 10A PSU	£4.80 each	24 pin dll low profile IC sockets £0.55/10	£4.60/100
Ground PSU 0-30V @ 5A Reduced to clear	£30.00 each	40 pin dll low profile IC sockets £0.60/10	£5.00/100
Disk Drive Data lead BBC Micro to Disk Drives	Single £2.00 Dual £4.00 each	CPU cards (Newbrain) Z80 CPU, 3 EPROMS & 65+ mostly 7ALS ICs	£2.00 each
Disk Drive Power lead BBC Micro to Disk Drives	Single £2.00 Dual £4.00 each	Circuit tester, finds faults in TTL & CMOS logic circuits, inc leads	£8.00 each
68000 CPUs (the first orders get 10MHz chips)	£3.50 each	Keyboard, 100 keys on board LCD & micro if	£8.00 each
8086 CPU chips	£2.00 each	Eurocard sub-racks, single height, 19" rack	£13.00 each
286A CPU, CTC, PIO £1.20 each, DMA £2.00	4.50 all 4	Metal project boxes drilled & painted but unused	£5.00 each
7ALS TTL, pick and mix, buy 10 or more for	£0.12 each	28 x 32.5 x 5cm	£5.00 each
Types available '00 '02 '04 '08 '11 '12 '13 '15 '20 '21 '26 '27 '30 '32 '33 '37 '38 '42 '74 '83 '85 '86 '96 '107 '108 '122 '132 '136 '138 '139 '149 '151 '153 '157 '158 '160 '162 '163		Toroidal mains transformer, 12V 4A & 0.4A, 12-0-12 1A & 2A, 9-0-9 2A	£4.00/1 £8.00/2 £8.00/3
Prices include postage. Add 50p (plus VAT) to orders below £5.00. All items new unless stated. Add 15% VAT to all prices. Send an SAE for our latest list or for more info.		Smoke detectors, small size	£7.00 each
		Smoke detectors, large with escape light and pause feature	£13.00 each

Dept ET1, 374 MILTON ROAD, CAMBRIDGE CB4 1SU
Tel: 0223 424602 or 0831 430496 (Please note mail order only)

DO YOU USE TELEPHONE LINES?

CONNECT YOUR EQUIPMENT TO THE TELEPHONE SYSTEM without the cost and delay of type approval.

ACHIEVE THIS BY USING OUR Approved transmit, receive and hybrid systems for use on P.S.N. (normal dial system), Private circuits, or Music Programme circuits.

THE LEGAL ECONOMICAL SOLUTION for broadcast signals — Security alarm signalling — Linking of remote factory sites for P.A. — intercom etc.

Call 0268 793381 or Fax 0268 565759 FOR FULL DETAILS

PARTRIDGE ELECTRONICS

UNIT D
318 HIGH ROAD
BENFLEET
ESSEX SS7 5HB

A. C. PARTRIDGE LTD.

SOLAR PANELS. 100mm x 60mm, 2.5V, 0.2W, £1.30. 6 for £7.00. 6" x 6", 6V, 0.7W, £5.00. 12" x 6", 12V or 6V, 1.4W, £8.00. 12" x 12", 12V, 3W, £14.00. 36" x 12", 12V 5-6W, £20.00. Prices include UK P&P. Complete panels available up to 12V, 12W, POA. Orders to, Bob Keyes GW41ED, 4 Glanmor Cres, Newport, Gwent NP9 8AX.

ETI, 98 issues, April 1972-August 1980, £60. B. Cortes, 60 Kitchener Street, Swindon. Days (0793) 513533 ext 2397.

SPECIAL OFFERS

CATALOGUE £1 + 25p P&P

Resistor pack, 85 different, E12 values + zero ohm link, total content 1000 resistors	£8.85
LEDs 3mm or 5mm red or green	50 each yellow, 11p each
Cable ties	1p each, £5.95 per 1000, £49.50 per 10000
Stepping motor 4 phase, 12V 7.5 step 50 ohms	8.95
SA402 stepping motor drive chip	£3.95
FM Transmitter kit, good quality sound	£8.80
High quality photo resist copper clad epoxy glass boards	
Dimensions	single sided double sided
3x4in	0.35p £1.07
4x8in	£2.40 £2.80
6x12in	5.37
12x12in	£10.66
Special offers	
Computer grade capacitors with screw terminals 38000uf 20v	£2.50
87000uf 10v, £1.95; 68000uf 15v, £2.95; 10000uf 16v, £1.50	
7 segment common anode led display 12mm	£0.45
LM2931A15.0 low drop out 5v regulator, 10.220 package	£0.85
68250 P channel mosfet £0.45; BC559 transistor £3.95 per 100; 74L805 hex inverter £10.00 per 100, used 848 Microcontroller £3.50	
Stereo LWMWFM tuner/preamp Assy with volumelene controls & tuning scale. Brand new in makers carton £6.95, faulty £3.50, circuit etc for above £0.50	
Hour counter used 7 digit 240v ac 50Hz	£1.45
LCD display 16 digit 7x5 dots, dot matrix	£2.50
QWERTY keyboard, 38 key, good quality switches, new	£3.00
QWERTY keyboard with serial output, no data	£5.00
Wide range of CMOS TTL 74HC 74F Linear Transistors kits, capacitors tools etc always in stock. Please add 95p towards P&P VAT included	

JPG ELECTRONICS

276-278 Chatsworth Road, Chesterfield S40 2BH
Access/Visa Orders (0246) 211202 Callers welcome

SERVICE MANUALS

SERVICE MANUALS

Available for most equipment

TV's, Video's, Test, Audio etc

Write or phone for quote

MAURITRON (HRT),
8 CHERRY TREE ROAD,
CHINNOR, OXON OX9 4QY
TEL (0844) 51694 FAX (0844) 52554

LOUDSPEAKERS



Send for our FREE price list PL20: all we ask is a large S.A.E. (32p) (Overseas U.S. \$2 bill) (Europe — 3 International reply coupons)

SYSTEM DESIGNS (Total Kits):
Focal, KEF Constructor Series, etc.

DRIVE UNITS FOCAL, KEF, Audax,
Peerless, Seas, Elac Metal Dome,
Siare, Scanspeak, etc.
Also Group/Disco Units

CROSSOVER NETWORKS —
Active & Passive Components,
Accessories, Polypropylene Caps.
Expert advice via our enquiry service.
Units, Networks & Components
Speaker Builder & Audio Amateur mags

Full details from
FALCON ELECTRONICS
(Dept. ET1) Tabor House, Mulbarton,
Norfolk NR14 8JT (0508) 78272
(Proprietors: Falcon Acoustics Ltd.)

FM Transmitter Kits
Also a Telephone Bug Detector Kit
Ready built FM transmitter 65.50 including Post & Packing
These are Commercial Kits — We also stock a selection of
Scanning Receivers, so telephone for latest stock or ask for
a free catalogue.

HOTLINE ELECTRONICS
97 LEIGH RD, ATHERTON, GT. MANCHESTER
Telephone Alherton (0942) 891140 Mail Order Only

WANTED

Turn your surplus
transistors, ICs etc, into
cash. Immediate settlement.
We also welcome the
opportunity to quote for
complete factory clearance.

Contact:
COLES HARDING & CO.
103 South Brink
Wisbech, Cambs.

NOW ESTABLISHED OVER 15 YEARS
Tel: 0945 584188
Fax Number: 0945 588844

MANUFACTURERS ORIGINAL SPARES

COMPONENTS for TV · Video · Audio · Computer

WE CAN SUPPLY A VAST RANGE FOR MANY MAKES — WRITE (encl SAE please) OR PHONE 0452 26883 FOR A 'PRICE & AVAILABILITY' ON YOUR REQUIREMENTS.

AMSTRAD · SINCLAIR	COMMODORE	OTHER MAKES
PEGATA (PC1840).....£32.72	6526 CIA.....£10.87	Sanyo/Fisher VCR Belt Kit
40010 G Array.....£20.63	8520 (Amiga).....£11.02	VTC6500/VB/S3500.....£2.49
CPC464 Serv Manual.....£8.49	8565 VIC.....£23.48	Ferguson 3V35/38/39
Spec 48K Membrane.....£4.50	8701 Clock Gen.....£6.90	Tuner contr door.....£1.95
+128K Membrane.....£7.90	901225 Char ROM.....£5.37	Toshiba St-L2/U2L Power
QL Membrane.....£7.95	C16 User Guide.....£5.37	Transformer.....£9.99
ULA6C001E.....£15.99	ATARI	TBA530.....£1.14 UY38912.....£5.74
ULA7K010/40056 (+2).....£16.99	'Basic' ROM (XE/L).....£4.49	TBA810P.....£1.40 UPC1378/H2.45
ZX 8302 (DL).....£10.75	CO25915 GLUE (ST).....£24.31	TBA1001B £2.66 2SC3156.....£4.59
ZXB401 (Spec).....£7.94	Thermistor (SP-PSU).....£1.34	TEA2000.....£3.69 ZT1850/1.....£0.47

This just a small sample of our stock — We are also holding Tools, Connectors, Aerial & Telephone Accts and much more. For our catalogue please send 50p stamps/cheq. MAIL ORDER ONLY. Please add 95p (UK) P&P but not VAT. All items subject to availability. Price can change without notice.

MARAPET (TE), 1 HORNBEAM MEWS, GLOUCESTER GL2 0UE

Courses



Start training now for the following courses. Send for our brochure — without obligation or Telephone us on 0626 779398

Ref: ETI/05/91

Name _____

Telecomms Tech C&G 271

Radio Amateur Licence C&G

Micro-processor

Introduction to Television

Radio & Telecommunications Correspondence School
12 Moor View Drive, Teignmouth, Devon TQ14 9UN

MAKE YOUR INTERESTS PAY!

Over the past 100 years more than 9 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your FREE INFORMATION PACK on the course of your choice. (Tick one box only!)

Electronics	<input type="checkbox"/>	TV Video & Hi-Fi Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Refrigeration & Air Conditioning	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Electrical Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>
GCSE/GCE/SCE over 40 examination subjects to choose from			

Name _____ Address _____



International Correspondence Schools, Dept. EB551 12/314 High Street, Sutton, Surrey SM1 1PR
Telephone: (01-843 9568 or 041-321 2926 (24 hours)) Dept EB551

PLANS

ELECTRONIC PLANS. Laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and computer graphics tablet. 150 projects. For catalogue. SAE to Plancentre Publications, Unit 7, Old Wharf Industrial Estate, Dymock Road, Ledbury, Herefordshire, HR8 2HS.

RING FOR MORE DETAILS ON ETI MAGAZINE AND ASK FOR JAMES TROTT CALL 0442 66551



NATIONAL COLLEGE OF TECHNOLOGY

PACKAGED SHORT COURSES

The National College of Technology (NCT Ltd) offers a range of packaged short courses in analogue electronics, digital electronics, fibres and optoelectronics and programmable logic controllers for study at home or at work. The advantages are that you may:

- commence at any time — work at your own pace
- have a tutor (optional) and there is no travelling involved.

BTEC certificates are available subject to the conditions of the award. These highly popular packed courses contain workbooks, a cassette tape, circuit board and components necessary to provide both theoretical and practical training.

Whether you are a newcomer to electronics or have some experience and simply need updating, there is probably a packaged short course ready for you. Write or telephone for details, quoting ETI to:

NCT Ltd, Bicester Hall
5 London Road, Bicester, Oxon OX6 7BU
or telephone (0296) 613067 Ext. 202

MISCELLANEOUS

KITS, plans, etc. for surveillance, protection (sonic and HV), "007" gear. Send 2 x 22p stamps. For list ACE(TI), 53 Woodland Way, Burntwood, Staffs.

HEATHKIT UK spares and service centre. Cedar Electronics, Cedar House, 12 Isbourne Way, Broadway Road, Winchcombe, Cheltenham, Glous, Tel: 0242 602402.

RETAIL OUTLETS

EDINBURGH

OMNI ELECTRONICS

stock a wide range of electronic components at

174 Dalkeith Road,
Edinburgh EH16 5DX
Tel: 031 667 2611

Open: Mon-Thur 9.15am-6pm, Fri 9.15am-5pm,
Sat 9.30am-5pm — 1990/91 Catalogue £1.50

LIVERPOOL

PROGRESSIVE RADIO

87/93 Dale Street Tel: 051 236 0154
47 Whitechapel Tel: 051 236 5489

Liverpool 2

'THE ELECTRONICS SPECIALISTS'

Open: Tues-Sat 9.30-5.30

LONDON

CRICKLEWOOD ELECTRONICS

One of the largest component retailers in the UK. Fast and efficient, same day personal service on 'IN STOCK ITEMS'. Very competitive prices. No minimum order. Call Cricklewood Electronics now.

40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET
Tel: 081-450 0995/452 0161

SOUTH COAST

ELECTRONIC COMPONENTS
are best seen at

FRASER ELECTRONICS
42 ELM GROVE ★ SOUTHSEA ★ HANTS
Telephone (0705) 815584

Barclaycard Access
COME AND BROWSE BEFORE YOU BUY

LONDON

RADIO AND TV COMPONENTS ACTON LTD
21 HIGH STREET, ACTON, LONDON W3 6NG

MAIL ORDER TERMS, POSTAL ORDERS and or
CHEQUES with orders

Nett monthly accounts to schools, colleges and PLC only
ACCESS, VISA Phone orders between 9.30-12pm please.
Overseas readers write for quote on delivery.

Phone 071 723 8432 or 081 992 8430
Callers 323 Edgeware Road, London W2. Closed Sun
21 High St, Acton, London W3 closed Sun, Mon, Tues & Wed

LONDON

DIRECT ELECTRONICS
ELECTRONICS COMPONENT SPECIALISTS

627 ROMFORD RD,
MANOR PARK
LONDON E12 5AD
Tel: 081-553 1174

Mon-Sat 10-6 pm/Thurs 10-1pm
We stock a large range of TV & Video spares

E
L
E
C
T
R
O
M
A
R
T

E
L
E
C
T
R
O
M
A
R
T

PHOTO -COPIES

ETI has been published for over 19 years and in this time a great many interesting and valuable projects and features have graced its pages. Although backnumbers are available for only the past 12 months issues we can supply photocopies of any individual article ever published in ETI.

Photocopies cost £1.50 per article regardless of their length. Please note that projects published over several issues must be ordered as a series of individual articles, each for £1.50.

PCB foil patterns (where published) and any errata are included with all photocopies as applicable.

NEXT MONTH

Next month we continue our Laser series with a look at building a receiver for the modulated laser project this month and delve into the minefield of applications this creative little idea could be used for. Ray Marston looks at temperature sensor circuits and if precise control of temperature is a requirement of yours then look no further than the next issue with a project on this theme.

We also have a modification to the Four-track cassette recorder we featured in November.

The theory of the Piezo-electric effect is always an intriguing subject to look at and Back to Basics, our beginners series, examines inductance.

In response to our never ending stream of letters regarding the quality of audio components, John Linsley Hood presents an article on 'Supercomponents' to give hi-fi nuts something else to debate.

All these to be consumed in the June edition of ETI, out on 3rd May.

The above articles are in preparation but circumstances may prevent publication

LAST MONTH

Projects which featured in the April issue of ETI were as follows:

- Active Direct Injection Box.
- A Digital Tachometer.
- Designing an electronic testmeter.
- A Radio Callibrator.
- Nicam TV conversion.
- An EPROM Eraser.

Features included: Lasers, Resistive networks, Mystery earth signals in VLF, Earth Loop Antennas, and Voltage Reference Generator Circuits. A limited back number of copies are available from Select Subscriptions (address on contents page).

ADVERTISERS' INDEX

BK ELECTRONICS.....	IFC	GNC.....	36
BLUE ROSE ELECTRONICS.....	36	GREENBANK ELECTRONICS.....	44
BUSINESS INTEGRATED.....		HAPPY MEMORIES.....	44
TEST SYSTEMS.....	50	HIGH Q ELECTRONICS.....	50
CIRKIT ELECTRONICS.....	3	J&N BULL.....	IBC
CRICKLEWOOD ELECTRONICS.....	21	LAB CENTER.....	33
DISPLAY ELECTRONICS.....	28	MAPLIN ELECTRONICS.....	OBC
ELECTRONIZE.....	36	NUMBER ONE SYSTEMS.....	57
ELECTRO VALUE.....	21	OMNI ELECTRONICS.....	50
EMINENCE.....	50	RADIO & TV COMPONENTS.....	49
ESR.....	50	REED ELECTRONICS.....	66
FRIENDS OF THE EARTH.....	50	STEWARTS OF READING.....	25
		WILMSLOW AUDIO.....	25

Please supply photocopies of the following articles from ETI (complete in block capitals):

Month Year Page (if known)

Title

Month Year Page (if known)

Title

Month Year Page (if known)

Title

I enclose a cheque/postal order made out to ASP Ltd. to the value of £1.50 per photocopy ordered.

Total remittance £ Date

Name

Address

..... Postcode

Send the completed form and your remittance to:

ETI Photocopy Service
Argus House
Boundary Way
Hemel Hempstead
Herts HP2 7ST





HIGH POWER AMPLIFIER For your car, it has 150 watts output. Frequency response 20-20 to 20 KHZ and a signal to noise ratio better than 60db. Has built in short circuit protection and adjustable input level to suit your existing car stereo, so needs no pre-amp. Works into speakers ref 30P7 described below. A real bargain at only £57.00 Order ref 5P11

HIGH POWER CAR SPEAKERS. Stereo pair output 100w each. 4ohm impedance and consisting of 6 1/2" woofer 2" mid range and 1" tweeter. Ideal to work with the amplifier described above. Price per pair £30.00 Order ref 30P7

PERSONAL STEREO Customer returns but complete with a pair of stereo headphones very good value at £3.00 ref 3P63

2KV 500 WATT TRANSFORMERS Suitable for high voltage experiments or as a spare for a microwave oven etc. 250v AC input. £10.00 ref 10P93

MICROWAVE CONTROL PANEL. Mains operated, with touch switches. Complete with 4 digit display, digital clock, and 2 relay outputs one for power and one for pulsed power (programmable). Ideal for all sorts of precision timer applications etc. £6.00 ref 6P18

FIBRE OPTIC CABLE. Stranded optical fibres sheathed in black PVC. Five metre length £7.00 ref 7P29

12V SOLAR CELL. 200mA output ideal for trickle charging etc. 300 mm square. Our price £15.00 ref 15P42

PASSIVE INFRA-RED MOTION SENSOR. Complete with day light sensor, adjustable lights on timer (8 secs -15 mins), 50° range with a 90 deg coverage. Manual override facility. Complete with wall brackets, bulb holders etc. Brand new and guaranteed. £25.00 ref 25P24

Pack of two PAR38 bulbs for above unit £12.00 ref 12P43

VIDEO SENDER UNIT Transmits both audio and video signals from either a video camera, video recorder or computer to any standard TV set within a 100' range! (tune TV to a spare channel). 12v DC op. £15.00 ref 15P39

Suitable mains adaptor £5.00 ref 5P19

FM TRANSMITTER housed in a standard working 13A adapter (bug is mains driven). £26.00 ref 26P2

MINIATURE RADIO TRANSCIEVERS. A pair of walkie talkies with a range of up to 2 kilometres. Units measure 22x52x155mm. Complete with cases. £30.00 ref 30P12

FM CORDLESS MICROPHONE. Small hand held unit with a 500' range! 2 transmit power levels reqs PP3 battery. Tuneable to any FM receiver. Our price £15 ref 15P42A

10 BAND COMMUNICATIONS RECEIVER. 7 short bands, FM, AM and LW DX, local search, tuning eye, mains or battery. Complete with shoulder strap and mains lead. £34.00 ref 34P1

WHISPER 2000 LISTENING AID. Enables you to hear sounds that would otherwise be inaudible! Complete with headphones. Cased. £5.00 ref 5P179

CAR STEREO AND FM RADIO. Low cost stereo system giving 5 watts per channel. Signal to noise ratio better than 45db, wow and flutter less than .35%. Nec earth. £25.00 ref 25P21

LOW COST WALKIE TALKIES. Pair of battery operated units with a range of about 150'. Our price £8.00 a pair ref 8P50

7 CHANNEL GRAPHIC EQUALIZER plus a 60 watt power amp! 20-21KHZ 4-8R 12-14v DC negative earth. Cased. £25 ref 25P14

NICAD BATTERIES. Brand new top quality. 4 x AA's £4.00 ref 4P44. 2 x C's £4.00 ref 4P73. 4 x D's £9.00 ref 9P12. 1 x PP3 £6.00 ref 6P35

TOWERS INTERNATIONAL TRANSISTOR SELECTOR GUIDE. The ultimate equivalents book. Latest edition £20.00 ref 20P32

CABLE TIES. 142mm x 3.2mm white nylon pack of 100 £3.00 ref 3P104. Bumper pack of 1,000 ties £14.00

VIDEO AND AUDIO MONITORING SYSTEM



Brand new units consisting of a camera, 14cm monitor, 70 metres of cable, AC adapter, mounting bracket and owners manual. 240v AC or 12v DC operation complete with built in 2 way intercom. £119.00 ref 119P1

1991 CATALOGUE AVAILABLE NOW IF YOU DO NOT HAVE A COPY PLEASE REQUEST ONE WHEN ORDERING OR SEND US A 6"X9" SAE FOR A FREE COPY.

GEIGER COUNTER KIT. Complete with tube, PCB and all components to build a battery operated geiger counter. £39.00 ref 39P1

FM BUG KIT. New design with PCB embedded coil. Transmits to any FM radio. 9v battery req'd. £5.00 ref 5P158

FM BUG Built and tested superior 9v operation. £14.00 ref 14P3

COMPOSITE VIDEO KITS. These convert composite video into separate H sync, V sync and video. 12v DC. £8.00 ref 8P39

SINCLAIR C5 MOTORS. 12v 29A (full load) 3300 rpm 6" x 4" 1/4" O/P shaft. New. £20.00 ref 20P22

As above but with fitted 4 to 1 inline reduction box (800rpm) and toothed nylon belt drive cog £40.00 ref 40P6

SINCLAIR C5 WHEELS 13" or 16" dia including treaded tyre and inner tube. Wheels are black, spoked one piece poly carbonate. 13" wheel £6.00 ref 6P20. 16" wheel £6.00 ref 6P21

ELECTRONIC SPEED CONTROL KIT for c/s motor. PCB and all components to build a speed controller (0-95% of speed). Uses pulse width modulation. £17.00 ref 17P3

SOLAR POWERED NICAD CHARGER. Charges 4 AA nicads in 8 hours. Brand new and cased £6.00 ref 6P3.

MOSFETS FOR POWER AMPLIFIERS ETC. 100 watt mosfet pair 2SJ99 and 2SK343 £4.00 a pair with pin out info ref 4P51. Also available is a 2SK413 and a 2SJ118 at £4.00 ref 4P42

10 MEMORY PUSH BUTTON TELEPHONES. These are 'customer returns' so they may need slight attention. BT approved. £6.00 each ref 6P16 or 2 for £10.00 ref 10P77

12 VOLT BRUSHLESS FAN 4 1/2" square brand new ideal for boat, car, caravan etc. £5.00 ref 5P206

acorn data recorder ALF503. Made for BBC computer but suitable for others. Includes mains adapter, leads and book. £15.00 ref 15P43

VIDEO TAPES. Three hour superior quality tapes made under licence from the famous JVC company. Pack of 10 tapes £20.00 ref 20P20.

ELECTRONIC SPACESHIP. Sound and impact controlled, responds to claps and shouts and reverses when it hits anything. Kit with complete assembly instructions £10.00 ref 10P81



PHILIPS LASER. 2MW HELIUM NEON LASER TUBE. BRAND NEW FULL SPEC £40.00 REF 40P10. MAINS POWER SUPPLY KIT £20.00 REF 20P33 READY BUILT AND TESTED LASER IN ONE CASE £75.00 REF 75P4.

SWITCHED MODE POWER SUPPLY (Boshert) +5 at 15A, +12 at 3A, -12 at 2A, +24 at 2A. 220 or 110v input. Brand new £20.00 ref 20P30

SOLDER 22SWG resin cored solder on a 1/2kg reel. Top quality. £4.00 a reel ref 4P70

600 WATT HEATERS Ideal for air or liquid, will not corrode, lasts for years. coil type construction 3"x2" mounted on a 4" dia metal plate for easy fixing. £3.00 ea ref 3P78 or 4 for £10.00 ref 10P76

TIME AND TEMPERATURE MODULE. A clock, digital thermometer (Celsius and Fahrenheit (0-160 deg F) programmable too hot and too cold alarms. Runs for at least a year on one AA battery. £9.00 ref 9P5

Remote temperature probe for above unit £3.00 ref 3P60

GEARBOX KITS. Ideal for models etc. Contains 18 gears (2 of each size) 4x50mm axles and a powerful 9-12v motor. All the gears etc are push fit. £3.00 for complete kit ref 3P93

ELECTRONIC TICKET MACHINES. These units contain a magnetic card reader, two matrix printers, motors, sensors and loads of electronic components etc. (12"x12"x7") Good value at £12.00 ref 12P28

JOYSTICKS. Brand new with 2 fire buttons and suction feet these units can be modified for most computers by changing the connector etc. Price is 2 for £5.00 ref 5P174

QUALITY PANEL METERS. 50uA movement with 3 different scales that can be brought into view with a lever! £3.00 each ref 3P81

CATIONIZER KIT. Improve the air in your car! clears smoke and helps to reduce fatigue. Case required. £12.00 ref 12P8

METAL DETECTOR. Fun light weight device for buried treasure! 33" long with tune and fine tune controls. £10.00 ref 10P101

6V 10AH LEAD ACID sealed battery by yuasha ex equipment but in excellent condition now only 2 for £10.00 ref 10P95

12 TO 220V INVERTER KIT. As supplied it will handle up to about 15w at 220v but with a larger transformer it will handle 80 watts. Basic kit £12.00 ref 12P17. Larger transformer £12.00 ref 12P41

VERO EASI WIRE PROTOTYPING SYSTEM Ideal for designing projects on etc. Complete with tools, wire and reusable board. Our price £6.00 ref 6P33

MICROWAVE TURNTABLE MOTORS. Ideal for window displays etc. £5.00 ref 5P165

STC SWITCHED MODE POWER SUPPLY. 220v or 110v input giving 5v at 2A, +24v at 0.25A, +12v at 0.15A and +90v at 0.4A £12.00 ref 12P27

TELEPHONE AUTODIALERS. These units, when triggered will automatically dial any telephone number. Originally made for alarm panels. BT approved. £12.00 ref 12P23 (please state telephone no req'd)

25 WATT STEREO AMPLIFIER ic STK043. With the addition of a handful of components you can build a 25 watt amplifier. £4.00 ref 4P69 (Circuit dia included)

LINEAR POWER SUPPLY. Brand new 220v input +5 at 3A, +12 at 1A, -12 at 1A. Short circuit protected. £12.00 ref 12P21

MAINS FANS. Small type construction. Approx 4"x5" mounted on a metal plate for easy fixing. New £5.00 5P166

POWERFUL IONIZER KIT. Generates 10 times more ions than commercial units! Complete kit including case £18.00 ref 18P2

MINI RADIO MODULE. Only 2" square with ferrite aerial and tuner. Superhet. Req's PP3 battery. £1.00 ref BD716

HIGH RESOLUTION MONITOR. 9" black and white Philips tube in chassis made for OPD computer but may be suitable for others. £20.00 ref 20P26

SURFACE MOUNT KIT. Makes a high gain snooping amplifier on a PCB less than an inch square! £7.00 ref 7P15

SURFACE MOUNT SOLAR. In easy to use tube. Ideal for above project £12.00 ref 12P18

CB CONVERTORS. Converts a car radio into an AM CB receiver. Cased with circuit diagram. £4.00 ref 4P48

FLOPPY DISCS. Pack of 15 3 1/2" DSD £10.00 ref 10P88. Pack of 10 5 1/4" DSD £5.00 ref 5P168

SONIC CONTROLLED MOTOR. One click to start, two click to reverse direction, 3 click to stop! £3.00 each ref 3P137

FRESNEL MAGNIFYING LENS. 83 x 52mm £1.00 ref BD827.

LCD DISPLAY. 4 1/2 digits supplied with connection data £3.00 ref 3P77 or 5 for £10.00 ref 10P78

ALARM TRANSMITTERS. No data available but nicely made complex transmitters 9v operation. £4.00 each ref 4P81

100M REEL OF WHITE BELL WIRE. figure 8 pattern ideal for intercoms, door bells etc £3.00 a reel ref 3P107

ULTRASONIC LIGHT. This battery operated unit is ideal for the shed etc as it detects movement and turns a light on for a preset time. (light included). Could be used as a sensor in an alarm system. £14.00 each ref 14P8

CLAP LIGHT. This device turns on a lamp at a finger 'snap' etc. nicely cased with built in battery operated light. Ideal bedside light etc. £4.00 each ref 4P82

ELECTRONIC DIPSTICK KIT. Contains all you need to build an electronic device to give a 10 level liquid indicator. £5.00 (ex case) ref 5P194

UNIVERSAL BATTERY CHARGER. Takes AA's, C's, D's and PP3 nicads. Holds up to 5 batteries at once. New and cased, mains operated. £8.00 ref 8P36

ONE THOUSAND CABLE TIES! 75mm x 2.4mm white nylon cable ties only £5.00 ref 5P181

PC MODEMS 1200/75 baud modems designed to plug into a PC complete with manual but no software £18.00 ref 18P12

ASTEC SWITCHED MODE POWER SUPPLY. 80mm x 165mm (PCB size) gives +5 at 3.75A, +12 at 1.5A, -12 at 0.4A. Brand new £12.00 ref 12P39

VENTILATED CASE FOR ABOVE PSU with IEC filtered socket and power switch. £5.00 ref 5P190

IN CAR POWER SUPPLY. Plugs into cigar socket and gives 3.4, 5, 6.7, 5.9, and 12v outputs at 800mA. Complete with universal spider plug. £5.00 ref 5P167

CUSTOMER RETURNED switched mode power supplies. Mixed type, good for spares or repair. £2.00 each ref 2P292

DRILL OPERATED PUMP. Fits any drill and is self priming. £3.00 ref 3P140

PERSONAL ATTACK ALARM. Complete with built in torch and vanity mirror. Pocket sized, req's 3 AA batteries. £3.00 ref 3P135

POWERFUL SOLAR CELL 1AMP .45 VOLT! only £5.00 ref 5P192 (other sizes available in catalogue)

SOLAR PROJECT KIT. Consists of a solar cell, special DC motor, plastic fan and turntables etc plus a 20 page book on solar energy! Price is £8.00 ref 8P51

RESISTOR PACK. 10 x 50 values (500 resistors) all 1/4 watt 2% metal film. £5.00 ref 5P170

CAPACITOR PACK 1. 100 assorted non electrolytic capacitors £2.00 ref 2P286

CAPACITOR PACK 2. 40 assorted electrolytic capacitors £2.00 ref 2P287

QUICK CUPPA? 12v immersion heater with lead and cigar lighter plug £3.00 ref 3P92

LED PACK. 50 red leds, 50 green leds and 50 yellow leds all 5mm £8.00 ref 8P52

FERRARI TESTAROSSA. A true 2 channel radio controlled car with forward, reverse, 2 gears plus turbo. Working headlights. £22.00 ref 22P6

ULTRASONIC WIRELESS ALARM SYSTEM. Two units, one a sensor which plugs into a 13A socket in the area you wish to protect. The other, a central alarm unit plugs into any other socket elsewhere in the building. When the sensor is triggered (by body movement etc) the alarm sounds. Adjustable sensitivity. Price per pair £20.00 ref 20P34. Additional sensors (max 5 per alarm unit) £11.00 ref 11P6

TOP QUALITY MICROPHONE. Unidirectional electret condenser mic 600 ohm sensitivity 16-18khz built in chime complete with magnetic microphone stand and mic clip. £12.00 ref 12P42

WASHING MACHINE PUMP. Mains operated new pump. Not self priming. £5.00 ref 5P18

IBM PRINTER LEAD. (D25 to centronics) 2 metre parallel. £5.00 ref 5P186

COPPER CLAD STRIP BOARD. 17" x 4" of 1" pitch 'vero' board. £4.00 a sheet ref 4P62 or 2 sheets for £7.00 ref 7P22

STRIP BOARD CUTTING TOOL. £2.00 ref 2P352

3 1/2" disc drive. 720K capacity made by NEC £60.00 ref 60P2

TV LOUDSPEAKERS. 5 watt magnetically screened 4 ohm 55 x 125mm. £3.00 a pair ref 3P109

TV LOUDSPEAKERS. 3 watt 8 ohm magnetically screened 70 x 50mm. £3.00 a pair ref 3P108

BBC TRACKBALLS Once again in stock only £4.00 ref 4P86

CROSS OVER NETWORKS 8 ohm 3 way Japanese made units. Excellent units available at only £2.00 for a pair! ref 2P363

SPEAKER GRILLS. set of 3 matching grills of different diameters. 2 packs for £2.00 (6 grills) ref 2P364

50 METRES OF MAINS CABLE £3.00. 2 core black precut in convenient 2 m lengths. Ideal for repairs and projects. ref 3P91

4 CORE SCREENED AUDIO CABLE 24 METRES £2.00. Precut into convenient 1 2 m lengths. Ref 2P365

TWEETERS 2 1/4" DIA 8 ohm mounted on a smart metal plate for easy fixing £2.00 ref 2P366


COMPUTER MICE Originally made for Future PC's but can be adapted for other machines. Swiss made £8.00 ref 8P57. Atari ST conversion kit £2.00 ref 2P362

6 1/2" 20 WATT SPEAKER Built in tweeter 4 ohm £5.00 ref 5P205

5" X 3" 16 OHM SPEAKER 3 for £1.00! ref CD213

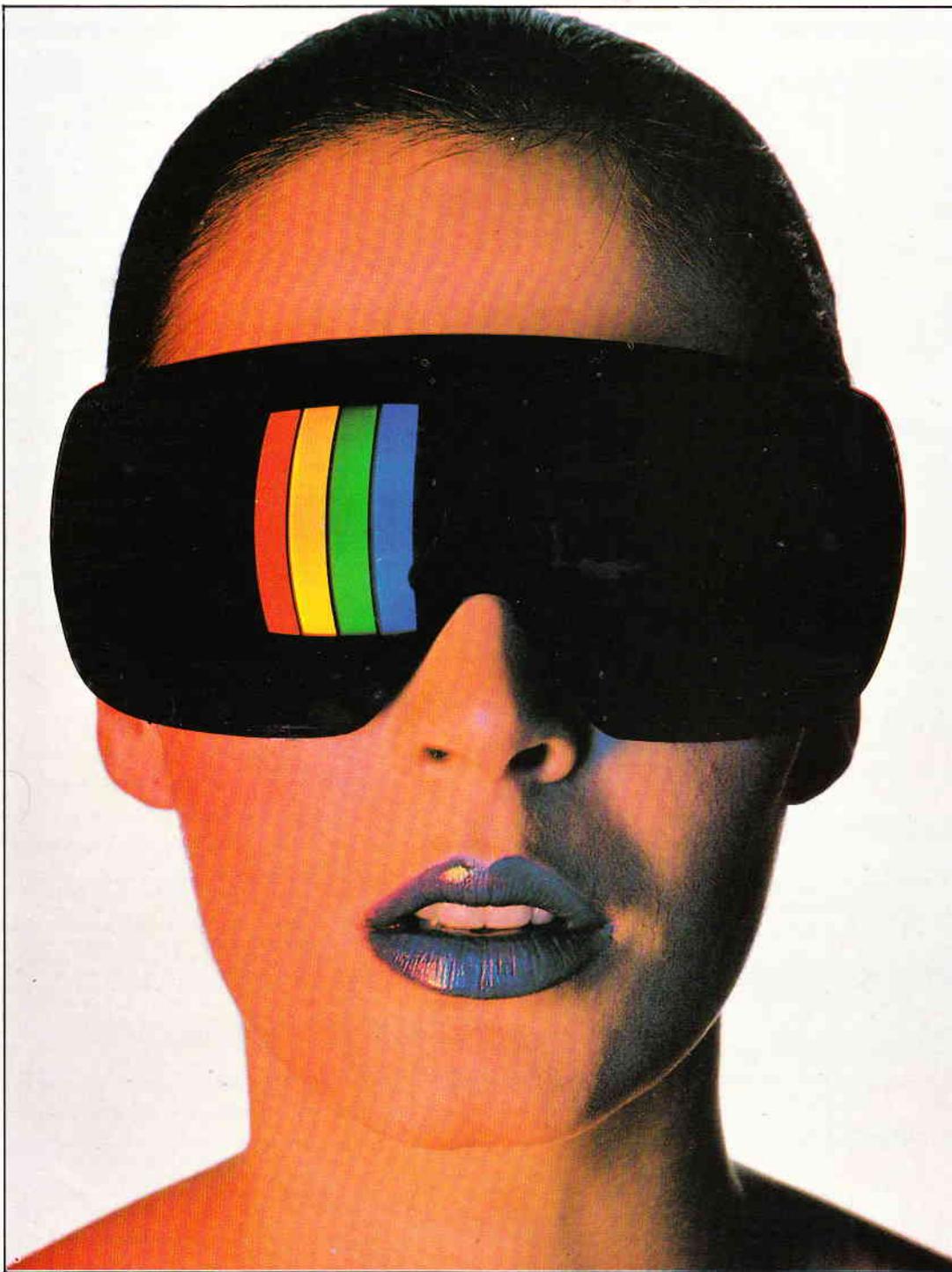BULL ELECTRICAL
 250 PORTLAND ROAD HOVE
 SUSSEX BN3 5QT DEPT ETI
 TELEPHONE 0273 203500
 MAIL ORDER TERMS: CASH PO OR CHEQUE
 WITH ORDER PLUS £2.50 POST
 FAX 0273 23077





NICAM!

...set your sights on a better sound!

Experience a new sensation. An experience that opens up a whole new spectrum of sound.

Put yourself on stage at the Albert Hall, surrounded by a great orchestra. Imagine the sound you will hear, every nuance, every note; or travel up the Nile with an intrepid explorer, a journey not only full of breathtaking beauty and colour, but rich in the sounds of another continent; or capture the hidden gasps of 100,000 hardened fans at Wembley for the F.A. Cup Final, when the ball skims the crossbar with the last kick of the match; follow with your ears as well as your eyes, dodging the bullets, as your favourite hero battles out of yet another tight corner, it's just like being in a cinema!

Nicam hi-fi stereo will turn your living-room into a living room of

sound! You don't settle for second best with television picture quality, why settle for second best in television sound quality? Nicam sound is the new high quality digital stereo sound system, pioneered by BBC, ITV and TV/video manufacturers. In fact so good is Nicam it is comparable to the superb sound reproduction of the compact disc, when played through your existing hi-fi arrangement. If your television hasn't got a built-in Nicam decoder, you will need the Maplin Nicam Tuner System. Ultimately almost all of your favourite programmes will be broadcast in superb hi-fi quality stereo-sound. Without a Maplin Nicam Tuner you won't be able to capture every sound to its full.

Nicam hi-fi stereo. Catch your breath, open your eyes, and pin back your ears! It's what your hi-fi system was made for... It's what your ears are made for!

DIGITAL STEREO TV SOUND FROM YOUR HI-FI

The complete kit contains all the components required to build the unit. However you will also need: a power supply, 12V at 600mA regulated e.g. Y221X at £8.95; a co-ax Y adaptor e.g. FS23A at £1.20; a co-ax lead to connect to your TV or video; RW36P 2m long at £1.28, JW39N 5m long at £1.98, or JW40T 10m long at £2.95; a phono lead to connect to your hi-fi e.g. RW50E at 98p or a SCART/Peritel lead JW36P at £4.95. An infra-red remote control kit is also available LP20W at £29.95.

Complete kit LP19V only £139.95 incl. VAT + £1 mail-order handling charge.



Maplin ELECTRONICS

**CREDIT CARD HOTLINE
0702 554161**

For a friendly welcome and the very best of service why not visit our shops in Birmingham, Brighton, Bristol, Leeds, London (Edgware and Hammersmith), Manchester, Newcastle-upon-Tyne, Nottingham, Reading, Southampton and Southend-on-Sea.

Subject to availability. Prices subject to change.



Digital stereo sound companion for your TV set.