

ETI
ELECTRONICS
TODAY INTERNATIONAL

TOMORROW'S
TECHNOLOGY TODAY

6
PROJECTS
FOR YOU TO BUILD

THE ART OF ANIMATRONICS THE SCIENCE OF ROBOTICS



BUILD THE PALESAVER SPEAKER ATTENUATOR
DIGITAL SHUTTER TIMER FOR PHOTOGRAPHERS
BUILD A BRAKE LIGHT MONITOR
THE MYSTERIES OF RS-232 COMMUNICATIONS

May 1994 £1.95


BEST VALUE
Argus
SPECIALIST
PUBLICATION



At last, a fully functional upgradeable PCB CAD system to suit any budget. Substantial trade-in discounts are available against other "professional" PCB design packages ...

... call now for details.

Board Capture

Schematic Capture Design Tool

£395

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

Board Maker

BoardMaker1 - Entry level


£95

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount and metric support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

BoardMaker2 - Advanced level

£295

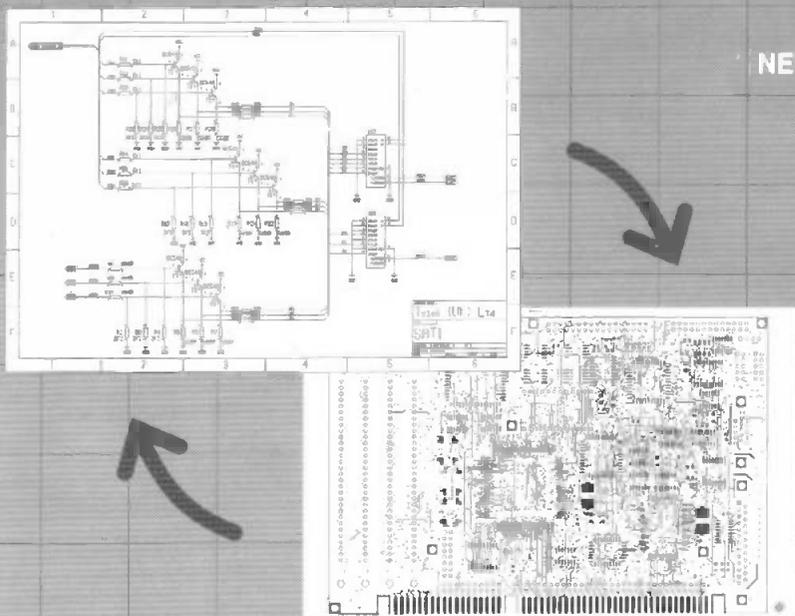- All the features of BoardMaker1 +
- Full netlist support - BoardCapture, OrCad, Schema, Tango, CadStar and others
- Full Design Rule Checking both mechanical and electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC



NEW

Board Router

Gridless re-entrant autorouter

£200

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing


Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill and Annotated drill drawings (BM2)

Call, write or fax for more information
or a full evaluation kit

Tsien (UK) Limited
Aylesby House
Wenny Road, Chatteris
Cambridge
PE16 6UT


Tel (0354) 695959
Fax (0354) 695957

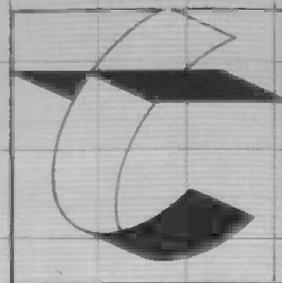

tsien



Contents

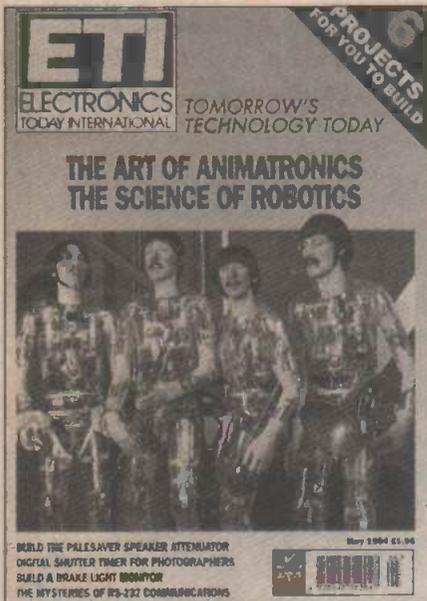

**Volume 23 No.5
May 1994**

Features & Projects

Animatronics Today - Robotics Tomorrow? 14

A look at how the technology used to create sophisticated moving characters, for use in theme parks, is converging with the technology used in building the next generations of free moving robots



Brake Light Monitor 18

Are your brake lights working properly? This project from Terry Balbyrne makes testing them easy

An Experimenter's Computer 22

Part 2 of Jim Spence's project to build a Z-80 based computer, especially designed for experimenters. This month we look at programming the computer using the Forth language and a full listing of the more common Forth commands and their use

Digital Shutter Timer 34


A useful little circuit, from Robert Penfold, to enable photographers to generate accurate timed exposures

Palesaver Load/Attenuator 42

This useful little unit, designed by Dave Bradshaw, acts as a flexible loudspeaker attenuator and as an accurate 8 ohm load

Turning a PC into a Chart Recorder 46

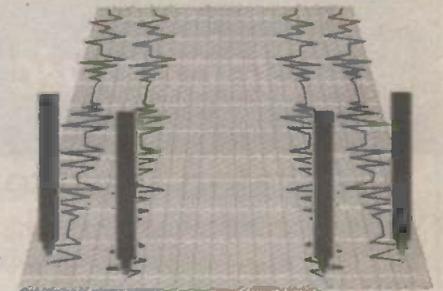In Part 2 of Keith Garwell's project to turn a PC into a virtual chart recorder we look at the control software



Computer Communications and RS232 52

A detailed look at parallel and serial data communications between a microprocessor and a peripheral, with particular emphasis on serial RS232C communications. Also, a special section on how to make your own computer cables




Regulars

News	6
PCB Foils	63
Open Forum	66



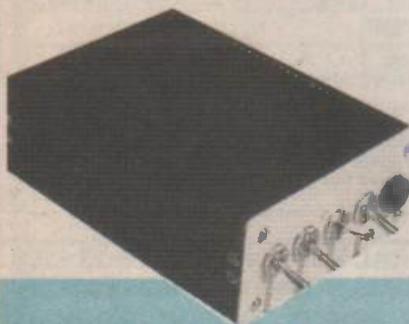**Project
An Experimenter's Computer
42**



**Project
Palesaver Load/Attenuator
42**




Subscribe & Save

Phone the hotline and take advantage of our special offer detailed on page 43

EASY-PC, Schematic and PCB CAD

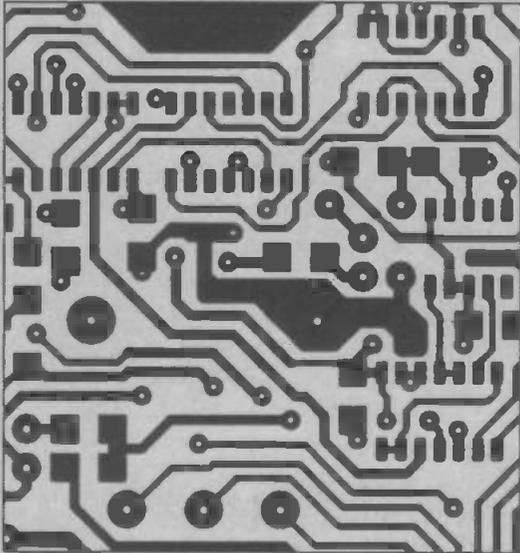
Over 18,000 Installations
in 80 Countries World-wide!



- Runs on:- PC/XT/AT/ 286/ 386/ 486 with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design:- Single sided, Double sided and Multi-layer (8) boards.
- Provides full Surface Mount support.
- Standard output includes Dot Matrix / Laser / Ink-jet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Tech Support - free.
- Superbly easy to use.

**Still
Only
£98.00!**
Plus P&P+VAT



**BRITISH
DESIGN
AWARD
1989**

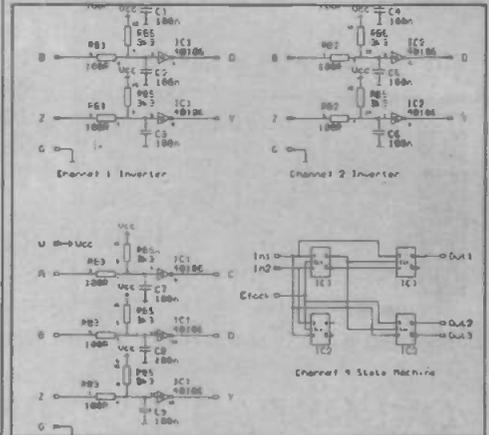


Options:-500 piece Surface Mount Symbol Library £48,
1000 piece Symbol Library £38, Gerber Import facility £98.

Electronic Designs Right First Time?

Integrated Electronics CAD

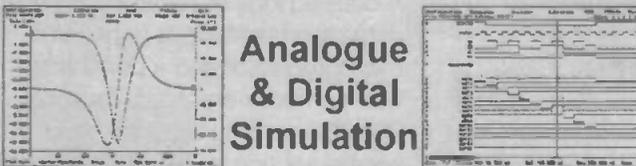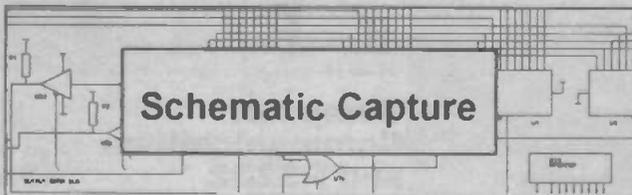

Analogue
& Digital
Simulation

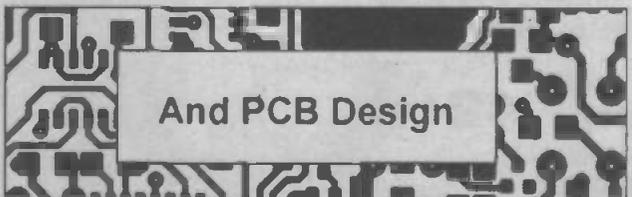

And PCB Design

Prices from UK£195 / US\$375

Affordable Electronics CAD

EASY-PC: Entry level PCB and Schematic CAD.	\$195.00	£98.00
EASY-PC Professional: Schematic Capture and PCB CAD. Links directly to ANALYSER III and PULSAR.	\$375.00	£195.00
PULSAR: Digital Circuit Simulator ~ 1500 gate capacity.	\$195.00	£98.00
PULSAR Professional: Digital Circuit Simulator ~ 50,000 gate capacity.	\$375.00	£195.00
ANALYSER III: Linear Analogue Circuit Simulator ~ 130 node capability	\$195.00	£98.00
ANALYSER III Professional: Linear Analogue Circuit Simulator ~ 750 node capability.	\$375.00	£195.00
Z-MATCH for Windows: NEW Windows based Smith-Chart program for RF Engineers.	\$475.00	£245.00
<small>We operate a no penalty upgrade policy. You can upgrade at any time to the professional version of a program just for the difference in price.</small>	<small>US\$ prices include Post and Packing</small>	<small>UK£ prices exclude P&P and VAT</small>

For full information, please write, phone or fax:-

Number One Systems

UK/EEC: Ref. ETI, HARDING WAY, ST.IVES, CAMBS., ENGLAND, PE17 4WR.

Telephone UK: 0480 461778 (7 lines) Fax: 0480 494042 International +44 480 461778

USA: Ref. ETI, 1795 Granger Avenue, Los Altos, CA 94024

Telephone/Fax: (415) 968 9306

- TECHNICAL SUPPORT FREE FOR LIFE
- PROGRAMS NOT COPY PROTECTED.
- SPECIAL PRICES FOR EDUCATION.

ACCESS, MASTERCARD, VISA Welcome.


Low cost data acquisition for IBM PCs & compatibles


PICO TECHNOLOGY

A unique range of easy to use data acquisition products designed for use with IBM compatible computers. Combined with the software they allow your PC to be used as a host of useful test and measurement instruments, or as an advanced data logger.


Installed in seconds they simply plug into the parallel port (except the ADC-16 which connects to the serial port). They are self contained, require no power supply and take up no expansion slots.


Each device comes with a comprehensive manual. C, Pascal and Basic drivers are included for users who wish to write their own software. Software supplied on 3.5" disk.

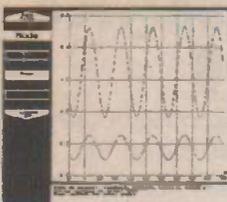PicoScope 'Virtual instrument' software package. Storage oscilloscope with trigger, timebase, rulers and offset functions. Realtime spectrum analysis with min/max frequency and signal averaging. Multiple meters on screen (digital and bargraph).

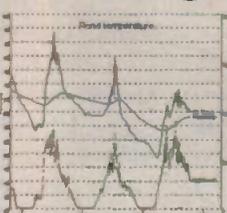 Scope, voltmeter, spectrum analyser
 Printer and file handling support


PicoLog Collect, store, display and print data from 1 sample per ms to 1 per day. Record average, min/max values or scaled values (linear, equation, table look up). Report types: monitor (with min/max alarms), y-t graphs, x-y graphs, tabulation.

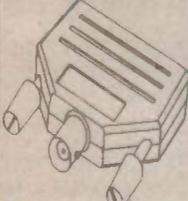 Advanced datalogging software package

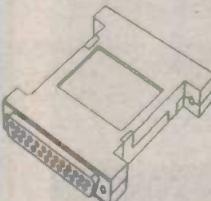OVERSEAS DISTRIBUTORS WANTED: TEL +44 954 211405 FAX +44 954 211880

ADC-10 single channel 8 bit
 Up to 24kHz sampling rate from a 386/33MHz machine
 0-5V Input range
 BNC input connector allows use of standard scope probes
 30V overload protection
 Parallel port connection


ADC-11 eleven channel 10 bit
 Up to 18kHz sampling rate from a 386/33MHz machine
 0-2.5V Input range
 Digital output
 D25 input connector
 30V overload protection
 Parallel port connection

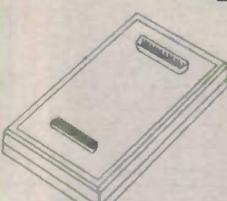
ADC-12 single channel 12 bit
 Up to 18kHz sampling rate from a 386/33MHz machine
 0-5V Input range
 BNC input connector allows use of standard scope probes
 30V overload protection
 Parallel port connection


ADC-16 eight channel 16 bit
 Software selectable single ended or differential inputs
 Resolution programmable between 8 (200Hz sampling) and 16 bits + sign (2Hz)
 ±2.5V input range
 Connects to serial port


Typical application	ADC	ADC	ADC	ADC
	-10	-11	-12	-16
Oscilloscope	●	●	●	
Voltmeter	●	●	●	●
Spectrum analyser	●	●	●	
Audio sampling	●	●	●	
Chart recorder emulation		●		●
Temperature measurement	●	●	●	●
Pressure measurement	●	●	●	●
Automotive monitoring		●		●
Medical research		●	●	●
Education	●	●	●	●

Prices

ADC-10 with PicoScope	£49
ADC-10 with PicoScope and PicoLog	£59
ADC-11 with PicoScope	£85
ADC-11 with PicoScope and PicoLog	£95
ADC-12 with PicoScope	£85
ADC-12 with PicoScope and PicoLog	£95
ADC-16 with PicoLog	£109
PicoLog (for ADC-10/11/12)	£25
Oscilloscope probes (x1 x10)	£10
UK carriage free, overseas carriage	£6



Pico Technology Ltd. Broadway House, 149 -151 St Neots Road, Hardwick, Cambridge. CB3 7QJ.


TEL: 0954-211716 FAX: 0954-211880



Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT.

ETI NEWS

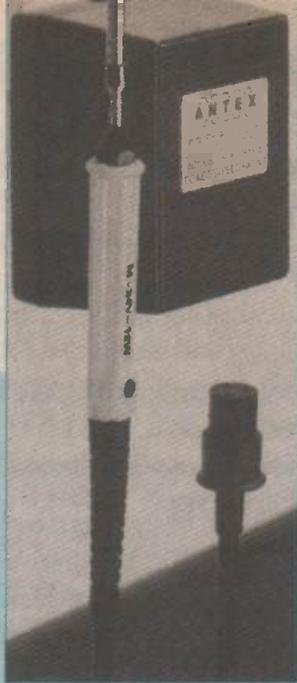
New 24V plug in power supply for soldering irons



Many soldering iron users require 24V power supply for operator safety. Now, any 24V soldering iron (up to 25W) can be used with the new Antex low cost plug in power supply. It is a 24V power supply which simply plugs into a standard mains socket, saving valuable bench space and avoiding trailing leads to a transformer.

Even if your work bench has a 24V power supply already installed, this new single plug-in unit allows much greater user flexibility.

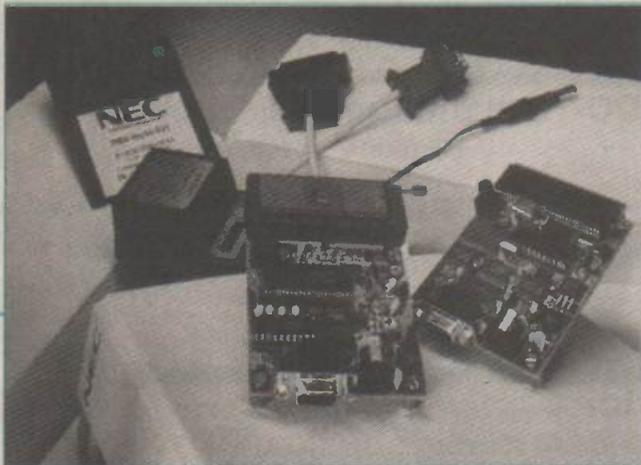
For further information contact Antex, of Tavistock, on 0822 613565.



Low cost micro- controller design kit

NEC Electronics has reduced the cost of designing embedded systems twentyfold with the introduction of a starter kit for just £300. The low cost starter kit contains everything an engineer needs to design systems based on NEC's popular 78K0 range of 8-bit microcontrollers, at a fraction of the price of the full design kit.

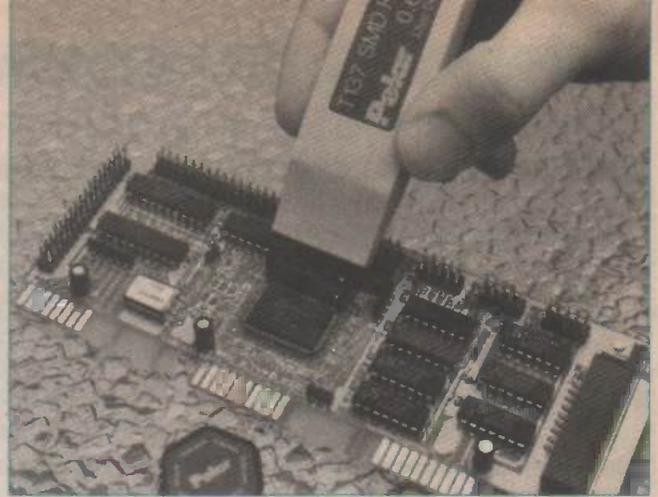It is intended for use by small engineering firms, design consultancies in development projects and by larger firms that wish to evaluate the devices. It includes an assembler and debugger (for use on an IBM compatible PC), an evaluation board with 32k of RAM, a programmer for UV and one time programmable (OTP) devices, a UV erasable 78K0 microcon-



Simplifying service testing

A major advance in fault diagnostics technology for service testing has been launched by Polar Instruments. The company's new T4000 family of analogue signature analysers (ASAs) utilise PC technology to automate V/I trace signature capture, storage and comparison. These new instruments put automated ASAs within the reach of all, thanks to the incorporation of cost effective, software based, virtual instrument techniques which dispense with conventional front panel electronics.

Using a friendly PC interface, signature files can be learnt and stored quickly for auto comparison at any future point. This eliminates the need for expert knowledge of the circuit under test and speeds component level diagnostics, allowing companies to implement far more cost effective maintenance and repair strategies.

ASA is based on impedance signatures, which are the response of circuit nodes to current limited AC stimuli. They provide an accurate guide to in-circuit behaviour, suitable for establishing the functionality of passive and active devices, including digital, analogue and mixed signal ICs, in rework/repair applications. IC complexity is immaterial - the technique is as relevant to complex ASICs and VLSIs as it is to analogue voltage regulators. Moreover, because ASA does not require boards to be powered up, it is intrinsically safe and easy to use.

For more information contact Polar Instruments Ltd, of Guemsey, on 0481 53081.

troller and all the necessary cables and power supplies.

The designer can therefore write code and perform three levels of prototyping. Firstly, the code can be downloaded into the RAM on a stand-alone evaluation board. The evaluation board can also be connected to the target hardware, enabling users to debug code in a fully functional prototyping system. The full screen debugger allows real time execution, single step operation, multiple break points and watching and modifying memory.

When testing is complete, the UV erasable device can be programmed and plugged directly into the prototype system, for example for field testing. Any bugs detected at this stage can be modified and the new code blown into the erased UV device. The programmer board can also be used to program OTP devices, which can then be used for short production runs, perhaps to produce prototypes for key customers.

The only equipment the user of this development system requires is a PC and a UV eraser.

For further information contact NEC Electronics UK Ltd at Cygnus House, Linford Wood Business Centre, Sunrise Parkway, Linford Wood, Milton Keynes MK14 6NP.

Home theatre speakers

The new Cerwin-Vega HTE-10 SenSurround! (tm) Home Theatre System brings the impact of 'Cinema Sound' into the home. Although relatively compact, the system is said to have tremendous dynamic punch and awesome bass. The speakers use the technology that added heightened reality to such blockbuster movies as Earthquake and Midway. The HTE-10 system consists of four identical compact surround speakers, one 'point source' centre channel and a dual voice-coil 10in sub-woofer. With the

sub-woofer behind the sofa and the other speakers tucked away, the system can be very unobtrusive.


To generate the cinema type sound, the speaker system needs to deliver high volume (when required), deep bass, strong dynamics and an enveloping sound-field. The HTE-10 does all

this and the design allows owners of modestly powered mid-price AV receivers and amplifiers to get the dynamic sound that is normally the sole province of powerful expensive amplification.

The HTE-10 is designed to be part of a Dolby Pro-Logic set up. Each speaker has a high sensitivity of 91dB (sub-

woofer 93dB) at 8 ohms. The four satellites and the centre channel are voiced to produce consistent vocal clarity, are overload protected and are fully magnetically shielded. The elliptical source point driver in the centre channel offers coherency in the critical mid-band. All the tweeters are Ferro-fluid cooled dome designs and the sub-woofer uses a dual voice-coil driver with a cast alloy frame, tuned to 40Hz for a deep powerful bass. All the speakers use quality 4mm cable connectors.

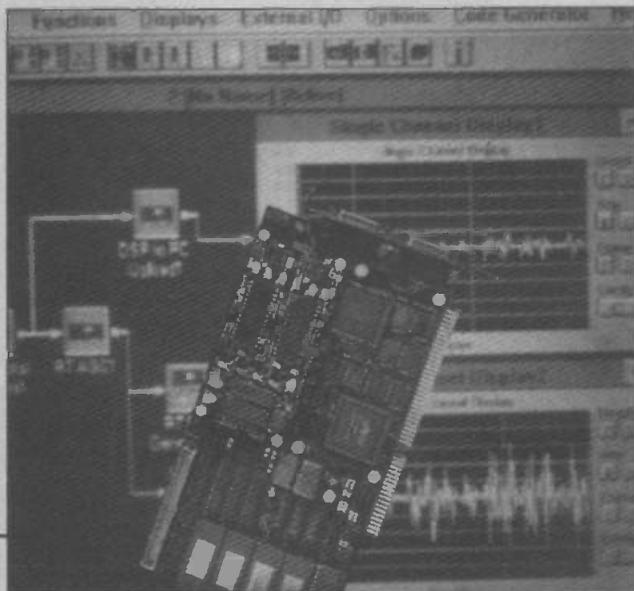The HTE-10 system has a recommended retail price of £499. For further details contact Cerwyn Vega on 0423 359054.




World's first 40MHz TMS320C31 PC board

Loughborough Sound Images has launched the world's first PC board based on the Texas Instruments' TMS320C31 digital signal processor, running at 40MHz. This plug in PC board combines 40MFLOPS of 32-bit real time processing power with high level development support and flexible I/O options. These features mean that, in addition to its role as a development system, it will be used in OEM applications as a target system.

Designers working in applications areas such as telecomms., embedded control, noise and vibration, digital audio and aerospace could benefit from the board's real time performance. It can interface with a wide variety of external signals, via LSI's existing daughter modules, including A/D and D/A conversion, at a range of speeds and resolutions, as well as an industry standard AES/EBU interface for digital audio applications.

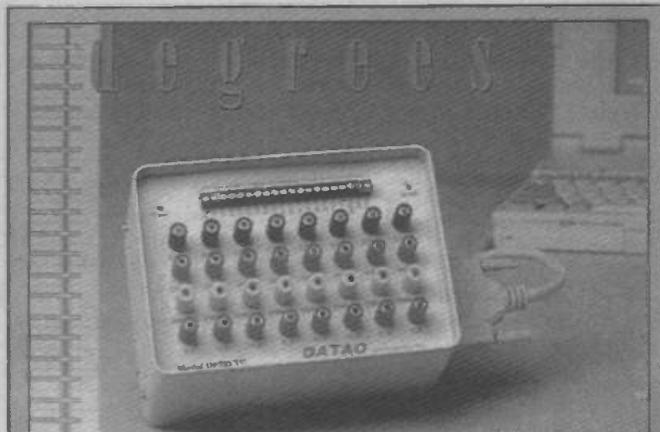For further details contact Loughborough Sound Images on 0509 231843.



Portable data acquisition

Keithley Instruments has introduced a 12-bit, 16-channel portable data acquisition system that is particularly well suited for thermocouple based temperature measurement, as well as any other type of analogue signal input.

The new DI-221TC allows users to connect up to 16 grounded thermocouples or other analogue inputs, in any desired combination, via a built in signal I/O panel. A sensor, attached to the signal termination receptacles on the DI-221TC's printed circuit board, provides cold junction compensation.

This unit linearises thermocouple signals in real time, with DSP based 10th order polynomial calculation software. Thermocouple voltage signals are automatically converted to temperature measurements in the user's choice of ranges - +/-1200C or +/-120C. This polynomial calculation software also allows users to linearise signals from other types of non-linear transducers.

The DI-221TC can be plugged into the parallel (printer) port of any PC compatible computer, be it a portable or a desktop machine. An internal battery means that it does not draw any power from the computer, an important consideration when using a portable PC.

For further information, contact Keithley Instruments Ltd; of Reading, on 0734 575666.

EXPRESS COMPONENTS

MAINS IONIZER KIT. Very useful kit that increases the flow of negative ions, helps clear cigarette smoke, dust, pollen etc. Helps reduce stress and respiratory problems. £15. kit, £20 built.

COMBINATION LOCK. Electronic 9 key combination lock suitable for alarms, cars, houses etc, easily programmable. Includes mains 2A relay o/p. 9v operation. £10 kit, £14 built.

VARIABLE POWER SUPPLY. Stabilized, short circuit protected. Gives 3-30v DC at 2.5A, ideal for workshop or laboratory. £14 kit, £18 built. 24VAC required.

LEAD ACID CHARGER. Two automatic charging rates (fast and slow), visual indication of battery state. Ideal for alarm systems, emergency lighting, battery projects etc. £12 kit, £16 built.

PHONE LINE RECORDER. Device that connects to the 'phone line and activates a cassette recorder when the handset is lifted. Ideal for recording 'phone conversations etc. £8 kit, £12 built.

ROBOT VOICE. Turns your voice into a robot voice! answer the phone with a different voice! £9 kit, £13 built.

PHONE BUG DETECTOR. This device will warn you if somebody is eavesdropping on your 'phone line. £6 kit £9 built.

PHONE BUG. Small bug powered by the telephone line. Only transmits when the phone is used. Popular surveillance product. £8 kit, £12 built.

STROBE LIGHT. Bright strobe light with an adjustable frequency of 1-60hz. (a lot faster than conventional strobes!) £16 kit, £20 built.

4W FM TRANSMITTER. 3 RF stages, audio preamp. 12-18vDC. Medium powered bug £20 kit, £28 built.

3 CHANNEL LIGHT CHASER. 3x 800w output, speed and direction controls, can be used with 12 led's (supplied) or TRIACS for mains lights (also supplied). 9-15v DC. £17 kit, £23 built.

25W FM TRANSMITTER. 4 stage, a preamp will be required. (Our preamp below is suitable) £79 built. (no kits).

SOUND EFFECTS GENERATOR. Produces any thing from bird chips to sirens! add sounds to all sorts of things £9 kit £13 built.

FM/AM SCANNER. Well not quite, you have to turn the knob yourself but you will hear things on this radio (even TV) that you would not hear on an ordinary radio! A receiver that covers 50-160MHZ both AM and FM. Built in 5w amplifier. £15 kit, £20 built.

CAR ALARM SYSTEM. Works on vibration and/or voltage drop from door etc being opened. Entry and exit delays plus adjustable alarm duration. Low cost protection! £12 kit, £16 built.

15W FM TRANSMITTER. 4 stage, high power bug. You will need a preamp for this (see our preamp below which is ok) £69 built. (no kits).

1W FM TRANSMITTER. 2 stage including preamp and mic. Good general purpose bug. 8-30VDC. £12 kit, £16 built.

50 IC's for £1.50
Nice mix of chips at a bargain price!

CERAMIC CAPACITOR PACK
Good mixed pack of 100 capacitors for just £1.00

ELECTROLYTIC PACK 1
100 small mixed electrolytic capacitors just £1.00

ELECTROLYTIC PACK 2
50 larger electrolytic mixed capacitors

RESISTOR PACK NO 1
250 low wattage resistors, ideal for most projects etc. Just £1.00

RESISTOR PACK NO 2
Hi wattage pack, good selection of mixed wattages and values 50 in all, bargain price just £1.00

PRESET PACK
Nice selection of 25 mixed preset pots for just another £1!

RELAY PACK NO 1
6 mixed relays for £1, that's just 17p each.

CONNECTOR PACK
10 different connectors, again for £1

FUSE PACK NO 1
40 mixed 20mm fuses, ideal for repairs etc, or just to stock up the spares box! Just £1.00

FUSE PACK NO 2
30 mixed 1.25" fuses again ideal for spares etc. Just £1.00

WIRE PACK
25 Metres of insulated wire for just £1.00, good for projects etc.

SLEEVING PACK
100 assorted pieces of sleeving for connectors etc. Yours for just £1.00

DIODE PACK
100 assorted diodes for just £1.00

LED PACK
20 light emitting diodes for £1.00

TRANSISTOR PACK
50 mixed transistors, another bargain at £1.00

BUZZER PACK
10 things that make a noise for just £1.00!

POT PACK
10 pots for £1, (5 different types) a snip at £1.00

DISPLAYS
10 seven segment displays for £1.00

ORDER 10 PACKS OR MORE AND CHOOSE ONE FREE PACK!!

FREE COMPONENT CATALOGUE WITH EVERY ORDER!!

BULK PACKS

99p
Post

KITS 'N MODULES

PREAMP MIXER. 3 channel input, independent level and tone controls. Ideal for use with the hi power FM transmitters. £15 kit, £19 built.

TREMBLER ALARM. Designed for bikes etc, adjustable sensitivity, preset alarm time, auto reset. Could be adapted for all sorts of "borrowable" things £12 kit, £16 built.

ULTRASONIC RADAR. A project that can be used as a movement detector in an enclosed space. Range about 10 metres, 12vDC. Good basis for car, shed, caravan alarm etc. £14 kit, £19 built.

PHONE CALL RELAY. Very useful kit that incorporates a relay that operates when the phone rings. Can be used to operate more bells, signalling lights etc. Good for noisy environments or if you have your headphones on! £10 kit, £14 built.

PORTABLE ALARM SYSTEM. Small 9v alarm system based on a mercury switch. The alarm continues to sound until disabled by the owner. Buzzer included. £11 kit £15 built.

800W MUSIC TO LIGHT EFFECT. Add rhythm to your music with this simplesound to light kit. £8 kit, £12 built.

MOSQUITO REPELLER. Modern way to keep the midges away! Runs for

about a month on one 1.5v battery. Frequency is set to drive away mosquitos etc. £7 kit, £11 built.

3 CHANNEL SOUND TO LIGHT. Can be used anywhere as no connection is made to hi fi. Separate sensitivity controls for each channel. 1,200W power handling. Microphone included. £14 kit, £19 built.

MINI METAL DETECTOR. Detects pipes, wires etc up to 20cm deep. Useful before you drill those holes! £8 kit, £12 built.

0-5 MINUTE TIMER. Simple time switch adjustable from 0-5 mins, will switch 2A mains load. 12v op. Ideal for laboratory, photographic projects etc. £7 kit, £11 built.

7 WATT III FI AMPLIFIER. Useful, powerful amplifier 20hz-15hz, 12-18vdc. Good for intercoms, audio systems, car etc. £7 kit £11 built.

INCAR SOUND TO LIGHT. Put some atmosphere in your car with this kit. Each channel has 6 led's that create a beautiful lighting effect! £10 kit, £14 built.

VOX SWITCH. This is a sound activated switch, ideal for use on transmitters, CB's, tape recorders etc. Adjustable sensitivity, built in delay. Mic input. £7 kit, £11 built.

LIQUID LEVEL DETECTOR. Useful item, can be used to detect fluid levels in watertanks, baths, ponds fish tanks etc. Could also be used as rain alarm with an easily constructed sensor. £5 kit, £9 built.

FM TRANSMITTER. Mini FM transmitter 2 transistor, comes with FET miniature mic and is tuneable from 63 to 130MHZ. £7 kit, £11 built.

FUNCTION GENERATOR. Generates sinusoidal, saw tooth and square waveforms from 20hz up to 20khz. Separate level controls for each waveform. 24vac. £15 kit, £20 built.

5 WATT SIREN. Powerful siren kit with an impressive 5 watts output. Ideal for alarms etc. £6 kit £10 built.

TELEPHONE AMPLIFIER. Very sensitive amplifier which using a 'phone pickup coil (supplied) will let you fol-

low a telephone conversation without holding the handset to your ear! £11 kit £15 built.

SWITCH PACK
10 switches for just £1.00

12v FLOURESCENT. A useful kit that will enable you to light large flourescent tubes from your car battery etc. 9v mains transformer required. £8 kit, £12 built.

KNOB PACK
10 knobs for just £1.00

REMEMBER! YOUR FREE COPY OF OUR CUT PRICE COMPONENTS CATALOGUE SENT WITH EVERY ORDER!!!

How to place your order.....

By phone.....0273 771156

By FAX.....0273 206875

By Post...PO box 517 Hove Sussex BN3 5QZ

Payment by ACCESS, VISA, CHEQUE OR POSTAL ORDER.

Cheques and postal orders should be payable to Express Components.

ALL PRICES ARE SUBJECT TO 99p POST AND VAT. Some of our products may be unlicensable for use in the UK (particularly the FM transmitters.)

VIEWDATA RETURNS £6 made by Tandata, includes 1200.75 modem, kb/d, RGB and comp op, printer port. No PSU. £6 MAG6P7

IBM PC CASE AND PSU Ideal base for building your own PC. Ex equipment but OK. £14.00 each REF: MAG14P2

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LEDs, wire, buzzer, switch plus 1 relay or motor. Superb value kit just £5.99 REF: MAG6P8

SOLID STATE RELAYS Will switch 25A mains. Input 3.5-26v DC 57x43x21mm with terminal screws £3.99 REF: MAG4P10

300DPI A4 DTP MONITOR Brand new, TTL/ECL inputs, 15" landscape, 1200x1664 pixel complete with circuit diag to help you interface with your projects. JUST £24.99. REF: MAG25P1

ULTRAMINI BUG MIC 6mmx3.5mm made by AKG, 5-12v electret condenser, Cost £12 ea, Our 7 for £9.99 REF: MAG10P2

RGB/CGA/EGA/VTL COLOUR MONITORS 12" in good condition. Back anodised metal case. £99 each REF: MAG99P1

GX4000 GAMES MACHINES returns so ok for spares or repair £9 each (no games). REF: MAG9P1

C64 COMPUTERS Returns, so ok for spares etc £9 ref: MAG9P2

FUSELAGE LIGHTS 3 foot by 4" panel 1/8" thick with 3 panels that glow green when a voltage is applied. Good for night lights, front panels, signs, disco etc. 50-100v per strip. £25 ref: MAG25P2

ANSWER PHONES Returns with 2 faults, we give you the bits for 1 fault, you have to find the other yourself. BT Response 200's £18 ea REF: MAG18P1, BT Response 400's £25 ea REF: MAG25P3

Switched power supply £5 REF: MAG5P12

SWITCHED MODE PSU ex equip, 60w +5v @ 5A, -5v @ 5A, +12v @ 2A, -12v @ 5A 120V/220v cased 245x88x55mm IEC input socket £6.99 REF: MAG7P1

PLUG IN PSU 9V 200mA DC £2.99 each REF: MAG3P9

PLUG IN ACORN PSU 19v AC 14w £2.99 REF: MAG3P10

POWER SUPPLY fully cased with mains and op leads 17v DC 900mA output. Bargain price £5.99 ref: MAG5P9

ACORN ARCHIMIDES PSU +5v @ 4A on/off sw uncased, selectable mains input, 145x100x45mm £7 REF: MAG7P2

GEIGER COUNTER KIT Low cost professional twin tube, complete with PCB and components. £29 REF: MAG29P1

SINCLAIR C6 13" wheels complete with tube, tyre and cycle style bearing £8 ea REF: MAG6P10

AA NICAD PACK encapsulated pack of 8 AA nicad batteries (tagged) ex equip, 55x32x32mm. £3 a pack. REF: MAG3P11

13.8V 1.8A psu cased with leads. Just £9.99 REF: MAG10P3

360K 6.25 baud new half height floppy drives IBM compatible. Industry standard. Just £6.99 REF: MAG7P3

PPC MODEM CARDS These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud full up unit complete with leads. Clearance price is £5 REF: MAG5P1

INFRA RED REMOTE CONTROLLERS Originally made for hi spec satellite equipment but perfect for all sorts of remote control projects. Our clearance price is just £2 REF: MAG2

TOWERS INTERNATIONAL TRANSISTOR GUIDE. A very useful book for finding equivalent transistors, leadouts, specs etc. £20 REF: MAG20P1

SINCLAIR C6 MOTORS We have a few left without gearboxes. These are 12v DC 3,300 rpm 6"x4", 14" OP shaft. £25 REF: MAG25

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the above motor but suitable for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2

***FM CORDLESS MICROPHONE** Small hand held unit with a 600' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG 8P1 2 x PP3 req'd.

***MINATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range of up to 2 kilometers in open country. Units measure 22x52x155mm. Complete with cases and earpieces. 2xPP3 req'd. £30.00 pair REF: MAG30.

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

LQ3600 PRINTER ASSEMBLIES Made by Amstrad they are entire mechanical printer assemblies including printhead, stepper motors etc In fact everything but the case and electronics, a good stripper! £5 REF: MAG5P3 or 2 for £8 REF: MAG8P3

SPEAKER WIRE Brown 2 core 100 foot hank £2 REF: MAG2P1

LED PACK of 100 standard red 5m leds £5 REF: MAG5P4

JUG KETTLE ELEMENT good general purpose heating element (about 2kw) Ideal for heating projects. 2 for £3 REF: MAG3

UNIVERSAL PC POWER SUPPLY complete with flyleads, switch, fan etc. Two types available 150w @ £15 REF: MAG15P2 (23x23x23mm) and 200w @ £20 REF: MAG20P3 (23x23x23mm)

***FM TRANSMITTER** housed in a standard working 13A adaptor! the bug runs directly off the mains so lasts forever why pay £700? or price is £26 REF: MAG26 Transmits to any FM radio.

***FM BUG KIT** New design with PCB embedded coil for extra stability. Works to any FM radio. 9v battery req'd. £5 REF: MAG5P5

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

TALKING COINBOX STRIPPER originally made to retail at £79 each, these units are designed to convert and ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? Price is just £3 REF: MAG3P1

100 WATT MOSFET PAIR Same specs 25K343 and 2S413 (8A, 140v, 100w) 1N channel, 1P channel, £3 a pair REF: MAG3P2

VELCRO 1 metre length of each side 20mm wide (quick way of fixing for temporary jobs etc) £2 REF: MAG2P3

MAGNETIC AGITATORS Consisting of a cased mains motor with lead. The motor has two magnets fixed to a rotor that spin round inside. There are also 2 plastic covered magnets supplied. Made for remotely stirring liquid! you may have a use? £3 each REF: MAG3P3

BULL'S BULLETIN BOARD

100MHZ DUAL TRACE OSCILLOSCOPES JUST £259 RING FOR DETAILS

MASSIVE WAREHOUSE CLEARANCE FANTASTIC £20.00 REDUCTION REFURBISHED PC BASE UNITS COMPLETE WITH KEYBOARD

FROM ONLY £29.00 AMSTRAD 1512 BASE UNITS GUARANTEED PERFECT WORKING ORDER.

A LOW COST INTRODUCTION TO THE HOME COMPUTER MARKET.

AMSTRAD 1512SD 1512 BASE UNIT, 5.25" FLOPPY DRIVE AND KEYBOARD. ALL YOU NEED IS A MONITOR AND POWER SUPPLY. WAS £49.00 NOW ONLY £29.00 REF: MAG29

AMSTRAD 1512DD 1512 BASE UNIT AND KEYBOARD AND TWO 5.25" 360K DRIVES. ALL YOU NEED IS A MONITOR AND POWER SUPPLY. WAS £69.00 NOW ONLY £39.00 REF: MAG39

SOLAR POWER PANELS

3FT X 1FT 10WATT GLASS PANELS 14.5v/700mA NOW AVAILABLE BY MAIL ORDER £33.95

(PLUS £2.00 SPECIAL PACKAGING CHARGE)

TOP QUALITY AMORPHOUS SILICON CELLS HAVE ALMOST A TIMELESS LIFESPAN WITH AN INFINITE NUMBER OF POSSIBLE APPLICATIONS, SOME OF WHICH MAY BE CAR BATTERY CHARGING, FOR USE ON BOATS OR CARAVANS, OR ANYWHERE A PORTABLE 12V SUPPLY IS REQUIRED. REF: MAG34

FREE SOFTWARE!

Brand new, UNUSED top quality Famous brand licensed software discs. Available in 5.25" DSD or 6.25" HD only. You buy the disk and it comes with free BRAND NEW UNUSED SOFTWARE. We are actually selling you the floppy disc for your own "MEGA CHEAP" storage facilities. If you happen to get software that you want/need/like as well..... you get a "MEGA BARGAIN" too!

DSD PKT10 £2.99 REF: MAG3P7 PKT100 £16.00 REF: MAG16

WE BUY SURPLUS STOCK

TURN YOUR SURPLUS STOCK INTO CASH. IMMEDIATE SETTLEMENT. WE WILL ALSO QUOTE FOR COMPLETE FACTORY CLEARANCE.

1994 CATALOGUE.

PLEASE SEND 45P, A4 SIZED SAE FOR YOUR FREE COPY. MINIMUM GOODS ORDER £8. TRADE ORDERS FROM GOVERNMENT, SCHOOLS, UNIVERSITIES & LOCAL AUTHORITIES WELCOME. ALL GOODS SUPPLIED SUBJECT TO OUR CONDITIONS OF SALE AND UNLESS OTHERWISE STATED GUARANTEED FOR 30 DAYS. RIGHTS RESERVED TO CHANGE PRICES & SPECIFICATIONS WITHOUT PRIOR NOTICE. ORDERS SUBJECT TO STOCK. QUOTATIONS WILL ONLY BE GIVEN FOR QUANTITIES HIGHER THAN THOSE STATED.

*SOME OF OUR PRODUCTS MAY BE UNLICENSEABLE IN THE UK

BULL ELECTRICAL

250 PORTLAND ROAD HOVE SUSSEX BN3 5QT

MAIL ORDER TERMS: CASH PO OR CHEQUE WITH ORDER PLUS £3.00 POST PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY

TELEPHONE ORDERS WELCOME

TEL: 0273 203500

FAX: 0273 323077



TOP QUALITY SPEAKERS Made for Hi Fi televisions these are 10 watt 4R Jap made 4" round with large shielded magnets. Good quality general purpose speaker. £2 each REF: MAG2P4 or 4 for £6 REF: MAG6P2

TWEETERS 2" diameter good quality tweeter 140R (ok with above speaker) 2 for £2 REF: MAG2P5 or 4 for £3 REF: MAG3P4

AT KEYBOARDS Made by Apricot these quality keyboards need just a small modification to run on any AT, they work perfectly but you will have to put up with 1 or 2 foreign keycaps! Price £6 REF: MAG6P3

XT KEYBOARDS Mixed types, some returns, some good, some foreign etc but all good for spares! Price is £2 each REF: MAG2P8 or 4 for £6 REF: MAG6P4

PC CASES Again mixed types so you take a chance next one off the pile £12 REF: MAG12 or two the same for £20 REF: MAG20P4

COMMODORE MICRODRIVE SYSTEM mini storage device for C64's 4 times faster than disc drives, 10 times faster than tapes. Complete unit just £12 REF: MAG12P1

SCHOOL STRIPPERS We have quite a few of the above units which are 'returns' as they are quite comprehensive units they could be used for other projects etc. Let us know how many you need at just 50p a unit (minimum 10).

HEADPHONES 16P These are ex Virgin Atlantic. You can have 8 pairs for £2 REF: MAG2P8

PROXIMITY SENSORS These are small PCB's with what look like a source and sensor LED on one end and lots of components on the rest of the PCB. Complete with flyleads. Pack of 5 £3 REF: MAG3P5 or 20 for £8 REF: MAG8P4

SNOOPERS EAR? Original made to clip over the earpiece of telephone to amplify the sound - it also works quite well on the cable running along the wall! Price is £5 REF: MAG5P7

DOS PACKS Microsoft version 3.3 or higher complete with all manuals or price just £5 REF: MAG5P8 Worth it just for the very comprehensive manual 5.25" only.

DOS PACK Microsoft version 5 Original software but no manuals hence only £3 REF: MAG3P8 5.25" only.

FOREIGN DOS 3.3 German, French, Italian etc £2 a pack with manual. 5.25" only. REF: MAG2P9

CTM644 COLOUR MONITOR. Made to work with the CPC464 home computer. Standard RGB input so will work with other machines. Refurbished £59.00 REF: MAG59

PIR DETECTOR Made by famous UK alarm manufacturer these are hi spec, long range internal units. 12v operation. Slight marks on case and unboxed (although brand new) £8 REF: MAG8P5

WINDUP SOLAR POWERED RADIO AM/FM radio complete with hand charger and solar panel! £14 REF: MAG14P1

COMMODORE 64 TAPE DRIVES Customer returns at £4 REF: MAG4P9 Fully tested and working units are £12 REF: MAG12P5

COMPUTER TERMINALS complete with screen, keyboard and RS232 input/output. Ex equipment. Price is £27 REF: MAG27

MAINS CABLES These are 2 core standard black 2 metre mains cables fitted with a 13A plug on one end, cable the other. Ideal for projects. Low cost manufacturing etc. Pack of 10 for £3 REF: MAG3P8

Pack of 100 £20 REF: MAG20P5

SURFACE MOUNT STRIPPER Originally made as some form of high frequency amplifier (main chip is a TSA5511T 1.3GHz synthesiser) but good stripper value, an excellent way to play with surface mount components £1.00 REF: MAG1P1.

MICROWAVE TIMER Electronic timer with relay output suitable to make enlarger timer etc £4 REF: MAG4P4

MOBILE CAR PHONE £6.99 Well almost complete in car phone excluding the box of electronics normally hidden under seat. Can be made to illuminate with 12v also has built in light sensor so display only illuminates when dark. Totally convincing! REF: MAG6P6

ALARM BEACONS Zenon strobe made to mount on an external bell box but could be used for caravans etc. 12v operation. Just connect up and it flashes regularly! £5 REF: MAG5P11

FIRE ALARM CONTROL PANEL High quality metal cased alarm panel 350x165x80mm. With key. Comes with electronics but no information. sale price 7.99 REF: MAG8P6

SUPER SIZE HEATSINK Superb quality aluminium heatsink. 365 x 183 x 61mm, 15 lins enable high heat dissipation. No holes! sale price £5.99 REF: MAG6P11

REMOTE CONTROL PCB These are receiver boards for garage door opening systems. You may have another use? £4 ea REF: MAG4P5

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF: MAG6P12

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref: MAG5P13 ideal for experimenters! 30 m for £12.99 ref: MAG13P1

LOPTX Line output transformers believed to be for hi res colour monitors but useful for getting high voltages from low ones! £2 each REF: MAG2P12 bumper pack of 10 for £12 REF: MAG12P3.

SHOP OPEN 9-5.30 SIX DAYS A WEEK

PORTABLE RADIATION DETECTOR

£49.99

A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30K eV to over 1.2M eV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. Supplied complete with handbook.

REF: MAG50

Wafer contamination

Particle formation resulting from chemical and physical processes inside CVD reactors is a primary source of contamination in semi-conductor manufacture. Researchers from NIST's Chemical Science and Technology Laboratory estimate that more than 80% of total contaminant particles come from chemical processing steps and the mechanical movement of equipment.

Moreover, as much as 75% of the yield loss in chips with sub-micron feature sizes can be attributed to particle contamination of the wafer.

The NIST team tackled the problem by running a numerical simulation of particle dynamics in a vertical rotating-disk CVD reactor. They focused on identifying the factors influencing particle contamination of the deposition substrate, concluding that spin rate, disk temperature and particle size influence how close an individual particle gets to the disk.


Inverting the reactor, so that gas and heat flowed up instead of down, eliminated contamination in both rotating and non-rotating disks.

According to the NIST researchers, contaminant particles approaching the spinning disk tend to be flung away from the wafer surface by a combination of centrifugal and thermal forces. The researchers' computer model charts the predicted trajectory of particles based upon the particles' size and the temperature and speed of the rotating CVD disk. In most cases, the disk spun at a rate of 1000 rpm.

The smooth axisymmetric flows of heat and CVD gases across the surface of a rotating wafer lend themselves to numerical modelling. Nonetheless, the CVD reactor operating conditions had to be carefully selected to obtain the best flows. For example, the researchers found that a downward flow against a heated, non-rotating disk often results in the formation of what they call unstable buoyant recirculation zones, above the substrate. The deposition process is destroyed by the zones.

A rotating disk usually overcomes the problem by creating a suction, that pulls the gas towards the disk, spinning it out radially. The technique eliminates recirculation zones, resulting in uniform deposition layers.

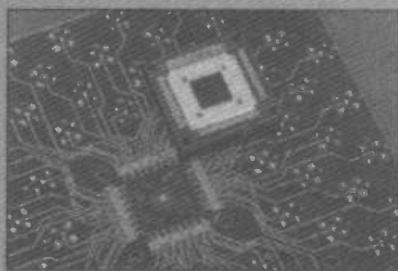Digital gallium arsenide ASICs take on silicon



Digital gallium arsenide technology is now making significant inroads into commercial markets, particularly when high speed and low power are required.

With GaAs device manufacturers now showing density levels as high as 350,000 gates, and device features as small as 0.4

micron, the speed and low power consumption of digital GaAs, as well as reduced prices, are attracting designers in such growing commercial markets as telecommunications, test equipment and high performance workstations.

According to vice president Jerry Worchel, of market research firm InStat Inc. of Scottsdale, Arizona, "recent times have seen the cost of GaAs gate arrays decline below that of high performance ECL (emitter coupled logic) bipolar gate arrays, and GaAs arrays are approaching parity with BiCMOS gate arrays, across a wide spectrum of product families."

Now that applications such as digital telecommunications and data communications have moved to higher frequencies - where the cost performance of GaAs is competitive, or even superior to silicon - digital GaAs is moving into the mainstream. In fact, it has already put a crimp into the growth of ECL and is

taking on BiCMOS in applications at 100MHz and higher.

The two most common logic schemes used in digital GaAs are direct coupled FET logic (DCFL) and source coupled FET logic. DCFL is close to silicon NMOS in topology and uses NOR structures instead of the usual NAND gate structures of CMOS. SFCL resembles ECL, in that it is a current switched logic. It therefore tends to dissipate more power than DCFL but is still lower than CMOS in applications that involve a lot of switching.

The transistor structure in both technologies is a metal semiconductor FET (MESFET), in which the metal gate resides directly on the substrate. Rockwell International Corp. of Newbury Park, California, uses a bipolar structure called the heterojunction bipolar transistor, which permits considerably faster operation than either of the FET types of logic.

Diary...

April 2nd, 9th, 16th, 23rd, and 30th -

The Computer Fair
Central Club, 16/22 Great
Russell Street, London.
Telephone 0985 844360.

April 2nd -

Northern Computer Markets
Manchester. Telephone
061 681 0569.

April 2nd -

Country Wide Computer
Fairs Slough. Telephone
0225 868100.

April 3rd -

UK Computer Fairs
Peterborough. Telephone
0533 402206.

April 4th -

Centre of England
Computer, Satellite
and Ham Radio Show
Coventry. Telephone
0952 598173.

April 9th -

All Formats Computer Fair
Brentwood Centre, Essex.
Telephone 081 856 8478.

April 9th -

Traderdesk Auctions

Motorcycle Museum,
Birmingham. Telephone
021 445 1794.

April 9th -

Northern Computer Markets
Bradford. Telephone
061 681 0569.

April 10th -

All formats Computer Fair
University Union,
Park Place, Cardiff.
Telephone
081 856 8478.

April 10th-12th -

ECTS
Business Design Centre,

Islington, London.
Telephone
081 742 2828.

April 10th -

Northern Computer Markets
Birmingham. Telephone
061 681 0569.

April 10th -

UK Computer Fairs
Ryton on Dunsmore.
Telephone 0533 402206.

April 10th -

Northern Computer Markets
Manchester. Telephone
061 6810569.



FM Radio Smaller than a 50p Piece

A tiny FM radio, built using state of the art miniaturisation, is now available from Maplin Electronics. The auto tuning, FM radio receiver produces a quality of reception that is normally only expected from radios many times its size.

The little radio is provided with an on/off switch, 'seek' button and a 'reset' button, plus a pair of earphones attached to 800mm of cord, that also doubles as an aerial. To operate, the 'reset' button is pressed once for each station that is automatically tuned in to, until the desired station is found. However, if the user has a favourite station, then tuning is not required every time the radio is switched on, as the last station selected is always remembered when the power is switched off.

Ideal for commuters, cyclists, walkers, etc., this little radio costs just £9.95 and is available from any Maplin store or direct by phoning 0702 554161.

New High Sensitivity Electronic Voltmeter

The Kenwood VT176 is a two channel electronic analogue voltmeter with a large display, providing AC RMS measurements from 0.3mV to 100V (full scale) over 12 ranges (-90db to +45db).

The AC impedance is 10m ohm 45pf and the frequency response is 5Hz to 1MHz. An AC amplifier provides a gain of 70db. Linked and independent input are switch selected.

The VT176 is priced at £399 and complements Kenwood's existing range of meters. For more information contact Trio-Kenwood UK Ltd, of Watford, on 0923 816444.



April 11th -
Cable and Satellite 94
London. Telephone
021 705 6707.

April 16th -
All Formats Computer Fair
Haydock Park
Racecourse.
Telephone 081 856 8478.

April 16th -
Spring all Micro Show
Bingley Hall,
Stafford.
Telephone
0473 272002.

April 16th -
Traderdesk Auctions

Reading. Telephone
021 445 1794.

April 17th -
All Formats
Computer Fair
Ulster hall,
Bedford Street,
Belfast. Telephone
081 856 8478.

April 17th -
Countrywide Computer Fairs
Brighton.
Telephone
0225 868100.

April 22nd -
Midi and Electronic Music

Wembley, London.
Telephone 0222 512128.

April 23rd -
All Formats Computer Fair
Northumbria Centre,
Washington.
Telephone 081 856 8478.

April 23rd -
MCD Auctions
Surrey.
Telephone
0932 571911

April 24th -
All Formats Computer Fair
National Motorcycle
Museum, Birmingham.

Telephone 081 856 8478.

June 26th - 27th
Longleat Amateur Radio Rally
- Bristol Group RSGB
Longleat Park, Warminster,
Wiltshire. Telephone
0272 860442.

If you are organising an event of any description which would be of interest to ETI readers and would like to have it included in this diary section then please send details to: Event Diary, ETI, Argus House, Boundary Way, Hemel Hempstead, HP2 7ST.

WINTER 1993/94 CATALOGUE



The new enlarged Catalogue is out now!

- New direct phone lines for prompt service
- 16 more pages
- £££'s worth of discount vouchers
- 100's new products
- 240 pages, 26 sections, over 4000 products
- New section of entertainment and accessories including disco equipment, audio mixers, car amplifiers, crossovers, speakers and boosters
- Complete range of Velleman kits now stocked
- The latest scanning receivers and accessories
- New Ni-cad batteries and chargers
- New range of telephone equipment and accessories
- Published December 1993
- Available from most large newsagents or direct from Cirkit
- **Send for your copy today!**

£1.90
+ 30p p&p

Cirkit




CIRKIT DISTRIBUTION LTD

Park Lane · Broxbourne · Hertfordshire · EN10 7NQ
Telephone (0992) 448899 · Fax (0992) 471314

PCB Designer

For Windows 3.0 & 3.1
Runs on any PC running
Windows in standard or
enhanced mode
with 2MB
RAM

Only
£49
All
Inclusive

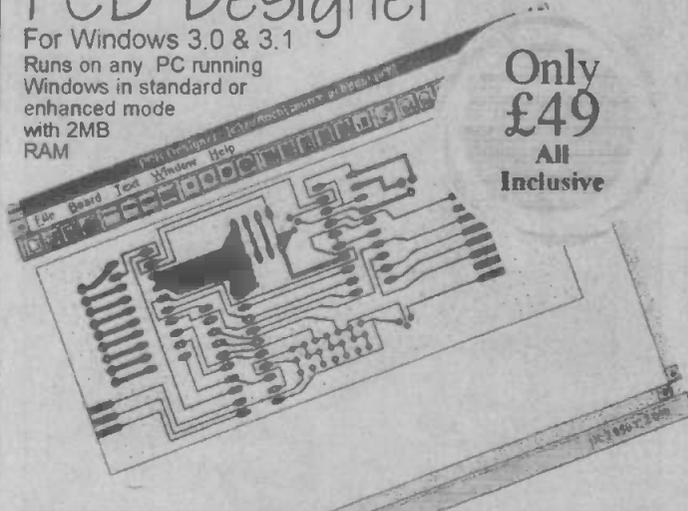

'...at that price many users will find it (PCB Designer) preferable to the freeware competition, or the more expensive commercial alternatives...'

'...I must have tried over a dozen PCB design programs in the last few years and PCB Designer is certainly the easiest to learn and use...'

R A Penfold

Everyday with Practical Electronics

Niche Software

22 Tavistock drive, Belmont, Hereford, HR2 7XN
Phone (0432) 264 800, FAX (0432) 264 800

Please Note: Since PCB designer is so easy to use, and to keep costs down, PCB Designer has an On-Line manual, in Windows Help format. A tutorial is also supplied online.

THIS IS THE COUPON

that brings the 1993-94
CATALOGUE

140 pages, A4, copiously
illustrated, bang up to date and
with bonus vouchers. Send
cheque/PO for £1.50

that brings the
SERVICE

with choice of very wide ranges of famous-name
quality electronic components and associated gear
sent promptly on receipt of your order. A service

that **ElectroValue**

have been providing constructors with continuously
since 1965. With *this* Catalogue, you will find our
service the best ever. Send for your copy **NOW!**



ELECTROVALUE LTD., 3 CENTRAL TRADING ESTATE, STAINES
TW18 4UX Telephone 0784 442253 Fax 0784 460320

I enclose cheque/PO/Credit Card No.
value £1.50 to your 1993-94 Catalogue

Name

Address

Post Code

TE 2



Chelmer Valve Company

For audio valves

Audio valves with famous brand names of yesteryear such as MULLARD, MOV, GEC, RCA etc, are in very limited supply and their scarcity also makes them very expensive.

We at Chelmer Valve Company however provide high quality alternatives to these old makes. We have over 30 years experience in the supply of electronic valves of all types and during this time have established close ties with factories and sources worldwide.

For high fidelity use we further process valves from these sources using our specially developed facilities. After rigorous testing - including noise, hum, microphony, post burn-in selection and matching as needed - we offer this product as CVC PREMIUM valves.

A selection of the more popular types are listed below.

Price list & order form for CVC PREMIUM Audio Valves

	UNIT PRICE	QTY.	TOTAL PRICE		UNIT PRICE	QTY.	TOTAL PRICE
PRE-AMP VALVES				CARRIED FORWARD			
ECC81/12AT7	5.00			RECTIFIERS			
ECC82/12AU7	4.00			GZ32	4.50		
ECC83/12AX7	5.00			GZ34/5AR4	5.00		
ECC85	4.00			5U4G	5.00		
ECC88	5.00			5Y3GT	3.20		
BF86	4.00			5Z4GT	3.50		
E81CC(GOLD PIN)	6.00			SOCKETS			
E82CC " "	6.00			B9A (PCB)	1.60		
E83CC " "	6.00			B9A (CHASSIS)	1.60		
E88CC " "	7.00			OCTAL (CHASSIS)	1.75		
E80F	9.00			4 PIN (UX4)	3.00		
E83F	5.50			4 PIN (FOR 211)	11.00		
6SL7GT	4.00			MATCHING CHARGES*			
6SN7GT	4.20			POST & PACKING (UK)			3.00
6922	5.00			TOTAL EXC. VAT			
POWER VALVES				VAT @ 17 1/2% (UK & EEC)			
2A3 (4 PIN)	14.00			TOTAL TO PAY £			
2A3 (OCTAL)	14.00			*MATCHING, if required; state valve types & if PAIRS, QUADS or QCTETS - Allow £1.00 per valve for this service.			
211	22.00						
300B	50.50			Make CHEQUES payable to 'CHELMER VALVE COMPANY or pay by ACCESS/MASTER CARD/VISA, give details:			
811A	9.50			<input type="text"/>			
845	29.90			Signature			
EL34/6CA7	7.50			Expiry			
EL84/6BQ5	4.00			Name			
EL84/7189A'	5.10			Address			
KT66	9.20					
KT77	12.00					
KT88	12.50					
KT88 (GOLD Q)	18.50					
6L6GC	6.50					
6L6WGC/5881	8.00					
6V6GT	5.00					
6146B	10.20					
6336A	38.00					
6550A	11.00					
6550A-S	13.50					
7581A	11.00					
TOTAL CARRIED FORWARD				Post Code			

Valve amplifiers sound better still with CVC PREMIUM valves!

Animatronics today, robotics tomorrow?



In theme parks across the world, dinosaurs roar and gnash their teeth, familiar looking pop musicians play familiar sounding songs. Are they real? They may look it, but they are robots, the first generation of the machines of the future

In many ways it is perhaps incorrect to describe these moving creatures as robots. They perform a fixed repetitive routine and have few, if any, in-built sensors which allow them to interact with the outside world. In many ways it is easier to think of them as sophisticated, stringless, computer controlled puppets.

The makers of such systems have, in fact, been very careful to avoid using the word 'robot' when describing these 'creatures'. Instead, they have coined the word 'animatronics' to describe the technology, a word you will probably not find in your dictionary, it is too new, but it is a word which rather descriptively owes its origin to a fusion of 'animation' and 'electronics'.

Obviously a 'creature' which can move in a carefully controlled way, even though tethered and performing a


repetitive sequence of movements under computer control, is only a step away from being a robot. All it needs is the added ability to react to the world around it, to have sensory input and to use that input to modify and control its movements and reactions.

So when and how will the animatronic dinosaurs step over the boundary and become robotic dinosaurs? When will they start to roam free in a robotic Jurassic Park?

Animatronics Today

Animatronics is a big business today in most of the technologically advanced nations, with dozens of companies producing and using animatronic products, ranging from sophisticated talking 'people' to the simple moving characters often used in shop window displays.

True animatronics, as

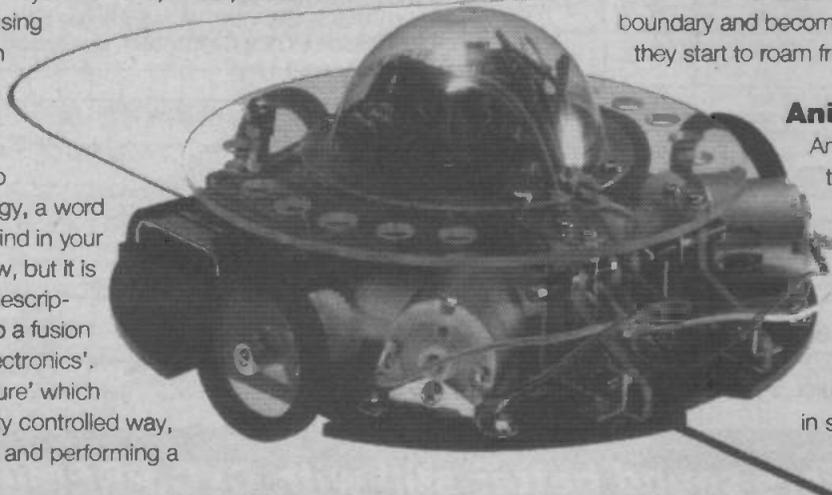

opposed to simple mechanical automatons, can be defined as mechanical moving characters which work under computer control. The earliest such systems first appeared about fifteen years ago and were primarily the result of work by Disney and the University of Utah. These animatronic characters were used in Disney World and were an immediate hit with the public.

The characters used pneumatic actuators operating under computer control. Pneumatics were used primarily because they were easy to implement using off the shelf components. They are quiet and, unlike electrical actuators, free from jerky movements. They are also safe, a factor which turned users against hydraulic systems. There is a story that the entire board of directors of one major animatronics company went to look at the first such product created by their R&D people. It was a hydraulic system and half way through the demonstration a hydraulic hose came loose and drenched the directors in warm oil. From that day forth pneumatics were used.

The success of animatronics at Disney World has led to their being developed and used in a wide range of different theme park, entertainment and even museum environments around the world. One of the world's leaders in animatronics, and apart from Disney probably the largest operator of such systems in Europe, is Madam Tussauds.

This company's most sophisticated animatronics set up is Rock Circus in the London Pavilion on London's Picadilly Circus. Here, on the largest revolving stage in Europe, visitors can see 'live' performances by animatronic versions of some of the world's best known rock and pop legends.

The animatronic figures used at Rock Circus move naturally and have fully animated faces. Unless you look at them very closely and critically, you could be mistaken for almost thinking that they were real. The naturalism comes from a combination of technological sophistication in their design and construction and in Tussauds traditional skills in creating lifelike copies of famous people.

Inside an Animatronic Figure

The animatronic characters at Tussauds are all made and designed by the company at their workshops in north London. The work with the aid of electronically controlled pneumatic actuators, with each character having dozens of different actuators, rotary ones, linear ones, big ones and small ones. A blinking eyelid has its own actuator, the moving eyeball another, others control movement of the mouth, the hands, neck, arms, etc.

Each animatronic character is thus a very sophisticated pneumatic and mechanical structure and, at about £150,000, is also very expensive. They are designed to be robust and as maintenance free as possible. The shows go on seven days a week and operate continuously for over twelve hours per day so, for example, the eyelid actuator on a character will operate about 18,000 times a day and some of the characters have been operating continuously for over 87,000 shows - that is a lot of eye blinks.

For reliability, the systems are very well engineered, they have robust steel 'skeletons' and use high grade miniature pneumatic actuators, with steel rods providing the mechanical linkage. The actuators are controlled by high precision and, most importantly in this type of application, very quiet electronic valves and pressure controllers (the system works on air pressure of 130psi from a large central compressor).

Very few positional sensors are used, it is mainly switches and the odd potentiometer based rotational position sensor. In most cases, current generation of animatronics uses simple open loop control systems, with limit switches to stop any malfunction tearing the system apart by having actuators

Robots and the Amateur

Building and developing your own robots is not only practical, but a great challenge and an enormous amount of fun. Robotics brings together a wide range of different engineering and technological skills, mechanics, electronics, computer programming and, if you are feeling really ambitious, pneumatics and hydraulics. This means that robots are ideal as educational and club projects, where people with different skills and ideas can be brought together.



Robotics is also one of the few areas of technology where an amateur can produce original work, do something that no one has

managed to do before. Be at the cutting edge of new technology. It is an area where ingenuity and imagination can count for as much as knowledge, and where high budgets are not necessary. Indeed many university research projects on robotics are very poorly funded and have relied on surplus and scrap materials to build their systems.

There is also the aspect that many potential applications for robotic systems are being commercially ignored because the perceived market is too small, in comparison to manufacturing and development costs. This need not deter the amateur robot builder. For example, how about a robot lawn mower, or a robot cleaner trained to pick up pieces of litter? Both ideas would be possible using off the shelf technology and there are many more potential applications like those two!

In future issues of ETI we will be looking at different aspects of electronics which will be of use to robot builders, such as motor and actuator control, a more detailed look at subsumption architecture, microcontrollers and servo loop systems. Indeed, we will be going even further and promoting a series of amateur robot competitions, to discover the most ingenious systems and those best able to perform a specific task. Watch out for more details in future issues of ETI.

working against their limits or against each other. However, the next generation of animatronics, currently being introduced by Disney, makes extensive use of closed loop control systems to create some quite spectacular performances.

The systems all rely on a hierarchy of electronic control. At the lowest level, the movement of an individual joint is controlled by a local control circuit, which uses an EPROM programmed to generate the exact sequence of actuator movements necessary to move the limb smoothly and naturally from its current position to a new designated position. These local control circuits are the same for a wide range of different limbs and compound movements, the EPROM will be tailored exactly to produce the necessary movements required of the particular application.

The data stored in the EPROM of the local control circuit is generated when the system is first created and it allows complex movements to be executed, using just a simple command to move from one set of co-ordinates to another. This frees the higher levels of control hierarchy from any need to perform a lot of repetitive actions and the modularity inherent in this approach also makes the system easier to design and maintain.

At Rock Circus, the higher level control is performed by a special dedicated computer system from ElectroSonics. In fact, three such computer systems are used, each one having the control data sequences, as well as sound output, lighting and stage elevation controls, stored on massive optical disk systems.

At all stages in the system's integration, from individual limbs to the complete show, the designers have provided automatic safety features and cut-outs. This is sufficiently sophisticated that if a portion of the system fails, then the show will not stop but will simply compensate for that failure. With long opening hours, there is very little time to repair and maintain the system. You cannot shut down the show when there are five hundred enthusiastic French youngsters waiting outside!

Animatronics Tomorrow

Rock Circus contains some of the most sophisticated animatronics currently in use, the main constraints at the moment being size and freedom of movement. Even using the smallest available actuators, it is very difficult, if not impossible, to create an animatronic 'person' the size of a child, or a large dog. It is a question of trying to pack the mechanics, pneumatics and control electronics into a small space. The problems associated with size are one reason why dinosaurs have been a popular type of 'creature' with animatronic designers.

Freedom of movement is the other main constraint. Once again, size is an important consideration - with an animatronic 'creature' the size of an elephant or a tyrannosaurus rex, one could pack pneumatic/hydraulic pumps, power supply and computer inside and thus have something that was self contained and free moving. But with anything smaller, this could prove extremely difficult, if not impossible. Such self contained large animatronic systems suffer from the weight/power ratio vicious circle; the more weight the more power, but the more power the more weight.

There has, however, been one recent success in free moving self contained animatronics and that was the animatronic killer whale used in certain sequences in the film 'Free Willy'. At a cost of reputedly £1/2million, the makers of this film produced an exact copy of the real whale, which was able to swim and move in a natural looking manner without being visibly attached. Here the unit was large enough to be self contained and thanks to the buoyancy of sea water did not require the power and

structural strength of a land based system.

The animatronic whale used in Free Willy was capable of looking and moving just like the real thing. However, the naturalness of the movements was really due to the skill of the operators, since it was in fact simply a large radio controlled puppet. The movements were all dictated by human operators, rather than by a control computer.

What About Robotics?

All the animatronic systems we have looked at so far have all been designed to either perform repeated sequences of movements or have been, in essence, sophisticated puppets. Thus, the animatronic Beatles will go through a performing sequence of movements lasting several minutes, then at the next show they will repeat the same performance. At no time will they be called upon to interact with their environment.

This is the difference between a robot and an animatronic system. The robot can interact with its environment. Even a simple industrial arm robot will have sensors that allow it to modify its actions in relation to a change in its environment. Such a robot arm equipped with a gripper will have sensors in the gripper which allow it to pick and place an object as delicate and variable in size and weight as an egg, or a standard 10kg block of metal. The sensors will tell the robot's control system when the object has been gripped sufficiently tightly to allow it to be picked up without, in the case of an egg, breaking it.

Similarly, an industrial robot needs to be equipped with sensors which will ensure that it moves in a very precise manner - animatronic devices do not need a great deal of positional accuracy. This means that an animatronic system can function with a simple system which has no positional feedback, while every actuator on a robot will be equipped with a full servo loop positional feedback system.

It is this question of how to design systems that will interact with the world around them that is exercising the minds of researchers in robotics all around the world. If you stop and think about how many senses we are all using at any one time and how we feel lost if we are deprived of any single one of them, you can get an idea of the enormity of the problem.

We use complex interactions of our senses all the time. As I type this article I am using touch to feel the keys, sight to look at the screen and hearing to confirm that the key has been pressed. We can make a robot see, hear and in a rudimentary way feel, but we are still a long way from making systems which can smell and taste more than a few chemical compounds. We are even further away from making a robot which can fully utilise all such sensory input.

The Robotics Researchers

There are thus several key areas of research in robotics and the associated discipline of artificial intelligence, which are currently exercising some of the world's finest brains. These are the development of suitable sensors, the interpretation of the data coming from these sensors, especially the area of machine vision, the creation of a knowledge base of the world in which the robot lives with respect to this sensory input, a knowledge of and interpretation of natural language, so that it can communicate with its developers and the ability to reason and plan, so that it can perform tasks and overcome problems without human assistance.

The ultimate goal of all the researchers at work in these



areas today is to build not just 'smart' computers, but electro/mechanical 'creatures', which could function independently in the world. In other words, a free roaming device which demonstrates some degree of intelligent behaviour.

This is, of course, the image that we all have in the back of our mind when we talk about robots, the image of the metal men of Hollywood movies and science fiction novels. Ten years ago, researchers in AI and robotics may have shared that image and sought to create human like intelligent systems. Today, in the face of the enormous problems involved, such researchers are more likely to be thinking more in terms of a mechanical ant than a mechanical man.

By and large, this is an approach which is generating a considerable degree of success and the lessons learnt will enable more complex systems to be built in the future. This is still a very controversial area, but much of the success has tended to indicate that a lot of the traditional approaches have been based upon the wrong premises and are not what is needed for building machines designed to live in the real world.

Many researchers are now arguing that complex behaviour is not derived from some knowledge representation system but from the interaction of simple behaviours. The traditional approach to the design of a robotic 'brain' has been an analytical one, where the engineer first decides what the robot will sense, then decides how it will analyse that input and finally decides what it will do in response to that input. A process that can be extremely complex even for a simple robot.

The new approach has been pioneered by Rodney Brooks of MIT and is a robot architecture called subsumption. Subsumption relies on a network of processors and hardware, each demonstrating simple behaviour patterns, such as moving a leg, to create a system showing much more complex behavioural patterns. Thus subsumption architecture relies on the behavioural pattern developing in response to the nature of the world in which the robot lives, rather than a sophisticated analysis of that world by the robot's designer.

Rodney Brooks argues that if a robot encounters an obstacle, the important thing is that it can find its way around that obstacle, not that it can analyse the object and its position. A knowledge of the world in which it lives is not really necessary, but an ability to survive in that world and react appropriately to it is. This way, it is possible to circumvent the thorny AI problem of constructing and maintaining a logical model of the outside world and making a correspondence between that model and reality.

To test the theory of subsumption, Brooks' team at MIT has created a range of artificial creatures, which have been designed to wander around and avoid obstacles. These creatures use legs for movement and have been dubbed 'insectoids'.

One of these insectoid robots, called Ghengis, clearly demonstrates how subsumption works. This foot long robot consists of six legs and sensors consisting of two whiskers and six infra-red 'eyes'. Each of the six legs has two electric motors, one, the Alpha motor, moving the leg backwards and forwards, the other, the Beta motor, lifting the leg up and down. Each leg has its own microcontroller which controls the movement of that leg and monitors the sensors associated with it, using a system of augmented finite state machines within the software.

The processor on each leg spends most of its time checking the leg's position and maintaining the correct attitude to keep

the robot standing. All the leg processors work independently and the robot will walk or run in response to a signal from a high level processor. This processor will send a 'walk' command to each of the legs, but does not actually co-ordinate them.

Co-ordination is achieved by interaction between the various 'leg' processors and the system learning to walk in the most efficient manner. To do this, each leg experiments with a set of basic behaviours to see what the neighbouring legs were doing and whether, as a result, the body fell down or not. With this learning system Ghengis learnt how to walk with a proper alternating tripod like gait, in about one and a half minutes.

This shows how a properly designed subsumption system can acquire complex behaviour patterns, without any need to have those patterns pre-programmed into the system. A simple insectoid like Ghengis uses just two levels of processor hier-

archy, but there is no reason why much more complex systems should not be built which use many more layers.

This is a concept which runs contrary to the popular 'folk psychology' concept of a centralised, all powerful, all-controlling, conscious mind. Instead, subsumption sees intelligence as a

distributed hierarchical structure. Indeed, subsumption architecture systems have already been built which incorporate 'beliefs' and 'motivations'. However, a lot of researchers believe that, at higher levels, more traditional approaches will be found

more appropriate.

It should always be remembered that AI and robotics are littered with intellectual minefields. The big success story of today might turn out to be a forgotten technique tomorrow, although it has to be admitted that we have come a long way since Shakey, the first mobile robot, wandered around a lab at Stanford University over twenty years ago.

Where Animatronics meets Robotics

In this article, I have briefly looked at some of the current technical developments in both animatronics and robotics. It is true that animatronics is only a high tech form of puppetry and, as such, is dismissed by many in robotics, but the development of animatronics performs several valuable functions. It acts as a test bed for the complex mechanical and actuator systems which will be needed by future generations of robots. It is a test bed with the emphasis on reliability and safety, two very important factors in future robot development. The other valuable function performed by animatronics is a public relations role. They remove the often irrational fear so often associated with the word 'robot'.

In the future, of course, animatronic systems will incorporate many of the advances being made in robotics. Work in the area of subsumption should be of particular interest to animatronic system developers and it is probably only a matter of time before free roaming animatronic/robotic systems are being produced. I am sure that at this very moment someone, somewhere, is thinking about the practicality of producing a robotic Jurassic Park.





BRAKE LIGHT MONITOR

Stay within the law with Terry Balbirmie's light checking circuit

The problem with filament lamps is that they eventually fail. Car bulbs are especially vulnerable due to the bumping and vibration which they experience during the normal course of driving. The ability of these bulbs to survive in such a hostile environment has improved over the years, but they still rank as one of the most unreliable components in the car's electrical system.

The law requires that all lights be kept in good working order and the annual UK MOT test will be failed if a lamp does not work properly. In theory, all lights should be checked before the start of a journey. However, there will be difficulty testing the brake lights, unless an assistant is available to press the pedal. Many readers will therefore find the Brake Light Monitor makes a worthwhile and inexpensive add-on unit. It detects filament failure when it happens and provides an audible signal in the form of a high-pitched bleep each time the brake pedal is pressed. If the driver carries a spare bulb, the problem can be corrected before any significant danger or inconvenience has been caused to other road users. Note that the warning does not indicate which of the brake lights has failed - only that one of them has done so. This is not thought to be a problem, as the faulty one will soon be located once the signal has been given.

The Brake Light Monitor is simple to construct. It does not involve breaking any wires to insert components and will not cause the lamps to go off if the unit itself fails for some reason. It imposes no drain on the battery while the car is left parked because it draws current only while the brake pedal is pressed. Any small plastic box of sufficient size may be used as an enclosure and this may be sited under the dashboard in an inconspicuous position. The specified internal buzzer will sound clearly above engine and other noises.

It is likely that the circuit could be used to monitor other car lamps, such as side and tail light bulbs, but this has not been tried and readers would possibly need to experiment to obtain reliable operation.

Before constructing this circuit, it would be wise to check that the unit will be easy to fit to the car. Access is needed to the foot brake switch wires and to the wiring at either stop light at the rear. On most cars, the foot brake switch is located above the brake pedal itself and easy to find. It will be necessary to run a wire from this position and from the brake light to the main unit. Check that it will be possible to route these wires unobtrusively.

Basic Theory

Operation of the Brake Light Monitor relies on the voltage developed across a resistor when it carries current. This is referred to as the voltage drop. Figure 1a shows a 12V battery, bulb and resistor connected in series. In this example, the

resistance of the lamp filament is 11Ω and that of the resistor, 1Ω. A total resistance of 12Ω is therefore connected across the 12V supply. Ignoring the internal resistance of the battery and the small resistance of the connecting wires, the current can be predicted by Ohm's Law which states:

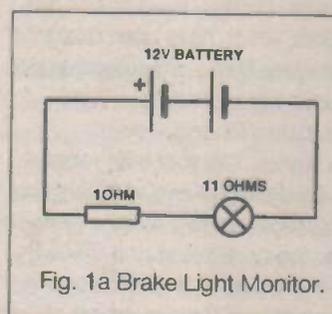


Fig. 1a Brake Light Monitor.

$$I = V/R$$

Where I is the current, V is the supply voltage and R is the resistance. The current (flowing through both the lamp and resistor) is therefore $1A$. Ohm's Law can be applied again but this time to the lamp alone, using the re-arranged version of Ohm's Law:

$$V = I \times R$$

This calculates the voltage developed across the bulb to be $11V$ and there will be $1V$ appearing across the resistor. Assuming the bulb is designed to operate from a $12V$ supply, it would be dimmed somewhat. Now consider Figure 1b, which shows an automotive circuit in which a $12V$ lamp operates through a length of wire from the supply. The car chassis (metal bodywork) forms the return connection to the negative battery terminal. Here, the resistor in Figure 1a is replaced by the resistance of the connecting wire itself. Although small, this is significant - typically around 20 milliohms (0.02 ohms) per metre ($3ft$ approximately) depending on its thickness. Over a run of $3m$ of wire (a typical length), a resistance of $60m\Omega$ could therefore be expected.

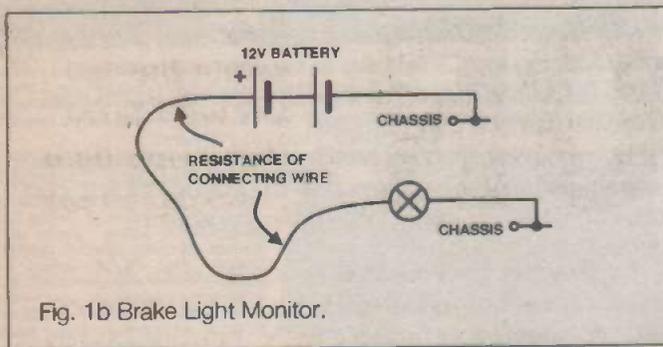


Fig. 1b Brake Light Monitor.

A standard brake light bulb rated at $21W$ requires a current of $1.75A$ - that is, $3.5A$ for the pair. Using $V = I \times R$ again, a voltage drop of some $200mV$ may therefore be expected over $3m$ of wire. This will be halved to around $100mV$ when one of the lamps fails, since the current is halved. The voltage across the bulb(s) will therefore be nominally $11.8V$ with both operating and $11.9V$ with only one. The dimming effect here is negligible which is important in practice. With a monitoring circuit adjusted to trigger above about $11.85V$ it will remain off with two lamps illuminated but will operate when there is only one.

In the circuit to be described, the operating voltage threshold is adjusted to suit the length of wire over which monitoring takes

place. As long as the monitoring points are close to the brake light switch and one of the brake lights, there will be sufficient voltage drop for correct operation.

Circuit Description

The circuit is shown in Figure 2 and this uses IC1 as its main component. This is an operational amplifier used as a voltage comparator. Although various general purpose op-amps could be used here, the inexpensive and robust 741 type works perfectly well. When the non-inverting (+) input voltage exceeds the inverting (-) one, the output (pin 6) is high. Otherwise, it will be low. In this circuit, the inverting input (pin 2) voltage is determined by the setting of preset potentiometer, VR1. Fixed resistor, R2, limits VR1 operating range and, with the values stated, this can be adjusted between nominal limits of 11 and $12V$. The non-inverting input (pin 3) voltage is that existing across the brake light bulbs. R1 has virtually no effect and is included simply to prevent an excessive current flowing in the event of some catastrophic failure. VR1 will be adjusted to provide the correct threshold voltage at the inverting input. Thus, the inverting input voltage will exceed the non-inverting one (output off) when both lamps are operating, but when a filament falls, the conditions will reverse and the output will become high. While high, current enters the base of transistor, Q1, through R3 and buzzer, BUZ1 operates. With the

741 op-amp, the output is about $2V$ when the device is nominally off. Fixed resistors R3 and R4 form a potential divider which scales down this output voltage so that the transistor is not turned on under these conditions. Note that the circuit receives its feed and therefore draws current only while the brake pedal is pressed.

In the normal course of operation, the supply voltage will vary between around $10.5V$ and $14V$, but this will not affect correct operation. This is because the voltages applied to the op-amp inputs are effectively derived from potential dividers connected across the supply, so as this varies,

the input voltages will rise and fall in sympathy. Thus, the operating conditions will remain virtually the same.

Construction

All the components for the Brake Light Monitor are mounted on a single-sided printed circuit board apart from the 3-way piece of screw terminal block which is used for the external connections. Figure 3 shows the component view (parts placement diagram) for the PCB.

Begin by drilling the two mounting holes as indicated. Solder the components in the following order. Firstly, the IC socket, then the preset and all fixed

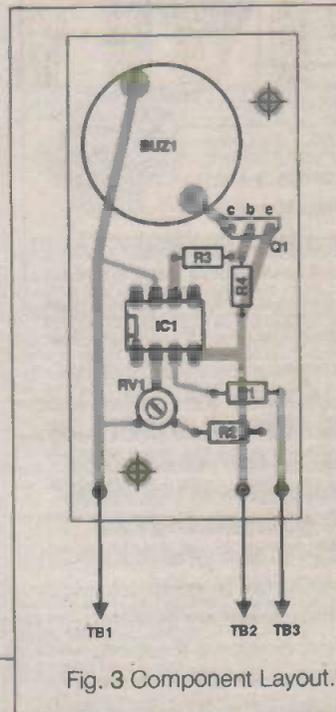


Fig. 3 Component Layout.


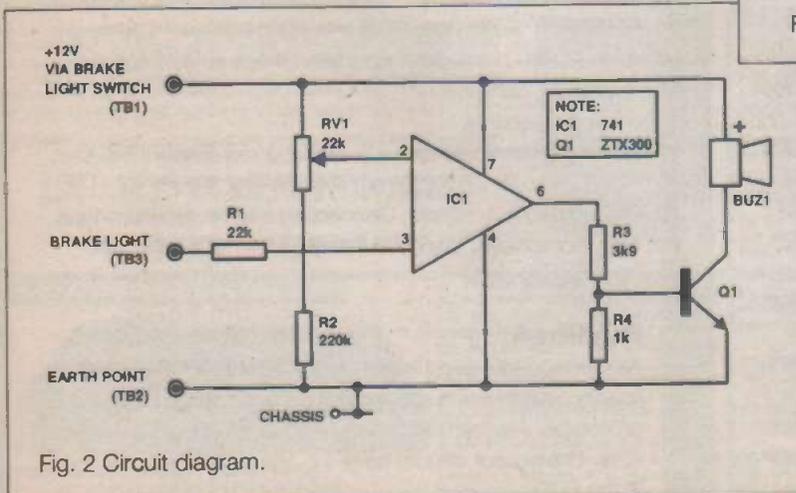


Fig. 2 Circuit diagram.

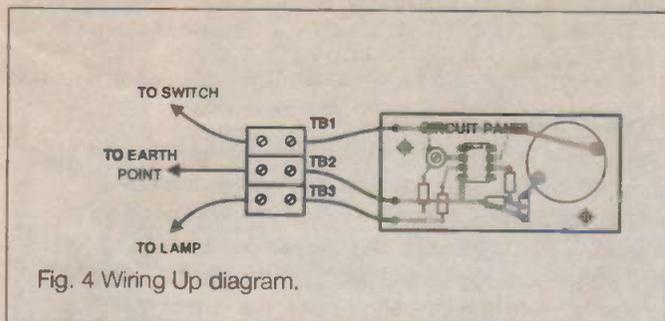

resistors, flat with the board. Add the transistor and buzzer, observing the polarity. Solder 5cm pieces of light-duty stranded connecting wire to the three pads for terminal block connections, as indicated.

Prepare the box by drilling holes in the base to correspond with those already made in the circuit panel and for terminal

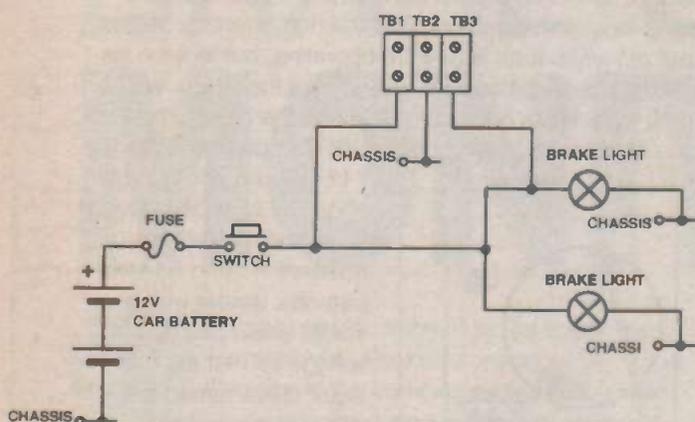


Fig. 5 Layout for typical brake system.

block mounting on the side. Drill a hole for the wires passing through the box to the terminal block. Mount the panel on short plastic stand-off insulators and attach the terminal block using small fixings. Pass the wires through the hole in the box and, shortening them as necessary, connect them as indicated in Figure 4. Drill a hole in the lid above BUZ1 position for the sound to pass through. Insert the IC into its socket. Adjust VR1 to approximately mid-track position. Do not fit the lid yet.

It would be wise to disconnect the car battery positive terminal as a precaution against short-circuits. If a security coded radio is fitted it may be more appropriate to simply remove the fuse feeding the brake lights. This is because if one of these radios is left without a supply, it 'loses' its code number and this would have to be re-entered when the supply was connected again. Refer to Figure 5 which shows the layout of a typical brake light system. Locate the brake light switch and identify the wires leading to it. You will need to make a connection to the wire which runs to the brake lights. Similarly, find a suitable place to make a connection to the wire leading to the live side of either brake light. Alternatively, this could be done at the existing connector where the wires divide to feed the individual lamps. The important point is that monitoring should take place over as long a distance as possible and with both lights being fed through most of the wire. Decide on the final position of the unit and measure the two pieces of wire needed to reach between these positions and the terminal block. Automotive-

type wire must be used, although it can be of any light-duty type since only very small currents flow in it. Make the actual connections using Scotchloks. These are available from any car accessory store and allow permanent connections to be made to existing wiring without actually breaking into it. Connect the wires to the terminal block - TB1 to the switch wire and TB3 to the lamp. Connect TB2 to an existing earth point. If no such earth point can be found, drill a small hole in a metal part and use a solder tag secured with a self-tapping screw.

Testing

Testing is simply a matter of adjusting VR1 for correct operation. Removing a bulb will simulate failure of its filament. With both lamps in position, re-connect the supply and press the brake pedal (it may be necessary to switch on the ignition). The buzzer will probably sound. Rotate VR1 wiper clockwise (as viewed from IC1 position) until it just fails to do so. If when the brake pedal is pressed the buzzer fails to sound, rotate VR1 anti-clockwise until it does, then clockwise until it just stops. When correctly adjusted and with both bulbs intact, the buzzer will not sound. With one bulb removed, it should sound when the brake pedal is pressed. Check operation several times and with the engine running. Make any small adjustments as necessary. Fit the lid. With the engine running, the buzzer may give a slightly warbling tone. This is due to the unsmooth charging system output and may be ignored. The box may be mounted behind the dashboard and forgotten.

Failure of a filament is signalled by a continuous tone when the brake pedal is pressed. Intermittent operation indicates poor connections such as those due to loose connectors or corroded lamp holders.

PARTS LIST

Resistors

R1	22k
R2	220k
R3	3k9
R4	1k0
VR1	22k

Semiconductors

IC1	LM741CN
Q1	ZTX300

Miscellaneous

- BUZZ1 Solid state PCB mounting buzzer - 12V operation 23mm diam. 5mA operation. Frequency 3.5kHz. (Maplin KU58N)
- 8-pin d.i.l. socket
- 3A screw terminal block - 3 sections required
- Plastic box 75 x 50 x 25mm (Maplin FK73Q)
- Printed circuit materials. Connecting wire, automotive-type wire, Scotchloks, stand-off insulators, small fixings, etc.

Buylines

All components used in the Brake Light Monitor are readily available and were obtained from Maplin for the prototype. Any bipolar 741-type op-amp should be suitable. The buzzer should have 17-18mm spaced pins to fit the PCB.

OMP MOS-FET POWER AMPLIFIERS
HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS
FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)
ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★ Independent power supplies with two toroidal transformers ★ Twin L.E.O. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19"xH3 1/4" (2U)xD11"
MXF400 W19"xH5 1/4" (3U)xD12"
MXF600 W19"xH5 1/4" (3U)xD13"
MXF900 W19"xH5 1/4" (3U)xD14 1/2"

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH

OMP XO3 STEREO 3-WAY ACTIVE CROSS-OVER




Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable OIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE ★ ECHO & SOUND EFFECTS ★

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** Including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 8 Line for CD, Tape, Video etc.

Price £144.99 + £5.00 P&P

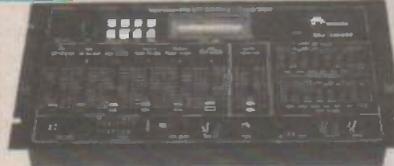

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.

TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
TYPE 'C' (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

TYPE 'A'

TYPE 'B'

TYPE 'C'

TYPE 'D'

TYPE 'E'

IBI FLIGHT CASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET
FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz

IBI FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR
IBI FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR

OPTIONAL STANDS PRICE PER PAIR £49.00
Delivery £6.00 per pair



IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £89.99
400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS
150 WATTS (75 + 75) Stereo, 150W Bridged Mono
250 WATTS (125 + 125) Stereo, 250W Bridged Mono
400 WATTS (200 + 200) Stereo, 400W Bridged Mono
ALL POWERS INTO 4 OHMS

Features:
★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. industry, leisure, instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre PCB and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P



OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P



OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P



OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P



OMP/MF 1000 Mos-Fet Output power 1000 watts R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm.
PRICE £259.00 + £12.00 P&P

NOTE MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. PFC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PFC.

LOUDSPEAKERS

LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.

McKenzie and Fane Loudspeakers are also available.

EMINENCE:- INSTRUMENTS. P.A., DISCO, ETC

ALL EMINENCE UNITS 8 OHMS IMPEDANCE
8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £32.71 + £2.00 P&P
RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB.
10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. PRICE £33.74 + £2.50 P&P
RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB.
10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. PRICE £49.47 + £2.50 P&P
RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB.
12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. PRICE £35.64 + £3.50 P&P
RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB.
12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB. PRICE £36.67 + £3.50 P&P
12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. PRICE £46.71 + £3.50 P&P
RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 98dB.
12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. PRICE £70.19 + £3.50 P&P
RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB.
18" 200 WATT R.M.S. ME18-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. PRICE £50.72 + £4.00 P&P
RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 95dB.
15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. PRICE £73.34 + £4.00 P&P
RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB.

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohms)
BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
8" 50watt EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz, SENS 97dB.
10" 50watt EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, STUDIO. PRICE £13.65 + £2.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 96dB.
10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.
12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P
RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.
FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
5 1/2" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.
6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P
RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.
8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 95dB.
10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 96dB.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P



PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR.

Tel: 0702-527572 Fax: 0702-420243

POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.






PROJECT

The *Experimenter's* Computer

FORTH is a complex language but fortunately, like all languages, programming or otherwise, you don't need to know every aspect of it to use it effectively. It is a language based on 'words', each word carrying out some low level function, and words can call other words to produce more complex functions.

Most of the words are built into the firmware. Using the board is simply a matter of defining your own words, to suit your needs. Apart from learning some of the built in words and what they do, there are two fundamental concepts which must be (at least partially) under-

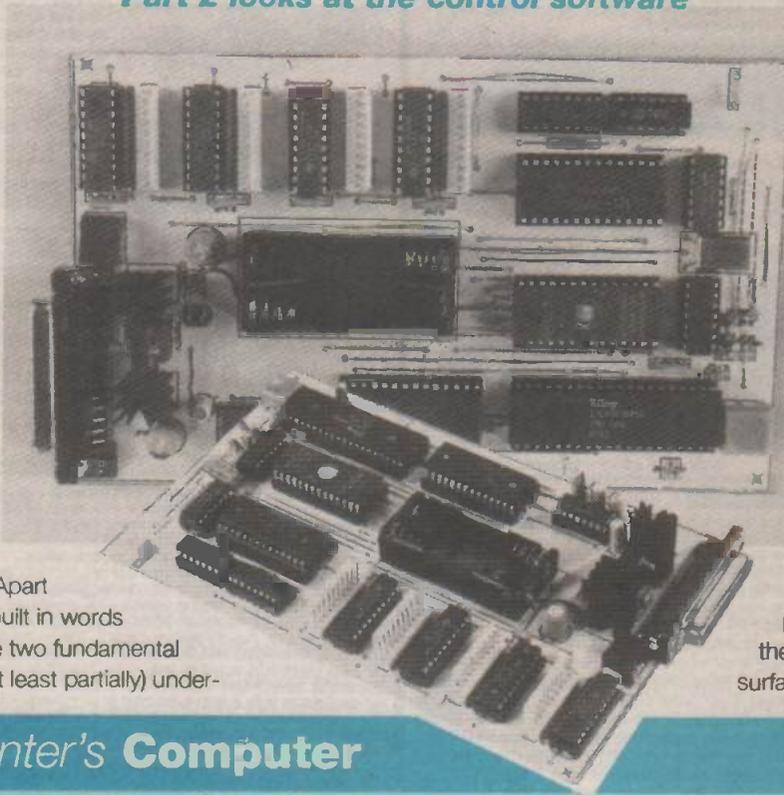Jim Spence's project to build a low cost FORTH control computer. Part 2 looks at the control software



stood - the stack and post fix notation.

```
ok [H]
12 ok-1 [H]
20 30 ok-3 [H]
.S
top
 30
 20
 12
ok-3 [H]
```

The Stack

The most fundamental thing about the FORTH language is the stack. Think of this as the spring loaded plate holder at a self service restaurant. As you take a plate from the stack of plates, the others rise and the next one comes to the surface. If you put a plate onto

An *Experimenter's* Computer

As no doubt many readers will have realised, this project is a very versatile, low cost microprocessor system. If you shop around for the components and make your own PCB, then it should cost under £25 to build. This means that this system is an ideal building block for use in constructing a wide range of different microprocessor based applications, from the friendly robot to the intelligent home minder system.

For many such applications FORTH is an ideal programming language, especially Jim Spence's version with its in-built Z-80 assembler. FORTH may be a hard language to learn, but if you are prepared to take the time to do so, then I am sure you will find it well worth the effort.

If you do not want to use FORTH, then this is still a very useful board. Z-80 code can be written and assembled using the TASM assembler included on the free disk with the March issue of ETI. Or, of course, it could be assembled with the FORTH assembler. In either case, the code could be blown onto an EPROM, which would then be used in place of the FORTH EPROM used in this system.

It is the availability of good quality standard building blocks like this system which can make the design of an electronics system, especially one using a microprocessor, so much easier. In future issues, we will be showing how to construct other add-on components, such as a keyboard and an alphanumeric LCD display. Yet more valuable building blocks for the MPU user.

the stack, the other plates are pushed down. Instead of plates, we use numbers, 16 bit numbers to be precise and the first one in is the last one to come out.

To get a feel of this type 12 (greater than)ent(less than) ((greater than)ent(less than) is the enter or return key on your terminal). The board will respond with ok-1 [H], the 1 meaning there is one item on the stack and the [H] indicating that the numbering 'BASE' is set to HEX. Now type 20 (greater than)space(less than) 30 (greater than)ent(less than) and the response should be ok-3 [H], meaning there are three items on the stack. To verify the contents of the stack type .s (dot-s) - see Box 1

The .s (dot-s) prints out the stack contents and we can see that the top of the stack is 30, which was the last one in and the bottom of the stack is 12, which was the first one in. The basic unit of language in FORTH is the WORD and .s (dot-s) was one of these words. Most words consume one or more items of stack. Try . (dot). The function of this word is to print the number on top of the stack to the terminal. Notice now that you have only two items left on the stack.

Postfix Notation

I suppose this is what puts most people off even trying this language, but it is well worth the effort of getting to grips with. So what is it? Well, in normal algebra, we use the INFIX notation, i.e. $2 + 2 = 4$. The bit that does the work, the '+' sign, is in-between the numbers, hence infix. PREFIX languages such as LISP have the operator in front of the number, i.e. $+ 2 2$. The space between the 2s distinguish them from a twenty-two. As you may have guessed by now, in POSTFIX the operator comes after the numbers, i.e. $2 2 +$. This notation does, believe it or not, have advantages over the infix notation, but readability is not one of them. The best way of looking at it is to say that the job of the '+' is to take two items from the stack, add them up and leave the result on the stack. You can try this by entering 2 (greater than)space(less than) 2 (greater than)ent(less than) OR 2 (greater than)ent(less than) 2 (greater than)ent(less than) which will put two 2s on the stack. Notice that either the enter key OR a space will act as a separator (delimiter) between items. Now type + and then . (dot) to view the result. As you can see the '+' did its job.

```
2 2 ok-2 [H]
+ ok-1 [H]
. 4 ok [H]
```

Input Output

Now to get to some real control stuff and test the board at the same time. Taking output first and referring to Table 1, we can see that IC8 is an 8 bit output port at address 0. The word for output is P! (p-store). This word expects two items on the stack, the first being the value you want to output and the second, or top item, the address where you want the first item to go. Incidentally, although the words are shown in upper case, this version of FORTH is not case sensitive.

Type 0 0 P! (greater than)ent(less than) and all the lines of the port should go low. Now type FF 0 p! and all the lines should go high. Check this with an LED, meter or logic probe.

The default number system of this board is HEX, but if you prefer to work in decimal, simply type DECIMAL and the above instructions would translate to 0 0 p! and 255 0 P! respectively. You can work in any numbering system you like, by altering the variable BASE. For example typing 2 BASE 1 (two-base-store) will place the value 2 into the variable BASE - now you will be

working in binary.

The word for input is P(at sign) (p-fetch). This requires the address of the port on the stack. P(at sign) will replace the address given on the stack with the contents of the address. IC7 has an address of 4, try 4 P(at sign) (greater than)ent(less than) and then print the contents out with . (dot). With nothing connected, this usually returns FF or 0. Try the same thing again, keeping one line held low and observe the results. Don't go overboard on this just yet, as adjacent lines tend to pick up each other values.

Writing Your Own Words

The real power of this language is being able to write your own words. We do this with the : (colon) and ; (semi-colon) words. In the above input example, we can define a word, say INA, which will input the port at address 4. This is done as follows

```
: INA 4 P(at sign) ;
```

The board will respond with an 'ok'. Note that there must be a space between the : and the INA. We can now use this word by simply typing INA, which will leave the contents of the port on the stack which we can look at by typing . (dot). Once defined, it can be used in other colon definitions. For example, suppose we wanted to see the contents of the port rather than leave it on the stack. We can define a word as follows

```
: .INA . ;
```

Again the board will respond with an 'ok'. I have called the new word .INA (dot-ina), by convention words that print something usually begin with a dot. The action of the word is to use INA to get the contents and then print them out using the . (dot) word. Now, when we type .INA, the contents of the port are printed at the terminal.

In a similar way, we can write a word to output to port address 0 by typing

```
: OUTA 0 p! ;
```

I have called this word OUTA. In this case, when using the word we have to be careful because OUTA expects you to put the value you want to output onto the stack before calling it. So, 3 OUTA (greater than)ent(less than) would put lines 0 and 1 high and the rest low. Now try the following code

```
: REFLECT
  BEGIN
    KEY? IF ABORT ENDIF
    INA OUTA
  AGAIN
; ok [H]
```

In the above word REFLECT, the output port will reflect the input port, until you press a key at the terminal. If you hold line 0 low on the input, the output will also go low. The words BEGIN AGAIN would normally keep the word REFLECT in an endless loop, but each time it goes round, the terminal is tested with the word KEY?. This will return a TRUE value if a key has been pressed at the terminal, thus activating the IF word and aborting the program.

To understand this and the operation of the stack, KEY? will either put a 0 or 1 onto the stack. After this, IF consumes the top value of the stack which will, of course, be either a 0 or 1

left by KEY?. If the value is 0 (false) then nothing happens and the IF is bypassed. If the value is 1 then the words between IF and ENDIF will be executed. In this case it is ABORT.

Once again be careful - to see the true results you must control all the lines. The HC devices are very sensitive to signals on adjacent lines.

Warm and Cold Start

The first time the board is switched on with undetermined contents in the RAM, the firmware will initialise with a cold start, ready to receive your programs. After this, with the battery connected, pressing reset or switching off and on again, the board will perform a warm start. Anything you have programmed into the board will remain intact, ready to use again. If you want to start again, you can type the word COLD, which will perform a cold start, or disconnect the battery, switch off and then on again, although with this method I found I had to short out the power supply pins to the RAM in order to make it forget!

Loading Programs

After a while, you will want to write down the programs you write and use a text editor. It's not practical to type everything in at the terminal, as this is error prone and laborious. All COMMS programs will upload text files after some fashion or another and I used the Terminal program provided free with Windows and the notepad as a text editor, also provided free with Windows. A word of warning here, TABS are not recognised by the board and will cause an error, so make sure you use spaces, or that the text editor converts the tabs to spaces, Notepad doesn't.

The COMMS program should be set to send one line at a time and then wait for a control A (hex 01) before sending another line. Terminal can be set to do this and so can QMODEM, a shareware COMMS program.

At the terminal, type LOAD and the board will wait for you to send the file. If you change your mind simply type (greater than)ent(less than) and then ;end (semi-colon-end) which will terminate the file transfer. As an example type the following into the text editor

```
\ Alternate pulse all
output lines
```

```
: outa 0 pl ;      (
output port A )
```

```
: delay f00 0 do loop
```

```
; ( short delay )
```


```
: pulse          ( Pulse all round )
  FF 0 do        ( 0 to FF )
    delay        ( delay )
    i outa       ( get number and output )
    loop         ( again )
```

```
;
;end
```

The word PULSE will step through all the combinations from 0 to 255. The words OUTA and DELAY must have been previously defined. Comments can take two forms, anything following a slash \ ON THAT LINE will be ignored and anything in brackets-space will be ignored. Note that it is a bracket followed by a space, not simply a bracket and likewise a closing bracket followed by a space terminates the comment.


The DO — LOOP structure is very similar to the FOR NEXT loop in BASIC. The 'i' is the index and when used it places the current index on the stack. So, the first time round i will place 0 on the stack, the next time 1 and so on. We have already seen the action of OUTA, which is to take a value from the stack and output it. The final ;end terminates the loading and is only required when uploading files from the terminal.

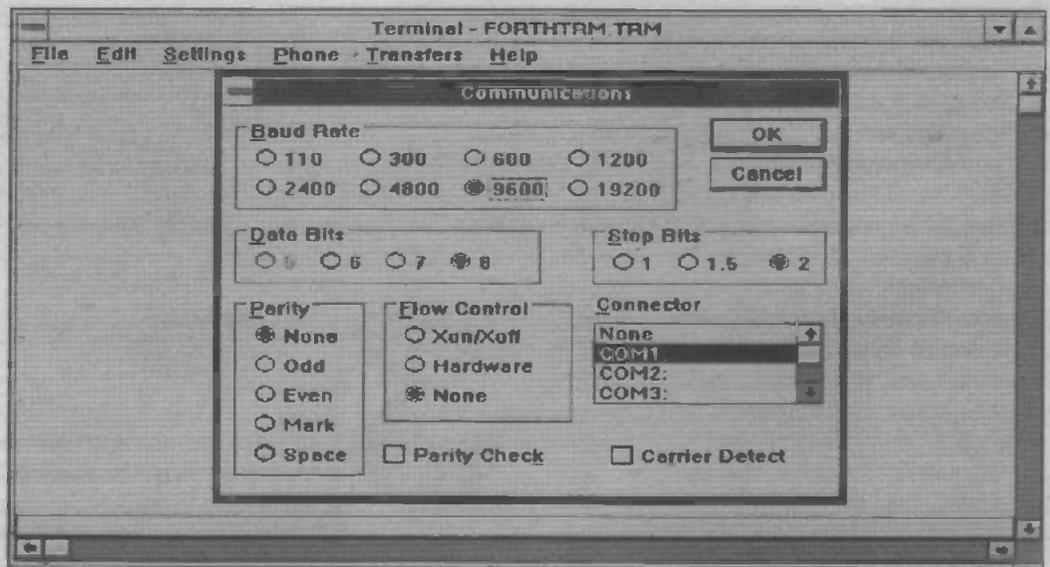Type LOAD and you will get a message, then start your




Terminal set-up in Windows

Forth power-up screen

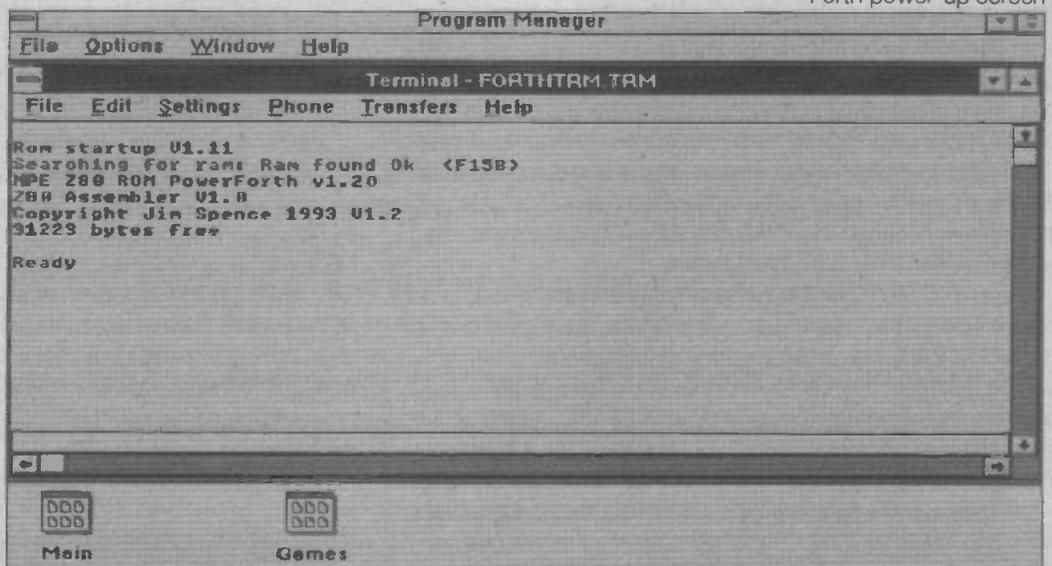

POWERFUL SCHEMATIC CAPTURE, PCB DESIGN AND AUTOROUTING ALL FOR JUST £395

PROPAK AR provides all the features you need to create complex PCB designs quickly and easily. Draw the circuit diagram using the powerful facilities of ISIS DESIGNER+ and then netlist into ARES AUTOROUTE for placement, autorouting and tidy up. Advanced real time design rule checks guarantee that the final PCB will correspond exactly with the schematic thus saving you from costly layout errors and time consuming debugging.

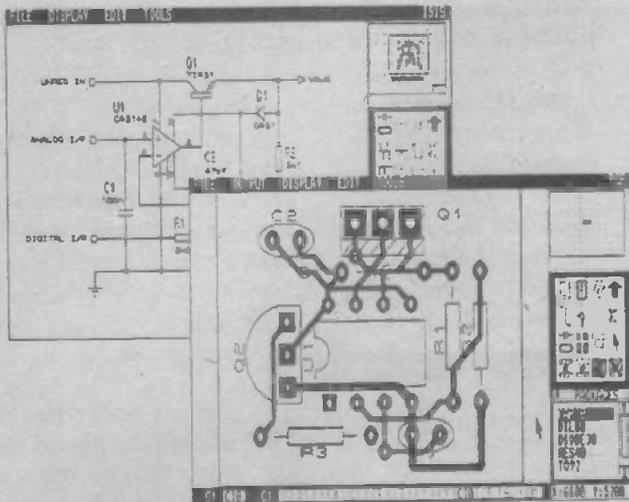

- Attractive, easy to use graphical interface.
- Object oriented schematic editor with automatic wire routing, dot placement and mouse driven place/edit/move/delete.
- Netlist generation for most popular CAD software.
- Bill of Materials and Electrical Rules Check reports.
- Two schemes for hierarchical design.
- Automatic component annotation and packaging.
- Comprehensive device libraries and package libraries including both through hole and SMT parts.
- User definable snap grids (Imperial and metric) and Real Time Snap to deal with tricky SMT spacings.
- Manual route editing features include Auto Track Necking, Topological editing and Curved tracks.
- Autorouting for single, double and multi-layer boards.
- Non autorouting PROPAK is available for just £250 if you do not need or want the router.
- Full connectivity and design rule checking.
- Power plane generator with thermal relief necking.
- Graphics support to 800x600 Super VGA.
- Output to dot matrix and laser printers, HP and Houston plotters, Postscript devices, Gerber and Excellon NC machines plus DXF and other DTP file formats.

CADPAK

Two Programs for the Price of One

ISIS SUPERSKETCH

A superb schematic drawing program for DOS offering Wire Autorouting, Auto Dot Placement, full component libraries, export to DTP and much more.

**Only
£79**

Exceptionally easy and quick to use. For example, you can place a wire with just two mouse clicks - the wire autorouter does the rest.


PCB II

High performance yet easy to use manual PCB layout package. Many advanced features including curved tracks, auto track necking, DXF export, Gerber and NC file generation, Gerber viewing and more.

Alan Chadwick writing in ETI (January 94) concluded... "At £79 I thought this was an excellent buy."

ISIS ILLUSTRATOR

Schematic Drawing for Windows

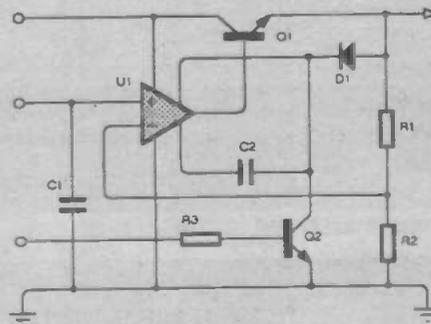

**From
£99**

Running under Windows 3.1, ISIS ILLUSTRATOR lets you create presentation quality schematic drawings like you see in the magazines. Furthermore, when the drawing is done, transferring it to another document is just a matter of pasting it through the Clipboard.

Now used by a number of prominent technical authors to illustrate their latest books and magazine articles.

Labcenter
Electronics



Call us today on 0274 542868 or fax 0274 481078 for a demo pack - state DOS or Windows. Multi-copy and educational discounts available.

Prices exclude p&p (£5 for U.K.) and VAT. All manufacturers' trademarks acknowledged.

14 Mariner's Drive, Bradford, BD9 4JT.

upload. As each line is loaded, it is echoed to the terminal. This is useful if you have any errors, as you can more easily see what caused the error. You can switch this off by typing LOG-OFF first. Only dots will appear as lines are loaded and this will speed up the transfer.

You may have noticed by now that if you define a word twice you get a warning. This is simply a reminder to yourself that you are using the same word twice. There is a word FORGET, which is used in the form FORGET WORD, which will do just that.

```
ok [H]
forget pulse ok [H]
```

I hope you will notice that almost every line I have given is commented. Get into this habit, it takes a little longer loading but occupies no program space on the board. Six months later your programs have a chance of making some sense.

The Assembler

FORTH, because it is compiled, is much faster than BASIC. However, nothing is as fast as the native machine code and in some instances strict timing may be required, which can only be achieved at machine level.

Traditionally, FORTH assemblers have used Postfix notation and so ld a,12 becomes a, # 12 ld. Again this has its advan-

tages but I find assembler hard enough without having to translate it to this odd notation. The assembler included in this firmware is very close to a standard assembler, so ld a,12 becomes ld a,12, i.e. it's the same. The main differences are

- Comments are preceded by \ and not by a ;
- Labels are preceded by L: example L: label
- EQU is not supported
- The BIT instructions are not supported (use AND, OR instead)
- Numbers must be in upper case, i.e. A34D not a34d. The first is taken to be a number the second is a label.
- CREATE and ;CODE not fully implemented
- Labels are truncated to 6 characters and the maximum number of labels in any one word is 10

FORTH uses BC, IX, SP and IY. These must be preserved if you want to use them and return back to FORTH.

A Simple Example

```
:code plus
    pop hl          \ Get top item
    pop de          \ get next item
    add hl,de       \ Add them
    push hl         \ put result on
stack
;end-code
```


Define a word called PLUS, which takes the top two items from the stack, adds them together and places the result on the stack (i.e. same as '+')

Use in the form 2 2 plus. Note now how the word PLUS is defined within :code (colon-code) and ;end-code (semi-colon endcode) These are directly equivalent to the colon and semi-colon used for defining FORTH words. In the example, notice how the machine stack is used for storing the values. The DE register can be used freely and the HL register can be used, but only in the same definition.

A More Complex Example


```
\ Assembler example

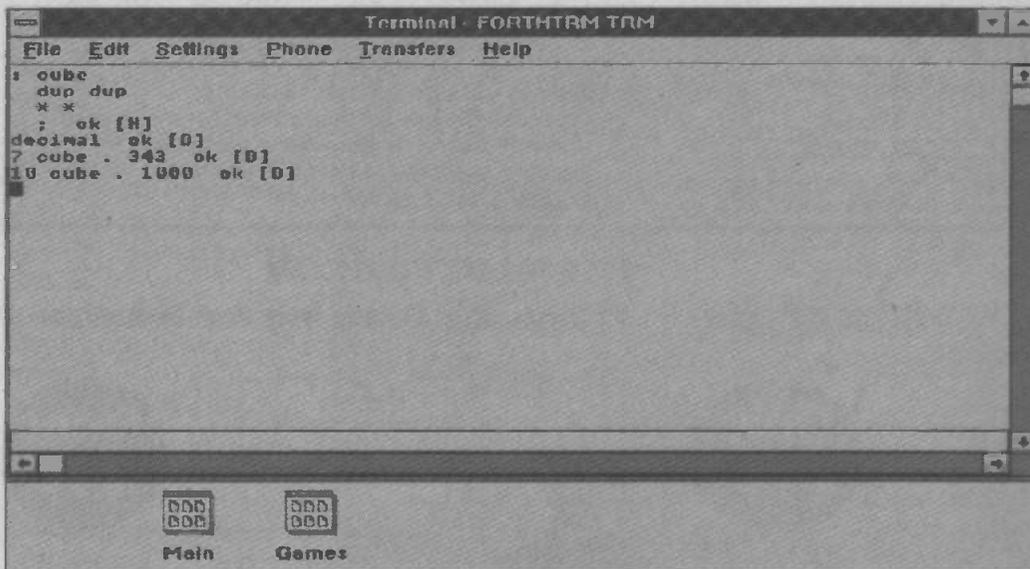\ This code will wait
until input port bit
0
\ goes low
:code waita
l: waitl
\ define a label
in a,(4)
```



Forth program to cube a number

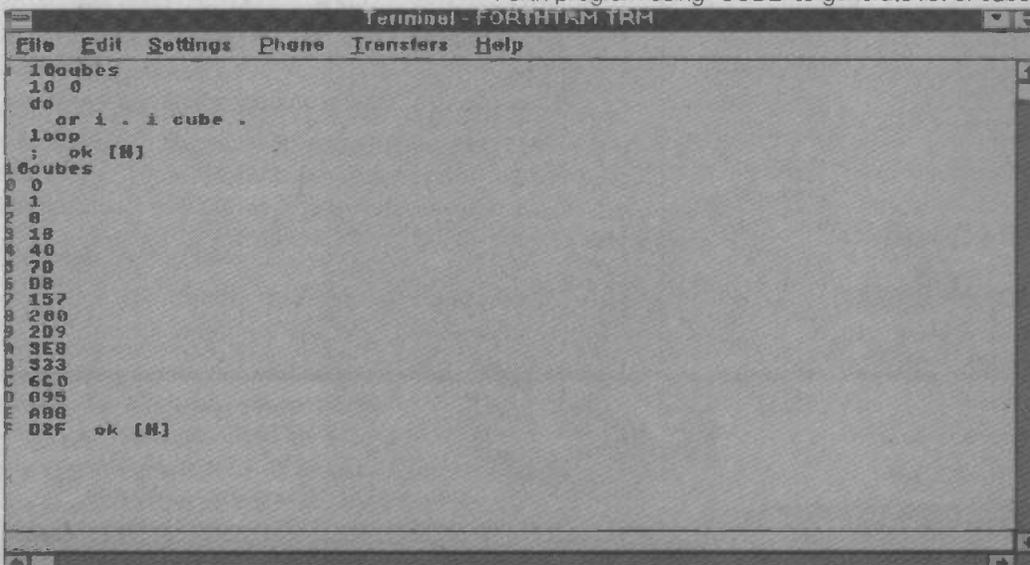Forth program using 'CUBE' to generate list of cubes




```

\ Get input port A
  and 1          \ mask all but bit 0
  jr  nz,wait1  \ wait until bit 0 goes
low
;end-code

: test
  cr ." Waiting for input"
  waita
  cr ." Input occurred"
;
;end

```

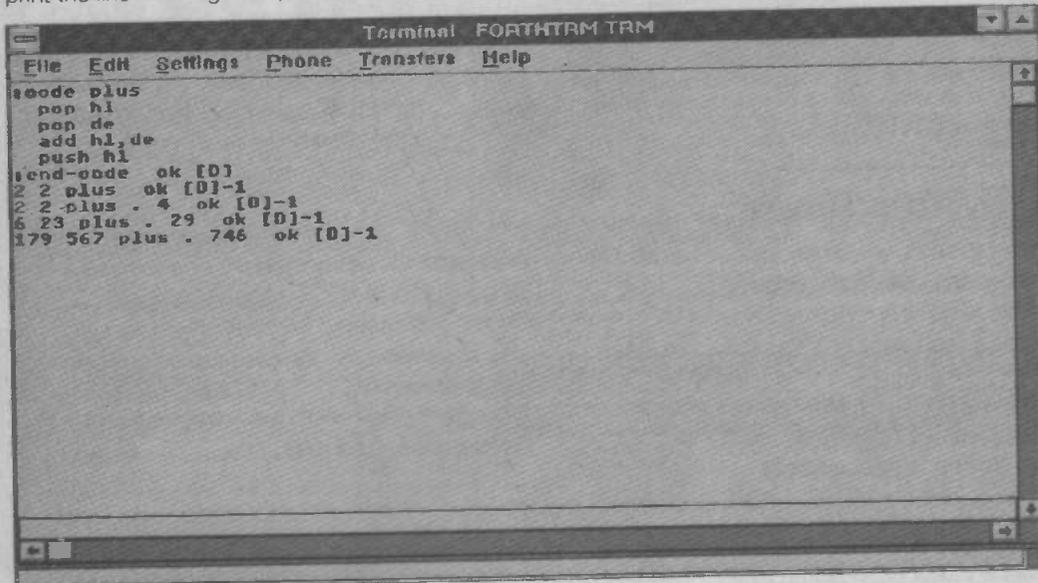In the above example, when you type TEST the machine will print the line 'Waiting for input' and hang until bit 0 of port A




Z80 assembly code programming in Forth

goes low, when the other message will occur, 'Input occurred'. The things to notice about this are that the assembler is defined between :code and ;end-code and you can call assembly code the same way you can call a FORTH word. Incidentally, you could have typed WAITA itself - there is no requirement to call it from another FORTH word. Two new words have been introduced and these are CR, which is simply carriage return and ." (dot-quote) which prints to the terminal the text between the quotes. Note that there must be a space after the ."

Stand Alone Running

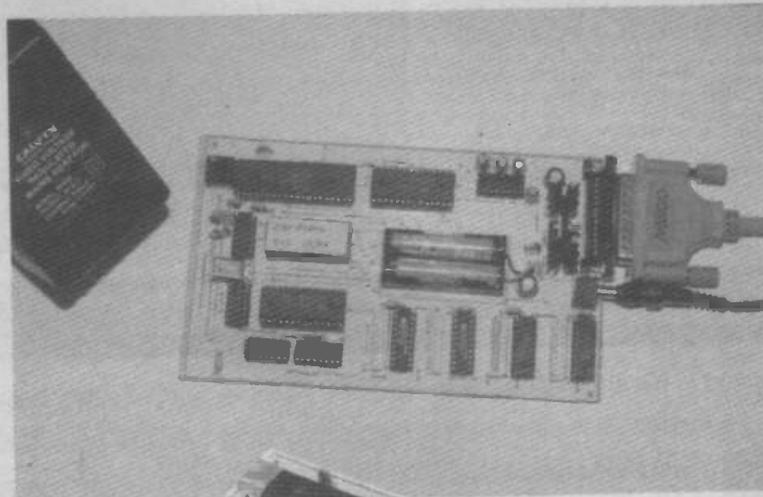As you have, seen the board does not forget anything you have done unless the battery goes flat, you use the word FORGET or you type COLD to initiate a cold start. There is a



Conclusion

The words used in FORTH are like key words and functions in BASIC and a list of these words is called a glossary. There are many books written about FORTH and this implementation follows, with some exceptions, the 83 standard of direct threaded code. Most of the words found in a glossary in one of these books have been implemented. Table

further enhancement with this, in that it can be made to perform a word of your choice at start up. All FORTH applications eventually culminate in one word which runs the application, no matter how big the program is. In a serious application, this word will be a closed loop program which may or may not involve the terminal. In fact, all you need to do is add a keyboard and a display to this board, along with some software and you have a portable terminal.

For this example, we will not have a closed loop application but one that simply signs on and lets you get on with the normal running of the board

\ Sign on message example

: application

```

CR CR
." This is my sign
on message "
CR
;

```

Type in the above and test it by typing the word APPLICATION. You should see the sign on message. To make the word, "APPLICATION" run at switch on or reset, you need to do two things.

- 1) Type ASSIGN APPLICATION TO-DO JOB (greater than)ent(less than)
- 2) Type AUTO (greater than)ent(less than)

Auto will give you a reminder to do number 1, it does not matter which order you do them in. Now press reset, or switch off then on again and your message will appear.

You may assign another word to JOB at any time after this to run a different application. If you want to switch off the automatic running of the program, then type AUTO-OFF or COLD.

2 shows words which will only be found on this board. The FORTH was compiled into ROM using a cross compiler supplied by MPE Engineering, 133 Hill Lane, Shirley, Southampton, Telephone 0703 631441. Books and other FORTH systems can be obtained from this company. The Assembler has been added by myself and I have removed the words concerning disk access, which are not applicable for this board. The auto running and loading extensions have also been added by myself. The compiled code occupies just under 20k with the assembler taking over half of this space.


On a personal note, I would recommend FORTH for

experimenting with devices to see how they work. A good example of this is stepper motors. Its surprising how much you can learn about their characteristics by using FORTH to try 'what if' situations. As far as largish applications are concerned, I find that for some reason FORTH tends to get out of hand and I prefer to use assembler.

One of the major criticisms of FORTH is that it produces 'write only' code. I can only agree with this as, even if you

document your code fairly well, you can do such complex things that it is difficult to read later on.

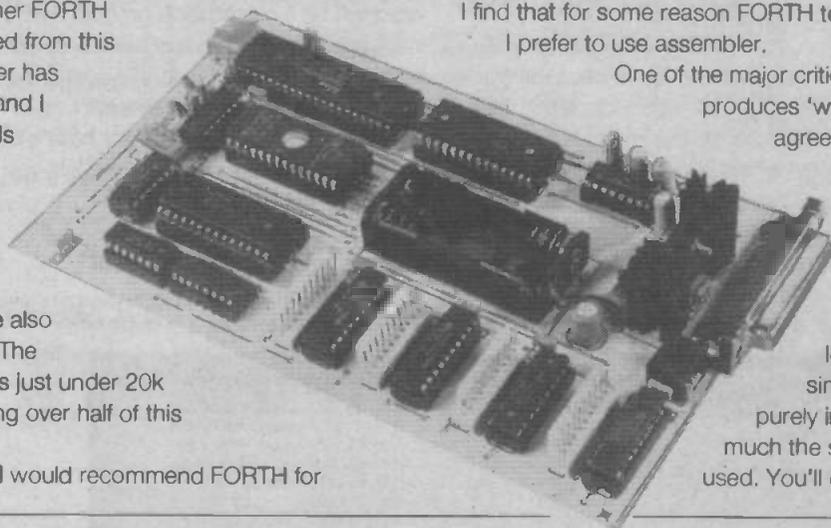FORTH is such a challenge that it is possible to simply develop programs as purely intellectual exercises, in much the same way as pure maths is used. You'll either love it or hate it.



Words only used by this board.

LOAD	Waits for the terminal to send words until an error is encountered or the input is terminated by ;END. To give the compiler time to respond, the terminal should not send another line until it receives a CTRL A (hex 01).	LOG-OFF	After using this word, during a file transfer the file contents will NOT be echoed to the screen. Each line transferred will be replaced by a dot.
;END	Correctly terminates a serial file transfer.	HLOAD	This will load a machine code file in INTEL HEX format to memory.
LOG-ON	After using this word during a file transfer, the file contents will be echoed to the screen.	AUTO	Activates the automatic word start up (see text).
		AUTO-OFF	Reverses the effect of AUTO

The firmware for this project can be supplied on a 32k EPROM, direct from the author at the address given below. The price is £15 including P&P (no VAT) and this includes a 3.5in MS-DOS disk with a text file containing the documentation to go with the EPROM. For an extra £2, the documentation can be supplied on paper.

Jim Spence,
1 Gerard Avenue,
Morley,
Leeds LS27 9LZ.

Next Month...

We continue this project with the construction of a hex keypad & LCD display

Don't miss it!

FORTH - The Language

As Jim Spence has already stated in his article, FORTH is extremely powerful and versatile, but unfortunately not an easy language to learn. To make matters worse there is also very little readily available published literature on the language. I am therefore printing a list of the standard FORTH commands.

When using this command list, the first thing to note is that FORTH is a stack oriented language, and the columns marked 'uses' and 'leaves' shows how the execution of that command affects the top of the stack. When writing FORTH programs it is very important that the programmer keeps track of stack usage, hence in the notes that follow each command there is an indication of the state of the stack before and after the command's execution.

It should be said that this is not an exhaustive list of FORTH commands, there are many more than this. But it should give readers some indication of how the language looks and behaves. Over the coming months, we will have several projects using this board and these will come with the appropriate FORTH control programs, which can be used as the software building blocks for more sophisticated applications.


Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

Surplus always wanted for cash!

LOW COST PC SPECIALISTS - ALL EXPANDABLE - ALL PC COMPATIBLE

8088 XT - PC99

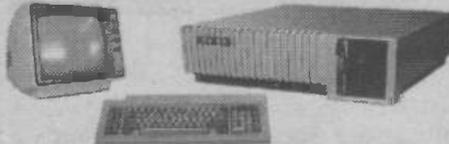

- 256k RAM - expandable to 640k
- 4.7 Mhz speed
- 360k 5-1/4" floppy
- 2 serial & 1 parallel ports
- MS-DOS 4.01
- Factory burnt-in
- Standard 84 key keyboard
- 12" green screen included
- In good used condition

Optional FITTED extras: 640K RAM £39. 12" CGA colour monitor with card £39. 2nd 5-1/4" 360K floppy £29.95. 20 mbyte MFM hard drive £99.

Only £99.00 (F)

FLOPPY DISK DRIVES

5 1/4" from £22.95 - 3 1/2" from £21.95!

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported).

- 3.5" Panasonic JU363/4 720K or equivalent £29.95(B)
- 3.5" Mitsubishi MF355C-L 1.4 Meg. Laptops only £29.95(B)
- 3.5" Mitsubishi MF355C-D 1.4 Meg. Non laptop £29.95(B)
- 5.25" EXTRA SPECIAL BRAND NEW Mitsubishi MF501B 360K. Absolutely standard fits most computers £22.95(B)

* Data cable included in price.

- Shugart 800/801 SS refurbished & tested £175.00(E)
- Shugart 851 double sided refurbished & tested £275.00(E)
- Mitsubishi M2894-63 double sided switchable hard or soft sectors - BRAND NEW £250.00(E)

Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply! Ideal as exterior drives! £499.00(F)
End of line purchase scoop! Brand new NEC D2246 8" 85 megabyte of hard disk storage! Full CPU control and industry standard SMD interface. Ultra hi speed transfer and access time leaves the good old ST506 interface standing. In mint condition and comes complete with manual. Only £299(E)

THE AMAZING TELEBOX!

Converts your colour monitor into a QUALITY COLOUR TV!



TV SOUND & VIDEO TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by manufacturers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD and many more. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable "off air" UHF colour television or video channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Composite and RGB video outputs are located on the rear panel for direct connection to most makes of monitor. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

- Telebox ST for composite video input monitors £32.95
- Telebox ST as ST but with integral speaker £36.50
- Telebox MB as ST with Multiband tuner VHF-UHF-Cable, & hyperband for overseas PAL versions state 5.5 or 6mhz sound specification. £69.95
- Telebox RGB for analogue RGB monitors (15khz) £69.95

Shipping code on all Teleboxes is (B)
RGB Telebox also suitable for IBM multisync monitors with RGB analog and composite sync. Overseas versions VHF & UHF call. SECAM / NTSC not available.

No Break Uninterruptable PSU's

Brand new and boxed 230 volts uninterruptable power supplies from Densel. Model MUK 0565-AUAF is 0.5 kva and MUD 1085-AHBH is 1 kva. Both have sealed lead acid batteries. MUK are internal, MUD has them in a matching case. Times from interrupt are 5 and 15 minutes respectively. Complete with full operation manuals.....MUK.....£249 (F) MUD.....£525 (G)

286 AT - PC286



- 640k RAM expandable with standard SIMMS
- 12 Mhz Landmark speed
- 20 meg hard disk
- 1.2 meg 5-1/4" floppy
- 1.4 meg 3-1/2" floppy
- EGA driver on board
- 2 serial & 1 parallel ports
- MS-DOS 4.01
- Co-processor socket
- Enhanced 102 key keyboard
- Clock & calendar with battery back up

BRAND NEW AND BOXED!

Only £249.00 (F)

The Philips 9CM073 is suggested for the PC286 and the CM8873 for the PC386. Either may use the SVGA MTS-9600 if a suitable card is installed. We can fit this at a cost of £49.00 for the PC286 and £39.00 for the PC386.

POWER SUPPLIES

Power One SPL200-5200P 200 watt (250 w peak). Semi open frame giving +5v 35a, -5v 1.5a, +12v 4a (8a peak), -12v 1.5a, +24v 4a (6a peak). All outputs fully regulated with over voltage protection on the +5v output. AC input selectable for 110/240 vac. Dims 13" x 5" x 2.5". Fully guaranteed RFE. £85.00 (B)

- Power One SPL130. 130 watts. Selectable for 12v (4A) or 24v (2A). 5v @ 20A. ±12v @ 1.5A. Switch mode. New. £59.95(B)
- Astec AC-8151 40 watts. Switch mode. +5v @ 2.5a. +12v @ 2a. -12v @ 0.1a. 6-1/4" x 4" x 1-3/4". New. £22.95(B)
- Greendale 19AB0E 60 watts switch mode. +5v @ 6a. ±12v @ 1a. +15v @ 1a. RFE and fully tested. 11 x 20 x 5.5cms. £24.95(C)
- Conver AC130. 130 watt hi-grade VDE spec. Switch mode. +5v @ 15a. -5v @ 1a. ±12v @ 6a. 27 x 12.5 x 6.5cms. New. £49.95(C)
- Boshert 13090. Switch mode. Ideal for drives & systems. +5v @ 6a, +12v @ 2.5a, -12v @ 0.5a. -5v @ 0.5a. £29.95(B)
- Famell G6/40A. Switch mode. 5v @ 40a. Encased. £95.00(C)
- Famell G24/5S. As above but 24v @ 5a. £65.00(C)

BBC Model B APM Board

WIN £100 CASH!
£100 CASH FOR THE MOST NOVEL DEMONSTRABLE APPLICATION!

BBC Model B type computer on a board. A major purchase allows us to offer you the PROFESSIONAL version of the BBC computer at a parts only price. Used as a front end graphics system on large networked systems the architecture of the BBC board has so many similarities to the regular BBC model B that we are sure that with a bit of experimentation and ingenuity many useful applications will be found for this board! It is supplied complete with a connector panel which brings all the I/O to 'D' and BNC type connectors - all you have to do is provide +5 and ±12 v DC. The APM consists of a single PCB with most major ic's socketed. The ic's are too numerous to list but include a 6502, RAM and an SAA5050 teletext chip. Three 27128 EPROMS contain the custom operating system on which we have no data. On application of DC power the system boots and provides diagnostic information on the video output. On board DIP switches and jumpers select the ECONET address and enable the four extra EPROM sockets for user software. Appx. dims: main board 13" x 10". I/O board 14" x 3". Supplied tested with circuit diagram, data and competition entry form.

Only £29.95 or 2 for £53 (B)

SPECIAL INTEREST

- Trio 0-18 vdc bench PSU. 30 amps. New £ 470
- Fujitsu M3041 600 LPM band printer £2950
- DEC LS/02 CPU board £ 150
- Rhode & Schwarz SBUF TV test transmitter 25-1000mhz. Complete with SBTFF2 Modulator £6500
- Calcomp 1036 large drum 3 pen plotter £ 650
- Thurlby LA 160B logic analyser £ 375
- 1.5kw 115v 60hz power source £ 950
- Anton Pillar 400 Hz 3 phase frequency converter 75Kw POA
- Newton Derby 400 Hz 70 Kw converter POA
- Nikon PL-2 Projection lens meter/scope £750
- Seikonid SD 150H 18 channel Hybrid recorder £2000
- HP 7580A A1 8 pen high speed drum plotter £1850
- Kenwood DA-3501 CD tester, laser pickup simulator £ 350

BRAND NEW PRINTERS

- Microline 183. NLQ 17x17 dot matrix. Full width. £139 (D)
- Hyundai HDP-920. NLQ 24x18 dot matrix full width. £149 (D)
- Qume LetterPro 20 daisy. Qume QS-3 interface. £39.95 (D)
- Centronics 152-2 9 x 7 dot matrix. Full width. £149 (D)
- Centronics 159-4 9 x 7 dot matrix. Serial. 9-1/2" width £ 99 (D)

386 AT - PC386



- 2 meg RAM expanded by slots
- 20 Mhz with 32k cache. Expandable to 64k
- 40 meg hard disk
- 1.2 meg 5-1/4" floppy
- VGA card installed
- 2 serial & 1 parallel ports
- MS-DOS 4.01
- Co-processor socket
- Enhanced 102 key keyboard
- Kwik Disk Accelerator Software - FREE

BRAND NEW AND BOXED!

Only £425.00 (F)

MONITORS

- 14" Forefront Model MTS-9600 SVGA multisync with resolution of 1024 x 768. 0.28 pitch. "Text" switch for word processing etc. Overscan switch included. Ideal for the PC-386 or PC-286 with SVGA card added. Also compatible with BBC, Amiga, Atari (including the monochrome high resolution mode), Archimedes etc. In good used condition (possible minor screen bums). 90 day guarantee. 15" x 14" x 12". Only £159(E)
- 14" Philips Model CM8873 VGA multisync with 640 x 480 resolution. CGA, EGA or VGA, digital/analog, switch selectable. Sound with volume control. There is also a special "Text" switch for word processing, spreadsheets and the like. Compatible with IBM PC's, Amiga, Atari (excluding the monochrome high resolution mode), BBC, Archimedes etc. Good used condition (possible minor screen bums) 90 day guarantee. 15" x 14" x 12". Only £139(E)

Philips 9CM073 similar (not identical) to above for EGA/CGA PC and compats. 640 x 350 resolution. With Text switch with amber or green screen selection. 14" x 12" x 13-1/2". £99(E)

KME 10" high-definition colour monitors. Nice tight 0.28" dot pitch for superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13.5" x 12" x 11". Also works as quality TV with our Hitab Telebox. Good used condition. 90 day guarantee. Only £125 (E)
KME as above for PC EGA standard £145 (E)
Brand new Centronic 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 Mhz bandwidth. A super monitor in attractive style moulded case. Full 90 day guarantee. Only £129 (E)
NEC CGA 12" IBM-PC compatible. High quality ex-equipment fully tested with a 90 day guarantee. In an attractive two tone ribbed grey plastic case measuring 15" L x 13" W x 12" H. The front cosmetic bezel has been removed for contractual reasons. Only £69 (E)

20" 22" and 26" AV SPECIALS
Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attractive teak style case. Perfect for Schools, Shops, Discos, Clubs. In EXCELLENT little used condition with full 90 day guarantee. 20"....£135 22"....£155 26"....£185 (F)

CALL FOR PRICING ON NTSC VERSIONS!

Superb Quality 6 foot 40u

19" Rack Cabinets

Massive Reductions

Virtually New, Ultra Smart!

Less Than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half covered back door and removable side panels. Fully adjustable internal fixing struts, ready

punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels or stand singly. Overall dimensions are 77-1/2"H x 32-1/2"D x 22"W. Order as:
Rack 1 Complete with removable side panels.....£275.00 (G)
Rack 2 Less side panels£145.00 (G)

1992 Winter Issue of Display News now available - send large SAE - PACKED with bargains!

DISPLAY

MAIL ORDER & OFFICES
Open Mon-Fri 9.00-5.30
Dept ET.32 Biggin Way,
Upper Norwood,
London SE19 3XF.

LONDON SHOP
Open Mon-Sat 9-5.30
Thursday till 9.00pm
215 Whitehorse Lane,
South Norwood,
London. SE25.

DISTEL © The Original
Free dial-up database!
1000's of Items+info on line
V21, V22 & V22 bis
081-679-1888

ALL ENQUIRIES
081-679-4414
Fax: 081-679-1927



-ELECTRONICS-

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. PO orders from Government, Universities, Schools & Local Authorities welcome - minimum account order £30. Carriage charges (A)=£2.00. (B)=£3.75. (C)=£9.50. (D)=£11.50. (E)=£14.00. (F)=£18.00. (G)=Call. Scotland surcharge: call. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guarantee for 90 days. All guarantees on a return to base basis. Rights reserved to change prices & specifications without prior notice. Orders subject to stock. Quotations willingly given for higher quantities than those stated. Bulk surplus always wanted for cash.

FORTH - The Language

WORD	USES	LEAVES	NOTES
{!} (store)	2	0	Sees top-of-stack as address of a 2-byte variable and stores second-on-stack in this variable. For example, suppose that address 20000 points to a 2-byte variable; then before: 9 9 -1150 20000 after: 9 9(-1550 is stored in a 1-byte variable.)
{ " }	0	0	{ "HI THERE!" }, when executed, prints HI THERE! on the video display.
{ ' } (tic)	0	1	Puts onto top-of-stack the address of the word that follows it.
{ (}	0	0	{ (THIS IS A COMMENT) }, if included in a definition, will not be compiled; { (} requires a {) } to end the comment
*	2	1	Multiplication; example: before: 9 9 3 5 after: 9 9 15 The word * multiples 5 and 3, leaving 15.
+	2	1	Addition; example: before: 9 9 3 5 after: 9 9 8 The words + adds 5 and 3, leaving 8.
{ . }	1	0	Embeds the number on the top of the stack into a dictionary definition, incrementing the dictionary pointer
-	2	1	Subtraction; example: before: 9 9 3 5 after: 9 9 -2 The word - subtracts 5 from 3, leaving -2.
{ . }	1	0	Displays the number on the top of the stack; example: before: 9 9 3 5 after: 9 9 3 (5 is printed on screen).
/	2	1	Division; example: before: 9 9 13 2 after: 9 9 6 The word / divides 13 by 2, leaving 6 (remainder is lost).
0<	1	1	If top-of-stack is <0, it is replaced with a 1 (true); if top-of-stack is >= 0, it is replaced with a 0 (false); example before: 9 9 3 5 after: 9 9 3 0
1+	1	1	Adds 1 to top-of-stack; example: before: 9 9 3 5 after: 9 9 3 6
{ : ... ; }	*	*	{ : } begins the definition of a word, { ; } ends the definition; example: { : 3* 3* ; } defines the word 3*.
=	2	1	If the two top items on the stack are exactly equal, both of them are removed and replaced with a single 1 (true), if not, both are replaced with a single 0 (false); example: before: 9 9 3 5 after: 9 9 0
<	2	1	If the second item on the stack is less than the top item on the stack, both of them are removed and replaced with a single 1 (true); if not both of them are replaced with a single 0 (false); example: before: 9 9 3 5 after: 9 9 1

FORTH - The Language

WORD	USES	LEAVES	NOTES
>	2	1	Similar to entry for <; example: before: 9 9 3 5 after: 9 9 0 (3 is not less than 5)
{?}	1	0	Sees top-of-stack as address for 2-byte variable; displays value of that variable; using the example for {}, then: before: 9 9 20000 after: 9 9(-1150, contents of 20000, prints on screen).
@ (fetch)	1	1	Sees top-of-stack as address for 2-byte variable and replaces it with value of that variable; using the example in {}: before: 9 9 20000 after: 9 9 -1150 (-1150 is contents of 2-byte variable at 20000).
ALLOT	1	0	Sees top-of-stack as number of bytes to be reserved (and filled in later) during the definition of a word.
AND	2	1	Does an AND operation on the corresponding bits of the top two stack entries (both 16-bit numbers); example: before: 9 9 3 5 after: 9 9 1 (3 AND 5, in binary, is 1).
BASE	0	1	BASE is a 1-byte variable that contains the number base being used; for example, { 2 BASE C } causes all subsequent input and output to be in binary (base 2); execution of this word causes the address of this 1-byte variable to be placed on top-of-stack. After the phrase has been executed, the stack looks like: 9 9 and the word CON, when executed, will place 25140 on the top of the stack.
CR	0	0	Causes the cursor to jump to the beginning of the next line of the display.
{ DO ... LOOP }	2	0	Looping construct that specifies a beginning and an ending-value-plus-one.
DROP	1	0	Drops top entry from stack; example: before: 9 9 3 5 after: 9 9 3
DUP	1	2	Duplicates item on top-of-stack; example: before: 9 9 3 5 after: 9 9 3 5 5
ECHO	1	0	Isolates the low-order byte of the 2-byte entry on top of the stack and writes it to the video display; example: before: 9 9 32 after: 9 9(A space, ASCII decimal 32, is printed.) ECHO is named EMIT in some versions.
FILL	3	0	Fills an area of memory with a given value; for example, { 255 3000 100 FILL } fills memory locations from 3000 thru 3099 (100 bytes) with the value 255.
FORGET	0	0	Causes system to delete all definitions including and after the word following FORGET; for example, { FORGET BASEPGM } causes the system to delete BASEPGM and all FORTH words, variables and constants defined after it.
H	0	1	2-byte variable containing address of the top of the dictionary; execution of this word causes the address of the variable H (not its value, which equals the address of the top of the dictionary) to be placed on top of the stack.
HERE	0	1	Places the address of the next byte in the dictionary (the value of H) on top of the stack.

FORTH - The Language

WORD	USES	LEAVES	NOTES
I	0	1	When executed within a { DO ... LOOP }, the word I pushes onto the top of the stack the value of the index counter; for example: { 10 0 DO I. LOOP } prints the numbers from 0 to 9.
{ IF ... ELSE ... THEN }		1	0 Conditional execution of words depending on value of top-of-stack. If non-zero, execute words between IF and ELSE. If zero, execute words between ELSE and THEN. For example, { IF " NUMBER ON TOP IS NONZERO" ELSE " NUMBER ON TOP IS ZERO" THEN } prints the appropriate message, depending on the value on top of the stack.
KEY	0	1	Gets a single character from the keyboard; for example, if the stack before we press the space bar is: 9 9 3 5 Then, after we press the space bar (ASCII value decimal 32), the stack is: 9 9 3 5 32
MAX	2	1	Compares the two top entries on the stack and leaves only the larger; example: before: 9 9 3 5 after: 9 9 5
MIN	2	1	Compares the two top entries on the stack and leaves only the smaller; example: before: 9 9 3 5 after: 9 9 3
MINUS	1	1	Changes the sign of the entry on top of the stack; example: before: 9 9 3 5 after: 9 9 3 -5
OVER	2	3	Copies the second-to-top entry onto the top of the stack; example: before: 9 9 3 5 after: 9 9 3 5 3
PAD	0	1	PAD is a 2-byte variable that points to the beginning of a 64-byte area for temporary storage of character strings. Execution of this word causes the address of this 2-byte variable to be placed on top of the stack.
SWAP	2	2	Exchanges the two top entries on the stack; example: before: 9 9 3 5 after: 9 9 5 3
U*	2	1	The lower 8 bits of the two top entries on the stack are isolated and multiplied together, leaving their unsigned 16-bit product; example: before: 9 9 3 5 after: 9 9 15 Each factor will effectively be 255 or less, giving a product that will not overflow in 16 bits.
VARIABLE	1	0	Creates a variable that has the value of top-of-stack; example, before executing the phrase { VARIABLE VAR }, the stack looks like: 9 9 -14017 After the phrase has been executed, the stack looks like: 9 9 and the word VAR, when executed, will place the address of the variable on the stack. (The 2-byte number stored at that address will contain the value -14017). Unlike a constant, the value of a variable can be changed using { ! } (store).
{ }			Resumes compilation of a colon definition.



**8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF**
Tel: 0203 650702
Fax: 0203 650773
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

OSCILLOSCOPES

Gould 400 - 20MHz D.S.O. 100 Ms/s	£1000
Gould 4072 - 100MHz D.S.O. 400 Ms/s	£2000
Gould OS4000, OS4200, OS4020, OS245	from £125
Hewlett Packard 1740A, 1741A, 1774A, 1774AA, 100MHz dual ch.	from £350
Hewlett Packard 182C - 100MHz 4 ch.	£350
Hewlett Packard 1707A, 1707B - 75MHz 2ch	from £275
Hewlett Packard 1715A 200MHz with DMM Ch.	£650
Hewlett Packard 1745A 100MHz dual channel (+ DMM)	£450
Tektronix 2201 - 20MHz D.S.O. dual ch.	£675
Tektronix 2246 100MHz-4 channel	(as new) £995
Tektronix 2215 60MHz dual trace	£450
Tektronix 2235 Dual trace 100MHz (portable)	£800
Tektronix 2335 Dual trace 100MHz (portable)	£750
Tektronix 2225 -50MHz dual ch.	£450
Tektronix 465/465B -100MHz dual ch.	from £350
Tektronix 475 - 200MHz dual ch.	£450
Tektronix 468 -100MHz D.S.O. dual ch.	£850
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch	from £300
Tektronix 7704 - 250MHz 4 ch	from £650
Tektronix 7834/7844 - 400MHz 4 ch	from £750
Tektronix 7904 - 500MHz	from £850
Phillips 3070 -100MHz 2+1 channel + cursors, as new	£900
Phillips 3206, 3211, 3212, 3217, 3226, 3240, 3243, 3244, 3261, 3262 (2ch + 4 ch.)	from £125 to £350
Solartron Schlumberger CD1740 - 20MHz 4 ch.	£250

Other scopes available too

SPECTRUM ANALYSERS

Alltech 727 -20GHz	£2200
Advantest TR4131 -10KHz - 3.5GHz	£4500
Hewlett Packard 3580A -5Hz-50KHz	£1250
Hewlett Packard 3585A - 20Hz - 40MHz (GPIB)	£4250
Hewlett Packard 8590A - 10MHz - 1.5GHz - 1.5GHz (as new)	£4500
Hewlett Packard 182T with 8559A (10MHz - 21GHz)	£3750
Hewlett Packard 141T with 8554B/8552B - (1250MHz)	£1500
Marconi 2370 - 110MHz	£1250
Hewlett Packard 4953 Protocol analyser	£2500
Tektronix 7L18 with 7603 main frame 1.5 GHz/18GHz	£3500

MISCELLANEOUS

Anritsu ML93B/ML92B Optical power meter with sensor	£2000
Anritsu ME538C Microwave system analyser (BX + Tx)	£3500
B&K 2511 + 1621 Vibration test set	£2000
B&K 2511 Vibration meter	£1500
B&K 2515 Vibration analyser	£4500
Datron 1061A Autocal digital multimeter (6 1/2 digits)	£850
Datron 1071 Autocal digital multimeter (7 1/2 DIGITS)	£1150
Daymarc 1735 Transistor tester/sorter (with all jigs)	£5000
Dranetz 305 Phase meter	£250
Dymar 1585 AF Power meter	£175
Dymar 2085 AF Power meter	£200
Farnell RB 1030-35 Electronic load 1Kw	£450
Farnell AMM/B Automatic modulation meter	£150
Farnell 2081 R/F Power meter	POA
Feedback TWG300 Test waveform generator	£200
Fischer Betascope 2040/2060 Coating thickness computer & non destructive coating measurement instrument & many jigs and extras	all for £2000
Fluke 8840A Multimeter (1EEE)	£300
Fluke 515A Portable calibrator	£500
Fluke 8010A Digital multimeter	£125
Fluke 8922A True RMS voltmeter	POA
Fluke 95020 Current shunt	POA
Gay Milano FTMIC/FTM3C - FTM - Fast transient monitor	£250
General Rad 1658 LCR Diglbridge	£250
General Rad 1621 Precision capacitance measurement system	POA
Hewlett Packard 180TR Display unit with 8755B swept. amp. an.	£350
Hewlett Packard 3200B VHF oscillator, 10-5000MHz	£175
Hewlett Packard 3325A Synthesizer/function generator	£1450
Hewlett Packard 3400A RMS voltmeter	£150
Hewlett Packard 3406A Broadband sampling voltmeter	£175
Hewlett Packard 3437A System voltmeter	£350
Hewlett Packard 3456A Digital voltmeter	£650
Hewlett Packard 3476 Digital multimeter	£100
Hewlett Packard 347 Digital voltmeter, 4 wire system, 1EEE	£650
Hewlett Packard 3702B/3705A/3710A/3716A Microwave link analyser	£1500
Hewlett Packard 3730A Down converter (with 3738A or 3737A)	£200
Hewlett Packard 3760/3761 Data gen + error detector	each £300
Hewlett Packard 3762/3763 Data gen + error detector	each £350
Hewlett Packard 3777A Challen selector	£250
Hewlett Packard 3779A Primary multiplex analyser	£800

Hewlett Packard 400E/F AC voltmeter	£150
Hewlett Packard 4204A Oscillator 10Hz-1MHz	£250
Hewlett Packard 435A Power meter (less sensor)	£350
Hewlett Packard 456A AC current probe	POA
Hewlett Packard 415E SWR meter	£275
Hewlett Packard 4193A Vector Impedance meter	£3500
Hewlett Packard 5335A Universal counter with 1EE	£1800
Hewlett Packard 5342A Microwave freq. count. 18GHz	£1400
Hewlett Packard 7402 Recorder with 17401A x 2 plug-ins	£300
Hewlett Packard 8005B Pulse generator	£250
Hewlett Packard 8011A Pulse gen. 0.1Hz-20MHz	£500
Hewlett Packard 8013B Pulse gen. 1Hz-50MHz	£750
Hewlett Packard 8012B Pulse generator	£750
Hewlett packard 8406A Frequency comb. generator	£500
Hewlett Packard 8443A Tracking gen/counter with 1EEE	£450
Hewlett Packard 8445B Automatic presetter	£700
Hewlett Packard 8601A 110MHz Gen/sweeper 110MHz	£350
Hewlett Packard 8620C Sweep oscillator mainframe	£250
Hewlett Packard 8750A Storage normaliser	£400
Hewlett Packard 938A Freq. doubler	£250
Keithley 197 20MHz with 1EEE	£400
Lyons PG73N/PG75/PG2B/PG Pulse gnerator	from £225
Marconi 2019A 80KHz-1040MHz sig. gen.	£1800
Marconi 2432A 500MHz digital freq. meter	£2000
Marconi 2337 Automatic dist. meter	POA
Marconi 2356 20MHz level oscillator	£300
Marconi 2306 Programmable interface	£500
Marconi 2610 True RMMS voltmeter	£900
Marconi 2830 Multiplex tester	£1250
Marconi 2831 Channel access switch	£500
Marconi 6920 Power sensor	£400
Marconi 5390 1GHz signal gen.	£1250
Phillips PM 5167 10MHz function gen.	£400
Phillips 5190 LF synthesizer w/th G.P.I.B.	£800
Phillips PM 5519 Colour TV pattern gen.	£400
Phillips PM 2525 Multimeter WF 1EEE	£850
Phillips 5716 Pulse generator high freq. MOS	£600
Phillips PM 5770 Pulse gen. - 1MHz-100MHz	£150
Phillips PM 6672 1GHz timer/counter WF 1EEE	£650
Phillips PM 8272 XYT chart recorder	£500
Photodyne 800 Fibre optic attenuator	£350
Projectina CH9345 Microscope	£800
Racal 9009 Modulation meter	£225
Racal Dana 922 Logic analyser + 68000 disassembler	£250
Racal Dana 9242D Programmable PSU 25V-2A	£300
Racal Dana 9246S Programmable PSU 25V-10A	£400
Racal Dana 3100 40-130MHz synthesiser	£750
Racal Dana 5002 Wideband level meter	£650
Racal Dana 5003 Digital m/meter	£150
Racal Dana 9000 Microprocessing timer/count. 52MHz	£550
Racal Dana 9081 Synth. sig. gen. 520MHz	£550
Racal Dana 9084 Synth. sig. gen. 104MHz	£450
Racal Dana 9303 True RMS/RF level meter	£650
Racal Dana 9341 LCR databridge	£250
Racal Dana 9500 Universal timer/counter 100MHz	£200
Racal Dana 9917 UHF frequency meter 560MHz	£175
Racal Dana 9919 UHF frequency meter 1GHz	£275
Rohde & Schwartz BN36711 Digital Q meter	£400
Solartron Schlumb 1170 Freq. response analyser	£500
Tektronix TM503, SG503, PG506, TG501 Scope callibrator	£2200
Tektronix 834 Data comms analyser	£500
W&G SPM12 Level meter 200Hz-6MHz	£500
W&G PS12 level generator 200Hz-6MHz	£500
W&G SPM60 Level meter 6KHz-18.6MHz	£500
W&G PS60 Level meter 6KHz-18.6MHz	£500
W&G SPM6 Level meter 6KHz-18.6MHz	£250
W&G PS6 Level generator 6KHz-18.6MHz	£250
W&G SPM6 Level meter 6KHz-18.6MHz	£250
Wavetek 157 Programmable waveform synthesiser	£300
Wayne Kerr B424/N LCR Component meter set	£200
Wayne Kerr 4250 LCR meter	(as new) £1000
Wayne Kerr 642 Autobalance universal bridge	£200
Wayne Kerr B905 Automatic precision bridge	£800
Weller D800/D801 Desoldering station	£175
Weller D900 Desoldering station	£150
Wiltron 352 Low freq. differential input phase meter	£350
Wilton 560 Scalar network analyser + 2 heads	£900
Yokogawa 3655 Analyser recoredr	£850

SPECIAL OFFERS - Phoenix 5500A Telecoms analyser, ex. demo. as new with 12 months calibration + 12 months guarantee fitted with V24 interface. A variety of interface options available - Ring/Fax for details. Navtel 9440 Protocol analyser, ex. demo. as new £8000 new - cost now £3500. Navtel 9410 PCB based protocol analyser ex. demo. as new £3000 new - cost now £1500.

MANY MORE ITEMS AVAILABLE - SEND LARGE S.A.E. FOR LIST OF EQUIPMENT ALL EQUIPMENT IS USED - WITH 30 DAYS GUARANTEE. PLEASE CHECK FOR AVAILABILITY BEFORE ORDERING - CARRIAGE & VAT TO BE ADDED TO ALL GOODS

Shutter Timer

Robert Penfold builds a simple device for testing photographic shutter speeds



Electronic test equipment is no longer restricted to testing electronic components and equipment. In the modern world electronic test gear is used to check just about everything, including things that are completely non-electronic in nature. This project is an example of an electronic testing device for a piece of non-electronic equipment.

It is primarily intended for checking the timing of focal plane shutters in single lens reflex cameras. However, it works equally well with most rangefinder or viewfinder cameras which have interchangeable lenses and focal plane shutters. The only exceptions are Leica screw-mount cameras and close copies such as the Russian FED. The backs of these cameras are fixed, making it impossible to get the shutter timer's sensor into position behind the shutter.

Cameras of this type require the shutter to be removed from the body for testing (which is something that should only be undertaken by a suitably experienced camera technician). The timer also seems to work quite well with large format lenses, which have built-in leaf shutters and most compact cameras which have leaf shutters. When used with a focal plane shutter, it will measure the effective shutter speed at any point on the focal plane. It can, therefore, be used to check for uneven exposure due to one shutter curtain operating at a higher velocity than the other.

Resolution

For this application, it is not essential to have a very high degree of resolution, because the tolerances allowed on shutter times are surprisingly generous. An analogue read-out would give perfectly adequate accuracy, but these days a three or four digit counter circuit probably costs no more than a moving coil panel meter of reasonable quality. Also, this application lends itself well to the digital approach. The unit finally evolved with a four digit LED display and three measuring ranges. These have full scale values of 99.99 milliseconds, 999.9 milliseconds, and

9.999 seconds. An overflow LED is included.

With most cameras, it is possible to check all the shutter speeds using this tester. The only cameras which go beyond its capabilities are those which have marked shutter speeds beyond 9.999 seconds, but only a few modern cameras fall into this category. The Canon EOS RT, for instance, has a maximum shutter speed setting of some 30 seconds. The maximum limit of 9.999 seconds is not really a major limitation since longer shutter times are easily checked against a clock or watch with seconds indication.

At fast shutter speeds, the 0.01 millisecond electronic resolution of the unit comfortably accommodates most cameras. However, it is not the electronic resolution that is likely to be the

main limitation when checking fast shutter speeds. The way in which focal plane shutters operate makes it difficult to produce precise measurements on the faster settings. The basic scheme of things is to have two fabric or metal shutter curtains. With the shutter cocked, one of these is in place in front of the film to prevent exposure. This curtain rapidly moves out of the way when the shutter is fired. After the appropriate period the other curtain

moves into place in front of the film to end the exposure.

This method works well for long shutter times, but the finite speed at which the shutter curtains move becomes problematic at short shutter durations. The time taken for the first shutter curtain to move out of the way and fully expose the film varies from one camera design to another, but it is generally between 4 and 30 milliseconds. It takes the same time for the second curtain to move into place and close the shutter. In order to obtain fast effective shutter speeds, the second curtain must start to close the shutter before the first curtain has fully opened it.

This gives what is effectively a slit moving across the film plane, with the shutter speed being controlled by varying the width of the slit. The faster the shutter speed, the narrower the slit. It is for this reason that normal electronic flash is unusable



on the higher shutter speeds. With the shutter never fully opening, the flash can only expose the part of the film that is revealed by the shutter at the instant the flash fires and this could be less than 10% of the full frame area.

Although each crystal of the film's emulsion might be exposed for precisely the correct length of time, the duration of each exposure is relatively long. At a thousandth of a second, any point on the film will be exposed for about 1 millisecond, but it would typically take around 15 milliseconds for the shutter to produce the complete picture. Checking the effective shutter speed at the film plane, therefore, requires a sensor that has a very small light sensitive area.

A focal plane shutter will typically produce a slit about 3 or 4mm at the highest shutter speeds, so even something like a 3mm diameter phototransistor has quite a wide detection area, relative to the width of the slit. This tends to give a relatively long output pulse from the sensor and significantly elongated shutter timings. The phototransistor used in the prototype timer has a width of 1mm, which gives reasonable accuracy. However, even using a sensor as small as this it is possible to obtain greater accuracy by masking it to give an even smaller effective detection area.

New Leaf

Leaf shutters are normally fitted within a multi-element lens, although in some cases they are mounted immediately behind the lens. They operate in a manner which is similar to the diaphragm which controls the effective lens aperture. Normally, the shutter is stopped right down so that no light can pass, but when triggered, the shutter rapidly opens up and, after the appropriate time span, it then closes right down again. In practice, the shutter blades are quite an elaborate shape so that the semi-opened shutter produces a sort of six pointed star shape. This ensures that the shutter has little effect on the effective aperture of the system by using the full diameter of the lens, even when the shutter is not fully opened.

Measuring the effective speed of a leaf shutter also tends to be problematic. At the highest shutter speed, the shutter opens and then almost immediately closes again. A typical leaf shutter has a maximum shutter speed of 1/500th of a second, but the shutter would typically be open to significant degree for about 3 milliseconds rather than 2. The exposure given is still quite

accurate, because for much of the 3 milliseconds the shutter is effectively stopping down the lens to some extent.

This unit is not primarily designed for testing leaf shutters and has no way of combating this problem of elongated timings at fast shutter speeds. You simply have to allow for the fact that the indicated times will be up to about 50% too long at the fastest shutter speed.

System Operation

The timer uses a simple pulse counting technique, with the camera's shutter and optical sensor generating the gate pulse. Figure 1 shows the block diagram for the shutter timer.

A crystal oscillator and divider chain generates clock frequencies of 100kHz, 10kHz and 1kHz, which give the unit its three measuring ranges. A switch is used to select the required clock frequency. The sensor is a phototransistor and, in use, this is aimed at a bright light source via the camera's shutter. The phototransistor drives a switching transistor which generates a logic compatible output. This stage controls a simple logic gate circuit. Under stand-by conditions, the phototransistor receives a relatively low light level and the gate blocks the clock signal. When the shutter is open, the phototransistor receives a higher light level and the gate couples the clock signal through to a counter circuit.

The counter is a basic four digit type which drives seven segment LED displays. Using the 1kHz clock signal, the counter obviously registers shutter times in milliseconds and therefore handles a maximum shutter time of 9999 milliseconds, or 9.999 seconds. Using the 10kHz clock signal increases the resolution to 100 nanoseconds, but the maximum time that can be accommodated is reduced to 999.9 milliseconds. Similarly, using the 100kHz clock frequency improves the resolution to 10ns, but with a maximum time of 99.99 milliseconds. A flip/flop operates an overflow indicator if the maximum count is exceeded.

The circuit is designed to automatically reset itself about 3 seconds after a timing run has been completed. This is very much more convenient in use than having to manually reset the counter. A monostable is activated by the trailing edge of the gate pulse and, after about 3 seconds, the output pulse from the monostable ends. This falling edge is processed by a pulse shaper and used to reset the counter and the overflow flip/flop.

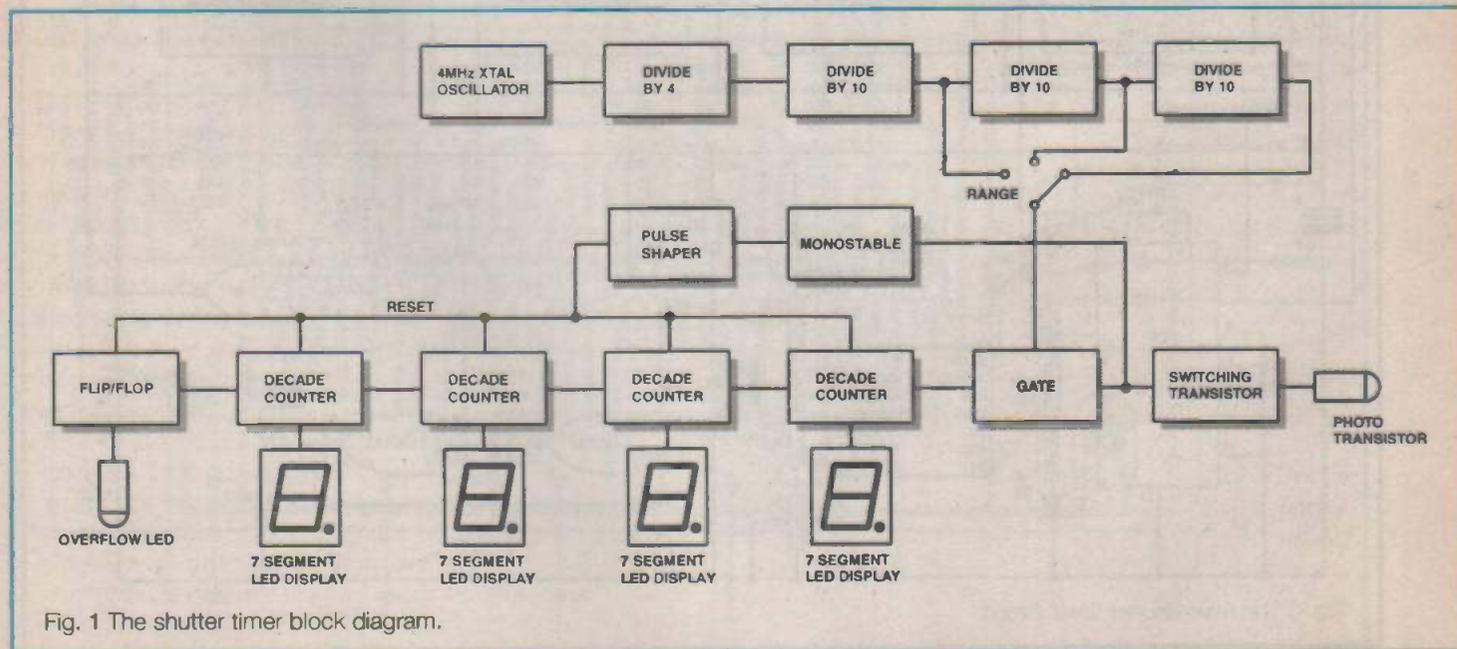


Fig. 1 The shutter timer block diagram.

and that the circuit will not work with common anode displays. The 4026BE has a built-in gate at the clock input, making the use of an external clock gating circuit unnecessary. The count is controlled via the gate at the input of the least significant counter (IC8). The clock inputs of the other three counter chips are wired to ground so that they are permanently enabled.

IC9 is a CMOS dual D type flip/flop, but in this circuit only one section of the device is used. This is used as the basis of the overflow indicator. The clock input of the flip/flop is fed from the 'carry out' output of IC5. The data input of IC9 is connected to the positive supply rail. If an overflow occurs, IC9 is fed with a clock pulse which results in the high level on its data input being latched onto the Q output. The Q output drives LED indicator D1 via current limiting resistor R32.

The light detector circuit must be reasonably sensitive, so that the unit does not require a very strong light source in order to operate properly, but it must also operate very fast, in order to give good accuracy on fast shutter speeds. Both requirements are met by using a phototransistor (TR3) as an emitter follower, driving a common emitter switch (TR4). VR1 is a preset sensitivity control which is used to set a suitable light threshold level.

Under stand-by conditions (with TR3 in a low light level), the collector of TR4 is high and the clock signal is blocked. When the shutter opens, TR3 has a much higher leakage current, TR4 is switched on, its collector goes low and the clock signal passes through to the counter circuit. When the shutter closes again, TR4 switches off, the clock signal is blocked from the counter circuit and the display shows the period for which the shutter was open.

As the collector of TR4 returns to the high state, it triggers a monostable made up from NOR gates (IC10a and IC10b). C5 and R36 set the output pulse duration at approximately three seconds. At the end of the monostable pulse, the negative transition is coupled to the input of an inverter formed from IC10c.

This produces a short positive output pulse from IC10c, which resets the counter and the overflow indicator. The unit is then ready to take another reading.

Figure 4 shows the circuit for the decimal point switching. This is just a matter of driving the decimal point segment of the appropriate display from the positive supply, via current limiting resistor R38. The unit requires a 5 or 6V supply and the average current consumption is approximately 75mA. Four HP7 size cells are adequate as the power source.



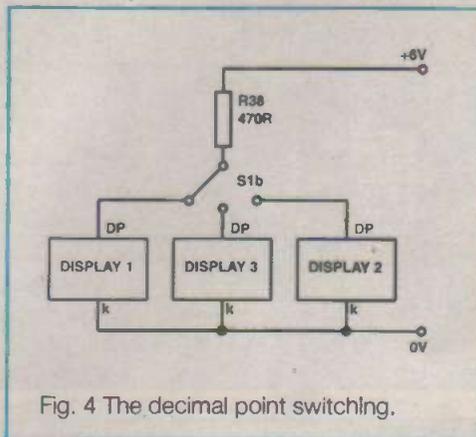


Fig. 4 The decimal point switching.

Fig. 5 The printed circuit overlay.

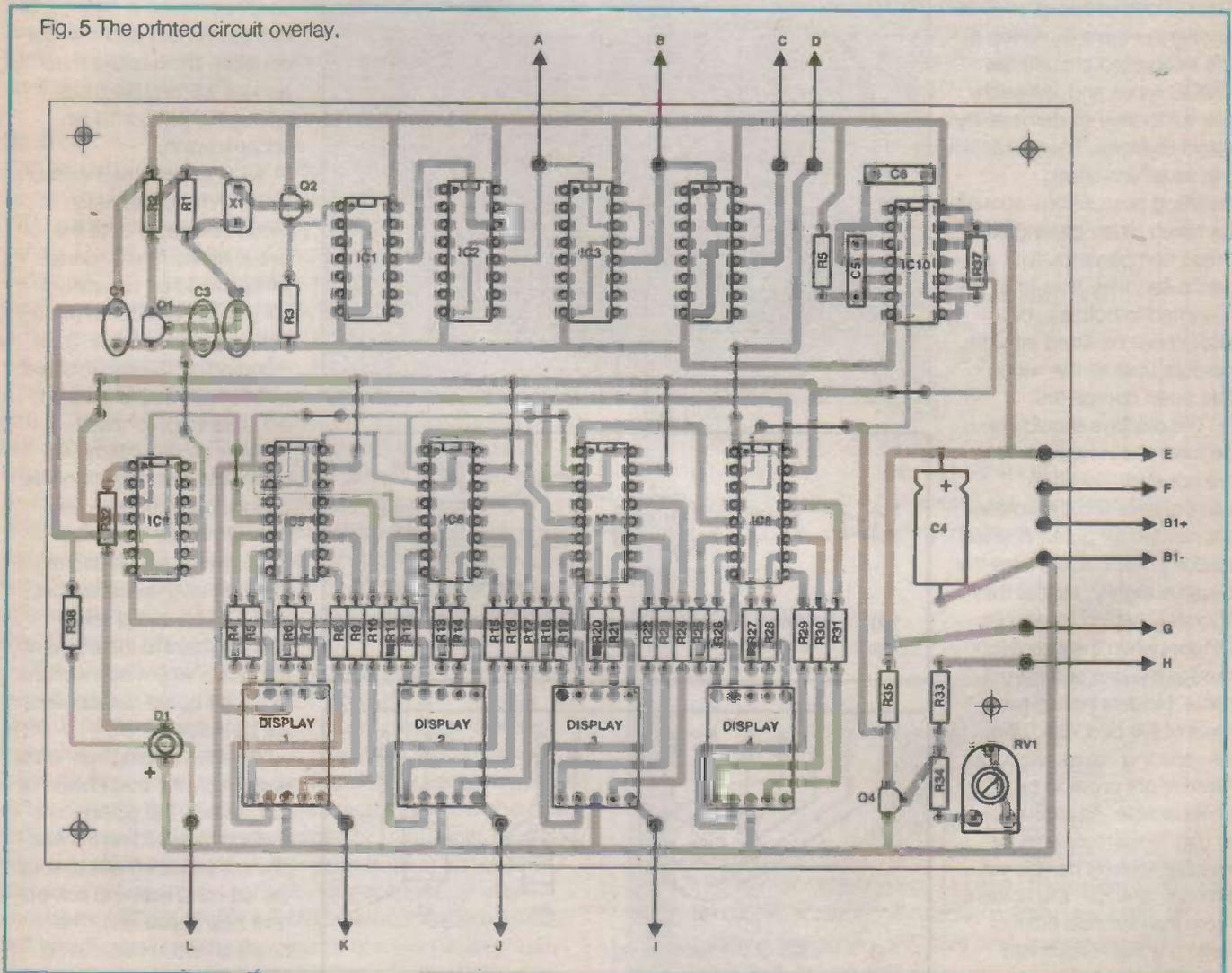

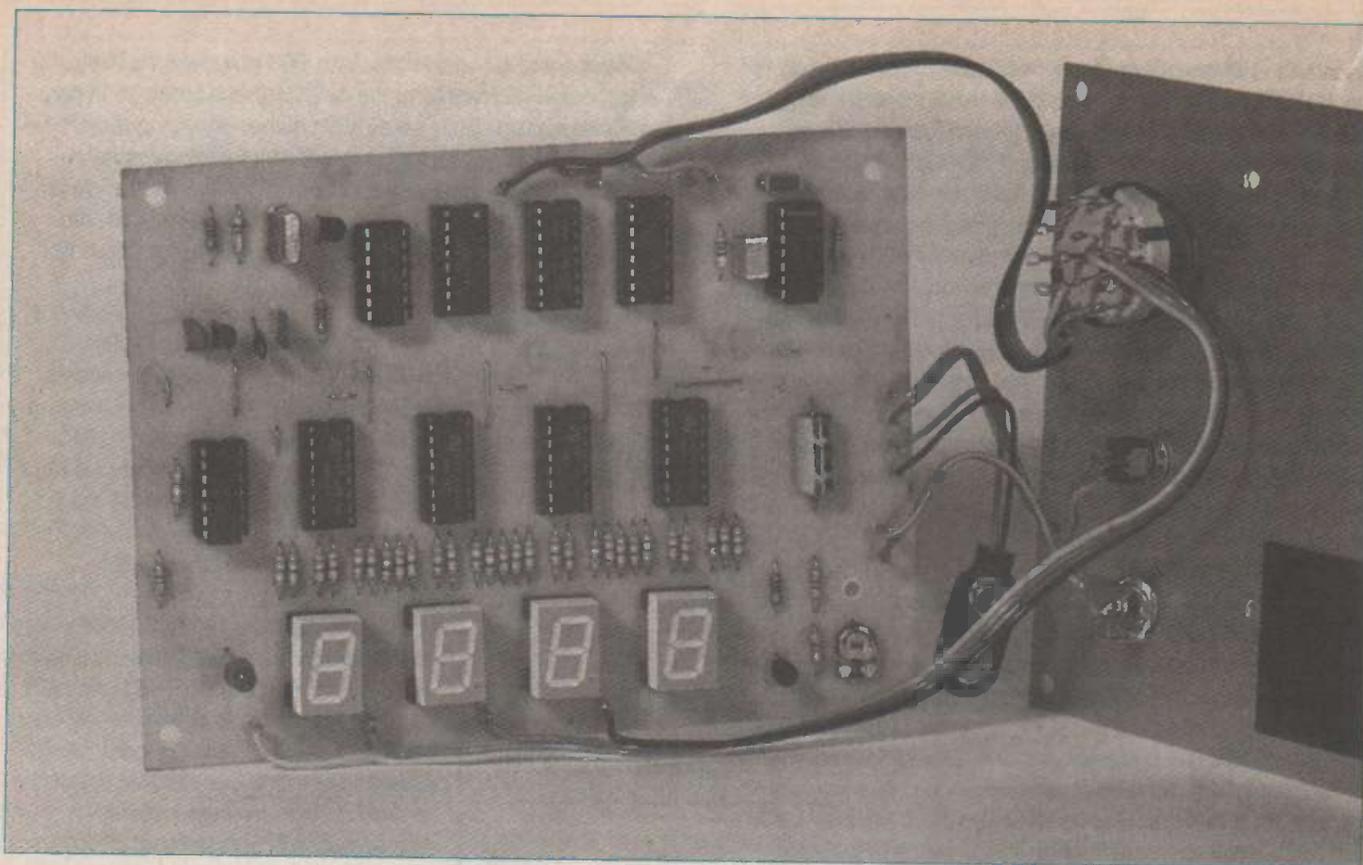

Construction

The printed circuit overlay is shown in Figure 5. All ten of the integrated circuits are CMOS types and, as such, are vulnerable to damage by static charges. Therefore, the usual anti-static handling precautions should be taken when dealing with these components. In particular, they should all be mounted in holders, but should not be fitted into the holders until all the wiring has been completed.

The displays should also be mounted in holders. They are not static-sensitive components and the holders are needed for purely physical reasons. The holders raise the displays slightly, so that they fit closely behind the display window when the board is fixed to the rear of the front panel. Holders having two rows of five pins with 0.6in row spacing are required, but these might prove to be unobtainable. An alternative is to use 'Soldercon' pins, or suitable sockets can be cut from 28 to 40 pin DIL holders. From the electrical point of view, any high brightness seven segment common

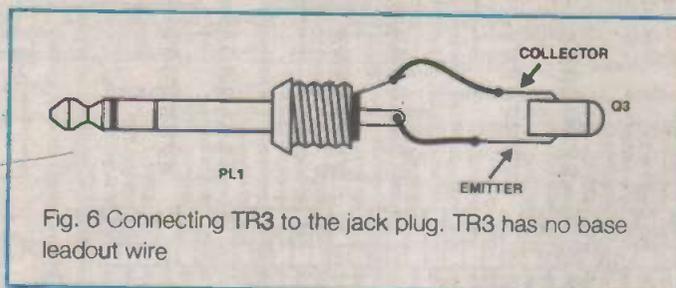
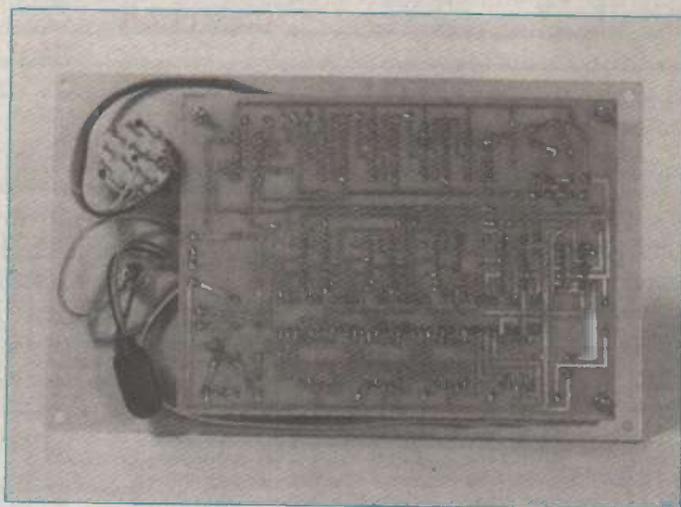


Fig. 6 Connecting TR3 to the jack plug. TR3 has no base leadout wire

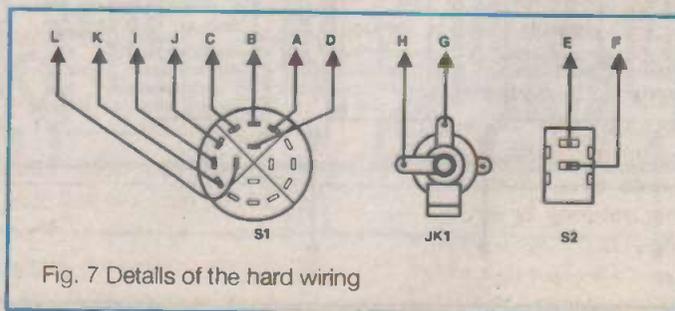


Fig. 7 Details of the hard wiring

cathode LED displays can be used. However, in order to fit into this printed circuit layout correctly, the displays must also be 0.5 or 0.6in types having the correct 10 pin encapsulation.

X1 is a 4MHz wire-ended (HC-49/U) crystal, which is mounted directly onto the circuit board. The soldered joints should be completed fairly swiftly in order to avoid damage to the crystal. D1 is mounted on the circuit board and its lead-outs should be left quite long, so that it projects several millimetres above the other components on the board. Do not overlook any of the eleven link wires, which are made from 22 or 24 swg tinned copper wire. Double-sided solder pins are fitted to the board at the points where connections to the off-board components will be made.

A largish sloping front case is probably the best choice for this project. The component panel is mounted on the rear of the front panel, well over to the left hand side and component side uppermost. The board is held in place using M3 or 6BA fixings, including

spacers to hold the board about 14 to 15mm clear of the front panel. This should bring the tops of the displays within a few millimetres of the front panel. A rectangular 'window' for the displays must be cut in the front panel. A rough initial cut-out can be made using a fretsaw, 'Abrafile', etc., with a small flat file then being used to tidy things up. A piece of red display filter material is glued in place behind the cut-out and a 5mm hole for D1 must be drilled at the appropriate point on the panel.

S1, S2 and JK1 are mounted on the right hand section of the front panel. TR3 could be mounted in the main unit, but in use it is more convenient to have it fitted in a separate probe type assembly. This is connected to the main unit via 3.5mm jack connectors and a twin cable about 0.5m long. It is necessary to improvise a little with the probe assembly, but it is not difficult to produce a reasonably neat probe based on something like an old ball-point pen.

The SFH305/2 phototransistor only has two lead-out wires, since the base terminal is not externally accessible. The shorter lead is the collector and Figure 6 shows the correct method of connecting TR3 to the jack plug (PL1). The inexpensive SFH309/5 phototransistor also works well in this circuit, but due to its larger diameter of 3mm it will not give good results at fast shutter speeds, unless it is masked down to a smaller effective size. Even with the SFH305/2 results can be significantly improved if it is masked down to an effective width of about 0.3 to 0.5mm. It is worth experimenting a little in order to optimise accuracy.

To complete the unit, the hard wiring is added. This is illustrated in Figure 7 (which should be used in conjunction with Figure 5). S1 is a 3 way pole rotary switch, but in this case only two poles are used. The four HP7 size cells are fitted in a plastic battery holder. Connections to the holder are made via a standard PP3 size battery clip.

In Use

VR1 should be set initially for about one third of maximum resistance. The light threshold level used and therefore the setting of VR1, is not likely to be particularly critical. If, in the light of experience, a lower light threshold level is found to be necessary, try setting VR1 for a higher resistance. If a higher light threshold level is required, set VR1 for a lower resistance.

For the unit to work properly, the camera must be aimed at a reasonably bright light source, which can simply be a torch, a table lamp, or even daylight coming through a window. The lens in the phototransistor renders the sensor quite directional, but it is still necessary to avoid having strong light falling directly onto the sensor. Where the camera to be tested has an interchangeable lens, it is generally easier to get thing working properly if the lens is removed. However, with a little experimentation it should still be possible to get good results with the lens in place. Remember to set the lens for maximum aperture though, so that it transmits as much light as possible through to the sensor.

The 'B' setting of the shutter is useful when trying to get everything set up correctly. This enables the shutter to be held open while the sensor position, etc., are adjusted for reliable operation. The sensor should be positioned quite closely behind a focal plane shutter, but you must obviously be careful not to damage the shutter. Remember to orient the phototransistor so that the shutter runs across its 1mm width, especially when checking the faster shutter speeds. Bear in mind that camera shutters are not generally very accurate, or very consistent. Firing a shutter several times at the same speed setting will usually produce variations of a few per cent from one firing to the next. A shutter that keeps within 20% of its

marked speeds is considered to be very good. At the higher speeds, most shutters significantly over expose and you should remember that the timer will tend to give slightly long readings on these speeds. Modern cameras having electronic timing circuits are generally more accurate and consistent than older cameras, which have clockwork timers. However, even some modern, electronically timed shutters are less accurate and consistent than one might expect.

PARTS LIST

Resistors (All 0.25W 5% carbon film)

R1	680k
R2	1k
R3	1k
R4 to R32	390R (29 off)
R33	470R
R34	4k7
R35	1k
R36	10M
R37	100k
R38	470R

Potentiometer

VR1	100k min hor present
-----	----------------------

Capacitors

C1	100n ceramic
C2	47p ceramic plate
C3	22p ceramic plate
C4	100µ 10V axial elect
C5	470n polyester
C6	47n polyester

Semiconductors

TR1, 2, 4	BC549 (3 off)
TR3	SFH305/2 (see text)
IC1	74HC4024
IC2, 3, 4	4017BE (3 off)
IC5, 6, 7	4026BE
IC9	4013BE
IC10	4001BE
D1	5mm red panel LED
Display 1, 2, 3, 4	7 segment LED, high brightness, common cathode

Miscellaneous

B1	6V (4 x HP7 size cells)
S1	3 way 4 pole rotary (only two poles used)
S2	SPST sub-min toggle
X1	4MHz wire-ended crystal;
JK1	3.5mm jack socket
PL1	3.5mm jack plug
Printed circuit board, sloping front case about 215 x 130 x 78/47mm, control knob, 14 pin d.i.l. IC holder (3 off), 16 pin d.i.l. IC holder (7 off), display holders (see text), battery holder for 4 x HP7 size cells, battery clip (PP3 type), wire, solder, solder pins, etc.	

FANTASTIC SAVINGS ON METERS AND MORE !!!

ALL PRICES INCLUDE VAT



METEX 4X DIGIT DMM M4630 ■ 30 Range 4X Digit Display 17mm ■ 0.05% Accuracy. Features: ■ 5 range capacitance test ■ 5 ohms ranges to 20M ■ Transistor and Diode Test ■ Continuity LED and buzzer ■ Data hold switch ■ 5 ranges AC/DC volts ■ AC/DC current to 20 Amps ■ With leads, battery instructions and hard case (was £84.95) **NOW ONLY £59.95**

T1.34 ■ 33 Range ■ 3 1/2 digit 24mm Large Display. Features: ■ 5 Capacitance ranges ■ 8-resistance ranges to 20M ohm ■ Diode and transistor test ■ 5 AC/DC volts ranges Basic 0.5% accuracy. ■ 5 ranges AC/DC current to 20 Amps ■ With leads, battery and instructions (was £32.95) **NOW ONLY £29.95**

MX190 ■ 19 Range 3 1/2 Digit. Features: ■ AC/DC VOLTS (0.7%), ■ 0-10 ADC current ■ 0/2W/2MEG ohmmeter ■ Diode test ■ Signal injector function ■ With leads, battery and instructions (was £16.95) **£14.95**

TEST METERS
 LCR Meter ■ 3 1/2 Digit ■ 7 Cap ■ 6 Inductance ■ 7 resistance ranges **£69.95**
 Capacitance Meter ■ 3 1/2 Digit ■ 9 ranges ■ 18mm LCD display **£69.95**
Digital Lux Meter
 ■ 3 ranges ■ 3 1/2 digit LCD ■ Data hold output terminal **£68.95**
Sound Level Meter
 ■ 40 to 120 db ■ Two ranges **£51.95**
Analogue Clamp Meter
 ■ 0/300 amps ■ AC 6 ranges ■ 0/750 VAC 0/75v DC ■ 0/200 K Ohm **£36.95**
Digital Clamp Meter
 ■ 3 1/2 Digit ■ 11 ranges incl temperature ■ Data hold etc. **£63.50**
AC/DC Current Clamp
 ■ 0/2000 amps AC/DC two ranges for use with Dmm's **£58.95**
Temperature Measurement
 ■ Dual input 3 1/2 Digit °C/°F with thermocouple (X) **£45.95**
BENCH INSTRUMENTS
 Digital LED Capacitance autorange bench meter 0.1% **£99.95**
 LCR bridge **£124.00**
 7 Digit frequency 10KHz to 200MHz **£89.95**

POWER SUPPLIES
 Single meter twin meter
 0/24v dc 0/3amps **£79.95**
 0/24v dc 0/5amps **£67.00**
 0/30v dc 0/3 amps **£145.00**
 Twin version **£265.00**
 5-15v dc 0/4 amps **£137.95**
SIGNAL SOURCES 220/240V AC
 8 Range RF Gen 100 KHz to 150 MHz (350MHz Harmonics) **£236.00**
 5-range Audio Gen 10KHz to 1 MHz **£190.00**
 Sine/square **£190.00**
 0.5Hz to 500KHz Function Gen Sine/Sq/Triang **£228.00**

Full details send for instruments into pack (SAE 36p UK) Ref: TG


ALL PRICES INCLUDE VAT OPEN 6 DAYS A WEEK

HENRY'S
 AUDIO ELECTRONICS
 (Reg. Prnc. Chichester Ltd)

404 Edgware Rd, London W2 1ED
 Tel: 071-724 3564/071-258 1831
 Fax: 071-724 0322

Discounts for quantity and education

READER OFFER

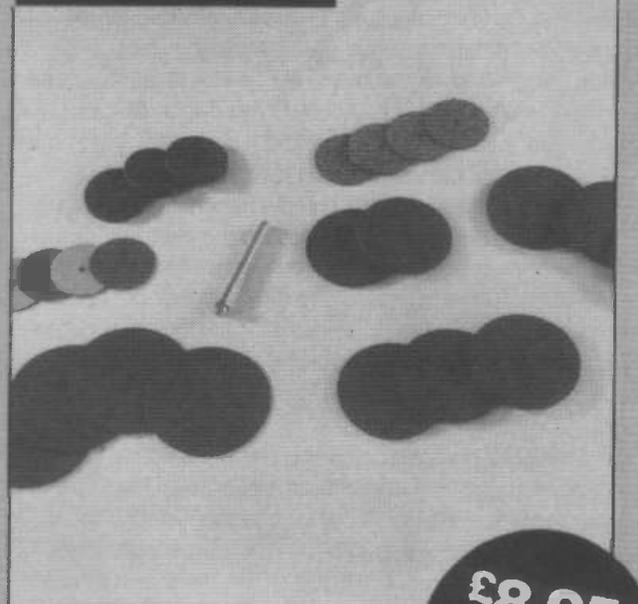

£8.95
 inc p&p & VAT

Cutting Discs

Suitable for use with most, if not any of the miniature electric drills currently available and always useful in any workshop, this collection of slitting discs and cutting wheels is supplied as a pack complete with a mandrel.

Packed in a variety of diameters and thicknesses appropriate for many applications, this selection of 24 aluminum oxide discs ranges in diameter from:

- 1/2in. (12mm) to 1 1/2in.
 - (40mm) and thickness from 1/32in
 - (1mm) to 5/32in. (4mm)
- (quantity and dimensions may vary).

If you already use these abrasive wheels, at less than 40p each you should consider replenishing your stock; if you haven't yet used them, at this price you might like to see how they assist in your own particular modelling activity.

SAVE OVER £16! (R.R.P. £25)

Please supply ROCB/3 @ £8.95
 I enclose my cheque / P.O. for £..... payable to ASP or please debit my Access/Visa

Signature..... Expiry.....

Name.....

Address.....

Post Code.....

Please allow 28 days for delivery U.K. Overseas upon request
 Coupon to: ASP Reader Offers, ASP Reader Offers, Argus House, Boundary Way, Hemel Hempstead, Herts. HP2 7ST.
 Data Protection: Occasionally we may make names and addresses available to carefully vetted companies who sell goods and services by mail that we believe to be of interest to our readers. If you would prefer not to receive such mailings please tick this box

Inventor toroidal transformers 225VA 10.5-0-10.5 primary 0-260-285 secondary..... £29.95	Airpax A82903-C large stepping motor 14v 7.5t step 270ohm 68mm dia body 6.3mm shaft..... £3.95 of £200.00 for a box of 30
LEDs 3mm or 5mm red or green..... 6p each yellow..... 11p each	Polyester capacitors box type 22.5mm lead pitch 0.9uf 250vdc..... 28p each 14p 100- 9p 1000- 1uf 250vdc..... 16p each 15p 100- 10p 1000- 2.2uf 250vdc (27.5mm pitch) 30p each, 20p 100- 15p 1000-
Cable ties..... 1p each £5.95..... per 1000 £49.50	3.3uf 100vdc..... 30p each, 20p 100- 15p 1000- 1uf 50v bipolar electrolytic axial leads 15p each, 7.5p 100-
High quality photo resist copper clad epoxy glass boards	0.22uf 250v polyester axial leads... 15p each, 7.5p 100-
Dimensions	100-
3x4 inches £1.09	Polypropylene 1uf 400vdc (Wima MKP10) 27.5mm pitch
4x8 inches £2.75	32x28x17mm case..... 75p each 60p 100-
6x12 inches £6.20	Philips 123 series solid aluminium axial leads 33uf 10v & 2.2uf 40v..... 40p each, 25p 100-
12x12 inches £12.25	Philips 108 series 22uf 63v axial..... 30p each, 15p 100-
Rechargeable batteries	Multitlayer AVX ceramic capacitors all 5mm pitch 100v
AA (HP7) 500MAH £0.99	100p, 150p, 220p, 10,000pf (10n) 10p each, 5p 100- 3.5p 1000-
AA 700MAH £1.75	500pf compression trimmer 60p
C 2AH with solder tags £3.90	40uf 370vdc motor start capacitor (dielectric type containing no pcbs)..... £5.95 or £49.50 for 10
4AH with solder tags £4.95	Welwyn W23 9W 120ohm 35p each 20p 100-
1/2AA with solder tags £1.55	880 ohm 2W metal film resistor 4p 100-, 2p 1000-
AAA (HP18) 180MAH £1.75	Solid carbon resistors very low inductance ideal for RF circuits
AAA 500MAH with solder tags £1.55	27ohm 2W, 68ohm 2W 25p each 15p each 100- we have a range of 0.25w 0.5w 1w and 2w solid carbon resistors please send SAE for list
C (HP11) 1.8AH £2.90	P.C. 400W PSU (Intel part 201035-001) with standard motherboard and 5 disk drive connectors, fan and mains inlet/outlet connectors on back and switch on the side (top for tower case) dims 212 x 149 x 148mm excluding switch..... £26.00 each £138.00 for 8
D (HP2) 1.2AH £4.95	MX180 Digital multimeter 17 ranges 1000vdc 750vac 2Mohm 200mA transistor Hfe 9v and 1.5v battery test..... £12.95
PP3 8.4V 110MAH £4.95	AMD 27256-3 Eproms £2.90 each, 1.25 100-
Sub C with solder tags £2.50	DIP switch 3PCD 12 pin (ERG SDC-3-023) 50p each 40p 100-
1/3 AA with solder tags (philipsCTV) £1.95	Disk drive boxes for 5.25 disk drive with room for a power supply light grey plastic 67x268x247mm £7.95 or £48.50 for 10
Standard charger charges 4 AA cells in 5 hours or 4Cs or Ds in 12-14 hours + 1xPP3 (1,2,3 or 4 cells may be charged at a time)..... £5.95	Hand held ultrasonic remote control £3.95
High power charger as above but charges the Cs and Ds in 5 hours AAAs Cs and Ds must be charged in 2s or 4s..... £10.95	CV2486 gas relay 30 x 10mm dia with 3 wire terminals will also work as a neon light 20p each or £7.50 per 100
Special offers please check for availability	A23 12v battery for car alarms or lighters 75p each £20.00 per 100
F cells 32dia x 87mm £3.95 F cell with solder tags 1.2v £4.30 42 x 16mm dia 1.2v £1.45	All products advertised are new and unused unless otherwise stated
Stick of 4 171mm x 16mm dda with red & black leads 4.8v..... £5.95	wide range of CMOS TTL 74HC 74F Linear Transistors kits rechargeable batteries capacitors tools etc always in stock
Computer grade capacitors with screw terminals 38000uf 20v..... £2.50	Please add £1.95 towards P&P vat included in all prices
87000uf 10v £1.95, 68000uf 15v £2.95, 10000uf 16v £1.50, 58000uf 80v £4.95	
7 segment common anode led display 12mm..... £0.45	
LM2931AT5.0 low drop out 5v regulator TD220 package..... £0.85	
7812 and 7912 12v 1A regulators..... £20.00 per 100	
LM337K TO3 case variable regulator..... £1.95 £1.44 100-	
GaAs FET low leakage current 58873..... £12.95 each £9.95 10-£7.95 100-	
BS250 P channel mosfet £0.45, BC559 transistor..... £3.95 per 100	
74LS05 hex inverter £10.00 per 100, used 8748 Microcontroller £3.50	
SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet..... £1.95	
AM27502 £1.25 each 90p 100-, CD4007UB 100-ns 100-	
Sinclair light gun terminated with a jack plug and PP3 csp gives a signal when pointed at 50Hz flickering light with output wave form chart..... £3.95	
DC-DC converter Reliability mode V12P5 12v in 5v 200ma out 300v input to output isolation with data sheet..... £4.95 each or pack of 10 £38.50	
Hour counter used 7 digit 240v ac 50 Hz £1.45	
OWERTY keyboard 58 key good quality switches new..... £5.00	


JPG ELECTRONICS
 276-278 Chatsworth Road
 Chesterfield S40 2BH
 Access Visa Orders (0246) 211202
 Callers welcome

OLP
TRANSFORMERS from

JAYTEE

**UK Distributor for
Standard Toroidal Transformers**

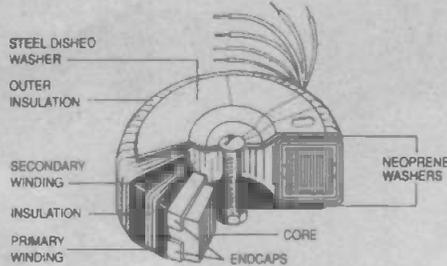
- 107 types available from stock
- Sizes from 15VA to 625VA
- Dual 120v primaries allowing 110/120v or 220/240v operation



TYPE	SERIES NO.	SEC VOLTS	RMS CURRENT	TYPE	SERIES NO.	SEC VOLTS	RMS CURRENT
15VA £10.68	03010	6+6	1.25	225VA £21.04	63012	12+12	9.38
	03011	9+9	0.83		63013	15+15	7.50
	03012	12+12	0.63		63014	18+18	6.25
	03013	15+15	0.50		63015	22+22	5.11
	03014	18+18	0.42		63016	25+25	4.50
	03015	22+22	0.34		63017	30+30	3.75
	03016	25+25	0.30		63018	35+35	3.21
30VA £12.21	03017	30+30	0.25	63026	40+40	2.81	
	13010	6+6	2.50	63025	45+45	2.50	
	13011	9+9	1.66	63033	50+50	2.25	
	13012	12+12	1.25	63028	110	2.04	
	13013	15+15	1.00	63029	220	1.02	
	13014	18+18	0.83	63030	240	0.93	
	13015	22+22	0.68	300VA £22.94	73013	15+15	10.00
13016	25+25	0.60	73014		18+18	8.33	
13017	30+30	0.50	73015		22+22	6.82	
50VA £13.84	23010	6+6	4.18		73016	25+25	6.00
	23011	9+9	2.77		73017	30+30	5.00
	23012	12+12	2.08		73018	35+35	4.28
	23013	15+15	1.66		73026	40+40	3.75
	23014	18+18	1.38	73025	45+45	3.33	
	23015	22+22	1.13	73033	50+50	3.00	
	23016	25+25	1.00	73028	110	2.72	
80VA £15.43	23017	30+30	0.83	73029	220	1.36	
	23028	110	0.45	73030	240	1.25	
	23029	220	0.22	500VA £29.57	83016	25+25	10.00
	23030	240	0.20		83017	30+30	8.33
	33010	6+6	6.66		83018	35+35	7.14
	33011	9+9	4.44		83026	40+40	6.25
	33012	12+12	3.33		83025	45+45	5.55
33013	15+15	2.66	83033		50+50	5.00	
33014	18+18	2.22	83042		55+55	4.54	
120VA £16.45	33015	22+22	1.81	83028	110	4.54	
	33016	25+25	1.60	83029	220	2.27	
	33017	30+30	1.33	83030	240	2.08	
	33028	110	0.72	625VA £32.64	93017	30+30	10.41
	33029	220	0.36		93018	35+35	8.92
	33030	240	0.33		93026	40+40	7.81
	43010	6+6	10.00		93025	45+45	6.94
	43011	9+9	6.66		93033	50+50	6.25
	43012	12+12	5.00		93042	55+55	5.68
	43013	15+15	4.00		93028	110	5.68
	43014	18+18	3.33	93029	220	2.84	
	43015	22+22	2.72	93030	240	2.60	
	43016	25+25	2.40	13.8V DC POWER SUPPLY TRANSFORMERS			
43017	30+30	2.00	8C267	500VA	18+18V	£32.64	
43018	35+35	1.71	9T845	675VA	16.1V	£38.06	
43027	20+20	3.00	Prices include VAT and carriage				
43028	110	1.09	Quantity prices available on request				
43029	220	0.54					
43030	240	0.50					
160VA £19.21	53011	9+9	8.89				
	53012	12+12	6.66				
	53013	15+15	5.33				
	53014	18+18	4.44				
	53015	22+22	3.63				
	53016	25+25	3.20				
	53017	30+30	2.66				
	53018	35+35	2.28				
	53026	40+40	2.00				
	53028	110	1.45				

SURVEILLANCE
SURVEILLANCE

A SMALL SAMPLE OF OUR RANGE	KIT	MODULE	PROF. FINISHED
ROOM TRANSMITTER RT1 An extremely sensitive miniature transmitter with long battery life. Dimensions: 20 x 20mm	9.95	13.75	19.00
MAINS TRANSMITTER MT4 Can be connected inside any equipment that is mains powered. Dimensions 35 x 20mm	19.75	31.50	40.00
TELEPHONE TRANSMITTER TTS Small enough to conceal within a telephone. Will transmit both sides of a conversation (series connection) Dimensions: 10 x 20mm	12.75	17.50	25.00
TELEPHONE SOCKET TRANSMITTER TSTS Replace your telephone socket with this one within which a transmitter has been concealed.	14.74	—	29.00
ROOM AND TELEPHONE TRANSMITTER RTT Operates as a room transmitter, then switches to telephone transmitter mode during telephone calls. Dimensions: 30 x 25mm	31.50	45.50	68.00
AUTOMATIC TELEPHONE RECORDER SWITCH TRS2 Record telephone conversations with this interface unit and your own tape recorder. Dimensions: 36 x 50mm	18.80	25.90	39.00
AUTOMATIC TELEPHONE RECORDER ATR1 Adapt the tape recorder included to record telephone calls automatically.	34.95	—	69.00
TELEPHONE TAP ALERT TTA1 Visual warning of any invasions of privacy on your telephone line. Dimensions: 38 x 52mm	21.95	31.50	45.00
RF DETECTOR RFD1 Highly sensitive hand-held detector. Range between 10Mhz and 600Mhz. Silent operation. Dimensions: 70 x 50mm	42.75	69.00	95.00
CAMERA DETECTOR CD8 Detects hidden video cameras (even miniature CCD models). Dimensions: 63 x 38mm	69.00	89.00	125.00
RECORDING BRIEFCASE RBC1 Completely discreet recordings at a value for money price.	—	—	148.00
SHOTGUN MICROPHONE AMPLIFIER SMA Ideal for surveillance. The amplifier will pick up sounds from a long distance.	24.95	36.00	48.00
SIGNALLING TRANSMITTER SIGT Sends a continual audio pulse. Can be integrated into alarm, tracking or warning systems. Dimensions: 20 x 50mm	21.95	34.89	45.00
TELEPHONE AMPLIFIER TAs Connected directly to the telephone, this unit will amplify both sides of a telephone call. Dimensions: 25 x 52mm	10.95	16.95	19.95
PROFESSIONAL SOUND TO LIGHT UNIT SK72 Custom built for disco or home use. Audio signal divided into bass, mid and treble bands, with internal microphone and spotlight option. Dimensions 210 x 45mm	21.95	32.49	44.95
MICRO METAL DETECTOR MMD Detect the presence of ferrous and various non-ferrous metals. Useful for all those DIY jobs. Dimensions: 40 x 25mm	9.95	16.95	—

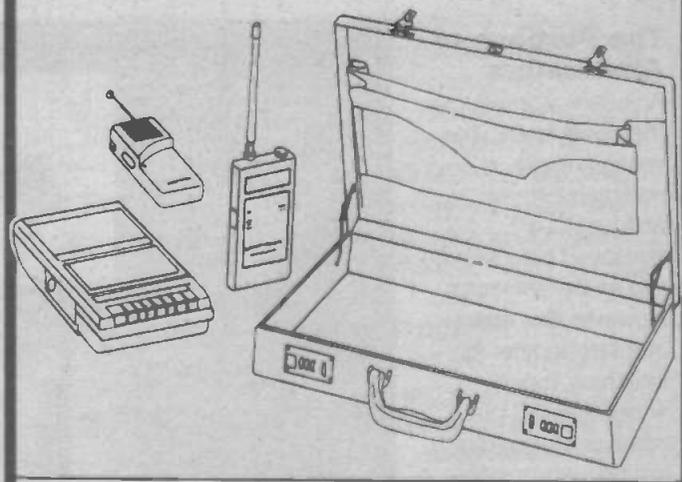

Please add £2.00 P & P to all orders and 17.5% VAT on all U.K. orders.
For full catalogue please send two 1st class stamps or 2 IRC'S

Write, phone or fax for free Data Pack
Jaytee Electronic Services
Unit 171/172, John Wilson Business Park,
Whitstable, Kent CT5 3RB. U.K.
Tel: (0227) 265333 Fax: (0227) 265331

172 Caledonian Road
Dept ET
CANAL
London N1 0SG
BRIDGE AUDIO
071-837 4423

Palesaver Load/ Attenuator



Also known as the spouse saver, this little project acts as both a dummy load and as a loudspeaker attenuator. Design by Dave Bradshaw


This little unit serves two purposes. Firstly, it acts as a flexible loudspeaker attenuator, but secondly, it is also an accurate 8 ohm load, for setting up and testing power amplifiers. It was mainly designed for the first use, as an attenuator for the Paleface series of amplifiers, the second use coming as a bonus. There are three versions, with different power levels: 25W, 50W and 100W.

An attenuator makes it easier to play instrument amplifiers at low volume levels for practising. Even the Paleface Minor's 15W is very noisy indeed in a domestic environment. My experience, when using it for regular practice, was that cutting the signal by a few dB just wasn't enough. Quite a large degree of attenuation was needed, particularly as some of the effects I was using generated lots of hiss and mains hum (I'm proud to say that the amp itself contributed hardly any). The attenuation needed to be 10 to 15dB and there had to be an even quieter setting for late night use.

Now, using the attenuator, low level volume settings are much more controllable. A slip of the finger doesn't result in instant deafening for the neighbours. Of course, it's not really like playing loud, but it is now possible to overload the power amplifier - and obtain the much sought-after valve distortion - without alienating the entire family.

The Purpose of Attenuators

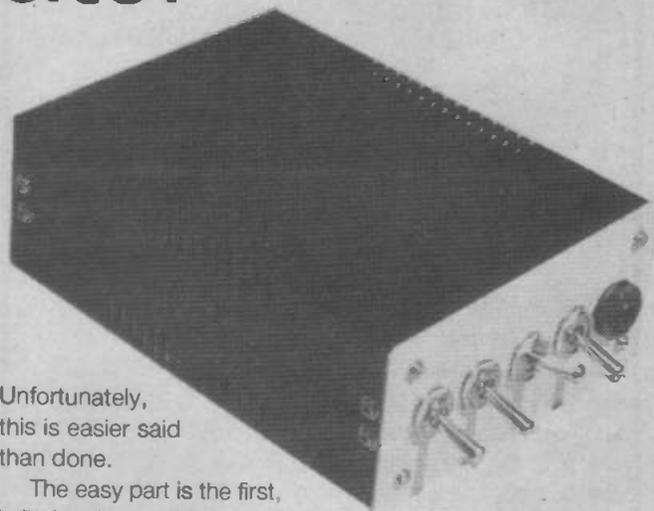
An attenuator reduces the signal levels. The voltage divider, a common form of attenuator, is employed here with a few embellishments. However, this attenuator has another job - matching impedances. Ideally, loudspeaker attenuators are two-way mimics, the loudspeaker should see the same source impedance as it would from the amplifier and the amplifier should see the same load.



Unfortunately, this is easier said than done.

The easy part is the first, imitating the amplifier's output impedance, but even this is not straightforward. Transistor amplifiers often have output impedances well under an ohm. To imitate this you have to put a very low resistance, say a tenth of an ohm, in parallel with the loudspeaker, but then you are not going to get very much signal going into the speaker. The lowest impedance the Palesaver has is slightly under 0.5 ohm, with the output level switch set to LOW and all the ballast resistors out of circuit. Although this is still higher than the better semiconductor amplifiers, it is going to be comparable with the minimum impedance added by most cross over units.

However, valve amplifiers generally have much lower levels of feedback in the power amplifier and, as a result, they have much higher impedances. For example, the output impedance of the Paleface Minor guitar amp varies from around 4 ohms at

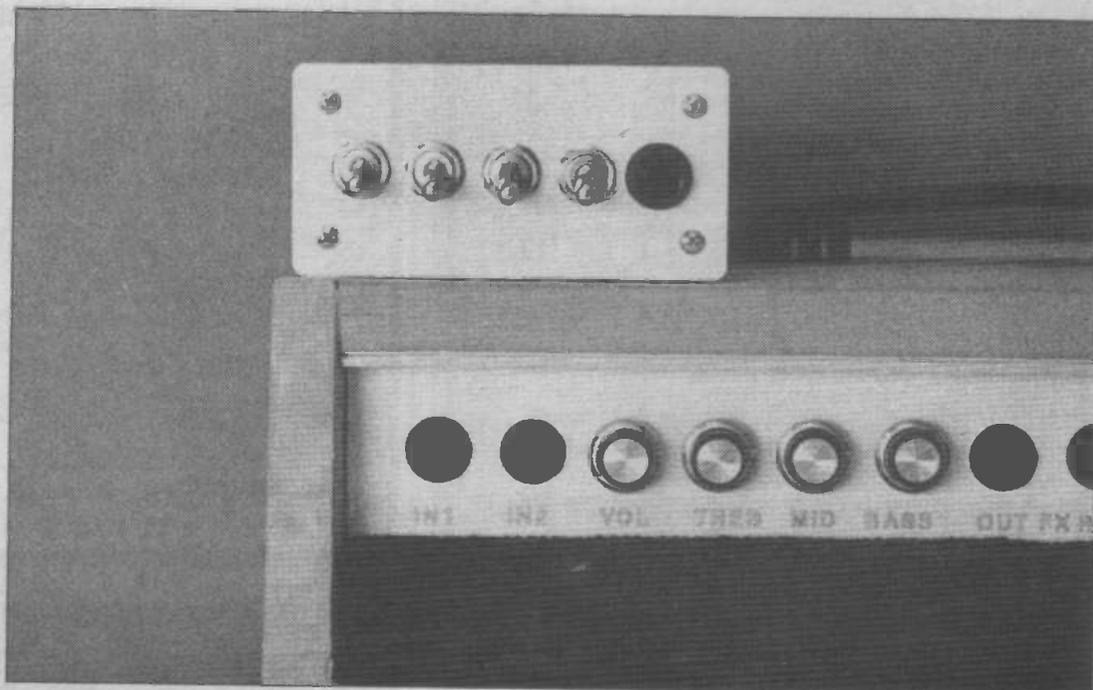

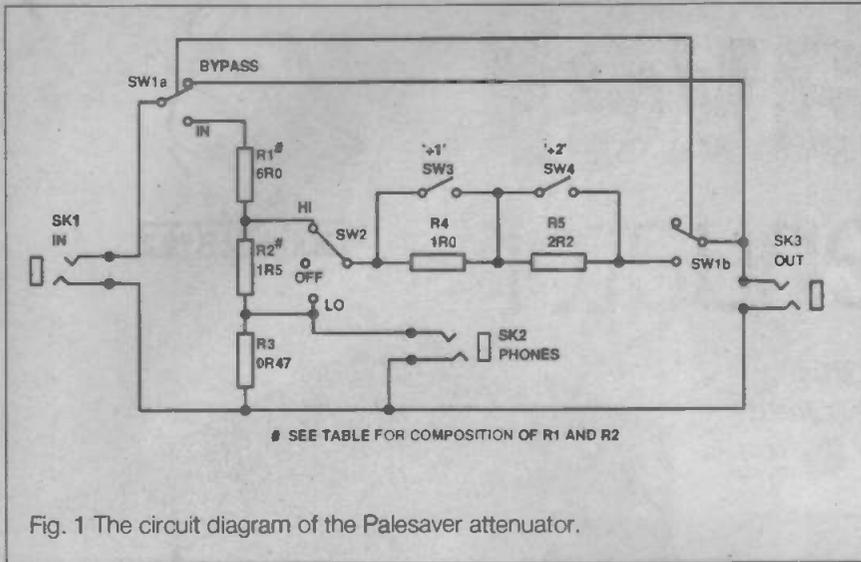


Fig. 1 The circuit diagram of the Palesaver attenuator.

100Hz to 2 ohms at 1kHz, almost completely resistive. Here we will need to add extra resistance to the basic attenuator. There are two switchable ballast resistances to increase its output impedance. However, the Palesaver cannot emulate the frequency dependency, so a mid-value should be used. For example, to emulate an output impedance of around 3 ohms, use a single 1 ohm ballast resistor on the HIGH output setting, but 2 ohms on the LOW setting.

The other aspect of a loudspeaker attenuator is how well it mimics the impedance of the loudspeaker which the amplifier normally drives. Loudspeakers have lots of variation in their impedances and they also have strong reactive elements. The Palesaver confines itself to emulating the resistive part of the impedance only. If I ever get a year or two to experiment with a room full of acoustic measuring gear, I'll make Palesaver II emulate the frequency-dependent reactive part of the typical loudspeaker.

The Circuit

An input selector, SW1, allows the attenuator to be taken completely out of circuit. With the attenuator in circuit, the signal passes through three resistors in series, the top one (R1) of around 6 ohms, the second (R2) of around 1.5 ohms and the third (R3) at 0.5 ohms. Switch SW2 controls the tapping point that the loudspeaker is attached to. It is a centre-off switch, so the loudspeaker can be

disconnected completely.

Using the limited range of values of high power resistors, I have assembled multiple parallel resistors for R1 and R2, to get as close as I can to 8 ohms overall impedance, with at least the rated power capability. I have used 3W to 10W resistors - I considered using 25W types, but the very limited range of values and expense stopped me. Table 2 shows the values for the three different versions. In fact the 25W and 50W versions are identical except for power ratings. However, the 100W version had to have a different R2, and this meant a small change in R1 as well. Assuming perfect components, all versions are well within 1% of 8 ohms in input impedance with no loudspeaker connected. Even with some component variance, the impedance will be

pretty close, as paralleling resistors together effectively averages their values.

Output Level Settings	HIGH	LOW
Power Attenuation	13.5dB	24.5dB
Output Impedance (no ballast resistors, zero source impedance)	1.6 ohm	0.45 ohm

Table 1 Attenuation and output impedance of the Palesaver, all versions.

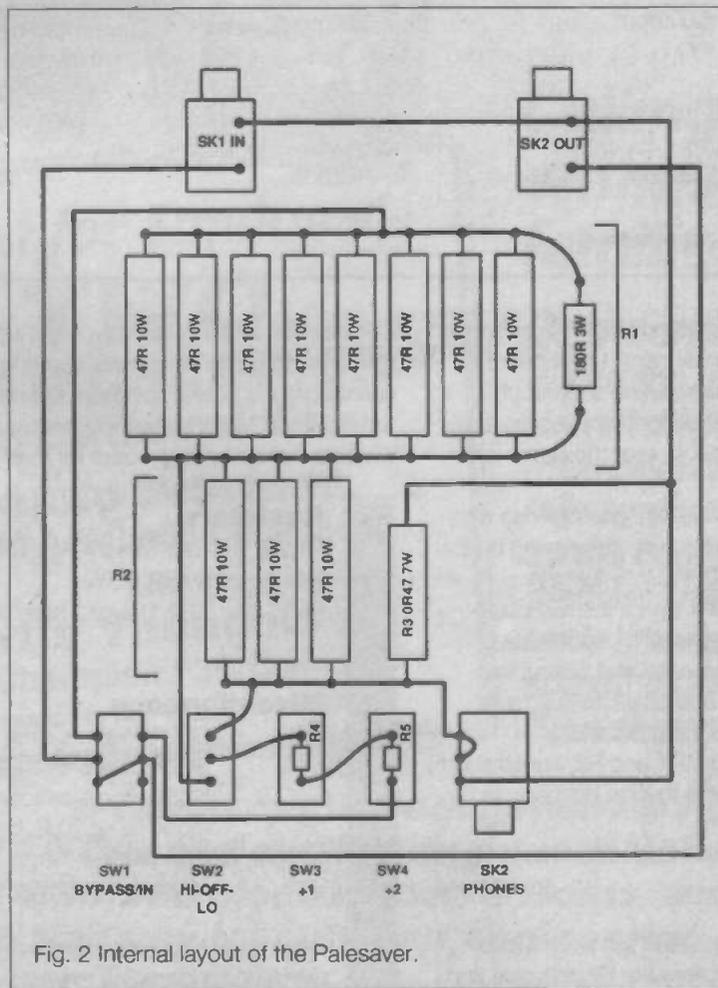


Fig. 2 Internal layout of the Palesaver.


Table 1 shows the attenuation levels and the output impedances without ballast resistors. To emulate valve amplifier outputs, the ballast resistors (R4 and R5) can be switched in or out of the signal path by two switches (R3 and R4).

When it is being used for measurements, the speaker should be turned off as this affects the impedance. A phones socket is included so that the output can be monitored over phones. Most types of phones will make negligible difference to the input impedance of the unit.

Construction

The layout shown in the diagram and photographs is for the 100W unit, but the 25W and 50W versions are similar. The extra connectors in the prototype are XLR sockets in parallel with SK1 and 3, to give some extra versatility with the connections.

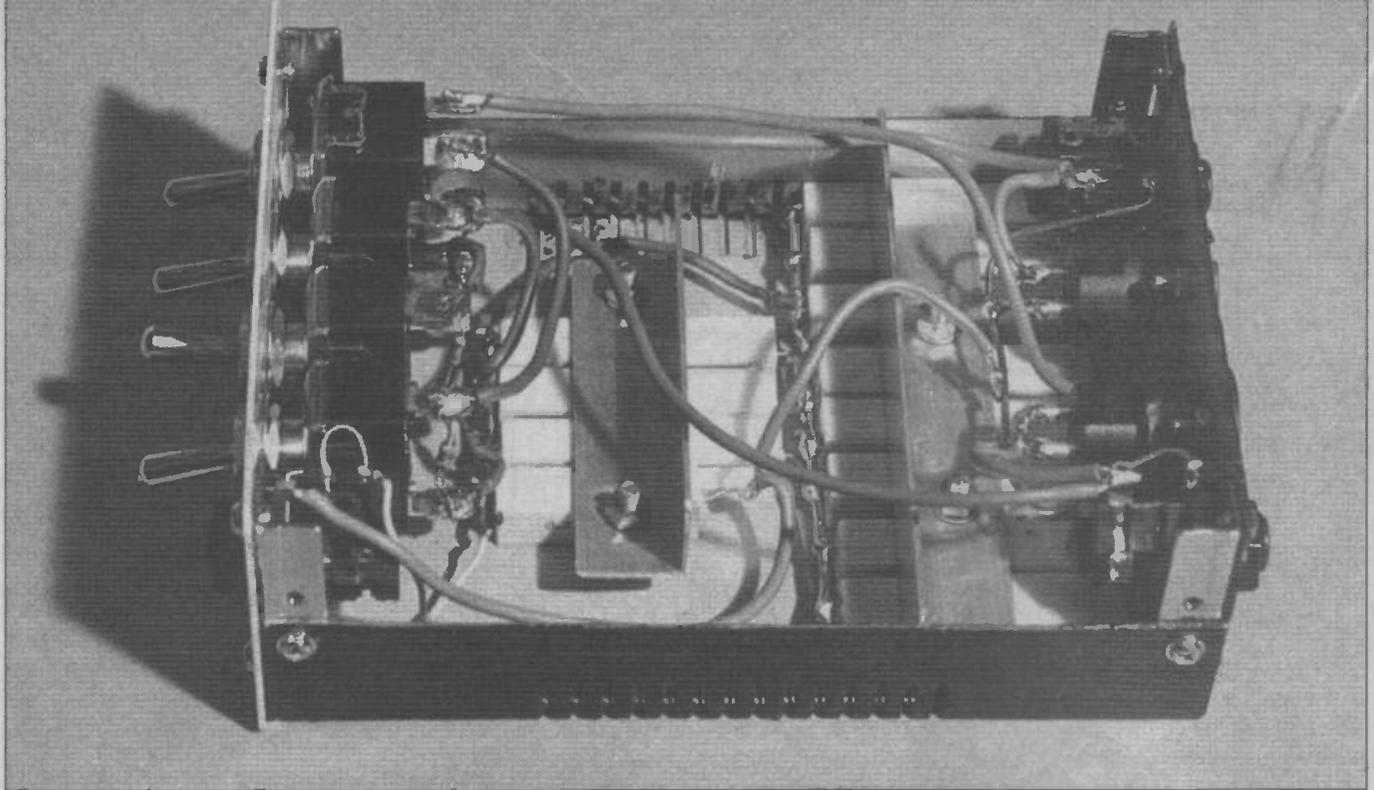The main constructional effort goes into preparing the case. As the unit gets hot, I



Power	25W	50W	100W
R1	8 x 47R 3W (5.88 ohm)	8 x 47R 7W (5.88 ohm)	8 x 47R 10W + 180R 3W (5.69ohm)
R2	2 x 3R3 3W (1.65 ohm)	2 x 3R3 5W (1.65 ohm)	3 x 4R7 10W (1.87 ohm)
R3	0R47 2W	0R47 3W	0R47 7W
Resistance with no load	8.00 ohm	8.00 ohm	8.03ohm
Resistance with 8 ohm load on HIGH setting and no ballast	7.55ohm	7.55ohm	7.50ohm

Table 2 Component values for different power levels.

built it into a metal box with no plastic fittings or vinyl covering and painted it using heat-resistant black paint. I clamped the high power resistors to the case bottom, using a piece of aluminium L-channel and some bolts, so that whole case acts as a heatsink. I used some epoxy resin to seat the clamp on the resistors.

With this type of construction, the 100W Palesaver can withstand around five to ten minutes of full power, depending on the amount of ventilation. To withstand 100W RMS for long periods, the Palesaver needs a heatsink with a thermal coefficient of around 0.5C/W, or two heatsinks with coefficients of 1.1 to 1.2C/W. Rather than choosing a case and bolting the heatsinks to it, it is probably cheaper and easier to build a simple case using the heatsinks as an integral part.

To make up the compound resistors R1 and R2, I used short lengths of copper wire from mains cable to form busbars, to which I soldered the individual resistors.

The remainder of the construction is straightforward.

BUYLINES

Nothing here should present problems. The high power resistors came from Maplin, but other suppliers like Electrovalue and

Cricklewood stock suitable types. It's always safer to under-rate resistors, so go for the power above rather than below if you cannot get the power specified. Buy the case once you have the resistors, switches and connectors, so you can work out whether there's enough room for them all.

PARTS LIST

Resistors

R1,2,3	See Table 1
R4	0.47R 0.5W
R5	2R2 1W (or 2 ohm 3R9 0.5W)

Miscellaneous

SW1	DPDT toggle switch
SW2	SPDT centre off toggle switch
SW2,3	SPST toggle switches
SK1,3	mono jacks, XLR, or any suitable connectors, to choice
SK2	headphone socket (e.g. stereo jack)

Case, wire, heat resisting paint, aluminium L-channel extrusion for clamping resistors, M4 bolts to fit clamps



AN **ARGUS**
SPECIALIST EXHIBITION

Don't miss the
19TH

SANDOWN PARK MODEL EXHIBITION & DISPLAY

Sandown Exhibition Centre
Esher, Surrey.

May 14th & 15th

1994

9.30am - 6pm

**Calling all model
enthusiasts and
families..**

*Come one. Come all!
Watch the incredible model
aircraft displays and check out
the model car racing, model
railway displays and novelties
on the boat pool.
Wander around the numerous
trade stands. There's
something for everyone at
Sandown...*

A first for Sandown!
TWO
WORLD CHAMPIONS
display their skills...

Hanno Prettner
World Aerobatic Champion


AND

Curtis Youngblood
World Champion F3C Helicopters

(Sponsored by Northern Helicopters Ltd.)

- Radio control equipment ● Aircraft
- Car and marine engines ● Helicopters
- IC and electric cars ● Boats and yachts
- Railway layouts and engineering products.

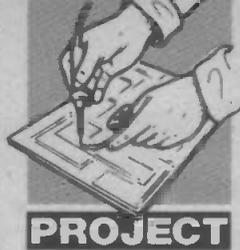
Further details and advance tickets available from: Argus Specialist Exhibitions
Argus House, Boundary Way, Hemel Hempstead, Herts. HP2 7ST. Tel: 0442 66551.



PROJECT

A Virtual Chart Recorder

- Part 2

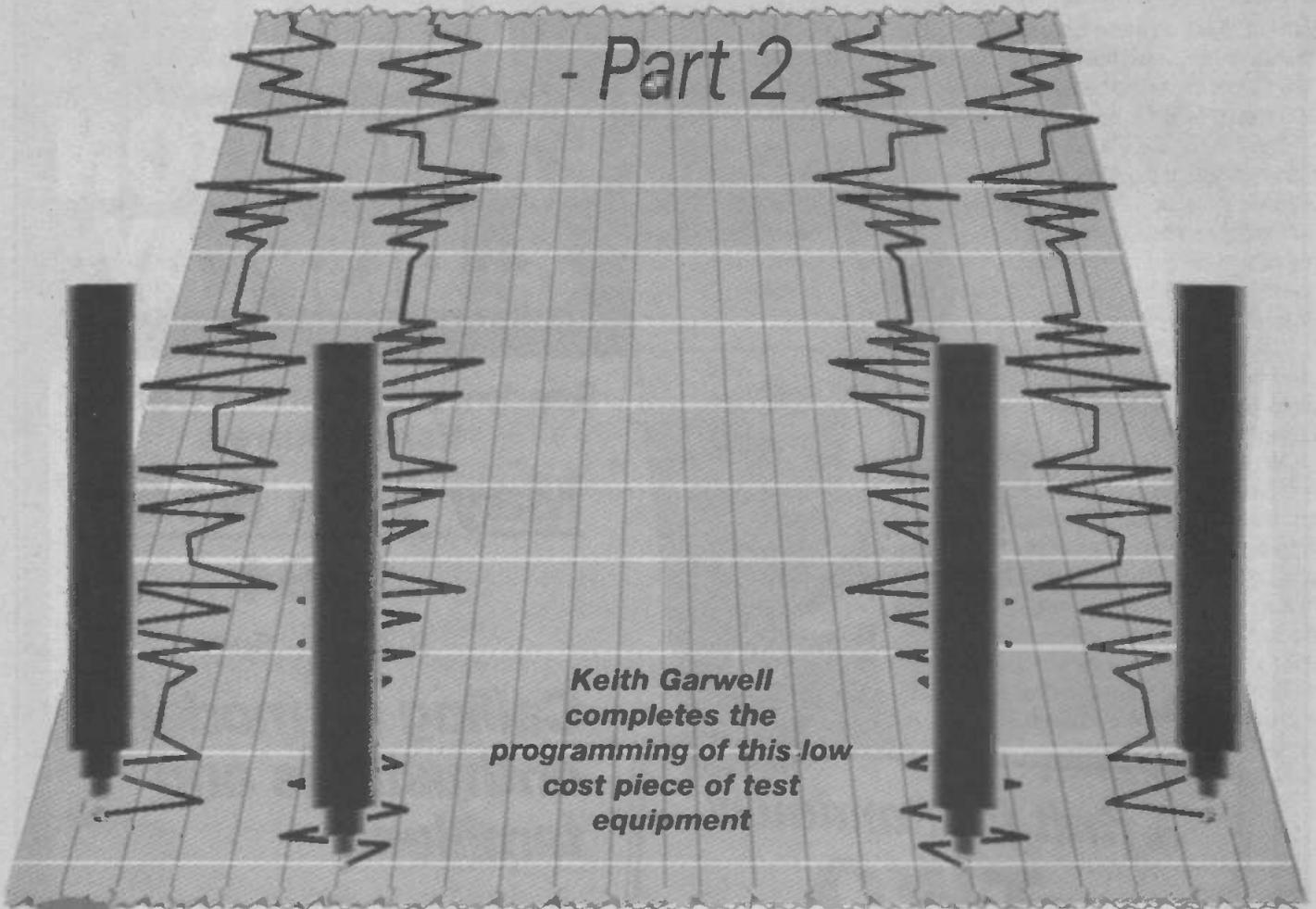

*Keith Garwell
completes the
programming of this low
cost piece of test
equipment*

Now that we have the hardware for the chart recorder and the ADC routine at line 200, the next step is to plan and then write the rest of the program. The outline of the software is quite simple viz-

Set up the buffer and other variables

Put up headings

Read in from the user any controls e.g.
Clock time, number of traces (inputs)
Any notes for the start of the run
Starting time

Calculate any values required for clock, etc.
Calculate the maximum duration of the run and put it on the screen

Start recorder loop
Read keyboard to see if action required
Read ADCs and put on screen and in buffer

Check for buffer full
Wait for clock tick
Repeat loop

Perform any actions required
Back to loop or finished

If finished
End of run notes
Dump data to file

END

Although simple the outline does require a number of design questions to be answered. These are centred around two functions - how to display the data on the screen and how to save the data in the buffer? Unfortunately, life is made a little difficult because these two questions cannot be dealt with in isolation.

The size of the screen in this case has to be measured in pixels and the usual common values are around the following, horizontal first.

256 x 192
 640 x 200
 640 x 350
 640 x 480
 720 x 348

I will assume the chart will be drawn horizontally to fit the normal convention of time along the X or horizontal axis and amplitude along the Y axis. This doesn't have to be the case and it should be fairly easy to turn the argument through 90 degrees.

It will be most convenient to set the horizontal axis in a multiple of 60, so that it fits either seconds or minutes. Consequently, using the above figures then 240, 600, 660 or 720 fits the bill. In the demonstration program coming shortly, 600 seems to fit the bill nicely.

The vertical axis will, on the face of it, be dependant upon the resolution of the ADC. However, there is really a more immediate consideration, namely the user. I think it will be difficult to appreciate a trace more than 128 pixels vertically. Indeed my chart recorder uses a Dragon, the ADCs of which only have a resolution of 6 bits, i.e. 0 to 63, giving charts only 64 pixels deep and I have never (so far) found this restrictive.

So those are the basic arguments about the screen. When I come to talk about the software in detail it should be possible to make these dimensions variable or at least easily changed, by changing the code.

Now for the buffer. At first sight there doesn't seem to be any problem with the buffer. Since most of the ADCs are 8 bit, just bang the data in, one sample per byte. Which is fine, so long as it's only ADC data that's being put into the buffer. But what about the notes at the start and end of the run? How about some comments during the run? What about details of the run, like start time, tick time, etc.? Where will they be kept? Will the ADC data ever be sent over a serial RS232 link? I do this, sending the data from the Dragon buffer to a file on the PC and the snag is that low values are used as control characters on serial links. In fact, decimal 26 is the end of file character and, if sent, would stop the PC in its tracks!

The only problem really is to mark the start and finish of different types of data. Why not have some control codes such as 255 for start of ADC data and 254 for end of ADC data. 253 for start of text message and 252 for end of text message.

Take this a step further and never use a value of less than 40. If we do this, then all the data can go into the buffer of whatever type and there is no problem transferring it around any system, or recording it on disk and so on.

If we are using 8 bit ADCs, how about restricting the scale to 0 to 200, i.e. 0 to 2 V? Then adding 40 so that nothing less than 40 appears in the data. That gives a maximum ADC data value of 240, leaving 241 to 255 to be used as control codes.

If you are going to use one of the units that will digitise up to 16 bits, then a similar technique could be used, while using two bytes of the buffer for each item.

There are various ways of encoding data of different types, as our MIDI users will know. For example, if the byte has its most significant bit set, it's a control code and there is only one byte to it. If the most significant bit is zero, then it is the first byte of a pair containing ADC data.

Software in Detail

Its time to get down to the nitty gritty, enough talking. I am going to design a system using BASIC, a PC and an ADC-16. This will enable me to illustrate most of the points, using a fairly universal language and a hardware sub-routine for gathering the

data. This will be the only bit that might be different to your own system.

5 DATA Chart Recorder for PC and ADC-16
 V1.00
 8 DATA Copyright K.Garwell 1993.

(But free etc.)

```
10 DEFINT A-Z:DEF SEG=&H9000:DIM
  ADCVAL(7),DIFFVAL(8)
20 DIFFVAL(0)=128:DIFFVAL(1)=64:DIFFVAL
  (2)=32:DIFFVAL(3)=16
30 DIFFVAL(4)=8:DIFFVAL(5)=4:DIFFVAL
  (6)=2:DIFFVAL(7)=1
40 DIFFVAL(8)=1:BUFLIMIT!=64000:RESMODE
  =15
90 GOTO 1000
```

The DEF SEG defines a segment address 64K below the top of my memory, which is 640K. If you don't have this facility and the buffer has to be within the BASIC area, then use the CLEAR instruction, e.g. :CLEAR 100,&H2900-1:. This will save 100 bytes for strings and set the top of memory so that the buffer can start at &H2900. This allows sufficient for the program I should think. If you get an out of memory error, increase the value in steps until it works. BUFLIMIT! sets the value at which the buffer warning is given, while RESMODE defines the resolution and mode for use by the line 200 routine.

```
100 IC$=INKEY$:IF IC$="" THEN 100
110 RETURN
```

A simple keyboard routine to read single characters.

```
200 FOR CHAN=0 TO 7
210 CTRLBYTE=RESMODE+CHAN*32
220 PRINT #1,CHR$(CTRLBYTE);
230 IF LOF(1)
230 IF LOF(1)<0 THEN 230
240 ADC$=INPUT$(3,#1)
250 ADCVAL(CHAN)=ASC(MID$(ADC$,3,1))
260 IF ADCVAL(CHAN)<MINVAL THEN
  ADCVAL(CHAN)=MINVAL
270 IF ADCVAL(CHAN)>MAXVAL THEN
  ADCVAL(CHAN)=MAXVAL
280 NEXT:RETURN
```

This is the same as the previous driver, except that the ADC value is limited to 8 bits positive, otherwise more than 1 byte would be needed to store it. The other difference is that the channel number is generated within the routine. RESMODE is part of the control byte and identifies resolution and mode. In addition, two lines are added, 260 and 270, which enforce the limits allowing the inclusion of control characters in the buffer.

```
300 LINE INPUT"MSG ? ";IC$
310 POKE BPTR!,253:BPTR!=BPTR!+1
320 FOR I=1 TO LEN(IC$)
330 POKE BPTR!,ASC(MID$(IC$,I,1)):BPTR!=
  BPTR!+1
340 NEXT
350 POKE BPTR!,252:BPTR!=BPTR!+1 360
  IC$="" :RETURN
```

This routine allows a message to be inserted in the buffer, updating the buffer pointer BPTR! as it goes along. The message is surrounded by two control characters, values 253 as start-message and 252 as end-message.

That's all the subroutines, now for the start of the main code.

```
1000 SCREEN 2:CLS:RESTORE:READ IC$:PRINT
      IC$:READ IC$:PRINT IC$
```

Put up the header messages. Screen 2 indicates the type of graphics screen in use and is one of the commands/functions that does depend on the origin of the BASIC. It is dependant also on the machine in use. For example, to the BASIC compiler which I usually use, SCREEN 2 indicates the high resolution graphics screen often referred to as "Hercules". However, to the ancient IBM XT that I have also used, this means the colour graphics screen. Oddly enough, therefore, this program will run unchanged on either machine, either compiled or interpreted.

```
1010 PRINT"Dump, Stop, Restart, Quit,
      Message"
1020 INPUT"Tick time in seconds ";TICK-
      TIME:LOCATE CSRLIN-1,40
1030 INPUT"Number of traces ";NUMTRACES
1040 LINE INPUT"Start message ?
      ";STMSG$:LOCATE CSRLIN-1,40
1050 PRINT"Chart duration ";
1060 PRINT USING "####.# HOURS";2^16
      /NUMTRACES*TICKTIME/3600
1070 OPEN"COM1:9600, N,8,1,RS,CS, DS,CD"
      AS #1
1080 INPUT"Start time hhmm ";STTIME$
1090 TW=100:OF=190:DS=40:BPTR!=1:MINVAL=
      0:MAXVAL=200
1100 LOOPTIME!=INT(TIMER):POKE 0,255
```

Fairly straightforward, setting up the working variables after reminding the user (1010) what the options will be when running. As I am going to use a full segment of 64K for the buffer, line 1050 uses 2^{16} as the buffer length. Any other way of giving the correct figure for 64K will do. This method just saved me from having to think about it as I wrote it.

TW is the trace width and OF the offset to position the traces up or down the screen. 190 is suitable for many screens but can be changed as necessary, to accommodate particular machine/BASIC combination.

DS is the data shift added so that no values less than 40 are inserted in the buffer, in case its contents are ever passed over a serial link where low values may be interpreted as control codes. BPTR! is the buffer pointer. Note that the buffer pointer cannot be an integer as declared at the beginning in line 10, because it would cause overflow. A BASIC integer only handles -35K to +35K and so would be too small for a 64K pointer.

MINVAL and MAXVAL are the limits placed on the ADC value to allow control codes and data to be included in one byte. I have used two letter identifiers in one or two places to shorten the lines of code, really only for the purpose of this article, give them their proper names by all means. A word about the time statements later, and lastly poke 255 as the first byte of the buffer, indicating beginning of ADC values. I am going to take the easy option and have two separate files, one for text and one for binary.

Now for the main loop

```
1140 IC$=INKEY$:IF IC$>" " THEN 2000
1150 LINE(X,OF)-(X,OF-TW),0
1160 IF X<600 THEN LINE(X+1,OF)-(X+1,OF-
      TW),1
```

The first line checks to see if a key has been pressed and, if it has, bombs off to line 2000 to do something about it. The code at line 2000 doesn't exist yet (I hadn't written it at the time of writing - remember this has all been edited in the light of experience since it was first written) but it's a good line number to start on when we get there. The next two lines clear a vertical line and draw the cursor. The 0 and 1 refers to black and white - again it may be machine/BASIC dependant.

Now for the heart of the matter. To actually put useful information on the screen.

```
1200 GOSUB 200
1220 FOR CHAN=0 TO NUMTRACES-1
1230 PSET(X,OF-ADCVAL (CHAN)/2):POKE
      BPTR!,ADCVAL(CHAN)+DS:BPTR!=BPTR!+1
1240 NEXT
1250 X=X+1:IF X>600 THEN X=0
1260 IF BPTR! <BUFLIMIT! THEN 1300
1270 PRINT"BUFFER OVERFLOW, PRESS ANY KEY
      TO DUMP"
1280 GOSUB 100:GOTO 3000
```

Again fairly straightforward. Each channel selected by NUMTRACES (it could have been NUMCHANS) is put on the screen and into the buffer. If the screen pointer, or X as I've called it, is greater than 600, then it starts again at 0. This is one of the best of reasons for having the cursor. 600 seemed a suitable choice of value as many systems provide a horizontal resolution of 600-720 or more.

Likewise, the buffer pointer is checked. If it has reached the end of the buffer, we must stop the recorder and make it clear that we have run out of buffer space.

The next step is slightly tricky. We have to wait until the tick time has expired before going round the loop again for the next set of samples. On the PC this is fairly easy to achieve as we have two options. There is a TIMER, which gives the time since midnight in 100ths of a second and a TIME\$, which returns the time in hours, minutes and seconds. Either of these can be used, it's just a question of getting the thinking straight to allow for the advent of midnight in one case and the clock number base of 60 for seconds and minutes.

There is also the possibility of another type of TIMER function, as is provided on the Dragon. This has a timer which ticks 50ths of a second but which is not linked to real time. It can be set, e.g. :TIMER=0; and read, e.g. :TI=TIMER:. The problem with this is that you may not know at what value the timer spills, i.e. goes back to zero. If this is the case, try the following. I have used fictitious line numbers so as not to confuse it with the program for the PC.

```
X000 IF TIMER<LT THEN X000 ELSE LT=LT+TT
X010 IF LT>50000 THEN TIMER=0:LT=TT
X020 GOTO start of loop
```

LT is the loop time, the time at which the loop should continue. TT is the number of ticks between readings, as set at the beginning of the run. In this case it is seconds multiplied by 50.

At the beginning of the run, LT is set equal to TT. Thus, at the end of the loop, the program waits for this value to be

reached. TT is then added to LT to give the value for the next time round and so on, but not ad infinitum because at some point the time will spill to zero (the equivalent of midnight for the PC type of timers already mentioned). To avoid trying to get the arithmetic right, the second line, X010, resets the counter when it gets to 50000.

However, with the PC we have to get the arithmetic right because resetting the timers would alter the PC's clock.

Using the PC timer function is easiest, so here goes.

```
1300 LOOPTIME!=LOOPTIME!+TICKTIME
1310 IF INT(TIMER) <LOOPTIME!-86400 THEN
    LOOPTIME! =LOOPTIME!-86400
1320 IF INT(TIMER) <LOOPTIME! THEN 1320
1330 GOTO 1140
```

First calculate LOOPTIME, the time at which the loop repeats and then, in line 1310, check that the timer has not reset, i.e. just gone past midnight, and correct the LOOPTIME if it has by subtracting 86400, the number of seconds in a day. Then wait for the time to expire in line 1320.

This timer routine is written such that the time is in seconds and the fastest recording speed is therefore 1 sample every second. The TIMER function usually returns hundredths or tenths of a second as a decimal fraction (hence the INT functions) so, in fact, the program could be tweaked to run faster than in 1 second steps.

In any case, it would be wise to add a line which checks that the program is not running slow, by adding a line which checks for this in front of line 1320. Do the experiment with all channels selected. For instance:

```
1315 LOCATE CSRLIN,1:IF INT(TIMER)>LOOP-
    TIME! THEN PRINT"L"; ELSE PRINT"E";
```

The "E" indicates early, i.e. ready and waiting. I'm sure you will guess what the "L" stands for! This would give, by experiment, the fastest the program will run - then take the line out. I have tried this program on an early IBM and it ticks seconds perfectly with all 8 channels in operation.

Next the actions, dump, quit, etc.

```
2000 IF IC$="d" THEN 3000
2010 IF IC$="s" THEN END
2020 IF IC$="q" THEN SYSTEM
2030 IF IC$="r" THEN RUN
2040 IF IC$="m" THEN GOSUB 300:GOTO 1140
2050 GOTO 1140
```

The actions offer dump to disk, stop but remain in BASIC, quit, i.e. leave BASIC, restart and message, i.e. insert a message in the buffer. You will find that after inserting a message it ticks quickly to make up the time lost while typing the message. I have found the in-line message very useful to note unforeseen changes during a run, e.g. "It just blew up!".

Which leaves only the dump to disk.

```
3000 LINE INPUT"End message ? ";ENDMSG$
3010 INPUT"File name without suffix
";FILENAME$
3020 IF FILENAME$="" THEN RUN
3030 OPEN"O",#2,FILENAME$+".CRT"
3040 PRINT #2,STMSG$;" : ";STR$(TICK-
TIME);" : ";STR$(NUMTRACES);" : ;
```

```
3050 PRINT #2,STTIME$;" : ";ENDMSG$
3060 CLOSE #2
```

```
3100 POKE BPTR!,254
3110 BSAVE FILENAME$+" . CRB",0,BPTR!+1
```

Nothing very spectacular here, I even took the easy way and put the setting up text in one file, filename.CRT and the ADC data in another called filename.CRB. The first is a simple text file, the second a simple binary file. And that is why the file name is ask for "without suffix".

So here are the last two lines -

```
3120 PRINT"Finished" 3130 GOSUB 100:GOTO
2000
```

The gosub line 100 is so that nothing is cleared from the screen until a key has been pressed.

The Display Program

Although the chart recorder program puts the trace(s) on the screen as well as in the buffer, it is useful to have a program which will replay the recording.

Much of what follows will have appeared already in the recorder program and the comments will apply to this also. Anyway here it is.

```
5 DATA Chart Recorder Display for ADC16
V1.00
8 DATA Copyright K.Garwell 1993
10 DEFINT A-Z:DEF SEG=&H9000:DIM
ADCVAL(7)
90 GOTO 1000
```

Not much setting up this time and the comments about the buffer, DEF SEG, etc., will be the same as before. In fact the statements in this program should be the same as those in the recorder program.

```
100 IC$=INKEY$:IF IC$="" THEN 100
110 RETURN
```

Wait for a key being pressed.

```
300 LINE(X,OF)-(X,OF-TW),0:IF X<600 THEN
LINE(X+1,OF)-(X+1,OF-TW),1
310 RETURN
```

The same code as used to clear a line and set the cursor but this time used also to mark the position at which comments were made by means of the in line message facility.

```
1000 SCREEN 2:RESTORE:READ IC$:PRINT
IC$:READ IC$:PRINT IC$:PRINT
```

Put up the heading and then read all the control values and the start and end messages from the text file filename.CRT. These were all separated by colons so the code looks for the colons to find the appropriate fields.

```
1010 INPUT"FILE NAME WITHOUT SUFFIX
";FILENAME$:LOCATE CSRLIN-1,40
1020 OPEN"i",#2,FILENAME$+".CRT"
1030 LINE INPUT #2,TEXT$
```

```

1040 COLON=INSTR (1,TEXT$,":")
1050 STMSG$=LEFT$ (TEXT$,COLON-1)
1060 START=COLON+1
1070 COLON=INSTR(COLON+1,TEXT$,":")
1080 TICKTIME=VAL(MID$(TEXT$,START,COLON-
  START))
1090 START=COLON+1
1100 COLON=INSTR(COLON+1,TEXT$,":")
1110 NUMTRACES=VAL(MID$(TEXT$,START,
  COLON-START))
1120 START=COLON+1
1130 COLON=INSTR(COLON+1,TEXT$,":")
1140 STARTTIME$=MID$(TEXT$,START,COLON-
  START)
1170 ENMSG$=RIGHT$(TEXT$,LEN(TEXT$)-
  COLON)
1180 CLOSE
1190 PRINT"Start msg ";STMSG$
1200 PRINT"Tick time seconds ";TICK-
  TIME;:LOCATE CSRLIN,40
1210 PRINT"Num traces ";NUMTRACES
1220 PRINT"Start time
  ";STARTTIME$;:LOCATE CSRLIN,40
1230 PRINT"End msg ";ENMSG$

```

The descriptors ticktime, etc., having been recovered from the text file, now recover the ADC data from the binary file.

```

2000 BLOAD FILENAME$+".CRB"
2200 TW=100:OF=190:DS=40:BPTR!=0:TRACE=0:
  X=0:MSG=0
2210 GOSUB 300

```

Variables set up and cursor on screen, now read the buffer byte by byte.

```

2300 BUFVAL=PEEK(BPTR!):BPTR!=BPTR!+1
2310 IF BUFVAL=255 THEN 2300

```

ADC data starts skip to next byte

```

2320 IF BUFVAL=254 THEN PRINT"
  Finished":GOSUB 100:GOTO 4000

```

ADC data ends, finished but wait for key press before exit.

```

2330 IF BUFVAL=253 THEN MSG=-
  1:LINE(X,OF)-(X,OF-
  TW),1:PRINT"/";:GOTO 2300

```

Start of inline message detected. Set the MSG flag to show a message is in progress, set the cursor to show where message was inserted, print a / to show start of message (there might be more than one, so there needs to be a separator).

```

2340 IF BUFVAL=252 THEN MSG=0:GOTO 2300

```

If it's the end of a message, clear the message flag and read the next byte.

```

2350 IF MSG THEN PRINT CHR$(BUFVAL);:GOTO
  2300

```

If there's a message in progress, print the byte as a character and read the next byte. Don't miss the semicolon.

```

3010 PSET(X,OF-(BUFVAL-DS)/2)
3030 TRACE=TRACE+1
3040 IF TRACE>NUMTRACES THEN
  X=X+1:TRACE=0:GOSUB 300

```

Otherwise it's ADC data set the appropriate pixels for each trace, advance the screen pointer X and set the cursor.

```

3050 IF X>600 THEN X=0:GOSUB 100

```

If the full width has been reached, reset the screen pointer and wait for a key press before starting at the beginning of the screen again.

```

4000 IF IC$="q" THEN SYSTEM
4010 IF IC$="r" THEN RUN
4020 GOTO 2300

```

If the key pressed was a q, then leave BASIC, else if the key pressed was an 'R' restart the program, otherwise continue reading the buffer.

In Conclusion

The programs shown are adaptable to considerable enhancements to suit your own purpose, which is one big advantage of this type of DIY exercise. Possible enhancements which occur to me.

If you use a colour monitor then the traces can be coloured to ease identification. Change the colour identity in the PSET instruction for each channel.

The screen vertical offset OF could be altered from trace to trace, so that the traces were positioned one above the other, rather than on top of each other as they are here. I know the latter sounds bad but, in practice, unless the traces are all similar quantities, e.g. temperatures, or there are a lot of them, it is fairly easy to distinguish one from the other.

The easiest way to do it would be to have an array of channel offsets which could be set by the user, along with tick-time, etc. Then include this value in the loop which sets the pixel for each channel.

Adding any arithmetic to modify the value measured by the ADC is probably best done in the line 200 routine. You may then need to move the message handling routine up to line 400 from 300 to allow the ADC routine more elbow room.

Printing details from the screen is most easily done by using the print-screen supplied with the computer. This is a possible candidate for DIY but it's not so easy to get right. Most printers can be set into graphics mode and for the 9 pin models this allows 8 pins to be driven by every byte sent to the printer. Thus, 0 to 200 would be spread over 25 lines, the line spacing being adjusted so that there is no gap between successive lines. Use an array of 25 strings to represent the print lines and direct the data to them by dividing the ADC value by 8. This selects the string number and the remainder selects the pin to be activated.

The X value selects the byte in the string. Don't forget to OR the values into the bytes, so that if two traces select the same byte, one doesn't delete the other!

ADC-16 is available from: **Pico Technology Ltd.**
Broadway House, 149-151 St. Neots Road,
Hardwick. Cambs. CB3 7QT. Tel: 0954 211716.

BADGER BOARDS

Printed Circuit Boards

Prototype-Singles-Multiple runs. Minimum charge £15.00. Artwork, Plotting from Schematic to final board layout. Send S.A.E. now for Catalogue of Kits-Boards-Projects available. Many magazine boards produced for individual customers.
 Dept: HRT 87, Blackberry Lane, Four Oaks, Sutton Coldfield,
 B74 4JF *** 021-353 9326

MPU Fundamentals

In the last part of this series we look at communications between computers, and between a processor and peripheral I/O devices, as well as taking an in depth look at the mysteries of the RS232

Conventionally, when we talk about input and output from a microprocessor system we are talking about parallel communications. The use of an eight line I/O port to output, or input, a logic pattern corresponding to a single byte in the processor's memory, with each bit in that byte corresponding to a specific I/O line on the port.

Thus, if we want to output text from a computer system to a peripheral device, say a printer, we could use a parallel port to transmit the text as ASCII code (see table 1 for ASCII character codes) one character at a time. If we were to use the full ASCII code, we would require all eight I/O lines on a port, but we would also need a means of telling the peripheral device that there was valid data being output on the port. We can do this with the aid of one or more special lines, known as a handshaking lines. These are shown in Figure 1.

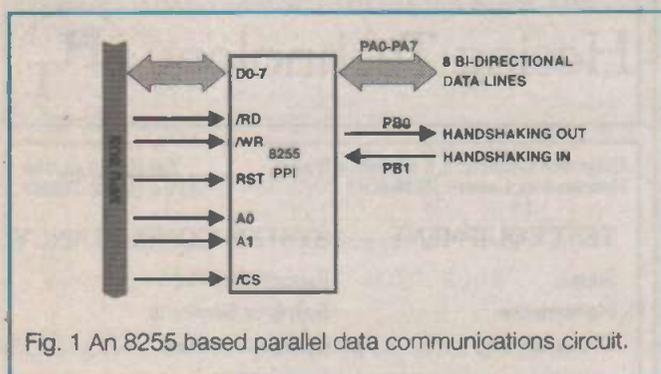


Fig. 1 An 8255 based parallel data communications circuit.

We cannot just keep changing the data on the I/O port lines without some way of synchronising this sequence of data output bytes with the hardware that is reading the incoming data. We cannot rely on the system reading the data being able to recognise a change in the data. For example, we might output the text word 'NEED' in ASCII code form. This has two consecutive Es and without some form of synchronisation, how is the receiving system expected to recognise that there are two Es rather than just one?

A bidirectional parallel I/O port would use two handshaking lines, one to synchronise output and one to synchronise input. The synchronisation function of either of these handshaking lines consists simply of toggling the line when there is valid data on the I/O port, this can be seen in the waveform diagram in Figure 2.

As far as the processor transmitting the data is concerned, handshaking simply consists of toggling the handshake line, but the processor or peripheral receiving the data has to keep

looking at the state of the handshake line before it can read the data from its I/O port. There are two ways of doing this, one is to poll the handshake line and the other is to attach the handshake line to the processor interrupt.

Polling means that the processor is running a program which repetitively looks at the state of the handshake line, and checks to see if there is valid data waiting to be input. If there is, then the polling program branches to a routine which inputs the data. If the state of the handshake line indicates that there is no data waiting to be input then program control will return to the main task. Usually, the polling routine is initiated by a regular interrupt generated by some form of timing circuit. However, if the main application allows, it could be just a simple software loop.

The trouble with a polling technique is that it slows down a processor's operating speed, since program control is repeat-

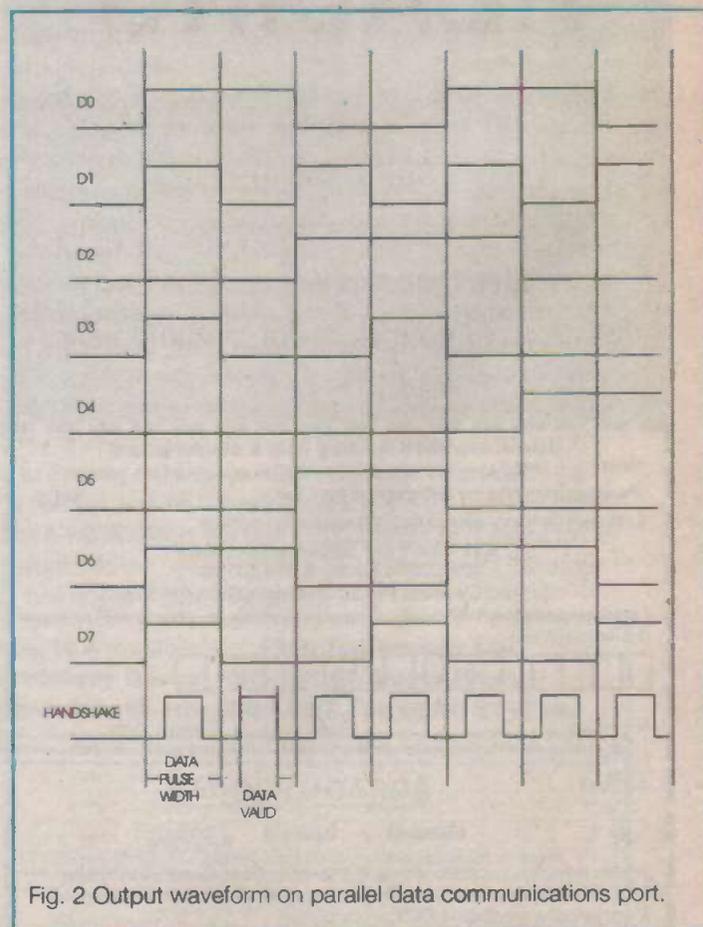


Fig. 2 Output waveform on parallel data communications port.

edly being diverted to check the state of the handshake line and perhaps also to input data. The higher the data transfer rate the greater this problem, since the polling rate needs to be considerably higher than the transfer rate.

For these reasons, the preferred technique is to attach the handshake line to a processor interrupt. In this way, the processor is not tied up looking at the state of the handshake line and there is no constraint on the speed of data transfer, it can be fast, slow or even of variable speed.

This means that an interrupt connected handshake system is a lot more versatile and also a lot simpler to implement.

Parallel data communications offer a very good way of rapidly transferring large quantities of data between two computing devices. Indeed with a properly designed parallel communications system, it is possible to transfer data at millions of bytes per second, though only over very short cable lengths. This high data transfer rate means that parallel communications are the preferred solution for linking computers to data hungry peripherals, such as laser printers.

Serial Communications

Parallel data communications may be easy to implement, but they also suffer from some major problems. The first drawback is that a parallel data communications system utilises a full eight bit I/O port as well as a couple of handshake lines and, in some systems, such hardware I/O resources are at a premium. Another drawback is that they require eleven separate wires - the eight data lines, two handshaking lines (one for data input and one for data output) and a ground line.

The large number of wires means that the cables are bulky and have to be kept fairly short because of signal degradation. This degradation is the result of many factors, including cross-talk, signal reflection, low drive voltage (you will rarely find a parallel printer cable more than two or three metres long). There is also the problem that data in a parallel form can not be transmitted long distances over conventional telecommunications systems.

The solution is to trade a high data transfer rate for a reduction in the number of wires. In other words send the data in serial form rather than parallel form. In its most fundamental form such a bidirectional serial communications link will consist of just three wires - one carrying data coming into the system, one carrying data being transmitted by the system and the third being a common ground line.

In a serial communications system, the data, in eight bit chunks, is converted from the parallel format used on the processor data bus to a string of pulses representing one bit after another in strict time sequence, which is output on a single line. The device receiving such serial data reverses the procedure and converts the sequence of eight pulses back into eight bit parallel form. This procedure can be seen in the diagram in Figure 3.

As can be seen in the diagram in Figure 3 the hardware used

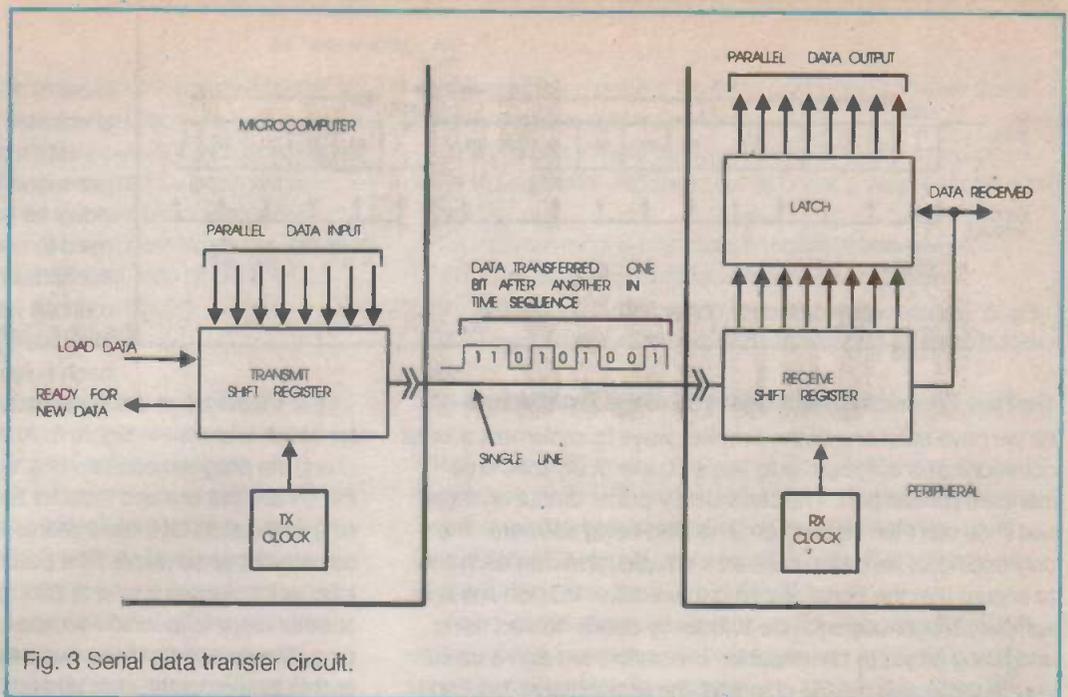


Fig. 3 Serial data transfer circuit.

to implement serial data communications is relatively simple. Indeed a simple serial communications port can be constructed using just two lines on a conventional I/O port and performing the serial to parallel data conversion using software. However, in most cases, special hardware is used.

Since serial communications take place asynchronously, in other words there is no handshaking or clocking line, it is necessary for the serial data to include its own synchronisation signal. This synchronisation is achieved by the use of start and stop bits, these are shown in Figure 4. Note that in this waveform there is one start bit and two stop bits.

The normal state of the line is 'logic 1', allowing the system to test that the line is functioning. When receiving serial data, the computer or peripheral device waits for the falling edge of the start bit before clocking in the data. It is this falling edge

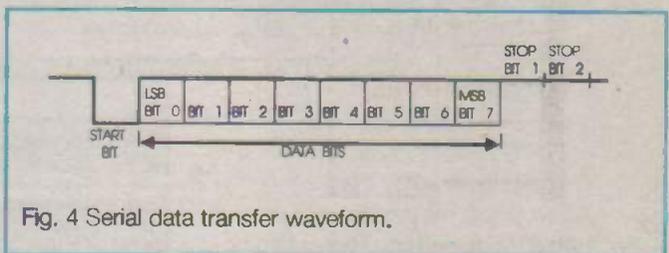


Fig. 4 Serial data transfer waveform.

which starts the synchronisation and it means that slight discrepancies in the clocking rate, up to a maximum of about 1/2 bit time, will not be added onto each other over successive bytes but will be corrected at the start of each byte. This automatic correction of clocking rate errors can be seen in Figure 5.

In order for the data to be correctly clocked in, it is of course important that transfer rates are at a predetermined frequency. This frequency is usually referred to as the Baud rate and is equal to the number of bits that are transmitted each second down the serial line. It should be noted that this count includes not just the eight data bits but also the start bit and the two stop bits. This means that a 300baud serial link will be capable of transferring data at the rate of 300/11 or 27.273 bytes per second. (There are other serial data formats than the one mentioned here, for example there may be only six data bits and perhaps just one stop bit. Obviously it is very important that the data formats of receiver and transmitter match, just as their baud rates should match)

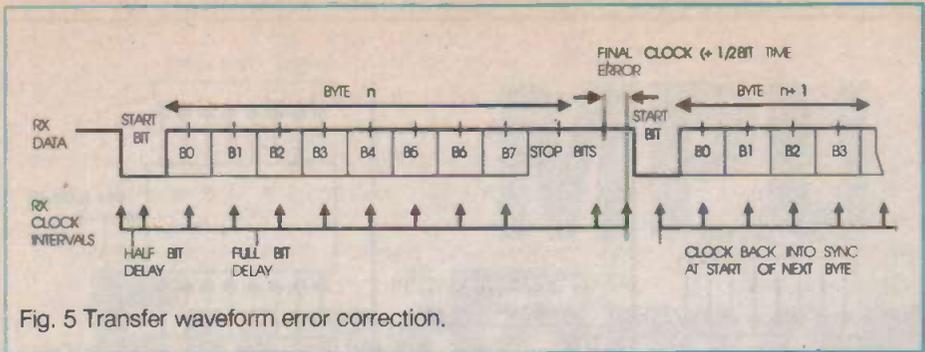


Fig. 5 Transfer waveform error correction.

Serial Communications Using Software

As we have seen one of the simplest ways to implement a serial communications system is to use a couple of I/O lines on a standard parallel port. The serial data input or output on those two lines can then be read or generated using software. The only additional hardware needed is a buffer/driver on each line, to ensure that the signal reaching the receiver I/O port line is of sufficient magnitude and has sufficiently clearly defined rising and falling edges to be readable. The buffers are also a useful way of protecting the I/O chip from the accidental introduction of higher voltages, which might result from the user connecting it to the wrong type of equipment.

The first thing to decide when designing such a system is the data transfer rate and the data format. These should correspond to one of the common standards and will probably be dictated by the equipment with which the system is communicating. Thus, we might decide to use the commonly used 2400baud data transfer rate, with a data format consisting of one start bit, eight data bits and two stop bits. In other words, a system

capable of transferring data at 218.182 characters per second.

With a data transfer rate of 2400 bits per second, we can say that each individual bit has a duration of 417µs. We need to know this time duration, since the software serial input and output routines will have to generate a correctly timed delay in order to be able to clock each pulse in.

Let's first look at the serial data input routine, the flow chart for which is shown in Figure 6. At the beginning of the flow chart, the program consists of a loop which checks the state of the serial input line and tests for the falling edge at the beginning of the start bit (note that this is where the synchronisation adjustment takes place). The processor then goes into a delay loop which causes it to wait 208.5µs, half a bit time, then another delay loop which causes it to wait 417µs, a whole bit time. The reason for these two delays is to wait through the entire duration of the start bit and then half way through the duration of the first data bit. In this way the state of each bit in the data stream is tested in the middle of each pulse, to ensure optimum reading accuracy.

The serial input routine then repeatedly loops around the serial input part of the code - waiting 417µs, inputting the state of the serial line, adding that bit to the assembled character, decrementing a counter set to 8 at the start of the byte input routine, then checking to see whether that counter is zero and all eight bits have been input and if so exiting the bit input loop.

RS232 Communications Revealed

Virtually anyone who uses computers will be familiar with the tag RS232, used in association with serial data communications. We talk of RS232 cables and of RS232 ports, so what exactly is meant by RS232?

It stands for the Recommended Standard (RS) number 232, which was produced by the Electronic Industries Association (EIA). This standard, and we are now in fact on revision RS232C, specifies the interconnections between two systems, so that they can communicate serially over reasonably long distances, up to about 500ft in some applications. This is purely a physical standard, covering the permissible connectors, the pin designation on those connectors, the control lines and the way that the data is transmitted, the voltage levels, etc.

Let's first look at the electrical specifications. The first thing to note about the RS232 specifications is that they entail using much higher voltages. This has been done in order to reduce the problem of electrical noise. In most modem RS232 communications systems, a signal in the range +3V to +12V represents a 'logic 1', while a signal in the range -3V to -12V represents a 'logic 0'.

The specifications say that an RS232 trans-

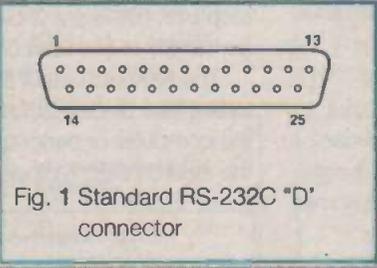


Fig. 1 Standard RS-232C 'D' connector

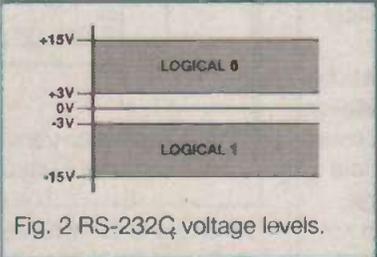


Fig. 2 RS-232C voltage levels.

mitter should have a minimum output voltage swing of ±5V when loaded with the nominal 5kohm input resistance of an RS232 receiver. The specifications also dictate that the slew rate of the transmitter is limited to less than 30V/µs, a factor which limits the maximum usable RS232 baud rate to 19200.

The specifications indicate that the maximum baud rate can be traded for cable length - the shorter the cable the higher the baud rate. The factors which govern this are cable load capacitance, slew rate of the driver under high capacitive loading and the receiver's threshold and hysteresis. When determining the maximum cable length, bear in mind that the load capacitance of the cable should not exceed 2500pf.

Having looked at the electrical specifications of RS232 now lets look at the interconnections.

Considering that part of the rationale for serial data communications is that it uses as few lines as possible, it is rather surprising that the RS232 standard specifies a 25 pin D connector as the interconnection device. It is even more surprising to discover that all but three of those 25 lines have been assigned some particular function. In other words a full specification RS232 cable would have 22 separate wires and the following table shows these specified connections:

Pin	Description	Name	RS232
1	Protective ground	Prot	AA
2	Transmitted data	TXD	BA
3	Received data	RXD	BB
4	Request to send	RTS	CA

The rest of the routine just consists of a further set of delays equal to the time period of the two stop bits.

We now move on to the serial data output flowchart in Figure 7. This is very straightforward and requires little explanation. Obviously, in the above examples different baud rates would require different delay times and different data structures, different numbers in the bit counter and a different stop bit delay time.

Hardware Based Serial Data Communications

A software based serial data communications system is quite easy to implement, but it has several drawbacks which lead many designers to implement serial communications using hardware. One major limitation is that the use of software timing loops means that the processor is tied up performing data transfer and cannot be used for any other task while this is taking place. This could be a major problem in systems which have interrupt signalled data input functions. All the timing of a serial data transmission or reception will be thrown out if a system interrupt occurs during data transmission. Since the processor will have to jump to the interrupt handling routine, perform that and then return to the serial data routine, the result is that synchronisation will have been lost and input data will either be lost or garbled.

The other problem with software controlled serial communications is that they are specific for a particular system. In most cases, programs will run equally well on different systems, with different system clock rates (in other words, different processing speeds). But change the clock rate and our software generated

delays are also changed, thereby making the software serial communications system useless.

The solution to both these problems is to use a dedicated serial I/O controller and these come under a variety of acronyms:

ACIA - asynchronous communications interface adaptor
 UART - universal asynchronous receiver/transmitter
 SIO - serial input/output
 USART - universal synchronous/asynchronous receiver/transmitter
 DART - dual asynchronous receiver/transmitter

These devices all perform the same kind of task and, by and large, the only real difference lies in the manufacturer and the family of microprocessors for which they were designed. Thus 6800/6502 MPU family users might use the 6850 ACIA and Intel or Z-80 users, the 8251A USART.

As far as the processor is concerned, chips like the 8251A and the 6850 look like a couple of memory or I/O locations which can be written to, or read from. In the 6850, the two addressable locations contain four registers, two of which are read only, the other two being write only. The read only registers are a status register and a receive data register. The write only registers are a control register and a transmit data register.

A circuit diagram for a typical USART based hardware serial communications system is shown in Figure 8. This circuit shows a 8251A, with associated 74138 address line decoder, producing a serial input line and a serial output line. The timing, in other words the baud rate at which the system will operate, is

5	Clear to send	CTS	CB
6	Data set ready	DSR	CC
7	Signal ground	GND	AB
8	Data carrier detect	CD	CF
9	-		
10	-		
11	Select XMT frequency	STF	CG
12	Secondary DCD	dcd	SCF
13	Secondary CTS	cts	SCB
14	Secondary XMT	xmt	SBA
15	Transmit clock	Xclk	DB
16	Secondary RCV	rcv	SBB
17	Receive clock	Rclk	DD
18	-		
19	Secondary RTS	rts	SCA
20	Data terminal ready	DTR	CD
21	Signal quality	SQ1	CG
22	Ring indicator	RI	CE
23	Data rate select	DRS	CH
24	External transmit clock	-	DA
25	Busy - standby	BY	-

Lets look at some of these lines in greater detail:

Prot

This is the protective ground line and will probably form a connection between the metal screening on the cable and the metal chassis of the two linked pieces of equipment.

GND

This is the signal ground line and provides a common reference for both input and output signals.

TXD

This is the line on which all serial data is transmitted, provided that the CTS signal, line 5, is active.

RXD

This is the line on which all serial data is received from other connected RS232 devices.

RTS

The logic level on this line indicates that an RS232 device is ready to transmit data. In order to find out when to expect data, this line is tested by the receiving device.

CTS

The state of this line is used to indicate that a device is ready to receive data transmitted to it by a connected RS232 device. It is used to inhibit data transfer until the receiving device is ready to accept it.

DTR

This line is used to indicate that the RS232 transmitting device is switched on.

DSR

This line is used to indicate that a connected RS232 receiving device is switched on.

Fortunately, hardly anyone would need to use a full specification cable and most applications require no more than three or four wires. Indeed, as one can see from the above table, many of the specified connections are exclusively for use with modems and thus unlikely to be used in any other application.

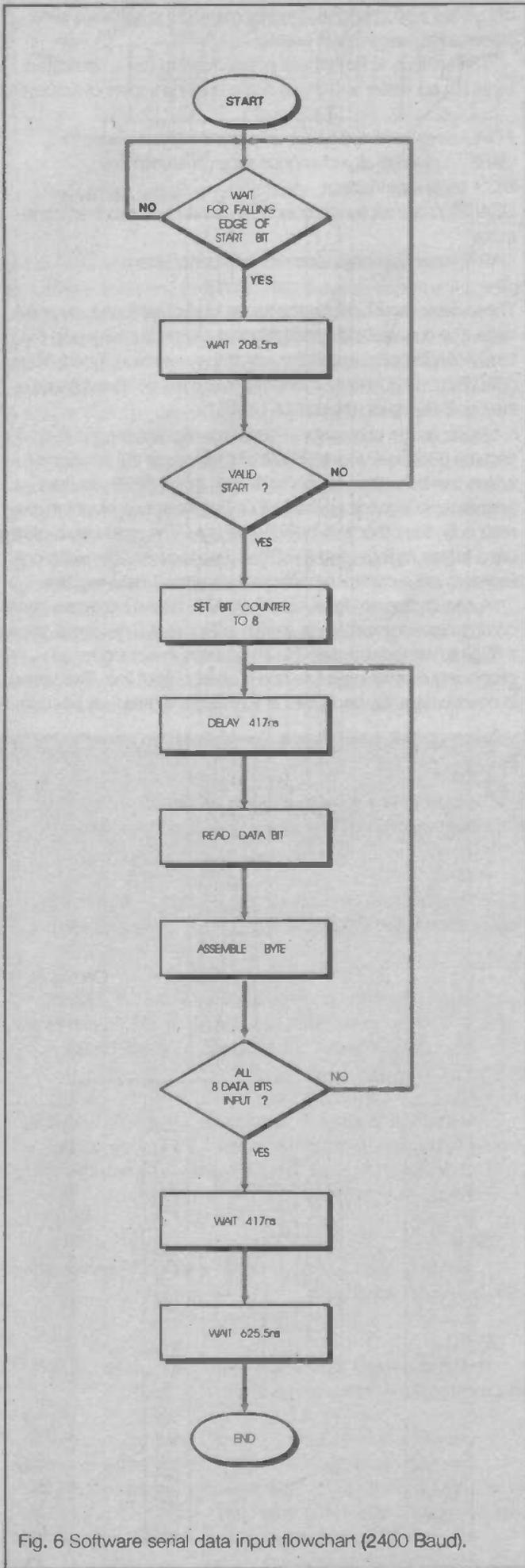


Fig. 6 Software serial data input flowchart (2400 Baud).

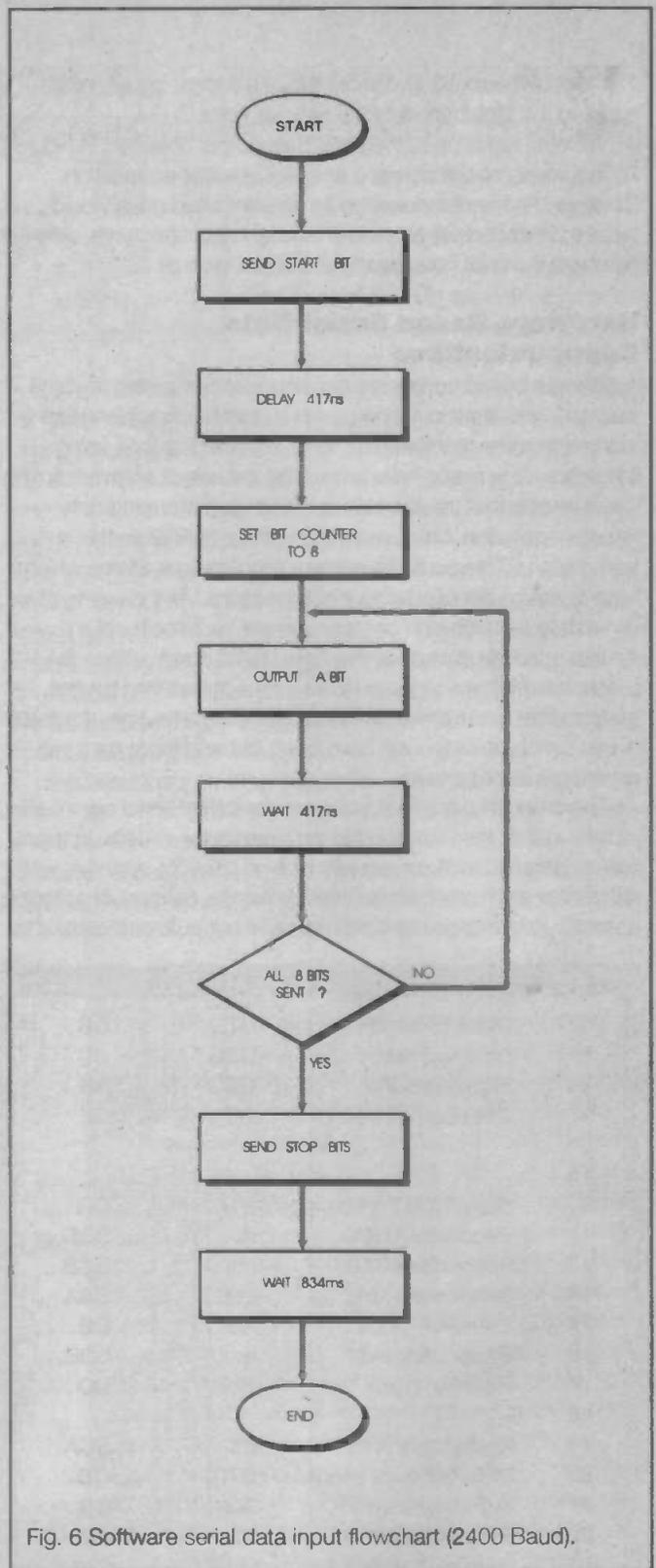


Fig. 6 Software serial data output flowchart (2400 Baud).

determined by a clock pulse input to the TXC and RXC lines of the 8251 (here they are tied together and receive the same clock frequency, but it is perfectly feasible to have a system with different transmit and receive baud rates).

The USART transmit/receive clock input can be derived from a special purpose external clock generator, but it is far more usual to derive it from the system clock, which has been divided down. In this example the system has a clock rate of 7.32728MHz, which is divided by 12 using a 7492 to give an input to TXC and RXC of 614.4kHz. This is then divided internally by 64, by the 8251, to give a baud rate of 9600. The derivation of the serial clock from the system clock accounts for some of the rather strange system clock frequencies which are employed in some systems.

Making Your Own Cables

If there is one thing that is guaranteed to cause computer users considerable frustration, it is the question of cables between the processor and various peripherals, and between two or more computers.

It looks so easy. The average PC comes with one or more serial ports and one or more parallel ports, with peripherals having either a serial or a parallel port, or in some cases both. It should be just a matter of directly connecting them together, but in practice this is all too often not the case. You connect them together, but it does not work!

The problem is most acute with serial cables, since there is little standardisation. This means that finding the correct commercially made cable can be quite difficult and the best solution is to make your own.

Parallel Cables

In some situations, it may be necessary to make your own parallel cables. Although these are readily available from commercial sources, it is rare to find one that is longer than about 20ft, so if you want something a bit longer, you will have to make it yourself.

Officially, parallel cables can be up to about 50ft long. However, if the cable is shielded properly and carefully grounded then, assuming the interfaces at either end of the cable are properly designed, it should be possible to use cables of up to 100ft.

In fact, any parallel cable more than about 10ft long should be properly shielded and grounded, otherwise you run the risk of spurious signals being picked up and data corrupted. The diagram in Figure 1 shows the standard cable interconnection between a standard male D type 25 pin PC parallel port connector and a standard 36 pin Centronics printer connector.

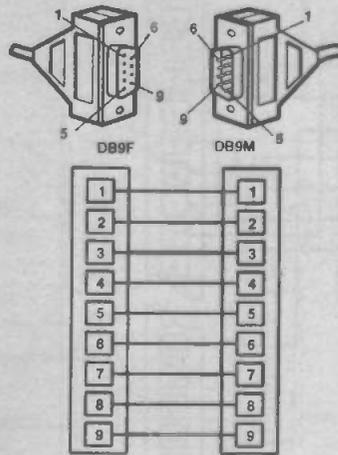
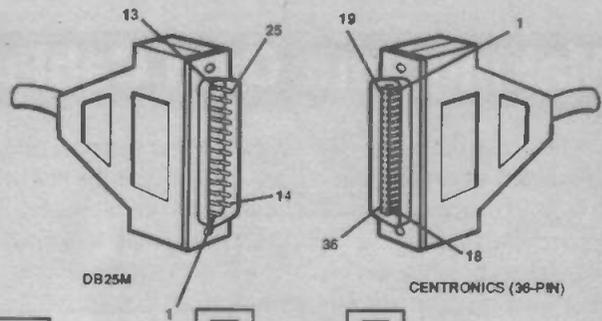


Fig. 2a Serial cable connections.

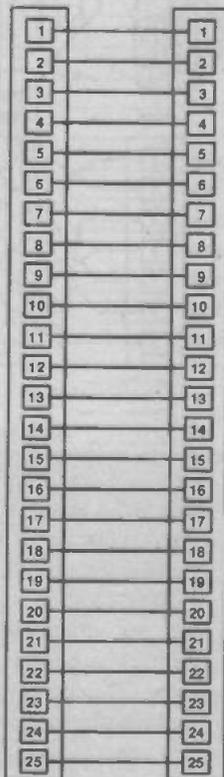
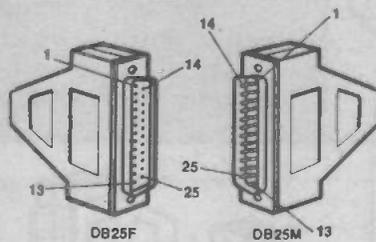


Fig. 2b

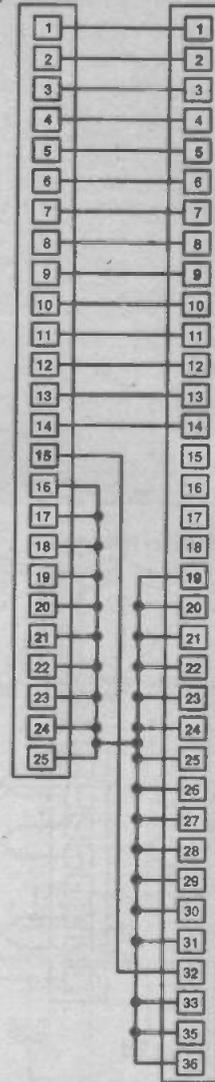


Fig. 1 Standard P.C. to Centronics parallel printer cable.

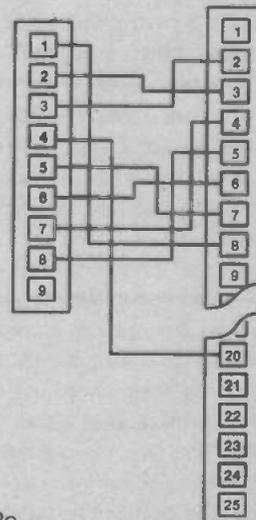


Fig. 2c

Making Your Own Cables

In this diagram note how all the ground line pins are connected together. This is most important if the cable is to work properly and unfortunately not seen on many commercial cables. Depending on the printer, this may not matter, but in some cases it will prevent the printer from working properly. For proper functioning over longer cable lengths, one should ensure that both the PC and the peripheral device have their cases connected to the same electrical ground (always a good practice) and that the shielding on the cable is connected to the PC's case.

Serial Cables

Serial cables driven by a standard RS232 port can, of course, be much longer than parallel ones, according to the specifications up to about 500ft, but in practice with a properly constructed cable, up to about 1200ft. This long cable length is one reason why it is difficult to find the appropriate commercial serial cables. The other reason is a lack of standardisation.

Lack of standardisation is a real problem, some systems have 9 pin connectors, some have 25 pin connectors, so some cables will have 25 pin connectors on either end, some 9 pin on either end and some 25 pin on one end and 9 pin on the other. Some cables have the lines straight through, connecting pin 1 to pin 1, pin 2 to pin 2 and so on. Other serial cables have the wires crossed over. Not to mention the fact that some systems will only use two or three of the connecting wires, whereas others might require ten or more for special purpose signals (see Box 1 for RS232 line specifications).

There are two main classifications of RS232 cable - straight-through and crossover. Broadly speaking, if the cable is linking the computer to a communications device, such as a modem, then a straight-through cable will be used - in other words, one where the transmit line is connected to the same pins at either end of the cable, as is the receive line, etc. However, if the cable is connecting the computer to a peripheral such as a printer, then the transmit line from the computer needs to be connected to the peripheral's receive line and vice versa. The two lines

have to be crossed over.

The diagrams in Figure 2 show the main types of serial cable connections. The two simplest are the 9 pin and 25 pin straight-through cables (Figures 2a and 2b). These have a male connector on one end and a female

connector on the other (some systems will need a male at both ends - without standards life can be very trying). Be warned, however, that just to make life more difficult not all 9 pin connectors have the same connector designations. It is a good idea to always check the documentation first. Slightly more complex is the 9 pin to 25 pin straight-through cable (Figure 2c). Here, which connector is male and which is female depends on the system.

We now come to the crossover cables which are used to transfer data between two computers or between a computer and a peripheral other than a modem. These are sometimes known as null-modem cables. The standard crossover cable (Figure 2d)

has a 25 pin female D type connector at both ends. We can also have a crossover cable between a 9 and 25 pin connector (Figure 2e). Finally, there is the minimalist three

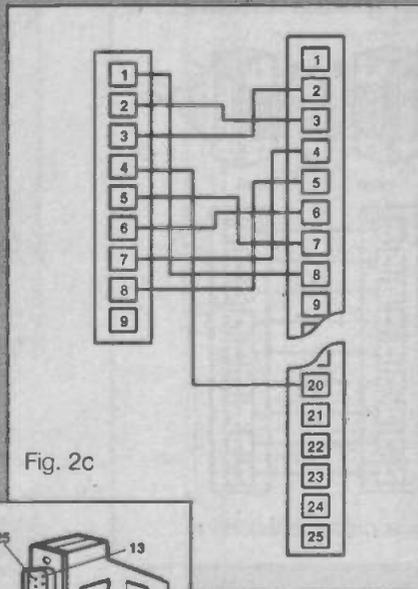


Fig. 2c

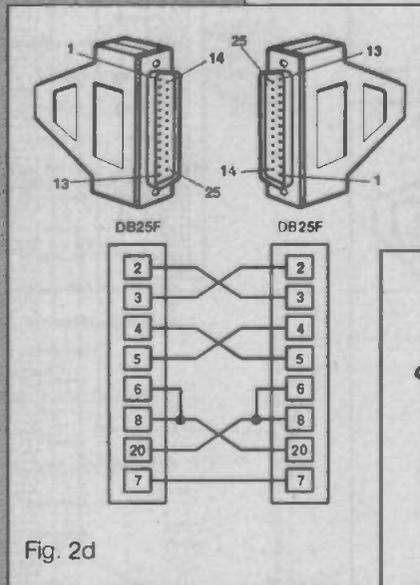


Fig. 2d

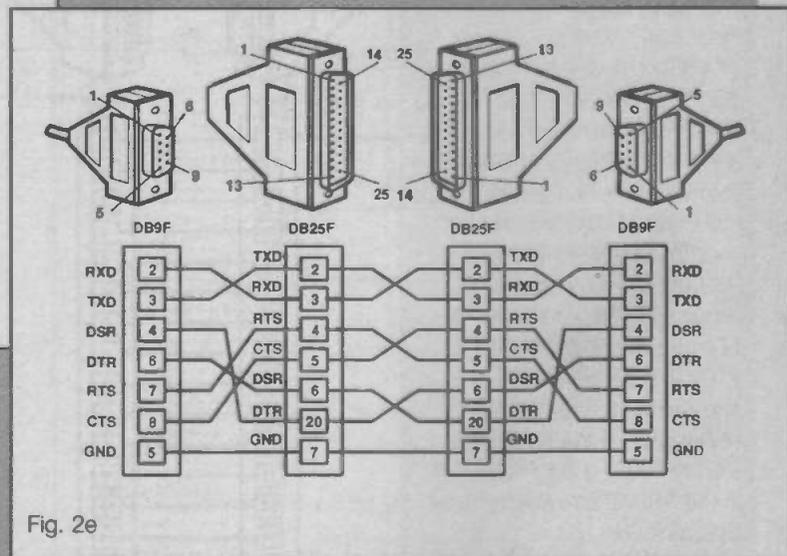


Fig. 2e

wire serial system, which makes no use of any handshaking lines and relies exclusively on software handshaking (Figure 2f).

(Note: for PC users, DOS 5 and 6 include a utility called Interlink, which allows data to be transferred between two computers connected via a null modem cable on their serial I/O ports. This utility allows one computer to read the files or run programs on the other computer. It is a very useful way of transferring data between systems.)

Practical Aspects of Making Cables

It has to be said that cable making is a rather fiddly

Making Your Own Cables

process, but if you are reasonably good at soldering, not very difficult. The most important thing to remember when choosing the cable is that it should be clearly colour coded, with all the wires easily distinguishable from each other. Unfortunately, on many cables it can be difficult to tell some colours apart.

The chosen cable should have enough cores for the application and, in the case of serial cables, probably a few to spare, since different applications might require extra


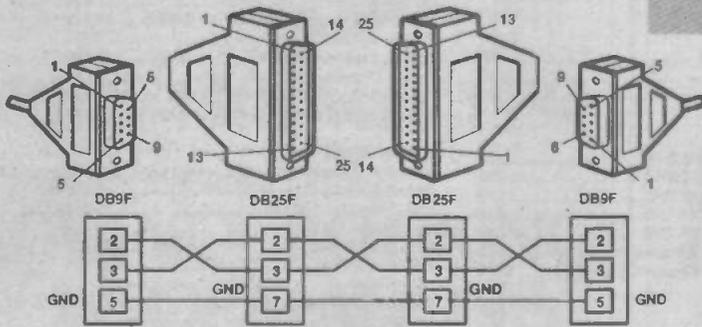
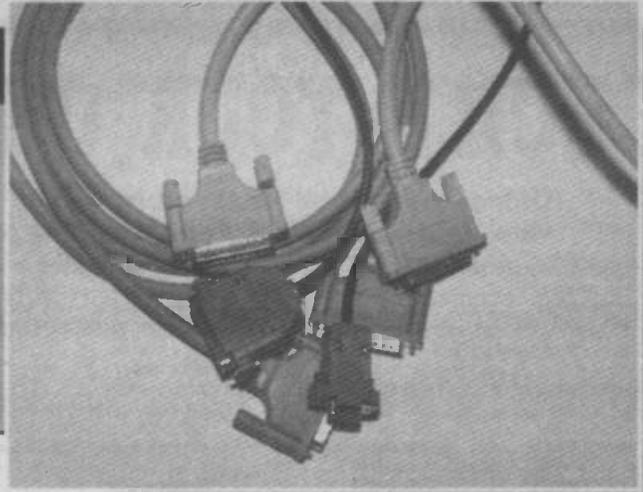


Fig. 2f

repeatedly or strained. Neither is ribbon cable a good choice, since it is easily damaged. In the long run, it is worth paying more for good quality cable, preferably screened.

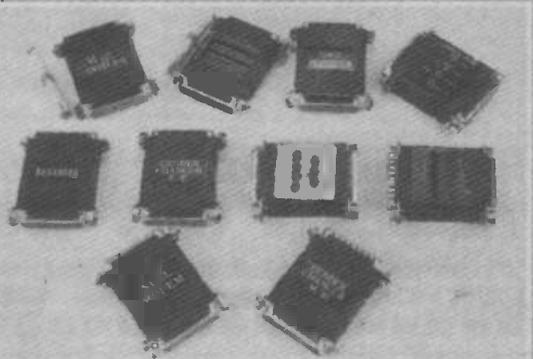lines and it is easier to modify an existing cable than make a new one. Although telephone cable is cheap, it is not a good choice for minimalist connections, since it uses solid instead of stranded wire and is thus liable to break if flexed



You will notice on the circuit diagram in Figure 8 that the serial input and output from the 8251 are fed into a MAX232 chip, before being available as a standard RS232 serial I/O port. The MAX232 is a special RS232 receiver/transmitter circuit which converts the 5V TTL output of the 8251 into the $\pm 12V$ RS232 standard voltages, without any need for special power supply lines - see Box 1 for a full description of the RS232 serial communications standard.

Last Word

This look at parallel and serial data communications techniques ends this series of articles, which has examined some of the fundamentals of microprocessor design. I hope that it has persuaded readers that building microprocessor based systems is not that difficult and, with the low price of MPU chips, they offer an ideal way of implementing some interesting and sophisticated applications.

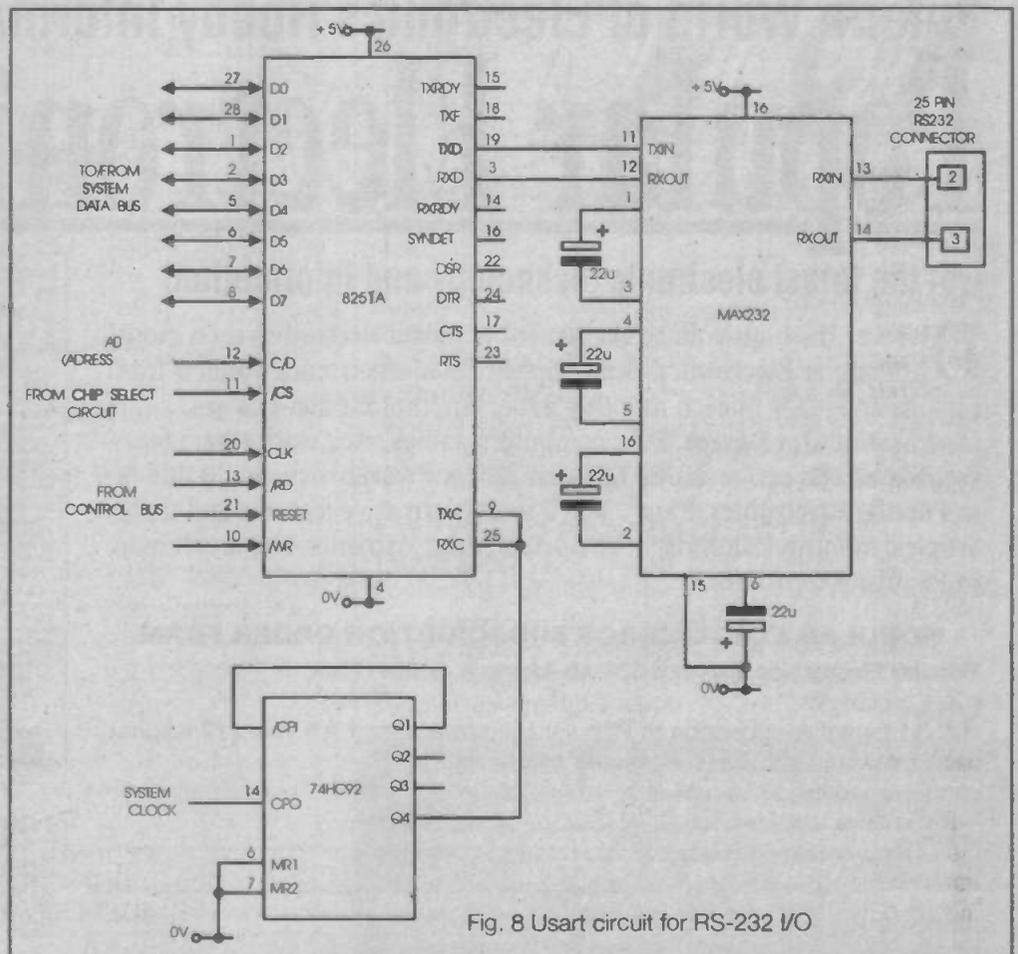


Fig. 8 Usart circuit for RS-232 I/O

BUILD YOUR OWN PC

Using our low cost component parts or we can assemble for you for only £25



386 MOTHERBOARDS	
386SX-33MHz	£72
386DX-40MHz	128k Cache £99

486 MOTHERBOARDS With VESA Local Bus	
2 Slots & Pentium P24T Socket.	
486SX-25MHz	256k Cache £159
486DX-33MHz	256k Cache £279
486DX-40MHz	256k Cache £299
486DX2-50MHz	256k Cache £290
486DX-50MHz	256k Cache £369
486DX2-66MHz	256k Cache £399
486DX-33MHz EISA	256k Cache £399
486DX-40MHz EISA	256k Cache £420
486DX2-50MHz EISA	256k Cache £425
486DX-50MHz EISA	256k Cache £480
486DX2-66MHz EISA	256k Cache £520

HARD DISK DRIVES	
130MB	IDE 16ms £150
170MB	IDE 15ms £159
213MB	IDE 15ms £179
250MB	IDE 12ms £189
330MB	IDE 12ms £229
420MB	IDE 12ms £360
540MB	IDE 12ms £430
1GB	SCSI-2 9ms £699
2GB	SCSI-2 10ms £980
Hard Disk Mounting Brackets	

FLOPPY DISK DRIVES	
3 1/4" 1.44Mb Floppy Disk Drive	£33
3 1/4" 1.44Mb Floppy with 5 1/4" Frame	£36
5 1/4" 1.2Mb Floppy Disk Drive	£35

MONITOR	
14" Mono VGA	£89
14" SVGA Colour (Interlaced) (0.28mm)	£175
14" SVGA Colour (Non Interlaced) (0.28mm) ..	£199
17" High Resolution (0.28mm)	£640

MEMORY	
256K x 9 Simm 70ns	£13
1M x 9 Simm 70ns	£36
4M x 9 Simm 70ns	£125

DISPLAY CARDS	
Oak 16-Bit SVGA Card 256k	£25
Oak 16-Bit SVGA Card 512k	£30
Oak 16-Bit SVGA Card 1MB	£49
VESA Local Bus SVGA 1MB	£70
VESA Local Bus SVGA 2MB	£99
VESA Local Bus S3 Windows Accel 1MB	£110
VESA Local Bus S3 Windows Accel 2MB	£140

KEYBOARDS	
102 Key Standard	£22
102 Key Deluxe	£27

ADD-ON CARDS	
I/O Card 2S/1P/1G	£12
IDE Card 2HD/2FD with Cables	£12
IDE I/O Card 2HD/2FD/2S/1P/1G with cables ..	£16
VL-Bus IDE I/O card as above	£29
VL-Bus IDE Caching controller 4HD/2FD	£129
VL-Bus SCSI-2 IDE I/O card	£125
SCSI-2 card with software	£89
Future Domain SCSI with cables	£45
Future Domain SCSI 2S/1P/1G with cables ..	£59
16-bit Ethernet card (NE2100 compatible)	£59

OTHER ITEMS	
Microsoft Compatible Mouse	£12
Deluxe Desktop Case (200W PSU)	£55
Mini Tower Case (200W PSU)	£59
Tower Case (250W PSU)	£89
MS-DOS 6.2	£39
Windows 3.1	£35

CD ROM DRIVES	
Mitsumi CD-ROM Drive with interface card	£129
Panasonic CR-562B Double speed CD-ROM	£165
Toshiba XM3401 D Speed SCSI CD-ROM	£295

Eurocom International Ltd

Telephone (035 388) 325

The Old School, Prickwillow, Ely, Cambridgeshire, CB7 4UN.

Call for free catalogue or send cheque with order. Carriage £12.00 per order. All prices exclude VAT please add at current rate to total order.

Enter a World of Electronics Hobby Information with

Popular Electronics®

Get the latest electronic technology and information!

Discover the high-voltage excitement of hobby electronics each month in Popular Electronics. Build sophisticated electronics projects from circuits and plans in each monthly issue. Whether it's add-ons or modifications for stereos, TV's, computers, radios, etc.; work savers for your home and car; or useful test gear for your workbench, you'll find it in Popular Electronics. Plus... you'll find informative features and theory articles, monthly columns, hobby-oriented departments, and much more in Popular Electronics.

POPULAR ELECTRONICS SUBSCRIPTION ORDER FORM

Popular Electronics, P.O. Box 338, Mt. Morris, IL 61054 U.S.A.

YES! I want to subscribe to Popular Electronics for 1 full year (12 issues) for only \$26.45 (U.S. Funds only).

Please print clearly

Name _____

Address _____

City, etc. _____

A GUIDE TO TODAY'S SATELLITE TV

JUNE 1993

Popular Electronics

DESIGN AND INSTALL YOUR OWN SATELLITE-TV SYSTEM

A component-by-component primer on setting up a system, selecting the equipment, and doing your own installation

200 CHANNELS TO CHOOSE FROM

A look at today's satellite-TV technology, and a preview of tomorrow's systems

BUILD A SOLID-STATE BEVERAGE COOLER

Easy-to-build project keeps your favorite beverage at the perfect temperature almost indefinitely

1 NEW FunCams at \$99.95

480000

480000


480000

SPECIAL COLUMNS

—Circuit Circus, Think Tank, Computer Bits, DX Listening, Antique Radio, Amateur Radio, Scanner Scene.

ET11

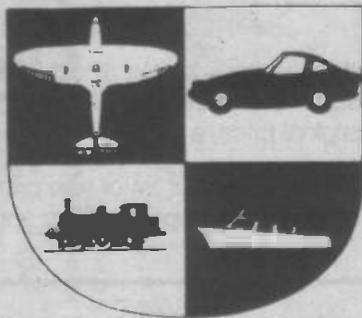SANDOWN PARK MODEL SYMPOSIUM EXHIBITION & DISPLAY



14th & 15th May 1994

Sandown Park Racecourse, Esher, Surrey

ADVANCE BOOKING INFORMATION

ADULTS	£4.50	NO	£
SENIOR CITIZENS	£3.00	NO	£
CHILD	£2.00	NO	£
FAMILY	£12.00	NO	£
(2 adults & up to 4 children)					

GROUPS 10-20 PERSONS

ADULT	£4.00	NO	£
SENIOR CITIZENS	£2.80	NO	£
CHILD	£1.80	NO	£

GROUPS 21 and MORE PERSONS

ADULT	£3.80	NO	£
SENIOR CITIZENS	£2.60	NO	£
CHILD	£1.70	NO	£

(Coach Drivers Free of Charge)

TOTAL ENCLOSED £

Please complete and return the enclosed form with your cheque/P.O. made payable to Argus Specialist Exhibitions, at Argus House, Boundary Way, Hemel Hempstead, Herts. HP2 7ST.

Name

Address

Name of coach operator

Signed Date

CLOSING DATE - 29th APRIL 1994

ORGANISED BY
ARGUS SPECIALIST EXHIBITIONS
IN ASSOCIATION WITH
THE ELMBRIDGE MODEL CLUB


SYSTEM 200 DEVICE PROGRAMMER

SYSTEM: Programs 24, 26, 32 pin EPROMS, EEPROMS, FLASH and Emulators as standard, quickly, reliably and at low cost.

Expandable to cover virtually any programmable part including serial E², PALS, GALS, EPLD's and microcontrollers from all manufacturers.

DESIGN: Not a plug in card but connects to the PC serial or parallel port; it comes complete with powerful yet easy to control software, cable and manual.

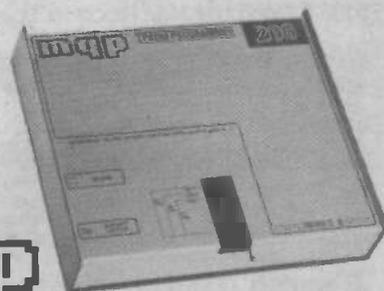SUPPORT: UK design, manufacture and support. Same day dispatch, 12 month warranty. 10 day money back guarantee.



ASK FOR FREE
INFORMATION
PACK



MQP ELECTRONICS Ltd.
Park Road Centre,
Malmesbury, Wiltshire, SN16 0BX UK
TEL. 0666 825146 FAX. 0666 825141

GERMANY 089-74602071
NORWAY 0702 17890
ITALY 02-92-10-3 554
FRANCE (1) 89-30-13-79
SWEDEN 08-735-5360



ALSO FROM ELECTROSPEED UK



DELICIA

THE TRANSMITTER PEOPLE

4 WATT PPO FM BROADCAST (Built) TRANSMITTER: with Low Pass Filter

Modulation 75KHz Wide Band
Range up to 4.2 miles
Supply 10-16 Volts AC/DC
Current 250mA
Audio Input 100mV (ADJ)
Frequency Range 88-108MHz FM
Stability +/- 20KHz
Size W. 70mm, D. 90mm, H. 50mm.
MANY USER CONTROLS Price: £23.50

7 WATT PPO FM BROADCAST (Built) TRANSMITTER: Higher Watt Version of above Transmitter 7 miles range Price: £52.50

KIT: 3 WATT TRANSMITTER 80-108MHZ Coil Tank Controlled up to 3 miles range. Supply 12V dc at 0.5 amps Price: £12.50

ALL PRICES INCLUDE VAT
PLEASE ADD £1 P&P PAYMENT WITH ORDERS TO:

**DELICIA ELECTRONICS,
14 ST. MERYL PARK, GLEN ROAD,
BELFAST, BT11 8FY.**

Tel: (0232) 611995 24 Hour Turn Around
Please send 2 x 1st class stamps for our catalogue



PCB SERVICE

- E9109-5 Nightfighter Main Processor Board.O
- E9110-1 Freeze AlarmE
- E9110-2 Document Saver.....E
- E9110-3 Prototype DesignerJ
- E9110-4 Nightfighter - Sound to light
(2 sided).....L
- E9110-6 Nightfighter - Cyclic Crossfade
(2 sided).....M
- E9110-7 Nightfighter - Strobe Board
(2 sided).....J
- E9111-1 Digital Code LockL
- E9111-2 Switched Mode Power Supply.....E
- E9111-5 Nightfighter - Bass Beat Trigger
(2 sided).....L
- E9111-6 Nightfighter - Sequence Select
(2 sided).....H
- E9111-8 Nightfighter - Output Switch
(2 sided).....M
- E9112-4 Nightfighter Connector BoardF
- E9112-5 Nightfighter Sensor Switch PSUK
- E9201-1 Laboratory Power SupplyF
- E9201-2 Test Card Generator BoardM
- E9201-3 LED Star (2 sided).....L

Most readers will have noticed that we have not been offering a PCB service for the last couple of months. I wish to reassure readers that this is not a permanent situation and is due to a change in PCB suppliers. In the very near future we shall be resuming the service and will be able to offer all PCBs, including those for the last few months' issues of ETI. I would like to apologise for this delay.

In the mean time we are clearing our back stocks of old PCBs, some of which go back to projects run four or five years ago. We are offering these at a bargain price of 2/3 of the original price, a bargain for project builders!

This month we are running the first half of our list of sale price PCBs. Don't miss out, because this is a never to be repeated offer and once sold out, we will not be restocking!

Telephone your order on (0442) 66551 Access or Visa

- E9201-4 Enlarger Timer Main PCB
(2 sided)N
- E9201-5 Enlarger Time Selector Board
(2 sided)K
- E9201-6 Enlarger Timer Switch PCB.....E
- E9203-1 MIDI Switcher Main BoardL
- E9203-2 MIDI Switcher Power SupplyE
- E9203-3 Sine Wave Generator
(surface mount).....F
- E9204-1 Auto Car Lights.....F
- E9205-1 Bat DetectorE
- E9205-2 Pond Controller.....F
- E9206-FC Stereo amplifier.....G
- E9206-2 Xenon flash trigger Main BoardJ
- E9206-3 Xenon flash trigger Flash BoardF
- E9206-4 Scanner for audio generatorD
- E9207-1 Improved Rear Bike Lamp.....D
- E9110-4 Nightfighter - Sound to light
(2 sided).....L
- E9209-2 Alarm protectorC
- E9209-3 Temperature controllerM
- E9209-FC 45W Hybrid power amp.....F
- E2910-2 Rapid Fuse CheckerE
- E9210-3 Heartbeat/Audio Listener.....E
- E9210-FC Wizards Hat.....E
- E9211-1 Electronic DieE
- E9211-FC Car AlarmF
- E9212-1 Digital Circuit Tester.....F
- E9212-2 Communications Link by RS232.L
- E9212-FC Mains Inverter.....E
- E9301-2 Fading FestooneryG
- E9301-FC Infra Red ReceiverF
- E9302-3 Puddle Tec.....E
- E9302-FC Infra Red Transmitter.....E
- E9303-2 IC TesterE
- E9303-3 Disco Amiga
(motor driver board)H
- E9303-4 Direct Conversion Receiver
(2 Sided)N
- E9303-FC LED StoboscopeF
- E9304-1 Solo Mic Pre-AmplifierF
- E9304-3 The Keepsafe AlarmF
- E9304-4 Proving Unit.....E
- E9304-6 Infra Guide TransmitterF
- E9304-FC (AutoMate) Peak Program Meter.F
- E9305-4 Vibration DetectorD
- E9305-FC The Fuzztone.....E
- E9306-1 Graphic EqualiserF
- E9306-2 Super Spooker.....H
- E9306-3 Middle & Side Stereo CodingD
- E9306-FC The Chaperon.....F
- E9307-2 Mind TrainerF
- E9307-FC Microwave MonitorF
- E9308-1 Window Monitor (4 Boards).....K
- E9309-1 RF Signal GeneratorF
- E9309-2 MIDI Analyser CPU BoardK
- E9309-3 MIDI Analyser Display BoardJ
- E9309-4 MetronomeG
- E9310-1 Hot Wire Cutter.....F
- E9310-2 Electronic PictureH
- E9310-5 Home Minder (2 Boards).....N
- E9310-FC Continuity TesterD
- E9311-1 Car AlarmG
- E9311-2 MIDI Change Pedal
(double sided)H
- E9311-4 PSU MonitorN
- E9311-FC RF HoundD
- E9312-1 Car Alarm.....D
- E9312-2 NiCd Battery ChargerF
- E9312-4 Video StabiliserG

ETI PCB Service, Reader Services, Argus House Boundary Way, Hemel Hempstead, Herts HP2 7ST

Please Supply:

Quantity	Ref No.	Price Code	Price	Total Price
	E		£	£
	E		£	£
	E		£	£
			Post & Packing	£ 0.75
			Total Enclosed	£

Please send my PCBs to:

Name


Address

Postcode

CHEQUES SHOULD BE MADE PAYABLE TO ASP

SALE PRICES

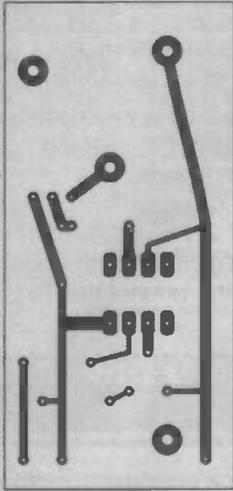- G.....£.60
- D.....£0.83
- E.....£1.08
- F.....£1.33
- G.....£1.59
- H.....£1.83
- J.....£2.21
- K.....£2.40
- L.....£2.94
- M.....£3.54
- N.....£4.37
- O.....£5.28




Brake Light Monitor

OOPS

Figure 8 of John Linsley Hood's article 'Power Supplies for Electronic Equipment' (page 24, April 1994) is incorrect. Please amend the values of R5 and R6 to 4k7, and delete C2 (2u2f) entirely. Also, PCB foil for Raymond Haigh's 'Radio Revisited' (page 21, March 1994) has a small error. Break the track to pin 17 of IC1 and use a wire link to connect pin 16 of IC1 to -9V plane.

Digital Shutter
Timer

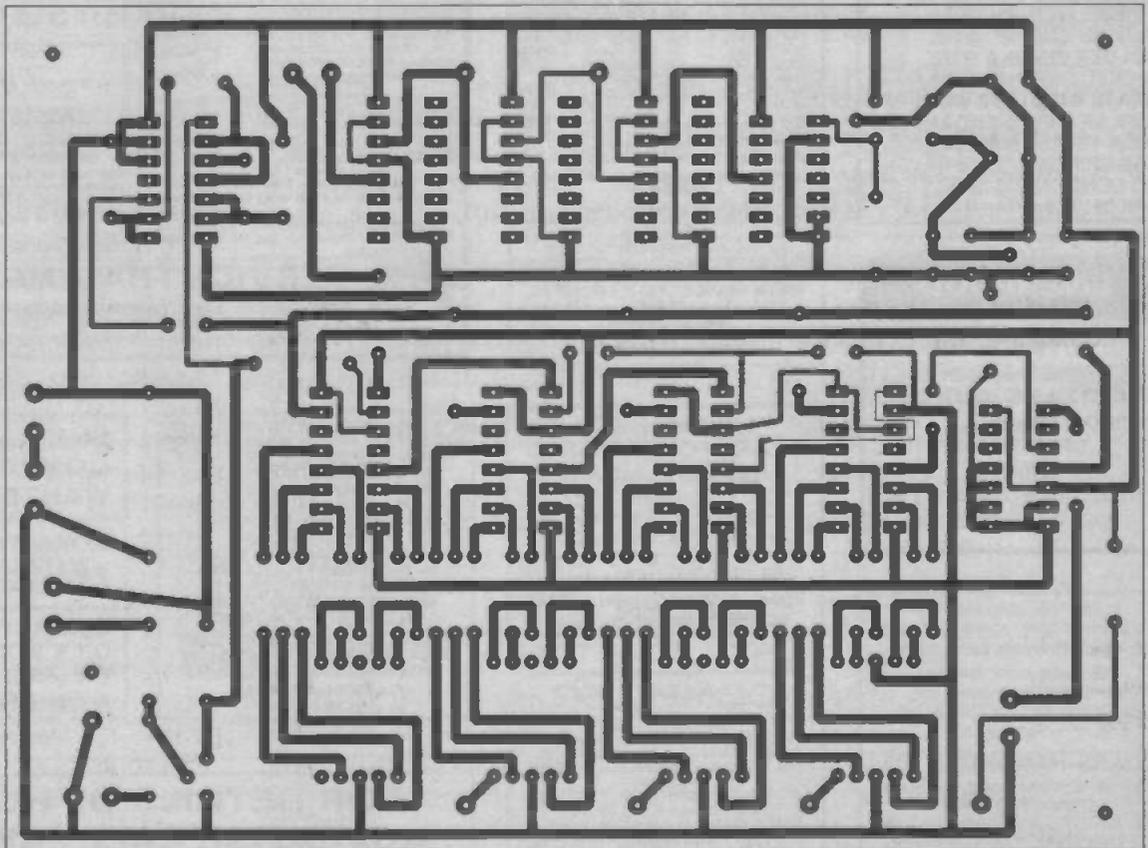

ETI Classified



James Gale
0442 66551

Send your requirements to:
ETI Classified Department, ASP, Argus House,
Boundary Way, Hemel Hempstead, HP2 7ST
Lineage: 65p per word (+ VAT) (minimum 15 words)
Semi display: (minimum 2.5cms)
£8.70 + VAT per single column centimetre



Ring for information on series bookings/discounts.
All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

FOR SALE

COOKE INTERNATIONAL

SUPPLIER OF QUALITY USED TEST INSTRUMENTS

ANALYSERS, BRIDGES, CALIBRATORS, VOLTMETERS,
GENERATORS, OSCILLOSCOPES, POWER METERS, ETC
ALWAYS AVAILABLE

ORIGINAL SERVICE MANUALS FOR SALE
COPY SERVICE ALSO AVAILABLE

EXPORT, TRADE AND U.K. ENQUIRIES WELCOME
SEND LARGE S.A.E. FOR LISTS OF EQUIPMENT AND MANUALS
ALL PRICES EXCLUDE VAT AND CARRIAGE
DISCOUNT FOR BULK ORDERS SHIPING ARRANGED

OPEN MONDAY TO FRIDAY 9AM - 5PM
COOKE INTERNATIONAL
ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham, Bognor Regis,
West Sussex, PO22 0EB Tel (+44) 0243 545111/2 Fax (+44) 0243 542457

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V AC 50/60
OUTPUT 0-260V

	Price	P&P
0.5KVA 2.5 amp max	£31.90	£8.00
	£44.53 inc VAT	
1KVA 5 amp max	£41.15	£7.00
	£56.58 inc VAT	
2KVA 10 amp max	£59.40	£8.50
	£79.78 inc VAT	
3KVA 15 amp max	£78.65	£8.50
	£102.40 inc VAT	
5KVA 25 amp max	£139.15	

(Plus Carriage)

Buy direct from the Importers. Cheapest prices in the country

COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO (110-240V Auto transfer either cased with American socket and mains lead or open frame type. Available for immediate delivery.

WIDE RANGE OF XENON FLASH TUBES

Write/Phone your enquiries

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4H 40 watt	£12.00 (callers only)	£14.10 inc VAT
2H 20 watt	£7.44 + £1.25 p&p	£10.21 inc VAT
12in 8 watt	£4.80 + 75p p&p	£6.52 inc VAT
9in 6 watt	£3.98 + 50p p&p	£5.24 inc VAT
6in 4 watt	£3.98 + 50p p&p	£5.24 inc VAT

230V AC BALLAST KIT
For either 6in, 9in or 12in tubes £8.05 + £1.40 p&p (£9.75 inc)

400 WATT UV LAMP £42.89 inc VAT

160 WATT SELF BALLASTED BLACK LIGHT MERCURY BULB Available with BC or ES fitting, price inc VAT & p&p and VAT £26.55

12V D.C. BILGE PUMPS
500 GPH 15ft head 3 amp £19.98
1750 GPH 15ft head 5 amp £34.95
Also now available 24V D.C. 1750 GPH 15ft head 5 amp £35.55. All designed to be used submerged. PRICES INCLUDE P&P & VAT

EPROM ERASURE KIT
Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Argon Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £18.00 + £2.00 p&p (£19.98 inc VAT)

SUPER HY-LIGHT STROBE KIT
Designed for Disco, Theatrical use etc. Approx 18 joules. Adjustable speed £50.00 + £3.00 p&p (£52.28 inc VAT)

Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT). SAE for further details including Hy-Light and industrial Strobe Kits.

"BOFFINS SPECIAL" - UNIQUE OFFER

Surplus Precision Medical Unit, internally in excellent condition. Designed primarily to eject a precise controllable amount of fluid from a medical syringe (later not supplied). Contains the following removable components: Dual Micro Processor Boards and EPROMS Escap Precision 12V DC Motor with 300:1 Gear Box and optical encoder coupled to a precision threaded drive mechanism. Mains supply with 6 x 1.5V Ni-Cad A.A. cells back-up. L.C.D. Digital read-out 17mm high with legends. Audible warning.

These are sold for the dismantling of the exceptional quality components. Request no Circuits available. Ridiculously low price: £18.00 + £4.00 p&p (£23.50 inc VAT)

12V D.C. GEARED MOTOR
12V D.C. Reversible precision-Built Motor Output speeds no load approx: 12V-26 rpm; 9V-20 rpm; 6V-12 rpm. Will work at lower voltages and still retain a reasonable torque. Ideal for robotics etc. Size: L 40mm W 29mm H 39mm Shaft: 3mm dia x 10mm long. Price: £8.00 + 50p p&p (£10.00 inc VAT)

TO RIN CENTRIFUGAL BLOWER
230V AC, 2.800 RPM, 0.9 amp, 130mm diameter, impeller outer 63 x 37mm, overall size 195 x 160 x 150mm. long. Price £17.50 + £2.50 p&p (£23.50 inc VAT)

SOLID STATE RELAY
7 amp @ 240V, A.C. when mounted on suitable Heat-sink. Can be driven from T.T.L. or Computer output between 3-10V D.C. Size: 24mm x 17mm x 15mm High. Fixing centres 30mm (TO-3). Price: £3.00 + 40p p&p (£4.00 inc VAT)

GEARED MOTORS
71 RPM 200 inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price inc VAT & p&p £23.80.

SOLID STATE EHT UNIT
Input 230/240V AC, Output approx 16kV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec, 30 sec etc continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (£12.81 inc VAT) NMS

SAVE POUNDS!!!
Build your own forged bank note detector. Can detect counterfeiters amongst a quantity of notes. Complete kit of parts less case 240V U.L. including 5" uv black light tube, starter and holder, a pair of 1" pin tube holders. Total price including p&p & VAT only £13.99

WASHING MACHINE WATER PUMP
Brand new 240V AC, fan cooled. Can be used for a variety of purposes. Inlet 1 1/2", in. outer 1 in. dia. Price includes p&p & VAT £11.20 each or 2 for £20.50 inclusive

MICROSWITCH
Pye 15 amp changeover lever microswitch, type S171 Brand new price 5 for £7.05 inc VAT & p&p

SWC SCIENTIFIC WIRE COMPANY

ENAMELLED COPPER WIRE
TINNED WIRE SILVER
PLATED COPPER WIRE
SOLDER EUREKA WIRE
NICKEL CHROME WIRE.
BRASS WIRE LI TZ WIRE
BIFILAR WIRE MANGANIN
WIRE TEFZEL WIRE NICKEL
SAE BRINGS LIST 18 RAVEN
RD LONDON E18 1HW
FAX 081 559 1114

!!!! ON OFFER THIS MONTH !!!!

Red Super Led 5mm	15p	Crystal	
IR Receiver	20p	Earphone	65p
0.1uF X rated	65p	Neon Bulb	
0.1 Pol	5p	250AC	15p
33uF 16v RAD	10p	BD332 PNP Dart	40p
47uF 35v RAD	10p	BC639 100V 1A	30p
4.7uF 16v RAD	10p	LM337 VREG	45p
2.2uF Non Pol	30p	LM7924 VREG	45p
250uF 16v RAD	10p	2718 Eprom	£1.00
2700pF 16v Tol	10p	2732 Eprom	£1.65
Contact Cleaner	£1.25	Contact	
Flux-Off	£1.25	Restorer	£1.25
2pl-26pF	65p	2pl-10pl Trim	40p
1N4001	6p	Tilt Switch	£1.00
47uF 35v DC	45p	4Way Tilt SW	£2.95
74AC75	30p	5 Watt 300 OHM	10p
Crystal 45MHz	40p	200uF 300V DC	85p

STRIP OF ASSORTED COMPONENTS 1M LENGTH £1.

LE33 9FF

WIDE RANGE OF ELECTRONIC COMPONENTS ALWAYS IN STOCK RING FOR DETAILS
- FM TRANSMITTERS ALSO IN STOCK -

FIELD ELECTRIC LTD

TEST & MEASUREMENT EQUIPMENT
IBM COMPATIBLE COMPUTERS:
POWER SUPPLIES, MONITORS:
AUDIO EQUIPMENT: DISK DRIVES:
MOTHERBOARDS: TELEPHONE EQUIPMENT: PLUGS & CONNECTORS: PRINTERS: WE ALSO BUY EQUIPMENT PLEASE RING.
MAIL ORDER SERVICE PAY BY CHEQUE: PO ACCESS OR VISA.
CALLERS BY APPOINTMENT

FIELD ELECTRIC LTD., UNIT 2 MARY MEAD WORKSHOPS, WILLOWS LINK STEVENAGE HERTS SG2 8AB
0438 353781 ; 0836 640328 ; Fax 0438 359397

LIVERPOOL

PROGRESSIVE RADIO

87/93 Dale Street
Tel: 051 236 0982 051 236 0154

47 Whitechapel
Tel: 051 236 5489
Liverpool 2

THE ELECTRONICS SPECIALISTS'
Open: Tues-Sat 9.30-5.30

ELEY ELECTRONIC LTD

100-104 BEATRICE ROAD, LEICESTER, LE33 9FF
TEL: 0533 515944
PAY BY: VISA/ACCESS
OPEN 10-6 MON-SAT

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB
FAX 081 995 0549 081-995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10

TURN YOUR SURPLUS TRANSISTORS, ICS ETC INTO CASH immediate settlement.
We also welcome the opportunity to quote for complete factory clearance.
Contact:
COLES-HARDING & CO.
Unit 58, Queens Road, Wisbech, Cambs PE13 7PQ
BUYERS OF SURPLUS INVENTORY ESTABLISHED OVER 15 YEARS
Tel: 0945 584188
Fax: 0945 475216

NEWMARKET TRANSFORMERS LTD

Mail Order Transformer Specialists.
Toroidal and Laminated Transformers, 3VA to 1kVA.
Fast delivery. Competitive prices. Quality guaranteed.
Phone: Michael Dornan on 0638 662989 for Immediate Quote

FIELD ELECTRIC LTD

TEST & MEASUREMENT EQUIPMENT
IBM COMPATIBLE COMPUTERS:
POWER SUPPLIES, MONITORS:
AUDIO EQUIPMENT: DISK DRIVES:
MOTHERBOARDS: TELEPHONE EQUIPMENT: PLUGS & CONNECTORS: PRINTERS: WE ALSO BUY EQUIPMENT PLEASE RING.
MAIL ORDER SERVICE PAY BY CHEQUE: PO ACCESS OR VISA.
CALLERS BY APPOINTMENT

FIELD ELECTRIC LTD., UNIT 2 MARY MEAD WORKSHOPS, WILLOWS LINK STEVENAGE HERTS SG2 8AB
0438 353781 ; 0836 640328 ; Fax 0438 359397

SURPLUS COMPONENTS WANTED

☆ COMPLETE CLEARANCE
☆ BEST PRICES PAID
☆ PCB BOARDS POPULATED

CONTACT
D.T.S. SERVICES
Tel: (0602) 208955
or Fax: (0602) 484530

COMPELEC

1994 BARGAIN LIST
THE ELECTRONIC ESSENTIAL. MILLIONS OF COMPONENTS AT UNBEATABLE PRICES. FOR A FREE COPY PHONE, FAX OR WRITE (TRADE ONLY)
COMPELEC,
14 CONSTABLE ROAD, ST IVES, HUNTINGDON, CAMBS. PE17 6EQ
0480 300819
WE ALSO PURCHASE ALL TYPES OF ELECTRONIC COMPONENTS, LISTS TO ABOVE ADDRESS

FOR DETAILS OF HOW TO ADVERTISE CALL JAMES ON 0442 66551

Open Forum

A few days ago, I had a phone call from a reader who was complaining that the magazine now had too much emphasis on microprocessors and computing and not enough on traditional electronics. I am always interested to hear what readers have to say and, I was curious to know what he meant by traditional electronics. His response was simply that he considered traditional electronics to consist of circuits built from logic ICs, OP-Amps, transistors, etc.

Traditional electronics uses logic ICs and Op-Amps? Now, I am not that old, but I can remember when the first ICs were produced. If he had said transistors or valves, then I would perhaps have understood what he meant by traditional. In a technology which is developing as rapidly as electronics you cannot sit down and say this is classical traditional technology and everything developed from now on is of dubious worth.

The reason for this tale is to allow me to expound on a key element of editorial philosophy.

This magazine is about electronics, about all forms of electronics devices and about things that are controlled by electronics. Computers are electronic devices, we cannot draw a line between computing and electronics, they are one and the same thing.

In pure cybernetic terms, any digital IC is just a 'black box' which has a specific table of transformations controlling relationships between the inputs and the outputs. A computer is just another cybernetic 'black box' with input, output and a transformation table relating the two.

The only real difference is that a computer is a general purpose circuit, which allows the user to change the transformation table by changing the program. This means that we can use a computer to behave in exactly the same way as any other 'black box', simply by writing the appropriate program. And it matters little whether we are talking about digital input and output or analogue input and output.

Filling a foot square board with dozens of ICs may qualify for the term traditional electronics, but what is the point of designing and building such a board, when it could be replaced by a simple four or five chip microprocessor system programmed to behave in exactly the same way as our board full of ICs.

There has to be a proper balance of course, simple circuits will always be constructed using basic ICs, transistors, and discrete components. But most of the more complex applications are a lot easier to implement using a microprocessor or microcontroller. I, for one, am all for making life easier. Then, of course, there is the added bonus that processor based circuits are a lot easier to modify and update.

A lot of applications will consist of both a microprocessor and a reasonable number of analogue or digital circuits that are connected to it. In these cases we should think of the processor and its software as providing the 'glue' which links all the other pieces together. A 'glue' which allows us to design easily tested modular systems of considerable complexity. Systems which would probably be considered too complex to be built in any other way.

I feel, therefore, that it is only right that a magazine like ETI should reflect the current trends in electronics and cover what my caller referred to as 'traditional electronics', as well as the use of microprocessors and computers. Only by understanding all these elements can we make full use of the technology available to us.

My apologies to readers who think that computing has no place in an electronics magazine, but I think such readers are mistaken and I hope that the kind of projects which we shall be running over the coming months and years will demonstrate why.

This magazine and its readers have to move with the technology and be at the forefront of that technology. Traditional technology is the technology of today, not the technology of yesterday.

Next month...

We continue Jim Spence's project to build an experimenter's computer, with the design for a keyboard and LCD display. For cyclists, there is an electronic speedometer project from Bob Noyes and, on the home front, a passive infra-red alarm from Robert Penfold. We will also be starting a project to build an infra-red data communications system that can be used to link two computers in different buildings, without the need for cables.

Robert Penfold will be beginning an introductory series on MIDI and June also sees the start of series on repairing and upgrading PCs, and on basic electronic circuits, while our main feature article will be looking at circuit simulation software.



EDITORIAL

Editor **Nick Hampshire**
Sub Editor **Jim Bluck**

CREATIVE

Art Editor **Peter Kirby**
Technical Illustration **John Puczynski**
Photography **Manny Cefai**

ADVERTISEMENT SALES

Display Sales
Tony Hill
Advertisement Copy Control
Marie Quilter
Classified Sales
James Gale

MANAGEMENT

Managing Director
Terry Pattison
Circulation & Promotions Manager
Debra Stuppel
Production Manager
Tony Dowdeswell
Group Editor
Stuart Cooke
Group Advertisement Manager
Claire Jenkinson



ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, plans, drawings and programs and all copyright and all other intellectual property rights therein belong to Argus Specialist Publications. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications and reproduction requires the prior written consent of the company ©1990 Argus Specialist Publications. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Subscription rates-UK £23.40 Europe £30.30 Sterling Overseas £31.50 US Dollars Overseas \$52.00

Published by Argus Specialist Publications, Argus House, Boundary Way, Hemel Hempstead HP2 7ST, Telephone (0442) 66561, UK newstrade distribution by SM Distribution Ltd, 6 Leigham Court Road, London SW18 2PG, Telephone 081-867 8111. Overseas and non-newstrade sales by Magazine Sales Department, Argus House, Boundary Way, Hemel Hempstead, HP2 7ST, Telephone (0442) 66561. Subscriptions by Argus Subscription Services, ETI, Queensway House, 2 Queensway, Redhill, Surrey RH1 1QS, Telephone (0737) 768611. US subscriptions by West Owl Worldwide Publications, 4314 West 236th Street, Torrance, CA90505 USA. For Visa/Mastercard orders in USA - Telephone (310) 373 6258 Fax (310) 375 0548. Pacific Time: 9am-9pm Weekdays, 10am-6pm Weekends. Typesetting and origination by Ebony, Liskeard, Cornwall. Printed by Wiltshire Ltd, Bristol.



Argus House, Boundary Way,
Hemel Hempstead HP2 7ST
Telephone (0442) 66551
Fax (0442) 66998

SURVEILLANCE PROFESSIONAL QUALITY KITS

No. 1 for Kits

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics SUMA DESIGNS has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

Genuine SUMA kits available only direct from Suma Designs. Beware inferior imitations!

UTX Ultra-miniature Room Transmitter

Smallest room transmitter kit in the world! Incredible 10mm x 20mm including mic. 3-12V operation. 500m range.....£16.45

MTX Micro-miniature Room Transmitter

Best-selling micro-miniature Room Transmitter
Just 17mm x 17mm including mic. 3-12V operation. 1000m range.....£13.45

STX High-performance Room Transmitter

Hi performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm including mic. 6-12V operation, 1500m range.....£15.45

VT500 High-power Room Transmitter

Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm. 9-12V operation. 3000m range.....£16.45

VXT Voice Activated Transmitter

Triggers only when sounds are detected. Very low standby current. Variable sensitivity and delay with LED indicator. Size 20mm x 67mm. 9V operation. 1000m range..£19.45

HVX400 Mains Powered Room Transmitter

Connects directly to 240V AC supply for long-term monitoring. Size 30mm x 35mm. 500m range.....£19.45

SCRX Subcarrier Scrambled Room Transmitter

Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to the receiver. Size 20mm x 67mm. 9V operation. 1000m range.....£22.95

SCLX Subcarrier Telephone Transmitter

Connects to telephone line anywhere, requires no batteries. Output scrambled so requires-SCDM connected to receiver. Size 32mm x 37mm. 1000m range.....£23.95

SCDM Subcarrier Decoder Unit for SCRX

Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm. 9-12V operation.....£22.95

ATR2 Micro Size Telephone Recording Interface

Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line.....£13.45

★★★ Specials ★★★

DLTX/DLRX Radio Control Switch

Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output, momentary or alternate, 8-way dial switches on both boards set your own unique security code. TX size 45mm x 45mm. RX size 35mm x 90mm. Both 9V operation. Range up to 200m.

Complete System (2 kits).....£50.95
Individual Transmitter DLTX.....£19.95
Individual Receiver DLRX.....£37.95

MBX-1 Hi-Fi Micro Broadcaster

Not technically a surveillance device but a great idea! Connects to the headphone output of your Hi-Fi, tape or CD and transmits Hi-Fi quality to a nearby radio. Listen to your favourite music anywhere around the house, garden, in the bath or in the garage and you don't have to put up with the DJ's choice and boring waffle. Size 27mm x 60mm. 9V operation. 250m range.....£20.95

UTLX Ultra-miniature Telephone Transmitter

Smallest telephone transmitter kit available. Incredible size of 10mm x 20mm! Connects to line (anywhere) and switches on and off with phone use. All conversation transmitted. Powered from line. 500m range.....£15.95

TLX700 Micro-miniature Telephone Transmitter

Best-selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 1000m range.....£13.45

STLX High-performance Telephone Transmitter

High performance transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm. 1500m range.....£16.45

TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output giving range up to 3000m. Size 25mm x 63mm. 9V operation.....£22.95

CD400 Pocket Bug Detector/Locator

LED and piezo bleeper pulse slowly, rate of pulse and pitch of tone increase as you approach signal. Gain control allows pinpointing of source. Size 45mm x 54mm. 9V operation.....£30.95

CD600 Professional Bug Detector/Locator

Multicolour readout of signal strength with variable rate bleeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDID CONFORM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm. 9V operation.....£50.95

QTX180 Crystal Controlled Room Transmitter

Narrow band FM transmitter for the ultimate in privacy. Operates on 180 MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm. 9V operation. 1000m range.....£40.95

QLX180 Crystal Controlled Telephone Transmitter

As per QTX180 but connects to telephone line to monitor both sides of conversations. 20mm x 67mm. 9V operation. 1000m range.....£40.95

QSX180 Line Powered Crystal Controlled Phone Transmitter

As per QLX180 but draws power requirements from line. No batteries required. Size 32mm x 37mm. Range 500m.....£35.95

QRX180 Crystal Controlled FM Receiver

For monitoring any of the 'Q' range transmitters. High sensitivity unit. All RF section supplied as a pre-built and aligned module ready to connect on board so no difficulty setting up. Outpt to headphones. 60mm x 75mm. 9V operation.....£60.95

A build-up service is available on all our kits if required.

UK customers please send cheques, POs or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft and add £5.00 per order for shipment. Credit card orders welcomed on 0827 714476.

OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO FIRST CLASS STAMPS OR OVERSEAS SEND TWO IRCS.

**SUMA
DESIGNS**

DEPT. ETI
THE WORKSHOPS, 95 MAIN ROAD,
BAXTERLEY. NEAR ATHERSTONE,
WARWICKSHIRE CV9 2LE

VISITORS STRICTLY BY APPOINTMENT ONLY



Tel/Fax:
0827 714476

NEW


FULL COLOUR GUIDE TO ELECTRONIC PRODUCTS

Maplin



BS 5750
Part 2 1987

Level B:
Quality Assurance
RS12750

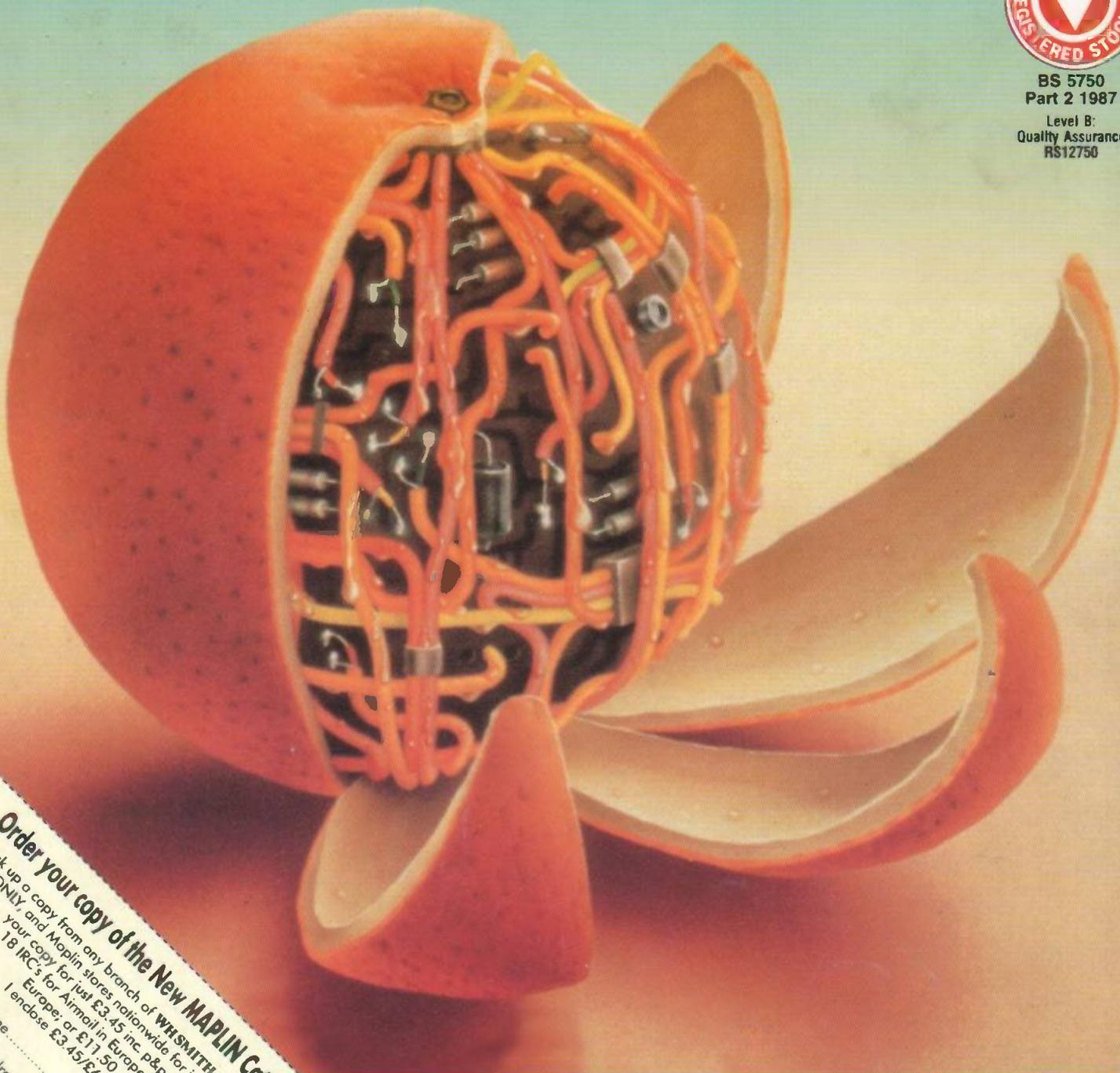

Order your copy of the New MAPLIN Catalogue on sale NOW!
Pick up a copy from any branch of WHSMITH, selected branches of RSMCOLL in Scotland ONLY, and Maplin stores nationwide for just £2.95 or post this coupon now to receive your copy for just £3.45 inc. p&pa. If you live outside the U.K. send £6.80 or 16 IRC's for Airmail in Europe/£5.20 or 13 IRC's for Airmail outside Europe. Europe, or £11.50 or 30 IRC's for Airmail outside Europe. I enclose £3.45/£6.80/£5.20/£11.50 (delete as applicable).

Name.....
Address.....
Post Code.....
Send to Maplin Electronics,
P.O. Box 3, Rayleigh,
Essex, England
SS6 8LR
ET194

Over 700 colour packed pages, with hundreds of brand New Products at Super Low Prices, on sale now, only £2.95.

Available from all branches of WHSMITH, selected branches of RSMCOLL in Scotland ONLY, and Maplin stores nationwide. The Maplin Electronics 1994 Catalogue - UNIQUELY DIFFERENT!
Southern Africa customers please contact Maplin (South Africa) Telephone (024) 51-5124