



ELECTRONICS
TODAY INTERNATIONAL


TOMORROW'S
TECHNOLOGY TODAY

**SUPER
PROJECTS
FOR YOU TO BUILD**



Where on Earth am I?

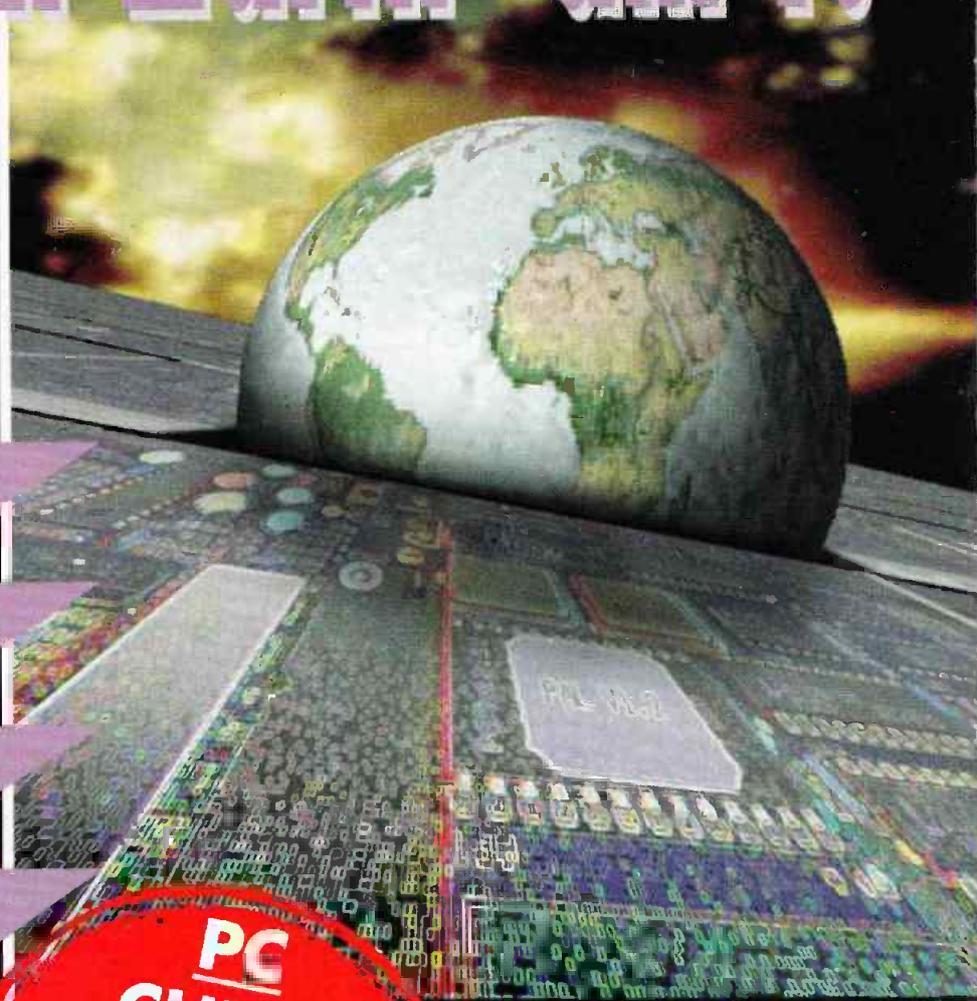**A LOOK AT HOW
GLOBAL
POSITIONING
SYSTEMS CAN PLACE
YOU
WITHIN METRES**



**Microprocessor
Motor Control**

**Build a car lights-on
reminder**

**Turbo speed
Indicator for PC**

**Make a video light
meter**

**Measure minute
changes in the
earth's magnetic
field**

**PC
CLINIC**
PROCESSORS
CO-PROCESSORS
AND CACHE
MEMORY

August 1994 £2.15



9 770142 722054



ARGUS SPECIALIST
asp
PUBLICATIONS


Low cost data acquisition for IBM PCs & compatibles

A unique range of easy to use data acquisition products designed for use with IBM compatible computers. Combined with the software they allow your PC to be used as a host of useful test and measurement instruments, or as an advanced data logger.

Installed in seconds they simply plug into the parallel port (except the ADC-16 which connects to the serial port). They are self-contained, require no power supply and take up no expansion slots.

Each device comes with a comprehensive manual. C, Pascal and Basic drivers are included for users who wish to write their own software. Software supplied on 3.5" disk.

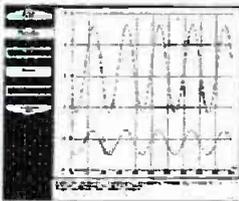PicoScope "Virtual instrument" software package.




Scope, voltmeter, spectrum analyser

Storage oscilloscope with trigger, timebase, rulers and offset functions. Realtime spectrum analysis with min/max frequency and signal averaging. Multiple meters on screen (digital and bargraph).

Printer and file handling support

PicoLog

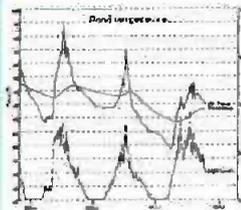

Advanced data logging software package

Collect, store, display and print data from 1 sample per ms to 1 per day. Record average, min/max values or scaled values (linear, equation, table look up). Report types: monitor (with min/max alarms), y-t graphs, x-y graphs, tabulation.

NEW ADC 100 Virtual Instrument Dual Channel 12-bit resolution

The ADC 100 offers both a high sampling rate (100kHz) and a high resolution. It is ideal as a general purpose test instrument either in the lab or in the field. Flexible input ranges ($\pm 200\text{mV}$ to $\pm 20\text{V}$) allows the unit to connect directly to low output sensors such as microphones or to high level signals ($\pm 200\text{V}$ with a x10 scope probe).



NEW from PICO

- Digital Storage Scope
- Spectrum Analyser
- Voltmeter
- Frequency Meter
- Chart Recorder
- Data Logger

ADC 100 with PicoScope £199
PicoScope & PicoLog £209

ADC 10

1 Channel 8-bit

- Lowest cost
- Up to 22kHz sampling
- 0-5V input range

The ADC 10 gives your computer a single channel of analogue input. Simply plug into the parallel port and your ready to go.

ADC 10 with PicoScope £49
PicoScope and PicoLog £59

ADC 11

11 Channel 10-bit

- Digital output
- Up to 18kHz sampling
- 0-2.5V input range

The ADC 11 provides 11 channels of analogue input in a case slightly larger than a matchbox. It is ideal for portable data logging using a "notebook" computer.

ADC 11 with PicoScope £85
PicoScope and PicoLog £95

ADC 12

1 Channel 12-bit

- High resolution
- Up to 17kHz sampling
- 0-5V input range

The ADC 12 is similar to the ADC 10 but offers an improved 12-bit (1 part in 4096) resolution compared to the ADC 10's 8-bit (1 part in 256).

ADC 12 with PicoScope £85
PicoScope and PicoLog £95

ADC 16

8 Channel 16-bit + sign

- Highest resolution
- 220Hz sampling
- 2Hz sampling - 16-bit

The ADC 16 has the highest resolution of the range, it is capable of detecting signal changes as small as $40\mu\text{V}$. Pairs of input channels can be used differentially to reject noise. Connects to serial port.

ADC 16 with PicoLog £115

PicoLog for ADC 10/11/12 £25. Oscilloscope Probes (x1, x10) £10. Carriage UK free. Overseas £6




Pico Technology Ltd., Broadway House, 149-151 St Neots Road, Hardwick, Cambridge. CB3 7QJ.

TEL: 0954-211716 FAX: 0954-211880



PICO TECHNOLOGY

Contents

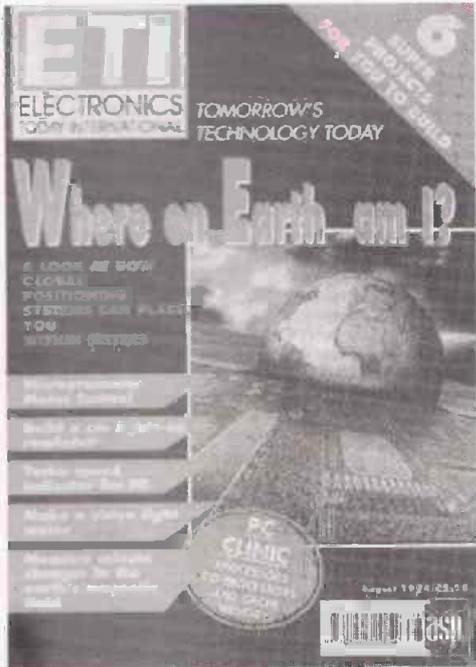

Volume 23 No.7

& Features Projects

Where on Earth Am I? 12

Global Positioning Systems rely on a complex fusion of space technology and electronics to give a position accurate to just a few metres. We look at how such systems work and now that their price has dropped to just a few hundred pounds, how they are being used.

Microprocessor Motor Control 18

Hot on the heels of his FORTH programmable Experimenter's Computer project, Jim Spence shows how to use this processor board to accurately control a number of stepper motors.

Turbo Speed Indicator 24

This little add-on indicator circuit from John Lanigan can be added to any PC and will show which clock rate it is running at.

Bite Alarm 28

Those lazy days fishing will never be the same again, after you construct Bob Noyes' project to sound an alarm whenever a fish has taken the bait.

PC Clinic 35

Part 3 of the series that shows readers how to repair, maintain, upgrade and build circuits for their personal computers. In this issue, we look at the CPU, coprocessors, cache memory and making good use of the BIOS software.

Video Light Meter 44

In this project, Terry Balbirnie shows how to build a small light meter that should help video users to produce better images.

Magnetism and Magnetometers 50

In Part 1 of this two part article, Keith Garwell looks at the design of sensitive instrumentation that can detect minute changes in the Earth's magnetic field.

Car Lights On Reminder 56

Build this cheap and simple project from Len O'Connor and you need never worry about leaving your lights on and running down your car's battery.



An Introduction to MIDI 60

In Part 3 of this series, Robert Penfold continues his introduction to the mysteries of MIDI - the now universally accepted standard for communications between electronic musical instruments.

Regulars

- News and events diary 6
- Balbirnie's Workshop
- Terry Balbirnie divulges some more practical hints and tips for the electronics enthusiast.
- Talkback 65
- Your letters, and ideas, plus club news.
- PCB foils 68
- Open Forum 74



Competition 64

In this issue of ETI we have another great competition for readers to enter. Win a Maplin Blood Pressure Monitor, worth £75.

Subscribe & Save
 Phone the hotline and take advantage of our special offer detailed on page 67

SUBSCRIPTION & BACK ISSUES HOTLINE 0737 768611



**8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF**
Tel: 0203 650702
Fax: 0203 650773
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

OSCILLOSCOPES

Gould 1602 - 2 Channel D.S.O.	£1300
Gould 1604 - 4 Channel D.S.O.	£1750
Gould 1421 - 2 Channel D.S.O.	£375
Gould OS4000, OS4200, OS4020, OS245	from £125
Hewlett Packard 1740A, 1741A, 17744A, 100MHz dual ch	from £350
Hewlett Packard 182C - 100MHz 4 ch	£350
Hewlett Packard 1707A, 1707B - 75MHz 2ch	from £275
Hitachi V.U22 - 40 MHz Dual Channel	£300
Nicolet 3091 - LF D.S.O.	£1100
Philips 3055 - 60 MHz Dual Channel	£550
Tektronix 2201 - 20MHz D.S.O. dual ch	£675
Tektronix 2213 - 60 MHz Dual Channel	£425
Tektronix 2246 100MHz-4 channel	(as new) £995
Tektronix 2215 60MHz dual trace	£450
Tektronix 2235 Dual trace 100MHz (portable)	£800
Tektronix 2335 Dual trace 100MHz (portable)	£750
Tektronix 2225 -50MHz dual ch	£450
Tektronix 465/465B -100MHz dual ch	from £350
Tektronix 475 - 200MHz dual ch	£450
Tektronix 468 -100MHz D.S.O. dual ch	£850
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch	from £300
Tektronix 7704 - 250MHz 4 ch	from £650
Tektronix 7834/7844 - 400MHz 4 ch	from £750
Tektronix 7904 - 500MHz	from £850
Philips 3070 -100MHz 2+ 1 channel + cursors, as new	£900
Philips 3206, 3211, 3212, 3217, 3226, 3240, 3243, 3244, 3261, 3262 (2ch + 4 ch.)	from £125 to £350
Solartron Schlumberger CD1740 - 20MHz 4 ch	£250

Other scopes available too

SPECTRUM ANALYSERS

Ailtech 727 -20GHz	£2200
Advantest TR4131 -10KHz - 3.5GHz	£4500
Hewlett Packard 3580A - 5Hz-50KHz	£1250
Hewlett Packard 8590A - 10KHz - 1.5GHz - (as new)	£4500
Hewlett Packard 182T with 8599A (10MHz - 21GHz)	£3750
Marconi 2370 - 110MHz	£1250
Hewlett Packard 4953 Protocol analyser	£2500
Tektronix 492 - 21GHz	£6000
Tektronix 7L18 with 7603 main frame 1.5 GHz - 18GHz	£3500
Texscan AL51A (4MHZ - 1GHZ)	£1300

MISCELLANEOUS

Anritsu ML93B/ML92B Optical power meter with sensor	£2000
Anritsu ME538C Microwave system analyser (BX + Tx)	£3500
B&K 2511 + 1621 Vibration test set	£2000
B&K 2511 Vibration meter	£1500
B&K 2515 Vibration analyser	£4500
Datron 1061A Autocal digital multimeter (6 1/2 digits)	£850
Daymarc 1735 Transistor tester/sorter (with all jigs)	£5000
Dranetz 305 Phase meter	£250
Dymar 1585 AF Power meter	£175
Dymar 2085 AF Power meter	£200
Farnell RB 1030-35 Electronic load 1Kw	£450
Farnell ANM/B Automatic modulation meter	£150
Farnell 2081 R/F Power meter	POA
Feedback TWG300 Test waveform generator	£200
Fischer Betascope 2040/2060 Coating thickness computer & non destructive coating measurement instrument & many jigs and extras	all for £2000
Fluke 8840A Multimeter (1EEE)	£450
Fluke 515A Portable calibrator	£500
Fluke 8010A Digital multimeter	£125
Fluke 8922A True RMS voltmeter	POA
Fluke 95020 Current shunt	POA
Gay Milano FTMIC/FTM3C - FTM - Fast transient monitor	£250
General Rad 1658 LCR Digibridge	£250
General Rad 1621 Precision capacitance measurement system	POA
Hewlett Packard 180TR Display unit with 8755B swept. amp. an.	£350
Hewlett Packard 3200B VHF oscillator, 10-5000MHz	£175
Hewlett Packard 3400A RMS voltmeter	£150
Hewlett Packard 3406A Broadband sampling voltmeter	£175
Hewlett Packard 3437A System voltmeter	£350
Hewlett Packard 3456A Digital voltmeter	£650
Hewlett Packard 3476 Digital multimeter	£100
Hewlett Packard 3478 Digital voltmeter, 4 wire system, 1EEE	£650
Hewlett Packard 3702B/3705A/3710A/3716A Microwave link analyser	£1500
Hewlett Packard 3730A Down converter (with 3738A or 3737A)	£200
Hewlett Packard 3760/3761 Data gen + error detector	each £300
Hewlett Packard 3762/3763 Data gen + error detector	each £350
Hewlett Packard 3777A Channel selector	£250

Hewlett Packard 3779A Primary multiplex analyser	£800
Hewlett Packard 400E/F AC voltmeter	£150
Hewlett Packard 4204A Oscillator 10Hz-1MHz	£250
Hewlett Packard 435A Power meter (laser sensor)	£350
Hewlett Packard 456A AC current probe	POA
Hewlett Packard 415E SWR meter	£275
Hewlett Packard 4193A Vector impedance meter	£3500
Hewlett Packard 5335A Universal counter with 1EE	£1400
Hewlett Packard 5342A Microwave freq. count. 18GHz	£1400
Hewlett Packard 7402 Recorder with 17401A x 2 plug-ins	£300
Hewlett Packard 8005B Pulse generator	£250
Hewlett Packard 8011A Pulse gen. 0.1Hz-20MHz	£500
Hewlett Packard 8013B Pulse gen. 1Hz-50MHz	£750
Hewlett Packard 8012B Pulse generator	£750
Hewlett Packard 8406A Frequency comb. generator	£500
Hewlett Packard 8443A Tracking gen/counter with 1EEE	£450
Hewlett Packard 8444A Tracking Generator	£750
Hewlett Packard 8445B Automatic presetter	£700
Hewlett Packard 8601A 110MHz Gen/sweeper 110MHz	£350
Hewlett Packard 8620C Sweep oscillator mainframe	£500
Hewlett Packard 8750A Storage normaliser	£400
Hewlett Packard 938A Freq. doubler	£250
Keithley 197 20MHz with 1EEE	£400
Lyons PG73N/PG75/PG2B/PG Pulse generator	from £225
Marconi 2019A 80KHz-1040MHz sig. gen.	£1850
Marconi 2432A 500MHz digital freq. meter	£200
Marconi 2337 Automatic dist. meter	POA
Marconi 2356 20MHz level oscillator	£300
Marconi 2306 Programmable interface	£500
Marconi 2610 True RMS voltmeter	£900
Marconi 2830 Multiplex tester	£1250
Marconi 2831 Channel access switch	£500
Marconi 6920 Power sensor	£400
Philips 5390 1GHz signal gen.	£1250
Philips PM 5167 10MHz function gen.	£400
Philips 5190 LF synthesizer w/ th G.P.I.B.	£800
Philips PM 5519 Colour TV pattern gen.	£400
Philips PM 2525 Multimeter WF 1EEE	£850
Philips 5716 Pulse generator high freq. MOS	£600
Philips PM 5770 Pulse gen. - 1MHz-100MHz	£150
Philips PM 6672 1GHz timer/counter WF 1EEE	£650
Philips PM 8272 XYT chart recorder	£500
Photodyne 800 Fibre optic attenuator	£350
Projectina CH9345 Microscope	£800
Racal 9009 Modulation meter	£225
Racal Dana 202 Logic analyser + 68000 disassembler	£250
Racal Dana 9242D Programmable PSU 25V-2A	£300
Racal Dana 9246S Programmable PSU 25V-10A	£400
Racal Dana 3100 40-130MHz synthesiser	£750
Racal Dana 5002 Wideband level meter	£650
Racal Dana 5003 Digital m/meter	£150
Racal Dana 9000 Microprocessing timer/count. 52MHz	£550
Racal Dana 9081 Synth sig gen 520MHz	£550
Racal Dana 9084 Synth. sig. gen. 104MHz	£450
Racal Dana 9087 1.3 GHz low noise sig. generator	£2750
Racal Dana 9303 True RMS/Rf level meter	£650
Racal Dana 9341 LCR databridge	£250
Racal Dana 9500 Universal timer/counter 100MHz	£200
Racal Dana 9917 UHF frequency meter 560MHz	£175
Racal Dana 9919 UHF frequency meter 1GHz	£275
Rohde & Schwartz BN36711 Digital Q meter	£400
Rohde & Schwartz URV5 - 18 GHz R/F Millivolt-meter (with various probes)	£1850
Solartron Schlumb 1170 Freq. response analyser	£250
Tektronix TM503, SG503, PG506, TG501 Scope calibrator	£2000
Tektronix 834 Data comms analyser	£500
Tektronix TM5003 + AFG5101 arbitrary function generator	£1750
W&G SPM12 Level meter 200Hz-6MHz	£500
W&G PS12 level generator 200Hz-6MHz	£500
W&G SPM60 Level meter 6KHz-18.6MHz	£500
W&G PS60 Level meter 6KHz-18.6MHz	£500
W&G SPM6 Level meter 6KHz-18.6MHz	£250
W&G PS6 Level generator 6KHz-18.6MHz	£250
W&G SPM6 Level meter 6KHz-18.6MHz	£250
Wavetek 157 Programmable waveform synthesiser	£300
Wayne Kerr B424/N LCR Component meter set	£200
Wayne Kerr 4250 LCR meter	(as new) £1000
Wayne Kerr 642 Autobalance universal bridge	£200
Weller D801/D802 Desoldering station	£175
Weller D900 Desoldering station	£150
Wiltron 352 Low freq. differential input phase meter	£350
Hewlett Packard 8640B with OPT 001	£825
Marconi 2022E (10KHz - 1.01GHz) SIG GEN	£1850


SPECIAL OFFERS - Phoenix 5500A Telecoms analyser, ex. demo. as new with 12 months calibration + 12 months guarantee fitted with V24 interface. A variety of interface options available - Ring/Fax for details. **Navtel 9440** Protocol analyser, ex. demo as new **£8000** new - cost now **£3500**. **Navtel 9410** PCB based protocol analyser ex. demo. as new **£3000** new - cost now **£1500**.

MANY MORE ITEMS AVAILABLE - SEND LARGE S.A.E. FOR LIST OF EQUIPMENT ALL EQUIPMENT IS USED - WITH 30 DAYS GUARANTEE. PLEASE CHECK FOR AVAILABILITY BEFORE ORDERING - CARRIAGE & VAT TO BE ADDED TO ALL GOODS

PCB software for Windows

Pentica Systems of Wokingham has launched a new entry level version of its powerful Tango circuit design and board layout software, which runs under Windows and offers users work-station class performance at one fifth of the cost. TangoPRO Schematics Lite and TangoPRO PCB Lite are both sub-sets of the higher end TangoPRO software, with the benefit of the Windows environment. Their capacity and features are suitable for 80% of PCB designs being produced today.

TangoPRO Schematic Lite offers powerful placement and editing tools, keyboard short-cuts and instantaneous netlist generation. There are over 20,000 unique library components and new components can be created on the fly. Advanced features include intelligent wires and busses and support for user defined attributes. Junctions and bus entries are placed automatically. Capacity is up to 200 components, 500 nets and three sheets per design.

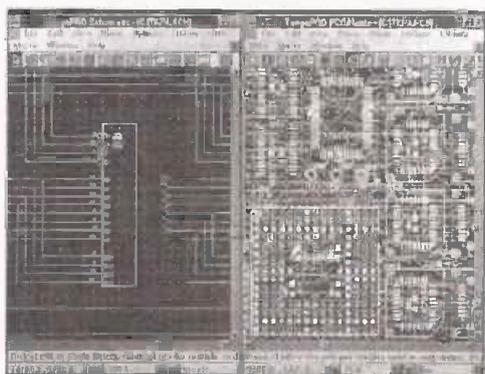

The PCB design program includes a Cut/Copy/Paste capability for moving selected items to and from the Windows Clipboard, design error indicators with on-screen highlighting, enhanced report formats and improved attribute editing, with the ability to change reference designators on previously placed components. The 32 bit database gives imperial and metric support down to a tenth mil, or 10 microns. Capacity is for 200 components, 500 nets, and six layer designs.


TangoPRO Lite Schematics costs £175 and the PCB design program £685. For further details on these two products contact Pentica Systems on 0734 792101.

70W Titanium Composite Tweeter

The latest product to be added to the fully comprehensive range of speakers and sounders from Maplin Electronics is the 70W Titanium Composite Tweeter. This is a dome tweeter, where the diaphragm is made from pure titanium which is ion deposited onto an advanced, glass-fibre reinforced, soft polymer 1in diaphragm. The composite that results offers increased stiffness with high internal damping, combining the advantages of pure metal domes while retaining the low distortion of soft dome, leading to detailed sound reproduction for the best musical quality. Efficiency is up to 93dB

and the voice coil is ferrofluid cooled. The Faceplate is of a fibre reinforced polymer.

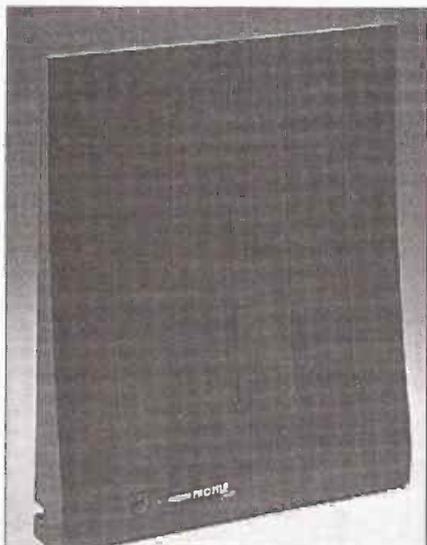This tweeter is available from all branches of Maplin Electronics and costs £13.95. For more details ring 0702 552911.



Ultra bright laser diode modules

Imatronic, the leading semiconductor laser diode module manufacturer, has released a new addition to its world beating range of OEM laser diode modules - a 633nm wavelength option. The new wavelength optics are available in the popular LDM115 (11mm diameter) and the LDM145 (16mm diameter) package styles. The 633nm wavelength offers 9 times improvement in visibility over the 670nm versions available to date. This improvement in visibility makes both indoor and outdoor operations such as alignment, positioning and levelling far simpler and effective. Particular applications include machine tool alignment, target sighting, patient positioning, robotic control and bar code systems. These highly reliable modules have been specifically designed to make the user's life easy. They feature simple DC operation (4-6V DC) and low current consumption of around 80mA. The focusing optics can be adjusted by the user with a simple tool provided with each module, so that the focus of the laser can be optimised for his own application. The integrated output power stabilisation circuitry regulates the laser output to be always



PC based PLD trainer

Programmable Logic Devices (PLDs) are now very widely used and there is a considerable need for systems which can be used to train students and engineers in their use. To cater for this need, Southampton based Flight Electronics International has launched a menu driven PC based PLD training system, the PAL Trainer. It is aimed at universities and colleges, although engineers working on their own could also use it to learn quickly about PALs and PALASMs, eventually using it as a laboratory tool for PAL programming.

Flight Electronics claims that it is the only completely self contained system available which successfully introduces students to the world of PLDs, without the need to source the hardware, software and documentation separately. This not only saves time, resources and money, but also ensures that lecturers are provided with an integrated teaching tool that gives students more than just a cursory glimpse of the real world of industry.

The PAL Trainer will run on IBM XT, AT, or compatible PCs and consists of a complete training course ranging from initial logic design to



PC simulation, device programming and testing, there are 18 ready to run examples. Programming of actual devices is done with the aid of a GAL programmer and test unit which is connected to the PC via an interface card and cable. The programmer is controlled by software running on the PC. Programming is performed with the aid of the widely used industry standard PALASM V4 programming language.

The programmer/test unit has one ZIF 24-way textool for programming and three ZIF 24-way textools for testing, there is a matrix display, four 7 segment displays, a LED array, ten debounced switches and a variable frequency counter. There is a separate demonstration area for use with the worked examples and jumper wires allow the pins of the PLD to be quickly and simply connected to other areas of the main board.

The full training system costs £695 and for further details contact Flight Electronics International Ltd, on 0703 227721.

Cutting PCBs by laser

The Berkshire based company Tracks CAD Systems has launched a multifunction laser prototyping machine which is aimed at anyone who involved in the development or production of high density Printed Circuit boards, in particular those used with surface mounted devices. Modern PCBs call for closely spaced pins and conductor or isolation paths, three or more times finer than those that have been traditionally produced using chemical etching or mechanical cutting. With its laser system, Tracks has been able to easily cut seven conductor paths, separated by 40µm isolation channels between two IC pads, the laser having a cutting resolution of 1µm and an accuracy of 2µm.


This laser system will cut standard FR4 PCB materials or copper coated ceramic material with equal facility and all track edges will be clean and square to a degree impossible to achieve in any other way. The laser will not wear, so maintenance is simple and repeatable quality assured. In addition, the system does away with the need to treat large quanti-

ties of highly polluting aqueous chemical solutions.

The system can be installed in any normal laboratory or production area and, apart from power, compressed air and water has no special requirements. A floating focus system is used on the laser, to eliminate risk of optical hazard.

The system can be directly driven from a PC CAD system for flexible prototyping. With more powerful laser cutters, it can be used to cut metal stencils, cut and score ceramics, make board corrections and label products.

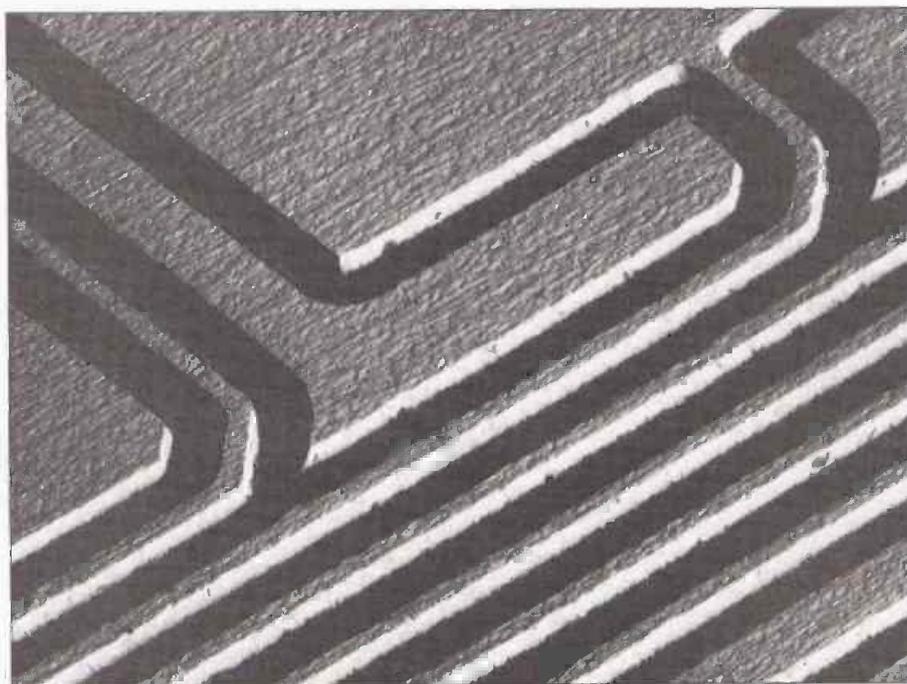For more information, contact Tracks CAD Systems on 0344 55046





386 system on an STEbus board.

Arcom Control Systems has developed a powerful new 386SX single board computer for embedded control applications, which fits on a single standard STEbus board. Compatible with PC based development and debug tools and offering a DOS like, but royalty free, stand alone operating environment, it delivers far superior real time performance to conventional embedded PCs. Called the SCIM386T, the board provides a complete hardware solution for many embedded tasks, but is also highly configurable, offering a choice of three expansion routes - STEbus, SCIM mezzanine bus and signal conditioning system.

The board is available with 25 or 16MHz versions of the 386SX CPU. Eight surface mount memory sites allow up to 4MB of dynamic RAM to be fitted. This can be extended to 16MB, using the SCIM mezzanine bus expansion facility. Further hardware includes a 32 pin EPROM socket for the stand alone operating environment and application firmware, keyboard interface, real time clock, a parallel port and two serial ports.

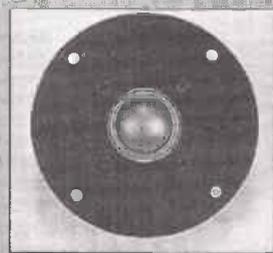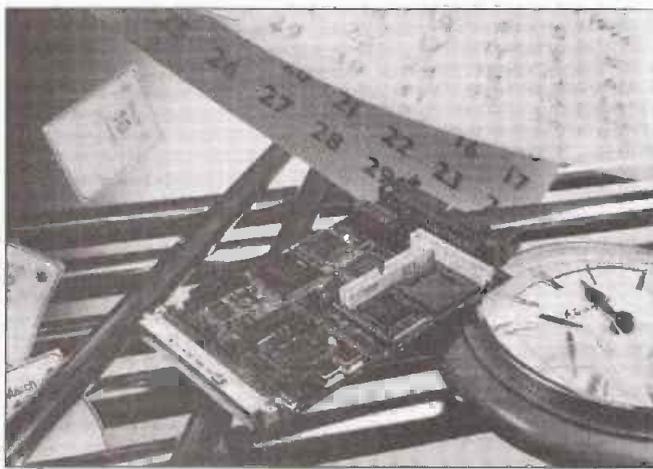For more information, contact Arcom Control Systems Ltd of Cambridge on 0223 411200.



Profile Plus Indoor FM Aerial.

New from Maplin Electronics is the profile Plus Indoor FM Aerial. This unit is a unique innovative design of an indoor aerial that would pass any critical eye test for modern styling. This bi-directional aerial is suitable for all FM applications in the frequency range 88 to 108MHz. It includes an integrated low noise signal amplifier/booster, for weak signal areas.

The aerial measures 320 x 220 x 50mm and is coloured slate grey. It requires two AA batteries and is supplied with a flylead 2m long. It costs £19.95 and is available from all branches of Maplin Electronics or via mail order. For further details ring 0702 552911.

Negative differential resistance

Negative differential resistance (NDR), a novel transistor effect that occurs in compound semiconductors, is being exploited by advanced device researchers in a bid to build a new, highly compact, digital logic family. NDR logic cuts through much of the complexity of traditional gate design, by exploiting the folded current-voltage (I-V) curves of advanced super lattice transistors. While standard transistors have only one operating point, a variety of experimental devices built with super lattice junctions can have two or more stable points, which are used to implement several logic functions with the same circuit.

While the new approach to digital logic offers the usual advantage of speed that comes with hetero-junction transistors, it more importantly could form the basis for a new kind of Ultra Large Scale Integration (ULSI) technology. In the past, gallium arsenide technology was used for its speed advantage, but that proved to be a critical factor only in niche areas, such as microwave technology. The new generation of NDR logic designs indicates a new direction for compound semiconductors, augmenting the speed advantage with large gains in functional density.

As the voltage across the junction increases, the resulting current begins to increase in a manner similar to a conventional p-n diode. However, at a critical point, the resonant tunnelling effect kicks in and the current begins to decrease as the voltage increases. The negative slope of the I-V curve in this region represents the unique negative differential resistance of these

diodes, the basic effect that is now being tried in novel logic families.

At Texas Instruments Central Research Labs. (Dallas), TI researchers were the first to build a three-terminal resonant tunnelling device that directly modulated the potential inside the super lattice junction. Previous devices had simply been monolithic realisations of the RT diode HBT pair.

The University of Michigan group is attempting to push the technology to the next stage by developing a comprehensive set of design principles and simulation tools. Rather than focusing on specific devices, the group is learning general rules for controlling the NDR effect in logic design. A device simulator that solves the quantum mechanical equations that govern resonant tunnelling effects has allowed the researchers to explore design aspects of the NDR devices. The group has also built a circuit simulator that takes either data generated by the device simulator or actual experimental data to simulate NDR logic designs.

In addition, different digital logic styles, making use of the more complex behaviour of NDR transistors, have been developed. In conventional circuit design, logic 0 and 1 values are represented by 0 and +5V levels. The I-V characteristics of the NDR devices allows for multiple logic values via multiple stable operating points. The University of Michigan group is using a logic representation that exploits two stable points in the I-V characteristic to represent Boolean logic, with two positive voltage levels

Big successes for ARM RISC

The UK RISC processor company Advanced RISC Machines Ltd seems to be on to a winner. This company, jointly owned by Acorn Computers, Apple and VLSI, has just announced two significant developments. Firstly it has signed an agreement which will allow Korean electronics and semiconductor giant Samsung to embed ARM6, ARM7, and ARM610 RISC technology into products jointly developed by Samsung and ARM for the emerging markets, where computing, communications, and consumer electronics converge. These will include wireless personal digital assistants, cellular fax/phones and interactive TV, plus more traditional products such as hard disk drives, laser printers and multimedia processors.

The second development is the announcement by IBM that the ARM RISC technology is to form the heart of its new Serial Storage Architecture (SSA) interface. This technology, developed at IBM's UK research facility in Havant, is seen as a key component in linking the computers of the future and will replace existing serial and SCSI interfaces. It is an extremely powerful interfacing system capable of full duplex operation at a minimum 20MB/s in each direction, with sophisticated error detection, isolation and recovery features. SSA is destined to be a standard for communications with peripherals such as disk drives.

Low cost microcontroller development kit



Mitsubishi has introduced a new low cost Designer's Kit which will enable users to cost effectively develop 16 bit microcontroller applications. The easy to use kit comes as a complete system and is simply installed on a PC with a text editor. At the heart of the kit is a DB16 designer board which incorporates an M37702S1ASP chip that is representative of the Mitsubishi 16 bit range and boasts the widest range of features available in single chip microcontrollers.

The on-board device operates in microprocessor mode and together with an M5M82C55 I/O expanded mapped in page zero, preserves the I/O operations by replacing the ports used as data and address buses. Ample space is provided for user software by 64KB each of battery backed RAM and EPROM. A decoder chip select is also included. Other on-board features include 52 I/O lines, together with eight 8 bit analogue to digital inputs. There are two serial ports with RS232 drivers, eight 16 bit multifunction timers and a watchdog timer, three external and 16 internal interrupts.

The software provided with the kit is a relocatable assembler which allows software to be written in pure Assembly language with user defined macro functions. Example programs in source code format can be used as templates, including those of the on board Debug monitor. This monitor includes facilities to examine and set processor registers and memory contents, upload programs from host to RAM, go to program from an address, set break point in RAM, fill memory and read analogue port. Drivers are also provided for serial and analogue to digital ports.

The designers kit operates from 5V supplies and comes complete with serial cable and 9 to 25 way adaptor, comprehensive documentation, software and the development board. The kit costs £299 and for details of suppliers contact Mitsubishi in Hatfield, Herts., on 0707 276100.

Event Diary.

- 27-29 June 5th Satellite Systems for Mobile Communications & Navigation Conference, Institute of Electrical Engineers, London. Tel: 071 240 1871
- 4-7 July HF Radio Systems and Techniques Conference, Institute of Electrical Engineers, University of York. Tel: 071 240 1871
- 5 July Talk on propagation. Sudbury and District Radio Amateurs. Tel: 0787 313212.
- 14 July Special Event Station in Woodhall School, Sudbury and District Radio Amateurs. Tel: 0787 313212
- 16 July Annual Outing. Crystal Palace and District Radio Club, All Saints Parish Church Rooms, Beulah Hill. Tel: 081 699 5732.
- 19-21 July 6th Electronic Engineering in Oceanography Conference, Institute of Electrical Engineers, Churchill College Cambridge. Tel: 071 240 1871
- 20-24 July Electrotech 94, National Exhibition Centre, Birmingham. Tel: 071 240 1871.
- 13 Nov. Midland Amateur Radio Society rally at Stockland Green Leisure Centre, Slade Road, Erdington, Birmingham. Doors open at 10am, admission £1. For further details ring 021 422 9787 or 021 443 1189 (evenings only).

If you are organising an event which you would like to have included in this section, please send full details to ETI, Argus House, Boundary Way, Hemel Hempstead, Herts. HP2 7ST, clearly marking your envelope Event Diary.

SEALED LEAD ACID Battery, 6v 80/100 AH made for BT, ex equipment but ok £45 each ref APR47. Ideal electric vehicle etc

ASTEC SWITCHED MODE PSU Gives +5 @ 3.75A, +12 @ 1.5A, -12 @ .4A 230/110, cased, BM41012. E9.99 ref APR10P3.

TORRODIAL TX 30-0-30 480VA, Perfect for Mosfet amplifiers etc. 120mm dia 55mm thick. £18.99 ref APR19.

MOD WIRE Perfect for repairing PCB's, wire wrap etc. Thin insulated wire on 500m reels. Our price just £9.99 ref APR10P8.

12v MOVING LIGHT Controller. Made by Hella, 6 channels rated at 90watts each. Speed control, cased. £34.99 ref APR35.

ELECTRON FLASH TUBE As used in police car flashing lights etc, full spec supplied, 60-100 flashes a min. E9.99 ref APR10P5.

24V 96WATT Cased power supply. New £13.99 ref APR14.

STETHOSCOPE Fully functioning stethoscope, ideal for listening to hearts, pipes, motors etc. E6 ref MAR6P6.

OUTDOOR SOLAR PATH LIGHT Captures sunlight during the day and automatically switches on a built in lamp at dusk. Complete with sealed lead acid battery etc. £19.99 ref MAR20P1.

ALARM VERSION Of above unit comes with built in alarm and pir to deter intruders. £24.99 ref MAR25P4.

CLOCKMAKER KIT Hours of fun making your own clock, complete instructions and everything you need. E7.99 ref MAR8P2.

CARETAKER VOLUMETRIC Alarm, will cover the whole of the ground floor against forced entry. Includes mains power supply and integral battery backup. Powerful internal sander, will take external bell if req'd. Retail £150+, ours? £49.99 ref MAR50P1.

TELEPHONE CABLE White 6 core 100m reel complete with a pack of 100 clips. Ideal phone extns etc. E7.99 ref MAR8P3.

VIEWDATA RETURNS E6 made by Tandata, includes 1200.75 modem, kb/d, RGB and comp o/p, printer port. No PSU E6 MAG6P7.

IBM PC CASE AND PSU Ideal base for building your own PC. Ex equipment but OK. £14.00 each REF: MAG14P2.

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit just £5.99 REF: MAG6P8.

SOLID STATE RELAYS Will switch 25A mains. Input 3.5-26V DC 57x43x21mm with terminal screws £3.99 REF: MAG4P10.

300DPI A4 DTP MONITOR Brand new, TTL/ECL inputs, 15" landscape, 1200x1664 pixel complete with circuit diag to help you interface with your projects. JUST £24.99 REF: MAG25P1.

ULTRAMINI BUG MIC 6mmx3.5mm made by AKG, 5-12v electret condenser. Cost £12 ea, Our? four for £9.99 REF: MAG10P2.

RGB/CGA/EGA/TTL COLOUR MONITORS 12" in good condition. Back anodised metal case. E9.99 each REF: MAG99P1.

GX4000 GAMES MACHINES Returns so ok for spares or repair E9 each (no games). REF: MAG9P1.

C64 COMPUTERS Returns, sook for spares etc E9 ref MAG9P2.

FUSelage LIGHTS 3 foot by 4" panel 1/8" thick with 3 panels that glow green when a voltage is applied. Good for night lights, front panels, signs, disco etc. 60-100w per strip. E25 ref: MAG25P2.

ANSWER PHONES Returns with 2 faults, we give you the bits for 1 fault, you have to find the other yourself. BT Response 200's £18 ea REF: MAG18P1. PSU E5 ref: MAG5P12.

SWITCHED MODE PSU ex equip, 60w +5v @5A, -5v @.5A, +12v @2A, -12v @.5A 120/220v cased 245x88x55mm IEC input socket E6.99 REF: MAG7P1.

PLUG IN PSU 9V 200mA DC E2.99 each REF: MAG3P9.

PLUG IN ACORN PSU 19v AC 14w, E2.99 REF: MAG3P10.

POWER SUPPLY fully cased with mains and o/p leads 17v DC 900mA output. Bargain price E5.99 ref: MAG6P9.

ACORN ARCHMEDES PSU +5v @ 4.4A on/off sw uncased, selectable mains input, 145x100x45mm E7 REF: MAG7P2.

GEIGER COUNTER KIT Low cost professional twin tube, complete with PCB and components. E29 REF: MAG29P1.

SINCLAIR C6 13" wheels complete with tube, tyre and cyde style bearing E6 ea REF: MAG6P10.

AA NICAD PACK encapsulated pack of 8 AA nicad batteries (tagged) ex equip, 55x32x32mm E3 a pack. REF: MAG3P11.

13.8V 1.9A psu cased with leads. Just E9.99 REF: MAG10P3.

360K 6.25 brand new half height floppy drives IBM compatible industry standard. Just E6.99 REF: MAG7P3.

PPCMODEM CARDS. These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is E5 REF: MAG5P1.

INFRA RED REMOTE CONTROLLERS Originally made for hi spec satellite equipment but perfect for all sorts of remote control projects. Our clearance price is just E2 REF: MAG2.

TOWERS INTERNATIONAL TRANSISTOR GUIDE. A very useful book for finding equivalent transistors, leadouts, specs etc. E20 REF: MAG20P1.

SINCLAIR C6 MOTORS We have a few left without gearboxes. These are 12v DC 3,300 rpm 6"x4", 1/4" OP shaft. E25 REF: MAG25.

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the above motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. E17.00 REF: MAG17.

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Prices E15 REF: MAG15 12v psu is E5 extra REF: MAG5P2.

***FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is E15 REF: MAG15P1.

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is E8 a pair REF: MAG 8P1 2 x PP3 req'd.

***MINATURE RADIO TRANSCEVERS** A pair of walkie talkies with a range of up to 2 kilometres in open country. Units measure 22x52x155mm. Complete with cases and earpieces. 2xPP3 req'd. E30.00 pair REF: MAG30.

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video 12v DC. E8.00 REF: MAG8P2.

LQ3600 PRINTER ASSEMBLIES Made by Amstrad they are entire mechanical printer assemblies including printhead, stepper motors etc etc in fact everything bar the case and electronics. a good stripper! E5 REF: MAG5P3 or 2 for E8 REF: MAG8P3.

NEW BULL ELECTRICAL STORE WOLVERHAMPTON BRANCH

**NOW OPEN AT 55A WORCESTER
ST TEL 0902 22039**

100MHZ OSCILLOSCOPES now in stock, 12x10cm screen, delayed sweep, 1Mohm/25pfinputs, modes-ch1, ch2, add, chop, alt, dual. 460 x 305 x 200mm, 17kgs, £267+Vat includes insurance and carriage.

INFRARED LASER NIGHT SCOPES Second generation image intensifier complete with hand grip attachment with built in laser lamp for zero light conditions. Supplied with Pentax 42mm camera mount, 1.6kg, uses 1xPP3, 3xAA's (all supplied) £245+Vat

NEW HIGH POWER LASERS 15mW, Helium neon, 3 switchable wave lengths .63um, 1.15um, 3.39um (2 of them are infrared) 500:1 polarizer built in so good for holography. Supplied complete with mains power supply. 790x65mm. Use with **EXTREME CAUTION AND UNDER QUALIFIED GUIDANCE.** £349+Vat.

'PC PAL' VGA TO TV CONVERTER Just plug in and it converts your colour television into a basic VGA screen, perfect for laptops, saves lugging monitors about or just as a cheap upgrade. Intro price £49.99 +Vat.

AMSTRAD 1512DD
1512 BASE UNIT AND KEYBOARD AND TWO 5.25" 360K DRIVES. ALL YOU NEED IS A MONITOR AND POWER SUPPLY WAS £59.00
NOW ONLY **£39.00**
REF: MAG39

3FT X 1FT 10WATT SOLAR PANELS
14.5v/700mA
NOW AVAILABLE BY MAIL ORDER
£33.95

(PLUS £2.00 SPECIAL PACKAGING CHARGE)

TOP QUALITY AMORPHOUS SILICON CELLS HAVE ALMOST A TIMELESS LIFESPAN WITH AN INFINITE NUMBER OF POSSIBLE APPLICATIONS, SOME OF WHICH MAY BE CAR BATTERY CHARGING, FOR USE ON BOATS OR CARAVANS, OR ANYWHERE A PORTABLE 12V SUPPLY IS REQUIRED. REF: MAG34

*****WE BUY SURPLUS STOCK*****
TURN YOUR SURPLUS STOCK INTO CASH
IMMEDIATE SETTLEMENT WE WILL ALSO QUOTE FOR COMPLETE FACTORY CLEARANCE

1994 CATALOGUE.

PLEASE SEND 45P, A4 SIZED SAE FOR YOUR FREE COPY.
MINIMUM ORDER: £5.00 TRADE ORDERS FROM GOVERNMENT, SCHOOLS, UNIVERSITIES, & LOCAL AUTHORITIES WELCOME. ALL ORDERS SUBJECT TO OUR CONDITIONS OF SALE AND INCLUDE OTHER WISE WRITTEN QUANTITIES FOR 30 DAYS. RIGHTS RESERVED TO CHANGE PRICES & SPECIFICATIONS WITHOUT NOTICE. ORDERS SUBJECT TO STOCK. QUOTATIONS WILLINGLY GIVEN FOR QUANTITIES HIGHER THAN THOSE STATED.

*SOME OF OUR PRODUCTS MAY BE UNLICENSEABLE IN THE UK

BULL ELECTRICAL
250 PORTLAND ROAD HOVE SUSSEX
BN3 5QT
**MAIL ORDER TERMS: CASH PO OR CHEQUE
WITH ORDER PLUS £3.00 POST PLUS VAT.**
PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY
TELEPHONE ORDERS WELCOME
TEL: 0273 203500
FAX: 0273 323077

SPEAKER WIRE Brown 2 core 100 foot hank E2 REF: MAG12P1.

LED PACK of 100 standard red 5m leds E5 REF: MAG5P4.

UNIVERSAL PC POWER SUPPLY complete with flyback switch, fan etc. Two types available 150w at E15 REF: MAG15P1 (23x23x23mm) and 200w at E20 REF: MAG20P3 (23x23x23mm).

***FM TRANSMITTER** housed in a standard working 13A adapter! The bug runs directly off the mains so lasts forever! why pay E700? or price is E26 REF: MAG26 Transmits to any FM radio.

***FM BUG KIT** New design with PCB embedded coil for extra stability. Works to any FM radio. 9v battery req'd E5 REF: MAG5P5.

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. E14 REF: MAG14.

TALKING COINBOX STRIPPER originally made to retail at £79 each, these units are designed to convert and ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? Price is just E3 REF: MAG3P1.

100 WATT MOSFET PAIR Same spec as 25K343 and 2SJ413 (8A, 140v, 100w) 1 N channel, 1 P channel, £3 a pair REF: MAG3P2.

TOP QUALITY SPEAKERS Made for Hi Fi televisions these are 10 watt 4R Jap made 4" round with large shielded magnets. Good quality. E2 each REF: MAG2P4 or 4 for E6 REF: MAG6P2.

TWEETERS 2" diameter good quality tweeter 140R (ok with the above speaker) 2 for E2 REF: MAG2P5 or 4 for E3 REF: MAG3P4.

AT KEYBOARDS Made by Apnecot these quality keyboards need just a small mod to run on any AT, they work perfectly but you will have to put up with 1 or 2 foreign keycaps! Price E6 REF: MAG6P3.

PC CASES Again mixed types so you take a chance next one off the pile E12 REF: MAG12 or two the same for E20 REF: MAG20P4.

COMMODORE MICRODRIVE SYSTEM mini storage device for C64's 4 times faster than disc drives, 10 times faster than tapes. Complete unit just E12 REF: MAG12P1.

SCHOOL STRIPPERS We have quite a few of the above units which are 'returns' as they are quite comprehensive units they could be used for other projects etc. Let us know how many you need at just 50p a unit (minimum 10).

HEADPHONES Ex Virgin Atlantic 8 pairs for E2 REF: MAG2P8.

PROXIMITY SENSORS These are small PCB's with what look like a source and sensor LED on one end and lots of components on the rest of the PCB. Complete with fly leads. Pack of 5 E3 REF: MAG3P5 or 20 for E8 REF: MAG8P4.

SNOOPERS EAR? Original made to dip over the earpiece of telephone to amplify the sound-it also works quite well on the cable running along the wall. Price is E5 REF: MAG5P7.

DOS PACKS Microsoft version 3.3 or higher complete with all manuals or price just E5 REF: MAG5P8. Worth it just for the very comprehensive manual! 5.25" only.

DOS PACK Microsoft version 5 Original software but no manuals hence only E3 REF: MAG3P6 5.25" only.

CTM644 COLOUR MONITOR Made to work with the CPC464 home computer. Standard RGB input so will work with other machines. Refurbished E59.00 REF: MAG59.

PIR DETECTOR Made by famous UK alarm manufacturer these are hi spec, long range internal units. 12v operation. Slight marks on case and unboxed (although brand new) E8 REF: MAG8P5.

WINDUP SOLAR POWERED RADIO AM/FM radio complete with hand charger and solar panel! E14 REF: MAG14P1.

COMMODORE 64 TAPE DRIVES Customer returns at E4 REF: MAG4P9. Fully tested units are E12 REF: MAG12P5.

MAINS CABLES These are 2 core standard black 2 metre mains cables fitted with a 13A plug on one end, cable the other. Ideal for projects, low cost manufacturing etc. Pack of 10 for E3 REF: MAG3P8. Pack of 100 E20 REF: MAG20P5.

MICROWAVE TIMER Electronic timer with relay output suitable to make enlarger timer etc. E4 REF: MAG4P4.

MOBILE CAR PHONE £5.99 Well almost! complete in car phone excluding the box of electronics normally hidden under seat. Can be made to illuminate with 12v also has built in light sensor so display only illuminates when dark. Totally convincing! REF: MAG6P6.

ALARM BEACONS Zenon strobe made to mount on an external bell box but could be used for caravans etc. 12v operation. Just connect up and it flashes regularly! E5 REF: MAG5P11.

FIRE ALARM CONTROL PANEL High quality metal cased alarm panel 350x165x80mm. With key. Comes with electronics but no information. sale price 7.99 REF: MAG8P6.

REMOTE CONTROL PCB These are receiver boards for garage door opening systems. Another use? E4 ea REF: MAG4P5.

6"x12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just E5.99 ea REF: MAG6P12.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for E4.99 ref: MAG5P13 ideal for experimenters! 30m for E12.99 ref: MAG13P1.

LOPTX Line output transformers believed to be for hi res colour monitors but useful for getting high voltages from low ones! E2 each REF: MAG2P12 bumper pack of 10 for E12 REF: MAG12P3.

**BOTH SHOPS OPEN 9-5.30
SIX DAYS A WEEK**

PORTABLE RADIATION DETECTOR
£49.99

A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30K eV to over 1.2M eV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. Supplied complete with handbook.

REF: MAG50

EXPRESS COMPONENTS

MAINS IONIZER KIT. Very useful kit that increases the flow of negative ions. Helps clear cigarette smoke, dust, pollen etc. Helps reduce stress and respiratory problems. £15. kit, £20 built.

COMBINATION LOCK. Electronic 5 key combination lock suitable for cars, houses etc, easily programmable. Includes mains 2A relay o/p. 9v operation. £10 kit, £14 built.

VARIABLE POWER SUPPLY. Stabilized, short circuit protected. Gives 3-30v DC at 2.5A, ideal for workshop or laboratory. £14 kit, £18 built. 24VAC required.

LEAD ACID CHARGER. Two automatic charging rates (fast and slow), visual indication of battery state. Ideal for alarm systems, emergency lighting, battery projects etc. £12 kit, £16 built.

PHONE LINE RECORDER. Device that connects to the 'phone line and activates a cassette recorder when the handset is lifted. Ideal for recording 'phone conversations etc!. £8 kit, £12 built.

ROBOT VOICE. Turns your voice into a robot voice! answer the phone with a different voice!. £9 kit, £13 built.

PHONE BUG DETECTOR. This device will warn you if somebody is eavesdropping on your 'phone line. £6 kit £9 built.

PHONE BUG. Small bug powered by the telephone line. Only transmits when the phone is used. Popular surveillance product £8 kit, £12 built.

STROBE LIGHT. Bright strobe light with an adjustable frequency of 1-60hz. (a lot faster than conventional strobes!) £16 kit, £20 built.

4W FM TRANSMITTER. 3RF stages, audio preamp. 12-18vDC. Medium powered bug £20 kit, £28 built.

3 CHANNEL LIGHT CHASER. 3x 800w output, speed and direction controls, can be used with 12 led's (supplied) or TRIACS for mains lights (also supplied). 9-15vDC. £17 kit, £23 built.

25W FM TRANSMITTER. 4 stage, a preamp will be required. (Our preamp below is suitable) £79 built. (no kits).

SOUND EFFECTS GENERATOR. Produces any thing from bird chips to sirens! add sounds to all sorts of things £9 kit £13 built.

FM/AM SCANNER. Well not quite, you have to turn the knob yourself but you will hear things on this radio (even TV) that you would not hear on an ordinary radio! A receiver that covers 50-160MHZ both AM and FM. Built in 5w amplifier. £15 kit, £20 built.

CAR ALARM SYSTEM. Works on vibration and/or voltage drop from door etc being opened. Entry and exit delays plus adjustable alarm duration. Low cost protection! £12 kit, £16 built.

15W FM TRANSMITTER. 4 stage, high power bug. You will need a preamp for this (see our preamp below which is ok) £69 built. (no kits).

1W FM TRANSMITTER. 2 stage including preamp and mic. Good general purpose bug. 8-30VDC. £12 kit, £16 built.

50 I/C's for £1.50
Nice mix of chips at a bargain price!

CERAMIC CAPACITOR PACK
Good mixed pack of 100 capacitors for just £1.00

ELECTROLYTIC PACK 1
100 small mixed electrolytic capacitors just £1.00

ELECTROLYTIC PACK 2
50 larger electrolytic mixed capacitors

RESISTOR PACK NO 1
250 low wattage resistors, ideal for most projects etc. Just £1.00

RESISTOR PACK NO 2
Hi wattage pack, good selection of mixed wattages and values 50 in all, bargain price just £1.00

PRESET PACK
Nice selection of 25 mixed preset pots for just another £1!

RELAY PACK NO 1
6 mixed relays for £1, thats just 17p each.

CONNECTOR PACK
10 different connectors, again for £1

FUSE PACK NO 1
40 mixed 20mm fuses, ideal for repairs etc, or just to stock up the spares box! Just £1 00

FUSE PACK NO 2
30 mixed 1.25" fuses again ideal for spares etc. Just £1.00

WIRE PACK
25 Metres of insulated wire for just £1 00, good for projects etc

SLEEVING PACK
100 assorted pieces of sleeving for connectors etc. Yours for just £1.00

DIODE PACK
100 assorted diodes for just £1.00

LED PACK
20 light emitting diodes for £1 00

TRANSISTOR PACK
50 mixed transistors, another bargain at £1.00

BUZZER PACK
10 things that make a noise for just £1.00!

POT PACK
10 pots for £1, (5 different types) a snip at £1.00

DISPLAYS
10 seven segment displays for £1.00

ORDER 10 PACKS OR MORE AND CHOOSE ONE FREE PACK!!

FREE COMPONENT CATALOGUE WITH EVERY ORDER!!

99p
Post

BULK PACKS

PREAMP MIXER. 3 channel input, independent level and tone controls. Ideal for use with the hi power FM transmitters. £15 kit, £19 built.

TREMBLER ALARM. Designed for bikes etc, adjustable sensitivity, preset alarm time, auto reset. Could be adapted for all sorts of "borrowable" things £12 kit, £16 built

ULTRASONIC RADAR. A project that can be used as a movement detector in an enclosed space. Range about 10 metres, 12vDC. Good basis for car, shed, caravan alarm etc. £14 kit, £19 built.

PHONE CALL RELAY. Very useful kit that incorporates a relay that operates when the phone rings. Can be used to operate more bells, signalling lights etc. Good for noisy environments or if you have your headphones on! £10 kit, £14 built

PORTABLE ALARM SYSTEM. Small 9v alarm system based on a mercury switch. The alarm continues to sound until disabled by the owner. Buzzer included. £11 kit £15 built.

800W MUSIC TO LIGHT EFFECT. Add rhythm to your music with this simple sound to light kit. £8 kit, £12 built.

MOSQUITO REPELLER. Modern way to keep the midges away! Runs for

about a month on one 1.5v battery. Frequency is set to drive away mosquitos etc. £7 kit, £11 built.

3 CHANNEL SOUND TO LIGHT. Can be used anywhere as no connection is made to hi fl. Separate sensitivity controls for each channel, 1,200W power handling. Microphone included. £14 kit, £19 built.

MINI METAL DETECTOR. Detects pipes, wires etc up to 20cm deep. Useful before you drill those holes! £8 kit, £12 built.

0-5 MINUTE TIMER. Simple time switch adjustable from 0-5 mins, will switch 2A mains load. 12v op. Ideal for laboratory, photographic projects etc. £7 kit, £11 built.

7 WATT HI FI AMPLIFIER. Useful, powerful amplifier 20hz-15hz, 12-18vdc. Good for intercoms, audio systems, car etc. £7 kit £11 built.

INCAR SOUND TO LIGHT. Put some atmosphere in your car with this kit. Each channel has 6 led's that create a beautiful lighting effect! £10 kit, £14 built.

VOX SWITCH. This is a sound activated switch, ideal for use on transmitters, CB's, tape recorders etc. Adjustable sensitivity, built in delay. Mic input. £7 kit, £11 built.

KITS 'N MODULES

LIQUID LEVEL DETECTOR. Useful item, can be used to detect fluid levels in watertanks, baths, ponds fish tanks etc. Could also be used as rain alarm with an easily constructed sensor. £5 kit, £9 built.

FM TRANSMITTER. Mini FM transmitter 2 transistor, comes with FET miniature mic and is tuneable from 63 to 130MHZ. £7 kit, £11 built.

FUNCTION GENERATOR. Generates sinusoidal, saw tooth and square waveforms from 20hz up to 20khz. Separate level controls for each waveform. 24vac. £15 kit, £20 built.

5 WATT SIREN. Powerful siren kit with an impressive 5 watts output. Ideal for alarms etc. £6 kit £10 built.

TELEPHONE AMPLIFIER. Very sensitive amplifier which using a 'phone pickup coil (supplied) will let you fol-

low a telephone conversation without holding the handset to your ear! £11 kit £15 built.

SWITCH PACK
10 switches for just £1.00

12v FLOURESCENT. A useful kit that will enable you to light large fluorescent tubes from your car battery etc 9v mains transformer required. £8 kit, £12 built.

KNOB PACK
10 knobs for just £1.00

REMEMBER! YOUR FREE COPY OF OUR CUT PRICE COMPONENTS CATALOGUE SENT WITH EVERY ORDER!!!

How to place your order.....
By phone.....0273 771156
By FAX.....0273 206875
By Post...PO box 517 Hove Sussex BN3 5QZ
Payment by ACCESS, VISA, CHEQUE OR POSTAL ORDER.
Cheques and postal orders should be payable to Express Components.
ALL PRICES ARE SUBJECT TO 99p POST AND VAT. Some of our products may be unlicensable for use in the UK (particularly the FM transmitters.)

Where on Earth am I?

A network of US military satellites can now be used to pin point your position in three dimensions, to within just a few metres anywhere on the surface of our planet. We look at how this system works and how it is being used as the basis for a range of new devices that could affect all our lives.

During the Gulf War, the US military and their allies made unprecedented use of high technology to give them a strategic advantage over their Iraqi opponents. This allowed them to attack key targets with enormous precision and minimum risk to their own forces. Remember the news shots of cruise missiles flying low along a main street in Baghdad? Missiles capable of locating and destroying a specific building or installation and so accurate that they could fly into an air conditioning duct on a concrete bunker. There were also SAS teams who were capable of moving across the desert at high speed, under cover of dark, to accurately locate and destroy Iraqi supply columns and SCUD missile launchers.

The technology which allowed the allied forces to precisely target missiles, aircraft and troops gave them an enormous edge. It was based on a highly sophisticated network of satellites, orbiting the Earth at a height of 20,200 kilometres, known as GPS, or Global Positioning System. With this system, the US military and NATO allies can pinpoint any piece of hardware with an accuracy in three dimensions ranging from a few metres to a few centimetres or even less.


This is no ordinary military development, since the US has made it possible for anyone to use it, on a somewhat less accurate level, to locate their

geographical position or that of some piece of mobile equipment. All over the world, merchant ships, yachtsmen, commercial and private aircraft are now using GPS systems to track their current position. Transport companies are using it to locate their vehicles, emergency services are using it to identify the nearest team to a particular incident, even taxi companies are using it to locate the nearest cab to a customer.

Very soon GPS systems will influence the lives of all of us. The big car companies, for example, are developing techniques which will allow drivers to know exactly where they are on an electronic atlas. Air traffic control systems are being developed which will utilise GPS to allow increasing numbers of aircraft to fly on busy routes. GPS systems are so accurate that they are even being used to measure and survey new buildings, roads and bridges, to remotely check for dangerous distortions in dams and earth movement in earthquake zones.

The development of GPS

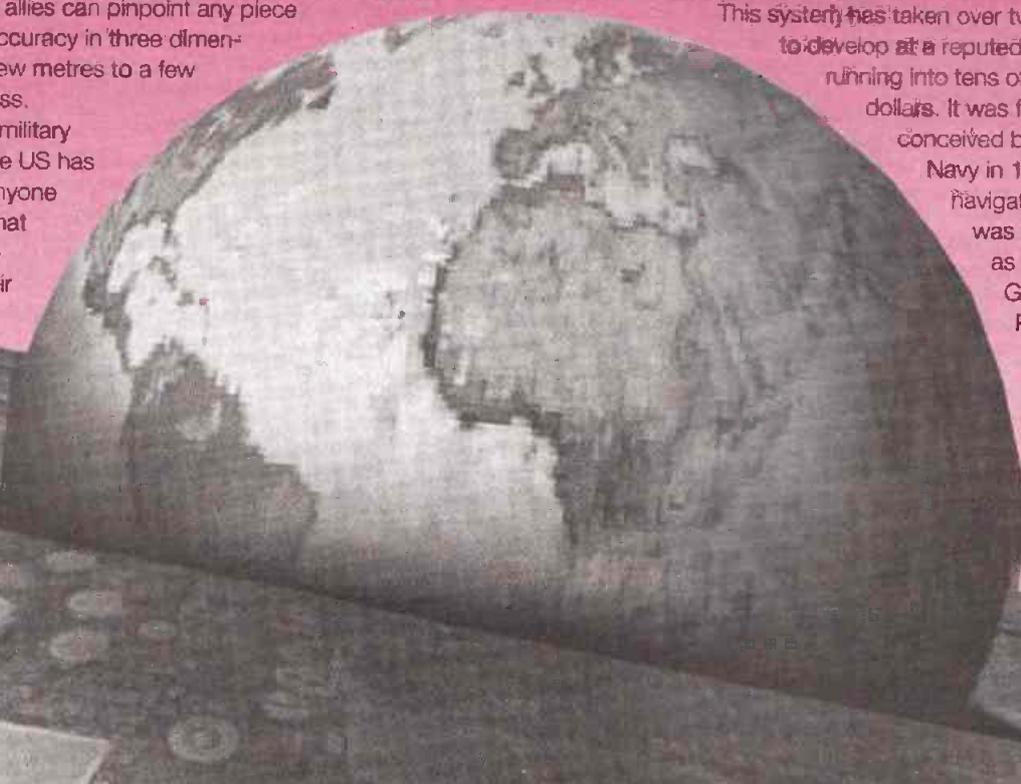This system has taken over twenty years to develop at a reputed cost running into tens of billions of dollars. It was first conceived by the US Navy in 1973 as a navigation aid and was then known as the Navstar Global Positioning System. This was based upon a technology derived from



earlier, land based, radio beam navigation systems, such as the well known Loran in America and the Decca in Europe. These had been developed during and after World War II for maritime navigation purposes.

The designated function of Navstar GPS was, like Loran and Decca, to provide an accurate all weather naval navigation system. However, this function was broadened as a result of its being merged with the US Air Force 612B programme, to provide highly accurate three dimensional positioning which could be used not just by naval vessels, but also by aircraft and for the new generation of smart missiles.

The GPS concept was the subject of an enormous amount of very careful design work, both from the practical aspect and from the strategic aspect. The system had to be capable of very high accuracy, but also had to be proof against jamming by an enemy. The result of this design work was the launch of a test satellite in June 1977.

The first test system was sufficiently successful to persuade the Pentagon to go ahead with launching a network of GPS satellites. The first of these were launched from the USAF's rocket launch facility at Vandenberg Air Force Base in California, in 1978 and a limited two dimensional positioning system was first possible in October of that year. Three dimensional positioning was demonstrated two months later.

This early system relied on just a small number of satellites and thus provided only a few hours of operation each day. To give a 24 hour global, high accuracy, three dimensional positioning capability required the launch of a lot more satellites, so that at any time at least one and preferably more satellites were above the horizon at any position on Earth. These have been launched over the years, using the space shuttle or Delta rockets.

At the moment, the GPS satellites system can provide full two dimensional high accuracy positioning, 24 hours a day, anywhere on the surface of the Earth, but it is still only capable of providing about 22 hours per day worth of full, high accuracy, three dimensional positioning, depending of course on latitude and altitude. The network is expected to be completed and fully operational with 24 hour three dimensional positioning capability by mid 1995.

The only real problem which remains is the fact that GPS signals will not penetrate buildings or rock and consequently a GPS receiver can be effectively shielded from the satellites, thus reducing its ability to give an accurate position. This can lead to problems with accurate positioning in built up or mountainous areas. Another source of problems is ionospheric distortion, a signal distortion which can easily account for a positional error of 20 or 30 metres.

The signal shielding problem can, to a degree, be overcome by use of advanced software techniques in the receiver, coupled with an increased number of GPS satellites. The ionospheric distortion problem, on the other hand, is overcome by having the satellite produce two signals at different frequencies. Since the degree of distortion varies with signal frequency, it is thus possible to compare the two signals and compensate for the ionospheric distortion. Again, this is a problem which requires advanced software in the receiver for a satisfactory solution.

The military and civilian modes

The fascinating thing about the US military GPS system is that it is probably the only military system which civilians are allowed to use. Indeed, the US government has guaranteed free access for civilian users until at least the year 2005 and probably longer. However, they are not giving civilian users unlimited access, otherwise they would be handing over the technology to any potential enemy.

The result is that, although a GPS system in stand alone mode has a positional accuracy of about 20 metres, this is degraded to 100 metres in civilian systems. Civilian systems can, however, be used to

How GPS works

The GPS system consists of a network of satellites orbiting Earth at an altitude of 20,200 kilometres twice per sidereal day (a sidereal day is 23 hours and 56 minutes long). This means that they cover the same track each day, but four minutes earlier. There are six orbiting planes of three satellites at 55 degrees inclination to the horizon.

Each of the eighteen satellites in current operation transmits continuously on the same frequency, the carrier frequency being 1575MHz. The actual signal is transmitted using spread spectrum modulation, which means that the carrier wave is phase inverted by a pseudo-random code running, at 1.023MHz. In order to recover the signal, it is multiplied by a replica of the code used in the satellite. There are two versions of this code the normal civilian version and the secret, highly accurate, military P-code.

Each satellite has its own code which identifies the satellite, its current position and the current time. The code containing this information is 1023 bits long and repeated once every millisecond. Timing has to be very accurate and on each satellite is derived from an atomic clock.

Using this system, the receiver finds the position using two techniques. Firstly, it measures the Doppler shift of the signal that results from the satellite's motion relative to Earth. Secondly, it measures the signal propagation delay between several satellites. The data from these two techniques is combined by the controlling computer with data on the satellite orbits and the exact position of the satellites in those orbits, to generate the receiver's exact position.

Accurate position calculation requires that a lot of factors are taken into account. Thus, corrections need to be made for ionospheric distortions and even the effect of relativity (due to an increase in frequency from the signal interacting with the gravity gradient) has to be taken into account and corrections made to the calculations. GPS systems rely upon an enormous amount of highly sophisticated computation to produce their results, hence their need for powerful processor chips.

achieve much higher accuracy when used in other modes. Thus, a five metre accuracy is possible when used in differential mode with corrections from a reference receiver at a known location. Even greater accuracy, down to a few millimetres, is possible when the system is used with carrier phase tracking.

The primary military and civilian use for GPS systems is in the form of real time, stand alone systems, rather than those involving linkage with other receivers and a considerable amount of post processing. For this reason, it is the stand alone mode which is degraded in the civilian versions.

This degradation, known as 'Selective Availability' is achieved by use of a secondary code, the P or 'precise' code, that is transmitted by the satellite along with the conventional positional and time data. This P-code contains the information which allows far greater positional accuracy to be obtained. This P-code can be changed at regular intervals to prevent enemy access and has also been designed so that an enemy can not generate spurious GPS signals and thus deceive the receiver into giving a false location.


Of course, as one would expect, the Russians have an equivalent GPS system known as GLONASS. To date, this Russian system has not been used commercially, but moves

are underway to incorporate it into the GPS network with the development of combined GPS/GLONASS receivers. Such combined receivers will have the benefit of a far larger number of satellites and thus be less prone to error.

The commercial application of GPS

A practical GPS system consists of two components, the radio receiver/antenna system and the signal analysis computer. Thanks to the military origin of the system, the radio receiver/antenna system is already available as highly integrated units, indeed GEC Plessey Semiconductors has produced a single chip which contains most of the receiver electronics. Similarly, the analysis computer can be one of the high power microprocessor chips that are now widely available and here the Transputer seems to be a common choice. All this means that the actual hardware for a basic commercial GPS system can now be obtained for just a couple of hundred pounds.

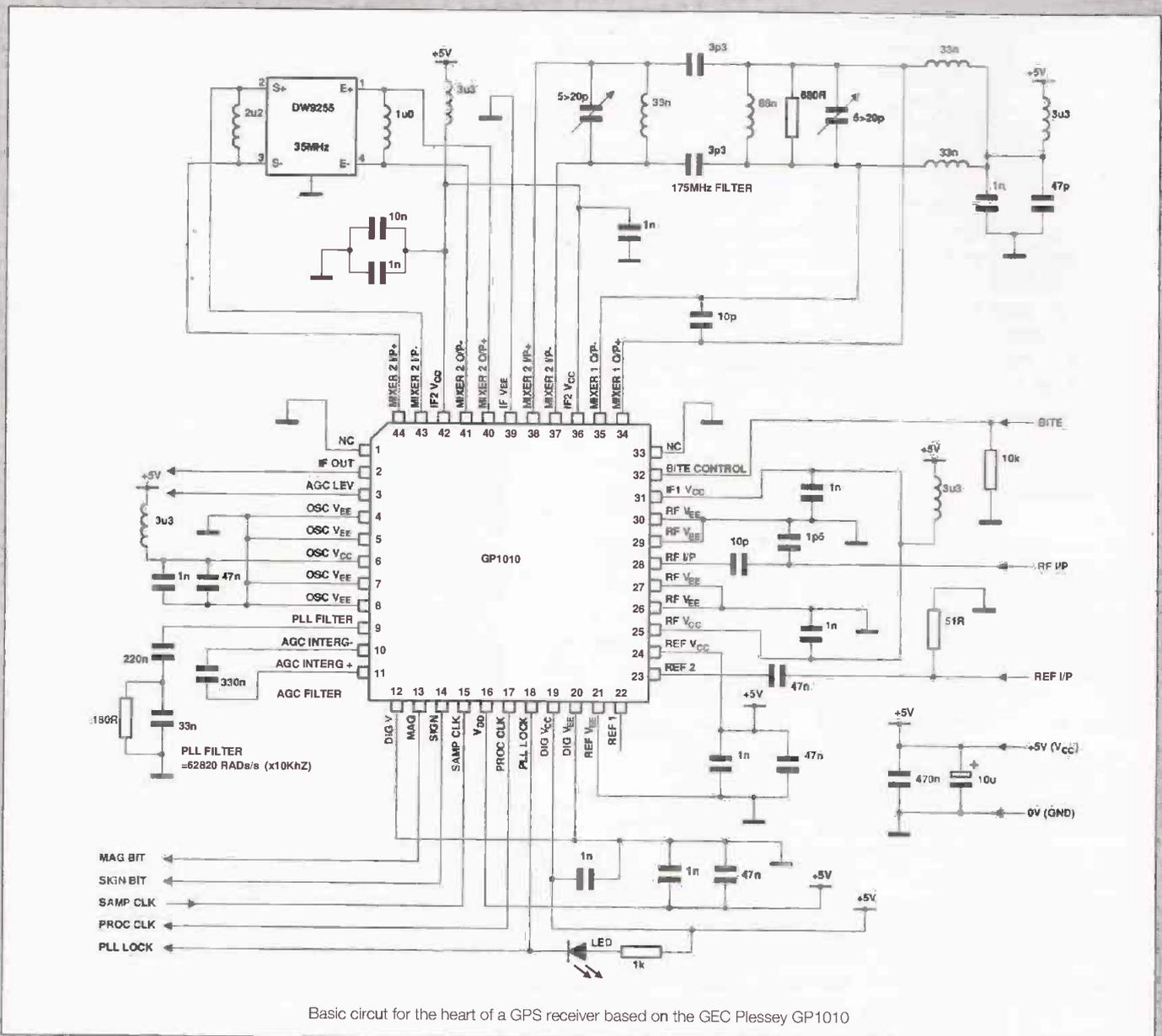The relative low cost of commercial GPS systems has meant that over the last few years there has been an enormous boom in the sales of sets. As one would expect with a system that was initially conceived as a maritime navigation aid, the first big market to appear for commercial GPS was among professional



Basic circuit for the heart of a GPS receiver based on the GEC Plessey GP1010

and amateur boat owners. Boat owners were also the first to benefit from 24 hour GPS coverage, because the wide, uninterrupted horizon at sea allowed position fixing with a network of fewer satellites, while sailors did not need the more complex three dimensional positioning capability of the full GPS system.

There was initially considerable competition from the existing Loran and Decca navigation systems, but as the price of GPS has come down, it has become more popular, particularly in the professional market and with the serious yachtsman. Indeed, one only has to pick up a copy of any one of the yachting magazines to find dozens of adverts for GPS equipment, at prices ranging from three or four hundred to several thousand pounds.

This increasing popularity is due to a combination of factors. Firstly, the decreasing cost and secondly, the integration of GPS systems with electronic charts and course plotting software that will run on personal computers. Amongst certain professional users the very high accuracy of differential and carrier phase tracking GPS systems has been employed with considerable success. For example, oil rigs are now routinely positioned in oil fields such as the North Sea with enormous accuracy, thanks to GPS, in fact so accurately that a production platform can be exactly positioned above the well head left by a drilling rig. Ferry companies are amongst the other users of GPS

systems that require high accuracy. In many busy and confined navigation channels, such as the Channel and large navigable rivers like the Mississippi or the Rhine, GPS systems can be used to accurately keep a vessel in navigable channels and also in the correct channel to avoid collisions with vessels going in the opposite direction.



The maritime emergency services have also started to make considerable use of GPS. Here, the International Maritime Organisation was one of the first to realise that search and rescue operations could be made much more effective if a GPS system was used to give an accurate position of a vessel in distress. It is now an IMO requirement that all commercial vessels carry a GPS receiver, which means that search and rescue craft can be sent directly to a site and locate it using their own GPS receivers.

Private and commercial pilots were also quick to realise the potential of GPS as an additional aid to navigation. For years they had been relying upon a network of VHF radio beacons to provide accurate fixes, while commercial jets also had an Inertial Navigation System, or INS, for navigation across oceans. Pilots used a combination of these two position location systems, with radar, altimeters and of course voice links with air traffic control, to provide accurate navigation.

GPS on a chip

For anyone interested in experimenting with GPS systems, GEC Plessey Semiconductors has made life a lot easier with the development of a single IC, including all the active circuitry needed to convert global positioning information in rf spread spectrum form to a 4.309MHz if form, that can be used for subsequent processing. The diagrams in this box show how this chip, the GP1010, functions, as well as a basic applications circuit.

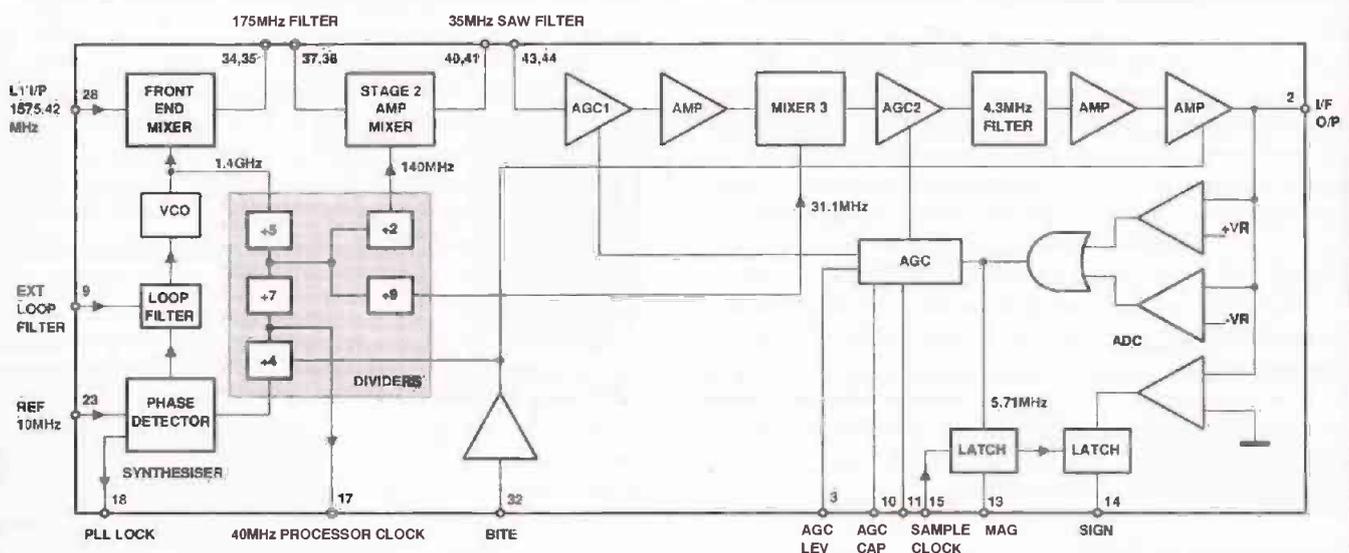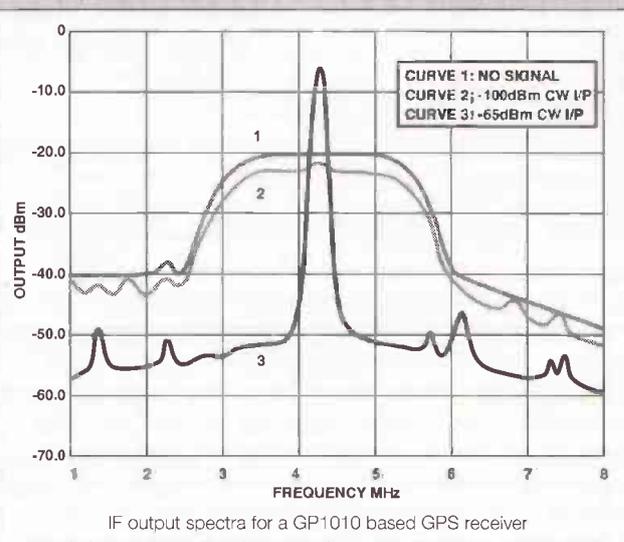For more information on the GP1010 contact GEC Plessey Semiconductors, in Swindon on 0793 518000.



Block diagram of a GP1010 GPS chip

The problem with the network of beacons is that it automatically creates a system of lanes in the sky, along which aircraft travel from one beacon to another. The result is a localised build up of aircraft in a particular part of the sky, thereby putting limits on the number of aircraft which can safely fly a particular route. The other limitation is that many leisure flyers, such as microlights, small aircraft and balloons may be unable to properly utilise the beacon system.

This is less of a problem over oceans, where there is no beacon network and pilots have to rely upon their INS. But INS systems are notoriously inaccurate and can quite often register a drift of one degree per flying hour, a drift which can result in a serious positional error after a long ocean flight.

The use of GPS systems solves all these problems. They can give accurate positional fixes to within 100 metres on the horizontal and 150 metres in the vertical, which means that there need be no positional drift over oceans, deserts, etc., and where air traffic is heavy, many more lanes can be created and the separation between aircraft reduced. Furthermore, because GPS systems are cheap and lightweight, they can be installed in any type of aircraft, even microlights.

Perhaps the most spectacular use of GPS systems in terms of accuracy is in ground based surveying with the aid of carrier phase tracking. Besides being used in building and civil engineering construction surveying, it can be used to create extremely accurate maps. Maps that are being combined with satellite images to provide information on a wide range of geological, economic and environmental subjects. They can, for example, be used to accurately measure movements in the tectonic plates of the Earth, or in a major fault line and thus help predict earthquakes.

Stand alone GPS systems are also being used by freight companies to accurately locate the position of heavy goods vehicles, trains or even individual freight containers. These systems involve linking the GPS to either existing voice VHF networks for automatically relaying vehicle position within a local area, or via the Inmarsat satellite system for global position location. This not only enables the operator to accurately locate the vehicles in a fleet, thereby optimising their use, but it also allows them to track any stolen vehicles. This is a particularly important feature of the system when one considers that goods vehicles and their freight loads worth over £500 million are stolen every year and most of them are never located.

Automatic location of mobile units with the aid of GPS systems is also proving useful to the various emergency services, since it allows police, ambulance and fire services to locate the nearest appliance to an incident and thus reduce the time taken to reach it. A similar system is also being deployed by the London cab company, Computacabs, to enable them to get a cab to a customer as quickly as possible and also via VHF links to warn drivers of problems on the roads, check customer credit cards and advise on optimum routes. Other potential users of such systems include bus companies and service/maintenance vehicles for power and telecommunication companies.

Surprisingly enough, GPS systems are also being used in applications which do not involve position location. In fact, GPS systems can also be used as very accurate time and frequency sources (the satellites all contain highly accurate atomic clocks) and moreover, as a time source which is globally synchronised. The BBC time signal is no longer derived from a time source in Greenwich, but from a GPS receiver.

The future of GPS

As we have seen, GPS systems are already being employed in

a wide range of non military applications. However, the development of GPS applications is still in the early stages and we have yet to see some of the most exciting of these developments, which look likely to have an impact on the lives of nearly all of us.

The application which will undoubtedly have the widest impact is the development of GPS systems for cars. All round the world, the major motor manufacturers are working on such systems. These products range in sophistication from a simple emergency beacon to full scale navigation systems, complete with electronic map displays. Prototype in car navigation systems are already undergoing tests in Japan, the US, the UK and Germany.

Probably the most sophisticated of these projects is being developed by a consortium of Japanese car companies. It involves storing a high precision 50,000:1 vector map database in the car as part of the GPS system, which is displayed on a PC quality flat screen display. This database is linked to a sensor system, allowing the car to be precisely positioned on the map with the aid of dead reckoning and map constraints, all based upon a GPS reference. This gives the navigation system far greater accuracy than is possible with the GPS system alone.

Because the navigation system must not distract the driver, the Japanese system will only function when the car is stationary or moving at under ten miles per hour. At higher speeds, it will simply display trunk roads without any finer detail. The problem of driver distraction has led some European developers to propose a purely voice command system (I can see this driving people mad very quickly!, Ed.)

Car navigation systems based on GPS could be on the market today and, indeed some simpler systems are, but their further development is constrained by one major factor - the lack of high precision electronic map data for many areas of potential use. It is the availability of such maps that has allowed the Japanese to gain an early lead in this market.

Car navigation systems may well prove to be the big commercial market for GPS systems but the future for this technology is no less exciting in other areas. For example, in maritime applications, experimental GPS receivers are now being linked with communications systems that utilise the low flying COSPAS SARSAT satellites to continuously report on a vessel's position. In future they will probably be linked to geostationary satellites as part of a system which will allow accurate control of shipping movements.

Moves are also afoot to use GPS systems to replace some elements of air traffic control and permit planes to fly much closer to each other. Again, this will rely upon GPS systems on the plane continuously reporting exact positions to air traffic control, via a geostationary satellite. Problems associated with a failure of the actual GPS system have now been overcome and the safety aspect of relying on GPS has been satisfactorily resolved.

Another aeronautical application for GPS is for precision approach and landing systems. This is a particularly important development, since it will considerably improve safety at countless airports, particularly in the third world, where no MLS system is installed.

This article has, I hope, shown that satellite base global positioning systems are likely to have a considerable impact over the coming decade in a wide range of different non military applications. GPS should improve efficiency and safety in a great many transport operations, and allow scientists and engineers to measure minute movements in the environment, providing vital clues to climatic changes or impending earthquakes.

This is one piece of military expenditure for which we should all be thankful!

POWER AMPLIFIER MODULES-TURNTABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

• PRICES INCLUDE V.A.T. • PROFESSIONAL SERVICE • FRIENDLY SERVICE • LARGE (A4) S.A.E. 80p STAMPED FOR CATALOGUE •

OMP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W) MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: *Independent power supplies with two toroidal transformers * Twin L.E.D. Vu meters * Level controls * Illuminated on/off switch * XLR connectors * Standard 775mV inputs * Open and short circuit proof * Latest Mos-Fets for stress free power delivery into virtually any load * High slew rate * Very low distortion * Aluminium cases * MXF500 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19"xH3 1/4" (2U)xD11"
MXF400 W19"xH5 1/4" (3U)xD12"
MXF600 W19"xH5 1/4" (3U)xD13"
MXF900 W19"xH5 1/4" (3U)xD14 3/4"

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH

OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: Bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches for each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SJDJ3400SE * ECHO & SOUND EFFECTS *

STEREO DISCO MIXER with 2 x 7 band B & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders, auto cross fade, Cue Headphone Monitor, 8 channel Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.




Price £144.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

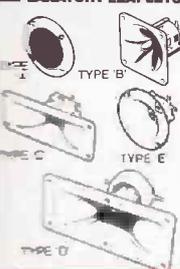Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
TYPE 'C' (KSN1016A) 2"x5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
TYPE 'D' (KSN1025A) 2"x6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

FM FLIGHT CASSED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complemented with heavy duty black covering. The enclosures are fitted as standard with top rails for optional loudspeaker stands.



POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz
12" FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR
12" FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR
 SPECIALIST CARRIER DEL. £12.50 PER PAIR
OPTIONAL STANDS PRICE PER PAIR £49.00
 Delivery £6.00 per pair

CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS
 150 WATTS (75 + 75) Stereo, 150W Bridged Mono
 250 WATTS (125 + 125) Stereo, 250W Bridged Mono
 400 WATTS (200 + 200) Stereo, 400W Bridged Mono
ALL POWERS INTO 4 OHMS
Features:
 * Stereo, bridgable mono * Choice of high & low level inputs * L & R level controls * Remote on-off * Speaker & thermal protection

OMP MOS-FET POWER AMPLIFIER MODULES SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to cut the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P



OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P



OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P



OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P



OMP/MF 1000 Mos-Fet Output power 1000 watts R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm.
PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz, PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (80p STAMPED) FOR COMPLETE LIST.

McKenzie and Fane Loudspeakers are also available.

EMINENCE:- INSTRUMENTS, P.A., DISCO, ETC

- ALL EMINENCE UNITS 8 OHMS IMPEDANCE**
- 8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £32.71 + £2.00 P&P
 - RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB.
 - 10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. PRICE £33.74 + £2.50 P&P
 - RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS97dB.
 - 10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. PRICE £43.47 + £2.50 P&P
 - RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB.
 - 12" 100 WATT R.M.S. ME12-100L GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. PRICE £35.64 + £3.50 P&P
 - RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB.
 - 12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB. PRICE £36.67 + £3.50 P&P
 - 12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. PRICE £46.71 + £3.50 P&P
 - RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 98dB.
 - 12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. PRICE £70.19 + £3.50 P&P
 - RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB.
 - 15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. PRICE £50.72 + £4.00 P&P
 - RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB.
 - 15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. PRICE £73.34 + £4.00 P&P
 - RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB.

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

- ALL EARBENDER UNITS 8 OHMS (Except EBB-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)**
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
 - 8" 50watt EBB-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £0.90 + £2.00 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB.
 - 10" 50WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB.
 - 10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P
 - RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.
 - 12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P
 - RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.
 - FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
 - 5 1/2" 60WATT EBB-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
 - RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.
 - 6 1/2" 60WATT EBB-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P
 - RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.
 - 8" 60WATT EBB-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 89dB.
 - 10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
 - RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 96dB.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

- 3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P
- FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P

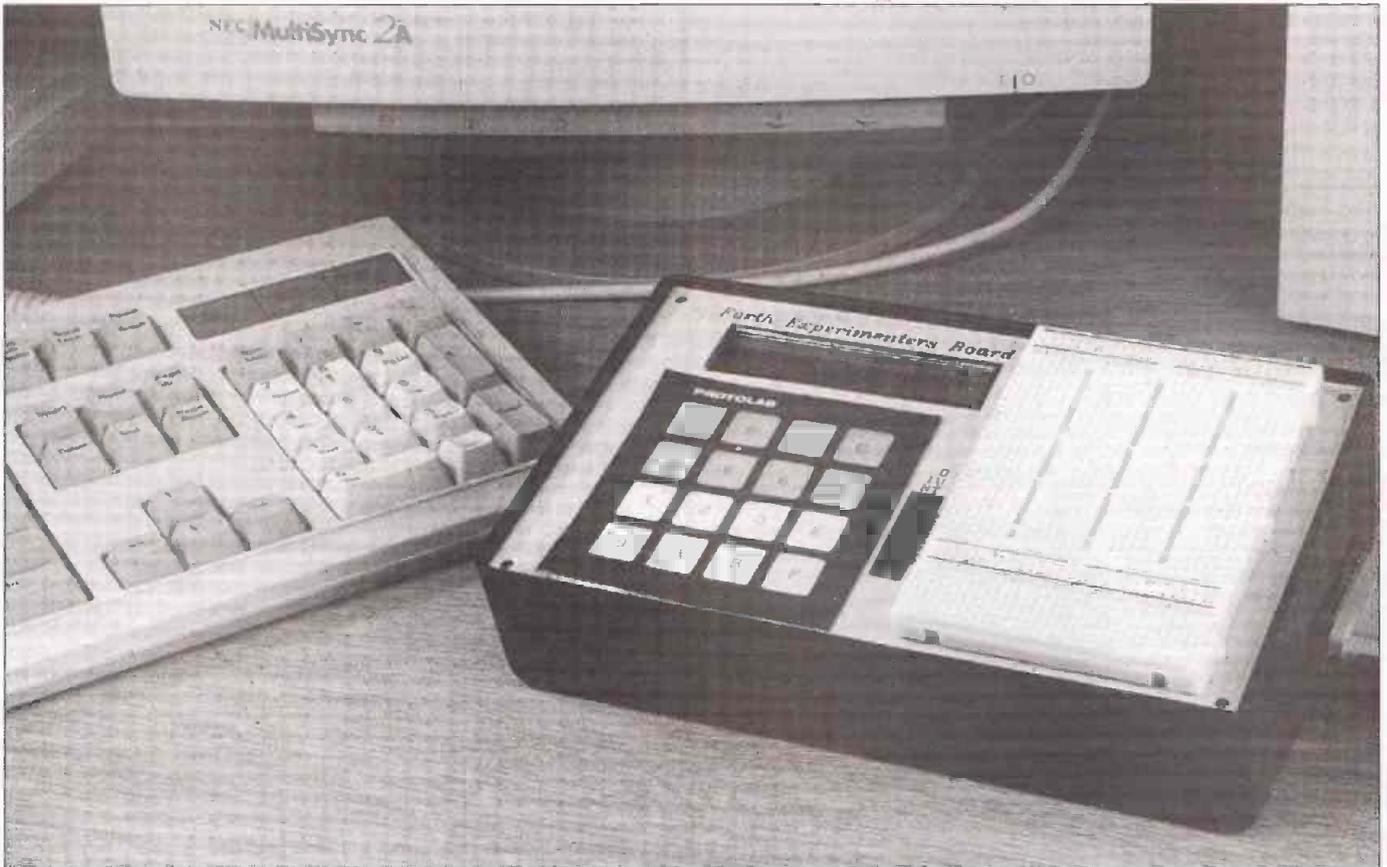


PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS
 UNITS 1 & 5 COMET WAY, SOUTHBEND-ON-SEA, ESSEX, SS2 6TR.
 Tel.: 0702 - 527572 Fax.: 0702 - 420243

POSTAL CHARGES PER ORDER £1.00 MINIMUM OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.

Computer controlled stepper motors



This month, Jim Spence looks at an application for the ETI Forth Experimenters Computer - using it to accurately control the rotation of a stepper motor.

Have you ever experimented with a stepper motor? Did it work? Were you pleased with the results? This is a practical article, the intention of which is to tell you how to use stepper motors and make them work for you in your application. Described is an unusual way of driving the ordinary stepper motor and obtaining a much improved performance. Stepper motors seem to be used everywhere - in printers, disk drives, robots, fruit machines, in fact anywhere where mechanical positioning is important.

This is good news for the average electronics enthusiast, if there is such a thing. Why is it good news? Well, you can pick up at a car boot sale, or better still at a Radio Rally, 'junk' disk drives and printers

for next to nothing. The old daisy wheel printers (if you can lift

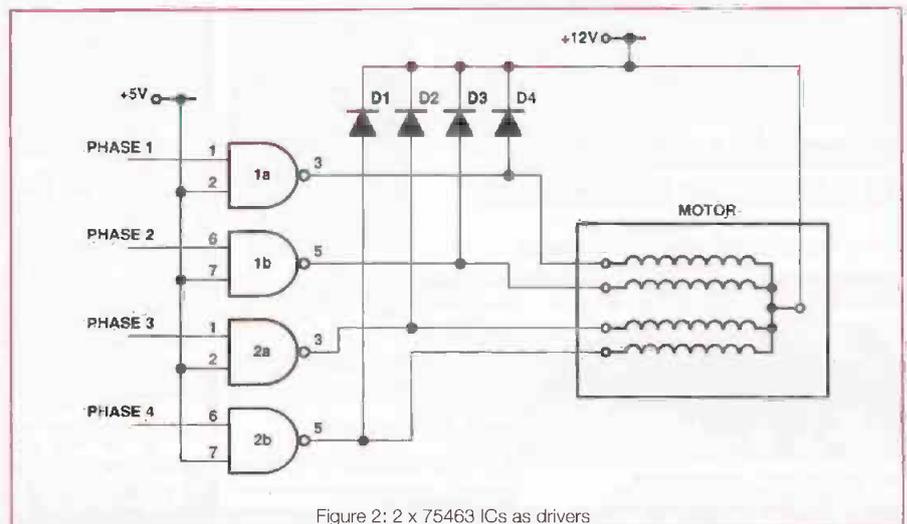


Figure 2: 2 x 75463 ICs as drivers

one) have about 5 stepper motors in and these would have cost a fortune to buy new.

Types of stepper motor

The two most common types of stepper motor are unipolar and bipolar. The type you are most likely to encounter is the unipolar, which is shown in Figure 1. They come in two types, 5 wire and 6 wire. Bipolar motors only have two windings and therefore 4 wires (Figure 1d), while modern motors have 8 wires and can be wired either as unipolar or bipolar (Figure 1c).

Before you can use one of these motors you must establish two things. Firstly the common connection, as in the case of Figure 1a and 1b, and secondly the sequence of the phases. The colours of the wires are of no help, as every manufacturer appears to have their own scheme.

The first step can be achieved with a meter. Usually, the motor windings will be between about 6 and 150 ohms. Obviously, the resistance between two windings will be twice that of the resistance between the common connection and a winding.

Having established the phases, you must determine which phase steps the motor to which position. Do this by wrapping a piece of stiff wire round the shaft of the motor, to act as a kind of clock hand or pointer. Connect each phase in turn to a power source and mark the top of the motor. You will easily establish the sequence of phases this way.

Typical Motor Characteristics

Basically, a stepper motor is a motor capable of revolving in fairly accurate discrete steps, a kind of digital motor if you like. Stepper motors have definite characteristics, they are good for some things but not for others. To begin with, they are not very fast in terms of RPM. An average stepper motor will go up to about 1000 steps per second if driven correctly and this translates to 150 RPM for a 1.8 degree per step motor, driven in half step mode. Now for a ballerina that's fast, but for a motor it isn't and it certainly wouldn't be suitable for use on the end of a garden strimmer! Having said that, modern motors are capable of quite reasonable speeds, as high as 10,000 steps per second without appreciable loss of torque.

Stepper motors also need special arrangements to make them work. You can't simply connect them up to a battery and watch them go round. As you will see later, the arrangements for driving this type of motor can make all the difference.

So what's the good news? Well, in spite of the special arrangements needed for driving, for positioning type applications they make life very simple because there is no need to have a constant feedback (as in closed loop). They can also be very accurate. For example, you can do things like move in extremely small increments. All of these options are simply not

possible or practical with an ordinary motor.

With these properties, the motor lends itself to 'positioning' applications such as plotters and CNC (computer numerically controlled) machines, the main advantage being that there is no feedback required as to the position of the machine. This is known as an open loop system. For example, all you would need to do is to tell the motor to advance a certain number of steps and this would cause an exact and repeatable location to be realised.

In practice there is always some kind of feedback, even in an open loop system. Take a pen plotter. At switch on, how would the controller know where the pen was if there wasn't a 'home' position? There could also be an intermediate monitoring position so that whilst plotting, if this position was crossed. The controller could work out if it should have been there or not, issuing an error if an anomaly occurred.

The point is that in a system like this, the monitoring is minimal. In contrast, a closed loop system requires a constant update of the position. A closed loop system is 'safer' in the sense that if external forces interfere with the motor, e.g. you stick your hand in the machine, the effects are known immediately and corrective action can be taken, whatever that may be. An open loop system would not know if anything had gone wrong until the monitoring position, if any, which may be too late.

Fundamentals of stepper motor control

Although this text is of a practical nature, there are a few fundamental things about stepper motors which must be covered in order to make sense of the rest of the text and to enable you to put your 'junk' motor to good use.

Steps

Most stepper motors, you are likely to encounter, will step either 7.5° or 1.8° per step. This will give 48 and 200 steps per revolution respectively. Ninety degrees per step is also common but these are usually geared down. Obviously, the smaller the step, the better the resolution that can be obtained for a given gear ratio.

Pull-in and Pull-out Rate

The pull in rate is the maximum switching rate at which a loaded motor will start without losing steps. The pull-out rate is the maximum switching rate a loaded motor can go at. The pull-in rate is always lower than the pull-out rate and from this statement it can be seen that, if you want to drive a motor at its full speed, the pull-out rate, then you must progress to this, stepping slowly at first and increasing gradually to the pull-out rate. This is called ramping.

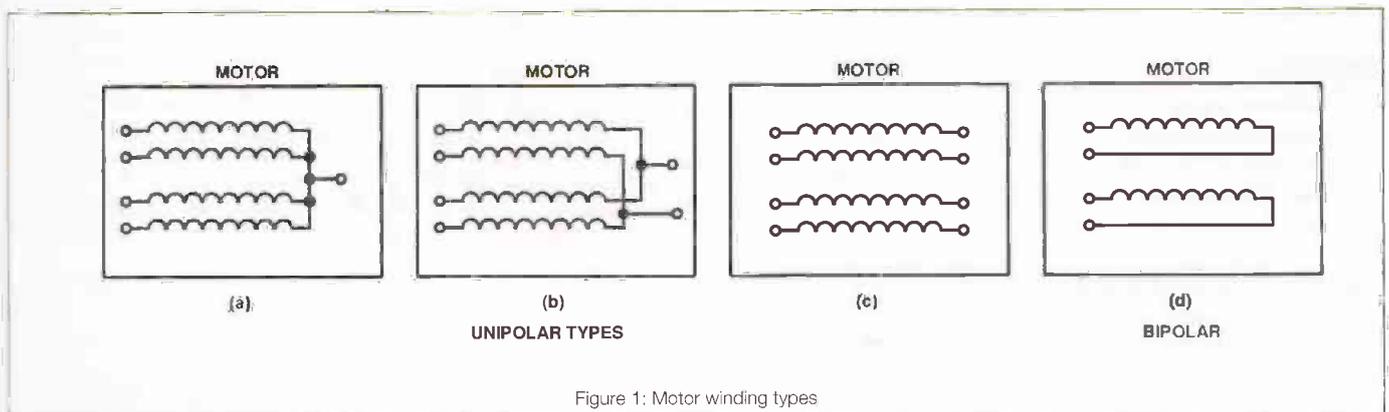


Figure 1: Motor winding types

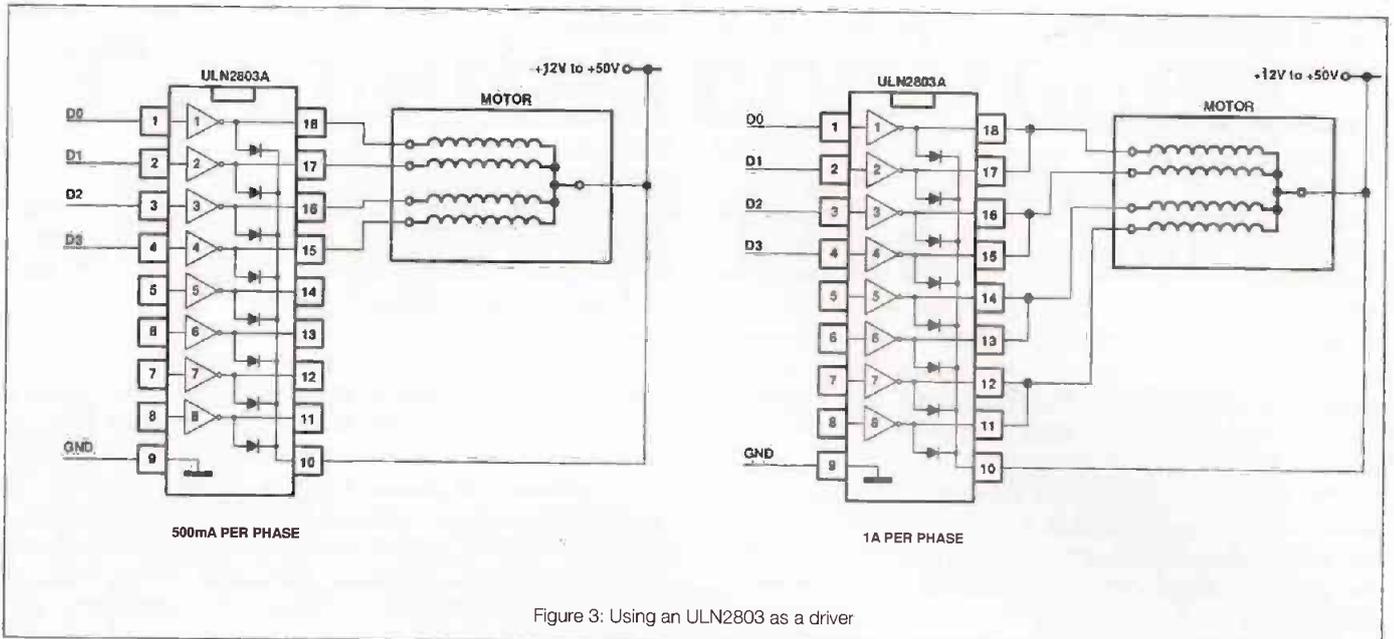


Figure 3: Using an ULN2803 as a driver

Resonance

Certain operating frequencies cause the motor to resonate. You can actually hear this and it may cause the motor to lose steps. These frequencies should be avoided.

General

There are, of course, many other parameters but for practical purposes the above will suffice. It is also important to realise that the motor will behave very differently when installed in a machine than it does when it is driving nothing.

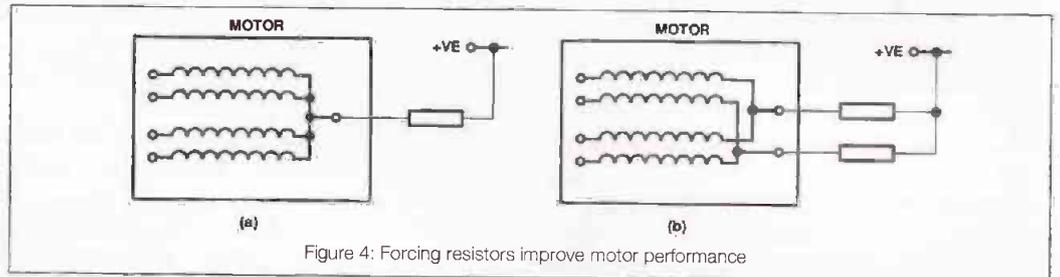


Figure 4: Forcing resistors improve motor performance

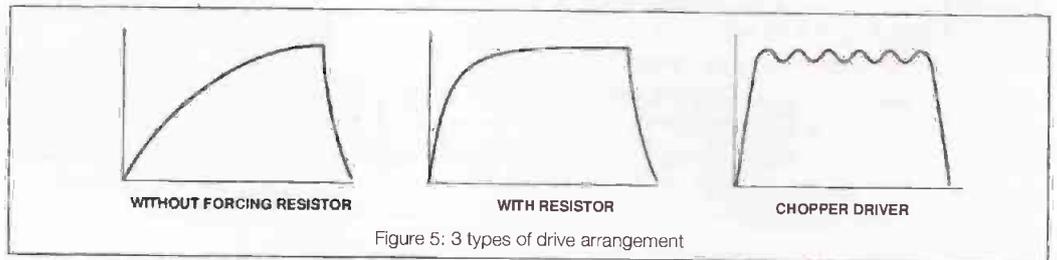


Figure 5: 3 types of drive arrangement

Motor drivers

How you drive a stepper motor can make all the difference. You may be able to stop a motor with your thumb and finger when it is driven by one method, but take the same motor and drive it differently and it will be unstoppable and probably consume less average current.

Unipolar

As mentioned earlier, there are two broad types of motor - unipolar and bipolar. This, however, refers as much to the way motors are driven as to the way the motors are constructed. Some motors are designed to be driven either way. For example Figure 1c. The term unipolar, meaning

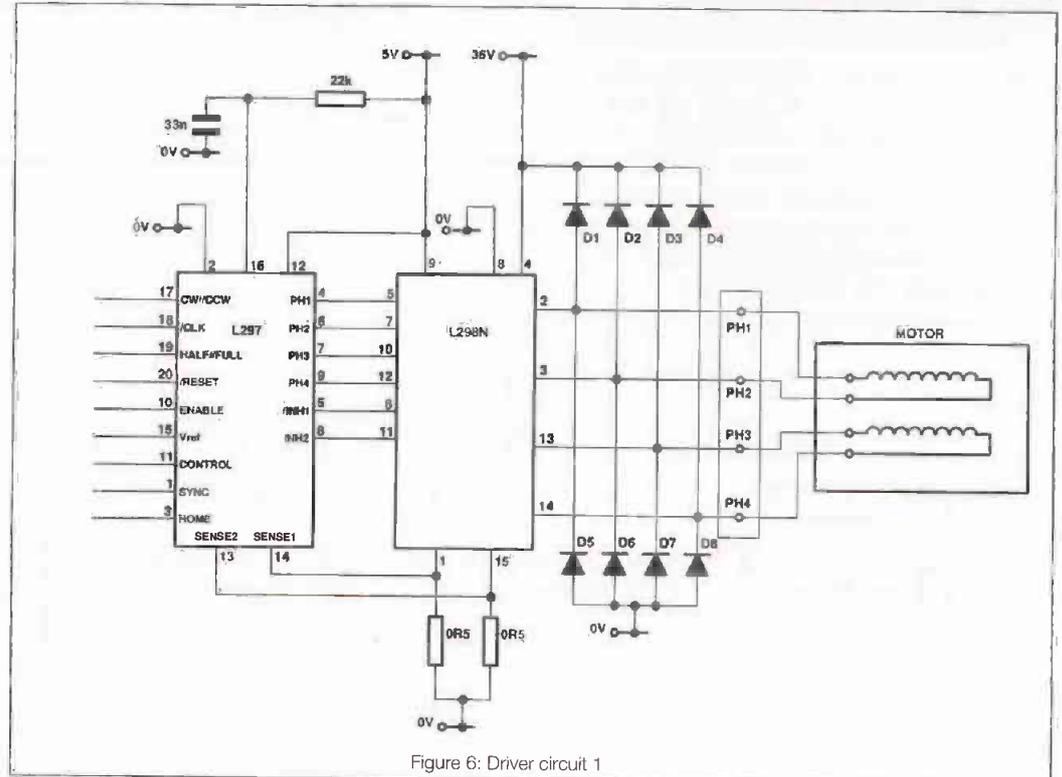


Figure 6: Driver circuit 1

one direction through the windings.

The old full height 5 1/4in disk drives have a small 12V stepper motor to position the heads. This is driven very simply by two 75463 driver chips (see Figure 2). This is a very simple circuit indeed and I am sure that no attempt is made to get the maximum performance from the motor. However, for this application it obviously fits the bill.

A more practical and modern circuit for driving a stepper motor this way is to use an octal driver chip, ULN2803. This incredible device has eight Darlington driver outputs capable of sinking 500mA each, at up to 50V. The outputs may also be paralleled to give greater output current and all this for less than 21 (see Figure 3). Be warned here however, the device is an 18 pin DIL with no heat sink, so don't put your finger on the top to see if it's getting warm. I still have a blister!

More performance

The main problem with the circuits shown so far is in obtaining the full pull-out rate (maximum speed). If the motor is fed with its rated current at a low 12V voltage, it may take, say 10 ms, for the winding to become fully energised. This will be the determining factor for the maximum speed. In order to get more performance, the motor can be driven with a higher voltage but through a resistor to limit the current. The effect of this is to reduce the time taken for the winding to reach its maximum energy and thus increase the maximum speed. It is common practice to use a resistor, which is generally called a Forcing

resistor. Using a resistor also gives improved torque and as a rule the higher the value the resistor, the better the improvement, providing the current is maintained.

The jargon used is L/nR, where nR is the sum of the external resistance plus the winding resistance R. The idea is to maintain the rated current but with a higher voltage. For example a 20 Ohm 10V motor (0.5A per phase) driven in L/4R mode would have a 60 Ohm series resistor (60+20=80=four times phase resistance) and be driven with a 40V supply, thus maintaining the 0.5A. See Figure 4.

It is normal practice for manufacturers to quote torque in the performance figures using a particular L/nR value.

The forcing resistor needs to be fairly hefty and the above example would require a 20W resistor which would get quite hot, therefore probably requiring a heat sink. This is the main problem with the forcing resistor arrangement, it is very inefficient. The alternative is to dispense with the resistor but still use a high voltage and monitor the current in the phase winding. Just as the current begins to exceed the rated value, switch off the supply. As the current falls switch the supply back on again, so on and so forth at high speed. This is called chopping, see Figure 5. This is the best arrangement of all and because of the near ideal waveform, gives very much improved performance. For unipolar types of drive, it is usually adequate to use either direct or L/nR types of driving arrangement.

Bipolar

This method of driving stepper motors gives quite a remarkable improvement in performance over unipolar. The phases need to be driven in opposite directions and so the driver circuit needs to be able to source current as well as sink it. In the unipolar arrangement, the unwanted phase is simply switched off. In the bipolar arrangement the phase is either connected to ground or +ve. The main disadvantage, in the past, has been the difficulty, and complexity of the driving circuits, but there are now ICs available which take care of all the driving complexities.

Chop It

The maximum performance which can be obtained from a stepper motor will be achieved with a bipolar circuit and some

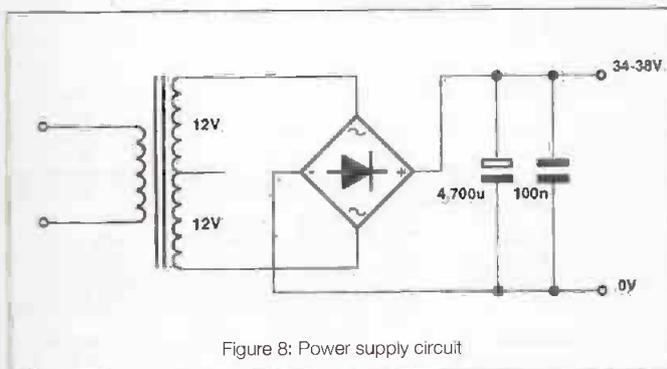


Figure 8: Power supply circuit

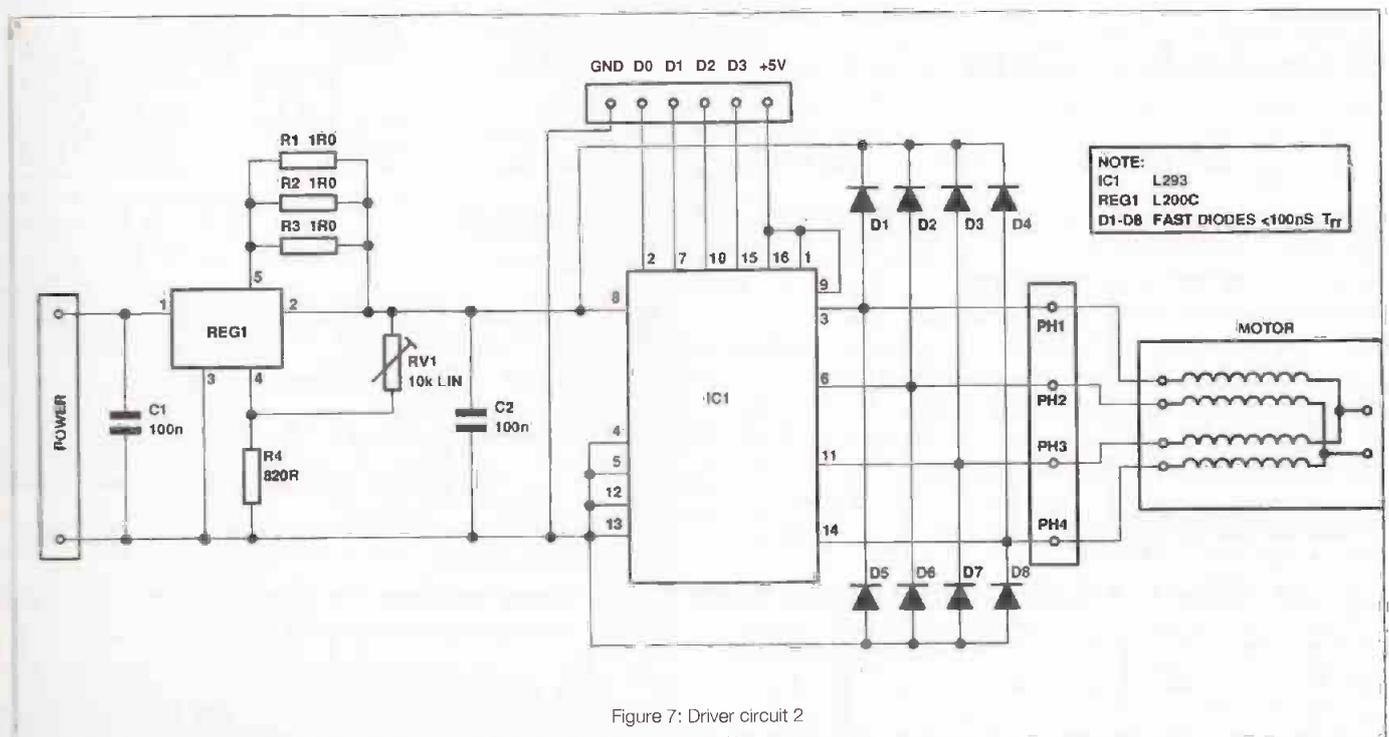


Figure 7: Driver circuit 2

form of chopping mechanism driving a motor designed for bipolar operation. This can be achieved fairly simply using just 2 IC's, Figure 6. The first IC (L297), is the controller IC and the second (L298N) is the driver IC. This is very similar to the L293, except the package enables it to handle greater currents. The two sense lines monitor the voltage across the motor windings and cut off the current at a predetermined value. This value is set by the input Vref. It is beyond the scope of this article to go into the details of this circuit, as the circuit proposed in Figure 7 performs almost as well. For a lower cost system, the added expense of the chopper circuit will make no practical difference.

The Circuit

The philosophy behind the circuit in Figure 7 was to construct a general purpose high performance stepper motor driver, capable of working with as many different types of motor as possible. The circuit is configured to drive a bipolar motor, but as you can see, a unipolar motor is shown connected. We can get away with this by leaving the common connections unconnected. The circuit will even work with a 5 wire type although some losses can be expected and the 5 wire motor may not reach its maximum performance. It will, however, perform far better with this circuit than it will with the unipolar circuit.

IC1 is a general purpose motor controller capable of supplying 1A per channel, which is more than adequate for a lot of motors. The board has an on board variable voltage regulator which will need a heat sink. This is so that the current can be adjusted to suit the particular motor. Also, there is a Link on the board which is for an ammeter. Four output lines from the computer are needed as well as +5V and ground. This is provided by the 6 way connector. Only 4 wires are needed for the motor (see How It Works) and two pins are provided for the power input.

In practice, the circuit will supply about 1A for short periods without getting too hot. 300 to 500mA is a realistic figure for continuous operation and you will be surprised how powerful some motors can be at this current.

Power Supply

Modern stepper motors have winding resistances as low as 1 to 2 ohms. A low voltage supply can therefore provide adequate currents. Older, cheaper motors however, have winding resistance's of 50 ohms and up. Connecting unipolar motors to run in bipolar mode effectively doubles the resistance. The practicality of the above means that to drive motors with a high resistance, a high voltage supply is needed. The circuit shown in Figure 8 will provide about 35V, which is the maximum rating of IC1.

How It Works

REG1 is a virtually indestructible variable voltage regulator. Resistors R1 to R3 limit the current to about 1.5A and VR1 controls the voltage output, which will swing between 3 and 36V. C1 and C2 help to reduce the noise caused by switching the motor windings. IC1 is an L293 which is intended as a general purpose motor driver, not just stepper motors. Diodes D1 to D8 prevent the normal voltage spikes exceeding the 0V and 36V rails, usually associated with inductive loads. There exists a variation of the IC, L293D, which has the diodes already built in. If you are using this chip, then the diodes are unnecessary.

As mentioned earlier, only 4 wires are required. The common connections are simply not used (see Figure 7) Figure 7 shows a 6 wire unipolar motor connected to IC1, ready to be driven in bipolar mode. Because current flows through two phases, for example from phase 1 to phase 3, rather than from phase 1 to

common, twice as much torque is available. If phase 1 and phase 3 are opposite each other, physically on opposite sides of the motor, one will be pushing and the other will be pulling so to speak. This gives double the torque that can be obtained from a unipolar system. A five wire motor also works driven by this method. Although current is flowing through the other two, unused phases, it has the same magnitude and direction. They therefore cancel each other out and do not mechanically affect the operation of the motor. This is not ideal, but it does give good results. A bipolar motor only has four wires and this circuit is ideal for driving one of these.

Construction and Testing

Use of the PCB is highly recommended, unless very low currents are to be used. You will notice that the PCB has large areas of copper connected to the ground pins and this is to help dissipate the heat from the IC. The chip is physically bonded to the ground pins for this purpose.

It goes without saying that for once an IC socket should not be used. Solder in all the components except the IC, taking particular care over the orientation of the diodes.

Connect up a power supply and check that the regulator IC is working and varies the voltage as you turn VR1. If everything is functioning correctly, solder in the IC. Make absolutely certain you get it the right way round.

After completing the board, connect a motor to the 4 way connector, a suitable power supply to the two pins, +5V and ground, to the six way connector and an Ammeter across the pins marked Link.

With nothing connected to D0-D3, there should be no current flowing. Connect D0 to the +5V pin and adjust VR1 to give about 150mA. The motor should jerk at this point, indicating current flowing through it. The actual current depends very much on the type of motor you have connected.

150mA is a fairly safe starting point.

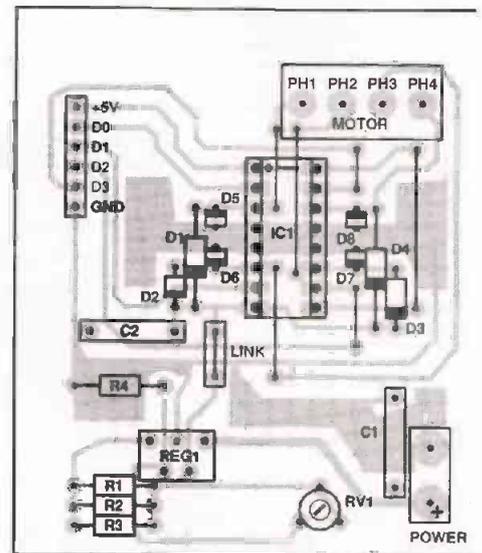


Figure 9: PCB component overlay

PARTS LIST

IC1	L293 or L293D
REG1	L200CV
R1, 2, 3	1R 0.25W
R4	820R 0.25W
VR1	10K lin pre-set
C1, 2	0.1µF
D1-D8	BYW98-100 *
4 x PCB pins, 1 x 6 way PCB connector, 2 x PCB 2 way terminals	
* Diodes must have a Trr of less than 200ns, not needed if type L293 is used.	

Next month ...

we will look at the software for driving the stepper motor circuit described in this month's article.

Surplus always
wanted for cash!


THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

LOW COST PC's - ALL EXPANDABLE - ALL PC COMPATIBLE

THE OFFER OF 1994!

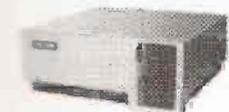


SPECIAL BUY AT 286 40Mb HD + 3Mb Ram

LIMITED QUANTITY only of these 12Mhz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 30 DAY Full Guarantee. Ready to Run!
Order as HI GRADE 286

ONLY £169.00 (E)

Optional Fitted extras: VGA graphics card	£29.00
2x 5 1/4" floppy disk drive (instead of 1.2 Mb)	£32.95
1000 Ethernet (thick, thin or twisted) network card	£49.00

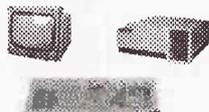PC SCOOP COMPLETE COLOUR SYSTEM ONLY £99.00



A massive bulk purchase enables us to bring you a COMPLETE ready to run colour PC system at an unheard of price! The Display Electronics PC99 system comprises of fully compatible and expandable XT PC with 256k of RAM, 5 1/4" 360k floppy disk drive, 12" CGA colour monitor, standard 84 key keyboard, MS DOS and all connecting cables - just plug in and go! Ideal students, schools or anybody wishing to learn the world of PC's on an ultra low budget. Don't miss this opportunity. Fully guaranteed for 90 Days.

Order as PC99COL £99.00 (E)

Optional Fitted extras: 640k RAM	£29.00
2nd floppy drive, specify 5 1/4" 360k or 3 1/2" 720k	£29.95
Above prices for PC99 offer ONLY.	



Computer Controlled Laser Video Disk Player

One of the most amazing surplus deals that we ever been able to offer you! The Philips VP410 LaserVision player, in as new condition, unit features full computer control, Plays standard 12" LaserVision disks with startling visual and audio quality in two channel stereo or mono. When controlled by a computer, it may also be used as a versatile high quality storage / retrieval medium. It will play back either LaserVision CAV (active play) or CLV (Long Play) discs (which covers most types of commercially available video discs). Some of the many features of this incredibly machine are:
RS-232 INTERFACE RGB / COMPOSITE VIDEO OUTPUT
BNC-SCART INTERFACE PAL / RGB DECODER
IR-WIRED REMOTE CONTROL FAST RANDOM ACCESS

SPECIAL PURCHASE Only £399.00 (F)

FLOPPY DISK DRIVES 3.5" - 8"

5.25" from £22.95 - 3.5" from £24.95
Massive purchases of standard 5.25" and 3.5" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3.5" supported on your PC)

Panasonic JU363/4 720K or equivalent	£24.95(B)
Mitsubishi MF355C-L, 1.4 Meg. Laptops only *	£36.95(B)
Mitsubishi MF355C-D, 1.4 Meg. Non laptop	£29.95(B)
Teac FD-55GFR 1.2 Meg	£29.95(B)
BRAND NEW Mitsubishi MF501B 360K	£22.95(B)
* Data cable included in price.	
Shugart 800/801 8" 5S refurbished & tested	£195.00(E)
Shugart 851 8" double sided refurbished & tested	£250.00(E)
Mitsubishi M2894-63 8" sided switcheable NEW	£250.00(E)
Mitsubishi M2896-63-02U 8" DS slimline NEW	£285.00(E)
Clari 8" drives with 2 mbyte capacity housed in a smart case with external power supply. Ideal as exterior drives!	£499.00(F)

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte hard disk storage! Full industry standard SMD interface. Ultra hi speed data transfer and access time, replaces Fujitsu equivalent model complete with manual. Only £299.00 (E)
FUJITSU FK-309-26 20mb MFM I/F RFE £59.95(C)
CONNER CP3024 20 mb IDE I/F (or equiv) RFE £69.95(C)
CONNER CP3044 40mb IDE I/F (or equiv) RFE £99.00(C)
RODIME R03085S 70mb SCSI I/F (Mac & ACM) £129.00(C)
MINISCRIBE 3425 20mb MFM I/F (or equiv) RFE £49.95(C)
SEAGATE ST-238R 30 mb ML I/F Refurb £69.95(C)
CDC 94205-51 40mb HH MFM I/F RFE tested £89.95(C)
FUJITSU M2322K 160Mb SMD I/F RFE tested £195.00(E)
Hard disc controllers for MFM, IDE, SCSI, RLL etc. from £16.95

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit containing all electronics ready to plug into a host of video monitors made by manufacturers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD and many more. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable VHF/UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPER-BAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most types of monitor. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input type monitors	£32.95
TELEBOX STL as ST but with integral speaker	£36.50
TELEBOX MB Multiband VHF-UHF-Cable- Hyperband tuner	£69.95
For overseas PAL versions state 5.5 or 6mhz sound specification.	
For cable / hyperband reception Telebox MB should be connected to cable type socket. Shipping code on all Teleboxes is (B)	

FANS & BLOWERS

SUBSUSHI MMF-D6D12DL 60 x 25 mm 12V DC	£4.95 10 / £42
SUBSUSHI MMF-09B12DH 92 x 25 mm 12V DC	£5.95 10 / £53
FAIRCHILD 12-3.5.92 x 18 mm 12V DC	£7.95 10 / £59
EL-EQUIP 120 x 38mm AC fans - tested specify 110 or 240 V	£6.95
EL-EQUIP 90 x 38mm AC fans - tested specify 110 or 240 V	£5.95
EL-EQUIP rack mount 10 x 19" fan tray specify 110 or 240V	£45.95
EL-EQUIP 225 1900 rack mnt 3U x 19" Blower 110/240V NEW	£79.95
Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL	

IC'S TRANSISTORS DIODES

OBSOLETE - SHORT SUPPLY - BULK
5,000,000 items EX STOCK
For MAJOR SAVINGS - SAE or CALL FOR LATEST LIST

Issue 12 of Display News now available - send large SAE - PACKED with bargains!



LONDON SHOP
Open Mon-Sat 9:00-5:30
215 Whitehorse Lane
South Norwood
LONDON SE25

DISTEL © The Original
FREE On line Database
Info on 1000's of items
V21,V22, V22 BIS
081 679 1888

ALL MAIL & OFFICES
Open Mon-Fri 9.00-5.30
Dept ET1. 32 Biggin Way
Upper Norwood
LONDON SE19 3XF

ALL ENQUIRIES
081 679 4414
FAX 081 679 1927



All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Carriage charges (A)=£3, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. TOP CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1994. E & O E.

Turbo speed indicator

In this month's PC project, John Lanigan shows how to build a simple little display which will indicate how fast your PC is running.



The old IBM XT spends more time in bits on my desk than in one piece running software. It's the one that gets all the tinkering, adding this,

tweaking that. It started out as a Portable with twin floppy drives and a built-in mono monitor. Now it is in a new case with updated power supply, 3-1/2in and 5-1/4in floppies, hard disk,

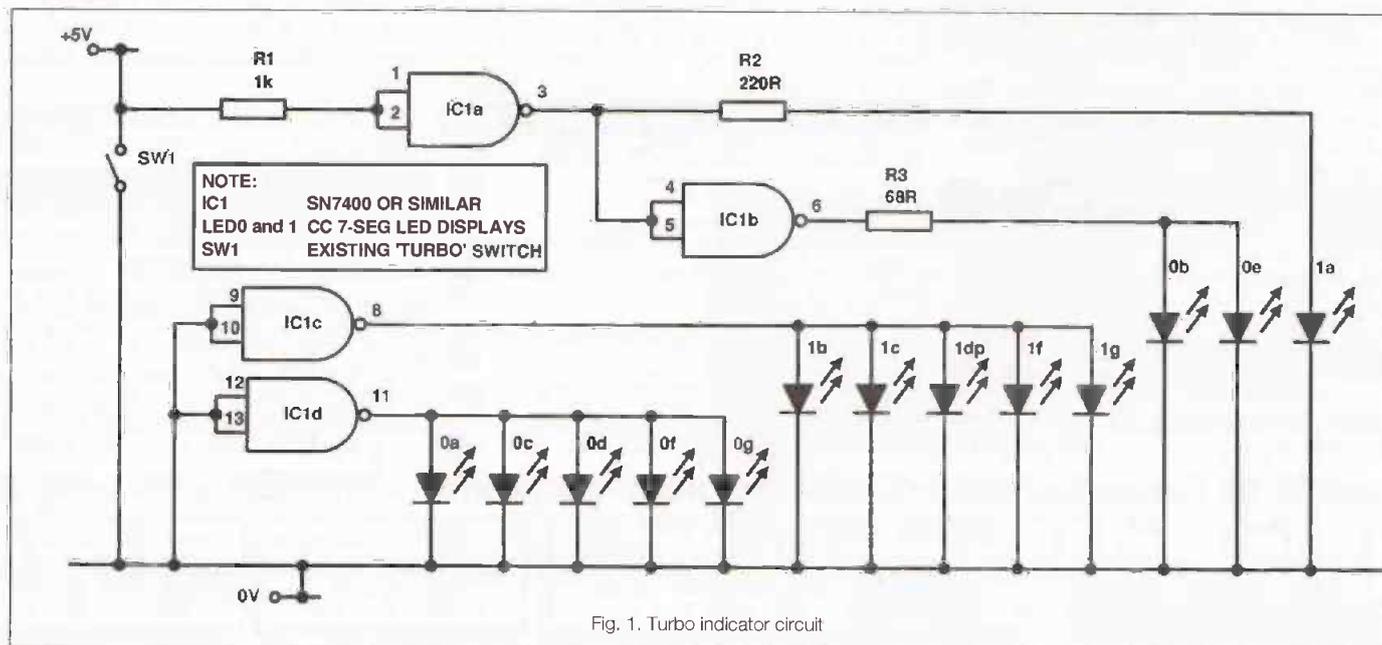


Fig. 1. Turbo indicator circuit

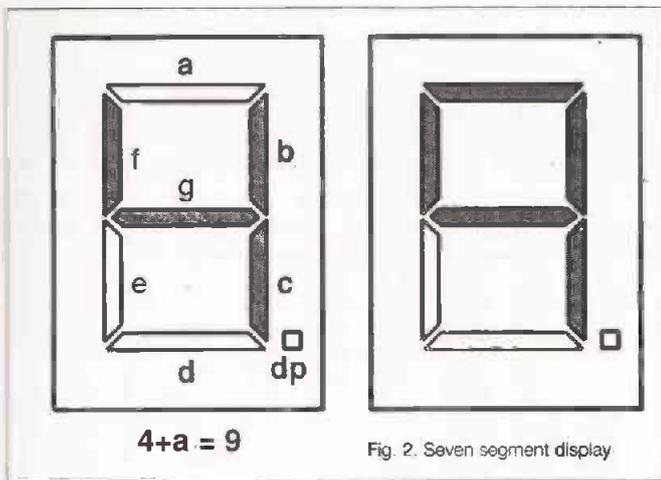


Fig. 2. Seven segment display

colour display and turbo motherboard. It was while I was putting in the turbo board that I thought about digital speed indicators, like those on some of the flashier AT clones. It is not necessary to build a counter and decoder-driver circuit to display the two speeds at which turbo boards normally run. All we need is a switching element (a turbo switch for example) and a little hard-wired logic.

The 7-segment display provides a crude but universally recognisable rendering of the digits 0 to 9 by illuminating 2 or more bars of its 7 bar array. For any given 2 digits, several of the illuminated bars will be the same. For example, 0 and 8, where the only difference is the centre bar. The board I used for the XT had a base speed of 4.77 and in turbo mode 9.54 MHz. To show 4.8, and in turbo mode 9.5, 10 of the segments involved remain unchanged, including the decimal point of course. A 4 becomes a 9 by adding one more segment and an 8 is made into 5 by removing 2 segments (see Figure 2). If we can hold the unchanging segments on and switch only those that change, we can produce a display of the CPU speed with a simple logic circuit.

How It Works

In the diagram (Figure 1), with SW1 open, the 2 inputs of IC1a are held high, giving a low output. This keeps LED1a turned off and at the same time holds the inputs to IC1b low. A low on both inputs switches IC1b output to high, so lighting the segments LED0b and 0e. A truth table is given in Figure 3 and the display segments are identified in Figure 2.

IC1c and IC1d have permanent high outputs, because their inputs connect to the 0V line. These outputs drive the segments LED0a, c, d, f, g and LED1b, c, d, p, f, g. They are the permanent segments.

Closing SW1 pulls IC1a inputs low and consequently the output goes high, lighting segment LED1a. The same 'high' connects to the inputs of IC1b causing its output to go low and turn off the segments LED0b and 0e.

The 2 resistors, R2 and R3, in the lines to the switched segments adjust their brightness to

match that of the permanent segments. This is necessary because 5 of the permanent segments are driven by each of the remaining 2 gates. If the current to the switched segments was not limited they would be noticeably brighter than the rest.

Assembly and Testing

Before starting this project you should determine the switching levels on your turbo switch, SW1. Almost certainly, it will be switching between 0 and 5V, but it is always more comfortable to be sure. You need to find the 'high' side of the switch for connecting up anyway. You can check this with a 20k-ohm/V meter set to the 10V range. You should connect the common lead to a known ground such as the chassis metalwork. If you have more than 5V, (up to 15V), on your turbo switch, you must use a potential divider network to reduce it to 5V. Use high value resistors to minimise the current drawn down the network.

Assembly should not present any problems with only a few components. Start with the low profile parts, the resistors, then the IC followed by the 7-segment displays. While soldering, do not concentrate on one device at a time. Move from one to another as this will avoid overheating and possible damage. This is particularly important if you have difficulty with one

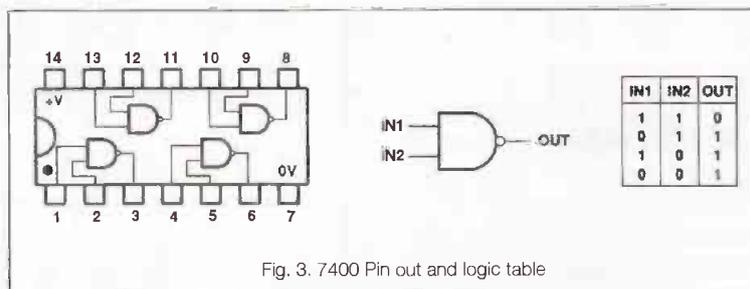


Fig. 3. 7400 Pin out and logic table

joint. Do not keep trying to complete it in one go, move to another component so that the first can cool.

When all the parts and the leads are in place, connect to a DC supply set at less than 5V. I usually use 3.5 or 4V, in case I have forgotten a current limiting resistor that should be protecting something either expensive or impossible to replace on a Sunday afternoon! Now connect the lead that goes to the turbo switch, SW1, to a 10k resistor and then to the supply. If you get the expected response - a dim 4.8 on the displays - you can take the supply up to 5V. Grounding the lead to SW1 should change the display to 9.5.

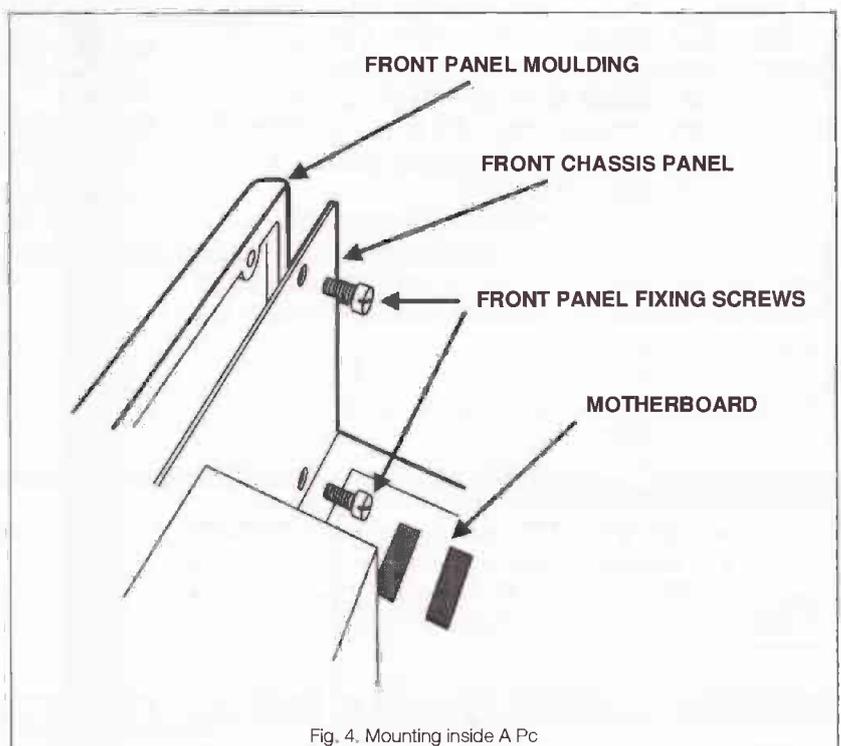


Fig. 4. Mounting inside a PC

LED Shot?

If the circuit does not perform as expected, trace the connections on the board and compare to the diagram. If you don't have a display at all, even when you turn up to 5V, then switch off and start checking the power supply connections.

Meaningless shapes or unexpected numbers on the display mean that the connections to the segment pins are incorrect. If you are using a socket for the IC and/or displays, then look carefully to ensure there are no bent pins. Of course, you didn't insert ICs the wrong way around did you? (Yes so did I.)

Those of you in-the-know will have realised that NAND gates are not essential for this project. It will work perfectly well with inverters, like SN7414, as that is exactly how a NAND gate behaves when both inputs are connected together. The 7400 however, has just the right number of gates and it was on the top of the 'bits box' when I started work on the prototype.

Some applications may need to show different figures from those given, but the How It Works section should allow the confident beginner to alter the circuit to display any value from 0.0 to 99.

Micro Surgery

It is not possible to describe fitting the board into all of the possible case types. They are, however, largely similar and the metalwork should not be too difficult.

Most cases have a lift and slide-off top, secured with a number of screws around the base of the unit. Under this is a chassis of sheet steel to which most of the sub-assemblies fix. The front panel moulding is held by screws to the front of the chassis from inside (see Figure 4), so some of the peripheral devices and driver cards may have to be removed first. There is usually a void between the front panel and the metalwork to which it mounts. This is where we will be fitting the new circuit board. You need to find a place for the circuit board that puts the 7 segment displays near to the front panel moulding. It may be necessary to mount the board on stand-offs or spacers, depending on the distance from the moulding to the chassis. The prototype was mounted on a sub-chassis that eventually made it easier to fit. If possible, pick a space where there is some room for a little adjustment. This will allow you to align the board/assembly when all the surgery has been completed.

When you are satisfied with the position of the board, fit it temporarily and measure from a fixed point on the metalwork, such as one of the holes for the front panel moulding fixing screws, to the LED display. Take care, as this dimension locates the cut-out in the front panel. Mark out the hole on the front of the panel and cut it out.

This is best done by drilling in the corners and cutting between them, then filing or scraping to your marked lines. Better still, if you know a toolmaker or machinist, ask them to do it for you, because the results of any poor craftsmanship will be visible on the front panel!

To finish off the front panel, cut a piece of tinted Perspex and either glue or heat-stake (melt the panel and the Perspex together with a soldering iron) it in place, over the hole. If you have been unlucky cutting the hole and have made less than a perfect job, it may be useful to fix the window on the outside. In this case, you will have to glue it of course. A useful 'dodge' is to use a bezel to cover the hole, so it is not so important to cut a good hole. With the front panel back on, you will need to adjust the position of the circuit board to align it with the window.

There are 3 connections to make - to SW1, the 5V and 0V lines. The supply is fairly easy just connect to the nearest disk

drive power supply but make sure you don't pick the 12V line! I use a lot of 5A screw or block connectors for this sort of thing. For the switch, it is probably easiest to solder directly to the switch terminal. If you have one of the older PCs whose hard disk drives do not self park on power off, park your disk heads before dismantling or moving the case. This precaution will save you from considerable anguish later. Do not use the switch lead for your 5V supply. It may work, but more likely you will be trying to draw more current than was expected of the switch.

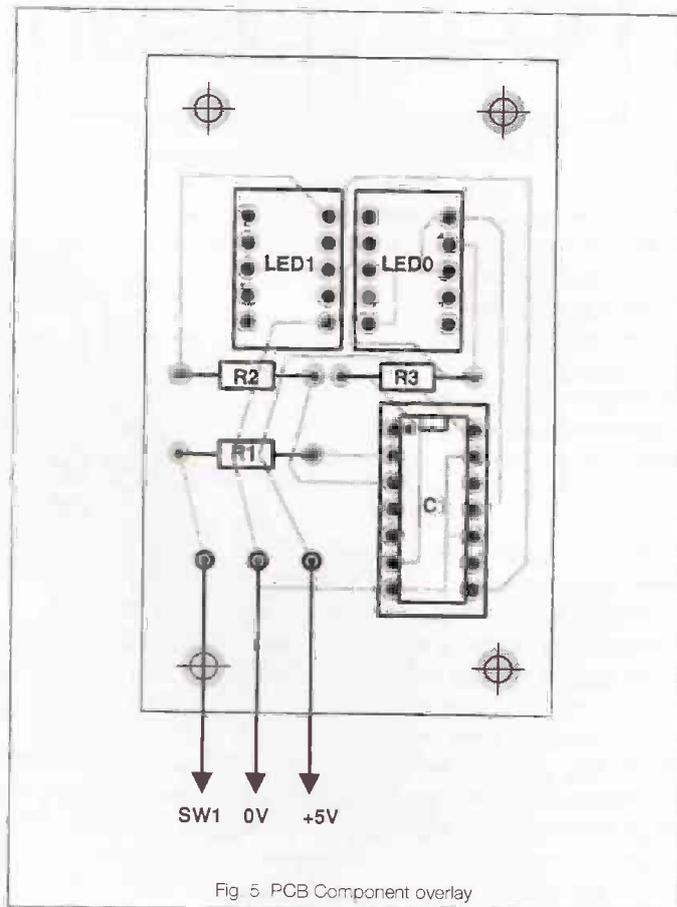


Fig. 5 PCB Component overlay

PARTS LIST

None of the components are difficult to obtain. Only the 7-segment displays are important in that they are low current, high brightness types.

Resistors

R1	1k
R2	220R
R3	68R
(all 1/8 W 5% carbon film)	

Semiconductors

C1	SN7400	4 2-input NAND gate
LED0 and 1		low current, high brightness, common cathode 7-segment LED display (MAPLIN QY54J)

Miscellaneous

PCB or suitable Veroboard
Machine screws, nuts, washers and spacers
Connecting wire



ESR ELECTRONIC COMPONENTS



Station Road, Cullercoats,
Tyne & Wear NE30 4PQ
Tel. 091 251 4363 Fax. 091 252 2296

741S-Series		4000 Series		TRANSISTORS		LINEAR ICs		SOLDERING IRONS		RF CONNECTORS			
74LS00	£0.22	4000	£0.17	2N1613	£0.31	BC186	£0.33	B0534	£0.47	Antex Soldering Irons		BNC Solder Plug 50R	£0.93
74LS01	£0.14	4001	£0.21	2N1711	£0.26	BC204C	£0.72	B0535	£0.50	M12 Watt	£8.18	BNC Solder Plug 75R	£0.96
74LS02	£0.29	4002	£0.17	2N1893	£0.29	BC206B	£0.72	CA555	£0.22	C15Watt	£8.18	BNC Chmp Plug 50R	£0.66
74LS03	£0.14	4006	£0.40	2N2216A	£0.28	BC207C	£0.72	CA741CE	£0.28	G18Watt	£8.41	BNC Solder Plug 75R	£1.08
74LS04	£0.14	4007	£0.28	2N2219A	£0.25	BC208	£0.72	CA747CE	£0.39	CS17Watt	£8.41	BNC Solder SKT	£1.08
74LS05	£0.14	4008	£0.31	2N2222A	£0.18	BC209A	£0.72	CA3046	£0.39	XS25Watt	£8.41	BNC Chassis SKT	£0.80
74LS08	£0.23	4009	£0.19	2N2646	£0.80	BC212	£0.08	CA3080	£0.72	ST4 Stand	£2.97	PL259 5.2mm	£0.68
74LS09	£0.14	4010	£0.23	2N2904A	£0.25	BC212L	£0.08	CA3130	£0.36	35Watt Gas Iron	£11.58	PL259 11mm	£0.62
74LS10	£0.14	4011	£0.26	2N2905A	£0.23	BC212LB	£0.08	CA3130E	£0.36	Low Cost 15 Watt Iron	£3.93	RND UHF socket	£0.68
74LS107	£0.21	4012	£0.16	2N2967	£0.20	BC213	£0.08	CA3240	£0.22	Desolder Pump	£3.00	SQR UHF socket	£0.45
74LS109	£0.21	4013	£0.21	2N2926	£0.16	BC213L	£0.08	CA3240E	£0.22	Antistatic Pump	£4.25	F Plug RGS	£0.30
74LS11	£0.17	4014	£0.30	2N3053	£0.27	BC214	£0.08	CA3240E	£0.22	Clear-Drawing (A4 size)	£7.40	N Plug RGS	£1.60
74LS112	£0.21	4015	£0.30	2N3054	£0.90	BC214L	£0.08	CA3240E	£0.22	1mm 3 Way Solder	£0.62	N Socket RGR	£1.40
74LS113	£0.21	4016	£0.18	2N3055	£0.62	BC237B	£0.08	CA3240E	£0.22	Desolder Braid	£0.87	BNC Crmp Piers	£17.40
74LS114	£0.21	4017	£0.35	2N3440	£0.50	BC238C	£0.08	CA3240E	£0.22				
74LS12	£0.14	4018	£0.27	2N3702	£0.09	BC239C	£0.10	CA3240E	£0.22				
74LS122	£0.31	4019	£0.19	2N3703	£0.10	BC251	£0.13	CA3240E	£0.22				
74LS123	£0.31	4021	£0.31	2N3705	£0.10	BC252	£0.13	CA3240E	£0.22				
74LS125	£0.21	4022	£0.32	2N3705	£0.10	BC252B	£0.24	CA3240E	£0.22				
74LS126	£0.21	4023	£0.16	2N3771	£1.44	BC267B	£0.30	CA3240E	£0.22				
74LS132	£0.14	4024	£0.21	2N3772	£1.51	BC307	£0.10	CA3240E	£0.22				
74LS133	£0.35	4025	£0.16	2N3772	£1.79	BC308	£0.10	CA3240E	£0.22				
74LS136	£0.16	4027	£0.18	2N3820	£0.66	BC327	£0.10	CA3240E	£0.22				
74LS138	£0.24	4028	£0.22	2N3904	£0.10	BC337	£0.10	CA3240E	£0.22				
74LS139	£0.25	4029	£0.26	2N3905	£0.10	BC338	£0.10	CA3240E	£0.22				
74LS14	£0.25	4030	£0.17	2N3906	£0.10	BC341C	£0.40	CA3240E	£0.22				
74LS145	£0.56	4030	£0.17	2N3906	£0.31	BC41	£0.40	CA3240E	£0.22				
74LS147	£1.26	4031	£0.70	2N5296	£0.57	BC461	£0.40	CA3240E	£0.22				
74LS148	£0.70	4033	£0.56	2N5221	£0.67	BC463	£0.29	CA3240E	£0.22				
74LS148	£0.70	4034	£0.34	2N5221	£0.67	BC478	£0.32	CA3240E	£0.22				
74LS151	£0.25	4040	£0.29	AC126	£0.30	BC479	£0.32	CA3240E	£0.22				
74LS153	£0.25	4041	£0.31	AC127	£0.30	BC490	£0.24	CA3240E	£0.22				
74LS154	£0.70	4042	£0.28	AC128	£0.45	BC517	£0.20	CA3240E	£0.22				
74LS155	£0.25	4044	£0.35	AC129	£0.45	BC518	£0.20	CA3240E	£0.22				
74LS156	£0.36	4045	£0.22	AC188	£0.37	BC527	£0.20	CA3240E	£0.22				
74LS157	£0.22	4046	£0.31	ACV17	£3.84	BC528	£0.20	CA3240E	£0.22				
74LS158	£0.25	4047	£0.25	AD148	£1.57	BC537	£0.20	CA3240E	£0.22				
74LS160	£0.32	4048	£0.31	AD162	£0.92	BC546C	£0.08	CA3240E	£0.22				
74LS161	£0.32	4049	£0.20	BC107	£0.14	BC548C	£0.08	CA3240E	£0.22				
74LS162	£0.32	4050	£0.20	BC107B	£0.15	BC549C	£0.10	CA3240E	£0.22				
74LS163	£0.32	4051	£0.26	BC108	£0.13	BC550C	£0.10	CA3240E	£0.22				
74LS165	£0.48	4053	£0.25	BC108A	£0.14	BC555A	£0.08	CA3240E	£0.22				
74LS166	£0.30	4054	£0.56	BC109	£0.17	BC558C	£0.08	CA3240E	£0.22				
74LS173	£0.24	4055	£0.34	BC109C	£0.17	BC559C	£0.08	CA3240E	£0.22				
74LS174	£0.24	4060	£0.48	BC114	£0.41	BC560B	£0.08	CA3240E	£0.22				
74LS175	£0.24	4063	£0.29	BC115	£0.41	BC638	£0.21	CA3240E	£0.22				
74LS190	£0.25	4066	£0.18	BC116	£0.41	BC639	£0.21	CA3240E	£0.22				
74LS191	£0.24	4067	£1.98	BC132	£0.38	BC640	£0.21	CA3240E	£0.22				
74LS192	£0.42	4068	£0.16	BC134	£0.36	BCY70	£0.21	CA3240E	£0.22				
74LS193	£0.24	4069	£0.20	BC134	£0.36	BCY72	£0.20	CA3240E	£0.22				
74LS195	£0.24	4070	£0.17	BC135	£0.36	BCY73	£0.20	CA3240E	£0.22				
74LS196	£0.24	4071	£0.20	BC140	£0.25	BCY74	£0.20	CA3240E	£0.22				
74LS197	£0.24	4072	£0.17	BC141	£0.27	BD135	£0.20	CA3240E	£0.22				
74LS20	£0.16	4073	£0.17	BC142	£0.28	BD136	£0.21	CA3240E	£0.22				
74LS21	£0.14	4075	£0.17	BC143	£0.34	BD137	£0.23	CA3240E	£0.22				
74LS22	£0.14	4076	£0.30	BC149	£0.21	BD138	£0.22	CA3240E	£0.22				
74LS221	£0.40	4077	£0.17	BC154	£0.36	BD139	£0.23	CA3240E	£0.22				
74LS240	£0.32	4081	£0.14	BC157	£0.12	BD140	£0.24	CA3240E	£0.22				
74LS241	£0.32	4082	£0.21	BC159	£0.12	BD150C	£0.82	CA3240E	£0.22				
74LS242	£0.32	4083	£0.26	BC170	£0.16	BD166	£0.35	CA3240E	£0.22				
74LS244	£0.32	4089	£0.55	BC170B	£0.16	BD187	£0.39	CA3240E	£0.22				
74LS245	£0.36	4093	£0.18	BC171	£0.11	BD201	£0.40	CA3240E	£0.22				
74LS247	£0.32	4094	£0.16	BC171B	£0.16	BD202	£0.40	CA3240E	£0.22				
74LS251	£0.24	4095	£0.56	BC172	£0.13	BD203	£0.40	CA3240E	£0.22				
74LS252	£0.24	4097	£1.20	BC172B	£0.13	BD204	£0.40	CA3240E	£0.22				
74LS255	£0.24	4098	£0.48	BC177	£0.18	BD222	£0.40	CA3240E	£0.22				
74LS258	£0.24	4099	£0.38	BC178	£0.18	BD225	£0.42	CA3240E	£0.22				
74LS26	£0.14	4502	£0.38	BC179	£0.17	BD232	£0.38	CA3240E	£0.22				
74LS266	£0.14	4503	£0.40	BC182	£0.08	BD237	£0.32	CA3240E	£0.22				
74LS271	£0.14	4508	£1.40	BC182L	£0.08	BD238	£0.32	CA3240E	£0.22				
74LS279	£0.25	4510	£0.25	BC183	£0.08	BD243B	£0.50	CA3240E	£0.22				
74LS30	£0.14	4512	£0.32	BC183L	£0.08	BD244A	£0.53	CA3240E	£0.22				
74LS32	£0.14	4514	£0.77	BC183LB	£0.08	BD246	£1.06	CA3240E	£0.22				
74LS305	£0.21	4515	£0.98	BC184	£0.08	BD41	£0.41	CA3240E	£0.22				
74LS307	£0.21	4516	£0.31	BC184L	£0.08	BD42	£0.41	CA3240E	£0.22				
74LS317	£0.14	4518	£0.27					CA3240E	£0.22				
74LS373	£0.32	4520	£0.26					CA3240E	£0.22				
74LS374	£0.32	4521	£0.42					CA3240E	£0.22				
74LS375	£0.34	4527	£0.40					CA3240E	£0.22				
74LS377	£0.32	4528	£0.40					CA3240E	£0.22				
74LS378	£0.19	4529	£0.44					CA3240E	£0.22				
74LS38	£0.19	4532	£0.32					CA3240E	£0.22				
74LS390	£0.25	4534	£2.48					CA3240E	£0.22				
74LS393	£0.24	4536	£1.00					CA3240E	£0.22				
74LS395	£0.26	4538	£0.37					CA3240E	£0.22				
74LS399	£0.62	4541	£0.33					CA3240E	£0.22				
74LS40	£0.14	4543	£0.46					CA3240E	£0.22				
74LS42	£0.25	4556	£0.34					CA3240E	£0.22				
74LS43	£0.72	4556	£0.34					CA3240E	£0.22				
74LS51	£0.14	4560	£1.18					CA3240E	£0.22				
74LS670	£0.69	4566	£1.96					CA3240E	£0.22				
74LS73	£0.17	4572	£0.25					CA3240E	£0.22				
74LS74	£0.25	4584	£0.24					CA3240E	£0.22				
74LS75	£0.19	4585	£0.32					CA3240E	£0.22				
74LS76	£0.25	4724	£0.70					CA3240E	£0.22				

BITE ALARM

builds three different bite detectors for anglers, designed for varying stages of the National Curriculum.

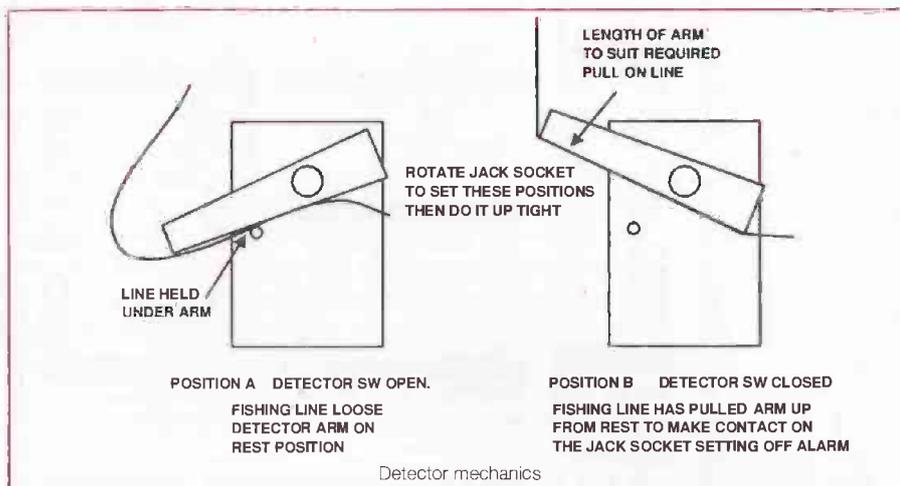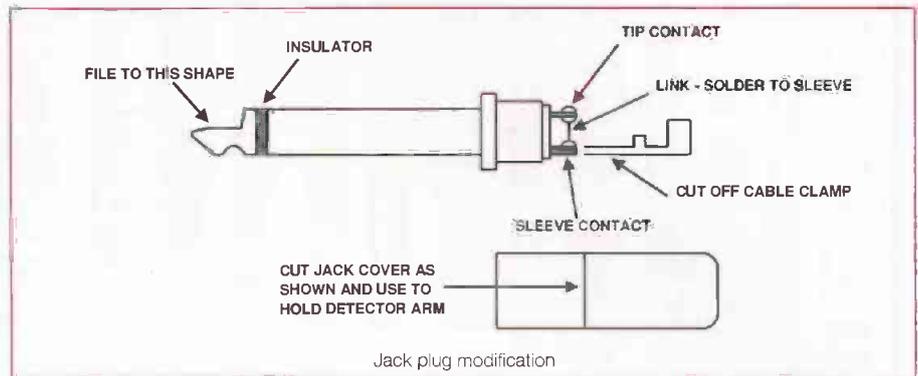This project has been designed to be compatible with the new National Curriculum ideals, where students of varying ability face



the same problems but choose different levels of technology to overcome them.

The object in this case is to indicate audibly, via a beeper and visually through an LED, when a 'bite' is detected while fishing. This can be extremely useful, either when using two rods as a monitor for the second, or for night fishing.

There are three versions of this alarm to allow for the varying abilities of students, but all three use the same detector, box, LED and beeper, although the electronics varies from a couple of components to a dozen or more. Here are the three models, together with their appropriate levels within the National Curriculum and as assessed by the CDT Head of Department at Denefield School, Reading.

Model 1000 - very basic, no active electronics, suitable for pupils working at level 3, minimum.

Model 2000 - simple two stage circuit using a thyristor and a 555 IC, suitable for pupils working at Level 6 or at a range

of levels from 4-7, provided they use the circuits and data supplied for justifying their solutions.

Model 3000 - a digital approach using 3 CMOS ICs. The complexity of this circuit is such that pupils using it could, if it is used as a basis for their own development of a bite alarm, achieve the highest levels. With the right description and folder work, this model is suitable for pupils working at Level 7 or higher.

General Background


There are a lot of good quality bite alarms on the market, but their prices seem well out of the reach of many enthusiasts. Several of those looked at seem to draw a fair amount of current when switched on but not indicating, which means battery replacement would be a frequent occurrence and with a good quality PP3 costing £2 a go, also expensive. So here are my cheaper, low current versions.

The single most important part of the Bite Alarm is the detector. Somehow, this must detect the increased tension

caused by a fish pulling on the line but be able to ignore the constant tension due to current or wind. Many of the ready made units use a disc, which the line rotates when pulled tight and an opto detector is used to monitor dark and transparent sections of this disc. The manufacture of this rotating disc module in production terms and quantities is relatively easy, but trying to make a one off with tools readily available to the amateur is quite a different matter. The most difficult problem is making a spindle to run freely, but strong enough to take the punishment handed out during a day's fishing in all weathers and to survive the average fishing box. Several attempts were made, but all ended up using tools or materials not always available to the amateur. Another approach was required and this was to use a standard 1/4in mono jack plug socket. This, with slight modification, was found to be ideal - cheap, strong and effective.

The spring contact of the socket on the sleeve terminal is bent slightly backwards, to reduce the pressure it exerts on the jack plug. The tip contact on the plug is filed to produce a flat (as per diagram), so that when it is plugged into position A, no contact is made with the socket tip contact, but when the plug is rotated to position B, contact is made. By loosening the shaft contact, by bending it back slightly, we have reduced the current handling capacity of the jack plug/jack socket, but this is unimportant as we are only going to pass a few milliamps through it.

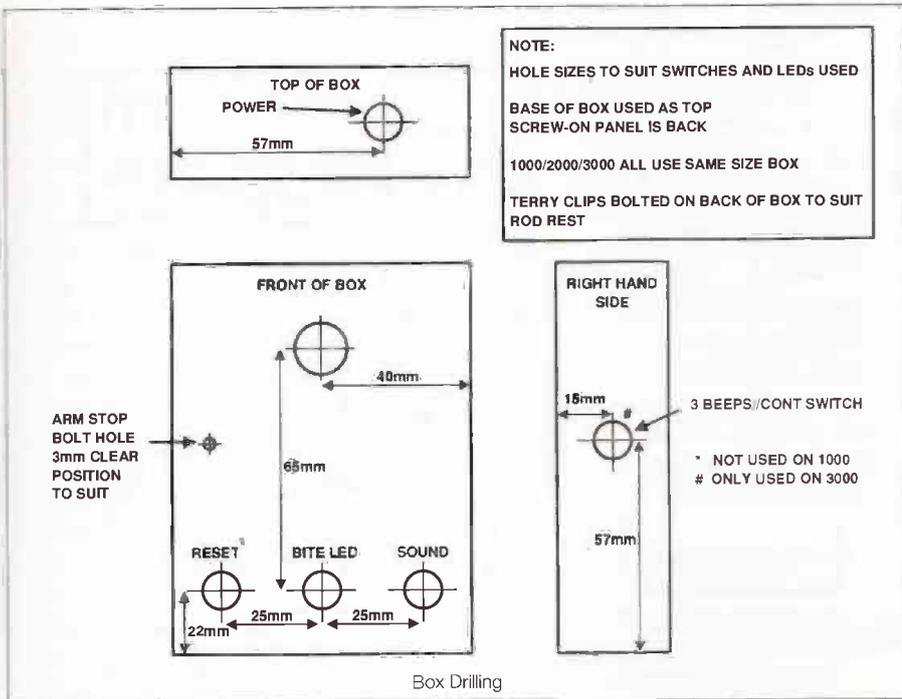All three versions of the Bite Alarm use this type of detector switch. By filing different amounts off the tip contact on



the jack plug, the distance between the position A and B can be varied to suit. Care must be taken not to file away too much or the tip connection is broken as this goes up the centre of the jack plug. To reduce the force required to turn the jack plug in the socket, a simple lever is used. The length of this lever can vary to suit, but remember the longer the lever, the less force is required to turn the jack plug, but the further the lever must be moved. For practical purposes, several levers can be made to suit conditions, short for fast moving water and longer for water that is still or slow flowing.

The jack plug top is also modified. The two connectors are cut off as near to the base as possible to allow them to be soldered together. The screw thread has two flats filed in it in order to stop the lever turning without turning the jack plug.

A short length of the screw cap is cut off to cover these shorted connections and to hold the lever arm in place. If only one arm is going to be used on each jack plug, it is advised that it is glued to the jack plug to give added support. Remember several lever arm jack plug assemblies can be made. The top of the short length of screw cap can be filled with glue gun glue and a small screw cap insert can be fitted to give it a profes-



sional look. These come in different colours and can be used to instantly recognise which one is most suitable for the conditions, e.g. blue for slow water and red for fast water, etc.

The position of the jack plug on the lever arm is also important as the metal to the right of the jack plug acts as a counterbalance weight, making this heavier and effectively decreasing the force required to turn the lever. Too heavy and it keeps the lever in position B, too light and it only detects Great Whites - quite rare here on the Thames.

The fishing line is passed under the detector lever arm in position A so that when the line is pulled taught by a fish, the lever moves to position B. In order for this to happen easily, the bite alarm is clipped on to the rod rest by a couple of small terry clips. The top of the rod rest has a short bar mounted on it, which has two uses. Firstly, it stops the Bite Alarm from rotating on the rod rest and secondly, it holds the rod in the correct position above the detector arm, to the left of the Bite Alarm. All three versions of

the alarm use this type of detector switch, as well as using the same type of box. The switches are all mounted in the same position where applicable - this is to allow an upgrade at a later date if skill and confidence increase during the life of the alarm.

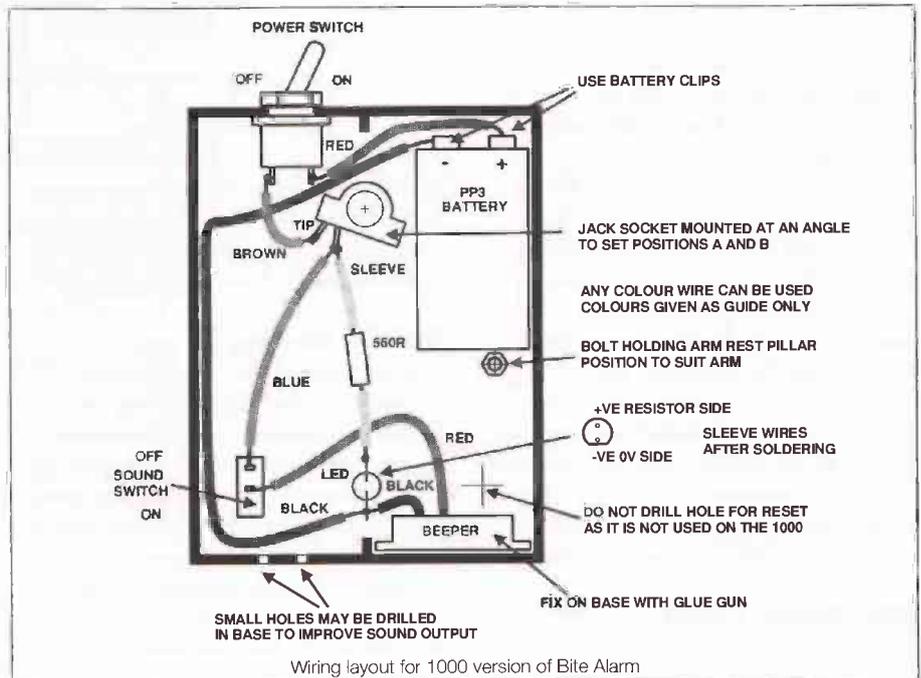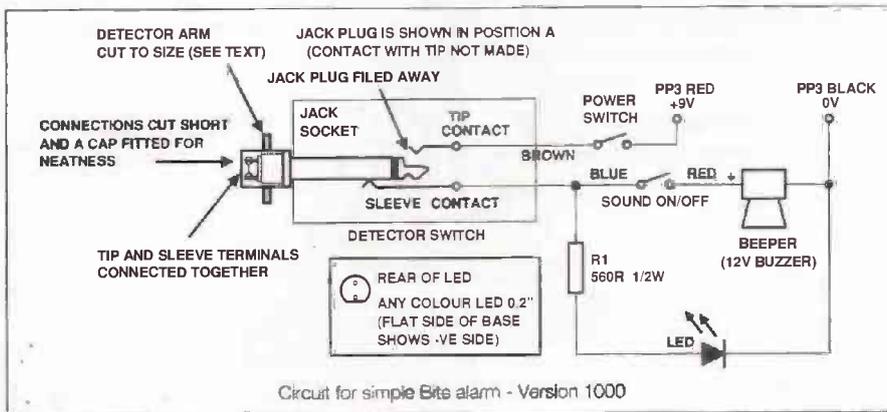All three versions have a LED as well as switchable sound which indicates a 'bite'. The sound can be switched off if it is thought that it might disturb the fish or other people nearby. All versions have been extensively tested and their varying



complexity only determines the way a bite is indicated. It doesn't affect the sensitivity of detection, which remains the same in all three. Each version is equally useful, something not usually found in graded ability projects.

Bite Alarm 1000

This is the simplest version, but is still a very rewarding project which effectively has no active electronics.

How It Works

When the Power switch is On, the +9V from the PP3 battery goes to the jack socket tip terminal. If the jack plug on the detector lever is in position A, i.e. fishing line loose, the circuit is effectively broken as no contact is made to the tip of the jack plug. However when the jack plug is rotated to position B by the action of the line being pulled taught by a fish, the tip contact of the jack plug make contact with the tip contact of the jack socket and a circuit is made. The jack plug must have its two terminals connected together as shown in the

diagram. The +9V now flows into R1, the current limit resistor and into the positive side of the LED. The negative side of the LED (the lead nearest the flat on the side of the LED) completes the circuit to battery 0V.


If the Sound switch is On, 9V is also passed to the positive side of the beeper, the red lead. The black lead goes to battery 0V. A low current, low price buzzer rated at 12V is used in my projects although any small low current piezo sound (active type with oscillator built in) will do.

Although in this version there is plenty of room, it is recommended that the alarm is built to the drawing and the controls fitted roughly where indicated - this then allows the project to be upgraded if required later, as the other projects use the same box, etc.


Although this is the simplest of the three alarms it does have the advantage that when the detector lever is in position A, not indicating a bite, no current flows at all, so increasing the life of the battery. Current is only drawn while indicating.

Bite Alarm 2000

This circuit can be broken down into two

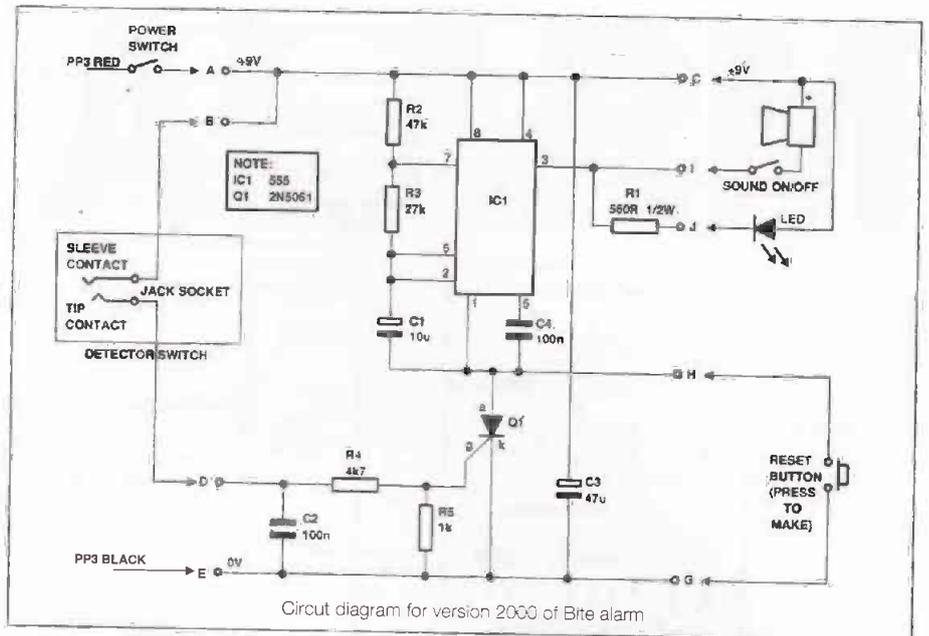

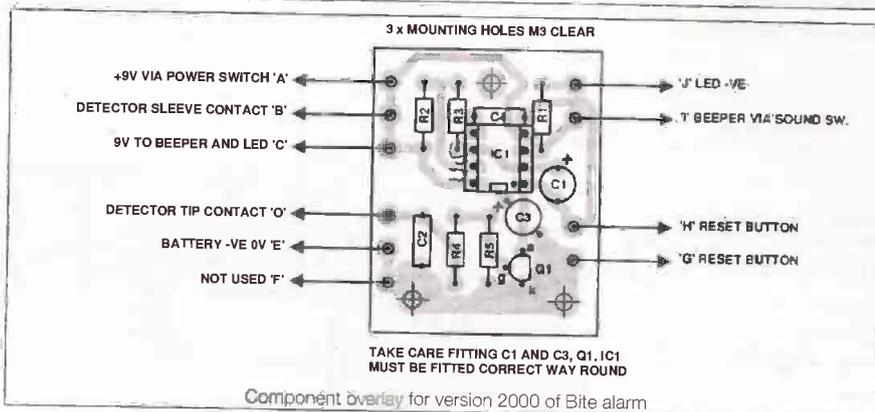
Circuit diagram for version 2000 of Bite alarm



Component overlay for version 2000 of Bite alarm

contacts close, switching 9V to R4. R4 and R5 produce a voltage divider and current limiter, essential to the safe operation of the thyristor.

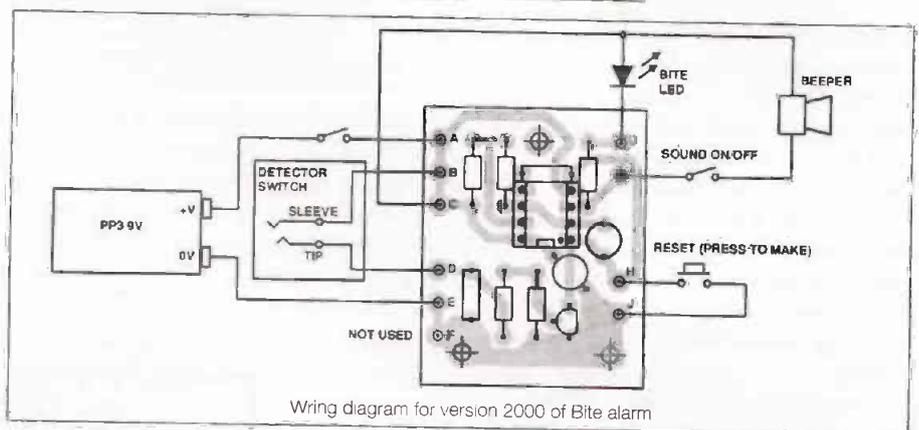Thyristors vary considerably in their sensitivity and if a different one is used, it must have a similar



Wiring diagram for version 2000 of Bite alarm

distinct parts, both of which use components commonly found in school projects - the latch, built around a thyristor and the oscillator, built around the 555 timer.

How It Works

The latch part of the circuit uses the property of a thyristor that once it is turned on it stays on, even if the input signal is removed. It will stay on until the current passing through it is taken away. The input signal comes from the detector switch which, when in position A, receives nothing as the switch is effectively open. When rotated to position B by a fish on the line, the detector

specification. C2 is used to try to remove any RF (radio frequency) signals that may be present, shorting them down to 0V. If present in any quantity they could cause the thyristor to turn on, giving a false indication.

When the detector lever is in position B and the alarm power is switched On, the thyristor turns on, effectively going from open circuit to short circuit. This turning on to a short circuit condition will remain, even if the detector lever drops back from position B, removing the gate signal from the thyristor. From now on, the thyristor applies 9V to the 555.

In the oscillator, the 555 is connected

to drive the output transistor Q1 to power the LED and beeper. A transistor is required to amplify the current output of the CMOS IC which can only supply 1mA or so directly.

The counter IC3 is a walking 1 type, which means that when the first pulse is received, assuming the counter has previously been reset, the output corresponding to count 1, pin 2 goes high, all the other remain low. On receiving the second pulse from the oscillator, the count 1 output goes low and the count 2 output pin 4 goes high. On receiving the third pulse from the oscillator pin 7, count 3 output goes high and pin 4 goes low. The pulses, as well as going to the counter, go to the LED and beeper, if switched on. So far, 3 flashes on the LED along with 3 beeps will have passed. The fourth pulse will cause pin 10 of IC3 to go high and pin 7 to go low. Assuming the 3 beeps option has been selected, pin 6 of IC2 will be high, pulled up by R7. Now the 4 output on the counter pin 10 makes pin 5 on IC1b high. Two highs in on a 2 input NAND makes the output go low, so IC2 pin 4 goes from a high to a low - this is fed to IC2 pin 2, the input, to another NAND gate. Any low into a NAND causes its output to go high, regardless of the other inputs. This high on the output of IC2a pin 3 resets the counter as well as the D type, returning the bite indicator to its start position, regardless of the position of the detector lever. All this from the generation of the

fourth pulse happens so quickly that the beep is never heard, so it is cancelled before it has had time to sound or even illuminate the LED.

If the 3 beeps function is not selected, IC2 pin 6 remains low (switched to 0V by the selector switch), ensuring a high on the output pin 4 no matter what is on pin 5 due to the counter, so the oscillator will run on until reset by pressing the reset button. This puts a low on IC2 pin 1 causing pin 3 to go high, resetting the counter and D type.

D1, R6 and C4 form a switch on reset so that when the alarm is first powered up from the power switch, C4 from being fully discharged by D1, charges up via R6. So to start with, IC2 pin 1 is low until C4 charges up to above 60% of rail, or about 6V. During this charging up time, pin 3 is high, resetting IC1a, the D type and IC3 the counter, but as soon as pin 1 reaches 60% of rail it is seen as a 1 and IC2 pin 3 goes low, cancelling the reset.


If all this seems a bit complicated, it is advised that the truth tables are consulted on the NAND operation. Although IC2 is a NAND Schmitt, its truth table is identical to a normal NAND, like the 4011. The difference is only in the hysteresis allowing it to be used as an oscillator, unlike a normal NAND gate.

IC1b is not used in the circuit but, as is required by all CMOS ICs, all unused inputs are either tied up or down, i.e. connected to rail or 0V and, not left unconnected to float.

It will be noted that the first beep is longer than the others - this is due to the fact that C2, the timing capacitor for the oscillator, charges up to rail volts, i.e. 9V, when the oscillator is off, so C2 must discharge from 100% to 40% of rail, taking longer than continuous oscillation where it only charges from 40-60% and back to 40%.

Although three possible options are given in this article, there are several other approaches to overcome the Bite Alarm problem. Even following one of the suggested circuits, there is still a lot of experimenting to be done with the lever length and shape, where to mount the jack plug, even the possible use of a counterbalance weight and so on.

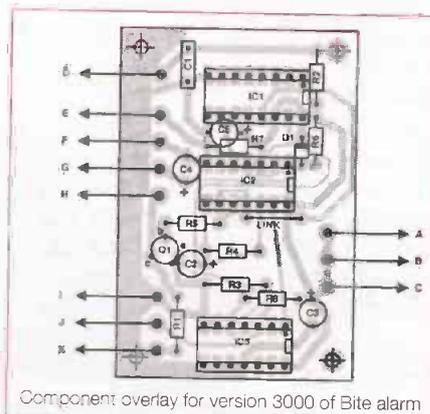I have experimented with making a very small alarm, actually mounted on the rod. Although it adds weight to the rod it still works, even if it does get in the way a little.



Component overlay for version 3000 of Bite alarm

Good luck with the project and good luck with the fishing too!

PARTS LIST

Model 1000

- R1 560
- LED1 Red or green, 0.2in round LED
- 12V buzzer
- 1 Jack socket (mono)
- 1 Jack plug (mono)
- 1 box
- 1 On/Off switch, 1 pole On/Off
- 1 On/Off sound switch, 1 pole On/Off
- 2 small Terry clips to suit
- 1 battery connector
- 1 battery, PP3

Model 2000

Resistors

- R1 560
- R2 47K
- R3 27K
- R4 4K7
- R5 1K

Capacitors

- C1 10µF 16 V Rad Elect
- C2 0.1µF 25V Ceramic
- C3 47µF 16V Rad Elect

Miscellaneous

- IC1 NE 555 timer
- 1 8 pin IC socket
- T1 thyristor 2N5061 or similar
- LED1 red or green 0.2in round
- 1 Jack socket (mono)
- 1 Jack plug (mono)
- 1 buzzer
- 1 On/Off switch, 1 pole On/Off
- 1 On/Off sound switch, 1 pole On/Off
- 1 press to make switch
- 1 box
- 1 battery connector
- 1 battery, PP3
- Vero pins 0.1in to suit

Model 3000
Resistors

- R1 560
- R2 680K
- R3 27K
- R4 470K
- R5 15K
- R6 47K
- R7 47K

Capacitors

- C1 0.22µF
- C2 2 µF TANT 16V
- C3 47µF 16V Radial
- C4 1µF 16V Radial
- C5 47µF 16V Radial
- ICs
- IC1 4017 CMOS
- IC2 4093 CMOS
- IC3 4013 CMOS

Miscellaneous

- IC holders, 2 off 14 pin, 1 off 16 pin
- Q1 BC107
- D1 IN4148
- 1 On/Off switch, 1 pole On/Off
- 1 On/Off sound switch, 1 pole On/Off
- 3 beeps switch, 1 pole On/Off
- 1 press to make switch
- 1 box
- 1 Jack socket (mono)
- 1 Jack plug (mono)
- 1 buzzer
- 1 battery connector
- 1 battery connector
- 1 battery, PP3
- Vero pins 0.1in to suit


EASY-PC, Schematic and PCB CAD

Over 18,000 Installations
in 80 Countries World-wide!


Still
Only
£98.00!

Plus P&P+VAT

**BRITISH
DESIGN
AWARD
1989**

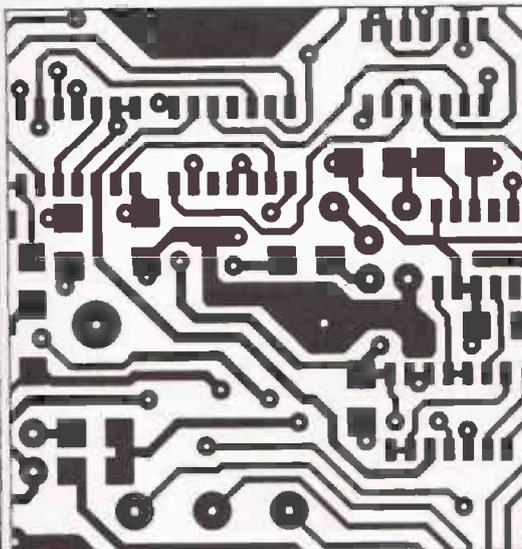

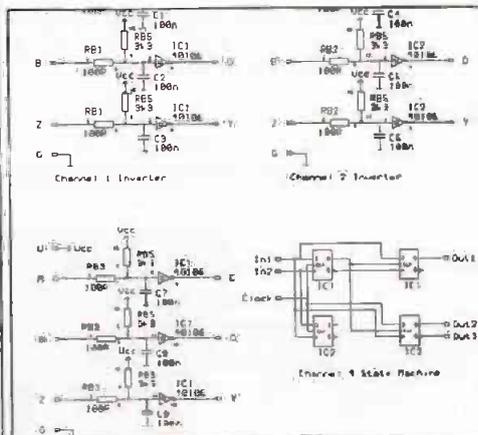
- Runs on:- PC/XT/AT/286/386/486 with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design:- Single sided, Double sided and Multi-layer (8) boards.
- Provides full Surface Mount support.
- Standard output includes Dot Matrix / Laser / Ink-jet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Tech Support - free.
- Superbly easy to use.



Options:-500 piece Surface Mount Symbol Library £48,
1000 piece Symbol Library £38, Gerber Import facility £98.

Electronic Designs Right First Time?


Integrated Electronics CAD

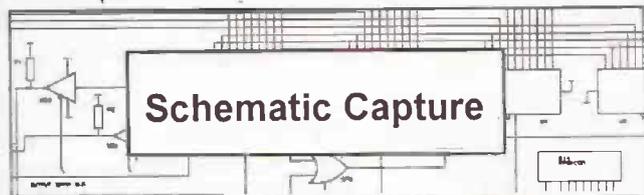

Schematic Capture



Analogue
& Digital
Simulation

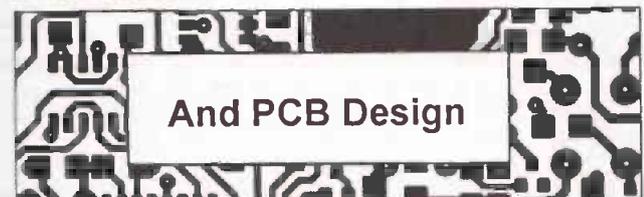

And PCB Design

Prices from UK£195 / US\$375

Affordable Electronics CAD

EASY-PC: Entry level PCB and Schematic CAD.	\$195.00	£98.00
EASY-PC Professional: Schematic Capture and PCB CAD. Links directly to ANALYSER III and PULSAR.	\$375.00	£195.00
EASY-PC Pro' XM: Extended Memory Version - Greatly increased capacity	\$475.00	£245.00
PULSAR: Digital Circuit Simulator ~ 1500 gate capacity.	\$195.00	£98.00
PULSAR Professional: Digital Circuit Simulator ~ 50,000 gate capacity.	\$375.00	£195.00
ANALYSER III: Linear Analogue Circuit Simulator ~ 130 node capability	\$195.00	£98.00
ANALYSER III Professional: Linear Analogue Circuit Simulator ~ 750 node capability.	\$375.00	£195.00
Z-MATCH for Windows: NEW Windows based Smith-Chart program for RF Engineers.	\$475.00	£245.00
FILTECH: Active and Passive Filter Design program	\$275.00	£145.00

We operate a no penalty upgrade policy. You can upgrade at any time to the professional version of a program just for the difference in price.

US\$ prices include Post and Packing.

UK£ prices exclude P&P and VAT

For full information, please write, phone or fax:-

Number One Systems

UK/EEC: Ref. ETI, HARDING WAY, ST.IVES, CAMBS., ENGLAND, PE17 4WR.

Telephone UK: 0480 461778 (7 lines) Fax: 0480 494042 International +44 480 461778

USA: Ref. ETI, 1795 Granger Avenue, Los Altos, CA 94024

Telephone/Fax: (415) 968 9306

- TECHNICAL SUPPORT FREE FOR LIFE
- PROGRAMS NOT COPY PROTECTED.
- SPECIAL PRICES FOR EDUCATION.

MASTERCARD, VISA Welcome.


SYSTEM 200 DEVICE PROGRAMMER

SYSTEM: Programs 24, 26, 32 pin EPROMS, EE-PROMS, FLASH and Emulators as standard, quickly, reliably and at low cost.

Expandable to cover virtually any programmable part including serial E², PALS, GALS, EPLD's and microcontrollers from all manufacturers.

DESIGN: Not a plug in card but connects to the PC serial or parallel port; it comes complete with powerful yet easy to control software, cable and manual.

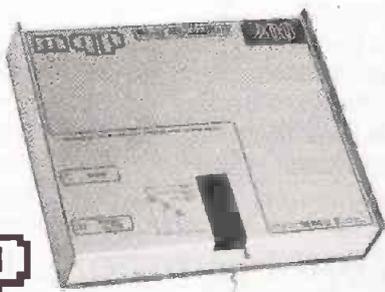SUPPORT: UK design, manufacture and support. Same day dispatch, 12 month warranty. 10 day money back guarantee.



ASK FOR FREE INFORMATION PACK

mqp

MQP ELECTRONICS Ltd.
Park Road Centre,
Malmesbury, Wiltshire, SN16 0BX UK
TEL. 0666 825146 FAX. 0666 825141



GERMANY 089-/4602071
NORWAY 0702 17890
ITALY 02-92-10-3 554
FRANCE (1) 69-30-13-79
SWEDEN 08-735-5360

ALSO FROM ELECTROSPEED UK

DELICIA

The transmitter people

4 WATT PPO FM BROADCAST (built) TRANSMITTER: with low pass filter

Modulation	75KHz wide band
Range	up to 4.2 miles
Supply	10-16 volts AC/DC
Current	250mA
Audio Input	100mV (ADJ)
Frequency Range	88-108MHz FM
Stability	+/- 20KHz
Size	W. 70mm, D. 90mm, H. 50mm
MANY USER CONTROLS	£23.50

7 WATT PPO FM BROADCAST (built) TRANSMITTER: Higher watt version of above transmitter 7 mile range **£52.50**

KIT: 3 WATT TRANSMITTER 80 - 100MHZ: Coil tank controlled up to 3 miles range, supply 12V DC at 0.5amps **£52.50**

All prices include VAT
Please add £1 P&P payment with orders to:

DELICIA ELECTRONICS, 14 St. Mary Park, Glen Road, Belfast BT11 3FZ Tel 02822 811995

24 hour turn-around

Please send 2 x 1st class stamps for our catalogue

PCB Designer

For Windows 3.1
Runs on any PC running Windows in standard or enhanced mode with 2MB RAM

Only
£49
All
Inclusive

- ✓ Produce *Single* or *Double* sided PCBs.
- ✓ Print out to *any Windows supported* printer.
- ✓ *Toolbar* for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pads sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.
- ✓ Positive reviews by Robert Penfold and Paul Stenning, copies available on request.


Phone (0432) 355 414 (Access and Visa welcome)

Niche Software

22 Tavistock Drive, Belmont, Hereford, HR2 7XN.

Please Note: Since PCB designer is so easy to use, and to keep costs down, PCB Designer has an On-Line manual, in Windows Help format. A FREE tutorial is also supplied.

EPROM EMULATOR

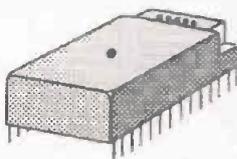

Only 11mm high, it plugs directly into your Eprom socket. Compatible with standard Eproms. Allows faster product development.

Data is written to the emulator directly from your computer, via a 4mm cable which plugs into the emulator.

The MicroRom Eprom Emulator offers non-volatile storage and can download a 27256 file in only 1 SECOND. Prices from £99 + VAT

TEL / FAX 081 880 9889

SquareWave Electronics Ltd., Imperial House, 64 Willoughby Lane, LONDON N17 0SP

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX · 031 667 2611

- The supplier to use if you're looking for —
- ★ A WIDE RANGE OF COMPONENTS AIMED AT THE HOBBYIST ★
 - ★ COMPETITIVE VAT INCLUSIVE PRICES ★
 - ★ MAIL ORDER - generally by RETURN OF POST ★
 - ★ FRIENDLY SERVICE ★



Open: Monday-Thursday 9.15-6.00
Friday 9.15-5.00 Saturday 9.30-5.00



PC Clinic

This month in PC Clinic, we examine the heart of every PC - the CPU. We look at how it can be made to work faster with the aid of coprocessors, clock doublers and cache memory. We will also be looking at the BIOS software and its Power On Self Test routines, which enable us to track down system faults.

At the very heart of every personal computer, no matter what its make or design, there is a processor chip of some sort. In the IBM PC and all compatibles, this processor chip will belong to the Intel x86 family of processors, the familiar 8086, 80286, 80386, 80486 and most recently the Pentium. These processor chips were all originally designed and manufactured by the US semiconductor giant Intel, although the processor in your PC will not necessarily be manufactured by Intel, but maybe by one of the half dozen or so, mostly US based, manufacturers of 'clone' processors. These 'clone' processor chips will all run the same software as those from Intel, but often have slightly different performance ratings.

The function of the processor chip, or Central Processing Unit - CPU for short - is to execute the sequence of instructions which make up the program code. This code and its associated data is stored in memory and accessed by the CPU under control of the clock timing signals. In general, the faster the clock can be made to run; the more instructions can be executed in a given period and therefore the more powerful the processor is in computational terms.

Program instructions and data are all stored in memory and processed within the CPU in binary form and are organised in units of eight bits, or one Byte. Since most instructions and data occupy more than one byte, a processor can be speeded up by handling two or more bytes in parallel. Thus, a 16 bit processor is approximately twice as fast as an 8 bit processor and likewise a 32 bit CPU is four times faster, assuming of course that they are all running at the same clock rate.


The processing power of a personal computer is thus dependent upon a combination of clock speed and the number of bits it can access from memory and process during any one clock cycle. This processing power is most commonly rated in terms of Millions of Instructions Per Second, or MIPS. The very first processor in this range, the Intel 8086, was launched in June 1978 and had a power rating of just .33 MIPS. Five generations of processor later and the Pentium, launched in March 1993, had a rating of 112 MIPS. This is about 300 times the processing power of the CPU found in the very first IBM PCs.

Historically, Intel has launched a new

generation of processor chip every 44 months, but under competitive pressure from manufacturers of new very powerful RISC based processors, this development rate has been accelerated. Peak power from the Pentium will be more than doubled later this year with a 150MHz version and the next generation, code named the P6, is already undergoing testing prior to launch next year, only 30 plus months after the Pentium. The P6 looks set to at least double the power output of the best Pentium.

So why do we need more power? The answer is simply that new software applications, particularly those which are highly graphics oriented, need more and more power. Try running Windows or a CAD/DTP package on an old 8MHz 286 and then compare it with the same software running on a 66MHz 486. On a slow machine, such software is virtually unusable, it cannot perform all the calculations and update the screen sufficiently quickly to prevent the display hardware having to wait for the processor.

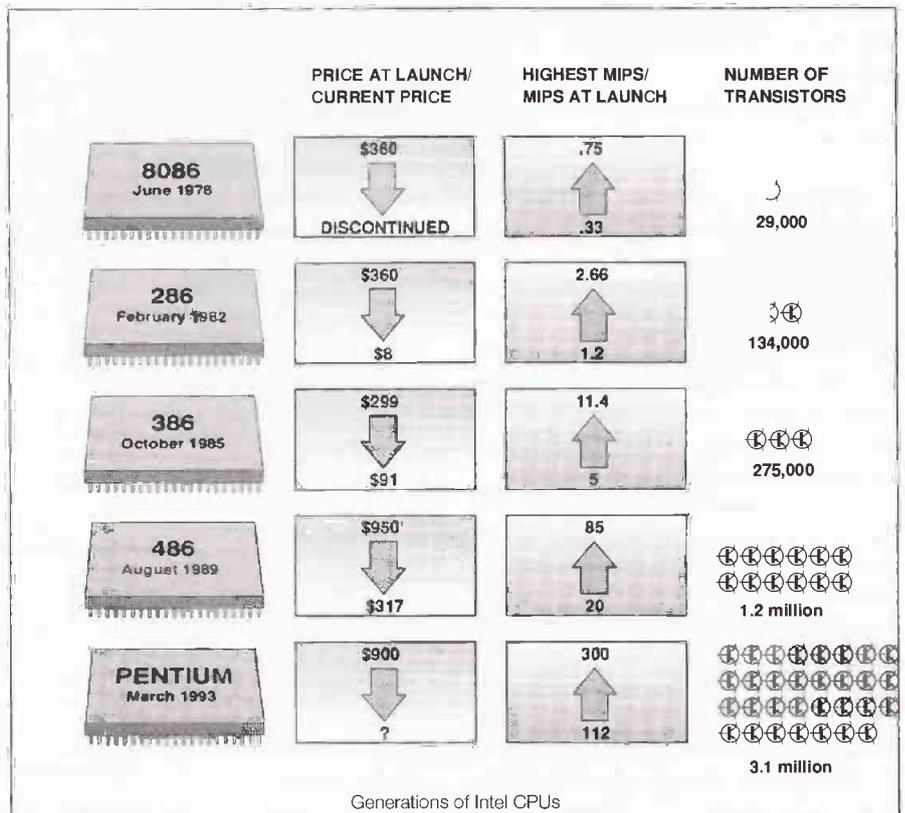This means that if you want to have a more powerful computer, but do not want to buy an entirely new system, then you will need to look at upgrading the processor. On the following pages we will show some of the ways in which this



Coprocessors

A coprocessor is essentially a piece of hardware, we could call it an assistant processor, which is designed to perform high speed operations which would otherwise have to be executed using much slower software routines, monopolising the main processor. It is called a coprocessor because its hardware is very closely integrated with that of the main processor so that in essence it extends the processor's instruction set with a number of new special purpose instructions, that can replace frequently used software routines.

Thus, a coprocessor might perform a specific function in two or three instruction cycles which would otherwise need a code sequence lasting fifty instructions. In specific applications, a coprocessor can give enormous improvements in processing speed.

Most people, when they talk about coprocessors, think about maths coprocessors, a coprocessor designed to perform a range of complex arithmetic operations which are not normally included in a processor's instruction set, such as calculations involving sine and cosine. However, coprocessors can also be used for other operations.

Some networking and communications systems use special coprocessors to relieve the main processor of the overheads inherent in communications and error checking. Similarly, advanced multimedia systems that are designed to handle video images use special image compression and decompression coprocessors. Indeed, literally hundreds of different types of coprocessor have been designed for the 80x86 CPU family alone.

The most commonly encountered coprocessor is the maths coprocessor and there are two principle types - the Intel 80x87 range and the Weitek range. The Weitek maths coprocessors offer a better performance than a typical Intel version, but programs will have to be specially written to take advantage of it. Although the 486DX has a math coprocessor on the CPU chip, some systems also have provision for installation of a Weitek 4167.

As one can see from the two diagrams accompanying this section, the 386/387 interface is relatively simple, with the 387 being mapped into the high I/O address space of the 386 (A31 high and M/IO low). Address line 2 distinguishes command transfers from data transfers. Far more efficient is the much more closely coupled Weitek extended maths coprocessor interface, since it makes full use of both the address and data bus, thereby allowing commands and data to be transferred simultaneously. This interface means that the coprocessor runs about three times faster than the conventional 387 interface and it is thus worth checking to see if your motherboard supports it.

The most common choice of maths coprocessor is the Intel family and adding one to a 286/386 system is relatively easy, since nearly all motherboards designed for these processors have a dedicated coprocessor socket. When choosing a coprocessor, it is important that it matches the system into which it will be installed. Thus, if it is going into a 20MHz 386 system then the coprocessor will have to be a 20MHz 387, a 25MHz 386 will require a 25MHz 387 and so on.

When installing a coprocessor chip, always make

REPLACING AND UPGRADING

In theory, we can improve the performance of a system by changing the CPU. A faster processor with a wider data width will give us more processing power, so if we swap a 286 for a 386 we should get about five times the processing power. Similarly, by changing from a 286 or earlier processor to a 386 or later, we can overcome the memory limitations that were inherent in these earlier systems.

But, unfortunately, changing processors is not that easy and in all but the most recent systems it is certainly not a case of simply removing one chip and plugging in another. The problem is that there are too many sub-systems and interrelated components for us to simply be able to change the current processor for a more powerful one.

We therefore have to think about the complete system, about the fact that the clock circuitry will be the wrong frequency and about the fact that the address, data, and control lines of the new processor could be entirely different. Not forgetting the simple fact that the processor chip could be a different size and have a lot more pins.

What this means is that simply changing the processor chip more often than not also involves changing the whole motherboard. However, we can improve the processing power of a system in certain applications with the aid of a maths coprocessor. The type of applications where this will be of value are those which involve a lot of mathematical calculations, rather than simply moving and manipulating data bytes - in other words applications such as image transforms in 3-D CAD packages, or system simulations.


Thus if you are running this type of mathematically intensive application on a 286 or 386 based PC, then a coprocessor of some sort will give quite a considerable boost in performance since it will allow calculations to be performed using hardware rather than software. The result is a reduction in the number of processor cycles needed to perform a specific calculation and thus an overall improvement in the speed at which the application works.

With the 486 and Pentium processors, the situation is slightly different since both chips were designed to include a maths coprocessor integrated on the same slice of silicon as the processor. However, when the 486 was first launched there were apparently some problems associated

sure that the power is disconnected before installing and that any static is fully discharged. Before attempting to insert it in the socket, first check that no pins are bent or damaged. If they are bent, gently straighten them with pointed nose pliers. Then make sure that the board under the socket is well supported as it is easy to crack a track by being over enthusiastic when pushing a chip into a socket. Finally check that the orientation of the chip is correct by matching the dot on the top of the chip to the dot or notch on the socket or the motherboard.

Having carefully done all these things, press the chip firmly in place. On some motherboards, it will be necessary to set a jumper or DIP switch to inform the system that a coprocessor is installed. You will have to check your motherboard documentation for details on which jumper or switch needs to be set. When this has been done, check it by switching the PC on and checking for any error messages. If your

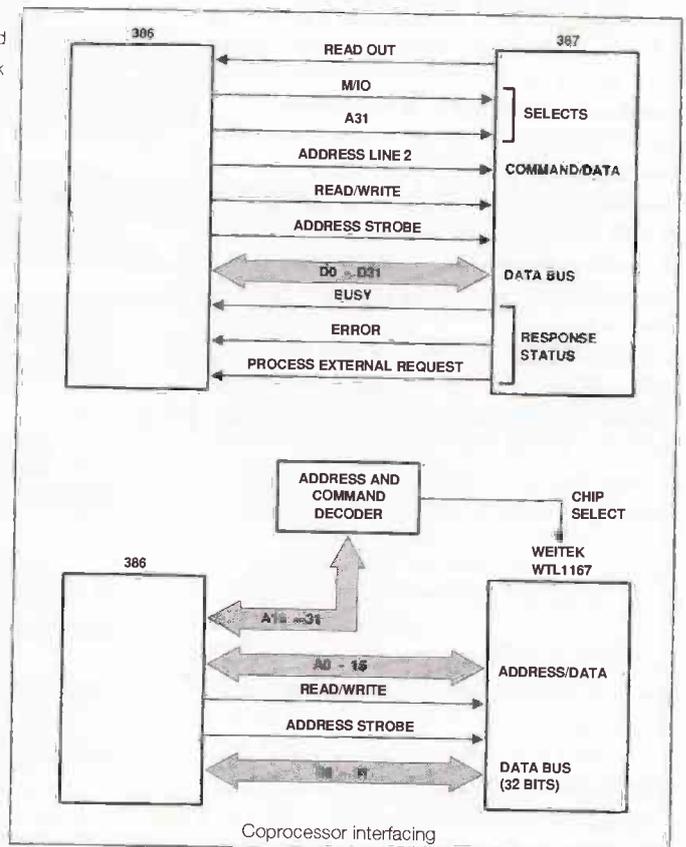coprocessor chip comes with a diagnostic program then run this, otherwise enter the system's CMOS set-up program and check that it indicates that a maths chip is installed. If it does not, then switch off and carefully recheck that the chip is installed properly.



UPGRADING THE CPU IN A PC

with the coprocessor and rather than withdrawing the chip, it was decided simply to disable the coprocessor and relabel the device the 80486SX, as opposed to the 80486DX which has the coprocessor.

Apart from the presence or absence of the coprocessor, these two 486 chips are identical, so adding a maths coprocessor to a 486SX based system is simply a matter of removing the SX chip and replacing it in the same socket with a DX chip of the same speed.

At this stage in the development of the 80x86 family of processors, Intel introduced a new innovation which allows the user to increase the power of a system by simply replacing the processor chip. This technique is known as clock doubling (now we also have clock tripling and clock quadrupling) and overcomes a lot of the earlier problems associated with the close relationship between the processor and allied systems.

The clock doubling technique is an ingenious one, since it allows the processor to run at twice the speed (a clock tripler runs at three times the speed, and so on) that would otherwise be permissible. This means that, for example, a processor could run at 66MHz on a motherboard which is only rated for 33MHz. In this way, a processor chip is upgradable without having to upgrade the whole motherboard and, equally important, all the problems associated with designing and building very high speed motherboards are overcome. Board designers can thus optimise their design to give the best speed at the lowest cost.

System manufacturers have also discovered that this gives them a great flexibility, a single motherboard design can be used in a range of different models simply by changing processor and peripherals. This of course reduces the need for expensive stock holding, allows them to respond quickly to the development of new processors and new system requirements. It also acts as a good sales incentive to be able to say to customers that a system is relatively future proof and can easily be upgraded, a factor which has encouraged a great many manufacturers to use Zero Insertion Force - ZIF - sockets for processor chips, thereby making removal and replacement very easy.

Using a DX chip

As can be seen from the chart on page 35, the 80x86 family of processor chips has become bigger, more powerful and much faster. This posed an enormous problem for system designers, the processor was getting too fast for the system. Memory access times were becoming too fast for the type of memory chips which could economically be used on a PC, high clock speeds were starting to give rise to board design problems due to such factors as signal propagation delays.

These factors all meant that, although it was feasible to build much faster system boards, it was uneconomic to push motherboard clock speeds much beyond the 30MHz area. Neither was it practical to do so, since the number of wait states entailed in accessing standard memory chips would effectively slow the system back down to that sort of level.

Processor manufacturers were nevertheless capable of making their processor chips run at substantially higher speeds. Furthermore, users and software producers had an insatiable demand for more power. There are of course only two ways in which processing power can be increased for a given type of processor. One way is to increase clock speed and the other is to increase the data bus width, but data bus width increase also adds a substantial overhead to system board production costs and would entail the use of an entirely new expansion bus interface.

The solution to these problems involved carefully examining the system and looking at which parts of the circuit needed to operate at high speed and which could continue to operate at lower speed. The high speed components would then be integrated onto the same slice of silicon as the CPU, thereby allowing the processor to work at maximum speed.

The result was the DX2, or clock doubling chip, which is in every way compatible with a DX chip but runs twice as fast internally. The bus interface unit on a DX2 chip allows the processor to work with the lower speed external circuitry with a 2:1 speed reduction, so that in such situations, the DX2 functions exactly like a DX. However, the area of memory currently being accessed is mapped onto an 8K block of memory within the DX2 chip, the processor cache, so that whenever the processor needs to access this memory, use its internal registers or perform a floating point operation, it can do so at twice the external clock speed.

In practice this clock doubling technique means that a processor can effectively spend 90 to 95% of its time operating at the higher speed, thus effectively increasing the processing power of a system by between 70 and 80%. Indeed, this is a technique which can be extended even further. Intel has just launched its clock tripling series of DX4 processors (not as one would logically expect, quadrupling!) offering internal clock speeds of up to 100MHz.

In theory therefore, one can simply double the processing power of, say, a 25MHz 486DX by replacing the DX chip with a 50MHz DX2 chip. On some motherboards this simply involves replacing the DX chip with a corresponding DX2. Many newer designs of motherboard have ZIF sockets for the processor chip, thus making removal and replacement very easy.


Not all motherboards are the same and on older boards there is an additional socket for what is called an OverDrive chip, the function of which corresponds to that of a DX2 and not, as some vendors would have one believe, a coprocessor. Another type of overdrive socket found on more recent 486 system boards is the P24T socket, which allows the system to be upgraded to a Pentium. Doing so will simply involve putting the P24T chip into the 238 pin socket provided for it on the motherboard, which will then preempt the existing 486 processor.

In the case of an original 486SX with a maths coprocessor socket, it is possible in some cases to upgrade the system to run a DX2 chip. Thus, a 20MHz 486SX could be replaced by a 40MHz DX2. This will entail carefully prising out the old CPU chip and replacing it with the new one, but before attempting to do this and certainly before buying the replacement processor chip, it is a good idea to check with the manufacturer that such an upgrade is feasible.

In practice, upgrading from a DX to a DX2 is not quite that simple.

One major problem is that an increase in processor speed also means an increase in power consumption and thus in heat output. A DX2 chip consumes about 40% more power than the equivalent DX and outputs a correspondingly increased amount of heat. This means, that if you upgrade from a DX to a DX2 you will need to take special measures to dissipate the additional heat.

A miniature fan which is mounted directly on top of the processor chip is one solution to this problem and such fans can be readily obtained from the many vendors of PC upgrade equipment. Since overheating, where the chip temperature exceeds 185F, can easily damage the processor chip (and bear in mind that this is probably the most expensive component in the system and a new one can cost you several hundred pounds) it is also a good idea to use an audible monitor to indicate when the system is overheating - we will show how to build such a monitor in next month's E.T.I.

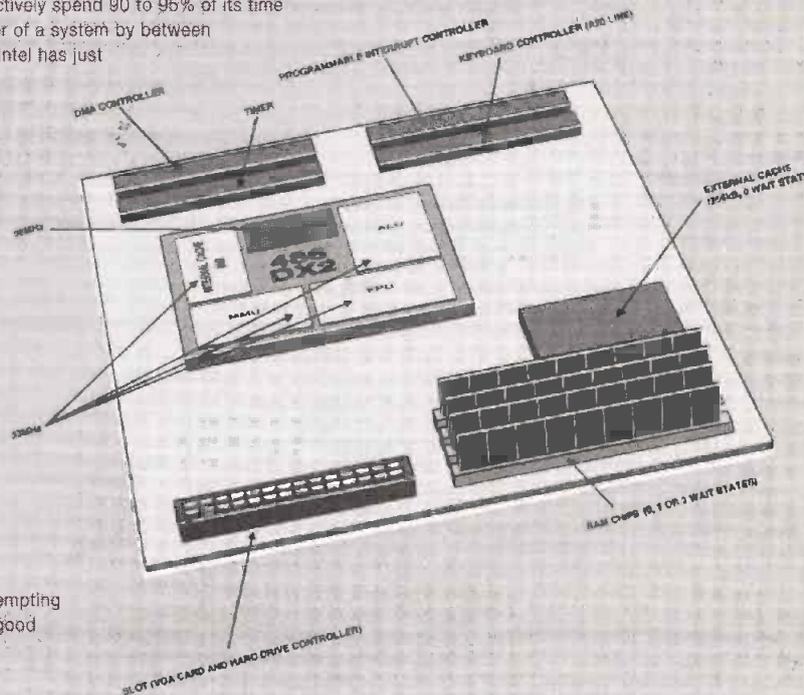

Inside an Intel CPU

The Pentium is the most powerful member of the Intel 80x86 family of processor chips. By every standard it is a truly massive chip, the packaging is a pin gate array (PGA) and measures 2.13in square with 273 pins. Inside the packaging is a 0.8 micron fabrication technology BiCMOS chip with 3.1 million transistors etched on it and at 66MHz it draws over 13W of power. All of which allows it to deliver 112 MIPS of processing power. On these two pages we take a look at what is inside a Pentium chip and compare it with a typical 486DX.

Instruction decode

At the heart of every processor is an area of circuitry which converts the instruction code into a sequence of operations which are performed by the other parts of the CPU. The circuitry which performs this function works at two levels. Simple instructions, such as moving a byte of data between registers, are initiated directly by the circuitry, but more complex instructions require a more sophisticated approach: In essence these instructions are executed by small programs stored within the microcode ROM, which is part of the decode circuitry. They are stored as sequences of simple instructions. It should be noted that nearly all simple instructions are executed in one clock cycle, whereas complex instructions usually take two or more.

Code cache


To overcome the need to use wait states when accessing relatively slow RAM, the Pentium has a high speed 8KB instructions cache.

Code TLB

Translation lookaside buffers for the code cache.

Clock driver

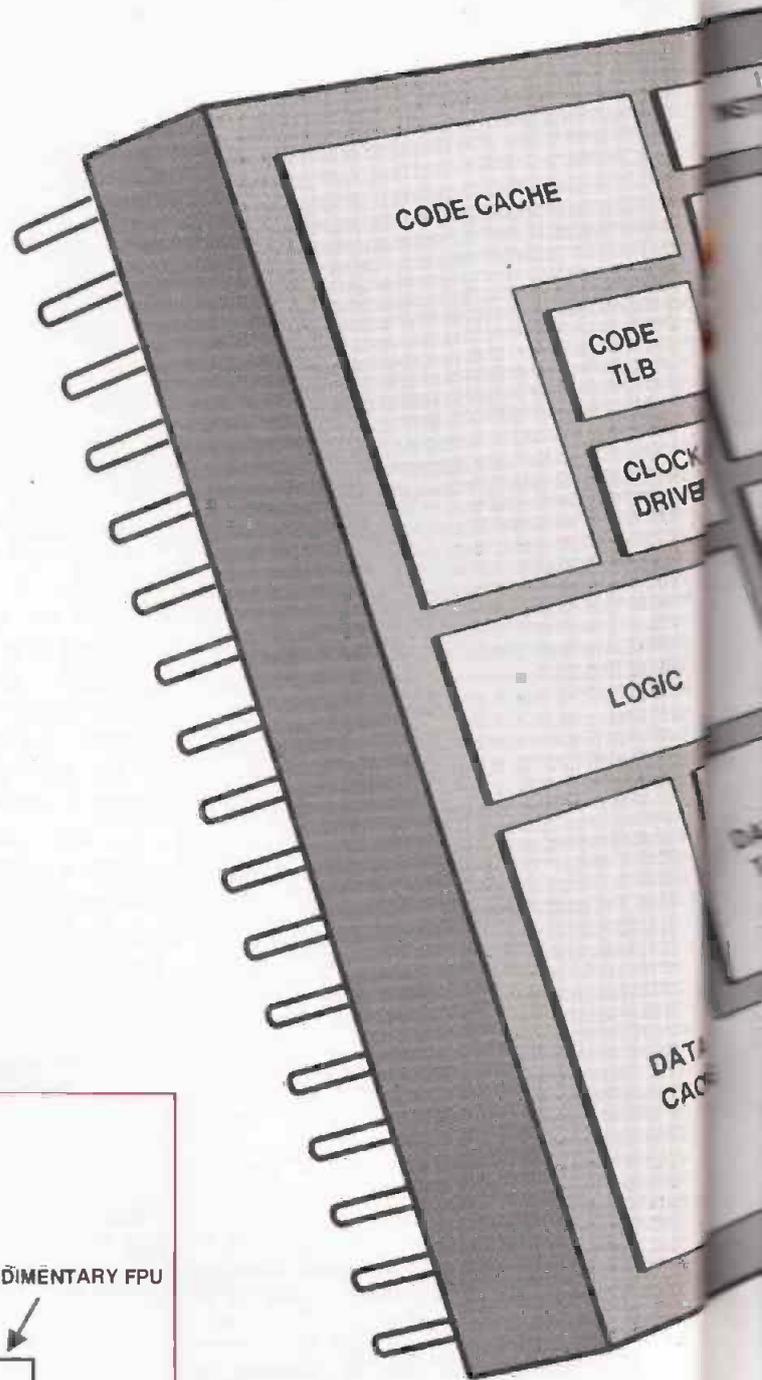This circuitry provides the complex synchronisation pulses, all



derived from the main system clock, which are necessary to ensure that the processor works properly.

Bus interface logic


This interface logic connects the address, data and control buses of the main system to those within the CPU.

Data TLB


Translation lookaside buffers for the data cache.

Data cache

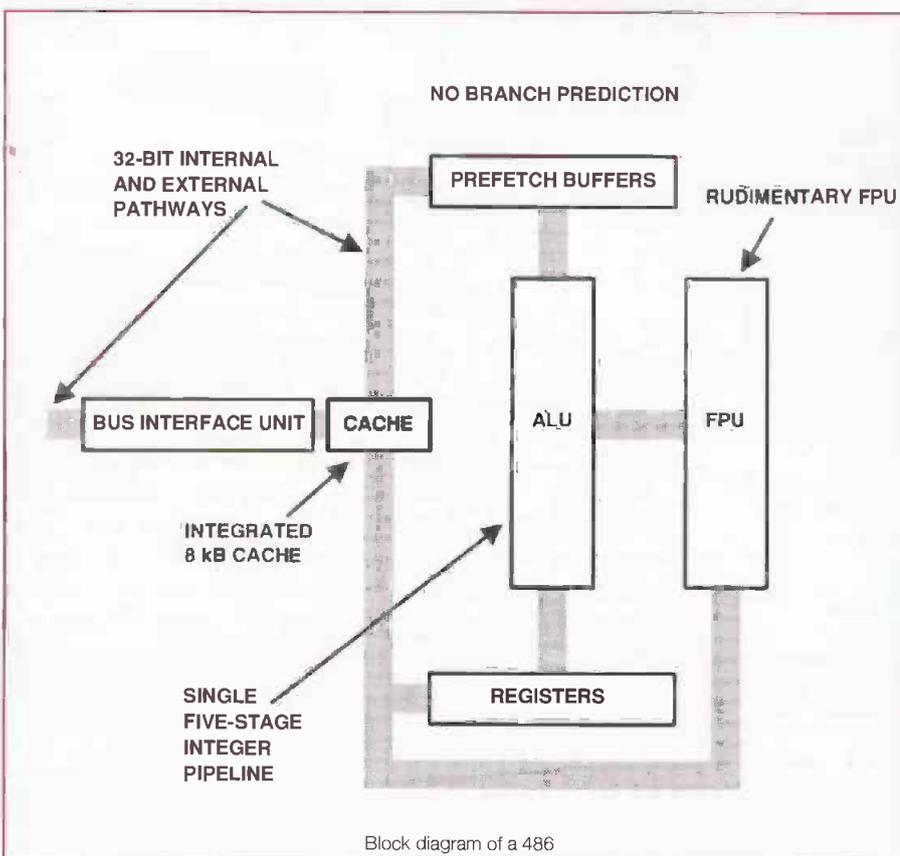To overcome the need to use wait states when accessing relatively slow RAM, the Pentium has a high speed 8KB data cache.



Block diagram of a 486

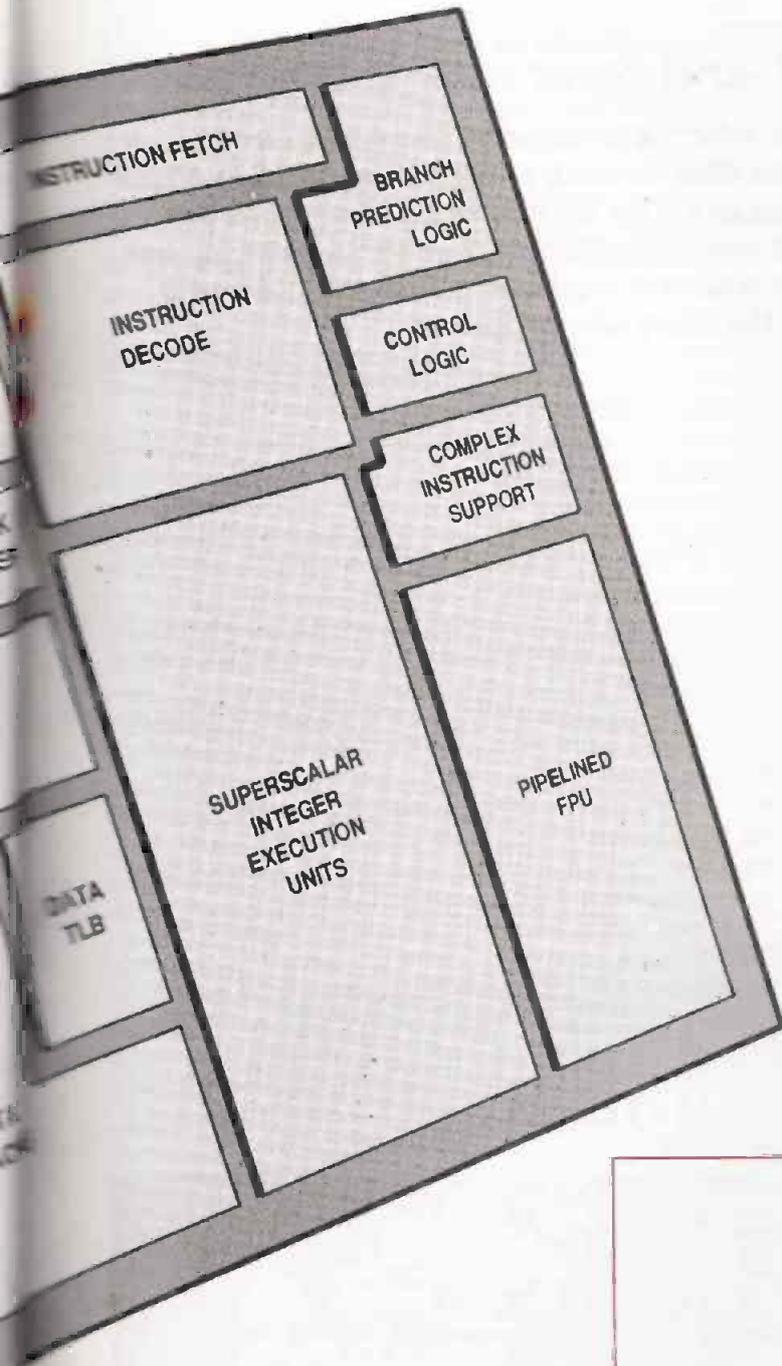

predictions. If the BTB prediction is wrong, then the pipeline is flushed and the correct instruction fetched, thereby causing a 3 clock cycle delay.

Control logic

The control logic circuitry handles the processor control bus and things such as interrupts, I/O requests, etc.

Complex instruction support

This is the part of the instruction decode circuitry which handles complex instructions that rely upon the ROM microcode. This circuitry can be regarded as a processor in its right, but one which is embedded within the much larger processor.

Pipelined FPU

This is a pipelined floating point arithmetic unit with dedicated addition and division circuitry. The use of dedicated circuitry means that no matter what the precision of the calculation, addition and multiplication is performed in just 3 clock cycles. Division will produce 2 bits of quotient per clock cycle. However, because of the pipelined architecture, it can actually achieve one addition or multiplication per cycle after the initial two cycle latency to fill the pipe is complete.

Superscalar integer execution units


In the Pentium, there are two parallel five stage integer pipelined arithmetic logic units. The fact that there are two integer ALUs means that the processor can fetch and decode two integer instructions at a time and, if possible, execute them in parallel. This means that when processing simple instructions, the processor's power can be considerably increased thanks to this parallelism.

Instruction fetch

There are two 32 byte instruction prefetch buffers, which process instruction addresses sequentially until it reaches a branch instruction. It then calls upon the branch target buffer to find the new instruction address.

Branch target buffer

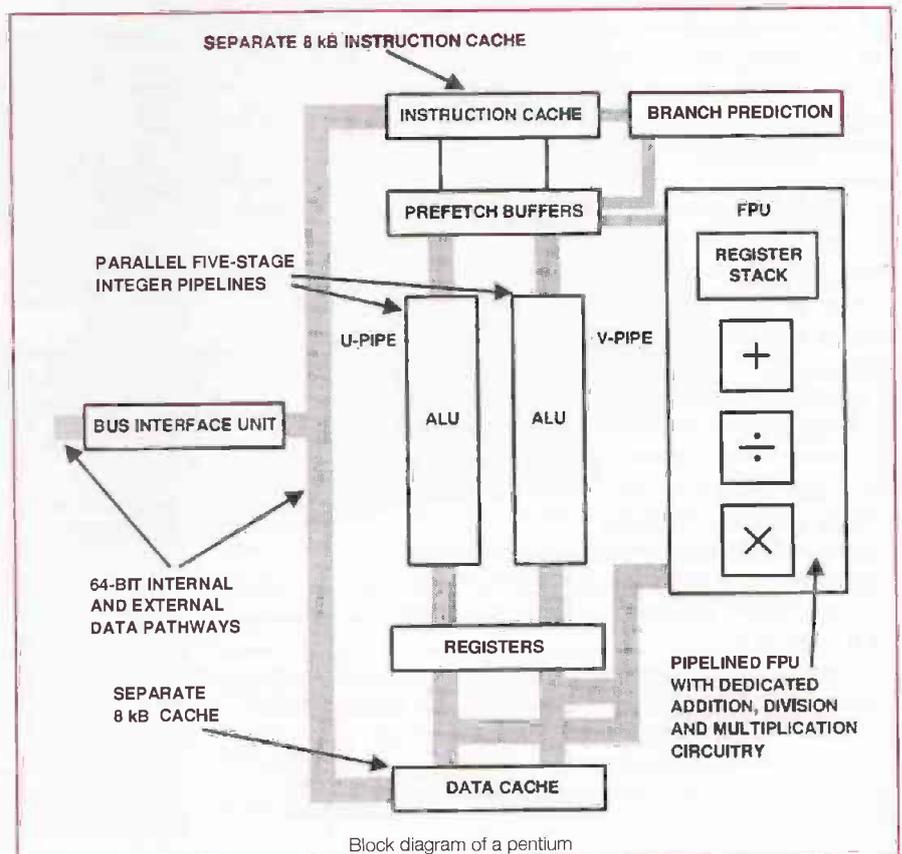The BTB contains information about previous branches and predicts whether the prefetched branch instruction will result in a branch or not. If not, then the prefetch will continue sequentially, otherwise the second prefetch buffer will begin to prefetch instructions based upon the BTB



Block diagram of a pentium

BIOS - what is it and how can it be used?

When any processor is first powered up, or when it is reset by the reset circuitry, it is incapable of using programs straight from disk. In fact, it will know nothing about the system of which it is a part. It will not even be able to input data from the keyboard or output data to the screen. The only information that the processor has coded into it is a single memory address where it expects to find the start of a program, or a pointer to the start of a program.

Because the processor cannot yet load data from disk, this power up/reset system initialisation program has to be stored in non-volatile memory. Because it performs the task of actually defining the system and because it is permanently stored in ROM, it constitutes what is often referred to as firmware.

The PC is no different to any other computer system in this respect and this initial program is known as the system BIOS. If you look carefully at the motherboard you should be able to locate the one or two ROM chips in which it is stored (they often have a printed label stuck on top of the chip which identifies the source of the BIOS).

The name BIOS stands for Basic Input/Output System. Initially, the BIOS was developed by IBM, but comparable versions of BIOS are now produced by a number of other manufacturers, foremost of which are AMI and Phoenix. The different types of BIOS are all more or less identical, although the system has changed slightly over the years and old versions of BIOS may not work properly with some modern software.

The first function of the BIOS program is to test the system, to check that all its various components are working properly. This is the so called Power On Self Test, or POST, feature. If any failures are found, then they are reported as coded signals output on a special POST output port (this can only be accessed if you have the appropriate hardware). Errors are also signalled as coded beeps from the system's internal speaker.

Having checked that the system is running properly, the BIOS software then sets up a basic input/output system which allows user programs to have easy access to all the system components, by simply communicating with the BIOS I/O routines. This gives all PCs a universal software interface, irrespective of the actual system design and thus allows software to be easily moved from one PC to another without any compatibility problems. It also makes it far easier for the programmer, since he does not have to write specialist routines to directly communicate with disk drives, video cards, etc.

The final function of the BIOS program is to act as a bootstrap loader for the main operating system. In most PCs, this would be MS-DOS, but it could equally well be DR-DOS, one of the many different flavours of UNIX, or OS/2. The bootstrap loader searches for the operating system on disk, loads it and then transfers control to it.

One thing to remember is that BIOS routines can be extended and regularly are. The video display card will probably have a ROM containing a set of routines which extend the function of standard BIOS so that it can handle the hardware of the particular video display. Similarly, a hard disk controller may have a BIOS extension on the card. These applications card extensions of BIOS allow the operating system and hence application programs to utilise these devices, despite the fact that they are all probably very different from each other.

As has already been mentioned, older versions of BIOS can cause problems. A fairly general problem is that they can restrict the type of hard disk that can be used. Other problems are more applications oriented, but on some older 286 ATs the BIOS may cause problems when attempting to run advanced operating

systems, in particular Windows 3.x. This is because the BIOS handles switching between real and protected mode operation and these early BIOSs were written before specifications on this operation were standardised.

Replacing the BIOS chip with a more modern version will unfortunately not do the trick and allow one to run this type of software - you will also need to replace the keyboard controller chip, since it seems that this chip is also involved in switching modes. Unfortunately finding any details of how the BIOS actually works is extremely difficult, a task made even harder for anyone living outside the US since all the BIOS producers are American.

However, unless you are involved in designing PC systems at firmware level, it is not really necessary to know about the inner workings of BIOS. What is important, however, is the fact that BIOS is the lowest level at which the system will operate. A system will run BIOS even without any functioning keyboard, display, or disk drives. This means that we can use BIOS to help us when attempting to repair a faulty system.

We can thus remove all the adapter cards and monitor the POST codes to prove that the motherboard is functioning properly, thereby proving that the fault lies in one of the adapter cards. If the motherboard, is faulty we can use the POST codes to tell us where the fault lies. A knowledge of BIOS can also be of considerable use when developing hardware and software which interfaces directly to the PC - it is the most fundamental level at which the system operates.

POST Error Beeps

Problem area	Sound sequence	Repeating short or continuous beeps
Power supply or system board		Repeating short or continuous beeps
System board, display board, or PSU		One long and one short beep
System board or power supply		One long and two short beeps
System board or power supply display		One short beep and blank display
Disk drive, disk controller, or cable for disk		One short beep and prompt for disk

Some of the more common POST Error Codes

Problem area	Error code number
System board	100-199
Battery error	161
Configuration error	162
Time and date error	163
System options not set	165
Memory error	200-299
Keyboard	301, 303, 305
Keyboard fuse	305
Parallel port	401
Floppy disk drive	600-699 (except 602)
Reference disk	602
Math coprocessor	701
Serial port	1100-1299
Hard disk drive	1700-1799
System board video	2400-2499
Pointing device	8600
Hard disk drive	10400-10499

Using a POST probe card to check processor status

When you boot up your PC, one of the first functions of the BIOS routines is to perform a range of Power On Self Test, or POST, routines. These POST routines will check every part of the PC, the memory, the communications ports, the keyboard, video display and the disk drives. Unless your machine is faulty you will in most cases not be aware that the tests are taking place. Remember the way that your keyboard lights flash and the double beep before the hard disk is accessed and DOS loaded? These are the POST routines at work. However, if your machine is faulty, POST error codes could provide you with a valuable and accurate guide as to what is wrong.

There are three different ways in which the BIOS POST routines will tell us what is wrong with the system. The first is that it will generate a sequence of beeps on the internal speaker, with the beep sequence roughly indicating the fault area. The second way relies on the video display functioning, and POST generates one or more error messages which indicate where faults have been located.

The third way is probably the most powerful, since it can be used to diagnose faults in a motherboard without functioning video display or keyboard. Here, the error codes are output through an I/O port (on most EISA and ISA systems this is port 80) and can be displayed using a special plug in adapter card, commonly referred to as a POST card. The error codes displayed on the POST card's two digit hexadecimal display can be used to accurately pinpoint a fault to a specific area of the motherboard, or even a specific component.

At some stage in their lifetime, most PCs will generate some sort of POST code error. This is particularly likely to happen when adding or removing expansion boards or altering the configuration. It is also likely to happen when the internal battery fails and needs replacing. The fact that these can all cause POST errors means that whenever a POST error is encountered, the first step is to check that the batteries are OK, that all adapter cards are inserted properly, as are all cables and that the system configuration is correct. Only then should one start looking for faults.

The first step in any fault locating procedure using a POST card is to check the power supply to the system board (with the Micro 2000 POST card this is easy since the card has a built in logic probe and voltage test circuitry). Next, try removing and reinserting adapter cards in order to ensure that they are not the cause of the problem (not forgetting to switch off the power every time you remove or reinsert a card).

If you still have no luck, then power down the system, remove all the

adapter cards one by one, except the POST card, reapplying power between each card removal. If the symptoms stay the same then the motherboard is probably failing. It is here that the POST card really comes into its own, since without it, problems can be very hard to track down. Shorts are a major source of problems and using the area indicated by the POST error code can be further traced with the aid of the logic probe.

First check the supply voltage and ground leads to the suspect chip. If a voltage is missing, then trace the line to its source. Shorts may be produced by defective resistors, ICs, or decoupling capacitors. In fact, such capacitors should always be checked, since this can be the cause of the failure.

With a POST card, it is a lot easier to track down and repair faults on a PC system board and it is surprising how often a fault is caused by the failure of a very cheap and easily replaced component. If you know what you are looking for, there is often every chance that a faulty board can be successfully repaired - forget those people who say that it is not worth doing and far better to just chuck the board away and replace it with a new one.

Note that this table can only be approximate, since the exact error codes used are different for each type of BIOS and for each type of hardware platform. Thus POST code 04 in Phonex BIOS signifies an error with the 8253/4 programmable interval timer chip, on the C&T BIOS that the 8237 DMA controller has failed and on AMI BIOS that there is a fault either with the 8259 programmable interrupt controller or with the CMOS RAM.


In order to get detailed information from the POST codes, it is

essential to have a list of the codes and their associated errors for the version of BIOS installed in the system under test. In most cases, the BIOS POST diagnostics are very accurate, since individual versions of BIOS are specifically tailored to individual hardware designs. However, it should be noted that some versions of BIOS, in particular AMI BIOS, are written for a wide variety of boards with the same chipset, meaning that although generally correct, some codes may point to the wrong error.

For anyone involved in serious PC maintenance and repair a POST card is a good investment since it makes tracking down most faults on a PC a lot easier. A good example of such a card is the Micro 2000 POST Probe card and its associated diagnostic software, with which one can track down faults at all levels of functionality, even faults on boards unable to produce POST codes.

For more details on the POST Probe card contact Micro 2000 in Letchworth, on 0462 483483.

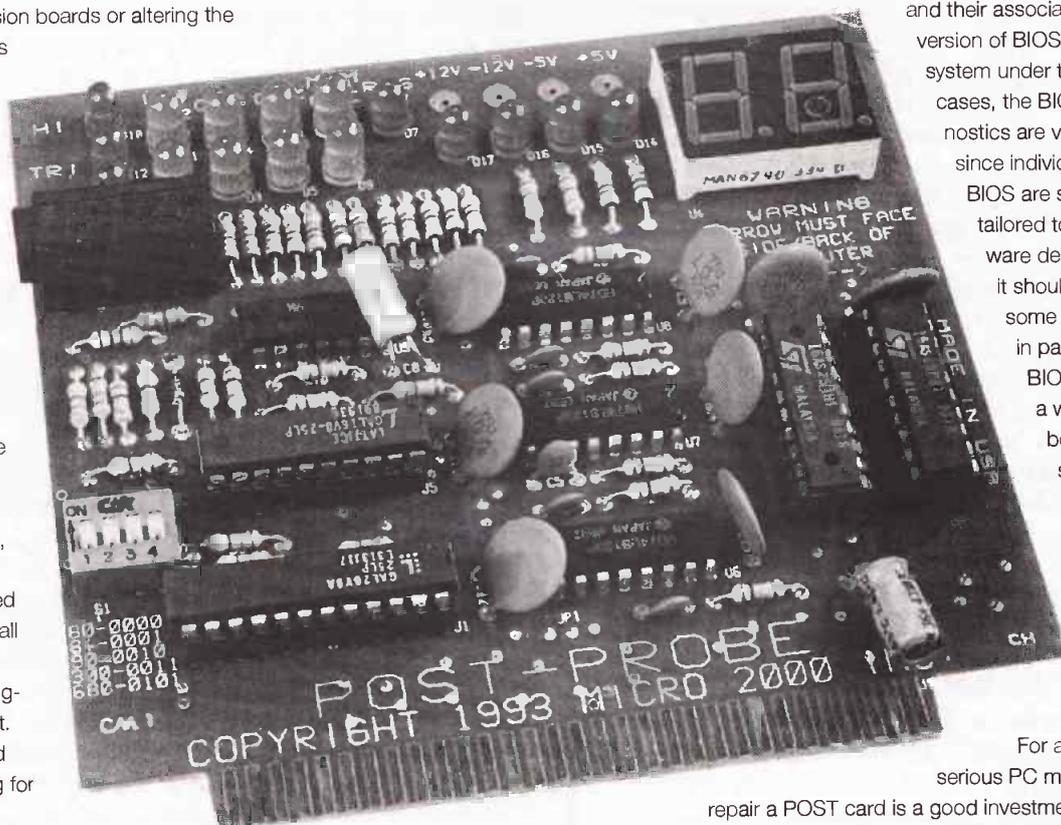Watch out in future issues of ETI for our special build it yourself POST card project!



Cache Memory

Over the last few years, we have seen processor clock rates go up from 12MHz on a 286 AT to 66MHz on a Pentium or 486DX2 system. At the same time we have seen the amount of RAM in a system go up from 640K to 4, 8, or even 16+ MB, and the amount of hard disk storage go up from 20MB to 200MB or more. By any standard, a modern PC is thus an extremely powerful computer.

However, despite the powerful processor, lots of memory and a big disk we can no longer say that the performance of one make of PC is much like another, simply because it has the same processor, runs at the same speed and has the same general architecture. You only have to look at the benchmarks published by some of the PC magazines to realise this.

The truth is that, as well as bringing enormous processing power, high speed systems have also brought with them a lot of problems for the computer system designer. Problems which, in the way that they are solved, or are not solved, can make enormous differences to the performance of seemingly similar systems.

The problem with bottlenecks

The main reason for these design problems lies in the bottlenecks which can occur in the flow of data and instructions between the processor and the various types of memory used in the system. Bottlenecks can seriously reduce the actual processing power of the system, compared with its theoretical potential power and are moreover exacerbated by processor intensive applications such as Windows, CAD and DTP systems.

The reason that these bottlenecks exist is fairly simple. They are due to the fact that parts of the system are working much faster than data can be accessed from, or stored to, other part of the system. Thus, the access time of a standard RAM memory chip is longer than the fetch cycle of a 66MHz 486, the result being that the processor has to wait maybe two or three clock cycles for memory to be accessed. If we take statistical standard usage of a system with standard reasonably fast RAM, then the effective speed of a 66MHz system is reduced to an equivalent of one running at less than 55MHz, simply because the processor has to wait for memory.

• The result of having a processor that is too fast for the available memory is quite a serious reduction in power. Computer system designers try to overcome these slow access speed related bottlenecks by using a special type of memory known as cache memory.

Cache memory is simply a block of memory which works at a higher speed than the ordinary RAM memory. By transferring the block of data and/or instructions currently being used into this cache memory, it is possible to eliminate a high percentage of the delays that would otherwise occur. This makes it possible for the system designer to more closely approach the theoretical maximum power of a given processor.

Memory hierarchy

In order to understand how cache memory works, we need to look at how a computer uses different types of memory. We can divide the memory resources of a computer into a

hierarchy and on most systems there are two levels - short term, fast access RAM memory and long term, slow access, disk memory.

No programmer would attempt to write a program which ran directly from disk memory, in theory it could be done, but it would be terribly slow. Instead, the program stored on disk is transferred to RAM memory and run from there. The same applies to data - rather than slow down the system by accessing the disk directly for each byte of data, a whole block of data is transferred to RAM memory and accessed there.

The function of a CPU cache is to add another one or two levels to that hierarchy, which lie above RAM memory. At the highest level is the primary, or on chip, cache. The 486 has an 8KB cache on the processor chip and the Pentium has two 8KB caches. The level below this and immediately above RAM memory is the external or secondary CPU cache, which consists of between 64K and 1MB of very fast static RAM.

If we think of RAM memory as being short term memory, then the primary and secondary CPU caches are a type of selective memory in which are stored the most commonly requested pieces of program code and data. Thus, when the processor accesses instructions or data from main memory, a copy is simultaneously transferred to cache memory and all future accesses to that information will be to cache memory rather than main memory. This means that only the first access will be slowed down, all subsequent accesses will be at top speed. So, the more primary cache memory that is built into the actual processor chip, the better the overall improvement in performance. There are, however, limits to the amount that can be put on a processor chip, and anyway it is pre-set by the chip manufacturer, hence the need for external cache memory. Once again, a simple statement such as 'the system has 256K of cache' is insufficient to indicate performance quality, although of course, broadly speaking, the larger the cache the better the performance improvement.

Cache operation

The type of cache design used is very important, since there can be very significant differences in performance between different designs, especially when the cache is fairly small. There are three commonly used secondary CPU cache designs, fully associative cache, direct mapped cache and set associative cache. Of these, the fully associative cache is too slow for today's processors.

The cheapest and easiest design for a manufacturer to implement is the direct mapped cache, but this will only offer good performance if it has been properly designed. Indeed, if badly designed, a direct mapped cache can actually degrade a system's performance so that it is worse than a cacheless system. This is the result of a process called thrashing and can be a really serious problem when running multi-user operating systems.


Set associative cache offers all the best features of the other two designs but with few of the associated problems. It is fast and flexible and this technique has been used by the Intel designers for the primary processor cache on the 486 and Pentium. It is also the favoured design among top range PC manufacturers and is particularly good with multitasking operating systems.

Next month...

In PC Clinic next month we will be looking at how memory is used and organised in a PC, at upgrading the memory in your system and at tracking down elusive memory faults

POWERFUL SCHEMATIC CAPTURE, PCB DESIGN AND AUTOROUTING ALL FOR JUST £395...

PROPAK AR for DOS provides all the features you need to create complex PCB designs quickly and easily. Draw the circuit diagram using the powerful facilities of ISIS DESIGNER+ and then netlist into ARES AUTOROUTE for placement, autorouting and tidy up. Advanced real time design rule checks guarantee that the final PCB will correspond exactly with the schematic thus saving you from costly layout errors and time consuming debugging.

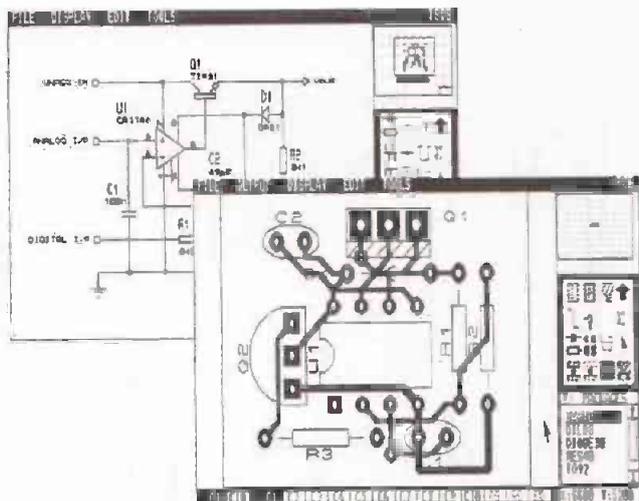

- Attractive, easy to use graphical interface.
- Object oriented schematic editor with automatic wire routing, dot placement and mouse driven place/edit/move/delete.
- Netlist generation for most popular CAD software.
- Bill of Materials and Electrical Rules Check reports.
- Two schemes for hierarchical design
- Automatic component annotation and packaging.
- Comprehensive device libraries and package libraries including both through hole and SMT parts.
- User definable snap grids (imperial and metric) and Real Time Snap to deal with tricky SMT spacings.
- Manual route editing features include Auto Track Necking, Topological editing and Curved tracks.
- Autorouting for single, double and multi-layer boards.
- Non autorouting PROPAK is available for just £250 if you do not need or want the router.
- Full connectivity and design rule checking
- Power plane generator with thermal relief necking.
- Graphics support to 800x600 Super VGA.
- Output to dot matrix and laser printers, HP and Houston plotters, Postscript devices, Gerber and Excellon NC machines plus DXF and other DTP file formats.

CADPAK Two Programs for the Price of One

ISIS SUPERSKETCH

A superb schematic drawing program for DOS offering Wire Autorouting, Auto Dot Placement, full component libraries, export to DTP and much more.

Only
£79


Exceptionally easy and quick to use. For example, you can place a wire with just two mouse clicks - the wire autorouter does the rest.

PCB II

High performance yet easy to use manual PCB layout package. Many advanced features including curved tracks, auto track necking, DXF export, Gerber and NC file generation, Gerber viewing and more.

Alan Chadwick writing in ETI (January 94) concluded...
"At £79 I thought this was an excellent buy."

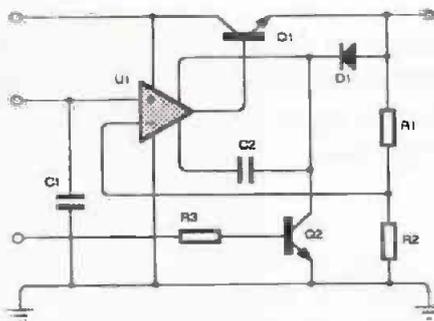ISIS ILLUSTRATOR Schematic Drawing for Windows



From
£99

Running under Windows 3.1, ISIS ILLUSTRATOR lets you create presentation quality schematic drawings like you see in the magazines. Furthermore, when the drawing is done, transferring it to another document is just a matter of pasting it through the Clipboard.

Now used by a number of prominent technical authors to illustrate their latest books and magazine articles.

labcenter
Electronics




WE HAVE MOVED - NOTE NEW ADDRESS

Call us today on 0756 753440 or fax 0756 752857 for a demo pack - state DOS or Windows. Multi-copy and educational discounts available.

Prices exclude p&p (£5 for U.K.) and VAT. All manufacturers' trademarks acknowledged.

53-55 Main St, Grassington, North Yorks. BD23 5AA.

VIDEO LIGHT METER

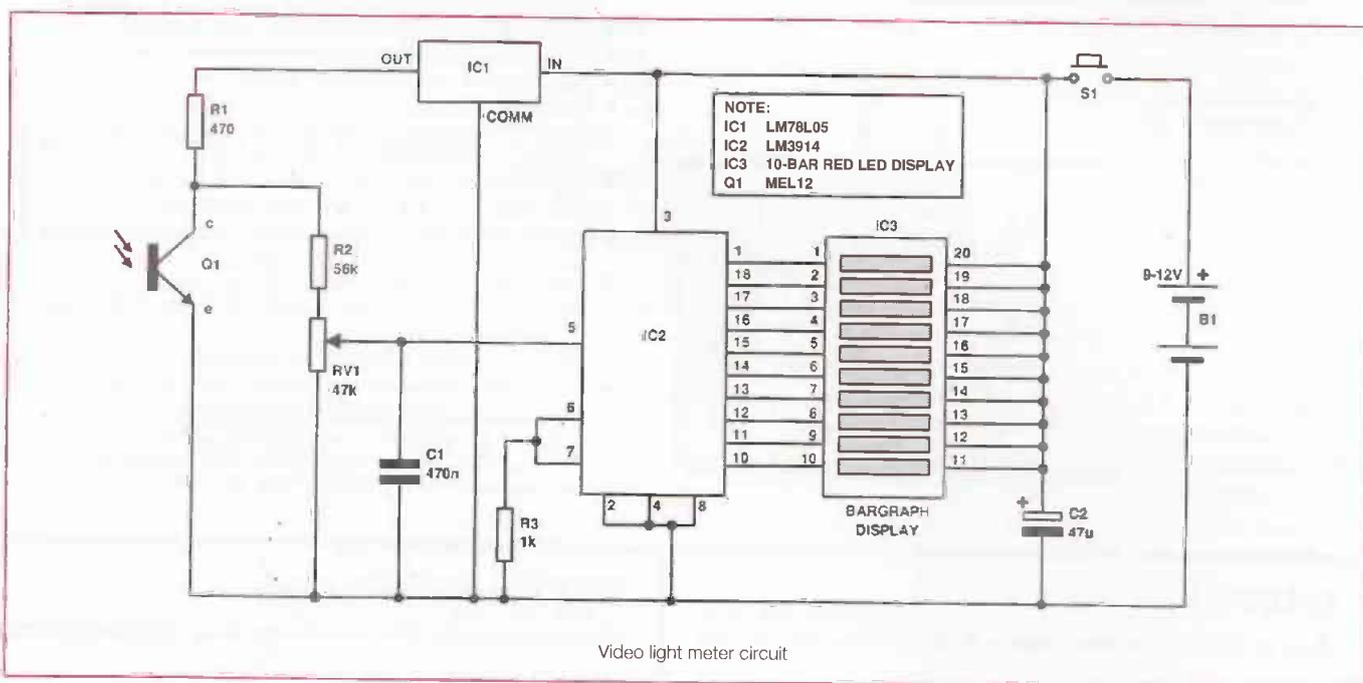

Is it bright enough for good camcorder pictures? Terry Balbirnie's light 'meter' will tell you - instantly!

Modern camcorders will operate in extremely low light levels. However, the picture quality is often not very good under these conditions - a fact avoided in the advertising hype. Although some models do perform better than others, insufficient light shows itself with grainy pictures and degraded colours. The black-and-white viewfinder picture gives little indication of performance. Poor recordings will only show up when the tape is played back through a full-size colour TV and it may then be too late for a re-take. If the camera operator had been made aware of the problem at the outset, some extra

light could have been laid on or the shots, arranged to exploit the existing light more effectively. Without a lot of practice, the eye itself is not good at judging light intensity, because of its ability to adjust to the conditions.


This Video Light Meter will indicate the ambient light level and hence the performance to be expected from the camcorder. In use, it will normally be pointed from the subject position towards the light - that is, it measures incident light. When a push-button switch is operated, one of the LED bars in a display glows to indicate the brightness. Since no current is drawn until the switch is pressed, and even then less than 30mA, a miniature battery will have a very long life.




Circuit Description

The Video Light Meter comprises four main parts - the light sensor itself, bargraph driver, LED display

and stabilised supply for the light-sensing section.

Figure 1 shows the complete circuit diagram. The light

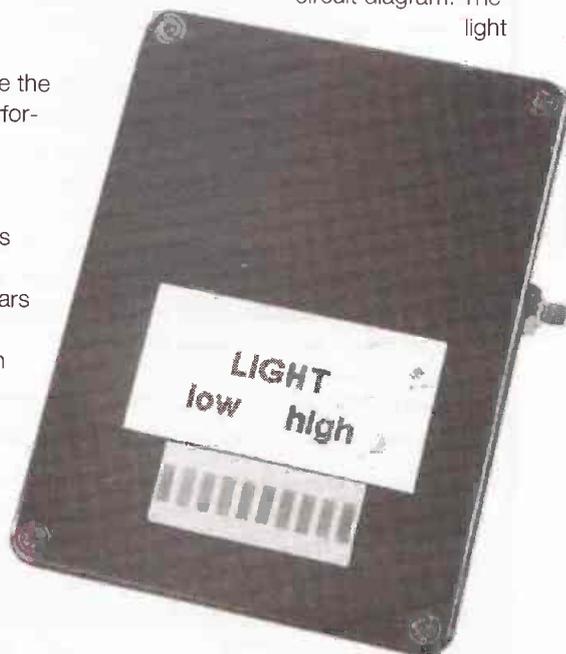


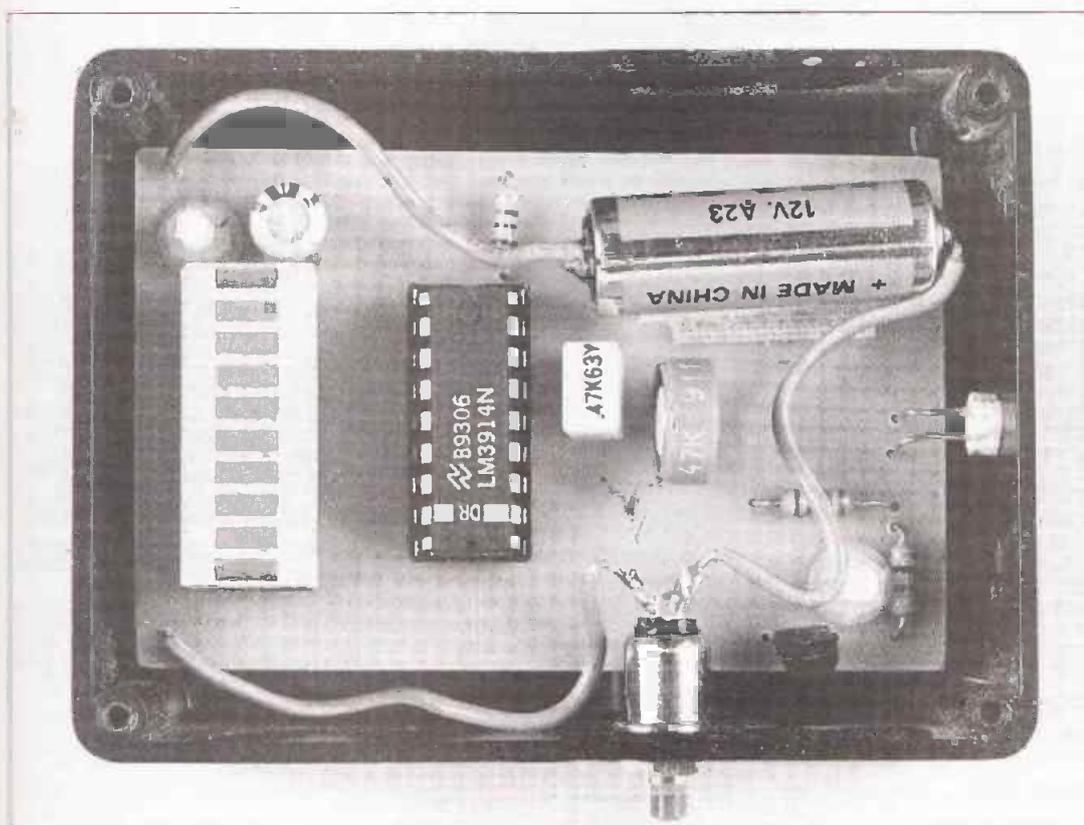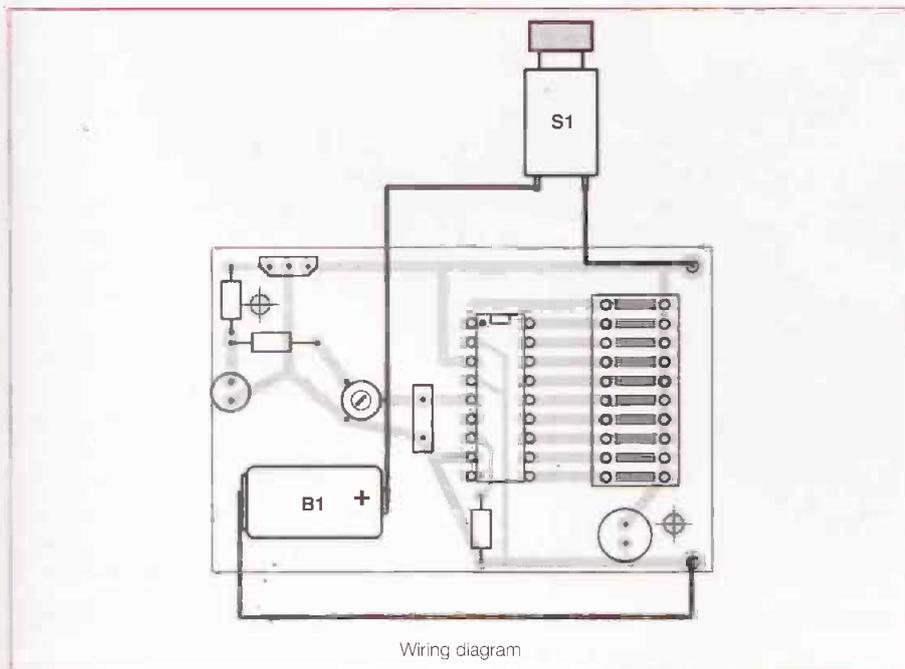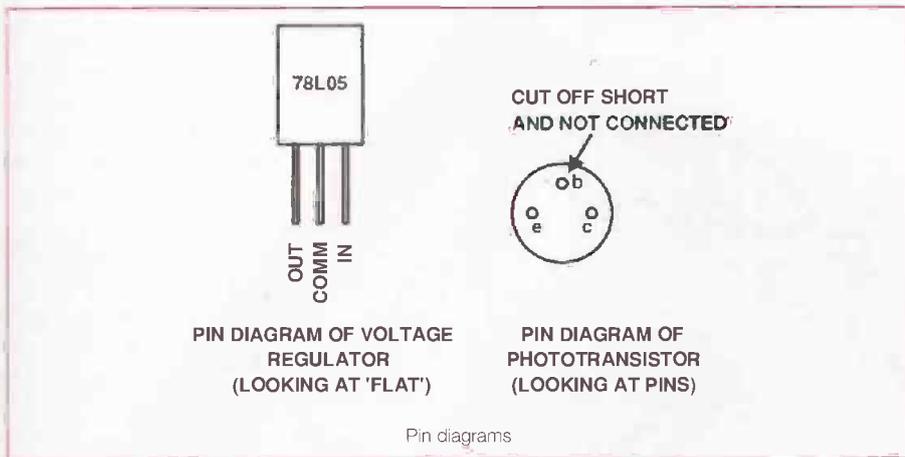

sensor is phototransistor, Q1, which has a window in the end that allows light to enter and strike the base-collector junction. The effect is equivalent to a photo diode and the light causes a small current to flow, which is subsequently amplified by transistor action. The brighter the light, the higher this current will be, up to a point. Increasing light intensity will therefore cause an increasing current to flow through load resistor, R1, and this will result in a greater voltage being developed across it. A falling voltage will then appear between Q1 collector and emitter. It is this reducing voltage which operates the rest of the circuit. Note that no bias is needed for the specified phototransistor, so the base is left unconnected.

The circuit is powered by a 9V or 12V battery. However, the phototransistor section is fed from a 5V supply derived from voltage regulator IC1. Without this, the voltage between Q1 collector and emitter would decrease as the voltage available from the battery fell with age. This would be interpreted by the rest of the circuit as brighter light and would upset the bargraph operating points. As it is, the circuit will operate correctly until the regulator fails to deliver a 5V output. This will happen when the battery voltage drops below 7V approximately. After that, the regulator output voltage will fall in sympathy. It is therefore necessary to check the battery every so often and the method for doing this is described at the end.

With phototransistor Q1 in bright light, approximately 0.7V will be developed between its collector and emitter. As the light level falls, it will approach that of the supply, i.e. 5V. This voltage is scaled down by the potential divider consisting of fixed resistor, R2 and preset potentiometer, VR1. It is then applied to the input, pin 5, of bargraph driver IC2. This device accepts a smoothly changing voltage so that as it increases, successive outputs 1 to 10 (pin 1, then pins 18 to 10 respectively), go low in turn to provide current sinks. The first output operates at 0.125V and the tenth one at 1.25V, so the

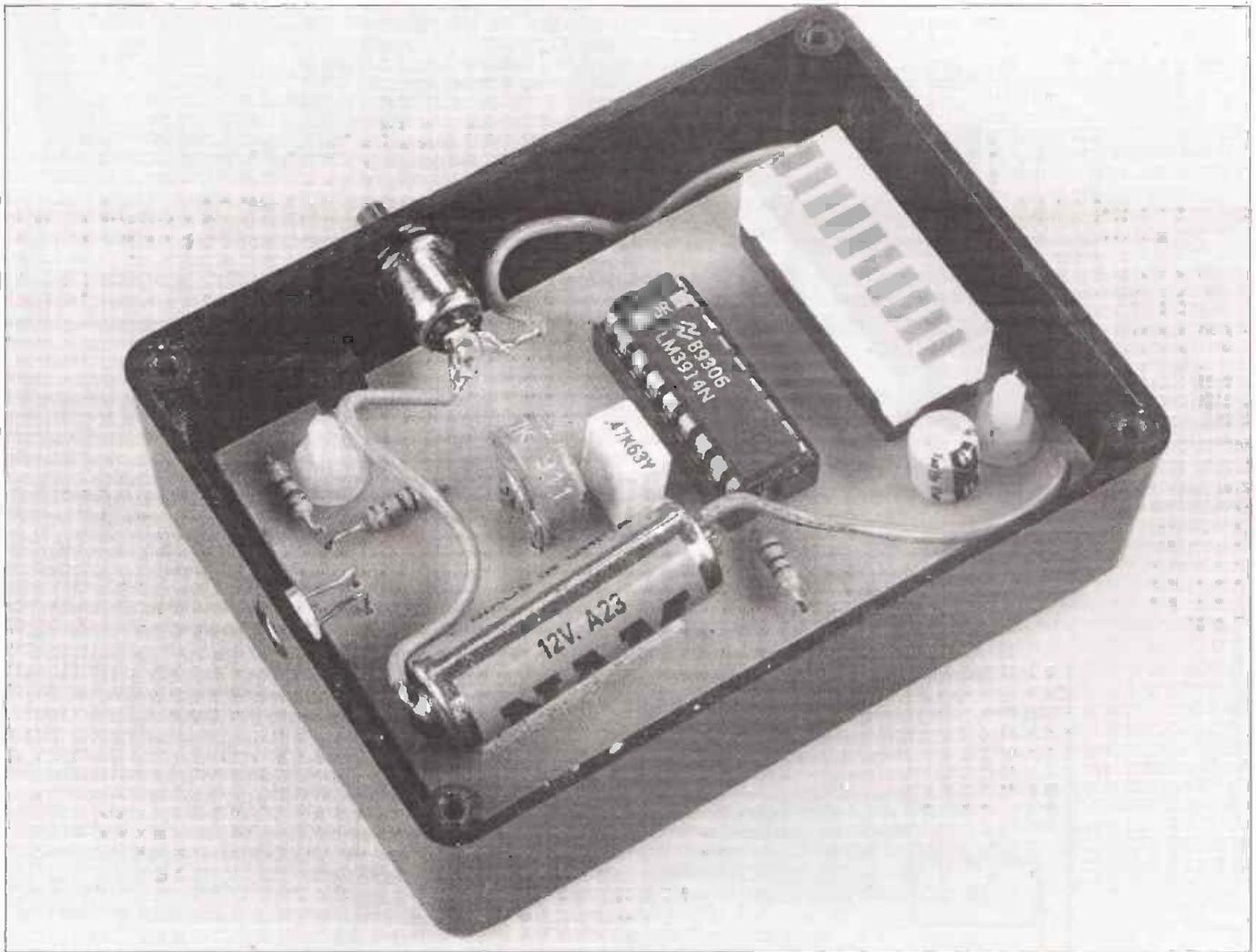

voltage provided by Q1 collector needs to be divided by four. This is achieved when VR1 wiper is at approximately mid-track position. However, the voltage at the wiper may be adjusted through wide limits. This provides the adjustment for the correct operating levels and will be made at the end of construction.

Capacitor C1 promotes stable operation.

The bargraph display, IC3, consists of ten horizontal LED bars. All the positive (anode) ends - pins 11 to 20 respectively - are connected together and hence to the positive supply rail. The other (cathode) ends of the LEDs (pins 1 to 10) are connected to the corresponding IC2 outputs. As each output goes low, the corresponding LED bar glows. No conventional series resistors are required since current-limiting is carried out on chip with R3 determining the LED operating current, in this case 13mA approximately.

Construction

Before proceeding, decide on the type of box to be used as an enclosure. This will depend on the size of battery being used. Any small 9V or 12V battery will be

suitable. In the prototype unit, a sub-miniature cylindrical 12V battery of the type used in cigarette lighters was chosen (see Parts List). Using this allows the small plastic box specified in Buy Lines to be used. A PP3 battery may be used if preferred, but the box will need to be larger.

Construction is based on a single-sided PCB and Figure 2 shows full topside details (parts placement diagram). Drill the two mounting holes then solder the two IC sockets into position. Follow with all fixed resistors (flat with the board), capacitors, C1 and C2 (observing the polarity of C2), preset VR1 and voltage regulator IC1 (taking care with the orientation, see Figure 3). Cut Q1 base lead short and gently bend the other two leads at right-angles (see photograph). Solder Q1 into position, so that its top points to the left. Do not insert IC2 or IC3 into their sockets yet. Adjust VR1 to approximately mid-track position.

Solder 8cm pieces of light-duty stranded connecting wire to the pads marked 'S1' and 'Batt -'. If a PP3 battery is being used, solder the negative wire of

the battery snap to the pad marked 'Batt -'. Drill the holes in the case for the switch and for circuit panel mounting. Insert IC2 and IC3 into their sockets. It would be wise to touch something which is earthed, such as a water tap, before handling IC2 pins, because this device is static sensitive. The product lettering on IC3 as used in the prototype was on the right hand side - if it is inserted the wrong way round, it will not work.

Mount the circuit panel temporarily and carefully measure the position of IC3. Make a hole in the lid of the box directly above this and the same size. Mount the panel on short stand-off insulators so that when the lid of the case is in position, the display is level with the face of the box. Mark the inside of the box opposite Q1 position, remove the circuit panel again and drill a hole with the same diameter as Q1 at this point. Fit the switch and complete the wiring as shown in Figure 4. Replace the circuit panel and adjust the phototransistor leads so that its face protrudes slightly through the hole drilled for the purpose.

If the sub-miniature 12V battery is used as in the prototype, mount it in the

free area of the circuit panel, as shown in the photograph, using a pair of Velcro fixing pads. The connecting wires may be soldered to its terminals using minimum heat from the soldering iron. A PP3 battery could be secured to the base of the box in the same way.

Testing

A basic test can be made by pointing the sensor towards bright light and pressing the switch. By slowly covering the hole with a finger, there should be a response from the LED bars. If this test works, it is then only necessary to adjust VR1 for correct operation. The lid of the case will need to be in position (although not screwed down yet) so that Q2 receives light only through the hole. Adjustment to VR1 is made in a series of small steps with the lid replaced after each one. Cover the sensor with black tape to prevent all light reaching it. It will probably be found to be impossible to adjust VR1 so that all LED bars are off. It will therefore be set for the first bar to represent total darkness. Press the button and adjust VR1 so that the first bar is on and just before the point of changing to the second one.

Set the camcorder on a tripod and zoom in on a detailed picture such a colour magazine advertisement pinned to a wall. Vary the amount of light in the room and make some test recordings to determine the level at which picture quality just begins to degrade. Point the sensor towards the camera from the subject position and note which bar operates. The other bars may then be interpreted and labelled. Colour-coding could be used, possibly red, orange and green, but this was not thought worthwhile in the prototype. Note that it is normal for there to be a slight overlap so it is possible for two adjacent bars to be illuminated at once. After making any final adjustments to VR1, it only remains to secure the lid and put the Video Light Meter into service.

The device may also be used in reflected light mode, by pointing the sensor towards the subject. Experiment to find out which method gives the best results.

Battery Check

The condition of the battery should be checked every so often. To do this, cover the sensor so that no light can enter. Press the button and observe the display. The first bar should light. If a higher one glows, the battery must be replaced.

PARTS LIST

Resistors

- R1 470
- R2 56k
- R3 1k
- VR1 47k

Capacitors

- C1 470n ceramic
- C2 47µ 16V PCB electrolytic.

Semiconductors

- Q1 MEL12
- IC1 LM78L05
- IC2 LM3914
- IC3 10-bar red LED display


Miscellaneous

- S1 Miniature push-to-make switch
- B1 Miniature alkaline 12V battery type GP23A or PP3 battery and battery snap (see text).

18-pin d.i.l. socket; 20-pin d.i.l. socket. PCB materials, plastic box

Buy Lines

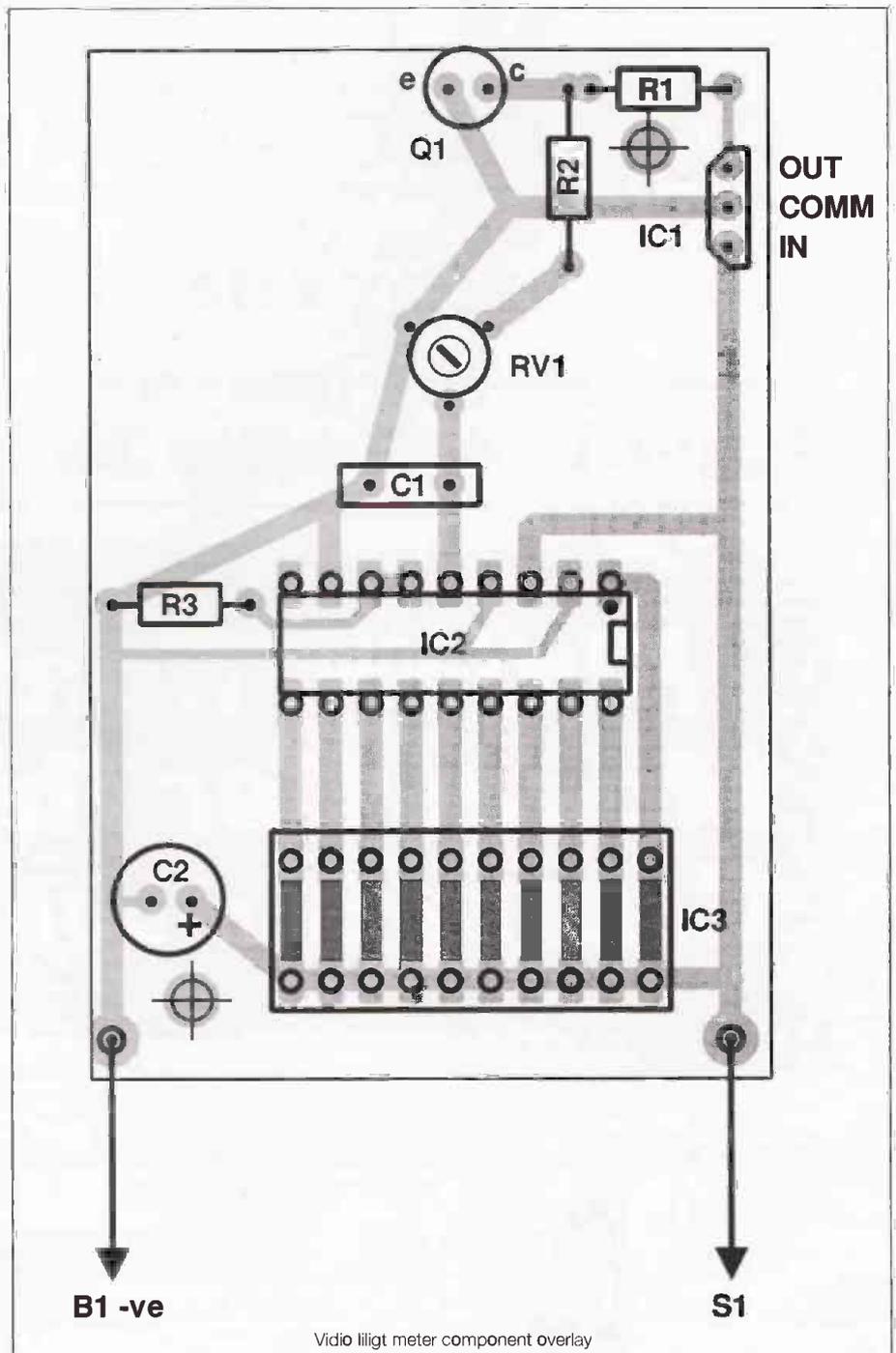Most of the components for the Video Light Meter are freely available. The MEL12 phototransistor may be obtained from Maplin. The box used in the prototype was type T2 size 75 x 56 x 25 mm from Maplin. A larger one will be needed if a PP3 battery is used.



Why not make a date?

INTERNATIONAL
**MODEL
SHOW**
GOOSEDALE

Moor Road, Bestwood (M1 Junction 27)
NOTTINGHAM

10am - 6pm

Saturday & Sunday 30/31 July 1994

***Flying, Boating,
Model Car Racing,
Crafts & much more...***

Flying - KING TEAM & TEAM ZAHN Trade displays

ENTRANCE: Adult £4, Children & Senior Citizens £2.50, Family £10 (2 adults & up to 4 children)



ORGANISED BY

**THE
INTERNATIONAL
MODEL
CENTRE**

FURTHER DETAILS FROM ARGUS SPECIALIST EXHIBITIONS
ARGUS HOUSE, BOUNDARY WAY, HEMEL HEMPSTEAD, HERTS HP2 7ST TEL: 0442 66551

At last, a fully functional upgradeable PCB CAD system to suit any budget. Substantial trade-in discounts are available against other "professional" PCB design packages ...

... call now for details.

Board Capture

Schematic Capture Design Tool

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

£395

BoardMaker

BoardMaker1 - Entry level

£95

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount and metric support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

BoardMaker2 - Advanced level

£295

- All the features of BoardMaker1 +
- Full netlist support - BoardCapture, OrCad, Schema, Tango, CadStar and others
- Full Design Rule Checking
 - both mechanical and electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC

NEW

Board Router


Gridless re-entrant autorouter

£200

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

Output drivers - Included as standard

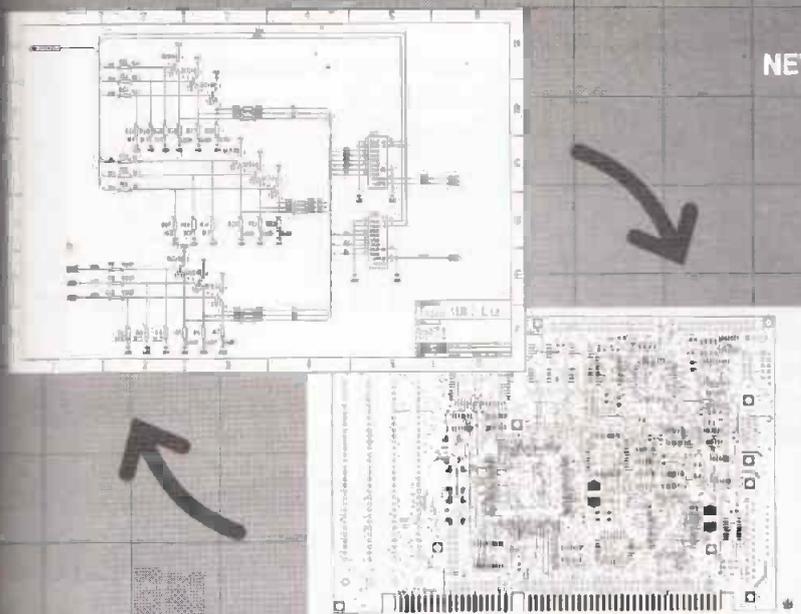
- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill and Annotated drill drawings (BM2)



Call, write or fax for more information or a full evaluation kit

Tsien (UK) Limited
Aylesby House
Wenny Road, Chatteris
Cambridge
PE16 6UT

Tel (0354) 695959
Fax (0354) 695957

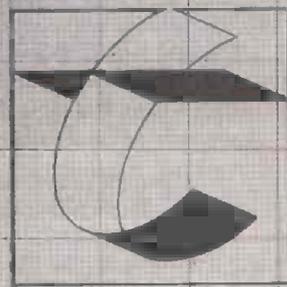

tsien

MAGNETISM AND MAGNETOMETERS

Magnetism is a subtle and mysterious force that influences a lot of things around us. Keith Garwell embarks on a practical exploration of how to measure minute changes in a magnetic field

For the radio enthusiast, changes in the earth's magnetic field can be used to indicate likely changes in propagation. For the astronomer, the same changes are likely indicators to the advent of auroras and similar heavenly signs. Down to earth, measurements of local magnetism are very helpful to the archaeologist, amateur or otherwise. Unfortunately, while one can go into many a local shop and buy a combination voltmeter/ammeter/ohmmeter for only a few pounds, one cannot easily go into one's local emporium and buy a magnetism meter (magnetometer) and certainly not for a few pounds. Hopefully, I am about to redress this balance, at least in part.

Before delving into the nitty gritty, it may be as well to know something of what we are talking about.

The first dreadful shock to older readers will be to discover that Gauss is out and a new unit is in, to wit the Tesla. This is a very large unit - the field which would generate 1V along a wire 1m long moving at 1m/sec.

If you cast your mind back to the classroom, you will hopefully remember that the earth's magnetic field has a horizontal component that appears just West of North. Indeed, if you look at your friendly large scale Ordnance Survey map you will find a note giving the deviation between true North and Magnetic North, the Magnetic North being currently some 5 degrees West of true North.

You may also be able to remember something about the 'angle of dip'.

Imagine an ordinary magnetic compass mounted on its side so that the needle could point downwards. Orienting the compass case North/South would leave the needle pointing downwards at an angle of some 67° to the horizontal. Remember, these are approximate UK figures, they differ both locally and globally.



If you think about it, this is all fairly reasonable as the North Pole isn't really where the compass is pointing when it is hori-

zontal, because it will be at a tangent to the earth's surface and the earth being a sphere, it will be pointing out into space. Only if it were pointing downward as well would it be pointing to the true (well, nearly) origin. However, everybody is used to compass needles which only rotate in the horizontal plain and it's much more convenient too.

Figure 1 suggests the situation. Unfortunately, if drawn to scale the situation gets worse. The line set by the dip angle points to the interior of the earth. In fact the source of the earth's field is believed to be due to some form of dynamo effect within the earth's core which has a very high iron content.

This is expected to be a fluid or semi fluid movement which will perhaps account for the continuous change in position. My Ordnance Survey map shows the yearly change as 9 minutes of arc to the East.

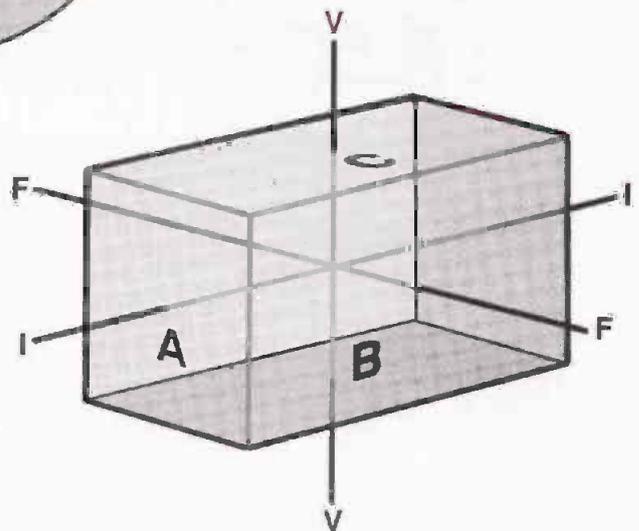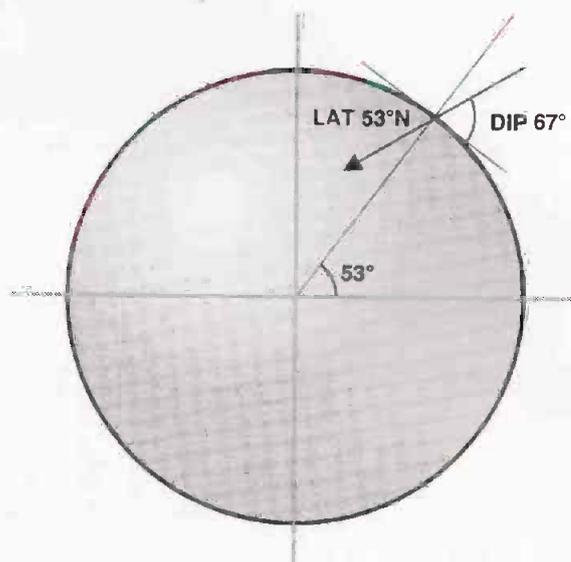The earth's field, or to give it its more usual name in exalted circles, the geomagnetic field, is quoted as two vectors with respect to true North and a true horizontal (tangent). Where I'm sitting, these are 18.5 micro Teslas at 5.3° West




of North and 48.6 micro Teslas at 67.6°. Further North, for instance, at Eskdalemuir, the figures are 6.3 West and 69.3° (Ref. Dr D R Barraclough. British Geological Survey. Edinburgh).

These figures are from time to time upset by disturbances which have various effects on our environment. The changes are quite small, primarily being a change in direction. There is a small daily variation of around 15 minutes of arc in the horizontal, but a disturbance (often referred to as a magnetic storm) may amount to as much as one degree and last for a day or two. The corresponding variation in field strength is normally about 4 nano T for the horizontal and maybe 20nT for the vertical. A 'storm' may produce a change of a few hundred nT.

This suggests that, for those interested in the earth's field, the equipment should be able to show changes of a few minutes of arc, not necessarily in absolute values.

Types Of

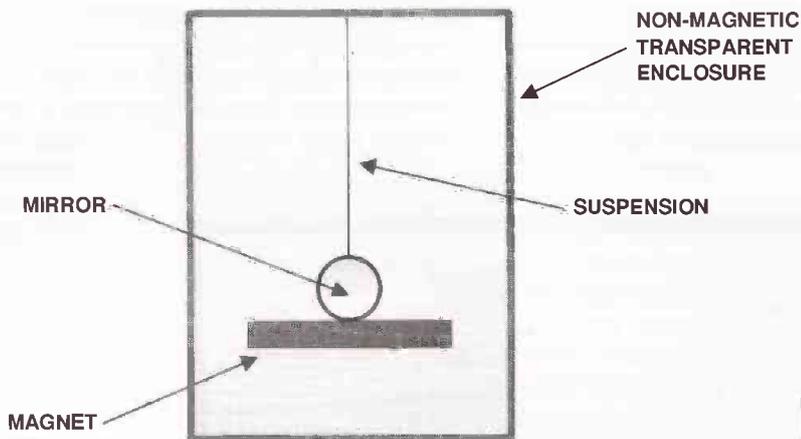

Magnetometer And Their Characteristics

There are several types of magnetometer, some more suitable for a particular kind of task than others. They can be classified by the basic principles on which they operate.

The oldest type and one of the simplest to construct is the moving magnet. It consists of a simple magnet, operating in the same way as a compass except that the magnet is suspended by a thread either of a metallic but non magnetic material such as phosphor bronze, or in this day and age nylon or similar. The most important features are that it must not have a twist in its construction, discounting threads such as cotton and it must be thin enough to allow free movement of the magnet.

This type of device is not really portable because of the flimsy nature of the suspension. If it is to be ported, then some special feature must be incorporated to support the magnet whilst in transit. Consequently, this type is popular for fixed stations where the interest is primarily in changes of direction in the geomagnetic field. As it is always aligned with the field, it cannot show change in magnitude. I shall discuss later the design of such an instrument in two forms - one that is read by a visible indication and one that is read electronically.


One of the latest types makes use of the Hall-effect. Consider a block of some conducting material (Figure 2), the three visible faces being A, B and C. A current is maintained between face A and its corresponding hidden face, with the flux to be measured applied to face B. This flux will cause electrons to diverge towards the C face or its hidden counterpart, establishing a voltage between the two faces (I seem to remember Fleming had a rule about the direction of motion).

It is now possible to obtain semi-conducting versions of the Hall-effect device. For simple indications of magnetic intensity this type of device is convenient and portable, but the linearity of the devices is more or less in direct proportion to their cost and sensitivity. For example, in the Electromail/RS catalogue one available at around #8 generates 9mV per mT. Changes in the earth's field are rather beyond them and they are not inherently suitable for determining direction. However, they are very small and simple to set up and are thus ideal as probes for investigating magnetic circuits.

The most versatile is the fluxgate magnetometer and modern electronic components have really brought this type to the fore.

A fluxgate magnetometer is portable, its sensitivity is good and with care in construction can be very accurate, reading down to nano Teslas. It is also direction sensitive, which has the advantage that it can distinguish more than one field and unwanted fields, such as the earth's, can be balanced out.

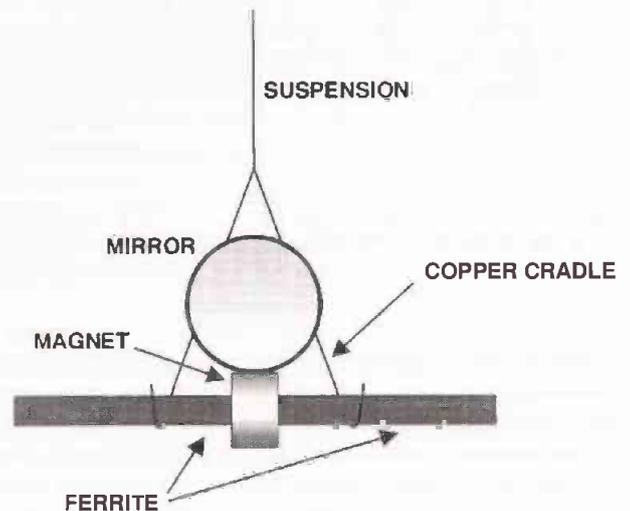Briefly, it consists usually of two ferrite rods, each of which carries a winding. The rods are



arranged side by side and the windings excited by a pure (no harmonics) AC drive. Around the pair of rods is arranged a third winding, the sense winding. Any external field causes the second harmonic of the excitation to be generated and it is this harmonic which is used to indicate field strength. The construction of this type will be discussed in a fairly simple form in detail. The earth's horizontal field (18.5μT) will give an output of around 3V DC on the divide by 10 range. The windings don't have many turns (300 is the most) and the electronics can be assembled on strip board. This will be followed by the enhancements which can be made to improve it further.


There is one other type that must be mentioned, which depends on atomic behaviour - the proton precession magnetometer. This also has the advantage that it is portable and it measures total flux from whatever direction. It is useful in that a

general survey of flux density can be carried out, without the necessity of pointing it in the right direction. The other side of the coin is that it is unable to distinguish more than one source of flux.

The principle is that a small container of liquid, usually alcohol, is subjected to a strong steady field, the polarising field, perhaps by means of a coil wrapped round the container. This field is switched off and the frequency of precession of the protons is measured by means of the same coil, or a second one. This frequency indicates the flux strength remaining after the polarisation is removed. The effect dies away in a few seconds, allowing measurements to be repeated fairly rapidly. As it has a limited, use I am not proposing to give more detail in this article.

Moving Magnet Magnetometer

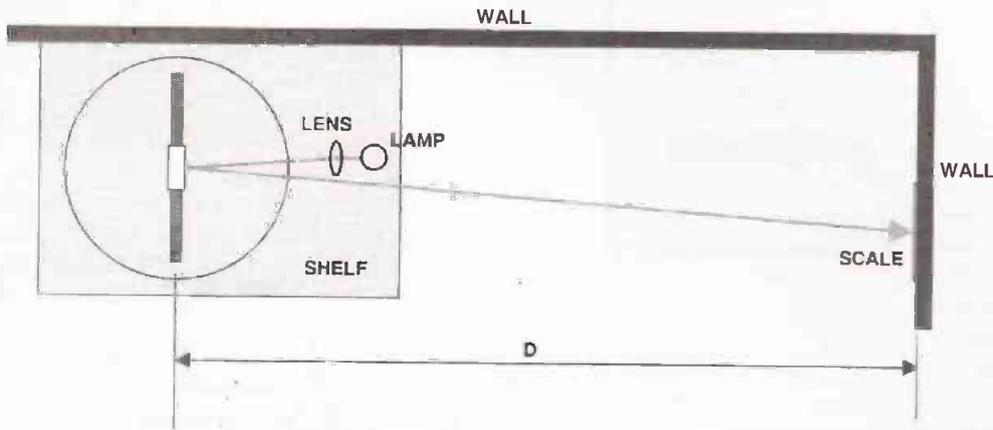The MMM is constructed fairly easily from items to be found in most bits and bobs boxes. A fair bit of patience is needed with the setting up and a bit of dexterity in making it, but otherwise it



should be fairly straightforward. Don't make a start until you have read the whole of this section, as there are one or two points which are critical

It consists of a suspended magnet to which a small mirror is attached. If you know a dentist, then the small surface silvered inspection mirror is ideal. Failing that, a small mirror can be cut from a back silvered mirror, about 3/4 of an inch square will do.

The device will be very susceptible to drafts and therefore must be enclosed within a suitable draft proof enclosure. It must also be transparent, of course. Figure 3 suggests the arrangement. Sweet jars, jam jars and unused gold-fish bowls are all typical of the type of container which is suitable. The gold-fish bowl will require a lid. Don't use any absorbent material such as wood, because it is not dimensionally stable and of course iron or steel is out. The amateur electronic engineer's favourite - aluminium - is ideal.

Since the modus operandi is to shine a light on the mirror and use the reflection as the indicator, moulding marks on glass jars can be a nuisance. However, you will be very unlucky if you cannot find a large enough clear patch as the movement is very small. It may just be necessary to experiment a little when you come to set it all up. An excellent scheme if you are handy with Perspex is to make a case up and there is no need for it to be circular.

The suspension can be either fine fishing line or very thin


copper wire. The fixtures in the fishing line are best sealed by heating. The big advantage of copper wire is that the joints can be soldered and Figure 4 suggests a possible construction.

The type of magnet is not dramatically important. The longer and more powerful it is, the better it will align itself in the magnetic field and the small magnets used to operate read relays and security switches may be too small. However, I can see no reason why several should not be set end to end until the available length is four or five inches.

I tried cheating, with quite good results. As it happened, I had some small disc magnets about a half an inch in diameter. A ferrite rod about 5in long was cut in half and the magnet arranged in the centre. Incidentally ferrite rod is extremely hard and you will not be able to saw through it without a diamond saw. Much simpler is to make a small notch at the centre with a hack-saw, then put pressure on this point until it snaps. Maybe I was lucky, but having made the shallow notch I held it against the thumbs of both hands with my fingers and just applied thumb pressure. It snapped with quite a clean break, but in any



case the two original ends were quite square so they were used as the inside ends against the magnet. A cradle or stirrup was made from thick copper wire as shown and some Araldite or similar resin will complete this part of the exercise.

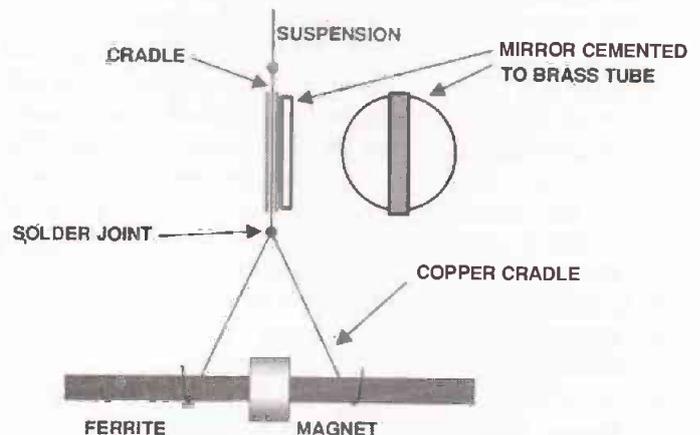The next requirement is a small bulb with preferably a straight filament, because we shall have to use the image of the filament as the indicator. A round MES



12V is probably the best. Run it from a suitable transformer and either adjust the voltage down or add a series resistor, to extend the life of the bulb and limit any filament movement. Only enough light to see the projected image clearly is needed.

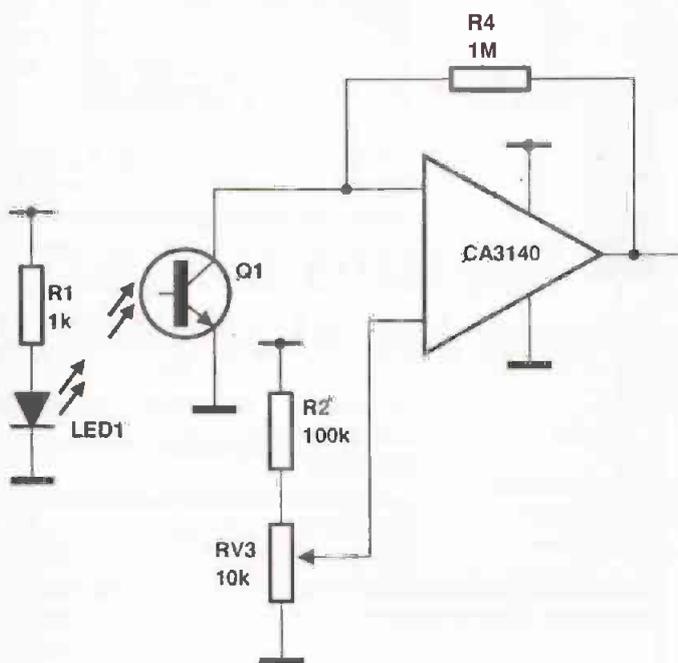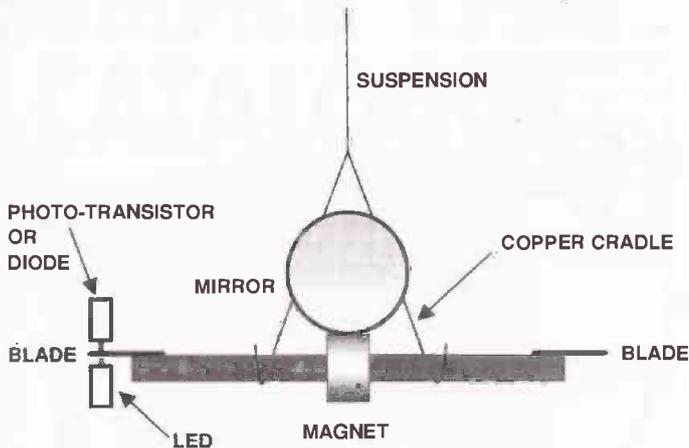A lens will be required which is capable of projecting an image of the filament onto a surface 2 or 3 metres away. This is



also a matter of experiment. I happened to have one or two lenses in my 'photographic' box and an old projector lens seemed to be best.

Remember, the lens will of necessity be separated from the mirror by the 'anti draft' container. It is best to make a mock up of this part of the device so that you are sure it will work. Clearly, the more elegant the lens, the clearer the image of the filament will be. However, the object of the exercise is really to give a patch of light that has some clearly defined point which can be used as the reference, not necessarily a perfect image of the lamp filament.

If you don't have lenses, how about trying one of the fairly

cheap plastic eye glass lenses? Alternatively, a small laser would do the trick. And set you back about £60!

Figure 5 suggests the layout in plan view. Before any construction starts, it is essential to decide on the location to be used. There are one or two restrictions. The first depends on the minimum distance D between the mirror and the scale, the very least is 2m, 4m is nearer the mark. The arithmetic behind this statement comes in a moment.

Just as importantly, there must be absolutely no movement between the support for the magnet, i.e. its enclosure, the lens assembly and the scale. If it's at all possible, much the best arrangement would be to mount the assembly on an aluminium shelf fastened to a brick wall. Then fasten the scale on the brickwork also as suggested in Figure 5.

A wooden building would be unsuitable because there would be too much movement dependant on weather conditions. However, if there is no option, the only suggestion I have is either a rigid aluminium frame to which all the parts are attached, or to mount the magnet assembly and lamp on a concrete base and arrange that the spot from the mirror shines in through a window.

Figure 5 is drawn as if it were attached to a wall which runs due East-West, in which case the magnet will be slewed by just 5° and Figure 5 will work like a charm. In practice walls are not built conveniently and accurately in this way, so as a consequence the mirror may have to be attached at an angle to the magnet. This can best be done by rehashing Figure 4 slightly, so that the stirrup is extended vertically by a piece of the same copper wire, cementing the mirror to a piece of brass tube and sliding it over the extension. Then attach the extension to the suspension. The mirror can then be turned relative to the magnet until it all works and then be fixed with a dab of cement. See Figure 6 for the alternative to Figure 4.

Now some fairly simple arithmetic.

The sort of movement we are looking for is around 5 minutes of arc or less and up to 1° . To arrange that 1 minute of arc gives one millimetre of movement on the scale:

1 minute = $1/(360 \times 60)$ th part of a circle and this must be 1mm. The circumference of a circle is $2\pi r$, but in our particular case the distance D in Figure 5 is the radius, so the circle is $2\pi D$ and this equals $1/(360 \times 60)$.

So, $D = 360 \times 60 / 2 \times \pi = 3438\text{mm}$.

However, the reflection from the mirror will turn through twice the angle of the mirror movement so in fact the above distance can be halved to 1719mm, say 1.72m.

The minimum D of Figure 5 is 1.72m and in fact it would be easier to read changes if it could be made greater than this. To cover the general case therefore, given the distance D in metres, one minute of arc will be represented by $D \times 0.582\text{mm}$. ($D \times 4000 \times \pi / 360 \times 60$). If it's more convenient the other way round then, if there are M millimetres of scale per minute of arc, then the required distance D in metres will be $M \times 1.72$.

Setting Up

There are no short cuts, it's just a painstaking job of getting the magnet assembly and lamp lens assembly together on a rigid non magnetic base as the first step.

It may need a fair bit of patience to set the mirror so that the reflection appears in the right place - after the magnet assembly has finished swinging! If the mirror is movable in respect to the magnet, use a dab of cement (one of the resin glues is good) which is not quick setting so that you have time to adjust it before the cement hardens.

Don't take the readings too seriously for a day or so as it does need time to settle.

Making The Moving Magnet Magnetometer Machine Readable

The MMM as built so far can only be read by inspection. However, as we now all have chart recorders (ETI April 94 et seq), a much better picture of the way the geomagnetic field changes can be obtained if the readings are recorded. It also helps to avoid the slightly embarrassing moments when in the middle of a social evening one has to announce "Excuse me a few moments, I just have to go and read my magnetometer".

A quite simple arrangement is suggested in Figure 7, in which the ends of the magnet have been extended with thin aluminium blades. One of these intercepts the light from an LED shining onto a photo transistor and there is no absolute need for a blade at each end of the magnet, it's just a simple way of making sure it remains balanced by adding an identical weight at each end.

It is best to use infra-red devices encapsulated in black infra-red transmissive plastic to reduce the effect of ambient light. Even so, you may find it necessary to enclose the device in a light proof cover.

One can obtain the two infra-red devices in one moulding, which makes mounting much easier. However, be careful - some of these are switches, the detector includes a trigger so the device does literally switch from one state to the other. Such a device is not suitable for this application as the detector must be a linear device.

A suitable circuit is suggested in Figure 8. This shows a photo transistor as the sensor but a photo diode is a suitable alternative. Two comments are valid here. A photo transistor frequently does not have its base connected and the base connection is often not available. Secondly, the photo diode is usually operated in the reverse biased mode.

I suggest the value of R1 as 1K for the first trial, R2 and R3 are 100K and 10K respectively and R4 is 10M. Using a CA3140 as IC1, output can swing between 0 and approximately 9V. Aim for somewhere round the middle of this range when setting up.

Setting the device up is quite tricky, as the blade of the magnet has to just intercept the beam. To do this, note the maximum and minimum voltages at the output of the op-amp. One is with the blade fully covering the photo device and the other with the blade fully withdrawn. R3 can be adjusted to help get this right. If this is not sufficient, then the value of R4 may

have to be changed. A little experimentation may be called for.

The next step is to move the device so that with the magnet free to move and when it has settled down to pointing North, the output from the op-amp is roughly in the middle between the limits noted above.

If using a cover, it may upset the readings when fitted. Try carefully moving the device clockwise or anticlockwise to see if the reading can be restored.

One point which I nearly forgot and may not be obvious. The 12V supply must be regulated. The current consumption is very small, about 20 mA, so the power supply need not be anything very extravagant.

The Fluxgate Magnetometer

Those who have worked with magnetic amplifiers or mag-amps will find the workings of the flux gate magnetometer familiar. The FGM to be described illustrates all the principles involved, but leaves the enthusiast room for experiment and enhancement.

It is also designed to be adjustable in gain and offset so that it can be a bit of a jack of all trades, but with adjustment and enhancement at least master of some.

For example, its sensitivity is such that it gives about 3V for the horizontal component of the earth's flux, with the design sensitivity reduced by 10. If required, therefore, the gain can be altered so that it gives 5V for 50mT, 10 μ T per volt. This is a convenient scale where direct readings of field strength are required, enabling both horizontal and vertical components to be measured.

Similarly, its circular sensitivity is about 3V for 7° as developed, (7mV/minute) This sensitivity to rotation means that the normal small changes in the earth's field (5 to 10 mins of arc) would produce an output change of 35 to 70mV.

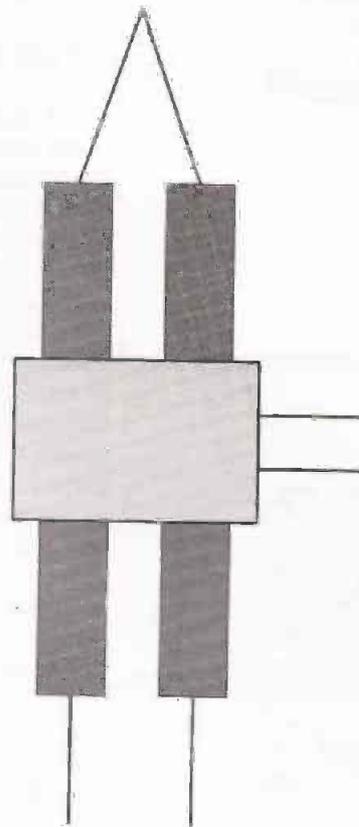


Figure 9a: Plan view of Fluxgate Magnetometer, showing sense winding arrangement

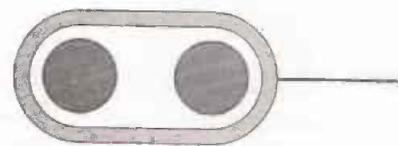


Figure 9b: End view of Fluxgate Magnetometer

Next month...

We will continue with building the fluxgate magnetometer, plus two other magnetometer designs.

SUMMER 1994 CATALOGUE



NEW EDITION!

The new enlarged Catalogue is out now!

Included in this issue:

- A further 16 extra pages
- £200 worth discount vouchers
- 100's new products
- 256 pages, 26 sections, over 4000 products from some of the worlds finest manufactures and suppliers
- Expanded entertainment section with in-car amps, speakers, crossovers and low cost disco equipment
- Further additions from Europe's leading kit manufacture - Velleman
- Available from most large newsagents or direct from Cirkit
- **Send for your copy today!**

STILL ONLY
£1.90
+ 30p p&p

Cirkit



CIRKIT DISTRIBUTION LTD

Park Lane · Broxbourne · Hertfordshire · EN10 7NQ
Telephone (0992) 448899 · Fax (0992) 471314



**UK Distributor for the
complete ILP Audio Range**



BIPOLAR AMPLIFIER MODULES

Encapsulated amplifiers with integral heatsink.

HY30P	15W Bipolar amp	£9.95
HY60	30W Bipolar amp	£12.62
HY6060	30W Stereo Bipolar amp	£26.46
HY124	60W Bipolar amp (4 ohm)	£20.69
HY128	60W Bipolar amp (8 ohm)	£20.69
HY244	120W Bipolar amp (4 ohm)	£27.38
HY248	120W Bipolar amp (8 ohm)	£27.38
HY364	180W Bipolar amp (4 ohm)	£42.86
HY368	180W Bipolar amp (8 ohm)	£42.86

MOSFET AMPLIFIER MODULES

Encapsulated amplifiers with integral heatsink.

SMOS60	30W Mosfet amp	£23.15
SMOS6060	30W Stereo Mosfet amp	£39.95
SMOS128	60W Mosfet amp	£30.95
SMOS248	120W Mosfet amp	£42.50

CLASS A AMPLIFIER MODULE

Encapsulated Class A amplifier with integral heatsink

HCA40	20W Class A amp	£36.60
-------	-----------------	--------

POWER SUPPLIES

Full range of transformers and DC boards available for the above amplifiers.

100 VOLT LINE TRANSFORMERS

Full range of speech and music types for amplifiers from 30 watt to 180 watt

PREAMPLIFIER MODULE

General purpose preamplifier for a wide range of applications.

Prices include VAT and carriage



Quantity prices available on request

Write, phone or fax for free Data Pack

Jaytee Electronic Services

Unit 171/172, John Wilson Business Park,
Whitstable, Kent CT5 3RB. U.K.

Tel: (0227) 265333 Fax: (0227) 265331

Headlight Reminder

Don't let your car battery go flat by forgetting to turn off your lights. L.S. O'Connor builds a lights-on reminder for your vehicle.


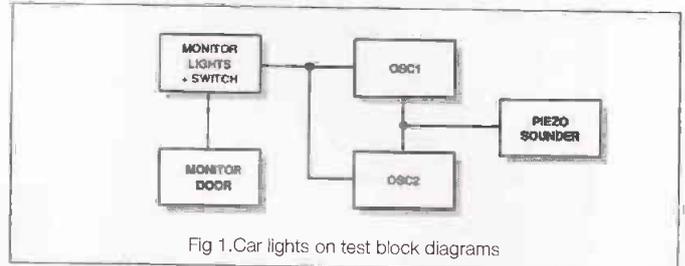


Fig 1. Car lights on test block diagrams

This car lights reminder circuit warns you with a warbling tone should you try to exit your vehicle with the car lights still on. It has a variable volume control, enabling you to set your own desired volume level and is built from three separate modules - Monitor Lights checks whether the lights are on or off, the Monitor Door checks whether the door is open or shut and the Switch, which is activated if the lights are on and the door is open, switching on the two oscillators that drive the piezo sounder (see Figure 1).

How It Works

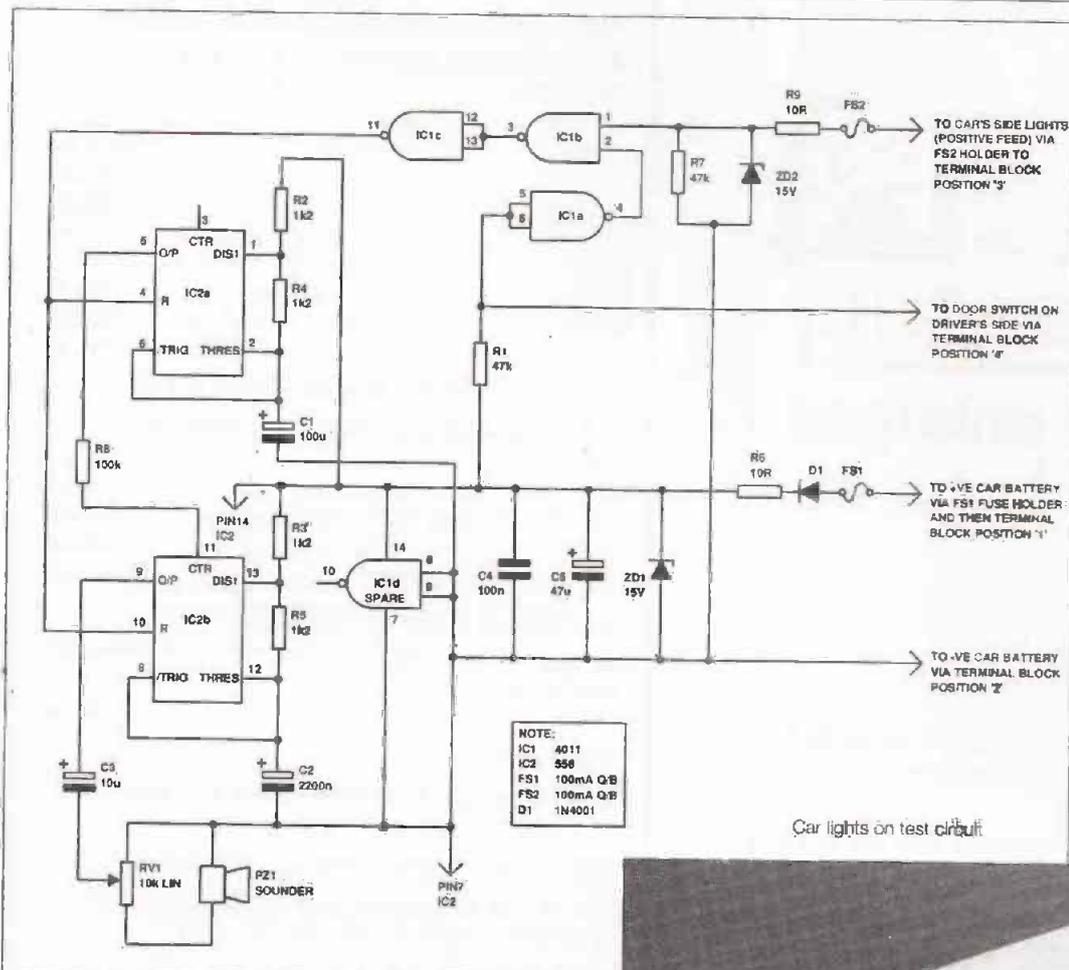The circuit is based upon a quad two input NAND




NOTE:
IC1 4011
IC2 555
FS1 100mA Q/B
FS2 100mA Q/B
D1 1N4001

Car lights on test circuit

IMPORTANT


This circuit has been designed for negative earth vehicles only and will not function with the positive earth type.

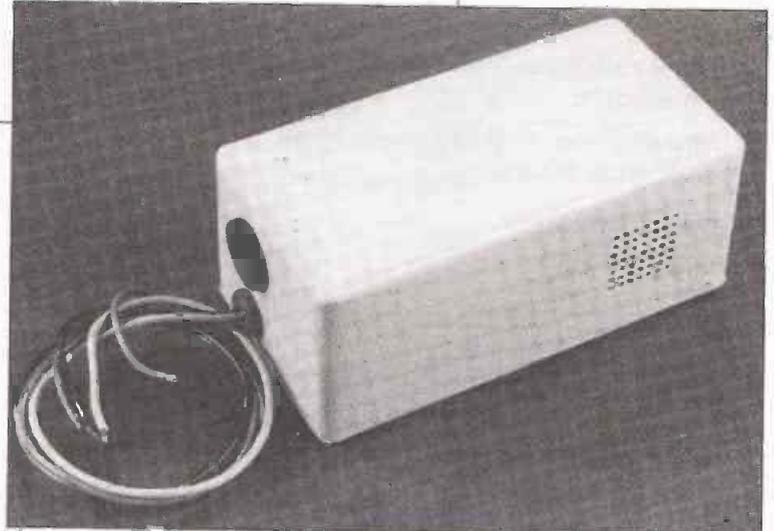To determine your car's polarity, look at your battery terminals and note which terminal is connected to the car's chassis. If it is the negative terminal then your car is a negative earth, if it is the positive then it will be positive earth. Most cars are of the negative earth type.



gate, IC1, and a dual version of the 555 timer, IC2. IC1a is connected as an inverter and checks whether the door is open or closed. With the door closed, the door switch is open circuit and R1 pulls the input high, so the output is low (see Figure 3 for truth table). However, when the door is opened, the door switch grounds the input of IC1a, changing the output to a high. This is fed to one half of the input of IC1b, the other half being connected to the car's side lights power feed. R7 is a pull down resistor and ensures that the input is low when the lights are switched off. The output of IC1b remains in a high state until both the inputs are taken high so with the lights switched on and the door open, the output would change to a low. This is fed to IC1c wired as another inverter, which is used to provide the correct logic level required by the IC2a and IC2b reset pins.

Both IC1a and IC1b are connected as astable multivibrators, producing square wave outputs. IC2a is operating at 4Hz and is determined by the formula $1.44/(R2+2R4)C1$, while IC2b is operating at 1.8KHz $1.44/(R3+2R5)C2$. Both IC2a and IC2b are held switched off by the low output from IC1c, connected to the reset pins 4 and 10, so therefore they are only allowed to oscillate when the reset pins are taken high. This only occurs when the lights are on and the door is open. The output of IC2a is fed via R8 to the control input of IC2b, which has the affect of modulating the output of

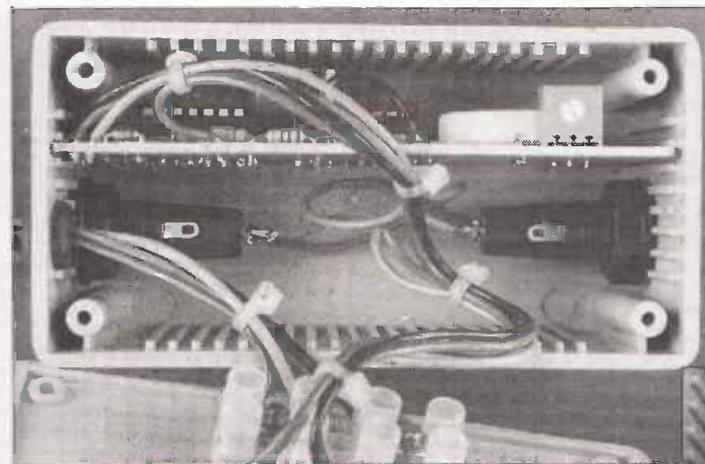

IC2b by changing the threshold set internally, giving us the warbling affect.


The output of IC2b is passed through C3 and VR1 to drive the piezo sounder directly, with VR1 setting the desired volume level.

D1 protects the circuit from reverse polarity connections and R6, R9, ZD1 and ZD2 clamp any high voltage spikes present in car electrical systems to a safe level. C4 and C5 smooth the supply.

FS1 and FS2 are there should the circuit start to draw an excess of current due to a fault.

Construction

The prototype used an ABS box from Maplin (Part no: YU52G). This has slotted walls to accept the PCB and internal dimensions of 49.5 x 99.5 x 40mm. The Veroboard was cut to fit the slots and was 39 strips x 14 holes. Using these dimensions, cut the tracks at the various points (see photograph of layout). Next, solder the appropriate links and then the components (smallest first). When complete, solder suitable lengths of cable from the various points on the circuit board to reach the fuse holders and the 4 way terminal block, where they are to be fitted.

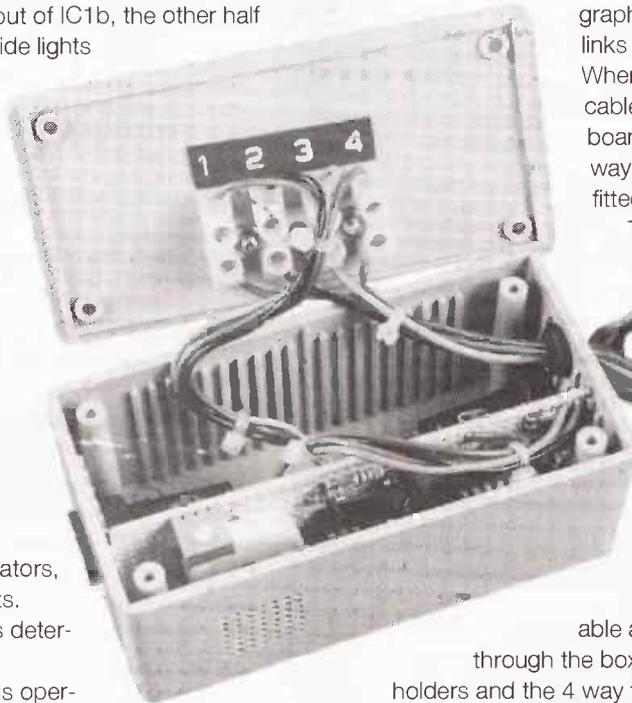


The terminal block was mounted to the lid on the inside, using two 6BA nuts and bolts and the fuse holders at either end of the box. These were done last to ensure that neither fouled the PCB. Insert the PCB as near to one side of the box as possible and mark the position of the piezo sounder, so you can drill a suitable amount of holes to allow the sound

through the box. Also mark the positions of your fuse holders and the 4 way terminal block, ensuring that they do not block the PCB. An additional hole was drilled at one end and a grommet fitted, to allow for the through cables connecting to the various points of the car.

Finally, with the fuse holders and terminal block in place, solder the positive feed from the terminal block (position 1) to the fuse holder FS1, and from FS1 to the positive cable from the circuit board. Solder the lights from the terminal block (position 3) to the fuse holder FS2 and from FS2 to the lights feed cable, from the circuit board. Connect the -ve cable from the circuit board to Position 2 and the door switch cable from the circuit board to Position 4 of the terminal block.

Testing

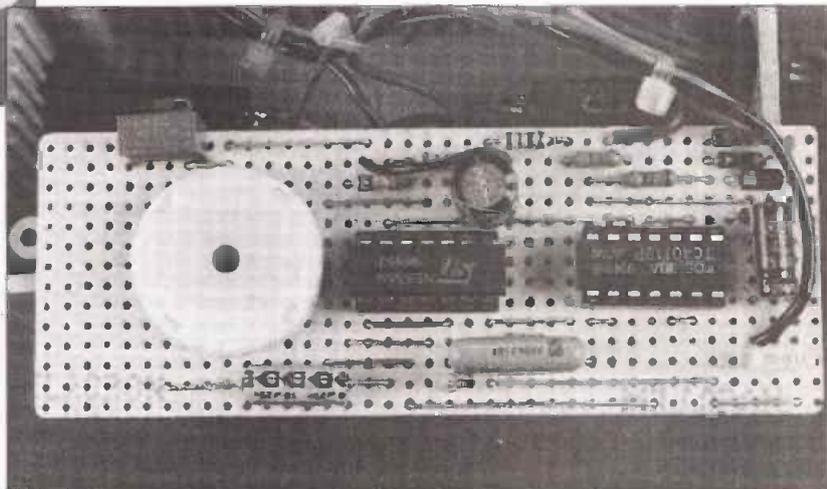With the unit fully assembled, testing can be carried out as follows. Using a PP3 battery or similar, connect the positive terminal to Position 1 of the terminal block and the negative terminal to Position 2. Link Position 3 to Position 1, which simulates the lights being switched on. Now momentarily link Position 4 to Position 2 to simulate the door being opened



and the sounder should now be operating.

Remove the link from Position 3 to 1 to simulate the lights being switched off. Momentarily link Position 4 to Position 2 and the sounder should remain silent.

If any of the above tests fail, then check all your connections, the cutting of the tracks and that all of the components have been inserted the correct way round. Finally, check the fuses.

Installation

There should be no problem with the installation, provided that you follow these procedures. You will require a suitable multimeter in order to make the correct connections.

Normally, I would recommend disconnection of the car battery prior to fitting, but due to the ever increasing number of car radios that are security coded and cars fitted with micro-processor controlled management systems which require a constant source of power for their operation, it would be advisable to do the installation with the battery still connected.

Ensure that both FS1 and FS2 are removed and that the car ignition switched off. Locate a constant source of power and using auto type cable, connect to Position 1 of the terminal block, housed inside the control box. If you use the Scotch-Lock type connectors, this will allow you to crimp your cables in parallel with the existing cable and so avoid the need to break the existing cable. Next, find a suitable earth and connect to position 2 of the terminal block.

Now connect position 3 of the terminal block to the live feed of the car's side lights. Switch on your side lights and they should still come on, even with the ignition switched off. I found the best place to make a connection was down by the side light itself, unless of course you have easy access to behind the side lights switch, in which case you can make your connection there.

Wherever you decide, check with your multimeter that it is the live feed for the side lights, by switching the lights off and observing that the power is indeed removed.

Connect Position 4 of the terminal block to the door switch on the driver's side, which operates the car's interior light. If there is a single wire on the door switch, this means that the switch is earthed by the cars' chassis and operation of the switch connects this wire to earth and completes the circuit. All that is required is to make your connection to that single wire. If, on the other hand, you have two wires attached to your door switch, then this means that the switch is of the plastic type and that there is a separate earth to the switch. Operation of the switch just connects the two wires together and you need to make your connection to the non-earthed wire, which can be found by switching your multimeter to the ohms position and attaching one probe to the car's chassis and the other to either of the two wires. Make your connection to the wire that breaks the continuity when the door switch is operated.

Making sure that the side lights are now switched off, insert both FS1 and FS2 into the fuse holders, switch the lights back on and open the door. You should hear the sounder emitting the reminder tone. You can now adjust VR1 to the desired volume level. When you either switch the lights off or close the door, the sounder should cease.

Finally, fit the lid and tuck the control box up under the dashboard. If any of the above fails, then re-check all your connections and fuses.

R1, 7 47K

PARTS LIST

R2, 3, 4, 5 1K2
R6, 9 10
R8 100K
VR1 10K

Capacitors

C1 100µF 25V DC Radial
C2 0.22µF 25V DC Polyester
C3 10µF 25V DC Axial
C4 100N Mylar
C5 47µF 25 V DC Radial

Semiconductors



IC1 4011 CMOS QUAD 2-Input NAND
IC2 556 CMOS DUAL 555 Timer
D1 IN001
ZD2 15V Zener
PZ1 Piezo Sounder

Miscellaneous

ABS Box (Internal) 49.5mm x 99.5mm x 40mm
2 x Fuse Holders 20mm Flush
2 x Fuses 100 NA Q/Blow 20mm
1 x Rubber Grommet
Stripboard 0.1in Matrix, 39 Strips x 14 Holes
4 Way Screw Terminal Block
2 x DIL Sockets, 14 Way
2 x 6BA Nuts and


Bolts (counter-sunk)
Required length of Auto Cable (16 0.2mm)

Approximate Cost: £8.00

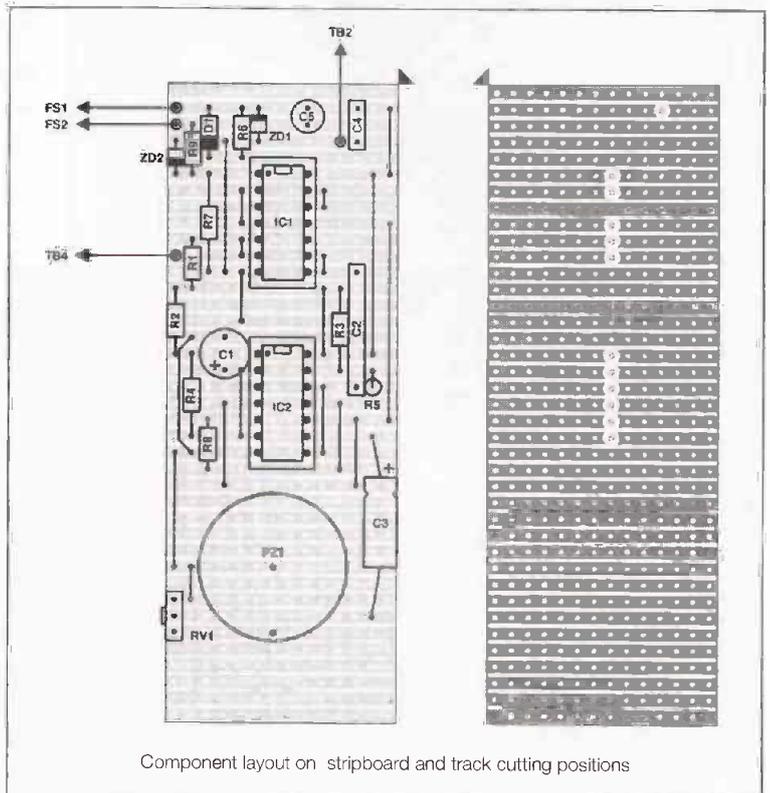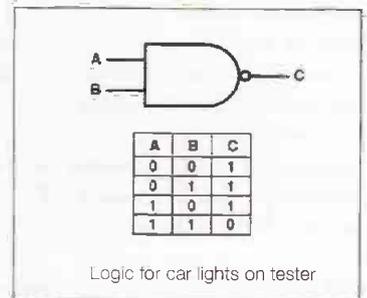

SURVEILLANCE SURVEILLANCE

A SMALL SAMPLE OF OUR RANGE	KIT	MODULE	PROF. FINISHED
ROOM TRANSMITTER RT1 An extremely sensitive miniature transmitter with long battery life. Dimensions: 20 x 20mm	9.95	13.75	19.00
MAINS TRANSMITTER MT4 Can be connected inside any equipment that is mains powered. Dimensions 35 x 20mm	19.75	31.50	45.00
TELEPHONE TRANSMITTER TTS Small enough to conceal within a telephone. Will transmit both sides of a conversation (series connection). Dimensions: 10 x 20mm	12.75	17.50	25.00
TELEPHONE SOCKET TRANSMITTER TSTS Replaces your telephone socket with this one within which a transmitter has been concealed.	14.74	—	29.00
ROOM AND TELEPHONE TRANSMITTER RTT Operates as a room transmitter, then switches to telephone transmitter mode during telephone calls. Dimensions: 30 x 25mm	31.50	45.50	65.00
AUTOMATIC TELEPHONE RECORDER SWITCH TRS2 Record telephone conversations with this interface unit and your own tape recorder. Dimensions: 36 x 50mm	16.60	25.90	39.00
AUTOMATIC TELEPHONE RECORDER ATR1 Adapt the tape recorder included to record telephone calls automatically.	34.95	—	59.00
TELEPHONE TAP ALERT TTA1 Visual warning of any invasions of privacy on your telephone line. Dimensions: 38 x 52mm	21.95	31.50	48.00
RF DETECTOR RFD1 Highly sensitive hand-held detector. Range between 10MHz and 600MHz. Silent operation. Dimensions: 70 x 50mm	42.75	69.00	95.00
CAMERA DETECTOR CD8 Detects hidden video cameras (even miniature CCD models). Dimensions: 63 x 38mm	69.00	89.00	125.00
RECORDING BRIEFCASE RBC1 Completely discreet recordings at a value for money price.	—	—	145.00
SHOTGUN MICROPHONE AMPLIFIER SMA Ideal for surveillance. The amplifier will pick up sounds from a long distance.	24.95	36.00	45.00
SIGNALLING TRANSMITTER SIGT Sends a continual audio pulse. Can be integrated into alarm, tracking or warning systems. Dimensions: 20 x 50mm	21.95	34.89	45.00
TELEPHONE AMPLIFIER TA5 Connected directly to the telephone, this unit will amplify both sides of a telephone call. Dimensions: 26 x 52mm	10.95	16.95	19.95
PROFESSIONAL SOUND TO LIGHT UNIT 9K72 Custom built for disco or home use. Audio signal divided into bass, mid and treble bands, with internal microphone and spotlight option. Dimensions 210 x 45mm	21.95	32.49	44.95
MICRO METAL DETECTOR MMD Detects the presence of ferrous and various non-ferrous metals. Useful for all those DIY types. Dimensions: 40 x 25mm	9.95	16.95	—

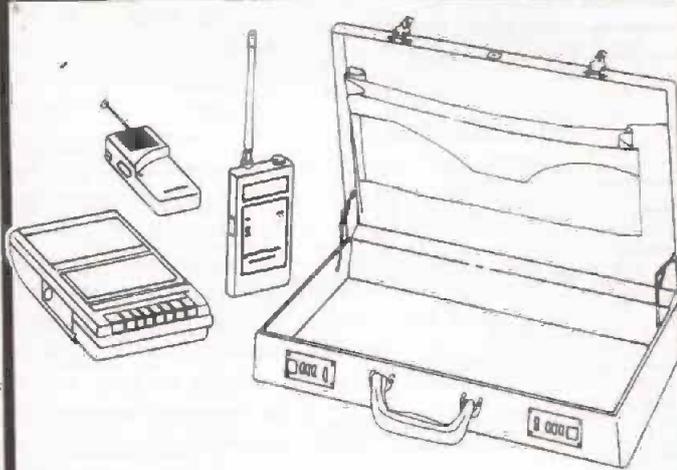

Please add £2.00 P & P to all orders and 17.5% VAT on all U.K. orders

For full catalogue please send two 1st class stamps or 2 IRC'S

172^{1/2} Caledonian Road
Dept EJ



London N1 0SG
BRIDGE AUDIO
071-837 4423



DATONG
ELECTRONICS LIMITED


Clayton Wood Close
West Park
Leeds LS16 6QE
Tel: 0532 744822
Fax: 0532 742872

For products you can rely upon to give amazing results

For information on **Active Antennas, RF Amplifiers, Converters, Audio Filters, the Morse Tutor and Speech Processors** send or telephone for a free catalogue and selective data sheets as required.

All our products are designed and made in Britain.

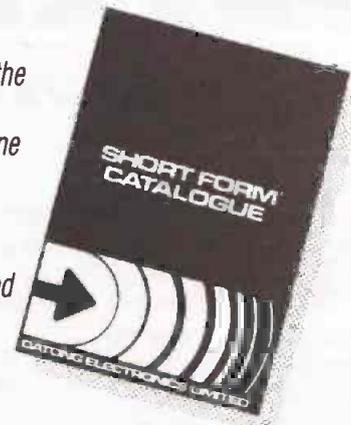Orders can be despatched within 48 hours subject to availability.



VISA AND ACCESS WELCOME



WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 7000 SERIES OSCILLOSCOPES AVAILABLE FROM £200 PLUG-INS SOLD SEPARATELY

TEKTRONIX 2245A 4 Channel 100MHz Delay Sweep Cursors	£980
TEKTRONIX 2235 Dual trace 100 MHz Delay Sweep	£800
PHILIPS 3065 2+1 Channels 100MHz Dual TB Delay Sweep	£700
TEKTRONIX 485 Dual Trace 350MHz Delay Sweep	£750
TEKTRONIX 475 Dual Trace 200 MHz Delay Sweep	£550
TEKTRONIX 465 Dual Trace 100 MHz Delay Sweep	£450
TEKTRONIX 2215 Dual Trace 60 MHz Delay Sweep	£450
TEKTRONIX 455 Dual Trace 50 MHz Delay Sweep	£400
TEKTRONIX SC504 Dual Trace 60MHz in TRMS/DB	£500
WITACH V852P Dual Trace 60MHz Delay Sweep	£400
HAMEG 656 Dual Trace 60MHz Delay	£400
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep	£400
GOULD OSI100 Dual Trace 30MHz	£160
WATSUB SS5702 Dual Trace 20MHz	£225
GOULD OS300 Dual Trace 20MHz	£200
GOULD OS250B Dual Trace 15MHz	£125
TELEQUIPMENT D32 Dual Trace 10MHz Mains/Battery	£200
TEKTRONIX 2430 Dual Trace 150MHz Digital Storage	£2000
TEKTRONIX 466 Dual Trace 100MHz Delay Sweep Analogue Storage	£450
H.P. 1741A Dual Trace 100MHz Delay Sweep Analogue Storage	£450

THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE

HEWLETT PACKARD 1740A OSCILLOSCOPES DUAL TRACE DELAY SWEEP 100MHz

For only £350

MARCONI 2818 Synthesised AM/FM Sig Gen 80KHz-520MHz	£900
SYSTEM DMMER 1762 Syn AM/FM Sig Gen 100Hz/1GHz	£900
RACAL D51 Synthesised Sig Gen 1.5 - 50MHz	£900
EPIDIANA 3410 Microwave Frequency Counter 50Hz - 18GHz	£900
RACAL/DANA 1991 Nanosecond Universal Counter	£900
RACAL 9302 RF Millivoltmeter True RMS 10KHz - 1.5GHz	£450
RACAL 9301A RF Millivoltmeter True RMS 10KHz - 1.5GHz	£450
RACAL 9009 Automatic Mod. Meter 10MHz-1.5GHz Wide Deviation	£250
LYONS PG79M Pulse Gen. PRF 1Hz - 20MHz	£150
KESTLEY 224 Programmable Current Source	£1000
PHILIPS PM6309 DISTORTION Meter 0.01%	£300
H.P. 5341A Frequency Counter 1.3GHz (GP/B & High Slab)	£900
RAY MILANO Line Voltage Analyser	£500
H.P. 7470A Plotter 2 pen HP/B	£200

BRUEL & KJOER Vibration Exciter System Consisting of Exciter Control 1047: Power Amp 2700 & Exciter Body 4802 (up to 1700M - 400lb) OTHER B&K EQUIPMENT AVAILABLE

SPECTRUM ANALYSERS

H.P. 1550A 1MHz-500MHz	£1900
ANALYTICAL 15502B with Tracking Generator 10KHz - 1700MHz	£1900
POLARAD 54 (-) 10MHz - 180MHz	£1500
H.P. 411 with B&K & 8552B 10MHz - 18GHz	£1700
H.P. 1411 with 8554B & 8552B 500KHz - 1250MHz	£1200
H.P. 411 with 8553B & 8552A 1KHz - 110MHz	£900
H.P. 411 with 8553B & 8552A 1KHz - 110MHz	£700
MARCONI TP2370 30Hz - 110MHz	£1900
H.P. 8444 & 8443 Tracking Generators Available	From £300

H.P. 9640B Sig Gen 35Hz - 100MHz	£1900
H.P. 8620C Sweep Osc with 8625A 6.9-82 KHz	£750
MARCONI Digital Freq. Meter 10KHz	£900
BRADLEY 195 Oscilloscope Calibrator	£900
WILTRON 308 Solaris Network Analyser with Detectors	£1900
FERRIDGRAPH Audio Test Set with ATU	£350
LINDOM LA1 1620 Audio Analyser	£500
DATRON 1061A - 8.5 digit True RMS AC Datalog	£1250
DATRON 1188 Multimeter AC/DC Ohms IEC	£599
HEWLETT PACKARD 3404 Bench Multimeter 5 Digit AC/DC/Ohms	£200
PHILIPS PM254 4 1/2 Digit Function DMM 3.5 - 6.5 digit with GP/B/E/E	only £650
MARCONI Digital Frequency Meter 2430A 10Hz-60MHz	£125
MARCONI Digital Frequency Meter 231A 10Hz-200MHz	£150
MARCONI Universal Counter Former 2431 DC - 100MHz	£175
MARCONI Universal Counter Tester 2438 DC	£225
FEEDBACK FG600 0.01Hz - 100KHz Sine/Sq/Tri	£80
TRANDAR TR311 Func. Gen. 0.00Hz-200MHz 20V-50V TTL	£80

SOLARTRON/SCHLUMBER 1250 FREQUENCY RESPONSE ANALYSER

H.P. 8620B Sweep Osc with 9674 Plug-in 26.5-400Hz	£300
RACAL/DANA RF Power Meter 9104	£400
WAYNE KERR 9905 Automatic Precision Bridge 0.05%	£900
WAYNE KERR B24 Digital LCR Meter	£125
CONCOR 1000 Optical Cable Fault Locator	£1500
BICOCOTEST T43 IM Cable Test Set	£1000
FARNEL PSU LV570M22 70V 5A/10A	£200
FARNEL 9010 0.1-30V 20mA	£250
FARNEL 82016 0.30V 10AMPs	£200
BRANDENBURG 4721 PSU 0-30V	£200
MARCONI TP2700 Universal LCR Bridge Battery from FARNEL	£55
FARNEL LA320 RF Power Amp. 1.5-220MHz 200mW	£175
RACAL 9100 Absorption Wavemeter 1MHz-1GHz 2W	£100
CONCOR 1000 AC Voltmeter Dual 10Hz - 500kHz	£100
AVD Value Tester CT150	£75
FARNELL LINE 6-30V 0-5A	£125
FARNELL LINE 0-50V 0-500mA	£50

FARNELL ISOLATING TRANSFORMERS GUS00 210V 50VA Un-Used £80 ISOLATING TRANSFORMERS 500VA Un-Cased £30

NEW EQUIPMENT

HAMEG OSCILLOSCOPE HM 1005 Triple Trace 100MHz Delay Traces	£847
HAMEG OSCILLOSCOPE HM 404 Dual Trace 60MHz	£553
Duple Sweep	£553
HAMEG OSCILLOSCOPE HM200 7" Dual Trace 20MHz	£362
HAMEG OSCILLOSCOPE HM200 3" Dual Trace 20MHz Digital Storage	£553
All other models available - all oscilloscopes supplied with 2 probes.	
BLACK STAR EQUIPMENT (p&p all units £5)	
APOLLO 10 - 100MHz Counter Timer Ratio/Period/Time interval etc	£222
APOLLO 10 - 100MHz (As above with more functions)	£325
METEOR 1000 FREQUENCY COUNTER 100MHz	£119
METEOR 600 FREQUENCY COUNTER 600MHz	£145
METEOR 1000 FREQUENCY COUNTER 1GHz	£189
JUPITOR 500 FUNCTION GENERATOR 0.1Hz-500KHz Sine/Sq/Tri	£119
ORION COLOUR BAR GENERATOR Pal/TV/Video	£229
All other Black Star Equipment available	
OSCILLOSCOPE PROBES Switchable x1 - x10 (P&P £3)	£12

Used Equipment Guaranteed - Manuals supplied if possible This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering CARRIAGE all units £16 VAT to be added to Total of Goods and Carriage

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Telephone: (0734) 268041 Fax: (0734) 351696 Callers Welcome 9am-5.30pm Mon-Fri (until 8pm Thurs)

MIDI

EXPLAINED

In Part 3 of Robert Penfold's series on MIDI, he takes an in depth look at channel messages

In last month's article, the subject of MIDI modes was covered, and a start was made on the related subject of channel messages. In this article we will consider all the remaining channel messages in some detail. These are the most important messages, since they are the ones that are used to play notes, provide touch sensitivity and pitch bends, change to a different set of sound generator settings, etc. Every MIDI user needs to know what channel messages are available, and have at least a fundamental understanding of the way in which they function. Anyone who is involved in the writing of MIDI software and/or the design of MIDI hardware needs to understand every bit of every MIDI channel message. Full details of MIDI channel message coding will therefore be provided, for those who need it. If you are not into do-it-yourself MIDI software or hardware, this sort of detailed information is of purely academic importance. As note on and note off messages were fully covered in last month's, article they will not be considered again here.

All Change

Program change messages are one of the most simple forms of MIDI channel message. The name of this message is a

slightly perplexing one, but in this context a 'program' is normally a set of sound generator parameters. This message is therefore used with a synthesiser to change from one sound to another. For instance, this message could be used to change an instrument from a trumpet sound to a guitar sound. Although this might not seem to be particularly useful, most instruments will respond to this type of message very

rapidly, making it possible to use program changes mid-sequence. This is a form of channel message and it is therefore possible to individually change the sound of each voice of an instrument operating in mode 4 or a multi-mode. This may still

seem to be a clever but not particularly useful feature, but it can greatly enhance the capabilities of a sequencer system, particularly a budget system. Suppose you have an eight channel instrument operating in mode 4. On the face of it, this system can only operate using eight different instrument sounds (one per MIDI channel). However, by using program change messages it is possible to use several times this number of sounds. A channel could play a piano sound first, then a cello sound, then a bass guitar

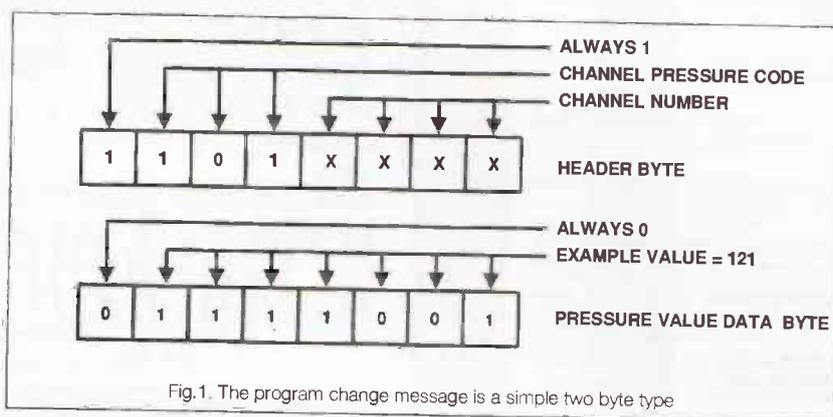


Fig.1. The program change message is a simple two byte type

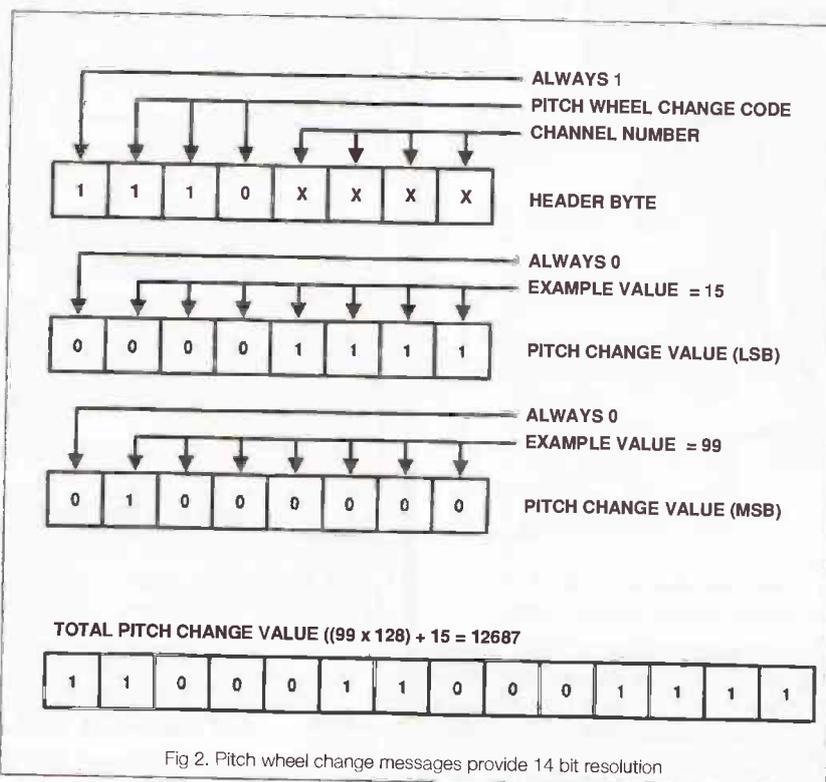


Fig 2. Pitch wheel change messages provide 14 bit resolution

and so on. By having several different sounds on each channel, with each one being played in turn, it is quite possible to have eight channels but a total of a hundred or more different sounds.

There is an obvious limitation in that our example system can provide no more than eight different sounds at any one time. For most users, this is not a major drawback though, since they would not wish to use large numbers of sounds simultaneously. Of course, even with a system that has a separate voice assigned to each of the sixteen MIDI channels, program change messages are still a useful means of squeezing a little bit more power out of the system.

Although only envisaged originally as a means of switching an instrument from one sound to another, program change messages can be used to change any MIDI device from one set of control settings to another. These messages could therefore be used to control a lighting unit, MIDI patchbay, audio mixer, digital effects unit, or any MIDI equipped device. Some non-instrument MIDI units do make use of program change messages, but it is only fair to point out that this method of control is not always used. There seems to be an increasing use of system exclusive messages to control patchbays, mixers, etc. Where an instrument or other MIDI unit can be controlled via program change messages, this is often a very easy and convenient means of control. Generating the right system exclusive messages can be difficult, particularly if it is a slightly obscure piece of equipment that you are trying to control.

Practically any MIDI controller can produce program change messages. Most keyboard instruments can be set up so that they will transmit the appropriate program change message each time they are set to a new program number. Consequently, there should be no difficulty in getting the slave instruments to follow changes implemented on the master instrument.

Program change messages have great potential in sequencing work, but their usefulness in 'live' performances should not be overlooked either. For any user of program change messages, there are a couple of important points which must be kept in mind. One of these is simply that this is a form of channel message. If you have several instruments or voices of instruments operating on different MIDI channels and you require them all to switch to a new program number, a different program change message is needed for each channel. This problem does not arise in a simple system that has the slave instruments in an 'Omni on' mode, or all operating on the same channel.

Sequencing using program change messages is usually quite straightforward. It is not normally necessary to become involved in getting a certain sound assigned to a particular program number. There should be no difficulty in using the default settings of the instrument and using the appropriate program numbers in the program change messages. The same is not true for those who use these messages during 'live'

performances. The slave units have to be carefully set up so that they always provide the correct sounds, as they follow the program change messages from the master instrument. It should always be possible to assign any set of sound generator parameters to any program number and many instruments have facilities that make it easy to copy a group of settings from one program number to another. Getting everything set up correctly may not be very time consuming, but it is advisable to have a 'dummy run' to ensure that everything will be all right on the night.

General MIDI

The original MIDI specification did not make any recommendations about the type of sound assigned to each program number. There probably seemed to be no point in doing so at the time the MIDI specification was devised, but more recently, music has become available in the form of standard MIDI sequencer files, which can be played on a MIDI sequencing system.

The problem with this approach to recorded music is that it

gives a different result on each system, due to different sounds being assigned to each program number. Program 23 might be a grand piano sound on the system used to produce the sequencer file, but it could be a banjo, saxophone, jet plane, or anything on the systems used to reproduce the sequence. It

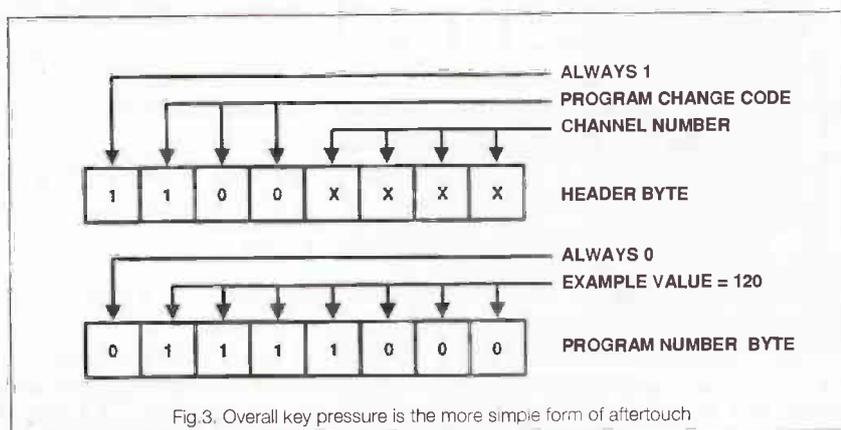


Fig.3. Overall key pressure is the more simple form of aftertouch

was therefore deemed necessary to add a set of standard sound assignments to MIDI and this is known as General MIDI. This is not a subject we will pursue further at the present time, but if you wish to produce Standard MIDI files that others can play back properly on their systems, you must adhere to the standard sound assignments. If not, you are free to assign whatever sound you like to any program number.

A program change message is a two byte type which uses the method of coding shown in Figure 1. The header byte has the program change code (1100) in the most significant nibble and the channel number in the least significant nibble. This is followed by the program number, which in decimal numbering is in the usual MIDI data range of 0 to 127. Note that equipment manufacturers do not necessarily number programs from 0 to 127. Some use numbers from 1 to 128, others have sounds arranged in banks, giving program numbers such as A-1 and D-7. The equipment manuals should clarify the relationship between the manufacturer's method of numbering and the true program values.

This is not just of academic importance. When using equipment from several different manufacturers it is quite easy to end up selecting the wrong sounds due to differences in the numbering methods. Most modern instruments have the full complement of 128 different sounds, but many older instruments only have 63 or 99. Again, it is a matter of checking the equipment manuals to determine exactly what each instrument can achieve. With some modern instruments, there is the luxury of several banks of sound data, with each one containing 128 different sounds.

Pitching In

In theory, a pitch wheel change message can be generated by any MIDI control unit, but in practice it is unlikely to be produced by any means other than operating the pitch wheel of an instrument. This message is a three byte type which uses the method of coding shown in Figure 2. The header byte has the pitch wheel change code (1110) in the four most significant bits and the channel number in the other four bits. The seven bits of data in each of the next two bytes are combined to produce a 14 bit value.

The first data byte provides the seven least significant bits - the second data byte furnishes the seven most significant bits. In decimal terms, the total pitch change value is obtained by multiplying the most significant byte by 128 and then adding the least significant byte. 14 bit resolution gives a pitch wheel value in the range 0 to 16383. The zero pitch change value is 8192 (01000000000000 in binary). Sending higher values gives an increase in pitch and lower values give a decrease in pitch.

The human ear is very sensitive to changes in pitch and can readily detect stepping rather than smooth changes. Even so, 14 bit resolution almost certainly provides a substantial amount of overkill. In practice, it is unlikely that varying a pitch wheel would result in a series of MIDI messages having the data value incremented or decremented one at a time. Doing this would almost certainly result in a severe case of MIDI choke. Pitch wheel changes are a potential cause of MIDI choke anyway, and this type of message is probably best used in moderation.

Under Pressure

As explained in the previous article, MIDI accommodates touch sensitive keyboards via the velocity values in the note on and note off messages. These values are a measure of how hard a key is pressed initially and how quickly it is released.

MIDI has provision for additional touch sensitivity in the form of 'after touch' messages. The data value in an after touch message reflects the amount of pressure applied to the key. After touch messages are only transmitted for notes that are sustained for a reasonably long time and they are therefore only sent after a key has been held down for a suitable length of time. This would typically be after a key had been pressed for about half a second to one second. Any significant changes in the pressure applied to the key thereafter will result in further after touch messages.

I suppose that a keyboard could implement after touch without having normal (velocity) touch sensitivity, but in practice, any keyboard that has after touch will also have velocity sensitivity. The latter controls the initial volume of a note and might also have some effect on the filtering or other sound generator settings. If a note is sustained for long enough, after touch then takes over and varies the volume of the note in sympathy with changes in the pressure applied to the key. Compared to just having velocity sensing, this system clearly gives greatly

improved control over the dynamics of an instrument. It is a feature that is certainly more than a little desirable.

Velocity sensitivity was not common in the early days of MIDI, and any form of after touch was virtually unknown. Things have changed over the years and it is probable that all current MIDI keyboard instruments implement at least basic velocity sensitivity. Most now have some form of after touch as well. Of course, after touch is not restricted to keyboards and it can be implemented on practically any form of MIDI controller. MIDI guitars represent the only common exception. With a guitar, it is

only possible to control the dynamics of the notes by plucking the strings more or less hard. This can be handled by the velocity values in note on messages and after touch does not really apply to any sound that is percussive in nature and of relatively short duration. It only applies to sounds that can be sustained for a long period (wind, organ, strings, etc.).

MIDI provides two versions of after touch, and the more basic form is channel after touch. This type is also known as 'overall' after touch. The data value in this type of message is a sort of average figure for all the keys that are being played on that particular MIDI channel. Although this gives only a rather unrefined method of control, it is still a great improvement on having no after touch facility at all.

This after touch message is a simple two byte type. Figure 3 shows the bit-by-bit make-up of a channel key pressure message. The header byte carries the channel key pressure code (1101) and the channel number. The second byte is the channel pressure data byte. A value of 0 is used for no pressure, through to 127 for maximum pressure.

The other form of after touch message is the polyphonic key pressure type. This provides individual after touch for each note that is played, which clearly provides very precise control of the dynamics of a piece. In theory at any rate, in terms of the amount of expression that can be put into your playing, it makes electronic instruments the equal of any acoustic instruments. Although polyphonic after touch was a rarity until quite recently, it is now becoming much more common. It is even to be found on some low cost MIDI keyboard instruments. Polyphonic after touch is a three byte message which uses the arrangement shown in Figure 4. The header byte contains the polyphonic key pressure code (1010) and the channel number. The second byte contains the note value. The system of note values used here is identical to the one used for note on and note off messages. The third byte carries the key pressure value.

In Control

Last and by no means least, we reach the MIDI control change message. Originally this type of message was used to control any aspect of an instrument which was not covered specifically by one of the other MIDI message types. This included control over the sound generator circuits. An update to the MIDI specifi-

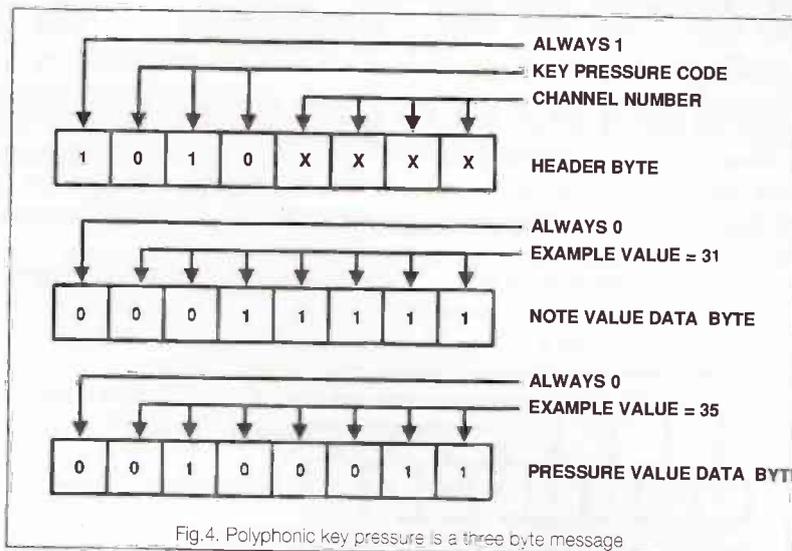


Fig.4. Polyphonic key pressure is a three byte message

cation banned the general use of control change messages to control the sound generator circuits, but control of the sound generator circuits via these messages is still permitted, provided it is done strictly in the prescribed manner. This is something we will consider in detail later.

The MIDI controls are now primarily used as a means of controlling such things as master volume and switching built-in effects units on and off, rather than as a means of making fine adjustments to the sound generator circuits. When using a MIDI instrument that is not as young as it used to be, bear in mind that it might not conform to the current MIDI recommendations and could use MIDI controls for practically any purpose.

There are two broad categories of MIDI control change message. These are the switching and continuous controller varieties. The switch type is only used to switch something on or off, such as some form of effects unit. The continuous type provides variable control and is used for something like a volume or balance control.

A switch type control is operated using a three byte message. The first byte is the header type, which contains the control change code (1011) and the channel number. The next byte is the number

of the control which must be changed, which gives some 128 different controls numbered from 0 to 127. The switch type controls are those having numbers in the range 64 to 127, but some of these now have special functions and operate in a non-standard fashion. This includes a few which operate as continuous controls. We will not consider these special cases at the present time. The third byte controls the on/off setting. Originally only two values were recognised here, which were 0 for 'off' and 127 for 'on'. The Detailed MIDI Specification altered this and recent equipment should accept values from 0 to 63 as 'off' and 64 to 127 as 'on'. MIDI controls having numbers from 0 to 63 are the continuous types, but these are used in pairs. If only seven bit resolution is adequate, only controls from 0 to 31 are used. The message then takes the same basic form as a

switching type, but the value in the third byte is the new setting for the control. This normally works on the basis of 0 for minimum and 127 for maximum.

The two exceptions to this are controls 8 and 10, which are respectively the balance and pan controls. These have 64 as the central setting, 0 as full left volume and 127 as full right volume. If more than 7 bit resolution is needed, controls 0 to 31 are paired with controls 32 to 63, so that up to 14 bit resolution can be accommodated. Control numbers in the range 0 to 31 carry the most significant bytes, while those from 32 to 63 carry

the least significant bytes. Control 0 is paired with control 32, control 1 is paired with control 33, and so on through to control 31 which is paired with control 63. This works in a manner that is similar to the way in which the pitch wheel message provides 14 bit resolution. However, the pitch wheel change message carries the two 7 bit bytes in one message, whereas they are in separate messages for a control change.

Note, however, that it is perfectly in order to change only the higher control number if only minor adjustment of a control is required. Control of the most significant and least significant bytes is totally independent. Figure 5 shows an example six byte sequence which

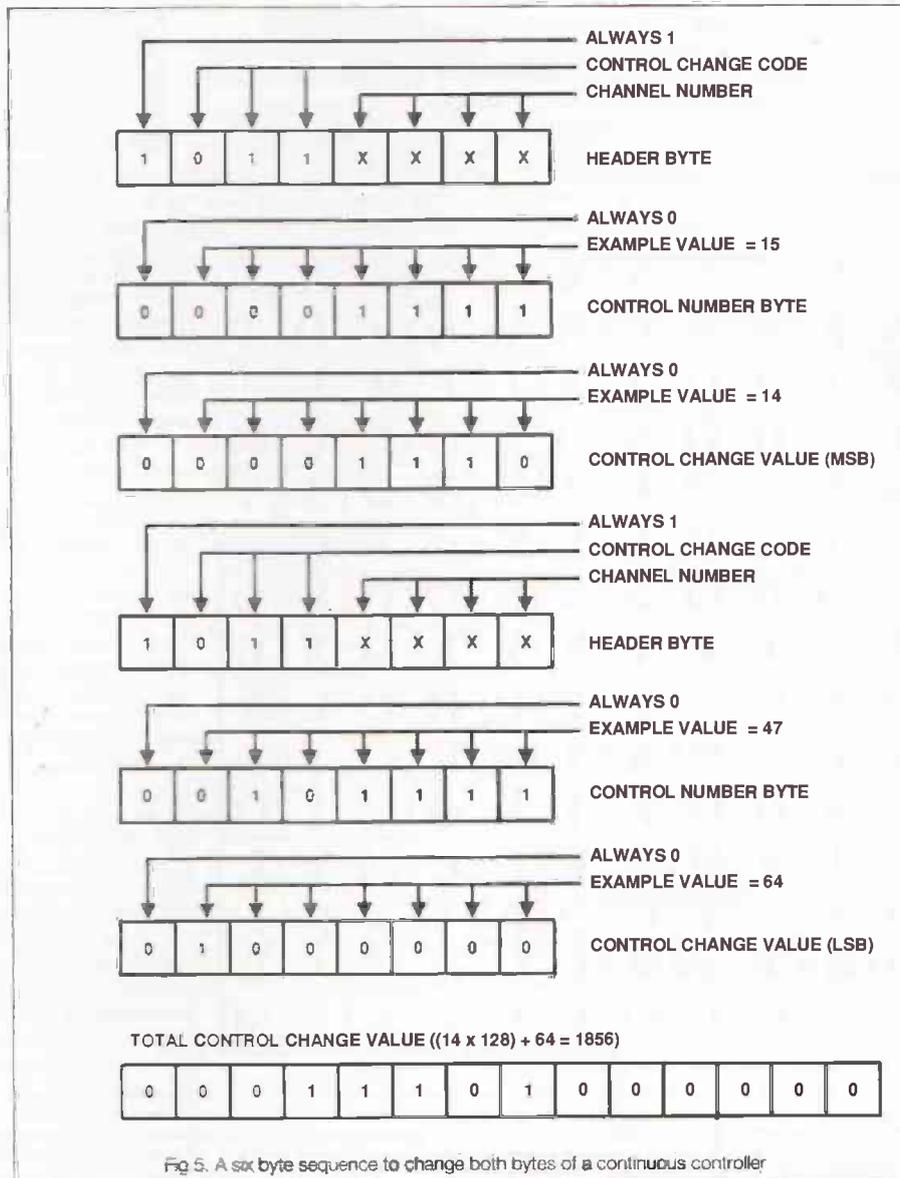


Fig 5. A six byte sequence to change both bytes of a continuous controller

changes both bytes of a high resolution control.

This method of obtaining high resolution control has proved to be something less than universally popular and many consider it to be an inefficient way of handling things. Few instruments seem to utilise the higher control numbers and have 7 bit resolution for the continuous controls. In fact some do not even implement 7 bit resolution and only utilise the five or six most significant bits of the coarse control. However, there are a few instruments which do use the full 14 bit resolution, or something close to it.

Next month we will consider MIDI controller assignments, special function controls and system messages.


Competition

In this month's ETI competition you could win a sophisticated electronic blood pressure monitor from Maplin Electronics.

With the increasing popular awareness of the importance of living a healthy lifestyle, it is hardly surprising that electronics systems are being employed to monitor body function and warn the user of impending problems, without the need for a lot of medical knowledge and otherwise complex measuring techniques. An example of this kind of electronic device is the newly released Maplin Blood Pressure Monitor.

This is an easy to use digital blood pressure tester which has been specifically designed to remove the complexities of measuring blood pressure and pulse rate, particularly for those who are not familiar with the technique. The monitor takes readings from the left index finger and shows the systolic and diastolic pressures, as well as pulse rate on an LCD display.

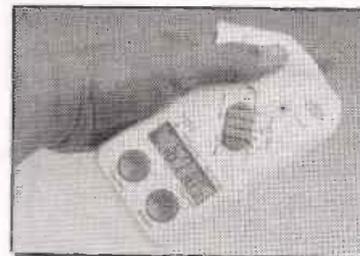The system is very easy to use and at various stages in operation will display a 'ready to measure' and 'heart' symbol to indicate the current stage of the operation. The monitor has its own pump, so no manual pumping is required, it will automatically inflate to a pressure of around 200mmHg and then start decreasing the pressure gradually.



Once measurement is complete, the monitor bleeps, deflates automatically and then displays the blood pressure and pulse rate. These alternate every few seconds until the monitor is reused or switched off. Also shown is the 'ready to measure' symbol. If it is not reused immediately the monitor will switch itself off automatically after 1 1/2 minutes, to conserve power.

To win this sophisticated blood pressure monitor, valued at £75, simply find all twelve of the hidden words in the following puzzle. To make it easier we will give you one clue - all the hidden words come from the text on this page.

Send your list of the words you have found, written on a postcard or the back of an envelope, to: ETI, Blood Pressure Monitor Competition, Argus House, Boundary Way, Hemel Hempstead, Herts. HP2 7ST.

All entries must be received before August 30th when a draw will be made from all correct entries to decide the winner.

Rules. The competition is open to all UK residents other than employees of ASP and Maplin or their families. The prizes are as stated and there is no cash alternative. The editor's decision is final and no correspondence can be entered into.

B	B	S	G	G	X	C	N	Y	E	U	C	W	R	P
R	V	V	L	N	P	E	V	U	B	W	N	T	D	T
F	F	U	Q	K	Y	O	D	I	S	D	E	W	V	T
T	M	C	T	T	V	H	Q	N	H	C	O	O	C	M
Q	H	G	I	W	F	L	T	F	I	K	T	O	J	V
I	X	E	B	L	I	R	B	L	S	K	O	V	C	O
I	M	F	L	J	O	P	O	A	A	S	G	U	E	D
O	M	M	E	E	U	T	R	T	Y	E	X	M	X	B
E	B	A	E	M	S	N	S	E	I	H	H	D	L	Y
F	L	E	P	Y	Y	L	C	A	S	N	K	O	I	L
H	T	I	S	L	N	D	U	E	I	S	O	G	I	O
V	N	K	B	N	I	W	H	P	V	D	U	M	W	L
G	H	K	D	Q	S	N	Y	C	O	W	T	R	E	L
D	V	J	I	O	R	W	Y	R	F	R	H	T	E	B
Y	O	N	X	F	Y	L	L	M	K	E	V	V	N	M

PROGRAMMER EPROM, EPROM & FLASH for all types 2k (2716) to 8 meg (27C080) 12.5 to 25 volt. Connects to printer port on IBM, fast program (27512 = 45 secs). Comprehensive editor software Requires 15-30 volt AC or DC power supply (optional extra £6.50) **only £99.95**

ROM EMULATOR. Works on ANY computer with a printer port. Code sent to printer appears in rom on target board. Fast download, switchable to emulate up to 32k Rom. **only £39.95**

PC SCOPE. Fast 8 bit A/D converter connects to printer port on IBM PC. Supplied with Scope and Voltmeter software with Data and A/D routines to write your own programs. **only £29.95**

PIC16C54/55/56/57/84/71 PROGRAMMER. Runs on IBM PC, with editor software, protection fuse blowing etc. requires 15-20 volt AC or DC power supply (optional extra £6.50) **only £69.95**

LOW COST PIC16C54/56/71/84 L.C.E. Connects to printer port on IBM PC. In circuit emulator with single step/go with breakpoints etc. **only £89.95**

Supplied with connection information and PIC DEV 54 or PIC DEV 71 software as below. **only £89.95**

PIC DEV 54. Integrated Text editor/Assembler/Disassembler/Simulator for 54/55/56/57 Pics. Runs on IBM PC. Single step trace, go with breakpoint etc. etc. Everything you need to write and debug programs. Runs with or without the L.C.E. unit. **Software only £29.95**

PIC DEV 71. As above but for PIC16C71/84 controllers. **Software only £29.95**

ASM51 + SIMS1. Text Editor/Assembler plus simulator for Micro controllers 8051/52. Runs on IBM PC. Full control of registers & memory. Label disassembly, program trace, single step etc. **Software only £19.95**

ASM48 + SIM48. Same as Asm51 but for 8748/49 Micro controllers. **Software only £19.95**

All hardware carries a 12 month parts & labour Guarantee. S.A.E. or telephone for further details. Please add £1.50 for Post/packing.

JOHN MORRISON (MICROS) Dept ETI,
4 REIN GARDENS, TINGLEY, WEST YORKSHIRE WF3 1JR
Telephone 0532 537 507



ATTENTION ALL NORTH AMERICAN READERS!

Did you know that you can order an annual subscription to this magazine direct from our official U.S. subscription representative?

For more information and rates contact:
Wise Owl Worldwide Publications,
4314 West 238th Street,
Torrance, CA 90505
Tel: (310) 375 6258

Talkback



Dear ETI

I have developed a small circuit which readers of ETI might find useful. This circuit monitors an 8-bit value on a set of data lines, and latches the peak value onto a further eight data lines. This output could be processed further or, as shown here, be used to drive two seven segment displays. An ideal application for such a circuit would be, for example, a vibration monitoring system where the peak vibration that occurs needs to be stored and displayed.

The circuit is based around a binary comparator, IC3 and a latch, IC1. The comparator constantly compares the input data, on inputs P, with the current peak value on inputs Q. If the input data is greater than the current peak value then the P>**greater than** Q line from the comparator goes low. A single NOT gate, IC2a, inverts this signal, causing the data to be latched into IC1. In order for the start-up to be orderly, i.e. the current peak value to be zero, a reset upon power up is provided by R1, C1 and IC2b. IC4 and IC5 are hexadecimal display drivers used to display the higher current value from RS.

The component values used in this circuit are as follows:

IC1	74LS273
IC2	74LS04
IC3	74LS684
IC4, 5	Hex Display (RS 586-734)
RN1	3K resistor SIL
R1	330K
R2,3	330ohm
C1	1µF
Vcc	+5V

T.B.Grant. Glamorgan.

Club contacts

Our regular list of amateur electronics clubs

British Amateur Electronics Club.
Contact the club secretary Mr
J.F.Davies on 0606 883742

Crystal Palace and District Radio Club, tel: 081 699 5732.

Lincoln short Wave Radio Club,
Lincoln. tel: 0427 788356.

London Live DIY Hi-Fi Circle, contact
Launcelot Dow, 7 Pymmes Gardens
South, Lower Edmonton, London N9
9NT.

Midland Amateur Radio Society, tel:
021 422 9787 or 021 443-1189
(evenings only).

Sudbury and District Radio Amateurs, tel: 0787 313212.

Thanet Electronics Club, A youth
group for school age people in East
Kent. Contact the club secretary Roy

Ashley, tel: 0304 812723.

If you run a club that is concerned with some aspects of electronics and computing we would like to hear from you so that we can include your club in our regular listing.

Feedback

Here at the editorial offices of ETI we want to provide you, our readers, with the sort of magazine that you want to read. We can of course guess what you would like to see in each issue of ETI, but a far better way is to rely upon feedback from readers. To help us in this process we are instituting a new concept, the 'Feedback Box'. We are asking readers to take a few minutes and write down on the back of a postcard the ratings which they would award to each article in this issue. Ratings should vary between 1 and 10, with 1 being poor and 10 being brilliant.

- A - Where on Earth am I?
- B - Computer controlled stepper motor
- C - Turbo speed indicator
- D - Anglers bite alarm
- E - PC Clinic
- F - Video light meter
- G - Magnetism and magnetometers
- H - Car lights on reminder
- I - An Introduction to MIDI

Just write the article letter followed by your score for that article and send to


Feedback Box August 94,

ETI,

Argus House,
Boundary Way,

Hemel Hempstead, Herts. HP2 7ST.

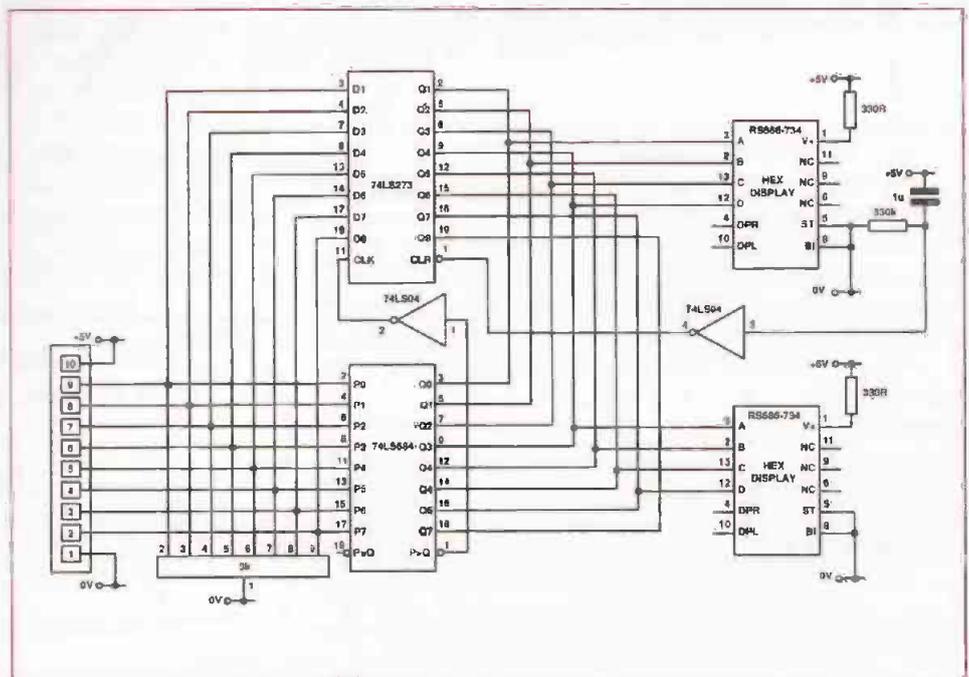To add an extra incentive, all replies received before August 30th 1994 will go into a draw and the winner will receive a 'goodies bag' of electronic components.




Practically Speaking

by Terry Balbirnie

Health and Safety

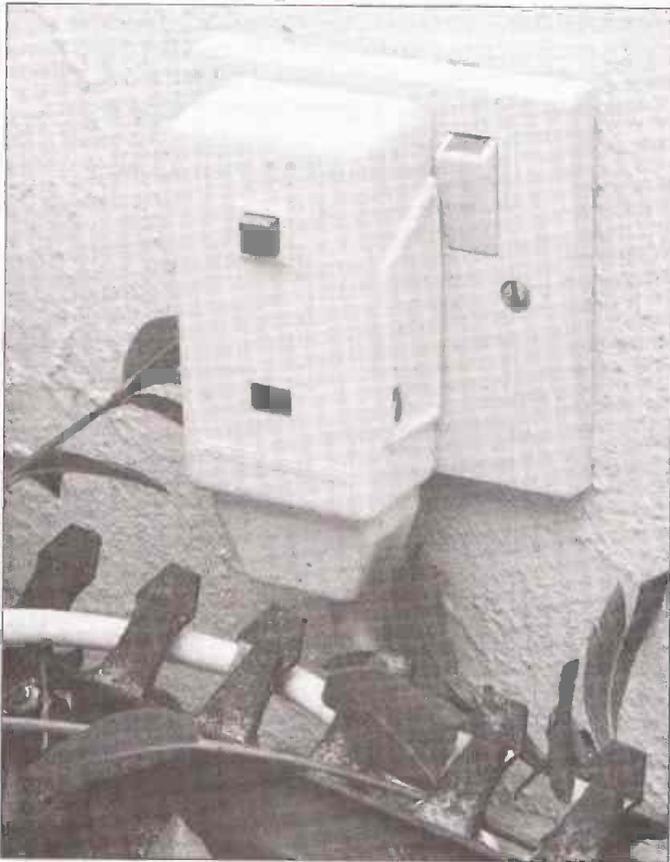Last month, we looked at the siting of a workshop inside the house. However, this will not be possible for many readers. An alternative idea is to use a partitioned section of the garage or a garden shed. This will be relatively inexpensive to set up, but the drawback is that such places are likely to be damp and certain



aspects of safety must be taken into consideration if mains electricity is to be used.

First decide if mains electricity is really needed. It is possible to operate a workshop without it and if there is any hesitation over safety, this must be the course to follow. Such a mains-free workshop will be discussed next month.

If you do decide to lay on mains power, you should use a qualified electrical contractor to provide advice on how to install it. Unless you know your IEE Wiring Regulations you should not attempt this job. If a supply already exists, it must be checked by a competent electrician to ensure that it was properly installed in the first place and is fit for the purpose. The Electricity at Work Regulations apply to private houses as well as work places - the person installing the supply is responsible for the safety of those using it.

Considerations

These are the most important points to consider. The wiring from the supply must be of adequate current rating, carry an earth conductor and be of the correct physical type. It must

terminate in a small consumer unit from where it will feed the circuits for power sockets, heating and lighting.

There will be a double-pole switch and separate fuses - 5A for lighting, 10A for heating and 15A for power sockets (only 5A if used for low-power experimental equipment). Rather than conventional fuses, miniature circuit breakers (MCBs) will be found more convenient because they can be instantly reset. Earthing must be efficient and any exposed metalwork earth bonded according to latest IEE regulations.

For safety reasons, the consumer unit must be of the type containing a RCD (Residual Current Device) - see illustration - or have separate RCDs for each circuit. The H98 PowerBreaker RCBO units are useful, because they combine miniature circuit breakers with RCDs. These are available in ratings from 6A to 32A.


A fluorescent light, rather than the tungsten filament, variety should be used because it is relatively shadow free and promotes safe working. A spotlight could also be used for close work. If a heater is needed, use the infra-red bathroom type rather than a free-standing one. This should be wall-mounted, as high as possible and operated through a cord switch.

You should fit a smoke detector in case the soldering iron or other equipment is left switched on and touching something, causing insulation to melt and burn. This must be of the type which can 'repeat' in the house. An add-on circuit which can provide a repeat facility using an ordinary cheap smoke detector will be given as a project in a future issue.

Another must is to provide some means of communicating with the house in an emergency. A simple bell push with a loud buzzer in the house will do, but more useful is a two-way system with a buzzer at each end. This can be built using 3-core wire as shown in Figure 1. Of course, a cheap intercom is even better.


It is essential to provide a good lock on the door - this will prevent a child entering in your absence. You are likely to leave things lying around with their lids removed and this could injure a child playing. They could end up with a very nasty burn trying their hand at soldering! In addition to a lock, it may be necessary to provide an intruder alarm arranged to give a warning inside the house. A circuit for such a simple alarm will also be described as a project in a future issue.

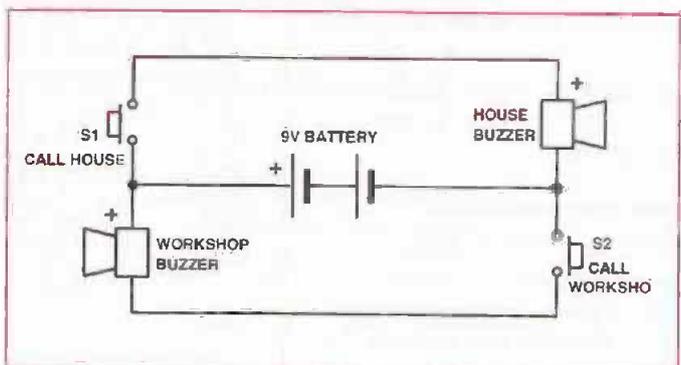Where a mains supply must be avoided, either because of the cost of installing it or on grounds of safety, then some alternative means of operating the workshop will need to be found. We shall see how this can be done next month.







Foils for this issue

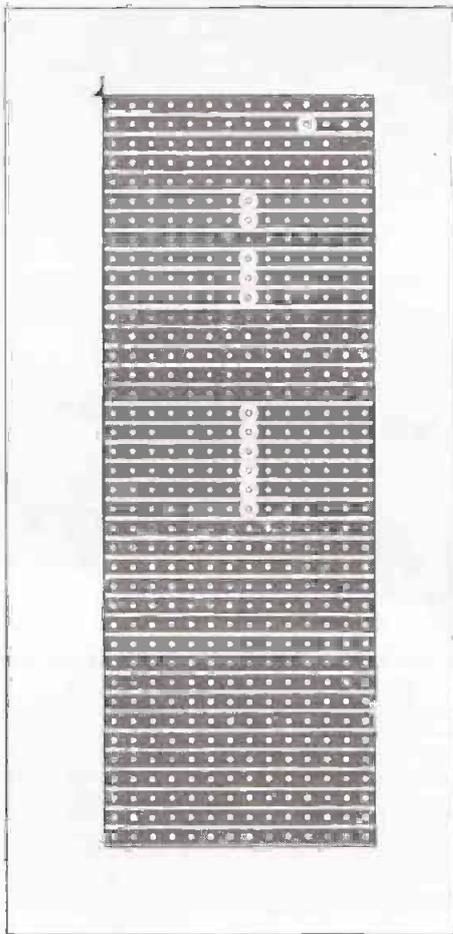


Car lights

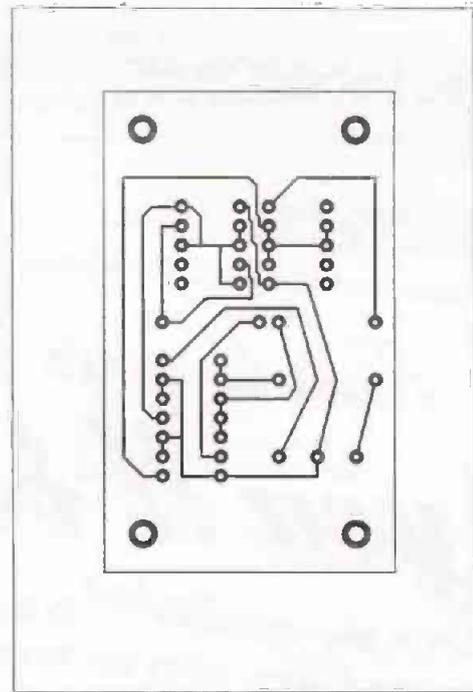


Turbo speed

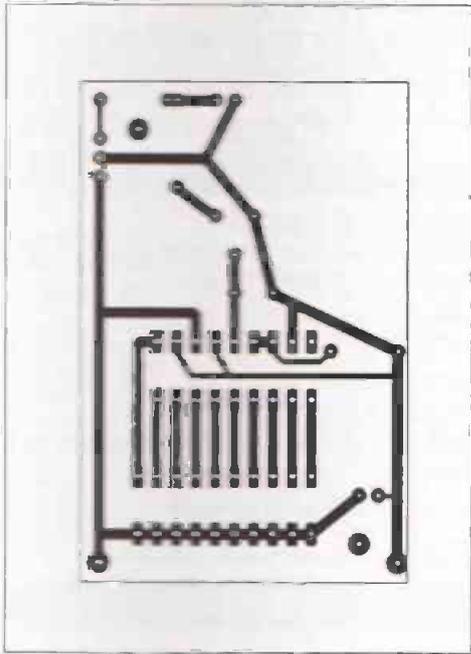


Video light meter

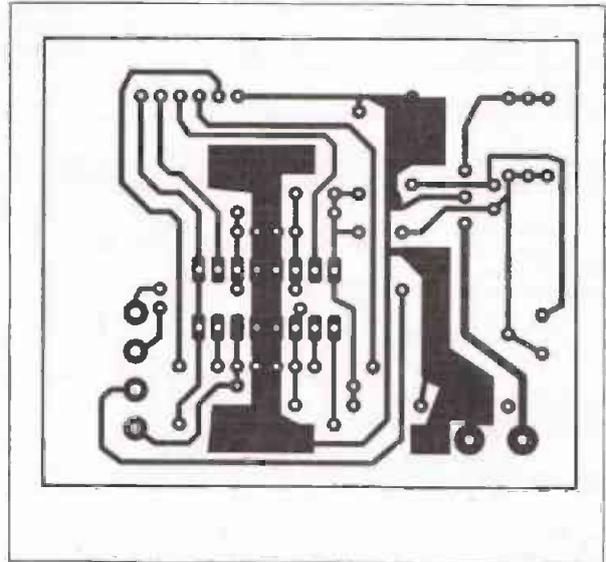

Stepper Motor control

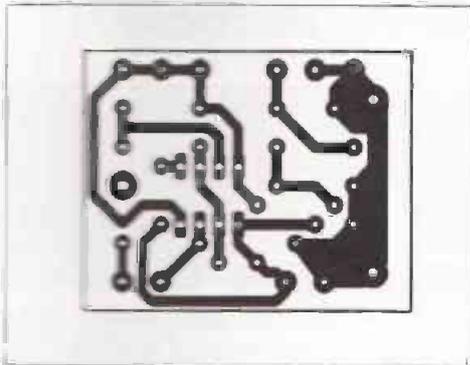

Bite alarm 2000

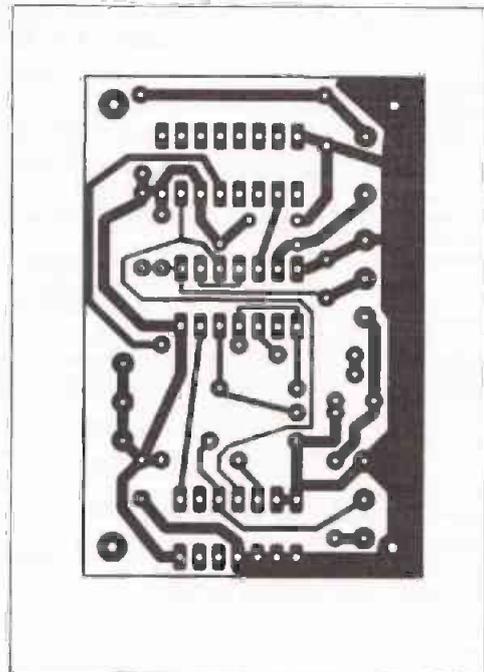


Bite alarm 3000

SEETRA X CAE - RANGER - PCB DESIGN

Ranger1 £100

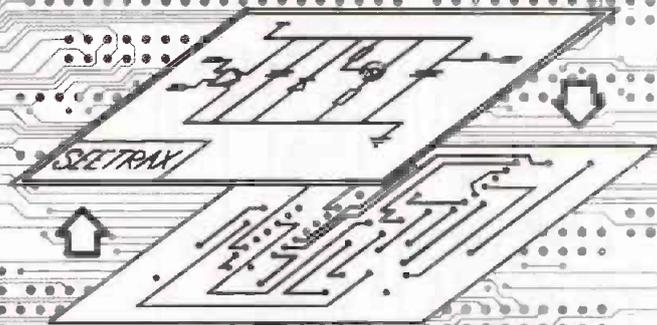- * Schematic capture linked to PCB
- * Parts and wiring list entry
- * Outline (footprint) library editor
- * Manual board layout
- * Full design rule checker
- * Back annotation (linked to schematic)
- * Power, memory and signal autorouter - £50



All systems upward compatible. Trade in deals available.

Call Seetray CAE for further information (demo packs).

Tel: 0705 591037

Fax: 0705 599036

Seetray CAE, Hinton Dunbar House, Broadway Lane,

Rowdean, Hampshire, RG8 0SG

All trademarks acknowledged

Ranger2 £599

- All the features of Ranger1 plus
- * Gate & pin swapping (linked to schematic)
- * Track highlighting
- * Auto track necking
- * Copper flood fill
- * Power planes (heat-relief & anti pads)
- * Rip-up & re-try autorouter.

Ranger3 £3500

- All the features of Ranger2 plus
- * UNED or DQ3 versions
- * 1 Micron resolution and angles to 1/10th degree
- * Hierarchical or flat schematic
- * Unlimited design size
- * Any shaped pad
- * Split power planes
- * Optional on-line DRC
- * 100% rip-up & re-try, push & shove autorouter

Outputs to:

- * 485 and 24 pin dot-matrix printers
- * HP Desk/Laser Jet, Canon BJet, Postscript (R) only
- * HP-GL, Houston Instruments plotters
- * Gerber photoplotters
- * NC Drill Excellon, Birch & Meyer
- * AutoCAD DXF

inventor toroidal transformers 225VA 10 5-0-10.5 primary D-260-285 secondary	£29.95	Airpax A82903-C large stepping motor 14v 7.5' step 27ohm 68mm dia body 6.3mm shaft	£8.95 or £200.00 for a box of 30
LEDs 3mm or 5mm red or green	6p each	Polyester capacitors box type 22.5mm lead pitch	
yellow	11p each	0.9uf 250vdc	18p each 14p 100+ 8p 1000+
High inlanely red, green or yellow 5mm	30p each	1uf 250vdc	20p each, 15p 100+, 10p 1000+
Cable ties	1p each	2.2uf 250vdc (27.5mm pitch)	30p each, 20p 100+, 15p 1000+
£49.50	per 10,000	3.3uf 100vdc	30p each, 20p 100+, 15p 1000+
High quality photo resist copper clad epoxy glass boards		1uf 50v bipolar electrolytic axial leads	15p each, 7.5p 100+
Dimensions	single sided	0.22uf 250v polyester axial leads	15p each, 7.5p 100+
3x4 inches	£1.09	Polypropylene 1uf 400vdc (Wima MKP10) 27.5mm pitch	100+
4x6 inches	£2.75	32x29x17mm case	75p each 60p 100+
5x12 inches	£5.20	Philips 123 series solid aluminium axial leads	33uf 10v & 2.2uf 40v
12x12 inches	£12.25	Philips 108 series 22uf 63v axial	30p each, 15p 1000+
Rechargeable batteries			
AA (HF7) 500mAh	£0.99	Multilayer AVX ceramic capacitors all 5mm pitch	
AA 700mAh	£1.75	100v	
C 2AH with solder tags	£3.80	100pf, 150pf, 220pf, 10,000pf (10n) 10p each, 5p 100+	
4AH with solder tags	£4.95	3.5p 1000+	
1/2AA with solder tags	£1.55	500pf compression trimmer 60p	
AAA (HP16) 180mAh	£1.75	40uf 370vac motor start capacitor (dielectric type containing no pcbs)	£5.95 or £49.50 for 10
AA 500mAh with solder tags	£2.55	Welwyn W23 9W 120ohm 35p each 20p 100+	
CH(HP1) 1.8AH	£2.20	680 ohm 2W metal film resistor 4p 100+, 2p 1000+	
D(HP2) 1.2AH	£2.60	Solid carbon resistors very low inductance ideal for RF circuits	
PP3 3.4V 1100mAh	£4.95	27ohm 2W, 68ohm 2W 25p each 15p each 100+	
Sub C with solder tags	£2.50	we have a range of 0.25w 0.5w 1w and 2w solid carbon resistors please send SAE for list	
1/3 AA with solder tags (phipsCTV)	£1.95	P C 400W PSU (Intel part 201035-001) with standard mother board and 5 disk drive connectors, fan and mains inlet/outlet connectors on back and switch on the side (top for tower case) dims 21x 149x 149mm excluding switch	£26.00 each £138.00 for 6
Standard charger charges 4 AA cells in 5 hours or 4Cs or Ds in 12-14 hours ±1xPP3 (1,2,3 or 4 cells may be charged at a time)	£5.95	MX180 Digital multimeter 17 ranges 1000vdc 750vac 2Mohm 200mA transistor Hfe 9v and 1.5v battery test	£12.95
High power charger as above but charges the Cs and Ds in 8 hours AAs Cs and Ds must be charged in 2s of 4s	£10.95	AMD 27256-3 Eproms £2.00 each, 1.25 100+ DIP switch 3PCO 12 pin (ERG SDC-3-023) 60p each 40p 100+	
Special offers please check for availability		Disk drive boxes for 5.25 disk drive with room for a power supply light grey plastic 67x268x247mm	£7.95 or £49.50 for 10
42 x 16mm dia 1.2v	£1.45	Hand held ultrasonic remote control £3.95	
Stick of 4 171mm x 16mm dds with red & black leads 4.8v	£5.95	CV2486 gas relay 30 x 10mm dia with 3 wire terminals will also work as a neon light 20p each or £7.50 per 100	
Computer grade capacitors with screw terminals		A23 12v battery for car alarms or lighters 75p each £50.00 per 100	
38000uf 20v	£2.50		
87000uf 10v £1.95, 68000uf 15v £2.95, 10000uf 16v	£1.50	All products advertised are new and unused unless otherwise stated	
£1.50, 58000uf 60v £4.95		wide range of CMOS TTL 74HC 74F Linear Transistors kits rechargeable batteries capacitors tools etc always in stock	
7 segment common anode led display 12mm	£0.45	Please add £1.95 towards P&P vat included in all prices	
LM2931A T5.0 low drop out 5v regulator TO220 package	£0.85		
7812 and 7912 12v 1A regulators	£20.00 per 100		
LM4337K TO3 case variable regulator	£1.95		
LM4337K TO3 case variable regulator	£1.95		
GsAs FET low leakage current 58873	£12.95 each £9.95 10+ £7.95 100+		
BS250 P channel mosfet £0.45, BC559 transistor	£3.95 per 100		
74L505 hex inverter	£10.00 per 100, used £7.48		
Microcontroller £3.50			
SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet	£1.95		
AM27502 £1.25 each 90p 100+ CD4007UB 10p 100+ 6p 1000+			
Sinclair light gun terminated with a jack plug and PP3 clip gives a signal when pointed at 50Hz flickering light with output wave form chart	£3.95		
DC-DC converter Reliability model V12P5 12v in 5v 200ma out 300v input to output isolation with data sheet	£4.95 each or pack of 10 £39.50		
Hour counter used 7 digit 240vac 50 Hz	£1.45		
QWERTY keyboard 58 key good quality switches new	£5.00		

JPG ELECTRONICS

276-278 Chatsworth Road
Chesterfield S40 2BH
Access Visa Orders (0246) 211202

Callers welcome

HAM RADIO TODAY

HRT is Ham Radio explained, appreciated and discussed from a practical point of view.

There are features on construction, conversions, packet radio and club news to appeal to experts and novices alike.

FIRST with news, FIRST with reviews, HAM RADIO - Today!

PHONE

SUBSCRIPTION & BACK ISSUES HOTLINE

0737 768611

Published 1st Friday of every month only £1.80

Order your copy from newsagent now or subscribe and we'll deliver every issue FREE!* * UK only

ETI Classified



James Gale
0442 66551

Send your requirements to:
ETI Classified Department, ASP, Argus House,
Boundary Way, Hemel Hempstead, HP2 7ST
Lineage: 65p per word (+ VAT) (minimum 15 words)
Semi display: (minimum 2.5cms)
£8.70 + VAT per single column centimetre.



Ring for information on series bookings/discounts.
All advertisements in this section must be prepaid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

KITS

STOP CAR THEFT FOR JUST £6

Revolutionary system to deter
with and prevent car
Kit = PCB - All Components
Assembled £5.95
Version 1 Battery
2 Cigarette lighter powered.
Simply write a cheque to
Mr. Massey at: 81, Darnley Road,
MK18 2ET with address and
version required for use.
**ORDER NOW FOR YEARS OF
PEACE OF MIND**

**NEW VHF MICROTRANSMITTER
KIT** tuneable 70-115MHz, 500
metre range, sensitive electret
microphone, high quality PCB,
SPECIAL OFFER complete kit
ONLY £5.95 assembled and
ready to use £9.95 inclusive P&P.
3 Watt FM transmitter kit £15.95.
Credit card orders Telephone:
021 457 7994, Fax: 021 457 9745.
Cheques/PO's to: C.E.C. (Dept
ETI), 1678 Bristol Road South,
Birmingham B45 9TZ. Send 2 x
1st Class stamps for details of
these and other kits.

SURVEILLANCE KITS

MRT1 MICRO TRANSMITTER, 25mm x 20mm including
sensitive mic., tuneable 80-115MHz. 500M range. Kit £4.95
Assembled £8.95
MTT1 TELEPHONE TRANSMITTER 35mm x 10mm,
powered from line, discreetly transmits all conversations.
500M range, 80-120MHz. Kit £5.95 Assembled £10.95
All prices include p&p. Send 2x2nd class stamps for
catalogue. Cheques/PO's payable to:
EXCEL PRODUCTS (Dept ETI)
Unit 14, Sunningdale,
Bishop's Cleeve, Herts CM23 2PA

SLIDER VARIABLE Power-
supplies, 9-25V. DC - regulated
£3 - 100 watt poweramps + 3
heatsinks £9 - Stereoamps +
selector 10W £5 - K.I.A. 1
Regent Road, Ilkley LS29... New
+ Directions!

COMPONENTS

EPROM, PLDs + Microcontrollers
copied or programmed, we supply
devices/convert discrete logic to
PLDs. PO Box 1561 Bath 0225
444467.

COURSES

Start training now with the specialists for
the following courses. Send for our
brochure - without obligation or
Telephone us on 0626 779398 ETI 8/94

- | | |
|------------|---|
| Name _____ | <input type="checkbox"/> Telecomms
Tech C&G 2710 |
| _____ | <input type="checkbox"/> Radio Amateur
Licence C&G |
| _____ | <input type="checkbox"/> Micro-
processor |
| _____ | <input type="checkbox"/> Introduction to
Television |

Radio & Telecommunications Correspondence School
12 Moor View Drive, Teignmouth, Devon TQ14 9UN

DESIGN SERVICE

SUMMER RAIN DESIGN SERVICES

Circuit Diagrams • Schematics • Assembly
Details • PCB Drilling • Mounting • Parts
Lists • Netlists • Gerber Files • NC Drilling •
Wiring Schematics • Service Diagrams •
Mechanical Details • Manuals
If you require any of these services, you can have a
quote for the design of a prototype PCB, prototyped
PCB design packages (quantity of 100), your design needs,
great or total, are welcome. Delivery: competitive rates
from a new specialist company.
If you desire a quality service at an affordable rate, do not
hesitate to call 0800 800 800.
John Partridge, an experienced PCB designer,
97 Old Street Road, Hemel Hempstead, HP2 0DG

**THIS SPACE
COULD BE
WORKING FOR
YOU!
CALL 0442 66551**

Falcon DIY SPEAKERS

Send for our FREE price list PL22:
All we ask for is a large S.A.E.
36p stamp or \$2 bill U.S. overseas.
(Europe - 3 International reply coupons)
SYSTEM DESIGNS (Total Kits)
Focal, KEF Constructor, Seas, etc.
DRIVE UNITS FOCAL, KEF, Audax,
Coles, Peerless, Seas, Siare, Elac Metal
Dome, Scanpeak, etc.
Also Group/Disco Units
CROSSOVER NETWORKS -
Active & Passive Components,
Accessories, Polypropylene Caps.
AUDIO AMATEUR PUBLICATIONS
BACK ISSUES:
Speaker Builder, Audio Amateur & Glass
Audio, L/S Cookbook + books
Full details from
FALCON ELECTRONICS
(Dept E.T.I.) Tabor House, Mulbarton,
Norfolk NR14 8JT (0508) 78272
(Proprietors: Falcon Acoustics Ltd)

RACKS EQUIPMENT

19" RACK-MOUNT EQUIPMENT?

Frames, cabinets and flight cases for
rack - and non-rack - equipment.
A wide range of accessories available.
For further information and brochure
contact:

**GROVESTREAM ENGINEERING
SERVICES, 29 Silverdale Road,
Tadley, Hants RG26 6JL.
Tel/Fax: 0734 813395**

**FOR DETAILS OF
ADVERTISING
RATES CALL
JAMES ON
0442 66551**

SOFTWARE

SHAREWARE REFERENCE GUIDE

Find out what really is available in PD &
Shareware - ham radio, graphics, business,
scientific, electronics, maths, education, etc. You'll
find them all here, every thing you need in one
book. Thousands of the best PD & shareware
programs for DOS & Windows, described in
detail with the hardware requirements for each.
This is probably the most complete and up-to-
date shareware reference book available today.
For your copy, send £2.50 by cheque, PO, cash or
pay by Access/Visa to:
**PD&S, Winscombe Hse, Beacon Rd.,
Crowborough, Sussex, TN6 1UL,
Tel 0892 663296 Fax 0892 667473**

PLANS

ELECTRONIC PLANS, laser
designs, solar and wind generators,
high voltage teslas, surveillance
devices, pyrotechnics and com-
puter graphics tablet. 150 projects.
For catalogue, SAE to Plancentre
Publications, Unit 7, Old Wharf
Industrial Estate, Dymock Road,
Ledbury, Herefordshire, HR8 2HS.

FOR SALE



COOKE INTERNATIONAL SUPPLIER OF QUALITY USED TEST INSTRUMENTS

ANALYSERS, BRIDGES, CALIBRATORS, VOLTMETERS,
GENERATORS, OSCILLOSCOPES, POWER METERS, ETC
ALWAYS AVAILABLE

ORIGINAL SERVICE MANUALS FOR SALE
COPY SERVICE ALSO AVAILABLE

EXPORT, TRADE AND U.K. ENQUIRIES WELCOME
SEND LARGE S.A.E. FOR LISTS OF EQUIPMENT AND MANUALS
ALL PRICES EXCLUDE VAT AND CARRIAGE
DISCOUNT FOR BULK ORDERS SHIPPING ARRANGED

OPEN MONDAY TO FRIDAY 9AM - 5PM

COOKE INTERNATIONAL
ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham, Bognor Regis,
West Sussex, PO22 0EB Tel (+ 44) 0243 545111/2 Fax (+ 44) 0243 542457

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V 50/60Hz

OUTPUT	Price	P&P
0.5KVA 2.5 amp max	£31.90	£6.00
1KVA 5 amp max	£44.53 inc VAT	£7.00
2KVA 10 amp max	£59.40	£8.50
3KVA 15 amp max	£79.78 inc VAT	£8.50
5KVA 25 amp max	£139.15	(Plus Carriage)

Buy direct from the Importers. Keenest prices in the country.

COMPREHENSIVE RANGE OF TRANSFORMERS - I.T. ISOLATION & AUTO

(110/240V Auto transfer either cased with American socket and mains lead or open frame type. Available for immediate delivery)

WIDE RANGE OF KENON FLASHTUBES

Write/Phone your enquiries

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt	£12.00 (callers only)	(£14.10 inc VAT)
2ft 20 watt	£7.44 + £1.25 p&p	(£10.21 inc VAT)
12in 8 watt	£4.80 + 75p p&p	(£6.52 inc VAT)
8in 6 watt	£3.98 + 50p p&p	(£5.24 inc VAT)
6in 4 watt	£3.98 + 50p p&p	(£5.24 inc VAT)

230V AC BALLAST KIT

For either 6in, 9in or 12in tubes £6.05 + £1.40 p&p (£8.75 incl)

400 WATT UV LAMP

Only £34.00 + £2.50 p&p £42.89 inc VAT

160 WATT SELF BALLASTED BLACK LIGHT MERCURY BULB

Available with BC or ES fitting, price inc VAT & p&p and VAT £23.55

12V D.C. BILGE PUMPS

500 GPH 15ft head 3 amp £19.98
1750 GPH 15ft head 9 amp £34.55
Also now available: 24V D.C. 1750 GPH 15ft head 5 amp £35.55. All designed to be used submerged. PRICES INCLUDE P&P & VAT

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Argon Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £15.00 + £2.00 p&p (£19.98 inc VAT)

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical use etc.
Approx 16 joules. Adjustable speed £60.00 + £3.00 p&p (£62.28 inc VAT)
Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT)
SAE for further details including Hy-Light and industrial Strobe Kits.

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB
FAX 081 995 0549 081-995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10

Showroom open Monday/Friday

Ample Parking Space

"BOFFINS SPECIAL" - UNIQUE OFFER

Surplus Precision Medical Unit, internally in excellent condition. Designed primarily to inject a precise controllable amount of fluid from a medical syringe (latter not supplied). Contains the following removable components: Dual Micro Processor Boards and EPROMS Escap Precision 12V DC Motor with 300:1 Gear Box and optical encoder coupled to a precision threaded drive mechanism. Mains supply with 6 x 1.5V Ni-Cad A.A. cells back-up. L.C.D. Digital read-out 17mm high with legends Audible warning.

These are sold for the dismantling of the exceptional quality components. Regret no Carcans available. Ridiculously low price £20.00 - £4.00 p&p (£28.20 incl VAT)

12V D.C. GEARED MOTOR

12V D.C. Reversible precision built Motor Output speeds no load approx. 12V-26 rpm, 9V-20 rpm, 6V-12 rpm. Will work at lower voltages and still retain a reasonable torque. Ideal for robotics etc. Size L: 40mm W: 29mm H: 39mm Shaft: 3mm dia x 10mm long. Price: £8.00 + 50p p&p (£10.00 inc VAT)

240V AC CENTRIFUGAL BLOWER

New Manul. Surplus Skeleton Blower suitable for mounting inside an enclosure to cool equipment. Overall size 130x110x85mm Outlet 90x35mm Impeller 60mm dia x 60mm long £14.10 incl P&P & VAT

SEWING MACHINE MOTOR

Brand new 220/240V AC/DC SEWING TRIC 2 lead Brush Motor. Size L: 100mm x H: 70mm x W: 55mm Spindle 1.4in dia x 1in long £14.10 incl P&P & VAT

GEARED MOTORS

71 RPM 20lb inch torque reversible 115V AC in-pul including capacitor and transformer for 240V AC operation. Price inc VAT & p&p £23.50.

SOLID STATE EHT UNIT

Input 230/240V AC. Output approx 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec. 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (£12.81 inc VAT) NIMS

SAVE POUNDS!!!

Build your own forged bank note detector. Can detect counterfeiters amongst a quantity of notes. Complete kit of parts less case 240V a.c. including 5" UV black light tube, starter and holder, a pair bi-pin tube holders Total price including p&p & VAT only £13.99

WASHING MACHINE WATER PUMP

Brand new 240V AC fan cooled. Can be used for a variety of purposes. Inlet 1 1/2 in outlet 1 in dia. Price includes p&p & VAT £11.20 each or 2 for £20.50 inclusive.

MICROSWITCH

Pye 15 amp changeover lever microswitch, type S171 Brand new price 5 for £7.05 inc VAT & p&p

LEN COOKE ENTERPRISES

UNIT 5 SOUTHALL ENTERPRISE CENTRE BRIDGE ROAD SOUTHALL MIDDXX. UB2 4AE

Tel: 081 813 9946 Fax: 081 574 2339

We Buy, Sell, Repair & Calibrate Electronic Test Instruments

HP 8165A Programmable Signal Source	£2,500
HP 3580A Spectrum Analyser	£1,500
HP 141T/8552B/8554B	£1,450
HP 8590B opt. 001 Spectrum Analyser	£4,500
HP 54500D Digitising Scope	£2,500
HP 9303 Audio Analyser	£2,650
Marconi 2955 Comms Test Set	£3,000
Marconi 2018 RF Signal Generator	£1,650
Marconi 2019 RF Generator	£1,850
Marconi 2022D RF Generator	£2,000
Marconi 2370/1 Spectrum Analyser	£1,750
Racal 9303 RF Level Meter	£850
Racal 9902A Frequency Counter	£195
Bradley 192 Scope Calibrator	£1,200
Balatine Calibrator	£1,000
Tektronix 2215 Scope	£450
Tektronix 465	£450
Tektronix 2235	£750
Tektronix 2211 Digital Storage	£1,200
Tektronix 492 Spectrum Analyser	£5,500
DC Power Supplies 0-50V/2A	from £50
Gould OS3000 40Mhz Scope	£250
Hameg 203-6 20Mhz Scope	£295
Ferograph Recorder Test Set	£395
Wayne Kerr 4225 LCR Meter	£525

TELEPHONE: 081 813 9946 FAX: 081 574 2339

TECHNICAL & SCIENTIFIC SUPPLIES

- Professional second user equipment.
- Components
- Special spares
- Transducers
- Instrumentation
- Professional Consultancy

Please write, phone or fax anytime

PO Box 19, Hythe, Southampton, Hampshire SO4 6XQ.
Tel. 0703 848666 Fax. 0703 897079

BURGLAR ALARMS

FREE TECHNICAL ADVICE
FREE DESIGN GUIDE
FREE 16 PAGE FULL COLOUR CATALOGUE & FREE DELIVERY

TRADE ENQUIRIES WELCOME

STOP SHOP *by mail*

2A EALING ROAD, AINTREE, LIVERPOOL L9 0LR
TEL: 051-523 8440
FAX: 051-523 8121

SWC SCIENTIFIC WIRE COMPANY

ENAMELLED COPPER WIRE
TINNED WIRE SILVER
PLATED COPPER WIRE
SOLDER EUREKA WIRE
NICKEL CHROME WIRE.
BRASS WIRE LI TZ WIRE
BIFILAR WIRE MANGANIN
WIRE TEFZEL WIRE NICKEL
SAE BRINGS LIST 18 RAVEN
RD LONDON E18 1HW
FAX 081 559 1114

NEWMARKET TRANSFORMERS LTD

Mail Order Transformer Specialists.
Toroidal and Laminated Transformers, 3VA to 1kVA.
Fast delivery. Competitive prices. Quality guaranteed.
Phone: Michael Dorman on 0638 662989 for Immediate Quote

Solid State Relays

Switch 240V from transistor, logic or computer outputs 3-32V D.C. control optically isolated.
4A pcb mount £5.45
10A tag connect £8.54
delivery incl apply for full range
Eric Jones, Dept. ETI, 01
85 Birchwood Av., Hatfield AL10 0PT
Tel: 070 726 5936 Fax 070 727 0877

LIVERPOOL

PROGRESSIVE RADIO

87/93 Dale Street
Tel: 051 236 0982 051 236 0154

47 Whitechapel
Tel: 051 236 5489
Liverpool 2

THE ELECTRONICS SPECIALISTS'
Open: Tues-Sat 9.30-5.30

TURN YOUR SURPLUS TRANSISTORS, ICS ETC INTO CASH immediate settlement.

We also welcome the opportunity to quote for complete factory clearance.

Contact:

COLES-HARDING & CO.

Unit 58, Queens Road, Wisbech, Cambs PE13 7PQ

BUYERS OF SURPLUS INVENTORY ESTABLISHED OVER 15 YEARS

Tel: 0945 584188
Fax: 0945 475216

COMPELEC

1994 BARGAIN LIST
THE ELECTRONIC ESSENTIAL MILLIONS OF COMPONENTS AT UNBEATABLE PRICES FOR A FREE COPY PHONE, FAX OR WRITE (TRADE ONLY)

14 CONSTABLE ROAD, ST IVES, HUNTINGDON, CAMBS. PE17 6EQ
0480 300619

WE ALSO PURCHASE ALL TYPES OF ELECTRONIC COMPONENTS, LISTS TO ABOVE ADDRESS.

ADVERTISING IN ETI COULDN'T BE EASIER - SIMPLY CALL JAMES ON 0442 66551

WANTED

WANTED

Receivers, Transmitters, Test Equipment,
Components, Cable and Electronic, Scrap.
Boxes, PCB's, Plugs and Sockets, Computers,
Computer Scrap, Edge Connectors.

**TOP PRICES PAID FOR ALL TYPES OF
ELECTRONIC EQUIPMENT.**

**A.R. Sinclair Electronics,
Stockholders, 2 Normans Lane,
Rabley Heath, Welwyn, Herts AL6 9TQ.
Telephone: 0438 812 193.
Mobile: 0860 214302. Fax: 0438 812 387**

**STAND OUT FROM THE
REST WITH**

SPOT COLOUR

**CALL JAMES ON 0442
66551 FOR ADVERTISING
DETAILS**

**ARGUS BOOKS PUBLISHING
FOR THE SPECIALIST**


**THE FULL
RANGE OF
ARGUS BOOKS**

*are available from
all good book
and hobby
shops or con-
tact Argus*

*Books direct
for a 1993*

Complete List.

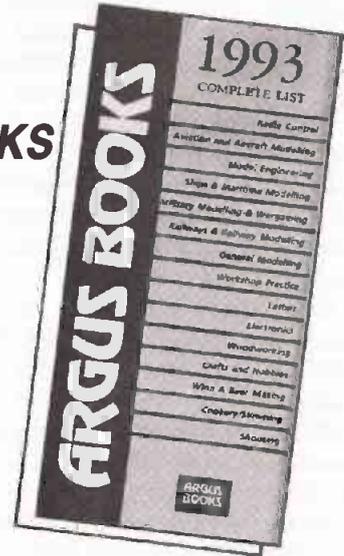**COMPLETE LIST, Argus Books,
Argus House, Boundary Way,
Hemel Hempstead, Herts. HP2 7ST
OR PHONE 0442 66551 EXT. 203**



**ELECTRONICS TODAY INTERNATIONAL, CLASSIFIED
ADVERTISEMENT DEPARTMENT, ARGUS HOUSE, BOUNDARY
WAY, HEMEL HEMPSTEAD HP2 7ST**

Rates: Lineage 65p per word + VAT minimum 15 words.

Semi-display £8.70 per single column cm plus VAT. No reimbursements for cancellations.

All ads must be pre-paid.

Name

Address

Daytime Tel. No:

Signature Date

PLEASE DEBIT MY ACCESS/BARCLAYCARD No.

Expire Date

FOR SALE COMPONENTS PLANS OTHER - PLEASE STATE

Open Forum

It is normal practice today for electronics system engineers to incorporate microprocessor systems into their designs.

Indeed, you will probably find a microcontroller chip embedded into the most mundane of products. Doing so makes the design simpler, cheaper to make, quicker to design and, of course, easier to change in the face of changing customer needs.

It is hardly surprising, therefore, that chip designers are moving in the same direction. Rather than design a complex chip from scratch as a purely hardware implementation, it is often much quicker and cheaper to use a dedicated embedded microcontroller to do the job. Chip manufacturers have found that such an approach allows complex products to be quickly developed to exploit new niche markets.

In the face of this trend, it is good to discover that a British designed and produced microprocessor is being adopted by two major semiconductor manufacturers as their choice for an embedded processor to be employed in future chip designs.

The British company is ARM, the RISC processor manufacturer set up jointly by Acorn Computers, Apple and chip manufacturer VLSI. The two big semiconductor producers are Samsung, one of the world's top ten, and IBM, who besides being still the world's largest computer company are also, surprisingly, the world's biggest semiconductor company.

With licensing agreements like these, ARM has placed itself among the top players at the very leading edge of semiconductor and information technology. It shows what is possible, since this is a company founded by men of technical vision as well as men of commercial acumen. It was not founded by UK Government or EEC directives, or aided by subsidies.

This is a typical high technology venture, one that may have seemed risky to the man in the street and extremely risky to the average bank manager or civil servant, but not to the founders, the men who have the technical vision that others so often lack. Equally importantly,

they are men who have faith in their vision and the technical and commercial acumen to turn that vision into reality.

If a country is to succeed in high technology manufacturing then it needs people like this. People like Bill Gates in the US, a man whose vision of what personal computers should be and how they will be used, coupled with his own commercial and technical genius has, in just twenty years, allowed him to build from scratch the world's largest software company and in the process become one of the world's richest men. Or, on this side of the Atlantic in the UK, another example is someone like Robert Madge, a man who foresaw the future demand for computer networks and developed the technology for them. An outstanding businessman and engineer, he has built up a company valued at over £300 million from nothing, in under ten years. Just as ARM has been successful without government aid and intervention, so the above two examples and many more like them, have also been successful without and often in spite of, governments, civil servants and their like. Indeed, if the government really wants to foster the growth of new high technology industries, then it should provide the appropriate encouragement for such individuals.

These people are the modern equivalent of the great Victorian engineer industrialists, such as Parsons, Bell and Eddison. Such people are rare, but not that rare. Governments should help them by freeing them to do what they do best, build high technology businesses.

Governments cannot direct the development of high technology, however much they might like to think that they can. They just don't have the expertise for a start. Furthermore, committees of so called experts will never agree on the proper direction for the application of grants and subsidies, the compromise agreements of such committees will always be wrong. Leave such decisions to the engineering entrepreneur, give him tax breaks and free him of red tape, but don't tell him what to do.

Next Month...

In the next issue of ETI we will be bringing you a number of interesting and useful projects. They include a handy transistor tester from Robert Penfold, a caravan low bar alarm from Terry Balbirnie and for PC users, a handy little alarm which will warn you if your PC is getting too hot and prevent any damage to expensive components. We will also be concluding the computer controlled stepper motor project and continuing our look at measuring magnetism with the construction of a flux gate magnetometer.

In the next issue we will also be introducing the start of a sensational new computer project, the ETI Transputer board. This high power super-processor board could be the main building block for a parallel computer, a sophisticated robot vision system, or a high speed signal processor.

We will also be continuing our regular series. Robert Penfold will delve further into the mysteries of MIDI and PC Clinic will look at the organisation and upgrading of memory systems. The 'Tomorrow's Technology' feature looks at the fascinating advances being made in the fusion of biochemistry with electronics - the world of bioelectronics.



EDITORIAL

Editor **Nick Hampshire**

Sub Editor **Jim Bluck**

CREATIVE

Art Editor **Peter Kirby**

Technical Illustration **John Puczynski**

Photography **Manny Cefai**

ADVERTISEMENT SALES

Display Sales

Hellen Taylor

Advertisement Copy Control

Marie Quilter

Classified Sales

James Gale

MANAGEMENT

Managing Director

Terry Pattison

Circulation & Promotions Manager

Debra Stuppel

Production Manager

Tony Dowdeswell

Group Editor

Stuart Cooke

Group Advertisement Manager

Claire Jenkinson



ISSN
0142-7229

ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, plans, drawings and programs and all copyright and all other intellectual property rights therein belong to Argus Specialist Publications. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications and reproduction requires the prior written consent of the company ©1990 Argus Specialist Publications. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Subscription rates-UK £23.40 Europe £30.30 Sterling Overseas £31.50 US Dollars Overseas \$52.00

Published by Argus Specialist Publications, Argus House, Boundary Way, Hemel Hempstead HP2 7ST. Telephone (0442) 66551. UK newstrade distribution by SM Distribution Ltd, 6 Leigham Court Road, London SW16 2PG. Telephone 081-667 8111. Overseas and non-newstrade sales by Magazine Sales Department, Argus House, Boundary Way, Hemel Hempstead, HP2 7ST. Telephone (0442) 66551. Subscriptions by Argus Subscription Services, ETI, Queensway House, 2 Queensway, Redhill, Surrey RH1 1QS. Telephone (0737) 768611. US subscriptions by Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA90505 USA. For Visa/Mastercard orders in USA - Telephone (310) 375 6258 Fax (310) 375 0548. Pacific Time: 9am-9pm Weekdays. 10am-6pm Weekends. Typesetting and origination by Ebony, Liskeard, Cornwall. Printed by Wiltshire Ltd Bristol.



Argus House, Boundary Way,
Hemel Hempstead HP2 7ST
Telephone (0442) 66551
Fax (0442) 66998

M & B RADIO (LEEDS)

THE NORTH'S LEADING USED TEST/EQUIPMENT DEALER

SIGNAL GENERATORS

MARCONI 2018 80KHZ TO 520MHZ SYNTHESIZED	£750
MARCONI 2020 50KHZ TO 520MHZ SYNTHESIZED	£500
MARCONI 2008 10KHZ TO 520MHZ INC RF PROBE KIT	£300
MARCONI 2015/2171 SYNCHRONIZER 10MHZ TO 520MHZ	£325
MARCONI 2016 10KHZ TO 520MHZ AM/FM	£200
MARCONI 2015 10MHZ TO 520MHZ AM/FM	£195
ADRET 740A 100KHZ TO 1120MHZ SYNTHESIZED	£1450
HP8643D 2.3GHZ TO 13GHZ OPT001/003 SOLID STATE GENERATOR	£4750
HP3336A SYNTHESIZER/LEVEL GENERATOR	£650
HP8640A 500KHZ TO 512MHZ OPT001	£550
HP8640B 500KHZ TO 512MHZ OPT001	£650
HP8640C 500KHZ TO 512MHZ OPT004 A/VIONICS VERSION	£1000
HP8610C SWEEPER MAINFRAME (AS NEW)	£300
HP8620C/86220A RF PLUG-IN 10MHZ TO 1300MHZ	£1200
HP8620C/86290B RF PLUG-IN 2GHZ TO 18.6GHZ	£2750
HP4204A 10KHZ TO 1MHZ OSCILLATOR	£250
FARNELL SSG1000 10KHZ TO 100MHZ SYNTHESIZED (AS NEW)	£1500
FARNELL SSG2000 10KHZ TO 2000MHZ SYNTHESIZED (AS NEW)	£2250
FARNELL SSG520 10MHZ TO 520KHZ SYNTHESIZED	£400
POLRAD 1106ET 1.8GHZ TO 4.6GHZ WITH MODULATOR	£400
GIGA GR1101A 12GHZ TO 18GHZ PULSE GENERATOR (AS NEW)	£750
SAYROSA MA30 FREQUENCY OSCILLATOR 10KHZ TO 0KHZ	£300
RHODE & SCHWARZ SMC1 4.8GHZ TO 12.8GHZ	£450
HP8618A 1.8GHZ TO 4.5GHZ	£195
TEKTRONIX 141A PAL TELEVISION TEST SIGNAL GENERATOR	£500
ADRET 2023DA 1MHZ SYNTHESIZED SOURCE	£195
HP8673A SYNTHESIZED SIGNAL GENERATOR 2GHZ TO 18GHZ	£6200
HP3586A SELECTIVE LEVEL METER 50HZ TO 32.5MHZ	£1850
TEXSCAN VS-60C SWEEP GENERATOR 1000MHZ	£450

SPECTRUM ANALYSERS

B&K 2033 1KHZ TO 20KHZ AUDIO ANALYSER	£2750
HP3581A WAVE ANALYSER 15KHZ TO 50KHZ (AS NEW)	£850
HP3582A 0.02HZ TO 25.5KHZ DUAL CHANNEL AUDIO ANALYSER	£3000
HP8558B 10MHZ TO 1500MHZ WITH 182T MAINFRAME	£2000
HP141T 8552B/8553B 110MHZ WITH 8413A TRACKING GENERATOR	£2000
HP141T 8552A/8554B 100KHZ TO 1250MHZ (AS NEW)	£1250
HP141T 8555A/8552B 10MHZ TO 18GHZ SPECTRUM ANALYSER SUPPLIED WITH ADDITIONAL HP8553B 1KHZ TO 110MHZ RF PLUG-IN	£2000
HP8444A TRACKING GENERATOR OPT05B	£1500
HP8553B 1KHZ TO 110MHZ LATE MODEL ANALYSER PLUG-INS	£200
WAYNE KERR RA200 FREQUENCY RESPONSE ANALYSER	£400
HP3580A 50KHZ TO 50KHZ AUDIO ANALYSER	£1500
HP3581C SELECTIVE VOL METER 15KHZ TO 50KHZ	£750
TEXSCAN AL51 4MHZ TO 1000MHZ ANALYSER	£750
EATON 2075B NOISE GAIN ANALYSER 10MHZ TO 2GHZ	£2000

OSCILLOSCOPES

TEKTRONIX SC504/TM503/DM501 PORTABLE 80MHZ SCOPE/DVM	£600
TEKTRONIX 475 200MHZ DUAL TRACE	£400
TEKTRONIX 465 100MHZ DUAL TRACE	£345
TEKTRONIX 465B 100MHZ OSCILLOSCOPE	£400
TEKTRONIX 466 100MHZ STORAGE	£395

HP1722B 275MHZ MICROPROCESSOR CAL MEASUREMENTS

(AS NEW)	£700
HP1725A 275MHZ DELTA TIME AND DELAYED SWEEP (AS NEW)	£550
TEKTRONIX 7A13/7A12/7A11/7B53 100MHZ 4 CHANNEL STORAGE	£600
TEKTRONIX 7603/7A28/7A29/7B53A 1GHZ OSCILLOSCOPE	£750
PHILIPS PM3217 50MHZ 2 CHANNEL DELAYED TIME BASE	£400
IWA TSUI 556123 100MHZ 4 CHANNEL CURSOR READOUT	£900
KIKUSUI CM6100 100MHZ 5 CHANNEL	£500
NICOLET 4094A D O DIGITAL OSCILLOSCOPE (TO CLEAR)	£250
TELEQUIPMENT D14 15MHZ PORTABLE NICADS FITTED	£150
GOULD OS400 10MHZ DIGITAL STORAGE	£195
GOULD DS2808 5MHZ 3 CHANNEL	£95
TEKTRONIX 7704/7A13/7A12/7B13/7B53A/N 4 CHANNEL	£500
TEKTRONIX 5103N/5101N/5A20N/5A20M OSCILLOSCOPE	£500

TEST EQUIPMENT

EPRATRON FRT ATOMIC FREQUENCY STANDARD	£2500
HP3770A PRIMARY MULTIPLEX ANALYSER	£600
HP3780A PATTERN GENERATOR/ERROR DETECTOR	£350
HP3762A DATA GENERATOR	£350
HP3488B DIGITAL MULTIMETER LCD	£400
HP3401C TRUE RMS VOLTMETER DIGITAL	£200
HP8750A STORAGE NORMALISER	£395
HP8405A VECTOR VOLTMETER & ACCESSORIES 1000MHZ	£650
HP3400A TRUE RMS VOLTMETER ANALOGUE	£145
HP3401C TRUE RMS VOLTMETER DIGITAL	£200
HP3406A BROADBAND SAMPLING VOLTMETER	£225
HP11883A RANGE CALIBRATOR	£300
HP11447A DIGITAL MULTIMETER LED	£200
HP10529A LOGIC COMPARATOR	£85
HP394A VARIABLE ATTENUATOR 1GHZ TO 2GHZ	£85
HP374A DISTORTION METER OPT 1H5	£250
HP3488A SWITCH CONTROL UNIT	£125
HP5381A 225M-Z FREQUENCY COUNTER	£125
MARCONI 2300B MODULATION METER 1200MHZ	£300
MARCONI 2331A DISTORTION FACTOR METER	£200
MARCONI 2432 560MHZ FREQUENCY COUNTER	£150
MARCONI 2432A 560MHZ FREQUENCY COUNTER	£200
MARCONI 2404 ELECTRONIC VOLTMETER 1500MHZ	£45
MARCONI 2405 RF MILLIVOLT METER 1500MHZ	£95
MARCONI 2910A TV LINEAR DISTORTION ANALYSER	£600
MARCONI 2911 TEST LINE GENERATOR 4 INSERTOR	£400
MARCONI 2911A INSERTION SIGNAL GENERATOR	£600
MARCONI 2106 PROGRAMMABLE INTERFACE UNIT	£450
MARCONI 2700 LCR BRIDGE BATTERY	prices from £95
FARNELL AB103035 ELECTRONIC LOAD	£495
FARNELL TOP30 TRIPLE OUTPUT DIGITAL PSU	£95
FARNELL L50 500ma POWER SUPPLY	£95
FARNELL B30/5 POWER SUPPLY 0.30 VOLT 5 AMP	£45
FARNELL B30/20 POWER SUPPLY 0.30 VOLT 20 AMP	£100
FARNELL LA510 RF AMPLIFIER 1.5MHZ TO 520MHZ	£155
FARNELL TMB TRUE RMS SAMPLING RF METER (AS NEW) 1 GHZ	£150
FLUKE 3310B PROG CONSTANT CURRENT/VOLTAGE CALIBRATOR	£750
FLUKE 103A FREQUENCY COMPARATOR	£295
ROTCH AC/DC PRECISION CALIBRATOR	£650
EXACT 334 PRECISION CURRENT CALIBRATOR	£195
BALLANTINE 6125C PROG TIME/AMPLITUDE TESTSET	£600
HALLYON 500B/51A URINAL TEST SYSTEM	£500
AVO RM15 L2 A/C DC BREAKDOWN/IONISATION TESTER	£300

AILTECH 533K-11 CALIBRATOR 1HP3550A HP3550 ATTENUATORS

100' TEN LINE 120W 60B ATTENUATORS (NEW)	£400
BIRD TERMINALINE B18 80W COAXIAL RESISTOR	£100
NARDA 769/8 150W 60B ATTENUATORS	£45
NARDA 3001-3D DIRECTIONAL COUPLER 460MHZ TO 950MHZ	£180
NARDA 10221 B DIRECTIONAL COUPLER 1GHZ TO 4GHZ	£215
KEMO D P1 PHASE METER 1HZ TO 100KHZ (NEW)	£150
IWATSUI SC7104 10KHZ TO 1000MHZ FREQUENCY COUNTER	£225
RACAL 9919 10HZ TO 1100MHZ FREQUENCY COUNTER	£300
RACAL 9903 50MHZ TIMER COUNTER	£95
RACAL 9904M 50MHZ TIMER COUNTER	£145
RACAL 9915 10HZ TO 520MHZ FREQUENCY COUNTER	£150
RACAL DANA 1998 10-HZ TO 1300MHZ FREQ/TIMER COUNTER	£500
RACAL DANA 9000 520MHZ MICROPROCESSING TIMER COUNTER	£250
RACAL DANA 6000 MICROPROCESSING DVM	£300
RACAL DANA 5082 WIDEBAND LEVEL METER	£700
RACAL DANA 9303 TRUE RMS RF LEVEL METER	£700
RACAL DANA 9304 TRUE RMS SIBUS ANALYSER	£200
RACAL DANA 9302 RF MILLIVOLT METER 10KHZ TO 1500MHZ	£400
RACAL DANA 1002 THERMAL PRINTER	£150
RACAL 9063 TWO TONE GENERATOR SYNTHESIZED	£250
WAYNE KERR CT496 LCR BRIDGE BATTERY PORTABLE	£95
PHILIPS PM8252A DUAL PEN RECORDER	£295
DIAR 2085 AF POWER METER	£300
TEKTRONIX SERA VIDEO WAVEFORM MONITOR	£300
TEKTRONIX 574 CURVE TRACER/72 PROG TEST FIXTURE	£650
TEKTRONIX 33B LOGIC ANALYSER 31 CHANNEL 20MHZ	£400
TEKTRONIX 31B LOGIC ANALYSER 16 CHANNEL 50MHZ	£450
SIEMENS U23233 PSCM/CM TESTER	£500
SIEMENS D3108 LEVEL METER 200HZ TO 30MHZ	£650
SIEMENS W3108 LEVEL OSCILLATOR 30MHZ	£650
WANDEL & GOLTERMAN SPM 19 LEVEL METER 50HZ TO 25MHZ	£650
WANDEL & GOLTERMAN P55 19 LEVEL GENERATOR 25MHZ	£650
SAYROSA AWM AUTOMATIC MODULATION METER 2GHZ	£200
BRUEL & KJOER 2425 ELECTRONIC VOLTMETER 0.5HZ TO 500KHZ	£195
DRANETZ 42AA MAINS DISTURBANCE ANALYSER FITTED WITH 60/36 INTERFACE 2402A dc monitor/6001 line analyser/6006 ac monitor/6020 broadband rf monitor	£1250
SCHLUMBERGER 7702 DIGITAL TRANSMISSION ANALYSER	£1250
MARCONI 6951A/610 POWER METER 10MHZ TO 20GHZ	£850
MARCONI 6951A VSWR INDICATOR	£495
HP432A/478A RF POWER METER 10KHZ TO 10GHZ	£400
HP435A/481A RF POWER METER 10KHZ TO 43GHZ	£650
HP435B/482B RF POWER METER 10KHZ TO 2GHZ	£850
HP435B/481A RF POWER METER 10KHZ TO 18GHZ	£1000
HP436A DIGITAL POWER METER	£650
HP844D AMPLIFIER 0.1MHZ TO 1300MHZ	£500
HP432A CRYSTAL DETECTOR	£150
SCD RF AMPLIFIER 10MHZ TO 1000MHZ 10 WATT 46dB	£1000
BIRD COAXIAL ATTENUATOR 500W 30dB	£300

BULK PURCHASE SPECIALS

BECKMAN DM110 DIGITAL MULTIMETERS WITH CASE/PROBES	£50
AVO 8 MKV MULTIMETERS	£40
BIRD 43 THRU LINE WATT METERS	£75
SIEMENS PDRM2 PORTABLE LCD RADIATION METER (NEW)	£45
EX GERMAN ARMY PORTABLE RADIATION METERS	£35

ALL PRICES PLUS VAT AND CARRIAGE. ALL EQUIPMENT SUPPLIED WITH 30 DAYS WARRANTY

86 Bishopgate Street, Leeds LS1 4BB

Tel: (0532) 435649 Fax: (0532) 426881

HEWLETT PACKARD Spectrum Analysers



HP 141T / 8555A 10 MHz to 18 GHz System

Complete with 8552B IF Section

High Sensitivity to -125 dBm

Resolve to 100 Hz

Scan up to 8 GHz full screen

£1700.00

HP 141T / 8554B 100 KHz to 1250 MHz System

Complete with 8552B IF Section

High Sensitivity to -122 dBm

Resolve to 100 Hz

£1000.00

With the purchase of any of the above systems we will supply FREE of charge one HP 8553B 1 kHz to 110 MHz RF section. Normal retail price of £350.00.

All systems covered by 30 day warranty


All prices plus Vat and carriage



M & B RADIO (LEEDS)

86 Bishopgate Street, Leeds LS1 4BB

Tel: (0532) 435649 Fax: (0532) 426881

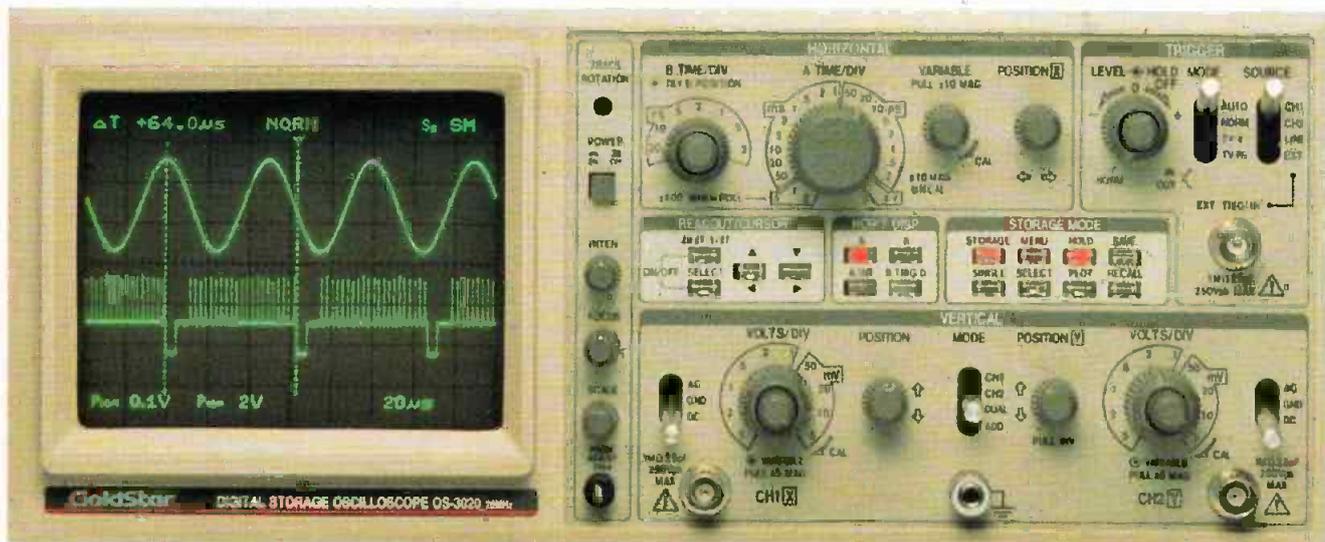

Model OS-3020 illustrated above

Star Quality, Reliability, and World Class Performance

from only **£269.95**

NEW Maplin Electronics are pleased to announce their superb new range of precision, laboratory grade Oscilloscopes from Goldstar.

NEW The range starts with the super value-for-money, 20MHz Dual-trace Oscilloscope, OS-9020A. Features include a large 6in., high luminance CRT with internal 8 x 10cm graticule, TV field or line triggering and X-Y mode producing Lissajous patterns for phase shift measurements.

NEW For higher frequency applications, the 40MHz Dual-trace Oscilloscope, OS-9040D, is ideal for TV and video signals and a trigger delay facility allows observation of fast leading edges.

NEW For RF signals and high-speed logic applications, the highly specified 100MHz triple-trace Oscilloscope, OS-9100D, has 3 independent input channels and is ideal for simultaneous display of 3 logic pulse trains for timing comparison.

NEW The dual-trace, 40MHz Oscilloscope, OS-904RD, is similar in specification to OS-9040D, but with the additional facility of a digital readout on the CRT. The readout displays information such as timebase and attenuator settings, and on-screen measurements can be performed using movable cursors, the value appearing on the CRT screen.

NEW Top-of-the-range is the excellent 20MHz Digital Storage Oscilloscope, OS-3020, with on-screen digital readout and measurement facilities. The digital storage function enables one-off events to be captured and stored for detailed analysis. Stored waveforms can be printed out on a suitable X-Y plotter via the built-in RS232 interface. Repetitive high-speed waveforms up to 20MHz can be digitised using equivalent sampling techniques and pre-trigger mode allows events occurring before the triggering point to be captured.

All models are supplied complete with probes, mains lead, spare fuses and detailed operating manual. Full details and specifications can be found in the 1994 **Maplin Full Colour Catalogue**, available from **WHSMITH** and selected branches of **RSMcColl** in Scotland for £2.95 (£3.45 by post direct from Maplin). To order, Phone the Credit Card Hotline, 0702 554161, or send your Mail Order to P O Box 3, Rayleigh, SS6 2BR, or visit your local Maplin store. Please note latest models all now cream in colour as Model OS-3020.

Maplin ELECTRONICS. UK AGENTS FOR **GoldStar**

Visit our stores in: **Birmingham, Brighton, Bristol, Cardiff, Chatham, Coventry, Dudley, Edinburgh, Glasgow, Ilford, Leeds, Leicester, London (Edgware, Forest Hill and Hammersmith), Manchester (Oxford Road and Cheetham Hill), Middlesbrough, Newcastle-upon-Tyne (The Metro Centre, Gateshead), Nottingham, Portsmouth, Reading, Sheffield, Slough, Southampton, Southend-on-Sea, Stockport, Milton Keynes** plus new stores opening soon. Phone 0702 552911 for further details.

All items subject to availability, prices include VAT and are subject to change. Carriage charge per order £5.70. Handling charge £1.40 per order. Overseas customers please phone 0702 552911.




OS-9020A GW03D £269.95




OS-9040D GW04E £399.95



OS-904RD GW06G £499.95

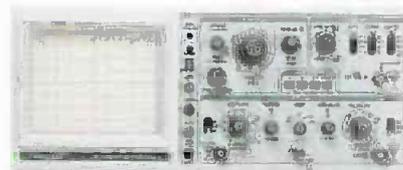

OS-9100D GW05F £699.95

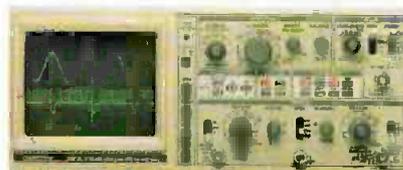

OS-3020 GW07H £749.95

GoldStar
Technology with the human touch

WHETHER ELECTRONICS IS YOUR HOBBY OR YOUR LIVELIHOOD . . . YOU NEED THE MODERN ELECTRONICS MANUAL

ORDER NOW
and get a
FREE SUPPLEMENT
plus our
30 DAY MONEY BACK GUARANTEE



The essential reference Work

- Easy-to-use format
- Clear and simple layout
- Regular Supplements
- Sturdy ring-binder
- News of latest developments
- Full components checklist
- Extensive data tables
- Detailed supply information
- Ready-to-transfer PCBs
- Comprehensive subject range
- Detailed assembly instructions
- Professionally written

EVERYTHING YOU NEED TO KNOW ABOUT ELECTRONICS!

If the fascinating and fast-changing world of electronics is your livelihood, your study subject or simply your passion, the revised edition of **THE MODERN ELECTRONICS MANUAL** is the reference work for you to have at your side.

The Base Manual contains information on the following subjects:

BASIC PRINCIPLES: Symbols, components and their characteristics, passive component circuits, power supplies, acoustics and electroacoustics, the workshop, principles of metrology, measuring instruments, digital electronics, operational amplifiers, timers, physics for electronics.

CIRCUITS TO BUILD: Construction techniques, radio, telephony, microcomputing, measuring instruments, vehicle electronics, security, audio, power supplies, electronic music (over 25 different projects).

REPAIRS AND MAINTENANCE: Basic circuit operation for radio, television, audio/hi-fi, telephones.

DATA: Diodes, transistors, thyristors and triacs, digital and linear i.c.s, microprocessors.

The Manual also covers **Safety, Specialist Vocabulary with Abbreviations** and **Suppliers**.

OVER 1,000 pages, with over 900 diagrams and photographs, A4 looseleaf format weighing over 3.5kg.

ALL-IN-ONE AND EASY-TO-USE: A sturdy ring-binder allows you to use the Manual on your workbench. The looseleaf format also means you can slot in the regular supplements as they arrive – so all your information is there at a glance.

EXTENSIVE GLOSSARY: Should you come across a technical word, phrase or abbreviation you're not familiar with – simply turn to the glossary included in the Manual and you'll find a comprehensive definition in plain English.

GUARANTEE

Our 30 day money back guarantee gives you **complete peace of mind**. If you are not entirely happy with the Manual, for whatever reason, simply return it to us in good condition within 30 days and we will make a **full refund of your payment** – no small print and no questions asked. (Overseas buyers do have to pay the overseas postage charge).

Now – at last – the most comprehensive reference work ever produced at a price you can afford, the revised edition of **THE MODERN ELECTRONICS MANUAL** provides you with **all the essential information you need**.

Over 1,000 pages of well-organised and clearly explained information is brought to you by an expert editorial team whose combined experience ensures the widest coverage.

Regular supplements to this unique publication, each around 160 pages, mean that you will always be kept abreast of the latest developments from around the world as they occur

REGULAR SUPPLEMENTS

Unlike a book or encyclopedia, the Manual is a living work – continuously extended with new material. Recent or upcoming supplements include radio, superconductors, electric motors, basic electronic building blocks for beginners which can be joined together to construct elaborate circuits, filters, IBM PC and compatibles (including updating/expanding PCs). Supplements are sent to you approximately every two months. Each supplement contains approximately 160 pages – all for only £23.50 + £2.50 p&p. You can of course return any supplement (within 10 days) which you feel is superfluous to your needs.

RESPONDING TO YOUR NEEDS

We are able to provide you with the most important and popular, up to the minute, articles in our supplements. Our unique system is based on readers


requests for new information. Through this service you are able to let us know exactly what information you require in your Manual. You can also contact the editor directly in writing if you have a specific technical request or query relating to the Manual.

ASSEMBLING

There's nothing to beat the satisfaction of creating your own project. From basic principles to circuit-building, the Manual describes clearly, with appropriate diagrams, how to assemble radios, loudspeakers, amplifiers, car projects, measuring instruments etc. The revised edition of The Modern Electronics Manual contains practical, easy-to-follow instructions for building a wide range of projects. It shows you how to make fun gadgets such as a remote control door opener and a digital rev. counter for your car. It also tells you how to construct useful devices like test gear, security and

baby alarms – plus – many more popular devices.

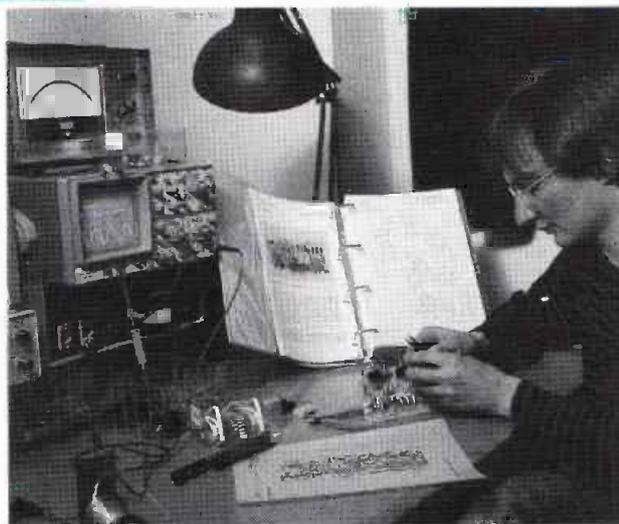**Wimborne Publishing Ltd.,
6 Church St, Wimborne,
Dorset BH21 1JH
Tel: 0202 881749 Fax: 0202 841692**



THE MODERN ELECTRONICS MANUAL

Revised Edition of Basic Work: Now contains over 1,000 pages of information.

Regular Updates: Approximately 160-page supplements of additional information which are forwarded to you immediately on publication. These are billed separately and can be discontinued at any time.

Presentation: Durable looseleaf system in large A4 format (297mm × 210mm)

Price of the Basic Work: £39.95 + £5.50 p&p (to include a recent supplement free).

PLEASE send me **THE MODERN ELECTRONICS MANUAL** plus a **FREE SUPPLEMENT**. I enclose payment of **£45.45** (£39.95 plus £5.50 postage and packing). Should I decide **not** to keep the Manual I will return it to you in good condition within 30 days for a full refund of this payment. I shall also receive the appropriate supplements several times a year. These are billed separately and can be discontinued at any time.

FULL NAME
(PLEASE PRINT)

ADDRESS

.....

..... **POSTCODE**

SIGNATURE

I enclose cheque/PO payable to Wimborne Publishing Ltd.

Please charge my Visa/Mastercard/Access

Card No. **Card Ex. Date**

Aug 1 2 3

ORDER FORM

Simply complete and return the order form with your payment to the following address:

**Wimborne Publishing Ltd, 6 Church Street
Wimborne Dorset BH21 1JH**

**We offer a 30 day MONEY BACK
GUARANTEE – if you are not happy with
the Manual simply return it to us in good
condition within 30 days for a full refund.**

Overseas buyers do have to pay the overseas postage – see below.

OVERSEAS ORDERS: All overseas orders **must be prepaid** and are supplied under a money-back guarantee of satisfaction. If you are not entirely happy with the Manual return it within a month for a refund of the purchase price (you do have to pay the overseas postage). **SEND £39.95 PLUS THE POSTAGE SHOWN BELOW:**

EIRE	AIR MAIL ONLY £11
EUROPE (E.E.C. Countries)	AIR MAIL ONLY £20
EUROPE (non E.E.C.)	SURFACE MAIL £20, AIR MAIL £26
U.S.A. & CANADA	SURFACE MAIL £25, AIR MAIL £32
FAR EAST & AUSTRALIA	SURFACE MAIL £31, AIR MAIL £33
REST OF WORLD	SURFACE MAIL £25, AIR MAIL £44

Note surface mail can take over 10 weeks to some parts of the world. Each manual weighs about 4.5kg including the free supplement when packed.

All payments must be made in £'s Sterling payable to Wimborne Publishing Ltd. We accept Mastercard (Access) and Visa credit cards.