

ETI

ELECTRONICS TODAY INTERNATIONAL

TOMORROW'S TECHNOLOGY TODAY

**Build a versatile
digital message
display**

**Fibre optic MIDI
link for music
without
interference**

**Introducing the
ETI ultra low
cost BASIC
programmable
micro computer**

Plus

- 8088 interrupt based control computer
- Dry battery tester
- Using the Stamp microcomputer
- Practical approach to the PIC

5 Ariane



**The
technology
behind
Europe's new
space
launch
system**

SEPTEMBER 1995 £2.15



NEXUS

"moving from schematic to layout could not be easier"



Electronics World & Wireless World Jan 1995

**PRO+ now
with SPICE
file export
& SpiceAge
DDE link!**

Quickroute 3.0 for Windows 3.1 has been designed from the start to be as easy to use as possible, without sacrificing the power professional engineers need to get the job done. Quickroute is available with schematic capture, support for busses & power rails, 1-8 layer auto-routing, SPICE file export, and our new extended library pack. Quickroute 3.0 PRO+ can also connect to the Windows simulation package SpiceAge using Windows DDE. Contact POWERware for more details!

Quickroute 3.0

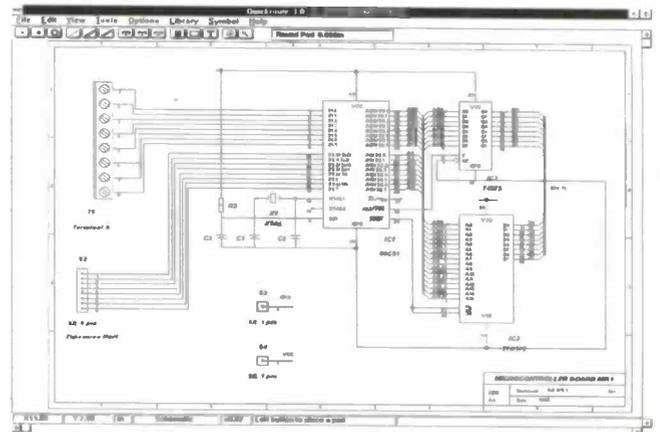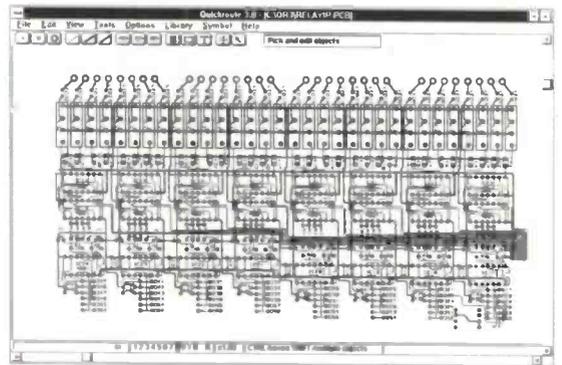**Integrated Schematic and PCB
Design for Windows 3.1**



**Busses and Power rails handled easily
using Global Nets on PRO+**

DESIGNER £99

*Schematic & PCB Drawing *1/2 layer auto-router
*Supports Windows printers/plotters *Full set of
libraries *Clipboard support *Designer Special (manual
on disk) also available.

PRO £199

*Schematic & PCB Design *Schematic Capture
*Integrated Rats-Nest Generation *1-8 layer Auto-router
(faster than Designer) *Net-List Export *Supports
Windows printers/plotters *CAD-CAM outputs.

PRO+ £299


As the PRO but also includes *Advanced Schematic Capture
(Busses, Power rails, etc) *Larger Schematic & PCB Designs
*Gerber file IMPORT for File Exchange *Extended libraries
(CMOS, SMT, etc) *SPICE Export *SpiceAge DDE link.

**Prices exclude P+P and V.A.T. VISA/MasterCard
Accepted *Network versions available.*

**POWERware, 14 Ley Lane, Marple
Bridge, Stockport, SK6 5DD, U.K.**

Tel/Fax 0161 449 7101

email info@powrware.demon.co.uk

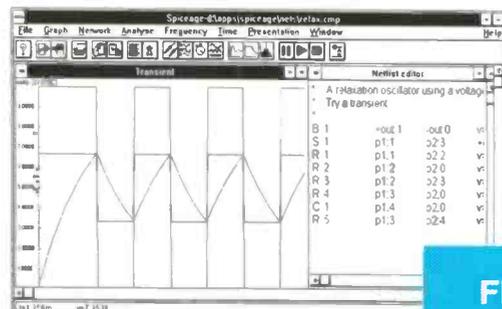

**DDE link to SpiceAge
Simulator with PRO+**

**FREE
Demo Pack
Available.**

Contents



Volume 24 No.9

& Features Projects

The Ariane 5 12

In October, the European Space Agency are due to launch the first of a new generation of highly reliable, and high lift capacity rockets. Douglas Clarkeson takes a look at this European designed and built space launch system which will make it possible to put very large payloads into space, as well as providing a potential European manned launch system

Dry battery tester 20

Save waste and money and extend the life of dry batteries with this battery tester, designed by Stephen Lenham

The ETI Basic microcontroller 24

An introduction to ETI's new premier project for the autumn

Hello Mum 32

This project by Bob Noyes is a versatile, but simple, electronic message board system which will find a wide range of uses



Fibre optic MIDI link 40

Robert Penfold shows how to build a low noise communications link between MIDI electronic music devices

Stamp Duty 44

Roland Oliver describes how he used the Parallax Stamp to build a serial relay controller that could be attached to a PC

Designing a PIC microcontroller based project 50

In Part 3 of this short tutorial series, Bart Trepak looks at the circuit and design of a PIC based alarm clock

8088 Interrupt based single board control computer 56

In part two of this computer project designed by R.Grodzik, he continues his look at designing and building the 8088 processor based board and examines the software which makes it particularly suitable for multitasking control applications

Regulars

- News and event diary 7
- Practically speaking 66
- PCB Foils 69
- Open Forum 74





Subscribe & Save


SUBSCRIPTIONS & BACK ISSUES HOTLINES:
01858 435344

ORDERS:
ENQUIRES:
01858 435322
Lines Open 9am - 6.30pm

Phone the hotline and take advantage of our special offer detailed on page 65

Pico Releases PC Potential

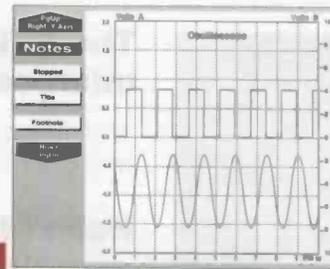Pico's Virtual Instrumentation enable you to use your computer as a variety of useful test and measurement instruments or as an advanced data logger.




PicoScope
'Virtual instrument' software.

Hardware and software are supplied together as a package - no more worries about incompatibility or complex set-up procedures. Unlike traditional 'plug in' data acquisition cards, they simply plug into the PC's parallel or serial port, making them ideal for use with portable PC's.

Call for your Guide on 'Virtual Instrumentation'.

PicoLog
Advanced data logging software.

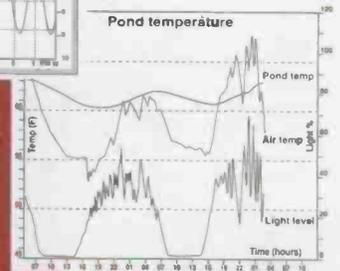

NEW from Pico TC-08 Thermocouple to PC Converter 8 channel Thermocouple Interface

- Connects to your serial port - no power supply required.
- Supplied with PicoLog datalogging software for advanced temperature processing, min/max detection and alarm.
- 8 Thermocouple inputs (B,E,J,K,N,R,S and T types)
- Resolution and accuracy dependant on thermocouple type. For type K the resolution is better than 0.1°C.

TC-08 £ 199

TC-08 + Calibration Certificate £ 224

complete with PicoLog, software drivers and connecting cable. A range of thermocouple probes is available.



SLA-16 & SLA-32 Logic Analysers

Pocket sized 16/32 channel Logic Analysers

- Connects to PC serial port.
- Up to 50MHz sampling.
- Internal and external clock modes.
- 8K Trace Buffer.



SLA-16 £ 219
SLA-32 £ 349
with software, power supply and cables



ADC-100 Virtual Instrument

Dual Channel 12 bit resolution

- Digital Storage Scope
- Spectrum Analyser
- Frequency Meter
- Chart Recorder
- Data Logger
- Voltmeter

The ADC-100 offers both a high sampling rate (100kHz) and a high resolution. It is ideal as a general purpose test instrument either in the lab or in the field. Flexible input ranges ($\pm 200\text{mV}$ to $\pm 20\text{V}$) allows the unit to connect directly to a wide variety of signals.

ADC-100 with PicoScope £199
with PicoScope & PicoLog £219

ADC-10 1 Channel 8 bit

- Lowest cost in the Pico range
- Up to 22kHz sampling
- 0 -5V input range



The ADC-10 gives your computer a single channel of analog input. Simply plug into the parallel port.

ADC-10 with PicoScope £49
PicoScope & PicoLog £59

Carriage UK free, Overseas £9 Oscilloscope Probes (x1, x10) £10

PICO TECHNOLOGY



Pico Technology Ltd. Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ
Tel: (0)1954 - 211716 Fax: (0)1954 - 211880 E-mail: 100073.2365 @compuserve.com




Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT



A mini FM transmitter, very high gain preamp, supplied complete with FET electret microphone. Designed to cover 88-108 Mhz but it is easy to change it to cover 63-130Mhz Works with a common 9v (PP3) battery. 0.2W RF. £8.22 Kit no 1001.



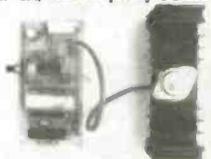Electronic siren kit with an impressive 5 watt power output. Ideal for car/bike alarms etc. 6-12vdc, max current 1A, tone frequency 1.2khz. £7.05 Kit no 1003.



3-30v Power supply, variable, stabilized power supply for laboratory use. Shortcircuit protected, suitable for professional or amateur applications. 24v 3A transformer is also needed to complete the kit. £16.45 Kit 1007.




Powerful 1 watt FM transmitter supplied complete with piezoelectric microphone. 8-30vdc. At 25-30v you will get nearly 2 watts! £14.10 Kit no 1009.



FM/AM Scanner, well not quite you have to turn the knob yourself but you will hear things on this radio (even TV) that you would not hear on an ordinary radio! Receiver covers 50-160Mhz both AM and FM. Built in 5 watt amplifier. £17.62 Kit no 1013.



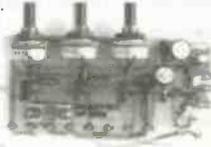Mosquito repeller, modern way to keep midges at bay! Runs for about a month on a 1.5v battery. £8.22 Kit no 1015.



3 channel wireless sound to light system, mains operated, separate sensitivity adjustment for each channel, 1,200 watt power handling. Microphone included. £16.45 Kit no 1014.



Motorbike/cycle trembler alarm, adjustable sensitivity, preset alarm time, auto reset. Could be connected to bikes horn etc. £14.10 Kit no 1011



0-5 minute timer, adjustable from 0 to 5 mins, will switch up to 2A mains. Perfect for alarms, photographic laboratories etc. 12vdc. £8.22 Kit no 1020.



4 watt FM transmitter, small but powerful transmitter, 3 RF stages, microphone and an audio preamp include in kit. £23.50 Kit no 1028.




25 watt FM transmitter 4 RF stages, preamp required (our kit 1068 is suitable). Due to the complexity of the transmitter it is supplied in built up form only. £92.82 Kit no 1031.



Strobe light, adjustable frequency from 1- to 60 Hz (a lot faster than conventional strobes) mains operated. £18.80 Kit no 1037.



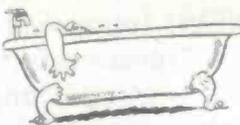Ultrasonic radar ideal as a movement detector with a range of about 10 metres, automate your cat flap! 12v operation so ideal for cars, caravans etc. £16.45 Kit 1049.




Liquid level detector useful for detecting fluid levels in tanks, fishponds, bathtubs as a rain or leak alarm. Will switch 2A mains. £5.37 Kit no 1081.



Combination lock 9 key, easily programmable, will switch 2A mains. Complete with keypad. 9v operation. £11.75 Kit 1114.



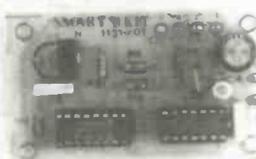Phone bug detector, this device will warn you if somebody is eavesdropping on your phone line. £7.05 Kit no 1130.



Robot voice, interesting circuit that distorts your voice! adjustable, answer the phone with a different voice! 12vdc £10.57 Kit no 1131.



Telephone bug, small bug powered by the telephone line, starts transmitting as soon as the handset is picked up! £9.40 Kit no 1135.



function generator, produces sine, square, sawtooth and square waves adjustable from 20hz-20khz, separate level controls for each shape. Will produce all 3 together. 24vac £17.62 Kit no 1008.



3 Channel light chaser, 800 watts per channel, speed and direction controls supplied with 12 leds and mains triacs, so you can use mains light bulbs if you want. 9-15vdc £19.97 Kit no 1026.




12v fluorescent. A useful kit that will enable you to light 4' fluorescent tubes from your car battery! (you will also need a 9v 2A transformer, not supplied) £9.40 Kit no 1069.




VOX switch, sound activated switch ideal for turning tape recorders on and off when sounds are heard. Makes the tape last a lot longer! Adjustable sensitivity, built in delay. £9.40 Kit 1073.



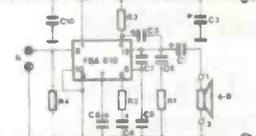Incar sound to light, Put some atmosphere in your car with this mini 3 channel sound to light. Each channel has 6 led's. £11.75 Kit no 1086.



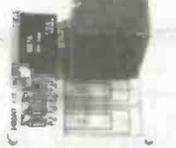7 watt HI FI power amplifier useful, powerful, ideal for intercomms, audio systems, car use etc. 12-18vdc 500mA. £8.22 Kit No 1025.



Phone call relay, useful device that operates a relay when ever the 'phone rings, could be used to operate more bells or signalling lights etc. Will switch mains at 2A. £11.75 Kit no 1122.



Lead acid charger, two automatic charging rates, visual indication of battery state, ideal for alarm systems, emergency lighting etc. 100mA 12vdc. £14.10 Kit no 1095.



Car alarm system, works on voltage drop and/or vibration, entry and exit delays plus adjustable alarm duration. Good for cars, caravans etc. £14.10 Kit no 1019.



Portable alarm system, based on a mercury switch. The alarm continues to sound until the unit is disabled by the owner. Buzzer included. £12.92 Kit no 1150.



Preamp mixer, 3 Input mono mixer, separate bass and treble controls plus independent level controls. 18vdc, input sens 150mv. 100mA. £17.62 Kit no 1052.

Mini metal detector, suitable for locating pipes in walls etc, range 15-20 cm, complete with case. 9v operation. £9.40 Kit no 1022.



800 watt single channel sound to light kit, mains operated, add rhythm to your party for only £9.40 Kit no 1006.



Sound effects generator, produce sounds ranging from bird chirps to sirens, complete with speaker, add sound effects to your projects for just £10.57 Kit no 1045.



Guitar preamp with tone controls, small enough to fit inside any guitar, based on TL082 IC, 9-12vdc, 50mA. £9.40 Kit no 1091.



15 watt FM transmitter, 4 stage high power, preamp required. 12-18vdc. Can use either ground plane, open dipole, or Yagi. Supplied in built form only at £81.07 Kit 1021.



Telephone amplifier, Very sensitive amplifier which uses a 'phone pickup coil (supplied) will let you follow a conversation without holding the phone. £12.92 Kit no 1059.

TOP 10 BEST SELLING KITS CORNER

1. Variable speed control kit for 12v DC motors up to 30A! (you may need a heat sink for 30A) £19.97.
2. Composite video kit, converts composite signals into separate H sync, V sync and video £9.40.
3. Geiger counter kit, contains everything you need to build a working counter £22.32.
4. Solar energy kit, contains a solar panel, motor, buzzer and cable for experiments £5.87.
5. Electronic acupuncture kit, may help with migraine, poor circulation, backache etc. £8.22.
6. Electrifying apparatus kit, produces a weak adjustable high tension of 80-300v from a 9v battery, ideal for catching worms etc! £9.40.
7. A adapter bug kit, contains everything you need to build a professional bug built inside a standard 13A mains adapter! the bug is mains powered so it operates all the time the adapter is plugged in. Price is £16.45 for the complete kit including adapter. Hand tools and glue required.
8. Nicad charger kit automatic charger for cells from 1.2v to 15v, 7 setting x 50600mA, transformer required 18-20v 600mA. £9.40.
- 9&10. Inverter kits, produce 240vac from a 12vdc supply, two versions are available a 15w one at £14.10, and an 80w version at £23.50.

EXPRESS COMPONENTS

how to order.....
Remember to add £1.50 p&p.
By phone with a credit card.
By post with either a cheque, postal order or credit card details.
By fax with credit card details.
EXPRESS COMPONENTS, PO BOX 517 HOVE SUSSEX BN3 5QZ. DEPT ETI
TEL 01273 771156
FAX 01273 206875
Overseas orders please add £3.50 post and packing.

R.F Modem Transceiver



UK MPT1340
418MHz or
433.93MHz

- ✓ High speed up to 40K bps
- ✓ Price 100+ < £30.00 1+ £49.95
- ✓ Ideal for Radio Modems & EPOS

R.F Modem Packet Controller



TX/RX C.R.C
Only £79.95
4-bit I/O port

- ✓ Parallel microprocessor interface
- ✓ Automatic tx/rx protocol & CRC
- ✓ PIC micro with user E²PROM

Radio - Tech Radio - Tech Limited
LOW POWER RF TELEMETRY MANUFACTURERS

Overbridge House, Weald Hall Lane, Thornwood, Epping, Essex. CM16 6NB
Sales 0181-368 8277 Fax 0181-361 3434, Admin 01992-576107 Fax 01992-561994

Radio Data Modules

- ✓ Approved Transmitter Modules
- ✓ Receiver Modules & Systems
- ✓ Transceiver Modules
- ✓ Evaluation Kits Available
- ✓ 173MHz, 418MHz & 433.92MHz
- ✓ Free Catalogue & Support
- ✓ Credit Card Orders  
- ✓ Same Day Dispatch



Applications:
Remote Controls
Wire-free Security
Remote Monitoring
RF Computer links

NEW! Transceiver evaluation kit. Includes:
2 x Transceivers, test PCB with PIC micro,
bit error rate, range & self test firmware
batteries, antenna and carry case. £149.00

Radio - Tech Radio - Tech Limited
DISTRIBUTOR OF RADIOMETRIX PRODUCTS

Overbridge House, Weald Hall Lane, Thornwood, Epping, Essex. CM16 6NB
Sales 0181-368 8277 Fax 0181-361 3434, Admin 01992-576107 Fax 01992-561994

R.F Linked Safety Aids

- ✓ Approved off the shelf systems
- ✓ Aids for the disabled and elderly



Fall-over Triggers
 μ Power Receivers
Auto-diallers, Sirens
FM Pagers
Repeater Stations

- ✓ High quality lone worker systems
- ✓ Hand held FM remote controls
- ✓ Battery operated FM receivers



Relay Outputs!
Built-in Antennas

Applications for tenders welcome from Local
Authorities, Retail Trade and Heavy Industry.
Prices start from under £30.00 ex VAT & Carriage.

Radio - Tech Radio - Tech Limited
LOW POWER RF TELEMETRY MANUFACTURERS

Overbridge House, Weald Hall Lane, Thornwood, Epping, Essex. CM16 6NB
Sales 0181-368 8277 Fax 0181-361 3434, Admin 01992-576107 Fax 01992-561994

10mW VHF Modules

- ✓ 173.225MHz Approved MPT1344
- ✓ 173.250MHz Approved MPT1328
- ✓ Remote Meter Reading Modules
- ✓ Evaluation Kits Available
- ✓ New low prices 1+ £25.45 ex.
- ✓ Compatible with existing RXM-173-4666-60 receiver.
- ✓ Pin compatible with 1mW version




Applications:
Industrial Controls
Wire-free Monitors
Remote Metering
RF Data links

Note: VHF @ 10mW ERP gives a typical
unobstructed TX range of up to 2.5Km.
MPT1344 should be used for security and
MPT1328 telemetry / telecommand applications.

Radio - Tech Radio - Tech Limited
DISTRIBUTOR OF RADIOMETRIX PRODUCTS

Overbridge House, Weald Hall Lane, Thornwood, Epping, Essex. CM16 6NB
Sales 0181-368 8277 Fax 0181-361 3434, Admin 01992-576107 Fax 01992-561994

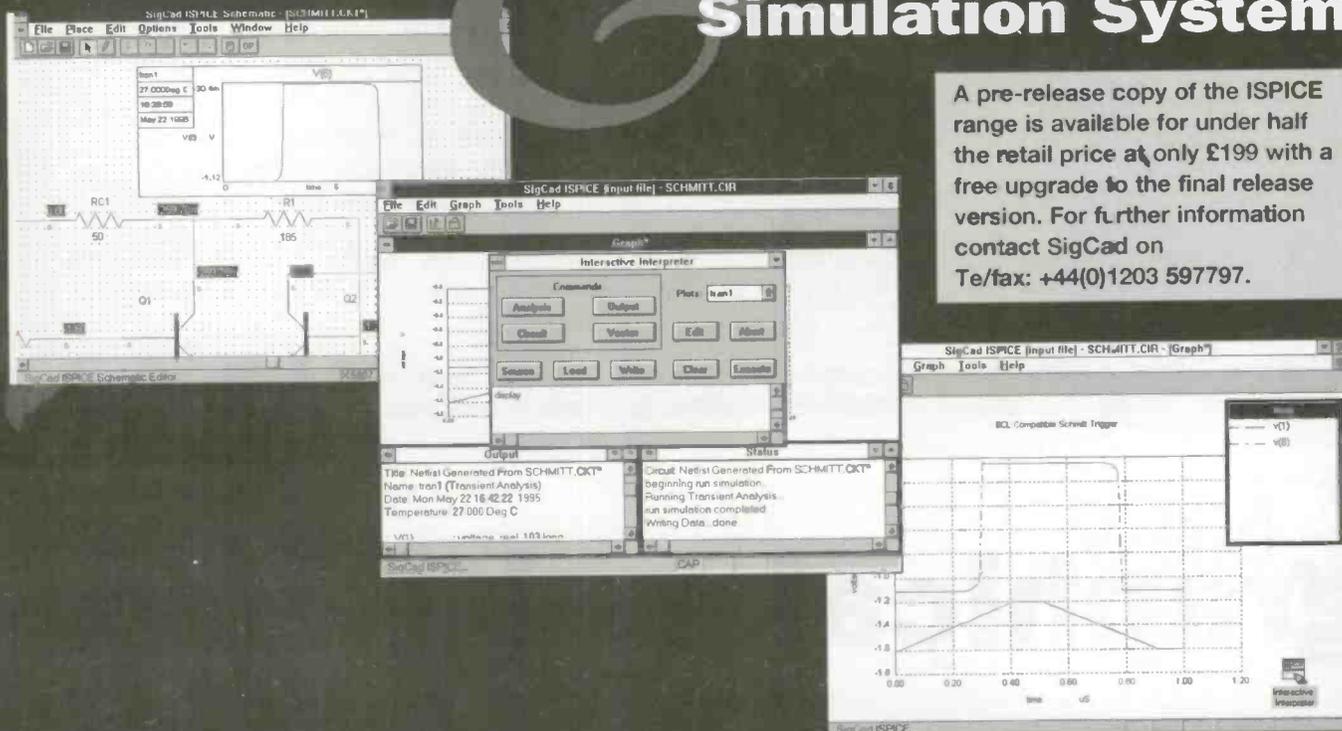New Windows Based Integrated Electronic Circuit Design Simulation System



A pre-release copy of the ISPIICE range is available for under half the retail price at only £199 with a free upgrade to the final release version. For further information contact SigCad on Te/fax: +44(0)1203 597797.

The New SigCad ISPIICE range of products provides unlimited analogue simulation capabilities in Windows for all levels of users. The logical design steps have been broken down into multiple modules allowing users to bypass certain steps easily. This allows seasoned professionals and novices to interface to ISPIICE at different levels.

ISPIICE is an integrated system composed of four modules, each providing different functions to ease difficulties encountered during circuit design and simulation. These are: ISPIICE Schematic Editor, SPICE Component Editor, ISPIICE Netlist Editor and ISPIICE (simulator and postprocessor)

SigCad ISPIICE is based on Berkeley SPICE 3F5 with a number of extensions and improvements. Unlike other SPICE3 simulators, ISPIICE has been interfaced with an advanced postprocessor so simulations and data analysis can be carried out in the same environment. Interactive communication with both the simulator and postprocessor is achieved via the Interactive Interpreter using its own command language.

SigCad has not limited the simulation capabilities of ISPIICE, which has 10 types of analyses, including AC, DC Transfer Curve, Transient, Noise, Distortion, Temperature, Sensitivity (AC and DC) etc. The built in models include 6 types of MOSFETs, 3 types of transmission lines (lossless/lossy), SPICE2 nonlinear dependent sources including the new arbitrary source (B element), MESFET model and all other standard SPICE primitives.

The ISPIICE Schematic Editor is designed to be an interactive front-end to ISPIICE that greatly eases the burden of creating a complete SPICE netlist directly from the schematic. Most components can be placed on the schematic with a single keystroke and automatic node numbering is done in real time. Simulations can be run from the Schematic Editor environment allowing waveforms to be interactively cross-probed on the schematic and circuit operating point voltages can be updated as component values are changed. This provides a powerful debugging tool for designers as they are constructing their circuit!

New symbols for user defined models can be created and loaded in by using the ISPIICE Component Editor. The ISPIICE Netlist Editor allows designers to either create netlists or edit those generated by the Schematic Editor. SPICE2-style output and simulator generated errors and warnings can also be viewed, together with the netlist, in the Netlist Editor's environment.

ISPIICE requires Windows 3.1 or higher on PC compatibles with 4MB of RAM. ISPIICE does not require a co-processor and circuit size is unlimited!

New low voltage **4 bit microcontroller**

NEC's new KPC753017 4-bit microcontroller has one of the most powerful LCD drive capabilities available on a product of this type. The device, which is part of the company's enhanced performance, low voltage 75XL range, has an integral 32 x 4 segment LCD driver enabling it to drive complex information displays.

75XL devices are enhanced performance versions of NEC's 75X range, currently the world's best-selling 4-bit microcontroller. They are particularly aimed at low cost applications which traditionally use more expensive 8-bit products, and the uPD753017 is particularly suitable for automotive electronics and industrial control. The devices also feature a powerful instruction set and a wide variety of on-chip peripherals.

The ultra-low power uPD753017 has guaranteed operation from 1.8V to 6.0V, the lower voltage enabling it to be driven from the 'load' voltage of two lithium cells. This allows the construction of systems that are lighter and more compact than ever before.



For further information contact NEC Electronics (UK) Ltd, 01908 691133

New **graphical multimeter**



The new 860 series of Graphical Multimeters provide the user with the means of viewing waveforms, graphs, in-situ component signatures, trend plotting and logic activity. They are also quality digital multimeters with all the functions you would expect from the world's leading source of Dmms.

B:Waveform Display mode provides a clear picture of noise, distortion, intermittent failures and glitches with either a fully automatic or manual set-up.

Trendgraph mode plots high resolution meter readings for up to 30 hours, in intervals from 1 second to 15 minutes, to detect such anomalies as power sags/surges and droops.

In-Circuit Component Test mode can view component signatures in-circuit. This allows for comparison of good/bad circuits and components.

Logic Activity mode offers a simple and effective method of isolating digital failures.

Meter mode is more traditional, offering both digital and analogue information of all parameters via a 32,000 count (4.5 digit) display and an analogue NeedleGraph.

The 860 Series of handheld graphical multimeters is readily available from all members of the Professional Instrument Distributors Association throughout the UK together with a full and competent back-up service.

For further information contact Quiswood Ltd
on 01756 799737.

SocketModems Evaluation Kit



For further details,
contact Telecom Design
Communications
Limited on
01256 332800.

Basingstoke based Rockwell distributor, Telecom Design Communications Limited, have announced a range of evaluation and development boards for Rockwell's 'Plug. and.Play' SocketModems.

The new boards are available with or without DAA's (Data Access Arrangement or Line Interface), either as PC-plug in cards, or as external serial types. The serial versions can be connected either directly as TTL level serial, or with full RS-232 drivers.

Rockwell SocketModems are available for their entire range of modem capabilities, from simple 2400 bps data-only devices, to high speed 14400 bps data/fax modems with voice facility, error correction, data compression and cellular compatibility. V.Fast class versions will be announced shortly. All SocketModems may be used with the evaluation boards, enabling designers to quickly configure a range of products for desktop or portable use.

Additionally, TDC provide a range of BABT recognised line interfaces suitable for use with Rockwell's SocketModems. Available as DIP and low-profile SIP versions, their certificate of recognition will aid the gaining of approvals for connection to the PSTN, greatly enhancing time to market. TDC also provide demonstration code for use with the boards further speeding up the design and modem integration process.


Best Selling Oscilloscope

The new Hameg HM 303 Oscilloscope is available from BK Electronics, priced at £392.00 plus VAT, which includes 2 switched probes and a manual. Carriage is free of charge.
Tel: 01702-527572 Fax:- 01702 420243.

The new Hameg HM303 standard Oscilloscope succeeds the HM203, which sold over 170,000 worldwide. The bandwidth has been extended to 30Mhz. A lighter weight of only 5.6Kgs and a lower panel height reduced by 20mm has been achieved by incorporating a switch mode power supply. Another advantage is that the new oscilloscope will work from a mains supply of between 90 and 240V AC, without adjustment.

Brief specification:

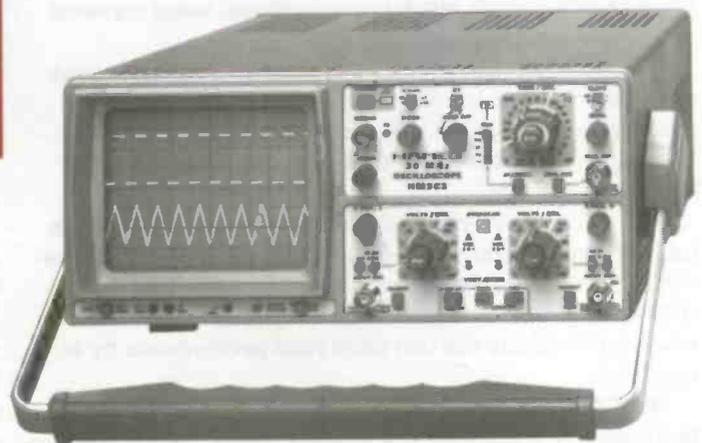Dual Channel, DC to 30Mhz 2mV/Div.; Overscan Indicator Time Base : 10nS to 0.5s/Div.: Variable holdoff: X10 Magnification Triggering : DC-1000Mhz Active TV-Sync-Separator : LED Trigger Indication Additional Features: Component Tester, 1Kv/1Mhz Calibrator



External printer port to RS232 card



For further
information contact
Brain Boxes on
0151 220 2500.

PC adapter card manufacturers Brain Boxes have now added a parallel printer port to their own extremely flexible dual Serial Port card.

The LPT parallel printer port is accessible from the 25 pin female connector. It may be set as LPT1 to LPT3 with Interrupts 5 or 7. Thus allowing users of OS/2, OS/2 Warp V3, Novell, and Unix full interrupt driven printer output. Full bi-directional capability is obtainable for scanners, file transfer etc.

Two Serial ports are included on the card, the first accessible externally using the standard 9 pin male D-connector, and the second using a serial cable to on-board headers. Each independent Serial Port may be jumper configured as COM 1 - COM8 with interrupt line jumpers set to IRQ 2-7,10-12,14-15.

A fully detailed installation guide showing jumper settings for DOS, Windows and OS/2 is included in the 41 page manual. Also included is a utility disk with sample programs, Test and Terminal software with source code. Maximum performance for Windows users can be obtained with the optional 16550 FIFO chip version. This provides a 16 bit input and 16 bit output hardware buffer for each serial port allowing high data rates without data loss or overrun errors.

Fast JEDEC compliant

2Mbit VRAM


NEC Electronics is sampling fully JEDEC-compliant 2Mbit video RAMs (VRAMs) with random access times of 60ns. JEDEC is a US-based standards body that defines the functionality and pin-outs for many semiconductor devices. Compliance means that users of the uPD482234 and uPD482235 products, such as PC manufacturers, will not be tied to a particular manufacturer and will have flexibility of supply.

A VRAM is essentially a DRAM with an extra I/O port, enabling a faster data transfer rate. They are used in desktop and portable PCs (particularly those running Windows-type applications), workstations, video cameras and video recorders.

The 2Mbit devices are organised as 256K x 8 bits, and are ideal for use in graphics applications. They are functionally compatible with previously released 2Mbit VRAMs but offer the advantage of faster serial access times down to 18ns.

The 2Mbit VRAM is available in two operational modes, both with random access performance down to 60ns. The HPD482234 is a fast page mode device, while the HPD482235 is an extended output fast page mode device which can improve the fast page read performance by at least 20%.

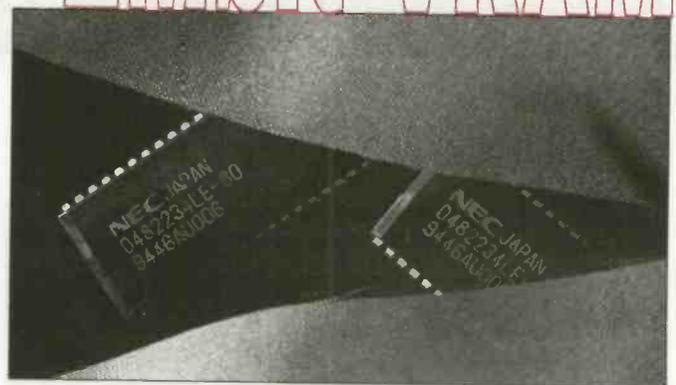Both versions feature a full-width split serial buffer, the two halves of which function independently. Hence one half can be outputting data while the other half is being loaded with the next data to be output. This removes the need to pause between reading rows (that is, it eliminates "flyback" time) and permits data to be output



continuously at full speed.

The serial buffer is bi-directional, so the VRAMs are suitable for use in serial input applications such as video cameras or video recorders.

Other capabilities of the devices include a flash write mode, a block write mode, and the stopping column mode, which accelerates tiling operations. These features greatly increase the performance of the system when running Windows-type operations.

For more information contact NEC
Electronics (UK) Ltd on 01908 691133.



FIELD ELECTRIC LTD

TEL: 01438 353781 FAX: 01438 359397

MOBILE: 0836 640328/0860 213370

UNIT 2, WILLOWS LINK, STEVENAGE, HERTS SG2 8AB



SONY 9" COLOUR MONITOR SUPER FINE PITCH CASED WITH DATA FOR RGB MODEL KTM 1000UB £45
SLO-SYN HS25 STEPPER MOTOR NEW + BOXED 40 OZ IN TORQUE £8.95 C/P 4.50
INTEL FLASH MEMORY CARDS 1Mb TO 4Mb FROM £60
5VDC @ 40AMP SWITCH MODE PSU NEW + BOXED £19 C/P 6
COUTANT DC/DC CONVERTERS NEW 48V IN 5V OUT @ 5A £6 C/P 3
12 VDC fans 90mm x 25mm £4 C/P 1.50
NEC CMV 123NE 12" COLOUR MONITOR WILL WORK ON PC VGA/AMIGA/ATAR/BBC. SUPPLIED WITH PC VGA LEAD. CASED 240 VAC £85.00 c/p 12.00
12VDC CENTRIFUGAL BLOWER NEW £6 C/P 2
240V TO 110V 80 WATT AUTO TOROIDAL TRANSFORMER £7 C/P 3
TEKTRONIX 453 OSCILLOSCOPE 50 MHz DUAL BEAM £175

REDMOND 12VDC 3000 RPM 80 WATT MOTOR NEW £6 C/P 3
RS 207-065 AUTO TRANSFORMER 1000 WATT £40 C/P 10
BERCO STAT 20HM 5A POT £2.50
MICROVETEC (CUB) COLOUR MONITORS T.L.L. 6 PIN DIN INPUT £29 C/P 10.00
MICROSOFT MS-DOS 6 UPGRADE IN SEALED PACKS ON 3.5" DISKS. UPGRADE FROM 2.11 OR LATER £15.50 C/P 4:00
NEC 256 30 PIN SIPP MEMORY NEW £5 FOR 256K C/P 90P
12" MONO VGA CHASSIS (PAPER WHITE) ENCLOSED 240 VAC £35 C/P 12.00
YUASA NP 10-6.6V 10Ah SEALED LEAD ACID BATTERY NEW £7.95 C/P 3.50
PC PSU ENCLOSED. NEW +5@20A +12@8A -5@3A 200 WATT £15.95 C/P 5
102 KEY AT IBM COMPATIBLE KEYBOARD TERMINATOR TO 6 PIN DIN MINI PLUG £8 C/P 3.50
ALL ITEMS UNDER £5 MIN ORDER £10.
C/P £2.75

PLEASE ADD 17.5% VAT TO ORDER. RING FOR C/P PRICES NOT SHOWN. OFFICIAL ORDERS AND OVERSEAS ENQUIRIES WELCOME.

Semiconductors, connectors, capacitors, fans, resistors, relays, manuals, data books and much more...

— All available at very low VAT inclusive prices —

Large SAE for current list


BHA Trading

15 OAKWELL CLOSE, STEVENAGE, HERTS SG2 8UG

TEL: 01438 816474

FAX: 01438 812569

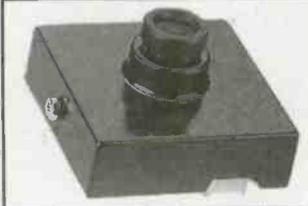HIGH QUALITY LOW COST C.C.T.V. CAMERA
LOW LIGHT LEVEL 0.03 LUX @ F1.4.
AUTO ELECTRONIC SHUTTER.
COMPOSITE VIDEO OUT VIA BNC PLUG.
SMALL DISCRETE SIZE.
CAN BE USED WITH PC DIGITISER.



This super quality CCD camera can be connected to your existing TV or video using the AV channel and can be used for discrete surveillance or observing your property externally using a suitable weatherproof housing. Can accommodate lighting levels ranging from daylight to street lighting using its built-in electronic shutter. Excellent when using with an infra red source. Built-in wide angle fixed focus lens, the camera has a resolution of 380 TVL. Can be housed inside an empty floodlight case. (extra). Camera size only 45mm x 45mm.

Special offer price of only: **£79.95 plus VAT (P&P £3.00)**

For full range of CCTV products send SAE to: **DIRECT CCTV LTD., DEPT ETI, UNIT 6, CARRICK COURT, FORREST GROVE BUSINESS PARK, MIDDLESBROUGH TS2 1QE**

COMPUTER KNOWLEDGE

CALL NOW ON:

0891 515 066

MODEM DOWNLOAD SERVICE V21 UP TO V42bis & V.F.C.

* Over 330 file areas to download from *

The latest Shareware, updates & Additions via daily file links to Europe & USA for the PC, Amiga & Atari

Areas of specialisation include DOS, OS/2, Windows/Windows NT, DESQview, Novel, Virus Protection, Dbase/Clipper, Engineering/Electronics & recently DOOM + Much More.

Recreational

* Multi User Games Available *

Calls cost 39p per minute cheap rate & 49p per minute at all other times. MODEM PARAM'S: -8 Data Bits, No Parity, 1 Stop Bit.

Komputer Knowledge, 3 Station Cottages, Cheddington, LU7 OSQ

★★ FOR SALE ★★

DEFENCE & AEROSPACE INDUSTRY ELECTRONIC EQUIPMENT & COMPONENTS ALL HIGH QUALITY SURPLUS MANY SPECIALS. WE STOCK 1000 + ITEMS & IF WE DON'T STOCK IT WE MAY BE ABLE TO GET IT FOR YOU PLEASE WRITE OR PHONE FOR LISTS OR REQUIREMENTS

MAYFLOWER ELECTRONICS
48 BRENDON ROAD,
WATCHET, SOMERSET, TA23 0HT
TEL (01984) 631825 FAX 634245

Create your own Mobile Robot v2

CONTROLLED BY COMPUTERS VIA PRINTER PORT
EXPENDABLE TO RADIO CONTROLS

33.00 pounds +£2 P&P

A complete Kit including hard/software for you to build

A Catalogue Full of PC interfacing ideas and plans

IE Innovative Interfacing Enterprise

Other PC Interfacing kits are available!
Centronic and RS232 Explorer kits, Centronic and RS232 24-line programmable I/O cards
Data logging systems, triple stepper motor boards, Radio controllers, see our catalogue!

Add £2 P&P in UK (£3.5 abroad) and make cheque payable to 'Innovative Interfacing Enterprise'
58 Lamport Court, Lamport Close, Manchester M1 7EQ, UK. **Tel/Fax: +44-(0)161-272-8279**

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 7000 SERIES OSCILLOSCOPES
Available from £200 - PLUG-INS SOLD SEPARATELY

TEKTRONIX T5475 4Ch 100MHz Delay Cursors	£1300
TEKTRONIX T5453 Dual Trace 60MHz Delay Cursors	£300
TEKTRONIX T465 4 Channel 300MHz Sweep Cursors	£1750
TEKTRONIX 2335 Dual trace 100MHz Delay	£750
TEKTRONIX 445 Dual Trace 350MHz Delay Sweep	£380
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep	£350
TEKTRONIX 465 Dual Trace 100MHz Delay Sweep	£300
TEKTRONIX SC504 Dual Trace 80MHz in TM003	£400
TEKTRONIX 2215 Dual Trace 50MHz Delay Sweep	£340
TEKTRONIX 455 Dual Trace 50MHz Delay Sweep	£400
PHILIPS PM3217 Dual Trace 20MHz Delay Sweep	£980
HITACHI V223 Dual Trace 20MHz Delay Sweep	£250
BECKMAN 9020 Dual Trace 20MHz Delay Sweep	£240
HAMEG 412 Dual Trace 20MHz Delay Sweep	£280
GOULD OS1103 Dual Trace 30MHz Delay Sweep	£240
GOULD OS11051 Dual trace 30MHz	£280
GOULD OS300 Dual Trace 20MHz	£200
WATSU S55742 Dual Trace 20MHz	£280
GOULD OS4000 Dual Trace 100MHz Digital Storage	£700
TEKTRONIX 484 Dual trace 100MHz Analogue Storage	£350
H.P. 1741A Dual Trace 100MHz Analogue Storage	£400

THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE

KIKUSUI 5530A DUAL TRACE 30MHz ONLY £180

EATON/ALTECH 380K11 Syn Sig Gen 1-200MHz with PM1602 AMFM Phase Mod.	£204
MARCONI 2019 Syn AMFM Sig Gen 800Hz-1040MHz	£1300
MARCONI 2018 Syn AMFM Sig Gen 800Hz-520MHz	£700
H.P. 8620C Sweep Osc 5-12.4GHz or 8-12.4GHz	£2800
H.P. 8620C Sweep Oscillator Main Frame only	£880
RACAL 5281 Syn AMFM Sig Gen 5 - 520MHz	£450
FARNELL SS520 Syn AMFM Sig Gen 10 - 980MHz	£480
MARCONI TF2237 Automatic Distortion Meter	£300
MARCONI TF2231 Distortion Factor Meter 20Hz-200KHz 0.05%	£150
MARCONI TF2235 Audio Power Meter Stand	£350
MARCONI TF2163 Attenuator DC-1GHz	£100
H.P. 8495B Attenuator DC-18GHz 0-11dB in 1dB Steps	£350
TEKTRONIX TDR1502	£1250
R & S Video Noise Meter UPSF27 with UPSF22	£880
R & S Mobile Tester SMSFP2 0.4 - 1000MHz	£1280


BRUEL & KJOER EQUIPMENT AVAILABLE PLEASE ENQUIRE

SPECTRUM ANALYSERS

JFR A7500 Synthesised 1 GHz	£4000
H.P. 8565A 0.01-22GHz	£4500
ANDO AC6291 with AC2811 1700MHz	£1550
POLARAD 841.1 10MHz-180MHz	£1000
H.P. 182 with 8558A & 8558B 100Hz-1500MHz	from £1500
H.P. 141T with 8554A & 8552B 10MHz - 18GHz	£1700
H.P. 141T with 8554B & 8552B 500MHz - 1350MHz	£1880
H.P. 141T with 8553B & 8552A 10Hz - 110MHz	£880
H.P. 141T MAIN FRAMES ONLY, GOOD TUBES	£225
MARCONI TF2370 30Hz - 110MHz	£1000
TEKTRONIX 7L12 with Main Frame 100Hz-1800MHz	£1200
TEKTRONIX 7L5 with Main Frame 20MHz - 5MHz	£1000

Used Equipment - Guaranteed. Manuals supplied if possible. This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

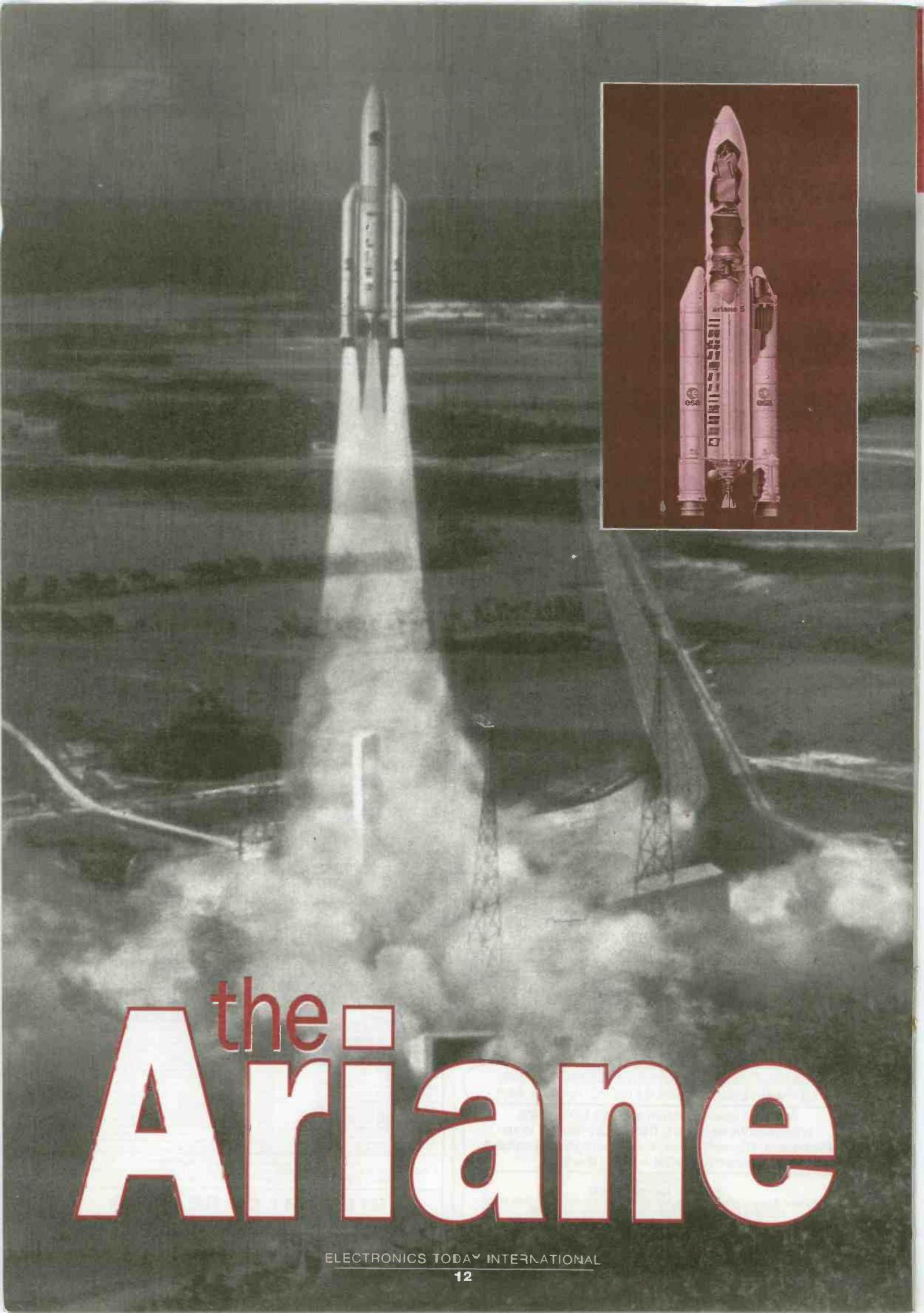STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Tel: 01734 268041 Fax: 01734 351696 Callers welcome 9am to 5.30pm MON-FRI (UNTIL 8pm THURS)



the **Ariane**

ELECTRONICS TODAY INTERNATIONAL

The European Space Agency is about to launch a new ultra-reliable, high technology, rocket which is powerful enough for manned space launches. Douglas Clarkson takes a look at the system and the technology

The development of a new space launch system is one of the most expensive areas of modern technology. Such projects require specialist scientific and technical skills of a very diverse and precise nature.

Also, the emphasis on ultra-high reliability places special emphasis on rigorous testing and proving of all components - both in the unassembled form and also in assembled modules such as rocket motors. This forces medium sized countries such as exist within Europe to form a collaborative agency such as the European Space Agency (ESA). The current membership and locations of major sites and offices of the European Space Agency (for which Ariane 5 Project is a major development item) is shown in figure 1.

The Ariane 5 programme was commissioned in November 1987. Few could have anticipated the major political changes that have subsequently taken place. The Soviet Union is no more, Germany is again a unified country and a severe recession has been experienced by Western countries. The key theme of the Ariane 5 rocket was to give Europe an independent launch capability for both routine launch satellites and also servicing the planned Space Station.

In its prime, initial role, however, the new Ariane 5 is an unmanned commercial launch vehicle with only minimal re-usable elements - the twin solid fuel rockets of the system. Such solid booster rockets are also used on NASA's Space Shuttle. The aspect of catering for a manned crew and the necessary life support infrastructure increased significantly the size

and weight of NASA's 're-usable' Shuttle compared with that of an unmanned vehicle. A very significant element of NASA's budget is spent on the Shuttle missions. Each Shuttle mission costs in excess of \$150 million. NASA is well aware of the desirability of reducing the cost of the next generation of launch vehicles.

While other designs such as HOTOL and its variants are still on the drawing board for the next generation of ESA launch vehicles, Ariane 5 will provide a continuing independent capability for Europe well into the next century. Within the European Space Agency, the FESTIP programme is seeking to identify the optimum post Ariane 5 launch vehicle.


There seems, however, a clear window of opportunity to develop a significantly cheaper launch vehicle. There is every reason to believe that the solution could be a HOTOL variant - a single stage to orbit vehicle with extra light superstructure and with an air breathing engine for the ascent in the atmosphere to 28 km. Such developments, however, are very closely tied to materials science. There is a requirement to produce materials with lightweight, increased strength and for specific zones of the craft high temperature tolerance e.g. on heated re-entry surfaces. While such development would have a direct relevance to space flight, such developments in materials science would also find useful application throughout the aerospace and other high technology industries.

The Ariane Family

The first test flight of Ariane 1 took place on 24th December 1979. The first operational flight of an Ariane rocket, however, took place on 4th of August 1984 as an Ariane 2/3 system. The first flight of the Ariane 4 system took place on 15th June 1988 and a typical Ariane 4 launch is shown in Figure 2. The central rocket motor is flanked by four peripheral rocket motors units. The Ariane 4 can deliver a single payload of around 10 tonnes into low earth orbit.

5

Figure 1: Participating states and locations of major sites and offices of the European Space Agency.

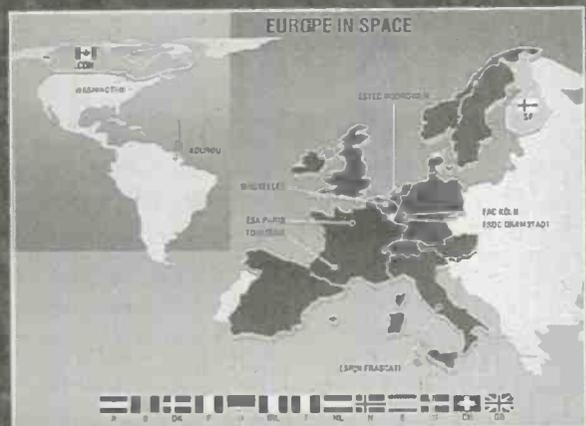

Ariane 5: A Summary

The basic design of the new Ariane 5 can be separated into the lower standard propulsion section and the upper payload section as indicated in figure 3. There is some degree of flexibility in the upper payload section which can be a single payload launch (unmanned), a dual payload launch (unmanned) or a manned flight stage. The prime interest now is to develop the vehicle system as a commercial launch craft for unmanned satellites. The final design of the Ariane 5 was approved during 1988 after the first successful launch of the Ariane 4 system. Figure 4 shows a cut away representation of the Ariane 5 craft.

The main difference between Ariane 4 and Ariane 5 is that the payload capacity has been almost doubled to 20.5 tonnes for low earth orbit or 6.8 tonnes to a high geostationary orbit such as is required for satellite broadcast and telecommunications. Also, part of the assembly - the new solid fuel booster stages are recoverable items. After being jettisoned from the cryogenic stage at a height of around 60 km, parachutes in the nose section of each spent booster rocket will be deployed in the atmosphere and the sections recovered by surface ships for subsequent inspection and possible re-use. While Ariane 5 is designed to be cheaper per launch than the Ariane 4 by around 10%, future generations of launch vehicles, utilising single stage to orbit technology will hopefully be significantly cheaper.

Ariane 5: The Fingers on the button

Table 1 shows the relative contribution from member states of the European Union and other associated countries to the Ariane 5 project.

Table 1
Contributions from participating countries

Country	Percentage Contribution
France	46.2
Germany	22
Italy	15
Belgium	6
Spain	3
Holland	2.1
Sweden	2
Switzerland	2
Norway	0.6
Austria	0.4
Denmark	0.4
Ireland	0.2
Not Covered	0.1

There is one major member of the European Union missing from this list - the UK, whose government seems to think that the development of space technology is a waste of money, and is therefore denying this country's aerospace industry any significant role in the future of a very rapidly expanding high technology area.

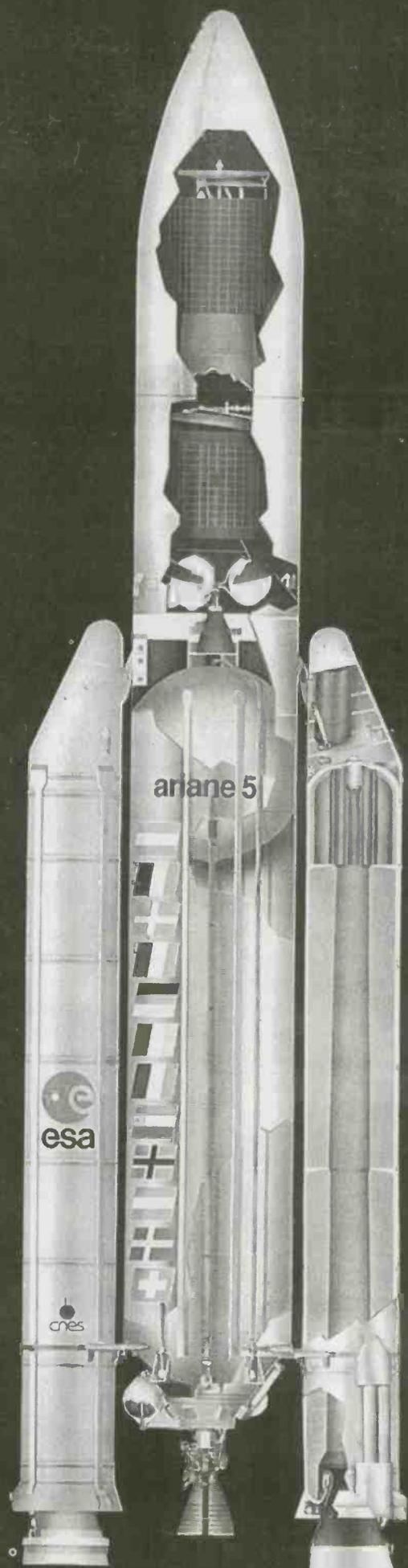


Figure 4: Cutaway representation of the Ariane 5 craft.

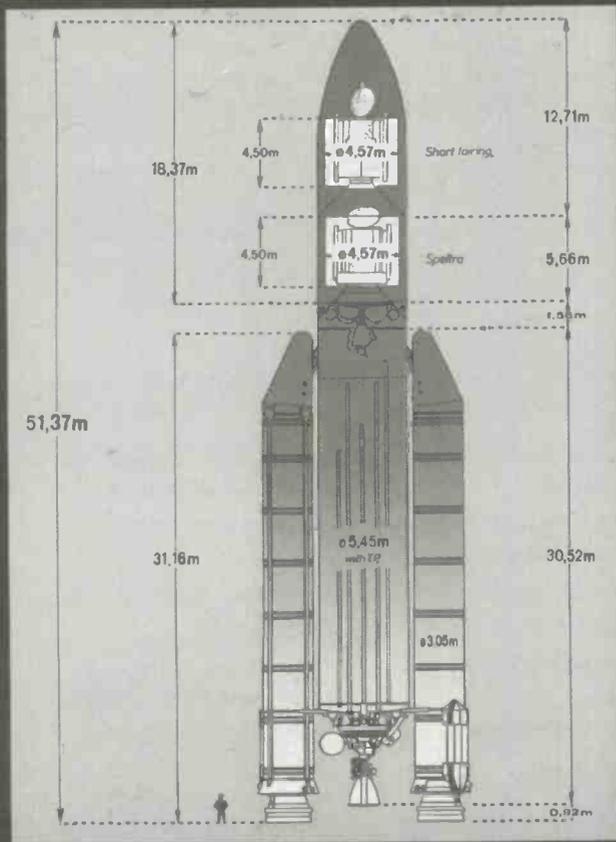


Figure 3: Structural design of Ariane 5 dual launch facility. The propulsion system consists of a central cryogenic stage and twin solid fuel boosters.

The Cryogenic Main Stage

Liquid hydrogen and liquid oxygen are used as fuel for the main cryogenic stage. This combination generates an excellent exhaust velocity of combustion products. Only liquid hydrogen and liquid fluorine react to produce a slightly higher exhaust velocity. The unit is some 5.4 m in diameter and 30.5 metres high and powered by a single Vulcain engine which is shown in figure 5. Between 114 and 120 tonnes of thrust are developed in a vacuum. The fuel contents of 25 tonnes of liquid hydrogen and 130 tonnes of liquid oxygen are burnt in just 570 seconds. The cryogenic stage with all its superb engineering, however, is expendable. When the cryogenic stage is exhausted it will fall away from the flight path and be lost in the Atlantic Ocean.

Testing of the cryogenic main stage is a key point of the Ariane project. The first test firing of a completed engine took place at Vernon (France) in July 1990. A second engine test facility was later commissioned later that year in Lampoldshausen in October 1990. By April 1994, around 180 tests had been completed on a total of 13 engines. The test programme should enable 350 tests to be completed on 16 engines and accumulate a total burn time of 90,000 seconds. This is equivalent to the burn time of some 160 missions. The test programme, however, is designed to optimise the manufacture and quality control of entire cryogenic systems.

Key components of the rocket motor such as the oxygen turbo pump are manufactured under clean room conditions. Part of the extensive series of tests undergone by the main cryogenic motor include vibration tests on a specifically designed shaker system. Such tests ensure that the structures remain secure during the initial ascent mode.

Solid Booster Stage

In common with the Space Shuttle, Ariane 5 makes use of twin solid stage booster rockets. Each booster is 3.03m in diameter, 30 metres high and has a lift-off mass of 270 tonnes. At take-off, each rocket delivers some 540 tonnes of thrust, though this is reduced after take-off to reduce the aerodynamic load on the launcher in the lower atmosphere. The solid stage boosters burn for a total of 130 seconds and contain 237 tonnes of solid propellant. The design and construction of the Ariane 5 solid rocket stages is somewhat reminiscent of an exotic 5th of November rocket. All of the components, the containment case, the propellant mixture and nozzle etc are designed to very high levels of precision and on a much larger scale.

As was discovered in the Challenger accident with NASA's Space Shuttle, a key feature is the robustness of the seals between the segments of the containment structure. The segments of the steel booster case are extensively checked by ultrasound to detect defects and cracks in metal structures. Each nozzle is fitted with a flexible bearing which can angle the booster thrust direction by up to 6 degrees on two axes.

During project development, elements of the booster stage are manufactured and tested at various sites. Booster cases are produced at Augsburg; thermal protection of casing and filling of forward booster section with propellant is undertaken at Colleferro (near Rome); nozzle manufacture and assembly is undertaken at Bordeaux while filling of the central and rear booster propellant, booster stage assembly and function tests have been undertaken at Kourou (French Guyana) since early 1993. Figure 6 shows an assembled booster stage. Performance can be checked on a gantry mounted over a solid granite trench some 60m deep and 200m long as indicated in figure 7.

Upper Composite:VEH, SPELTRA and Fairings

The 'Upper composite' sits on the top of the main cryogenic stage and represents essentially the facilities for delivering the system payload into orbit. This stage has also a propulsion system but with much smaller fuel load than the main cryogenic stage. A specific engine - the Aestus - has been developed to deliver a maximum thrust of 27.5 kN. Girdled round the lower propulsion stage in the upper composite is the Vehicle Equipment Bay. This is where the complex control equipment such as internal navigation, on board computer and switching unit are housed.

The SPELTRA satellite carrier structure is designed to securely contain multiple payloads. The maximum outer diameter of this structure is 5.4 metres and is 20 metres high. For this configuration, a short fairing unit (twin shells at nose of rocket) is used. For single stage payloads, either a long or a short fairing unit (split shells) is required. The fairings are jettisoned at an altitude of around 110 km.

It is interesting to note a subtle difference between launches such as the Shuttle and rockets such as Ariane 5. In terms of adding to the clutter of rubbish in space, the Ariane system, much like traditional rocket systems, will add in orbit round the earth the Vehicle Equipment Housing for single stages and in addition the SPELTRA



Figure 5: View of main vacuum cryogenic engine

unit for multiple payloads. The Shuttle, however, should add very little by way of space junk into space. The large 'drop tank' of cryogenic fuel jettisoned by the Shuttle falls into the sea and the solid booster rockets are recovered.

Ground Facilities in French Guyana

It is planned to undertake up to 8 launches per month at the new launch pad facilities - ELA 3. This complex is based on the ELA 2 site used currently for the Ariane 4. Figure 8 shows an artist's impression of an Ariane 5 launch.

While the forward segment of the propellant stage is packed in Italy, the centre and rear segments are packed in a specially constructed Solid Propellant Production Unit which has been in service since 1992. For safety reasons these facilities are remote from other installations. As part of the process of final filling of propellant in French Guyana, the booster cases lined with a highly efficient insulating liner.

A cryogenic production unit for supply of liquid hydrogen and oxygen has been established close to the new Ariane 5 launch pad.

General Industrial Framework

Table 2 summarises the key industrial partners involved in the Ariane 5 Project.

Often, the main contractor will sub-contract work to a

further range of sub-contractors. Thus, over 30 key sub-contractors are involved in the manufacture of the main cryogenic stage. The cost of the Ariane programme is set at 6130 MAU (Million Accounting units) at 1993 economic activity levels. The distribution of work among contractors reflects also the budget contributions of countries associated with the Ariane 5 project.

It is clear that the aerospace companies of major members of the European Union are not benefiting from the Ariane 5 project.

Table 2
Key industrial partners involved

Feature	Main Contractor
Solid Booster Housing	Aerospatiale
Booster Propellant /thermal system	Europropulsion
Main Cryogenic Stage	Aerospatiale
Cryogenic Motor	SEP
EPS	Deutch Aerospace/ERNO
Vehicle Equipment bay	Matra Marconi Space
Speltra	Domier/Deutsche Aerospace
Fairings	Oerlikon Contraves

While the ESA retains overall management of the Ariane 5 programme, CNES, the French Space Agency, is responsible for project management. Aerospatiale, in turn, is contracted to be the key industrial architect for system design and general software development. Aerospatiale therefore has the primary role of overall design and specifications of the major system components and modules.

The Ariane 5 project is not only demanding in relation to the development of appropriate technology, it is also demanding in relation to project management. Even the best of technology can succumb to poor organisation and communications. The programme of development, however, since the beginning of the Ariane project has hopefully allowed such skills to develop. Also, the increasing ease of interchange of data across computer networks has allowed remote sites to exchange data in increasingly effective ways so that physical distance is not now an obstacle to collaborative development.

Summary



Whatever the pros and cons of development by Europe of the Ariane 5 at a political level, the one positive point is that by participating in such a project, Europe can be seen to be developing and retaining skills which will maintain a high level of competence in space vehicle launch technology. The investment in specific areas of technology will also allow the various companies involved to establish a foothold in such space technology niches on a global scale - to the benefit of the European Union as a whole.

Point of Contact:

European Space Agency,
8-10, rue Mario-Nikis,
75738 PARIS Cedex 15,
France.

Main pic, Figure 6: Solid rocket booster in assembly structure, French Guyana

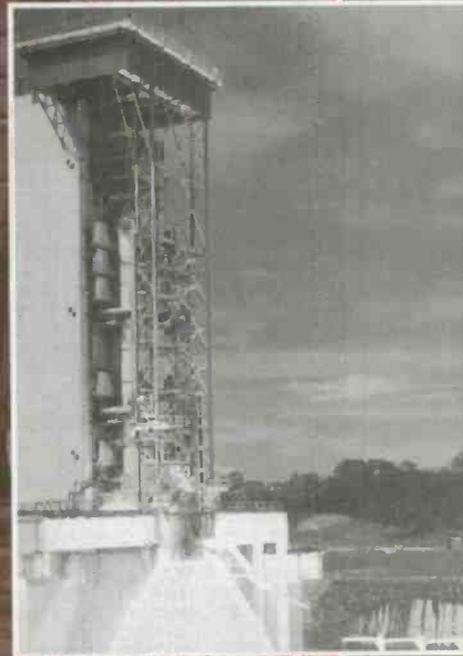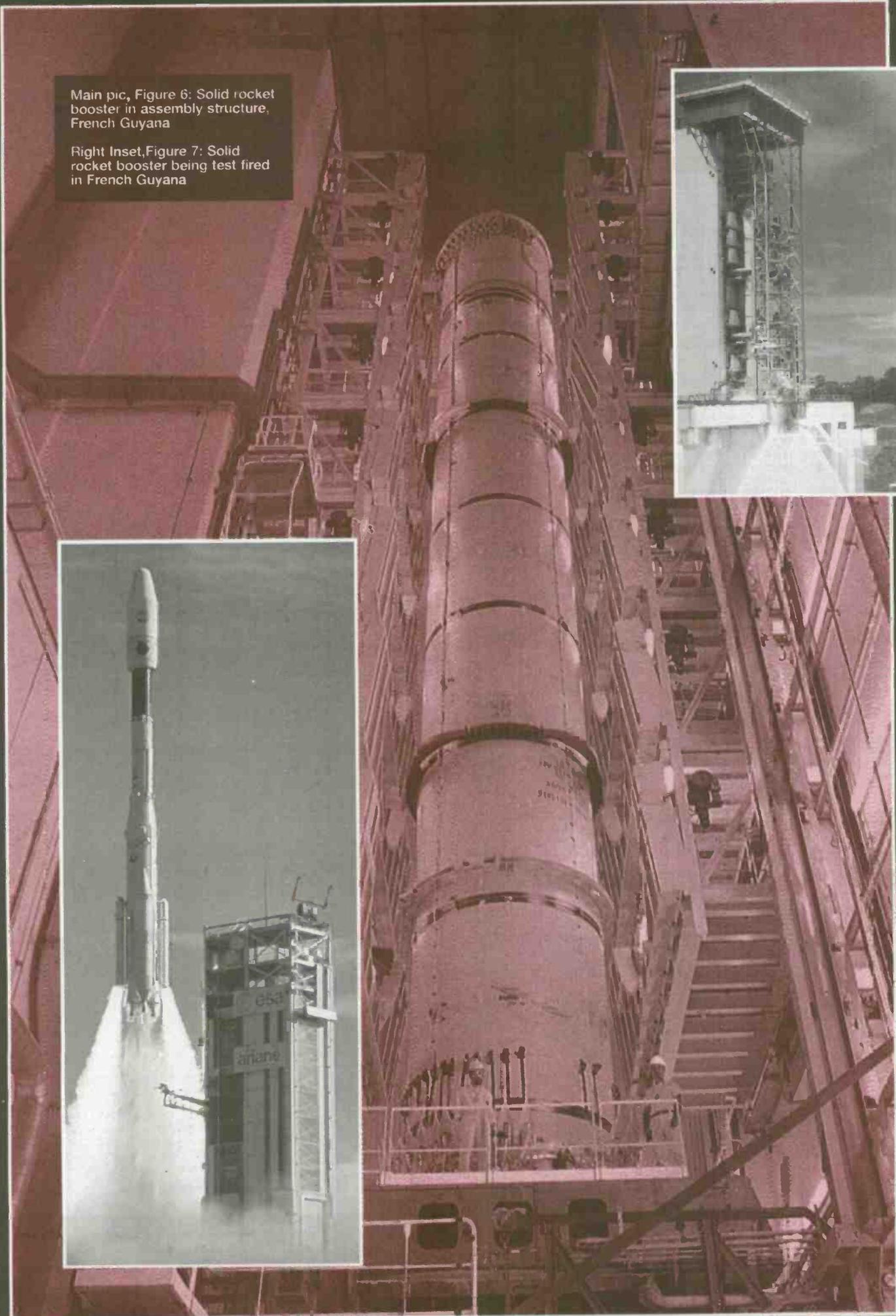Right Inset, Figure 7: Solid rocket booster being test fired in French Guyana





**8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF**
Tel: 01203 650702
Fax: 01203 650773
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access)

OSCILLOSCOPES

Gould OS3000/ADVANCE 3000 - 30MHz Dual ch.....	£200
Gould 4035 - 20MHz Digital storage.....	£500
Gould 4050 - 35MHz Digital storage.....	£650
Gould 5110 - 100MHz Intelligent oscilloscope.....	£850
Gould OS4000, OS4200, OS4100, OS1000B.....	from £125
Hewlett Packard 1740A, 1741A, 1774A, 100MHz dual ch.....	from £350
Hewlett Packard 1707A, 1707B - 75MHz 2ch.....	from £275
Hewlett Packard 54201A - 300MHz Digitizing.....	£1750
Hewlett Packard 54501A - 100MHz - Digitizing 4 channel.....	£1950
Hewlett Packard 54504A - 400MHz Digitizing.....	£3500
Hewlett Packard 54100D - 1GHz Digitizing.....	£4500
Tektronix 468 - 100MHz - D.S.O.....	£800
Lecroy 140 - 100MHz - D.S.O.....	£POA
Hitachi V212 20MHz Dual Channel.....	£175
Nicolet 3091 - LF D.S.O.....	£1100
Phillips PM 3315 - 60MHz - D.S.O.....	£750
Phillips 3206, 3211, 3212, 3217, 3226, 3240, 3243, 3244, 3261, 3262 (2ch + 4ch).....	from £125 to £350
Phillips PM 3295A - 400MHz Dual Channel.....	£1950
Tektronix 2213 - 60MHz Dual Channel.....	£425
Tektronix 2215 60MHz dual trace.....	£450
Tektronix 2235 Dual trace 100MHz (portable).....	£800
Tektronix 2236 - 100 Mhz - 4 channel with Counter/Timer/D.M.M.....	£995
Tektronix 2335 Dual trace 100MHz (portable).....	£750
Tektronix 2225 - 50MHz dual ch.....	£450
Tektronix 2465B - 400 Mhz 4 channel.....	£3950
Tektronix 464/466 - 100MHz An storage.....	from £350
Tektronix 465/465B - 100MHz dual ch.....	from £350
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch.....	from £300
Tektronix 7704 - 250MHz 4 ch.....	from £650
Tektronix 7844 - Fitted with 7A42, 7B80, 7B85 Plug-Ins.....	£1500
Tektronix 7904 - 500MHz.....	from £850
Tektronix 468 - 100MHz Digital Storage.....	£800
Tequipment D68 - 50MHz Dual Channel.....	£200
Iwatsu TS 8123 - 100 Mhz - D. Storage.....	£850

Other scopes available too

SPECTRUM ANALYSERS

Alltech 727 - Spec. Analyser 22.4 GHz with Alltech 70727 - Tracking Generator (10KHz - 12.4 GHz).....	£2000
Hewlett Packard 3580A - -5Hz-50KHz.....	£995
Hewlett Packard 3709B - Constellation Analyser with 15709A High Impedance Interface (As New).....	£6750
Hewlett Packard 182T wth 8559A (10MHz - 21GHz).....	£3750
HP 3582A - 25KHz Analyser, dual channel.....	£2500
Hewlett Packard 35601A - Spectrum Analyser Interface.....	£1000
Hewlett Packard 8754A - Network Analyser 4 - 1300MHz.....	£3250
Marconi 2370 - 110MHz.....	£995
Marconi 2371 - 30KHz - 200MHz.....	£1250
Poird 641-1 - 10MHz - 18GHz.....	£1500
Rohde & Schwarz - SWOB 5 Polyskop 0.1 - 1300MHz.....	£2500
Schlumberger 1250 - Frequency Response Analyser.....	£2500
Tektronix 7L12 with 7603 mainframe (1.8GHz).....	£1500
Tektronix 7L14 with 7603 mainframe (1.8GHz).....	£2000
Tektronix 7L18 with 7603 mainframe (18GHz).....	£2950
Texscan AL51A (4MHz - 1GHz).....	£850

MISCELLANEOUS

Anritsu MG642A Pulse Pattern Generator.....	£1500
Ballantine 323 True RMS Voltmeter.....	£350
Datalab DL 1080 Programmable Transient Recorder.....	£350
Dyanpert TP20 Intelliplace - Tape peel Tester - immaculate condition.....	£1950
Farnell 2081 R/F Power meter.....	£350
Farnell TSV 70 MkII Power Supply (70V-5A or 35V-10A).....	£200
Ferrogaph RTS-2 Audio Test Set with ATU 1.....	£500
Fluke 8010A/8012A/8050A Digital multimeters - from.....	£125
Fluke 5101A AC/DC Calibrator.....	£3500
Fluke 5101B AC/DC Calibrator.....	£6500
Marconi - 2019A - 80KHz - 1040MHz - Synthesised Signal Generator.....	£1950
Hewlett Packard 8662A - (10KHz-1280MHz) - Synthesised Signal Generator.....	£7950
Hewlett Packard 4953A - Protocol Analyser.....	£3500
Hewlett Packard 1630G - Logic Analyser - 65 Channels.....	£850
E.I.P. 548A - Frequency Counter (26.5 GHz).....	£3500
Marconi 6950 Power Meter with 6910 Sensor.....	£800
Racal 1992 - 1.3GHz Frequency Counter.....	£850
Datron 1061 - Precision Multimeter.....	£650
Fluke 5220A Transconductance Amplifier (20A).....	£3000
Fluke 720A Kelvin-Variety Voltage Divider.....	£450
Fluke 750A Reference Divider.....	£450
Gould TA 600 - Thermal Array Recorder.....	£400
Gould K100D - 100MHz Logic Analyser with Pods.....	£350
Heiden 1107 - 30V-10A Programmable Power Supply (IEEE).....	£650
Hewlett Packard 3437A System voltmeter.....	£350
Hewlett Packard 3456A Digital voltmeter.....	£850
Hewlett Packard 3760/3761 Data gen + error detector.....	each £300
Hewlett Packard 3762/3763 Data gen + error detector.....	each £350
Hewlett Packard 5420A Digital Signal Analyser.....	£350
Hewlett Packard 5423A Structural Dynamics Analyser.....	£350
Hewlett Packard 54470B Digital Filter.....	£100
Hewlett Packard 54410A Analogue/Digital Converter.....	£100
Hewlett Packard 7402 Recorder with 17401A x 2 plug-ins.....	£300

Hewlett Packard 8011A Pulse gen. 0.1Hz-20MHz.....	£500
Hewlett Packard 8443A Tracking gen/counter with 1EEE.....	£300/400
Hewlett Packard 8620C Sweep oscillator mainframe.....	£400
Hewlett Packard 8750A Storage normaliser.....	£375
Hewlett Packard 8684A 5.4GHz to 12.5GHz Sig-Gen.....	£3000
Hewlett Packard 8640B - AM/FM Signal Gen (512MHz).....	£850
Hewlett Packard 5340A - 18GHz Frequency Counter.....	£900
Hewlett Packard 5356A - 18GHz Frequency Converter head.....	£450
Hewlett Packard 432A - Power Meter (with 478A Sensor).....	£275
Hewlett Packard 435A or B Power Meter (with 8481A/8484A).....	from £750
Hewlett Packard 3438A Digital multimeter.....	£200
Hewlett Packard 6181C D.C. current source.....	£150
Hewlett Packard 59501B HP.1B isolated D/A power supply programmer.....	£150
Hewlett Packard 3711A/3712A/3791B/3793B Microwave Link Analyser.....	£3500
Hewlett Packard 5316A Universal Counter HP1B.....	£550
Hewlett Packard 5316B Universal Counter HP1B.....	£775
Hewlett Packard 5385A Frequency Counter - 1GHz - (HP1B) with OPTS 001/003/004/005.....	£995
Hewlett Packard 3779C Primary Multiplex Analyser.....	£1000
Hewlett Packard 6623A Triple output system power supply.....	£1950
Hewlett Packard 3764A (Opt 002) Digital Transmission Analyser.....	£2250
Hewlett Packard 3586A Selective level meter.....	£1750
Hewlett Packard 3325A - 21MHz Synthesiser/Function Gen.....	£1500
Hewlett Packard 8152A - Optical Average Power Meter.....	£1250
Hewlett Packard 8158B - Optical Attenuator (OPTS 002 + 011).....	£1100

HEWLETT PACKARD 6261B

Power Supply 20v-50A £500 Discount for Quantities

International Light - IL 1700 Research Radiometer with Erythermal Sensor Head.....	£1250
Krohn-Hite 2200 Lin/Log Sweep Generator.....	£995
Krohn-Hite 4024A Oscillator.....	£250
Krohn-Hite 6500 Phase Meter.....	£250
Lyons PG73N/PG75/PG28/PG Pulse generator.....	from £225
Marconi 2432A 500MHz digital freq. meter.....	£200
Marconi 2337A Automatic dist. meter.....	£150
Marconi 2356 20MHz level oscillator.....	£300
Marconi 2306 Programmable interface.....	£450
Marconi 2830 Multiplex tester.....	£850
Marconi 2831 Channel access switch.....	£250
Marconi 2019 - AM/FM Signal generator - 1040 MHz.....	£1800
Multicore "Vapourrette" Bench Top Vapour Phase SMD Soldering Machine (New + Unused).....	£650
Phillips PM 5167 10MHz function gen.....	£400
Phoenix 5500A - Telecomms Analyser with various Interface Options.....	£2500
Racal Dana 9242D Programmable PSU 25V-2A.....	£300
Racal Dana 9246S Programmable PSU 25V-10A.....	£400
Racal Dana 3100 40-130MHz synthesiser.....	£750
Racal Dana 5002 Wideband eval meter.....	£650
Racal Dana 5003 Digital m/meter.....	£150
Racal Dana 9000 Microprocessing timer/count. 520MHz.....	£550
Racal Dana 9081 Synth. sig. gen. 520MHz.....	£550
Racal Dana 9084 Synth. sig. gen. 104MHz.....	£450
Racal Dana 9303 True RMS/R/Fevel meter.....	£650
Racal Dana 9341 LCR databridge.....	£250
Racal Dana 9500 Universal timer/counter 100MHz.....	£200
Racal Dana 9917 UHF frequency meter 560MHz.....	£175
Racal Dana 9302A R/F millivoltmeter (new version).....	£375
Racal Dana 9082 Synthesised am/fm sig gen (520MHz).....	£500
Racal 9301A - True RMS R/F Millivoltmeter.....	£300
Racal 9921 - 3GHz Frequency Counter.....	£450
Rohde & Schwarz BN36711 Digital Q meter.....	£400
Rohde & Schwarz - Scud Radio Code Test Set.....	£995
Rohde & Schwarz - LFM 2 Sweep Generator 0.02 - 60MHz.....	£1500
Rohde & Schwarz SUF 2 Noise Generator.....	£300
Rotek 3980A AC/DC Precision Calibrator with Rotek 350A High Current Adaptor.....	£POA
Schlumberger S.I. 4040 Stabilock - High accuracy 1GHz Radio Test Set.....	£5950
Schlumberger 4923 Radio Code Test Set.....	£1500
Schlumberger 2720 1250 MHz Frequency Counter.....	£500
Solarton Schlumb 1170 Freq. response analyser.....	£250
Systems Video 1258 Waveform Analyser + 1255 Vector Monitor + 1407 Differential Phase and Gain Module + 1270 Remote Control Panel.....	£2250
Systron Donner 1702 Synthesised Sig. Gen 1GHz.....	£900
Systron Donner 6054B or D 18GHz or 24GHz Freq. Counter.....	from £800
Tequipment CT71 Curve Tracer.....	£250
Tektronix TM5003 + AFG 5101 Arbitrary Function Gen.....	£1750
Tektronix 1240 Logic Analyser.....	£750
Tektronix 1480 Waveform Monitor.....	£POA
Tektronix 651 HR Monitor.....	£POA
Tektronix DAS9100 - Series Logic Analyser.....	£500
Tektronix - Plug-ins - many available such as SC504, SW503, SG502, PG508, FG504, FG503, TG501, TR503 + many more.....	£POA
Time 9811 Programmable Resistance.....	£600
Time 9814 Voltage Calibrator.....	£750
Wayne Kerr B424/N LCR Component Meter Set.....	£200
W&G SPM12 Level Meter (200Hz - 6MHz).....	£500
W&G PS12 Level Oscillator (200Hz - 6MHz).....	£500
Weller D801/D802 Desoldering station.....	£175
Willtron 560 Scalar Network Analyser.....	£800
Willtron 352 Low Frequency Differential Input Phase Meter.....	£350
EIP 331 - Frequency counter 18GHz.....	£700

MANY MORE ITEMS AVAILABLE - SEND LARGE S.A.E. FOR LIST OF EQUIPMENT ALL EQUIPMENT IS USED - WITH 30 DAYS GUARANTEE. PLEASE CHECK FOR AVAILABILITY BEFORE ORDERING - CARRIAGE & VAT TO BE ADDED TO ALL GOODS

BULL CLEAROUT SALE

WIRELESS VIDEO BUG KIT Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! All the components including a PP3 battery will fit into a cigarette packet with the lens requiring a hole about 3mm diameter. Supplied with telescopic aerial but a piece of wire about 4" long will still give a range of up to 100 metres. A single PP3 will probably give less than 1 hours operating time. £99 REF EP79. (probably not licensable!)

GOT AN EXPENSIVE BIKE? You need one of our bottle alarms, they look like a standard water bottle, but open the top, insert a key to activate a motion sensor alarm built inside. Fits all standard bottle carriers, supplied with two keys. SALE PRICE £7.99 REF SA32

GOT AN EXPENSIVE ANYTHING? You need one of our cased vibration alarms, keyswitch operated, fully cased just fit it to anything from videos to caravans, provides a years protection from 1 PP3 battery, and protect it! UK made. SALE PRICE £4.99 REF SA33

DAMAGED ANSWER PHONES These are probably beyond repair so they are just £4.99 each. Mainly response 200 machines. REF SA30

COMMODORE GAMES CONSOLES Just a few of these left to clear at £5 ref SA31. Condition unknown.

COMPUTER DISC CLEAROUT We are left with a lot of software packs that need clearing so we are selling at disc value only! 50 discs for £4, that's just 8p each!! (our choice of discs) SALE PRICE £4 ref EP66

IBM PS2 MODEL 150Z CASE AND POWER SUPPLY Complete with fan etc and 200 watt power supply. SALE PRICE £9.95 ref EP67

DELL PC POWER SUPPLIES 145 watt, +5, -5, +12, -12, 150x150x85mm complete with switch, flyleads and IEC socket. SALE PRICE £9.99 ref EP55

1.44 DISC DRIVES Standard PC 3.5" drives but returns so they will need attention SALE PRICE £4.99 ref EP68

1.2 DISC DRIVES Standard 5.25" drives but returns so they will need attention SALE PRICE £4.99 ref EP69

PP3 NICADS New and unused but some storage marks. SALE PRICE £4.99 ref EP52

SOLAR PANELS 3v output with two flyleads, 100x60 mm pack of 10 SALE PRICE £6.99 ref EP56

DELL PC POWER SUPPLIES (Customer returns) Standard PC psu's complete with fly leads, case and fan, pack of two psu SALE PRICE £5 FOR TWO!!! ref EP61

GAS HOBS AND OVENS Brand new gas appliances, perfect for small flats etc. Basic 3 burner hob SALE PRICE £24.99 ref EP72. Basic small built in oven SALE PRICE £79 ref EP73

BITS AND BOBS We have a quantity of cased modems, multiplexers etc different specs but ideal strippers. SALE PRICE £4 each ref EP63

RED EYE SECURITY PROTECTOR 1,000 watt outdoor PIR switch SALE PRICE £9.99 ref EP57

ENERGY BANK KIT 100 6"x6" 6v 100mA panels, 100 diodes, connection details etc. £69.95 ref EF112.

CCTV CAMERA MODULES 46X70X29mm, 30 grams, 12v 100mA. auto electronic shutter, 3.6mm F2 lens, CGIR, 512x492 pixels, video output is tv p-p (75 ohm). Works directly into a scart or video input on a tv or video. IR sensitive. £79.95 ref EF137.

IR LAMP KIT Suitable for the above camera enables the camera to be used in total darkness! £5.99 ref EF138.

PASTEL ACCOUNTS SOFTWARE, does everything for all sizes of businesses, includes word processor, report writer, windowing, networkable up to 10 stations, multiple cash books etc. 200 page comprehensive manual. 90 days free technical support (0345-326009 try before you buy!) Current retail price is £129, SALE PRICE £9.95 ref SA12. SAVE £120!!!

MINI MICRO FANS 12V 1.5" sq SALE PRICE £2. Ref SA13.

C PTH PRINTERS 80 col, 9 pin matrix, serial/parallel, NLQ/draft, 3 mth warranty, good condition, SALE PRICE £39 ref SA14.

REUSEABLE HEAT PACKS. Ideal for fishermen, outdoor enthusiasts elderly or infirm, warming food, drinks etc, defrosting pipes etc. reusable up to 10 times, lasts for up to 8 hours per go, 2,000wh energy, gets up to 90 degC. SALE PRICE £9.95 REF SA29

A4 DTP MONITORS Brand new, 300 DPI. Complete with diagram but no interface details. (so you will have to work it out!) Bargain at just £7.99 each!!! Ref EF185

12V2AMP LAPTOP psu's 110x55x40mm (includes standard IEC socket) and 2m lead with plug. 100-240v IP. SALE PRICE £6.99 REF SA15.

PC CONTROLLED 4 CHANNEL TIMER Control (on/off times etc) up to 4 items (8A 240v each) with this kit. Complete with Software, relays, PCB etc. £25.99 Ref 95/26

COMPLETE PC 300 WATT UPS SYSTEM Top of the range UPS system providing protection for your computer system and valuable software against mains power fluctuations and cuts. New and boxed, UK made Provides up to 5 mins running time in the event of complete power failure to allow you to run your system down correctly. SALE PRICE just £89.00.

SOLAR PATH LIGHTS Low energy walklights powered by th sun! builtin PIR so they work when you walk past. Includes solar panel & rechargeable bat. SALE PRICE £19.99 REF EP62

BIG BROTHER PSU Cased PSU, 6v 2A output, 2m c/p lead, 1.5m input lead, UK made, 220v. SALE PRICE £4.99 REF EP7

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is a certificate enabling you to reproduce the manuals as much as you like! SALE PRICE £14 REF EP74

RACAL MODEM BONANZA! 1 Racal MPS1223 1200/75 modem, telephone lead, mains lead, manual and comms software, the cheapest way onto the net! all this for just £13 ref DEC13

HOW LOW ARE YOUR FLOPPIES? 3.5" (1.44) unbranded. We have sold 100,000+ so ok! Pack of 50 £24.99 ref DEC16

6mw LASER POINTER. Supplied in kit form, complete with power adjuster, 1-5mw, and beam divergence adjuster. Runs on 2 AAA batteries. Produces thin red beam ideal for levels, gun sights, experiments etc. Cheapest in the UK! just £39.95 ref DEC49

RADIO PAGERS Brand new, UK made pocket pagers clearance price is just £4.99 each 100x40x15mm packed with bits! Ref SEP5.

BULL TENS UNIT Fully built and tested TENS (Transcutaneous Electrical Nerve Stimulation) unit, complete with electrodes and full instructions. TENS is used for the relief of pain etc in up to 70% of sufferers. Drug free pain relief, safe and easy to use, can be used in conjunction with analgesics etc. £49 REF TEN/1

COMPUTER RS232 TERMINALS. (LIBERTY) Excellent quality modern units, (like wyse 50.s) 2xRS232, 20 function keys, 50 thro to 38,400 baud, menu driven port, screen, cursor, and keyboard setup menus (18 menu's). £29 REF NOV4.

PC PAL VGA TO TV CONVERTER Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and s/ware. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. SALE PRICE £25 REF SA34

EMERGENCY LIGHTING UNIT Complete unit with 2 double bulb floodlights, built in charger and auto switch. Fully cased. 6v 8AH lead acid req'd. (secondhand) £4 ref MAG4P11.

SWINGFIRE GUIDED MISSILE WIRE. 4,200 metre reel of ultra thin 4 core insulated cable, 28lbs breaking strain, less than 1mm thick! Ideal alarms, intercoms, fishing, dolls house's etc. SALE PRICE £13.99 ref EP51

ELECTRIC CAR WINDOW DE-ICERS Complete with cable, plug etc. SALE PRICE JUST £4.99 REF SA28

ASTEC SWITCHED MODE PSU BM41012 Gives +5 @ 3.75A, +12@ 1.5A, -12@ .4A. 230/110, cased, BM41012. £5.99 ref AUG6P3.

AUTO SUNCHARGER 155x300mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2watt SALE PRICE £8.99 REF SA25.

TOP QUALITY CENTRIFUGAL MAINS MOTORS SALE PRICE 2 FOR JUST £2.60 REF SA38

ECLATRON FLASH TUBE As used in police car flashing lights etc, full spec supplied, 60-100 flashes a min. SALE PRICE £6.99 REF SA15.

24v AC 96WATT Cased power supply. New. SALE PRICE JUST £9.99 REF SA40

MILITARY SPEC GEIGER COUNTERS Unused an straight from Her majesty's forces. SALE PRICE £44 REF SA18

MICRODRIVE STRIPPERS Small cased tape drives ideal for stripping, lots of useful goodies including a smart case, and lots of components. SALE PRICE JUST £4.99 FOR FIVE REF SA28

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit SALE PRICE JUST £4.99 REF SA27

RGB/CGA/EGA/TTL COLOUR MONITORS 12" In good condition. Back anodised metal case. SALE PRICE £49 REF SA16

SWITCHED MODE PSU ex equip, 60w+5v@5A, -5v@.5A, +12v@2A, -12v@.5A 120/220v cased 245x88x55mm IEC input socket £6.99 REF MAG7P1

PLUG IN ACORN PSU 19v AC 14w, £2.99 REF MAG3P10

POWER SUPPLY fully cased with mains and o/p leads 17v DC. 900mA output. Bargain price £5.99 ref MAG6P9

*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX
BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE
WITH ORDER PLUS £3 POST PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS
WELCOME (ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

TEL: 01273 203500
FAX 01273 323077

ACORN ARCHIMEDES PSU +5v @

4.4A. on/off sw uncased, selectable mains input, 145x100x45mm
SALE PRICE £4.99 REF SA1

13.8V 1.9A psu cased with leads. Just £9.99 REF MAG10P3

PPC MODEM CARDS. These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is £5 REF: MAG5P1

200 WATT INVERTER Converts 10-15v DC into either 110v or 240v AC. Fully cased 115x36x156mm, complete with heavy duty power lead, cigar plug, AC outlet socket Auto overload shutdown, auto short circuit shut down, auto input over voltage shutdown, auto input under voltage shut down (with audible alarm), auto temp control, unit shuts down if overheated and sounds audible alarm. Fused reversed polarity protected, output frequency within 2%, voltage within 10%. A well built unit at an keen price. Just £64.99 ref AUG65.

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

COMPUTER COMMUNICATIONS PACK Kit contains 100m of 8 core cable, 100 cable clips, 2 line drivers with RS232 interfaces and all connectors etc. Ideal low cost method of communicating between PC's over a long distance. Complete kit £8.99

ELECTRIC MOTOR KIT Comprehensive educational kit includes all you need to build an electric motor. £9.99 ref MAR10P4.

VIEWDATA SYSTEMS made by Phillips, complete with internal 1200/75 modem, keyboard, psu etc RGB and composite outputs, menu driven, autodialler etc. SALE PRICE £12.99 REF SA18

AIR RIFLES .22 As used by the Chinese army for training purposes, so there is a lot about! £39.95 Ref EF78. 500 pellets £4.50 ref EF80.

PLUG IN POWER SUPPLY SALE FROM £1.60 Plugs in to 13A socket with output lead. three types available, 9vdc 150mA £1.50 ref SA19, 9vdc 200mA £2.00 ref SA20, 6.5vdc 500mA £2 ref SA21.

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2

***FM CORDESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

***MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range up to 2 km in open country. Units measure 22x52x155mm. Including cases and earpieces 2xPP3 req'd. £30.00 pr. REF: MAG30

FUTURE PC POWER SUPPLIES These are 295x135x60mm, 4 drive connectors 1 mother board connector. 150watt, 12v fan, iec inlet and on/off switch. SALE PRICE £7.99 REF SA 22

***FM TRANSMITTER KIT** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever! why pay £700? or price is £15 REF: EF62 Transmits to any FM radio. (this is in kit form with full instructions.)

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

TALKING COINBOX STRIPPER COMPLETE WITH COINSLIP MECHANISMS originally made to retail at £79 each, these units are designed to convert an ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? SALE PRICE JUST £2.50 REF SA23

GAT AIR PISTOL PACK Complete with pistol, darts and pellets £12.95 Ref EF82 extra pellets (500) £4.50 ref EF80.

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. SALE PRICE £4.99 REF SA24

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30m for £12.99 ref MAG13P1

WE BUY SURPLUS STOCK FOR CASH FREE CATALOGUE

1995 100 PAGE CATALOGUE NOW
AVAILABLE, 45P STAMP OR FREE
WITH ORDER.

PORTABLE RADIATION DETECTOR

WITH NEW COMPUTER INTERFACE £59

A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30K eV to over 1.2M eV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. ref NOV18

Dry Battery tester

Most ETI readers could probably turn up, without much effort, several sizes of dry cell in unknown states of charge, and the proud owner of a multimeter will be familiar with requests to "just check these out". A meter can tell you when a battery is beyond hope, of course, but to determine whether the remaining charge is sufficient for a particular application requires something a little more. Equally, cells known to balk at the 500mA drain of a torch might give hours more service in a portable radio and, with the tester presented here, it only takes a moment to check.

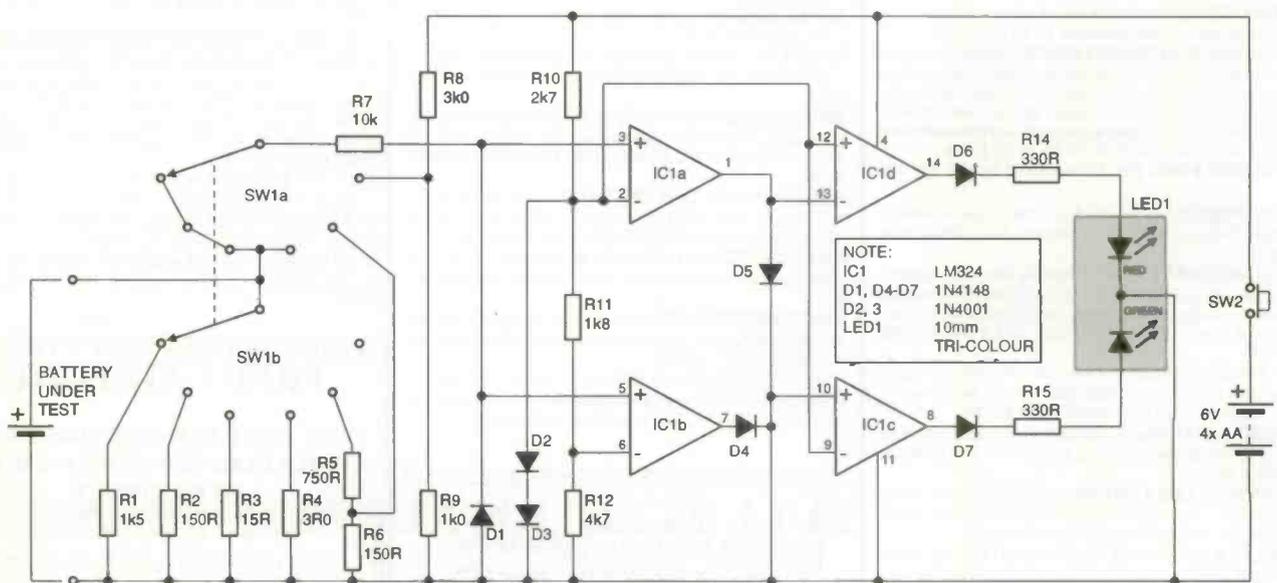


Fig. 1. Dry battery tester circuit



he common types of non-rechargeable batteries - zinc/carbon, zinc/chloride, and alkaline/manganese - give a nominal terminal voltage of 1.5V per cell when fresh. As a cell is discharged by its load, its internal impedance rises and this impedance forms a potential divider with the load, resulting in a reduced terminal voltage. Transplanting a partially discharged cell from a high to a low-drain application can therefore temporarily "restore" some extra terminal voltage, and allow some more life to be squeezed from what is nowadays a fairly expensive commodity. Of course, the environmental advantages of this approach are well known.

This design offers the following combinations of battery type and loading (suggestions are made of applications with similar loading):

**Table 1
Battery types**

Battery type	Voltage	Current loading	Application
1)	1.5V	1mA	alarm clocks
2)	1.5V	10mA	portable radio, remote control
3)	1.5V	100mA	personal stereo
4)	1.5V	500mA	torch, doorbell
5)	9V	10mA	multimeter, smoke alarm, etc.
6)			Internal 6V battery check

I have found that an alarm clock running off one 1.5V AA cell will work for in excess of a year on a battery that is no good for anything else.

Construction

Figure 2 shows the component overlay if the PCB is used, but experienced constructors should have no trouble laying it out on stripboard. As usual, take care with the polarities of the diodes and IC. The rotary switch is likely to be supplied in solder tag form, so it will be necessary to snip off the "eyes" leaving pins to fit through the board. The off-board wiring is also shown in Figure 2, and the whole circuit is a comfortable fit into an ABS box, type MB3, as long as the tags on SW2 are bent perpendicular to its body to avoid fouling the circuit board. Figure 3 shows the box drilling details used on the prototype, although there's plenty of scope for personal taste. Connections to the battery under test were made with extra-flexible wire terminated in standard test prods.

In use

Operation of the unit is straightforward. To see if a battery is sufficiently charged for a given application, use the rotary switch to select a similar loading to that which the battery will see when in use (refer to the above table for examples). Then, with the test prods held to the corresponding battery terminals, depress the push-button. A green light indicates that the battery can maintain its voltage while operating into the selected loading, and hence that it is suitable for the chosen application. A yellow light implies a borderline situation, usually meaning that the battery will operate into the selected loading for only a short period of time before becoming too deeply discharged to be suitable - this advance warning can hopefully be used to obtain fresh cells. Finally, red indicates that the battery under test is incapable of sustaining the selected loading, and is suitable only for lower drain applications or the dustbin.

The self-test position should be used occasionally, though with sporadic use the life of the internal batteries should be long. Suitable replacements can be auditioned using the IOMa test Position!

How It Works

The reference voltages to which that of the cell under test is compared are derived from a pair of forward biased power rectifiers, D2 and D3. At the low current fed to them by R10, the forward voltage of an 1N4001 is approximately 0.6V (a signal diode such as a 1N4148 is somewhat higher), giving an upper reference of 1.2V which is fed to comparator IC1a. R11 and R12 divide this down to a lower reference of 0.9V for the second comparator IC1b.

SW1 carries out the combined task of selecting both the

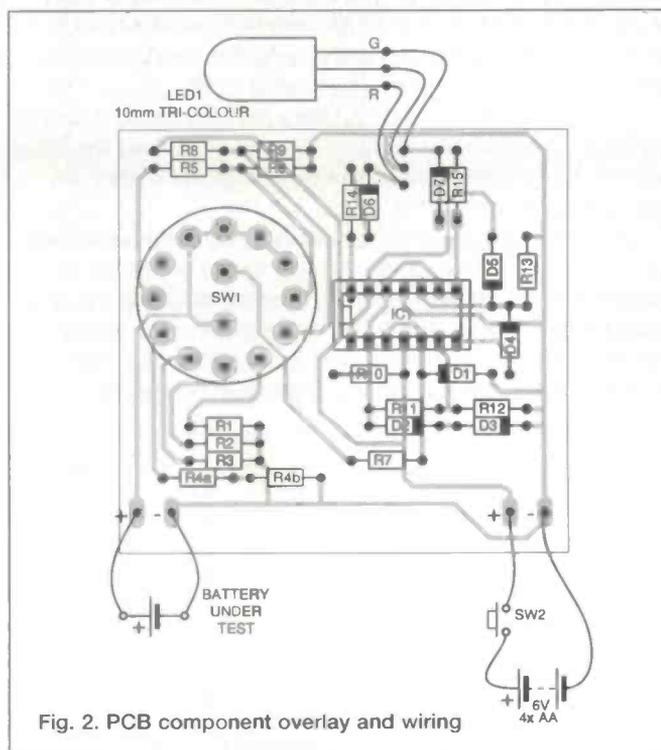


Fig. 2. PCB component overlay and wiring

type of cell to be tested and the loading presented to it. The first four positions are intended for 1.5V cells, and the loading ranges from 1mA (from a 1k5 load resistor, R1) to 500mA (with 3R0 of resistance from R4). In these positions, the cell voltage is fed directly - except for R7 and D1, which protect the tester against reverse cell connection - to the non inverting inputs of the two comparators. The fifth position is for 9V PP3 batteries, R5 and R6 providing 10mA of loading whilst also dividing a full scale input of 9V down to 1.5V for the comparators. With the switch in

the final position, the tester gives an indication of the state of its own batteries, with R8 and R9 dividing in a similar way.

To translate the comparator outputs - IC1b output goes high with a cell voltage exceeding 0.9V, IC1a when it exceeds 1.2V - to ones suitable for driving a tri-colour LED requires a bit of simple logic. Rather than use another IC, it seemed better to exploit the fact that a quad op-amp is often as cheap as a dual, and configure IC1c and IC1d as crude logic gates. The 1.2V reference is used to set their "logic threshold", and IC1d acts as an inverter while IC1c with D4, D5, and R13 is an OR gate. To get the LED to illuminate red for cell voltages less than 0.9V, amber for between 0.9V and 1.2V, and green for 1.2V or greater, the following truth table is needed:

Table 2
Truth table for different devices

IC1a O/P	IC1b O/P	red half LED	green half LED
0	0	1	0
0	1	1	1
1	0	0	1
1	1	0	1

Keen-eyed logicians will notice that the third row of the truth table is actually irrelevant, since a cell voltage cannot simultaneously register as less than 0.9V AND greater than 1.2V, and that this makes D5 similarly redundant. I have to own up to this oversight, and it is up to the constructor whether to save three pence by leaving it out!

The outputs of IC1c and IC1d drive the LED sections directly through current limiting resistors. D6 and D7 protect the LEDs while in the off-state from a reverse voltage of 6V (they are specified at 5V maximum).

SW2 provides power to the circuitry only while held down, preventing accidental battery drain while out of use. By its nature, the unit will only be used "every so often" so this is a useful measure. Note, however, that the cell under test is loaded even when the tester itself is off, so it is important not to leave one connected for any longer than necessary.

PARTS LIST

Resistors (0.25W, 5% unless otherwise stated)

- | | | | |
|---------|----------------|--------|------|
| ● R1 | 1K5 | R8 | 3K0 |
| ● R2,6 | 150R | R9 | 1K0 |
| ● R3 | 15R | R10 | 2K7 |
| ● R4 | 2 off IR5 0.6W | R11 | 1K8 |
| ● R5 | 750R | R12 | 4K7 |
| ● R7,13 | 10K | R14,15 | 330R |

Semiconductors

- IC1 LM324
- DI,4,5,6,7 IN4148
- D2,3 IN4001
- LED1 10mm Tricolour with clip

Switches

- Sw1 2-pole, 6-way rotary
- SW2 Miniature push-to-make (momentary action)

Miscellaneous

- Plastic box type MB3
- Red and black test prods
- Red and black extra-flexible wire
- 14 way IC Socket (optional)
- Knob for Switch (to personal taste)
- 4 off AA batteries plus plastic holders
- PCB or Stripboard welcome datacomp


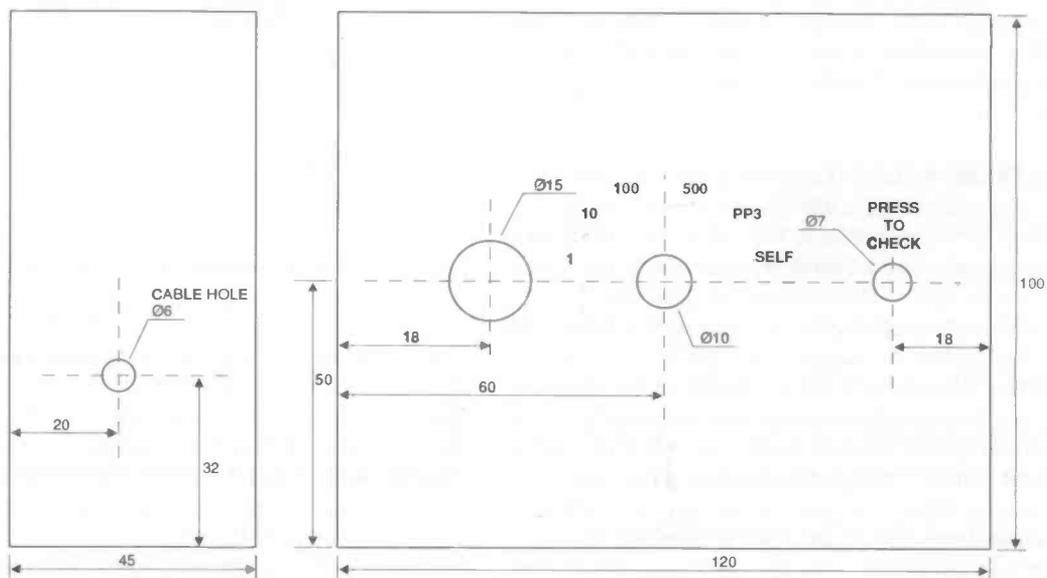


Fig. 3. Case construction and legend

CADPAK for Windows

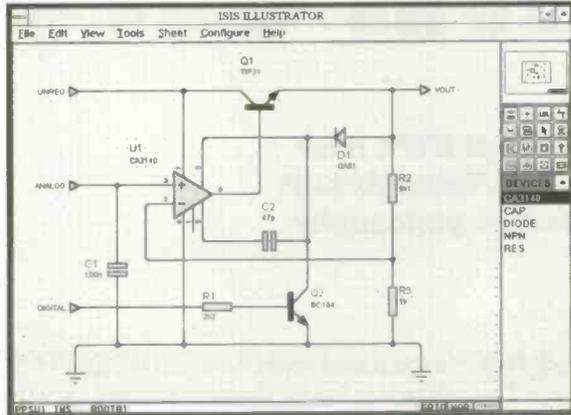CADPAK is especially suited to educational, hobby and small scale schematic and PCB design. CADPAK includes both schematic drawing and 32-bit PCB drafting tools but as an entry level product, there is no netlist link between them.




The schematic drawing module of CADPAK, ISIS ILLUSTRATOR, enables you to create circuit diagrams like the ones in the magazines.

- Runs under Windows 3.1 making full use of Windows features such as on-line help.
- Full control of appearance including line widths, fill styles, fonts, colours.
- Automatic wire routing & dot placement.
- Fully automatic annotator.
- Complete with device and comprehensive package libraries for both through hole and SMT parts.
- Advanced route editing allows deletion or modification of any section of track.
- Gerber, Excellon and DXF outputs as well as output via Windows drivers. Also includes Gerber viewer.
- Exports diagrams to other applications via the clipboard.
- CADPAK is also available for DOS.

CADPAK FOR WINDOWS £ 149
CADPAK FOR DOS £ 79

PROPAK for Windows

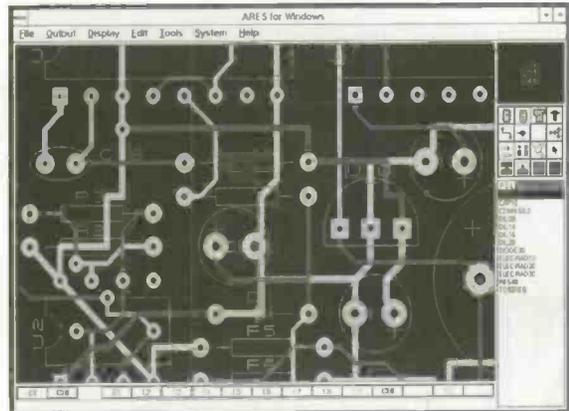PROPAK has all of the features in CADPAK plus netlist based integration, automatic power plane generation and a powerful auto-router. PROPAK includes enough schematic capture and PCB design functionality for all but the most demanding applications.



PROPAK's schematic drawing editor ISIS ILLUSTRATOR+ includes even more features than ISIS ILLUSTRATOR. PROPAK's 32-bit PCB design tool, ARES for Windows, is our most powerful and easy to use yet.

- Multi-sheet and hierarchical designs.
- Netlist link between modules guarantees consistency between schematic and PCB.
- Netlists are also compatible with SPICE-AGE and most other electronics CAD packages.
- Generates a full bill of materials.
- ASCII data import facility.
- Electrical rules and connectivity checkers.
- Ratsnest display with automatic update during placement and routing.
- Multi-strategy autorouter gives high completion rates.
- Power plane generator creates ground planes with ease.
- PROPAK is also available for DOS.

PROPAK FOR WINDOWS £ 495
PROPAK FOR DOS £ 395

Call or fax us today for a demo pack. Please state whether you would like a DOS or Windows pack.

Prices exclude postage (£5 for UK) and VAT. ISIS ILLUSTRATOR and ARES for Windows are also available separately. All manufacturers trademarks acknowledged.

abcenter

E l e c t r o n i c s
 53-55 Main St. Grassington, N. Yorks. BD23 5AA
 Tel: 01756 753440 Fax: 01756 752857

The ETI Basic microcontroller

In this introductory look at ETI's new autumn premiere project, Robin Abbott looks at the overall design philosophy

Next month ETI will be sold with a free PCB which is specially designed for the ETI Basic microcontroller. This is a major new project starting next month concerning a BASIC language for use with PICs. In this brief article we will take a look at the circuit of the PCB and how the peripherals may be programmed. The PCB will also be useful to anyone designing with 18 pin PIC devices since it can act as a PIC prototyping board. It will hold any 18pin PIC with crystal oscillator, a 5V power regulator, a low cost RS232 serial interface and an I2C interface for 8 pin devices. I/O access is provided through a 16 pin IC socket.

Figure 1 shows the circuit diagram of the PCB. IC3 provides the power supply, the 78L05 may be used for lower consumption projects and the 7805 can be used for projects of up to 1A consumption.

IC2 is the I2C device. The pin out shown is for EEPROM devices. However, most I2C devices have the same pinout. Operation of I2C devices is described in detail below. R1 and R2 pull up the data and clock lines used on the I2C interface. Link 1 is provided for use with the BASIC project. For normal operation, the link is left unconnected.

IC1 is the PIC. Any 18 pin device may be used - 16C54, 56, 58, 71, 84 etc. The lower 4 bits of port A are used for the I2C interface, and for the external serial interface. These bits are not available for use directly by the application- however, the RTCC input (which forms the RA4 input of the PIC16C71 and PIC16C84) can be freely used. TR1 and its associated circuitry form a power down reset circuit which clamps the clear input of the PIC to 0V when power is removed and drops below 4V. Without this, the PIC may write invalid values to the serial port or I2C device when power is removed.

The oscillator circuitry around pins 15 and 16 of the PIC is based on crystal or ceramic resonator devices. The frequency of the oscillator may be selected between 4MHz and 20MHz to allow the timing of the EEPROM and serial interfaces to operate successfully; the actual frequency is selected at compile time. Rs is shorted out by a copper track on the PCB, which should be cut if Rs is to be used with certain high frequency crystals.

The serial interface is provided as standard. It may be used with any serial interface which provides standard RS232 levels

such as a PC; the output levels below 0v are taken from the input. The interface at the PIC is inactive high - i.e. when the interface is idle the input and output of the PIC is held at +5V. The start bit is signalled by a low going pulse followed by the 8 data bits.

The serial interface is a simple (and cheap) circuit which works well in practice with half duplex or full duplex links. D201 ensures that C201 can store the negative voltage which is normally present on the inactive input line, filters it, and uses it as a negative supply for the signal driven from the module. In testing, the average voltage on pin 2 of PL101 stayed below -3v which is sufficient to maintain RS232 levels although this will depend on the input impedance of the interface being driven. This circuit worked well with all PCs with which it was tested.

The I/O support from the module is provided through PL1. This is a 16 pin IC socket which should be connected to the application circuit using 16-way IDC cable with a 16 pin DIL IDC header. The pin out of the socket is shown in figure 2.

Using the serial port

I have found that a serial port is very useful when developing PIC applications, mainly as a debugging tool, even if the final project is to be a stand-alone system. It is often convenient when some trigger event occurs to print a value to the serial port which can then be read using a terminal emulator program on the host PC. Serial port driving routines take very little code on a PIC. Figure 3 shows a simple 9600bps serial driver for use with 16C5x or 16C71/84 devices and the general purpose PCB with a 3.58MHz crystal. This example was taken from the PIC Programmer project recently featured in ETI. It occupies only 41 words of program space and needs only three bytes of memory, two of which are temporary variables which can be used elsewhere in the program.

To use the receiver, simply call RXCHAR which will wait for the next incoming byte and stores it in RXSER; on the 71/84 devices, the byte will also be returned in W. To use the transmitter save the byte to be transmitted in RXSER and call TXCHAR. As an example the program below is a complete 16c84 program which uses the code in Fig 3 to read every byte received on the serial port and send it back twice.

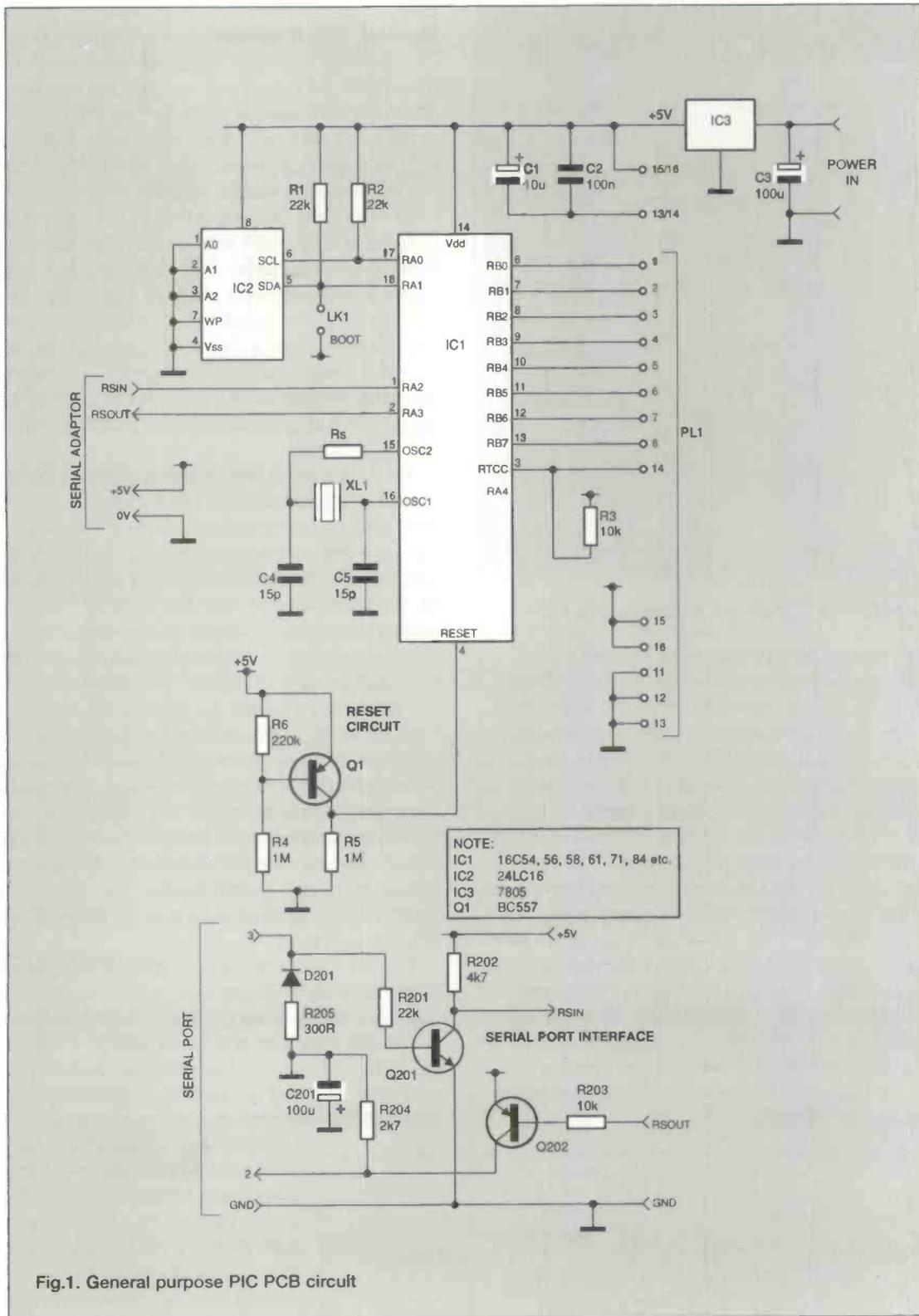


Fig.1. General purpose PIC PCB circuit

```
SAVEBYTE EQU .15
ORG 0
```

```
MOVLW 0F7H ; SET SERIAL OUTPUT TO
DRIVE
TRISA
CLRW
OPTION
LOOP CALL RXCHAR ; RECEIVE CHAR
MOVWF SAVEBYTE ; SAVE IT
CALL TXCHAR ; TRANSMIT
MOVWF SAVEBYTE ; STORE IT
MOVWF RXSER ; BACK IN RXSER
```

```
CALL TXCHAR ; TRANSMIT AGAIN
GOTO LOOP ; AND GO AGAIN
```

Interrupt driven serial port

The code shown above is extremely simple, and will not transmit and receive simultaneously. Any incoming bytes during times when the processor is busy will be missed or misread. To correct this, Figure 8 shows the code for an advanced interrupt driven serial port. The application shown receives information on the serial port and sends it straight back at a full rate of 300bps with no flow control while the processor is free to perform other tasks. This is only available

Fig 2

Socket Pin	
1	Port B bit 0
2	Port B bit 1
3	Port B bit 2
4	Port B bit 3
5	Port B bit 4
6	Port B bit 5
7	Port B bit 6
8	Port B bit 7
9	Not Used
10	Not Used
11	Ground
12	Ground
13	Ground
14	RTCC/RA4, pulled up with 10K resistor
15	+5V
16	+5V

Fig.2. Pin out of General Purpose PIC PCB control socket

for the 16C71/84 devices as it uses timer interrupts.

The serial port operates at 300bps with a crystal of 4MHz, and would operate at 1200 BPS at 20MHz. The serial port operates in full duplex mode and can receive and transmit information simultaneously and at the same time as the application program is running, using about 20% of the processor time with bytes being sent and received continuously, a lot less when the port is idle. It uses 63 words of program memory in the interrupt routine, and 11 bytes of RAM (although this could be cut down by making memory use more efficient at the cost of interrupt processing time).

Examine the example for the initialisation code which sets RTCC to operate at the 1MHz clock and to interrupt on overflow. To transmit a byte, write the byte to TXVAL, and execute the instruction BCF FLAGS, TXFREE. When the byte has been transmitted the TXFREE bit of register FLAGS will be set back to 1. When a byte has been received then the RECEIVED bit of register FLAGS will be set and the received byte will be found in RXBYTE.

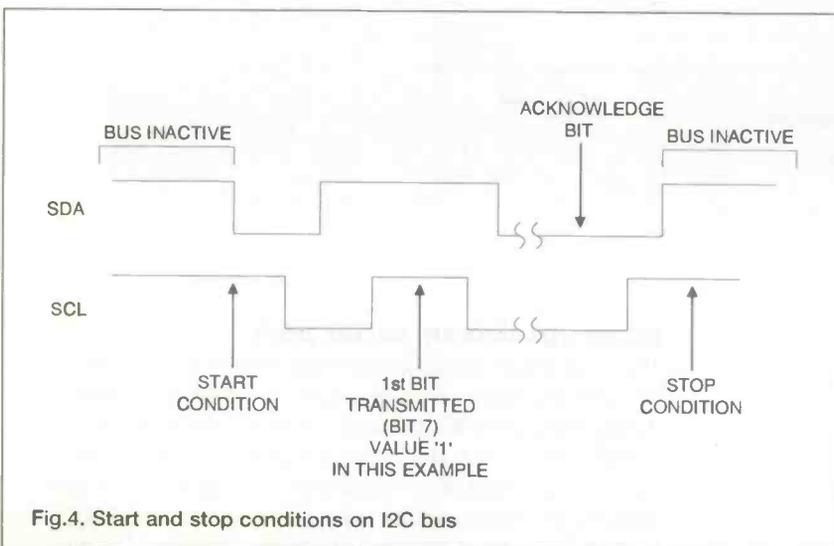


Fig.4. Start and stop conditions on I2C bus

Use of I²C devices

The operation of the I²C bus is explained here - it is used for a serial EEPROM in the BASIC project and may also be used for other peripheral devices which can be controlled from the module. We will look in detail at driving a 24LC16 serial EEPROM which provides a 2Kx8 EEPROM function.

The protocol is serial in nature, the SDA line is the data interface and the SCL line is the clock. In normal operation, both the SCL and SDA lines are high. The SDA line is only allowed to change when the SCL line is low. However, the exception to this is when a start or stop condition is signalled. A start condition is signalled by the SDA line dropping whilst the SCL line is high, a stop condition is signalled by the SDA line rising whilst the SCL line is high. All commands and data operations are preceded by a start condition, and transfers are ended with a stop condition. Fig 4 shows the timing for a start and stop condition.

An I²C bus has a master device (in this case, the PIC) which controls all transfers on the bus by using the SCL and SDA lines. Data is transferred on the SDA line when the SCL line is high, and may change when the SCL line is low. Data is transferred 8 bits at a time, followed by a single acknowledge bit. Data is transferred most significant bit first. The acknowledge bit is sent either by the master or the slave device depending on the transfer, and is low for an acknowledgement, or high for no acknowledgement.

Fig 5 shows a transfer for reading the current address of a 24LC16 device. In this cast the first byte (A1 hex) is the command for reading the byte at the current address. There is no acknowledgement of the transfer and the master generates a stop condition at the end of the transfer. If the master device acknowledges the transfer then the EEPROM will continue to output bytes from the EEPROM incrementing the address counter at the end of each transfer. This is the mode used by Control BASIC for rapid reading of the EEPROM when a program is running.

Figure 7 shows the full code for interfacing to a 24LC16 (or similar serial EEPROM devices). It uses four temporary registers - temp4 to temp7. Port A must be set on initialisation to drive the serial port and the I²C SCL line. Call the routine EEREADRAND with a 2 byte address to which FSR points to read the contents of any address in EEPROM. Calling EEREADNEXT will read consecutive addresses in the EEPROM, and is much faster than calls to EEREADRAND. In both cases the read value is written to temp7, and to the W register. To write a byte put the value in the TOS register, point FSR to a 2 byte address and call EEWRITE, which takes a minimum of 10ms. Consult individual device data sheets for the control bytes and modes for I²C devices. In a later article, a control program for interfacing to I²C devices will be shown.

PIC BASIC

Next month, ETI will be starting a new series which allows developers to program PIC devices in BASIC. It is based on the general purpose PCB and uses 16C56, 16C71, or 16C84 devices, together with an EEPROM to hold the program. The BASIC language allows programs to be developed and tested

much more rapidly than programs using PIC assembler. The EEPROM may be up to 8K in size, allowing programs of up to about 1,000 lines of BASIC code to be developed, although smaller and cheaper EEPROMS may be used. The language saves memory by allowing variables to be anywhere between 1 and 16 bits in length. Versions are also available for the larger PIC devices in the series making use of the extended memory and peripherals on these devices. The system is based on the Windows development system which allows multiple files to be edited, assembled, and linked, and for programs to be downloaded and tested. Finally, an autoboot facility allows the module to automatically run programs when it is powered up allowing stand-alone systems to be developed.

```

temp EQU tosh+1 ; Two
temporary files
temp2 porta EQU 5 ;
Address of port A
rx EQU 2 ; Bit on port A used for
receiving
tx EQU 3 ; Bit
on port A used for
transmitting
rxser EQU .12 ; Holds byte
received or transmitted
intindex EQU .13 ; Temporary
variable
intindex1 EQU .14 ; Temporary
variable
;
; This is the receive handler - used for
; reception of data on the serial port
at9600bps
; at 9600bps and clock=3.58MHz then 1 bit=93
; instructions, 1/2bit=47 instructions
;
; Return character in rxser and w
;
rxchar btfsc porta,rx ; 1/2
average time out of here = 2T
goto rxchar ; 2 Wait for start bit

movlw 8 ; 1 pick up 8 bits
movwf intindex ; 1
call delay46 ; 48 delay to just
after middle of start bit
; so that
first sample is 1.5 bits after start

rxloop call delay83; 85
nop ; 1
bcf status,c ; 1 sample incoming
bit
btfsc porta,rx ; 1/2
bsf status,c ; 1
rrf rxser,f ; 1 rotate in data,
LSB arrives first
decfsz intindex ; 1
goto rxloop ; 2
movfw rxser
waitend btfss porta,rx ; now wait
for end of last bit if it was 0.
goto waitend
return

; Transmit single character in W
;
txchar movlw 9 ; 9 bits in
total send stop afterwards
movwf intindex
bcf status,c ; first bit is start bit

txloop btfss status,c ; 1/2
Set output bit

```

```

bct porta,tx ; 1
btfsc status,c ; 1/2
bsf porta,tx ; 1
call delay83 ; 85
rrf txwork,f ; 1
decfsz intindex ; 1
goto txloop ; 2
bsf porta,tx ; 1
call delay83 ; 85 ; should be long
enough for stop bit

return ; 2
; delay routines for serial port stuff

delay46 movlw .14 ; 1 loop
time=3.(n-1)+7
delex movwf intindex1 ; 1
d34loop decfsz intindex1 ; 1/2
goto d34loop ; 2
nop ; 1
return ; 2

delay83 movlw .25 ; 1 loop
time=3.(n-1)+11
nop ; 1
nop ; 1
goto delex ; 2

```

Fig.3. A simple 9600bps serial driver for use with the 16C5x or 16C71/84 devices and the general purpose PCB with a 4MHz crystal.

```

flags EQU FIRST ; Flags byte (see below)
cpc EQU flags+1 ; Program
counter lower
cpchEQU cpc+1 ; PC upper
sp EQU cpch+1 ; stack
pointer
tos EQU sp+1 ; Useful storage for
Top of Stack
tosheQU tosh+1
tempEQU tosh+1 ; Two
temporary files
temp2 EQU temp+1
temp3 EQU temp2+1
temp4 EQU temp3+1
temp5 EQU temp4+1
temp6 EQU temp5+1
temp7 EQU temp6+1
temp8 EQU temp7+1 ; Available
for use during program-only used by PC control
temp9 EQU temp8+1 ; Available
for use during program-only used by PC control
temp10 EQU temp9+1

lastEQU temp7+1

; Bits in flags byte

rfshadd EQU 0 ; Set to
indicate EEPROM
address need refreshing
int EQU 1 ; An interrupt
occurred

rfshaddv EQU 1
intv EQU 2


;
; Communications ports
;

picio EQU 5

scl EQU 0 ; Serial clock, port
a, bit
sda EQU 1 ; serial data
rsin EQU 2
rsout EQU 3

sclveQU 1 ; values of bits
sdaveQU 2
rsinv EQU 4

```

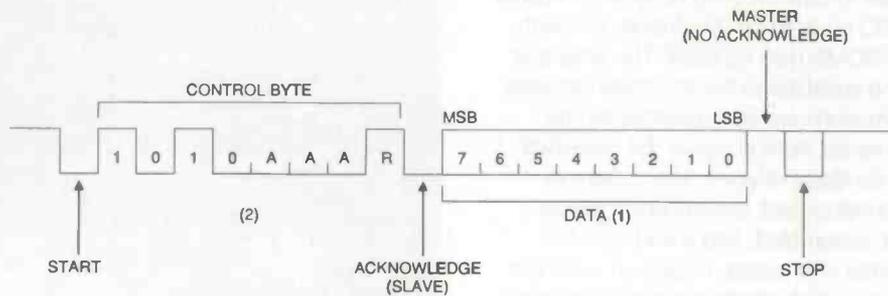

- NOTES: 1 DATA IS SENT FROM SLAVE, MASTER MUST TRI-STATE SDA DURING THIS PERIOD
 2 AAA IS THE ADDRESS OF THE I²C DEVICE, HOWEVER FOR SOME DEVICES (EG. 24LC16) IT IS THE UPPER ADDRESS BITS OF THE MEMORY BEING ADDRESSED

Fig.5. Example I²C bus read

```

rsoutv          EQU 8
;
; 12 bit addressing model
;
; Read a random byte from EEPROM - address in
FSR return in temp7 & w

eereadrand call eewrtadd ; set write address
bsf picio,sda
bsf picio,scl ; drive clock high
movlw 5
movwf temp6 ; ack & start bit
incf fsr ; address upper
clrc ; move address left into
control

rlf 0,w ; address upper
iorlw 0A1h ; control byte
call weeprom0w

; Read next byte from EEPROM return in temp7 &
w

eereadnext movlw 0ch
eerdgo movwf temp6 ; ack, no
start or stop
movlw ~(sclv|rsoutv) ; Now read from data
line

tris picio
call weeprom0w ; read byte, generate
STOP
retee movfw temp7
return

; Write a byte to EEPROM, address in FSR, byte
in TOS

eewrite call eewrtadd
movlw 6
movwf temp6 ; ack & stop bit
movfw tos
goto weeprom0w

; Write address part of read or write algorithm
eewrtadd movlw 0ah
call eerdgo ; Read a byte with stop
bit set to end seq read
movlw 5
movwf temp6 ; ack & start bit
incf fsr ; address upper
clrc ; move address left into
control

rlf 0,w ; address upper
iorlw 0A0 ; control byte
call weeprom0w ; write control byte
decf temp6 ; Set temp6 to 4 - ack
low from eeprom
decf fsr ; MUST LEAVE FSR
  
```

```

POINTING AT LOWER ADDRESS!
movfw 0 ; address lower

; Write/read 8 bits to EEPROM, check ack
; Call with scl driving
; sda is set to read for a read, and drive for
; write
; temp4 is index
; temp5 is the data to write
; temp6 bit 0 indicates to generate start
; temp6 bit 1 indicates to generate stop
; temp6 bit 2 indicates to generate ack if set
; (nack if reset)
; temp6 bit 3 indicates to read
; temp7 reads input byte
; Ends driving sda & scl

weeprom0w movwf temp5
weeprom9 movlw 8
movwf temp4
btfss temp6,0 ; check startbit
goto nostart
bcf picio,sda ; start bit drops data
nostart bcf picio,scl ; drop clock
btfsc temp6,3 ; leap forward if read
goto rdeelop

;
wrteelop bcf picio,sda ;
rlf temp5 ; now get correct port
bit

skpnc ;
bsf picio,sda ;
bsf picio,scl ; clock now high
bcf picio,scl ; clock low again
decfsz temp4 ; and loop
goto wrteelop
goto endthis

;
rdeelop bsf picio,scl; clock now high
clrc ;
btfsc picio,sda ; now read input
setc ;
rlf temp7 ; Read in bit
bcf picio,scl ; clock low again
decfsz temp4 ; and loop
goto rdeelop

;
endthis bcf picio,sda; 1 Ack low or high ?
(low if eeprom is acking)
btfss temp6,2 ;
bsf picio,sda
movlw ~(sclv|rsoutv|sdav) ; Drive scl
& sda
tris picio
bsf picio,scl ; 1 Send a clock
bcf picio,scl
  
```

```

btfss temp6,1      ; 1/2 stop bit ?
return             ; 1 If no stop
                  bit return with scl low

bcf picio,sda
bsf picio,scl     ; otherwise clock
                  high
bsf picio,sda     ; If stop bit return
                  driving high on scl/sda
return

```

Fig.7. Code for interfacing to a 24LC16

```

include "16c84.equ"
rx equ 2           ; Bit for receiving
tx equ 3           ; Bit for transmitting
seropt equ 8       ; options reg
saveintst equ .12  ; save
                  status in intrt
saveintw equ .13   ; saves w in
                  interrupt
txintcnt equ .14   ; Interrupt
                  counter
txcnt equ .15      ; Transmit
                  bit counter
txval equ .16      ; transmitted
                  byte
rxval equ .17      ; Receiving
                  work space
rxintcnt equ .18   ; Interrupt
                  counter
rxcnt equ .19      ; receiving
                  bit count
rxbyte equ .20     ; received
                  byte
flags equ .21
txfree equ 0       ; 1 if tx
                  can start
txgoequ 1          ; 1 when transmitting
rxgoequ 2          ; 1 when receiving
received equ 3     ; 1 when
                  byte received

ORG 0
goto start
;
; Interrupt handler
;
org 4
movwf saveintw    ; save w and status
swapf saveintw,f
swapf status,w
movwf saveintst

decfsz txintcnt
goto chkrx
movlw .13
movwf txintcnt    ; 13 interrupts/bit
btfss flags,txgo
goto chktxst
tstf txcnt       ; stop bit over
skpz             ; so clear flag
goto chktx
bcf flags,txgo

chktxst
btfsc flags,txfree ; tx request ?
goto chkrx
bsf flags,txgo     ; We are sending
movlw 9           ; 9 bits in total
movwf txcnt
bcf porta,tx      ; start bit
goto chkrx

chktx             decfsz txcnt; flag
transmitting
goto txlop
bsf flags,txfree  ; Free for tx      goto

```

```

setop             ; stop bit high
txlop rrf txval   ;
btfss status,c   ; Set output bit
bcf porta,tx     ;
btfsc status,c   ;
setop            bsf porta,tx;
;
; Receiving interrupt check
;
chkrx btfsc flags,rxgo; receiving ?
goto rxing
btfsc porta,rx   ; start bit ?
goto endint
movlw 8          ; 8 bits
movwf rxcnt
movwf rxcnt      ; delay to 1/2 way
movlw .19       ; thru 1st bit
movwf rxintcnt
bsf flags,rxgo  ; show receiving
goto endint

rxing            decfsz rxintcnt ;
check timer count
goto endint
tstf rxcnt      ; end of byte ?
skpz
goto nxtbit
bcf flags,rxgo  ; Stop bit
goto endint
nxtbit movlw .13
movwf rxintcnt
bcf status,c    ; sample input bit
btfsc porta,rx ;
bsf status,c    ;
rrf rxval       ; move to rxval
decfsz rxcnt    ;
goto endint
movfw rxval     ; save rxid byte.
movwf rxbyte
bsf flags,received ; Show received
                  byte
;
; Interrupt over - restore flags & w
;

endint          movlw 0f8h ; clear
flags
andwf intcon,f
swapf saveintst,w
movwf status
swapf saveintw,w ;

restore w
retfie
; Start up code and test routine
start          movlw 0ffh ;
clear port a
movwf porta
movlw 0f7h    ; set drive
tris porta
movlw seropt ; option reg.
option
bsf status,rp0
movlw gievrtrtiev ; enable interrupts
movwf intcon
bcf status,rp0

movlw .13     ; Initial transmit
movwf txintcnt ; states
clr f txcnt
clr f flags
bsf flags,txfree ; free to transmit
;
; Test - look for bytes and send back
;
loopbtfss flags,received ; Byte rxid ?
goto loop
bcf flags,received ; clear flag
movfw rxbyte     ; send it back
movwf txval
bcf flags,txfree ; request tx
goto loop

end

```

Fig.8. Code for an advanced interrupt driven serial port

TRANSISTORS + ICS + SEMICONDUCTORS



Very Interesting Catalogue

- RESISTORS + CAPACITORS + INDUCTORS
- SURVEILLANCE + SECURITY + SECURITY
- PLUGS + SOCKETS + LEADS + CONNECTORS
- TV & VIDEO SPARES (INC. VIDEO HEADS)
- HIFI + DISCO + HIFI GADGETS + SPEAKERS
- AUDIOPHILE COMPONENTS (inc capacitors)
- IN CAR AUDIO + SPEAKERS (inc bass tubes)
- COMPUTER ACCESORIES + BOARDS
- TOOLS + TEST EQUIPMENT + BENCHWARE

& much much more (over 10,000 lines).
 send today for the very interesting catalogue.
 Pay by PO, cheque, credit card or tape coins to paper.

Please send me.....copies of the 1995 Cricklewood Catalogue.
 I enclose £2.50 per copy (UK & Europe) £5 overseas.

Name.....
 Address.....

Please charge my credit card. No.....
 Expiry Date..... Tel. No..... ETI

Cricklewood Electronics Ltd, 40-42 Cricklewood Broadway,
 London NW2 3ET. Tel: 0181-450 0995 Fax: 0181-208 1441

JCG Electronic projects

PO BOX HP79 WOODHOUSE STREET
 HEADINGLEY LEEDS LS6 3XN

RADIO KITS/TRANSMITTERS/REMOTE CONTROL

MICRO FM (a) 1KM range transmitter. 80 - 100Mhz preset. received on any FM radio. Includes FET mic.	£6.95
MICRO FM (b) Variable mc sensitivity. Tuneable 80 - 110 Mhz. 1KM range 2x3.5cm PCB.	£7.95
ULTRA MINI FM 200m range. BC - 100 Mhz. runs off watch battery (inc) only 1 x 2cm PCB.	£8.95
FM TRACKER Transmits a constant tone for direction finding, tracking etc. 80 - 110 Mhz	£8.50
FM RECEIVER (a) Small high quality FM receiver. Covers standard FM broadcast bands Will drive headphones (not inc)	£10.90
FM RECEIVER (b) As (a) but with 3 watt audio power amp and tuning LED.	£13.50
CRYSTAL RADIO Great introduction to radio electronics. Includes tuner, ferrite aerial and earphone	£7.50
AM RADIO Single chip radio for use with headphones. (not inc) or an external amplifier.	£8.90
I.R. REMOTE CONTROL - Single channel for lights, Garage doors etc.	
TRANSMITTER - £6.95 RECEIVER (with mains relay)	£15.45
MICRO TRANSMITTER GUIDE - Packed with useful circuits and info - How to build surveillance devices, short range TX's etc.	Only £3.95

PREAMPS/AUDIO

AU10 GENERAL PURPOSE PREAMP for audio applications where low noise isn't a priority - guitar amps etc. 9-15v, variable gain and high output.	£4.20
AU11 LOW NOISE PREAMP for more critical input stages. Ideal for mixers etc. 9 - 15v, variable gain.	£4.50
AU12 ULTRA LOW NOISE PREAMP. Professional standard. Uses an NE5534 IC. 9 - 15v, variable gain	£5.99
AU13 SMALL SIGNAL. Single FET preamp for boosting low output piezo pickups or acoustic transducers	£3.90
AU14 SMALL SIG + EQ. An AU13 with a simple three band passive EQ circuit. Designed for piezo pu's	£6.90
AU15 SINGLE TRANSISTOR. low noise preamp for electric guitars etc. Preset gain. BC184L.	£3.90
AU16 ACTIVE TONE CONTROL. 12dB cut and boost, bass and treble with preamp. Includes pots.	£8.95
AU17 7 BAND EQ board for graphic/equalizer control applications. Pots included	£12.95
AU18 NOISE REDUCTION SYSTEM. High quality dynamic noise gate with variable effect and level.	£15.95
AU19 ANALOGUE DELAY. Bucket brigade delay line. Variable clock frequency for producing double track and echo effects etc. Delay times from 2.5 to 51ms.	£18.50
AU20 CONTROL OSC. Low frequency osc to modulate the analogue delay line for flanging, chorus and other effects.	£8.50
AU21/21 DIGITAL DELAYS. 200 and 800ms digital delay lines with 10 bit a/d conversion. Variable sample rate from 25 - 50Khz variable delay time. 200ms - £20.40 800ms - £24.95	

POWER AMPS

P2 15WATT General purpose upgrade. Uses TDA2030. 24v single rail supply with heat sink	£9.95
P3 40 WATT High quality poweramp for compact disc and other demanding applications. Switch on mute, thermal/short protection. Distortion less than 0.003% 27v + with heat sink	£15.50
P4 150 WATT Rugged and powerful MOSFET design. excellent response and reliability 50v + with heat sink. Ideal for guitar amps. PA or sound system.	£22.95

GUITAR/INSTRUMENT KITS

Most of the kits in this section are designed to be small enough to be installed inside Instruments, but can easily be adapted for other applications such as effects pedals.

TL10 VOLUME BOOSTER. Compact circuit for low output pickups	£3.95
TL11 OVERDUE. Will provide enough clean output to overdrive any guitar amp. Variable	£7.95
TL12 DISTORTION. Smooth distortion and sustain. Variable.	£7.95
TL20 HI BOOST. Variable hi frequency booster for guitar or bass.	£6.50
TL21 LOW BOOST. Variable low frequency booster for guitar or bass	£6.50
TL22 MID BOOST. Variable mid range booster for guitar and bass. Can also produce Wah Wah effects.	£6.75
TL23 GUITAR ACTIVE TONE. Fully active tone controls for guitar. Includes control pots	£12.95
TL24 BASS ACTIVE TONE. As above but for bass guitar	£12.95
TL25 HALL EFFECT WAH WAH. Tunable band pass filter controlled by the proximity of a magnet to a hall effect sensor. Makes for a smooth filter sweep without the noise associated with potentiometer arrangements. (pedal assembly not included)	£10.75
TL26 HALL EFFECT VOLUME. Circuitry for making a high quality volume pedal (pedal assembly not included)	£9.50

SEND FOR A LIST OF OUR FULL RANGE OF RADIO AND AUDIO KITS. ALL KITS
 COME COMPLETE WITH PRE DRILLED P.C.B.'S, HIGH SPEC COMPONENTS AND
 FULL INSTRUCTIONS - MAIL ORDER ONLY - MAKE CHEQUES/P.O.s PAYABLE TO:
 J.C.G. PRICES INCLUDE POSTAGE & PACKING

PCB Designer

For Windows 3.1

Runs on any PC running Windows 3.1 in standard or
 enhanced mode with 2MB RAM
 Will work with any Windows supported printer and monitor



Looking for the price?
 It's just £49.00 all inclusive!
 ...no VAT...no postage...
 ...no additional charges for
 overseas orders.
 Dealers and distributors
 wanted.

- ✓ Produce Single or Double sided PCBs.
- ✓ Print out to any Windows supported printer.
- ✓ Toolbar for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pad, track & IC sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.
- ✓ Prints at the resolution of your printer - much higher than the screen shot shown here.

Internet
 A working demo is available via anonymous FTP from
<ftp.demon.co.uk> as /pub/ibmpc/windows/pcbdemo/pcbdemo.zip
 e-mail enquiries can be addressed to orders@niche.demon.co.uk

Niche Software (UK)

22 Tavistock Drive, Belmont, Hereford, HR2 7XN.

Phone (01432) 355 414

POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE (A4) S.A.E. 60p STAMPED FOR CATALOGUE *

OMP MOS-FET POWER AMPLIFIERS HIGH POWER. TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W) MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★ Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" x H3 1/2" (2U) x D11"
MXF400 W19" x H5 1/2" (3U) x D12"
MXF600 W19" x H5 1/2" (3U) x D13"
MXF900 W19" x H5 1/2" (3U) x D14 1/2"

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH



OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE ★ ECHO & SOUND EFFECTS★

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.




Price £144.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series. **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**

TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
TYPE 'C' (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

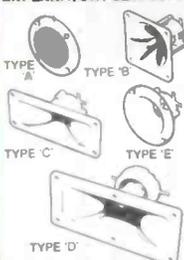


OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

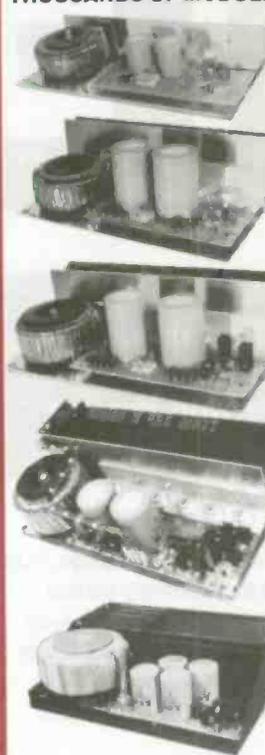THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm. PRICE £40.85 + £3.50 P&P

OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm. PRICE £64.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm. PRICE £81.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm. PRICE £132.85 + £5.00 P&P

OMP/MF 1000 Mos-Fet Output power 1000 watts R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm. PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.

LOUDSPEAKERS

LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.



McKenzie and Fane Loudspeakers are also available.

EMINENCE:- INSTRUMENTS, P.A., DISCO, ETC

ALL EMINENCE UNITS 8 OHMS IMPEDANCE
8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £32.71 + £2.00 P&P
RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB
10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. PRICE £33.74 + £2.50 P&P
RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB
10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. PRICE £43.47 + £2.50 P&P
RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB
12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. PRICE £35.64 + £3.50 P&P
RES. FREQ. 49Hz, FREQ. RESP. TO 3KHz, SENS 100dB
12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB. PRICE £36.67 + £3.50 P&P
12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. PRICE £46.71 + £3.50 P&P
RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 98dB
12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. PRICE £70.19 + £3.50 P&P
RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB
15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. PRICE £50.72 + £4.00 P&P
RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB
15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. PRICE £73.34 + £4.00 P&P
RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB.

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)
BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND
8" 50watt EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz, SENS 97dB
10" 50watt EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB
10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB
12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P
RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB
FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND
5 1/2" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB
6" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P
RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB
8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 99dB
10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

ibf FLIGHT CASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.



POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz

ibf C 12-100WATTS (100dB) PRICE £159.00 PER PAIR
ibf D 12-200WATTS (100dB) PRICE £175.00 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR

OPTIONAL STANDS PRICE PER PAIR £49.00
Delivery £6.00 per pair

IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

THREE SUPER HIGH POWER CAR STEREO BOOSTER AMPLIFIERS

150 WATTS (75 + 75) Stereo, 150W Bridged Mono
250 WATTS (125 + 125) Stereo, 250W Bridged Mono
400 WATTS (200 + 200) Stereo, 400W Bridged Mono
ALL POWERS INTO 4 OHMS
Features:
★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P



PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHERN-ON-SEA, ESSEX. SS2 6TR

Tel. 01702 - 527572 Fax: 01702-420243

POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.



"HELLO

"Hello Mum" - this is just one of the printable messages that have been illuminated in the following project


A couple of years ago I was asked to design, build and supply a sign for a local primary school which would flash "Merry Christmas" in a way that would attract attention, just in case any of the parents had not been aware of the impending season of "I want". It was felt that flashing lights would add a Christmassy touch.

Recently, this project has been re-vamped to allow a class of fifth form secondary students to participate in a class project to build a message board display that would allow a message to be changed easily and that would bring into play several of the skills learnt in CDT lessons; these were to include electronics, woodwork, metalwork, corriflute construction graphics, planning delegation etc. The spec stated that the message board had to run independently of any external computers etc but could have a mains supply - only after the expense of rechargeable batteries had ruled their use out.

Three separate new PCBs were laid, the original having

been built on vero board or strip board. The principle is that the display consists of 15 little boxes side by side in one larger box; each of the little boxes has an oblong cut out in the front and contains a Christmas tree lightbulb in its holder. The message is made up on transparent film and placed in front of these boxes and behind a diffusion screen (or nobbly bit of plastic to you and me). This has the effect of hiding the message until the light bulbs illuminate it from the rear. One of two methods can be used here - either to use a black character on a clear background or a clear letter on a blackened background.


The display scans from left to right building up the message one letter at a time. When a letter illuminates it stays on until the sequence has finished i.e. all 15 lights are on. After a delay it then blanks out and the message now builds up from the other end, one letter at a time, until all the lights are on, then after another delay the lights blank. This sequence repeats itself continuously - the speed is externally controllable. A switch option allows the direction to be frozen i.e. only build up

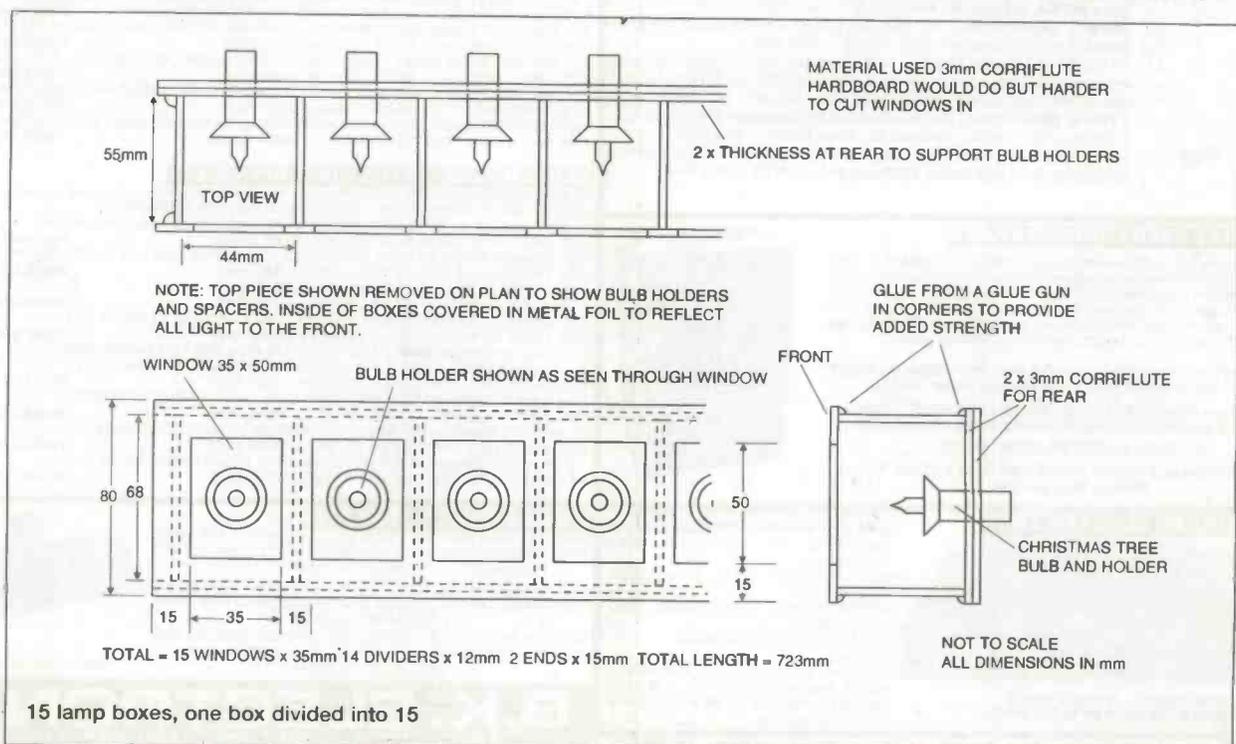


MUM™

ANY SUITABLE CASE/BOX MAY BE USED. REAR PANEL MUST BE METAL AND USED AS A HEATSINK.
ALL PIECES - FRONT, BACK, BASE AND LID - IF OF METAL MATERIAL MUST BE EARTHED

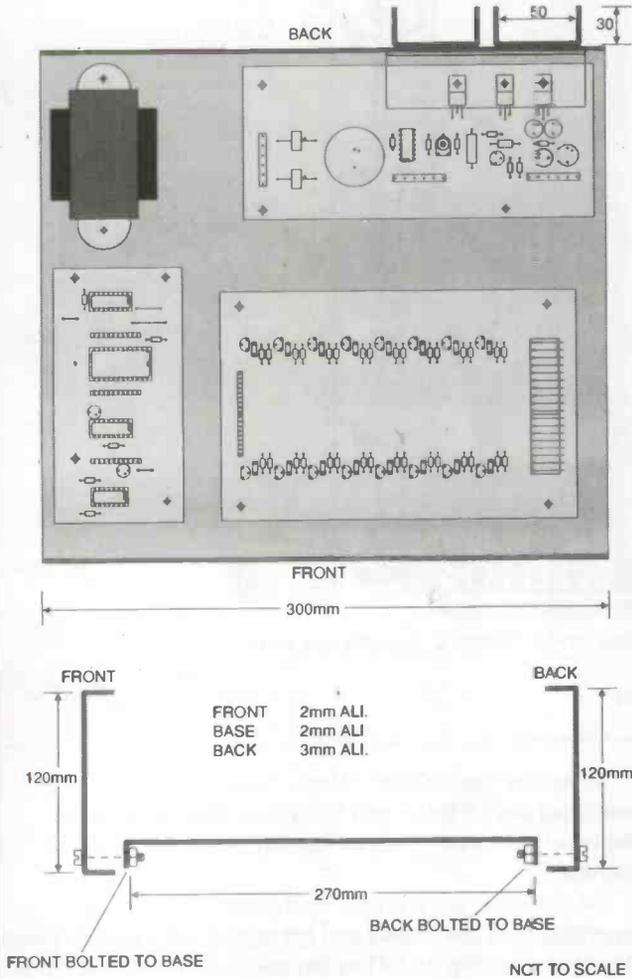
2 OFF METAL RNS
BOLTED ON REAR PANEL
2mm ALI. SIZE NOT CRITICAL



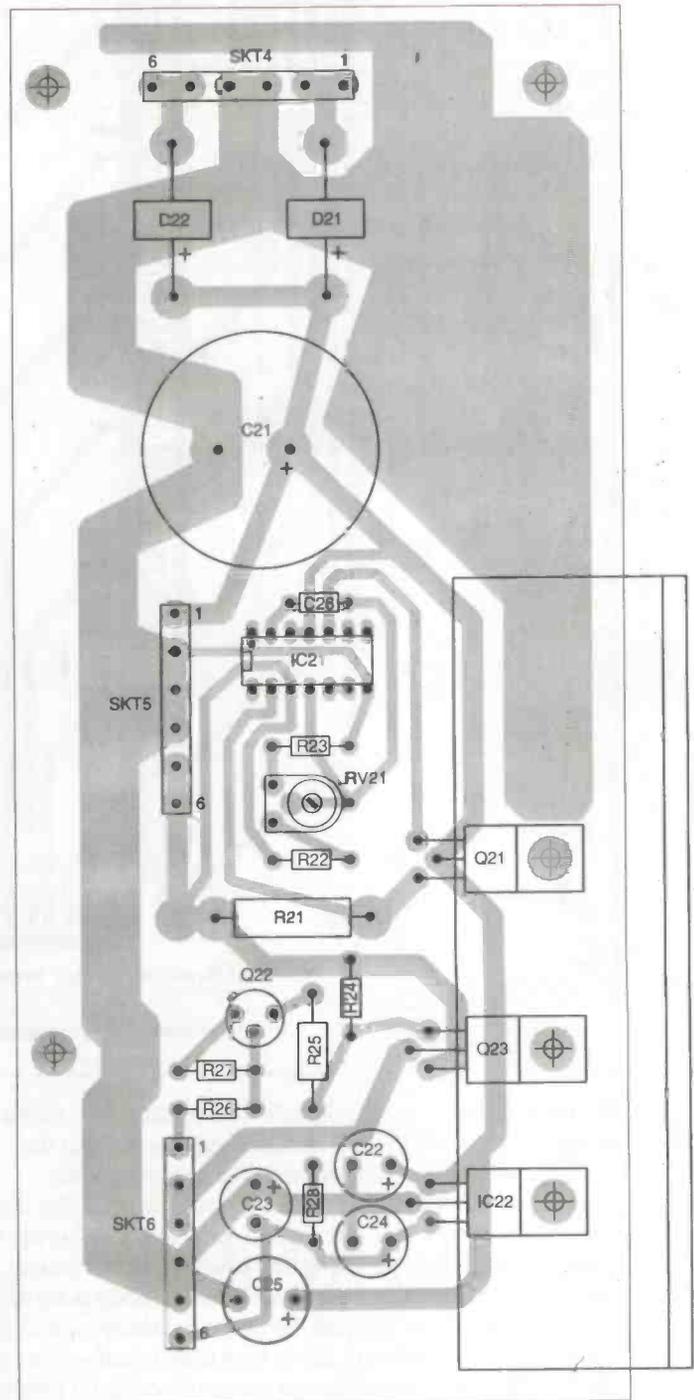Suggested layout and construction of control box



PSU PCB component layout

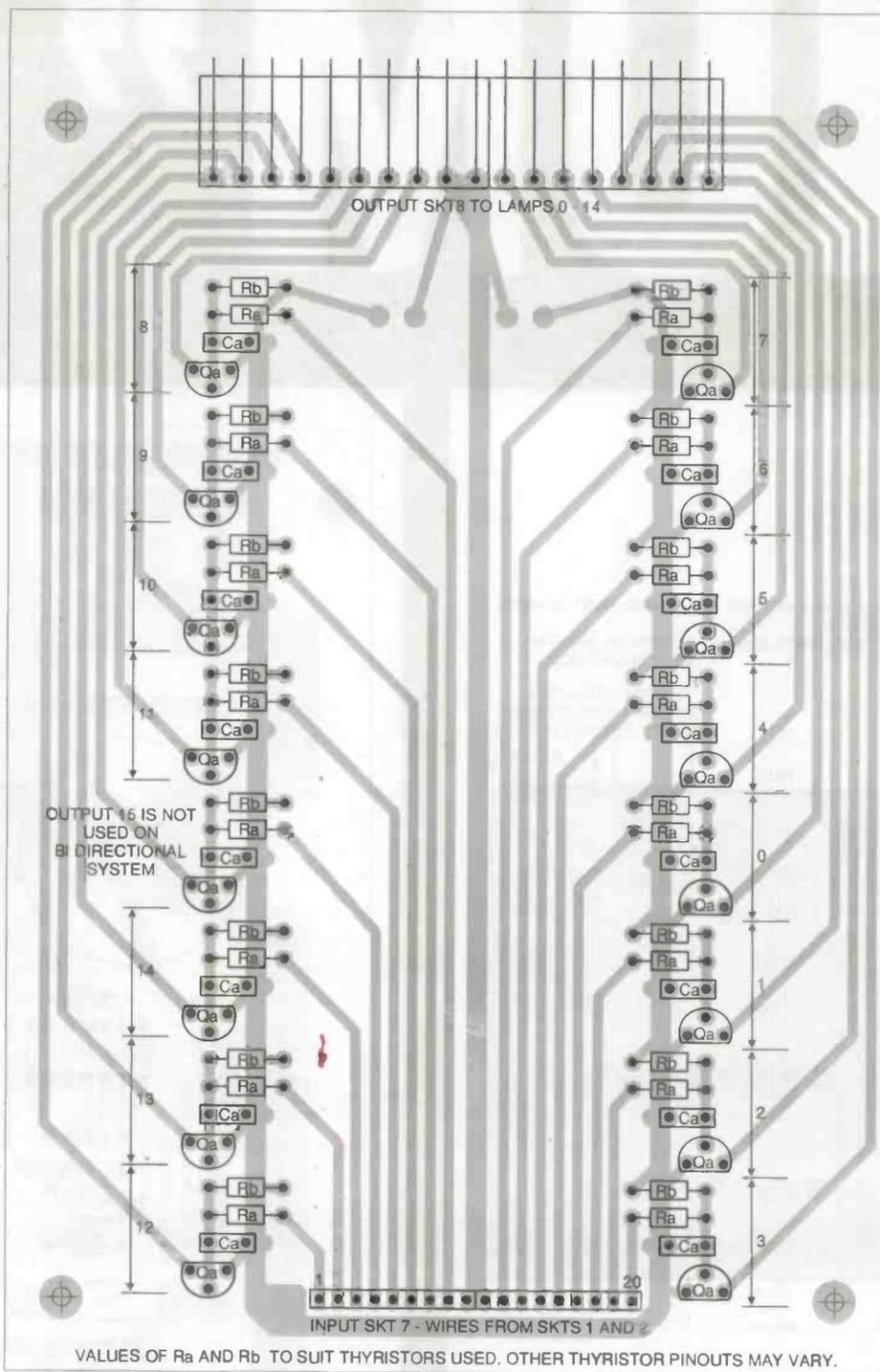

Driver board PCB component layout

from one end and, to allow instant 're-setability' after all the lamps are on rather than allowing a short time to read the message: this facility is provided with the option switch.

By using different coloured bulbs from a string of Christmas tree lights and metal foil reflectors in the little boxes behind the bulbs, an extremely interesting and effective multi-coloured display is produced very economically. The display is limited to 15 letters because of the way the direction change works; if the direction is limited from left to right then 16 letters can be used i.e. after a direction change, lamp 16 comes on before lamp 1; although this could have been sorted out electronically it would have complicated an otherwise simple, easy to follow circuit.

As well as "Hello Mum", "Happy New Year" other messages like "Toilets" and "Sale This Way" have been displayed with great effect as flashing lights always attract attention.

For domestic use it is best for the control box to be separated from the display and connected via a multiway lead. This keeps the size of the display box to a minimum and has only 12 volts on any of the wires to it so it is completely safe when little Jimmy tries to modify it with his new Duplo screwdriver set. The mains and controls are kept well clear in a metal case out of harm's way.

For work or school use the control box can be built on to the display box, care being taken not to expose any mains

SKT1	FUNCTION	TO
1	NOT USED	
2	'7' OUT	7/13
3	'6' OUT	7/14
4	'5' OUT	7/15
5	'4' OUT	7/16
6	'3' OUT	7/20
7	'1' OUT	7/18
8	'2' OUT	7/19
9	'0' OUT	7/17
10	0V	5/3

SKT3	FUNCTION	TO
1	+12 VOLTS OUT	3/2
2	PSU SWITCH OUT	6/1
3	SPEED POT	RV1
4	SPEED POT	RV1
5		
6		
7	0V	NOT USED
8	HOLD SET	SW1
9	0V	NOT USED
10	DIRECTION SET	SW1

SKT5	FUNCTION	TO
1	21VDC UNREG OUT	
2	0V	
3	0V	
4	0V	
5	DIRECT DC OUTPUT	
6	NOT USED	
	DIRECT DC OUTPUT	
	NOT USED	

1/10

SKT7	FUNCTION	TO
1	0V	6/4
2	0V	6/5
3	INPUT TO THY 12	2/9
4	INPUT TO THY 13	2/10
5	INPUT TO THY 14	2/7
6	INPUT TO THY 15	2/8*
7	INPUT TO THY 11	2/4
8	INPUT TO THY 10	2/3
9	INPUT TO THY 9	2/6
10	INPUT TO THY 8	2/5
11	LAMP SUPPLY (+V)	6/2
12	LAMP SUPPLY (+V)	6/3
13	INPUT TO THY 7	1/2
14	INPUT TO THY 6	1/3
15	INPUT TO THY 5	1/4
16	INPUT TO THY 4	1/5
17	INPUT TO THY 0	1/9
18	INPUT TO THY 1	1/7
19	INPUT TO THY 2	1/8
20	INPUT TO THY 3	1/6

SKT2	FUNCTION	TO
1	+12 VOLTS IN	6/6
2	NOT USED	
3	'10' OUT	7/8
4	'11' OUT	7/7
5	'8' OUT	7/10
6	'9' OUT	7/9
7	'14' OUT	7/5
8	'15' OUT	7/6*
9	'12' OUT	7/3
10	'13' OUT	7/4

SKT4	FUNCTION	TO
1	15VAC IN	
2	15VAC IN	
3	TRANSF. CT.	
4	TRANSF. CT.	
5	15VAC IN	
6	15VAC IN	

15-0-15 VOLT 50VA TRANSFORMER

SKT6	FUNCTION	TO
1	PSU SWITCH IN	3/2
2	LAMP SUPPLY OUT	7/11
3	LAMP SUPPLY OUT	7/12
4	0V LAMPS	7/1
5	0V LAMPS	7/2
6	+12 VOLTS OUT	2/1

THY 0 TURNS ON BULB 0 FIRST
 THY 1 TURNS ON BULB 1 SECOND
 THY 2 TURNS ON BULB 2 THIRD

* ONLY USED ON 16 ONE DIRECTION SET UP

PCB LINKED

Inter-board connections

circuitry when the lid is removed to change the message. The one described in this article has separate boxes connected with a cable. To make transporting it easier, plugs and sockets were used to connect the cables between the two boxes; this is expensive but is a useful addition.

Board I: Electronic Control Board (Sequence Board)

An oscillator built around IC3b and using an external potentiometer RV1 220kn as the resistive element provides the running speed of the unit (R1 is there to prevent the potentiometer from shorting out the IC at minimum resistance). Pulses from this oscillator are fed to a counter, IC1. This is a rather complex counter but several of its features are not used; the features used in this project are binary/denary.

The counter is selected to binary, a "1" on pin 9 which gives it a count of 16 volts rather than 10. The direction pin 10 is used to change the direction of the build up of lights and is


driven by a stat (see later in text). The outputs A to D build up in binary from all zero's to all 1's. This is fed to a 4 to 16 line decoder, IC2. It is enabled by holding pin 23 down to 0V and not engaging the latch facility i.e. holding pin 1 high via R3. This IC has 16 active outputs i.e. they are normally low (0V) and switch to a high one at a time giving an output according to the inputs on A-D. The outputs are from 0-15 - a little confusing but this is because zero out of the counter is decoded to an output on the decoder - this activates lamp 1, output 1, controls lamp 2 and so on.

These are taken off the control board to the driver board via sockets 1 and 2. The 16th output, output 15 is taken to the clock input of a "D" type stat wired as a ÷2. The first time pin 15 - the 16th output of the decoder - goes high, it clocks the Q of the D type to the Q output remains in this state until the clock receives another pulse i.e. the decoder has gone through the complete count again this time the Q changes state again. The effect of this is to divide by two the signal present at pin 15 of the decoder.

Now the direct output from pin 15 is ANDed with the divide by two signal from the D type. This ANDing is done in IC3a because it is a NAND gate and the output only goes low when the two inputs are high. As there are two unused gates they are placed in series. This saves grounding their inputs as unused gates but has no electronic effect. This ANDed output is fed to the output switch to switch off the lamp supply on the power supply board. The other stat in IC4 is used as another divide by 2 using the already divided by 2 signal from the decoder, pin 15. The output of this is fed back to the direction pin on the counter, making a total ÷ 4.

The combined effect is to illuminate the bulbs in turn until they are all on. They stay on for another complete scan 0-15 when they are

CORRECT WAY TO JOIN

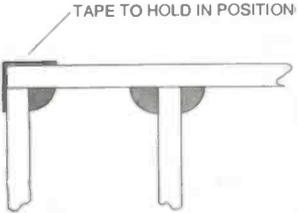

TAPE TO HOLD IN POSITION


NOTE: TO JOIN CORRAFLUTE HOLD IN PLACE WITH TAPE AND APPLY GLUE GUN IN CORNER

BLACK CORRAFLUTE WAS USED ON PROTOTYPE. TO MAKE LINES SHOW UP, STICK MASKING TAPE ON THE CORRAFLUTE AND DRAW ON THE TAPE. CUT WITH CRAFT KNIFE THROUGH BOTH AND REMOVE MASKING TAPE WHEN PIECE CUT TO SIZE.



MASKING TAPE ON PANEL

INCORRECT WAY TO JOIN


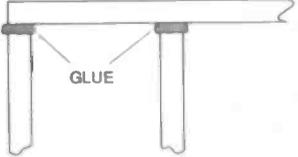



GLUE

DO NOT USE GLUE GUN TO BUTT JOINT AS THE GLUE ADDS TO THE SIZE

TO CUT PERSPEX FRONT PANEL, AGAIN USE MASKING TAPE. THIS IS EASY TO DRAW LINES ON AS WELL AS HELPING TO PREVENT SPLITS. USE A FINE TOOTH TENON SAW AND CUT VERY SLOWLY.

Construction details

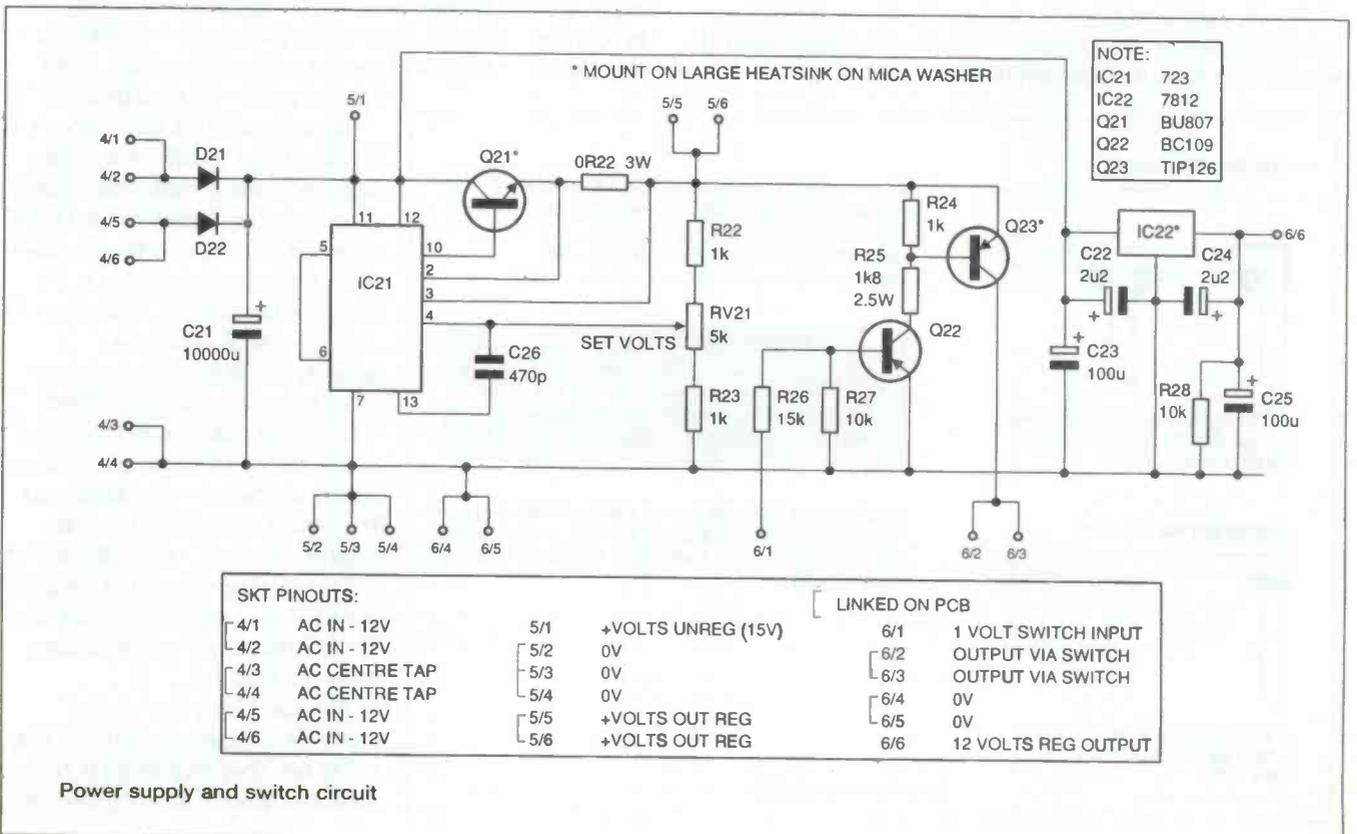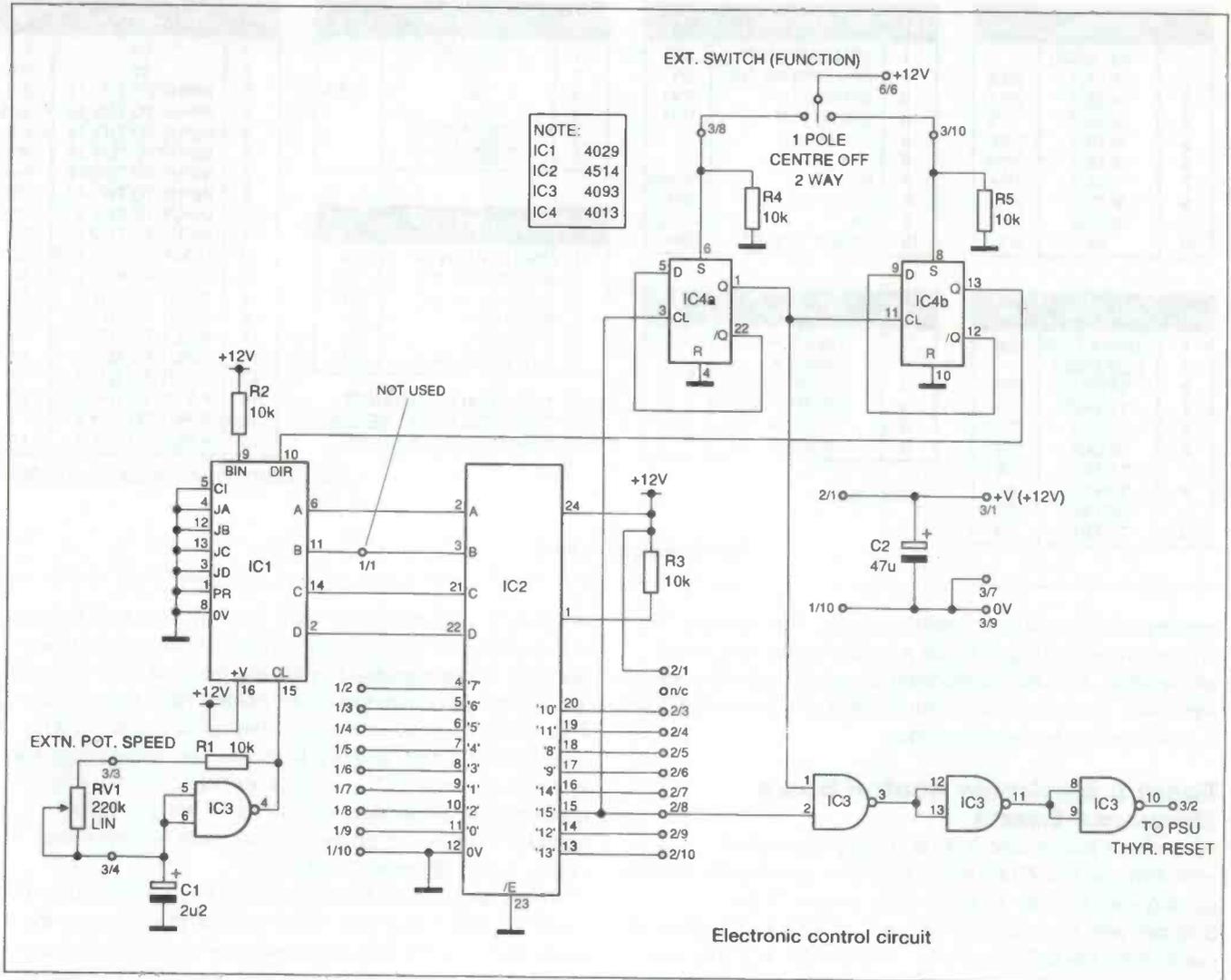

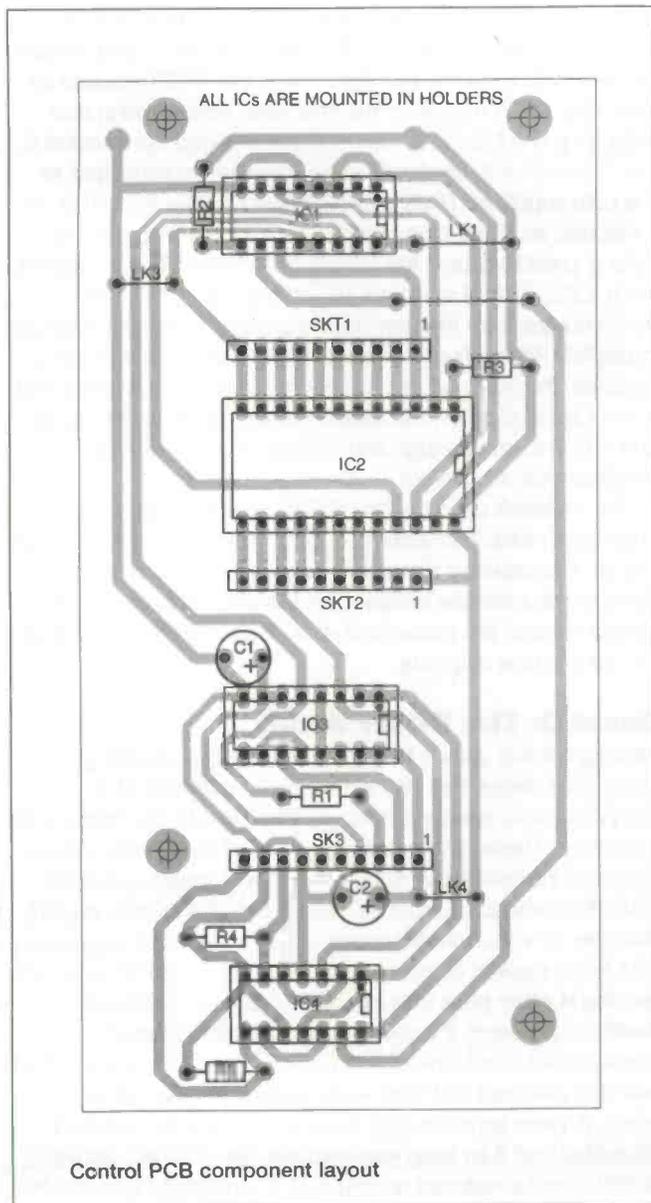

all reset. Now the bulbs illuminate from the other direction and stay on for a complete scan before resetting and starting all over again, making a total of 64 pulses from the oscillator for a complete sequence.

Both of the D type stats have their sets brought out to a switch. If the set of a stat is taken high, the Q output goes

high and stays high, overriding the clock and D signals. If IC4a set is taken high, there is no holding the light on for one scan and the direction freezes. If IC4b is taken high, the hold still works but the direction is always the same.


Although all the inputs and outputs to this board can be connected directly with wires, the use of plugs and sockets aids fault-finding and any possible modification or repair is highly recommended as the board can be completely disconnected and worked on without the restriction of wires connected to other boards etc.

Board 2: The Power Supply Board

Firstly the bulbs used set the voltage required. The ones used in our model were a cheap string of 20 lights sold as Christmas tree decorations. They consisted of 20 lights so, with a 240 supply, the voltage of each bulb must be $240 \div 20 = 12V$: to produce long life in the bulbs they must be run slightly under this voltage.

Because the supply is going to be subjected to very light loads i.e. one bulb on, to heavy loads i.e. all 15 bulbs on, a regulated supply is necessary to maintain this voltage. Each bulb, depending upon type, may require up to 150mA - a total of around 2.25 amps may then be required, although not continuously. The regulator must be variable to allow the voltage to the bulbs to be adjusted to just below its rated voltage i.e. a 12 volt bulb should be run at around 11.5 volts across the bulb. Allowing for voltage drops in the switching darlington the supply is set to around 12 volts.

To produce this supply, a transformer of 15-0-15 is required at, at least, 50Va. As we have already seen, the maximum load is not continuous and is averaged out when only one or two bulbs are on. From here, the 15-0-15 is passed on to the PSU PCB. As only three connections of the 6-pin socket are required they are doubled up to reduce the current on each pin. From here, two large diodes, D21 and D33, convert the AC into DC which is smoothed by C21. A 723 regulator is used to stabilise the supply; this is a standard regulator circuit. As well as regulated, the supply is variable by adjusting VR21 and current is limited by use of R21. This will reduce the output voltage to maintain a maximum of about 0.65 volts across it. This then acts as a current limit of around 3 amps. A power darlington is used as the main series pass transistor - BV 807, TR21. These are both rugged and reliable and easier to mount than a T03 style of transistor (note that its metal heatsink is connected to its collector and so must be mounted on the heatsink with an insulating set). To allow the PCB to be used as a standard supply in other projects, the

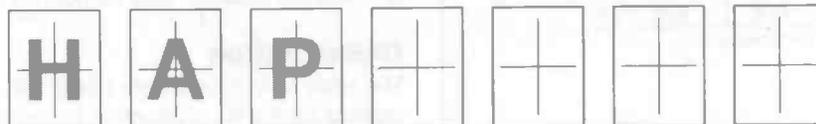


USE FRONT PANEL WITH THE 15 WINDOWS AS THE MASTER TO MAKE A TEMPLATE. THIS IS THEN USED BEHIND THE FILM WHEN MAKING THE MESSAGE TO ENSURE THE LETTERS ARE IN THE MIDDLE OF THE WINDOWS.


THE MESSAGE IS BUILT UP USING A STENCIL SO ALL THE LETTERS ARE THE SAME SIZE AND STYLE. GAPS BETWEEN WORDS CAN BE LEFT BLANK OR THE BULB BEHIND IT CAN BE REMOVED.

THE FILM USED IS DRAFTING FILM CUT TO SIZE OR PCB MASTER FILM OR SIMILAR. SEVERAL MESSAGES CAN BE MADE TO SUIT TIME OF YEAR

The message film

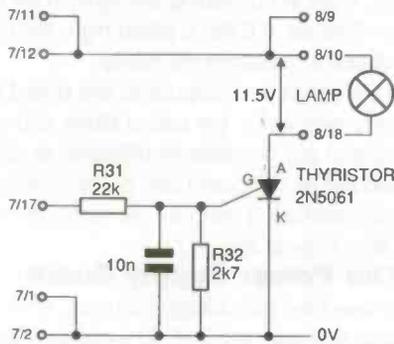

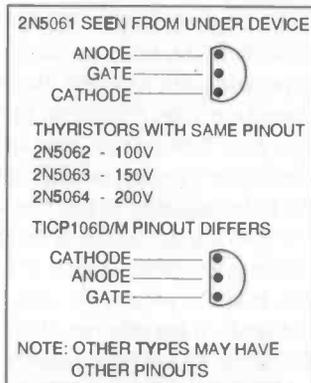THYRISTOR SWITCH CIRCUIT
 15 OR 16 REQUIRED - SEE TEXT
 15 ON BI DIRECTIONAL SYSTEM
 16 ON SINGLE DIRECTION



LAMP NO.	INPUT SKT.	OUTPUT SKT.
0	7/17	8/18
1	7/18	8/17
2	7/19	8/16
3	7/20	8/15
4	7/16	8/14
5	7/15	8/13
6	7/14	8/12
7	7/13	8/11
8	7/10	8/8
9	7/9	8/7
10	7/8	8/6
11	7/7	8/5
12	7/3	8/4
13	7/4	8/3
14	7/5	8/2
15*	7/6	8/1

* NOT REQUIRED ON 15 LAMP SET UP

SUPPLY	INPUT SKT.	OUTPUT SKT.
0V	7/1	—
0V	7/2	—
#+11.5V	7/11	8/9
#+11.5V	7/12	8/10

ACROSS BULB

Thyristor switches

variable DC output is provided in socket 5, pins 5 and 6 with 0V on pins 2, 3 and 4 (note that this output is not required in this project). The unregulated supply across the reservoir capacitor is also taken out. This can be used to ensure there is at least 4 volts difference between this and the output voltage to maintain stability on heavy loads (not used in this project).

Where this supply differs from most is the inclusion of TR22 and TR23; these form a power switch which, normally, is on i.e. the output in the collector of TR23 is around 11.5 volts. This is due to TR22 being turned on by a signal from the

control board. This in turn drives TR23 but, when TR22 is turned off, TR23 is also turned off reducing the output to zero, necessary to reset the thyristors. Note that TR23 requires an insulating set to mount on the heat sink. When testing and setting up this board by itself, a link is required from socket 6, pin 1 to socket 5, pin 5 otherwise there will be no output to the bulb supply as TR22 and TR23 will both be turned off, i.e. it requires an active high signal to turn it on. A separate 12 volts is used to supply the control board logic. This is catered for in IC22, a 7812 standard 12 volt regulator, the input of which comes from the unregulated supply across the reservoir capacitor. Although all the power devices are mounted on a heatsink, the 7812 will not get hot because of its minimal load in the CMOS logic on the control board. Again, all the inputs and outputs are via plugs and sockets to allow testing, modifications, repairs etc.

The heatsink used on the PCB is a piece of aluminium angle 3mm thick and 35mm x 35mm x 140mm long, size not critical. It is essential that even this is bolted to a metal back panel to minimise the temperature increase while in use. A couple of extra fins bolted onto the exterior of the back panel will aid this (see diagram).

Board 3: The Driver Board


Although at first glance this board looks a little daunting, a closer look shows that the same circuit consisting of 4 components is repeated 15 times. The drive to the lamps is via a thyristor. These devices, once turned on by a positive drive signal on the gate input, stay on until the supply is removed. R31, R32 produce a potential divider to limit the drive current from the 12 volts from the control board. The small capacitor C31 helps prevent false triggering. The values of R31 and R32 and the 14 other pairs may need to be altered if different thyristors are used. It is recommended that if different thyristors are used, one of them is wired and the values of R31 and R32 checked that they work before the other 14 are wired. If a less sensitive type is used R32 may be removed altogether and if an even less sensitive type is used, the value of R31 may be reduced accordingly. Do not reduce below 8K2 as this may overload IC2. Once one of the thyristors is working reliably, the others can be wired using similar values if different from the ones shown in the drawing.

Again, all the inputs and outputs are taken in and out on sockets to aid fault-finding and modifications or repairs. The input socket is a 20-way 0.1 type while the output is an 18-way 0.156. This prevents them from being swapped during construction.

Great care must be taken when connecting these plugs and sockets because they do not run in sequence.

Construction

The small lamp boxes were made out of corriflute, a fantastic material similar in construction to corrugated cardboard but made out of plastic. It is reasonably cheap and is very easy to work with. It can be joined either by tape or glue from a glue gun. The 15 boxes each contain a coloured bulb mounted in its holder at the rear of the box and a foil reflector behind (take care the foil does not short out the bulb). The holders were cut from the Christmas tree string of lights with about 6" (about 1500mm) of cable. These were then joined to longer wires to connect to the driver board. Care must be taken not to allow these to short. Heatshrink sleeving is useful here to protect the joints. These corriflute boxes, each the same size, allows the message to be made up from a template. I used the front

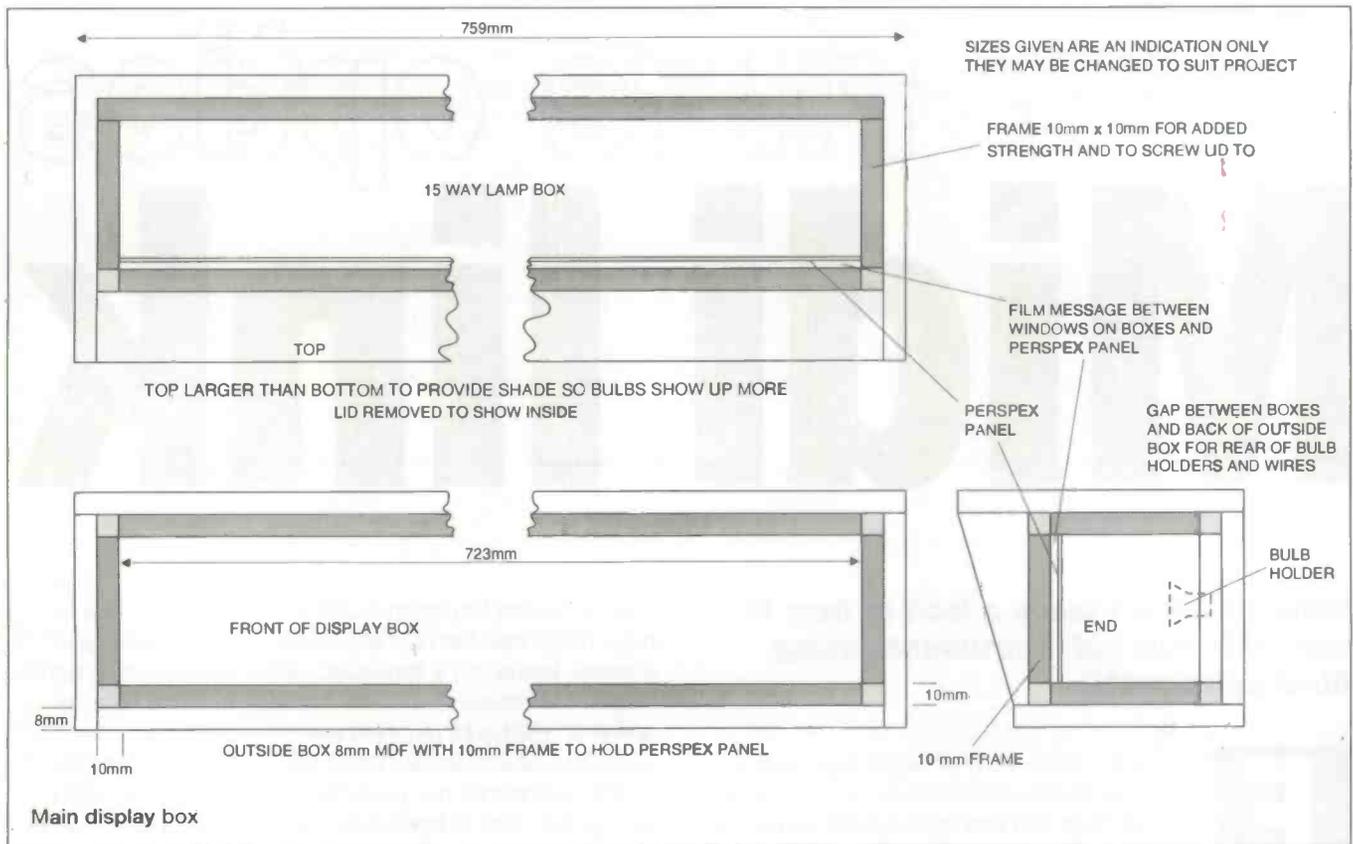

panel of the boxes i.e. one piece with 15 oblong holes cut in it as the template. The oblong cutouts were traced onto a piece of card. This was then placed under the transparent film when making the message, thus ensuring that the letters on the film are in the centre of the cutout of each box. Great care must be taken to ensure it is the right way round. Common sense should prevail here.

The boxes containing the bulbs are placed in a larger box leaving room to slide the message film between the boxes and the plastic front panel. The outer box is made from MDF board 3/8" (10mm) thick. The size is determined by the size of the 15 boxes and if they are each only 1/4" different to the sizes shown, the outer box must be nearly 4" different to accommodate this - so each one must be measured and built to the size required rather than working to a drawing. To enhance its appearance, the MDF box is covered in sticky-back wood effect plastic - yes, I used to watch Blue Peter. The control box, if built separately, should be big enough to lay each of the three boards flat with the mains transformer mounted far enough away from them so as not to risk shorting the terminals that normally protrude. All mains connections should be shrouded and, if in any doubt, a qualified engineer's help should be sought.

The box must have a metal rear panel and the heatsink should be bolted to it. Extra fins should be added on the outside to help dissipate the heat (see diagram). Nearly all the heat is produced by the series pass regulator transistor TR21. This is because TR21 has voltage across it as well as current through it, whilst the switching transistor TR23 is either on or off and therefore does not produce so much heat.

In the prototype (yes, I actually made one), the front panel, rear panel and base were three separate pieces bolted together which enabled the project to be laid out and gave better accessibility while constructing and working on the project. Doing it this way means that more people can work on it at

the same time.

Again, the actual size is not critical but safety must always be at the top of the list when deciding - if in doubt, go for a larger rather than smaller box.

The whole project uses reasonably priced components. The cable connecting the two boxes could have a plug and socket at each end but this increases the overall cost. A cheaper method is to have a long lead on the display box and mount the 18-way housing for plug 8 on this lead. It is slightly less convenient but much cheaper and still retains the boxes as completely separate units, making moving them around much easier.

PARTS LIST

Off PCB pieces

- 15-0-15 volt 50Va transformer (Maplin DH 315)
- 1 pole 2 way centre off switch (toggle)
- 2 pole on/off mains switch
220kn linear pot
- 1 piece of aluminium angle approx
30 x 30 x 160mm long x 3mm thick
- To make 10 and 20 way sockets
2 strips of pins (Maplin JWS9P)
- 5 x housings to suit 10 way (Maplin PY94C)
- Terminal pins, 5 packs of 10 (Maplin YW2SC)
- 3 x 6 way plugs (Maplin JZ01B)
- Pins for above (Maplin JY9 1 Y)

Fibre optics

Midi link

Robert Penfold takes a look at how to link MIDI musical instruments using fibre-optic cable

Fibre-optic cables are now beginning to play a major role in the world of telecommunications, but they have had less impact in the home and office. Optical cables are used to some extent in computer network systems and digital audio gear, but they remain relatively rare outside these niche markets. In truth, fibre-optic cables have no real advantages in many day-to-day applications and would simply provide lower performance at higher cost. However, there are some areas where they have one or two potential advantages, and for the home-constructor fibre-optics have a strong novelty value. Although fibre-optic communications tends to be associated with expensive hi-tech systems, surprisingly simple and inexpensive circuits can be used in applications that involve the interchange of data at relatively slow rates.

The system described in this article is for use with MIDI (musical instruments digital interface) systems. MIDI is basically just an ordinary asynchronous serial communications system, much like a standard RS232C computer interface. It uses a 5

milliamp current loop system and an opto-isolator at each input, rather than the RS232C positive and negative signal voltages. Interfacing a fibre-optic system to this type of signal presents no difficulties though. The MIDI baud rate is quite high at 31250 baud, but this baud rate is well within the capabilities of inexpensive fibre-optic LEDs and photocells.

This system has two potential advantages over ordinary wire cables. One of these is simply that this system will work reliably at up to at least 30 metres, which is twice the maximum cable length that should be used with normal MIDI interfacing.

The second advantage is that an optical cable radiates no electro-magnetic interference. This can be an important factor in situations where there are long cables, some carrying digital signals and the others carrying audio signals. Digital noise is very good at finding its way into audio signal paths. Even with a fibre-optic cable running alongside a sensitive microphone cable there is no possibility of any cross-coupling.

How It Works

With equipment of this type it is possible to use a modem style f.s.k. (frequency shift keying) technique, or a very simple d.c. system. With modern optical cables and photocells it is only necessary to resort to an f.s.k. system if a very long operating

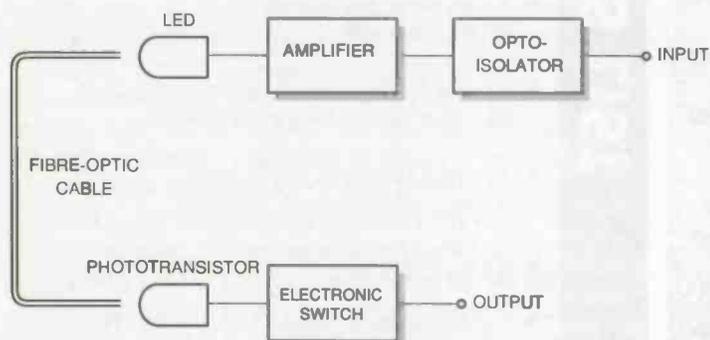


Fig.1. The MIDI fibre-optic link block diagram

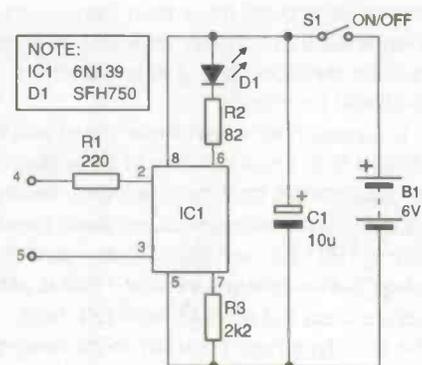


Fig.2. The fibre-optic transmitter circuit

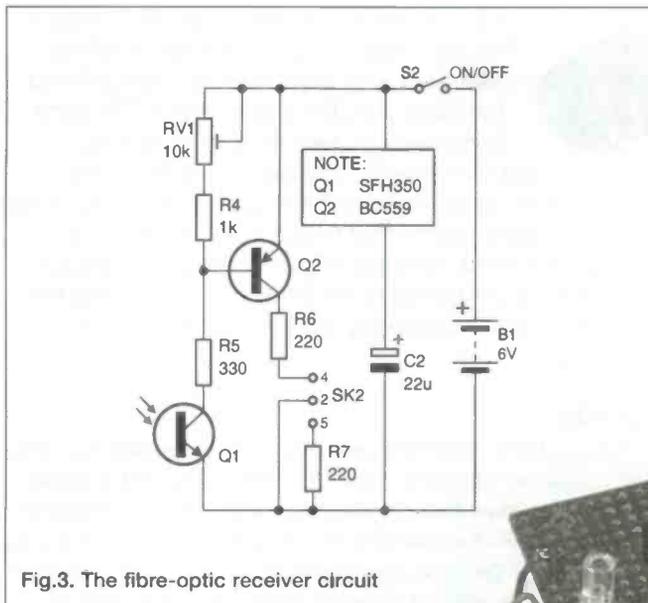


Fig.3. The fibre-optic receiver circuit

range is required, which is highly unlikely in a MIDI application. A simple d.c. link is therefore used in this case.

Fig.1 shows the block diagram for the MIDI fibre-optic link. The transmitter could just consist of a LED and a current limiting resistor, but the limited drive current from a MIDI output would probably not give very good results. The LED would only have an "on" current of about 5 milliamps, whereas a current about ten times higher than this is needed in order to guarantee good performance. The LED at the transmitter end of the system is therefore driven via an amplifier which provides a suitably high drive current.

The amplifier is driven with the MIDI input signal via an opto-isolator stage. The latter is to a large extent superfluous in this case, since the fibre-optic link is effectively a sort of giant opto-isolator! However, the MIDI specification stipulates that all items of MIDI equipment should have an opto-isolator input stage, and MIDI outputs are designed to drive the LED in an opto-isolator. It is advisable to use an opto-isolator input stage, if for no other reason than ensure good compatibility


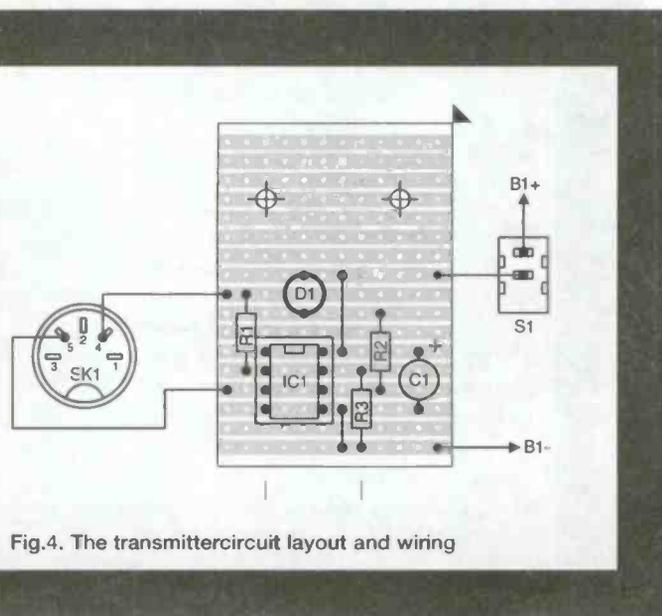


Fig.4. The transmitter circuit layout and wiring

with the MIDI output which drives the transmitter circuit.

At the receiving end of the system there is just a phototransistor driving an electronic switch. When the LED at the transmitter is switched on, the phototransistor has a relatively high leakage current, and this is used to turn on the electronic switch. When the LED at the transmitter is switched off, the phototransistor has only a minute leakage level, and the electronic switch is turned off. The switch controls the LED in the opto-isolator at the MIDI input of the unit driven from the receiver circuit, and this LED switches on and off in sympathy with the one at the transmitter.

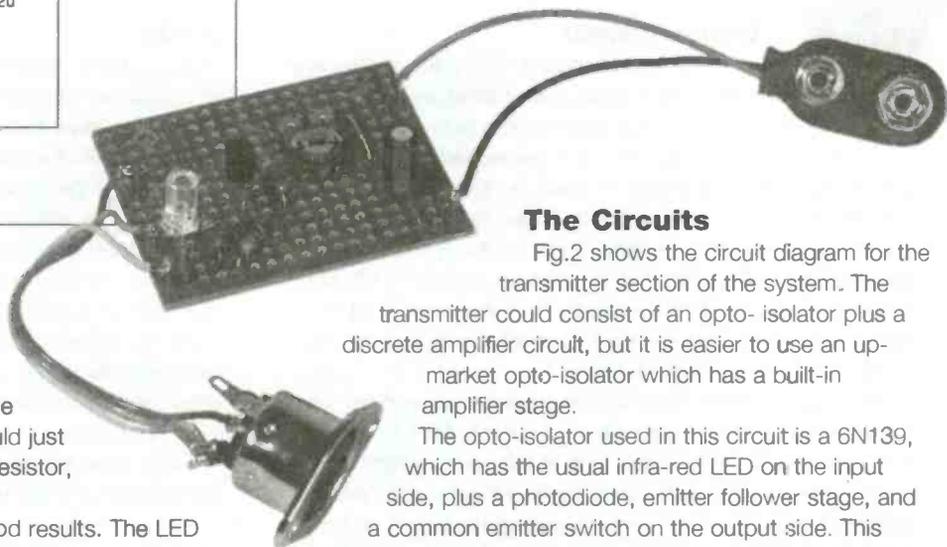


The Circuits

Fig.2 shows the circuit diagram for the transmitter section of the system. The transmitter could consist of an opto-isolator plus a discrete amplifier circuit, but it is easier to use an up-market opto-isolator which has a built-in amplifier stage.

The opto-isolator used in this circuit is a 6N139, which has the usual infra-red LED on the input side, plus a photodiode, emitter follower stage, and a common emitter switch on the output side. This arrangement provides high-speed operation by the standards of opto-isolators, and the 6N139 can actually handle baud rates of up to about ten times the MIDI baud rate. It also provides good efficiency, with an output current at around ten times the 5 milliamp input current. R2 is the current limiter for D1 which is a special fibre-optic LED. R1 provides part of the current limiting for the LED at the input of IC1. The remaining current limiting is provided by resistors in the MIDI output circuit that drives SK1. R3 is the load resistor for IC1's emitter follower stage. The current consumption of the circuit depends on the amount of MIDI activity the unit handles. Under standby conditions the current consumption is negligible, but it rises to a maximum average level of about 20 milliamps with a continuous stream of data. In normal use, the average consumption is unlikely to be more than a few milliamps, and the four HP7 size batteries have an extremely long operating life.

The receiver circuit appears in Fig.3. TR1 is the phototransistor, and this is a special fibre-optic type. Its base terminal is externally accessible, but in this circuit it is left unused. TR1 drives a p.n.p. common emitter switching transistor (TR2), which in turn drives the output socket via current limiting resistors R6 and R7. When TR1 is in darkness, its leakage level is negligible and TR2 is turned off. When TR2 receives a pulse of light from the optical cable, its leakage level increases to a few hundred microamps, and TR2 is biased hard into conduction. This arrangement is similar to the one used in the 6N139 opto-isolator, and it provides a switching speed that is more than adequate for the present application. VR1 controls the sensitivity of the circuit, and it is adjusted to give an output signal that accurately retains the mark-space ratio of the input signal.

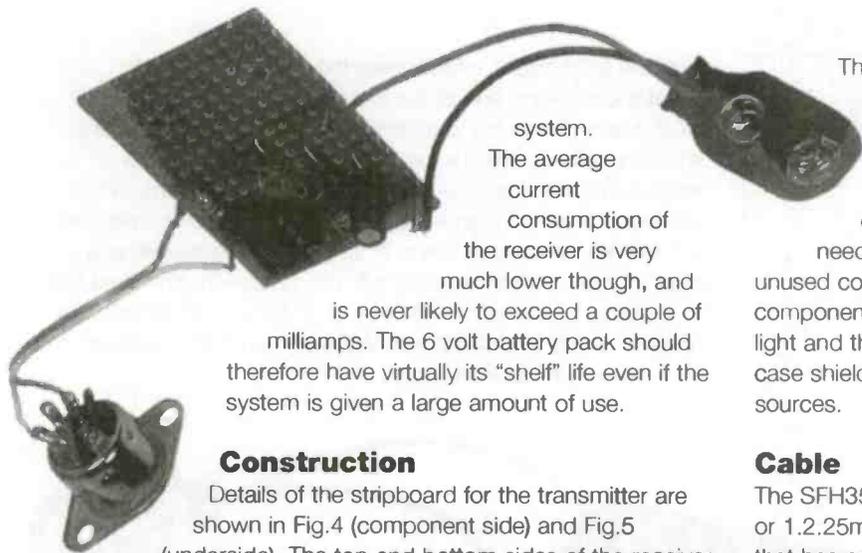Like the transmitter circuit, the current consumption of the receiver depends on the density of the data fed through the



system.
The average current consumption of the receiver is very much lower though, and is never likely to exceed a couple of milliamps. The 6 volt battery pack should therefore have virtually its "shelf" life even if the system is given a large amount of use.

Construction

Details of the stripboard for the transmitter are shown in Fig.4 (component side) and Fig.5 (underside). The top and bottom sides of the receiver board appear in Figs. 6 and 7 respectively. The transmitter board measures 12 holes by 17 copper strips. Cut out a board of this size using a hacksaw, and then file any rough edges to smooth finish. Then drill the two 3.3 millimetre diameter mounting holes, which will take 6BA or metric M3 mounting bolts. Next, make the four breaks in the copper strips, using either the special tool or a hand-held twist drill of about 5 millimetres in diameter.

The board is then ready for the components and the two link-wires to be fitted. The cathode (+) lead of D1 is the shorter lead. Use single-sided solder pins at the points where connections to off-board components will be made. Virtually any small plastic case will accommodate the board and other components. Fit the component board on the rear panel of the case, and SK1 and S1 on the front panel. A 2.3 millimetre diameter hole for the fibre-optic cable is drilled in the front panel directly in front of D1. The cable is a push-fit into D1 (and TR1 in the receiver) and it may tend to pull out of place unless it is clamped or glued in place. If it is clamped in place, be careful not to clamp it too hard, or the inner filament might be damaged.

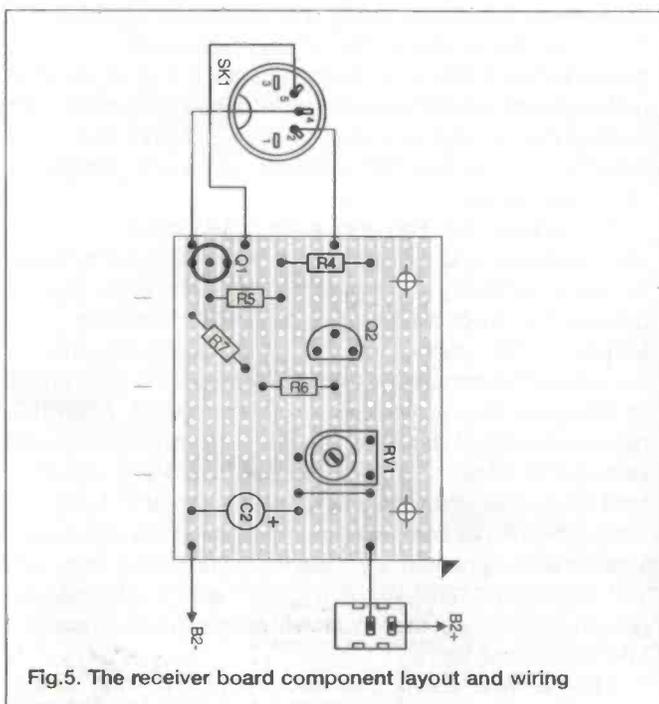


Fig.5. The receiver board component layout and wiring

The stripboard for the receiver measures 18 holes by 14 strips. Construction of the receiver follows along much the same lines as construction of the transmitter. The shorter lead of TR1 is the emitter leadout, and the middle one is the collector leadout. The base lead of TR1 is not needed in this circuit, but it is connected to an otherwise unused copper strip in order to secure TR1 firmly to the component panel. Note that TR1 is sensitive to extraneous light and the receiver might not function properly unless the case shields TR1 reasonably well from any strong light sources.

Cable

The SFH350 and SFH750 are designed for use with 1/2.2mm or 1.2.25mm fibre-optic cable. In other words, with a cable that has an inner filament which is one millimetre in diameter, and an overall diameter of 2.2 or 2.25 millimetres. As supplied, the cable will probably have rather roughly cut ends which will not provide an efficient coupling. It is easy to cut the ends properly, and it requires nothing more than a sharp modelling knife and a cutting board. Simply trim a few millimetres from each end of the cable, using plenty of pressure so that each cut is completed in a single stroke. Make the cut reasonably perpendicular to the cable. Also, make sure that the cable is fully pushed home into TR1 and D1, or only a weak coupling will be obtained.

Even using an old fibre-optic cable that was not particularly efficient with the red light from the SFH750 I found that an

PARTS LIST

Resistors (0.25 watt 5% carbon film)

- 2 82R
- R3 2k2
- R4 1k
- R5 330R

Potentiometer

- VR1 10k min hor preset

Capacitors

- C1 10u 25V radial elect
- C2 22u 16V radial elect

Semiconductors

- IC1 6N139 opto-isolator
- TR1 SFH350
- TR2 BC559
- D1 SFH750

Miscellaneous

- B1,2 6 volt (4 x HP7 size cells in holder - ● 2 off)
- SK1,2 5 way 180 degree DIN (2 off)
- S1,2 p.s.t. min toggle (2 off)
- 0.1 inch stripboards having 12 holes by 17 strips, and 18 holes
- by 14 strips, battery connector (2 off), 8-pin DIL IC holder,
- 1/2.2mm fibre-optic cable, wire, solder, etc.

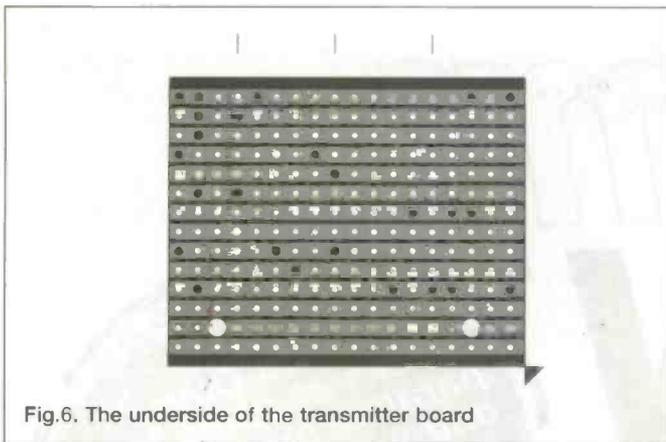


Fig.6. The underside of the transmitter board


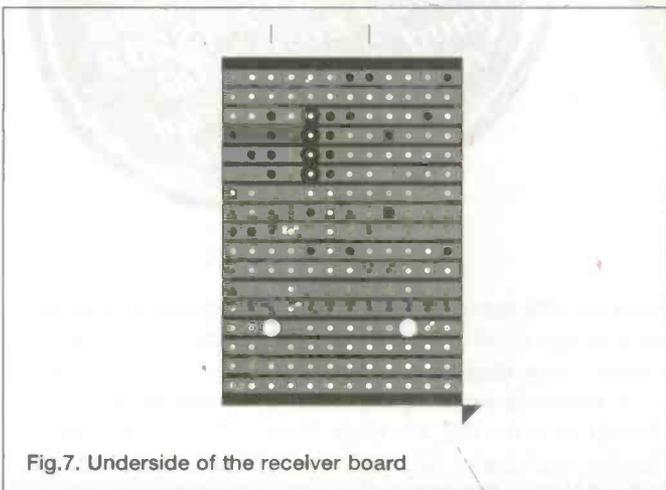


Fig.7. Underside of the receiver board

wavelength of the SFH750, and a much greater operating range should be possible using a cable of this type. I have not tested the system over a range of more than 30 metres though. Do not take fibre-optic cables through tight bends as this can seriously damage the inner filament. Most fibre-optic cable have a minimum bend radius of about 15 to 25 millimetres.


In Use

SK1 on the transmitter connects to the MIDI OUT socket of the master unit via a short MIDI cable. SK2 on the receiver connects to the MIDI IN socket of the slave device via another short MIDI cable. A suitable setting for VR1 can be found by trial and error. Any setting that gives reliable operation is suitable. Provided a strong signal is reaching the receiver, there will be a wide range of settings that give reliable results. Simply set VR1 at roughly the middle of this range.

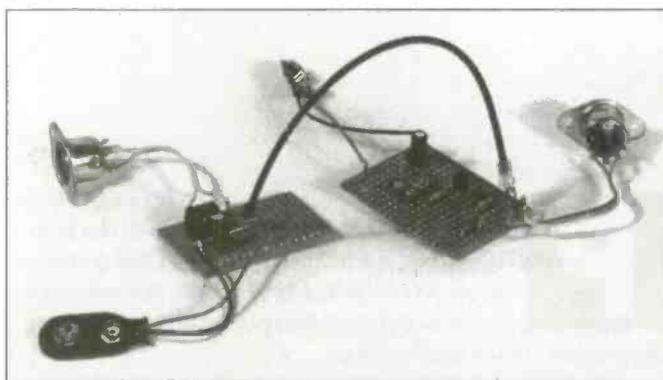

DEVELOPMENT AND PRODUCTION SOLUTIONS

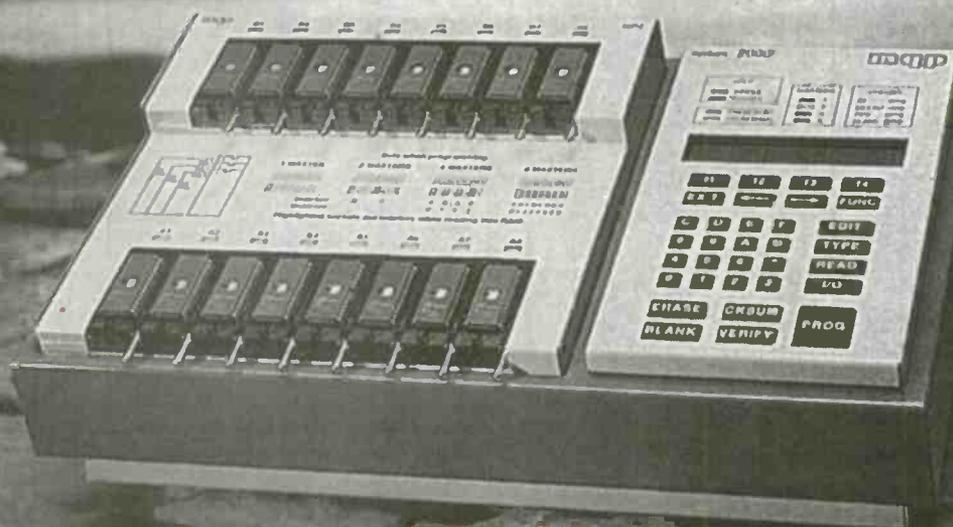- Gang Programmers
- Development Programmers
- Universal Cross Assembler
- Package Converters
- Development Tools
- Emulator Pods + Adapters



E.ELECTRONICS Ltd

Park Road Centre, Malmesbury, Wiltshire SN16 0BX UK

Tel: 01 666 825146 Fax: 01 666 825147

e/mail 100447.1124@compuserve.com

IRELAND 1-2800395
 GERMANY 089/4602071
 NORWAY 0702-17290
 ITALY 02 92 10 35 54
 FRANCE 1 69 30 13 79
 SWEDEN 08 590 32185
 Also Sell ELECTRONICS UK



©1991 E.ELECTRONICS LTD

Stamp Duty

Roland Oliver looks at using the parallax basic stamp and your pc's RS232 serial port 2400 baud 3 wire serial relay controller

PICs - or, by their real name, Peripheral Interface Controllers - have been around for some time now. They are present in many of the common-or-garden mice that we use with our ever more powerful personal computers and in many embedded control applications.

In their 16/17/1 8cxx clothing they are programmable in machine code via various development tools which also vary in

price from the sublime to the ridiculous, depending what you want to pay. C compilers are available for the so inclined making things easier.

In this article we are going to use one of the newer derivations of the PIC, the Basic Stamp. Manufactured by Parallax Inc, Rocklin, CA, USA, the Basic Stamp is produced in three forms - the original Basic Stamp with the processor, memory and voltage regulator mounted discreetly on a pcb,

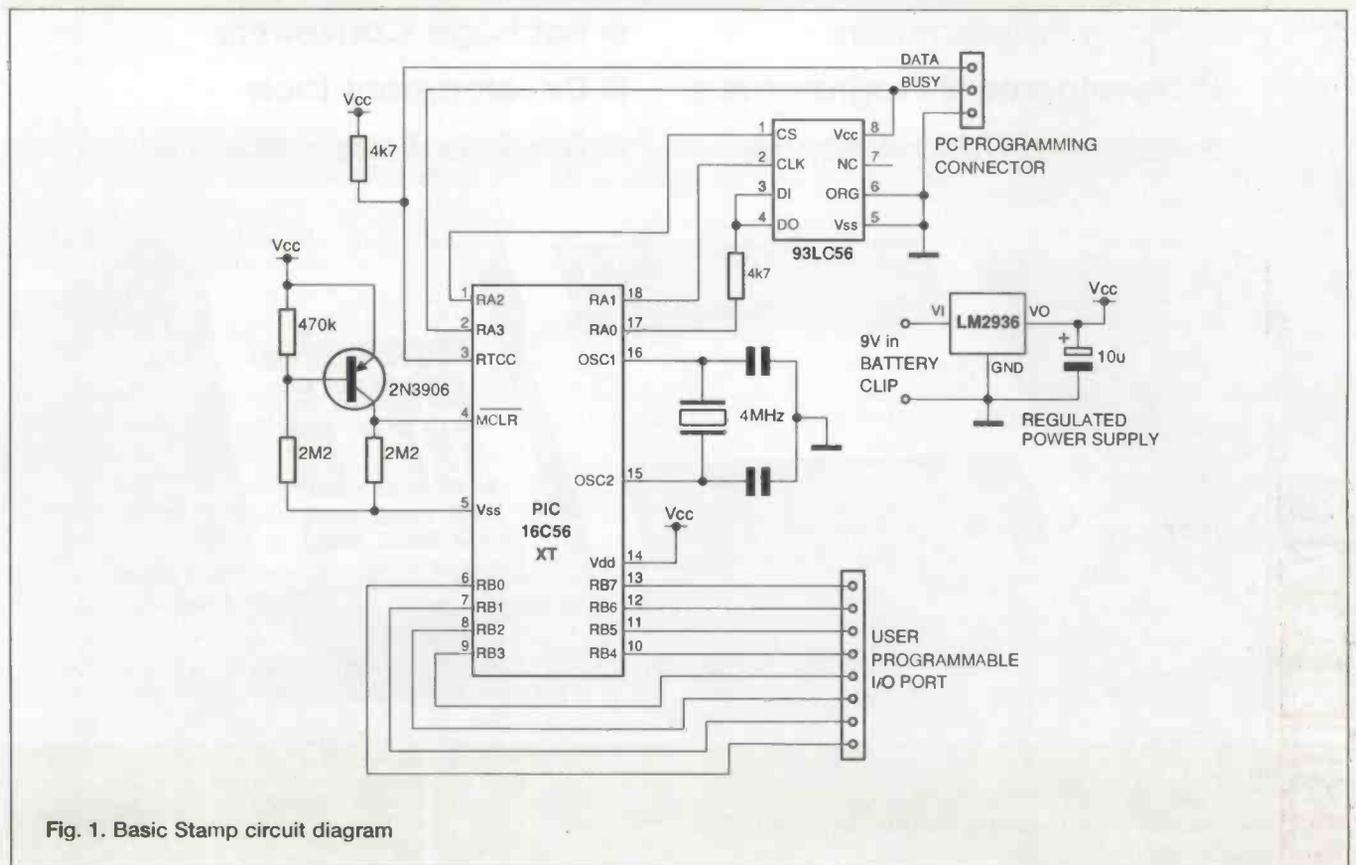


Fig. 1. Basic Stamp circuit diagram

complete with PP9 battery clips, 14 pin sip and prototyping area. The second style of Basic Stamp is hybridised on its own pcb and is terminated with a 14 pin male sip, which is soldered into the stamp motherboard. The motherboard also has a prototyping area (larger than the original Stamp), 14 pin sip and battery clips, part number for this Basic Stamp is BS1-IC.

The third type of Basic Stamp is the 24 pin dil version - its part number is BS2-1C.

The Parallax Basic Stamp is about as basic as you are going to get with any processor. Programming is carried out in Parallax PBASIC- an interpreter developed by Parallax to run on a PIG 16C56 Micro controller.

PBASIC is available complete with a parallel interface cable, extensive notes, programming manuals, built in Editor and free Technical support ready to run on any IBM compatible PC. Note that this development kit does not include the Basic Stamp itself. These must be purchased separately. The price of the development kit is roughly £99 in the UK and \$99 from Parallax in the US. The Basic Stamps themselves run at £29 in the UK and \$39 in the US.

Basic Stamp topology

Referring to photo of the Basic Stamp we see it is mounted on a roughly 4 x 6.5 cm board with header (SIP) pins with which to connect the I/O and two battery clips to connect the ppt 9 volt battery. A further three pins are provided to connect to the parallel cable which in turn connects to LPT 1 on the PC (arrows on the cable connector and the board make sure you are connected the right way round).

Figure 1 shows the circuit diagram for the Basic Stamp. Communications with the PC are carried out via the PC programming connector connected to pin 3 (RTCC) of the Stamp with handshaking on pin 2 (RA3). Power up reset is applied to pin 4 (MCLR) resetting the stamp to the beginning of the programme in memory. A 4MHz resonator is connected to pins 15 and 16 ,OSC 1-OSC 2 to serve as a clock.

Connected to pins 1 - 17 - 18 is a 93IC56 serial EEPROM of 256 Bytes capacity pin 17 (RA0) being the data I/O (bi directional), pin 18 (RA1) is the clock to sync the serial data line to the EEPROM Pin 1 (RA2) is the chip select for the EEPROM and is held high during read/write cycles, pin 8 (Vcc) of the EEPROM is also held high via pin 3 (RA3) of the Micro Controller during read writes to supply power to the EEPROM.

The I/O for the Basic Stamp consists of pins 6 through to pin 13 (RB0 - RB7) or 8 pins in total. All eight pins are pin programmable as either input or outputs and can sink a maximum of 25 ma or source 20 mA when used as outputs. However, parallax recommends a maximum chip total of 50 ma

PARTS LIST

Basic stamp based RS232 relay driver

- IC1 75492 relay driver
- D1-d4 1N4001
- LED1—4 general purpose LEDs
- R1—4 870 ohm quarter watt resistors
- R5 22 K quarter watt resistor
- REL 1—4 rs 349-648
- DB 9 male connector (pcb right angled mount type)
- 14 pin stripline 0.1 inch type
- 2 female 10 pin connectors (stripline) available from RS
- length of ribbon cable 10 core (to suit), see text.

when sinking and 40 mA when sourcing.

All the above refers to the original BASIC stamp which we are using in this project. The 051 is the hybridised version of the original and contains all its features, including the Voltage regulator, but will fit in a much smaller PCB footprint thanks to its sip construction.

The Basic Stamp Type BS2-1C as mentioned above is a 24 pin DIL device, and has all the characteristics of the other two Basic Stamps plus the advantage of 16 I/O pins.

As I have not had the chance to review this latest addition to the Parallax range I cannot comment on it in detail but looking at its specifications - 2048 bytes of programme space, enough for 600 lines of code, 20 MHz clock and serial port baud rates up to 9600, it sure gladdens the heart of a old hardware Tech, (it even has a real time clock interface).

Basic Stamp 'basic's & hardware'

I grew up in a teletype world where you loaded the bootstrap loader from a paper tape, fitted to the teletype into a DEC pdp 8 with 4k of memory and you thought you were in heaven with such a powerful machine. However, times have changed and 'booting up' means nothing more than switching on the PC and waiting for the 'C:' prompt or Bill Gates' Windows Programme Manager. How boring.

Oh for the days when the exhilaration of debugging a programme coupled with "Am I reading this hardware right?" and then finally it comes good.

Stamp Basic is like that. You get hooked on its capabilities, and try to get more and more out of it.

Looking at the Basic Stamp you first think its too basic to do anything but very rudimentary stuff like switching on a LED etc, but on further observation you find it contains a lot more than expected.

Instructions such as SERIN, SEROUT, PWM, SOUND, PAUSE, OUTPUT, LOW HIGH, TOGGLE - the list goes on. We are

PARTS LIST

Power supply parts

- BR1 GI WO4-9027 full wave bridge rectifier
- C1 1000 micro farad 16 VDC electrolytic capacitor
- C2 0.1 microfarad mylar or equivalent capacitor.
- voltage regulator LM 7805 +5VDC regulator

going to use SERIN and SEROUT as the main highlights of this project.

The Basic Stamp has a built in UART (universal asynchronous receiver transmitter) which can be assigned to any pins of the Stamp by issuing the appropriate SERIN pin, baud rate, (qualifier, qualifier), variable, variable - for instance:

```
SERIN 7,n2400, (">00"), B0, B1
```

would tell the Basic Stamp to wait at the serial port pin assigned - in this case, pin 7 for a 2400 baud signal transmitted from the FC (let's say COM1) with the ASCII characters >00 embedded as a lead in code,. If the lead in code was not transmitted, the Basic Stamp would sit and wait for the next set of characters that matched the lead in code. Once the lead in code was detected the Basic Stamp would then store the next two ASCII characters transmitted into registers B0 and B1 for later processing - its that simple!

If half a dozen Stamps were hung on a net then the lead in code becomes useful as it uniquely identifies each individual Stamp. For instance, STAMP 2 could have a lead in code of ">01" and so on - all it takes is to programme each Stamp with its own address at programme time.

Of course, any good programme sending serial data has a feedback or error checking loop (somebody may have pulled the serial plug out of the PC connected to the Stamp) In this case we would retransmit the data we received back to the PC from the Stamp using the SEROUT pin, baudrate, (data, data,), for instance SEROUT 6,n2400, (">00",B0,B1, "RECEIVED",13, 10) would transmit the lead in code the contents of B0 B1, the ASCII characters "RECEIVED" and finally a carriage return ,linefeed, to the PC.

This, of course, is not foolproof error checking but is good enough at this Baud rate and the distances involved.

Now that we have got the data into a couple of registers (B0 B1),and we have established how to format a reply to the PC's com port, we can start organising the Stamp to do some work, which in this project is to control four relays connected to the Stamp via a Driver (IC1 see fig 2).

Relay controller criteria

The criteria for this project was based on the premise that I would be able to use any old communications programme on my PC to communicate to the Stamp and, as most comms programmes in Terminal mode communicate in ASCII, the Stamp programme would have to allow for this.

I required that once a relay was switched on by a command from the PC then it stayed on until a further turn off command was transmitted from the PC (except under power failure condition when the relays would switch off anyway and remain switched off until the PC commanded them on again).

First panic set in - "how am I going to convert all of those ASCII characters to Hex or binary to get the ones and zeroes out on the pins without running out of memory - I only have 256 bytes?". Well, once the panic died down, it proved simple - a lookup table is another one of the Stamp's instructions which we will attack in just a while.

First thing I needed to do was to get the Stamp to recognise a lead in code, I decided to use >00 . This code is not strictly needed, but as I had grander ideas of setting up a net based on a RS 422/RS485 multidrop , then eventually I would need the lead in codes so that the net could broadcast to all the Stamps, and only the Stamp addressed would respond.

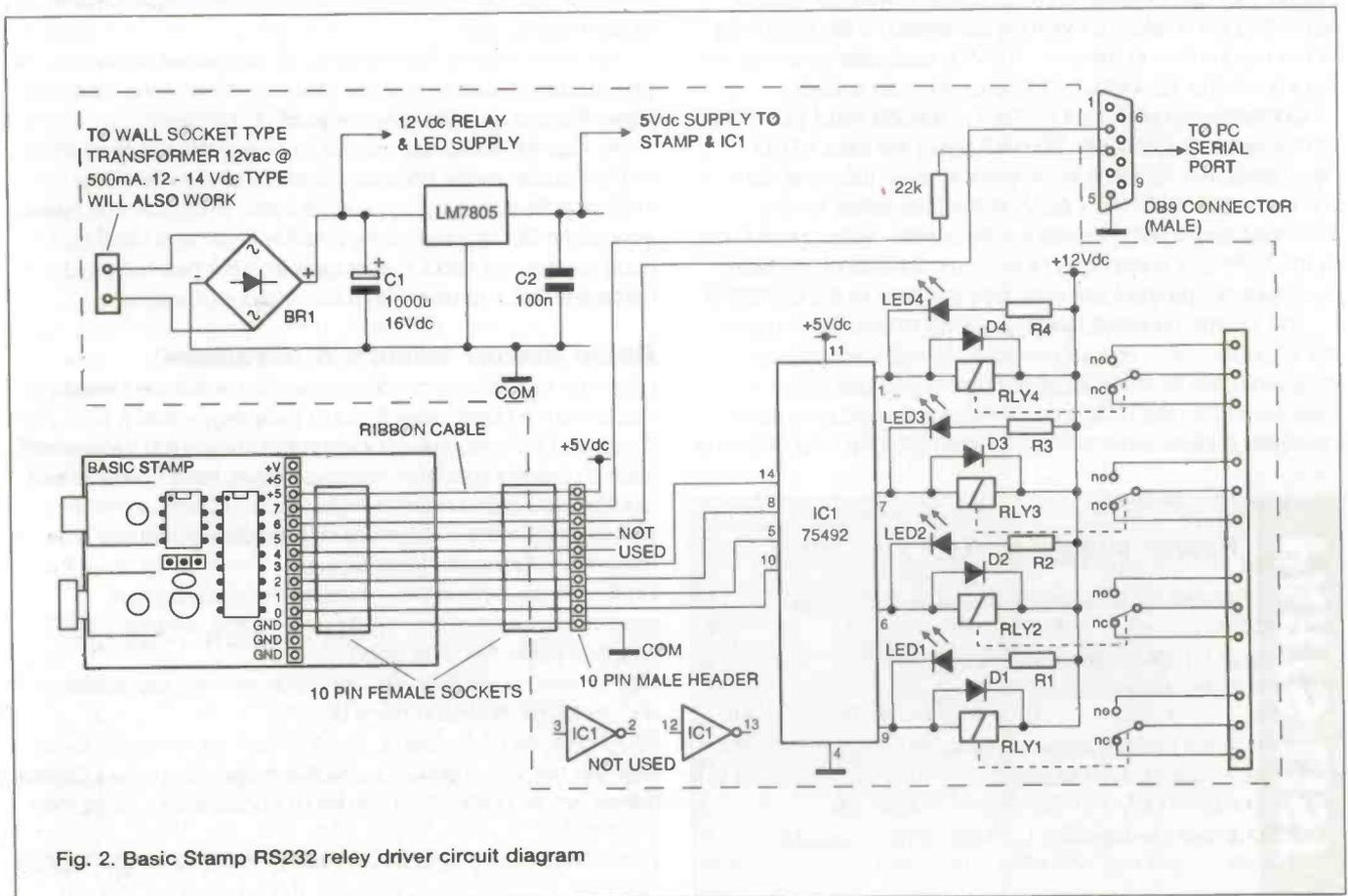


Fig. 2. Basic Stamp RS232 relay driver circuit diagram

The next step was to assign a register to hold the switch on/switch off character so B0 was chosen for this. The characters chosen to signify switch on and switch off were K (uppercase) for ON and L (uppercase) for OFF.

After this, all I had to do was assign register B1 to the data the Stamp was going to see coming from the PC com port. This data of course contains the ASCII code for the particular relay I wished to switch on, or off. If I also wished to have the facilities to switch on and off multiple, or all relays in one go I could also do this with the one data byte.

Pin 13 (bit 7) of the Stamp was then selected to use as the serial input (see circuit diagram fig 2). Note the strangely simple connection from pin 3 on the DB9 connector to pin 7 on the Stamp and the lack of a RS232 line receiver - only a 22k resistor limiting the current, apparently Parallax included clipping diodes on all the inputs so the Stamp will accept the + and - RS 232 signals with ease.

Pin 12 (bit 6) of the Stamp was chosen as the serial output and is connected directly to the DB9 connector pin 2. You may ask where the RS232 line driver is. Well, Parallax say in their manual "The Stamp's serial output uses 0-5 volt levels, so it may not drive RS232 devices without additional circuitry. We have found however, that most PC serial ports will work without additional circuitry".

Do you think they are telling you porkies here? Well they are not the three totally different PCs I tried the project on, all worked well at 2400 Baud.

However, if you intend to use the project over long lines then you should consider using line driver/receivers such as the MAX 232.

Finally, pins 6 through 9 are used to drive the relays (see fig 2) via a 75492. The 75492 is really a MOS digit driver that I found in my parts box, which is capable of sinking the relay currents at the required 12 vdc so I pressed it into service for this project.

D1 through D4 are 1N4001 diodes to protect the Driver IC from relay back EMF, LEDs 1 through 4 and their associated resistors give visual indication which relays are switched on. The relays used are 12vdc types RS part number 349-658. This brings us to another Basic Stamp instruction, PINS. First you set up the direction you want the data to flow either in or out. The instruction for this is DIRS. This can be in decimal hex or binary - just add the appropriate prefix symbol nothing for decimal, \$ for hex, and for binary, pick the pins you wish to use as input they are signified by a '0', then pick the pins you wish to make outputs signified by a '1'.

In our case we would start the programme with a line that looks like this DIRS =%00001111. This will set up the pins in binary, RBO—RB3 will act as outputs RB4—RB7 will be inputs.

After setting up the DIRS we just issue the statement (let's say) PINS = \$0F and all the relays switch on.

Serial relay controller software

I remember not so long ago been asked to design and build a Relay controller similar to this project, using a 1015 UART all in hardware and one of the constraints was that it had to fit in a box not bigger than 4 x 4 x 2 inches.

After looking at the size of the UART chip, the baud rate generator and all the support devices needed, it looked like an impossible task and indeed it was. It ended up on a piece of 8 x 4 inch strip board, and that did not include the Transformer or Relays.

The moral of this is why use complicated hardware when

with a little software you can do it better with a Basic Stamp.

The whole programme for the Serial relay controller fits in just 13 lines of code, so there is plenty of scope left to expand on the basic theme.

Referring to figure 3 Software listing, notice the familiar DIRS statement setting up the pins. Line 2 declares a label; this is signified by the colon following the word loop; this is followed by a statement to zero out b3 separated by a colon from the now familiar SERIN (Multiple statements can be included in Stamp Basic use a colon to do the separation.

Line 3 tells the program to gosub to label 'txout' on line 12. This line retransmits the contents of b0 and b1 back to the PC to signal that it has received the transmission, line 13 returns the programme back to line 4.

As I mentioned earlier, a lookdown table is used to convert the ASCII characters received in b1 back to a binary number the Pins can handle.

The Stamp handles the lookdown table like so; first give the Stamp the instruction LOCKDOWN, then the register it is going to find the data, in our case b1. After this, give it a series of ASCII numbers (48, 49) (the table) Finally assign it a register to store the result b3.

In our case, during operation, the lookdown instruction will look through all the numbers in the table, until it finds a match for the ASCII character it has stored in b1; if it does not find a match it ignores the line and b3 stays set at '0'.

If it does find a match it counts which number it was from left to right within the table. If it is the first number in the table b3 will store the number '1', if it is the fourth number in the table b3 will store the number 4, and so on.

Notice that the numbers in the table are the ASCII numbers 0 through 9 and uppercase A through F, or 0 -15 in binary; b3 will be used later in the programme to operate the relays indirectly.

Line 5 looks to see what character was transmitted into b0 and directly analyses the ASCII character, hence the quotation marks around it. If the character "k" is not found, the programme moves to line 6.

If the character "k" is found (switch on) then the programme jumps to the label 'swon' line 8. At this point the PINS instruction comes into action. The outputs on the lower four bits of the Stamp will assume the result of the OR operation, based on the present state of the lower 4 bits (pins 6, 7, 8, 9) ORED with b3 (remember our LOOKDOWN table stored b3), note the OR symbol:

As can be seen from the line we have just looked at, the OR operator will switch on further relays as instructed by the last PC transmission but will mask off any that are already switched on, leaving them in the on state.

Line 11, GOTO returns the programme to the 'loop' label line 2, and the processor waits for the next character to be transmitted from the PC.

In the above we assumed that the Stamp had received the "k" character in b0. However, it could easily have been the "L" character (switch off).

Figure 3. Basic stamp serial relay driver, basic programme listing.HEXRS.TXT

```
1DirS =%00001111 `Set up the pin directions
2loop : b3=0 : serin 7 ,n2400, (">00") ,b0 ,b1
`Zero b3,set pin 7 ser input
3gosub txout `GOSUB to label txout and Return the
data to the PC
`Select the Hex ASCII code and put it in b3
4 lookdown b1, {43, 49, 50, 51, 52, 53, 54,
```

```

55, 56, 57, 65, 66, 67, 68, 69, 70), b3
5   if b0 = "K" then swon `If lead in char in b0
   is "K" then goto label swon
6   if b0 = "L" then swoff `If lead in char in
   b0 is "L" then goto label swoff
7   goto loop
8   swon: pins = pins : b3 `OR the PINS with b3
   and set PINS
9   goto loop
10  swoff : pins = pins&/b3 `AND/NOT the PINS
   with b3 and set PINS
11  goto loop
12  txout : serout 6,n2400,(13, 10, ">00", b0
   ,bl," received", 13,10)
13  return

```

NOTE Line numbers are for reference only and are not included in the programme, Stamp Basic uses labels as line identifiers.

The programme in this case would have analysed line 6, and moved to the label 'swoff' line 10. Here we go again with the PINS instruction except this time we do an AND/NOT operation, then the result is put on the lower 4 bits (pins 6,7,8,9) of the Stamp. Again note the AND/NOT symbol &/.

This again checks the relay output pins and makes sure that only the relays instructed in the last transmission will be switched off and the rest will stay on.

Line 11, GOTO the label 'loop' instructs the programme to return to line 2 and wait for another transmission from the PC.

Talking to the Stamp from the PC

Well that's your department, as I do not know what communications programme you are using. You may wish to write a BASIC programme, or in some other language; I can only give you the codes you use to switch the relays on and off. Here are some tips though.

First thing is to make up a suitable transmission cable with female DB9 connectors at either end, the PC transmits out on pin 3 and pin 3 on the Stamp end is set to receive so connect pin 3 to pin 3 on the DB9 connectors.

The PC receives data on pin 2 and the Stamp end is set to send data on pin 2 so, again, connect pin 2 to pin 2 on the DB9 connectors.

We also need a ground or earth. This will be pins 5 at both end of the DB9 connectors.

NOTE: You may have to experiment some with the above.

With some comms programmes, the PC may refuse to send out data until the handshaking lines have been either Jumpered or disabled in Software. In this case, you have no alternative but to read the appropriate manual, to find out how to do it.

Set your baud rate to 2400,8 data bits, no parity, 1 stop bit put your comms into terminal mode; Teletype will do just fine.

Make sure you do not have a modem selected; this contains lead in characters for the modem itself. Turn on the local Echo so you can see what you are typing to avoid confusion.

If you have Windows, you have it made. Go into terminal and set up the above, and you are online.

Codes to send to the Stamp

it does to switch . The relay off the data byte is transmitted as ASCII but formatted in Hex for transmission.

If you wished to switch on relay '1' and leave all the others off you would type >00K1 and relay 1 would switch on. If you already had relay 1 switched on and wanted to switch it off, you would type in >00L1 and the relay would switch off.

As can be seen from Figure 3, the ASCII characters matching the Hex numbers 0-9 and (uppercase) A-F. This is to enable you to switch on any or all of the relays with one byte of data instead of having to switch on individual relays with separate transmissions
Example: Typing in >00KF would switch on all the relays and as the same applies to switching off relays >00LF would switch them all off. Individually the relays can be switched on and off

using using the following codes
Relay 1 >00K1 (on) ,>00L1 (off).
Relay 2 >00K2 (on) ,>00L2 (off).
Relay 3 >00K4 (on) , >00L4 (off).
Relay 4 >00K8 (on) , >00L8 (off).
welcome datacomp

When typing in the codes for transmission, type exactly as it appears above; do not include spaces ,if you type in lower case the Stamp will ignore the transmission.

What can I use it for?


The Basic Stamp is a quick and easy method of getting your project up and running fast. After that, you could machine code it into one of the cheaper Pics for production use. Although I can see it being used in its own right (SIP Version) in limited production situations such as programmable thermostats, serial transmission humidity detectors, and portable equipment applications.

Maybe I will get to try the 24 pin version next.

BASIC Stamp -Stamp sized Computer runs BASIC


The Basic Stamp by PARALLAX measures only 40x60mm yet is a true microcomputer that runs BASIC programmes written on your PC. Its size, ease of use and extensive I/O features make it an ideal tool for both educational and industrial applications as well as for the serious hobbyist.

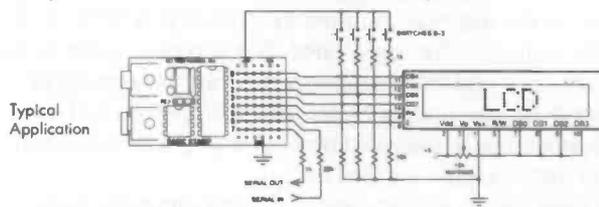Writing programmes for the Stamp is easy. A 3-pin cable connects the Stamp to your PC printer port. One piece of software is used to enter, debug and download your programme. Features include 8 I/O lines, non-volatile memory, serial comms, pulse measurement and PWM; all achieved with a minimum of external components.



The BASIC Stamp Development Kit at £99 includes; 1 BASIC Stamp, instruction manual, PC cable, software and extensive application notes. Further Stamps are available from £29.

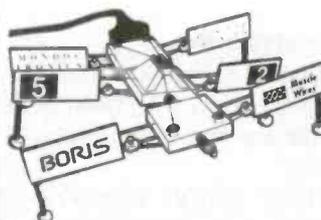Muscle Wires -wires that contract when heated!



Fascinating, highly processed Shape Memory Alloy wires that actually contract when electrically heated producing a useful amount of force.

Low cost linear actuators at last!
Their light-weight makes them excellent for use in models, robots and many other types of project. Low voltage and power allows simple control by computer or electronics (eg The BASIC Stamp).
Detailed Data and Project Book (128 pages) plus Muscle Wire kit suitable for 13 projects including BORIS the walking, six-legged robot; only £44.95.

All prices excl VAT and £3 postage per order. For further details of the Stamp, Muscle Wires and other products please call for our NEW colour catalogue.

MILFORD INSTRUMENTS

24hr Answerphone : 01977 683665, Fax 01977 681465
Milford House, 120 High Street, South Milford LEEDS LS25 5AQ

Is your PCB design package not quite as "professional" as you thought? Substantial trade-in discounts still available.

Board Capture

Schematic Capture Design Tool

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

£395

Board Maker

BoardMaker1 - Entry level



- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount and metric support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

£95

BoardMaker2 - Advanced level

- All the features of BoardMaker1
- Full netlist support- BoardCapture, OrCad, Schema, Tango, CadStar
- Full Design Rule Checking both mechanical and electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator- Database ASCII, BOM
- Thermal power plane support with full DRC

£395

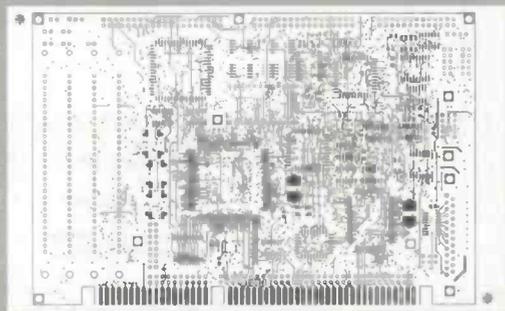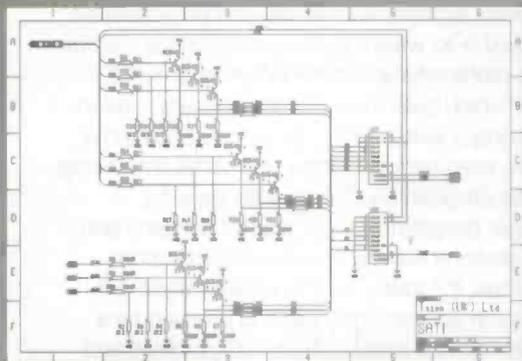

Board Router


Gridless re-entrant autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

£200

Output drivers - Included as standard

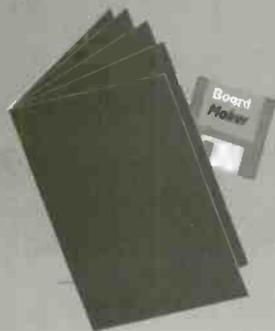- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill and Annotated drill drawings (BM2)



For further information contact

Tsien (UK) Limited

Aylesby House


Wenny Road, Chatteris

Cambridge, PE16 6UT

Tel 01354 695959

Fax 01354 695957

E-mail Sales@tsien.demon.co.uk

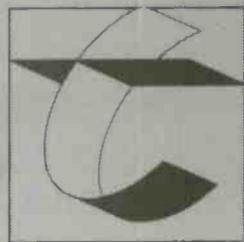

tsien

Designing a Pic Micro controller based project

PART 3

In part 3 of this short tutorial series, Bart Trepak continues his construction of a PIC based alarm clock

Last month's article dealt with the instruction set for the PIC and developed the circuit for the digital alarm clock. This month, we will deal with developing a flowchart and writing a programme to generate a time base for the clock and also discuss the use of an assembler programme.

Timebase

The most important part of the clock is the timebase which the clock counts to determine when each second, minute or hour has passed. This can be any regular waveform such as the 50Hz mains or that obtained from a crystal oscillator. This circuit uses a crystal oscillator making it independent of the mains supply, but the same basic programme could be used for a 50Hz system, taking into account the much lower frequency. This part of the programme will be tackled first but,

before we do this, it is perhaps useful to look at how this would normally be done when using a microprocessor and then how it can be done using the PIC15C54.

In a microprocessor system, a timebase can be generated in two ways. One way is to write the programme in such a way that all programme paths take the same length of time to execute. No matter which path the programme takes, due to, say, someone pressing a switch or not pressing it, the same number of steps are executed resulting in the same time being taken to execute the programme. This can be done by breaking down longer programmes into shorter sections and padding out short sections with NOP instructions or other short sequences. Thus, if it takes, for the sake of argument, 100uS to execute each section, then this can be used as a time base. A counter can be initially set to 100 (decimal) and decremented each time such a segment of code is executed.

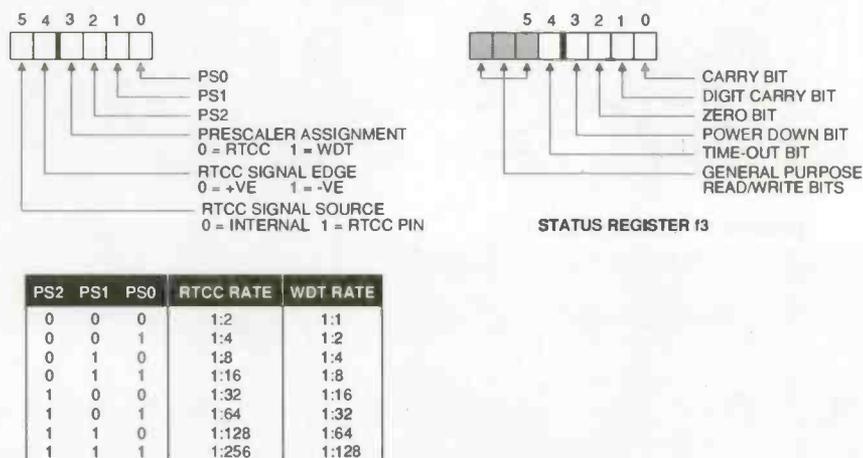


Fig.2a. Pictorial representation of data memory in PIC

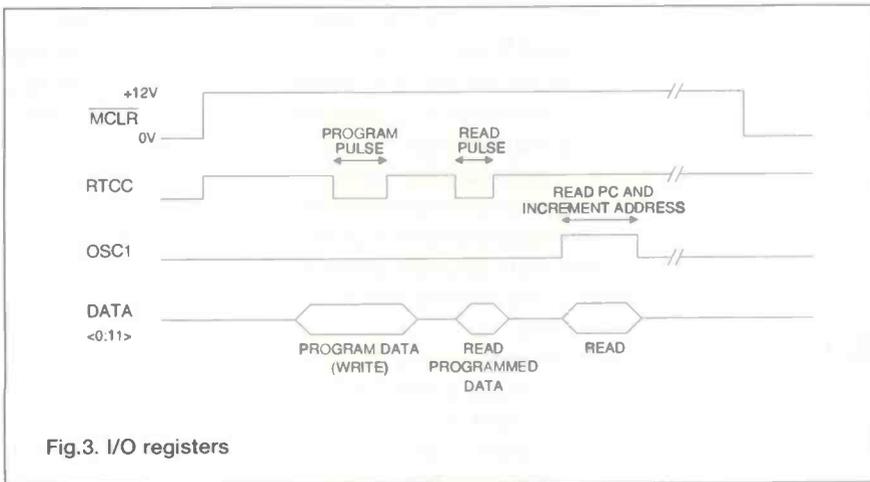


Fig.3. I/O registers

It would therefore reach zero every 10mS which could be further counted (divided) to obtain seconds, or half seconds or whatever. Quite mind-boggling, especially in a complicated programme with many different paths and, if the processor has a counter/timer, this is often used instead.

With this method, the counter/timer is loaded with a number and then decremented, either in response to a signal at an input pin (such as the 50Hz mains frequency) or by an internal signal obtained from the micro-processor clock which, if a crystal oscillator is used, would also be a regular frequency. Since this goes on independently of the processor, the processor can get on with the other tasks that it has to do, such as driving the displays, scanning keyboards etc. When the counter reaches zero after some required period of, say, 0.01 second - which of course depends on the number originally loaded into the counter and the frequency at which it is decremented - an interrupt is generated. This causes the processor to suspend execution of the current programme and go to a subroutine which would increment another counter which after so many counts, 100 in this example, would increment the seconds counter and also the minutes and hours counters if required before resuming the original programme.

Although the PIC16C54 series micro controller has a counter/timer (RTCC f01), it does not support any interrupts, so a slightly different approach must be used. The RTCC counter can be incremented automatically by the crystal oscillator or by a signal to the external RTCC input pin. Here it is also loaded with a suitable value but it must be read each time it is incremented to ensure that the zero state is not missed. Otherwise, the counter would simply overrun and start counting again leaving no indication that the zero point had been reached and passed. From this it would seem that there would be very little time to run any other programme because each read instruction would increment the counter and would need to be followed by another read and another to ensure that the zero state had not been missed. However, if the original number loaded into the counter was, say, 100, then after a zero was detected we could execute, say, 90 or so instructions before returning to the programme to read the RTCC counter and still be sure that the next zero had not been missed. (Note that the RTCC register can only be incremented and not decremented by the clock so to count to 100 it would need to be initially loaded with 156 decimal so that it reached 256, the equivalent of zero since the maximum count is 255, after one hundred counts.) The PIC also has a prescaler which can be set to give a division ratio of up to 256,

allowing the RTCC counter to be incremented at a much lower rate than the crystal frequency to provide a slower time base.

If a 3.2768MHz crystal is used in the oscillator and the prescaler division ratio set at 256 by suitably programming the OPTION register, the RTCC register will be incremented at a frequency of 3200Hz (i.e. 3276800 divided by 4, divided by 256). By loading the RTCC register initially with 224 decimal, the zero state (equivalent to a decimal count of 256) will be reached after $256-224=32$ cycles, giving a period of $32/3200=0.01$ Sec or 10mS. Therefore, as soon as the RTCC zero is detected, the processor can deal with this and then

happily execute the rest of the programme safe in the knowledge that another RTCC zero would not occur for another ten milliseconds. During this time, it would need to execute the whole programme, including displaying all the digits, reading the switches, adjusting all the counters, comparing them to the alarm time set and switching on the buzzer if required. As long as this took less than 10mS, it could get back to reading the RTCC before it reached zero again. This may sound like a tall order until it is realised that a 3.2768MHz oscillator, even when divided by four, will result in an instruction time of 1.2uS, thus enabling some 8,000 instructions to be executed in this time!

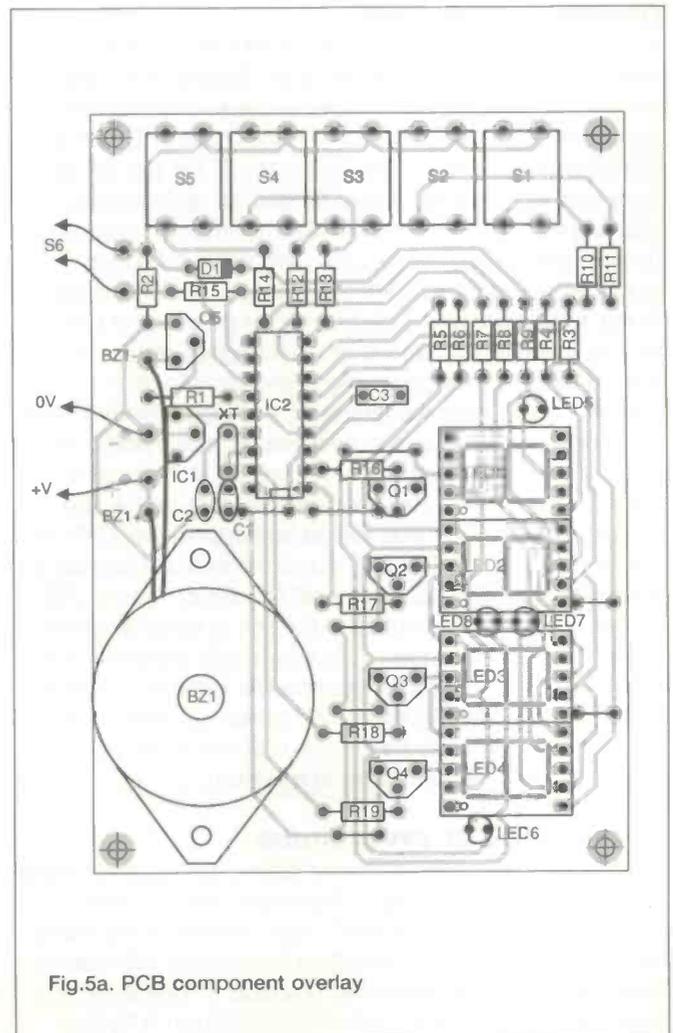


Fig.5a. PCB component overlay

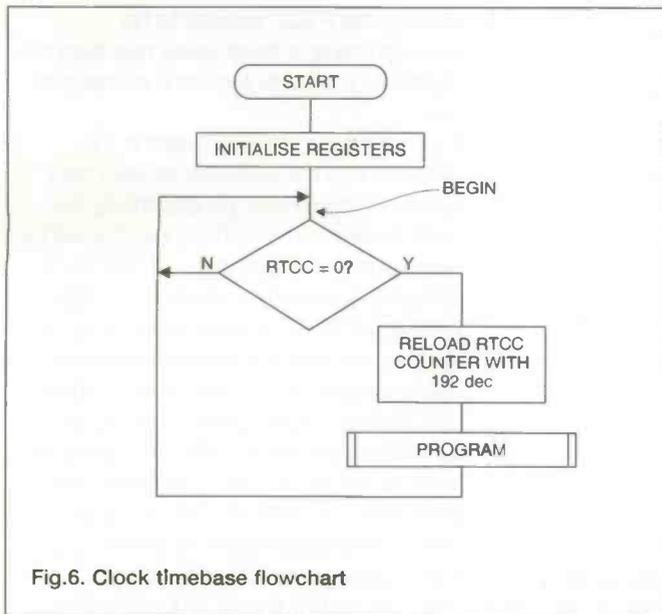


Fig.6. Clock timebase flowchart

After each 10mS period, it is an easy matter to decrement another counter which, if it is initially loaded with 50 decimal, will reach zero every 0.5 Seconds (to flash the colon) and this can be further divided to give seconds, minutes and hours. Note that a 10mS period is chosen because this will also determine the frequency with which the display is refreshed and lower frequencies could cause the display to flicker since each digit is only on for a fraction of the 10mS period.

Timebase flowchart

A basic flowchart can now be drawn for this part of the programme and this is shown in Fig 6. Starting at the point marked BEGIN, the RTCC counter is checked to determine if it has reached zero. If it has not (N), it goes back to BEGIN and checks again. Eventually (once every 10mS) the test will be successful and the programme will take the other branch, reloading the RTCC counter with 224 decimal and executing the part of the programme marked PROGRAM. This will eventually consist of the various counting operations, display driving, keyboard reading etc but, for the purposes of testing this part of the programme, it simply complements port A and then goes back to the beginning as shown in fig 6b.

Before this programme can work, the microcontroller must be set up to run it. When it is powered up, all the ports are configured as inputs and, if it is required (as in this routine) to connect an oscilloscope or frequency meter to port A, then this port must first be made into an output port. The OPTION register must also be set up to assign the internal prescaler to the internal instruction clock and set the division ratio to 256. These functions are performed in the part of the programme marked INITLSE and shown in fig 6a. As with the part marked PROGRAM, this will also be expanded as in the final version the initial conditions at power up of the various other counters (not yet defined) will also need to be specified in this part of the programme when we come to add them.

The Assembler programme

The flowchart must now be converted into a programme using the instructions shown in fig 3. The micro-controller itself, however, does not "understand" these instructions any more than it understands the flowchart as it deals only with data in binary form (machine code) which consists of 1s and 0s. A programme written using the mnemonics shown in fig 3.

(called the source code) will therefore have to be converted into this binary form at some stage before it can be loaded into the EPROM on the chip and executed. This could be done by hand, by converting each instruction into its binary equivalent by looking it up in a table, for example. All these 1s and 0s could then be loaded into a programmer (bit by bit or typed in, depending on your programmer) and a chip blown. This would be a very tiresome and error prone process which, thankfully, is not necessary because special programmes called Assemblers are available which do the job quickly and with no errors.

An Assembler programme for the PIC series of micro-controllers is available from Microchip Technology which runs on a standard IBM or compatible PC and converts the source code into machine code. The mnemonics (or source code) are simply typed into the computer using any standard word processor programme which can produce ASCII code and the Assembler programme produces the machine code version ready to load into the programmer. To do this, however, the mnemonics have to be written in a special format so that the Assembler programme can operate on it and the rules for this are shown (and explained) in fig. 7, together with a typical listing.

Assembler programmes from other suppliers may have different features and different protocols to those discussed here. Even upgraded and later versions from the same supplier may also have changed in some details. The reader should, therefore, consult the manual supplied with the particular Assembler programme before use and regard what follows as typical of most Assemblers but not necessarily correct for your particular one.

Before going on to write the mnemonics for the timebase programme, it would be useful to discuss some of the advantages of a typical Assembler programme. This would have a number of features which are very helpful to the programmer beyond simply converting the mnemonics into machine code. Often in a programme, instructions will refer to registers such as the RTCC (01) or PORT B (06) as well as other registers which the programmer may wish to invent such as MINCTR (ie. minute counter) which would be assigned to one of the general purpose registers such as 09 for example.

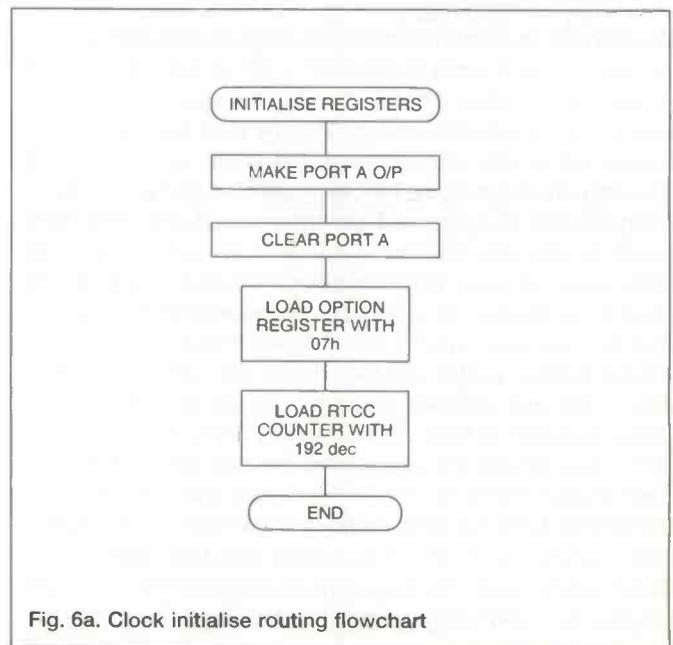


Fig. 6a. Clock initialise routing flowchart

In a complicated programme, where many registers are being used, it would be difficult to follow the operation if all the registers had to be referred to as 01 or 09 and the programmer would need to keep referring to a list to know which register was which and what it was doing to be able to follow the programme. The assembler programme therefore allows such registers to be defined before the programme is run so that instead of typing 01 or 09 the programmer may write RTCC or PORTB or even MINCTR and leave the programme to interpret this as required.

Many of the often used symbols such as the special function registers RTCC, PORTA, STATUS and so on together with words like "zero", "w" and "same" can be assigned values such as 01, 05 and 03 or 0, 1. As these would always be the same for every programme using the PIC (the RTCC register is always register 01 for example), to save having to type them in at the beginning of every programme these can be stored in a separate list which can be included in the programme listing by using the "include" statement. An example of such a list (PIC.H) is shown in FIG. 8 where for example RTCC is equated (equ) to 01h and PC equ 02 and so on. Programmes may now therefore be typed using instructions such as MOVF PORTA,w instead of MOVF 05,0 which makes the whole listing much easier to understand and the assembler will substitute 05,0 or the binary equivalent of this in the instruction when it is run. Thus although from the timebase listing shown in FIG. 9 it may appear that RTCC, PORTA etc. have not been defined, this has in fact been done by the "include PIC.H" statement. Another extremely useful feature is the ability to use labels to mark points in the programme. In FIG. 7, for example, there is a point marked BEGIN to which the programme has to go to if the RTCC register has not reached zero. Normally, the programmer would use a "goto k" instruction in this situation where k is the address (in binary or hex) of the point in the programme where BEGIN is located. While this may be easy to work out for the timing programme now, as more instructions are added to the INITIALISE routine the point marked BEGIN will move to another address and the k in the "goto" instruction will need to be changed. With many "goto" instructions to keep track of, only some of which would need changing as new instructions were added, there would be many mistakes and finding them would be extremely difficult. Instead, the assembler allows the programmer to write "goto BEGIN" and as long as there is only one unique label called BEGIN, the programme will alter the address for all the "goto" instructions affected as more lines are added and the programme re-assembled.

This is not the end of the story and some assembler programmes offer other features such as a Macro capability. Macros allow solutions to frequently used functions to be designed and stored as self-contained programmes. These may be added to a programme as required without having to re-define register names and avoid the tedium of re-typing the same programme sequence each time it is used in a new application. A discussion of these is beyond the scope of this article but they are described in the manual supplied with the programme

CHOOSING YOUR OPTIONS

We are now in a position to convert the flowchart to a source code programme using the mnemonics and a solution to the timing programme is shown listed in FIG. 9 using the layout outlined above which will allow the assembler programme to

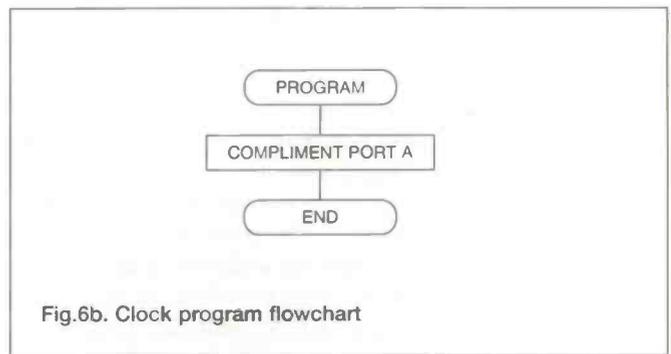


Fig.6b. Clock program flowchart

interpret it correctly and convert it into object code (the binary 1s and 0s) required to programme the device. This can now be explained in detail and compared to the flowchart of FIG 6. The INTLSE routine starts by setting up the I/O ports which, as mentioned, are all inputs at switch on. This is done by first loading the W register with a binary number (putting 0s in the bits which are to be programmed as outputs) using the "movlw" instruction. This moves the literal number (specified as 00h in this instance which is of course 0000 0000 in binary) into the W register and this is transferred to the TRISA register using the "tris PORTA" instruction to make port A an output. Note that in the case of port A, only the lower four bits are used since the port is only four bits wide, so that the hex number could just as well have been X0h (where X is any valid hex digit). This does illustrate an important point as far as the Microchip assembler is concerned however and it is that all hex numbers must start with a numeral so that F0h, A5h, C3h etc. would not be acceptable and would generate an error and so would have to be written as 0F0h, 0A5h or 0C3h while numbers such as 9Fh or 5Bh would be interpreted correctly. If the port A were to remain as an input, then of course, nothing would need to be done while if a mixture of inputs and outputs were required on a port, then the literal loaded into W would have a number with 0s corresponding to outputs and 1s corresponding to inputs in it. These I/O lines may change during the course of a programme as some subroutines may require certain lines which were outputs to function as inputs or vice-versa so the "tris" instructions may be used again at the beginning of some subroutines. Even if none of the lines are required to change, it is often a good idea to redefine input and output ports at intervals during the execution of a programme because in noisy environments, the TRIS registers could become corrupted with disastrous results as far as the programme is concerned.

The rest of this routine is similar and simply loads different values into W using the "movlw" instruction and transfers them to the required register such as the OPTION and RTCC registers using the appropriate instructions "option" (which loads the OPTION register) and "movwf" (which moves the value in W into the register specified).

As mentioned in PART 1 of this series, the OPTION register is a special register which allows the programmer to define how the RTCC counter will work. By setting or clearing certain bits in this register the prescaler may be set for a division ratio from 1:2 to 1:256. The signal source for the RTCC counter (ie internal clock or external pin) as well as the signal edge (positive or negative going) on which the RTCC is to be incremented can also be defined. Setting bit 3 enables the internal prescaler to be assigned to the Watch Dog Timer. In this project, a division ratio of 1:256 is required with the internal signal source and the prescaler assigned to the RTCC register and from FIG 2a. this translates to a value of XX0X

0111 in binary (where X is don't care) so a value of 07h will give the required results.

The timing routine starts at BEGIN and uses the "movf RTCC,w" instruction which causes the zero flag to be set in the STATUS register if RTCC=0 without actually changing the value in the register. This flag is then tested using the "btfss STATUS,2" instruction which skips the next instruction if the zero bit is set. If it is not set (ie. RTCC is not zero) the next instruction "goto BEGIN" is executed which takes the programme back to BEGIN to check the RTCC for zero again. If RTCC is zero, then the "goto BEGIN" instruction is skipped and the RTCC is re-loaded with the value .224 by the instructions "movlw .224" which moves the binary equivalent of 244 into the W register and "movwf RTCC" which moves the contents of the W register into RTCC. After this, the rest of the programme PROGME (called PROGRAMME in the flowchart) is executed.

In this case, as mentioned, the PROGME routine consists of simply complimenting output port A so that it can be monitored on an oscilloscope or frequency meter to test that the timebase is operating correctly which is done by the instruction "comf PORTA" followed by "goto BEGIN" which will return the programme back to BEGIN to check the RTCC for zero again. Once the programme has been checked, this part will be deleted and replaced by other routines for updating counters, driving displays, reading the key board and doing all the other operations required.

The "ORG 1FF" statement at the end of FIG. 9 sets the programme origin and this is the address 1FFh which is the point that the PIC16C54 starts from following a power on reset. The first thing that the PIC does after this is to increment the Program Counter (which overflows to zero) and the first instruction is therefore fetched from the EPROM at address 0. This is the "goto START" instruction shown on FIG. 9 and causes the programme to jump to the location of the label "START" which in this instance happens to be the next instruction anyway and seems pretty pointless. In this

```
This file defines labels for ports, reset
vectors, registers etc. for the standard PIC
parts. It is saved under the name PIC.H
```

```

;
;
PIC54          equ          1FFH
;define reset vectors
PIC55          equ          1FFH
PIC56          equ          3FFH
PIC57          equ          7FFH
;
RTCC           equ          01H
;define registers
PC             equ          02H
STATUS        equ          03H
FSR           equ          04H
;
PORTA         equ          05H
PORTB         equ          06H
PORTC         equ          07H
;
w             equ          0H
same          equ          1H
```

Fig 8 Program Include Statement

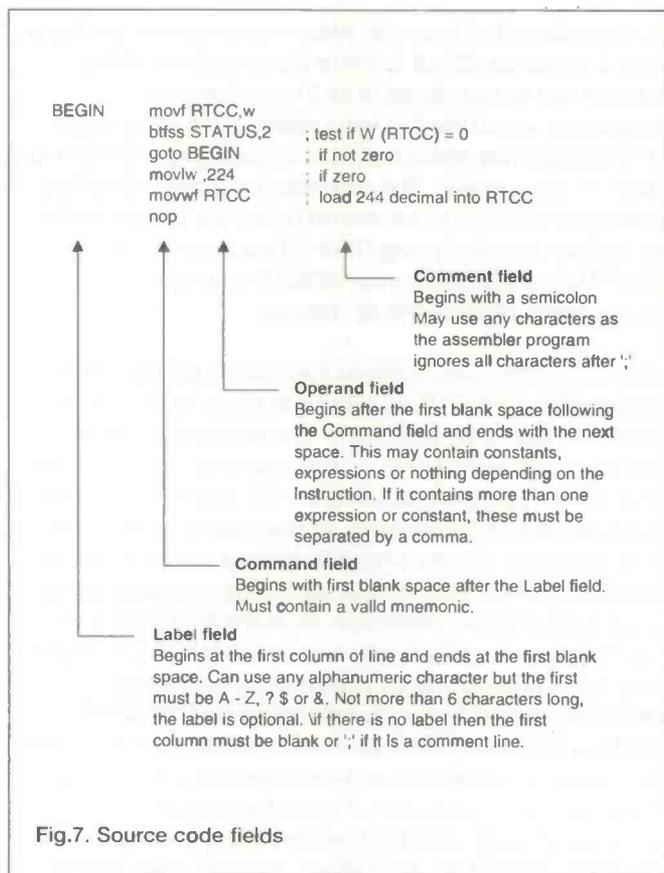


Fig.7. Source code fields

simple programme it is and the initial "goto START" instruction could be left out but with more complex programmes, the start of the programme will in all probability not be at the beginning especially when subroutines are used as we shall see later. Finally the "END" statement is required to tell the assembler that there are no more instructions to be executed. Anything after the END statement will be ignored by the assembler.

FROM PAPER TO SILICON

As mentioned earlier, the micro-controller does not understand the mnemonics that have been used so far and the programme has to be re-written in binary with 1s and 0s and this is the job of the assembler programme which is supplied with the chip programmer for the PIC or can be downloaded from Microchip Technology's bulletin board via a modem. All that needs to be done is to type the programme of FIG. 9 into a PC using a standard word processor programme and stored in a file called say CLOCK.ASM (the .ASM extension presumably stands for "assembler code" but it is in fact a standard ASCII file).

Once this has been done the assembler programme is run and this goes through the CLOCK.ASM file and checks that there are no errors such as "goto BENIG" which tells the programme to branch to a label which does not exist, or two or more identical labels have been used. It also checks that correct extensions have been used on instructions which specify a file register address and destination and that all subroutine calls end with a return "retlw" instruction. What it cannot do is tell if the programme is logically correct and does what the programmer intended it to do. That is up to him!

When this programme has run (which takes a few seconds depending on your machine) it will show any errors encountered on the screen. Errors are specified by the line

number where they occur together with a brief description and how serious the error is eg. fatal or just a warning that something may be wrong. These have to be corrected before the next step can be taken and will involve going back into the CLOCK.ASM file, making the necessary corrections and re-running the assembler programme again. When the assembler has been run and no errors have been detected, the programme will have generated a number of files called CLOCK.LST, CLOCK.OBJ and various other output files. Some of these are required for use with the simulator programme and will not be discussed here. The .LST file is a copy of the .ASM file with the location or programme counter and object code (the code that will be loaded into the EPROM in the micro-controller) also shown together with the line numbers. This makes it possible to locate any errors which are reported when the assembler programme is run but it is the .ASM file which needs to be corrected. Most mistakes are usually simple typing errors and are easily found. At the end of the .LST file there may also be a cross reference table listing every symbol used and which lines it appeared on. The .OBJ file contains the object code (the 1's and 0's) which can be loaded directly into the chip using a suitable programmer. This file can be output in different formats for use with Microchip's and other manufacturer's programmers. Microchip also supply a software simulator which enables the programme to be executed or single stepped one instruction at a time on the host PC or compatible computer while selected registers are displayed on the screen. This is useful

in finding some faults in a programme which would not be apparent from the logic. It is also possible to change inputs at various stages in the programme execution to see what effect these have and show up any faults which may then be apparent. Another useful feature is the ability to set "breakpoints" in the programme to make the programme stop when it reaches a particular address in its execution, enabling the user to single step the programme from that location while executing sections of the programme known to be working quickly. The use of this programme will not be discussed but it is very easy to use and can be very useful in finding tricky faults when the processor does not seem to do what the programmer intended. Using the simulator and observing how each register changes following each instruction will usually reveal the source of the trouble. A suitable programmer is now required to programme the chip with the code generated by the assembler. There are many programmers on the market and some have even appeared as constructional articles in hobby magazines. A low cost programmer, the PICSTART 16B is also available from Microchip Technology which is a small printed circuit board with a socket to accept an 18 or 28-pin micro-controller. This is powered by a small d.c. supply and connected to a serial port of the IBM compatible PC via a cable (all supplied). As well as this, the pack contains the Assembler and Simulator software together with data books manuals and a few sample chips all for around £120. The software supplied allows the assembled machine code (in this case the CLOCK.OBJ file) to be sent to the programmer module and a chip programmed. During this procedure, the Oscillator configuration fuses must be set to "XT" and the WDT fuse set to disable the Watch Dog Timer function which is not used in this design. The details for doing this will depend on the programmer used so the user is referred to the manual supplied with the programmer. Assuming that the printed circuit board shown in FIG. 5a has been constructed, the programmed chip can be plugged into the socket and any port A pin checked to see if it has a 50Hz signal on it which would prove that, so far at any rate, the programme is working correctly. Alternatively, the chip itself may be connected up to a crystal as shown in the circuit diagram on a breadboard and the operation checked. Sooner or later however, the displays and keyboard will need to be checked so it is probably as well to build the circuit to begin with on a printed circuit board and perform all the tests on this. The chip can now be erased using a UV EPROM eraser and the next new piece of code developed for the clock. This will in turn be added to the current programme and the process repeated so that the full programme for the clock will begin to take shape.

```

;
LIST P=16C54      ;f=inhx16
INCLUDE iPIC.Hf
;
goto START
START      nop
;
;INITIALISE ROUTINE
INTLSE     movlw 00h      ;ie 000 000
           tris PORTA    ;make PORTA o/p
           movwf PORTA   ;make PORTA 0000
           ;
           movlw 07h     ;ie 0000111
           OPTION        ;int signal, L to H,
                           presclr 256 to RTCC
           movlw .224     ;move 224 decimal into
           movwf RTCC    ;RTCC - gives 10mS with
                           3.2768mhz xtal
           ;
BEGIN      movf RTCC, w
           btfss STATUS, 2 ;test if w (RTCC) = 0
           goto BEGIN     ;w (RTCC) not zero
           ;
           movlw .224     ;if RTCC=0 move
           movwf RTCC    ;224 dec. into RTCC
PROGME     comf PORTA, same ;switch port A on
           and off
           goto BEGIN
           ;
           ;
ORG 1ffh
END

```

FIG. 9. Code for CLOCK.ASM TIMEBASE (seeFlowchart 6)

Next Month...

Next month's article in this series will deal with LED display driving and counting techniques and introduce some of the other instructions available to the programmer.

8088

Interrupt based control computer

PART 2

The first part of a new computer project designed by R. Grodzik based around the popular 8088 processor and specifically designed for multitasking control applications

F Last month we looked at the overall design of a multitasking 8088 processor based single board computer. In this issue we continue by first looking in greater depth at one of the key features of a multitasking system, the hardware and software interrupts

Interrupts can occur by hardware (external) or software (internal) means. The hardware interrupt system is controlled by the 8259 peripheral controller. This chip is a complex IC and contains several internal registers which have to be initialised in order for the PIC to function. In a PC, the EPROM resident software known as the BIOS, runs on switch-on and is quite transparent to the user. This software locates all the hardware peripherals attached to the system and allocates an interrupt number (TYPE) to each. For example, the TYPE 9 interrupt activates when a key is pressed or released, a TYPE 14H occurs on the serial port. All these interrupts are termed 'hardware interrupts' since they are activated on the receipt of a positive going logic pulse on one of the 8259 PIC interrupt lines (known as IRQ lines on the IBM expansion slot).

Associated with the 8088 range of processors are internal 'software interrupts' which occur when certain conditions are met inside the processor. These are sometimes error conditions which occur when the software is liable to 'crash' i.e. a TYPE 0 interrupt occurs if a numerical division by zero is attempted. A pocket calculator will usually indicate an E or error condition. Both hardware and software interrupts can be evoked at any time in software by the use of the 'INT <TYPE>' instruction - useful in checking the effects of an external hardware interrupt without one actually occurring in hardware.

As previously mentioned, the PIC supplies the identity of

the hardware interrupt by sending an 8-bit <TYPE> number to the 8088. This TYPE number is internally multiplied by 4 by the 8088 to provide a 'pointer' (address) in external memory RAM which holds the start address of the interrupt service routine program. Since the start address consists of a CODE SEGMENT word and an INSTRUCTION POINTER word (CS:IP) - each pointer occupies 4 bytes. These 4 bytes are located in the bottom of the 8088 memory map (0000-01FFFH). For example, a TYPE 6 interrupt will generate a double word pointer of 0018H - an address location containing the IP offset pointer and 001AH - the next word location containing the CS of the interrupt service routine. When a TYPE 6 interrupt occurs, a double word VECTOR address of 001AH/0018H addresses external RAM and the 8088 'picks up' the CS:IP start address at this location in RAM, at which point the 16-bit CODE SEGMENT register and the 16-bit INSTRUCTION POINTER are loaded with these new values. The old CS:IP register contents are saved on stack, the interrupt program runs until a RETI (return from interrupt) software instruction is encountered, at which point the old CS:IP values are reloaded into their respective registers and the main 'background' program re-commences execution. Similarly, a software interrupt will generate an interrupt TYPE number which is again multiplied by 4 to provide a vector address in memory which contains the double word start address of the interrupt service routine.

In summary, if the background program is interrupted by a TYPE 6 hardware or software interrupt at address C123:4567H and, for example, the interrupt service routine for a TYPE 6 interrupt occurs at address F000H:1234H (CS:IP), RAM location 0018H must be loaded with 1234H and RAM

location 001AH must contain F000H. When the interrupt is generated, execution begins at address F000H:1234H. On a IRET instruction, the CS:IP registers are popped from the stack and loaded with C123:4567H, and the background program recommences execution.

The 8088 interrupt structure

Since at switch-on RAM contents are indeterminate, EPROM-based software has to load the relevant locations in RAM with the interrupt vectors of any hardware or software interrupt that may occur during the execution of the main 'background' program. This operation is described as the loading of interrupt vectors into the interrupt vector table - the interrupt vector table being the first two RAM page locations in memory. Since this information is lost on power-down, this process has to be repeated whenever the system is powered-up.

The 8088 SBC contains a 8155 peripheral i.c. which contains a programmable IO port, a timer and 256 bytes of RAM. This RAM is selected by the Y0 line of the 74138 decoder, allocating addresses 0000 to 00FFH for this area of RAM. Since this area is also used as a STACK only the lower addressing range is used to form the interrupt vector table.

The vector addresses for software interrupts are located at the bottom of memory, specific address locations which are unchangeable for the 8088/86 range of processors:

The first five locations of the interrupt pointer table are reserved for dedicated 8088 processor functions as follows:

Type 0, divide by zero.

This interrupt activates when a DIV or IDIV instruction produces a quotient that is too large to be contained in the results register. If this occurs, the 8088 automatically generates a type 0 interrupt.

Type 1, single-step

Usually this points to an IRET instruction. If the trap flag has been previously set, a single instruction of the user program will be executed, returning to the type 1 pointer.

Type 2, non-maskable (NMI)

Is reserved for interrupts generated by the NMI pin of the 8088. The IF flag status is ignored and therefore this interrupt will always be acknowledged, since it cannot be 'locked-out' or disabled.

Type 3, one byte INT instruction

Used to implement a breakpoint function in a system. If byte CCH (INT 3) is inserted in a program, execution of the program will stop when CCH is encountered, and a type 3 interrupt routine can then be used for example to examine the contents of the CPU's registers.

Type 4, INTO.

An interrupt will be issued conditionally, where the INTO

instruction is executed if the OF (overflow) flag is set.

Type 6, Undefined opcode.

Interrupt occurs if an illegal OP CODE is generated - by a faulty assembler or corruption of data.

Interfacing the PIC

The 8259 is a device specifically designed for use in real time, interrupt driven micro-computer systems. The bi-directional data bus (D0-D7) interfaces directly with the system data bus - control words, status information and interrupt vector information is transferred on this bus. The 8 interrupt lines of the 8259 labelled IR0 - IR7 can be programmed as level (high) or edge (low to high transition). When an external device raises any of these lines high, an interrupt (active high) signal is issued from the INT -pin17 output of the 8259 PIC.

This interrupt request signal is applied to the 8088 through the INTR (pin 18), - a logic active high input. Once the interrupt is recognised by the 8088, the CPU completes its current instruction and issues an interrupt acknowledge pulse from its INTA output (pin 24) to the 8259. Upon receiving an INTA signal from the 8088, the 8259 releases an 8-bit pointer onto the data bus which is read by the CPU. The INTA active low signal is also routed to pin 6 of the 74138 address decoder which tri-states the Y outputs, thereby preventing any data bus contention from other peripheral devices. The pointer value is derived from a combination of initial software programming of the 8259 and by a 3-bit value dependent on which IRQ line was activated. The CPU then uses this value to determine which interrupt service routine is executed for the relevant interrupting device.

Programming the 8259 PIC

The PIC needs to be initialised and programmed, so that each external interrupting device can be allocated its own pointer number. Each interrupt line on the 8259 will, when asserted, be allocated its own interrupt service routine. Additionally, individual IR lines can be prioritised and also disabled by software masking and thus preventing specific external devices from generating an interrupt. Since the 8259 is a fairly sophisticated device, only the basic programming details have been included, which should suffice for most purposes. The 8259 is similar to any other programmable peripheral device in that it contains internal registers which have to be programmed.

The sequence of programming the PIC is as follows:

Loading the command words.

Loading further control words, if required.


Three ICW (initialisation command words) words-ICW1, ICW2 and ICW4 are written to the internal registers by the CPU. An additional operational control word (OCW1) specifies which IRQ lines are enabled.

ICW1

The eight interrupt lines (IR0-IR7) of the 8259 will generate eight different pointer type numbers, which will each point to eight separate interrupt vectors in the vector table at four byte intervals. Level (high) or edge (+ve) triggering of interrupts is controlled by bit 3 of the ICW1 command byte.

ICW2

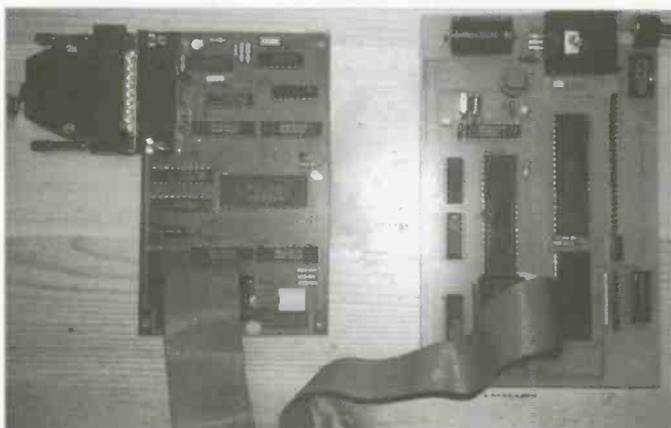The vector pointer generated by the 8259 when an interrupt is asserted is dependent on a combination of the initial programming of bits 3 - 7 of the ICW2 register and by the



contents of bits 0 - 2. Bits 3 - 7 of the ICW2 word remain common to all eight vector numbers, since they are written into the ICW2 register during the initialisation of the 8259. Bits 0 to 2 of the pointer type are generated internally by the hardware of the 8259-an interrupt on IR0 generates 0, 0, 0, an interrupt on IR7 generates 1, 1, 1. So for example. If the ICW2 was initialised as 20H, interrupt IR0 will generate a type 32 (20H) pointer, (the contents of ICW2 (0 0 1 0 0 0 0 0), whereas IR7 will generate a type 39 (27H) pointer - (ICW2 contents 0 0 1 0 0 1 1 1).

ICW4

The programming of the ICW4 register determines the action taken by the 8259 at the commencement and conclusion of the interrupt service routine. Interrupt requests are ordered in priority from 0 through 7, with an interrupt issued at IR0 having the highest priority. For a nominal mode of operation the ICW4 register is loaded with 13H: when an interrupt is acknowledged, further interrupts of a lower priority will be locked out until the INTA pulse is issued, which will automatically re-enable the interrupt mechanism once the IRET instruction of the interrupt service routine has been executed.

OCW1

An operational command word (OCW1) can be written to the PIC at any time during the execution of a program. Masking of individual interrupt lines of the PIC is achieved by writing a logic 1 at the corresponding IR positions of the OCW1 word, disabling the interrupt sources of that particular line. Writing FFH to this register will disable all of the interrupt lines.

Initialising the PIC

The example below shows how the 8259 may be initialised. Four command words-ICW1, ICW2, ICW4 and OCW1 are written into the control registers of the 8259. ICW1 is written into PIC base address 6000H, the remaining registers are written into at address 6001H.

```
ICW1 =17H ;edge triggered interrupt
;level triggered interrupt ICW1 = 1FH
ICW2 =20H ;bit3 to bit7 of pointer
ICW4 =13H ;Fully nested mode
OCW1 =00H ;all interrupts enabled
PIC EQU 6000H ;8259 peripheral base address.
MOV AL, ICW1 ;Write control words to PIC
MOV DX, PIC ;A0 = 0
OUT DX, AL
MOV AL, ICW2
MOV DX, PIC+1 ;A0 = 1
OUT DX, AL
MOV AL, ICW4
MOV DX, PIC+1 ;A0 = 1
OUT DX, AL
MOV AL, OCW1
MOV DX, PIC+1 ;A0 = 1
OUT DX, AL
```

Once the 8259 operational command and control words have been written, the device is active and will respond to an interrupt. The address of the interrupt service routine (interrupt vector) for each interrupting device has to be pre-written into the interrupt vector table. An interrupt on the IRQ0 line of the 8259 will cause a TYPE 32 (20H) pointer which, when multiplied by 4, the 8088 will result in a doubleword vector address found at locations 80H and 82H in RAM. The following program shows how the vector table is programmed for a base pointer of TYPE 32.

This model program will assemble to 2 Kbytes of ROMable code which will run on the 8088 board. On reset, the 8088 boot address (FFFF0H) will generate address location 07F0H of the EPROM area, at which a jump to start of EPROM (address FF800H) instruction will cause execution of the program. The assembler directive 'page , 132 will allow the listing (FILENAME. LST) to be printed in a small font 132 column format.

```
; INTERRUPTS
page , 132
CODE SEGMENT
ASSUME CS:CODE
; MAIN PROGRAM
CLI ;Disable interrupts
MOV SP, 0FFH ;Stack Pointer at RAM top
CALL VECTORS ;Load interrupt vector
CALL INITIALISE ;Initialise 8259
STI ;Enable interrupts

; Background Program
AGAIN: JMP AGAIN ;Wait for interrupts ;Repeat

; Load vector table
VECTORS PROC NEAR
CODE_SEGMENT EQU 0FF80H ;CODE SEGMENT

RAMTABLE =ICW2 ;ICW2 base TYPE 32 pointer
;Interrupt pointers for IRQ0-IRQ7
IRQ0 = RAMTABLE ;TYPE 32 POINTER
IRQ1 = RAMTABLE +1 ;TYPE 33 POINTER
IRQ2 = RAMTABLE +2 ;TYPE 34 POINTER
IRQ3 = RAMTABLE +3 ;TYPE 35 POINTER
IRQ4 = RAMTABLE +4 ;TYPE 36 POINTER
IRQ5 = RAMTABLE +5 ;TYPE 37 POINTER
IRQ6 = RAMTABLE +6 ;TYPE 38 POINTER
IRQ7 = RAMTABLE +7 ;TYPE 39 POINTER

; Load vectors into table
MOV WORD PTR DS:[IRQ0*4], OFFSET ISR0
MOV WORD PTR DS:[IRQ0*4+2], CODE_SEGMENT

MOV WORD PTR DS:[IRQ1*4], OFFSET ISR1
MOV WORD PTR DS:[IRQ1*4+2], CODE_SEGMENT

MOV WORD PTR DS:[IRQ2*4], OFFSET ISR2
MOV WORD PTR DS:[IRQ2*4+2], CODE_SEGMENT

MOV WORD PTR DS:[IRQ3*4], OFFSET ISR3
MOV WORD PTR DS:[IRQ3*4+2], CODE_SEGMENT

MOV WORD PTR DS:[IRQ4*4], OFFSET ISR4
MOV WORD PTR DS:[IRQ4*4+2], CODE_SEGMENT

MOV WORD PTR DS:[IRQ5*4], OFFSET ISR5
MOV WORD PTR DS:[IRQ5*4+2], CODE_SEGMENT

MOV WORD PTR DS:[IRQ6*4], OFFSET ISR6
MOV WORD PTR DS:[IRQ6*4+2], CODE_SEGMENT

MOV WORD PTR DS:[IRQ7*4], OFFSET ISR7
MOV WORD PTR DS:[IRQ7*4+2], CODE_SEGMENT

RET
VECTORS ENDP

INITIALISE PROC NEAR ;Initialise 8259 PIC
ICW1 =17H ;edge triggered interrupt
ICW2 =20H ;level triggered = 1FH
ICW4 =13H ;bit3 to bit7 of pointer
OCW1 =00H ;Fully nested mode
;all interrupts enabled
```

```

OCW2 = 080H
;Rotate interrupts

PIC EQU 6000H ;8259
peripheral base
address.

MOV AL, ICW1 ;Write
control words to PIC
MOV DX, PIC ;A0 = 0
OUT DX, AL
MOV AL, ICW2
MOV DX, PIC+1 ;A0 = 1
OUT DX, AL
MOV AL, ICW4
MOV DX, PIC+1 ;A0 = 1
OUT DX, AL
MOV AL, OCW1
MOV DX, PIC+1 ;A0 = 1
OUT DX, AL
MOV AL, OCW2
MOV DX, PIC ;A0 = 0
OUT DX, AL

RET
INITIALISE ENDP
;Interrupt service
routines for IRQ0 -
IRQ7

ISR0: ;Start of
'Interrupt service
routine'
;USER CODE
GOES HERE
IRET ;Return from
interrupt.
ISR1: ;User
programs to service
Interrupts
IRET
ISR2:
IRET
ISR3:
IRET
ISR4:
IRET
ISR5:
IRET
ISR6:
IRET
ISR7:
IRET
ORG 07F0H
JMP FAR PTR BOOT
ORG 0800H
CODE ENDS
CODEBOOT SEGMENT AT
0FF80H
ASSUME CS:CODEBOOT
ORG 0000H
BOOT PROC FAR
BOOT ENDP
CODEBOOT ENDS
END

```

Since each interrupt service routine (ISR0 - ISR7) is located at address CS:IP, the vector table in RAM occupies four addresses for each pointer. Procedure VECTORS loads the CS:IP values for each interrupt type in successive RAM locations starting at address 0080H. Procedure INITIALISE loads the 8258 control registers and

initialises the PIC. Any hardware interrupts will now cause the relevant interrupt service routine to be activated.

Interrupts are ordered in priority from highest - IRQ0, to lowest -IRQ7. Thus, if two or more Interrupts occur simultaneously, the higher priority interrupt will be serviced. Operational control word OCW2 automatically rotates the priority of interrupts so that even if all eight IRQ lines are activated at the same time, all of them will be serviced in sequential order.

Programming the I/O port

The 8155 consists of two 8-bit ports (port A and port B) and an additional 6-bit port (port C). Port C port lines PC0 - PC3 are connected to the D0 - D3 pins of an intelligent HEX display (0 - F) for a nibble input of 0000 - 1111. Line PC5 controls the RH decimal point and line PC4 is used to blank (logic high) the display. All ports can be configured as outputs or inputs, but are not bit addressable. The port command register is located in IO space at address 0000, to which a command word is sent to configure the ports. Command register bit assignments are shown below. So, for example, to program ports C and B as outputs and port A as an input the following byte is written to the command register:

```

D7 D6 D5 D4 D3 D2 D1 D0
---
X X X X 1 1 1 0

```

PORT_COMMAND REGISTER BIT ASSIGNMENT:

0000H	D7	D6	D5	D4	D3	D2	D1	D0
PORT C INPUT					0	0		
PORT C OUTPUT					1	1		
PORT B INPUT							0	
PORT B OUTOUT							1	
PORT A INPUT								0
PORT A OUTPUT								1

The following procedure will write the display the contents of the CL register (lower nibble) on the intelligent display

```

DISPLAY PROC NEAR
PORT_COMMAND EQU 0000 ;COMMAND
register address
PORT_C EQU 0003 ;Port C
address
PORT_B EQU 0002 ;Port B
address
PORT_A EQU 0001 ;Port A
address

MOV DX, PORT_COMMAND
MOV AL, 00001100B ;Port C output port
OUT DX, AL
MOV DX, PORT_C
MOV AL, 5
OUT DX, AL ;Send 5 to hex display
RET
DISPLAY ENDP

```

The procedure can simply be called by instruction 'CALL DISPLAY'

Programming the 8088 board

The MASM assembler was used in programming examples. Since it does not produce romable code (pure binary code) which is sent to an EPROM emulator connected to the board's EPROM socket, a small batch file (8088 . BAT) needs to be run. The procedure is as follows:

*The source code is written using any ASCII (DOS) text editor such as 'EDIT' 'RPED' etc. The file is then saved as FILENAME. ASM, the ASM extension signifying that the file is text source code.

- *A single square wave
- *Continuous square wave
- *A single pulse on terminal count
- *Continuous pulses.

To program the timer IO address 0005 is used to configure the mode and to load the MSB (6 bits) count length. IO address 0004 is used to load the LSB (8 bits) count length. See diagram.

To program the timer for x N division, the count (N) value is loaded into the timer's count length register as shown below.

M2	M1	T13	T12	T11	T10	T9	T8
0	0	Single square wave					
0	1	Continuous square wave					
1	0	Single pulse on terminal count					
1	1	Continuous pulses					

0004H	T7	T6	T5	T4	T3	T2	T1	T0
LSB OF COUNT								

Bits T0-T13 specify the length of the count, bits 14 and 15 will specify the timer mode. For a continuous square-wave M2 will be 0 and M1 will be 1. In addition, the command register at address location 0000 controls the timer start/stop sequence. Bits 6 and 7 of the command word determine the timer command as follows:

- 00 No operation
- 01 Stops the timer
- 10 stops the timer after terminal count is reached
- 11 starts the timer by loading the mode and count length.

The following program demonstrates the use of the timer in providing a frequency division of 3FFEh (16382). This will result in a square wave 1/16383 of the Tin frequency (1.8432 Mhz/16382 = 112 Hz), at the Tout output pin.

```
TIMER PROC NEAR
COMMAND EQU 0           ;COMMAND REGISTER ADDRESS
TIMER_HIGH EQU 5       ;TIMER MSB ADDRESS
TIMER_LOW EQU 4        ;TIMER LSB ADDRESS

TIMER_COMMAND =1100000B;START COUNTER
HIGH_COUNT =01111111B ;MODE 01, MSB COUNT 3FH
                ;Continuous square wave
LOW_COUNT =11111110B  ;LSB COUNT FEH

MOV DX, TIMER_LOW      ;LOAD TIMER
MOV AL, LOW_COUNT
OUT DX, AL
MOV DX, TIMER_HIGH
MOV AL, HIGH_COUNT
OUT DX, AL

MOV DX, COMMAND
MOV AL, TIMER_COMMAND  ;START TIMER
OUT DX, AL
RET
TIMER ENDP

8088 SBC MEMORY MAP:
FFFFF.....
FFFF0.....reset      2 K BYTE EPROM AREA
FF800.....

06000.....8259 PIC ADDRESS
06001.....

00FF
STACK
VECTOR TABLE        256 BYTES RAM
0000
```

I/O Addresses:

0005.....	TIMER HIGH BYTE/MODE
0004.....	TIMER LOW BYTE
0003.....	PORT C
0002.....	PORT B
0001.....	PORT A
0000.....	PORT COMMAND

Programming the PC for Interrupts.

While we are on the subject of interrupts, and the fact that the PC uses the same 8259 PIC, the following text describes how the PC's serial port can receive data on an interrupt basis.

Program S_INT. PAS demonstrates how incoming serial data is streamed to the hard disk in real time into file 'SAMPLES'. Since it is an ASCII text file it may easily be imported into any spreadsheet - for example into Lotus 123 using the familiar 'File Import Numbers' commands.

The program consists of the main Pascal program S_INT and three assembler subroutines which are first converted to OBJ code format before final compilation into an EXE file by the Pascal compiler. The PC's serial USART needs to be initialised to provide the necessary communications protocol of 9600 baud: Procedure 'COM. ASM', : the USART'S internal registers are enabled for RS232 communications by Procedure 'ENABLECOM1. ASM'.

Part of the initialisation process in the Pascal program is to write the CS:IP values of the interrupt service routine ('INTHANDLER') to the vector table (variable 'INTERVECTOR'). A TYPE 12 (0CH) interrupt is issued whenever a serial byte enters the PC's serial port. Since the PC's BIOS has already loaded the vector pointers for all interrupts into the interrupt pointer table at the bottom of memory (0000:0000 onwards), the users interrupt service routine address is loaded into the vector table, having first saved the original pointer in variable ('ORGVECTOR'). The OCW1 PIC register - PC's port address 21H is loaded with 00 to enable all interrupts. Once the interrupt structure has been enabled by setting the interrupt flag by instruction 'STI' - inline code FAH, a serial byte entering the PC's serial port will activate the COM1 interrupt and cause the interrupt service routine to be executed: in this case Procedure RSINT.

This procedure reads the byte received by the PC's USART and assigns this value to variable 'HEX' by 'passing it over the stack' to the Pascal environment. A sample number associated with each sample increments for every byte and is also written to text file 'SAMPLES'. Finally, if the ENTER key is pressed, the original pointer is written into the vector table and the program aborts.

```
PROGRAM S_INT(INPUT, OUTPUT);

{$f+}
{$I-}
{$L COM}           (*External . obj file*)
{$L ENABLECOM1}   (*External . obj file*)
{$L RSINT}         (*External . obj file*)
USES dos, crt;
TYPE
DIGITS=0 . . 255; (*data 00 - FF*)
VAR
ORGVECTOR:POINTER; (*Pointer in interrupt table
                    for serial*)
                    (*interrupt*)
INTERVECTOR :ARRAY [$00 . $FF] of POINTER
ABSOLUTE $0000:$0000;
NUMBER:INTEGER;   (*Sample number*)
SAMPLES:TEXT;    (*ASCII text file*)
HEX:DIGITS;      (*serial data variable*)
PROCEDURE RSINT(VAR HEX:DIGITS);EXTERNAL;
PROCEDURE COM;EXTERNAL;
PROCEDURE ENABLECOM1;EXTERNAL;
```

```

PROCEDURE MESSAGE;
BEGIN
CLRSCR;
WRITELN('Ready for data');
WRITE('Press enter key to exit to DOS');
END;

(*Main data acquisition program*)
(*Interrupt service routine*)

PROCEDURE INTHANDLER; INTERRUPT;
BEGIN
RSINT(HEX); (*Fetch data*)
WRITE(SAMPLES, HEX:5); (*Write ASCII
                        data + sample*)
                        (*No. *)
WRITELN(SAMPLES, ' ', NUMBER); (*to hard
disc*)
NUMBER:=NUMBER+1; (*increment sample
number*)
PORT[$20]:= $20; (*issue end of interrupt*)
(*command to PIC*)
END;

(*Initialise variable*)
BEGIN
ASSIGN (SAMPLES, 'SAMPLES'); (*Open textfile
'samples'*)
REWRITE (SAMPLES);
NUMBER:=1; (*Initialise sample No.
to 1*)
ORGVECTOR:=INTERVECTOR [$c]; (*get interrupt
vector for*)
(*COM1, ($b COM2)*)
INTERVECTOR[$c]:= @ inthandler; (*Place CS:IP
offset of*)
(*interrupt service*)
(*into vector table*)
(*Define RS232 protocol*)
(*Initialise USART
registers*)
PORT[$21]:=0; (*Enable all IRQ
(*keyboard, video,
harddisc and*)
welcome datacomp(*serial port*)
MESSAGE;
REPEAT (*Wait for serial
interrupt*)
UNTIL KEYPRESSED; (*Exit to DOS if enter
key*)
(*pressed*)
INLINE($FA);
CLOSE(SAMPLES); (*Close data file*)
INTERVECTOR [$c]:=ORGVECTOR; (*Restore original
interrupt
(*vector*)
END.

;Initilise COM1 (COM2) port for 9600 baud, 1 stop
bit, 8 data
bits, no parity.
CODE SEGMENT BYTE PUBLIC
ASSUME CS:CODE
PUBLIC COM
COM PROC FAR
PUSH BP
MOV BP, SP
;Main Program begins

MOV AL, 0E3H ;9600 baud
MOV AH, 0
MOV DX, 0 ;com2=1
;com1=0
INT 014H ;BIOS interrupt

;Main program ends

```

```

POP BP
RET 2
COM ENDP
CODE ENDS
END

;Initialise USART registers
CODE SEGMENT BYTE PUBLIC
ASSUME CS:CODE
PUBLIC ENABLECOM1
ENABLECOM1 PROC FAR

PUSH BP
MOV BP, SP
MOV DX, 03F9H ;Enable Rxd bit in
control register
MOV AL, 1 ;02F9H = COM2
OUT DX, AL
MOV DX, 03FCH ;Enable USART
MOV AL, 0BH ;02FCH = COM2
OUT DX, AL
POP BP
RET 2
ENABLECOM1 ENDP

CODE ENDS
END

;Fetch serial data byte and pass to Pascal
variable HEX
CODE SEGMENT BYTE PUBLIC
ASSUME CS:CODE
PUBLIC RSINT
RSINT PROC FAR
CLI

PUSH BP ;Save BP contents
MOV BP, SP ;Copy stack pointer to
base pointer
MOV DX, 03FDH ;Usart base address (COM1)
02FDH=COM2

LDS SI, [BP+6] ;Point SI to stack
location for data

SUB DX, +5 ;Usart data buffer address
IN AL, DX ;Fetch data
MOV BYTE PTR [SI], AL ;Place data in stack
POP BP ;readjust stack
pointer

STI
RET 4 ;and return
RSINT ENDP
CODE ENDS
END

```

A floppy disk is available from the author which contains 'Boardmaker' PCB files for both the 80188 and 8088 SBC's, A86 assembler and source code example software. Available from:

Mr. R. Grodzik (Micros)
53 Chelmsford Road
Bradford BD3 8QN
West Yorkshire.
Price £12. 50 P&P inc. welcome datacomp

SEETRAX CAE RANGER PCB DESIGN

WITH COOPER & CHYAN AUTOROUTER

RANGER2 + SPECCTRA £400.00

RANGER & SPECCTRA AUTOROUTER
Together giving the most cost effective PCB design system on the market TODAY!
SEETRAX'S ease of use combined with COOPER & CHYAN'S renowned gridless autorouter, at an outstanding price.

R2 Outputs: 8/9 & 24 pin printers, HP Desk & Laser Jet, Cannon Bubble Jet, HP-GL, Gerber, NC Drill, AutoCAD DXF
Demo Disk available at £5.00 +VAT

RANGER2 £150

Upto 8 pages of schematic linked to artwork
Gate & pin swapping - automatic back annotation
Copper flood fill, Power planes, Track necking,
Curved tracks, Clearance checking,
Simultaneous multi-layer auto-router

RANGER2 UTILITIES £250

COOPER & CHYAN SPECCTRA auto-router (SPI)
Gerber-in viewer, AutoCAD DXF in & out

**UPGRADE YOUR PCB PACKAGE
TO RANGER2 £60**

TRADE IN YOUR EXISTING PACKAGE TODAY

Seetrax CAE, Hinton Daubnay House, Broadway Lane, Lovedean, Hants, PO8 0SG
Call 01705 591037 or Fax 01705 599036 + VAT & PP

All Trademarks Acknowledged

Study for a successful career in Electronic Engineering on our BEng (Hons) Degree courses

Bolton Institute is an internationally renowned centre for providing Electronic Engineering courses in the university education sector. Expertise, modern equipment and a friendly atmosphere provide an ideal environment for study on our BEng (Hons) Degree courses, which are accredited by the IEE.

Subjects include:

▪ **Microelectronic Design**

Electronic circuits, implemented directly in Silicon and fabricated on single chips is rapidly developing as a major industry of the future. We are the DTI North of England Microelectronics in Business Centre and our course equips prospective engineers with the knowledge and skills to enter this exciting and revolutionary technology field.

▪ **Electronic Instrumentation and Control**

This course provides a strong education in Electronic Systems, in Instrumentation and in Control and enables prospective engineers to enter this flourishing area with an appropriate mix of skills and knowledge.

▪ **Electronic Signal Processing**

This course focuses on Electronic processing of the signals in communications, instrumentations, control, medical and other applications. We are a centre of expertise in DSP, having many years of experience in running MScs in this area.

We offer flexible routes of entry to our courses including:

▪ **3 Year Standard Degree, or**

▪ **One A level for entry onto 2 + 2 (HND first), or**

▪ **Foundation first then onto either HND or Degree**

Call us on 01204 528851, ext. 3478 for a copy of our School of Engineering Prospectus and book your day to visit.


Deane Road, Bolton, Lancashire, BL3 5AB. Telephone 01204 528851. Fax 01204 399074

Establishing a new University

**BOLTON
INSTITUTE**

Great Value with Direct Debit.

Subscribe now and subscribe for less.

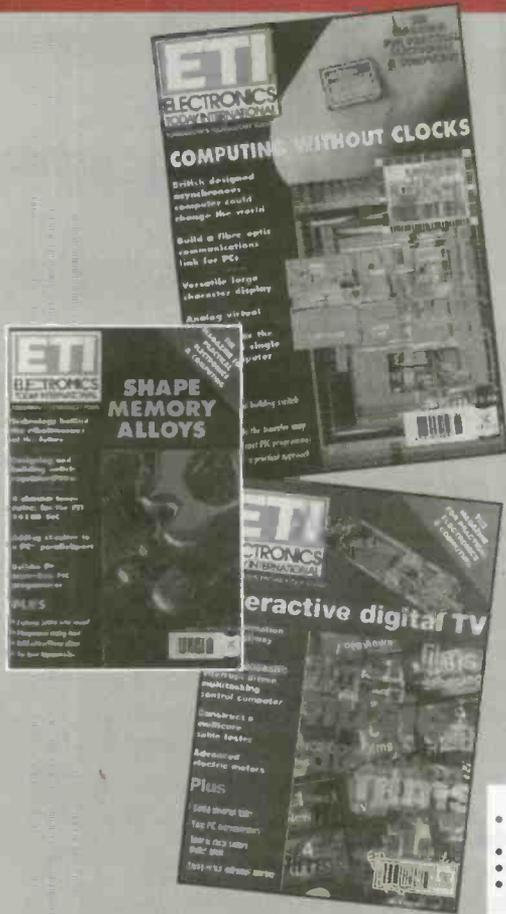

Make life easier...

- Never miss a single issue
- Don't worry about renewing
- Save money on the retail price, 53p per issue if you subscribe by direct debit!
- No paperwork and no fuss. Take the easy option, subscribe by direct debit today.

Option A

Direct Debit Introductory Offer

The easiest way to subscribe yet!

Pay for your 6 month subscription by Direct Debit and we will send you the next 8 issues for the price of 6, a saving of 53p per issue on your first 8 copies. Using Direct Debit means that your account will be automatically debited by £12.90 when we receive your order, and by the same amount at each renewal date thereafter.

Option B

For credit card, cheque or P.O. payments.

Subscribe for 1 year (12 issues) at £25.80

Direct Debit Guarantee

- This guarantee is offered by all Banks and Building Societies that take part in the Direct Debit scheme. The efficiency and security of the scheme is monitored and protected by your own Bank or Building Society.
- If the amounts to be paid or the payment dates change, you will be told of this in advance by at least 14 days as agreed.
- If an error is made by us or your Bank/Building Society, you are guaranteed a full and immediate refund from your branch of the amount paid.
- You can cancel a direct debit at any time, by writing to your Bank or Building Society. Please also send a copy of the letter to us.

Send off the coupon now or order by CREDIT CARD on: 01858 435344

Please complete this section

Yes, I would like to subscribe to ETI

DD U.K Direct Debit £12.90 every 6 Months. Please remember to fill in the direct debit instruction opposite.

Plus, 2 free issues with your first payment.

- | | |
|---|----------------------------|
| <input type="checkbox"/> 1 year (12 Issues) | U.K. Cheque/CC/P.O. £25.80 |
| <input type="checkbox"/> 1 year (12 Issues) | Europe & Eire £34.70 |
| <input type="checkbox"/> 1 year (12 Issues) | Sterling O/Seas £36.20 |
| <input type="checkbox"/> 1 year (12 Issues) | U.S. \$ O/Seas \$54.00 |

Please commence my subscription from the next available issue
Please quote subscription number if renewing/extending

Your Details

Name(Mr/Mrs/Miss)Initial.....Surname.....

Address.....

.....Post Code.....

Telephone.....

Method of Payment

Access/Visa Cheque/P.O.payable to Nexus Direct Debit

Card number:

Signature.....Expiry.....

Please post this coupon together with your cheque or direct debit form to: Nexus Subscription Department, Tower House, Sovereign Park, Lathkill Street, Market Harborough, Leicestershire. LE16 9EF.

Please tick this box if you do not wish to receive information from any other companies which may be of interest to you.

ETI DIRECT DEBIT INSTRUCTIONS

This card instructs your bank or building society to make payments direct from your account. Please fill in parts 1,2,3,4 and 6 and then send to us at the address opposite. Banks or Building Societies may not accept direct debit instructions for some types of account.

1. Please write the full postal address of your Bank or Building Society branch

To: The Manager
Bank or Building Society.....
Address.....
.....Post Code.....

2. Name(s) of account holder(£)

3. Branch Sort Code: - -

4. Bank or Building Society Account No:

5. Ref No:..... (Office use only)

6. Instruction to your bank or building Society. Please pay Nexus Media Ltd. Direct Debits from the account detailed on this instruction subject to safeguards by the Direct Debit Guarantee.
Originators Identification: 800132

Signature(s):.....

Date:.....

ET10

This exclusive offer must close on: 1/9/95

Practically SPEAKING

BY TERRY BALBIRNIE

Last month, we looked at repairs to mains-operated appliances found around the home. This time we shall look at electronic equipment where a low-voltage supply is derived from the mains using a step down transformer

For some tests, the equipment will need to have its inner circuitry exposed and for it to be plugged in to the mains. It is therefore essential to shield any unprotected mains connections so that it is impossible to touch them. If in doubt about your ability to do this safely, confine yourself to those tests which may be carried out with the equipment isolated from the mains.

Most tests involve using a multimeter set to either a low resistance range (or buzz test) or to voltage. Current measurements must be taken with great care and only with the necessary knowledge to interpret the readings. One of the worst things which can be done with a multimeter is to leave it set to a high (often unfused) current range and to apply the probes direct to the mains. An enormous current will flow, possibly ruining the meter and burning out the test probes. For this reason, it is best to store a multimeter set to a high voltage range.

Regard any voltage over 20V as potentially dangerous. With damp hands, it is possible for this to send a lethal current through the body. Remember, it is also possible to receive a dangerous shock from a capacitor which is charged up to any voltage greater than this. Certain pieces of equipment - notably photoflash units - charge a capacitor to several hundred volts using a battery-operated circuit. This type of equipment needs special care since it can deliver a lethal shock.


As mentioned in last month's Practically Speaking, blown fuses are probably the most common reason for a piece of equipment failing to work. Fuses should be removed to test them and the multimeter used on a low-

resistance range. A good fuse will indicate almost zero resistance. Inspect the fuse in the standard UK mains plug first, then check other fuses inside the equipment or those in panel fuseholders. Do not assume that a blown fuse is the source of trouble. It often indicates a fault elsewhere and this must be investigated.

Practical example

One common source of trouble is the plug-in power supply used for rechargeable tools, laptop computers, games, cordless telephones and similar devices. These are not treated well by their owners. The plug at the equipment end is often removed by pulling on the wire itself. This causes the output wire to snap or break from its soldered connections. The wire is often twisted mercilessly and the device often knocked harshly or dropped on the floor.

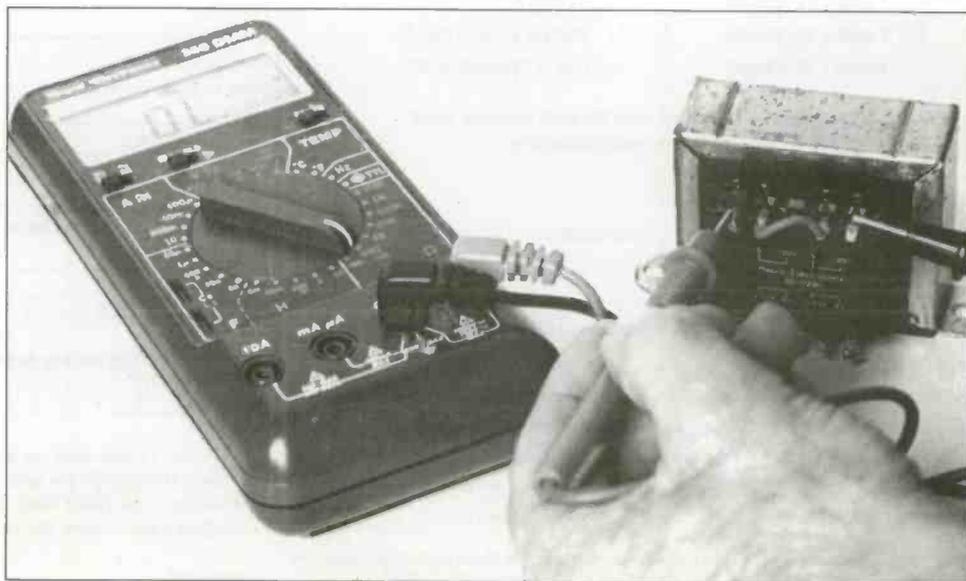Damaged output plugs are easily replaced and joints re-soldered. With the appliance unplugged from the mains, check both input and output wires for continuity by applying the probes



between the ends of each. A wire often breaks near one end where most bending occurs. By cutting off the last few centimetres, it may be re-connected giving the unit a new lease of life. If the break is near the middle of the wire, it should be replaced with a length of the same type. If the plastic case is cracked or the transformer is rattling around loose, the unit must be discarded. Never tape over cracks and splits or attempt to stick components down inside.

Often power supplies have a "polarity reversal" plug and socket somewhere along the length of the output wire. This is often pulled out by the owner and re-connected in the opposite sense. The equipment fails to work and it is reported as faulty when nothing else is amiss.

If a fault persists after checking wires and fuses for continuity, test the switch if there is one. To do this, remove the wires from it and check using the multimeter set to a low resistance range. It should show near-zero resistance when on. If there is a step-down transformer, check that an a.c. voltage exists across the transformer secondary winding. If it does not, check that mains voltage exists at the primary. This must be done very carefully indeed using the multimeter set to an a.c. range greater than 240V. If mains voltage exists at the primary but there is no output at the secondary, the transformer has failed. Depending on the nature of the equipment, it may not be worthwhile replacing it. If no mains supply exists at the primary, the fault probably still lies in the input lead, a fuse, connector or switch, so check more carefully. If the fault persists, look for obvious signs of trouble such as overheating. However, in the absence of a circuit diagram and specialist knowledge, it may be as well to leave the repair to the professionals.

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX • 0131 667 2611

The supplier to use if you're looking for -
★ A WIDE RANGE OF COMPONENTS AIMED AT THE HOBBYIST ★
★ COMPETITIVE VAT INCLUSIVE PRICES ★
★ MAIL ORDER - generally by RETURN OF POST ★
★ FRIENDLY SERVICE ★
★ 1995/96 CATALOGUE NOW AVAILABLE
Price £2.00 ★



Open: Monday-Thursday 9.15-6.00
 Friday 9.15-5.00 Saturday 9.30-5.00



EQT LTD STEVENAGE

Professional Sub-Contract Manufacturing & Suppliers to the Electronics Industry

Do you have a requirement for any of the following services:

PCB Assembly (Conventional and Surface Mount)	Product Design/Consultation
Wave & Hand Soldering	Full Procurement Service
Complete Equipment Manufacture	PCB Test & "Burn in" Facilities
Device Programming from hand written sheets or PC 3 1/2" disc	Enclosure Design & Manufacture
Cable Harness Assembly/loom Manufacture	PCB Artwork Manufacture
Card Cage and Module Wiring	Circuits Drawn Professionally
Full Inspection	Kit Procurement & Supply
	Component Sales
	Refurbishment a speciality
	Top Quality Work at Reasonable Rates

Phone Angela on (01438) 360406 or fax details of your requirements to us on (01438) 352742
 EQT LTD, Cromer House, Caxton way, STEVENAGE, HERTS, SG1 2DF

High quality stepping motor kits (all including stepping motors) Complete independent control of 2 stepping motors by PC (Via the parallel port) with 2 motors and software.

Kit	£67.00 ready built	£99.00
Software support and 4 digital inputs kit		£27.00
power interface 4A kit		£36.00
power interface 8A kit		£46.00
Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit		£23.00

We are now stocking a range of stepping motors and kits to drive them please ask for the stepping motor data sheet for full information.

Inverter toroidal transformers 225VA	10.5-0-10.5	
primary 0-260-285 secondary		£29.95
LEDs 3mm or 5mm red or green		7p each
yellow		11p each
LED cable ties	1p each	£5.95 per 1000
£49.50	per 10,000	

High quality photo resist copper clad epoxy glass boards

Dimensions	single sided	double sided
3x4 inches	£1.09	£1.23
4x8 inches	£2.75	£2.99
6x12 inches	£6.20	
12x12 inches	£12.25	

Rechargeable Batteries

AA (HP7)	£0.99
AA 700mAh	£1.75
C 2AH with solder tags	£3.60
D 4AH with solder tags	£4.95
12AA with solder tags	£1.55
AA (HP16) 180mAh	£1.75
AA 500mAh with solder tags	£1.55
C (HP11) 1.8AH	£2.20
D (HP2) 1.2AH	£2.60
PP3 8.4V 110mAh	£4.95
Sub C with solder tags	£2.50

1/3 AA with tags (philips CTV) £1.95
 Standard charger charges 4 AA cells in 5 hours or 4Cs or Ds in 12-14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time) £5.95
 High power charger as above but charges the Cs and Ds in 5 hours AAs Cs and Ds must be charged in 2s or 4s £10.95

Nickel Metal Hydride AA cells high capacity with no memory. If charged at 100ma and discharged at 250ma or less 1100mAh capacity (lower capacity for high discharge rates) £3.75

Special offers please check for availability
 stick of 4 42 x 16mm nicad batteries 171mmx16mm dia with red & black leads 4.8v £5.95
 Computer grade capacitors with screw terminals 5800uf 60v £4.95

115v ac 80v ac motor 4mm x 22mm shaft 50mm dia x 60 long body (excluding the shaft) it has replaceable thermal fuse and brushes £4.95 each £3.95 100-7 segment common anode led display 12mm £0.45
 LM337K TO3 case variable regulator £1.95
 £1.44 100+

GaAs FET low leakage current S8873 £12.95 each
 £3.95 10+ £7.95 100+
 BS250 P channel mosfet £0.45, BC559 transistor £3.95 per 100

74LS05 hex inverter £10.00 per 100, used 8748 Microcontroller £3.50
 SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet £1.95
 AM27502 £1.25 each 90p 100+, CD4007UB 10p 100+, 6p 1000+

Sinclair light gun terminated with a jack plug and PP3 clip gives a signal when pointed at 50hz flickering light with output wave form chart £3.95
 DC-DC converter Reliability model V12P5 12v in 5v 200ma out 300v input to output isolation with data £4.95 each or pack of 10 £39.50
 Hour counter used 7 digit 240v ac 50hz £1.45
 QWERTY keyboard 58 key good quality switches new £6.00

Airmax AB2903-C large stepping motor 14v 7.5 step 27ohm 68mm dia body 6.3mm shaft £8.95 or £200.00 for a box of 30
 Polyester capacitors box type 22.5mm lead pitch
 0.9uf 250vdc 18p each 14p 100+ 9p 1000+
 1uf 250vdc 30p each, 20p 100+, 10p 1000+
 3.3uf 100vdc 30p each, 20p 100+, 15p 1000+
 1uf 50v bipolar electrolytic axial leads 15p each, 7.5p 1000+
 0.22uf 250v polyester axial leads 15p each, 7.5p 1000+ Polypropylene 1uf 400vdc (Wima MKP10) 27.5mm pitch

32x29x17mm case 75p each 60p 100+
 Philips 123 series solid aluminium axial leads
 33uf 10v & 2.2uf 40p each, 25p 100+
 Philips 103 series long life 22uf 63v axial 30p each 15p 1000+

Multilayer AVX ceramic capacitors all 5mm pitch 100v
 100pf, 150pf, 220pf, 10,000pf (10n) 10p each, 5p 100+, 3.5p 1000+
 500pf compression trimmer 60p
 40 uf 370vac motor start capacitor (dielectric type containing no pcbis) £5.95 or £49.50 for 10
 Solid carbon resistors very low inductance ideal for RF circuits

27pwm 2W, 68ohm 2W 25p each 15p each 100+ we have a range of 0.25w 0.5w 1w and 2w solid carbon resistors please send SAE for list
 P.C. 400W PSU (Intel part 201035-001) with standard motherboard and 5 disk drive connectors, fan and mains inlet/outlet connectors on back and switch on the side (top for lower case) dims
 212x49x149mm excluding switch £26.50 each
 £138.00 for 6

MX180 Digital multimeter 17 ranges 1000vdc 750vac 2Mohm 200mA transistor Hfe 9v and 1.5v battery test £12.95

AMD 27256-3 Eproms £2.00 each, £1.25 100+
 DIP switch 3PCO 12 pin (ERG SDC-3-023) 60p each 40p 100+

Disk drive boxes for 5.25 disk drive with room for a power supply light grey plastic 67x268x247mm £7.95 or £49.50 for 10
 Hand held ultrasonic remote control £3.95
 CV2486 gas relay 30 x 10mm dia with 3 wire terminals will also work as a neon light 20p each or £7.50 per 100

All products advertised as new and unused unless otherwise stated. Wide range of CMOS TTL 74HC 74F Linear Transistors kits rechargeable batteries capacitors tools etc. always in stock.
 Please add £1.95 towards P&P
 vat included in all prices

£138.00 for 6
 MX180 Digital multimeter 17 ranges 1000vdc 750vac 2Mohm 200mA transistor Hfe 9v and 1.5v battery test £12.95

AMD 27256-3 Eproms £2.00 each, £1.25 100+
 DIP switch 3PCO 12 pin (ERG SDC-3-023) 60p each 40p 100+

Disk drive boxes for 5.25 disk drive with room for a power supply light grey plastic 67x268x247mm £7.95 or £49.50 for 10
 Hand held ultrasonic remote control £3.95
 CV2486 gas relay 30 x 10mm dia with 3 wire terminals will also work as a neon light 20p each or £7.50 per 100

All products advertised as new and unused unless otherwise stated. Wide range of CMOS TTL 74HC 74F Linear Transistors kits rechargeable batteries capacitors tools etc. always in stock.
 Please add £1.95 towards P&P
 vat included in all prices

JPG ELECTRONICS


ETI 276-278 Chatsworth Road,
 Chesterfield S40 2BH
 Access Visa Orders (01246) 211202
 Callers Welcome

ADVERTISERS INDEX

BHA Trading	11
BK Electronics	31
Bolton Institute	64
Bull Electrical	5
Classified Section	71, 72
Cricklewood Electronics	30
Direct CCTV	11
EQT Ltd	67
Express Components	19
Field Electric Ltd	11
Innovative Interfacing Enterprise	11
JCG	30
JPG Electronics	67
Komputer Knowledge	11
Labcenter Electronics	23
Maplin Electronics	OBC
Mayflower Electronics	11
Mega Download	60
Milford Instruments	48
MQP Electronics Ltd	43
Niche Software	30
Number One Systems	68
Omni Electronics	67
Pico Technology	4
Powerware	IFC
Radio Tech	6
Seetrex CAE	64
Stewarts of Reading	11
Telnet	18
Tsien (UK) Ltd	49
United Guild of International Photographers	IBC

EASY-PC, Schematic and PCB CAD

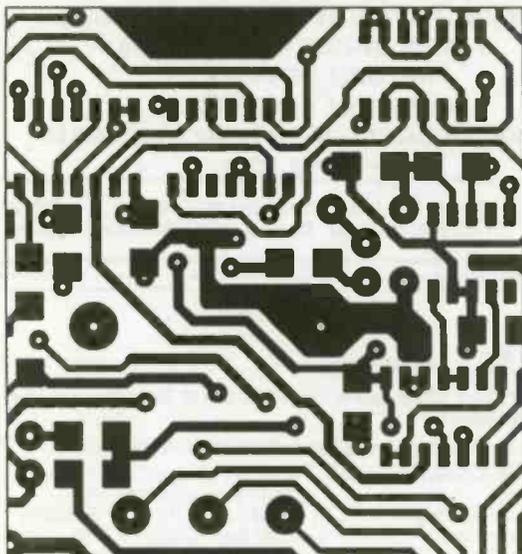Over 19,000 Installations
in 80 Countries World-wide!



- Runs on:- PC/XT/AT/286/386/486 with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design:- Single sided, Double sided and Multi-layer (8) boards.
- Provides full Surface Mount support.
- Standard output includes Dot Matrix / Laser / Ink-jet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Tech Support - free.
- Superbly easy to use.


Still
Only
£98.00!

Plus P&P+VAT

BRITISH
DESIGN

AWARD


1989

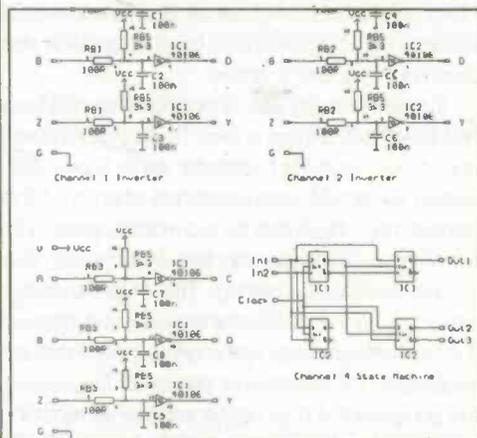

Options:-500 piece Surface Mount Symbol Library £48,
1000 piece Symbol Library £38, Gerber Import facility £98.

Electronic Designs Right First Time?

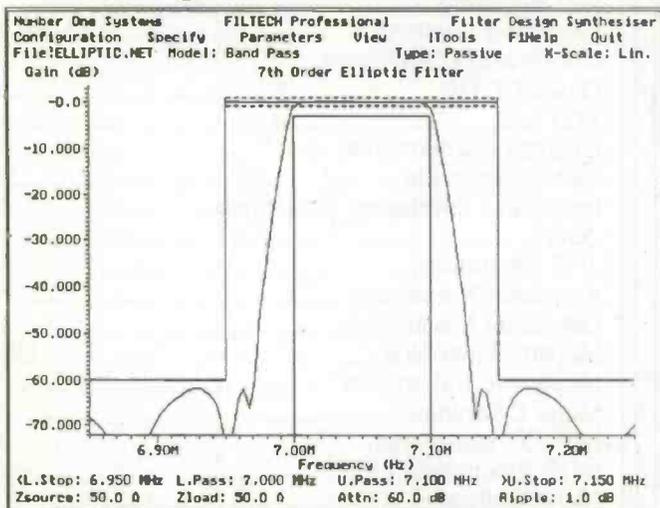Active and Passive Filter Design - FILTECH -



From only **£145!**

Affordable Electronics CAD

FILTECH: Active and Passive Filter Design program	From \$275	£145
LAYAN: New Electro-Magnetic layout Simulator. Include board parasitics in your Analogue simulations. Links with and requires EASY-PC Professional XM and ANALYSER III Professional	\$950	£495
EASY-PC Professional: Schematic Capture and PCB CAD. Links directly to ANALYSER III, LAYAN and PULSAR.	From \$375	£195
PULSAR: Digital Circuit Simulator	From \$195	£98
ANALYSER III: Analogue Linear Circuit Simulator	From \$195	£98
STOCKIT: New comprehensive Stock control program for the small or medium sized business	\$275	£145
EASY-PC: Entry level PCB and Schematic CAD.	\$195	£98
Z-MATCH for Windows: Windows based Smith-Chart program for RF Engineers.	\$475	£245

We operate a no penalty upgrade policy.
US\$ prices include Post and Packing
Sterling Prices exclude P&P and VAT.

For full information, please write, phone or fax:-

Number One Systems

UK/EEC: Ref. ETI, HARDING WAY, ST.IVES, CAMBS., ENGLAND, PE17 4WR.

Telephone UK: 01480 461778 (7 lines) Fax: 01480 494042

USA: Ref. ETI, 126 Smith Creek Drive, Los Gatos, CA 95030


Telephone/Fax: (415) 968-9306

International +44 1480 461778





ada4all5


FOILS FOR THIS ISSUE

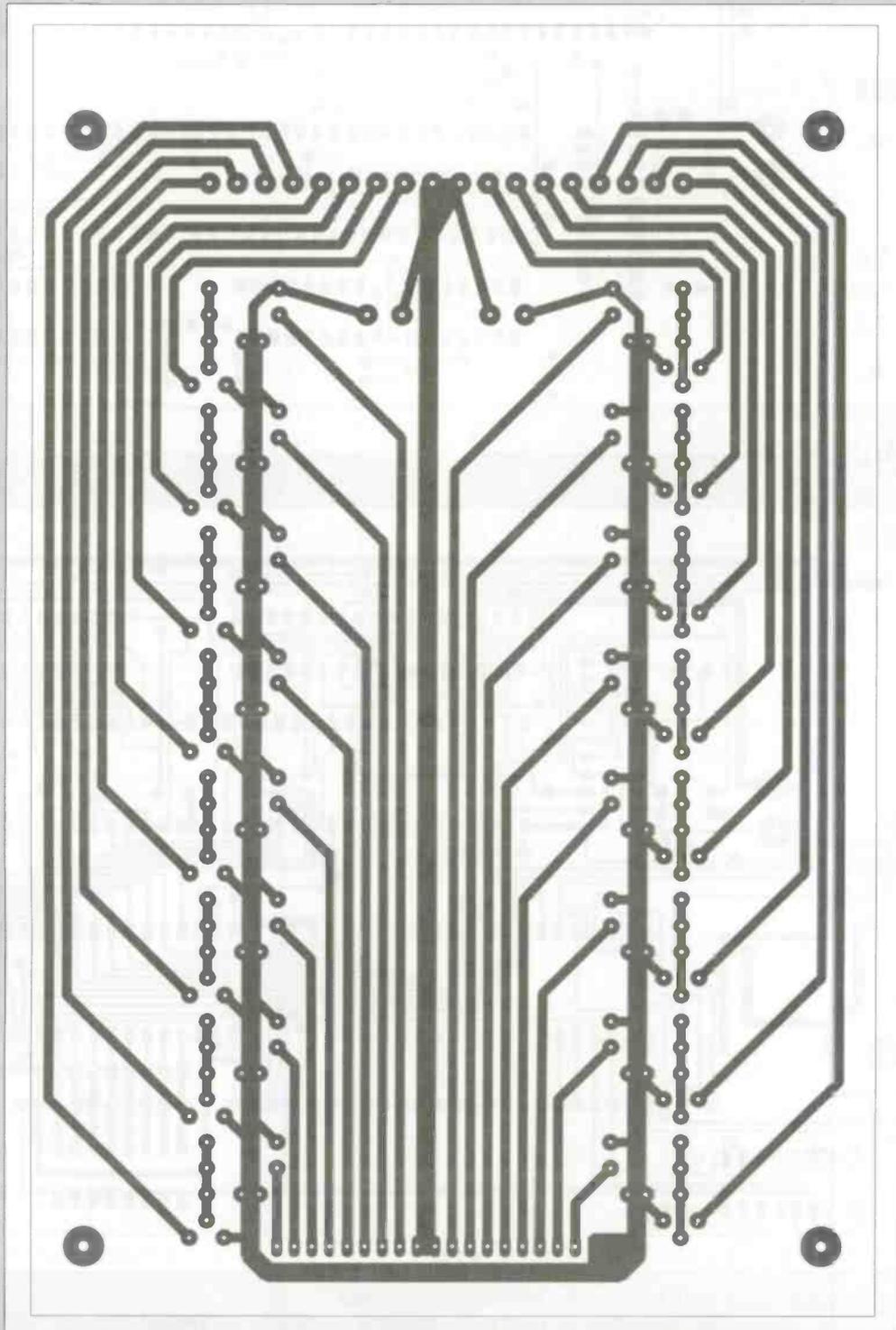


HELLO MUM DRIVE BOARD

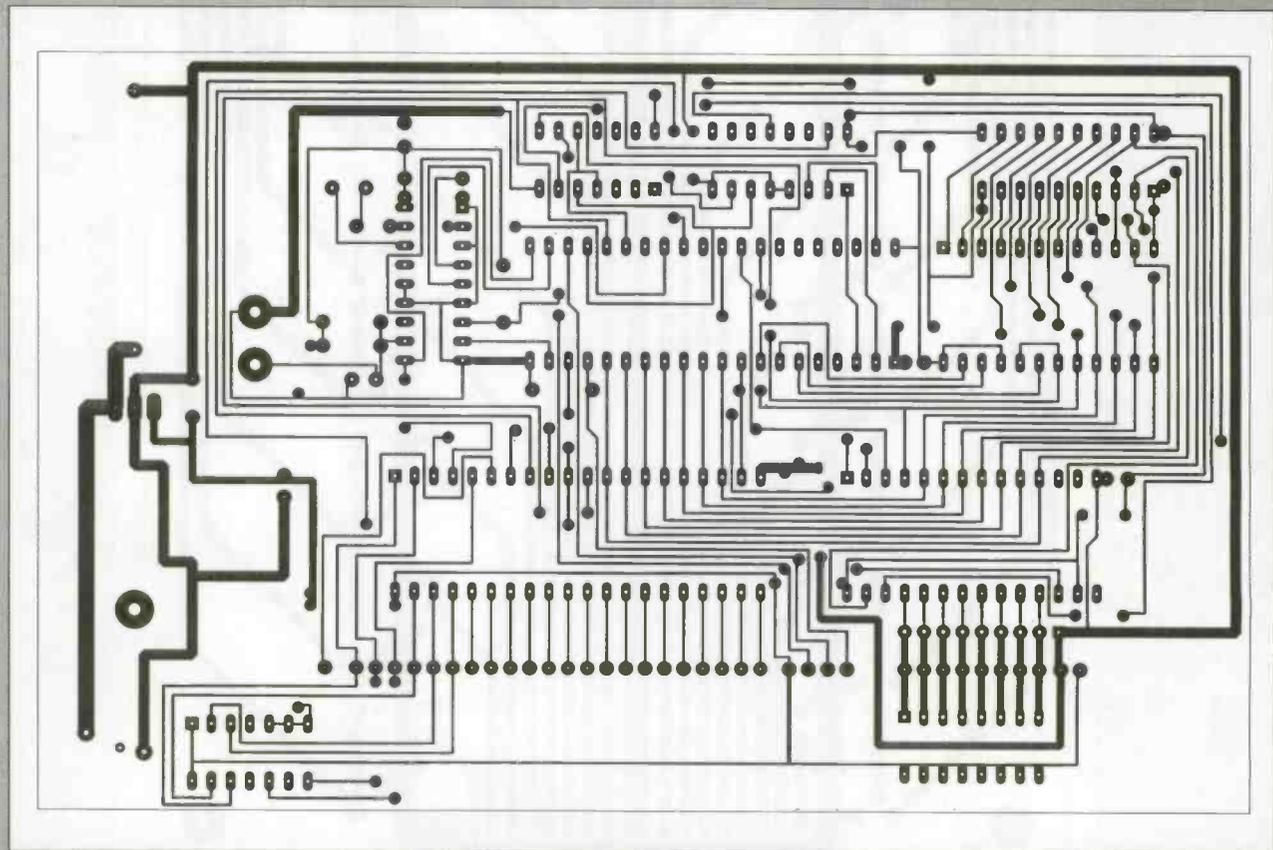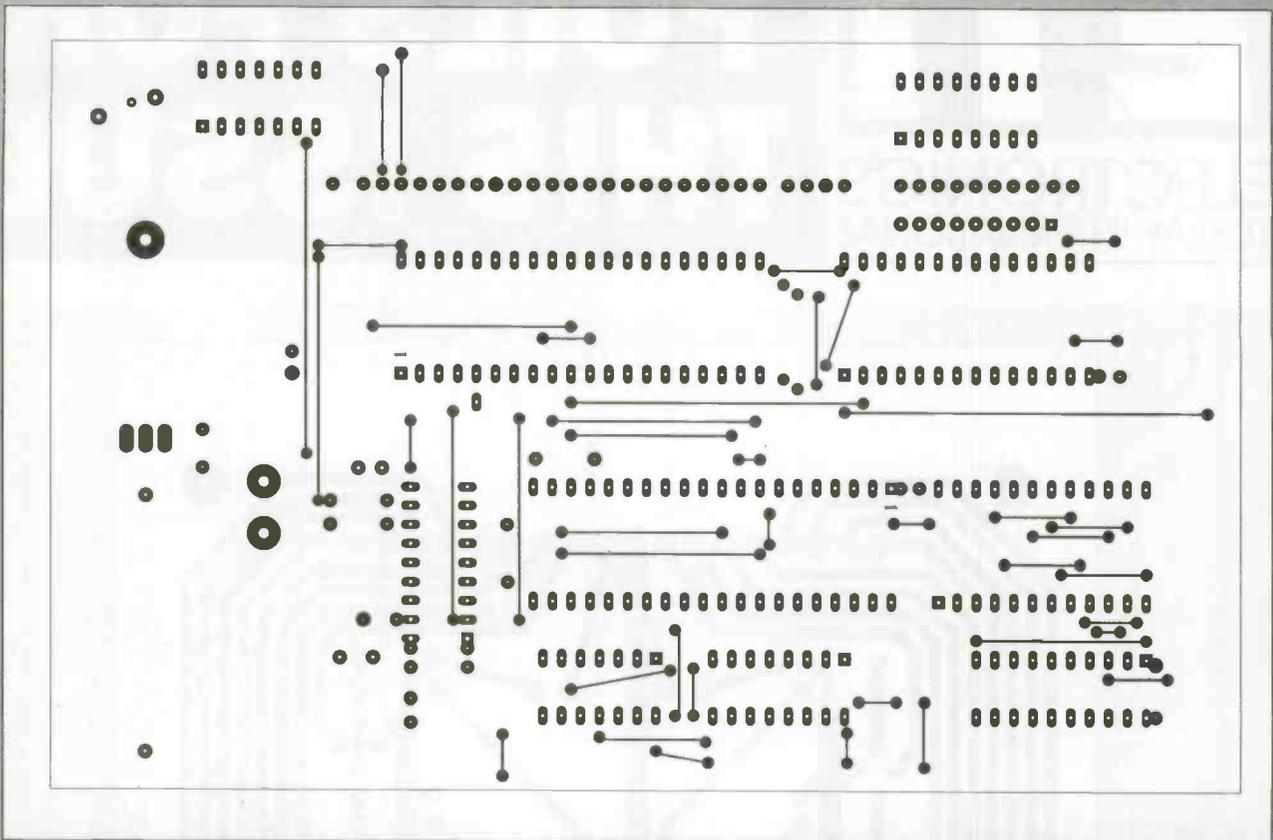


8088 Interrupt based control computer

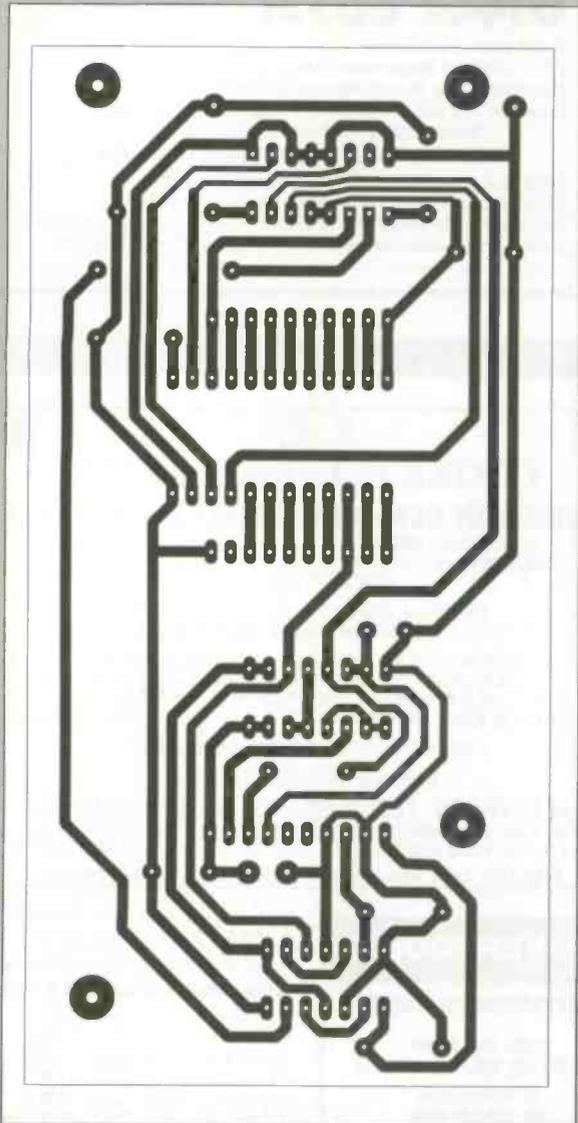

HELLO MUM CONTROL BOARD

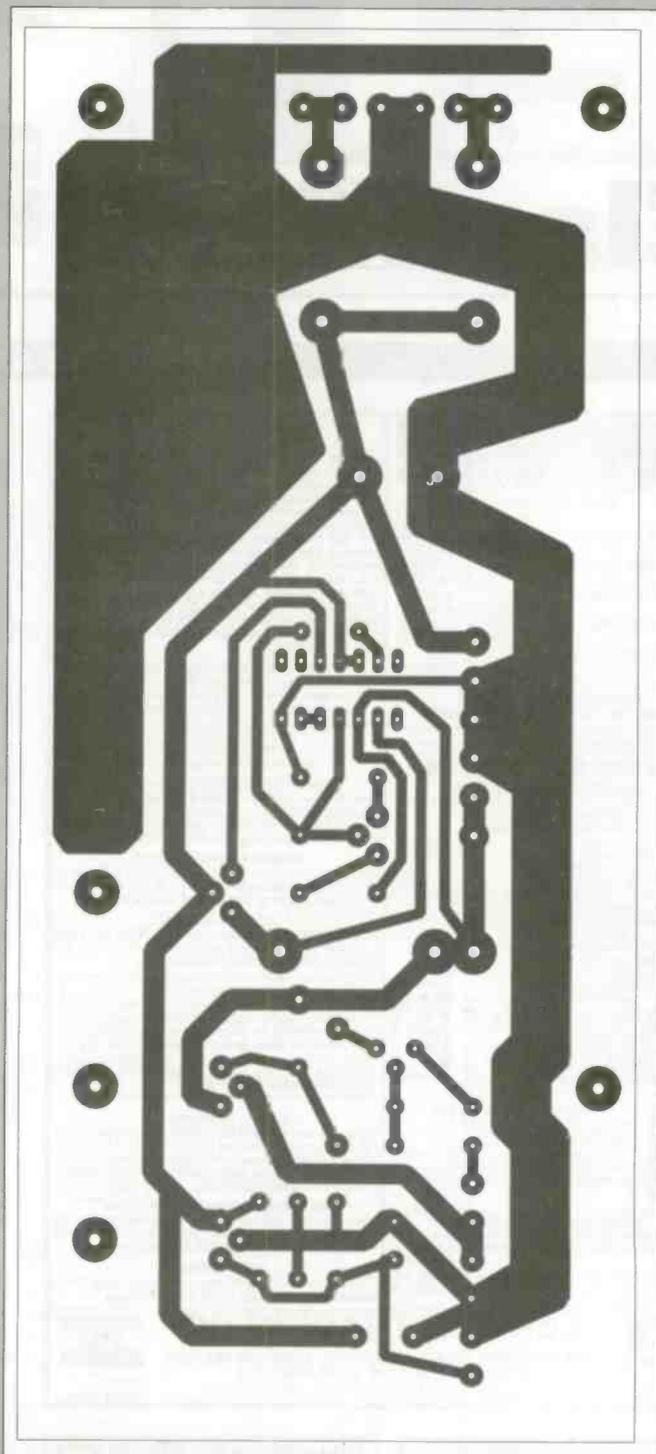

HELLO MUM CONTROL BOARD

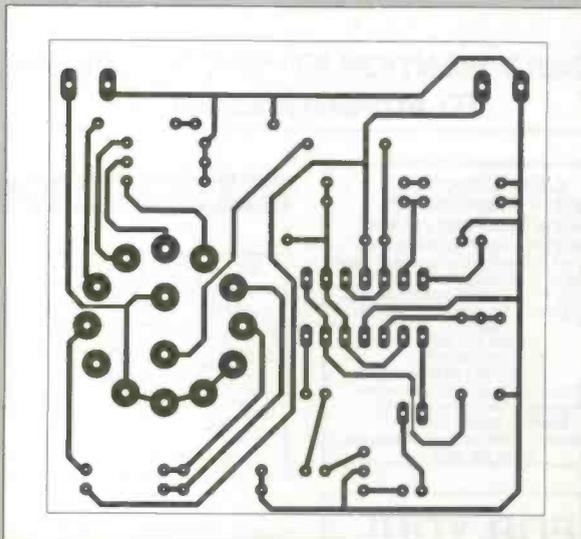

DRY BATTERY TESTER

Classified



James Gale
01442 66551

Send your requirements to:
ETI Classified Department, Nexus, Nexus House,
Boundary Way, Hemel Hempstead, HP2 7ST
Lineage: 75p per word (+ VAT) (minimum 15 words)
Semi display: (minimum 2.5cms)
£10.50 + VAT per single column centimetre



Ring for information on series bookings/discounts.
All advertisements in this section must be pre-paid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

FOR SALE

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60

OUTPUT 0-260V

	Price	P&P
0.5KVA 2.5 amp max	£31.90	£6.00
	(£44.53 inc VAT)	
1KVA 5 amp max	£41.15	£7.00
	(£56.58 inc VAT)	
2KVA 10 amp max	£59.40	£8.50
	(£79.78 inc VAT)	
3KVA 15 amp max	£78.65	£8.50
	(£102.40 inc VAT)	
5KVA 25 amp max	£139.15	
	(Plus Carriage)	

Buy direct from the Importers. Keenest prices in the country
COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO
(110-240V Auto transfer either cased with American socket and mains lead of open frame type. Available for immediate delivery.

WIDE RANGE OF XENON FLASHTUBES

Write/Phone your enquires

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt £14.00 (callers only)	(£16.45 inc VAT)
2ft 20 watt £9.00 (callers only)	(£10.58 inc VAT)
12in 9 watt £4.80 + 75p p&p	(£5.52 inc VAT)
9in 8 watt £3.96 + 50p p&p	(£5.24 inc VAT)
6in 4 watt £3.96 + 50p p&p	(£5.24 inc VAT)

230V AC BALLAST KIT

For either 6in, 9in or 12in tubes £6.05 + £1.40 p&p (£8.75 inc VAT)
The above Tubes are suitable for Forged Bank Note detection, security marking etc.
Other Wave Lengths of U.V. TUBE available please telephone your enquires.

400 WATT UV LAMP

Only £38.00 + £4.00 p&p (£49.35 inc VAT)
160 WATT SELF BALLASTED BLACK LIGHT MERCURY BULB
Available with BC or ES fitting, Price inc VAT & p&p and VAT £25.55



12V D.C. BILGE PUMPS

500 GPH 15ft head 3 amp £19.98
1750 GPH 15ft head 9 amp £34.55
Also now available 24V D.C. 1750 GPH 15ft head 5 amp £35.55. All designed to be used submerged. PRICES INCLUDE P&P & VAT

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical uses etc.
Approx 16 pulses. Adjustable speed £50.00 + £3.00 p&p (62.28 inc VAT)
Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT)
SAE for further details including Hy-Light and Industrial Strobe Kits.

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB
FAX 0181-995 0549 0181-995 1560
ACCOUNT CUSTOMERS MIN. ORDER £10



Showroom open Monday-Friday

Ample Parking Space

"BOFFINS SPECIAL" - UNIQUE OFFER

Surplus Precision Medical Unit, Internally in excellent condition. Designed primarily to eject a precise controllable amount of fluid from a medical syringe (letter not supplied). Contains the following removable components: Dual Micro Processor Boards and EPROMS Escap Precision 12V DC Motor with 300:1 Gear Box and optical encoder coupled to a precision threaded drive mechanism. Mains supply with 6 x 1.5V Ni-Cad A.A. cells back-up. L.C.D. Digital read-out 17mm high with legends. Audible warning.
These are sold for the dismantling of the exceptional quality components, regret no Circuits available. Ridiculously low price: £20.00 + £4.00 p&p (£28.20 incl VAT)

5KVA ISOLATION TRANSFORMER

As New Ex-equipment fully shrouded Line Noise Suppression, Ultra Isolation Transformer with terminal covers and Knock-out cable entries. Primary 120/240V Secondary 120/240V 50/60 Hz. 005 pF Capacitance. Size L.37 x W.19 x H.16cm Weight 42 Kilos.
PRICE £120.00 +VAT
ex-warehouse Carriage on request.

240V AC CENTRIFUGAL BLOWER

New Manuf. Surplus Skeleton Blower suitable for mounting inside an enclosure to cool equipment. Overall size 130x110x85mm. Outlet 80x35mm. Impeller 60mm dia x 60mm long. £14.10 incl. P&P & VAT

SEWING MACHINE MOTOR

Brand new 220/240V AC/DC SEW-TRIC 2 lead Brush Motor, Size L. 100mm x H. 70mm x W.55mm. Spindle. 1/4in. dia x 1in. long. £14.10 incl. P&P & VAT

GEARED MOTORS

71 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price inc VAT & p&p £27.73

SOLID STATE EHT UNIT

Input 230/240V AC. Output approx 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (£12.81 inc VAT) NMS

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Angst Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £15.00 + £2.00 p&p (£19.98 inc VAT)

WASHING MACHINE WATER PUMP

Brand new 240V AC, fan cooled. Can be used for a variety of purposes. Inlet 1 1/4in, outlet 1 in. dia. Price includes p&p & VAT £11.20 each or 2 for £20.50 inclusive.

MICROSWITCH

Pye 15 amp changeover lever microswitch, type S171. Brand new price 5 for £7.05 inc VAT & p&p

COOKE INTERNATIONAL

SUPPLIER OF QUALITY USED TEST INSTRUMENTS.

ANALYSERS, BRIDGES, CALIBRATORS, VOLTMETERS, GENERATORS, OSCILLOSCOPES, POWER METERS. ETC ALWAYS AVAILABLE

ORIGINAL SERVICE MANUALS FOR SALE
COPY SERVICE ALSO AVAILABLE

EXPORT, TRADE AND U.K. ENQUIRIES WELCOME
SEND FOR LIST OF EQUIPMENT AND MANUALS
ALL PRICES EXCLUDE VAT AND CARRIAGE

DISCOUNT FOR BULK ORDERS SHIPPING ARRANGED

OPEN MONDAY TO FRIDAY 9AM - 5PM

COOKE INTERNATIONAL

ELECTRONIC TEST & MEASURING INSTRUMENTS

Unit Four, Fordingbridge Site, Main Road, Barnham, Bognor Regis, West Sussex, PO22 0EB Tel (+44) 01243 545111/2 Fax (+44) 01243 542457

WANTED TEST EQUIPMENT & MANUALS TO PURCHASE

LIVERPOOL

PROGRESSIVE RADIO

87/93 Dale Street
Tel: 051 236 0982 051 236 0154

47 Whitechapel
Tel: 051 236 5489
Liverpool 2

'THE ELECTRONICS SPECIALISTS'
Open: Tues-Sat 9.30-5.30

SWC SCIENTIFIC WIRE COMPANY

ENAMELLED COPPER WIRE TINNED WIRE SILVER PLATED COPPER WIRE SOLDER EUREKA WIRE NICKEL CHROME WIRE BRASS WIRE LI TZ WIRE BIFILAR WIRE MANGANIN WIRE TEFLON WIRE NICKEL SAE BRINGS LIST 18 RAVEN RD LONDON E18 1HW FAX 081 559 1114

KINDLY MENTION ETI WHEN REPLYING TO ADVERTISEMENTS

LEN COOKE ENTERPRISES

For the best value in Used Electronic Test Instruments

We buy, sell and service oscilloscopes, signal generators, frequency counters, spectrum Analysers, Power meters, logic testers, etc.
Spare parts available for most Textronix scopes.

Tel: 081-813-9946
Fax: 081-574-2339
Mobile: 0374 759984

Mail order address: Unit 5, Southall Enterprise Centre, Bridge Road, Southall, Middx. UB2 4AI

We engineer what we buy, we support what we sell.

SOFTWARE

PC SCIENTIFIC & TECHNICAL PROGRAM LIBRARY

Low cost specialist software and GOOD QUALITY PROGRAMS THAT WORK are our forte.

We have the largest scientific and technical software library as well as the best mainstream programs available anywhere. Software supplied on CD ROM or floppy.

Discover the true gems of shareware with our 250,000 word book "The Encyclopedia of Shareware". Over 3000 programs listed, and described in 178 different categories.

For your copy send £2.50 or phone/fax your order. Major credit cards accepted. You also receive a money saving special offer voucher.

PDSL, Winscombe House, Beacon Rd, Crowborough Sussex TN6 1UL Tel 01892 663298, Fax 01892 667473

TURN YOUR SURPLUS TRANSISTORS, ICs ETC INTO CASH immediate settlement.

We also welcome the opportunity to quote for complete factory clearance

Contact:
COLES-HARDING & CO
Unit 58, Queens Road, Wisbech, Cambs PE13 7PQ
BUYERS OF SURPLUS INVENTORY ESTABLISHED OVER 20 YEARS
Tel: 01945 584188 Fax: 01945 475216

SMART CARD PRODUCTS

Smartcards, Readers/Writers, OEM couplers, Evaluation kits and more.

EPSILON ELECTRONICS
Brynsengwyn, 1A, 0667 Oslo,
Norway TEL/FAX
+4722640810

**THIS SPACE COULD BE WORKING FOR YOU!
FOR DETAILS OF ADVERTISING RATES CALL
JAMES ON 01442 66551 OR FAX YOUR
ADVERTISEMENT ON 01442 66998**

ASTRA Desk Top Accounting

Overture - Inviting, Sales, Purchases, Nominal, VAT, etc
Premier - plus Stock, Jobs, DPOs, Barcodes, Serial No, etc
Professional - plus Multi-Currency, Depreciation, etc

S&S Systems Ltd, Breton Court, Manor Road, Wales
Sheffield, S31 8PD, UK. (Software distributors and Apple dealers)
Tel: (01909) 773999 • Fax: (01909) 773645 • Inc Code: (+44 1909)

COMPONENTS

EPROMS PLDs + MICRO CONTROLLERS copied or programmed. We supply devices/convert discrete logic to PLDs. PLDs for ETI PC Post Card supplied at £10/P.C.B. £12. PO Box 1561, Bath 01225 444467.

BOOKS & PUBLICATIONS

THE BUG CONSTRUCTOR'S MANUAL

All you will ever need to know about Bugs. Over 40 Bug circuits for every application. Telephone, High Power, Crystal Controlled and UHF bugs and many pages of useful information. Many previously unavailable circuits. This is the very latest book, and the "ONLY" book of its kind in the UK. A valuable asset for the hobbyist and professional. Introductory offer price only **£9.95** inc. P&P.

For immediate despatch, send cheque or P.O.'s payable to:

GAINSFORD ELECTRONICS
71 Gainsford Road, Southampton SO19 7AW.

PRINTED CIRCUIT SERVICES

For the VERY best in:-

- :Photoplotting
- :Printed Circuit Design
- :Screen Printing Metal Panels
- :Graphic Reproduction

It's GOOD to talk to

R P PHOTOGRAPHIC
tel: 0181 - 777 4407

PLANS

ELECTRONIC PLANS, laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and computer graphics tablet. 150 projects. For catalogue, SAE to Plancentre Publications, Unit 7, Old Wharf Industrial Estate, Dymock Road, Ledbury, Herefordshire, HR8 2HS.

DIY PLANS!! Windgenerators, petrol generators, Inverters, portable welding generators, engine crane, electric bike, solar projects, boats and the famous Homebuilt Dynamo. Plus books on sterling engines, mechanical wonders, the writings of Thomas Tesla, electromagnets etc Hundreds of exciting projects. 2x1st stamps for descriptive catalogue. Jemmett Engineering 8 Hallam Gardens Pinner Middlesex HA54PR.

PRINTED CIRCUIT BOARDS

PCB's, PROTOTYPES AND PRODUCTION, Artwork copied or raised from your draft designs or schematics. Quoteline 01232 473533 or write to P Agar, 36 Woodcot Avenue, Belfast, BT5 5JA

FAX YOUR ADVERT ON 01442 66998

COURSES

Start training now with the specialists for the following courses. Send for our brochure — without obligation or Telephone us on 01626 779398

ETI 9/95

Name _____ Telecomms Tech C&G 2710
 _____ Radio Amateur Licence C&G
 _____ Micro-processor
 _____ Introduction to Television

Radio & Telecommunications Correspondence School
12 Moor View Drive, Teignmouth, Devon TQ14 9UN

Commercial Reality
EUREKA!!!

See your ideas come to life using this exciting home study course.

For free details write to:
Commercial Reality (Ref ET9), Tritaq St. Mary's House, 40 London Road, Newbury, Berks. RG14 1LA
or Telephone: 01635 873775 (24hrs)

READERS PLEASE NOTE that some telephone dialling codes may recently have changed. If you experience any difficulty in contacting advertisers, ring our advertising department on 01442 66551



ELECTRONICS TODAY INTERNATIONAL, CLASSIFIED ADVERTISEMENT DEPARTMENT, NEXUS HOUSE, BOUNDARY WAY, HEMEL HEMPSTEAD HP2 7ST

Rates: Lineage 75p per word + VAT minimum 15 words.

Semi-display £10.50 per single column cm plus VAT. No reimbursements for cancellations.

All ads must be pre-paid.

Name

Address

Daytime Tel. No:

Signature Date

PLEASE DEBIT MY ACCESS/BARCLAYCARD No.

Expiry Date

FOR SALE COMPONENTS PLANS OTHER - PLEASE STATE

Open Forum

This month in Open Forum we shall not be looking at the state of the electronics industry in general but at the state of hobby electronics, and in particular the role that ETI plays.

I am sure that every reader is acutely aware that the whole nature of hobby electronics is changing very rapidly, a change that is mirroring the equally rapid changes in the electronics industry as a whole. The main driving force behind this change is that circuitry is being replaced by software, where there was once a board full of ICs and discrete components there is now a single microcontroller chip and perhaps a half dozen other components.

In industry this has enormous advantages in terms of reduced costs, ease of updating designs, and greatly improved reliability. But it also means that the circuits used in different applications are all starting to look remarkably similar, the difference between them being in the software rather than the hardware.

The trend towards embodying the functionality of a design in software rather than in hardware is something which a magazine like ETI cannot ignore. We live in the real world, and in that world people no longer build crystal sets, or construct devices using simple logic gates, masses of transistors etc. Today we live in a world where electronics equals microcontrollers, programmable logic arrays, and highly integrated special purpose ICs.

For the reader of ETI this trend has two effects; on the one hand it actually makes it easier to build more complex applications, but on the other it removes a lot of the electronics from a project and replaces it with computer programming.

Hence the fact that magazine is increasingly filled with pages of code listings.

I personally think that we are at a transition point, where the electronics enthusiast, in the old sense, is disappearing and being replaced by the enthusiast who designs and builds electro-computing systems. Someone who is as heavily into computing as electronics, and who sees electronics as simply a means of practically implementing what is primarily a software design.

With the actual circuitry becoming more and more just a matter of plugging together standard building blocks (such as the PIC based Basic programmable microcontroller system), the function of a magazine like ETI has to be one of providing those building blocks, and also providing a source of ideas on how they can be used for inventive and useful applications.

I could well be wrong, but it is important for ETI, for the hobby electronics industry, and for you the readers, that we decide exactly where we are all going. One interesting pointer to the future is the success of the new BBC TV programme Eureka. It is evidence of an increasingly popular interest in invention and engineering, particularly where they can be applied to the solution of everyday problems. The enthusiast is no longer viewed as being rather strange, but as a pioneer, a builder of the future.

So I would like to finish off this piece with an appeal; if you are working on an unusual idea, or an invention which you think would be of interest to other readers of ETI, be it an electronically controlled home, a back yard spaceship or a thought controlled computer, why not let us know?. Who knows, it could be the start of something big.

Next Month...

In the October 1995 issue of Electronics Today International we will be featuring an interesting range of new projects. The main project in this issue is the ETI Basic programmable microcontroller

Amongst the other projects in this issue, there is one from Terry Balbirnie that will interest all parents of young children - a low intensity child's night light with micropower consumption. For all music buffs there is a 16 channel MIDI mixer from Tom Scarff.

Dr Pei An shows how to build a computerised radio control system that will allow a PC to remotely control any device within a range of several hundred yards. From David Geary there is a timed isolator system which should prevent mains equipment being accidentally left on. From Tim Parker there is a versatile upgradable bench power supply, and Bart Trepak continues his practical look at designing a project around the PIC microcontroller.

In the main feature article in next month's ETI, Dave Clarkeson takes a look at the technology behind some of the current advances in electron microscopy. Terry Balbirnie takes a practical look at the use of solar panels.



EDITORIAL

Editor **Nick Hampshire**
Sub Editor **Eamonn Percival**
Editorial Assistant **Wendy Butler**

CREATIVE

Designer **Nadia Ahdout**
Technical Illustration **John Puczynski**
Photography **Manny Cefai**

ADVERTISEMENT SALES

Display Sales
James Gale
Advertisement Copy Control
Marie Quilter

MANAGEMENT

Divisional Director
Terry Patisson
Production Administrator
Theresa Davis
Group Editor
Stuart Cooke
Group Advertisement Manager
Claire Jenkinson
Marketing Manager
Jason Doran
Copy Sales Manager
David Pegendam



ISSN
0142-7229

ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, plans, drawings and programs and all copyright and all other intellectual property rights therein belong to Nexus Special Interests. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Nexus Special Interests and reproduction requires the prior written consent of the company ©1990 Nexus Special Interests. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Subscription rates-UK £25.80 Europe £34.70 Sterling Overseas £26.20 US Dollars Overseas \$54.00

Published by Nexus Special Interests, Nexus House, Boundary Way, Hemel Hempstead HP2 7ST, Telephone (01442) 66551, UK newstrade distribution by SM Distribution Ltd, 8 Leigham Court Road, London SW16 2PG, Telephone (0181) 667 8111, Overseas and non-newstrade sales by Magazine Sales Department, Argus House, Bourdury Way, Hemel Hempstead, HP2 7ST, Telephone (01442) 66551, Subscriptions by Nexus Subscription Services, ETI, Queensway House, 2 Queensway, Redhill, Surrey RH1 1QS, Telephone (01737) 768611.

US subscribers by Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA 90505 USA. For Visa/Mastercard orders in USA - Telephone (310) 375 6258 Fax (310) 375 0548. Pacific Time: 9am-9pm Weekdays, 10am-6pm Weekends. Typesetting and origination by Ebony, Liskeard, Cornwall. Printed by Wiltshire Ltd, Bristol.



Nexus House, Boundary Way,
Hemel Hempstead HP2 7ST
Telephone (01442) 66551
Fax: (01442) 66998

NEW MEMBERS
SPECIAL OFFER



MEMBERS SAVE £££'s
JOIN TODAY!

The United Guild of International Photographers


Even if you are a person who only takes photographs on holidays abroad or just occasionally for fun - you will benefit by joining us. We have special offers, FREE NEWSLETTERS and discounts to both ensure you increase your enjoyment and improve your photographic art. Nobody is too old to join us and few are too young. If you love life and people or simply want to save money and develop your interests, please join us today. We can even help you to become an award winning photographer. Join us and ENJOY LIFE.

AMATEURS - JOIN US TODAY &
SAVE ON EVERYDAY COSTS

PROFESSIONALS - JOIN US TODAY &
SAVE ON EVERYDAY COSTS - your account is open

THE COST OF JOINING US IS LESS THAN THE PRICE OF THE FREE GIFTS YOU RECEIVE

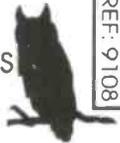APPLICATION FORM - PLEASE COMPLETE AND SEND FREEPOST TODAY
TOGETHER WITH YOUR CHEQUE FOR £44 TO COVER 2 YEARS MEMBERSHIP
Cheque to be made payable to: THE UNITED GUILD OF INTERNATIONAL PHOTOGRAPHERS
YOU MAY PHOTOCOPY THIS APPLICATION FORM



MEMBER
REF: 9108

Surname.....First Names..... Mr/Ms

Address.....
.....

PLEASE TICK THIS BOX IF YOU
WISH US TO SEND YOU A FREE
NATIONAL LOTTERY INSTANTS
TICKET - TOP PRIZE £50,000

Please post today together with your cheque for £44 to: THE UNITED GUILD OF INTERNATIONAL PHOTOGRAPHERS,
84 VICTORIA ROAD, HORLEY, SURREY RH6 7AB. Please mark envelope FREEPOST and no postage stamp is necessary

EACH NEW MEMBER WILL RECEIVE FREE OF CHARGE:-

10 x FREE 35mm FILMS RRP £29.90

10 x FREE ENLARGEMENTS up to size 12" x 8" RRP £40.00


2 x FREE MEMBERSHIP WINDOW STICKERS RRP £6.00

2 x FREE 'OFFICIAL PHOTOGRAPHER' Badges RRP £8.00

TOTAL VALUE OF FREE GIFTS£83.90. PLUS £50,000?

£50,000? PLUS £50,000?

As a member you will have low cost access to our laboratory services, which use the most modern equipment available in the world today. We are currently offering TO MEMBERS ONLY:-
Developing and printing each film up to 39 exposures. Prints size 6" x 4". Price just £2.00 x 2.5 'X' RATED
Printing enlargements up to size 12" x 8" price just £1.00 x 2.5 'X' RATED
Printing 6" x 4" reprints price just 20p each x 2.5 'X' RATED

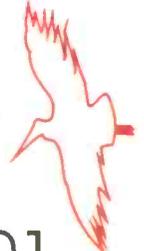

GET YOUR BARGAINS - JOIN US TODAY!
**FOR A FULL MEMBERS ONLY PRICE LIST, PHOTOGRAPHIC HELP LINE
AND FURTHER DETAILS, OFFERS AND DISCOUNTS
AVAILABLE ONLY TO MEMBERS, TELEPHONE NUMBER FOR**

MEMBERS AND NON-MEMBERS IS 0839 393 001

Calls cost 39p per minute cheap rate and 49p per minute at all other times

MAPLIN

ELECTRONICS AND BEYOND

**FULL COLOUR
GUIDE TO
ELECTRONIC
PRODUCTS**

NEW **1996
CATALOGUE**

Bigger, Brighter and *Better Value* than ever before. Over 1180 Full Colour pages with hundreds of Brand New Products at Super Low Prices

on sale from 1st September

only £2.95

from all branches of WHSMITH and other major retail outlets.

Order by post including P & P £3.45

01702 554161



TEST GEAR



**PCB
EQUIPMENT**




**COMPUTER
ACCESSORIES**



**ELECTRONIC
COMPONENTS**



TOOLS

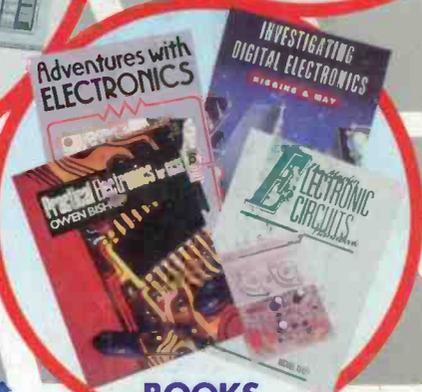

BOOKS

**VISIT YOUR LOCAL
MAPLIN STORE TODAY**
To place your order and
to discover a world of electronics
and beyond

Belfast 357-359 Lisburn Road. **Birmingham** Sutton New Road, Erdington. **Bradford** 28 Valley Road, Hamm Strasse. **Brighton** 65 London Road. **Bristol** 302 Gloucester Road. **Cardiff** 29-31 City Road. **Chatham** 2 Luton Road. **Coventry** 12 Bishop Street. **Dudley** Unit 7, Pedmore Road. **Edinburgh** 126 Dairy Road. **Glasgow** 264-266 Great Western Road. **Ilford** 302-304 Green Lane. **Leeds** Carpet World Building, 3 Regent Street. **Leicester** Office World Building, Burton Street. **Liverpool** Edge Lane, Fairfield. **London** 146-148 Burnt Oak Broadway, Edgware; 107-113 Stanstead Road, Forest Hill; 120-122 King Street, Hammersmith. **Manchester** 8 Oxford Road; 169 Cheetham Hill Road, Cheetham Hill. **Middlesbrough** Unit 1, The Forbes Building, Linthorpe Road. **Milton Keynes** Unit 2, Office World Building, Snowdon Drive, Winterhill. **Newcastle-upon-Tyne** Unit 4, Allison Court (The Metro Centre), Gateshead. **Northampton** 139 St. James Road. **Nottingham** 86-88 Lower Parliament Street. **Portsmouth** 98-100 Kingston Road. **Preston** Unit 1, Corporation Street. **Reading** 129-131 Oxford Road. **Sheffield** 413 Langsett Road, Hillsborough. **Slough** 216-218 Farnham Road. **Southampton** 46-48 Bevois Valley Road. **Southend-on-Sea** 282-284 London Road, Westcliff-on-Sea. **Stockport** 259-261 Wellington Road South. **Stoke-on-Trent** 39-45 London Road. Plus many NEW stores opening soon. Tel: (01702) 552911 for details of your nearest store.