



**ELECTRONICS**  
TODAY INTERNATIONAL

# RS232 I/O CARD FOR THE PSION 3

Makes your Organiser into A  
Controller

## 5 RANGE CAPACITANCE METER

Designed to give good  
accuracy down to very  
low capacitance values

## MEDIUM WAVE LOOP AERIAL

An adjustable - stand antenna  
for better medium - wave  
reception

## AVR: THE NEW CHIP ON THE BLOCK

Flash memory microcontrollers  
move in

**PLUS**

- *MIDI Drum Pads*
- *GCSE Bargraph Module*
- *Fast Fivers - A Digital Die*



# Electronics Principles 5.0

'A COMPLETE PC BASED ELECTRONICS COURSE'

If you are looking for an easy and enjoyable way of studying or improving your knowledge of electronics then this is the software for you.

Now includes the PIC16C84 & PIC16C71 hardware and instruction set.


Electronics Principles 5.0 is a significant upgrade of our popular educational software. Now contains even more analogue, digital and microcomputer theory, PLUS over a hundred new mathematics topics to further your understanding of formulae and calculations. Telephone for a comprehensive list or upgrade details.

This software has been developed to teach electronics and is suited to both the complete novice and the more advanced student or hobbyist wanting quick revision and access to hundreds of electronics formulae. It is extremely easy to use. Just select a topic, which is always presented as a default diagram (no blank screens!) and input your own values. Alternatively, use those from any standard electronics text book to see the results. frequency response curves, calculation of logic states, voltages and currents etc.

Graphics presentation has been enhanced and speeded-up with new menus and indexing which enables a quicker access and more informative description of the extended range of five hundred and sixty electronics and mathematics topics.

The PIC16C84 microcontroller hardware and instruction set has been introduced and brought to life through colourful interactive graphics where you can study the architecture of this device by changing the data values to simulate all of the registers, direct/indirect addressing, program/data memory and input/output port configuration. Along with those analogue to digital functions of the PIC16C71. If you would like to learn more about the principles of these popular microcontrollers then it could not be made easier.

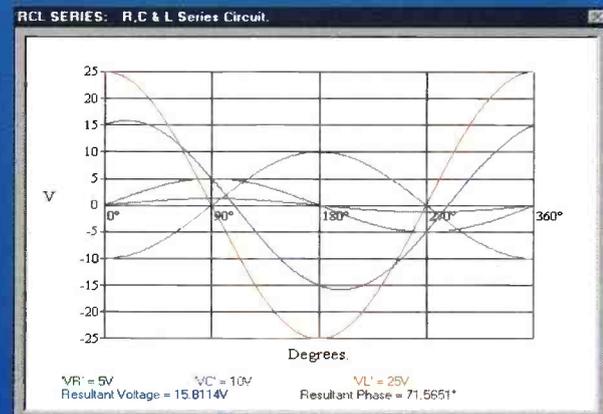Electronics Principles software is currently used in hundreds of UK and overseas schools and colleges to support City & Guilds, GCSE, A-Level, BTEC and university foundation courses. Also NVQ's and GNVQ's where students are required to have an understanding of electronics principles.



Still only £99.95\*

EPT Educational Software. Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ.

Tel/Fax: 01376 514008. sales@eptsoft.demon.co.uk <http://www.eptsoft.demon.co.uk>

\*UK and EC countries add £2 per order for post & packing. VAT should be added to the total.

Outside Europe £3.50 for air mail postage by return.



Switch, Delta, Visa and Mastercard orders accepted - please give card number and expiry date. Cheques & Postal Orders should be made payable to EPT Educational software.

# Contents

**Volume 27 No.3**

## **& Features Projects**

**Next Issue 27th March 1998**

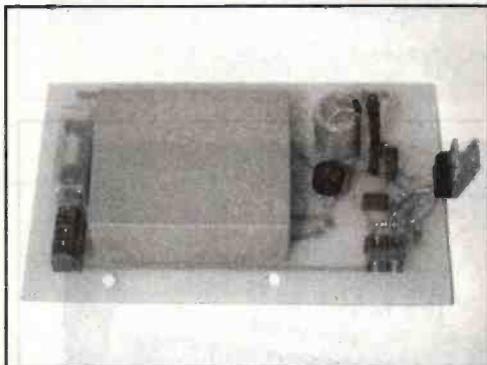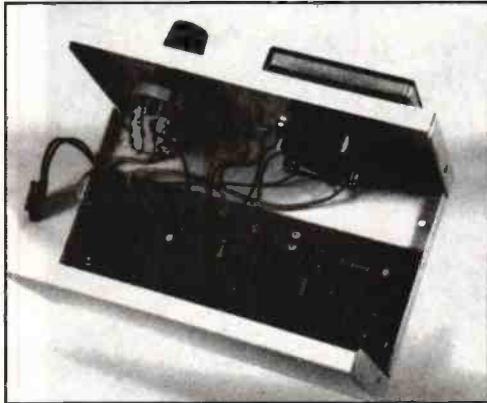

### **AVR: The New Chip on the Block**

Kevin Kirk describes a recent arrival on the microcontroller market, the Atmel AVR 1200, with Flash memory and a nanosecond instruction cycle time.

**9**

### **AA Cell Eliminator**

Reduce your AA battery throughput by powering your gadget collection from the mains around the house and workshop with Terry Balbirnie's dedicated battery eliminator.

**19**

### **Five Range Capacitance Meter**

Many capacitance meters have difficulty returning accurate measurements for low-value capacitors such as those widely used in radio and other high-frequency circuits. Robert Penfold's design uses close-tolerance components to give good accuracy down to very low values.

**25**

### **An RS232 I/O Card for Psion 3s and PCs**

The Psion Organiser 3, 3A, 3C and Sienna conceal a general-purpose computer behind the popular electronic diaries. This interface card by Pei An enables you to program the palmtops for control or data logging.

**33**

### **Medium Wave Loop Aerial**

Raymond Haigh's inexpensive aerial for the serious listener unit is designed to greatly improve reception on the medium wave band, especially under difficult conditions. The design includes a guide to building a compact wooden stand and casing.

**47**

### **GCSE Grounding: Bargraph Module**

Terry Balbirnie continues a series of adaptable circuits for GCSE projects with a voltage-sensitive 10-LED Bargraph module with adjustable sensitivity, based on the LM3914 display driver.

**54**

### **Fast Fivers 8 - A Digital Die**

Owen Bishop's electronic die shows all the faces from 1 to 6, but won't roll under the sofa just as the game is getting exciting. The display uses red LEDs and is driven by a counter with a built-in oscillator.

**57**

### **Pic-Based Double Bass Tuner**

Samuel Dick designed this portable tuning aid, based on the PIC 16C64, with the lower frequencies of the double bass in mind. It uses good quality earphones rather than a loudspeaker for better bass reproduction and portability.

**60**

### **Midi Drum Pads**

Probably the easiest way to transfer rhythm to your computer or hardware sequencer is to use MIDI drum pads that can be hit with drumsticks. Tom Scarff designed this low cost unit around the PIC 16C84 microcontroller.

**64**

## **Regulars**

<b>News</b>	<b>4,5,7</b>
<b>ETI PCB Service</b>	<b>46</b>
<b>PCB foils</b>	<b>68, 69</b>
<b>Practically Speaking</b>	<b>73</b>
Terry Balbirnie tailors an analogue panel meter to read volts using just a resistor.	
<b>Round the Corner</b>	<b>74</b>

  
**Subscribe & Save**  
SUBSCRIPTIONS & BACK ISSUES HOTLINES:  
**01858 435344**  
ORDERS: ENQUIRES:  
**01858 435322**  
Lines Open 9am - 6.30pm

Phone the hotline and take advantage of our special offer detailed on page 32

## OVERSEAS READERS


To call UK telephone numbers, replace the initial 0 with your local overseas access code plus the digits 44.

### Electronics Lessons on Video from the Maplin Catalogue

Maplin has launched a series of electronics training videos in its Spring catalogue. The Ucando range of educational videos is described as providing comprehensive instruction on electronics theory, covering a wide range of topics including DC/AC circuits, semiconductors, amplifiers, power supplies and oscillators, digital electronics, radio theory, fibre optics and laser technology.

The hour-long videos use animation, text and commentary to make the learning material more eye-catching. Maplin sees them as particularly relevant to schools, colleges and industrial departments, as well as students following distance-learning courses.

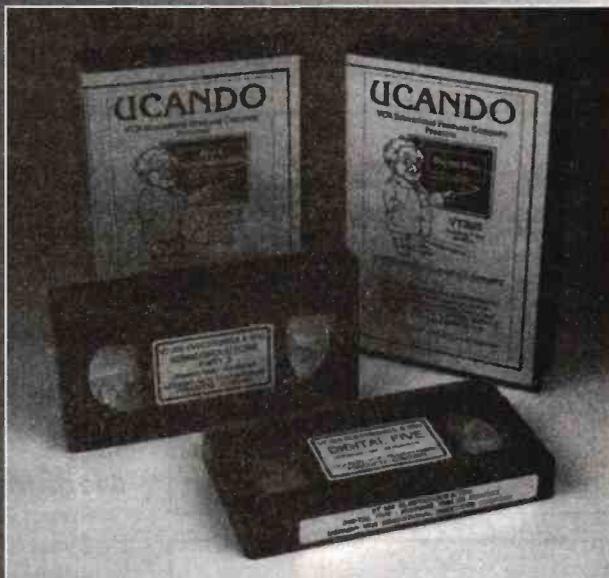The tapes are available from the current Maplin catalogue and from Mondo Maplin superstores. For further information on ordering codes and store locations, call 01792 554002



### DSP Chip Brings Parametric EQ to Auto and Home Electronics

Medianix Semiconductor has introduced the MED25022 Digital Cross-over; parametric Equaliser, a single-chip, multi-channel digital filter ic that uses digital signal processing (DSP) to provide parametric equalisation and crossover filtering in a range of audio applications that includes car audio, home entertainment centres, multimedia computers, and audio engineering and mixing consoles.

This is the first time these functions have been made available in a single application-specific standard product (ASSP).

The CMOS chip provides five bands of parametric equalisation with up to 24 dB per octave crossover filtering for each of two audio channels. Devices can be used in parallel for more channels, or can be cascaded to achieve higher order filters. All the desired eq band amplitudes and filter cutoff frequencies are programmable. On-chip memory provides up to 35 microseconds of programmable digital delay that allows time alignment of audio signals from speakers that are different distances from the listener.

Filtering characteristics can be changed by changing the contents of a finite number of registers. The centre frequency, (the -3 dB bandwidth) and level of each of the five eq bands can be independently adjusted over a +/-



16dB range by sending a 24-bit word in three 8-bit blocks, or by calculation using formulae stored in the on-chip rom. The cutoff frequencies of the crossover filters on each channel are digitally programmable at either 12 dB/octave or 24 dB/octave, and can create lowpass, highpass or bandpass filters as needed, providing very precise control. The chip allows dynamic system reconfiguration so that, for example, the performance of a car stereo in a convertible can remain optimised whether the top is up or down.

For more information, contact Medianix Semiconductor Inc., 100 View St., Suite 101, Mountain View, CA 94041, USA. Tel +1 650 960 7081 ex. 225 Fax +1 650 960 0478. Web: [www.medianix.com](http://www.medianix.com)

The Institution of Electrical Engineers (IEE) has produced a leaflet to warn embedded systems users and manufacturers about the "Year2000 problem", or the "Millenium problem" as it is sometimes known in a more apocalyptic vein. When the world's timing devices click over to the year 2000, a proportion of them will not be able to interpret dates starting with 01/01/00, and may not be able to deal with operational cycles such as "do X every 100 days" under the new dates. The IEE leaflet flags with problem with a concise checklist of action for organisations that depend on computer systems to take, starting with "Get more information"; "Appoint a team" and "Investigate" to "Organise formal reporting and review." The IEE will be providing general guidance based on information supplied by industry and Government. The first line of access to this guidance is the IEE website at <http://www.iee.org.uk/2000risk>. Later in the year a guidance document for small and medium sized businesses will follow. The IEE can be contacted via Alasdair Kemp, the Public Affairs Department, IEE, Savoy Place, London Wc2R 0BL. Fax only 0171 497 2143.

## Orchid Vehicle Tracking uses GSM and DGPS

European Telecom and Racal Survey, world leaders respectively in the distribution of wireless communications products and the development of satellite positioning technology, have combined to launch a mobile telephony-based vehicle tracking, navigation and on-line driver information service, Orchid, under the joint venture name Global Telematics. Orchid will integrate GSM and digital technology, cellular telephone and satellite DGPS (Differential Global Positioning System) to provide telematic services using a voice-based system safety-compliant for motorists and fleet-operators, and expects to turn cellular telephony into a fast, accurate 24-hour comms system.

Orchid has been launched in the UK and will begin its international launches with South Africa in early 1998. Starting, as have most vehicular cellular telephony systems, with the commercial fleet market, Orchid will allow entire fleet positions can be viewed at a glance, drivers contacted with updated information, and data sent to and from vehicles. Routes can be planned and re-planned and emergencies dealt with quickly.

Orchid is available now for all types of vehicle users, however, as the system expands more into private cars, vehicles are more likely to have the system as a factory fitted option, rather than retro fit.

Among other organisations already involved are the Automobile Association (AA) which will provide a 24-hour monitoring and information bureau service, and Vodaphone as

the mobile network carrier.

Current services include a 24-hour year-round monitoring and information service; precise vehicle tracking; navigational assistance, route planning and real time traffic updates; roadside assistance and emergency service callout; local service information such as hotels, restaurants, service stations and so on; fleet management packages with mapping and reporting facilities. Future services will include security vehicle tracking and authorised assisted recovery; remote vehicle diagnostics; remote lock and unlock capabilities and floating car data.

For more information or a tariff list, call 0800 731 6677 or 0181 974 1100, fax 0181 974 1133.



## Logging Goes Walkabout

Lascar Electronics have responded to customer demand and produced EI-Link-IR as an easy cable-free short distance data transfer solution. The EI-Link-IR module allow easy construction of an infra red link for EasyLog or other instrumentation systems where a remote control is required. @B:It converts RS232 serial data into infra red, and vice versa. The EI-Link-IR offers original equipment manufacturers (OEMs) "plug-&-play" accessibility to IR serial communications, and has the added benefit of being totally self-contained in a 9-to-25-way adapter shell.

Needing no additional software, EI-Link-IR plugs straight into a PC serial COM port or a Pison Workabout. It uses the industry standard IrDA comms standard to achieve half-duplex comms

over a distance of up to one metre. The EI-Link-IR needs no external power supply, drawing the little current it consumes (approximately 2.5mA) from its host equipment through the 9-way D-type connector. The baud rate is preset to 9600 baud. EI-Link-IR can be used with the EI-2-IR module to form part of a wireless data logging system. It can be used with Panel-IR to provide infra red control capability.

For more information, contact Lascar Electronics, Module House, Whiteparish, Salisbury, Wilts SP5 2SJ, UK. Tel. 01794 884567.



Surplus always wanted for cash!

# THE ORIGINAL SURPLUS WONDERLAND!


THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

## LOW COST PC's

### SPECIAL BUY 'AT 286'

40Mb HD + 3Mb Ram

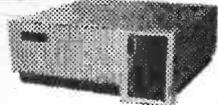

Industrial grade 12Mhz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & Integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!

Order as HIGRADE 286 **ONLY £99.00 (E)**

Optional Fitted extras:	VGA graphics card	£29.00
	1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)	£19.95
	Wordperfect 6.0 for Dots - when 3 1/2" FDD option ordered	£12.50
	NE2000 Ethernet (thick, thin or twisted) network card	£29.00

## INTEL 486DX-33 SYSTEMS

Limited quantity of this 2nd year, superb small size desktop unit. Fully featured with standard simm connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor output, 256k cache and integral 120 Mb IDE drive with single 1.44 Mb 3.5" floppy disk drive. Fully tested and guaranteed. Fully expandable. Only **£199.00 (E)**

## FLOPPY DISK DRIVES 3 1/2" - 8"

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call for over 2000 unlisted drives for spares or repair.

- |  |             |
|--|-------------|
| 3 1/2" Panasonic JU363/4 720K or equivalent RFE            | £24.95 (B)  |
| 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only           | £25.95 (B)  |
| 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop             | £18.95 (B)  |
| 5 1/4" Teac FD-55GFR 1.2 Meg (for IBM pc's) RFE            | £18.95 (B)  |
| 5 1/4" Teac FD-55F-03-U 720K/40/80 (for BBC's etc) RFE     | £22.95 (B)  |
| 5 1/4" BRAND NEW Mitsubishi MF501B 360K                    | £22.95 (B)  |
| Table top case with integral PSU for HM 5 1/4" Flopp or HD | £29.95 (B)  |
| 8" Shugart 801/801 8" SS refurbished & tested              | £210.00 (E) |
| 8" Shugart 810 8" SS HH Brand New                          | £195.00 (E) |
| 8" Shugart 851 8" double sided refurbished & tested        | £260.00 (E) |
| 8" Mitsubishi M2894-63 double sided NEW                    | £295.00 (E) |
| 8" Mitsubishi M2896-63-02U DS slimline NEW                 | £295.00 (E) |
| Dual 8" cased drives with integral power supply 2 Mb       | £499.00 (E) |

## HARD DISK DRIVES

- |  |         |
|--|---------|
| 2 1/2" TOSHIBA (19 mm H) MK2101MAN 2.16 Gb. New                    | £199.00 |
| 2 1/2" TOSH. (12.5 mm H) MK1002MAV 1.1 Gb laptop. New              | £115.00 |
| 2 1/2" to 3 1/2" conversion kit for PC's, complete with connectors | £15.95  |
| 3 1/2" FUJII FK-309-26 20mb MFM I/F RFE                            | £59.95  |
| 3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE                 | £59.95  |
| 3 1/2" CONNER CP3044 40mb IDE I/F (or equiv.) RFE                  | £69.00  |
| 3 1/2" RODIME R03057S 45mb SCSI I/F (Mac & Acorn)                  | £69.00  |
| 3 1/2" QUANTUM 40S Prodrive 42mb SCSI I/F, New RFE                 | £149.00 |
| 3 1/2" WESTERN DIGITAL 850mb IDE I/F New                           | £185.00 |
| 5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv.) RFE                | £49.95  |
| 5 1/4" SEAGATE ST-238R 2 Gb RLL I/F Refurb                         | £69.95  |
| 5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested                     | £69.95  |
| 5 1/4" HP 97548 850 Mb SCSI RFE tested                             | £99.00  |
| 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested               | £195.00 |
| 8" NEC D2246 85 Mb SMD interface. New                              | £199.00 |
| 8" FUJITSU M2322K 160Mb SMD I/F RFE tested                         | £195.00 |
| 8" FUJITSU M2392K 2 Gb SMD I/F RFE tested                          | £345.00 |
- Many other drives in stock - Shipping on all drives is code (D)

## THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER  
CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers\* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

- |  |        |
|--|--------|
| TELEBOX ST for composite video input type monitors | £36.95 |
| TELEBOX STL as ST but fitted with integral speaker | £39.50 |
| TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner | £69.95 |
- For overseas PAL versions state 5.5 or 6 mHz sound specification. \*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Teleboxes\*, code (B)

## DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock Call for info / list.

## IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK

6,000,000 items EX STOCK

For MAJOR SAVINGS - CALL FOR SEMICONDUCTOR HOTLIST

## VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCEL-

LENT little used condition. Tilt & Swivel Base £4.75 Only £119 (E) Order as MITS-SVGA VGA cable for IBM PC included. External cables for other types of computers CALL.

As New - Ex Demo  
17" 0.28 SVGA Mitsubishi Diamond Pro monitors  
Full multisync etc. Full 90 day guarantee. £325.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed Dimensions: W14" x H12 3/4" x 15 1/2" D.

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen blem). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered. Only £79.00 (D)


KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition. Only £125 (E)

20" 22" and 26" AV SPECIALS  
Superbly made UK manufacture. Pll. all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. in EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

## SPECIAL INTEREST ITEMS

- |   |       |
|---|-------|
| MTS. FA3445ETKL 14" Industrial spec SVGA monitors 1Kw to 400 kw - 400 Hz 3 phase power sources - ex stock | £245  |
| IBM 8230 Type 1, Token ring base unit driver  | £760  |
| Wayne Kerr RA200 Audio frequency response analyser  | £2500 |
| IBM 53F5501 Token Ring ICS 20 port lobe modules   | £750  |
| IBM MAU Token ring distribution panel 8228-23-5050N   | £95   |
| AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE   | £550  |
| Trend DSA 274 Data Analyser with G703(2M) 64 v  | £600  |
| Marconi 6310 Programmable 2 to 22 GHz sweep generator   | £6500 |
| HP1650B Logic Analyser  | £3750 |
| HP3781A Pattern generator & HP3782A Error Detector  | £1800 |
| HP6821A Dual Programmable GPIB PSU 0-7 V 160 watts  | £675  |
| HP6264 Rack mount variable 0-20V @ 20A metered PSU  | £600  |
| HP54121A DC to 22 GHz four channel test set   | £1850 |
| HP7580A 1 8 pen HPGL high speed drum plotter  | £650  |
| F&B Wardrobe safe, insurance spec 1 hour rated fire safe  | £650  |
| Ex-G Brookfield 95035C Precision lock in amp  | £650  |
| View Eng. Mod 1200 computerised inspection system   | £1100 |
| Sony DXC-3000A High quality CCD colour TV camera  | £1100 |
| CSZ VERY Large 3 cavity thermal shock chamber   | £2000 |
| Phillips PW1730/10 XRAY generator with accessories  | £1150 |
| Keithley 590 CV capacitor / voltage analyser  | £3750 |
| Racal ICR40 dual 40 channel video recorder system   | £9500 |
| Fiskers 45KV 3 ph On Line UPS - New batteries   | £1900 |
| ICI R50300JV34 Cleanline ultrasonic cleaning system   | £2200 |
| Mann Tally MT645 High speed line printer  | £945  |
| Intel SBC 486/133SE Multibus 486 system, 8Mb Ram  | £1450 |
| Intel SBC 486/125C08 Enhanced Multibus (MSB) NEW  | £1150 |
| Zeta 3220-05 A0 4 pen HPGL fast drum plotters   | £1450 |
| Nikon HF11 (Ephiphot) exposure control unit   | £550  |
| Motorola VME Bus Boards & Components List. SAE / CALL   | £1950 |
| Trio 0-18 vdc linear, metered 30 amp bench PSU. New   | £1250 |
| Fujitsu M3041R 600 LPM band printer   | £500  |
| Fujitsu M3041D 600 LPM printer with network interface   | £500  |
| Perkin Elmer 2998 Infrared spectrophotometer  | £3750 |
| Perkin Elmer 597 Infrared spectrophotometer   | £2495 |
| VG Electronics 1035 TELETEXT Decoding Margin Meter  | £1995 |
| LightMetric SD 150H 18 channel digital hybrid chart recorder  | £2495 |
| Sekonic SD 150H 18 channel digital hybrid chart recorder  | £1995 |
| Taylor Hobson Talysurf amplifier / recorder   | £485  |
| System Video 1152 PAL waveform monitor  | £2950 |
| Siemans K4400 64Kb to 140Mb demux analyser  | £2950 |

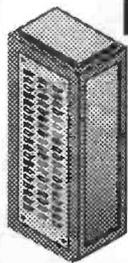

## 19" RACK CABINETS

Superb quality 6 foot 40U Virtually New, Ultra Smart Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile you have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

- |   |             |
|---|-------------|
| OPT Rack 1 Complete with removable side panels. | £345.00 (G) |
| OPT Rack 2 Rack, Less side panels               | £245.00 (G) |

Over 1000 racks, shelves, accessories 19" 22" & 24" wide 3 to 46 U high. Available from stock !!

## 32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enhance status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, pre-punched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal Blue. External dimension mm=1625H x 635D x 603 W. (4" H x 25" D x 23 3/4" W) Sold at LESS than a third of makers price !!

A superb buy at only £245.00 (G) 42U version of the above only £345 - CALL

## BATTERY SCOOP - 50% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12v DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SB51, featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. MB bot terminals. Fully guaranteed. Current makers price over £7 each! Our Price £35 each (c) or 4 for £99 (c)

## RELAYS - 200,000 FROM STOCK

Save ££££'s by choosing your next relay from our Massive stocks covering types such as - Military, Octal, Cradle Hermetically Sealed, Contactors, Time Delay, Reed, Mercur Wetted, Solid State, Printed Circuit Mounting, CALL US WITH YOUR NEEDS. Many obsolete types from stock. Save ££££'s

## LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-X and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 process and above) memory. Full data and driver disks supplied. RFE Fully tested and guaranteed. Windows compatible. £59.95 Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data. Order as: XT RAM UG. 256k. £34.95 or 512k £39.95

## SIMM SPECIALS

- |   |                       |
|---|-----------------------|
| 1 MB x 9 SIMM 9 chip 120ns                          | Only £8.50            |
| 1 MB x 9 SIMM 3 chip 80 ns                          | £10.50 or 70ns £11.95 |
| 1 MB x 9 SIMM 9 chip 80 ns                          | £10.50 or 70ns £11.75 |
| 4 MB 70 ns 72 pin SIMM -with parity-                | Only £35.00           |
| INTEL 486-DX33 CPU £19.95 INTEL 486-DX66 CPU £59.00 |                       |
- FULL RANGE OF CO-PROCESSOR'S EX STOCK - CALL FOR £££
- MOTOROLA 25 Mhz 68040 (XC68040RC25M) CPU'S £59.00 shipping charges for RAM / CPU upgrades is code B

## SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack and licence - OEM packaged. Special Price ONLY £99.00 Microsoft - Windows for Workgroups 3.11 & DOS 6.22. Supplied on 3 1/2" disks with license & documentation documentation. £39.95 DOS 5.0 on 3 1/2" disks with concise books c/w QBasic. £14.95 Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95 shipping charges for software is code B

Visit our London shop for a full range of Test Equipment and other bargains

DISPLAY  
-ELECTRONICS-

ALL MAIL & OFFICES  
Open Mon - Fri 9.00 - 5.30  
Dept ETI, 32 Bliggin Way  
Upper Norwood  
LONDON SE19 3XF

LONDON SHOP  
Open Mon - Sat 8.00 - 5.30  
215 Whitehorse Lane  
South Norwood  
On 68A Bus Route  
N.Thornton Heath & Selhurst Park SR Rail Stations

NEW DISTEL ©  
Visit our web site  
www.distel.co.uk  
email admin@distel.co.uk

ALL ENQUIRIES  
0181 679 4414  
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, School Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (AT)=£4.00 (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=£20.00. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of S&C and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1997. E & O E. 10/18

## **Dedicated Wireless Internet for Homes Before 2000?**

DECT (digitally enhanced cordless telecommunications) technology will be at the heart of a wireless Internet revolution in homes before the year 2000, according to Cambridge-based designers Symbionics.

The high-speed internet system will use technology similar to that in digital cordless telephones (like the former Rabbit cellular handsets, now in use as domestic cordless phones) to link PCs to a network of outdoor base stations with access to the internet. The base stations will link into the internet through fibre-optic cabling, copper wiring or microwave links. All three methods are capable of high-speed data transfer, and would operate separately from the telephone network.

At 550 kB/second, DECT technology can already transfer data ten times faster than telephone wires that use analogue modems. Symbionics aims to increase this to x20 over the next two years, using higher rate modulation schemes and equalisation technology. They say that the outdoor base stations will be accessible to PCs within a range of a few kilometres. The system will allow new operators without access to existing fixed-wire telephone lines to offer internet facilities. Connecting customers to the internet using DECT technology should prove cheaper than using telephone lines.

Italy will be the first country to adopt the system. Networks of DECT base stations are already being installed throughout the country's major towns and cities by telephone suppliers, who are expected to offer a service later in 1998. The new systems will handle voice mail, but significant demand for internet access and email is expected. Because internet and email will no longer tie up the telephone lines, it would be possible to use the PC and call out on the phone line simultaneously without installing a second line.


For more information contact Symbionics Ltd., St. Johns Innovation Park, Cowley Road, Cambridge CB4 4WS. Tel. 01223 421025 Fax 01223 421031.

## **Improved Resistor Paste Formula Doubles Pot Life**

Manufacturer Omeg has doubled the life of its 20mm potentiometers from 10,000 to more than 20,000 cycles. The life enhancement was achieved by improving and refining the conductive polymer resistor paste formulation used to make the resistive track.

The pastes contain hardwearing resins and polymers, solvents, lubricant, and carbon to provide the conductive/resistive properties. The track is made by screen printing the paste onto a paper based phenolic substrate, and then curing it in an oven. The curing process removes all solvents, and allows the conductive polymer to polymerise and cross-link. This produces a hard wearing track with good stability in terms of temperature and electrical resistance during its working life.

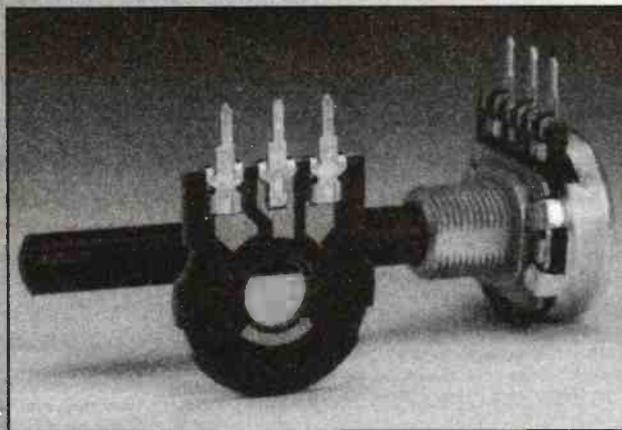The life of Omeg's 16mm potentiometers has also been increased to more than 20,000 cycles, a boost of 33 percent. The new life expectancy figures apply to all potentiometers in the catalogue, and any non-catalogue



specials with resistances higher than 1megohm (linear) or 470 kilohm (non-linear).

For more information contact M. Grantham, Omeg Ltd., Imberthorne Industrial Estate, East Grinstead, W. Sussex RH19 1RJ, UK. Tel 01342 410420 Fax 01342 316253. email: Omeg.Sales@Omeg.co.uk Web: [www.omeg.co.uk/omeg/](http://www.omeg.co.uk/omeg/)

Eurosoft (UK) have provided a solution to the "year 2000" computer date change known popularly as the "millennium problem". Their find-and-fix utility assists with the automatic date rollover of AT-style PCs and applications that were not originally programmed for the imminent 1999-to-2000 century year change. Using a small software utility, users can now automatically find out whether their PCs have the year 2000 date change problem, and fix the date change without adjusting the hardware setup. "Fix 2000" identifies the PC's BIOS to reveal whether the date rollover is supported or not, and then performs the correction to update the stored century value. For more information, contact Sharon Richards, Eurosoft (UK) Ltd., Hanover House, 136 Old Christchurch Rd., Bournemouth, Dorset BH1 1NL. Tel. 01202 297315.

## £1 BARGAIN PACKS

If you would like to receive the other four £1 lists and a lot of other lists, request these when you order or send SAE.

TEST PRODS FOR MULTIMETERS with 4mm sockets. Good length very flexible lead, Ref: D86.

8 OHM PM SPEAKERS, size 8" x 4", pack of two. These may be slightly rusty and that is why they are so cheap but are electrically OK. Ref: D102.

PAXOLIN PANELS, size 8" x 6", approximately 1/18" thick, pack of two, Ref: D103.

13A SOCKET, virtually unbreakable, ideal for trailing lead. Ref: D95.

PIEZO BUZZER with electronic sounder circuit, 3V to 9V D.C. operated, Ref: D76.

DITTO but without internal electronics, pack of two, Ref: D75.

LUMINOUS ROCKER SWITCH approximately 30mm sq, pack of two, Ref: D64.

ROTARY SWITCH, 9-pole, 5-way, small size ?? spindle, pack of two, Ref: D54.

FERRITE RODS, 7" with colls for Long and Medium waves, pack of two, Ref: D52.

DITTO but without colls, pack of three, Ref: D52.

MAINS DP ROTARY SWITCH with 1/4" control spindle, pack of five, Ref: D49.

ELECTROLYTIC CAP, 800µF at 6.4V, pack of 20, Ref: D48.

ELECTROLYTIC CAP, 1000µF + 100µF 12V, pack of 10, Ref: D47.

MINI RELAY with 5V coil, size only 26mm x 19mm x 1mm, has two sets of changeover contacts, Ref: D42.

MAINS SUPPRESSOR CAPS .1µF 250V A.C., pack of 10. Ref: 1050

TELESCOPIC AERIAL, chrome plated, extendable and folds over for Improved F. M. reception. Ref: 1051.

MES LAMP HOLDERS, slide on to 1/4" tag, pack of 10, Ref: 1054

PAXOLIN TUBING 3/16" internal diameter, pack of two, 12" lengths, Ref: 1056.

ULTRA THIN DRILLS, 0.4mm, pack of 10, Ref: 1042.

20A TOGGLE SWITCHES, centre off, part spring controlled, will stay on when pushed up but will spring back when pushed down, pack of two, Ref: 1043.

HALL EFFECT DEVICES, mounted on small heatsink, pack of two, Ref: 1022.

12V POLARISED RELAY, two changeover contacts, Ref: 1032.

PAXOLIN PANEL, 12" x 12" 1/18" thick, Ref: 1033.

MINI POTTED TRANSFORMER, only 1.5VA 15V-0V-15V or 30V, Ref: 964.

ELECTROLYTIC CAP, 32µF at 350V and 50µF section at 25V, in aluminium can for upright mounting, pack of two, Ref: 995.

PRE-SET POTS, one megohm, pack of five, Ref: 998.

WHITE PROJECT BOX with rocker switch in top left-hand side, size 78mm x 115mm x 35mm, unprinted, Ref: 1006.

5V SOLENOID, good strong pull but quite small, pack of two, Ref: 1012.

FIGURE-8 MAINS FLEX, also makes good speaker lead, 15m, Ref: 1014.

HIGH CURRENT RELAY, 24V A.C. or 12V D.C., three changeover contacts, Ref: 1016.

LOUDSPEAKER, 8 Ohm 5W, 3.7" round, Ref: 962.

NEON PILOT LIGHTS, oblong for front panel mounting, with internal resistor for normal mains operation, pack of four, Ref: 970.

3.5MM JACK PLUGS, pack of 10, Ref: 975.

PSU, mains operated, two outputs, one 9.5V at 550mA and the other 15V at 150mA, Ref: 968.

ANOTHER PSU, mains operated, output 15V A.C. at 320mA, Ref: 989.

PHOTOCELLS, silicon chip type, pack of four, Ref: 939.

LOUDSPEAKER, 5" 4 Ohm 5W rating, Ref: 939.

LOUDSPEAKER, 7" x 5" 4 Ohm 5W, Ref: 949

LOUDSPEAKER, 4" circular 6 Ohm 3W, pack of 2, Ref: 951

FERRITE POT CORES, 30mm x 15mm x 25mm, matching pair Ref: 901.

PAXOLIN PANEL, 81/2" x 31/2" width electrolytics 250µF and 100µF, Ref: 905.

CAR SOCKET PLUG with P.C.B. compartment, Ref: 917.

FOUR-CORE FLEX suitable for telephone extensions, 10m, Ref: 918.

PROJECT CASE, 95mm x 66mm x 23mm with removable lid, held by four screws, pack of two, Ref: 876.

SOLENOIDS, 12V to 24V, will push or pull, pack of two, Ref: 877.

2M MAINS LEAD, 3-core with instrument plug moulded on, Ref: 879

TELESCOPIC AERIAL, Chrome plated, extendable, pack of two, Ref: 884.

MICROPHONE, dynamic with normal body for hand holding, Ref: 885

CROCODILE CLIPS, superior quality flex, can be attached without soldering, five each red and black, Ref: 886

BATTERY CONNECTOR FOR PP3, superior quality, pack of four, Ref: 887.

LIGHTWEIGHT STEREO HEADPHONES Ref: 898.

PRESETS, 470 Ohm and 220 kilohm, mounted on single panel, pack of 10, Ref: 849.

THERMOSTAT for ovens with 1/4" spindle to take control knob, Ref: 857.

12V-QV-12V 10W MAINS TRANSFORMER, Ref: 811.

18V-QV-12V 10W MAINS TRANSFORMER, Ref: 813.

AIR-SPACED TRIMMER CAPS, 2pF to 20pF, pack of two, Ref: 818.

AMPLIFIER, 9V or 12V operated Mullard 1153, Ref: 823.


2 CIRCUIT MICROSWITCHES, Iicon, pack of 4, Ref: 825.

LARGE SIZE MICROSWITCHES changeover contacts, pack of two, Ref: 825.

MAINS VOLTAGE PUSH SWITCH with white dolly, through panel mounting by hexagonal nut, Ref: 829.

POINTER KNOB for spindle which is just under 1.4", like most thermostats, pack of four, Ref: 833.
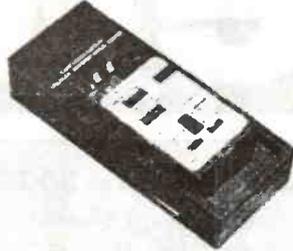
## CAMCHARGER CAMRECORDER BATTERY QUICK CHARGER (WITH RECONDITIONER & TESTER)



Brand new and boxed. Normal price £35, yours for £15, Order Ref: 15P73.

## TOROIDAL MAINS TRANSFORMERS

All with 220/240V primary winding, 0.30V + 0.30V at 120VA, would give you 30V at 4A or 60V at 2A, price £8. Order 8PE2. Order Ref: 8PG2. 0.110V + 0.110V at 120VA would give you 110V at just over 8A or 220V at 1/2A, price £8. Order Ref: 8PG3. 0.35V + 0.35V at 150VA would give you 35V at 4A or 70V at 2A. Price £8. Order Ref: 8PG9. 0.35V + 0.35V at 220VA would give you 35V at 61/2A or 70V at 31/4A, price £9. Order Ref: 9PG4. 0.110V + 0.110V at 220VA would give you 110V at 2A or 220V at 1A, price £10. Order Ref: 10PG5. 0.45V + 0.45V at 500VA would give you 45V at 11A or 90V at 51/2A, price £20. Order Ref: 20PG7. 0.110 + 0.110V at 500VA would give you 110V at 5A or 220V at nearly 3A, price £25, Order Ref: 25PG7.

SUPER WOOFERS. A 10" 4ohm with a power rating of 250W music and normal 150W. Normal selling price for this is £55 + VAT, you can buy at £29 including VAT and carriage, Order Ref: 29P7. The second one is a 8" 4ohm. 200W music, 200W normal. Again by Challenger, price £18, Order Ref: 18P9.

Deduct 10% from these prices if you order in pairs or can collect. These are all brand new in maker's packing.

## SOLDERING IRON.

Super mains powered with long life ceramic element, heavy duty 40W for that extra special job. Complete with plated wire stand and 245mm leads, £3, Order Ref: 3P221.



## YOU SAVE £40

THE JAP MADE 12V 12A-SEALED BATTERY from regular suppliers costs £50, you can have one from us for only £10 including VAT if you collect or £12 if we have to send. Being sealed it can be used in any position and is maintenance free. All in tip top condition and fully guaranteed, Order Ref: 12P32. Or if you want a smaller one we have 12V 2.3AH, regular price £14, yours for only £3.50, Order Ref: 3.5P11.



FLASHING BEACON. Uses an XENON tube and has amber-coloured dome with separate bracket, 12V operated. Price only £5. Order Ref: 5P 267.

HIGH RESOLUTION MONITOR. 9" by Philips, in metal frame for easy mounting. Brand new, offered at less than the price of the tube alone. £15, Order Ref: 15P1.

15W 8" SPEAKER AND 3" TWEETER. Amstrad, made for their high quality music centre. £4 per pair. Order Ref: 4P57.

INSULATION TESTER WITH MULTIMETER. Internally generates voltages which enables you to read insulation directly in megohms. The multimeter has four ranges. AC/DC Volts, 3 ranges millamps, 3 ranges resistance and 5 amp range. These instruments are ex-British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50, yours for only £7.50 with leads, carrying case £2 extra. Order Ref: 7.5P4.

We have some of the above testers but slightly faulty, not working on all ranges, should be repairable, we supply, diagram, £3, Order Ref: 3P176.

250W LIGHT DIMMER. Will fit in place of normal wall switch, only £2 each. Order Ref: 2P380. Note these are red, blue, green or yellow but will take emulsion to suit the colour of your room. Please state colour required.

LCD 31/2" DIGIT PANEL METER. This is a multi-range voltmeter/ammeter using the A-D converter chip 7106 to provide five ranges each of volts and amps. Supplied with full data sheet. Special snip price of £12, Order Ref: 12P19.

MINI BLOW HEATER. 1kW, ideal for under desk or airing cupboard, etc. Needs only a simple mounting frame, £5, Order Ref: 5P23.

MEDICINE CUPBOARD ALARM. Will warn when cupboard door is opened. Light makes the bell ring. Neatly cased, requires only a battery, £3, Order Ref: 3P155.

DON'T LET IT OVERFLOW. Be it bath, sink, cellar, sump, etc., this device will tell you when the water has risen to the pre-set level. Adjustable, neatly cased for wall mounting, £3, Order Ref: 3P156.

DIGITAL THERMOMETER. Suitable for outdoors or indoors, has an extra wide temperature range -50° to +70°C, complete with heavy duty battery which should last several years. Its sensor can be outside, but with the read-out inside. £4, Order Ref: 4P104.

## SMART HIGH QUALITY ELECTRONIC KITS

All kits are complete with PCB and other components in a blister pack. If you want more information about them, we have copies of the illustrated Smart catalogue available price £1.

Cat. No.	Description	Price £	Cat. No.	Description	Price £
1003	5 watt electronic siren	2.55	1089	L.E.D. flasher/555 tester	1.61
1005	Touch switch	2.87	1090	Stress meter	3.22
1008	SF function generator	6.90	1093	Windscreen wiper controller	3.68
1010	5-input stereo mixer, with monitor output	19.31	1094	Home alarm system	12.42
1016	LOUDspeaker protection unit	3.22	1095	Lead acid battery charger	3.45
1017	Linear CB 30W amp	4.70	1100	2 x 18 watt integrated amplifier	18.39
1020	0.5 min. time switch	4.70	1101	Dollar tester	4.70
1023	Dynamic headphone preamp	2.50	1103	L.E.D. power meter	1.84
1025	7 watt hi-fi power amplifier	2.53	1106	Thermometer with l.e.d.s.	6.90
1026	Running lights	4.60	1107	Electronics to help win the pools	3.68
1027	NiCad battery charger	3.91	1112	LOUDspeaker protection with delay	4.60
1030	Light dimmer	2.53	1113	2 x 18 watt power amplifier	5.98
1032	Stereo tone control	3.55	1115	Courtesy light delay	2.07
1035	Space sound effects	2.30	1118	Xxxx-switch, with triac, 0.10 mins	4.14
1039	Stereo VU meter	4.60	1119	Telephone line recording device	5.25
1042	AF generator 250Hz-16kHz	1.70	1123	Morse code generator	1.84
1043	Loudness stereo unit	3.22	1124	Electronic bell	2.76
1047	Sound switch	5.29	1125	Telephone lock	2.68
1048	Electronic thermostat	3.68	1126	Microphone preamplifier	4.60
1050	3-input hi-fi stereo preamplifier	12.42	1127	Microphone tone control	4.60
1052	3-input mono mixer	6.21	1128a	Power flasher 12V d.c.	2.53
1053	Electronic metronome	3.22	1133	Stereo sound-to-light	5.26
1054	4-input instrument mixer	2.76			
1056	8V-20V 8A stabilised power supply	12.42			
1057	Cassette head preamplifier	3.22			
1059	Telephone amplifier	4.60			
1060	+40V 8 A power supply	8.28			
1061	12V 1/2A stabilised power supply	3.36			
1062	5V 0.5A stabilised supply for TTI	2.30			
1063	12V 2A power supply	2.30			
1064	+12V 0.5A stabilised supply	3.22			
1067	Stereo VU meter with leads	9.20			
1068	18V 0.5A stabilised power supply	2.53			
1070	HI-FI preamplifier	7.47			
1085	D.C. converter: 12V to 6V or 7.5V or 9V	2.53			
1086	Music-to-light for your car	4.60			

### TERMS

Send cash, PO, cheque or quote credit card number - orders under £25 add £3.50 service charge.

**J & N FACTORS**  
Pilgrim Works (Dept. E.T.I.)  
Stairbridge Lane, Bolney,  
Sussex RH17 5PA  
Telephone: 01444 881965

# AVR

## the new chip on the block

*Development kit designer Kevin Kirk tells what he likes about the Atmel AVR 1200, the microcontroller with the nanosecond instruction cycle time.*

**O**ne of the fastest growing sectors of the electronics market is microcontrollers. In 1994 the market was quantified as 7 billion US dollars. It is now 14 billion US dollars, and is expected to be 20 billion US dollars in 1999 - and this is just the 8-bit market. If you add the 4-, 16- and 32-bit markets you could double those figures at least. In the hobbyist sector, the best known microcontroller is the PIC, which finds its way into a good proportion of all projects published. The appeal of the PIC is obvious: it is cheap, small and has a low-cost starter kit that everyone can afford.

But the electronics industry moves on all the time, and now there is a plethora of microcontrollers available, some general-purpose and others targeted at specific markets, such as the new Cypress CY7C63xxx microcontroller, designed specifically for USB bus applications.

We, the developers and end-users, are becoming more discerning. If we were to create a wish list for the ideal microcontroller, we would probably list the following much-desired features:

- Low cost
- Low power consumption
- High speed
- A low-cost starter kit
- Re-programmable hundreds of times
- Interrupt capabilities
- Re-programmable without removing it from the circuit into which it is soldered
- Programming will not need any special programming voltages
- At least some analogue capabilities
- Easy to use
- A rich instruction set
- The option of an on-board clock for minimal component designs
- A watchdog timer (primarily for EMC purposes)
- High level (C) language support
- Substantial source and sink capabilities on each I/O pin (enough at least to drive an LED)
- Some security features (such as lock bits) to ensure the onboard code cannot be read
- Quite a tall order!

But we are the customers, and we are getting choosy. After a considerable amount of research we came up with only one

device that would fit the bill. You've guessed it - it was the Atmel AVR. Atmel, the manufacturers, are a bit coy about how their new offspring got its name. Suffice it to say that it is a RISC processor, and the design team leaders are called Alf and Vergard, so if you are any good at crossword puzzles you could probably make an estimate.

### The internal architecture

Most microcontrollers perform their operations using some kind of central register, through which all the mathematics and Boolean operations are carried out. In the venerable old 51 series you had the 'A' register. The PIC has its 'W' register. While this is fine for chip designers, it does create some problems for the circuit designer trying to shoehorn a multiple interrupt operating system into the parsimonious amount of memory generously allocated by the manufacturers. Students of the history of computing will recognise the origins of this type of structure, for instance, the DEC PDP8. The designers of the AVR have decided to write their own story here, and have created a multiple register based system, of 32 registers (see the block diagram in **figure 1**), each of which is effectively capable of this task. So dealing with interrupts becomes easy: just use another register as your main working register. Then you can get out and away before comparable processors have finished shuffling data to let you get at the main register. So ISRs can be fast and neat.

While we're talking about speed, it is a good idea to look at exactly what a processor does with its clock pulses. The clock is the heart of the processor. Without the clock, you've just got a black slab of plastic with some shiny legs. The 51, bless it, divides the clock pulses by 12 (called 'p' states by Intel and 't' states by the rest of the universe). It uses these time slots to perform various tasks like setting high byte memory addressing, low byte memory addressing, instruction fetches, instruction decoding and so on. So if you start with a clock of, say, 12MHz, after the division the internal clock lumbers along at a sedate rate of 1MHz. So an instruction cycle takes at least 1 microsecond. The PIC did better than this: there, the clock was divided by 4 and, if you count the fact that the processor actually performs a pre-fetch while executing the last instruction, then we could say that they have a divide-by-2 on the clock. But the AVR doesn't bother with dusty old divides - it just performs everything in one clock cycle. If your clock is 16MHz, then your instruction cycle time is 62.5 nanoseconds. No other small, low



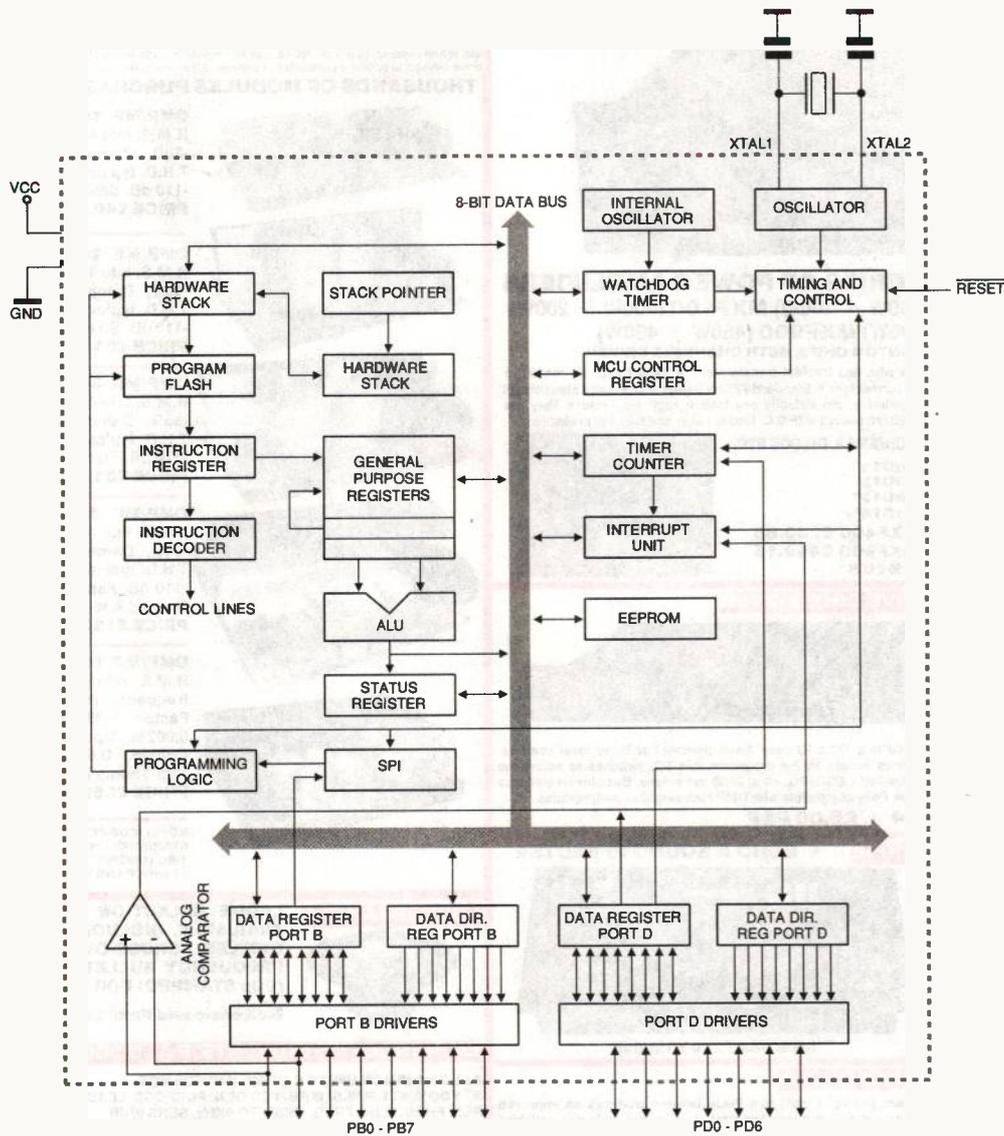


Figure 1: the block diagram of the AT90S1200

cost chip comes close to this performance.

Another way of speeding the beast up is to have a reduced instruction set, aka RISC. Essentially, microprocessors are fairly stupid animals: every time they get an instruction, they have to go and look up how to deal with that instruction. So, in theory, if you reduce the number of instructions then the processor will spend less time hunting through its internal library, and so it moves faster. The PIC is an excellent example of this. Its makers Microchip couldn't have reduced the instruction set more if they'd tried. And they probably did. That's a clever bit of work! If you study the instruction set of the AVR (see **figure 2**), you will immediately be struck by the fact that, with over 180 instructions it is hardly a reduced instruction set. However, if you root around in the binary structures of the instruction coding, you will find see that many of the instructions are actually duplicates under a different name. So, in reality, you are getting a RISC core with a CISC (complex) instruction set.

### Reprogramming

OK, so now we've dealt with the speed issue. To many hobbyists this isn't an issue at all - getting the thing to work in

the first place is what matters. If you are one of those fortunate (or weird) people that can write code and get it to work first time, reprogramming the device is not something you need concern yourself about. To the rest of us it is of vital importance. If you belong to the 'masochist' school of designers, you will probably be happy with the EPROM version of a device that you can program, test and then spend 20 minutes waiting for it to erase. Microchip, with the 16C84, added some EEPROM on so that you could electrically erase the program memory and reprogram it up to 100 times.


Atmel have taken a different route and have stuffed Flash ram (see **figure 3**) in as their main program memory, which gives you at least 1,000 reprogramming lives. So even if you have the confidence of a Conservative candidate in the middle of the last Election Count, you are unlikely to use up that many programming lives. It also has ISP (In-System Programming) capability, which is a fancy way of saying that you can program the device even if its soldered into a circuit. Arguably, the PIC 16C84 has had this facility all along, and there have been some pretty neat circuits banded around that let you do it. The problem is Vpp, which is the voltage you must apply to the

**POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS**

↑ PRICES INCLUDE V.A.T. & PROMPT DELIVERY & FRIENDLY SERVICE ↑ LARGE (A4) S.A.E. €5 STAMPED FOR CATALOGUE ↑

**OMP MOS-FET POWER AMPLIFIERS HIGH POWER. TWO CHANNEL 19 INCH RACK**

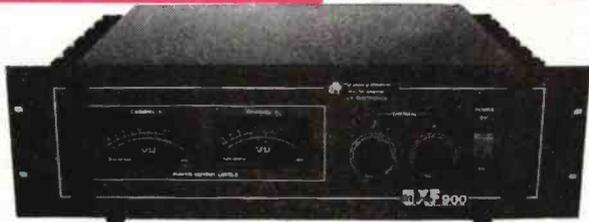**THOUSANDS PURCHASED BY PROFESSIONAL USERS**



**THE RENOWNED MXF SERIES OF POWER AMPLIFIERS FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W) MXF600 (300W + 300W) MXF900 (450W + 450W) ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN**

**FEATURES:** ★ Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

**USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.**

**SIZES:-** MXF200 W19"xH3 1/2" (2U)xD11"  
MXF400 W19"xH5 1/4" (3U)xD12"  
MXF600 W19"xH5 1/4" (3U)xD13"  
MXF900 W19"xH5 1/4" (3U)xD14 1/2"

**PRICES:-** MXF200 £175.00 MXF400 £233.85  
MXF600 £329.00 MXF900 £449.15  
SPECIALIST CARRIER DEL. £12.50 EACH



**OMP XO3 STEREO 3-WAY ACTIVE CROSS-OVER**



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DCL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

**Price £117.44 + £5.00 P&P**

**STEREO DISCO MIXER SDJ3400S ★ ECHO & SOUND EFFECTS ★**

**STEREO DISCO MIXER** with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.



**Price £144.99 + £5.00 P&P**

**SIZE: 482 x 240 x 120mm**

**PIEZO ELECTRIC TWEETERS - MOTOROLA**

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**

**TYPE 'A'** (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.  
**TYPE 'B'** (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.  
**TYPE 'C'** (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.  
**TYPE 'D'** (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.  
**TYPE 'E'** (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.  
**LEVEL CONTROL** Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

TYPE 'A' TYPE 'B'  
TYPE 'C' TYPE 'E'  
TYPE 'D'

**IBI FLIGHT CASED LOUDSPEAKERS**

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complemented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.



**POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz**

**IBI FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR**  
**IBI FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR**

SPECIALIST CARRIER DEL. £12.50 PER PAIR

**OPTIONAL STANDS PRICE PER PAIR £49.00**  
Delivery £6.00 per pair

**IN-CAR STEREO BOOSTER AMPS**



**PRICES:-** 150W £49.99 250W £99.99  
400W £109.95 P&P £2.00 EACH

**THREE SUPERS HIGH POWER CAR STEREO BOOSTER AMPLIFIERS**

150 WATTS (75 + 75) Stereo, 150W Bridged Mono  
250 WATTS (125 + 125) Stereo, 250W Bridged Mono  
400 WATTS (200 + 200) Stereo, 400W Bridged Mono  
**ALL POWERS INTO 4 OHMS**  
**Features:**  
★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

**OMP MOS-FET POWER AMPLIFIER MODULES SUPPLIED READY BUILT AND TESTED.**

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

**THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS**



**OMP/MF 100 Mos-Fet Output power 110 watts** R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/us, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.  
**PRICE £40.85 + £3.50 P&P**



**OMP/MF 200 Mos-Fet Output power 200 watts** R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/us, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.  
**PRICE £64.35 + £4.00 P&P**



**OMP/MF 300 Mos-Fet Output power 300 watts** R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/us, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.  
**PRICE £81.75 + £5.00 P&P**



**OMP/MF 450 Mos-Fet Output power 450 watts** R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/us, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.  
**PRICE £132.85 + £5.00 P&P**



**OMP/MF 1000 Mos-Fet Output power 1000 watts** R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/us, T.H.D. typical 0.002%, input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm.  
**PRICE £259.00 + £12.00 P&P**

**NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. P.C. (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR P.C.**

**LOUDSPEAKERS**

**LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.**



McKenzie and Fane Loudspeakers are also available.

**EMINENCE:- INSTRUMENTS, P.A., DISCO, ETC**

**ALL EMINENCE UNITS 8 OHMS IMPEDANCE**

8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £32.71 + £2.00 P&P  
RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB.  
10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. PRICE £33.74 + £2.50 P&P  
RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB.  
10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. PRICE £43.47 + £2.50 P&P  
RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB.  
12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. PRICE £35.64 + £3.50 P&P  
RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB.  
12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB. PRICE £36.67 + £3.50 P&P  
12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. PRICE £46.71 + £3.50 P&P  
RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 98dB.  
12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. PRICE £70.19 + £3.50 P&P  
RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB.  
15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. PRICE £50.72 + £4.00 P&P  
RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB.  
15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. PRICE £73.34 + £4.00 P&P  
RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB.

**EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC**

**ALL EARBENDER UNITS 8 OHMS** (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)  
**BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND**  
8" 50watt EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P  
RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB.  
10" 50watt EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P  
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 99dB.  
10" 100watt EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P  
RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.  
12" 100watt EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P  
RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.  
**FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**  
5 1/4" 60watt EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P  
RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.  
6" 60watt EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P  
RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.  
8" 60watt EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P  
RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 89dB.  
10" 60watt EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P  
RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

**TRANSMITTER HOBBY KITS**

**PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS**  
3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P  
FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P



PHOTO: 3W FM TRANSMITTER

**B.K. ELECTRONICS**

UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA.

ESSEX SS2 6TR

Tel. 01702 52752 Fax 01702 420243

POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.



Mnemonics	Operands	Description	Flags
ADD	Rd,Rr	Add without Carry	Z,C,N,V,H
ADC	Rd,Rr	Add with Carry	Z,C,N,V,H
SUB	Rd,Rr	Subtract without Carry	Z,C,N,V,H
SUBI	Rd,K	Subtract Immediate	Z,C,N,V,H
SBC	Rd,Rr	Subtract with Carry	Z,C,N,V,H
SBCI	Rd,K	Subtract Immediate with Carry	Z,C,N,V,H
AND	Rd,Rr	Logical AND	Z,N,V
ANDI	Rd,K	Logical AND with Immediate	Z,N,V
OR	Rd,Rr	Logical OR	Z,N,V
ORI	Rd,K	Logical OR with Immediate	Z,N,V
EOR	Rd,Rr	Exclusive OR	Z,N,V
COM	Rd	One's Complement	Z,C,N,V
NEG	Rd	Two's Complement	Z,C,N,V,H
SER	Rd,K	Set Bit(s) in Register	Z,N,V
CER	Rd,K	Clear Bit(s) in Register	Z,N,V
INC	Rd	increment	Z,N,V
DEC	Rd	Decrement	Z,N,V
TST	Rd	Test for Zero or Minus	Z,N,V
CLR	Rd	Clear Register	Z,N,V
SER	Rd	Set Register	none
CP	Rd,Rr	Compare	Z,C,N,V,H
CPC	Rd,Rr	Compare with Carry	Z,C,N,V,H
CPI	Rd,K	Compare with Immediate	Z,C,N,V,H
RJMP	k	Relative Jump	None
RCALL	k	Relative Call Subroutine	None
RET		Subroutine Return	None
RETI		Interrupt Return	I
CPSE	Rd,Rr	Compare, Skip if Equal	None
SBRC	Rd,b	Skip if Bit In Register Cleared	None
SERS	Rd,b	Skip if Bit in Register Set	None
SBIC	P,b	Skip if Bit in I/O Register Cleared	None
SBIS	P,b	Skip if Bit in I/O Register Set	None
BRBS	s,k	Branch if Status Flag Set	None
BRBC	s,k	Branch if Status Flag Cleared	None
BREQ	k	Branch if Equal	None
BRNE	k	Branch if Not Equal	None
BRCS	k	Branch if Carry Set	None
BRCC	k	Branch if Carry Cleared	None
BRSH	k	Branch if Same or Higher	None
BRLO	k	Branch if Lower	None
BRMI	k	Branch if Minus	None
BRPL	k	Branch if Plus	None
BRGE	k	Branch if Greater or Equal, Signed	None
BRLT	k	Branch if Less Than, Signed	None
BRHS	k	Branch if Half Carry Flag Set	None
BRHC	k	Branch if Half Carry Flag Cleared	None
BRTS	k	Branch if T Flag Set	None
BRTC	k	Branch if T Flag Cleared	None
BRVS	k	Branch if Overflow Flag Set	None
BRVC	k	Branch if Overflow Flag Cleared	None
BRIE	k	Branch if Interrupt Enabled	None
BRID	k	Branch if Interrupt Disabled	None
MOV	Rd,Rr	Copy Register	None
LDI	Rd,K	Load Immediate	None
LD	Rd,Z	Load Indirect	None
ST	Z, Rd	Store Indirect	None
IN	Rd,P	In Port	None
OUT	P,Rd	Out Port	None
LSL	Rd	Logical Shift Left	Z,C,N,V,H
LSR	Rd	Logical Shift Right	Z,C,N,V
ROL	Rd	Rotate Left Through Carry	Z,C,N,V,H
ROR	Rd	Rotate Right Through Carry	Z,C,N,V
ASR	Rd	Arithmetic Shift Right	Z,C,N,V
SWAP	Rd	Swap Nibbles	None
BSET	s	Flag Set	SREG(s)
BCLR	s	Flag Clear	SREG(s)
SBI	P,b	Set Bit in I/O Register	None
CBI	P,b	Clear Bit in I/O Register	None
BST	Rr,b	Bit Store from Register to T	T
BLD	Rd,b	Bit Load from T to Register	None
SEC		Set Carry	C
CLC		Clear Carry	C
SEN		Set Negative Flag	N
CLN		Clear Negative Flag	N
SEZ		Set Zero Flag	Z
CLZ		Clear Zero Flag	Z
SEI		Global Interrupt Enable	I
CLI		Global Interrupt Disable	I
SES		Set Signed Test Flag	S
CLS		Clear Signed Test Flag	S
SEV		Set Two's Complement Overflow Flag	V
CLV		Clear Two's Complement Overflow Flag	V
SET		Set T in SREG	T
CLT		Clear T in SREG	T
SEH		Set Half Carry Flag in SREG	H
CLH		Clear Half Carry Flag in SREG	H
NOP		No Operation	None
SLEEP		Sleep	None
WDR		Watchdog Reset	None

Figure 2: the AVR instruction set

device to allow it to go into programming mode. On the PIC, this is 12 volts, applied on the reset pin. On the AVR it is 0 volts; in other words, you only need to apply a low to the reset line, which then configures itself with a synchronous serial port into which you stuff your program code. So you really can solder it in and then program it (see **figure 4** for details of the programming interface pin-outs) without the need for an extraneous Vpp supply rail.

This particular device has 1K bytes of program code space, which is a little disingenuous, as it uses two bytes per instruction, and 64 bytes of EEPROM data space. The EEPROM operation is self-timed, which is nice, and is good for over 100,000 erase/write cycles and the data will last for 100 years (That kind of specification always makes me want to ask: how do they know?). This particular version has no static RAM as such, as it uses the registers, but later versions of the family are surprisingly rich in program storage, RAM and EEPROM.

The main weakness on the AVR is the way you get to the I/O ports. The PIC treats the I/O ports like registers, which makes them very easy to use. The AVR uses a different approach, which is to treat them as ports (it does sound logical when you put it like that, doesn't it?) using IN and OUT instructions, just like in a PC. Inevitably, this reduces the flexibility, as you should really have a shadow register set up to move byte-wide data in and out of the port. Bit instructions like Test, Set and Clear are directly available on the port pins, however. The consolation is that it does have a slightly more flexible port-reading mechanism. You have two methods of reading the port: one is to go ahead and read the port pins, and the other is to read the output registers associated with that port pin. What's the difference? Look at it like this: imagine you are using the port to directly drive the base of a bipolar transistor. Basic transistor theory tells you that the base is not going to go higher than 0.7 volts (or thereabouts) with respect to the emitter. So, if you switch the transistor on by applying a 1 to the port, it actually goes up to 0.7V and no further. If you then read the port, the processor reads this as a 0. Now if you were doing a read/modify/write sequence of instructions, you would read all 8 bits of the port, twiddle them a bit, and then write them back. Unfortunately, because you read the port as a 0 it will write it back as a 0 and so the transistor will turn off. Therein lies madness! Of course, if you read the register, it will happily send back the 1 it is set to. The ports are, like the PIC but unlike the 51 series, true tri-state, and they can source up to 4mA and sink a good 28mA, which is enough for even the thirstiest LED. It could probably even drive a laser diode if you're not hoping to illuminate parts of the moon.

It really is handy having some sort of analogue capability on your microcontroller. A full-blown Analogue to Digital converter, with at least 10 bits of resolution, would be nice, but any analogue interface is useful. The AVR has a comparator. This may sound boring, but you can create all sorts of neat tricks with one of these, particularly if it is tied to the interrupt structure and has a propagation delay of only 500ns. Now, what if I promised ETI readers some projects using this facility to perform all sorts of clever little jobs?

## The watchdog

Microcontrollers need to be able to perform control tasks on their own, which means that if they crash then they must be able to recover without recourse to human intervention. If your PC crashes when running Windows 95 then you can press reset and off you go, no harm done, except to your blood pressure and anything you forgot to save up to that point. If your microcontroller is controlling the nuclear fusion project you have

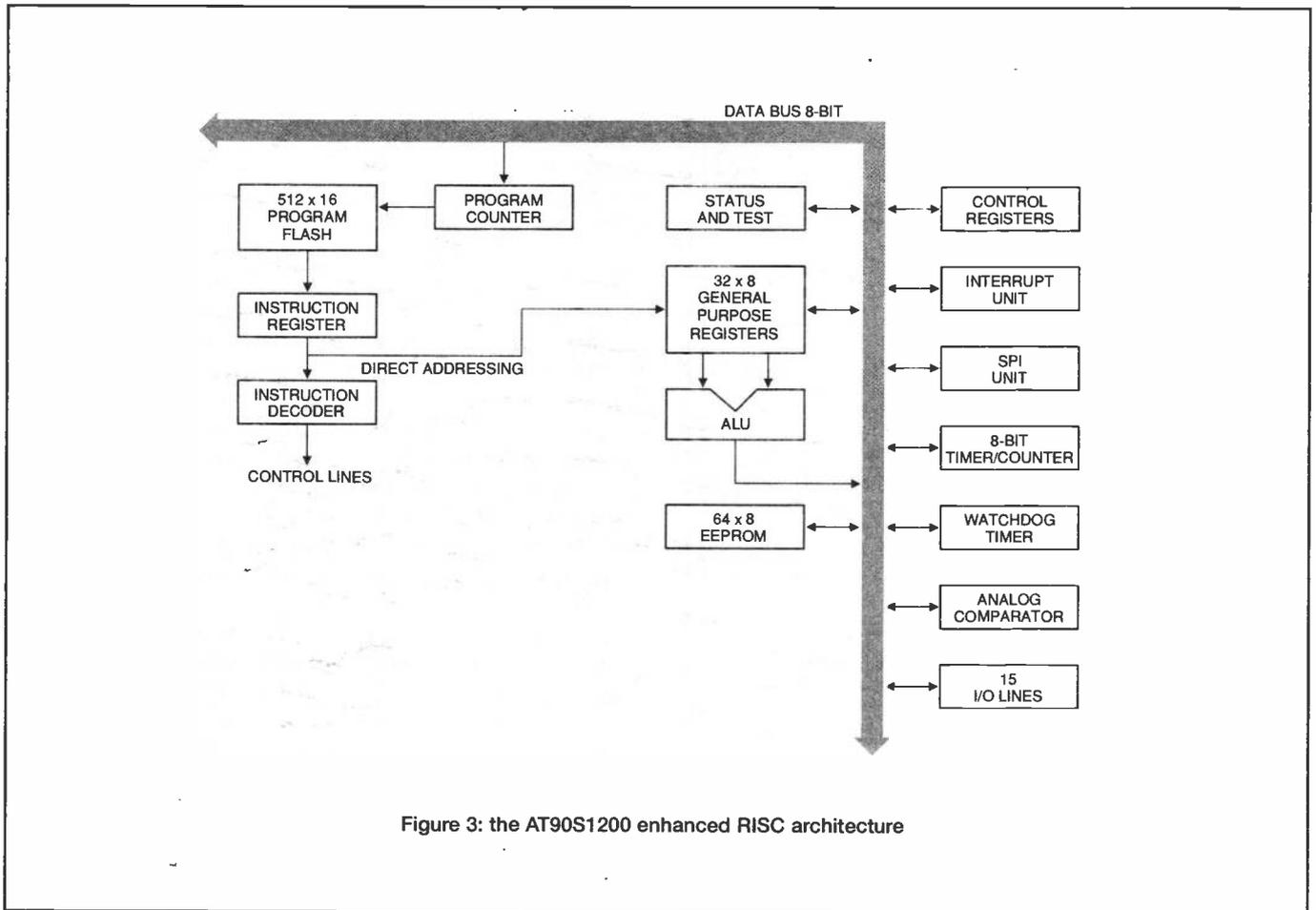


Figure 3: the AT90S1200 enhanced RISC architecture

in your basement, then it is annoying if it crashes and the reactor goes critical. The worst thing with a microcontroller crash is that you usually don't know that it has happened. When Windows 95 crashes then it glares balefully at you and refuses to do anything. You may now know why, but at least you know. With a microcontroller, you may not have any user feedback at all, so it has to be self-sufficient. Atmel recognised this and included a watchdog circuit. The operation of a watchdog is surprisingly simple. Imagine you are sitting in your mother in law's house with her pet Pit Bull terrier. You need to tell it 'good boy' every couple of minutes, or it will sink its fangs into anything it can reach. You keep up the 'good boys' and everything is fine, but forget for a moment, or go to sleep and ... The watchdog on the microcontroller is very similar. It is a timer which must be reset by the processor at regular intervals. If the processor doesn't reset it (because it has crashed), then the timer times out and resets the processor.

A processor crash takes one of two forms. The first is that it leaps into a software loop from which there is no escape, which is usually because of poor software design, and the other is where it slips a cog and gets its operators and operands mixed up. In order for a processor to process an instruction, it needs details of both the instruction (the operator) and the register(s) on which it is to perform the operation and store the result (the operand). If it gets these two mixed up, usually because a glitch in the power has created a knot in its lingerie, then it tries to decode operands as

operators. The only way out of this is to reset the processor. Under the rules for EMC compliance, the system must be immune to electrical interference; put more bluntly, this means that if you zap the system with more volts than it wants for operation, then it should be capable of recovering itself and carrying on sweetly as before. Put very simply indeed, if you want to design microcontroller-based equipment with the (required) CE mark, then it must have a watchdog.

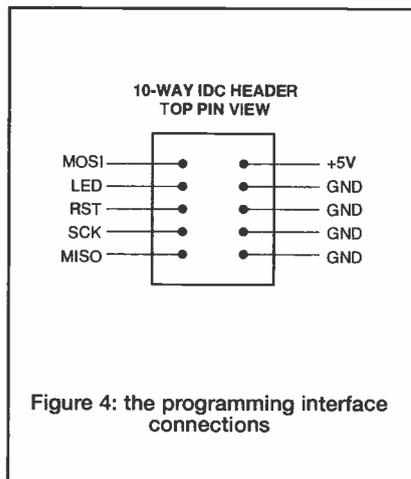



Figure 4: the programming interface connections

### Pulse width modulation

This may be a good time to look at pulse width modulation and what it can do for you. If you've ever looked at hi-fi, you will be aware of the various classes of amplifier. First there is class A, in which the output stage is biased to the mid point in the device's swing. This means that the output device will conduct the whole of the waveform, so that distortion is lower. The problem here is inefficiency, as much of the power is wasted as it consumes power even in its quiescent state. Next is class B, with two transistors (or valves) arranged

such that one conducts on positive half cycles and the other on negative. During its quiescent stage both transistors are off, so that it is very much more efficient. The fact that you need to put about 0.7V on the base of the transistor before it conducts means that there will be a point where both transistors are off during the crossover stage. This introduces crossover distortion. Class C is for RF applications, so I'll skip that.

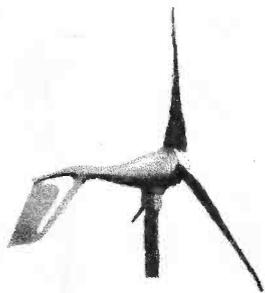Class D (or class E if you happen to be Japanese) uses a



## WIND GENERATORS 380 WATT

1.14 metre dia blades, carbon matrix blades, 3 year warranty, 12vdc output, 24v version available, control electronics included, brushless neodymium cubic curve alternator, only two moving parts, maintenance free, simple roof top installation, start up speed 7mph, max output (30mph) 380w. £499 ref AIR1

## PLANS

**PORTABLE X RAY MACHINE PLANS** Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £6/set. Ref FJXP1.

**TELEKINETIC ENHANCER PLANS** Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon. £4/set Ref F/TK1.

**ELECTRONIC HYPNOSIS PLANS & DATA** This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15/set. Ref F/EH2.

**GRAVITY GENERATOR PLANS** This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means- cause it to levitate. £10/set Ref F/GRA1.

**WORLDS SMALLEST TESLA COIL/LIGHTENING DISPLAY GLOBE PLANS** Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects, 'Plasma in a jar', St Elmo's fire, Corona, excellent science project or conversation piece. £5/set Ref F/BTC1/LG5.

**COPPER VAPOUR LASER PLANS** Produces 100mw of visible green light. High coherency and spectral quality similar to Argon laser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £10/set Ref F/CV1.

**VOICE-SCRAMBLER PLANS** Miniature solid state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £6/set Ref F/V59.

**PULSED TV JOKER PLANS** Little hand held device utilises pulse techniques that will completely disrupt TV picture and sound! works on FM too! DISCRETION ADVISED. £8/set Ref F/TJ5.

**BODYHEAT TELESCOPE PLANS** Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent security device or very interesting science project. £8/set Ref F/BHT1.

**BURNING, CUTTING CO2 LASER PLANS** Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting, plastics, textiles etc. £12/set Ref F/LC7.

**DYNAMO FLASHLIGHT** Interesting concept, no batteries needed just squeeze the trigger for instant light apparently even works under water in an emergency although we haven't tried it yet! £6.99 ref SC152

**ULTRASONIC BLASTER PLANS** Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PC boards, jewellery, coins, small parts etc. £6/set Ref F/ULB1.

**ANTI DOG FORCE FIELD PLANS** Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate. £6/set Ref F/DOG2.

**LASER BOUNCE LISTENER SYSTEM PLANS** Allows you to hear sounds from a premises without gaining access. £12/set Ref F/LLIST1.

**PHASOR BLAST WAVE PISTOL SERIES PLANS** Handheld, has large transducer and battery capacity with external controls. £6/set Ref F/PSP4.

**INFINITY TRANSMITTER PLANS** Telephone line grabber/room monitor. The ultimate in home/office security and safety! simple to use! Call your home or office phone, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 Ref F/TELEGRAB.


**BUG DETECTOR PLANS** is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome interference. Detects low, high and UHF frequencies. £5/set Ref F/BD1.

**ELECTROMAGNETIC GUN PLANS** Projects a metal object a considerable distance-requires adult supervision £5 ref F/EML2.

**ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND!** £5/set Ref F/EMA1.

**PARABOLIC DISH MICROPHONE PLANS** Listen to distant sounds and voices, open windows, sound sources in 'hard to get' or hostile premises. Uses satellite technology to gather distant sounds and focus them to our ultra sensitive electronics. Plans also show an optional wireless link system. £8/set ref F/PM5

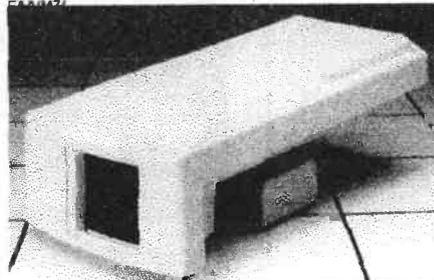**2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATOR PLANS** Operates on 9-12vdc, many possible experiments. £10 Ref F/AMZ1.



## COLOUR CCTV VIDEO CAMERAS,

BRAND NEW AND, CASED, FROM £99.  
Works with most modern video's, TV's, Composite monitors, video grabber cards etc

Pal, 1v P-P, composite, 75ohm, 1/3" CCD, 4mm F2.8, 500x582, 12vdc, mounting bracket, auto shutter, 100x50x180mm, 3 months warranty, 1 off price £119 ref XEF150, 10 or more £99 ea 100+ £89



Smallest Integrated Radar + Laser Detector

## SUPERWIDEBAND RADAR DETECTOR 360 deg COVERAGE

Detects both radar and laser, X, K, superwide KA bands. LED signal strength display Audio and visual alerts, Alert priority, Rear and front facing optical waveguides, Triplecheck verification, city mode, tutorial mode, dark mode, aux jack, volume control. These may be illegal to use in certain countries.

1.1"x2.7"x4.6"  
Superband £149 ref RD2

PLACE YOUR ORDER VIA OUR WEBSITE AT [BULL-ELECTRICAL.COM](http://BULL-ELECTRICAL.COM)

## BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.  
BN3 5QT. (ESTABLISHED 50 YEARS).


MAIL ORDER TERMS: CASH, PO OR CHEQUE WITH ORDER PLUS £3.50 P&P PLUS VAT.

24 HOUR SERVICE £5.00 PLUS VAT.

OVERSEAS ORDERS AT COST PLUS £3.50 (ACCESS, VISA, SWITC, AMERICAN EXPRESS)  
phone orders : 01273 203500

FAX 01273 323077

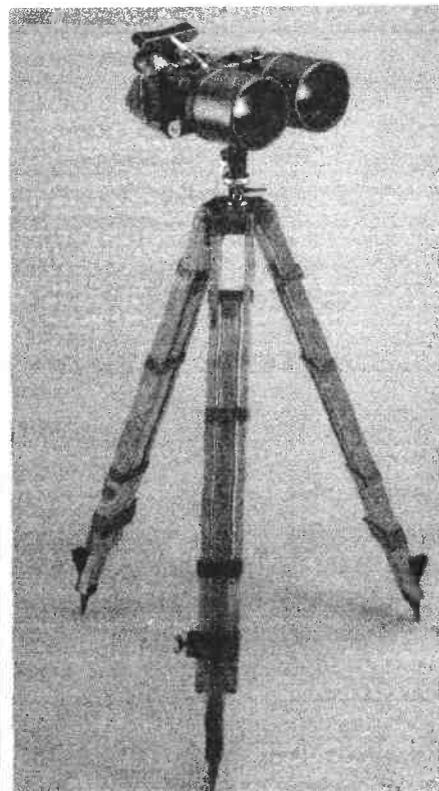E-mail [bull@pavilion.co.uk](mailto:bull@pavilion.co.uk)




## HELIOS PNB-2 RUSSIAN BORDER GUARD OBSERVATION BINOCULARS £1799

Intended for the medium to long range observation of air and ground targets and the determination of their angular co-ordinates. These giant binoculars are a tribute Russian optical ingenuity, with a performance that simply has to be seen to be believed. A large exit pupil diameter of 7.33mm provides exceptional light passing power, which when combined with its high

magnification of x15 allows the user to view over vast distances with delightfully bright, crisp, high resolution images. Robust and able in construction incorporating an uncomplicated yet thoughtfully designed mechanical layout ensuring ease of operation and quick precise targeting. These binoculars have a wide variety of applications and are suitable for use by coastguards, law enforcement organizations, customs, farmers etc.

Specifications  
x15 magnification, 110mm objective, 6 deg angle of view, Field at 100m=105m, focusing 10m-inf, fully coated precision ground optics, orange and neutral filters, rubber lens caps, rapid targetting hand grips, padded headrest, screw in silica gel cartridges, wooden tripod, operating temperatures -40 c to +50 c, weight 25kg, (15kg without tripod), supplied in wooden carrying case.  
Border guard binoculars £1799 ref PNB2

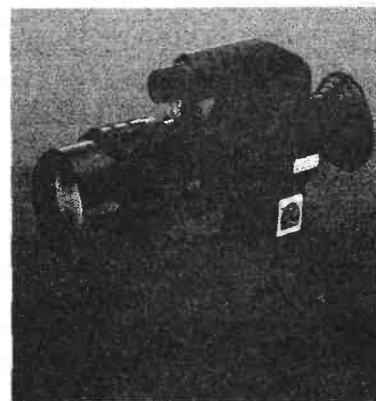

## TZS4 INFRARED NIGHT SIGHT

One of our top most selling night sights is this Russian TZS4. This sight enable you to see in very low light levels, or with the aid of the built in infra red illuminator- in total darkness. In 1/4 moonlight you would spot a man at 150m, in total darkness at 75m. Magnification 2.3x, 240x66x190mm, 0.9kg, focusing range 1.5m-infinity, M42 camera mount included, runs on 2xAA batteries, 100mm focal length, 8 deg illuminator divergence, 50hrs continuous (no illuminator) 10hrs with carrying case and strap.

TZS4 Nightsight £199 ref BAR61


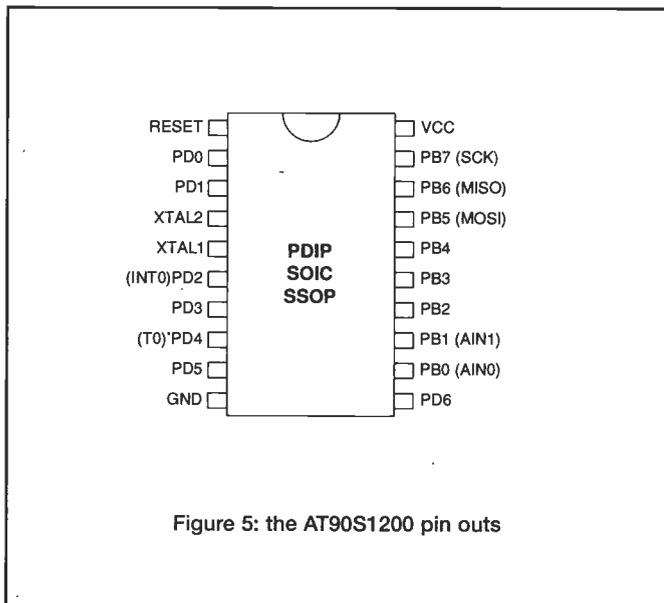


Figure 5: the AT90S1200 pin outs

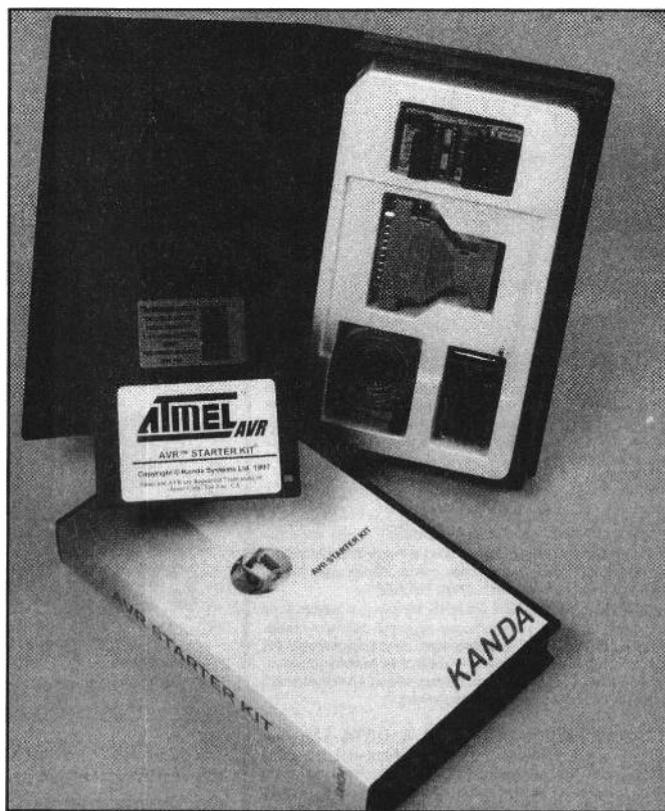

different approach, which curiously enough was pioneered by Sir Clive Sinclair many years ago in his X10 amplifiers. This is a completely digital amplifier. We know that inefficiencies occur when you need to bias a bipolar transistor to On. It sits eating up current even at low revs. However, if we use it at either end of its conduction curve, in other words when it is turned hard on (saturated) or hard off, then it is very efficient. This can be proved using the power theorem. If the current through the device is 0 (we'll assume a perfect transistor with no leakage current), then the power dissipated across the device is 0 ( $I^2 \times R$ ) similarly if the voltage across the device is 0 then again the power dissipated is 0 ( $V^2/R$ ). So if we could devise a system whereby the transistors can always be used only as switching devices, then we could achieve maximum efficiencies. To do this we use Pulse Width Modulation. In a nutshell, this means varying the mark (high) to space (low) ratio of a pulsed waveform, so that the mean power delivered to the load is based on the ratio between the 1s and the 0s. The more 1s, the higher the output. To achieve this we need to provide some form of storage device to integrate the mean power. In a fi-fi this is easy; the speaker is just a type of inductor and naturally acts as an integrator. In a digital system, we can use a filter with a long time constant, in other words a capacitor charged via a resistor.

So what use is it in a digital system? The answer is that we can use it for digital to analogue conversion. If we need a voltage output, or we need to control the speed of a motor, then we can use the PWM output.

### The relatives

At the time of writing there are three versions of the AVR in the family. The first off the line was the 1200, which is the one I have been discussing up to now. That was followed by the 8515, which has the same pin-out as the ubiquitous 51 series (see figure 5). Apart from all the features listed above, the 8515 has an asynchronous serial port (sometimes, wrongly, referred to as an RS232 port), a synchronous serial port, pulse width modulation, and the ability to use external data memory. This device was followed by another 20-pin device, the 2313, which has further program memory capability, PWM and an asynchronous serial port. Finally, there is an 8-pin device called the 2313, which is going to provide a bit of competition to the Microchip 1200 series. Further units, scheduled for early next year, include a part with 1 megabit of program memory and another with precision 10 bit A/D converters built in.

The outstanding feature of this device family is that it was designed around a high level C compiler. The C compiler manufacturer actually worked with the chip designers to create the chip, so that you can use C to write the code, instead of assembler, and the resulting code is fully optimised. So, unlike many processors, the compiled object code is very nearly as efficient as the code created by the native assembler. You also have access to the range of professional standard debugging tools that are, optionally, supplied by the makers of the C compiler, IAR Systems. Atmel have commissioned a special version of the compiler for less than half the normal price. Contact numbers follow.

AVR Starter kit available from Maplin and Rapid Electronics  
 AVR Training System (AVR Explorer) and a "Get Going with AVR" book are available from Maplin  
 AVR Devices available from Maplin, Rapid Electronics and Farnell

C Compilers available from Kanda Systems (demos available on request).

Programming software is available from Kanda's website [www.kanda-systems.com](http://www.kanda-systems.com)

Free development tools are available from Atmel's website [www.Atmel.com](http://www.Atmel.com)

Maplin: PO Box 3, Rayleigh, Essex SS6-8L. Tel 01702 554161.

Farnell Electronic Components: Canal Road, Leeds, LS12 2TU. Tel 0113 263 6311.

Rapid Electronics: 40 Heckworth Close, Severalls Industrial Park, Colchester, Essex CO4 4TB. Tel 01206 751166.


Kanda Systems: PO Box 2, Ystrad Meurig, Ceregigion, UK SY25 6DX. Tel 01974 282670.

Cover picture: Atmel's AT90S1200 is based on the AVR architecture, the world's first 8-bit RISC. The AT90S1200 combines an AVR core, 1KB of Flash memory and 64 bytes of eeprom on a monolithic 20-pin chip.

# PROTEUS


## Schematic Capture

NEW Version IV

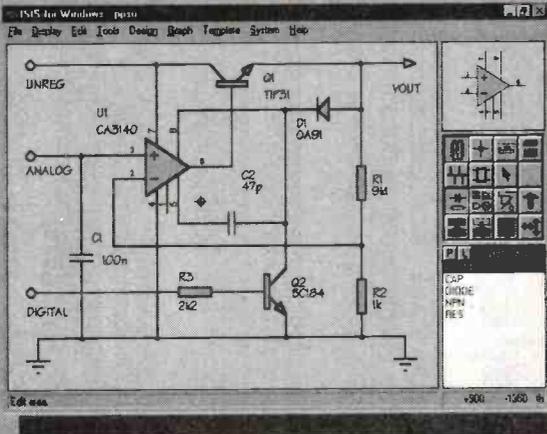

- Produces attractive schematics like you see in the magazines.
- Netlist, Parts List & ERC reports. ● Hierarchical Design. ● Full support for buses including bus pins. ● Extensive component/model libraries. ● Advanced Property Management.
- Seamless integration with simulation and PCB design.

## Simulation

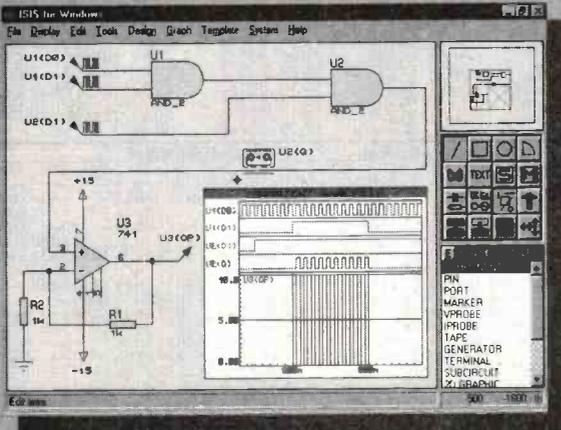

- Non-Linear & Linear Analogue Simulation. ● Event driven Digital Simulation with modelling language. ● Partitioned simulation of large designs with multiple analogue & digital sections. ● Graphs displayed directly on the schematic.

# The IV<sup>th</sup> Generation


## New Features

- Component Auto-Placer
- Pinswap/Gateswap Optimizer
- Background Regeneration of Power Planes
- Enhanced Autorouting with Tidy Pass
- Full Control of Schematic Appearance
- Extensive New Component Libraries

Available in 5 levels - prices from £295 to £1625 + VAT.  
Call now for further information & upgrade prices.

## PCB Design

NEW Version IV

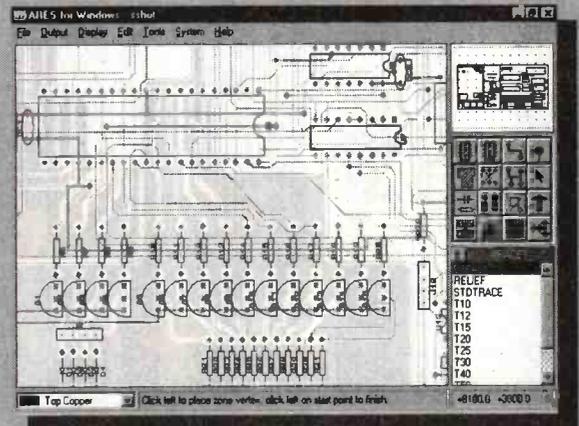

- Automatic Component Placement. ● Rip-Up & Retry Autorouter with tidy pass. ● Pinswap/Gateswap Optimizer & Backannotation. ● 32 bit high resolution database. ● Full DRC and Connectivity Checking. ● Shape based gridless power planes. ● Gerber and DXF Import capability.

**"PROTEUS**  
is particularly good

with its rip-up-and-retry **autorouter"**  
EWW January 1997

labcenter  
Electronics

Write, phone or fax for your free demo disk, or ask about our full evaluation kit.  
Tel: 01756 753440. Fax: 01756 752857. EMAIL: info@labcenter.co.uk  
53-55 Main St, Grassington, BD23 5AA. WWW: http://www.labcenter.co.uk

Fully interactive demo versions available for download from our WWW site.  
Call for educational, multi-user and dealer pricing - new dealers always wanted.  
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.



**Station Road, Cullercoats, Tyne & Wear, NE30 4PQ**



All Major Credit cards Accepted

Prices Exclude Vat @17.5%. Add £1.25 carriage & Vat to all orders. Cheques / Postal orders payable to ESR Electronic Components.

**4000 Series**

4000	£0.17	74HC00	£0.20	74LS37
4001	£0.18	74HC02	£0.21	74LS38
4002	£0.17	74HC03	£0.21	74LS40
4003	£0.17	74HC04	£0.17	74LS47
4007	£0.18	74HC08	£0.21	74LS51
4008	£0.23	74HC10	£0.16	74LS73
4009	£0.19	74HC12	£0.22	74LS74
4010	£0.23	74HC14	£0.20	74LS74
4011	£0.19	74HC20	£0.22	74LS76
4012	£0.16	74HC27	£0.18	74LS83
4013	£0.19	74HC30	£0.22	74LS85
4014	£0.20	74HC32	£0.20	74LS86
4015	£0.24	74HC42	£0.36	74LS90
4016	£0.30	74HC73	£0.40	74LS92
4017	£0.26	74HC74	£0.22	74LS93
4018	£0.27	74HC75	£0.40	74LS107
4019	£0.48	74HC76	£0.20	74LS109
4020	£0.31	74HC85	£0.24	74LS131
4021	£0.31	74HC86	£0.22	74LS114
4022	£0.32	74HC107	£0.40	74LS122
4023	£0.16	74HC123	£0.33	74LS123
4024	£0.32	74HC125	£0.46	74LS125
4025	£0.15	74HC126	£0.37	74LS126
4026	£0.78	74HC132	£0.46	74LS126
4027	£0.25	74HC133	£0.29	74LS132
4028	£0.34	74HC138	£0.25	74LS133
4029	£0.40	74HC139	£0.31	74LS136
4030	£0.70	74HC151	£0.33	74LS138
4031	£0.70	74HC153	£0.27	74LS139
4034	£1.24	74HC154	£0.85	74LS145
4035	£0.10	74HC155	£0.40	74LS147
4040	£0.38	74HC158	£0.23	74LS148
4041	£0.31	74HC158	£0.23	74LS151
4042	£0.22	74HC161	£0.28	74LS153
4043	£0.28	74HC162	£0.45	74LS154
4044	£0.35	74HC163	£0.27	74LS155
4045	£0.52	74HC164	£0.35	74LS156
4047	£0.44	74HC165	£0.35	74LS158
4048	£0.28	74HC165	£0.35	74LS158
4049	£0.22	74HC173	£0.38	74LS160
4050	£0.26	74HC174	£0.27	74LS161
4051	£0.38	74HC175	£0.35	74LS162
4052	£0.32	74HC192	£0.72	74LS163
4053	£0.40	74HC195	£0.32	74LS164
4054	£0.56	74HC240	£0.37	74LS165
4055	£0.34	74HC241	£0.37	74LS170
4060	£0.44	74HC243	£0.48	74LS173
4063	£0.29	74HC244	£0.42	74LS174
4066	£0.22	74HC245	£0.46	74LS175
4067	£0.20	74HC251	£0.25	74LS190
4068	£0.16	74HC253	£0.25	74LS191
4069	£0.20	74HC257	£0.25	74LS192
4070	£0.25	74HC259	£0.57	74LS193
4071	£0.23	74HC273	£0.35	74LS195
4072	£0.17	74HC299	£0.64	74LS196
4073	£0.17	74HC356	£0.45	74LS197
4075	£0.30	74HC365	£0.34	74LS211
4076	£0.77	74HC367	£0.25	74LS220
4077	£0.28	74HC368	£0.25	74LS241
4078	£0.20	74HC373	£0.35	74LS242
4081	£0.22	74HC374	£0.40	74LS243
4082	£0.21	74HC390	£0.52	74LS244
4085	£0.28	74HC393	£0.38	74LS245
4086	£0.26	74HC423	£0.37	74LS247
4089	£0.55	74HC553	£0.42	74LS251
4093	£0.23	74HC563	£0.56	74LS257
4094	£0.31	74HC564	£0.48	74LS258
4095	£0.26	74HC565	£0.10	74LS259
4097	£1.20	74HC573	£0.38	74LS273
4098	£0.48	74HC574	£0.45	74LS279
4099	£0.38	74HC640	£0.73	74LS365
4502	£0.38	74HC688	£0.64	74LS367
4503	£0.40	74HC4002	£0.31	74LS368
4508	£1.40	74HC4017	£0.64	74LS373
4510	£0.36	74HC4020	£0.34	74LS374
4511	£0.38	74HC4040	£0.45	74LS375
4512	£0.32	74HC4049	£0.31	74LS377
4514	£0.99	74HC4050	£0.25	74LS378
4515	£0.99	74HC4051	£0.25	74LS390
4516	£0.44	74HC4065	£0.42	74LS393
4518	£0.44	74HC4075	£0.27	74LS395
4520	£0.41	74HC4078	£0.32	74LS399
4521	£0.62	74HC4511	£0.34	74LS670
4526	£0.40	74HC4514	£0.84	
4527	£0.40	74HC4538	£0.41	
4529	£0.40	74HC4543	£0.90	

**74 Series**

7407	£0.40	74LS32	£0.21	74LS32
7408	£0.40	74LS32	£0.21	74LS32
7409	£0.40	74LS32	£0.21	74LS32
7410	£0.40	74LS32	£0.21	74LS32
7411	£0.40	74LS32	£0.21	74LS32
7412	£0.40	74LS32	£0.21	74LS32
7413	£0.40	74LS32	£0.21	74LS32
7414	£0.40	74LS32	£0.21	74LS32
7415	£0.40	74LS32	£0.21	74LS32
7416	£0.40	74LS32	£0.21	74LS32
7417	£0.40	74LS32	£0.21	74LS32
7418	£0.40	74LS32	£0.21	74LS32
7419	£0.40	74LS32	£0.21	74LS32
7420	£0.40	74LS32	£0.21	74LS32
7421	£0.40	74LS32	£0.21	74LS32
7422	£0.40	74LS32	£0.21	74LS32
7423	£0.40	74LS32	£0.21	74LS32
7424	£0.40	74LS32	£0.21	74LS32
7425	£0.40	74LS32	£0.21	74LS32
7426	£0.40	74LS32	£0.21	74LS32
7427	£0.40	74LS32	£0.21	74LS32
7428	£0.40	74LS32	£0.21	74LS32
7429	£0.40	74LS32	£0.21	74LS32
7430	£0.40	74LS32	£0.21	74LS32
7431	£0.40	74LS32	£0.21	74LS32
7432	£0.40	74LS32	£0.21	74LS32
7433	£0.40	74LS32	£0.21	74LS32
7434	£0.40	74LS32	£0.21	74LS32
7435	£0.40	74LS32	£0.21	74LS32
7436	£0.40	74LS32	£0.21	74LS32
7437	£0.40	74LS32	£0.21	74LS32
7438	£0.40	74LS32	£0.21	74LS32
7439	£0.40	74LS32	£0.21	74LS32
7440	£0.40	74LS32	£0.21	74LS32
7441	£0.40	74LS32	£0.21	74LS32
7442	£0.40	74LS32	£0.21	74LS32
7443	£0.40	74LS32	£0.21	74LS32
7444	£0.40	74LS32	£0.21	74LS32
7445	£0.40	74LS32	£0.21	74LS32
7446	£0.40	74LS32	£0.21	74LS32
7447	£0.40	74LS32	£0.21	74LS32
7448	£0.40	74LS32	£0.21	74LS32
7449	£0.40	74LS32	£0.21	74LS32
7450	£0.40	74LS32	£0.21	74LS32

**See Next / Last Months Ad. for COMPONENT ACCESSORIES**

ADM221AH	£3.55	TL061TCP	£0.35
ADM232AA	£3.55	TL062CP	£0.60
ADM485JN	£2.97	TL064CN	£0.72
ADM690AN	£5.13	TL071CP	£0.39
ADM691AN	£6.48	TL072CP	£0.38
ADM695AN	£6.48	TL078CN	£0.48
ADM699AN	£3.58	TL081CP	£0.33
CA741CE	£0.26	TL082CP	£0.54
CA747CE	£0.39	TL084CN	£0.50
CA304A	£0.37	TL084CN	£0.50
CA3059	£1.33	TL7705ACP	£1.46
CA3080E	£0.73	TL271T	£0.54
CA3130E	£0.87	TL272T	£0.88
CA3140E	£0.49	TMP01FP	£5.60
CA3189E	£1.22	ULN2003	£0.52
CA3240E	£1.12	ULN2004A	£0.48
DG211CJ	£1.55	ULN2803	£0.90
DG212CJ	£1.55	ULN2804A	£1.64
DG411DJ	£3.11	XR2206	£5.37

**EPROM's**

ICL7106	£2.95	2716	£4.74
ICL7611DCP	£1.06	2732	£4.84
ICL7621	£1.70	2764-20	£4.26
ICL7660SCP	£1.92	2764-25	£3.70
ICL8038	£4.89	2764-25	£3.70
ICM7555	£0.32	27C128-15	£3.02
ICM7556	£0.98	27C128-15	£3.02
L165V	£2.72	27C256-20	£4.85
L272M	£1.86	27C256-20	£4.85
L293E	£4.35	27C512-2	£3.30
L297	£6.39	27C1001-20	£3.02
L298	£6.39	27C4001-12069.7E	
L6219	£4.48		
LF347N	£0.46		
LF351N	£0.43		
LF353N	£0.40		
LF356	£0.84		
LM3001A	£0.25		
LM3008N	£0.58		
LM3011N-B	£0.29		
LM318	£0.98		
LM319N-14	£0.93		
LM324	£0.24		
LM335Z	£1.52		
LM339N	£0.24		
LM348N	£0.31		
LM358N	£0.27		
LM380N	£0.88		
LM381N	£2.64		
LM386	£0.79		
LM392N	£0.79		
LM393N	£0.36		
LM709T	£0.79		
LM748CN-8	£0.37		
LM1458	£0.30		
LM1881	£3.92		
LM2917NB	£3.13		
LM3900N	£0.72		
LM3909N	£0.72		
LM3914	£2.16		
LM3915	£2.70		
LM3960N	£1.66		
LMC602CN	£1.55		
LMC6032IN	£1.55		
LP111N	£0.74		
LP324N	£0.67		
LP339N	£0.93		
MAX202CPE	£2.97		
MAX208CN	£6.99		
MAX220CPE	£5.06		
MAX222CPE	£1.61		
MAX232CPE	£1.61		
MAX483CP	£3.13		
MAX485CP	£2.58		
MAX631ACPE	£4.99		
MAX635ACPE	£4.99		
MAX1232CP	£2.96		
MC1488	£0.39		
MC1489	£0.39		
MC3302	£0.56		
MC3303	£0.66		
MC4558B	£0.40		
MV601DP	£2.97		
NE521N	£6.39		
NE555N	£0.23		
NE566N	£0.36		
NE565	£1.84		
NE567N	£0.39		
NE572	£2.47		
NE582N	£0.45		
NE5532N	£0.45		
NE5534N	£0.64		
NE5539N	£4.35		
NE5560N	£2.31		
OP07CN	£1.42		
OP27CN	£2.90		
OP77GP	£1.99		
OP90GP	£3.11		
OP97FP	£2.43		
OP113CP	£3.44		
OP177CP	£2.09		
OP177GP	£1.89		
OP200CP	£5.60		
OP213FP	£5.20		
OP275CP	£2.57		
OP282CP	£2.27		
OP283CP	£5.20		
OP290CP	£5.40		
OP297CP	£11.81		
OP495CP	£8.79		
RC4136	£1.00		
SAA1027	£4.49		
SG3524N	£0.96		
SG3543	£6.88		
SL486	£2.88		
SSM2017P	£3.38		
SSM2131P	£4.21		
SSM2141P	£4.19		
SSM2142P	£5.78		
SSM2143P	£6.78		
TBA1205	£0.91		
TBA800	£0.70		
TBA810S	£0.64		
TBA820M	£0.40		
TDA1170S	£2.48		
TDA2002	£1.04		
TDA2004	£1.18		
TDA2009	£1.18		
TDA2050V	£1.18		
TDA			

# AA Cell Eliminator

**Time to round up your AA-cell dependent appliances and save costs by running them from the mains. By Terry Balbirnie.**

**L**ook around the house and you are bound to find several devices powered from two, three or four AA cells. All those radios, games, personal stereos, photographic equipment and computer add-ons that you haven't already thought of an energy-saving strategy for. They build up all the time, especially after Christmas. Many of these things need less than 300mA, which puts them well within the scope of a mains-powered eliminator like this one. Mains electricity is about three thousand times cheaper than the equivalent power from alkaline "AA" cells. Where there is a mains supply, it makes sense to use it, especially if you have anything that you use for long stretches of time.

Certain pieces of equipment, such as photoflash guns, require a large current for a relatively short time. My photoflash unit, for example, needs about 3A at the beginning of its operating cycle. This kind of item is *not* suitable to use with this battery eliminator.

## Good substitute

Although this circuit was originally designed as a substitute for AA cells, there is no reason why it could not replace other batteries. In any event, you will need to look at the way in which the output will be connected to the terminals inside the battery compartment. You must also check that the equipment needs a maximum of 300 milliamperes. For AA cells, the connections will possibly be made using a pair of dummy cells. More will be said about this later. Make sure that there is enough space inside the battery compartment for the wires. Also, check that it will be possible to file a small section out of the cover to allow the wires to pass through. A number of appliances have a separate cell holder inside the battery compartment to which connections are made via a PP3-type battery snap. If this is the case, the cell holder may be discarded. The eliminator output can then be linked to

the existing connector using a similar battery snap.

This eliminator provides the correct output voltage via the value of a single "program resistor" on the circuit panel. However, to make sure that the voltage is correct, you will need to use a voltmeter at the end of construction. **The output voltage must not be taken on trust.** The current limit (that is, the maximum current which the unit can deliver) is set by another resistor. This provides protection in the event of a short circuit or overload, and takes the place of a fuse in the output. In fact, such a fuse would be undesirable because of the rather large voltage drop across it.

**This eliminator must not be used by children. Because it receives power from the mains, it must be regarded as potentially dangerous. This is an "adults only" circuit. For the same reason, it must only be used in a dry indoor location.**

## How it works

The circuit is shown in **figure 1**. The mains is applied to transformer T1 primary via the fuse, FS1. The secondary provides an ac output of about 12V (with both 6V windings


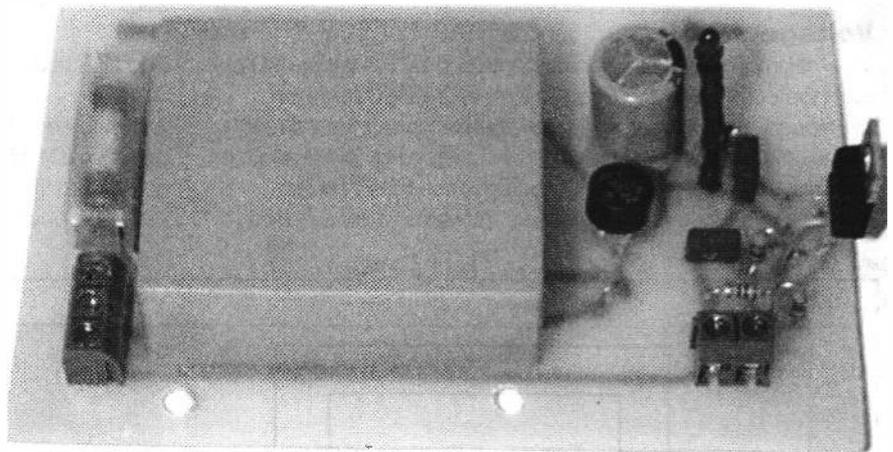


Figure 1: the circuit of the AA Cell Eliminator

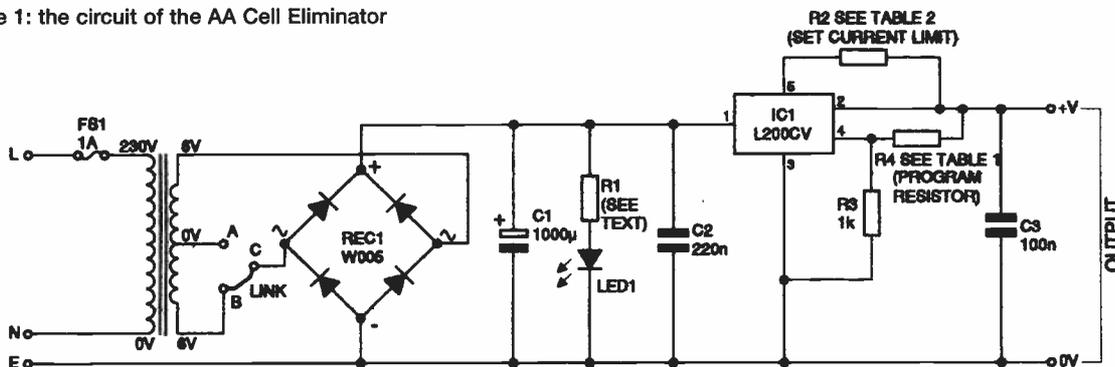

connected in series, that is, by connecting C to B as shown) or 6V (with the link connecting C to A instead - this uses only one secondary section). For equipment designed for two cells, the latter is used. For three or four cells, both secondaries will be needed. The mains earth wire is connected to the case and also runs through to the negative (0V) output terminal.

The transformer output is connected to bridge rectifier REC1 and smoothed by C1. The result is an on-load dc supply of some 7V (if one secondary has been selected) or 15V (for two). LED1 glows to show that the circuit is on. The value of series resistor R1 will be chosen according to whether the higher or lower secondary voltage has been selected. This will enable it to draw the correct operating current.


The positive rail is connected to the input (pin 1) of voltage and current regulator IC1. The output is provided at pin 5. Current then flows through R2 to the positive output. The output voltage depends on the values of R3 and R4. These should be of the 1 percent tolerance type so that the voltage may be accurately predicted. Since R3 is fixed in value, the output is determined by R4 (the program resistor) alone. The value of this is chosen from **Table 1** according to which voltage output is required. For two cells this will be 3V, for three cells, 4.5V and for four, 6V. In fact, the voltages as calculated are slightly on the low side for safety. Capacitors C2 and C3 are necessary for stable operation of the regulator.

**Table 1**

For nominal output	Use R4 value (0.1 percent)
3V	33R
4.5V	560R
6V	1k1
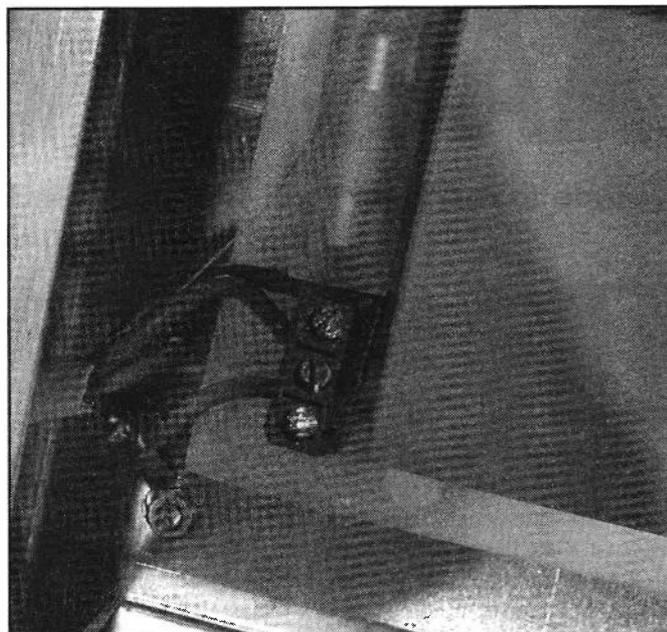
### Voltage sensing

The maximum output current is controlled by the value of R2. With the current flowing through this, a certain voltage is developed across it according to Ohm's Law. As the current increases so does the voltage. This is sensed by pin 2 and if it reaches 0.4V, the output is turned down so that it never exceeds this figure. **Table 2** shows the value of R2 required to



produce various current limits up to the maximum of 300mA. Note that these are not accurately determined and may only be regarded as nominal values.

**Table 2**

For current limit (mA)	Use R2 value (ohms)
50	8.2
100	3.9
150	2.7
200	1.8
250	1.5
300	1.2

See also text.

The difference between the input and output voltage appears between IC1 pins 1 and 5 (less the small voltage developed across R2). This, multiplied by the current flowing in the circuit gives the power which must be dissipated by the device. This

is converted into heat, and measures must be taken to release this into the air without causing overheating. The maximum normal (non-fault) power dissipation will occur when the highest allowed current (300mA) is drawn and the circuit is configured for a 6V output. If 15V appears at pin 1, there will be a voltage difference of some 9V which, when multiplied by 300mA, will result in a power a little under 3W. This will produce a small amount of heat which is easily dissipated by the aluminium box in which the circuit is housed (and to which IC1 is bolted). Many pieces of equipment require less than 300mA and the heat developed will be correspondingly less. Under

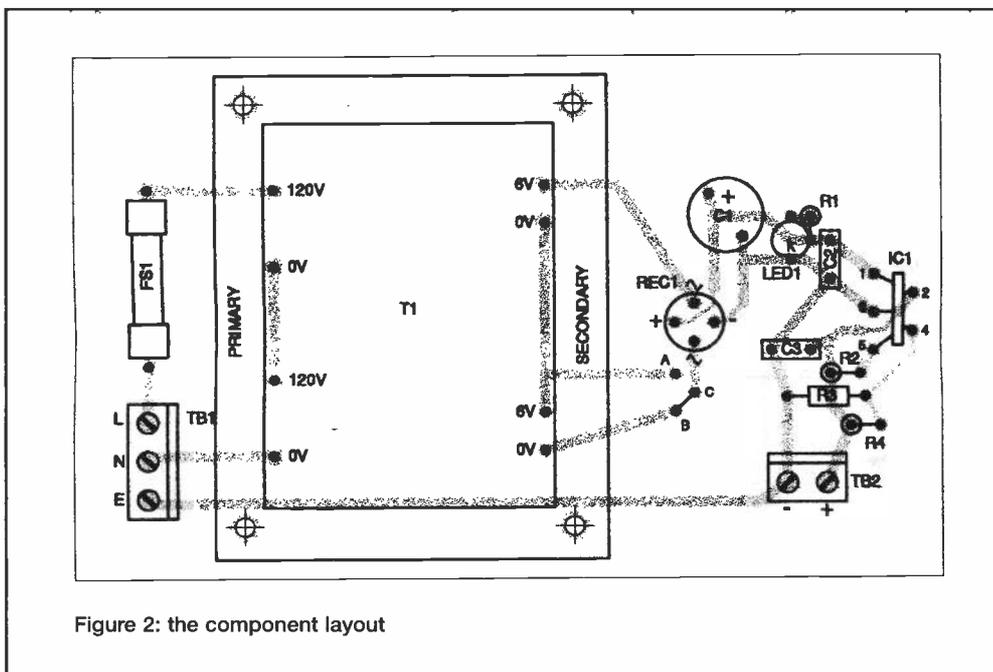


Figure 2: the component layout

short-circuit conditions, the power will be greater because the full 15V will now appear across the ic. With a set limit of 300mA, this will be in the region of 5W. It will be safe, but the box may become quite warm especially if the short circuit is applied for a long period of time.

## Construction

All soldered connections must be made with care. **In some circumstances where there is a faulty connection, the output voltage could rise to that at IC1 pin 1 causing damage to the equipment connected to the unit.**

The PCB design, as given, connects both 120V transformer primary windings in series for use with European (nominally 230V) supplies. Readers in the USA should make the following modifications: Cut away a section of track linking the Neutral (N) terminal on TB1 to the lower 0V transformer pin. Hard wire the lower transformer 120V pin to TB1 Neutral instead.

This project must be built in an earthed metal case. This provides sufficient mechanical strength and also acts as a heat sink for the ic. Drill holes for entry of the mains lead and for the output wires. Make these large enough for the strain relief bushes which are needed to hold them securely and prevent them from pulling free. Drill a small hole in the base close to TB1 position for a solder tag.

Drill the four mounting holes in the PCB. Four are necessary because the transformer is a heavy component and needs plenty of support. Mount the transformer, terminal blocks TB1 and TB2 also the fuseholder as shown in the photographs. Solder the link wire in position. This connects the common position (C) with either A (for 3V or 4.5V output) or B (for 6V output). Solder R1 in place - if one transformer secondary is used, the correct value is 330R; if both are used, it should be 820R. Refer to Table 1, choose the correct program resistor (R4) and solder it in position. Refer to Table 2 and select the resistor required for R2 according to the maximum current required. Remember, a personal stereo draws more current when winding and re-winding the tape than when it is playing, so this must be allowed for. It is not prudent to set a higher current limit than is actually required.

Solder all remaining components taking care to mount the bridge rectifier and electrolytic capacitor C1 with the correct polarity. Solder short pieces of wire to the LED position and solder the LED to these observing the polarity. It should be arranged for the top of this component to take up a position about 2mm higher than that of the lid of the box when this is in position. It is important to sleeve the LED wires (including the extension) along their entire length so that they cannot touch one another or anything else. Heat-shrinkable sleeving is best

for the job. Solder the ic in position. Its metal backing is towards the right-hand edge of the PCB and should overhang it slightly. The pins will need to be bent slightly; this must be done with care, as they break off easily. Insert the fuse in the holder and fit the insulating cover.

Hold the PCB in position on the base of the box with IC1 pressing against the side and mark through the mounting holes. Drill these and attach the PCB using 8-mm length minimum plastic stand-off insulators on the bolt shanks. Check carefully that all the soldered connections on the underside of the PCB remain at least 5 millimetres clear of the metal. Mark the hole in IC1 tab, remove the PCB again and drill this hole. Replace the PCB and bolt the ic firmly to the side of the box using a metal nut and bolt - heat transfer compound is not necessary, because the ic is being used well below its operating limit. The metal tab is connected internally to pin 3 which, in turn, becomes the negative (0V) output. Thus, the tab may make electrical contact with the case because this is at the same potential. Take care to ensure that pins of IC1 are not put under any strain, because they break easily. Measure the position of the LED and drill a small hole in the lid of the box so that it will protrude through it when the case is assembled. Make any adjustments as necessary. Attach the solder tag securely. Fit self-adhesive plastic feet to the bottom of the case to protect the work surface.

## Testing

**Note: For safety reasons, the lid of the case must be in position whenever the unit is plugged into the mains.**

Make up an input lead using light-duty three-core mains-type wire. Fit a plug to one end and, if it is of the UK type, insert a 2A or 3A fuse. Pass the wire through the hole drilled for it and secure it using one of the strain relief bushes leaving a little slack. Make certain that the wire is tightly held. Connect the Live and Neutral wires to TB1 as shown in **figure 3**. Twist the end of the earth wire to a further short piece of mains earth wire. Hook the wires through the hole in the solder tag and solder them securely. Attach the short piece of earth wire to TB1 as shown. **Make certain that the mains earth wires are securely attached to the solder tag.** Make up an output wire. This should be kept as short as practicable to minimise voltage drop. This is especially important if a high current is being drawn. If a long lead is essential, use thicker wire. Secure this with the second strain relief bush and connect the wires to TB2. Note which colour is the positive. Just leave the other ends bare for the moment. Replace the lid of the case. Connect a voltmeter to the output and plug in the unit. The


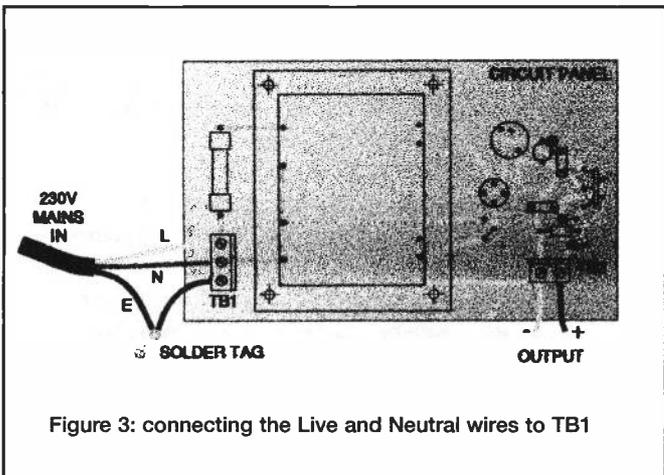


Figure 3: connecting the Live and Neutral wires to TB1

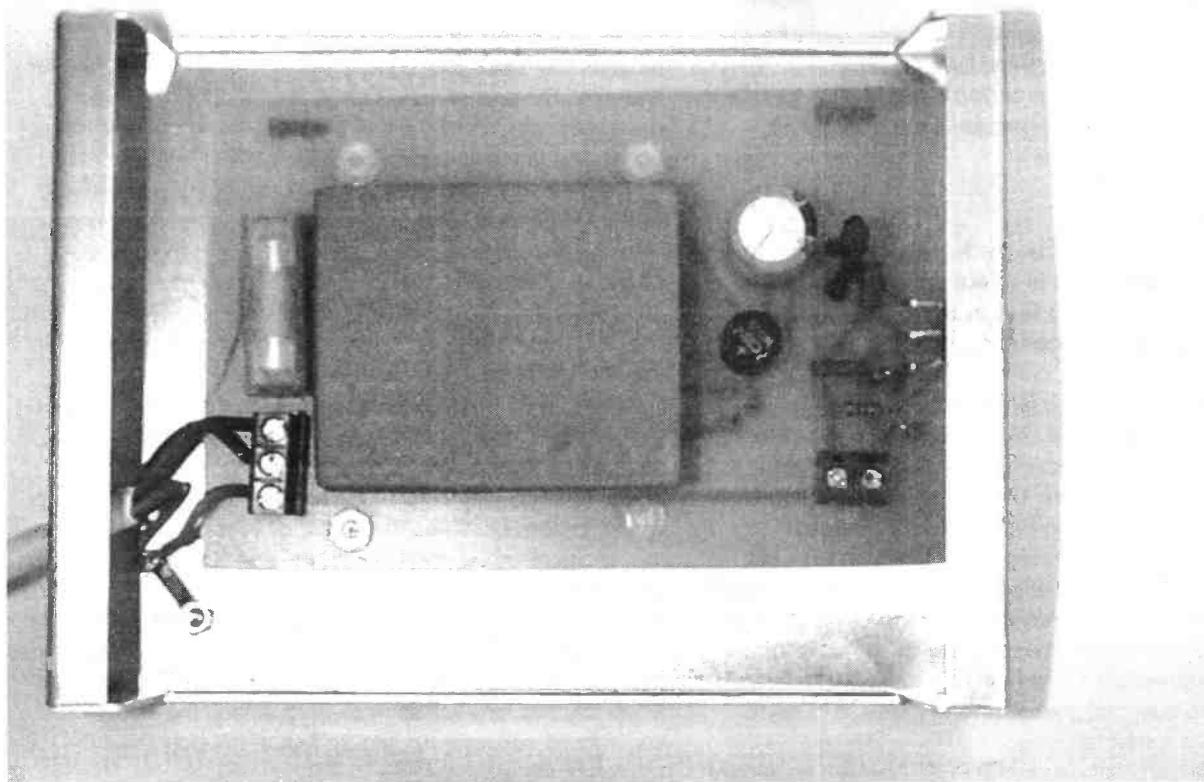



LED should glow and the voltmeter reading should be slightly below the nominal voltage (say, 95 percent of it). As a guide, these are the actual off-load voltages given by the prototype: 2.81V (for 3V), 4.25V (for 4.5V), 5.71V (for 6V). The voltage will fall a little according to the current drawn but it will still operate the equipment correctly. If it is found that 300mA is needed and this cannot be obtained, reduce the value of R2 slightly. In the unlikely event of the voltage being higher than the correct value, reduce the value of R4.

### Finishing off

If all is well, arrangements can be made to connect the output lead to the battery connector in the appliance. However this is done, make absolutely certain that the wires are applied with the correct polarity. **Some pieces of equipment do not have an internal diode which protects them against incorrect connection. Check and double check this point before connecting the wires and switching on.**

The dummy AA cells referred to earlier consist of a plastic body with the ends linked by a thin metal strip. Depending on the particular arrangements, it may not always be necessary to cut through the strips. However, it will be safer if you do. Remove a small section of strip from each "cell" so that the ends cannot re-touch. The positive wire is soldered to the positive piece of link wire on one "cell" and the negative wire to the negative on the other. If the equipment uses three or four cells, it will be necessary to find which one makes the positive connection and which the negative. Only two dummy cells will normally be needed. However, some equipment relies on the mechanical support of all the cells to make a reliable connection, so more dummy units may be needed depending on the use. Careful inspection will reveal to which terminals the wires from the circuit panel inside are connected.

**Due to safety regulations, this circuit must not be used to operate a battery-type electric razor in the bathroom.**

After a long period of use, the case will become warm, especially if the maximum current is drawn.

## PARTS LIST for the Cell Eliminator

### Resistors

All resistors 0.6W 1 percent

R1	820R (6V or 4.5V output) 330R (3V output)
R2	Current limit resistor - see Table 2
R3	1k
R4	Program resistor - see Table 1

### Capacitors



C1	1000u 25V PCB electrolytic
C2	220n 5-mm pin spacing
C3	100n 5-mm pin spacing

### Semiconductors

IC1	L200CV
REC1	W005 bridge rectifier
LED1	3-mm LED


### Miscellaneous

T1	Fully encapsulated PCB mains transformer with twin 6V secondaries rated at 4VA.
FS1	20mm chassis fuseholder with cover and 1A ceramic mains type fuse
TB1	Three sections of PCB-mounting screw terminal block - 5-mm pin spacing
TB2	Two sections of PCB-mounting screw terminal block - 5-mm pin spacing
	PCB materials; solder tag; aluminium box for project. Possible dummy AA cells - see text. Dummy AA cells are available from Maplin, as are the other components used in this project.

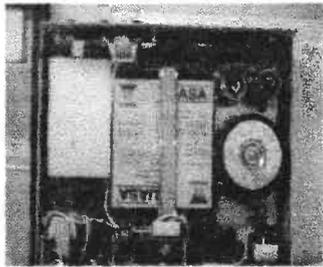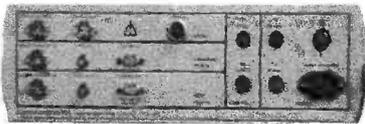

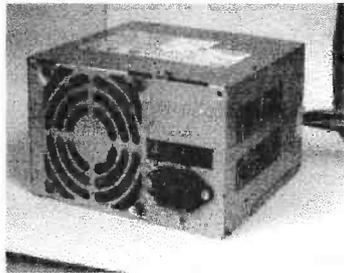**SALE PRICE £9.95**

**VIDEO PROCESSOR UNITS?/6v 10AH BATTS/24V 8A TX** Not too sure what the function of these units is but they certainly make good strippers! Measures 390X320X120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear. Inside 2 x 6v 10AH sealed lead acid batts, pcb's and a 8A? 24v toroidal transformer (mains in), sold as seen, may have one or two broken knobs etc due to poor storage. £9.95 ref VP2X




**Dell switched mode psu  
12v 15amp £9.95**

140x 150 x 90mm, fully cased with built in fan, +12 @ 13A, +5 @ 15A IEC power inlet, flylead output. £9.95 ref DEL2



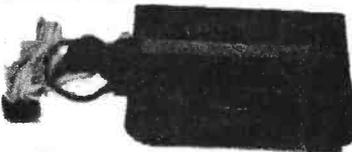UK made energy saving device that can give you a 15% saving on the running costs of fridges etc. Suitable for mains appliances fitted with a motor of up to 2A rating. We have tried the device on other things like soldering irons, conventional bulbs and still achieved a saving. One off price is £9 ref LOT71 Pack of 10 is £69 ref LOT72 Pack of 20 is £119 ref LOT73




**SALE PRICE £10**

These units must be cleared at the absurd price of just £10!! you get loads of leads, an infra red remote keyboard and receiver, a standard uhf modulator, a standard bt approved modem 1200/75 and loads of chips, resistors, capacitors etc etc all for just £10 ref bar33




**Switched mode  
psu special offer  
£2.99**

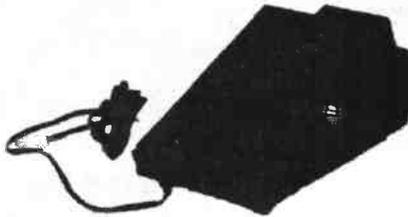Brand new psu's giving 5v at 4.4Amps. Originally made for the Archimedes but obviously have many other uses. Fitted on/off switch and fly lead. 150 x 100 x 42mm. £2.99 ref ARCH1X



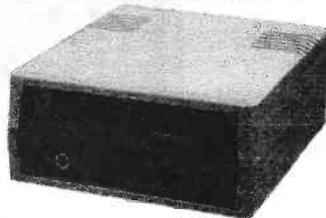**SALE PRICE £2.50**

Customer returns, domestic telephone coin boxes, used to convert ordinary phones in to pay phones. ref CBT1X



**The ultimate enclosure for  
your projects must be one of  
these!**

Well made ABS screw together beige case measuring 120 x 150 x 50mm. Already fitted with rubber feet and front mounted LED. Inside is a pcb fitted with other bits and pieces you may find useful. Sold either as a pack of five for £10 ref MD1 Or as a pack of 20 for £19.95 ref MD2

**Order via our web site at  
www.bull-electrical.com**

**SOLAR PANELS**

3' x 1' Amorphous silicon, 7 watt 12-14v  
output. Unframed. Ref SOLX  
**SALE PRICE 4 for £59**

**PC KEYBOARDS**

**sale price just £2.99**

Standard ps2 type connector, 104 keys. ref  
PCX



**Compaq  
244 watt pc power supplies  
buy 2 for £16**


Ex equipment but in full working order direct from one of the top manufacturers. 145 x 175 x 85mm, fitted fan and IEC inlet, switch on flylead. Outputs are 3.3vdc, +5vdc, -5vdc, +12vdc, -12vdc. You may need to change the mother board connector so we have included another one with the power supply to help. £16 for 2 ref COM2

**BULL ELECTRICAL**

250 PORTLAND ROAD, HOVE, SUSSEX.  
BN3 5QT. (ESTABLISHED 50 YEARS).  
MAIL ORDER TERMS: CASH, PO OR CHEQUE  
WITH ORDER PLUS £3.50 P&P PLUS VAT.  
24 HOUR SERVICE £5.00 PLUS VAT.  
OVERSEAS ORDERS AT COST PLUS £3.50  
(ACCESS, VISA, SWITCH, AMERICAN EXPRESS)  
**phone orders : 01273 203500**

FAX 01273 323077

**E-mail bull@pavilion.co.uk**

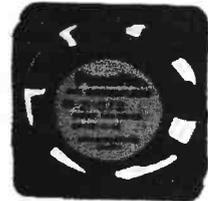

**12V FANS, EX EQUIPMENT  
COMPLETE WITH METAL CASES  
PACK OF 10 FOR £9.95**




**RCB UNITS £2.99**

This in line miniature earth leakage unit instantly shut off the mains supply in the event of any current flowing between live and earth thus preventing a potentially lethal shock. IEC plug one end, socket the other, fitted in seconds, reset button. The ultimate safety aid when working on electronic equipment, computers etc. As these units are fitted with an in-line IEC plug on one end and socket on the other than could even be used to extend standard IEC computer leads.

**Complete accounts system  
for your PC for just £9.95**


Unlimited companies, general ledger, multiple cash books, debtors and creditors, stock, invoicing, purchasing, budgets, report writer, calculator, wordprocessor, automated backups, on line help, windowing, networkable up to 10 workstations. Free telephone support for 30 days from MAP computer products 01616788413 all for the bargain price of just £9.95! worth it for the 200 page Pastel manual alone! ref SA12 3.5" disk version only. £9.95 ref PAS2

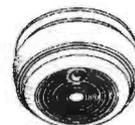

**MAINS SMOKE ALARMS (GENT)  
NEW AND BOXED £4.99 ref SMKX**

**BBC selector videocrypt 's'  
tv tuner with smart card  
sale price £9.95**


Interesting new item in this week is this Selector. Originally made for the BBC to send encrypted video films to your VCR at night time. The project seems to have failed. Very complex units consisting of a smart card slot in the front plus several switches and an IR receiver. Fully cased and measuring 230 x 430 x 90mm, new and boxed. On the back of the unit is a smart socket plus a UHF input and output. A channel tuning control numbered 28 to 40 and an IR socket. Inside is a comprehensive tuner section, smart card reader mechanism and control electronics plus a power supply section. These units are sold as strippers but we imagine you could use one to convert a monitor into a TV or maybe use the videocrypt side of things for something else. Supplied complete with manual and mains lead. Clearance price just £9.95 ref BBC1X.

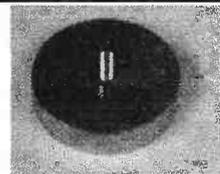


**Introducing our mega magnet  
that lifts 33 kilo's!**

Just in this week are these incredible Neodymium magnets that will lift an incredible 33 kilo's! Each magnet has a threaded bolt protruding from the rear for easy fixing. 32mm diameter. £15 ref MAG33


# Electronic CAD

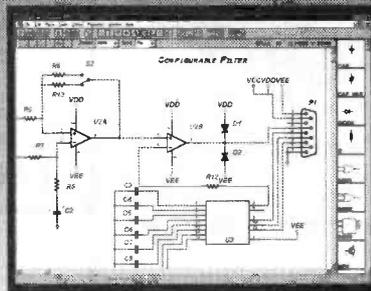

**WinDraft**  
Schematics

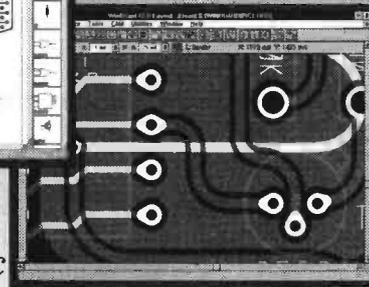

**WinBoard**  
PCB Layout

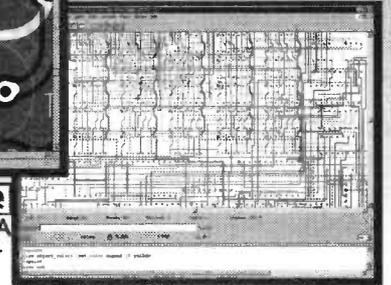

**Cadence**  
**SPECCTRA**  
Autorouter

*The complete, powerful schematic and PCB layout tools for Windows.*

① Design your schematic with WinDraft...

- Choose from over 10,000 parts in WinDraft's complete library of components.
- All the utilities you need are included in the package from an Electrical Rules Checker to netlist output to printing and plotting outputs.
- Cut and Paste into other Windows applications such as Microsoft Word. Makes it easy to document your projects!

② Create the artwork for the PCB with WinBoard...

- Quickly route boards on up to 16 layers.
- Use SMD or through-hole components — or mix them for maximum flexibility.
- Unique pad-stack editor can create pads of virtually any size or shape.
- Rotate components in 0.01° increments.

③ Create a Gerber photoplot, NC Drill, pick and place, and other manufacturing outputs!

**Tel 0181 926 1161**

The PC Solution, 2a High Road Leyton, London, E15 2BP. Fax 0181 926 1160 <http://www.thepcsol.demon.co.uk>

## HOW DOES YOUR EQUIPMENT MEASURE UP? AT STEWART OF READING THERE'S ALWAYS 'SCOPE' FOR IMPROVEMENT!



**PHILIPS PM3217** (This is a Proper Scope)  
Dual Trace 50MHz Delay Sweep Incl 2 Probes £400



**HC3502**  
Dual Trace 20MHz 5mV/20V/Div, 0.2µSec/0.5Sec/Div, X-Y, X5 Magnifier, TV Sync etc  
Hardly used £150 Un-Used £200

**THE CLASSIC TEKTRONIX 400 SERIES**



468 Digital Storage Dual Trace 100MHz Delay  
466 Analogue Storage Dual Trace 100MHz Delay  
475 Dual Trace 200MHz Delay Sweep  
465 Dual Trace 100MHz Delay Sweep

- PHILIPS PM3296A Dual Trace 400MHz Dual TB Delay Cursors IEEE £1750
- FLUKE PM3082 2+2Ch 100MHz Delay TB Cursors £1200
- TEKTRONIX 2465 4 Ch 300MHz Delay Sweep Cursors etc £2000
- TEKTRONIX 2445 4 Ch 150MHz Delay Sweep Cursors etc £1500
- TEKTRONIX TAS465 Dual Trace 100MHz Delay Cursors £900
- TEKTRONIX 2235 Dual Trace 100MHz Delay Sweep £800
- TEKTRONIX 2215 Dual Trace 60MHz Delay Sweep £400
- HWATSU S35711 4 Ch 100MHz Delay Sweep £550
- PHILIPS 3055 2+1 Ch 50MHz Delay DualTB £475
- GOULD 05100 Dual Trace 50MHz £200 With Delay
- GOULD 05300 Dual Trace 20MHz £200

AND REMEMBER ALL OUR EQUIPMENT IS TESTED PROPERLY



MARCONI 2019A Syn AM/FM Signal Gen 80KHz-104MHz £1900  
MARCONI 2019 Syn AM/FM Signal Gen 80KHz-104MHz £1500  
MARCONI 2018 Syn AM/FM Signal Gen 80KHz-520MHz £800  
MARCONI 2017 AM/FM Signal Gen 10KHz-1024MHz £1750



FARNELL SSG520 Syn AM/FM Signal Gen 10-520MHz £325  
FARNELL PSG520 Syn AM/FM Sig Gen 10-520MHz Portable £450

- MARCONI 6311 Programmable Sweep Gen 10MHz-20GHz £4500
- MARCONI 2022C AM/FM Signal Gen 10KHz-1GHz £2000
- H.P. 8656A Syn Signal Gen 0.1 - 990MHz £1500
- H.P. 8640B PhaseLockSyn Sig Gen 500KHz-512MHz £750
- H.P. 8640A AM/FM Signal Gen 500KHz-1024MHz £350
- PHILIPS PM5103 Programmable Syn Func Gen 0.1MHz-50MHz £1500
- PHILIPS PM5182 Programmable Syn Func Gen 0.1MHz-20MHz £1000
- H.P. 3325A Syn Function Gen 21MHz £1250
- PHILIPS PM5134 Sweep Func Gen 0.001Hz-20MHz Sine/Sq/Tri etc £400
- PHILIPS PM5132 Sweep Func Gen 0.1Hz-2MHz Sine/Sq/Tri etc £250



CLASSIC AV08 Mk5 in Case with Batteries & Leads £50



FLUKE 77 DMM 3 1/2 digit with Carrying Case & leads £50



**RACAL COUNTERS**  
9918 10Hz-50MHz £125  
9916 10Hz-50MHz £150  
9904 DC-50MHz £80



RACAL 1998 Counter 1.3GHz GPIB £650  
RACAL 1991 Counter/Timer 160MHz £450  
RACAL 1990 Counter 120MHz £300



SOLARTRON 7151 DMM 6 1/2 digit IEEE £450  
SOLARTRON 7150 DMM 6 1/2 digit IEEE True RMS £300

**LOOK!!**  
BRAND NEW OSCILLOSCOPES - NEVER USED LIMITED STOCK



**DMS 9850A DIGITAL STORAGE/DMM**  
Handheld LCD Display 2 Channel 50MS/S. Auto range. 4 digit DMM/Capacitance/Frequency Counter Battery Operation or external 7.5-9VDC i.e. AC Adaptor (Not supplied). RS232 Comes in Black Carrying Pouch complete with 2 scope probes, DMM leads; Manual FOR ONLY £400



**DTS 40 DIGITAL STORAGE**  
Dual Trace 40MHz 20MS/S Storage. Cursors + On Screen Readout. Sweep Delay, Interface etc. etc. Supplied Unopened in original box complete with 2 Probes & Manual  
**AMAZING VALUE AT £400**



**DTA 204050 DUAL TRACE**  
with All Magnification; TV Trig etc. etc. Lots of Specification  
DTA20 Dual Trace 20MHz £225  
DTA40 Dual Trace 40MHz-12KV EHT £300  
DTA60 Dual Trace 60MHz-12KV EHT £375  
All unused & boxed supplied with 2 probes & Manual

- POWER SUPPLIES**
- FARNELL AP100/30 0-100Volts, 0-30Amps Auto Ranging £1000
  - FARNELL H60/25 0-60Volts, 0-25Amps £400
  - FARNELL TS370M/2 70Volts, 5Amps/35Volts 10Amps £200
  - FARNELL L12-10C 0-12Volts, 0-10Amps £175
  - FARNELL LT30-2 0-30Volts, 0-2Amps Twice £160
  - FARNELL LT30-1 0-30Volts, 0-4Amps Twice £130
  - THURLBY-THANDAR TSP3222 Programmable 32Volts, 20Amps GPIB Digital £275
  - THURLBY PL320 0-30Volts, 0-2Amps GPIB Digital £450
  - THURLBY PL310 0-30Volts, 0-1Amps Digital £150
  - THURLBY PL310 0-30Volts, 0-1Amps Digital £110
- MANY MORE POWER SUPPLIES AVAILABLE

**NEW & HARDLY USED**



**PANASONIC VP8177A FM/AM SIGNAL GENERATOR**  
100KHz-100MHz, FM 0-100KHz, Output -10dB-99dB AM 0-60%; 32 Preset Memory; Digital Display Frequency & Output.  
Used £450 Un-Used £750



**PANASONIC VP637A STEREO SIGNAL GENERATOR**  
Generates Broadcast FM-RDS/ARI; Preset Memory; GPIB  
Used £400 Un-Used £700



**KENWOOD FL180A WOW/FLUTTER METER**  
0.003%-10%; Freq 30KHz/3.15KHz  
RMS/AVERAGE/PEAK; Weighted Filters;  
Digital Display or rpm, 4 digit Free Counter  
(0.01KHz-9.999KHz/0.01KHz-55KHz)  
Used £400 Un-Used £500



**POWER SUPPLY MODEL HSP3010**  
0-30 Volts; 0-10 Amps  
Current Limiting; 2 Meters  
Used £160 Un-Used £200



**GOODWILL GVT427 DUAL CHANNEL AC MILLIVOLTMETER**  
10µV 300V in 12 Ranges  
Frequency 10Hz - 1MHz  
Used £100 Un-Used £125




**GOODWILL GAG-8086 AUDIO GENERATOR**  
Range 1Hz - 120MHz  
Sine/Square 10Hz-1MHz in 5 Steps  
Range 0.1% Low Distortion 5 Steps  
Output Attenuator  
Un-Used £80



**GOODWILL GFC 80100 FREQUENCY COUNTER**  
Range 1Hz - 120MHz  
8 Digit Display 15mV RMS Sensitivity  
Un-Used £75



 **ANALOGUE MULTIMETER Model HC260TR AC/DC Volts; DC Current 10Amps; 17 Ranges; Continuity Buzzer; Transistor Tester**  
Un-Used £15



**STEREO AUDIO BALANCE to UNBALANCED CONVERTOR**  
for Car Radio Servicing Un-Used £20



**STEWART of READING**

110 WYKEHAM ROAD, READING, BERKS. RG6 1PL  
Telephone: (0118) 9268041. Fax: (0118) 9351696  
Callers Welcome 9 am - 5.30 pm Monday to Friday (other times by arrangement)



**Used Equipment - GUARANTEED. Manuals supplied**

This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

# Five Range Capacitance Meter

**The careful use of close-tolerance components on this meter gives good results for low capacitance values where many meters fail. By Robert Penfold.**

**A**n analogue capacitance meter can be very simple indeed, often consisting of little more than an oscillator and a monostable. Many designs of this type have been published in the past, and no doubt they all perform quite well. The problem with the ultra-simple approach is that it usually provides a relatively confined measuring range. In particular, the accuracy at low values can be very poor, and it is often impossible to check components having values of less than about 50 to 100pF. This is a serious drawback for anyone interested in radio circuits, or high frequency circuits in general, where a large number of low-value capacitors are used. Even in low frequency circuits, there is usually a sprinkling of small capacitors to provide frequency compensation and so on.

This analogue capacitance meter has five ranges with full scale values of 100pF, 1nF, 10nF, 100nF, and 1 $\mu$ F. Its coverage is less extensive at the high value end than some other designs, but high value capacitors are easily checked using a multimeter. Good results are provided at low values where the unit will happily measure values down to a few picofarads. Excellent accuracy is obtained on all five ranges provided close tolerance resistors are used in the range-switching circuit. The circuit is powered from a PP3 size battery, or a simple unregulated 9V battery eliminator can be used if preferred.

## Operation


The block diagram (figure 1) shows the general arrangement used in this capacitance meter. The first three stages generate a sinewave signal of pre-set amplitude. A simple C-R oscillator generates a low frequency triangular waveform, and lowpass filtering is then used to reduce the harmonic content of this signal. This




rounds the waveform to give a reasonable sinewave signal of adequate purity for the present application. A variable gain amplifier enables the amplitude of the output signal to be controlled, and this stage provides a small amount of additional lowpass filtering.

The sinewave output signal is fed to an operational amplifier which is used in an inverting mode circuit of sorts.

Figure 1: the block diagram of the Five-range Capacitance Meter

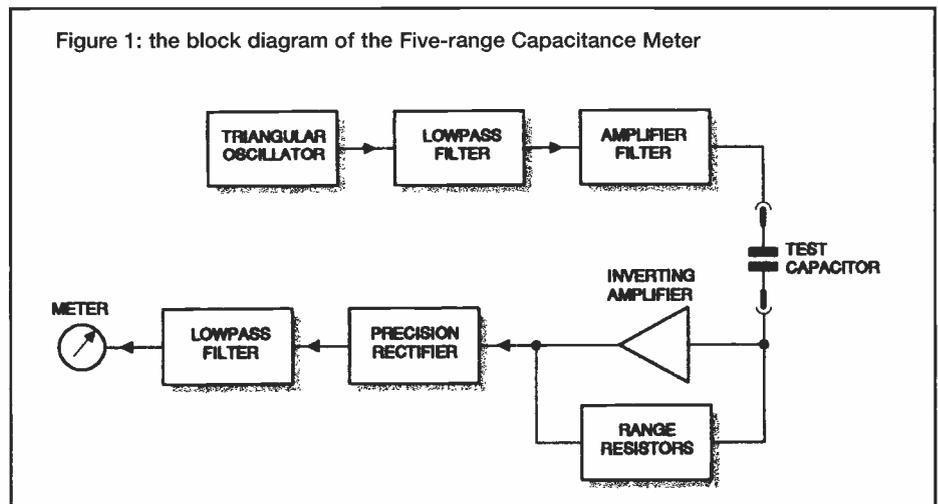

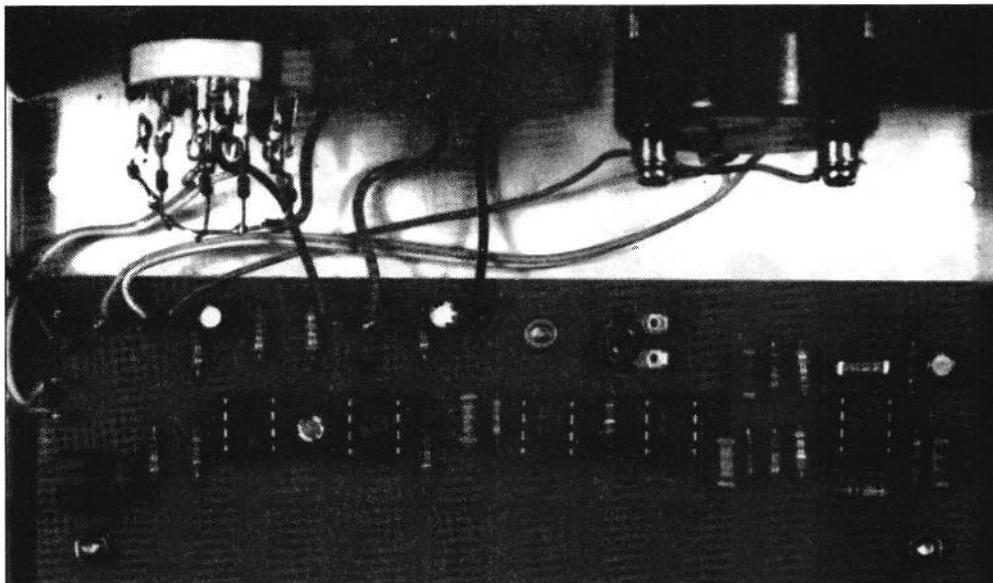

is therefore dependent only on the value of the test component.


This method of capacitance measurement relies on the fact that the reactance of a capacitor is inversely proportional to its value. For example, at a given frequency a 10nF capacitor will have a reactance that is ten times higher than that of a 100nF component. Suppose that a 100nF test capacitor has a reactance that is equal to the selected feedback resistor. This gives unity voltage gain through the inverting amplifier, and an output level that is equal to the input level. The

What would normally be the input resistor is actually the capacitor under test, and the feedback resistor is one of five switched resistors (one for each range). The closed loop voltage gain of this modified arrangement is governed by the normal rules, and is simply equal to the feedback resistance divided by the reactance of the test capacitor. The reactance of the test capacitor is dependent on the applied frequency and the value of the capacitor. In this case the input frequency is fixed, and the reactance value

reactance of a 50nF test capacitance would be double the value of the feedback resistor, giving a voltage gain of 0.5. The output level from the inverting amplifier would therefore be half the input level. A 10nF test capacitor would have a reactance value some ten times higher than the value of the feedback resistor, giving a voltage gain of just 0.1. The amplitude of the output signal from the inverting amplifier would obviously be one tenth of the input level.

It should be apparent from this that there is a linear

Figure 2: the Five-range Capacitance Meter circuit diagram

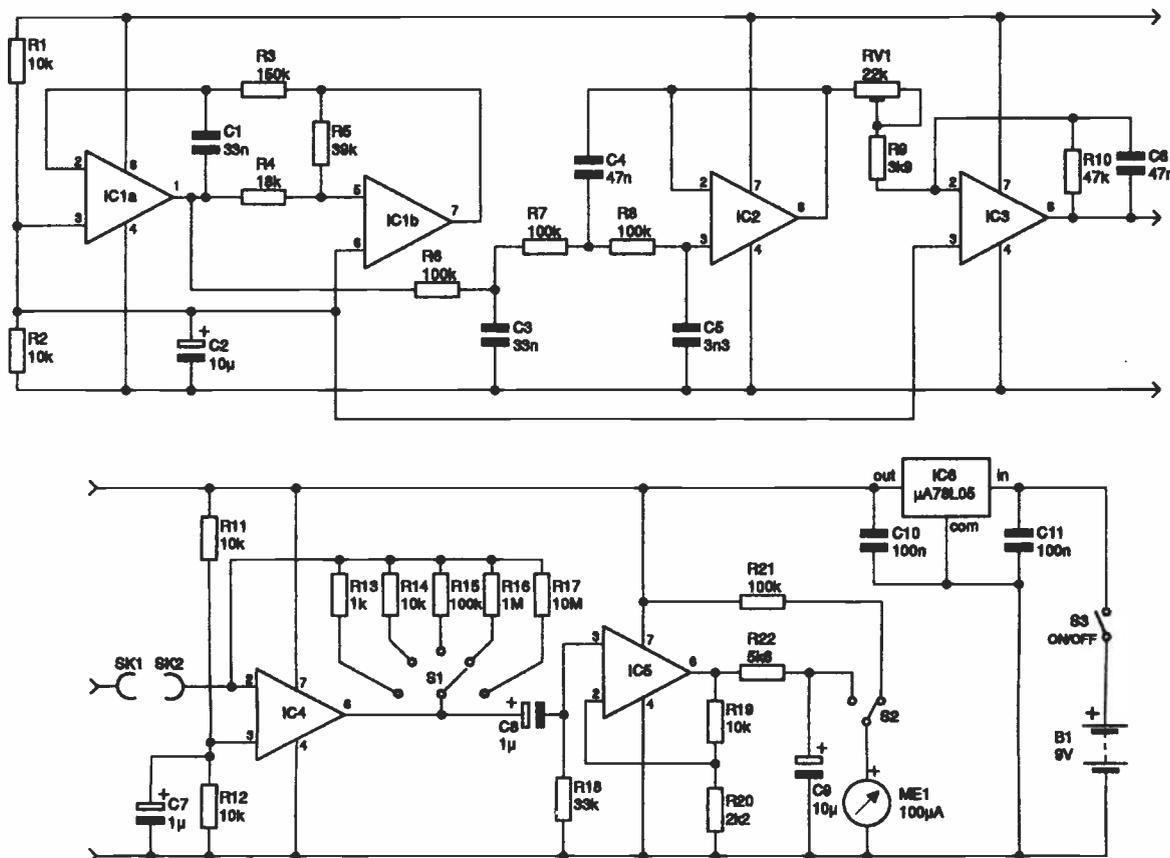



**8 CAVANS WAY,  
BINLEY INDUSTRIAL ESTATE,  
COVENTRY CV3 2SF**  
Tel: 01203 650702  
Fax: 01203 650773  
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

## OSCILLOSCOPES

Beckman 9020 - 20MHz - Dual Channel.....	£150
Cossor 3102 - 60MHz Dual Channel.....	£250
Gould OS 245A/250/255/300/3000/3351/4000.....	from £125
Hameg 203/203-5 - 20MHz - Dual Channel.....	from £150
Hewlett Packard 180A/180C/181A/182C.....	from £200
Hewlett Packard 1740A, 1741A, 1744A, 100MHz dual ch.....	from £350
Hewlett Packard 54100D - 1GHz Digitizing.....	£2995
Hitachi V650F - 60MHz Dual Channel.....	£350
Hitachi V152F/V302B/V302F/V353F/V550B/V650F.....	from £125
Intron 2020 - 20MHz Digital Storage (NEW).....	£650
Niitsu SS 5710/SS 5702 - 20MHz.....	from £125
Kikusui COS 6100 - 100MHz, 5 Channel, 12 Trace.....	£475
Kikusui 5100 - 100MHz - Dual Channel.....	£350
Meguro - MSO 1270A - 20MHz Digital Storage (NEW).....	£650
Nicolet 310 - L.F. D.S.O. with twin Disc Drive.....	£550
Nicolet 3091 - L.F. D.S.O.....	£900
Leeroy 9450A - 300MHz/400 Ms/s D.S.O. 2 ch.....	£2250
Philips PM 3211/PM 3212/PM 3214/PM 3217/PM 3234/PM 3240/PM 3243/PM 3244/PM 3261/PM 3262/PM 3263/PM 3540.....	from £125
Philips PM 3295A - 400MHz Dual Channel.....	£1750
Philips PM 3335 - 50 MHz/20Ms/s D.S.O. 2 ch.....	£1500
Philips PM 3055 - 50 MHz/20M Timebase.....	£125
Tektronix 434 - 20MHz - 2 Channel Analogue Storage.....	£250
Tektronix 454 - 150MHz - 2 Channel.....	£400
Tektronix 468 - 100MHz D.S.O.....	£750
Tektronix TDS 520 - 500 Mhz/500Ms/s D.S.O. 2 Ch.....	£4000
Tektronix 2213 - 60MHz Dual Channel.....	£425
Tektronix 2221 - 100MHz Digital Storage 2 Channel.....	£1750
Tektronix 2221 - 60MHz Digital Storage 2 Channel.....	£1500
Tektronix 2235 - 60MHz Dual trace.....	£450
Tektronix 2235 - 100MHz Dual trace.....	£800
Tektronix 2335 - Dual trace 100MHz (portable).....	£750
Tektronix 2225 - 50MHz dual ch.....	£450
Tektronix 2440 - 300 MHz/500 Ms/s D.S.O. 2 Ch.....	£4250
Tektronix 455 - 50MHz Dual Channel.....	£350
Tektronix 464/466 - 100MHz An storage.....	from £350
Tektronix 465/465B - 100MHz dual ch.....	from £350
Tektronix 475/475A - 200MHz/250MHz Dual Channel.....	from £475
Tektronix 485 - 350MHz - 2 channel.....	£900
Tektronix 5403 - 60MHz - 2 or 4 Channel.....	from £250
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch.....	from £300
Tektronix 7704 - 250MHz 4 ch.....	from £650
Tektronix 7904 - 500MHz.....	from £850
Tektronix 7934 - 500MHz with storage.....	from £1000
Trio CS-1022 - 20MHz - Dual Channel.....	£125

Other scopes available too

### SPECIAL OFFER

HITACHI V212 - 20MHz DUAL TRACE.....	£180
HITACHI V222 - 20 MHz DUAL TRACE + ALTERNATE MAGNIFY.....	£200

## SPECTRUM ANALYSERS

Advantest 4131 - 10KHz - 3.5GHz (G.P.I.B.).....	£4500
Advantest 4133B - 10KHz - 20GHz (60GHz with external mixers) + Ext. Keyboard.....	£7250
Ando ACB211 - Spectrum Analyser 1.7GHz.....	£2250
Avcom PSA65 S - 1000MHz - portable.....	£2750
Eaton/Altech 757 - 10KHz - 22GHz.....	£2750
Hewlett Packard 3580A - 5Hz-50KHz.....	£995
Hewlett Packard 182T with 8559A (10MHz - 21GHz).....	£3750
Hewlett Packard 35601A - Spectrum Analyser Interface.....	£1000
Hewlett Packard 141T + 8552B + 8555A - (10MHz - 18GHz).....	£1600
Hewlett Packard 3562A Dual Channel Dynamic Sig. Analyser.....	£7500
Hewlett Packard 8505A - Network Analyser 500KHz - 1300MHz.....	£2950
Hewlett Packard 853A + 8558B - 0.1 to 1500MHz.....	£3250
Hewlett Packard 182T + 8558B - 0.1 to 1500MHz.....	£2750
Hewlett Packard 8754A - Network Analyser 4-1300MHz.....	£2000
Hewlett Packard 8591E (HP - 1B) - 9KHz - 1.8GHz (calibrated).....	£6500
Marconi 2370 - 110MHz.....	£399
Marconi 2371 - 30KHz - 200MHz.....	£1250
Meguro MSA 4901 - 1-300GHz (AS NEW).....	£1995
Meguro MSA 4912 - 1-1GHz (AS NEW).....	£3000
Polrad 641-1 - 10MHz - 18GHz.....	£1500
Rohde & Schwarz - SWOB 5 Polyskop 0.1 - 1300MHz.....	£1800
Takeda Riken 4132 - 1.0GHz Spectrum Analyser.....	£2500
Tektronix 7L18 with mainframe (1.5-60GHz with external mixers).....	£2000

## MISCELLANEOUS

Adret 740A - 100KHz - 1120MHz Synthesised Signal Generator.....	£2000
ANRITSU ME 462B DF/3 Transmission Analyser.....	£3000
Danbridge JP30A - 30KV Insulation Tester.....	£1500
Anritsu MG642A Pulse Pattern Generator.....	£850
Drantz 626 - AC/DC - Multifunction Analyser.....	£700
EIP 331 - Frequency counter 18GHz.....	£1500
EIP 545 - Frequency counter 18GHz.....	£1600
EIP 545A - Frequency counter 18GHz.....	£1750
EIP 575 - Frequency counter 18GHz.....	£750
Farnell AP70-30 Power Supply (0-70V/30A) Auto Ranging.....	£200
Farnell TSV-70 MKII Power Supply (70V - 5A or 35V - 10A).....	£125
Farnell DSG-1 Synthesised Signal Generator.....	£1650
Farnell ESG-1000 Synthesised Signal Generator 1GHz (as new).....	£2500
Flure 5100A - Calibrator.....	£2500
Flure 5100B - Calibrator.....	£1500
Gigatronics 8541 - Universal Power Meter.....	£550
Guidline 9152 - 112 Bette Standard Call.....	£300
Hewlett Packard 333A - Distortion Analyser.....	£2250
Hewlett Packard 3314A - Function Generator.....	£1000
Hewlett Packard 3336C - Synthesised Signal Generator (10Hz - 21MHz).....	£350
Hewlett Packard 3437A System voltmeter.....	£850
Hewlett Packard 3456A Digital voltmeter.....	£200
Hewlett Packard 3438A Digital multimeter.....	£3750
Hewlett Packard 35600A Dual Ch. Dynamic Signal Analyser.....	£2250
Hewlett Packard 3711A/3712A/3791B/3793B Microwave Link Analyser.....	£1000
Hewlett Packard 3776A - PCM Terminal Test Set.....	£1500
Hewlett Packard 3325A - 21MHz Synthesiser/Function Gen.....	£650
Hewlett Packard 3488A - HP - 1B Switch control unit (various Plug-ins available).....	£300
Hewlett Packard 334A - Distortion Analyser.....	£750
Hewlett Packard 3455A 6 1/2 Digit M/Meter (Autocal).....	£550
Hewlett Packard 3478A - Multimeter (5 1/2 Digit) + HP - 1B.....	£POA
Hewlett Packard 3776A - PCM Terminal Test Set.....	from £600
Hewlett Packard 3779A/3779C - Primary Mux Analyser.....	from £1000
Hewlett Packard 436A + Sensor.....	£3950
Hewlett Packard 4275A - LCR Meter (Multi-Frequency).....	£2000
Hewlett Packard 4338A - Millionmeter (As New).....	£395
Hewlett Packard 4342A 'Q' Meter.....	£2500
Hewlett Packard 4352A - Protocol Analyser (with interfaces).....	£2500
Hewlett Packard 4353A - Protocol Analyser.....	£2750
Hewlett Packard 432A - Power Meter (with 478A Sensor).....	£275

Hewlett Packard 435A or B Power Meter (with 8481A/8484A).....	from £750
Hewlett Packard 4271B - L.C.R. Meter (Digital).....	£900
Hewlett Packard 4278A - 1KHz/1MHz Capacitance Meter.....	£3750
Hewlett Packard 4279A - 1MHz C/V Meter.....	£500
Hewlett Packard 4848A (TIMS) Transmission Impairment M/Set.....	£2000
Hewlett Packard 4972A - Lan Protocol Analyser.....	£2000
Hewlett Packard 5420A Digital Signal Analyser.....	£350
Hewlett Packard 5335A - 200MHz High Performance Systems Counter.....	£600
Hewlett Packard 5314A - (NEW) 100MHz Universal Counter.....	£250
Hewlett Packard 5183 - Waveform Recorder.....	£2250
Hewlett Packard 5238A Frequency Counter 100MHz.....	£250
Hewlett Packard 5370A - 100MHz Universal Timer/Counter.....	£450
Hewlett Packard 5384A - 225 MHz Frequency Counter.....	£950
Hewlett Packard 5385A Frequency Counter - 1GHz - (HP1B) with OPTS 001/003/004/005.....	£995
Hewlett Packard 6031A - 100W Autoranging p.s.u. (20v - 120A).....	£1550
Hewlett Packard 6234A - 6V - 10A System Power Supply.....	£1500
Hewlett Packard 6253A Power Supply 20V - 3A Twin.....	£200
Hewlett Packard 6255A Power supply 40V - 1.5A Twin.....	£200
Hewlett Packard 6266B Power Supply 40V - 5A.....	£220
Hewlett Packard 6271B Power supply 60V - 3A.....	£225
Hewlett Packard 6034A - 0-60V - 10A System P.S.U.....	£1500
Hewlett Packard 7475A - 6 Pen Plotter.....	£250
Hewlett Packard 7550A - 8 Pen Plotter A3/A4.....	£450

### HEWLETT PACKARD 6261B Power Supply 20V-50A £450 Discount for Quantities

Hewlett Packard 8349B - Microwave Broad Band Amplifier.....	£3500
Hewlett Packard 8355A - Millimeter - Wave source Module 33-50GHz.....	£4250
Hewlett Packard 8015A - 50MHz Pulse Generator.....	£750
Hewlett Packard 8405A - Vector Voltmeter.....	£500
Hewlett Packard 8165A - 50MHz Programmable Signal Source.....	£1650
Hewlett Packard 8350B - Sweep Oscillator Mainframe (various Plug-Ins available) extra.....	£2650
Hewlett Packard 8152A - Optical Average Power Meter.....	£1250
Hewlett Packard 8158B - Optical Attenuator (OPTS 002 + 011).....	£1100
Hewlett Packard 8180A - Data Generator.....	£1500
Hewlett Packard 8182A - Data Analyser.....	£1500
Hewlett Packard 83554A - Wave Source Module 26.5 to 40GHz.....	£3500
Hewlett Packard 8684A 5.4GHz to 12.5GHz Sig-Gen.....	£2750
Hewlett Packard 8620C Sweep oscillator mainframe.....	from £250
Hewlett Packard 8565B - Synthesised Signal Generator.....	£250
Hewlett Packard 8750A Storage normaliser.....	£375
Hewlett Packard 8756A - Scaler Network Analyser.....	£2000
Hewlett Packard 8903A - Audio Analyser (20Hz - 100KHz).....	£2600
Hewlett Packard 8958A - Cellular Radio Interface.....	£2000
Hewlett Packard 8901A - Modulation Analyser.....	£3400
Hewlett Packard 8920A - R/F Comms Test Set.....	£6000
Hewlett Packard P382A Variable Attenuator.....	£250
Hewlett Packard 1630D - Logic Analyser (43 Channels).....	£650
Hewlett Packard 16500A - Fitted with 16510A/16515A/16530A/16531A - Logic Analyser.....	£4000
Hewlett Packard 11729B - Carrier Noise Test Set.....	£2000
Krohn-Hite 2200 Lin/Log Sweep Generator.....	£95
Krohn-Hite 4024A Oscillator.....	£250
Krohn-Hite 5200 Sweep Function Generator.....	£350
Krohn-Hite 6500 Phase Meter.....	£250
Marconi 2019 - 80KHz - 1040MHz Synthesised Sig. Gen.....	£1850
Marconi 2019A - 80KHz - 1040MHz - Synthesised Signal Generator.....	£1900
Marconi 2022A - 10KHz - 1GHz AM/FM Signal Generator.....	£2500
Marconi 2432A 500MHz digital freq. meter.....	£200
Marconi 2610 - True RMS Voltmeter.....	£850
Marconi 2871 Data Comms Analyser.....	£1000
Marconi 2955 - Radio Comms Test Set.....	£3000
Marconi 2950A - Radio Comms Test Set with Cellular Adaptor.....	£3500
Marconi 6960 - Power Meter & Sensor.....	from £950
Marconi 6960A - Power Meter & Sensor.....	from £150
Philips PM 516MHz function gen.....	£800
Philips 5190 L.F. Synthesiser (G.P.I.B.).....	£800
Philips PM5519 - TV Pattern Generator.....	£350
Philips PM5667 - Vectorscope.....	£500
Philips PM5716 - 50MHz Pulse Generator.....	£525
Philips PM6652 - 1.5GHz Programmable High Resolution Timer/Counter.....	£900
Philips PM6670 - 120MHz High Resolution Universal Counter.....	£350
Philips PM6673 - 120MHz High Resolution Universal Counter.....	£430
Prema 4000 - 6 1/2 Digit Multimeter (NEW).....	£450
Racal 1992 - 1.3GHz Frequency Counter.....	£800
Racal Dana 9081/9082 Synth. sig. gen. 520MHz.....	from £500
Racal Dana 9084 Synth. sig. gen. 104MHz.....	£450
Racal Dana 9303 R/F Level Meter & Head.....	£1500
Racal Dana 9917 JHF frequency meter 560MHz.....	£175
Racal Dana 9302A R/F multivoltmeter (new version).....	£375
Racal Dana 9082 Synthesised am/fm sig gen (520MHz).....	£500
Racal 9301A - True RMS R/F Multivoltmeter.....	£300
Rohde & Schwarz LFM2 - 60MHz Group Delay Sweep Gen.....	£1600
Rohde & Schwarz SAMP2 - 1GHz Radio Comms T/set.....	£2500
Rohde & Schwarz USPF2 - Video Noise Meter.....	£1400
Rohde & Schwarz URE - RMS Voltmeter (10Hz-25MHz).....	£500
Rohde & Schwarz SCF Radio Code Test Set.....	£300
Rohde & Schwarz SUD 2 Noise Generator.....	£300
Rohde & Schwarz SMDU - 15MHz to 525MHz Signal Gen (FM & AM).....	£300
Schaffner NSG 203A Line Voltage Variation Simulator.....	£850
Schaffner NSG 222A Interference Simulator.....	£950
Schaffner NSG 223 Interference Generator.....	£850
Schaffner WSG 431 Electrostatic Discharge Simulator.....	£1250
Schlumberger 4923 Radio Code Test Set.....	£950
Schlumberger 4031 - 1GHz Radio Comms Test Set.....	£6500
Schlumberger 2720 1250MHz Frequency Counter.....	£500
Schlumberger 7060/7065/7075 Multimeters.....	from £350
Solatron 1250 - Freq. Response Analyser.....	£2500
Stanford Research DS 340 - 15MHz Synthesised Function (NEW) and arbitrary waveform generator.....	£1200
Systron Donner 6030 - Microwave Frequency Counter (26.5GHz).....	£2500
Teletquipment CT71 Curve Tracer.....	£2500
Tektronix TM5003 - AFG 5101 Arbitrary Function Gen.....	£1750
Tektronix 1240 Logic Analyser.....	£500
Tektronix DAS9100 - Series Logic Analyser.....	£500
Tektronix - Plug-ins - many available such as SC504, SW503, SG502, PG508, FG504, FG503, TG501, TR503 + many more.....	£POA
Tektronix 577 Curve Tracer.....	£1150
Tektronix AM503 + TG501 + P6302 - Current Probe Amplifier.....	£995
Tektronix PG506 + TG501 + SG503 + TG503 - Oscilloscope Calibrator.....	£1995
Tektronix AA5001 + TM5006 M/F - Programmable Distortion Analyser.....	£2500
Tektronix 577 - Curve Tracer.....	£1150
Time 9811 Programmable Resistance.....	£600
Time 9814 Voltage Calibrator.....	£750
Tecliner 7720 - Programmable 10MHz Function Gen (AS NEW).....	£700
Valhalla Scientific - 2724 Programmable Resistance Standard.....	£P.O.A.
Wandel & Goltermann PCM4 (+ options).....	£9950
Wayne Kerr 4225 - LCR Bridge.....	£600
Wayne Kerr 6425 - Precision Component Analyser.....	£275
Wayne Kerr 8905 - Precision LCR Meter.....	£850
Wavetek 171 - Synthesised Function Generator.....	£250
Wavetek 172B Programmable Sig Source (0.0001Hz - 13MHz).....	£P.O.A.
Wavetek 184 - Sweep Generator - 5MHz.....	£250
Wavetek 3010 - 1-1GHz Signal Generator.....	£1250
Wiltron 6620S - Programmable Sweep Generator (3	

More than

0 0 2 5 8 1/2

Electronic

**DESIGNERS**

know how to get their

**PROTOTYPE PCBs**

from their **usual manufacturer** for a

**FRACTION** of the **COST!**

DO YOU ?

STOP WASTING YOUR MONEY!

CALL NOW: 00353 65 66500

**Beta**  
LAYOUT  
**PCB-POOL®**

**get**  
**connected**  
pcbpool@betalayout.ie  
<http://www.pcb-pool.com>



 **00353 65 66500**  
**FAX 66514**


relationship between the value of the test capacitor and the amplitude of the output signal from the inverting amplifier. Feeding the output of the inverting amplifier to a precision rectifier and smoothing circuit produces a dc output voltage that is proportional to the ac output voltage from the inverting amplifier. This drives a moving coil meter which indicates the value of the test components, and has linear scaling. The gain control in the sinewave generator circuit enables the unit to be calibrated against a precision capacitor which should preferably have a tolerance of one percent or better.

### The circuit

The full circuit diagram for the five range capacitance meter appears in **figure 2**. IC1 is used in a standard triangular/squarewave oscillator of the type that uses an integrator (IC1a) and a trigger circuit (IC1b). In this case it is only the triangular output signal from IC1a that is required. The oscillator circuit has an operating frequency of about 115Hz. The triangular output signal is fed to a conventional third order (18dB per octave) lowpass filter based on IC2. This filter has its cut-off frequency at approximately 100Hz. It therefore allows the fundamental input frequency to pass with little attenuation, but severely attenuates even the lower order harmonics. IC3 is used in the variable gain amplifier, which is a simple inverting mode circuit. Its gain can be varied from approximately 12 with VR1 at minimum resistance, to just under two with VR1 set for maximum resistance. C6 applies increased feedback at high frequencies, which gives some additional lowpass filtering, and a slightly improved sinewave output signal.


The test capacitors are connected across SK1 and SK2. IC4 is the operational amplifier in the inverting mode amplifier, and R13 to R17 are the range resistors. These must have a tolerance of one percent or better if good accuracy is to be achieved on all five ranges. R13 is the feedback resistor on the 1uF range, running through to R17, which is the feedback resistor for the 100pF range.

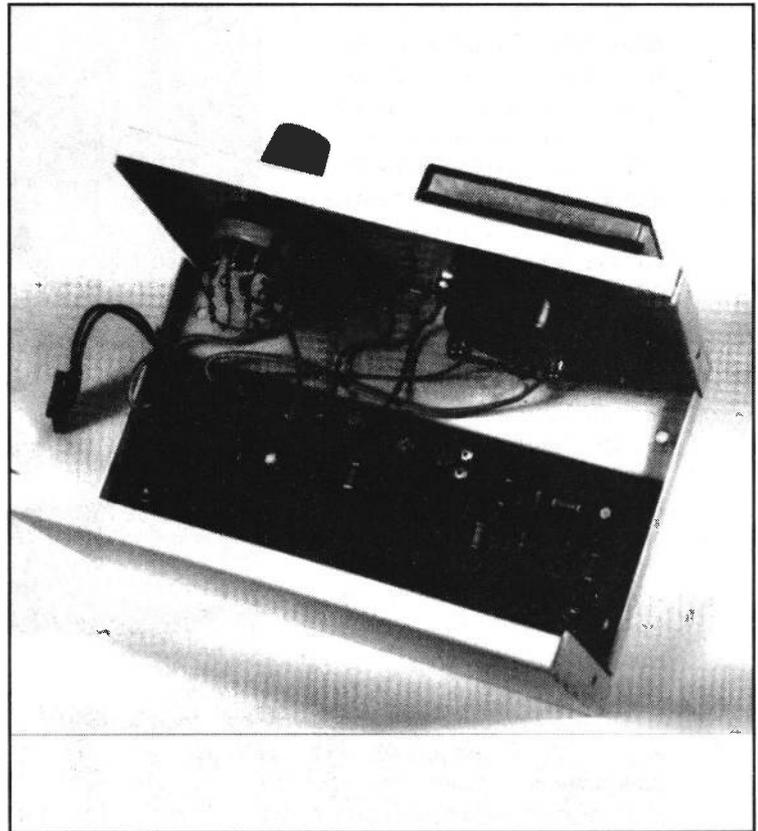The precision rectifier uses IC5 as (in effect) a non-inverting amplifier with a voltage gain of about 5.5. However, IC5 is used without a negative supply, which means that it cannot provide negative output signals. The



CA3140E specified for IC5 is a type which can operate with its inputs and output at very low potentials, and the circuit therefore functions normally on positive input half cycles. This circuit therefore provides a half-wave rectified and slightly boosted output signal which is fed to the meter via the simple lowpass filter circuit comprising R22 and C9. Note that most operational amplifiers cannot operate with their inputs and output at less than about one or two volts above the negative supply terminal, so devices such as the TL071CP, LF351N, uA741C, and so on, will not work in the IC5 position of this circuit. It is also worth noting that the circuit operates from a five-volt supply, and that this is too low for many operational amplifiers. The use of alternatives for IC1 to IC4 is not recommended, either.

Figure 3: the pcb component layout for the Five-range Capacitance Meter

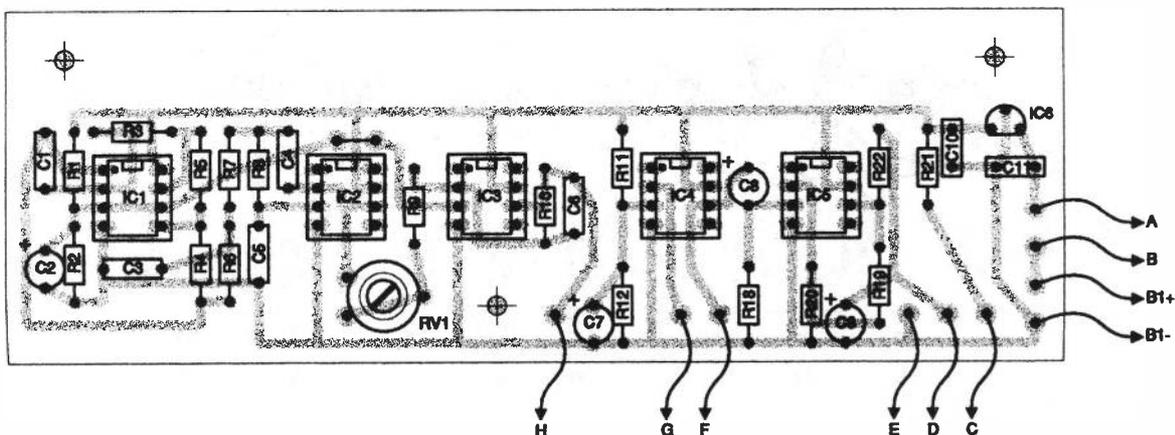

It is essential that the circuit is powered from a stable supply, since the output level from the sinewave generator circuit varies with changes in the supply voltage. A stabilised five volt supply is derived from the nine volt battery supply by monolithic voltage regulator IC6. S2 connects the positive terminal of meter ME1 to R22 and C9 in normal operation, but it can be set to the other position to check that the battery voltage is acceptable. The meter is then connected across the stabilised five-volt supply via R21, which effectively converts the meter to a simple voltmeter having a full scale value of 10 volts. If any "sagging" of the stabilised supply is evident, the battery is exhausted and must be replaced immediately.

The total current consumption of the circuit is about eight to 10 milliamps, and a PP3 size battery is just about adequate to supply this. Alternatively, any nine-volt battery eliminator should be able to supply such a modest current. Due to the inclusion of IC6 it is not necessary to use a battery eliminator that has a built-in regulator circuit, but a supply of this type is, of course, perfectly suitable for use with this unit.

### Construction

Most of the components are assembled on a printed circuit board, as detailed in **figure 3**, the component layout. Construction of the circuit board is largely straightforward, but there are a few points that merit amplification. Bear in mind that the CA3140E used for IC5 is a MOS input device which requires standard anti-static handling precautions. The most important of these is to fit the device in an ic holder, and not to plug the ic into place until the circuit board and all the wiring are otherwise complete. Before that it should be left in its anti-static packing. Try to handle IC5 as little as possible when fitting it into the holder, and




keep it away from any obvious sources of static charges. Although IC1 to IC4 all have fet input stages, they do not require any special handling precautions as they have jfet rather than mosfet input stages. However, it is still advisable to use ic holders for all four of these devices.

In order to fit neatly into this board layout the non-electrolytic capacitors should be small printed circuit mounting types having 7.5 millimetre lead spacing. The only exceptions are C10 and C11 which are miniature ceramic capacitors having five millimetre lead spacing. VR1 must be a miniature (0.1 or 0.15 watt) horizontal mounting preset. Fit single-sided one-millimetre diameter pins to the board at the positions where connections will eventually be made to the off-board components such as the switches and ME1. Tin the tops of the pins with a liberal amount of solder.

A metal instrument case measuring about 150 by 100 by 75 millimetres is adequate to accommodate this project. The exact layout is not critical, but try to use one that avoids having long connecting wires to SK1, SK2, and S1. Excessively long connecting wires can give problems with stray capacitance, causing reduced accuracy when

Figure 4: the hard wiring (use in conjunction with figure 3)

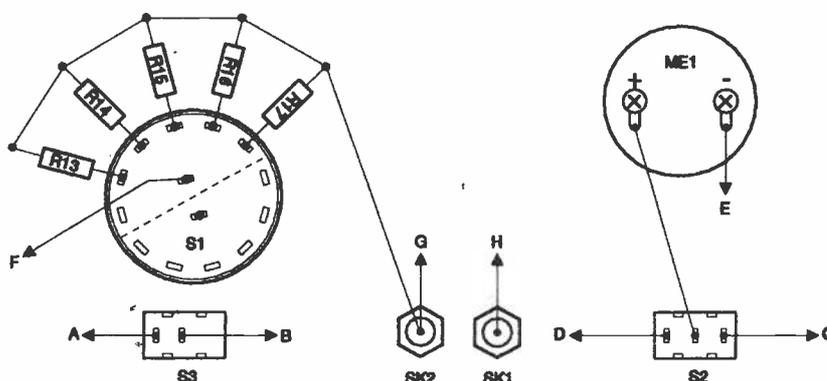

measuring very low value capacitors. On the prototype, SK1 and SK2 are one-millimetre sockets mounted about 15 millimetres apart. Many capacitors will plug straight into these, but a set of small test leads fitted with miniature crocodile clips must be made up so that small printed circuit mounting capacitors can be tested.

Fitting the meter on the case is slightly awkward because the meter requires a sizeable cut-out. A 38-millimetre diameter hole is required for a standard 60 by 45 millimetre panel meter. This can be cut using an Abrafile or any other miniature round file. It is advisable to cut just within the perimeter of the required cut-out, and then carefully enlarge the hole using a large half-round file. A special tool for making large diameter holes is available from some do-it-yourself stores, and this represents the quickest and easiest way of making the mounting hole. These hole-cutters are also known as "tank cutters", and they are intended for use in hand drills or (preferably) a brace, as they must be used at very slow speeds. They can be adjusted to produce any size of hole from about 20 millimetres in diameter to 60 millimetres or more. The meter also requires four 2.5 millimetre diameter mounting holes for its built-in threaded mounting rods. The positions of these can be located using the meter itself as a sort of template.

Details of the hard wiring are provided in **figure 4**. In order to keep stray capacitance to a minimum the range resistors (R13 to R17) are mounted on SW1. I used a six-way two-pole switch for SW1, with its adjustable end-stop set for five-way operation, but a standard 12-way single pole switch is also suitable. There should be no difficulty in fitting the resistors in place provided the ends of the leadout wires and the tags of SW1 are tinned with solder first. Try to make the connections reasonably swiftly so that there is no danger of the resistors becoming overheated, and their accuracy being impaired. In other respects the hard wiring offers nothing out of the ordinary.

### Calibration and use

A close tolerance (one percent or better) capacitor is needed in order to calibrate the unit, and this capacitor should ideally have a value that is equal to the full scale value of one of the capacitance meter's ranges. If a suitable component has to be bought specially it is advisable to calibrate the unit on the 100pF or 1nF range, because close tolerance capacitors with higher values tend to be quite expensive. To calibrate the unit, simply switch it to the appropriate range, connect the calibration capacitor across SK1 and SK2, and then adjust VR1 for the correct reading on ME1. The meter should then function with good accuracy on all five ranges.

In theory it is not possible to test small electrolytic capacitors using this meter because the test capacitor is fed with a pure ac signal that does not include a dc component. In practice though, accurate measurements seem to be obtained with electrolytic capacitors connected either way round. When using the unit, try not to touch either leadout wire of the test components, as this could result in noise picked up in your body being fed into the rectifier circuit. This could significantly inflate readings. This is especially important when testing low value components, as the tester is more sensitive to stray pickup on the 100pF and 1nF ranges.

It is perhaps worth bearing in mind that the circuit

responds to the impedance across SK1 and SK2 at the test frequency. A capacitor that is faulty with a high leakage level might give a reading on one range of the unit, but the indicated value would be much higher than the marked value of the test component. If a high leakage level is expected, a quick test with a multimeter set to a resistance range will soon show whether or not the test component exhibits this fault.

One final important point is that with any practically any capacitance meter, it is courting disaster to test a capacitor that is charged to anything more than a few volts. If there is any risk of a test component having a significant charge voltage, discharge it prior to connection to the capacitance meter.

## PARTS LIST for the Five-range Capacitance Meter

### Resistors

(All 0.25 watt 5 percent carbon film unless noted)

R1,2,11,12,19	10k
R3	150k
R4	18k
R5	39k
R6,7,8,21	100k
R9	3k9
R10	47k
R13	1k (metal film 1 percent)
R14	10k (metal film (1 percent)
R15	100k (metal film 1 percent)
R16	1M (metal film 1 percent)
R17	10M (metal film 1 percent)
R18	33k
R20	2k2
R22	5k6
VR1	22k min hor preset

### Capacitors

C1,3	33n polyester, 7.5mm lead spacing
C2,9	10u 25V radial elect
C4,6	47n polyester, 7.5mm lead spacing
C5	3n3 polyester, 7.5mm lead spacing
C7,8	1u 50V radial elect
C10,11	100n disc ceramic

### Semiconductors

IC1	TL072CP dual bifet op amp
IC2,3,4	TL071CP bifet op amp
IC5	CA3140E PMOS op amp
IC6	uA78L05 5V 100mA positive regulator

### Miscellaneous

ME1	100uA moving coil panel meter
SW1	6-way 2-pole rotary switch with adjustable end-stop (set for 5-way operation, only one pole used)
SW2	SPDT min toggle switch
SW3	SPST min toggle switch
B1	9 volt (PP3 size)
SK1,2	1mm socket
	Metal instrument case about 150 x 100 x 75mm, printed circuit board, 5 x 8-pin DIL holder; battery clip, control knob, wire, solder, etc.

# SUBSCRIBE AND SAVE UP TO £9


... and LET THE POSTMAN DO THE WORK!



SUBSCRIBE AND BEAT THE ETI PRICE INCREASE
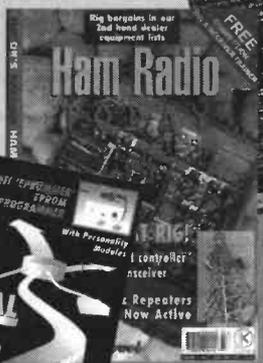
## ACORN ARCHIMEDES WORLD

13 issues  
UK: WAS £48.75, NOW £39.75, YOU SAVE £9,  
Europe: £60.50, Overseas: £62.50, USA: \$100.00



## HAM RADIO TODAY

13 issues  
UK: WAS £32.50, NOW £29.00, YOU SAVE £3.50,  
Europe: £39.50, Overseas: £41.50, USA: \$66.00

## E.T.I. PRICE FREEZE OFFER!

13 issues  
UK: WAS £32.50, NOW £27.00, YOU SAVE £5.50,  
Europe: £40.00, Overseas: £41.80, USA: \$64.00

Now this just has to be a good deal! Not only will you save a considerable amount of money, but your postman will also deliver the next 13 issues of your favourite electronics magazine directly to your door - with no fuss, no hassle, and no future price increases.

So go on, subscribe now, save your shoe leather, and up to 70p per issue.

Here's why YOU should subscribe to either ETI, Ham Radio Today or Acorn Archimedes World:

- ♦ FREE home delivery in the UK.
- ♦ A saving of up to £9 a year.
- ♦ Price protection - you won't pay any more if the cover price goes up.
- ♦ Guarantee receiving every issue.

This is one deal where you really can't lose.

**REMEMBER, it's always cheaper to subscribe!**

All savings are based upon buying the same number of issues from your newsagent. UK only.

The cover price of ETI has now risen to £2.50 BUT you can still subscribe at the old price - if you order today! After this issue we will have to charge a new, higher rate - so take advantage of this offer now!

## SUBSCRIPTION ORDER FORM

YES, I would like to subscribe to (please tick):  Acorn Archimedes World  Ham Radio Today  E.T.I.  
for the next 13 issues (all subscriptions will start with the next available issue, unless extending).

The total value of my order is £.....I enclose a cheque/PO payable to 'Nexus Special Interests', or please debit my Access/Visa/Mastercard/AMEX account:

Card No:

Expiry...../.....  
Signature.....

### Your Details:

Name: Mr/Mrs/Miss Initial:.....Surname:.....

Address:.....  
.....Post Code:.....

Tel no:.....

Please return, together with your payment, to: Nexus Subscriptions, Tower House, Sovereign Park, Lathkill Street, Market Harborough, Leics LE16 9EF  
Offer closes: 31/8/97 Code: 0210

**TO ORDER BY PHONE, PLEASE CALL OUR CREDIT CARD HOTLINE ON 01858-435344 (Mon to Fri, 9am - 5.30pm)**

Please tick this box if you do not wish to receive information from other companies

# An RS232 I/O Card for Psion 3s and PCs

*The Psion Organiser can be more than an electronic diary. Using this interface by Pei An, you can program it to control things for you, or work as a simple data logger.*

**T**he Psion series 3, 3A, 3C and Sienna are palmtop computers.

Although they are packaged as personal organisers, they are really general-purpose computers. They are equipped not only with powerful built-in organiser applications like word processing, spreadsheet, agenda and database management (such as telephone and address books), but also contain a powerful built-in Basic-like programming language, the Organiser Programming Language (OPL). The latter allows the user to

write sophisticated software for applications other than the ones that are built in. Psion organisers have a comprehensive power saving scheme, which makes them excellent computers with the major benefits of compactness and long battery life. Psions also have an I/O port which allows them to be connected up to desktop computers, modems and printers. The I/O ports on the Psion 3 and 3A can be converted into a standard RS232 or a Centronics port by means of external plug-in devices. The Psion 3C/Sienna, however, already has an industrial-standard RS232 interface and an IrDA data communications port incorporated.

Like other PCs, the Psions can be used for computer interfacing applications. Using the RS232 port, external circuits can be connected up to form PC-based systems for applications such as data acquisition and control, which can be made truly portable and mobile owing to the compactness and low power consumption of the Psions.

This article describes a general purpose RS232 I/O card for the Psion 3C organiser as well as for PCs. It is connected



The Psion 3C and RS232 I/O card


to the port by three wires, and offers eight digital inputs and eight digital outputs. **Figure 1** shows the I/O system connected to a Psion 3C. The card itself is shown in one of the photos accompanying this article. It allows the user to explore the RS232 port and make use of the port for other PC interfacing applications using the Psion and PCs.

## Fundamentals

The RS-232C port is an industrial-standard asynchronous serial data communications interface for passing serial data between two devices. It is included in almost all types of desktop and notebook PCs and is used mainly for connecting printers, modems, mice and other peripherals.
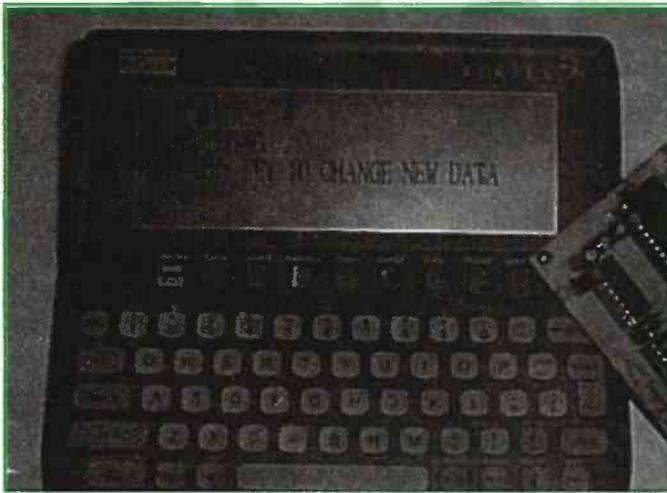
## Serial data

Unlike a parallel port, which normally has eight data lines and transmits one 8-bit byte in each go, a serial port only has one data line to transmit 8 bits. The byte is transmitted serially.



The RS232 I/O card from above

There are two serial data transfer schemes, synchronous and asynchronous. With synchronous data transfer, additional lines are needed to transmit handshake signals along with the data line to indicate when the next bit is to be transmitted. The advantage of this is that the receiver is able to respond to the clock rate of the transmitter automatically.

With asynchronous data transfer, the transmitted data itself contains the synchronisation information, and no handshake signal is needed. The transmitted serial data comprises a start bit, which indicates the beginning of a data transmission, followed by serial data bits and then stop bits indicating the end of the transmission. An optional parity bit can be added between the serial data bits and the stop bit for parity checking.

The receiver device detects the start bit and receives the subsequent data bits. This scheme requires that the transmitter and the receiver must have the same clock frequency. Asynchronous data transmission is used in most personal computers. The asynchronous standard is facilitated by a family of industrial peripheral ucs known as the UARTs (Universal Asynchronous Receivers and Transmitters). The card in this project employs a 6402 UART.

### The format

The format of the serial data transmission generated by UARTS is in four parts: a start bit, data bits, one parity bit, and at least one stop bit (see **figure 2**). When no data is sent, the transmitting data line is in the high state (2V-5V TTL level). The beginning of a data transmission is indicated by the line going low (0-0.8V TTL level) for the duration of 1 bit. This the start bit. The data bits are then sent out one after another with the least significant bit sent first. The length of the data bit can be 6, 7 or 8. Following the data bits is the parity bit, which is used to check for errors occurring in the data transmission. The last bits are the stop bits. The data line goes high for at least 1 bit, to identify the end of the data transmission. The stop bit can be 1, 1.5 and 2 bits in length.

The serial data transmission format is generated by the electronics inside the transmitting UARTs. The electronics in the receiver detect the leading edge of the start bit. The chip then waits for one and a half bits before reading the data bit. The reading should therefore come exactly in the middle of the first data bit. Then it waits for one bit, and reads the second bit. This time the reading comes exactly in the middle of the second data bit. After completing the reading of the data bits, the electronics detects the parity of the received


data for error checking, and resets itself during the stop bit to wait for the next data transmission.

The rate at which data bits are sent is measured by the Baud rate. It is defined as  $1/(\text{the time between the shortest signal transition period})$  - see **figure 2**). The standard Baud rates for RS232 serial port are 110, 150, 300, 600, 1200, 2400, 4800, 9600 and 19200. Knowing the Baud rate, the number of characters (or bytes) to be transmitted per second can be calculated. For example, if the serial data transmission has 8 data bits, no parity bit and 1 stop bit, the total length of serial data bits is 10. The transfer rate for characters is the Baud rate divided by 10; for example, a Baud rate of 9600 transfers 960 characters per second.

The parity check can be Odd, Even or None. The odd and even parity checks indicate that the total number of ones in the transmitted serial data is an odd number or an even one. This method is the simplest way of checking for errors during data transmission. However, it is only reliable for detecting single-bit errors. Errors with several bits may not be detected. The parity bit is generated by the electronics of the transmitting UART in such a way that the number of ones in the data bits plus the parity bit is odd or even as declared. Suppose we send a binary byte 01000011 (there are three 1s in the byte) from the computer to an external device and the parity has been declared as odd (the total number of ones is odd). The parity bit will be set 0, since the number of ones in these nine data bits is already odd. At the receiver end, the receiver must also be configured to have an odd parity check. The electronics in the receiver UART will count the number of ones in the received data. If the data does not have an odd parity, an error signal is generated indicating that a transmission error has been occurred. If parity check is declared as None, the parity bit will not be generated and checked.
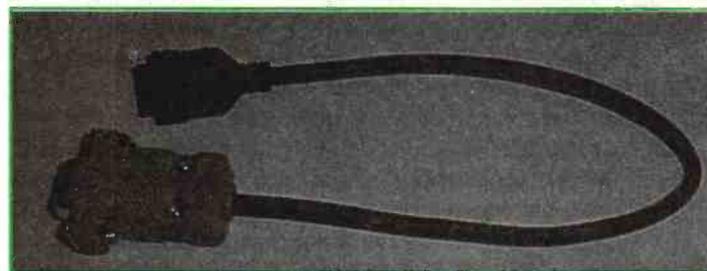
### Line drivers and receivers for the RS232 link

The signal from the UARTs has a TTL level. A logic high corresponds to a voltage ranging from 2V to 5V and a logic low corresponds to a voltage between 0V and 0.8V. Signals of this voltage level cannot be transmitted reliably over a long distance. To solve the problem, RS232 transceivers are used to boost up the voltage of the transmit signal from the TTL level to the RS232 level, which is substantially higher than the former. Receivers are used in the receiving device to convert the RS232 voltage level to the TTL level. This arrangement enables the RS232 interface to communicate over a maximum distance of about 30 meters. The voltage conversion between TTL and RS232 is facilitated by a family of industrial RS232 transceiver ics. The current project uses a MAX232CPD. All the RS232 transceivers have an inverting action. A TTL logic high is translated to -3V to -12V at the RS232 side, and a TTL logic low is translated to +3 to 12V. It



A home-made Psion 3C serial cable

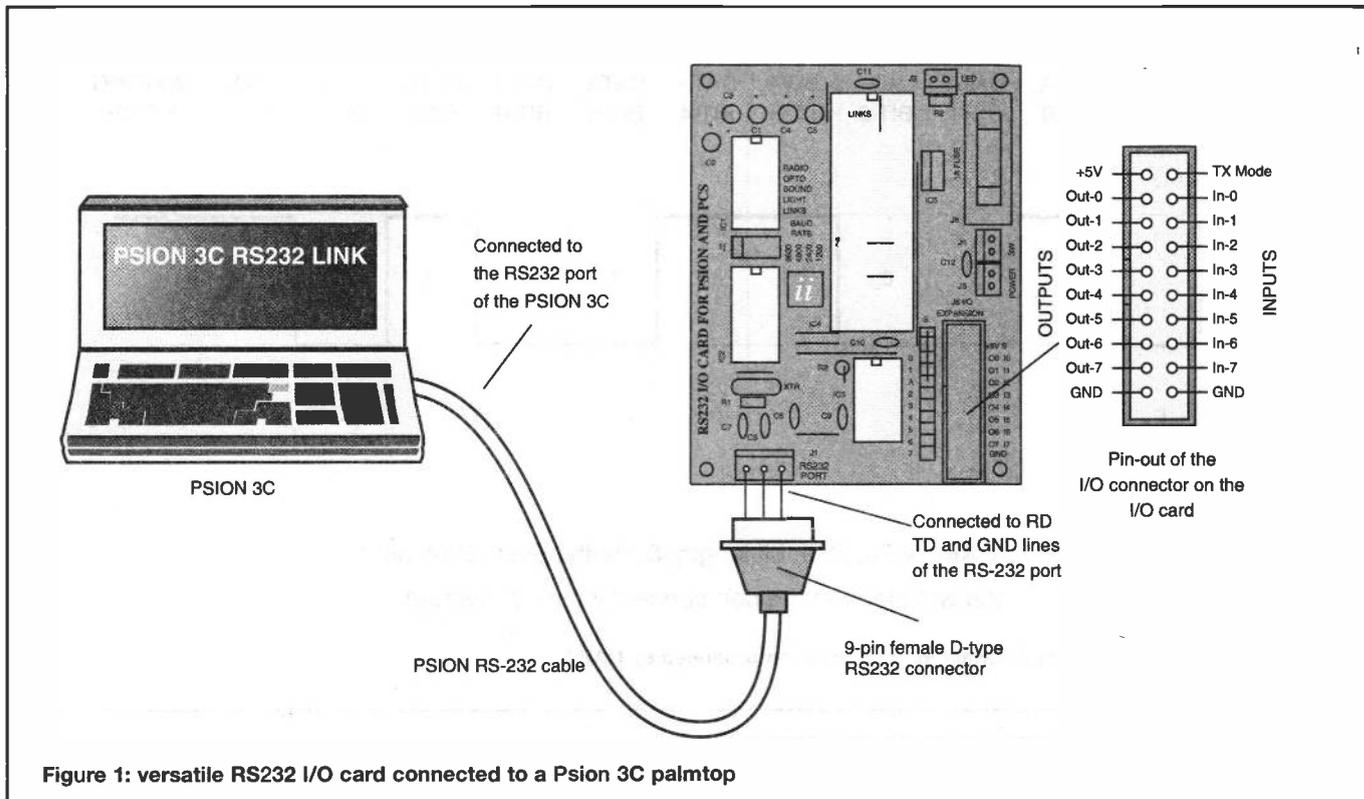


Figure 1: versatile RS232 I/O card connected to a Psion 3C palmtop

23 PINS ON COMPUTER	9 PINS ON COMPUTER	CONNECTOR ON PSION	9 PINS ON PSION CABLE	DIRECTION	SIGNAL	DESCRIPTION
1	-	4	2	OUTPUT	TX	PROTECTIVE GROUND
2	3	8	3	INPUT	RD	COMPUTER TRANSMITS DATA
3	2	8	3	OUTPUT	RTS	COMPUTER RECEIVES DATA
4	7	2	8	OUTPUT	RTS	REQUEST TO SEND
5	8	7	7	INPUT	CTS	CLEAR TO SEND
6	6	5	4	OUTPUT	DSR	DATA SET READY
7	5	15	5	-	GND	SIGNAL GROUND (COMMON)
8	1	nc	1	INPUT	DCD	DATA CARRIER DETECT
20	4	3	6	OUTPUT	DTR	DATA TERMINAL READY
22	9	6	9	INPUT	RI	RING INDICATOR
23	-	6	9	INPUT	DSRC	DATA SIGNAL RATE DETECTOR

Table 1: the pin functions of the RS232 ports on PCs and Psions

should be noted that, for IBM PCs, the voltage swing is from -12V to +12V, while for the Psion the output voltage swing is from -5V to +5V (not -12V to +12V). It can, however, receive an RS232 signal with a swing from -12V to +12V.

### RS232 interfaces on Psion 3Cs and PCs

The RS232 port is a 15-pin male PCMCIA-type connector on the left-hand side of the Psion 3C/Sienna computers. Although it is not a standard version, the pins are the same as those in a standard RS232 port. As mentioned earlier, the voltage swing of the signal line is from -5V to +5V instead of -12V to +12V, but it does accept standard RS232 voltage levels.

A cable is used to connect a Psion 3C/Sienna to an external device. The cable is screened 15-core with a 15-pin PCMCIA female connector at one end and a 9-pin D-type female connector at the other. It can be purchased with the PsiWin software package, or you can make one up yourself (see the construction section). **Figure 3** shows the pin-outs of the RS232 port on the Psion, and of the D-type connector. The RS-232 interface on computers is a 25-pin interface housed in a 25-pin male D-type connector. An abbreviated version is also commonly used on PCs: this is a 9-pin male D-type connector. The pin functions of the connectors are shown in **figure 4**. The pin functions of the RS232 ports on PCs and Psions are summarised in **Table 1**. The signal transmission direction is related to Psion or PC computers.

### Operation of the RS232 port



Data is transmitted from the computer via the TX line, and the computer receives data from external devices via the RX line. Handshake lines are used to manage data flow between the computer and the external device. RTS (active high) is issued by the computer to instruct the external device to prepare for a data transfer from the computer. CTS (active high) is issued by the external device to tell the computer that the external device is ready to accept data. RTS and CTS are used as a handshake for data transfer. DCD (active high) is issued by the external device to tell the computer that it has detected the carrier signal. DSR is generated by the external device to inform the computer that it is switched on. DTR is a signal generated by the computer to tell the external device that the computer is switched on and is ready to communicate with the external devices. DSR and DTR are used to indicate an established connection between a computer and an external device.

A simple communication can be achieved between a computer and an external device using just three lines: TD, RD and GND. This simple communication scheme is the one adopted for the present project - all the handshake lines are not used; in fact, in order to use this scheme, the Psion and PC computers have to disable all handshake functions.
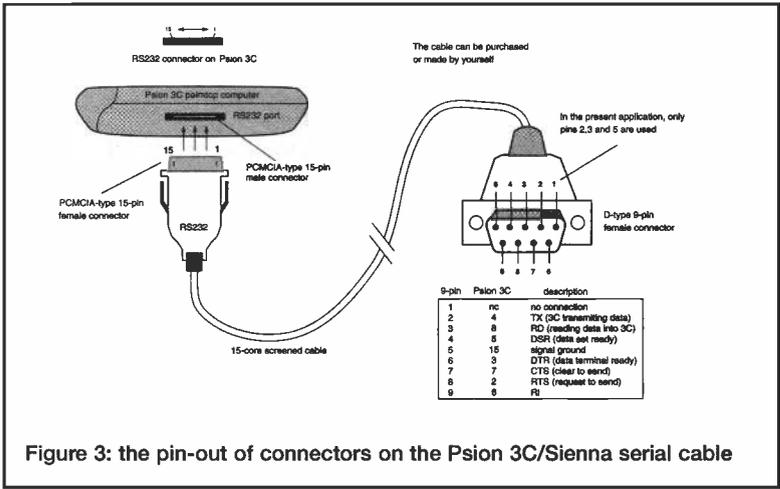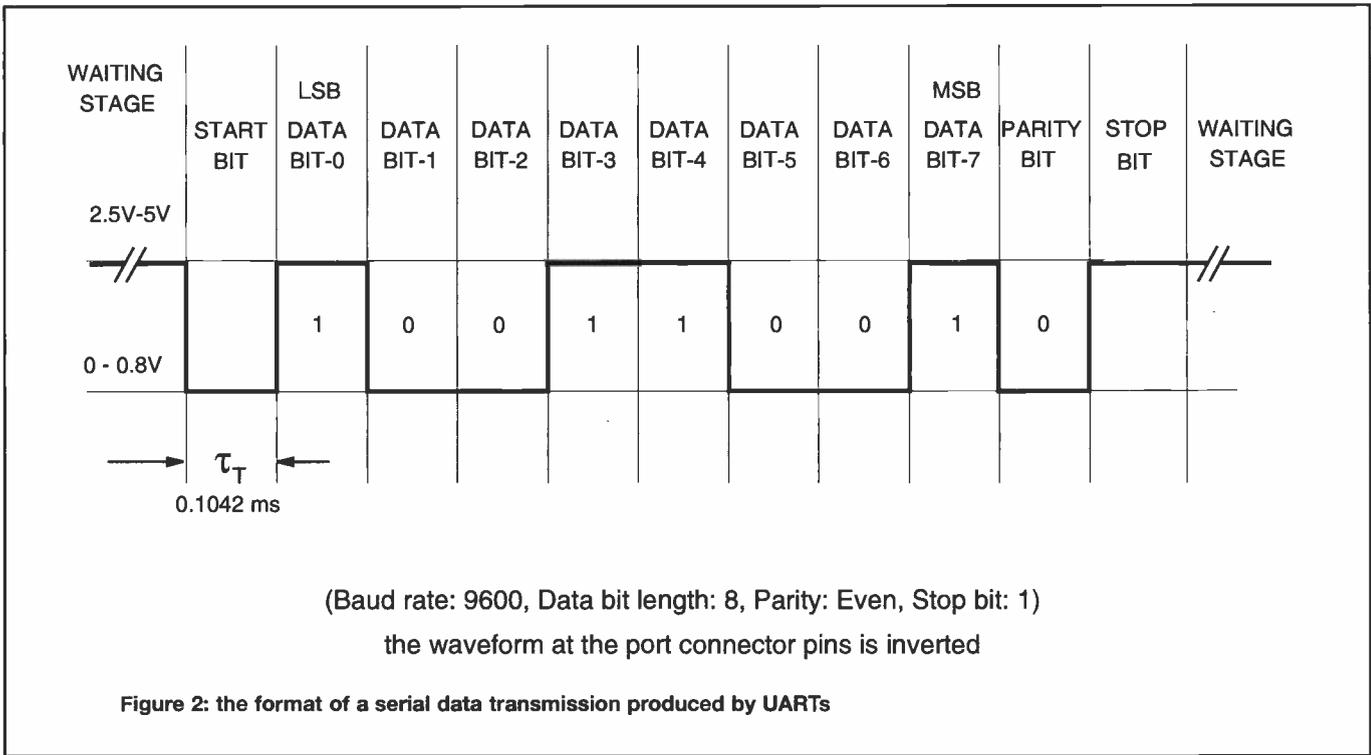
### Hands-on experiments with the Psion 3C

Using a Psion 3C, users can conduct a simple experiment to find out how to use the RS232 port on the Psion 3C and to understand RS232 data transmission. The experimental set-up is shown in **figure 5**. The Psion 3C continuously transmits the same byte from the TX line of the RS232 port. The waveform of the TX signal can be viewed using an oscilloscope. **Figures 5a to f** show the waveforms for output bytes of 0, 1, 2, 64, 128 and 255.

To output data from the RS232 port of a Psion 3C, use the following set-up: at the system screen (press the SYSTEM keypad), press MENU, then select SPECIAL and



```

PROC RS232TX:
REM RS232 output test program
REM communication setting: None or Infrared

REM define local variables to be used in the
program
LOCAL term%, baud%, parity%, data%
LOCAL stop%, hand%, frame%, srchar%(6)
LOCAL err%, dummy%
LOCAL outbyte%

REM open RS232 port
LOPEN "TTY:A"

```

```

REM define RS232 configuration parameters
REM RS232 setting: 9600, 8 bit, no parity,
1 stop, no handshake
baud%=15 : parity[percent]=0 :
data[percent]=8
stop%=1 : hand[percent]=4 : term%=&0
frame%=data%-5
IF stop%=2 : frame%=frame% OR 16 : ENDIF
IF parity% : frame%=frame% OR 32 : ENDIF
Srchar%(1)=baud% OR (baud% * 256)
Srchar%(2)=frame% OR (parity% * 256)
Srchar%(3)=(hand% AND 255) OR $1100
Srchar%(4)=$13

```

COMMUNICATIONS. Next, make sure USE is set to either INFRARED or NONE (not LINK CABLE). This ensures that the series link is used solely by the user's program and is not used by other programs. If the serial port is used by the communication link, an error will appear when you run your program.

After this, you are in full control of the RS232 port from your own OPL program. An OPL program which repeatedly outputs the same byte from the RS232 port is given below. This program first configures the RS232 port to the following specification:

Baud rate: 9600; data bit: 8; stop bit 1; parity: none; handshake: none

Then the program continuously outputs a byte to the RS232 port. The program code must be typed in exactly as it appears here. A detailed explanation of the commands will be given later in the OPL programming section. When the program is running, the waveform of the TX signal can be viewed with an oscilloscope.

PSION 3C OPL program listing, RS232TX:

```

REM configure the RS232 port using the above
parameters
err%=IOW(-1,7,srchar[percent](1), dummy%)

DO
    CLS
    clear screen
    FONT 8,8
    set fonts
    PRINT "INPUT DATA = ",
    INPUT outbyte%

```

# T.I.S.

2 John Street, Larkhall, Lanarks, ML9 1HE  
 Tel: 01698 883334 / 884585 Fax: 884825  
 Send a S.A.E. for your **FREE** Catalogue & Quote.

# T.I.S.

**Unconditional replacement or refund on any item if not as requested**

### TOP SELLING BOOKS

Pract' TV or VCR Repairs-£16.95 (Both £30)  
 Buy/Sell/Serv/Repair Used Equipment :-  
 CD, TV or VCR - £10.95 each (All 3 £27)  
 6 Giant IC Ref' Manuals - £12.95 each  
 Data Ref' Guide - Identifies/ prices/ cross-ref's  
 data for most models - £9.95 (3.5" Disk £5)  
 Microwave Energy & Ovens - £9.95  
 3.5" Disk Drives - £9.50  
 The Giant Fault-Finding Guides:-  
 CTV's £16.95 / VCR's £16.95

### SERVICE MANUALS

#### DESIGNER COLLECTIONS

**Comprehensive Circuits Collections** of any make of CTV as requested, prices from £8 to £49 (IE. Alba/Bush £20) Full list in Free Catalogue.

**Amateur Kit:** 10 Service Manuals (as needed), Data Ref', Pract' TV & VCR Repairs, Radio Repairs, Thorn Serv' Set & any 3 CTV Circ Collections. **£199**

**Professional Kit:** As above + 10 Serv' Man's, Microwave E&O, Buy/Sell/Serv' Collection & 2 More CTV Circ's. **£370**

### 3 UNIQUE SERVICE MANUAL OFFERS GUARANTEED SAVINGS TO YOU NOW!!

**\*LIBRARY** Joining fee £65.00  
 You receive any Service Manuals, no matter how expensive, for £10 each, and you get a £5 credit for any you return.

**\*PRE-PAY MANUALS**  
 You get 20 Service Manuals, as and when you need them, as many or few at a time as you want, for a one-off payment of £185.

**\*SERVICE MANUAL EXCHANGE**  
 If you have a Service Manual we don't have and need another manual (ie. TV for TV, VCR for VCR), we will exchange it for FREE.

**Please add £2.50 to all orders to cover Postage & Handling**

## WORLD'S LARGEST SERVICE MANUAL COLLECTION

*Normal Prices Given (Some Manuals may be Cheaper or more Expensive)*



VCR/VIDCAM - FULL MANUALS £16.50 - CIRCUITS £8.00 COMPLETE  
 CTV's / CD's - FULL MANUALS £12.50 - CIRCUITS £6.00 COMPLETE



**AUDIO, CD, COMPUTERS, MONITORS, DOMESTIC / TEST EQUIP', ETC.. FROM £4.00**

## The Low Cost Controller That's Easy To Use

### Features

The K-307 Module provides the features required for most embedded applications

- Analogue** • 4 Channels in 1 Channel out
- Digital** • 36 Digital in or out & Timers
- Serial** • RS-232 or RS-485 plus I2C
- Display** • LCD both text and graphics
- Keyboard** • Upto 8 x 8 matrix keyboard
- Memory** • > 2Mbytes available on board
- Low Power** • Many modes to choose from

### Development

The PC Starter Pack provides the quickest method to get your application up & running

- Operating System** • Real Time Multi Tasking
- Languages** • 'C', Modula-2 and Assembler
- Expansion** • Easy to expand to a wide range of peripheral cards

### Other Features


Real Time Calendar Clock, Battery Back Up, Watch Dog, Power Fail Detect, STE I/O Bus, 8051 interface, 68000 and PC Interface

## Cambridge Microprocessor Systems Limited



Units 17 - 18 Zone 'D'  
 Chelmsford Road Ind Est  
 Great Dunmow Essex CM6 1XG  
 E-mail cms@dial.pipex.com

**Phone 01 371 875 644**

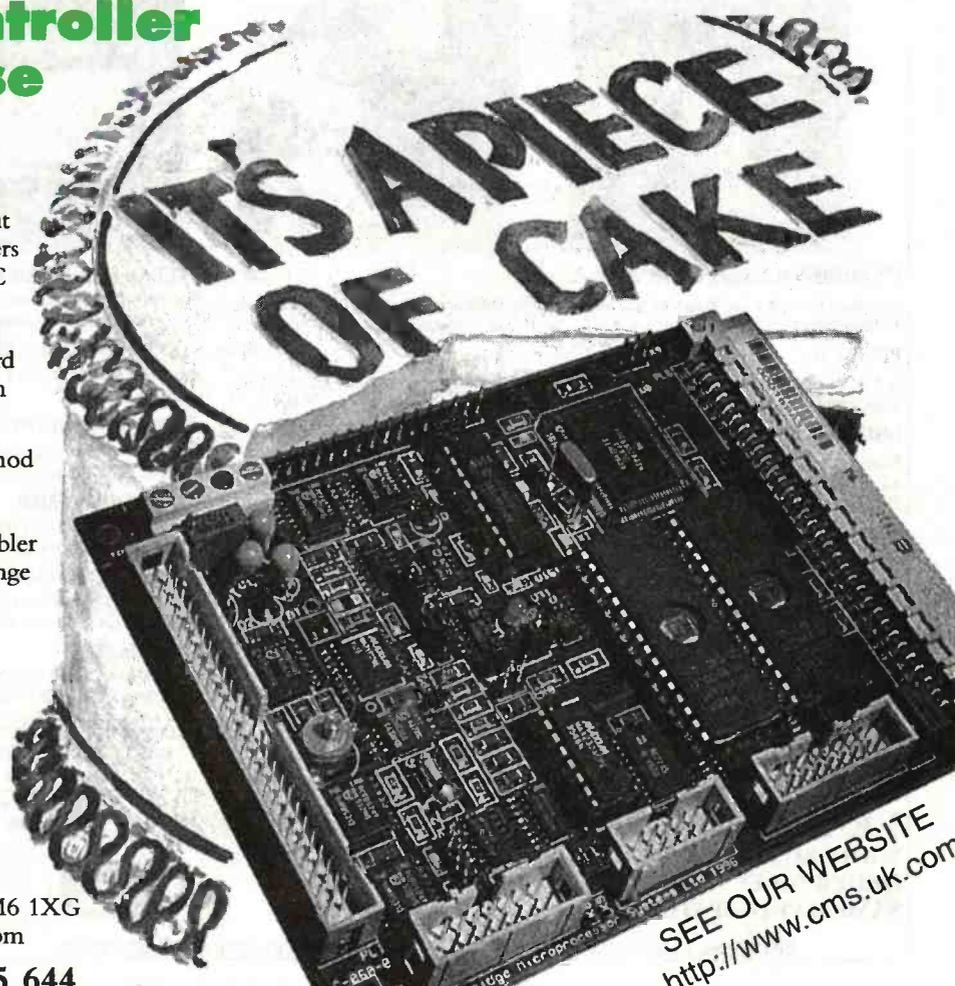

**SEE OUR WEBSITE**  
<http://www.cms.uk.com>

# CROWNHILL ASSOCIATES LIMITED

The Old Bakery, New Barns Road, Ely Cambs. CB4 7PW  
Tel: +44 (0)1353 666709 Fax: +44 (0) 1353 666710

www.crownhill.co.uk  
Sales@crownhill.co.uk

## Colour Brochures

1998 Catalogue available NOW

OFFICIAL DISTRIBUTORS FOR  
**LEADING EDGE TECHNOLOGY**  
PIC DEVELOPMENT TOOLS AND PROGRAMMERS

### PIC DEVICES

New '98 manufacture direct from **MICROCHIP**  
PIC 16C84/04p or I04sm £2.00 each  
PIC16F84/04p or I04sm £2.20 each  
PIC 12C508 & 509 Ip £1.15 each

### SMART CARDS

PIC 16C84/10 £4.50 each  
PIC 16F84 & 24LC16 £9.00 each

### NEW I - PIC PROGRAMMER KIT

PIC 16C84 & F84 development system & programmer  
all components, screen printed PCB, Circuit diagram etc  
\*\*\*\* £10.00 + VAT \*\*\*\*

### GSM SIM CARD EDITOR / PROGRAMMER

Complete system to read and write to all USER and SERVICE PROVIDER areas of GSM SIM CARDS. Available NOW

READ - EDIT & COPY DATA  
create your own **MOTOROLA**

**179.95 + VAT**

## SMART CARD EVALUATION SYSTEM



- Smart Card Reader/ Writer (Programming Interface)
- Smart Card Interrogation System, to identify the commands accepted by any valid SmartCard and log them to disk for evaluation.
- Will allow the user to "re send" known commands and monitor the result.
- Passive interface to allow the user to monitor the data flow between Card and host system.
- 244 page Hard Back reference book, covering all aspects of Smart Card design and programming.

- Sample program to read memory type Phone cards
  - Data on NEW Visa Smart Cards.
  - Sample Smart Cards, Electronic Purse, Credit / Debit card, ID Card
  - **£169.95 + VAT**
  - Other systems available for specific projects, credit / debit, access control, GSM etc etc
- AS SUPPLIED TO POLICE, GOV't & GSM Operators**

Intelligent programmer for Smart Cards using the International Standard T=0 or T=1 protocols also Memory and Secure Memory using I<sup>2</sup>C, 2-wire & 3-wire interfaces. Supplied with software to read and write to most popular secure smart cards, inc GSM, PAY PHONE and ACCESS CONTROL cards.


CALL FOR FULL SPEC + CATALOGUE

T=0 or T=1 @ 3.579MHz  
RS232 @ 9600 -11500 bps  
Internal Supply / Ni-MH  
Size: 100x70x80 mm  
Weight 660 Gram

CE COMPLIANT

**CHIPDRIVE PROFESSIONAL  
SMART CARD PROGRAMMING SYSTEM**  
<http://www.towitoko.co.uk>

**£79.95 + VAT**

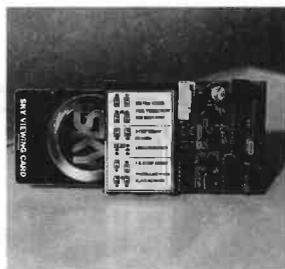

### PIC12C508/9 ICE and PROGRAMMER.

In Circuit Emulator and Programmer. Supplied with Software, Data sheets Manual, leads, 10 breadboard circuits which include DVM, StopWatch, Smoke Alarm, Sound & Light.

### PIC ICE II

In Circuit Emulator for 54/55/56/57/71/84 PICs. A/D emulated for 16C71. Supplied with leads, manual and hardware projects.

### UNIVERSAL PIC PROGRAMMER

Read/Write/Copy PIC's 52, 54+A, 55, 56, 57+A, 58A, 61, 62, 64, 65, 71, 73+A, 74, 83, 84, 554, 558, 620, 621, 622, 14000. 12C508/9. Memory 24C01, 2, 16, 32, 65. Universal ZIF socket, best value on the market. FREE Software upgrades.

### SERIAL EEPROMER

Read/Write all 8 pin Serial EEPROMs. 24, 93, 85 series. 12C, MicroWire etc. Found in Satellite, Digital Dashboards & TVs, Centronics port self powered.

### EPROM EMULATOR

128k by 8 bit or 2 x 64k by 8 bit. Software to Read/Write when connected to target board. CPU's or Car EM Systems.

### PICPOCKET

Standalone D2mac/VC2 programmer, computer not required. Supplied with latest D2mac Code. Runs from 9v Battery


All products manufactured in MALTA and carry 12 months Parts & Labour guarantee.

## LEADING EDGE TECHNOLOGY LTD

WHITE ROSE HOUSE, XINTILL STR, TARXIEN PLA11 MALTA  
ORDER DIRECT: Tel: (00 356) 678509 Fax (00 356) 667484  
SAME DAY DESPATCH

P/P UK. EEC £4.00 NO VAT PAYABLE

ALL MAJOR CREDIT CARDS ACCEPTED

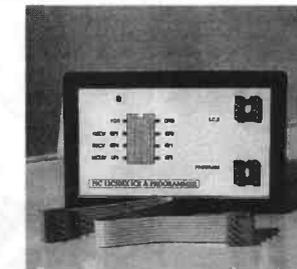

### DELUXE SMARTCARD PROGRAMMER

Read/Write/Copy ALL types of Smartcard ISO, Memory, PIC, GSM, VideoCrypt, Telephone, D2Mac, Mondex etc. Supplied with interesting Card information, and software.

### STANDARD ISO SMARTCARD PROGRAMMER

Read, Program ISO7816 Cards (GSM, VC, Mondex etc). Supplied with ISO card information.

### MEGAPROM EPROM PROGRAMMER

Programs up to 8 Meg devices (32pin), including EEPROM, FLASH and 24X series. Built in Ram tester. Universal quality ZIF socket, free software updates.

### GAL PROGRAMMER

Read/Write/Copy SGS / NSC / Lattice etc 16V8A/B/Z and 22V10NSC standard JEDEC files. Smart case with ZIF. Supplied with PSU, Manual & Compiler software.

### P87/C51/2 PROGRAMMER

Read/Write/Copy all makes of 87C51/2 including ATMEL flash 89 series. Universal 40 pin ZIF. Smart case user friendly.

### CODEMASTER

Hand Held D2mac / VC2 programmer 32 Char LCD screen & Keyboard. Store up to 7 Cards in unit. Supplied with Latest D2mac, VC2 Codes.


ALL PRODUCTS REQUIRE AN IBM PC TO OPERATE UNLESS OTHERWISE STATED.  
FOR FURTHER INFORMATION SEE OUR WEB SITE OR TELEPHONE/FAX.  
<http://LET.cambs.net/> [johnmorr@mail.keyworld.net](mailto:johnmorr@mail.keyworld.net)

We also manufacture **DASH MASTER** the handheld Digital Dashboard tool.  
Always in stock: Blank SmartCards & PICs, Tel/Fax for current prices.




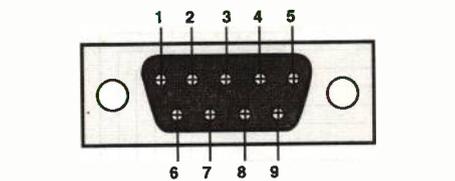DISTRIBUTORS Telephone  
UK CROWNHILL 01353 666709  
SPAIN COELMA 00341 3290523  
FRANCE MULTIPOWER 0033169301379





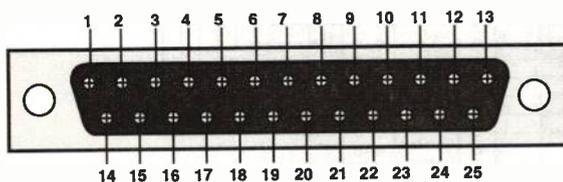(a) 9-pin male socket viewed from the back of the computer



(b) 25-pin male socket viewed from the back of the computer

Pin functions of the RS232 connectors

25 PIN	9 PIN	NAME	DIRECTION (FOR PCS)	DESCRIPTION
1		Prot	-	Protective ground
2	3	TD	OUTPUT	Transmit data
3	2	RD	INPUT	Receive data
4	7	RTS	OUTPUT	Request to send
5	8	CTS	INPUT	Clear to send
6	6	DSR	INPUT	Data set ready
7	5	GND	-	Signal ground (common)
8	1	DCD	INPUT	Data carrier detect
20	4	DTR	OUTPUT	Data terminal ready
22	9	RI	INPUT	Ring indicator
23		DSRD	I/O	Data signal rate detector

Figure 4: pin-out and functions of the RS232 connectors on computers

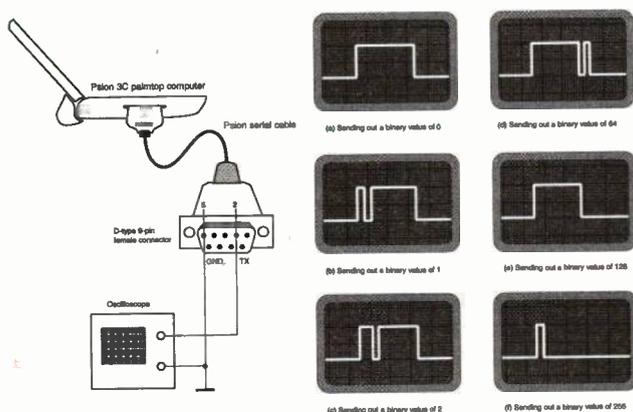


Figure 5: experimental setup and waveforms of TX shown on the oscilloscope when outputting a binary byte from the RS232 port

```

PRINT "TRANSMITTING..."
PRINT "PRESS ANY KEY TO CHANGE NEW DATA"
REM the following commands are repeated
until a key is pressed
DO
REM to output data from RS232 port
LPRINT chr$(outbyte%); REM output
a byte to RS232 port
UNTIL KEY$=CHR$(13 REM if key is
pressed, then stop
UNTIL outbyte%[right arrow]=256

```

## The RS232 I/O card

The circuit diagram of the RS232 card is shown in figure 6. In the diagram, IC1 (MAX232CPE) is the RS232/TTL transceiver; IC2 (CD4060) is the Baud rate generator and IC4 (CPD6402) is the UART. The card is connected to the RS232 interface via three lines: TX (transmit data), RX (receive data) and GND.

## CPD6402 UART

The CDP6402 (Harris semiconductors) is a CMOS Universal Asynchronous Receiver/Transmitter for interfacing to asynchronous serial data channels. It has a programmable serial data format. It can have a length of 5,6,7, or 8 bits. The parity check can be odd, even or none. Stop bits can be 1, 1.5 or 2. The ic requires a power supply voltage of 4 to 10 volts. The quiescent supply current is 1.5 mA for a supply voltage of 5V.

The pin-out and the internal block diagram are shown in figure 7. Pin 21 is the Master Reset (MR), which should be at the logic low state in normal operations. Pins 35 through 39 control the serial data format. To enable the control pins, pin 34 (Control Register Load, CRL) must be at logic high. A high level on pin 35 (Parity Inhibit, PI) inhibits parity generation and check. It also forces the Parity Error (PE, pin 13) pin to stay low. When PI is low, a high level on Even Parity Enable (EPE, pin 39) selects even parity. A low level on EPE pin selects odd parity. Pin 36 (Stop Bit Select) high selects 1.5 stop bits for 5-character format and two stop bits for other data lengths. If it is low, one stop bit is selected. Pins 37 (Character Length Selected, CLS2) and 38 (CLS1) select the data length: CLS1=0, CLS2=0 for five bits; CLS1=1, CLS2=0 for 6; CLS1=0, CLS2=1 for seven bits and CLS1=1 and CLS2=1 for eight bits.

Pins 17 (Receiver Register Clock) and 40 (Transmitter Register Clock) are the clock inputs for the receiver and transmitter. The two inputs are driven by a clock which runs at 16 times the required Baud rate. They are normally connected together.

Pin 20 (Receiver Register Input, RRI) is the serial data input. The received data is stored in the receiver buffer registers which are accessed via pins 5 to 12 (Receiver Buffer Registers). Pin 4 (Receiver Register Disable, RRD) should be low. When a datum is successfully received and loaded into the receiver buffer registers, pin 19 (Date Received) goes from low to high. It can be set to low by making pin 18 (-Data Received Reset) low. This enables the UART to receive the new data. Pins 13 (Parity Error), 14 (Framing Error) 15 (Overrun Error) give the status of errors occurring during a data transmission and they are all high active. To enable these status outputs, pin 16 (Status Flag Disable, SFD) should be low.

Pin 25 (Transmitter Register Output, TRO) is the serial data output. Data to be sent is written into the transmit buffer registers via pins 26 to 33 (Transmitter Buffer Registers). When pin 23 (-Transmitter Buffer Register Load, -TBRL) goes low, the data is loaded into the transmitter buffer registers and when it goes from low to high, it loads the data into the transmitter register and initiates the serial data transmission. Pin 22 is Transmitter Buffer Register Empty. A high level on this indicates that transmitter buffer register has transferred data into the transmitter register and is ready for new data. Pin 24 is Transmitter Register Empty. A high level on this pin indicates the completion of a serial data

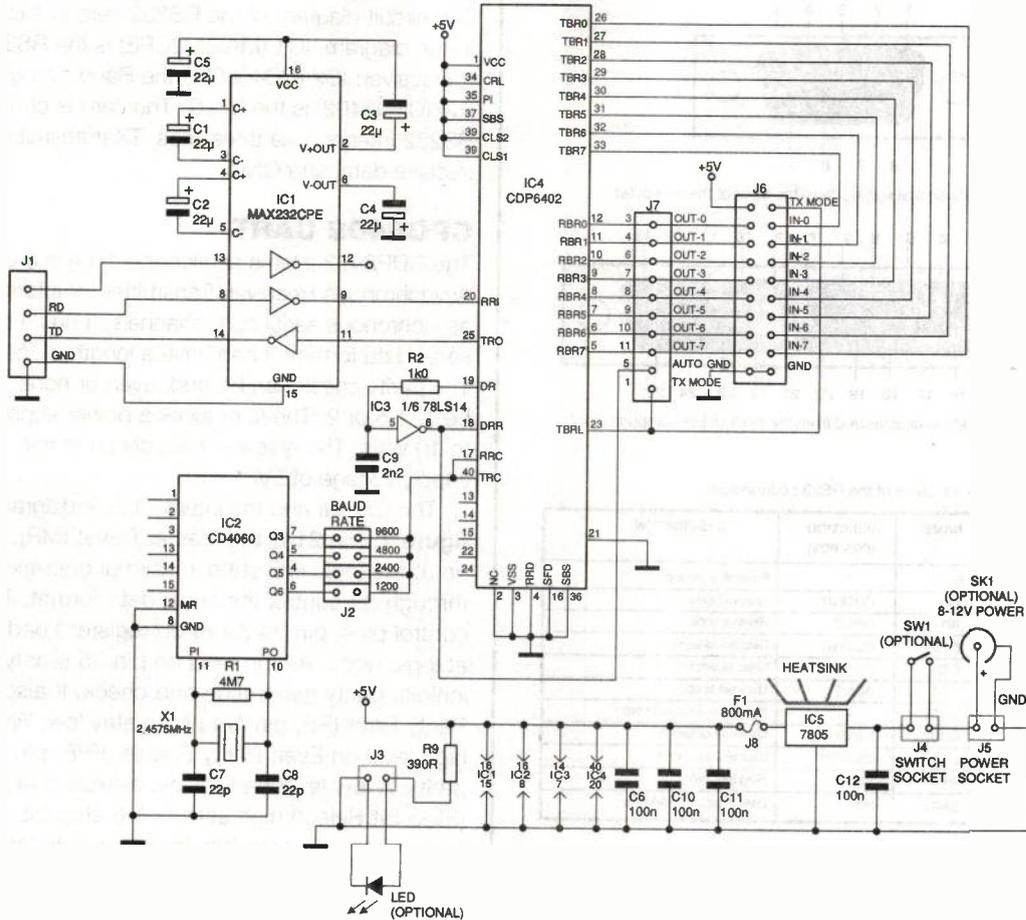


Figure 6: circuit diagram of the TS232 explorer card

transmission.

A receive timing sequence is shown in **figure 8a**. Data is received at the RRI input. When no data is being received, the RRI input must be high. At stage A, a low level on -DDR clears the DR line. At stage B, during the first stop bit of the transmission, the data is transferred from the receiver register to the receiver buffer registers. An overrun error occurs when DR has not been cleared before the present character is transferred to the registers. At stage C, half a clock cycle after B, DR goes high, indicating that a new data is received. A logic high on FE indicates that an invalid stop bit has been received and a logic high on PE indicates a parity error. If the UART operates in a continuous mode, DDR can be pulled down to ground.

A transmit timing procedure is shown in **figure 8b**. At stage A, Data is loaded into the transmitter buffer register from the inputs TBR1 through TBR8 at the high-to-low transition on the -TBRL input. Valid data must appear on TBR1-TBR8 before and after the rising edge of -TBRL. If the data bit length is less than 8, only the least significant bits are used. At stage B, the rising edge of -TBRL clears TBRE. After a short delay, data is transferred to the transmitter register and TRE is low. TBRE goes to a logic high showing that the transmit buffer registers are empty. Output data is clocked out by TRC. The clock rate is 16 times the data Baud. At stage C, -TBRL goes from high-to-low-then-high again. This loads the second data to the transmit buffer register. Data transfer to the transmitter register is delayed until the transmission of the current character is complete. At stage D, Data is automatically transferred to the transmitter

registers and the transmission of the second data begins.

In the present circuit, after the 6402 receives a valid data, DR goes high. The C9 is charged up and the output of the inverter, IC3, goes low. This resets the data receive register and enables the 6402 to receive new data. A low at -DDR also makes DR to become low. For transmitting data, -TBRL should be brought from low to high. -TBRL is programmable on the card using jumper wires. It can be connected to -DDR, OUT-0, OUT-1... OUT7 or other signal sources. If -TBRL is connected to -DDR, every time the 6402 receives a valid datum, it automatically transmits a byte. If it is connected to OUT-0, the 6402 will only transmit data if OUT-0 goes from high to low and to high again.

### Baud rate generator

The clock signal to the UART is generated by a circuit around a CD4060 (IC2) and a 2.4575-MHz crystal. From pins 7, 5, 4 and 6 of IC2, clock signals at 153.6kHz, 76.8kHz, 38.4kHz and 19.2kHz are generated which set a Baud rate of 9600, 4800, 2400 and 1200 for the UART. The Baud rate is selected by a jumper selector J2.

### RS232 driver

The conversion of the voltage levels between the RS232 and TTL is achieved by the MAX232CPD (IC1). This chip requires a single +5V power supply and can produce the right voltage level specified by the RS232 standard.

### Power supply

The power supply incorporates a 7805 (1A, 5V) voltage

1	VCC	TRC	40
2	NC	EPE	39
3	GND	CLS1	38
4	RRD	CLS2	37
5	RBR7	SBS	36
6	RBR6	PI	35
7	RBR5	CRL	34
8	RBR4	TBR7	33
9	RBR3	TBR6	32
10	RBR2	TBR5	31
11	RBR1	TBR4	30
12	RBR0	TBR3	29
13	PE	TBR2	28
14	FE	TBR1	27
15	OE	TBR0	26
16	SFD	TRO	25
17	RRC	TRE	24
18	DRR	TBRL	23
19	DR	TBRE	22
20	RRI	MR	21

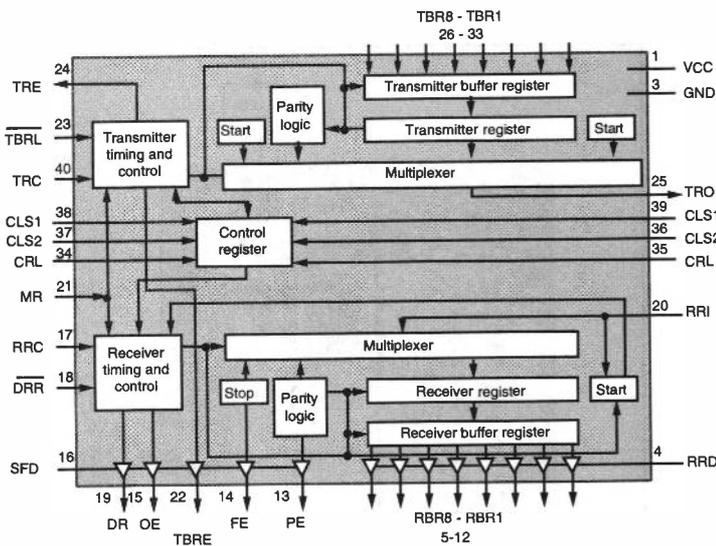


Figure 7: pin-out and the internal block diagram of the 6402 UART

and RX, respectively. Pin 5 is the ground. If the card is to be connected to the serial cable of an IBM PC, pin 2 and pin 3 are the RX and TX. Pin 5 is the ground.

The Psion 3C serial cable used for the I/O card can be constructed by you. You need a 15-pin PCMCIA cable assembly, which is available from CPC. The assembly has a PCMCIA connector which is inserted into Psion's RS232 port. A 9-pin female D-type plug is connected to the assembly at the other end. Although the cable has 15 cores, only three lines (RX, TX and GND) are connected to the D-type connector. The connection details of these three wires are given in figure 10. All handshake lines are left unconnected.

### I/O programming using the Psion OPL

The Organiser Programming Language is a powerful Basic-like programming language: the program is fairly demanding to learn. There are about 260 keywords; on the other hand, the extensive instructions enable users to write sophisticated and professional window-driven programs quite easily. Details of the language are beyond the scope of this article, but they can be found in the programming manual of the Psion 3a.

The demo program listed below is a very simple program which allows user to type in a byte. Then the Psion 3C outputs the byte from the TX line of the RS232 port continuously. After each transmission, the Psion 3C reads data from the RS232 port and displays the data on the screen. Once the basic input and output through the RS232 port is realised, it is up to the reader's imagination to write programs for other applications.

regulator, which requires an 8-12V DC external power supply. The card consumes about 120mA. An 800mA fuse is used to limit the current usage by the external circuitry connected to the card. Figure 6 shows the circuit diagram of the power supply unit.

### Construction

The I/O card is constructed on a single-sided PCB board. The component layout is given in figure 9. Before soldering the components on the PCB boards, a careful inspection of the PCB board must be excised to check if there are unwanted joints or cuts. Soldering may then begin. Components may be soldered onto the board in the following order: links, resistors, diodes, ic-sockets, capacitors, connectors, and so on. After soldering, another careful inspection must be carried out to check if there are some joints due to excessive use of solder and bad soldering points. Then ics can be inserted into the sockets. Before connecting the power supply to the board, check again that all the components are in the right place and the right orientation. This card does not require any adjustment, and should work straight away.

When making the connection from the Psion 3C serial cable to the I/O board, care must be taken to ensure the TX, RX and GND lines are connected correctly. Pin 2 and pin 3 of the D-type connector on the Psion 3C serial cable are TX

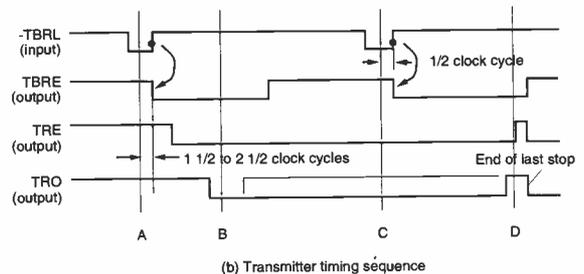
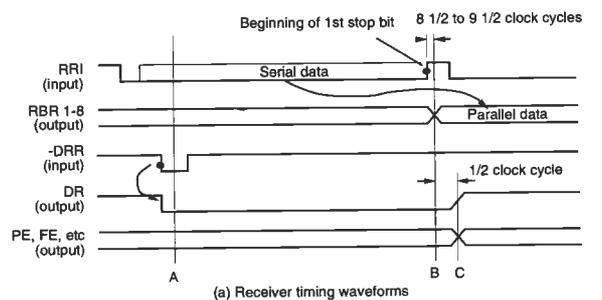


Figure 8: (a) receiver timing sequence and (b) transmitter timing sequence

Psion 3C OPL program list, RS232IOTEST:

PROC RS232IOTEST:

REM PSION 3A OPL test program for RS232 port and i/o port

REM COPYRIGHT to Pei AN

REM communication setting: None or Infrared

REM define local variables to be used in the program

LOCAL term%,baud%, parity%, data%  
 LOCAL stop%, hand%, frame%,srchar%(6)  
 LOCAL d1%, dummy%,err%,ret%,len%  
 LOCAL outbyte%

REM open the RS232 channel

LOPEN "TTY:A"

REM dedine RS232 configuration parameters

REM RS232 setting: 9600, 8 bit, no parity, 1 stop, no handshake

baud%=15 : parity%=0 : data%=8  
 stop%=1 : hand%=4 : term%=&04002400  
 frame%=data%-5

IF stop%=2 : frame%=frame% OR 16 : ENDF  
 IF parity% : frame%=frame% OR 32 : ENDF  
 Srchar%(1)=baud% OR (baud% \* 256)  
 Srchar%(2)=frame% OR (parity% \* 256)  
 Srchar%(3)=(hand% AND 255) OR \$1100  
 Srchar%(4)=\$13

REM configure the RS232 port using the above parameters

err%=IOW(-1,7,srchar%(1), dummy%)

REM PSION output the outbyte% from the port

REM PSION input data

DO

FONT 8,8

PRINT "INPUT NEW DATA ",

INPUT outbyte%

CLS

PRINT "OUTPUT BYTE ",outbyte%

DO

LPRINT CHR\$(outbyte%); REM

output data from PSION

len%=1 REM number

of data read =1

ret%=IOW(-

1,1,d1[percent],len%) REM input data. It only read 1 data

REM and assign the data to d1%

AT 1,3

PRINT "INPUT BYTE ",d1%

REM display d1% which is the data input to 3C via serial port

UNTIL KEY\$=CHR\$(13)

UNTIL outbyte%>=256

BAUD baud %	150 5	300 6	1200 8	1800 9	2000 10	2400 11	3600 12	4800 13	7200 14	9600 15	19200 16
PARITY parity%	none 0	even 1	odd 2								
DATA data%	5 5	6 6	7 7	8 8							
STOP BITS stop%	2 2	1 1									
HANDSHAKING hand%	ALL 11	None 4	XON 7	RTS 0	XON+RTS 3	DSR 12	XON+DSR 15	RTS+DSR 8			
term&	only used when reading data from the port										

Table 2: data for configuring various RS232 ports

ENDP

The 'IOW(handle%, function%, variable1, variable 2)' command is used to provide access to various devices inside the Psion

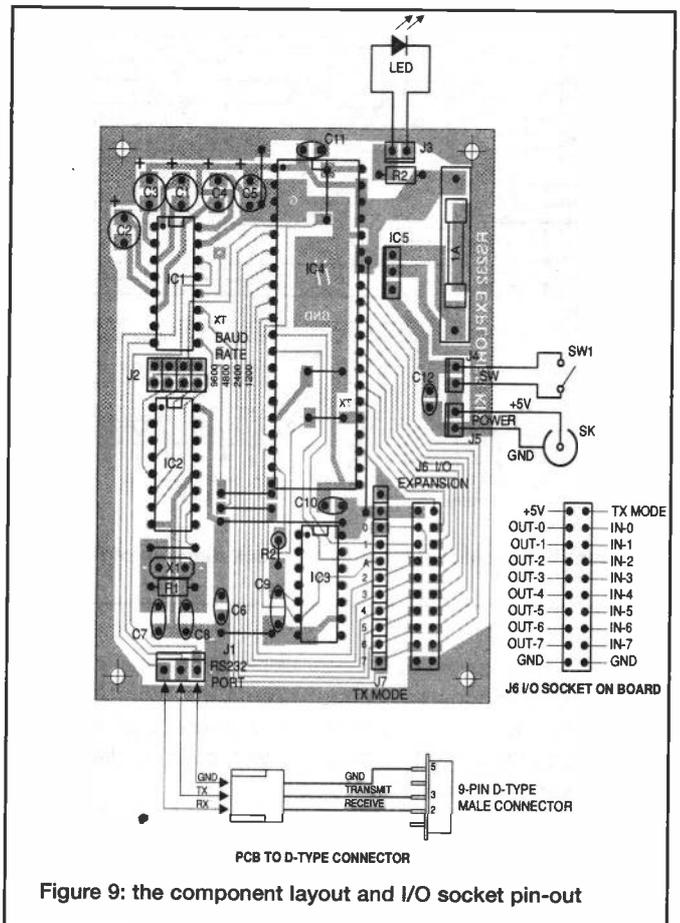


Figure 9: the component layout and I/O socket pin-out

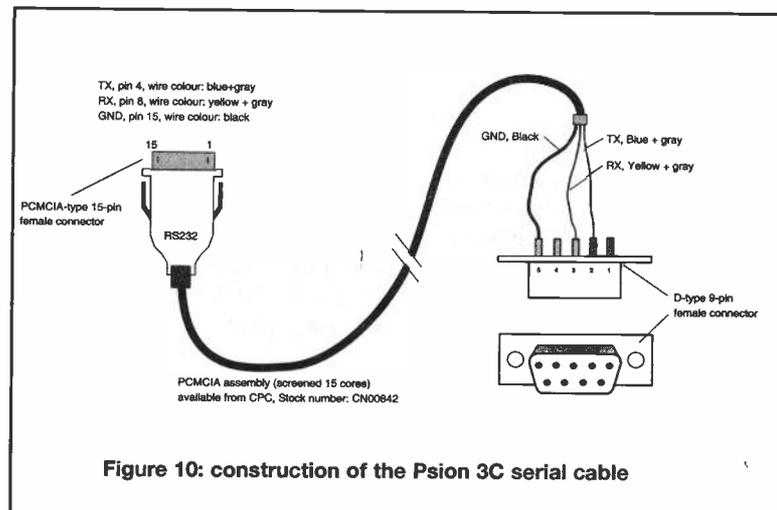


Figure 10: construction of the Psion 3C serial cable

# Video Surveillance



Pinhole Board Camera (B&W) 12v DC, 0.1LUX, 380 TV Resolution  
Size: 35mmx35mm **£35.00**

Pinhole Board Camera (Color) 12v DC, 0.5 LUX, 420 TV Resolution  
2 board foldable  
Size: 40mmx40mm **£190.00**

Audio/Video Transmitter module  
12v DC, 4 Channel Selection  
900MHz-1200MHz, FM Modulation  
**£120.00**



4 Channel Receiver + Switcher  
12v DC, Composite Audio/Video  
Output **£150.00**



TFT 4" Colour Monitor  
12v DC **£150.00**

We also stock:  
Time & Date Generator, Miniature PIR etc.

## Confidential Communications Limited


344 Kilburn Lane, Maida Vale  
London W9 3EF

Tel (44)(0) 181 968 0277 Fax: (44)(0) 181 968 0194

Email: 106075.276@Compuserve.com

osziFOX  
A universal 20 MHz  
storage oscilloscope

**£75**  
Inc.

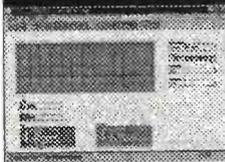

A slimline storage oscilloscope and digital voltmeter with a sampling rate of up to 20 MHz. Inclusive software enables the recorded signals to be displayed simultaneously on a PC screen.

Sample Rates: From 50 ns to 1 ms. Purveyors of Quality  
Input Voltage: 1 V, 10 V, 100 V. Electronic Thingsies at  
Trigger: ±Internal, ±External, Auto. Very Friendly Prices  
Voltmeter: AC and DC.

Supply Voltage: 9 V to 13 V DC, 13 mA, external.  
Trigger, ground, power & serial cables included.

*Nuts*  
*Limited*  
2 Chase Cottages,  
New Road, Aldham,  
Essex CO6 3QT Tel. & Fax 01206 213322

**Also Available:**  
CCD Camera Modules from £60  
Complete CCD Kits, with housing,  
cable and connectors. Ready to run.  
B/W + Audio CCD Kit £85  
Colour + Audio CCD Kit £150  
Please add £2 p&p to all orders.

Mini waterproof TV camera 40x40x15mm requires 9 to 13 volts at 120mA with composite video output (to feed into a video or a TV with a SCART plug) it has a high resolution of 450 TV lines Vertical and 380 TV lines horizontal, electronic auto iris for nearly dark (1 LUX) to bright sunlight operation and a small lens with a 92 degree field of view, it focuses down to a few CM. It is fitted with a 3 wire lead (12v in gnd and video out). Now also available with wall mount tilt and swivel case (at the same price). £93.57 + vat = £109.95 or 10+ £89.32 + vat = £104.95  
Board cameras all with 512x582 pixels 4.4x3.3mm sensor 9-13 volts power supply and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. 47MIR size 60x36x27mm with 6 infra red leds (gives the same illumination as a small torch would) £50.00+vat = £58.75 40MP size 39x38x23mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole. £57+vat = £66.98 40MC size 39x38x28mm camera for 'C' mount lens this gives a much clearer picture than with the small lenses £68.79+vat = £80.83 standard 'C' mount lens F1.6 16mm for 40MC £26.43+vat = £31.06  
High quality stepping motor kits (all including stepping motors) 'Comstep' independent control of 2 stepping motors by PC (Through the parallel port) with 2 motors and software. Kit £67.00 ready built £99.00 software support and 4 digital inputs kit £27.00 power interface 4A kit £36.00 power interface 8A kit £46.00 Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit £23.00

DTA30 Hand held transistor analyser it tells you which lead is the base, the collector and emitter and if it is NPN or PNP or faulty (NEW VERSION does not say FETs & SCRs are transistors) DTA30 £38.34  
HMA20 hand held MOSFET analyser identifies gate drain and source and if P or N channel HMA20 £38.34  
Speaker cabinets 2 way speaker systems with Motorola tweeters

speaker dia	15"	2"	8"
power rating	250WRMS	175WRMS	100WRMS
impedance	8ohm	8ohm	8ohm
frequency range	40hz-20khz	45hz-20khz	60hz-20khz
sensitivity(1W/1M)	97dB	94dB	92dB
size in mm	500x720x340	450x640x345	315x460x230
weight	21.1kg	16.8kg	7.4kg
price each for:			
black vinyl coating	£139.95	£99.99	£54.94
grey felt coating	£159.97**	£119.97**	£64.99

(\* = not normally in stock allow 1 week for delivery)  
Power amplifiers 19" rack mount with gain controls & VU meters  
STA300 2x190Wrms (4ohm load) 11kg £339.00  
STA900 2x490Wrms (4ohm load) 15kg £585.00  
LED's 3mm or 5mm red or green .7p each yellow 11p each cable ties 1p each £5.95 per 1000 £49.50 per 10,000

Rechargeable Batteries  
AA(HP7) 500mAh £0.99 AA 500mAh with solder tags £1.55 AA 950mAh £1.75 C(HP11) 1.2AH £2.20 C 2AH with solder tags £3.60 D(HP2) 1.2AH £2.60 D 4AH with solder tags £4.95 PP3 8.4V 110mAh £4.95 1/2AA with solder tags £1.55 Sub C with solder tags £2.50 AAA (HP16) 180mAh £1.75 1/3 AA with tags (philipsCTV) £1.95 Nickel Metal Hydride AA cells high capacity with no memory, if charged at 100ma and discharged at 250ma or less 1100mAh capacity (lower capacity for high discharge rates) £3.75  
Special offers please check for availability stick of 4 42 x 16mm nicad batteries 171mmx16mm dia with red & black leads 4.8v £5.95

## JPG ELECTRONICS


ETI 276-278 Chatsworth Road,  
Chesterfield S40 2BH  
Access Visa Orders (01246) 211202 fax 550959  
Callers Welcome 9.30am-5.30pm Monday-Saturday

# CONTROL & ROBOTICS

from  
Milford  
Instruments

## 3-AXIS Machine

NEW

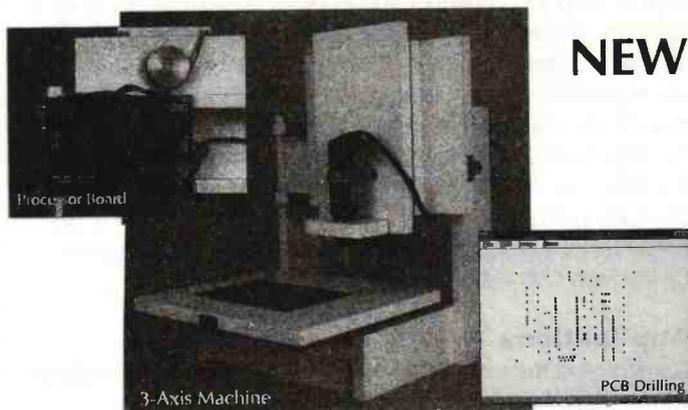

**JUST RELEASED:** This 3-axis machine has been designed for students to explore real CAD/CAM machine control. Based on the popular BASIC Stamp, the user has complete control of all machine functions and interface protocol in easy-to-read PBASIC language. The 3-axis machine is supplied with a standard suite of Stamp2 processor routines and Windows software to drill PCBs using industry standard Excellon drill files.

### FEATURES INCLUDE:

- Powerful 200 Steps/rev drive motors
- 0.1mm resolution in all axes
- 180 x 180 x 160mm working area
- BASIC Stamp Programming Language
- 12v DC Operation
- Easy to assemble from ready machined parts.
- Kits start at only £249.00 plus VAT

For further details of the 3-Axis machine and our other products please call or fax Milford Instruments Tel 01977 683665; Fax 01977 681465  
www.milinst.demon.co.uk

3C. It opens a device driver with handle% and performs the I/O operation function% with two further arguments. The size and structure of these two arguments depend on the requirements of the particular device driver.

When configuring the RS232 port, the handle% is -1, the function% is 7, the first argument is the serial port characteristic parameters group, srchar[percent](1) to srchar[percent](5), and the second argument is dummy%. After running this command, the RS232 port is configured in accordance with the parameters specified by srchar[percent](1) to srchar[percent](5). In the program list above, the srchar[percent](1) to srchar[percent](5) are calculated from input variables: baud%, parity%, data%, stop%, hand% and term%. To find the value for each RS232 characteristic, use **Table 2**.

When reading data from the serial port, handle% is -1 and function% is 1. A terminator mask (term%) may be supplied. This parameter allows users to specify one or more characters to be treated as terminating characters. The number of bytes to be received should be also specified. A reading terminates if a terminating character is received or if the number of bytes read is exactly the number of bytes requested. If term% is not supplied (that is, term%=&0), the 3C terminates only if the number of bytes read into the 3C is exactly the number of bytes requested. In the present application, the input data is a binary data which could be any value from 0 to 255. The terminating character cannot therefore be used. The number of bytes to be received has to be set to 1. Consequently, the Psion 3C only reads one byte a time. Variable1 is the variable which stores the value of the byte read from the serial port. Variable2 is the number of data to be read. Every time, the command is issued, a byte is read from the serial port and is assigned to variable1. You could then process the data. In the above example, this data is displayed on the screen.

### Testing

After soldering, check all the joints and connections to make sure there are no shorts due to excess solder. Do not connect the power supply to the card until you have checked thoroughly that the board is properly constructed. Since the card is simple to construct and involves no adjustment at all, it will work straight away if all the ics are functional and properly located. To test the output of the ports, connect the card to the RS232 port of the Psion or PC via the RS232 cable and run the sample program. A logic probe can be used for testing the logic level of the outputs. If a logic generator is at hand, the input function of the card can be also tested. By connecting the eight output bits to the eight input bits, a loop-back test can be conducted. In this case, the data received by the Psion 3C will be equal to that sent out.

### Applications

Constructing the card and writing a software driver will enable you to understand the RS232 port in depth. After construction, you can use the card for various PC interfacing applications using the powerful Psion 3C palmtop computers.

Eight digital outputs, eight digital input lines and a regulated +5V power supply (800mA) are all available from the I/O expansion socket, J6. A ribbon cable is used to connect the card to your application circuit. Some applications ideas are given below:

A mobile data acquisition system with a PC link (the cable link or infrared); a mobile control system for home automation or

for controlling laboratory experiments; a mobile heart beat monitor and analyser, for example.

### Technical support

All components are available from RS Electromail or Maplin Electronics except the PCMCIA assembly which is available from CPC, Component House, Faraday Drive, Fullwood, Preston PR2 9PP, UK. Tel+44 1772 654455, stock no. CN00842. The Psion 3C serial cable and PsiWin software package are available from Psion dealers. The PCB board is available from the author at a price of £9 and the ready-made Psion 3C serial cable for the I/O card is also available at a price of £16. A kit including all the parts is available from me. Please address enquires to Dr. Pei An. 11 Sandpiper Drive, Stockport, Cheshire, SK3 8UL, U.K. Tel/Fax/Ans: +44 (0)1614779583, e-mail: pan@fs1.eng.man.ac.uk.

## PARTS LIST

## For The RS232 I/O Card

### Resistors

(Metal film, 0.25W 1[percent])

R1	4M7
R2	1k
R3	390R

### Capacitors

C1-C5	22uF electro
C6,10,11,12	100nF ceramic disc
C7,8	22pF ceramic disc
C9	2n2 ceramic disc

### Semiconductors

IC1	MAX232CPE single voltage RS232 transceiver ic
IC2	CD4060 binary counter
IC3	74LS14 Hex NOR gate ic
IC4	CDP6402 UART
IC5	7805 +5V voltage regulator

### Others

Links	0.6 diameter copper wire or similar
J1	3-way PCB connector
J2	4-way dil PCB pins
J3,4,5	2-way PCB connector
J6	20-way PCB dil male connector
J7	11-way PCB sil socket
J8	Fuse holder
F1	800mA fuse
HS	Heat sinks for 7805 power regulator
XTR	2.4575MHz crystal oscillator
	Three-pin PCB connector to male D-type connector assembly
	Psion 3C/Sienna serial cable

### Optional

LED	Standard LEDs
SW	Toggle switch
SK	2.5mm power socket

Maplin: PO Box 3, Rayleigh, Essex SS6 8L.  
Tel 01702 554161.

(RS) Electromail: PO Box 33, Corby, Northants NN17 9EL. Tel 01536 405555.

CPC, Component House, Faraday Drive, Fullwood, Preston PR2 9PP. Tel 01772 654455.

# An opportunity not to miss

Did you know that there is an organisation which has 30,000 research assistants at your disposal?

Members with creative ideas - they've done it - not just talked about it!

Valuable resource information including:

- EMC advice
- Propagation forecasting
- Technical data
- Recruitment adverts

Plus, a comprehensive list of specialist publications and much, much more!

As a member you would receive RadCom, the 100 page colour magazine delivered to your door every month

Who are we?

We are the national society for radio amateurs and if you are interested in electronics we can help you



**Radio Society of Great Britain (Dept ET19) Lambda House Cranborne Road Potters Bar Herts EN6 3JE**  
**Tel: 01707 659015 Fax: 01707 645105;**  
**e-mail: sales@rsgb.org.uk**



## DISTANCE LEARNING COURSES in:

Analogue and Digital Electronic Circuits, Fibres & Opto-Electronics  
 Programmable Logic Controllers  
 Mechanics and Mechanisms  
 Mathematics

- Courses to suit *beginners* and those wishing to *update* their knowledge and practical skills
- Courses are delivered as self-contained kits
- No travelling or college attendance
- Learning is at your own pace
- Courses may have BTEC Certification and Tutoring


For information contact:  
 NCT Enterprises  
 Barnfield Technology Centre  
 Enterprise Way, Luton LU3 4BU  
 Telephone 01582 569757 • Fax 01582 492928


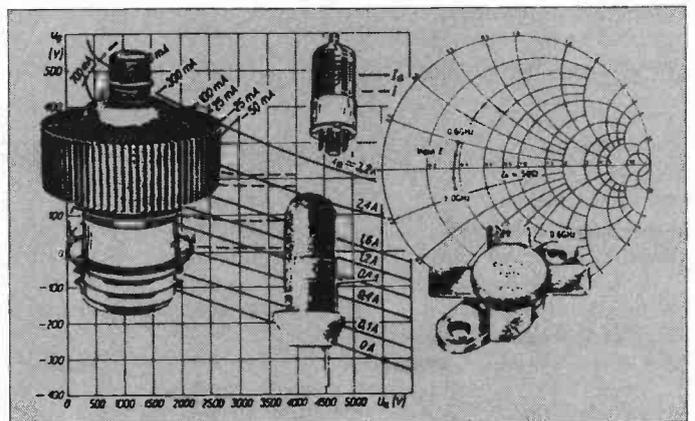
## CHELMER VALVE COMPANY

*If you need Valves/Tubes or RF Power Transistors etc. ...then try us!*

We have vast stocks, widespread sources and 35 years specialist experience in meeting our customers requirements.



*Tuned to the needs of the Radio Amateur*

Chelmer Valve Company, 130 New London Road,  
 Chelmsford, Essex CM2 0RG, England.

**Tel: 44-01245-35296/265865**

Fax: 44-01245-490064

ETI can supply printed circuit boards for most of our current projects - see the list below for boards available. For recent boards not listed, check the constructional article for an alternative supplier.

Please use this order form or a copy of it. Check that all relevant information is filled in, including the Unit Order Code, and that you have signed the form if sending a credit card number. Overseas customers please add postage appropriate to the number of units you are ordering. Make cheques/POs/money orders, in £ sterling only, payable to Nexus Special Interests Limited. Please allow 28 days for delivery. Access/Visa orders may be made on 01442 266551 (ask for Readers Services).

Only boards listed here are available from our PCB Service. For past issues of magazines, copy articles or binders, please see the admin panel (page 74) or contact Readers Services (see below) for information.

Name and Issue of project	Unit code	Price
<b>ETI Issue 3 1998</b>		
Medium Wave Loop	E/398/1	£5.64
AA Cell Eliminator	E/398/2	£7.32
PIC Based Double Bass Tuner	E/398/3	£5.64
5 Range Capacitor Meter	E/398/4	£6.77
MIDI Drum Pads	E/398/5	£5.64
<b>ETI Issue 2 1998</b>		
Smartcam main board	E/298/1	£5.09
Smartcam opto-sensor board	E/298/2	£5.09
Both smartcam boards	E/298/1&2	£7.00
Switched Mode Internal Power Supply	E/298/5	£7.87
Auto Cupboard Light	E/298/3	£5.64
<b>ETI Issue 1 1998</b>		
Control Centre Desk-Top Unit	E/0198/1	£9.99
Control Centre Main Section	E/0198/2	£7.87
<b>ETI Issue 13 1997</b>		
4-Go Rocket Launcher - main board	E/1397/1	£5.64
4-Go Rocket Launcher - relay board	E/1397/2	£6.22
Mighty Midget	E/1397/3	£9.54
<b>ETI Issue 12 1997</b>		
PC Phonocard Reader: ITT Cannon only	E/1297/1	£6.22
Minute Minder	E/1297/2	£13.98
Medium Wave Receiver - RF board	E/1297/3	£11.76
Medium Wave Receiver - Tuning board	E/1297/4	£5.09
Medium Wave Receiver - Audio board	E/1297/5	£5.09
Medium Wave Receiver - PSU board	E/1297/6	£6.77
<b>ETI Issue 11 1997</b>		
Total Harmonic Distortion Meter	E/1197/1	£13.43
Alphanumeric Morse Touchkey	E/1197/2	£5.09
<b>ETI Issue 10 1997</b>		
The IQ Tester	E/1097/1	£5.64
Fake Flasher	E/1097/2	£5.09
DC Motors (Part 2)	E/1097/3	£6.77
Valve Tester - Main Board	E/1097/4	£21.22
Valve Tester - Socket Board	E/1097/5	£5.09
Valve Tester - Heater Regulator	E/1097/6	£5.09
All three Valve Tester boards	E/1097/4/5/6	£30.30
<small>(Due to price breaks there is a small discount on this item.)</small>		
The IQ Tester (previously E/897/2)	E/1097/7	£5.64
<b>ETI Issue 9 1997</b>		
Eprom Emulator	E/997/1	£16.49
The Power Supply	E/997/2	£5.09
Electronic Door Chimes	E/997/3	£5.09
Digital Power Supply	E/997/4	£10.11
<b>ETI Issue 8 1997</b>		
The Brake Light Tester	E/897/1	£5.09

DC Motors (3 experimental boards)		
DC Motors: The first Control Unit	E/897/3	£5.09
DC Motors: The 4046 Circuit	E/897/4	£5.09
DC Motors: The Crystal Drive Circuit	E/897/5	£5.09
All three DC Motors boards	E/897/3/4/5	£11.50

<b>ETI Issue 7 1997</b>		
Eprommer: main board (double sided)	E797/1	£13.32
Eprommer: PSU board	E797/2	£5.64
Eprommer: personality modules (double sided):	E797/3	
Any ONE module board		£5.09
Any two modules		£7.90
Any three modules		£11.85
Any four modules		£15.80
Any five modules		£19.75
Any six modules		£23.70

Please specify which Eprom modules you require. Modules are for 2716, 2732, 2764, 27128, 27256 or 27512. One order code/overseas postal charge applies whether a selection or all six. Personality module boards are provided.

Are Your Lights On?	E/797/4	£5.09
Peak Reading VU Meter	E/797/5	£5.00

#### Terms of trade

Terms strictly payment with order. We cannot supply credit orders, but will supply a proforma invoice if requested. Proforma orders will not be processed until payment is received. All boards are manufactured from the foils that appear in the ETI Foils Pages for the appropriate issue. Please check that our foils are suitable for the component packages you intend to use before ordering as we cannot supply modified boards or replace boards that have been modified or soldered. Boards are only supplied in the listed units. Sorry, we cannot break units. Prices and stock may be altered without prior notice. Prices and stock listed in this issue supersede prices and stock appearing in any previous issue. ETI, Nexus Special Interests and their representatives shall not be liable for any loss or damage suffered howsoever arising but of or in connection with the supply of printed circuit boards or other goods or services by ETI, Nexus Special Interests or their representatives other than to supply goods or services offered or refund the purchaser any money paid in respect of goods not supplied.

**Please supply:**  
Quantity Project Unit Order Code Price Total price

Prices are inclusive of post and packing in the UK. Overseas Post and Packing (if applicable): Add £1 per unit

Name .....

Address .....

I enclose payment of £ ..... (cheque/PO/money order in £ Sterling only) to:

PCB Service, READERS SERVICES DEPARTMENT, Nexus Special Interests Ltd., Nexus House, Boundary Way, Hemel Hempstead, Herts HP2 7ST UK.

Signature: .....

Card expiry date: .....

# Medium Wave LOOP AERIAL

**Intended for the serious listener, Raymond Haigh's inexpensive unit will greatly improve reception on the medium wave band, especially under difficult conditions**

**A** loop aerial is a standard item for the serious medium wave listener. Although the design described here has been prepared with the 'High Performance Medium Wave Receiver' (published in ETI 12 and 13 of 1997) very much in mind, it should work well with most receivers that have provision for the connection of an external aerial and earth. It will also greatly enhance the performance of portables with internal ferrite rod aeriels.

Loop aeriels have been used for medium wave reception since the early days of radio. They fell out of favour for domestic table sets during the 30s and 40s, but the introduction of ferrite materials at the close of the next decade enabled good signal pick-up to be achieved with a very small coil, and loop aeriels wound on ferrite rods became standard fitments.

## Basic design

The most important attribute of the loop aerial is its directional properties; in particular, its ability to null out an unwanted station or interference. This is not very pronounced in loops wound on ferrite rods because of the form and very small dimensions of the coil, and a larger, air-cored loop is required for serious medium wave listening.

Maximum signal pick-up is obtained when the plane of the loop is at right angles to the advancing wave. When the loop is parallel to the wave front, equal and opposing voltages are induced in the loop windings and the output is, in theory, zero.


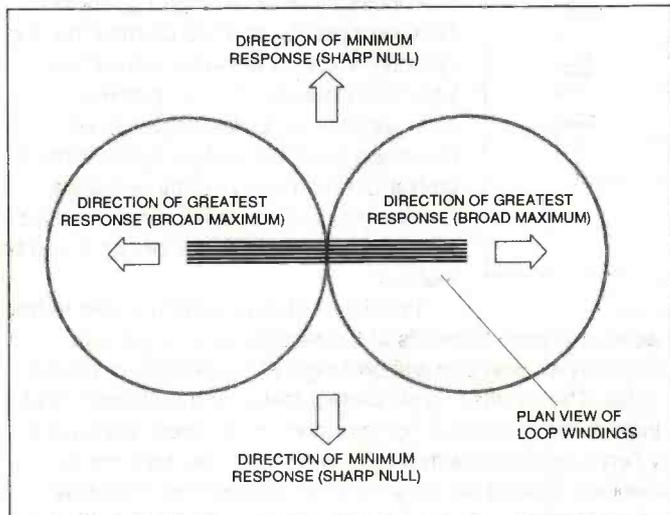


Figure 1: the response pattern of a loop aerial

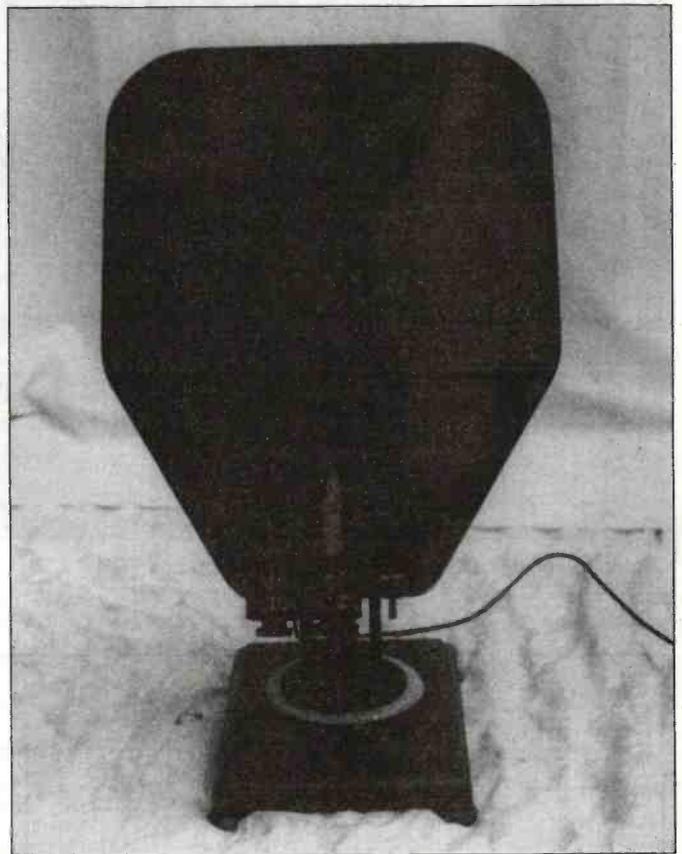


The loop aerial from the front with the case assembled

It is this feature that enables it to null out a signal.


Figure 1 shows the response pattern of a loop aerial. The loop is viewed from the top or side, and it will be appreciated that the setting for a strong response to a signal is quite broad, but the null position is extremely sharp (in practice well within a degree of angular rotation).

Signal pick-up is directly proportional to loop area and the number of turns of wire wound on the loop. Number of turns is, of course, determined by the required frequency coverage, and care must be taken to keep the self-capacitance of the winding as low as possible or the tuning range will be excessively curtailed at the HF end of the band. A widely published loop design consists of six or seven turns of wire, wound to a 10mm pitch on a 1-metre square frame, and tuned by a 500pF variable capacitor.

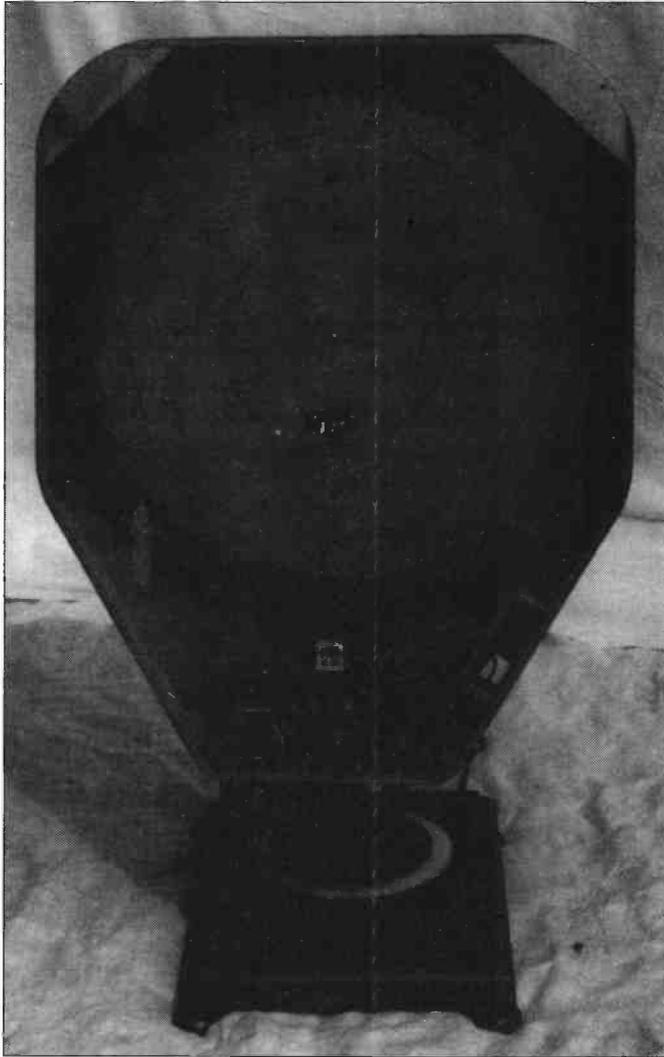An aspect of loop design seldom touched upon is the need for it to tilt as well as rotate in order to obtain the deepest



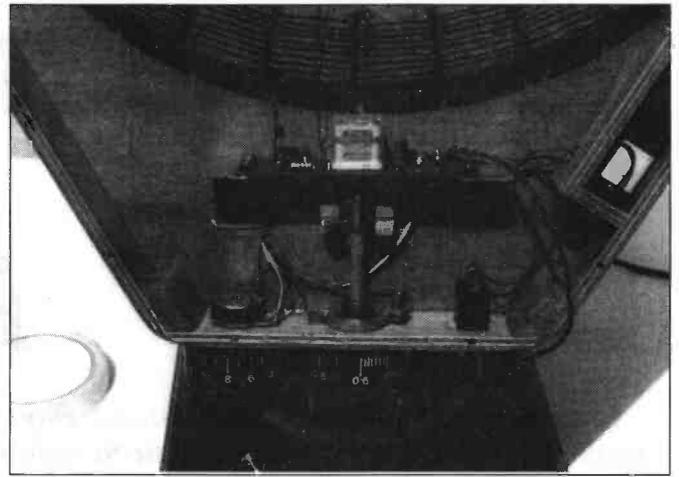The loop aerial from the front showing the loop and PCB assembled



The PCB and switch assembly in the aerial



Detail of the tuning pots mounted on the case

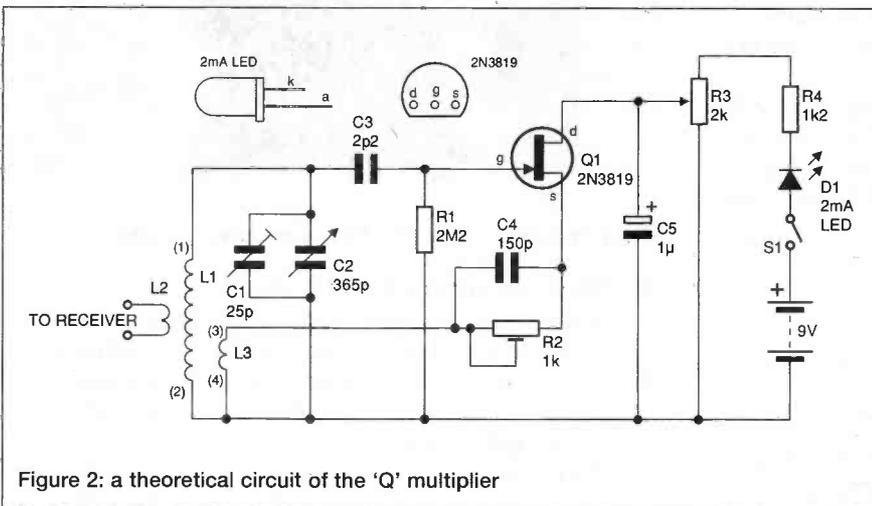


Figure 2: a theoretical circuit of the 'Q' multiplier

possible null. Electromagnetic waves radiated by transmitters reach the receiver by a number of paths: directly (line of sight), reflected up from the ground, diffracted around the earth's surface, and reflected down from the ionosphere. Because of this, the vertical angles the advancing waves present to the loop vary considerably, and the positioning of the aerial in the vertical plane is often as critical as its horizontal bearing when searching for a null. Despite this, few, if any, designs published

for the home constructor incorporate a tilting adjustment.

The sheer size of the standard 1-metre square loop militates against dual pivoting. Loops as large as this are certainly inconvenient to handle and rather out of place in a domestic setting.

Windings can be arranged solenoid fashion or spirally, and it is claimed that the optimum width-to-diameter ratio of the latter improves directivity. In practice, however, little or no difference can be discerned between the two types. What is crucial is the symmetry of the windings (there must be a whole number of turns) if the nulling properties of the device are to be realised.

Traditionally, loops are connected to the aerial and earth terminals of the receiver via a single turn coupling winding and a short length of twisted flex or coaxial cable. This results in an imperfect match to the 50 ohm input impedance of modern communications receivers, particularly when a large loop with a main winding of only six turns is involved. Field effect transistors, configured in a differential amplifier circuit, are sometimes used to make the energy transfer more efficient. While some designers claim that this





The stand before the rotating column, aerial case and counterweight are mounted

main winding, L1, is tuned by variable capacitor C2. An integral trimmer, C1, sets the upper limit on the HF coverage. Field effect transistor Q1 buffers the signal voltage across the resonant circuit and feeds a portion back, in phase, via the single-turn feedback winding L3. This positive feedback, or regeneration, enhances the 'Q' of the tuned circuit and signal magnification and selectivity are very considerably increased. Full control over the amount of feedback, from zero to the point of oscillation, is provided by potentiometer R3, which varies the voltage on the drain of Q1. Smoothing capacitor C5 eliminates potentiometer noise.

A low value coupling capacitor C3, together with C4 and R2, ensure that the action of the 'Q' control is smooth and completely free from backlash. The value of C4 has been determined experimentally to ensure that its setting is as constant as possible over the full swing of the tuning capacitor. R2 is pre-set to suit the characteristics of the particular FET used, and its adjustment is not critical.

Equipment of this kind can be inadvertently left switched on, and low-current LED, D1, makes use of the current flowing through the 'Q' control potentiometer chain to provide a visual indication. Series resistor R4 sets the voltage across the potentiometer. On/off switch S1 controls the 9V supply.

The loop and associated circuitry are completely 'floating'. Connection to the receiver is via the single turn coupling loop L2.

## Components

The only item requiring comment is the tuning capacitor. A component with a low minimum capacitance (not more than 10pF) and a maximum capacitance of at least 365pF is needed to secure full coverage of the medium wave band. An inexpensive Toko polyvaricon solid dielectric variable is fitted in

the prototype unit. With one of its FM and one of its AM gangs connected in parallel, a 10 to 365pF swing is achieved.

Trimmer capacitor C1 is integral with this unit, which is retailed by Cirkit, who supply a suitable extender for the short spindle.

Front-end 'Q' multiplying circuits can be microphonic when critically adjusted, and the solid dielectric in the Toko capacitor inhibits this tendency. (The prototype unit did not display any problems of this kind.)

The remaining components and construction materials are widely available.

## Construction

Details of the loop are given in Figure 3 and the photographs. A 380-mm diameter hardboard or MDF disc supports the windings. Cut 33 radial slots, each 25mm deep, around the circumference to accommodate L1. (The slots are spaced a trifle less than 11 degrees, and 'tight' setting out to this angle should result in even spacing).

Drill 1-mm diameter anchor holes at the top and bottom of one of the slots, and wind on 18 turns of 22 SWG enamelled copper wire, weaving it 'in and out' of the slots, basket fashion. Keep the turns tight and space them as evenly as possible. This form of winding is necessary in order to separate the turns and reduce the self-capacity of the coil, and an odd number of slots must be cut to produce the basket-weave effect.

Draw an inner concentric circle, 70mm in diameter, and drill twelve, 1-mm diameter holes around its circumference. Thread 22 SWG enamelled wire 'in and out' of these holes to produce the coupling winding L2.

Draw a 130-mm diameter circle, drill eighteen 1-mm diameter holes and repeat the process to produce feedback winding L3.

Drill a 6-mm diameter hole for the output leads, close to the ends of L2, and mount a three-way tag strip over it. Solder the ends of L2 to the outer tags.

## Spacing the turns of L1

The upper frequency limit of the medium wave band is usually taken as 1600kHz. However, in Europe, Africa and the near and Middle East, transmissions extend up to 1620kHz. Australia boasts low powered transmitters working at 1720kHz, and stations in the USA have, fairly recently, begun to operate at frequencies up to 1700kHz. In the UK, cordless 'phones use channels between 1600 and 1700kHz. Notwithstanding the possibility of interference from this allocation, it is clearly desirable to extend loop coverage up to 1700kHz.

This can only be achieved by carefully spacing the turns of L1 in order to reduce the self capacity of the winding. Using the tip of a small screwdriver, ease the winding segments on both sides of the disc apart, and take care to ensure that adjacent turns don't touch where they cross in the slots. Half an hour spent on this task increased the HF coverage of the prototype coil from 1600 to 1750kHz.

Apply ribbons of Durofix or some similar general-purpose tube glue across the turns to keep them in place.

## The 'Q' multiplier.

Most of the components, including the loop tuning capacitor, are mounted on a small PCB. The layout of the component side of the board, and details of the off-board wiring, are given in Figure 4. Vero pins inserted at the lead-out points will ease the task of off-board wiring.

**Resistors**

- All 0.25 watt, 5 percent or better
- R1 2M2
- R2 1k linear preset
- R3 2k linear potentiometer
- R4 1k2

**Capacitors**

- C1, C2 Toko polythene dielectric variable with integral trimmer (see text).
- C3 2p2 ceramic
- C4 150p ceramic
- C5 1u radial electrolytic

**Semiconductors**

- Q1 2N3819 field effect transistor
- D1 Low current (2mA) LED

**Miscellaneous**

100g reel of 22 SWG enamelled copper wire for the loop windings, PCB materials, Vero pins, hook-up wire, and screened twin cable. LED holder and battery connector. PP3 battery. Toggle switch. Spindle extender for tuning capacitor, spindle coupler, 50mm of 6.3mm plastic spindle and reduction drive. Two control knobs. Three-way tag strip. Hardboard or medium density fibreboard, plywood and blockboard for loop former, case and stand. Length of 25-mm dowel or broom handle. One large circular and one small semicircular protractor. Glue, screws, pins, bolts, nuts, wing nuts, washers and finishing materials.

**Initial testing**

Loop and 'Q' multiplier can be tested before being mounted on a stand. Check the PCB for bridged tracks and poor soldered joints, and check the orientation of D1, TR1, C1 and C2, and C5. If all is in order, set R2 to half-travel and connect up a fresh 9V battery. Current consumption should be around 3mA.

Connect the loop to the PCB and prop it in a vertical position. Connect L2 to the receiver with a short length of twisted flex (not much more than 1 metre), and tune the receiver to a station around the centre of the dial. Set C2 to resonate the loop at the same frequency.

Switch on the 'Q' multiplier and advance R3. The increasing selectivity will expose any inaccuracies in the setting of the tuning capacitor, and it may have to be adjusted slightly to peak the output from the loop. Gently advance R3. If the transmission is reasonably strong, the 'S' meter pointer should be moving across the scale now. Band noise should reduce, then the upper audio frequencies will disappear and, finally, the audio will become muffled just before the onset of oscillation.

Set R2 to the highest possible resistance consistent with 'Q' control R3 being able to just bring the system into oscillation at any setting of the tuning capacitor. Six different specimens of 2N3819 were tried in the prototype. All enhanced the 'Q', but one failed to oscillate with the component values shown. If advancing R3 produces no increase in loop output, check that L3 has been connected, as shown, to inject positive feedback.

**Tuning and hand-capacitance**

The initial test will reveal that loop tuning is critical when the 'Q' multiplier control is well advanced, and the tuning capacitor must be fitted with a reduction drive. Most loop aerals are prone to hand-capacity effects, but this unit is comparatively free from problems of this kind. An insulated extension (40mm waste cut from a plastic potentiometer shaft), fitted to the tuning capacitor, almost eliminates the effect, even when 'Q' is


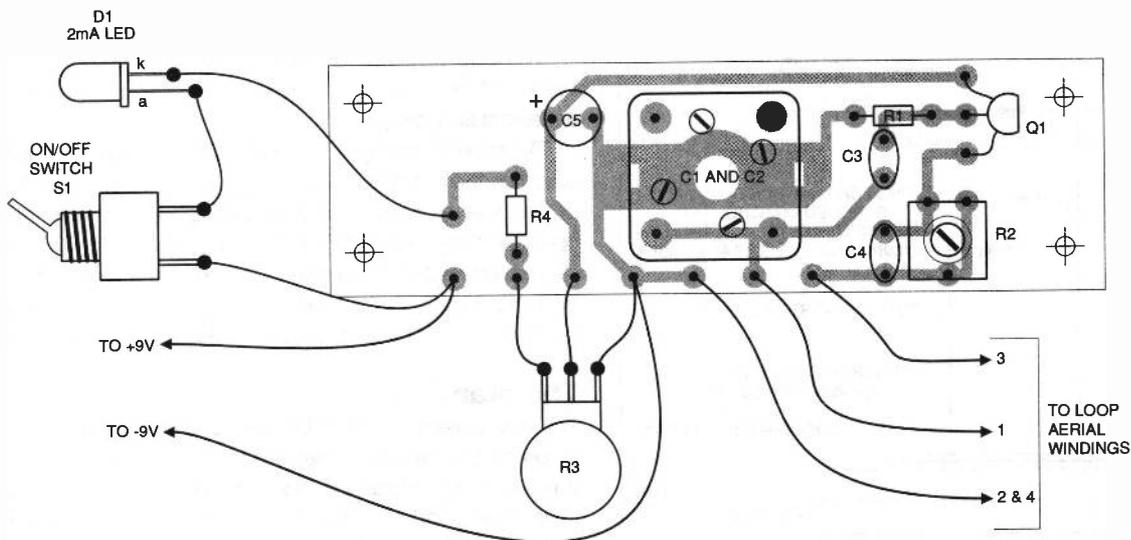


Figure 4: the component layout of the PCB, and the offboard wiring

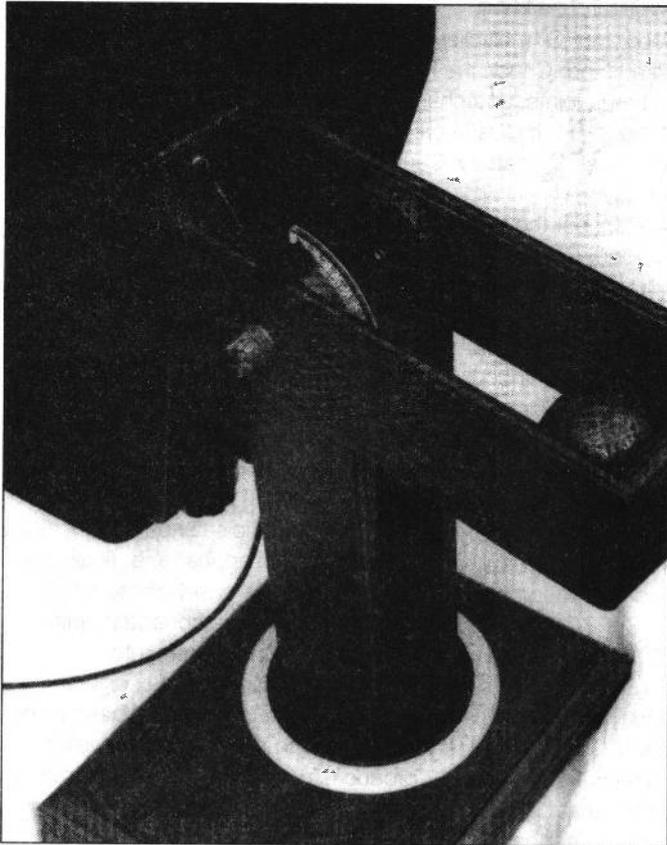

The aerial mounting used on the prototype, showing the angle adjustment and the counterweight

set high. Any residual traces when the loop is tuned to the HF end of the band can be eliminated by earthing the metal reduction drive and the case of the 'Q' control potentiometer.

NB: no other parts of the loop or its circuitry should be earthed, or its performance will be impaired. The centre contact on the lead-out tag strip can be used to anchor the earth wire, and the earth connection made via the screening braid of the cable between loop and receiver.

### Simple loop mountings

The loop cannot be used without an adjustable mounting. The method adopted will depend on the time and resources of individual constructors. It need not be complicated. A 50 x 50-mm softwood post, screwed to a 250 x 250-mm blockboard or chipboard base, and free to rotate, will act as a vertical pivot. The loop disc can be attached to the top of this post by a stiff hinge to provide a means of tilting it.

The 'Q' multiplier PCB, the various controls, and the battery must be mounted as close as possible to the loop and be rigidly fixed to it. A metal or plastic box could be used to house these parts, and it could be slung just beneath the loop on plastic or wooden battens. If a metal case is used, it should be earthed.

This basic arrangement was adopted for the initial testing, and it worked tolerably well. It soon became clear, however, that in order to make the most of the loop's potential, and maximise the pleasure of using it, a more elegant mounting is required.

### Case construction

Figures 3, 5 and 6, and the photographs, show how the prototype loop is housed and mounted. A little more time and effort (but very little cash) will be required to duplicate these arrangements, and no doubt individual constructors will have some excellent ideas for improving on them. Bearing in mind that the only comparable commercial loop (which is somewhat smaller than this unit) retails in the UK for around £350, the extra time and effort spent on these refinements is worthwhile.

### The loop case

The loop case consists of a hardboard tray with 35-mm deep plywood sides. Back and sides are glued and pinned together: the front is held in place by screws to facilitate access. Softwood blocks permit the rounding of the corners, and the lower end is extended and tapered to accommodate the PCB and controls.

The loop is spaced off the back of the case by four softwood blocks, 15-mm thick, and a compartment for the battery is accessed from the rear.

Because the loop sometimes has to be rotated away from the operator, the controls are best brought out through the lower end of the case rather than the front. Arranged in this way they can be operated fairly easily with the loop in any position. Dials are useful rather than essential. On the prototype, these were made from thick discs of ply cut out with an electric drill-powered hole-saw. Lids from small tins or jars would probably serve just as well.

### The stand

The vertical pivot needs to be elevated if the loop is to rotate smoothly and without judder. It is formed at the top of a length of 25-mm dowel or broom handle, which is glued into a substantial base. A plywood box column is pivoted on, and rotates around, the dowel. Use a bolt for the top pivot, and form the hole for the bottom bearing around the dowel with the hole saw. (This tool can also be used to form the dowel hole in the base.)

Some form of counterbalancing is required for the loop case, and a horizontal arm, comprising another box member, carries the

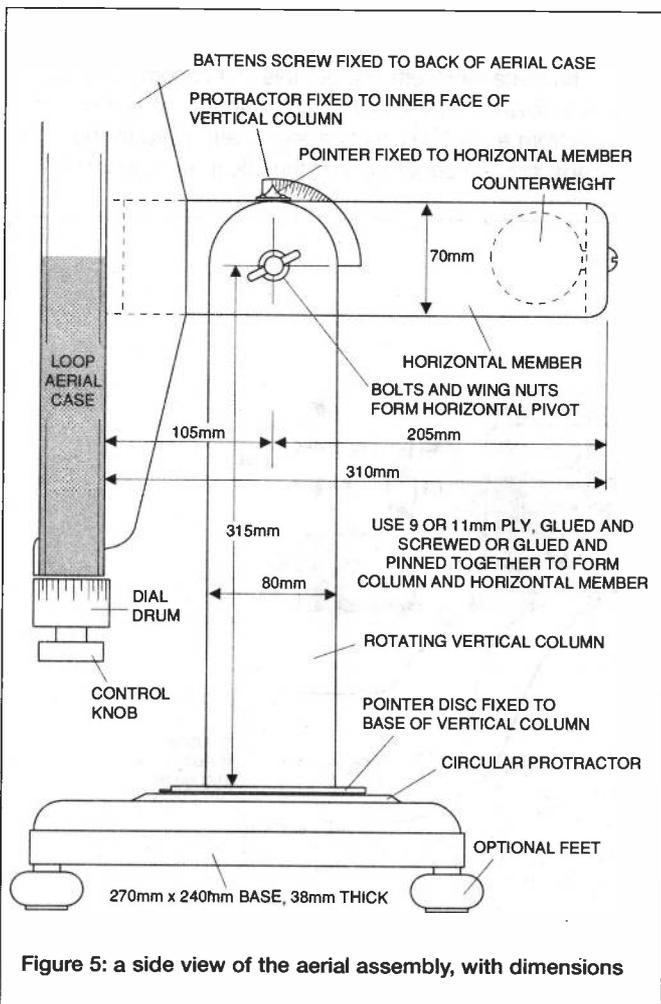


Figure 5: a side view of the aerial assembly, with dimensions

loop at one end and a counterweight at the other. Two bolts pivot the arm at the top of the column, and wing nuts control the friction of these bearings. Tapered battens strengthen the fixing between the arm and the back of the loop case. A burnt out mains transformer or a tin filled with scrap lead will act as a counterweight. (An old iron ball was used in the prototype. Located at a distance of 300mm, the mass of metal did not affect the performance of the loop.)

Some means of measuring the horizontal and vertical position of the loop is helpful. Fix a circular protractor to the base and a hardboard pointer disc to the underside of the rotating column. There must, of course, be a millimetre or so clearance between protractor and pointer disc. Fine adjustment of the clearance can be made by placing washers on the top pivot bolt. If the centre of the protractor is drilled or cut so that it can rotate around the dowel or another hardboard disc, it can be set with 0 degrees pointing north to make bearing calculations easier.

Cut a semicircular protractor into two quadrants and sandwich a slip of paper between the pieces to produce a readable means of measuring the tilt angle. This is fixed at the rounded top of the rotating column, and a pointer is secured to the horizontal arm.

Plywood for the column, arm, and battens should be at least 9mm thick, and parts should be glued and screwed, or glued and pinned, together.

### Finishing the case

The loop case, plywood dials and hardboard pointer disc were sprayed satin black with car paint. The stand parts were stained and French polished, but a few coats of clear satin varnish would have served just as well. The tuning dial is best calibrated, after the final setting up process, by matching it to the receiver dial. Rubdown transfers were used to annotate the dial and form the pointers.

### Connecting the loop

For best results, link the loop to the receiver by means of twin screened cable. The cable's inner cores connect the ends of the coupling coil L2 to the floating input on the 'High Performance Medium Wave Receiver', or to the aerial and earth terminals on other receivers. The outer screen is connected to earth at the receiver.

The loop has been checked out on a high performance communications receiver with an unbalanced 50ohm input, and it worked well. Damping caused by the low input impedance did not inhibit the operation of the 'Q' multiplier. Experiments with impedance matching transformers wound on dust iron toroids did not reveal any discernible improvement over the direct connection of the coupling loop.

Portable receivers should be placed in close proximity to the loop with the coils on their internal ferrite rods parallel to it. Small portables can be rested inside the counterbalance arm.

### Using the aerial

Loop tuning must, of course, be kept in step with main receiver tuning, and the 'Q' multiplier control is best switched off while band browsing in order leave selectivity as wide as possible. When using the loop, always switch any aerial attenuators out of circuit.

It will be found that perfect nulls cannot be obtained on all signals (the BBC and commercial operators transmit the same programme material, on the same frequency, from a number of locations). Careful adjustment of the horizontal and vertical bearings of the loop will, however, usually result in a deep null when the signal is being received from a single source, and the drop of the 'S' meter pointer will be sudden and pronounced.

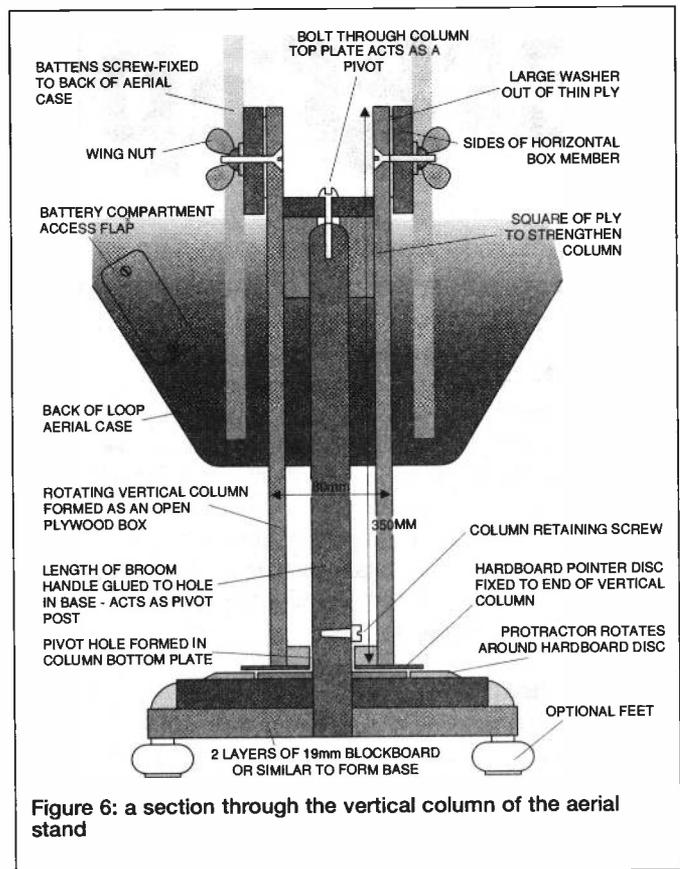


Figure 6: a section through the vertical column of the aerial stand

Local electrical interference and interference from different stations on the same or adjacent channels can usually be nulled out, and this is the loop's main virtue. Sometimes, nulling out a strong signal will reveal a more distant station operating on the same frequency.

Selectivity is greatly increased by advancing the 'Q' multiplier control, and bandwidth can be reduced to the point where the signal loses intelligibility. A slight shifting of loop tuning then enables clear reception to be obtained from one or other of the transmitted side bands. This sometimes improves reception under difficult conditions. Reducing bandwidth also improves the signal-to-noise ratio.

Signal magnification, that is, loop output, is greatly increased when the 'Q' control is advanced, and weak signals can be lifted right out of the noise. When a station has been accurately tuned in, operation of the 'Q' multiplier control is extremely smooth, completely free from back lash, and has no perceptible effect on the setting of the tuning control.

When 'Q' is turned up, the loop will 'pull' the tuning of portables and simple receivers (that is, the loop, not the receiver, will determine, within narrow limits, what station is received).

Don't operate the loop in close proximity to computers, television receivers, fluorescent lights and other sources of radio interference. In this connection, it should be noted that the digital circuits driving the frequency displays of some communications receivers can radiate quite strong interference. (The internal circuits of the receiver are appropriately screened.) Bringing the front panel of the receiver close to the loop will expose any problems of this kind. Sometimes the arrangement of house wiring and metal conduits in the vicinity of the loop will impair its nulling properties. If this is suspected, try the loop in another room or, better, in the garden.

A compass to set the bearing protractor and conventional and great circle maps will assist in seeking out and identifying stations.

# Bargraph Module

**Terry Balbirnie continues a series of adaptable circuits for GCSE projects with a voltage-sensitive Bargraph module based on the LM3914 display driver**

**I**n this series we are describing some electronic modules that will be useful to students of GCSE Technology and those following similar courses at school or college. The circuits may be used as a basis for practical projects.

All the designs are given as a circuit diagram and a stripboard (Veroboard) layout. Details such as what the circuit is to be used for and how it will be built into a box are left for you students to apply to your needs.

## Drawing a graph

This month we shall describe a Bargraph module. This responds to a voltage applied to its input, and lights up one of a row of LEDs according to the value of this voltage. The sensitivity is adjustable using a preset potentiometer on the circuit panel. The most sensitive setting is 0.125V per LED - that is, it requires 0.125V to light the first one, 0.25V for the second and so on up to 1.25V for the last. With the component values stated, the least sensitive setting corresponds to about 3V per LED - that is, the first one operating at 3V and the last one at 30V.

The display used in the prototype was a commercial package consisting of ten LEDs arranged in the form of horizontal bars, so that a small voltage will light up the first bar and increasing voltages will light up successive ones. It would also be possible to use separate LEDs. This would involve a lot more building work, but it would have the advantage that different colours could be used, so that the first LEDs to light could be green, followed by yellow, orange and red (for example).

The finished circuit could be used to indicate the output voltage of a power supply unit. It could also be used to check the voltage of a car-type battery to give an indication of its state of charge. It could also determine the state of standard throw-away batteries and nickel-cadmium cells. A further use would be to display sound levels by connecting the input to the headphone socket of a personal stereo. The circuit will respond to the positive peaks of the ac input. The negative excursions will have no effect.

A novel use for the circuit would be to sense position or movement by using the object to rotate the sliding contact of a potentiometer which would vary the voltage applied to the input. In that case, you would need to obtain the supply for the potentiometer from a voltage regulator, because the circuit responds to absolute voltage levels.

## The circuit

The circuit for the Bargraph module is shown in **figure 1**. The device requires a supply of its own, and any battery having an output of between about 6V and 9V will be found to work well. Diode D1 provides protection to the circuit if the battery were to be connected with the wrong polarity, as it would then not

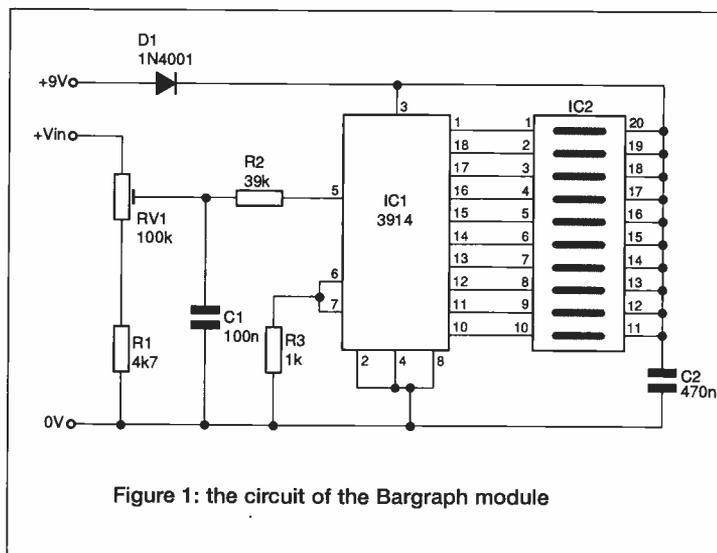



Figure 1: the circuit of the Bargraph module

conduct and no current would flow.

The circuit centres on IC1, an LM3914 bargraph driver ic. This is a complex device which contains a set of ten op-amps connected as voltage comparators. The inverting inputs are all connected together and receive a voltage from the external source applied to pin 5. The non-inverting inputs are connected to a resistor chain. The top end of this is connected to a precision on-chip 1.25V reference. The chain of resistors provide a set of potential dividers which apply fractions of the reference voltage to each of the ten op-amp non-inverting inputs. These fractions increase in 0.125V steps. With no voltage applied to pin 5, all non-inverting inputs are at zero voltage, so all the op-amps will be on. As the voltage applied to pin 5 increased from zero to, say, 1.3V, the non-inverting input voltage of each op-amp will exceed the voltage applied to its non-inverting input and the output will switch off. This will allow current to sink through the LED connected to it. This will happen at 0.125V, 0.25V, 0.375V etc. up to the reference value of 1.25V.

Pin 9 is the "mode pin". If it is left unconnected as shown, the display will be in "dot" mode. This means that as each successive LED bar lights up, the one before it will go out. In fact, there is a small crossover where two bars may be on at the same time.

By connecting pin 9 to supply positive, the display will enter "bar" mode. Here, the display will look rather like a thermometer. As each successive bar lights up, those before it will remain on. Although other approaches are interesting and possibly a subject for experiment, using a practical circuit in dot mode is strongly advised because it has certain advantages. The most important is that only the current for one LED is drawn from the supply at any time. If bar mode were used, with all ten bars lit, the current requirement would be considerable

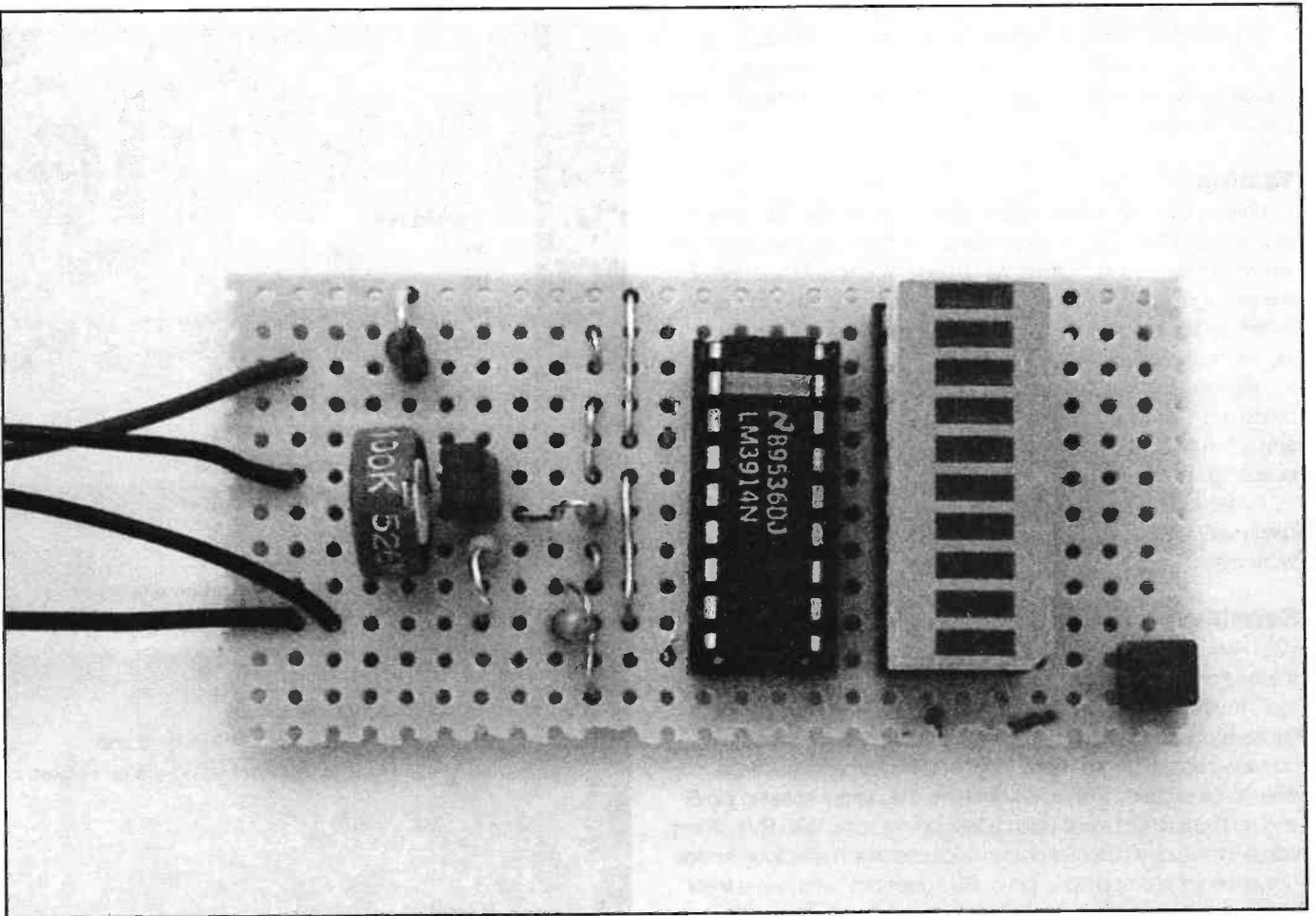

and this would quickly drain the battery. A further point is that the power required for this could exceed the limit of IC1 (about 600mW) and it could be destroyed.

The circuit would not be very versatile if the input voltage had to lie within the "basic" range set by IC1, that is, 0.125V to 1.25V. Preset potentiometer RV1 is therefore used to scale

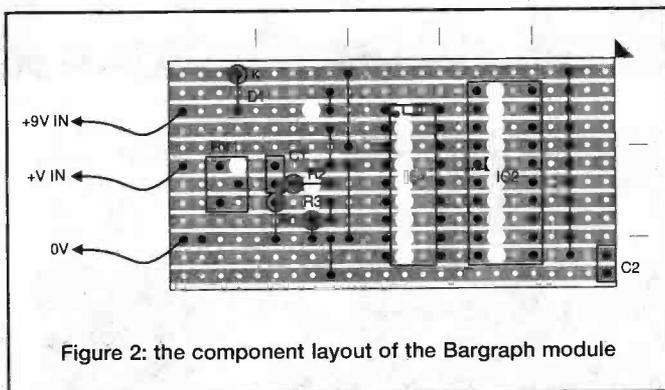


Figure 2: the component layout of the Bargraph module

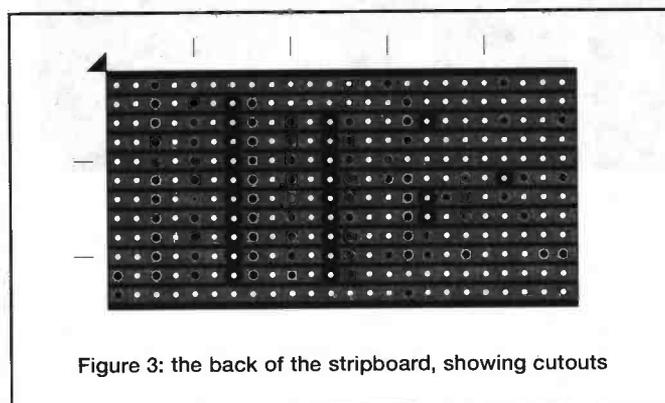


Figure 3: the back of the stripboard, showing cutouts

down the input voltage so that, with any voltage within range, it will apply the basic voltage to pin 5.

### Construction

The topside stripboard layout (component side view) is shown in figure 2. As shown, the LEDs will light from the top. It will need to be turned upside down if the bars are to progress from the bottom.

There are a large number of inter-strip links and a few track breaks needed in this circuit. Begin with the track breaks then solder the link wires in place. If the circuit does not work, it is almost certainly due to a strip not being properly broken, a break or link wire being left out or a blob of solder or particle of copper bridging adjacent copper tracks. Note how all strips to the right-hand side of IC2 (pins 11 to 20) are connected together and taken to the positive supply rail. This is done by soldering a piece of connecting wire on the copper strip side of the circuit panel as shown in the diagram.

Solder the ic sockets and all other components in position. Take care to mount diode D1 with the correct orientation. Solder battery connectors to the "+9V" and one of the "0V" points. Solder short pieces of wire to the "+Vin" and the other "0V" point. Adjust RV1 to approximately mid-track position, which will give medium sensitivity to start with.

Insert IC1, taking care over its orientation. This is a CMOS device and could be damaged by static charge on the body. To make sure this does not happen, touch something which is earthed - such as a water tap - before handling the pins. Insert the LED display (this is labelled IC2, although it only contains an array of LEDs). It seems that the only simple way of identifying which way round this should be placed is to look at the lettering on the side. This should be placed to the right. If the circuit does not work at the end, it may be that it is the wrong way round.

Capacitors C1 and C2 promote stability. They bypass the small amount of alternating current which could be induced in the wiring and this could cause several LED bars to flicker on at the same time.

### Testing

Connect a 6V or 9V battery. Apply a 9V battery to the "Vin" wire (positive) and the inner 0V wire (negative). If the wires are connected the wrong way round, nothing will happen. You should see one of the bars light up. By adjusting RV1, it should be possible to make others do so. If more than two bars are lit at the same time, try increasing the value of C1, C2 or both.

The input is protected and no harm will result if the voltage being measured is either connected in the wrong sense or is too high. An applied voltage above the range will simply keep the tenth bar operating.

Resistor R3 determines the brightness of the LEDs, and this will hardly vary with changes in supply voltage. The value stated should work well.

### Sensitivity adjustment

With RV1 sliding contact turned fully anti-clockwise (as viewed from the left-hand edge of the circuit panel), the circuit will be as sensitive as IC1 will allow - that is, 0.125V per bar. Here, the input voltage is effectively connected direct to pin 5 via resistor R2. This resistor normally has virtually no effect. However, if an excessive voltage were to be applied to pin 5, it would limit the current entering pin 5 and no harm would result up to a few tens of volts. With RV1 sliding contact rotated, a potential divider is formed which effectively scales down the voltage applied to pin 5. RV1 does not behave in a linear way but, with the values shown and with maximum rotation the sensitivity of the prototype was 3V per LED.

## PARTS LIST for the Bargraph Module

### Resistors

R1	4.7k
R2	39k
R3	1k
RV1	100k min vertical preset.

### Capacitors

(2.5mm pin spacing)

C1	100n
C2	470n

### Semiconductors

IC1	LM3914 bargraph display driver
IC2	10-segment bargraph display
D1	1N4001

### Miscellaneous

0.1-in matrix stripboard; PP9 battery and connectors; 18-pin dil socket; 20-pin dil socket.

**ETI**  
ELECTRONICS  
TODAY INTERNATIONAL


# News...

## DSP Comms Chip Requires Fewer Support ICs

The DSP16000 from Lucent Technologies Microelectronics Group is a new-generation digital signal processing core for applications such as cellular telephones, multi-channel modems and, in the case of the first device, the DSP16210, wireless base stations. The 16210, which has a large on-chip RAM and so requires no external memory, is expected to lower the cost of wireless base stations by reducing the number of chips required in future base stations.

Features of the DSP16000 core include dual 32-bit access in one cycle, dual MAC in one cycle and mixed signal 16/32-bit ISA (instruction set architecture) for high performance with reduced code size. The core also has a system cache for ultra low power, extensive support for high-level languages, and is source code backwards-compatible with the Lucent DSP1600 range of comms DSPs. The core includes a dual MAC architecture, 62k x 16 SRAM, DMA on the host port (PHIF) and serial port (SIO). The peripheral mix includes DMA I/O and direct connection to E1, T1 and TDMA interfaces common in infrastructure architectures. The DSP16000 gives sufficient performance at 2.7V, say Lucent, to implement at least four complex speech coders, such as GSM, HR or EFR), and many channels of error correction, equalisation or modems such as V.34.

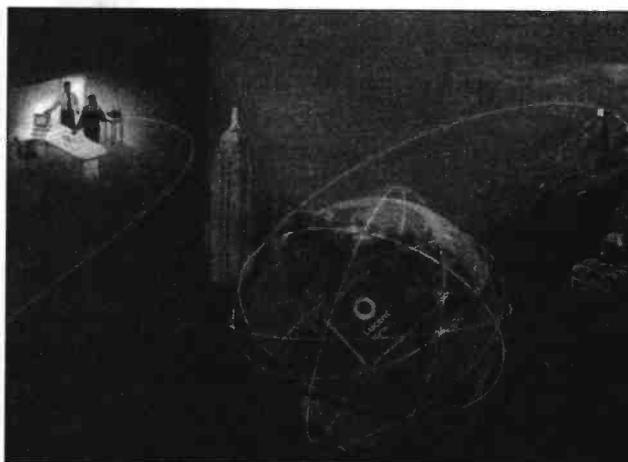Lucent Technologies designs, builds and delivers public and




private networks, comms systems and software, consumer and business telephone systems and microelectronic components. The R&D arm of the company is Bell Laboratories.

For more information contact the Lucent Technologies Dataline at Tel 0118 932 4299 Fax 0118 932 8148 or Simon Cosgrove, Lucent Technologies Microelectronics Group, Microelectronics House, Broad Lane, Bracknell, Berks RG12 9GX. Tel 01344 865910 Fax 01344 865923. Web [www.lucent.com/micro](http://www.lucent.com/micro)

# Fast Fivers

**Adaptable, affordable - handy circuits for around £5. By Owen Bishop**

## 8. A Digital Die

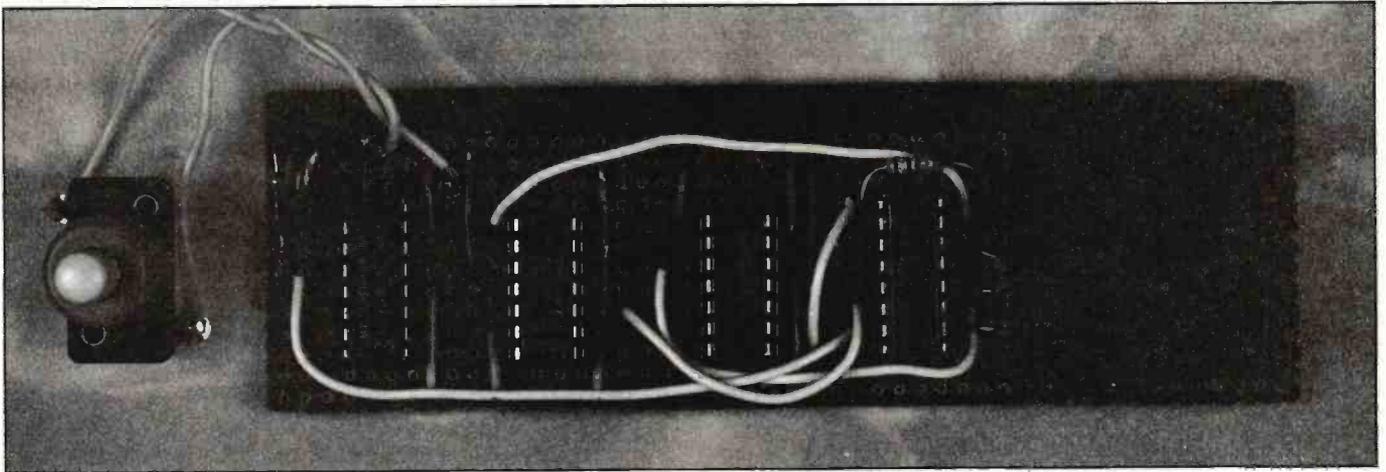

**H**ere is a die that shows all the expected faces, from 1 to 6, but does not have the irritating habit of rolling off the table and under the sofa just as the game is getting exciting. The die consists of a square black box bearing seven red 'dots' (actually LEDs). When battery power is supplied, the display of dots repeatedly cycles through all the conventional dot patterns, but runs so quickly that you have no time to recognise them. When the button is pressed the display halts at one of the numbers. Release the button and off it goes again.

### How it works

The display is driven by a counter (IC1 in figure 2), which has a built-in oscillator. The counter has 14 stages but we use the outputs from only three of these, stages 5, 6 and 7. With the

given resistor and capacitor values, the outputs of these stages cycle through the binary states 0 (000) to 5 (101) at just about the right rate to make the display impossible to follow. The next part of the circuit consists of logic gates connected so as to light up the appropriate LEDs at each state. What we need to do is set out in the following table; figure 2 (the stripboard layout) shows the numbering of the LEDs:

Decimal State	Binary State CBA	Display value	LEDs to be lit up
0	000	1	4
1	001	2	1, 7
2	010	3	1, 4, 7
3	011	4	1, 2, 6, 7
4	100	5	1, 2, 4, 6, 7
5	101	6	1, 2, 3, 5, 6, 7
6	110		

Reset to 1

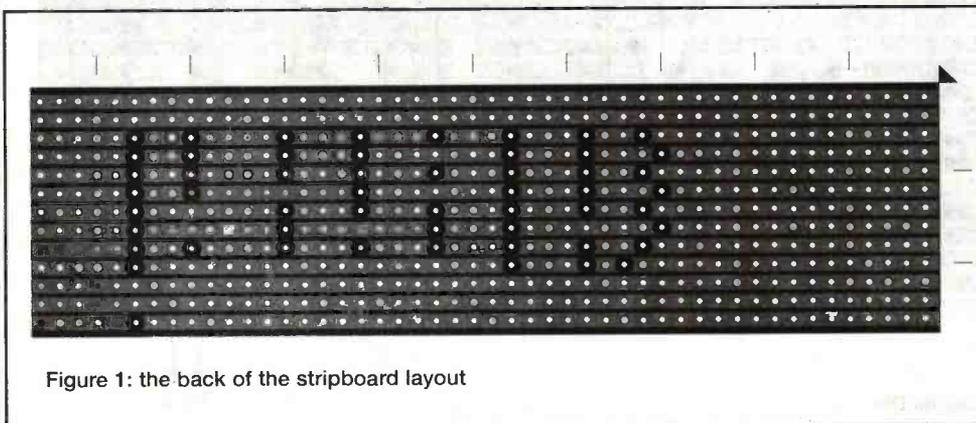


Figure 1: the back of the stripboard layout

All the logic is done with two types of gate. The NAND gates (IC2) give a low output (1) when and only when both of their inputs are high. The NOR gates (IC3) give a high output when and only when both of their inputs are low. The function of the buffer gates (IC4) is to provide enough current to drive the LEDs. Because these are inverting buffers, they need a low input to turn the LEDs on.

The table shows that LEDs 1

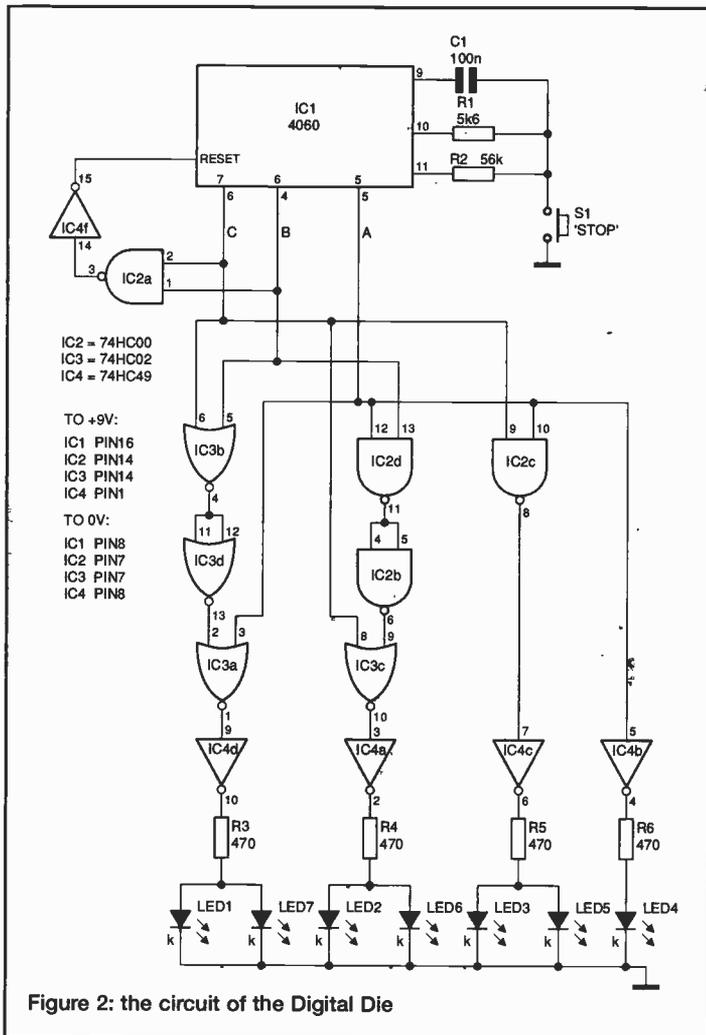


Figure 2: the circuit of the Digital Die

and 7 always come on together, so we can control these from a single buffer. The same applies to LEDs 2 and 6, and LEDs 3 and 5. LED 4 operates on its own. The table shows that LED 4 is to be on when digit A is low. This makes the logic very simple; the buffer for LED4 (4b) is connected directly to the A logic line.

LEDs 3 and 5 are slightly more complicated. They are to be on only at state 5. This state is distinguished by the fact that A and C are both high during this state, but not in any other state. 'Both high' implies using a NAND gate (2c). When A and C are both high, the output of 2c goes low; this logic low is fed

to the buffer (4c), turning on LEDs 3 and 5.

LEDs 2 and 6 need even more elaborate logic. They are to be on for states 3 to 5, that is when A AND B are high OR when C is high. Gate 2d takes care of the A AND B logic, except that its output is low when this state occurs. We use gate 2g with its inputs wired together to act as a INVERT (or NOT) gate and turn this low into a high. Then we use gate 3c to OR this with the state of C, to give a low when (A AND B) OR C occurs. The low supplied to buffer 4a turns on LEDs 2 and 6.

LEDs 1 and 7 must be on when all outputs are low. To make use of the gates available, we take the opposite viewpoint and say that they must be on when A OR B OR C are high. Gate B looks for high B OR C and goes low when this happens. Gate 3d changes this to a high. Gate 3a goes low when it receives a high from gate 3d OR a high directly from A. The resulting low, arriving at buffer 4d, turns on the LEDs.

If we let the counter continue beyond stage 5 it goes through stages 6 and 7 giving us an extra 5 or 6 in each cycle. The die is loaded! To prevent this, we reset the counter immediately it goes into stage 6, as soon as both digits B and C are high. We detect this with the fourth NAND gate (2a), and use a buffer (4f) to invert its low output to give a high pulse to reset the counter.

### Construction

The circuit is most conveniently assembled on a single piece of stripboard with the display at one end (figure 3). But you can adapt the design to put the display on a separate board. You can use larger, jumbo-sized LEDs, but we preferred 'dot' LEDs, which are cylindrical and 3mm in diameter. The circuit is powered from a 9V battery, such as 6 AA cells in a battery box or a 9V PP3 battery. It also runs at 6V, in which case you need to reduce the value of R3-R6 to 270 ohms.

Begin with IC1, its associated resistors and capacitor and the push-button S1. Leave a few millimetres of the leads of C1 showing above the board, to make it easier to connect another capacitor in parallel with C1 when testing (see below). Note that some of the copper strips are NOT cut beneath the ics (though they are all cut beneath IC1) or between one ic and its neighbours. This helps reduce the number of wired connections required. Also note that we have used solder blobs in some places, to make connections between adjacent copper strips. The best technique is to build up a large blob on each side of the intended joint, then let the blobs cool. Finally

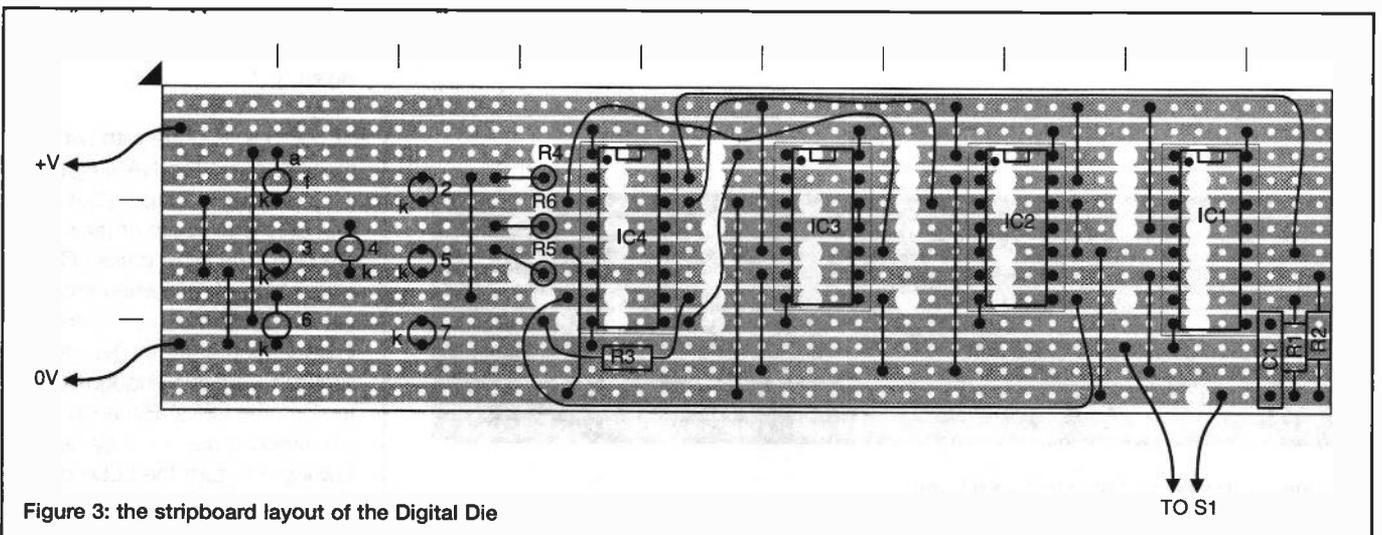


Figure 3: the stripboard layout of the Digital Die

touch the soldering iron to both blobs simultaneously and apply a little solder across the gap.

When IC1 is assembled, temporarily connect pin 12 (reset) to ground and use a testmeter or digital probe (from an upcoming Fast Fiver, for instance) to check that the oscillator is working at a suitable rate. You should see the meter needle (yes, an old-fashioned analogue meter or a digital meter with analogue display is best for this kind of testing) flickering rapidly on all pins 4 to 6.

Next assemble IC1 and IC2, including the inter-pin blobs at F34/G34 on IC2 and at E29/F29 on IC3. Remember that the pinout of the four gates in the 74HC02 is entirely different from that in the 74HC00, so check back to the pin numbering in figure 1. IC4 comes next; gate 4e is a spare and, in order not to leave it with its input floating, it is connected to the output of gate 4c by means of the copper strip left uncut at H19.

At this stage you could use a testmeter or digital probe to confirm that everything is working properly. It helps to connect a larger-value capacitor (for example, a 10 microfarad electrolytic) in parallel with C1 to slow down the rate of cycling. Or you may prefer to carry on and complete the wiring of the resistors and LEDs before testing. A heat shunt is strongly recommended when soldering the LEDs. Unfortunately, not all manufacturers keep to a standard way of indicating which wire is the anode and which is the cathode. Before you begin to solder in the LEDs, test one with a 1.5V cell or with a higher voltage and a series resistor (9V and 470 ohms) to see which way round they should go.

The appearance of the display is improved by fitting a small square box around the LEDs, to make them look like the dots of a typical die. When all is ready, connect the battery and watch the LEDs flicker. To 'shake' the die, press and hold S1. There is no way of telling what stage the counter is at when the button is pressed so the 'throw' is in effect random.

## PARTS LIST for the Digital Die

### Resistors

(All 5 percent, 0.25W)

R1	5.6 kilohm
R2	56 kilohm
R3 - R6	470 ohm (4 off)

### Capacitor

C1	100 nF, polyester.
----	--------------------

### Semiconductors

IC1	4060 CMOS 14-stage counter with oscillator
IC2	74HC00 CMOS quadruple 2-input NAND gate
IC3	74HC02 CMOS quadruple 2-input NOR gate
IC4	4049 CMOS hex inverting buffer
LED1 - LED7	Light-emitting diodes, preferably 'dot'-shaped

### Miscellaneous

S1	push-to-make push-button
Stripboard 34mm x 124mm (13 strips x 48 holes), terminal pins (4 off), 14-pin dil sockets (2 off), 16-pin dil sockets (2 off), 9V battery box or PP3 battery clip.	

**THE ETI BOOK OF ELECTRONICS**  
DAVE BRADSHAW

**SCANNERS 3**  
Putting Scanners into Practice

INTERNATIONAL VHF/UHF Communications Guide

NEW EDITION

Expiry Date.....Signature.....  
Name.....  
Address.....  
.....Post code.....  
Telephone Number.....

Complete details and return coupon to: Nexus Direct, Nexus House, Boundary Way, Hemel Hempstead, Herts, HP2 7ST. If you do not wish to receive mailing from other companies, please tick box.

## ETI Book of Electronics

This book is both a theoretical and practical introduction to electronics. It clearly explains the theory and principles of electronics and each chapter includes a project for the beginner to make. The projects are a loudspeaker divider, continuity tester, 'brown-out' alarm, freezing alarm, loudspeaker, mini-amplifier and a burglar alarm.  
NB214 £12.45 UK £12.95 Overseas

## Scanners 2 International.

The companion book to Scanners provides even more information on the use of VHF and UHF communication bands and gives details on how to construct accessories to improve the performance of scanning equipment. The book is international in its scope and contains frequency allocations for all three ITU regions, including country-by-country variations.  
NB216 £11.45 UK £11.95 Overseas

## Scanners 3 - Putting Scanners into Practice

This is the fourth revised and completely updated edition of Scanners, the complete VHF/UHF radio listeners guide and contains everything you need to know to put your scanner to better use. There is vastly more information than ever before on frequency listing: in particular actual frequencies used by coastal stations, airfields and the emergency services. Also included for the first time is a section on the HF (short wave) band as many scanners now cover this range.  
NB217 £11.45 UK £11.95 Overseas

Telephone orders: 01322 616300 ask for Nexus Direct:

Please send me.....copies of NB.....@.....  
Please send me.....copies of NB.....@.....  
Please send me.....copies of NB.....@.....

I enclose my remittance of £.....

I enclose my cheque/PO for.....made payable to Nexus Special Interests or please debit my Access/Visa.

# PIC-based Double-Bass Tuner

**Samuel Dick wanted a small and portable tone-generating tuning aid, so he designed his own, with the help of the PIC 16C64.**

**K**eeping musical instruments in tune is an everyday task for musicians, so a simple tuning device is a welcome addition to their music bag. Commercial tuners usually have a visual indication of correct tuning - either a row of LEDs or an analogue meter is used to indicate pitch offset. These are electronically very convenient, but most musicians are more accustomed to tuning to a reference sound. For example, orchestras often tune to the first oboe, chamber groups to the keyboard instrument (a harpsichord, for example), if present, and string groups agree among themselves to tune up to one of their string instruments. So tuning by ear is a skill needed by both professional and novice musicians.

The simple tuner described in this article helps the aural

tuning process by generating the correct tones for - in this particular model - a double bass. To make the tuner as simple and as accurate as possible, a PIC microcontroller is used to do all the waveform timing. Using a microcontroller reduces the complexity of the project compared with a hard-wired logic design, and the microcontroller has features useful in battery-powered equipment, such as hibernation, that dedicated keyboard synthesiser chips lack.

One of the troublesome aspects of a double bass tuner is the need to reproduce very low notes. The lowest frequency needed is that of the E strong, at 82.4 Hz. Such a low frequency is not efficiently handled by the size of loudspeaker, up to around 50 mm in diameter, normally acceptable in a portable tuner, so this tuner uses good quality earphones instead.

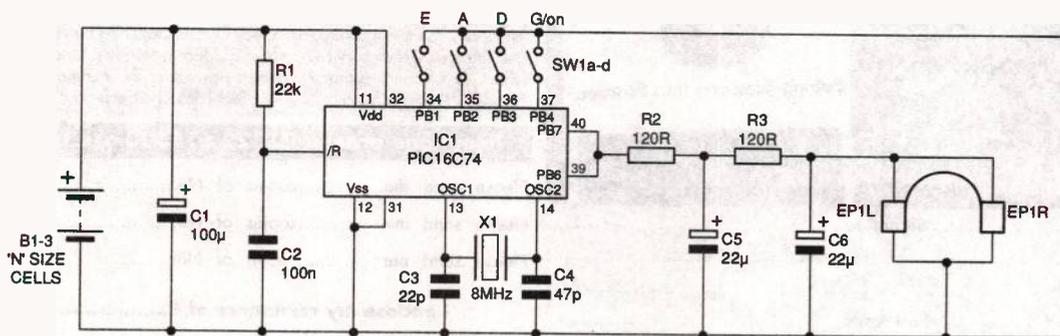


Figure 1: the circuit of the Double-Bass Tuner

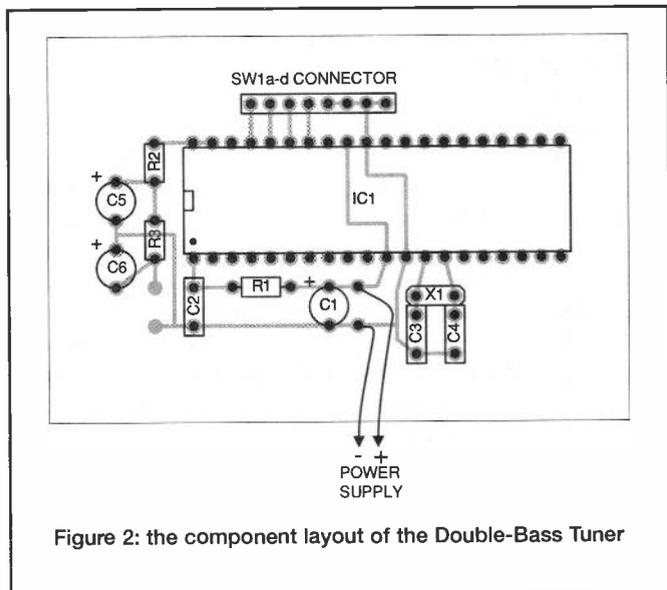


Figure 2: the component layout of the Double-Bass Tuner

## Timing

The heart of the tuner is a PIC 16C64 microcontroller which contains a 16-bit timer. In total, the microcontroller has three timer units. Timer-0 and Timer-2 are 8-bit counters; Timer-1 is a 16-bit counter, which is configured by the software to count pulses from the system's crystal oscillator and, when a particular value (stored in that counter's compare register) is reached, issue an interrupt request. When the microcontroller receives the interrupt request, it executes an interrupt service routine which toggles the state of two of the output pins on Port-B, one of the digital input/output ports.

The use of a 16-bit counter combined with a fairly high system oscillator frequency (8 MHz, resulting in 2 MIPS performance) allows the tuner to be very accurate. The frequencies that can be generated by this technique are given by the simple equation  $2 \times 10^6 / n$ , where  $n$  is the number in the counter's compare register. A little experimentation with  $n$  will show that an 8-bit counter ( $0 < n < 256$ ) cannot generate frequencies sufficiently accurate for use as a musical tuner.

When it is active, the PIC spends its time looking at the keypad (SW1a, b, c, or d), either waiting for a user to press one of the switches, or servicing an interrupt. When one of the note-selection keypad buttons is pressed, it clears its corresponding bit in Port-B (Port-B pins have an internal weak pull-up that is enabled in the software). When a keypress is detected, bit-test functions are used to determine which key was pressed. Timer-1's compare register is then loaded with the particular value needed to ensure that an interrupt is generated each half-cycle of the note requested, Timer-1 is cleared and enabled, and interrupts from Timer-1 are enabled. Timer-1's compare register is a 16-bit register each half of which (the high and low bytes, CCPR1H and CCPR1L) is accessed independently.

For example, to generate an E with a frequency of 82.4 Hz and a cycle time of 12136 microseconds, the PIC needs to change the state of the output pin every 6068 us. A sine wave spends half its cycle positive and half negative, so the output pin spends half a cycle on, half a cycle off. Timer-1 is incremented every four system-oscillator periods, that is, steps of 0.5 us with an 8-MHz

system oscillator. So the Timer-1 compare register is loaded with 2F68h: every 12,136 steps (6068 us) an interrupt is generated that, in turn, calls the interrupt service routine to change the state of the output pin. Thus the output pin is high for 6068 us and low for the next 6068 us.

This scheme generates a squarewave at the correct frequency but, because of the many powerful harmonics in a squarewave, the note actually sounds to the ear as though it is perhaps one or two octaves higher. To filter out the harmonics, a simple high-cut filter (R2, C5, R3, C6) is placed between the microcontroller (IC1) and the earpiece (EP1).

Other features of the microcontroller are disabled by the software during the start-up process when power is applied or when the device wakes from sleep. Except when actually generating a note or hibernating, interrupts from all other sources within the microcontroller are disabled; when hibernating, only interrupts signalling that the keypad has been pressed are allowed; when generating a note, only interrupts from Timer-1 are allowed.

## Sleep

The PIC 16C64 has a sleep facility which cuts power consumption down to a level typically less than the self-discharge rate of a battery. The chip is powered-down by

## PARTS LIST for the Double Bass Tuner

### Resistors

All 0.24 watt carbon

R1	22 kohm
R2, R3	120 ohm

### Capacitors

C1	100 uF 16V electro
C2	100 nF 25V ceramic
C3	22 pF 25V ceramic
C4	47 pF 25V ceramic
C5, C6	22 uF 25V electro

### Other major parts

IC1	PIC16C64-JW or -10P microcontroller
X1	8 MHz crystal
SW1	Four-way membrane keypad

### Miscellaneous

BH1 to 33	N-size battery holders
B1 to 3	N-size 1.5 V batteries
40-way DIL socket; small plastic box (140mm x 75 mm x 35 mm with battery compartment and access hatch; one pair of earphones)	

Software: The code can also be obtained from the author by email at [SamDick@aol.com](mailto:SamDick@aol.com)

issuing the SLEEP instruction which halts the crystal oscillator; the prototype's supply current drops to less than 1uA during sleep. By using the hibernation facility, no on/off switch is needed and the tuner cannot be left on accidentally.

The hibernation works as follows: as described above, the PIC's main task when producing a musical note is to switch two of the digital port pins on and off at a certain rate, according to which note has been requested. In the software, two of the RAM locations within the microcontroller are allocated to a counter which is set to zero when the note starts and which is incremented each time an interrupt from the PIC's Timer-1 is serviced. Thus, whenever the PIC changes the state of the output pins, the counter has one added to its value.

After the counter has been incremented, its value is checked to see if it exceeds 4000h and if so, the PIC executes the SLEEP command. The counter has to be a 16-bit counter. For the highest note (196 Hz), an 8-bit counter would roll-over in 1.3 seconds - too short a time for tuning! So two 8-bit counters are used in series to make a 16-bit counter. When the first counter reaches 128 (bit 7 switching on), the second counter is incremented and the first counter cleared to zero. When the second counter reaches 128, it is cleared, the output pins are set to logic zero to minimise current drain through them during sleep, interrupts are disabled, and the processor is put to sleep. This scheme gives a time-to-sleep of about 40s for the highest note, which is adequate for tuning purposes but ensures that the tuner's battery life is long - a set of batteries should last for around a thousand tuning sessions with the 12mA active current drain. The choice of a 128 count for both 8-bit counters is somewhat arbitrary, but gives a sensibly long active period prior to hibernation; the natural roll-over 256 count of an 8-bit counter would have given a 160s active period which was judged to be needlessly long.

The PIC software clears the general interrupt-enable bit before hibernating so that, upon wake-up, it continues executing the software after the SLEEP instruction: it continues to watch the keypad for key presses.

How does the PIC wake-up? Although hibernating, the microcontroller can be stirred into activity by any one of a small number of events. For example, a master reset signal or some interrupts will trigger wake-up. Before the PIC is sent to sleep, the wake-up logic is configured so that a change in level of the voltage applied to bits 4 through 7 of Port-B will initiate wake-up. One of the keypad switches is connected to bit 4 of Port-B, so when that key is pressed, the microcontroller wakes up.

So the PIC normally sleeps. It wakes up when one of the keypad buttons (the G) is depressed, plays notes as requested by pressing momentarily any of the keypad buttons, and goes back to sleep some tens of seconds later. No on/off switch is required, and there is no need to remember to switch it off after use.

## Miscellaneous

The PIC is powered by three N-size alkaline-manganese batteries. The 4.5 V supplied from the cells is within the PIC's 3.0 to 6.0 V operating range and means that no voltage regulator device is needed. Because of the sleep feature, no on/off switch is necessary.

C1 smooths any supply ripple due to the activity of the

microcontroller. R1 and C2 reset the microcontroller on power-up and X1, C3, and C4 function as the system oscillator.

The tuner is built into a small plastic box which has a hatch for access to the battery compartment. Normally, a PP3 9-volt battery would fit into the battery compartment but the three N-size cells that power the tuner can be held in three individual battery holders which, if placed at an angle of 45degrees, will fit into the same space and will be accessible via the hatch. The earphones (wired in parallel to provide some redundancy should one of them go open-circuit) and the membrane keypad are connected directly to the circuit board, with their connecting wires requiring only small slits in the plastic case.

### PIC-based Double-Bass Tuner - Code

```

; tuner program

list p=16c64,f=inhx8m

include "a:\pic\p16cxx.inc" ;definitions file

; variables

        opVal equ 0x20           ;output value
        cntrA equ 0x22           ;counter A
        ; timeout
        cntrB equ 0x23           ;counter B
        ; timeout

; start administration

        org 0x00                 ;reset/power-up
vector
        goto Start

        org 0x04                 ;irq vector
        goto irqserv

        org 0x05                 ;program start

Start
        bsf STATUS,RP0 ;switch pages to 1
        movlw 0x3F             ;port-B b0..b5 as
input
        movwf TRISB
        bcf OPTION_REG,7       ;port-B pullups on
        bcf STATUS,RP0 ;switch pages to 0
        bcf opVal,7             ;off - output bits
        bcf opVal,6
        movfw opVal
        movwf PORTB
        clrf T1CON              ;stop timer-1 &
initialise

Again
        movfw PORTB             ;read port B
        btfss PORTB,1
        goto makeE              ;82.4hz
        btfss PORTB,2
        goto makeA              ;110hz
        btfss PORTB,3
        goto makeD              ;146.8hz
        btfss PORTB,4
        goto makeG              ;196hz
        goto Again

```

```

makeE
bcf INTCON,GIE ;disable irqs
clrf T1CON      ;stop count,
                ;internal osc/4,
                ;prescale=1
movlw 0x0B      ;set tmr1 control
                ;soft irq, cmp
                ;mode

movwf CCP1CON
movlw 0x2F      ;load ccp regs
movwf CCPR1H
movlw 0x68
movwf CCPR1L
bcf PIR1,CCP1IF ;clear irq flag

clrf cntrA      ;clear timeout
clrf cntrB

bsf STATUS,RP0 ;switch page
bsf PIE1,CCP1IE ;allow irqs
bcf STATUS,RP0 ;switch page
bsf INTCON,GIE ;enable irqs
bsf INTCON,PEIE ;enable pe irqs
bsf T1CON,TMR1ON ;start counting
goto Again

makeA
bcf INTCON,GIE ;disable irqs
clrf T1CON      ;stop count,
                ;internal osc/4,
                ;prescale=1
movlw 0x0B      ;set tmr1 control
                ;soft irq, cmp
                ;mode

movwf CCP1CON
movlw 0x23      ;load ccp regs
movwf CCPR1H
movlw 0x83
movwf CCPR1L
bcf PIR1,CCP1IF ;clear irq flag

clrf cntrA      ;clear timeout
clrf cntrB

bsf STATUS,RP0 ;switch page
bsf PIE1,CCP1IE ;allow irqs
bcf STATUS,RP0 ;switch page
bsf INTCON,GIE ;enable irqs
bsf INTCON,PEIE ;enable pe irqs
bsf T1CON,TMR1ON ;start counting
goto Again

makeD
bcf INTCON,GIE ;disable irqs
clrf T1CON      ;stop count,
                ;internal osc/4,
                ;prescale=1
movlw 0x0B      ;set tmr1 control
                ;soft irq, cmp
                ;mode

movwf CCP1CON
movlw 0x1A      ;load ccp regs
movwf CCPR1H
movlw 0x9B
movwf CCPR1L
bcf PIR1,CCP1IF ;clear irq flag

clrf cntrA      ;clear timeout
clrf cntrB

bsf STATUS,RP0 ;switch page
bsf PIE1,CCP1IE ;allow irqs
bcf STATUS,RP0 ;switch page
bsf INTCON,GIE ;enable irqs
bsf INTCON,PEIE ;enable pe irqs
bsf T1CON,TMR1ON ;start counting
goto Again

makeG
bcf INTCON,GIE ;disable irqs
clrf T1CON      ;stop count,
                ;internal osc/4,
                ;prescale=1
movlw 0x0B      ;set tmr1 control
                ;soft irq, cmp
                ;mode

movwf CCP1CON
movlw 0x13      ;load ccp regs
movwf CCPR1H
movlw 0xEE
movwf CCPR1L
bcf PIR1,CCP1IF ;clear irq flag

clrf cntrA      ;clear timeout
clrf cntrB

bsf STATUS,RP0 ;switch page
bsf PIE1,CCP1IE ;allow irqs
bcf STATUS,RP0 ;switch page
bsf INTCON,GIE ;enable irqs
bsf INTCON,PEIE ;enable pe irqs
bsf T1CON,TMR1ON ;start counting
goto Again

irqserv      ;interrupt service routine
bcf PIR1,CCP1IF ;clear irq flag
movlw 0xC0      ;toggle op bits
xorwf opVal,1
movfw opVal
movwf PORTB

; sleep time?

incf cntrA,1 ;a=a+1
btfss cntrA,7 ;a=128?
goto endISR ;no, return
incf cntrB,1 ;yes, b=b+1
clrf cntrA ;a=0
btfss cntrB,7 ;b=128?
goto endISR ;no, return
clrf cntrB ;yes...b=0

bcf INTCON,GIE ;stop irqs
clrf PORTB ;zero output
movfw PORTB ;read B
bcf INTCON,RBIF ;clear portB wakeup

flag
bsf INTCON,RBIE ;enable wake irq
sleep
nop
nop
nop
bcf INTCON,RBIE
bcf INTCON,RBIF
goto Start

endISR ;end of service routine
retfie

end

```

# MIDI DRUM PADS

*A neat way to get your rhythm tracks into your hardware. By Tom Scarff*

**H**ave you got rhythm? Do you want to transfer that rhythm to your computer or hardware sequencer? Probably the easiest way of achieving this is to use MIDI drum pads that can be hit with drumsticks, and the data can be stored in real time with any errors corrected afterwards. While there are commercial units available, they can cost hundreds of pounds, so I designed and built this unit based around the PIC 16C84 microcontroller.

While this unit is cheaper, it does have some limitations. It provides MIDI data which has to be sent to a drum/synthesiser or sound module. The velocity byte is fixed at maximum volume and the drum selection and MIDI transmit channel are fixed at the time of programming. The software as it is written is set up for the drum sounds in the Creative Labs AWE64 or equivalent sound card on channel 10, but the drums can be mapped to suit any sound card or module. Even though the velocity bytes are fixed on record they can be edited afterwards in the sequencer software.

The MIDI data stream is a unidirectional asynchronous bit stream at 31.25 Kbits/sec with 10 bits transmitted per byte (a start bit, 8 data bits, and one stop bit). The MIDI interface on a

MIDI instrument will generally include three different MIDI connectors, labelled IN, OUT, and THRU. The MIDI data stream is usually originated by a MIDI controller, such as a musical instrument keyboard, or by a MIDI sequencer. A MIDI controller is a device that is played as an instrument, and it translates the performance into a MIDI data stream in real time (as it is played). A MIDI sequencer is a device that allows MIDI data sequences to be captured, stored, edited, combined, and replayed. The MIDI data output from a MIDI controller or sequencer is transmitted via the device's MIDI OUT connector.

Each MIDI bit is transmitted for 32 microseconds, and so the timing is fairly critical. In the software this is achieved by timing loops which are accurate to the fundamental frequency of the 10MHz crystal divided by four which is 0.25µs. The real time clock counter (RTCC) would not be as accurate for the MIDI transmission of 31.25 Kbits/sec because of the overheads associated with the operation of the timing overflow and interrupt routines, but obviously works fine for lower baud rates.

## The circuit

The circuit in **figure 1** is based around the PIC 16C84

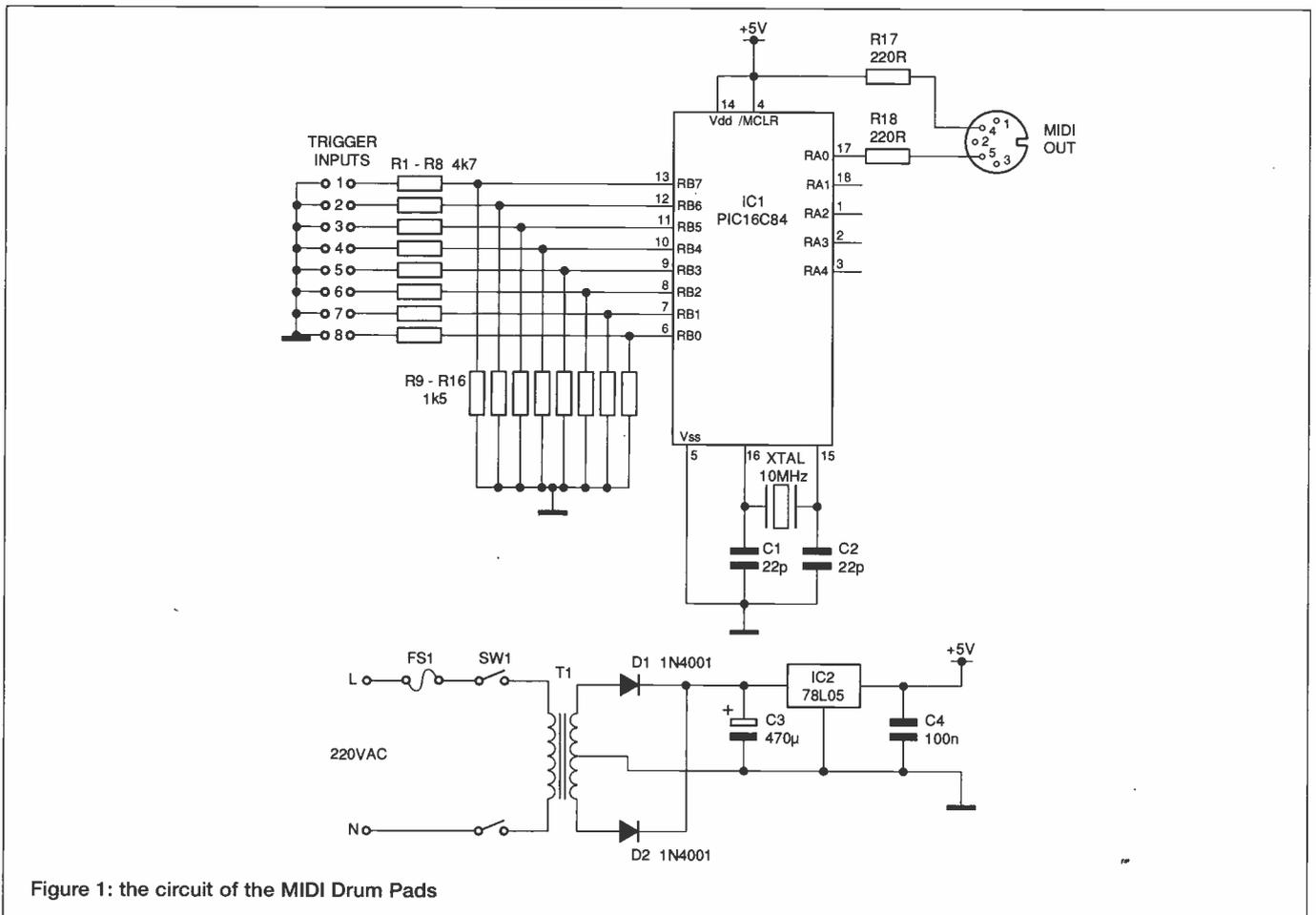


Figure 1: the circuit of the MIDI Drum Pads

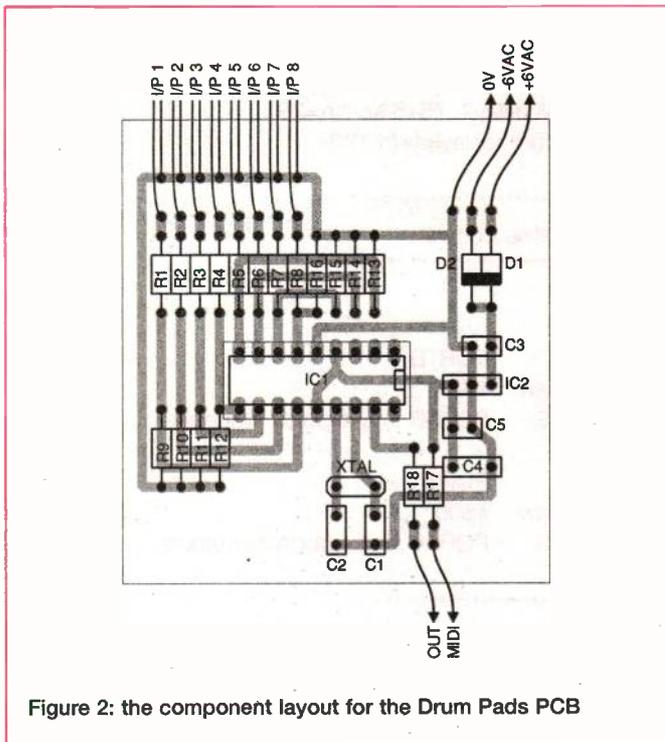


Figure 2: the component layout for the Drum Pads PCB

microcontroller which scans the inputs on RB0 to RB7. When a high is detected the software transmits the equivalent note-on ( and then the MIDI note-off after a short delay) for the required drum sound on the MIDI output on RA0.

The inputs are provided by the piezo-electric transducers which can provide up to 40Vp-p depending on how hard they are hit. This voltage is reduced by the potential dividers R1 to R8 and R9 to R16 respectively. The values chosen reduce the input level by approximately a quarter, and it is further reduced by internal clamping inside the microcontroller. If different transducers are used on the input then the potential dividers may need to be adjusted. Note that the inputs float high so the resistor values R9 to R16 need to be reasonably low so that when the microcontroller software scans the inputs it reads them all as low, with no transducer triggered. Also the maximum input continuous injection current into an I/O is specified as +/- 500uA, although it will sustain larger currents (more than 100mA) for short periods of time.

The timing is generated from the 10MHz crystal and associated capacitors C1 and C2.

The MIDI output is fed to the 180 5-pin DIN socket via two 220R resistors which provide the required 10mA current loop. The power supply is a standard arrangement using a 9V-0-9V centre tapped transformer, which is rectified by diodes D1 and D2 smoothed by C3 and regulated to 5V by IC2.

## Software Operation

The software consists of initialisation of the variable addresses, the constants, the ports and the drum assignments. The drum assignments can be mapped for any drum module, in the original the bass drum is decimal 36, the snare decimal 38, and so on.

For the 16C84 the origin (org) is set to 00h and the programme resets via the goto INIT where PortB is initialised as all inputs and PortA as all outputs. The main program section then polls the inputs and waits for a high input representing a drum being triggered. The particular triggered input is then detected using the "drum?" section, and is converted by the drum sound convert table. The value is

placed in the drum variable and the note-on subroutine called then the note-off subroutine is called which is required for some drum modules.

## Construction

The layout of components on the board is shown in figure 2. The unit can be mounted in any suitable enclosure and only requires connections for a mains cable, via a rubber gland if a metal enclosure is used, the on/off switch, the 5-pin DIN connector and the 8-input transducers. Originally I had the transducers mounted on the same metal panel, which worked if the transducers were hit accurately but if they were missed slightly and the panel hit instead then the incorrect drum could be triggered. To avoid this problem the transducers could be mounted in separate diecast boxes. Also each separate transducer could be mounted onto real drums and triggered when each drum is played separately.

MIDI DRUM PADS DRUMLIST1.ASM  
LIST p=16C84

```
;Program to tx MIDI data with 10Mhz clock
;MIDI Drum-Pads
```

```
;PROGRAM: T. Scarff
;DATE: 03/12/97
;FILENAME: drm_lee1.asm
;ITERATION: 1.1
;NOTE: Channel 10 for drums is 09h
```

```
*****
; Variable Assignment Addresses
*****
```

```
dlyreg      equ    0C
xcount     equ    0D
xmtreg     equ    0E
delay1     equ    0F
count      equ    10h
timer      equ    11h
clkdown    equ    12h
drum       equ    13h
value1     equ    14h
```

```
*****
; Constant Assignments
*****
CARRY      equ    00
MSB        equ    07
BORROW     equ    00
LED        equ    07
W          equ    00
F          equ    01
Z          equ    02
C          equ    00
Dx         equ    00
```

```
*****
; Port Assignments
*****
PCL        equ    02
STATUS     equ    03
PORTA     equ    05
PORTB     equ    06
```

```

;*****
;      Drum Assignments
;*****

drum0      equ    00h ;dummy, never used
drum1      equ    .36 ;bass
drum2      equ    .38 ;snare
drum3      equ    .43 ;low tom
drum4      equ    .42 ;closed hh
drum5      equ    .45 ;high tom
drum6      equ    .46 ;open hh
drum7      equ    .49 ;crash
drum8      equ    .51 ;ride

;*****
;      PROGRAMME Reset Point
;*****

                org    0
                goto   INIT

;*****
;      Subroutines
;*****

delay2  movwf dlyreg ;delay=1+(n-1)*3+3 cycles
dly2    decfsz dlyreg ;where n is in W reg.
        goto dly2 ;n=18 for delay=55 cycles
        nop
        return

bit_set  nop
        nop
        bsf PORTA,dx
        return

bit_clr  bcf PORTA,dx
        nop
        nop
        return

txmidi  movlw .8
        movwf xcount
        bcf PORTA,dx
        movlw .02
        movwf delay1
dly1    decfsz delay1
        goto dly1

xnxt    movlw .20 ;This loop has 25 cycles
        call delay2 ;Plus delay2 value.
        rrf xmtreg ;number of cycles to
        btfsc STATUS,CARRY ;bit set/clear =1+55+9=65.
        call bit_set ;number of cycles from
        btfss STATUS,CARRY ;bit set/clear =15.
        call bit_clr ;Total=80*0.4us=32uS
        decfsz xcount
        goto xnxt

        movlw .22 ;This loop requires 65 cycles
        call delay2 ;61 +4 so if n=20
        nop

```

```

bsf PORTA,dx ;delay=4+(n-1)*3=61

        movlw .25 ;This loop requires 80 cycles
        call delay2 ;75+5 so if n=25
        return ;delay=4+(n-1)*3=76

;*****
;      Initialise Software
;*****

INIT    clrf    PORTB
        movlw  #$FF
        TRIS   PORTB ;make portB all inputs

        clrf    PORTA
        movlw  #$00
        TRIS   PORTA ;make portA all outputs

;*****
;      Main Program Start
;*****

main    clrf PORTB
        movf PORTB,W
        movwf value1
        xorlw #$00
        btfsc STATUS,Z
        goto main

        movlw #$00
        movwf count
drum?   incf count,F
        rrf value1
        btfss STATUS,C
        goto drum?

        movf count,W
        call convert

        movwf drum
        call noteon

        call noteoff
        goto main

;*****
;note-on subroutine
;*****

noteon  movlw  #$99 ;note-on channel 10
        movwf xmtreg
        call txmidi

        movf drum,W ; drum note
        movwf xmtreg
        call txmidi

        movlw  #$7f ;max velocity
        movwf xmtreg
        call txmidi
        return

```

```

;*****
;note-off subroutine
;*****
noteoff movlw #$89 ;note-off channel 10
        movwf xmtreg
        call txmidi

        movf drum,W ; drum note
        movwf xmtreg
        call txmidi

        movlw #$7f ;max velocity
        movwf xmtreg
        call txmidi
        return

```

```

;*****
;Table to convert drum sound
;*****
convert addwf PCL
        retlw drum0
        retlw drum1
        retlw drum2
        retlw drum3
        retlw drum4
        retlw drum5
        retlw drum6
        retlw drum7
        retlw drum8

```

end

**PARTS LIST for the MIDI Drum Pads**

**Resistors**

R1 to R8	4k7
R9 to R16	1k5
R17, R18	220

**Capacitors**

C1,C2	22pF
C3	470uF
C4	100nF

**Semiconductors**

IC1	PIC16C84 (10 MHz version)
IC2	78L05
D1, D2	IN4001

**Miscellaneous**

10 MHz crystal, 5-pin 180 DIN connector, transformer 9V-0-9V, SPST switch and a suitable enclosure. The transducers used in the prototype are Maplin order code YU87U and a rubber disc (27mm) to cover the transducer is order code QY16S. A pre-programmed PIC 16C84 is available for £15.00 and the program software is available on disk for £4.00 from the author at 1 Martello Court, Portmarnock, Dublin, Ireland.

**NEW FROM NEXUS!**

*An Introduction to Robotics*

A fascinating and unique book that breaks new ground by exploring the exciting world of robotics in a clear and concise way. Both the theoretical and practical aspects are presented in an uncomplicated fashion using everyday English, which makes this an ideal book for the amateur. Divided into two sections, the first part explains how and why robots work and are controlled, while the

second shows you how to make a simple two legged humanoid robot that can be programmed to walk. There are no complicated formulas or equations to grapple with or incomprehensible circuit diagrams to decipher, - this robot can be built on your kitchen table and can be run from any personal computer! All you need are model aeroplane servos, a controller, a power supply and some

plywood - and all parts are easily available in the UK and the USA. This is a book that will be of interest to modellers and everyone with a fascination for things mechanical and electronic. This is the way of the future, stay one step ahead and order your copy today! Only £11.50 UK & £12.50 Overseas (Includes Postage & Packing).

Telephone orders: 01442 266551 and ask for Nexus Direct

Please send me..... copies of NB299 @.....

I enclose my cheque/PO for £..... made payable to Nexus Special Interests OR please debit my Access/ Visa.

□□□□ □□□□ □□□□ □□□□


Expiry date..... Signature..... Name.....


Address.....

.....


Post code..... Telephone No.....

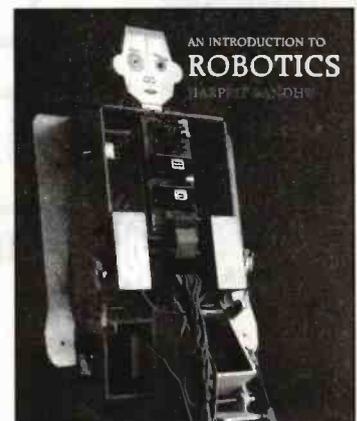Complete details and return coupon to: Nexus Direct, Nexus House, Boundary Way, Hemel Hempstead, Herts, HP2 7ST. If you do not wish to receive mailing from other companies, please tick box.




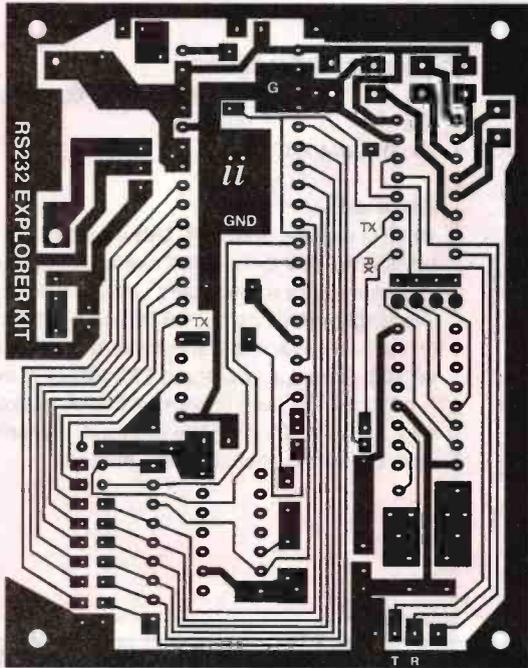

RS 232 I/O Card for Psion 3s



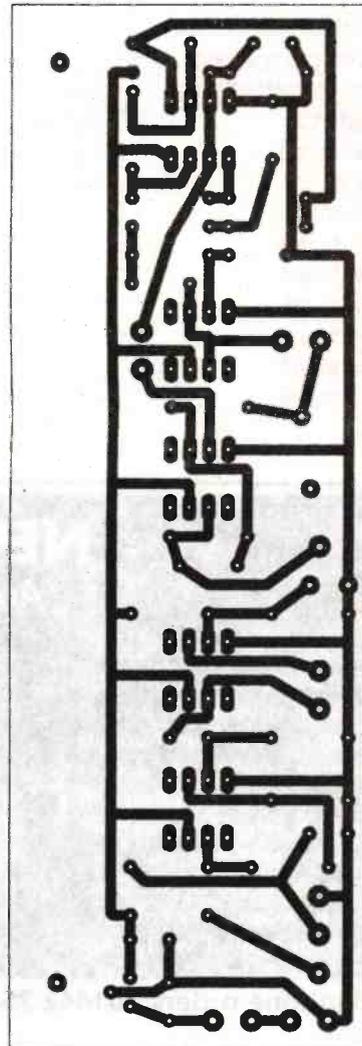


5 Range Capacitor Meter

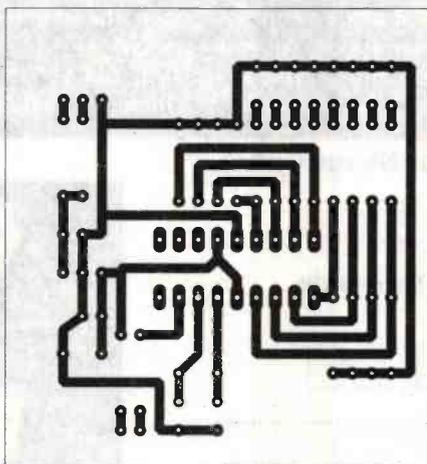

Midi Drum Pads

# FOILS FOR THIS ISSUE

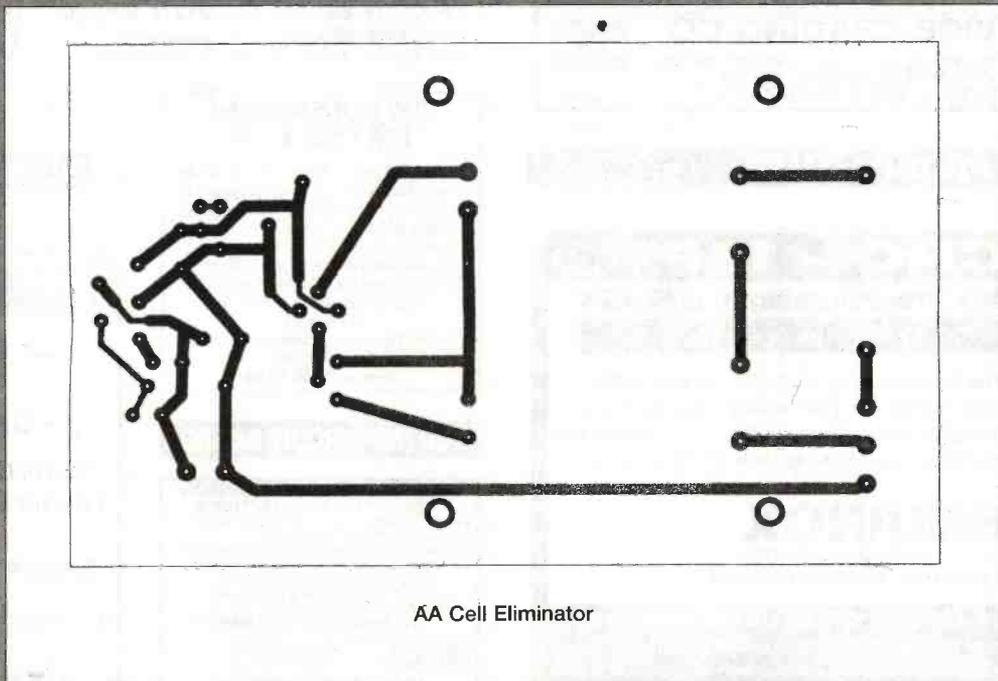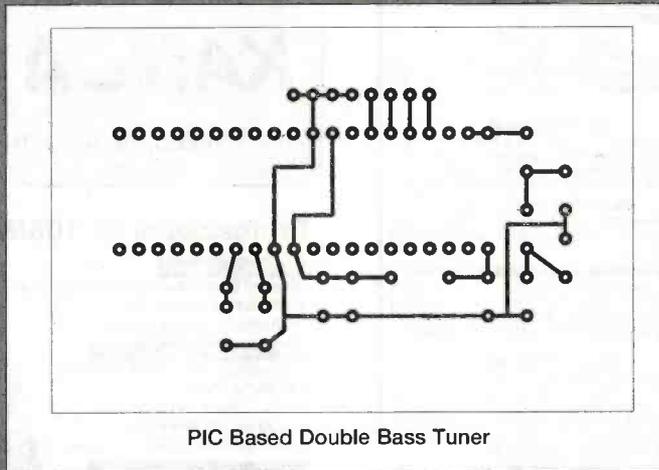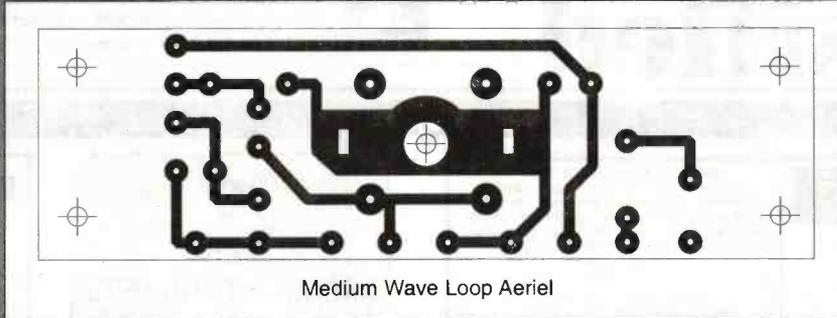

# ETI Classified



**Andy Forder**  
**01442 266551**

Send your requirements to:  
ETI Classified Department, Nexus, Nexus House,  
Boundary Way, Hemel Hempstead, HP2 7ST  
Lineage: 85p per word (+VAT) (minimum 20 words)  
Semi display: (minimum 3cms)  
£12.50 + VAT per single column centimetre



Ring for information on series bookings/discounts.  
All advertisements in this section must be pre-paid.  
Advertisements are accepted subject to the terms and conditions  
printed on the advertisement rate card (available on request).

## FOR SALE

### VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60  
OUTPUT 0-260V

Price P&P

	P&P	
0.5KVA 2.5 amp max	£3.00	£5.00 (£45.83 inc VAT)
1KVA 5 amp max	£4.25	£7.00 (£61.39 inc VAT)
<b>PANEL MOUNTING</b>		
0.5KVA 2.5 amp max	£4.00	£5.00 (£47.00 inc VAT)
1KVA 5 amp max	£4.25	£7.00 (£62.57 inc VAT)
2KVA 10 amp max	£6.50	£8.50 (£86.36 inc VAT)
3KVA 15 amp max	£8.50	£3.50 (£111.63 inc VAT)
5KVA 25 amp max	£15.00	Plus Carriage & VAT
10KVA 45 amp max	£30.00	Plus Carriage & VAT
6KVA 3 PHASE Star	£285.00	Plus Carriage & VAT

Buy direct from the Importers. Keenest prices in the country  
**COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO**  
(110-240V Auto transfer either cased with American socket and mains lead of open frame type. Available for immediate delivery.

**500VA ISOLATION TRANSFORMER**  
New manuf. surplus 'C Core' tropicalised with top plate and solder connections. 0.240V AC Prim. 5-0-110-110-120V & Screen Sec. Wt 10.5kg.  
Size: H195 x 155 x 135mm. Price £35.00. Carr. £7.00 (£49.94 incl.)

**RANGE OF XENON FLASH TUBES**  
Write/Phone your enquiries

**ULTRA VIOLET BLACK LIGHT BLUE FLUORESCENT TUBES**

4ft 40 watt	£14.00 (callers only)	(£16.45 inc VAT)
2ft 20 watt	£9.00 (callers only)	(£10.58 inc VAT)
12in 8 watt	£4.90 + 75p p&p	(£6.52 inc VAT)
9in 8 watt	£3.96 + 50p p&p	(£5.24 inc VAT)
6in 4 watt	£2.96 + 50p p&p	(£5.24 inc VAT)

**230V AC BALLAST KIT**  
For either 6in, 9in or 12in tubes £6.05 + £1.40 p&p (£8.75 inc VAT)

The above Tubes are 3500/4000 angst (360-400nm) ideal for detecting security markings, effects lighting & Chemical applications.

Other Wave Lengths of U.V. TUBE available for Germicidal & Photo Sensitive applications.  
Please telephone your enquiries.

**400 WATT BLACK LIGHT BLUE UV LAMP**  
GES Mercury Vapour lamp suitable for use with a 400W P.F. Ballast  
£39.95 INCL. P&P & VAT



**12V D.C. BILGE PUMPS**

500 GPH 15ft head 3 amp	£19.98
1750 GPH 15ft head 9 amp	£34.55

Also now available 24V D.C. 1750 GPH 15ft head 5 amp £35.55.  
All designed to be used submerged. PRICES INCLUDE P&P & VAT

**SUPER HY-LIGHT STROBE KIT**

Designed for Disco, Theatrical uses etc.  
Approx 16 joules. Adjustable speed £50.00 + £3.00 p&p (£2.28 inc VAT)  
Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT)  
SAE for further details including Hy-Light and Industrial Strobe Kits.



### SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB  
TEL 0181-995 1560 FAX 0181-995 0549  
ACCOUNT CUSTOMERS MIN. ORDER £10



Ample Parking Space

### 5KVA ISOLATION TRANSFORMER

As New Ex-equipment fully shrouded Line Noise Suppression, Ultra Isolation Transformer with terminal covers and Knock-out cable entries. Primary 120/240V Secondary 120/240V 50/60 Hz. .005 pF Capacitance. Size L.37 x W.19 x H.16cm Weight 42 Kilos. PRICE £120.00 + VAT  
ex-warehouse. Carriage on request.

### 24V DC SIEMENS CONTACTOR

Type 3TH8022 DB 2 x NO and 2 x NC 230V AC 10A contacts Screw or Din Rail fixing. Size H 120 x W 45 x 0.75mm. Brand New Price £7.63 incl. P&P and VAT.

### 240V AC WESTOOL SOLENOIDS

TT2 Mod 1 flat. 1 MAX stroke 1/4 in. Base mounting 1/2in. stroke 5lbs pull approx. TT6 Mod 1 Flat. 2 Max stroke 1/8 in. Front mounting 1/2in. Front mounting 1/2 in. stroke 15lbs pull approx. Price incl. p&p & VAT. TT2 £5.88, TT6 £8.81. SERIES 400 £7.64.

### AXIAL COOLING FAN

230V AC 120mm square x 38mm 3 blade 10 watt Low Noise fan. Price £7.29 incl. P&P and VAT. Other voltages and sizes available from stock. Please telephone your enquiries.

### INSTRUMENT CASE

Brand new Manuf. by Imhof L31 x H18 x 19cm deep. Removeable front and rear panel for easy assembly of components. Grey finish complete with case feet. PRICE £16.45 INCL. P&P & VAT 2 off £28.20 Inclusive.

### DIE CAST ALUMINIUM BOX

with internal PCB guides. Internal size 265 x 165 x 50mm deep. Price £9.93 incl p&p & VAT. 2 off £17.80 incl.

### 230V AC SYNCHRONOUS GEARED MOTORS

Brand new Ovoid Gearbox Crouzet type motors H 85mm x W 55mm x D 35mm 4mm die shaft x 10mm long. 6 RPM anti cw £9.99 incl p&p & VAT. 20 RPM anti cw Depth 40mm £11.16 incl p&p & VAT.

### SOLID STATE EHT UNIT

Input 230/240V AC, Output approx 15KV. Producing 0mm spark. Built-in 10 sec timer. Easily modified for 20sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (£12.81 inc VAT) NMS

### EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Angst Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £15.00 + £2.00 p&p (£19.98 inc VAT)

### WASHING MACHINE WATER PUMP

Brand new 240V AC. fan cooled. Can be used for a variety of purposes. Inlet 1 1/2in. outlet 1 in. dia. Price includes p&p & VAT. £11.20 each or 2 for £20.50 inclusive.

'C'

FOR

MICROCONTROLLERS

Phone: 01974 282670 or  
Sales@kanda-systems.com

**KANDA**

www.kanda-systems.com

### BASIC COMPILER for PICS

*The answer to your prayers!*

Forget assembly language - use simple but powerful Basic commands and then compile to hex code to program a standard 18, 28 or 40 pin PIC chip.

The MEL PicBasic Compiler from

Pineapple Presentations

Tel (0115) 903 1851 for details

(10.00 + 8.00 - 7 days)


http://www.melabs.com/mel/pbc.htm

### Professional 88-108MHz FM Broadcasting Kits

All Our Kits Include  
Detailed Instructions with Schematics  
High Quality Screen Printed PCBs  
High Quality Components

Our Product Range Includes  
Transmitters from 0.05W to 220W  
FM Stereo Coders  
Audio Compressor Limiters  
Antennas RF Power Amps  
Link Transmitters and Receivers

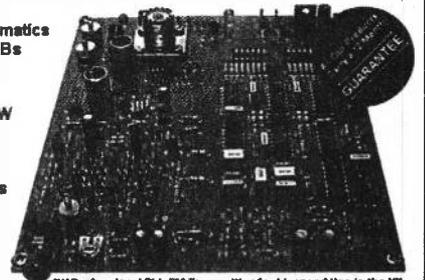Our Kits Are Also Available  
Fully Assembled And Tested



1W Professional PLL FM Transmitter for Licensed Use in the UK

WE DELIVER WORLD-WIDE AND ACCEPT MAJOR CREDIT CARDS

Contact Us Now For A Free Brochure

Tel 01274 883434 Fax 01274 816200

email veronica@legend.co.uk 18 Victoria St, Queensbury  
Bradford, BD13 1AR  
www.legend.co.uk/~veronica/



### £50 BT INSTRUMENT FOR ONLY £7.50

We refer to the BT insulation tester and multi-meter with which you can read insulation directly in megohms, AC volts up to 230, 4 ranges of DC volts up to 500, 3 ranges of milliamps and one 5A range and 3 ranges of resistance. These are in perfect condition, have had very little use, if any, tested and fully guaranteed. Complete with leads and probes £7.50. Order Ref 7.5P4. Carrying case which will take small tools as well, £2 extra. Postage £3 unless your order is £25 and over.

J & N Factors

Dept ETI, Pilgrim Works, Stairbridge Lane, Bolsoy, Sussex, RH17 5PA  
Telephone: (01444) 881965

### PRINTED CIRCUIT BOARDS

### ??? PCB DESIGN OVERLOAD ???

- EDWIN -  
- EED3 -  
- CADSTAR -

WE COULD BE THE ANSWER.  
CONTACT SWIFT DESIGNS LTD

Email: Designs@SwiftDesigns.co.uk

Phone: 01438 310133 - 01438 821811

Web: www.swiftdesigns.co.uk

### PRINTED CIRCUIT BOARDS

PRINTED CIRCUIT BOARDS  
DESIGNED & MANUFACTURED

- PROTOTYPE OR PRODUCTION QUANTITIES
- FAST TURNROUND AVAILABLE
- PCBs DESIGNED FROM CIRCUIT DIAGRAMs
- ALMOST ALL COMPUTER FILES ACCEPTED

EasyPC / Aries / VUTrax / CadStar  
Gerber / HPGL / IDraw and many others.

• ASSEMBLY & TEST AVAILABLE

TELEPHONE 01232 738897

INTERNATIONAL +44 1232 738897

Unit 5, East Belfast Enterprise Park,  
308 Albertbridge Road, Belfast, BT5 4GX

agar FAX - 01232 738897  
Circuits Email - agar @ argonet.co.uk

### PROGRAMMES

## MICRO - ISP

In-system 8051 Programming in a FLASH!

Now supports the AVR Microcontroller Family

Code development for the 8051 family could not be easier. Simply plug the "Socket Stealer Module" into your existing 8051 socket and then use the Micro-ISP Programmer to download code (and data) to your target microcontroller without even removing it from the target socket.

**EQUINOX TECHNOLOGIES**

The Embedded Solutions Company

Sales: 01204 492010 Technical: 01204 491110 Fax: 01204 494883

Visit our web page at: www.equinox.tech.com

Email: sales@equinox.tech.com





STEVENAGE

**Professional Sub-Contract Manufacturing & Suppliers to the Electronics Industry**

Do you have a requirement for any of the following services:

- PCB Assembly (Conventional and Surface Mount)
- Wave & Hand Soldering
- Complete Equipment Manufacture
- Device Programming from hand written sheets or PC 3 1/2" disc
- Cable Harness Assembly/loom Manufacture
- Card Cage and Module Wiring
- Full Inspection
- Product Design/Consultation
- Full Procurement Service
- PCB Test & "Burn in" Facilities
- Enclosure Design & Manufacture
- PCB Artwork Manufacture
- Circuits Drawn Professionally
- Kit Procurement & Supply
- Component Sales
- Refurbishment a speciality
- Top Quality Work at Reasonable Rates

Phone Steve on (01438) 360406 or fax details of your requirements to us on (01438) 352742

EQT LTD, UNIT 5, First Floor, Caxton Point, Bessemer Drive, Stevenage HERTS SG1 2XT

**WIDEBAND SCANNER AERIALS**

"REVCONE" premium quality British VHF/UHF Discone 1.6 element for all-round coverage, SO239 connector £38.95 or N-type connector for improved UHF performance £39.95. "REVCONE PLUS" with improved low frequency coverage £48.95. "REVCONE EXTRA" ready to go package: discone, 10m coax fitted PL259, mast clamps, BNC plug £49.95.

THE "REVCONE" IS THE UK'S ORIGINAL QUALITY DISCONE

**VHF/UHF MOBILE AERIALS**

REVCO premium quality aerials (established 37 years) - full range for Amateur bands. **ASK FOR "AMCAT"**

**"NOMAD" PORTABLE SCANNER AERIAL**

Lightweight design using ribbon cable elements: rolls into a small bundle for ease of transport, hang from any convenient point, ideal for travelling, with 4m coax & BNC plug. £17.95.

**ACTIVE "NOMAD"**

With built-in wideband preamp complete with supply/splitter box (internal battery or external 9 - 15v supply) £29.95.

**SCANNER AERIAL FILTER**

Is your scanner useless due to breakthrough? Then this product could solve your problem: a specially designed tunable filter to be fitted in-line with the aerial feeder, reduces breakthrough from strong VHF signals; (e.g. Band II, pagers, police) also includes HPF to reduce SW & MW interference, BNC connectors £28.95

Write, phone or fax for lists.

Callers by appointment only, please.  
ALL PRICES INCLUDE UK CARRIAGE AND VAT AT 17.5%



**GAREX ELECTRONICS**

Unit 8 Sandpiper Court Harrington Lane Exeter EX4 8NS

Phone: (01392) 466899 Fax: (01392) 466887

**Write in BASIC, Run in a FLASH**

**NEW AVR™ BASIC LITE**

- Compiled BASIC generates tight AVR™ machine code
- Not a Run-Time Interpreter; NO code overhead!
- Target speeds comparable with assembler
- Breaks the cost barrier for small projects
- Ideal for educational, hobbyist and professional use
- AVR™ BASIC LITE only supports the Atmel 90S1200 RISC Microcontroller (512 words code)
- 8K version also available to support entire family

**FROM ONLY £24.95** Excluding Carriage & VAT



Sales: +44 (0) 1204 529000 Technical: +44 (0) 1204 521133 Fax: +44 (0) 1204 535555

Visit our web site on: [www.equinox-tech.com](http://www.equinox-tech.com)

E-mail: [sales@equinox-tech.com](mailto:sales@equinox-tech.com)

**SERVICE MANUALS & Technical Books**

Available for most equipment, any make, age or model.  
Return the coupon for your FREE catalogue

**MAURITRON TECHNICAL SERVICES (ETI)**

8 Cherry Tree Road, Chinnor, Oxon, OX9 4QY,

Tel:-01844-351694, Fax: 01844 352554 email:- mauritron @ dial.pipex.com  
Please forward your latest catalogue for which I enclose 2 x 1st Class Stamps, or £4.11 inc. vat for the complete, Service Manuals Index on PC Disc plus catalogue.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

POSTCODE \_\_\_\_\_

Photocopy this coupon if you do not wish to cut the magazine

**ADVERTISERS INDEX**

Agar Circuits . . . . .	70	Lasertech . . . . .	72
BETA Layout . . . . .	28	Leading Edge . . . . .	38
B.K. Electronics . . . . .	12	Mauritron . . . . .	72
Bull Electrical . . . . .	15, 17	Milford Instruments . . . . .	45
Chelmer Valves . . . . .	45	NCT . . . . .	45
CMS . . . . .	37	No Nuts . . . . .	43
Cooke International . . . . .	71	Pineapple Presentation . . . . .	70
Confidential Communications . . . . .	43	Plancentre Publications . . . . .	71
Crown Hill Associates . . . . .	38	RSGB . . . . .	45
Dataman Programmer Ltd . . . . .	OBC	Scientific Wire Co. . . . .	72
Display Electronics . . . . .	6	Service Trading Co . . . . .	70
EPT Educational Software . . . . .	IFC	Stewarts of Reading . . . . .	24
EQT . . . . .	72	Swift Designs . . . . .	72, 10
Equinox . . . . .	IBC, 72	Techno Info Services . . . . .	37
ESR Electronic Components . . . . .	18	Telnet . . . . .	27
Garex Electronics . . . . .	72	The PC Solution . . . . .	24
J & N Factors . . . . .	8, 70	Variable Voltage Technology Ltd . . . . .	71
JPG . . . . .	43	Veronica FM . . . . .	70
Kanda Systems . . . . .	73	Wilson Valves . . . . .	71
Labcenter Electronics . . . . .	23		

**ATTENTION ALL NORTH AMERICAN READERS!**

Did you know that you can order an annual subscription to this magazine direct from our official U.S. subscription representative?

For more information and rates contact:

**Wise Owl Worldwide Publications**  
4314 West 238th Street,  
Torrance, CA 90505 4509  
Tel: (310) 375 6258

# Practically Speaking

TERRY BALBIRNIE

This month we continue with some of the calculations used in developing and testing circuits.



A single resistor, used to make the meter read in volts

**B**

In this edition and the next, we shall look at how the scale of a pointer-on-scale (analogue) panel meter may be "tailored" to suit the application you have in mind. This month we shall concentrate on making voltmeters, and next time we shall look at milliammeters and ammeters.

## On the panel

These days, it seems that panel voltmeters are less common than those scaled in milliamps or microamps. Even where a voltmeter is available, it often has a scale that is not ideal for the purpose to which the meter is going to be used. For example, you might require a meter to monitor the voltage of a nominal 12V lead-acid battery. When this is fully charged, its terminal voltage may approach 15V. You will therefore need a voltmeter scaled 0 - 15V. It may be possible to buy one scaled 0 - 30V, but then half of the scale would be unused. To make a meter read up to 15V would obviously be better.

Suppose your meter has a 0 - 500 $\mu$ A scale. From the manufacturer's or supplier's data, it is found to have a resistance of 430 ohms. You know that when 15V is applied to a pair of terminals, 500 $\mu$ A must flow through the meter to make it read full scale. The solution is to connect a fixed resistor in series with the meter. Suppose the value of the required series resistor is R. For the moment, forget the resistance of the meter itself - pretend it is zero.

Using Ohm's Law, and remembering that a voltage of 15V applied to the terminals results in 500 $\mu$ A flowing through the meter:

$$R = V/I = 15/0.0005 = 30,000 \text{ ohms (30k)}$$

(500 $\mu$ A is equal to 0.0005A)

However, the meter itself has a resistance of 430 ohms so, in theory, the value of the resistor will only need to have a value of 30,000 ohms minus 430 ohms, that is, 29,570 ohms. You will probably

decide to forget the difference and just use a 30 kilohm resistor since the error is only 1.4 percent. You will need to check the values of the resistors available from stock in the supplier's catalogue. These should be of the 1 percent tolerance metal film type to provide an accurate reading. In some cases, such as this one, the value is obtainable "off the shelf". The procedure is shown in

figure 1.

In many cases it will be necessary to use more than one resistor to make up the correct value. Remember, to find the result of two or more resistors connected in series, you add the values. It is interesting to note that if the tolerance of the required resistor is 1 percent, then connecting any number of 1 percent tolerance resistors in series to obtain this value will still result in an overall tolerance of 1 percent.

Some readers will prefer to use Standard Form (Scientific Notation) when performing the calculations. In this form, 500 $\mu$ A would be called  $5.0 \times 10^{-4}$  A. Use of Standard Form will be the subject of a future Practically Speaking and will not be used here.

A further example will make this all clear.

Example:

You require a voltmeter to read 0 - 25V and you have available a microammeter scaled 0 - 100 $\mu$ A and having a resistance of 3750 ohms.


Using Ohm's Law and remembering that 100 $\mu$ A is equal to 0.0001A:

$$R = V/I = 25/0.0001 = 250,000 \text{ ohms (250k)}$$

In theory, you need only the difference between this and the resistance of the meter - 246,250 ohms. However, as in the last example, the error is very small (about 1.5 percent), so it is probably not worthwhile taking it into account. Since 250,000 ohms (250 kilohms) is not a stock item, you will need to use a 240k resistor connected in series with a 10k unit.

You will need to make a new scale for the meter. The old one is easily removed and may be sprayed matt white. The new numbering may then be applied using dry print lettering.

Figure 1: Using a series resistor to make the meter read volts

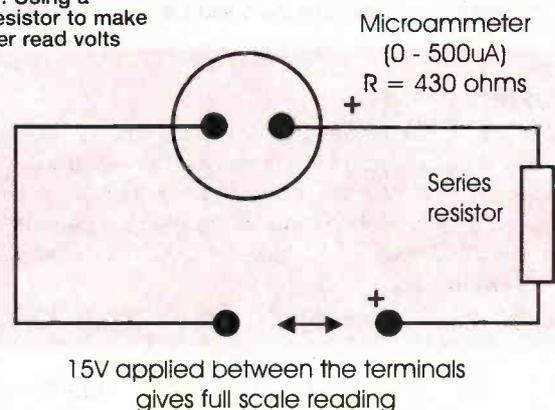

# Around the Corner

## Analogue or Digital?

**A**mong electronics designers there seems to be a division between those who favour digital techniques and those who are happier with

analogue. Sometimes it seems as if there are two different mindsets - but are they?

It is true that individual designers will think first of what they are most familiar with, a fact immortalised in the saying that to the man who has only a hammer, every problem looks like a nail (or simply looks insoluble). We have all seen examples of this - an expensive dsp used where an op-amp, two resistors, and a capacitor would do the job very well, or a complicated circuit of op-amps, diodes, and resistors to put in simple control sequencing that could be done easily with a single CMOS logic chip.

Of course, there is a place for this philosophy: if you have a microcontroller in the system, any amount of code added without actually increasing the prom size is cheaper in production than the cost of a single extra resistor.

Equally, the addition of a couple of diodes to an analogue system to avoid the need for a logic chip, possibly with a different supply voltage, is likely to be the best course. But everything depends on who makes the decision. To do this, the main requirement is to understand a wide range of electronics and, preferably, other engineering disciplines. This understanding need not be sufficiently detailed to undertake advanced design in every field - there is always a time to call in somebody else who has the relevant expertise - but it is at least necessary to appreciate what can be done, approximately how it may be done properly and (of the greatest importance once you move above a single prototype) what the cost will be.

Returning to the area of dsp, who is more likely to design better dsp systems - a designer who understands analogue,

digital, and software to a reasonable standard, or a computer programmer of the highest calibre? Perhaps both, working as a team?

In this era of narrowing specialisations, I suggest that for large projects the team leaders, and preferably a number of other designers, should have as broad a knowledge as possible. Experts in specific fields may be needed to make sure that crucial areas are designed as thoroughly as possible, but it is counterproductive for the dsp expert to write superb code to duplicate the functions of a simple analogue circuit if the dsp is not otherwise needed.

It is interesting that people specialising exclusively in digital design, perhaps because it initially appeared to be a simpler and more efficient solution, free from messy electrical behaviour, are now having to take into account electrical effects that were previously the domain of analogue circuit designers only. The combination of increased bus speeds and the stringent power supply requirements for fast processors forces designers to consider transmission line effects in digital circuit pcb tracks.

As another example, correct placement of decoupling capacitors is vital. If the ground current of a chip as it switches passes the ground connection of another one on its return to the decoupling capacitor, the second chip's ground pin may receive a transient voltage of sufficient level that it interprets certain logic 1 inputs briefly as logic 0.

So the digital designer must now take steps to ensure that the 1s and 0s retain sufficient noise margin under all conditions of bus and power supply loading, before making the bold assumption that they actually will be one or zero when required. The analogue designer would do well to learn enough about digital processing to apply analogue expertise, for example, in coding dsp applications.



Published by  
Nexus Special Interests Limited  
Nexus House, Boundary Way,  
Hemel Hempstead, Herts HP2 7ST  
Tel: 01442 266551 Fax: 01442 266998

Sorry, we cannot answer queries about projects or other technical question on the phone. Please write to the address above. Our admin assistant can often help with other queries about this issue

## EDITORIAL

Editor

Helen Armstrong

Administration Assistant

Sandra Ballantyne

Consultant

Andrew Armstrong

## PRODUCTION

Designer

David Rice

Technical Illustrator

John Puczynski

Production Executive

Marie Quilter

Printed By

Wiltshire Ltd., Bristol

Origination by

Atelier, St. Austell

## SALES

Midland and Southern Area Sales

Andrew Forder

01442 266551

Northern Area Sales

Denise Barrow

0161 776 4460

Group Advertisement Manager

Diane Farnham

## MANAGEMENT

Divisional Managing Director

John Bridges

Business Manager

Stuart Cooke Circulation Manager

William Pearson

Copy Sales Manager

David Pagendam

## SUBSCRIPTIONS


UK: Orders 01858 435344

Enquiries 01858 435322

USA: Wise Owl Worldwide Publications, 4314 West 238 Street, Torrance, CA 90505-4509, USA. For VISA/Mastercard orders phone: (310) 375 6258. Fax: (310) 375 0548. Pacific Time 9am - 9pm weekdays 10am - 6pm weekends. Visa/MC/Discover accepted.
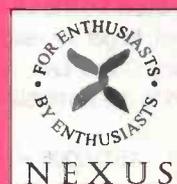
## READERS SERVICES

Back issues (last 12 months) £3.20 per issue if available. Older issues: photocopies of older articles often available. Write to: Photocopy Service, Readers Services Department, at Nexus House, Boundary Way, Hemel Hempstead, Herts HP2 7ST. Binders for ETI: £7.50 each including UK post and packing. Overseas please add £11.50. Cheques to Nexus Special Interests at Nexus House, or phone VISA/Mastercard orders to Readers Services Department 01442 266551



© Nexus Special Interests Limited 1998  
All rights reserved  
ISSN 0142-7229

The Publisher's written consent must be obtained before any part of this publication may be reproduced in any form whatsoever, including photocopies, and information retrieval system. All reasonable care is taken in preparation of magazine contents, but the publishers, editors and their agents cannot be held legally responsible for loss howsoever arising from errors or other published material.

## Next Month

Volume 27 no. 4 of Electronics Today International will be in your newsagents on 27th March 1998 ... Harprit Sandhu opens the door on DIY robotics and his walking robot design ... We have an unusual UHF model radio controller by Geoff Pike GIOGDP in preparation ... Robert Penfold presents the capacitance meter for his inductance-capacitance pair ... PIC-driven Tic Tac Toe for gamers by Rose and Andy Morrell ... plus all the regulars, and more.

Contents are in preparation but are subject to space and availability.

# The Ultimate 8051 Microcontroller Programmer

- Supports Atmel FLASH 89C +89S, Generic 87C51/52/FA/FB/FC microcontroller derivatives
- FLASH & E<sup>2</sup> libraries also available as chargeable update

**NOW  
FROM ONLY  
£125.00**

▲ **£125.00** Order Code: MPW-SYS


## 8051 2K Starter System

For C51 Project Development...in a FLASH  
Includes: Programmer, Evaluation module and PK51-2K ▶

▲ **£199.00** Order Code: AT-89C-2K-ST

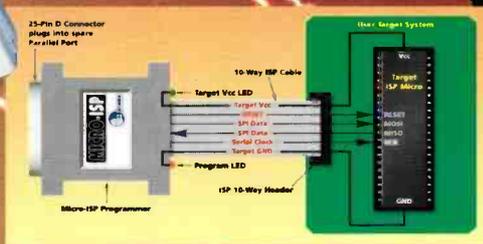
## MICRO-ISP In-System Programming (ISP)

"Now you can program the 8051 or the AVR™ without removing the device from the socket!"



▼ Order Code: AVR-ST **£59.95**

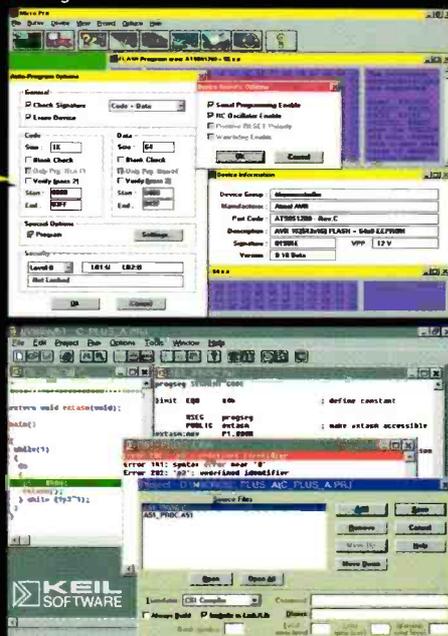▼ Programmer Interface Software for Windows™



▲ Keil 8051 C compiler, Assembler, Simulator (2K code), Windows™ IDE

▲ **£99.00** Order Code: PK51-2K

## 89S Socket Stealer Module

Simply plug this into your existing 8051 or AVR™ socket for **INSTANT** In-System Programming **NO** Target System redesign required.



▲ **£49.00** Order Code: SS-89S-DIL40 ▲

**MICRO-PRO**

**MICRO-ISP**

▲ **£39.95** Order Code: UISP-V2-SYS ▲

# AVR™ Professional Starter System

### FEATURES

- Supports Atmel 90S (AVR) RISC microcontroller family
- Supports Parallel Programming mode in ZIF socket
- Supports In-System Programming via ribbon cable (provided)
- Equinox FAST ISP Programming Algorithm
- All on-chip facilities supported e.g. RC Osc.

### SYSTEM CONTENTS

- Professional Device Programmer
- Atmel AVR™ Assembler
- AVR™ Basic Lite Compiler (NEW)
- Atmel Databook on CD ROM
- Power Supply
- ISP Ribbon Cable (to target)
- Serial Cable (to host PC)

Write in **BASIC**, Run in a **FLASH**

- Compiled BASIC generates tight AVR™ machine code
- Not a Run-Time Interpreter; NO code overhead!
- Target speeds comparable with assembler
- Breaks the cost barrier for small projects
- Ideal for educational, hobbyist and professional use

From Only **£24.95!**

## AVR™ BASIC LITE

- \* AVR™ BASIC LITE only supports the AT90S1200 (512 words code)
- \* 8K version also available

Order Code: AVR-BAS-LIT **£24.95**



The Embedded Solutions Company

# PROVIDING THE SOLUTIONS TO YOUR PROBLEMS!

Tel: +44 (0) 1204 529000  
Fax: +44 (0) 1204 535555

For product information visit our web site at:

[www.equinox-tech.com](http://www.equinox-tech.com)

E-mail: [sales@equinox-tech.com](mailto:sales@equinox-tech.com)

3 Atlas House, St Georges Square, Bolton, BL1 2HB UK



EQUINOX DISTRIBUTORS: AUSTRALIA Farnell +61 2 9645 8888 AUSTRIA Farnell +43 0660 87 75 BELGIUM Alcom Electronics Nv/sa +32 3 227 36 47 BRAZIL HasteC +55 11 522 1799 ANACOM +55 11 453 5588 DENMARK Farnell +45 44 53 66 44 EIRE Farnell +353 1 8309277 FINLAND Farnell +358 9 3455 400 FRANCE Farnell +33 474 65 94 66 NEWTEK +33 1 4687 2200 GERMANY Farnell +49 89 61 39 39 39 INTELTEK GmbH +49 7321 93850, MSC Vertriebs GmbH +49 08 9945532 12 GREECE Microlec +30 1 5395042 4 HONG KONG Farnell 800 968 280 (HK Direct Toll Free) ITALY Farnell +44 113 231 1311 Grifo Italian Technology +39 51 89 20 52, Newtek Italia +39 2 33 10 53 08 MALAYSIA Farnell +60 3 773 8000 NETHERLANDS Alcom Electronics BV +31 10 4519533 ANRATK +31 10 450 4949 Farnell +31 30 241 2323 NEW ZEALAND Farnell +64 9 357 0646 NORWAY ACTE NC +47 63898900 Jakob Hatteland Electronic AS +47 53763000 PORTUGAL Anatronc +35 119 371 834 Farnell +44 113 289 0040 SINGAPORE Farnell +65 788 0200 SPAIN Anatronc SA +34 1 366 01 59 Farnell +44 113 231 0447 SWEDEN ACTE NC +46 8 445 28 70 Farnell +46 8 730 50 00 SWITZERLAND Anatec Ag +41 41 748 32 41 Farnell +41 1 204 64 64 UNITED KINGDOM Abacus Polar +44 1925 626626, Farnell +44 113 263 6311 Rapid Electronics +44 1206 751166 Quarndon Electronics +44 1332 332651 USA Hitools Inc +1 408 298 9077 Newark Electronics +1 800 718 1997, Peachtree Technology +1 770 888 4002 Pioneer Standard +1 888 832 3976

Equinox reserves the right to change prices & specifications of any of the above products without prior notice. E&OE. All prices are exclusive of VAT & carriage. AVR™ is a trademark of the Atmel Corporation

# STILL THE WORLD'S MOST POWERFUL PORTABLE PROGRAMMERS?

£495+VAT



NEW MODEL



£795+VAT

SURELY NOT.  
SURELY SOMEONE SOMEWHERE HAS  
DEVELOPED A PORTABLE PROGRAMMER  
THAT HAS EVEN MORE FEATURES, EVEN  
GREATER FLEXIBILITY AND IS EVEN  
BETTER VALUE FOR MONEY.

ACTUALLY, NO. BUT DON'T TAKE OUR  
WORD FOR IT. USE THE FEATURE  
SUMMARY BELOW TO SEE HOW OTHER  
MANUFACTURERS' PRODUCTS COMPARE.

CIRCLE NO. 103 ON REPLY CARD

## DATAMAN - 48LV

- Plugs straight into parallel port of PC or laptop
- Programs and verifies at 2, 2.7, 3.3 & 5V
- True no-adaptor programming up to 48 pin DIL devices
- Free universal 44 pin PLCC adaptor
- Built-in world standard PSU - for go-anywhere programming
- Package adaptors available for TSOP, PSOP, QFP, SOIC and PLCC
- Optional EPROM emulator

## DATAMAN S4

- Programs 8 and 16 bit EPROMs, EEPROMs, PEROMs, 5 and 12V FLASH, Boot-Block FLASH, PICs, 8751 microcontrollers and more
- EPROM emulation as standard
- Rechargeable battery power for total portability
- All-in-one price includes emulation leads, AC charger, PC software, spare library ROM, user-friendly manual
- Supplied fully charged and ready to use

## S4 GAL MODULE

- Programs wide range of 20 and 24 pin logic devices from the major GAL vendors
- Supports JEDEC files from all popular compilers

## SUPPORT

- 3 year parts and labour guarantee
- Windows/DOS software included
- Free technical support for life
- Next day delivery - always in stock
- Dedicated UK supplier, established 1978

**Still as unbeatable as ever.** Beware of cheap imitations. Beware of false promises. Beware of hidden extras. If you want the best, there's still only one choice - Dataman.

Order via credit card hotline - phone today, use tomorrow.

Alternatively, request more detailed information on these and other market-leading programming solutions.

**MONEY-BACK  
30 DAY TRIAL**

If you do not agree that these truly are the most powerful portable programmers you can buy, simply return your Dataman product within 30 days for a full refund

**hotline**  
01300 320719



Orders received by 4pm will normally be despatched same day.  
Order today, get it tomorrow!

**DATAMAN**

Dataman Programmers Ltd, Station Rd,  
Maiden Newton, Dorchester,  
Dorset, DT2 0AE, UK  
Telephone +44/0 1300 320719  
Fax +44/0 1300 321012  
BBS +44/0 1300 321095 (24hr)  
Modem V.34/V.FC/V.32bis  
Home page: <http://www.dataman.com>  
FTP: <ftp.dataman.com>  
Email: [sales@dataman.com](mailto:sales@dataman.com)