

PRACTICAL

SEPTEMBER 1989 • £1.25

ELECTRONICS

SCIENCE & TECHNOLOGY

WIN
A MAPLIN
TRIPLE-TRACE
OSCILLOSCOPE



HOME SECURITY **CONTROLLER**

Let a Micro Take the Strain
for Property Protection

FREQUENCY COUNTER **AND GENERATOR**

Improve Your Workshop: Build Our
Multifunction Test Gear Project



ASK PE!

A NEW SERIES
OF IN-DEPTH
ANSWERS

MOLE-DETESTER

Be Green-Conscious With Our
Mini Mole Deterrent

MICRONTA[®]

MULTIMETERS FROM TANDY[®]



BENCHTOP DIGITAL LCD MULTIMETER £79⁹⁵

- Measures AC/DC Volts, Current And Resistance
- Manual Or Autoranging Facility

22-195

POCKET AUTORANGING MULTIMETER £19⁹⁵

- Measures To 400V AC/DC
- Includes Mini Probes And Folding Case

22-171



PROBE-STYLE MULTIMETER 22-165

£29⁹⁵

- Fully Automatic Range And Polarity




Tandy[®]

For The Best In High Quality Electronics


Over 400 Tandy Stores And Dealerships Nationwide.
See Yellow Pages For Address Of Store Nearest You.

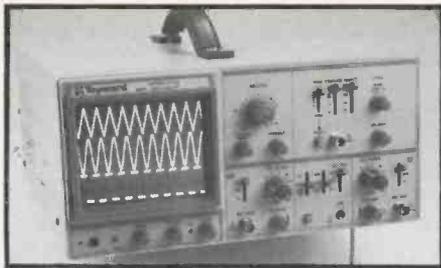InterTAN U.K. Ltd., Tandy Centre, Leamore Lane,
Walsall, West Midlands. WS2 7PS Tel: 0922 710000



Page 61 ▲

Page 12 ▼

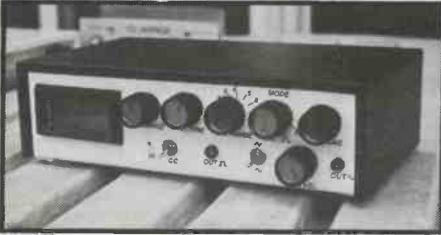

Page 4 ▼



NEXT MONTH

Designed for telescope monitoring, our computer controlled interface can track the heavens or be used for more down-to-earth functions. Are the days numbered for snap-shot films? - Barry Fox examines the emerging electronic technology that could revolutionise the still-photography scene. Transputers already revolutionise significant areas of digital processing, for an elite minority, but anyone with computing experience can learn to use them, as Robert Penfold found when reviewing a new transputer training system. All these features and many more are in an advanced state of preparation - we're already shaping the future for you :

★ DON'T MISS OUR
OCTOBER 1989 ISSUE

★ ON SALE FROM FRIDAY
SEPTEMBER 1ST

★ AND STILL AT ONLY £1.25

★ YOU CAN'T BEAT
OUR VALUE

★ OR OUR HI-TECH
GOOD LOOKS!

PRACTICAL ELECTRONICS

VOL 25 NO 9

SEPTEMBER 1989

CONTENTS

COMPETITION

WIN A MAPLIN TRIPLE-TRACE 20MHZ SCOPE!61

Three Maplin precision laboratory oscilloscopes worth nearly £300 to be won - and one could be yours for the price of a stamp!

CONSTRUCTIONAL PROJECTS

FREQUENCY COUNTER AND GENERATOR by John Becker ..12

Your Ed's new multipurpose workshop test aid: a 4MHz frequency counter with 8-digit lcd, plus integral audio and digital frequency generators.

HOME SECURITY CONTROLLER by Kevin Browne25

Let a hi-tech alarm system monitor your precious property. With microprocessor control, numerous complex facilities can be implemented.

ELECTRONIC MOLE-DETESTER by Edwin Chicken MBE .42

If you're at war with underground mini-miners, reorientate their territorial ambitions with our bleep-squeak humane mole-deterrent.

EASI-BUILD CIRCUIT by John Becker49

In this month's project a simple audio compressor keeps your mono mods in limited peak condition.

64-LINE OUTPUT PORT by R. Milner and A. Horsman52

Another imaginative idea in our Ingenuity Unlimited series. Two innovative PE readers multiplex 64 control lines from an 8-bit source.

SPECIAL FEATURES

HF RADIO - PART TWO by Mike Sanders21

In which we investigate the mysteries of oscillators, phase locked loops, phase detectors, and balanced mixers.

DIGITAL ELECTRONICS by Owen Bishop35

How great an impact does digital electronics have on our lives; what are the benefits, the problems and future prospects; and will you pass the test?

ASK PE - NUMBER ONE by Andrew Armstrong41

"How can I remotely control audio levels?", asks a PE reader. Master-mind Andrew shows one way of doing it in the first of our new query-quest columns.

REGULAR FEATURES

EDITORIAL by John Becker - Consumer scoring9

LEADING EDGE by Barry Fox - Blooming pianos8

SPACEWATCH by Dr Patrick Moore - Voyager 2 and Neptune46

INDUSTRY NOTEBOOK by Tom Ivall - Mergers and takeovers57

PRODUCT FEATURES

MARKETPLACE - what's new, where and when4

BOOKMARK - your Ed looks at some new books45

ARMCHAIR BOOKSHOP - haven for practical bookworms58

PCB SERVICE - professional PCBs for PE Projects60

BAZAAR - Readers' FREE advertising service53

ADVERTISERS' INDEX - locating favourite stockists62

PE TAKES TECHNOLOGY FURTHER - BE PART OF IT!

TANDY PHONES



Representing the latest in active telephone technology the two new Tandy cordless phones offer the facility to receive or make telephone calls anywhere in the office, home, or outside, up to 100 metres from the base unit.

Both the ET1100 and ET1200 telephones offer the following features: The handset will operate up to approximately 100 metres from the base station. A security system which prevents unauthorised use of the telephone line. The handset is powered by nickel cadmium

batteries which are automatically recharged by the base station.

Other features include a low charge indicator; base station may be wall and desk mounted; pushbutton dialling; last number redial facility; easy plug in connection to British Telecom socket; and headset earpiece volume control.

The ET1200 has a memory recall facility and can store up to 16 digits in each of nine memory locations. These numbers can be erased whenever required by storing a new number in the same memory location.



LOOK NO HANDS!

Conducting a telephone conversation when occupied in domestic pursuits has never been easy. Trying to do both usually results in burning the sauce, dripping paint all over the carpet, ruining the flower arrangement or at the very least creating a crick in the neck!

The 'hands-free' operated telephone has been available to the business sector for some time but now Audioline is introducing a hands free telephone, MODEL TEL 38, which is

ideal for active telephone users. The TEL 38 allows the user to conduct a conversation without picking up the receiver and is operated simply by pressing a 'speaker' button when the telephone is ringing.


This stylish phone is also suitable for the design-conscious business as it features tone/pulse switching and compatibility with professional switchboards. Other features include a ten number memory and speaker and ringer volume control.

So whether at home or in the office the Audioline TEL 38 is the telephone you can use with your hands tied! It is available in white, grey and beige at approximately £49.95 from all good telephone stockists.

For further information please contact Liz Bolton and Associates on 01-328-4992/4729.

Both cordless telephones are styled in white and grey. The ET1100 (catalogue no 43-7302) is priced at £69.95, and the ET1200 (catalogue no 43-7303) is priced at £79.95. The telephones are on sale at all 258 Tandy stores and also through selected authorised Tandy dealers.

CATALOGUE

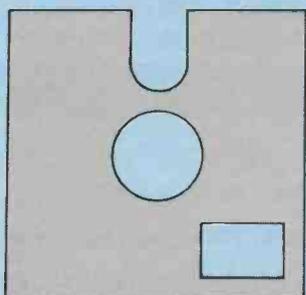

DATABASE

Continuing our alphabetical browse through advertisers' literature.

Cirkit have sent their biggest catalogue I have yet seen. It has over 300 A4 pages which reflect the company's growth in their specialised field of electronic component distribution. Many new names and products have been added, and there's a new and easy to use index which allows component selection by manufacturer, part number or description. With 25 main sections covering alarms to wound components, this catalogue belongs in the workshop of anyone seriously interested in electronic components. Cirkit

Holdings plc, Park Lane, Broxbourne, Herts, EN10 7NQ. 0992 444111.

Compstock have sent a massive computer printout of their semiconductor product ranges, 40 pages of them. In addition to listing the products by type, description and price, they quote the quantity held in stock. A glance down the lists suggests that you are likely to find nearly any semiconductor for which you are searching. This a list you should not miss. Compstock (Hobby) Electronics Ltd, Compstock House, London Road, Stanford le Hope, Essex, SS17 0JU. 0375 360062.

Cricklewood's 1989 component catalogue I gave publicity to a few months back, but as they have been kind enough to send me another, I am only too pleased to mention it again. It has a cover price of £1, but it's an extremely worthwhile cat to have around, with 100 pages, liberally illustrated, full of components and hardware essential to any constructor. They also have quantity price structuring for many items, so you can save money on bulk purchases. Cricklewood Electronics Ltd, 40 Cricklewood Broadway, London NW2 3ET. 01-450 0995.

Display Electronics have sent a News Flyer of several pages highlighting a few of their goods. The flyer lists a variety of products, including acoustic couplers, computer joysticks, computer mains filters, disc drives, motors and pumps, and much more. One interesting product is the Telebox, which they say turns most computer monitors into a quality colour tv, from around £30. Their bundle packs look appetising as well, mixes of components at remarkable prices. Display Electronics, 32 Biggin Way, Upper Norwood, London SE19 3XF. 01-679 4414.

SOLARPHONICS



When Alan Amos, MP for Hexham, and the Greenhead Parish Council asked for lights in the village payphone kiosks at Greenhead in Northumberland, British Telecom stepped in with space-age power, using a solar panel to harness the energy required.

The solar panel charges a battery during the daytime. At night the light operates for around four minutes each time the door is opened, which is usually long enough for most calls. Battery life is extended by using timed lighting periods in this way. The panel is almost maintenance-free, except for the occasional wipe over with a damp cloth by British Telecom

technician Michael Algeo.

Two designs of solar panels are now to be tested in 40 payphones around the country over the next three months.

British Telecom's Payphone maintenance manager in Cumbria, Dave Randall, said "We try to provide lights wherever possible in public payphones. In this case laying on mains electricity was out of the question, so I am very pleased that we have been able to get both of Greenhead's kiosks included in the trial.

"We were looking for sites throughout the UK where a broad range of daylight conditions existed, and Greenhead was considered ideal."

CALL MINDER

The solution to the £6,000 domestic telephone bill could be finally with us, thanks to Britain's leading telephone accessories manufacturer Commtel Consumer Electronics plc. It has just announced the availability of the all British call-barring unit - the Callminder.

Callminder locks into the master



telephone socket and can only be removed by a special key. It gives total control of all outgoing calls from the socket, with the exception of emergency (999), freephone (0800) and operator faults (151) calls which can still be dialled.

In addition, the unique unit enables the worried parent to programme up to seven different call-barring permutations. These range, for example, from local calls permitted at cheap rate only, to restricting STD calls to three minutes. The programming is done from the telephone handset and any calls outside the set programme can only be made via the owners special secret pin number.

Families can regulate the amount of time people spend on the telephone and more importantly, control the numbers that they dial. With

EVENTS DIARY

If you are organising any event to do with electronics, big or small, drop us a line - we shall be glad to include it here.

Please note: Some events listed here may be trade or restricted category only. Also, we cannot guarantee information accuracy, so check details with the organisers before setting out.

Aug. 25-Sep 3. International Audio and Video Fair. Berlin. 01-408 0111.

Sep. 4-6. Eurobus 89 - UK Conference. Novotel Hotel, London. 01-940 4625.

Sep. 12-14. Optical Systems. Ramada Inn, London.


Sep. 12-15. EPOS 89. The World's largest exhibition of retail information systems. Alexandra Palace, London. RMDP. 0273 722687.

Sep. 26-28. British Laboratory Week 89. Incorporating Computer Aided Sciences. Olympia, London.

Oct. 16-20. Systems, Computers and Communications. 11th International Trade Fair and Congress. Munich Trade Fair Centre. 01-948 5166.

Oct. 24-26. Sensors and Systems - International Transducer Exhibition and Conference. Wembley Conference Centre. 0822 614671.

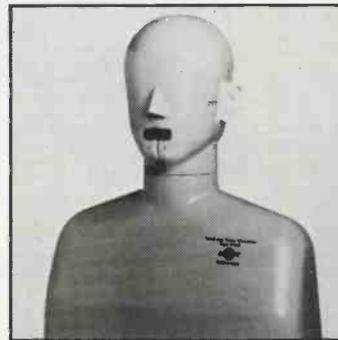Nov. 7-11. Productronica. 8th International Trade Fair for Electronics Production. Munich Trade Fair Centre. 01-948 5166.



BODYTALK!

Available from Bruel & Kjaer is a Head and Torso Simulator (HATS) with a wide range of applications including simulated in-situ and insertion performance measurements on telephones, headsets and hearing aids, evaluation of hearing protectors and close-talking or noise-cancelling microphones, investigation of room acoustics and speech intelligibility, and stereo sound-field evaluation.

The manikin accurately simulates the acoustic field around a human head and torso. It also features a built-in low-distortion mouth simulator which closely replicates the sound field generated by the human mouth, including the frequency-dependent motion of the acoustic centre in the frequency-range which is important for testing noise-cancelling microphones.

For further information on this marvellous manikin, contact: Les Minnikin, Bruel & Kjaer (UK) Ltd, 92 Uxbridge Road, Harrow HA3 6BZ. Tel: 01-954 2366.

Callminder, parents can automatically stop their children spending hours on the phone to their friends, listening to fantasy games and playing interactive video games.

Other than Star Services, which is an on-going rental facility, there is nothing available which offers the same total protection.

Callminder retails at £49.95 and is available from stock.

For further information contact: Steve Harper, Sales Director, Commtel Consumer Electronics plc, Fengate, Peterborough PE1 5XB. Tel: 0733 313444.



BENCH MARK

Now available from Alpha Electronics is a high accuracy $4\frac{1}{2}$ digit multimeter primarily for bench use. Gold Star model DM 7241 had a basic dc voltage accuracy of 0.05%, with all ranges having full overload protection.

Laid out for clear and easy operation the manual ranges and functions are via front panel push buttons. Readings on the large clear 19999 count liquid crystal display can be held by a switchable measured value hold control.

Both dc and ac voltage have five ranges, a 10 microvolt resolution and maximum readings of 1000V and 750V respectively. Alternating and direct current is to 20A in five ranges with a best resolution on the 1.9999mA range of 0.1microA.

Resistance, with its own front panel adjust control for the 199.99 ohms range, goes from 10m ohms to 20M ohms in six very useful ranges. Continuity indication with an audible tone is a separate function.

Housed in a sturdy and robust abs case with an adjustable tilt stand/carrying handle model 7241 measures 210 x 76 x 260mm and weighs 1.5kg. Fully guaranteed by Alpha for 12 months, this latest high accuracy, low cost instrument is supplied with a mains lead for switchable 110V or 240V mains use, test leads, spare fuse and operating instructions. The price quoted is £169 plus vat.

For further information contact: Alpha Electronics Ltd, Unit 5, Linstock Trading Estate, Wigan Road, Atherton, Manchester M29 0QA. Tel: 0942 873434.



PHASE POWER

Newly available from the IR Group is the Kenwood PD Series of benchtop regulated dc power supplies, which employ a novel phase-control technique with a built-in pre-regulator to ensure fast response and efficient high-stability supply of high currents.

Eight models are available in the range: two versions of the PD18 with 0-10A and 0-30A; four versions of the PD35 with 0-36V output at 0-10A or 0-20A and a choice of analogue or digital readouts; the PD56 with an output of 0-110V at 0-5V.

All the units feature high-accuracy voltage setting and excellent temperature characteristics and thermal response. Remote sensing and protection against overvoltage, overcurrent and overheating are provided as standard, and voltage and current limits are indicated by leds.

The PD Series is available from the IR Group on a sales, rental or leasing basis.

Contact: IR Group, Doran House, Meadfield Road, Langley, Slough SL3 8AL. Tel: 0753 44878.

SOARING VALUE

SOAR's newest series of cost-saving, value rated, digital multimeters feature 3200 counts, $3\frac{1}{2}$ digit readout, full scale analog bar graph displays and lsi circuit technology for enhanced accuracy, high sampling speed and operating ease.

Available from Solex International, the SOAR hand held multimeters, models 3210/3220/3230, incorporate manual and auto ranging circuits; high speed sampling for the 32 segment analog bar graph display, which is many times faster than numerical displays; and resolutions far better than conventional $3\frac{1}{2}$ digit dmm's. An important added benefit is the longer battery life - 2500 hours of operation or more from normal alkaline "AA" battery cells. This is directly attributed to use of the special lsi circuit design. Audible continuity and diode testing functions are also included.

Durable and built for easy, long term use, the new models are rated as follows: Model 3210 - 0.7% basic accuracy with high speed auto ranging and 10 amp current measurements, ac/dc; Model 3220 - 0.5% basic accuracy with 30mA to 10A ac/dc current measurements with auto ranging function; Model 3230 - 0.35% basic accuracy, auto or manual ranging with measurements of 300 micro A to 10A, ac/dc current ranges.

All models are supplied with one set of test leads, two AA 1.5V batteries, a spare fuse and an instructional manual. Solex International are sole UK agents for SOAR products.

For further details, together with a free copy of their full test and measurement catalogue, contact Solex International, 95 Main Street, Broughton Astley, Leics LE9 6RE. Tel: 0455 283486.



DELTA LIGHT

The new HD8366 from Delta Ohm is a digital light meter that may be used for measuring lighting levels outside and inside buildings for scientific or industrial purposes, accident prevention, aesthetics and agriculture.

Electricians and lighting experts, accident prevention officers (checking against glare or insufficient lighting), architects, designers of stands for exhibitions and fairs, decorators and horticulturists have all found that this portable lightmeter is a reliable measuring instrument.

Being a digital instrument, there is

no risk of possible damage due to intense lighting, a fault commonly found in instruments using a traditional analogue meter. A self-zeroing circuit allows the measurement of a very low lighting levels with excellent stability.


Most commercial light meters use a selenium cell as the sensor, as its spectral response is very similar to that of the human eye. Selenium cells, however, have the disadvantage of the so-called "memory effect" (the value indicated may be influenced by the previous readings, particularly



readings taken with a high degree of lighting). For this reason the HD8366 uses a silicon sensor, which does not possess this disadvantage.

The spectral response has been adapted to that of the human eye by means of a filter fitted onto the sensor, with an integral error of less than 4%. The linearity of the sensor is better than +1% in the field from 0 to 100,000 lux and +1.4% in the field from 100,000 to 200,000 lux.

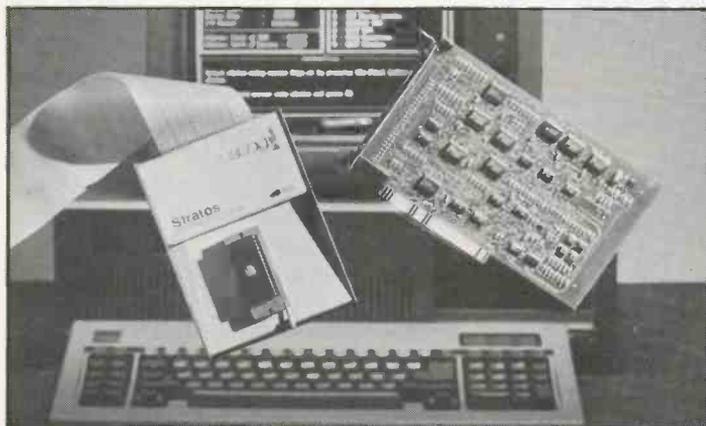For further information contact: Delta Ohm, PO Box 81, Worthing, Sussex BN14 3PW. Tel: 0903- 214335.



PC BASED EPROM PROGRAMMER

Stag have introduced the first high quality programmer in their range specifically designed for use with any PC, (IBM PC, XT, AT or compatible), and catering for all the most common eprom device types. Known as Stratos, it is priced at a competitive £249.

Stratos has been completely designed by Stag in the UK and is manufactured, using the latest smd technology, in their own fully automated Welwyn Garden City factory. It consists of a PC-bus compatible interface card which fits inside the computer together with a cable connected to an external unit which is the programming site for the device. The interface card is less than half the length of a standard PC expansion card format, allowing it to be installed in any slot in a PC or compatible computer. The interface operates reliably in any system, independent of clock speed. Full protection is offered to the

motherboard and bus loading is minimal.

At the remote programming site, a 32-pin, wide blade zif socket is used to accept the device to be programmed. This is housed in a robust metal casing and all connections are short circuit protected and current limited, preventing damage. A single led indicates when the unit is 'busy'. Like all Stag programmers, this PC based system performs a range of integrity tests in addition to simply programming the device. The hardware caters for all variants of Vpp and Vcc, including programming and verification at elevated voltages. All approved programming algorithms are used including Snap, Flashrite, and QuickPulse.

For further information contact: Stag Electronic Designs Limited, Stag House, Tewin Court, Welwyn Garden City, Herts AL7 1AU. Tel: 0707 332148.

BARCODE PC CARD

The special products division of Multiprobe Limited has launched the Multibar PC Card. By simply slotting the card into their computer, existing IBM PC or compatible users can now enjoy the benefits of barcode scanning, printing and verifying at a fraction of the usual cost.

At just £499 plus vat, the card is ideal for those companies wishing to take advantage of a flexible and competitively priced barcoding system on the factory floor, or in the shop or warehouse. With Multibar,



say the makers, you can produce almost any type of barcode label from your existing PC terminal, using the printer you would normally use for wordprocessing.

Comprehensive print facilities are available and these include negative and mirror image printing, image rotation, serialised output (increment and decrement), and the reproduction of company and product logos on the barcode label itself. Label formatting is extremely flexible with Multibar and can be previewed on screen prior to printing.

Multibar will operate in conjunction with all the recognised input devices - ccd scanner, wand, laser - and a wide range of printers. For example, 9 and 24 pin dot matrix printers, ink jet and laser printers, thermal and thermal transfer printers. **For further details please contact:** Kevin Cookson, Multiprobe Limited, Rock Bank, Clarence Road, Bollington, Macclesfield, Cheshire SK10 5JZ. Tel: 0625 74505.

CHIP COUNT

This month we highlight one of the industry's first fully integrated smart H-bridge power ics, jointly developed by National Semiconductor and International Rectifier.

LMD18200

The LMD18200 H-bridge driver, targeted at the smart-power market, can drive dc and stepper motors up to a quarter-horsepower. Integrated on the single chip are four power dmos transistors and control logic, which includes internal current sensing, output short-circuit protection and two-stage thermal shutdown capability.

The features, performance, reliability and size of the LMD18200 make it perfectly suited for use in many motor-control applications. They include computer peripherals, such as tape and disc drives, printers and plotters, office equipment like scanners, copiers and fax machines, and automation - ie robots.

Before the introduction of this chip, designers required separate power transistors and logic components in order to construct an H-bridge power ic. With the new device, they save time and enjoy the advantages that integrated intelligence brings to system designs. The 3-amp H-bridge is fabricated with a multiple-technology process that uses cmos and bipolar control technology at the front end and dmos fet power devices as the outputs. The circuit operates at supply voltages from 12 to 55 volts, with a continuous output of 3A (6A peak).

The on-resistance of each of the four output mosfets is 0.3 ohms, and turn-on/turn-off switching times are typically 100ns. Input voltage requirements provide high noise immunity and are cmos and ttl compatible. The device interfaces with pulse-width modulation input signals and is suitable for both locked antiphase (one-wire) or sign-magnitude (two-wire) forms.

The H-bridge uses Hexsense current sensing, introduced by IR and integrated with its Hexfet power mosfet discrete technology. Hexsense circuits are nearly lossless and eliminate the need for external low resistance, high thermal dissipation series sensing resistors.

Two stage thermal shutdown sends a warning flag to the host system at 135°C and the device shuts down at 170°C. This feature prevents equipment damage or human injury in motion systems, and allows orderly computer system shutdowns.

The LMD18200 H-bridge is offered in an 11-pin plastic power single-in-line package. Power dissipation at a case temperature of 75°C is 25 watts in free air at an ambient temperature of 25°C. Maximum junction temperature is 150°C, and the ambient operating temperature range is -40°C to +125°C.

Fig.1 shows the basic block diagram as published by National.

For further information contact: National Semiconductor (UK) Ltd, The Maple, Kembrey Park, Swindon, Wilts, SN2 6UT. 0793 614141.

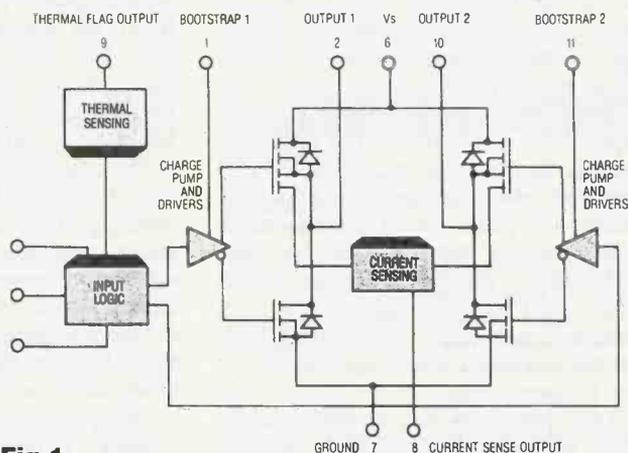



Fig.1.

An anyone who works in an office, or uses a wordprocessor, will know that daisy wheel printers and typewriters make a truly horrid noise. It is the price you pay for letter quality text. But perhaps not any more.

Ten years after making the daisy wheel head a world standard of LQ printers, the Xerox Corporation has acknowledged that it creates a "cloud of noise". The company says its Palo Alto Research Centre has spent four years and \$40 million developing Piano, a daisy wheel which sounds much quieter.

The design change is so radical that offices must buy new machines to benefit, starting at over £1000 each. Xerox says it has "no plans" to licence Piano technology to competitors.

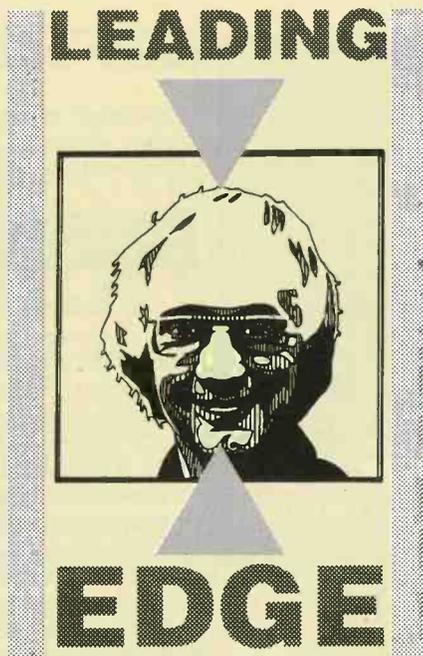Piano was developed by Dr Andrew Gabor whose company, Diablo, invented the original daisy wheel in 1972. Xerox bought Diablo, and licensed manufacturers round the world to use what Gabor



spokes near the centre, rather than the tyre at the edge. He stresses the lack of audibility of the sound produced and theorises that it would be impossible to cram enough Pianos into one room, however large, to produce sound as loud as from one conventional daisy wheel machine. Piano is undoubtedly very quiet but the machines demonstrated in London emitted a potentially disturbing low frequency drumming sound which could well prove irritating and fatiguing in an office, especially if several machines were in use at the same time. Xerox admits to the problem, but says it was caused because the tables used for the launch demonstration were "monstrosities". It does seem odd that a company the size of Xerox, launching a new concept as potentially important as Piano, should hire a theatre for the launch and put the prize exhibit on totally unsuitable tables.

Also there is considerable confusion over the audio effect which Piano

BLOOMING PIANOS

describes as "the most valuable patents ever owned by Xerox". The new invention takes advantage of the fact that the ear is less sensitive to low frequency noise. It pushes the frequency of the impact noise from the wheel down in frequency.

It is surely no coincidence that Xerox is offering Piano at a time when the original daisy wheel patents are approaching the end of their life and the computer industry is turning to ink jet printers as a way of achieving letter quality text with almost no noise.

Although Piano uses clever tricks to make a daisy wheel sound much quieter, the demonstration machines used by Xerox for a grand launch at a London theatre recently showed potential flaws in the system. Also Xerox has offered confusing and contradictory technical data on the sound produced. The Health and Safety Executive says it would like to see more technical evidence before giving the system an official blessing.

Daisy wheel printers make a nasty impact noise when flexible leaf hammers, carrying the negative impression of text characters, slam into paper on a backing platen. The platen briefly deforms into a dimple which behaves like a tiny loudspeaker. Because the mass of the daisy wheel leaf is small, only 2 or 3 grammes, its resonant frequency is high and the percussive sound spreads over a high frequency band.

Gabor rejects the idea of using ink jet, which he refers to dismissively only as

BY BARRY FOX
Winner of the
UK Technology Press Award

**Hit a key, any key.
The silence is
deafening.**

"other non-impact" technologies. While still culling royalties from daisy wheel impact technology, Xerox could not risk making it obsolete. So Xerox PARC researchers were stuck with the obligation to improve the daisy.

Gabor found it was impractical to kill the sound by changing the platen, because there was then incompatibility with existing papers and inks. So he tried to lower the resonant frequency, and thus push the sound down in frequency, to make it less intrusive. It was also impractical to increase the mass of the leaves, so he combined two tricks.

The physical mass of each daisy wheel leaf is increased to 1.2kg, by directly coupling it to a lever mechanism and heavy metal bale bar driven by a motor with heavy armature. The effective mass of the lever mechanism is also increased to 2.25kg by connecting the levers close to the axis of rotation of the bale arm. This increases the moment of inertia.

Gabor compares this to the difficulty of stopping a bicycle wheel by grabbing

achieves. Xerox cites conventional daisies as generating between 60dB and 80dB, with Piano at 46dB. Xerox employed Dr Geoff Leventhal, head of the Institute of Environmental Engineering at the Southbank Polytechnic, as a consultant. Leventhal used techniques specified by the International Standards Organisation, ISO, to measure between 64dB and 68dB, from old machines and 54dB from Piano.

Dr Gabor says that dropping the sound by six octaves, halving the frequency six times, makes the pitch "so low it is hardly heard". Dr Leventhal says he found the peak energy to be at between 500 and 1000Hz but admits he is not so sure about the six octave drop, which would put Piano's sound output into the infrasonic band. Dr Gabor sticks to his six octave claim but quotes much higher frequencies of conventional daisies.

Xerox says the sound levels quoted are all on the "A" scale to match human hearing and differ widely because they were taken at different distances from the machines. Xerox says it is confident that there is no risk of long term fatigue from the low frequency noise.

The Health and Safety Executive is keeping an open mind.

"If low frequencies become dominant, the dull drumming sound could cause irritation after a while" says the HSE. "We need to see a frequency spectrum for old machines, and new machines. That is only to see exactly what Piano is doing".

So far Xerox has released no such quantifying data.

In my editorial comment of PE July 89, I enthused over the excitements and benefits of Exhibitions. For me, they probably rate as the most potent source of information on how the technological world is developing. Coming not far behind in my ratings, are Reports - the busy person's guides to the universe without hitch hiker's leg-ache.

Ferguson have been so kind as to save me a lot of leg-ache, and telephonist's ear-ache, by sending me a report on the Consumer Electronics scene.

We all know that consumer electronics are now a vital part of our daily lives. Ferguson's report says that we spent £4500 million pounds on related products in 1988. An amazing sum, but all is not yet rosy for manufacturer's bank balances. In the last quarter of 1988 there was a reduction in growth, as a result of Government efforts to curb consumer spending. With this pressure likely to continue throughout 1989, Ferguson predict difficult times ahead for manufacturers.

One area likely to suffer is satellite tv. Ferguson's research indicates that whilst there is potential for a considerable satellite tv market, it is likely to develop more slowly than many people, particularly the broadcasters, had hoped. Despite the reasonable levels of consumer interest shown in satellite tv, apparently their current intention to purchase is at a relatively low level, with around only 14% of those interviewed interested in receiving the new channels

PRACTICAL ELECTRONICS



CONSUMER SCORING

on offer. Not surprisingly, many prospective purchasers seem unwilling to pay subscription fees for film channels, an obvious blow to the broadcasters to whom the fees are one of the main revenue sources.

Furthermore, the confusion over the two competing and incompatible systems of Sky and BSB is causing the majority of respondents to wait until they know what programmes are on offer. However, once Sky encrypts and BSB is in operation, the demand is likely to increase.

Those involved in tv generally can probably also take heart from the fact the tv viewing is reportedly the UK's favourite activity. (Odd - I thought reading PE and doing electronics would have been ...) In 1988

purchases of colour tvs grew by 9% to 4.4 million. With nearly 100% of the UK population already owning sets, over half the tvs were bought as additional sets. Only 4% of sales were first-time purchases. Interestingly, sales of small screen sets have overtaken those of large screen.

Video penetration grew from 50% in 1987 to 64% in 1988, though the market is forecast to decline in 1989. Long play video recorders, however, are likely to continue increasing their market share. I, for one, have been converted to regarding long play recorders as beneficial - there can be few aggravations worse than running out of tape because of programme mistiming! Sales of hifi stereo models are forecast to rise with increased consumer awareness, and the introduction of more Nicam models. At the top end of the market, Super VHS will continue to find popularity.

Surprisingly, although video photography is growing, only about 1.5% of the UK participates and we are well behind other Western countries in taking up this activity.

The audio market findings are also revealing - in brief, 82% of us have stereo systems and 12% have more than one, while 13% of us own compact disc players.

Although not covered by Ferguson's report, one consumer area that could soon make an enormous impact is electronic still photography. Barry Fox will be taking a look at this next month - a full length feature well worth reading.

THE EDITOR

Editor:

John Becker

Sub-Editor:

Helen Armstrong

Technical Illustrator:

Derek Gooding

Advertisement Sales:

Sarah Holtham

Business Manager:

Mary-Ann Hubers

Circulation:

David Hewett

Publisher:

Angelo Zgorelec

Editorial and Advertising Address:

Practical Electronics,
Intra House, 193 Uxbridge Road,
London W12 9RA
Tel: 01-743 8888
Telecom Gold: 87: SQQ567
Fax: 01-743 3062

Advertisements

All correspondence relating to advertise-



ments, including classified ads, should be addressed to: **The advertisement department, Practical Electronics, at the above address and telephone number.**

Readers' Enquiries

All editorial correspondence should be addressed to the editor and any letters requiring a reply should be accompanied by a stamped addressed envelope, or equivalent payment.

We regret that lengthy technical enquiries cannot be answered over the phone.

Subscription Address:

Practical Electronics, Subscription Dept.,
P.O. Box 500, Leicester LE99 0AA.

Annual Subscription Rates:

U.K. £15.00 Overseas £18.00

Cover Illustration

Mark Taylor

© Intra Press 1989. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. All material is accepted for publication on the express understanding that the contributor has the authority to permit us to do so. **ISSN 0032-6372**

Published on 1st Friday of each month by Intrapress, 193 Uxbridge Road, London W12 9RA. Typesetting, artwork and film by Gilfillan Ltd. Mitcham, Surrey and printed in England by McCorquodale Magazines Ltd. Andover, Hants. Distributed by Seymour Press 01-679 1899. PRACTICAL ELECTRONICS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

MAGENTA ELECTRONICS Ltd

PROJECT KITS

Magenta supply Full Kits: Including PCB's (or Stripboard), Hardware, Components, and Cases (unless stated). Please state Kit Reference Number, Kit Title and Price, when ordering. REPRINTS: If you do not have the issue of P.E. which includes the project, you will need to order the instruction reprint as an extra: 80p each. Reprints are also available separately - Send £1 in stamps. Magazine dates refer to Everyday Electronics.

REF NO.	KIT-TITLE	PRICE	REF NO.	KIT-TITLE	PRICE
812	ULTRASONIC PET SCARER May 89	£13.80	581	VIDEO GUARD Feb 87	£8.39
811	MIDI PEDAL Mar 89	£39.98	584	SPECTRUM SPEECH SYNTH. (no case) Feb 87	£20.92
810	MIDI MERGE Mar 89	£11.59	578	SPECTRUM I/O PORT less case Feb 87	£9.44
809	CALL ALERT Mar 89	£13.51	569	CAR ALARM Dec 86	£12.47
807	MINI PSU Feb 89	£22.71	563	200MHz DIG. FREQUENCY METER Nov 86	£62.98
806	CONTINUITY TESTER Feb 89	£10.28	561	LIGHT RIDER LAPEL BADGE Oct 86	£10.20
505	4 CHANNEL LIGHT DIMMER Feb 89	£37.99	560	LIGHT RIDER DISCO VERSION	£19.62
803	REACTION TIMER Dec. 88	£29.98	559	LIGHT RIDER 16 LED VERSION	£13.64
802	PHASOR (Light Controller) Dec 88	£25.61	556	INFRA-RED BEAM ALARM Sept 86	£28.35
801	DOWBEAT METRONOME Dec 88	£17.57	544	TILT ALARM July 86	£7.82
800	SPECTRUM EPROM PROGRAMMER Dec 88	£26.97	542	PERSONAL RADIO June 86	£11.53
796	SEASHELL SYNTHESISER Nov 88	£24.99	528	PA AMPLIFIER May 86	£26.95
795	LR. OBJECT COUNTER Nov 88	£29.63	523	STEREO REVERB Apr 86	£26.44
790	EPROM ERASER Oct 88	£24.95	513	BBC MIDI INTERFACE Mar 86	£27.94
786	UNIVERSAL NICAD CHARGER July 88	£6.99	512	MAINS TESTER & FUSE FINDER Mar 86	£8.82
780	CABLE & PIPE LOCATOR April 88	£15.35	497	MUSICAL DOOR BELL Jan 86	£18.72
775	ENVELOPE SHAPER Mar 88	£14.99	493	DIGITAL CAPACITANCE METER Dec 85	£41.55
769	VARIABLE 25V-2A BENCH POWER SUPPLY Feb 88	£48.73	481	SOLDERING IRON CONTROLLER Oct 85	£5.47
	CAR LAMP CHECKING SVST. Feb 88	£7.10	464	STEPPER MOTOR INTERFACE FOR THE BBC	
763	AUDIO SIGNAL GENERATOR Dec 87	£13.64		COMPUTER less case Aug 85	£11.68
739	ACCENTED BEAT METRONOME Nov 87	£20.95		1035 STEPPER MOTOR EXTRA	£14.50
744	ACOUSTIC PROBE Nov 87 (less bolt & probe)	£16.26		OPTIONAL POWER SUPPLY PARTS	£5.14
740	VIDEO CONTROLLER Oct 87	£29.14	461	CONTINUITY TESTER July 85	£6.20
745	TRANSTEST Oct 87	£9.70	455	ELECTRONIC DOORBELL June 85	£7.56
734	AUTOMATIC PORCH LIGHT Oct 87	£17.17	453	GRAPHIC EQUALISER June 85	£26.94
736	STATIC MONITOR Oct 87	£8.66	444	INSULATION TESTER Apr 85	£19.58
723	ELECTRONIC MULTIMETER Sept 87	£46.96	430	SPECTRUM AMPLIFIER Jan 85	£6.91
728	PERSONAL STEREO AMP Sept 87	£14.31	392	BBC MICRO AUDIO STORAGE SCOPE	
730	BURST-FIRE MAJNS CONTROLLER Sept 87	£13.57		INTERFACE Nov 84	£36.25
724	SUPER SOUND ADAPTOR Aug 87	£38.39	387	MAINS CABLE DETECTOR Oct 84	£5.53
718	3 BAND 1.6-300MHz RADIO Aug 87	£26.53	386	DRILL SPEED CONTROLLER Oct 84	£8.68
719	BUCCANEER I.E. METAL DETECTOR inc. coils and case, less handle and hardware July 87	£26.45	362	VARI-CAP AM RADIO May 84	£13.15
720	DIGITAL COUNTER/FREQ METER (10MHz) inc. case July 87	£67.07	337	BIOLOGICAL AMPLIFIER Jan 84	£24.14
722	FERMOSTAT July 87	£12.14	263	BUZZ OFF Mar 83	£5.68
711	VISUAL GUITAR TUNER Jun 87	£22.99	242	2-WAY INTERCOM no case July 82	£5.69
715	MINI DISCO LIGHT Jun 87	£12.59	240	EGG TIMER June 82	£6.86
707	EQUALIZER (IONISER) May 87	£15.53	205	SUSTAIN UNIT Oct 81	£17.63
700	ACTIVE I/R BURGLAR ALARM Mar 87	£35.65	108	IN SITU TRANSISTOR TESTER Jun 78	£9.42
			106	WEIRD SOUND EFFECTS GEN Mar 78	£7.82
			101	ELECTRONIC DICE Mar 77	£6.26

'EQUALISER' IONISER



KIT REF 707 £15.53

A mains powered Ioniser that produces a breeze of negative ions in the air. A compact, safe, simple unit that uses a negligible amount of electricity.

ULTRASONIC PET SCARER



Produces high power ultrasound pulses. L.E.D. flashes to indicate power output and level. Battery powered (9V-12V or via *Mains Adaptor).


KIT REF 812 £13.80
*Mains Adaptor £1.98

DIGITAL FREQUENCY 200 MHz METER

KIT REF 563

£62.98

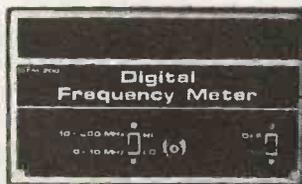An 8 digit meter reading from A.F. up to 200 MHz in two ranges. Large 0.5" Red LED display. Ideal for AF and RF measurements. Amateur and C.B. frequencies.




VISUAL GUITAR TUNER



Crystal controlled, with a super rotating LED display. Indicates high, low, and exact degree of mistuning. Use with pick-up or mic. Also has audible output.

KIT REF E711 £21.99

3 BAND SHORTWAVE RADIO

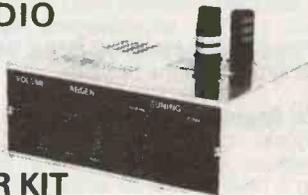


OUR KIT REF 718 £26.53

Covers 1.6-30 MHz in 3 bands using modern miniature coils. Audio output is via a built-in loudspeaker. Advanced design gives excellent stability, sensitivity and selectivity. Simple to build.

TOP KITS

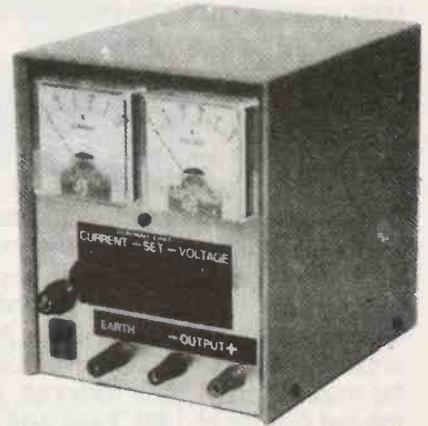MOSFET VARIABLE BENCH 25V 2.5A POWER SUPPLY




A superb design giving 0-25V and 0-2.5A. Twin panel meters indicate Voltage and Current. Voltage is variable from zero to 25V. Current-Limit control allows Constant Current charging of NICAD batteries, and protects circuits from overload. A Toroidal transformer MOSFET power output device, and Quad op-amp IC design give excellent performance.

OUR KIT REF. 769 £49.73

COMPONENTS, KITS, BOOKS, TOOLS, MOTORS, GEARS, PULLEYS, OPTICAL FIBRES, ROBOTICS, AND MUCH MUCH MORE - IN OUR CATALOGUE £1.00

MOTOR-GEARBOX ASSEMBLIES

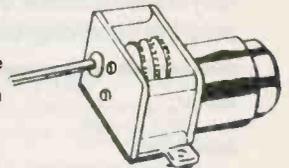Miniature gearboxes complete with quality electric motor. Variable ratios by fitting 1 to 6 gears. 1.5-4.5v, 3-2200 rpm. Long 3mm shaft. Ideal for robots and buggies.



SMALL (MGS) £3.49 LARGE (MGL) £3.98

ADVENTURES WITH ELECTRONICS

BOOK £4.75 PACK £20.98
An easy to follow book suitable for all ages. No soldering, uses an S DEC breadboard. Lots of clear diagrams and instructions to build 16 projects. Component pack includes S DEC and all components for the projects.

LEGO Technic Sets
TEACHERS WE ARE STOCKISTS OF THE WHOLE RANGE. CONTACT US FOR BROCHURES. VERY COMPETITIVE PRICES AND QUICK DELIVERIES

STEPPING MOTORS 12 VOLT

48 STEPS 1035 £14.50
200 STEPS MD200 £18.80

OPTICAL FIBRES TRIAL PACK OF 10 METRES.
Nine assorted types & data.

£1.99

0283 65435



MAGENTA ELECTRONICS LTD
 PE 13 HUNTER STREET,
 BURTON-ON-TRENT,
 STAFFS. DE14 2ST.
 0283 65435, Mon-Fri 9-5 Sat 9-2
 Access/Barclaycard (Visa) by
 phone or post.
 24 hr Answerphone for credit
 card orders.
 Our prices include VAT

ADD £1 P&P TO ALL ORDERS.
 PRICES INCLUDE VAT.
 SAE ALL ENQUIRIES.
 OFFICIAL ORDERS WELCOME
 OVERSEAS: Payment must be
 sterling.
 IRISH REPUBLIC and BFPO. UK
 PRICES.

FROM MAGENTA

A SELECTION OF OUR BEST PROJECT KITS

As usual these kits come complete with printed circuit boards, cases, all components, nuts, screws, wire etc. All have been tested by our engineers (many of them are our own designs) to ensure that you get excellent results.

INSULATION TESTER


An electronic High Voltage tester for mains appliances and wiring. An inverter circuit produces 500 volts from a PP3 battery and applies it to the circuit under test. Reads insulation up to 100 Megohms. Completely safe in use.



OUR KIT REF 444 £19.58

DIGITAL CAPACITANCE METER

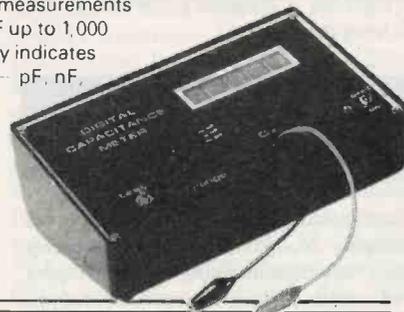Simple and accurate (1%) measurements of capacitors from a few pF up to 1,000 uF. Clear 5 digit LED display indicates exact value. Three ranges — pF, nF, and uF. Just connect the capacitor, press the button and read the value.



£41.55
 OUR KIT
 REF 493

MAGENTA

LOWCOST

68000

**CROSS-ASSEMBLER
 FOR BBC. ALSO
 AVAILABLE
 £60.00
 (DISK)**

**68020
 PLUG-IN UPGRADE
 NOW AVAILABLE
 PLEASE ASK FOR DETAILS**

**USED
 BY SCHOOLS
 COLLEGES &
 UNIVERSITIES
 U.K & WORLDWIDE**

**MICROPROCESSOR
 TRAINER
 AND SINGLE
 BOARD
 COMPUTER**

***PERFECT FOR ROBOTICS
 APPLICATIONS REQUIRING
 POWER AND SPEED***

**KIT PRICE
 £110 INC VAT**

**OTHER OPTIONS, DATA PACKS,
 AND LITERATURE AVAILABLE
 — SEND FOR DETAILS.**

- Full 8MHz 68000 Processor with 16 bit data bus.
- Top-class monitor program included on two Eproms.
- Communicates via RS232 Interface to terminal, BBC computer, P.C. computer etc.
- Use as a Trainer, or as a stand-alone computer system.
- Fast, powerful processing — ideal for real time control systems.

- Dual U.A.R.T. allows simultaneous connection of printer and terminal.
- Add-on options include: G64 Bus, 68230 P.I.T. 8k and 32k Ram upgrades, and line by line assembler.
- Available from stock now — with support literature and full technical back up.


STANDARD SYSTEM IN KIT FORM (Ref 600)	£110.00	68230 P.I.T. ADD ON OPTION (Ref 603)	£ 11.97
STANDARD SYSTEM BUILT & TESTED	£190.00	G64 BUS ADD-ON (Ref 604)	£ 5.49
LINE BY LINE ASSEMBLER PROGRAM (IN EPROM)	£ 27.00	8K x 16 RAM UPGRADE (Ref 605)	£ 19.25
POWER SUPPLY (Ref 609)	£ 13.99	32K 16 RAM UPGRADE Ref 606	Phone

As part of the competition we held in PE Feb 89 we also ran a mini-survey on the types of test gear you rated as workshop favourites. Regular readers will have seen that from the results published in the June issue signal generators came fourth, and frequency counters came eighth. I commented at the time that I agreed with the fourth position but regarded a frequency counter as the fifth most important.

COUNTING IMPORTANCE

Confirmation of that importance was thoroughly brought home to me recently when I was experimenting with a complex set of circuits relating to precision analysis of certain long wave radio transmissions. All five principle categories of test gear were in use, two digital multimeters, a multi-trace scope, two power supplies, two signal generators and a frequency counter. As the circuit complexity and monitoring requirements grew, so too did my frustration. It became increasingly obvious that the signal generators and the frequency counter had seen better days and were showing acute signs of senile dementia.

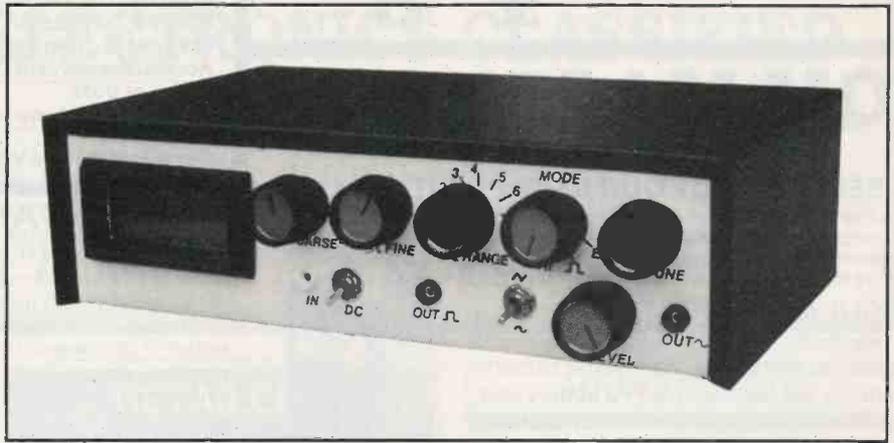The stabilities of the tuning controls and range switches were the main problems with the generators, though the XR2206



The Editor's completed unit

By counting time as a frequent function your Ed bridges the generation gap with his multipurpose workshop test aid.

8-DIGIT COUNTER

Browsing through the catalogues of many PE advertisers and other suppliers, I found that Cirkit sell a PCIM300 8-digit lcd up/down counter which appeared to meet my needs. It features 8mm display height, Schmitt trigger clock input, leading zero blanking, and store and reset inputs for operation as either a frequency or period counter. It has a power supply operating range of 3V to 6V, drawing only 1.7mA.

The internal circuit is based on two synchronously cascaded MM74C947 four-digit counter circuits which directly drive

FREQUENCY COUNTER AND DUAL-GENERATOR

BY JOHN BECKER

vco chip of one of them seemed to have developed an internal linearity problem as well. The accuracy of the frequency counter also became questionable. So too for a while did the scope accuracy, but after running a series of tests, it was confirmed that the scope was ok, but that it was the counter that had become inaccurate, by about 6%.

I had designed and built the counter and generators quite a few years ago and decided that rather than completely overhaul them I would replace them with a new combined design. At the same time the counter readout range would be increased from four digits to eight, taking advantage of one of the newer families of integrated counter and lcd display modules.

Dropping the experimental radio circuit for a while I got out paper, pencil and pcb pads, and came up with the design I now share with you.

It consists of an eight digit frequency counter capable of monitoring frequencies to around 4MHz, an audio sine/triangle wave generator with a range from nearly-dc to in excess of 20kHz, and a squarewave generator with a range from

around 0.5Hz to about 1.4MHz. The complete block diagram is shown in Fig.1. Let's look at the counter first.

the built-in 8-digit lcd display. The manufacturer's quoted clock frequency is typically 3MHz, though in practice could be either side of this (my own sample appears to have a limit of about 1.5MHz).

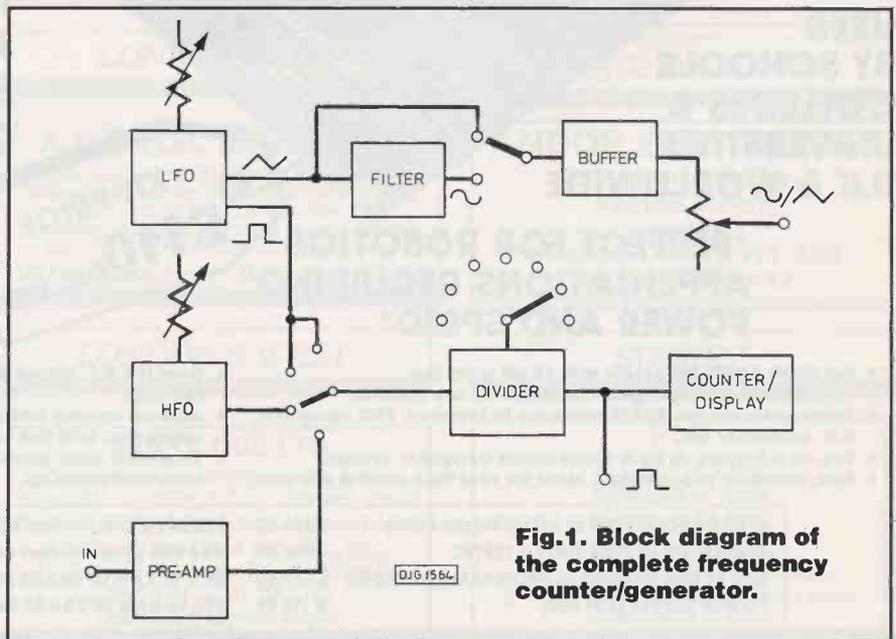


Fig.1. Block diagram of the complete frequency counter/generator.



Fig.2 shows the block diagram of the MM74C947 and Fig.3 shows the internal connections of the counter and display module, both as given in the *National Semiconductor CMOS Logic Databook*.

CONTROL CONDITIONS

For correct operation of the module as a frequency counter, there are five control conditions to be met. The Enable pin must be high to allow the chips to count. The Up/down pin should be high to allow the count to proceed upwards. With the Store pin high the results of the counting will not be displayed on the lcd readout; the count will proceed but will not be seen on the display until Store is taken low, whereupon the counter contents will be transferred to internal latches feeding the display. Normally, Reset is held high; taking it low will reset the counter to zero. The counter clock input is triggered by the trailing (negative) edge of the clock pulse (a fact that doesn't really concern us in this application).

The function of the two pins marked EL was quoted on the data sheet supplied with the counter module as being the backlight connections, but their use was not explained. So, purely out of academic interest, I rang the source company whose name was on the data sheet (not Cirkit) and asked how they should be connected. This appeared to cause a little consternation. Apparently their engineers had never used them! Later they rang me back and said that the module had no backlight built in and that a separate module was required for that function. As I don't really intend to use the counter in the dark I didn't pursue the matter further!

SAMPLING RATES

Much thought was given to the rate at which the counter should sample the input frequency. There is much to be said for having a high sampling update rate since short-term variations in clock frequency can be monitored. On my previous counter I used a sample rate of 10Hz which allowed for rapid updating when changing frequency generator rates. In reality I found this to be a bit too fast since the less significant digits tended to jitter in their readout. For this new circuit I have opted for a sampling period of precisely one second, so automatically ensuring that the readout is in Hertz on the normal range. It also simplifies the control circuit.

By using a 32768Hz crystal as the basic sample rate controller, it is only necessary to divide by 32768 in order to achieve a rate of 1Hz. Since 32768 is 2^{15} , all we need is a 15-stage binary divider after the crystal oscillator. However, a sampling



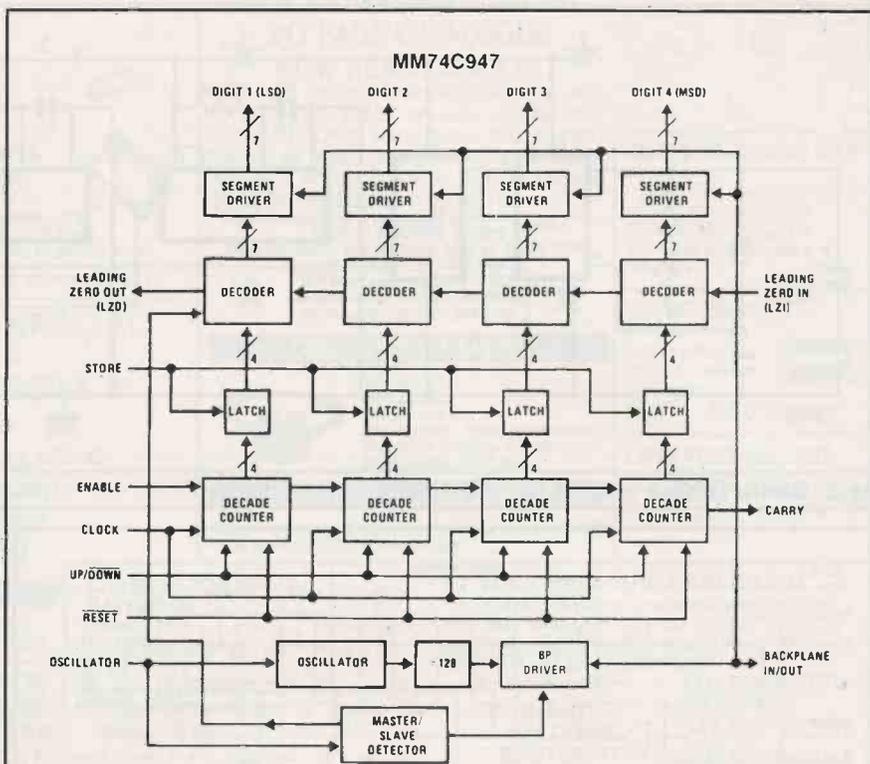


Fig.2. (above) Block diagram for the MM74C947, and Fig.3. (below) How two may be cascaded.

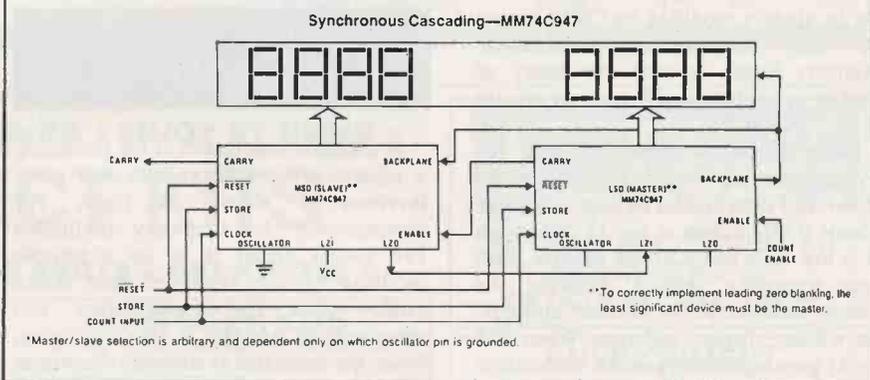

rate of one second must take into account how you use the clocking pulse. A squarewave of 1Hz consists of a pulse having a high period of 0.5secs and a low period of 0.5secs. I felt it was easier to control the counter allowing it to count only during a low logic period of precisely one second. To achieve this, of course, all

Fig.4. Timing waveforms

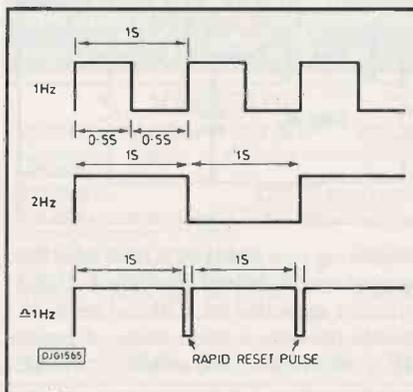

we do is to add a further binary division stage, making it 16 stages in all. Then, by using a very rapid store and reset cycle, the high period of what in theory has become a 0.5Hz sample rate can be terminated early. The result is a sampled read out at almost exactly once per second. Fig.4.

Fig.5 shows how we achieve the control sequence as a practical circuit.

TIMING CIRCUIT

The cmos 4060 chip used for IC3 is a combined oscillator and 14-stage binary divider. Its basic block diagram, as given by Motorola, is shown in Fig.6. There are several ways in which it can be made to oscillate; the method I've chosen consists of the configuration around the crystal, R16, R17, C6 and C7. Although the crystal would prefer to oscillate at the nominal frequency of 32768Hz, this rate

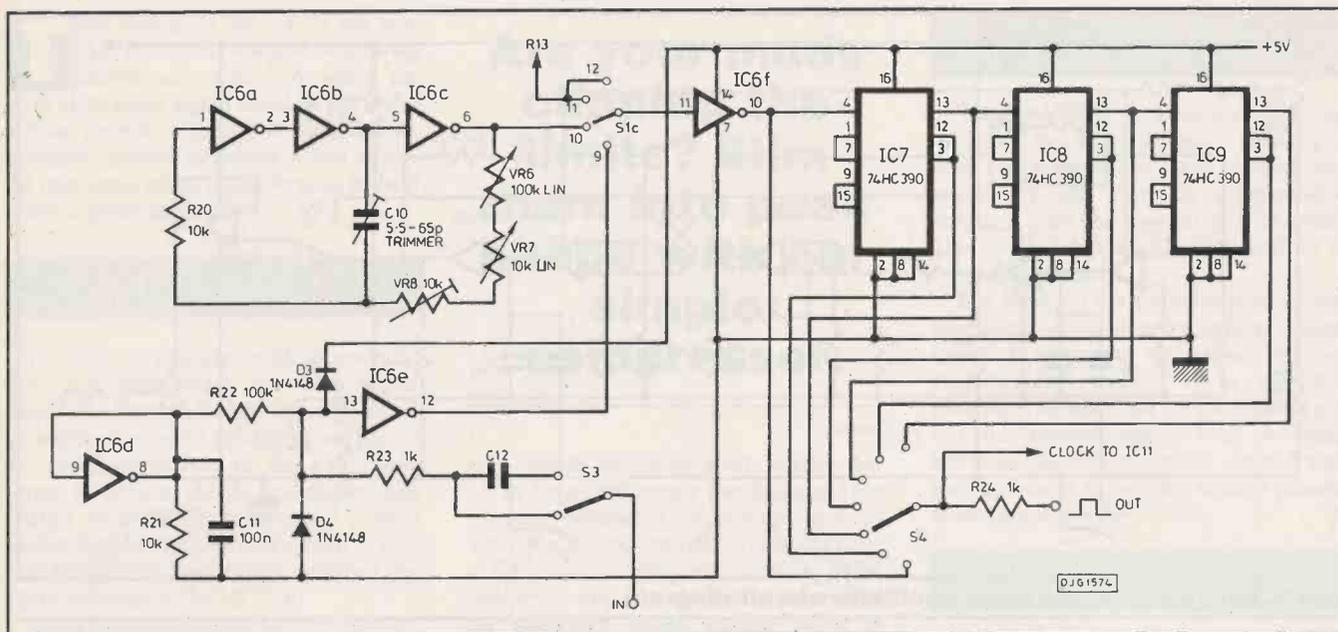


Fig.9. Combined circuit for the squarewave generator, decade dividers and input circuit.

With six decade counters available, S4 can select from seven options of frequency division, including the original frequency. So a 1MHz input can be selected for 1MHz, 100kHz, 10kHz, 1kHz, 100Hz, 10Hz, 1Hz. Since the controllable frequency range of IC6a-c is greater than a factor of ten, there is reasonable overlap between each switched range.

INPUT CIRCUIT

By taking advantage of the linear range of one of the spare inverters of IC6, we can use it as a simple signal input amplifier. IC6d has its input and output connected together, forcing it to a mid-voltage output level. This becomes the reference level for the input to IC6e. Consequently, ac-coupled signals from the input socket are biased around that midway point. IC6e then behaves as an amplifier.

S3 selects whether the input signal is ac-coupled via C12, or dc-coupled by bypassing C12. R23, D3 and D4 restrict the input voltage level seen by IC6e to within its safe region. In other words the signal input to S3 can exceed the 5V rating of IC6. Up to about $\pm 7.5V$ at S3 is acceptable (the rated limits set by D3 and D4). Input signals down to about 0.5V p-p satisfactorily swing the output of IC6e through the full 5V logic range providing the frequency is above about 50Hz. For lower frequency signals the input swing needs to be progressively greater until at 1Hz it needs to be 4V p-p.

The 74HC390s used for IC7-IC9 have a maximum frequency capability of around

40MHz, though the maximum input frequency allowed by IC6 is in the region of 10MHz. Although the counter module will only accept frequencies up to around 3MHz (as qualified above), by selecting a lower division range by S4, frequencies up to the limit set by IC6 can be monitored. (If an additional switch were to be included to bypass IC6f, taking the input directly to IC7, 5V logic frequencies up to the maximum capability of IC7 could be monitored.)

ASSEMBLY

The audio oscillator circuit is a derivative of that formed by the two opamps in Fig.12 in which the capacitor across ICA is charged at a rate set by VR, and in the direction determined by the output state of comparator ICB. A slight variation on this circuit was shown in the *Vodlek* circuit of PE Aug 89.


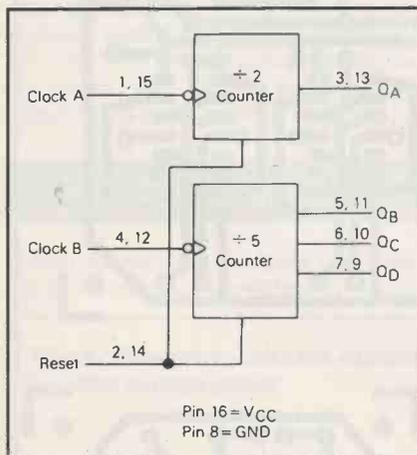
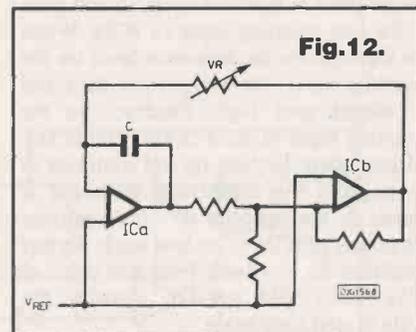


Fig.10. (above) Block diagram for the 74HC 390 and, Fig.11. (below) The timing diagram with QA connected to clock B.

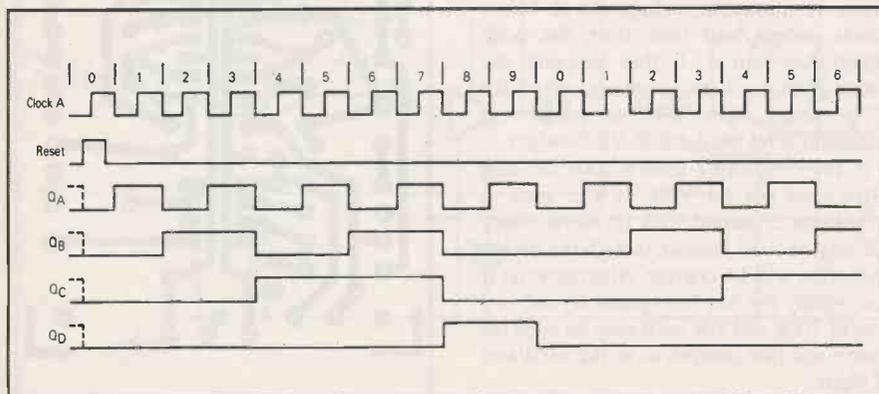

(You may perhaps wonder why I have not used an 8038 or XR2206 chip as the generator. Quite frankly, I'm bored with seeing circuits based on the 8038. It's a useful chip, there's no doubt, but year after year variations on its use have appeared with monotonous regularity. I really felt disinclined to add yet another variation to

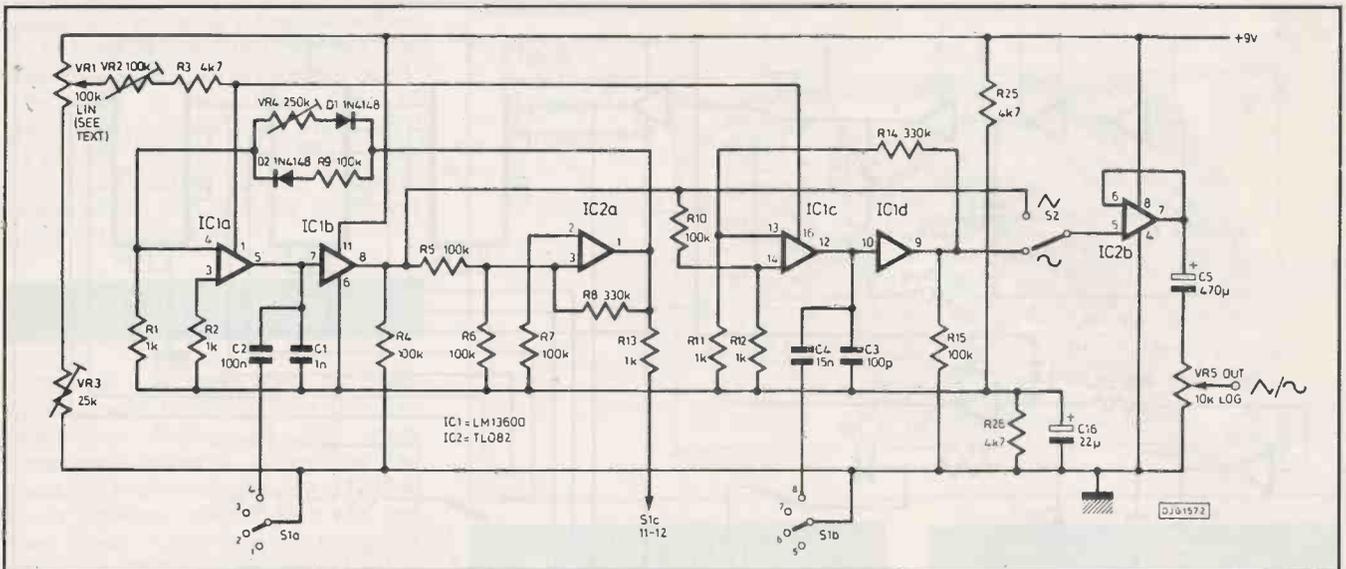


Fig.13. Sine and triangle wave oscillator circuit diagram.

the repertoire. I like the XR2206, and might have used it, but unfortunately it appears to be less widely available than it used to be, making its choice less viable for a project also destined for publication. So far as I can see no manufacturer has come up with an alternative function generator chip. Will someone please enlighten me if I'm wrong!

In Fig.13, IC2a is the equivalent of ICB, but ICA is replaced by the configuration around IC1a and IC1b. These form one half of an LM13600 dual transconductance amplifier (tca).

OSCILLATION FACTORS

With a tca the current present at its principle output, in this case pin 5, is determined by the current flowing into its control node, pin 1, and by the voltage differential at the two signal inputs, pins 3 and 4. In the configuration shown here the current flows into C1, so charging it. The charge level is buffered by IC1b and goes to the non-inverting input of IC2a. When the level passes the reference level on the inverting input, the comparator trips and its output goes high. Feedback to the inverting input of IC1a is via R9 and D2. C1 now starts discharging and continues to do so until the comparator threshold is passed in the opposite direction, causing the output of IC2a to go low again. In this condition the feedback from the input of IC1a is via VR4 and D1, allowing the cycle to start over again.

The oscillation rate is set by four main factors, the value of C1, the current flowing into the control node from the wiper of VR1, the feedback resistances of VR4 and R9, and the hysteresis control resistor R8.

VR1 and VR3 form a potential divider across the power lines. Relative to the voltage level selected by VR1's wiper,


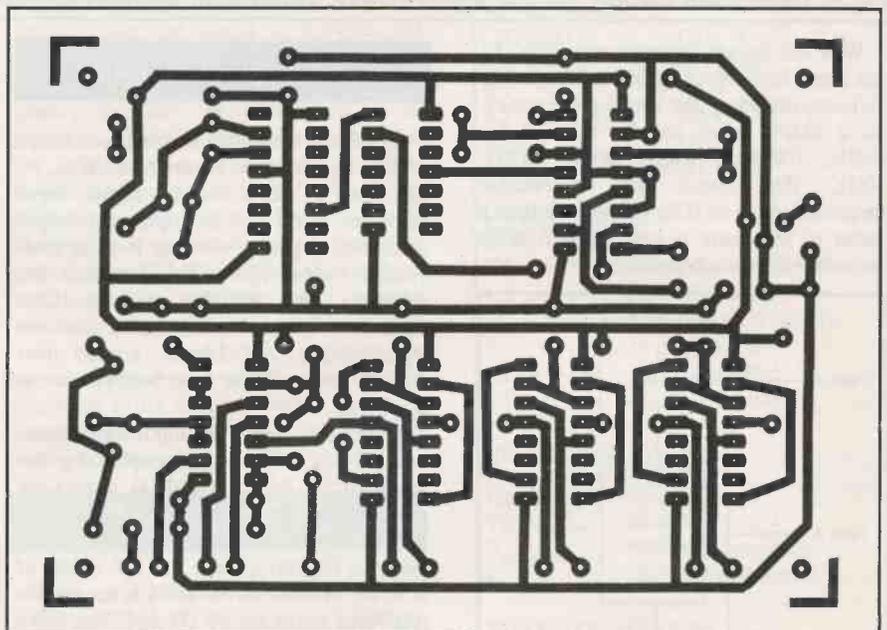


Fig.14. Pcb track foil patterns for (above) The digital logic and (right) The analogue oscillator.

current flows into the control node via VR2 and R3, the former presetting the maximum flow, the latter limiting it in the event of VR2 being set for zero resistance. There is minimum voltage level below which current will flow from the node rather than into it. If that happens, the circuit stops oscillating, consequently VR3 is in series with VR1 to preset the minimum level available at VR1's wiper.

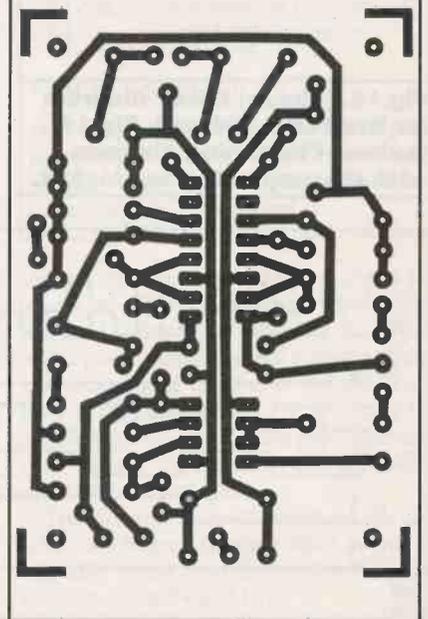In my own unit I used a 100k ten-turn wirewound pot for VR1. If you wish to economise, a normal 100k lin mono rotary pot may be used instead, though the tuning resolution will be coarser. Alternatively, if you modify the box front panel layout, two pots of 100k and 10k each may be used for coarse and fine control, as in the oscillator of Fig.9.





COMPONENTS FOR COMPLETE FREQUENCY COUNTER AND TWIN OSCILLATOR

RESISTORS

R1, R2, R11-R13,	
R23, R24	1k (7 off)
R3, R25, R26	4k7 (3 off)
R4-R7, R9, R10,	
R15, R22	100k (8 off)
R8, R14	330k (2 off)
R16, R17	10M (2 off)
R18-R21	10k (4 off)

All 0.25W 5% carbon film or better.

CAPACITORS

C1	1n polystyrene
C2, C11, C12,	
C14, C15	100n polyester (5 off)
C3	100p polystyrene
C4	15n polyester
C6, C10	5.5p-65p trimmer (2 off)
C7	15p polystyrene
C8, C9	22p polystyrene (2 off)
C13, C16	22uF 16V elect (2 off)

POTENTIOMETERS

VR1	100k 10-turn
wirewound,	or 100k lin mono rotary
	(see text)
VR2	100k skeleton preset
VR3	25k skeleton preset
VR4	250k skeleton preset
VR5	10k log mono rotary
VR6	100k lin mono rotary
VR7	10k lin mono rotary
VR8	10k skeleton preset

SEMICONDUCTORS

D1-D4	1N4148 (4 off)
IC1	LM13600
IC2	TL082
IC3	4060
IC4	4024
IC5	74HC4538
IC6	4584
IC7-IC9	74HC390 (3 off)
IC10	7805

SWITCHES

S1, S2	min spdt (2 off)
--------	------------------

MISCELLANEOUS

32768Hz crystal, box 9 x 5.25 x 2.5 in, pcb supports (8 off), stick on feet (4 off), knobs (6 off), input/output sockets to suit needs (4 off), 8-pin ic socket, 14-pin ic sockets (5 off), 16-pin ic sockets (3 off), printed circuit board set counter-display module type PCIM300 plus bezel type BEZ10 (from Cirkit Distribution Ltd).

WAVEFORM SHAPING

The waveform at the output of IC1b is roughly triangular, and that of IC2a approximately a squarewave. The lack of linearity is caused by the nature of IC1b. Strictly speaking it is not an ic, but a Darlington transistor pair whose emitter voltage at pin 8 will normally be below the base voltage at pin 7. This voltage differential causes IC2a to generate an uneven mark-space ratio pulse train. This is compensated for by slightly varying the feedback and feedforward currents between IC2a and IC1b. Hence D1, D2 and VR4. The diodes control the current flow direction, and VR4 changes the rate for that path compared to the path via R9. VR4's value allows for the feedforward rate to be set either slower or faster than the feedback rate, and is adjusted until the waveform at pin 8 is a symmetrical triangle wave.

The triangular waveform is fed to the shape selector S2, and then to the unity gain buffer IC2b. From there it goes to the audio output socket at an amplitude level controllable by VR5. Additionally, the triangle wave goes to the low pass filter circuit around IC1c and IC1d, and then to S2. The filter's cut off frequency is determined by the value of C3 and the current flowing into the control node at pin 16. Since this node is directly connected to that of IC1a, the two circuits track together. The effect of the filter is to reshape the triangle into a more sinusoidal shape. It is not a perfect sinewave, but is sufficiently close it to for most purposes. If a more precise shape is required the best value for C3 should be found by experimentation, though note that decreasing its value too far may result in diminishing the signal amplitude.

The squarewave output from IC2a is taken to S1c so that it can be fed to the counter module. It can also be used as squarewave source in its own right, at the division rate selected by S4. R13 is included in the squarewave path to limit the maximum input voltage seen by IC6f.

With C1 as the sole capacitor controlling the oscillation rate, the frequency variable by VR1 can be set for a range from almost zero to about 30kHz. On my own unit I've set for a range of 10Hz to 20kHz. Using S1a, by switching in C2 in addition to C1 the range is lowered by about 100 times, roughly 0.1Hz to 200Hz. S1b simultaneously switches in C4 so maintaining the filter tracking for sinewaves. If preferred, the capacitor values may be decreased to increase the frequency ranges.

POWER SUPPLY

The logic circuits of Fig.5 and Fig.9 require a 5V power line. The audio

oscillator can also be run from a 5V supply, though the maximum output amplitude will be restricted to the maximum swings at IC1b and IC1d, which will always be at least a volt or so lower than the power line voltage. The audio circuit power line may alternatively be as high as 15V. Although the psu level will determine the signal voltage swing, it will also affect the frequency range. A lower psu voltage will produce a lower range, and viceversa.

Since I already use a well stabilised 9V supply to drive other workshop test equipment, this is the psu voltage I use to drive the audio circuit. IC10 in Fig.15 then regulates the 9V down to 5V for the logic circuits. The total current drawn varies with the oscillator frequencies selected, but the maximum is around 13mA.

If you don't already have a suitable psu, the circuit shown in the *Easi-Build PSU* project of PE July 89 is recommended.

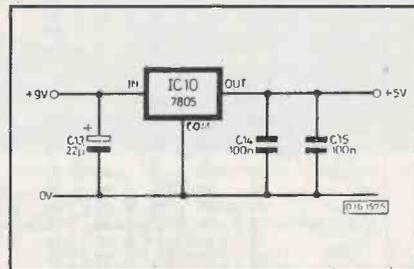


Fig.15. 5V regulator


ASSEMBLY

You will have seen that the circuits split into three principle sections, counter, audio generator and logic generator. If you prefer, you can build any of the three sections without the others.

The audio generator has its own pcb, as shown in Fig.18. The counter and logic generator are on the same pcb, shown in Fig.17.

There's nothing unusual about either board, so just follow normal assembly and checking procedures. Fig.16 shows the master wiring diagram for the pcbs and panel controls.

There is a point to note, though, about the input and output sockets. Since I use a common ground line connecting all test equipment and experimental circuits I prefer to use single leads without additional earth leads to interconnect circuits. For this reason I use 2mm plugs and sockets rather than jack or BNC sockets. The wiring diagram reflects this preference. If you do not use a common ground line, then in addition to the signal lead you must also use a another lead to produce a common ground connection. Therefore, if your connections are via jack sockets or similar, the respective ground tags must be connected in order to complete the circuit.

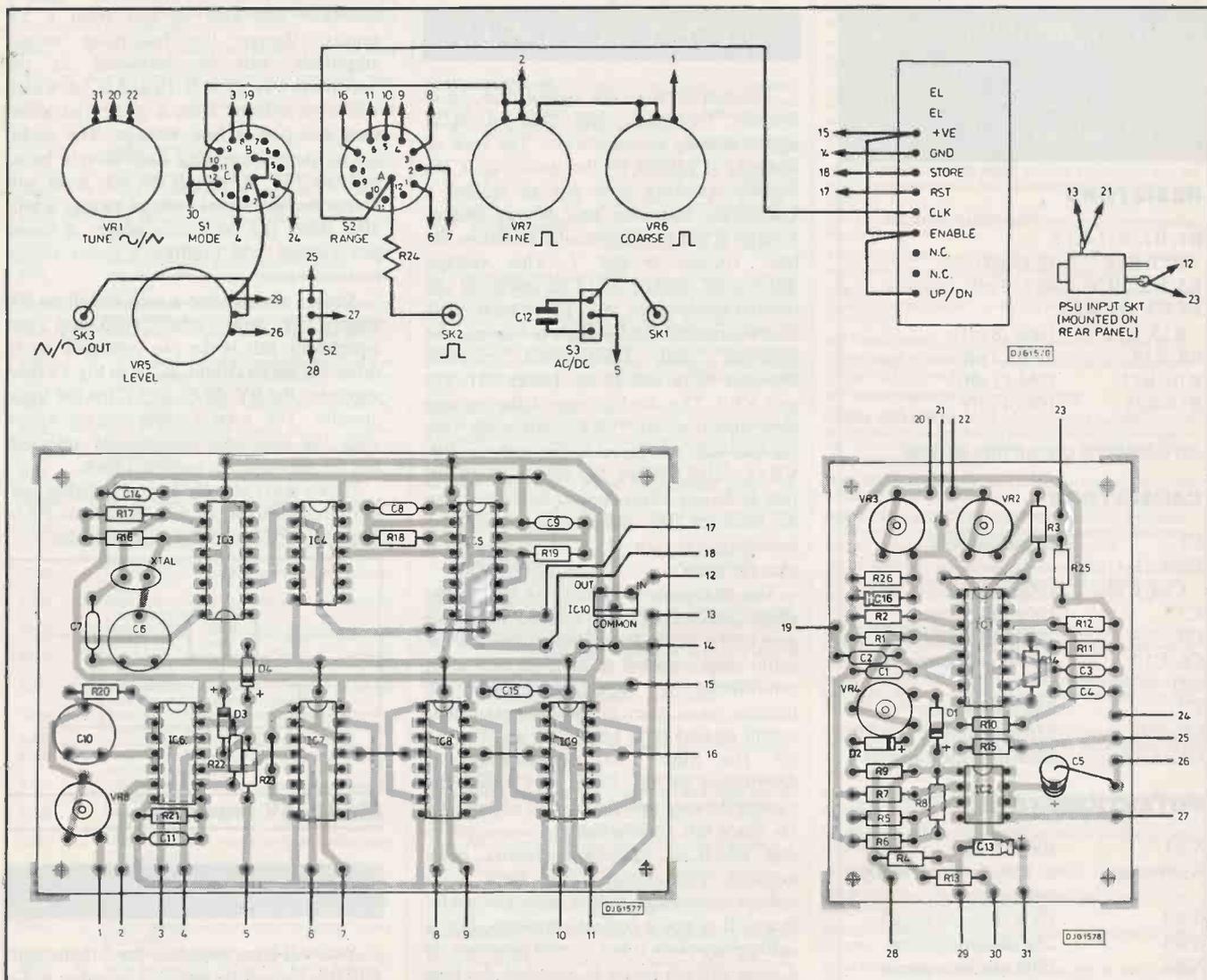

ASSEMBLY DIAGRAMS

- Fig.16. (Top) Wiring details for controls and clock-counter module.**
- Fig.17. (Above) Component layout for the digital circuits pcb.**
- Fig.18. (Right) Component layout for the analogue oscillator.**
- Fig.19. (Below) Front panel legends as used on author's unit. It is a reduced size image which should be enlarged to give 1.1 inches between pot centres.**

SETTING-UP

Setting-up of the preset pots and capacitors has been covered in the circuit descriptions above. Most of them can be adjusted correctly by observing the numerical readout on the lcds. The most critical one in terms of timing accuracy is C6. If you don't have an oscilloscope or known frequency source, leave it at a midway setting. Likewise, the linearity preset VR4 may be left in a midway position if a scope is not available for more precise alignment.

If you are using a scope for checking and alignment, don't expect to see the Store and Reset pulses from IC5 unless the scope is a good one, since the pulses are extremely short and only occur once a second.

It was with relief that I put this piece of test equipment into service, replacing other items that had seen better days. Perhaps I may sometime overhaul the other items, but this unit has removed the frustration I had been experiencing for a few weeks, and also takes up less space. It's now in constant use - may yours be likewise.

PE



POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

OMP POWER AMPLIFIER MODULES

Supplied ready built and tested.

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP100 Mk 11 Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 355 x 115x65mm. PRICE £33.99 + £3.00 P&P.



NEW SERIES II MOS-FET MODULES

OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor, >300, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB. Size 300 x 123 x 60mm. PRICE £39.99 + £3.00 P&P.



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB. Size 300 x 155 x 100mm. PRICE £62.99 + £3.50 P&P.



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. Typical 0.008%, Input Sensitivity 500mV, S.N.R. -139dB. Size 330 x 175 x 100mm. PRICE £79.99 + £4.50 P&P.

NOTE:— MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS, STANDARD — INPUT SENS. 500mV BAND WIDTH 100KHz, PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) — INPUT SENS. 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 + 50p P&P.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE S.A.E. (30p STAMPED) FOR COMPLETE LIST.

McKENZIE:— INSTRUMENTS, P.A., DISCO, ETC.

ALL MCKENZIE UNITS 8 OHMS IMPEDENCE

- 8" 100 WATT C8100GPM GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. RES, FREQ. 80Hz. FREQ. RESP. TO 14KHz. SENS. 99dB. PRICE £28.59 + £2.00 P&P.
- 10" 100 WATT C10100GP GUITAR, VOICE, ORGAN, KEYBOARD, DISCO. EXCELLENT MID. RES, FREQ. 70Hz. FREQ. RESP. TO 6KHz. SENS. 100dB. PRICE £34.70 + £2.50 P&P.
- 10" 200 WATT C10200GP GUITAR, KEYBOARD, DISCO. EXCELLENT HIGH POWER MID. RES, FREQ. 45Hz. FREQ. RESP. TO 7KHz. SENS. 103dB. PRICE £47.48 + £2.50 P&P.
- 12" 100 WATT C12100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. RES, FREQ. 45Hz. FREQ. RESP. TO 7KHz. SENS. 98dB. PRICE £36.66 + £3.50 P&P.
- 12" 100 WATT C12100TC TWIN CONE) HIGH POWER WIDE RESPONSE, P.A., VOICE, DISCO. RES, FREQ. 45Hz. FREQ. RESP. TO 14KHz. SENS. 100dB. PRICE £37.63 + £3.50 P&P.
- 12" 200 WATT C12200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. RES, FREQ. 40Hz. FREQ. RESP. TO 7KHz. SENS. 100dB. PRICE £64.17 + £3.50 P&P.
- 12" 300 WATT C12300GP HIGH POWER BASS LEAD GUITAR, KEYBOARDS, DISCO, ETC. RES, FREQ. 45Hz. FREQ. RESP. TO 5KHz. SENS. 100dB. PRICE £85.79 + £3.50 P&P.
- 15" 100 WATT C15100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO. RES, FREQ. 40Hz. FREQ. RESP. TO 5KHz. SENS. 99dB. PRICE £53.70 + £4.00 P&P.
- 15" 200 WATT C15200BS VERY HIGH POWER BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 99dB. PRICE £73.26 + £4.00 P&P.
- 15" 250 WATT C15250BS VERY HIGH POWER BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 99dB. PRICE £80.53 + £4.50 P&P.
- 15" 400 WATT C15400BS VERY HIGH POWER, LOW FREQUENCY BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 102dB. PRICE £94.12 + £4.50 P&P.
- 18" 400 WATT C18404BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. RES, FREQ. 27Hz. FREQ. RESP. TO 3KHz. SENS. 99dB. PRICE £167.85 + £5.00 P&P.

EARBENDERS:— HI-FI, STUDIO, IN-CAR, ETC.

- ALL EARBENDER UNITS 8 OHMS EXCEPT EB8-50 AND EB10-50 DUAL 4 AND 8 OHM. BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED FOAM SURROUND**
- 8" 50 WATT EB8-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES, FREQ. 40Hz. FREQ. RESP. TO 7KHz. SENS. 97dB. PRICE £8.90 + £2.00 P&P.
- 10" 50 WATT EB10-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES, FREQ. 40Hz. FREQ. RESP. TO 5KHz. SENS. 99dB. PRICE £12.00 + £2.50 P&P.
- 10" 100 WATT EB10-100 BASS, HI-FI, STUDIO. RES, FREQ. 35Hz. FREQ. RESP. TO 3KHz. SENS. 96dB. PRICE £27.50 + £3.50 P&P.
- 12" 60 WATT EB12-60 BASS, HI-FI, STUDIO. RES, FREQ. 28Hz. FREQ. RESP. TO 3KHz. SENS. 92dB. PRICE £21.00 + £3.00 P&P.
- 12" 100 WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES, FREQ. 26Hz. FREQ. RESP. TO 3KHz. SENS. 93dB. PRICE £32.00 + £3.50 P&P.
- FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
- 5 1/2" 60 WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 63Hz. FREQ. RESP. TO 20KHz. SENS. 92dB. PRICE £9.99 + £1.50 P&P.
- 6 1/2" 60 WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 38Hz. FREQ. RESP. TO 20KHz. SENS. 94dB. PRICE £10.99 + £1.50 P&P.
- 8" 60 WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 40Hz. FREQ. RESP. TO 16KHz. SENS. 89dB. PRICE £12.99 + £1.50 P&P.
- 10" 60 WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 35Hz. FREQ. RESP. TO 12KHz. SENS. 86dB. PRICE £16.49 + £2.00 P&P.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS



3 watt FM Transmitter

3W FM TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.49 + £1.00 P&P

FM MICRO TRANSMITTER (BUG) 100-108MHz VARICAP TUNED COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATT, PRICE £8.62 + £1.00 P&P



POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS WELCOME FROM SCHOOLS, COLLEGES, GOVT. BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER. VISA ACCESS ACCEPTED BY POST, PHONE OR FAX.



* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E., 30p STAMPED FOR CURRENT LIST.

OMP VARISPEED TURNTABLE CHASSIS.



★ MANUAL ARM ★ STEEL CHASSIS ★ ELECTRONIC SPEED CONTROL 33 & 45 ★ VARI PITCH CONTROL ★ HIGH TORQUE SERVO DRIVEN DC MOTOR ★ TRANSPARENT SCREWS ★ 12" DIE CAST PLATTER ★ NEON STROBE ★ CALIBRATED BAL WEIGHT ★ REMOVABLE HEAD SHELL ★ 1/2" CARTRIDGE FIXINGS ★ CUE LEVER ★ POWER 220/240V 50/60Hz ★ 390x305mm ★ SUPPLIED WITH MOUNTING CUT-OUT TEMPLATE
PRICE £59.99 + £3.50 P&P.

OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500
PRICE £16.99 + 50p P&P

GOLDRING G850
PRICE £6.99 + 50p P&P

OMP MOS-FET POWER AMPLIFIERS, HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



NEW MXF SERIES OF POWER AMPLIFIERS

THREE MODELS:— **MXF200 (100w + 100w)**
MXF400 (200w + 200w) **MXF600 (300w + 300w)**

All power ratings R.M.S. into 4 ohms.

FEATURES: ★ Independent power supplies with two Toroidal Transformers ★ Twin L.E.D. Vu meters ★ Rotary interlocked level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 Fan Cooled with D.C. Loudspeaker and Thermal Protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:— MXF 200 W19" x H3 1/2" (2U) x D11"
MXF 400 W19" x H5 1/4" (3U) x D12"
MXF 600 W19" x H5 1/4" (3U) x D13"

MXF200 £171.35

MXF400 £228.85

MXF600 £322.00

SECURICOR DELIVERY £12.00 EACH



OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE



MADE ESPECIALLY TO SUIT TODAY'S NEED FOR COMPACTNESS WITH HIGH OUTPUT SOUND LEVELS. FINISHED IN HARDWEARING BLACK NYLON WITH PROTECTIVE CORNERS GRILLE AND CARRYING HANDLE. INCORPORATES 12" DRIVER PLUS HIGH FREQ. HORN FOR FULL FREQ. RANGE. 45Hz-20KHz. BOTH MODELS 8 OHM, SIZE H18" x W15" x D12".

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100 (100W 100dB) PRICE £159.99 PER PAIR

OMP 12-200 (200W 102dB) PRICE £209.99 PER PAIR

SECURICOR DEL.— £12.00 PER PAIR

OMP SLIDE DIMMER 1K WATT & 2.5K WATT

CONTROLS LOADS UP TO 1KW & 2.5KW. SUITABLE FOR RESISTIVE AND INDUCTIVE LOADS. BLACK ANODISED CASE. READILY FLUSH MOUNTED THROUGH PANEL/CABINET CUT-OUTS. ADVANCED FEATURES INCLUDE:—

- ★ FULL 65mm SLIDE TRAVEL
- ★ NEON MONITOR INDICATOR
- ★ FLASH OVERRIDE BUTTON
- ★ HIGH & LOW LEVEL PRESETS
- ★ FULLY SUPPRESSED TO BS 800


SIZES:— 1KW H128xW40xD55mm
2.5KW H128xW76xD79mm

PRICES:— 1K WATT £15.99
2.5K WATT £24.99 + 60p P&P

PIEZO ELECTRIC TWEETERS—MOTOROLA

PIEZO ELECTRIC TWEETERS — MOTOROLA

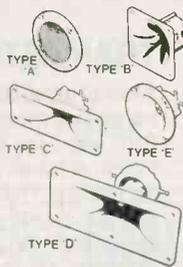Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.90 each + 50p P&P.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.00 each + 50p P&P.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £6.99 each + 50p P&P.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £9.99 each + 50p P&P.

TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each + 50p P&P.

LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £3.99 + 50p P&P.

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features 5 inputs with individual faders providing a useful combination of the following:—
3 Turntables (Mag), 3 Mics, 4 Line including CD plus Mic with talk over switch Headphone Monitor, Pan Pot L & R, Master Output controls. Output 775mV. Size 360x280x90mm. Supply 220-240V.
Price £134.99 — £4.00 P&P



B. K. ELECTRONICS Dept PE
UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR
TEL: 0702-527572 FAX: 0702-420243

HIGH GRADE COMPONENT PARCELS

**EVERYTHING
MUST
GO!**

UNIVERSAL EVERYTHING PARCEL

This one contains some of just about any component you care to name! There are passives (resistors, capacitors, tants, presets), opto devices (couplers, LEDs of all shapes and sizes, infra-red components, 7-segment displays), semiconductors (transistors, diodes, ICs, rectifiers), and all kinds of other odds and ends (relays, VDRs, neons, battery connectors, mixed components packs). A stunning range of components – enough to get a workshop or lab. started – at a ridiculously low price.

The components are of excellent quality, in packs originally intended to sell at £1 each. To make sure you get a good variety, the 20-pack parcel will have no more than two of any one pack, the 100-pack parcel will have at most five of any one pack. Packs supplied as they come – our choice.


PARCEL 1A: 20 PACKS for £10 + VAT
PARCEL 1B: 100 PACKS for £39! + VAT



INTEGRATED CIRCUITS

This parcel contains nothing but ICs. The mixture offers TTL and CMOS logic, interface ICs, linear, data converters, op-amps, special functions, and so on. Some of the ICs are pre-packed with data sheets, some (TTL, CMOS, op-amps) we expect you to identify for yourself, others will be covered by the free *data pack* provided, and the rest you'll have to identify under your own steam. If you know your ICs you'll be in for a few nice surprises.

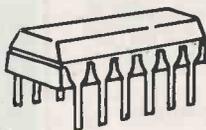
PARCEL 3A: 100 ICs for £12! + VAT
**PARCEL 3B:
500 ICs for £49!
+ VAT**



ELECTROLYTICS

A first class selection of good, modern electrolytics. The mixture ranges from small coupling caps up to huge power supply electrolytics – you'll be hard pressed to find any value between 1 μ F and 2200 μ F that isn't represented. A wide range of very useful components. Go for it!

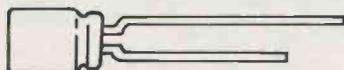**PARCEL 5A:
1000 ELECTROLYTICS for £8 + VAT**
**PARCEL 5B:
2500 ELECTROLYTICS for £16 + VAT**



HIGHGRADE COMPONENTS LTD

Unit 108, 8 Woburn Road, Eastville, Bristol BS5 6TT

Unless otherwise stated, all the clearance parcels we offer contain brand new, top grade components. If some of the offers look too good to be true, all I can say is that the optimists will get some stunning bargains, the cynics will never know what they've missed, so everybody will be happy! All offers apply only while current stocks last – watch out for next month's parcels or, better still, be the first to hear about any new offers by putting your name on our mailing list. (Please write in, or phone Pete Leah on 0272 522703 after 6.30 pm).

MASSIVE CLEARANCE SALE

Once again, a general purpose parcel containing a huge variety of components: resistors, capacitors, ICs, transistors, electrolytics, tants, triacs, LEDs, diodes, thermistors, trimmers, VDRs, all sorts. All new, top quality components. This is mostly remainders from our own stock – stuff we forgot to advertise, or have in too small a quantity to sell individually. Guaranteed to be worth at least eight times the price if valued from any standard component catalogue! What more can I say?

PARCEL 2A: 1000+ top grade components for £12! + VAT
(Value £100+)
PARCEL 2B: 5000+ top grade components for £49! + VAT
(Value £500+)



TANTALUM CAPACITORS

A nice range of tants in values up to 47 μ F. Lots of useful caps, and we're not mean with the most expensive ones. A fine selection.

PARCEL 4A: 100 TANTS for £6.80 + VAT
PARCEL 4B: 500 TANTS for £29! + VAT



TRANSISTORS

A mix of general purpose silicon transistors, mostly bipolar NPN and PNP, with a few FETs and unijunctions thrown in (when available) to spice the mixture. The contents vary from month to month – at the moment there are BC212s, BC213s, BC548s, BC238Bs, MTJ210s, and so on. Next month – who knows? All top quality components.


**PARCEL 6A:
200 TRANSISTORS for £7.80! + VAT**



LEDs

All shapes, sizes and colours of LEDs. Round ones in various sizes, rectangular ones, red, green, amber and yellow ones, clear and tinted lenses, all sorts.

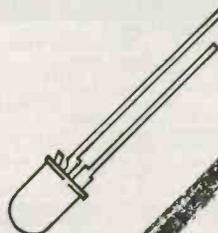PARCEL 7A: 100 LEDs for £5.90 + VAT
PARCEL 7B: 500 LEDs for £24.90 + VAT



CAPACITORS

An exciting selection of capacitors. There are ceramics for decoupling and general use, Polystyrenes for high performance circuits, dipped and moulded polyesters in values from a few nF up to 2.2 μ F (very expensive!), tants and aluminium electrolytics – just about any capacitor you'll ever need. Don't miss this one!

**PARCEL 8A:
1000 CAPACITORS for £6.50 + VAT**

**PARCEL 8B:
2500 CAPACITORS
for £14.90 + VAT**



UK Orders:

Please add £2.50 towards postage and packing and 15% VAT to the total

Europe and Eire:

Please add £6.00 carriage and insurance. No VAT

Outside Europe:

Please add £12.00 carriage and insurance. No VAT



The hf receiver is made of many parts which can basically be thought of as three parts, namely the radio frequency (rf) stage, the detector and the audio frequency (af) stage, Fig. 1. There is little point in spending a lot of time and money designing one of these stages to perfection if the other two stages are going to be of poor quality.

One of the most useful stages is the oscillator driving the mixer, Fig. 2. That is not to say that the other stages are less important, but an important aspect of the oscillator is that it has to be set as close as possible to the selected frequency. A drifting oscillator will produce overlapping sidebands in an analogue transmission system (Fig. 3a) when a single channel is modulated, or Fig. 3b when several channels are modulated onto an rf carrier.

In a digital radio system drifting oscillators cause intersymbol interference, Fig. 4, since the pulses are drifting and this leads to timing problems when the pulse has to be regenerated, and the regenerator (repeater) cannot decide whether the centre of the pulse is A or B.

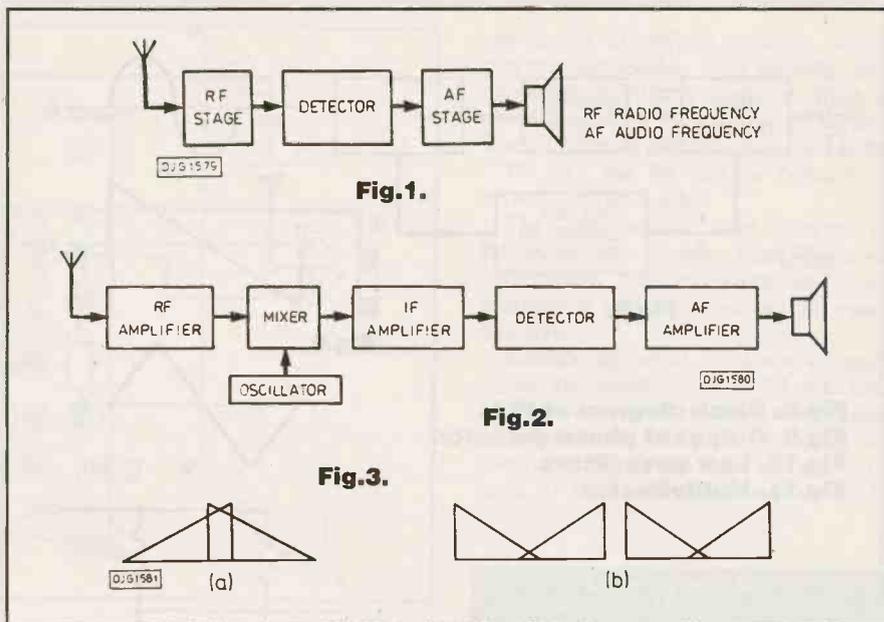


Fig.1. Basic radio receiver.
Fig.2. Expanded radio receiver.
Fig.3. Overlapping sidebands.

HF RADIO

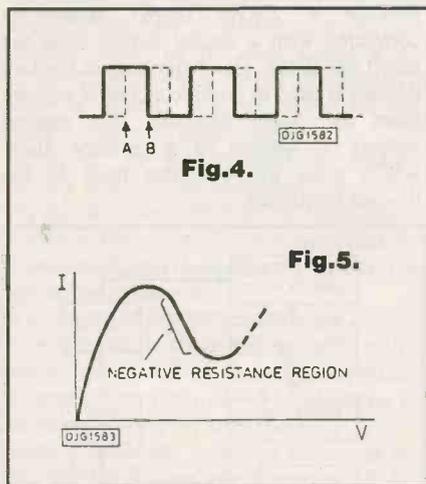


Fig.4. Intersymbol interference
Fig.5. Negative resistance

OSCILLATORS AND LOOPS

One method of keeping the oscillator frequency steady is by means of a phase locked loop, but first let us look at oscillators briefly. The criteria for oscillation is that there should be positive feedback with zero phase shift.

Some devices exhibit negative resistance, that is they absorb dc power and output power at hf. Examples of such devices are tunnel diodes, Gunn diodes and unijunction transistors with current/voltage characteristics as in Fig. 5. Fig. 6 shows how a crystal could be used

PART TWO BY MIKE SANDERS

Mike Sanders continues his radio investigations with oscillators, loops phase detectors and mixers.

in a Miller circuit to produce oscillation, and in a Colpitts oscillator as in Fig. 7.

The GT cut of crystal is almost immune to temperature changes, but the maximum frequency is only a few hundred kilohertz. The AT cut is the most commonly used with a frequency variation of a few parts per million between -50°C and +100°C. (Crystals were discussed in *Time and Frequency*, PE Feb and Mar 89. Ed)

Fig.6. Crystal in Miller circuit.

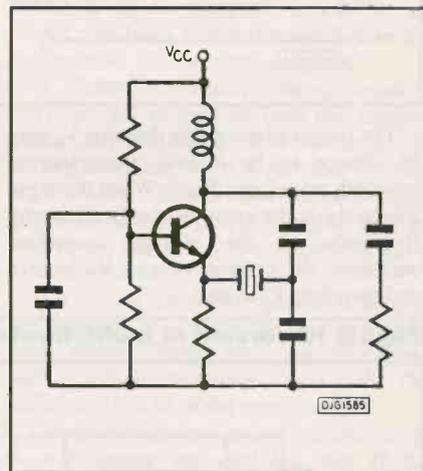
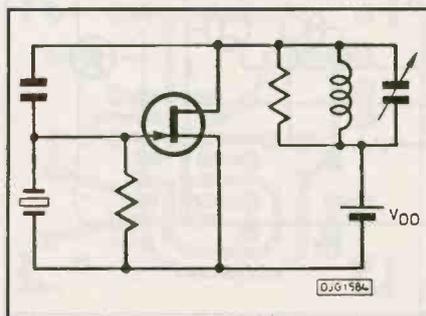


Fig.7. Crystal in Colpitts circuit.

PHASE LOCKED LOOPS

A phase locked loop is a circuit which allows an external reference signal to control the phase and frequency of an oscillator within the loop. If the reference has a varying frequency as in an fm (frequency modulated) wave, the loop frequency will track the input. This is used in fm and fsk (frequency shift keying) and tracking filters.

In Fig. 8, the tracking range depends on the values of the components in the loop. The output voltage (V_e) of the phase detector depends on the phase difference $\phi_d = \phi_s - \phi_o$, where ϕ_s is the phase of the input signal and ϕ_o is the phase of the voltage controlled oscillator.

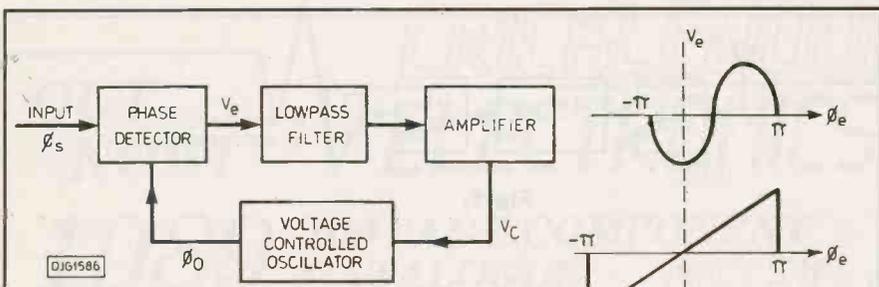


Fig.8.

Fig.8. Block diagram of PLL.
Fig.9. Output of phase detector.
Fig.10. Low pass filters.
Fig.11. Multivibrator.

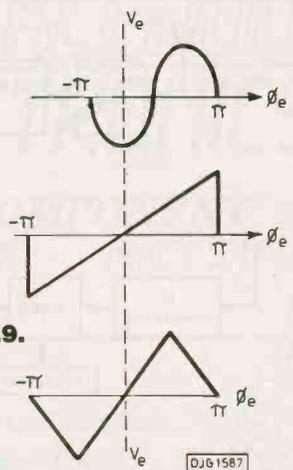


Fig.9.

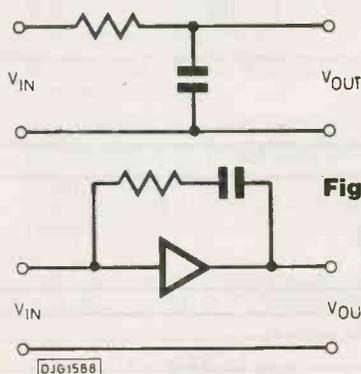


Fig.10.

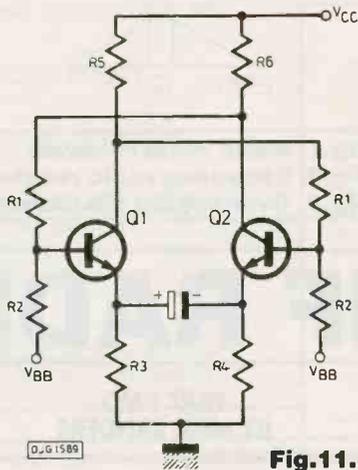



Fig.11.

The output of the phase detector V_e may be chosen to be a sine, triangular or sawtooth waveform. Fig.9. When the input frequency is the same as the free running frequency of the voltage controlled oscillator, the control voltage V_c is zero and therefore V_e is zero.

When the loop is locked, ϕ remains within $\pm \pi$ for the sawtooth waveform and within $\pm \pi/2$ for the sine and triangular waves. This is called the locking range, tracking range, holding range or synchronisation range.

The low pass filter is one of the types

Fig.12. IC version of multivibrator

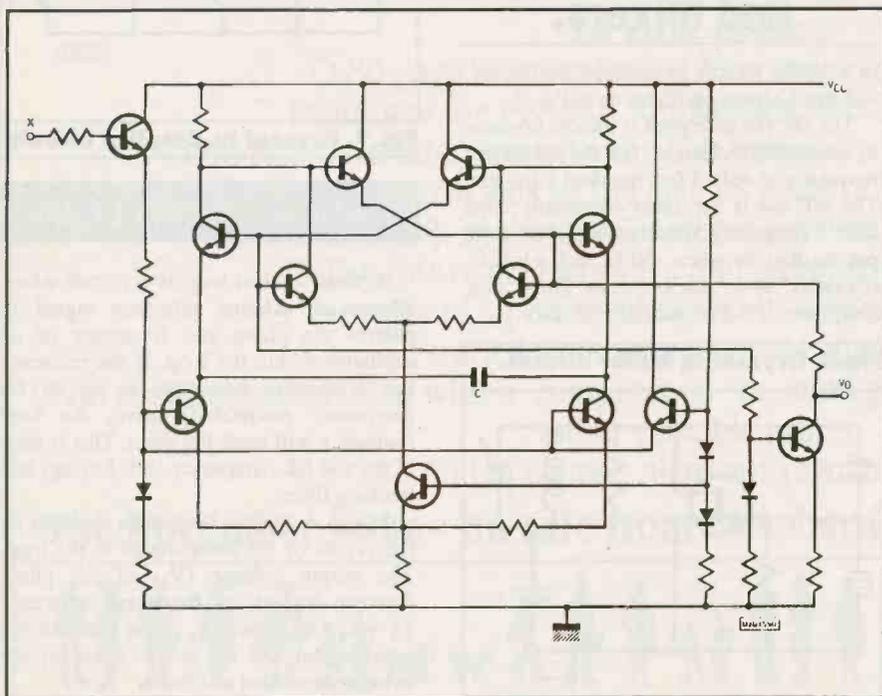

shown in Fig. 10. The oscillator may be sinusoidal or a square wave multivibrator, the latter being preferred in digital circuits. The voltage controlled oscillators for digital circuits have the basic form shown in Fig. 11.

Assume Q1 is on and Q2 off and the capacitor C is charged to voltage V_c with the polarity shown. As the charge on the capacitor decreases, the potential at the emitter of Q2 decreases and Q2 is switched on. This causes a drop in voltage at the collector of Q2 which is connected to the base of Q1, switching it off.

If R_3 and R_4 are large most of the emitter current from Q2 flows into C charging it with the opposite polarity. As the current decays through R_3 , Q1 turns on and the cycles repeat.

An integrated circuit version of the multivibrator is shown in Fig. 12 with the emitter resistors and the resistors coupling the collectors to the bases replaced by transistors. These transistors act as constant current sources, providing constant current charging to capacitor C, making the oscillation period a linear relation to the control voltage (V_c) which is applied to point X.

A block diagram of a phase locked loop which could be used in an fm tuner is shown in Fig. 13. The frequency of the crystal oscillator is divided by four to provide a 25kHz output which is compared with a similar output from the tuned oscillator. The difference in the two outputs is used to provide a control voltage from the phase detector. This control voltage is applied to a varactor diode which pulls the oscillator back to the desired frequency.


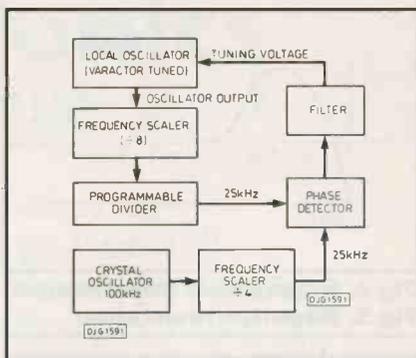


Fig.13. Phase locked loop for fm tuner.

PHASE DETECTOR

The principle of the phase detector is shown in Fig. 14. The two signals to be compared are passed through amplifiers and limiters and then differentiated. The spikes from the differentiator are used to turn the multivibrator on and off and the time that the multivibrator remains on is proportional to the phase difference. The output voltage is proportional to this phase difference and the RC combination acts as a low pass filter.

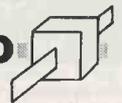

hand if there are several frequencies in the input, sum and difference frequencies are produced in addition to harmonics.


Sum and difference frequencies are generated by the squared terms and called the second order intermodulation products and those generated by the cubed term are called the third order intermodulation products, etc. Square law devices are ideal for mixer applications since they produce only a small number of undesirable frequencies.

Fig. 16 shows a basic diode mixer. The disadvantages are the high noise figure and the non-linearity of the diode characteristic. There is no isolation between the local oscillator and the radio frequency therefore the local oscillator could feed into the receiver's antenna. Also a large local oscillator current could overload the if stage and the conversion loss (rf in to if out) is greater than for other mixer configurations.

Fig. 17 shows a balanced diode mixer and the output voltage across a resistive load. This helps cancel most of the diode's non-linearity, isolate the local oscillator from the rf input and generally improve efficiency. This configuration can be used as a modulator or demodulator as well as a mixer since sum and difference frequencies are produced from two inputs.

Fig. 18 shows a double balanced diode mixer and the difference in configuration from Fig. 17 produces the full amplitude output from which it derives its names. The transistor version of a single ended mixer is shown in Fig. 19 and the balanced version in Fig. 20. Both these figures will be shown next month.

Fig. 18. Double balanced diode mixer.

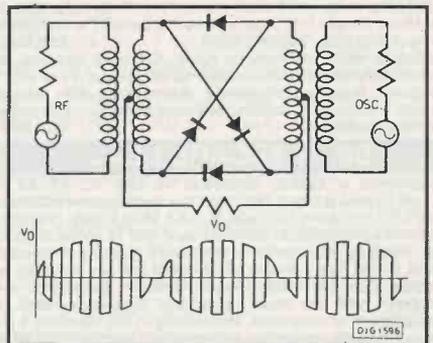

GLOSSARY

- AM amplitude modulation
- CW continuous wave
- DSB/SC double sideband suppressed carrier
- FM frequency modulation
- PAM pulse amplitude modulation
- PCM pulse code modulation
- PPM pulse position modulation
- PWM pulse width modulation
- SSB/SC single sideband suppressed carrier

Next month we shall continue by looking at modulation and amplifiers.

Fig. 14. Block diagram of phase detector.


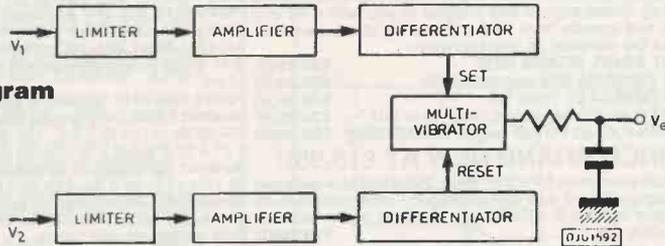


Fig. 15. Phase detector circuit.

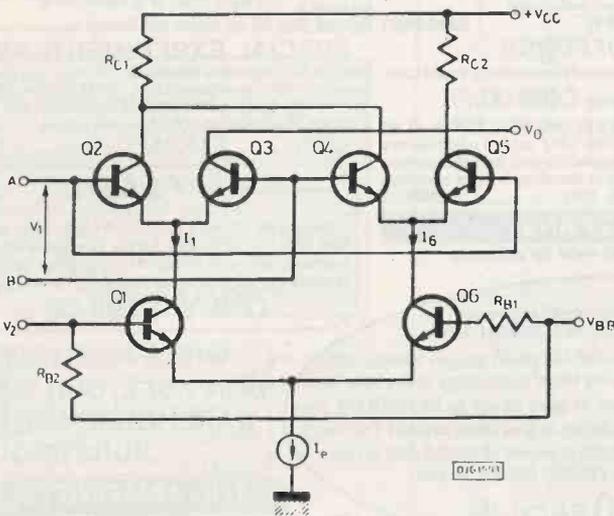

The circuit of one type of phase detector circuit used widely in phase locked loops (pll) as well as in product detectors, mixers and balanced modulators is shown in Fig. 15, Ie is a constant current generator drawing currents I1 and I6 through Q1 and Q6.

Therefore, if a voltage V2 is applied to the base of Q1 the current I1 increases and I6 decreases. The voltage V1 to be compared in phase with V2, is applied to terminals AB and the output V0 is a function of their phase difference.

MIXERS

With reference to Fig. 2, mixers are used to progressively reduce the frequency from rf down to a lower intermediate (if) frequency. This assists the rejection of interference caused by image frequencies.

Armstrong invented a mixer which he called the first detector. Almost any non-linear device will serve as a crude mixer since it will provide products not present in the input. The input output relationship in the time domain can be expressed by the Taylor series:

$$I_0(t) = I_0 + aV_i(t) + b[V_i(t)]^2 + c[V_i(t)]^3 + \dots$$

where I0 is the quiescent current and Vi(t) is the sum of the input signals. If there is only one frequency in the input, the non-linear device will generate harmonics and also shift the dc value. On the other

Fig. 16.

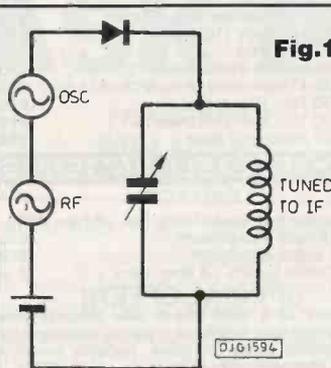


Fig. 16. Basic diode mixer.

Fig. 17. Balanced diode mixer.


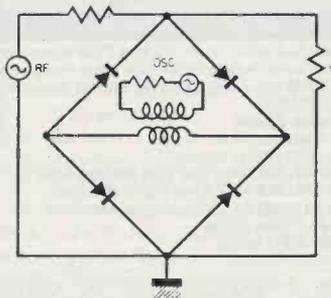


Fig. 17.

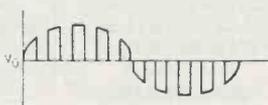

THE ORIGINAL SURPLUS WONDERLAND!

SPECIAL PURCHASE V22 1200 baud modems

We got a tremendous buy on further stocks of this popular **Master Systems 212** microprocessor controlled V22 full duplex 1200 baud modem - we can now bring them to you at **half last advertised price!** Fully BT approved unit, provides standard V22 high speed data comm, which at 120 cps, can save your phone bill and connect time by a staggering 75%! Ultra slim 45 mm high. Fully featured with LED status indicators and remote error diagnostics. Sync or Async use; speech or data switching; built in 240v mains supply and 2 wire connection to BT. Units are in used but good condition. Fully tested prior despatch, with data and a full 90 day guarantee. What more can you ask for - and at this price!!

ONLY £69 (D)

MONITORS

COLOUR MONITORS

Decca 16" 80 series budget range colour monitors. Features include PIL tube, an attractive teak style case and guaranteed 80 column resolution, features which are only normally seen on colour monitors costing 3 times our price! It is absolutely ready to connect to a host of computer or video outputs. Manufacturers fully tested surplus, sold in little or hardly used condition with 90 day full RTB guarantee.

Decca 80 RGB TTL and sync input for BBC and similar type Interface etc.
Decca 80 COMPO 75 ohm composite video input with integral audio amp & speaker. Ideal for use with video recorder or our Telex ST, or any other audio visual use.

Any type only **£99.00 (E)**

HI-DEFINITION COLOUR MONITORS

Brand new Centronic 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 Mhz bandwidth. A super monitor in attractive style moulded case. Full 90 day guarantee. Only **£149 (E)**

20", 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attract-

**WRITE FOR OUR EIGHT
WEEKLY BARGAIN SHEET &
GET ON OUR MAILING LIST -
FREE!**

ive teak style case. Perfect for Schools, Shops, Disco, Clubs. In EXCELLENT little used condition with full 90 day guarantee.
20"....£155 22"....£170 26"....£185 (F)

MONOCHROME MONITORS

Motorola M1000-100 5" black & white compact chassis measuring 11.6H x 12W x 2.2D. Ideal for CCTV or computer applications. Accepts standard composite or individual H & V syncs. Needs 12vdc at only 0.8a. Some units may have minor screen blemishes. Fully tested with 30 day guarantee and full data. **£29.00(C)**

Fully cased as above in attractive moulded desk standing swivel. Dim 12 x 14.5 x 26cm. **£39.00(C)**

JVC 751 ultra compact chassis monitor for 12vdc 0.7a. Dim 11 x 14 x 18cm. Simple DIY data included to convert to composite video input. Full data. **BRAND NEW £65.00(B)**

20" Black & white monitors by Aztek, Cotron & National. All solid state, fully cased monitors ideal for all types of AV or CCTV applications. Standard composite video inputs with integral audio amp and speaker. Sold in good used condition - fully tested with 90 day guarantee. **£85.00(F)**

IBM KEYBOARD DEAL

A replacement or backup keyboard for IBM PC, PC-XT or PC-AT. All in one! It has a switch on the rear to convert between models! LED indicators for Caps, Scroll & Num Locks. Standard 10 function keys plus 56 on the main bank and 19 on the keypad, 85 in all. Made by NCR for the English & US markets. Absolutely standard. Brand new & boxed with manual and key template for user slogans on the function keys. Attractive beige, grey and cream finish, with the usual retractable legs underneath. A generous length of curly cord, terminating in the standard 5 pin DIN plug. A beautiful clean piece of manufacturers surplus. What a deal! **BRAND NEW AND BOXED ONLY..... £59 (B)**

COMPUTER SYSTEMS

TATUNG PC2000. Big brother of the famous Einstein. The TPC2000 Professional 3 piece system comprises: Quality high resolution Green 12" monitor. Sculptured 92 key keyboard and plinth unit containing Z80A CPU and all control circuits. PLUS 2 integral TEAC 5.25 80 track double sided disk drives. Generous other features include dual 8" IBM format disk drive support. Serial and parallel outputs, full expansion port, 64K ram and ready to run software. Supplied complete with CPM, Wordstar and Basic. Brand new and covered by our famous 90 day guarantee and backup. Normal price of this unit is over £1400!
Our Price ...only.....£299 (E)

FLOPPY DISK DRIVES BARGAINS GALORE!

NEW 5 1/4 inch from £29.95!

Massive purchases of standard 5 1/4" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from +5 & +12vdc, are of standard size and accept the standard 34 way connector.

SHUGART SA405. BRAND NEW £29.95(B)
TANDON TM100-2A IBM compatible DS £39.95(B)
TANDON TM101-4 80 Track DS £49.95(B)
CANON, TEC etc. DS half height. State 40 or 80T £75.00(B)
TEAC FD-55-F. 40-80 DS half height. BRAND NEW £99.00(B)

3 1/2 INCH BRAND NEW AT £19.95!!

Never before seen price for a 3 1/2" drive. Standard size believed to be by Canon. Brand new and packaged - mint condition! 40 track SS, run from +5 & +12vdc with standard power connector..... Only..... **£19.95(B)**

CHOOSE YOUR 8 INCH!

Shugart 800/801 SS refurbished & tested **£125.00(E)**
Shugart 851 double sided refurbished & tested **£195.00(E)**
Mitsubishi M2994-63 double sided switchable hard or soft sectors - **BRAND NEW £250.00(E)**

SPECIAL OFFERS!!

Dual 8" drives with 2 megabyte capacity housed in a smart case with built in power supply **Only £499.00 (F)**
Ideal as exterior drive!

End of line purchase scoop! Brand new **NEC D2246 8" 85** megabyte of hard disk storage! Full CPU control and industry standard SMD interface. Ultra hi speed transfer and access time leaves the good old ST506 interface standing. In mint condition and comes complete with manual. Only..... **£399 (E)**

COOLING FANS

Please specify 110 or 240 volts for AC fans.

THIS MONTH'S SPECIAL!

Very high res, fully cased, mains powered 14" green screen monitor with non-glare screen & swivel/tilt base. The very latest technology at the very lowest price! Fully compatible PC type input to plug direct to HERCULES card outputs, enabling superb graphics and resolution at give away prices!! The many features include aux +5 & 12v DC output's to power at least 2 disk drives or other equipment. Supplied **BRAND NEW & Boxed.**

ONLY £69.00 EACH (E)

3 inch	AC. 1 1/2" thick	£ 8.50(B)
3 1/2 inch	AC ETRI siltline. Only 1" thick.	£ 9.95(B)
4 inch	AC 110/240v 1 1/2" thick.	£10.95(B)
4 inch	AC 1 1/2" thick	£ 9.95(B)
10 inch	Round 3 1/2" thick. Rotron 110v	£10.95(B)
62 mm	DC 1" thick. No.812 for 6/12v.814 24v.	£15.95(A)
92 mm	DC 12v. 19 mm thick.	£10.95(A)
4 inch	DC 12v. 12w 1 1/2" thick	£12.50(B)
4 inch	DC 24v 8w. 1" thick.	£14.50(B)

RECHARGEABLE BATTERIES

LEAD ACID

Maintenance free sealed long life, all type A300.
12 volts 12 volts 3 amp/hours **£13.95(A)**
6 volts 6 volts 3 amp/hours **£ 9.95(A)**
6-0-6 volts Centre tapped 1.8 amp hours **£ 5.95(A)**

SPECIAL OFFER!

100 amp/hours at 6 volt! Brand new Chloride Powersafe 3VB11. Leakproof with additional snap-on security lid. Perfect for uninterruptable power supplies, portable power source, caravans etc. Normally costs £80!
£39 (E)

NICKEL CADMIUM

Quality 12v 4ah cell pack. Originally made for the Technicolor video company. Contains 10 GE top quality D nicad cells in a smart robust case with a DC output connector. Ideal for portable equipment. Brandnew. **£19.95(B)**
Ex-equipment NICAD cells by GE. Removed from equipment and in good, used condition: **D size 4ah 4 for £5(B)**
F size 7ah 6 for £8(B)

SPECIAL INTEREST

Rascal-Redac real time colour drafting PCB layout system. Includes furniture and huge monitor. Complete ready to go! **£3950**
DEC VAX11/750 Inc. 2 Meg Ram DZ and full documentation, in brand new condition! **£3900**
Large Calcomp plotter **£ 650**
CHEETAH Telex machine. **£ 550**
1.5kw 115v 60hz power source. **£ 950**
Wayne Kerr RA200 audio real time freq.res. analyser. **£3000**
Tektronics 1411/R PAL TV test signal standard. **£6900**
Tektronics R140 NTSC TV test signal standard. **£ 875**
Versatek V80 Printer plotter **£1500**
DEC LS11/02 CPU board **£ 150**

POWER SUPPLIES

All power supplies operate from 220-240vac. All power supplies are **BRAND NEW** unless stated. We have many other types ranging from 3v to 10kv always in stock.

Byte Drive BD301 Dual output 5vdc @ 1.6 amp & 12vdc @ 1.5 amp. Perfect for disk drives. Has standard Molex sockets. Attractively encased. Dim 15 x 12 x 7 cm. **£19.50(B)**

Plessey PL122 fully enclosed 12vdc 2 amp. Regulated and short proof. Dim 13.5 x 11 x 11cm. **£16.95(B)**

AC-DC Linear PSU with outputs of -5v @ 5.5a, -5v @ 0.6a, -24v @ 5a. Fully regulated and short circuit proof. Dim 28 x 12.5 x 7 cm. **£49.50(C)**

Power One PHC 24vdc 2 a. Linear & regulated **£19.95(B)**

Bosher 13090 switch mode ideal for drives or complete system. +5v @ 6a, +12v @ 2.5a, -12v @ 0.5a and -5v @ 0.5a. Dim 5.6 x 21 x 10.8 cm. **£29.95(B)**

Bosher 13085. Same as above but outputs of +5v @ 6a, +24v @ 1.5a, +12v @ 0.5a, -12v @ 0.5a. **£39.95(B)**

Greendale 19AB0E 60 watt switch mode outputs -5v @ 6a, +12v @ 1a, -12v @ 1a, +15v @ 1a. Dim 11 x 20 x 5.5 cm. Removed from equipment and tested. **£24.95(B)**

Conver AC130-3001. High grade VDE spec. Compact 130 watt switch mode. Outputs -5v @ 15a, -5v @ 1a, -12v @ 6a. Dim 6.5 x 27 x 12.5cm. Reg price £190! Ours new... **£59.95(C)**

Farnell G6/40A Compact 5v 40a switch mode and fully enclosed. **£140.00(C)**

Farnell G24 5S As above but 24v @ 5a. **£95.00(C)**

SPECIAL EXPERIMENTS PSU's

Built to BT's rigorous standards. We have no data so units are supplied for experimentation. EPSU1: +5v 2a, -12v 1a, +24v 1a, +5v fully floating 50ma. EPSU2: +5v 6a, +12v 1a, -12v 0.5a & 5 others. 30-70vdc input. Parts alone value!

EPSU1..... **£16.95(C)** EPSU2..... **£9.95(C)**

FLASH!


Lowest ever priced 8 mhz PC-AT 286 clone with 20 mb hard disk and one 5.25" 360k floppy. Complete with a regular type keyboard and very hi-res 14" mono green screen monitor and Hercules graphic card. Guaranteed for 90 days!

ONLY £799.00 (E)

**WRITE FOR ITEMS YOU
DON'T SEE, OUR SHOP AND
WAREHOUSE ARE FULL TO
BURSTING!**

THE AMAZING TELEBOX!

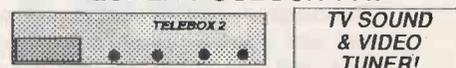Converts your colour monitor into a **QUALITY COLOUR TV!!**



**TV SOUND
& VIDEO
TUNER!**

Brand new high quality, fully cased, 7 channel UHF PAL TV tuner system. Unit simply connects to your TV aerial socket and colour video monitor turning same into a fabulous colour TV. Don't worry if your monitor doesn't have sound, the TELEBOX even has an integral audio amp for driving a speaker plus an auxiliary output for Headphones or Hi Fi system etc. Many other features: LED Status Indicator, Smart moulded case, Mains powered, Built to BS safety specs. Many other uses for TV sound or video etc. Supplied **BRAND NEW** with full 1 year guarantee.

Telebox ST for composite video input monitors..... **£29.95(B)**
Telebox STL as ST but with integral speaker..... **£34.95(B)**
Telebox RGB for analogue RGB monitors..... **£59.95(B)**

NOT suitable for IBM clone type colour monitors.

BRAND NEW PRINTERS

Epson MX-90 F/T One of the most popular printers around! Bi-directional printing with full logic seeking. 9 x 9 dot matrix for enlarged, bold, condensed etc. Standard parallel interface. Brand label removed from front. Handles tractor, fanfold and individual paper. OK with IBM PC and most others. A tremendous buy!
£129.00 (E)

Hazeltine Esprint small desktop, 100 cps with RS232 and standard parallel. Full pin addressable and 6 user selectable fonts. Up to 9.5" paper. Sheet & tractor feed. **£149.00(E)**
Centronics 150 series. Always known for their reliability in continuous use - real workhorses in any environment. Fast 150 cps with 4 fonts and choice of interfaces.

150-SN up to 9.5" paper.....£155.00(E)
150-SW up to 14.5" paper.....£199.00(E)

Specify whether serial or parallel required.

**CALL FOR THE MANY OTHERS IN STOCK
INCLUDING DAISY WHEELS.**

Visit our Shop - Technical help always on hand plus many un-advertised specials. You can buy a colour television for as little as £29! Come and join the gang at 215 Whitehorse Lane!

MAIL ORDER/OFFICES

Open Mon-Fri 9.30-5.30
32 Biggin Way,
Upper Norwood,
London SE19 3XF.

LONDON SHOP

100's of bargains for callers!
Open Mon-Sat 9-5.30
215 Whitehorse Lane,
South Norwood,
London, SE25 6PB.

DISTEL © The Original

Free dial-up database!
1000's of items/info On Line
30063 01-679-1888, 1200/75
01-679-8183, 1200/1200
01-679-8769

ALL ENQUIRIES

01-679-4414
Fax: 01-679-1927
Telex 894502

BANKCARD

VISA

ACCESS



All prices for UK Mainland. UK customers ADD 15% VAT to total order amount. Minimum order £10. PO orders from Government, Universities, Schools & Local Authorities welcome - minimum account order £25. Carriage charges (A)=£1.50, (B)=£3.50, (C)=£6.50, (D)=£8.50, (E)=£12.50 (F)=£15 (G)=Call. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guaranteed for 90 days. All guarantees given on a return to base basis. We reserve the right to change prices & specifications without prior notice. Orders accepted subject to stock. Quotations willingly given for higher quantities than those stated.



This article describes the construction and operation of a basic home alarm control system, based on a single chip microcontroller. The advantage of using a microcontroller is that complex facilities can be implemented, and even changed, without a large number of discrete chips.


FACILITIES

The main facilities of the alarm controller are:

- Variable entry and exit delays.
- Variable alarm timing with auto reset.
- A main alarm and strobe light output.
- Entry and exit delay warning output.
- Two independent switchable zones.
- A panic, fire and anti-tamper zone circuit.
- Automatic system test facility.
- User changeable four digit security code.

MICROCONTROLLER CHIPS

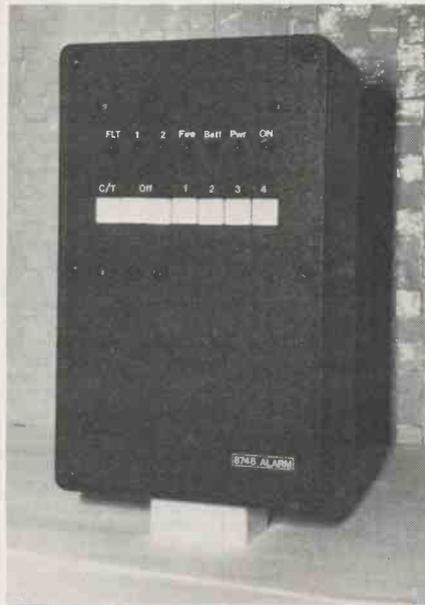Microcontroller chips are a complete microprocessor system, consisting of rom (read only memory), ram (random access



A basic alarm system based on the 8748 Microcontroller

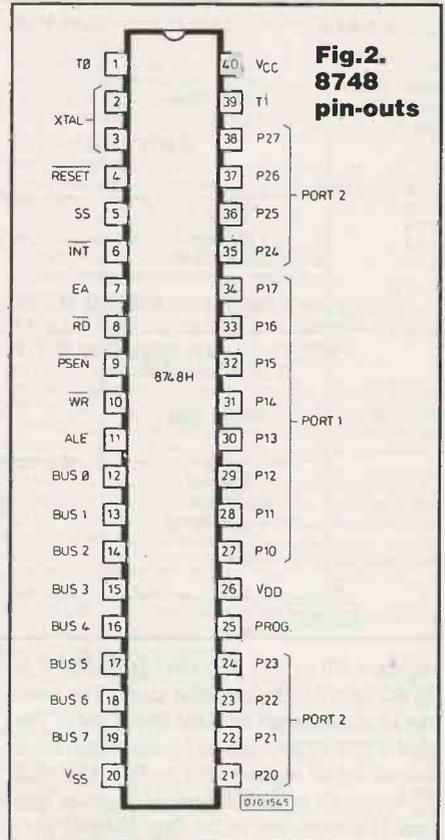


Fig.2. 8748 pin-outs

HOME SECURITY CONTROLLER

BY KEVIN BROWNE

memory), cpu (central processing unit), i/o (input and output interface), timer and clock circuitry all on one chip.

The microcontroller chosen for this project is the 8748H. This is manufactured by Intel and is one of a family of microcontrollers. (Table A).

Table A MCS XX-48 Microcontrollers.				
Device	ROMLESS type	EPROM type	ROM (bytes)	RAM (bytes)
8048AH	8035AHL	8748H	1024	64
8049AH	8039AHL	8749H	2048	128
8050AH	8040AHL	-	4096	256

The functional block diagram of the 8748 is shown in Fig.1 and the pin layout in Fig.2.

ROM PROGRAM MEMORY

The 8748 has 1024 bytes of program memory available on chip. This at first glance may not seem much but since the majority of instruction codes for the 8748 processor are single byte, quite complex control programs can be accommodated with ease, indeed the program for this project is only 774 bytes in length. The rom memory

in the 8748 is of the eeprom type which can be programmed and erased in much the same way as ordinary eeprom chips.

There are three locations in program memory of special importance:

Location 00 First instruction fetched after reset.

03 Interrupt routine start.

07 Timer interrupt routine start.

RAM DATA MEMORY

64 bytes of data memory are available, allocated as shown in Fig.3. The first eight bytes 0 to 7 are used for the general purpose

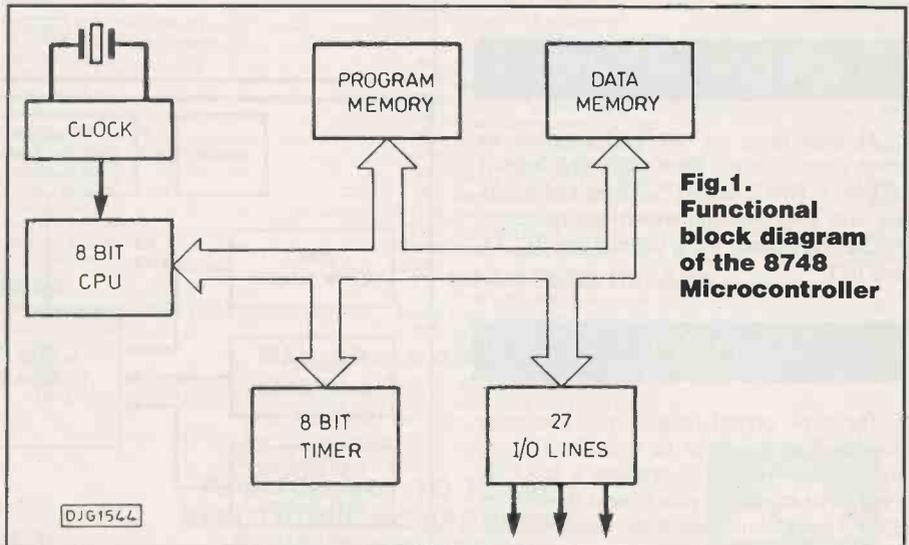


Fig.1. Functional block diagram of the 8748 Microcontroller

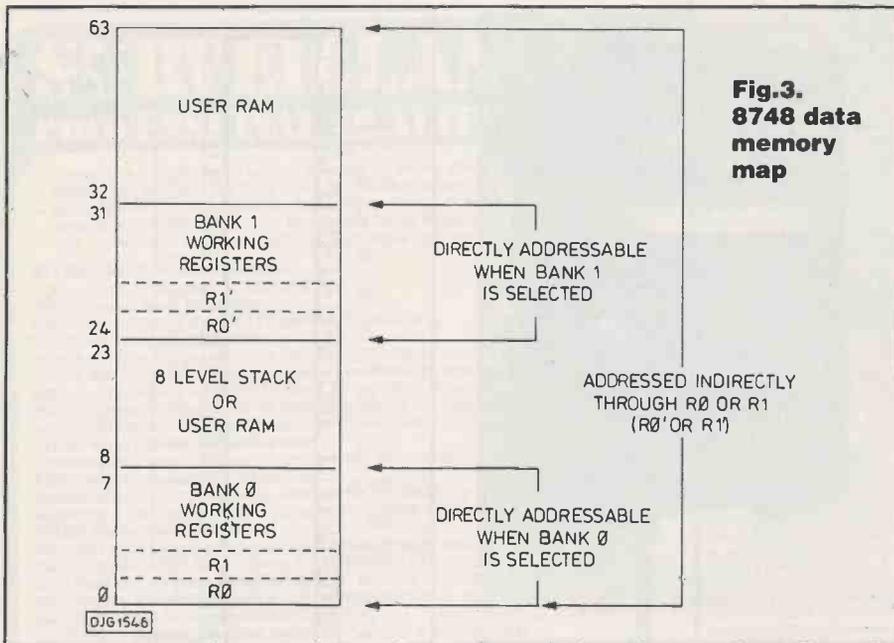


Fig. 3.
8748 data
memory
map

registers R0 to R7. The next 16 bytes, 8 to 23 are used for the machine stack. The stack can be a maximum of eight levels deep. The next eight bytes, 24 to 31 are used for a second set of registers R0' to R7'. The final 32 bytes, 32 to 63 are general purpose user ram. However, any of the first 32 bytes may also be used as general purpose ram, provided that its primary allocation is not used. That is, restricting the stack size to four levels will allow a further eight bytes (16 to 23) to be used as general purpose ram.

REGISTERS

There are two sets of registers, consisting of eight general purpose registers, R0 to R7, and a second set of eight, R0' to R7', which may be selected to replace the main set using a Select Register Bank instruction. (SEL RB0 or SEL RB1). Registers R0 and R1 are also used to indirectly address the ram memory. The 8748 also has an accumulator 'A' and a timer register 'T'.

INPUT AND OUTPUT

27 data lines are grouped together as three ports of eight lines each, and known as Port 1, Port 2 and BUS. Three test inputs are also provided and which can be tested by the conditional jump instructions T0, T1 and INT.

TIMER

The basic crystal frequency is internally divided first by three to provide a clock signal, then by five to produce a machine cycle. The machine cycle is next divided by 32 and used to increment the timer register.

Using a 6.14 MHz crystal the timer register can be made to overflow every 50 milliseconds, and when enabled generate a timer interrupt signal, so forming the basis of the Alarm Controller timing. See Fig. 4.

CIRCUIT OPERATION

Fig. 5 shows the block diagram of the complete alarm system. Figs. 6 and 7 show the control and display circuits.

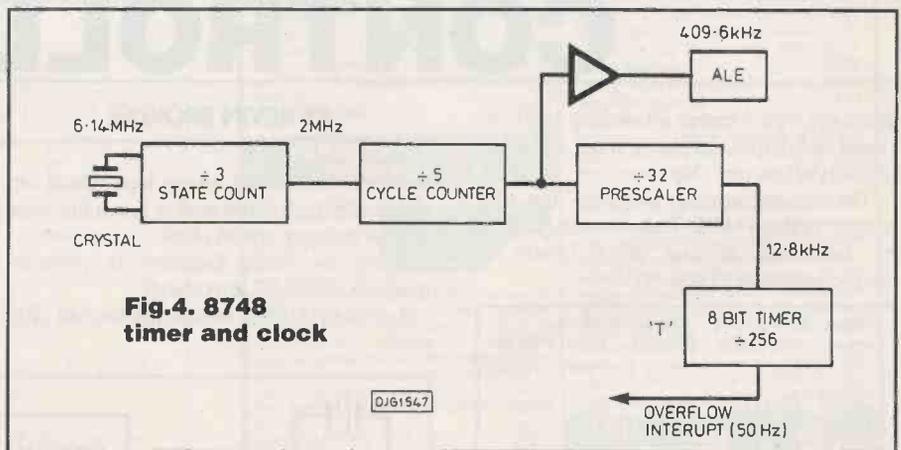


Fig. 4. 8748
timer and clock

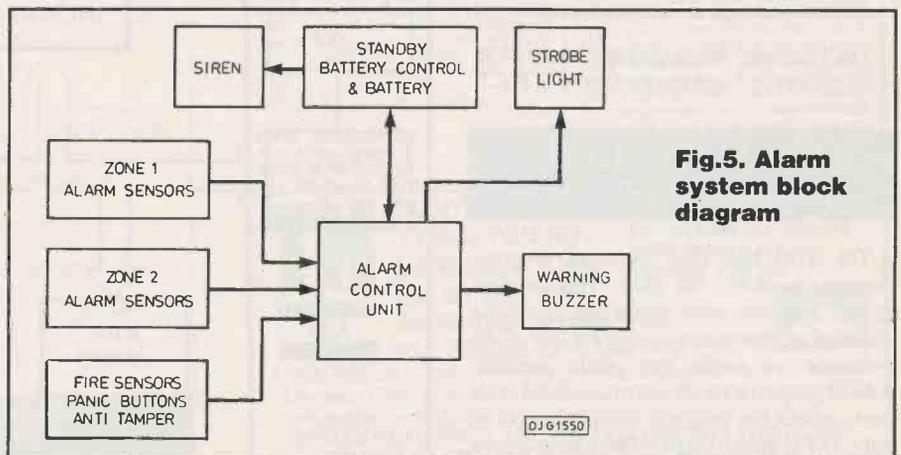


Fig. 5. Alarm
system block
diagram

DATA INPUT

Setting of various alarm timings and the security codes is implemented by two sets of eight dil switches applying a binary code to eight lines of the cpu input. These switches are read by the cpu on power up and during a test sequence. Their status is stored in internal ram for use when required.


All inputs and outputs to the 8748 are normally in the logic 1 high state. To read dil switchblock S1, logic 0 is output on port line P26. Any switches which are operated in this block will pull down the corresponding input line on Port 1 via D10 and D17. The port status is then transferred to internal ram and output P26 returned to logic '1'. Similarly, output P27, via D20 and D27, reads dil switchblock S2.

ALARM INPUTS

Each of the three zones has two alarm inputs, a closed loop circuit which, when broken activates the alarm, and an open loop activated by a short circuit.

Alarm inputs to the cpu are normally low. Consider Zone 1. Both inputs to IC1a are normally held high, one by R11 and one by IC1b, the input of which is held low by the closed loop circuit. A break in this circuit allows the input of IC1b to go high which in turn takes the output of IC1a high. This is

Fig.8. Alarm control power supply

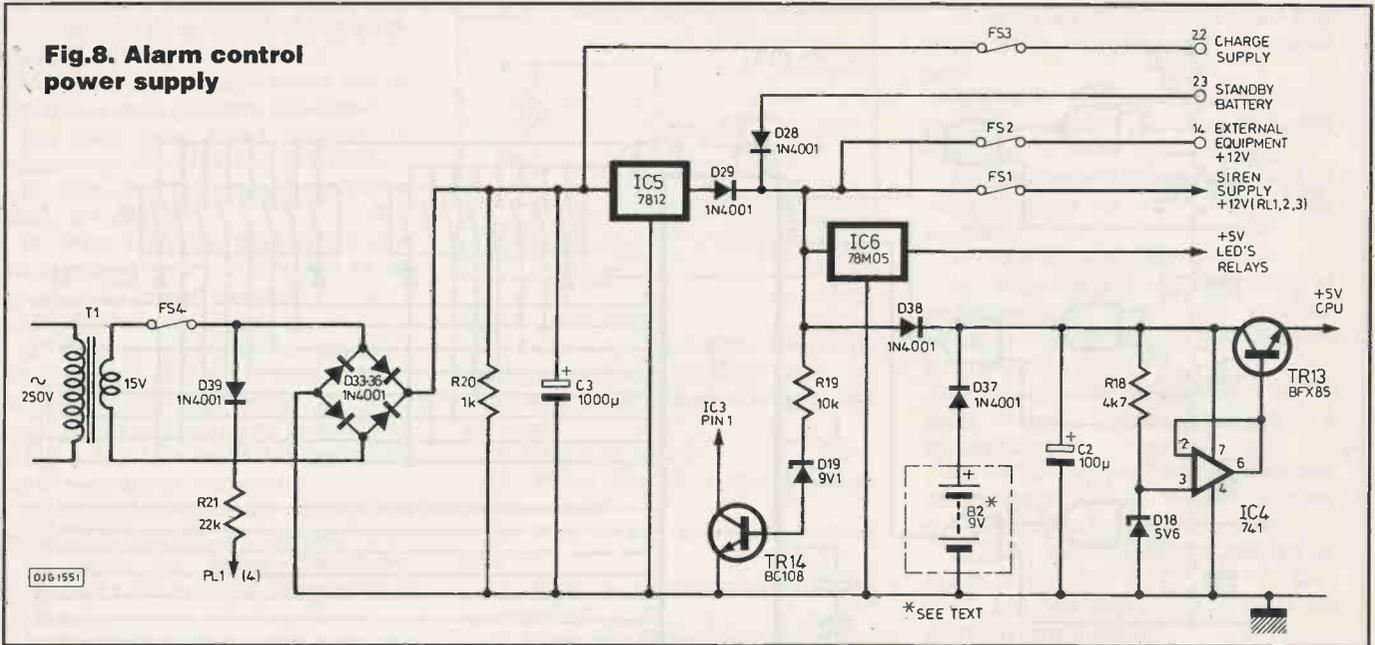

maintain power just to the cpu in the event of a mains failure. Without this battery the alarm controller would re-initialise in the deactivated state when mains power is restored.

The cpu keeps a check on the use of this battery. Input T0 of the cpu is held low by the circuit around TR14, D19 and R19. Failure of the mains power supply results in the loss of this 12V supply. Input T0 thus goes high indicating to the cpu that power is being supplied from battery B2. The time

B2 is on load, and the time since this battery was last changed are calculated by the cpu. The battery led indicates when this battery requires changing. This is after approximately two years unused, or 16 to 18 hours of use, based on alkaline AA size cells.

Input T1 (pin 39) of the cpu should be linked to Port P27 (pin 38) if battery B2 is fitted, this enables the battery check section of the cpu program. Input T1 should be left disconnected if a standby battery controller is fitted (battery B2 is also not required).

STANDBY BATTERY CONTROL

The circuit in Fig.9 is optional though would normally be mounted inside the external bell housing. A four wire cable connects this to the main alarm control unit.

The 20V charge supply, taken from the alarm control unit is regulated by IC3, TR1 and TR2 to form a constant voltage supply

Fig.9. Standby battery control


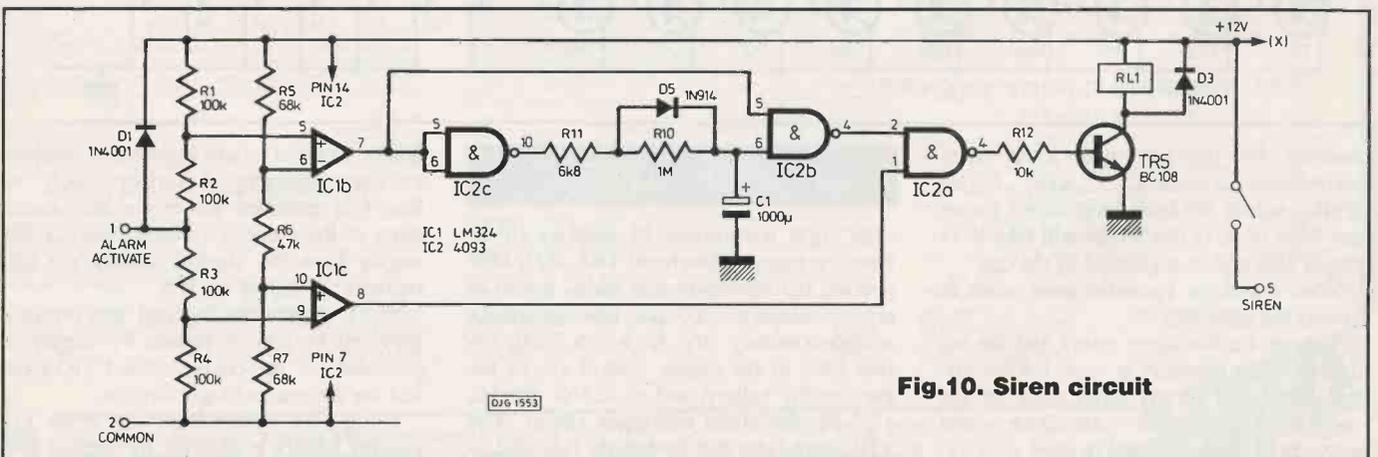


Fig.10. Siren circuit

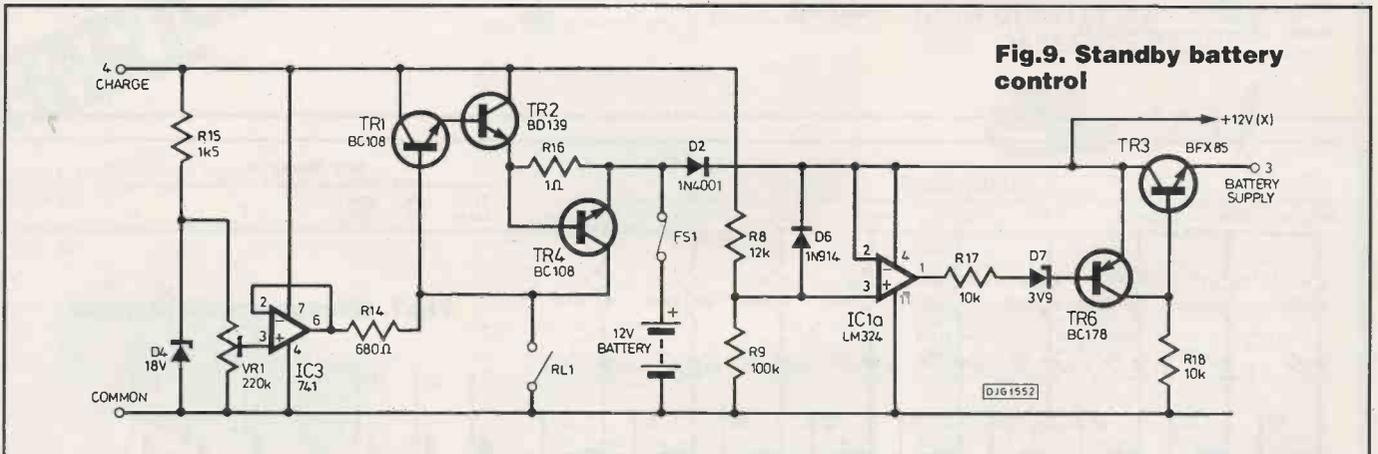

suitable for charging the sealed type of lead acid battery. The precise charge voltage is set by VR1. TR4 and R16 provide a current limiting circuit of approximately 800mA, the charge voltage being gradually dropped across R14 as this limit is reached.

TR3, TR6 and IC1a control the switching of the 12V battery supply back to the main alarm unit. While the charge supply is present IC1a output is high, so turning off TR6. TR3 disconnects the battery from the main alarm unit. When the charge supply is lost (in the event of a mains failure) this is detected by IC1a, the output of which goes low, turning on TR6. TR3 connects the battery supply to the main alarm control unit. R8 and R9, forming a potential divider, set the voltage at which the detector circuit operates (15V). D6 is included to prevent the voltage at the input of IC1a from exceeding the supply voltage to IC1.

SIREN CONTROL

The main siren, in Fig.10, is controlled via the alarm input lead. This is normally at 0V via R17 in the main alarm control unit. IC1b and IC1c are used as voltage comparators. The switching voltages being set by resistor chain R5, R6 and R7 to 7.6V and 4.4V respectively. The output of IC1b is normally logic 0 and that of IC1c at logic 1. IC2c keeps C1 charged. IC2b and IC1c both feed logic 1 to IC2a. TR5 remains off and the relay unoperated.

When an alarm signal is generated by the alarm control unit, the condition on the alarm input lead changes from 0 volts to 12 volts. This change is detected by IC1c, and the alarm relay is operated via TR5 and IC2a. The 12V alarm condition is also fed via D1 to supply power to the relay and alarm siren. The battery charge supply is turned off by the relay contacts RL1 in Fig.9.

If, at any time, the alarm input lead is disconnected from the main alarm unit this condition is detected by IC1b, the output of which goes high. Both inputs of IC2b go high together, one input supplied from IC1b and the other from the charge on C1. The relay is then operated via IC2a, the 12V in this case being supplied from the battery. C1 slowly discharges through R10 and R11 to time the siren operation to approximately five minutes. When C1 is sufficiently discharged, IC2b turns off TR5 via IC2a and stops the siren. Reconnection of the alarm input to the alarm control unit will reset the circuit, C1 being quickly charged via R11 and D5.

SYSTEM SOFTWARE

This is a brief description of the main points of the system software. The flowchart shown in Fig.11 shows only these main points.

The first part of the program consists of system initialisation. This is the routine

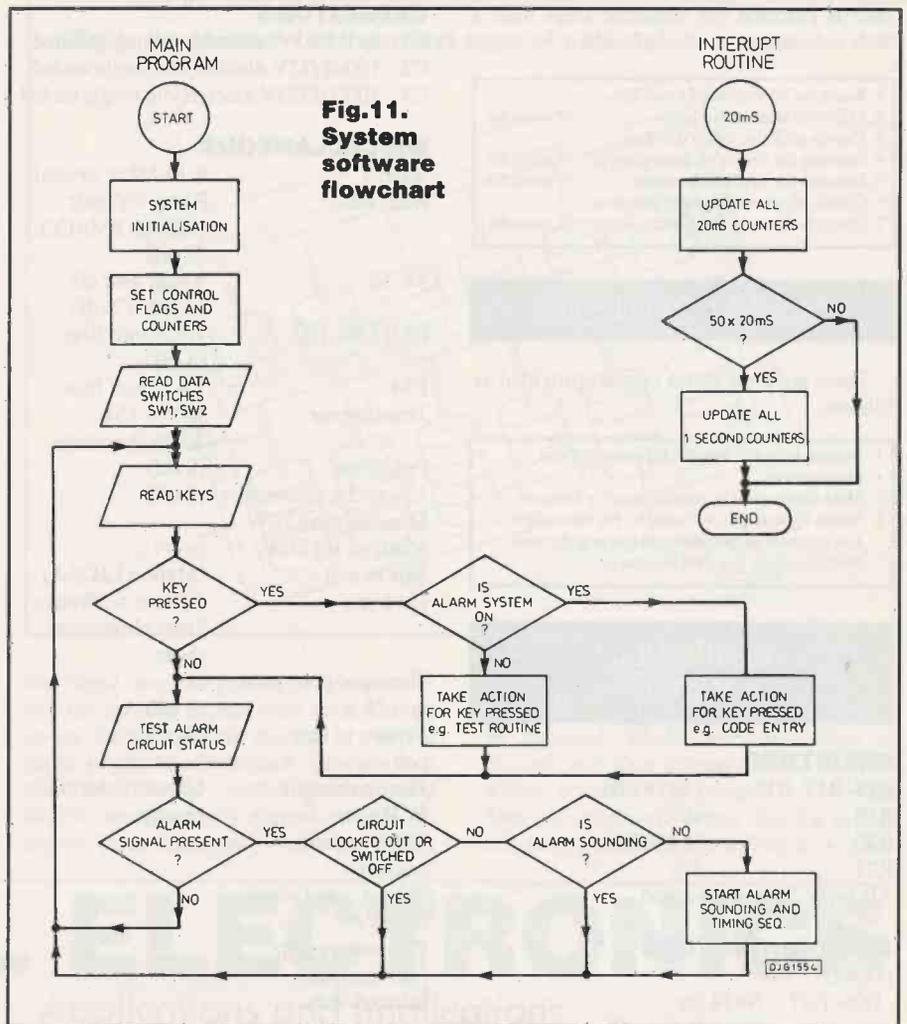


Fig.11. System software flowchart

Key	Action taken when the Alarm system is OFF.	Action taken when the Alarm system is ON.
T/C	Initiates the self test sequence.	Clears the security code input register.
Zone off	Toggles the status of a Zone.	Ignored.
Keys 1-4	Turns system ON after an exit delay period. A second press cancels the exit delay and switches the system ON Immediately.	Correct sequence turns the system OFF. Three incorrect entries of activates the alarm.

Table B

Zone	Action taken when the Alarm system is OFF.	Action taken when the Alarm system is ON.
1	No action.	Initiate entry delay then alarm. (note 1)
2	No action.	Immediate alarm activation (note 1)
Fire	Alarm motivation. (note 2)	Immediate alarm activation.

Notes. 1. Only if zone is in the ON state otherwise no action.
2. If Zone is triggered when the alarm system is in the OFF state the subsequent key actions are as though the alarm system is in the ON state, ie, entry of the security code will deactivate the alarm.

Table C

work required to configure the system to our particular needs, clearing all memory, setting the timer and interrupt mode, storing the basic data and reading the two dil switches. The system is initialised in the disarmed state with all zones active.

After system initialisation, the main program loop is entered. First the seven key switches are tested and action is taken if any key is found operated. The action taken depends upon the status of the alarm system. (Table B.)

Next the three alarm inputs are tested, and again the action taken depends upon the status of the alarm system. (Table C.)

These operations form the main program loop. This loop is interrupted every 20 milliseconds by the internal timer. This is used primarily to debounce the key and alarm inputs; a key has to be operated or an alarm present for a minimum of 60 milliseconds, ie, three interrupt periods before it is considered valid. The 20 millisecond interrupt is then used to decrease a counter (programmed to divide by 50) so that every second the alarm output timers are updated.

TEST SEQUENCE

The self-test sequence performs the following operations. It takes approximately 18 seconds. If at any stage a



HOME ALARM CONTROLLER

fault is detected the sequence stops with a fault indication.

1. Reads the dil switches S1 and S2.
2. Lights all alarm status lamps. (5 seconds)
3. Checks all alarm inputs are clear.
4. Operates the entry/exit buzzer output. (5 seconds)
5. Operates the strobe light output. (5 seconds)
6. Checks all alarm inputs are still clear.
7. Operates the main alarm siren output. (2 seconds)

ALARM OUTPUTS

There are three alarm outputs provided as follows:

1. Buzzer, activated only during entry and exit delay periods.
2. Main alarm, reset by internal timer or keycode.
3. Strobe light output, activated by the main alarm. It is not reset by the timer and can only be reset by the keycode or a Test Sequence.

MAIN PCB COMPONENTS

RESISTORS

R10-R17, R19	10k (9 off)
R18	4k7
R20	1k (0.5W)
R21	22k

All 1/4W 5% unless stated.

SEMICONDUCTORS

D10-D17,	D20-D27	1N914 (or 1N4148) (16 off)
D28-D39	1N4001 (12 off)	
D18	BZY88C5V6 5V6 zener	
D19	BZY88C9V1 9V1 zener	
IC1, IC2	4011 (2 off)	
IC3	8748 microcontroller	
IC4	741 opamp	
IC5	µA7812 12V 1A regulator	
IC6	µA78M05 5V 500mA regulator	
TR10-12	BC178 (3 off)	
TR13	BFX85	
TR14	BC108	

CAPACITORS

C1	1µF 1/63V electrolytic single ended
C2	100µF/25V electrolytic single ended
C3	1000µF/35V electrolytic single ended

MISCELLANEOUS

Xstal 1	6.14 MHz crystal
RL1-RL3	Relay 6V spdt (Maplin FM91Y) (3 off)
S1, S2	8-way spst dil switch (2 off)
FS1, FS2, FS3	1A 20mm fuse (3 off)
FS4	2A 20mm fuse
Transformer	15V + 15V 20VA miniature
Fuse clips	(8 off)
12way 2A connectors	(2 off)
Minicon plug 20W	
Minicon skt 20W	
Box to suit	(Maplin LH23A)
Heatsink	120mm x 50mm x 1mm aluminium sheet
Threaded pcb space	is 0.75 in
Screws to suit	(4 off)
pcb	
Plastic sheet	120mm x 50mm
PCB pins	(2 off)
T05 transistor	
heatsink	
9V AA size battery	holder
PP3 battery clip	
Sub miniature	microswitch

DISPLAY PCB COMPONENTS

RESISTORS

R1-R9	390R (9 off)
-------	--------------

All 1/4W 5%

SEMICONDUCTORS

TR1-TR9	BC178 (9 off)
D1-D5	led 5mm red (5 off)
D6	led 5mm green
D7-D9	led 5mm orange (3 off)

MISCELLANEOUS

S1-S7	spst non locking switch (Maplin FF87U) (7 off)
Switch caps white	(Maplin FF94C) (7 off)
LED clip	5mm (9 off)
PCB	
6BA pcb spacers	
0.25 in	(4 off)
6BA nuts/bolts	(4 off)

STANDBY CONTROL COMPONENTS

RESISTORS

R1, R2, R3, R4, R9	100k (5 off)
R5, R7	68k (2 off)
R6	47k
R8	12k
R10	1M
R11, R12	6k8 (2 off)
R14	680R
R15	1k5
R16	1R (0.5W)
R17, R18	10k (2 off)
VR1	220k hor min preset sealed

All 1/4W 5% unless stated

CAPACITORS

C1	1000/16V electrolytic
----	-----------------------

SEMICONDUCTORS

IC1	LM324 quad opamp
IC2	4093 quad nand Schmitt
IC3	741 opamp
D1, D2, D3	1N4001 (3 off)
D4	BZY88C18V 18V zener
D5, D6	1N914 (or 1N4148)
D7	BZY88C3V9 3V9 zener
TR1, TR4, TR5	BC108 (3 off)
TR2	BD139
TR3	BFX85
TR6	BC178

MISCELLANEOUS

RL1	Relay 12V dpdt (Maplin YX95D)
FS1	Fuse 1A 20mm (2 off)
Fuse clips	
PCB	
Spade terminals	(2 off)
Battery 12V	Sealed lead acid (Maplin YJ69A)
Heatsink	130mm x 60mm x 1mm aluminium
PCB spacers 10mm	(4 off)
6BA 0.75 inch nuts and bolts	(4 off)
Transistor mounting kit	
2 Amp connector 6 way	

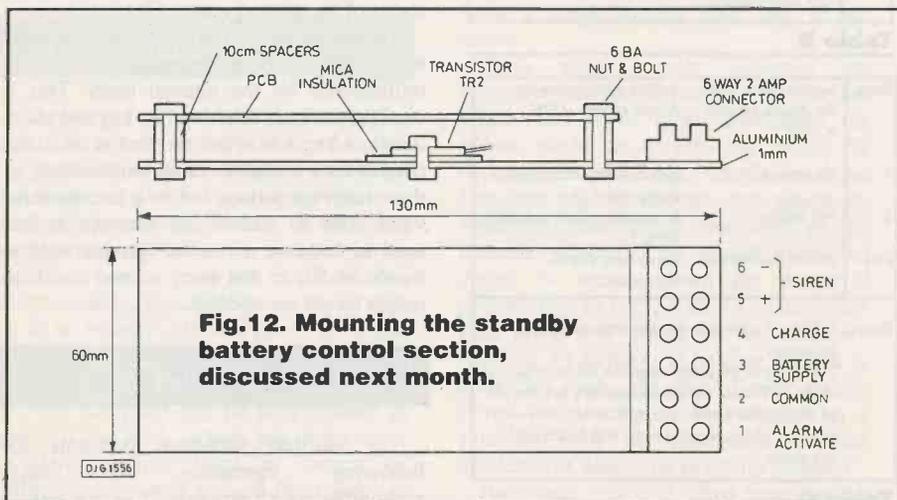


Fig.12. Mounting the standby battery control section, discussed next month.

NEXT MONTH WE DESCRIBE THE CONSTRUCTIONAL DETAILS AND GIVE THE HEX DUMP LISTING.

GREENWELD

ELECTRONIC COMPONENTS

SALE

NEARLY EVERYTHING ON THESE PAGES IS

HALF PRICE OR LESS!!

We must clear last years surplus to make room for more parcels we are expecting soon!! So snap up these unrepeatable bargains now - most goods will not be

available once existing stocks are sold!!

In order to sell at these low, low prices and cover our costs, the minimum order value is £10 & postage is £3.00 regardless of quantity (orders can be made up with non-sale goods if required) state "Sale prices" when you order, whether by post, phone or fax. See back page for more info.

KRAZY KEYBOARD KLEARANCE



Z8852 Keyboard: Superb brand new keyboard 392 x 181 with LCD displaying 1 line of 10 characters and a further line with various symbols. 100 keys, inc separate numeric keypad. Chips on board are 2x77HO5, 80C48. LCD + driver chips are easily removable from board. Looks like it was used with a comms package. Has anyone any more info?

SALE PRICE £15.00 £7.50



Z8857 High quality Alphameric keyboard on aluminium frame 314 x 150mm. Contactless keys good for 20 million operations. Originally sold at over £100 each, they were used in a 'Printcom' portable terminal. Fully ASCII encoded output. Power supply + 5v and -12v @ 35mA supplied with comprehensive data.

SALE PRICE £14.95 £7.50



Z8856 Cherry computer keyboard. Very slim model 340 x 130 by only 14mm deep, including keys. Matrix output. 67 keys in pale/dark brown. No idea what computer they're from - but they're an absolute bargain at only £4.

SALE PRICE £2.00



Z8848 Keyboard Alpha numeric separate numeric keypad. 104 keys. Also chips on board: LS373x2, LS374, LM3086x2. LS138x3, 555, LS08, 6805. Size 442x175mm.

SALE PRICE £12.00 £6.00



Z8863 Keyboard. High quality unit made by Micro Switch 69 pale grey and blue keys. 6 red 5mm LED's, 15 various LS chips and socketed D8048 by Intel. Output via 7 way plug and there's a 4 way edge connector too. Keyboard frame is 317 x 128mm. PCB on which it's mounted is 285 x 170mm.

Excellent value at £12.00
SALE PRICE £6.00



Z4116 24 way (8 x 3) membrane keypad. Large (200 x 90mm) area - these were originally used as a teaching aid. Overlay template and pinout supplied. Now only £2.00

SALE PRICE £1.00



Z8833 Tatung VT4100 Keyboard. As previously advertised on earlier bargain lists (but these do not have a lead attached). New stocks just received of this popular cased 85 key with separate numeric pad keyboard. Supplied with circuit diagram. 450x65x125mm.

SALE PRICE £14.95 £7.50

Z8842 Also available are some with broken keytops (usually 2 or 3) Only £9.95

SALE PRICE £5.00




Z8835 Keytronic keyboard. We've had these before, too, PCB contains MCT210, 7406, INS8035, LS373, 2708. 95 x 405 x 180mm.

SALE PRICE £14.95 £7.50

CURRAH

μSPEECH

& SPEECH 64

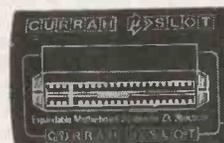

Z4140 New complete set for ZX. Spectrum unboxed. (They were bulk packed) £7.95
SALE PRICE £4.00

Z4142 Speech 64 for the C64 computer. Better than the Spectrum version as no software needed, and can be programmed in plain English! We only have the bare boards but these are new and working. A photocopy instruction book is included.

£6.00
SALE PRICE £3.00

Z4138 μSlot. 'T' connector (1 female, 2 male) for the Spectrum enabling 2 peripherals to be connected to one time. Further μSlots can be added allowing more peripherals to be added: New and boxed.

£2.00
SALE PRICE £1.00

**OUR 1989 PAGE
CATALOGUE +
SUPPLEMENTS GIVING
FULL DETAILS OF ALL
ITEMS IN THIS PULL OUT
COSTS JUST £1 POST
FREE BUT WE HAVEN'T
MANY COPIES LEFT, SO
BE QUICK!**

COMPONENT PACKS – ALL 1/2 PRICE

GREENWELD – THE PACK PEOPLE!

More packs – more in them – more value! All our packs contain brand new, marked full spec. components (unless otherwise stated) at a fraction of the normal price and offer constructors the widest range of parts at the lowest cost! How do we do it? By buying manufacturers end-of-run and surplus components. Because we purchase from many sources, we have an extremely wide range of top quality parts – too costly to sort hence the packs described below. Our larger packs are ideal for schools, groups or clubs.

SEMICONDUCTORS

K517 Transistor Pack – 50 assorted full spec. marked plastic devices PNP NPN RF AF. Type numbers include BC114 117 172 182 183 198 239 251 255 320 BF198 255 394 2N3904 etc., etc.

Retail cost £7+ Special low price £2.75
SALE PRICE £1.37

K547 Zener Diodes – Glass and plastic, 250mW to 5W ranging from 3V to 180V. All ready identifiable. 100 for £4.50
SALE PRICE £2.25

K537 I.C. Pack – a mix of linear and logic chips, from 6 to 40 pin. All are new and marked, but some may not be full spec. 100 £6.75
SALE PRICE £3.37

K538 Diode Pack – untested small signal diodes like IN4148 etc. at a price never before seen!! 1000 £2.50
SALE PRICE £1.25

K560 Semiconductors – Over the years we have purchased many transistors, diodes, ICs etc which for one reason or another have accumulated in one of our stock rooms. Rather than spend weeks sorting and listing them, we have decided to make them into packs. All components are full spec marked devices. Some may be coded. We believe this to be one of the best value packs ever offered, as many high value components are included. Packs are made up by weight; this means contents are very approximate – if there are several bulky power devices, there will be considerably fewer parts than those packs containing all small signal items.

Normally **SALE PRICE**
Pack of approx 100 £5.00 £2.75
Pack of approx 250 £12.00 £6.00
Pack of approx 1000 £40.00 £20.00

RESISTORS

K540 Resistor Pack – mostly 1/8, 1/4 and 1/2W, also some 1 and 2W in carbon, film, oxide etc. All have full length leads. Tolerances from 5 to 20%. Excellent range of values. 500 £2.50 2,500 £11.00
SALE PRICES 500 £1.25 2,500 £5.50

K503 100 Wirewound Resistors – From 1W to 12W, with a good range of values. £2.00
SALE PRICE £1.00

K523 Resistor Pack – 1000 – yes, 1000 1/4 and 1/2 watt 5% hi-stab carbon film resistors with preformed leads for PCB mounting. Enormous range of preferred values from a few ohms to several megohms. Only £2.50
SALE PRICE £1.25

K531 Precision Resistor Pack – High quality, close tolerance R's with an extremely varied selection of values mostly 1/4 and 1/2w tolerances from 0.1% to 2% – ideal for meters, test gear etc. 250 £3.00 1000 £10.00
SALE PRICES 250 £1.50 10000 £5.00

K505 20 Assorted Potentiometers – All types including single, ganged, rotary and slider. £1.70
SALE PRICE £0.85

K572 Networks 7,8,9 pin SIL; 14 & 16 pin DIL. Lots of different values. Pack of 100 £4.50
SALE PRICE £2.25

K554 Thermistors – Mostly disc, rod and some valuable bead types. Identification/data sheet included. Big variety up to 40mm dia! Catalogue value over £50.00 100 for £8.00
SALE PRICE £4.00

K525 Preset Pack – Big, big variety of types and sizes – submin, min and std, MP slider, multiturn and cermet are all included. Wide range of values from 20R to 5M. 100 assorted £6.75 250 £12.95
SALE PRICES 100 assorted £3.37 250 £6.50

CAPACITORS

K549 Variable Capacitors – Mostly small trimmers – airspace, mica and polyprop dielectrics, but also included are a few full size tuning caps. 25 for £5.75
SALE PRICE £2.87

K544 Mullard Polyester Caps – Cosmetic imperfections, electrically OK. Wide range of values from 0.01 to 0.47µF in 100, 250 and 400V working. 200 for £4.75
SALE PRICE £2.37

K546 Polystyrene/mica/ceramic caps. – Lots of useful small value caps up to about .01µF in voltages up to 8kV. Good variety. 100 £2.75
SALE PRICE £1.37

K528 Electrolytic Pack – All ready cropped for PCB mounting, this pack offers excellent value for money. Good range of values and voltages from 0.47µF to 1000µF, 6V to 100V. £3.95 250 £8.95
SALE PRICES 100 £2.00 250 £4.50

K518 200 Disc Ceramic Caps – Big variety of values and voltages from a few pF to 2.2µF; 3V to 3kV. £1.00
SALE PRICE 50P

K530 100 Assorted Polyester Caps – All new modern components, radial and axial leads. All values from 0.01 to 1µF at voltages from 63 to 1000!! Super value at £3.95
SALE PRICE £2.00

K558 Jumbo electrolytic pack – 10kg of screw top computer grade electrolytic capacitors. Values from 400µF to 83,000µF, voltages 15V to 200V. About 40 caps per parcel. Value if bought individually over £100! Our price? Just £20.00. Order now!
SALE PRICE £10.00

SWITCHES & RELAYS

K520 Switch Pack – 20 different assorted switches – rocker, slide, push, rotary, toggle, micro etc.... Amazing value at only £2.00
SALE PRICE £1.00

W4700 Push Button Banks – An assortment of latching and independent switches on banks from 2 to 7 way, DPCO to 6PCO. A total of at least 40 switches for £2.95 100 £6.50
SALE PRICES 40 £1.50 100 £3.25

K532 Relays – Wide selection of styles voltages and contacts. 4v-240v, AC/DC, SP and 4PCO 20 for £6.00
SALE PRICE £3.00

K542 Reed Relays

Mostly DIL, single pole & double pole also some changeover, these are manufacturers rejects, but a good proportion work. 5V-50V coils 50 assorted £3.30
SALE PRICE £1.65

K569 Reed Switch Pack. A selection of about 15 types of reed switch from submin 12mm long to 5A rated 50mm long, mostly form A (make), few form C (Changeover). Pack of 30 £2.75
SALE PRICE £1.37

OPTO

K539 Led Pack – not only round but many shaped leds in this pack in red, yellow, green, orange and clear. Fantastic mix. 100 £5.95 250 £13.50
SALE PRICES 100 £3.00 250 £6.75

K524 Opto Pack – A variety of single point and seven segment LEDs (incl. dual types) of various colours and sizes, opto isolators, numicators, multi digit gas discharge displays, photo transistors, infra red emitters and receivers. 25 assorted £3.95
SALE PRICE £2.00

HARDWARE

K551 6BA screws – In a variety of lengths and heads from 3/16" to 20mm long. Steel. 200 £2.00
SALE PRICE £1.00

K559 Knobs – Wide selection of sizes, shapes and styles for various diameter shafts and sliders 25 for £1.95
SALE PRICE £1.00

K535 Spring Pack – approx. 100 assorted compression, extension and torsion springs up to 22mm dia. and 30mm long £1.70.
SALE PRICE 85P

K571 Cable Clips – 6 or 7 different sizes from 3.5mm to double T & E mostly black and grey. 100 assorted 99p
SALE PRICE 50P

K564 PCB stand-offs. A mixture of 8 different styles and sizes from 4.75 to 12.7mm high. 100 £2.40
SALE PRICE £1.20


K567 Wire Ties. 5 types to take 4-15mm dia cable bundles. 100 £1.70
SALE PRICES 85P

K565 Miniature PCB supports in nylon. 6 different styles – sizes from 6.35 to 13.24mm high. 100 £2.20
SALE PRICE £1.10

K566 Self adhesive cord clips in moulded nylon. 5 styles/sizes. Base size from 15.9 to 31.8mm square Pack of 100 £2.70
SALE PRICE £1.35

K568 Giant Plastic Pack Approx. 1000 pieces – standard and miniature PCB supports, self adhesive ribbon cable clips, straps, ties, cord clips. This lot would normally cost around £50.00
Our Special Price £12.00
Sale price £6.00

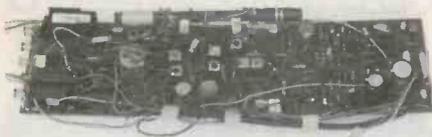K563 Cable markers (ident sleeving). Over 1000 pieces, all with either letter or number. Assorted colours and sizes from 1-5mm dia. over 50 different! Pack of 1000 £2.50
SALE PRICE £1.25



Z497 AM/FM Stereo Tuner Panel. Complete radio chassis with push-button selection for LW/MW/FM and ON/OFF. Ferrite rod for LW & MW selection, co-ax socket for FM aerial. Supplied with mains transformer and rectifier/smoothing cap, and wiring details. PCB is 330 x 90mm. Reduced to £7.95
SALE PRICE £4.00

1W Amplifier – mono



Z914 Audio amp panel 95x65mm with TBA820 chip. Gives 1W output with 9V supply. Switch and vol. control. Just connect batt. and speaker. Full details supplied. Only £1.50; 10 for £12.00; 25 for £25.00; 100 for £75.00

SALE PRICES 75p each; 10 £6.00; 25 £12.50; 100 £37.50

1W Amplifier – stereo

Z915 Stereo version of above 115x65mm featuring 2xTBA820M and dual vol. control.

£3.50, 10 for £30, 25 for £65, 100 for £200

SALE PRICES £1.75, 10 £15, 25 £32.50, 100 £100



Z974 Mixer Amp Panel – 115x115mm and gives 1W O/P from a TBA820M chip. There are two inputs, one via a pre-amp, from phono sockets and separate volume controls. A third pot is used to fade from one input to the other. There are also 2 4p 3w rotary switches. Attached to the PCB by flying leads is a panel on which are mounted the 2 input skts, 2x5 pin DIN skts and 2 pin DIN speaker skt. A data sheet is supplied. All this for just £2.50
SALE PRICE £1.25



Z4134 Speaker remote control box. This is a cream case 125x95x42mm housing a 57mm dia speaker and 2 control knobs, one for volume and one to switch main-remote-dual, the 3 core 6m long lead enables volume to be controlled from chair or bed. Simple to fit, instructions included. £3.95
SALE PRICE £2.00



Z4135 'STETHOPHONE' mini stereo head-phones, complete with stereo jack plugs, 8R. Hinged headband. £1.75
SALE PRICE 87P

Hi-Res Monitor



Brand new and boxed, complete apart from case, the super high definition (1000 lines at centre) makes this monitor ideal for computer applications. Operated from 12V DC at 1.1A. Supplied complete with circuit and 2 pots for brilliance/contrast + connecting instructions. Standard input from IBM machines, slight mod (details included) for other computers.

Price £24.95 4 for £99.00

SALE PRICE £12.50; 4 FOR £45.00

Z494 Newbrain Motherboard. Micro-processor panel 265 x 155mm. Complete PCB for computer, Z80, EPROM, etc. 68 chips altogether + other associated components, plugs, sockets, etc. Brand new in original packing. £5.50
SALE PRICE £2.75

Z672 Newbrain motherboards. Complete but probably faulty. £3.50

SALE PRICE £1.75

Z620 68000 PANEL PCB 190 x 45mm believed to be from ICL's 'one per desk' computer containing MC68008PB (8MHz 16/8 bit microprocessor) + 4 ROMs all in sockets. TMP52220CNL, 74HCT245, HCT138, LS38 & LS08, also 2 x 20w SIL sockets & 2 x 14w SIL sockets. £5.00
SALE PRICE £2.50

Set Top Converter




Z8828 Made by Thorn EMI, this was used to receive cable television. 2 part aluminium case 211x158x82mm (no front panel) contains 2 PCB's: (a) control board with multiway switch, dual 7 seg plug in display, couple of chips. (b) main board with mains transformer, tuner, RF section etc. Rear panel has input and output sockets. 2m mains lead with moulded on 13A plug. £9.00
SALE PRICE £4.50



Z803 Auto Dialler. Sloping front case 240 x 145 x 90/50mm contains 2 PCBs: one has 4 keypads (total 54 switches) + 14 digit LED display. 2xULN 2004, ULN2033 and 4067; the other has 12 chips +4 power devices etc. Case contains speaker. For use with PABXs, could probably be modified for exchange line. Needs 12V ac supply £9.00
SALE PRICE £4.50

Prestel Unit

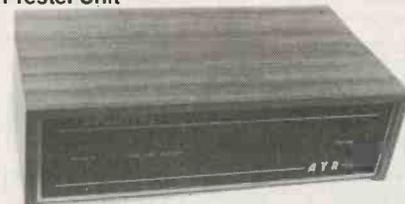

Z819 Brand new and boxed, complete with co-ax T connector, aerial lead and instruction book. Only one snag – the remote control hand-set is missing. Size of smart wooden case is 347x187x100mm. Mains operated. Old style BT plug. Made by Ayr Electronics, Model P £22.00
SALE PRICE £11.00



Z8862 Video game unit with 10 games, utilizing the AY-3-8610 chip. Consists of 2 handheld units 145 x 60 x 45mm made of light and dark grey high impact plastic. Unit 1 has a control panel with 0-9, serve and reset buttons, 3 switches for ball size, ball speed and sound on or off, and built in joystick. Unit 2 has a serve button and joystick. The two units have 2m of 5 core cable between them, and the 3m lead from unit 1 has 3 x 3.5mm plugs; 1) 7-5V input; 2) audio out; 3) composite video out. Worth what we're asking just for the cases! £9.95
SALE PRICE £5.00

Dual Sheet Feeder



Z8837EXXON DUAL SHEET FEEDER Z200. Overall 395x210x285mm. Brand new and containing some very high class electronics. although of little practical use as it stands, it makes a great break down unit. It contains:
 3x12V 36R 7.5° stepper motors by Airpax and associated gear trains drive belt etc.
 2x12V Solenoids
 1x12V electronic buzzer
 2 extremely sensitive micro-switches.
 1 PCB containing 4xTIP115, 4xTIP110, 2x7407, LM3302 comparator + T's, R's, C's, plugs, sockets etc.
 1 control panel containing 4 LED illuminated push buttons + green LED on small PCB
 1xOPB703A opto coupler
 1xOPB7111 opto coupler


Obviously, a very expensive piece of machinery to produce – but once again our contacts in the trade have enabled GREENWELD to procure a few hundred for a fairly modest sum, allowing us to offer them at the bargain price of £24.95
SALE PRICE £12.50

Touch Pad



Z811 Cumana Touch Pad for the BBC computer. This remarkable add-on enables you to draw on the screen using a stylus with the touch sensitive pad. Supplied with 2 stylii, power/data connecting lead and demo tape with 4 progs. Contains state-of-the-art electronics. Originally being sold at £79.95 – but we can offer a limited quantity of these brand new and boxed for just £19.95
SALE PRICE £10.00

Fibre Optics

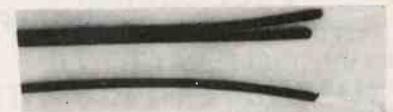

Scoop purchase of single and twin cable. For use with visible light or infra-red. Core 1mm dia, overall 2.25mm dia.

Single 50p/m; 20m coil £4.00
 Twin 90p/m; 20m coil £6.00
SALE PRICES 20M SINGLE £2.00
 20M TWIN £3.00

JIMMY

the electronic football game of skill



Z817 Exciting electronic football game - Waddingtons' 'JIMMY'. Brand new models in full working order, but without plastic peripherals, stickers etc. Red plastic case 420mm long x 93mm wide contains keypad and seven segment LED's to keep score either end. The centre section 'players' are represented by red 5mm LED's, 14 altogether. The main chip is the TMS1000, programmed to make odd noises whilst playing and a tune when a goal is scored. Also inside are 13 plastic transistors, 57mm 8R speaker, power supply socket, R's, C's etc. Powered by 2xPP3 batts. Solo or dual play. Supplied with instruction sheet, playing field complete with coloured 'players'. Good fun to play as a game and good value for the electronics within. Originally retailed at £19.95.

Only £5.00

Sale price

£2.50

SPEECH CHIPS

SPO256A

Only £1.00

10 for £7.00 100 for £50.00

OTHER SEMICONDUCTORS:

See pages 82-83 of catalogue 25% off all prices!!

POWER FET'S

Pair of 140V 100W Hitachi devices 2SJ49 & 2SK134. List price **£10.72**

Our Price

£6.00

SWITCH MODE PSU BARGAINS



ASTEC Model AA12531

I/P: 115/230V ac 50/60Hz

O/P: V1 + 5v 5A

V2 + 12v 0.15A

Size: 160 x 104 x 45mm

Partially enclosed panel with fixing holes in steel case on 120 x 125mm centres.

Inputs and Outputs are on colour coded leads; there is also an EEC socket on a flying lead.

£6.95



ASTEC Model AC9231

I/P: 115/230V ac 50/60Hz

O/P: 50Watt max:

V1 + 12v 2.5A

V2 + 5v 6.0A

V3 12v 0.5A (+ or -)

V4 5v 0.5A (+ or -)

Size: 203 x 112 x 60mm

Fully enclosed case with built in tapped mounting holes.

Inputs and Output pins on edge of panel.

£9.95

KNOCKOUT KNOBS!!

Sim to K9 - 19mm high x 20mm dia with coloured tops.

Pack of 25 **£3.00**

DISK DRIVE PSU KIT

Ideal for powering single 3 1/2" or 5 1/4" drive. Mains input, stabilized smoothed outputs, 5V@1A + 12V@1A. Simple, easy to assemble kit with all parts and full instructions. **£4.95**


VEROBLOC

AMAZING OFFER!!

RRP **£6.69**

ONLY

£4.95

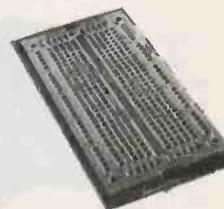

ANTEX

All Soldering Equipment 15% off!!

SOLDER

16g 500gm reels resin-cored solder. Only **£3.95**; 10 reels **£33.00**

PHONE YOUR ORDER THROUGH NOW - VISA & ACCESS ACCEPTED.
(0703) 772501

GREENWELD
ELECTRONIC COMPONENTS

443C MILLBROOK ROAD, SOUTHAMPTON, SO1 0HX.

ORDERING INFORMATION

All prices include VAT; just add £3.00 P&P; Min order value £10.00. Official orders from schools welcome - Min invoice charge £10.00. Our shop has enormous stocks of components and is open 9-5.30 Mon-Sat. Come and see us!

HOW TO CONTACT US:

By post using the address above; **by phone** (0703) 772501 or 783740 (ansaphone out of business hours); **by FAX** (0703) 787555; **by E Mail** Telecom Gold 72:MAG36026; **by Telex** 9312131093 (GWG)

1989 CATALOGUE SALE PRICES BY PAGE NUMBER

P1-18	10% off	P72	All 1/2 price	P87	Relays 25% off
P25	10% off	P73	All 1/2 price		Rest 1/2 price
P31-34	10% off		except SB15	P88	All 1/2 price
P35-36	5% off	P74	All 1/2 price	P89	All 1/2 price
P55	10% off	P75	All 1/2 price		except:
P57-59	10% off	P76	All 1/2 price		Z4072 25% off
P62-63	20% off	P77	All 1/2 price		Z656 25% off
		P78	All 1/2 price		Z802 20% off
BARGAIN LIST PAGES		P79	All 1/2 price	P90	All 25% off
P68	All 1/2 price	P80	All 1/2 price	P91	All 25% off
P69	All 1/2 price	P81	All 1/2 price	P92	Z4100 £2.00
P70	SB17 £1.00	P82-83	25% off		Z488 £2.00
	Z8827 £2.00	P84	All 1/2 price		J001-3 £1.20/10
	Hi-Res Monitor	P85	All 1/2 price		Rest 1/2 price
	£12.50	P86	All 1/2 price	P93	All 1/2 price
	SB14 £1.50		except joysticks	P94	All 1/2 price
P71	All 1/2 price				

1989 SPRING SUPPLEMENT SALE PRICES


P3-10	10% off		Rest 1/2 price	P26	All 25% off
P12-13	10% off	P24	SB10 £2.00	P27	Z8862 1/2 price
P15-17	10% off		Rest 1/2 price		Rest 25% off
P18	20% off	P25	Z4162 20% off	P28	All 1/2 price
P19-22	All 1/2 price		Z4163 20% off	P29	All 1/2 price
P23	Z8858 20% off		Z4164 Sold out	P30	10% off
	Z4167 20% off		SB6 Sold out	P32	Headphones all given away
	Z8861 20% off		Rest 25% off		

To bring this series towards the end, we take stock of the impact of digital electronics on our lives. What is the nature of this impact? Does it improve the quality of our lifestyle? Does it raise problems too? What of the future?

END OF THE ABACUS

The abacus is an ancient type of calculator (Fig. 1). It was particularly common in the Far East. I first saw abacuses (or is it abaci?) when I visited Hong Kong in 1970. Every shop in that city had an abacus on the counter for totting up the customer's bill. It was fascinating to watch a proficient operator frenziedly clicking the beads up or down the rods and rapidly obtaining the total. Old-tech it may be but, for adding up accounts, using an abacus can still be as quick as using a pocket calculator. Despite this, in 1970 the day of the abacus was nearly at an end. When I visited Hong Kong again two years later, there was not a single abacus to be seen. The shop counters were littered with pocket calculators – every shop assistant seemed to have at least one – with which to work out the account. Digital electronics had had its devastating impact on tradition.

Fig. 1. An abacus – the earliest type of calculator

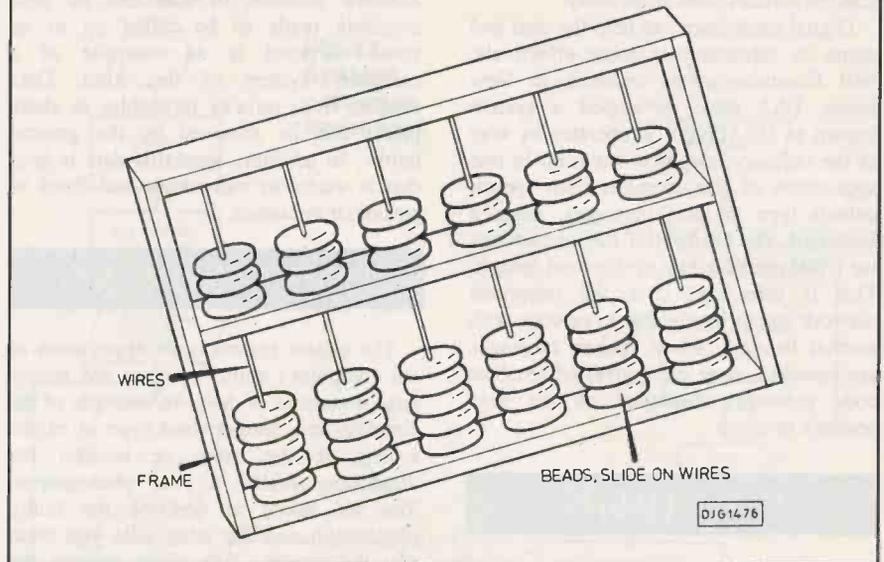

too. Hand your charge-card to the operator, and the account is paid from your account in an instant. 'Plastic money' is itself a result of digital electronics. Charge-cards and credit-cards, cash-dispensers and similar equipment all depend heavily on digital electronics and would be almost

over-typing them with 'X's. Nowadays, using a word-processor, all the errors can be removed, whole sentences added or deleted, and long passages of text can be shifted around at the press of a key. This does not necessarily mean that the text is any more interesting and informative when

DIGITAL ELECTRONICS

Part II – Applications and implications

BY OWEN BISHOP

Owen takes an overall look at how digital electronics affects our lives, and sets an end-of-term exam!

unworkable if one had to rely on traditional manual book-keeping. Such innovations are a great convenience, helping to make life smoother and easier.

COMMUNICATING

One of the biggest differences that digital electronics has made to the author's working life is the use of a wordprocessor. When I prepared my first contribution to PE in 1971 it was laboriously typed by hand. Having had no training in typing, my manuscript was a mass of typing errors with words and sentences crossed out by

it is written, but it must be very much easier for the Editor to check and for PE's typesetter to deal with! (*Yes! Ed*) But technology has its drawbacks. In the good old days of the typewriter I used to be able to sit outdoors on sunny days, enjoying the garden and getting a good sun-tan while working. Now I'm kept indoors, chained to the computer in a semi-darkened room. Perhaps a lap-top portable is the answer.

If it's a matter of getting material quickly to the Editor, digital electronics helps again. Fax machines are ideal for transmitting documents, including handwritten letters, drawings, diagrams and photographs through the public telephone network. Over 900,000 machines were installed world-wide in 1986 and the numbers continue to grow rapidly. Fax (short for *facsimile* – 'an exact copy') uses an optical scanner to read a document and converts this into digital signals, which it sends through a modem over the telephone system. At the receiving end, the signals are used to produce a copy of the document on a special thermal printer. A fax machine looks rather like an ordinary photocopying machine, and it takes less than a minute to transmit or receive an A4 page. The quality is about the same. Moreover, transmission is instantaneous. As a document is fed into a fax machine in

an office in, for example, New Zealand, the copy emerges from a fax machine in a London office 12000 miles away.

Digital electronics can help the deaf and dumb to communicate more effectively. Bell Communications research in New Jersey USA have developed a system known as DEAFNET. It operates by way of the ordinary telephone network. In one application of this, persons with speech defects type in their messages, using a keyboard. The DEAFNET device converts the typed message into synthesised speech. This is then sent over the telephone network and is intelligible to persons with normal hearing. When spoken messages are received, they are converted to short code messages displayed on the deaf person's terminal.

COMPUTERS

All of the above-mentioned advances in the use of digital electronics depend upon computers. This is taking the word 'computer' in its widest sense. It includes not only the micro, mini and mainframe computers, used for wide-ranging purposes, but also the digital circuitry built into such devices as fax machines, washing machines and cash registers.

The essential point about a computer is that it is designed to process data. It can process

- * large amounts of data
- * very quickly and
- * without making a mistake.

In the early days it became a habit to blame all kinds of mistakes on the computer. But a computer doesn't make mistakes. It only does what it is told to do. Practically all of the errors blamed on 'our computer' were the fault of the humans who programmed the computer wrongly or fed it with incorrect data. Nowadays, with people becoming more computer-aware, such excuses are no longer acceptable. This in turn means that persons using computers today have to accept full responsibility for the use they make of them.

DATA BANKS

The storage of masses of data is nothing new. Libraries have fulfilled this function for hundreds of years. What is new about the computer data storage is that it can be accessed so rapidly. Instead of browsing through several books for an hour or so, the data you need is available in microseconds. This puts the using of data on to an entirely different plane. Data that would take a life-time to collect and collate can now be processed in an hour or so. The computer can be programmed to search a data bank, extract any given items of data, analyse them in dozens of different ways, and present the results as

printed tables or coloured graphics displays – all in a few seconds or minutes. Massive amounts of data can be held available ready to be called up in an instant. Prestel is an example of a computer system of this kind. Data ranging from railway timetables to share prices can be accessed by the general public. In addition, specialist data is held that is useful to individuals and firms in particular industries.

EXPERT SYSTEMS

The *expert system* is an application of the computer's ability to store and access large quantities of data. An example of the simplest non-computerised type of expert system is the table or booklet for diagnosing faults in your photographs. You are asked to describe the faulty photograph and the table tells you what you did wrong. You might consult the table under the heading 'Photo is plain black', for example, and be told that (a) you forgot to take off the lens cap; or (b) you forgot to press the shutter; or (c) it's a photo of a coal-cellar. The table gives you the expert's opinion.

A computerised expert system carries this idea many stages further. An expert system on poisons has been devised recently at the University of Surrey. It is intended to help doctors diagnose cases of poisoning in children under five. Almost half the cases of poisoning occur in children of that age group so rapid diagnosis, leading to rapid treatment, can be an important factor in saving lives.

The computer stores data on the 100 most toxic substances. The data for each poison includes its physical form (solid, liquid etc), distinguishing features such as smell, descriptions of the types of bottles or packaging used for each, the nature of the poisonous principle, how harmful it is, what symptoms it produces and what treatment is required. The computer asks the doctor to key in details of the poison as far as they are known. Possibly the doctor may have only a tablet to base the diagnosis on, or perhaps only a label torn from a bottle bearing only part of the name.

With such slender evidence the computer searches its database and decides which one more more substances the poison might be. It asks the doctor for details of the child (age, weight, sex), and can then tell the doctor what symptoms would be produced in that child by the possible poisons. This should allow the doctor to narrow down the range of possibilities to one poison. The computer then prints out details of the treatment required. In addition to helping doctors in individual cases, the data of each case is stored in memory so as to build up a valuable fund of information on the incidence of poisoning in young children.

An expert system is often based on the

expert knowledge of a world authority or group of authorities on a given subject. The working day of an expert is of limited length so, in effect, this enables the expertise of that person or persons to be made available to many more people than would otherwise be possible.

ARTIFICIAL INTELLIGENCE

Using an expert system is almost like consulting with the expert directly. If the programme is planned with sufficient care, the questions asked and the answers given by the computer are identical with those that would be asked or given by the real expert in a live consultation. The computer *seems* to act as an intelligent human being. Indeed many people using such programs strongly feel that there *is* a human there, somewhere behind the scenes. Expert systems have been used in this way for the preliminary questioning of hospital out-patients, prior to their being examined by a qualified physician. The computer takes over the routine work, saving the time of the consultants for dealing with the more difficult aspects of each case. But the apparently human nature of the computer is merely a matter of clever programming. It is not real intelligence.

Artificial intelligence is an aspect of computer technology that has attracted many researchers. Is it possible to build a computer that will think for itself, that will think up its own responses, that will be able to solve problems that it has not been specifically programmed to solve? There are several aspects to AI:

ASPECTS OF AI

* *problem-solving* – a chess program solves the problem of what to do next by trying out all the possible combinations of moves on both sides for several moves ahead. Then it selects the one that gives the best outcome. It is successful against a human player because it can do all this very quickly, and it does not get confused or make mistakes. But a human player is able to solve the next-move problem in much 'cleverer' ways. The human may have a 'feel' for a situation, perhaps based on previous experience of similar situations. The human may try shock tactics – such as sacrificing a queen to put the opponent off-guard. The human player may vary tactics according to the known weaknesses of the opponent. Such psychological warfare is something of which computers are not yet capable.

* *pattern-recognition* – the computer is programmed to recognise regularities and patterns in masses of raw data. This includes the ability of the computer to recognise visual patterns, such as when a robot is able to identify nuts and bolts or mechanical parts by their shape.

* **automatic programming** – instead of writing a program, you tell the computer what the program has to do and the computer writes, tests and debugs its own program.

* **natural-language processing** – this is a major aspect of AI, important because it opens the way for humans to communicate with computers by speech. Programmes for translating one language into another (eg English into Russian) also fall into this category. The most difficult aspect of natural language processing is speech recognition. As Tom Ivall explained recently (PE Nov 1988), sentences or phrases with entirely different meanings may sound exactly alike. He quoted two examples 'A tax on shipping' and 'Attacks on shipping'. Spoken with unnaturally long gaps between the words these sentences are distinguishable, but spoken at normal speed they are not. How is the computer to know which is which? One of the goals of AI is to enable the computer to understand the context of the sentence sufficiently well to know which of the two is intended. Similarly, if the computer is going to be able to *completely* take over the function of the office typist, it must be able to distinguish between the letter that is being dictated to it and asides such as 'Oh help! Where did I put that file?' and 'Thanks, no milk and two sugars please.'

PARALLEL PROCESSING

According to Sir Clive Sinclair, reported in PE June 1988, the computers that will be able to further the aims of AI are on their way. Computers employing risc microprocessors are already with us and give a tenfold increase in speed as explained last month. But the big development is that of *parallel processing*. The current generation of computers have a single processor of cpu. With parallel processing the computer has many processors all working simultaneously. Sir Clive predicts that there may be as many as 65000 processors in one machine. Such machines developed over the next 20 years will be able to recognise speech intelligently and you will be able to talk to them very much as you would talk to another human. Machines of this kind, incorporating one or more expert systems will be there in the home to act as family doctor, lawyer and adviser in general. Of course, even then, the computer will not be able to take the place of a human adviser completely. But it will know its own limitations and, in such cases, tell you from whom to obtain advice. We might also see the demise of the school as we know it today. Instead of crowding 30 children in a room to be taught by a human teacher, each child will be taught at home by a specialised expert system. The computer will respond to the needs and

difficulties of the child in a way that the over-worked school-teacher can never hope to do. Schools will exist only for the more 'social' side of education, such as discussion groups, seminars, dramas and sport.

EVER ONWARD

As well as developing computer architecture and design, manufacturers are continually striving to improve the hardware. One of the latest innovations is the surface mounted device. Instead of the component having wire leads which are soldered to the circuit-board tracks (Fig. 4).

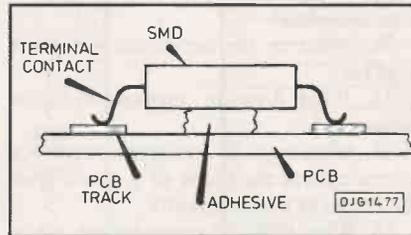


Fig.2. Mounting a surface-mounting device

Prior to soldering the smds are held in place by a spot of adhesive. Alternatively, a special solder paste is used that acts as an adhesive and then as a solder when heat is applied. SMDs are used in non-digital electronics as well as digital electronics. Their main advantage is that they are very small. For example one of the standard sizes, the 0805 package, measures only 0.08in by 0.05in (approx 2mm by 1.3mm). This allows more components to be mounted on each board, an important consideration in computer design. The shortness of the leads between the smd and the board results in reduced lead inductance. This means that circuits can operate at higher speeds, an important factor in digital circuits.

MEGACHIPS

Another continued trend is toward larger and larger memory chips. One of the latest is Philips Megachip, capable of storing 131,072 (128K) 8-bit words. The total of 1,048,576 bits (just over 1 megabit) is stored in memory cells each consisting of six transistors. This gives a total of 6,291,456 cmos transistors on a chip measuring only 7.7mm by 12.2mm. Yet the time to access any individual byte is only 25 nanoseconds. Even larger chips are becoming available, so the computer has virtually immediate access to an enormous amount of information. If even more data is required, there is bulk storage in the form of optical discs, capable of storing up to 20,000 megabits each, with fairly rapid access time. Videotapes can store up to 150,000 megabits.

RECAPPING

Before we take a deep breath next month and look at not only the benefits of computers but also some of the problems they bring, why not check what you have learned in the series by trying the questions below. We'll give the answers next month.

1. Write these decimal numbers in binary: 4, 15, 110, 254.

2. Write these binary numbers in decimal: 10, 110, 1101, 10101010.

3. In what ways do we usually represent 'true' in binary logic?

4. Identify these two truth tables:

(a) Inputs		Outputs	(b) Inputs		Outputs
A	B	Z	A	B	Z
0	0	0	0	0	0
0	1	0	0	1	1
1	0	0	1	0	1
1	1	1	1	1	0

5. What does ttl stand for and what is its operating voltage?



6. Name one of the cmos logic series and state its operating voltage range.

7. Work out the truth table of logic circuit in Fig. 3. What is the name of this logical operation?

8. (a) Complete the diagram of a bistable flip-flop in Fig. 4.

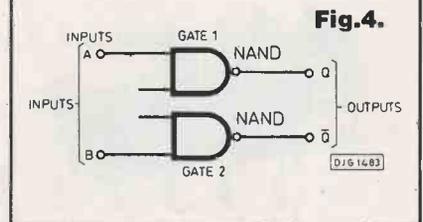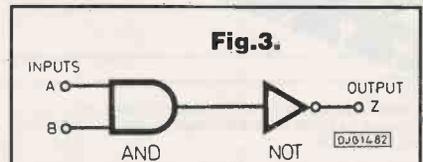(b) Both inputs A and B are high; output Q is high; output \bar{Q} is low.

How do we make the outputs change state, so that Q is low and \bar{Q} is high?



9. What are the features of a Schmitt trigger gate?

10. A monostable multivibrator is built from a pair of NAND gates, a resistor and a capacitor. State two ways of making the pulse length longer.

11. What is the difference between the output of a monostable multivibrator and the output of an astable multivibrator?

12. A 555 timer is wired as a monostable multivibrator. The resistor is 33 kilohms, the capacitor is 47 microfarads. What is the length of the pulse?

13. What are the three main sections of a typical logic system?

14. Describe the action of a D-type flip-flop (TTL 7474).

15. What types of logic circuit can be built from a chain of D-type flip-flops?

16. Write these binary numbers in hexadecimal: 1101, 1011000, 11110001.

17. Write these hexadecimal numbers in binary: &4, &C, &56.

18. What is the essential feature of a synchronous counter, as opposed to an asynchronous (ripple) counter?

19. What is meant by *fanout*?

20. What do the initials ldr stand for? What happens to the resistance of an ldr as the amount of light falling on it is increased? Explain the action of the circuit in Fig. 5. If it is in the dark to begin with and the light is then increased.

21. Name three types of sensor that can be used in a light-sensitive interface.

22. Name the device that shows decrease of resistance as its temperature is increased.


23. Suggest two devices you could use to interface a logic circuit to a small dc motor.

24. What is meant by the term *tri-state output*?

25. What is meant by the term PISO?

26. The registers of an 8-bit shift register hold the data '01101010'. What would they hold after a single shift left? What effect does this have on the value in the register?

27. What are the differences between a

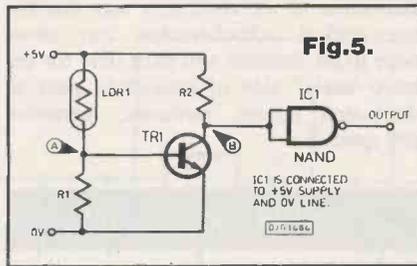

register and a latch?

28. What is the action of the WE (write-enable) input of a 2114 memory chip?

29. What is the difference between ram and rom?

30. What is an eeprom?

31. Which part of a microprocessor processes data?

32. What is the accumulator register used for?

33. What does an analogue-to-digital converter do?

34. What type of converter would you use to control the speed of a motor from the output of a logic circuit?

35. What types of converter are useful for sending analogue data along a single line or to the serial input of a microcomputer?

36. What is a computer?

37. What does cpu stand for?

38. What do we call the three sets of connections used for transferring data from one part of a computer to another?

39. What do we call the coded byte which tells a microprocessor what to do next?

40. Name four types of instruction commonly used in machine-code programs.

41. What type of program is used to make it easier to write machine-code programs?

42. What are *mnemonics*?

43. What do we call the branch of computing that deals with problem-solving, pattern recognition, and automatic programming?

44. Name some devices used in the home that usually contain a microprocessor.

45. What development in computer design makes use of several or many processors operating simultaneously?

46. List four benefits of the use of computers.

47. List four aspects of computer use that need careful control.

48. An audio digitising circuit samples that the audio signal 5000 times a second. What is the highest frequency that is reproducible by this circuit?

49. Why is it better to use a 12-bit a-to-d converter in a digitising circuit, rather than an 8-bit converter?

50. What are the advantages of digitising audio signals?

DON'T MISS NEXT MONTH'S CONCLUDING ARTICLE.

PI

HART

HART ELECTRONICS are specialist producers of kits for designs by JOHN LINSLEY-HOOD. All kits are APPROVED by the designer.

LINSLEY-HOOD CASSETTE RECORDER CIRCUITS



Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are optimised for our HS16 Super Quality Sendust Alloy Head. Switched bias and equalisation to cater for chrome and ferric tapes. Very easy to assemble on plug-in PCBs. Complete with full instructions.

Complete Stereo Record/Play Kit £33.70
VU Meters to suit £2.30 each
Reprints of original Articles 75p no VAT
860X Stereo Mic Amplifier £8.70

LINSLEY HOOD 300 SERIES AMPLIFIER KITS

Superb integrated amplifier kits derived from John Linsley-Hood's articles in 'Hi-Fi News'. Ultra easy assembly and set-up with sound quality to please the most discerning listener. Ideal basis for any domestic sound system if quality matters to you. Buy the kit complete and save pounds off the individual component price.

K300-35. 35 Watt. Discount price for Complete Kit £98.79
K300-45. 45 Watt. Discount price for Complete Kit £102.36
RLH4&5. Reprints of Original Articles from 'Hi-Fi News' £1.05 no VAT

LINSLEY-HOOD SUPER HIGH QUALITY AM/FM TUNER SYSTEM.



Our very latest kit for the discerning enthusiast of quality sound and an exotic feast for lovers of designs by John Linsley-Hood. A combination of his ultra high quality FM tuner and stereo decoder described in "ELECTRONICS TODAY INTERNATIONAL" and the Synchronyne AM receiver described in "Wireless World". The complete unit is cased to match our 300 Series amplifiers. Novel circuit features in the FM section to include ready built pre-aligned front-end, phase locked loop demodulator with a response down to DC and advanced sample and hold stereo decoder together make a tuner which sounds better than the best of the high-priced exotica but, thanks to HART engineering, remains easy to build. The Synchronyne section with its selectable bandwidth provides the best possible results from Long and Medium wave channels, so necessary in these days of split programming. If you want the very best in real HiFi listening then this is the tuner for you. Since all components are selected by the designer to give the very best sound this tuner is not cheap, but in terms of it's sound it is incredible value for money. To cater for all needs four versions are available with variations up to the top of the range full AM/FM model, with any unit being upgradeable at any time. Send for our fully illustrated details.

STUART TAPE RECORDER CIRCUITS

Complete stereo record, replay and bias system for reel-to-reel recorders. These circuits will give studio quality with a good tape deck. Separate sections for record and replay give optimum performance and allow a third head monitoring system to be used where the deck has this fitted. Standard 250mV input and output levels. These circuits are ideal for bringing that old valve tape recorder back to life.
K900W Stereo Kit with Wound Coils and Twin Meter Drive £65.67
RJS1 Reprints of Original Articles £1.30 no VAT

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks £7.66
HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response £14.86
HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head £14.60
HX100 Stereo Permalloy R/P Head. Special Offer £2.49
MA481 2/2 Language Lab R/P head £13.35
SM166 2/2 Erase Head. Standard mounting. AC type £8.85
SM150 2/2 Erase Head. DC Type £3.60
HQ751E 4/4 Erase Head for Portastudio etc. £46.80
Full specifications of these and other special purpose heads in our lists.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.66 plus VAT and 50p postage.

Tape Head De-magnetiser. Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback £4.54
Curved Pole Type for inaccessible heads £4.85

Send for your free copy of our LISTS. Overseas please send 2 IRCs to cover surface Post or 5 IRCs for Airmail.

Please add part cost of post, packing and insurance as follows:

INLAND
Orders up to £10 - 50p
Orders £10 to £49 - £1
Orders over £50 - £1.50

OVERSEAS
Please send sufficient to cover Surface or Air Post as required.

Personal callers are always very welcome but please note that we are closed all day Saturday

24hr SALES LINE
(0691) 652894

ALL PRICES EXCLUDE VAT UNLESS STATED

HART
HART ELECTRONIC KITS LTD
4 PENTYLAN MILL
OSWESTRY, SHROPSHIRE
SY10 9AF

ELMASET INSTRUMENT CASE

300 x 133 x 217mm deep £10 ea (£2.20)

REGULATORS

LM317T PLASTIC TO220 variable £1
LM317 METAL £2.20
7812 METAL 12V 1A £1
7805/12/15/24V plastic 35p 100+20p 1000+ 15p
7905/12/15/24 plastic 35p 100+20p 1000+ 15p
CA3085 T099 variable reg 2/£1
LM338 5A VARIABLE £5

COMPUTER ICS

IM6402 UART £3
8086 processor equipment £2
USED 41256-15 £3.00
9 x 41256-15 SIMM MODULE NEW £25
8 x 4164-15 SIP MODULE NEW £8
41256-10 SURFACE MOUNT EX NEW BOARDS £3
HD146818 CLOCK IC £2
2864 EPROM £3
27128A 250ns EPROM NEW £3.20
FLOPPY DISC CONTROLLER CHIPS 1771 £10 ea
FLOPPY DISC CONTROLLER CHIPS 1772 £16 ea
68008 PROCESSOR EX-EQPT £5
ALL USED EPROMS ERASED AND BLANK CHECKED CAN BE PROGRAMMED IF DESIRED.
2764-30 USED £2
2716-45 USED £2 100/£1
2732-45 USED £2 100/£1
2764-30 USED £2 100/£1.60
27128-25/30 USED £2.50
27256-30 USED £3
1702 EPROM EX EQPT £5
2114 EX EQPT 60p 4116 EX EQPT 70p
6264-15 8k static ram £4
4416 RAM £3.50
USED 4416-15 RAM £2
USED 41464-15 £7
ZN427E-8 £3.50
ZN428E-8 £3.50

CRYSTAL OSCILLATOR

1.8342 MHz £1 each

CRYSTALS

2.77 MHz/4.000 MHz/4.9152MHz 20MHz 49.504 MHz

TRANSISTORS

BC107, BCY70 PREFORMED LEADS £1 £4/100 £30/1000
full spec £1 £4/100 £30/1000
BC557, BC548B 30/£1 £3.50/100

SIL RESISTOR NETWORKS

8 PIN 10k 22k 5/£1
8 PIN 22k 5/£1
10 PIN 68R 180R 22k 5/£1

POWER TRANSISTORS

OC35 (Marked CV7084) £1
POWER FET IRF9531 8A 60V 2/£1
2SC1520 sim BF259 3/£1 100/£22
TIP141/2 £1 ea TIP112/125/42B 2/£1
TIP35B TIP35C £1.50
SE9301 100V 10A DARL. SIM TIP121 2/£1
2N3055 EX EQPT TESTED 4/£1
PLASTIC 3055 OR 2955 equiv 50p 100/£35
2N3773 NPN 25A 160V £1.80 10/£16

QUARTZ HALOGEN LAMPS

A1/216 24V 150 WATTS £2.25
H1 12V 50W (CAR SPOT) £1.50

ZIF SOCKETS

ZIF SOCKETS 2/£1.50
TEXTTOOL single in line 32 way. Can be ganged (coupling supplied) for use with any dual in line devices.
14 WAY AMP ZIF SOCKET 4/£1

LARGE ELECTROLYTIC CAPACITORS COMPUTER GRADE

3300uF 350V SIC SAFCO FELSIC 037 £6(£1.50)
2200uF 160V SIC SAFCO FELSIC CO38 £4(£1.20)

TURNS COUNTING DIALS FOR MULTI TURN POTENTIOMETERS

all for 0.25" shaft
10 turn dial 21 mm dia. fits 3mm spindle £2
10 turn digital dial (3 digits) for 3mm or 6mm shaft £3.50
10 turn clock face dial for 6mm spindle £4

MISCELLANEOUS

ASSORTED SWITCHES, ROCKER, SLIDE, PUSH £2.50
SLOPING FRONT PLASTIC CASE 225 x 215 x 76mm
76 mm WITH ALL FRONT PANEL 200 x 130mm £4.00(£1)
HUMIDITY SWITCH ADJUSTABLE £2
WIRE ENDED FUSES 0.25A 30/£1
NEW ULTRASONIC TRANSDUCERS 40kHz £2/pair
12 CORE CABLE 7/0.2mm OVERALL SCREEN. £1/3 metres
POURABLE SMALL CYLINDRICAL MAGNETS 3/£1
OP AMP LM10CLN £2.90

BNC 50 OHM SCREENED CHASSIS SOCKET 3/£1

BNC TO CROC CLIPS LEAD 1 metre £1

MOULDED INDUCTOR 470µH size of a 1 watt film resistor 5/£1

TO-220 HEAT SINK sim RS 403-162 10/£2.50

SMALL MICROWAVE DIODES AEI DC1028A 2/£1

D.I.L. SWITCHES 10 WAY £1 8 WAY 80p 4/5/6 WAY 50p

180 volt 1 watt ZENERS also 12v & 75v 20/£1

PLASTIC EQUIPMENT CASE 9 x 6 x 1.25 in. WITH FRONT AND REAR PANELS CONTAINING PCB WITH EPROM 2764-30

AND ICS 7417 LS30 LS32 LS74 LS367 LM311 7805 REG. 9 WAY D PLUG, PUSH BUTTON SWITCH, DIN SOCKET £1.90

VN10LM 60v 1/2A 50hm TO-92 mosfet 4/£1 100/£20

MIN GLASS NEONS 10/£1

RELAY 5v 2 pole changeover looks like RS 355-741 marked STC 47WB05T £1 ea

MINIATURE CO-AX FREE PLUG RS 456-071 2/£1

MINIATURE CO-AX FREE SKT. RS 456-273 2/£1.50

DIL REED RELAY 2 POLE n/o CONTACTS £1

PCB WITH 2N2646 UNIUNION with 12v 4 POLE RELAY £1

400m 0.5w thick film resistors (yes four hundred megohms) 4/£1

MINIATURE CO-AX FREE PLUG RS 456-071 2/£1

MINIATURE CO-AX FREE SKT. RS 456-273 2/£1.50

STRAIN GAUGES 40 ohm Foil type polyester backed balco grid alloy £1.50 ea 10+ £1

ELECTRET MICROPHONE INSERT £0.90

Linear Hall effect IC Micro Switch no 613 SS4 sim RS 304-267 £2.50 100+ £1.50

HALL EFFECT IC UGS3040 + MAGNET £1

OSCILLOSCOPE PROBE SWITCHED X1 X10 £10

CHEAP PHONO PLUGS 100/£2 1000/£18

1 pole 12 way rotary switch 4/£1

AUDIO ICS LM380 LM386 £1 ea

555 TIMER 5/£1 741 OP AMP 5/£1

ZN414 AM RADIO CHIP 80p

COAX PLUGS nice ones 4/£1

COAX BACK TO BACK JOINERS 3/£1

4 x 4 MEMBRANE KEYBOARD £1.50

15.000uF 40V £2.50 (£1.25)

INDUCTOR 20uH 1.5A 5/£1

NEW BT PLUG + LEAD £1.50

1.25" PANEL FUSEHOLDERS 3/£1

CHROMED STEEL HINGES 14.5 x 1" OPEN £1 each

12v 1.2w small wire ended lamps fit AUDI VW TR7 SAAB VOLVO 10/£1

12V MES LAMPS 10/£1

STEREO CASSETTE HEAD 10/£1

MONO CASS. HEAD £1 ERASE HEAD 50p

THERMAL CUT OUTS 50 77 85 120°C £1 ea

THERMAL FUSE 121°C 240V 15A 5/£1

TRANSISTOR MOUNTING PADS TO-5/TO-18 £3/1000

TO-3 TRANSISTOR COVERS 10/£1

STICK ON CABINET FEET 30/£1

PCB PINS FIT 0.1" VERO 200/£1

TO-220 micas + bushes 10/50p 100/£2

TO-3 micas + bushes 15/£1

PTFE min screened cable 10m/£1

Large heat shrink sleeving pack £2

CERAMIC FILTERS 6M/9M/10.7M 50p 100/£20

MAINS LEAD WITH MOULDED 13A PLUG AND IEC SOCKET £1.50

IEC chassis plug rfi filter 10A £3

Potentiometers short spindles values 2k5 10k 25k 1m 5/£1

2M5 lin 4/£1

500k lin 500k log 4/£1

40kHz ULTRASONIC TRANSDUCERS EX-EQPT NO DATA £1/pr

PLESSEY INVERTER TRANSFORMER 50 CYCLES

11.5-0-11.5V to 240V 200VA £6 (£3)

ZENERS

5.6V 1W3 SEMIKRON 50K AVAILABLE @£25/1000
SUPPRESSOR EP606 120V BI DIRECTIONAL ZENER
IN 3 AMP W/PACKAGE 5/£1

DIODES AND RECTIFIERS

1N4148 100/£1.50

1N4004/SD4 1A 300V 100/£3

1N5401 3A 100V 10/£1

BA158 1A 400V fast recovery 100/£3

BA159 1A 1000V fast recovery 100/£4

120V 35A STUD 65p

BY127 1200V 1.2A 10/£1

BY254 800V 3A 8/£1

BY255 1300V 3A 6/£1

6A 100V SIMILAR MR751 4/£1

1A 800V BRIDGE RECTIFIER 4/£1

4A 100V BRIDGE 3/£1

6A 100V BRIDGE 2/£1

8A 200V BRIDGE 2/£1.35

10A 200V BRIDGE £1.50

25A 200V BRIDGE £2 10/£18

25A 400V BRIDGE £2.50 10/£22

SCRs

PULSE TRANSFORMERS 1:1+1 £1.25

2P4M EQUIV C106D 3/£1

MCR72-6 10A 600V SCR £1

35A 600V STUD SCR £2

TICV106D 800mA 400V SCR 3/£1 100/£15

MEU21 PROG. UNIUNION 3/£1

TRIACS

BT137-600 8A TO-220 2/£1

BT138-600 12A TO-220 70p

NEC TRIAC AC08F 8A 600V TO220 5/£2 100/£30

TXAL225 8A 400V 5mA GATE 2/£1 100/£35

TRAL2230D 30A 400V ISOLATED STUD £4 each

DIACS 4/£1

BT137-600 8A TO-220 2/£1

BT138-600 12A TO-220 70p

NEC TRIAC AC08F 8A 600V TO220 5/£2 100/£30

TXAL225 8A 400V 5mA GATE 2/£1 100/£35

TRAL2230D 30A 400V ISOLATED STUD £4 each

CONNECTORS

D25 IDC SOCKET FUJITSU £2

34 way card edge IDC CONNECTOR (disk drive type) £1.25

CENTRONICS 36 WAY IDC PLUG £2.50

CENTRONICS 36 WAY IDC SKT £4.00

BBC TO CENTRONICS PRINTER LEAD 1.5M £3.50

CENTRONICS 36 WAY PLUG SOLDER TYPE £4

USED CENTRONICS 36W PLUG+SKT £3

USED D CONNECTORS price per pair

D9 60p, D15 £1.50, D25 £2, D37 £2, D50 £3.50 covers 50p ea.

WIRE WOUND RESISTORS

W21 or sim 2.5W 10 of one value £1

R10 OR15 OR22 2R0 2R7 4R7 5R0 5R6 8R2 10R 12R 15R 18R

20R 22R 27R 33R 47R 56R 62R 91R 120R 180R 390R 430R

470R 680R 820R 910R 1K15 1K2 1K5 1K8 2K4 2K7 3K3 3K0 5K0

R05 (50 milli-ohm) 1% 3w 4 FOR £1

W22 or sim 6W 7 OF ONE VALUE £1

R47 R62 1R0 1R5 1R8 3R3 6R8 9R1 12R 20R 24R 27R 33R 51R

56R 62R 68R 100R 120R 180R 220R 390R 560R 620R 910R

1K0 1K2 1K5 1K8 2K2 2K7 3K3 3K9 4K7 8K2 10k 15K 16K 20K

W23 or sim 9W 6 of one value £1

R22 R47 1R0 1R1 15R 56R 62R 100R 120R 180R 220R 300R

390R 680R 1K0 1K5 5K1 10K £1

W24 or sim 12W 4 OF ONE VALUE £1

R50 2R0 9R1 18R 22R 27R 56R 68R 75R 82R 100R 150R 180R

200R 220R 270R 400R 620R 1K0 6K8 8K2 10K 15K

PHOTO DEVICES

SLOTTED OPTO-SWITCH OPCA OPB815 £1.30

2N5777 50p

TIL81 PHOTO TRANSISTOR £1

TIL38 INFRA RED LED 5/£1

4N25, OP12252 OPTO ISOLATOR 50p

PHOTO DIODE 50p 6/£2

MEL12 (PHOTO DARLINGTON BASE n/c) 50p

RPY58A LDR 50p ORP12 LDR 70p

LEDs RED 3 or 5mm 12/£1 100/£6

LEDs GREEN OR YELLOW 10/£1 100/£6.50

LEDs ASSORTED RD/GN/YW + INFRA/RED 200/£5

FLASHING RED OR GREEN LED 5mm 50p 100/£35

STC NTC BEAD THERMISTORS

G22 220R, G13 1K, G23 2K, G24 20K, G54 50K, G25 200K,

G16 1M, RES @ 20°C DIRECTLY HEATED TYPE £1 ea

F522BW NTC BEAD INSIDE END OF 1" GLASS PROBE

RES @ 20°C 200R £1 ea

A13 DIRECTLY HEATED BEAD THERMISTOR 1k res.

Ideal for audio Wien £2 ea

CERMET MULTI TURN PRESETS 3/4"

10R 20R 100R 200R 250R 500R 2K 2K2 2K5 5K 10K 47K

50K 100K 200K 500K 2M2 50p each

IC SOCKETS

6 pin 15/£1 8 pin 12/£1 14/16 pin 10/£1 18/20 pin 7/£1,

22/24/28 pin 4/£1 40 pin 30p

SOLID STATE RELAYS

40A 250V AC SOLID STATE RELAYS £18

POLYESTER/POLYCARB CAPS

100n 63v 5mm 20/£1 100/£3 1000/£25

1n/3n/5n/6n/8n/2/10n 1% 63v 10mm 100/£6

10n/15n/22n/33n/47n/68n 10mm rad 100/£3.50

100n 250v radial 10mm 100/£3

100n 600v sprague axial 10/£1 100/£6 (£1)

2u2 160v rad 22mm 100/£10

10n/33n/47n 250v ac x rated 15mm 10/£1

470n 250v ac x rated rad 4/£1

1U 600V MIXED DIELECTRIC 50p ea.

RF BITS

MINIATURE CO-AX URM95 30Ω 100m/£12

12 volt CO-AXIAL relays sim. RS 349-686 £6

Ex-equipment, with BNC tails

TRIMMER CAPS ALL 4/50p

SMALL 5pf 2 pin mounting 5mm centres 4/50p

SMALL MULLARD 2 to 22pF 4/50p

SMALL MULLARD 5 to 50pF 4/50p

grey larger type 2 to 25pF black 15 to 90pf

TRANSISTORS 2N4427 60p

FEED THRU CERAMIC CAPS 1000pF 10/£1

MINIATURE RELAYS Suitable for RF

5 volt coil 1 pole changeover £1

5 volt coil 2 pole changeover £1

12 volt coil 1 pole changeover £1

KEYTRONICS

TEL. 0279-505543

FAX. 0279-757656

P O BOX 634

SURVEILLANCE PROFESSIONAL QUALITY KITS

A range of high quality kits as supplied to leading UK security companies, all in-house designed and produced, not to be confused with cheap imports. All kits come fully documented with concise assembly and setting-up details, fibreglass PCB and all components. All transmitters are fully tuneable and can be monitored on a normal VHF radio or tuned higher for greater security. All units available ready built if required.

MTX Micro Miniature audio transmitter. 17mm x 17mm. 9V operation. 1000m range	£10.95
VT500 Hi-power audio transmitter. 250mW output. 20mm x 40mm. 9-12V operation. 2-3000m range	£12.95
VOX75 Voice activated transmitter. Variable sensitivity. 30mm x 40mm. 9V operation. 1000m range	£15.95
CTX900 Sub-carrier scrambled audio transmitter. Cannot be monitored without decoder fitted to radio. 30mm x 40mm. 9V operation. 1000m range	£18.95
DSX900 Sub-carrier decoder unit for monitoring CTX900. Connects to radio earphone socket. Provides output for headphones. 35mm x 50mm. 9-12V operation	£17.95
HVX400 Mains powered audio transmitter. Connects directly to 240V AC supply. 30mm x 35mm. 500m range	£15.95
XT89 Crystal controlled audio transmitter. High performance. 100mW output. Supplied with xtal for 108MHz. Others available to 116MHz. 85mm x 28mm. 9V operation. 2-3000m range	£29.95
TKX900 Tracker/Beeper transmitter. Transmits continuous stream of audio pulses. Variable tone and rate. Powerful 200mW output. 63mm x 25mm. 9V operation. 2-3000m range	£18.95
ATR2 Micro size telephone recording interface. Connects between telephone line (anywhere) and cassette recorder. Tape switches automatically with use of phone. All conversations recorded. Powered from line. 10mm x 35mm	£10.95
TLX700 Micro Miniature telephone transmitter. Connects to line (anywhere) switches on and off with phone use. All conversations transmitted. 20mm x 20mm. Powered from line. 1000m range	£10.95
XML900 RF bug detector. Variable sensitivity. Triggers LED and beeper when in presence of RF field. Detects MTX 15-20 feet. 55mm x 55mm. 9V operation	£21.95
XL7000 Professional bug detector/locator. Variable sensitivity. Twin mode ten segment LED readout of signal strength with variable rate beeper. Second mode AUDIO CONFIRM distinguishes between localised bug transmission and normal legitimate signal such as pagers, cellular etc. 70mm x 100mm. 9V operation	£49.95

UK customers please send cheques, PO's or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft or Eurocheque and add £5.00 per order for shipment. Credit card orders accepted on 0827 714476. Full catalogue available on receipt of 28p stamp. Trade enquiries welcome.



THE WORKSHOPS
95 MAIN ROAD, BAXTERLEY
Nr Atherstone, WARCS CV9 2LE



0827 714476

A WORLD OF OPPORTUNITY FOR RADIO OFFICERS

We offer a secure and rewarding shore-based career in the forefront of modern telecommunications technology. Thirty weeks special training (plus 6 weeks for non-typists) will prepare you to undertake a wide range of specialist duties as a RADIO OFFICER covering the complete communication spectrum from DC to light.

To qualify **you need** to hold or hope to attain:
an MRGC or

BTEC HNC in a Telecommunications subject with the ability to read morse at 20 wpm.

City and Guilds 7777 at advanced level, incorporating morse transcription skills, would be advantageous.

Anyone without the above qualifications who has 2 years radio operating experience will also be considered.

Age - preferably under 45 years.

We offer you:

Comprehensive Training; Good Career Prospects; Opportunities for transfers within UK and Overseas; Generous Leave Allowances and a Non-contributory Pension Scheme; Job Security; Attractive Salaries - and much more.

Salary (Reviewed Annually) - As a Radio Officer after training: £11,568 rising to £17,057 pa in 5 annual increments. (includes shift and weekend working allowance)

CIVIL SERVICE IS AN EQUAL OPPORTUNITY EMPLOYER.

For more information and application form write or telephone:



THE RECRUITMENT OFFICE, GCHQ, ROOM A/1108
PRIORS ROAD, CHELTENHAM, GLOS GL52 5AJ
OR TELEPHONE (0242) 232912/3



THREE SIMPLE CONSTRUCTION KITS

Especially aimed for the beginner. Have fun with your project even after you have built it and also learn a little from building it. These kits include high quality solder resist printed circuit boards, all electronic components (including speaker where used) and full construction instructions with circuit description.

- SK1 DOOR CHIME - plays a tune when activated by a pushbutton £3.90
- SK2 WHISTLE SWITCH - switches a relay on and off in response to whistle command £3.90
- SK3 SOUND GENERATOR - produces FOUR different sounds, including police/ambulance/fire-engine siren and machine gun £3.90
- SPECIAL OFFERS FOR SCHOOL AND TRAINING CENTRES - Contact Sales Office for discounts and samples.

ELECTRONIC GUARD DOG KIT




One of the best deterrents to a burglar is a guard dog and this new kit provides the barking without the bite! The kit when assembled can be connected to a doorbell, pressure mat or any other intruder detector and will produce a random series of threatening barks making the would-be intruder think you have a guard dog and try his luck elsewhere. The kit is supplied complete with high quality PCB, mains transformer, all components and instructions. The kit even includes a horn speaker which is essential to produce the loud sound required. The "dog" can be adjusted to produce barks ranging from a Terrier to an Alsatian and contains circuitry to produce a random series of barks giving a more realistic effect. Don't delay, fit one before you go on holiday and let our dog help you guard your home.

XK125 Complete kit of parts £24.00

POWER STROBE KIT

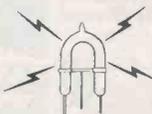Designed to produce a high intensity light pulse at a variable frequency of 1 to 15Hz, this kit also includes circuitry to trigger the light from an external voltage source (eg. a loudspeaker) via an opto isolator.



Instructions are also supplied on modifying the unit for manual triggering, as a slave flash in photographic applications or as a warning beacon in security applications. The kit includes a high quality pcb, components, connectors, 5Ws strobe tube and full assembly instructions. Supply: 240V ac. Size: 75x50x45.

XK124 Stroboscope Kit £13.75

VERSATILE REMOTE CONTROL KIT

This kit includes all components (+ transformer) to make a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits.

- Supply: 240V AC or 15-24V DC at 10mA.
- Size (excluding transformer) 9 x 4 x 2 cms.
- The companion transmitter is the MK18 which operates from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available MK9 (4-way) and MK10 (16-way), depending on the number of outputs to be used.
- MK12 IR Receiver (incl. transformer)** £16.30
- MK18 Transmitter** £7.50
- MK9 4-Way Keyboard** £2.20
- MK10 16-Way Keyboard** £6.55
- 601 133 Box for Transmitter** £2.60

SOLID STATE RELAY BARGAIN

- +ZERO VOLTAGE SWITCHING- No radio interference problems.
- +2.5KV INPUT to OUTPUT ISOLATION- No risk of damage to your computer or driver circuits.
- +4 KV TERMINALS to HEAT-SINK ISOLATION- Simply bolt onto a heatsink.
- +3V to 32V INPUT VOLTAGE- easily interfaced to TTL or CMOS LOGIC.



- +24V to 240V rms LOAD VOL.
- TAGE- allowing mains loads to be switched.
- +BUILT IN SNUBBER NETWORK- Enabling switching of inductive loads.
- +10A MAXIMUM CURRENT- 4A with no heatsink fitted at 40°C.

CD240/10 £2.25

SUPER-SENSITIVE FM MICROBUG

Highly sensitive FM transmitter measuring only 45 x 25 x 15mm, including the built-in microphone. Frequency 88-100MHz enabling reception on a standard domestic FM radio. Range approximately 300m depending on terrain. Powered by 9V PP3 (7mA). Its small size and highly sensitive electret microphone makes it ideal for surveillance, baby alarm, etc.

INTRODUCTORY PRICE £5.50

MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and off at present times over a 7-day cycle. LED display of time and day, easily programmed via 20 way keyboard. Ideal for central heating control including different switching time for weekends. Battery back-up circuit. Includes box 18 time settings.



- CT6000K** £47.20
- XK114 Relay kit for CT6000** includes PCB connectors and one relay. Will accept up to 4 relays 3A/240V c/o contacts ££4.30
- 701 115 Additional relays** £1.80

DISCO LIGHTING KITS

- DL1000K** This value-for-money 4-way chaser features by-directional sequence and dimming. 1kW per channel £19.25
- DLZ1000K** - A lower cost uni-directional version of the above. Zero switching to reduce interference £10.80
- DLA/1** Optional opto input allowing audio 'beat/light response 77p
- DL3000K** - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel. £15.60

GIANT SOLAR CELLS

The DL8000K is a 3-way sequencer kit built in opto-isolated sound to light input which comes complete with a pre-programmed EPROM containing EIGHTY - YES 80 different sequences including standard flashing and chase routines. The KIT includes full instructions and all components (even the PCB connectors) and requires only a box and a control knob to complete. Other features include manual sequence speed adjustment, zero voltage switching, LED mimic lamps and sound to light LED and a 300W output per channel. And the best thing about it is the price: **ONLY £31.50.**

NOW IN STOCK these giant size solar panels 12 x 12m will deliver 12 volts 200mA in bright sunlight and 11.5 volts 60mA on a typical British summer day (full and over-cast) **HUNDREDS OF USES** in the car or caravan, e.g. Charging NiCads, powering low voltage circuits where mains or battery supplies are inconvenient or coupled to a lead acid battery and a simple inverter you could build yourself a self contained mains supply for low power appliances. Stock No. 303 145. £14.50 (plus £1.75 for p&p on total order)

TR
13 BOSTON RD.
LONDON W7 3SJ
Tel: 01 567 8910

ORDERING INFORMATION:
ALL PRICES EXCLUDE VAT

FREE P&P on orders over £50 (UK only), otherwise add £1 + VAT.
Overseas P&P: Europe £3.50. Elsewhere £10. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.
LOCAL AUTHORITY AND EXPORT ORDERS WELCOME
GOODS BY RETURN SUBJECT TO AVAILABILITY

SEND 9" x 6" SAE & 50p FOR CATALOGUE OR CALL AT SHOP Mon-Fri 9-5 pm Saturday 10-4 pm



THE FIRST OF A NEW SERIES IN WHICH INTERESTING QUESTIONS ARE GIVEN IN-DEPTH ANSWERS.

Dear Ed,

I want to control the volume of my hifi system remotely, and the only way I can think of to do it is to use a motor to turn a pot. There must be another way to do it, because tv remote controllers don't work that way. Can anyone advise me how to tackle this problem?

R.V. Jones, Milton Keynes.

You picked just the right time to ask, as we start this new column of questions and answers.

Probably the lowest distortion means of adjusting gain over a wide range is to do as you suggest, and use a motor to adjust a potentiometer. This is not practical in any

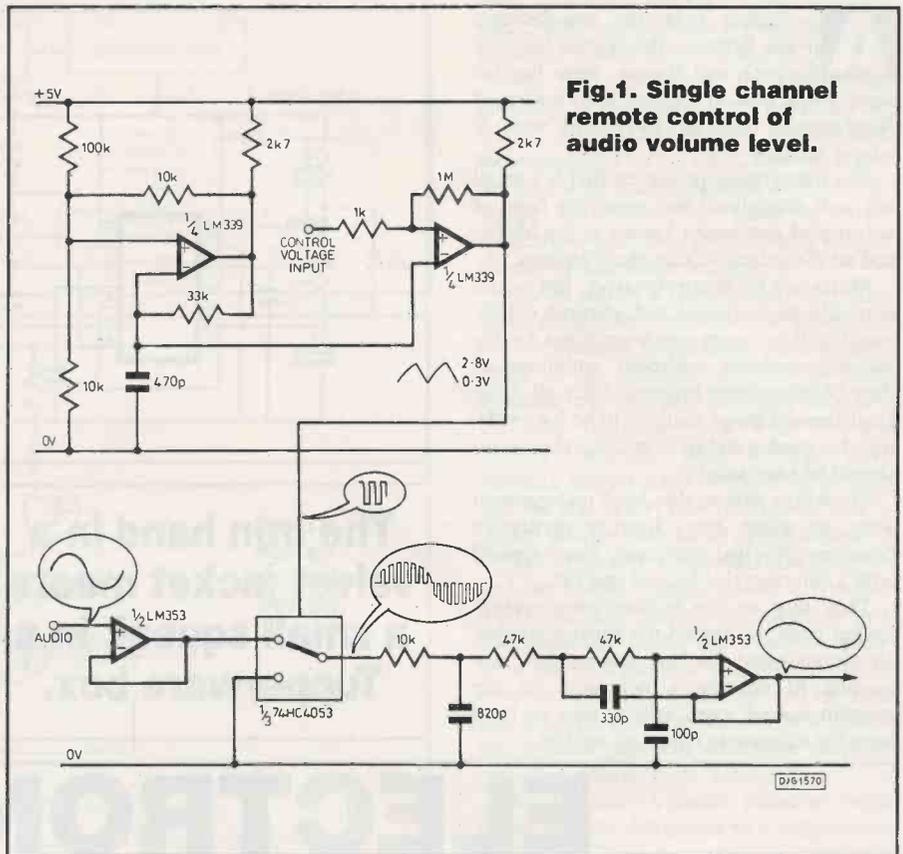


Fig.1. Single channel remote control of audio volume level.

ASK PE

NUMBER ONE WITH ANSWERS BY ANDREW ARMSTRONG

A possible circuit for this is shown below, together with sample waveforms. This circuit has not been prototyped in this form, though I have used the various circuit elements shown in other applications.

The 74HC chip is used because it operates much faster than its 4000 series counterpart. It has provision to be powered from split supplies, and it is powered from $\pm 5V$, with the $-5V$ connected to pin 7. The

LM393 comparator is powered from 0 and $+5V$ to provide a switching signal at normal logic levels.

The switched audio signal is fed to a single RC network followed by an active filter. This restores normal audio shape to the waveform, but at a lower average level. The switching signal can be used to control as many channels as necessary, so the obvious application is to use two of the three parts of the 74HC4053 to provide a stereo volume control. Don't forget to connect the inhibit pin of the 4053 (pin 6) to 0V to enable the chip.

PE

TOMORROW'S SOAP

I for one, have become increasingly disturbed that more programmes of a scientific nature are not shown on tv. Although there are many programmes which the broadcasters may consider to fall into that category, and even though they can be extremely interesting, there are very few which take a more academic look at science and technology. Yes, I know audience ratings have to be considered and that too academic an approach may have limited appeal, but I am sure that there are more viewers who have stronger scientific thirsts for knowledge than broadcasters appear to believe.

BBC's *Tomorrow's World*, which I usually watch, is an example of one programme I feel could be upgraded. The production team work hard; they make the programme interesting, but

why can't they give us more hard scientific facts? And why can't they video-record more of the session to get round demo-malfunxions? The statement, "well, it worked at the rehearsal ...", should now be a thing of the past. At present, malfunxions are frustrating to the viewer, and must be absolutely infuriating to the manufacturer of the demo item. I've also found that following-up on a programme item to obtain more information is not the easiest of procedures.

My ears thus pricked-up when I heard that Paul Bonner, director of programme planning at ITV, had announced that tv would be playing a greater role in scientific education. About time too, I thought. Hopes were dashed, though, when I learned that his statement related to the plan to have scientists on the scriptwriting teams of soap operas, to boost their scientific content! Honestly, isn't it about time we made better use of tv's educational possibilities, especially now we have more channels available?

As distinct from the non-declared peace between the border town of Berwick and Russia, there has for some years now in another rural corner of Northumbria been an unreported state of all-out warfare.

The transgressor in this conflict is a small but well disciplined and tenacious band of velvet-clad gentlemen known as the Moles, and on the defensive side, the Chickens.

Moles are by nature invasive, but would normally be respected and admired cohabitants of the countryside were it not for the recently declared territorial ambitions of their Northumbrian brigade. After all, if an Englishman's home really is to be his castle, then his garden and its horticultural produce should be sacrosanct!

Try telling that to this local underground army, on whom every form of persuasive deterrent ploy had previously been applied with a demonstrable lack of success.

They dug up the bi-directional spring-loaded traps, by-passed the sunken jam-jar, circumnavigated the concrete barriers, and seemed to develop a penchant for the paraffin-soaked earth which was to have been the ultimate in chemical warfare.

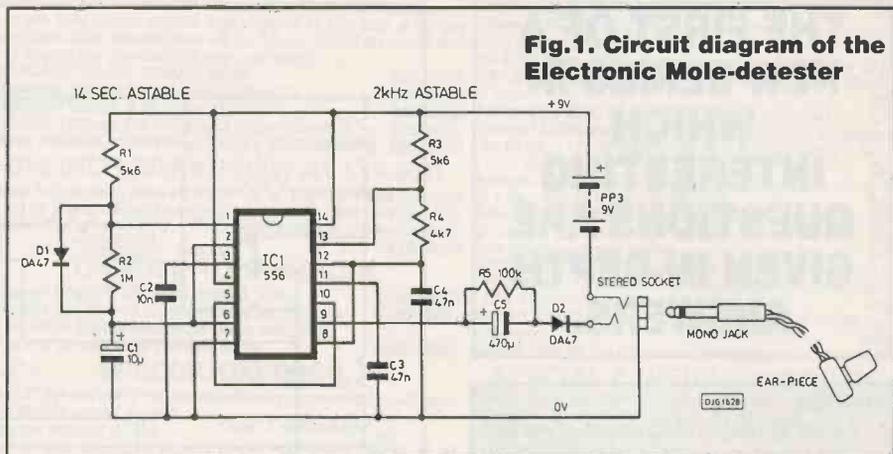


Fig.1. Circuit diagram of the Electronic Mole-detester

The iron hand in a velvet jacket meets a small squeak in a Tupperware box.

THE MOLE-DETESTER

In Fig.1., the first astable oscillates at a very low frequency with a time-period of about 14 seconds, and its output voltage excursions are used to switch on and off the succeeding astable B which oscillates at the higher frequency of 2kHz.

The 2 kHz output signal from astable B is

ELECTRONIC MOLE-DETESTER

Nothing it seemed would deter them in their determination to usurp this particularly well stocked garden – but wait! did not the Royal Air Force succeed in repelling hordes of invading starlings by broadcasting over loudspeakers the alarm-cries of a female starling in distress? and was it not stated in a nature programme on tv that moles were sensitive to noise especially if it be reminiscent of their own natural sound emissions?

Perhaps electronic warfare might succeed where psychological and chemical warfare

BY EDWIN CHICKEN MBE

had failed. The solution was elegant in its simplicity and it has subsequently proved to be a most successful dissuader.

An electronically generated audio-bleeper placed within the main burrow where it crossed the territorial boundary between open countryside and garden, stopped them dead in their tracks, metaphorically speaking of course, and persuaded them to re-orientate their line of advancement.

applied to a miniature sounding-device such as a crystal or electromagnetic earpiece from a transistor radio, to produce a burst of high-pitched sound at intervals of about 14 seconds, which while not very loud to the human ear is totally alien and confusing to the mole in its underworld kingdom.

There is nothing magical or biologically significant about the choice of 14 seconds for the on-off period, it is just an acceptable time-constant which results from the use of standard values of R and C components.

On the other hand, the choice of 2kHz for the bleep noise was adopted after careful consideration of the sounds made by the moles which starred in the tv nature film mentioned earlier.

In the astable multivibrator mode, the voltage at the output pin of a 555 timer circuit switches repetitively between almost 0V and almost full positive line voltage at a time-rate determined by the combination of two resistors and one capacitor, given by:-


$$T_s = 0.7 \times C1 \times (R1 + 2 \times R2) \text{ for Astable A} \\ = 0.7 \times 10 \times 10^{-6} \times (5.6 \times 10^3 + \\ \{2 \times 1.0 \times 10^6\}) \\ = 14 \text{ seconds}$$

and

$$T_s = 0.7 \times C4 \times (R3 + 2 \times R4) \text{ for Astable B} \\ = 0.7 \times 47 \times 10^{-9} \times (5.6 \times 10^3 + \\ \{2 \times 4.7 \times 10^3\}) \\ = 494 \times 10^{-6} \text{ seconds}$$

and since frequency Hz = 1/Time in seconds then:

$$F = 1/(494 \times 10^{-6}) = 2 \text{ kHz approx.}$$

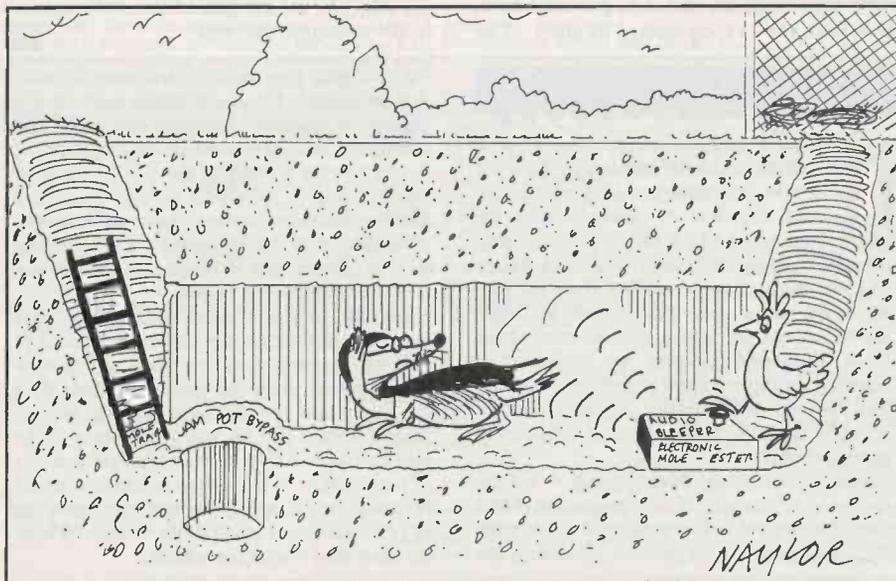

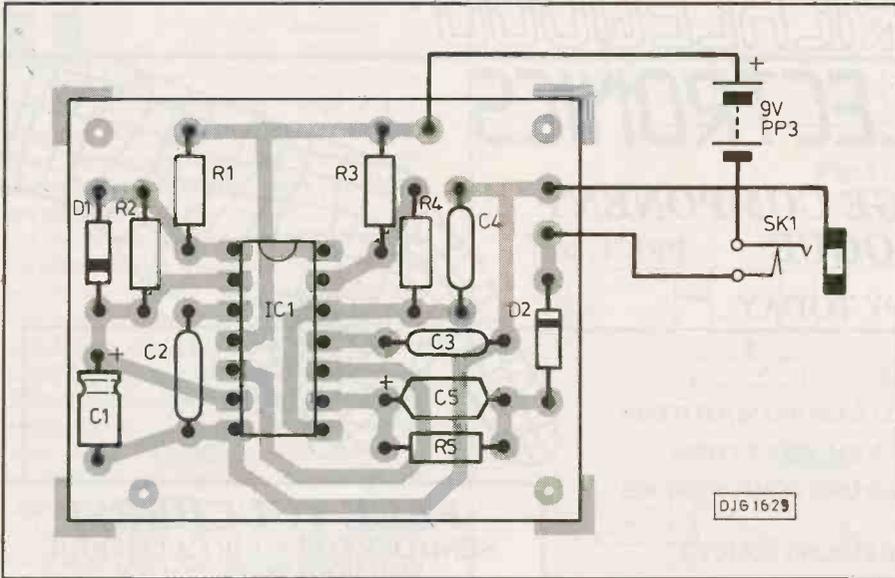


Fig. 2. Component layout on pcb.

Now the 2kHz astable can only oscillate if its Reset pin 10 is connected to the positive supply rail, so by connecting it instead to the output pin 5 of astable A, the 2 kHz oscillation will only occur while the output of the 14sec astable is voltage-HIGH.

Normally, the on/off time ratio (or duty cycle) for this type of astable multivibrator is 50/50, which in this case would mean that the 2 kHz astable would be operative for seven seconds and inoperative for the next seven seconds repetitively.

However, in the interests of battery economy and without detracting in any way from the deterring effect of the Mole-ester, the duty cycle of astable A is modified by the inclusion of D1 connected across the main timing resistor R2.

The result of this is to drastically reduce the on period to about 0.5 second, while retaining the overall 14 second time period, such that a short bleep of 0.5 sec duration is emitted once every 14 seconds.

Battery economy is further enhanced by using the low-power cmos version of the 556 integrated-circuit rather than the standard version. The pin connections are identical, but the difference in current demand is considerable:-

- Standard 556 12mA quiescent, 150mA/0.5sec bleep
- Cmos 556 2mA quiescent, 60mA/0.5sec bleep

At this low current drain even a standard PP3 battery would give considerable service, but better again the high-capacity type, albeit at extra initial financial outlay.

The cost of a battery on/off switch has been avoided by using instead the ear-piece socket, whereby the battery is automatically disconnected when the ear-piece is removed.

Capacitors C2 and C3 while not playing an active role in the astable operation, are necessary to ensure correct functioning of the circuits.

COMPONENTS

Resistors

- R1, R3 5k6
 - R2 1M
 - R4 4k7
 - R5 100k
- 0.25W carbon film 5%

Semiconductors

- IC1 556 Low-power cmos
- D1, D2 OA47 Germanium diodes

Capacitors


- C1 10µ 25V electrolytic
- C2, C3 10n ceramic
- C4 47n ceramic
- C5 470µ 25V electrolytic

Miscellaneous

- 3.5mm min stereo chassis-socket.
- PP3 Battery and twin miniature press-stud.
- Earpiece or crystal microphone insert.

Capacitor C5 and diode D2 at the output of the 2kHz multivibrator are only necessary if the chosen sounder is of the electro-magnetic type. C7 blocks the flow of dc current into the sounder device so

Fig. 3. Lifesize pcb foil pattern.

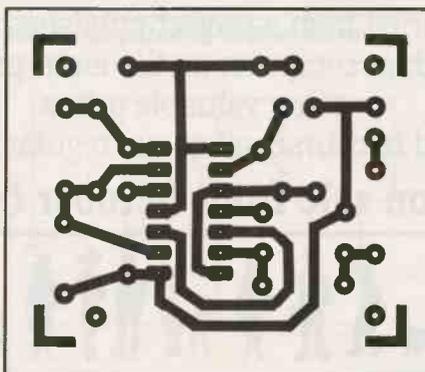

enabling it to perform correctly, and D2 prevents the astable from latching into a permanent oscillatory condition which can sometimes occur as a result of back-emf when driving an inductive load such as this.

C5, D2 and R5 can be omitted if a crystal-sounder is used.

The latter can be either a crystal ear-piece, or the insert from a crystal microphone, both of which are readily available at very low cost and are equally effective.

Resistor R5 which is shown connected across the output capacitor C5 was found by experiment to produce an intriguing *chirp* on the 2 kHz bleep, but only with cmos 556 chips, and then not with all of them. It may be omitted without adverse effect.

CONSTRUCTION

For simplicity and speed of construction, the components may be hard-wired onto a 25x30mm piece of copper strip-board 0.1 inch hole-spacing. Alternatively, a pcb may be used as shown in Fig. 2.

Connection to the PP3 battery is by a twin miniature press-stud with integral wire leads. The red lead is the positive supply which is to be soldered directly to the circuit, and black is negative which connects to the circuit via the sounder-socket.

A 3.5mm miniature chassis-mounting stereo-socket is used to feed the standard mono earpiece, while also acting as the battery isolating switch for the negative supply lead. The related contacts close when the sounder-jack is plugged into the socket, so connecting the battery negative to the circuit.

If a crystal-microphone insert is used as the sounder, its connecting lead should be made about 750mm long, and terminated with a 3.5mm miniature mono jack. The cable need not be of the screened type.

No adjustments are needed as the circuit is self-starting and reliable, but if for experimental reasons a continuously sounding output signal is required, this can be obtained by temporarily connecting pin 10 to the positive supply.

In practice, it was found best to contain the circuit and its PP3 battery within a small plastic container with snap-on lid, with the sounder-socket mounted on the lid, leaving the sounder with its cable external to the container, such that it could be readily lowered into the mole-run.

If however it is found to be more convenient or effective to place the complete assembly in the burrow, then the container must be of diameter no greater than 40mm, which is about the size of the average mole-tunnel.

A search of the kitchen cupboards should produce a suitable container and also some thin plastic food-bags to act as weather-protection for the container and earpiece-sounder.

**OUT
NOW!**

CRICKLEWOOD

ELECTRONICS


1989 100 PAGE COMPONENT CATALOGUE PRICE £1

SEND OFF FOR YOUR COPY TODAY...

- WE STOCK AN UNRIVALLED RANGE
- ALL OUR COMPONENTS ARE FIRST CLASS BRANDED ITEMS
- WE OFFER A SAME DAY SERVICE ON ALL STOCK ITEMS
- NO MINIMUM ORDER—IF YOU NEED ONE COMPONENT WE CAN SUPPLY ONE COMPONENT
- WE HAVE ADOPTED A NEW LOWER PRICING POLICY + QUANTITY DISCOUNTS
- FREE VOUCHERS WITH YOUR CATALOGUE—ORDER ONE NOW!..

JUST FILL IN THE COUPON OPPOSITE AND POST IT WITH YOUR £1 PAYMENT TO THE ADDRESS BELOW. YOU WILL RECEIVE NOT ONLY OUR SUPERB 100 PAGE CATALOGUE, BUT ALSO FREE VOUCHERS WHICH YOU CAN USE ON YOUR NEXT COMPONENTS ORDER.

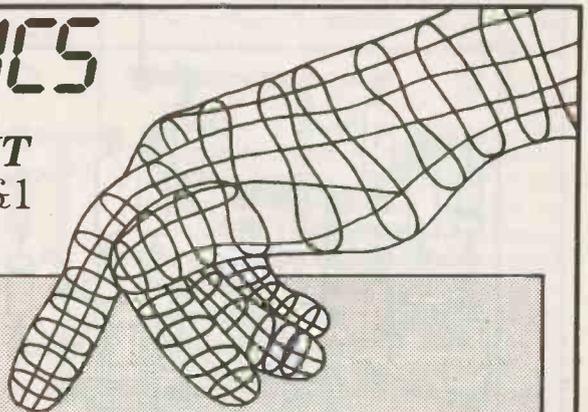CRICKLEWOOD ELECTRONICS LTD 40 CRICKLEWOOD BROADWAY LONDON
NW2 3ET TEL: 01-450 0985/452 0161 FAX: 01-208 1441 TELEX: 914977



FREE VOUCHERS!

SEND OFF FOR YOUR CATALOGUE
AND VOUCHERS TODAY.

I WOULD LIKE TO RECEIVE.....
COPY(COPIES) OF THE 1989
CRICKLEWOOD ELECTRONICS
COMPONENT CATALOGUE. I
ENCLOSE £.....
PLEASE ENCLOSE MY FREE
VOUCHERS.

Tape your £1 coin
here, or send a
cheque or postal
order for £1.00 for
every catalogue you
require.

NAME.....

ADDRESS.....




Worth waiting for!


Practical Electronics 25th Anniversary Issue

In this issue:

- 80 page bumper issue (16 more pages than usual)
- Results of the PE 25th Anniversary Technology Award Poll
- An exclusive interview with the Poll winner (a well known personality)
- A retrospective look at the last 25 years of Practical Electronics
- A historic look at the developments in electronics and technology
 - The future of electronics and technology by Barry Fox
 - The story of a person whose multi-million pound business started from a project published in PE
- An exciting competition with a computer as the main prize plus 25-year subs to PE and other valuable prizes
 - And of course, all of our regular features

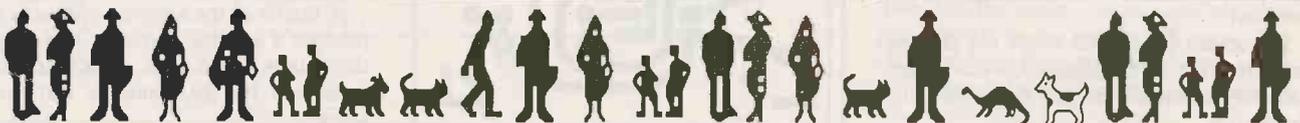The November issue - on sale from October 6th -Price still only £1-25



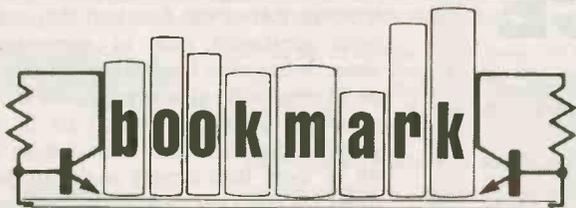

Your Ed looks at some of the new books recently received.

Master Handbook of 1001 Practical Electronics Circuits.

Edited by K.W.Sessions. Tab Books. £15.60. ISBN 0-8306-2980-7. In nearly 400 pages this book has nearly enough information to merit the title of encyclopaedia. The 1001 tested and proven circuits cover an enormous range of applications - alarms, audio, automotive, filter, logic, clocks, psus, radio, test and many more. The intention of the book is to minimise the time you need to spend searching for a circuit to use as part of a particular project. It is well categorised and indexed, and the circuit diagrams give examples of typical component values. Detailed descriptions of the circuits are not given, but those whose abilities have reached as far as the need for a book of this nature should usually have no difficulty in using the circuits. An extremely valuable source of information, and worth its list price.

All-Time Favourite Electronic Projects. Delton T.Horn. Tab Books. £5.25. ISBN 0-8306-3105-4. This is a useful little 100 page book that should find favour with readers who are beyond the early-starter stage. It is in two parts, one of projects for the home, the other for workshop items. The subjects covered include: intercom, car alarm, motor controller, digital clock, am/fm radio, audio and power amps, tape player amp, tone controls, constant current/voltage, d-a converter, logic probe, digital capacitance and frequency meters, multi-output psu, and dc voltmeter. There are good instructions and drawings, a little bit of maths in a place or two, and tabulated parts lists. All the parts appear to be readily available in the UK. I agree with the publisher's statement that the book should "provide many hours of fun, challenging, hands-on electronics experience".

A Concise Introduction to UNIX. N.Kantaros. Babani BP259. £2.95. ISBN 0-85934-202-2. Note should be taken of the word "concise" in the title. If you keep this in mind you will not be disappointed that the book does not take an in-depth look at the UNIX operating system commands. As yet I have no experience of UNIX, and I am not sure that I could get a firm grip on it from this information. However, the book states that it is written for the non-expert, busy person and, as such, it has an underlying structure based on "what you need to know first, appears first". It explains the structure of the UNIX operating system, how its directories can be employed, how to use the file commands, how to get the editor to write programs for various compilers, and how to use other important functions. The book will probably serve its purpose as an introduction to UNIX, and be a useful memory-jogging guide once you know the system.

Encyclopaedia of Electronic Circuits - Volume Two. Rudolf F. Graf. Tab Books. £23.40. ISBN 0-8306-3138-0. Ah! You'll love this book if you find pleasure from building circuits. Considering what it offers the price of this book is very low. With over 700 pages it is truly a giant of a book containing more than 700 electronic circuits - enough to make all but the most lethargic constructor switch on the soldering iron. There is no way I can list here the circuits or even their main subject headings, which range from alarms to touch switch circuits. The book is a companion to Volume One published in 1985. What a shame I don't have that volume as well. Definitely a book for the workshop library.

Digital Logic Gates and Flip-Flops. Ian R. Sinclair. PC Publishing. £8.95. ISBN 1-870775-06-6. Thank you PCP and Ian Sinclair for producing a book that intelligently looks at the basic building blocks of all digital circuits. (I have lately been inundated by books from America which have had several chapters on Logic as their standard beginnings. With many of those books I was left with the feeling that the chapters were there just to fill up space.) This (English) book is intended for enthusiasts, students and technicians who seek to establish a firm grasp of the fundamentals of digital electronics. It is not a book of self-contained constructional projects, but it will certainly assist those who wish to increase their knowledge of logic theory and to design their own digital circuits. I recommend this book as an adjunct to and extension of our own Digital Electronics series.


Babani Publishing Ltd., The Grampians, Shepherds Bush Road, London W6 7NF.

PC Publishing, 4 Brook Street, Tonbridge, Kent, TN9 2PJ.

Tab Books are imported by John Wiley and Sons Ltd, Baffins Lane, Chichester, W.Sussex, PO10 1UD. 0243 779777.

Z80A MICROCONTROLLER

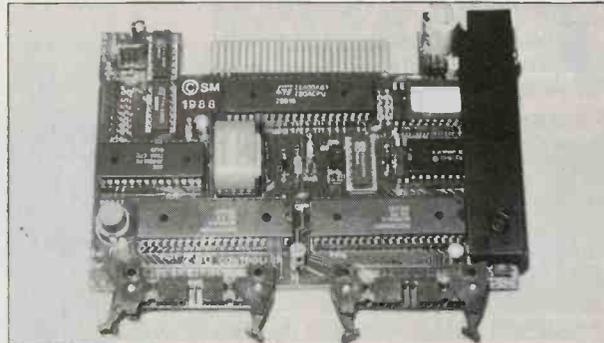A low cost single board micro-system providing all the requirements needed for many applications in industrial, experimental and educational fields.



Just some of its extensive features include:

- ★ Z80A CPU operating at 4MHz
- ★ EPROM socket - jumper link selectable as 2, 4, 8, 16 or 32K accepts 2716/2732/2764/27128/27256 EPROMS
- ★ RAM socket - jumper link selectable as 2, 8 or 32K accepts 6116/6264/62256 CMOS static RAMS - battery back up included
- ★ INPUT/OUTPUT - 2 Z80 PIOs providing 32 programmable I/O lines
- ★ HARDWARE COUNTER/TIMER - a Z80 CTC providing four independent counter/timer circuits
- ★ Expansion boards available - DtoA, 8 channel AtoD, RS232 serial I/O etc
- ★ Full documentation and user notes

Z80 Single Board Controller fitted with 2Kx8 CMOS static RAM ONLY £94.95 + VAT - BUILT AND TESTED !!

Specialising in microprocessor data logging and control applications, we provide a complete service covering any or all of the stages from initial hardware and software design through manufacture to final installation.

Phone/send for full details - OEM, trade and overseas enquiries welcome

SM ENGINEERING
Telephone 0323-766262

'St. Georges' Lion Hill Stone Cross
Pevensey, East Sussex BN24 5ED

TRAINING

HNC in Microprocessor Systems

A one year full time course, commencing on 4th September 1989, is offered by Milton Keynes Skillcentre.

The course includes 20 weeks work placement in Industry. This is a Training Agency funded equal opportunity course and training allowances will be paid.

Please phone 0908 670001 for an application form or write to:
Milton Keynes Skillcentre,
Chesney Wold,
Bleak Hall,
Milton Keynes,
MK6 1LX



Skills Training Agency

BINDERS for Sale!

Back copies of Practical Electronics are a valuable source of High-Tech information!

Keep them safe in a sturdy, red, gold-embossed binder, which costs only £5-95!

Send your cheque, P.O. or payment by Visa or Access to: Intra Press (PE Binders), Intra House, 193 Uxbridge Road, London W12 9RA



AUGUST 1989: NEPTUNE MONTH


Twenty years ago we were still marvelling at the first successful manned flight to the Moon. Now, we await the end of the first phase of our exploration of the Solar System: the pass of Neptune by Voyager 2, which was launched in 1977 and has therefore been travelling in space for a dozen years.

In fact, the first successful interplanetary probe was Mariner 2, which made its rendezvous with Venus in 1962; but by cosmical standards Venus is a very near neighbour, and when travelling to the outer parts of the Solar System all the so-called "minor" problems become anything but minor. For example, one cannot use solar power to generate energy, because there is not enough sunlight, and a deep-space probe has to carry what is to all intents and purposes a small nuclear power-plant. The distances, too, are immense. Neptune moves round the Sun at a mean distance of over 2,790,000,000 miles – and takes almost 165 years to complete one orbit.

At the time when I write these words, Voyager 2 is on course and in full operation. It has already passed by Jupiter (1979), Saturn (1981) and Uranus (1986), and is working as well as ever. So what can it be expected to tell us about Neptune?

Neptune, remember, is a giant planet, with a diameter of just over 30,000 miles. It is slightly smaller than Uranus, but appreciably more massive. Of course its surface is gaseous; but it and Uranus, as a pair, differ markedly from the

SPACE

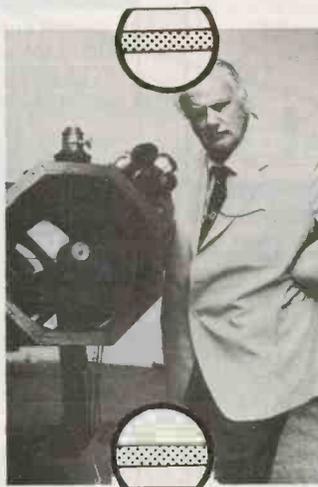

WATCH

BY DR PATRICK MOORE CBE

What mysteries will be revealed and what new questions raised when Voyager 2 passes Neptune and the first phase of Solar System exploration ends?

Jupiter/Saturn pair. Their composition is less like that of the Sun, and they contain more substances such as ammonia and water. It has even been suggested that they are in some ways akin to giant comets!

Uranus shows little detail on its pale, greenish disk, and the planet has an axial tilt of more than a right angle, so that at times (as now) one pole is directed toward the Sun and the Earth. There seems to be no major internal heat-source. Neptune differs from its "twin" in several important respects. It is bluish rather than green, and even from Earth some cloudlike features can be made out; as Voyager 2 approaches, these patches show up well, so that as long ago as last spring Neptune was displaying much more detail than Uranus had done from much closer range. Neptune does not share Uranus' strange inclination; the angle is less than 30 degrees – not so very different from that of the Earth. And like Jupiter and Saturn, but unlike Uranus, Neptune has a strong source of internal heat.

What about a magnetic field? All the giants have strong fields, and there is no reason to believe that Neptune will be the exception. Indeed, the field may be expected to be considerably stronger than that of Uranus. Presumably the inner satellite, Triton, remains immersed in the Neptunian magnetosphere. There will also probably be radiation zones, of the same basic type as our own Van Allen Zones but probably more marked.

The possibility of a ring-system has been widely discussed. Saturn's glorious system is unique; Jupiter has a thin, dark ring, and Uranus has revealed a set of rings which are also thin and dark, but contain large

THE SKY THIS MONTH

The early part of the evening is dominated this month by Venus, which is brilliant in the west after sunset. The phase is over 80 per cent at the beginning of August and still well over 75 per cent at the end, so that the planet shows up as a gibbous disk; do not expect to see any markings, even with a telescope. However, we know more about Venus than we had dared to hope a few years ago, and the latest probe, America's Magellan, is now on its way there, though it is going by a somewhat roundabout route and will not arrive at the neighbourhood of Venus until this time next year.

Mercury and Mars are close together in early August, and both are theoretically evening objects, but their elongation from the Sun is only about 20 degrees, and they will be hard to locate in the bright sky. Jupiter, in Gemini, is brilliant in the morning sky; Saturn, which passed opposition on 2 July, is visible for most of the hours of darkness, but is inconveniently low in Sagittarius. Saturn's senior satellite, Titan, is at eastern elongation on August 5 and 21, and at western elongation on August 13 and 29. A small telescope will show it, and it has been reported that keen-eyed people can glimpse it with good binoculars.

The Moon is new on the 1st and 31st, and full on the 17th. Unfortunately, moonlight will be obtrusive around August 12, which is the maximum of the annual Perseid meteor shower;

however, a good number of Perseids should be seen all through the first two and a half weeks of the month – this is a very reliable shower. The associated comet, Swift-Tuttle, has not put in an appearance (it was last seen in 1862), and if its period is indeed around 120 years, as is the official view, it may have returned unseen some time ago.


This month we had expected that another periodical comet, Brorsen-Metcalf, would be reaching naked-eye visibility, but it has failed to come up to expectations. By the law of averages, we are surely overdue for a brilliant comet!

The "summer triangle" of Vega, Altair and Deneb remains very prominent; Vega is near the zenith or overhead point, and is recognisable both because of its brilliance and because of its decidedly blue colour. Ursa Major, the Great Bear, is low in the north-west; the W of Cassiopeia, on the other side of the Pole Star, is high in the north-east. Very low in the south look for the glorious star-clouds of Sagittarius, which hide our view of the centre of the Galaxy. Sagittarius itself has no particular shape, but at the moment it is particularly easy to locate because of the presence of Saturn, which is much brighter than any star in the neighbourhood. In the east, the Square of Pegasus is coming into view, and will be very prominent all through the late summer and the whole of the autumn.

quantities of "dust". Normally it would be illogical to assume that Neptune, alone of the giants, is ringless; but the situation is complicated by the presence of a very large satellite, Triton, which is close to Neptune and has retrograde motion. In this Triton too is unique. All other known retrograde satellites are small and presumably asteroidal, but Triton is at least comparable with our Moon, and it has a powerful pull of gravity. Since it moves in a sense opposite to that in which Neptune spins, the conditions may be rather unstable. I have predicted that there will be no continuous ring-system; in a few weeks from now I will know whether I have been right or wrong. Ring-arcs are also possibilities, but again I admit to being somewhat sceptical.

Triton has probably a considerable atmosphere. What the surface conditions are like remains to be seen – we do not even know whether the atmosphere is as opaque as Titan's. The other known satellite, Nereid, is small and has a curious, cometary-shaped orbit; unfortunately Voyager will not make a close approach to it, but at least we ought to be able to tell whether or not it is icy and cratered.

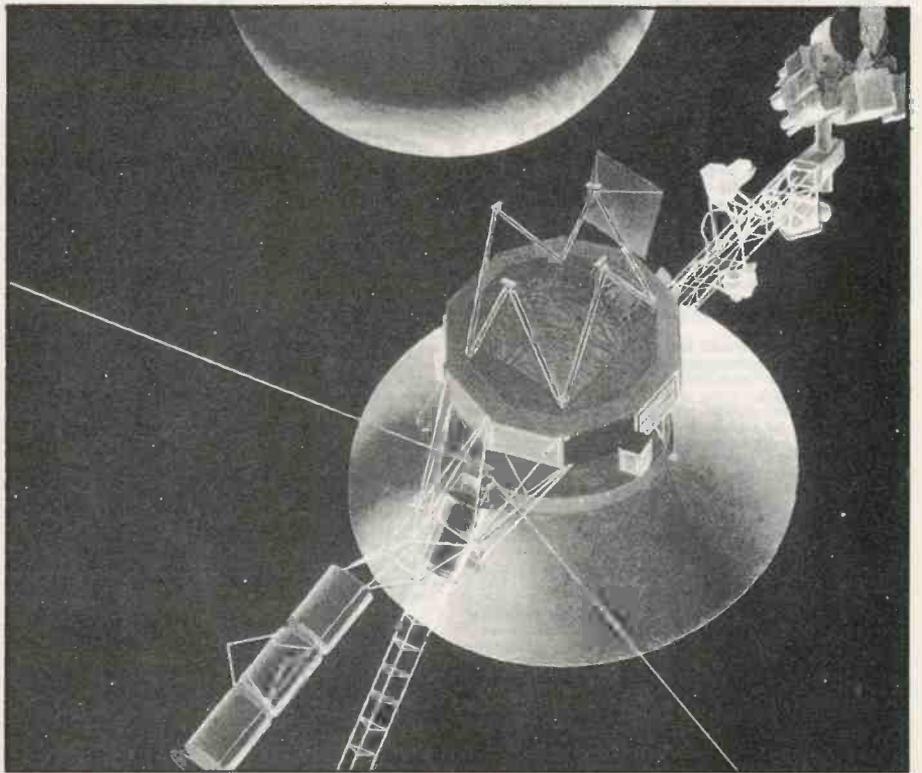The Voyagers have discovered extra satellites of all the three inner giants, and possibly some new Neptunian satellites will be detected – they may already have been found by the time you read these words. In any case, it is more than likely that Neptune



will provide its quota of surprises. By the next issue of PE, we should know a great deal more than we do now.

Let us hope that Voyager 2 functions perfectly. If not, then we may have to wait

many years before we can improve our knowledge of the outermost giant planet

The illustration of Voyager 2 is reproduced by courtesy of Astronomy Now and NASA JPL.

PE

Do not miss a single issue of

Astronomy Now

Britain's leading astronomical magazine

Edited by well known astronomer and regular contributor to *Practical Electronics*
Dr. Patrick Moore CBE

Place a regular order with your newsagent or for £15-00 (overseas £18-00) take out an annual subscription from Intra Press, Intra House, 193 Uxbridge Road, London W12 9RA



TUTORKIT

MICROELECTRONICS TUTORS



Logic Tutors
OP Amp Tutors
I.C. Patchboards
GCSE Units
Computer Interfaces

Prices from

£27.50
PLUS VAT

Including instruction manual and patch leads

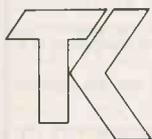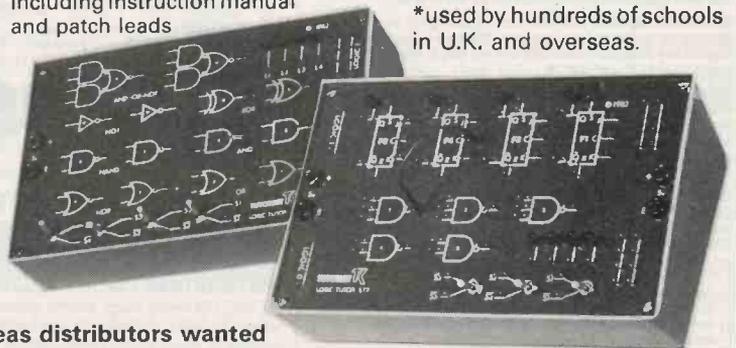*used by hundreds of schools in U.K. and overseas.



TUTORKIT PRODUCTS
(Div of Limrose Electronics Ltd)
Llay Industrial Estate
Wrexham, Clwyd, U.K.
LL12 0TU. Tel 097 883 2285

Overseas distributors wanted



No. 1 LIST BAKERS DOZEN PACKS

All packs are £1 each, if you order 12 then you are entitled to another free. Please state which one you want. Note the figure on the extreme left of the pack ref number and the next figure is the quantity of items in the pack, finally a short description.

- BD2 5 13A spurs provide a fused outlet to a ring main where devices such as a clock must not be switched off.
- BD7 4 In flex switches with neon on/off lights, saves making things switched on.
- BD9 2 6V 1A mains transformers upright mounting with fixing clamps.
- BD11 1 6 1/2in speaker cabinet ideal for extensions, takes our speaker. Ref BD137.
- BD13 12 30 watt reed switches, it's surprising what you can make with these - burglar alarms, secret switches, relay, etc., etc.
- BD22 2 25 watt loud speaker two unit cross-overs.
- BD29 1 B.O.A.C. stereo unit is wonderful breakdown value.
- BD30 2 Nicad constant current chargers adapt to charge almost any nicad battery.
- BD32 2 Humidity switches, as the air becomes damper the membrane stretches and operates a microswitch.
- BD42 5 13A rocker switch three tags so on/off, or change over with centre off.
- BD45 1 24hr time switch, ex-Electricity Board, automatically adjust for lengthening and shortening day original cost £40 each.
- BD49 10 Neon valves, with series resistor, these make good night lights.
- BD56 1 Mini uniselector, one use is for an electric jigsaw puzzle, we give circuit diagram for this. One pulse into motor, moves switch through one pole.
- BD59 2 Flat solenoids - you could make your multi-tester read AC amps with this.
- BD67 1 Suck or blow operated pressure switch, or it can be operated by any low pressure variation such as water level in water tanks.
- BD91 1 Mains operated motors with gearbox. Final speed 16 rpm, 2 watt rated.
- BD103A 1 6V 750mA power supply, nicely cased with mains input and 6V output leads.
- BD120 2 Stripper boards, each contains a 400V 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of condensers, etc.
- BD128 10 Very fine drills for pcb boards etc. Normal cost about 80p each.
- BD132 2 Plastic boxes approx 3in cube with square hole through top so ideal for interrupted beam switch.
- BD134 1 Motors for model aeroplanes, spin to start so needs no switch.
- BD139 6 Microphone inserts - magnetic 400 ohm also act as speakers.
- BD148 4 Reed relay kits, you get 16 reed switches and 4 coil sets with notes on making c/o relays and other gadgets.
- BD149 6 Safety cover for 13A sockets - prevent those inquisitive little fingers getting nasty shocks.
- BD180 6 Neon indicators in panel mounting holders with lens.
- BD193 6 5 amp 3 pin flush mounting sockets make a low cost disco panel. Need cable clips.
- BD196 1 in flex simmerstat - keeps your soldering iron etc. always at the ready.
- BD199 1 Mains solenoid, very powerful, has 1in pull or could push if modified.
- BD201 8 Keyboard switches - made for computers but have many other applications.
- BD211 1 Electric clock mains operated, put this in a box and you need never be late.
- BD221 5 12V alarms, make a noise about as loud as a car horn. Slightly soiled but OK.
- BD242 2 6in x 4in speakers, 4 ohm made from Radiomobile so very good quality.
- BD252 1 Panostat, controls output of boiling ring from simmer to boil.
- BD259 50 Leads with push-on 1/4in tags - a must for hook-ups - mains connections etc.
- BD263 2 Oblong push switches for bell or chimes, these can mains up to 5 amps so could be foot switch if fitted into pattern.
- BD268 1 Mini 1 watt amp for record player. Will also change speed of record player motor.
- BD275 1 Guitar mic - clip-on type suits most amps.
- BD283 3 Mild steel boxes approx 3in x 3in x 1in deep - standard electrical.
- BD293 50 Mixed silicon diodes.
- BD305 1 Tubular dynamic mic with optional table rest.
- BD400 4 Books, useful for beginners, describes amplifiers, equipment and kit sets.
- BD653 2 Miniature driver transformers. Ref. LT44. 20k to 1k centre tapped.
- BD553a 2 3.5V relays each with 2 pairs changeover contacts.

Most other packs still available and you can choose any as your free one.

CAMERAS. Three cameras, all by famous makers, Kodak, etc. One disc, one 35mm and one instamatic. All in first class condition, believed to be in perfect working order, but sold as untested. You can have the three for £10 including VAT, which must be a bargain - if only for the lenses, flash gear, etc. Our ref 10P58.

675VOLT MAINS TRANSFORMER PCB MOUNTING. 20va. A very well made (British) transformer. Ideal for laser power supply, etc. Price £4. Our ref 4P38.

PRETTY CASSETTE PLAYER In handy carrying pouch with silk type shoulder cord. Ideal present for young girl. New, tested and in perfect order. Just needs headphones and batteries. Price £4. Our ref 4P35.

EXTRA SPECIAL CROC CLIPS Medium size, just right for most hook-ups. Normally sell for around 10p to 15p each. These are insulated and have a length of wire connected to them but this is very easy to snip off if you do not need it. 20 for £1. Our ref BD117A.

IONISER FOR YOUR CAR Experts say that positive ions predominate in a car and can cause you to feel sleepy so we now offer a car ioniser to counteract this. It plugs into the cigarette lighter socket. Price £12 for the complete kit. Our ref 12P8. Our famous transformer operated room ioniser is still available at £12.50. We claim this to have ten times over output of ions than the ETI, the Equaliser and in fact most other popular kits and ready built ionisers.

COPPER CLAD PANEL for making PCB. Size approx 12in long x 8 1/2in wide. Double-sided on fibreglass middle which is quite thick (about 1/8in) so this would support quite heavy components and could even form a chassis to hold a mains transformer, etc. Price £1 each. Our ref BD683.

POWERFUL IONISER

Generates approx 10 times more IONS than the ETI and similar circuits. Will refresh your home, office, workroom, etc. Makes you feel better and work harder - a complete mains operated kit, case included. £12.50 plus £2 postage. Our ref 12P5/1.

MODERN TELEPHONES Two-piece push-button desk or wall mounting telephone. Fitted with standard BT flat plug for immediate use. Standard model £8. Our ref 8P31. Or similar but with 10 memory feature £10. Our ref 10P68. If not collecting add £2 for special packing.



ELECTRONIC SPACESHIP Sound and impact controlled, responds to claps and shouts and reverses when it hits anything. Kit with really detailed instructions. Ideal present for budding young electrician. A youngster should be able to assemble but you may have to help with the soldering of the components on the pcb. Complete kit £8. Our ref 8P30.

DATA RECORDER FOR COMPUTERS For playing games or listening to music cassettes. It has a built-in condenser microphone and loud speaker (muted if you use the extension socket). Has the following controls: pause, stop/eject, fast forward, rewind, play and record. Also has built-in tape counter, extension headphone and microphone socket and volume control. Built-in power supply enables it to run from the mains but provision also for battery operation. In 'as new' order condition, but customer reviews so may have fault. Price only £10 and if you order 4 you get a fifth one free. Our ref 10P65.

BUSH RADIO MIDI SPEAKERS Stereo pair, BASS reflex system, using a full range 4in driver of 4ohms impedance. Mounted in very nicely made black fronted walnut finish cabinets. Cabinet size approx 8 1/2in wide, 14in high and 3 1/2in deep. Fitted with a good length of speaker flex and terminating with a normal audio plug. Price £5 the pair plus £1 post. Our ref 5P141.

3 1/2 FLOPPY DISC DRIVE - DOUBLE SIDED, DOUBLE DENSITY, 80 TRACK Shugart compatible, has 34 way IDC connect and will interface with almost any computer. Made by the famous Japanese NEC Company. Price £59.50 plus £3 insured post.



ATARI 65XE COMPUTER

At 64k this is most powerful and suitable for home and business. Brand new, complete with PSU, TV lead, owner's manual and six games. Can be yours for only £45 plus £3 insured delivery.

65XE COMPENDIUM Contains: 65XE Computer, its data recorder XC12 and its joystick, with ten games for £62.50 plus £4 insured delivery.

AGAIN AVAILABLE: ASTEC PSU Mains operated switch mode, so very compact. Outputs: +12V 2.5A, +5V 6A, ±5V 5A, ±12V 5A. Size: 7 1/4 long x 4 1/8 wide x 2 3/4 high. Cased ready for use. Brand new. Normal price £30+, our price only £10. Our ref 10P34.

VERY POWERFUL 12 VOLT MOTORS. 1/3rd Horsepower. Made to drive the Sinclair C5 electric car but adaptable to power a go-kart, a mower, a rail car, model railway, etc. Brand new. Price £20 plus £2 postage. Our ref 20P22.

PHILIPS LASER

This is helium-neon and has a power rating of 2mW. Completely safe as long as you do not look directly into the beam when eye damage could result. Brand new, full spec. £30 plus £3 insured delivery. Mains operated power supply for this tube gives 1kv striking and 1.25kv at 5mA running. Complete kit with case £15. Ditto for 12v battery. Also £15. Our ref 15P22.

ORGAN MASTER Is there a three octave musical keyboard. It is beautifully made, has full size (piano size) keys, has gold plated contacts and is complete with ribbon cable and edge connector. Can be used with many computers. We can supply information sheet. Brand new, only £15 plus £3 postage. Our ref 15P15.

FULL RANGE OF COMPONENTS at very keen prices are available from our associate company SCS COMPONENTS. You may already have their catalogue, if not request one and we will send it FOC with your goods.

HAND-HELD VIDEO LAMP. Mains operated and will enable you to take professional standard videos. Made by the famous Ferguson Company, this uses a 1000w halogen lamp in a fan cooled, hand-held and hand switched metal housing. Comes complete with option of barn-door assembly and camera bar. Obviously intended to retail at over £60, we offer these as £30 each plus £3 insured delivery. Our ref 30P3.

HIGH RESOLUTION MONITOR. In black and white, used Philips tube M24/305W. Made up in a lacquered frame and has open sides. Made for use with OPD computer but suitable for most others. 5 and new. £16 plus £5 post. Our ref 16P1.


12 VOLT BRUSHLESS FAN. Japanese made. The popular square shape 1 1/2 x 4 1/2 x 1 7/8in. The electronically run fuse not only consume very little current but also they do not cause interference as the brush type motors do. Ideal for cooling computers, etc. or for a speaker. £8 each. Our ref 8P28.

MONO RADIO CASSETTE RECORDER AM/FM with all the normal controls. In 'as new' condition but customer returns or shop rejects, so may need attention. Price £10. Order 5 of these and get a sixth one free. Our ref 10P66.

FDD BARGAIN

3 1/2in made by Chicon of Japan. Single sided, 80 track, Shugart compatible interface, interchangeable with most other 3 1/2in and 5 1/4in drives. Completely cased with 4 pin power lead and 34 pin computer lead £40. Plus £3 ins del. Our ref 40P1.

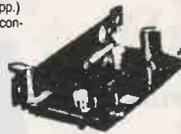MINI MONO AMP on p.c.b. size 4" x 2" (app.) Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 13 for £12.00.



J & N BULL ELECTRICAL

Dept PE, 250 PORTLAND ROAD, HOVE
BRIGHTON, SUSSEX BN3 5QT

MAIL ORDER TERMS: Cash, PO or cheque with order. Orders under £20 add £1.50 service charge. Monthly account orders accepted from schools and public companies. Access and B/card orders accepted minimum £5. Phone (0273) 734648 or 203500.

MOSFETS FOR POWER AMPLIFIERS AND HIGH CURRENT DEVICES 140v 100w pair made by the famous Hitachi Company. Reference 25K413 and its complement 25J118. Only £4 the pair. Our ref 4P42.

HI-VOLT CAPS Not ceramic but the much more reliable foil type. Good range from 1nf to 35uf at voltages 1kv to 2.5kv. Keen prices, good quantity discounts. Request list.

AGAIN AVAILABLE - THE SOLID STATE RELAY Will switch up to 10A AC load and can be triggered by very small current from photo cell, computer, etc. £2 each. Our ref 2P183.

BATTERY OPERATED TRAVEL MECHANISM On a plastic panel measuring approx 9in x 3 1/2in. Is driven by a reversible 12v battery motor, fitted with pulley and belt which rotates a threaded rod and causes a platform to travel backwards and forwards through a distance of approx 5in. Price £5. Our ref 5P140.

MAINS OPERATED WATER VALVE with hose connection for inlet and outlet suitable for low pressure. Auto plant watering, etc. Only £1 each. Our ref BD370.

20 VOLT 4 AMP MAINS TRANSFORMER Upright mounting with fixing feet. Price £3. Our ref 3P59.

12 VOLT SOLENOID Has good 1/2in pull or could be made to push if fitted with a rod. Approx 1 1/2in long by 1in square. Price £1. Our ref BD232A.

160HM PM SPEAKERS Approx 7in x 4in. 5 watts. Offered at a very low price so you can use two in parallel to give you 10 watts at 8 ohms. £1 for the two. Our ref BD684.

EHT TRANSFORMER 4kv 2mA Ex-unused equipment. £5. Our ref 5P139.

4 CORE TINSEL COPPER LEAD As fitted to telephones, terminating with flat BT plug. 2 for £1. Our ref BD639.

EHT TRANSFORMER 8kv 3mA. £10. Our ref 10P56.

DOUBLE MICRODRIVES We are pleased to advise you that the Double Microdrives which we were offering at about this time last year as being for the 'QL', 'OPD' and several other computers are again available, same price as before namely £5. Our ref 5P113.

VERY USEFUL MAGNETS Flat, about 1in long, 1/2in wide and 1/4in thick. Very powerful. 6 for £1. Our ref BD274(a).

ACORN COMPUTER DATA RECORDER REF ALF03 Made for the Electron or BBC computers but suitable for most others. Complete with mains adaptor, leads and handbook. £10.00. £2 special packing. Ref 10P44.

SOLAR CELLS Will give a good current (depending on size) from sunlight or bright daylight. Module A gives 100mA. Price £1. Our ref BD631. Module C gives 400mA. Price £2. Our ref 2P199. Module D gives 700mA. Price £3. Our ref 3P42.

SOLAR POWERED NI-CAD RECHARGER 4 Ni-Cad batteries AA (HP7) charged in eight hours or two in only 4 hours. It is a complete, boxed ready to use unit. Price £6. Our ref 6P3.

METAL PROJECT BOX Ideal size for battery charger, power supply, etc.; sprayed grey, size 8in x 4 1/4in high, ends are louvred for ventilation other sides are flat and undrilled. Order Ref. 2P191. Price £1.

4-CORE FLEX CABLE. Cores separately insulated and grey PVC covered overall. Each copper core size 7/0.2mm. Ideal for long telephone runs or similar applications even at mains voltage. 20 metres £2. Our ref 2P196 or 100 metres coil £8. Order ref 8P19.

6-CORE FLEX CABLE. Description same as the 4-core above. Price 15 metres for £2. Our ref 2P197 or 100 metres £9. Order ref 9P1.

13A PLUGS Good British make complete with fuse, parcel of 5 for £2. Order ref 2P186.

13A ADAPTERS Takes 2 13A plus, packet of 3 for £2. Order ref. 2P187.

20V-0-20V Mains transformers 2 1/2 amp (100 watt) loading, tapped primary. 200-245 upright mountings £4. Order ref. 4P24.

BURGLAR ALARM BELL - 8" gong OK for outside use if protected from rain. 12V battery operated. Price £8. Ref. 8P2.

CAPACITOR BARGAIN - axial ended, 4700uF at 25V. Jap made, normally 50p each, you get 4 for £1. Our ref. 613.

SINGLE SCREENED FLEX 7.02 copper conductors, pvs insulated then with copper screen, finally outer insulation. In fact quite normal screened flex. 10m to £1. Our ref DB668.

M.E.S. BULB HOLDERS Circular base batten type fitting, 4 for £1. Our ref DB127s.

SPRING LOADED TEST PROBE - Heavy duty, made by the famous Bulgin company, very good quality. Price 4 for £1. Ref. BD597.

3-CORE FLEX BARGAIN No. 1 - Core size 1.25mm so suitable for long extension leads carrying up to 13 amps, or short leads up to 10 amps. 15mm for £2. Ref. 2P190.

3-CORE FLEX BARGAIN No. 2 - Core size 1.25mm so suitable for long extension leads carrying up to 13 amps, or short leads up to 25A. 10m for £2. Ref. 2P190.

ALPHA-NUMERIC KEYBOARD - This keyboard has 73 keys giving trouble free life and no contact bounce. The keys are arranged in two number pad, board size is approx. 13" x 4" - brand new but offered at only a fraction of its cost, namely £3 plus £1 post. Ref. 3P27.

1/8TH HORSEPOWER 12 VOLT MOTOR Made by Smiths, the body length of this is approximately 3in, the diameter 3in and the spindle 9/16th of an inch diameter. It has a centre flange for fixing or can be fixed from the end by means of 2 nuts. It is a powerful little motor which revs at 3,000 rpm. We have a large quantity of them so if you have any projects in mind then you could rely on supplies for at least two years. Price £6. Our ref 6P1, discount for quantities of 10 or more.

3 VOLT MOTOR Very low current so should be very suitable for working with solar cells. £1 each. Our ref BD681.

MINI SPEAKERS to use instead of headphones with your personal stereos - simply plug in to earphone socket. Excellent sound quality, only £4 per pair. Our ref 4P34.

INNER EAR STEREO HEADPHONES Ideal for lady listeners as they will not mess up your hair! Do come complete in a neat carrying case. Price £3. Our ref 3P56.

STEREO HEADPHONE AMPLIFIER Very sensitive. A magnetic cartridge or tape head will drive it. Has volume control and socket for stereo headphones. 3v battery operated. £1 each. Our ref BD680.

FET CAPACITOR MICROPHONE EAGLE CI.200 Output equivalent to a high class dynamic microphone while retaining the characteristics of a capacitor microphone. Price £1. Our ref BD646.

SUM-MIN TOGGLE SWITCH Body size 8mm x 4mm x 7mm SBDT with chrome dolly fixing nuts. 4 for £1. Our ref BD649.

SUB-MIN PUSH SWITCH DPDT. Single hole fixing by hexagonal nut. 3 for £1. Our ref BD650.





This month, in the first of our new *Ask PE* series, Andrew Armstrong shows one method by which the level of an audio signal could be put under remote control. I shall now illustrate an automatic control technique which allows the maximum audio signal level to be held below a given amplitude.

ATTENUATION

As may be expected with electronics, there are many ways in which signal amplitudes can be limited or compressed by automatic control circuits. Since one of the design objectives of the *Easi-build* series is to use simple techniques and readily available components, I have chosen for the heart of this circuit a well established chip specifically designed for audio attenuation, the MC3340.

Being designated as an audio attenuator, it is a chip intended to reduce signal amplitude from a maximum to a minimum level. It does not, unlike some amplitude control chips, provide amplification. This means that although the maximum limit to

Are your mods clipping the limits? Slim them into peak shape with our simple compressor

to a certain maximum level, usually that set by the power supply line limits and the inherent parameters of opamps and so forth. For a good example of this, consider a 741 opamp supplied from a $\pm 15V$ dualpower line. The data sheet shows that the maximum output voltage swing is typically $\pm 14V$. Obviously, then that is maximum obtainable output signal amplitude. But of course (and experienced constructors will probably wonder why I bother to mention such a basic fact that

ATTENUATION CHIP

What we need is a circuit that will smoothly begin to attenuate the output level at some point well before the maximum, and then to progressively reduce it until the maximum is reached. This is just what the MC3340 will do if controlled correctly.

The MC3340 has been designed by the manufacturers to limit the output voltage swing in response to either of two methods. One method is to vary the resistance between the chip's control pin and the ground supply line, or other reference point. The second method that may be used is to vary the voltage present at the control pin.

CONTROL VOLTAGE

In the circuit here, I've chosen to use a technique based on the variable resistance method, though, as you will see, it's actually a voltage that is indirectly used to vary the effective resistance.

COMPRESSOR

BY JOHN BECKER

which the signal can be allowed to go can be preset, weak signals will not be brought up to that level. Within certain limitations, the circuit will simply attenuate any signals which try to go above the limit.


CLIPPING

Alert sceptics will no doubt retort that any circuit will only allow signals to go up

everyone should know from the cradle), amplitude limiting in this way is distinctly unclear. All that happens is that the nicely shaped tops and bottoms of signals become increasingly flattened as the signal tries to push beyond the limits. Unless you actually want to create distortion, such as fuzz effects, you won't like the sound of this harshly clipped limiting.

If you look at Fig.1, IC2 is the MC3340, and pin 2 is its control point. From there, R15 presets the minimum resistance between the control pin and the ground line. The resistor is not taken directly to ground, but is taken via the transistor TR1. If TR1 were to be fully turned on by a voltage on its base, then R15 would in effect be taken directly to ground. With TR1 turned off, the resistance between the control pin and ground would be virtually

Fig.1. Complete circuit diagram for the compressor

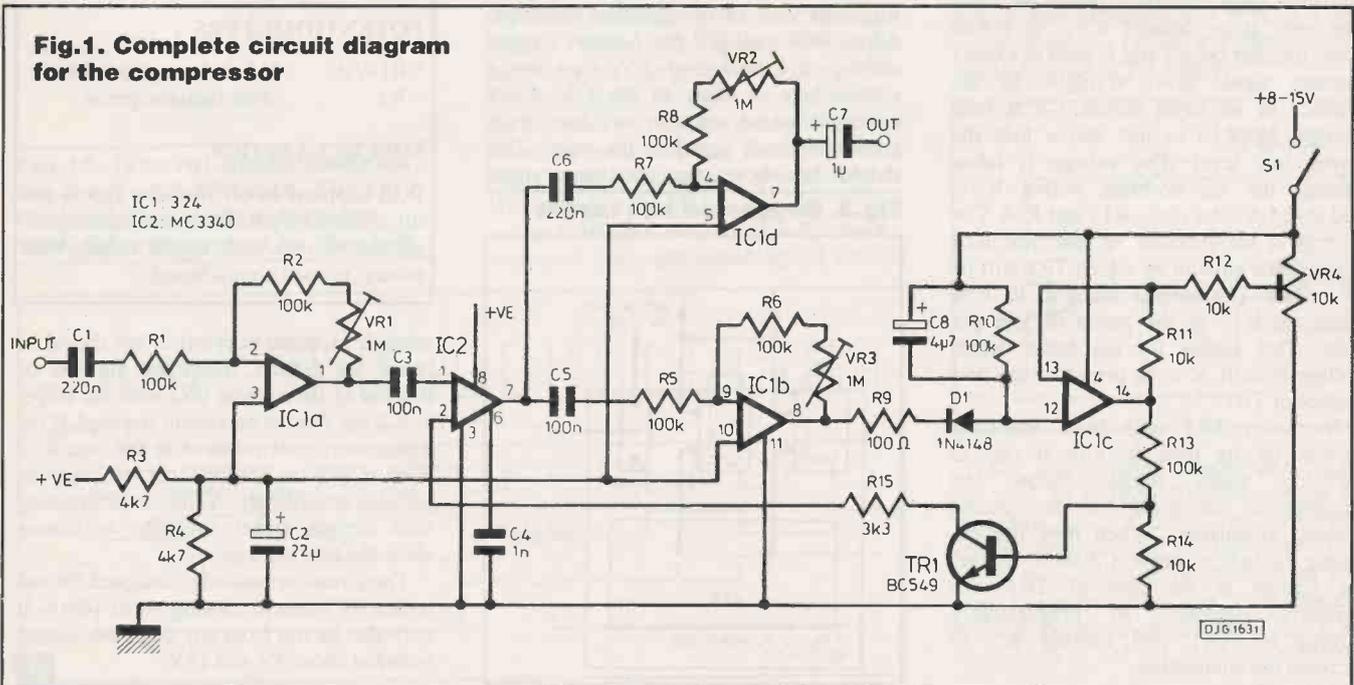

infinite. By varying the voltage on the base of TR1 between the two extremes, the effective resistance can be indirectly varied.

In order to use these facts to progressively limit the signal output level, we need to sense the level of the audio input signal and to generate a control voltage related to it, applying the control signal to the base of TR1.

INPUT BUFFER

Although you could apply the audio signal directly to the input of IC2, I've included a buffer and gain stage immediately before it, using IC1a. The preset, VR1, allows for the gain at IC1a to be set anywhere between times one, and times eleven. In this way you can preset the unit to suit the general output level of your source signal. However, don't regard IC1a as a general purpose preamp capable of bringing up extremely low level signals. It won't do it. It's simply there to allow you to trim the average signal level up a bit to suit the rest of the circuit.


The signal goes through IC2 and is split into two paths. The first path is that taking it through IC1d and to the output point at C7. IC1d is another buffer and gain stage where, as with IC1a, the output level can be trimmed upwards by VR2 from times one to times eleven. This allows you to compensate for any slight overall signal strength loss across IC2. If you prefer, you could also include a 10k log final output level control pot immediately after C7.

CONTROL EXTRACTION

The other path is the control voltage extraction route. IC1b is another buffer and gain stage, similarly preset by VR3. The next stage, around IC1c, is a half wave rectifier circuit and is used to extract average signal level voltages. In the absence of an input signal, C8 is held charged by R10 to just above half the power line level. The voltage is taken through the non-inverting buffer, IC1c, and to the divider chain R13 and R14. The current at the junction of R13 and R14 controls the amount by which TR1 will be on or off. The second input to IC1c is taken via R12 to the preset divider pot VR4. This allows for the basic output voltage from IC1c to be preset for the best control of TR1.

Normally, TR1 will have sufficient current on its base to turn it on, so allowing audio signals below the compression threshold to be passed without attenuation. When they become strong enough to cause C8 to discharge, the current at the base of TR1 will similarly decrease, so progressively turning off TR1, and causing IC2 to increase the attenuation.

Fig.2. Pcb layout for the compressor

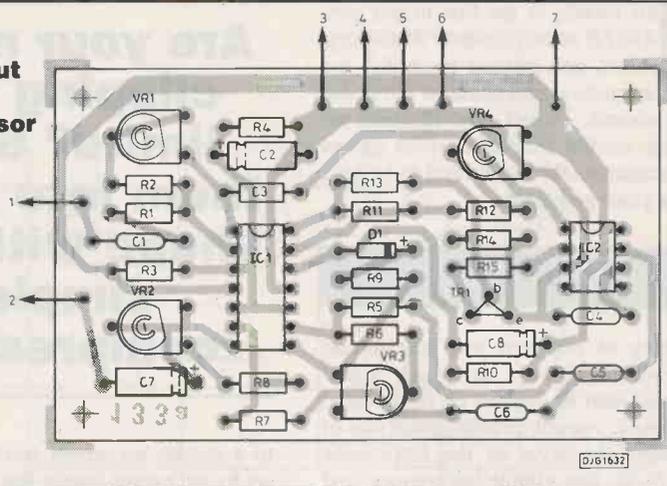


MOTOR BOATING

You will probably spot that if C8 was omitted, increased attenuation would instantly cause the output at IC1c to rise again, so decreasing attenuation at IC2, thus increasing the output at IC1, and consequently increase the attenuation ... ad infinitum! This most unsatisfactory situation has a name – motor boating; the effect sounds similar to the chugging of a motor boat. C8 has the purpose of slowing down the responses to increasing and decreasing outputs from IC2, and inhibits the feedback loop control to eliminate motor boating. Inevitably, the value chosen for C8 is a compromise between satisfactory responses to peak signals and instability. You might be interested to try different timing factors by using various values for C8 and R10, and seeing how the control responses vary.

SETTING UP

With no signal on the input, set VR1, VR2 and VR3 all to minimum resistance. Adjust VR4 until IC2 pin 2 shows a meter reading of a little over 3.5V (too low a voltage here is likely to result in motor boating when the unit is in use). Now apply a constant level signal to the input. This should be above the maximum signal

Fig.3. Suggested box layout

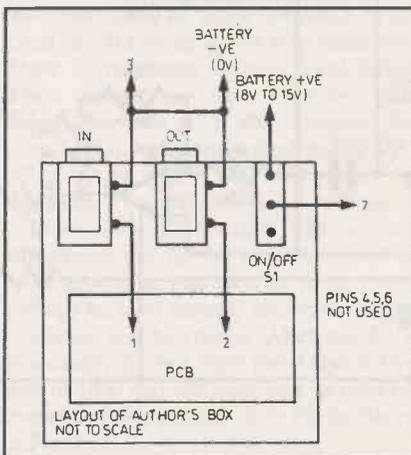

COMPONENTS

RESISTORS

R1, R2, R5-R8,	
R10, R13	100k (8 off)
R3, R4	4k7 (2 off)
R9	100R
R11, R12, R14	10k (3 off)
R15	3k3
All 0.25W 5% carbon film	

CAPACITORS

C1, C6	220n polyester (2 off)
C2	22µF 16V elect
C3, C5	100n polyester (2 off)
C4	1n polystyrene
C7	1µF 16V elect
C8	4.7µF 16V elect

SEMICONDUCTORS

D1	1N4148
TR1	BC549
IC1	324 quad opamp
IC2	MC3340 attenuator

POTENTIOMETERS

VR1-VR3	1M skeleton preset (3 off)
VR4	100k skeleton preset

MISCELLANEOUS

PCB supports (4 off), battery clip, 8-pin dil socket, 14-pin dil socket, mono jack sockets (2 off), spdt toggle switch, box to suit, printed circuit board.

strength expected in practice, but should be below the 500mV maximum allowed on IC2 pin 1. Then adjust VR2 until the output at IC2 pin 7 is the maximum required. If the maximum signal required at the output of IC1d is still too low, VR1 or VR2 may be adjusted accordingly. A little experimenting with various signal strengths will soon show the best settings.

The circuit is basically designed for use with a 9V battery, drawing about 10mA. It may also be run from any dc power supply between about 8V and 15V.

PI



MARCO trading
ELECTRONIC COMPONENTS & CONSUMABLES

THE MALTINGS, HIGH STREET, WEM.
SHROPSHIRE, SY4 5EN. DEPT EE9

Tel: 0939 32763 Telex 35565 Fax 3380

Electronic Component Mail Order Company - Established 1972
217+ PAGE CATALOGUE AVAILABLE - SEND £1 FOR YOUR COPY
Including Discount Tickets - 50p off £5+ order; £1 off £10+ order; £5 off £50+ order.

★ Please add £1.00 postage and packing to all orders unless stated. ★

MARCO TRADING'S LATEST
★ 217 PAGE CATALOGUE
NOW READY ONLY £1 ★

FULL OF CMOS, TRANSISTORS, LS, ICs, DIODES, BRIDGES, VALVES, RESISTORS, BOXES, BOOKS, SOLDERING TOOLS, TEST GEAR, METERS, CABLE, KITS, SPEAKERS, AERIALS, AUDIO ETC. ETC. AND INCLUDING £6.50 OFF IN DISCOUNT TICKETS.

Also with special offer list prepaid envelope & order form
VISIT OUR RETAIL SHOPS

WEM (MARCO), The Maltings, High st. (0939) 32763
WOLVERHAMPTON (WALTONS).
55A Worcester St. (0902) 22039
BIRMINGHAM (SUPERTRONICS).
65 Hurst Street (021) 666 6504



ANTEX SOLDERING KITS

C iron £7.65 Auto repair £10.75
CS iron £7.75 SK5 £10.75
XS iron £7.85 SK6 £10.85
ST4 Stand £2.99
Spare elements £3.75
Spare tips £1.60

SOLDER 60/40

A 500g reel of 22 swg multicore solder
60% tin, 40% alloy
non-corrosive.
£5.75 ALSO 18swg

ORYX PORTASOL GAS SOLDERING IRON

Price (1+) £18.75
Spare tips 1,2,4,3,2,4mm £5.50



FM TRANSMITTER
Very High Quality "MINI-BUG" - Ideal for Baby Alarm, etc!!
A very good range is obtainable - We have obtained over 1/2 mile, but it does depend on conditions. Simply remove cover - insert battery - and you're ready to go. Reception can be obtained on any FM ratio

Frequency: 06-109 MHz-Fm
Power: PPE 9V
£9.78

★ SEPTEMBER SPECIAL OFFER ★

★ SOLDER SPECIAL ★

- 1 x Antex 25w iron
- 1 x Antex soldering stand
- 1 x Desoldering pump
- 1 x Reel solder 18qm
- ALL FOR £12-50**

OSCILLOSCOPES

PLEASE TELEPHONE RE-MODELS CURRENTLY IN STOCK AND PRICES.

"CLOSED-CIRCUIT" TELEVISION SYSTEM COMPRISING:

PRICES
1XCAMERA

1XMONITOR

1XCAMERA BRACKET



COMPLETE WITH LENSE USED

USED

USED

NEW

ALSO NEW EQUIPMENT PLEASE RING

CHARGER FOR NI-CAD BATTERIES


Charges AA, AA, c. d& PP3 NI-CADS
£4.99



12 VOLT RECHARGEABLE UNIT

10xD size Ni-Cads (4Ah) encapsulated in a black plastic case, fused holder, gives 12V output when fully charged. Ex-equipment - fully tested and guaranteed. 245x75x75mm.
£9.19 PLUS £2.12 Carriage

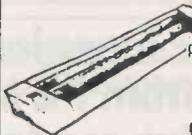12V Twin Fluorescent lamp 12" Double Tubes
IDEAL FOR BOATS, CARAVANS, VANS, ETC.



Attractive white fitting, ribbed perspex diffuser, on/off switch, 3ft cable, transistorised circuitry, keyhole fixing. 12V D.C. 8W tubes
£5.99 each 368x67x43mm

QUARTZ-HALOGEN SPOTLIGHT



£5.99

CHARGER FOR UNIT £12.50 PLUS £2.12 carriage

NI-CAD RECHARGEABLE BATTERIES


	1 off	10 off
AAA	£1.50	£1.30
AA	95p	85p
C	£1.95	£1.80
D	£2.00	£1.85
PP3	£3.90	£3.20



★ LEARN BY BUILDING ★ ENJOY BY USING ★

PROJECT KITS

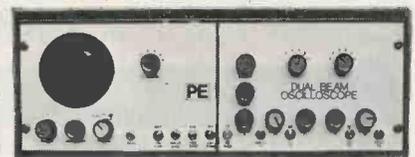★ BE CREATIVE ★ RAISE YOUR SKILLS ★ GET KITTED! ★



DUAL BEAM OSCILLOSCOPE

2Y-amps, 6 ranges, variable level, DC to over 1MHz. 4 modes - Y1, Y2, Y1 & Y2, Y1 & Y2 to X. Time base variable from 0.05Hz to 20KHz. Variable sync level, polarity and source. Separate bright-line, brilliance and focus controls. Independent trace deflection controls. Details in catalogue.

BURGLAR ALARM CONTROLLERS

MULTIZONE CONTROL

SET280

£23.90

Two entry-zones, anti-tamper loop, personal attack, entry-exit timing, timed duration, automatic resetting, latching LED monitors.

SINGLE ZONE CONTROL

SET279

£10.50

With timed duration control and latching LED monitor. Both units can be used with any standard detection devices, such as contact or magnetic switches, pressure pads, tremblers, ultrasonics, infrared etc., and will activate standard bells, strobes or sirens.

COMPUTER KITS

The software listings published with the computer kit projects are for use with C64, PET and BBC computers.

CHIP TESTER SET258F £41.50

Computer controlled logic and chip analyser.

EPROM PROGRAMMER SET277 £26.20

Computer controlled unit for 4K Eproms.

MICRO-CHAT SET276 £69.50

Computer controlled speech synthesiser.

MICRO-SCOPE SET247 £49.50

Turns a computer into an oscilloscope.

MICRO-TUNER SET257 £57.40

Computer controlled, tuning aid and freq counter.

MORSE DECODER SET269 £26.70

Computer controlled morse code-decoder.

MORE KITS IN CATALOGUE
SEND MEDIUM S.A.E. FOR CATALOGUE AND WITH ALL ENQUIRIES (OVERSEAS SEND £1.00 TO COVER POSTAGE)

VARIOUS

VOICE SCRAMBLER SET287 £49.50

32 switchable channels to keep your communications confidential.

STORMS! £35.50 each unit

Raw nature under panel control! Wind & Rain SET250W. Thunder & Lightning SET250T.

DISCO-LIGHTS SET245F £69.50

3 chan sound to light, chasers, auto level.

EVENT COUNTER SET278 £36.60

4-digit display counting for any logic source.



PE FREQUENCY COUNTER AND GENERATOR
DETAILS IN CATALOGUE

ENVIRONMENT

SIDEREAL CLOCK SET295 £54.50

Dual purpose star-time and solar-time digital clock with alarm.

WEATHER CENTRE

Keep the Met Office in check and monitor the wind speed and direction, rain, temperature, soil moisture and sunny days.

Six detector circuits - KIT 275.1 **£18.50**

Automatic metered control monitor - KIT 275.2

Optional computer control circuit - KIT 275.3 **£15.50**

ELECTRONIC BAROMETER

SET285 **£41.20**

Computer controlled unit for monitoring atmospheric pressure.

GEIGER COUNTER SET264 £65.50

A nuclear radiation detector for environmental and geological monitoring. With built in speaker, meter and digital output. This project was demonstrated on BBC TV.

ORDERING

Add 15% VAT. Add P&P - Sets over £50 add £3.00. Others add £2.00. Overseas P&P in catalogue. Text photocopies - Oscilloscope £3.00, Geiger £3.00, Weather £2.00, others £1.00, plus 50p post or large SAE. Insurance 50p per £50. MAIL ORDER, CWO, CHQ, PO, ACCESS VISA. Telephone orders: Mon-Fri, 9am - 6pm. 0689 37821. (Usually answering machine).

MORE KITS IN CATALOGUE

PHONOSONICS, DEPT PE99, 8 FINUCANE DRIVE, ORPINGTON, KENT, BR5 4ED.

MAIL ORDER



There are many situations in which a simple means of controlling devices external to a computer, other than standard peripherals such as printers or modems, is required. Such devices might include, for example, complex stage lighting systems, model railway point control systems, automated musical instruments and multiple d/a converters.

If the number of input lines required by such a device is limited to eight, then there is no reason why the data output lines from a standard parallel printer port can not be used for the purpose. One way or another, through a high level language, the computer's operating system or, most directly, by means of a machine code routine, it will be possible to set the states of the printer ports output lines high or low. Those output lines will either be directly connected to the input lines of

computer being used is one solution, and is usually expensive. Fortunately, it is very simple to make a parallel output port with 64 output lines that plugs directly into the parallel printer port of any computer. As explained below, the states of the 64 output lines are established by sending a simple command sequence to the device via the parallel printer port. Again, the command sequence can be issued in any language the user prefers. The component count for the 64-line device is very low (ten readily available chips and a few capacitors and resistors) as is the cost.

three input lines D3-D5 supply the address inputs to a decoder, the outputs of which serve to enable one of the eight addressable data latches. Input line D6 serves to trigger the whole circuit and data line D7 carries the data to be loaded into the specified output line as described in the section on programming.

Pull-up resistors are required on the buffer outputs because the chip has open-collector output stages. Decoupling capacitors adjacent to each chip are used to suppress power rail transients.

PROGRAMMING

The state of each output is independently established by sending a short command sequence on input lines D0-D7.

If the output lines are numbered 0-63,

THE CIRCUIT

The circuit diagram is shown in the diagram. The eight input lines are driven by the data output lines from the

64-LINE OUTPUT PORT

the external device to be controlled or connected to those lines through some simple buffering circuitry. The choice of programming approach will often depend on the level of familiarity with the language or system, but if the external device requires very rapid changes of state on its input lines it might be essential to use machine code.

However, if the number of input lines required by the external device is more than eight, there is a problem. Purchase of one or more special purpose parallel interface boards for the particular

Another ingenious idea from PE's innovative readers.

computers parallel printer port. Five of the input signals pass first through non-inverting buffers, the three 'lowest order' lines (D0, D1 and D2) driving a miniature address bus connected to the three address inputs (A0, A1 and A2) of the eight addressable data latches, each of which provides eight output lines. The

then input lines D0-D5 select the output line that will be affected. The states of D0-D5 can be regarded as the 6-bit address of the required output line. Input line D7 determines whether the chosen output line will be set high or low when the command sequence is effected. A transition of line D6 from high to low implements the command; for example, if D7 is high when the transition occurs, the selected output line will be forced high. Two examples will make everything clear.

Example 1. To set the state of output line 53 high.

	D7	D6	D5	D4	D3	D2	D1	D0
Stage 1:	1	1	1	1	0	1	0	1
Stage 2:	1	0	1	1	0	1	0	1
Stage 3:	1	1	1	1	0	1	0	1

In this example, D5-D0 represent 53 in binary. D7 is '1' because output line 53 is to be set high. D6 changing from 1 to 0 in Stages 1 and 2 causes the output line to be set high.


Example 2. To set the state of output line 22 low.

	D7	D6	D5	D4	D3	D2	D1	D0
Stage 1:	0	1	0	1	0	1	1	0
Stage 2:	0	0	0	1	0	1	1	0
Stage 3:	0	1	0	1	0	1	1	0

In this example, D5-D0 represent 22 in binary. D7 is '0' because output line 22 is to be set low. D6 changing from 1 to 0 in Stages 1 and 2 causes the output line to be set high.

The circuit described can be directly connected into the parallel printer port of any computer and the states of its output lines established by sending a short command sequence to the printer port in any language available to the user.

R. Milner and A. Horsman, Leeds, PE

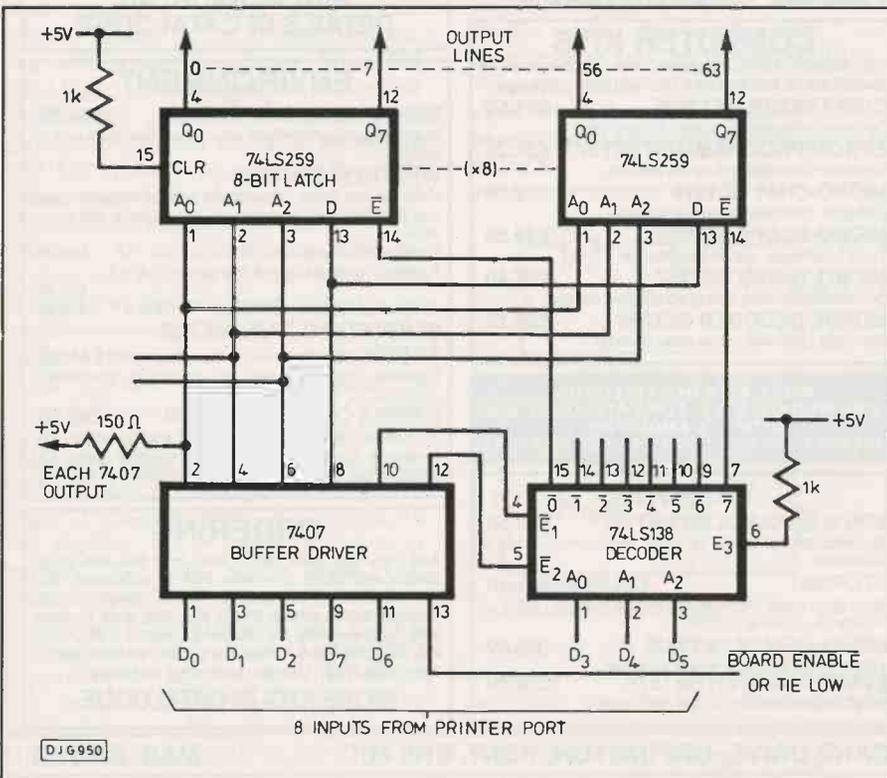

Free Reader Adverts

*Searching for that elusive component?
Surplus equipment to sell?
Read the rules and fill in the form below to have your free ad published in PE BAZAAR.*

Wanted: RPY58A photoresistor for dark activated switch. Edward Murray, Old Cardingham, Bodmin, Cornwall PL30 4ED. Tel: (0208) 82496.

Advance VM78 service manual £5.00
Gould scope manuals, 051100, 052000, 053350. £10 each. S.J. Austin, 8 Greenwood Avenue, Chinnor, Oxford, OX9 4HN.

Scope tubes with data base and screens 4 inch round £5. 3 1/2 inch CV2286 £5. 1 1/2 inch VCR522 £8. Mr. E. Hall, 39 Arch Bell Avenue, Brighouse, W. Yorkshire HD6 3SU.

Geiger counter £53. Texas speech synthesiser £29. Heathkit V7AU V.V.M. £27. Atari 8-Bit speech synthesiser £20. Mr. R. Hearn, 10 Speedwell Close, Pakefield, Lowestoft, Suffolk NR33 7DU. Tel: 0502 566026.

Wanted: Spectrum sound generator. Circuit diagram and all components sheet. J. Powell, 31 Eddystone Rise, Simpsons Lane Estate, Knottingley, W. Yorks WE11 0HS.

Philips MDCR200 test cert. and data. Cost over £100. As new £35 perfect tape storage. Tel: 061-799 7365.

Quad 405 100W/channel Amp. 33 control unit. FM3 tuner. Showroom condition £275. Perth (0738) 37165. C. Korycinski, 17 Pitcullen Terrace, Perth.

FM telephone transmitter. On/off switch, low battery indicator. Plugs directly into BT socket £20. B. Gohil Tel: 01-902 7233.

UK101 computer (24K0 cased with sound board Centronics port software and manuals £50 ono. Also Larnakit oscilloscope £45 ono. Tel: (0373) 826454 evening and weekends (Wiltshire).

Philips video tapes for N1500-1700 recorders (eg LVC 120), over 20, some new, £15 the lot. Tel: D. Starr, 54 Rickley Lane, Bletchley, MK3 6BT. Tel: (0908) 77139.

741 ICs, 555 ICs, Diodes, LEDs, 8 pin, 14 pin sockets. Clearing out - bag fulls £5.25. No dealers post only. Mr. D. Martin, 6 Downland Garden, Epsom, Surrey KT18 5SJ.

Ferrogram series seven open reel two track stereo. New heads, VGC. Lots of tapes. £200 ono. J. Preston, Dept. Elec. Eng. ASI. Bld., University of Hull, Cottingham Road, Hull, HU6 7RX.

Copper clad fibreglass boards, double sided, fifty square inches (approx 8" x 6"). £1.50 each inc. p&p. M. Harrod, 5 Brookside Drive, Oadby, Leicester LE2 4PB. Tel: (0533) 720663.

Quick data drive for VIC/C64 with operating system and wafers £10 inc. P&P. R. Yarwood, 14 Betony Vale, Royston, Herts SG8 9TF. Tel: (0763) 241587.

Wanted: service manual for Safgan DT-415 oscilloscope. Photocopy accepted. Will pay price. Mr. D. Walters, 53 Mount Libanus Street, Treherbert, Rhondda, M. Glam. CF42 5RH.

Components, transistors, resistors, capacitors, TTCs, Computer ICs etc. Also Spectrum 48K cassette software. Private sale. Offers. J.J. Hodge, 28 Snowden Court, Croesyceiliog, CwmBran, Gwent NP44 2JA.

Tektronix type 7603 oscilloscope. 4 trace (2 x 7A26 Amps), delay timebase (7B53A). 50 MHz B/W. Good condition. Offers? Tel: 021-550 8154.

Solartron dual beam oscilloscope, (valve type). Manual and/or circuit diagram, also test leads wanted. State price. Mr. J.W. Dixon, 19 Salkeld Road, Penrith, Cumbria CA10 1ND.

AVO multiminator £25 megger £50 FWKE digital £50 HT probe. £10 Tel: 01-554 2913, 6-8pm.

90W FM transmitter 88-108 MHz, 30 miles range, unused. Final reduction £130. Tel: 01-683 1394 after 5pm.

Wanted: instruction leaflet for Micronta 22.193 model Radio Shack as sold by Tandy. Mr. W.A. Yates, 34 Livesey Street, Chorley Lancs PR7 1AU. Tel: 78464.

2 x 8 inch disk drives, 1 meg each. Brand new, never used. Offers? Tel: (0732) 354311 evenings. Mr. E. Hoskins, 99 Deakin Leas, Tonbridge, Kent TN9 2JT.

For Sale: faulty equipment double manual electronic organ £50. Fax machine (Ricoh) £40. Tandberg monitor and keyboard £40. J. Pike Tel: 01-514 5918.

Computer monitor 11 inch green screen. BNC video input. Perfect working order - case a bit untidy, £25. Mr. M. Counsell, 51 Kempton Grove, Fiddlers Green Lane, Cheltenham, Glos GL51 0JX. Tel: (0242) 45564 after 6pm.

Surplus components for sale. Pack of 46, £4. SAE for list. Jason Young, 2 Woodside, Doddington, March, Cambs. PE15 0SB.

Magazines: Practical Electronics 1966 to 1980; Practical Wireless 1966 to 1978. Complete and in binders. B. Marshall, 2 Normanton Way, Histon, Cambridge CB4 4XS. Tel: (0223) 237188.

Needed: memory map for TRS-80 micro colour computer model MC-10 (cat no. 26-3011). Photocopy will do. Thankyou. Mr. N.C. Fairman, Basement Flat 6, 59 New Dover Road, Canterbury, Kent. Tel: (0227) 66395.

Morse tutor Datong £38. Active antenna AD370 £40. TU1000 RTTY terminal £35. Tel: (0227) 458970. after 6pm.

Wanted: for A level project: BBC User Guide, 6502 Second Processor, EPROM Eraser, Master Circuit diagram. R.D. Clark, 29 Knightscroft Ave., Rustington, W. Sussex BN16 2HN. Tel: (0903) 784792.

ZX 81 and power supply, all leads, two Sinclair ZX manuals - price £12. Buyer collects. A.C. Holdway, 20 Wherwell Road, Guildford, Surrey GU2 5JR.

Beulah Electronics 405 line CCTV camera and monitor and Link Electronics camera (1 inch tube) for sale. David Sweetman, 21 Norton Avenue, Surbiton, Surrey KT5 9DX. Tel: 01-390 0721.

PE BAZAAR

Name & Address			

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules.
Signature.....Date.....

RULES Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be posted within one month of cover date. (One month later for overseas readers).
Send this form (or a photocopy of it) to:
PE Bazaar, Practical Electronics, 193 Uxbridge Road, London W12 9RA.

PRACTICAL ELECTRONICS CLASSIFIED

Reach thousands of serious electronic and computer enthusiasts. Advertise in PE Classified pages: Rates 20p per word or £8.50 per single column cm (plus VAT). All classified advertisements must be pre-paid. Send your copy with the remittance (payable to Intra Press or payment by Visa or Access accepted) to: Practical Electronics, Intra House, 193 Uxbridge Road, London W12 9RA. Tel: 01-743 8888. Fax: 01-743-3062

LET PE WORK FOR YOU!

EDUCATION

FULL-TIME TRAINING COURSES

2 YEAR

BTEC NATIONAL DIPLOMA

Electronics and Communications Engineering

(TV, Computers, Programming, IT)

1 YEAR

BTEC NATIONAL CERTIFICATE

1. Electronic Equipment Servicing

(TV, Video, CCTV)

2. Computing Technology

(Microprocessors, DataComms, Interfacing)

3. Information Technology

(Telecomms, Satellite TV, Networks)

4. Software Engineering

(Assembler, BASIC, Pascal, CAD/CAM)

★ Those eligible can apply for E.T. grant support ★

★ An equal opportunities programme ★

COURSES COMMENCE

Monday 18th Sept. 1989

LONDON ELECTRONICS COLLEGE

Dep: AA, 20 Penywern Road, London SW5 9SU. Tel: 01-373 8721

HNC in Microprocessor Systems

Milton Keynes Skillcentre is offering a one year full-time course commencing on the 4th September 1989.

The course includes 20 weeks work placement in Industry.

This is a Training Agency funded equal opportunity course and training allowances will be paid.

Please phone 0908 670001 for an application form or write to:

Milton Keynes Skillcentre, Chesney Wold, Bleak Hall, Milton Keynes MK6 1LX.

RETAILERS

BATH

L.F. HANNEY

77 Lower Bristol Road, Bath, Avon.

Tel: 0225-24811

Your electronics component specialist for

AVON, WILTS. & SOMERSET

Open every day, except on Thursday

EDINBURGH

OMNI ELECTRONICS

stock a wide range of electronic components at

174 Dalkeith Road

Edinburgh EH16 5DX

Tel: 031 667 2611

Open Mon-Fri 9am-6pm

Sat. 9am-5am

Send 2x19 stamps for CURRENT CATALOGUE!

LONDON EAST

A & G ELECTRONICS LTD

If you are buying Electronics Components elsewhere you are almost certainly paying too much!. Write to us for a free 1989 catalogue and start saving money. Please send two 19p stamps towards postage.

100 Park Avenue, London, E6 2SR. Tel: 01-552 2386

LONDON S. WEST

MULTILODE LTD

For electronics components, leads, aerosols, aerials, I.C.'s, diodes, video heads, tools, telephone accessories, books, magazines etc., etc., etc.,

Multilode Ltd. 7 Arlington Parade, Brixton Hill, SW2 1RH Tel: 01-326 1793

Open Mon to Sat 9am to 6pm

MANCHESTER

DEANS GATE ELECTRONICS

We stock a large range of electronic components, test equipment, telephone accessories, computer accessories, microphones, speakers, disc lighting, mixers, meters, stylus, so call in and have a look around.

263 Deansgate, Manchester
Telephone: 061-834 1185

SOUTHAMPTON



BIG STOCK - KEEN PRICES!

See our display advertisement in this magazine!

SOUTHSEA

ELECTRONIC COMPONENTS

EVERYTHING FOR YOUR NEXT PROJECT
THE BIGGEST DISPLAY IN THE SOUTH IS AT

FRASER ELECTRONICS

42 ELM GROVE ★ SOUTHSEA ★ HANTS
Telephone: 0705-815584

Barclaycard

Access

STOKE-ON-TRENT

ANDOR ELECTRONICS

11 Victoria House,
Paxton Street,
Hanley,

Stoke-on-Trent, ST1 3SD
Tel: 0782 283642

SURREY

PLS

16 Central Road
Worcester Park
Surrey KT4 8HZ
Tel: 01-330 6540

Programmable device specialists.
(PAL's PROM's, PLD's etc). Many other components in stock

Resistors 1/4 W 5% carbon (E12) 1p metal film 1%3p
 Resistor Pack 85 different E12 values + zero ohm link total content
 1000 resistors£8.95
 LEDs red/green 3/5mm6p each. Yellow 11p
 Cable ties 75mm1p each £5.95/1,000 £49.50 per 10,000
 Stepping motor 4 phase 12v 7.5 step 50 ohms£8.95
 SAA1027 stepping motor driver chip£3.95
 FM transmitter Kit good quality sound£7.94
 High quality photo resist copper clad epoxy glass boards
 Dimensions single sided double sided
 3x4 inches £0.69 £0.76
 4x8 inches £1.64 £1.91
 6x12 inches £3.80
 12x12 inches £7.50

Special Offers
 Computer Grade Capacitors with screw terminals 38000uf 20v £2.50
 8700uf 10v £1.95, 6800uf 15v £2.95, 10000uf 16v £1.50
 7 segment Common anode led display 12mm£0.45
 LM2931A.TS.0 Low drop out 5V regulator T0220 package£0.85
 BS250 P channel MOSFET £0.45, BC559 transistor£3.95 per 100
 74LS05 hex inverter £10.00 per 100, used 8748 Microcontroller £3.50
 Stereo L.W/MW/FM Tuner pre-amp assembly complete with
 volume/tone controls and tuning scale Brand new in makers carton
 £5.95, faulty £2.50

Circuit diagram description and setting up procedure for tuner
 assembly described above £0.50. 5 digit 6v electromagnetic counter
 £1.95
 Hour counter (used) 7 digit mains 240V AC 50Hz£0.95
 LCD display 16 digit 7x5 dots dot matrix£2.50
 Query keyboard 38 key good quality switches£5.00
 wide range of CMOS TTL 74HC 74F Linear transistors kits
 capacitors, resistor tools etc always in stock
JPG Electronics 276 Chalsworth Road Chesterfield S40 2BH
 Access orders (0246) 211202. Callers welcome

Carbon Film Resistors 1/4W E24 series 0.51R to 10M01p
 100 off per value - 75p 1000 off in even hundreds per value - £7
 Metal Film 1/4W 10R0 to 1M0 5% E12 series - 2p 1% E24 series - 3p
 1/2Watt metal/carbon film E24 series 1R0 to 10M011p
 1 Watt metal/carbon film E12 series 4R7 to 10M05p
 BC107/B/9 - 12p BC547/B/9 - 8p BC182L 184L - 10p
 BFY50/51/52 - 20p 2N3055 - 50p TIP31A,32A - 25p TIP41,42, - 40p

Tantalum head subminiature electrolytics (Mids/Volts)
 0-1.35, 0-2.25, 0-4.7/35, 3-3/16, 4-7/16 - 14p 4-7/35 - 15p
 2-2/35, 4-7/25, 10/5 - 15p 4-7/35, 6/8/16 - 16p 10/16, 22/6 - 20p
 22/16 - 30p 33/10 - 30p 47/10 - 35p 100/6 - 40p

Aluminium Electrolytics (Mids/Volts)
 1/50, 2-2/50, 4-7/25, 4-7/50, 10/16, 10/25, 10/50 - 5p 22/16, 22/25 - 6p
 22/50, 47/16, 47/25, 47/50 - 6p 100/16, 100/25 - 7p 100/50 - 12p
 100/100 - 14p 220/16 - 8p 220/25, 220/50 - 10p 470/16, 470/25 - 11p
 1000/25 - 18p 1000/35, 220/25 - 22p 4700/25 - 70p

Miniature Polyester Capacitors 250V Wkg. Vertical Mounting
 .01, .015, .022, .033, .047, .068 - 4p 0-1 - 5p 0-15, .22 - 6p 0-47 - 8p

Mylar Capacitors 100V Wkg. Vertical Mounting E12 Series
 1000p to 8200p - 3p .01 to .068 - 4p 0-1 - 5p 0-15, 0-22 - 6p

Subminiature Ceramic Plate 100V Wkg. E12 Series Vertical Mounting
 2% 1P8 to 47P - 3p 56P to 330P - 4p 10% 390P to 4700P - 4p
 Ceramic plate/disc E6 Series 50V 22P to .047 - 2p

Polystyrene Capacitors 63V Wkg. E12 Series Axial Mounting
 10P to 820P - 3p 1000P to 10,000 - 4p 12,000P - 5p
 1N4148 - 2p 1N4002 - 4p 1N5404 - 14p W01 bridge - 25p
 0A91 - 6p AA143 - 8p W005 - 20p 1N4006 - 6p
 Zener diodes E24 series 3V3 to 33V 400mW - 8p 1 watt - 12p
 L.E.D.'s Red, Green & Yellow 3mm & 5mm - 10p 8mm - 35p
 20mm fuse 0-1A to 5A quick blow - 5p Anti Surge - 8p
 High Speed drills 0-8mm, 1-0mm, 1-3mm, 1-5mm, 2mm - 30p
 Expo Reliant drilling machines 12V d.c. with improved 3-jaw chuck 6.50
 Nicads AA - 80p HP11 - £2 PP3 - £4.20 Universal Chargers - £6.50
 Glass reed switches single pole make contacts - 8p Magnets - 12p

VAT inclusive. Return postage 25p (free over £5). Lists free.

THE C.R. SUPPLY CO.,
 127 Chesterfield Road,
 Sheffield S8 ORN. Tel. 557771.

>>>RESISTOR PACKS<<<

**1/4W 5% CARBON FILM
 E12 RANGE 10R to 10M
 10 of any 1 value 6p
 10 OF EACH VALUE
 Total 730 resistors
 £3.95**

Add 35p P&P & 15% VAT

**RMOS P.O. BOX 3
 USK GWENT NP5 2YF.**

TURN YOUR SURPLUS
 ICS transistors etc into cash, immediate
 settlement. WE welcome the opportunity to
 quote for complete factory clearance.
 Contact:
COLES-HARDING & CO.,
 103 South Brink, Wisbech, Cambs.
 ESTABLISHED 15 YEARS
 Tel:0945 584188 - Fax: 0945 588844


Cooke International
 DO YOU WANT
**SCOPES, GENERATORS, POWER
 SUPPLIES, POWER METERS, DVM'S,
 OSCILLATORS, ATTENUATORS.
 TEST EQUIPMENT.**

Contact: Cooke International, Unit Four,
 Fordingbridge Site, Main Road, Barnham,
 Bognor Regis, West Sussex PO22 0EB.
 Tel: 0243 545111, Fax: 0243 542457
 Wide range of items available. Send for lists.

**IS YOUR
 CLASSIFIED AD
 A TIGHT SQUEEZE?**

**STRETCH
 OUT**

**in display pages of
 PE! Phone Sarah
 Holtham on
 01-743-8888 for details!**

ROBOTICS
 Use your home computer to operate servo based
 Robots of your own design. Suitable for ZX
 Spectrum, Tatung, Einstein and Amstrad CPC.
 Send SAE for details to:
**PRF Software Dept. PE, 26 Olton Road,
 Mickleover, Derby DE3 5PL.**

**Are you an electronics
 hobbyist?**
 If so, you will benefit from joining
 British Amateur Electronics Club!
 BAEC, C. Bogod, 26 Forrest Rd.,
 Penarth, South Glamorgan

*** Series X Mixer Kits**
 * up to 1,000 inputs
 * 60+100 mm faders, pots,
 panels and audio switches
 * 6 auxiliaries
 * versions for recording PA,
 radio, disco
 * circuit diagrams
*** From £9.92**



Send 19p for catalogue to: K. Tek, P.O. Box 172a,
 Surbiton, Surrey KT6 6HN. Tel:01-399-3990

**SURPLUS/REDUNDANT ELECTRONICS
 COMPONENTS WANTED**
 ICs - Tuners - Transistors - Valves - Diodes etc - any
 quantity considered - immediate payment.
ADM ELECTRONICS SUPPLIES
 Tel 0827 873311 Fax: 0827 874835

CAMBRIDGE COMPUTER SCIENCE LTD

5.25 inch Disk Drives, 80 Trak DSDD £34.00 each
 3" Disk Drives, 40TK, SSDD £28.00 each
 5.25" Disk Drives, 80TK, DSDD Used, No Why £15.00 each
 5.25" Disks, DSDD, 48tpi boxes of 10 £3.00/box
 Dual Disk Drive Power Supply £20.00 each
 Lead to connect one drive to psu £ 2.00 each
 50W PSU 5V 6A, 12V 2.5A, -5V 0.5A, -12V 0.5A £16.00 each
 Bench PSU 0-30V @5A Limited quantity only at £45.00 each
 Single Data lead (BBC Micro to Disk Drives) £ 2.00 each
 Dual Data lead (BBC Micro to 2 Disk Drives) £ 4.00 each
 Power lead (BBC Micro to Disk Drive) £1.00 each
 Dual leads (BBC Micro to 2 Disk Drives) £ 2.00 each
 68000 CPUs (The first orders get 12MHz chips) £3.50 each
 74LS TTL assortments. 10 different devices £1.20 pack
 8K Byte NV ram chips £3.00 each £10.00 four
 20 pin dll low profile IC sockets £0.50 (ten) - £ 4.00 (100)
 40 pin dll low profile IC sockets £0.60 (ten) - £ 5.00 (100)
 Keyboard, 100 keys on board LCD & micro if £8.00 each
 Toroidal mains transformer 12V 4A & 0.4A, 12-0-12 @0.1A & 2A,
 9-09 @0.2A £4.00 each - £6.00 for 2 - £8.00 for 3

All items new unless stated. Add 15% VAT to all prices. Prices
 include postage. Add 50p to orders below £5.00. Send an SAE for our
 latest list or for more info.

Dept PE, 374 Milton Road, Cambridge, CB4 1SU
Tel: 0223 424602
SAE with all enquiries please!

74HC series ICs

74HC00 19p	74HC02 19p	74HC03 19p
74HC04 19p	74HC08 19p	74HC10 19p
74HC11 26p	74HC14 39p	74HC20 19p
74HC27 31p	74HC30 35p	74HC74 38p
74HC86 29p	74HC107 36p	74HC138 41p
74HC161 48p	74HC175 52p	74HC393 69p

74LS series ICs

74LS00 20p	74LS02 20p	74LS05 20p
74LS30 20p	74LS32 20p	74LS51 20p
74LS90 30p	74LS93 30p	74LS107 23p
74LS112 23p	74LS138 35p	74LS139 35p
74LS151 38p	74LS164 38p	74LS193 55p
74LS245 58p	74LS374 52p	74LS375 64p

74F series ICs

74F00 32p	74F02 32p	74F64 32p
74F174 77p	74F251 64p	74F353 64p
74F373 91p	74F398 96p	74F399 96p

ECL series ICs

10101 1.15	10102 1.15	10103 1.15
10104 1.15	10124 3.68	10125 3.68

A wide range of components and TTL, CMOS and
 ECL ICs are available. We also supply PC, XT and
 AT spares at LOW PRICES. Write or phone for our
 FREE catalogue.

Resistors at bulk prices Your Mix
 Carbon film, 0.25W, 5% 1p each or 45p for 50
 Metal film, 0.25W, 1% 3p each or £1.35 for 50

IC sockets, solder type (pin:price)
 14:10p, 16:11p, 20:14p, 24(0.6 or 0.3):16p.

IC sockets with 0.1uF decoupler
 14:60p, 16:65p.

Prototyping boards (Vero)
 IBM XT £45.00, IBM AT £52.00

ACCESS welcome by post or phone. Callers by
 appointment please. VAT INCLUDED. Please add
 50p for post and packing. Catalogue free. No mini-
 mum order charge.

BLACKMORE ELECTRONICS LTD.
 FREEPOST, Blandford Forum
 Dorset DT11 7BR

 0258 451347 (24hr answerphone) 

PROGRAM NOW
*The Professional Software Developers
 Journal*
 Available from all good newsagents price
 £1.50
 From The publishers of PE.

CLASSIFIEDS

SERVICES

We will make drilled PCBs to your specifications - one-offs to small production runs. Cost 6p/cm² single sided 12p/cm² double sided. An initial charge may be made for artwork transfer to acetate. Send your artwork to us or for further details contact Paul Oakes, PCB Production, Intec (Inverclyde) Ltd, 5 East Blackhall Street, GREENOCK, PA15 1HD.

For Electronic Design and
PCB Manufacture
call

PROTO DESIGN

Unit 8, Ilford Trading Estate
Paycocke Road Basildon
Essex SS14 4DR
Tel: 0268 289923



Help PE Readers!

Put projects into practice. Project
your component image here!

Phone PE on:
01-743-8888

TECHNICAL INFO SERVICES (PE)

76 Church St, Larkhall, Lanarkshire ML9 1HE
Phone 0698 884585 Mon-Fri, 9-5

any other time 0698 883334 FOR FAST QUOTES

WORLD'S LARGEST COLLECTION SERVICE MANUALS Most
unobtainable elsewhere. Prices range from only £4.50 - large s.a.e. any
quotation, no obligation to buy.

WORLD'S SOLE Suppliers of TV & Video Repair manuals, etc. from TV
TECHNIC, Thorn etc. Every published service sheet in stock, supplied
full size, not bits & pieces. CTV's or any combination £3.50 plus Lsae,
any other single item £2.50 plus Lsae. Complete Circuit Sets for most
Videorecorders only #7 set (no serv shis made).

LSAE for QUOTATIONS plus GIANT CATALOGUE NEWSLETTERS
BARGAINS FREE S/Sht as available.

Comprehensive TV Repair Manual £9.50. Complete Radio Service and
Repair Course £9.50. Complete Repair & Service Manuals Mono TV
£12.50; CTV £17.00; Video £19.50. Complete Repair Data with circuit -
Mono TV £9.50; CTV £12.50; Video £10.50.

£3.00 plus LSAE BRINGS THE ONLY COMPREHENSIVE SERVICE
SHEETS & MANUALS, CATALOGUES plus FREE CHASSIS GUIDE
and 04.00 OF VOUCHERS

WORKSHOP SERVICE MANUALS

Video Recorders - £12.50

Most Colour TV, Audio, Test, Vintage, Amateur etc. £6.00

Please state Make/Model/Type with order.

FREE Catalogue Unique Repair and Data Guides with all
orders or LSAE for your copy.

MAURITON ELECTRONICS LTD (PE),

8 Cherry Tree Road, Chinor, Oxfordshire OX9 4QY

Tel: (0844) 51694

ELECTRONICS DESIGN SERVICE

FOR FULL DETAILS SEND S.A.E TO:

SPIRETRONIKS

2 Woodside, Chesterfield,
Derbyshire, S42 6SD

SURVEILLANCE

NEW VHF MICROTRANSMITTER KIT,
tuneable 80-115 MHz, 500 metre range,
sensitive electret microphone, high quality PCB.
SPECIAL OFFER complete kit ONLY £5 or
assembled and ready to use £8.95. POST
FREE. Access orders telephone 021 411 1821.
Cheques/ P.O.'s to: Quantek Electronics Ltd,
(Dept P.E.), 45a Station Road, Northfield,
Birmingham, B31 3TE

Surveillance devices, lasers, Tesla coils,
scramblers, ultrasonic and many more,
over 150 designs. Send SAE to:
Plancentre, Old Wharf, Dynock Road,
Ledbury HR8 2HS

KITS MICROTRANSMITTER, VHF/FM,
received on standard radio, 25x15mm, free
microphone included - £4.50. Telephone
transmitter, amazingly uses no batteries -
£5.49. Bleeper transmitter vhf - £8.59 inc
p&p. SAE list. Remittance to: A.C.E. (PE),
99 Greenheath, Hednesford, Staffs. -
Access orders 05438 71902 - same day
dispatch

SURVEILLANCE & COUNTER SURVEILLANCE EQUIPMENT

WE MANUFACTURE AND SUPPLY
TOP QUALITY
SURVEILLANCE
AND SECURITY
EQUIPMENT




including VHF Transmitters
Automatic Telephone
Recorders Recording
Briefcases Bug
Detectors
Telephone
Counter-Tap Units
We also offer a complete
range of accessories
including microcassette recorders,
receivers, cassettes and batteries

CCTV AND SECURITY
SYSTEMS SPECIALISTS

Write or phone for a detailed catalogue to

ESKAN ELECTRONICS LTD.
DEPT. PE, 172 CALEDONIAN ROAD, LONDON, N1

01-278 1768

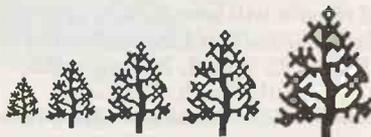


From little acorns
mighty oaks will grow!

Small businesses - use PE
Classified section for your
products or services and
watch your business develop!

Phone Richard Caplis on
01-743-8888 for details!

BOOKS

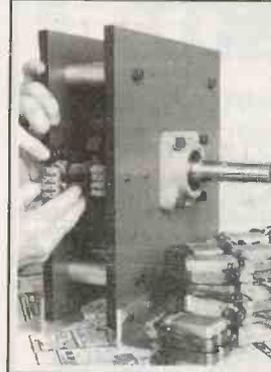

THE HOMEBUILT DYNAMO

by Alfred T. Forbes

ISBN 0-9597749-0-4

Reviewed in P.E.
January, 1989. £42
including air mail
post.

(Brochure £3
refundable) Trade
enquiries welcome.

Todd-Forbes
Publishing
PO Box 3919,
Auckland,
New Zealand

73 AMATEUR RADIO

World's leading ham radio
magazine.

Annual subscription \$39.00 (US
Funds) from: 73 Amateur Radio,
P.O. Box 58866, Boulder,
CO 80322-8866, U.S.A.

MISCELLANEOUS

Laboratory stock clearance equipment,
ECG transducers, Geigers, anemometers,
spare motors etc. SAE list. Laboratories,
Maplehurst, RH13 6LL Tel: 0403 891 236

Simple Computer Output. Dozens of
outputs possible! - any computer. No risk! -
no direct system connections. Easy circuit
construction. Only six inexpensive
components/circuit. Many uses - robotics,
security systems, model control etc. £1.99
for full instructions (components not
included). Tradewell Associates, 141
Devonshire Avenue, Sheerwater, Woking,
Surrey, GU21 5QB.

Solar Eclipse 22nd July 1990 - Finland.
For your travel and accomodation needs
phone Margaret at Salford Travel Agency
on 061-8329131. ABTA members. We are
Finland specialists.

VOICE/SOUND activated switches easy
to follow diagrams and uses only £1.00.
Components and P.C.Bs available:
Herrington, 63 Home Farm Road, Hanwell,
London W7 1NL.

Had a good Idea? Ideas, designs and
inventions wanted. S.A.E. for more
information: Martin Bliss Prop. MD, Adapta
Plan, Dept. PE, 28 Clerkenwell Crescent,
Malvern, Worcs WR14 2TX.

RM Nimbus Experimental Analogue
port. Two analogue and two digital
channels, using mouse socket. Circuit,
layout and listing £5.00; PCB £3.50.
Logical Answers, 24 Elmwood, Mersea,
Colchester, Essex CO5 8RD.

Azimuth Test Cassettes, £5.85. Ian
Harrison, 7 Mill Hill, Repton, Derby. Tel:
0283 702875.

Whatever the outcome of the GEC-Siemens bid to take over Plessey, you can be sure that the general process of redistribution of ownership in the electronics industry will continue. Apart from hostile takeover bids there will be plenty more agreed mergers, acquisitions, joint ventures and other such arrangements.

Experts are predicting that in the next few years the world computer industry will consolidate into a smaller number of larger companies. In Western Europe the coming of the single market in 1992, with its free trading conditions across frontiers, will certainly hasten the removal of the less competitive electronics businesses in this part of the world.

A few months ago I asked rhetorically "Why can't all these firms just settle down and get on with the job of making and selling electronics products without so much fuss about ownership?" And I promised to explore this question more deeply.

INDUSTRY



NOTEBOOK

EMI selling its vlsi subsidiary Inmos to SGS-Thomson Microelectronics.

The directors and managers who initiate mergers and takeovers on these objective principles are motivated by a self-interest which is identified with the collective interest of the company – its survival, prosperity, reputation and so on. This is what economics textbooks call "maximising satisfaction." It may take the form of pleasure from simply getting more money, pleasure from the use of that money, or pleasure from greater power in controlling more people and resources in a larger organization. In a takeover battle there is also the sense of achievement to be derived from winning it.

Satisfactions of this kind are not everybody's cup of tea. But we all have a need for psychological security. Some people get this by discovering a specific meaning in their lives. One school of psychology (Adlerian) says that this

WHY MERGERS AND TAKEOVERS?

BY TOM IVALL

"Why can't all these firms just settle down and get on with the job of making and selling electronics products without so much fuss about ownership?"

It seems to me that this continually shifting pattern of acquisition and ownership must be understood on two levels. One is more or less technical – the level of economic laws and imperatives of competition which determine the working of free trade in an almost mechanistic fashion. You hear industrialists and others talking about "the logic of the situation" as if human wishes or decisions didn't come into it. But this is misleading (sometimes deliberately so), because there is a second, deeper level of explanation which is entirely about primitive human drives. And here "primitive" doesn't mean simple, but close to the mainsprings of human action.

On the 'technical' level of explanation, everything derives from competition in a free market. To stay in business and produce satisfactory sales, profits and incomes for its owners, a manufacturing company must compete on price for a given design and quality of product. It must secure an adequate share of the available market. This means in fact that the products must be manufactured at sufficiently low unit cost to obtain the required profit when sold. Secondly, to ensure that the technological design features of the products keep up with the continuous research and development. This r&d cost is particularly high in the semiconductor sector.

Thus to achieve both competitive prices and state-of-the-art design the manufacturer must operate efficiently to minimise unit costs. Both of these ends can be achieved by becoming larger in terms of turnover.

One important advantage of being larger, for example, is that it gives you opportunities for economies of scale. Savings are obtained by better utilisation of resources. This applies not only to the manufacturing processes as such but also to the r&d, management, marketing, advertising and selling activities and their costs. Furthermore a large company can get better

financial terms for loans and purchasing materials and components than are available to a smaller one. And the larger a firm becomes, and thus the nearer it approaches the monopoly position it would like in its particular market, the greater the control it has over the price of the products in that market.

Firms can, of course, expand by internal growth, but in a fast-moving, highly competitive situation it is much quicker and surer to expand by acquisition.

Apart from reducing unit costs by economies of scale, there are many other possible reasons for mergers and takeovers. For example, a firm can acquire particular technology, skill or knowledge that it needs by buying up another company that already has them. Or a firm may be able to get into new markets or expand its existing markets by this means. Leaving aside complete acquisitions of other companies, there is a constant redistribution of resources going on as firms sell off parts of themselves which they don't want to other firms who do want them. A recent example was Thorn-

security depends on establishing a primary sense of self-worth. The very young child achieves it through bodily expressions which earn parental approval. Later this urge to self-esteem is socialized. It is transformed into a search for patterns of behaviour which everyone around will accept, support and perhaps admire. Thus self-esteem comes to depend on actions which have symbolic value.

In some cases there may be a symbolic value in things one already has, like good looks or inherited wealth. Or the symbolic value may lie in things achieved – physical, intellectual, spiritual and so on. One criterion of achievement is the amount of the world's goods you own. Here many people seem to obtain a sense of self-worth and psychological security by amassing far more than is necessary for ordinary material security.

From my own experience of industrialists, entrepreneurs and various assorted business types, I certainly think the Adlerian view is a plausible analysis of the drive behind merger and takeover activity. These barons of industry and commerce are able to satisfy their urge to self-esteem because the "logic of the situation" actually instructs them to increase their power over things and people. This power is real in a practical sense but its greatest value to them as members of society is symbolic. **PI**

POINTS ARISING

Dear Mr Becker

I am writing to clarify a slight misunderstanding which may have arisen from the Industry Notebook article 'In the Image of His Creation' published in the July 89 issue.

Brian Oakley was quoted as chairman of Logica. Whilst he is chairman of Logica Cambridge Ltd., one of Logica's subsidiary companies the chairman of Logica plc is in fact Philip Hughes.

I hope this clears up any questions which may have emerged.

Helen Pringle,
Corporate Relations, Logica International Ltd.

PRACTICAL ELECTRONICS BOOK SERVICE

Here is your Editor's choice of books he thinks will be of interest to electronics and computer enthusiasts

BEGINNERS AND EARLY STARTERS

NEW Mini-Matrix Board Projects.

R.A.Penfold. 112 pages. £2.50.
Order Code BP99

Shows a selection of 20 useful and interesting circuits that can be built on a mini-matrix board of 24 holes by 10 copper strips in size - an ideal book for early experimenters.

NEW From Atoms to Amperes.

F.A.Wilson. 160 pages. £2.95.
Order Code BP254.

For the absolute beginner, clearly explaining the fundamentals behind the whole subject of electricity and electronics.

NEW Electronic Projects for Beginners.

F.G.Rayer. 128 pages. £1.95.
Order Code BP48

Specially for the newcomer to electronics who is looking for a book containing a wide range of easily made projects. Some circuits need no soldering and many others show actual component and wiring layouts.

Electronics Build and Learn

R.A.Penfold. 128 Pages. £5.95.
Order Code PC 101

Combining theory and practice, the book describes a circuit demonstrator unit that is used in subsequent chapters to introduce common electronic components and circuit concepts, complete with practical experiments.

Practical Electronic Building Blocks

R.A.Penfold. There are two books -
Book 1 : 128 pages. £1.95.

Order Code BP117

Book 2 : 112 pages. £1.95.

Order Code BP118

Book 1 is about oscillators and gives circuits for a wide range, including sine, triangle, square, sawtooth and pulse waveforms and numerous others from voltage controlled to customised ic types.

Book 2 looks at amplifiers, ranging from low level discrete and opamp types to ic power amps. A selection of mixers, filters and regulators is included.

30 Solderless Breadboard Projects

R.A.Penfold. Two books each of 160 pages. Book 1 : £2.25. Order Code BP107. Book 2 : £2.25. Order Code BP113.

Each project is designed for building on a Verobloc breadboard and is accompanied by a description, circuit and layout diagrams and relevant constructional notes. Many of the components are common to several projects. Book 1 covers linear devices, and Book 2 covers cmos logic chips.

Beginners Guide to Building Electronic Projects R.A.Penfold. 112 pages. £1.95. Order Code BP 227

Shows the complete beginner how to tackle the practical side of electronics and includes simple constructional projects.



TEST AND MEASUREMENT

Getting the Most from Your Multimeter

R.A.Penfold. 112 pages. £2.95.
Order Code BP239

There's more to what you can do with a meter than meets the casual eye. The book covers the basics of what you can do with analogue and digital meters and discusses component and circuit testing.

NEW Test Equipment Construction

R.A. Penfold £2.95.

Order Code BP248

Describes in detail how to construct some simple and inexpensive, but extremely useful, pieces of test equipment.

Oscilloscopes

I.Hickman. £6.95.

Order Code NT3

Subtitled 'How to Use Them, How They Work' the book is illustrated with diagrams and photographs and is essential reading for any one who wants to know about scopes, from first principles to practical applications.

How to Get Your Electronic Projects Working.

R.A.Penfold. 96 pages. £2.50.

Order Code BP110.

Essential reading for anyone who wants first-time success in project assembly. Covers tracing mechanical faults as well as testing for failures of active and passive components of most types.

SATELLITE TV

NEW Satellite TV Installation Guide - 2nd edition John Breeds. £11.95. Order Code STV1

Full of vital information for any competent diyer who wishes to install a satellite tv antenna and obtain optimum reception quality.

An Introduction to Satellite Television

F.A.Wilson. 112 pages. £5.95.

Order Code BP195

Informative answers to many of the questions about this communications revolution. The information is presented on two levels, one aimed at the complete beginner, the other at professional engineers and serious amateur enthusiasts.

AUDIO AND MUSIC

Introducing Digital Audio

I.Sinclair. 112 pages. £5.95.

Order Code PC102

A non-mathematical introduction to the new digital technology, discussing the principles and methods involved in devices such as cd, dat and sampling.

Electronic Music Projects

R.A.Penfold. 112 pages. £2.50.

Order Code BP74

24 practical constructional projects covering fuzz, wah, sustain, reverb, phasing, tremolo etc. The text is split into four sections covering guitar, general, sound generation and accessory projects.

More Advanced Electronic Music Projects

R.A.Penfold. 96 pages. £2.95.

Order Code BP174

Complementing BP74 by covering more advanced and complex projects including flanging, chorus, ring modulation, plus a selection of drum, cymbal and gong circuits.

NEW Computer Music Projects

R.A.Penfold. 112 pages. £2.95.

Order Code BP173

Shows how home computers can produce electronic music and covers sequencing, analogue and Midi interfacing, digital delay lines and sound generators.

Practical Midi Handbook

R.A.Penfold. 160 pages. £5.95.

Order Code PC103

A practical how-to-do-it book for musicians and enthusiasts who want to exploit the capabilities of Midi. Covers keyboards, drums, sequencers, effects, mixers, guitars, and computer music software.

Midi Projects

R.A.Penfold. 112 pages. £2.95.

Order Code BP182

Practical details of interfacing many popular home computers with Midi systems, and also covering Midi interfacing to analogue and percussion synths.

NEW Electronic Synthesiser Construction.

R.A.Penfold. 112 pages. £2.95.

Order Code BP185.

Even relative beginners should find the monophonic synthesiser described here within their capabilities if the book is thoroughly read. Individual aspects of the synth are dealt with separately and pcb designs are shown for the main modules.

DIGITAL AND COMPUTING

NEW A Concise Introduction to MS-DOS.

N. Kantaris. 64 pages. £2.95.
Order Code BP232

A ready-reference guide for those who need a quick insight into the essential command functions of this operating system, but who don't have the time to learn it fully.

An Introduction to Computer Peripherals

R.A. and J.W. Penfold. 80 pages.
£2.50. Order Code BP170

Covers such items as monitors, printers, disc drives, cassettes, modems, etc, explaining what they are and how to use them with your computer and with each other.

Microprocessing Systems and Circuits

F.A.Wilson. 256 pages. £2.95.
Order Code BP77

A comprehensive guide to the elements of microprocessing systems, covering the fundamental principles behind this important subject.

Introduction to 6800/6802 Microprocessor Systems

R.J.Simpson and T.J.Terrell. 238 pages. £10.95. Order Code NT9

The book covers systems hardware, programming concepts and practical experimental work that will assist in understanding the 6800/6802 microprocessor, with additional information on the 6802D5E evaluation system.

NEW An Introduction to 68000 Assembly Language.

R.A. and J.W.Penfold. 112 pages.
£2.95. Order Code BP184

Covers the fundamentals of writing programs that will vastly increase the speed of 68000 based machines such as the Commodore Amiga, Atari ST range, Apple Mackintosh, etc.

Getting the Most from Your Printer

J.W.Penfold. 96 pages. £2.95.

Order Code BP181

How to use the features found on most dot-matrix printers from programs and popular wordprocessors, showing examples of what must be typed to achieve a given effect.

Micro Interfacing Circuits

R.A.Penfold. Two books, each of 112 pages.

Book 1 : £2.25. Order Code BP130.

Book 2 : £2.25. Order Code BP131

Both books include practical circuits and useful background information though pcb layouts are not included. Book 1 mainly covers computer input-output techniques. Book 2 deals primarily with practical application circuits.

NEW An Introduction to 6502 Machine Code.

R.A. and R.W. Penfold. 112 pages.
£2.50. Order Code BP147

Covers the main principles of machine code programming on 6502-based machines such as the Vic-20, Oric-1/Atmos, Electron, BBC and Commodore 64. It assumes no previous knowledge of microprocessors or machine code and gives illustrative programming examples.

NEW A Z-80 Workshop Manual.

E.A.Parr. 192 pages. £3.50.

Order Code BP112

A book for those who already know Basic but wish to explore machine code and assembly language programming on Z80 based computers.

Practical Digital Electronics Handbook

M.Tooley. 208 pages. £6.95.

Order Code PC 104

Nine constructional projects introduce digital circuits, logic gates, timers, microprocessors, memory and interface circuits - an essential book for anyone interested in digital devices.

DATA AND INFORMATION BOOKS

Digital IC Equivalents and Pin Connections

A.Michaels. 320 pages. £5.95.

Order Code BP140

Linear IC Equivalents and Pin Connections

A.Michaels. 256 pages. £5.95.

Order Code BP141

Between them these two books show equivalents and pin connections of a popular user-orientated selection of European, American and Japanese ics. They also include details of functions, manufacturer and country of origin. The Digital ICs book also quotes details of packaging and families.

Opamps

B.Dance. £6.50.

Order Code NT2

Subtitled 'Their Principles and Applications' this interesting book is written in a simple non-mathematical style and provides a source of practical circuits that use both commonplace and more sophisticated opamps.

Electronic Hobbyists Handbook

R.A.Penfold. 96 pages. £4.95. Order Code BP233

Provides a source of useful information that the amateur enthusiast is likely to need for day-to-day pursuance of hobby electronics.

Practical Electronics Handbook

I. Sinclair. £7.95.

Order Code NT1

A useful and carefully selected collection of standard circuits, rules-of-thumb and design data for enthusiasts, students and engineers involved in radio, computing and general electronics

Newnes Electronics Pocket Book

I.E.Parr. £6.95.

Order Code NT10

Presents all aspects of modern electronics in a readable and largely non-mathematical style, and is a good source of valuable information for enthusiasts and professional engineers alike.

NEW Key Techniques for Circuit Design

G.C. Loveday. £6.95.

Order Code BM 101

Tackles the problems of designing circuits from scratch, introducing the concept of target specifications, the design sequence, device selection, rules of thumb, and useful equivalent circuits.



GENERAL CONSTRUCTIONAL

NEW Electronic Science Projects.

Owen Bishop. 144 pages. £2.95.
Order Code BP104

A bumper bundle of experimental projects ranging in complexity and including a colour temperature meter, electronic clock, a solid state (led display) scope, an infrared laser, a fascinating circuit for measuring the earth's electrical field strength, and many more.

Electronic Security Devices

R.A.Penfold. 112 pages. £2.50. BP56

Full of ideas for keeping your valuables safe. The circuits include designs for light, infra-red, ultrasonic, gas, smoke, flood, door and baby sensors.

NEW More Advanced Electronic

Security Projects. R.A.Penfold. 112 pages. £2.95. Order Code BP190

Follows on from where BP56 leaves off and describes a number of more up-to-date and sophisticated projects, such as pyro-sensors, infra-red and doppler-shift detection, fibre-optic loops, and many others.

NEW Electronic Projects for Cars and Boats.

R.A.Penfold. 96 pages. £1.95.
Order Code BP94

15 fairly simple projects that can be used with a car and/or boat. Stripboard constructional details are included, as are explanations of the circuit theory.

Power Supply Projects

R.A.Penfold. 96 pages. £2.50.

Order Code BP76

A selection of power supply designs, including simple unregulated, fixed voltage regulated and variable voltage stabilised, ni-cad charger, voltage step-up, and inverter.

More Advanced Power Supply Projects

R.A.Penfold. 96 pages. £2.95.

Order Code BP192

Covers more advanced topics than BP76 and includes precision supplies, switch mode and computer controlled supplies, plus a selection of miscellaneous circuits.

NEW Popular Electronic Circuits.

R.A.Penfold. 160 pages. £2.95.

Order Code BP80

Containing a wide range of circuit designs for experienced constructors who are capable of producing working projects direct from a circuit diagram without specific constructional details.

HOW TO ORDER

State your order code and your name and address clearly. Enclose a cheque, PO or international money order (add 50p postage per book - £1.00 for overseas surface mail), and send to:

PE Book Service
Intra House
193 Uxbridge Road
London W12 9RA

Books are normally delivered within 10 days but please allow 28 days for delivery.

READY-MADE P.C. BOARDS

Simplify your project assembly – use a ready-made printed circuit board. All are fully drilled and roller tinned. Just slot in the components as shown in the project texts, and solder them. PCBs are the professional route to project perfection.

MAIL ORDERING

Select the boards you want, and send your order to
**PE PCB SERVICE, PRACTICAL ELECTRONICS,
193 UXBRIDGE ROAD, LONDON W12 9RA.**

Prices include VAT and postage and packing. Add £2 per board for overseas airmail. Cheques should be crossed and made payable to **Intra Press**.

Quote the project name and PCB Code Number, and print your name and address in **Block Capitals**. Do not send any other correspondence with your order.

TELEPHONE ORDERS (OPEN 24 HOURS)

Use your Access card and phone your order to

0268 289923

clearly stating your name and address, card number, and order details.


All orders receive priority attention, but allow 28 days for delivery in case a PCB is temporarily out of stock.

WE CAN ONLY SUPPLY THE PCBs LISTED HERE

**CHECK LATEST ISSUE FOR
PRICES BEFORE ORDERING**

PHOTOCOPIES OF THE TEXTS MAY BE BOUGHT FROM THE EDITORIAL OFFICE AT £1.00 EACH PART (£1.50 OVERSEAS), P&P INCLUSIVE.

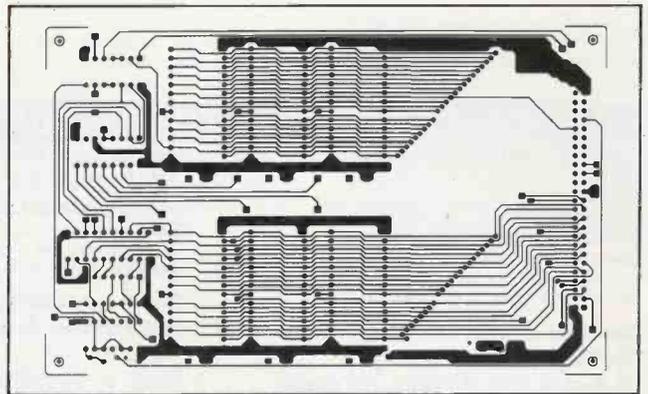COMPONENTS ARE AVAILABLE FROM ADVERTISERS.



NOV 86	REMOTE JOYSTICK – infrared computer controller. Set of 2 PCBs.	124	£10.86
	BABY ALARM – through-the-mains transceiver.	125	£10.71
DEC 86	VIDEO ENHANCER – manually adjustable video improvement.	126	£8.76
JAN 87	VIDEO FADER – simple inexpensive video mixer	127	£4.50
	VOICE SCRAMBLER – confidential trans.	128	£8.06
MAR 87	4 CHANNEL ENHANCER	135	£4.60
	LIGHT PEN – uses fibre optics for accuracy	136	£4.10
	ULTRASONIC TAPE MEASURE	138	£9.50
APR 87	VIGILANTE CAR ALARM – keeps cars alert	139	£5.90
	INDUCTIVE LOOP TRANSCIEVER – remote control for models:	143/144	£7.80
MAY 87	BRIGHT FUZZ – Foot operated overdrive	145	£3.90
JUN 87	AUDIO SIGNAL GENERATOR	146	£10.20
JUL 87	WORD GENERATOR – 16-bit binary words	147	£13.42
	SCOPE STORE oscilloscope add-on data storage	148	£11.94
SEP 87	SPEECH PROCESSOR – clarifies speech	150	£5.86
	GCSE TIMER UNIT – versatile variable delay	151	£5.18
	FUNGEN – triple waveform signal generator	152/153	£9.69
	LIGHT CONTROLLER – delayed switching	154	£4.64
OCT 87	TEACHER LOCKER – digital lock control	155	£7.50
	POWER SUPPLY – stabilised ±15V	156	£7.50
	GUITAR TO SYNTH – music interface	157A/B	£9.95

NOV 87	DUAL POWER SUPPLY – GCSE	158	£6.20
	MIDI EXPANDER – Music Interface	159	£5.04
DEC 87	RS 232C TO MIDI	160	£6.43
	TEACHER RADIO – GCSE	161	£5.58
JAN 88	LEGO BUGGY DRIVER	163	£6.42
FEB 88	TEACHER TALKBACK – GCSE	164	£6.36
	DC MOTOR SERVO	165	£7.53
MAR 88	APPLIANCE TIMER	166A/B	£9.38
	TEACHER LIGHTSHOW – GCSE	167A/B	£9.09
	LOGIC ANALYSER – Double-sided	168	£20.65
APR 88	LIGHT METAL EFFECTS	169	£7.10
	TEACHER COUNTER	170	£4.95
		171	£4.92
MAY 88	RF SPEECH PROCESSOR	172	£6.26
JUN 88	AMSTRAD ROM EXPANSION	173	£10.80
	MAINS MODEM	174	£4.27
JULY 88	VOCALS ELIMINATOR	175	£4.31
AUGUST 88	SPEAKING CLOCK	176	£16.75
SEPT 88	BBC MULTIPLEXER	177	£4.50
OCT 88	METAL DETECTOR	178	£6.50
DEC 88	PLD PROGRAMMER	179	£9.90
		180	£4.90
	PANNING MIXER	181	£7.80
JAN 89	RUDOLPH'S NOSE	182	£6.25
	ANGEL'S HALO	183A/B	£9.40
	CANDLE FLICKER	184	£6.25
MAR 89	CAMERA SHUTTER TIMER	187	£9.95
APR 89	PC MULTIPOINT	188A/B	£20-55
MAY 89	KIRLIAN CAMERA	189A/C	£10-50
JULY 89	PROJECTOR SYNCHRONISER	190-E	£9.50
AUG 89	EASI-BUILD – VODALEK	191	£4.90
	HAND CLAPPER	192	£6.50
SEP 89	EASI-BUILD – COMPRESSOR	193	£4.90
	FREQUENCY COUNTER-GENERATOR	194A/B	£12.50

PE COMPETITION

MAPLINOSCOPY!

YOU'VE TRIPLE SCOPE FOR WINNING!

Maplin AND PE

**COMBINE FORCES TO ENABLE
THREE OF YOU TO WIN A
SUPERB MAPLIN TRIPLE-TRACE
20MHZ OSCILLOSCOPE!**

WORTH NEARLY £300!

Generously donated by Maplin, these splendid XJ61R scopes are precision laboratory models that will enhance the workshop and test facilities for any reader fortunate enough to own one. And one could be yours just for the cost of a stamp!

Maplin's scopes have a wealth of facilities:


- 3 Channels - 3 Traces
- Sensitive 1mV/div vertical amplifiers
- 150mm rectangular screen with internal graticule
- X-Y mode for phase shift and frequency measurements
- TV sync separator for video signal monitoring
- 20ns/div X-sweep for fast signal observation
- Algebraic operation for Chans 1 and 2
- Easy and stable channel triggering
- 50mV/div Chan 1 output to counters etc
- Trigger hold-off for complex signal triggering

HOW TO ENTER

Just answer the five simple questions on the entry form and send the form to:

Practical Electronics, Scope Competition, 193 Uxbridge Road, London W12 9RA. All correct answers will be put into a draw which will take place on 29th September 1989. The first three names drawn will each win one these Maplin scopes. The Editor's decisions (and definitions!) are final.

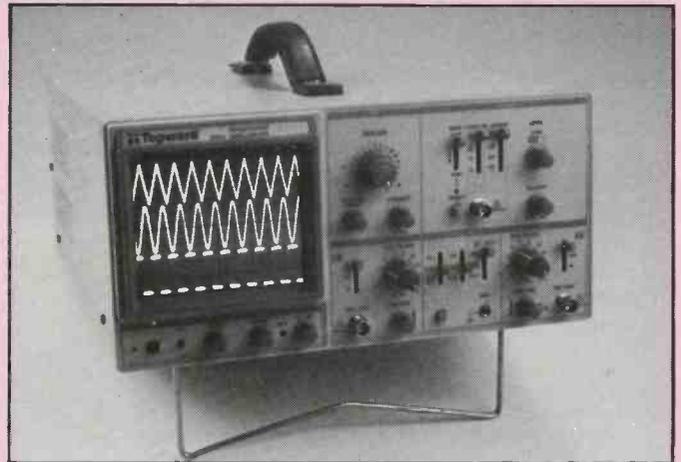You may send a photocopy of the entry form providing you also attach the original entry coupon clipped from the corner of this page (not a photocopy of it).



MAPLIN SCOPE ENTRY FORM

Circle the correct answer to the following questions, or write in your own answer:

1. The initial letters C.R.T. stand for:

- Cathode Radar Tube Caesium Ray Tube
Capacitive Resonance Trigger Other

2. The name Rayleigh is renowned for:

- Bicycles Plymouth Hoe Maplin Sands
Electronic Supplies Other

3. Signal phase and frequency comparison patterns on a scope screen are called:

- Lissotrichous Figures Lissajous Figures
Listeria Figures Other

4. In a scope tube the electron beam starts its journey to the screen from the:

- Anode Dynode Cathode
Pentode Other

5. Which of these (if any) is the odd one out?

- Oscilloscope Video Camera
TV set Radio Computer
Cash Dispenser Radar None of these

6. What is the common link in Q5?

Name and address (in block letters):

.....
.....
.....

Post Code:

PE COMPETITION
SEPT. 1989



TWO GREAT HOBBIES

ONLY
£124.50
INC VAT



...IN ONE GREAT KIT!

The K5000 Metal Detector Kit combines the challenge of DIY Electronics assembly with the reward and excitement of discovering Britain's buried past.

THE KIT — simplified assembly techniques require little technical knowledge and no complex electronic test equipment. All stages of assembly covered in a detailed 36 page manual.

THE DETECTOR — features Analytical Discrimination & Ground Exclusion, backed by the proven pedigree of C-Scope, Europe's leading detector manufacturer.

Ask at your local Hobby/Electronics shop or contact:—




C-Scope International Ltd., Dept. PE
Wotton Road, Ashford, Kent TN23 2LN.
Telephone: 0233 629181.

INDEX TO ADVERTISERS

A & G Electronics	54	J.P.G. Electronics	55
A.D.M. Electronics Supplies	55	Keytronics	39
Andor Electronics	54	K-Tek	55
Astronomy Now	47	Limrose Electronics	47
B.A.E.C	55	London Electronics College	54
B.K. Electronics	19	Magenta Electronics	10, 11
Blackmore Electronics	55	Maplin Electronics	OBC
Bull J.	48	Marco Trading	51
C-Scope	62	Mauriton Electronics	56
Cambridge Computer Science Ltd	55	Multilode Ltd.	54
Classified Ads	54-56	Omni	54
Coles Harding	55	Phonosonics	51
Cooke International	55	PLS	54
Cricklewood Electronics	44	PRF Software	55
C.R. Supply Co.	55	Program Now	55
Deansgate	54	Proto Design	56
Display Electronics	24	RMOS	55
Eskan Electronics	56	Service Trading Co	62
Fraser Electronics	54	Skills Training Agency	45
G.C.H.Q	40	S.M. Engineering	45
Greenbank Electronics	62	Specialist Semiconductors	IBC
Greenweld Electronics	31-34, 54	Spiretronics	56
Hanney, L.F.	54	Suma Designs	40
Hart Electronics	38	Tandy	IFC
High Grade Components	20	Technical Info Services	56
Intec (Inverclyde) Ltd.	56	T.K. Electronics	40
		Todd Forbes Publishing	56

PLEASE MENTION PRACTICAL ELECTRONICS
WHEN REPLYING TO ADVERTS

Interak 1 SINGLE BOARD COMPUTER

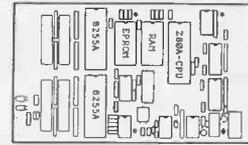

"SBC-1"

A computer doesn't *have* to look like you'd expect a computer to look. It doesn't have to *have* a keyboard and a screen and floppy disks and so on.

The SBC-1 has the bare minimum of chips a Z80 computer can have and still be a computer: A 4 MHz Z80-CPU chip, an EPROM chip (up to 32K), a static RAM chip (up to 32K) and a pair of 8255A I/O (input/output) chips giving 48 individual lines to waggle up and down. There are one or two additional "glue" chips included, but these are simple "74LS" or "HC" parts.

A star feature is that no special or custom chips (ie PALS, ULAs, ASICs etc) are used — and thus there are no secrets. The Z80A is the fastest and best established of all the 8-bit microprocessors — possibly the cheapest too!

Although no serial interface is included, it is easy for a Z80A to waggle one bit up or down at the appropriate rate — the cost is a few pence worth of code in the program: why buy hardware when software will do?

Applications already identified include: Magnetic Card reader, mini printer interface, printer buffer, push button keypad, LCD alphanumeric panel interface, 40-zone security interface for auto sending of security alarms, code converter (eg IBM PC keyboard codes to regular ASCII), real time clock (with plug in module), automatic horticultural irrigation controller.

By disabling the on-board Z80A-CPU this card will plug into our Interak 1 CP/M Plus disk-based development system, so if you don't fancy hand-assembling Z80 machine code you don't have to!

The idea is (if you are a manufacturer) you buy just one development system and then turn out the cheap SBC-1 systems by the hundred. If you are really lazy we can write the program for you and assemble the SBC-1 cards so you can get on with manufacturing your product, leaving all your control problems to us.

Greenbank

For more details write or phone us:
Greenbank Electronics, Dept (E9P), 460 New Chester Road,
Rock Ferry, Birkenhead, Merseyside. L42 2AE. Tel: 051-645 3391

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60	OUTPUT 0-260V
200W 0.1 amp max £24.00 p&p	£3.00 (£31.05 inc VAT)
0.5KVA 2.5 amp max £26.50	£3.75 (£34.75 inc VAT)
1KVA 5 amp max £34.00	£4.25 (£43.99 inc VAT)
2KVA 10 amp max £49.00	£5.50 (£62.68 inc VAT)
3KVA 15 amp max £65.00	£6.25 (£81.94 inc VAT)
5KVA 25 amp max £115.00	

Carriage on request



VOLTAGE CHANGING TRANSFORMER

1250 Watt auto. Tapped 0-90V, 100, 110, 115, 120, twice to obtain voltages between 80 and 240V. Fitted in heavy duty louvered metal case. Fused input. Price incl VAT & p&p £39.50.

COMPREHENSIVE RANGE OF TRANSFORMERS-IT ISOLATION & AUTO (110-240V Auto transfer either case) with American socket and mains lead or open frame type. Available for immediate delivery.

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt £10.44 (£12.00 inc VAT)	Caller only
2ft 20 watt £7.44 + £1.25 p&p	(£9.99 inc VAT)
13in 10 watt £5.80 + 75p p&p	(£7.53 inc VAT)
12in 8 watt £4.80 + 75p p&p	(£6.38 inc VAT)
9in 6 watt £3.60 + 50p p&p	(£5.12 inc VAT)
6in 4 watt £3.50 + 50p p&p	(£5.12 inc VAT)

230V AC BALLAST KIT for either 6in, 9in or 12in tubes £5.50 + 55p p&p (£6.96 inc VAT)
For 13in tubes £6.00 + 75p p&p (£7.75 inc VAT)



400 WATT UV LAMP

Only £28.00 + £2.50 p&p (£35.08 inc VAT)

175 WATT SELF BALLASTED BLACK LIGHT MERCURY BULBS Available with BC or ES fitting. Price incl VAT & p&p £18.65.

12 VOLT BILGE PUMPS

Buy direct from the importers
500 GPH 15ft head 3 amp
£16.00 inc.

1750 GPH 15ft head 9 amp
£19.25 + £2.00 p&p (£25.00 inc VAT)

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Angst Tube Ballast unit pair of bi-pin leads neon indicator on/off switch safety microswitch and circuit £14.00 + £2.00 p&p (£18.40 inc VAT)



SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical users etc.
Approx 16 pulses. Adjustable speed £48.00 + £2.00 p&p (£57.50 inc VAT)

Case and reflector £22.00 + £2.00 p&p (£27.80 inc VAT)
S&E for further details including Hy-Light and Industrial Strobe Kits.

WIDE RANGE OF XENON FLASH TUBES

Write/Phone your enquiries

SOLID STATE RELAY

Single make will switch up to 250 V AC 10 amp. operating voltage 3-32 V DC silent contactless opto-isolated. Fraction of maker's price £3.00 + 50 p p+p. Total inc VAT £4.03.

SPECIAL OFFER AC CAPACITORS

1.5 MFD 440V £2.00	5 MFD 440V £4.00
2 MFD 440V £2.50	5.4 MFD 280V £2.00
4.1 MFD 440V £3.50	5 MFD 660V £3.00
	12 MFD 400V £4.00

p+p 50p per unit plus VAT to be added to total.

TORIN CENTRIFUGAL BLOWER

230V ac 2,800 RPM 0.9amp 130mm diameter Impeller outlet 63 x 37mm overall size 195 x 160 x 150mm long. Price £17.50 + £2.50 p&p (£23 inc VAT)

SHADED POLE GEAR MOTORS

In the following sizes:
9 RPM 12 RPM 80 RPM 160 RPM 110V AC or 240V AC with capacitors (supplied). Price incl VAT & p&p £12.65

GEARED MOTORS

171 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price incl VAT & p&p £23.00.

12 V DC COOLER EXTRACTOR FAN

New brushless motor 92mm sq. Price incl VAT & p&p £11.50.

SOLID STATE EHT UNIT

Input 230/240V AC, Output approx 15kV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £1.00 p&p (£10.93 inc VAT) NMS

COOLING FANS-BRAND NEW!

200/400W AC American Boxer "Peewee" 7-bladed high efficiency cooling unit 80mm sq x 40mm deep 40cm approx. Price incl VAT & p&p £10.35.

EX-EQUIPMENT FANS 120mm sq x 38mm deep in either 115V or 230V AC Tested and guaranteed. Price incl VAT & p&p £7.76.

Large selection of various speed greased motors from stock. Phone or write for details.

From stock at prices that defy competition

C/F Blowers Program Timers
Microswitches Synchron Motors
write/phone your enquiries

NMS = NEW MANUF SURPLUS
R&T = RECONDITIONED AND TESTED

Ample
Parking Space

Showroom open
Monday/Friday

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB

01-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10



POWER CONDITIONER

FEATURED IN ETI
JANUARY 1988

The ultimate mains purifier. Intended mainly for lowering the noise floor and improving the analytical qualities of top-flight audio equipment.


The massive filter section contains thirteen capacitors and two current balanced inductors, together with a bank of six VDRs, to remove every last trace of impulse and RFI interference. A ten LED logarithmic display gives a second by second indication of the amount of interference removed.

Our approved parts set consists of case, PCB, all components (including high permeability toroidal cores, ICs, transistors, class X and Y suppression capacitors, VDRs, etc.) and full instructions.

PARTS SET £29.80 + VAT

A low cost (but high performance) mains conditioner is also available.

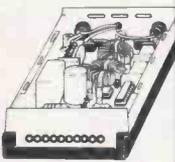MAINS CONDITIONER PARTS SET £5.40 + VAT
RUGGED PLASTIC CASE £1.80 + VAT



KNIGHT RAIDER

FEATURED IN ETI JULY 1987

The ultimate in lighting effects for your Lamborghini, Maserati, BMW (or any other car, for that matter). Picture this: eight powerful lights in line along the front and eight along the rear. You flick a switch on the dashboard control box and a point of light moves lazily from left to right leaving a comet's tail behind it. Flip the switch again and the point of light becomes a bar, bouncing backwards and forwards along the row. Press again and try one of the other six patterns. An LED display on the control box let's you see what the main lights are doing.

The Knight Raider can be fitted to any car (it makes an excellent fog light) or with low powered bulbs it can turn any child's pedal car or bicycle into a spectacular TV-age toy!

The parts set consists of box, PCB and components for control, PCB and components for sequence board, and full instructions.

Lamps not included.


PARTS SET £24.80 + VAT

RAINY DAY PROJECTS



All can be built in an afternoon!

- JUMPIN' JACK FLASH (ETI March 1988)
Spectacular rock, stage and disco lighting effect! £6.90 + VAT
- CREDIT CARD CASINO (ETI March 1987)
The wicked pocket gambling machine £5.90 + VAT
- MAINS CONTROLLER (ETI January 1987)
Isolated logic to mains Interface £6.20 + VAT
- MATCHBOX AMPLIFIERS (ETI April 1986)
Matchbox Bridge Amplifier (50W)
Listen: 50W of Hi-Fi power from an amp small enough to fit in a matchbox! £6.50 + VAT
- Matchbox Bridge Amplifier (50W)
L165V Power Amplifier IC, with data and circuits £8.90 + VAT
- TACHO/DWELL METER (ETI January 1987)
Turn your Metro into a Porsche! £16.40 + VAT
- HI-FI POWER METER (ETI May 1987)
Measures Hi-Fi output power: up to 100W - includes PCB, components, meters £3.90 + VAT
- Mono power meter £3.90 + VAT
- Stereo power meter £7.20 + VAT

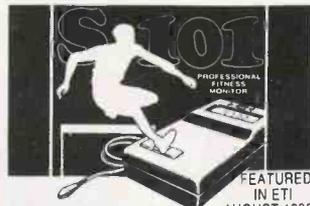

FEATURED IN ETI
AUGUST 1988

There's nothing quite so encouraging as having a quantifiable result to show for your training efforts. If you are not particularly fit, your resting heart rate will be around 80 beats per minute. As your jogging, aerobics or sport strengthens your heart, the rate will drop dramatically - possibly to 50bpm or less. With the S101, you can watch your progress day by day.

Breathing is important too. How efficiently do you take up oxygen? How quickly do you recover from 'oxygen debt' after strenuous activity? The S101 will let you know.

The approved parts set consists of: case, 3 printed circuit boards, all components (including 17 ICs, quartz crystal, 75 transistors, resistors, diodes and capacitors), LCD, switches, plugs, sockets, electrodes, and full instructions for construction and use.

PARTS SET £33.80 + VAT

Some parts are available separately. Please send SAE for lists or SAE + £2 for lists, circuit construction details and training print (free with parts set).



THE DREAM MACHINE

FEATURED IN ETI
DECEMBER 1987



Adjust the controls to suit your mood and let the gentle, relaxing sound drift over you. At first you might hear soft rain, sea surf, or the wind through distant trees. Almost hypnotic, the sound draws you irresistibly into a peaceful, refreshing sleep.

For many, the thought of waking refreshed and alert from perhaps the first truly restful sleep in years is exciting enough in itself. For more adventurous souls there are strange and mysterious dream experiences waiting. Take lucid dreams, for instance. Imagine being in control of your dreams and able to change them at will to act out your wishes and fantasies. With the Dream Machine it's easy!

The approved parts set consists of PCB, all components, controls, loudspeaker, knobs, lamp, fuseholders, fuse, mains power supply, prestige case and full instructions.


PARTS SET £19.80 + VAT

Ban Sweetland's best seller GROW RICH WHILE YOU SLEEP is now in stock.

£2.95 (NO VAT)

TV BOOSTER

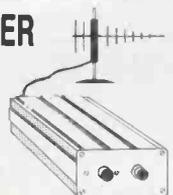Good TV pictures from poor aereals is what this project is all about. Keith Bromley's Aerial Booster gives a massive 23dB gain to ensure good viewing for campers and caravanners, from indoor aereals, or wherever a properly positioned high-gain antenna is not practical.



Based on the OM335 hybrid amplifier, the booster has specifications to rival the best: wideband operation from 10MHz to 1.4 GHz, mid-band gain of up to 26dB and a wide supply range of 9V to 26V (it will run from car batteries for caravanners, dry batteries for campers, or a mains 'battery eliminator' in the home). No special UHF construction skills are needed - the project could be made by a careful beginner.

There are two parts sets for the project. AA1 contains the printed circuit board, OM335 hybrid amplifier, components and instructions. AA2 is the optional case set: rugged screened box, front and rear panels, waterproofing gaskets, feet, sockets and hardware.

AA1 PARTS SET £12.80 + VAT

AA2 PARTS SET £4.80 + VAT

AA3 OPTIONAL MAINS POWER SUPPLY PARTS SET £6.80 + VAT

POWERFUL AIR IONISER

FEATURED IN ETI
JULY 1986

Ions have been described as vitamins of the air. In the health magazines, and have been credited with everything from curing hay fever and asthma to improving concentration and putting an end to insomnia. Although some of the claims may be exaggerated, there is no doubt that ionised air is much cleaner and purer, and seems much more invigorating than 'dead' air.

The DIRECT ION ioniser caused a great deal of excitement when it appeared as a constructional project in ETI. At last, an ioniser that was comparable with (better than?) commercial products. was reliable, good to build, and fun! Apart from the serious applications, some of the suggested experiments were outrageous!

We can supply a matched set of parts, fully approved by the designer, to build this unique project. The set includes a roller tinned printed circuit board, 66 components, case, mains lead, and even the parts for the tester. According to one customer, the set costs 'about a third of the price of the individual components'. What more can we say?

PARTS SET WITH BLACK CASE £12.60 + VAT

PARTS SET WITH WHITE CASE £12.80 + VAT



THE MISTRAL AIR IONISER



The best ioniser design yet - this one has variable ion drive, built-in ion counter and enough power to drive five multi-point emitters. For the technically minded, it has nine main drive stages, five secondary drives, and a four section booster to give an output capability of almost fifteen billion (1.47 x 10¹¹) ions every minute, or 2.45 x 10¹¹ ions per second. With extra emitters this can be increased still further!

PARTS SET £28.40 + VAT

The parts set includes case, printed circuit boards, 126 top grade components, all controls, lamps, hardware, a multi-point phosphor-bronze emitter and full instructions.

Some parts are available separately - please send SAE for lists, or SAE + £1 for lists, circuit and construction details and further information (free with parts set).

READY-BUILT MISTRAL

The Mistral Ioniser (and most of our other projects) can now be supplied built, tested and ready to go. For details, please contact Peter Leah at P.L. Electronics, 8 Woburn Road, Eastville, Bristol BS5 6TT. Tel: 0272 522703. Evenings Only

INTERNAL EMITTER £2.80 + VAT

Can be used in place of the P-B external emitter, or both can be used together for the highest ion output. Parts set includes PCB, ion emitters, components and instructions.

IPA BOARD CLEANER

Essential for removing grease and flux residues from the Mistral PCB to achieve peak performance. Applicator brush supplied.

£0.98 + VAT

ION FAN

An almost silent piezo-electric fan, mains operated, to pump ions away from the emitter and into the room. Increases the effectiveness of any ioniser by five times!

£9.80 + VAT

BURGLAR BUSTER

Be safe from intruders with our Burglar Buster alarm system! It has all the features you'd expect from a high-tech alarm: entry and exit delay, anti-tamper loop, delay warning and control-box protection.

The parts set includes all PCBs and all components to go on them. Other parts (case, switches, etc.) are available separately, if you haven't got anything suitable in your spare box. Set contains 4 PCBs, ICs, transistors, relays, capacitors, resistors, diodes, regulator, piezo sounder and full instructions.

BB1 PARTS SET £12.80 + VAT

LEDs

Green rectangular LEDs for bar-graph displays.

50 for £3.50 500 for £25
100 for £6 1000 for £45

DIGITAL AND AUDIO EQUIPMENT LEDs

Assorted 3mm LEDs: red, green, yellow and orange.
25 of each (100 LEDs) for £6.80

U.K. orders: please add 80p post and packing and 15% VAT to total.
Ireland and overseas:
no VAT. Carriage and insurance £4.50.
Please allow up to 14 days for delivery.

Specialist SEMICONDUCTORS LIMITED

Tel: (0600) 3715
SALES DEPT., ROOM 108, FOUNDERS HOUSE, REDBROOK, MONMOUTH, GWENT.

ION DISPERSION METER

FEATURED IN ETI
FEBRUARY 1989

The O-ion is a hand-held meter which sniffs out ions in the air. It can tell the good ones from the duds if you're thinking of buying a commercial ioniser, check the efficiency and output of one you've made yourself, help you set up fans and position the ioniser for best effect, do an ion-survey of your house or office - in short, it will tell you anything you want to know about ions in the air.

In direct mode the bar-graph readout will detect the presence of negative or positive ions and measure neg-ion strengths from 5 x 10⁷ to 10¹⁰ ions per second, which covers the levels you can expect when an air ioniser is in use. For the smaller concentrations of natural air ions, integrate mode will increase the sensitivity as far as you like.

Our approved parts set comprises: case, ion collector, printed circuit board, all components (including set ICs, schottky diode, ceramic, VDR, zener, 37 resistors and capacitors, LEDs, plug, socket, earth lead, etc.) and full instructions.

PARTS SET £18.40 + VAT

Some parts are available separately - please send SAE for lists, or SAE + £1 for lists, circuit, construction details and further information (free with parts set).



BIO-FEEDBACK

FEATURED IN ETI
DECEMBER 1986

Bio-feedback comes of age with this highly responsive, self-balancing skin response monitor! The powerful circuit has found application in clinical situations as well as on the bio-feedback scene. It will open your eyes to what GSR techniques are really all about. The complete parts set includes case, PCB, all components, leads, electrodes, conductive gel, and full instructions.

PARTS SET £16.80 + VAT

BIO-FEEDBACK BOOK £4.50 (no VAT)

Please note: the book, by Stern and Ray, is an authorised guide to the potential of bio-feedback techniques. It is not a hobby book, and will only be of interest to intelligent adults.



AMAZING LOW PRICE

SOLDERING IRONS

FLAME MASTER HOT GAS SOLDERING TOOL

Superb Pocket Size Portable Gas
Soldering Iron

ONLY
£12.95
FS110



★ Interchangeable Tips ★

- ★ Powered by Butane Gas
- ★ Simple to Refill
- ★ Temperature up to 400°C (750°F)
- ★ Up to 2 Hours Continuous Use

FLAME MASTER 5 IN 1 HOT GAS TOOL KIT

Complete with tough moulded to measure case and including:
MULTI-PURPOSE TOOL

- ★ 4 Interchangeable Soldering Iron Tips
- ★ Soldering Iron
- ★ Hot Cutting Knife
- ★ Wide Area Flame Torch
- ★ High Temperature Flame Torch
- ★ Hot Air Blower

GREAT FOR

- ★ Electrical and Electric Work
- ★ Cutting Plastics and Fibres
- ★ Sealing, Bonding and Shrinking
- ★ Removing Paint and Putty



ONLY
£19.95
FMK10

The Flame Master hot gas tool kit has many uses. It can be a soldering iron, a pencil flame torch, a hot air blower or a wide (flat) flame torch. You can fit the soldering head with a selection of soldering tips and the hot knife, or you can fit the flame head, onto which you can attach the hot blower or the wide flame unit. The choice is yours!

Post Your Order Now . . .

✂

Order Coupon		Send this coupon to P.O. Box 3, Rayleigh, Essex SS6 8LR	
Quantity	Description	Code	Price
Name		Add Carriage	50p
Address		If order below £5	please add 50p
Post Code		Total	

I authorise you to debit my Credit Card account for the cost of goods despatched.

Credit Card No.

Access Amex Visa Delete as required.

If ordering by Credit Card please sign

Expiry date of Credit Card PE

Maplin ELECTRONICS

CREDIT CARD HOTLINE



0702 554161

PHONE BEFORE 5PM FOR SAME DAY DESPATCH

ALL PRICES INCLUDE VAT.

All items subject to availability, both items will be on sale in our shops in Birmingham, Bristol, Leeds, Hammersmith, Edgware, Manchester, Nottingham, Southampton and Southend-on-Sea.

Thank you 29/11/10